


OCTOBER • 1957 25 CENTS



RF
PHOTOFACT[®]

REPORTER

FOR THE ELECTRONIC SERVICE INDUSTRY

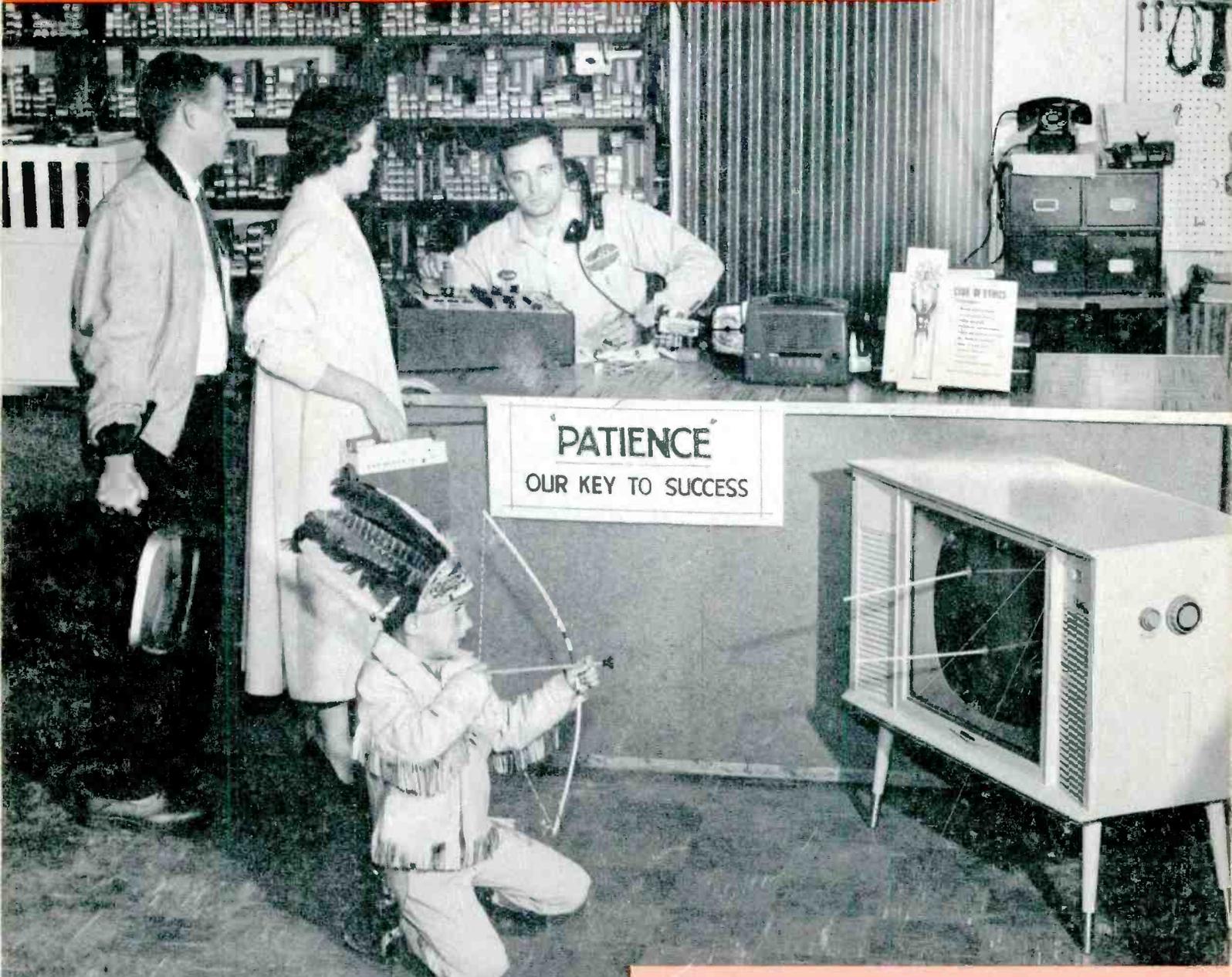

Capacitor Color Codes

AUXILIARY SYNC CIRCUITS

Servicing Transistor Radios

INDUSTRIAL ELECTRONICS—PART 2

... PLUS OCTOBER SUPPLEMENT
TO SAMS MASTER INDEX

SAVE MANY WAYS

You pay nothing extra for cabinet

Cabinets stack neatly with others

28 clearly identified compartments

Spend much less time ordering



with **IRC**[®] Resist-O-Cabinets

Four "Savingest" Assortments

IRC Resist-O-Cabinets come complete with a colorful all-metal cabinet and any one of four resistor assortments. All resistors are guaranteed fresh and packed in the cabinet at the factory. Cabinets are yours at no extra charge. They have 4 "non-spill" drawers with 28 clearly identified compartments. Design permits neat stacking.

Assortment	No. 3A 2 Watt	No. 4A ½ Watt	No. 5K 1 Watt	No. 6A Combination
Contents	120 BTB 2 Watt Fixed Composition and BW-2 Insulated Wire Wound Resistors. 33 different values from 4.7 ohms to 1 megohm.	150 BTS Fixed Composition and BW-½ Insulated Wire Wound Resistors. 47 ohms to 10.0 megohms.	125 BTA Fixed Composition and BW-1 Insulated Wire Wound Resistors. 28 different values from 47 ohms to 4.7 megohms.	Combination of 139 ½, 1, and 2 Watt Resistors and Type DCF Precistors. 63 different values from 47 ohms to 5 megohms.
List Price	\$39.60	\$25.50	\$31.25	\$31.65
Your Price	\$24.00	\$15.00	\$18.75	\$18.85


ORDER FROM YOUR IRC DISTRIBUTOR

Radio and TV technicians who use IRC Resist-O-Cabinets call them the "savingest" resistor deal they know of. Here's why. You save time and trouble in ordering—all of the resistors most used in TV repair work are pre-selected for you. You save money—you not only get resistors at regular dealer price, but also a handsome all-metal cabinet at no extra charge. And you save time on the job—you know what you have—and you have what you want when you want it. To trim costs and fatten profits, buy resistors in IRC Resist-O-Cabinet assortments.

Wherever the Circuit Says



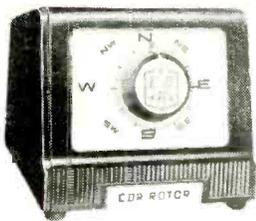
INTERNATIONAL RESISTANCE CO. Dept. 363 401 N. Broad St., Phila. 8, Pa. In Canada: International Resistance Co., Ltd., Toronto, Licensee



AR-22




TR-2

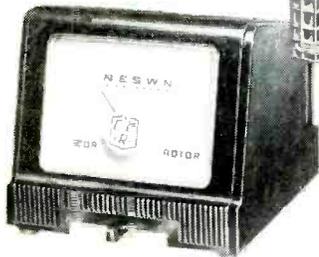


TR-4

CDR ROTORS

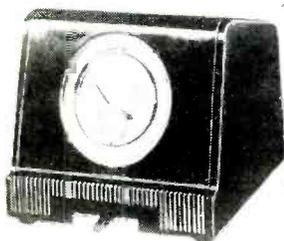

TR 11 and 12

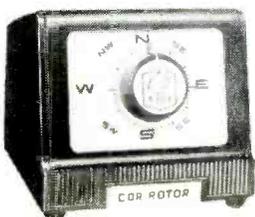

AR 1 and 2

5-star feature...

- 1 the best color TV picture**
the growth of color TV means an even greater demand for CDR Rotors for pin-point accuracy of antenna direction.
- 2 a better picture on more stations**
CDR Rotors add to the pleasure of TV viewing because they line up the antenna perfectly with the transmitted TV signal giving a BETTER picture . . . and making it possible to bring in MORE stations.

- 3 tested and proven dependable**
thousands and thousands of CDR Rotors have proven their dependability over years of unflinching performance in installations everywhere in the nation. Quality and engineering you know you can count on.
- 4 pre-sold to your customers**
the greatest coverage and concentration of full minute spot announcements on leading TV stations is working for YOU . . . pre-selling your customers.

- 5 the complete line**
a model for every need . . . for every application. CDR Rotors make it possible for you to give your customer exactly what is needed . . . the right CDR Rotor for the right job.



CORNELL-DUBILIER
SOUTH PLAINFIELD, N. J.



THE RADIART CORP.
CLEVELAND 13, OHIO

Reputation Builder #4: it pays to wear a smile




• "Not so courteous servicemen" get less than 20% repeat business



• BUT... "pleasant and courteous servicemen" get a healthy 85% repeat business

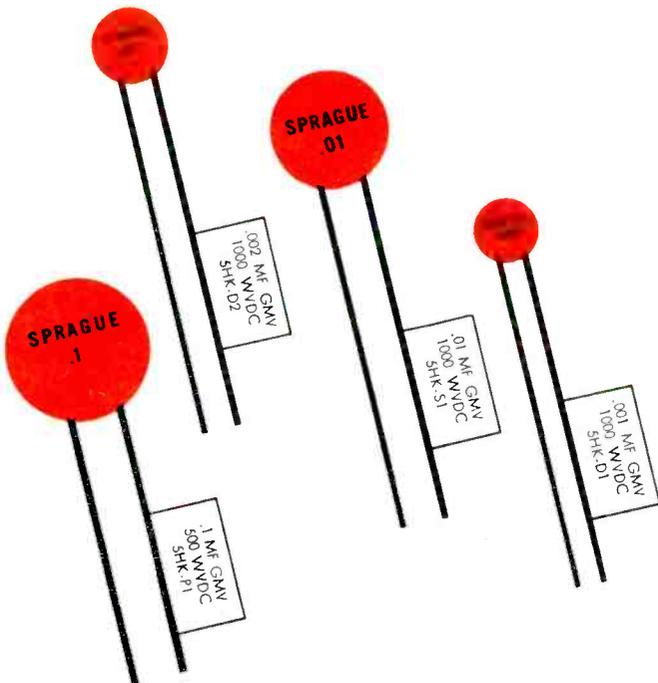it pays to replace with Sprague Cera-mite* Ceramic Capacitors



don't be vague ... insist on

• Another way to build and hold a reputation is to insist on top quality replacement parts. Callbacks due to replacement failures not only cost you money . . . they also cost you customers! Replace with less than the best and you place your reputation at stake. In capacitors, the best is Sprague.

• Take Cera-mite Ceramic Capacitors, for example. Their silvered flat-plate design gives Cera-mites low self-inductance . . . means very high by-pass efficiency in all TV circuits . . . permits higher self-resonant frequency than tubular ceramic or molded mica capacitors. And they often can replace paper capacitors, too! These capacitors are tough, tiny, and dependable in every application . . . even under severe humidity and vibration conditions. They fit easily into tight spaces. Designed for continuous operation at 85°C (185°F).

• For the complete list of ratings for all types of Sprague ceramics, get your copy of Sprague's latest radio and TV service catalog, C-456. Write Sprague Products Co., Distributors' Division of Sprague Electric Company, 105 Marshall Street, North Adams, Mass.

*Trademark

SPRAGUE[®]

world's largest capacitor manufacturer

SPRAGUE RESEARCH IS CONSTANTLY PRODUCING NEW AND BETTER CAPACITORS FOR YOU

PUBLISHER
Howard W. Sams

GENERAL MANAGER
Mal Parks, Jr.

EDITOR
Verne M. Ray

ASSOCIATE EDITORS
Leslie D. Deane
Thomas A. Lesh
Calvin C. Young, Jr.

CONSULTING EDITORS
William E. Burke C. P. Oliphant
Robert B. Dunham George B. Mann
Paul C. Smith

ART DIRECTOR **EDITORIAL ASSISTANT**
Glenn R. Smith Gwen Bigham

PHOTOGRAPHY **CIRCULATION**
Robert W. Reed Pat Tidd

ADVERTISING SALES OFFICES

MIDWESTERN
PF REPORTER,
2201 East 46th Street, Indianapolis 5, Ind.
Clifford 1-4531

EASTERN
Paul S. Weil and Donald C. Weil,
39-01 Main Street, Flushing 54, New York.
Independence 3-9098.

WESTERN
The Maurice A. Kimball Co., Inc.,
2550 Beverly Blvd., Los Angeles 57, Calif.
Dunkirk 8-6178; and 681 Market Street,
San Francisco 5, Calif. EXbrook 2-3365.

Published monthly by Howard W. Sams & Co., Inc., at Indianapolis 5, Indiana.

Entered as second class matter October 11, 1954, at the Post Office at Indianapolis, Indiana, under the Act of March 3, 1879.

Copyright 1957 by Howard W. Sams & Co., Inc. No part of the PF REPORTER may be reproduced without written permission. No patent liability is assumed with respect to the use of information contained herein.

A limited quantity of back issues are available at 35c per copy.

Subscription prices in U.S.A. and possessions:
1 yr., \$3.00; 2 yrs., \$5.00; 3 yrs., \$7.00. In Canada and Pan America: 1 yr., \$3.60; 2 yrs., \$6.00; 3 yrs., \$8.50. Foreign subscriptions: 1 yr., \$6.00; 2 yrs., \$11.00; 3 yrs., \$15.00.

next month

HIGHLIGHTS OF 1958 TV SETS

A picture story previewing many of the features you'll be seeing next year, with suggestions for practical servicing techniques that will save time.

KEEPING UP WITH VERTICAL SWEEP

An article describing a revised blocking oscillator and output circuit that is becoming more frequent in its appearance in modern TV sets.

ALIGNING VHF TUNERS

You won't want to miss Part 4 of "Inside TV Tuners," outlining the requirements for tuner alignment, including the equipment used, symptoms which indicate the need for alignment, and the reasoning behind some of the steps used in actual procedures.

VOLUME 7, No. 10



OCTOBER, 1957

PF REPORTER

FOR THE ELECTRONIC SERVICE INDUSTRY

CONTENTS

This Month's Cover	65
Letters to the Editor	6
Shop Talk	10
Transistorized TV Sync Circuits	<i>Milton S. Kiver</i>
Troubled by Color Codes?	14
Latest capacitor color coding data.	
Servicing Industrial Electronics—Part 2	16
All about industrial heat-sensing and temperature-controlling devices.	<i>Melvin Whitmer</i>
Theory of Auxiliary Sync Circuits	20
Theory and servicing hints on special sync-handling circuits.	
Removing Radio from 1955 Chevrolet	22
Servicing New Designs	24
Space-saving TV tuner in 1958 set; the Motorola "Tube Sentry."	<i>Thomas A. Lesh</i>
Notes on Test Equipment	30
Reports on intermittent analyzer, meter probes, transistor tester and millivoltmeter.	<i>Leslie D. Deane</i>
Dollar & Sense Servicing	40
<i>John Markus</i>	
More Facts on Servicing Transistor Radios	42
How to replace components and make voltage and resistance measurements.	
Quicker Servicing	56
<i>Calvin C. Young, Jr.</i>	
Inside TV Tuners—Part 3	60
Design and operation of oscillator-mixer circuits.	
Let's Talk Business	81
Product Report	85
Free Catalog & Literature Service	88
Supplement to SAMS Master Index	89

SUBJECT REFERENCE INDEX

BUSINESS		Oscillator adjustments, tuner	56
Estimates, hints for making		Oscillator-mixer circuits	60
accurate	81	Transistor radios	42
Personnel, considerations in		Yokes with width sleeves	58
managing	40	TEST EQUIPMENT	
Sales as a sideline	40	Eby Trans-Tester	36
CIRCUITS		Futuramic meter probes	32
Auxiliary sync	20	Bolometer	17
Filament, in new Motorola	28	Portable potentiometer	76
Oscillator-mixer	60	Scope-Probe	58
Temperature-controlling	16	Simpson millivoltmeter	38
Transistorized sync	10	Wintronix Intermittent Analyzer	30
COMPONENTS		THEORY	
Capacitors, color codes for	14	Bolometer	17
Thermistors	17	Oscillator-mixer circuits	60
Thermocouples	75	Sync circuits, special type	20
Transistors for video-frequency		Thermistor	16
applications	10	Thermocouple	75
SERVICING		Transistor circuits, TV sync	10
Auto radio removal	22	TRANSISTOR CIRCUITS	
Fine-tuning belt replacement	56	Portable radio	42
		TV Sync stages	10

USE HANDY CARD AT BACK TO ENTER YOUR SUBSCRIPTION

Sylvania TV Damper Tubes



...New design plus



New heater-cathode design helps Sylvania damper types pass this dynamic arc test with flying colors. Dynamic tests such as this have now been instituted by Sylvania on all important types in every

critical TV function. It's Sylvania's way of helping you overcome problems which often make the difference between profit and loss and a happy or unhappy customer.



new dynamic tests produce high E.L.A.*

Sylvania damper tubes scored an **Earned Life Average* of 99.54% in a recent test of types in the 6AX4GT family. This means greater service reliability for you with an absolute minimum of trouble resulting from arcing, heater-cathode shorts and heater burnouts. It's the result of a new heater-cathode design introduced by Sylvania to meet your service needs.

Earned Life Average is an established method for evaluating tube life performance; for the service industry it serves as an index of protection against call-backs. These tests

were performed in TV sets which simulated field service conditions where high line voltages are encountered.

109 Sylvania damper tubes performed for a total of 132,890 hours out of a possible 133,500 hours for an *Earned Life Average* of 99.54%.

To Sylvania this is satisfying evidence that the service industry has been provided with extra protection against the most common damper tube troubles. We think you'll agree too, that in the long run you'll profit more with Sylvania.



SYLVANIA

SYLVANIA ELECTRIC PRODUCTS INC.
1740 Broadway, New York 19, N. Y.
In Canada: Sylvania Electric (Canada) Ltd.
University Tower Bldg., Montreal



Get the
LION'S SHARE

of the new
transistor
business

STOCK and SELL



TRANSISTORS

Transistor receivers are now big business and before you know it, servicing these sets will be big business, too.

With Raytheon Transistors in stock, you'll be way ahead of your competitor in the race for this profitable business because the majority of these sets use Raytheon Transistors.

What's more, Raytheon Transistors are (1) low priced (2) available for every application (3) stocked by Raytheon Suppliers from coast to coast. With Raytheon on your shelves you have an excellent opportunity to cash in on the rapidly growing market for Transistors among experimenters, hobbyists and engineers.

Ask your Raytheon Tube Supplier about the profits to be earned with Raytheon Transistors.

Raytheon Transistor Applications Books Vol. I and Vol. II

Musts for Service Dealers . . . Full of practical circuit design information, transistor theory and shop practice . . . Many circuit applications including circuits for making useful transistorized shop equipment. Buy from your Raytheon Tube Supplier or send 50¢ for each book to Department PF2.



Excellence in Electronics

RAYTHEON MFG. CO.

Receiving and Cathode Ray Tube Operations
Newton 58, Massachusetts

Letters to the

EDITOR

Dear Editor:

Recently, I serviced an RCA KCS66C that would lose horizontal sync after about 30 minutes of operation. Adjustment of the hold control would not correct the condition, but turning the horizontal frequency slug would; however, a ragged vertical white streak then appeared at the center of the screen. All voltages and resistances were normal, and in an effort to stabilize the oscillator, I readjusted the transformer until the first peak in the waveform was quite a bit lower than the other. While loss of sync no longer occurs, I know the trouble has not been cured. Can you help me?

V. F. RIDDLE

Birmingham, Ala.

It would seem that some component in the frequency-determining circuit is changing value during operation. Normally, the signal with equal peaks will be obtained with the frequency and phasing slugs at about center range. Should either slug be adjusted toward one extreme, the jagged white streak would be a natural occurrence.

Components that could cause the trouble are the .01 mfd capacitor across the stabilizing coil, the coil itself, or the 330-mmfd mica feedback (which is the most likely suspect.)—Editor

Dear Editor:

On several occasions, we have observed CRT screens which light up after the set has been turned off. Often, this may not occur until the set has been off for 30 minutes or more. It is not just a dot of light; instead the entire screen flickers on and off. Also, the condition does not occur each time the set is turned off. Can you give us an explanation, please?

FRANK KNIGHT

Frank's TV Service
Mansfield, Ark.

The capacity between the coatings of the picture tube is capable of holding a charge for quite some time, thus maintaining a certain amount of 2nd-anode voltage after the set is turned off. This charge can only diminish by a transfer of electrons, which are in short supply with no heater current. As a small supply slowly builds up, they are drawn to the screen and cause it to fluoresce, sometimes hours after the set has been turned off.

If you will install a switch that will ground the CRT cathode when the set

is turned off, the tube will conduct heavily until the B+ filters have discharged and the anode current thus produced will discharge the anode capacitor.—Editor

Dear Editor:

The picture on page 16 of your July issue seems to be reversed, making a "lefty" out of Jim Schiffner. I thoroughly enjoy reading your magazine and find many helpful articles in every issue.

JOHN STERINER

Chambersburg, Pa.

You're right.—Editor

Dear Editor:

Just read "TV Waveforms" published in your July issue. How you expect to teach anyone about waveforms is beyond me. You say in the article that a scope "having fairly good wide-band response was used." It takes a bandwidth of at least 1.7 mc to properly display horizontal sync pulses. I am wondering if the scope used would even show audio signals properly.

If you want to upgrade the technician, waveforms should be shown as they really are. Gone are the days when 20,000 ohm-per-volt meters were used in high-impedance circuits.

LOU THELEMAN

Monterey Park, Calif.

You are very observant! Some of the waveforms shown do indicate that a narrow-band scope was used, but actually this was not the case. The lab-type instrument used has a switch so that it may be used in either wide-band or high-sensitivity applications. To get the desired effects, some of the waveforms were photographed with the switch in the high-sensitivity position, and therefore the response was down somewhat at the higher frequencies. In addition, the sweep frequency was off-set slightly and the intensity was far above normal. We were more interested in getting the various peculiarities than ideal waveforms because we felt that they would be more helpful to the practicing technician.—Editor

Dear Editor:

The schematic in the August "Coffee Break" shows a grounded-grid lead in a detector diode. How come? Have found your articles very informative.

D. MASTRO

Mastro TV
Portsmouth, Va.

The 6AL5 has often been shown to have what appears to be a grid, but it isn't a grid at all. Pin 6 connects to an internal shield which is always grounded for best performance.—Editor

PF REPORTER · October, 1957

ASTRON "Staminized" CAPACITORS HAVE . .

long life

**NO CALL-BACK CONSTRUCTION
ASSURED BY 10 INDIVIDUAL
PRODUCTION TESTS**

plus **100% FINAL INSPECTION**


Long life in capacitors is important to you as a serviceman. Complete confidence in the components you use is a necessity, because your business is built on reputation.

Astron considers the serviceman's reputation to be prime importance. That is why each capacitor is manufactured under Astron's "Staminized" system. Astron's "Selected Purchasing" guarantees that only the very finest of raw materials are chosen. Astron's special production techniques are supplemented by continuous inspection under strict quality controls. Production tests are made right on the production line . . . 10 separate tests in all. **A 100% final inspection is made before any capacitor can be shipped.**

You can put your trust in Astron . . . your assurance of top performance . . . every time.

There is an Astron "Staminized" Capacitor built especially to fill the specific, exacting replacement requirements of any job you tackle.

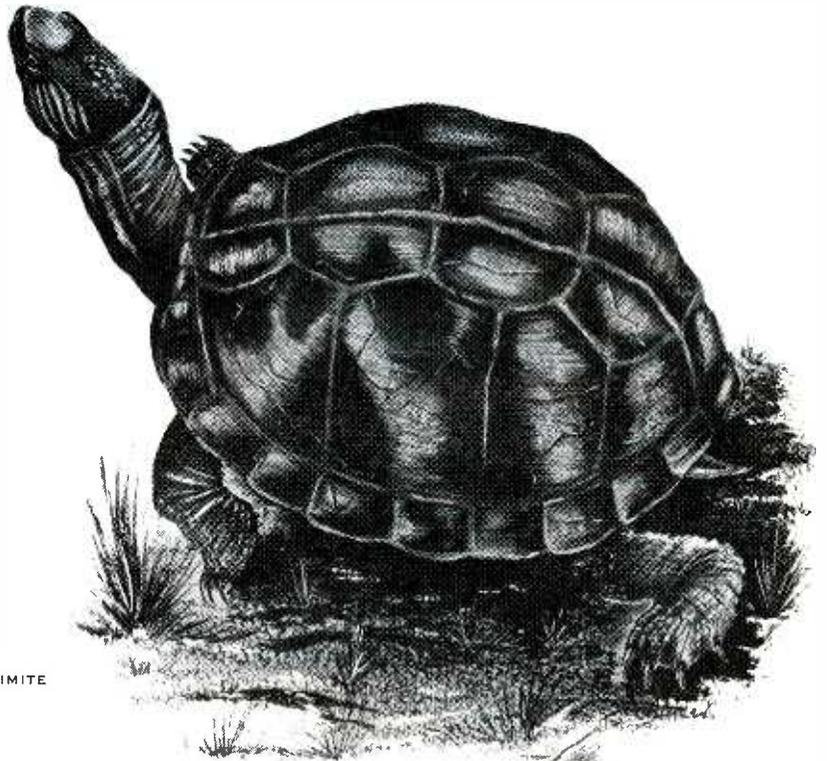Remember, your reputation is our business, too. Build it, guard it, protect it . . . Buy Astron!



*Trade-Mark



SAFETY MARGIN "SM" MINIMITE

BLUE-POINT® MOLDED
PLASTIC PAPER TUBULAR



Free Servicing Aid . .

Save time, use handy Astron pocket-sized Replacement Catalog and Pricing Guide (AC-4D) . . Write today!



ASTRON

C O R P O R A T I O N


255 GRANT AVENUE

EAST NEWARK, N. J.

Export Division: Rucke International Corp., 13 East 40th St., N. Y., N. Y.

In Canada: Charles W. Pointon, 6 Alcina Ave., Toronto 10, Ontario

**NO
MATTER
WHAT
THE
WEATHER...**

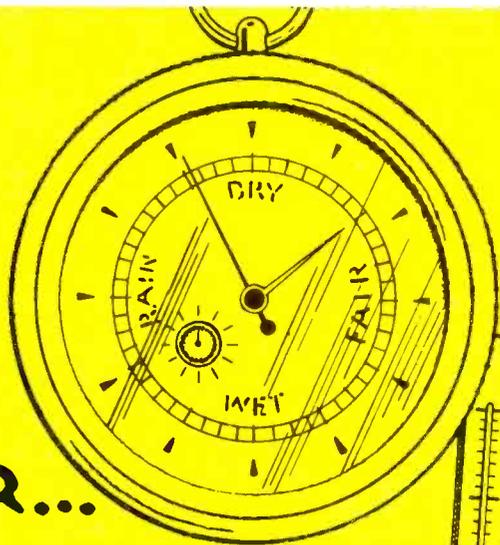

Hot-and-humid or cold-and-damp... Aerovox "DURAMIC" Capacitors give you "trouble-free" operation even under the most adverse weather conditions. You avoid costly call-backs when you specify-and-buy "DURAMIC" capacitors because the severe-service characteristics are built into each capacitor.

AEROVOX "DURAMICS"

...utilize a dense steatite case to provide exceptional protection against humidity. All terminal lead wires are firmly imbedded into the end seals so that they will not pull out or work loose even under the most severe operating conditions.

AEROVOX "DURAMICS"

...have that exclusive Aerovox end-fill which will not soften or flow nor separate from the case at any rated temperature.

AEROVOX "DURAMICS"

...have excellent power-factor, insulation resistance and temperature characteristics. Operating temperatures from -55°C. to $+85^{\circ}\text{C.}$ Available in 10 standard voltage ratings from 200 to 15,000 VDC.

Your local Aerovox Distributor always carries a stock of Aerovox "DURAMIC" Capacitors in a wide range of capacitance values and voltage ratings. While you're there ask for your free copy of the latest Aerovox Catalog with complete listings of all Aerovox components.



AEROVOX CORPORATION

**DISTRIBUTOR SALES DIVISION,
NEW BEDFORD, MASS.**

In Canada: AEROVOX CANADA LTD., Hamilton, Ont.
Export: Ad Auriema, 89 Broad St., New York, N. Y., Cable: Auriema, N. Y.

Dear Editor:

I have a Silvertone (chassis 100-700-10) with insufficient brightness. All voltages appear to be normal, including 2nd-anode potential. A new picture tube did not alter the performance. Any information you can provide would be appreciated.

MILTON E. VERDOOT

Green Bay, Wis.

Sounds like a misadjusted or defective ion trap. Suggest you substitute one having the correct magnetic strength.—Editor

Dear Editor:

The text in reference to Fig. 10 of the "Shop Talk" column in the June issue states that both halves of the input signal will give correct polarities in the output. While it is true that the polarities will be correct, only the positive half cycle of the input will give true reproduction. For conduction, the emitter-base junction of a transistor has to be biased in the forward direction. Without some amount of bias in addition to signal bias, the negative half cycle of the input can only cause the output signal to reach the supply voltage level. In this case, the output signal due to the negative half cycle of input is not a function of the amplitude of the input.

C. E. RODGERS

Torrance, Calif.

The entire circuit of Fig. 10 should be operated class A. This was not specifically stated, nor was a suitable biasing network shown. With proper biasing, both halves of the input signal will be effective in causing current to flow through the circuit.—Editor

Dear Editor:

I have a Philco TV Model 22BU4000, Code 130 in the shop that has me up a tree. At first, channel 46 did not come in at all, but channels 52 and 34 came in good. I tried substituting tubes, and when I put in a new 6T4 in place of the 6AF4, channel 46 came in perfect, but after about an hour the set went out on channel 34. After tuning the set off-channel and then back, channel 34 would come in for a few minutes and then go out suddenly. Could you help me with this problem?


JAMES P. GRACE

Elkhart, Ind.

Since Reader Grace has pretty well eliminated tubes as the source of this intermittent trouble, it is our suggestion that he replace the entire UHF tuner in this set.—Editor

You can do more than ever before with this new portable **B&K**

AUTOMATIC MONEY-MAKER

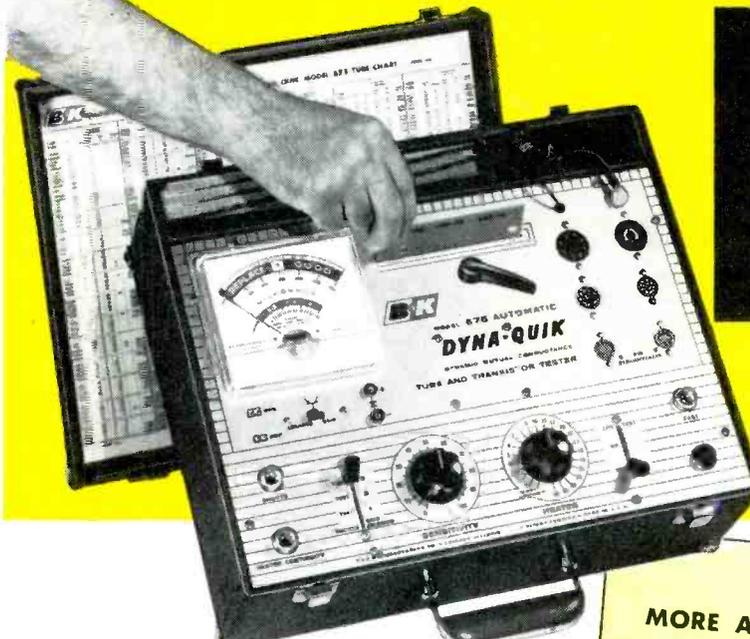

**TESTS TUBES
AND TRANSISTORS
Automatically
WITH LABORATORY ACCURACY**

- Saves Servicing Time
- Sells More Tubes
- Satisfies More Customers



B&K MODEL 675
AUTOMATIC
DYNA-QUIK
DYNAMIC MUTUAL CONDUCTANCE
TUBE & TRANSISTOR TESTER

MORE ACCURATE TEST

Tests Each Section of Multiple Tubes Separately for Gm, Shorts, Grid Emission and Life

Tests each tube for Gas Content and Grid Emission simultaneously with Short check. Instantaneous Heater Continuity test.

SIMPLIFIED AUTOMATIC DYNA-CARD SYSTEM

With only 60 heavy-duty, phenolic Dyna-Cards you can test over 500 tube types. Dyna-Card automatically sets socket connections for quick, accurate test. Each Dyna-Card is identified and indexed, ready to use. Always kept up-to-date simply by adding new Dyna-Cards. Minimizes obsolescence.

CHECKS OVER 99%

of the tubes most widely used in television receivers plus popular home and portable radio tubes.

ONE EXTRA TUBE SALE

on each of 5 calls a day pays for the Dyna-Quik in a few weeks.

TESTS TRANSISTORS, TOO

Transistor Section checks junction, point contact and barrier transistors, germanium and silicon diodes, selenium and silicon rectifiers.

Again, B&K helps servicemen give faster, better service at less cost and make more money. The new automatic Model 675 makes tube checking quick and easy in the home or shop. (Tests transistors, too.) Measures true dynamic mutual conductance. Makes complete tube test in seconds, under actual operating conditions of the set. Checks average set in a few minutes. Simple to operate. No multiple switching. No roll chart. Shows customer the true condition and life expectancy of tubes in the set, sells more tubes on-the-spot, saves call-backs. Quickly pays for itself.

Shows tube condition on "Good-Bad" scale and in micromhos. Large 4½" meter has two highly accurate ranges calibrated 0-6000 and 0-18,000 micromhos. 7-pin and 9-pin straighteners are mounted on panel. Automatic line compensation. Special bridge monitors line voltage continuously. Light weight, easily portable in handsome leatherette-covered carrying case. Operates on 105-125 volts 60 cycle a.c. Size: 15¼" x 12¼" x 6". Net wt: 10½ lb. Net, **\$16995**

Also makers of famous CRT, DYNA-SCAN, CALIBRATOR



See your B&K Distributor, or write for Bulletin 675-R

B & K MANUFACTURING CO.
3726 N. Southport Ave. • Chicago 13, Illinois

Canada: Atlas Radio Corp., 50 Wingold, Toronto 10, Ont. Export: Empire Exporters, 439 Broadway, New York 13, N.Y.

ShopTalk

MILTON S. KIVER

Author of ...
*How to Understand and Use TV Test Instruments
 and Analyzing and Tracing TV Circuits*

Transistorized Sync Stages

A portion of the video signal in a television receiver is taken from the video amplifier section and fed to the sync separators where the sync pulses are divorced from the rest of the signal. In vacuum-tube circuits this usually requires two stages. The same separating action can also be accomplished with transistor circuits, suitable examples of which are discussed in this article.

A two-stage transistorized sync separator which functions satisfactorily is shown in Fig. 1.* Both transistors are connected as common-emitter amplifiers, although

the first transistor is a p-n-p unit, while the second is of the n-p-n variety. To maintain the steep vertical sides of the sync pulses, it is desirable to use high-frequency units. A low-frequency transistor would not pass the higher order harmonics, and would cause sloping of the sides of the pulse, thereby degrading the timing accuracy of the sweep oscillators.

Within the circuit of X1, we find a combination of fixed and self-adjusting bias in the emitter leg. The fixed bias, which drives the emitter-base circuit into conduction, is furnished by a 20-volt battery. The self-adjusting bias is developed by the emitter current flowing through R1. The voltage developed across this resistor opposes the battery voltage and the

combination of R1 and C1 tends to keep X1 cut off at all times except when the negative-going sync pulse is active. At this time the cutoff bias is overcome, current flows and C1 is recharged. This flow of current will produce a positive-going sync pulse across R2. The values of E2 and R2 are chosen so that the collector is not driven to saturation; this enables the pulse amplitude across R2 to vary according to variations in input signal. The emitter current likewise varies with changes in the strength of the incoming signal so that the bias is kept at the proper level for sync separation on all signals, strong or weak.


The second stage, containing transistor X2, is used to amplify and limit the amplitude of the pulses appearing across R2. X2 is biased so that it is driven to saturation by the sync pulse tips of any usable signal. This not only establishes the sync pulse amplitude at a relatively fixed value, but it also serves to clip off noise spikes greater than sync.

In order to insure that the foregoing saturating action is achieved even with weak signals, a combination of fixed and variable bias is employed. (If only one type of bias were used, it would have to be set so that X2 would be heavily overdriven on strong signals. Under these conditions it is found that the sync pulses tend to broaden considerably and could introduce a phase shift when applied to some types of horizontal phase detectors.) The fixed bias is furnished by battery E3, while the variable bias is developed by C2 and R3. When the incoming signal tends to drive X2 far beyond saturation, the base-emitter circuit develops a voltage across R3 (with the polarity indicated) which reduces the extent of the overdriving.

The final output pulse has an over-all amplitude of 15 volts which, it will be noted, makes full use of the battery voltage applied to the collector. This action is possible because transistor characteristics are linear down to practically zero volts. Output pulse polarity is negative; if a positive-going pulse were desired, a phase inverter could be used.

• Please turn to page 70

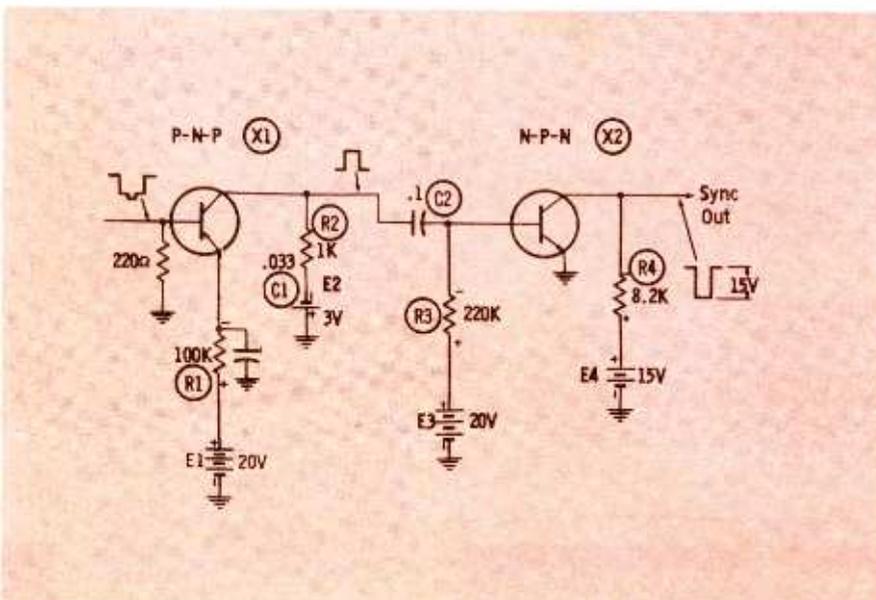
* "Transistorized Sync Separator Circuits For TV Receivers" by H. C. Goodrich, RCA Review, December, 1955.



(Courtesy RCA Review)

Fig. 1. A two-stage transistorized sync separator.

GOOD-ALL CAPACITORS

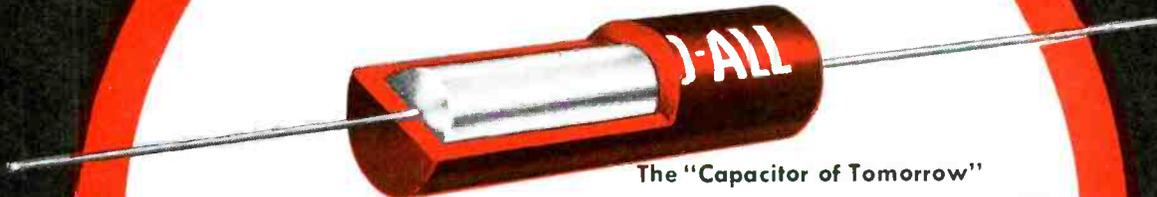

The "Capacitor of Tomorrow"

600-UE Mylar* Dielectric • Molded in Epoxy**

NEW to the replacement market! Widely used by leading equipment manufacturers.

The 600-UE is created by the skillful combination of new "wonder materials," and Good-All's advanced design, exclusive production technique and tight quality control. It is ideal for replacement use in today's modern circuitry.

FEATURES: • Low leakage • High stability • Long, trouble-free life • Rugged construction • Extremely reliable service in humid climates

SUPERIOR QUALITY • COMPETITIVE PRICE

DU PONT

***MYLAR**® is DuPont's trade name for their amazing space-saving polyester film. This thin, tough film makes an ideal capacitor dielectric. Its inherent electrical stability and exceptional dielectric strength contribute greatly to the trouble-free service of the 600-UE.


SHELL

****EPON**® is Shell's trade name for their epoxy resin wonder plastic molding compound base. Far superior to common molding materials, Epon forms an extremely rugged moisture-tight case. Leads adhere securely to the compound. High dielectric strength is also an attractive feature of this tough, dense material.



GOOD-ALL ELECTRIC MFG. CO.

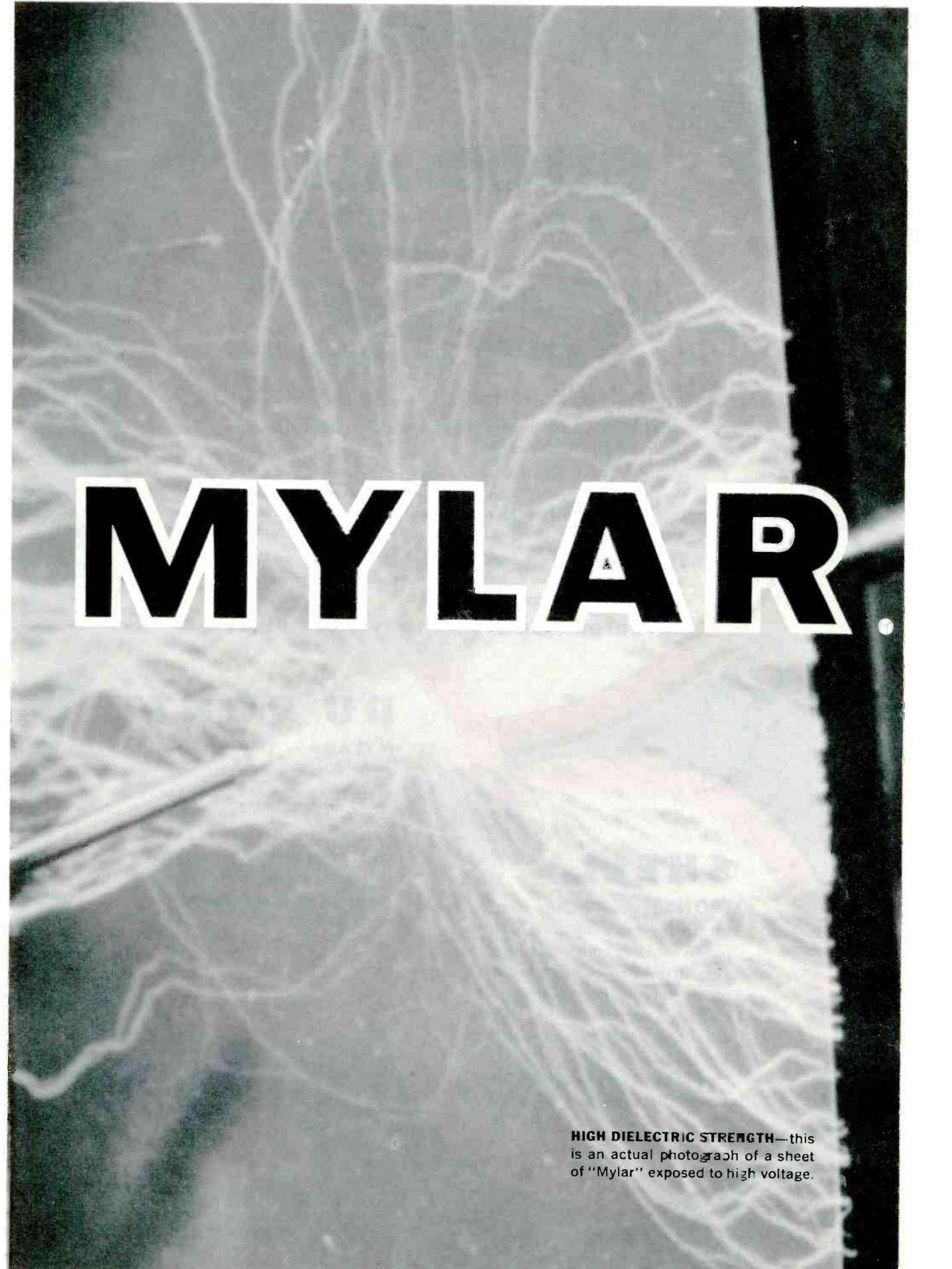Distributor's Division • 26 RITTENHOUSE PLACE • ARDMORE, PENNSYLVANIA



MYLAR

HIGH DIELECTRIC STRENGTH—this is an actual photograph of a sheet of "Mylar" exposed to high voltage.

Report
from Du Pont
for
electronic
service
dealers



• • THE MOST TALKED ABOUT NEW DIELECTRIC FOR CAPACITORS!

*Here are 5 important reasons you should
use capacitors made with Du Pont "Mylar"*

1. MYLAR* has high dielectric strength . . . average of 4,000 volts per mil . . . average power factor of 0.003 at 60 cycles . . . dielectric constant above 3.0 at 72°F., 1,000 cycles.

2. MYLAR is tough and durable . . . permits capacitor manufacturers to save space because the film is extra-strong even in the thinnest gauges.

3. MYLAR has long life . . . will not deteriorate with age or voltage stresses within normal operating ranges of most electronic equipment.

4. MYLAR is moisture-resistant . . . this polyester film performs equally well in hot, humid climates or cold, crisp air . . . it won't dry out and become brittle with age.

5. MYLAR has proved its value . . . capacitors made with "Mylar" as the dielectric are being used in guided missiles and sensitive electronic computers.

Yes, where high reliability and long life are concerned, capacitors made with "Mylar" assure the finest in

performance. Think of it! No more wasted call-backs for failure of newly installed capacitors . . . capacitors with "Mylar" assure longer shelf life, no storage problems.

So next time you order, ask your distributor for highly reliable, long-life capacitors made with Du Pont "Mylar". For detailed information on the basic properties of "Mylar", write: Film Department, Room EP-10, The Du Pont Co., Wilmington 98, Delaware.

*"MYLAR" is Du Pont's registered trademark for its polyester film.
Du Pont manufactures "Mylar"—not finished capacitors.



BETTER THINGS FOR BETTER LIVING . . . THROUGH CHEMISTRY

October, 1957 • PF REPORTER



Troubled By Color Codes ?


The "age-old" problem of deciphering color codes is still to a great extent unsolved by neophyte and old timer alike. For the most part, this is due to the fact that the code has been expanded to provide additional information for a greater variety of units.

In this article, we have selected the various capacitor types in current use to show the variety of color codes you are most likely to encounter.

The Paper Tubular

Molded paper tubular capacitors, at the discretion of the manufacturer, may have their value, tolerance, and working voltage expressed typographically or by colors. In the case of color, you will generally find five or possibly six color bands on the body of the component.

To read the color code in the proper sequence, orient the unit so that the closely-spaced group of four color bands appears at the left. Reading from left to right and referring to the chart, we find that the unit pictured has a value of 4,700-mmf, a tolerance of $\pm 20\%$, and a 600 working-voltage rating. The voltage rating will be indicated by either one or two color bands. One band indicates a rating of less than 1,000 volts, while two indicates 1,000 volts or more. Adding two zeros to the one or two significant figures will give the voltage rating.

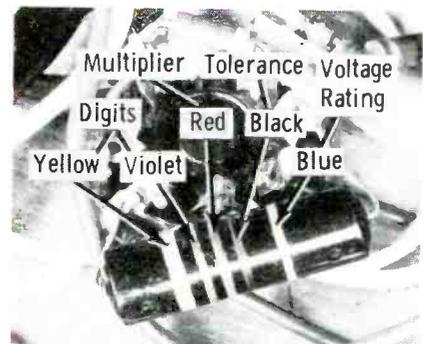


The Mica

Today, we find an increasing number of molded-mica capacitors using the RETMA 6-dot system. One can recognize this system by first orienting the unit so that the arrow on its body points to the right. If the dot in the upper left-hand corner is white, the code follows RETMA standards.

Using the chart, the second color dot in the upper row represents the first significant figure of the capacity value (gray or 8 in the example shown). Interpreting the other data, we find that this unit is an 82-mmf, $\pm 10\%$, class-B mica, coded under RETMA standards. The class designation reveals certain design requirements involving the Q and temperature coefficient.

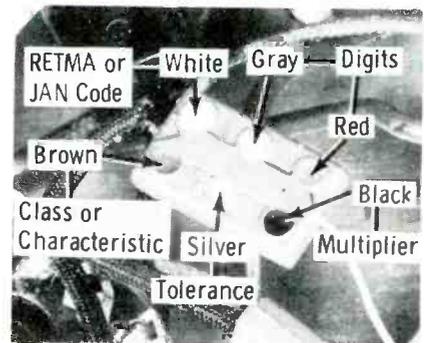
The JAN or Joint-Army-Navy 6-dot system is also employed for mica capacitors and differs from the RETMA system only in that the first dot is black instead of white.



The Insulated Ceramic Tubular


Constructed with radial leads, this style of capacitor generally uses a 5-dot system as shown and is oriented by placing the color dot closest to one end of the unit on the left. Referring to the chart and reading from left to right, we find that the capacitor is a bypass or coupling, 1,000-mmf unit, having a value tolerance of $\pm 20\%$.

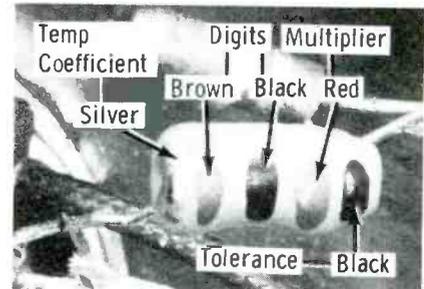In some instances, this style of capacitor may use a 6-dot color code, which is discussed under the non-insulated ceramic tubular type.



The Non-Insulated Ceramic Tubular

This type capacitor is currently coded with either a 5- or 6-dot system. The 5-dot system is identical to that given for the insulated-tubular or disc-ceramic. The 6-dot system, however, involves an extended temperature coefficient. The color dots or stripes will either be grouped slightly toward one end of the body or the first color dot will be larger to indicate the starting point. The first two colors are used to express the temperature coefficient and, in the example shown, these two colors are yellow and orange. Taking a look at the chart, we find that this unit is an N2200, 1-mmf capacitor, having a tolerance of ± 0.25 mmf.

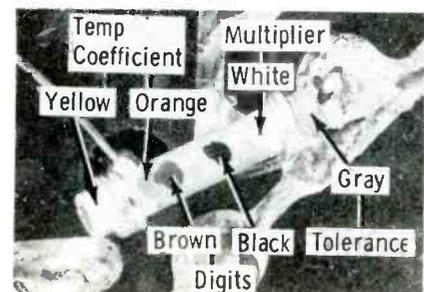



The Insulated Ceramic Disc

Although this type of capacitor is usually typographically marked, it may be color-coded with 5 dots or stripes. Using the chart, and reading from left to right with the unit oriented as shown, we find that this unit is an N150, 10-mmF capacitor, having a tolerance of ± 0.5 mmf.

The term NPO means negative-positive-zero or a zero temperature coefficient. With this designation, capacitance remains constant regardless of temperature change.

The abbreviation PPM/ $^{\circ}$ C in the chart stands for "parts per million per degree centigrade." In other words, if a temperature coefficient is given as N150, capacity will decrease 150 parts per million with every degree of increase in operating temperature. If the letter P precedes the number, capacity then increases with temperature rise.

A few late-model receivers are using a new 6-dot code on this style of capacitor. The first two colors represent the maximum capacitance change within a specified temperature range rather than a two-color temperature coefficient. The first color under this system will always be gold, silver, or brown. Reading the code for the unit pictured, we find that it has a ΔC of $\pm 15\%$ within a temperature range of -30° C to $+85^{\circ}$ C, a value of 1,500 mmf, and a GMV tolerance (guaranteed minimum value, -0% to $+100\%$).

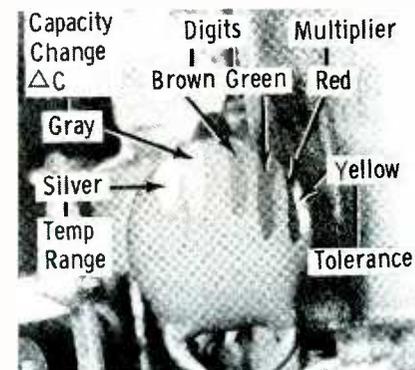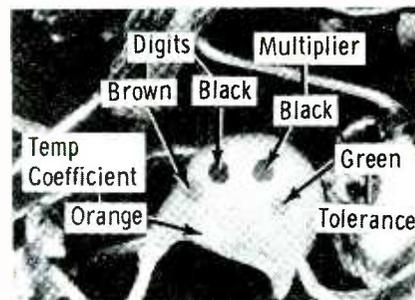


The Miniature-Molded Ceramic

About half the size of a standard $\frac{1}{4}$ -watt resistor, these low-valued capacitors are found in a limited number in RF-coupling applications. The markings for such units have not been completely standardized and may encompass the use of one to four color bands. A present-day capacitor of this design, however, generally uses a 4-dot system as illustrated. In this arrangement, the last color band is always gold or silver, indicating a value tolerance of $\pm 5\%$ or $\pm 10\%$, respectively.


Reading the bands and referring to the chart, we find that this capacitor is a 6.8-mmF unit with a tolerance of $\pm 10\%$.

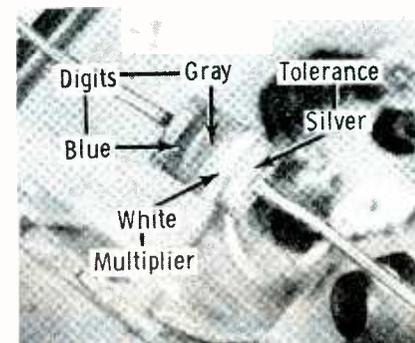
Capacity values for some of the units having less than four color bands are given in the chart. In this case, tolerance is assumed to be $\pm 20\%$.



CERAMIC TYPES ONLY

Color Marking	Digit	Multi	Value Tolerance	Under 10 MMF	Single-Color Temp. Coeff. PPM/ $^{\circ}$ C	Two-Color		Molded Miniature (Value)	Class or Characteristic (Molded Mica)	
						Temp. Coeff.				
						Sig. Fig.	Mult.			
Black	0	1	$\pm 20\%$	± 2.0 mmf	NP0	0.0	N1	—	A	
Brown	1	10	$\pm 1\%$	± 0.1 mmf	N033	—	N10 ¹	$+10^{\circ}$ C to $+85^{\circ}$ C	1.0 mmf	B
Red	2	10 ²	$\pm 2\%$	—	N075	1.0	N10 ²	$\pm 4.7\%$	2.2 mmf	C
Orange	3	10 ³	$\pm 3\%$	—	N150	1.5	N10 ³	$\pm 7.5\%$	3.3 mmf	D
Yellow	4	10 ⁴	GMV	—	N220	2.2	N10 ⁴	$\pm 10\%$	—	E
Green	5	10 ⁵	$\pm 5\%$	± 0.5 mmf	N330	3.3	P1	$\pm 15\%$	4.7 mmf	F (JAN)
Blue	6	10 ⁶	—	—	N470	4.7	P10 ¹	$\pm 25\%$	—	G (JAN)
Violet	7	—	—	—	N750	7.5	P10 ²	$+33\%$	—	—
Gray	8	10 ⁻²	—	$\pm .25$ mmf	P030	—	P10 ³	$+47\%$	—	I (RETMA)
White	9	10 ⁻¹	$\pm 10\%$	± 1.0 mmf	Gen. Appl.	—	P10 ⁴	$+75\%$	—	J (RETMA)
Gold	—	10 ⁻¹	$\pm 5\%$	—	—	—	—	-55° C to $+85^{\circ}$ C	—	—
Silver	—	10 ⁻²	$\pm 10\%$	—	Bypass & Coupl.	—	—	-30° C to $+85^{\circ}$ C	—	—
Grn-Gold	—	—	—	—	—	—	—	—	0.5 mmf	—
Blue-Gray Silver	—	—	—	—	—	—	—	—	0.68 mmf	—
Brn-Green	—	—	—	—	—	—	—	—	1.5 mmf	—

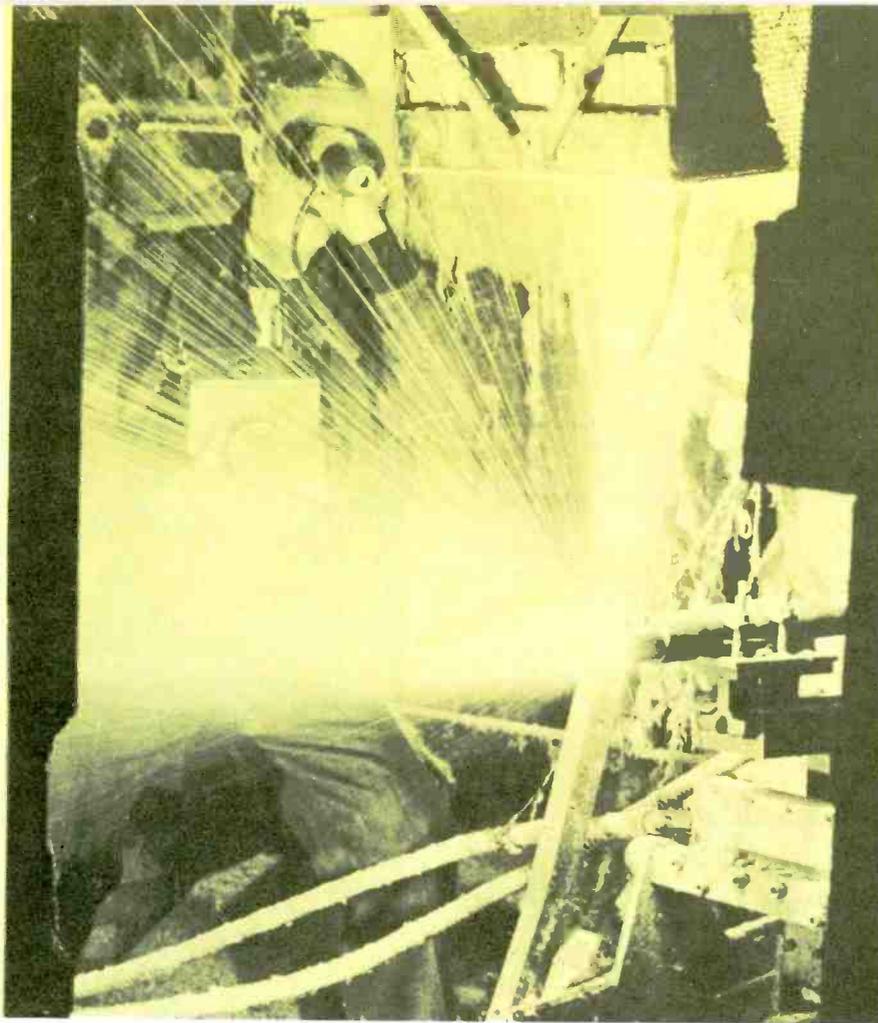

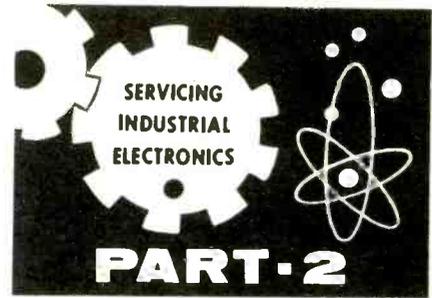

PART-2

by Melvin Whitmer

Man's first contact with the usefulness of heat probably came from cooking, which can be done successfully at many different temperatures with a minimum of control. The formation of bronze and steel was undoubtedly the next step forward in the use of heat. Although melting requires very high temperatures, the accuracy needed is satisfied by watching the color of the molten metal. Thus, man still did not need exact temperature indicators.

The conquest of metal forging was a great step forward, but it was the last step to be taken for many years. In the late 1700's Lavoisier, known to the world as the father of modern chemistry, began to drive heat into its final submission. His ideas may seem strange to us, but he used heat correctly in the separation of many chemicals. To Lavoisier, heat was a fluid, something tangible, but at the same time weightless, volumeless, and inseparable from physical bodies. He called this subtle fluid, "Caloric." Its properties should remind us of another medium theorized as responsible for the transportation of radio waves.

Heat has since been shown to be nothing more than a level of energy. Chemicals separate because heat adds enough energy for the molecules to overcome the bonds which hold the chemicals together. Liquids boil at different temperatures, and it is this property which makes their separation possible. A common example is the isolation of alcohol from water. Alcohol boils at 180° and water at 212°; thus distillation is possible only by careful control of the temperature. As the alcohol boils off, the vapor is passed through a condenser where it returns to a liquid state.

heat-sensing and temperature-controlling devices

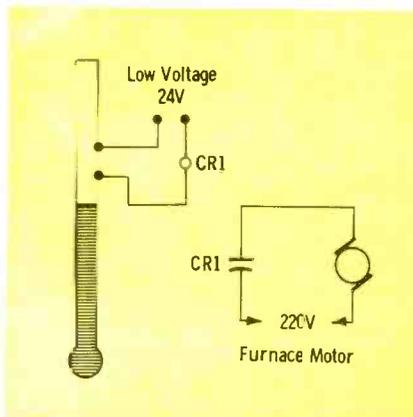


Fig. 1. Basic construction of a mercury temperature switch used to actuate a furnace control relay.

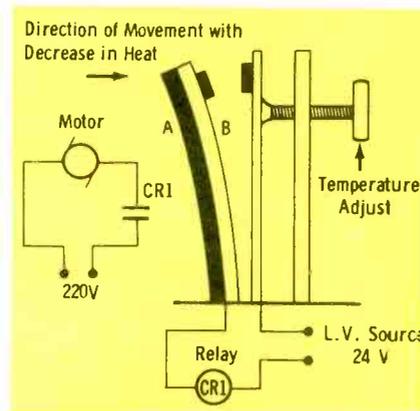


Fig. 2. The contacts of a bi-metal thermostat will open and close over a pre-determined temperature range of 2° to 3°F.

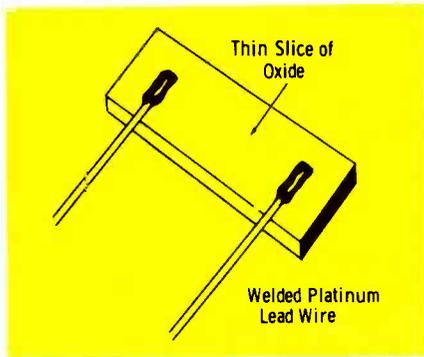



Fig. 3. Simple sketch of a thermistor.

As industrial processes required better control of heat, sometimes within only a few degrees, the ingenuity of man was called upon to devise electro-mechanical and electronic sensing units. Early devices could indicate the temperature on a calibrated dial, but could not actuate a control. The thermometer dates back to the 1500's, but its use as an electro-mechanical device is the product of the last 50 years.

Mercury is a good conductor of electricity, and it also responds readily to changes in temperature; therefore, it can be used as a simple control. The construction of the mercury temperature switch is shown in Figure 1. The bulb contains a reserve supply of mercury which extends into a narrow column with contacts placed permanently in the glass wall. This early switch was built for the control of only one temperature and could not be varied to suit the customer's needs.

The thermometer switch was replaced by a more flexible con-

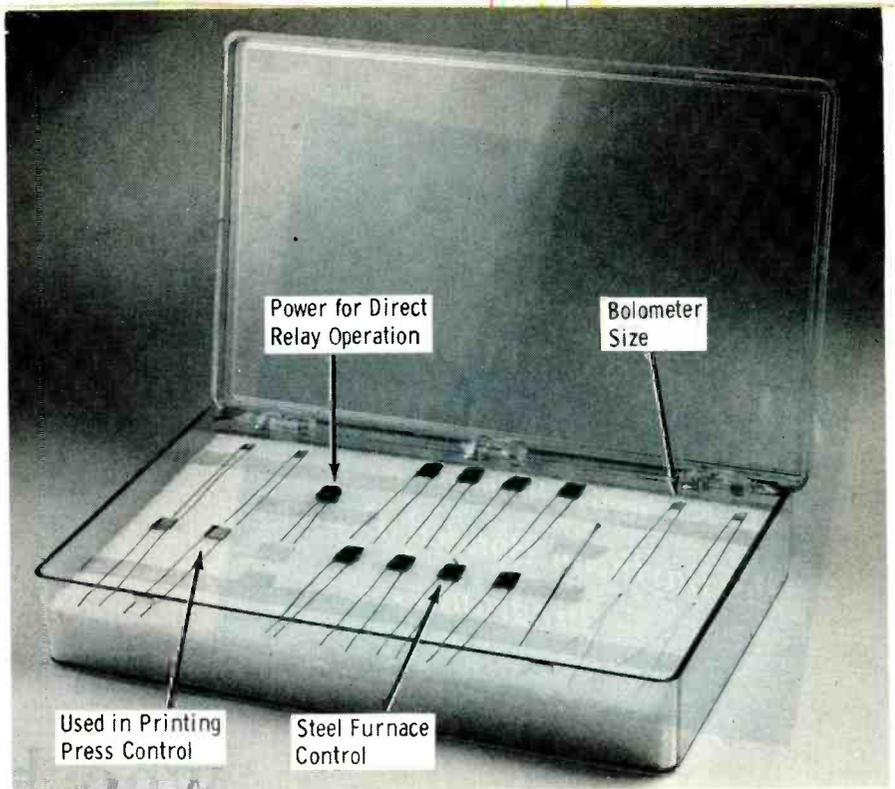Heat is detected through the infra-red window and the signal generated passed directly into a preamplifier. Notice the very short distance between senser and preamplifier.



Courtesy Glenite Thermistor Kits, Thermistor Division, Gulton Industries Inc.

A sample kit of thermistors for various applications. Several are painted black to increase their absorption characteristics.



Courtesy Servo Corporation of America

rol—the bi-metal thermostat. Figure 2 shows its construction. The bar labeled AB is constructed from two different metals, with B expanding more than A as temperature increases. When the bar AB cools, B will contract more than A and the bar will bend toward the contacts, which close when a predetermined temperature is reached. The temperature control is variable—with an upper limit of around 400°F—and will maintain a selected temperature within 2° to 3°F.

The thermistor is a relatively new device used to control temperatures ranging up to 1000°F and which has the ability to detect temperature differences of .05°F. Its construction is similar to a printed circuit resistor, but metal oxides rather than carbon compose the resistive elements. A sketch of the thermistor is shown in Figure 3. A thermistor can respond to the infrared radiation which is emitted by every mass. Even bodies which are considered cold, if they are above absolute zero, provide a characteristic radiation often called Black Body Radiation. The thermistor absorbs this energy and changes its resistance for each change in radiation intensity. The thermistor also emits energy itself, since it is a mass, and com-

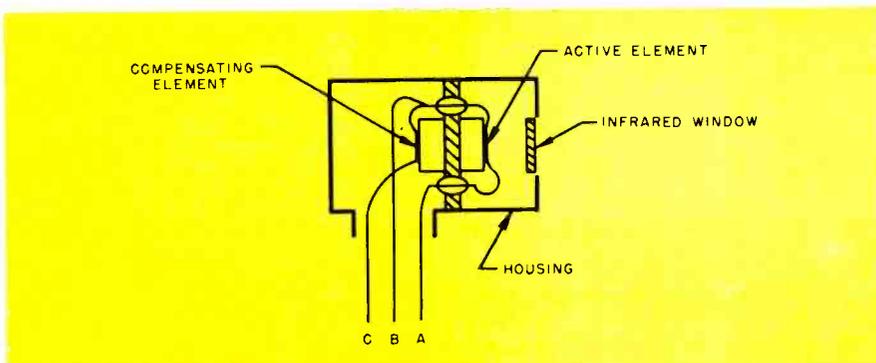


Fig. 4. Internal makeup of a bolometer.

• Please turn to page 75

A wonderful offer
 from the
**RAYTHEON RECEIVING
 TUBE DISTRIBUTORS**
 who sponsor
 the Raytheon Bonded Dealer
 Program . . .

at no added cost . . .

GROUP
 for Raytheon
 who by preference

Now, Registered Bonded Dealers can gain personal security for themselves and their families — automatically increase their life insurance coverage, through their regular purchases of Raytheon Receiving Tubes. The amount of coverage is determined by the quantity of Receiving Tubes the dealer buys. The New England Mutual Life Insurance Company has created a Group Life Insurance Plan for Raytheon Bonded Electronic Technicians — a plan offered exclusively by Raytheon Distributors who sponsor the Bonded Dealer Program. Any such Distributor who meets the necessary requirements for setting up a Group Life Insurance Plan for Bonded Dealers may give them this valuable protection without the necessity of a physical examination. Check with your Raytheon Sponsoring Distributor and see if he has it available to you.

If you're not at present a Raytheon Bonded Dealer, better see your Sponsoring Distributor as to whether you can qualify. You'll find being a Raytheon Bonded Dealer a real asset to you. You'll find using Raytheon quality receiving tubes is a big help, too.

**Administered and underwritten by New England Mutual Life Insurance Company*




RAYTHEON MANUFACTURING COMPANY			
Receiving and Cathode Ray Tube Operations			
NEWTON 58, MASS. 55 Chapel Street	CHICAGO, ILL. 9501 Grand Ave. (Franklin Park)	ATLANTA 6, GA. 1150 Zonolite Rd. N.E.	LOS ANGELES 7, CALIF. 2419 So. Grand Ave.
Raytheon makes all these	Receiving and Picture Tubes, Reliable Subminiature and Miniature Tubes, Semiconductor Diodes and Transistors, Nucleonic Tubes, Microwave Tubes.		

LIFE INSURANCE*

Bonded Electronic Technicians

use RAYTHEON RECEIVING TUBES



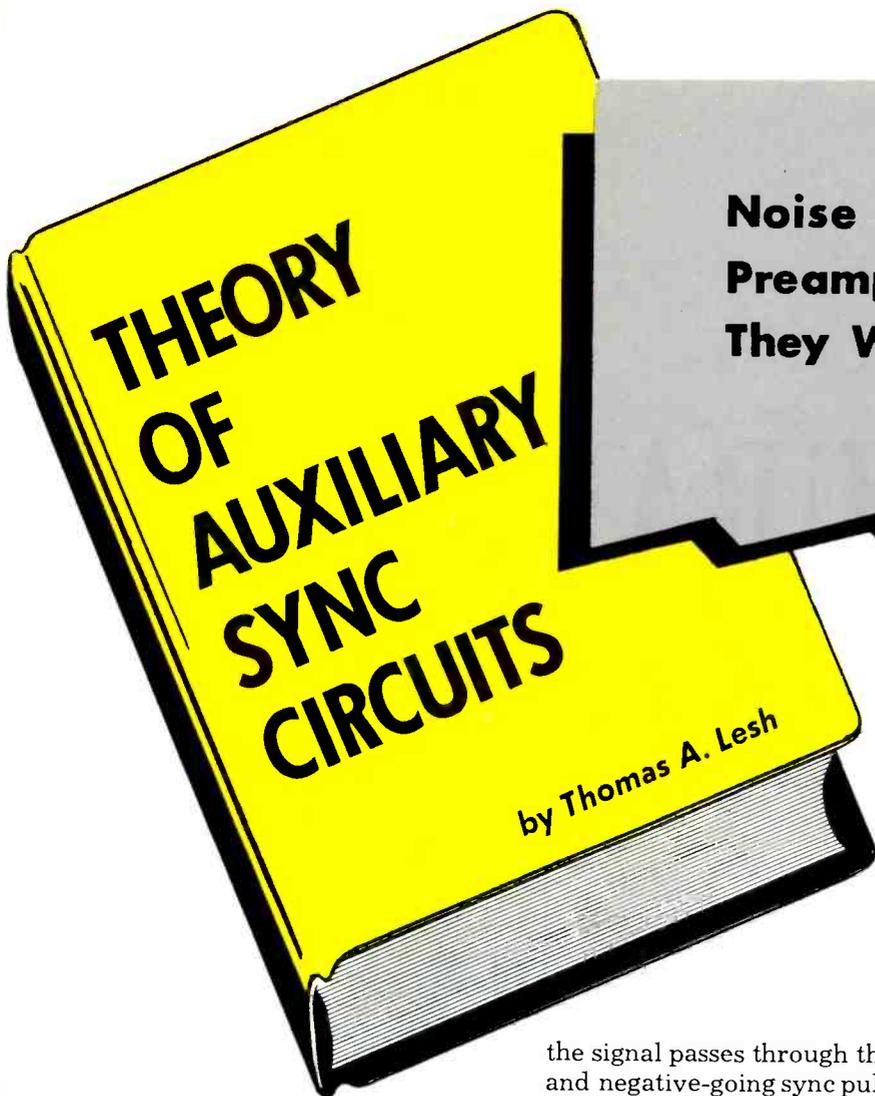

Noise Limiters and Sync Preamps and How They Work

TV sets of just a few years ago often included what might be called "auxiliary" sync stages—separate noise limiter tubes, sync preamplifiers, etc. Circuits of this type have not been receiving much attention lately, being victims of the trend toward simplified and standardized TV circuitry. Nevertheless, a great many sets still in service have unusual sync circuits, and these can slow you down during troubleshooting if you're a little rusty on their theory of operation. Thus, here is a short refresher course on sync circuits which have sometimes been used to supplement the standard dual-triode or pentagrid arrangements commonly used today.

Fig. 1 is an example of the familiar dual-triode circuit, in which the sync-processing function has been pretty well reduced to essentials. The first stage is a sync separator that receives at its grid a signal composed of video information and positive sync pulses. The video is stripped off as

the signal passes through the tube, and negative-going sync pulses are delivered at the plate. The second stage is an amplifier that "cleans up" the pulses and boosts them to sufficient height for application to the horizontal and vertical sweep circuits.

The pulses at the grid of this second stage are negative and normally drive the tube into cutoff. The resulting "sync clipping" action trims the pulses to a constant peak level and thus removes any amplitude irregularities that might have passed through the sync separator. In some cases, the sync amplifier also serves as a phase splitter, providing pulses of two polarities required by some types of horizontal phase detectors.

The operation of the dual-triode system in fringe areas is sometimes disturbed by strong noise pulses. If these pass through the sync stages, they can falsely trigger the sweep oscillators. In addition, they can interfere with the normal grid-leak biasing of the sync separator by placing an ex-

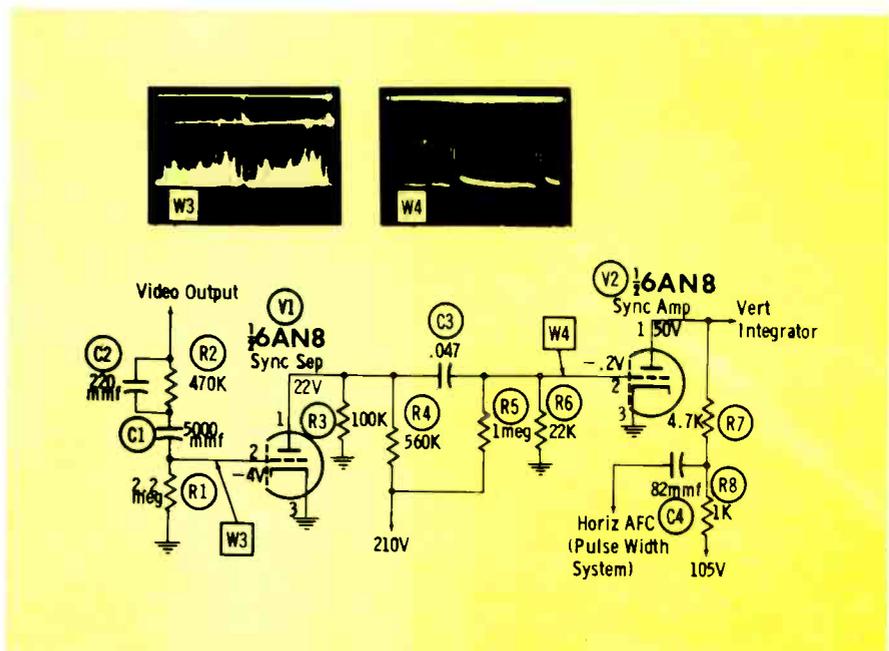


Fig. 1. Typical dual-triode sync section—Truetone Model 2D2423A.

cessive charge on the grid capacitor (C1 in Fig. 1). When considerable noise is present, the charges induced by the noise pulses drive the grid voltage excessively negative. As a result, the sync pulses at the output of the separator are reduced in amplitude and are less effective in controlling the sweep oscillators.

This situation can be remedied by cancelling out the noise pulses as they reach the sync separator. A circuit for this purpose is included in some current model TV sets, usually in the form of a pentagrid tube that combines the functions of both the separator and canceller. The main input, applied to the No. 3 grid, is a composite video signal (sync positive) from which a negative sync output is developed in the same manner as in the triode-type separator. The No. 1 grid of the pentagrid tube receives a secondary input signal—composite video of low amplitude and inverse polarity taken from the video detector load circuit. The tube is cut off by any strong noise pulse that appears in this secondary signal.

An occasional sync pulse is removed from the output, but the loss of a pulse here and there has much less of an effect on synchronization than the uncanceled noise pulses would have. The pentagrid circuit has been described from time to time in the pages of PF REPORTER; the most recent discussion was in "Servicing New Designs," April, 1957.

Noise Inverter

A forerunner of the pentagrid circuit is the separate noise-inverter stage still found in many receivers in the field. Its purpose is the same as that of the secondary circuit in the pentagrid tube—to introduce pulses that will cancel the noise pulses entering the separator. Instead of cutting off the separator tube, however, the noise inverter simply feeds a negative spike of voltage to the separator grid to counterbalance each positive noise spike that appears in the main input signal at this grid. If no high-amplitude noise is present in the video signal, the noise inverter produces no output and therefore does not affect the sync separator.

A separate triode section used as a noise inverter is shown in Fig. 2. Notice that the plate of the inverter V13A is connected to the input circuit of the sync separator. Since the cathode resistor R34 serves also as part of the video detector load, the inverter is cathode-driven by a sync-negative, composite video signal of low amplitude. The grid of V13A receives no signal, but obtains a negative bias voltage from the grid circuit of the horizontal output tube.

The "Noise Cancel" control is used to establish a grid voltage which will keep the tube cut off at all times except when a noise spike in the input signal extends beyond sync-tip level. Such a spike produces a pulse of cathode voltage which is negative enough to drive V13A into conduction. The resulting short burst of plate current develops a negative pulse of output voltage, which nullifies the positive noise pulse that simultaneously reaches the sync separator grid circuit.

The following procedure is used in adjusting the "Noise Cancel" control: Tune in the strongest signal available, and then turn the control to the maximum counter-

clockwise position, thereby applying maximum bias to the grid of V13A. Next, advance the control setting until pulling or sync loss is observed, indicating that V13A is conducting on normal sync pulses and reducing sync amplitude at the separator grid. Finally, back off the control until the picture returns to a stabilized condition.

Several varieties of noise inverter and limiter circuits have been employed from time to time. Instead of taking the inverter input from the video detector load, some manufacturers have tapped off a small portion of the video amplifier output signal (sync positive) and applied it to the grid of a triode inverter, which is biased so that the positive noise spikes on the grid drive it into conduction. Another variation is to connect a diode across the sync separator input so that noise voltages above a preset level will be shunted to ground by conduction of the diode.

Intermediate Sync Amplifier

Fig. 2 also illustrates another type of special sync circuit, an intermediate stage between sync

• Please turn to page 77

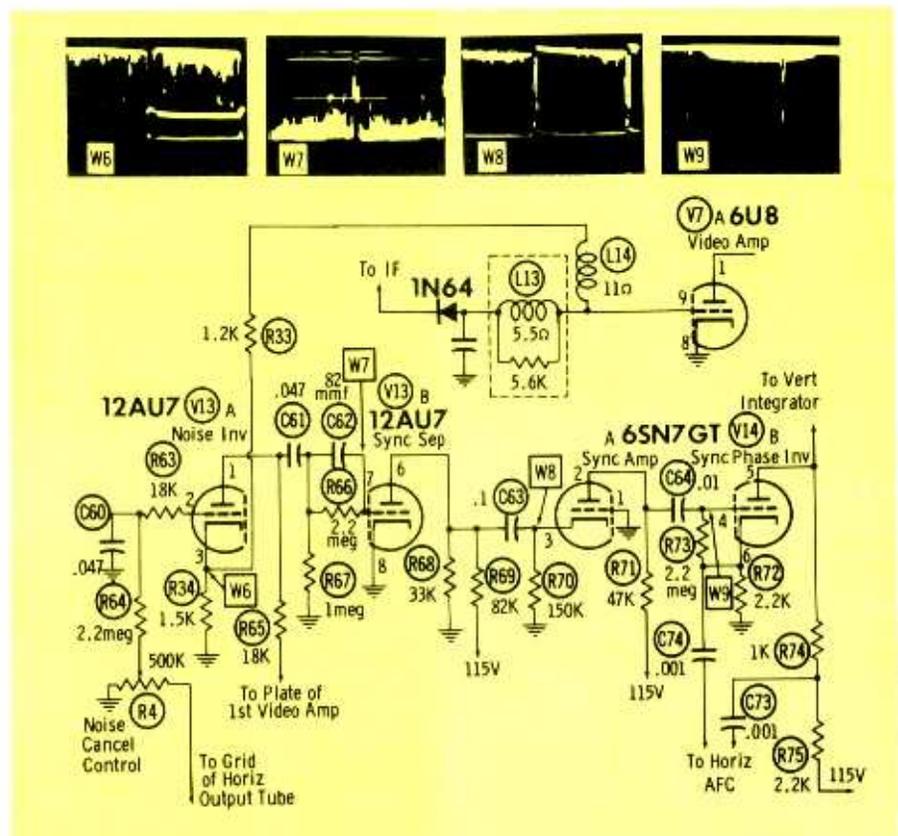


Fig. 2. Sync section plus triode noise inverter—Stromberg-Carlson Model 621.

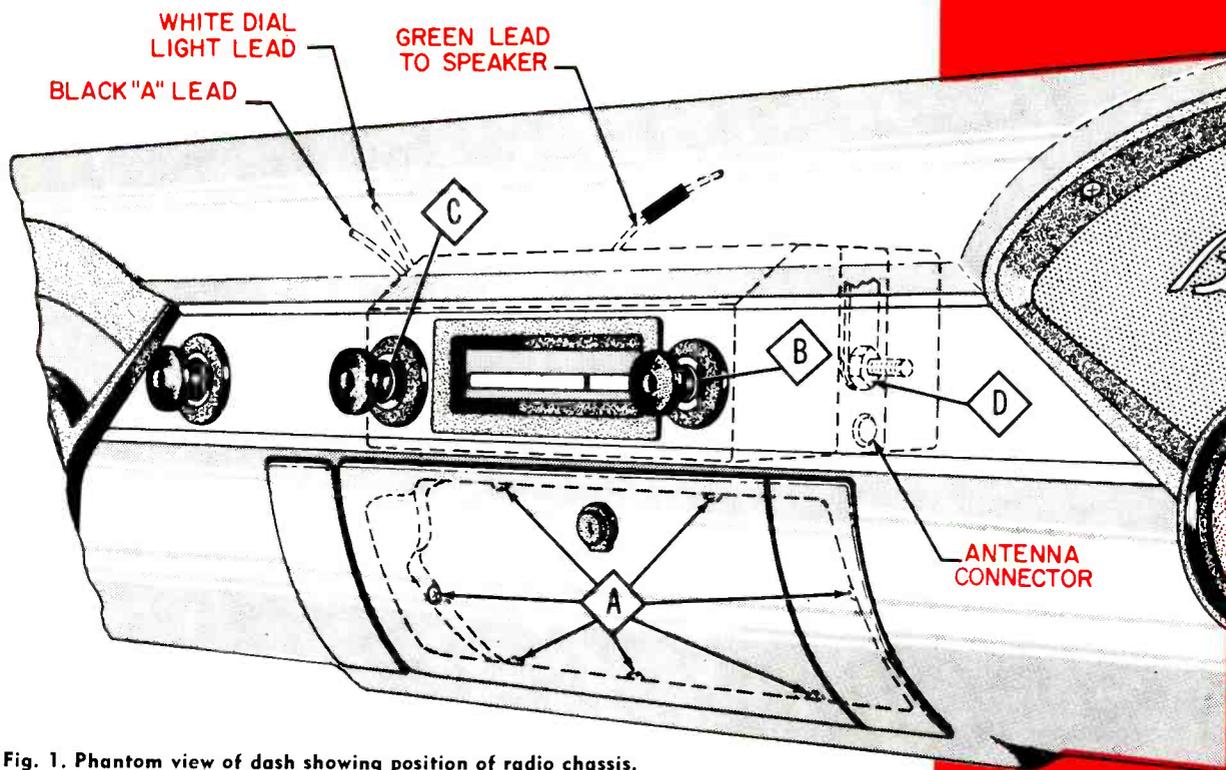


Fig. 1. Phantom view of dash showing position of radio chassis.

Removing an auto radio is basically more a physical task than anything else; however, it is one which can require some time and effort due to the awkward position in which the technician has to place himself in order to reach the screws, nuts and bolts under the dash panel. A knowledge of the correct procedure and the exact tools for removing radios in specific makes of cars will help to reduce the time and effort involved in these tasks.

The following is the procedure for removing radios in all 1955 Chevrolets except the Corvette. A list of the tools that are required is also included.

Removal Procedure

Main Chassis (Refer to Fig. 1.)

STEP 1

Take out 7 Phillips-head screws (A), using stubby-type Phillips screwdriver, and remove glove compartment.

STEP 2

Remove rubber bumper on end

of glove compartment door guide and take off door.

STEP 3

Remove 4 push-on knobs and two felt washers.

STEP 4

Remove the $\frac{1}{16}$ " lock nut (B) from the selector shaft using an $\frac{1}{16}$ " box-end wrench, and the $\frac{5}{8}$ " lock nut (C) from the volume control shaft using a $\frac{5}{8}$ " box-end wrench.

STEP 5

Remove the volume and selector escutcheons from the shafts.

STEP 6

Pull out the antenna lead from the right side of radio chassis.

STEP 7A (Applies only to pushbutton and signal-seeking models.)

Disconnect the power-supply plug from the left side of the power supply chassis and the black "A" lead at the snap connector, located between the main chassis and the power-supply chassis.

STEP 7B (Applies only to manual tuning models.)

Disconnect the green lead to the speaker. A snap connector is pro-

Removing Radio from 1955 Chevrolet

vided in the lead for this purpose. NOTE: In cars equipped with a rear-seat speaker, this lead is connected to the speaker control unit.

STEP 8

Remove the white dial-light lead from the upper left-hand terminal on the fuse block located on the firewall to the left of the steering column. Disconnect the black "A" lead from the terminal labeled "RADIO" on the fuse block.

EDITOR'S NOTE: This article is based on material from the book, "Instructions for 1955 Auto Radio Removal," published by Howard W. Sams & Co. Of all the makes of cars covered in the book, the 1955 Chevrolet was selected because of its popularity.

STEP 9

Remove the $\frac{7}{16}$ " nut (D) from the right side of chassis using a $\frac{7}{16}$ " box-end wrench. Support chassis with hand while removing nut.

STEP 10

Pull chassis back toward firewall until control shafts clear the dash, then rotate chassis until shafts are facing upward. Remove chassis as shown in Fig. 2.

Power Supply and Speaker Unit (Refer to Fig. 3.)

The power supply, audio output stage and speaker are combined into one unit and located to the right of the radio chassis on push-button and signal-seeking models. Only the speaker is mounted separately in manual tuning models. The removal procedure is the same for both types.

STEP 11 (Applies only if rear-seat speaker is employed.)

Disconnect the lead (or leads) to the rear-seat speaker control unit.

STEP 12

Detach the antenna lead from the clip attached to the right-hand mounting bolt (E). Remove the two Phillips-head bolts (E) from the bottom of dash using a $\frac{3}{8}$ " box-end wrench to hold the nuts and a Phillips screwdriver to loosen the bolts. Take off the antenna clip on the right side.

STEP 13

Steady chassis with one hand and remove two Phillips-head screws (F) from the top of the speaker-grill bezel.

STEP 14

Remove the power supply chassis (or speaker) by lifting the chassis up and back, then move sideways to the position which was occupied by the glove compartment and lower the unit toward the floorboard.

Tools Required

- 2—Phillips screwdrivers, 1 stubby type and 1 regular length.
- 1— $\frac{11}{16}$ " box-end wrench.
- 1— $\frac{5}{8}$ " box-end wrench.
- 1— $\frac{3}{8}$ " box-end wrench.

October, 1957 · PF REPORTER

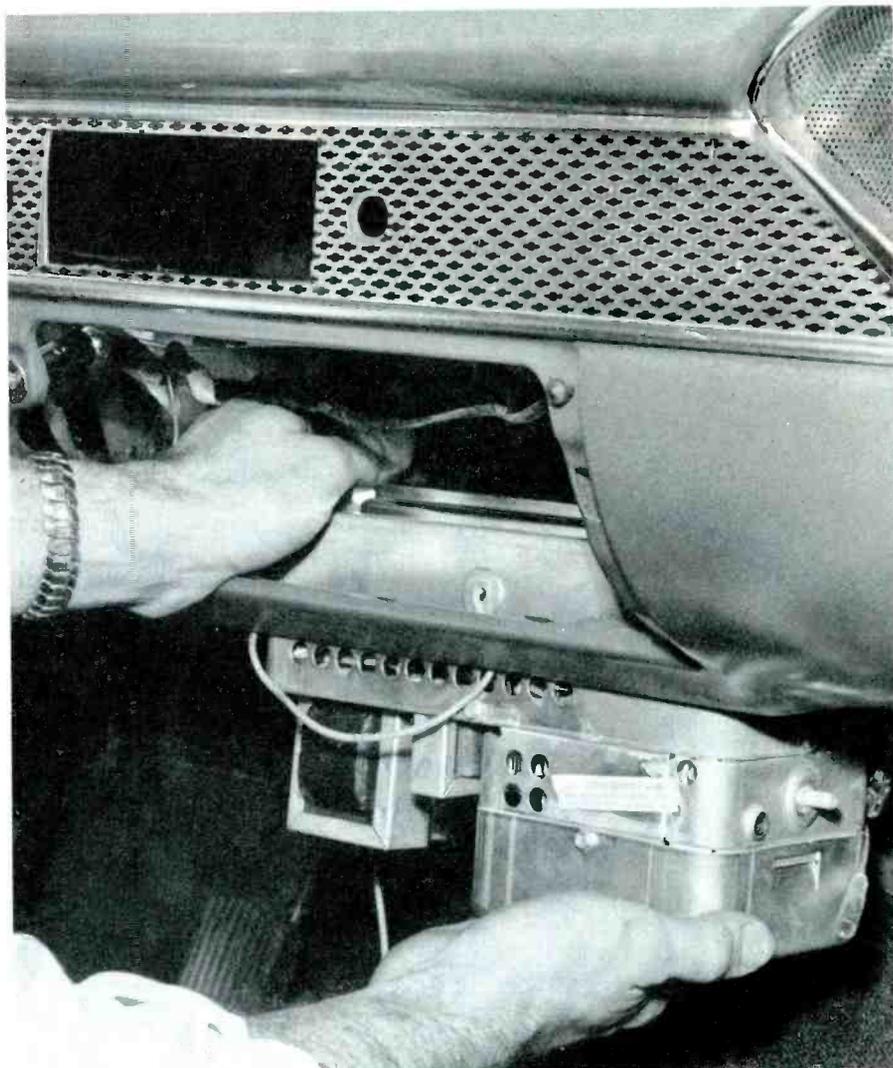


Fig. 2. Removing chassis.

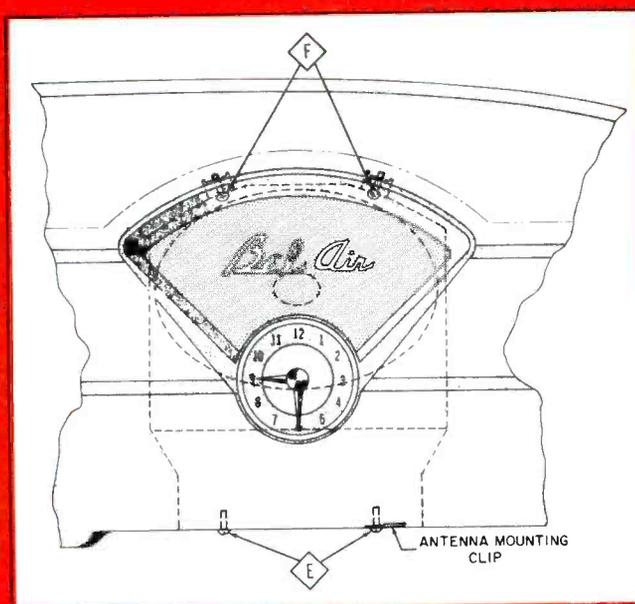


Fig. 3. Phantom view showing position of speaker unit.

servicing new designs

by Thomas A. Lesh

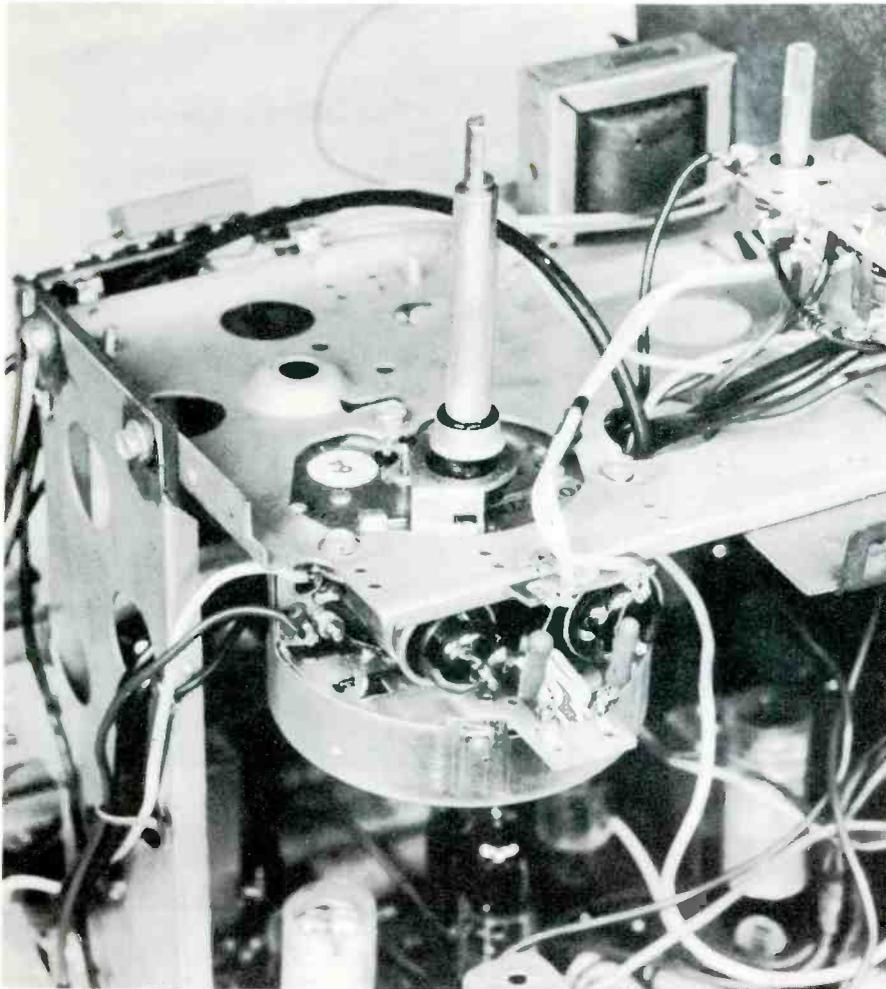


Fig. 1. New compact version of Standard Coil tuner in Airline Model GTM4031A.

Smallest TV Tuner

What appears to be an oversized potentiometer mounted on the upper deck of the TV chassis in Fig. 1 is actually a VHF tuner in Fig. 1 is actually a VHF tuner—one that sets a new record for compactness. This unit is a new version of the Standard Coil Neutrode tuner, electrically identical to previous models (except for some changes in component values) but radically changed in physical construction, in that it conforms to the compact layout requirements of the newest TV sets.

How has a complete television tuner been squeezed into such a

small package? Let's disassemble the unit and find out. The tuner can be removed from the TV chassis by unsoldering a half-dozen connections and taking out three $\frac{1}{4}$ " hex-head screws. When the cover is slipped off, the bottom view of the tuner is as shown in Fig. 2. Fastened to the underside of the tuner chassis is a movable wheel which serves as a mounting board for all the tuning coils. Oscillator, mixer, and RF coils for individual channels are wound on coil forms which are arranged like spokes on the wheel, and an antenna coil for each channel is separately mounted at a considerable distance from the

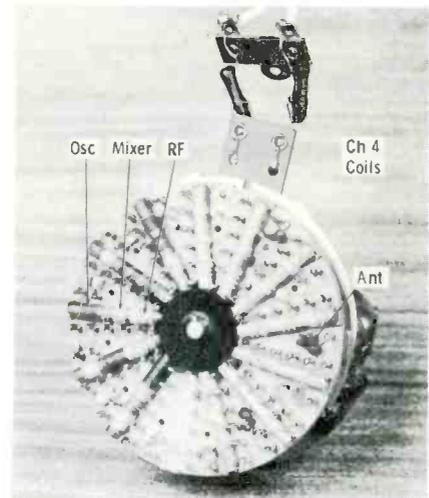


Fig. 2. Bottom view of new tuner showing tuner coils mounted on wheel.


other coils associated with that channel. (Note the positions of the Ch. 4 coils in Fig. 2.) This arrangement permits an extremely compact design while still preserving the necessary isolation between the antenna input circuit and the other tuned circuits.

Oscillator adjustment slugs are located inside the coil forms and can be reached through a hole in the tuner cover. In the Airline set shown in Fig. 1, adjustments are made from the right side as viewed from the rear of the receiver.

In Fig. 3, the wheel is shown removed from the tuner chassis. Note that contact buttons and springs similar to those on turret tuners are employed to make connections between the two parts. The tuning shaft, which is fastened to the wheel, is thrust through a hole in the center of the chassis and locked in place so that the buttons will be held in contact with the springs. The wheel is guided into the correct on-channel positions by a spring-loaded detent rod which rides on the rim of a detent gear fastened to the wheel.

Details of the procedure for removing the wheel from the tuner are as follows: First, a C-shaped retainer ring is pried out of a groove near the tip of the tuning shaft (see Fig. 4), and then one screw on the top wall of the tuner chassis is taken out so that the fine tuning shaft and its cam (Fig. 5) can be slipped off the main shaft. The next operation is to free the main shaft by removing

PF REPORTER · October, 1957

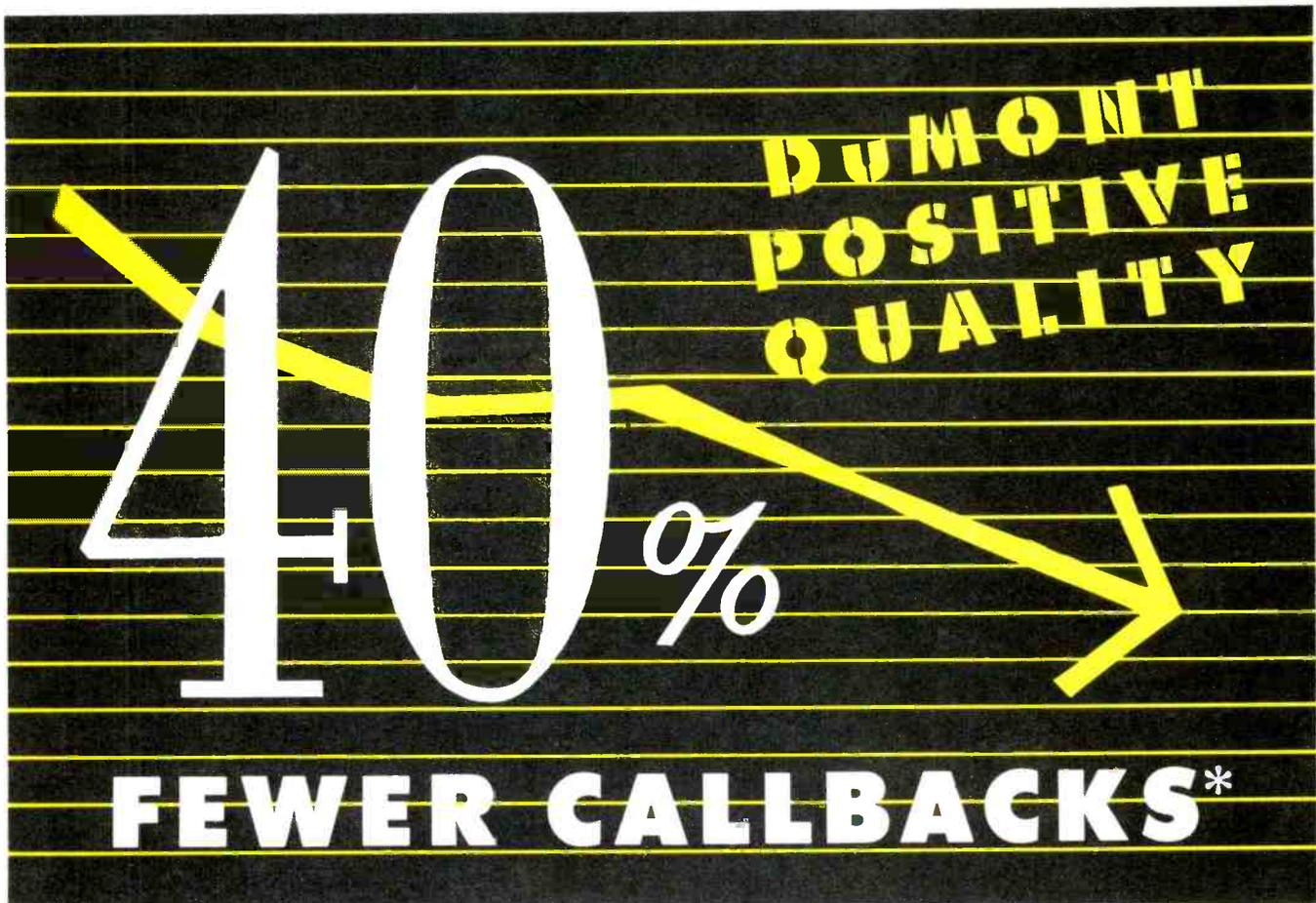


A positive fact about
Du Mont Positive Quality . . .

Du Mont Picture Tubes cut callbacks due to
tube failure by 40%. Consider what
this means to you — fewer callbacks,
greater profits.

Ask your distributor about
Du Mont Positive Quality Picture
Tubes and Electronic Tubes.

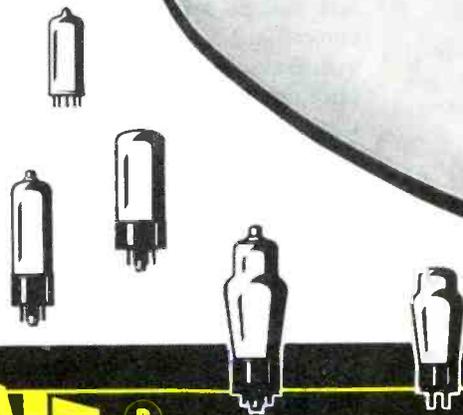- Send name and address for
your free copy of the Du Mont
Replacement Tube Chart.



*Based on actual
engineering figures.


DUMONT [®]

Television Tube Division

Allen B. Du Mont Laboratories, Inc., Clifton, N. J.

AMAZING

NEW

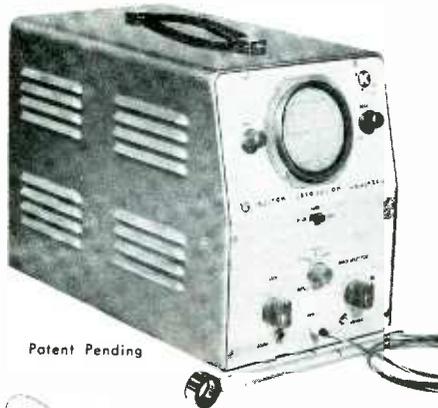

SIMPLIFIES
WAVE FORM ANALYSIS
SPEEDS
TV TROUBLE SHOOTING

- ✓ This revolutionary test equipment so simplifies wave form analysis that every TV service man can use it to save time and make more money.
- ✓ Follows composite video from antenna to CRT. Traces sound from sound IF's to speaker without any physical connection.
- ✓ Displays sweep and sync information through progressive stages . . . every tube becomes a test point for top-side servicing.
- ✓ Isolates defective circuit by displaying wave forms as they appear in each stage. Electrostatic pick-up minimizes loading.
- ✓ Light-weight and portable, may be taken on every call, to speed servicing, reduce call-backs and build customer confidence.

For complete information and the name of your nearest distributor, write today.

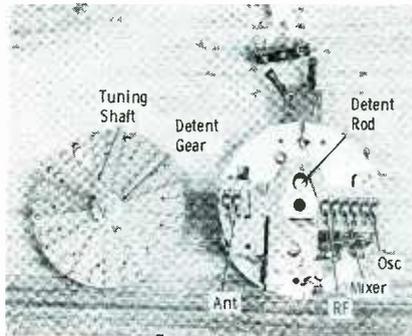


Fig. 3. Wheel removed to show contacts.

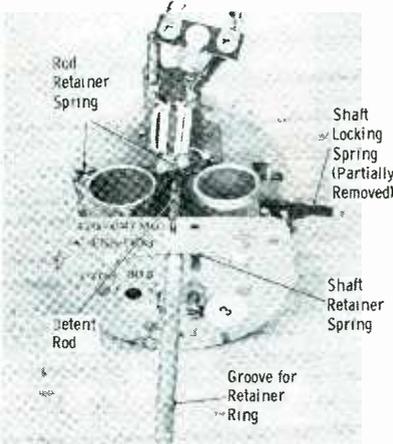


Fig. 4. Components which must be loosened or removed to free the coil wheel.

the retainer and locking springs that fasten it to the chassis. The locking spring is disengaged by grasping the tab at its outer end with pliers and pulling outward.

To simplify removal of the wheel and tuning shaft assembly, the detent mechanism should be loosened in order to relieve the pressure on the detent gear. This is easily done by freeing one end of the rod retainer spring—the left end as seen in Fig. 4 is most convenient. Normally, it is not necessary to disassemble the detent mechanism any further than this.

Inside the tuner chassis, the

main shaft passes through the cam follower and its spring, both of which are shown in Fig. 5. One ear on the follower projects through the top wall of the tuner and is held against the cam by spring tension. When the cam is turned by the fine tuning shaft, the follower is driven back and forth, causing the second ear on the follower to open and close the movable plate of a book-type fine tuning capacitor. Whenever a coil wheel is removed from one of these tuners, the technician should make sure that the follower and spring are correctly positioned before he reinserts the tuning shaft into the chassis.

The most important feature of this new tuner is that the wheel, which lies flat against the end of the chassis, has taken the place of the bulky turret used in previous models. All the waste space formerly occupied by the hollow interior of the turret has therefore been eliminated.

Receiver Design Minimizes Tube Failures

Several new design features aimed at lengthening the life of receiving tubes are included in the transformer-powered TS-544 chassis used in some 1958-model Motorola TV sets.

For example, there is the "Tube Sentry," a small component which is simply a Global resistor fastened to a thermal switch. The resistor is in series with one primary lead of the power transformer, and the switch is connected in the DC output lead of the 5U4GB rectifier tube. Since the switch is open when cold, the B+ circuit is not completed until the resistor heats up sufficiently to close the switch. This action does not take place until approxi-

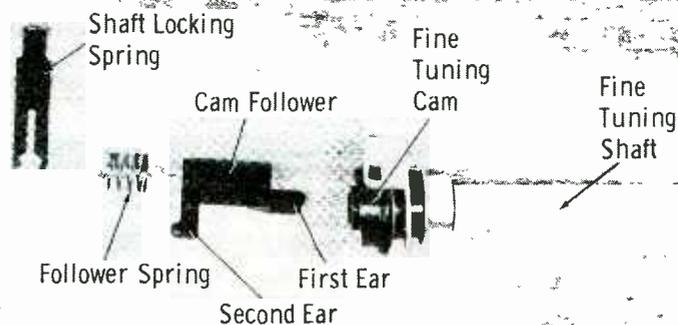


Fig. 5. These components fit around the tuning shaft. (C-ring not shown.)

**Make hay
while the
Moon shines...**



... stock and sell

**RCA
BATTERIES!**

Modern Americans play outdoors, day and night, twelve months a year. And, wherever they go, hayrides, football games, weenie roasts, ski lodges — they take their portable radios along!

Make sure your supply of RCA Batteries is adequate to meet public demand this fall!



RADIO CORPORATION of AMERICA

® COMPONENTS DIVISION

CAMDEN, N.J.



RCA BATTERIES...THE BRAND THAT COMMANDS PUBLIC DEMAND!

it's
new

The **TRC**
triple-duty microphone

by
American



Actual size of new TRC microphone



it's versatile...
lightweight...
low cost, too!

Elgin's new TRC dynamic microphone offers faithful audio reproduction in the 80-8500 cps range, yet lists from \$11.50. It is designed for use with tape recorders... yet has the versatility to perform ideally at meetings and assemblies, wherever p.a. systems are used. The TRC is less than five inches long, weighs only nine ounces, has a polished, chromeplated case. It is omnidirectional and picks up voices within a radius of ten feet under average conditions.

The TRC is also available in crystal and ceramic types.

Get the facts on this new addition to Elgin's complete line of "American" microphones. Write today for specifications and complete descriptive literature.

ELECTRONICS DIVISION

ELGIN NATIONAL WATCH COMPANY
107 National Street, Elgin, Illinois

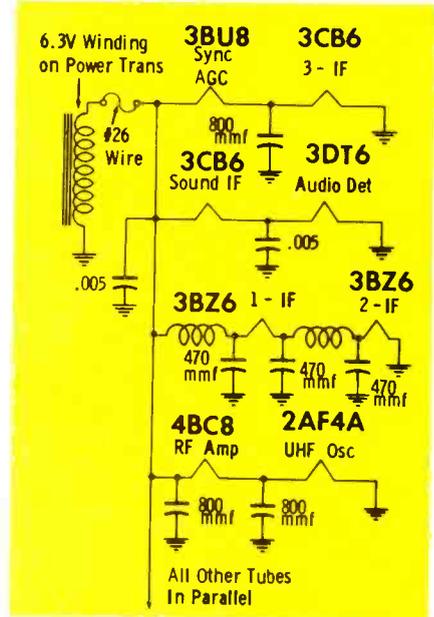


Fig. 6. Series-parallel hookup across 6.3-volt filament supply in Motorola TS-544.

mately 35 seconds after the receiver is first turned on. All tube filaments are then allowed to warm up thoroughly, permitting a cloud of electrons to build up around the heated cathode and thereby protecting the emitting surface against the initial shock which would result when plate voltage is applied.


Since the TS-544 chassis has a power transformer, it is surprising to find several 600-ma series-string tubes such as the 3CB6 in this set. Several pairs of these tubes are wired across the 6.3-volt filament winding of the power transformer in the manner shown in Fig. 6. This type of hookup is used in all-channel models; for VHF-only sets, a 6BC8 is substituted for the 4BC8 and 2AF4A in series.

Series-string tubes were used in this unconventional way for one good reason: Field experience has revealed a noticeably lower failure rate for the reduced-voltage, 600-ma tubes than for the 6.3-volt versions of the same types.

In another effort to increase tube life, a 3A3 has been employed as a high-voltage rectifier in place of a 1B3GT. The 3A3, a heater-cathode tube developed for color TV, is expected to have a long service life in the TS-544 high-voltage circuit, which develops a nominal 18.5 kv for the anode of a short-neck 90° picture tube.

ANODIZED

...it lasts forever

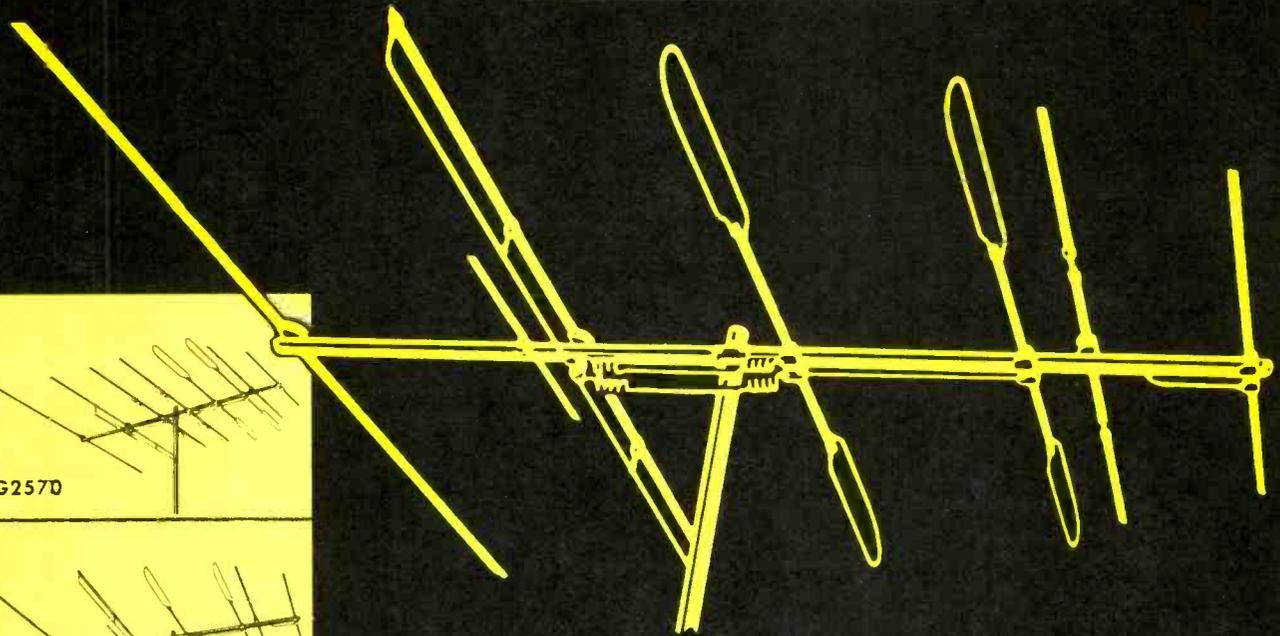

G257D

G2560

G2550

G254J

The new magnificent

GOLDEN

Topliner

Trade-mark

Completely anodized to lock out corrosive fumes and weather elements . . .

Designed to outperform any antenna, dollar-for-dollar, or size-for-size . . .

Designed to make your installation look better . . .

This is the new Taco Golden Topliner, the antenna you've been waiting for . . .

Install a Golden Topliner. You'll marvel at its performance.



TECHNICAL APPLIANCE CORPORATION
SHERBURNE, N. Y.

In Canada: Hackbusch Electronics, Ltd., Toronto 4, Ont.
U.S. PAT. 2799018

Notes On

TEST EQUIPMENT

Latest Information on Application,
Maintenance and Adaptability
of Service Instruments

by Leslie D. Deane

Intermittent Troubles?

The instrument shown in operation in Fig. 1 is helpful in solving those stubborn intermittent problems we all dread but so often encounter in the servicing field. Manufactured by Winston Electronics, Inc. of Philadelphia, the unit is identified as the Win-Tronix Model 828 Intermittent Condition Analyzer.

Using various probe techniques, the Analyzer operates on a signal monitoring principle, and is especially designed to isolate mechanical or electrical intermittents in a minimum amount of time.

Specification features are:

1. Power Requirements—105 to 125 volts AC, 50/60 cps, power consumption 20 watts.
2. RF output—television signal frequency for channel 2 adjust-

able for channels 3 and 4 or radio signal frequencies of 545 and 1090 kc.

3. RF Modulation—TV sound carrier of 4.5 mc and audio modulation of 400 cycles.
4. Signal Monitoring Provisions—audio output from built-in dynamic speaker or phone jack; attenuator control and gain switch provided on front panel.
5. General—built-in power outlets provide Medium, 10-volt line boost and High, 20-volt line boost; intermittent probe and attachments supplied with unit.

When I examined this outfit in the service lab the other day, I'm happy to say there were no intermittent TV chassis laying around. However, to properly acquaint myself with the instrument and its operation, I decided to introduce or simulate such a condition in a test receiver.

The usefulness of such an instrument naturally depends upon how it is employed and the interpretation of results, so my first task was to read the instruction manual carefully and completely. In doing so, I found several suggested steps that the technician might take to prepare the ailing set for intermittent testing. First, eliminate all obvious sources of trouble by giving the chassis wiring a complete visual inspection. Next, to duplicate the temperature and voltage conditions which exist in the customer's home, the heat from a 250-watt infrared or a 200-watt incandescent lamp should be directed at the under-chassis components. This will raise the ambient temperature, simulating the condition which exists when the chassis is in its cabinet. In order to force the intermittent to appear, it may also be advisable to increase the line voltage slightly. For this express purpose, the Analyzer has two AC outlets conveniently located on the front panel, one for increasing line voltage by 20 volts and the other by 10.

Returning to my little experiment, I introduced a poor contact in the sync separator circuit of the test receiver. I noticed that the slightest vibration would now throw both vertical and horizontal sweep oscillators off frequency. This type of symptom, according to the instruction manual, indi-

PF REPORTER · October, 1957


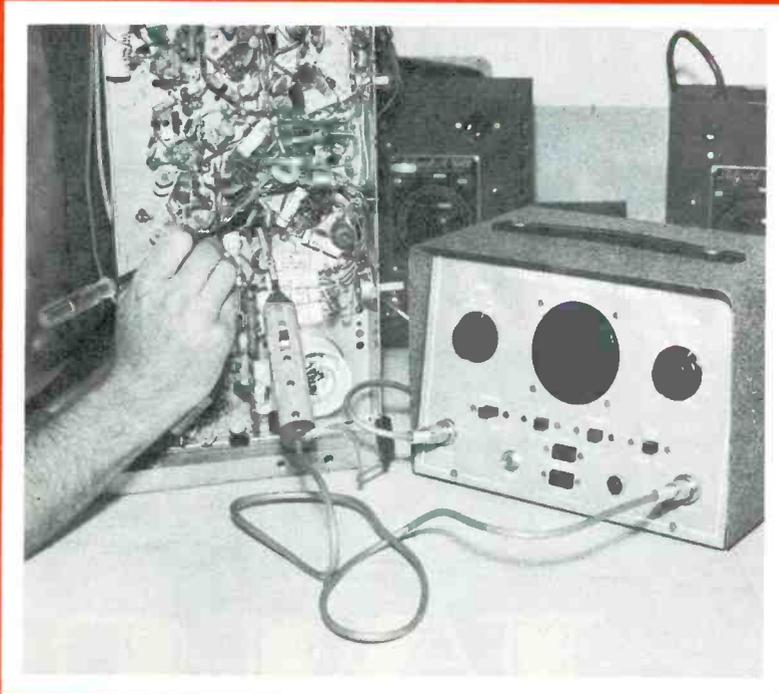


Fig. 1. New Win-Tronix Analyzer aids in quickly isolating intermittents.

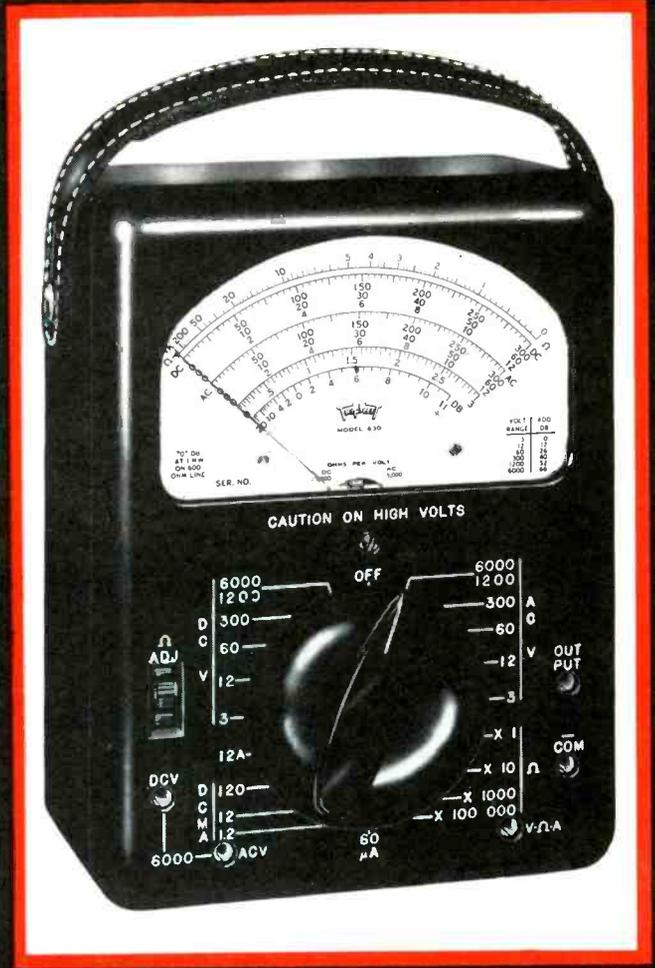

1,000,000,000

proofs a day...

that a VOM is electronics' most basic Test Instrument
Yes, over 1,000,000,000 measurements are made every day with Volt-Ohm-Milliammeters

and triplett model 630 leads all vom's

in design, quality, performance, operating simplicity, and value per dollar. The leader at only \$44.50
At leading electronic parts distributors everywhere.

TRIPLETT Model 630 VOM—the proof of 53 years' experience in test instruments.



631



630-NA



630-A



310



630-T



666-HH



625-NA



666-R

cates a mechanical intermittent.

Following instructions for this condition, I connected the RF output cable of the Analyzer to the antenna terminals of the receiver—thus feeding in a channel 2 RF signal modulated by both 4.5 mc and 400 cycles. I then connected the cable from the intermittent probe to the *tracer* in jack on the front panel of the instrument. Setting the Analyzer's switches and controls as recommended, I flipped the probe switch to the video/audio position and touched the probe tip to the sync

output circuit. Monitoring the 400-cycle signal with the instrument's speaker while probing components and wiring, I immediately detected the faulty condition.

Had the intermittent condition been of an electrical nature, any popping or abrupt change in signal level could have been traced from the output back through the circuit by placing the probe at different points. As the probe is moved past the defective circuit, the intermittent noise should cease to be heard.

If connecting the intermittent

probe directly to the suspected circuit temporarily causes the trouble to disappear, then it may be necessary to employ an indirect method of coupling. The two probe attachments pictured in Fig. 2 will help solve this problem. The small ring type, shown attached to the probe, is called an Electro-Wand. This unit is designed to slip over miniature tubes in various sections of the receiver, pick up intermittent noises by capacitive coupling, and is also handy for signal tracing without removing the chassis from its cabinet.

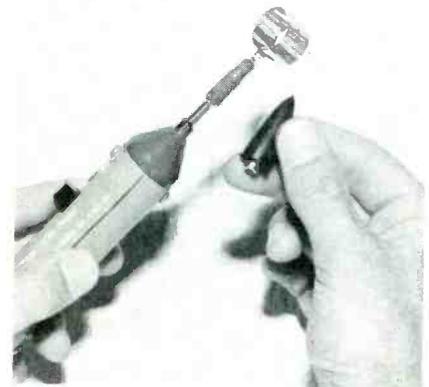


Fig. 2. Attachments for Win-Tronix intermittent probe permit signal sampling without direct circuit contact.

The other attachment, known as an Electro-Probe, is a metal probe tip insulated with thick pliable rubber. The insulated tip is placed against circuit components without making any electrical contact with the suspected circuit, and can be moved from stage to stage in order to isolate the intermittent.

Probe Your Meter

The Futuramic Company of Chicago, Ill., now has a complete line of meter test probes, four of which are designed for use with conventional volt-ohm-milliammeters, plus two recently-developed units for use with vacuum-tube voltmeters. These probes are especially designed to open up new fields of application for your meter. Through their proper use, the technician can realize more utility from such instruments.

In general, the units are sturdily constructed and very attractively designed. Each probe has a gold-plated steel housing and extra-long leads for maximum serv-

PF REPORTER · October, 1957




**WORLD'S LARGEST
MANUFACTURER OF
ANTENNAS PRESENTS**

America's Finest
LINE OF Conicals
with "PRESTO"
INSTANT MOUNT ASSEMBLY
THAT OPENS AS EASILY
AS AN UMBRELLA!






Remove from box

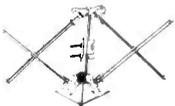

Open elements

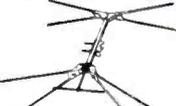


and Presto, it's ready!


COMPARE TENNA FEATURES!

- Arrays are full size and completely pre-assembled
- New Polyethylene Cable Anchor removes all tension from terminals
- Front Bracket made of heavy spring temper aluminum alloy with High Q molded plastic insulator
- Rear Bracket made of heavy gauge aluminum to resist strongest gales and heaviest ice
- Doweled elements prevent whistling
- Director Bar on Bar-X models improves performance on higher channels
- Full line: 8 single array models, 8 stacked models and 8 "Do-it-yourself" models.

THE TENNA MANUFACTURING CO.
CLEVELAND 25, OHIO

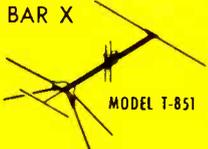

BAR X
MODEL T-851

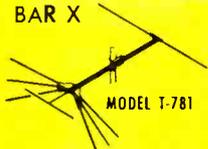


BAR X
MODEL T-781




BAR X
MODEL T-751

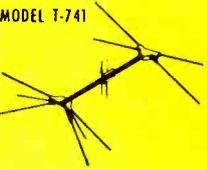
**ALL MODELS AVAILABLE SINGLE OR STACKED
IN INDIVIDUAL BOXES OR IN BULK**



MODEL T-741

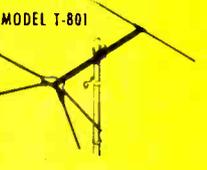

MODEL T-801

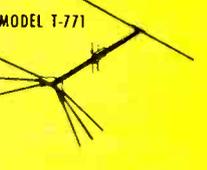

MODEL T-771



MODEL T-811



MODEL T-791



do this...

then this...



if it still works...

it's a

Greenohm*

WIRE-WOUND • CEMENT-COATED
POWER RESISTOR

Here's proof of the **BUILT-IN** dependability of every Clarostat "Greenohm" Power Resistor. Connect it across 110 v. line. Resistor will become hot enough to light a cigarette. Disconnect and plunge in water. Resistor will remain as good as new—no blisters, no cracks. You can count on "Greenohm" Cement-Coated Power Resistors for every application.

Your CLAROSTAT Distributor carries a Complete Stock (5- to 200-watt sizes) of "GREENOHM" Power Resistors!



*Reg. U.S. Pat. Off.

CONTROLS AND RESISTORS

CLAROSTAT MFG. CO., INC. • DOVER, NEW HAMPSHIRE, U.S.A.
In Canada: Canadian Marconi Co., Ltd., Toronto 17, Ont.

DO NOT BE ELECTROCUTED...


USE **SAFE**
A.C. POWER!

WITH



UNIVERSAL (ATR 6U-RHG for 6 volts
and 12U-RHG for 12 volts)
INVERTERS

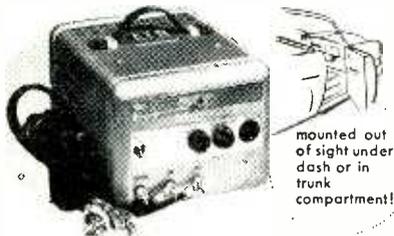for changing your storage
battery current to
A.C. HOUSEHOLD ELECTRICITY
Anywhere... in your own car!



Especially designed for operating standard 110-volt
A.C. 1/4" Electric Drill,

- also
- Electric Soldering Iron
 - Electronic Test Equipment
 - Electric Polisher
 - Hand Vacuum Cleaner
 - Portable TV Sets
 - Tape Recorder
 - PA Systems
 - Electric Razors



ATR Inverter mounted in Car



Using Electric Drill



Soldering ground lead



Splicing antenna lead-in



Tape Recording details of call

*In many Cities, the use of
commercial AC power for
outside electric hand tools
is prohibited by law
since AC line is grounded.
ATR INVERTERS provide
SAFE AC Power with no
possible danger of being
electrocuted.

SEE YOUR JOBBER OR WRITE FACTORY

- ✓ NEW MODELS "A" Battery Eliminators.
- ✓ NEW DESIGNS DC-AC Inverters,
- ✓ NEW LITERATURE Auto Radio Vibrators



AMERICAN TELEVISION & RADIO CO.
Quality Products Since 1931
SAINT PAUL 1, MINNESOTA, U. S. A.

icing convenience. The four VOM probes are pictured in Fig. 3. Fig. 3A is the high-ohms probe, type 261. I found that this unit will extend the limits of an ohmmeter by converting the $R \times 10,000$ ohm range to an $R \times 100,000$ ohm range, making it possible to read resistance values up to 200 megohms. Practical servicing applications may consist of measuring leakage in capacitors, transformers, tubes and sockets; measuring insulation resistance in high-voltage circuits, lightning arresters, isolation networks, wiring harnesses, etc. The 261 probe can be used with most VOM's having a center-scale indication of 12 ohms and a $7\frac{1}{2}$ volt internal battery.

The test instrument identified in Fig. 3B is the type 262 signal-tracing VOM probe which, when used in conjunction with a conventional volt-ohm-milliammeter, makes possible the measurement of signal voltages and thus the isolation of weak or inoperative stages in radio or TV sets. Checks can be made in almost any section of a television receiver, in many cases without pulling the chassis from the cabinet. The probe is capable of detecting signals from 60-cycles to 200 megacycles and is adaptable to any 20,000 ohm-per-volt meter.

The Futuramic type 263 polarity-reversing probe (Fig. 3C) provides an extra convenience for the technician in that it will reverse the polarity of any measured voltage quickly and easily. The probe will handle all voltages commonly encountered in radio and television servicing up to a value of 500 volts DC or peak-to-peak. It can be used with any VOM and will provide either a positive or negative indication with a flick of the finger-tip switch.

The range-splitter probe type 264 is pictured in Fig. 3D. This particular probe actually increases the utility of a meter by providing an extra 500-volt range where it is needed most. When measuring voltages between 250 and 400 volts on certain VOM's, it may be necessary to take the measurement on a 1,000-volt scale. A high degree of accuracy is sometimes difficult to obtain under these circumstances. By using this new

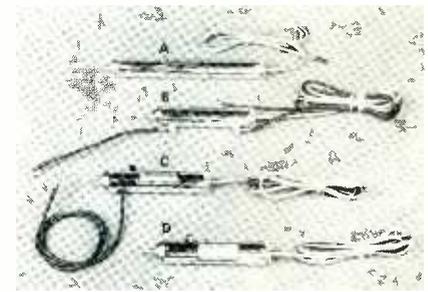


Fig. 3. Futuramic multimeter probes. (A) type 261, high-ohms probe; (B) type 262, signal-tracing probe; (C) type 263, polarity-reversing probe; and (D) type 264, range-splitter probe.

probe, the original 50-volt scale of the meter becomes a 500-volt scale. Voltages between 250 and 500 volts can then be read on the upper half of the scale where the meter is more accurate and the value can be more clearly interpreted. The range-splitter features a finger-tip slider switch for conveniently switching the additional range in or out of the circuit. The probe is suitable for use with many popular 20,000 ohm-per-volt VOM's having voltage scales of 2.5, 10, 50, 250, and 1,000.

In addition to the multimeter probes illustrated in Fig. 3, Futuramic has also designed a high-ohms probe for use with certain VTVM's. This probe, known as type 265, permits the measurement of resistance values up to 10,000 or 20,000 megohms, depending upon the scale calibration of the instrument with which it is used.

The probe houses a type Y-10 transistor battery and one pen-light cell. It not only makes possible the measurement of higher resistances, but can also increase the accuracy of measurements between 100 and 2,000 megohms by placing the meter indication on an expanded portion of its scale. Similar in outward appearance to the probes pictured in Fig. 3, it can be adapted to any VTVM having an $R \times 1$ meg scale, an input resistance of 10 megohms, and an internal battery supply of 1.5 volts.

The type 268 peak-to-peak VTVM signal-tracing probe is the latest addition to the Futuramic line. Shown in Fig. 4, this device makes it possible for your VTVM to indicate peak-to-peak voltage values directly on the DC scales of the instrument. Readings ob-



Whenever You Want Dependable Electrical Protection

... BUSS FUSES ARE YOUR ANSWER!

Here's why .. With BUSS fuses, dependable electrical protection isn't left to chance. Every BUSS fuse is tested in a sensitive electronic device that automatically rejects any fuse not correctly calibrated, properly constructed and right in all physical dimensions.

The result — when an electrical fault occurs, BUSS fuses quickly clear the circuit and the danger of damage to equipment is held to a minimum. Yet, BUSS fuses won't cause needless

shutdowns by blowing when trouble does not exist.

In sales, the dependability of BUSS fuses helps you avoid 'kicks' and complaints that the fuses you sold failed to protect or blew needlessly.

In service, by installing BUSS fuses you help prevent costly, unnecessary 'call-backs' because BUSS fuses operate properly under all service conditions.

With a complete line of fuses available to meet all your service needs, it is just good business to standardize on BUSS. They help protect both your good name and your profits.

For more information on BUSS and FUSETRON Small Dimension fuses and fuseholders . . . Write for bulletin SFB. Bussmann Mfg. Division (Mc-Graw-Edison Co.) University at Jefferson, St. Louis 7, Mo.

BUSS fuses are made to protect — not to blow, needlessly



Makers of a complete line of fuses for home, farm, commercial, electronic, automotive and industrial use.



SANDY SAYS!
Tests and Repairs **ALL**
CRT Tube Elements
for Opens and Shorts.

New and Improved
REACTO-TESTER

Model T-401
Tests and repairs
ALL picture tubes.

Only \$39.95
with Case and Cover

**FACTORY TESTED
AND FULLY
WARRANTED**



TESTS FOR:

- Open Connections
- Open Elements
- Useful Life
- Shorted Elements
- Cathode Emission
- Gaseous Tube

REPAIRS:


- Open Elements
- Corrects Shorts
- Reactivates Low Emission Tubes
- Restores Brightness

AT YOUR DISTRIBUTOR

anchor products co.
ELECTRONIC COMPONENTS
2712 W. Montrose • Chicago 18, Ill.

**Grips
the screw!
Drives it too!**

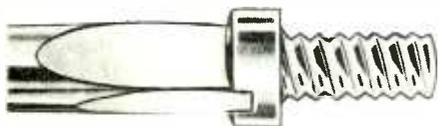**Quick-Wedge
SCREW-HOLDING
SCREWDRIVER**



2" to 14" blades, 4 bit sizes
Available with shockproof
plastic covered tubing
Unconditionally guaranteed



ASK FOR IT AT YOUR DEALER
Kedman Co., 233 So. 5th W., Salt Lake City

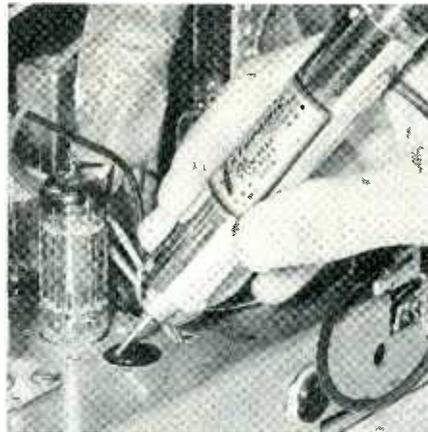


Fig. 4. Futuramic's type 268 is used with VTVM to measure peak-to-peak signals.

tained by using the probe should compare to those given in the service literature for peak-to-peak waveform values.

To avoid possible damage to the diodes built into the probe, measured values are limited to 100 volts peak-to-peak. The 268 can be employed with most popular VTVM's having an input resistance of 10 megohms.

I recently made use of this particular probe in connection with an analysis on loss of picture and sound in TV receivers. Following procedures outlined in the instruction sheet and using one of our TV test chassis, I decided to troubleshoot for loss of signal caused by a fault I had purposely introduced into the 1st IF amplifier stage. The first step called for a check at the video amplifier stage. Here, I pulled the tube and placed the probe on the input grid contact of the empty socket. With the probe's short ground lead connected to chassis, a normal indication is approximately 2 to 6 volts. I obtained a zero indication at this point which meant that no signal was reaching the video amplifier.

The next check point took me to the input of the video detector stage. Again I found a zero indication which naturally pointed to trouble toward the front end. A normal indication at the detector input would have been about 2 volts.

Continuing, I then pulled the last IF amplifier tube and measured the input grid signal on the proper socket pin. If the signal was reaching this stage, I should detect a peak-to-peak reading of from .2 to .3 volts. No signal was



Fig. 5. Eby's new Trans-Tester converts milliammeter to transistor checker.

present, however, so I proceeded with the recommended signal-tracing approach.

Tuning the receiver off-channel, I raised the mixer-oscillator shield until it no longer made contact with the chassis. With my fingers still in contact with the shield, I applied the probe to the video detector input. Here, a voltage indication would eliminate the mixer and all following stages. When I still obtained a zero reading, however, the trouble was then isolated to either the first IF stages or the mixer. A few quick voltage measurements then pinpointed the fault to the 1st IF amplifier circuit.

The 268 is also useful in localizing trouble in sound, sync, sweep and high-voltage circuits. Procedures for signal-tracing these sections are covered in the instruction sheet packaged with each unit.

**Check Transistors
On Your Own Meter**

The relatively small bench instrument pictured in Fig. 5 is the Eby Trans-Tester transistor tester, manufactured by Eby Sales Co., New York City.

Upon examination of this piece of equipment, I found that it operates in conjunction with any VTVM, VOM, or multimeter capable of accurately measuring currents between 0 and 10 ma. Two separate jacks are mounted on the front of the unit for connection of the meter test leads. In addition, two molded transistor sockets are provided—one for n-p-n and one for p-n-p types. The unit is self-powered by four 1½-volt penlight cells and is used in determining current gain by measuring collec-

Your Independent Service Advertising Program expands with your purchases of CBS tubes

One of a new series of full-page ads appearing in TV GUIDE



This family cook is your independent service-dealer. He's that busy neighbor who somehow finds time to be scoutmaster of his son's troop. He has his radio and TV service business in your town . . . and he knows he'll stay in business there only as long as he does superior work. In fact, when he works for you, he bets his family's bread and butter he'll do a better job . . . and he will.

for your radio and TV repairs, call the man who cares... your INDEPENDENT SERVICE-DEALER

He actually bets his family's bread and butter he'll do a better job for you . . . his business success depends upon it.

He is a highly skilled technician, trained and equipped to service promptly *all* makes of radio and TV sets at a fair price. So next time your radio or TV needs repairs, call the man who cares. Call your independent service-dealer.



For the best entertainment tune to CBS.

Look for this emblem . . .



Whenever your set needs a new tube, ask to have it replaced with a CBS tube. There are no better tubes made.

CBS-HYTRON, Danvers, Mass.
A Division of Columbia Broadcasting System, Inc.

We know you like your Independent Service Program and want it expanded. We know it from a nation-wide survey . . . and from your increasing purchases of CBS tubes. May we remind you: each time you buy CBS tubes, you support your own independent service-dealer campaign. Keep it going . . . keep it growing . . . always specify CBS tubes.

SUPPORTING MATERIAL ALSO EXPANDS

- "The Independent Service Business and Your Future" booklet
- Independent Service decal
- 10 new postal cards
- 16 new advertising mats
- Radio and television scripts
- Consumer booklet "On the Care of a Television Set"

Ask your CBS Tube distributor for this tie-in material . . . or write for illustrated broadside PA-181.



CBS-HYTRON - Danvers, Massachusetts
A Division of
Columbia Broadcasting System, Inc.

FOR THE BEST IN ENTERTAINMENT TUNE TO CBS

October, 1957 · PF REPORTER

37

tor current at two different bias levels.

To check a transistor, I first connected the test leads of a commercial VOM to the jacks provided. Leaving the gain switch of the instrument in the off position and placing the meter selector on a 1-ma range, I inserted a p-n-p transistor in the proper socket. Referring to the characteristic chart given in the operating instructions, I noted the readings should not exceed .75 ma for low-gain transistors and 2 ma for high-gain units. The particular one

tested produced a reading of 0.5 ma which eliminated the possibility of a short or open. I next moved the gain switch to the on position and observed the meter indication. The current had increased to approximately 0.8 ma, providing a net gain of 0.3 ma. This figure was satisfactory according to the chart, which indicated that the increase should be at least 0.2 ma.

Millivoltmeter by Simpson

The pocket-size tester shown in

Fig. 6 is the new Model 387 millivoltmeter manufactured by Simpson Electric Co. of Chicago, Ill. Especially designed for testing thermocouples in appliances, such as gas-fired hot water heaters, clothes dryers, furnaces, space heaters and gas refrigerators, the instrument is a highly accurate DC millivolt measuring device.

Specification features are:

1. Meter Range—five individual ranges from 0 to 10, 30, 100, 300, and 1,000 millivolts, range selected by connection of test leads.
2. Meter Accuracy— $\pm 3\%$ of full scale deflection at ambient temperatures of from 50° to 120° F, maximum deviation of $\pm 5\%$ from -55° to $+185^\circ$ F.
3. Test Leads—two 48" well insulated leads with alligator clips are provided.
4. Size and Weight— $3" \times 5\frac{7}{8}" \times 2\frac{1}{2}"$, $1\frac{1}{2}$ lbs.



Fig. 6. Simpson Model 387 millivoltmeter.

Although I have had little or no opportunity to employ this piece of equipment on gas-fired apparatus in the lab, I did make use of it by theoretically converting the unit to a direct reading milliammeter. I didn't actually modify the instrument, but merely placed a precision 1-ohm resistor in series with various circuits drawing between 1 and 1,000 ma. With the test leads across the 1-ohm resistance, the meter automatically indicated circuit current in DC ma. This measuring technique might be applied to transistor circuitry to check collector current or other allied measurements. The internal resistance of the meter, however, must be considered before calculating transistor current from a given circuit load. ▲

PF REPORTER · October, 1957

SPECIALLY PRICED DURING OCTOBER

TIMED RIGHT FOR YOUR BIG TV SERVICE SEASON!

SAVE 2 \$1.89

G-C SPRA-KLEEN SPECIAL! \$1.89

2

NEW ACTIVATED FORMULA

NO. 8666X

G-C SPRA-KLEEN

2 CANS FOR \$1.89 DEALER NET

VALUE \$2.40

special this month

2 CANS \$1.89

SEE YOUR G-C JOBBER NOW!

NOW, WHEN YOU NEED IT, is the time to stock up on G-C SPRA-KLEEN . . . the easy-to-use electrical contact cleaner and lubricant in the power spray can. Brushless, clean, convenient . . . SPRA-KLEEN makes servicing easier. Buy now and save during this special sale!


FREE G-C CATALOG . . . send postcard today!

GENERAL CEMENT MFG. CO.

Division of Textron Inc.

400 SOUTH WYMAN STREET

ROCKFORD, ILLINOIS

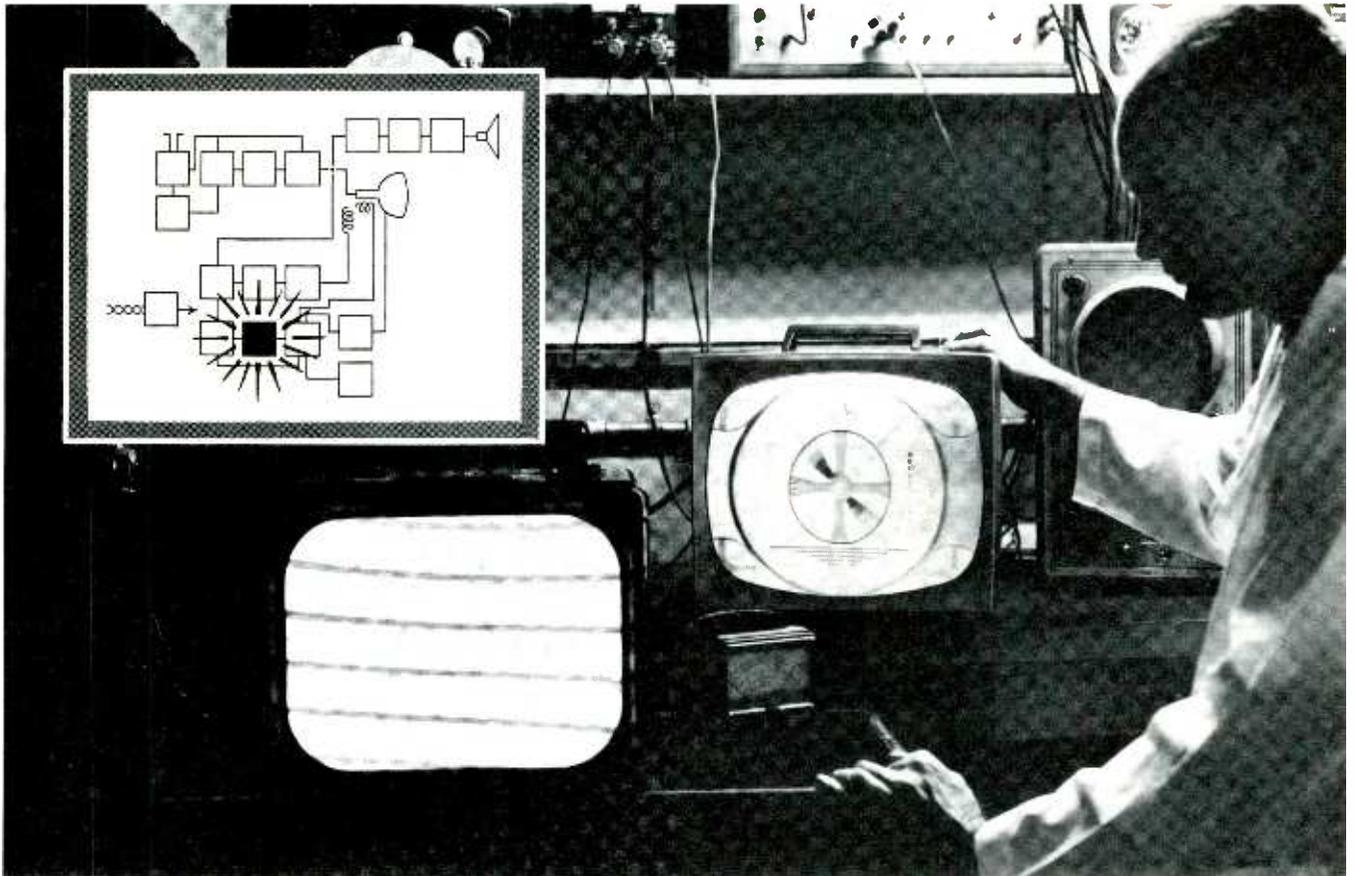

Here General Electric Application Engineer C. L. Taylor shows what can happen when an old-style horizontal-oscillator tube is used in two different TV sets. Image at left is completely

out of sync. To avoid this hazard, the cut-off and other electrical characteristics of General Electric tubes are held within limits that bring satisfactory operation in all television circuits.

Built-in high quality of G-E horizontal-oscillator tubes means fewer TV-servicing call-backs!

Call-back demands from television owners are cut when you install General Electric horizontal-oscillator tubes.

For example: tube microphonics in multivibrator circuits can cause eccentric sync, especially when a set such as a portable is moved or shaken. With G.E.'s 7AU7 and 12AU7, extra-heavy micas, the tight fit of grid side rods, plate, and cathode, and sturdy over-all construction result in minimum microphonics and a steady television picture.

Also, uniform tube-to-tube cut-off characteristics—achieved by care in grid manufacture and rigid testing—enable you to install General Electric types in any receiver knowing that minimum adjustment will be needed for superior picture performance.

Blocking-oscillator circuits require that a tube

throughout its life be able to produce peak plate currents 10 to 15 times higher than average. In the 6CG7 and 6SN7-GTB, General Electric scores with a specially processed high-emission, long-life cathode. Peak current capabilities remain high; sync drift is avoided.

For every set, for every socket, G-E receiving tubes mean greater assurance of owner satisfaction . . . and your G-E tube distributor makes prompt delivery. Phone him today! *Distributor Sales, Electronic Components Division, General Electric Co., Owensboro, Ky.*

Progress Is Our Most Important Product

GENERAL  ELECTRIC

161-1A9

Sidelines. Today's transistor radios will sell themselves if given half a chance. This is particularly true of the new 7-transistor models, several of which have volume and tone comparable to that of table radios.

Let's take the new Philco 7-transistor model as an example. This comes with a fine leather carrying-case having punched holes in front of the loudspeaker, plus a shoulder carrying strap. The serviceman has the set hung over his shoulder, tuned to a snappy musical program as he rings the doorbell. He enters, and the odds are it won't take more than 60 seconds before the customer comments on the music coming from the little leather box. Here is the chance to hand over the set to the customer and say, "Why don't you and your family try it out while I'm working on your own set? The batteries are guaranteed to last a year, so don't worry about letting it run at full volume."

After finishing the repair job, it's easy to ask how they liked it, and swing naturally into the special offer being made on that set to the serviceman's customers. It may take an evening callback, when hubby is home, to clinch the sale, but the profit possibilities will make that well worthwhile.

Another profitable sideline is the case of the profit-minded Indianapolis serviceman who brings a table-model FM receiver along on TV home service calls, and plugs it in with the explanation that he likes music while he works. The unsuspecting set owner is usually intrigued by the high-quality FM music, and in many cases he's impressed enough to find out more about the unit. Before you know it, he's bought the radio. The technician gets a nice extra profit on the side, and the new FM station in town also gets a promotional boost.

\$ & ¢

Names. The titles of television and radio service associations in the United States show considerable variation. A recent survey by "Guild News" points out that 52 of these associations use the word *technician* in their title, and 27 use *servicemen*. Three use *engineers*, and only two use *radiomen*.

With this much variation in established names, there is a real problem in getting any one name accepted by even just a majority of the over 200 associations in the



BY JOHN MARKUS

Editor-in-Chief, McGraw-Hill Radio Servicing Library

United States. Looking into the future, it would seem that a broader title for an association, a service business and an individual in the business would stand the best chances for widespread adoption. "Guild News" suggests *Electronic Service Technicians* as a title which is accurate, offers long-time usefulness and carries prestige from the viewpoint of the customer.

\$ & ¢

Fishing. Twelve service dealers in the communities surrounding Mineola and New Hyde Park on Long Island signed agreements to go *fishin' Wednesdays* this past summer. The arrangement was in effect from June 1 to August 31, and served to make the 5-day, 40-hour week a reality during these slower months of the year.

If you like the idea, now is the time to start the ground work for reaching such an agreement next summer in your own community.

\$ & ¢

Question. "A short circuit, you say. And just how much will it cost to lengthen it?" asked the shapely blonde housewife of her TV repairman.

\$ & ¢

Cutting Service Costs. A cost reduction campaign by Normandy Radio & Television in New Orleans revealed that costs of TV service can be cut by changing operating techniques and buying new equipment. Here are their methods for boosting net profit as described in *Electrical Merchandising*:

1. Cut travel time and mileage by delivering sets only on 3 scheduled days each week and handling only pickups on the other 3 days. Thus, the firm's trucks no longer flit back and forth over the town,

because their routes are carefully laid out for minimum mileage beforehand. The schedule is relaxed only occasionally, such as when a pickup happens to be right next door to a delivery.

2. Contract work for retail stores was dropped as being the least profitable, even though this was a big-volume operation. This made the same work force and equipment available for individual consumer jobs which paid better.

3. A complete shop survey showed that money could be saved by replacing existing equipment which was inadequate or high in operating cost.

4. The owner himself took over control of buying. Careful watching of inventory records permitted buying safely in maximum quantities, with corresponding price savings. Cash discounts are always taken when allowed on bills.

5. Unprofitable savings programs were dropped. Thus, the saving and selling of scrap was abandoned because the time and effort involved in collecting and marketing the scrap had not paid off.


\$ & ¢

Vacations. This year, 99% of all companies in this country will give paid vacations to their employees, as compared with only 46% before World War II. Length of vacation usually increases with years of service, up to the maximum set by company policy. This year, 24% of the companies gave maximums of 4 weeks or more and 53% gave up to 3 weeks, generally after 10 years service.

How much vacation did you get this year? If you have been operating your own business for 10 years, you certainly should have taken 3 weeks, and you should begin thinking of 4-week vacations. Vacation is a logical part of overhead expense.

NEW

HICKOK

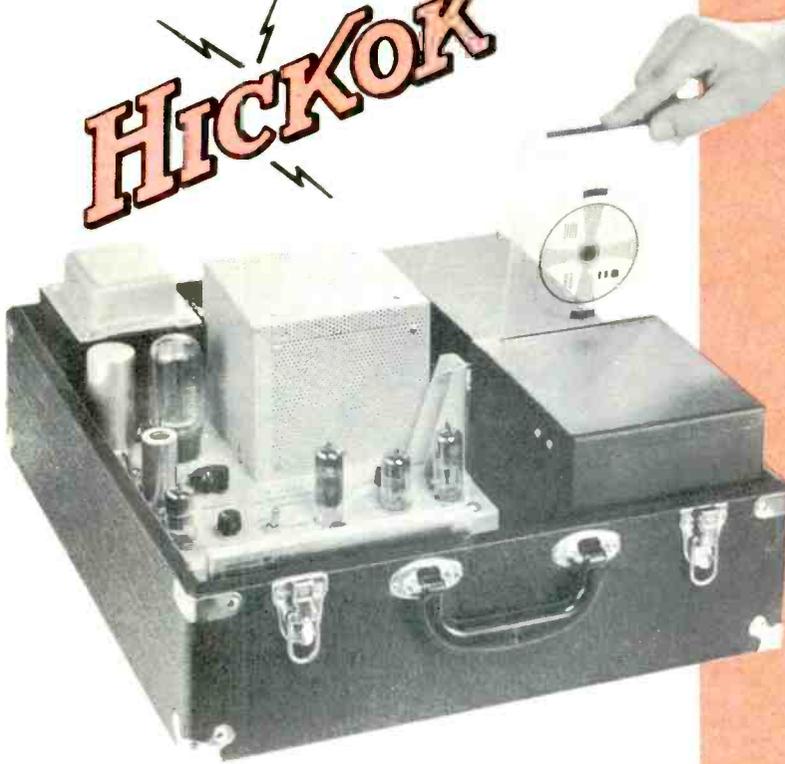

Model 760 Video Scanner

A COMPLETE
CABLE CONNECTED
TV TRANSMITTING STATION

Greatly
Simplifies TV Servicing

This extremely stable and versatile TV trouble shooter has many uses in TV service. It features innumerable signals and displays normally not available to the TV technician. The 760 will instantly scan and produce a video or RF signal for any slide that is inserted into the unit.

Through use of the 760, any TV technician can quickly analyze the frequency response of picture definition capabilities of any TV receiver. For color television, the slide to produce white dots on the raster will enable a quick and accurate convergence adjustment. (This white dot pattern is the most stable pattern available in any generator.) A rapid check of horizontal and vertical linearity along with height and width adjustments are easily accomplished by viewing a slide. The unit provides an excellent check for the sync stability of a TV receiver. The ratio of video information to sync is adjustable and consequently can be varied to determine how well a television receiver locks-in on either high or low sync levels. The 760 has both RF or Video outputs sufficient to drive several receivers simultaneously.




* Characteristics

- * ◆ Patterns furnished are Bar, Dot, Standard Test Pattern and transparent blanks for grease pencil use.
- ◆ Optional patterns are Gamma, Square Wave and Burst Wave Forms.
- ◆ Will operate with any TV receiver—black & white or color.
- ◆ Generates and scans at the 525 line, 60 field, and 30 frame systems.
- ◆ Completely crystal controlled—sync to RETMA specifications.
- ◆ Horizontal sync contains front and back porch.
- ◆ Vertical pulse is serrated to maintain horizontal sync.
- ◆ RF channel selector covers channels 2 thru 6.
- ◆ Video output is 2 volts peak-to-peak with an impedance of 100 ohms.
- ◆ Video output either positive or negative.
- ◆ Resolutions well over 450 lines or band width in excess of 5 MC.
- ◆ The unit is comprised of 17 tubes including the CRT, photo-multiplier and rectifier.
- ◆ The sync level is variable to permit any combination of sync to video information. This is preset at the factory to RETMA standards.
- ◆ RF output of 100,000 microvolts is sufficient to drive several receivers simultaneously. With the aid of a distribution system an unlimited number of TV sets can be added.

THE HICKOK ELECTRICAL INSTRUMENT COMPANY
10566 Dupont Avenue • Cleveland 8, Ohio

Stark Electronic Sales Co., P.O. Box 2407, Ajax, Ontario, Canada
Export Department, 431 Fifth Avenue, New York

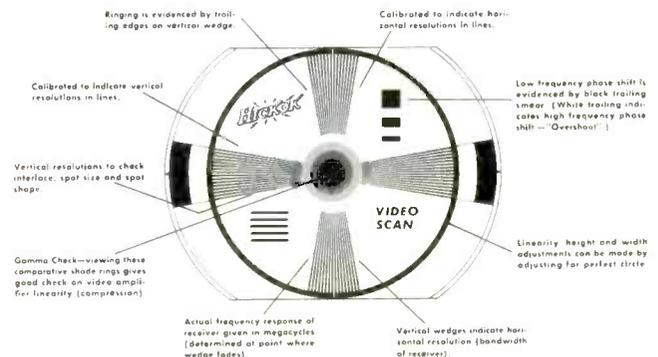Quickly and Accurately Permits These TV Receiver Checks:



More Service Facts About TRANSISTOR PORTABLES



by Leslie D. Deane

Fig. 1. Check points in an initial troubleshooting approach.

Transistorized radios are here to stay, and service shops all over the country will soon begin to realize a fair share of the potential servicing business they will bring. Although the prescribed servicing approach for these miniaturized circuits will not entirely obsolete existing test instruments or troubleshooting procedures, it will require certain new techniques and precautions.

In the March 1957 PF REPORTER, we gave consideration to batteries and their replacement, disassembly problems, tools, and bench power required in the servicing of transistor radios. In the June issue, we presented several hints and made suggestions for localizing troubles. This month we will continue with our practical servicing approach and deal more directly with measurements and component replacements.

Visual Inspection

Before digging into an inopera-

tive transistor portable with a signal generator, meter, or a hot soldering iron, let's first consider a more simple, time-saving measure. When actually repairing these miniature radios, an intense examination of all components and wiring will prove to be more fruitful than any other initial troubleshooting procedure. Mainly, this

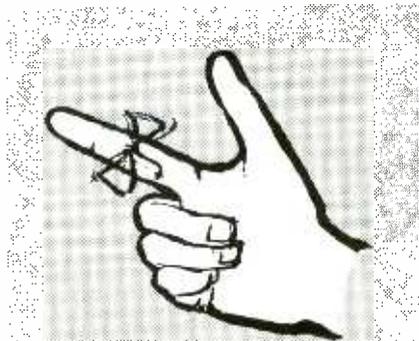


Fig. 2. A needle-point probe is ideal for transistor-radio testing.


is because the units are portable and will normally undergo rough treatment that often results in some form of physical damage. Then, too, transistors and certain other components can be easily ruined by careless, impromptu test methods; and even with reasonable care, there is some chance of damage being caused when circuit components are replaced or a soldering iron is applied to the delicate printed-wiring boards. With these considerations in mind, one can readily understand that a close visual inspection should be the first and most important step in troubleshooting a portable transistor radio.

After testing the battery by substitution or measurement, regardless of the symptoms involved, the technician should check for some of the possible faults pointed out in Fig. 1. Troubles in the RF section of the receiver often can be traced to broken leads or a damaged loopstick. Improper


REMEMBER...
when you
SPECIFY STANCOR



**YOU WON'T HAVE
TO DO THIS...**

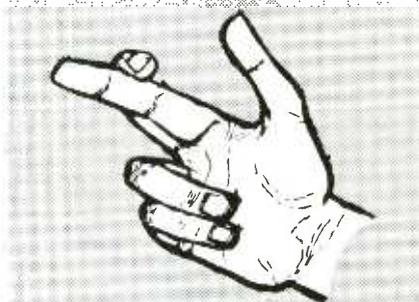

**because
YOUR CUSTOMERS
WILL DO THIS**

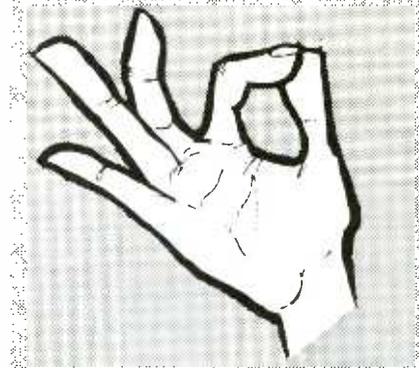

**STANCOR
TRANSFORMERS
are available at better
distributors everywhere**

free!

The latest up-to-date Stancor TV Transformer Replacement Guide and Catalog—from your distributor or write us for your copy.



CHICAGO STANDARD TRANSFORMER CORPORATION

3503 ADDISON STREET • CHICAGO 18, ILLINOIS

Export Sales: Roburn Agencies, Inc., 431 Greenwich St., New York 13, N.Y.

the specs are the proof . . .
the BEST BUYS are **EICO**TM
for COLOR & Monochrome TV servicing

NEW COLOR
and Monochrome
DC to 5 MC LAB & TV
5" OSCILLOSCOPE

=460
Factory-wired
and tested \$129.95
Also available as kit \$79.95

• Features DC Amplifiers!

Flat from DC-4.5 mc. usable to 10 mc. VERT. AMPL.: sens. 25 rms mv/in; input Z 3 megs; direct-coupled & push-pull thruout; K-follower coupling bet. stages; 4-step freq-compensated attenuator up to 1000:1. SWEEP: perfectly linear 10 cps-100 kc (ext. cap. for range to 1 cps); pre-set TV V & H positions (30 & 7875 cps); auto. sync. ampl. & lim. PLUS: direct or cap. coupling; bal. or unbal. inputs; edge-lit engraved lucite graph screen; dimmer; filter; bezel fits std photo equip. High intensity trace CRT. 0.06 usec rise time. Push-pull hor. ampl., flat to 400 kc, sens. 0.6 rms mv/in. Built-in volt. calib. Z-axis mod. Sawtooth & 60 cps outputs. Astig. control. Retrace blanking. Phasing control.

NEW TV-FM SWEEP GENERATOR & MARKER

=368
Factory-wired
and tested \$119.95
Also available as kit \$69.95

Entirely electronic sweep circuit (no mechanical devices) with accurately-biased inductor for excellent linearity. Extremely flat RF output: new AGC circuit automatically adjusts osc. for max. output on each band with min. ampl. variations. Exceptional accuracy: edge-lit hairlines elim. parallax. Swept Osc. Range 3-216 mc in 5 fund. bands. Variable Marker Range 2-75 mc in 3 fund. bands; 60-225 mc on harmonic band. 4.5 mc Xtal Marker Osc., xtal supplied. Ext. Marker provision. Sweep Width 0-3 mc lowest max. deviation to 0-30 mc highest max. dev. 2-way blanking. Narrow range phasing. Attenuators: Marker Size, RF Fine, RF Coarse (4-step decade). Cables: output, scope horiz., scope vertical

NEW DYNAMIC CONDUCTANCE Tube & Transistor Tester

=666
Factory-wired
and tested \$109.95
Also available as kit \$69.95

COMPLETE with steel cover and handle. SPEED, ease, unexcelled accuracy and thoroughness. Tests all receiving tubes (and picture tubes with adapter). Composite indication of Gm, Gp & peak emission. Simultaneous sel. of any 1 of 4 combinations of 3 plate voltages, 3 screen voltages. 3 ranges of continuously variable grid voltages (with 5% accurate pot). New series-string voltages: for 600, 450, 300 ma types. Sensitive 200 ua meter. 5 ranges meter sensitivity (1% shunts & 5% pot). 10 SIX-position lever switches: free-point connection of each tube pin. 10 pushbuttons: rapid insert of any tube element in leakage test circuit & speedy sel. of individual sections of multi-section tubes in merit tests. Direct-reading of inter-element leakage in ohms. New gear-driven rollchart. Checks n-p-n & p-n-p transistors: separate meter readings of collector leakage current & Beta using internal dc power supply. CRA Adapter \$4.50

See the 50 EICO models IN STOCK at your neighborhood distributor. Write for FREE Catalog PF-10

Prices 5% higher on West Coast

EICO[®] 33-00 Northern Blvd. Long Island City 1, N.Y.

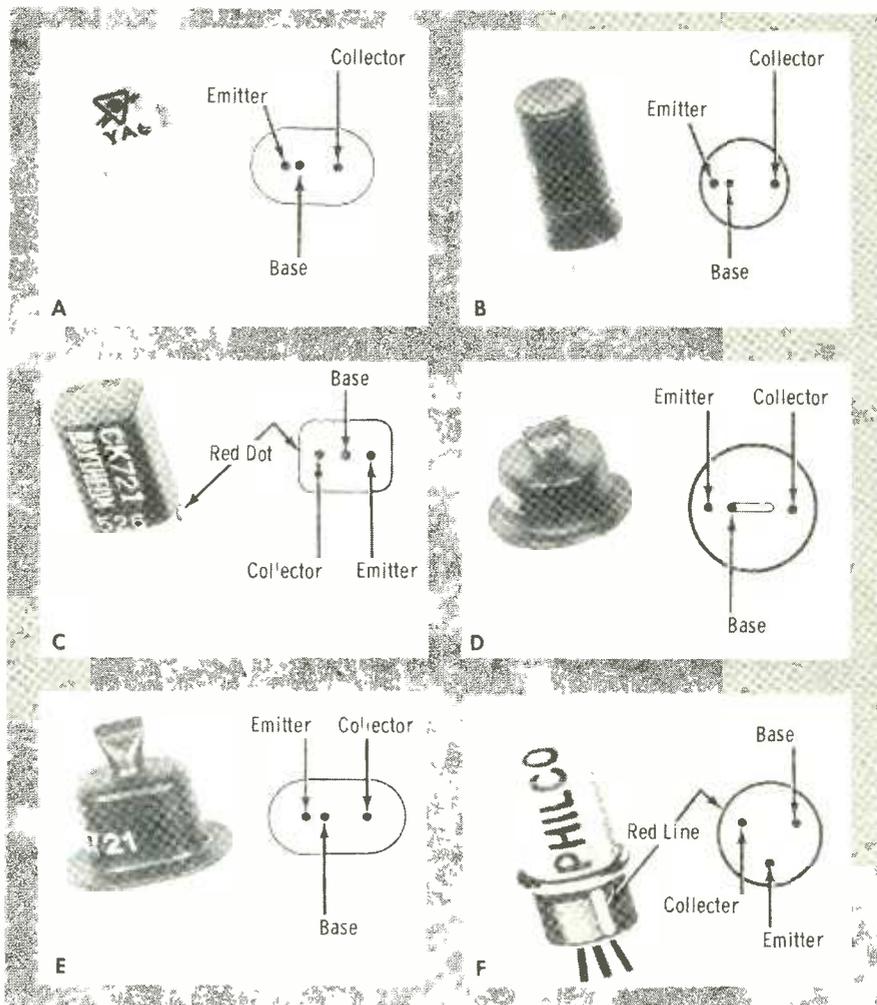


Fig. 3. Element connections for common portable-radio transistors.

ground connections, dirty or bent tuning-gang plates and improper lead dress in the converter section are also faults which can be located visually. Others are intermittent troubles caused by damaged or corroded contacts, shorts between the closely spaced components and printed wires, or broken conductors on the wiring board itself. If a broken or cracked wiring board is encountered, the break usually can be repaired with a nonconductive cement and reinforced with short pieces of wire. The wires should be soldered to both sides of all broken conductors after the cement has hardened.

The miniaturized on-off switches employed in many of the transistor portables are somewhat delicate and more prone to failure than those found in larger receivers. A damaged or worn switch may not open the supply circuit when in the off position, thereby shortening battery life. Due to the lack of a positive detent or

click in the switch action, owners will often leave the set on unintentionally. This possibility should be explained to the customer if frequent battery replacements become necessary.

Voltage Measurements

At one time or another, most servicemen have been cautioned about the care one must exercise when metering transistor circuits. Actually, these warnings are not intended to discourage the technician from performing such tests, but rather to help prevent him from damaging a perfectly good transistor or some other component in the apparatus. The technician need not be a transistor specialist or an engineer to take voltage and resistance measurements in these portable receivers. All he needs to do is use a little common sense and become better acquainted with the ways in which a transistor or its affiliated components might be damaged.

Although conventional multi-PF REPORTER · October, 1957



SC57-9

CAPACITY CHART

Rated Voltage	Surge Voltage	Max. Cap. 1 3/8 x 4 1/8	Max. Cap. 1 3/4 x 4 1/8	Max. Cap. 2 x 4 1/8	Max. Cap. 2 1/2 x 4 1/8	Max. Cap. 3 x 4 1/8
5	7	8500	15000	20000	33000	45000
15	20	6000	10500	13500	24000	35000
25	40	4500	8000	10000	17500	25000
50	75	1750	3250	4250	8000	10000
75	100	1000	1500	2250	4250	6000
100	135	675	1250	1500	3000	4000
150	185	600	1000	1250	2500	3500
200	250	300	500	600	1000	1500
250	300	225	375	450	850	1200
300	350	200	350	400	750	1100
350	400	170	300	375	700	1000
400	475	140	250	325	575	850
450	525	125	225	275	500	800

For additional capacity and voltage combinations, write us.

**BUILD STABILITY
and LONG LIFE
into your low voltage
power supplies**

**with
SANGAMO
Type DCM
Electrolytic
Capacitors**

These high quality electrolytic capacitors are especially designed for use as energy storage components in DC circuitry where peak power requirements exceed the maximum output of the associated power supply.

Sangamo Type DCM Capacitors provide exceptionally low equivalent series resistance . . . have extremely high capacity for case size in low voltage ranges . . . are designed to permit high ripple current without overheating. They minimize ripple voltage and insure steady, stable DC voltage. Use of the Sangamo DCM eliminates any need for heavy, bulky choke components.

Type DCM Capacitors can be supplied in maximum energy content rating of 80-watt seconds in voltage ratings from 15 to 450 VDC. Maximum capacity value of 33,000 mfd. can be supplied at 15 WVDC.

Write for Engineering Bulletin TSC-114C.

**SANGAMO
Electric Company**

SPRINGFIELD, ILLINOIS

it's **SELL SEASON!**



with

AMPHENOL

Color **COUPLERS!**

Fall is the season for selling—and AMPHENOL's new Color-Couplers are profitable selling items! Connecting two, three or four TV sets to one antenna system, Color-Couplers work with flawless efficiency — effective isolation, low loss and properly matched impedances for clear, bright pictures. Flat signal response makes them tops for color and equally good for Black & White TV—can be used with FM radio, too.

114-097	Two Set Color-Coupler	\$2.95 List
114-098	Three Set Color-Coupler	3.95 List
114-099	Four Set Color-Coupler	4.95 List

FREE COUNTER-TOP DISPLAY

An attractive, 3 color display comes free with Color-Couplers at a special introductory price. On your counter, this display will not only catch the eye—it will catch the sale, too!



ADDITIONAL SELLING FEATURES

- Super-reliable Resistive Network
- Built in Strain Relief for Twin Lead
- Decorator Colors—Grey or Cocoa
- Two-way Mounting; Indoors or Out
- Modern Design; Tough, Weatherproof Case

see your



Distributor—today!

AMPHENOL ELECTRONICS CORPORATION *chicago 50, illinois*

meters may be used for voltage checks in a transistor radio, a VTVM is highly recommended because its high input impedance provides better accuracy. A fair degree of accuracy is desired in the measurement of potentials between 0 to 1 volt and 0 to 25 volts.

When taking voltage measurements, remember that one slip of the test probe may ruin a transistor. Because of the close spacing between components in most transistor portables, it's a good idea to use a sharply-pointed probe insulated as shown in Fig. 2. Terminals in the set are usually small, rounded solder joints which are spaced closely together. A needle-point probe is less likely to slip from a smooth contact and will easily penetrate any varnish or lacquer coating the solder junction.

The average service technician is undoubtedly familiar with the basing connections for vacuum tubes. When taking voltage measurements from the bottom of a tube socket, he counts in a clockwise direction from the reference point. Measuring voltages at the elements of a transistor, however, presents somewhat of a new problem. Being able to quickly identify base, collector, and emitter connections on various transistors will definitely speed the troubleshooting process.

Fig. 3 illustrates six of the most popular transistor types currently employed in portable radios. In each case, both a photograph of the transistor and a drawing of its lead positions are given. The most common type, pictured in Fig. 3A, has its base and emitter leads closely spaced at one end of the transistor body, while the collector is positioned at the opposite end. Bearing in mind that the center lead is always the base element, the technician should have little trouble in distinguishing between leads on this type of transistor. Connections for those units given in Figs. 3B, 3D and 3E are determined in a like manner.

The spacing between the three leads of the square-shaped transistor in Fig. 3C is equal. In this case, a red dot is located on the side of the unit adjacent to the collector terminal. The base element lead is located at the center,

20,000 HOURS!

...and still going strong



103 Locked TV "Torture Tests" Prove Westinghouse Tubes Last Longer, Cut Call-Backs!

More than words, this picture proves the superior *quality* of Westinghouse RELIATRON® Tubes. "Torture tested" coast-to-coast in full view in distributor showrooms, 103 standard make TV sets with RELIATRON Tubes are making history! All sets are chained and padlocked. One of these sets has already run an incredible 20,000 hours . . . more than 13 years' average viewing time . . . and still going strong!

All sets tested are exactly like those owned by

your customers—with one important difference. They're equipped with Westinghouse RELIATRON Tubes—the most reliable, most profitable tubes you can sell—bar none!

But see it to believe it! Stop by your Westinghouse Tube Distributor's today and watch famous "Locked TV" roll up even more hours—in the most strenuous TV performance test ever! Your best proof that you *profit much more* when you sell Westinghouse RELIATRON Tubes.



YOU CAN BE SURE...IF IT'S **Westinghouse**
Electronic Tube Division Elmira, New York

SAMS "BEST SELLER" BOOKS

FOR THE TECHNICIAN • STUDENT
EXPERIMENTER • HOBBYIST



USE THIS HANDY ORDER FORM

- Pinpoint TV Troubles in 10 Minutes.** Amazingly practical procedures for solving TV troubles. Includes over 50 time-saving check charts, dozens of diagrams and test Methods, circuit explanations, etc.—a real timesaver for TV repairs. 299 pages; 5½ x 8½"; fully illustrated. Only **\$3.95**
- TV Servicing Guide.** Quick reference guide for Technicians. Trouble symptoms are illustrated by picture tube screen photos and proper repair procedures are clearly described. Covers all sections of the TV circuit. 132 pages; 8½ x 11"; illust. Only **\$2.00**
- Tape Recorders.** Explains recorder theory, tape characteristics, how recorders work; covers motorboard mechanisms, drive motors, volume indicators, bias oscillators, amplifiers, magnetic heads, equalization circuits. 176 pages; 5½ x 8½"; illust. Only **\$2.75**
- Transistor Circuit Handbook.** The authoritative book on transistor types, construction, characteristics, applications, circuitry, techniques for wiring and testing. Covers every phase of the subject. 430 pages; 6 x 9"; illust. Only **\$4.95**
- Hi-Fi Handbook.** Invaluable data on Hi-Fi design, selection and installation, including fidelity, sound theory, analysis of all components (speakers, enclosures, amplifiers, tuners, etc.), systems design, proper selection and installation. 240 pages; 5½ x 8½"; illust. Only **\$3.00**
- Servicing AGC Systems.** Describes operation and circuit variations of AGC systems; explains applicable servicing techniques. Illustrated by actual case histories and photos of symptoms. 132 pages; 5½ x 8½"; illust. Only **\$1.75**
- Learning Electricity Fundamentals.** The complete, fascinating story of electricity; history, electron theory, static electricity, uses of switches and fuses, resistance, Ohm's Law, magnetism, electro-magnetism, transformers, generators and motors, circuits and controls, practical wiring, etc. 416 pages; 6 x 9"; illust. Only **\$5.95**
- Transistors.** A very practical, complete book on Transistors and their application in TV-Radio-Electronics. Explains theory, circuitry, installation, testing techniques and servicing. 100 pages; 5½ x 8½"; illust. Only **\$1.50**
- Color Television.** An outstanding training course for Technicians. Covers principles of the color TV system; color receiver circuits; installation and servicing of color receivers. Includes color blocks outlining use of color test equipment. 260 pages; 8½ x 11"; profusely illustrated. Only **\$6.95**
- Electronic Metal Locators.** Explains basic types and their operation; tells how to construct your own units; describes applications. Covers interesting uses in industry as well as in prospecting and mine location. 124 pages; 5½ x 8½"; illust. Only **\$2.50**

HOWARD W. SAMS & CO., INC.

Order from your Parts Jobber, or mail to
Howard W. Sams & Co., Dept. 3 K7
2201 E. 46th St., Indianapolis 5, Ind.

Send books checked above. My (check) (money order)
for \$..... is enclosed.

Name _____

Address _____

City _____ Zone _____ State _____

(outside U. S. A. priced slightly higher)

and the emitter lead is closest to the uncoded side of the transistor.

A code system is also used for the rounded style pictured in Fig. 3F. Here, a red line, painted on the body of the unit, lies adjacent to the collector terminal. In a clockwise direction from this point, one finds the base and emitter leads in that order when viewing the transistor from the bottom or lead end.

After eliminating the possibility of a weak or dead battery, the technician might decide to make a spot check of the AGC voltage. (For transistor radios, the term AGC is employed rather than AVC.) If the AGC system is operating properly, the voltage between the base and emitter elements of the controlled IF stages should vary as the tuning gang is rotated, indicating the general condition of the circuits up to and including the detector.

Using a reliable source of service information, one should be able to compare given voltage values with readings obtained from base, collector and emitter elements. Typical operating voltages for a conventional IF or converter stage are given in the diagram of Fig. 4. Two voltage ranges are given for each element—one for n-p-n and one for p-n-p type transistors. The negative voltage readings in Fig. 4 also typify those found in audio amplifier and output stages using p-n-p transistors. Fig. 5 gives typical voltage ranges for p-n-p amplifier and output stages when the collector returns to chassis ground rather than to the negative battery terminal.

Voltage values for n-p-n audio stages, where the collector returns to the positive battery terminal, are shown in the circuit of Fig. 6. All voltages given in Figs. 4, 5, and 6 are based on averages obtained from commercial portables employing the popular 9-volt battery supply.

If an accurate and sensitive voltmeter is not available, the technician can check the operation of a transistor circuit by measuring collector or emitter current. This procedure, however, requires a low-range milliammeter and additional reference data for comparative purposes.

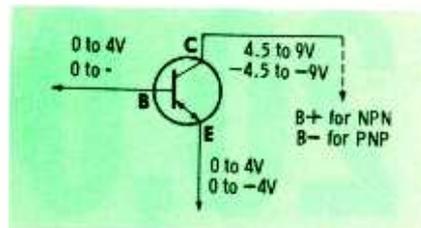


Fig. 4. Typical DC voltages for converter, IF, and some audio circuits.

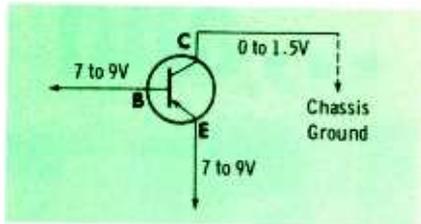


Fig. 5. Operating voltages for a conventional p-n-p audio stage.

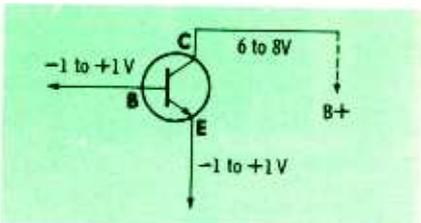


Fig. 6. Typical voltages for audio circuits employing n-p-n type transistors.

Resistance Measurements

Normally, when servicing a radio or TV receiver, the technician will seldom concern himself with the possibility of damaging a circuit component with an ordinary ohmmeter. When troubleshooting transistor circuitry, however, look out! There are two major components which can be permanently damaged by the internal battery voltage of what might be termed an ordinary ohmmeter. Transistors, for one, are particularly sensitive in this respect. The emitter-base circuit, for example, is biased in a forward direction and presents a relatively low-impedance path. Voltages which exceed the specified values should never be applied to the unit, not even for an instant. If they are, breakdowns will occur at the junctions of the dissimilar metals and cause permanent damage to the unit.

If the applied voltage rating of the collector element (known as the Zener voltage) is exceeded, the transistor may rupture and cause excessive reverse current to flow. The collector-to-emitter breakdown voltage for transistors employed in the average portable



\$169.95 Net


INDUCED WAVEFORM ANALYZER

MODEL 850

Top-O'-Chassis Troubleshooting . . . greatest servicing advance in years!

Perfect for Portable TV

Localizes defective stage in entire TV receiver in less than 5 minutes—without a direct circuit connection. Adapts any 'scope for spotting defects quickly by the modern, easy-to-use Induced Waveform Method. Unique, Phantom Detector Probe makes any tube a convenient test point. Just slip probe successively over each tube, then view and trace waveforms on scope from antenna thru RF, IF, audio, video & sync. Speeds servicing of TV, radios, amplifiers, instruments, industrial and laboratory equipment tool Compatible for color. Phone jack for audio monitoring.

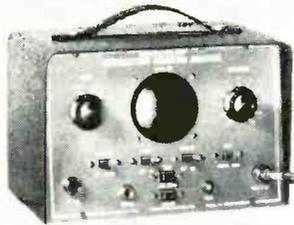

\$89.95 Net

INTERMITTENT CONDITION ANALYZER

MODEL 828

Pinpoints Intermittents without waiting...cooking...or freezing.

Exclusive new principle makes any TV or radio super-sensitive to intermittents and noisy components . . . without waiting for breakdowns. Saves time and bench space. Cuts callbacks by detecting borderline components before they fail. Special Wintronix Probe and capacity pickup attachments let you hear intermittents thru built-in speaker.



\$79.95 Net

AGC CIRCUIT ANALYZER


MODEL 825

AGC Troubles Won't Fool You Any More!

Saves hours by detecting hard-to-find AGC faults that may look like sync trouble, etc. Furnishes standard, adjustable r-f signal to antenna; monitors AGC action; checks AGC buss for opens and shorts; measures action of gated pulse systems; supplies AGC bias to restore operation by substitution.

Wintronix ANALYZERS

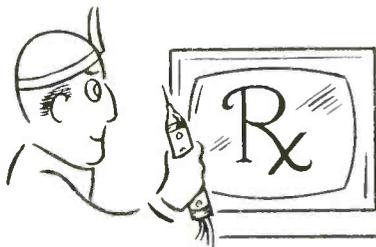Electronic "Wonder Drugs" for Troubleshooting Pains



Here are the instruments you need to diagnose ailments fast and profitably in today's complicated—often inaccessible—TV, radio & hi-fi sets.

These four Wintronix *Analyzers* swiftly turn wasted trouble-shooting time into profitable parts replacement time on more and more jobs. Obscure radio and TV faults get tracked down fast by Winston's specialized reference signals and measurements. Like X-rays, they quickly give a complete picture of circuit operation—at far lower cost, with fewer circuit connections, and with less set-up time than with separate conventional instruments.

Today, issue a prescription to yourself for a healthier servicing business—see and try these new Wintronix *Analyzers* at your local parts distributor or write for detailed literature.

SWEEP CIRCUIT ANALYZER

MODEL 820

Rapid, Dynamic Sweep Testing

\$69.95 Net




Completely troubleshoots entire sweep circuits and restores raster by substituting for defective stage. Tests all flybacks and yokes for continuity and shorts. Self-calibrating. Compatible for color.

Model 915/960 Adapter converts Model 820 to a Sync Circuit Analyzer for signal substitution of vertical and horizontal sync pulses.

\$14.95 Net

WINSTON ELECTRONICS INC.

4312 Main Street, Philadelphia 27, Pa.

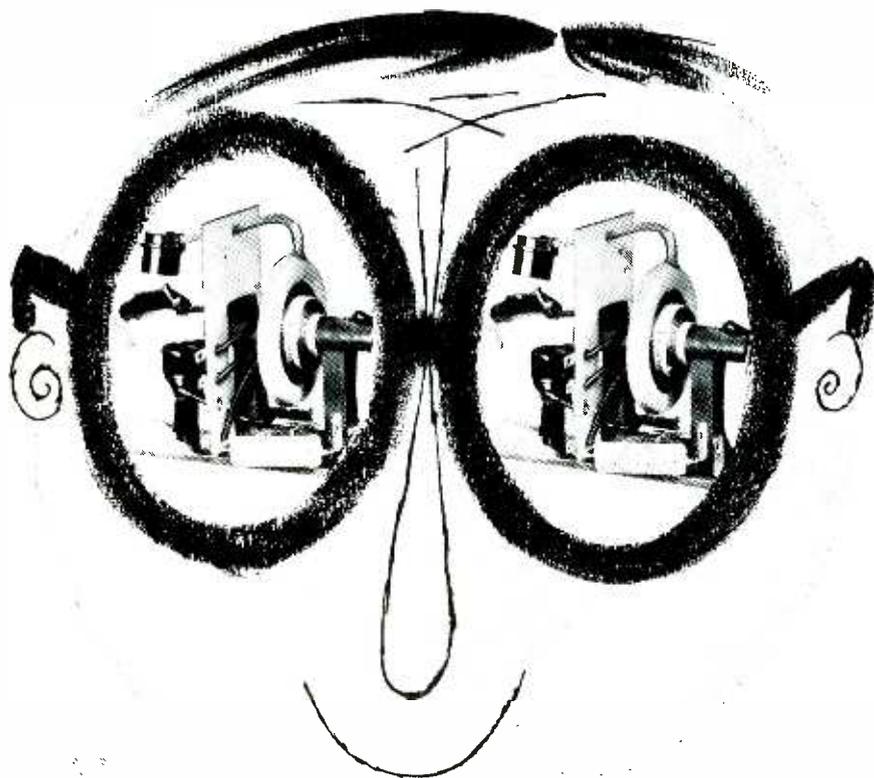

Seeing Double?

**SURE...THEY LOOK ALIKE BECAUSE
THEY ARE EXACTLY ALIKE**

Each Merit product of the same type is exactly the same as another—both in construction and appearance.

COMPARE IT WITH MERIT

Take a Merit product off the shelf. Compare it with any other similar product on the market. You'll find Merit *is* superior!

COMPARE IT WITH MERIT

Only Merit live tests its products to insure uniform quality.



MERIT


MERIT COIL AND TRANSFORMER CORP
4427 North Clark Street · Chicago 40, Illinois

radio is from 10 to 25 volts. This might indicate that the use of an ohmmeter having an internal battery voltage lower than 10 volts is permissible. However, the ratings of a few transistors are as low as 4.5 to 6 volts. If a meter operates on an internal battery voltage higher than 3 volts, it's a good idea to remove all transistors from the circuit before making resistance measurements.

The other circuit components, which are perhaps even more prone to damage by improper voltages, are the miniature electrolytic capacitors (see Fig. 7). This stands to reason, for naturally the working voltages of these small units are lower by far than those of conventional electrolytics found in equipment using 100- to 300-volt power supplies. Generally, the ratings of the electrolytic capacitors in portable transistor radios range from 3 to 10 volts. Some receivers, however, may incorporate units rated as low as 2 volts and as high as 25 volts.

When connecting an ohmmeter across an electrolytic or across other components in a circuit containing these units, one should use a meter with an internal battery voltage which is lower than the rated value of the units involved. Never attempt to test one of these electrolytics with a conventional capacitor bridge. The potentials used in this type of instrument exceed the voltage ratings of the capacitors.

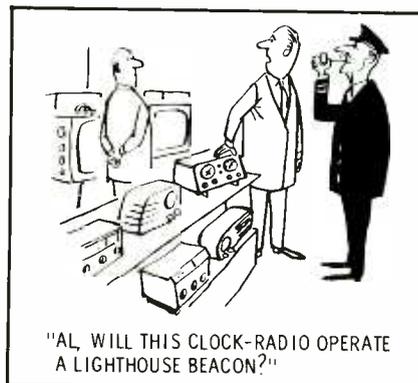Another important point to keep in mind is that these capacitors are also polarized. Placing a voltage of the wrong polarity across an electrolytic is very likely to damage the unit. The technician should therefore check the polarity of his ohmmeter connections. After selecting the desired ohms




Bull's-eye every time!

We hit the target again . . .
with this new, modern version of the
most wanted service-test instrument.

Pyramid introduces the CRA-2 Capacitor-Resistor Analyzer, a versatile, up-to-date, moderately priced test instrument. The CRA-2 is the perfect multi-purpose analyzer for the technician, serviceman and engineer, in industrial and military electronics, black and white, and color television, and all related fields.

The guesswork has been removed from circuit trouble shooting. When making leakage-current measurements, the values are read directly from the meter while the rated operating voltage is applied to the capacitor. A vacuum-tube ohmmeter circuit displays accurate insulation-resistance values on the meter for many types of capacitors. The extended range calibrated power factor control permits power factor measurements of electrolytic capacitors rated as low as 6 volts DC working and as high as 600 volts DC working. This special "QUICK CHECK" circuit performs rapid "IN CIRCUIT" test for short, open, intermittent high RF impedance and high power factor without removing or disconnecting the component from its operating circuit.

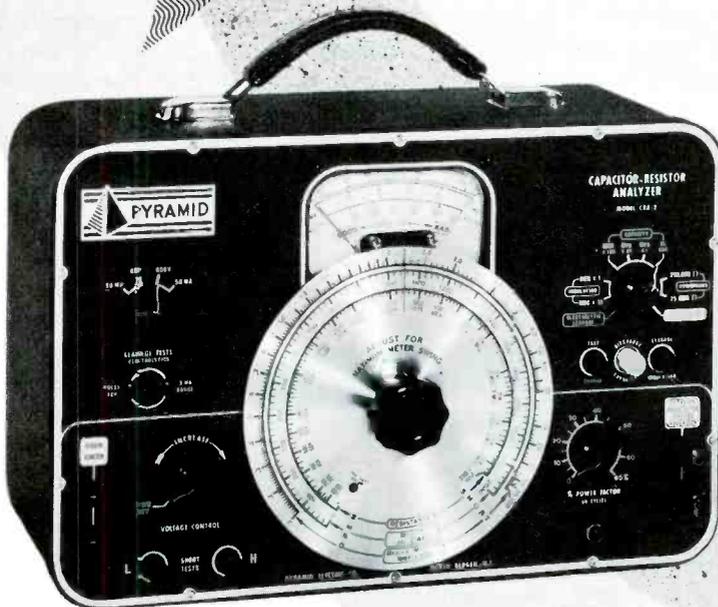

FEATURES

- "Quick Check" in circuit test for Open Circuits. Short Circuits. Intermittents. High RF Impedance. High Power Factor.
- Speedily and accurately checks: Capacitance. Power Factor. Resistance. Insulation-Resistance. Leakage Current.
- Precision meter for accurate readings of leakage current, applied voltage and insulation resistance.
- Combination Wien and Wheatstone bridge.
- Accurate vacuum-tube meter circuit.
- Parts of the highest quality are used. Wire and wiring meet military specifications.

Examine it today
Being introduced by leading Electronic Parts Distributors

PYRAMID ELECTRIC COMPANY

1445 Hudson Blvd., North Bergen, New Jersey

industrial
electronic
servicing

plus

OHMITE®
quality
components

equals

satisfied customers
and higher profits
for YOU

Industrial electronic servicing is profitable business for you. Especially when you stock and replace with dependable Ohmite components... the line your industrial customers know and prefer. With Ohmite you eliminate call backs, insure quality replacement, build customer satisfaction, and increase your industrial (and home) electronic servicing business. Service such industrial equipment as mobile radio, aircraft and marine radar and radio, electronic controls for factory processes and automation, industrial P.A. and intercom systems, and—medical and dental electronics. It's a big market!



**BROWN DEVIL®
RESISTORS**

Vitreous-enamelled.
In 5, 10, and
20-watt sizes.

**MOLDED
COMPOSITION
POTENTIOMETERS
TYPE AB**



Resistance material is solid
molded, noise-free.
Rated at 2 watts.

**LITTLE DEVIL®
COMPOSITION
RESISTORS**



Meet all
MIL-R-11A
requirements.
Available in 1/2,
1, and 2-watt sizes
in all standard
RETMA values.

Also:

- RHEOSTATS
- PRECISION
RESISTORS
- RELAYS
- R.F. CHOKES

BE RIGHT WITH

OHMITE®

DEPENDABLE RESISTANCE UNITS

OHMITE MANUFACTURING CO.
3644 Howard Street, Skokie, Illinois

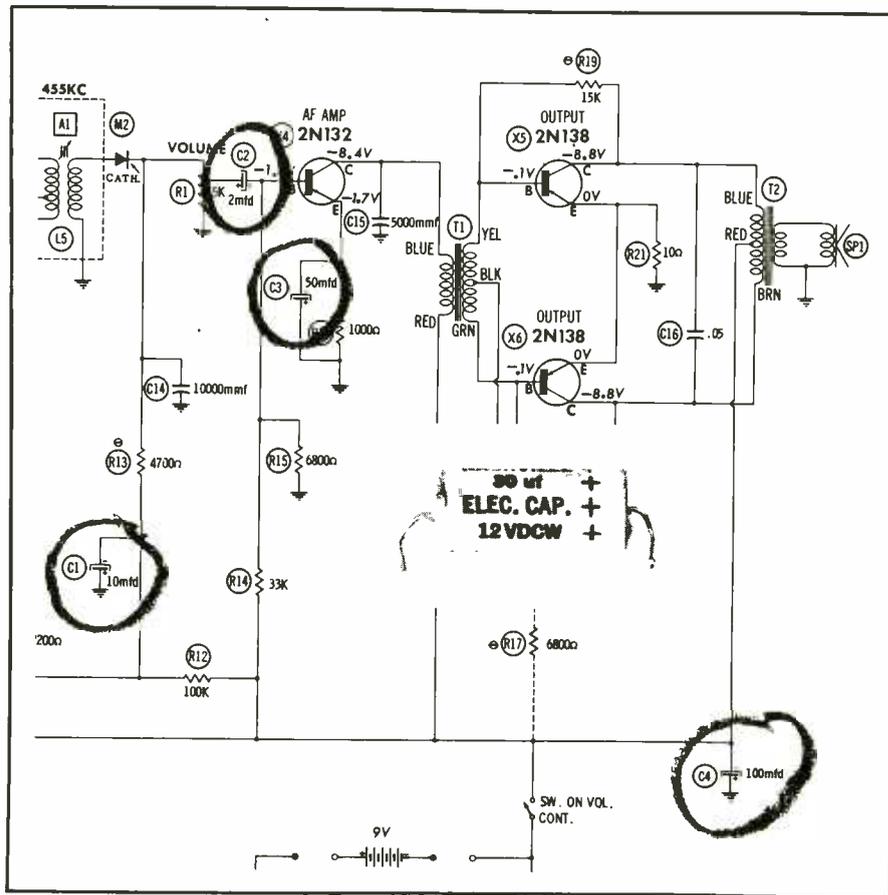


Fig. 7. Low-voltage electrolytics are found in all transistor portables.

scale, merely connect a voltmeter across the two test leads and determine which lead is positive and which is negative. When working on transistorized equipment, keep the red test lead in the positive meter terminal and the black lead in the negative terminal. This will help you to determine immediately the polarity applied to any circuit under test.

Resistance measurements in any circuit containing a transistor will often result in misleading indications. Unlike a vacuum tube, a transistor will conduct with only a small voltage applied to its elements. Therefore, if a transistor is

in parallel with a component under test, the measured resistance may be much lower than anticipated. Resistance readings in a transistor circuit will also depend on the value and polarity of the applied test voltage. Reversing ohmmeter leads may result in a reading that is 10 to 20 times higher or lower than the original reading.

At this point, the technician might wonder exactly how these various limitations will affect him and his particular ohmmeter. The average multimeter or VOM usually makes use of a 1.5- to 3-volt battery on resistance scales of


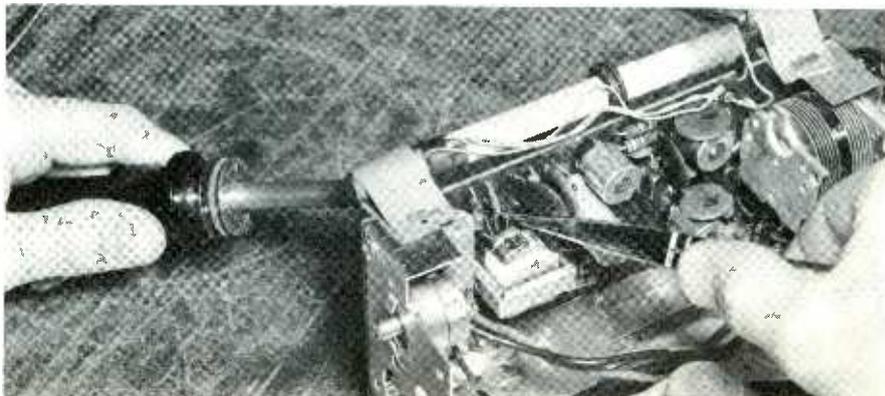


Fig. 8. Use of a heat sink is very important when soldering transistor leads.


Electro-Voice® POWER-POINT

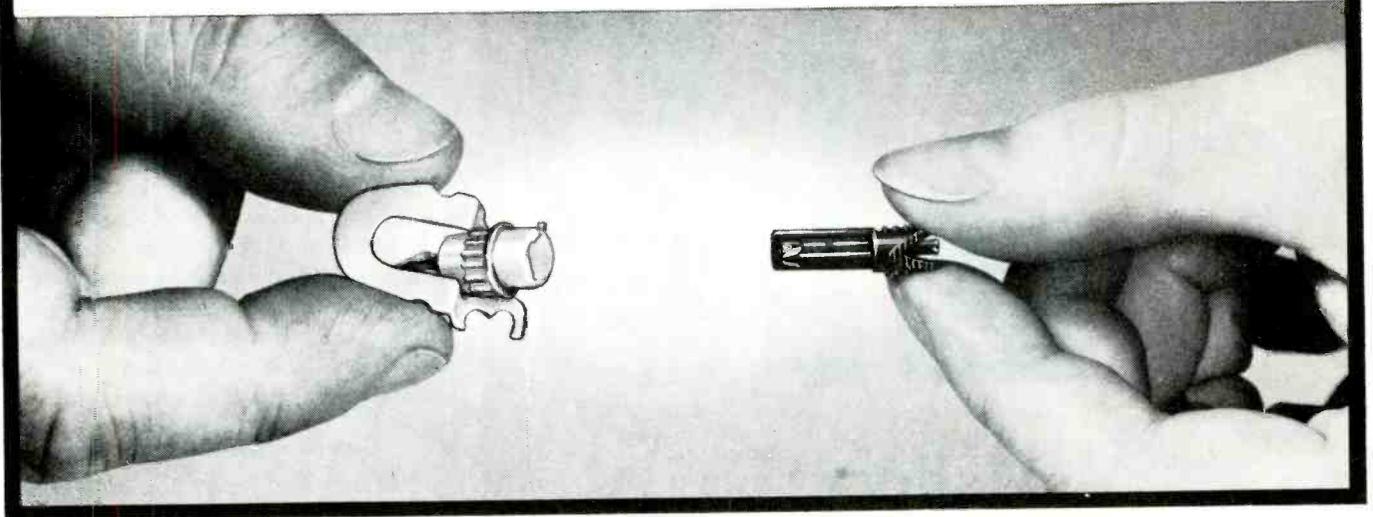For Profit and Customer Service Without Problems!



POWER-POINT is the unique, easily installed, miniaturized unit containing BOTH a fresh ceramic cartridge and jeweled playing tips. You sell **POWER-POINTS** for LESS than the cost of a separate cartridge or two comparable phono needles alone! Most models \$3.75 list. Only $\frac{3}{4}$ " long and less than $\frac{1}{2}$ " in diameter, they're in color-coded nylon cases, blister-packed in plastic to keep them clean, factory-fresh, easy to handle.

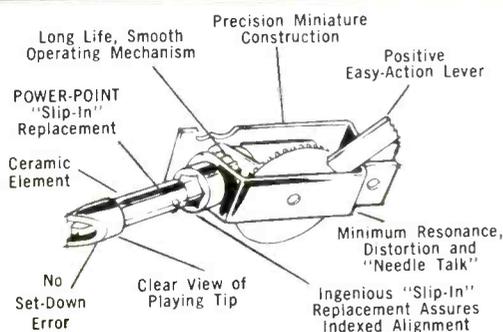YOU install the mount. Once that's done, the **CUSTOMER** can remove and replace units in a matter of seconds. You get the replacement business but none of the grief. You stock just three types of mounts and seven types of **POWER-POINT** units to service virtually all modern phonos. You save on inventory costs, conserve shelf space, take no risk of obsolescence.



Typical **POWER-POINT** and Turnover Mount
POWER-POINT
Case—Nylon
Element—Ceramic
Tip Material—Superior Synthetic Sapphire or Natural Diamond
Tracking Force—5 to 8 grams
Net Weight—300 milligrams
Terminals—Beryllium Copper, Self-cleaning Type
Load—1 meg. 100 mmfd
Compliance—1 x 10.8 cm/dyne
Average Output Voltage at 1000 cps
Test Record RCA 12-5-49V.85 Volt Col. 10004M 1.75 Volt
PT1 Mount
Material—Steel and Nylon
Finish—Cadmium Plate
Connector Size—.050"

THE MARKET IS BIG: OVER TWO MILLION NEW PHONOGRAPHS USE **POWER-POINTS** AS ORIGINAL EQUIPMENT! THE PROFITS ARE BIG—AND E-V HELPS YOU SELL WITH THESE MERCHANDISING AIDS.



Fact-cramped folder tells the full **POWER-POINT** story. Ask for Bulletin No. 223. Colorful, compelling envelope stuffer for mailing. Bulletin No. 225. Write Dept. R710.



Plastic-sealed blister-packed **Power-Points** are always in perfect condition. Package gives model identification, color-coding and instructions.

These are the color-coded **POWER-POINT** units, actual size



RED
Model 51-1,
two 1-mil
sapphire tips,
\$3.95 list.



GREEN
Model 52-2,
two 2-mil
sapphire tips,
\$3.95 list.



BLACK
Model 53-3,
two 3-mil
sapphire tips,
\$3.95 list.



BLUE
Model 55,
one 1-mil,
one 3-mil
sapphire tip,
\$3.95 list.



ORANGE
Model 56DS,
one 1-mil
diamond,
one 3-mil
sapphire tip,
\$21.50 list.



WHITE
Model 76S,
one 1-mil,
one 3-mil
sapphire tip,
\$4.20 list.



PINK
Model 76DS,
one 1-mil
diamond,
one 3-mil
sapphire tip,
\$21.50 list.

CALL YOUR
E-V DISTRIBUTOR
TODAY!

Electro-Voice

ELECTRO-VOICE, INC. • Buchanan, Michigan
Export: 13 East 40th Street, New York 16,
U.S.A. Cables: ARLAB

Tops in performance and value
for today's growing market...




Mallory *Mercury* Batteries . . .

To get your share of the growing, profitable battery market—sell the batteries that helped make the new transistor radios possible. Amazing Mercury Batteries, pioneered by Mallory, lead all others in small size, long life, fade-free performance. No wonder they're the leading choice of set manufacturers and distributors!

Mallory Mercury Batteries stay at full strength for months on the shelf. They last far longer and cost far less per hour of use. They deliver the unequalled performance that builds repeat sales. And they're backed by consistent Mallory promotion and strong Mallory advertising in the Saturday Evening Post, Time, Newsweek and Business Week.

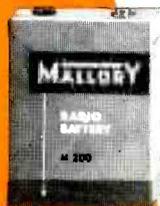Get full facts today from your Mallory distributor, on the TWIN-LINE of Mallory Mercury and Zinc-Carbon Batteries... leaders in profit and performance for both transistor and vacuum-tube portable radios.



For vacuum tube radios—Mallory Zinc-Carbon Batteries.

- Capacitors
- Vibrators
- Resistors
- Power Supplies
- Mercury and Zinc-Carbon Batteries
- Controls
- Switches
- Rectifiers
- Filters

P. R. MALLORY & CO. Inc.
MALLORY

P. R. MALLORY & CO. Inc., INDIANAPOLIS 6, INDIANA


R × 10,000 or less. However, when these same meters are placed on a high-ohms range such as R × 100,000, they may use a supply as high as 30 volts. Applying potentials of this value to transistors or low-voltage electrolytics is asking for trouble.

Many commercial VTVM's have provisions for resistive measurements, and the internal battery supply very seldom exceeds 3 volts for any range. Taking advantage of the internal vacuum-tube amplifier, these meters are highly recommended for both voltage and resistance measurements in transistor circuitry. Regardless of the type of meter employed, however, the technician should always be aware of its voltage values and polarities.

Component Replacement

After one locates a defective component in a transistor portable, a difficult task still remains. Replacing certain components will usually require special tools, a different soldering technique and a good deal of patience. This is especially true for parts having several lugs or contacts soldered to a small wiring board. Component leads or mounting lugs are often bent or twisted, and the removal of these parts requires a procedure similar to that used on can-type electrolytics, only on a smaller and more delicate scale.

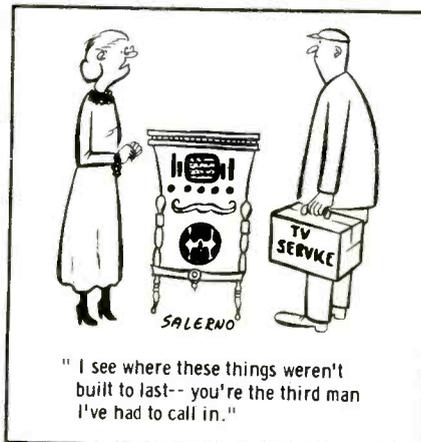As the technician may know from working with any printed wiring assembly, resistors and capacitors with short wire leads may be cut so that the replacement can be soldered to part of the remaining leads. In some cases, it may be necessary to crush the body of the component so that the old leads will be long enough.



Transistors, like conventional germanium diodes, are extremely sensitive to heat. If they are the plug-in variety, always remove them before soldering associated socket connections. Should they be soldered into the circuit, it's a good idea to protect them in some manner before applying heat. One of the easiest ways to dissipate some of the heat is to grasp the lead with a pair of conventional long-nose pliers as demonstrated in Fig. 8. If space is limited, one might use needle-nose pliers or a heavy piece of copper wire.

Never remove or install a component in a transistor radio while the set is on, as surge currents may permanently damage a transistor. When replacing a relatively large component, the technician may have trouble melting the solder at some of the larger mountings with a small, low-wattage iron. It is often more advantageous to use a larger iron to heat the joint for only an instant rather than to apply a small iron for any length of time.

Although the experienced technician may be extremely careful when working on these small wiring boards, at some time or another he will probably use too much solder or perhaps slip with a probe or iron and cause one of the printed conductors to blow. If this occurs, however, the break can usually be repaired by bridging it with a piece of hookup wire. After completing this type of repair, always check to see that all shorts have been removed before restoring power to the circuit.

Troubleshooting Check List

1. Make a complete visual inspection first.
2. Use an accurate VTVM for all voltage measurements.
3. Remember, transistors can be damaged by applying too much heat or subjecting them to improper voltages.
4. Know your ohmmeter and the supply voltage it utilizes.
5. Avoid resistance measurements around low-voltage electrolytic capacitors.
6. When replacing components, solder quickly and use some form of heat sink to protect transistors. ▲

... another
P. R. MALLORY & CO. INC.
MALLORY
service-engineered
product



MALLORY VIBRATORS

to meet every service requirement

1

FOR THE VERY BEST IN PERFORMANCE...

Mallory Gold Label Vibrators are the result of over 27 years of vibrator pioneering and leadership. Employing the exclusive Mallory buttonless contact design, they eliminate problems of sticking contacts... insure positive starting... provide far longer life... are unbelievably quiet. For utmost dependability, and to build your reputation for service, make Mallory Gold Label Vibrators your standard of quality.

Depend on Mallory
for vibrator dependability
—for any job



2

FOR ECONOMY JOBS...

The Mallory Highlander is a new line designed expressly for the jobs that must be done at a lower price. It delivers trouble-free service longer than any vibrator in its price class—second only to the Gold Label line. Ask your Distributor for the new Mallory Highlander—in the handy new 10-pack carton.

P. R. MALLORY & CO. Inc.
MALLORY

P. R. MALLORY & CO. Inc., INDIANAPOLIS 6, INDIANA

- Capacitors
- Vibrators
- Resistors
- Power Supplies
- Mercury and Zinc-Carbon Batteries
- Controls
- Switches
- Rectifiers
- Filters



QUICKER SERVICING

by Calvin C. Young, Jr.

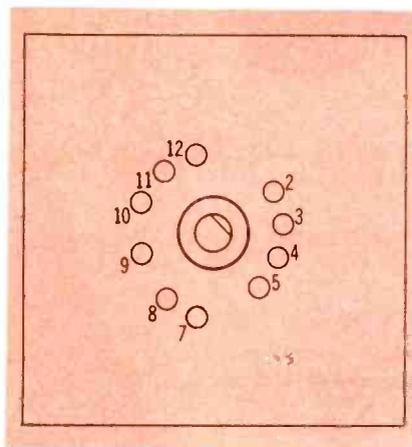


Fig. 1. Front of RCA tuner showing local oscillator adjustments.

Oscillator Adjustments for Switch Type Tuners

The local oscillator in turret tuners may be expediently adjusted by simply switching to the active channels and turning the oscillator slugs in the corresponding strips. This procedure will not produce consistent results on the switch type tuner. Best results in this case are obtained by following the alignment procedure recommended by the manufacturer.

Naturally, this can be done only in the shop where a signal generator capable of producing a swept RF signal at each channel frequency and accurate marker signals at the video and sound carrier frequencies of each channel, plus an oscilloscope, are available.

It is generally acknowledged that suitable results can be obtained in adjusting the local oscillator without using any test equipment, provided the proper procedure is followed. In step-by-step form, this procedure is as follows:

1. Set the fine tuning control to the center of its range.
2. Turn the channel selector to the highest channel received in the area. If a rotator is employed in the antenna system, be sure that the antenna is pointing toward the station being adjusted.
3. Adjust the local oscillator screw for best picture and sound reception.
4. Turn the channel selector successively to the next highest channels and adjust as in step 3 until all stations have been correctly tuned.

This procedure works very well until you're called upon to adjust the local oscillator for channels 6 or 13, and find that the adjustments are not accessible from the front of the tuner (see Fig. 1). If you are in the customer's home and have the receiver repaired except for the oscillator adjustments, you may be torn between two desires—wanting to get the receiver operating the way it should and not wanting to take the set to the shop for what is seemingly a minor adjustment procedure.

Fortunately, there are adjustments for these channels and they are located in almost identical positions on different models. Channel 6 (Fig. 2) is located on the left side of the tuner and is a variable inductor which is reached through the hole nearest the front of the tuner. The channel 13 adjustment is on top of the tuner (Fig. 3) and is located immediately to the rear of the fine tuning capacitor.

The only trick is knowing where the adjustments are located; the adjustment procedure is identical to the one outlined above.

Fine Tuning Belt

In RCA tuners with this type of local oscillator adjustment setup, a belt arrangement is employed in the fine tuning assembly. It is not always possible to obtain replacement belts on short notice; however, a pair of shoe strings serves as a good makeshift substitute, provided a bottle of dial cord dressing is also available. You simply make two belts

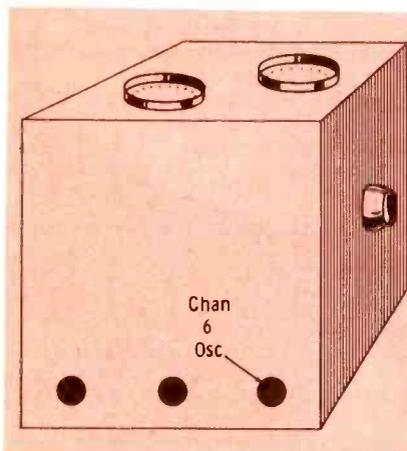


Fig. 2. Left side of RCA Tuner showing location of channel 6 adjustment.

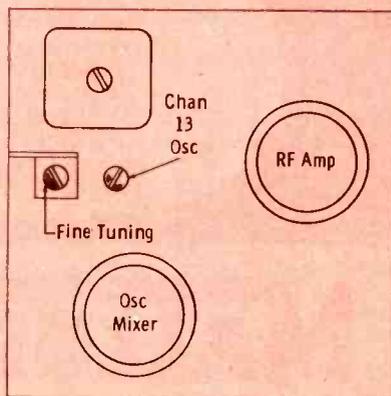


Fig. 3. Channel 13 oscillator adjustment on top of tuner.


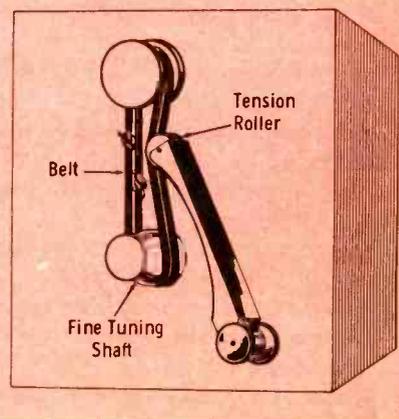



Fig. 4. Belt drive for fine tuning replaced with "treated" shoe strings.

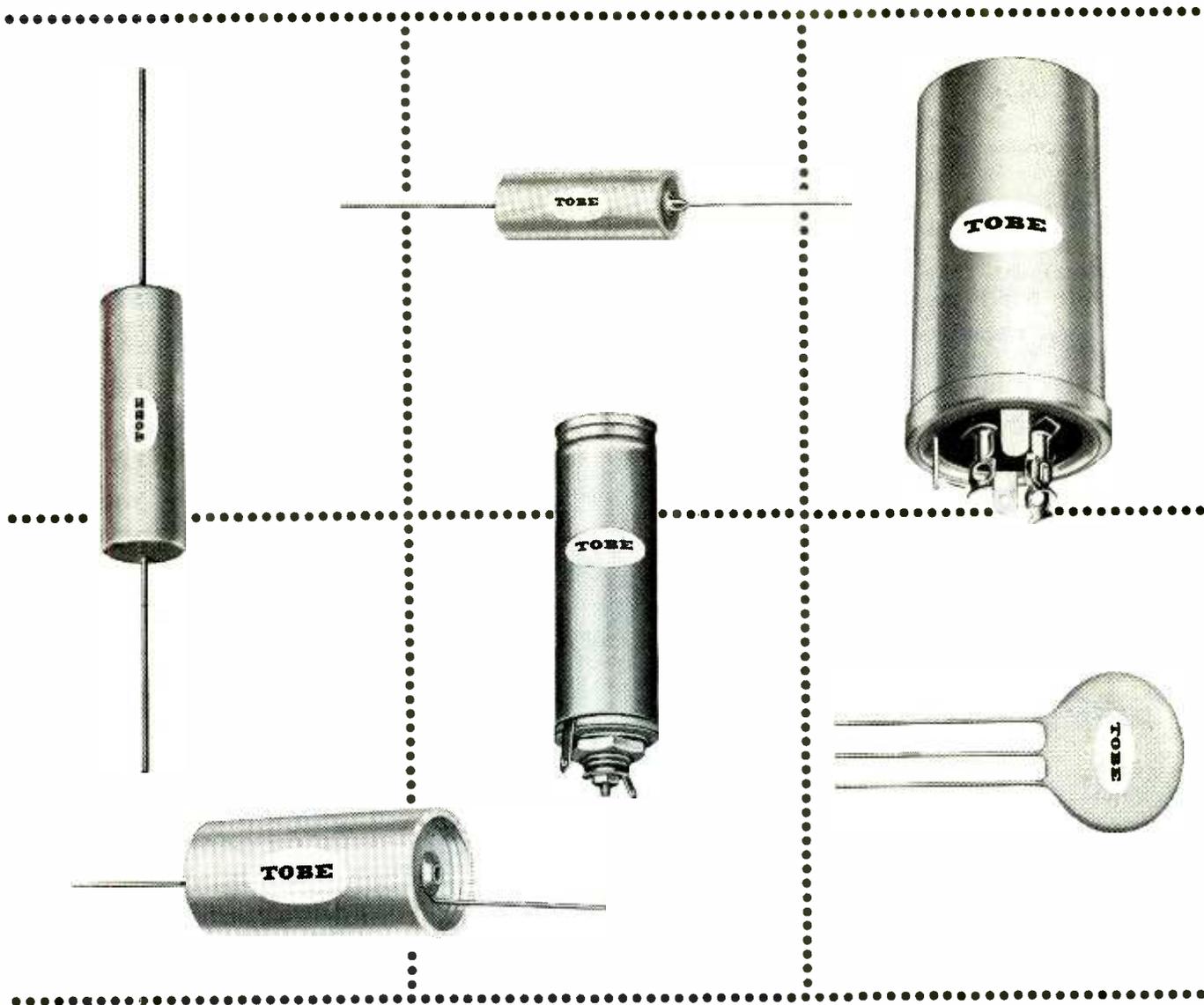

thousands of servicemen have happily discovered

TOBE QUALITY SERVICE CAPACITORS

have you?

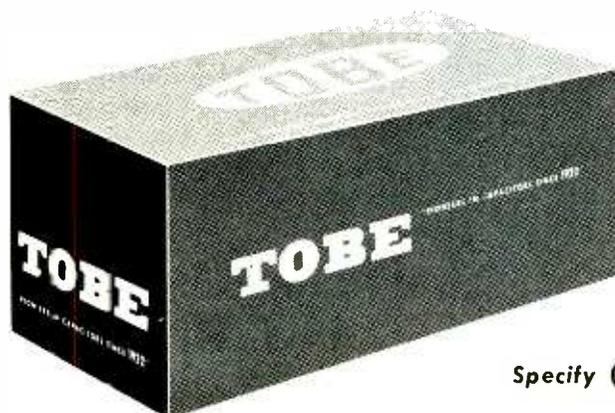

Specify **TOBE** Capacitors • Pioneers since 1922

of the shoe strings (Fig. 4) and then apply a liberal coating of the dressing to the entire "shoe-string belt." This arrangement has been known to give many months of trouble-free service and should also work out for emergency repairs on other receivers which use belt drives in tuning applications.

Replacement Yokes and Brass Width Sleeves

By now most technicians have encountered a TV receiver that employs a brass width sleeve. This

sleeve is slid into the yoke core to reduce width and out to increase the width. A special lining is used around the inside of the original yoke (Fig. 5) to prevent this width sleeve from coming in contact with the yoke windings and causing a short. This lining is not furnished with standard replacement yokes, but a lining which will serve the purpose can be made out of fish paper. A piece about 2" wide and 4.7" long should work satisfactorily for most replacement yokes.


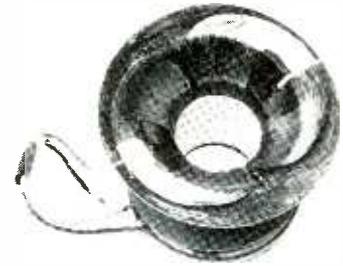


Fig. 5. Lining in yoke to prevent shorts through contact with width sleeve.

QUAM

Adjust-a-Cone®

SPEAKERS

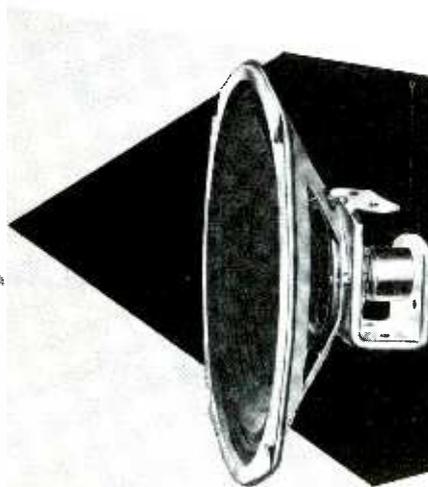

are the
SAME PRICE
but they
COST LESS

They cost less because they fit right the first time . . . and they work right . . . the first time.

With Quam Adjust-a-Cone Speakers there are no callbacks—caused by defective or non-fitting speakers—to eat up your profits.

Remember: a guarantee does not pay for your time or protect your reputation and customer goodwill . . . so use Quam, the "no-callback" speaker.

*ask for QUAM,
the quality line,
for all your speaker needs*

QUAM-NICHOLS COMPANY
234 EAST MARQUETTE ROAD • CHICAGO 37, ILLINOIS

Shielded Scope Probe

The oscilloscope probe shown in Fig. 6 is one of three variations being produced by Scope-Probe



Fig. 6. Scope-Probe Model 10 type LC.

Co. of San Fernando, Calif. These probes (low-capacity, crystal-diode and isolation-direct) all feature completely shielded coaxial construction and have a plunger-type hook-on tip. This means that a very minimum of extraneous signal pickup will be experienced, permitting the examination of even very low-amplitude waveforms.


The hook-on tip features an insulated sleeve which permits the probe to be connected into a circuit without the danger of introducing a short. The low-capacity Model 10 features a variable capacitor which can be adjusted for an impedance match between the probe and the oscilloscope, thus insuring minimum distortion of the signals passed through the probe. No adjustments are required with either the crystal-diode or isolation-direct types. ▲

how long would it take you to solve this service problem?

PHOTOFACT

helps you lick problems
like this in just minutes
for only *2½¢ per model!

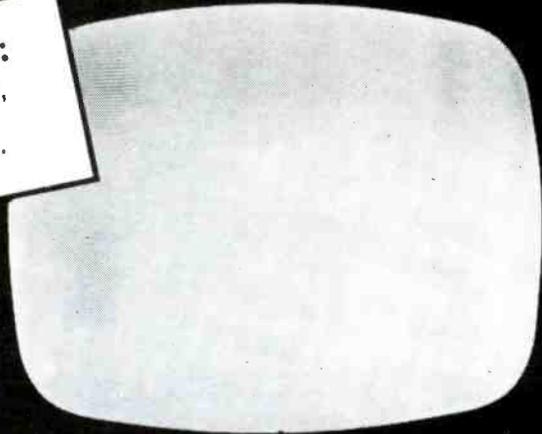SYMPTOM:
Raster, No Sound,
No Picture,
and No Snow . . .




Let's take a look at this problem: A condition such as this can exist only when there is no signal reaching the picture tube or the audio output stage. Using the Tuner Service data (found in every PHOTOFACT TV Folder), first isolate the trouble by connecting an amplitude-modulated signal to the mixer-grid test point "D." The appearance of one or more black bars on the face of the tube would indicate that the trouble is probably in the tuner. So look for the following possible causes:

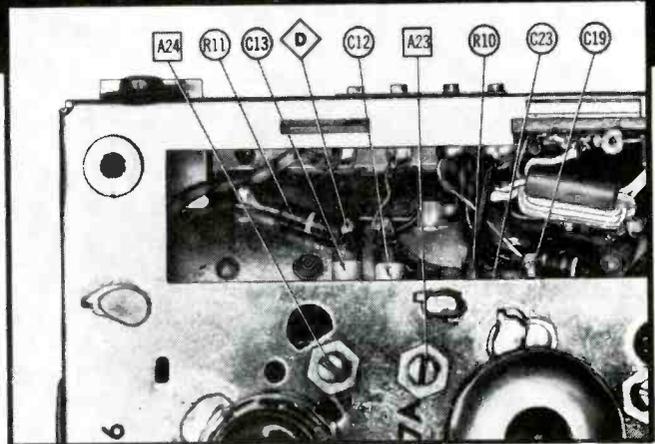1. Defective oscillator-mixer tube
2. Defective RF amplifier tube
3. Open plate-load resistor in the oscillator stage
4. Failure of the feedback capacitor in the oscillator stage
5. Open decoupling resistor
6. Dirty or faulty contacts
7. Cold solder joint

Using the applicable PHOTOFACT Folder you can troubleshoot and solve this problem in minutes. Here's how:

Check the oscillator-mixer and RF amplifier tubes. Tubes okay?—then: Check voltages on the tube pins (they're right on the schematic) for open oscillator plate-load



(Based on an actual case history taken from the Howard W. Sams book "TV Servicing Guide")

resistor, open RF decoupling resistor, faulty feedback capacitor, dirty switch contacts or cold solder joints.

Every PHOTOFACT Television Folder contains complete detailed information on Tuners, including separate Schematics, separate Keyed Chassis Photographs, Parts Lists, Alignment Points, Test Points, and Field Service Adjustments that will help you quickly locate the proper parts to replace and tell you how to do a touchup or thorough alignment job after making the necessary repairs. These features are a *plus* exclusive in PHOTOFACT.

Whatever your problem or favorite servicing procedure may be—you will always find all of the information you need at your fingertips in PHOTOFACT. For only *2½¢ per model, PHOTOFACT helps you solve your service problems in just minutes—helps you service more sets and earn more daily!

*Based on the average number of models covered in a single set of PHOTOFACT Folders.



**MONEY BACK
GUARANTEE!**

Got a tough repair? Try this—at Howard W. Sams' own risk: see your Parts Distributor and buy the proper PHOTOFACT Folder Set covering the receiver. Then use it on the actual repair. If PHOTOFACT doesn't save you time, doesn't make the job easier and more profitable for you, Howard W. Sams wants you to return the complete Folder Set direct to him and he'll refund your purchase price promptly. **GET THE PROOF FOR YOURSELF—TRY PHOTOFACT NOW!**

FREE



**FOR SERVICE
TECHNICIANS ONLY**

Fill out and mail coupon today for Free subscription to the Sams Photofact Index—your up-to-date guide to virtually any receiver model ever to come into your shop. Send coupon now.

HOWARD W. SAMS & CO., INC.

Howard W. Sams & Co., Inc.
2201 E. 46th St. Indianapolis 5, Ind.

Put me on your mailing list to receive the Sams Photofact Index and Supplements. My (letterhead) (business card) is attached.

I'm a Service Technician: full time; part time

My Distributor is: _____


Shop Name _____

Attn: _____

Address: _____

City _____ Zone _____ State _____

inside TV tuners

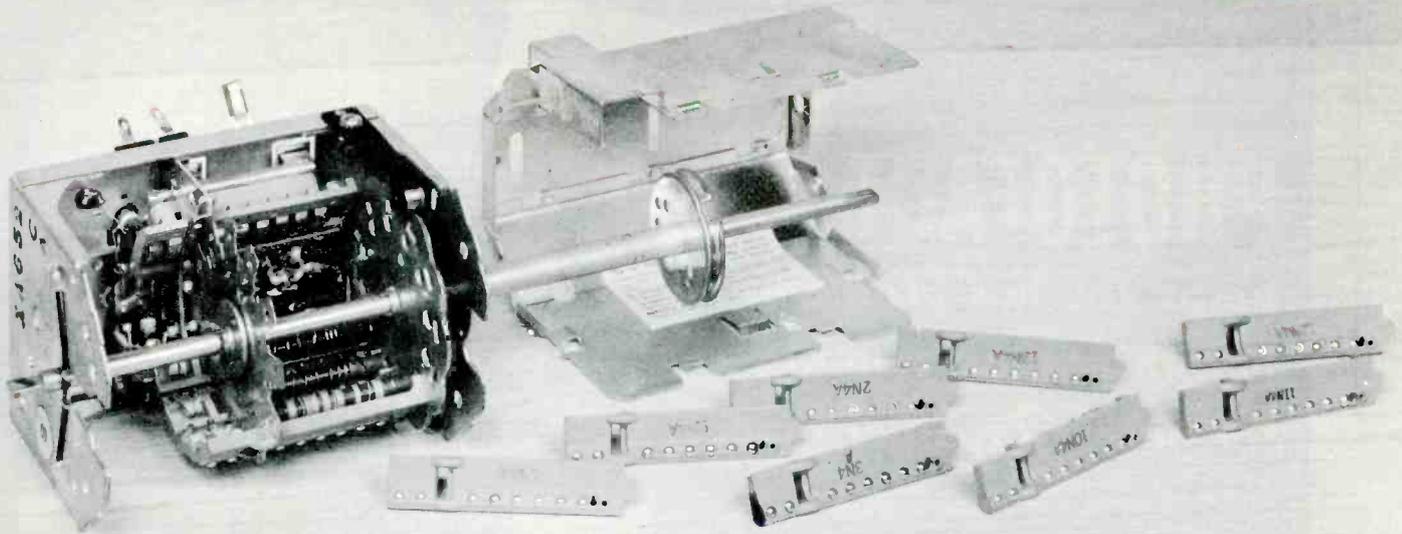

part 3 Mixer and Oscillator Circuits

by Calvin C. Young, Jr.

Having previously covered the RF amplifier and input circuits of VHF tuners, we now come to the point where a detailed analysis of the two most common types of oscillator-mixer circuits is in order. Since VHF tuners are divided into two general categories, switch and turret, let's examine a pentode mixer used in a popular switch-type tuner (Fig. 1) and a triode mixer employed in a popular turret tuner (Fig. 2). Thus, we will be dealing with the circuits and the associated problems you are most likely to encounter in service work. Before going into the characteristics of the individual circuits, however, let us first examine the purpose and general functions of the mixer and oscillator sections.

In order to utilize a single string of amplifiers to amplify each station signal to the level required by the video detector, some means must be provided for the conversion of each incoming carrier to a common (IF) intermediate frequency. By utilizing the heterodyne principle, a tunable CW signal can be mixed with incoming station carriers and an interme-

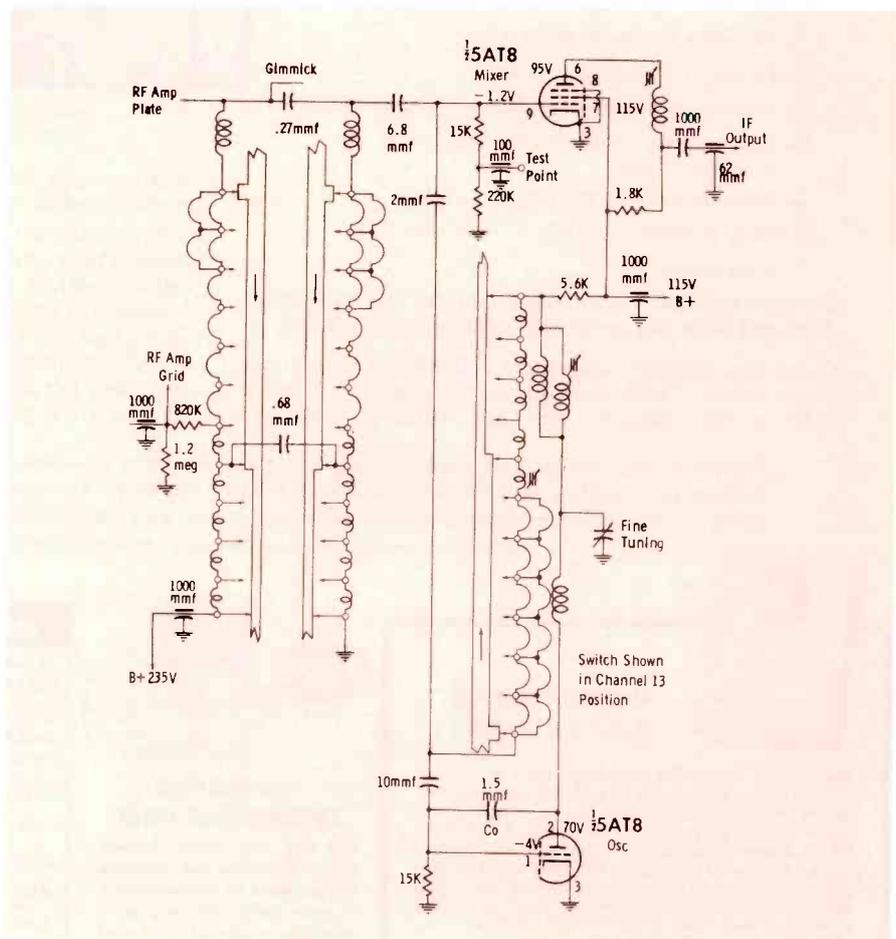



Fig. 1. Mixer and oscillator section of switch-type tuner.

To install or service COLOR-TV...

you must have these 5 new Walsco tools



Cat. #2548

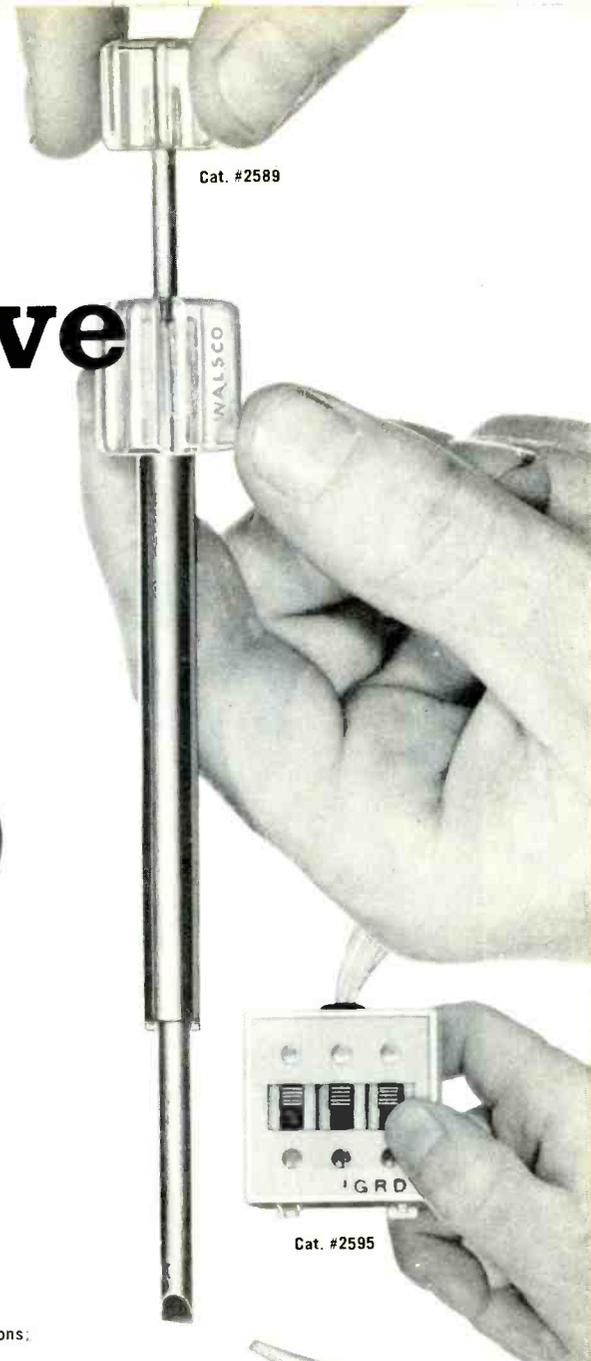

Cat. #2589

Cat. #2595



*Specially designed... absolutely essential
to make Color-TV servicing easy and profitable!*

Cat. #2548 NEW WALSCO COLOR-TV INTERLOCK CHEATER.

Lets you service color sets with rear panel removed. Blocks grounding of high voltage supply. Special design permits safe insertion of high voltage probe. Net \$94

Cat. #2590 NEW WALSCO COLOR-TV DEGAUSSING COIL.

Required to eliminate stray magnetic fields prior to purity adjustments. Made to standard industry specifications. Enclosed in molded plastic cover. Momentary switch safely de-energizes coil without pulling plug.

Cat. #2590 with momentary switch... Net \$16.90. Cat. #2591 without switch... Net \$14.90

Cat. #2589 NEW WALSCO COLOR-TV ALIGNMENT TOOL.


Adjusts and aligns all concentric controls on color, as well as black-and-white sets. Makes two separate adjustments at the same time: outer shaft aligns outer control shaft, inner shaft aligns inner control shaft. Net \$1.19

Cat. #2595 NEW COLOR-TV GRID GROUNDING BOX.

Essential for grounding controlled grids of color tube to permit convergence and matrix adjustments. Special "insulation piercing" terminals make application easy. Net \$5.10

Cat. #2596 NEW WALSCO TV COLOR VIEWER.

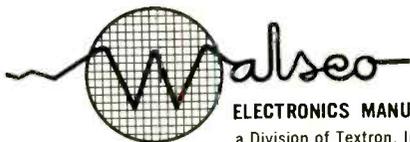Balanced optical filters speed accurate color phase and matrix adjustments on all color TV sets...without using an escilloscope. Net \$1.50



ELECTRONICS MANUFACTURING COMPANY

a Division of Textron, Inc.


100 West Green Street, Rockford, Illinois

Western Division:

3225 Exposition Place, Los Angeles 18, California

In Canada:

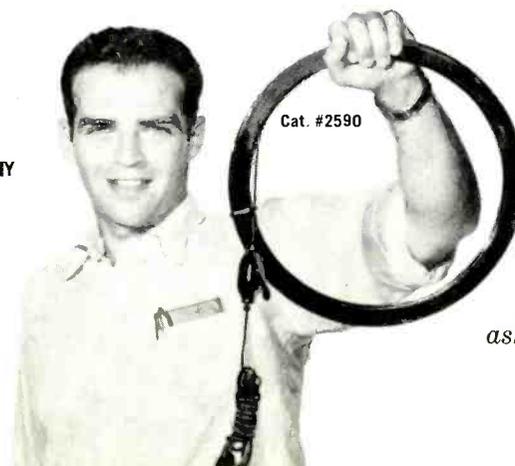Altas Radio Corp., Ltd., 50 Wingold Avenue, Toronto, Canada




Cat. #2590




Cat. #2596

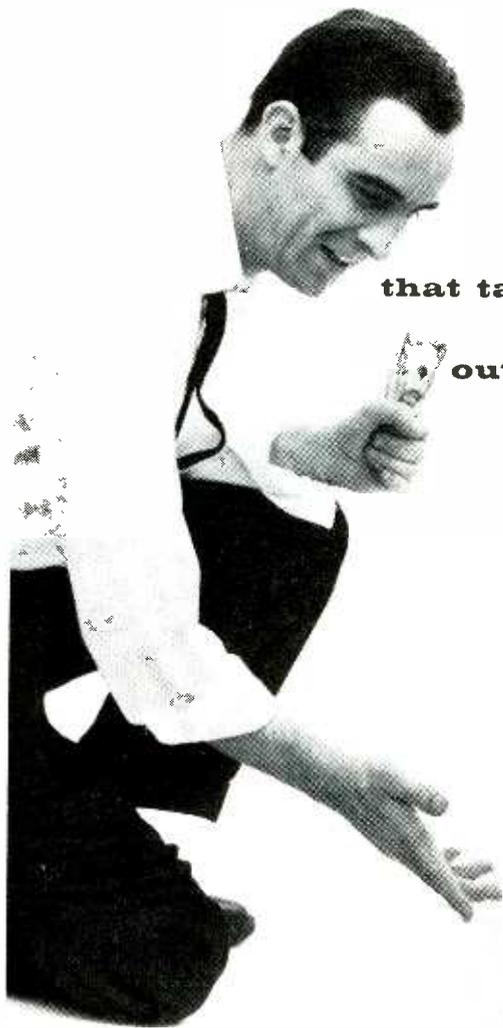FREE!
*Special folder
explaining how to use
these new Color-TV tools...
ask your jobber or write direct.*




Here's the number

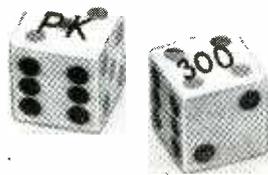that takes the "gamble"
out of your service
reputation



Centralab PK-300 dual-speaker switch kit

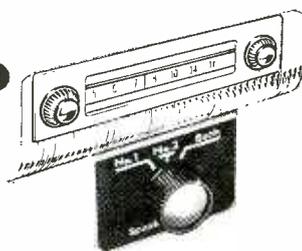

Surely your reputation means more to you than the pennies you save by installing an inferior dual-speaker switch. Then, why gamble? Especially when it costs so little more to go first class with the PK-300 switch kit.

The PK-300 is your "seven-come-eleven" combination that keeps customers sold. Here's real quality — a switch with silver-plated, double-wiping contacts — a dial plate that's etched to stay legible long after conventional painted types have worn off.

So don't settle for just any switch kit for your auto-radio and other dual-speaker jobs. Pick up a PK-300 kit at your Centralab distributor. Write for Catalog 30.

PK-300 switch kit includes:

1. Dual-speaker switch
2. Etched mounting bracket and dial
3. Split-knurl pointer knob
4. Self-tapping screws
5. Easy-to-follow instructions

Centralab A DIVISION OF GLOBE-UNION INC.
942J EAST KEEFE AVENUE • MILWAUKEE 1, WISCONSIN


P-1658

diate carrier having all of the modulation characteristics of the original carrier will be developed. Station selection then becomes a matter of changing the CW signal frequency to provide a beat frequency difference which corresponds to the IF carrier frequency.

It is the job of the local oscillator to generate the CW signal, and of the mixer to simultaneously receive the incoming modulated carrier and oscillator signals so that the heterodyne action will take place. Since it is possible to re-

Arcing Damper Tubes in RCA Victor KCS-47A Chassis

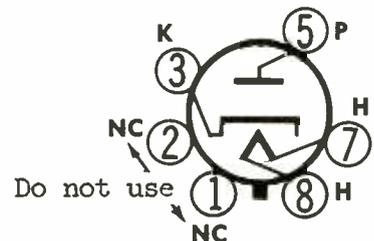When replacing the 6W4GT horizontal damper in an RCA Victor Chassis KCS-47A, make sure the replacement tube does *not* have a pin 1 in the base. Terminal 1 on the socket in this set—and possibly in other types and models of TV sets as well—is used as a ground connection, and therefore an internal ground will be present in the damper tube if it has a pin 1 in its base. Since damper circuits



operate at a high potential above ground (in some cases, thousands of volts), extreme arcing may occur within the tube and overload the circuit to the extent that the horizontal output tube can be ruined in a very short time. Some 6W4GT tubes are supplied with pin 1 on the base. When installing such a tube, cut the extra pin off with side cutters rather than risk a recall.

—George D. Philpott

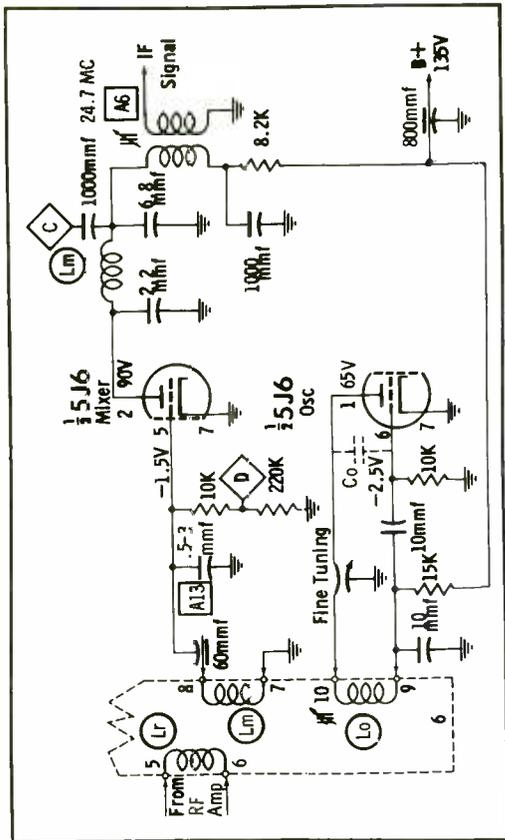


Fig. 2. Mixer and oscillator section of turret-type tuner.

ceive two carriers at about the same distance above and below the oscillator frequency, common practice has been to operate the oscillator above the desired frequency and to choose an IF range into which no image frequencies will fall. (The 40-mc range best fulfills this requirement because there are no station carriers 40 mc below the oscillator frequency when tuned to receive a desired TV channel.)


Switch Tuner With Pentode Mixer

The pentode-mixer, triode-oscillator combination is the most popular of the designs appearing in newer receivers. There are twelve different triode-pentode tubes used in this application (including both 5 and 6 volt versions) which have been designed and placed on the market for mixer-oscillator use in VHF tuners, while there are only three dual triode types. In the triode-pentode combination are the 5AT8, 6AT8, 5BE8, 5BR8, 6BR8, 5CG8, 6CG8, 5U8, 6U8, 5X8 and 6X8. This wide variety of similar tubes has evolved from the original 6U8 and 6X8 types because of the trend



Looking for new numbers?

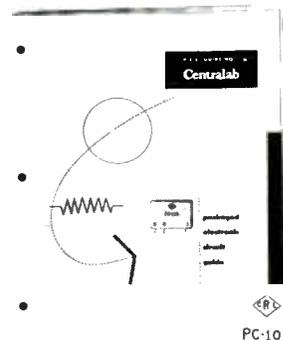All the hot ones are in Centralab's new, free PEC* Guide



Twenty-five fresh new beauties to choose from. Currently keeping company with the entertainment industry's most popular chassis.

Brand-new edition of the Discriminating Serviceman's Guide — loaded with vital statistics, on both the old favorites and the new models. Gives practical techniques for testing — how to tell good ones from bad.

Get the lowdown on what models have been engaged, and where, by 130 radio and TV manufacturers.

These are facts it pays to have — you encounter more and more of these slim, trim PEC's every day. Over 75,000,000 now in circulation.

These beauties are waiting to be picked up at your Centralab distributor. Write us for your copy of PEC Guide No. 4.

New—Free PEC Guide No. 4

3	2	1


Centralab A DIVISION OF GLOBE-UNION INC.
942J EAST KEEFE AVENUE • MILWAUKEE 1, WISCONSIN

* Trademark

Howard W. Sams 1958

TEST EQUIPMENT ANNUAL

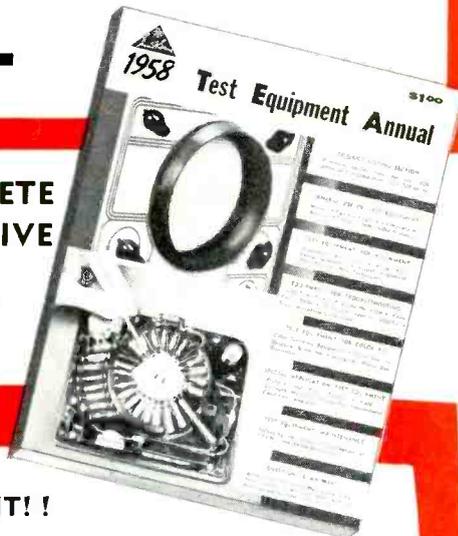THE MOST COMPLETE AND AUTHORITATIVE VOLUME EVER PUBLISHED ABOUT TEST EQUIPMENT



NOTHING ELSE LIKE IT!!

A completely NEW and DIFFERENT volume containing the most needed, the most requested information about all types of Test Equipment and Accessories. 100% practical for anyone who uses test equipment, it covers the complete range of test equipment in down-to-earth language and sparkling illustrations.

8 FACT-FILLED EDITORIAL SECTIONS

- Use and Selection of Test Equipment for Color
- Test Equipment for Special Applications
- Test Equipment Maintenance
- Questions and Answers About Test Equipment
- Test Equipment Methods, Measurement Analysis, and General Information
- Using Test Equipment for Alignment
- Using Test Equipment for Troubleshooting

All the down-to-earth information you need on operation, theory, and maintenance of Test Equipment. Each section filled with articles designed to save you time and money—techniques that make your present equipment more versatile and valuable to you—information about new equipment designed for service of new components and chassis.

plus An editorial Product Listing Section which features over 400 units of test equipment and accessories. Pertinent specifications are given on all equipment, and most models are illustrated.

For the first time anywhere the product listing section will group test equipment by the following logical product classifications:

- | | | |
|---------------|--------------|--------------------|
| Oscilloscopes | Meters | Transistor Testers |
| VOM's | Decade Boxes | Component Testers |
| VTVM's | Bench Eqpt. | Probes |
| Generators | Tube Testers | And Many Others |

LIMITED EDITION - RESERVE YOUR COPY TODAY!

AVAILABLE AT YOUR ELECTRONIC PARTS DISTRIBUTORS IN NOVEMBER

ONLY \$1.00



HOWARD W. SAMS & CO., INC

2201 EAST 46TH STREET INDIANAPOLIS 5, IND.

toward the use of printed boards and circuitry having a minimum of local oscillator radiation. (Refer to "A Gallery of Triode Pentodes" in the June PF REPORTER for a thorough analysis of these tube types.)

The popularity of the pentode as a mixer, even though it has a higher noise figure than a triode, is due to two factors: (1) The development of high-gain, low-noise RF tubes and (2) the added IF signal gain which a pentode mixer affords.

Now for the actual circuits. In Fig. 1, notice that RF signal energy is coupled into the tuned mixer grid circuit at two points, (across the entire coil assembly and also across the lower five coils). The .68-mmF capacitor across the lower coils provides additional coupling at the lower channel frequencies (7 and below) so that a linear response over the entire tuning range will be achieved. The .27-mmF coupling capacitor is effectively increased in value by the gimmick which is set for optimum performance when the tuner is aligned at the factory; so when you see what is apparently the free end of an extra long pigtail alongside the body of a capacitor, don't cut it off—it's probably a gimmick.

The oscillator signal in this circuit is coupled to the mixer from the oscillator grid through the 10-mmF and 2-mmF capacitors. The negative 1.2 volts at the mixer grid is the result of the oscillator signal developed across the grid load resistors. The amount of signal injection is adjusted for optimum conversion transconductance over the entire VHF band. Any material increase or decrease in



THIS MONTH'S COVER



This month's cover pretty well sums up what the average serviceman faces during the month of October—work, work, work!

As with most PF REPORTER covers, we pose a choice of scenes; for those of our readers who are avid science-fictionists, we present above one of the "other" cover shots we took, but didn't use.

Incidentally, our young "Indian" (Associate Editor Les Deane's son) really worked himself up to the spirit of the cover; he scored a brilliant coup over 2 table model TV sets and a transistor portable.

Our sincere thanks to Lane TV Sales & Service, Indianapolis, for the use of their modern store.

(Advertisement)

latest **JACKSON** tube test data

TUBE TYPE	MODEL 648 CIRCUIT		PLATE TEST	MODEL 115/715/561				
	FIL. D.	E.		FIL.	X.	PLATE YZ		
6DS5	6.3	A237	AC156	21WZ	6.3	5	9	2LMS
6CA4	6.3	123	4	15W	6.3	-	8	2S
EZ81	6.3	123	9	15W.	6.3	-	8	5S
6V4	6.3	129	4	18W.	6.3	-	8	9B
EZ80	6.3	129	9	18W.	6.3	-	8	5S
TUBE TYPE	SEC.	A.	B.	C.	D.	CATH. SHORTS E.		
6DS5	P	6.3	3	7	156	2	4.	
6CA4	D	6.3	4	-	1	3	4	
EZ81	D	6.3	4	-	7	3	4	
6V4	D	6.3	4	-	1	3	10	
EZ80	D	6.3	4	-	7	3	10	

Latest Chart Form 648-18, 115/715/561-9, 49-3

the oscillator injection voltage can cause a decrease in the signal-to-noise ratio. A change in the capacity of the 2-mmf coupling capacitor from the oscillator, for example will result in a change of the oscillator injection voltage. This voltage may be measured at the test point provided between the 15K and 220K resistors. Only a VTVM or an equally high-impedance instrument should be used to measure this voltage; a low-impedance meter will load the circuit and provide erroneous readings.

Turret Tuner With Triode Mixer

There are only three dual-triodes that have seen widespread use as mixer-oscillators in TV tuners—the 6J6, 5J6 and the 12AT7. Even though the triode generates less noise than a pentode, it has less gain and must be neutralized to prevent it from breaking into oscillation. Neutralization in the mixer stage of Fig. 2 is accomplished by the inclusion of a small RF choke (L_N) in the plate circuit.

Note that this figure illustrates a triode-mixer, triode-oscillator circuit employed in a turret tuner. If a triode mixer is employed in a switch-type tuner, its operation does not differ; however, the problems associated with incremental inductance tuning must be considered. By the same token, a pentode mixer could be used in a turret tuner, and the special considerations associated with the turret tuner would then apply to the pentode mixer.

One of the first differences that you will notice between the circuits in Fig. 1 and Fig. 2 is that the latter seems to be less complicated. This is due to the fact that only a single set of channel coils is shown. You will further notice that there is no coupling capacitor between the oscillator and mixer sections. None is employed because of the mutual coupling between L_O and L_M . Mutual coupling is also employed between L_R and L_M in feeding RF signal energy to the mixer grid circuit. The multiple coupling arrangement used in the switch tuner is not necessary in the turret tuner, since the fixed mutual coupling

3 KEYS TO SUCCESSFUL SERVICING

ARE YOURS

WHEN YOU USE...

RCA Gold Label Speakers

Brand Acceptance

Parts That Fit

Dependable Performance

For sound customer satisfaction
... try an RCA Speaker on
your next speaker replacement!



**RADIO CORPORATION
of AMERICA**

COMPONENTS DIVISION

CAMDEN, N. J.

The Case of The Serviceman WHO SAVED A MARRIAGE!




Smith wanted to watch the fights; Mrs. Smith insisted on "This Is Your Wife". Fights they got, since a second set was within their means but there was only one antenna and no multi-set coupler they tried had worked satisfactorily.




"You won't need another antenna with this 'NEW' Jerrold Multi-set COUPLER", said the TV Serviceman. "Its special design allows for equal distribution of the signal with *exceptionally low loss* and without smearing or ghosting".



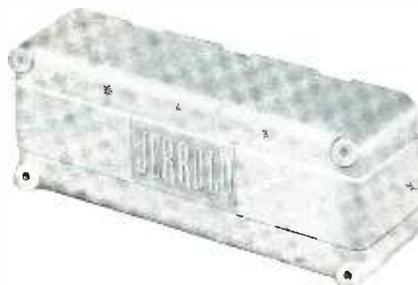The Jerrold multi-set coupler took only minutes to install... now, both the Smiths watch their favorite TV shows.



UNIVERSAL MOUNTING

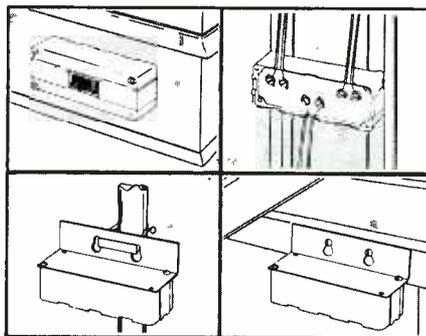

- On the baseboard. Connectors completely concealed.
- In the attic or basement with terminals exposed for ease of servicing.
- Outdoors, on the antenna mast or on the side of the house.

New! JERROLD LOW LOSS COUPLERS

Available in 3 models

- M-2—for strong signal areas . . . list \$3.50
- MF-2—for fringe areas list 4.50
- MF-4—up to 4 sets—all areas . list 5.75

Engineered for V.H.F., U.H.F., Color reception. See your Jerrold Distributor or write for complete information to Dept. P.D. #17

JERROLD ELECTRONICS CORPORATION

Main Office: 23rd & Chestnut Streets, Philadelphia 3, Pa.

Export Representative: C.B.S. International, New York 22, N.Y.

LOOK TO JERROLD FOR AIDS TO BETTER TELEVIEWING

of each channel strip is such that relatively constant bandwidth is achieved for all channels.

Oscillators

We have already discussed the purpose of the local oscillator signal. Now let's look at the circuit that generates this signal. The local oscillator in TV tuners almost invariably uses a triode tube. When using a triode as an RF amplifier or a mixer, neutralization is necessary for the prevention of oscillations which would otherwise occur due to the feedback capacity between the plate and control grid. In an oscillator application, this capacity comes in handy for use as a portion of the feedback network; thus, instead of being a hindrance, it now is quite a desirable characteristic.

In Fig. 1, a 1.5-mmf capacitor (C_0) has been connected between the plate and grid of the oscillator tube. This adds to the internal capacity of 1.5 mmf to produce a total capacity of 3 mmf, permitting the passage of a sufficient amount of feedback signal to sustain oscillations at the desired level in the switch-type tuner.

In Fig. 2, the internal capacity (C_0) of the tube alone is sufficient for the feedback application. The 10-mmf capacitor between the turret strip and the oscillator control grid is a grid-leak and DC blocking capacitor. Its value is critical in determining the oscillator frequency, as is that of the 10-mmf capacitor from terminal 9 of the strip to ground.

In both the switch-type and turret tuners, fine tuning is accomplished by varying the capacity of the oscillator tank circuit. However, the turret tuner circuit shown incorporates the so-called "book" fine tuning system in which the distributed capacity between the small inductor and a grounded plate or leaf is varied. In a turret tuner, the oscillator frequency may be adjusted on each channel by turning the associated oscillator adjustment slug, and an adjustment on one channel has absolutely no effect on the oscillator frequency of any other channel.

On the switch-type tuner, where a small amount of inductance tunes with the oscillator capacity

on channel 13 and additional increments of inductance are added in series for each lower channel selected, the oscillator must be adjusted in a different manner. First, the fine tuning is preset to the center of its range and then the oscillator slug on the highest receivable channel is adjusted. Following this, the next highest receivable channels are adjusted in succession, taking care not to disturb the setting of the fine tuning.

When the tuner has been set-up in this manner, aging of the oscillator tube or minor changes in component values won't result in detuning of the oscillator on only one channel. Setting the oscillator to produce the best picture and sound at the center of the fine tuning makes it unnecessary for the set operator to readjust the frequency vernier each time the channel is changed—a feature the customer is sure to like.

Oscillator radiation is a problem that the tuner manufacturers have made a successful effort in curbing. Keeping this radiation at a minimum is your responsibility, and there are a few points to remember in this respect. Always replace the oscillator tube shield and see that, when necessary, all bypass capacitors and RF chokes


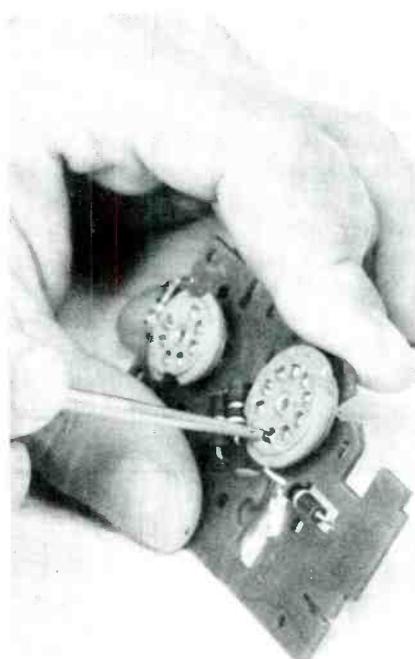


Fig. 3. Using a soldering aid to tighten tube socket contacts.

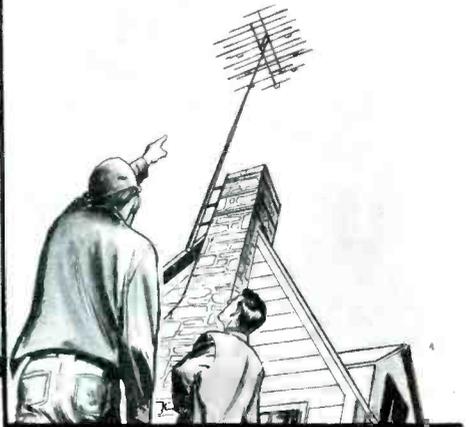
The Case of The Serviceman WHO KEPT IT CLEAN!




The fringe area Jones family wanted TV entertainment but got "snow". When Junior's favorite show was ruined once too often, the serviceman was called in.



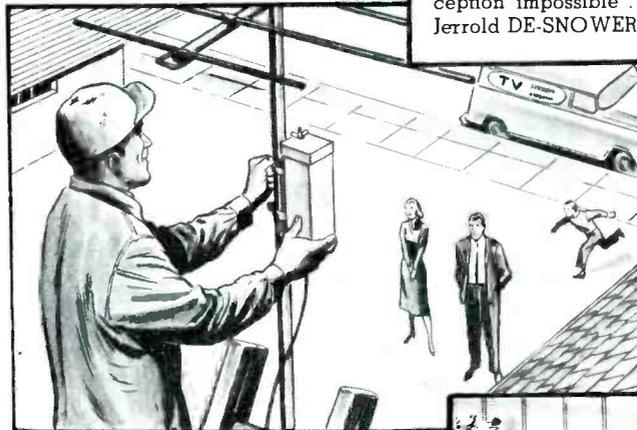
He pointed out that even with a good antenna weak signals are affected by line loss and noise, making good reception impossible... recommended a Jerrold DE-SNOWER.



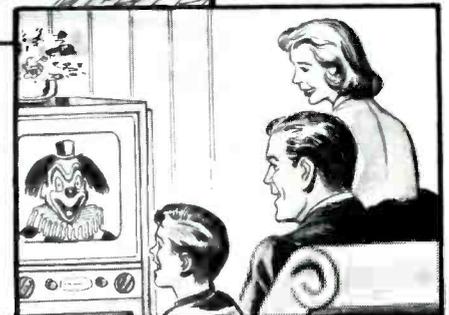Antenna mounted, the DE-SNOWER captures the signal before loss and noise affect it, delivers it to the set over shielded coax... providing snow-free pictures.



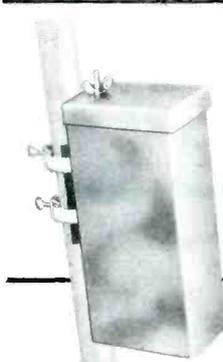Thanks to the serviceman and Jerrold the Joneses get high fidelity color and black and white pictures every time!



THE JERROLD DE-SNOWER

A high profit pre-amplifier accepted everywhere! Combines 25 db gain with low noise input—only 6 db. No AC outlet or separate wiring on mast.

Available in 3 models—Single Channel; Broadband Chs. 2-6, Broadband Chs. 2-13. Packed complete with remote 24 volt power supply. See the DE-SNOWER line at leading distributors or write direct for illustrated brochure to: Dept. P. D. #17

JERROLD ELECTRONICS CORPORATION

Main Office: 23rd & Chestnut Streets, Philadelphia 3, Pa.
 Jerrold Electronics Ltd., Toronto 10, Canada
 Export Representatives: CBS International, New York 22, N.Y.
 LOOK TO JERROLD FOR AIDS TO BETTER TELEVIEWING

NEW!

Simpson COLOR BAR GENERATOR MODEL 430



SINGLE MASTER CONTROL has all outputs pictured in color. Shows what you should see on TV screen.



HINGED SIDE PANEL opens for fine adjustments and maintenance. Allows use from shelf or bench.

PROVIDES TRUE 100% SATURATED NTSC SIGNAL—Here's the new color bar generator you've heard so much about. It's literally packed with features to save you time, to do more jobs, to operate simply. And what's more, Model 430 will service any color-TV receiver—past, present, or future. You'll find it to be the finest, most complete instrument of its type.

IMPORTANT SPECIFICATIONS

Exceptional Range of Outputs—Y; chroma; color bar (8 bars simultaneously—color phase accuracy, $\pm 5^\circ$); R-Y; B-Y; R-Y and B-Y simultaneously; I; Q; I and Q simultaneously; G-Y at 90° (demodulator color phase accuracy, $\pm 3^\circ$); sync and burst; horizontal sync; high level 3.58 megacycle output; high level modulated RF output; positive or negative video output. 4.5 Megacycle (crystal controlled) marker for proper tuning.

Chroma Level Switch—0 db for checking older style receivers and some current models; -6 db for video check of newer receivers using vestigial IF alignment; -15 db for checking color sync lock under weak signal conditions. Variable chroma control position for other chroma levels.

Color Bar Display Pattern—Left to right: red, yellow, green, cyan, white, magenta, blue, black.

Model 430, complete with Operator's Manual and Leads **\$395⁰⁰**

See your Electronic Distributor, or write

SIMPSON ELECTRIC COMPANY

5200 W. Kinzie St., Chicago 44, Ill.

Phone: EStebrook 9-1121

In Canada: Bach-Simpson Ltd., London, Ontario



WORLD'S LARGEST MANUFACTURER OF ELECTRONIC TEST EQUIPMENT



Fig. 4. Putting a thin film of conductive lubricant on tube pins.

in the oscillator stage are replaced with suitable (identical) units. One more thing—the filter and trap circuits in the input sections of the tuner must be in good working order and correctly adjusted.

Servicing

Oscillator and mixer stages are relatively free from trouble, but when it does develop, it can be very difficult to locate. Probably the two most-often-encountered problems will be a failure to oscillate on high channels (usually a defective oscillator-mixer tube) and intermittent flashing (often caused by dirty contacts or tube socket pins). Contact trouble that can be traced to the tube socket is probably the most difficult to remedy because even some amount of conductive film on the socket itself can be the cause. Since some cleaners will leave a slight film on the surfaces to which they are applied, such liquids should be applied with caution if an apparently "unreasonable" trouble is to be avoided.

Probably the best way to clean a tube socket is to squirt a little carbon-tet into each pin contact, and then, using air pressure, clean





Fig. 5. Standard Coil "ContaCare Kit."

the socket and expel the carbon-tet.

If the socket pins are loose, they can be tightened up with the use of a solder tool or other sharp pointed instrument (Fig. 3). To avoid causing damage in this operation, care should be taken not to exert too much pressure. After applying a thin film of conductive lubricant (such as Walsco's *Lubriplate* or General Cement's *Lube-Rex*) on each pin (Fig. 4), the tube should then be worked in and out of the socket a few times to coat the socket contacts and protect them against possible corrosion. Should a socket contact become damaged, an attempt should be made to install one taken from a new socket rather than face the tedious job of replacing the entire socket.

The contacts on switch-type tuners and the drum and slider contacts on turret types can be cleaned with any of the commercially-available cleaners. If compressed air is available, it should be used to evaporate excess fluid and to blow away the dirt which might cling to the dampened surfaces. If no compressed air source is available, be sure to wipe the excess fluid away and allow time for the remainder to evaporate.

A tuner contact care kit has been recently introduced by Standard Coil Products Co. under the name of "ContaCare Kit" (Fig. 5) which is especially designed for use with turret tuners. This kit consists of a specially-treated cleaning cloth and a special oil. The proper use of this kit duplicates original factory treatment of contact surfaces, affording lubrication and protection against corrosion for about one year. ▲

GET YOURS NOW!

SONOTONE

PHONOGRAPH MODERNIZATION MANUAL
SECOND EDITION
PRICE 10 CENTS

ELECTRONIC APPLICATIONS DIVISION
SONOTONE CORPORATION
ELMSFORD, N. Y.

PACKED WITH VALUABLE INFORMATION

- Advantages, operation and use of ceramic cartridges
- Replacement data

IT'S FREE!

This handy booklet will help you make proper and intelligent use of the amazing new Sonotone Ceramic Cartridges. It will enable you to make profitable replacements, modernizing your customer's phonograph. It will give him extra satisfaction and bring you prestige.

Be sure to get your up-to-date manual.

Just fill in the coupon and mail to Sonotone. Attach to a postcard if you wish.

SONOTONE® Corporation

Department CP-107
Elmsford, N. Y.

Please send me, without cost or obligation, a copy of the newly revised "SONOTONE Phonograph Modernization Manual."

NAME _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____

Shop Talk

(Continued from page 10)

It is possible, by driving a transistor to saturation, to utilize the sharp cutoff and saturation characteristics of a junction transistor in a one-stage sync separator. Such a circuit is shown in Fig. 2. The incoming signal must be strong enough to drive the transistor into saturation so that the full output of 15 volts peak-to-peak is obtained; thus, for a one-stage separator, an input amplitude greater than that used in the two-stage system is required. As before, fixed and variable bias is employed to provide automatic adjustments for varying signal conditions.

The choice of values for R1 and C1 will greatly influence the noise immunity characteristics of the circuit. If their values are made relatively low, (i.e., $R1 = 100,000$ ohms, $C1 = .022$ mfd), the circuit will enjoy good horizontal impulse noise immunity because it will be able to respond quickly to sharp spike voltages.

On the other hand, a long time constant is necessary for the best separation of vertical sync pulses. If this design is followed, the ability of the circuit to cope with short noise pulses will be impaired. A compromise could be worked out, but a more desirable solution is shown in the circuit of Fig. 3 where two separate time constant circuits are employed. R1, R2, and C2 form a short time constant combination while R3, R4, and C3 provide the long time constant network. When a sync pulse is active in this circuit, the X1 emitter current biases D1 in the forward direction, thereby causing both time constant networks to be effective. By having R3, R4 and C3 active, the emitter


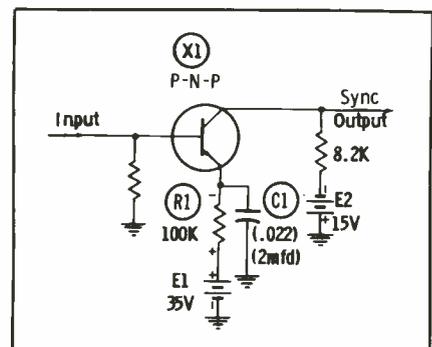


Fig. 2. A single-stage sync separator.

PF REPORTER · October, 1957

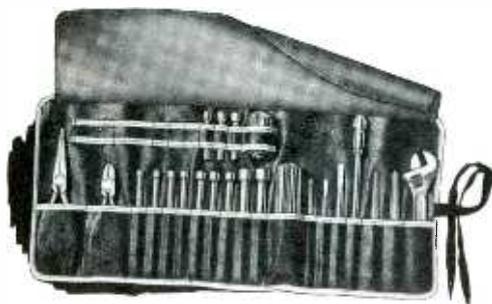I OWE IT ALL TO THE
RECOTON
 "DEALS OF THE YEAR CLUB"



**CONVENIENCE
 UNLIMITED!**

New
**XCELITE
 Kit**

Holds ALL Your Most-Needed Tools!

Yes, with the 99 SM Service Master, you'll be able to handle 99% of your service calls... quickly, easily, profitably. This convenient, attractive non-scratch roll kit contains 23 — yes, twenty-three — of the most popular items from the famous XCELITE "99 Line" of precision-made tools.

Your professional Radio, TV, Hi-Fi and Electronics Servicemen will have your favorite XCELITE Nutdrivers, Screw-

drivers, Detachable Handles, Pliers, Reamers, Adjustable Wrench — all "filed" for instant access in the 99 SM Kit. Included is the highly useful 99X-10 6" Snap-In Extension Blade.

If you have certain specialized service needs, you can "custom-assemble" your own selection of tools from XCELITE'S "99 Tool Line". Then your 99 SM Kit will fit your own service jobs to a "T".

See Your Dealer Today... Order YOUR 99 SM Service Master Kit
 To Handle 99% of ALL Your Service Calls!

XCELITE, INCORPORATED
 Dept. Q, Orchard Park, N. Y.
 In Canada: Charles W. Pointon, Ltd.
 6 Alcina Ave., Toronto, Ont.

For Originality
LOOK TO XCELITE

bias is maintained for the duration of a vertical sync pulse, permitting its proper separation.

Now, let us suppose that a noise pulse appears, and further, that it possesses a greater amplitude than any of the sync pulses. It too, will cause D1 to conduct but because of its amplitude, will charge C3 to a higher voltage than a normal sync pulse. This higher potential on C3 will reverse the bias on D1 and keep it cut off until the excess voltage has discharged through the parallel combination of R3 and R4. This may take some time. In the meantime, horizontal sync separation can resume as soon as the excess charge across C2 (due to the same noise pulse) discharges through R1 and R2. The latter action will occur much faster because of the far smaller value of C2 as compared to C3.


The foregoing circuit will give a performance comparable to vacuum-tube sync separators in standard commercial receivers. Furthermore, transistor interchangeability has been found to be good.

Beyond the sync separators, the pulses are fed to the vertical and horizontal deflection sections. Because transistorized vertical sweep circuitry is simpler and has progressed farther, let us examine it first, starting with the oscillator. In vacuum-tube circuits, either multivibrators or blocking oscillators have been utilized. In transistorized systems, at least to the present time, only blocking oscillators have been used because transistorized multivibrators have thus far exhibited frequency changes due to temperature variations, whereas the blocking oscillator is considerably more stable in this respect.

In many respects the blocking oscillator in Fig. 4* is similar to its vacuum-tube counterpart. For example, the blocking transformer T1 serves to provide feedback from the collector output circuit to the base input circuit. Also, sync pulses are fed to the base while a sawtooth deflection wave is developed across the 8-mfd capacitor from collector to ground. Furthermore, the charge capacitor receives its voltage build-up

* "Transistorized Vertical Deflection For Television Receivers," by M. B. Finkelstein, Transistors I, published by RCA.

PHAOSTRON

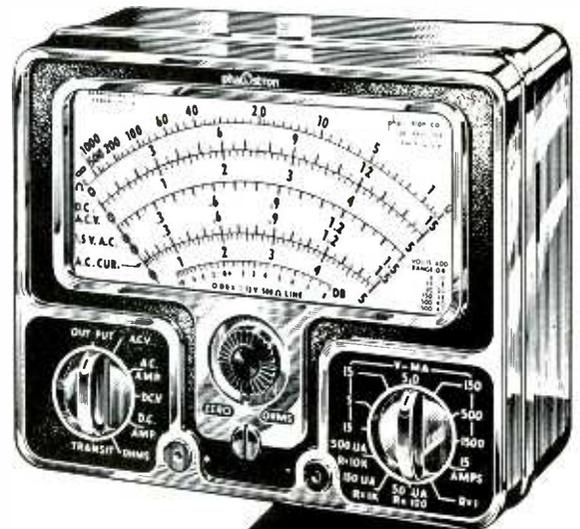

Here Is The
Best Value
Ever Offered In
An Electrical
Measuring
Instrument...

METER PROTECTION

The meter movement is protected up to 1000 times overload by rectifier network.

"555A"
A.C.-D.C. V.O.M.

ONLY THE PHAOSTRON "555A" V.O.M. (VOLT OHM MILLIAMMETER) MEASURES A. C. and D.C. CURRENT and VOLTAGE AS WELL AS RESISTANCE AND HAS ALL THESE FEATURES:

- Unbreakable Metal Case of Highly Polished Chrome
- Separate Range and Function Switches
- Anti Magnetic Shielding
- Easy-to-Read, Large 4-Color Scales
- 43 Unduplicated Ranges
- Only 2 jacks
- 3% D. C. ... 4% A. C. Permanent Accuracy

ACCESSORIES AVAILABLE

Genuine Leather Carrying Case \$7.95
Panel Mounting Adapter \$1.50

Other Fine Phaostron Products

MODEL "777"—Vacuum Tube Voltmeter... 42 unduplicated ranges with permanent accuracy—3% D.C., 5% A.C.

CUSTOM PANEL INSTRUMENTS—2½", 3½", 4½", 6"... all shielded by their metal cases from stray magnetic fields. 2½" and 3½" models available in round or square face.

PORTABLE LABORATORY INSTRUMENT...with double probe outlets and full overload protection.

RUGGEDIZED AND SEALED PANEL INSTRUMENTS...available in 1½" (Square Bezel) and 2½", 3½", 4½" Round Bezel models in AC, DC or Null Indicators.

NEW LOW PRICE

Not \$49.50, but priced lower than ever before. Complete with probes and batteries. (Replaces former model 555)

NOW ONLY

\$44⁹⁵

Write today for full details or ask your dealer

PHAOSTRON INSTRUMENT AND ELECTRONIC COMPANY
151 Pasadena Avenue, South Pasadena, California

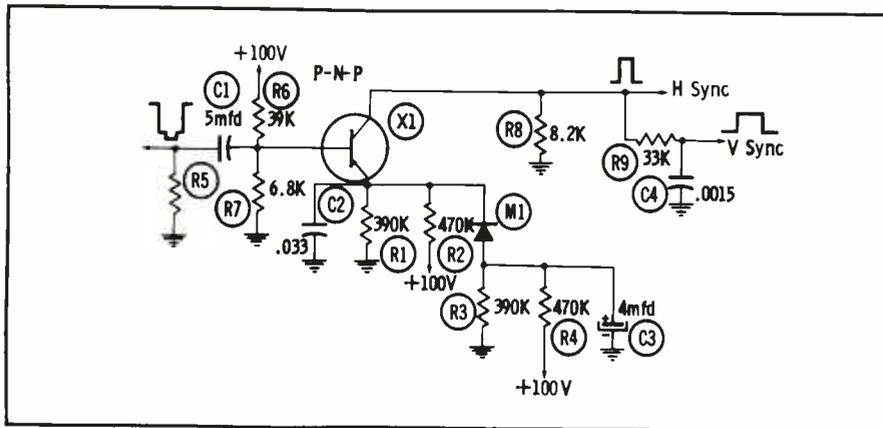


Fig. 3. A one-stage sync separator using a diode-controlled time constant.

while the transistor is cut off and then discharges when the transistor is pulsed into conduction. There are, however, some significant differences between the two circuits, and these stem from the dissimilarity in operational characteristics of tubes and transistors. This will be evident from the following analysis of circuit operation.

The transistor is biased beyond cutoff by the negative voltage present across R1. The value of this cutoff voltage is determined by the resistance setting of R2; hence R2 is equivalent to the conventional hold control. At the same time, capacitor C1 charges through R5 until the voltage across R3 becomes more negative than the voltage at the emitter. When this occurs, current will flow through the transistor and the conductive part of the cycle will begin. The current flowing through the collector circuit causes a voltage to be induced in the base side of T1, increasing the forward bias and the transistor current. This, in turn, couples a greater voltage into the base winding and increases the collector current even more. As a result, the transistor very rapidly becomes a virtual short circuit, permitting capacitor C1 to discharge quickly through T1 and R1. The discharge is practically complete and the voltage across C1 essentially drops to zero.

At this point the voltage across R3 and R4 is also zero, and the transistor is driven into cutoff by the difference between the emitter voltage at the arm of R2 and the voltage induced at the base by the collapsing field around T1. The sequence of events now repeats itself at a frequency determined by the various resistance and capacitance values in the circuit.

The major frequency determining components are C1, R5 and R2; C1 and R5 also develop the output wave. Here is a major difference between transistor and vacuum-tube blocking oscillators. In the latter circuits, the frequency determining parts are separate and distinct from the wave-forming circuit; in the transistor circuit, one set of components performs both functions.




STOP CB* WITH C-D

*STOP CALL BACKS by always using C-D "CUBS"®—the tubular that has proven itself the champ in the service field. They out-perform any other replacement because they're the only molded tubular with built-in extras that insure call-back-free servicing. C-D "CUBS" are made exclusively for the service trade.

SPECIAL! "CUB SERVICE KIT" in all-plastic dispenser. You pay only for the capacitors. Ask your distributor salesman to show you the new C-D "CUB SERVICE KIT" or write for details Cornell-Dubilier Electric Corporation, South Plainfield, N.J. *stop callbacks...insist on*

CORNELL-DUBILIER CAPACITORS

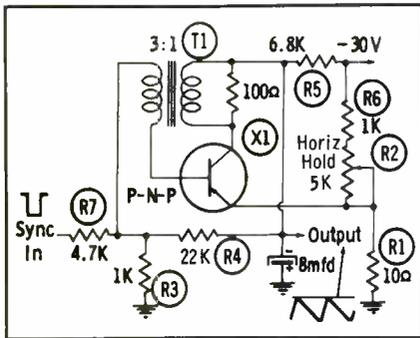SOUTH PLAINFIELD, N. J.; NEW BEDFORD, WORCESTER & CAMBRIDGE, MASS.; PROVIDENCE & HOPE VALLEY, R. I.; INDIANAPOLIS, IND.; SANFORD, FUQUAY SPRINGS & VARINA, N. C.; VENICE, CALIF.; & SUB.: THE RADIART CORP. CLEVELAND, O.; CORNELL-DUBILIER ELECTRIC INTERNATIONAL, N. Y.



(Courtesy RCA Review)

Fig. 4. A transistor blocking oscillator.

The sawtooth output waveform produced by the circuit of Fig. 4 is negative; if a positive-going signal is desired, an n-p-n transistor would be employed in conjunction with a positive voltage source. Obtaining reversal in this way is another unique feature of transistors and cannot be duplicated by tubes.

Another sawtooth blocking oscillator, in which the output wave is developed in the emitter leg, is shown in Fig. 5. This circuit is similar to the previous arrangement in that one RC combination (here, R3 and C2) provide both the timing and the output deflection waveform. It differs, however, in the way in which the sawtooth wave is produced. It has become customary in vacuum-tube circuits to have the charge time of the deflection capacitor correspond with beam trace and the discharge period with beam retrace. In the arrangement of Fig. 5, C2 charges through the transistor during the retrace period and discharges through R3 during trace time. Just how this is accomplished can be seen from the following discussion.

The base-emitter circuit is biased in the forward direction by

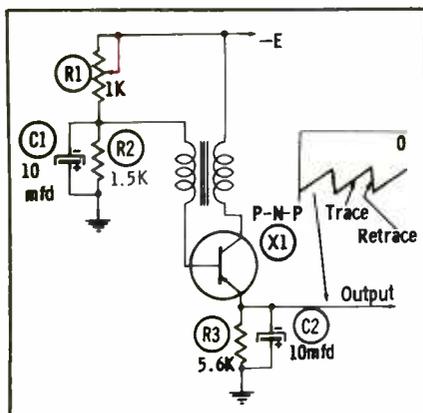


Fig. 5. Development of the sawtooth wave in this circuit differs from Fig. 4.

NOW—
Get it from
your Parts
Jobber!

Admiral—
rated by servicemen
as the most foolproof
and trouble-free of
all changers!

Admiral—
built into more
phonos and combinations
than any other
changer in the world!

Admiral®

4-Speed Record Changer



Beige and Coral
with Golden trim
(Base Optional).


- **PLAYS ALL FOUR SPEEDS—** 33 $\frac{1}{3}$, 45, and 78 plus "talking book" 16 $\frac{2}{3}$ r.p.m. Has neutral position. Changes 12 to 14 records; intermixes those of same speed. Automatic 2-way shut-off after last record. Returns tone arm to rest, stops turntable motor completely. NOTE: Can be wired to shut-off radio or amplifier chassis.

- **RUBBER TURNTABLE MAT**

- **FEATHERWEIGHT TONE ARM—** new resonance-free design. Less than $\frac{1}{8}$ oz. pressure. Positive tracking . . . no "skip" or "jump" on loud passages.

- **DIAMOND LP STYLUS—** separate LP diamond and 78 r.p.m. sapphire needles for finest sound reproduction, long record life.

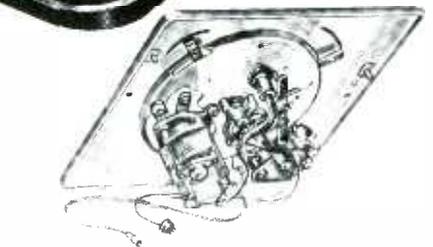- **ATTACHED 40" SHIELDED AMPLIFIER CABLE—** eliminates pickup of unwanted noise. Cable has phono tip plug for quick easy connection into standard input phono-tip jack.



HEAVY DUTY MOTOR— powerful 4-pole constant speed shaded pole induction type motor. Operates without hum, rumble or "wows" (as little as 0.1590). Maintains even speed even if line voltage varies. Six foot line cord attached.



CERAMIC PICK-UP CARTRIDGE— twin lever hi-fi cartridge changes with flick of the finger from LP to 78 r.p.m. needle. Impervious to heat and humidity. High lateral compliance minimizes wear, eliminates hum and distortion. Smooth even response (± 3 db) over the full high-fidelity frequency range (30-15,000 c.p.s.).


Write for Illustrated Specification Sheet.

Admiral®

SPECIAL PRODUCTS DIVISION
3800 West Cortland Street
Chicago 47, Illinois

Ward's New Complete Disappearing

AUTO ANTENNA
MODEL DCF-3C

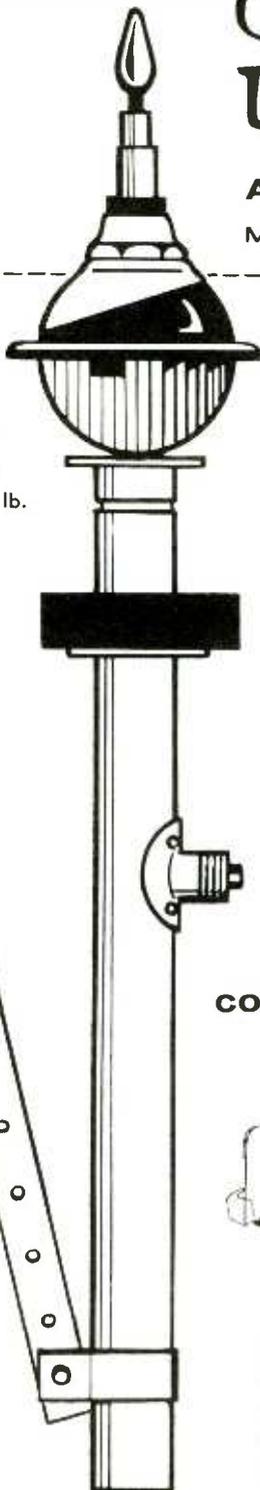

Model DCF-3C
54" lead cable
Shipping wt—1 lb.
12 to master
carton, 12 lbs.

NEW flame tip for streamlined appearance and better reception.




NEW water-seal grommet for double fender...the *ONLY* disappearing antenna specially designed to fit Chevy and other cars with double fender.

NEW lightweight aluminum shield tube for easier handling and better reception characteristics.

NEW lead take-off for much easier installation.

COLLAPSES FROM 45" TO 1"

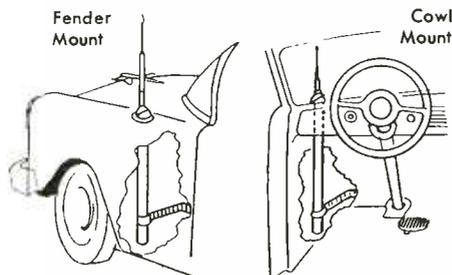

It's a new, fast-selling model; car owners will demand on sight. Makes car washing easier. Adds a top-quality appearance to any car. Avoid disappointment—order *NOW!*

NEW reinforcing bracket for sturdy mounting

Ward
PRODUCTS CORP.

DIV. OF THE GABRIEL COMPANY

1148 EUCLID AVE. • CLEVELAND 15, OHIO

IN CANADA, ATLAS RADIO CORPORATION • 50 WINGOLD AVE • TORONTO, ONTARIO

R1 and R2. This produces a current flow through the transistor which starts charging capacitor C2. The collector current flowing through the primary of T1 induces a voltage in the base winding which acts to increase the base current. This serves to further raise the collector current and thus the induced base voltage until the transistor is conducting to its fullest extent. This current buildup through the transistor is exceedingly rapid, and during this interval capacitor C2 is charging through the resistance of the transformer primary and the transistor. The ultimate value of the charge is determined by the fixed base bias and the induced voltage in the transformer secondary winding.

When this point is reached, the base current ceases and the transistor is driven into cutoff because the voltage across C2 is sufficient to bias the base-emitter circuit in the reverse direction. While the transistor is cut off, C2 discharges slowly through R3, thereby developing the trace portion of the deflection wave. Note that this wave gradually rises toward zero from its initial high negative value.

When C2 has discharged to the point where its voltage is equal to the fixed bias voltage, current again starts flowing in the base-emitter circuit and the same sequence of events recurs. Since R1 determines the value of fixed base bias, it determines the frequency of operation (together with the time constant of R3 and C2) and hence would function as a hold control.

A negative sync pulse could be introduced to the base circuit either through the use of capacitive coupling or a third winding on the blocking transformer. Both methods have been employed and both are satisfactory.

A positive-going sawtooth wave is produced by the above circuit. If a negative-going sawtooth is desired, an n-p-n transistor could be used with a positive power supply.

All of the circuits discussed above are practical designs which have been employed for the purposes indicated, and each has performed in an entirely satisfactory manner. ▲

Industrial Electronics

(Continued from page 17)

penations must be made in order to obtain the proper reading from the sensed body.

A device for correcting the error caused by ambient temperature, as the temperature around a body is called, is the bolometer. It is composed of two thermistors, one of which measures the ambient temperature, and one that is trained on the body or sensed heat. Its internal construction is shown in Figure 4. Two oxide flakes are placed within a heavy shield to keep out external noise pulses, with the compensating flake facing the inside of the wall. The sensitive flake faces an infrared window which admits the low frequency radiations but excludes all others. Connection to a typical amplifier circuit is usually made by the use of a bridge with the thermistors in opposite legs. Figure 5 shows the DC source used in conjunction with R1 and R2 to provide linear operation about some specified temperature. The signals from the two thermistors will oppose each other and the resultant signal will pass on to the grid of the amplifier. Capacitors C1 and C2 filter out the noise and 60-cycle signals picked up by the batteries and leads.

Minneapolis - Honeywell uses thermistors to great advantage in their residential heat controls. The requirements of home heating are quite different from the industrial heat controls previously described. When the outside temperature falls, the "Moduflow System" increases the inside temperature at the rate of 1°F for each 38°F fall in outside temperature; thus, the goal of home heat-

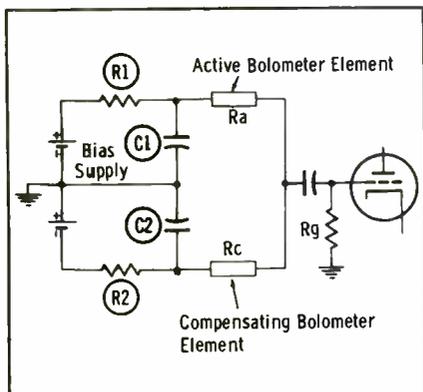


Fig. 5. Typical bolometer bridge circuit.

ing is to provide comfort for the individual, rather than constant temperature control.

If two different metals are joined together, a difference of potential will be created. The voltage developed is a function of the temperature and the work function of the metals. Work function is an energy level which is just great enough to cause one electron to escape the force exerted on it by the nucleus of an atom. Each metal has its own characteristic work function, and the addition of energy will cause more electrons to escape. When metals with different work functions are joined at both ends as shown in Figure 6, a current can be generated simply by heating one end. The heated end is called the "hot junction" and the other end the "cold junction." A device of this type is referred to as a "thermocouple."

The current through the leads is proportional to the difference in temperature between the hot and cold junctions. Both junctions develop a voltage with polarities which oppose the other; therefore, the current is a measure of the difference in voltage, and it will vary just as much with a change in cold junction temperature as with a change in the temperature of the hot junction. To obtain a true reading, the cold junction must be maintained at an even temperature. When very accurate readings are required, the cold junction can be held at the melting point of ice or placed in a controlled oven, and the temperature can be calculated from a chart supplied by the thermocouple manufacturer. The range of a thermocouple extends from about

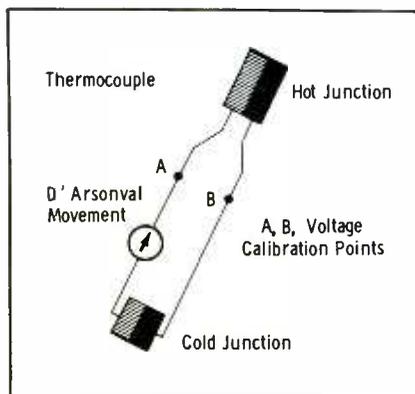


Fig. 6. Structure of a thermocouple.

FOR HOUSE CALLS

— it's

HEXA-CON

FEATHERWEIGHT

INSTANT SOLDER GUN

FITS TUBE CADDY—Takes Half the Space of Transformer Guns

SMALLEST SOLDER GUN WEIGHS ONLY 8 OUNCES

— but

POWER-PACKED AT 150 WATTS and

SOLDERS IN SECONDS

No heavy bulky transformer — sturdy lifetime tip—never wears or bends—effective spotlight

Model G14 with 1/4" tip — \$7.95
Order from your distributor today

HEXA-CON ELECTRIC COMPANY


589 W. CLAY AVE., ROSELLE PARK, N.J.

SERVING INDUSTRY AND CRAFTSMEN FOR A QUARTER OF A CENTURY

RADIO AND TV

SERVICEMEN

make more money with this

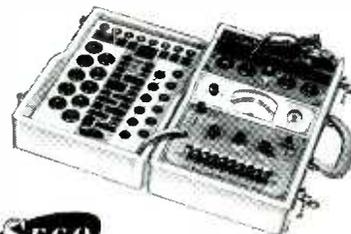

SECO

Model 107

TUBE TESTER

3 complete tests in one handy instrument

Here's the tube tester every serviceman has been asking for! Designed for outstanding performance and accuracy—provides 3 important tests: Dynamic Mutual Conductance Test of all popular radio and TV amplifier tubes—Cathode Emission Test for all tubes by free point selector system—nationally accepted Grid Circuit Test developed and patented by Seco. Saves you valuable time—quickly pays for itself by justifiably culling and selling more tubes for you!

Completely self-contained in compact portable carrying case. Furnished with handy flip-chart for fast, easy tube set-up data. **\$139⁵⁰** net

SECO

Write today for free literature
MANUFACTURING CO.
5015 Penn Ave. So., Mpls., Minn.

Dave Rice's
OFFICIAL
ORDER BOOK
 for every TV-Radio
 service call



TV-RADIO SERVICE
OFFICIAL ORDER BOOK

Triplicate forms serve as order form, invoice and office record with spaces for complete information on every job. Separate listings for receiving tubes, pix tube, parts, serial numbers, labor and tax charges, signatures, etc. 75c a book, \$6.50 for dust-proof box of 10.

... and for customer's prices on every replacement part, Dave Rice's

OFFICIAL PRICING DIGEST
 listing over 60,000 items. \$2.50

In stock at your distributor, or write


ELECTRONIC PUBLISHING CO. INC.
 180 North Wacker Drive Chicago 6, Illinois

DON'T REMOVE THAT CRT TUBE!



Snap it back to normal brilliance with new improved Kinecure. INSTANTLY and PERMANENTLY corrects 33 different CRT defects. Saves time, money, and irritation for both servicemen and customers. Thousands of TV servicemen now use new, improved Kinecure. Now time tested and job proven on over 50,000 sets. There is just nothing else like patented Kinecure. It looks different — operates different — works like a charm! Ask your Jobber. Or write for free full information.

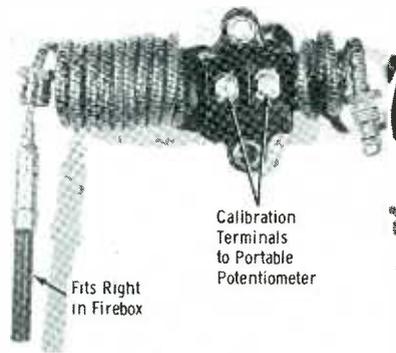CIRCUIT MANUFACTURING CO., INC.
 923 Shadeland Ave.,
 Drexel Hill, Pa.



Courtesy Minneapolis-Honeywell Regulator Co.

The thermocouple hot junction is housed within the protective cover at left. Special alloy wire completes the circuit to the indicator connector at the right, with the cold junction contained in the temperature indicator.

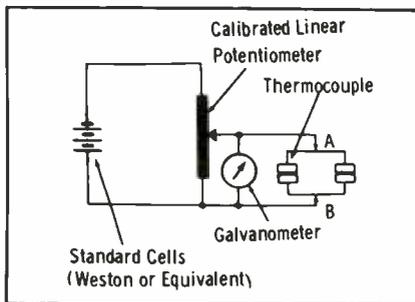


Fig. 7. A portable potentiometer connected across a thermocouple unit can be used in conjunction with a chart to determine temperature of the hot junction.

—100°F to 1,000°F, the exact limits being determined by the materials used and the method of construction.

The output voltage is measured in millivolts, requiring the use of a very sensitive voltage measuring device called a "Portable Potentiometer." As shown in Figure 7, the potentiometer is placed across a standard voltage cell such as the Weston unit. The voltage of the thermocouple is placed between the slider and one side of the potentiometer. When the voltages at points A and B are equal, there will be no current through the galvanometer, and the voltage of the thermocouple can be read directly from a calibrated dial on the potentiometer shaft. The voltage measured in this manner is then located on a chart from which the temperature is calculated. Most charts assume a cold junction of 32°F, and when the cold junction is other than this, a correction voltage must be determined from the chart and added to the dial reading. For example, suppose the voltage

CHART I—Temperature correction figures used in conjunction with portable potentiometer.

0°	-.922	1.96	4.92
5°	-.778	2.11	5.07
10°	-.634	2.26	5.22
15°	-.490	2.40	5.37
20°	-.346	2.55	5.53
25°	-.202	2.70	5.68
30°	-.058	2.85	5.83
35°	.088	3.00	5.98
40°	.228	3.14	6.13
45°	.378	3.29	6.28
50°	.518	3.44	6.44
55°	.658	3.59	6.58
60°	.808	3.74	6.74
65°	.948	3.88	6.89
70°	1.10	4.03	7.04
75°	1.24	4.18	7.19
80°	1.38	4.33	7.34
85°	1.53	4.48	7.50
90°	1.67	4.62	7.65
95°	1.82	4.77	7.80
100°	1.96	4.92	7.95

Figures are in millivolts

reading were 3.5 millivolts, but the cold junction is at a room temperature of 75°F and Chart 1 assumes a cold junction temperature of 32°F. To determine the correct voltage, locate 75°F on the chart; directly opposite you will find the correction voltage of 1.24 millivolts. This must be added to the 3.5-mv reading to get the proper voltage. The cold junction is developing a voltage which is 1.24 mv greater than that at which the chart is calibrated; thus the hot junction is 3.5 mv above the cold junction and the cold junction is 1.24 mv above the reference of the chart. The sum of the two voltages is 4.74 millivolts and, according to the chart, the actual temperature of the hot junction is 194°F.

The heat sensing devices described in this article deal with units which change in their physical characteristics for each change in temperature. The thermometer and the bi-metal strip respond to temperature variations by expansion or contraction of the sensitive parts; the thermistor changes its resistance, while thermocouples develop a voltage difference. In addition to the physical changes, there are heat sensors which detect a change in the characteristics of heat itself. These are the radiation-sensitive devices which will be described in the next part of this series. ▲

Auxiliary Sync

(Continued from page 21)

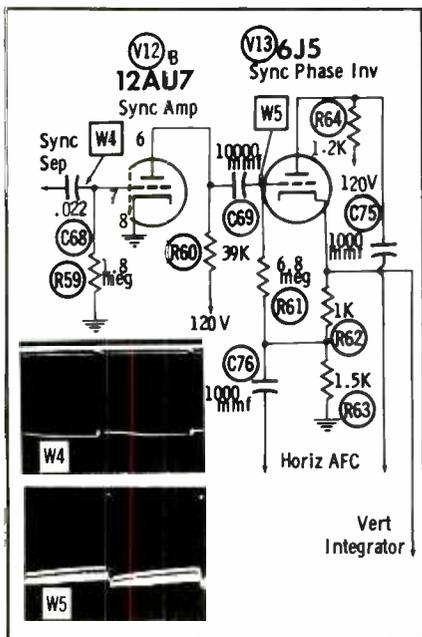


Fig. 3. Intermediate sync amplifier with grid input—Fada Model H274T.

separator and sync output. In this particular case, the extra stage V14A is a grounded-grid triode which amplifies the rather low-level output of the separator and applies it to a phase splitter. Any video information which might get through the separator tends to be eliminated by the amplifier, since video is the most positive portion of the signal at the cathode, and biases V14A beyond cutoff. The main job of this stage, however, is to provide sync pulses of fairly constant amplitude to the phase inverter. In order to do this, the sync tips must drive the tube into saturation, which they do during the reception of all usable signals. The grounded-grid stage does not invert the sync signal, but passes it on to the phase inverter in the same polarity as in Fig. 1.

Another intermediate amplifier is presented in Fig. 3. V12B is a conventional grid-fed stage which takes over the "sync-clipping" function normally handled "as a sideline" by the output stage of an ordinary two-triode circuit. Since V12B inverts the sync signal, the output from the phase splitter to the vertical sweep circuits must be taken from the cathode of the splitter, rather than from the plate as in Fig. 2.

Sync Preamplifier

Quite a few receivers have a
October, 1957 • PF REPORTER



**"REALIZING THAT WE'RE TAMPERING WITH THE
VERY FOUNDATIONS OF THE HOME LADY,
OUR FINAL TEST IS 5 MINUTES OF MUSICAL
APPRECIATION TO INSURE A FLAWLESS JOB . . ."**

Your customers, will renew their appreciation for music, Gus, when you use Webster replacement cartridges.

And there's a Webster for 'most any job you'll run into. Each one fits perfectly—and restores the original qualities to the player.

There's more money in it for you, too, because there's no call-backs — no unhappy customers.

BUY WISELY...BUY WEBSTER!



Model B202—3-speed; push-in mounting; clip-mounted needles.


Free—large print of this Lichy cartoon suitable for framing. Request on your own letterhead.

ELECTRONICS DIVISION

WEBSTER ELECTRIC
RACINE, WIS.



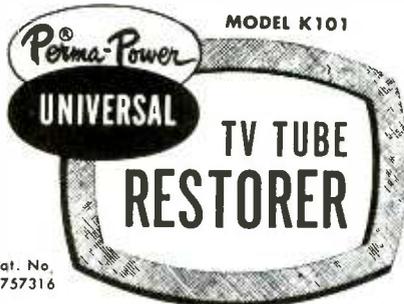"What say we organize a safari and hunt up a JENSEN NEEDLE."



Pat. No. 2757316

RESTORES PICTURE TO DEFECTIVE PICTURE TUBE OF ANY TV SET —

Model K-101
\$550
List Price



LOCATES AND CORRECTS FOR

- Open Cathode
- Heater-Cathode Short
- Open Control Grid
- Control Grid-Cathode Short
- Low Emission
- Combinations of above

Perma-Power COMPANY
3100 N. ELSTON AVE. • CHICAGO 18, ILLINOIS
There's Always Something NEW Being Developed by Perma-Power

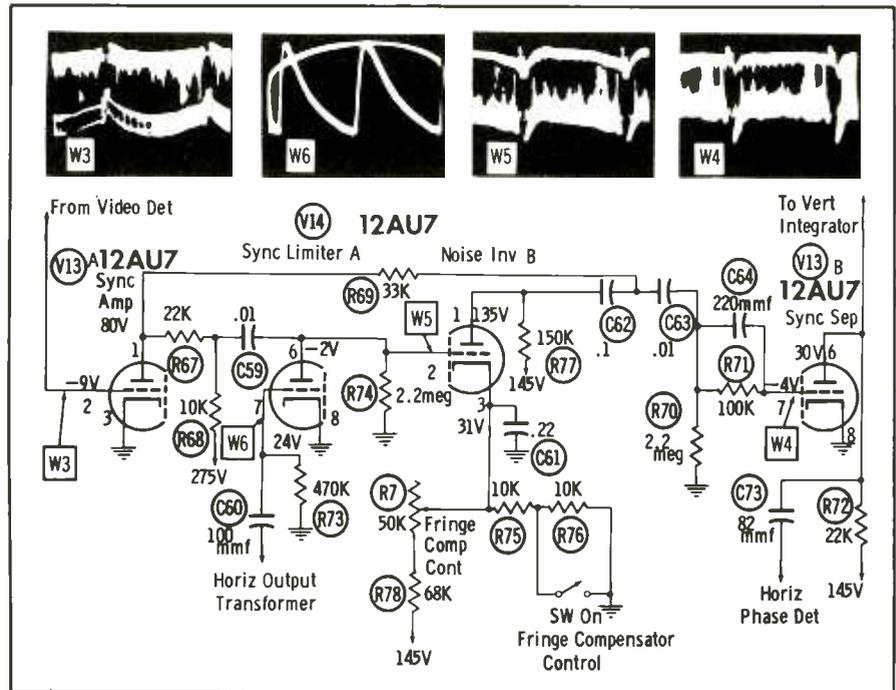


Fig. 4. Sync preamplifier and keyed noise inverter—Emerson Model 748B.

stage labeled "Sync Amp" which, on examination, actually precedes the sync separator. This type circuit will be classified as a "sync preamplifier" for discussion purposes. Its name is a bit misleading, since it is basically a video amplifier in which both the input and output are composite video signals. A sync preamplifier differs from a typical video output stage, however, in that the former requires no peaking coils or other components to boost the high-frequency response. A stage such as V13A in Fig. 4 needs only a wide enough bandpass to maintain reasonably steep-sided sync pulses.

Note that the input for V13A is taken from the video detector load circuit, and that the output is fed to the sync separator. This means that the preamp stage takes the place of the regular video amplifier in the path of the sync signal through the receiver.

Keyed Noise Inverter

Included in Fig. 4 is an unusual noise inverter circuit of a type found in several Sylvania and Emerson chassis. The sync-positive, composite video output of the sync amplifier V13A is fed through C59 to the grid of the noise inverter V14B, and the inverter is driven into conduction only by the peaks of strong noise pulses in this signal. Each time V14B conducts, it applies a nega-

tive pulse to the grid circuit of the sync separator via C62.

The inverter cannot properly set its own grid-leak bias because it is triggered only by random noise pulses and thus conducts irregularly. To provide a means of adjusting the inverter grid voltage to compensate for changes in the strength of the incoming signal, a sync limiter (V14A) is included in the circuit. This tube conducts only during horizontal retrace time, when it is keyed at the grid by a positive pulse obtained from the horizontal output transformer. The level of the sync pulse tips in the incoming signal determines the amount of conduction through V14A, which in turn determines the charge on C59. The RC circuit composed of C59 and R74 then establishes the grid voltage of V14B.

The bias on the limiter tube is also partly determined by the cathode voltage, which can be varied by a "Fringe Compensator" control. Adjustment of the control allows the technician to set the bias on V14B so that the entire input signal (including sync tips) will remain below the cut-off level; yet the bias must be such that noise pulses above the sync tip level will drive the tube into conduction.

In practice, the control is adjusted for the most stable picture obtainable on all weak channels.

In strong-signal areas, the control can be turned until it clicks "Off," placing extra resistance between the cathode of V14B and ground and increasing the bias on the tube to prevent it from conducting excessively.

Note that V14 is not absolutely essential for operation of the receiver. In low-noise areas, no difference in performance would be observed if this tube were entirely removed from the circuit.

Twin Separators


The conventional sync separator is really a compromise design, required to handle two pulses of widely different durations. Under some conditions, the horizontal and vertical sync pulses can interact and reduce sync stability. For example, consider what happens to the grid-leak bias of the separator tube each time a vertical pulse arrives. Being broad, this pulse draws grid current for a longer time than the horizontal pulses, and so it temporarily increases the bias on the separator. Then the first several horizontal pulses of each field are reduced in height. This effect is not normally severe enough to interfere with synchronization, but some conditions, such as an abnormally high contrast setting, may cause the shifts in pulse amplitude to affect horizontal AFC operation. Bending or twitching then occurs at the top of the picture.

If the vertical and horizontal pulses could be separated from the video signal by two different circuits, each designed to provide optimum conditions for one type of pulse, a highly stable sync system should be the result. Several such arrangements have actually been employed. In the circuit shown in Fig. 5, two triode separators are connected in parallel. Both are supplied with identical composite video signals, and both feed their output signals into a common sync amplifier. Notice the difference between the grid circuits of the two separators; while the vertical circuit has a conventional grid-bias network, the horizontal circuit derives its DC grid voltage from a divider across B+ so that it will be relatively unaffected by the vertical pulses.

New Automation Punched Card TV Tube Tester

PROVED!

IN OVER 1-MILLION TUBE TESTS!

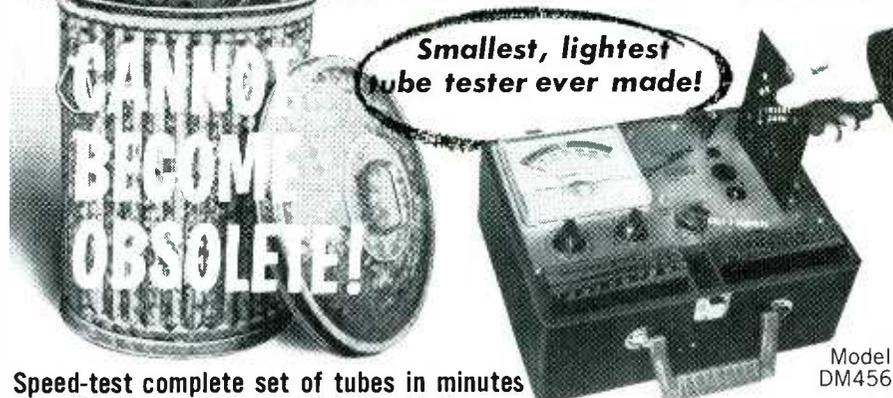


Speed-test complete set of tubes in minutes with the new DynaMatic Tube Tester

- So simple to use—a customer can operate it!
- **LIGHTEST** and **SMALLEST** Gm tester available. Take it on ALL house calls.
- Perforated plastic cards set up socket pin connections and test voltages.
- Permits full-complement tube testing.
- DynaMatic is a dynamic mutual conductance tester—NOT an emission checker.
- Accurately measures mutual conductance in micromhos on 2 ranges. 0-6000, 0-18000.
- Also checks battery tubes.

Model DM456
Dealer Net 149⁹⁵
 Price Slightly Higher West of Rockies
IMMEDIATE DELIVERY!



136-10 31st Rd., Flushing 54, N. Y.

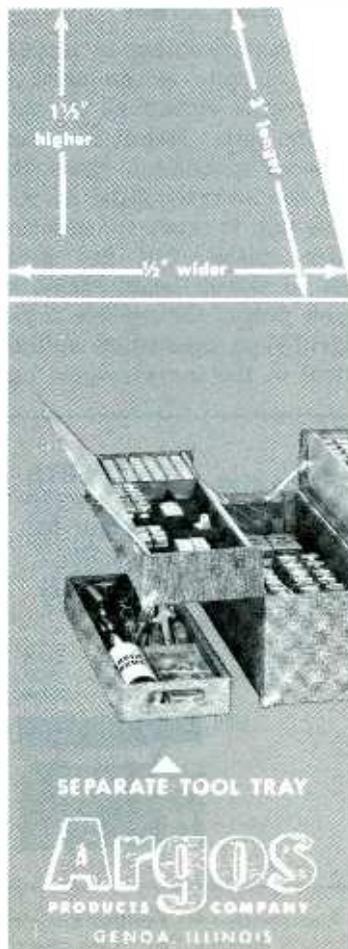

new

Super tube caddy

TRADE MARK®

carries 1/3 more

Biggest mile-saver ever offered. Built for the technician with ability to do more jobs on the spot—who would rather carry a few extra tools than lug a chassis.

Pays for itself quickly in time saved, and in getting more profits for efficient repair work.

TC-5
 \$21.95 net

Ask your Parts Distributor or write Dept. P

Other Tube Caddies

- TC-3 —225 tubes max.....\$16.95 Net
- TC-4 —262 tubes max.....\$15.95 Net
- TC-2A—143 tubes max.....\$10.50 Net

SEPARATE TOOL TRAY

ARGOS

PRODUCTS COMPANY
 GENOA, ILLINOIS

Craftsmanship in Cabinets

Another Sencore Time-Saver

SENCORE Handy "36" R-C Substitution Unit



"36" Most Often Needed Components At Your Fingertips!

3 pole, 12 position switch individually selects one of the "36" components for direct substitution.

Contains:

- ★ 12—1 watt 10% resistors from 10 ohms to 3600 ohms
- ★ 12—½ watt 10% resistors from 10K ohms to 3.6 megohms
- ★ 10—600 volt capacitors from 100-mmfd. to .5mfd.
- ★ 1—10mfd., 450V Electrolytic
- ★ 1—40mfd., 450V Electrolytic

Completely isolated

★ For Shop, Lab, or outside service AVAILABLE AT ALL PARTS DISTRIBUTORS!

ONLY \$1275 DEALER NET

POPULAR SENCORE PRODUCTS

- Transistor Tester
- Leakage Checker
- Filament Tester
- Voltage Regulator
- Bias Supply

SENCORE SERVICE INSTRUMENTS CORP.
171 OFFICIAL RD., ADDISON, ILL.

Cut out this ad now for further information.

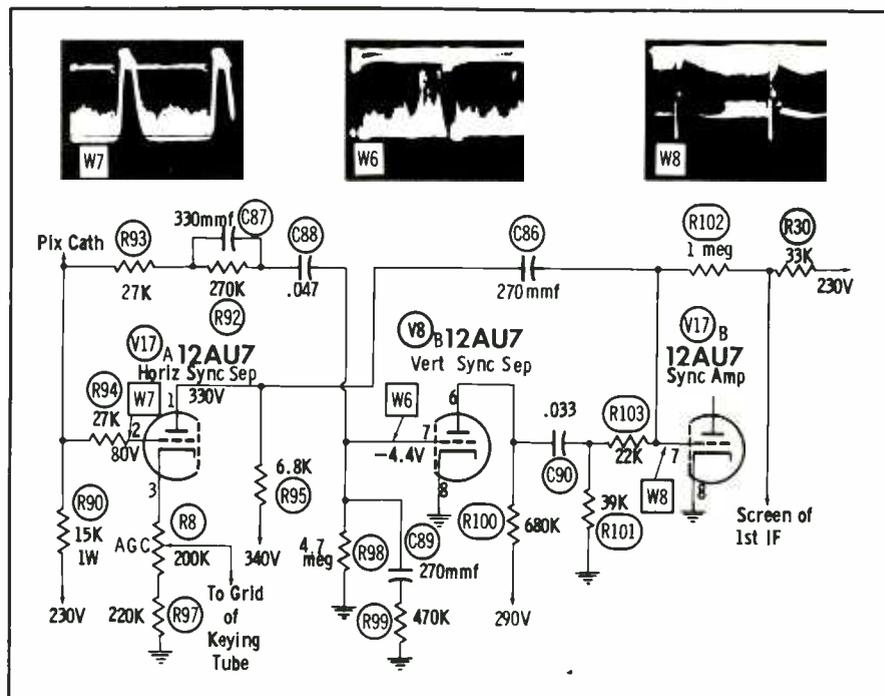


Fig. 5. Separate horizontal and vertical sync separators—ATR Model 26001.

In some other receivers, individually separated signals are not recombined at the sync amplifier grid, but pass through completely separate horizontal and vertical sync amplifiers.

Bias Setters

A constant problem in designing sync circuits is the need to allow for wide variations in input signal strength. Noise inverters are especially critical, since the bias on the inverter must be just great enough to cause cancellation of noise spikes, but not great enough to cause degeneration of the sync pulses themselves. Most pentagrid-type separators include a control in the inverter cir-

cuit which allows the DC bias on this grid to be varied to accomplish the desired results.

The use of a manual control offers a certain disadvantage in some areas where the available signals differ widely in strength. This factor is growing more important as the practical limits of "fringe areas" are being extended. An automatic bias clamper which takes care of this problem (Fig. 6) has been used in many General Electric sets. Inverter-grid voltage on the 6BY6 pentagrid separator is varied according to the conduction of bias clamper V6B, and conduction is controlled by the same AGC voltage which is applied to the IF strip. When input signal strength increases, the grid voltage goes in a negative direction and the clamper plate voltage accordingly rises. This positive swing of voltage is passed along to the inverter grid of the pentagrid tube. As a result, this grid has less bias and requires a greater input signal to effect tube cutoff on noise peaks. The composite sync signal coming into the circuit actually is somewhat larger, and so the balance of the circuit is maintained. Remember that the inverter-grid circuit is quite critical, so that a variation of less than a volt in signal amplitude at this point will have considerable effect.


HIGH FIDELITY BY



COMPONENTS-ACCESSORIES

AMPLIFIERS "quadnaural"
(TRADE MARK REGISTERED)

4 SPEAKER SYSTEM

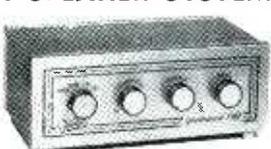

AS LOW AS **\$39.50** LIST

- RECORD COMPENSATORS
- RUMBLE FILTERS
- HI-PASS FILTERS
- LOW-PASS FILTERS
- SPEAKER SELECTORS
- TRI-SET COUPLERS
- MOLDED-ON CONNECTORS
- DUO-JACK ADAPTERS
- FILTER-TENNA

Sold by
Better Distributors Everywhere

Send for Catalog Sheets
on all Dynamic Products

Manufactured By
DYNAMIC ELECTRONICS-NEW YORK, INC.
Forest Hills, Long Island, N. Y.

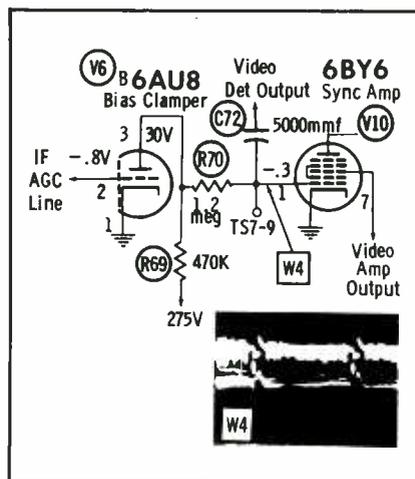


Fig. 6. Bias clamper for pentagrid separator—General Electric "ST" Line chassis.



Let's Talk Business

by H.M.Layden

HOW MUCH WILL IT COST TO FIX IT ?

Selling TV service today is like selling groceries, drugs, or any of a thousand and one other commodities clamoring for the consumer's dollar!

Take the situation where the technician finds a set with no raster but good sound. From these symptoms, what can he really tell about the over-all condition of the set? Let us suppose he accounts for the absent raster by testing for high voltage, which he finds missing. For all he knows, the CRT may be on its last legs or there may be trouble in the video section or in the sweep system. But all these would be hidden, as a consequence of the dark screen. Yet, when the technician tells the lady her set must go to the shop, invariably she wants to know, "How much will it cost to fix it?"

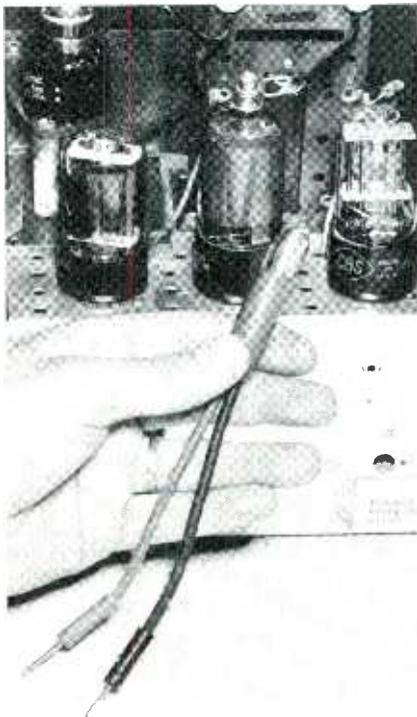


Fig. 1. Neon test lamp being used to check for the presence of oscillator energy at the horizontal output tube.

At this point the technician can do one of two things. He can gamble that the only malfunction is in the high voltage system, and base his cost-of-repair estimate on what he has learned from past experience. Or, if he is a fellow who has read this article, he can make a few simple tests to satisfy himself that his estimate won't put him out on a limb.

Customers have been known to live with a set in need of repair for months. It is only when the picture or sound goes completely out that they phone for service. All too often, you restore the set to proper operation and the customer hits the ceiling in indignation because you charged for "extras." Naturally, additional repairs were necessary to cure deficiencies of long standing, which the customer "swears" were not evident before you took the set to the shop! The only way to avoid a hassle of this sort is to know, at least approximately, the over-all condition of the set before you quote any repair charges.

Of course, if the technician is still mentally lingering in the past, when TV was a luxury, he might answer the question of cost with: "I won't know how much it will cost until I get the set on the bench." While such an answer may be honest, it is not altogether satisfactory today from the customer's standpoint. All she knows is that her viewing pleasure has been interrupted, and she wants the set back as soon as possible and at a price within her budget. Obviously, if the technician is to avoid a rupture in public relations, he must do something to get over the hurdle of hit-or-miss estimates.

With the limited equipment the average technician carries on a house call, it is unlikely that he will be in a position to give a com-

NEW E-Z-HOOK TIP



CONVERTS YOUR STANDARD TEST PROD TO A SELF-HOLDING CONNECTOR IN SECONDS!

Frees Your Hands • Won't Slip Off • Shock-Proof

For your special test Probe assemblies

Use the NEW E-Z-HOOK Custom PROBE

Pat No. 2702892



- ① Saves time and money
- ② Has the E-Z-Hook connector
- ③ Built-in terminal board

ORDER THROUGH YOUR PARTS DISTRIBUTOR

E-Z-HOOK TEST PRODUCTS TODAY
Dept. F, 1536 Woodburn Ave. Covington, Ky.

ask the "Man-on-the-Roof" why he prefers


South River



COMBINATION PEAK & FLAT ROOF MOUNT

MODEL PFM-30
(Fits Masts up to 1 1/2")

MODEL PFM-30 LM
(Fits Masts up to 2")

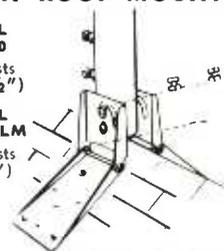

Features the patented South River "Walk-Up" — "Drop-Lock" mast socket for easy installation on either Peak, Flat or Pitched roofs. Heavy gauge pipe mast socket has two heavy duty screws and locknuts to secure mast. Factory assembled and supplied in a heavily plated rust resistant finish. U.S. PAT. #2734708

WRITE FOR NEW 1957 CATALOG

SOUTH RIVER
METAL PRODUCTS CO., INC.
South River, New Jersey

pioneer & outstanding producer of finest line of antenna mounts

prehensive estimate when the screen is without a raster. If his equipment is augmented by a few small aids, however, the situation can become tolerable. These aids consist of: a neon test lamp, a CRT emission indicator (which will operate from voltages available in the set), a set of tube-socket adapters (for octal and 7- and 9-pin miniatures) and a fused cheater cord. These items add little to the weight or bulk of a caddy, but in usefulness they are priceless.

Neon Test Lamp

A neon test lamp (Fig. 1) when immersed in a high potential AC field will glow without being directly connected to the potential. This feature makes such a lamp very useful when tracing high voltage around the flyback transformer and the horizontal output circuit. If the neon glows when the lamp is held close to the envelope of the output tube, it indicates that the horizontal oscillator is working. Furthermore, if the lamp glows when it is held five

inches from the high voltage rectifier tube, the chances are that the lack of high voltage at the second anode is due to a bad rectifier. This is a lot simpler and far safer than drawing an arc from the horizontal output plate.

A further use for the neon test lamp is in checking fuses. If the fuse is open, the lamp will glow when it is bridged across the fuse. If the fuse is in the primary circuit of the flyback transformer, it can be checked from the top of the chassis by touching one lead of the neon lamp to the plate of the output tube and the other to the chassis. The lamp will glow if the fuse is good.

CRT Emission Indicator

There is also much need for a small, easily-carried CRT emission indicator. A technician is not long in this game before he realizes, only too well, that you can't believe everything the customer says about his set. The picture tube may be on its death bed, but some customers never mention the dim screen they have been viewing for months. It is exasperating to cart a set to the shop for replacement of an open flyback, only to discover a dead or weak CRT. This is something the technician usually has not bargained for and naturally he dislikes calling the customer to alter his estimate. How much better it would be if he had some means by which he could check the picture tube before giving an estimate.

The most accurate method would be to use a commercially available CRT checker, but this is not always convenient on home calls. The schematic of a simple CRT checker which the technician can construct and carry in his case is shown in Fig. 2. The checker is inserted between the socket and the base of the CRT like a booster.

The second-anode connection should be removed from the picture tube and the set turned on. If there is any useful emission left in the tube, the lamp will glow. A switch in the grid lead permits the tube to be tested with the grid either floating or connected in the circuit. With the grid connected, manipulation of the set's brightness control should

**Our
Guarantee
is printed
on our
product**



On every packaged PLANET electrolytic capacitor sold through distributors you will find this statement:

GUARANTEED FOR ONE YEAR

Because PLANET CAPACITORS ARE "ENGINEERED FOR QUALITY", because they are carefully controlled through all stages of production and because the finished product is given a 100% electrical and mechanical check—our one-year guarantee is not only made possible, but is conservative.

Actually thousands and thousands of Planet capacitors five, six and even seven years old are performing excellently, every day, in TV and radio sets all around the world. When you solder a Planet capacitor into a circuit your guarantee of satisfactory performance is right there in front of you—and will be in the circuit for a long, long time. So when you order capacitors—order PLANET.

PLANET SALES CORPORATION

227 BELLEVILLE AVE.

BLOOMFIELD, NEW JERSEY

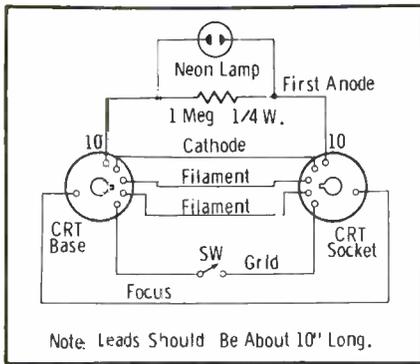


Fig. 2. CRT emission indicator which utilizes a neon lamp shunted by a 1-meg resistor in the first-anode lead.

vary the brightness of the lamp. At one extreme, the control should extinguish the lamp entirely, thus indicating beam cutoff.

Variation of the contrast control will indicate the presence or absence of picture information reaching the CRT. Flickering in the lamp indicates the signal is reaching the grid or cathode, depending on which is the driven element of the tube. This gadget is useful in those cases where the sound seems normal but the screen is dark. It is assumed, of course, that pin 10 is receiving first anode voltage and the heater is intact.

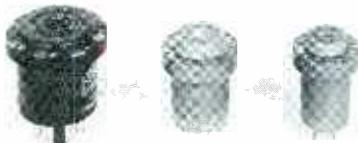


Fig. 3. Tube-socket adapters make it possible to measure pin voltages from the tube side of the chassis.

To test for first anode voltage, insert one leg of the neon test lamp in pin 10 of the CRT socket and touch the other to the chassis. The busy technician may find the neon test lamp more convenient than his meter in checking for the presence of voltages throughout the receiver. It is only a rough test, to be sure; but there are many occasions when a rough indication is all that is necessary.

Socket Adapters

The set of tube-socket adapters in Fig. 3 will often enable the technician to avoid the embarrassment of a wrong diagnosis. A typical example of this occurred recently with a late-model Zenith where snow was the problem. A

October, 1957 • PF REPORTER

new 6BQ7 RF amplifier, right out of the carton, failed to cure the trouble. The technician, knowing that trouble which involves dismantling of the tuner can be expensive, decided to check some voltages before breaking the news to the customer. To check voltages on a 6BQ7 requires, however, that the tube be in its socket since it is a dual-triode with direct coupling between sections. A 9-pin adapter was inserted in the socket, and the tube was placed in the adapter. The technician found that the plate of the first triode section

was not receiving DC voltage, possibly indicating an open element in the new tube! When another tube was used, the trouble was licked. This case poses an interesting question. Would the customer have given the technician the job if it had involved carting to set to the shop? Possibly yes, but then again, possibly not. "A bird in the hand, etc., etc.!"

Cheater With a Fuse

Now we come to the fused cheater, which also has a tale attached.

ALL OVER THE U.S.
utah **STANDS for**
UNSURPASSED SERVICE

Yes...
ALL OVER THE U.S.
UTAH STANDS for UNSURPASSED SERVICE

Yes, all over the U. S.—Utah stands for Unsurpassed Service.

US—Utah and the Service Man—because Utah stands behind you—the Service Man.

Utah stands behind you—with a speaker name that for over 30 years has signified the finest in quality, design, engineering and production.

Utah stands behind you with a speaker that gives installation performance. You can sell customer satisfaction with a Utah—because Utah gives performance satisfaction.

Utah stands behind you—with a secure source of supply. Leading jobbers all over the U. S. handle Utah—because Utah has the finest and widest line of replacement speakers available to the trade.

Utah your one complete speaker source auto * Rear Deck Kits * Standard Replacement * Television * Public Address * High Fidelity * Outdoor * Inter-Com * Wood & Metal Baffles

Utah is your one, complete satisfactory speaker source. When you order speakers today — **THINK**—then order Utah.

Get your **FREE** copy of the latest Utah Catalog S-157 listing over 100 replacement speakers. Available at your distributors or write direct.

utah **RADIO PRODUCTS CORPORATION**
HUNTINGTON • INDIANA

Export Dept. Fidevox International, Chicago, Illinois

EXCLUSIVE! NEW!

SINGLE POLE INSTANT HEAT GUN

Makes Soldering
Easier and Safer!



AT LAST!
A SINGLE POLE
INSTANT-HEAT
SOLDERING
GUN

THE LONG THIN REACH (over 5 inches) of this exclusive new "Gregg 250" soldering gun permits deep-in-close work to be done easily without danger of damage to other components and insulation.

This single pole built-in transformer type gun heats instantly in 2 SECONDS—no waste time—no waste current—greatly increases the life of the tip. Gregg guns pay for themselves in weeks. **LOW COST REPLACEABLE GREGG PENCIL AND CHISEL TIPS.** Tip change in seconds now a reality with the "Gregg 250." No need for set screws, wrenches or trouble, simply unscrew and change using only finger pressure.

CHANGEABLE POLE LENGTHS. The "Gregg 250" offers additional soldering convenience and savings with changeable barrel assemblies available in standard length and in other desired lengths by special order.

Pre-focused spot light instantly locates even the deepest work.

See your local jobber or write direct to:

Write for circular on printed circuit tips for Gregg gun; P-KIT-1.

GREGG ELECTRIC CO.

Dept. PF 2 South Broadway

Lawrence, Mass.



Fig. 4. Cheater cord fitted with Elmenco plug and a pair of 5-amp fuses.

A call came in on a set which was blowing the house fuse. The owner had located the fuse box in the basement, replaced the fuse, and then witnessed the lights fail again in a few moments. He summoned an electrician, who quickly traced the short to the TV set.

When the TV technician arrived and examined the clues, he suspected a DC short, since the lights had come on and had remained on briefly. He wasn't sure however. It might be an AC short in the transformer; in which case, if he tried the power, he would have to stumble around in the basement to replace the fuse. To avoid this, he used a fused cheater cord (Fig. 4) carried just for such cases. With this arrangement, he was able to watch for the cherry-red glow in the 5U4's commonly associated with a DC short and at the same time prevent the house fuse from blowing if it was an AC short. It paid off—the trouble proved to be a DC short in the primary of the audio output transformer.

Selling TV service today is a highly competitive business. TV has long since left the lap of luxury for the more mundane ranks of an everyday necessity. Homo Sapiens Americanus would sooner go without a meal than be deprived of his "window on the world." But this does not mean he will not shop around when his set needs service.

He is on a budget, like everyone else. His pay check is often spent in advance paying for things he thinks he needs. He will watch any cash outlay, such as TV repairs, like a hawk. This puts the TV technician in an unenviable position. He must see to it that his customers, pressed as they are with bills and not above seeking something for nothing, do not find it at his expense! ▲

SO SAFE!




won't damage glass tubing
let alone wire or cable!

ARROW STAPLE GUNS can't damage wire or cable because driving blade automatically stops staple at right height! That's why Arrow Staple Guns are proved safer on jobs all over the country. And Arrow staples have tremendous holding power because they're rosin-coated, have diverging points that lock into wood.

T-25 (shown) for wires up to 1/4" in diameter. (Hi-Fi wire, radiant heating, bell, thermostat, telephone, inter-com, etc.) tapered striking edge gets into tight corners. Uses 3/8", 1/2", and 5/8" staples. List \$15
T-25B For burglar alarm wiring. Drives staples flush . . . List \$15
T-75 For non-metallic sheathed cable, Romex cable or any other object (such as copper tubing) up to 1/2" in diameter. Uses 3/8", 1/2", and 5/8" Arrow staples List \$15

ARROW FASTENER COMPANY, INC.

ONE JUNIUS STREET, BROOKLYN 12, N. Y.

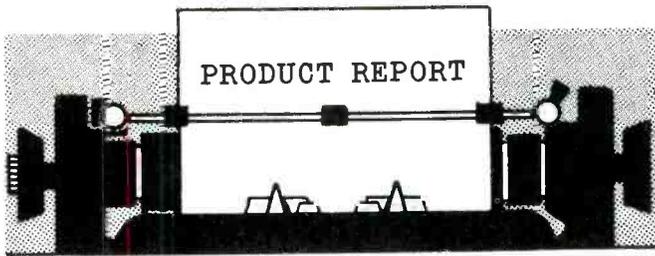


Cartridge-Needle Combination



Astatic Corp., Conneaut, Ohio, has announced the "Soundflo," a plug-in combination ceramic cartridge and needle with frequency response from 30-15,000 cps. The unit includes both 1- and 3-mil synthetic sapphire tips, or an optional 1-mil diamond tip. A complete kit, used to install the "Soundflo" in place of another cartridge, consists of a cartridge-needle assembly plus a holder that fits any standard manual or changer arm. Two basic versions are available—Model 81TB with 1-volt output and compliance greater than 1, and Model 89TB with 1.3-volt output and compliance greater than 2.

Adapter for CRT Tester

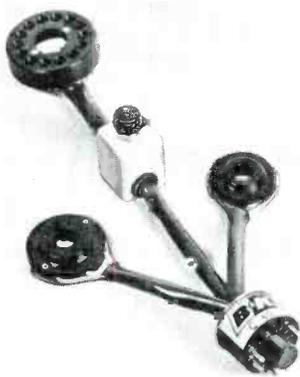

B & K Mfg. Co., 3731 N. Southport Ave., Chicago, Ill., is offering a new Model C40 Adapter that equips B & K Cathode Rejuvenator Testers (Models 400 and 350) for checking 110° and color picture tubes. Both types of new 110° tube bases are included so that all testing and rejuvenating operations can be performed on these tubes. In addition, all three guns of a color tube can be checked, one at a time. User's net price of the accessory is \$9.95.


Multiple-Branded Picture Tubes

To help simplify the service industry's picture tube stock requirements, Sylvania Electric Products, Inc., has introduced 26 new multiple-branded types, specifications of which are controlled so that these tubes will serve as exact replacements for a total of 60 regular types. Examples of the multiple types are: 17ATP4A/17AVP4A, 17HP4/17RP4, 20CP4B/20DP4B, 21ALP4A/21ALP4B, 21ATP4/21ATP4A, 21XP4/21AYP4, and 24CP4A/24VP4A/24ADP4/24TP4.

IT'S NEW! IT'S A BARGAIN! IT'S "IN THE BAG"!

VACO®
5-PIECE
ALL HOLLOW SHAFT
**Nut Driver
Kit**
No. K 505

Only
\$3.68
NET

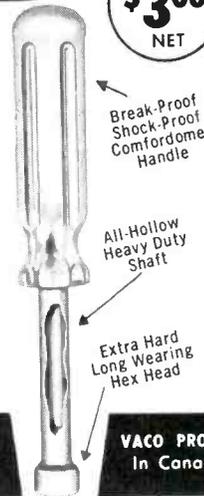

Convenient! Compact!

Here's a practical, quality built nut driver kit . . . economically priced, too! 5 popular sizes . . . 3/16", 1/4", 5/16", 11/32", 3/8" ideal for every service need . . . in one convenient plastic bag with button-down flap to keep drivers in place! Made to VACO professional quality standards throughout backed by our famous unconditional guarantee.

See Your Parts Distributor, Today!

VACO PRODUCTS CO., 317 E. Ontario St., Chicago 11, Ill.
In Canada: ATLAS RADIO CORP., Toronto 10, Ontario

Columbia

Contro-Roller

STOPS TV KNOBS FROM TURNING TOGETHER

- ★ Simple Half Minute Installation
Any set owner can do-it-himself without tools.
- ★ High Quality Precision Bearings
- ★ Simple to Display
- ★ Easy to Sell

Twenty-five million TV sets in America have two knobs on one shaft (concentric controls). The two knobs usually turn together — in fact it is often impossible to turn one knob without the other knob turning with it. Contro-Roller stops this!

Catalog No. 888 DISPLAY CARD OF 24 PACKAGES
Every Service Dealer should have a display card of 24 Contro-Roller sets on his counter!

WRITE FOR COMPLETE CATALOG TODAY!

Columbia **WIRE & SUPPLY CO.**
2850 Irving Park Road Chicago 18, Illinois
"America's Most Complete Wire Line"

IT'S Blue Chip



Quality

Tung-Sol Magic Mirror Aluminized Picture Tubes mirror twice the light to create a picture twice as bright. They bring out the best in every set. Install these superior tubes and see the difference . . . the difference that pays off in smooth, callback-free service and satisfied customers. Tell your supplier you'd rather have Tung-Sol Tubes.

Blue Chip Quality

ts TUNG-SOL®

Magic Mirror Aluminized
PICTURE TUBES

TUNG-SOL ELECTRIC INC., Newark 4, N. J. Sales Offices: Atlanta, Ga.; Columbus, Ohio; Culver City, Calif.; Dallas, Tex.; Denver, Colo.; Detroit, Mich.; Irvington, N. J.; Melrose Park, Ill.; Newark, N. J.; Seattle, Wash.

Marker and Sweep Generators



A new crystal-calibrated marker generator, WR-99A, is being produced by RCA Components Division, Camden, N.J. This instrument covers a frequency range of 19 to 260 mc in eight bands, with crystal calibration points at 1-mc intervals.

Its slide-rule dial scale is linked to the band switch so that the portion of the dial corresponding to the band in use is automatically displayed. User price is \$242.50.

Also new from RCA is the WR-69A TV-FM Sweep Generator (\$295), which includes two built-in variable bias supplies and a video sweep for alignment of color TV sets.


Hi-Fi Console Cabinets



The "Viscount" console cabinet manufactured by Electro-Voice, Inc., Buchanan, Mich., is designed to accommodate a hi-fi amplifier, tuner, and record changer of the user's choice, and is styled to match the "Empire," "Centurion," and other E-V speaker enclosures.

The lid can be lifted and the cabinet front tilted to give access to components. A differently styled "Sovereign" console is also offered as a companion to the E-V "Suzerain" enclosure. Both consoles are available in mahogany, limed oak, and walnut finishes.

Screw-Holding Screwdriver

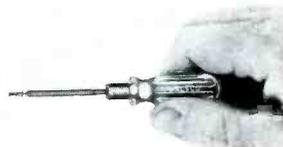

Walsco Electronics Mfg. Co., 100 W. Green St., Rockford, Ill., has introduced a new "Mini-hold" screwdriver (Catalog No.


2568) which can grip a tiny #1 to #4 screw with a wedge action, thus providing greater convenience in working with miniature screws such as those found in phono cartridges. Over-all length of the tool is 2 $\frac{7}{8}$ "; dealer net price is \$1.98.

Multi-Purpose Tool




The "Crimcut" combination tool designed by Vaco Products Co., 317 E. Ontario St., Chicago, Ill., features jaws for crimping wire, five holes for shearing common sizes of bolts and screws, wire-cutting edges $\frac{1}{2}$ " long, and a row of six slots for stripping insulation off various sizes of wire from #10 to #22. The tool is 8" long and is chrome-plated with plastic-covered handles.

Handy AC Plug

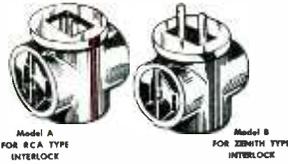

The "Cheater Cube" developed by R-Columbia Products Co., Inc., Highwood, Ill., is a three-way AC outlet which plugs into the back cover of a TV set after the cover has been taken off, enabling the technician to utilize the receiver's line cord as a convenient source of AC power for soldering irons, lamps and other accessories during repair work in the home. The cube is available in two models, Type A to fit RCA-style interlocks and Type B to fit Zenith interlocks.

Snap-Together Dual Controls

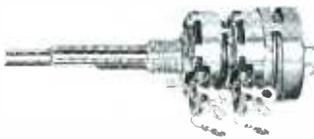

P. R. Mallory & Co., Inc., Indianapolis, Ind., has introduced a new line of controls which can be custom-assembled by the distributor into almost any desired dual-concentric combination. Assembly takes under a minute, since it consists of only three operations as follows: A shaft (selected from a wide assortment of pre-cut parts) is attached to each of two preassembled controls, and then these two subassemblies are fastened together with a built-in snap-action coupling.

Replacement Capacitors




Good-All Electric Mfg. Co., Ogallala, Nebr., is now supplying its Type 600-UE "Mylar" dielectric capacitors to the replacement market. These units, molded in epoxy resin, have previously been used by original equipment manufacturers. Competitively priced, the line features long life and excellent resist-

ance to humidity.

Capacitors of 43 often-used values, mounted on cards wrapped in plastic film, are being featured on a display "tree" made from a cedar log. Each card includes either two, three, or four identical pieces.

Air-Dielectric Bowtie

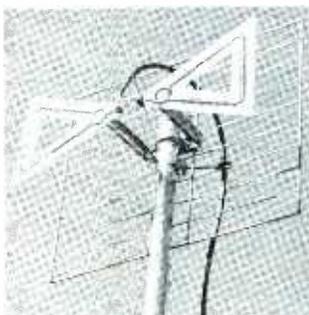

Technical Appliance Corp. (TACO), Sherburne, N. Y., has announced a new weather-resistant UHF bowtie antenna for strong-signal areas, the Model 3011 "Golden Grid." The dipole elements are supported on brackets designed so that the lead-in terminals are separated by an air gap instead of a solid dielectric. This arrangement helps prevent signal losses in wet weather and, incidentally, reduces vibration of the elements in strong winds. Stacking lines are available for making two-bay installations.

October, 1957 • PF REPORTER

IT'S Tung-Sol



Quality

Tung-Sol receiving tubes for TV, radio and Hi-Fi replacement are exactly the same as those supplied to leading independent set makers. This one quality—Blue Chip Quality—is your assurance of long, trouble-free service that keeps customers with you year after year. Tell your supplier you'd rather have Tung-Sol Tubes.

Blue Chip Quality

TUNG-SOL®
RECEIVING TUBES

TUNG-SOL makes All-Glass Sealed Beam Lamps, Miniature Lamps, Signal Flashers, Picture Tubes, Radio, TV and Special Purpose Electron Tubes and Semiconductor Products.

Advertisers	Page No.
Admiral Corp.— Special Products Div.	73
Aerovox Corp.	8
American Television & Radio Co. (ATR)	34
Amphenol Electronics Corp.	46
Anchor Products Co.	36
Argos Products Co.	79
Arrow Fastener Co.	84
Astron Corp.	7
B & K Mfg. Co.	9
Bussmann Mfg. Co.	35
CBS-Hytron	37
Centralab, A Div. of Globe-Union, Inc.	62, 63
Chicago Standard Transformer Co.	43
Circuit Mfg. Co.	76
Clarostat Mfg. Co., Inc.	33
Columbia Wire & Supply Co.	85
Cornell-Dubilier Electric Corp.	72
DuMont Labs., Inc., Allen B.	25
duPont, de Nemours & Co., Inc., E. I.	12-13
Dynamic Electronics, New York, Inc.	80
EICO	44
Electro-Voice, Inc.	53
Electronic Publishing Co.	76
Elgin Nat'l. Watch Co. (Electronics Div.)	28
E-Z-Hook Test Products	81
General Cement Mfg. Co.	38
General Electric Co.	39
General-All Electric Mfg. Co.	11
Gregg Electric Co., Inc.	84
Hexacon Electric Co.	75
Hickok Electrical Instrument Co.	41
International Resistance Co. (IRC)	2nd cover
Jackson Electrical Instrument Co.	65
Jensen Industries, Inc.	78
Jerrold Electronics Corp.	66, 67
Kedman Co.	36
Kingston Electronic Corp.	26
Littelfuse, Inc.	4th cover
Mallory & Co., Inc., P. R.	54, 55
Merit Coil & Transformer Corp.	50
Ohmite Mfg. Co.	52
Perma-Power Co.	78
Phaotron Instrument & Electronic Co.	71
Planet Sales Corp.	82
Pyramid Electric Co.	51
Quam-Nichols Co.	58
Radiart Corp.—Cornell- Dubilier Electric Corp.	1
RCA Components Div.	27, 65
RCA Electron Tube Div.	3rd cover
Raytheon Mfg. Co.	6, 18-19
Recoton Corp.	70
Sams & Co., Inc., Howard W.	48, 59, 64
Sangamo Electric Co.	45
Seco Mfg. Co.	75
Service Instruments Corp.	80
Simpson Electric Co.	68
Sonotone Corp.	69
South River Metal Products Co.	81
Sprague Products Co.	2
Sylvania Electric Products, Inc.	4-5
Technical Appliance Corp. (TACO)	29
Teletest Instrument Corp.	79
Tenna Mfg. Co.	32
Tobe Deutschmann Corp.	57
Triplett Electrical Instrument Co.	31
Tung-Sol Electric, Inc.	86, 87
Utah Radio Products Corp.	83
Vaco Products Co.	85
Walsco Electronics Mfg. Co.	61
Ward Products Corp.	74
Webster Electric Co.	77
Westinghouse Electric Co.	47
Winston Electronics, Inc.	49
Xcelite, Inc.	70

- 11J. **AMPHENOL**
New Dealer Catalog with part numbers and prices of antennas, twin lead, accessories, connectors, cables, sockets and plugs. *See ad page 46.*
- 2J. **ANCHOR**
Literature on connecting cables, replacement parts, service aids, (CRT ext. cables adapters, pilot light). *See ad page 36*
- 3J. **ARGOS**
New 6-page catalog lists data on the new Super Tube Caddy (3,300 cu. in.). *See ad page 79.*
- 4J. **B & K**
Bulletin 1050 tells how you can transmit video and audio to any TV set with new Model 1050 Dyna-Scan. Bulletin 650 describes the new Model 650 Dyna-Quik portable dynamic mutual conductance tube and transistor tester. Bulletin 400-C40 describes CRT Cathode Rejuvenator Tester. *See ad page 9.*
- 5J. **BELDEN**
New electronic wire and cable catalog.
- 6J. **BUSSMANN**
Television fuse chart Form TVC. Shows components protected and proper fuse for all TV and auto radio sets. *See ad page 35.*
- 7J. **CBS-HYTRON**
Catalog sheet describing "Engineer's Handbook and Technician's Handbook." *See ad page 37.*
- 8J. **CHICAGO STANDARD**
Stancor TV Transformer Replacement Guide and supplemental sheets. *See ad page 43.*
- 9J. **CLAROSTAT**
TV & radio line voltage regulators—Form No. 751772. *See ad page 33.*
- 10J. **CORNELL-DUBILIER**
Reference guide 200D-4E on electrolytic capacitors. *See ad page 72.*
- 11J. **DYNAMIC**
Booklet entitled "Accessories and Service Aids to Help Solve Most Hi-Fi and TV Problems." *See ad page 80.*
- 12J. **EICO**
12-page catalog shows how to save 50% on electronic test instruments and hi-fi equipment in both kit and factory-wired form. *See ad page 44.*
- 13J. **ELECTRO-VOICE**
Power Point Interchangeability Guide, a complete cross-reference of hundreds of phono-cartridges and their correct Power Point replacements. Also, "ABC's of Microphones," a primer on microphone application. *See ad page 53.*
- 14J. **E-Z-HOOK**
A convenient reference sheet titled "How to Build the Five Most Useful Scope Probes" gives the schematic, mechanical component layout, and a brief description of five scope probes you'll find most useful in your servicing. *See ad page 81.*
- 15J. **HICKOK**
New 8-page technical brochure describing functions of circuits used in latest methods of tube testing. *See ad page 41.*
- 16J. **IRC**
DLR-57 (form S035A) dealer replacement parts catalog. *See ad 2nd cover.*
- 17J. **JACKSON**
Condensed catalog sheet listing all products. *See ad page 65.*
- 18J. **JENSEN INDUSTRIES**
Jensen needle sales aids. *See ad page 78.*
- 19J. **JERROLD**
"Aids to Better Televiewing"—new jobber product line catalog. Gives complete details on equipment for improving TV reception in the home; TV distribution systems; accessories and test equipment. *See ads pages 66, 67.*
- 20J. **KEDMAN**
Catalog sheet describing 4 screw-driver displays and specifications of 14 kinds of screwdrivers in the company's line. *See ad page 36*
- 21J. **KINGSTON**
"Puts Money in the Pockets of TV Servicemen," a 4-page, two-color brochure, gives details on the operation of the Kingston Absorption Analyzer. *See ad page 26.*
- 22J. **LITTELFUSE**
Handy cross-reference card showing LC fuses and list prices. *See ad 4th cover.*
- 23J. **MERIT**
Merit exact replacement wall chart—No. 700. *See ad page 50.*
- 24J. **PERMA-POWER**
Illustrated brochure to be used as an envelope stuffer describes the new line of Picture Tube Restorers. Also, brochure describing color service aids, featuring the new Color Gun Killer and Color Kinescope Adapter. Technical catalog sheet describing the A-400 Transistor Power Supply. *See ad page 78.*
- 25J. **QUAM-NICHOLS**
Catalog sheet (S757) on full line of all PA, intercom and outdoor speakers. *See ad page 58.*
- 26J. **RCA ELECTRON TUBE DIV.**
Folder describing new RCA color "Pict-O-Guide." *See ad 3rd cover.*
- 27J. **SECO**
Complete information on the features and operation of the new Seco Model 107 Tube Tester plus a folder on other instruments. *See ad page 75*
- 28J. **SENCORE**
Two-color line folder of all Sencore products (Form #106). *See ad page 80.*
- 29J. **SOUTH RIVER**
New 1957 catalog on antenna mountings and accessories, magnesium extension and stepladders. *See ad page 81.*
- 30J. **TELETEST**
Literature on the new "Dynamic" Automatic Tube Tester—Model DM456. *See ad page 79.*
- 31J. **TACO**
Promotional Kit on the "Golden Topliners." *See ad page 29.*
- 32J. **TRIAD**
Triad Replacement Guide, TV-57.
- 33J. **TOBE DEUTSCHMANN**
New 26-page catalog on Quality Service Capacitors. *See ad page 57.*
- 34J. **TRIPLETT**
New catalog No. 35-T on test equipment. *See ad page 31.*
- 35J. **V-M CORP.**
C-13-FO line folder.
- 36J. **WARD**
Mailing folder "The Shape of Things to Come." *See ad page 74.*
- 37J. **WINSTON**
One-page flyer on full line of equipment. *See ad page 49.*
- 38J. **XCELITE**
New catalog of company's products. *See ad page 70.*

ORDER YOUR SUBSCRIPTION TODAY TO THE INDUSTRY'S LEADING MAGAZINE -

PF REPORTER

★ SUBSCRIPTION ORDER CARD ★

Please enter my subscription to PF REPORTER for:

- 1 Year \$3.00 2 Years \$5.00 3 Years \$7.00

Bill Me Remittance Enclosed*

Add 60¢ per year postage for Canada and Pan-America; \$3.00 per year for all other foreign countries.

Give to your parts distributor or mail to
PF REPORTER, 2201 East 46th Street, Indianapolis, Ind.

Name _____

Firm _____

Address _____

City _____ Zone _____ State _____

- Independent Serviceman Full-Time
 Dealer with Service Shop Part-Time
 Service Manager Student
 Other (please explain) _____

* Two extra issues free if remittance accompanies order.

Please send me the following literature checked below:

Please indicate number of items you have checked.

1	J	20	J	2	J	21	J	3	J	22	J	4	J	23	J	5	J	24	J	6	J	25	J	7	J	26	J	8	J	27	J	9	J	28	J	10	J	29	J	11	J	30	J	12	J	31	J	13	J	32	J	14	J	33	J	15	J	34	J	16	J	35	J	17	J	36	J	18	J	37	J	19	J	38	J
---	---	----	---	---	---	----	---	---	---	----	---	---	---	----	---	---	---	----	---	---	---	----	---	---	---	----	---	---	---	----	---	---	---	----	---	----	---	----	---	----	---	----	---	----	---	----	---	----	---	----	---	----	---	----	---	----	---	----	---	----	---	----	---	----	---	----	---	----	---	----	---	----	---	----	---

Print plainly or type below

Name _____

Firm _____

Firm Address _____

City _____ Zone _____ State _____

Has your address changed since you last wrote us No Yes

To guarantee receipt of literature please check one of boxes below:

- Independent Serviceman Full-Time
 Dealer with Service Shop Part-Time
 Service Manager Student
 Other (please explain) _____

OFFER GOOD ONLY UNTIL DEC. 1, 1957

FIRST CLASS
PERMIT No. 1076
(Sec. 34.9, P. L. & R.)
Indianapolis, Ind.

BUSINESS REPLY CARD
No Postage Stamp Necessary If Mailed in the United States

3¢ POSTAGE WILL BE PAID BY

PF REPORTER

Reader's Literature Service Dept.

2201 EAST 46TH STREET
INDIANAPOLIS 5, IND.



FIRST CLASS
PERMIT No. 1076
(Sec. 34.9, P. L. & R.)
Indianapolis, Ind.

BUSINESS REPLY CARD
No Postage Stamp Necessary If Mailed in the United States

3¢ POSTAGE WILL BE PAID BY

PF REPORTER

2201 EAST 46TH STREET
INDIANAPOLIS 5, IND.



Supplement to Sams August, 1957 Master Index

This Supplement is your handy index to the new models covered by PHOTOFAC Coverage since August, 1957. For prior model coverage see the Sams Master Index dated August, 1957. To stay up-to-date, always use the latest issue of this supplement *with* the Sams Master Index—together, they are your complete index to PHOTOFAC coverage of over 28,000 receiver models.

PHOTOFAC Coverage for

OCTOBER, 1957

(Set Numbers 369 through 375)

IMPORTANT: DISCARD ALL PRIOR SUPPLEMENTS

	Set No.	Folder No.
ADMIRAL		
Chassis 4P2	374	-1
Chassis 7L1	375	-6
Chassis 7M1	369	-1
Chassis 8B1 (See Photofact Servicer)	373	
● Chassis 14YP3D, DK, DM	370	-1
● Chassis 17AF1	367	-13-5
● Chassis 17AF1	367	-13-5
● Chassis 201Z, Z (See Photofact Servicer)	373	
● Chassis 23B1AZ (See Photofact Servicer)	374	
● Chassis 23E1AZ, 23E1Z (See Photofact Servicer)	375	
● Chassis 23F1Z (See Photofact Servicer)	374	
● C2516Z, C2517Z (Ch. 23E1AZ, Z) (See Photofact Servicer)	375	
● CA2236A (Ch. 201Z, Z) (See Photofact Servicer)	373	
● CU2516Z, CU2517Z (Ch. 23F1Z) (See Photofact Servicer)	374	
● F2817Z (Ch. 23B1AZ) (See Photofact Servicer)	374	
● FA2226 (Ch. 201Z, Z) (See Photofact Servicer)	373	
● H2516Z (Ch. 23E1AZ, Z) (See Photofact Servicer)	375	
● H2816Z (Ch. 23B1AZ) (See Photofact Servicer)	374	
● HU2516Z (Ch. 23F1Z) (See Photofact Servicer)	374	
● T18A11, T18A12, T18A13 (Ch. 17F1)	367	-13-5
● T170, T171, N, T172AL, T173AL (Ch. 14YP3D)	370	-1
● T1710 (Ch. 14YP3D)	370	-1
● TA1811, TA1812, TA1813 (Ch. 17AF1)	367	-13-5
● TA2216A, TA2217A (Ch. 201Z, Z) (See Photofact Servicer)	373	
4P21, 4P22, 4P24, 4P28 (Ch. 4P2)	374	
7C64 (Ch. 8B1) (See Photofact Servicer)	373	
7L12, 7L14, 7L16, 7L18 (Ch. 7L1)	375	-6
7M12, 7M14, 7M16, 7M18 (Ch. 7M1)	369	-1
AIRLINE		
GAA-861A, GAA-862A, GAA-863A	369	-2
GAA-864A	374	-2
● GTM-4031A, GTM-4032A	364	-18-5
● GTM-4131A, GTM-4132A	364	-18-5
ALLSTATE		
5028 (Ch. 528.50280, 1)	372	-1
5033 (Ch. 528.50330, 1)	372	-1
Ch. 528.50280, 528.50281	372	-1
Ch. 528.50330, 528.50331	372	-1
ANDREA		
CP-12W (Ch. PA, P12W)	369	-3
W69P	371	-1
Ch. PA	369	-3
Ch. P12W	369	-3
BRAUN		
MM3	375	-7
BUICK		
981813	369	-4
BULOVA		
100, 110	371	-2
220 Series	372	-2
230 Series	372	-2
270 Series	369	-5
300 Series	369	-6
310, 320 Series	370	-2
CADILLAC		
7268005	370	-3
7268035	370	-3
COLUMBIA RECORDS		
512, 540	373	-1
CORONADO		
● TV2-9422A, TV2-9423A, TV2-9424A, TV2-9425A	342	-16-5
● TV3-9395A	373	-2
● TV3-9401A	374	-3
● TV3-9404A	361	-4
● TV3-9408B, TV3-9409B, TV3-9410B, TV3-9411B	361	-4

	Set No.	Folder No.
CRAFTSMEN (Also See Radio Craftsmen)		
CTA-5	369	-7
DUMONT		
RA-378, RA-379	373	-3
● RA-392, RA-393, A	373	-4
● RA-394, RA-395	372	-3
● RA-902	375	-8
1210	375	-8
Balladier	373	-3
Minstrel	373	-3
EMERSON		
845B (Ch. 120321B)	369	-8
851B (Ch. 120327B)	372	-4
852B (Ch. 120334B)	372	-4
853B (Ch. 120335B)	372	-4
854A, B (Ch. 120321B)	369	-8
865B (Ch. 120243B)	287	-7
867B (Ch. 120349B)	370	-4
● 1212 (Ch. 120351E)	365	-16-5
● 1213 (Ch. 120352G)	365	-16-5
● 1228 (Ch. 120351E)	365	-16-5
● 1229 (Ch. 120352G)	365	-16-5
● 1238 (Ch. 120351E)	365	-16-5
● 1239 (Ch. 120352G)	365	-16-5
● 1244 (Ch. 120351E)	365	-16-5
● 1245 (Ch. 120352G)	365	-16-5
● 1246 (Ch. 120351E)	365	-16-5
● 1247 (Ch. 120352G)	365	-16-5
● 1254 (Ch. 120341H)	365	-16-5
● 1255 (Ch. 120342R)	365	-16-5
● 1264 (Ch. 120341H)	365	-16-5
● 1265 (Ch. 120342R)	365	-16-5
● 1272 (Ch. 120351E)	365	-16-5
● 1273 (Ch. 120352G)	365	-16-5
● 1274 (Ch. 120351E)	365	-16-5
● 1275 (Ch. 120352G)	365	-16-5
● 20345, 20385 (Ch. 120345V)	363	-21-5
● 20405, 20425 (Ch. 120346V)	363	-21-5
● 2056 (Ch. 120343E)	363	-21-5
● 2057 (Ch. 120344G)	363	-21-5
● 2058 (Ch. 120343E)	363	-21-5
● 2059 (Ch. 120344G)	363	-21-5
● 2060 (Ch. 120343E)	363	-21-5
● 2061 (Ch. 120344G)	363	-21-5
● 2062 (Ch. 120343E)	363	-21-5
Ch. 120343B	287	-7
Ch. 120321B	369	-8
Ch. 120327B	372	-4
Ch. 120334B	372	-4
Ch. 120335B	372	-4
Ch. 120341H	365	-16-5
Ch. 120342R	365	-16-5
Ch. 120343E	363	-21-5
Ch. 120344G	363	-21-5
Ch. 120345E, V	363	-21-5
Ch. 120346V	363	-21-5
Ch. 120349B	370	-4
Ch. 120351E	365	-16-5
Ch. 120352G	365	-16-5
FAIRCHILD		
255A	371	-3
FIRESTONE		
4-A-145, 4-A-146 (Codes 389-5-3146, 389-5-3149, 389-6-3149A)	369	-9
4-A-150 (Code 364-6-445)	372	-5
4-A-163 (Code 297-6-623)	370	-5
● 13-G-211, 13-G-212 (Code 280-6-2158)	369	-10
● 13-G-213 (Code 280-6-2159)	369	-10
● 13-G-214, 13-G-215 (Code 280-6-2158)	369	-10
● 13-G-216, 13-G-217 (Code 280-6-2159)	369	-10
● 13-G-220, 13-G-221, 13-G-222, 13-G-223 (Codes 334-6-A62/A, 334-6-N62/A)	375	-2
● 13-G-225, 13-G-226 (Codes 334-6-A63/A, 334-6-N63/A)	373	-5
GENERAL ELECTRIC		
C405, C406	373	-6
P710A, B, C, P711A, B, C	375	-9
● 14P1209, 14P1210, 14P1211, 14P1212 ("Q2" Line)	363	-21-5
● 17P1329, 17P1330, 17P1331 ("M3" Line)	359	-18-5
● 21C143 ("U" Line)	344	-7
● 21C159 ("U" Line)	344	-7
● 21C1439 ("M3" Line)	359	-18-5
● 21C1449 ("M3" Line)	359	-18-5

	Set No.	Folder No.
GENERAL ELECTRIC—Cont.		
● 21C1550, 21C1551 ("U2" Line)	362	-17-5
● 21T056, 21T057 ("U" Line)	344	-7
● 21T1540, 21T1541, 21T1542 ("U2" Line)	362	-17-5
860, 861, 862	374	-5
935, 936	373	-5
940, 941, 942	372	-6
GRANCO		
780	350	-5
GROMMES		
221	375	-10
HALLCRAFTERS		
● 17T5740B, M, 17T5740B, B1X, M, 17T5780B, M (Ch. A2007, E2007)	348	-18-5
Ch. A2007	348	-18-5
Ch. E2007	348	-18-5
HAMILTON ELECTRONICS		
W-7	375	-11
HOFFMAN		
● 81007 (Ch. 315)	318	-15-5
● 81011, U (Ch. B1091, U, B1111, U (Ch. 321, U))	372	-7
● 81121, U (Ch. 322, U)	372	-7
● 81161, U (Ch. 323, U)	370	-6
● 83061, U (Ch. 321, U)	372	-7
● 83071, U (Ch. 322, U)	372	-7
● 83081 (Ch. 419)	321	-15-5
● 83101, U (Ch. 321, U)	372	-7
● 83114, U (Ch. 322, U)	372	-7
● 83151, U (Ch. 324, U)	373	-8
● 83191, U (Ch. 420, U)	352	-17-5
● 83201, U (Ch. 323, U)	370	-6
● 83214, U (Ch. 324, U)	373	-8
● 8G1151, U (Ch. 323, U)	370	-6
● 8T1144, U (Ch. 326, U)	371	-4
● 8W1144, U (Ch. 326, U)	371	-4
● 8K1081, U (Ch. 321, U)	372	-7
● 8K1151, U (Ch. 323, U)	370	-6
● M1007 (Ch. 315)	318	-15-5
● M1091, U (Ch. M1111, U (Ch. 321, U))	372	-7
● M1121, U (Ch. 322, U)	372	-7
● M1161, U (Ch. 323, U)	370	-6
● M3061, U (Ch. 321, U)	372	-7
● M3071, U (Ch. 322, U)	372	-7
● M3081 (Ch. 419)	321	-15-5
● M3101, U (Ch. 321, U)	372	-7
● M3114, U (Ch. 322, U)	372	-7
● M3151, U (Ch. 324, U)	373	-8
● M3181, U (Ch. 420, U)	352	-17-5
● M3201 (Ch. 323, U)	370	-6
● M3214, U (Ch. 324, U)	373	-8
● MG1151, U (Ch. 323, U)	370	-6
● P1007 (Ch. 315)	318	-15-5
● P1121, U (Ch. 322, U)	372	-7
● P1151, U (Ch. 323, U)	370	-6
● P3071, U (Ch. 324, U)	372	-7
● P3081 (Ch. 419)	321	-15-5
● P3091, U (Ch. 322, U)	372	-7
● P3101, U (Ch. 321, U)	372	-7
● P3114, U (Ch. 322, U)	372	-7
● P3214, U (Ch. 324, U)	373	-8
● P11144, U (Ch. 326, U)	371	-4
● SG1144, U (Ch. 326, U)	371	-4
● SP1161, U (Ch. 323, U)	370	-6
● SP1001, U (Ch. 321, U)	372	-7
● SP131, U (Ch. 324, U)	373	-8
● SP3161, U (Ch. 324, U)	373	-8
● SP3181, U (Ch. 420, U)	352	-17-5
● SP3201, U (Ch. 323, U)	370	-6
● W1007 (Ch. 315)	318	-15-5
● W1081, U (Ch. 321, U)	372	-7
● W1111, U (Ch. 321, U)	372	-7
● W1121, U (Ch. 322, U)	372	-7
● W1161, U (Ch. 323, U)	370	-6
● W3061, U (Ch. 321, U)	372	-7
● W3071, U (Ch. 322, U)	372	-7
● W3081 (Ch. 419)	321	-15-5
● W3101, U (Ch. 321, U)	372	-7
● W3114, U (Ch. 322, U)	372	-7
● W3201, U (Ch. 323, U)	370	-6
● W3214, U (Ch. 324, U)	373	-8
● W1191, U (Ch. 329, U)	358	-14-5
● 1201, U (Ch. 329, U)	358	-14-5
● 1211, U (Ch. 329, U)	358	-14-5
● 1221 (Ch. 706)	350	-18-5
● 3234, U (Ch. 331, U)	359	-18-5
● 3241, U (Ch. 329, U)	358	-14-5
● 3251, U (Ch. 330, U)	358	-14-5
● 3261, U (Ch. 331, U)	359	-18-5
● 3271, U (Ch. 331, U)	359	-18-5

	Set No.	Folder No.
HOFFMAN—Cont.		
● 3304, U (Ch. 331, U)	359	-18-5
● 4041, 4051, 4061 (Ch. 706)	350	-18-5
Ch. 315	318	-15-5
Ch. 321, 322	372	-7
Ch. 323, U	370	-6
Ch. 324, U	373	-8
Ch. 326, U	371	-4
Ch. 329, U, 330, U	358	-14-5
Ch. 331, U	359	-18-5
Ch. 419	321	-15-5
Ch. 420, U	352	-17-5
Ch. 706	350	-18-5
KNIGHT (Also See Recorder Listing)		
935Z505	375	-12
935Z737	375	-12
LINCOLN (Auto Radio)		
HK-18805-A	370	-7
78BL (HK-18805-A)	370	-7
MAGNAVOX		
● 23 Series	344	-18-5
● 73 Series	369	-12
● 74 Series	375	-3
● 117 Series	370	-8
Chassis AMP-161AA	375	-13
Chassis CMU4487DC, ED	370	-8
● Chassis CMU4490DC, ED	370	-8
● CMU4491DC, ED	370	-8
● Chassis CMU4499DC, ED, CMU4500DC, ED	370	-8

	Set No.	Folder No.
SCOTT (H. H.)		
99-C	370	11
280	373	7
310B	374	6
SENTINEL		
● 19 Series	371	8
● Chassis U19-01AA, U19-02AA	371	8
● Chassis V19-01AA, V19-02AA	371	8
SILVERTONE		
● PC-7114, PC-7115, PC-7116, PC-7117 (Ch. 456.51000, 10, 20)	368	14
● PC-7120, PC-7121, PC-7122, PC-7123, PC-7124 (Ch. 456.51000, 10, 20)	368	14
● PC-7128, PC-7129, PC-7130, PC-7131 (Ch. 456.51000, 10, 20)	368	14
● PC-7132, PC-7133, PC-7134, PC-7135 (Ch. 456.52000, 1, 10, 11)	370	12
● PC-7136 (Ch. 456.51000, 20)	368	14
● PC-7172, PC-7173 (Ch. 456.51000, 10, 20)	368	14
● PC-7174, PC-7175, PC-7176, PC-7177, PC-7178, PC-7179 (Ch. 456.52000, 1, 10, 11)	370	12
● PC-7190, PC-7191, PC-7192 (Ch. 456.51000, 10, 20)	368	14
4244 (Ch. 137.916, -A)	371	9
● 6102, 6103 (Ch. 549.20040, 50)	351	22-5
6244, 6245, 6246, 6247 (Ch. 567.33006)	357	7
6253F (Ch. 567.33006)	357	7
7038, 7040 (Ch. 528.47500, 528.48500)	375	14
7053, B, 7054, B (Ch. 528.47300)	374	10
● 7132, 7133, 7134, 7135 (Ch. 528.52000, 1, 2, 10, 11, 12, 20, 21, 22, 23, 24, 25, 26, 30, 31, 32, 33, 34, 36)	370	12
● 7174, 7175, 7176, 7177, 7178, 7179 (Ch. 528.52000, 1, 2, 10, 11, 12, 20, 21, 22, 23, 24, 25, 26, 30, 31, 32, 33, 34, 36)	370	12
8222 (Ch. 528.53160)	350	14
8250, 8251 (Ch. 528.59070)	355	11
42441 (Ch. 137.916, -A)	371	9
Ch. 137.916, -A	371	9
Ch. 456.51000	368	14
Ch. 456.51010	368	14
Ch. 456.51020	368	14
Ch. 456.52000, 1	370	12
Ch. 456.52010, 11	370	12
Ch. 528.47300	374	10
Ch. 528.47500	375	14
Ch. 528.48500	375	14
Ch. 528.52000, 528.52001	370	12
528.52002	370	12
Ch. 528.52010, 528.52011	370	12
528.52012	370	12
Ch. 528.52020, 528.52021	370	12
528.52022, 528.52023	370	12
528.52024, 528.52025	370	12
528.52026	370	12
Ch. 528.52030, 528.52031	370	12
528.52032, 528.52033	370	12
528.52034, 528.52036	370	12
Ch. 528.53160	350	14
Ch. 528.59070	355	11
Ch. 549.20040, 549.20050	351	22-5
Ch. 567.33006	357	7
Ch. 567.35024	362	9
SONORA		
537, 538	372	13
610	375	15
617	374	11
625, 626, 627	373	11
● 664, 665, 666, 667	374	12
SPARTAN		
Chassis CR-734	370	13
Chassis CR-741AA	374	13
SYLVANIA		
● 17P101, 17P102, 17P201 (Ch. 1-537, -1, -3, -4)	360	16-5
● 21C407 Series (Ch. 1-540-1, -2)	374	17-5
● 21C408 Series (Ch. 1-540-3, -4)	374	17-5
● 21C409 Series (Ch. 1-539-1, -2)	374	17-5
● 21C512, 21C513 Series (Ch. 1-540-1, -2)	374	17-5
● 21P101 Series (Ch. 1-539-1, -2)	374	17-5
● 21T113 Series (Ch. 1-539-1, -2)	374	17-5
● 21T114, 21T115 Series (Ch. 1-540-1, -2, -3, -4)	374	17-5
● 21T213 Series (Ch. 1-540-1, -2)	374	17-5
1202 (Ch. 1-615-1, -2)	371	10
2301 (Ch. 1-615-1, -2)	371	10
3202GR, LG, PI (Ch. 1-612-2)	371	11
3303TA, 3304E, RE, TA (Ch. 1-612-2)	371	11
4301, 4303, 4305 (Ch. 1-609-3, -4)	374	14
4403 (Ch. 1-619-1)	375	16
Ch. 1-537-1, -3, -4	360	16-5
Ch. 1-539-1, -2	374	17-5
Ch. 1-540-1, -2, -3, -4	374	17-5
Ch. 1-609-3, -4	374	14
Ch. 1-612-2	371	11
Ch. 1-614-1	375	16
Ch. 1-615-1, -2	371	10

	Set No.	Folder No.
TRAVLER		
● 621-300, U, 621-302, U (Ch. 631-36, -56, 632-36, -56)	372	14
● 621-740, U, -750, U (Ch. 631-26, 632-26)	347	18-5
● 721-8400, U (Ch. 631-26, 632-26)	347	18-5
● 1700, 1710 (Ch. 72916)	371	13
● 1710U (Ch. 73016)	371	13
Ch. 631-26	347	18-5
Ch. 631-36, 631-56	372	14
Ch. 632-26	347	18-5
Ch. 632-36, 632-56	372	14
Ch. 72916	371	13
Ch. 73016	371	13
TRUETONE		
D2850A, D2852A, D2853A, D2854A, D2855A	370	14
D3784A, D3785A	371	14
D5570A, D5571A, D5572A, D5573A, D5575A	373	14
D5770A, D5771A, D5772A	373	14
DC2850A, DC2852A, DC2853A, DC2854A, DC2855A	370	14
● 2D1720A, B, 2D1721A, B, 2D1722A, B	375	5
● 2D1737A, 2D1738A	372	15
● 2D2726A, B, 2D2727A, B	375	5
V-M		
560A-1, -2, -3, -4	372	16
565A-1, -2, -3, -4	373	15
1250	374	15
WELLS-GARDNER		
● 321N62/U-A-612, 321N62/U-A-672	369	19
● 2321N/U-A-614, 2321N62/U-A-674	369	19
WESTINGHOUSE		
H-570T4, H-571T4, H-572T4 (Ch. V-2239-4)	301	14
Ch. V-2239-4	301	14
ZENITH		
A400G, W, Y, A404L (Ch. 4A40, 4A42)	373	16
A510F, W, Y (Ch. 5A10)	359	17
A515F, L, V, W, Y (Ch. 5A06)	362	16
A835E, R (Ch. 8A02)	325	17
● A1510L, A1511G, A1512, A1515W (Ch. 15A25)	373	17-5
● A1817G, L, A1819J, A1820W (Ch. 15Z31)	355	18-5
● A2241E, M, R, (Ch. 17Z32)	355	18-5
HF17E, H, R (Ch. 5Z21)	346	21
HF20R, HF21E (Ch. 5Z21)	346	21
HF774E, H, R (Ch. 7Z20)	360	14
HF1180R, HF1182R (Ch. 11Z20)	379	15
HF1183E, HF1185M, R (Ch. 11Z20Z)	370	15
HF1284, E, G, L, Y, HF1286R (Ch. 12Z20)	370	15
● Z1817GZ, LZ, Z1819JZ (Ch. 15Z31)	355	18-5
● Z2221RZ, YZ, U (Ch. 17Z30, U)	372	17
● Z2232CZ, CZU, EZ, EZU, RZ, RZU, YZ, YZU (Ch. 17Z31, U)	374	16
● Z2229RZ, Z2230EZ, RZ (Ch. 19Z32)	357	14-5
● Z2243EZ, EZU, RZ, RZU, Z2244EZ, EZU, RZ, RZU (Ch. 17Z32, U)	374	16
● Z2249EZ, EZU, RZ, RZU, Z2251EZ, EZU, RZ, RZU (Ch. 17Z32, U)	374	16
● Z2257EZ, MZ, RZ (Ch. 19Z32)	357	14-5
● Z2282EZ, EZU, RZ, RZU (Ch. 17Z32, U)	374	16
● Z2359EZ, RZ, Z, Z2360RZ (Ch. 22Z30)	358	14-5
● Z2675EZ, RZ (Ch. 17Z33)	357	14-5
● Z3000EZ, EZU, RZ, RZU (Ch. 17Z32Q, QU)	374	16
● Z3001EZ, EZU, RZ, RZU (Ch. 17Z34Q, QU)	374	16
● Z3004EZ, EZU, RZ, RZU (Ch. 17Z32Q, QU)	374	16
● Z3008EZ, EZU, RZ, RZU (Ch. 17Z34Q, QU)	374	16
● Z3010EZ, HZ, RZ, YZ (Ch. 19Z32Q)	357	14-5
● Z3012HZ, RZ, Z3014HZ, RZ (Ch. 22Z30Q)	358	14-5
● Z4000EZ, RZ (Ch. 17Z33Q)	357	14-5
● Z4006EZ, RZ (Ch. 17Z33Q)	357	14-5
Ch. 4A40, 4A42	373	16
Ch. 5A06	362	16
Ch. 5A10	359	17
Ch. 8A02	325	17
Ch. 11Z20, Z	370	15
Ch. 12Z20	370	15
Ch. 15A25	373	17-5
Ch. 15Z31	355	18-5
Ch. 17Z30, U	372	17
Ch. 17Z31, U, 17Z32, Q, QU, U	374	16
Ch. 17Z33, Q	357	14-5
Ch. 17Z34Q, QU	374	16
Ch. 19Z32, Q	357	14-5
Ch. 22Z30, Q	358	14-5
RECORD CHANGERS		
CRESCENT		
C606, C607	374	4
C708, C709	374	4



Howard W. Sams 1958

TEST EQUIPMENT ANNUAL

THE MOST COMPLETE AND AUTHORITATIVE VOLUME EVER PUBLISHED ABOUT TEST EQUIPMENT

NOTHING ELSE LIKE IT!!

A completely NEW and DIFFERENT volume containing the most needed, the most requested information about all types of Test Equipment and Accessories. 100% practical for anyone who uses test equipment, it covers the complete range of test equipment in down-to-earth language and sparkling illustrations.

8 FACT-FILLED EDITORIAL SECTIONS

- Use and Selection of Test Equipment for Color
- Test Equipment Methods, Measurement Analysis, and General Information
- Test Equipment for Special Applications
- Test Equipment Maintenance
- Questions and Answers About Test Equipment
- Test Equipment Methods, Measurement Analysis, and General Information
- Using Test Equipment for Alignment
- Using Test Equipment for Troubleshooting

All the down-to-earth information you need on operation, theory, and maintenance of Test Equipment. Each section filled with articles designed to save you time and money—techniques that make your present equipment more versatile and valuable to you—information about new equipment designed for service of new components and chassis.

plus An editorial Product Listing Section which features over 400 units of test equipment and accessories. Pertinent specifications are given on all equipment, and most models are illustrated.

For the first time anywhere the product listing section will group test equipment by the following logical product classifications:

Oscilloscopes	Meters	Transistor Testers
VOM's	Decade Boxes	Component Testers
VTVM's	Bench Eqpt.	Probes
Generators	Tube Testers	And Many Others

LIMITED EDITION - RESERVE YOUR COPY TODAY!

AVAILABLE AT YOUR ELECTRONIC PARTS DISTRIBUTORS IN NOVEMBER

ONLY \$1.00

HOWARD W. SAMS & CO., INC

2201 EAST 46TH STREET INDIANAPOLIS 5, IND.

	Set No.	Folder No.		Set No.	Folder No.		Set No.	Folder No.
RECORDERS			SYMPHONIC			TELEFUNKEN		
KNIGHT			BR-1200, R-1200	373	13	TW560	371	12
99RZ177	372	8	SILVERTONE			WECOR		
99RZ936	372	8	567.40010	365	13	151, 152	375	17
RCA VICTOR			567.40110	365	13			
8-STP-1, 8-STP-2	370	10	567.41020	365	13			
Ch. RS-162	370	10	567.41108	365	13			
			567.41120	365	13			

NOTE: PCB Denotes Production Change Bulletin. ● Denotes Television Receiver. S Denotes Schematic Coverage Only.



Have YOU Given Your Service Business Its COLOR Transfusion?

This TV service-dealer is "hep". He's getting ready now for healthy, wealthy business. "Doctor", of course, is his RCA Tube Distributor. And he'll give you your "booster shot", the new RCA PICT-O-GUIDE for COLOR TV, with your order for RCA TUBES—free of extra charge!

Written by RCA's well-known TV-service authority John R. Meagher (who also wrote the famous RCA Pict-O-Guide series for black-and-white TV), this volume is profusely illustrated with full-color photos, packed with step-by-step alignment and trouble-shooting instructions, and loaded with labor- and time-saving short cuts for *profitable color-TV servicing*. See for yourself what other service technicians have learned—*color-TV servicing has been simplified!* See your RCA TUBE DISTRIBUTOR with your order today!



RCA COLOR-TV PICT-O-GUIDE CONTAINS SECTIONS ON:

Color Mixing • RCA Compatible Color TV System • Purity • Convergence • Gray-Scale Tracking Color Operating Controls • Antenna Considerations • RF-IF Bandpass Alignment • Color Test Equipment • Color-Bar Patterns • Troubleshooting • Signal Tracing • Interference • "Green Stripe" Test Signals



RECEIVING TUBES

RADIO CORPORATION OF AMERICA

© Electron Tube Division Harrison, N. J.

In Electronic Circuits . . .

ALL AROUND PROTECTION

Diagram illustrating various electronic components and fuse types arranged around a central text area:

- SCREW TERMINAL MOUNTING
- SOLDER TERMINAL MOUNTING
- 4AG FINGER OPERATED POST
- TERMINAL CLIP
- FUSE CLIP EARLESS
- FUSE CLIP
- LC FUSE HOLDERS
- MOUNTINGS FOR RECTIFIERS
- 3AG FUSES
- 3AG SLO-BLO
- 3AB FUSE U/L
- LC FUSES 250V TYPE C
- LC FUSES 125V TYPE C
- LC SLO-BLO 125V TYPE N
- 8AG INSTRUMENT FUSES
- 8AG FUSES U/L
- AIRCRAFT FUSES
- 4AG SLO-BLO
- IN LINE FUSE RETAINERS
- 3AG POST SCREWDRIVER OPERATED
- 3AG POST FINGER OPERATED
- 3AG POST MINIATURE
- CAN COVER MOUNTING
- THROUGH PANEL MOUNTING

It's **LITTELFUSE** First!
 DES PLAINES, ILLINOIS