


MARCH • 1958 25 CENTS

RF REPORTER

FOR THE ELECTRONIC SERVICE INDUSTRY



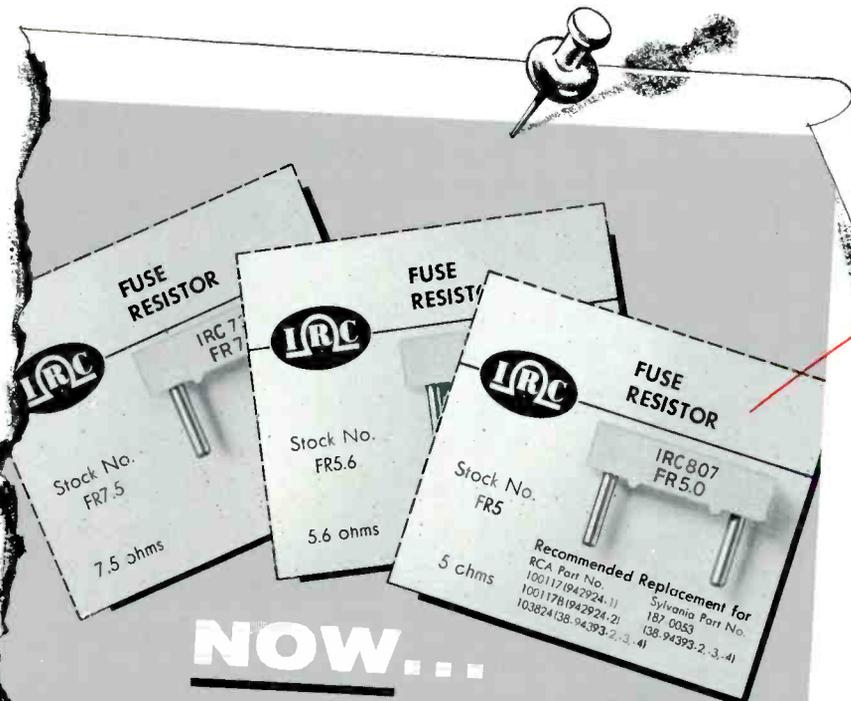EDM A. GURTOWSKI
1452 KENHORST BLVD
KENHORST
READING, PA. 658



NOW...

**THREE Sizes of IRC®
"Skin-Packed" Fuse Resistors**

IRC's quality 5 ohm fuse resistor—the FR5—is a replacement for

RCA Stock No.	RCA Part No.	Original Value
100117	942924-1	5.6 ohms
100117B	942924-2	5.0 ohms
103824	38-94393-2,-3,-4	4.7 ohms
Sylvania Stock No.	Sylvania Part No.	Original Value
187-0053	38-94393-2,-3,-4	4.7 ohms

This new 5 ohm IRC Fuse Resistor provides you with the same fine features as IRC's dependable FR5.6 at 5.6 ohms and FR7.5 at 7.5 ohms:

- Sturdy terminal pins—both attached inside a rugged ceramic case.
- Improved plug-in type for fast, easy replacement in the newer TV receivers. Terminal pin holes facilitate attaching leads where necessary.
- Projections on bottom of ceramic case leave air space—prevent receptacle from overheating.
- "Skin-Packed" cards protect each fuse resistor from dirt and handling.
- Type and range clearly identified on both fuse resistor and "Skin-Packed" card.

You can depend on the quality and reliability of IRC "Skin-Packed" Fuse Resistors.

Dealer Net
\$.45 each

GET YOURS SOON!



Wherever the Circuit Says
INTERNATIONAL RESISTANCE CO.
Dept. 363, 401 N. Broad St., Phila. 8, Pa.
In Canada: International Resistance Co., Ltd., Toronto, Licensee

*Good!
New size!*


Needed something like this! Now one resistor can take the place of three—fewer to lug around

Sure saves me a heck of a lot of time and trouble

I like "Skin-Packs" can buy as few or many as I need and there's less breakage and damage and losses

No chance of making a mistake

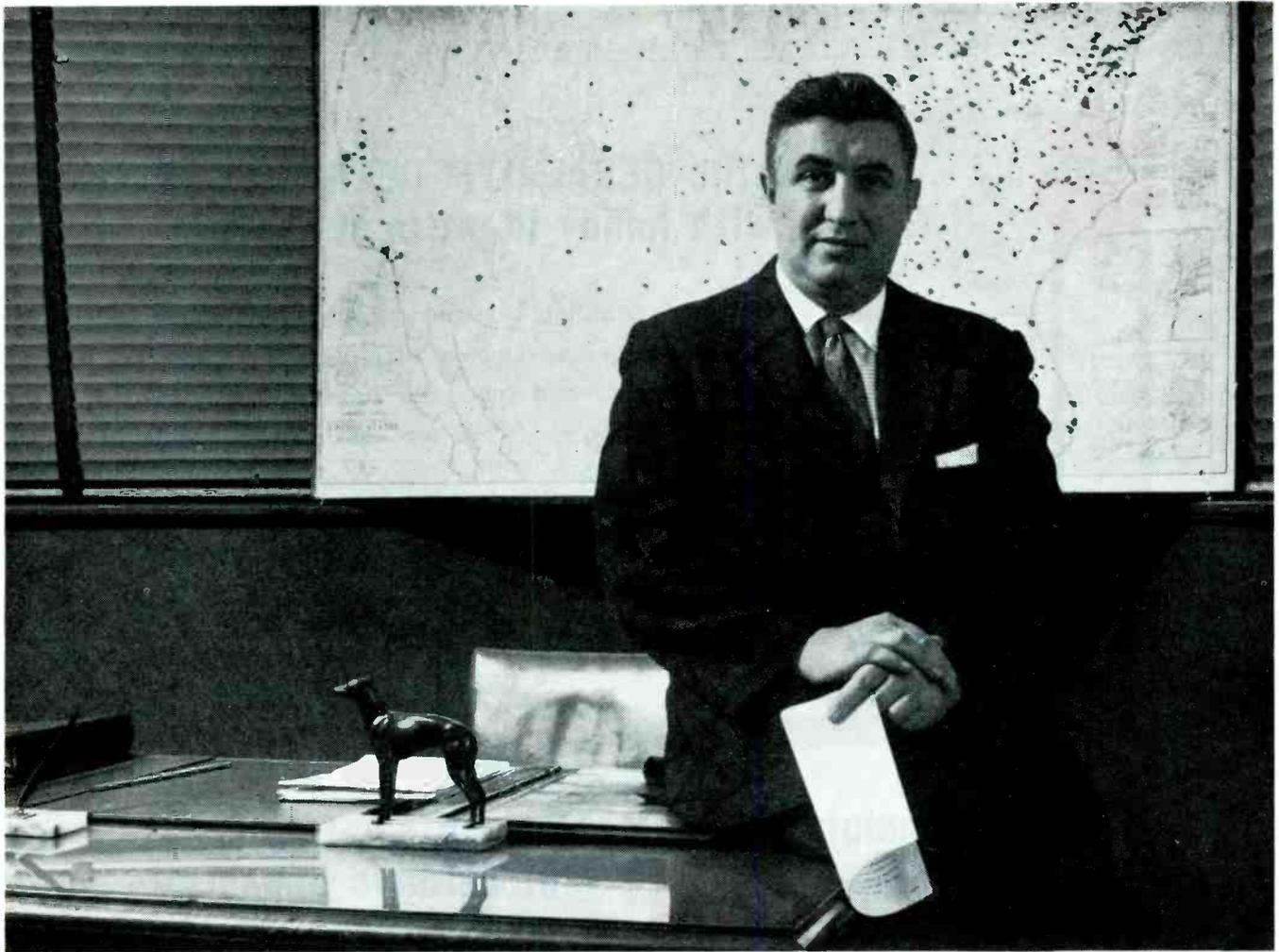I'll get mine tomorrow TODAY from my IRC Distributor



The new JFD Satellite-Helix a Giant step in television antenna science

Yesterday we crossed the frontier of the atomic age. Today, we are entering the era of interplanetary space travel. There are no visible limits to the "miracles" to be developed tomorrow.

Great things have been happening at JFD, too. Nineteen months of intensive research into a virtually unknown principle of antenna performance has achieved a major breakthrough in television reception. For the first time, the science of antenna engineering has overcome the two primary barriers to long-distance pick-up — uneven antenna bandpass and reactive impedance components.

These significant improvements are made possible by the development of a spectacular new dipole system. As a result, the *Satellite-Helix* dipole system captures up to **35 per cent more signal and intensifies color reception**—has less low band ghost pick-up and less back and side interference, and closer 300 ohm match.



Pioneers in Electronics since 1929

JFD ELECTRONICS CORP.

6101 Sixteenth Avenue Brooklyn 4, New York

PF REPORTER • March, 1958


Here are a few of the "extras" the new *Satellite-Helix* configuration will give you over other leading types:

Over Reinforcing Wave Type	Over Focus-Lens Type	Over Bat Dipole Type	Over Dipoles With Phase-Reversing Stubs
*1-2.5 db more gain *sharper low-band pattern *less reactive impedance *higher front-to-back ratio *better side rejection	*flatter bandpass *2-3.5 db more gain *less reactive impedance *higher front-to-back ratio	*flatter bandpass *2-3 db more gain *less reactive impedance *higher front-to-back ratio *better side rejection	*2-4 db more gain *flatter bandpass *higher front-to-back ratio *better side rejection

Take a giant step today into the flawless reception of tomorrow. Install the remarkable *Satellite-Helix* on your next "problem" job with our money-back guarantee. See for yourself its "selling edge" that will keep you out front in TV antenna profits and customer confidence in *your* area in the competitive years ahead. Priced realistically at a non-inflated level, the *Satellite-Helix* is now on its way to your JFD distributor.

Edward Finkel
General Sales Manager

Sprague Service-Aids for servicemen:

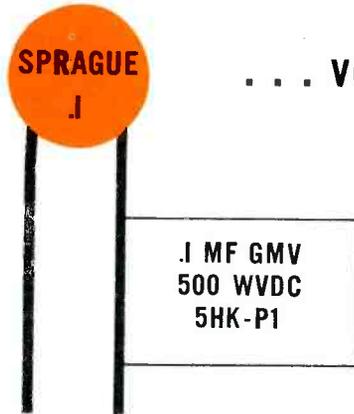


... versatile CERA-MITE* CERAMIC CAPACITORS with handy identification tags

Sprague's complete ceramic capacitor line is now individually tagged for quick, *complete* identification — capacitance, tolerance, voltage, and type. No fumbling, no guessing about ratings ... you're always sure with Sprague *tagged* disc capacitors. Use them all the time. You'll find that they also make excellent replacements for molded mica, ceramic tubular, and paper tubular capacitors in many applications

Stock up today! Ask your distributor about Sprague CERAMIKITS ... they contain the ceramic disc capacitors you need most ... they keep them in order ... ready to use.

*Trademark

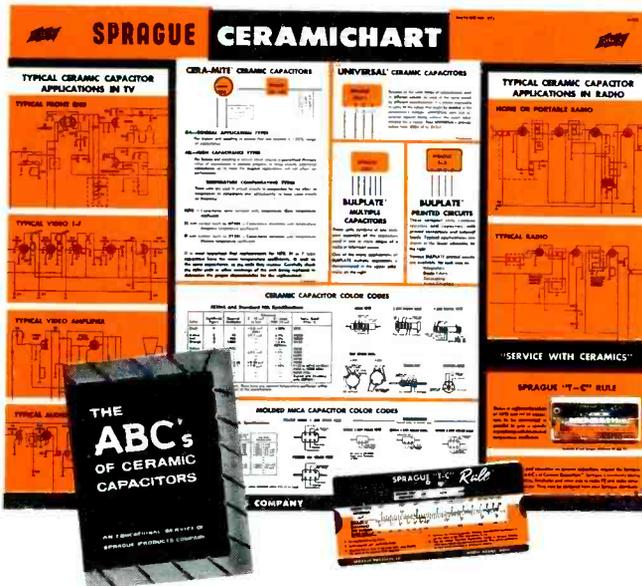... helpful INFORMATION on what, when, and how of ceramic capacitors



Sprague offers you plenty of service information ... the kind you need and use everyday:

Sprague CERAMICHART: illustrates various types of ceramic capacitors and shows where to use them; details color codes.—FREE

Sprague "ABC's of Ceramic Capacitors": a compact booklet containing basic facts on all types of ceramic capacitors.—FREE

Sprague "T-C" Slide Rule: shows at a glance the values of the N750 and NP0 type ceramic capacitors to connect in parallel to equal a capacitor of desired intermediate temperature coefficient of the required capacitance; available from your distributor for only 15c.

Be sure you get this useful and valuable information from your Sprague distributor, today! Or write Sprague Products Co., Distributors' Division of Sprague Electric Company, 105 Marshall Street, North Adams, Mass.

Pioneer in ceramic capacitors ... First in ceramic capacitor information

don't be vague ... insist on



SPRAGUE RESEARCH IS CONSTANTLY PRODUCING NEW AND BETTER CAPACITORS FOR YOU

PUBLISHER
Howard W. Sams
GENERAL MANAGER
Mal Parks, Jr.

EDITOR
Verne M. Ray

ASSOCIATE EDITORS
Leslie D. Deane
Thomas A Lesh
Calvin C. Young, Jr.

CONSULTING EDITORS
William E. Burke C. P. Oliphant
Robert B. Dunham George B. Mann
Paul C. Smith

ART DIRECTOR EDITORIAL ASSISTANT
Don W. Bradley Judy Ann Hurley

PHOTOGRAPHY CIRCULATION
Robert W. Reed Pat Tidd

ADVG. PRODUCTION
Carol B. Gadbury

ADVERTISING SALES OFFICES

MIDWESTERN
PF REPORTER,
2201 East 46th Street, Indianapolis 5, Ind.
Clifford 1-4531

EASTERN
Paul S. Weil and Donald C. Weil,
39-01 Main Street, Flushing 54, New York.
Independence 3-9098.

WESTERN
The Maurice A. Kimball Co., Inc.
2550 Beverly Blvd., Los Angeles 57, Calif.
Dunkirk 8-6178; and 681 Market Street,
San Francisco 5, Calif. EXbrook 2-3365.

Published monthly by Howard W. Sams & Co.,
Inc., at Indianapolis 5, Indiana.
Entered as second class matter October 11,
1954, at the Post Office at Indianapolis, Indiana,
under the Act of March 3, 1879.

Copyright 1958 by Howard W. Sams & Co., Inc.
No part of the PF REPORTER may be repro-
duced without written permission. No patent
liability is assumed with respect to the use of
information contained herein.

Subscription prices in U.S.A. and possessions:
1 yr., \$3.00; 2 yrs., \$5.00; 3 yrs., \$7.00. In
Canada and Pan America: 1 yr., \$3.60; 2 yrs.,
\$6.00; 3 yrs., \$8.50. Foreign subscriptions:
1 yr., \$6.00; 2 yrs., \$11.00; 3 yrs., \$15.00.
A limited quantity of back issues are available
at 35c per copy.

next month

AGC CIRCUITS FOR '58

Several manufacturers have made design changes in this circuit, so you'll want to bone up on your theory. This feature describes the 6BU8 stages used in the Admiral Chassis 16J1 and Zenith 15A25 and 17A20 chassis. A subsequent article will deal with other popular-make AGC circuits.

HOW TO ALIGN THE IF'S

Okay—we give up. Your requests have been too numerous to ignore any longer—so in April's picture story, we'll give you all the "dope" you'll need to solve your alignment problems.

USING A SCOPE FOR SIGNAL TRACING

With good reason, many of you readers have been hungering for information on this subject. And the more you get, the more you want! Well, here's another one we're sure you'll like. Don't miss it!

VOLUME 8, No. 3



MARCH, 1958

PF REPORTER

FOR THE ELECTRONIC SERVICE INDUSTRY

CONTENTS

This Month's Cover	66
Letters to the Editor	6
Shop Talk	10
Improving dipole gain, directivity and bandwidth with added elements.	<i>Milton S. Kiver</i>
What Do You Know About Indoor Antennas?	12
Outline of basic operating principles plus descriptions of several popular commercial models.	
Signal Tracing RF & IF Circuits	14
For those who experience troubleshooting problems ahead of the detector.	
Servicing Industrial Electronics—Part 7	16
Electronic devices for sensing mechanical vibrations and flaws.	<i>Mel Whitmer</i>
Dollar & Sense Servicing	18
The Troubleshooter	20
Quicker Servicing	22
Damping resistor applications; new color tube precaution; change in focus circuit; color-stripe test jack.	<i>Calvin C. Young, Jr.</i>
Do-It-Yourselfers are Soldering Now	30
And woe is you if you don't beware!	<i>G. M. Carrier</i>
Selection and Use of Hand Tools	34
Part 2—Pliers, cutters, wrenches, wire strippers and miscellaneous items for the technician.	
Notes on Test Equipment	42
Capacitor analyzer, VOM, pattern-scanning generator, multi-socket tube-transistor tester.	<i>Les Deane</i>
Using A Scope to Troubleshoot Sweep Circuits	52
Admiral "Son-r" remote control; Rockland battery-powered radio-phonograph.	<i>Robert G. Middleton</i>
Servicing New Designs	60
Admiral "Son-r" remote control; Rockland battery-powered radio-phonograph.	<i>Thomas A. Lesh</i>
Guide to Auto-Battery Polarities	70
Product Report	77
Free Catalog & Literature Service	80
Supplement to SAMS Master Index	81

SUBJECT REFERENCE INDEX

ANTENNAS		Wire cutters	34
Dipole and reflector	10	Wrenches, adjustable	36
Dipole and director	65	TEST EQUIPMENT	
Folded dipole	67	Capacitor analyzer,	
Indoor types	12-13	Sprague Model TO-5	42
BUSINESS		Demodulator probe	15
Color TV home demonstrations ...	18	Flaw detector,	
CIRCUITS		Sperry "Reflectoscope"	76
Remote control, Admiral "Son-r" ..	60	Flying-spot scanner,	
Transistorized portable		Hickok Model 760	47
radio-phonograph	62	Oscilloscope,	
Vibration sensor	17	bandwidth requirements	52
COLOR TV		input attenuators	52
"Burn-in" of test pattern	26	viewing current waveforms ...	56
Color stripe test jack	28	Sweep generator,	
Focus control, field change	26	setup for tuner	42
COMPONENTS AND MATERIALS		troubleshooting IF defects	14
Auto batteries,		Thickness gauge	74
voltage and polarity	70	Tube-transistor tester,	
Contact cleaner "injector"	26	B & K Model 650	50
Resistors used for damping	22	VOM, Simpson Model 260	45
SERVICING		VTVM, checking RF-IF stages ...	72
Horizontal sweep,		THEORY	
resistor troubles	22	Dipole antennas	10
Pliers, types and uses	34	Flaw detection in solids	76
Signal substitution, RF-IF	71	Signal tracing RF-IF stages	14
Sweep circuit waveforms	52	Thickness measurement	75
Tools, miscellaneous	37	Vibration sensing	16
Tuners,		TRANSISTORS	
checking RF response	42, 71	Radio-phonograph circuit applications ..	63
cleaning contacts	26	Recognizing n-p-n and	
		p-n-p types	18

USE HANDY CARD AT BACK TO ENTER YOUR SUBSCRIPTION




INTRODUCING

the new SCOTCHMAN[®] line of TV Antennas by WINEGARD

Gives you all three!... performance... adaptability... low cost

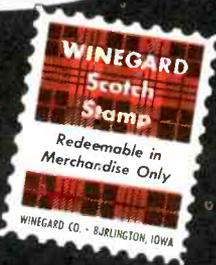MAN! These Scotch Stamps Are Worth Money to You! Get Free Antennas, tool sets and other valuable nationally advertised merchandise.



The thrifty way to buy your merchandise! With every Scotchman antenna you buy, you get valuable Scotch Stamps which you can turn in for useful premiums or for more antennas! Start saving Scotch Stamps now! Ask your distributor for free Scotch Stamp Saver.

This offer is void in any state (territory or other jurisdiction) in which such offers are prohibited, restricted, licensed, taxed or otherwise regulated.



This Free Pegboard Tool Set is yours with Scotch Stamps— Start Saving Scotch Stamps Now!

There's a Winegard Scotchman antenna for every signal area... for every budget! With just four basic Scotchman models (priced as low as \$6.95 list) you can now solve just about any reception problem you run into.

In most of your installations, you will find that one or a stack of the four basic antennas is all you need. But for those tough reception problems, where you need more gain—or have severe interference, you can tailor-make a special Scotchman as needed, simply by using the new plug-in attachments shown on the opposite page. And you can do this at no more cost than your competitors charge for ordinary, less effective antennas.

Economy and adaptability are not all you get in the Scotchman! You get quality, too... the kind of quality features you are proud to point out to your customer... like: unbreakable TDM styrene insulators, special fatigue-resisting aluminum tubing, closed element and boom ends to eliminate windwhistle and vibration, precision die-cut elements... features usually found only in the highest priced antennas

And, of course, all Winegard Scotchmen are completely factory pre-assembled. Elements lock into place automatically when you unfold them. Absolutely no antenna installs easier or quicker... and they're wonderfully compact and rugged.

On your next installation, do this: Try a Scotchman antenna in the only place it really counts... on one of your own customer's homes. See for yourself that the Scotchman can't be beat for performance and adaptability at such low cost!

A NOTE FROM JOHN WINEGARD

As an addition to our popular line of gold anodized Colorceptors and Twilights, I am pleased to announce this new Scotchman series to give you a complete price range of quality all-channel Winegard antennas. You'll find valuable Scotch Stamps in each Scotchman carton which we will redeem for free antennas and other valuable premiums. This is our way of saying "thank you" for your business.

Sincerely,

John R. Winegard



John R. Winegard
President, Winegard Co.

Priced
as low as

\$6.95
LIST




MODEL 504: All-channel, high performance, 7-element fringe area antenna. Exclusive impedance-compensated Vee driven elements and patented Electro-Lens design. Easily converted to 13 element antenna for tough reception areas with Kit A.

\$19.95 list



MODEL 502: 4-element with new improved Vee driven element design for city and suburban areas. Exceptionally good reception in the high channels . . . almost bi-directional on low channels. Higher gain and better ghost rejection than conicals. A natural with Kit D.

\$9.95 list

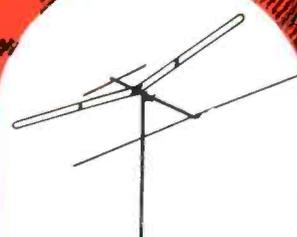


MODEL 501: 3-element antenna recommended for use in place of conicals. New Vee driven element design. Smooth forward response lobes and accurate impedance match on both high and low bands. Cuts ghosts. No finer antenna for city and suburban areas at this low price.

\$6.95 list

MODEL 503: Near fringe and suburban area, all-channel 5-element antenna with new improved Vee driven elements. Can be used with attachment Kits A, B, C or D. Ideal for stacking.



\$14.95 list

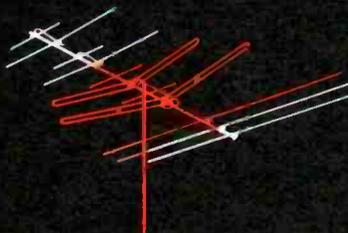4 BASIC SCOTCHMAN TV ANTENNAS AND 4 ATTACHMENT KITS COMBINE TO MAKE MORE THAN 30 DIFFERENT COMBINATIONS! YOU CAN INCREASE THE GAIN OR FRONT-TO-BACK RATIO OF ANY MODEL




KIT A: HI-LO BOOST for higher gain and co-channel suppression. Adds two reflectors for extremely high front to back ratio. Adds 4-element patented Electro-Lens director for increased gain on all channels. Use with models 503 (illus.), 501 and 504. Gives up to 22% more gain.

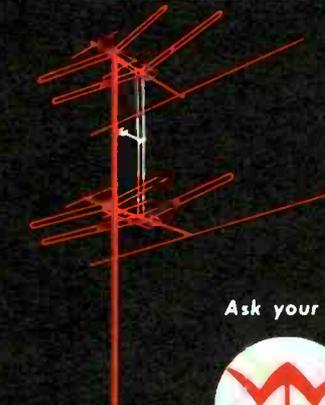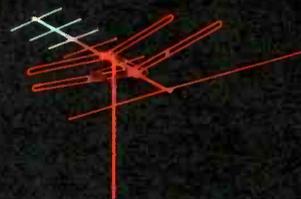KIT B: HI-BAND BOOST for peaked gain on channels 7 through 13. Gives antenna sharper directivity. Reduces ghosts. Adds 3 high band director elements to front of antenna. Fits all Scotchman models 501, 502, 503 (illus.) and 504.



KIT C: STACKING BAR KIT consists of two stacking bars, heavy duty support bracket and terminal insulator. Stacking two antennas of the same model increases sensitivity up to 40%. Can be used with all Scotchman models 501, 502, 503 (illus.) and 504.

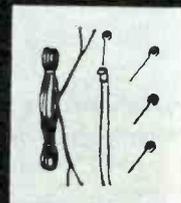KIT D: INSTALLATION KIT (pat. pend.). Universal tripod mount fits any gable, pitched or flat roof. All aluminum. Can't stain roof. No guy wires. 5 1/2 ft. tall. One man can install. Includes, mount, mast, lead-in wire, stand-offs and lightning arrester. Can be used with rotor. Works well with all Scotchman models.



Ask your distributor or write for details on the money-making Winegard Scotchman line.



Winegard Co.

HOW TO CUT CALL BACKS!

Costly irritating call backs! — The servicemen's dilemma — and everybody claims a cure. Astron's not shouting any claims, but simply presents the facts on how Astron designs capacitors to end call backs.

Callback Causes

1. Very high leakage due to poor shelf life.
2. High leakage due to corrosion in the tab and risers.
3. High leakage due to improper impregnation.
4. Particles and impurities in paper, causing breakdown.
5. Overloading the circuit due to faulty parts in the circuit.
6. Improperly hot aged.
7. Extreme heat build-up within the capacitor.
8. Continual power loss throughout the circuit.
9. Failures due to explosion and fire.

Astron Facts

1. Astron uses 99.99% pure foil.
2. Proper handling during assembly and close attention to manufacturing purities in chemicals and raw materials.
3. An extra long impregnation cycle.
4. 100% inspection and the use of only premium quality paper.
5. Safety margin foil is used and foil is formed at high voltage ratings which will stand higher surges.
6. A complete heat aging system is used.
7. Astron Capacitors have exceptionally low D. C. leakage current.
8. Astron Capacitors have low equivalent series resistance.
9. The use of high purity paper separators and safety vents.

Today's circuits require top performing capacitors. That's the way we build them at Astron. Use Astron Capacitors and do away with bothersome and costly call backs!! Insist on Astron.

ASTRON
CORPORATION
255 GRANT AVENUE E. NEWARK, N. J.



SKOTTIE ELECTRONICS CORPORATION
A Wholly-owned subsidiary
of ASTRON CORPORATION
PECKVILLE,
PENNSYLVANIA

Letters to the EDITOR

Dear Editor:

I would like to see articles about the practical uses of the oscilloscope, showing setups using the scope alone and also with auxiliary test equipment. Include waveforms! Most literature I've read seems to stress the theory of the scope's circuit.

V. HARRIS

East Orange, N. J.

You must really read "Coming Next Month" carefully. This issue contains the second of a 3-part series on this very subject. Part 1, "Regeneration," appeared in February, and Part 3, "Using a Scope in Signal-Tracing Tests" will show up in April.—Editor

Dear Editor:

In my experience, the serviceman is constantly approached by his customers with the question, "How much is my set worth?" He has little difficulty answering his regular customers because he is familiar with their sets, but there always seems to be some new customer who has just moved into town with an unfamiliar brand of TV set which is not sold in the community. Rather than being completely stymied, the serviceman would like to have statistics that would help him to give some kind of an answer in such cases.

CHARLES O. DONALDSON

Ann Arbor, Mich.

Suggest you get a copy of "TV Trade-In Blue Book," published by the National Appliance Trade-In Guide Co., Madison, Wis. at \$5 per copy. —Editor

Dear Editor:

In "The Troubleshooter" in the January issue, an answer is furnished a gentleman who is concerned about proper magnetic strengths of various "ion traps"—a name which both he and your author seem to insist on applying to beam bending devices.

Actually, from the very outset of magnetically deflected CRT's, the "ion trap" has been built into the gun; it is an integral part of that assembly. At the worst, the beam bender might be called an "ion trap magnet" but certainly it is incorrect to refer to it as the ion trap.

Just one of those little errors that become a fixed part of our established electronic nomenclature. Two others come to mind: Calling the plural of antenna by the "no such" term of antennas instead of antennae, and the consistent failure to distinguish the property of inductance from the noun inductor when speaking of a device.


B. H. "BURT" HANSEN

Inglewood, Calif.

Thanks, "Burt," for reminding us of our position as a "guiding light." We got to admit we ain't been to karefull

You can do more than ever before with this new portable **B&K**

AUTOMATIC MONEY-MAKER

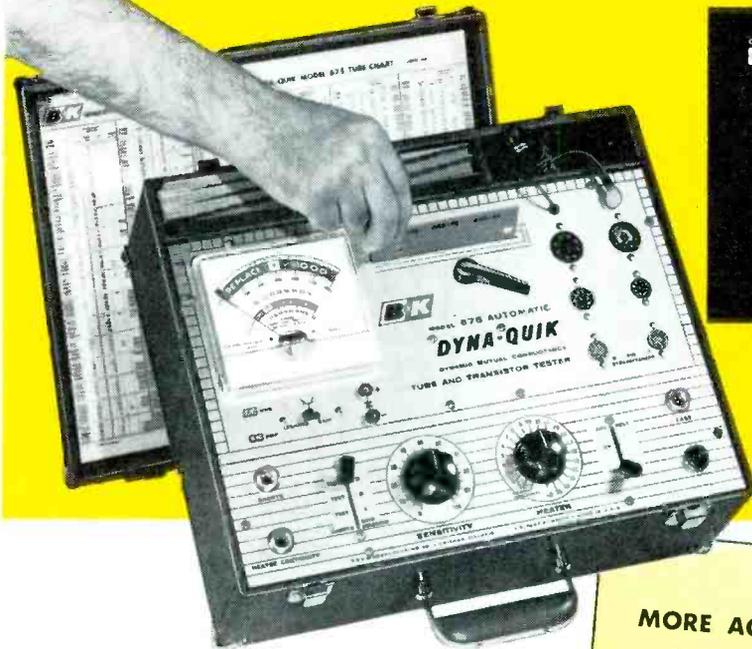

**TESTS TUBES
AND TRANSISTORS
Automatically**
WITH LABORATORY ACCURACY

- Saves Servicing Time
- Sells More Tubes
- Satisfies More Customers



B&K MODEL 675
AUTOMATIC
DYNA-QUIK
DYNAMIC MUTUAL CONDUCTANCE
TUBE & TRANSISTOR TESTER

MORE ACCURATE TEST

Tests Each Section of Multiple Tubes Separately for Gm, Shorts, Grid Emission and Life

Tests each tube for Gas Content and Grid Emission simultaneously with Short check. Instantaneous Heater Continuity test.

SIMPLIFIED AUTOMATIC DYNA-CARD SYSTEM

With only 60 heavy-duty, phenolic Dyna-Cards you can test over 500 tube types. Dyna-Card automatically sets socket connections for quick, accurate test. Each Dyna-Card is identified and indexed, ready to use. Always kept up-to-date simply by adding new Dyna-Cards. Minimizes obsolescence.

CHECKS OVER 99%

of the tubes most widely used in television receivers plus popular home and portable radio tubes.

ONE EXTRA TUBE SALE

on each of 5 calls a day pays for the Dyna-Quik in a few weeks.

TESTS TRANSISTORS, TOO

Transistor Section checks junction, point contact and barrier transistors, germanium and silicon diodes, selenium and silicon rectifiers.

Again, B&K helps servicemen give *faster, better service at less cost and make more money*. The new automatic Model 675 makes tube checking quick and easy in the home or shop. (Tests transistors, too.) *Measures true dynamic mutual conductance*. Makes complete tube test in seconds, under actual operating conditions of the set. Checks average set in a few minutes. Simple to operate. *No multiple switching. No roll chart*. Shows customer the true condition and life expectancy of tubes in the set, *sells more tubes on-the-spot, saves call-backs*. Quickly pays for itself.

Shows tube condition on "Good-Bad" scale and in micromhos. Large 4½" meter has two highly accurate ranges calibrated 0-6000 and 0-18,000 micromhos. 7-pin and 9-pin straighteners are mounted on panel. Automatic line compensation. Special bridge monitors line voltage continuously. Light weight, easily portable in handsome leatherette-covered carrying case. Operates on 105-125 volts 60 cycle a.c. Size: 15¼" x 12¼" x 6". Net wt: 10½ lb. Net, **\$169⁹⁵**

Also makers of famous CRT, DYNA-SCAN, CALIBRATOR

See your B&K Distributor, or write for Bulletin 675-R



B & K MANUFACTURING CO.
3726 N. Southport Ave. • Chicago 13, Illinois

Canada: Atlas Radio Corp., 50 Wingold, Toronto 10, Ont. Export: Empire Exporters, 439 Broadway, New York 13, N.Y.



"THERE'S ABSOLUTELY NOTHING, MADAME,
THAT WILL MAKE ROCK 'N ROLL
SOUND LIKE RACHMANINOFF."

Right — but a new Webster cartridge *will* bring out the best in any record. Equally important, there's a Webster replacement cartridge to fit most every model record player and changer. You'll make money on them, too. They're priced right — they're easy to install — there's never a call-back.

BUY WISELY...BUY WEBSTER!



V-8 Plug-in Cartridge —

Ceramic cartridge and needle combination installs as a unit when needles are replaced. Available with a 1-mil and 3-mil sapphire point, or a 1-mil natural diamond and 3-mil sapphire point.

Free — large print of this Lichty cartoon suitable for framing. Write today!

ELECTRONICS DIVISION

WEBSTER  **ELECTRIC**
RACINE · WIS

Y-122

about this here thing, but we feel that slightly relaxing our usage of terms to those most common to the average technician makes for easier reading. Definitions, after all, are (or will be) based on common usage.

We must take issue with you, however, on the plural of "antenna." "Antennae" are strictly for insects; those aluminum things on housetops are Americanized enough to be formally classified as "antennas." Webster's Unabridged backs us up if you'd care to check.—Editor

Dear Editor:

In the December PF REPORTER, John Markus says the Better Business Bureau warns that any repairman who charges less than \$4 to \$7 base fee is suspect. If the Better Business Bureau made pamphlets on their survey of this information, please advise where I can get them. I would like very much to distribute them among my customers.

JAMES M. IVEY

Bladenboro, N. C.

Two pamphlets on TV service are available from BBB. "Safeguard" (4 pp., 5¢) describes in detail the cost factors that make it expensive to equip and maintain a competent service shop. "TV Without Tears" (12 pp., 10¢) gives case histories of service gyms and warns readers to stick to reputable concerns and not fall for price lures. By all means, your customers should read these pamphlets. This type of material can only increase their confidence in you.—Editor

Dear Editor:

I have recently found a method of unsoldering components from a printed wiring board which lessens the chance of breaking the board.

Take an ordinary vacuum cleaner and reduce the nozzle opening of the vacuum hose to approximately 3/8". Heat the solder joint, and vacuum the solder away as soon as it melts. The component then can be removed very easily.

RAY URBAN

Ray's Electronics
Austin, Texas

Sounds like a dandy idea, Ray. By the way, have you lost any pocket-sized radios this way?—Editor

Dear Editor:

I waited for your January issue to see if it contained any explanation for the absence of the annual index in the December issue. I use your magazine as a reference quite often and the index saves a lot of time. PF REPORTER is, to me, like a set of law books to a lawyer. Is an index for 1957 available?

FRANK AVILA

Richmond, California

Sorry you didn't see our notice on page 55 of the January issue, Frank. Yes, a 4-page index has been prepared and a copy has been sent you post-haste. Anybody else want one? It's free!—Editor

PF REPORTER · March, 1958

Mr. Independent Service Dealer:
**are you helping to support
 your "competitors"?**




Not if you buy and use Raytheon Television and Radio Tubes. Raytheon does not have a factory TV-Radio service organization — does not compete with you in any way for service business. Raytheon believes that TV-Radio service is *your* business and serving you is Raytheon's.

Every time you buy a Raytheon Tube you buy from the first tube manufacturer to help independent service dealers. For more than thirteen years Raytheon, through their Distributors, has offered independent service dealers the many benefits of the Raytheon

Bonded Dealer Program. Support through national advertising, Western Union Operator 25 service and Group Life Insurance are among other business building dealer helps that Raytheon has pioneered for "independents".

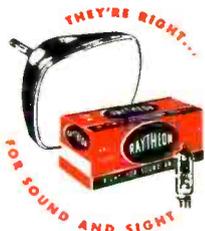But most important of all, Raytheon makes TV and Radio Tubes that are ideal for all replacement work, because they are designed to provide quality performance in all makes and models of TV and Radio sets. Use them with complete confidence that they are best for you . . . and for your customers, too.



RAYTHEON MANUFACTURING COMPANY

Receiving and Cathode Ray Tube Operations

NEWTON 58, MASS. 55 Chapel Street
 CHICAGO, ILL. 9501 Grand Ave. (Franklin Park)
 ATLANTA 6, GA. 1150 Zonolite Rd. N.E.
 LOS ANGELES 7, CALIF. 2419 So. Grand Ave.

Raytheon makes all these
 { Receiving and Picture Tubes, Reliable Subminiature and Miniature Tubes,
 } Semiconductor Diodes and Transistors, Nucleonic Tubes, Microwave Tubes.



ShopTalk

MILTON S. KIVER

Author of . . .
*How to Understand and Use TV Test Instruments
 and Analyzing and Tracing TV Circuits*

Adding Elements to Change Dipole Response

As we have seen, the simple dipole possesses a bidirectional or figure-eight response pattern, making it susceptible to the reception of signals coming from two directions. Furthermore, since each lobe of the pattern is rather broad, we can move considerably off center and still obtain fairly appreciable amounts of signal. This means that the directivity of this array is only fair and unwanted signals from many directions will be received quite readily.

A simple way to improve dipole directivity is to position a wire (or rod) parallel to the dipole and a quarter wavelength behind it. See Fig. 1. This additional wire is about 5 per cent longer than the dipole and is not connected to either the receiver or the dipole. The name given to this wire is reflector, and its purpose is to respond to a portion of the arriving signal and re-radiate it. The direction of the radiation is perpendicular to the rod, so naturally some of the re-radiated signal reaches the dipole. Since there is a time lapse at the dipole between

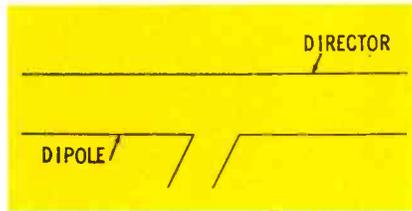


Fig. 1. Dipole with reflector.

reception of the directly-received and re-radiated signals, cancellation will occur in one direction and reinforcement in the other.

This is illustrated in Fig. 2 where the responses of a single dipole and of a dipole with a reflector are compared. Note that what we actually have done is to considerably reduce the size of the lobe which extended in the direction of the reflector. A portion of this lobe still exists, indicating that some signal can still be received from this direction, but it will be considerably weaker than the same signal approaching the antenna from the opposite direction. Thus, where the simple dipole was bidirectional, the same array with the addition of the reflector is now largely unidirectional. Furthermore, the amplitude of the remaining large lobe is greater by an average of about 4 to 5 db.

The gain of a dipole and reflector will depend on the distance between the two wires and the length of the reflector (assuming that the dipole is resonant at one specific frequency). For the sake of this discussion, and because it is generally true, we will assume that the reflector is 5% longer than the dipole. Under these conditions, the gain of this combination will vary with reflector spac-

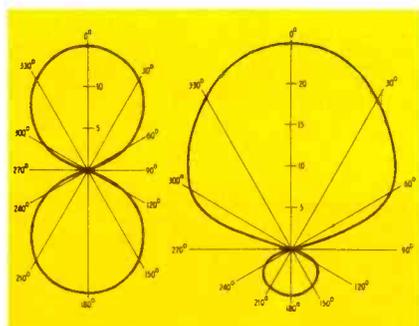


Fig. 2. Response patterns of dipoles with and without a reflector.

ing in the manner shown in Fig. 3. For very close spacing, the gain drops far below that of a simple dipole alone. As the distance between the two wires increases, the gain rises sharply, reaching a maximum at about 0.2 of a wavelength (at the operating frequency). The gain here is about 5 db; beyond this point, it slowly drops again.

This behavior can be explained by first noting the effect of the reflector element on the dipole and then by taking into account the distance between the two. An oncoming signal, approaching the dipole, energizes it. At the same time, some of this signal travels on to the reflector and excites this wire. If the two wires are .25 wavelength apart, the reflector interception occurs a quarter of a cycle later. At the time this happens, the dipole is re-radiating half of the energy it received* and some of this signal travels on to the reflector. This, too, takes a quarter of a cycle, and by now the reflector is ready to re-radiate all the energy it received a half cycle before. (Essentially all the energy received is re-radiated because the reflector is not loaded down by a transmission line.) Some of this energy travels back to the dipole where it combines (in phase) with the signal present here.

The foregoing, while revealing only a part of the energy interchange between the dipole and reflector, does demonstrate how the two wires interact with each other. The signal which the reflector re-transmits to the dipole is dependent on the spacing between the wires plus the length (i.e., resonant frequency) of the

* The other half of the signal received by the dipole is transferred to the transmission line if the two are matched.

• Please turn to page 65

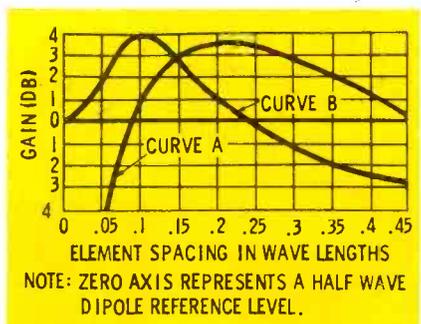


Fig. 3. Gain curves of dipole and reflector (A) and dipole and director (B).


THERE IS A DIFFERENCE IN P. A. SPEAKERS

you get a lot more to sell with

Electro-Voice[®]

CDP[®] SPEAKERS

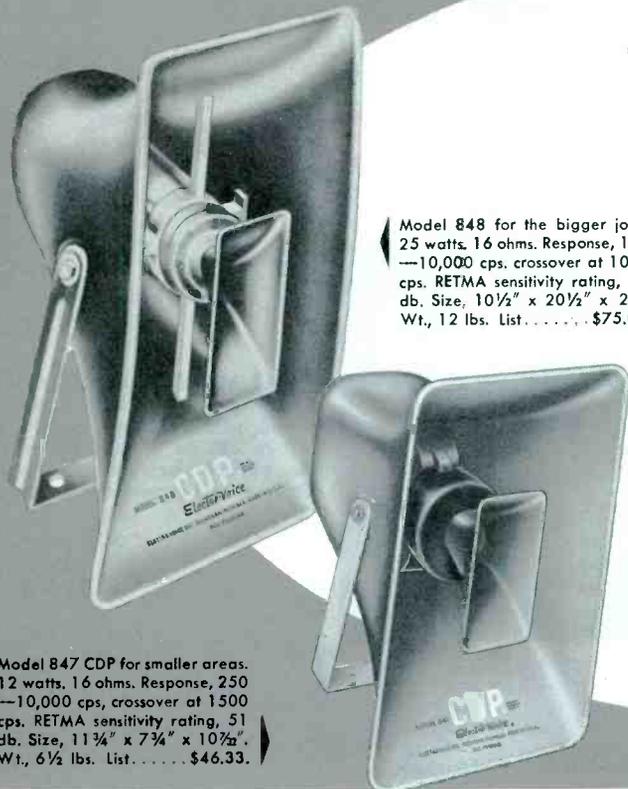Yes, Electro-Voice gives you more to sell and more help in selling P. A. speakers. Hard-hitting, sales-pulling ads pre-sell architects, buyers in schools, universities, colleges, industry and all your prime P. A. prospects. They are told the CDP story . . . and what a terrific story it is. To tell it is to sell them!



Model 848 for the bigger jobs.
25 watts. 16 ohms. Response, 175
—10,000 cps. crossover at 1000
cps. RETMA sensitivity rating, 52
db. Size, 10½" x 20½" x 20."
Wt., 12 lbs. List. \$75.00.

Model 847 CDP for smaller areas.
12 watts. 16 ohms. Response, 250
—10,000 cps. crossover at 1500
cps. RETMA sensitivity rating, 51
db. Size, 11¾" x 7¾" x 10½".
Wt., 6½ lbs. List. \$46.33.


HERE'S WHY CDP SPEAKERS ARE SO SUPERIOR, SO MUCH EASIER TO SELL THAN CONVENTIONAL P. A. HORNS . . .

High frequencies require one throat size and one horn taper rate; low frequencies require a different throat size and a different taper rate. The Electro-Voice CDP gives you a large horn (A), for lows and a second, smaller horn (B), coaxially mounted, for highs working from both sides of a single diaphragm (C). The Electro-Voice CDP gives you 2½ more octaves of sound reproduction . . . frequencies up to 10,000 cps. These 2½ octaves are indispensable for highest intelligibility. See the curve, compare response and efficiency. In addition, Electro-Voice CDP speaker disperses sound through a solid 120° angle for the widest coverage available in P. A. speakers.


You can hear the difference.

Conventional reentrant horns using single throat (D) and single horn (E) transmit highs along the same circuitous path (F) as required for lows. As a result, the highs become attenuated, sharply decreasing intelligibility. Electro-Voice gives you P. A. speakers with a large horn for lows and a second, smaller horn, coaxially mounted, for highs. **There is a difference and you can hear it.**

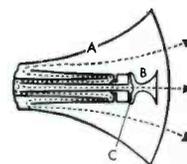1 This is a CDP Speaker with its two coaxially mounted diffraction horns.




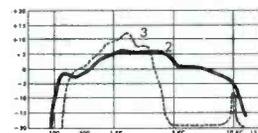2 This is the frequency response curve of a CDP.



3 This is the frequency response curve of a conventional P. A. horn.

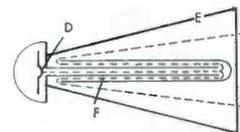4 This is a conventional reentrant-type P. A. horn.



Electro-Voice

ELECTRO-VOICE, INC., BUCHANAN, MICHIGAN

EXPORT: 13 East 40th Street, New York 16,
U. S. A. CABLES: ARLAB.

CDP speakers are weather-proof, blast-proof and splash-proof, virtually indestructible. They're molded of fiberglass for better acoustical properties and extra strength.

Sell CDP Speakers . . . the speakers that sell because they are clearly superior. See your Electro-Voice Distributor TODAY. Get the facts and start selling the most revolutionary speakers in P. A. history . . . the Electro-Voice CDP.

Send for bulletin 195-R 83

what do INDOOR

Basically, all indoor antennas operate on the simple dipole principle. This means that in order to be useful on all channels, the dipole arms must be adjustable from approximately 25" to 103" which are the lengths necessary to resonate at the lowest frequencies of channels 13 and 2, respectively. To form a dipole, the arms of the antenna must be extended to the correct length and placed in a horizontal plane; however, since a perfect picture may not always be received (using the antenna in this configuration), it may be necessary to incline the arms of the dipole into a wide "V" shape. In this position the antenna is no longer a strict dipole but is instead something between a dipole and a tuning stub. Raising the arms of the antenna shortens them electrically, so you may find it necessary to physically lengthen them to achieve maximum signal pickup.


The lead-in wire is almost always 300-ohm twin-lead because it matches the receiver input impedance, a must if standing waves are to be avoided. However, there is an automatic 4-to-1 mismatch at the dipole, which is essentially a 72-ohm device. This mismatch causes a loss of signal, but this usually isn't serious except in weak or noisy signal areas.

Matching or phasing stubs that can be switched in and out of the dipole circuit in several combinations have been added to the indoor antenna to improve its reception ability. The switch may have anywhere from 5 to 12 positions and is generally adjusted to the position that gives best reception by a "trial-and-error" method. This switch tuning is used in conjunction with rotating the antenna and lengthening or shortening the dipole arms to obtain the best possible reception. In addition to (or instead of) a switch for connecting the phasing or matching stubs, some designs include variable-value inductors or capacitors which can be adjusted to change the electrical length of the dipole elements; thus, the dipole arms can be physically shorter than $\frac{1}{4}$ wavelength each and yet be the electrical equivalent. Also, antenna tuning is less susceptible to the hand capacity effects encountered when trying to lengthen or shorten the dipole.

Normally you think of an antenna as being properly oriented when the broadside of the dipole faces the station. This does not always hold true for indoor antennas, since there are usually many reflections within any given room. Thus, best reception on some stations is often obtained with the antenna pointed at some odd angle and reorientation is usually required when switching to other stations.



TV Channel No.	Approximate Length
2	103"
3	92"
4	84"
5	73"
6	67"
7	31"
8	30"
9	29"
10	28"
11	27"
12	26"
13	25"

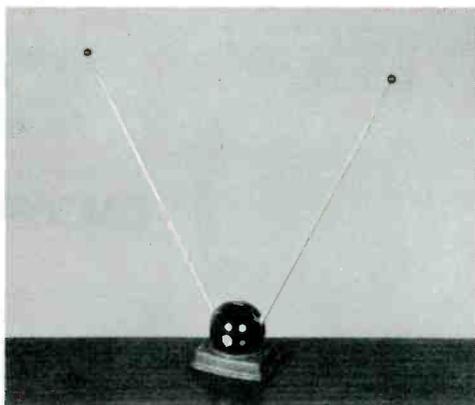**HALF-WAVE DIPOLE
LENGTHS FOR TV CHANNELS**




<RMS Model SV-A3 features 3-section aluminum arms which stem from a round, plastic housing and extend from 16" to 39" in length along axes from the vertical extreme to within a few degrees of horizontal.

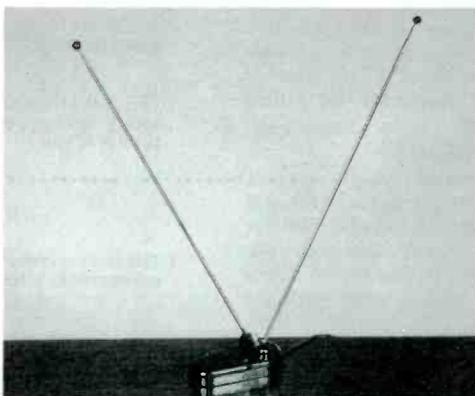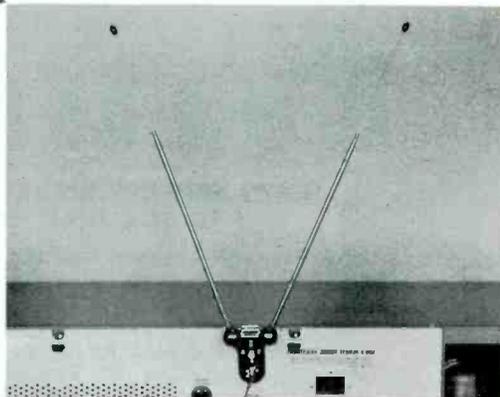Radian Model 900S is designed for rear mounting with 3-section arms which extend from 12" to 30½" and swivel on adjustable-friction ball-and-socket joints, permitting 40° forward or rear arc and 180° side arc from a straight-up to straight-down position (latter when not in use). >




Channel Master Super Showman which, for all VHF channels as well as FM, has switch indexing that varies the inductors in series with the dipole arms. These internally-mounted inductors, combined with the inductive, end-loaded "hats" and extendable dipole arms, permit an accurate electrical dipole length to be obtained over a range of 54 to 216 mc. A parasitic reflector, physically spiralled at the center to increase its electrical length, provides a front-to-back ratio of up to 5:1, and a transformer matches antenna to receiver impedances. The housing swivels 360° on its tripod base. >
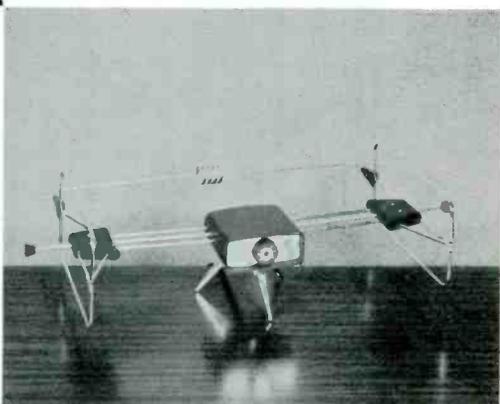
<Radiart Model CT-231 uses 2-section dipole arms which will pivot on their axes more than 180° and extend from 20" to 37½". The plastic, tear-shaped base has recessed screw-mounting facilities and a slotted thumb screw for adjusting pivot friction.




you know about

ANTENNAS ?

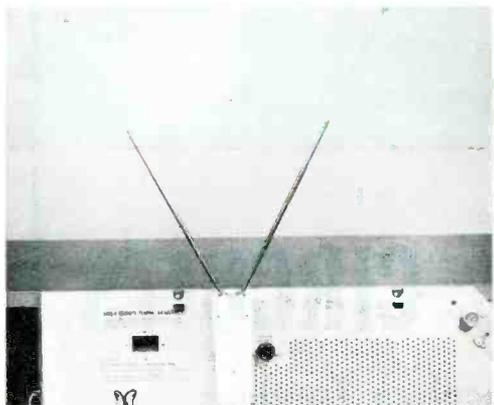

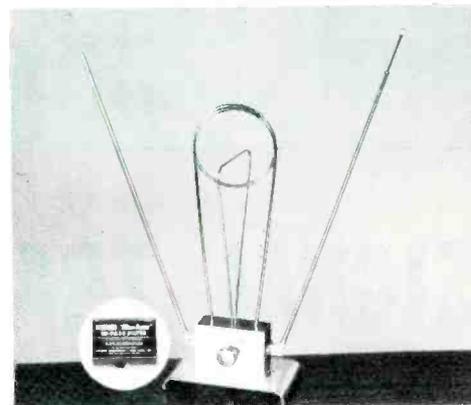
< **Brach Model 5609** has extendable (total 38") 4-section arms that telescope into a rear-mounted plastic housing when not in use and that swivel in any direction to a maximum of 55° from vertical on ball-and-socket joints held in place by spring tension.




^ **Dynamic Model DB500** has two phasing elements oriented 90° from each other and connected in various configurations to the dipole (adjustable from 18" to 34") through a 12-position switch. A high-pass filter in the twin-lead serves to minimize low-frequency noise interference. The dipole arms can be positioned individually at any point from vertical to horizontal.

JFD Magic Genie is designed for rear-set mounting, which can be accomplished with the use of a special solvent (making the rubber mounting surface adhesive), bolts and nuts or wood screws (all hardware and solvent supplied). The 4-section, turret-mounted arms (maximum length 38") can be swiveled in practically any direction within the upper spherical area and can therefore assume a horizontal "V" position if desired. An inductive printed-circuit stub can be switched into the dipole circuit in series and parallel combinations to provide optimum performance on each channel. >

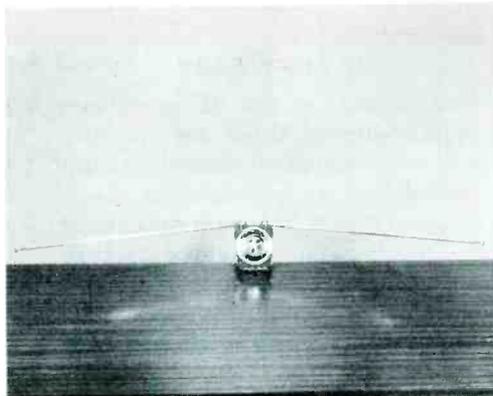



< **Amphenol Vi-Fi Model** features 5-section, ball-and-socket mounted, 27" arms which can be folded down and hidden with a hinged cover. The electrical length of the arms is extended through the use of variable-value inductors contained within the housing, which also conceals a separate UHF folded dipole having its own 300-ohm lead-in. The VHF 4-conductor lead-in is wired and connected to act as a matching transformer between the 72-ohm antenna and 300-ohm set impedances.

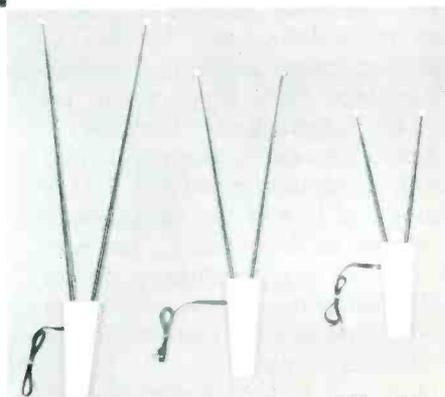

^ **G-C Telco Models 8146, 7 and 8** are rear-mounting units having 4, 5, and 6-section dipole rods which are extendable to 29", 37" and 44", respectively, and which can be stored within the housing when not in use. Ball-and-socket joints permit each arm to be swiveled approximately 55° from vertical in any direction.

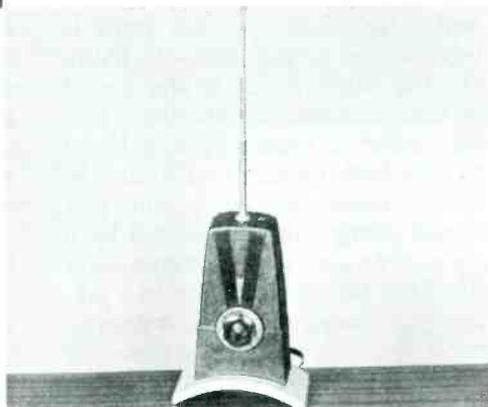Snyder Imperial Model 10D has only one visible dipole arm, a 4-section unipole which can be extended to 48" and collapses to 7". This unit takes advantage of the vertically-polarized signal components developed within a room by reflection. A 12-position switch connects a concealed dipole arm and a 300-ohm matching stub in and out of the circuit for improved reception at various frequencies. >



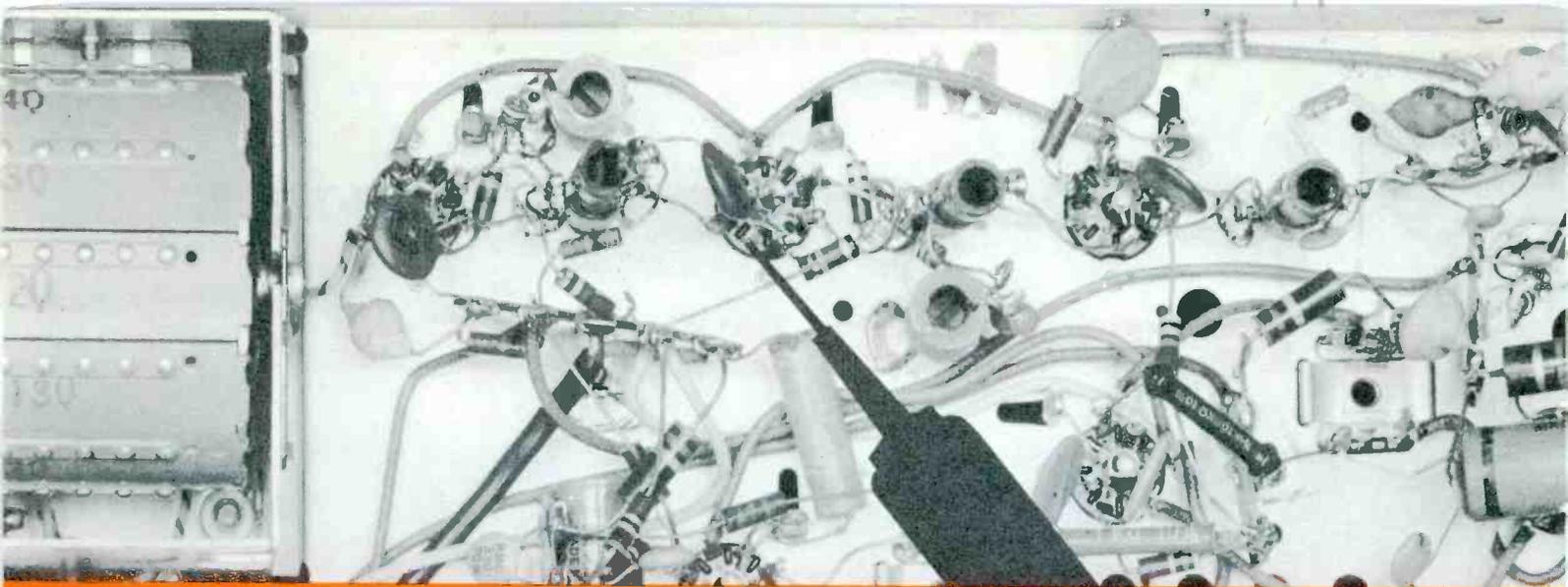

SIGNAL TRACING RF & IF CIRCUITS

Using a Scope and Signal Generator to Localize Troubles

by Les Deane

Unfortunately, signal tracing in itself seldom will correct a fault in a receiver—yet without some expedient means of trouble localization, the technician may find himself making needless time-consuming measurements and parts substitutions. Signal tracing is of tremendous value in overcoming the first and seemingly ominous barrier—namely, that of isolating the trouble to one particular stage or section. Why place such an emphasis on trouble localization? Because it not only represents the major time spent on most shop repairs, but is also a real test of the technician's servicing skill. Actually, the mechanics of pin-pointing a defect and making necessary corrections are only secondary factors in successful servicing.

Due to a lack of knowledge of either circuit functions or the application of test equipment (or the lack of necessary equipment), many technicians feel a little lost when probing ahead of the video detector circuit. This article should clear up some of the uncertainties connected with RF and IF signal tracing besides presenting several logical methods of approach.

Aside from a complete loss of signal, there are many other trouble symptoms that may result

from a fault in the RF or IF circuits. Some of these are: picture and sync distortion caused by hum modulation or interference, weak or snowy pictures, ringing caused by regeneration, smeared picture or loss of detail and last but not least, intermittent picture and sound. When confronted with any one of the symptoms just mentioned, we often come to the realization that the trouble is originating somewhere ahead of the video detector. Sometimes we can further isolate the trouble, however, by carefully analyzing all of the symptoms involved. For example, with loss of video, we should also check for the presence of sound and/or snow.

Practically all modern receivers employ an intercarrier sound system; therefore, a missing picture with the presence of sound normally indicates that the fault is beyond the sound take-off point. On the other hand, if the sound is also affected, we should direct our search to those stages designed to pass both picture and sound. In a few cases, however, sufficient sound energy may be passed by a defective stage which is apparently blocking picture information. Actually, some picture carrier energy must get through to the detector in order for the heterodyne action

which produces the 4.5-mc sound signal to take place. It is conceivable, however, that the video frequencies may be too low in amplitude to reproduce a noticeable picture.

Snow in a raster is also a key clue in the isolating procedure, since it is the result of thermal agitation within the converter tube. Its absence usually indicates that the trouble is beyond the mixer stage. When snow does appear, however, the signal is being lost ahead of this stage and may be due to a faulty antenna system. We should never lose sight of the fact that our trouble may be resulting from only a poor antenna connection, from more than one defective tube, or from a simple misadjustment of an AGC or sensitivity control. In the same vein, we must remember that proper operation of the tuner and IF strip depends not only on received signal strength, but also on AGC and B+ voltages. A quick check of these may save precious time when trouble is apparently affecting RF or IF operation.

When loss of signal is encountered, the first step the technician usually takes, after tube substitutions, is a few quick voltages measurements with a VTVM. Checking all plate, grid, and cathode points

along the IF strip requires little time and will often locate the defective stage immediately, but what happens in those all-too-often instances when the voltages appear to be within tolerance? At this point, the average technician might wonder if the tuner is delivering a signal, if the crystal detector is bad, or even if the transmitter is on the air. Undoubtedly the only way to be sure is to adopt a signal tracing procedure of some sort.

The RF Probe

The oscilloscope is very useful as a signal tracer in practically all circuits of a television receiver. This also holds true for the RF/IF stages, but because even a wide-band TV service scope will not

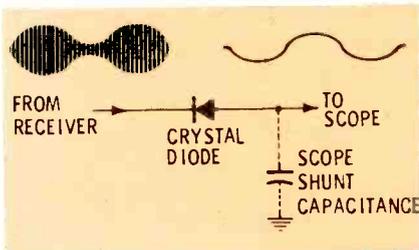


Fig. 2. Use of this simple detector circuit demodulates RF or IF signal.

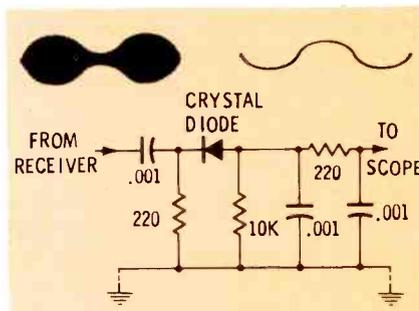


Fig. 3. Demodulator circuit often used in TV alignment work.

respond to frequencies much over 3 to 4 megacycles, one cannot observe signals in these sections using an ordinary direct probe. To overcome this problem, the technician need only use a demodulator probe, which, in actuality, serves as a mobile video detector circuit and converts the modulation to frequencies which will be readily passed by the scope's amplifier circuits.

The schematic of Fig. 2 represents a simple detector probe suitable for signal tracing with an oscilloscope. A crystal diode, such as a 1N34 germanium type, rectifies the modulated RF or IF frequency, and the output developed

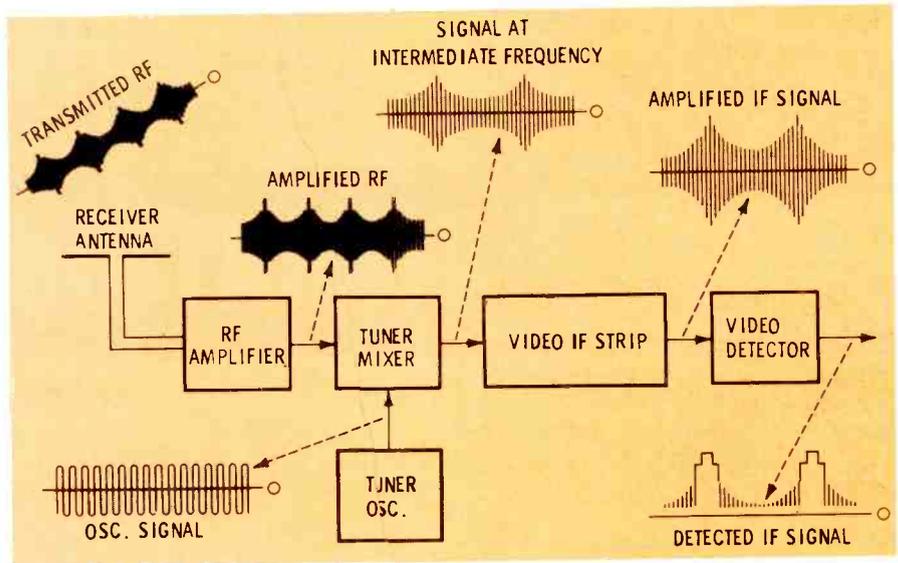


Fig. 1. Block diagram of RF and IF sections and signals present at various points.

across the input shunt capacitance of the scope varies in accordance with the peak amplitude of the input signal. A somewhat more elaborate probe circuit, designed primarily for TV alignment work, is shown in Fig. 3. The capacitor and resistor at the input of the probe are used for isolation purposes, while a conventional germanium crystal diode serves as the rectifier. The 10K-ohm resistor acts as a diode load and the 220-ohm resistor, together with a pair of .001 mfd capacitors, forms an RF filter network.

Scoping the TV Signal

Several signal tracing methods may be used, but the one chosen by the technician is usually determined by the nature of the trouble, the test instruments available and how well acquainted he is with the circuitry involved. Generally, a signal tracing procedure will require less time than

is necessary to tell about it.

A completely dead stage in an IF strip can sometimes be located by merely touching a metal-tipped probe to the grids and plates of the amplifier tubes and noting whether or not there are clicks in the sound or flashes on the screen. When encountering the inoperative stage, one will usually find that he can obtain a click or flash by contacting the plate connection, but not when touching the grid of the same stage. Sometimes this simple approach may work for the experienced screwdriver mechanic, but it's far from fool-proof and is of little value when running down troubles other than a completely dead stage.

A more reliable and systematic approach is to use a detector probe and an oscilloscope. Using a probe to demodulate the TV signal of a local station, the technician can

• Please turn to page 71


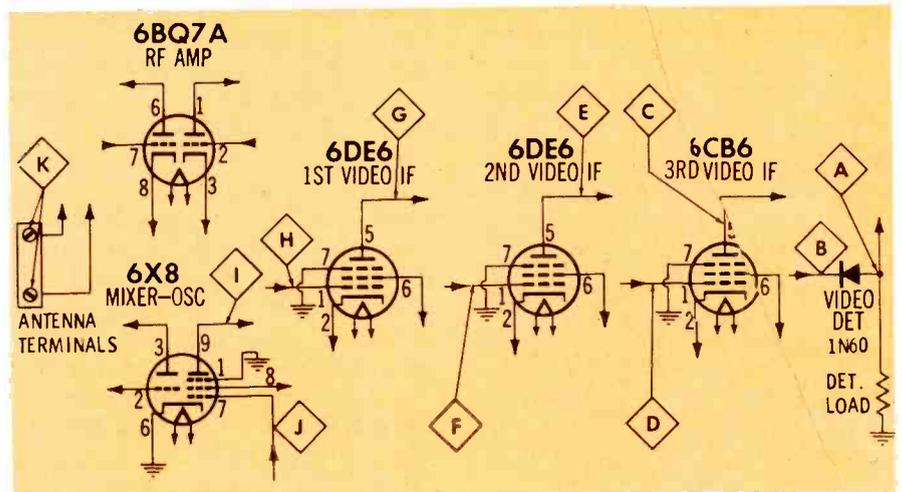


Fig. 4. Test points used in RF/IF signal tracing a typical receiver.

MAGNETIC
PICKUP MOUNTED
ON TOOL POST

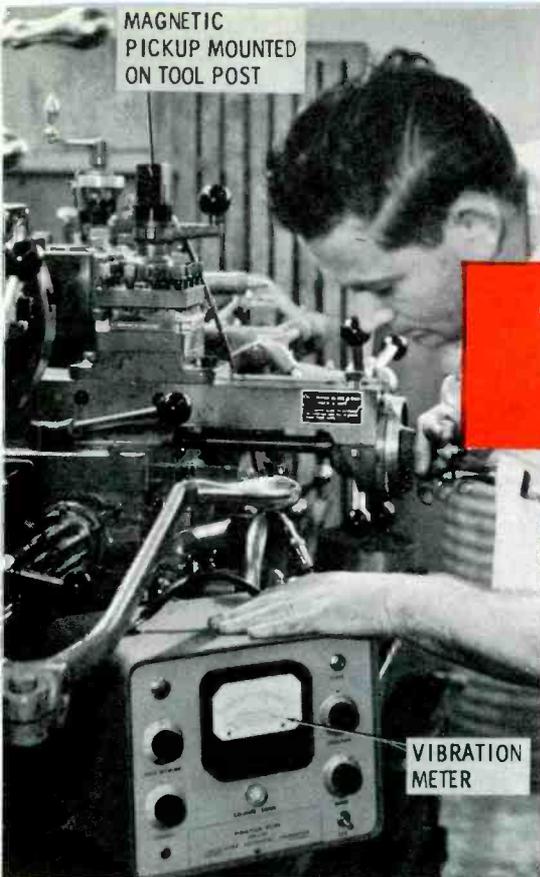

(Courtesy Consolidated Electrodynamics Corp.)

Fig. 1. Measurement of machine vibration aids in producing quality products.

Undesirable vibrations which develop during industrial processing can be the result of any number of causes, among which are liquid hammer, valve singing, shaft movement and cutting-tool chatter. The consequences of vibration are noise, discomfort, wear, malfunction, or destructive failure which must be limited to acceptable levels. Machine tool operations are often hampered by minute vibrations which produce rough, inaccurate finishes and result in damage to cutting tools. The machines used in our daily living, transportation vehicles on land, sea, and air and our complete mechanical environment exhibit vibratory motion; therefore, in research, production and usage,


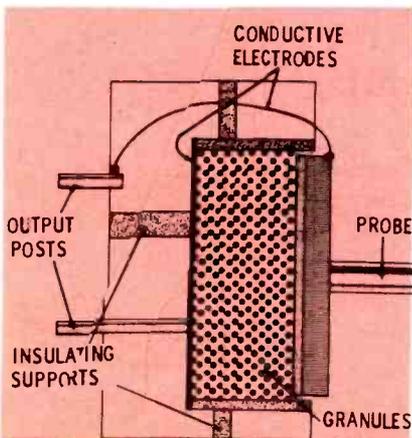


Fig. 2. Carbon granule vibration pickup

part 7

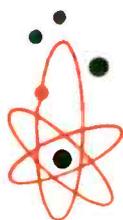

Servicing Industrial Electronics

VIBRATION SENSERS

by Melvin Whitmer

vibration must be sensed, measured and controlled.

The vibration sensors of today make the smooth-running, high-powered automobile engine a reality instead of an engineer's dream. The forge plant controls the quality of each casting by ultrasonic flaw detection. The castings are milled on machines which are checked for vibrations originating from their cutting and rotating members. Drilling and boring machines must be free of vibrations to assure accurately-machined pieces. The shape, weight and composition of each engine part must not contribute to harmful resonant frequencies. Finally, the completed engine is tested for vibration, and the hoped for result is a quiet engine with a soft, even purr.

Vibration is a recurrent physical movement which has three qualities: amplitude or displacement, frequency and velocity of motion. These three are related very simply by the formula $F = \frac{V}{2D}$; where F = cycles per second, V = inches per second, and D = peak-to-peak displacement in inches. Thus, when any two vibration characteristics are known, the third can be easily determined. To illustrate the use of this formula, let's see how it was applied in an actual case.

A production line was halted because a turret lathe had developed the trouble symptom of abnormally short tool life. A microscopic view of the cutting edge indicated very little wear; however, severe chipping and fracturing had obviously taken place, a condition which could be the result of an abnormal vibratory action. The first step toward localizing the problem was to de-

termine the values of two of the vibration characteristics. This was done with the use of the vibration pickup instrument shown in Fig. 1. The unit was bolted to the tool post and connected to the meter which indicated that the vibration was most excessive at 600 cps and that the amplitude (displacement) was .0003". Knowing this, the foregoing equation was applied and the velocity was determined to be .36 inches per second. The combination of data indicated that the trouble was isolated to the tool supports or was the result of improper cutting speed.

Tightening the tool post and changing cutting speeds did not correct the trouble. The complete tool mount and base were then disassembled, and the trouble was found to be the result of improper seating of the tool post to the base. Regrinding and lapping the post and seat eliminated the vibration.

The production line was stopped only 20 minutes by this problem. Vibration tracers reduced the down-time of this production line from 3 or 4 hours to a short 20 minutes for problem analysis and corrective measures. Since the importance of such test units is obvious, we shall now examine the workings of some typical instruments.

Resistive and Capacitive Sensors

Vibration sensors generate an electronic signal by sensing at least two of the three variables, usually frequency and displacement as in the foregoing example. The carbon-granule pickup shown in Fig. 2 is very much like the carbon mike used in audio work and functions as a resistive sensor. The compression of the carbon reduces its resistance in proportion

PF REPORTER • March, 1958

to the degree of pressure; thus, displacement is determined by the change in resistance, and frequency is indicated by the number of compressions per second.

The capacitive sensor of Fig. 3 resembles the capacity mike in both construction and operation; i.e., the diaphragm serves as the movable plate of a capacitor connected across the output terminals. Displacement is thus determined by the amount of change in capacity value, and the rate of change indicates the frequency. The plates are heavier than those used in the standard microphone since these sensors must be capable of rather severe shock measurements in addition to dynamic vibrations.

Magnetic Sensors

Another common type of vibration sensor involves the use of an induction coil and two basic principles of magnetism. The amount of voltage generated across a coil by a magnetic field cutting its windings is a function of the rate of field movement. When the magnet moves slowly, the voltage across the coil will be small regardless of the total movement. Also, reversing the direction of movement will reverse the generated voltage polarity; thus, velocity and frequency are the two vibration characteristics which can be measured by this unit.

A magnetic sensing unit is shown schematically in Fig. 4. As vibration moves the magnet, the coil generates a voltage which is applied to an RC-coupled, wide-band amplifier consisting of several stages. After the signal is amplified, it is applied simultaneously to the two sections of a dual diode V1. V1A couples only the

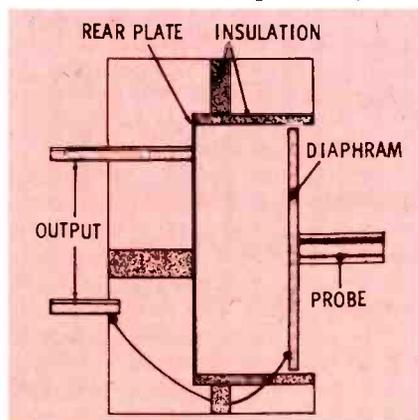


Fig. 3. Capacitive vibration sensor.

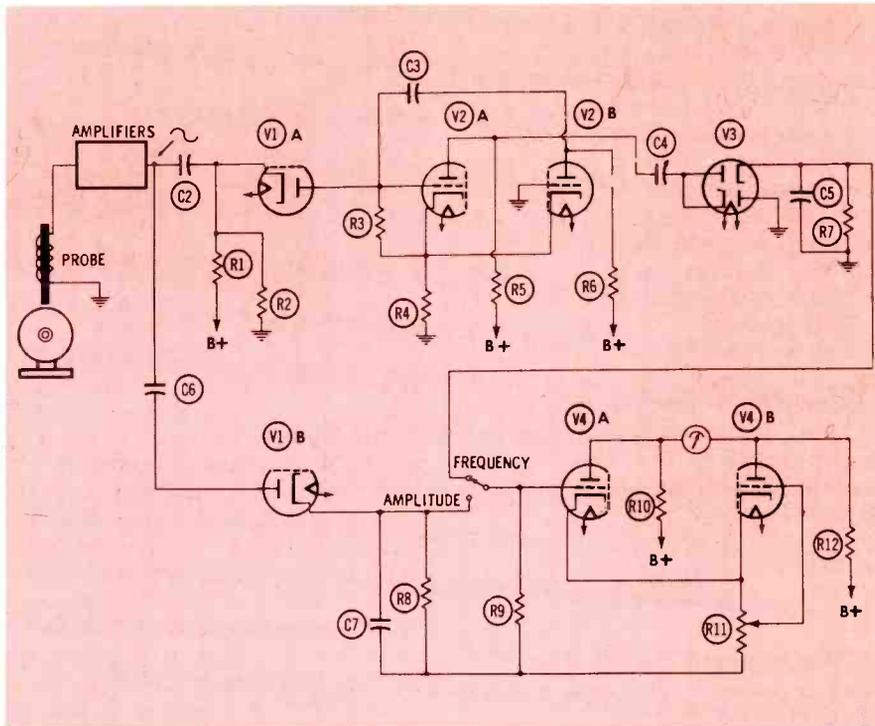


Fig. 4. Diagram of vibration instrument which measures frequency and velocity.

negative portion of the signal to V2, a cathode coupled multivibrator with its input grid resistor R3 returned directly to cathode rather than ground.

This circuit is similar to the vertical sweep oscillator in many television sets, the only difference being that fixed bias on the input section is always zero and V2B therefore cannot bias V2A into cutoff via the cathode resistor R4. The voltage developed across R4 during V2A conduction will bias V2B beyond cutoff, however, V2A conducts until a negative pulse is applied to its grid; and as conduction decreases, so does the voltage across R4, until it reaches a level which will permit V2B to conduct. Capacitor C3 will then couple a negative pulse back to the grid of V2A, and V2A will stay cut off until C3 discharges. When this happens, V2A comes back into conduction and remains in this stage until the next input pulse reaches its grid.

Since this circuit goes through one complete cycle for every input pulse, it is called a one stable state (V2A conducting) multivibrator. The primary reason for using this type of pulse generator is the constant amplitude, constant duration pulse it forms. The input pulse may be of varying shapes and amplitudes, but the output will always be the same (changing

in frequency, of course, in accordance with the input signal).

V2A generates a positive pulse which is coupled through a small value capacitor to a clipping circuit. Diode V3A passes the negative spike to ground and diode V3B couples the positive pulse to capacitor C5. Resistor R7 completes the conduction path for the diode. The voltage across C5 is proportional to the average voltage of the pulses applied to V3B, and since the amplitude and duration of the applied pulses are constant, the average voltage depends only upon their repetition rate. Thus, the voltage across C5 is actually a measure of the frequency of vibration. The VTVM circuit of V4 is used to determine what that voltage is.

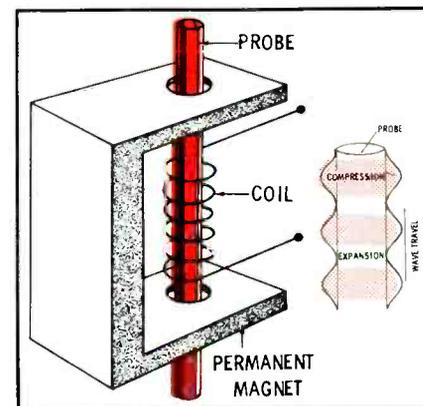


Fig. 5. Ultrasonic pickup device and wave action of air molecules.

Chip In. We salute the technicians of Western Electronics Assn., Cheyenne, Wyo., who banded together to take care of member Joe Delhaute's service calls during his illness. They donated their time and presented all servicing receipts to Mr. Delhaute. When an ad was placed in the local newspapers to inform the public of the situation, calls to the Delhaute shop increased.

The good will generated by this incident should last for a long time. We know that most TV servicemen are honest human beings, but it makes us feel good to see somebody demonstrating this fact to the world.



"No School Today; The TV Blew a Tube!" The next generation of youngsters may be pinning their fondest hopes on "tough dog" sets to provide a good excuse for getting out of schoolwork. About 200 schools are already using closed-circuit classroom TV in some way, and a tremendous boom could develop in this field as electronic teaching techniques become better developed. The largest single installation is in the Hagerstown, Md., area, where a 5-year investigation of school TV's possibilities is being backed by EIA and the Ford Foundation. All schools in an entire county are being connected by cable, and a variety of courses are being taught from central studios.

Here's another opportunity for the alert service shop to create new business. How about letting school boards know that competent service will be promptly available for any TV equipment they decide to buy?



Stay Put. How can dealers afford to give home demonstrations of color TV sets, in view of the high labor cost involved? The answer is that dealers who successfully follow this practice sell an extremely high percentage (up to 90%) of the receivers they bring into prospects' homes. They also try their best to avoid unnecessary expense in providing demonstrations. A smart installer's first move is to establish a set location which the customer will accept as permanent. Then the purity and convergence touch-up adjustments



made for the demonstration will be the final adjustments.

When helping a customer plan a receiver location, consider the following points: Will bright light fall directly on the screen at any time of day? Does the heating system in the room make a "hot spot" near the set? Will it be awkward to run a lead-in from an outdoor antenna? If the answer to any of these questions is "Yes," suggest a different place in the room.



Transistor TV. Motorola unveiled a fully transistorized 14" portable recently, but doesn't plan to market it commercially until the price of transistors comes down. (The set requires 31 of them.) Far from being a miniaturized unit, it's fairly hefty—32 lbs. But it's a true cordless portable, powered by two nickel-cadmium batteries which are recharged after each 6 hours of operation by plugging the set into an AC line for 2 hours. Longer playing time for any battery-operated TV won't be practical until someone figures out a way of drastically reducing sweep-power requirements.



Test Your Tact. Success in making home service calls depends on a lot of little things, such as your ability to keep a straight face while making sensible replies to customers' comments. No matter how wacky or downright ignorant such comments may sound to you, they are usually spoken in all earnestness.

One time we answered a call from an old lady whose complaint was intermittent flashing and streaking in the picture. We were unable to induce these symptoms in the set, and told her, "The

trouble may be in the transmitter."

"Oh, but it couldn't be," she declared. "I'm sure we had that replaced the last time the set was fixed."

Could you have maintained your professional dignity after that one? Better try; for all you know, she might own the station!




Sample of Pay TV. Subscription television may get its first real on-the-air test soon. Sometime after the first of this month, the FCC plans to act on station applications which it began accepting last December. The first request for toll operation was filed by a Philadelphia firm seeking to try out pay TV on UHF Channel 29. The proposed station would furnish to subscribers a combination decoder and UHF converter, and would supply a program of major sports events for a flat yearly fee—\$30 for homes and \$100 for commercial establishments. Special events such as stage shows would also be put on periodically, with an extra fee collected for these.



Transistor Tip. When circuit tracing in transistorized equipment, do you have trouble telling a p-n-p transistor from an n-p-n? If so, check the collector voltage. If this is negative with respect to the emitter voltage, the transistor is of the p-n-p class; if positive, the transistor is n-p-n.

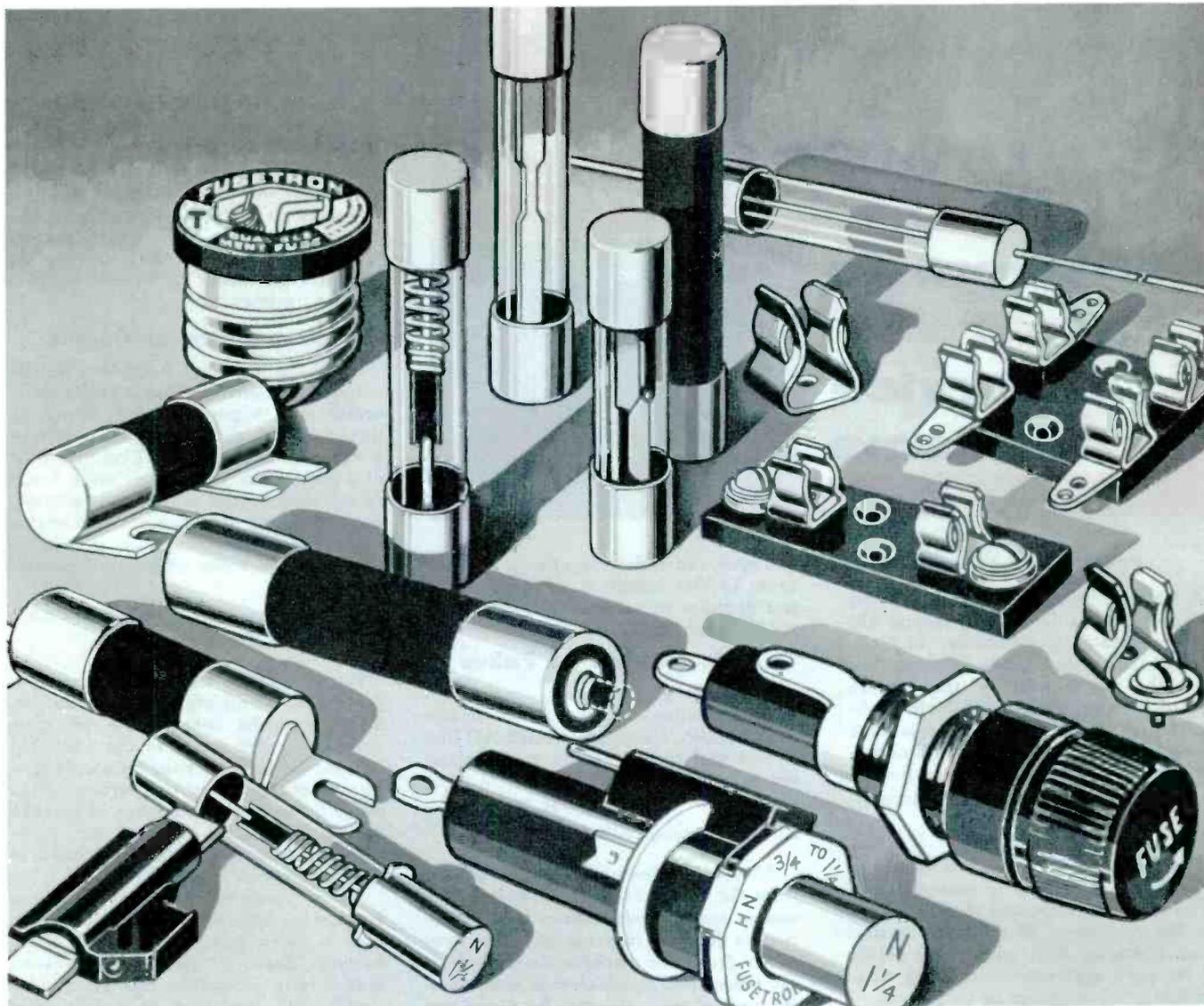Understanding this point will also help you remember how to connect a battery to a transistor circuit—provided that you know which class of transistor you are working with. The *middle* letter of the class designation (p-n-p or n-p-n) always indicates whether the *positive* or *negative* terminal of the battery should be returned to the collector circuit.



You can rely on BUSS FUSES to operate as intended.

Here's why—With BUSS fuses, dependable electrical protection isn't left to chance. BUSS fuses are tested in a sensitive electronic device. Any fuse not correctly calibrated, properly constructed and right in all physical dimensions is automatically rejected.

The result,—BUSS fuses provide maximum protection against damage due to electrical faults. And just as important, they eliminate useless shut-downs caused by faulty fuses blowing needlessly.

With a complete line of fuses available, it is just good business to standardize on BUSS. Their "trouble-free" performance helps to safeguard your reputation for quality and service and . . . BUSS fuses help servicemen avoid costly, unnecessary call-backs.

BUSS fuses have ready customer acceptance . . .

Over the past 42 years, millions upon millions of BUSS fuses have been used in homes, industries and on farms. As a result, BUSS is the known brand of

fuses—accepted by the trade and consumer as the finest available. This means sales are easier to make because BUSS quality is never questioned.

For more information on BUSS and Fusetron small dimension fuses and fuseholders . . . Write for Bulletin SFB, Bussmann Mfg. Division, McGraw-Edison Co., University at Jefferson, St. Louis 7, Mo.

BUSS fuses are made to protect—not to blow, needlessly



Makers of a complete line of fuses for home, farm, commercial, electronic, automotive and industrial use.

the TROUBLESHOOTER

answers to
readers'
service
problems



Poor Vertical Sync

A Philco Model A-T1818 has always had poor vertical hold. By changing R95 to its original value, vertical hold was made perfect, but then the lower half of the picture tended to weave back and forth horizontally at a rapid random rate. Is some change in the sync separator still necessary to compensate for this condition?


CARL H. MILLER

N. Wildwodo, N. J.

The best approach would be to restore good horizontal sync by restoring R95 to its original value, and then to search for the real cause of the poor vertical sync. Changing R95 reduced the ability of the sync separator to produce clean horizontal sync pulses in its output.

Check the waveform at the grid of the phase inverter V15A, using a scope sweep frequency of 30 cps. Are the vertical and horizontal pulses of equal height and normal appearance? If so, look beyond the grid of V15A for your trouble. The vertical integrator circuit may not be operating properly because of a defective capacitor or some other cause. Instead of replacing individual components, you might be able to install a modern "packaged-circuit" type of integrator.

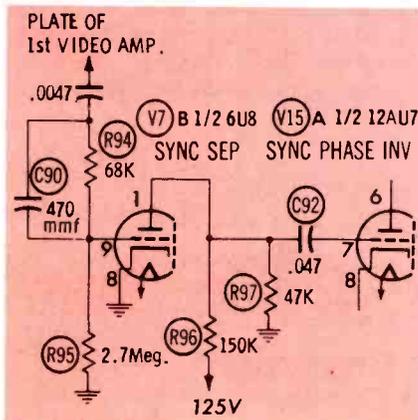If the vertical pulses at the grid of V15A are lower in amplitude than the horizontal pulses, check back through



the sync and video circuits to find the cause of this condition. One possibility is a decrease in value of a coupling capacitor such as C92.

P. A. Interference Pickup

In our place of business, we have an adding machine that "sounds off" in our P. A. system. Using an isolated AC line circuit and grounding the machine has not cured the trouble.

B. W. PREMO

Arroyo Grande, Calif.

You have eliminated direct pickup from the power line as a possible cause, and so we can only assume that radiation is feeding into the P. A. system either from the machine itself or from the power line to which it is connected. By any chance, do the P. A. system wires run parallel to the power line wiring for any distance? If so, shielding of the audio cables may help.

Oscillator Adjustments

In some TV sets, the oscillator adjustment slugs for individual channels are not accessible without removing the chassis. I understand there is often a general oscillator adjustment which is located on top of the tuner. Sometimes there are two adjustments, one for low channels and one for high. How can I identify these adjustments on the chassis and on the schematic?

ANTHONY C. JULIANO

Findlay, Ohio

The trend is away from general oscillator adjustments of the type you describe. In most late-model sets, individual channel slugs and the fine tuning control provide the only means of changing oscillator frequency. However, some tuners—particularly the older RCA and Standard Coil types—do have a coarse oscillator frequency adjustment on top of the chassis. On a schematic, it is shown in parallel with the fine tuning control. Check its location before turning any screws! This adjustment may improve over-all oscillator alignment in some cases, but probably you will

also have to check the individual channel slugs to obtain a really good job of alignment.

The Channel 6 and 13 screws located on the top and side of certain RCA tuners, as described on page 56 of the October, 1957 issue, are entirely conventional single-channel adjustments except for their physical location. Since they are in a switch-type tuner, they do have some effect upon oscillator frequency on lower channels; nevertheless, they are not meant to be used as "general" adjustments.

Sweep Generator Output

In all the articles I have read on the subject, it is advised that a sweep generator with a perfectly flat output be used to avoid misleading results. I have a sweep generator which I believe to be of a good make, but I have some doubt as to whether the output is absolutely flat. Assuming that some slight variations occur in the output, is it possible to align a TV tuner with any degree of accuracy?

ROY A. HIGH

Oakland, Calif.

The outputs of most generators used for TV servicing are not perfectly flat. There may be considerable variation over the entire range of the unit, but you should be concerned only with amplitude changes over the portion of the range being used. A variation of as much as ± 2 db can be tolerated for alignment of tuners—except those used in color receivers.

Many makes of sweep generators on the market have reasonably flat outputs over a given sweep range (± 1 db or better). Even if output varies considerably, a technician can use a generator with success if he knows what variations to expect and takes these into account when inspecting response curves.


Slight Vertical Trouble

On a Motorola Chassis TS-52, the vertical hold just barely locks in. If the height control is adjusted for an undersized raster, hold is improved; but if the raster is made even slightly oversized, all hold is lost and the picture rolls slowly. The blanking bar appears normal. Tubes have been checked and substitutions made in the sync and vertical stages, and voltage checks have also been tried.

CHARLES ANDREWS

Rochester, N. Y.

We assume that the vertical hold control will barely lock in the picture at one extreme of its rotation. This behavior indicates that the free-running frequency of the oscillator is too far from the normal value of 60 cps, with the result that the range of the hold control is insufficient to bring the circuit to the correct frequency. The vertical oscillator in this chassis is a multi-vibrator, so its natural frequency is determined by RC time constants and a check of resistor and capacitor values in the circuit is in order.

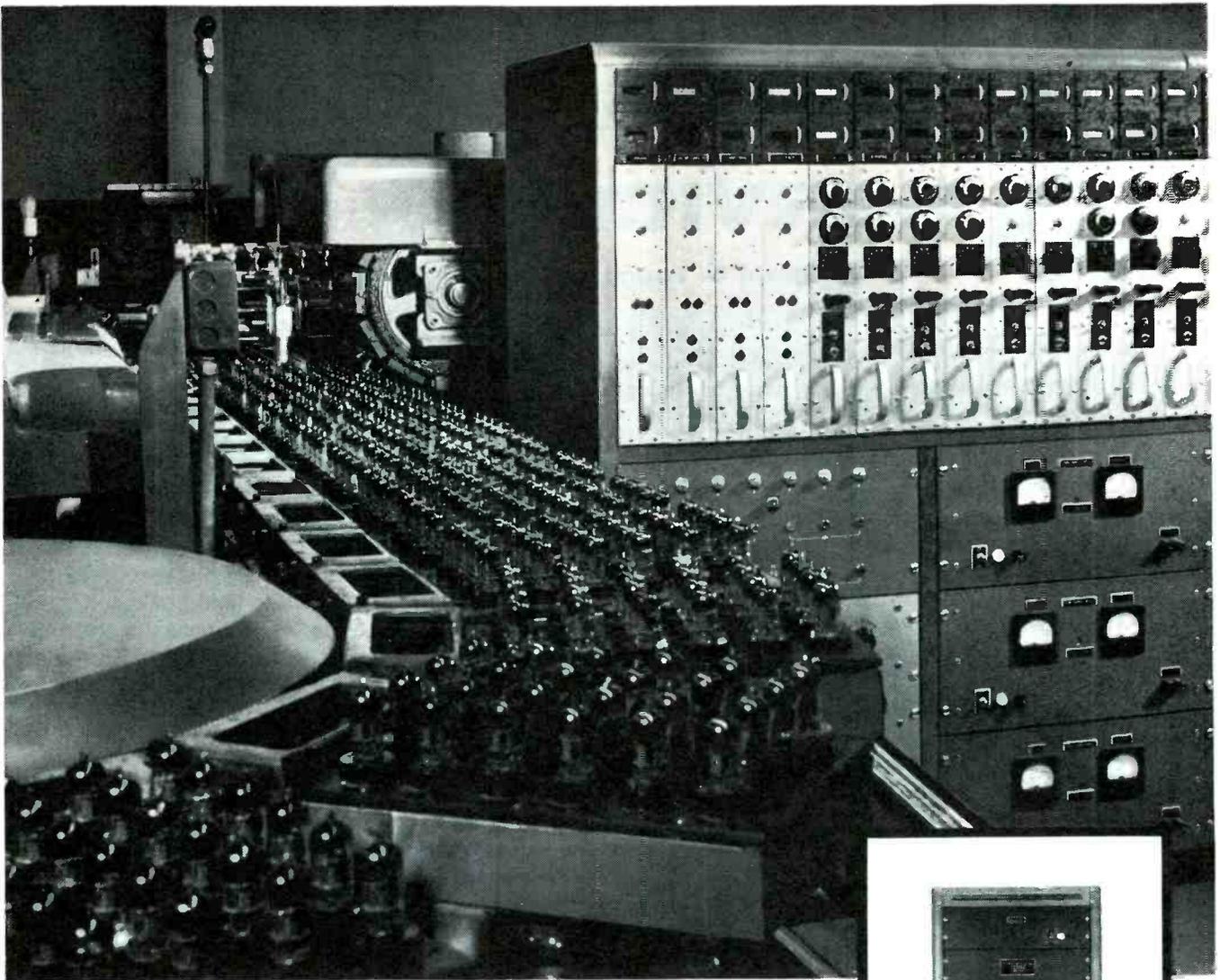

CBS tubes are mechanically transferred from the aging conveyor (left) to the automated tester (right) where they undergo up to 27 characteristics tests controlled by adjustable plug-in units.

Quality is Automatic with CBS


LET IT CUT YOUR CALL-BACKS AUTOMATICALLY

These automated test stations are part of a plan that makes quality automatic with CBS. They check CBS tubes and semiconductors more precisely, more completely. And they eliminate human error. To you, this advanced engineering means quality you can depend upon to cut your call-backs . . . automatically. Start using CBS tubes and semiconductors. Prove to yourself that automation does make a difference.

*Reliable products
through Advanced-Engineering*



tubes • semiconductors

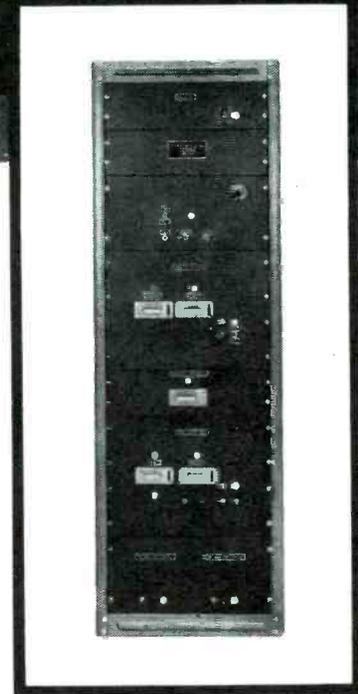

IN SEMICONDUCTORS, TOO! Matched to CBS mechanized diode production, this meterless test station double-checks automatically the quality built in by CBS automation.

FOR THE BEST IN ENTERTAINMENT TUNE TO CBS

CBS-HYTRON, Danvers, Massachusetts
A Division of Columbia Broadcasting System, Inc.



QUICKER SERVICING

by Calvin C. Young, Jr.

Special Resistor Applications

Do you know the purpose and function of each resistor in the horizontal output and high voltage circuit? Through a more complete knowledge of these components, discussed below, you will be better able to deal with any problems that arise. Fig. 1. shows the five resistors associated with the horizontal output tube. Two 47-ohm, 1/2-watt resistors are used as parasitic suppressors to prevent oscillations which would otherwise be sustained by the lead inductance and stray capacitance associated with the respective tube elements. The values of these components are not critical and can vary between 47 and 150 ohms. A substantial increase in the resistance of the grid-circuit unit, however, could cause distortion of the driving signal and a resultant nonlinear horizontal sweep. Should the 47-ohm unit in the screen grid increase by any appreciable amount, there would be a reduction of the screen potential and a corresponding reduction of horizontal sweep width.

The 1-meg, 1/2-watt resistor in the control grid circuit serves as a load for the drive signal. Any increase or decrease in the value of this unit will result in improper input impedance to the horizontal output stage and also change the loading on the hori-

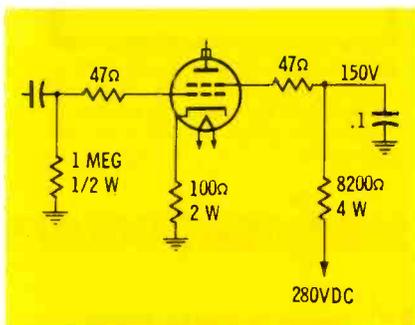


Fig. 1. Resistors associated with the horizontal output stage.

zontal oscillator stage. This can cause width or linearity troubles in addition to possible oscillator instability.

The 100-ohm, 2-watt resistor in the cathode circuit provides a self-bias voltage so that the tube will operate on the linear portion of its curve and, in addition, act as a protector for the tube should there be a loss of grid-drive signal.

The 8,200-ohm, 4-watt resistor in the screen grid circuit reduces screen voltage to the desired level and limits screen current to the specified value. Any material increase in the value of this resistor would reduce the screen voltage and cause a reduction of width, while a decrease in resistance would increase screen voltage and thus screen current to the point where it could damage the tube.

In Fig. 2, the 6.8K-ohm, 2-watt resistor is used to decouple the vertical and horizontal sweep sections. There is a filter capacitor (not shown) on the vertical end of this resistor to shunt all vertical signals to chassis ground. Any decrease in the value of this resistor will reduce the isolation between the two circuits and cause interaction, while any significant increase will lower the voltage applied to the vertical section and possibly cause insufficient vertical sweep.

Fig. 3 features a horizontal yoke circuit. The placement of the 1,000-ohm resistor is familiar to most technicians, and the fact that it helps to prevent yoke ringing is also general knowledge. Just how this is accomplished is not well understood. The capacitor is included to lower the resonant frequency of the winding and reduces its susceptibility to oscillate when pulsed. The resistor lowers cir-

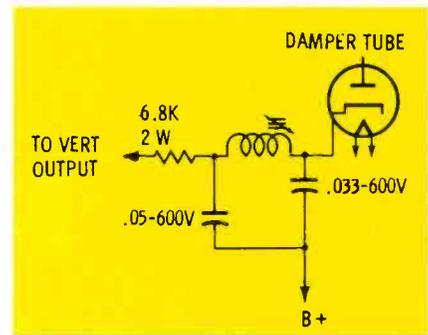


Fig. 2. Decoupling resistor used between vertical and horizontal sweep stages.

cuit Q and further reduces the tendency of the yoke to ring. Omission of this resistor (when it is specified) will result in severe ringing. The voltage across the top half of the yoke coil divides between the resistor and the capacitor in the ratio of their impedances and makes it possible to use a capacitor having a lower voltage rating.

The 470-ohm, 1/2-watt unit shown in parallel with the .22 mfd, 400-volt yoke return capacitor is included for centering purposes. Since the yoke is connected across the flyback transformer and the plate current of the horizontal output tube flows through the transformer, a portion of this DC current, limited principally by the resistor, flows through the yoke. This sets up a reference magnetic field and helps to center the raster. The .22-mfd capacitor is included to prevent pulses from developing across the resistor and lowers its wattage requirements.

In the circuit configuration of Fig. 4, the 1,000-ohm resistor is the only component installed to prevent yoke ringing; however, it also is important to raster centering since it provides a DC path to the yoke. This, in addition to the fact that it is subject to a small amount of pulse voltage, is the reason for

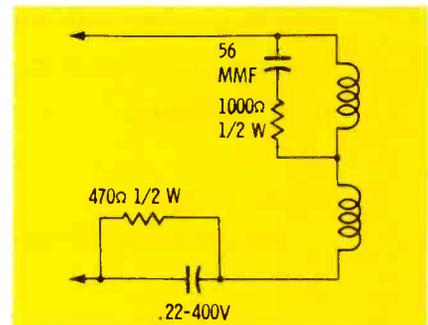


Fig. 3. Resistors used in yoke circuit to control ringing and centering.

... for bigger sales,
the big new

Super "8"

It's brand new! Extra heavy. The King-size "8" Ball, for today's king-size market . . . but at a regular price! Popular proved ball mount . . . adjusts up to 35°. Sleek and modern for today's cars. Triple chrome plated. 4 sections extend to 57". 54" lead cable. Outside, one-man installation. Boost your profits with this King of new antennas. Order the Model TCF-4 Super "8" today!

watch

w

a

r

d

WARD
PRODUCTS
CORP.

1148 Euclid Avenue, Cleveland 15, Ohio
Division of The Gabriel Company
In Canada: Atlas Radio Corp., Ltd.,
50 Wingold Ave., Toronto, Ontario

WILL YOUR REPLACEMENT

Fuse Resistor BURN OUT AGAIN?

Another
Sencore
Time-Saver

Not if you use—
The NEW SENCORE
"FUSE-SAFE"
CIRCUIT TESTER

Save costly call backs by testing the circuit before replacing fuse, fuse resistor or circuit breaker.



Individual scale for each value fuse resistor — no interpretation, just read in red or green area.

★ Measures line current and up to 1100 watts of power at 115 volts using line cord and socket.

★ Two convenient current ranges — 0 to 2 amps and 0 to 10 amps. Test leads clip in place of fuse or fuse resistor.

★ 5 ohm, 10 watt resistor prevents TV circuit damage and simulates operating conditions.

As Recommended by Leading Manufacturers

SENCORE Mfg. by **SERVICE INSTRUMENTS CORP.**
171 OFFICIAL RD., ADDISON, ILL.

Cut out this ad now for further information



\$895 DEALER NET
MODEL FS-3
AC-DC, or both as needed for Fuse Resistor Circuits

Dave Rice's OFFICIAL ORDER BOOK for every TV-Radio service call

Triplicate forms serve as order form, invoice and office record with spaces for complete information on every job. Separate listings for receiving tubes, pix tube, parts, serial numbers, labor and tax charges, signatures, etc. 75c a book, \$6.50 for dust-proof box of 10.



... and for customer's prices on every replacement part, Dave Rice's

OFFICIAL PRICING DIGEST
listing over 60,000 items. \$2.50

In stock at your distributor, or write

ELECTRONIC PUBLISHING CO. INC.
180 North Wacker Drive Chicago 6, Illinois

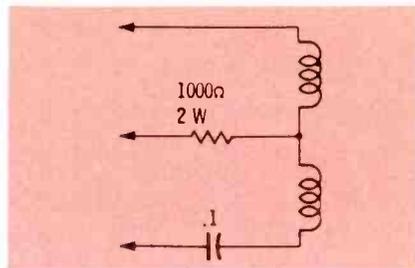


Fig. 4. Resistor used to prevent yoke ringing also provides DC current path.

its 2-watt power rating. The presence of ringing in the picture or a failure for the raster to center normally would indicate that this resistor may be defective.

The circuit shown in Fig. 5 is only the portion of the flyback transformer to which the width coil connects. The sharply resonant circuit of the .001 capacitor, width coil and transformer winding could generate spurious oscillations which might introduce ringing in the picture, overheating of the width coil or damage to the flyback. The 4.7K-ohm, 1-watt resistor acts as a damper by reducing the Q of the circuit, thereby limiting or eliminating the undesirable oscillations.

The resistors in Fig. 6 are usually incorporated in the high voltage circuit when a simple half-wave rectifier is employed. The 3.3-ohm unit will vary in value from less than one ohm up to 6 or 7 ohms depending on circuit requirements, and will either be of a special wirewound or composition construction. The primary purpose of this resistor is to limit rectifier filament current, but in so doing, it also reduces the load presented to the transformer by the filament circuit.

The first use needs no explanation, but since the latter may not be so universally understood, let's consider it for a moment. You can readily see that the total impedance of a single turn of large wire (such as the high voltage filament wire) and the

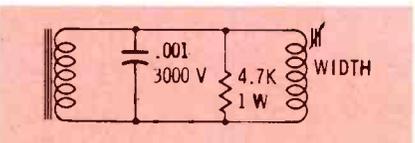


Fig. 5. Resistor across resonant width circuit serves to dampen oscillations.

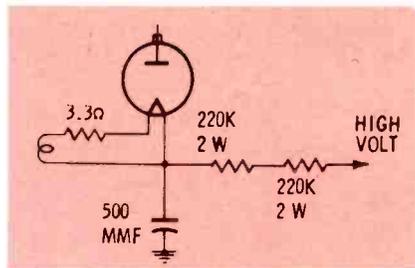


Fig. 6. Small-value resistor limits filament current, while those in anode lead are part of pi filter.

rectifier tube filament is extremely low, and the lower this impedance, the greater is the load it presents to the transformer. The addition of a small resistor increases the total impedance and reduces the load placed on the transformer. The net result is an increase of high voltage and a reduction of heat loss in the transformer.

This doesn't mean that you can add a resistor to a circuit not designed for it and improve or increase the high voltage, because in actual practice this will cause the rectifier to operate at too low a filament temperature and result in filament "suck out" and short tube life.

The 220K-ohm resistors in this same circuit may be of different values in other receivers, but the function will remain the same—serving as the resistive element in a pi-section RC filter (Fig. 7) where the second capacitor (not shown in Fig. 6) is the capacity between the inner and outer coatings of the picture tube. Resistors having ratings of from 1/2 to 2 watts will be found in this application; however, when replacing them, it is best to use a unit having as high a wattage as possible. Physical size should be the controlling factor and either a carbon or composition unit may be used.

Tuner and Control Cleaner

An idea developed by Injektorall Co. of Brooklyn, N. Y. is the needle-spray applicator incorporated with their tuner and control cleaner (see Fig. 8.). The applicator makes it possible to inject


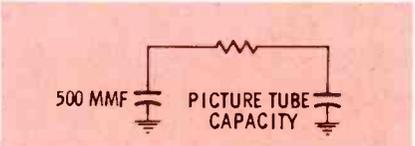


Fig. 7. Pi-network filter circuit.

Use Delco Radio Service Parts!

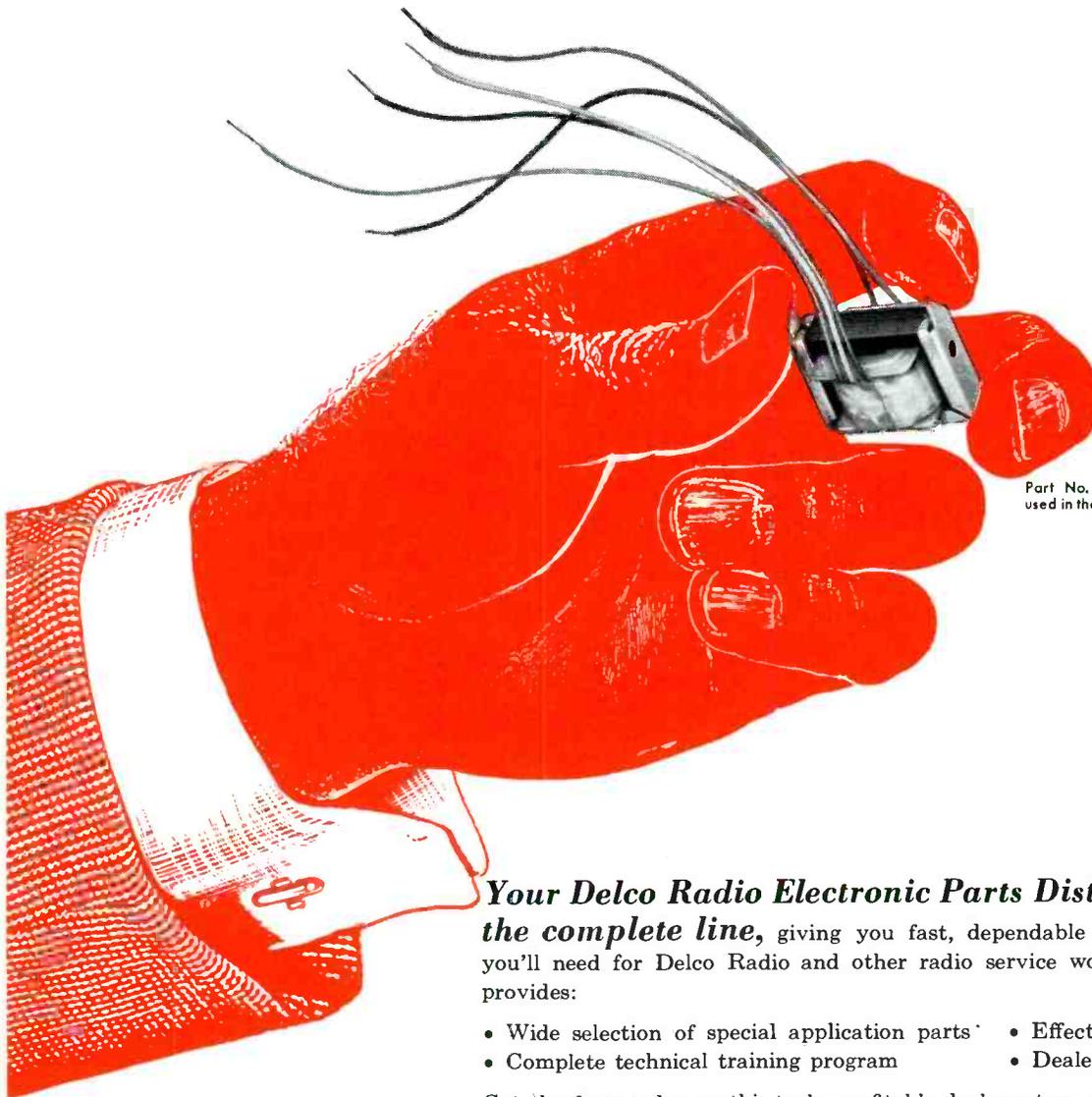

Part No. 7270804—output transformer used in the new Delco Portable Car Radio.

Your Delco Radio Electronic Parts Distributor carries the complete line, giving you fast, dependable service on the items you'll need for Delco Radio and other radio service work. Delco Radio also provides:

- Wide selection of special application parts
- Complete technical training program
- Effective warranty program
- Dealer identification signs

Get the facts today on this truly profitable dealer setup, and grow with General Motors!

Available everywhere through Electronic Distributors associated with . . .



DELCO RADIO

DIVISION OF GENERAL MOTORS, KOKOMO, INDIANA

<p>SPEAKERS</p>	<p>TUNER PARTS</p>	<p>TUBES</p>	<p>IRON CORES</p>
<p>TRANSISTORS</p>	<p>COILS</p>	<p>COILS</p>	<p>RESISTORS</p>
		<p>VIBRATORS</p>	<p>CAPACITORS</p>
			<p>CONTROLS</p>

the wax-free lubricant and cleaner into small and otherwise inaccessible areas and thus not only permits the technician to do a better job more quickly, but saves on the use of the fluid itself. Incidentally, actual trial uses of the fluid prove that it does a good job in eliminating noisy operation due to dirty tuner contacts or control elements.

Color CRT "Burn-In"

A recent Sylvania service manual gives the following warning on set-up and convergence pro-

cedures. "Caution: Before performing the set-up and convergence procedures on a new color receiver or a color receiver with a new picture tube, the receiver should be operated for at least four hours under normal station reception conditions to prevent burning the color lines or dots into the unaged phosphor of the picture tube."

Since a color bar pattern was recently burned into a receiver of another make during a troubleshooting procedure in our labs, it is our suggestion that this pre-

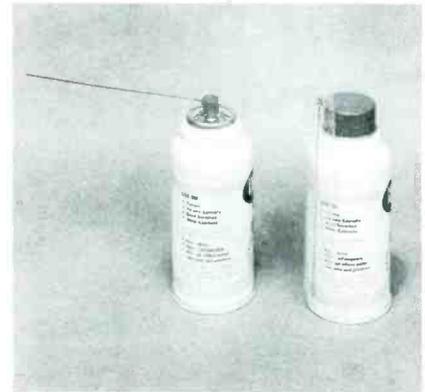


Fig. 8. Injectorall cleaner-lubricant.

caution be observed for all color receivers. In our own case, we found that the "burned-in" bar pattern could be erased by tuning in a station and adjusting the vertical hold control to produce a slow rolling of the picture. Several hours of operation cured the "burn-in" condition, but the preventive measure rather than the cure should be employed if possible.

Change in RCA Focus Circuit

The resistive element of the 200K-ohm focus control used in many RCA color chassis (Fig. 9.) may become charred or burned at the setting where best focus is obtained due to focus-rectifier current. To eliminate this condition, RCA specifies that a 56K-ohm, 1-watt resistor be installed between the variable arm of the control and the 1V2 plate. The leads in this resistor should be insulated with vinyl spaghetti and dressed away from all other components as much as possible. The RCA part number of the focus control in question is 102150 and the recommended replacement is 102150-B, the B indicating that the 56-ohm resistor is included. Make the addition of the resistor on the next service call and prevent subsequent focus-control failure.

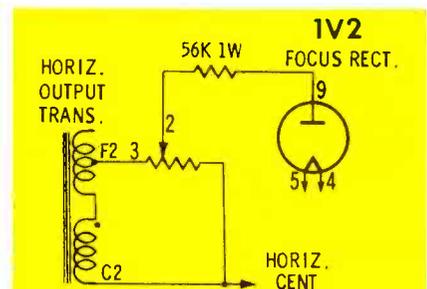


Fig. 9. Focus-circuit change in late-model RCA color television receivers.

ADDS INCOME 2 WAYS

1. Tests and Repairs Picture Tubes
(110° Tubes and Color Tubes too, with new C40 Adapter)

2. Makes New Tube Sales Easier

CATHODE REJUVENATOR TESTER

CRT 400 PROVES REAL MONEY-MAKER

Thousands of servicemen today make money and keep customer good-will by checking and correcting b&w picture tube troubles with the famous B&K CRT 400, right in the home without removing tube from set. Restores emission and brightness. Repairs inter-element shorts and open circuits. Checks leakage. Indicates picture quality customer can expect. Life Test checks gas content and predicts remaining useful life of picture tube. Makes new picture tube replacement sales easier!

Model 400 (without adapter) Net, \$59⁹⁵

NEW MODEL C40 ADAPTER DOUBLES VALUE OF B&K CRT

Designed for use with all B&K Models 400 and 350 CRT's. Makes it easy to test and rejuvenate TV color picture tubes and 110° picture tubes. Isolates and detects difficult color troubles. Tests and rejuvenates each gun of the color picture tube separately the same way as a black & white tube.

Model C40 Adapter Net, \$9⁹⁵

See your B&K distributor, or write for Bulletin AP10-R


New C40 Adapter for 110° Tubes and Color Tubes

Makers of CRT, DYNA-QUIK, DYNA-SCAN and CALIBRATOR

B & K


MANUFACTURING CO.
3726 N. Southport Ave. • Chicago 13, Illinois

**DU MONT
POSITIVE
QUALITY**

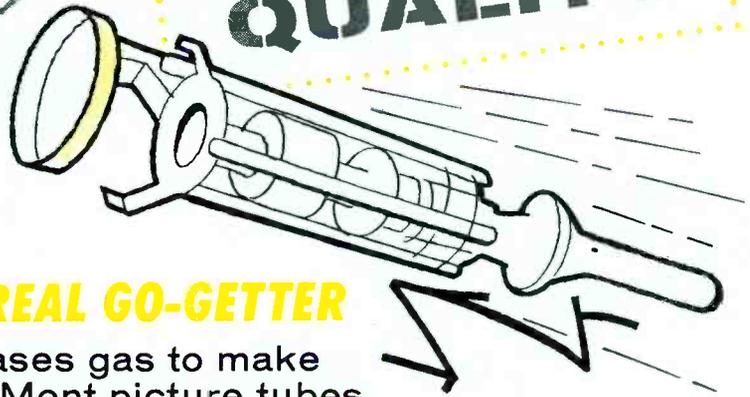

A REAL GO-GETTER

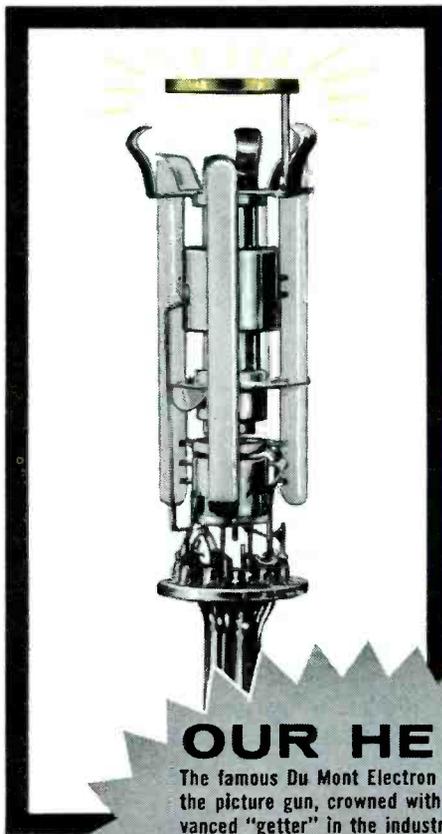Chases gas to make
Du Mont picture tubes
sharper and to assure
longer life



**400%
BETTER!***

Another positive fact about Du Mont positive quality . . .

Du Mont picture tubes are 400% better when it comes to gas, and the *less gas, the better* the tube.

A gassy picture tube produces a "soft" picture, lacking the snap and sparkle customers like. Furthermore, gas in a tube greatly reduces its life.


So, for the sake of your service and profits—make that next picture tube a Du Mont!

OUR HERO!

The famous Du Mont Electron Gun, heart of the picture gun, crowned with the most advanced "getter" in the industry. In the production of the tube, the "getter" is flashed to coat the inside of the envelope with materials that absorb gases in the tube. The Du Mont "getter" is unsurpassed for efficiency in this operation.

*Based on Quality Control figures

DU MONT[®]

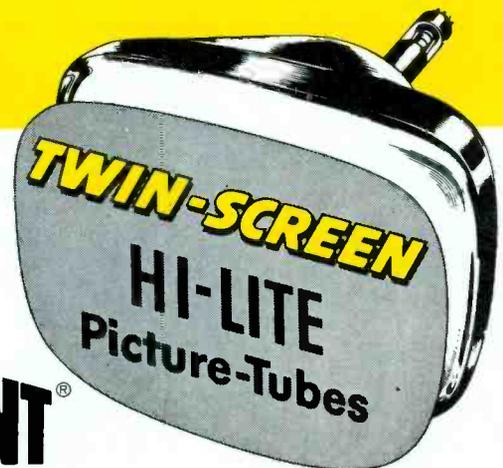

TELEVISION TUBE DIVISION, ALLEN B. DU MONT LABORATORIES, INC., CLIFTON, N. J.

When a Serviceman Needs a Friend



He naturally turns to Pyramid.

For in Pyramid twist-mount electrolytic capacitors he has the advantages of flexibility . . . where one TM type may be safely interchanged with others. The result? You save servicing time and give your customers faster service with a minimum investment.

Write today for Pyramid's new TM Interchangeability Guide and see how you can simplify repairs with Pyramid Twist-mounts.

And remember, a serviceman always has a friend in Pyramid, and his Pyramid distributor.

CAPACITORS—RECTIFIERS
FOR ORIGINAL EQUIPMENT—AND REPLACEMENT

PYRAMID
ELECTRIC COMPANY
North Bergen, New Jersey

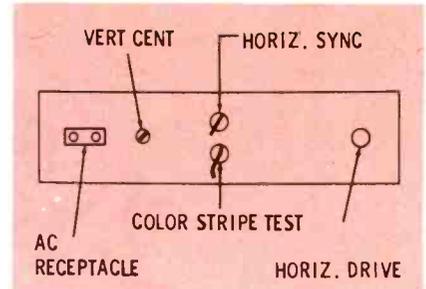


Fig. 10. Color-stripe test jack on rear panel of new Admiral color receivers.

Admiral Color-Stripe Test Jack

The test point (Fig. 10) on the rear of the Admiral 29Z1 series color chassis is provided so that color reception may be tested using the stripe signal transmitted during black and white broadcasts. This signal consists of a few cycles of 3.58 mc at burst phase and is added to the standard transmitted signal immediately before and after horizontal blanking. Since, in the receiver, a small amount of overscan is normally employed, the color stripes may not be visible during normal reception. As shown in Fig. 11, the color stripe test point is one end of a .001-mfd capacitor which is coupled to the sync inverter grid. Grounding the test point changes horizontal sync-pulse phase and causes the raster to shift to the left so that the color stripe on the right side of the picture will move into view. All conditions being normal, the stripe will be a greenish-yellow.

This test point eliminates the need for shifting horizontal centering to view the stripe—a most desirable feature since beam convergence changes with a change of centering. ▲

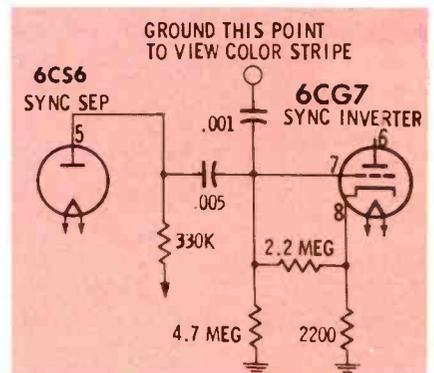


Fig. 11. Schematic of sync circuit showing circuit connection from test jack.

FREE! from **HOWARD W. SAMS...**

these valuable all-steel file cabinets with your purchase of **PHOTOFACT** *the world's finest TV-Radio Service Data*



NOW—FOR PHOTOFACT


SUBSCRIBERS! You can get these File Cabinets **ABSOLUTELY FREE** from Howard W. Sams if you are a regular subscriber to PHOTOFACT and buy each Set as issued monthly...

NOW—FOR PHOTOFACT LIBRARY PURCHASERS!

You can get **FREE** File Cabinets as you complete your PHOTOFACT Library. What's more, you can own the PHOTOFACT Library the **NEW EASY-BUY WAY:**

There's no interest. There's no carrying charge. And Howard W. Sams will give you **ABSOLUTELY FREE** all the steel file cabinets you'll need for your Library.

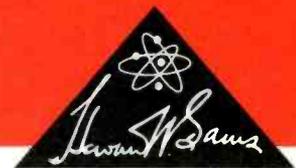Take advantage of this money-saving opportunity. See your Sams Distributor today, or write to Howard W. Sams for full details...



HOWARD W. SAMS & CO., INC.
2201 E. 46th St., Indianapolis 5, Indiana

Send me full details on your FREE File cabinet offer and EASY-BUY Plan.

I'm a Service Technician: full time; part time

My Distributor is: _____

Shop Name: _____

Attn.: _____

Address: _____

City _____ Zone _____ State _____



FREE file cabinets

NEW easy-buy plan

DO-IT-YOURSELFERS ARE SOLDERING NOW

**"Unusual Symptoms?—
Maybe your customer
owns a soldering gun."**

by G.M. Carrier

At one time or another, you've probably had do-it-yourselfers bring in sets with tubes missing, in the wrong sockets, etc. But, boy! This past week, I had it; not one but two—and they both owned soldering irons!

The symptoms on the first set seemed simple enough; the horizontal blanking bar appeared at the center of the screen—the left half of the picture was on the right side and the right half on the left side. The set was brought to the shop by the customer, who left after explaining that the picture could not be straightened out by adjustment of the usual controls.

I made the usual attempts, without success, to correct the trouble by adjustment of the service controls. I tried new tubes, of course, and after being satisfied that a little scope-snooping was called for, relegated the set to the "Ham Shack" for further study. Perhaps I'm peculiar, but I like this TV service work and often take the tough ones home to the basement workshop where the amateur radio station adds diversion in the evening hours. I "hang around" on 3910 kc, where the Indiana Fone Net meets, and breeze with the gang after net time for many happy hours.

The first evening with this

troubled TV found me devoting most of my attention to the sounds from the short wave receiver—only half consciously probing at the test points, reading scope patterns, etc., until it finally became obvious that this job was not going to be so easy. Everything seemed to check good, but the trouble still existed!

I listened less and less attentively to the banterings on the air, even began talking to myself a little, and when someone suddenly passed the frequency to me, I'm afraid I might have transmitted something like this, "This is . . . why doesn't that pattern stay steady? . . . W9PQZ . . . what is that slight oscillation? . . . Sorry gang, I'm afraid I wasn't listening . . . this thing should line up ok . . . Say fellows, sign me out. I've got an idea. W9PQZ clear."

Well, that idea didn't work, and neither did any other I could come up with. A glance at the clock sent me reluctantly off to bed with that divided picture night-marishly entering my dreams for the night.

The press of business kept my mind off that freakish set the ensuing day, but at dinner the wife sensed my impatience to fly off to the basement "shack." Normally I'm an easy-going guy and enjoy those evenings when fellow "hams" or would-be novices drop in through the convenient outside door to spend time with me in the shack. But I was probably a little curt when an unexpected license aspirant came bounding in with a cheery greeting. While I planned to devote all my attention to that 180° phase shift problem, I succumbed and turned on the rig, but carried almost no part of the conversation with the hams nor with my guest. I checked and re-

checked every portion of that circuitry, but the only thing I could find that was even a little off-base was the 6AL5 AFC detector. No bad parts could be found, and even substitutions made no changes in the symptoms. There was a slight oscillation of the voltmeter needle when measuring on the feedback side of the tube; but man, believe me, there were no bad parts in that TV set! Another wasted evening, another sleepless night, and my regular business found me growing tired and often flashing back mentally to that two-eyed monster in the basement.

We live in a typical small town, so it was not unusual that I should happen to meet the owner of this set on the town square. When he inquired as to the progress on his set, I could only confess that I was nowhere and that it looked as if the road ahead led to the same place. After paying him pleasant respects I started to hurry away, but his parting remark brought me back with a suddenness which to him must have been startling. "Did you say it has been like this ever since YOU replaced the high-voltage transformer? Is that what you said?"


"Yeah!" There was pride in his voice. "Everything worked swell right off the bat, all but for that darn line."

I gulped my food, skipped the coffee and sneaked down to the basement full of new hope, and as you may have guessed by now, I quickly traced out and corrected the customer's wiring job and had the set humming like a top. He had done a beautiful bit of workmanship, each joint faultlessly connected and carefully soldered, but the leads to the AFC coil had been reversed; hence the 180° phase shift.

The next evening found me, as usual, with another set that had been a little too much to finish during the day. This set had an


NEWEST
NEWEST
NEWEST

Jensen TRIAXIAL*

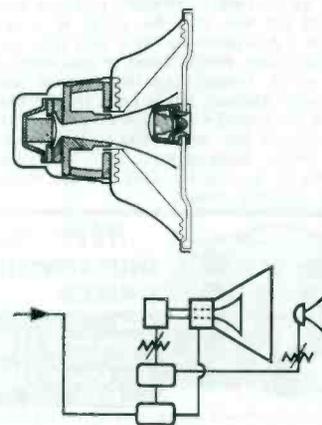

*Jensen's New True 3-Way
High Fidelity Loudspeaker
... With Superb Performance!
Only \$129.50*

Jensen, the only maker of true 3-way unitary loudspeakers (with 3 separate radiating systems, each independently driven), now brings you the G-600 TRIAX* at half the cost of the famous G-610A! Now you can enjoy the advantages of a true 3-way speaker . . . solid bass, full middles and smoothly extended highs out to the limits of audibility, with ultra low distortion, ultra high listening quality . . . at this new low cost.

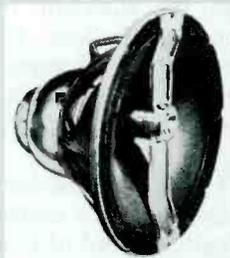

Lows from 30 to 900 cps are handled by the heavy duty 15" 3 1/2 lb. magnet edge-damped woofer. Midchannel is a compression driver horn-loaded thru-bore unit for 900-4,000 cps. New compression horn supertweeter with phase balancing covers the range from 4,000 cps to limits of audibility (very high indeed by our standards). Power rating is 35 watts. Separate network with MF and HF Controls is included. Write for free Catalog 165-B

THE FAMOUS TRIAXIAL...JENSEN G-610A. Easily rated the world's most wanted speaker, the G-610A is "tops" in a unitary 3-way speaker assembly. It has the advantages of higher efficiency, higher power rating (40 watts). Desirable very low first crossover of 600 cycles is achieved by using the entire woofer cone as the final section of the midchannel horn. Priced at \$252.75, complete with crossover network and controls.

*TRIAXIAL and TRIAX are registered trademarks of Jensen Mfg. Co.

In Canada: J. R. Longstaffe Co., Ltd., Toronto
In Mexico: Radios Y Television, S. A., Mexico D.F.

JENSEN MANUFACTURING COMPANY • Division of The Muter Company
5501 South Laramie Avenue, Chicago 38, Illinois

the specs are the proof . . .
the BEST BUYS are EICO
 for COLOR & Monochrome TV servicing



NEW COLOR
 and Monochrome
 DC to 5 MC LAB & TV
 5" OSCILLOSCOPE

= 460
 Factory-wired
 and tested \$129⁵⁰
 Also available as kit \$79⁹⁵

• Features DC Amplifiers!


Flat from DC-4.5 mc, usable to 10 mc. VERT. AMPL.: sens. 25 rms mv/in; input Z 3 megs; direct-coupled & push-pull thruout; K-follower coupling bet. stages; 4-step freq-compensated attenuator up to 1000:1. SWEEP: perfectly linear 10 cps-100 kc (ext. cap. for range to 1 cps); pre-set TV V & H positions (30 & 7875 cps); auto. sync. ampl. & lim. PLUS: direct or cap. coupling; bal. or unbal. inputs; edge-lit engraved lucite graph screen; dimmer; filter; bezel fits std photo equipt. High intensity trace CRT. 0.06 usec rise time. Push-pull hor. ampl., flat to 400 kc, sens. 0.6 rms mv/in. Built-in volt. calib. Z-axis mod. Sawtooth & 60 cps outputs. Astig. control. Retrace blanking. Phasing control.



NEW TV-FM
 SWEEP GENERATOR
 & MARKER

= 368
 Factory-wired
 and tested \$119⁹⁵
 Also available \$69⁹⁵
 as kit

Entirely electronic sweep circuit (no mechanical devices) with accurately-biased inductor for excellent linearity. Extremely flat RF output: new AGC circuit automatically adjusts osc. for max. output on each band with min. ampl. variations. Exceptional accuracy: edge-lit hairlines elim. parallax. Swept Osc. Range 3-216 mc in 5 fund. bands. Variable Marker Range 2-75 mc in 3 fund. bands; 60-225 mc on harmonic band. 4.5 mc Xtal Marker Osc., xtal supplied. Ext. Marker provision. Sweep Width 0-3 mc lowest max. deviation to 0-30 mc highest max. dev. 2-way blanking. Narrow range phasing. Attenuators: Marker Size, RF Fine, RF Coarse (4-step decade). Cables: output, 'scope horiz., 'scope vertical.

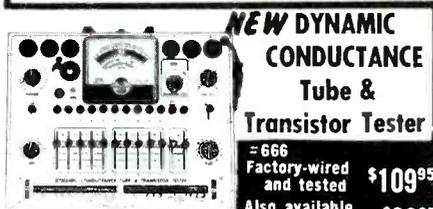

NEW DYNAMIC
 CONDUCTANCE
 Tube &
 Transistor Tester

= 666
 Factory-wired
 and tested \$109⁹⁵
 Also available \$69⁹⁵
 as kit

COMPLETE with steel cover and handle.

SPEED, ease, unexcelled accuracy and thoroughness. Tests all receiving tubes (and picture tubes with adapter). Composite indication of Gm, Gp & peak emission. Simultaneous sel of any 1 of 4 combinations of 3 plate voltages, 3 screen voltages, 3 ranges of continuously variable grid voltage (with 5% accurate pot). New series-string voltages: for 600, 450, 300 ma types. Sensitive 200 ua meter. 5 ranges meter sensitivity (1% shunts & 5% pot). 10 SIX-position lever switches: free-point connection of each tube pin. 10 pushbuttons: rapid insert of any tube element in leakage test circuit & speedy sel. of individual sections of multi-section tubes in merit tests. Direct-reading of inter-element leakage in ohms. New gear-driven rollchart. Checks n-p-n & p-n-p transistors: separate meter readings of collector leakage current & Beta using internal dc power supply. CRA Adapter \$4.50

See the 50 EICO models IN STOCK at your neighborhood distributor. Write for FREE Catalog PF-3

Prices 5% higher on West Coast

EICO BROOKLYN 11, N. Y.

interesting history. It was a split-chassis Philco. The customer came in carrying the sweep chassis and asked for a new 6BQ6 horizontal output tube, also informing me that the fuse was blown. I replaced the tube, which was obviously bad because the plate cap had been torn off, and bridged across the fuse with a snap-on double-ended fuse holder, casually remarking that I was putting in a 1.6-amp fuse. The customer was interested in the neat little device that bridges pigtail fuses, and volunteered that the fuse which had blown was actually a 2-amp fuse instead of the specified 1.6-amp rating. I thought very little of his comment at the time because I, too, have been guilty of going to the next highest fuse when necessary, especially out in the field where an exact replacement would require a round trip back to the shop.

Since he had not brought the picture tube, yoke, speaker with field-coil choke, and RF chassis, all I could do was take a quick look for obvious problems, and, seeing none, send him on his way. But he didn't stay away long. He returned soon with the whole set and announced that it had barely started to warm up when the fuse blew again. Being busy, I had him leave the set for further attention, and had already resolved to take this one to the shack for my evening's entertainment.

Another would-be novice dropped into the shack on this eventful evening. Since he was building a power supply on which he wanted some advice, I pushed aside the ailing TV, which by this time had already defied my systematic search for the short which was blowing fuses, and turned my attention to the novice's problems. He was trying for an ambitious voltage-doubler circuit, one well beyond his knowledge, and I was hard put to describe its principles and explain his errors. So I took him to the ailing Philco to show him how the selenium rectifiers and filter capacitors worked together to develop the AC input voltage to a higher usable DC value.

At the risk of losing another fuse (which I did), I fired up the set, intending to show him the 250 volts of output from the sec-

ond selenium. I placed the meter probe on the rectifier, fired up the set with the "suicide" cord, watched the needle climb to a sizzling 80 volts, and quickly fade to nothing as the fuse blew! Being a blow-hard know-it-all, I started to explain to him that whatever was shorting out and causing the fuse to blow was drawing such a large amount of current that the voltage was being affected drastically. But I knew I was wrong even as the words were rushing out! I had already used the ohmmeter enough to know that no such drastic short could possibly exist in this set. In fact, as I studied over what I had said to the poor unsuspecting chap, I realized that for the second set in a row, I was stuck by a do-it-yourselfer! I had already used the capacitor checker on the filters, had killed the horizontal oscillator and determined that it wasn't development of boosted B+ that was doing it and, in fact, after 3 hours on the set I was no further along than I had been at the beginning. In short, I was stuck!

With a shrug and a promise to get back to it the next night, I turned full attention to the problems of the would-be ham and suggested that he should not only make the corrections required in his power supply but should also provide fusing to protect his equipment. To demonstrate this principle of fusing, what could be better than to let him again examine the ailing Philco to note first hand how fusing should be installed and how a relatively inexpensive little fuse could save extensive damage. Thus, the Philco came in for study under the unpracticed eye of the novice (bless him). He, of course, had to follow the entrance of the house current into the filament transformer, through the fuse, to the selenium rectifiers and thence to the filters—but he couldn't get there. He said there was a "dead end!"

By now I was tired of looking at that Philco, and as a matter of fact, I was getting tired of looking at the novice too. Let's face it, I was just plain tired and wanted to go to bed, but my mother taught me to be a gentleman at all costs, so I propped open my eyelids and with a sigh of resigna-

the selection and use of

Hand Tools | part 2

by Calvin C. Young, Jr.

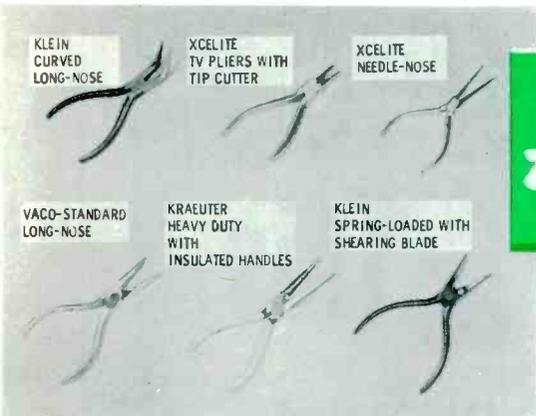


Fig. 1. Assorted wiring pliers for TV.

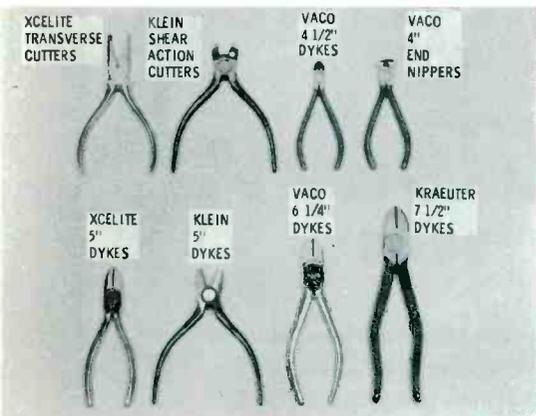


Fig. 2. Assorted styles, sizes of cutters.

The previous article on hand tools (January, 1958) dealt with the various hand drivers used in radio and TV servicing. This concluding installment covers the remainder of the common hand tools such as wiring pliers, cutters, adjustable wrenches, adjustable pliers, hex and spline wrenches, wire strippers, bolt cutters, wire and cable tackers, tube aids and miscellaneous tools.

Wiring Pliers

In the broad category of wiring pliers, we find everything from a standard long-nose plier to a special TV plier with a tip cutter. Let's have a look at each type and see how they differ in characteristics and usage. The standard long-nose plier is the most common type and, as shown at lower left in Fig. 1, may incorporate a cutting surface along its jaws. The long jaws that protrude from the pivot point are tapered to facilitate the making of connections in confined spaces and have serrations or teeth at the tip to provide a gripping surface.

Even though this tool can be used to grasp a nut or bolt hav-

ing a head size of $1\frac{3}{4}$ " or smaller, it is not designed for removing or installing bolts and nuts because the gripping surfaces of the jaws, when opened, are not parallel to each other, and are therefore, prone to slippage when used in this application. The only time a bolt or nut should be gripped with any wiring plier is when you are inserting the bolt in a recessed space or starting a nut on a bolt that cannot be reached with the fingers. Because of their slenderness, the jaws of long-nose pliers can be broken by the normal stress required to remove or tighten a nut or bolt.

Fig. 1 shows a number of variations in long-nose pliers, and each has a particular usefulness. The plier with insulated handles (lower center) is particularly designed for work involving heavy wire and large surfaces and is very useful in working on "hot" circuits (where utmost caution should always be observed).

The removable cutter blade on the spring-loaded pliers is easily replaced should it become nicked or dulled in usage. This cutter has a shearing action (like scissors) instead of the pinching action of most cutters, and may be used for both very soft and very hard wire as well as regular hookup types. The spring-loaded jaws open automatically when the handles are released so that they are always ready to grasp the next connection.

The curved-nose pliers shown at the upper left in Fig. 1 are very helpful in getting into corners and other places in which a straight plier cannot readily be used. The special plier developed especially for TV wiring (upper center in Fig. 1) features a gripping surface at its extreme tip (narrow tip on small slender jaws) and a cutter only $\frac{1}{4}$ " from the tip. This special construction makes much simpler the job of

connecting wire and component leads to terminals, tube-socket lugs and other confined spaces. The small tip cutter permits excess lead length to be removed after soldering, even in very compact units. The needle-nose pliers (upper right) are most useful when working with small wire in extremely confined spaces. Due to the long, tapered jaws, heavy wire should not be handled (bent or twisted) with these pliers. To do so will result in damage to the pliers.

Cutters

The most familiar wire cutters are the standard $6\frac{1}{4}$ " diagonal cutters commonly referred to as "dykes." The jaws of this cutter are small enough to fit into many places in a TV or radio chassis and large enough to cut the largest sizes of wire normally used in TV and radio work. This plier may also be used to cut the smaller sizes of guy wire if the extreme inner portion of the jaws is employed. However, this use, if extensive may make the "dykes" unsuitable for cutting copper wire.

There are a variety of other sizes and styles of cutters (Fig. 2) which are intended for use in the TV and radio service trades. The heavy $7\frac{1}{2}$ " type is just the thing for cutting larger sizes of copper wire and guy wire of the sizes normally used in antenna work. The plastic coating on the handles provides voltage insulation and also a very comfortable hand grip. The head of this cutter features heavy jaws and a large, heavy-duty pivot to prevent springing during the cutting action.


The smaller $5\frac{1}{2}$ " style with spring-loaded jaws features both a smaller handle and a smaller head than the standard $6\frac{1}{4}$ " size, and is suitable for cutting all copper wire, aluminum wire and copper braid used in TV and radio receivers. The spring-loaded

SOUNDLY ENGINEERED BY

CLAROSTAT


These new controls handle up to 4-watts audio and are small enough to fit standard electrical wall boxes. Ideal for remote control of speakers, in the home, office, stock-room, sound truck, or studio monitor speakers. All units have attenuation range of 0 to 30 db over 90% rotation and 60 db in remaining 10%. Insertion loss less than 0.5 db. **Miniaturized Sound System Controls.**

CIL43

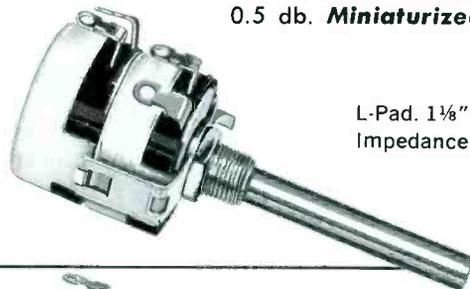


L-Pad. 1½" Diameter. 1½" depth from mounting surface. Impedance values from 4 ohm to 500 ohm.

CIT43

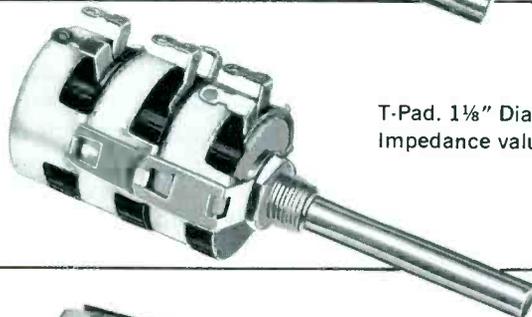

T-Pad. 1½" Diameter. 1¾" depth from mounting surface. Impedance values from 4 ohm to 500 ohm.

CIBT43

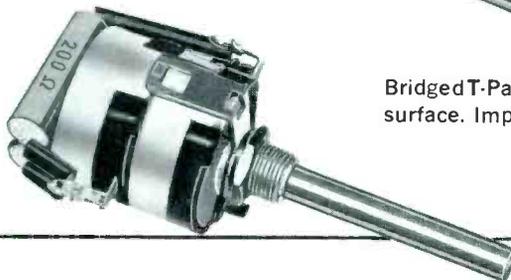

Bridged T-Pad. 1½" Diameter. 1½" depth from mounting surface. Impedance values from 4 ohm to 500 ohm.

Hardware Note: All shafts and bushings insulated from circuit elements. ⅜-32 x ⅜" long bushing. ¼" dia. shaft, round, 1½" long. Complete with bar knob and dial plates.



ASK YOUR CLAROSTAT DISTRIBUTOR FOR DETAILS




Controls and Resistors

CLAROSTAT MFG. CO., INC., DOVER, NEW HAMPSHIRE
In Canada: Canadian Marconi Co., Ltd., Toronto, Ontario

RADIO AND TV SERVICEMEN

make more money with this

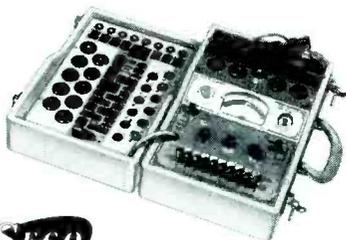

SECO

Model 107

TUBE TESTER

3 complete tests in one handy instrument

Here's the tube tester every serviceman has been asking for! Designed for outstanding performance and accuracy—provides 3 important tests: Dynamic Mutual Conductance Test of all popular radio and TV amplifier tubes—Cathode Emission Test for all tubes by free point selector system—nationally accepted Grid Circuit Test developed and patented by Seco. Saves you valuable time—quickly pays for itself by justifiably culling and selling more tubes for you!

Completely self-contained in compact portable carrying case. Furnished with handy flip-chart for fast, easy tube set-up data. **\$13950 net**

SECO

Write today for free literature
MANUFACTURING CO.
5015 Penn Ave. So., Mpls., Minn.

AT LAST!

Workman TV, Teaneck, N. J., an electronic parts manufacturer well known to the TV service industry as a source for many hard-to-find replacement parts, has now introduced a rather complete line of CANDOHM metal-clad wire wound resistors. These are exact replacement resistors for use in Admiral, CBS Columbia, Dumont, Emerson, G. E., Magnavox, Philco, R. C. A., Teletone, USL (Dewald), Warwick (Sears), Westinghouse and Zenith television receivers and for some equipment manufactured by Talk-A-Phone and Webcor.

Previously very difficult to procure, these CANDOHM resistors will very shortly be available at all leading electronic parts jobbers. They will be featured on an attractive rotating peg-board counter display. Each CANDOHM resistor is individually "skin packaged" and is clearly marked with all necessary information such as make of set, value of resistance, etc., for easy selection. Dealers may obtain copies of the #CS 40 replacement guide on CANDOHM resistors, free of charge, by writing to Workman TV, Inc. Box 85, Teaneck, N. J.

At last, Workman TV, Inc. has provided the service dealer with a single source for procuring CANDOHM resistors! Look for the display of Workman CANDOHM resistors at your favorite jobber.

feature makes cutting jobs easier since the cutters will automatically open when the handle is released. The smaller, thinner jaws and smaller pivot point make this cutter a poor bet for antenna work, but these same features make it excellent for TV bench use.

The 4 $\frac{1}{4}$ " design features both a very small, narrow head and closely-matched cutting surfaces. Cutters of this size are meant only for use on small size hookup wire and component leads. Using them to cut anything larger or harder will cause damage to the jaws or the pivot.

The 5 $\frac{1}{2}$ " unit has a replaceable blade which operates on a shearing action to cut extremely soft or hard wires and also features spring-loaded jaws. Even though the cutter blade is replaceable if it becomes dulled,

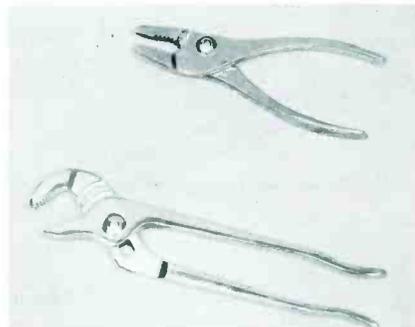


Fig. 3. Slip-joint and adjustable pliers.

wire of too large a size should not be cut since this could loosen the pivot and ruin the pliers. They will cut standard guy wire and aluminum ground wire with equal ease.

The small-size 4" end nippers and 5 $\frac{1}{2}$ " transverse cutters are most valuable for working on printed wiring boards. The transverse cutters with their longer, slimmer jaws will reach into confined spaces for flush cut-off of wires and component leads, while the end cutters with heavier and wider jaws will permit cutting old terminals from filter capacitors, potentiometers, etc. Larger end cutters, 5 $\frac{1}{2}$ " and 7 $\frac{1}{2}$ ", are also available for heavier-duty flush cut-off work.

Adjustable and Slip-Joint Pliers

These tools (Fig. 3) are probably the most misused of any ever invented. Turn the average

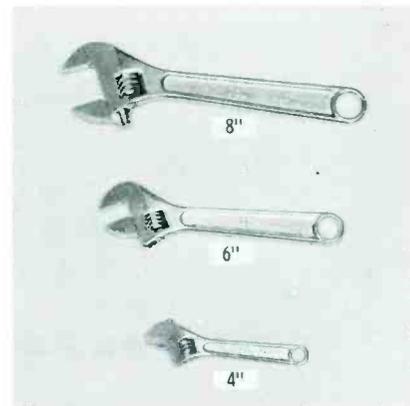


Fig. 4. Adjustable (Crescent) wrenches.

man loose with a pair of pliers and he will "goof up" every bolt and nut in sight. Pliers have a very useful place in the service kit, providing they are correctly employed.

Both the slip-joint and the adjustable plier are intended for use in holding irregularly-shaped objects for which no wrench is available. They are designed with machined teeth that bite into the object being held—a necessity if the object is to be held firmly. This causes a certain amount of marring to the surface of the object; therefore, a good rule to follow is never to use pliers if the resultant damage to the object will interfere with its subsequent use or appearance.

If you find it necessary to employ a pair of pliers to remove a bolt or nut, grip the head of the bolt with the pliers and then remove the nut with a wrench. If a bolt or nut does become damaged

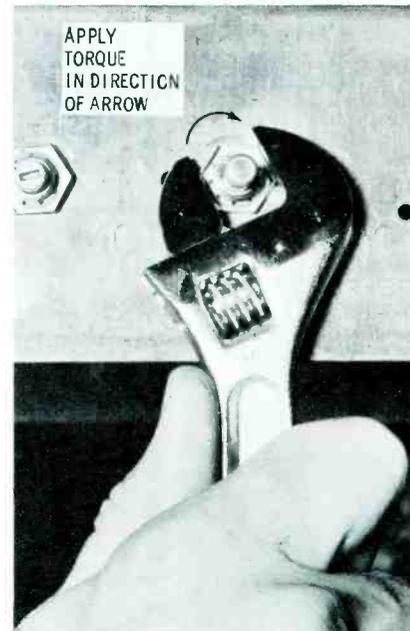


Fig. 5. Using adjustable wrench correctly.

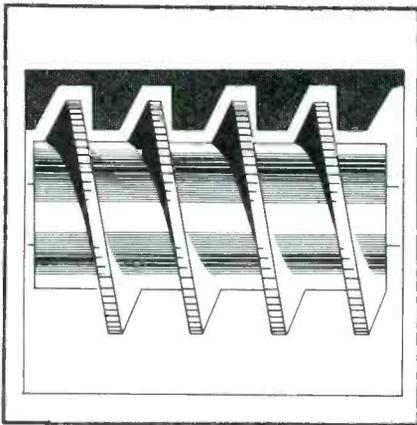


Fig. 6. Clearance between gear teeth and adjusting wheel on adjustable wrench.

in the process, replace it rather than have chewed-up screw heads class you as a novice or sloppy workman.

Adjustable Wrenches

The 4", 6" and 8" versions (Fig. 4) have jaw openings of $\frac{1}{2}$ ", $\frac{7}{8}$ " and 1" respectively, and are a very handy assortment of tools to have on hand. A word here—just because these tools offer extreme versatility in the sizes of their jaw openings, don't depend on them for your entire wrench requirements, since they do have certain limitations. The adjustable wrench is not as strong as a one-piece wrench, and should not be used to tighten or loosen bolts or nuts under high torque levels. It is far better to use them as they were intended—as a second wrench or to fit bolts and nuts of sizes not commonly encountered in your work.

In order to provide a reasonable measure of strength, and at the same time be adjustable, these wrenches have rather large heads for their span; this precludes them from use in confined areas. In line

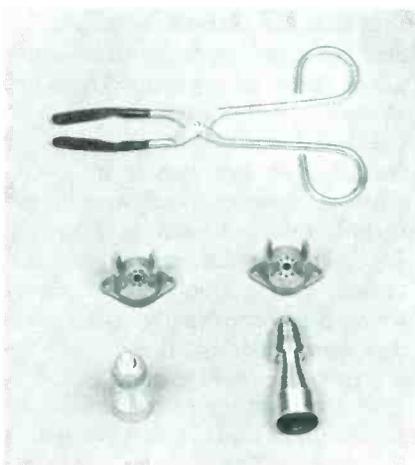


Fig. 7. General-Cement tube aids.

CORNELL-DUBILIER VIBRATORS



Built to last... a type for every radio

The C-D brand name on a vibrator is your guarantee of dependable performance, long trouble-free service. Because C-D vibrators are built to last, you can use them with full confidence. That's why it pays to reach for a C-D when a replacement is called for.

Remember, too, that there's a C-D vibrator type for every make and model car on the road. And the C-D VIBRATOR REPLACEMENT GUIDE makes it quick and easy for you to select the exact type required. Ask your local C-D distributor for a free copy of VIB-3, or write to Cornell-Dubilier Electric Corp., South Plainfield, N. J. Dept. PR 38



CORNELL-DUBILIER VIBRATORS

Old Hands at Dependability

NAME THIS C-D-R ROTOR



Name the great new CDR TR-16 Rotor

Your name can win the Plymouth Station Wagon

Here Are the Features to Help You Pick a Name

- Entirely new with features never before available in the popular price range.
- Quick-mounting mast collet permits speedy installation (no loose parts to assemble).
- Self-centering sawtooth clamps take masts up to 1½" in diameter.
- Instant locking prevents drift.
- Mechanical brake releases magnetically.
- Direction of rotation is instantly reversible.
- Rotor makes complete 360° revolution in 45 seconds.
- Completely weather-sealed, rotor meets rigid MIL salt water test.
- Fits standard towers.
- Streamlined to reduce wind resistance.
- Streamlined control box, non-breakable, impact-resistant case. *Better still visit your jobber today and try it.*

CORNELL-DUBILIER ELECTRIC CORP.
South Plainfield, New Jersey

THE RADIART CORPORATION
Indianapolis, Indiana



CDR Antenna Rotors

Old Hands at Dependability

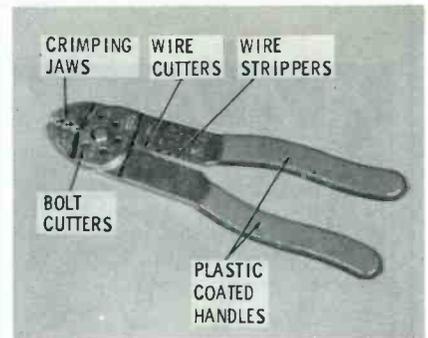


Fig. 8. Combination bolt cutter, terminal crimper, wire stripper and cutter.

with the inherent strength of the adjustable wrench, it is weakest when opened to its maximum limit. Furthermore, there is a right and a wrong way to apply torque with an adjustable wrench. Fig. 5 illustrates the correct way. The force on the movable jaw should always be into the head, not away from it. This places minimum strain on the wrench and prevents springing of the movable jaw.

If you closely examine an adjustable wrench, you will see that there is a certain amount of play between the fixed and movable jaws. This is due to normal clearance between the gear teeth on the movable jaw and the threads on the adjusting wheel (see Fig. 6). For this reason, always tighten the wrench to take up all the slack after slipping it around the bolt head or nut.

Miscellaneous Tools

In this group are such tools as tube pullers, slug retrievers, plastic hammer, bolt cutters, wire strippers, tube-pin straighteners, plus hex and spline wrenches. These are items the technician is sure to need periodically.

In Fig. 7 we have pictured tools that can be classed as tube aids, and for brevity we will consider all of these as a group. The miniature tube-pin straighteners are constructed so that they can be fastened to the bench in a convenient location and are of different colors (9-pin is blue and 7-pin is red) for ease in identification. Since the pins of miniature tubes can easily (and often do) become bent, these tools are a must for every shop.

The miniature tube pullers are available in both 7- and 9-pin sizes as shown. The rubber insert in each unit grips the tube and per-



Fig. 9. Arrow tacker Model T 50.

mits it to be extracted. Pushing on the top plunger causes a plastic cap to press down on the tube and free it from the puller. The plastic cap is hollowed out to clear the glass nipple on top of the tube.

The long tongs are most useful in removing either octal-based tubes that have become too hot to handle, or any tube located in such a way that tube removal and subsequent reinstallation would be almost impossible without a tube-handling device of this type.

The combination solderless-terminal connector, bolt cutter, wire stripper and wire cutter (Fig. 8) is a handy tool for any service shop. When used with a supply of assorted solderless terminals, antenna installations and the replacement of lead wire on indoor-type antennas is a breeze. The bolt-cutter feature is a real time saver. You've undoubtedly experienced the need for a 1/4" or 1/2" bolt and could find none shorter than 3". With this handy tool, you


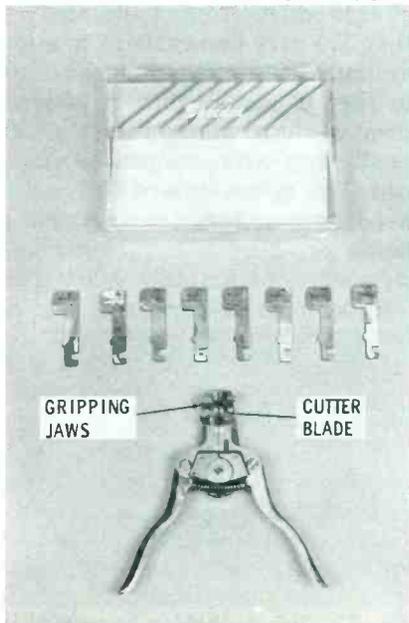


Fig. 10. Speedex wire stripper kit.

WIN THIS PLYMOUTH STATION WAGON

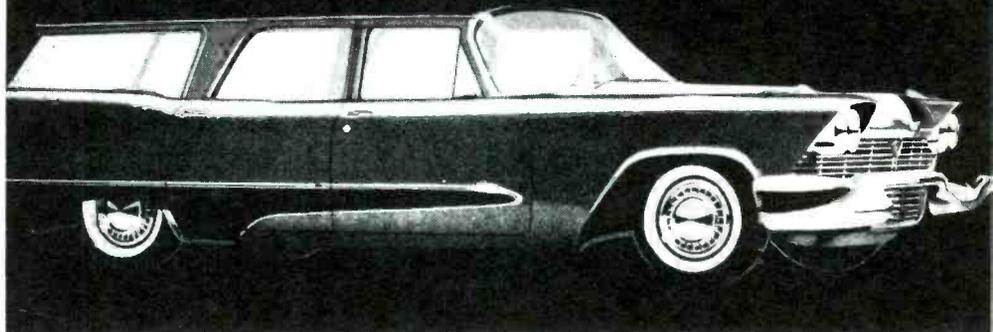

The name you pick may win

this beautiful 1958 Plymouth Station Wagon

Here's all you do... There's not a thing to buy. Just visit your local CDR Distributor and look over the new TR-16 Rotor — then ask the Counter Man for an Official Entry Blank. Select a name, fill in the blank and mail... that's all there is to it!

This contest is open to any person over 21 years of age, and residing in the continental U. S. Officers, employees and members of the sponsoring organization and advertising agency are not eligible. Contest is subject to Federal, State and local regulations.

No entries will be returned, and the decisions of the Judges will be final. Contest closes April 30, 1958.

CORNELL-DUBILIER ELECTRIC CORP. THE RADIART CORPORATION
South Plainfield, New Jersey Indianapolis, Indiana




CDR

Antenna Rotors

Old Hands at Dependability

www.americanradiohistory.com


25 WORDS

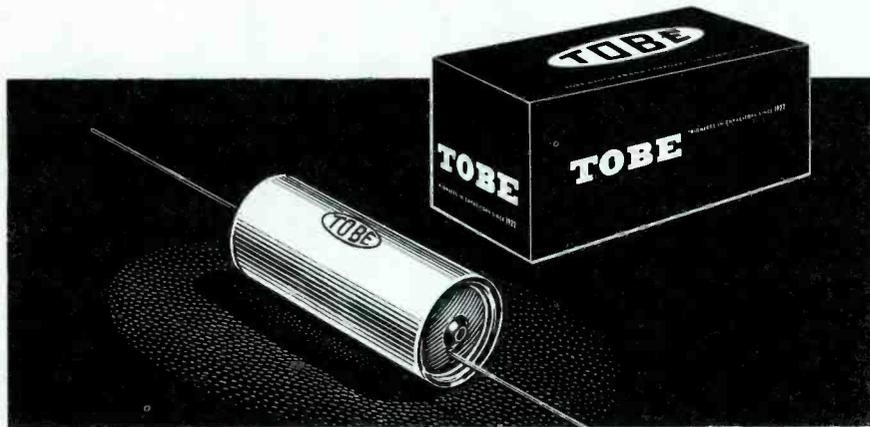

Tell Why You Like Tobe Service Capacitors

Your 25 words can win the Ford Ranch Wagon

And Here Are the TSC* Features to Help You Win • No substandard materials can possibly enter the manufacture of TOBE SERVICE CAPACITORS, because *everything* is quality-checked beforehand • Highest grade dielectric materials prevent voltage breakdown in service • TSC's are designed for high-temperature operation — will not dry out or deteriorate in service • Copperweld leads soldered directly to foil insure you against opens • Moisture-tight seals guard against shorts • Pigtail leads will not pull out or break off • No danger of hot soldering iron opening internal connection or melting sealing compound • TSC's will maintain specified capacity over entire operating temperature range • TSC's receive 100% quality-control inspection prior to shipment • Continuous production-line testing automatically rejects "duds" • Maintenance of large inventories on complete line means faster delivery to your TOBE DISTRIBUTOR and you.

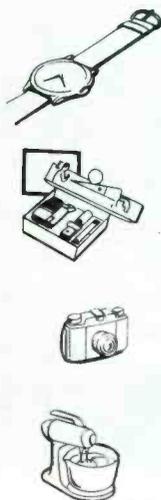

*Tobe Service Capacitors



HERE'S YOUR ENTRY BLANK

Tobe Deutschmann Corporation, Dept. C
2900 Columbia Avenue, Indianapolis 5, Indiana

"I prefer Tobe Service Capacitors in my work because _____

NAME _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____

I enclose a Tobe boxtop

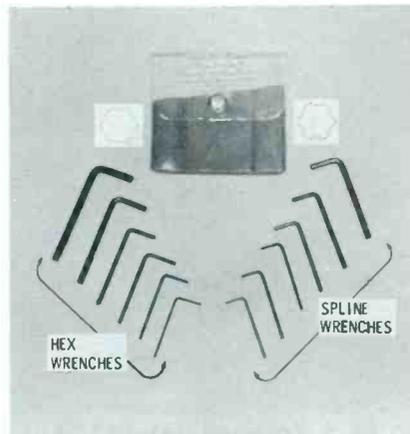


Fig. 11. Assortment of hex and spline wrenches most often needed.

just screw the bolt into the correct hole (10-32, 10-24, 8-32, 6-32 and 4-40 can be cut) and cut it to the desired length, allowing approximately $\frac{1}{8}$ " for the thickness of the top cutter blade. Unscrewing the shortened bolt from the cutter readies it for use—no filing or honing of the bolt is necessary.

The hand tacker shown in Fig. 9 is a heavy-duty stapler which uses 50-gauge wire staples in lengths of $\frac{1}{4}$ ", $\frac{5}{16}$ ", $\frac{3}{8}$ ", $\frac{1}{2}$ " and $\frac{9}{16}$ ". This unit is handy for such jobs as securing acoustic insulation to hi-fi speaker cabinets, fastening speaker and intercom wire or cable to wooden beams and stapling heavy cardboard window displays together. Another excellent use (and one that should be considered much more often than it is) is the restapling of interconnecting cables on the insides of cabinets.

Wire strippers are often thought of as production-line tools, and yet they are very handy items to have around the service shop. The kit in Fig. 10 comes with an assortment of cutter blades so that practically any wire size can be stripped. This is the type of tool you'll need on that P.A. installation, or when rewiring a complete chassis section or building a kit. The wire stripper features two sets of

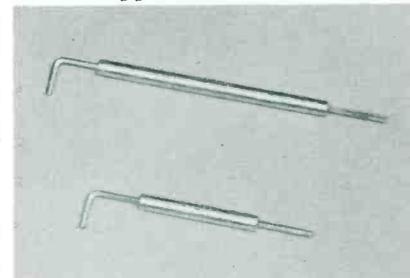


Fig. 12. Stevens-Walden screw-holding hex (Allen) wrenches.

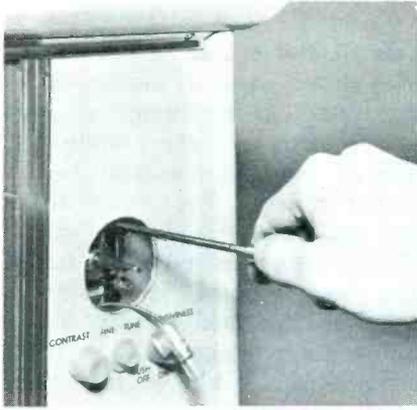


Fig. 13. Hunter slug retriever in use.

jaws—one set to grip and hold the wire and the other to cut and strip the insulation away. The cutter jaws are removable, and 9 sets of cutter blades are supplied, expanding the usage to 24 sizes of wire including twin-lead conductors of both small and large diameter.

The hex and spline wrenches in Fig. 11 are most often required in the servicing of record changers, tape recorders and any number of small electrical appliances. While not needed as often as some of the other tools, nothing will take the place of a hex or spline wrench, so it's a good idea to be prepared and always have them on hand.

The screw-holding units in Fig. 12 feature one split end which spreads by spring action to grip an Allen screw and permit its easy installation. The 90° end may then be used to tighten the screw to the desired torque.

Have you ever, in the course of adjusting the local oscillator slugs in a turrent tuner, turned the slug too far and had to pull the chassis to retrieve it? If you have, then you know the value of the retriever tool being used in Fig. 13. This tool can save up to 15 or 20 minutes every time a slug is accidentally screwed in too far.

Summary

While this two-part series hasn't covered all of the possible hand tools a technician might employ in his daily work, we have dealt with those most often used. Employing your tools skillfully will not only save you time and energy, but will also impress your customers with your craftsmanship, as well as increasing word-of-mouth advertising to your benefit. ▲

WIN THIS FORD



RANCH WAGON

Or one of 49 other valuable prizes



Here's all you do . . . In 25 words or less, tell us why you prefer TOBE SERVICE CAPACITORS.

Then, send your entry to us with the top from any TOBE capacitor carton, or the plastic box some TOBE capacitors are packed in.

That's all there is to it. Enter as many times as you wish, providing each entry is accompanied by a TOBE carton top or the plastic box. Use entry blank below. Additional entry blanks can be obtained from your TOBE DISTRIBUTOR.

Contest Closes May 30

Contest is open to all service-men over 21 years of age residing in the continental United States. Employees of the TOBE DEUTSCHMANN CORPORATION and their advertising agency are excluded. All entries become the property of TOBE DEUTSCHMANN CORPORATION. Decisions of the judges are final. In case of ties, duplicate prizes will be awarded. Contest closes May 30, 1958. Winners will be announced June 30th.



HERE'S YOUR ENTRY BLANK



TOBE RADIART
CAPACITORS

Tobe Deutschmann Corporation, Dept. C
2900 Columbia Avenue, Indianapolis 5, Indiana

"I prefer Tobe Service Capacitors in my work because _____

NAME _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____

I enclose a Tobe bortop

Notes On

TEST EQUIPMENT

Latest Information on Application,
Maintenance and Adaptability
of Service Instruments

by Leslie D. Deane

Checking RF Response

Since the alignment procedure for TV tuners is often omitted in service information, many TV service technicians ask the question: "How do I set up my generator and scope to check the RF response of a tuner?" Here then, are a few basic instructions and hints for setting up equipment to perform this particular operation.

The arrangement in Fig. 1 will serve for most practical applications of this type. In this setup, the sweep generator is connected to the receiver antenna terminals through a simple resistive matching network. Matching and termination of the output cable is usually necessary to obtain a

maximum generator output and to prevent the development of interfering standing waves. The network is designed to present an input impedance that matches the characteristic impedance of the output cable (50 to 100 ohms), and to present an output impedance that matches the input of the receiver (75 ohms unbalanced or 300 ohms balanced).

The center frequency of the sweep generator should be set midway between the video and sound RF carriers of the channel selected. The sweep width should be adjusted for approximately 10 mc, and the sweep modulation voltage applied to the horizontal input terminals of the scope for a synchronized sweep.

From the vertical input terminals of the scope, the *hot* lead of a direct cable is connected to the tuner "looker point" through a 10K-ohm resistor, while the ground lead is attached to receiver chassis. The series resistor can be eliminated if one is already incorporated in the tuner. The "looker point" is usually located in the grid circuit of the tuner-mixer stage and is often terminated on top of the tuner housing.

It is often desirable to clamp the tuner AGC at approximately 1.5 volts negative. This can be accomplished by using a battery or special bias supply, connecting the positive terminal to chassis ground and the negative terminal to the AGC line at the tuner input. If a response curve of sufficient amplitude cannot be obtained, however, the negative supply should then be removed and the tuner AGC point grounded to chassis.

To obtain a usable response curve, especially on the higher channels, it may be necessary to operate the generator at maximum output and the scope at maximum gain. Once the curve is established on the scope screen, the frequency response can be checked by injecting video and sound carrier marker signals. A separate generator should be employed if the sweep generator has no marker output of its own. The signal from the marker generator can be applied (or loosely coupled) to the sweep output through a small series capacitor or by merely laying the marker output cable across the matching network to the antenna terminals.

4-in-1 Capacitor Analyzer

Sprague Products Co., North Adams, Mass., has recently introduced their Model TO-5 "Tel-Ohmike" Capacitor Analyzer, designed especially for measuring capacitance, power factor, leakage, and insulation resistance of capacitors. In addition, the instrument (Fig. 2) will also check the turns-ratio of certain iron-core transformers.

Specifications and test features are:



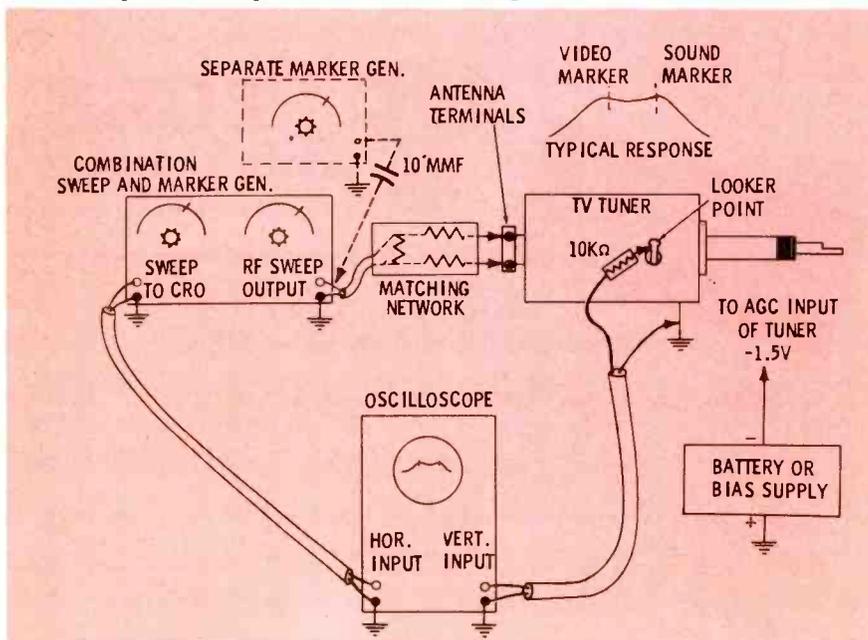


Fig. 1. Diagram of instrument setup for RF response check of TV tuner.

the mighty nine plus two!

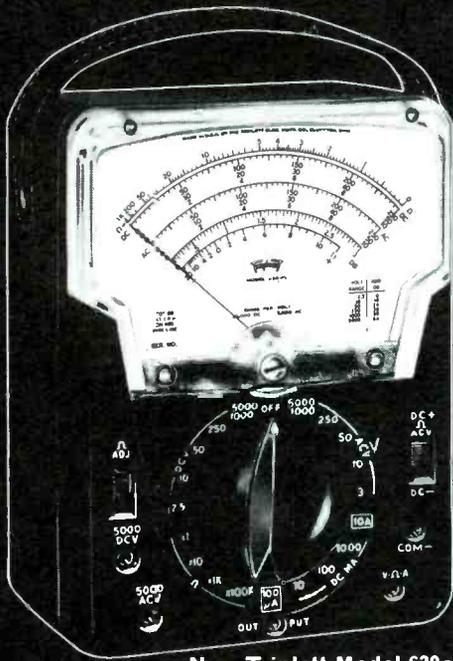

New Triplet Model 630-PL

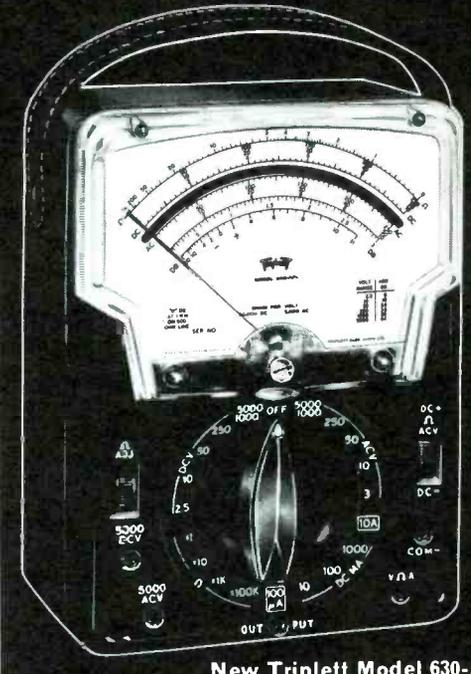

New Triplet Model 630-APL

TWO NEW VOLT-OHM-MILLIAMMETERS

Now the Triplet Mighty Nine Has Expanded to A Line of 11 VOMs Tailored to Meet Your Preference, Purse or Purpose. Only Triplet Offers So Complete A Variety.

With the new 630-PL and 630-APL you get these important new features:

- Voltage scales for those who want ranges reading by 10's (2.5-10-50-250-1000-5000).
- Instant-vision, wider spread scales; streamlined case, handsome modern design.

- D.C. Polarity Reversing Switch.
- 5 to 500,000 Cycles per second frequency response in A.C. measurements.
- 5000 ohms per volt sensitivity in A.C. ranges; 20,000 ohms per volt D.C.

Both new testers — with the popular continued Models 630 and 630-A—offer these proved Triplet advantages:

- One switch will select any range; minimizes chance of incorrect settings and burnouts.

- Reads from .1 ohm (4.4 ohm center scale) to 100 megohms; four ranges.

- Molded circuit panel for instant component replacement.
- Models 630-APL and 630-A feature 1/2% resistors for greater accuracy; long mirrored scales to eliminate parallax in reading.
- Banana-type leads for low contact resistance at jacks.

how do you want it?

X 3s or X 10s

Triplet Models 630 and 630-A read volts 0-3-12-60-300-1200-6000); or Triplet New Models 630-PL and 630-APL reading 2.5-10-50-250-1000-5000.

Choose your preference in range reading.

MODEL 630-PL... Dealer Net \$44.50
 MODEL 630-APL... Dealer Net \$54.50
 MODEL 630... Dealer Net \$44.50
 MODEL 630-A... Dealer Net \$54.50

Only Triplet offers 11 VOM's—a line complete enough to give you exactly what you want.




Triplet Electrical Instrument Co.
Bluffton, Ohio

53 Years of Experience




Triplet Model 630

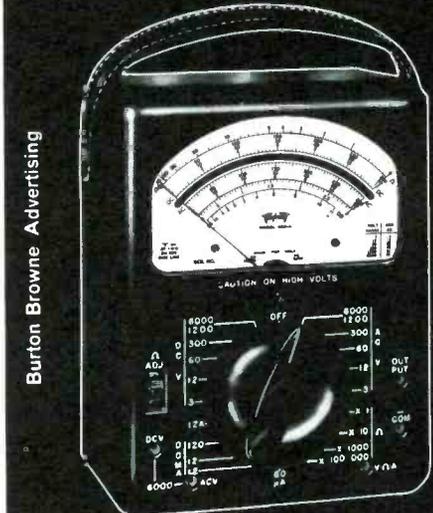

Triplet Model 630-A

Burton Browne Advertising

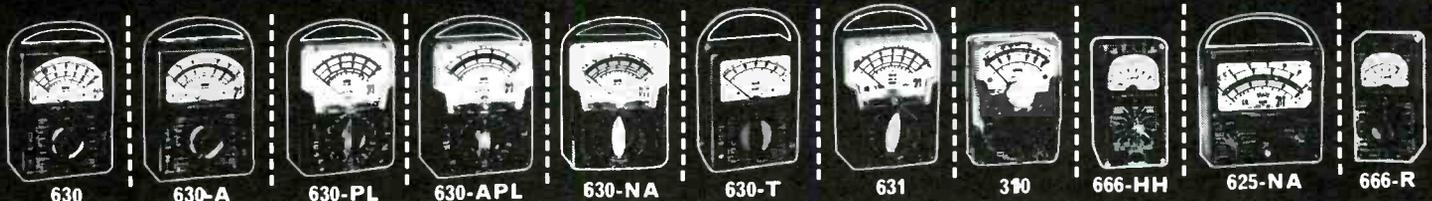



**faster...easier
more efficient**



KRYLON Crystal-Clear Acrylic Spray Coating

... standard equipment for TV and radio servicemen.

- Prevents corona in high voltage section
- Keeps lead-in connections tight
- Prevents rusting and pitting of antenna
- Goes on in seconds—dries in minutes



KRYLON Spray Enamels

(19 decorator colors) ... perfect for touchup and maintenance work ... covers practically any surface ... dries in minutes.



KRYLON Varnish Sprays

... HIGH-GLOSS and SATIN-FINISH (alcohol and hot liquid resistant) for professional finish ... dries in minutes.



KRYLON Dulling Spray

... a "must" in TV, movie and photographic studios.

- Eliminates glare, bothersome high-lights
- Simplifies lighting arrangements
- Easy to apply ... sets in seconds
- For both black and white and color use



KRYLON Foaming Window Spray

... removes finger marks and dust from TV masks and screens ... good antistatic properties.



KRYLON Rust Release Penetrating Oil Spray

... instantly, easily frees rusty bolts and nuts and "frozen" parts ... lubricates as it penetrates.



The choice of professionals
Call your jobber or write
KRYLON, INC., NORRISTOWN, PA.

1. *Power Requirements*—115 volts, 50/60-cycle AC, power consumption 35 watts.
2. *Capacitance*—5 ranges from 1 mmf to 2,000 mfd, special low range for values from 1 mmf to 100 mmf to obtain greater accuracy, push-button selection and automatic discharging features included.
3. *Power Factor*—3 ranges provided—0 to 20, 20 to 40, and 40 to 55; direct-reading scale for all electrolytics.
4. *Electrolytic Leakage*—adjustable DC supply permits measurement at exact rated voltage up to 600 volts, monitored by panel meter on either a 6- or 60-ma range, normal leakage values provided in manual.
5. *Insulation Resistance*—panel meter provides 2 scales for direct measurement of from 100 to 20,000 megohms; checks paper, mica, and ceramic capacitors for leakage with average minimum value given in manual.
6. *Turns Ratio*—2 ranges for ratios of from 1:1 to 100:1 and for impedance ratios of from 1:1 to 10K:1, three test leads provided.
7. *Size and Weight*—8⁷/₈" × 14⁵/₈" × 6¹/₈", 12¹/₂ lbs. net.

Reading over the instruction manual accompanying the TO-5, and boiling down some of the unit's specifications, I found that not only will the piece of equipment measure capacities of electrolytics and small ceramics from 1 mmf up to 2,000 mfd, but even molded gimmick capacitors. Other noteworthy features include an electrolytic leakage test at rated working voltages, an automatic capacitor-discharge arrangement after each test, and a provision for measuring turns-ratio of power and audio-type transformers. A complete operating procedure for all measurements is given in the TO-5 manual.

One application for which I used this new analyzer involved a TV receiver, a 100-watt light bulb, and a Christmas-tree effect. Realizing that technicians are always interested in new and different troubleshooting procedures, I thought I might relate this particular experience.

A two-year old TV chassis which we often use in our test

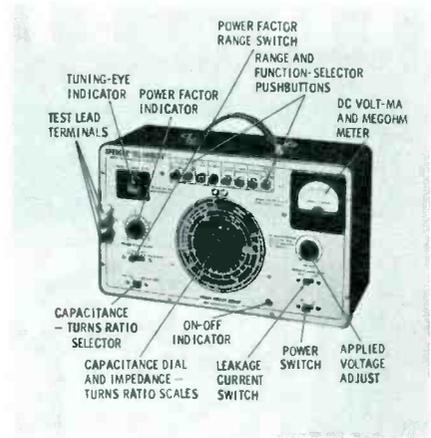


Fig. 2. The Model TO-5, "Tel-Ohmike"—Sprague's latest capacitor analyzer.

lab started developing a Christmas-tree trouble whenever it was left operating for any length of time. This horizontal instability was somewhat intermittent and its cause rather difficult to pin down.

Having a strong suspicion that one of the capacitors in the oscillator circuit was changing value as it heated, I decided to make a hot and cold check of certain ones with the Model TO-5. I planned to remove each capacitor from the circuit and measure its value while it was relatively cool—then apply heat, using a 100-watt bulb from a bench lamp, and measure it again. In this manner, I thought I might detect any unusual capacitance drift. Well, as it turned out, I failed to notice any change in the first two attempts, which involved molded mica units. In my third try, however, I struck pay dirt.

Removing an .01 paper tubular from the horizontal oscillator circuit and placing it directly across the positive and negative test terminals of the TO-5, I first measured its capacitance cold. I depressed the range pushbutton "B," rotated the capacitance dial until I reached the widest tuning-eye opening, and then noted the value indicated under the hairline on the dial scale marked "C3." The unit measured exactly .011, which was well within its fixed manufacturing tolerance of 20%.

Disconnecting the capacitor from the analyzer and placing it under the lit bench lamp until I was sure it was at least as warm as it would ever get under normal operating conditions, I again connected it across the test terminals

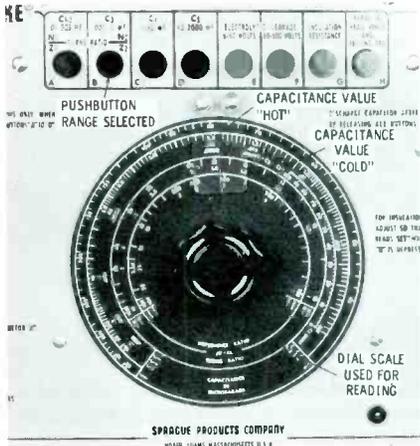


Fig. 3. Close-up: Model TO-5 panel. Note various scale calibrations on large dial.

of the instrument and measured its capacitance. I once again varied the dial for the widest eye opening and found that the capacitor's value had changed considerably (see Fig. 3). The unit now measured .019 mfd, and as it cooled the capacitance gradually returned to the original value. Replacement of this capacitor cured the trouble.

Simpson's New "260"

The somewhat familiar-looking test instrument shown connected to the circuitry of an ailing TV in Fig. 4 is a completely new VOM announced recently by Simpson Electric Co. of Chicago. Designated the Model 260, Series III, this volt-ohm-milliammeter contains many design improvements over its older brother—the 260, Series II.

Specifications and functions are:

1. DC Voltmeter—7 ranges of 0 to 250 mv, 0 to 2.5v, 0 to 10v, 0 to 50v, 0 to 250v, 0 to 1,000v, and 0 to 5,000v; sensitivity 20,000 ohms/volt; accuracy $\pm 3\%$ of full-scale deflection.
2. AC Voltmeter—6 RMS ranges of 0 to 2.5v, 0 to 10v, 0 to 50v, 0 to 250v, 0 to 1,000v, and 0 to 5,000v; sensitivity 5,000 ohms/

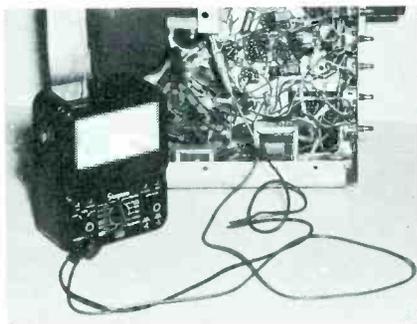


Fig. 4. Simpson Model 260 "Series III."

BETTER BUSINESS is in the cards

with the
Centralab[®]
FR-22A
FASTATCH[®]
Control Kit



It's like playing with a stacked deck! The odds are 80 to 1 that you can draw the dual-concentric control you need from this kit. Avoid delays—avoid extra trips to your distributor. Over 120 different combinations can be assembled from this small stock!

You'll be flush with new profits when you pair these units . . . so ante up \$30.73 (Your resale price totals \$49.55!)—keep a full house always—and you can bet you'll end up a big winner.


Every control factory assembled and tested—all you do is snap them together.

Catalog 30 listing the full line of Centralab products is available free from your distributor, or write us for it.

Centralab products are listed in COUNTERFACTS and PHOTOFACTS.

Centralab  A DIVISION OF GLOBE-UNION, INC.
942 B E. KEEFE AVE. • MILWAUKEE 1, WIS.
In Canada: 804 Mt. Pleasant Rd. • Toronto, Ontario

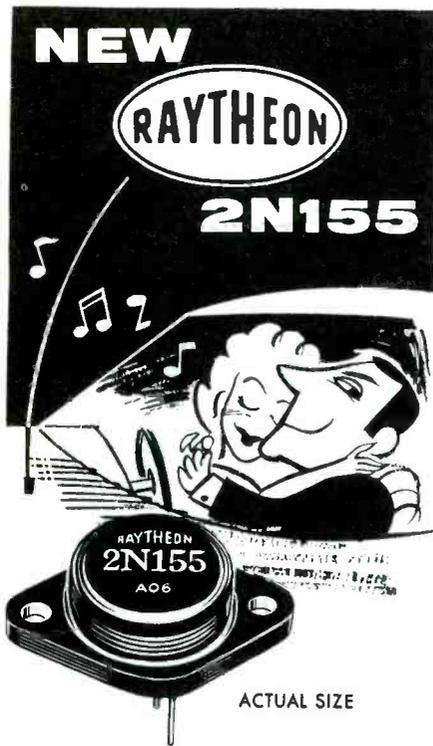CONTROLS • SWITCHES • PACKAGED ELECTRONIC CIRCUITS
CERAMIC CAPACITORS • SEMI-CONDUCTOR PRODUCTS



POWER TRANSISTOR for AUTO TRANSISTOR RECEIVERS

This new Raytheon PNP alloy-junction germanium transistor helps Service Dealers do more auto transistor receiver servicing. Designed especially for the output stage in automobile receivers, the 2N155 is used in the Ford receiver, and is an ideal replacement transistor for the power units in many other car receivers. Here is a list of the many transistor types this one, high quality, low cost Raytheon 2N155 transistor can be used to replace:

AR5	2N242
2N176	2N250
TS176	2N257
2N235	2N285
2N235A	2N301

For the complete service dealer profit picture on Raytheon Transistors, get in touch with the Raytheon Tube Distributor nearest you.



- volt; frequency response essentially flat to over 10kc, within ± 1.5 db to 50kc, useful to 500kc.
3. *AF Output*—ranges of 0 to 2.5v, 0 to 10v, 0 to 50v, and 0 to 250v; output jacks provided with blocking capacitor; direct db scale from -20 to +10, zero db corresponds to 1 milliwatt of AC power across a 600-ohm impedance; on 10v-range add 12db, on 50v range add 26db and on 250v range add 40db to scale reading.
 4. *Ohmmeter*—3 ranges of $R \times 1$ (center-scale 12), 100, and 10,000; zero ohms-adjust provided on front panel, accuracy to within 3 degrees of value on scale arc; ranges operate on 1.5 and 7.5 volts DC, five 1.5-volt batteries supplied.
 5. *DC ammeter*—6 ranges of 0 to 50 μ a, 0 to 1 ma, 0 to 10 ma, 0 to 100 ma, 0 to 500 ma, and 0 to 10 amps; separate 50 μ a- and 10-amp jacks provided on front panel.
 6. *Size and Weight*— $5\frac{1}{4}'' \times 7'' \times 3\frac{1}{8}''$, 3 $\frac{1}{2}$ lbs.

When examining this meter and making use of it in various test and measurement checks over a period of several weeks, I discovered several new features that are not found in the older 260 line. One is a polarity-reversing switch which eliminates the need for lead reversal during DC-voltage or certain resistance measurements. Another is the fact that the meter scales of the new 260 are wide and the markings well spread out, making it very easy

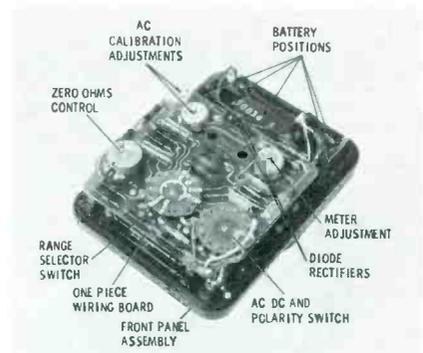


Fig. 5. Model 260 with case removed—note the new printed-board construction.

to interpret readings. The AC sensitivity of the new meter is now 5,000 ohms-per-volt with a usable frequency response of from 5 to 500,000-cycles.

Since the test procedures are relatively simple and the servicing applications fairly obvious, you may be interested in a brief description of the instrument's construction. From Fig. 4, one can see that the front panel has a 12-position range selector located in its center. The "zero

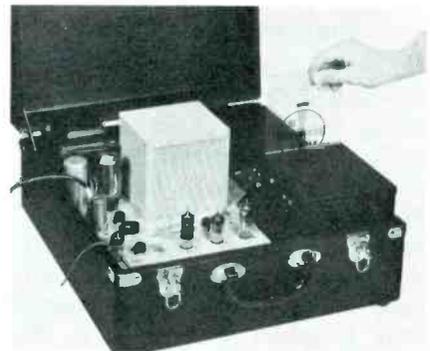


Fig. 6. The Hickok "Video Scanner"—a self-contained TV generator for servicing monochrome and color receivers.

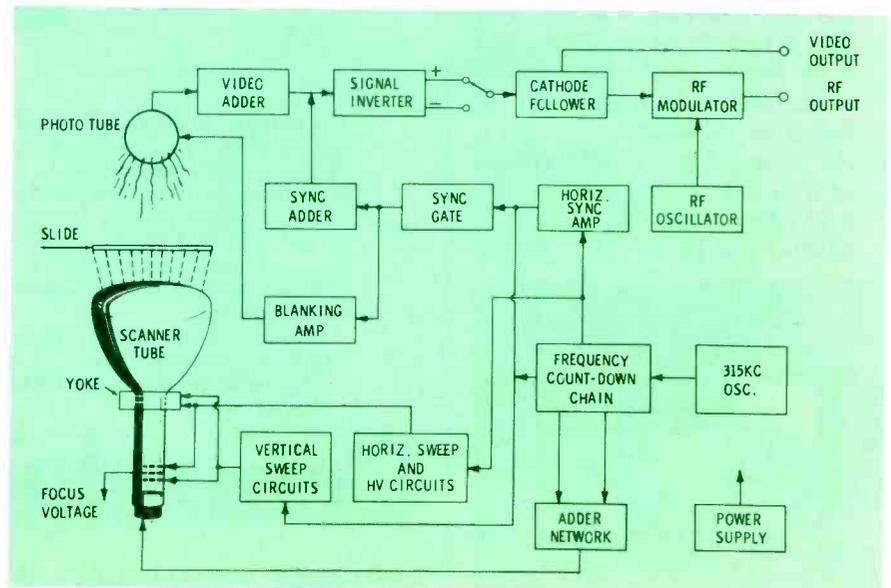


Fig. 7. Simplified block diagram of the Model 760 "Video Scanner."

ohms" adjustment is directly to the right of the selector, while the combination AC/DC and polarity-reversing switch is to the left. Two separate jacks are located in each corner of the lower panel with white lettering identifying their functions. The carrying handle is attached to each side of the bakelite case and will pivot to support the instrument in a convenient sloping position if desired.

All circuit components of the meter are mounted to the front panel and the entire assembly can be slipped from its case by removing only four screws. A photograph of the instrument's working parts is shown in Fig. 5. When removing it from its case, I immediately noticed that the meter circuitry reflects modern design through the use of printed-wiring and the neat, systematic placement of components. Although the instrument is relatively compact, all replaceable parts are easily accessible as shown in Fig. 5.

Portable TV Transmitter

The relatively complex piece of equipment pictured in Fig. 6 is manufactured by Hickok Electrical Instrument Co. of Cleveland, Ohio. Identified as the Model 760 "Video Scanner," the instrument is capable of generating signals that can reproduce pictures or patterns on the screen of any TV receiver and is especially suited for signal-tracing, analyzing frequency response, making linearity or color convergence adjustments, and general TV troubleshooting.

Specification features are:

1. Power Requirements—105 to 125 volts AC, 50/60 cps; power consumption 145 watts at 115 volts.
2. RF Output—video-sync modulated RF carrier for VHF channels 2 through 6; pretuned and selected by channel switch, variable from 50,000 microvolts down to snow-producing level; output impedance 90 ohms.
3. Video Output—video-sync signal in either positive or negative polarity, variable up to 2 volts peak-to-peak; output impedance 75 ohms; controlled sync to video modulation provided.

March, 1958 • PF REPORTER

Admiral
rated by servicemen as the
most foolproof and trouble-free
of all changers!

Admiral
built into more phonos and
combinations than any other
changer in the world!

Admiral®

4-Speed Record Changer

Hi-Fidelity




Beige and Coral
with Golden trim
(Base Optional)

- **PLAYS ALL FOUR SPEEDS**—33 1/3, 45, and 78 plus "talking book" 16 2/3 r.p.m. Has neutral position. Changes 12 to 14 records; intermixes those of same speed. Automatic 2-way shut-off after last record. Returns tone arm to rest, stops turntable motor completely. NOTE: Can be wired to shut-off radio or amplifier chassis.
- **HEAVY DUTY MOTOR**—powerful 4-pole constant speed motor operates without hum, rumble or "wows" (as little as 0.15%). Maintains even speed even if line voltage varies.
- **RUBBER TURNTABLE MAT**—cushions records, prevents slippage.
- **FEATHERWEIGHT TONE ARM**—new resonance-free design. Less than 1/2 oz. pressure. Positive tracking, no "skip" or "jump" on loud passages.
- **CERAMIC PICK-UP CARTRIDGE**—twin lever hi-fi cartridge changes with flick of the finger from LP to 78 r.p.m. needle. Impervious to heat and humidity. High lateral compliance minimizes wear, eliminates hum and distortion. Smooth even response (± 3 db) over the full high-fidelity frequency range (30-15,000 c.p.s.).
- **DIAMOND LP STYLUS**—separate LP diamond and 78 r.p.m. sapphire needles for finest sound reproduction, long record life.
- **ATTACHED 40" SHIELDED AMPLIFIER CABLE**—eliminates pickup of unwanted noise. Cable has phono tip plug for quick easy connection into standard input phono-tip jack.
- **SIX FOOT HOUSE CORD ATTACHED.**

See your Local Parts Jobber or Write for Illustrated Specification Sheet.

Admiral®

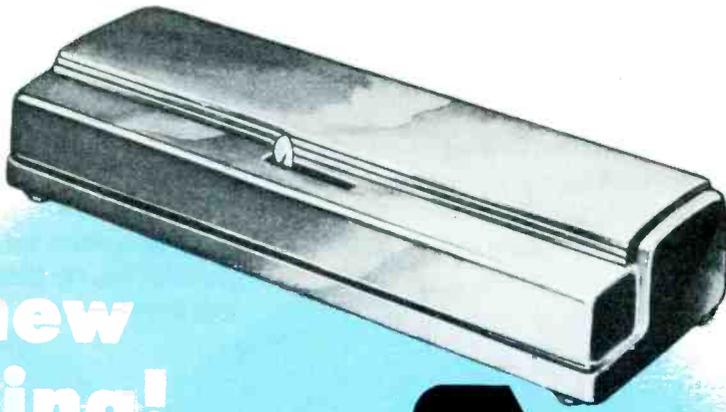SPECIAL PRODUCTS DIVISION
3800 West Cortland Street
Chicago 47, Illinois



new
styling!

vi-fi

INDOOR TV ANTENNA

AMPHENOL's new Vi-Fi is the most practical and functional indoor TV antenna ever designed. Its slender line styling matches the clean, beautiful look of the new TV sets and appliances; its colors (three choices) blend with the set—harmonize with the room.

Equally important, Vi-Fi's *Video Fidelity* provides outstanding reception. Through "Slide Rule" tuning, which inductively matches the antenna to transmitting frequencies, and Matching Transformer Coupling, which matches impedance between set and antenna, the Vi-Fi provides sharp, beautiful pictures.

TO HELP YOU MERCHANDISE VI-FI:
COLORFUL COUNTER TOP DISPLAY



AMPHENOL ELECTRONICS CORPORATION
chicago 50, illinois

AMPHENOL


4. *Other Features* — framing frequencies 60 and 15,750 cps crystal-controlled; resolution in excess of 450 lines or bandwidth in excess of 5 mc; output cable provided; set of transparent slides including standard test pattern, white dot/bar and crosshatch designs plus blanks for grease-pencil use supplied with instrument.

Checking out one of these instruments in our lab the other day, I found that this picture-pattern generator is capable of converting any positive transparency of the correct size into a modulated RF signal for TV channels 2, 3, 4, 5 and 6. Or, it will provide a video signal of either polarity for operational checks of the video-picture tube circuits of any conventional receiver. A block diagram of the Model 760 circuitry is presented in Fig. 7.


Consulting the manual, I learned that the instrument operates on the principle of a flying spot scanner; i.e., when a positive transparency is placed between the scanner and the phototube as shown in the block diagram, the image appearing on the transparent slide is transposed from variations of light to electrical impulses. The various voltages developed as the scanning tube sweeps the image are similar to a video output signal from a TV camera. In addition to generating this video signal, however, the instrument also forms both vertical and horizontal sync pulses for proper synchronization of the receiver under test.

The 60- and 15,750-cycle sync is accurately derived from a crystal-controlled 315-kc oscillator circuit. The vertical sync signal is pictured in the waveform of Fig. 8A, while horizontal sync is represented in Fig. 8B. These waveforms were obtained directly from the video output cable with the video polarity switch in its positive position and no slide in front of the scanning tube. Note the similarity between these pulses and those of a standard TV signal. The horizontal pulse contains a front and back porch, while the vertical is serrated to maintain horizontal sync during the vertical blanking interval.

When actually employing the

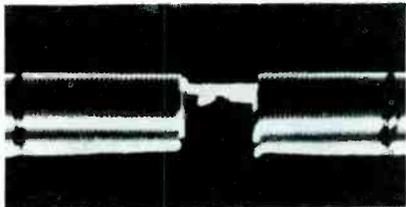

(A) Vertical sync at 30 cps.

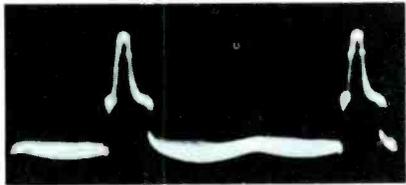

(B) Horizontal sync at 7,875 cps.

Fig. 8. Waveforms representing sync signals generated by the "Video Scanner."

"Video Scanner," I first decided to view a few patterns on the screen of a normally operating receiver. In order to check the receiver's response from tuner to picture tube, I set up the generator for an RF output on channel 2, and connected the RF output cable to the antenna terminals, turning the RF and video attenuators fully clockwise. My next step was to insert the test-pattern slide into the slotted cover surrounding the phototube area, as illustrated in Fig. 6. I was careful to note the markings on the slide — "Top Front" — before slipping it down in front of the scanning tube.

With the set's brightness and contrast controls adjusted for normal operation, I immediately detected video information on the screen. To synchronize the picture, however, I found it necessary to adjust the vertical and horizontal hold controls of the receiver. After reducing the generator's RF and video attenuators slightly, I obtained a very presentable pattern.

I also set up the unit to deliver a video output and injected this at various check points in the detector, video amplifier, and picture tube circuits. In my first attempt, the picture appeared negative on the screen — that is, the blacks were white and the whites were black. This I quickly corrected by merely flipping the video polarity switch to its opposite position.


Since the ratio between sync and video modulation is made variable by means of a sync-level control, the Model 760 is also use-

"GRIP" PRESENTING THE *New* GRIP SPINTITE® WRENCHES

PATENTS PENDING

FINEST QUALITY
STEEL SHANK
AND SLEEVE
•
BRIGHT PLATED
FINISH
•
STRONG
PLASTIC HANDLE

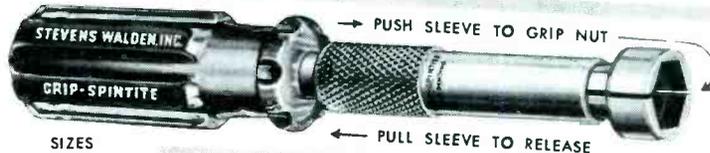WITH THE EASY "FINGER-CONTROL"
GRIP AND RELEASE ACTION
FOR THOSE
HARD-TO-GET-AT PLACES —



SIZES
3/16" TO 1 1/16"

BY THE MAKERS OF
THE ORIGINAL
SPINTITE
WRENCHES
OVER 150 STYLES
AND SIZES


ONE HAND OPERATION—

- GRIPS nuts or bolts of any material
- HOLDS firmly in any position
- TIGHTENS nut or bolt securely
- RELEASES at the pull of the fingers

Write for
catalogue

STEVENS WALDEN Inc.

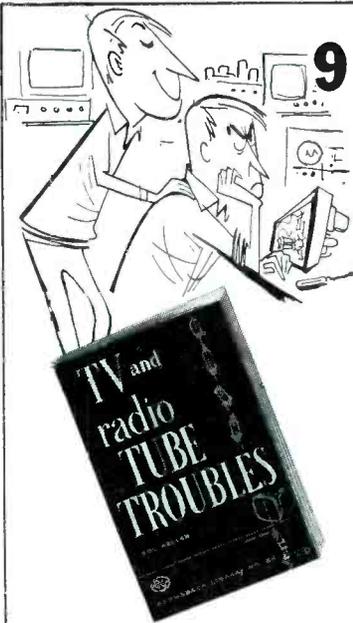500 SHREWSBURY STREET — WORCESTER, MASSACHUSETTS
MAKERS OF WORLD-FAMOUS HAND TOOLS FOR OVER 50 YEARS



9 TIMES OUT OF 10— IT'S A TUBE!

RIGHT! You can trace most radio and TV troubles right back to a tube. But which tube? Technician-writer Sol Heller's new book **TV AND RADIO TUBE TROUBLES** answers that question. With a new sure-fire symptom analysis technique he shows you how to put your finger on the weirdest TV or radio trouble in minutes. This book begins where tube checkers leave off. Today's complex and interdependent circuits make finding tube troubles a tough, nerve wracking job but with **TV AND RADIO TUBE TROUBLES** it's easy. This is the first and only book of its kind. Look over the contents and see for yourself how much you can get out of this remarkable volume. While you're at it, look over the other titles. You'll find them equally helpful.

MAIL THIS COUPON TODAY →

Gernsback Library, Inc., Dept. PR 28A
154 West 14th Street, New York 11, N. Y.

Here's my remittance of \$..... Please send me the books checked below, postpaid.

No. 68 TV AND RADIO TUBE TROUBLES
 Paper cover\$2.90 Hard cover\$4.60

Paper cover editions

<input type="checkbox"/> Servicing Color TV. No. 65\$2.90	<input type="checkbox"/> The VTVM. No. 57.....\$2.50
<input type="checkbox"/> Transistor Circuits. No. 63\$2.75	<input type="checkbox"/> Sweep and Marker Generators No. 55\$2.50
<input type="checkbox"/> Transistor Techniques. No. 61\$1.50	<input type="checkbox"/> The Oscilloscope. No. 52\$2.25
<input type="checkbox"/> Rapid TV Repair. No. 60\$2.90	<input type="checkbox"/> Transistors—Theory and Practice. No. 51\$2.00

NAME _____
 STREET _____
 CITY _____ ZONE _____ STATE _____

TV and RADIO TUBE TROUBLES By Sol Heller

Gernsback Library Book No. 68
224 pages. Paper cover.
\$2.90. Hard cover ed. \$4.60

NINE BIG CHAPTERS

Safety • Tube and Component Damage • Tube Troubles in TV • Picture and Sound Troubles • Sync Troubles • Interference • Picture Tubes • Radio Tube Troubles • Tube Replacements • Complete Index • Schematics • Diagrams • Photos.

NEW! IMPROVED!

SENCORE
TRC4
TRANSISTOR
CHECKER

Another
Sencore
Time-Saver

America's newest,
most popular test
instruments

NOW CHECKS:

- ★ **Transistors** for opens, shorts, leakage and current gain. Includes new gain test on power transistors.
- ★ **Crystal Diodes** checks forward to reverse current ratio on all diodes.
- ★ **Selenium Rectifiers** checks forward and reverse currents.

Controls are accurately set for each transistor by referring to replaceable set-up chart on rear. Test leads or socket provides for fast hook-up. See your parts distributor.



ONLY \$17.95
Dealer Net
Cannot become obsolete.
Approved by leading manufacturers.

Mfg by **SERVICE**
INSTRUMENTS CORP.
171 OFFICIAL RD., ADDISON, ILL.

Cut out this ad now for further information



all EYES
are on MERIT

...watch for new
catalog No. 5811
it's terrific!



"COMPARE IT
WITH MERIT"

MERIT COIL & TRANSFORMER CORP.
4427 N. CLARK ST., CHICAGO 40, ILLINOIS

ful for checking sync circuit operation. Using a scope, the technician can monitor the input and output of a sync system under various sync-to-video ratios and at different RF signal levels. As a portable TV transmitter, the 760 is of further value in servicing both monochrome and color TV receivers—not to mention its applications in checking TV boosters, antennas, and distribution systems.

Speedy Tube Testing

The piece of equipment shown in operation in Fig. 9 represents one of the new pre-wired socket-type portable tube checkers. Developed and produced by B&K Mfg. Co., Chicago, the Model 650 "Dyna-Quik" Mutual Conductance Tube-Transistor Tester is capable of performing tests on over 500 tube types, including those most commonly used in radio and TV. Due to its compactness and ease of operation, the instrument is ideal to carry on service calls.

Specifications and test features are:

1. **Power Requirements**—105 to 125 volts AC, 60 cps, line fuse and automatic voltage compensator provided.
2. **Panel Features**—53 pre-wired tube sockets plus 16 spares for future modernization; n-p-n and p-n-p transistor sockets; diode and rectifier test jacks; 7-pin miniature and 9-pin tube-pin straighteners; 4½" meter calibrated in REPLACE-?-GOOD, two ranges of 0-6,000 and 0-18,000 micromhos, a grid emission scale, and a GOOD-?-POOR scale for transistors; heater continuity and short indicators also provided.
3. **Size and Weight**—portable case 15¾" × 15" × 16½", 19¼ lbs. net.
4. **Leakage, Gas, and Shorts Test**—tubes are automatically checked for these defects plus grid emission; leakage and shorts up to 1 megohm are indicated on neon lamp; gas and grid emission by meter deflection.
5. **Dynamic Mutual Conductance Test**—all popular amplifier tubes including multisection types are tested in pre-wired sockets; Gm indicated on RE-



Fig. 9. "The Dyna-Quik" Tube and Transistor Tester features pre-wired sockets.

PLACE-?-GOOD or micromho scale; life-expectancy test also provided.

6. **Heater Continuity Test**—rapid test of filament continuity provided on heater-voltage switch, neon indicator on front panel.
7. **Diode-Rectifier Test**—forward-to-reverse conduction ratio for all germanium and silicon diodes as well as selenium, copper oxide, and silicon rectifiers.
8. **Transistor Tests**—checks all junction, point-contact, and barrier-type transistors for leakage and gain; indications shown on separate meter scale.

In order to familiarize you with the Model 650, let's see exactly how a tube is tested in the unit. As a typical example, I selected a 12AU7 which had been in operation over a year in one of our lab test receivers. Following instructions, I turned on the instrument by means of the OFF-ON LIFE switch in the lower right-hand corner of the test panel. In so doing, the red pilot light just above the switch came on. I noted that the most popular and frequently used tube types were listed beside their respective test sockets on both panels, so I located the appropriate one, set the heater switch to 12 volts, and plugged the tube in (making sure that the test lever was in its SHORT-GRID EMISSION position before placing the tube in the socket).

I next set the sensitivity control to the value stipulated beside the tube designation on the panel. Without touching another knob or button, the instrument



Fig. 10. The Model 650 tube-data pad—a flip-open index for quick reference.

was now supposed to test the tube for leakage, gas, grid emission and for any direct shorts. Leakage and shorts are indicated by a neon lamp located directly above the panel meter, while any gas or grid emission was to show up by a deflection of the meter needle.

Noting that the tube passed this first test, I then moved the test lever up to its next position marked TEST 1. Since a 12AU7 is a dual-triode, only one section of the tube is tested for mutual conductance when the test lever is in this position. I determined the condition of this triode section by referring to the REPLACE-?-GOOD scale of the meter. In this particular instance, the reading was okay, so I then moved the test lever up another notch to the TEST 2 position. I found that this second section was a little weaker than the first but that it still registered in the GOOD area.

This completed the tube testing procedure except for a special LIFE TEST which is somewhat of an additional feature in the Model 650. The life test consists primarily of a mutual conductance measurement under a condition of low heater voltage. The tube heater or filament is operated at a 10 to 15% reduction in line voltage by placing the ON-OFF-LIFE TEST lever in its upper position. If a sharp drop in Gm is noticed, the chances of continued trouble-free operation are doubtful.


Another interesting feature of the Model 650 is its built-in tube reference pad. (See Fig. 10.) The pad is an automatic flip-open index giving complete setup information for tube types, as well as an average Gm in micromhos for all amplifiers. ▲

XCELITE Hand Tools

PREFERRED BY THE EXPERTS

Featuring QUALITY

See Your Distributor!

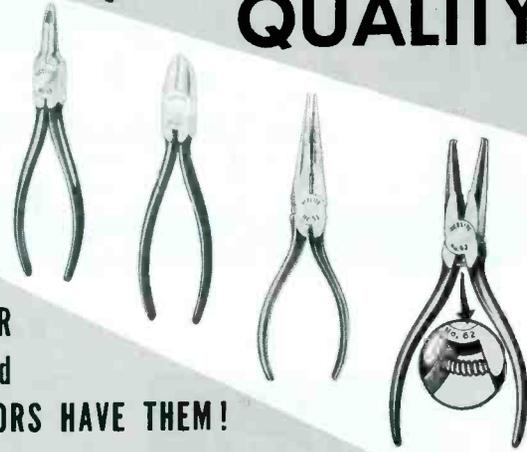

A TECHNICIAN MUST HAVE PROPER HAND TOOLS . . . and XCELITE DISTRIBUTORS HAVE THEM!

XCELITE hand tools are made especially for the professional Radio, T.V. and Electronic technicians . . . pliers for example, made of the finest steel, with perfectly matched tips and all cutting edges induction hardened and hand honed . . . fully polished heads and jaws. Available in a variety of regular or special types and sizes for greater utility and performance . . . remember XCELITE for the finest tools first!

Call or see your distributor today . . . get acquainted with the complete line of XCELITE quality tools.

XCELITE, INCORPORATED

Dept. Q, Orchard Park, N. Y.

In Canada: Charles W. Pointon, Ltd.

6 Alcina Ave., Toronto, Can.

For Originality

LOOK TO XCELITE



Write for the latest Oxford catalog



OXFORD Components, Inc.

Subsidiary of Oxford Electric Corp.
556 West Monroe Chicago 6, Ill
Export: Reburn Agencies, New York City
In Canada: Atlas Radio Corp., Ltd., Toronto

MAKE SURE IT FITS!

OXFORD SPEAKERS

When you order a speaker (for replacement or original installation), demand units that meet your most exacting needs.

Each OXFORD SPEAKER is "tailor-designed" to actually "fit the application."

The next time you specify speakers, make certain they fit the job by selecting OXFORD . . . unsurpassed quality for over thirty years.

<p style="text-align: center; font-weight: bold; margin: 0;">RADIO & TV SPEAKERS</p>  <p style="font-size: 0.8em; margin: 0;">OXFORD Speakers are used by more original set manufacturers — find out why!</p>	<p style="text-align: center; font-weight: bold; margin: 0;">OUTDOOR SPEAKERS</p>  <p style="font-size: 0.8em; margin: 0;">For rugged, steady performance under any conditions, OXFORD Weather-proof speakers will meet the need.</p>
<p style="text-align: center; font-weight: bold; margin: 0;">DUAL CONE HI-FI SPEAKERS</p>  <p style="font-size: 0.8em; margin: 0;">Oxford's newest development to provide maximum performance. For Hi-Fi and rear deck applications.</p>	<p style="text-align: center; font-weight: bold; margin: 0;">PORTABLE RADIO SPEAKERS</p>  <p style="font-size: 0.8em; margin: 0;">More Oxford speakers are used in portable sets than ever before . . . there must be reasons!</p>

using a scope to TROUBLESHOOT SWEEP CIRCUITS

Robert G. Middleton

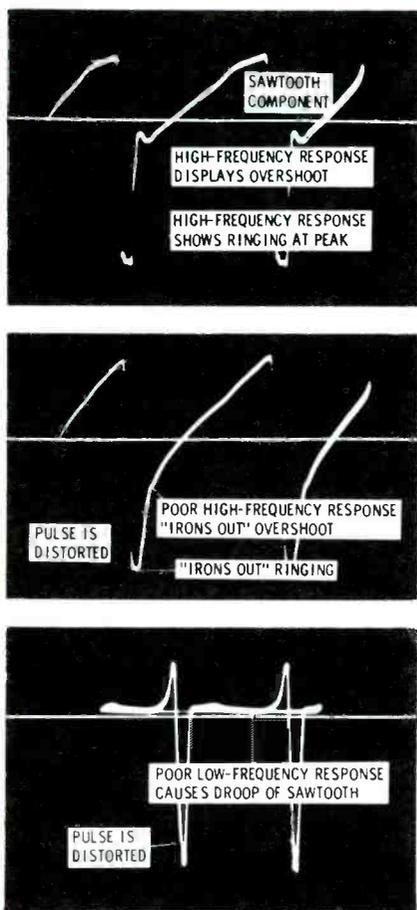


Fig. 1. Drive signals observed on scopes having different response characteristics.

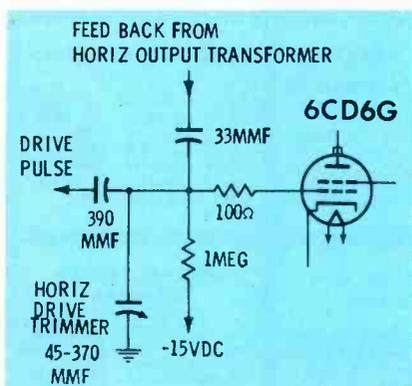


Fig. 2. To avoid waveform distortion, high-Z grid circuits of this type should be tested using a 10-to-1 low-C probe.

The oscilloscope is one of the most versatile instruments you can own—if you know how to use it, that is. Since many of the troubles encountered in TV servicing have to do with the sweep sections, this article will acquaint the reader with suitable methods of using an oscilloscope in making tests of sweep circuitry and will also inquire into the requirements of scope characteristics for sweep servicing. The emphasis is placed on how to apply a suitable scope in the correct manner and how to interpret the patterns which are displayed.

Oscilloscope Bandwidth Requirements

While extremely wide-band response is not required of a scope utilized in sweep-circuit servicing, there are certain minimum requirements which must be observed if waveform distortion is to be avoided. A scope having a flat response up to 2 mc is completely satisfactory and will faithfully reproduce fine details of sweep waveforms, such as transient ringing and peaking-pulse detail. This is best illustrated by a comparison of the waveforms in Fig. 1.

Medium frequency response in the vertical amplifier, such as provided by scopes intended primarily for alignment work and which have a flat response up to several hundred kilocycles, has the effect of smoothing off and filtering out such waveform details as transient ringing and tends to distort the waveshapes of pulses. The shape of such waveforms as sawtooth waves, which are of primary interest in sweep-circuit work, may also be distorted noticeably.

Poor frequency response (in terms of sweep-servicing requirements) as provided by oscilloscopes intended primarily for audio-frequency tests, causes the reproduced waveform to lack important higher-frequency components, and also introduces distortion due to phase shift of these components. The practical result of these deficiencies can be seen from the photographs in Fig. 1.


Waveform Voltage Considerations

When applying an oscilloscope in a sweep or high-voltage circuit, it is sometimes necessary to utilize a suitable probe to avoid overload due to excessive waveform voltage. Scopes are rated by their manufacturers for maximum input voltage on any setting of the attenuator, and the highest voltage which can be applied without distortion in the reproduced waveform is usually on the order of 600 peak volts.

Not only is waveform clipping and distortion encountered when the applied signal voltage is excessive, but actual damage to the scope may result. The input blocking capacitor may be punctured, the attenuator resistors may be charred, and similar damage incurred to the various components of the input system. Suitable probes should be utilized to avoid these difficulties.

The driving voltage to the horizontal-output tube has a value from 75 to 150 peak-to-peak volts in normal receiver operation. Thus, this waveform may be applied directly to the scope input terminals without danger of overload or damage. However, there

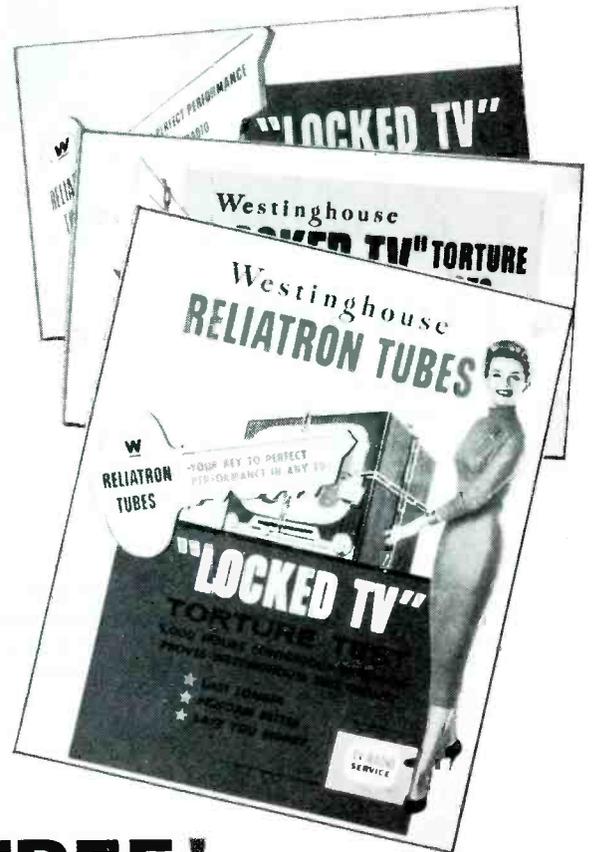WESTINGHOUSE HELPS TV SERVICEMEN "GET A FAIR SHAKE!"



FREE!

"Build Consumer Confidence" Promotion

Today most people are unaware of the buy they get in TV and radio service. Now, Westinghouse helps you educate them with a program designed to win you friends and influence sales! You get a complete kit *free!* Keystone of the promotion is the mailing piece shown left. It describes how many hundreds of parts there are to check . . . how much knowledge it takes to be a serviceman . . . equipment costs . . . etc. It shows how TV servicemen, like doctors and lawyers, constantly study to keep up with advances. In addition you get window displays, streamers, everything you need—all free! Don't wait, put this promotion to work for you now . . .

CALL YOUR WESTINGHOUSE DISTRIBUTOR

YOU CAN BE SURE... IF IT'S **Westinghouse**
Electronic Tube Division · Elmira, New York

... another
MALLORY
 service-engineered
 product



THE STRONG SILENT TYPE

FOR TOP PERFORMANCE

Mallory Gold Label Vibrators set a new standard of quality and performance. They're the quietest, most dependable vibrator you can find anywhere for replacement service. Gold Label Vibrators use the exclusive Mallory buttonless contact design that insures quick, positive starting—provides far longer life—keeps output constant.

Let Mallory's 27 years of vibrator pioneering and leadership be your standard of quality, to help build your service reputation.



**Have you tried the new
 Mallory Highlander Vibrator?**

For economy jobs, get performance second only to the Mallory Gold Label. Buy them in the handy 10-pack carton. Write for your copy of the latest edition of the Mallory Vibrator Guide.

P. R. MALLORY & CO. Inc.
MALLORY

P. R. MALLORY & CO. Inc., INDIANAPOLIS 6, INDIANA

- Capacitors
- Vibrators
- Resistors
- Power Supplies
- Mercury and Zinc-Carbon Batteries
- Controls
- Switches
- Filters
- Rectifiers

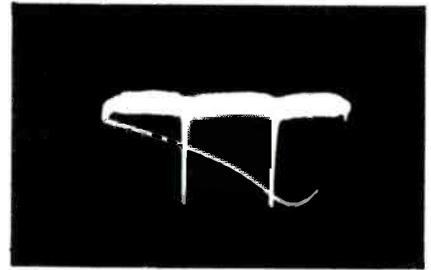


Fig. 3. Typical voltage waveform obtained across horizontal deflection coils.

is another consideration in checking this waveform which must be heeded in numerous cases—the grid impedance of the horizontal output tube may be sufficiently high that direct application of the scope input cable may load the grid circuit and produce waveform distortion. For example, the circuit shown in Fig. 2 is subject to such loading. The problem can be circumvented by utilizing a 10-to-1 low-capacitance probe, providing a step-up of input impedance of ten times and reducing the loading imposed on the grid circuit by the probe to a satisfactorily small value.

The deflection voltage across the horizontal-output coils, on the other hand, appears across a relatively low value of circuit impedance, so that the loading imposed by a direct input cable to the scope is not a matter of concern. However, this waveform has a peak-to-peak voltage value ranging from approximately 1,500 to 3,000 volts. This waveform, illustrated in Fig. 3, will accordingly overload the vertical amplifier in a scope which is intended for application at voltages under 600. The result of such overload is to clip the waveform, or drive the input stage into grid current flow, or both, with the result that the reproduced waveform exhibits severe distortion, as illustrated in



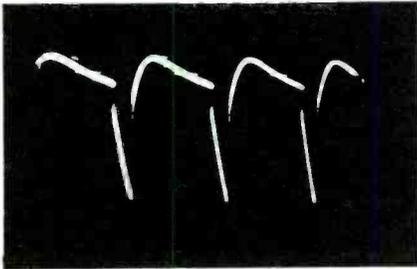


Fig. 4. Deflection waveform shows distortion when voltage exceeds scope rating.


Fig. 4. Again, this difficulty usually can be avoided by use of a 10-to-1 low-capacitance probe. In this application, the probe is not utilized to obtain increased input impedance, but to take advantage of the incidental signal attenuation which the probe provides. Thus, a deflection voltage waveform having a value of 2,500 p-p volts is reduced to a value of 250 p-p volts. The only limitation in this regard is the input voltage rating of the probe itself, which in some cases is limited to 1,000 volts. If the voltage rating of the probe would be exceeded, it will be necessary to utilize a 100-to-1 capacitance-divider probe with its typical input rating of 10 to 20 kv.

Technicians sometimes suppose that the requirement for a suitable probe in such applications can be circumvented by expedients, such as by holding the exposed end of a test lead near the yoke terminal. While it is true that the waveform can be displayed on the scope screen by this means without scope overload, the method is incapable of providing data concerning the peak-to-peak voltage of the waveform. This information is as important as the shape of the display, since it is a general rule in troubleshooting work that circuit trouble may be indicated if the waveform voltage deviates more than 20% from its



... another
MALLORY
service-engineered
product

MALLORY Push-Pull Switch

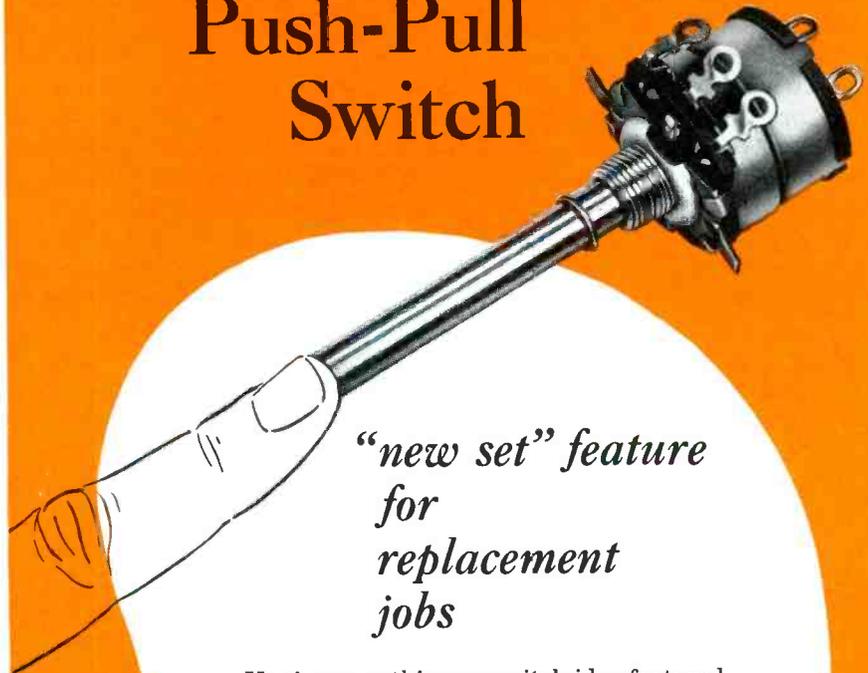

*“new set” feature
for
replacement
jobs*

You've seen this new switch idea featured in the latest TV sets. Now you can use it on many control replacements to add extra convenience for your customers.

Pull the control shaft and the set turns on; push, and the set turns off. No more “guessing” at volume setting. No more accelerated wear on the low end of the element every time the set is switched on or off.

The new Mallory switch far outlasts conventional switches; never sticks . . . never damaged by overloads. Get controls with this unique new switch from your Mallory distributor, in the ratings you need for any replacement.



*Shaft adapters to fit
any style knob.*



- Capacitors • Vibrators • Resistors • Controls • Switches • Filters
- Rectifiers • Power Supplies • Mercury and Zinc-Carbon Batteries

rated value. Some technicians are under the misapprehension that if the waveform voltage is far off value, the waveshape will also be incorrect. This is a very unsafe assumption, and one which is not true in numerous cases. The safe rule to follow in such work is to check the waveform *both* for proper shape and for its rated voltage within the 20% tolerance.

A particular word of caution is also in order concerning the use of such expedients when testing waveforms in vertical sweep circuits. The repetition rate in the

vertical sweep circuits is 60 cps, and only compensated probes can effectively be utilized to obtain attenuation or impedance step-up. If the technician attempts to use expedients in such situations, severe waveform distortion will usually be encountered due to low-frequency loss and phase shift. These remarks apply with equal force, it may be observed, to the use of capacitance-divider probes in making vertical sweep-circuit tests. Capacitance-divider probes can be used without imposing distortion on the waveform only if their ap-

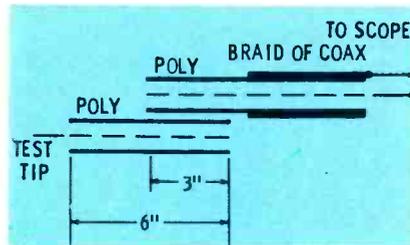



Fig. 5. Capacitance-divider which can be calibrated for 100-to-1 attenuation.

plication is restricted to circuits operating at frequencies of 10 kc or higher.


It should be noted, however, that certain improvisations which are somewhat out of the class of expedients will serve to attenuate the voltage by a known factor. For example, the arrangement shown in Fig. 5 can be improvised and calibrated by sliding the two lead sections to obtain the desired 100-to-1 attenuation ratio, following which the lead sections can be bound together with tape.

Current Waveform Considerations

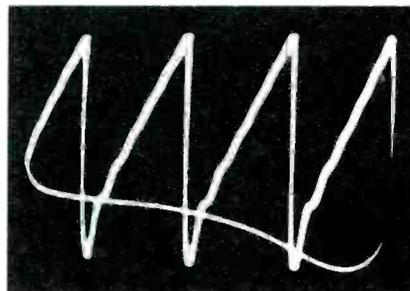Most technicians nowadays are aware of the possibility of viewing current waveforms in addition to voltage waveforms. To view a waveform of the horizontal deflection current, for example, a resistor of approximately 5 ohms may



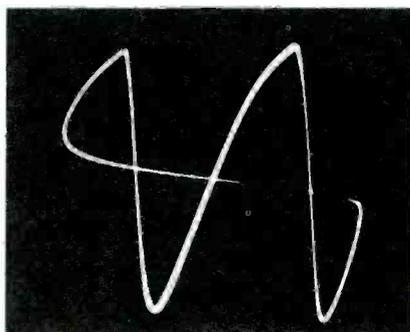(A) Ringing which produces alternate light and dark vertical stripes in raster.



(B) Nonlinear rise which causes cramping at right side of raster.

Fig. 6. Deflection current waveforms.

ALL OVER THE U.S.
Utah STANDS for
UNSURPASSED SERVICE

Yes . . .
ALL OVER THE U.S.
UTAH STANDS for UNSURPASSED SERVICE

Yes, all over the U. S.—Utah stands for Unsurpassed Service.

US—Utah and the Service Man—because Utah stands behind you—the Service Man.

Utah stands behind you—with a speaker name that for over 30 years has signified the finest in quality, design, engineering and production.

Utah stands behind you with a speaker that gives installation performance. You can sell customer satisfaction with a Utah—because Utah gives performance satisfaction.

Utah stands behind you—with a secure source of supply. Leading jobbers all over the U. S. handle Utah—because Utah has the finest and widest line of replacement speakers available to the trade.

Utah your one complete speaker source auto * Rear Deck Kits * Standard Replacement * Television * Public Address * High Fidelity * Outdoor * Inter-Com * Wood & Metal Baffles

Utah is your one, complete satisfactory speaker source. When you order speakers today — **THINK—then order Utah.**

Get your **FREE** copy of the latest Utah Catalog S-157 listing over 100 replacement speakers. Available at your distributors or write direct.

Utah RADIO PRODUCTS CORPORATION
 HUNTINGTON • INDIANA

Export Dept. Fidevox International, Chicago, Illinois

be inserted in series with the return lead from the horizontal deflection coils and the scope applied across the resistor. The current waveform in the deflection circuit then becomes displayed on the scope screen, as depicted in Fig. 6.

From this waveform, it is seen that various irregularities in circuit operation, such as nonlinearity and ringing, are set forth explicitly in this test. When ringing or other relatively high-frequency detail occurs in the pattern, it is necessary, of course, that the scope provide sufficient frequency response to accommodate the spurious frequency.

The scope can be calibrated in terms of peak-to-peak milliamperes just as it can be calibrated in terms of peak-to-peak volts. As an example of such calibration for current measurement, consider a situation in which a 5-ohm resistor is to be utilized to develop the current waveform. One milliamperere of current through the resistor produces five millivolts of potential across the resistor terminals. Hence, if the scope is calibrated for five millivolts per square, it will be calibrated for one milliamperere per square when utilized in combination with a 5-ohm resistor. The calibration is thus merely a routine application of Ohm's Law.

It is worth noting that when current waveforms are under consideration, it is the peak-to-peak current values which are measured. The same reasons for using p-p values apply for current checks as well as for voltage checks—the current waveforms in general are nonsinusoidal, and are best dis-

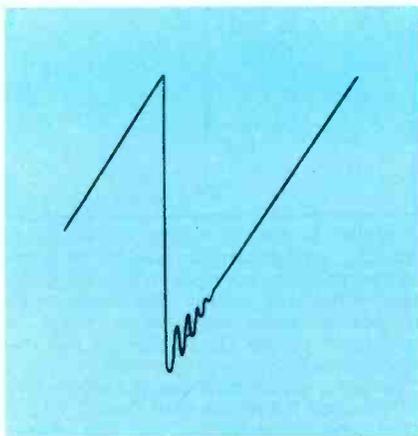


Fig. 7. This amount of ringing produces vertical stripes which are not overly objectionable at normal viewing distance.

cussed from a practical viewpoint in terms of peak-to-peak values. Note in this regard that Ohm's Law applies to peak-to-peak values in the same manner as it applies to RMS values or DC values. Thus, resistance is equal to peak-to-peak voltage divided by peak-to-peak current.

The technician finds it helpful to view current waveforms on occasion because various sweep-circuit faults, such as alternate light-and-dark vertical bars which receiver manufacturers sometimes refer to as "curtain effect," can be caused

by faults other than ringing in the current waveform. If the current waveform is displayed on the scope screen and is found to be free from ringing, then investigation must be directed elsewhere. It is worth noting that curtain effect will become apparent in the raster when the ringing in the current waveform is quite small, as illustrated in Fig. 7. The results of this amount of ringing would be visible at a normal viewing distance, although usually they would not be considered objectionable by the average observer.

"TOTEMASTER"

*most revolutionary new design
in over 20 years*

Lifetime molded handle

Order book and schematic holder

Non-distortion glass mirror for TV alignment

Built-in 7 and 9 pin straightener

Detachable hinge; cover fits any section

Adjustable web strap tilts cover at any angle

Heavy nickel-plated raised steel corner and angle protectors

4 different size sections for all tube sizes

Strong draw pull catches with locking ear for padlock or chain

3/8" steel bottom studs; self-aligning rubber feet on all other sections

Weights only 15 lbs.


Here is the newest idea in a tailored tote box. A master carrier convertible into any size box you require. Carry the whole box or any part of it. "Totemaster" is loaded with built-in service aids and quality features. See it at your Parts Jobber and ask for a demonstration today. "TOTEMASTER"... feature for feature the best tote box buy on the market!

MASTRA COMPANY


SUPERIOR AVE.
CLEVELAND 14, OHIO

PIONEER MANUFACTURERS OF THE TUBE AND TOOL TOTE BOX

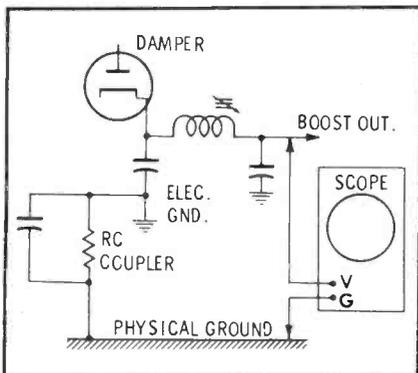
Scope Application Precautions in Sweep-Circuit Tests




The electrical chassis of some TV receivers is coupled to the physical chassis through an RC branch as illustrated. The scope ground must be made to the electrical chassis (or B— bus) to avoid introduction of hum voltage into the pattern. To obtain an idea of the values of resistance and capacitance which cause difficulty when they occur in series with the ground-return lead of the scope, it may be observed in a typical case that the damper waveform exhibits a considerable amount of hum interference when 100,000 ohms, or 0.03 mfd is inserted in series with the ground-return lead. Even half these values of resistance or reactance introduce an objectionable amount of hum interference.

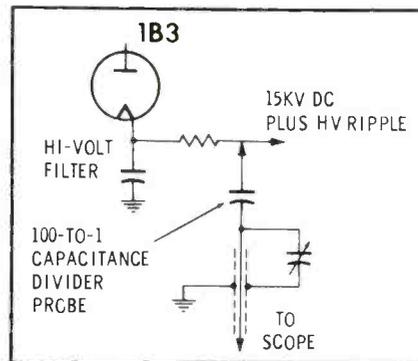

The use of a 100-to-1 capacitance-diver probe to check the waveform at the high-voltage filter is appropriate, provided the 100-to-1 probe is rated for this application. It is possible to use either an AC or a DC scope in this ripple test, since a capacitance-diver probe passes only AC and blocks the flow of DC. The only precaution is to utilize a probe having an input voltage rating which exceeds the output voltage of the high-voltage filter under test.

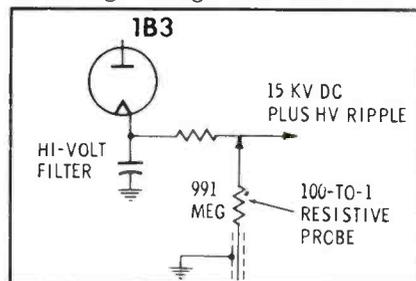


Use of a 100-to-1 resistive probe is not good practice in checking the waveform at the high-voltage filter. The frequency response of the probe is not appropriate, and its unshielded construction often permits the entry of stray fields, such as hum voltage. When used with a DC scope, the waveform is accompanied by a DC voltage of 25 or 30 volts, which may throw the pattern off-screen unless the scope has wide-range centering controls. When used with an AC scope, the full output voltage from the high-voltage filter will build up across the blocking capacitor in the scope input circuit and puncture the capacitor.

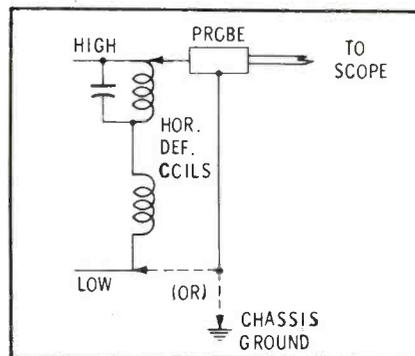

A choice of ground return is possible in making sweep-circuit checks in some instances. For example, when checking the waveform across the horizontal-deflection coils, the probe may be grounded to the "low" side of the deflection coils or to the receiver chassis. The latter connection has the advantage of keeping the scope case "cool", i.e., at true ground potential but the disadvantage of introducing some distortion into the display, in case the impedance of the decoupling circuit and power supply is appreciable.

SPECIALY PRICED DURING MARCH!

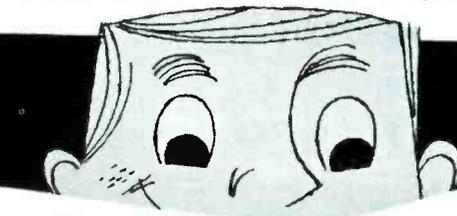

UNIVERSAL TEST KIT



No. 9290X

Here's your chance to get two useful service aids at a never-again low price. It's timed to help you get set for your spring TV servicing requirements... good this month only!



CONSISTS OF

No. 9250 TEST SOCKET ADAPTER KIT

Four adapters for 7-8-9 pin miniature receiving tubes and CRT top-of-the-set testing.

No. 9270 TUBE CHECKER

Pocket-size series filament tube checker and continuity tester for speedy TV servicing.



REGULAR DEALER NET \$9.50

SPECIAL this MONTH

only \$7.45


Send Postcard for Your FREE G-C Catalog!

Total value of these G-C service aids is \$14.75... but they're specially priced this month only to show you how G-C products help you do a better and more profitable servicing job. Buy now and save!


See Your G-C Jobber Now!

GENERAL CEMENT MFG. CO.

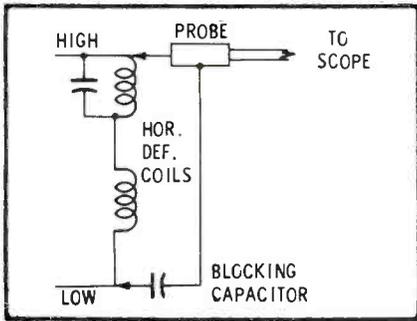
DIVISION OF TEXTRON Inc. • LOS ANGELES • ROCKFORD, ILLINOIS



When it is desired to make the scope ground return to the "low" side of the deflection coils to obtain undistorted waveform reproduction, it is a good precaution to insert a series blocking capacitor in the ground return lead to avoid raising the scope case to B+ potential. It is also necessary to choose a sufficiently high value of blocking capacitor that the AC impedance of the ground lead will be negligible.

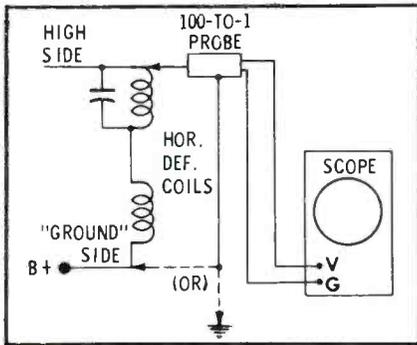




The peak-to-peak voltage across the horizontal-deflection coils usually falls in the range from 1,500 to 3,000 volts. This voltage is sometimes sufficient to break down the input circuit of a 10-to-1 low-capacitance probe. If the probe happens to withstand the applied voltage, distortion may be encountered due to scope overload. Good practice dictates the use of a 100-to-1 capacitance-divider probe in such tests.

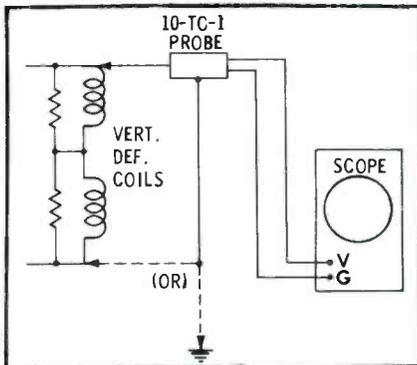

It is improper to attempt to use a 100-to-1 capacitance-divider probe in checking any of the waveforms in the vertical-deflection system. The reason for this limitation is the fact that vertical circuits operate at 60 cps and 100-to-1 capacitance-divider probes are uncompensated. Being uncompensated, such probes distort waveforms at frequencies below 10 kc. This is not a matter for concern, however, since the voltages encountered in vertical circuits are sufficiently low that a 10-to-1 low-capacitance probe can be utilized. Such 10-to-1 probes are compensated and reproduce 60-cycle waveforms without distortion.

In most cases, one side of the horizontal-deflection coil system is at or near ground potential. In some cases, however, as illustrated, both sides of the deflection system are well above ground potential. In such cases, it is not possible to insert a 5-ohm resistor in either of the leads to the deflection coils to view the current waveform, because the scope case must be connected to a point at or near ground potential. Failure to observe this precaution will result in severe impairment of circuit operation and possible damage to the scope.

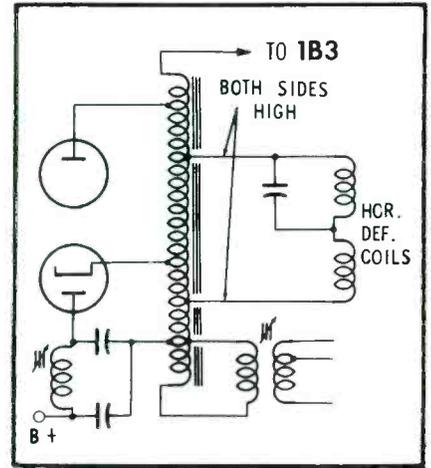
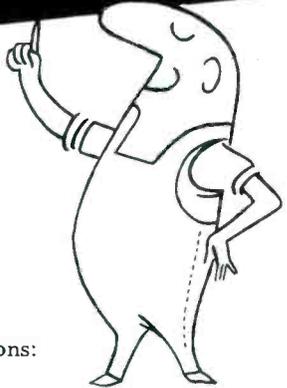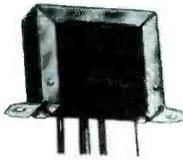
<p>110° Yokes DY-26A, DY-27A</p>  <p>Exact replacements for RCA in chassis KCS-107, 108F, 109 113 series</p>	<p>Exact Replacement Flybacks for PHILCO</p>  <p>HO-276 HO-277, HO-278 used in 171 models—with resistors and capacitors attached.</p>	<p>Exact Replacement for AIRLINE, FIRESTONE WELLS-GARDNER</p>  <p>HO-273 used in 19 models</p>
<p>Exact Replacement for MAGNAVOX</p>  <p>HO-279 Replaces 360632-1 in 350 series</p>	<div style="text-align: center;"> <p>new STANCOR TRANSFORMERS</p>  <p>to make your job easier</p> <p>Typical of the new Stancor units are these recent additions:</p> </div>	
<p>Exact Replacement Flyback for MOTOROLA</p>  <p>HO-281 used in 154 models</p>		
<p>Exact Replacement Vertical Outputs for RCA</p>  <p>VO-103 replaces 103093, 972151-1 VO-106 replaces 102146, 972725-1 VO-107 replaces 103266, 972725-2</p>	<p>90° Yoke for EMERSON</p>  <p>DY-25A exact replacement for Emerson 708288</p>	<p>FREE The Stancor TV Guide, listing the full line of Stancor exact replacement transformers for radio-TV and other applications is available free from any Stancor distributor, or by writing direct to Chicago Standard.</p>



CHICAGO STANDARD TRANSFORMER CORPORATION

3503 Addison Street • Chicago 18, Illinois

Export Sales: Roburn Agencies, Inc. • 431 Greenwich Street • New York 13, N. Y.

servicing new designs

by Thomas A. Lesh

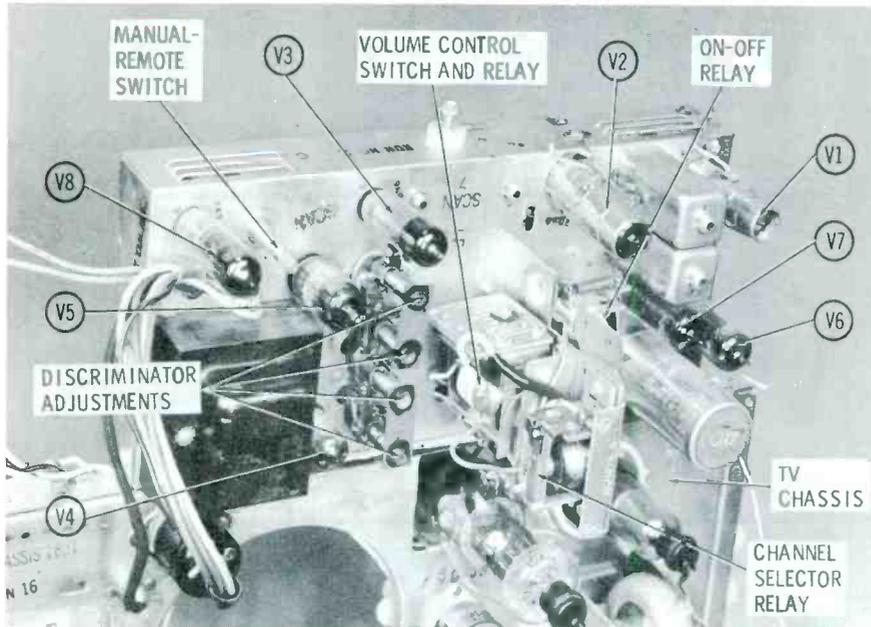


Fig. 1. "Son-r" control receiver mounted on Admiral TV chassis.

Remote Control for TV-Phono Combination

The "Son-r" remote control available on certain models of 1958 Admiral TV receivers is a wireless system of the acoustic type. In it, a hand-held remote transmitter contains metal rods which set up ultrasonic vibrations (in the 40-kc range) when keyed; these are picked up by a microphone on the TV set and converted to an electrical signal which is fed to an 8-tube control receiver. Set operation is regulated by relays mounted on this unit.

There are two versions of the "Son-r" system. The 8F1 is meant for use with a deluxe combination console that includes a 17D1 TV chassis, a record changer, an FM-AM radio tuner, and a hi-fi audio amplifier which receives inputs from all other units. The 8G1, very similar in layout to the 8F1, but equipped with much simpler switch and relay circuits, is employed with the 17J1, 16J1 and 16K1 TV chassis which have motorized tuning.

The control relays and their functions are as follows:

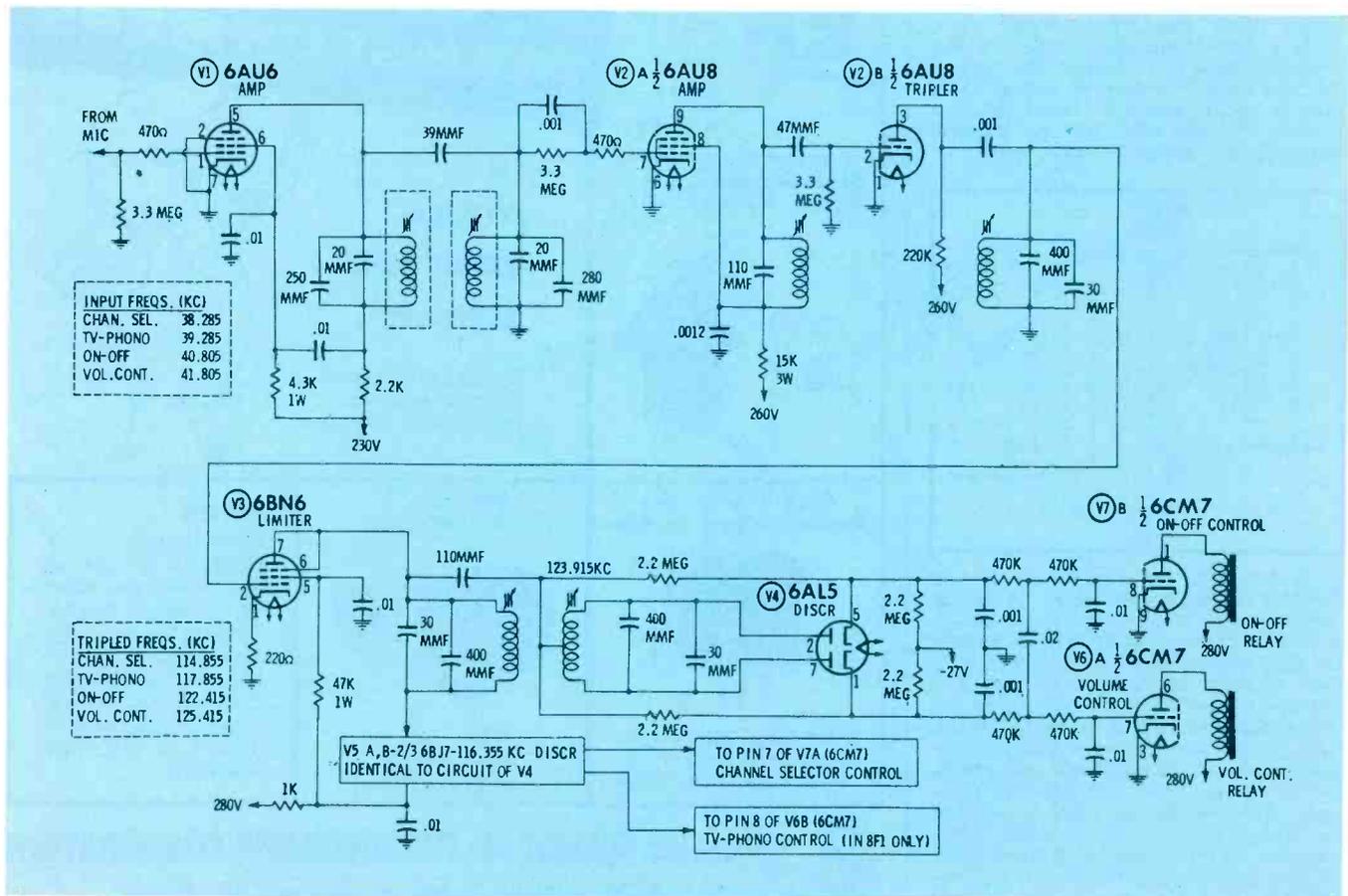


Fig. 2. Schematic of "Son-r" control receiver chassis.

ON-OFF—Makes and breaks the AC power circuit to the controlled chassis. Operation of the relay throws a switch to the "On" position, where it comes to rest. Another signal impulse must be applied to the relay in order to return the switch to "Off."

VOLUME CONTROL—Rotates the movable arm of an unusual 12-contact rotary switch that incorporates printed wiring. The contacts are parallel-wired into four groups so that there are effectively only four switch positions—zero, low, medium and high volume. The 12 contacts are necessary because the relay moves the switch arm through an arc of only 30° on each impulse. To produce the desired changes in volume, various combinations of resistors are shunted across the speaker voice coils (8F1) or the volume control circuit (8G1).

CHANNEL SELECTOR—Momentarily closes an AC power circuit and starts the cycle of the tuning motor. In the 8F1 only, this relay circuit passes through a "TV-Phono" switch so that the relay can be utilized to reject records when the TV is not in use.

TV-PHONO (8F1 only)—Moves a three-section switch back and forth between two resting positions. In the first or "TV" position, the channel selector relay is set up for remote TV tuning, AC power is applied to the TV chassis, and the output of the TV sound detector is connected to the hi-fi amplifier input. In the "Phono" position, the channel selector relay, AC power line and hi-fi input are switched to the phono reject trip coil, phono motor, and radio-phono signal output, respectively.

Fig. 1 is a photograph of the control receiver chassis, and Fig. 2 is a simplified schematic of that unit. Signals picked up by the microphone pass through a selective two-stage amplifier (V1 and V2A) and are tripled in frequency by the next stage, V2B. (Input and tripled frequencies associated with each relay are listed in Fig. 2.) The 6BN6 tube

V3 limits the amplitude of the signals and applies them to a pair of discriminators, which are identical except for the tube types used. Note that the tripled frequency of any one of the signals will always fall 1.5 kc higher or lower than the center frequency of one of the discriminators. This means that each input signal will produce an effective response in one discriminator. For example, an "On-Off" signal (122.415 kc) will cause a positive output voltage to appear at pin 5 of the 123.915-kc discriminator V4, and an equal negative voltage to appear at pin 1. A 125.415-kc "Volume" signal will produce the same output voltages at V4, but the polarities will be reversed. Similar responses take place in the other discriminator V5 when "Channel Selector" or "TV-Phono" signals arrive.


The 6CM7 relay control tubes V6 and V7 have a fixed -27 volt grid bias obtained from a bias rectifier (the third diode section of the 6BJ7 tube V5). All 6CM7 sections remain cut off until this bias is overridden by a positive signal voltage from one of the discriminators. Then one of the control triodes is driven into conduction, and a relay in its plate circuit is energized when plate current reaches the correct pull-in value. The "On-Off" and "TV-Phono" relays require more current than the other two; therefore, they are controlled by the B sections of the 6CM7's, which are designed for higher values of plate current than the A sections.

AC Power and Interconnecting Circuits

The "Son-r" control receiver, which is fastened to the top edge of the vertical TV chassis, has its own power transformer and 6X4 rectifier (V8). The "Manual-Remote" switch, a customer control on the back of the TV set, controls the application of power to the "Son-r" receiver. **IMPORTANT**—if the TV is turned off by means of the remote relay, the control receiver will continue to operate until the main on-off switch on the TV cabinet is turned off or the set is unplugged.

AC power wiring associated with the 8G1 is relatively simple.

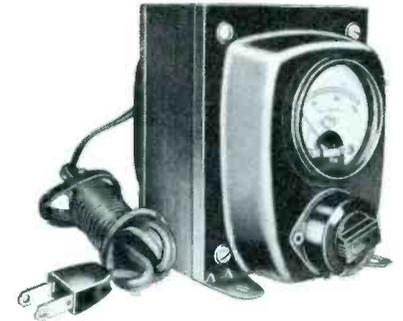THE HANDIEST TESTER YOU CAN HAVE IN YOUR KIT



THE ACME ELECTRIC T-8394 VOLTAGE ADJUSTOR

Smart service men, who like to save time and make more money by doing so, are using the Acme Electric T-8394M Voltage Adjustor on every service call. With this unit, varying voltage conditions ranging from 95 to 125 volts input can be simulated. Under these varying voltage conditions defective components that function properly at normal voltage, but cause trouble at low voltage or over voltage can be located and replaced.

And, in thousands of instances, service customers have insisted on buying this handy unit from the service man so that they may maintain a normal voltage at the set and enjoy top TV reception.

Furnished complete: primary cord and plug; secondary receptacle; accurate meter indicates output voltage; control switch regulates secondary voltage. Compact, inexpensive.

See this at your dealers.


ACME ELECTRIC CORPORATION
94 WATER STREET CUBA, NEW YORK

Acme Electric
TRANSFORMERS

SAVE UP TO 22%

on a genuine Argos Tube Caddy... newly designed "Pacemaker" models for the thrifty buyer... ruggedly built with Argos


Craftsmanship in Cabinets

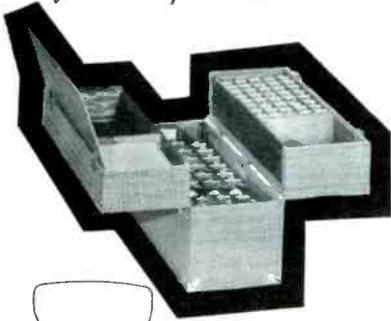

Pacemaker
tube caddy

TC-100
\$12.35

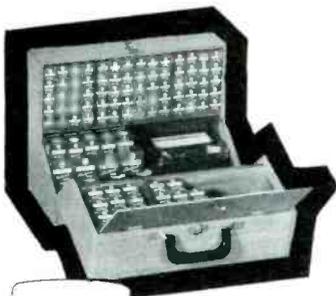Quickly pays for itself. Holds up to 262 tubes, plus tools, meter, etc. Same size as Argos "Carry-All" Tube Caddy.



Pacemaker Jr.
tube caddy

TC-200
\$8.95

Low cost Tube Caddy for quick trips. Holds up to 143 tubes, plus tools, meter, etc. Same size as Argos Tube Caddy "Junior."

®Registered TM of the Argos Products Co., originator and sole manufacturer. Ask your Distributor NOW!

Argos

PRODUCTS COMPANY
GENOA, ILLINOIS

Also wall and corner baffles, hi-fi speaker enclosures and kits.

The control receiver is connected to the TV chassis through an 11-pin plug and socket. During remote operation, the primary power circuit of the TV set is completed through the contacts of the "On-Off" relay, across pins 5 and 7 of the plug. The primary winding of the 8G1 power transformer is wired across pins 5 and 3, and the contacts of the channel selector relay are connected to the tuning motor via pins 3 and 9. A shielded lead from the volume control switch is plugged into an audio jack on the TV chassis.

Space does not permit a detailed description of the complex interconnections between the 8F1 and other units in the deluxe combination receiver, but the most important features should be pointed out. The AC line cord is connected to the 8F1 chassis. The remote receiver, TV, and hi-fi unit have separate power transformers, and one side of each is connected directly to one side of the AC line. Several switches and relays are employed to complete the power circuits to the various chassis. To operate the 8F1, its "Remote-Manual" switch and a separate "Remote On-Off" switch on the TV chassis must both be in the remote position.

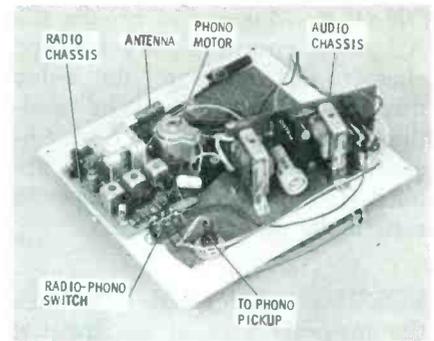


Fig. 3. Bottom view of motorboard, Rockland transistorized radio-phonograph.

If the 8F1 is operating, an "On-Off" keying signal will automatically turn on the power to the hi-fi amplifier, which in turn supplies power to the radio tuner. Power is also furnished to either the TV chassis or the phono motor, depending on the position of the "TV-Phono" relay contacts on the 8F1.

The manual TV power switch operates independently of the 8F1. When it is turned on, AC power energizes a special "TV Off-On" relay which closes the TV and hi-fi primary power circuits—provided that a special "TV-Radio" switch on the radio chassis is in the TV position.

Service Hints

Like their counterparts in other wireless remote systems, the

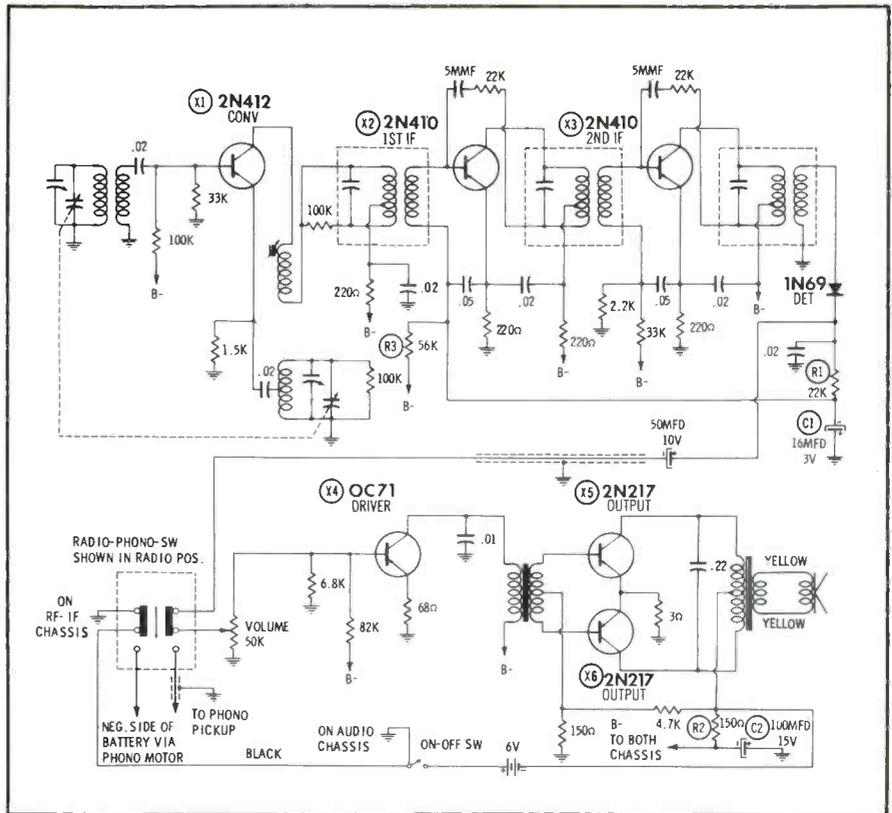


Fig. 4. Schematic of Rockland radio-phonograph.

"Son-r" relay control circuits require a positive signal of pre-determined strength in order to actuate the relays. In case a relay fails to operate, a quick troubleshooting check can be made by monitoring the grid voltage of the control tube while keying the transmitter. If this voltage does not rise enough to bring the tube out of cutoff, your next move should be to check the transmitter, microphone, and receiver tubes. If the grid voltage is OK, check the relay circuit itself.

Repeated or unwanted relay operation may indicate a loss of the fixed bias on the control tubes, or possibly regeneration or other troubles in the receiver circuits.

Realignment of the control receiver should be attempted only as a last resort. It is seldom required after changing tubes, but it might become necessary if the critical lead dress of the components in the tuned circuits is disturbed.

Portable Transistor Radio-Phonograph

A cordless transistorized radio and 45-rpm phonograph powered by four Size D flashlight batteries has been placed on the market by Rockland Precision Mfg., Orangeburg, N. Y. As shown in Fig. 3, all circuitry is mounted on two printed-board chassis fastened to the underside of the phono motorboard. One chassis includes a converter, two IF stages and a diode detector, while the other has a low-level audio driver and a push-pull audio output stage. Battery power is applied to the audio chassis at all times when the unit is in operation. Depending on the position of the "Radio-Phono" switch, power is also furnished to either the RF-IF chassis or the miniature phono motor. A second set of contacts on this switch connects the proper signal input to the audio amplifier.

The batteries are contained in a cardboard tube fastened to the case of the unit, and they can be taken out by unscrewing a metal retaining plate on one end of the case. Mounted in the other end of the case is a round 3" speaker.

A chassis schematic is shown in Fig. 4. In the unit studied, all transistors were RCA solder-in

Another Britener *First!*



Any Set-Any Tube
UNIVERSAL



Series or Parallel
C-BRITE



Grid Defects
RESTORER



110° Shell Base
C-BRITE



110° Button Base
C-BRITE



Lowest Cost-Parallel
VU-BRITE



Lowest Cost-Series
VU-BRITE



3 Gun Kine
COLD BRITE



110°
by the LEADER
Perma-Power

Designed by engineers for quality, low cost, small size. Attractively packaged for quick, easy selling... consistently profitable.

The Perma-Power TV Tube Britener design is original and unique. It is fully protected by U. S. Patent No. 2,757,316.

Perma-Power COMPANY
3100 N. ELSTON AVE. CHICAGO 18, ILL.
Manufacturers of Electronic Equipment Since 1928

VACO HAS "TWINS"

TWIN DRIVERS!
TWIN USES!


Two combination tools that make your servicing work easier... faster!

No. 1... 5/32" insulated blade screw driver with 1/4" nut driver. Pocket clip handle.

No. 2... genuine Phillips No. 1 point driver with 1/4" nut driver. Pocket clip handle.



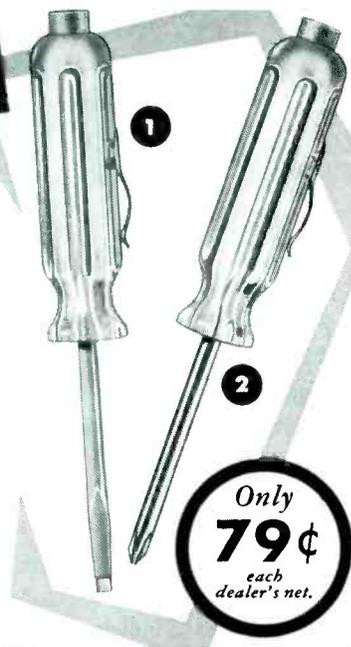Look for them on this handsome VACO Display Card at your favorite Parts Jobber.



Only **79¢**
each
dealer's net.

VACO PRODUCTS CO. 317 E. Ontario St., Chicago 11, Ill.

In Canada: Atlas Radio Corp., Toronto 19, Ontario

HOW TO SELL MORE **RECOTON** REPLACEMENT NEEDLES

JUST TELL YOUR CUSTOMERS THESE 6 IMPORTANT FACTS...

1. There is no such thing as a permanent needle.
2. There is a RECOTON needle for every purpose and every pocketbook.
3. RECOTON needles are the finest in fidelity, quality and value.
4. RECOTON needles are always priced lowest.
5. RECOTON replacement needles are mounted on large, easy-to-read cards.
6. All replacement data and installation instructions are printed right on the cards.

And remember — RECOTON backs you up with the most complete line in the industry, compelling advertising and intensive merchandising; plus most convenient reference, model numbering and inventory control.

Insist on RECOTON.



In Canada:
Quality Records, Ltd.,
Toronto

A RECOTON PLUS: Self-selling stylus merchandiser. 100 power microscope lets customers check their own styli. Increases sales, profits, turnover!

Recoton CORPORATION
52-35 Barnett Avenue Long Island City 4, N. Y.

types except X4, which was an Amperex Type OC71. All are of the p-n-p variety, requiring that the collectors be negative with respect to the emitters. Accordingly, the positive terminal of the battery stack is grounded and B— is applied to the collector circuits. DC bias voltages for the bases of all transistors except the first IF amplifier are obtained from separate voltage dividers between B— and ground. Values of the divider resistors were chosen to establish the correct forward bias voltage between base and emitter as well as the correct value of base current.

The first IF stage is AGC-controlled. Detector output voltage is filtered by R1 and C1 and fed back to the base circuit of the IF transistor X2. Since the average DC output voltage of the detector in this receiver is positive, the AGC voltage becomes more positive when signal strength increases. This control voltage opposes the fixed negative bias fed from B— through R3 and tends to reduce the difference between base and emitter voltages. As a result, the forward bias of the stage is reduced when a strong signal is received, and the transistor conducts less heavily.

X1 serves as both oscillator and mixer. A tunable feedback coil in the collector circuit is coupled to the oscillator tank in the emitter circuit. Note that the collector of each RF and IF transistor is returned to B— by way of a tap on the primary winding of the interstage transformer. This is for impedance-matching purposes, required because the primary impedance of a suitable IF transformer is higher than the output impedance of the transistor.

A neutralization network consisting of a 5-mmf capacitor and a 22K-ohm resistor is included in each IF stage. In addition, the collector circuits of the converter and first IF each contain a 220-ohm resistor and a .02-mfd capacitor which are included mainly for decoupling purposes.

In the audio amplifier, note that the collectors of the push-pull output transformer are supplied with B— voltage direct from the battery. The B— supply for all other circuits is filtered by R2 and C2. ▲

Looking for a
Steady?
(a steady pattern, that is!)



only
\$19.95
NET

The MODEL 50-A INDUCTIVE WINDING TESTER removes all guesswork in giving you a sharp, continuous pattern which accurately checks as small as a one turn short in:

1. Flyback Transformers
2. Yokes
3. Vertical Blocking Osc.
4. Vertical Output Trans.
5. Audio Transformers
6. And many others!

B & M ELECTRONIC MFG. CO.
2516 Dodge Avenue
Fort Wayne, Indiana



PROVEN:

Soldering tips
last 10 times
as long with

SAVBIT
A SPECIAL ALLOY AVAILABLE ONLY IN ERSIN
Multicore
FIVE-CORE SOLDER



Copper solder tips
last 900% longer
when you use
economical SAVBIT!

Sold only through radio parts jobbers
MULTICORE SALES CORPORATION PORT WASHINGTON, N. Y.

Shop Talk

(Continued from page 10)

reflector. Variation of either variable will have a direct effect on the response characteristics of the combination.

Now, when the reflector is positioned very close to the dipole, the voltage which the reflector radiates to the dipole is practically equal to the signal voltage which the dipole picks up directly, and is close to 180° out-of-phase with it.* As a result, the two cancel, and very little is left for the receiver to receive via the transmission line. As the reflector is moved away from the dipole, the time taken by the signal to travel to and from the reflector also enters the picture, and this alters the phase of the reflector signal reaching the dipole. This additional time lag serves to move the signals closer together in phase (at the dipole) and a strengthening occurs, raising the voltage in the dipole and producing a gain.

Beyond the optimum distance, the gain starts to drop off because the phases of the two signals in the dipole are again tending to move farther apart. Now, however, the drop-off is slow because with increased distance, less of the re-radiated reflector signal reaches the dipole. In other words, the coupling between the two wires decreases and less energy is transferred between them.

If the reflector completely eliminated one of the two original dipole lobes, the gain of the array would double or rise about 6 db. Since a small portion of the second lobe remains, the gain is somewhat less, on the order of 4 or 5 db.

Another effect that a reflector has on a dipole is to lower its impedance. It was noted previously that a dipole, by itself, had an impedance of 72 ohms. When a reflector is positioned near it, this value drops, becoming lower

* It might help the reader to understand this action by comparing it to two closely coupled circuits. In such circuits, the voltage in the primary and the induced voltage in the secondary differ by 180°

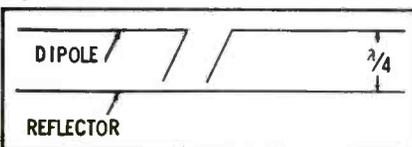


Fig. 4. Dipole with director.

as the reflector is moved closer. With a spacing of .2 wavelength, the dipole impedance decreases to about 40 ohms. If a 72-ohm transmission line is used, much of the signal gain achieved through the use of a reflector is lost. With a 300-ohm line, no gain at all is obtained. In both cases, however, the unidirectional directivity remains, and in this sense the combination of dipole and reflector is beneficial.

Dipole and Director

If we take a dipole and mount nearby a second parallel wire which is somewhat shorter, we obtain a combination which also essentially possesses a unidirectional response. Note from Fig. 4,

(Advertisement)

latest **JACKSON** tube test data

TUBE TYPE	MODEL 848			MODEL 115/715/661			CATH.	SHORTS	E.	Z
	FIL. D.	PLATE	TEST	FIL.	X	PLATE				
3CY5	2.3	A234	AC156	20YZ	2.3	5	23	2LMR		
3CY5	3.0	A234	AC156	20YZ	3.0	5	23	2LMR		
4CY5	5.0	A234	AC156	20YZ	5.0	5	23	2LMR		
6CY5	6.3	A234	AC156	20YZ	6.3	5	23	2LMR		
6DT5	6.3	129	B346	50VW	6.3	4	10	7JKS		
TUBE TYPE	SEC.	A.	B.	C.	D.	MODEL 49				
3CY5	P	2.3	3	2X	156	7	28			
3CY5	P	3.0	3	2X	156	7	28			
4CY5	P	5.0	3	2X	156	7	28			
6CY5	P	6.3	3	2X	156	7	28			
6DT5	P	6.3	4	6	139	7	5			

Latest Chart Form 648-19, 115/715/661-10, 49-4

R-COLUMBIA CHEATER CUBES*
STOPS FURNITURE MOVING and OUTLET HUNTING

CHEATER CUBES + TV SERVICE CORD
GIVES YOU BOTH TYPE INTERLOCK CONNECTIONS PLUS 5 ELECTRICAL OUTLETS

Now Only 79¢ EACH
DEALER NET

THE R-COLUMBIA TV Service Cord
R-Columbia TV Service Cord combined with Cheater Cubes A and B gives you an answer to almost every interlock problem which will be encountered in field servicing. Manufactured of 10-2 wire, UL approved, R-Columbia Service Cord eliminates extra cords and cuts out useless weight in service caddys. ONLY 79¢ dealer net.

THESE ARE THE FAMOUS SERVICEMAN-DESIGNED PRODUCTS OF **R-COLUMBIA** HIGH WOOD ILLINOIS

Modernize!... Simplify!... your billing methods with the

No. 225
RADIO · TV · APPLIANCE
REPAIR ORDER

THE COMPLETE SERVICE FORM for shop jobs or home calls. 50 triplicate sets in sales book style with detachable numbered claim check. "Not-At-Home" note and appointment schedule. Promissory note on backer #2 and #3. Guarantee and performance guarantee on back copy #1. 15 lines on face, 16 on backers. Blank heading for your rubber stamp. Imprinted with 4 line imprint on special order at attractive prices. See it at your parts jobber!

OR WRITE FOR FREE SAMPLE #225 FORM
FREE 24 PAGE CATALOG TOO! showing complete line of Service Reports, Statements, Job Tickets, Phone Message Books, File Systems, Warranties, etc.

Oelrich Publication 4308 N. MILWAUKEE AVE. CHICAGO 41, ILLINOIS
Please send **FREE** SAMPLE #225 FORM CATALOG

Name _____
Address _____
City _____ Zone _____ State _____

95¢ per book

ABOUT THE COVER

Dad is at work and Mom suffers from acrophobia. Who among us can ignore a child's tears? March is traditionally kite-flying month (although April weather is better), so you just might run into the situation pictured on this month's cover and get a chance to play the good Samaritan. (All in the cause of good customer relations, of course.)

however, that now the parasitic element, called a director, is in front of the dipole. In this position, the director first receives the incoming signal. This signal is partially absorbed, then re-radiated, with the dipole receiving some of the re-radiated signal. The phase of this signal is such that it combines favorably with the directly-received signal at the dipole, thereby providing a greater signal than if the dipole had been employed alone.

As with the dipole and reflector, the gain obtainable using a

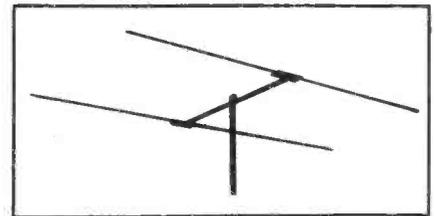


Fig. 5. Commercial dipole and reflector by Channel Master Corp.

director depends on the distance between this element and its dipole. (We are assuming that the director length is fixed.) A graph showing this variation is illustrated in Fig. 3. Note that it rises to a peak at about 0.1 wavelength and thereafter decreases slowly, for the most part being less than the gain provided by a reflector. Thus if we are to use a director profitably, it must be positioned at 0.1 wavelength from the dipole.

The close positioning, however, poses a rather serious problem because at this distance, the coupling between director and dipole is so high that the impedance of the dipole is reduced to only 10 ohms. If we attempted to use any sort of conventional transmission line with this combination, the mismatch would be so great that relatively little signal would be transferred to the line. For this reason and also because a dipole with director provides a uniform response over a very narrow band of frequencies, this combination is seldom found; rather, the dipole and reflector is used. For the record, however, a dipole-director combination will possess a directivity pattern similar to that of a dipole-reflector assembly.


When using this simple combination of dipole and reflector, reception is limited to a fairly narrow range of frequencies. For example, if we cut the dipole so that it will be resonant at the center of the low VHF band (channel 4), then it will oper-

CLEARER SHARPER PICTURES

at **LESS** cost!

Now

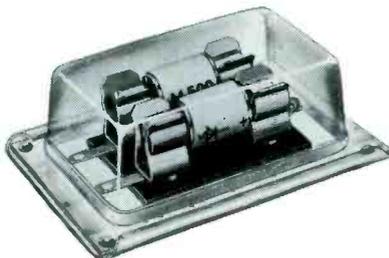Tarzian M-500 SILICON RECTIFIERS
Will Cost You **LESS** Than
SELENIUM RECTIFIERS
rated at 200 Milliamperes or higher



... and, as an extra bonus, Tarzian M-500 Silicons rated at 500 milliamperes give you wider safety margin. Send for your copy of the latest Service Information.

Sarkes Tarzian, INC.

Rectifier Division
DEPT. PF1, 415 N. COLLEGE AVE.
BLOOMINGTON, INDIANA

In Canada: 700 Weston Rd., Toronto 9, Tel. Rogers 2-7535 • Export: Ad Auriema, Inc., New York City

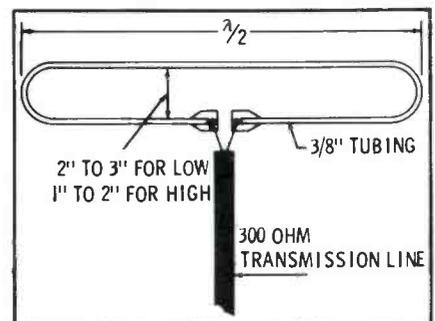


Fig. 6. Appearance of a folded dipole.

PF REPORTER • March, 1958

new Video Master

TV "HIGH GAIN" TUNED
R.F. DEMODULATOR PROBE

The D-200 VIDEO MASTER is a HIGH-GAIN (6CB6 I.F. Stage) Demodulator Probe arranged with two independently-calibrated and adjustable tuned I.F. bands for both 20 and 40 MC receivers. A frequency-compensated, low-impedance detector stage provides EXCELLENT FREQUENCY RESPONSE.

- ✓ ISOLATES ANY TV I.F. PROBLEM TO A STAGE
Allows signal analysis at any plate, grid, or tube shield.
- ✓ TESTS ANY TV TUNER DIRECTLY
High-gain allows signal analysis at tuner.
- ✓ EXCELLENT I.F. ALIGNMENT INSTRUMENT
Tunable characteristics provide alignment technique—no generators.

ADVANCED

TECHNIQUES OF TV TROUBLESHOOTING

by DOSS

ELECTRONIC RESEARCH



Model D-200
only \$19.95
NET

ate satisfactorily for channels 2 through 6, but on the two end channels, the gain will be easily less than half that achievable on channel 4. If it should happen that the signals at either or both extremes are weak, then it might become necessary to employ two separate antennas or a single antenna having a broader bandwidth. The simple dipole, even with reflector, is best reserved for those localities where the signals are strong and the over-all bandwidth (encompassing all desired channels) is not too wide.

Commercially, dipole antennas with reflectors appear as shown in Fig. 5. The rods are generally formed of hollow aluminum and are usually pinched at their ends to prevent the accumulation of moisture and dirt on the inside. The supporting rod is also constructed of aluminum, although its diameter is larger in order to provide the necessary rigidity and strength for support. Either a 72-ohm coaxial cable or 72-ohm flat twin lead should be used for connecting the antenna to the receiver. However, if a mismatch

of impedances is unavoidable, it should be made in accordance with the strength of the signal as indicated in last month's coverage.

The Folded Dipole

The folded dipole is formed using a conventional dipole with an equivalent additional section connected in parallel with it. See Fig. 6. By this simple act, the impedance, as seen at the antenna terminals, is increased by a factor of 4. Thus, the characteristic impedance of a folded dipole is 300 ohms (75 × 4).

The reason for this impedance increase cannot be explained simply, but the following will serve our purpose. Resistance of a circuit is determined by the current that flows when a voltage is impressed across it. In a comparison of the plain and folded dipole, we find that injecting the same power in both will produce less current flow in each section of the folded dipole. Actually, with parallel paths, the current flow is cut in half. From the equation for power ($P = I^2R$) we see that cutting I in half reduces the power to one-fourth. For the same received power, a current reduction of $\frac{1}{2}$ at the feed point of the antenna means that the resistance here has increased by a factor of 4.

The higher impedance of the folded dipole enables it to be used with a high impedance transmission line. This is advantageous because line loss is inversely proportional to line impedance for any given set of conditions. This is clearly brought out by the graph in Fig. 7. In each instance No. 20 A.W.G. wires were used to form

DOSS Sweep Analyzer MODEL D-100



Tests all TRANSFORMERS in TV Sweep Circuits.

Detects even one-turn shorts utilizing oscilloscope and NEW, extremely sensitive principle of measurement.

Checks: FLYBACKS, YOKES, VERT. BLOCKING, VERT. OUT. and others.

SENSATIONAL NEW TV INSTRUMENT only \$16.95 NET

DOSS Slave Oscillator MODEL D-500



Quickly isolates any Sweep or Sync. failure to CONTROL STAGE, OSCILLATOR STAGE, or OUTPUT CIRCUIT. SUBSTITUTES COMPLETELY for receiver Horizontal or Vertical Sweep Oscillator. Controls include: VERTICAL HOLD, VERTICAL HEIGHT, AND HORIZONTAL HOLD.

only \$19.95 NET

free Most distributors have extra quantities of DOSS Instruction Books. These are informative, well illustrated and complete.

ASK FOR YOURS TODAY—

ABSOLUTELY FREE! or write
DOSS ELECTRONIC RESEARCH
820 BALTIMORE
KANSAS CITY 5, MISSOURI


Please send me your free instruction books on:

- D-200 Video Master
- D-100 Sweep Analyzer
- D-500 Slave Oscillator

Name _____

Address _____

City and State _____

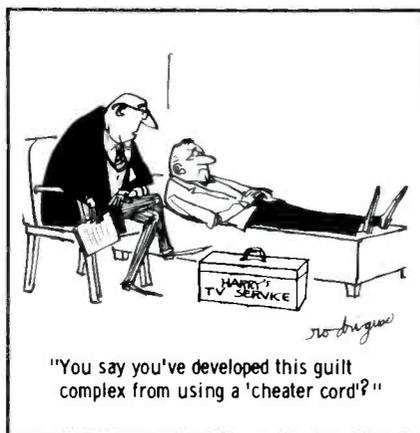

"You say you've developed this guilt complex from using a 'cheater cord'?"

RADIO AND TV
SERVICEMEN

Here's the perfect companion
to any tester!

Model GCT-8
**GRID
CIRCUIT
TUBE
TESTER**

(U.S. Pat. No. 2,784,372)



Quickly spots grid errors and leakage

Here's the perfect accessory for every serviceman! Checks critical "Control-Grid" condition of vacuum tubes faster, more accurately than any other tester! As many as eleven simultaneous checks—automatically! Stops guessing, substitution checking, and costly re-checks. Electron-eye tube indicates following faults at a glance: Control Grid Emission Excl., Grid-to-Cathode Shorts, Gaseous Condition, Cathode-to-Heater Shorts, Grid-to-Heater Shorts, Grid-to-Plate Shorts, Plate-to-Heater Shorts, Grid-to-Screen Shorts, Screen-to-Heater Shorts, Heater-to-Suppressor Shorts, Grid-to-Suppressor Shorts.


Truly portable—may be stored and carried anywhere. Complete, easy-to-assemble kit

\$19.95
net

Wired and factory tested.. **\$29.95** net

Write today for free literature
SECO MANUFACTURING CO.
5015 Penn Ave. So., Mpls., Minn.

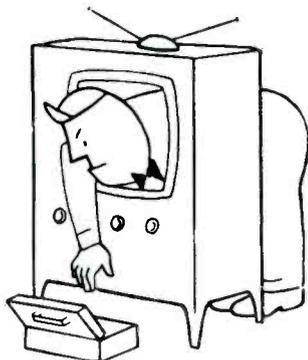repairing TV sets?
for the right part to do
the best job



you'll find it
faster in the

MASTER

new 1958 edition—world's largest
electronic catalog only **\$3.50** at
your local parts distributor—now

Free! Write for Panel Lamp Chart.

THE RADIO-ELECTRONIC MASTER
60 MADISON AVE., HEMPSTEAD, N. Y.

suitable open wire transmission lines having the impedances indicated. Note that with increasing impedance, the line loss at each frequency drops.

Another advantage of a folded dipole is its broader bandwidth. While it still produces maximum output at the frequency for which it was cut, the drop-off from this point is not as sharp as for a simple dipole. This is desirable for all types of television signals and is especially significant when color signals are to be received.

Finally, a folded dipole can be attached directly to the antenna supporting mast without upsetting the electrical balance or the operation of the unit. The connection should be made at the center of the folded rod; it is here that the voltage is zero and a ground at this point does not disturb the voltage or current distribution in the array.

The over-all length of the folded dipole is governed by the same design formula used for the simple dipole. The spacing between the two rods is not important as long as this distance is small compared to the over-all length of the array. In commercial units, this spacing is on the order of two or three inches. The figure-eight response pattern of the folded dipole is often converted to a unidirectional pattern by the addition of a reflector (Fig. 8). The latter element has the same effect on a folded dipole that it does on the simple dipole.

Popular versions of this array are shown in Fig. 9. Fig. 9A shows an in-line assembly designed for


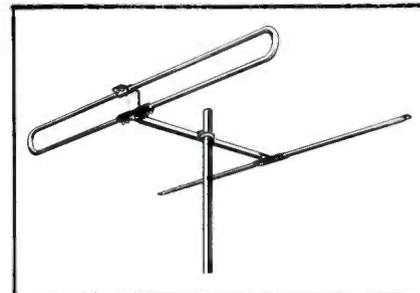


Fig. 8. Photograph of a commercial folded dipole and reflector made by JFD.


high-low VHF coverage, wherein the large folded dipole, being positioned behind the small dipole, serves as its reflector. Then a reflector rod is placed behind the large dipole and serves as its reflector. The two sections are connected by a short length of transmission line to combine their signals, and then a single 300-ohm line carries the full signal to the receiver. Fig. 9B shows another high-low arrangement whereby two antennas are mounted on the same mast and properly matched with a connecting harness.

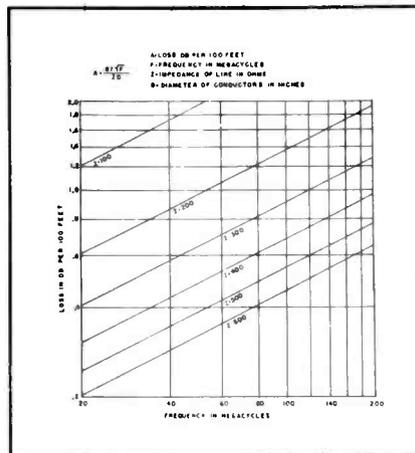The higher impedance of the folded dipole makes it attractive for use in larger arrays (such as the yagi) where the addition of re-



(Courtesy RCA Review)

Fig. 7. Computed loss of open wire transmission lines using No. 20 A.W.G. wire.

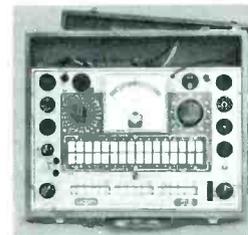

SAVE 4 WAYS

WITH A
JACKSON 648A
DYNAMIC® TUBE TESTER

SAVE ON TIME

Jackson 648A, with fingertouch sequence switching is the world's fastest fully-flexible tube tester.

SAVE ON CALL BACKS

Jackson 648A features famous Jackson Dynamic® circuit, for reliable tests on all radio, tv and most industrial tubes.

SAVE ON INVESTMENT

Jackson 648A is one of the lowest cost, fully-reliable, fully-wired testers on the market.

SAVE ON UPKEEP


Jackson 648A is fully flexible, provides for almost any new development in tube design. No cards to lose. No sea of sockets to confuse you. 23 Separate heater voltages—more than any other tester. Latest test data published monthly on page 65, PF Reporter.



Famous "Service-Engineered"
Test Equipment

JACKSON ELECTRICAL INSTRUMENT COMPANY
16-18 S. Patterson Boulevard • Dayton 2, Ohio

by
every
test

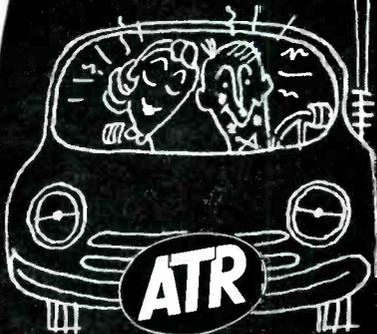

ATR
is **BEST!**



ATR AUTO
RADIO
VIBRATORS

Have Ceramic Stack Spacers

**A COMPLETE LINE
OF VIBRATORS**

Designed for Use in Standard
Vibrator-Operated Auto Radio
Receivers. Built with Precision
Construction, featuring Ceram-
ic Stack Spacers for Longer
Lasting Life. Backed by more
than 22 years of experience in
Vibrator Design, Develop-
ment, and Manufacturing.



"A" Battery Eliminators, DC-AC
Inverters, Auto Radio Vibrators



✓ NEW MODELS ✓ NEW DESIGNS ✓ NEW LITERATURE

See your jobber or write factory

AMERICAN TELEVISION & RADIO CO.
Quality Products Since 1931
SAINT PAUL 1, MINNESOTA—U. S. A.


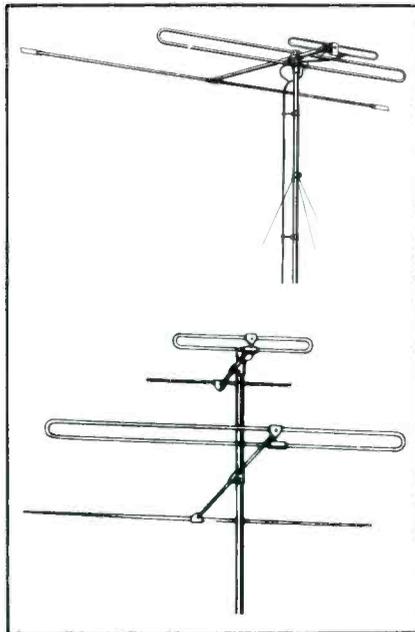


Fig. 9. Folded dipole in-line (Amphenol)
and high-low (Cornell-Dubilier) arrays.

flectors and directors would soon reduce the impedance of a simple dipole to a value too low to be practical. By starting with the higher impedance of a folded dipole, it is possible to achieve a final value which is still within a workable range. We will investigate such arrays later.

One final word about reflectors. These can be made more effective if a mesh screen is employed in place of a rod. The only reason screens are not used very much at VHF is because they tend to be quite bulky. A mesh structure, incidentally, is as effective as a solid metallic sheet, provided that the mesh openings are on the order of 0.2 of a wavelength or less at the highest operating frequency. Screen dimensions are not critical, but the edges should extend for a short distance beyond the dipole elements.

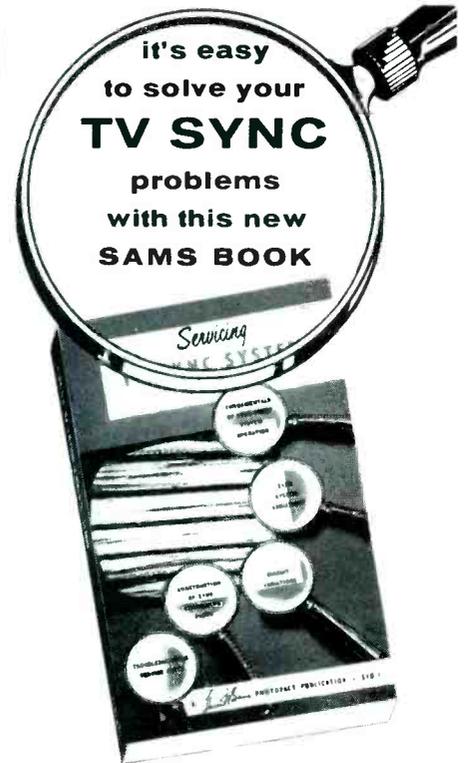

"Servicing TV Sync Systems"

by Jesse Dines

Valuable time-saving book for Service Technicians. Covers fully the theory of operation, circuit function and circuit variations of the 18 different types of sync systems used in TV receivers. Explains various types of sync separator, horizontal and vertical oscillator, and horizontal AFC circuits used in sync systems. Methods of analyzing and troubleshooting these circuits are supported by actual picture tube photos and waveforms illustrating types of sync troubles. Includes valuable data on oscillator coils, transformers and printed electronic circuits used in sync systems. Has chapter on practical servicing hints. This book will definitely help the technician to better understand and more easily service any type of sync system trouble. Written clearly and simply for quick and easy understanding. 320 pages; 221 illustrations, 5 1/2 x 8 1/2".

PRICE **\$3.95**
ONLY

SEE THIS MONEY-EARNING BOOK
AT YOUR ELECTRONIC PARTS
DISTRIBUTOR OR MAIL COUPON
TO HOWARD W. SAMS...

FREE TRIAL COUPON

Howard W. Sams & Co., Inc., Dept. 3-C8
2201 E. 46th Street
Indianapolis 5, Indiana

Send me Jesse Dines' book "Servicing TV Sync Systems" for 10 days FREE examination. In 10 days I will pay for the book, plus small delivery cost, or return postpaid.

We pay delivery costs if you remit with this coupon. Same return privilege.

Name.....

Address.....

City..... Zone..... State.....
(outside U.S.A. priced slightly higher)

SENCORE
Another Sencore Time-Saver
Handy "36"
 R-C
Substitution Unit



"36"
 Most Often Needed Components At YOUR Fingertips!

3 pole, 12 position switch individually selects one of the "36" components for direct substitution.

Contains:

- ★ 12—1 watt 10% resistors from 10 ohms to 5600 ohms
- ★ 12—½ watt 10% resistors from 10K ohms to 5.6 megohms
- ★ 10—600 volt capacitors from 100-mmf. to .3mf.
- ★ 1—10mf., 450V Electrolytic
- ★ 1—40mf., 450V Electrolytic

For Shop, Lab, or outside service
 COMPLETELY ISOLATED
 ONLY \$12.75 DEALER NET

POPULAR SENCORE PRODUCTS

- Transistor Tester
- Leakage Checker
- Filament Tester
- Voltage Regulator
- Bias Supply

AVAILABLE AT ALL PARTS DISTRIBUTORS!
SENCORE SERVICE
 INSTRUMENTS CORP.
 171 OFFICIAL RD., ADDISON, ILL.

Cut out this ad now for further information.



"You're using my Jensen Needle again, I see."

GUIDE

TO AUTO

BATTERY POLARITIES

This chart provides two basic items of information about the batteries in late-model automobiles: (1) the voltage; (2) the terminal (+ or -) grounded to the car frame.

These simple facts, which can so easily slip a person's mind, are good to have at your fingertips when you are planning a car radio installation or connecting a radio to a bench power supply.

In the chart, the number 6 or 12 opposite each make of auto indicates the correct battery voltage, and the + or - sign designates the terminal that should be grounded.

You'll note that listings of American cars are given only for 1954 and 1955 models, and here's why: Starting in

1956, the U. S. auto industry greatly simplified matters by standardizing on a 12-volt, negative-ground electrical system. The only exception is Willys; 6-volt batteries have been used on all passenger vehicles of this make except the '58 station wagon.

As many foreign cars as possible have been included. Information is given only for current models, which account for the great majority of foreign autos in use in this country. Here's a tip on installing radios in foreign cars: Dealers caution that the car should be brought in to them for adjustment of the voltage regulator. Failure to do so has been known to cause trouble in the car's electrical system.

U. S. CARS	'54	'55
Chevrolet Pontiac	6—	12—
Packard	6+	12+
Buick Cadillac Metropolitan Oldsmobile	12—	
DeSoto Dodge Ford Hudson Lincoln Mercury Nash Plymouth Rambler Studebaker	6+	
Willys	6—	
Chrysler	6+ or 12—	

Practically all U. S. Passenger Cars for '56-'58	12—
--------------------------------------------------	-----


SOME POPULAR FOREIGN CARS (Current Models)	
Alfa Romeo	12+
Austin	12+
Austin-Healey	12+
DKW	6—
Ford (English)	12+
Hillman	12+
Jaguar	12+
MG A	12+
Mercedes-Benz	12—
Morris	12+
Porsche	6—
Renault	6—
Simca	12—
Triumph	12+
Volkswagen	6—
Volvo	6—

Signal Tracing RF & IF

(Continued from page 15)

check for the presence of signal at all points between the tuner output and the video detector—limited only by the loading effect of his instruments and the sensitivity of his scope and the receiver itself. With a direct probe, we might first examine the composite signal across the detector load, point "A" in Fig. 4. If the signal at this point is weak, distorted, or absent entirely, the next step should be to clamp the AGC line at approximately -3 volts, thus eliminating the possibility of AGC trouble.

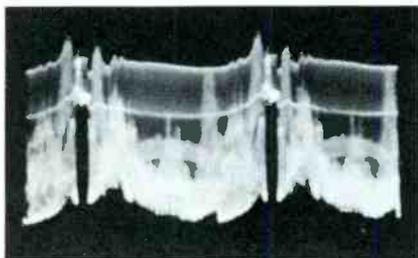Using a general purpose scope, the technician may find it impossible to detect a signal ahead of the 2nd IF stage even in a nor-



(A) Signal at grid of last IF stage.



(B) Signal at grid of first IF stage.

Fig. 5. Waveforms obtained with a detector probe and an oscilloscope.

mally operating receiver. With the use of a suitable scope preamplifier, however, a signal can often be detected at the antenna input terminals, particularly when homing in on a strong local station.

Although this procedure is usually limited by the sensitivity of the scope, in many cases the technician may be able to obtain a usable signal up to the output of the tuner. Fig. 5A represents a typical signal found on the 3rd IF grid of a normally operating receiver while Fig. 5B represents that obtained on the grid of the 1st IF. Notice the reduction in signal amplitude even with the scope gain set at maximum. Using this detector probe method, the technician should try sampling the signal at various IF points in a normally operating receiver before signal tracing a faulty set.

Signal Substitution

Rather than depend on a signal from a local TV station, the technician may prefer to use a signal generator in his signal tracing technique. Regardless of the type of generator used, the technician will have two general procedures to choose from. One is where he uses a direct scope probe at the video detector load and moves the generator lead from point to point, and the other is where he uses a scope detector probe at various points, leaving the generator connected to the input of the RF or IF section. Perhaps the one achieving most success is the method whereby a direct probe is employed and the signal generator applied to various key positions.

Let's first consider the method using a single-frequency generator. Requirements of such an instrument are that it cover the RF and IF range and contain provisions for internal modulation by a lower frequency such as 400 cycles. To trace a signal through the RF circuits of a receiver, checking the operation on all channels, the generator should cover both the high and low bands—54 to 88 mc and 174 to 216 mc. To check only the IF section, however, the instrument need cover only frequencies in the 20- and 40-mc bands.

In connecting the generator for a check of an IF system, the generator frequency is adjusted to approximately the center of the receiver's intermediate frequency and a direct probe from the vertical input terminals of the scope is connected across the video detector load. Internal modulation of the generator frequency is used and a capacitor of from 20 to 50 mmf is placed in series with the "hot" generator lead, the ground lead being connected to the receiver chassis. The series capacitor will lessen the loading or detuning effect of the generator and will also block DC. Never, under any circumstances, connect the generator lead directly to an IF plate, screen or other point of high potential. If you do, a low-voltage resistor or an IF coil may go up in a puff of smoke due to the low impedance path to ground offered by the generator's output circuit.


SUBSTITUTE PARTS WITH-OUT SOLDERING

Quickly with E-Z-Hook "SUB" Connectors Easily

Has 1001 Uses!

NEW E-Z-Hook "SUB" Connectors

Connect a speaker, or

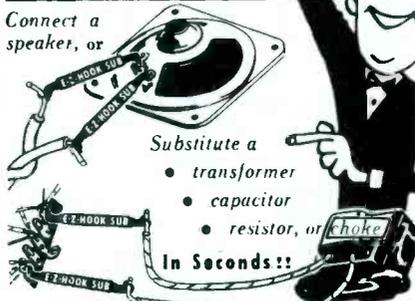

Substitute a

- transformer
- capacitor
- resistor, or choke

In Seconds!!

★ Makes connections instantly!
★ Won't pull off!
★ Insures positive contact!

Saves time, money and parts in servicing, experimenting, instructing and production.

E-Z-HOOK SUB

No. 71-1...SUB...Only 69¢.

Six Colors!- for Easy Lead Identification

E-Z-HOOK TEST PRODUCTS
SAFE • FAST • SURE

ORDER THROUGH YOUR PARTS DISTRIBUTOR
E-Z-HOOK TEST PRODUCTS
Dept. F, 1536 Woodburn Ave.
Covington, Ky.

ask the

"Man-on-the-Roof"

why he prefers

South River



TWO TO A SET



RATCHET TYPE CHIMNEY MOUNT

Model RT (Galv. Banding)
Model RT-ST
(Stainless Banding)

FASTEST, SIMPLEST, MOST CONVENIENT EVER MANUFACTURED — Mounts in 2 simple steps. Completely factory assembled with no eye-bolts, banding clips, nuts, etc., to handle. Furnished with flat-lay, non-coiling banding, heavy gauge embossed, welded steel construction. Forged, heat treated Alum. ratchets.

Write for new catalog

SOUTH RIVER

METAL PRODUCTS CO., INC.

South River, New Jersey

pioneer & outstanding producer of finest line of antenna mounts

**SPOT
INTERMITTENTS
FAST!**



\$89⁹⁵
NET

**NEW
Wintronix
INTERMITTENT
CONDITION
ANALYZER**

Makes any TV or Radio Super-Sensitive to Intermittents & Noisy Components . . .

NO WAITING 

NO "COOKING" 

NO "FREEZING" 

Save valuable time and bench space when troubleshooting intermittents. Just connect output of Model 828 to Radio or TV receiver antenna terminals, and use exclusive "Electro-Wand" (for tubes) or "Electro-Probe" (for components) to quickly pinpoint intermittent or noisy tubes, capacitors, resistors, coils, transformers, defective connections, etc. No direct circuit connection needed.

Special Wintronix circuit immediately makes any receiver super-sensitive to intermittents. Lets you *hear* intermittents through built-in speaker. Reduces callbacks by detecting borderline components *before* they fail.

See the Wintronix Model 828 at your local parts distributor or write for free literature.

**WINSTON
ELECTRONICS INC.**

4312 Main St., Phila. 27, Pa.

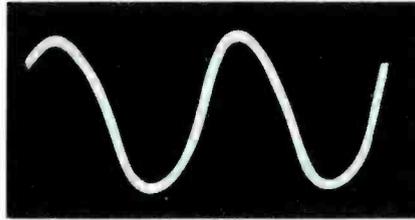


Fig. 6. 400-cycle signal at detector load.

The technician might begin the procedure by first placing the hot generator lead at the input of the video detector, which is shown as point "B" in Fig. 4. If the detector is passing a signal at all, the 400-cycle modulation will appear on the scope screen as shown in Fig. 6 and, providing the video section of the receiver is functioning properly, sound bars should appear on the picture tube screen as pictured in Fig. 7.

Stages preceding the detector can be checked in a like manner by injecting the signal into the IF and mixer grids, points "D," "F," "H," and "J." Under normal conditions, the output of the generator can be reduced as the point of injection is moved closer to the tuner because of the gain produced by each additional IF stage. It may be necessary, however, to vary the frequency of the generator to obtain a satisfactory indication on the scope or picture tube when switching the lead from point to point. The relative amplification of each IF tube can be checked by comparing the peak signal values obtained at the grid and plate.

Operation of the tuner can be checked by adjusting the generator to the center RF frequency of any given TV channel. As an example, suppose we adjust the tuner to receive channel 6, then set the generator frequency to approximately 86 mc and again modulate the carrier with a 400-cycle signal. With the scope connected across the detector load, we then apply the signal to the receiver's antenna terminals, and if the tuner and all succeeding circuits are operative, the 400-cycle modulation will appear on the scope screen as well as on the face of the picture tube.

Using a VTVM

If the technician has a signal generator without provisions for internal modulation, he can sub-

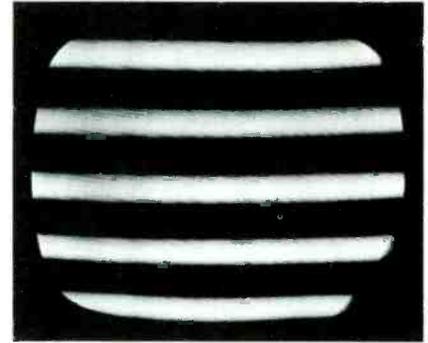



Fig. 7. Sound bars on TV screen produced by generator signal modulated at 400 cps.

stitute a vacuum-tube voltmeter in place of the scope and obtain a relative signal indication by the DC voltage developed at the video detector. In this arrangement, the VTVM is connected across the detector load and the unmodulated RF or IF signal from the generator applied to test points "D" through "K" of Fig. 4. A low DC voltage range of the meter is used and the generator frequency is varied for a maximum signal indication at each point. With the AGC line clamped at a -3 volts, this method of signal tracing is very effective in locating an inoperative stage in either the RF or IF section.


The Sweep Method

While the foregoing procedures are relatively simple and require only a minimum amount of test equipment, they are principally useful in locating weak or completely inoperative stages and are quite limited when it comes to pin-pointing causes of other troubles, such as regeneration, smear, loss of picture detail, etc.

A more complex, yet highly ac-

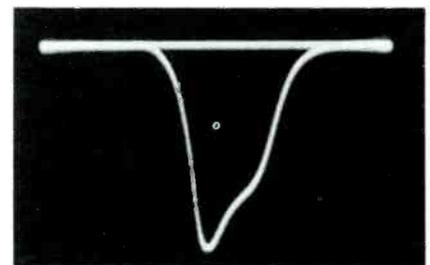

(A) Sweep input at 1st IF grid.

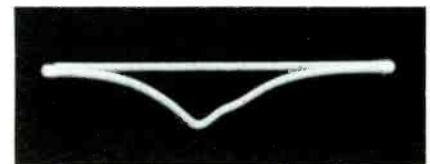

(B) Sweep input at 3rd IF grid.

Fig. 8. Normal IF response curves obtained across the video detector load.

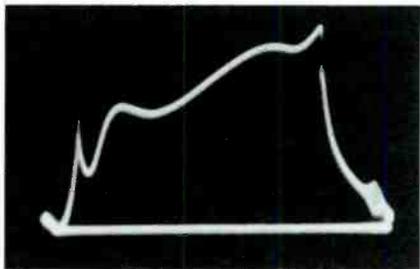


Fig. 9. Abnormal response curve resulting from overloading in the IF strip.

curate, means of tracking down RF and IF troubles is to pass a sweep frequency signal through the system while monitoring the resultant response curve with a scope. This operation is the same as that used for a conventional RF or IF alignment check. The AGC line is clamped, the generator is set to sweep the RF or IF band, a direct scope probe is connected across the detector load and the synchronized sweep voltage from the generator is applied to the horizontal input of the scope.

When checking the IF strip, the RF oscillator should be disabled and a small capacitor placed in series with the hot generator lead. Injecting the sweep signal into the 1st IF under normal conditions, the technician might obtain a response curve similar to that shown in Fig. 8A. Moving the generator lead to the 2nd or 3rd IF grid, the response will change somewhat and will naturally be of less amplitude, as pictured in Fig. 8B.

Using a suitable detector probe with the scope, the frequency response of individual IF circuits can be checked by placing the generator lead on the grid of one stage and the scope probe on the grid of the following stage. If the generator output is too high or if the generator lead is placed directly on an IF grid, the stage involved, or one following, may tend to overload. This condition will usually cause the response curve to reverse in polarity and take on a weird shape such as that shown by the waveform of Fig. 9.

Using a direct probe, the RF response of a tuner can also be determined by placing the scope probe on the grid test point of the mixer stage which is usually made available on top of the tuner. To prevent detuning, a 10K-ohm

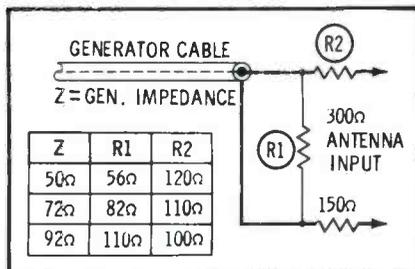


Fig. 10. Diagram of generator to antenna matching pad and resistance table.

resistor might also be placed in series with the scope probe at this point, although this component is often present in the tuner. In this operation, the signal generator should have an output of at least 100,000 microvolts and the scope should have fairly good sensitivity. (Its frequency response need not be considered at all.) For optimum performance, the sweep generator cable should be terminated and matched when connected to the antenna input terminals of the receiver. This can be accomplished by placing a resistive pad in series with the generator leads as illustrated in Fig. 10. The output impedance of the generator cable is represented by "Z" in the small table of Fig. 10, and values of the series and shunt resistors R1 and R2 are given for three typical impedances.

When merely signal tracing, the technician should not attempt to compare his findings with the response curves given in the receiver's alignment instructions. With a little practice on normally operating receivers, however, he should be able to easily locate a defective stage using this sweep signal method.

Other Instruments

Rather than to employ a conventional generator, the technician may prefer to use an instrument especially designed for signal tracing. Generators of this nature often provide simulated TV signals for operating RF, IF, sync, and even sweep circuits.

Specialized scopes incorporating preamplifiers and using an indirect method of coupling or sampling for troubleshooting the RF and IF sections of a TV receiver. Instruments of this select group, however, have distinctive operating procedures too specialized to be covered here. ▲

FOR TOP-O'-CHASSIS SERVICING

locates defective stage in
less than 5 minutes for average
TV receiver.



NEW FROM
Wintronix
MODEL 850
**INDUCED WAVEFORM
ANALYZER**
complete with
"Phantom Probe"
and attachments

ONLY
\$169⁹⁵

Localize troubles in TV, radios, amplifiers, etc., right from the top of the chassis . . . and without making a single direct connection to the circuit! The new Wintronix Model 850 does all this by the modern, easy-to-use Induced Waveform method. Helps you quickly spot those often overlooked tube and circuit defects that mean callbacks or extra troubleshooting.

Simply connect the output of the Model 850 to any scope, then slip the Phantom Detector Probe successively over each tube in the receiver under test. By viewing the waveform of the received signal (from b'dcast station or generator) at each stage, you quickly localize troubles to the offending stage. Works equally well for RF, IF, video, sync, and audio circuits. A real time and trouble-saver for portable TV.

See and try the new Wintronix Induced Waveform Analyzer at your local Wintronix dealer or write for free literature.

**WINSTON
ELECTRONICS INC.,**

4312 Main St., Phila. 27, Pa.

TRANSFORMER NEWS FROM TRIAD

GENERAL CATALOG TR-58

TRIAD

QUALITY ENGINEERED TRANSFORMERS

TRIAD TRANSFORMER CORPORATION
a subsidiary of Litton Industries
4055 Redwood Ave., Venice, California
812 East State St., Huntington, Indiana

TWO NEW TRIAD CATALOGS

Fresh from the printer are your new 1958 TRIAD reference books: the TRIAD GENERAL CATALOG TR-58, containing specifications and prices on 940 TRIAD transformers, including over 100 new items...and the TRIAD TELEVISION REPLACEMENT GUIDETV-58. Get your complimentary copies from your distributor—or write...



Visit our Booth #2244 at the IRE Show

4055 REDWOOD AVENUE,
VENICE, CALIFORNIA
812 EAST STATE STREET,
HUNTINGTON, INDIANA

A SUBSIDIARY OF LITTON INDUSTRIES

Now let's go back to point "A" and see what is happening to the positive half of the signal wave available at the output of the amplifier section. The positive portion of the wave is coupled through C6 to the plate of V1B. The rectified voltage is equal to the peak value of the input signal. Using the VTVM circuit to measure the voltage across C7 will indicate the velocity of the vibration, thereby providing the value of a second factor in the formula for vibration characteristics.

The magnetic pickup previously described is used principally in high frequency sensing units. As shown in Fig. 5A, a permanent magnet is usually used to provide the field for a soft iron core. As long as it is under the influence of the permanent magnet, the core can be used to induce a voltage across the coil. Ultrasonic displacement reverses direction so many times a second that the movement cannot be transmitted to the probe by actual physical contact; instead, shock waves are produced in the coil. Figure 5B shows the compression-expansion effects of shock waves, and under


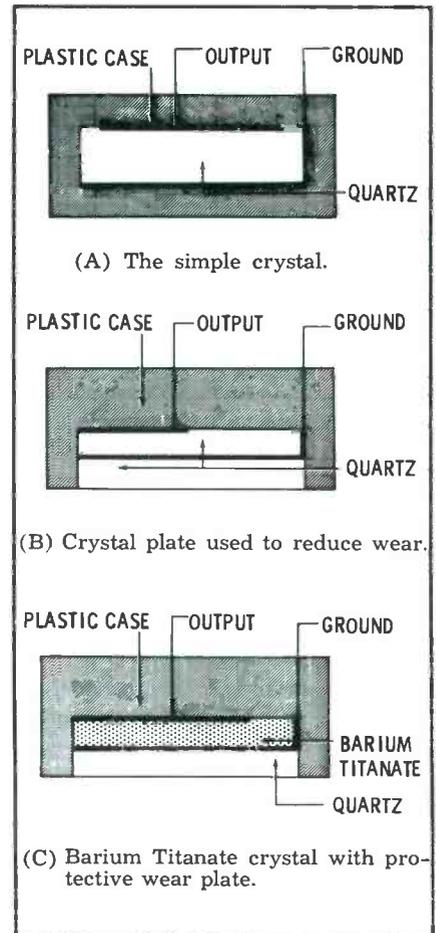


Fig. 6. Three types of crystal pickups.

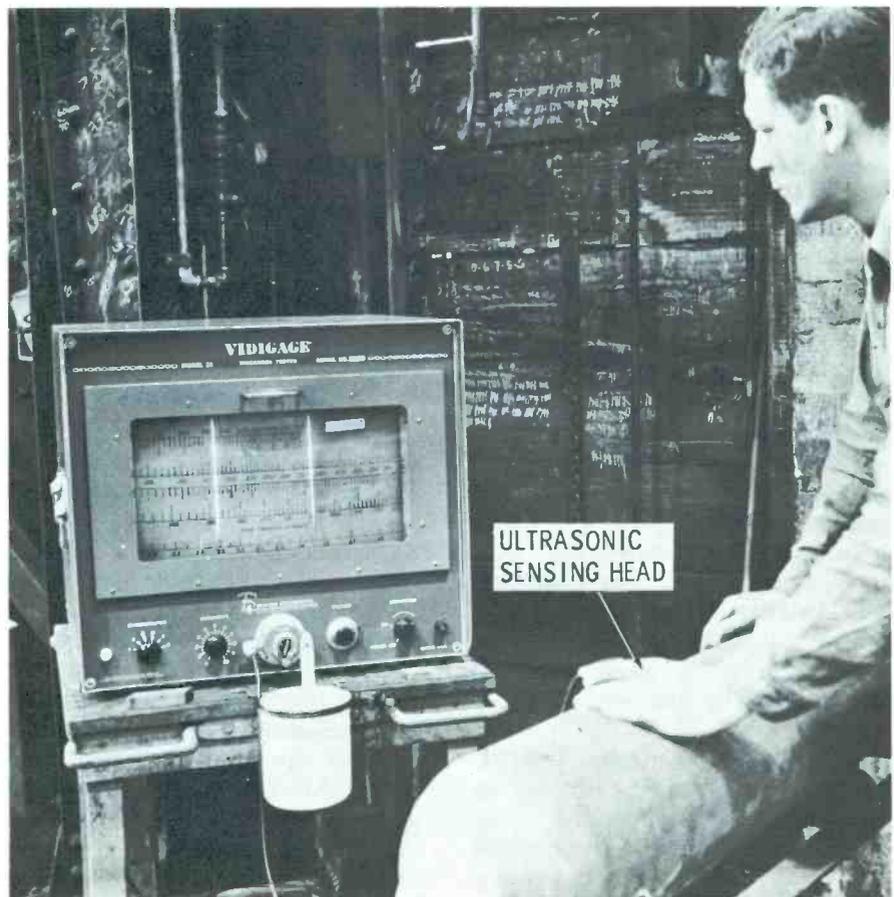

(Courtesy Branson Instruments, Inc.)

Fig. 7. Ultrasonic sensor being used to determine thickness of cylinder.

RADIO AND TV
SERVICEMEN

Troubleshoot TV Deflection
Circuits fast . . . with the



Model FB-4

**FLYBACK CIRCUIT
and INDUCTANCE
ANALYZER**

Checks complete horizontal coil circuit
. . . not just individual components!

Nothing faster! 100% accuracy! Just connect one test lead to plate of the horizontal output tube, ground the other—then without disconnecting anything, rotate control knob and electron-eye tube instantly tells you whether or not flyback transformer and yoke are all right. Resonant frequency and "Q" meter principle used for testing—will not be obsoleted due to variables in engineering design of circuits to be checked.

With self-contained power supply, matched 18" leads. **\$38.95** net



Write today for free literature
SECO MANUFACTURING CO.
5015 Penn Ave. So., Mpls., Minn.

FOR HOUSE CALLS

— it's
HEXA CON

FEATHERWEIGHT

**INSTANT
SOLDER GUN**

FITS TUBE CADDY—Takes Half
the Space of Transformer Guns

**SMALLEST SOLDER GUN
WEIGHS ONLY 8 OUNCES**

— but

**POWER-PACKED AT 150 WATTS
and
SOLDERS IN SECONDS**

No heavy bulky transformer —
sturdy lifetime tip—never wears or
bends—effective spotlight

Model G14 with 1/4" tip — \$7.95
Order from your distributor today

HEXA CON ELECTRIC COMPANY

589 W. CLAY AVE., ROSELLE PARK, N.J.

SERVING INDUSTRY AND CRAFTSMEN
FOR A QUARTER OF A CENTURY


their influence, the core of the coil changes diameter. In this case, induction by the magnetic field takes place as a result of the coil windings moving through the field rather than through motion of the field; however, frequency and magnitude of vibration are transmitted by the field to the coil just the same.

Crystal Transducers


Another type of ultrasonic transducer is the crystal. Transducers use either quartz or barium titanate; but unlike the frequency-controlling crystal used in communications, the ultrasonic crystal is relatively thick, with diameters ranging from 1/2" to 1 1/2". Fig. 6 shows three common constructions for crystal transducers. Fig. 6A is the simplest, with a quartz crystal imbedded in a molded plastic case and silvered on top and bottom to provide contact surfaces for the output leads. Fig. 6B shows a quartz plate used as a contact plate to reduce wear. The sensing element in Fig. 6C is barium titanate, but the protective quartz contact plate is retained.

The signal developed by a crystal is due to the effect deformation has on crystals. A small voltage is formed when a crystal is compressed, twisted, or bent. The crystal develops enough voltage to drive a single stage amplifier which can be used to control a recorder or produce a correction voltage. The reverse is also true; if a voltage is applied to a crystal, it will change its shape or dimensions.

For thickness measurement the crystal is driven by an FM sweep generator. As the resonant frequency of the material is passed over, there is a sharp rise in output current. This signal can be applied to the vertical input terminals of an oscilloscope, and by using the FM modulation signal for horizontal deflection, a frequency response curve of the crystal circuit will be obtained. Each division of the screen along the horizontal axis will correspond to a different frequency; thus, when the generator passes through the resonant frequency, the trace will rise very rapidly and then return to the base line. (This is the same procedure which is used to obtain

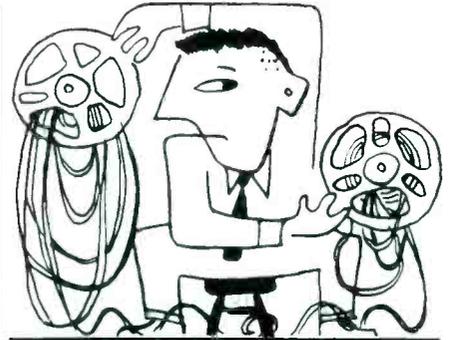

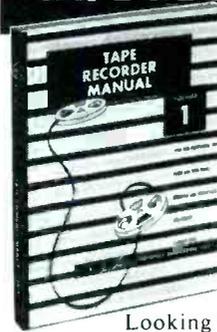**get the straight facts
on current model
TAPE RECORDERS**



Howard W. Sams
**"TAPE
RECORDER
MANUAL"**

VOL. 1

Looking for unbiased facts about various makes of tape recorders? This is the book that shows you the "inside story"—no sales pitches—just down-to-earth descriptions and illustrations of all mechanical and electrical features and how they work.

Sams "Tape Recorder Manual", Vol. 1, covers tape recorders and players produced in 1956 and 1957 by the following manufacturers: Ampex, Bell-Sound, Columbia Records, Ekotape, Ellamac, Magnecord, Silvertone, V-M and Wilcox-Gay.

Presents complete authoritative data on each model: exclusive "exploded" views of all mechanical parts; details of each adjustment and control; complete operating instructions; photographs of all external and internal parts; complete wiring diagrams and replacement parts lists. Includes tips on how to avoid and cure troubles such as wow, flutter, failure to erase and others. Shows you how to disassemble and assemble each recorder and how to check for source of trouble. A valuable book for everyone interested in tape recorder design, operation and servicing. 148 pages; 8 1/2 x 11"; profusely illustrated.

PRICE **\$2.95**
ONLY

SEE THIS AUTHORITATIVE BOOK
AT YOUR SAMS DISTRIBUTOR OR
MAIL COUPON TO HOWARD W. SAM'S

FREE TRIAL COUPON

Howard W. Sams & Co., Inc., Dept. 3-CC8
2201 E. 46th Street, Indianapolis 5, Ind.

Send me Sams "Tape Recorder Manual" Vol. 1, for 10 days FREE examination. In 10 days I will pay for the book, plus small delivery cost, or return postpaid. We pay delivery costs if you remit with this coupon, same return privilege.

Name.....
Address.....
City..... Zone..... State.....
(outside U. S. A. priced slightly higher)





(Courtesy Sperry Products, Inc.)

Fig. 8. This instrument tests quality right on the production line.

IF response curves in TV work.)

The ultrasonic thickness gauge being used in Fig. 7 to indicate the thickness of the tank wall is a sweep generator and oscilloscope all in one. The scope face is covered by a scale, but the two white lines are the vertical pulses representing particular frequencies. The first line is the fundamental resonant frequency of the tank wall. Several scales are provided to enable the operator to check his first-line reading by observing the harmonic line which appears

on the right side of the instrument. The pickup is similar to that illustrated in Fig. 6A; however, the crystal and case has been shaped to fit the curvature of the tank.

Flaw Detection

A slightly different approach is required for flaw detection. Resonance is very useful in thickness tests, but flaws do not affect resonance unless they are fairly large. The Sperry "Reflectoscope" shown in Fig. 8 operates on a time base rather than the frequency base used in the instrument of Fig. 7. Pulses of a particular frequency are transmitted through the unit under test. The pulses travel at a predictable rate through any material, and by sensing the time lapse between the transmitted and reflected pulse, the depth of a flaw can be directly measured. Notice from the scope waveform in Fig. 9 that the flaw stands out almost as well as the reflection from the bottom surface of the piece under test.

While the markers are spaced by frequency, it is a simple matter to convert frequency to time. The


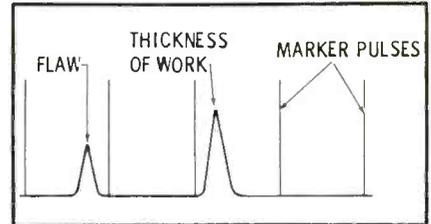


Fig. 9. Waveform obtained on unit of Fig. 8 shows depth of flaw.

formula, $T = 1/F$ shows that one operation will yield the time between marker pulses; thus, when the speed of sound through the substance under test is known, the thickness of the substance and the depth of any flaws can be determined. The markers in Fig. 9 are spaced one microsecond apart, and the speed of sound through this substance is one cm per microsecond. The flaw is located 1.75 cm below the surface, and the piece under test is 3.25 cm thick.

This is only one type of thickness measurement; there are many more. Thickness, width, length, height, and curved dimensions are all extremely important in industrial work. Electronic instruments used to determine these characteristics will be described next month. ▲

SO SAFE!

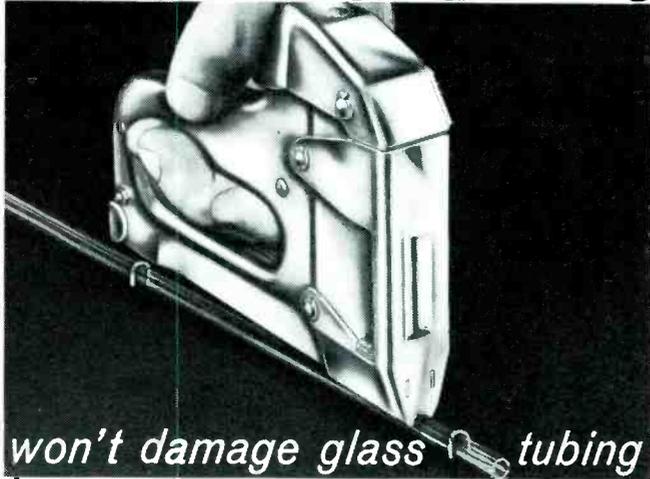

won't damage glass tubing
let alone wire or cable!

ARROW STAPLE GUNS can't damage wire or cable because driving blade automatically stops staple at right height! That's why Arrow Staple Guns are proved safer on jobs all over the country. And Arrow staples have tremendous holding power because they're rosin-coated, have diverging points that lock into wood.

T-25 (shown) for wires up to 1/4" in diameter. (Hi-Fi wire, radiant heating, bell, thermostat, telephone, inter-com, etc.) tapered striking edge gets into tight corners. Uses 3/8", 1/2", and 5/8" staples. List \$15
T-25B For burglar alarm wiring. Drives staples flush . . . List \$15
T-75 For non-metallic sheathed cable, Romex cable or any other object (such as copper tubing) up to 1/2" in diameter. Uses 3/8", 1/2", and 5/8" Arrow staples . . . List \$15

ARROW FASTENER COMPANY, INC.
ONE JUNIUS STREET, BROOKLYN 12, N. Y.

The NEW YEATS "Shorty" STATION WAGON & PANEL PICK-UP appliance dolly



YEATS Model No. 5
Aluminum alloy
Height 47"
Weight 32 lbs.

Only 47" tall, this new YEATS dolly is designed for TV and appliance men who make deliveries by station wagon or panel truck. No need to detach appliance for loading into the "wagon" or pick-up . . . the YEATS "Shorty" will slide into your vehicle with ease.



Folding platform is 13 1/2" x 24 1/2" —attaches instantly. (Platform only) \$9.95.

Has aluminum alloy frame with padded felt front, quick fastening (30 second) strap ratchet, and endless, rubber belt step glide. New YEATS folding platform attachment, at left, saves back-breaking work handling TV chassis or table models. Call your YEATS dealer today!



"Everlast" COVERS & PADS

YEATS semi-fitted covers are made of tough water repellant fabric with adjustable web straps and soft, scratchless white flannel liners. All shapes and sizes—Write.

Furniture Pad

SEND postcard for full information on our complete line TODAY!

YEATS appliance dolly

2103 N. 12th St.




TV Cover

sales co.
Milwaukee, Wis.

PRODUCT REPORT


Subminiature Electrolytics

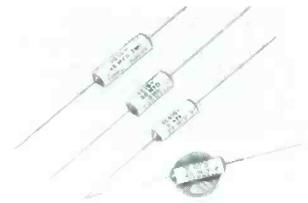

Type EC aluminum-foil electrolytic capacitors made by Cornell-Dubilier Electric Corp., South Plainfield, N. J., are new subminiature units designed for transistorized equipment or low-B+ vacuum-tube circuits. These components are available in working-voltage ratings from 3 to 75 volts DC and in capacitance ratings which range from 1 to 250 mfd, depending on voltage rating. Housed in tubular ceramic cases, they are sealed with a moisture and heat resistant resin. Stable capacitance value, low DC leakage current, and long shelf life are obtained with the use of special materials and processing techniques.

For further information, check 47P on Literature Card.


Chassis-Holding Jig

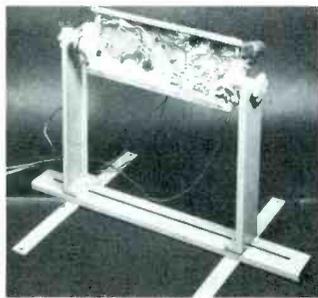

An improved type of chassis jig for use in bench servicing, the "Phono and Radio Repair Stand" (Cat. No. 5212), has been introduced by General Cement Mfg. Co., Rockford, Ill. The chassis to be serviced is suspended between two upright braces which can be adjusted to hold chassis of any length up to approximately 18". The clamps that grip the chassis are secured to the braces by large locknuts; when these are loosened slightly, the chassis can be rotated to any desired position. The opening between the jaws of the clamp is adjusted by turning a knurled locknut, and one jaw is equipped with a rubber insert to provide a non-marring grip.

For further information, check 49P on Literature Card.

Outdoor Antenna Kits

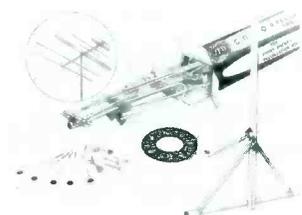

JFD Electronics Corp., Brooklyn, N. Y., is now making its Fireball, Junior-Helix, and Super-Helix Colortennas available in kits that contain all hardware needed for installation. Accessory parts furnished include an aluminum mast with "Tri-Mount" base, 50 feet of twin lead, 6 assorted stand-offs and 3 "self-sealing" nails. Model numbers and retail prices of "Colortenna-Paks" are as follows: Standard Fireball, FB500TP, \$29.95; Gold Anodized Fireball, AB500TP, \$34.95; Standard Super-Helix, RX511TP, \$29.95; Gold Anodized Super-Helix, AX511TP, \$34.95; Standard Junior-Helix, JX311TP, \$24.95; and Gold Anodized Junior-Helix, AX311TP, \$29.95.

For further information, check 48P on Literature Card.

Which one can prove her QUALITY?

Most brands of twin lead look alike! Also, the price brands make the same claims of quality and performance as the top quality brands.

What Reason . . . What Proof

Can you give your customer that he is getting something better when he pays a little more for twin lead?

WITH **Columbia PERMALINE**

Your Customer has the reason

- So GOOD that it's GUARANTEED up to 25 YEARS!
- DISTINCTIVE APPEARANCE
- HIGH MOLECULAR WT. POLYETHELENE
- DEVELOPED AFTER YEARS OF RESEARCH

See Ask him about Permaline — and ask to see the Laboratory Report on weathering studies of Polyethelene.

your Once you "Try" COLUMBIA . . . you'll want to always "Buy" Columbia . . . Because only, but only COLUMBIA gives you a complete guarantee for 25 YEARS.

Jobber

AVAILABLE AT ALL LEADING DISTRIBUTORS

Columbia WIRE & SUPPLY CO. 2850 IRVING PK. RD., CHICAGO 18

REAL VISION

FOR YOUR NEEDLE BUSINESS

The twin 1 mil needle at the same price as the 3 mil-1 mil double — another "first" from the company of "firsts"

Just what you would expect . . . Duotone was first with the 1 mil twin needle. For Duotone foresees your needs and meets them first. Real vision that brings you scores more needle sales! The Duotone 1 mil twin needle for every type cartridge — even foreign makes — sells for the same price as the 3 mil-1 mil double.

DUOTONE COMPANY, INC.

Keyport, New Jersey

In Canada — Charles W. Pointon, Ltd., Toronto

FOR A brighter TV picture



Rely on the tube that has always been specified by leading independent set makers.

Blue Chip Quality

TUNG-SOL[®]
 Magic Mirror Aluminized
PICTURE TUBES

TUNG-SOL ELECTRIC INC., Newark 4, N. J. Sales Offices: Atlanta, Ga.; Columbus, Ohio; Culver City, Calif.; Dallas, Tex.; Denver, Colo.; Detroit, Mich.; Irvington, N. J.; Melrose Park, Ill.; Newark, N. J.; Seattle, Wash.

Signal-Boosting TV Set Coupler



Blonder-Tongue Labs., Inc., Newark, N. J., has announced production of a Model B-23 Two-Set Booster which couples a single antenna to two or three TV sets through a one-tube broadband amplifier. When connected to two receivers, the unit provides a gain of 2 to 6 db instead of the loss encountered in passive couplers. The $6\frac{1}{4}'' \times 3\frac{3}{4}'' \times 2\frac{1}{2}''$ booster is designed to operate continuously, drawing 120 ma at 117 volts AC to supply power to the 6BK7A amplifier circuit. List price is \$23.95.

For further information, check 50P on Literature Card.


CRT Rejuvenator



A redesigned Model RE-2 "Rejuvatube," featuring facilities for testing and rejuvenating 110° and color picture tubes, has been introduced by Central Electronics, Inc., Chicago, Ill. Another new feature of the RE-2 is a gas-test circuit for picture tubes. All circuitry for handling color and 110° tubes is contained in a $2\frac{3}{4}''$ cube-socket adapter that plugs into the main chassis of the unit. This adapter is also available separately as an accessory for Model RE-1 rejuvenators.

For further information, check 51P on Literature Card.

Self-Holding Connector

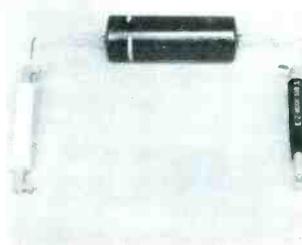

E-Z-Hook Test Products, Covington, Ky., is marketing a new item in its line of self-holding test prods and connectors. Called the "Sub," the unit is $2\frac{1}{2}''$ in over-all length and is equipped with "E-Z-Hook" spring-loaded connectors at both ends.

The principal use of "Subs" is to permit temporary circuit connections, such as component substitution during testing, to be made quickly and easily. These plastic-bodied connectors are supplied in 6 colors at a cost of 69¢ each.

For further information, check 52P on Literature Card.

DC Microammeter



A portable vacuum-tube microammeter (Type WV-84B) has been introduced by the Components Division of RCA, Camden, N. J. A bridge circuit consisting of two 3S4 tubes and two $22\frac{1}{2}$ -volt batteries is employed to measure

weak currents, and a choice of 6 meter ranges with full-scale readings of 0.01 to $1,000 \mu\text{a}$ is offered. The meter produces only slight loading of the circuit under test; voltage drop across the instrument at

full-scale deflection is only 0.5 volt. Leads from the external circuit are attached to the "High" and "Low" jacks on the front panel, with the lead carrying the higher potential being connected to the "High" terminal.

The instrument can be used as a voltmeter when external multiplier resistors (supplied with unit) are placed in series with one of the test leads. Extremely high input resistance of 100 megohms per volt on the 1- and 10-volt ranges and 10 megohms per volt on the 100-volt range minimizes loading of critical circuits.

By adding an external 90-volt battery, the user can operate the WV-84B as an ohmmeter to measure extremely high resistances up to 90,000 megohms.

For further information, check 53P on Literature Card.

Feed-Through Resistor-Capacitor



Centralab, A Division of Globe-Union, Inc., Milwaukee, Wis., has introduced a new feed-through version of its Tube-R-Cap combination resistor and capacitor—Cat. No. 732—designed principally for

antenna filter applications in TV tuners. Both the resistor and capacitor are incorporated in a ceramic tube $\frac{7}{16}$ " long and .190" in diameter. Capacitance ratings available range from 400 to 1,000 mmf (guaranteed minimum value) at 1,000 WVDC, and resistance values from 300K ohms to 1 megohm can be supplied.

For further information, check 54P on Literature Card.

Low-Ripple DC Supply




Electronic Instrument Co., Inc. (EICO), Long Island City, N. Y., offers a new Model 1060 Battery Eliminator and Charger which features improved filtering of the output voltage. The following specifications apply to the 0-16 volt

DC range: Output rating—continuous, 6 amps; intermittent, 10 amps. Ripple at 10 amps—1.5%. Specifications for the 0-8 volt DC range include: Output rating—continuous, 10 amps; intermittent, 20 amps. Ripple at 10 amps—4.5%. Price is \$38.95 in kit form or \$47.95 if factory-wired.

For further information, check 55P on Literature Card.

Soldering Tips

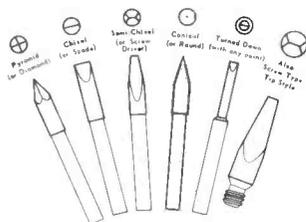

Hexacon Electric Co., Roselle Park, N. J., has developed a new "Xtradur" replacement tip for heavy-duty soldering irons, which is put through a special multiple-coating process that enables the shank of the tip to

repel solder. This feature prevents solder from running off the working surface of the tip onto the shank, and thus enables the tip to last longer under hard use. Shown in the picture are several of the 40 different sizes and shapes of tips available.

For further information, check 56P on Literature Card.

FOR A brighter



profit picture

Rely on the tube that has always been a favorite with leading independent service dealers.

Blue Chip Quality
TUNG-SOL[®]
RECEIVING TUBES

TUNG-SOL makes All-Glass Sealed Beam Lamps, Miniature Lamps, Signal Flashers, Picture Tubes, Radio, TV and Special Purpose Electron Tubes and Semiconductor Products.

March, 1958

Advertisers	Page No.
Acme Electric Corp.	61
Admiral Corp.	47
American Television and Radio Co. (ATR)	69
Amphenol Electronics Corp.	48
Argos Products Co.	62
Arrow Fastener Co., Inc.	76
Astron Corp.	6
B & K Mfg. Co.	7, 26
B & M Electronic Mfg. Co.	64
Blonder-Tongue Labs.	33
British Industries Corp.	64
Bussmann Mfg. Co.	19
CBS-Hytron	21
Centralab, A Div. of Globe-Union, Inc.	45
Chicago Standard Transformer Corp.	59
Clarostat Mfg. Co., Inc.	35
Columbia Wire & Supply Co.	77
Cornell-Dubilier Electric Corp.	37, 38, 39
Delco Radio Div., General Motors Corp.	25
Doss Electronic Research	67
DuMont Labs., Inc., Allen B.	27
Duotone Co., Inc.	77
EICO	32
Electro-Voice, Inc.	11
Electronic Publishing Co.	24
E-Z-Hook Test Products	71
General Cement Mfg. Co.	58
Gernsback Library, Inc.	49
Hexacon Electric Co.	75
International Resistance Co. (IRC)	2nd cover
JFD Electronics Corp.	1
Jackson Electrical Instrument Co.	65, 68
Jensen Industries, Inc.	70
Jensen Mfg. Co.	31
Krylon, Inc.	44
Littelfuse, Inc.	4th cover
Mallory & Co., Inc., P. R.	54, 55
Mastra Co.	57
Merit Coil & Transformer Corp.	50
Oelrich Publications	65
Oxford Components, Inc.	51
Perma-Power Co.	63
Pyramid Electric Co.	28
Radiart Corp.—Cornell-Dubilier Electric Corp.	38, 39
RCA Electron Tube Division	3rd cover
R-Columbia Products Co., Inc.	65
Raytheon Mfg. Co.	9, 46
Recoton Corp.	64
Sams & Co., Inc., Howard W.	29, 69, 75
Sarkes Tarzian, Inc.	66
Seco Mfg. Co.	36, 68, 75
Service Instruments Corp.	24, 50, 70
South River Metal Products Co.	71
Sprague Products Co.	2
Stevens-Walden, Inc.	49
Tobe Deutschmann Corp.	40, 41
Triad Transformer Corp.	74
Triplett Electrical Instrument Co.	43
Tung-Sol Electric, Inc.	78, 79
United Catalog Publs., Inc.	68
Utah Radio Products Corp.	56
Vaco Products Co.	63
Ward Products Corp.	23
Webster Electric Co.	8
Westinghouse Electric Co.	53
Winegard Co.	4-5
Winston Electronics, Inc.	72, 73
Workman TV, Inc.	36
Xcelite, Inc.	51
Yeats Appliance Dolly Sales Co.	76

ACCESSORIES

- 1P. *E-Z-HOOK*—A convenient reference sheet titled "How to Build the Five Most Useful Scope Probes," with schematic, mechanical component layout, etc. See ad page 71.
- 2P. *PERMA-POWER*—Brochure describing new 110° tube briteners. See ad page 63.

ANTENNAS

- 3P. *AMPHENOL*—Sales aids and technical data on new "VLF-I" indoor TV antenna. See ad page 48.
- 4P. *JFD ELECTRONICS*—1958 TV antenna catalog. See ad page 1.
- 5P. *TELCO (G-C)*—Catalog No. A-58 shows a complete range of over 100 different types of antennas. See ad page 58.

ANTENNA DISTRIBUTION

- 6P. *BLONDER-TONGUE*—Master TV specification folder, form AS-18. See ad page 33.

BOOKS

- 7P. *GERNSBACK*—Descriptive literature on Gernsback library books. See ad page 49.

BUSINESS FORMS

- 8P. *OELRICH*—24-page catalog pictures and describes 29 popular business forms, sales aids, and record systems. See ad page 65.

CAPACITORS

- 9P. *CENTRALAB*—Bulletin on new "Ultra-Kap," micro-miniature ceramic-disc capacitor for low-voltage uses which require extremely high capacities and low power factors. See ad page 45.
- 10P. *CORNELL-DUBILIER*—Free kit of molded "MYLAR" capacitors. See ad page 37, 38, 39.
- 11P. *SPRAGUE*—"The ABC's of Ceramic Capacitors"—a brochure covering both theory and applications of these components. See ad page 2.

COMPONENTS

- 12P. *IRC*—DLR-57A, Form S-035A Replacement Parts Catalog. See ad 2nd cover.

CHEMICALS

- 13P. *KRYLON*—Catalog pages describing crystal-clear rust release, dulling spray, spray enamels, varnish sprays, and metal primers. See ad page 44.
- 14P. *R-COLUMBIA*—Bulletin #23 on Fono Magic, a compound of special rubber and carbide that eliminates turntable slipping and dragging and keeps automatic changers cycling properly. See ad page 65.

FUSES

- 15P. *BUSSMANN*—Complete TV Fuse Guide, Form TVC, shows types and ampere ratings of fuses used in various TV sets. See ad page 19.
- 16P. *LITTELFUSE*—Up-to-date cross reference card showing LC fuses and list prices. See ad 4th cover.

GENERAL CATALOGS

- 17P. *UCP*—Information on "1958 Radio-Electronic Master," detailing the 150,000 products catalogued in this buying guide. See ad page 68.

PICTURE TUBES

- 18P. *DUMONT*—Picture tube data chart. See ad page 27.

POWER SUPPLIES

- 19P. *ACME*—Variable Voltage Adjustor Catalog VA-312. See ad page 61.

PHONO NEEDLES

- 20P. *JENSEN INDUSTRIES*—Assorted Dealer Aids. See ad page 70.

RESISTORS

- 21P. *CLAROSTAT*—No. 58 Distributor catalog of resistor products for radio, TV and other electronic applications. Form No. 755300010. See ad page 35.
- 22P. *WORKMAN TV*—#CS 40 replacement guide on CANDOHM resistors. See ad page 36.

SERVICE CASE

- 23P. *MASTRA*—Complete data on "Tote-master," a new convertible master tube and tool tote box with room for over 360 tubes plus tools and equipment. See ad page 57.

SOLDER

- 24P. *BRITISH INDUSTRIES*—Brochures on Multicore "SAHIT" Alloy and Multicore 5-core Solder. See ad page 64.

SPEAKERS

- 25P. *ELECTRO-VOICE*—Bulletin #211 gives complete story on CPD's, coaxial P.A. projectors. Includes data on diffraction horns, increased coverage, polar patterns and features of the CDP line. See ad page 11.
- 26P. *OXFORD COMPONENTS*—1958 general catalog. See ad page 51.
- 27P. *UTAH RADIO*—16-page S-157 catalog plus ABC's of Reproducers catalog. See ad page 56.

TEST EQUIPMENT

- 28P. *AFFILIATED TV LABS*—Catalog sheets, literature, and sales plans for servicemen about U-Check-Em "40" automatic tube testers.
- 29P. *B & K*—Bulletin AP10 gives information on B & K Dyna-Scan Model 1050 Portable Video and Audio Generator that transmits picture or pattern and sound at any time to any number of TV sets. Also bulletins on other B & K equipment. See ads pages 7 & 26.
- 30P. *B & M MFG.*—One-page flyer describing the inductive winding tester and its functions. See ad page 64.
- 31P. *DOSS*—Details on D-100 Sweep Analyzer, D-200 Video Master and D-500 Slave Oscillator. See ad page 67.
- 32P. *EICO*—12-page catalog shows how to save 50% on electronic test instruments and hi-fi equipment in both kit and factory-wired form. See ad page 32.
- 33P. *HICKOK*—Descriptive brochure on new "Cardmatic" portable tube tester priced for the TV technician.
- 34P. *SECO MFG.*—Information on TV tube testing and analyzing TV deflection circuits. See ads pages 36, 68, and 75.
- 35P. *SERVICE INSTRUMENTS*—New LC3 Leakage Checker literature. See ads pages 24, 50, and 70.
- 36P. *TRIPLETT*—Literature describing new 630-APL volt-ohm-milliammeter. See ad page 43.
- 37P. *WINSTON*—One-page flyer on full line of equipment. See ad pages 72 and 73.

TOOLS

- 38P. *ARROW FASTENER*—16-page multi-color catalog No. 13 of complete Arrow line, giving full details on stapling machines, gun tackers, hammer tackers, gun tacker kits and staples. See ad page 76.
- 39P. *CBS-HYTRON*—New CBS Tool Catalog PA-6. See ad page 21.
- 40P. *STEVENS-WALDEN*—Catalog on "Spintites" and "Grip Spintites." See ad page 49.
- 41P. *VACO*—Catalog on specialty service tools for radio-TV work. See ad page 63.
- 42P. *YEATS*—4-page catalog describing appliance dolly and padded covers for delivering TV sets. See ad page 76.
- 43P. *XCELITE*—Illustrated catalog on full line plus literature on new products. See ad page 51.

TRANSFORMERS & COILS

- 44P. *MERIT*—Catalog No. 5811 illustrates and describes more than 900 replacement items. See ad page 50.
- 45P. *CHICAGO STANDARD*—100-page TV Transformer Replacement guide, cross-referenced for over 7,000 chassis of 98 manufacturers. See ad page 59.

WIRE

- 46P. *WRIGHT STEEL*—Catalog sheet and folder including description and sizes of wire strand.

SUPPLEMENT TO SAMS FEBRUARY 1958 MASTER INDEX

**Covers PHOTOFACT Set Numbers 390 through 393 Released
in MARCH, 1958**

This Supplement is your index to new models covered by PHOTOFACT in March 1958. For model coverage prior to this date see the Same Master Index dated February 1958. Use this Supplement with the Sams Master Index— together they are your complete index to PHOTOFACT coverage of over 30,000 receiver models.

Set No.	Folder No.	Set No.	Folder No.	Set No.	Folder No.	Set No.	Folder No.	Set No.	Folder No.
ADMIRAL		GENERAL ELECTRIC—Cont.		METEOR		OLYMPIC—Cont.		RCA VICTOR—Cont.	
Chassis 3J1	392-5	●21T1539, -UHF, 21T1540, -UHF,		●7144 [Ch. 528.50060, 62, 63, 64,		●17TU93, 17TU94 [Ch. GU, GUU]		●14PD8053, U, 14PD8054, U, 14PD-	
●Chassis 17F1	367-13-5	21T1541, -UHF, 21T1542, -UHF,		65, 66, 67)	389-3	378-14-5	8055, U, 14PD8057, U [Ch.	
●T18A11, T18A12, T18A13	367-13-5	21T1543, -UHF, 21T1544, -UHF		●7145 [Ch. 528.50070, 71, 73, 74,		Ch. DY	391-2	KCS111C, D)	37-15-5
3114, 3J16 [Ch. 3J1]	392-5	(“U2” Line)	391-1	75)	389-3	Ch. CT, GTU	378-14-5	●14PT8021, U, 14PT8022, U [Ch.	
AIRLINE		●24C1660, -UHF, 24C1661, -UHF		●7146 [Ch. 528.50060, 62, 63, 64,		Ch. GU, GUU	378-14-5	KCS111A, B)	371-15-5
GAA-2642B, GAA-2643B	384-6	(“U2” Line)	391-1	65, 66, 67)	389-3			●17D8185, U, 17D8186, U, 17D-	
GTM-1109A	392-6	●24C1670, -UHF, 24C1671, -UHF		●7147 [Ch. 528.50070, 71, 73, 74,				8187, U [Ch. KCS109C, D]	392-3
●WG-4041A	376-20-5	(“U2” Line)	391-1	75)	389-3			●17PD8093, U, 17PD8094, U, 17PD-	
●WG-4051A	376-20-5	HOFFMAN		●7180 [Ch. 528.50060, 62, 63, 64,				8096, U, 17PD8099, U [Ch. KCS-	
●WG-5041A	376-20-5	●B1231, U [Ch. 332, U]	393-1	65, 66, 67)	389-3			109C, D]	392-3
●WG-5051A	376-20-5	●B1241, U [Ch. 332, U]	393-1	●7181 [Ch. 528.50070, 71, 73, 74,				●17PT8071, U, 17PT8072, U [Ch.	
ARVIN		●B1251, U [Ch. 332U, 333]	393-1	75)	389-3			KCS 109A, B)	392-3
956T1 [Ch. 1.42400]	391-5	●B3081 [Ch. 419]	321-15-5	Ch. 528.50060, 528.50062, 528-				●21CDB725, U, 21CDB727, U [Ch.	
5578 [Ch. 1.43500]	393-6	●B3321, U [Ch. 332U, 333]	393-1	50063, 528.50064, 528.50065,				CTC7A, B)	379-15-5
Ch. 1.42400	391-5	●B3364, U [Ch. 332, U]	393-1	528.50066, 528.50067, 528-				●21CDB875, U, 21CDB877, U, 21CD-	
Ch. 1.43500	393-6	●K1231, U [Ch. 332, U]	393-1	50070, 528.50071, 528.50073,				8777, U [Ch. CTC7A, B]	379-15-5
CHALLENGER		●K1241, U [Ch. 332, U]	393-1	528.50074, 528.50075	389-3			●21CD8865, U, 21CD8866, U, 21CD-	
CHA33, Y	391-6	MOTOROLA						8867, U [Ch. CTC7C, D]	379-15-5
CORONADO		TR-89R, T [Remote Control Unit]						●21CD8885, U, 21CD8886, U, 21CD-	
●TV3-9402A	385-13-5							8888, U [Ch. CTC7C, D]	379-15-5
●TV3-9450A	382-15-5							●21CD8906, U, 21CD8907, U [Ch.	
●TV3-9455A, TV3-9456A	382-15-5							CTC7A, D)	379-15-5
●TV3-9460A, TV3-9461A	382-15-5							●21CD8926, U, 21CD8927, U [Ch.	
●TV2-9465A, TV2-9466A	384-17-5							CTC7E, F)	379-15-5
●TV2-9470A, TV2-9471A	384-17-5							●21D8281, U, 21D8282, U [Ch.	
●TV2-9475A, TV2-9476A	384-17-5							KCS116A, B)	382-15-5
●TV2-9480, TV2-9481A	384-17-5							●21D8305, U, 21D8306, U, 21D-	
●TV2-9485A, TV2-9486A	380-12-5							8307, U [Ch. KCS116A, B]	382-15-5
CRESCENT								●21D8525, U, 21D8526, U, 21D-	
A-640A, B	391-7							8527, U, 21D8528, U [Ch.	
CROSLEY								KCS108C, D]	390-2
●F-24PDBH, PDBU, PDMH, PDMU [TV								●21D8545, U, 21D8546, U, 21D-	
Ch. 414, 414-1 and Radio Ch.								8547, U [Ch. KCS108C, D]	390-2
362-3] [See Photofact Servicer]								●21D8565, U, 21D8566, U, 21D-	
	390							8567, U [Ch. KCS108E, F]	390-2
G-200BD, EY, MY, WT [Ch. 200GA,								●21D8588, U [Ch. KCS108C, D]	390-2
GT] [See Photofact Servicer]								●21D8605, U, 21D8607, U, 21D-	
	392							8608, U [Ch. KCS108C, D]	390-2
●H-21LPKBF, H-21LPKB [Ch. 468,								●21D8628, U [Ch. KCS116C, D]	382-15-5
469] [See Photofact Servicer]								●21RD8525 [Ch. KCS108H]	390-2
	391							●21RT8202 [Ch. KCS113H]	375-18-5
●H-21LPKMF, H-21PKMU [Ch. 468,								●21RT8425 [Ch. KCS113K]	375-18-5
469] [See Photofact Servicer]								●21T7112, U, 21T7113, U [Ch. KCS-	
	391							98A, C)	347-14
Ch. 200GA, 200GT [See Photofact								●21T7117, U [Ch. KCS98A, C]	347-14
Servicer]								●21T7152, U, 21T7153, U [Ch.	
Ch. 362-3 [See Photofact Servicer]								KCS98A, C]	347-14
	390							●21T7352, U, 21T7355, U, 21T7357,	
Ch. 414, 414-1 [See Photofact Ser-								U [Ch. KCS98E, F]	347-14
vicer]								●21T7157, U [Ch. KCS98A, C]	347-14
Ch. 468, 469 [See Photofact Ser-								●21T7375, G, GU, U, 21T7377, H,	
vicer]								GU, U [Ch. KCS98B, K, L, M]	
	391							●21T8202, U, 21T8205, U, 21T8207,	
DAVID BOGEN								U [Ch. KCS113P, R]	375-18-5
L60	391-8							●21T8265, U, 21T8267, U [Ch.	
L300	392-8							KCS113A, B)	375-18-5
EMERSON								●21T8375, U, 21T8376, U, 21T8377,	
●1282 [Ch. 120380H]	386-15-5							U [Ch. KCS113P, R]	375-18-5
●1283 [Ch. 120381M]	386-15-5							●21T8395, U, 21T8397, U [Ch.	
●1284 [Ch. 120380H]	386-15-5							KCS113P, R]	375-18-5
●1285 [Ch. 120381M]	386-15-5							●21T8405, U, 21T8407, U [Ch.	
●1286 [Ch. 120388H]	386-15-5							KCS113P, R]	375-18-5
●1287 [Ch. 120389M]	386-15-5							●21T8425, U, 21T8426, U, 21T8427,	
●1420 [Ch. 120377C]	386-15-5							U, 21T8428, U [Ch. KCS113E, F]	
●1421 [Ch. 120370G]	386-15-5							375-18-5	
●1424 [Ch. 120377C]	386-15-5							●21T8445, U, 21T8447, U, 21T8448,	
●1425 [Ch. 120370G]	386-15-5							U [Ch. KCS113E, F]	375-18-5
●1426 [Ch. 120369C]	386-15-5							●21T8465, U, 21T8466, U, 21T8467,	
●1428 [Ch. 120369C]	386-15-5							U, 21T8468, U [Ch. KCS113E, F]	
Ch. 120369C, 120370G, 386-15-5								375-18-5	
Ch. 120377C	386-15-5							●21T8485, U, 21T8486, U, 21T8487,	
Ch. 120380H, 120381M, 386-15-5								U [Ch. KCS113E, F]	375-18-5
Ch. 120388H, 120389M, 386-15-5								●24D8655, U, 24D8657, U [Ch.	
FIRESTONE								KCS108C, D)	390-2
4-A-174	393-8							●24D867A, U, 24D867H, U [Ch.	
FISHER								Ch. KCS108C, D, E, F, H	390-2
TR-1	391-9							Ch. CTC7A, B, C, D, E, F	379-15-5
GENERAL ELECTRIC								Ch. KCS108C, D, E, F, H	390-2
●17P1326, 17P1327 (“M3” Line)	383-3							Ch. KCS109A, B, C, D	392-3
●17P1331, 17P1334, 17P1335 (“M3”	383-3							Ch. KCS111A, B, C, D	371-15-5
Line)	383-3							Ch. KCS113A, B, E, F, H, K	375-18-5
●21C1545, -UHF, 21C1547, -UHF,								Ch. KCS116A, B, C, D	382-15-5
21C1548, -UHF, 21C1549, -UHF,								Ch. RC-1168A	390-9
21C1550, -UHF, 21C1551, -UHF,								Ch. RS-165	383-11
21C1552, -UHF, 21C1553, -UHF,									
21C1554, -UHF, 21C1555, -UHF,									
21C1556, -UHF, 21C1560, -UHF,									
21C1562, -UHF, 21C1564, -UHF									
(“U2” Line)	391-1								

THIS IS YOUR LATEST INDEX SUPPLEMENT!
FOR COMPLETE PHOTOFACT LISTINGS
USE IT WITH THE FEBRUARY 1958 MASTER INDEX!

THROW AWAY
ALL OTHER SUPPLEMENTS

NOTE: PCB Denotes Production Change Bulletin. ● Denotes Television Receiver. S Denotes Schematic Coverage Only.

Set No.	Folder No.	
SHERWOOD		
S-1000 II	390-10	
SILVERTONE		
7114 (Ch. 528.51040) (See Photofact Servicer)	393	
7116 (Ch. 528.51040) (See Photofact Servicer)	393	
7120 (Ch. 528.51040) (See Photofact Servicer)	393	
7122 (Ch. 528.51040) (See Photofact Servicer)	393	
7124 (Ch. 528.51040) (See Photofact Servicer)	393	
7128 (Ch. 528.51040) (See Photofact Servicer)	393	
7130 (Ch. 528.51040) (See Photofact Servicer)	393	
7136 (Ch. 528.51040) (See Photofact Servicer)	393	
7172 (Ch. 528.51040) (See Photofact Servicer)	393	
7190 (Ch. 528.51040) (See Photofact Servicer)	393	
7192 (Ch. 528.51040) (See Photofact Servicer)	393	
7777 (Ch. 528.53190)	391-3	
8009, 8010, 8011, 8012 (Ch. 132.42800)	391-12	
8021, 8022, 8023 (Ch. 528.53040)	392-10	
8102AQ, CL, YL (Ch. 528.50125)	389-3	
8104CH, CO (Ch. 528.50125)	389-3	
8106 (Ch. 528.50125)	389-3	
8110, 8112 (Ch. 528.50144)	389-3	
8114 (Ch. 528.51100, 102, 104)	390-3	
8115 (Ch. 528.51110, 112, 113)	390-3	
8116 (Ch. 528.51100, 102, 104)	390-3	
8117 (Ch. 528.51110, 112, 113)	390-3	
8150, 8152 (Ch. 528.50144)	389-3	
8154 (Ch. 528.51100, 102, 104)	390-3	
8155 (Ch. 528.51110, 112, 113)	390-3	
8156 (Ch. 528.51100, 102, 104)	390-3	

Set No.	Folder No.	
SILVERTONE—Cont.		
8157 (Ch. 528.51110, 112, 113)	390-3	
8158 (Ch. 528.51100, 102, 104)	390-3	
8160 (Ch. 528.51140, 142, 143)	390-3	
8161 (Ch. 528.51150, 152, 153)	390-3	
8162 (Ch. 528.51140, 142, 143)	390-3	
8163 (Ch. 528.51150, 152, 153)	390-3	
8182 (Ch. 528.51100, 102, 104)	390-3	
8183 (Ch. 528.51110, 112, 113)	390-3	
8184 (Ch. 528.51140, 142, 143)	390-3	
8185 (Ch. 528.51150, 152, 153)	390-3	
8186 (Ch. 528.51140, 142, 143)	390-3	
8187 (Ch. 528.51150, 152, 153)	390-3	
8188 (Ch. 528.51140, 142, 143)	390-3	
8190, 8190A (TV Ch. 528.52100, 101, 102 and Radio Ch. 528.53190)	391-3	
8191, 8191A (TV Ch. 528.52110, 111, 112 and Radio Ch. 528.53190)	391-3	
8192, 8192A (TV Ch. 528.52100, 101, 102 and Radio Ch. 528.53190)	391-3	
8193, 8193A (TV Ch. 528.52110, 111, 112 and Radio Ch. 528.53190)	391-3	
Ch. 132.42800	391-12	
Ch. 528.51040 (See Photofact Servicer)	393	
Ch. 528.50125	389-3	
Ch. 528.50144	389-3	
Ch. 528.51100, 528.51102, 528.51104	390-3	
Ch. 528.51110, 528.51112, 528.51113	390-3	
Ch. 528.51140, 528.51142, 528.51143	390-3	
Ch. 528.51150, 528.51152, 528.51153	390-3	

Set No.	Folder No.	
SILVERTONE—Cont.		
Ch. 528.52100, 528.52101, 528.52102	391-3	
Ch. 528.52110, 528.52111, 528.52112	391-3	
Ch. 528.53040	392-10	
Ch. 528.53190	391-3	
SONIC		
465	390-11	
SPARTAN		
24 Series	383-14-5	
25 Series	384-17-5	
Chassis AMP-158AA	390-12	
Chassis U24-01AA, U24-02AA, U24-03AA, U24-04AA, U24-06AA	383-14-5	
Chassis U25-01AA, U25-02AA, U25-03AA, U25-04AA, U25-05AA, U25-06AA, U25-07AA, U25-08AA, U25-09AA, U25-10AA, U25-11AA	384-17-5	
Chassis V24-01AA, V24-02AA, V24-03AA, V24-04AA, V24-06AA	383-14-5	
Chassis V25-01AA, V25-02AA, V25-03AA, V25-04AA, V25-05AA, V25-06AA, V25-07AA, V25-08AA, V25-09AA, V25-10AA, V25-11AA	384-17-5	
STROMBERG-CARLSON		
AU-62	391-13	
SYLVANIA		
31C606 Series (Ch. 1-534-1, 2)	391-4	
31T304 Series (Ch. 1-534-1, 2)	391-4	
Ch. 1-534-1, 2	391-4	
TECH-MASTER		
21	391-14	
1930N	390-4	
2430N	390-4	
TRAV-LER		
TR-250-A, TR-251-A	392-11	
TRUETONE (Also See Auto Radio Listing)		
D28328, D28348	384-16	


Set No.	Folder No.	
V-M		
155A	393-11	
1276	391-15	
1290	392-12	
WESTINGHOUSE		
H-17T241, H-17T242, H-17T243, H-17T244, H-17T245 (Ch. V-2373-1)	392-4	
H-17TU241, H-17TU242, H-17TU243, H-17TU244, H-17TU245 (Ch. V-2383-1)	392-4	
H-21T2198, H-21T221B, H-21T2228 (Ch. V-2372)	388-3	
H-580T5, H-581T5, H-583T5, (Ch. V-2259-3)	392-13	
Ch. V-2259-3	392-13	
Ch. V-2373-1	392-4	
Ch. V-2383-1	392-4	
ZENITH (Also See Record Changer Listing)		
A1510L, A1511G, A1512J, A1515W (Ch. 15A25)	373-17-5	
A1815P, PU (Ch. 15Z31, U)	376-5	
A2221J, JU, Y, YU, A2223E, EU, H, HU, R, RU, Y, YU, (Ch. 17A20, U)	393-4	
A2245E, EU, R, RU (Ch. 17A20, U)	393-4	
A2250M, MU, R, RU, A2251E, EU, R, RU, (Ch. 17A20, U)	393-4	
A2282E, EU, R, RU, (Ch. 17A20, U)	393-4	
A2329J, A2330, H, R, (Ch. 19A20)	377-19-5	
A2358E, R, A2359E, H, R, A2362M, R (Ch. 19A20)	377-19-5	
A2673E, EU, R, RU, (Ch. 17A20, U)	393-4	
A3000E, R (Ch. 17A21Q)	393-4	
A3001E, H, R, (Ch. 17A20Q)	393-4	
A3004, E, R (Ch. 17A21Q)	393-4	
A3006E, H, R (Ch. 17A20Q)	393-4	
A3008E, R (Ch. 17A20Q)	393-4	
A3010E, H, R, A3011, E, Y, A3012H, R, A3013H, A3014H, R (Ch. 19A20Q)	377-19-5	

Set No.	Folder No.	
ZENITH—Cont.		
A4007E, R (Ch. 19A20Q)	377-19-5	
Z2675EZ, RZ (Ch. 17Z33)	357-14-5	
Z4000EZ, RZ (Ch. 17Z33Q)	357-14-5	
Z4006EZ, RZ (Ch. 17Z33Q)	357-14-5	
Ch. 15A25	373-17-5	
Ch. 17A20, Q, U, 17A21Q	393-4	
Ch. 17Z33, Q	357-14-5	
Ch. 19A20, Q	377-19-5	
AUTO RADIOS		
BLAUPUNKT		
"Frankfurt"	393-7	
"Kalin"	392-7	
BUICK		
981902 (See Photofact Servicer)	393	
CHEVROLET		
987724, 987727, 987730 (See Photofact Servicer)	393	
3748611 (See Photofact Servicer)	393	
MOPAR		
845, 846	390-6	
TRUETONE		
DC46238	350-16	
RECORD CHANGERS		
COLLARO		
"Conquest"	390-5	
RCA VICTOR		
RP-208-2, -3, -4, -5	391-11	
ZENITH		
S-14078, S-14079, S-14082, S-14083, S-14084, S-14085	392-14	
RECORDERS		
WEBCOR		
2812, 2816	393-12	
2822	393-12	
2892, 2896	393-12	

NOTE: PCB Denotes Production Change Bulletin. ● Denotes Television Receiver. S Denotes Schematic Coverage Only.



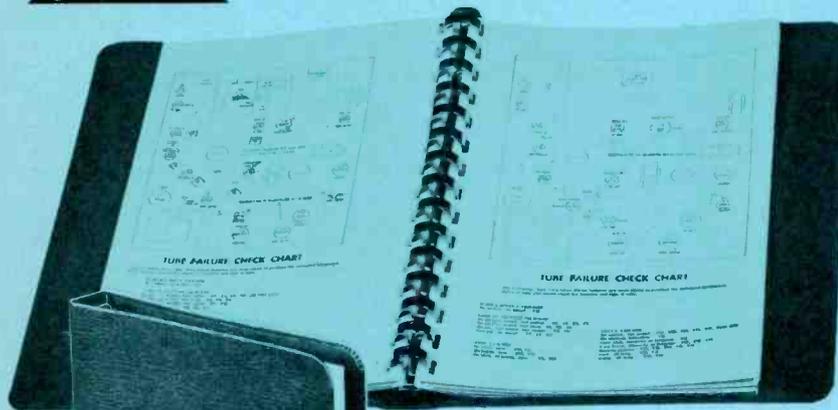1958 TELEVISION TUBE LOCATION GUIDE SUBSCRIPTION



YOUR NEW 1958 SUBSCRIPTION INCLUDES:

- ✓ 40 Charts plus index and new binder
- ✓ 40 Charts—new index mailed April 1958
- ✓ 40 Charts—new index mailed July 1958
- ✓ 40 Charts—complete cumulative index mailed Oct. 1958

... all for \$3.95

START RECEIVING TUBE LOCATION CHARTS ON CURRENT MODEL TV'S ALMOST A YEAR IN ADVANCE OF THE PAPER-BOUND EDITION! ! !

Start the year right . . . with a subscription to the new 1958 Television Tube Location Guide. Receive your new binder and first 40 charts almost a year in advance of the bound volume. Remember, this special and exclusive service costs you less than a penny-per-new-model for coverage you need today!

AVAILABLE NOW FROM YOUR SAMS DISTRIBUTOR

You're in the spotlight for the
BIGGEST SHOW
OF ALL TIME!

RCA offers every TV service-dealer a "front-row-center" ticket to a service-selling program! You are the "star" in this big performance:

☆ National Television Servicemen's Week—
 and you can win valuable prizes in the exciting
 RCA "Mystery Shopper" contest!



4th Annual NTSW
March 24-29, 1958!

"National Television Servicemen's Week"—
 "showing" for the 4th consecutive year in national magazines such as Life and TV Guide, television and radio commercials, nation-wide publicity... local newspaper advertising and special attention-getting displays and promotion kits—gives you the "star" billing.




Valuable Prizes Offered!

See the "RCA MYSTERY-SHOPPER CONTEST" ad appearing in other trade magazines this month. You can win one of 192 big awards. Every service-dealer who enters receives a gift, just for entering. Contact your RCA tube distributor for full details.



Attention Getters! Traffic Stoppers!
Business Builders!

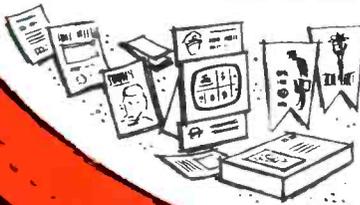A dazzling "cast" of NTSW stickers, streamers, cards, displays, premiums, mailers, broadsides, signs of all kinds—all available through your **RCA TUBE DISTRIBUTOR**.
 See him now!



Never before in the history of the TV service-industry has there been such a tremendous "cast" of featured "players" to back up a "star" performer—you, the *independent TV service-dealer*.

Yes, RCA is putting you in the spotlight to help you • gain greater public recognition than ever before • build customer good-will • promote your skill and experience • merchandise your sales and service business.

Take a bow! You're the "star"! Contact your **RCA TUBE DISTRIBUTOR** now for full details!




RADIO CORPORATION OF AMERICA

Electron Tube Division

Harrison, N. J.

LITTELFUSE

Des Plaines, Illinois

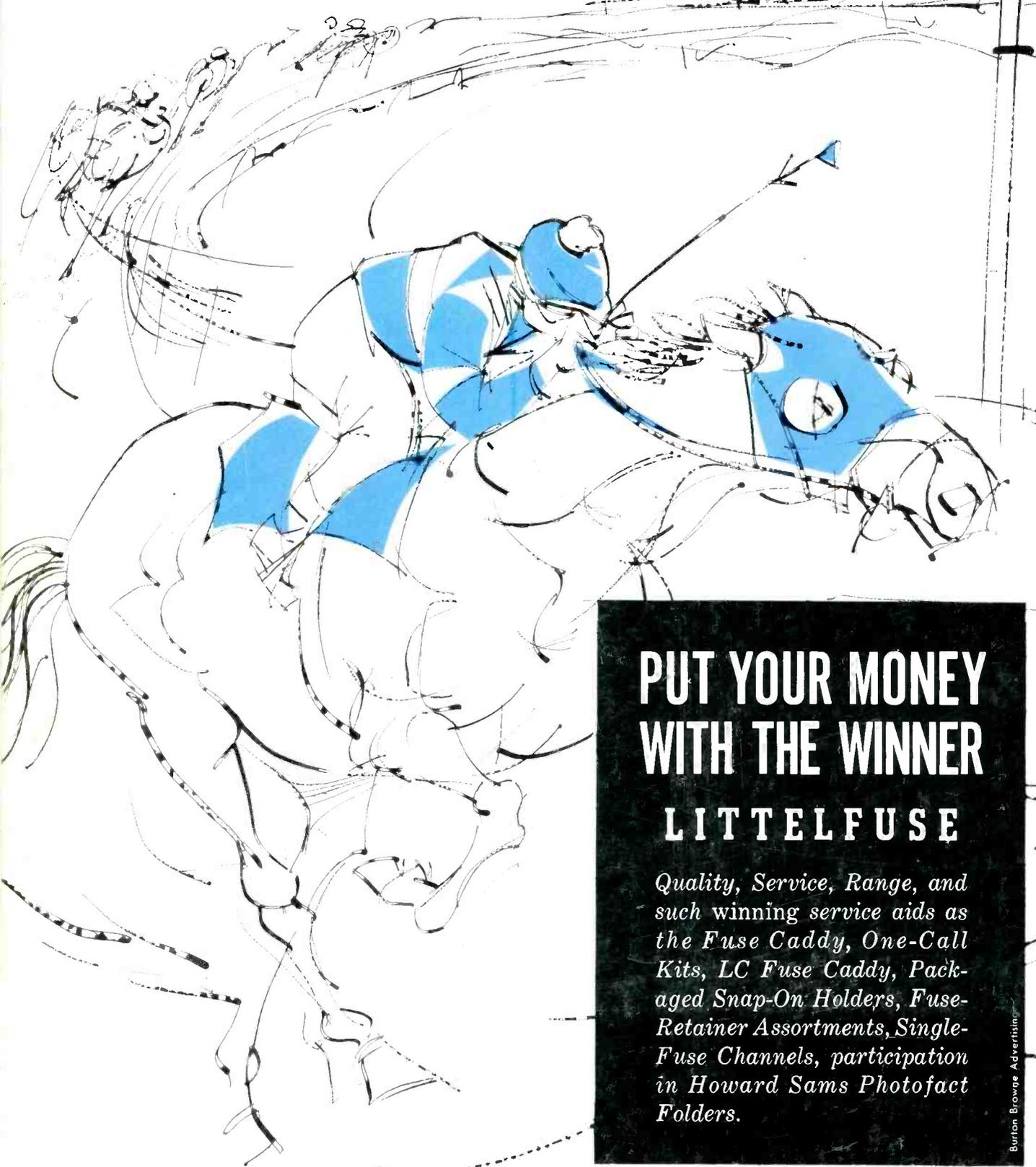

PUT YOUR MONEY WITH THE WINNER LITTELFUSE

Quality, Service, Range, and such winning service aids as the Fuse Caddy, One-Call Kits, LC Fuse Caddy, Packaged Snap-On Holders, Fuse-Retainer Assortments, Single-Fuse Channels, participation in Howard Sams Photofact Folders.

Burton Browne Advertising