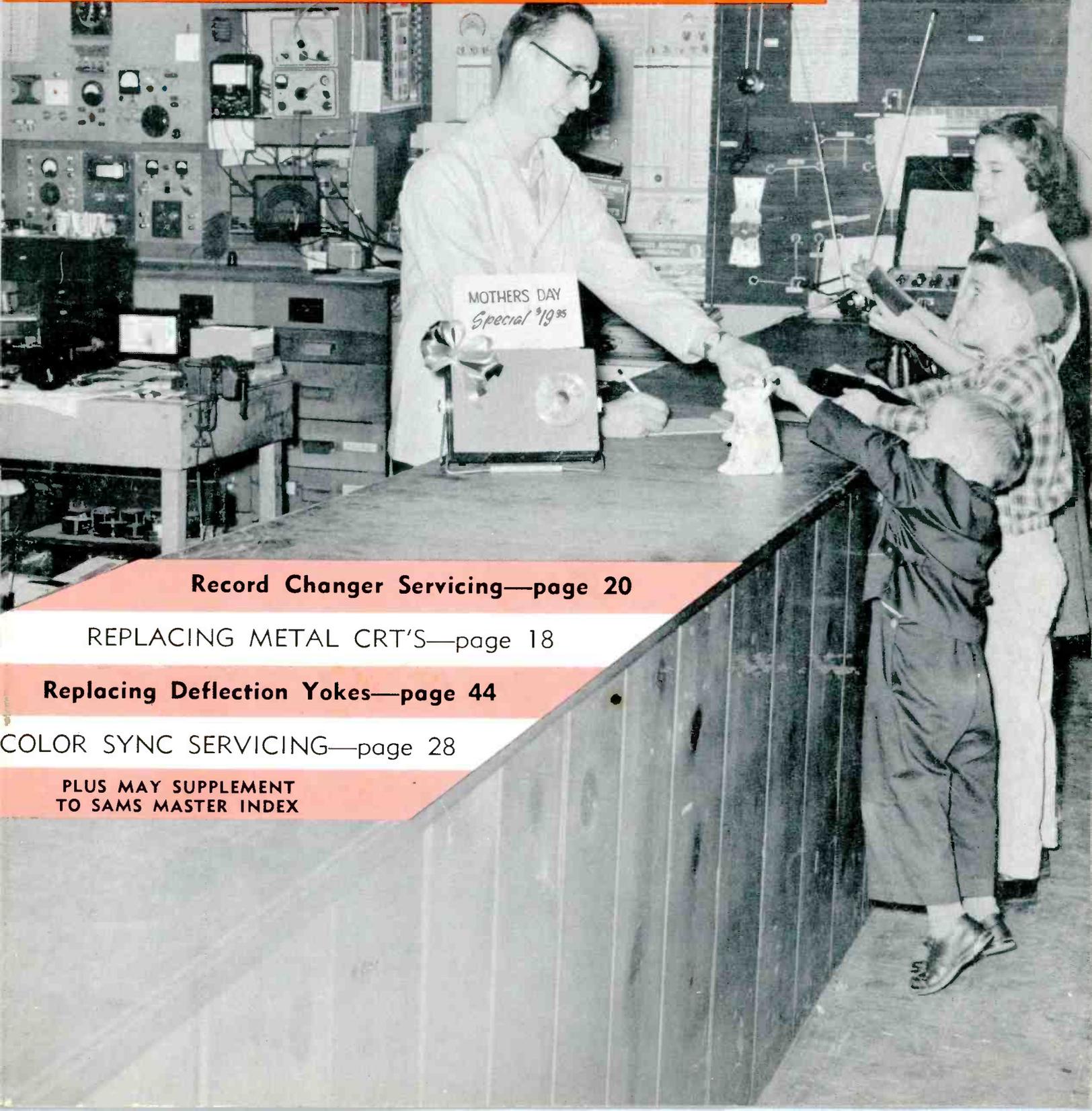


MAY • 1958 25 CENTS



REPORTER

FOR THE ELECTRONIC SERVICE INDUSTRY




Record Changer Servicing—page 20

REPLACING METAL CRT'S—page 18

Replacing Deflection Yokes—page 44

COLOR SYNC SERVICING—page 28

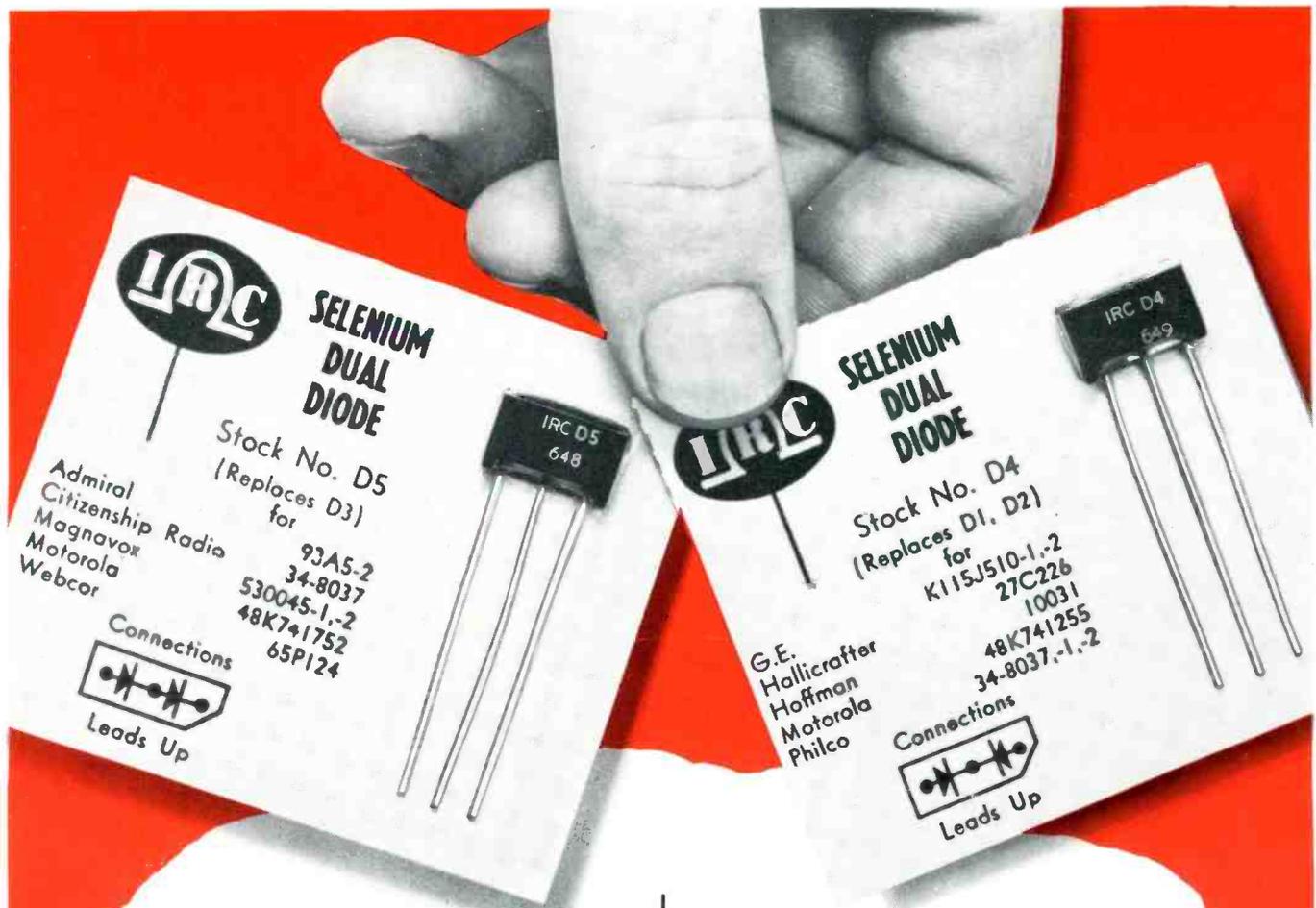**PLUS MAY SUPPLEMENT
TO SAMS MASTER INDEX**



TYPE D5 SERIES CONNECTED DIODE

Universal replacement for following Manufacturers' Parts: Admiral (93A5-2, 93B5-3, 93B5-4 and 93B5-5), Citizen Radio (34-8037), Emerson (817062), Magnavox (530045-1 and 530045-2), Motorola (48K741752, 48B742698), Silvertone (B48-110), Webcor (65P124), Zenith (63-3977).
New Type D5 takes place of IRC Type D3.

TYPE D4 COMMON CATHODE DIODE

Universal replacement for following Manufacturers' Parts: G. E. (K115J510-1 and K115J510-2), Hallicrafter (27C226), (027-300-226), Hoffman (10031), (744002), Motorola (48K741255), Philco (34-8037, 34-8037-1, 34-8037-2 and 34-8037-3), Muntz ([2] SR-0004, SR-0006).
Type D4 takes place of IRC Types D1 and D2.

NEW IRC® DUAL DIODES

meet replacement requirements
of 24 manufacturers' parts

- Only two IRC Universal Selenium Dual Diodes are now necessary to meet the replacement requirements of most big name TV sets, phonographs, hi-fi sets, plus model airplane radio controls and other circuits.
- Mounted on cards with a special plastic "skin" that seals out dust, dirt and handling . . . peels off quickly, easily and neatly.

ORDER FROM YOUR IRC DISTRIBUTOR

INTERNATIONAL RESISTANCE CO., Dept. 361, 401 N. Broad St., Phila. 8, Pa.



now available
to servicemen
from Radio Receptor

AUTOMATIC

SILICON RECTIFIER

for universal replacement

The choice of leading TV manufacturers as original parts in many new models.

- hermetically sealed
- no pressure contacts used
- no heat sinks required


Today more and more TV set manufacturers are turning to General Instrument Corporation's Automatic Manufacturing Division for the finest silicon rectifier made. Now Radio Receptor offers the service industry the *same* outstanding rectifier with characteristics that greatly improve the performance of any radio or TV set.

A single type — AUTOMATIC PT5 — can be used for all rectifier replacement. It's smaller, longer lived and cuts installation work in half. Pigtail leads can be connected to existing unused terminals or suitable terminal strips are available if needed. Start using them now and give those old sets a lift!

PT5
rated at
500 mA
at
130V A.C.

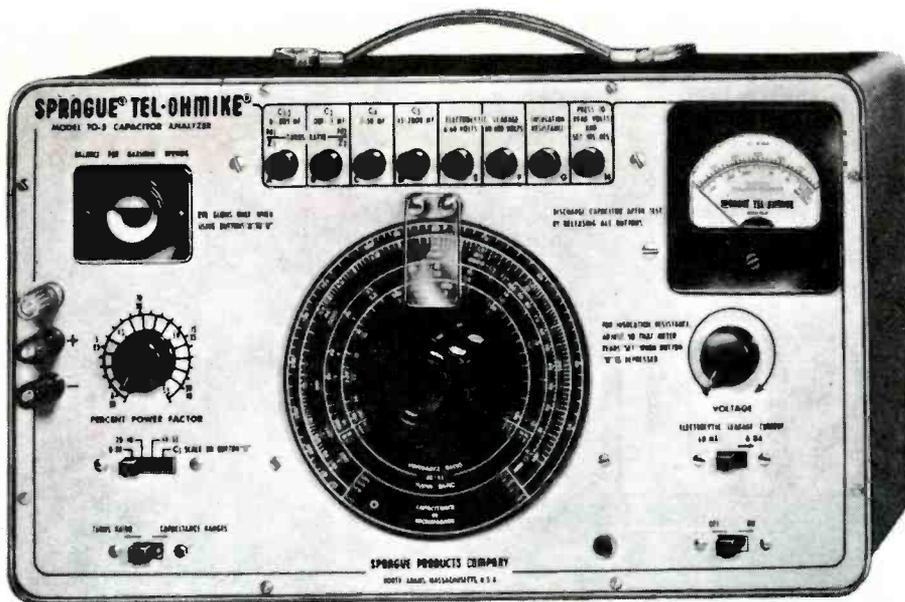General Instrument Distributor Division
RADIO RECEPTOR COMPANY, INC.
Subsidiary of General Instrument Corporation
240 Wythe Avenue, Brooklyn 11, N. Y., EVergreen 8-6000





NEW TO-5 TEL-OHMIKE® capacitor analyzer

measures all **4** . . . plus

1 CAPACITANCE	2 POWER FACTOR	3 LEAKAGE CURRENT	4 INSULATION RESISTANCE	extra feature TURNS RATIO
Measures up to 2000 μf in five overlapping ranges . . . including an accurate 1 to 100 μf range, exclusive with Sprague.	Power factor of electrolytic capacitors is measured by the highly accurate bridge method. Reads up to 55% in three ranges for convenience in measurement.	Leakage current of electrolytics is measured directly on the meter, with exact rated voltage up to 600 v. applied from continuously adjustable power supply. Two ranges — 0-6-60 ma.	Insulation resistance of paper, ceramic, and mica capacitors is read directly on meter . . . up to 20,000 megohms.	In addition to its function as a complete capacitor analyzer, the TO-5 also measures the turns ratio of power and audio transformers.

The NEW TO-5 TEL-OHMIKE Capacitor Analyzer is one of the fastest and surest ways of measuring . . . capacitance, power factor, leakage current, insulation resistance, and turns ratio. This compact, easy-to-use instrument has the highest accuracy of any instrument of its type available to the service trade.

New jumbo dial makes meter reading easy. Special color-keyed pushbuttons permit instant range selection . . . and allow automatic safety discharge of capacitors after testing. Magic-eye tube simplifies bridge balancing for capacitance and power factor measurements.

SEE THE NEW TO-5 TEL-OHMIKE IN ACTION . . . AT YOUR DISTRIBUTOR!

This 4-in-1 test instrument is only $8\frac{7}{8}$ " high, $14\frac{5}{8}$ " wide, and $6\frac{1}{8}$ " deep . . . weighs a mere $12\frac{1}{2}$ pounds. The complete price for . . .

MODEL TO-5 (115 VAC/50-60 cy) . . . Only **\$83⁹⁰** net

Also available: Model TO-5X for 115-230 V/25-60 cy. . . . \$89.90 net
Model TP-5RM for rack mounting \$93.90 net



SPRAGUE PRODUCTS COMPANY, DISTRIBUTORS' DIVISION OF SPRAGUE ELECTRIC COMPANY, NORTH ADAMS, MASS.

PUBLISHER
Howard W. Sams
GENERAL MANAGER
Mal Parks, Jr.

EDITOR
Verne M. Ray

ASSOCIATE EDITORS
Leslie D. Deane
Thomas A. Lesh
Calvin C. Young, Jr.

CONSULTING EDITORS
William E. Burke C. P. Oliphant
Robert B. Dunham George B. Mann
Paul C. Smith

ART DIRECTOR EDITORIAL ASSISTANT
Don W. Bradley Pat Moriarity

PHOTOGRAPHY CIRCULATION
Robert W. Reed Pat Tidd

ADVG. PRODUCTION
Carol B. Gadbury

ADVERTISING SALES OFFICES

MIDWESTERN
PF REPORTER,
2201 East 46th Street, Indianapolis 5, Ind.
Clifford 1-4531

EASTERN
Paul S. Weil and Donald C. Weil,
39-01 Main Street, Flushing 54, New York.
Independence 3-9098.

WESTERN
The Maurice A. Kimball Co., Inc.
2550 Beverly Blvd., Los Angeles 57, Calif.
Dunkirk 8-6178; and 681 Market Street,
San Francisco 5, Calif. EXbrook 2-3365.

Published monthly by Howard W. Sams & Co., Inc., at Indianapolis 5, Indiana. Entered as second class matter October 11, 1954, at the Post Office at Indianapolis, Indiana, under the Act of March 3, 1879.

Copyright 1958 by Howard W. Sams & Co., Inc. No part of the PF REPORTER may be reproduced without written permission. No patent liability is assumed with respect to the use of information contained herein.

Subscription prices in U.S.A. and possessions: 1 yr., \$3.00; 2 yrs., \$5.00; 3 yrs., \$7.00. In Canada and Pan America: 1 yr., \$3.60; 2 yrs., \$6.00; 3 yrs., \$8.50. Foreign subscriptions: 1 yr., \$6.00; 2 yrs., \$11.00; 3 yrs., \$15.00. A limited quantity of back issues are available at 35c per copy.

next month

PHONO CARTRIDGE REPLACEMENTS

You need to know more than how to remove a couple of screws and unsolder some leads if you want to be a real technician. This article discusses the various factors to be considered if a replacement cartridge is to operate satisfactorily.

WALK-IN SALES ITEMS FOR THE SERVICE SHOP

Although service is the mainstay of your business, over-the-counter purchases of such commodities as batteries, phono needles, antenna kits, etc. can put many dollars in your pocket, particularly during the summer months. This picture story will help you to formulate your plans.

BENCH NOTES

A new bi-monthly column by an author well seasoned in the practical servicing of TV. For the first of this series, we've chosen "Current Capers," a couple of case histories which seem to defy Ohm's law until our expert gives you his analysis.

VOLUME 8, No. 5



MAY, 1958

PF REPORTER

FOR THE ELECTRONIC SERVICE INDUSTRY

CONTENTS

This Month's Cover	65
Letters to the Editor	4
Shop Talk	12
Analyzing modern antenna designs.	<i>Milton S. Kiver</i>
Replacing Metal CRT's with Glass	18
With pictures to show you how it's done.	
Hints on Record Changer Servicing	20
Descriptions and service hints for Admiral, Collaro and V-M units.	<i>Calvin C. Young, Jr.</i>
Servicing New Designs	22
110° CRT's; new color receiver; Magnavox power input adjustment; TV with single IF.	<i>Thomas A. Lesh</i>
Fine Points in Color Sync Servicing	28
Quicker Servicing	32
Checking phono cartridge styli; tube failure in portables; 110° check tube; FM sweep alignment.	<i>Robert G. Middleton</i>
Servicing Industrial Electronics	40
Binary counters and how they work.	<i>Calvin C. Young, Jr.</i>
TV Service . . . A Living?	42
Replacing Deflection Yokes	44
Facts to help you do it right.	<i>Les Deane</i>
Dollar & Sense Servicing	50
Notes on Test Equipment	52
Signal pickup device, field strength meter, something new in probes, scope kit.	<i>Les Deane</i>
The Troubleshooter	60
Product Report	76
Free Catalog & Literature Service	80
Supplement to SAMS Master Index	81

SUBJECT REFERENCE INDEX

ANTENNAS	COMPONENTS AND MATERIALS
Multielement type,	Newly introduced
Channel Master "Rainbow"	76
Channel Master "Traveling Wave"	
Clear Beam "Tri-King"	
JFD "Wonder Helix"	
TACO "Trapper"	
AUDIO	PICTURE TUBES
Record changer,	Metal types,
Admiral Model RC 607	glass replacements for
Collaro "Conquest"	110° check tube
V-M Model 1200A	18
BUSINESS	34
Renting a shop	SERVICING
Selling outdoor antennas	Case histories
CIRCUITS AND DESIGNS	Damping networks in yoke
Line voltage adjustment,	FM tuner, sweep alignment of
Magnavox 26 Series chassis	Phonograph stylus
One-stage IF strip,	Portable radio tubes
Olympic Chassis DY	Record changers
110° picture tube bases	Yoke replacement
COLOR TV	20
Color sync servicing	44
RCA Victor Chassis CTC7,	TEST EQUIPMENT
color killer	Demodulator probe, Doss
convergence circuits	"Video Master" Model D-200 ...
	Field strength meter,
	Blonder-Tongue Model FSM-1 .
	Induced waveform analyzer,
	Winston Model 850
	Oscilloscope kit,
	PACO Model S-50
	58
	THEORY
	Basic computer circuits
	Binary numbers
	40
	40

USE HANDY CARD AT BACK TO ENTER YOUR SUBSCRIPTION

BURGESS BATTERIES

FOR TRANSISTOR AND TUBE MODEL RADIOS

Highest Quality—Longer Shelf Life

IT'S EASIER TO SELL THE BEST!

Depend on **BURGESS** the Complete Line

BURGESS—always the best in batteries for tube model portable radios—now leads the field again with the finest batteries for transistor model portable radios! You will prefer Burgess Batteries because they're fresher when you get them—fresher when you sell them. Stock and sell the Burgess Line! You're assured of money-making initial sales, plus more of that important repeat business!



BURGESS BATTERIES Are Pre-Sold by An Aggressive National Advertising Program in Leading Consumer Publications, Metropolitan Newspapers and Outstanding Sunday Supplements.

Plus

Jet Propelled Promotional Materials

KEYED TO

1958 BURGESS PORTABLE RADIO BATTERY PROGRAM



NEW "FRESHER" RETAIL "SALESMEN"



FLOOR STAND



PANEL DISPLAY



WIRE COUNTER RACK



METAL DISPLAY DEPT.

FREE! "FRESHER" Sales Promotion Aids



REPLACEMENT GUIDE



COLORFUL NEW WINDOW STREAMER



6-PAGE CATALOG

Contact your BURGESS Distributor for Full Details TODAY!

BURGESS BATTERIES
BURGESS BATTERY COMPANY
 FREEPORT, ILLINOIS

Letters to the

EDITOR

Dear Editor:

A 21FP4, the original picture tube in a Motorola Model 21K4W, shows a brown strip about one inch wide completely across the very bottom of the faceplate. This discoloration is internal and looks similar to an ion burn, but is not as dense as a typical ion burn. It looks more as if it had been painted on with a weak water color.

FRED K. NELSON

Cheviot, Ohio

You might get some customers to believe that it's just mud tracked in by the characters in all those Western shows. But from a technical viewpoint, it appears to us that the receiver must have been operated for an extended period with a slight vertical foldover at the bottom of the picture. This would have kept the strip of phosphor along the bottom at a relatively high brightness level, thus shortening its life.—Ed.

Dear Editor:

In regard to "Let's Talk Business" in the February issue, let's not forget that TV business is plain rough and overcomes quite a few men each year. Women are very capable and dependable in their woman's world, but seldom in a man's. A woman in the TV business is like a man at a typewriter—passable, but seldom if ever really good. I don't know of any shop that can make a living in the TV business if it is just passable.

BILL HENDRIX

South San Francisco, Calif.

Remembering the men's shoes that were filled by women during World War II, and also knowing several who are successful in business today, we're inclined to disagree. It's all a matter of personal opinion, however, in your case, why not train a man to take over.—Ed.

Dear Editor:

Why not leave an area on each month's cover where the reader can write in notes—for example, indexing data on articles of special interest? This clear area should be of such a color that the notes are legible, and it should be in the same place on the cover every month.

E. J. FLURE

Alton, Ill.

Why not just glue a piece of white paper on the cover? Other readers may prefer to use the Contents page.—Ed.

You can do more than ever before with this new portable **B&K**

AUTOMATIC MONEY-MAKER



**TESTS TUBES
AND TRANSISTORS
Automatically**
WITH LABORATORY ACCURACY

- Saves Servicing Time
- Sells More Tubes
- Satisfies More Customers



B&K MODEL 675
AUTOMATIC
DYNA-QUIK
DYNAMIC MUTUAL CONDUCTANCE
TUBE & TRANSISTOR TESTER

Again, B&K helps servicemen give faster, better service at less cost and make more money. The new automatic Model 675 makes tube checking quick and easy in the home or shop. (Tests transistors, too.) Measures true dynamic mutual conductance. Makes complete tube test in seconds, under actual operating conditions of the set. Checks average set in a few minutes. Simple to operate. No multiple switching. No roll chart. Shows customer the true condition and life expectancy of tubes in the set, sells more tubes on-the-spot, saves call-backs. Quickly pays for itself.

Shows tube condition on "Good-Bad" scale and in micromhos. Large 4½" meter has two highly accurate ranges calibrated 0-6000 and 0-18,000 micromhos. 7-pin and 9-pin straighteners are mounted on panel. Automatic line compensation. Special bridge monitors line voltage continuously. Light weight, easily portable in handsome leatherette-covered carrying case. Operates on 105-125 volts 60 cycle a.c. Size: 15¼" x 12¼" x 6". Net wt: 10½ lb. Net, **\$169⁹⁵**

Also makers of famous CRT, DYNA-SCAN, CALIBRATOR

MORE ACCURATE TEST

Tests Each Section of Multiple Tubes Separately for Gm, Shorts, Grid Emission and Life

Tests each tube for Gas Content and Grid Emission simultaneously with Short check. Instantaneous Heater Continuity test.

SIMPLIFIED AUTOMATIC DYNA-CARD SYSTEM

With only 60 heavy-duty, phenolic Dyna-Cards you can test over 500 tube types. Dyna-Card automatically sets socket connections for quick, accurate test. Each Dyna-Card is identified and indexed, ready to use. Always kept up-to-date simply by adding new Dyna-Cards. Minimizes obsolescence.

CHECKS OVER 99%

of the tubes most widely used in television receivers plus popular home and portable radio tubes.

ONE EXTRA TUBE SALE

on each of 5 calls a day pays for the Dyna-Quik in a few weeks.

TESTS TRANSISTORS, TOO

Transistor Section checks junction, point contact and barrier transistors, germanium and silicon diodes, selenium and silicon rectifiers.



See your B&K Distributor, or write for Bulletin AP12

B & K MANUFACTURING CO.
3726 N. Southport Ave. • Chicago 13, Illinois

Canada: Atlas Radio Corp., 50 Wingold, Toronto 10, Ont. Export: Empire Exporters, 458 Broadway, New York 13, N.Y.

*They're New...
Smart... Attract Customers.*



A. ILLUMINATED SIGN-A-RAMA. Visible for blocks. Brightly lit with six flashing lamps. Double-faced, large—48" by 24"—gives top identification to your store or shop. Mounting hardware is included.

B. ILLUMINATED SPECIAL-MESSAGE SIGN. Carries your name, or tells any brief message you select. Ideal for windows or interiors. 37" by 14". Uses two 30-watt bulbs. Kit of letters and numerals is included.

C. DISPLAY BACKDROP. Arrange this handy back-up display to meet your advertising needs. Material is flexible, can be curved or will mount flat. For window trim, walls, or counter fronts. Two 36" x 24" designs per strip.

D. GIANT TUBE CARTON. Eye-arresting... indicates the quality components you install and sell.

E. DOOR WINDOW DECAL. Neat, attractive, new dry-apply type. 12" diameter.

.. GENERAL ELECTRIC'S COLOR-KEYED SHOP SIGNS!

Color-keyed to the G-E tube carton—symbol of quality!



Here is your chance to give your shop-front and windows eye-appeal with "sell". Colors of all eleven new General Electric signs and displays match handsomely the famous G-E tube carton. Quality appearance is keyed to high quality of product—a message every passerby is sure to read.

Attractive and modern, General Electric's color-keyed signs and displays also stand for leadership. They identify your shop as a source for television repairwork done to professional standards, backed by up-to-the-minute facilities.

All your display needs are met by smart new G-E designs—from an eye-catching, easy-to-apply door or window decal, to metal and illuminated outdoor and indoor signs... plus colorful utility items like the electric clock and thermometer.

These brand-new signs and displays are waiting for you now at your General Electric tube distributor's. Ask him how to obtain them! *Distributor Sales, Electronic Components Division, General Electric Company, Owensboro, Kentucky.*

◀ **SERVICE CLOTHING**, smartly styled, also is available. Garments are color-keyed to new G-E signs and displays—give that professional look. Durable, launder easily.

◀ **SERVICE CASES** in three useful sizes—small, medium, and large—match color-theme of General Electric displays. Now you can carry with you neatly, compactly, everything you need for making home service calls!

Progress Is Our Most Important Product

GENERAL  ELECTRIC

11-11-102



METAL FLANGE SIGN. A display workhorse. Double-faced. Mount it anywhere! Compact—15" by 12"—handy for building corners, delivery entrances, and other side locations.



ILLUMINATED CLOCK, electric. Both useful and advertises your business. Easily read—16" diameter—with long-life bulbs. Hang on a wall, or mount on a counter (easel is provided).



COUNTER-WALL-WINDOW SIGN. Illuminated. Use it anywhere in your shop! Wrap-around cover has the attractive display on both sides. 15" by 11½" by 5".



OUTDOOR-INDOOR THERMOMETER. Tells temperature accurately. Every viewer will see your advertising message. Replaceable front. 12" diameter.



HANGING METAL SIGN. For shop front or service entrance. Message both sides, plus your nameplate. Large—48" by 36"—easily seen. Hanging hardware is included; lights are available.



METAL TACK-ON SIGN. Narrow, smart dimensions—14" by 42". Fasten against building, or mount as a free-standing display.

ASTRON CAPACITORS

KEEP CALL BACKS OUT OF YOUR SERVICE KIT

Call backs do not just happen! They are caused by the level of quality a manufacturer builds into his components. Astron's "Safety Margin"* capacitors PUT QUALITY IN YOUR SERVICE KIT.

Every time you install a component, your reputation as a serviceman is being made. Skilled as you are, your work is only as good as the components you carry with you on each call. With Astron's "Safety Margin"* capacitors you CARRY quality in your service kit.

Use Astron's Serviceman Line with:

- Low Leakage
- High Dielectric Strength
- Hermetic Seal
- 99.99% Pure Aluminum Foil
- Heat Aging
- Contamination Free Assembly

Designed to give service to the serviceman



ASTRON

C O R P O R A T I O N

255 GRANT AVENUE
E. NEWARK, N. J.

WEST COAST WAREHOUSE:
I. R. STERN AND COMPANY
4109 BURBANK BLVD.
BURBANK, CALIF.

*TRADEMARK

Letters

(Continued from page 4)

Dear Editor:

I found the article *Do-it-Yourselfers are Soldering Now* in your March issue very interesting and true-to-life. My experiences along these lines have been similar. I would like, however, to get an idea of how others charge for this type of work.

My policy has been to "average out" bench charges, using a more or less fixed price regardless of whether it is a "quickie" or a "toughie." What should you do when you spend hours or even days to solve what is not really a TV problem, but a "people" problem?

MURRAY SCHOEN

Murray's TV
Saddle River, N. J.

Our main reason for publishing the article, Murray, was to make technicians aware of the "menace" so that you wouldn't have to spend "hours or days" on the job. If you don't charge for the time, you lose; if you do, the customer may never forgive you. Flat-rate bench charges for any set are used by many TV service shops, which is in contrast with the flat-rate and hourly-rate charges used by others for specific repairs like alignment, tuners, etc. Some shops even use a combination of the three.—Ed.

Dear Editor:

In reading "Letters to the Editor," March, 1958, I noted that two pamphlets on TV Service, "TV Without Tears" and "Safeguard" are available from the Better Business Bureau—but I don't know where to send for them. To whom should I write?

CHARLES C. GRECO

Brant Lake, N. Y.

Dear Editor:

Where do I write to get pamphlets "Safeguard" and "TV Without Tears?" Your answer to James Ivey in the March issue does not give address of the Better Business Bureau.

MIKE SMOLICH

Radio & Television Service
Ramsay, Michigan

Dear Editor:

Please send me "Safeguard" and "TV Without Tears" as mentioned in March "Letters to the Editor."

FRANCIS CUNNINGHAM

Hillside TV & Radio
Holbrook, Mass.

The Better Business Bureau Association has district offices in most major cities, or you can write to the National Better Business Bureau, Chrysler Building, New York 17, N. Y. While you may be able to obtain single copies, the booklets are primarily intended for bulk distribution to your customers.—Ed.

40%

DUMONT POSITIVE QUALITY


FEWER CALLBACKS*

A positive fact about
Du Mont Positive Quality . . .

Du Mont Picture Tubes cut callbacks due to
tube failure by 40%. Consider what
this means to you — fewer callbacks,
greater profits.

Ask your distributor about
Du Mont Positive Quality Picture
Tubes and Electronic Tubes.

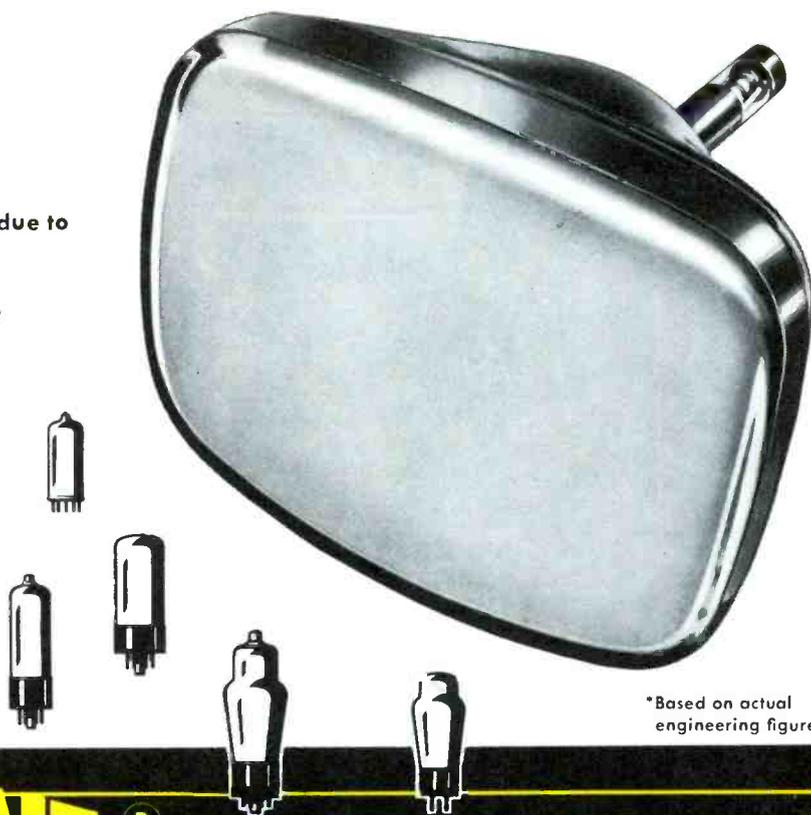● Send name and address for
your free copy of the Du Mont
Replacement Tube Chart.



*Based on actual
engineering figures.


DUMONT®

Television Tube Division

Allen B. Du Mont Laboratories, Inc., Clifton, N. J.



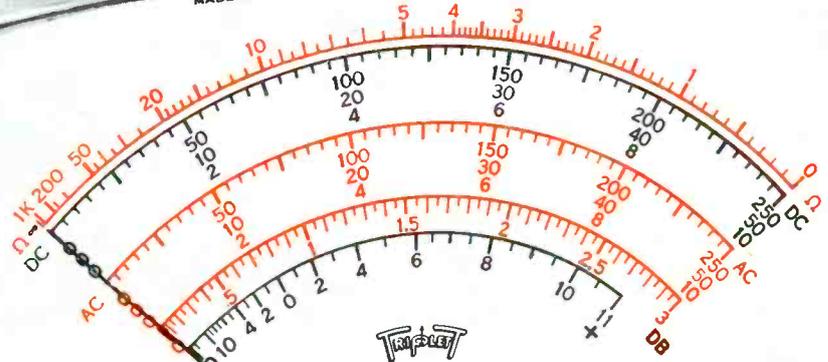MADE IN U.S.A. BY THE TRIPLET ELEC. INSTR. CO., BLUFFTON, OHIO



TRIPLET
MODEL 630-PL

"0" DB
AT 1 MW
ON 600
OHM LINE

OHMS PER VOLT
10,000 DC 5,000 AC

VOLT RANGE	ADD DB
2.5	0
10	10
50	24
250	38
1000	50
5000	64

SER. NO.

5000 OFF 5000

1000 1000

250 250

50 ACV

10

3

10A

1000

100 DC MA

10

100 μ A

5000 ACV

5000 DCV

ADJ Ω

DC+

ACV



DC-

COM-

V- Ω -A

OUT PUT

New Triplet Model 630-PL. \$44.50 net.

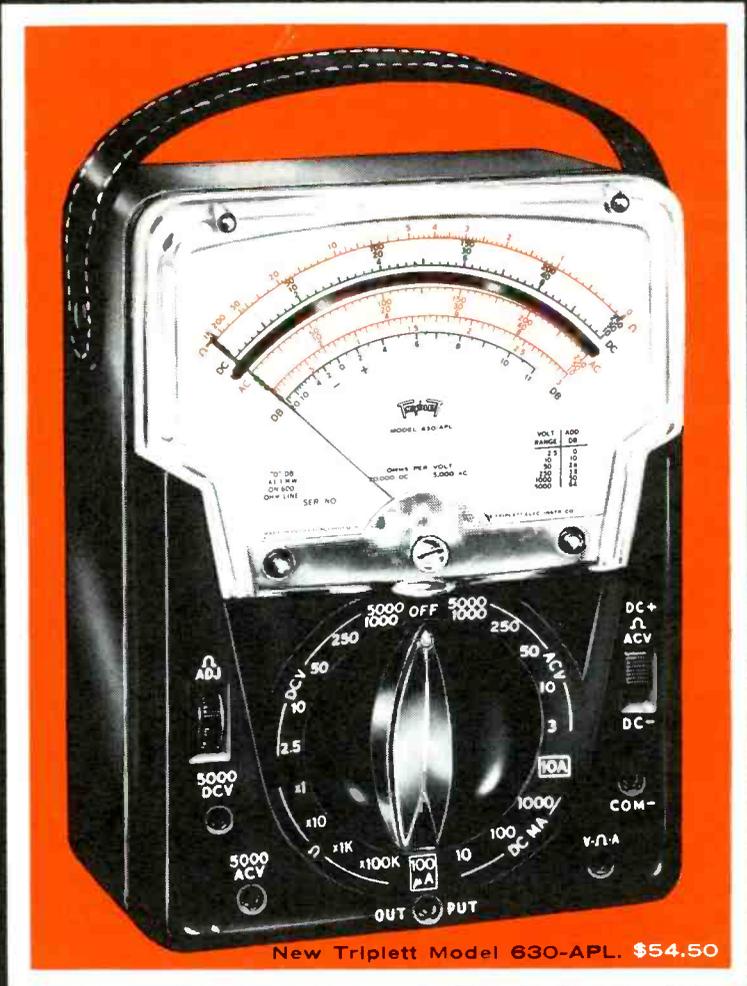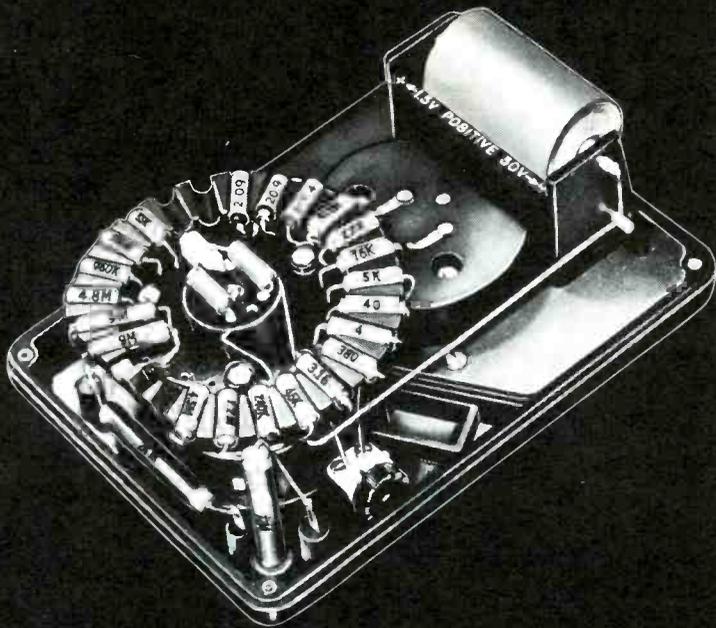

New Triplet Model 630-APL. \$54.50

...the new triplett twins!




Not one but two most advanced VOMs.

- Most easy to read — clear, unbreakable, shadowless front for instant wide vision.
- 5 to 500,000 cps on A.C.
- Continuous resistance reading from 0.1 ohm to 100 megohms.
- Polarity reversing switch.
- Only one (king sized) switch selects both circuit and range — minimizes wrong settings, burnouts.
- 630 APL — 1½% accuracy D.C.
- 630 APL — Mirror scale eliminates parallax.

Only Triplet affords you such a wide choice of VOMs. Whatever your application — broad or limited — there is a Triplet VOM particularly suited for it.

the mighty nine...plus two

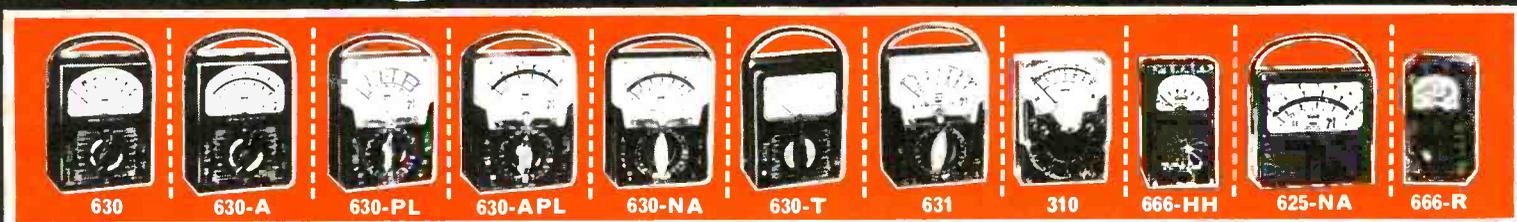

TRIPLET ELECTRICAL INSTRUMENT COMPANY • BLUFFTON, OHIO

ShopTalk

MILTON S. KIVER

Author of . . .
*How to Understand and Use TV Test Instruments
 and Analyzing and Tracing TV Circuits*

Complex, multielement antennas, like complex, multielement circuits, can usually be shown to be combinations of simpler, more familiar configurations. Sometimes the shape of the basic structure is recognizable immediately; at other times, the outlines are quite indistinct and it takes considerable probing before a familiar pattern is uncovered.

One of the difficulties experienced in attempting to design a single all-band array is the break-up of the figure-8 pattern at the high frequencies. Last month, it was shown that a conical antenna partially overcomes this multilobing effect by veering the arms of the array forward, causing some of the side lobes to combine with the main lobe.

To understand some of the other methods which have been employed to overcome this multilobing, let us see how the effect arises in the first place. A half-wave dipole, operated at its resonant frequency, possesses the current distribution shown in Fig. 1. Note that the current rises to a maximum at the center, gradually tapering off to zero at the ends. The response pattern follows the

same distribution, receiving signals best when they arrive broadside and poorest when they approach the antenna from the ends.

If we employ the same antenna at three times its original frequency, however, we find that the current distribution assumes the form shown in Fig. 2. There are now three half-cycles, with the center one 180° out of phase with the other two. The radiational effect of the out-of-phase section works in opposition to the other two sections, with the result that the pattern shown in Fig. 2 is obtained. In place of a single figure-8, we have now a pattern with 6 lobes, all pointing in different directions.

What we have just described happens when a half-wave dipole, cut for the low VHF band, is employed to receive high-band VHF stations. Center frequencies of both bands are roughly in the ratio of 3 to 1. Hence, where we have a half-wave current distribution on the low band, we obtain three half waves on the high band as shown in Fig. 2. If we could somehow reverse the phase of the center current section, then a figure-8 pattern would be obtained

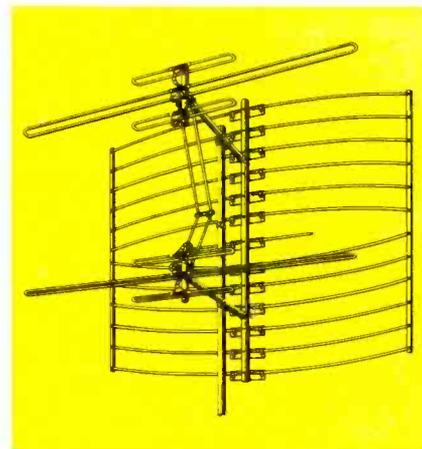


Fig. 3. Clear Beam "Tri-King" stacked array has three dipoles in each section.

for the high frequencies.

How It's Done

The "Tri-King" array (Fig. 3), being marketed by Clear Beam Antenna Corp., achieves such a reversal in the manner shown in Fig. 4A. Another small dipole, designed for half-wave current distribution, is connected to the large dipole in reverse manner so that the current wave it develops is opposite in phase to the current wave produced by the center section of the large dipole. Because of the close physical proximity of the two units, their fields will cancel. Since this would leave a gap in the response of the large dipole at the high frequencies, another small dipole is added to the combination. (Fig. 4B.)

This second dipole is connected in parallel with the first, so its current distribution possesses the same phase. Now the over-all system possesses three half-wave current sections, all having the same phase and thereby providing a close approximation to a figure-8 response on the high band. Low-band performance is relatively unaffected.

In the final design of this array, all dipoles are of the folded variety, properly interconnected to present a 300-ohm impedance to the transmission line. Two sets of dipoles are stacked for greater gain, and a screen-type reflector is positioned behind the array to kill any response to signals arriving from the rear. The reflector bars are bent to strengthen the screen structurally.

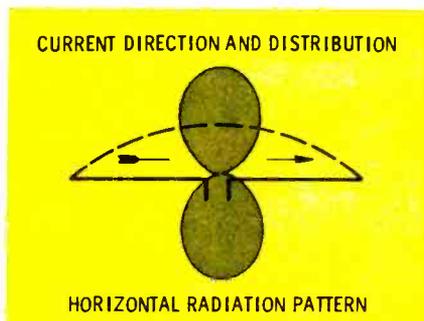


Fig. 1. Half-wave dipole with current distribution and radiational pattern.

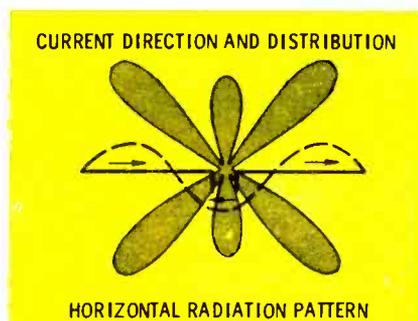


Fig. 2. Dipole response when operated at three times its resonant frequency.

• Please turn to page 63

Mr. Independent Service Dealer:



When you buy tubes are you robbing yourself?

Not when you buy Raytheon TV and Radio Tubes

First of all, Raytheon has no factory TV-radio service organization that competes with you for profitable servicing business — you're not helping a "competitor" when you buy Raytheon Tubes.

Then, too, when you buy Raytheon TV and Radio Tubes you get the finest quality tubes money can buy — tubes designed for top performance in all makes and models of receivers. Raytheon does not manufacture sets and therefore must make tubes that will meet the rigid performance requirements of the many sets pro-

duced — tubes ideal for all replacement work.

And last, but by no means least, when you buy Raytheon Tubes you deal with local *independent* tube distributors who are anxious to give you the best in service and technical assistance. They are eager to supply you with the hundreds of helpful shop and sales aids Raytheon makes available for you — helps that make your job easier, more efficient and more profitable.

Make all of your tube dollars work for you — always ask your Tube Distributor for Raytheon quality TV and Radio Tubes.



RAYTHEON MANUFACTURING COMPANY

Receiving Tube and Semiconductor Operations

NEWTON 58, MASS.
55 Chapel Street

CHICAGO, ILL.
9501 Grand Ave. (Franklin Park)

ATLANTA 6, GA.
1150 Zonolite Rd. N.E.

LOS ANGELES 7, CALIF.
2419 So. Grand Ave.

**Raytheon makes
all these**

Receiving and Picture Tubes, Reliable Subminiature and Miniature Tubes,
Semiconductor Diodes and Transistors, Nucleonic Tubes, Microwave Tubes.



Excellence in Electronics

EVEN THOUGH THE DADDY OF

**3 reasons why there are
NO printed circuits in Zenith TV chassis**

 standard HANDcrafted circuitry means:

1 LESS SERVICE HEADACHES

 standard HANDcrafted circuitry means:

**2 EASIER SERVICING FOR DEALER
AND SERVICEMAN ALIKE**

 standard HANDcrafted circuitry means:

**3 MORE SATISFIED CUSTOMERS
FOR ZENITH DEALERS**

We think it's worth the extra cost and extra care of HANDcrafted standard circuitry to get the best performance and least service headaches and so do thousands of dealers who would sooner sell customer satisfaction than a price tag.

ZENITH RADIO CORPORATION
Chicago 39, Illinois

The quality goes in before the Zenith name goes on.
Backed by 39 years of leadership in radionics exclusively.
Also makers of Radio, High Fidelity Instruments and fine Hearing Aids.



PRINTED CIRCUITRY IS HEAD OF
ZENITH'S RESEARCH DEPT.*, THERE'S


NO PRINTED CIRCUITRY IN ZENITH TV CHASSIS



*Even though Dr. Alexander Ellett, head of Zenith's research department, is recognized as the daddy of printed circuitry through his work on radio proximity fuses, still Zenith uses no printed circuitry in its TV chassis because it means more service headaches and often causes service delays.

QUALITY BY

ZENITH

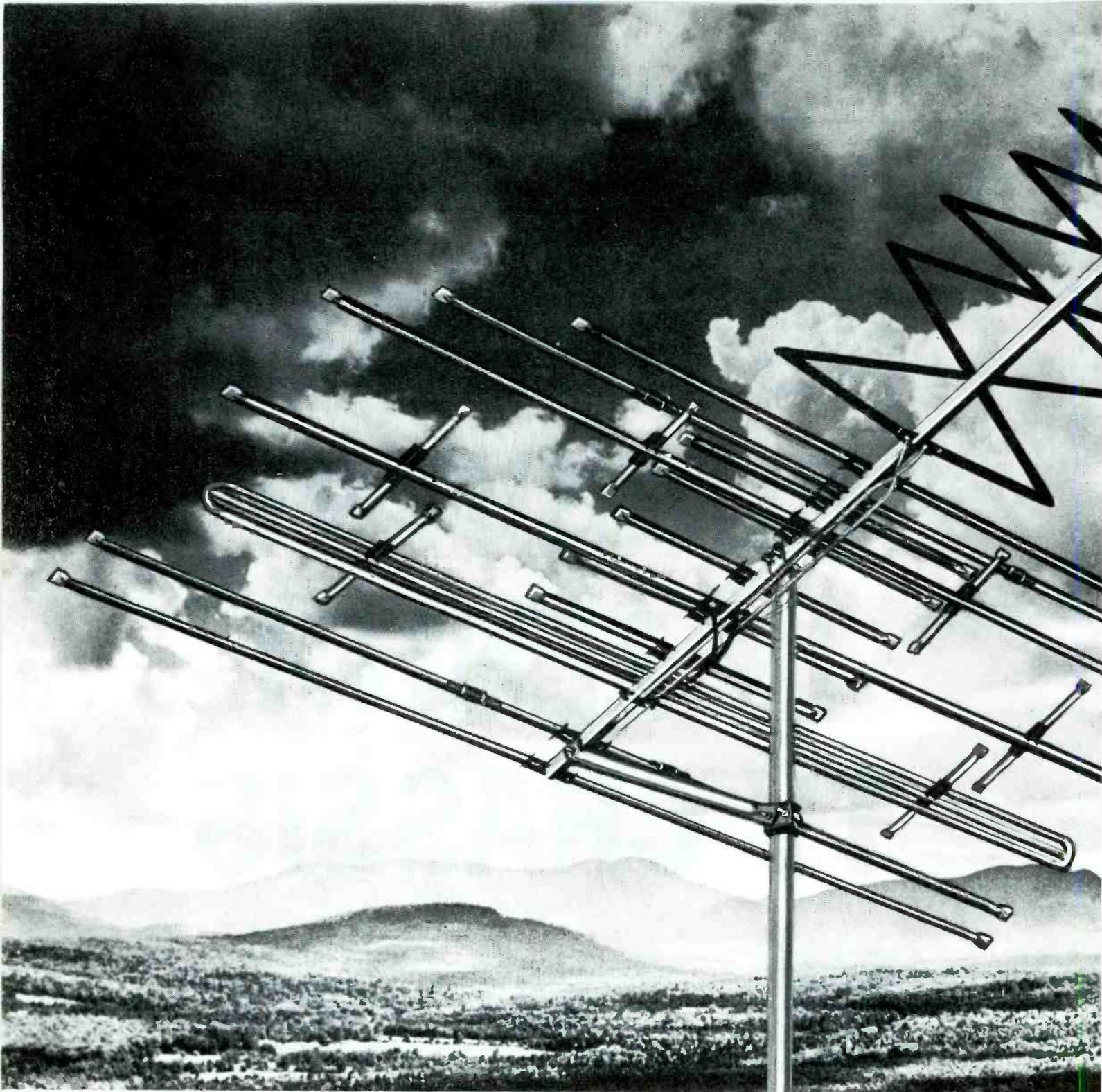

shrinks the miles!...

**28-WORKING ELEMENTS!—FULL THROTTLE POWER!
A REAL LONG RANGE PERFORMER!**

SATELLITE-HELIX

— an electrifying antenna break-through to new performance peaks

MODEL **VXIII** \$47.50 LIST


Pioneers in electronics since 1929

JFD ELECTRONICS CORPORATION
Brooklyn 4, N. Y.

JFD INTERNATIONAL
15 Moore Street
New York, N.Y.

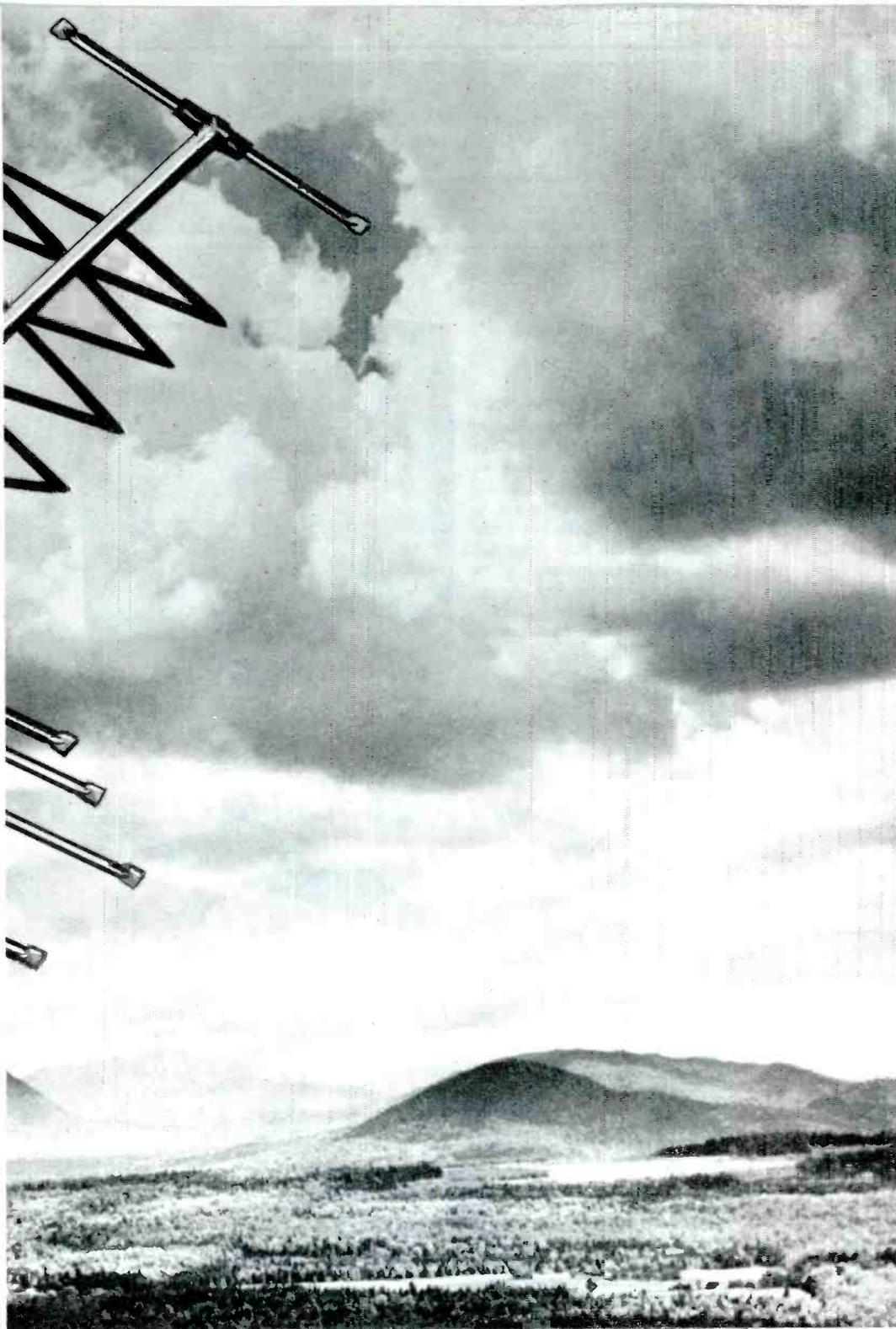JFD CANADA LTD.
51 McCormack Street
Toronto, Ontario, Canada





flattens mountains!

Merchandising reasons-why that turn prospects into profits!

Saturation PROMOTION! Repeat advertising impressions in leading newspapers and magazines sending thousands of antenna-replacement prospects into JFD service-dealer stores.

Co-op ADVERTISING! The biggest co-op program in TV antenna history. Hard-hitting newspaper mats, direct mail, radio-TV spots plus other traffic-pulling sales aids for profitable use in your own local market.

Top ACCEPTANCE! Because it's made by JFD—the antenna brand America knows best because it satisfies best.

Realistic PRICING! An honest antenna value priced at a non-inflated level. Gives you **more** antenna for your dollar.

Switch to the fabulous Satellite-Helix and be sure to get the lion's share of antenna installation profits in your area. Phone your JFD distributor now and see how.


REVOLUTIONARY NEW 28-ELEMENT DESIGN!

(no larger than other conventional fringe antennas) delivers unprecedented gain.




ROCK-OF-GILBRALTAR RUGGEDNESS!

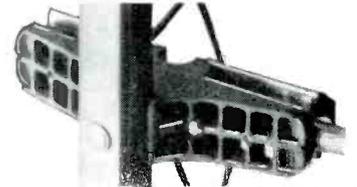Six 1/2 inch o.d. seamless aluminum elements. All 3/8 inch elements (over 30 inches) reinforced by 15 inch aluminum dowels.




UNBREAKABLE INSULATORS

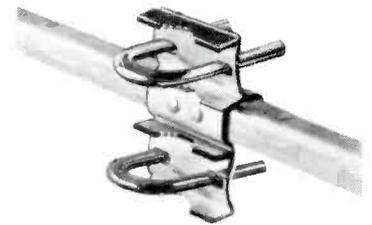made of low-loss weather-proof Kralastic B.



HEAVY-DUTY DOUBLE U-BOLT

and profile assembly for super-rigidity.

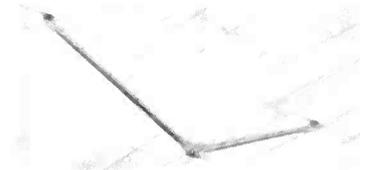

DOUBLE BOOM-BRACED

against sag and sway.

Introducing the balanced sleeve dipole

system...a giant step in TV antenna technology

- * Electrically enlarged capture area for as much as 35% greater gain on all channels.
- * New spatial relationship of parasitic and collector elements achieves up 15 to 1 (low band) and 18 to 1 (high band) front-to-back voltage ratios.
- * Multiple driver dipoles provide sharper directivity—cut down ghost and reflective pick-up.
- * Broadly resonant operation reduces reactance—leaves highly resistive 300 ohm impedance. Result: up to 95% of signal received becomes usable at set.
- * Flat band pass—ideal for color.
- * Wide vertical angle helps capture refracted signals in hilly terrain.

replacing METAL

Replacing a metal CRT with one of glass is more practical than you might think. First of all, metal tubes have generally proved to be short-lived and a nuisance to the servicing technician. On service calls, the substitution of tubes with power on is like picking the teeth of a lion who is awake and slightly hungry—you're apt to get bit at any time. Other considerations are the high cost, unavailability, and lack of aluminized screens on metal CRT's. An aluminized glass CRT and a mounting adapter kit such as the one used in this article are very often no more expensive than the metal CRT replacement.

Since it would be impossible to cover considerations for all of the TV receivers that have used metal CRT's, and since sets employing round metal tubes are quite old and should be retired from service, we are presenting a sample installation involving a 21" Arvin. Many other manufacturers have also used 21" metal CRT's.

Metal to Glass Conversion Chart

ORIGINAL TYPE	NEW TYPE	NOTES
17CP4	17BP4A 17JP4	Aluminized
17GP4	17FP4-A	Automatic Focus
17TP4	17HP4 A/B 17KP4 17RP4 17HP4/17RP4	
21AP4	21AWP4 21WP4 21ZP4A/B	
21DP4	21AUP4A/B	
21MP4	21AVP4 A/B 21AYP4 21ASP4 21AFP4 21BCP4	Typical Operation Anode = 14KV Anode = 14KV Anode = 16KV
	21BDP4 21XP4 21YP4	Built-in Ion Trap & Focus Magnet Internal Ion Trap 16KV 16KV
27AP4 27MP4	27SP4 27GP4 27EP4 27RP4 27NP4	Typical Anode = 18KV

Always Ground External Coating if Tube Is so Equipped

In addition to the contour of the face plate, the electrical design of the tube must be considered. In this chart, each metal tube is cross-referenced with glass units which are electrically and physically suitable.

1 Match Between CRT and Mask. One of the first things which must be considered when replacing a metal CRT with one of glass is the match between the mask and the tube face. All rectangular metal tubes have a spherical face shape, so the glass tube selected must also have this shape.




2 Mask Modifications. In many cases, no changes in the mask will be necessary; however, RCA and some other makes use the type of mask shown, requiring that it be modified slightly. These changes are not visible from the front and permit the slightly larger glass bulb to fit snugly in place.




3 Mounting Kit in Place. Once the proper glass tube has been selected, a mounting adapter kit (the one shown is made by Colman Tool and Machine Co.) is installed on the tube. Some set manufacturers also market kits specifically designed for their particular sets.


CRT's with GLASS

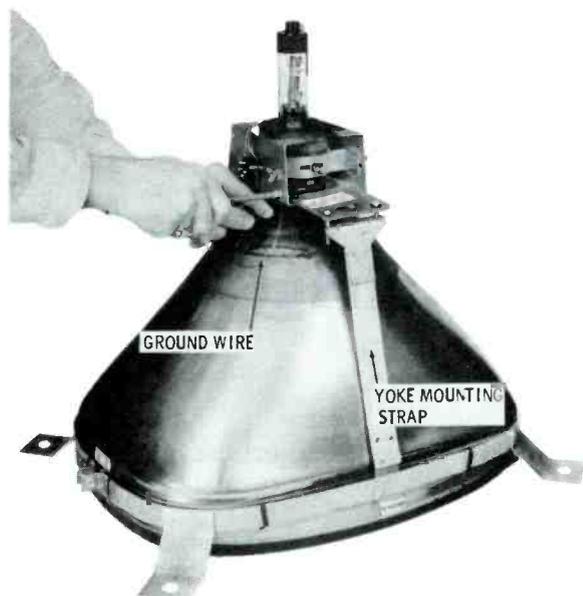

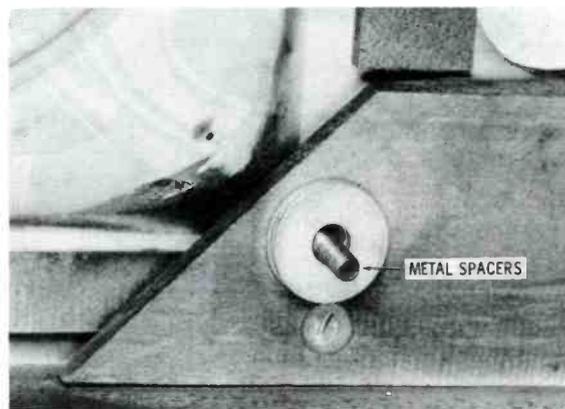
4 **Grounding the Outer Coating.** The yoke mounting is installed next and the grounding spring, furnished with the kit, is attached. Other necessary mounting hardware is usually supplied, including that for attaching the yoke mounting bracket.



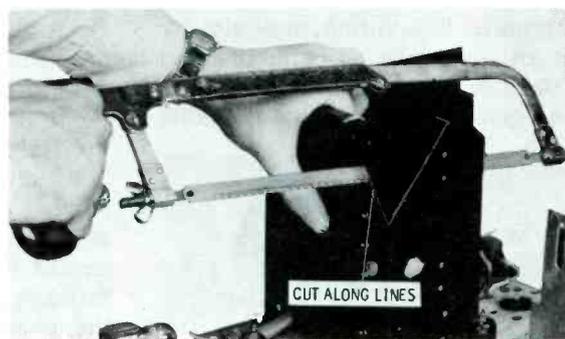5 **Mounting Bolt Spacers.** Spacers are supplied in the kit so that the thicker face of the glass CRT will not exert excessive pressure on the mask when the mounting nuts are installed.



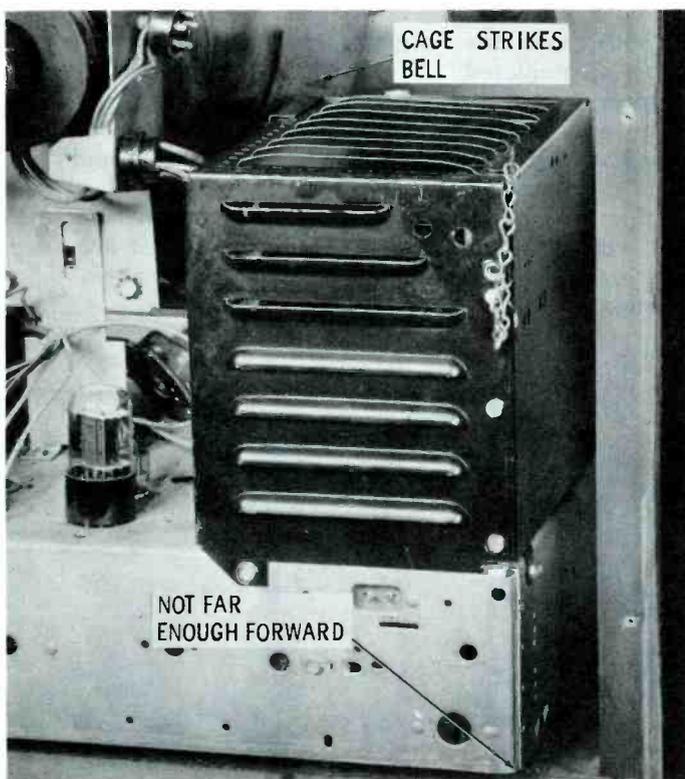7 **Cage Alterations.** The corner of the cage is removed and the top cover is then bent to cover the opening. This won't be necessary in all cases, but you should check for such unforeseen changes before talking conversion with the customer.



6 **Chassis Won't Fit.** Without any changes to the high-voltage cage assembly, this chassis won't go all the way into the cabinet due to the larger size of the glass bulb. Instructions for altering the high-voltage cage were included in the kit.



8 **Back Cover.** After cage modifications are completed, the chassis can be installed and, if necessary, the back cover adapted as shown to provide clearance for the neck (usually 1 to 2" longer) of the glass tube.



by Calvin C. Young, Jr.

hints on record changer servicing

One of the first problems that arises in the servicing of changers is that of holding or supporting the changer. It must be held level and allow for clearance of all moving parts; in addition, accessibility to all necessary adjustments and points requiring lubrication must be considered. The adjustable

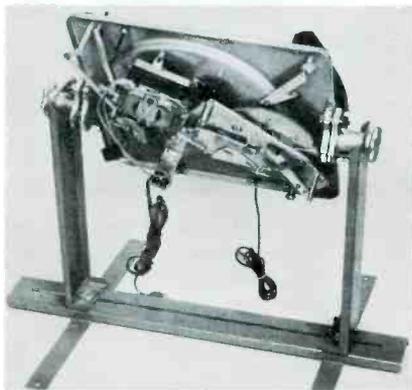


Fig. 1. General Cement phono stand being used to hold changer during servicing.

phono stand shown in Fig. 1 meets all of these requirements.

Another problem is determining which terminals should be used to apply power to the changer motor. Even though electrical diagrams aren't included in changer service data, it is a relatively simple matter to determine the proper hookup. Refer to the drawings in Fig. 2, which are the electrical circuits of the Admiral and V-M units, and note that, in both cases, the circuit to the motor is completed through the AC power switch on the changer. If, for any reason, you aren't sure just which two terminals should be connected to the AC line, connect an ohmmeter between one set of terminals and then another while operating the on-off switch. The right set of terminals will produce a reading of approximately 30 ohms (motor winding resistance) with the

switch in the on position, and infinite resistance in the off position.

The next problem is how to make the AC power connections, since the plugs are not all of the same size and type. An AC cord equipped with insulated alligator clips and a dpst switch (Fig. 3) solves this problem nicely. The switch permits the alligator clips to be connected or disconnected without having to unplug the cord.

Let us now consider the extra tools and equipment required in changer servicing. Sets of small wrenches, screwdrivers and cross-slot drivers are required, as is an assortment of cleaners and lubricants. Sizes of the tools are as follows: open-end wrenches— $\frac{1}{4}$ " to $\frac{7}{16}$ "; screwdrivers— $\frac{1}{8}$ " \times 8", $\frac{1}{8}$ " \times 12" and $\frac{3}{16}$ " \times 10"; cross-slot drivers—No. 0, 1 and 2. In the cleaner category, carbon-tet and

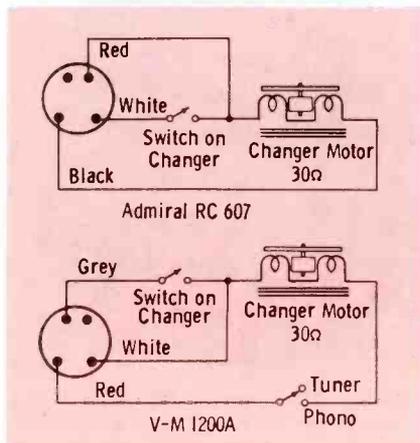


Fig. 2. Electrical circuits of Admiral and V-M changers showing AC connections.

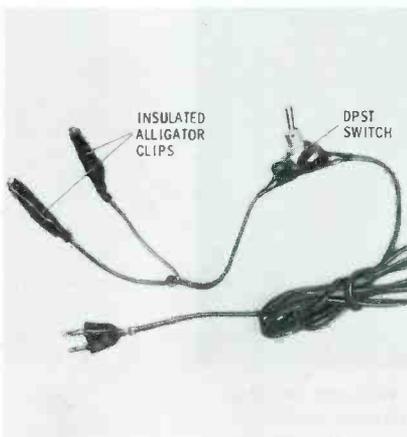


Fig. 3. AC cord with dpst switch and insulated clips for power connection.

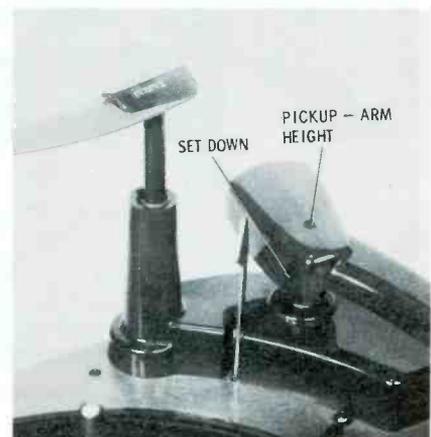


Fig. 4. Set-down and pick-arm height adjustments on Admiral RC 607 changer.

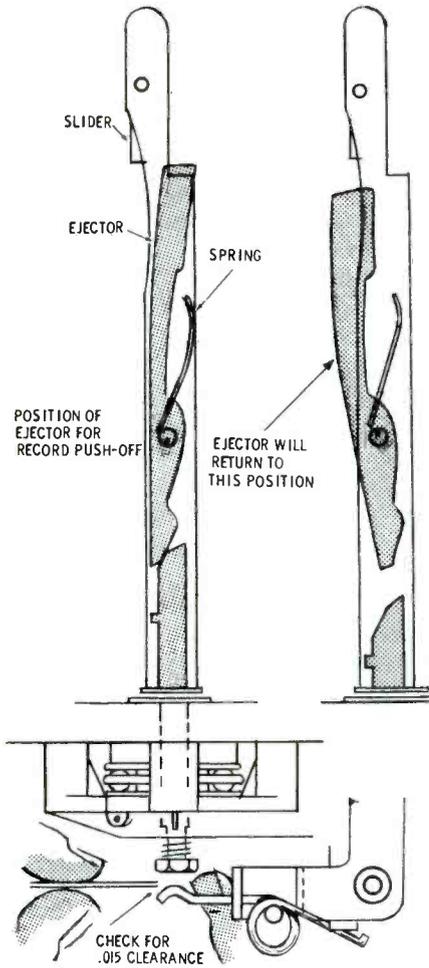
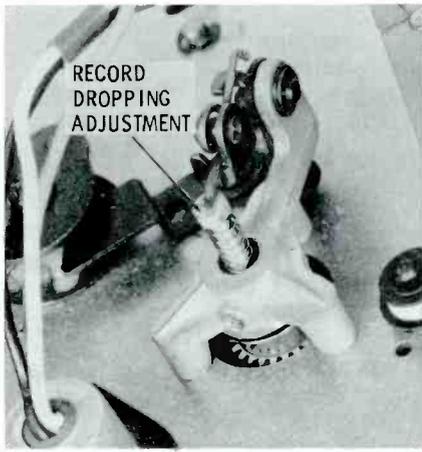


Fig. 5. RC 607 record-dropping adjustment. Drawing outlines setup procedure.

denatured alcohol are suggested solutions. Light oil (SAE 20), "Lubriplate," and "Cosmolube" No. 1 (Admiral part no. 418A50) will satisfy lubrication requirements.

Other items normally needed for changer servicing are crocus cloth (fine carborundum dust on cloth backing), assorted "C" clips, rubber grommets, and a small brush and pan set for cleaning parts.

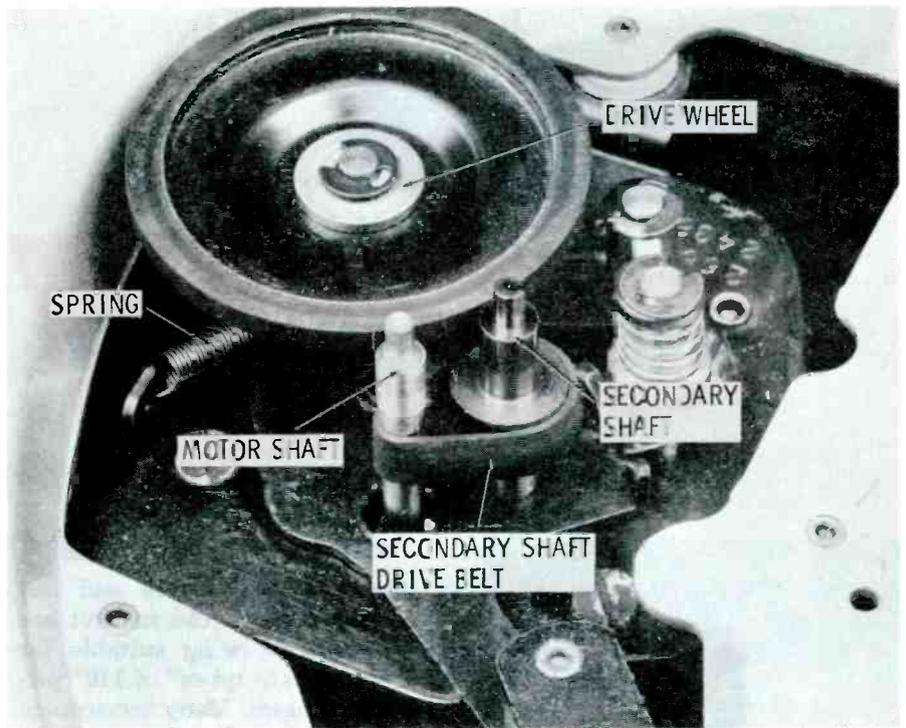


Fig. 6. Drive assembly on RC 607. Both motor and secondary shafts are stepped.

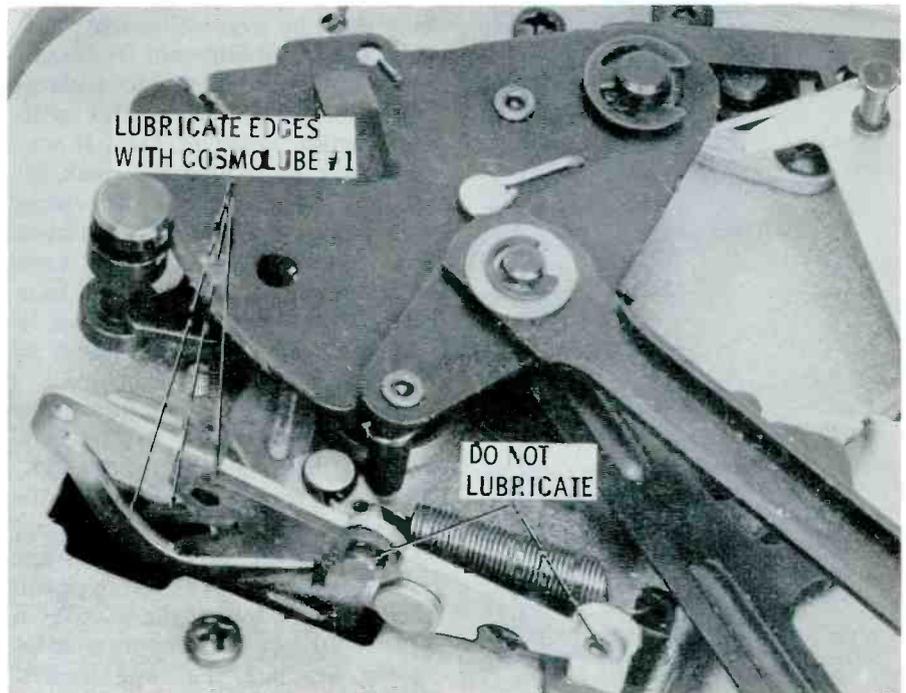


Fig. 7. Set-down index assembly on RC 607 requires no oil on two pivot points.

Cleaning and Lubrication

There are two reasons why a changer needs cleaning and re-lubricating: (1) Dust has contaminated the lubricant, or (2) extended operation causes a varnish to form on the bearing surfaces, or the non-liquid lubricant has hardened on sliding parts. In either event, the first step is to remove the necessary parts and clean the bearing surfaces with carbon-tet or another grease sol-


vent. If the surfaces are free of corrosion, relubricate as required. Be sure all excess oil is wiped away to avoid getting it on the rubber drive wheels or other driving surfaces. If corrosion is found, use crocus cloth to clean the part, soak it in solvent and then lubricate as necessary. In the case of porous bronze bearings, a drop or two of SAE 20 oil is usually all that is required. If any oil should

• Please turn to page 71


servicing

NEW DESIGNS

by Thomas A. Lesh

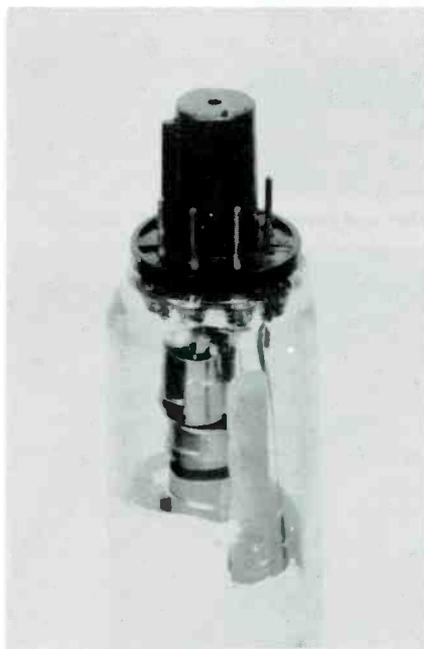

(A) Small-button type.

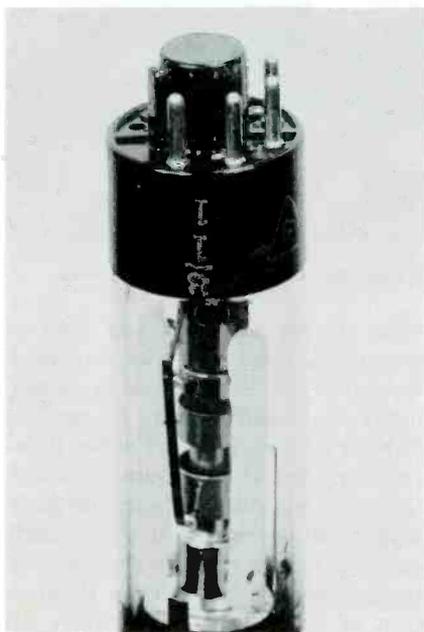

(B) Shell type.

Fig. 1. 110° picture tube bases.

110° Picture Tube Bases

Several CRT testers and test adapters now on the market are advertised as being suitable for use with "both types" of 110° picture tube bases. Many servicemen are probably unfamiliar with the differences between the two, and may even be wondering why 110° tube bases are different from conventional types in the first place.

To make possible a CRT with a deflection angle of 110°, it was necessary to reduce the neck diameter. (April, 1957, "Servicing New Designs.") The new thin neck does not have enough base area to accommodate the duodecal base and socket we are accustomed to seeing on 70° and 90° tubes, so new bases had to be designed.

Most types of 110° picture tubes are equipped with the "small-button" base shown in Fig. 1A. The pins, like those in miniature receiving tubes, are slender and sealed directly into the glass envelope of the tube. Fitted over the pins and bonded to the glass is a plastic button that supports a locating key for the tube socket. The latter is a lightweight plastic cylinder about the same length as the key and the same diameter as the base. The chief advantage of the small-button base is compactness, and this ties in with the main purpose of the 110° tube design—to minimize its over-all length in order to reduce cabinet depth as much as possible.

The "shell" base shown in Fig. 1B closely resembles the familiar conventional design except for its small diameter. The 17BVP4, 17BWP4, and 21CQP4 tubes employed in Sylvania and Philco

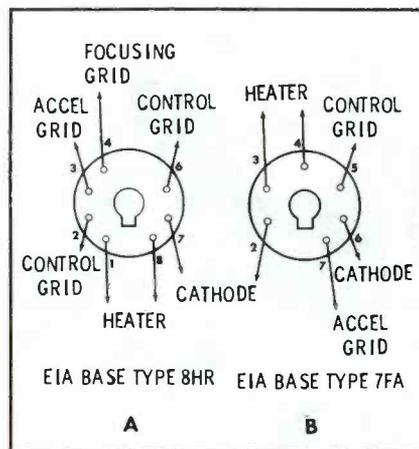


Fig. 2. Basing diagrams for 110° tubes.

receivers are the principal 110° types having shell bases.

Pin connections are arranged differently in the two varieties of 110° tubes. The small-button base shown in Fig. 2A has room for 8 equally-spaced pins, but the pin 5 position is blank. The control grid is internally connected to both pins 2 and 6, but pin 2 is usually the only one having an active socket connection. Fig. 2B is a diagram of the 110° shell base. Note that there is space for 7 pins but that the pin 1 position is blank. The single connection to the control grid is made through pin 5.

Regardless of base type, the necks of 110° tubes are more fragile than those on other types of CRT's; so be sure to use a little extra caution when removing sockets or otherwise handling the tubes.

Color TV Chassis

RCA's latest color TV models have several interesting new features, including more precise horizontal convergence adjustments, a redesigned color killer circuit, and a 3-stage sound section utilizing a 6DT6 quadrature-grid detector. In general, the new receivers can be described as conservatively-designed, deluxe models.

The CTC7 chassis used in the new 800 Series is vertically mounted on one side of the cabinet and is noticeably more compact than previous designs. Most of the various set-up adjustments are in new locations. All the dynamic convergence controls are on a printed-circuit subchassis which is connected to the main receiver chassis by a long cable. While



**faster...easier
more efficient**



KRYLON Crystal-Clear Acrylic Spray Coating

... standard equipment for TV and radio servicemen.

- Prevents corona in high voltage section
- Keeps lead-in connections tight
- Prevents rusting and pitting of antenna
- Goes on in seconds—dries in minutes



KRYLON Spray Enamels

(19 decorator colors) ... perfect for touchup and maintenance work ... covers practically any surface ... dries in minutes.



KRYLON Varnish Sprays

... HIGH-GLOSS and SATIN-FINISH (alcohol and hot liquid resistant) for professional finish ... dries in minutes.



KRYLON Dulling Spray

... a "must" in TV, movie and photographic studios.

- Eliminates glare, bothersome high-lights
- Simplifies lighting arrangements
- Easy to apply ... sets in seconds
- For both black and white and color use



KRYLON Foaming Window Spray

... removes finger marks and dust from TV masks and screens ... good antistatic properties.



KRYLON Rust Release Penetrating Oil Spray

... instantly, easily frees rusty bolts and nuts and "frozen" parts ... lubricates as it penetrates.



The choice of professionals
Call your jobber or write
KRYLON, INC., NORRISTOWN, PA.


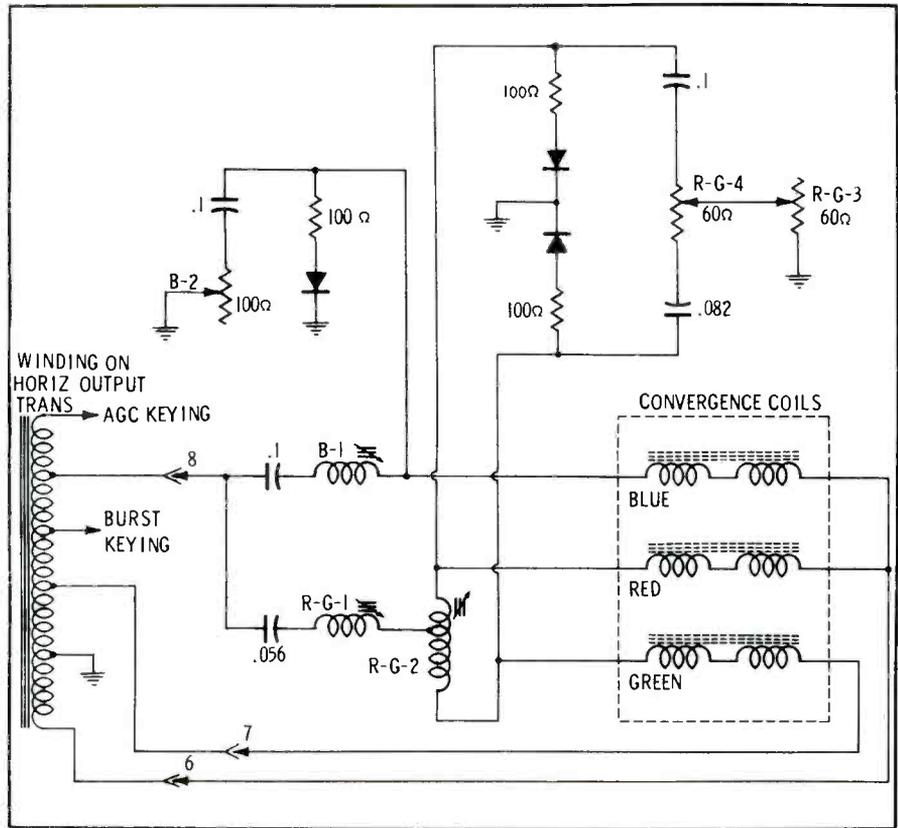


Fig. 7. Horizontal convergence circuits used in RCA Victor Chassis CTC7.

amplifier. This is accomplished by a "killer killer," a triode section of a 6BN8 connected as a diode detector. In the absence of a color signal, the only input to this latter stage is a sample of the CW output signal of the 3.58-mc oscillator, fed to the grid and plate of the 6BN8. This signal alone is insufficient to cause conduction of the detector, and so there is no effect on the 6U8A. But if a color signal arrives, a 3.58-mc burst signal appears at the burst transformer and is fed from there to the cathode of the killer detector. This signal is 180° out of phase with the grid-plate signal during normal color operation. The killer detector is biased so that it will conduct only for the short time that the cathode signal is near its negative peak and the grid-plate signal is near its positive peak. The result of this conduction is a negative output voltage which is fed to the grid of the 6U8A, cutting it off. Since the detector requires two different input signals with a definite phase relationship to drive it into conduction, it tends to be insensitive to noise pulses or other random signals that might produce color interference in monochrome programs.

An examination of the circuits on the small convergence subassembly shows, first of all, that there are three identical circuits (wired in parallel) for vertical convergence of the three electron beams. A typical circuit for one beam appears in Fig. 6. As in earlier models, a parabola-shaped waveform is obtained from the cathode of the vertical output tube via the "Amplitude" controls and then modified by a sawtooth wave which is fed from the vertical output transformer through the "Tilt" controls.

The horizontal convergence circuits have been redesigned to provide relatively independent adjustments for beam convergence at the left and right sides of the screen. The basic convergence waveform is produced by applying a pulse from the horizontal output transformer to a resonant circuit on the convergence subchassis. (See Fig. 7.) For the blue beam, this resonant circuit is made up of the blue convergence coils in series with adjustable coil B-1 and a .1-mfd capacitor. Slug B-1 affects the phase of the waveform; for the most part, it alters the pattern traced by the blue beam toward the right side of the picture. A

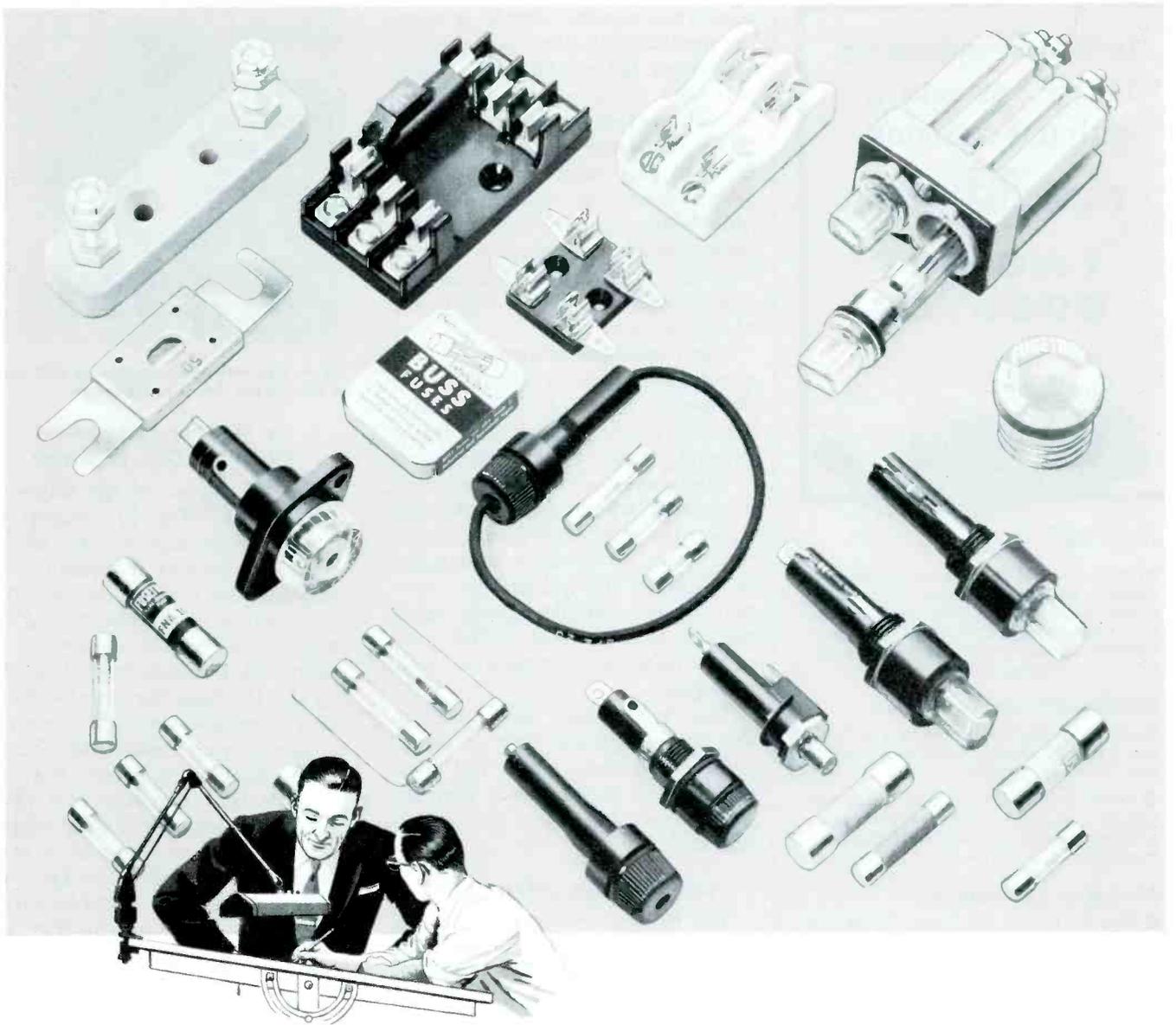

For Safe, Dependable Electrical Protection

. . . Standardize on BUSS Fuses!

To make sure of proper operation under all service conditions . . . every BUSS fuse is tested in a sensitive electronic device that automatically rejects any fuse not correctly calibrated, properly constructed and right in all physical dimensions.

This careful testing is your assurance BUSS fuses will provide equipment with maximum protection against damage due to electrical faults.

Just as important, BUSS fuses will not give a false alarm by blowing need-

lessly. Shutdowns due to faulty fuses blowing without cause are eliminated.

In sales and service, it is just good business to standardize on BUSS fuses.

By *selling* dependable BUSS fuses, sales organizations are helping safeguard their reputation as a reliable source for electrical supplies.

By *installing* BUSS fuses, service dealers are making sure the fuses they

install will not cause costly, unnecessary call-backs.

Why take a chance on anything less than BUSS quality in fuses? There is a complete BUSS fuse line to meet all your service needs.

For more information on the complete line of BUSS and FUSETRON Small Dimension Fuses and Fuse-holders, write for bulletin SFB.

Bussmann Mfg. Division McGraw-Edison Co. University at Jefferson, St. Louis 7, Mo.

BUSS fuses are made to protect—not to blow, needlessly

857



A COMPLETE LINE OF FUSES FOR HOME, FARM, COMMERCIAL, ELECTRONIC, AUTOMOTIVE AND INDUSTRIAL USE.

better reception on
1, 2 or 3 tv sets...
with one antenna

NEW  **B-23**

**TWO-SET
BOOSTER**



only \$23.95

From B-T comes the most important advance in better TV reception for 1958 — a broadband TV amplifier that boosts signal strength on all VHF channels and operates 1, 2 or 3 TV sets with one antenna — no tuning required.

Combines two functions in one —

● **BOOSTS** signal strength on 1 or 2 TV sets — up to 6 db gain operating two TV sets from one antenna.

● **COUPLES** 2 or 3 TV sets — using the present antenna. Outperforms non-powered couplers in any reception area by more than 2 to 1.

Check these B-23 features:

- Ideal for color — add a color TV set and keep present black-and-white set, use the same antenna — the result, sharper, clearer pictures on both sets
- Low noise figure — designed to work with new VHF sets
- Reduces interference
- Easily installed at antenna terminals of set
- Automatically amplifies channels 2-13
- Ideal small TV system

For operating 3 to 8 TV sets, use the B-T Labs DA8-B — more than 10 db gain on all VHF channels.

The DA8-B Distribution Amplifier is a broadband, all-channel unit that requires no tuning, impedance matching devices, pre-amps or other special fittings. Ideal for all small TV systems (garden apartments, motels, TV showrooms). Approved for color. Only \$94.50

The B-23, the DA8-B, and other B-T quality engineered products, are available at electronic parts distributors.

For further information, use coupon.

 **BLONDER-TONGUE LABS., INC. PF 5**
9 Alling Street, Newark 2, New Jersey

Please send me literature covering:

- B-T B-23 B-T TV Accessories

Name _____

Address _____

City _____ Zone _____ State _____

somewhat similar circuit is used for simultaneous control of the red and green beams. Slug R-G-1 adjusts the phase of the waveform in both the red and green horizontal convergence coils and therefore adjusts both the red and green beams in relation to the blue beam. Slug R-G-2 is a balancing adjustment which produces final convergence between the red and green beams at the right side of the screen.

The remaining controls are potentiometers which regulate the discharge time of RC circuits through crystal diodes. Generally speaking, they regulate the shape of that portion of the convergence waveform which affects the left side of the picture. B-2 adjusts the blue beam to produce a straight blue line, R-G-3 adjusts the other two beams simultaneously with respect to blue, and R-G-4 provides final convergence of red and green.

The "right" and "left" controls are not completely free of interaction with each other, but they do provide more exact convergence than has been previously obtainable.

Line Voltage Adjustment

The AC power systems in some localities are too "generous with the volts," and a steady overdose of power-line voltage causes excess wear and tear on television sets if they are not protected in some manner.

The Magnavox 26 Series chassis features built-in provisions for counteracting high line voltage. As shown in Fig. 8, a link can be connected to either of two terminals—"117V" for normal operation, or "127V" when voltage reduction is desired. In the latter position, extra turns are added to the primary of the power transformer, decreasing the effective step-up ratio from primary to secondary. This prevents B+ and heater voltage from increasing excessively when the line voltage rises to high levels.

The link is not a voltage regulator and cannot compensate for severe power-supply fluctuations. Nevertheless, it is useful in situations where the power-line voltage characteristically runs higher than normal.

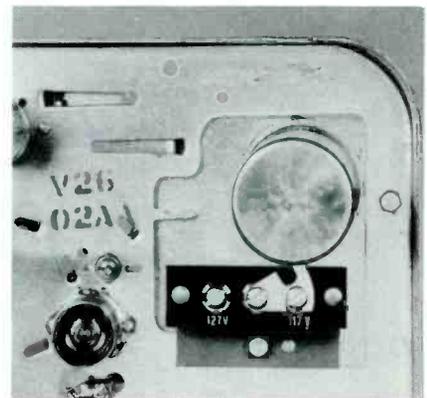


Fig. 8. Line-voltage adjustment link used in Magnavox 26 Series chassis.

**It Had to Happen—
TV With One IF Stage**

The "IF strip" of the Olympic Chassis DY (Fig. 9) consists of a pentode section of one 6AZ8. Adequate gain is maintained by reducing the over-all bandwidth, as indicated in the accompanying response curve. The narrowing of bandwidth not only permits peaking the IF stage for greater gain, but also enables the video detector to operate more efficiently. Since shunt capacitance across the detector output becomes less of a problem when the highest video frequencies do not have to be preserved, the video detector load resistor can be made larger in value than usual—18K ohms in this circuit. With a higher value of load resistance, a relatively large output signal can be developed.

AGC is not applied to the IF stage but is fed to the 2CY5 tetrode RF amplifier. There are three IF adjustments, all tuned to 44.5 mc. One of these, which is not shown in the schematic, is in the mixer plate circuit; it's accessible at the top of the tuner.

Other features of this chassis include a transformer-type power supply with 5U4G rectifier, a 21ALP4 picture tube, and a 6DT6 sound detector. ▲


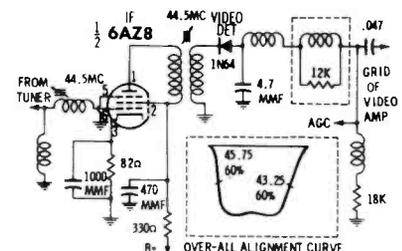


Fig. 9. IF and video detector circuits of Olympic Chassis DY. Inset—Over-all IF response curve.

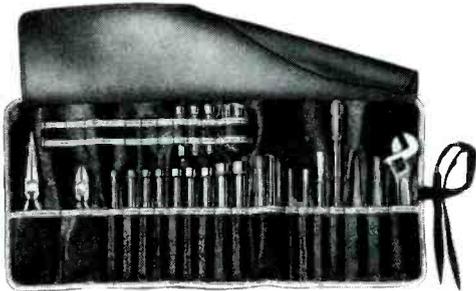

Quality Tools

ARE PREFERRED BY THE EXPERTS



New! No. 99 S.M. Kit — 21 tools


They Know Quality Tools do the job better, faster, retain their efficiency longer . . . and cost less in the long run.

You Can Choose XCELITE Tools with Confidence! . . . properly designed, skillfully made of the finest materials and fully guaranteed.

In addition to regular items and handy kits, XCELITE continually introduces new and original tools . . . we have many *Firsts!*

"99" TOOLS



cover the full range of electronic servicing — 3 popular "99" roll kits — the 26 individual "99" tools shown —

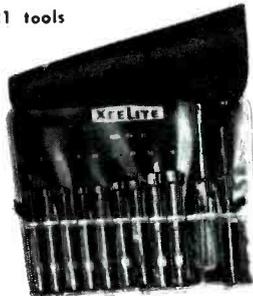

No. 99-JR Roll Kit — 11 Tools

No. 99-PR Roll Kit — 13 Tools

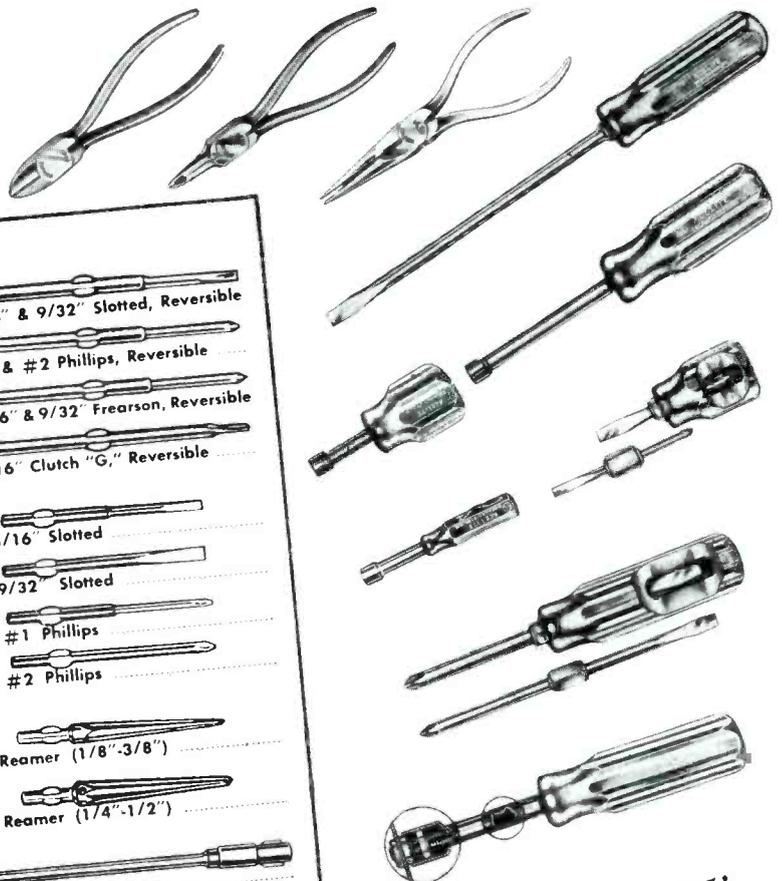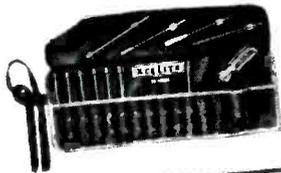See Your Distributor for the Complete Line!



SERIES "99" TOOLS

No. 99-1 Handle (Regular)

No. 99-2 Handle (Junior)

No. 99-3 Handle (Stubby)

No. 99-6 3/16" Nut Driver

No. 99-7 7/32" Nut Driver

No. 99-8 1/4" Nut Driver

No. 99-9 9/32" Nut Driver

No. 99-10 5/16" Nut Driver

No. 99-11 11/32" Nut Driver

No. 99-12 3/8" Nut Driver

No. 99-14 7/16" Nut Driver

No. 99-16 1/2" Nut Driver

No. 99-81 3/16" & 9/32" Slotted, Reversible

No. 99-82 #1 & #2 Phillips, Reversible

No. 99-83 3/16" & 9/32" Frearson, Reversible

No. 99-84 3/16" Clutch "G," Reversible

No. 99-811 3/16" Slotted

No. 99-812 9/32" Slotted

No. 99-821 #1 Phillips

No. 99-822 #2 Phillips

No. 99-38 Reamer (1/8"-3/8")

No. 99-39 Reamer (1/4"-1/2")

No. 99X10 Extension

No. 99-58

Stubby Nut Drivers No. 99-510

No. 99-512

Parts Show Booth 225!

XCELITE, INCORPORATED

ORCHARD PARK, NEW YORK

In Canada — Charles W. Pointon Ltd., 6 Alcina Avenue, Toronto, Ontario

XCELITE
Quality Hand Tools
PREFERRED BY THE EXPERTS

FREE from HOWARD W. SAMS!...valuable all-steel file cabinets with your purchase of **PHOTOFACT**—
the world's finest TV-Radio Service Data



FREE! FOR REGULAR PHOTOFACT SUBSCRIBERS

You get your File Cabinets FREE if you are a regular subscriber to PHOTOFACT Folders and buy all new Sets as issued each month. Your Folders come to you in special envelopes, each including a "Bonus Certificate." Sixty (60) of these entitle you to a single-drawer File Cabinet ABSOLUTELY FREE...



FREE! FOR PHOTOFACT LIBRARY PURCHASERS

Get FREE File Cabinets as you complete your profit-building PHOTOFACT Library... here's how:



FREE!
Single-Drawer File Cabinet with your purchase of 60 Sets of PHOTOFACT Folders.
Cabinet Worth... \$895



FREE!
Two single-drawer File Cabinets with your purchase of 120 Sets of PHOTOFACT Folders.
Cabinets Worth... \$1790



FREE!
Three single-drawer File Cabinets with your purchase of 180 Sets of PHOTOFACT Folders.
Cabinets Worth... \$2685



FREE!
Four single-drawer File Cabinets with your purchase of 240 Sets of PHOTOFACT Folders.
Cabinets Worth... \$3580

NEW EASY-BUY PLAN

It's easy to complete your present PHOTOFACT Library or start a PHOTOFACT Library. Use the EASY-BUY PURCHASE PLAN:

- NO INTEREST
- NO CARRYING CHARGE
- AS LITTLE AS \$10 DOWN
- UP TO 24 MONTHS TO PAY

Get the world's finest TV-Radio Service Data... get FREE File Cabinets with your PHOTOFACT purchases...take advantage of the Easy-Buy Plan. See your Sams Distributor today, or write to Howard W. Sams for full details.

get the full details of the HOWARD W. SAMS money-saving way to build your complete profit-making PHOTOFACT Library!

HOWARD W. SAMS & CO., INC.
2201 E. 46th St., Indianapolis 5, Indiana



Send details on your FREE File Cabinet offer and EASY-BUY Plan.

I'm a Service Technician: full time; part time

My Distributor is: _____

Shop Name: _____

Attn.: _____

Address: _____

City _____ Zone _____ State _____



3 Million Transistor Portables

*Mean Big Battery Business
and Bigger Dealer Profits*

That's a lot of transistor portables that are going to be needing batteries this year . . . nearly three times as many as a year ago, and the figure is still growing.

For this skyrocketing new market, Mallory offers a complete line of transistor and portable radio batteries.

Mercury batteries, pioneered by Mallory, last longer, give steadier volume than ordinary batteries. Mallory Zinc-Carbon batteries are dependable and economical—meet all the requirements of today's modern portable radio sets, and flashlights as well.

Mallory Battery Company
A Division of



In Canada, Mallory
Battery Company of
Canada Limited,
Toronto 4, Ontario

- Capacitors • Vibrators • Resistors • Controls • Switches • Filters
- Rectifiers • Power Supplies • Mercury and Zinc-Carbon Batteries

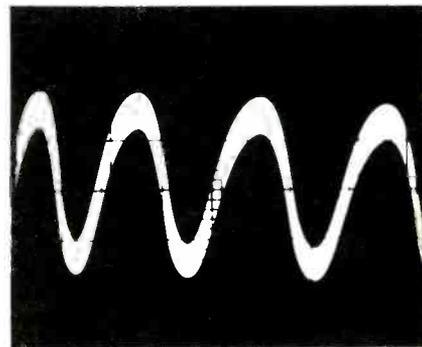


Fig. 2. This is the AC signal present at the arm of the AFC balance control when the receiver breaks color sync.

How is the AC Waveform Controlled?

The AC color-sync waveform seen in Fig. 2 is controlled by a filter network such as that shown in Fig. 3. First of all, the output from the AFC balance control is partially bypassed to ground. This eliminates the higher frequencies outside the control range of the oscillator since they would only interfere with its desired action. The 0.01-mfd capacitor, 33K-ohm resistor and 0.22-mfd capacitor form an antihunt network which prevents the color-sync system from feeding back positively and breaking into a squegging action.

For example, if the 0.01-mfd capacitor opens up, you cannot obtain color sync. The DC meter will indicate that operation is okay, but the scope will show that there is a large squegging voltage in the sync channel. This is due to a positive feedback, causing the system to hunt continuously and uncontrollable rainbows to appear on the screen.

If the 0.22-mfd capacitor opens up, color sync can still be maintained, although the stability will not be as great as with the capacitor functioning normally. A beginner might overlook the pos-



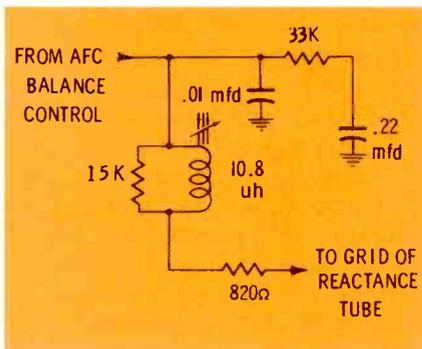


Fig. 3. How well the chroma oscillator pulls in depends upon the various components in this filter network.

sibility of an open 0.22-mfd capacitor and waste endless time looking for other causes of impaired pull-in.

Another thing to keep in mind, and that is we must have 3.58-mc voltage on the grid of the reactance tube to maintain oscillator control. If the 10.8- μh inductance becomes shorted, the 3.58-mc feedback voltage will be shorted to ground by the 0.01-mfd capacitor and color sync will be lost completely. The 15K-ohm resistor lowers the Q of the choke so that it will have ample impedance when the oscillator is slightly off frequency and when slight changes in the input grid impedance of the reactance tube tend to detune the inductor slightly.

Check the Filter

Hence, when color sync is bad, and usual measures do not restore proper pull-in, look to the filter circuit. One of the best ways to do this is with a scope. Published waveforms are not available, but after a bit of experience, you will have little trouble in buzzing through a color-sync filter with a scope and isolating the trouble. Oh yes—and don't forget to use a low-capacitance probe! ▲



Buy Mallory "Gems" in the new self-service Five-Pack

Mallory "Gem" capacitors now come in a convenient Five-Pack which has a sliding transparent cover that lets you remove exactly the number of capacitors you need, slides back in place to keep your spare "Gems" dust-free, with lead wires undamaged. You always know exactly how many capacitors of what values you have on hand. You can hang the "Gem" Five-Pack over your work bench within easy reach . . . ready for use.


Mallory "Gems" give you extra-cost features without premium price: • *Locked-in leads* can't loosen or open when pulled, even under soldering iron heat. • *"True center"* construction prevents premature failure. • *Moisture-proof* case of a high grade mica-filled bakelite gives real protection against humidity.

Use Mallory "Gems" for every by-pass, filter or buffer application. Get them today from your Mallory distributor.

- Capacitors—Electrolytic, Paper, Ceramic
- Controls & Resistors
- Vibrators
- Mercury & Zinc-Carbon Batteries
- Switches
- Power Supplies

P. R. MALLORY & CO. Inc.
MALLORY

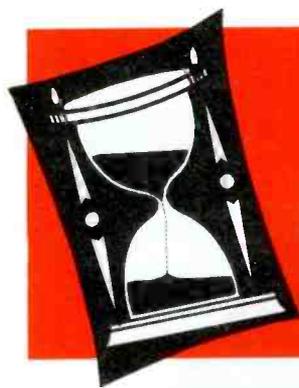P. R. MALLORY & CO. Inc., INDIANAPOLIS 6, INDIANA



QUICKER SERVICING

by Calvin C. Young, Jr.

Checking Phono Cartridge Styli

A phono cartridge stylus is not a permanent fixture—even a diamond will eventually show signs of wear. Generally speaking, a sapphire needle is satisfactory for about 50 hours of playing time on records in average to good condition, and an osmium tip is good for about half as long. A good quality diamond should show evidence of little or no wear at 400 hours if used on records in good condition. Badly-worn or dirty records will materially shorten the life of any needle.

When new, a stylus tip is shaped as shown in Fig. 1. A worn stylus will have flat spots on the tip, resulting in sharp edges which cause rapid and extensive record damage. You'll be doing your customer a favor by offering to check any stylus that has been in service for more than three months.

This brings up the question, "How do you check a stylus for wear?" It's too small to be checked with the naked eye. The answer is almost obvious—a microscope, 60-power or greater, must be used. Various needle manufacturers have suitable units available at nominal costs.

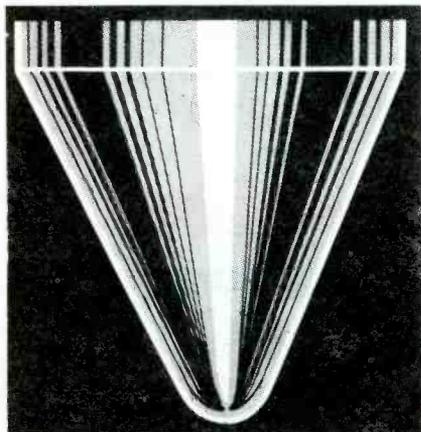


Fig. 1. Oversized drawing of stylus shows the shape it should have when new.

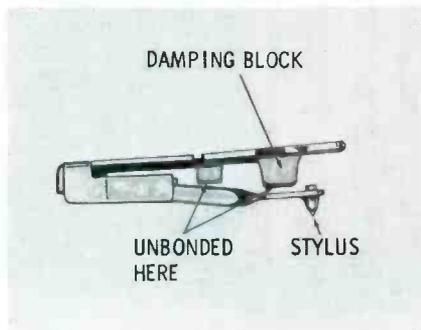


Fig. 2. Enlargement of 1-mil stylus assembly shows unbonding at damping block.

Wear is not the only thing that will make it necessary or desirable to replace a stylus. For example, the owner of a new hi-fi outfit called recently to complain of a loss of volume and groove-skipping. The stylus was a 1-mil diamond used in a variable-reluctance cartridge. Since the cartridge was one of the turn-over type, the technician tried the 1-mil side on a 33-rpm record and the 3-mil side on a 78-rpm record. Volume and tracking were satisfactory at 78 rpm, but the customer's complaint was verified at 33 rpm. The diamond was replaced with a new stylus, resulting in normal volume and tracking. An enlarged photograph (Fig. 2) shows that the stylus tip had become unbonded from the damping block. This, not a worn or broken tip, was the cause of the trouble.

Another point to look for when checking a stylus is proper alignment of the tip with the remainder of the assembly, since the angle at which the tip meets the record grooves must be accurate.

Rapid Tube Failure in Portable Radios

Each spring, when people are outdoors for longer periods of time and portable radios are pressed into service, there is a general rush for repairs. In many in-

stances, insertion of a new tube or two and a new battery seems to be all that is needed. However, this doesn't necessarily mean that the actual trouble has been cured; in fact, chances are that it hasn't.

Referring to the diagram in Fig. 3, filament power is applied via a voltage-dropping resistor from the B+ supply when the portable is operated from the AC line. The 1810-ohm resistor in series with the tube filaments serves as a voltage-dropping element so that the required 6 volts is applied across the filaments. The voltages indicated are obtained only at a normal line voltage of 117VAC and may actually be greater at higher input levels. This is permissible, as you will notice if you add up the individual filament ratings (1.4, 1.4, 1.4 and 3 = 7.2). If, for any reason, the voltage across the filament string should exceed 7.2 volts for an appreciable length of time, tube life will be shortened materially.

It is possible that a very innocent act, such as replacing the metallic rectifier with one having a more efficient rating, could raise the filament voltage above the danger level; or the dropping resistor could decrease in resistance.

If a portable radio employs a battery-saver switch, it should be placed in the *strong battery* or *save battery* position when a new battery is installed. This introduces a resistor in series with the battery and filaments and reduces the voltage to a safe level. Voltage will drop as the battery ages, and the switch can then be placed in the normal position. Failure to follow this procedure will place excessive voltage across the filaments when the battery is new.


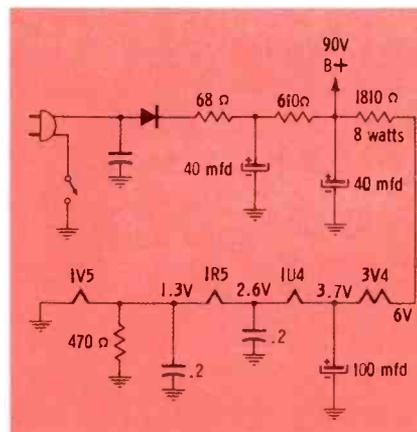


Fig. 3. Typical schematic of filament circuit used in modern portable radios.

For
“TOPS”
 in

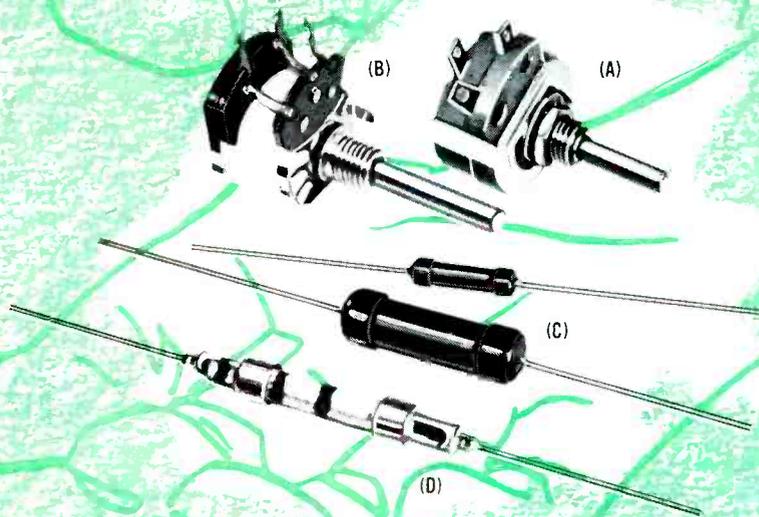

TRANSISTORIZED CIRCUITS

Clarostat

Miniaturized Controls and Resistors

So typical of Clarostat's application engineering! These miniaturized controls and resistors are geared to transistorized circuits. They achieve the highest degree of space-saving consistent with high level of performance.

It takes specialized skill and long experience to produce such tiny controls and resistors. Clarostat, "The House of Resistors,"* places over three and a half decades of collaboration with electronic designers, engineers and manufacturers, at the disposal of transistor users. Count on Clarostat!

Typical Clarostat "Miniatures" . . .

- (A) Series 49 wire-wound potentiometer. Only $\frac{25}{32}$ " dia. Molded phenolic casing. With or without switch. Single or dual. 1.5 watt rating. 1 to 20,000 ohms. Also Series 48 composition-element. $\frac{5}{8}$ " dia. 0.2 watt rating. Linear, 200 ohms to 5 megohms; tapered, 1500 ohms to 2.5 megohms. With or without switch. Single or dual.
- (B) Boiled-down version of popular $\frac{1}{8}$ " control, Series 44 is no bigger than a dime! 0.2 watt rating. 0.015 lb. 500 ohms to 5 megohms. With or without switch. Popular in hearing aids, pocket radios and other compact assemblies.
- (C) Fixtohm* deposited carbon precision resistors. $\frac{1}{4}$, $\frac{1}{2}$, 1 and 2 watt ratings. Plus/minus 1% tolerance. Extremely stable. Excellent characteristics. Popular in critical electronic assemblies and fine instruments.
- (D) Glasohm* flexible power resistors. Wire winding on fiber-glass core. Fiber-glass braided covering. Axial pigtail leads. 2-watt rating. Plus/minus 10% standard tolerance. 5 to 2000 ohms.




Ask for literature. either from your local Clarostat distributor, or from us. Submit your transistorized requirements and problems to us.

*Reg. U. S. Pat. Off.


Controls and Resistors
 CLAROSTAT MFG. CO., INC. • DOVER, NEW HAMPSHIRE
 In Canada: CANADIAN MARCONI CO., LTD., Toronto 17, Ont.

TRANSFORMER NEWS FROM TRIAD

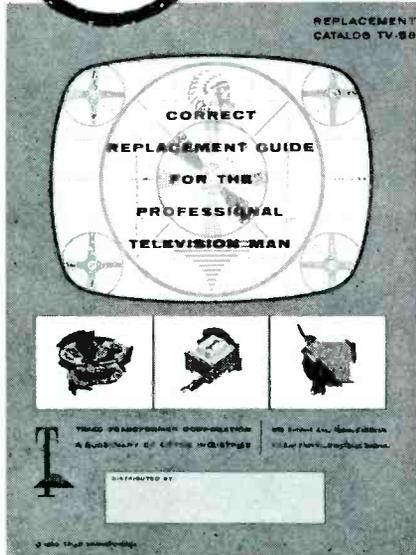

**NEW
REPLACEMENT CATALOG
& TELEVISION GUIDE
NOW AVAILABLE**

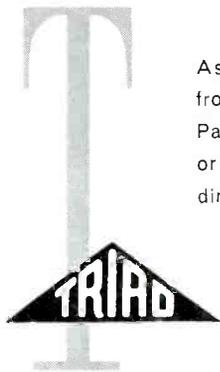The new TV-58 catalog & guide lists all of Triad's new replacement transformers...lists thousands of recommendations for television receivers...lists hundreds of recommendations not previously covered.



Ask for your copy from your Triad Parts Distributor—or write to us direct—

TRIAD TRANSFORMER CORPORATION
4055 REDWOOD AVE. | 812 E. STATE STREET
VENICE, CALIFORNIA | HUNTINGTON, INDIANA

A SUBSIDIARY OF LITTON INDUSTRIES

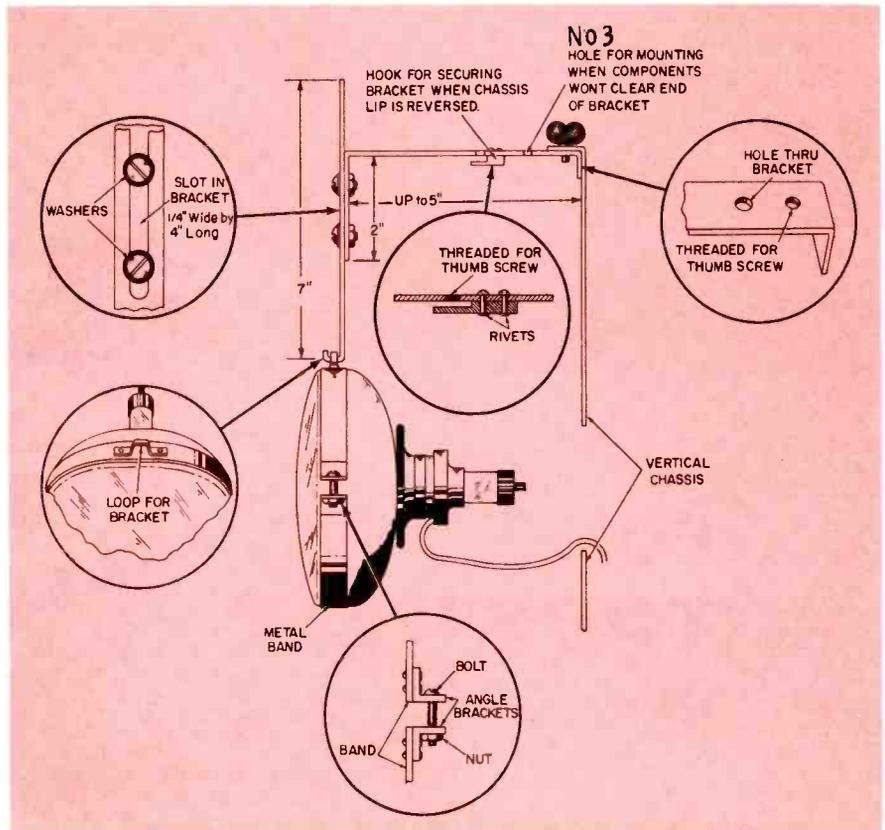


Fig. 4. Details for 110° 8YP4 check-tube bracket show how it may be constructed and used with practically any vertical-type chassis design.

**Using the 8YP4
110° Check Tube**

The recently-introduced Sylvania 8YP4, a 110° check tube, is almost a necessity for servicing receivers with 110° deflection circuits. In many of these sets, the CRT is cabinet-mounted, and either the component or wiring side of printed boards will be inaccessible for service. The original CRT could be removed and extension leads employed, but this creates several problems that aren't easily solved; namely, the danger of breaking the tube and supporting it while servicing the chassis on the bench. On the other hand, the 8YP4 is small and easily mounted or suspended.

The bracket pictured in the drawing of Fig. 4 will provide the necessary support for the 8YP4 and is adjustable so that it can be readily used with practically any chassis design. There is only one small hitch—you will have to make your own. It can be fabricated from two pieces of 1/8" × 1" × 7" malleable iron or ST grade aluminum and assorted screws, rivets, and washers. The distance between the sliding vertical mem-

ber and the chassis can be any length up to 5"; however, the shorter it is (down to about 2 1/2"), the less trouble you will have keeping the vertical chassis upright.

Three different means of attaching the bracket to the chassis are considered in the drawing: (1) Chassis lip turned forward with sufficient clearance between it and components to clear 1/2" "turn down" on the bracket. (2) Lip on chassis turned toward the rear. (3) Lip turned forward but components won't clear bracket "turn down." In the latter case, simply lay the bracket over the chassis, drill a hole through chassis to match hole no. 3 and secure with bolt and nut. In the other two cases, a thumb screw can be threaded into the bracket hole. In case no. 1, a hole must be drilled into the lip of the chassis if none already exists.

A strip of the metal band material used for antenna mounting (chimney strap, etc.) will serve very well for the band around the 8YP4 bulb. Small right-angle brackets can be used to provide a means of tightening the band. Details are shown in Fig. 4. A

NEW



ILLUSTRATES AND DESCRIBES...

... service tools • tube caddy • drop cloth • shop coat, shirt, pants • engineer's and technician's handbooks • reference guides, charts, manuals • Tube Tips • Transistor Course • price lists • job tag • repair sticker • door-knob hanger • ad mats • radio and TV scripts • direct-mail postal cards • consumer booklet • stationery • book matches • dealer giveaways • decals • window valance • window streamers • satin banner • giant tube carton • clock • clock-sign • flange and metal hanging signs • illuminated indoor and outdoor signs.

DEALER

BUSINESS

SALES PROMOTION MATERIAL

BUILDERS

TECHNICAL LITERATURE

CATALOG

SERVICE TOOLS

CBS-HYTRON SALES CORPORATION
A Subsidiary of Columbia Broadcasting System, Inc.



4th Edition

This book can build business for you.

That's a promise! Get a free copy of this new Fourth Edition of the Business Builders Catalog and see for yourself. Check the more than 90 items ranging from new Printed-Circuit Soldering Aids to new Illuminated Outdoor Signs. You'll find that each is designed with you, the independent service-dealer, in mind. Put them to work. Prove to yourself that they can build more service and tube business, more profits for you. Ask your CBS Tube distributor (or us) for your copy of Business Builders Catalog, PA-37 . . . today!

ELECTRON TUBES




CBS-HYTRON
Danvers, Massachusetts

A Division of
Columbia Broadcasting System, Inc.

For the best in entertainment tune to CBS

May, 1958 • PF REPORTER 35

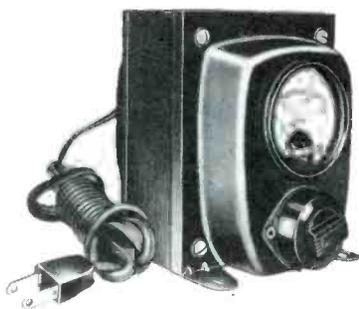**WHEN
PERFORMANCE
IS
AFFECTED BY
LOW VOLTAGE
CONDITIONS**



**SELL THIS
ACME ELECTRIC
VOLTAGE
ADJUSTOR**

TV sets are designed to operate best when voltage holds closely to 115-117 volts. Overloaded supply lines (the power industries greatest problem) may result in a voltage drop of 10 to 15% at certain times of day. Usually the TV set will function in a fashion under such low voltage conditions but with a great strain on its components. For example; narrowing of picture, output stage tube life shortened, frequent burn-out of filaments, fuzzy focus have been traced to lack of proper voltage.

These conditions can be corrected with an Acme Electric T-8394M Voltage Adjustor. Simply plug-in to convenient outlet. Plug-in television set cord into female receptacle built into adjustor. Voltmeter indicates output voltage. If voltage is incorrect turn regulating control until proper voltage is reached for best performance. Voltage range 95 to 125 volts. Tell your supply dealer you want the Acme Electric T-8394M. No other so compact, practical, inexpensive.

ACME ELECTRIC CORPORATION
94 WATER STREET CUBA, NEW YORK

Acme Electric
TRANSFORMERS

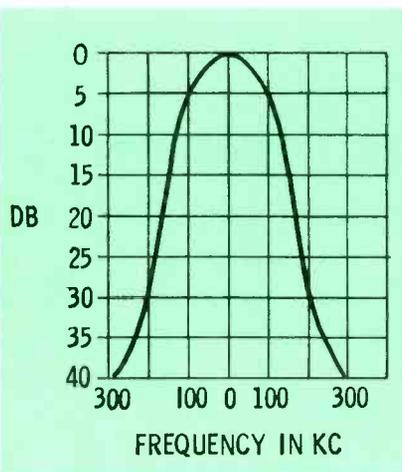


Fig. 5. Drawing of ideal response curve desired at the input of the FM detector.


double layer of friction tape, masking tape or a thin piece of rubber should be used between the glass bulb and metal strap to prevent slipping of the band and to provide a protective cushion for the bulb.

Using Sweep Generator to Service FM Sound Strips


A good technician's ability to repair electronic devices rapidly is limited by his knowledge of the applications of his test equipment. The sweep generator is the accepted unit for video IF alignment and troubleshooting, but most technicians have not seen fit to employ it in FM work. The bandpass requirements of a good FM tuner, while not as complex as those for video, are nonetheless critical.

In a typical hi-fi FM tuner, the desired bandwidth at the detector input is shown in Fig. 5. Note that the response is down only 5 db at points 100 kc either side of center frequency and is 40 db down at 300-kc deviation points. Correct alignment would therefore be extremely difficult to obtain with an AM signal generator and VTVM. To prove this point, the response curve obtained with an AM generator and VTVM is compared with a swept curve in Fig. 6. Discriminator curves obtained in the same manner are shown in Fig. 7.

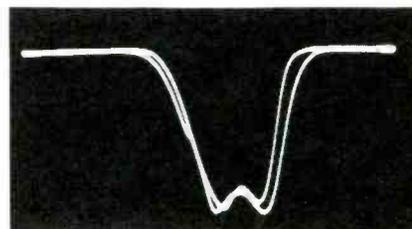Should the alignment instructions specify the AM generator-VTVM method and you wish to further improve operation of the receiver, the swept alignment method used here can be utilized. First of all, the signal must be




(A) Swept.

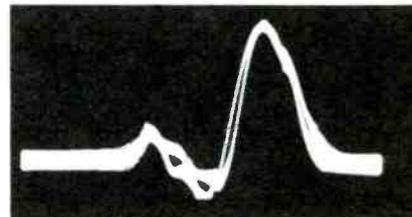


(B) Non-swept.

Fig. 6. Response curves obtained with swept, non-swept alignment techniques.

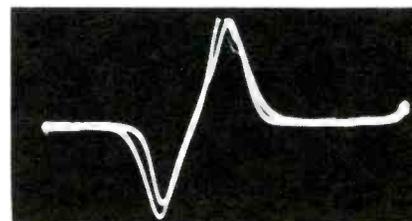

(A)

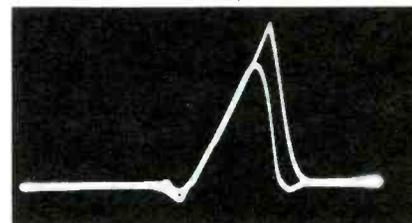

(B)

Fig. 7. Discriminator patterns obtained with swept and non-swept techniques.

injected at the proper point. A separate mixer is employed in this case, and as shown in Fig. 8, a 3.3 megohm resistor acts as the DC load for the mixer grid. The simplest way of introducing a signal into this circuit is to clip the


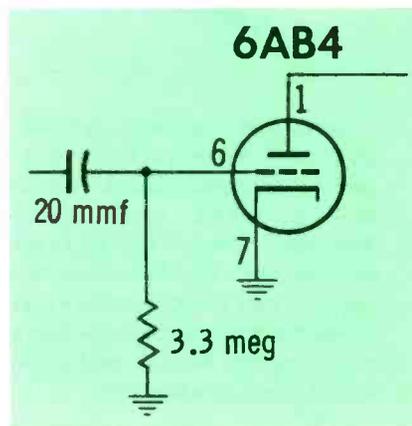


Fig. 8. Grid circuit of separate FM mixer stage used in some receiver designs.

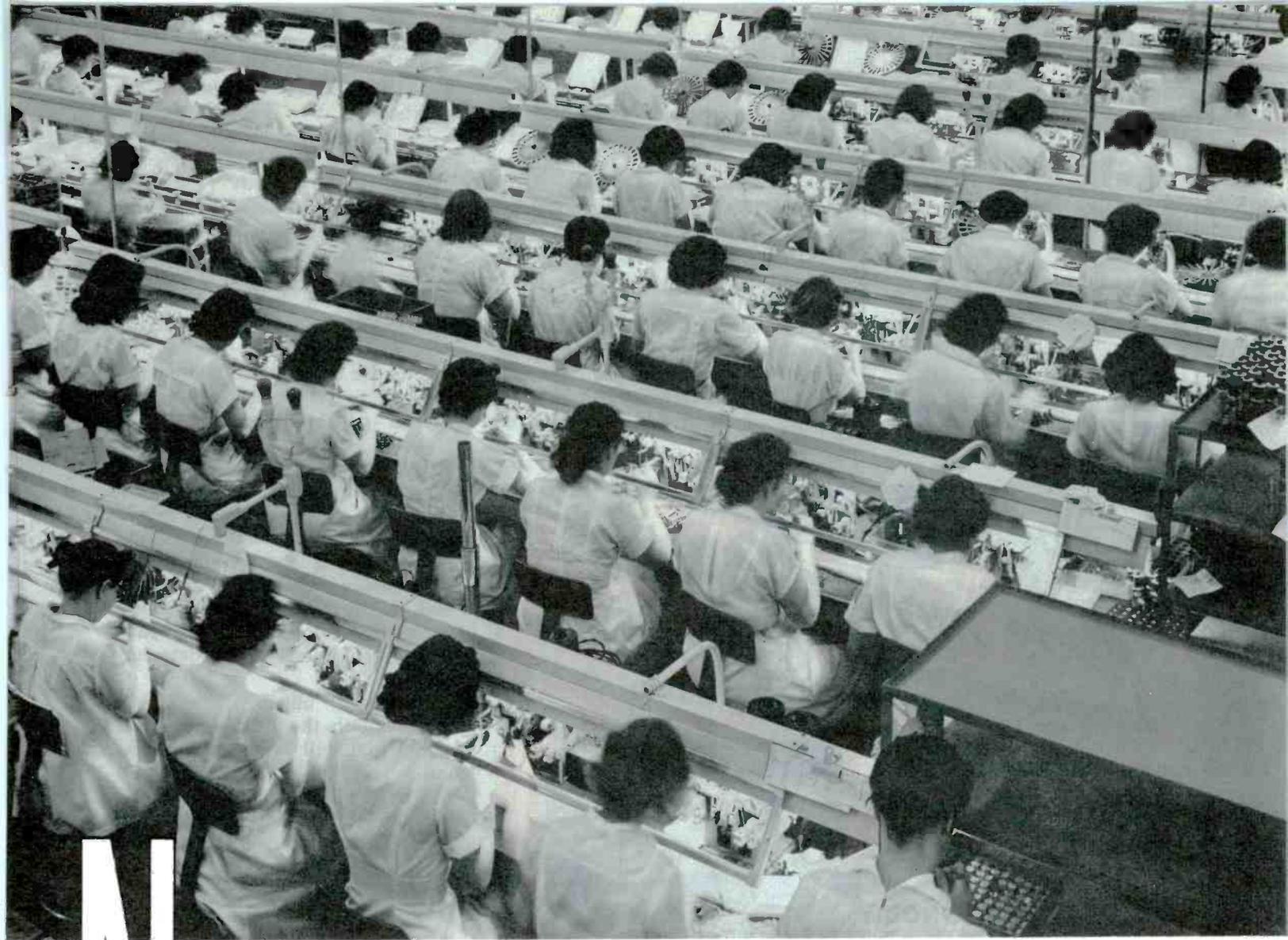

SUPERIOR-QUALITY G-E SERVICE-DESIGNED TUBES INCLUDE:

1B3-CT	6AL5	6BK7-B	6BZ7	6SN7-GTB
1X2-A/B	6AV5-GA	6BQ6-GA/6CU6	6CB6/A	12SN7-GTA
5U4-GB	6AX4-GT	6BQ7-A	6CD6-GA	25BQ6-GA/25CU6
5Y3-CT	6BC6-GA	6BX7-GT	6J6	25CD6-GB

NOW!

General Electric Service-Designed Tubes made even better...through "Snow White" cleanliness!

Lint-free Dacron and Nylon garments . . . filtered, conditioned air . . . floors cleaned many times a day . . . these and other steps toward "Snow White" cleanliness now make G-E Service-Designed Tubes still more dependable! Dust and lint—notorious for causing tube shorts—are banned in General Electric's immaculate receiving-tube factories.

General Electric Service-Designed Tubes increase your profit opportunity, build goodwill with customers. Performance is improved over prototypes; tube life is longer . . . yet Service-Designed Tubes cost the same as other receiving types. Phone your G-E Tube Distributor! *Distributor Sales, Electronic Components Division, General Electric Co., Owensboro, Ky.*

Progress Is Our Most Important Product

GENERAL  ELECTRIC

11-11-121

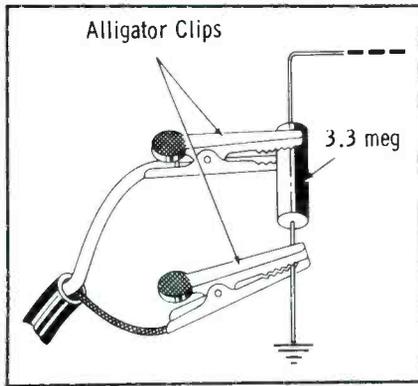


Fig. 9. Signal injection involves clipping hot lead to the top of resistor body.

hot lead of the signal generator to the upper end of the resistor body (Fig. 9), connecting the ground lead of the generator to the ground lead of the same resistor. The scope is then connected across the grid-leak network (Fig. 10) of the last limiter stage if one is employed. If no limiter stage is used, the scope should be connected across the 100K-ohm resistor between the center tap of the detector transformer and ground. The IF transformers can now be adjusted to produce the desired

200-kc response between 5-db points.

For adjustment of the detector transformer, the scope is connected to the output (Fig. 10) and the transformer slugs are adjusted for proper "S" pattern reproduction (see Fig. 11). If a ratio detector is employed instead of a discriminator, it will be necessary to disconnect the electrolytic capacitor used across the output during the IF bandpass alignment, reconnecting it when adjusting for the "S" pattern. Signal for the IF response curve is obtained across the 47K-ohm detector load when this circuit is used (see Fig. 12). When the sweep method is used, it isn't necessary to use the two 100K-ohm resistors specified for zero balance with a VTVM. As it was in the case of the discriminator, the ratio detector "S" pattern is obtained at the detector output.

Normally, alignment is performed with the least amount of signal that will produce a usable indication. When the alignment has been completed in this manner, the scope should be connected across the limiter grid-leak circuits and the generator gain advanced while the response curve is observed. The point where the curve no longer increases in amplitude is where full limiting occurs. While the shape of the curve will change during this procedure, it shouldn't become appreciably distorted. If it does, the signal input should be reduced until response is midway between the highest and lowest tolerable levels and the IF and detector circuits readjusted for the proper curves. A point should be reached where

ADDS INCOME 2 WAYS

1. Tests and Repairs Picture Tubes
(110° Tubes and Color Tubes too, with new C40 Adapter)

2. Makes New Tube Sales Easier

CATHODE REJUVENATOR TESTER

CRT 400 PROVES REAL MONEY-MAKER
Thousands of servicemen today make money and keep customer good-will by checking and correcting b&w picture tube troubles with the famous B&K CRT 400, right in the home without removing tube from set. Restores emission and brightness. Repairs inter-element shorts and open circuits. Checks leakage. Indicates picture quality customer can expect. Life Test checks gas content and predicts remaining useful life of picture tube. Makes new picture tube replacement sales easier!
Model 400 (without adapter) Net, \$59⁹⁵

NEW MODEL C40 ADAPTER DOUBLES VALUE OF B&K CRT
Designed for use with all B&K Models 400 and 350 CRT's. Makes it easy to test and rejuvenate TV color picture tubes and 110° picture tubes. Isolates and detects difficult color troubles. Tests and rejuvenates each gun of the color picture tube separately the same way as a black & white tube.
Model C40 Adapter Net, \$9⁹⁵

See your B&K distributor, or write for Bulletin AP12-R

Makers of CRT, DYNA-QUIK, DYNA-SCAN and CALIBRATOR
B & K MANUFACTURING CO.
3726 N. Southport Ave. • Chicago 13, Illinois

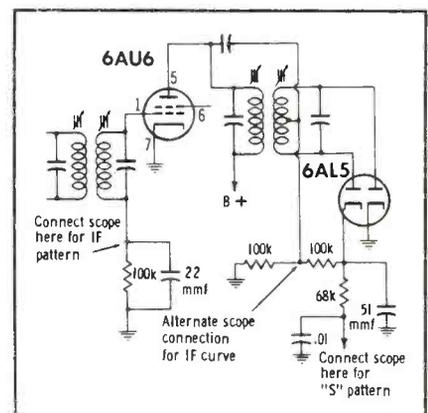


Fig. 10. Schematic showing scope connection points for IF and detector alignment.

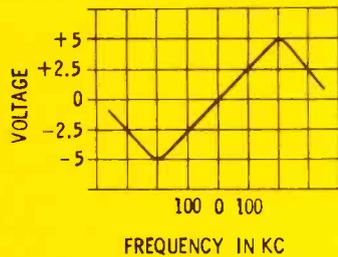


Fig. 11. Drawing of ideal "S" pattern desired at the output of the detector.

both high- and low-level responses are acceptable.

Some signal generators do not have 10.7-mc internal markers, but do have markers in the 88- to 108-mc range. In this event, a sweep signal with a center frequency of about 98 mc and a width of 600 kc to 1 mc should be applied to the antenna terminals; 120-ohm carbon resistors are connected in series with the generator leads for impedance matching. With the marker generator and station selector both tuned to 98 mc and the scope connected as previously outlined, the sweep frequency is varied slightly until the proper pattern is present on the scope. The IF and detector circuits can then be aligned for proper response.

One thing further—if the FM unit in question doesn't have an audio output stage (i.e., it is just a tuner), the discriminator curve can be viewed at the audio output jack. This provides more gain and permits the use of less input signal. If you should happen to be using RF instead of IF sweep, the added gain will be most welcome. With the output stage included in the unit, however, the extra audio stage cannot be used to this advantage because it includes the volume control, and its setting will affect response. ▲


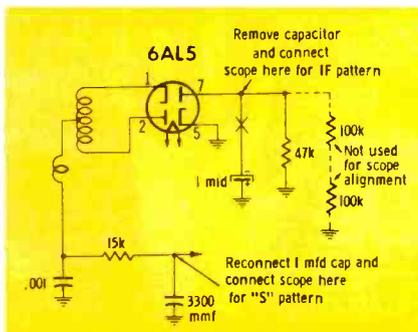


Fig. 12. Schematic of ratio detector stage showing scope connection points.

it takes two to **stereo**

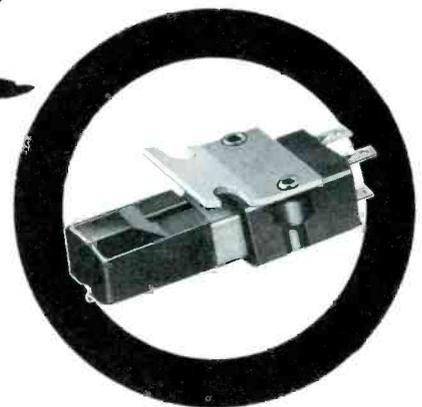

NEW WEBSTER

STEREO-CERAMIC CARTRIDGE AND YOU

Everyday, everywhere, more and more people are talking stereo discs. Now the cartridge to play 'em is here—the new Webster Stereo-Ceramic. Now is the time to tell 'em . . . sell 'em . . . install 'em!

Webster design makes it a cinch because the new Stereo-Ceramic is *completely compatible* with present monaural records. It's lighter tracking, too, and that means longer record life. More, the Stereo-Ceramic has an exclusive plug-in design—either cartridge or stylus can be replaced without tools. Staggered terminals mean easier spot soldering.

Be ready for the big switch to stereo—ask your jobber for the money-making facts.

REPLACE WITH WEBSTER . . . IT PAYS!

STEREO-CERAMIC

SC-1D Complete with cartridge, bracket, diamond stylus \$24.50*




MC-1 78 rpm insert with sapphire stylus, \$7.50*



ELECTRONICS DIVISION
WEBSTER ELECTRIC
RACINE · WIS

*List prices—standard discounts apply.

Franklin adv. V-125

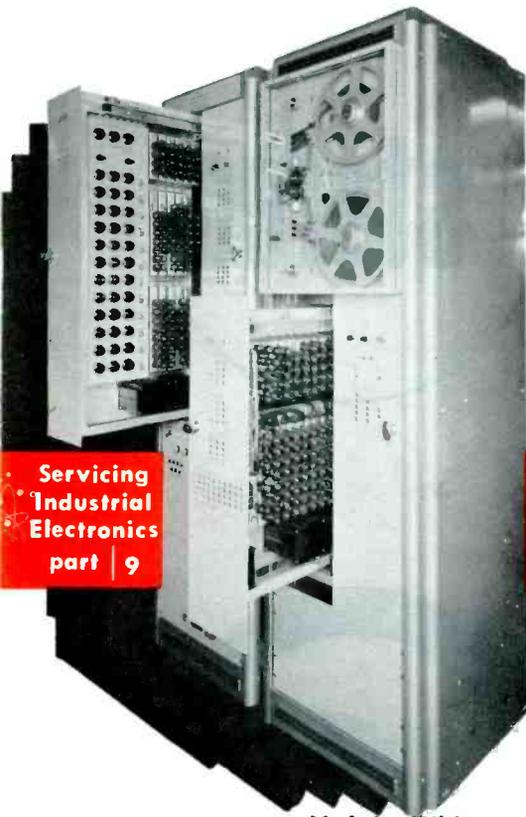

by Melvin Whitmer

machines that

COUNT

Do you realize that you can count up to 31 on the fingers of one hand! The common method of counting is based on the system of tens, where each finger represents one; however, a greater number can be counted if the fingers are assigned numbers as shown in Fig. 1. Thus, number 3 is formed by holding up the little and ring fingers, and number 7 requires these plus the middle finger. Table 1 is complete for numbers 0 through 32, where the

number 1 is used in place of an upright finger and a zero indicates a down finger. Note that each finger in Fig. 1 is valued at *twice* the number of the finger to the right, which is why this system is called binary notation.

Consider what you know about electronics. Is a two-condition circuit easier to think of than a ten-condition circuit? Switches are closed or open; tubes may conduct or be cut off; relays are energized or de-energized. All these are two-condition devices. Are there any ten-condition devices? No—at least not in common usage. Thus, with electronics, the binary notation system is more easily duplicated than is the decimal system. In fact, from the smallest to the largest digital com-

puter, the basic operating circuit is a two-condition device.

A service call was made recently for a packaging plant because an electronic counter always skipped the first digit, although the rest of the counter operated normally. The trouble was evidently in the first stage, a schematic of which is shown in Fig. 2. Note the similarity between it and an R-C coupled multivibrator, the only difference being that R3 and R4 are used in place of coupling capacitors. While the capacitors in a standard multivibrator would couple AC voltage changes between the two sections, resistors R3 and R4 are used for DC voltage coupling. Thus, instead of depending on capacitor charge and discharge for flip-flop action, the grids of Fig. 2 receive a DC voltage which remains constant until plate voltage changes. This circuit is called a two stable-state trigger or an Eccles-Jordan circuit. The DC voltage applied to the grid of V1 (assuming it is conducting) must cause its associated plate voltage to drop below the cutoff level of V2. This will account for the stable condition of V1 conducting, since nothing will cause V2 to conduct until one of the grids is pulsed with a signal of the proper polarity. Then V2 will conduct and V1 will be cut off.

Since the trouble was isolated to the first stage, it had to be something that would prevent the change in stable states but still allow pulses to pass on to the next stage. Voltage measurements at the two grids proved that the grid of V1 was more positive, but when pulses were applied, the circuit always returned to the state

Table 1—Binary Count for Digital Numbers From 1 to 32.

	ASSIGNED NO.						ASSIGNED NO.				
	16	8	4	2	1		16	8	4	2	1
1	0	0	0	0	1	17	1	0	0	0	1
2	0	0	0	1	0	18	1	0	0	1	0
3	0	0	0	1	1	19	1	0	0	1	1
4	0	0	1	0	0	20	1	0	1	0	0
5	0	0	1	0	1	21	1	0	1	0	1
6	0	0	1	1	0	22	1	0	1	1	0
7	0	0	1	1	1	23	1	0	1	1	1
8	0	1	0	0	0	24	1	1	0	0	0
9	0	1	0	0	1	25	1	1	0	0	1
10	0	1	0	1	0	26	1	1	0	1	0
11	0	1	0	1	1	27	1	1	0	1	1
12	0	1	1	0	0	28	1	1	1	0	0
13	0	1	1	0	1	29	1	1	1	0	1
14	0	1	1	1	0	30	1	1	1	1	0
15	0	1	1	1	1	31	1	1	1	1	1
16	1	0	0	0	0	32	0	0	0	0	0



Fig. 1. Numbering system used for binary counting requires fewer indicators.

of V1 conducting. Careful resistance measurements disclosed that R3 had almost twice the value of R4. The negative pulse would arrive at the grid of V1, cutting it off, and the plate of V1 would generate a positive pulse which was coupled to the grid of V2; however, the resultant negative pulse at the plate of V2 was not sufficient to hold V1 in cutoff because too much of the B+ voltage was being developed across R5 (since R4 was too low in value). Conduction of V2 would generate a negative pulse for the next stage, which accounted for the balance of the circuits working. Replacing resistor R4 with a 1% tolerance part restored the counter to normal operation and started the packaging line again.

Stages are cascaded to increase the number of applied pulses required to produce an output. For each one of the fingers in Fig. 1, a separate Eccles-Jordan circuit must be used. A block diagram of a 5-stage counter is shown in Fig. 3. Each stage requires two negative input pulses (one to each grid) to generate one negative output pulse. Thus, in order to generate a negative pulse at the output of the second stage, four pulses must be applied at the input of the first stage.

A rush call came in from a manufacturer of pulse generators. The trouble was in a production line frequency counter used to test the generators. The frequency would register up to 15 but no higher. From this bit of news, the trouble had to be in the fourth stage or in the input coupling to the fourth stage (see Fig. 4.) A 50V negative pulse is applied

at the input and coupled through the diode with the more positive plate (the one connected to the nonconducting triode plate V1. The negative pulse is generated across the nonconducting triode plate load resistor and coupled to the conducting triode grid, driving it into cutoff. C2 and C3 are included in most Eccles-Jordan circuits to couple the leading edge of an applied pulse to the grid because they aid in providing fast response to an incoming pulse, but the controlling action is still through the DC or resistive coupling. Tracking down the trouble in this particular case, it was found that no B+ was present at the diode cathodes because R8 was open.

Neon lamps are placed across one of the plate loads to indicate when the stage is in the "one" or zero state (when the triode containing the lamp is conducting). Before a count is begun, the stages must be tripped into the zero state. A common method of doing this is to open the ground return in the grid circuit of the triode without the lamp. Fig. 5 shows the connections for the lamp, the current limiting resistor, and the reset switch. When the reset switch is momentarily opened, the grid of V2 will be placed at B+ potential, causing V2 to go into conduction and V1 into cutoff. The lamp cannot light and the stage will be in its zero state.

On one occasion, the complaint was that a lamp could not be turned off although counting seemed normal. The tube in that circuit was checked and found to have grid-to-cathode leakage in the first section. When reset was

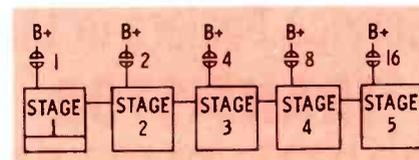


Fig. 3. Five Eccles-Jordan stages used in cascade can count up to 32.

attempted, V2 would conduct, but the leakage caused V1 to come back into conduction when the reset switch was closed. Counting was normal at high speeds, but a slow input rate caught V1 going from cutoff to conduction without the application of a pulse. The leakage added enough voltage to the grid to overcome cutoff.

Input pulses to an Eccles-Jordan circuit must contain a definite set of characteristics. The amplitude must always be the same, the width or duration of a pulse must be the same within a very small tolerance, and finally, rise time (t.) from 10% to 90% of pulse height must be very short. With all these restrictions, the shape of the applied pulse cannot be left to chance.

A pulse-forming circuit as shown in Fig. 6 is usually used ahead of a scaler or computing circuit. Even with a wide variety of negative input pulse shapes, the shape of the output pulses will be uniform. C1 and R1 form a timing circuit having a time constant which is greater than the duration of the input pulses. When a pulse is applied to the grid of V1, this tube is driven into cutoff. The voltage across R4 drops with the pulse until V2 comes out of cutoff. The voltage change at the plate of V2 is many times that of the input pulse, and the discharge

• Please turn to page 69

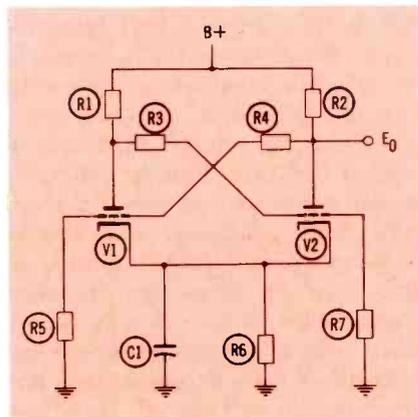


Fig. 2. Eccles-Jordan stable-state multivibrator used in binary counters.

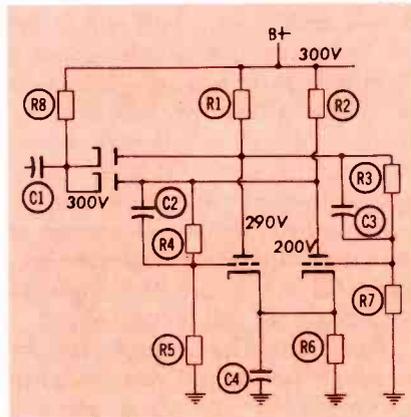


Fig. 4. Diode coupler circuit feeds input pulse to the conducting tube grid.

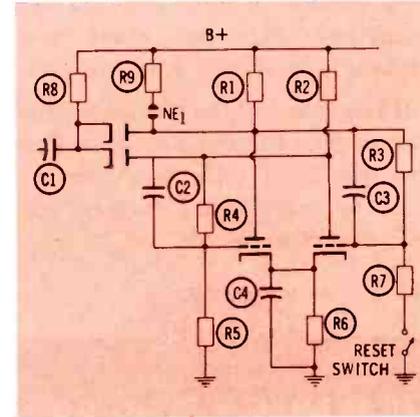


Fig. 5. R9, NE1 and a reset switch are commonly used in most binary computers.

Service Dealers in the TRANSISTOR PROFIT PICTURE



STOCK and SELL



TRANSISTORS

Most transistor receiver servicing problems can be solved with Raytheon Transistors — that's why Service Dealers who stock and sell Raytheon Transistors get a big share of this lucrative business.

Then, too, hobbyists, engineers, experimenters and beginners all prefer Raytheon Transistors. They like them because of their uniform electrical characteristics, their ready availability and their low, low price.

If you're not in the transistor profit picture yet, call your Raytheon Tube Supplier. He'll show you how easy it is to make more money with Raytheon Transistors.



Excellence in Electronics
RAYTHEON MFG. CO.
Receiving Tube and Semiconductor Operations
Newton 58, Massachusetts

TV SERVICE ...A LIVING ?

by W. C. Pecht

TV has been with us about ten years now, and what you fellows don't know about theory is pretty well compensated for by experience—and vice-versa. The newcomers have many sources of information, and if they tie up with an old-timer, they should be able to earn a living.

Which is the subject for today. Do you make a good living out of TV? If not, why not? Your ability to fix 'em needs no investigation; you have been and still are the most important cog in the whole TV machine. That sounds like big talk, but if we consider that the average TV breaks down at least four times a year and people still buy them . . . you guys must not only be fine servicemen, but also the world's greatest salesmen. Anything else requiring so much attention couldn't be given away even with two pairs of mukluks as a premium.

In spite of this, many of us may not be doing as well as we have a right to expect. Perhaps we've been too conscientious, too eager, too ready to accept fact, and too quick to reject fantasy. What's wrong with fantasy? A child's world you say—but aren't all men just bigger kids? In John Q. Public's mind the whole idea of television is about as fantastic as any fairy tale.

Gentlemen, we have overlooked the pearl in the oyster. When a customer gasps at the sight of a TV chassis and says, "How did you ever learn what all those things do?", you puff up a little and say with much modesty, "Nothing to it, ma'am—just a bit of study, a bit of curiosity and an old voltmeter willed to me by my drinkin' uncle." Man . . . you missed the boat. By stretching the truth a little and capitalizing on human nature, you could strike a powerful blow for the financial well-being of all servicemen.

You could have said, for instance, "Well, to tell you the truth, ma'am, there are some parts in there that nobody has yet been able to figure out. This set was

designed by a Yogi and before he could explain the thing to the engineers, he disappeared."

When faced with a technical problem of such magnitude as this, the customer can't help feeling that if you can fix this one, you can fix anything; and with compassion in her heart for your coming ordeal, she says, "Take as long as you like, do whatever has to be done and we'll have the cash waiting for you when you bring it back." If they think that a job is difficult, why spoil their fun?

Most people regard the scientist as a genius, an educated super-human, necessary, expensive, screwball. Get that, EXPENSIVE SCREWBALL! Of course, this is ridiculous; it doesn't even approach fact. You and I know that a scientist has to be level-headed and extraordinarily intelligent but, what's our opinion against millions of others?

So, let's go along with it. The next time a customer says, "No offense, Irving, but doesn't learning all that stuff make you a little punchy?" try to let your jaw hang a little slack and mumble, "If the aspect ratio equals pi times the reluctance of the first detector, then it proves that Barnum was right." Look him right in the eye and say, "Confound it, go back and tell them we take off when I'm ready and not one light year before!"

When this guy leaves your shop, he'll tell the first person he meets, "That guy really knows his stuff, but is he a nut—a first class filbert." As soon as you have established your position in the public eye as a "scientist," you can enjoy the financial reward that accompanies the title. People generally assume that genius is but a short putt from madness, and are as eager to patronize the genius as they are to shun the madman. People like to give money to science; don't disappoint them—get with it! A little showmanship and imagination will pay off. Hmmm—I wonder how I'd look in black tights with a space helmet? ▲



\$169.95 Net


INDUCED WAVEFORM ANALYZER

MODEL 850

Top-O'-Chassis Troubleshooting . . . greatest servicing advance in years!

Perfect for Portable TV

Localizes defective stage in entire TV receiver in less than 5 minutes—without a direct circuit connection. Adapts any 'scope for spotting defects quickly by the modern, easy-to-use Induced Waveform Method. Unique, Phantom Detector Probe makes any tube a convenient test point. Just slip probe successively over each tube, then view and trace waveforms on scope from antenna thru RF, IF, audio, video & sync. Speeds servicing of TV, radios, amplifiers, instruments, industrial and laboratory equipment tool. Compatible for color. Phone jack for audio monitoring.

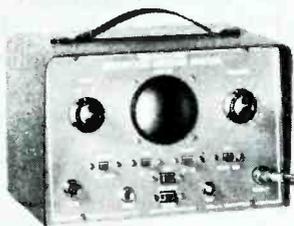

\$89.95 Net

INTERMITTENT CONDITION ANALYZER

MODEL 828

Pinpoints Intermittents without waiting...cooking...or freezing.

Exclusive new principle makes any TV or radio super-sensitive to intermittents and noisy components . . . without waiting for breakdowns. Saves time and bench space. Cuts callbacks by detecting borderline components before they fail. Special Wintronix Probe and capacity pickup attachments let you hear intermittents thru built-in speaker.



\$79.95 Net

AGC CIRCUIT ANALYZER


MODEL 825

AGC Troubles Won't Fool You Any More!

Saves hours by detecting hard-to-find AGC faults that may look like sync trouble, etc. Furnishes standard, adjustable r-f signal to antenna; monitors AGC action; checks AGC buss for opens and shorts; measures action of gated pulse systems; supplies AGC bias to restore operation by substitution.

Wintronix ANALYZERS

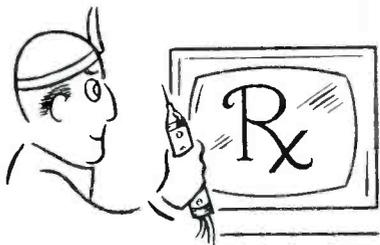Electronic "Wonder Drugs" for Troubleshooting Pains



Here are the instruments you need to diagnose ailments fast and profitably in today's

complicated—often inaccessible—TV, radio & hi-fi sets.

These four Wintronix *Analyzers* swiftly turn wasted trouble-shooting time into profitable parts replacement time on more and more jobs. Obscure radio and TV faults get tracked down fast by Winston's specialized reference signals and measurements. Like X-rays, they quickly give a complete picture of circuit operation—at far lower cost, with fewer circuit connections, and with less set-up time than with separate conventional instruments.

Today, issue a prescription to yourself for a healthier servicing business—see and try these new Wintronix *Analyzers* at your local parts distributor or write for detailed literature.

SWEEP CIRCUIT ANALYZER

MODEL 820

Rapid, Dynamic Sweep Testing

\$69.95 Net



Completely troubleshoots entire sweep circuits and restores roster by substituting for defective stage. Tests all flybacks and yokes for continuity and shorts. Self-calibrating. Compatible for color.

Model 915/960 Adapter converts Model 820 to a Sync Circuit Analyzer for signal substitution of vertical and horizontal sync pulses.

\$14.95 Net

WINSTON ELECTRONICS INC.

4312 Main Street, Philadelphia 27, Pa.



REPLACING DEFLECTION YOKES

It's no problem when you have the facts by Les Deane

On the surface, replacement of a deflection yoke should not present much of a problem to the average TV technician. Looking deeper, however, it is found that wiring hookups, damping and neutralizing elements, and mounting considerations have been causing servicemen a certain amount of trouble. The purpose of this article, therefore, is to acquaint the reader with underlying facts which must be considered even for some "run-of-the-mill" yoke replacements—also, to present a logical approach to the servicing angle. To do this, let's first examine a typical deflection yoke both physically and schematically.

Physical Description

Pictured in Fig. 1 is an actual yoke assembly which has been cut in two, leaving one complete hor-

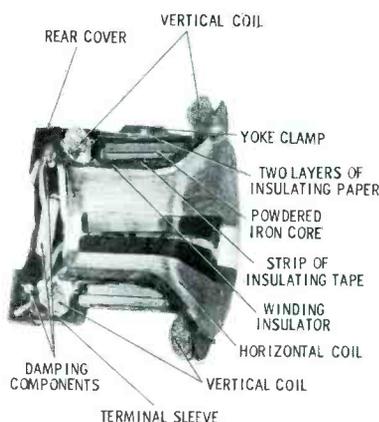


Fig. 1. Cross-sectional view of a typical 90° yoke showing its complex makeup.

izontal winding and half of each vertical winding intact. The horizontal windings are located on the inner surface and usually come in direct contact with the neck of the picture tube. In actual operation, the horizontal coils are placed in a vertical plane, so that the resultant field will deflect the electron beam in a horizontal direction. An insulating material, most often a plastic-like substance having high-voltage insulating and moisture-resistant qualities, is used to separate the vertical and horizontal windings. The vertical windings are located on top of the plastic insulator and at right angles with respect to the horizontal windings. In normal operation, the two vertical coils are positioned in a horizontal plane on each side of the picture tube neck and thus their fields control the beam in a vertical direction.

In this particular example, the core material is divided into four sections laid end to end, completely surrounding the circular form. Over the core pieces are two additional layers of insulation. In this case, a fairly heavy grade of fish paper is employed. The plastic terminal board is wedged beneath the core and insulation materials, and the entire assembly is held together by a single metal clamp. In many designs, especially the older 50° and 70° units, the core clamp may also have a built-in nut arrangement for mounting. Vertical and horizontal damping components, as well as a section of the rear cover, are also identified in the photo of Fig. 1.

Electrical Description

Investigating the yoke from another point of view, the technician may also become a little confused when called on to trace its

wiring schematically. A diagram of a typical yoke assembly is shown in Fig. 2. In service schematics illustrating all of the yoke windings in close proximity (such as Photofact Folders), the horizontal coils are generally drawn vertically and the vertical coils horizontally, as shown. On other schematics, the individual windings may be positioned with their appropriate output circuits.

Replacement instructions, operational theory and production changes will often use terms which may not be completely understood by the service technician. Such references as *high side* or *top* of a winding, yoke return, fifth yoke lead, or damping and neutralizing elements, are vernacular terms dealing with yoke circuits.

Contacts within the yoke assembly are usually identified by numbers stamped or printed on the terminal board; these in turn will often appear on the schematic diagram. It can be seen in Fig. 2 that one coil of the horizontal system is connected between terminals 2 and 1, while the other is connected between terminals 3 and 7. The



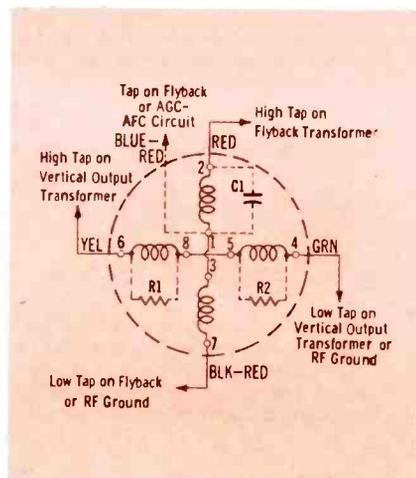



Fig. 2. Wiring diagram of a deflection yoke and most likely circuit connections.

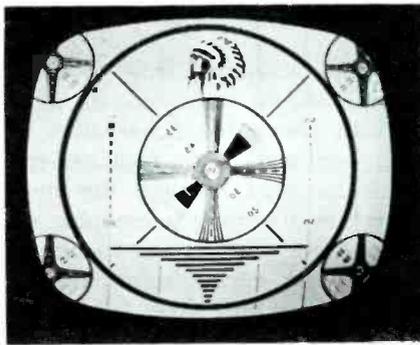

(A) Horizontal connections reversed.

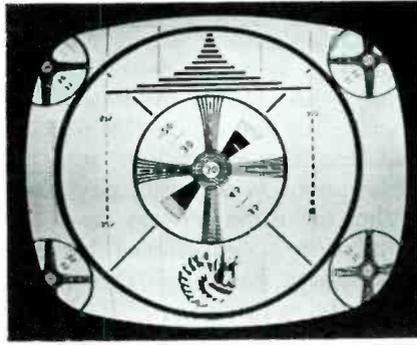

(B) Vertical connections reversed.

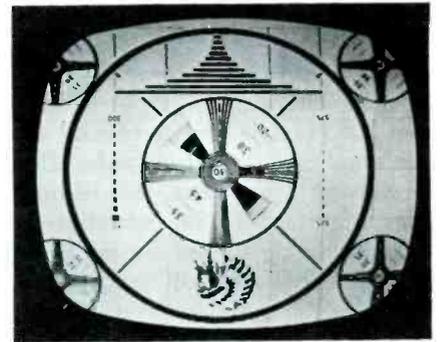

(C) Connections of both reversed.

Fig. 3. Improper picture orientations caused by incorrect yoke connections.

vertical coils are connected from terminals 6 to 8 and 5 to 4. When reference to the *high side* of the horizontal windings is made, it means the uppermost yoke connection on the flyback, where sweep energy is greatest. The high side may also be called the *top* or *hot side*, and in Fig. 2, this is represented by the connection at terminal 2. Although seldom described as such, the high side of the vertical windings is likewise the connection at the top of the vertical output transformer, or terminal 6 in the example.

Colors of the original yoke leads frequently are identified on the schematic. Referring again to Fig. 2, we see that the lead connected to the high side of the horizontal windings is coded red, while that to the high side of the vertical windings is yellow. Such identifications aid the technician when yoke replacement becomes necessary.

The expression *yoke return* or *low side* may refer to either the horizontal or vertical deflection circuits, indicating the lead returning to RF ground or nearest to it. This may be to one of the lower taps on the flyback, the boost line, the B+ supply, or chassis ground. A capacitor is often connected in series with the horizontal yoke return lead. This component is employed to prevent DC current flow in the windings and to meet certain centering requirements.

Many circuit designs will call for a fifth yoke lead, such as that represented by the broken line coded BLUE-RED in Fig. 2, and it may connect to the junction between either the horizontal or vertical windings. When tied in

with the horizontal circuit as shown in the schematic, the lead may return to a tap on the flyback between the high-side connection and RF ground, to an AGC keyer circuit, or to a horizontal AFC network. In some instances, the lead provides the connection to a damping component not physically located within the yoke housing. If the fifth lead is connected to the vertical deflection coils, it will generally return to RF or chassis ground. When replacing a five-lead yoke, make sure that you will be able to duplicate the original wiring or that proper instructions for circuit revision accompany the replacement.

Yoke-damping and neutralizing elements are merely electrical components added to the deflection circuit to reduce oscillation within, and interaction between, windings. As far as horizontal sweep is concerned, the damper tube prevents sustained oscillations; nevertheless, the ringing which results from the sudden reversal of yoke current during flyback time can result in damped oscillations during the trace period.

In Fig. 2, damping components R1, R2, and C1 are shown connected in a typical arrangement across the vertical and horizontal yoke windings. Units R1 and R2 are of equal resistance—normally a standard value between 150 to 2200 ohms. The shunt capacitor across the high side of the horizontal winding will range in value from 10 to 300 mmf and naturally, with the high peak voltages involved, will have a working voltage rating of 2 to 4 kv. Yoke circuits, especially some of the early

designs for 90° deflection, may incorporate a resistor of approximately 1000 ohms in series with the horizontal damping capacitor. Rarely, one may also encounter a network where the shunt capacitor is connected across the bottom horizontal coil (terminals 3 and 7 in Fig. 2) or even between vertical and horizontal windings. More will be said about these later on.

The Replacement

In choosing the proper yoke replacement, consideration must be given to the deflection angles, inductance values, internal coil connections, and even physical size in some cases. Other minor considerations include yoke plugs, additional leads, mounting assemblies, or special rear covers with centering devices.

While in some cases it may be desirable or even necessary, securing an exact duplicate from the set manufacturer usually is not expedient. Fortunately, yoke manufacturers have made standard replacements available for practically any unit; fortunately too, cross-reference data is available in abundance. Service data often recommends exact replacements and/or substitutes which require only slight electrical or physical alterations; however, it's a good idea to consult your distributor's latest catalogs and cross-reference guides before making a final choice, since a unit better suited to your needs may have been introduced after the initial reference data was published.

Wiring

Dealing more directly with the problem of making a replacement yoke work, let's turn our attention to the installation procedure.

Removal of the defective yoke is naturally the first step. This will not give rise to any problems unless, by chance, the yoke insulation has melted and hardened on the neck of the picture tube. Before using a crowbar, the technician might give the situation a little thought, unless he replaces picture tubes free of charge.

One recommended procedure is to heat the yoke until the insulation softens. Perhaps the easiest and safest way of producing the needed heat is through the use of controlled current through the windings; one ampere through the horizontal windings is usually sufficient.

In disconnecting the original yoke leads, it's a good idea to make a simple wiring diagram for later identification of the various lead colors and their circuit connections. If an exact duplicate is used as a replacement, the color-coded leads will probably agree with the originals. Standard or universal replacements, on the other hand, may

have different lead colors and terminal numbers. If so, it will be necessary to trace the circuitry of both the old and the new yoke in order to determine the proper lead connections. When such a replacement is selected, pay particular attention to any and all installation notes offered by the replacement guide and/or service literature.

If the replacement is nearly identical to the old yoke, chances are the installation note will read, "Connect same as original." This indicates that both yokes are wound in the same fashion and that the numbering of their terminals correspond. Installation notes accompanying universal replacements give detailed instructions for wiring the unit into the circuit. In many instances, the instructions will state exactly which leads of the replacement go to what pins of an original yoke plug. When making the substitution, the possibility of certain damping elements being part of the chassis wiring rather than the


yoke assembly should be kept in mind.

If the technician fails to heed special wiring notations or neglects to check the schematics of both original and replacement units, he may damage the new yoke, its damping elements, or even other chassis components. On occasion, certain minor installation errors will show up in the displayed picture, but will not result in any damage. (See the symptoms pictured in Fig. 3.)

Yokes employed in many modern, vertical-chassis receivers have lead openings and mounting devices located close together. Generally, a universal-type yoke has leads emerging from one side and mounting device from the other; thus the technician may find it necessary to loosen the core clamp and rotate it 180°.

Another case when this procedure might be called for is where the terminal numbers on the replacement are reversed from those of the original. In order for the installation note to read simply,

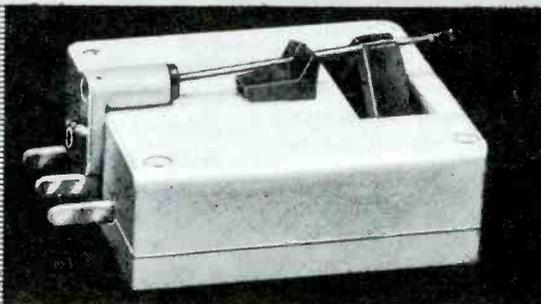DUOTONE proudly presents the **ACOS® * Hi-g®** **STEREOPHONIC** **PHONOGRAPH CARTRIDGE**



Manufacturers of the World's
Finest Phonograph Needles.



Company, Locust Street, Keyport, N. J.

SEE AND HEAR THE ACOS® Hi-g® CARTRIDGE DEMONSTRATED
AT THE ELECTRONIC PARTS DISTRIBUTORS SHOW, IN CHICAGO
ON MAY 19-21 IN ROOM 609A AND 611A.

From Duotone, first with the finest in High Fidelity, comes the GPS80-1 stereophonic phonograph cartridge.

ACOS research, engineering, and production have made these cartridges the finest pick-ups for the 45-45 stereophonic discs, and at a price that all can afford.

Featuring *extremely high vertical and lateral compliance—complete compatibility for monaural or stereophonic play back.

Place your orders now for future delivery—be prepared for the big shift to stereo.

DUOTONE IS A REGISTERED TRADEMARK.

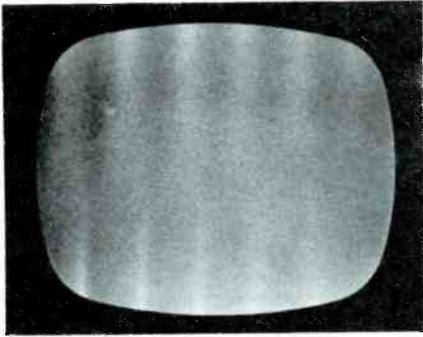


Fig. 4. Yoke ringing—the tell-tale evidence of incorrect damping.

“Connect same as original,” further instructions indicate the sweep should be reversed by merely rotating the yoke assembly 180°, leaving the clamp in the same mounting position. In this type of installation, the horizontal damping capacitor must be relocated and the yoke leads will naturally end up in a different position.

During a yoke replacement, one may encounter a number of different trouble symptoms on the screen caused by improper damping of the deflection system. The symptoms may range from only a slight ripple at the beginning of each horizontal scanning line to very noticeable light and dark vertical bars near the left side of the screen. This type of distortion often results from an unbalanced condition between the two horizontal coils or excessive coupling between vertical and horizontal windings.

Yoke ringing produces a fluctuation in the horizontal magnetic field, causing beam deflection to speed up and slow down accordingly. This results in nonlinear deflection and shows up on the screen as light and dark vertical bars as pictured in Fig. 4. If the ringing is not too severe, but suffi-

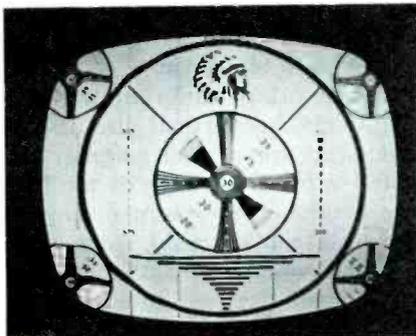


Fig. 5. Ripple at beginning of trace is due to interaction between deflection circuits.

CONTROL REPLACEMENT RECOMMENDATIONS FOR 18,000 TV MODELS!

a must
if you
service
TV!

\$
Only 1⁰⁰

Howard W. Sams

REPLACEMENT GUIDE FOR TV CONTROLS



A SAMS FIRST! Lists the recommended replacement TV controls of these manufacturers:

CENTRALAB
CLAROSTAT
IRC
MALLORY

nothing
else
like
it!

IT'S EASY TO FIND THE
PROPER REPLACEMENT BY
EXCLUSIVE NEW "INDUSTRY
PART NUMBER" SYSTEM



QUICK-ACTION REFERENCE:

You'll find the original control part number (or drawing number) in the special Index Section, listed either alphabetically or numerically under the TV set manufacturer's name. Opposite this listing is the exclusive *Industry Part Number* . . . such as X-400.

Simply look up the *Industry Part Number* (in this case, X-400), and you'll find the recommended replacement controls of four manufacturers (Centralab, Clarostat, IRC and Mallory) listed in the columns beside it . . . takes only seconds—it's that simple!

- The most complete replacement guide for TV Controls ever published—replacements for 18,000 TV models—covers virtually every TV set produced from 1947 to 1958!
- Every replacement control is *currently available* and recommended by the manufacturer to meet "Industry Part Number" specifications!
- Exclusive "Industry Part Number" system gives you quick, easy selection of all four manufacturers' recommended replacements!
- "Industry Part Number" listing helps you maintain inventory of most-needed controls for your service work—avoids needless duplication!
- Saves you time in selecting proper replacement controls—saves ordering time too. Guide actually pays for itself the first time you use it on a control repair job!

8 1/2 x 11"

IT BELONGS
ON YOUR
BENCH!

\$
Only 1⁰⁰

ORDER THIS BOOK FROM YOUR SAMS DISTRIBUTOR TODAY, OR MAIL COUPON BELOW

HOWARD W. SAMS & CO., INC.

Order from your Sams Distributor today, or mail to Howard W. Sams & Co., Inc., Dept. 3-E8 2201 E. 46th St., Indianapolis 5, Indiana

Send copy(ies) of "Replacement Guide for TV Controls." My (check) (money order) for \$ is enclosed.

Name

Address

City Zone State

(Outside U.S.A. priced slightly higher)

HOWARD W. SAMS & CO., INC.

Indianapolis 5, Indiana



Another Sencore Time-Saver

the **ALL NEW**
SENCORE
Align-O-Pak
TV
BIAS SUPPLY



For **BLACK and WHITE**
and **COLOR**

Just Dial any DC Voltage from 0 to 18 volts positive or negative—For AGC trouble shooting and alignment—Do away with messy bias batteries.

Completely isolated. Recommended by TV manufacturers. Wire wound control for calibration accuracy. For AGC trouble shooting, connect to AGC buss and vary voltage from 0 to 18 volts negative. If picture stabilizes at any voltage, AGC is defective. Complete with test leads.

MODEL BE3
\$785
Dealer Net
Leather Carrying Case... \$2.95

Mfg by **SENCORE**

SERVICE
INSTRUMENTS CORP.
171 OFFICIAL RD. ADDISON, ILL.

POPULAR SENCORE PRODUCTS

- Transistor Tester
- Leakage Checker
- Filament Tester
- Handy "36"
- Vibra-Dapter



Fig. 6. Yoke cover with centering device not standard on most replacement units.

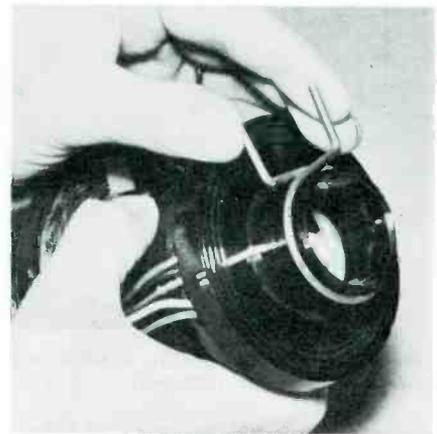


Fig. 7. Cover with clamping device holds deflection yoke in position.

cient coupling exists between vertical and horizontal windings, a ripple effect may appear as shown in Fig. 5. The vertical deflection appearing along each scanning line represents horizontal ringing current in the vertical yoke coils.

Although the limited amount of yoke ripple shown in Fig. 5 would not be too noticeable on stationary images, it becomes very apparent when the TV camera pans to either side. In more extreme cases, the ripples become very objectionable, and even the most congenial customer wouldn't let you get by without correcting it.

As mentioned previously, capacitors and resistors of various values are employed as damping and neutralizing elements in different circuit designs. These values are somewhat critical in some cases, while in others they are of relatively small consequence. This brings to mind another installation note often found in service literature—"May require use of original damping network." Simply stated, this means that if ringing is encountered when using the damping network supplied with the replacement, use of the original network (or equivalent replacements) is recommended.

An interesting feature concerning yoke damping components is the unique arrangement found in late-model Philco receivers. The yoke, a 90° unit, makes use of a fifth lead which connects between the two horizontal yoke windings and returns to a tap on the flyback transformer through a resistor. This lead, as well as all other yoke wires, terminates at a chassis plug. The fifth yoke lead, together with

the one connected to the high side of the horizontal windings, are confined in close proximity by a length of insulating spaghetti for the distance between the yoke terminals and the yoke plug. These two leads, running side by side, provide the required damping capacitance of 110 mmf. When replacing the yoke in this particular set, remember that it may be necessary to use the original plug and leads and also to remove the damping capacitor supplied with the new yoke.

When confronted with a ringing problem after yoke substitution has been made, check to see that the horizontal damping components are connected across the proper terminals. If no discrepancies are found, vary the capacitor value until ringing is minimized. In obstinate cases, ringing can sometimes be reduced further by connecting a capacitor between horizontal and vertical windings. A unit of approximately 270 mmf may be placed from the center of the vertical windings to the bottom or RF ground of the horizontal winding. When changing yoke components, use capacitors having adequate voltage ratings and noninductive resistors, preferably of 5% tolerance.

Substituting different resistor values in the vertical circuit will not affect horizontal ringing, but if the value is too high or too low, the height of the picture may be reduced considerably. Since the original damping network may have been exposed to high temperatures and voltages, it pays to use new components when the yoke is replaced.

COLMAN
Electronic
Products

TV PICTURE TUBE CONVERSION KIT

Complete conversion kits for replacing metal tubes with glass tubes. Kit contains everything except the picture tube. Average conversion less than one hour.



FROM THIS
TO THIS


9

Different Kits for RCA, Emerson, Stewart-Warner, Silvertone, True-tone, Coronado, Hallicrafters, Firestone, CBS-Columbia, Airline, Arlington, Wells-Gardner, Arvin, Crosley, Fedway.


In stock at leading parts jobbers everywhere.

COLMAN TOOL & MACHINE CO.
P. O. Box 7026—Amarillo, Texas

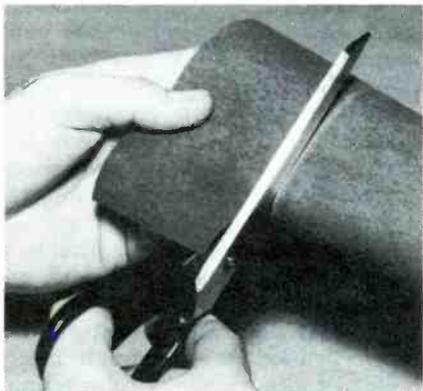Canadian Representative:
Wm. Cohen Ltd., 7000 Park Ave., Montreal, Canada



(A) Cutting fish paper to size.

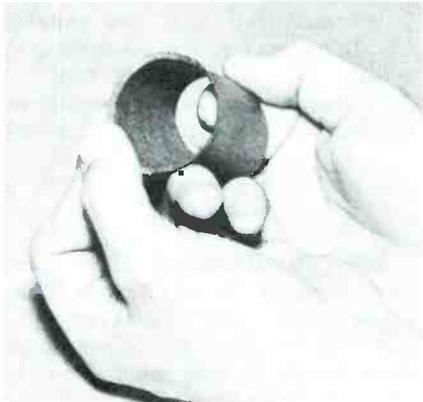

(B) Cut and roll to form flange.



(C) Cement, position, and allow to dry.

Fig. 8. Details for the construction of a width sleeve insulator.

Covers, Clamps, and Sleeves

The most important factor in the choice of a yoke replacement naturally concerns the electrical qualifications. There are, however, certain physical aspects that must also be taken into consideration. In many receivers, for example, the original yoke may include a centering device such as that shown in Fig. 6. The device is actually part of the yoke cover and is made up of two magnetic rings that can be rotated independently to achieve picture centering.

The installation note for a conventional replacement yoke may read, "Use original rear cover and centering device." Since these covers are standard in size, the technician need only remove the old one and place it in position on the new yoke.

Another design feature found only in modern receivers is a self-contained yoke-clamping device. This item may also be a part of the rear-cover assembly as pictured in Fig. 7, constructed so that the yoke clamps to the neck of the picture tube and no mounting bracket from yoke to chassis is needed. Here again, we find that the original rear cover assembly must be used.

Certain General Electric, Hotpoint, and Philco receivers employ special yoke-clamping devices which cannot be used with general yoke replacements; therefore, the technician may find it necessary to fabricate or purchase a new mounting. The yoke must seat against the flared bell of the picture tube and mount securely either to the chassis or picture tube before the replacement job can be considered complete. Otherwise, the customer eventually may find himself viewing a tilted picture with his neck bent to one side—and as a callback, the pain in the neck will be yours.

As a final physical consideration, mention should be made of receivers employing a metal sleeve which slips between the yoke and the neck of the picture tube. Movement of this sleeve along the neck varies the strength of the deflection field and thus affects raster width. When a yoke replacement is made, this width sleeve must be used in its original application. Since it is metal and comes in close contact with the horizontal yoke windings, however, some form of insulation must be used. In a few receivers, the sleeve itself may be insulated, but in most cases the original yoke will have the necessary insulation.

It's almost impossible to remove the insulating material from the original yoke without damaging it; so if it is not already incorporated in the replacement, the technician should follow the procedure outlined in Fig. 8 and form a new width-sleeve insulator. ▲

Operate your...

- tape recorder
- P. A. system
- portable TV set
- hand tools

FROM YOUR CAR, Boat or Plane!

with **ATR**

INVERTERS

FOR CHANGING YOUR STORAGE BATTERY CURRENT TO A.C. HOUSEHOLD ELECTRICITY ANYWHERE... in your own CAR, Boat or Plane!

OPERATES PORTABLE TV SET directly from your car!

OPERATES

- TAPE RECORDERS
- DICTATING MACHINES
- PUBLIC ADDRESS SYSTEMS
- ELECTRIC SHAVERS

directly from your car!

MAKE YOUR CAR, BOAT OR PLANE "A ROLLING OFFICE!"

OPERATES

- RADIOS
- RECORD PLAYERS
- MIXMASTERS, ETC.

directly from your car!

mounted out of sight under dash or in trunk compartment

ATR UNIVERSAL INVERTERS

Especially designed to change 6 or 12 volt D.C. to 110 volt A.C. 60 cycles. for...

- EXECUTIVES
 - SALESMEN
 - OUTDOOR MEN
 - POLICEMEN
 - REPORTERS
 - FIREMEN
 - PUBLIC OFFICIALS
- MODELS 6U-RHG (6 volts) 125 to 150 watts. Shipping weight 27 lbs. List price... \$89.95
DEALER NET PRICE... \$59.97
- 12U-RHG (12 volts) 150 to 175 watts. Shipping weight 27 lbs. List price... \$89.95
DEALER NET PRICE... \$59.97
- Write for literature on other Sizes and Models of ATR INVERTERS, priced as low as \$9.95 list.

SEE YOUR JOBBER OR WRITE FACTORY

✓ NEW MODELS ✓ NEW DESIGNS ✓ NEW LITERATURE

• "A" Battery Eliminators • DC-AC Inverters • Auto Radio Vibrators

ATR AMERICAN TELEVISION & RADIO CO.
 Quality Products Since 1931
 SAINT PAUL 1, MINNESOTA, U. S. A.



Relocate. Shops that specialize strictly in TV servicing are forced to keep rent costs low in order to hold overhead expenses to a minimum. In the past, this fact has relegated many service businesses to hole-in-the-wall locations on side streets.

However, the time is now ripe for such shops to seek better locations with more elbow room. In many cities, the stores which depend on heavy customer traffic have moved in droves to new shopping centers and other outlying locations with good parking facilities; consequently, many large store buildings in older areas near the middle of town have been left vacant. These "empty shells" are an excellent value for the rental dollar. In many cases, rents have dropped considerably because of a lack of demand for locations of this type, even though many of the buildings are in choice business districts.

Parking is usually a prime problem, but you have no worries about customer parking facilities when you are taking your services to the customer in his home! All you need is enough space to park a few service trucks. Some of this space is usually available behind the store; in addition, many cities will designate the curbside area in front of the store as a "loading zone" for a small fee, further easing your own parking problem.

Realtors emphasize that locations on heavily traveled streets are the best bargain for two good reasons:

1. People who read your advertisements will recognize the name of an important street and will know where you are located. This factor encourages people on your side of town to call you when they need service.

2. On a busy street, your shop will be noticed by larger numbers of passersby. Incidentally, you can call their attention to your place

of business by erecting a clearly visible sign that prominently features your telephone number.

\$ & ¢

Test Your Tact — III. Except in fringe areas, an outdoor antenna seems to be one of the most difficult to sell TV accessories. Unreasoning fear of the lightning menace, reluctance to have "that unsightly thing" on the roof of the house, or holes drilled in the siding, plus a tendency to balk at the added expense—all these customer attitudes can add up to stubborn resistance to an outdoor antenna installation. Your most skillful and tactful efforts are often required to jar the customer loose from his preconceived notions.

How would you present your case to him? It may be helpful to stop and think over the following points:

A careless technician named Cy,
While checking a power supply,
Put his hand on a spot
Where the B plus was hot,
And discovered that E causes I.

There was an oldtimer named Billy
Who thought that textbooks were silly,
Now new circuits amaze him
And transistors daze him,
And he doesn't know micro from milli.

What are your reasons for recommending an outside antenna? Besides the obvious profit motive, you also have an interest in improving picture quality so that the customer will be better satisfied with your service work. "A much clearer picture" is your strongest selling point, especially if you can show the customer slight faults in the picture that would be cleared up by a proper antenna installation.

If you run into customer resistance, why try to get across your point all at once? Mildly state the points in favor of an outdoor installation; after the customer has had time to think these over, he may come around to agreement without any further effort on your part.

Stress that you can make a neat-looking installation and reassure him that a well-grounded mast and lightning arrester have been proved safe through many years of experience with antennas much taller than the one you hope to install for him. You can even point out that you are making his home safer by equipping it with a type of lightning rod!

Above all—when the customer finally OK's the job, do it right!

\$ & ¢

Window Dressing. How many variations of the old "How Many Beans in the Jar?" guessing game can you recall seeing? One appliance dealer in Maryland dreamed up one more new twist on this theme. Taking a jumble of miscellaneous parts from junked TV sets, he dumped them all into a jar which he placed in his front window as the basis for a contest.

Here is a good idea for a simple but effective display to use in a TV shop window. If you conduct a "How Many Parts?" contest, a prize such as a free service call or a supply of radio batteries could be awarded to the winner.

\$ & ¢

Repairs Inside and Out. When you have to take a TV set into the shop for a couple of days, inspect the cabinet to see if it could stand a few repairs, too. By offering to have both the chassis and cabinet repaired at the same time, you encourage customers to have minor nicks and scratches removed instead of putting off this work indefinitely. In case you don't want to do your own cabinet touch-up jobs, or damage is beyond your ability to repair, hunt up a furniture-refinishing shop in your neighborhood and make an agreement. Both you and the furniture shop can profit, and the customer still gets the work done at less cost than if the furniture refinisher had to work on the TV set in the home or haul it away, chassis and all, to his shop.

Use Delco Radio Service Parts!

2N278—Highest power transistor used in auto radios.



SPEAKERS



IRON CORES



RESISTORS



CAPACITORS



CONTROLS




TUBES




COILS



VIBRATORS

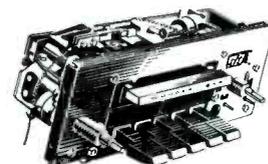

TUNER PARTS

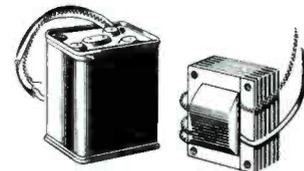

TRANSFORMERS

Your Delco Radio Electronic Parts Distributor carries the complete line, giving you fast, dependable service on the items you'll need for Delco Radio—and other radio—service work. Delco Radio also provides:

- Wide selection of special application parts
- Complete technical training program
- Effective warranty program
- Dealer identification signs

Get the facts today on this truly profitable dealer setup, and grow with General Motors!

Available everywhere through Electronic Distributors associated with . . .



DELCO RADIO

DIVISION OF GENERAL MOTORS, KOKOMO, INDIANA

notes on TEST EQUIPMENT

Informative reports from the lab

by Les Deane

Signal-Pickup Device

The Model 850 Induced Waveform Analyzer shown in action in Fig. 1 is a product of Winston Electronics, Inc., Philadelphia, Pa. The Model 850 provides for pickup and amplification of signals without direct connection to the circuit under test. Output of the analyzer is fed to an oscilloscope for observation and analysis. Tuned circuits are provided so that undesired signals can be rejected.

Specifications and Features are:

1. Power Requirements—105 to 125 volts, 50/60 cps; 30 watts at 117 volts, 60 cps.
2. Frequency Coverage—turret tuner provides for selection of VHF channels 2 through 13 plus inputs at 21, 41, 3.58 and 4.5 mc; fine tuning provided for all RF bands except 21 mc.
3. Functions—high gain audio-video, RF-IF, 3.58-4.5 mc and direct scope input.
4. Input Sensitivities—using oscil-

loscope with input sensitivity of 25 mv/inch, the following typical sensitivities will apply for the various functions of the instrument.

- a. High Gain Audio-Video—1 mv/inch or better.
 - b. RF-IF and 3.58-4.5 input functions:
 - ch. 2 to 6 -- 300 μ v/in. approx.
 - ch. 7 to 13 - 400 μ v/in. approx.
 - 3.58 mc --- 0.6 mv/in. approx. (assuming broad band scope)
 - 4.5 mc ---- 40 mv/in. approx. (assuming broad band scope)
 - 21 mc Band --- 350 μ v/in. ap.
 - 41 mc Band --- 300 μ v/in. ap.
 - c. Direct scope input—same as scope used.
5. Probes—two ring-shaped and one crescent-shaped pickup, small ring for 7- and 9-pin miniature tubes, larger ring for larger tubes, and crescent shape for dual-purpose tubes and other components.
 6. Gain Control—front panel con-

trol gives continuously variable attenuation and also varies tuner bias.

7. Audio Monitor Jack—phone jack on rear of instrument provides for audio monitoring.

8. Demodulation—modulated RF signals are automatically demodulated by the instrument and can be applied directly to scope.

While working with the Model 850, I was impressed by its sensitivity and the ease with which the pickup probes could be used to detect signals at various points on the receiver chassis. A usable indication was obtained when the smaller ring was slipped over the RF amplifier tube (shield removed, of course). I noticed a difference in indication as the ring was moved from the top to the bottom of the tube. Using the crescent-shaped probe, I was able to pick up the audio signal with the pickup next to the speaker leads.

A diagram of the test setup employed with this instrument is illustrated in Fig. 2. The output cable from the Model 850 comes from the rear of the instrument and connects to the vertical input of the scope. The ground lead is clipped to a common ground point in the receiver. No sweep signal is provided by the Analyzer, so the scope is set to sweep at the line frequency or some multiple thereof.

A closeup of one of the ring pickups appears in Fig. 3. The cable shield extends down to the probe and continues in the form of a metal ring around the outside of the pickup. The inside of the probe is another metal ring

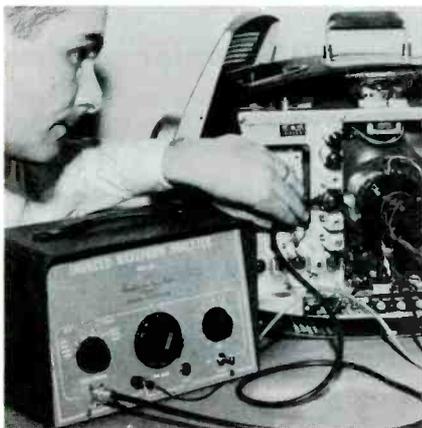


Fig. 1. Winston Model 850 picks up signals without direct contact to the circuit.

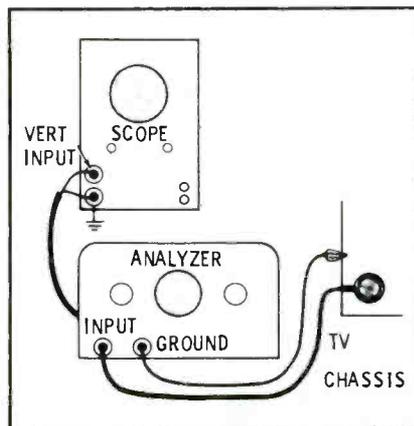


Fig. 2. Test setup for "Analyzer" requires the use of a general-purpose oscilloscope.



Fig. 3. Model 850 uses pickup rings to sample the signal from the receiver.

If it's worth engineers' time...

...it's worth engineered cable




Belden

**TV CAMERA
CABLE**

Belden quality built to exacting specifications for black-and-white or color cameras. Harmonizing color—lightweight for easier handling.

**MICROPHONE
CABLE**

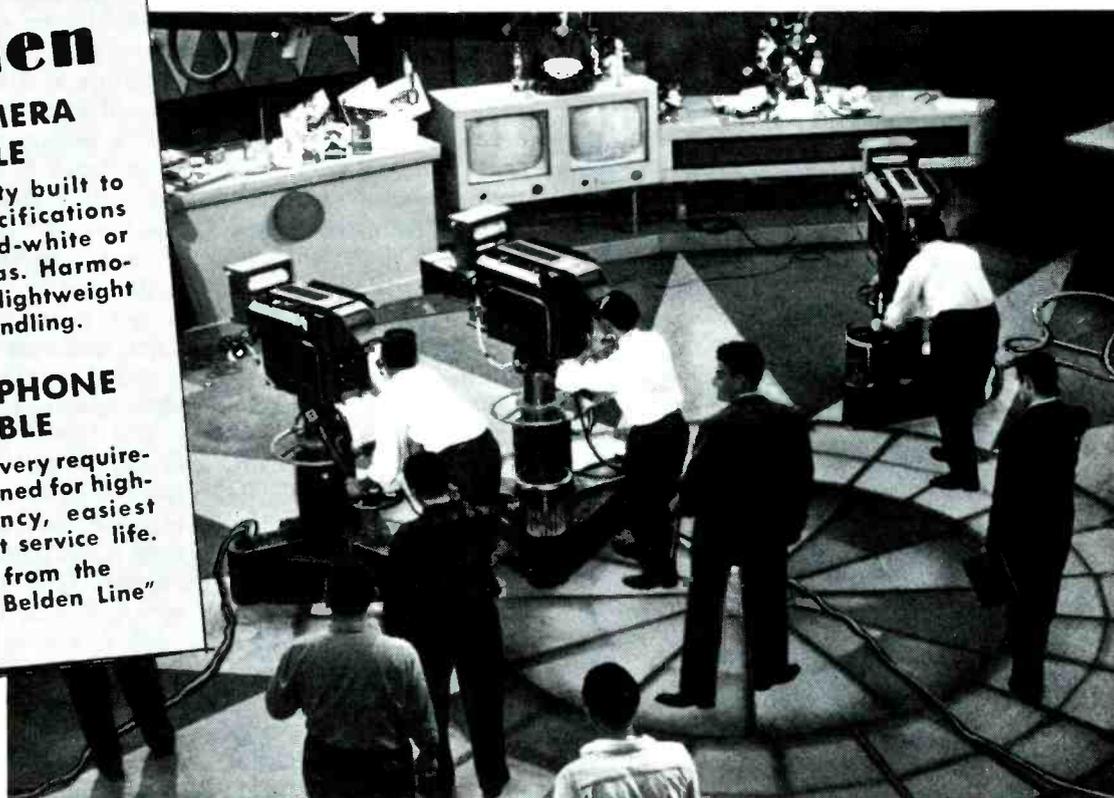A type for every requirement, designed for highest efficiency, easiest use, longest service life.
"Items from the Complete Belden Line"



Belden

WIREMAKER FOR INDUSTRY
SINCE 1902
CHICAGO

5-8

Magnet Wire • Lead and Fixture Wire • Power Supply Cords, Cord Sets and Portable Cord • Aircraft Wires
Welding Cable • Electrical Household Cords • Electronic Wires • Automotive Wire and Cable

NEW! IMPROVED!
SENCORE
 TRC4
TRANSISTOR CHECKER

Another Sencore Time-Saver

America's newest, most popular test instruments

NOW CHECKS:

- ★ Transistors for opens, shorts, leakage and current gain. Includes new gain test on power transistors.
- ★ Crystal Diodes checks forward to reverse current ratio on all diodes.
- ★ Selenium Rectifiers checks forward and reverse currents.

Controls are accurately set for each transistor by referring to replaceable set-up chart on rear. Test leads or socket provides for fast hook-up. See your parts distributor.

SENCORE Mfg. by **SERVICE INSTRUMENTS CORP.**
 171 OFFICIAL RD., ADDISON, ILL.

Cut out this ad now for further information

ONLY \$17.95
 Dealer Net
 Cannot become obsolete. Approved by leading manufacturers.

SIMPLE TO OPERATE

which is the sensitive part of the pickup, and the two metal rings are insulated from each other.

Portable Field-Strength Meter

The Model FSM-1 Field Strength Meter pictured in Fig. 4, manufactured by Blonder-Tongue Laboratories, Inc., Newark, N. J., covers a band of frequencies for VHF television, FM, aircraft, mobile, amateur, and other special services.

Specification Features are:

1. Power Requirements—battery-operated, using three 45-volt units in series for B+, two 1.5-volt batteries in parallel for tube filaments, single 1.345-volt cell for bias.
2. Frequency Range—continuously variable from 54 to 216 mc.
3. Sensitivity—minimum signal strength of 10 μ v up to a maximum of 3 v.
4. Input Impedance—75 ohms, 300- to 75-ohm matching network supplied.
5. Meter Ranges—ten ranges from 300 μ v to 3v full scale are provided using various combinations of built-in RF attenuators; meter provided with db and %AM scales.
6. Accuracy— ± 1 db at full scale using 1000- μ v input.
7. Signal Monitoring Provisions—output jack for both video or sound indications.
8. Size and Weight—8 $\frac{1}{4}$ " \times 12" \times 9 $\frac{1}{4}$ ", 14 lbs. less batteries.

By using a Model FSM-1 in the lab and examining its instruction manual, I found that the average service technician could certainly use an instrument of this nature in the installation and troubleshooting of TV or FM antenna systems. In the shop, it would also be of value when checking the output of a VHF generator, measuring the percentage of AM in an FM signal, or locating a source of interference. The signal accepted by the meter can also be viewed on an oscilloscope or heard through the use of earphones. Observing the sync pulses contained in a composite TV signal, for example, one can easily detect undesired clipping caused by an overloaded amplifier.

A photograph of the instrument's meter face is presented



Fig. 4. Blonder-Tongue Model FSM-1 direct-reading VHF Field Strength Meter.

in Fig. 5. The top scale has ten divisions and is used when the 10 db RF attenuator is out of the input circuit. Under these conditions, the scale may be used with any combination of the other four 20-db attenuators. A small table in the lower right corner of the meter face indicates the proper full-scale reading for attenuation from 0 to 80 in steps of 20 db.

The second scale has six divisions from 0 to 3 and is to be used when the 10-db pad is in the circuit. Reading from this scale, the technician refers to the table in the lower left corner which gives full scale value in volts, millivolts, or microvolts, depending on the number of attenuators being used.

The %AM scale located in the center of the meter is calibrated from 0 to 20 and is used to determine the percentage of amplitude modulation present in an FM carrier. With the meter properly set up, the scale will give a direct reading up to 20%.

The bottom scale on the meter face serves as a db reference indicator and is calibrated from minus 20 to minus 40 db. The scale

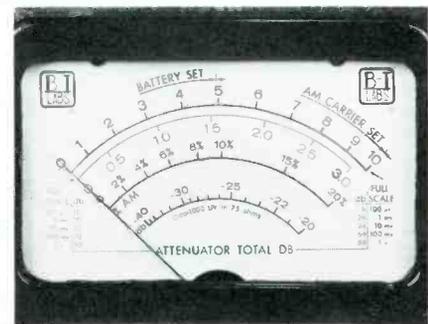


Fig. 5. Meter scales are calibrated against db attenuation used during measurement.

Seeing Double?
 SURE... THEY LOOK ALIKE BECAUSE THEY ARE EXACTLY ALIKE

Each Merit product of the same type is exactly the same as another—both in construction and appearance.

COMPARE IT WITH MERIT

Take a Merit product off the shelf. Compare it with any other similar product on the market. You'll find Merit is superior!

COMPARE IT WITH MERIT
 MERIT COIL AND TRANSFORMER CORP.
 MERIT PLAZA . HOLLYWOOD, FLORIDA

is based on a standard of zero db equals 1000 microvolts across 75 ohms. The measured signal will either be above or below this standard by the db value indicated on the scale.


When using the FSM-1 to test the signal strength of local TV stations on our antenna distribution system in the lab, I set up the instrument as follows: By placing the ATTR slide switches in their up positions, I started out with all db attenuators in the circuit. Next, I turned the AM CARR SET switch completely counterclockwise and placed the function selector to VIDEO/FIL position. I then adjusted the filament battery voltage until the meter pointer was directly over the BATTERY SET mark located at the very top of the meter face. Changing the function selector to SOUND/B+ position, I proceeded to adjust the B+ control until the pointer again fell over the BATTERY SET indication. With filament and B+ voltages properly set, I placed the function selector to the FS (field strength) position.

Since the antenna system being checked terminated into a balanced 300 ohms, I made use of the Model MB matching network supplied with the 75-ohm instrument. Following instructions for wiring the special solderless connectors and using a short piece of 75-ohm coax, I attached the antenna lead to the matching device and the coax connector to the instrument's RF input jack. Zeroing the meter and tuning to the desired channel frequency, I switched the attenuator pads out one by one until I obtained a usable meter reading.

I checked filament and B+ voltages periodically as I measured the available signal level from four local TV stations and our



To fit over 90% of all quality arms, use **SONOTONE** **CERAMIC CARTRIDGES**

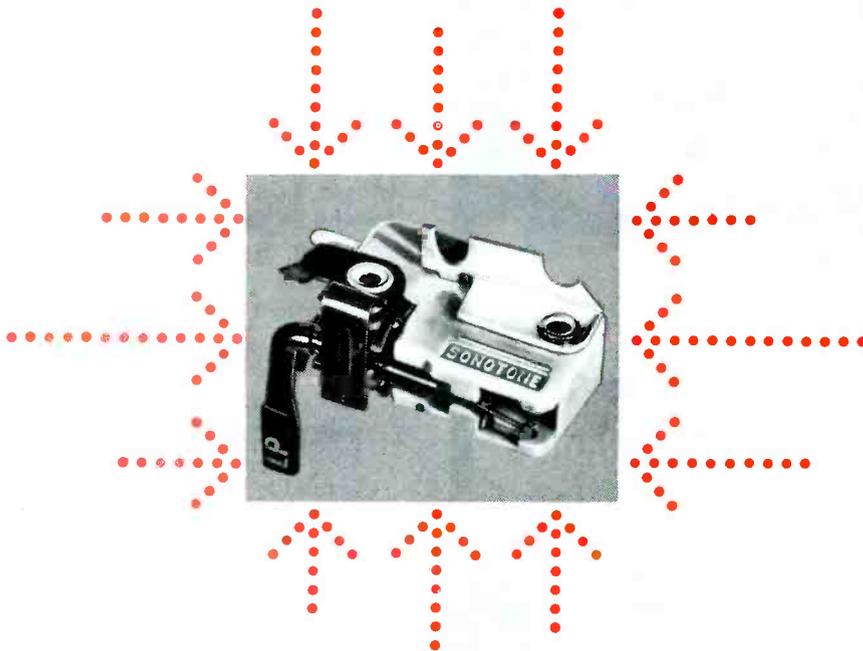

**because 50
manufacturers use
them now
as original equipment**

Concentrate your replacement work around the standard cartridge of the phonograph industry. Because Sonotone Ceramics fill the bill in so many cases, you have less cartridge lines to inventory and stock. You also cut down custom fitting and tedious adjustment ...actually save time and money.

Best of all, you give your customers better sound than they bargained for. Sonotone Ceramics give out full range—20 to 20,000 cps—flat, without pre-amp or equalizer. You're *all* ways ahead when you stock Sonotone Ceramic Cartridges.

Order today from your parts dealer. Write for replacement chart and further information about Ceramic Cartridges to:


Sonotone®

Electronic Applications Division, Dept. CP-58

ELMSFORD, NEW YORK

CO. L.

TRANSISTOR RADIO REPAIRS NOW EASY!

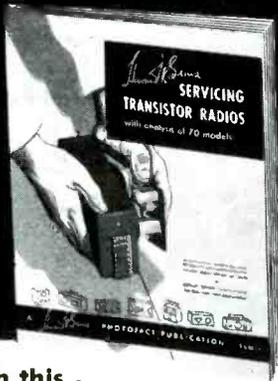

with this
NEW *Howard W. Sams* BOOK

"SERVICING TRANSISTOR RADIOS"

COMPLETE ANALYSIS OF 70 POPULAR TRANSISTOR RADIO MODELS

includes new
General Motors
(Delco)
Transistorized
Auto-Portable
Radio

Also Valuable Section—
"BASIC POINTERS ON SERVICING
TRANSISTORIZED RADIOS"...

COVERS LATEST MAKES AND MODELS

This book helps you earn big profits on Transistor Radio repairs—gives you complete, time-saving information—helps you become an expert on transistorized radios! Complete data on 70 latest models is based on actual lab analysis of each set. You get the famous Sams Standard Notation schematics—accurate, big, legible; full photo views of each chassis, with all components identified; complete alignment instructions; complete parts lists with full replacement data—everything you need to be successful in fast-growing transistorized radio servicing. Here's a "must" book for your bench. Order it now!

152 pages; 8½ x 11" **\$295**
PRICE ONLY

SEE THIS BOOK AT YOUR SAMS DISTRIBUTOR OR MAIL COUPON

FREE TRIAL COUPON

Howard W. Sams & Co., Inc., Dept. 3-EE8
2201 E. 46th St., Indianapolis 5, Ind.

Send me Sams "Servicing Transistor Radios" for 10 days FREE examination. In 10 days I will pay for the book, plus few cents delivery cost, or return postpaid.

We pay delivery costs if you remit with this coupon; same return privilege.

Name _____

Address _____

City _____ Zone _____ State _____

(Outside U.S.A. priced slightly higher)

own closed-circuit system. Using the scale called for in the tables on the meter face, I was able to read the various signal voltages directly.

Something Unique in Probes

Doss Electronic Research of Kansas City, Mo., has developed three interesting pieces of equipment especially designed with the TV technician in mind. Each can be held in the hand, the largest being about 7½" long and less than 2" in diameter. The unit shown in operation in Fig. 6 is known as the Video Master Model D-200, a tuned, high-gain RF demodulator probe.

Specifications and Test Features are:

1. Power Requirements—110 to 120 volts AC for tube filament supply, resistive-type line cord and series-dropping resistor provided; amplifier B+ voltage supplied from receiver under test through the special clip lead provided.
2. Accessory Equipment Needs—any normally operating general-purpose oscilloscope.
3. Frequency Ranges—built-in IF amplifier tunable over the 20- and 40-mc IF bands, separate calibration dial and adjustment for each range.
4. Test Applications—IF signal-tracing from TV tuner output to video detector; stage-by-stage IF and trap alignment; eliminating AGC circuit as source of trouble; general tuner and IF troubleshooting.

In my examination of the Model D-200, I found that it surpasses the usefulness of ordinary scope demodulator probes by having, in addition to a detector circuit, a complete tunable IF stage. This circuit furnishes amplification of the composite video signal prior to detection, and thus provides a sizable scope indication for the technician to analyze. Deciding to use the Video Master for signal tracing (its primary function), I followed the instructions outlined in the manual and connected its output cable to the vertical input terminals of an oscilloscope. I next attached the red lead to the IF B+ line of a TV chassis. After permitting the instrument and chassis to warm up for a short time, I placed

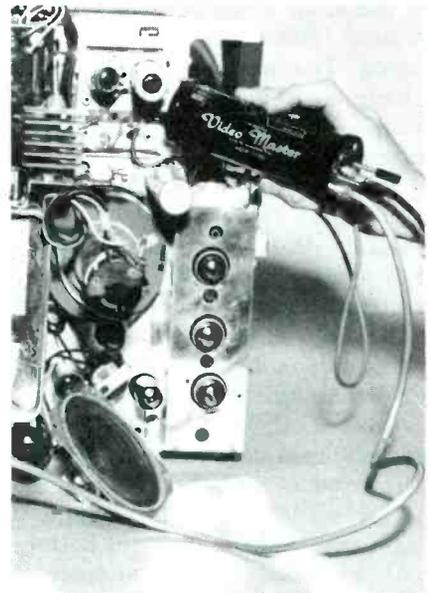


Fig. 6. Doss probe Model D-200 is used with a scope for RF and IF servicing.

the probe tip on the IF output point of the tuner.

Since the IF range of the receiver was in the 40-mc band, I placed the 20/40-mc switch in the appropriate position. The switch, a slide-type device, is located on the body of the probe where it can easily be operated with the thumb. Tuning the 40-mc slug at the rear of the probe. I was able to obtain the signal indication shown in Fig. 7. The strength of the signal obtained at this point was such that I didn't need all of the sensitivity offered by the scope. In weaker signal areas, the scope gain would have to be increased, especially when viewing a signal near the front-end of the receiver.

While performing other tests with the Model D-200. I checked its operation over a fairly wide range of B+ voltages and noticed little change in signal gain with B+ variations from 125 to 250 volts. This range is typical of that found in the IF section of most receivers. Methods for IF alignment and other troubleshooting

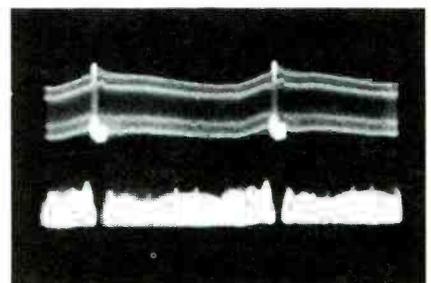


Fig. 7. Waveform of the tuner output signal produced by Doss "Video Master."



Fig. 8. Other TV troubleshooting probes manufactured by Doss.

procedures are clearly discussed in the instruction manual supplied with the Video Master.

Two additional Doss probes are pictured in Fig. 8. The Sweep Analyzer Model D-100 is used in conjunction with an oscilloscope to determine the condition of inductive components such as fly-back transformers, yokes, and vertical oscillator or output transformers. A sharp pulse is applied to the component, producing a ringing which can be observed momentarily on a scope screen. The scope pattern formed by this action will appear as a spiral, mushroom, or circular-shaped figure depending on the inductance value of the component under test. Certain components may be tested in-circuit; others must be at least partially disconnected.

By comparing the short-duration patterns flashed on the screen with those given in the instruction booklet, the technician can detect shorts, opens, or leakage in TV sweep components. In addition, the probe can be used to check power, audio, and interstage transformers as well as other inductive components.

The Slave Oscillator pictured in Fig. 8B is another probe designed especially for sweep troubleshooting. Identified as the Model D-500, the instrument is actually a gen-



BURTON BROWNE New York

When a Serviceman Needs a Friend



He uses Pyramid's unsurpassed Capacitor-Resistor Test Equipment to determine defective components in his repair jobs.

...And he replaces
Capacitors and Selenium Rectifiers
with top quality Pyramid Components.



PYRAMID
ELECTRIC COMPANY
North Bergen, New Jersey

Export: 458 Broadway, New York 13
Canada: Wm. Cohen, Ltd.,
7000 Park Ave., Montreal

NEW
IMPROVED
SENCORE
LC3
Leakage Checker

Another Sencore Time-Saver

Check these outstanding New Features
Now — For the first time . . .

Checks 130 different tube types — more than any other "grid circuit" type checker. Includes UHF and latest type tubes.

Checks picture tubes without removing tube from cabinet or chassis.

New Roll Chart prevents obsolescence — just dial the tube type and save time. Chart is easily replaced at no extra cost.

Dynamic Filament checks including heater to cathode leakage & shorts — no need for a second filament tester.

Two spare preheating sockets to cut down testing time.

Capacitor checks simplified.

The LC3 provides all these new improved features in addition to those employed in earlier leakage or "grid circuit" testers. A must for any TV service technician.

SENCORE SERVICE
INSTRUMENTS CORP.
 171 Official Rd • Addison, Ill.

In stock at your local parts distributor

\$28.95
 DEALER NET
Really Whips Tough Dogs

Cut out this ad now for further information

all new edition
 VOL. III. NO. 1

+ **PLUS**

up-to-date component prices
the quick easy way to figure service charges

Dave Riee's

OFFICIAL PRICING DIGEST

Flat rate and hourly service charges, based on and showing regional and national averages, plus up-to-date list or resale prices on over 63,000 components. Arranged alphabetically by manufacturers and products, numerically by part number. Compact, convenient size fits in tube caddy, toolbox or pocket. \$2.50 per copy from your distributor.

ELECTRONIC PUBLISHING COMPANY, INC.
 180 N. WACKER DRIVE, CHICAGO 6, ILL.

erator with output signals which may be substituted for either the vertical or horizontal oscillator signals in a TV receiver. The unit operates on 117 volts AC with B+ supplied from the receiver under test. A 12BH7A tube is required to complete the two individual oscillator circuits contained within the probe.

The unit can be used to isolate trouble from the grid of the vertical or horizontal output tube back to the video detector stage if necessary. When the sweep output circuits are operating normally, I found that I could substitute for either oscillator driving signal and reproduce a raster having sufficient sweep. Aside from vertical and horizontal hold controls, the probe also features a vertical size adjustment and a special jack for sync control.

Wire Your Own Scope

PACO Electronics Co., Inc., Glendale, L. I., has recently introduced a new line of test instruments to the industry. PACO, a subsidiary of Precision Apparatus Co., Inc., markets this line of equipment in kit form only. One of their instruments is the Model S-50 Oscilloscope shown completely assembled in Fig. 9. Designed for general-purpose applications, the unit features adequate sensitivity and frequency response for both radio and monochrome television servicing.

Electrical Specifications are:

1. Power Requirements — 105 to 125 volts AC, 50/60 cps; power consumption approximately 70 watts.
2. Cathode Ray Tube—5BP1 with green fluorescence and medium persistence, screen calibration mask provided.
3. Vertical Amplifier — sensitivity 90 mv rms/inch; sinusoidal response from 5 cps to 1.2 mc ± 3 db or ± 6 db to 2 mc; input impedance 1.5 megohms shunted by 25 mmf; push-pull operation with 3-step input attenuator and calibrated vernier; maximum input voltage 400 volts; direct connection to vertical deflection plates provided.
4. Horizontal Amplifier—sensitivity 250 mv rms/inch; sinusoidal response to 450 kc ± 3 db or ± 6 db to 700 kc; input impedance



Fig. 9. Model S-50, 5" Cathode Ray Oscilloscope—a new "PACO" kit instrument.

10 megohms shunted by 25 mmf; push-pull operation with calibrated vernier gain control.

5. Sweep — linear sawtooth from 20 cps to 150 kc, selector provides 4 overlapping ranges plus line and external positions; sync switch provides internal, external or line synchronization; sync amplitude and horizontal phase controls on front panel.
6. Internal Calibration — sinusoidal signal at line frequency, amplitude 1.0 volt p-p, on-off calibration switch on front panel.

Since many of our readers have expressed the desire to hear more about kit-type equipment, we recently obtained a Model S-50 kit for examination. The instrument was wired and assembled in the lab, giving me first-hand information concerning the construction procedures, tools required, and time spent.

I found that, in addition to a carefully written step-by-step assembly procedure, the manual contained drawings and a complete schematic of the instrument's wiring. These drawings accompany the manual and may be attached to the wall above your work bench as a quick reference guide. I might also mention that soldering instructions, as well as color code and symbol charts, are incorporated in the manual to assist the builder in wiring and in component identification.

The use of printed-board construction for a large portion of the instrument's circuitry lightens the wiring task considerably. A small-tipped pencil iron of 25 to 60 watts is recommended for the

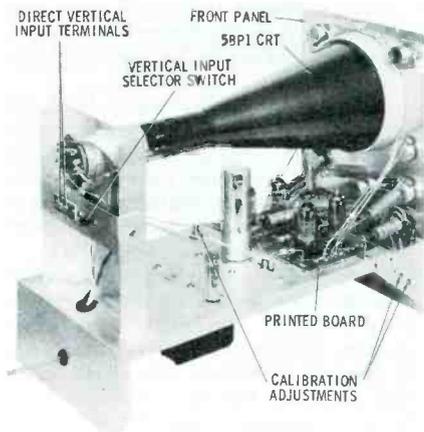


Fig. 10. PACO kit has printed-board assembly, neat lead dress, simplified layout.

soldering operation. Other tools required to complete the kit are of an ordinary variety and include such items as long-nose pliers, side cutters, screwdrivers, and a set of nut drivers or end wrenches.

A rear view of the finished chassis is pictured in Fig. 10. Some of the major items are pointed out, but the power transformer, line fuse and several others are on the underside of the chassis and cannot be seen.

Having seen how this kit was put together, I estimate that the average technician could assemble this scope in 6 to 10 actual working hours, including testing and calibrating. Naturally, allowances must be made for variations in the working speed of the individual and the facilities available to him.

Any piece of equipment, whether assembled by the user or by factory-trained personnel, must be constructed *exactly* as called for in the specifications or the instrument's over-all operation may suffer. A chain is only as strong as its weakest link—keep this in mind at all times during the assembly of a kit instrument. ▲

YOU SHOULD KNOW...

... the following about your
PF REPORTER subscription:


- ✓ To determine expiration date of your subscription, refer to number at right on bottom line of your address inscription. Example: 359 means that your subscription expires with the March, 1959 issue.
- ✓ To assure uninterrupted delivery when moving, please notify us at least a month in advance and include your present address or send along an address label from one of your back issues.
- ✓ Copies of the PF REPORTER are mailed by the first of the month at latest. If your copy arrives late it is due to conditions beyond our control.

Circulation Department, PF REPORTER
2201 East 46th St., Indianapolis 5, Ind.

**Customers Impatient?
It's full speed ahead**



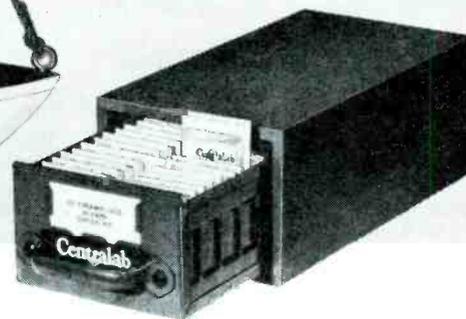**with
Centralab.
Hi-Kap*
Ceramic
Capacitor
Kits**



No delays! It's always smooth sailing when you use Centralab ceramic capacitor kits. No extra trips to your distributor, no wasted time. The units you need are on hand when you need them.

To keep you on an even keel, these heavy gauge steel kits contain balanced inventories of the most frequently used values. Individual values are prominently and clearly labeled, so you can locate the Hi-Kap you need, instantly. The new rigid plastic package permanently separates and protects the units—yet is easily opened to remove a single capacitor.

So don't be left at sea. Ask your distributor about these four time-saving kits—and while you're at it, be sure to get your free copy of Catalog 30, listing the full line of Centralab capacitors and other quality components.

FREE: \$4.75 cabinet (4"x7"x11") with each kit.

D6K-200 Kit—200 Tubular Ceramic BC Hi-Kaps (27 values)
DDK-200 Kit—200 Standard Ceramic Disc Hi-Kaps (31 values)
TCK-80 Kit—80 TC (Temp. Compensating) Hi-Kaps (40 values)
HVK-150 Kit—150 High Voltage Disc Hi-Kaps (19 values)

Centralab products are listed in COUNTERFACTS, PHOTOFACETS, and THE RADIO-ELECTRONIC MASTER.

Centralab
*Trademark

A DIVISION OF GLOBE-UNION, INC.
942E EAST KEEFE AVE • MILWAUKEE 1, WIS.
In Canada: 804 Mt. Pleasant Rd. • Toronto, Ontario

**SWITCHES • PACKAGED ELECTRONIC CIRCUITS • CERAMIC CAPACITORS
CONTROLS • ENGINEERED CERAMICS • SEMI-CONDUCTOR PRODUCTS**

the troubleshooter

answers your
service problems

Poor Vertical Sync


I have had considerable trouble with vertical roll in several General Electric "K" line television sets (Model 21T28). All components and voltages check OK in the sync and vertical circuits. I can find no production changes recommended by the manufacturer, so I have tried substituting parts of a slightly different value for almost all capacitors and some of the resistors in the sync and vertical sections of the receivers. So far, none of the changes have been of any help. Four identical sets have had this same trouble since they were new, and this leads me to believe that there is a defect in the design. Can you recommend anything to improve the vertical stability?

WILLIAM B. WOOD

Varnville, S. C.

The circuits surrounding the AGC switch were changed during the production run of these sets in order to improve vertical stability. See if the wiring in your receivers corresponds to the schematic shown, which gives the late-production circuitry. In addition to the changes shown, the value of the vertical hold control was reduced from 250K to 200K in later production.

In case the sets still do not work properly with the revised circuits installed, you probably will have to concentrate on trying to increase the p-p amplitude of the sync pulses applied to the vertical oscillator. Before modifying any part of the integrator or sync amplifier circuits for this purpose, make sure that you do not have excessive signal or DC bias at pin 1 of the 6CS6 sync separator. Either condition would cause this tube to cut off on sync tips, reducing the amplitude of the output pulses.

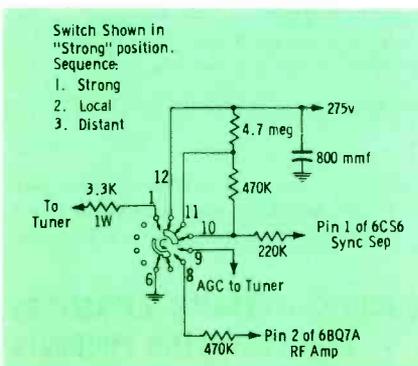

Overheated Flyback

The horizontal output transformer on a Capehart Chassis CT-157 overheated until the wax melted. I installed a replacement, but it also heated up after three or four hours of operation. I have replaced the yoke and all tubes and capacitors in the circuit, but have not cured the trouble. Voltages are correct when the set is first turned on, but they drop when the transformer starts to heat up.

MIKE MAKIDON

Television Service Eng'n'g, Inc.
Flint, Mich.

Try to find out what portion of the circuit is overloading the transformer. First, insert a DC milliammeter in the cathode circuit of the horizontal output tube. If the current is greater than the normal value of 90 to 100 ma, this may indicate that insufficient drive signal is reaching its grid. You should be able to bring this signal up to 75 volts p-p by adjusting the drive control; if you cannot, then look for trouble in the grid circuit or back in the horizontal oscillator circuit. Another possible cause of excessive current in the output tube is an open screen-bypass capacitor.

If output-tube current is normal, your trouble may be in the high-voltage rectifier circuit. One suspect would be the filter capacitor—a 500-mmf, 20-KV unit.

Pie-Crust Effect

In an Admiral Chassis 19K1, I recently installed an exact replacement flyback transformer. Since then, I have had pie-crust distortion around the edges of people and objects in the TV picture. This distortion, accompanied by lines or streaks, increases when the brightness control is turned up. Also, I sometimes hear arcing that I can't locate.

E. H. UNDERWOOD

Ernie's Radio & TV Service
Bluefield, W. Va.

If you installed the transformer correctly, and it is not defective, rule it out as a suspect. You mention that the distortion seems to increase at high brightness levels; this suggests two possibilities for trouble, neither of which are directly concerned with the flyback.

1. You might have AC ripple in the horizontal AFC voltage. To check for this condition, temporarily bridge a

large capacitor (about .05 mfd) from the grid of the horizontal oscillator to ground, and see if the pie-crust effect disappears.

2. The picture tube might be defective. Temporarily substitute a similar type or a universal check tube, and see if the picture clears up. Incidentally, does the aquadag coating on the outside of the picture tube have a secure connection to ground?

I suspect that the arcing is not directly related to the picture distortion; instead, it is probably caused by a lead-dress problem inside the high-voltage cage. If you had to reroute some leads when you installed the new flyback, check them for adequate spacing away from other leads and from the transformer windings.

Radio Design

Lately I have serviced several small radios that use a 12BA6 tube in the converter stage. Since this requires an extra winding on the oscillator coil, I am curious as to the advantages of this type of circuit over a conventional one using a 12BE6.

JOHN W. KELLER, JR.

Oaklyn Radio & TV Service
Sunbury, Pa.

The 12BA6 pentode, unlike the 12BE6 pentagrid tube, lends itself to use in a circuit design that provides some gain in the converter stage. Thus, the entire IF stage can be omitted, and the resulting cost reduction more than makes up for the small extra expense of a more complex oscillator coil.

Speaker Distortion

I have two radios on the bench with similar symptoms. When the volume on either set is turned up more than halfway, the output becomes extremely noisy. Below the halfway point, both sets sound very good, I have decided that some stage is overdriven, but haven't been able to cure the trouble.

F. WAYNE NEAL

Temple City, Calif.

You didn't specify the kind of noise you are hearing, but your comment about an overdriven stage leads us to believe that your complaint must be distortion or garbled sound rather than impulse-type noise.

The original speakers might have defects such as a rubbing voice coil or torn cone which could give rise to distortion, especially at high volume levels. It's even possible that the radios are capable of putting out more audio power than the speakers can handle. Try a substitute speaker or known good quality in each set, and see if the sound is improved.

If the trouble is not in the speaker, try injecting a signal at the second detector and viewing the output across the speaker voice coil with a scope. This will give you a clear visual indication of whether or not the signal is being distorted as it passes through the audio section of the receiver.


Poor Vertical Sync

A General Electric Model 21C238 loses vertical sync at times, and the vertical hold control has very little usable range. I changed all tubes several times in the vertical and sync circuits and also tried a new integrator unit and new height and vertical hold controls. Scope presentations appear normal. All voltages are normal except at pin 7 (the #3 grid) of the 6CS6 sync separator, where I read -25 volts instead of the -4.5 volts given on the PHOTOFAC schematic.

ROBERT G. JONES

Elliott, Ill.

There's a chance that -25 volts is normal at pin 7 under the conditions you are using for measurement. The reading of -4.5 volts is correct only when no signal whatsoever is being applied to the 6CS6. Any input signal will develop grid-leak bias, driving the voltage in a negative direction. Even with no video signal present, enough random noise might possibly be coming through to increase the bias to -25 volts.

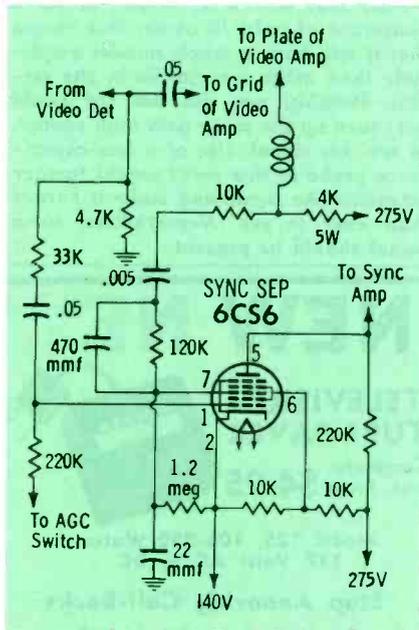

To help isolate the trouble, feed a signal to the set, adjust the scope sweep to 30 cps, and recheck the plate waveform of the sync separator. If it is normal in shape and amplitude, I would say your trouble is in the vertical circuits rather than the sync stage. But a faulty waveform would tend to confirm your suspicions about the #3 grid voltage of the 6CS6. If this is actually too negative, the basic trouble is probably too long a time constant in the grid-leak circuit. Check especially for high-resistance soldered connections and increased component values.

B+ Too High

A Westinghouse Chassis V-2192 came to me with the horizontal output screen resistor open. After replacing it, three new troubles showed up. It had visible

retrace lines, a slight horizontal fold-over at the left of the screen, and slight pulling at the top of the picture. I installed a retrace suppression circuit, but then the picture would come in rolling for 30 seconds or more after turning the set on. I put a cathode bias network on the horizontal output tube (33-ohm resistor in parallel with a .1-mfd capacitor between cathode and ground) and this eliminated the foldover. But I can't seem to put my finger on the cause of the pulling. B+ voltage is 370 volts. Is this too high?

NORRIS ASCHE

Leigh, Nebr.

If you have 370 volts of B+, this is too high. Some step should be taken to lower it to the prescribed value of 310 volts output from the rectifier filter network. Suggest correcting this trouble first—it may be the cause of all the troubles!

The bending or pulling you describe is most likely due to trouble within the horizontal AFC and multivibrator circuits. The DC output of the AFC circuit is filtered and applied to the horizontal multivibrator as a control voltage. A lack of filtering of this voltage would cause waving or bending to occur in the picture. You can check for this condition by viewing the waveform at the input grid of the multivibrator; the presence of ripple means poor filtering.

The vertical roll during the first 30 seconds of operation sounds as though a tube in the sync circuits is slow to heat up, unless your retrace suppression circuit has affected sync stability. See if sync is improved with the new retrace blanking circuit disconnected. If not, check by substitution the tubes in the sync circuits, also those in the AGC and video circuits.

Noisy Vibrator

I have just finished installing a new vibrator transformer, buffer, and vibrator in a 1953 Mercury push-button radio. It plays perfectly and all voltages are normal, but the vibrator makes an unusually loud and annoying buzz whenever the accelerator is depressed. The noise does not come through the speaker, but it is loud enough to be heard above the signal from the radio. I have tried several different vibrators, and they all do the same thing.


HOMER L. McANINCH

Texas City, Texas

A certain amount of increase in DC supply voltage is normal when you step on the accelerator; however, if the voltage rises much above 7 volts, you are likely to exceed the rating of the vibrator and produce a loud buzz.

Check the DC voltage at the "A" input of the radio; if this rises abnormally when you speed up the motor, have the car's voltage regulator checked over by an auto mechanic. Trouble there will shorten the life of the car battery as well as that of the radio.

CADDY TUBE TESTER

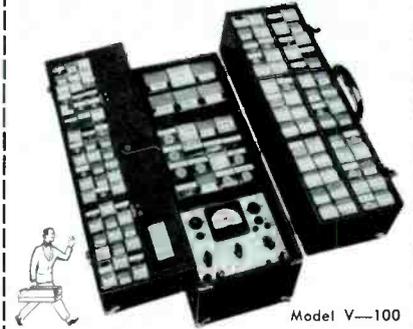

Model V-100

FOR RADIO-TV SERVICE CALLS

Here's the fastest, most reliable tube checker ever designed — built right into an excellent, large-capacity caddy! You can check an entire set of tubes for radio or TV in minutes, replace the faulty ones immediately and be on your profitable way. Checks picture tubes, selenium rectifiers, more than 500 receiving tubes. Only \$99.50 dealer net.

See your supplier or write for details.

VIS-U-ALL products company
303 Fuller N.E., Grand Rapids, Mich.

WORKMAN TV INC.


presents

The BELIMITER

USED IN RCA TV SETS FOR PROTECTION OF DEFLECTION CIRCUITS



Model # 200-10

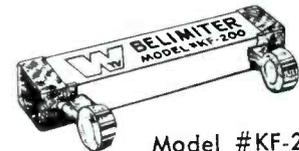

Model # KF-200



Model # LC-200


AVAILABLE AT YOUR LOCAL PARTS JOBBER
ASK FOR BULLETIN #SB1

WORKMAN TV INC.
TEANECK, N. J.

Another Sencore Time-Saver

SENCORE FILAMENT CHECKER

MODEL FC-4

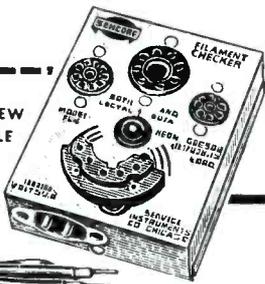

- ★ COMPLETELY NEW
- ★ MORE VERSATILE
- ★ LOWER COST



Quickly finds any open filament. Especially handy for servicing series filament TV sets and radios; only checker that checks all octals, lactals, 7 and 9 pin miniatures automatically.

Continuity and voltage tester — no switches, merely plug in test leads.

AT LEADING DISTRIBUTORS EVERYWHERE Mfg by

SENCORE SERVICE
INSTRUMENTS CORP.
171 OFFICIAL RD., ADDISON, ILL.

Only \$295

DEALER NET WITHOUT LEADS \$2.75

POPULAR SENCORE PRODUCTS

- Transistor Tester
- Leakage Checker
- Filament Tester
- Voltage Regulator
- Bias Supply

Poor Color Reception

I am unable to get a good color picture on my RCA Model 21CT661U color TV set. In this area, most of our color shows are on Channel 14, with some also on 50. Black-and-white reception is pretty good, but I get a strong RF interference pattern and color snow when I turn the color on. The receiver circuits seemed to be working all right when I went through a color alignment of the set.

MARVIN PEYTON

Henderson, Ky.

It sounds as if the high frequencies in the incoming signal, including the color information, are being attenuated. Have you checked the frequency-response curves in the RF, IF, video and chroma sections of the receiver?

Since Channel 14 is right on the edge of the UHF band, there is also a strong possibility that the response of your present antenna is not flat over the entire bandwidth of this channel. Try one having high-band response which extends well into the UHF range.

Intermittent Rolling

I have a Zenith Model R2671E that is giving me a headache. In the customer's home, the picture will roll vertically for a few seconds every once in a while, or else the vertical blanking bar will move up to the center of the screen and come to rest for a few seconds before moving back down. Adjustment of the vertical hold control will restore sync. With the chassis out on the bench in my shop, the set operates perfectly except that the picture will roll one frame whenever I change channels.


AC voltage in the customer's home varies from 105 to 117 volts.

CARLYLE WHEELER

Wheeler's Radio Service
Madison Heights, Va.

To help isolate the trouble, view the waveform at the output of the vertical integrator while you vary the applied AC line voltage with a variac. If the sync pulses (spikes on top of the waveform) momentarily decrease in amplitude when the voltage is shifted, make further scope checks in the sync, AGC, and video stages; there may be a defect in one of these circuits which causes a tendency toward clipping or compression of the sync pulses under certain conditions. You may be able to find a setting of the AGC and fringe lock controls which will minimize the loss of sync.

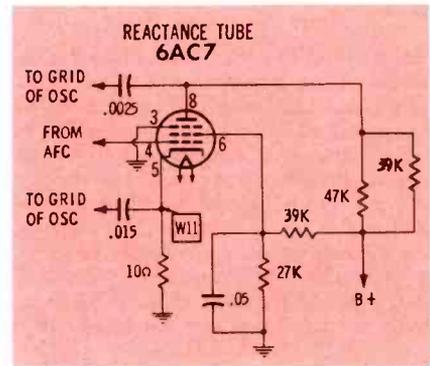If the amplitude of the vertical sync pulses is not much affected by changes in line voltage, you can assume that the vertical oscillator itself is unstable or abnormally sensitive to changes in B+ voltage. The vertical output transformer would be worth checking if other tests don't solve your problem.



AFC Analysis

I am working on a Gruen type of horizontal sweep system (sine-wave oscillator controlled by a reactance tube and discriminator). All waveforms in the circuit look normal as described in the article about this in the August, 1954 PF REPORTER, with the one exception of W11 at the cathode of the reactance tube. I am unable to get a waveform at this point.

J. G. RODRIGUEZ

Vista, Calif.

Note that W11 is developed across a resistance of only 10 ohms; this means that it will have a much smaller amplitude than other waveforms in the circuit. Possibly you did not (or could not) turn up the scope gain high enough to see this signal. Use of a low-capacitance probe at this point would further attenuate the signal and make it harder than ever to see. Nevertheless, some signal should be present.

ask the "Man-on-the-Roof" why he prefers

South River



TWO TO A SET

RATCHET TYPE CHIMNEY MOUNT

Model RT (Galv. Banding)
Model RT-ST (Stainless Banding)

FASTEST, SIMPLEST, MOST CONVENIENT EVER MANUFACTURED — Mounts in 2 simple steps. Completely factory assembled with no eye-bolts, banding clips, nuts, etc., to handle. Furnished with flat-lay, non-coiling banding, heavy gauge embossed, welded steel construction. Forged, heat treated Alum. ratchets.

Write for new catalog

SOUTH RIVER
METAL PRODUCTS CO., INC.
South River, New Jersey

pioneer & outstanding producer of finest line of antenna mounts

NEW NEW

TELEVISION TUBE-SAVER

Complete List Price \$4.95



Model 125, 100-250 Watts
117 Volts AC or DC

Stop Annoying Call-Backs

By absorbing damaging in-rush current so destructive to television and Hi-Fi tubes, the Tube-Saver eliminates 9 out of 10 callbacks by more than tripling the life of all tubes . . .



Model 101-2—100-300 watts, \$1.85 List

WUERTH SURGISTOR

A new component easily installed by a serviceman to reduce call-backs by eliminating surge current damage to television and Hi-Fi tubes.

Already available from:

Chicago Allied Radio
New York Lafayette Radio
AND OTHER DISTRIBUTORS
THROUGHOUT THE COUNTRY

Wuerth Tube-Saver Corp.
9125 Livernois Ave., Detroit 4, Mich.

Shop Talk

(Continued from page 12)

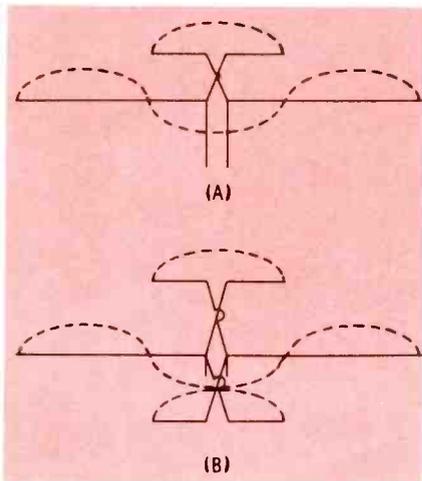


Fig. 4. Connections for small dipoles used in Clear Beam "Tri-King" array.

The same triple dipole arrangement is used in a yagi by Channel Master and given the name of "Rainbow" antenna. (See Fig. 5.) An interesting feature of this yagi is the use of separate reflectors and directors for the low and high bands. For the low band, the elements shown in heavy lines in Fig. 6A are the active ones, while the other elements, depicted by thin lines, are without much effect. For the high band, the dark elements in Fig. 6B are active, while the low-band elements are not.

Note, too, that the high-band directors and reflectors each possess three sections (Figs. 5 and 6C), with insulators between each section. The insulators hold the elements firmly in place, making the combination structurally strong. By this arrangement, the effect of three high-band yagis mounted side by side is achieved. The use of separate reflectors and directors for the low and high bands results in higher gain and sharper directivity. In effect, this is an all-channel yagi supported by a single crossarm.

Another Approach

Still another approach to the use of a low-band dipole at the higher frequencies was developed by Technical Appliance Corp. (TACO). Their method is derived from collinear arrays in which those sections producing out-of-phase currents are folded back on themselves so that the undesirable currents are eliminated.

HOW TO SELL MORE RECOTON REPLACEMENT NEEDLES

JUST TELL YOUR CUSTOMERS THESE 6 IMPORTANT FACTS...

1. There is no such thing as a permanent needle.
2. There is a RECOTON needle for every purpose and every pocketbook.
3. RECOTON needles are the finest in fidelity, quality and value.
4. RECOTON needles are always priced lowest.
5. RECOTON replacement needles are mounted on large, easy-to-read cards.
6. All replacement data and installation instructions are printed right on the cards.

And remember — RECOTON backs you up with the most complete line in the industry, compelling advertising and intensive merchandising; plus most convenient reference, model numbering and inventory control.


Insist on RECOTON.




A RECOTON PLUS: Self-selling stylus merchandiser. 100 power microscope lets customers check their own styli. Increases sales, profits, turnover!

Recoton CORPORATION
52-35 Barnett Avenue Long Island City 4, N. Y.

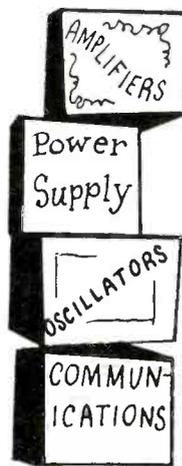93 ELECTRONIC BUILDING BLOCKS ...for your favorite projects!



Like to have fun with electronics? Enjoy building electronic garage door openers, treasure locators, burglar alarms, baby sitters and the like? Here's the book that goes along with you. Rufus P. Turner shows you 93 different circuits (many transistorized) to help you in your construction projects and electronic doodling. Circuits for amplifiers, oscillators, power supplies, communications equipment, control and photo-electronic devices! Use them as is. Change them. Group them together. Make them springboards for your own ideas—but have fun with them. Turner has tested every one of them—and they all work—debugged! This is a book you'll thumb through every time you have a brainstorm. Run down to your distributor and get a copy while they're still in stock and you'll see what we mean. Better still—buy two so you won't feel lost if the first one wears out.

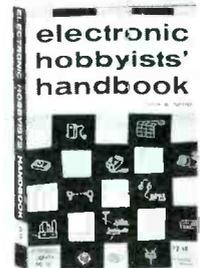

ELECTRONIC HOBBYISTS' HANDBOOK

By Rufus P. Turner. 160 pages. 114 illustrations. Paper cover. Gernsback Library Book No. 69.

\$2.50

See Your Distributor—Or Mail This Coupon Today

Gernsback Library, Inc., Dept. PF58
154 West 14th St. No. 69 Electronic Hobbyists' Handbook
New York 11, N. Y.

My remittance of \$_____ is enclosed. Please send me the books checked, postpaid.

67 63 61
 60 53 51
 44 43

Name _____ please print

Street _____

City _____ Zone _____ State _____

Other G/L Books

- No. 67—Elements of Tape Recorder Circuits—\$2.90
- No. 63—Transistor Circuits—\$2.75
- No. 61—Transistor Techniques—\$1.50
- No. 60—Rapid TV Repair—\$2.90
- No. 53—Radio Control Handbook—\$2.25
- No. 51—Transistors—Theory and Practice—\$2.00
- No. 44—Basic Radio Course—\$2.25
- No. 43—Model Control By Radio—\$1.00

the specs are the proof . . .
 the BEST BUYS are **TEICO**
 for COLOR & Monochrome TV servicing



NEW COLOR
 and Monochrome
 DC to 5 MC LAB & TV
 5" OSCILLOSCOPE

=460
 Factory-wired
 and tested \$129⁵⁰
 Also available as kit \$79⁹⁵

• Features DC Amplifiers!

Flat from DC-4.5 mc, usable to 10 mc. VERT. AMPL.: sens. 25 rms mv/in; input Z 3 meg; direct coupled & push-pull thruout; K-follower coupling bet. stages; 4-step freq-compensated attenuator up to 1000:1. SWEEP: perfectly linear 10 cps-100 kc (ext. cap. for range to 1 cps); pre-set TV V & H positions (30 & 7875 cps); auto. sync. ampl. & lim. PLUS: direct or cap. coupling; bal. or unbal. inputs; edge-lit engraved lucite graph screen; dimmer; filter; bezel fits std photo equipt. High intensity trace CRT. 0.06 usec rise time. Push-pull hor. ampl., flat to 400 kc, sens. 0.6 rms mv/in. Built-in volt. calib. Z-axis mod. Sawtooth & 60 cps outputs. Astig. control. Retrace blanking. Phasing control.



NEW TV-FM SWEEP GENERATOR & MARKER

=368
 Factory-wired
 and tested \$119⁹⁵
 Also available as kit \$69⁹⁵

Entirely electronic sweep circuit (no mechanical devices) with accurately-biased inductor for excellent linearity. Extremely flat RF output: new AGC circuit automatically adjusts osc. for max. output on each band with min. ampl. variations. Exceptional accuracy: edge-lit hairlines elim. parallax. Swept Osc. Range 3-216 mc in 5 fund. bands. Variable Marker Range 2-75 mc in 3 fund. bands; 60-225 mc on harmonic band. 4.5 mc Xtal Marker Osc., xtal supplied. Ext. Marker provision. Sweep Width 0-3 mc lowest max. deviation to 0-30 mc highest max. dev. 2-way blanking. Narrow range phasing. Attenuators: Marker Size, RF Fine, RF Coarse (4 step decade). Cables: output, 'scope horiz., 'scope vertical.



NEW DYNAMIC CONDUCTANCE Tube & Transistor Tester

=666
 Factory-wired
 and tested \$109⁹⁵
 Also available as kit \$69⁹⁵

COMPLETE with steel cover and handle.

SPEED, ease, unexcelled accuracy and thoroughness. Tests all receiving tubes (and picture tubes with adapter). Composite indication of Gm, Gp & peak emission. Simultaneous sel of any 1 of 4 combinations of 3 plate voltages, 3 screen voltages, 3 ranges of continuously variable grid voltage (with 5% accurate pot). New series-string voltages: for 600, 450, 300 ma types. Sensitive 200 ua meter. 5 ranges meter sensitivity (1% shunts & 5% pot). 10 SIX-position lever switches: free-point connection of each tube pin. 10 pushbuttons: rapid insert of any tube element in leakage test circuit & speedy sel. of individual sections of multi-section tubes in merit tests. Direct-reading of inter-element leakage in ohms. New gear-driven rollchart. Checks n-p-n & p-n-p transistors: separate meter readings of collector leakage current & Beta using internal dc power supply. CRA Adapter \$4.50

See the 50 EICO models IN STOCK at your neighborhood distributor. Write for FREE Catalog PF-5

Prices 5% higher on West Coast



33-00 Northern Blvd.
 Long Island City 1, N.Y.

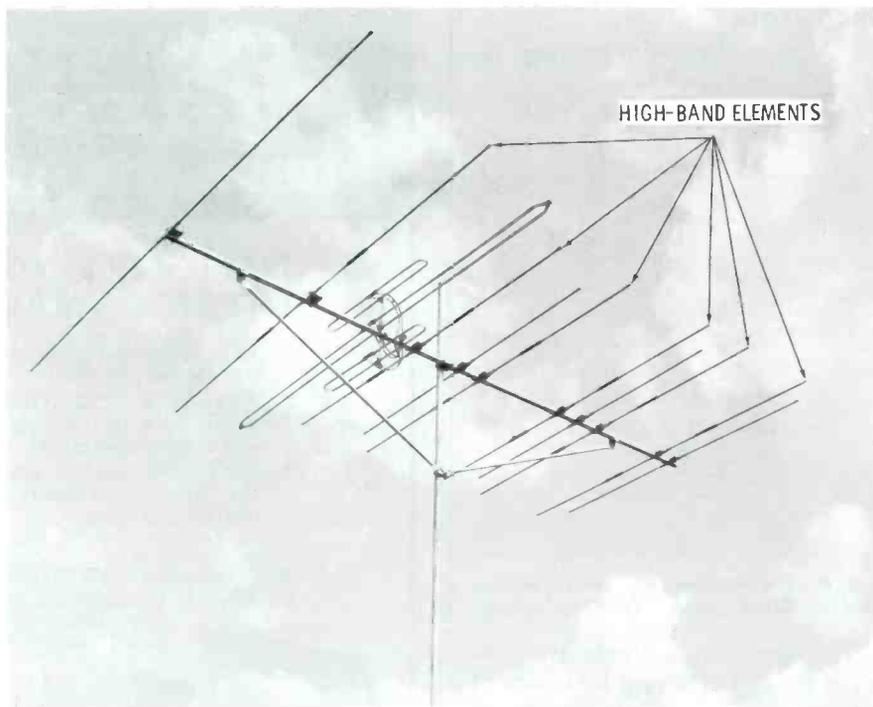


Fig. 5. High-band elements of Channel Master "Super Rainbow" have 3 sections.

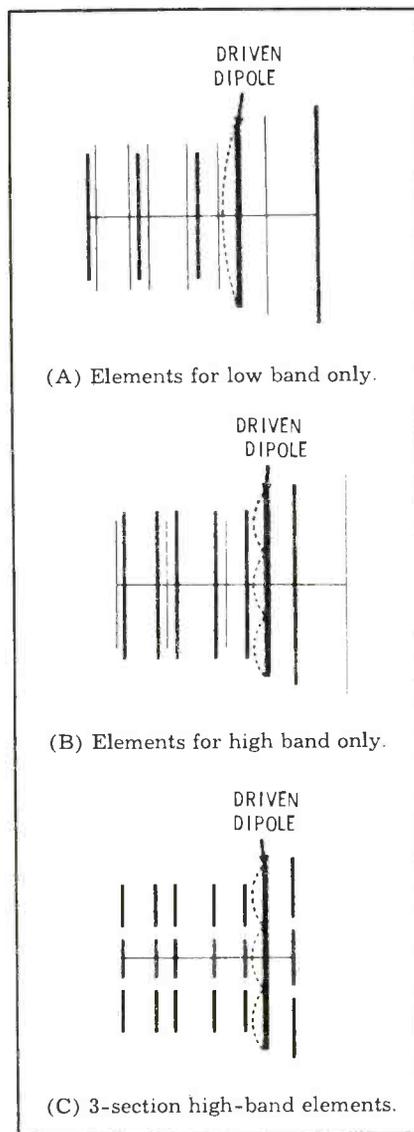


Fig. 6. Elements of the "Super Rainbow."

The dipole, which is one-half wavelength at the mid-point of the low VHF band, becomes one and one-half wavelengths in the upper VHF band. To avoid the out-of-phase condition just discussed, two additional half-wave sections are added to the antenna, one on each side of the center feed point. (Fig. 7A.) This antenna length will produce the current distribution shown in Fig. 7B. Sections I, III, and V produce currents similarly phased, while sections II and IV produce oppositely-phased currents. To eliminate the effect of the latter two sections, they are folded back on themselves as shown in Fig. 7C.

Because the folded wires, such as lengths AB and CD, are closely spaced and because the directions of their currents are opposite, their magnetic fields cancel, virtually removing the effect of the entire section from the response pattern of the antenna. The end result is a high-band pattern that is essentially a figure-8 with only minor secondary lobes. The effect of the folded sections on low-band operation is negligible.

Since the folded sections are in essence quarter-wave stubs possessing a fair amount of impedance, they tend to reduce the amount of RF current flowing from the center section to each end section and reduce the effectiveness of the array. This limi-


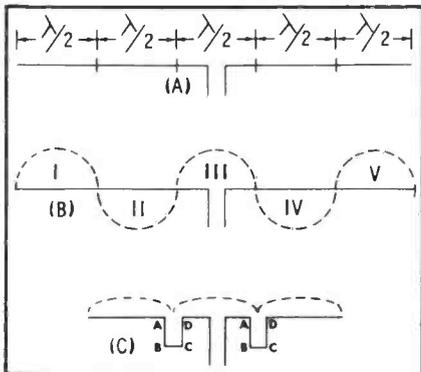



Fig. 7. Drawings which illustrate the evolution of the TACO "Trapper" array.

tation can be overcome by inserting folded dipoles in place of the stubs. (Fig. 8.) The folded dipole is designed to have a lower impedance than the stub, not only permitting more current to reach the outer sections, but also providing a broader effective bandwidth for the array. At the same time, the phase-reversing ability of the stubs is retained.

In the TACO "Trapper" array (Fig. 9), a director constructed similarly to the driven dipole is employed. The spacing between these two elements is $.34\lambda$ for channel 10 and $.12\lambda$ for channel 4. Furthermore, instead of permitting the director to serve as a parasitic element, it is connected to the driven dipole by means of metal strips; consequently, the total energy in the driven dipole

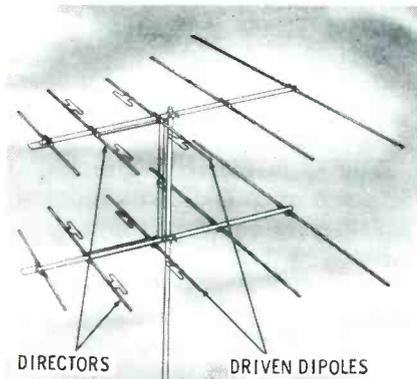

(A) Identification of elements.

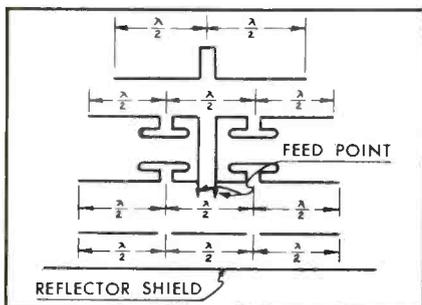

(B) Electrical dimensions on high band.

Fig. 9. The TACO "Trapper."

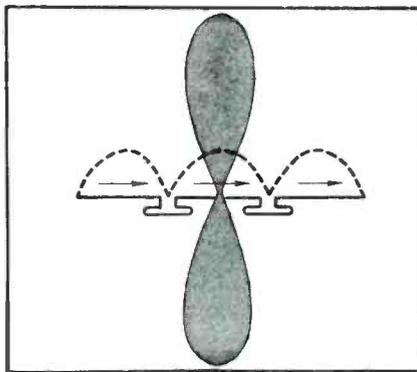


Fig. 8. Use of folded dipoles achieves better current distribution.

resulting from direct pickup of the oncoming signal and the parasitic radiations from the director are combined more closely in phase for all channels. Also, a second director, designed to act as a half-wave dipole on channel 6 (82 to 88 mc), is placed at the very front of the array. On channel 13, this rod is approximately one and one-half wavelengths long, possessing the current distribution shown in Fig. 2. To re-

(Advertisement)

latest **JACKSON** tube test data

TUBE TYPE	SECT	MODEL 648		MODEL 65		MODEL 65		CATH. SHORTS		E
		FIL.	D. C.	FIL.	D. C.	FIL.	D. C.	FIL.	D. C.	
6EA8	6.3	125	AC10	18W	6.3	5	3	4	15	3
6EB8	6.3	A125	C388*	20WY	6.3	-	34	5BS	2FS	32
12DF5	12.6	A128	679	10WY	6.3	-	20	7J0S	9LQ	32
		A124	A35	33XZ	12.6	7	8	2S	4S	17
					4	17W	6	17W	4S	17

ABOUT THE COVER

What better reason for robbing the piggy bank than to buy Mom a present—and that's exactly what this month's young trio is doing. And, even though the original idea of getting Mom a personal radio of her own was Sister's, the "baby" seems to have taken the play away from her—with the friendly cooperation of the neighborhood Radio-TV service shop. While we're on the subject, don't forget to send your Mother something extra-special for the one day in a year she can really call her own—May 11th.

COMPLETE LINE OF 110°

CRT HARNESSES and ADAPTERS
for the new RCA and SYLVANIA



- 57-15H Sylvania CRT exten. harness...List 2.50 ea.
- 57-16H RCA CRT extension harness...List 2.75 ea.
- 57-17DD Sylvania CRT replace. skt...List 1.00 ea.
- 57-18DD RCA CRT replacement skt...List 1.00 ea.
- 57-19H Sylvania adapter harness, test 110 degree chassis on standard CRT...List 2.55 ea.
- 57-20H RCA adapter harness, test 110 degree chassis on standard CRT...List 2.55 ea.

ADAPTERS




- 2000 Sylvania test point adapter. Incircuit voltage and current tests...List 3.25 ea.
- 3000 RCA test point adapter. Incircuit voltage and current tests...List 3.95 ea.
- 4000 RCA adapter. Test 110 degrees tube in your CRT tester...List 2.55 ea.
- 5000 Sylvania adapter...List 2.55 ea.

EBY SALES CO., INC.
130 Lafayette St., N. Y. 13, N. Y., WO. 2-7766

Castle Television Tuner Service

Aligned to Original Standards
Oscillator Tracking Assured by
Crystal Controlled Generators

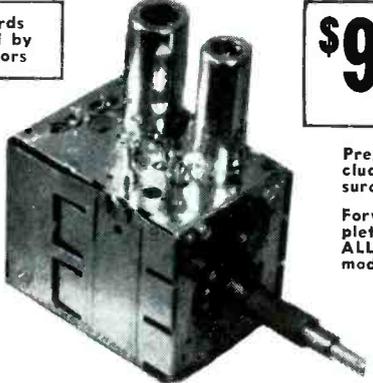IMPORTANT
Price includes WORN parts only.
F.O.B. CHICAGO or TORONTO.
DOES NOT include tubes needed; nor parts missing or damaged by abuse and negligent handling.
152 MAIN ST., TORONTO 13, ONT., CANADA
OXford 4-5637



\$9.95 Dealer Net
EACH TUNER COMBINATION
UHF/VHF \$19.90
UNITS
90 DAYS WARRANTY

Prepaid remittances must include return postage and insurance.
Forward defective tuner complete with GOOD tubes and ALL parts. Quote make and model.
1723 W. LUNT AVE., CHICAGO 26, ILL., U.S.A.
Ambassador 2-7505

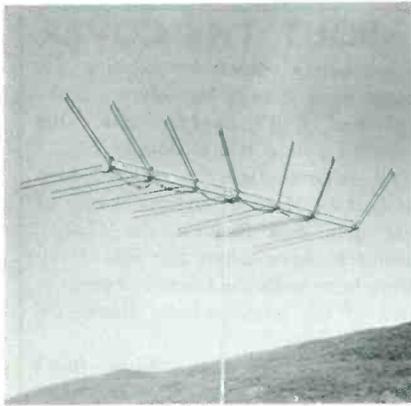


Fig. 10. The "Traveling-Wave" antenna by Channel Master has 6 driven elements.

move the central out-of-phase section, a stub is employed. Thus, on channel 6, the over-all length of this rod is one-half wavelength, while on channel 13 it is one full wavelength.

Behind the driven element there are two reflectors. The one closest to the driven dipole is designed specifically for the high band and toward that end it is divided into three half-wave sections, each separated from the other by insulator spacer rods. The other reflector, at the rear of the array, is designed to serve the low band.

When A Yagi Is Not A Yagi

The "Traveling-Wave" antenna (Fig. 10) is a development of the Channel Master Corp. and while it may, at first glance, appear to be a type of yagi array, it differs considerably from yagis in a number of important respects.

Physically, this antenna contains seven elements, six of which are driven. The seventh element is the reflector, and as such is positioned at the rear of the array. This element, incidentally, is a folded reflector. Of the six elements which are driven, i.e., connected together

NEW COUPLER
Operates 2 to 20 sets
from 1 ANTENNA

WIZARD 300*

CONDUCTIVE CAPACITANCE
Set Coupler HAS NO COILS or RESISTORS


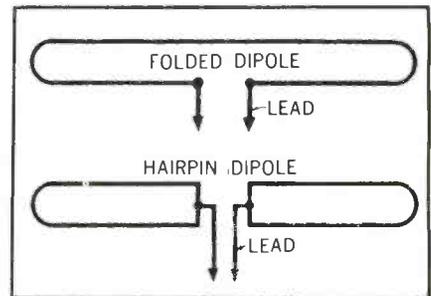
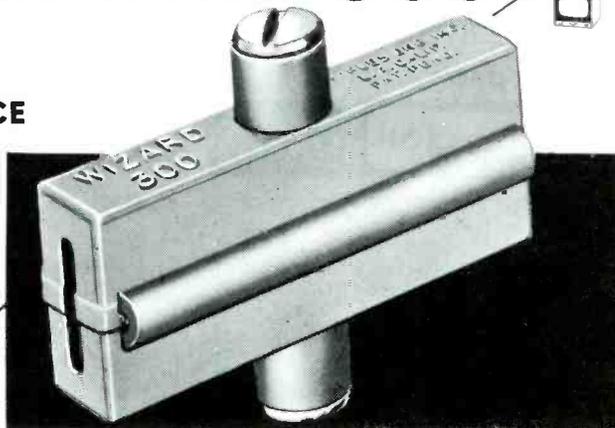
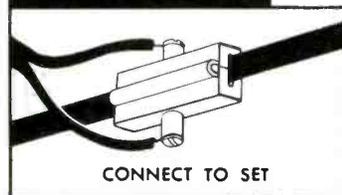
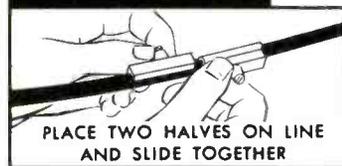


Fig. 11. Comparison of conventional folded dipole with "hairpin" or "fat" dipole.

and to the transmission line, the closest to the reflector possesses three rods in order to develop a high impedance. The others are known as "FAT" or "HAIRPIN" dipoles of the type shown in Fig. 11, a shape chosen for its ability to maintain its impedance over a wide range of frequencies. Finally, it can be seen that all of the dipoles are veered forward and that the over-all length of each dipole decreases in the progression from rear to front.

The folded dipoles are veered forward in order to minimize the breakup of the forward response pattern at the higher VHF frequencies (as discussed last month). Each of the six driven dipoles are interconnected and feed the transmission line, but if the array is examined closely, it will be noted that the length of each interconnecting line is greater than the physical spacing between the two dipoles connected to it. It was found that by properly selecting the line length, narrower response lobes and higher gain would be obtained than if the line length was equal to the dipole spacing. The principal reason for this, while quite complex mathematically, is governed by the phase relationships between the signals which

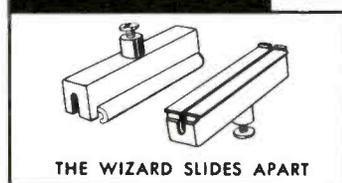

*Pat. Pend

1. FAST, SIMPLE INSTALLATION

No cutting, splicing, puncturing or soldering... no direct contact with the antenna line.

2. DESIGNED for 300 OHM FLAT LINE

Developed and proved during the past two years, Wizard Couplers are now used in thousands of residential and apartment installations to operate black and white TV, Color TV and FM.

3. PERFORMANCE FACTORS

No impedance mismatch. Insertion loss so slight that systems operating 20 or more sets from 1 antenna require no amplification in normal signal areas. Excellent isolation.

LISTS FOR \$1.95 — Write Dept. PF58 for additional information and name of your nearest representative.

CHARLES ENGINEERING, INC.
6053 MELROSE AVENUE • LOS ANGELES, CALIFORNIA

are picked up directly by the various dipoles and the signals which reach each dipole via the line. Also, there is an additional factor which has to do with the individual impedances of the driven dipoles.

It will be found that optimum performance of a multielement array of the type shown in Fig. 10 is achieved when each dipole receives an equal amount of current. It would seem that this can be achieved simply by connecting all of the dipoles in parallel, just as we connect equal resistors in par-

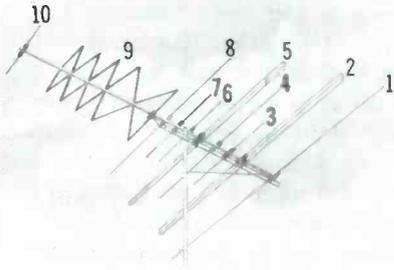


Fig. 12. Elements of JFD's "Wonder Helix" numbered for explanatory purposes.

allel. That this does not work with dipoles connected at various distances along a line stems from the fact that each dipole is separated by a significant portion of a wavelength from its nearest neighbor and, along a transmission line, the current will vary, not only in amplitude but also in phase.

To solve this problem, the "Traveling Wave" antenna is designed so that the dipole impedances decrease from the feed point to the front end. The feed point is at the input terminals of the 3-rod folded dipole closest to the reflector. This dipole possesses the highest impedance and is designed to provide one-sixth of the total signal current. As we move further toward the front end, each dipole has a progressively lower impedance, but each draws only

one-sixth of the current. As a safeguard against any back flow of current that may not be completely absorbed, a terminating resistor is inserted in the nose of the array to dissipate any current that remains.

Since much of the desirable action of this array depends on the even distribution of current in the six folded dipoles, it is imperative that their impedances decrease from feed point to front end on all received frequencies (which here means channels 2 to 13). This result is achieved by

use of progressively shorter dipole lengths. Dipoles of the "hair-pin" type were selected because they possess better impedance characteristics than either folded or straight dipoles.

A Variety of Elements

Just as a multielement filter uses a variety of components to a desired bandpass effect, a number of different half-wave elements can be combined to produce a sought-after frequency response. One such complex array is the "Wonder-Helix" antenna

HI-FI KITS FOR THE HIGHWAY!

G-C SPEAKER KITS . . . High Fidelity Sound for Every Automobile

G-C SONATA HI FIDELITY DUAL SPEAKER KITS

Breathtakingly realistic sound for rear deck installation. Includes two matched speakers—Tweeter & Woofer—with crossover network for balancing the high and low frequencies. Universal harness connector for custom-style hookup; 3-way switch; instructions; all hardware. Choice of grille colors.

List

No. 9502 (Classic Chrome) \$19.95
9503 (Springtime Gray) 19.95

GENERAL CEMENT MFG. CO.

DIVISION OF TEXTRON INC.

400 South Wyman Street • Rockford, Illinois

ALL G-C KITS PACKED IN SELF-MERCHANDISING DISPLAY BOX

ALSO A COMPLETE LINE OF G-C REAR DECK AUTO SPEAKER KITS AND ACCESSORIES FOR ANY REQUIREMENT.

G-C REAR DECK HI-FI DUO-SPEAKER KITS

Actually two speakers in one, this new G-C model gives the finest radio sound without taking extra space. Large permanent magnet. Ready to install complete, wired, switch, plate, knob and hardware.

List

No. 9506 (Chrome) \$15.95
9505 (Gray) 15.95

FREE . . . Send today for G-C Catalog and complete information.



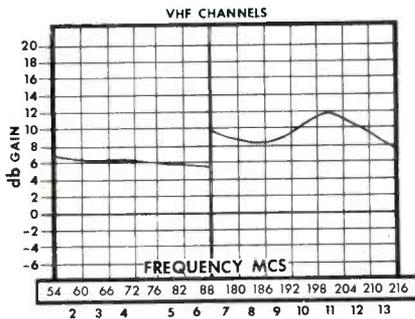


Fig. 13. Graph showing gain versus frequency for the "Wonder Helix" antenna.

developed by JFD Electronics Corp. As seen in Fig. 12, it con-

tains 10 driven or parasitic elements combined to provide the gain pattern shown in Fig. 13. Note that the gain is flat within ± 1 db on the low VHF band, and within ± 2 db over the high band.

The purpose of each element in this array is as follows: Elements 2 and 5 are cut for channels 2 and 5 respectively, and are driven in tandem. Element 1 is a channel-2 reflector. Element 8 is a channel-6 director. Element 4 has a dual function—it operates as a loading element on the shorter dipole (no.


5) and as a director for element 2. Elements 3 and 6 are phasing elements, their purpose being to prevent third harmonic lobe response on the low-band driven elements.

Element 9, known as a helix, is a high-band driven element. Its operation may best be understood by considering the circular helical antenna from which it is derived. The true or circular helix has a diameter of $1/\pi$ wavelength, at least 3 turns, and a spacing of approximately $1/4$ wavelength between turns. This antenna possesses an almost constant resistive impedance of 150 ohms between $3/4$ and $1/3$ wavelengths. The bandwidth is such that the gain is down only 1 db at 150% of center frequency, and gain at center frequency is about 8 db. By flattening the original cylinder so that the high current points are adjacent to each other, and by tapering the dimensions, an element was obtained having high inherent gain, a narrow directional pattern and a flat bandpass characteristic.

Returning to Fig. 12, element 7 is a channel-7 reflector for the helix and element 10 is a channel-13 director for the same. The signal take-off is located at the terminals of the forward folded dipole (element 5). This is made possible by transposition of the harness connecting the two low-band dipoles. The stub labelled 11 is for impedance matching. There is one further action which takes place. The first section of the helix, in conjunction with the harness, acts as a channel-2 peaking stub for elements 2 and 5. ▲

Editor's Note: Part 5, the last in this series, will round out the coverage on commercial antenna designs and how they work.

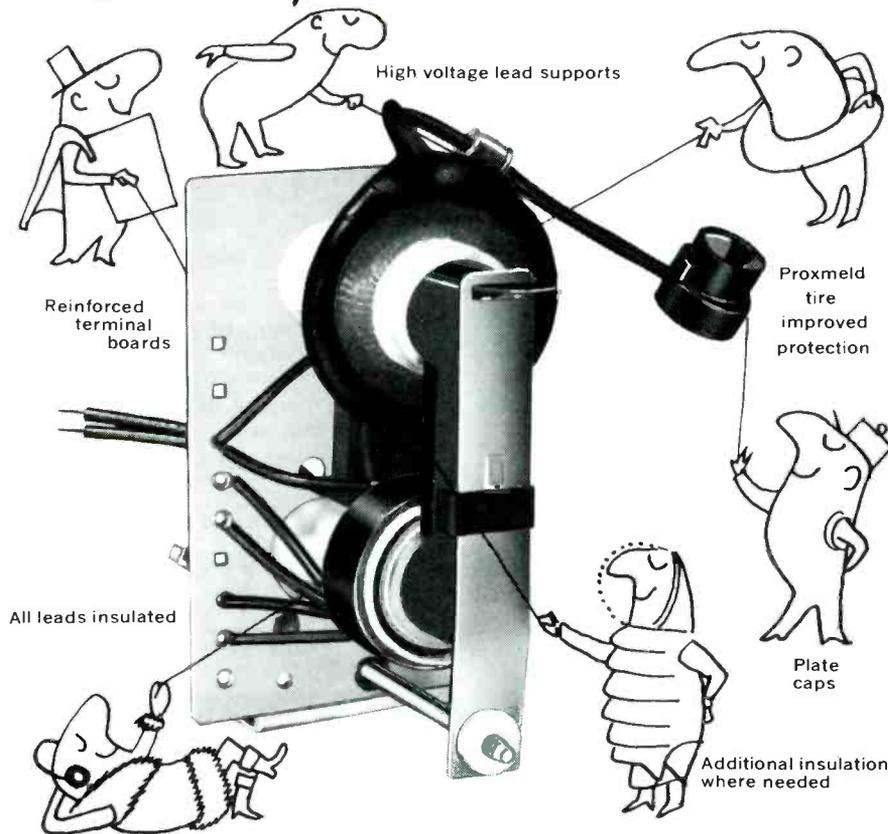You get these *plus* features with STANCOR



Stancor, the pioneer in the field of exact replacement flybacks, now goes one step further. The Stancor replacement represents an *improvement* over the original manufacturer's units. Additional features—like those above—are added when necessary to insure optimum performance. Stancor flybacks are engineered and improved replacements to help make your work more efficient and more reliable.

FREE —a new 100 page TV Replacement Guide with a brand-new format. Locates the replacement immediately—with or without the original part number. Models listed individually in numerical order. See your distributor or write us for your free copy.



CHICAGO STANDARD TRANSFORMER CORPORATION

3503 Addison Street • Chicago 18, Illinois

Export Sales: Roburn Agencies, Inc. • 431 Greenwich Street • New York 13, N. Y.



D'YA MIND IF I USE THIS?
THE BATHROOM'S OCCUPIED.

Industrial Electronics

(Continued from page 41)

of C1 through R1 will hold V1 in cutoff for a specified amount of time. V1 will then conduct and cause V2 to return to a cutoff condition (via the cathode voltage), and the output pulse will be ideally formed.

R1 is of sufficient value to drop the major portion of the B+ voltage when the grid of V1 draws a small current. All tubes used in computers and counters are especially designed to permit grid currents in the .7-ma range. One of

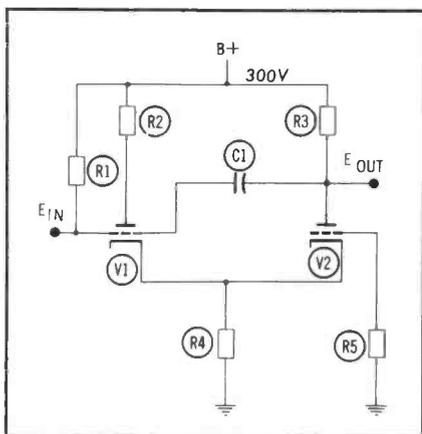


Fig. 6. Pulse shaper ahead of stages keeps pulse width and amplitude constant.

the most rugged of these tubes is the 6SN7. We know of one which has been in service for 2 years under conditions that require a grid-current surge in excess of 1 ma and still shows no abnormal fatigue. The grid in Fig. 6 draws .265 ma when there are no input pulses.

The output pulse of Fig. 6 is developed across R3, its value governing proportionately the amplitude of the output pulse. Since 50- to 100-volt pulses are usually required to drive an Eccles-Jordan, R3 must be of a value which will permit this amplitude to be developed. When pulses of greater size are applied to a counter stage, there is the possibility of coupling them right through one stage into the next. If R3 develops too small a pulse, the counter stage is likely to miss some of the counts; therefore, any change in R3 will have a serious effect on the counter stage operation.

It is a common practice to use plug-in units for many counter and computer circuits. A 4-stage counter of the plug-in design is

shown in Fig. 7. Connectors for power supply and pulse input are at the lower left. 6AL5's are used as coupling diodes and the first four 12AU7's provide a scale of 16. The last two 12AU7's are for pulse forming and amplifying. The lights are plugged into the lower right socket to provide a means for determining the number of input pulses which have been applied.

With the plug-in type of construction, service is performed by isolating the trouble to one particular unit. Then, instead of trying to locate the trouble right at

the computer, a good unit is plugged in as a replacement for the defective one. In this manner, the equipment is kept in operating condition for the maximum possible time, and the technician can repair the defective unit on the service bench where he has a greater variety of useful service aids.

In Fig. 8, both a recording instrument and a counter are shown. The counting stages are built-in rather than plug-in units, but this complete assembly plugs into a larger computer unit. Connectors



Lifetime molded handle

Order book and schematic holder

Non-distortion glass mirror for TV alignment

Built-in 7 and 9 pin straightener

Detachable hinge; cover fits any section

Adjustable web strap tilts cover at any angle

Heavy nickel-plated raised steel corner and angle protectors

4 different size sections for all tube sizes

Strong draw pull catches with locking ear for padlock or chain

3/8" steel bottom studs; self-aligning rubber feet on all other sections

Weights only 15 lbs.

"Complete line demonstrated at May Parts Show—Rm. 652"

Here is the newest idea in a tailored tote box. A master carrier convertible into any size box you require. Carry the whole box or any part of it. "Totemaster" is loaded with built-in service aids and quality features. See it at your Parts Jobber and ask for a demonstration today. "TOTEMASTER"... feature for feature the best tote box buy on the market!



MASTRA COMPANY 2104 SUPERIOR AVE. CLEVELAND 14, OHIO

PIONEER MANUFACTURERS OF THE TUBE AND TOOL TOTE BOX
CANADIAN DISTRIBUTOR: TENATRONICS LTD., NEW MARKET, ONTARIO

SENCORE
Another Sencore Time-Saver
Handy "36"
R-C Substitution Unit



"36"
Most Often Needed Components At YOUR Fingertips!

3 pole, 12 position switch individually selects one of the "36" components for direct substitution.

Contains:

- ★ 12-1 watt 10% resistors from 10 ohms to 5600 ohms
- ★ 12-1/2 watt 10% resistors from 10K ohms to 3.6 megohms
- ★ 10-600 volt capacitors from 100-mmfd. to .5mfd.
- ★ 1-10mfd., 450V Electrolytic
- ★ 1-40mfd., 450V Electrolytic
- ★ For Shop, Lab., or outside service

Completely isolated

ONLY \$1275 DEALER NET

POPULAR SENCORE PRODUCTS

- Transistor Tester
- Leakage Checker
- Filament Tester
- Voltage Regulator
- Bias Supply

AVAILABLE AT ALL PARTS DISTRIBUTORS!

SENCORE SERVICE
INSTRUMENTS CORP.
 171 OFFICIAL RD., ADDISON, ILL.

Cut out this ad now for further information.

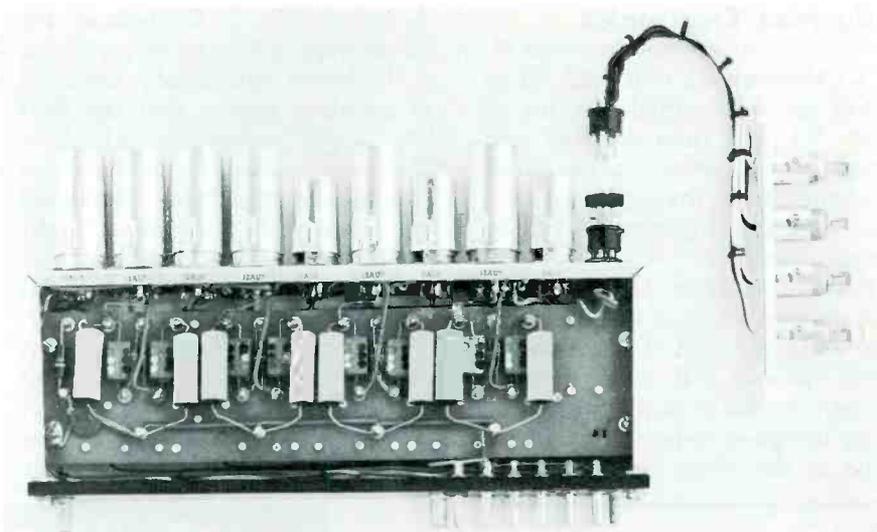


Fig. 7. Subassembly plug-in units can be substituted to make servicing easier.


for all the various functions are provided at the rear of the instrument. Six counter blocks, capable of accepting 16 input counts each, provide a total of 16,777,216 counts! The binary information from these counters is recorded on a paper tape (not shown), and tape movement is controlled by the motor and gear train which operate at a specific rate of speed. In addition to their mathematic value, permanent records obtainable with this machine aid in service and maintenance.

A computer was suspected of giving wrong answers, but the size of the computations being performed made a mathematic verification difficult. A common method of testing computers is to add the number 1 to the largest number

capable of being indicated by the computer. For instance, if a computer will indicate 9,999,999, then adding one to this number will make every stage in the computer work. This method was used on the problem, and at several points along the sequence train, the conditions of various stages were recorded on tape. The defective stage would cause all remaining counts to be low; thus, by a series of recordings, the defective counter block was easily located.

In this article, the basic circuits used in computers have been described along with several examples of actual service problems encountered in practice. Part 10 of this series will deal with other very useful modifications of the basic counter. ▲

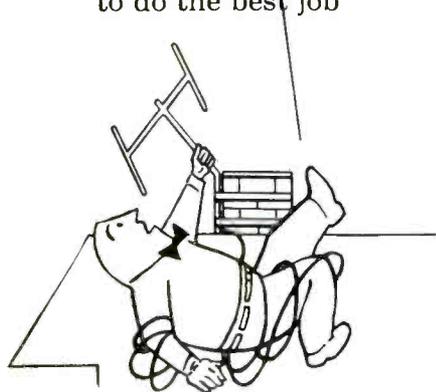installing TV antennas?
 for the right accessories
 to do the best job



you'll find it
 faster in the
MASTER

new 1958 edition—world's largest electronic catalog only \$3.50 at your local parts distributor—now Free! Write for Panel Lamp Chart.

THE RADIO-ELECTRONIC MASTER
 60 MADISON AVE., HEMPSTEAD, N. Y.

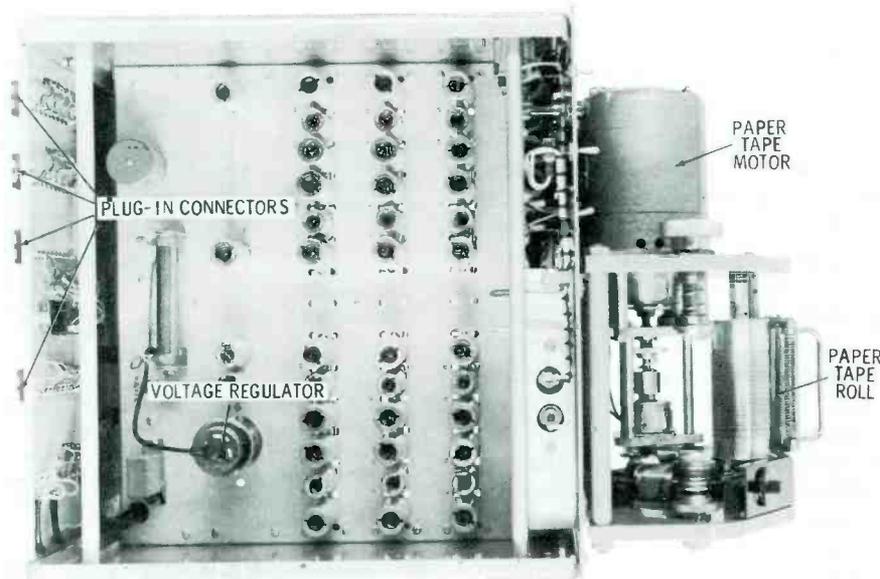


Fig. 8. A recording device which will provide both partial and complete answers can be a valuable aid in the servicing of complex computer circuits.

Record Changer Servicing

(Continued from page 21)

get on the rubber drive wheels, it can be removed with alcohol and a clean cloth. Incidentally, never lubricate a bearing that hasn't been properly cleaned, since chances are you'll overlubricate and cause future trouble.

For those parts requiring a non-liquid lubricant, it is best applied after the changer has been re-assembled. However, if it is necessary to apply the lubricant before reassembly, take care not to smear the grease where it doesn't belong or isn't needed.

So much for the general requirements of changer servicing; now, let's get right into the actual adjustments and repairs most often encountered.

Admiral Model RC 607

The Admiral RC 607 is a four-speed, intermixing type (10" and 12" records only) changer which employs a velocity-tripping mechanism. Set-down and pickup-arm height adjustments (Fig. 4) are made in the usual manner. When these are properly adjusted, the needle should drop into the lead-in groove and should be exactly $1\frac{3}{8}$ " above the set-down area before it starts its downward movement. If all sizes of records are not available for set-down tests, a ruler may be used. Measuring from the near side of the centerpost, the distance to point of set down should fall within the following limits: $3\frac{1}{4}$ " to $3\frac{5}{32}$ " for 7"; $4\frac{5}{8}$ " to $4\frac{11}{16}$ " for 10"; and $5\frac{19}{32}$ " to $5\frac{11}{16}$ " for 12".

Record dropping is accomplished by camming action at the spindle. If records fail to drop, too many drop, or if the action is erratic, check the adjustment (Fig. 5A) by hand-cycling the changer, stopping at the point where the push-off shaft is at maximum upper position. Raise the push-off adjustment nut (Fig. 5B) and check for .015" clearance as indicated. Also check the action of the ejector and slider to make sure they operate freely. A weak spring within the spindle assembly (see Fig. 5B) can also cause more than one record to drop.

Four speeds are obtained through the use of a stepped motor shaft, a belt-driven sec-

TWO MORE FIRSTS FROM THE COMPANY OF FIRSTS

THE DUOTONE PHOTO SELECTOR

- stands on counter—self service
- shows actual photos of every leading manufacturer's phonograph unit to customer
- with numbers for replacement needles right beside each photo
- reduces selling of replacements to a minimum for fastest needle identification

THE DUOTONE DEALER SALES MANUAL


- complete, clear, simple outline of needle sales information for your store personnel
- gives answers to customer's questions
- written for you by Duotone Sound Specialists after behind-the-counter and prolonged experience in actual selling in record stores

Manufacturer of the world's first commercial diamond needle

DUOTONE COMPANY, INC.

KEYPORT, NEW JERSEY

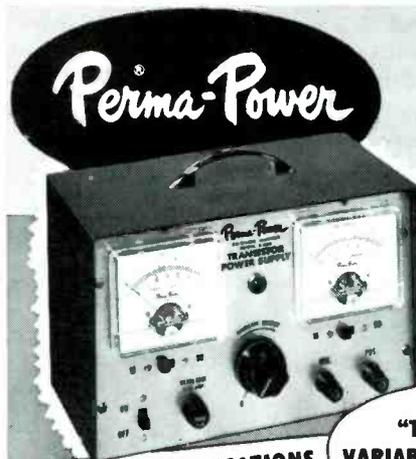In Canada, Charles W. Pointon, Ltd., Toronto



TRANSISTOR POWER SUPPLY

MODEL A-400

**Especially designed to operate, service
and test transistor portable radios
and low power transistor circuits.**

Highest quality components combined with careful engineering make this instrument extremely reliable and useful for laboratory and service applications.

\$64.50 from
Electronic Parts
Distributors only

"TRULY A
VARIABLE BATTERY"

SPECIFICATIONS

Input: 115 Volts 50/60 cycles
Output Voltage: 0-15 Volts and
0-30 Volts
Output Current: 0-15 MA and 0-60 MA
Accuracy: 2% on both voltage and current
Ripple: Less than 500 microvolts (.002%
at full output)
Regulation: 1.2 Volts Maximum; Zero to
full load current
Internal Impedance: Less than 20 ohms
DC to Radio Frequencies (including 7.0
ohm Meter Fuse, optionally removable)
Terminals: 5-Way Binding Post
Size: 10" x 6 1/2" x 5 3/4"
Weight: 16 pounds

FEATURES

- Continuously adjustable output using variable autotransformer control.
- Two output voltage ranges for accurate setting of all transistor battery voltages.
- Two output current ranges monitor current for single transistor or entire set.
- Extremely low ripple for testing lowest level transistor circuits.
- Very low internal impedance providing excellent regulation.
- Precision D'Arsonval meters provide laboratory accuracy.
- Milliammeter protected by front panel fuse; additional internal line fuse.
- Output isolated from line and case.
- Attractive Slope — Front, Maroon Hammerloid Cabinet — Rubber feet.

Perma-Power

Manufactured by
COMPANY 3100 N. ELSTON AVENUE CHICAGO 18, ILL.

There's always something new being developed by Perma-Power

MAKE YOUR STANDARD TEST PRODS


TEN TIMES

MORE EFFECTIVE IN SECONDS

WITH THE NEW

E-Z-HOOK TIP

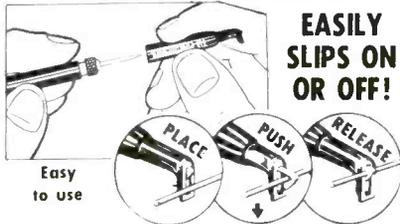CONVERTS YOUR STANDARD TEST PROD TO A SELF-HOLDING CONNECTOR



**EASILY
SLIPS ON
OR OFF!**

Here are the **TEN** added advantages you get with the E-Z-Hook Tip:

- | | |
|----------------------------------|-------------------------------------|
| 1. Frees your hands | 6. Fits irregular shaped conductors |
| 2. Won't slip off | 7. Fully insulated |
| 3. Insures positive connection | 8. Small and compact |
| 4. Makes difficult connections | 9. Hands clear of wiring |
| 5. Easy to connect or disconnect | 10. Easy to use |

No. 56-1 E-Z-HOOK Tip Only 89¢ ea.

ORDER THROUGH YOUR PARTS DISTRIBUTOR

E-Z-HOOK TEST PRODUCTS
Dept. H-1 1536 Woodburn Ave.
Covington, Ky.



**WORLD'S
FINEST
SOLDER!**

Made especially for the
RADIO AND ELECTRONIC MARKET

Guarantees your work —
FASTER! SURER! NO CALL-BACKS!

LOWEST POSSIBLE PRICES —
PROMPT DELIVERY

SOLD ONLY THROUGH
RADIO PARTS DISTRIBUTORS!



ME 948
MULTICORE SALES CORPORATION
PORT WASHINGTON, NEW YORK



Fig. 8. Tone arm and stabilizer bar adjustments of Collaro "Conquest" changer.

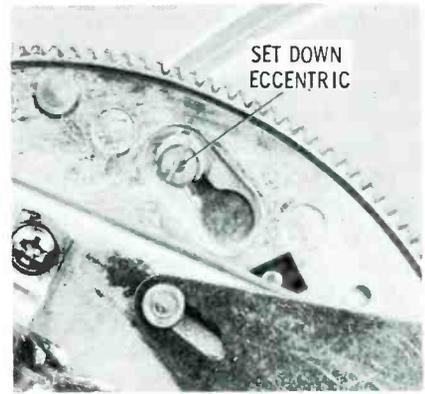


Fig. 10. Set-down eccentric can also be adjusted from beneath the changer pan.

ondary shaft (also stepped), and a single drive wheel as shown in Fig. 6. Failure of the changer to operate at 16 and 33 rpm, while working normally at 45 and 78 rpm, is due to a broken belt. Slow operation on 33- and 16-rpm positions is due to a stretched belt or oil on the belt, while slow operation at all speed settings is caused by low motor speed, a worn drive wheel or oil on the drive wheel surface. The spring indicated in Fig. 6 holds the drive wheel engaged with the turntable rim. A broken spring could also cause the changer to be inoperative on all speeds, while a weak spring could result in slow speeds.

Just as there are points in a changer that need lubrication, there are also points that do not.

On the set-down index assembly (Fig. 7) the two pivot points indicated must be clean and dry if they are to pivot freely; otherwise, erratic indexing may occur.

Shut-off occurs after the last record because the record stabilizer (Fig. 4) drops and actuates a series of arms which push the switch to the off position. If the stabilizer arm fails to drop, the last record will be repeated continuously until the switch is operated manually.

No separate tracking force adjustment is provided on this changer; therefore, any replacement cartridge must be exactly the same weight as the original if correct tracking force is to be maintained and excessive record and needle wear avoided.

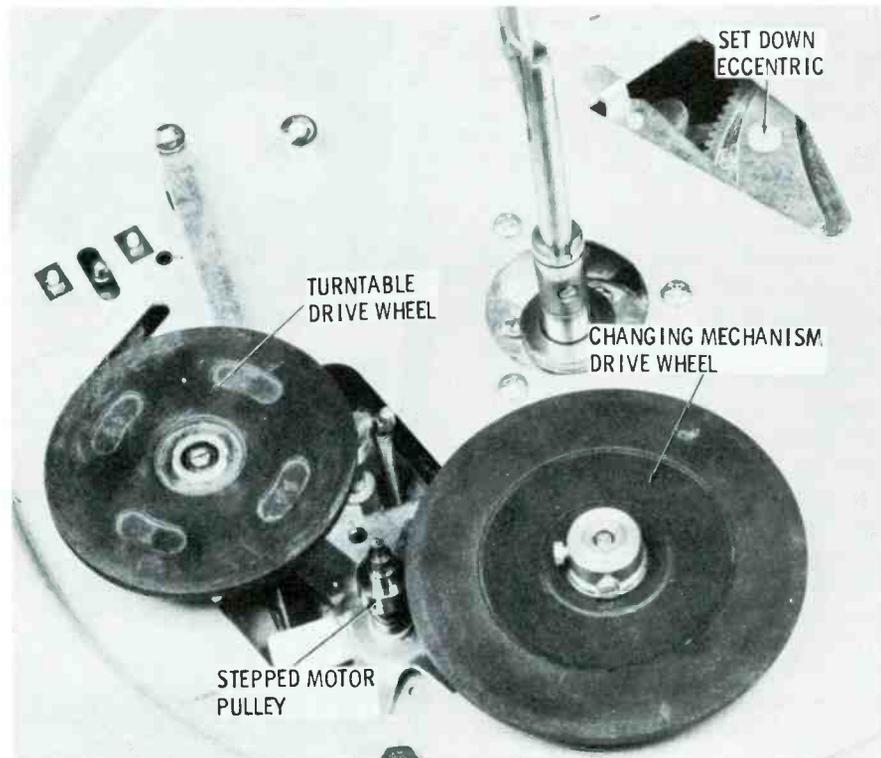


Fig. 9. Set-down eccentric is accessible when the turntable is removed (Collaro).

Video Master

TV "HIGH GAIN" TUNED R.F. DEMODULATOR PROBE

DOSS

See us at
Booth 674
May Parts Show

ADVANCED Techniques of TV Troubleshooting by ELECTRONIC RESEARCH

- ✓ ISOLATES ANY TV I.F. PROBLEM TO A STAGE. Allows signal analysis at any plate, grid, or tube shield.
- ✓ TESTS ANY TV TUNER DIRECTLY. High-gain allows signal analysis at tuner.
- ✓ EXCELLENT I.F. ALIGNMENT INSTRUMENT. Tunable characteristics provide alignment technique—no generators.



Model D-200
only \$19.95 Net

The D-200 VIDEO MASTER is a HIGH-GAIN (6CB6 I.F. Stage) Demodulator Probe arranged with two independently-calibrated and adjustable tuned I.F. bands for both 20 and 40 MC receivers. A frequency-compensated, low-impedance detector stage provides EXCELLENT FREQUENCY RESPONSE.

Collaro "Conquest"

The Collaro "Conquest" is a four-speed intermixing (7", 10" 12") changer with provisions for manual operation at any speed. Velocity tripping is employed. Tracking force and fine tone-arm height adjustments are located on top of the arm as shown in Fig. 8. (A coarse height adjustment is also provided, but is located below the changer pan, as you will see in Fig. 12.) The height adjustment must be set so that the tone arm clears records on the spindle by 1/8" at the completion of a cycle. Fig. 8 also shows a leveling adjustment for the stabilizer arm which must hold the records in a plane perpendicular to the spindle. This is a trial and error adjustment that should rarely, if ever, require adjusting.

The set-down adjustment is accessible when the turntable is removed (Fig. 9), or it may be reached from below (Fig. 10). To make this adjustment from the

underside of the changer, remove power, operate the starting switch, and turn the cam gear counterclockwise until the eccentric screw appears. Use a pencil to mark both the eccentric screw and the cam gear and adjust the eccentric to first one side of the mark and then the other until proper set down is obtained. A small dot of glue or paint can then be used to hold the eccentric firmly in place, but be sure it doesn't interfere with the normal trip cycle.

Referring back to Fig. 9, you will notice two rubber drive wheels, the smaller of which couples motor power to the turntable rim. The other wheel rides on the turntable and transmits the power to operate the changing mechanism. The stepped motor pulley provides the different speeds. Note—since this changer is designed for either 50- or 60-cycle operation, there are a variety of motor pulleys available. A different set of pulleys is used when the unit is powered with 50-cycle current, so make sure the correct pulleys are installed if there are any gross speed errors.

On the underside of the changer (Fig. 11), we find the record-dropping adjustment and a knurled limit screw. In the act of dropping a record, arm "A" moves over, causing adjustable plate "B" to actuate ejector lever "C," and this in turn moves the ejector mechanism in the spindle and causes a record to drop. Misadjustment of plate "B" or of the knurled limit screw can result in improper record dropping. The proper location for plate "B" is near the point where the two locking screws are centered in

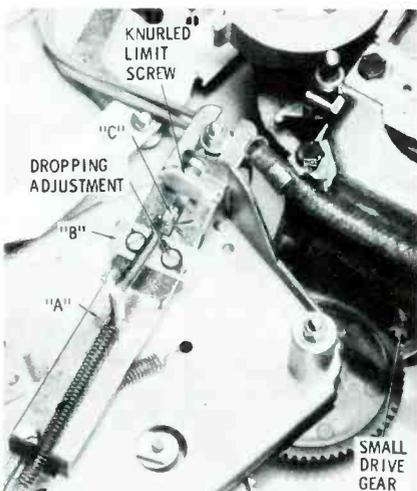


Fig. 11. Record-dropping adjustment and changer-mechanism drive gears (Collaro).

Sweep Analyzer DOSS MODEL D-100



Detects even one-turn shorts utilizing oscilloscope and NEW, extremely sensitive principle of measurement.

Checks: FLYBACKS, YOKES, VERT. BLOCKING, VERT. OUT. and others.

SENSATIONAL NEW TV
INSTRUMENT only \$16.95 Net

Slave Oscillator DOSS MODEL D-500



Quickly isolates any Sweep or Sync. failure to CONTROL STAGE, OSCILLATOR STAGE, or OUTPUT CIRCUIT. SUBSTITUTES COMPLETELY for receiver Horizontal or Vertical Sweep Oscillator. Controls include: VERTICAL HEIGHT, AND HORIZONTAL HOLD.

only \$19.95 Net

free Most distributors have extra quantities of DOSS Instruction Books. These are informative, well illustrated and complete.

ASK FOR YOURS TODAY—
ABSOLUTELY FREE! or write

DOSS ELECTRONIC RESEARCH
820 BALTIMORE
KANSAS CITY 5, MISSOURI

Please send me your free instruction books on:


- D-200 Video Master
- D-100 Sweep Analyzer
- D-500 Slave Oscillator

Name _____

Company _____

Address _____

City & State _____

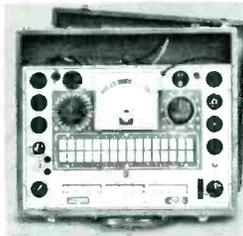

SAVE 4 WAYS

WITH A
JACKSON 648A
DYNAMIC® TUBE TESTER

SAVE ON TIME

Jackson 648A, with fingertouch sequence switching is the world's fastest fully-flexible tube tester.

SAVE ON CALL BACKS

Jackson 648A features famous Jackson Dynamic® circuit, for reliable tests on all radio, tv and most industrial tubes.

SAVE ON INVESTMENT

Jackson 648A is one of the lowest cost, fully-reliable, fully-wired testers on the market.


SAVE ON UPKEEP

Jackson 648A is fully flexible, provides for almost any new development in tube design. No cards to lose. No sea of sockets to confuse you. 23 Separate heater voltages—more than any other tester. Latest test data published monthly on page 65, PF Reporter.



Famous "Service-Engineered" Test Equipment

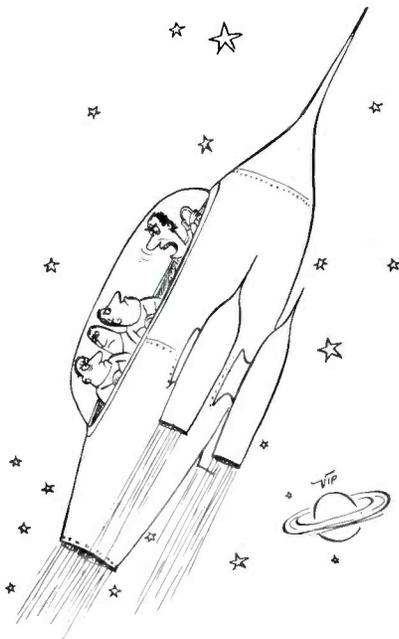JACKSON ELECTRICAL INSTRUMENT COMPANY
16-18 S. Patterson Boulevard • Dayton 2, Ohio



"O.K! O.K! We'll turn back to earth and get your JENSEN NEEDLES."

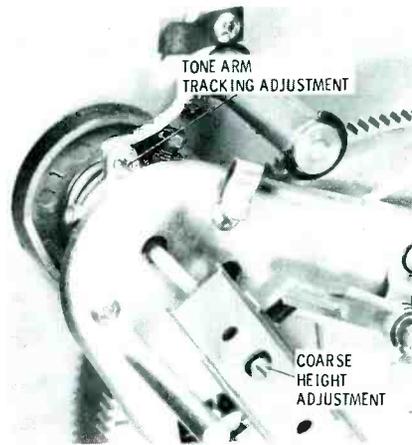


Fig. 12. Coarse height and tone-arm tracking adjustments on the Collaro unit.

their respective slots.

Two more adjustments (coarse tone-arm height and tone-arm tracking) are provided at the tone-arm end of the changer mechanism (Fig. 12). The tracking adjustment controls the position of the tone-arm cam-following pin which passes through a groove in the top of the cam. When correctly adjusted, the pin, over the center portion of its movement, clears the bottom of the cam groove. Over the 20% movement at each end of its normal arc, the pin rides along the bottom of the groove.

The signal lead from the cartridge is shown clamped to the changer base. This lead must not be pulled excessively tight as it will restrict tone-arm movement and cause improper tracking.

V-M Model 1200A

The V-M Model 1200A is a

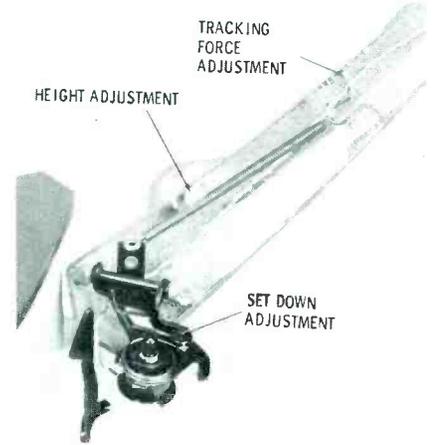


Fig. 13. Record-support arm and tone-arm adjustments on V-M 1200A changer.

four-speed, intermixing changer and features a velocity-tripping mechanism. The record-supporting arm holds the record stack until each record is dropped onto the turntable, and then drops down to actuate the mechanism which shuts the changer off after the last record is played. Set-down, tone-arm height and tracking-force adjustments, (Fig. 13) are made in the usual manner. The pickup should raise $1\frac{3}{8}$ " at the start of the change cycle, and needle pressure should be 8 to 10 grams.

The motor assembly (Fig. 14) is a separate unit mounted to the changer pan with two small screws and a hex nut under the speed selector knob. The entire motor is moved up or down to change speeds, since the four-step motor shaft is the speed selector. The rubber driving wheel mounting is stationary.

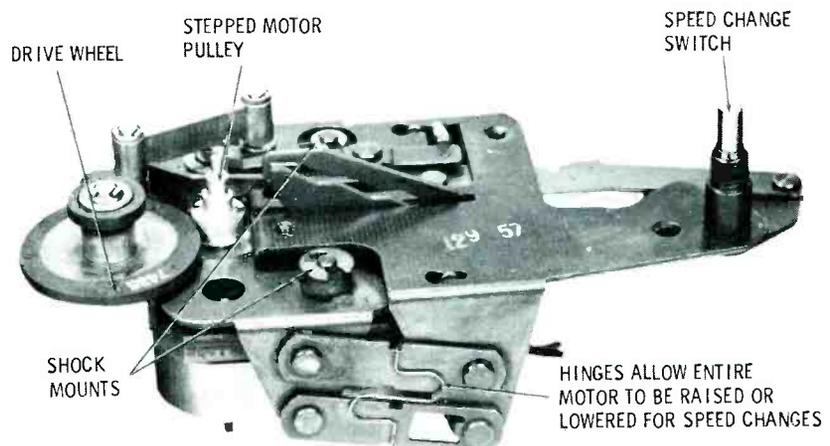


Fig. 14. Motor assembly of V-M has stepped motor pulley and rubber drive wheels.

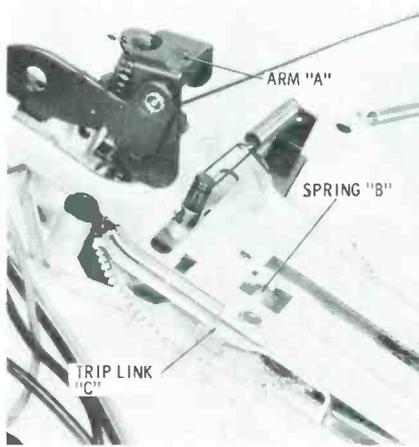


Fig. 15. Record-dropping mechanism on V-M 1200A. Bend arm "A" to adjust.

As mentioned earlier, over-lubrication is more of a problem than under-lubrication, especially around phono motors and rubber drive wheels. Remember that the brass bearing surfaces on the drive wheels and motor are oil-treated porous bronze which don't require oiling unless the bearing is cleaned. Should it become necessary to disassemble the motor unit and clean any of the bearings with solvent or crocus cloth, be sure the cleansed unit is free of all grit, and then lubricate with a single drop of oil on each bearing surface.

Fig. 15 shows that a rather simple, straight-forward mechanism is used. Unless some part becomes worn or bent, no adjustments should be required. At the beginning of each cycle, a record is dropped when arm "A" moves, causing the ejector in the spindle to move. If the ejector

doesn't move far enough, the record won't drop. Bend arm "A" as required to produce proper movement, or replace the entire assembly. Continuous tripping can occur if small spring "B" is missing. Another possibility is that trip link "C" is frozen in the reject position.

Jerky vertical motion of the tone arm can be caused by binding of the tone-arm lift pin or by burrs on the main slide and cam (Fig. 16). If the latter, remove the burrs with a fine file and re-lubricate the edges. If horizontal motion is jerky or rough, make sure the fibre washer is installed above the pickup-arm return locator.

This article would not be complete without a word or two of caution. The changers discussed herein, or comparable units of any make, make use of rather complex and somewhat delicate mechanisms; thus, mechanical know-how and physical dexterity are necessary attributes for the expert serviceman.

Stick to the simpler phases, such as adjustment, lubrication and minor replacements (drive and idler wheels), until you develop additional skill and knowledge. Most changers usually won't require more extensive work anyway. ▲

Editor's Note: The next article in this 2-part series will cover various aspects in the servicing of several other popular changers.

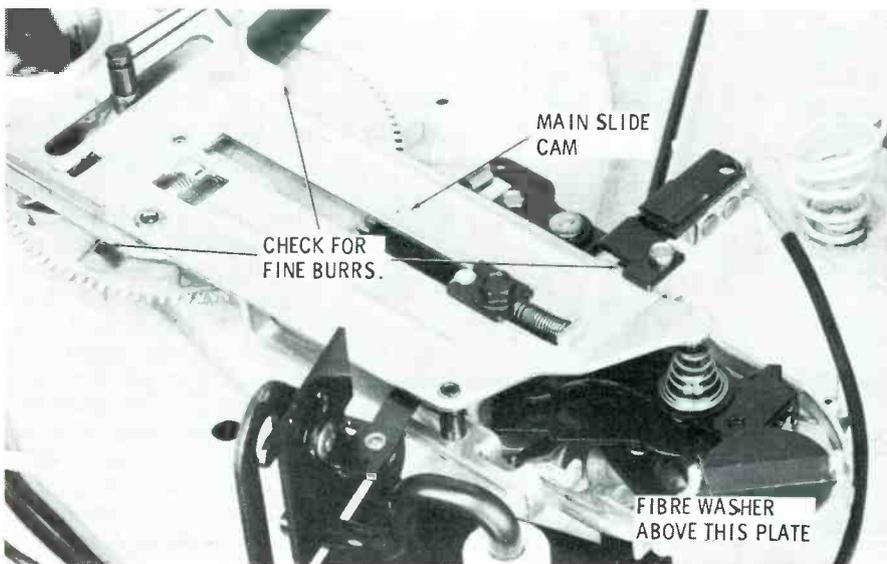


Fig. 16. Tone-arm mechanism on V-M showing pickup-arm return locator.

WILL YOUR REPLACEMENT Fuse Resistor BURN OUT AGAIN?
 Not if you use —
The NEW SENCORE "FUSE-SAFE" CIRCUIT TESTER

Another Sencore Time-Saver

Save costly call backs by testing the circuit before replacing fuse, fuse resistor or circuit breaker.

Individual scale for each value fuse resistor — no interpretation, just read in red or green area.

- ★ Measures line current and up to 1100 watts of power at 115 volts using line cord and socket.
- ★ Two convenient current ranges — 0 to 2 amps and 0 to 10 amps. Test leads clip in place of fuse or fuse resistor.
- ★ 5 ohm, 10 watt resistor prevents TV circuit damage and simulates operating conditions.

As Recommended by Leading Manufacturers

SENCORE Mfg. by **SERVICE INSTRUMENTS CORP.**
 171 OFFICIAL RD., ADDISON, ILL.

Cut out this ad now for further information

\$8.95 DEALER NET
MODEL FS-3
 AC-DC or both as needed for Fuse Resistor Circuits

YOUR BEST BUY!
 6V AUTO 12V

ADAPTER RESISTORS

USE 6-VOLT EQUIPMENT
 IN 12-VOLT AUTOMOBILES


Your jobber has them or
 can get them for you.

See us at Booth 688
 Parts Show, May 19-21

MILWAUKEE RESISTOR CO.

700 WEST VIRGINIA STREET
 MILWAUKEE 4, WISCONSIN

LEADING SET MAKERS SPECIFY TUNG-SOL

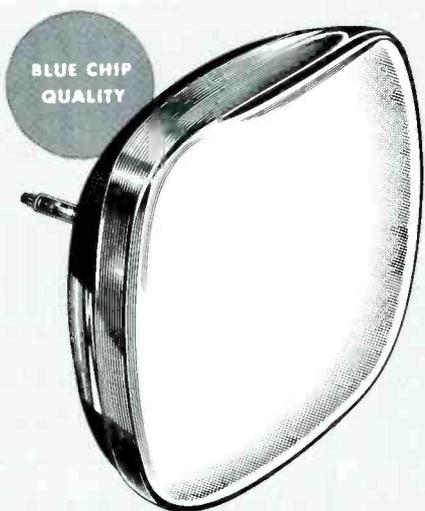


TUNG-SOL®
Magic Mirror Aluminized
PICTURE TUBES

ELECTRON TUBE DIVISION  **TUNG-SOL ELECTRIC INC.**
NEWARK 4, NEW JERSEY

PRODUCT REPORT

Unusual Phono Cartridge

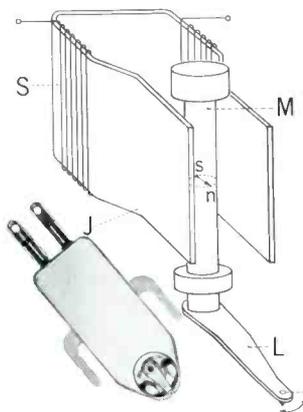

In most phono cartridges that operate on magnetic principles, the needle moves an unmagnetized object through the field of a fixed permanent magnet. The familiar electrodynamic cartridge has a moving coil from which the output signal is obtained. Another type, the variable-reluctance cartridge, contains a moving iron core that affects the field of the permanent magnet in

such a way as to induce a current in a coil wound on the magnet.

It is also possible to design a cartridge in which the permanent magnet is movable instead of stationary. Such an arrangement is employed in the Norelco "Magneto-Dynamic" cartridge just introduced by High Fidelity Products Div., North American Philips Co., Hicksville, L. I., N. Y. The magnet (M) is a rod of "Ferroxdure" ferrite material which is magnetized at right angles to the axis of the rod instead of having a north pole at one end and a south pole at the other. When the stylus (N) travels along the grooves of a record, the rod is rotated around its axis. This action introduces a varying magnetic field between the pole pieces of the nonmagnetized mu-metal core (J) of the output coil. The signal obtained from the coil is fairly high-level—on the order of 35 millivolts. The unusual construction of the unit is said to permit exceptionally linear frequency response.

Vertical tracking force of the stylus is 5 grams, and ideal load resistance is 68K ohms. Net price complete with 1-mil diamond stylus and installation hardware is \$29.

For further information, check 51R on Literature Card.

Alkaline Dry Cell




National Carbon Co., New York, N. Y., has begun production of the "Eveready Energizer," a new alkaline-type dry cell. Although the new units cost three times as much as standard-

type cells, they have many operating advantages, including an ability to withstand higher current drain, a much longer service life, and reliability of operation at extremely high or low temperatures where standard cells will not function properly. Two sizes, "D" and "½D," are now available—both with the same output voltage of 1.5 volts, but each with a different current capacity.

For further information, check 46R on Literature Card.

Ceramic Capacitors

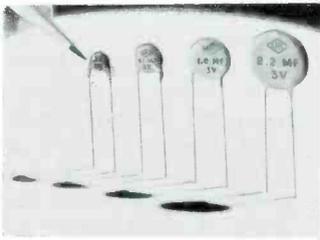


Type UK Ultra-Kaps are high-capacitance, low-voltage ceramic capacitors which are now being sold through parts distributors by Centra-lab, Milwaukee, Wis. These components, intended chiefly for use

in transistorized equipment, have previously been supplied only to original equipment manufacturers. Four standard values of .22, .47, 1.0, and 2.2 mfd, all at a rating of 3 WVDC, are now available. Dimensions range from 1/4" to 3/4".

For further information, check 43R on Literature Card.

Hi-Fi Amplifier

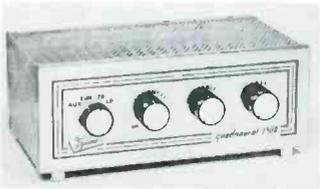


A new Model Q1500-PA hi-fi amplifier with built-in preamplifier has been introduced by Dynamic Electronics-New York, Inc., Forest Hills, L. I., N. Y., as a successor to the previous

Model Q1500. Among the features of the new amplifier are the following: 12-watt output, separate bass and treble controls, tone-compensated loudness control, record compensator with auxiliary tap, two phono input jacks plus a jack for tuner or tape recorder inputs, and separate output taps for 4, 8, or 16 ohm speakers. List price is \$59.50.

For further information, check 52R on Literature Card.

UHF Converter

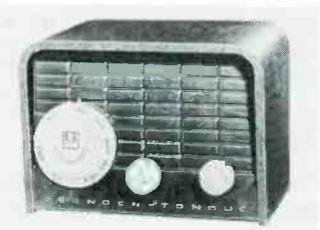

Blonder-Tongue Labs., Inc., Newark, N. J., has introduced a new Model BTU-2R "Ultraverter" all-channel UHF converter, engineered to meet the latest FCC standards with respect to oscillator radiation. Features include both

coarse and vernier channel tuning, a double-tuned input circuit, and a low-noise triode amplifier following the converter stage. Dimensions of the cabinet are 6 3/4" x 5" x 4 3/4", weight is 4 lb., and retail price is \$39.95.

For further information, check 53R on Literature Card.

FM Radio Antennas



Two types of antennas for FM radio reception have been added to the line manufactured by Winegard Co., Burlington, Iowa. Both have

a gold anodized finish. Model FM-3A, designed for strong signal areas, is a non-directional, preassembled unit complete with mast, roof mount, lead-in wire and other mounting hardware. Retail price is \$17.95. Model FM-Y8 is an 8-element yagi for long-distance reception, priced at \$22.95. Gain across the entire FM band is claimed to be 10.2 db over a tuned dipole.

For further information, check 44R on Literature Card.

LEADING INDEPENDENT SERVICE DEALERS CHOOSE TUNG-SOL

LOW IN CALLBACKS



TUNG-SOL® RECEIVING TUBES

ELECTRON TUBE DIVISION  TUNG-SOL ELECTRIC INC.
NEWARK 4, NEW JERSEY

Special Introductory Offer!

Red Cap

"At Your Service"

Screw Drivers

Here's your chance to get a beautiful 5-piece screw driver set at a true bargain price! All the most popular sizes (including No. 2 genuine Phillips) plus—a FREE tool hanger board complete with patented, adjustable hanger hooks for holding your most frequently used tools.




A \$5.50 VALUE!

Introductory Special...
Regular price \$3.69
\$2.98 net

FREE Tool Hanger Board and Patented Hanger Hooks

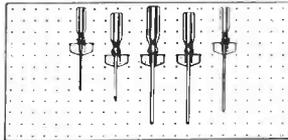
Just mail in the coupon enclosed in the RC 15 Boxed Set and VACO will send you this 12" x 24" perforated masonite panel and set of hanger hooks at no charge.



See Your Parts Jobber, Today!


VACO PRODUCTS CO., 317 E. Ontario St., Chicago 11, Ill.
In Canada: Atlas Radio Corp., Toronto 19, Ont.

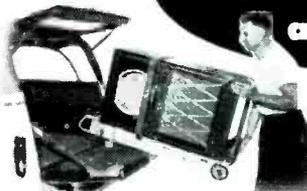The NEW YEATS "Shorty" STATION WAGON & PANEL PICK-UP appliance dolly



YEATS Model No. 5
Aluminum alloy
Height 47"
Weight 32 lbs.

Only 47" tall, this new YEATS dolly is designed for TV and appliance men who make deliveries by station wagon or panel truck. No need to detach appliance for loading into the "wagon" or pick-up... the YEATS "Shorty" will slide into your vehicle with ease. Has aluminum alloy frame with padded felt front, quick fastening (30 second) strap ratchet, and endless, rubber belt step glide. New YEATS folding platform attachment, at left, saves back-breaking work handling TV chassis or table models. Call your YEATS dealer today!

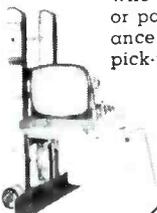

Folding platform is 13 1/2" x 24 1/2" —attaches instantly. (Platform only) \$9.95.

"Everlast" COVERS & PADS

YEATS semi-fitted covers are made of tough water repellant fabric with adjustable web straps and soft, scratchless white flannel liners. All shapes and sizes—Write.



Furniture Pad



TV Cover

SEND postcard for full information on our complete line TODAY!


YEATS

appliance dolly

2103 N. 12th St.

sales co.
Milwaukee, Wis.

110° Tube Brighteners

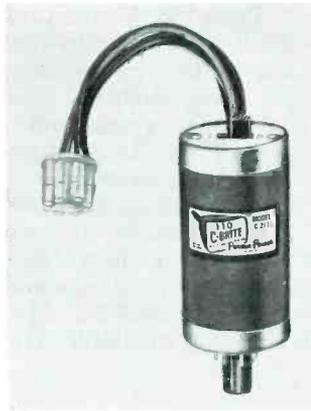


Perma-Power Co., Chicago, Ill., is all set to supply the trade with tube brighteners designed to fit the new 110° bases. Shown at left is "C-Brite" Model C-211 for use with the popular button-type (miniature-pin) bases. Also available is Model C-221, which fits the shell-type bases (with large pins) used mainly on Sylvania and Du-Mont 110° tubes. List

price of either type is \$3.75.

"C-Brites" boost heater voltage to 7.8 volts. A selector switch is provided so that the units can be used in either series or parallel heater circuits.

For further information, check 49R on Literature Card.

Low-Loss Lead-In

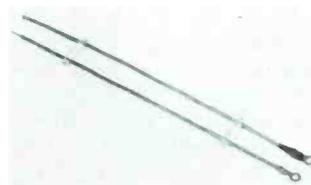

A 300-ohm television lead-in line for extremely difficult reception areas has been developed by New Products Engineering & Mfg. Co., Minneapolis, Minn. Features contributing to

low signal loss are open-wire construction, factory-sealing of terminals against moisture, and use of 14-gauge solid copper conductors with plastic insulation. "Weatherproof Signal Master" line is marketed in pre-cut lengths. "Antenna-Gard" weatherproofing compound for the antenna array is also sold as a companion product.

For further information, check 48R on Literature Card.

Tube Manual

Detailed information on over 1000 radio-TV tube types is included in the new edition of the "Receiving Tube Data Book" just published by Raytheon Mfg. Co., Newton, Mass. Data is current to within 30 days of issue and includes the latest series-string tubes. Basing diagrams appear on the same page as the tube data, making it unnecessary to refer back and forth for reference to pin connections. Copies are available from Raytheon distributors at 50¢ each.

For further information, check 47R on Literature Card.

Leakage Checker



Service Instruments Corp. (Sencore), Addison, Ill., has introduced a new Model LC3 Leakage Checker for specialized testing of tubes used in high-impedance circuits. Tests are made for heater-cathode leakage, grid emission, and related troubles, exactly as in the previous Model

LC2 checker; in addition, the LC3 has several new features including a heater continuity test, roll chart,

two extra sockets for preheating tubes, and a test cable for checking CRT's in the cabinet. Dealer net price of the LC3 is \$28.95, and the LC2 is also still available at \$24.95.

For further information, check 45R on Literature Card.

Variable Reluctance Cartridges



Recoton Corp., Long Island City, N. Y., announces two new variable-reluctance phono cartridges, the RG-500 and RG-550. Both types have the following specifications: Frequency response, flat from 20 cps to 20 kc; stylus

tracking pressure, 5 to 7 grams when used on a record changer or 3 to 4 grams on a transcription arm; output voltage, 10 millivolts; DC resistance, 1500 ohms; and recommended value of load resistance, 47K ohms. The units are available with either diamond or sapphire needles. The only difference between the RG-500 and RG-550 is that the latter has a mu-metal shield to eliminate hum.

For further information, check 50R on Literature Card.

Rugged Audio Tube



CBS-Hytron, Danvers, Mass., has developed a "ruggedized" replacement for the 12AX7 double triode tube that is widely used as a preamplifier in high-fidelity audio equipment. The new tube (type number 7025) has "folded-coil" heaters and more precise

physical tolerances for grids and mica supports, and these features keep hum and microphonism to a minimum. Electrical ratings are the same as for the 12AX7.

For further information, check 42R on Literature Card.

Auto Radio Tube Tester




A self-service checker for auto radio tubes and vibrators, intended for use as a counter merchandiser in service stations and garages, is being supplied to service technicians through parts distributors by Vis-U-All Products Co., Grand Rapids, Mich. The "Vis-U-All" Model V101 includes tests for

0Z4's and low-B+ tubes and has storage space for 66 tubes and vibrators. A substitution guide for interchangeable types is included in the set-up chart on the tester.

For further information, check 54R on Literature Card.

One
for all...

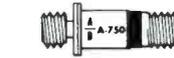


Audio's Silicon Rectifiers replace all 130 volt Selenium Rectifiers up to 750 ma in ALL repair jobs, in all radio, TV and electronic devices. See your distributor and demand the *best* reliability.

After all...

it screws and plugs in too
for various applications

WRITE FOR
YOUR COPY

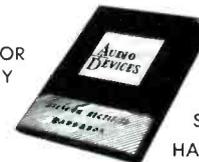

68 PAGE
SILICON RECTIFIER
HANDBOOK \$1

AUDIO DEVICES, INC.
Rectifier Division

620 E. DYER RD. • SANTA ANA • CALIFORNIA

Canadian Repr./Alex L. Clark, Ltd. • 3745 Bloor St. W., Toronto
Internatl. Repr./Rocke Internatl. Corp. • 13 E. 40th St., N.Y. 16, N.Y.

INQUIRE DEPT. PFR 5/58

May, 1958

Advertisers	Page No.
Acme Electric Corp.	36
American Television and Radio Co. (ATR)	49
Astron Corp.	8
Audio Devices, Inc.	79
B & K Mfg. Co.	5, 38
Belden Mfg. Co.	53
Blonder-Tongue Labs.	26
British Industries Corp.	72
Burgess Battery Co.	4
Bussmann Mfg. Co.	25
CBS-Hytron	35
Castle TV Tuner Service	65
Centralab, A Div. of Globe-Union, Inc.	59
Charles Engineering, Inc.	66
Chicago Standard Transformer Corp.	68
Clarostat Mfg. Co., Inc.	33
Colman Tool & Machine Co.	48
Delco Radio Div., General Motors Corp.	51
Doss Electronic Research	73
DuMont Labs., Inc., Allen B.	9
Duotone Co., Inc.	46, 71
EICO	64
E-Z-Hook Test Products	72
Eby Sales Co.	65
Electronic Publishing Co.	58
General Cement Mfg. Co.	67
General Electric Co.	6-7, 37
Gernsback Library, Inc.	63
International Resistance Co. (IRC)	2nd cover
JFD Electronics Corp.	16-17
Jackson Electrical Instrument Co.	65, 74
Jensen Industries, Inc.	74
Krylon, Inc.	24
Littelfuse, Inc.	4th cover
Mallory & Co., Inc., P. R.	30, 31
Mastra Co.	69
Merit Coil & Transformer Corp.	54
Milwaukee Resistor Co.	75
Perma Power Co.	71
Pyramid Electric Co.	57
RCA Electron Tube Division	3rd cover
Radio Receptor Co., Inc.	1
Raytheon Mfg. Co.	13, 42
Recoton Corp.	63
Sams & Co., Inc., Howard W.	29, 47, 56
Service Instruments Corp.	48, 54, 58, 62, 70, 75
Sonotone Corp.	55
South River Metal Products Co.	62
Sprague Products Co.	2
Triad Transformer Corp.	34
Triplett Electrical Instrument Co.	10-11
Tung-Sol Electric, Inc.	76, 77
United Catalog Pubs., Inc.	70
Vaco Products Co.	78
Vis-U-All Products Co.	61
Webster Electric Co.	39
Winston Electronics, Inc.	43
Workman TV, Inc.	61
Xcelite, Inc.	27
Yeats Appliance Dolly Sales Co.	78
Zenith Radio Corp.	14-15

ACCESSORIES

- 1R. **COLMAN**—Complete reference listing of all available metal-to-glass picture tube conversion kits. *See ad page 48.*
- 2R. **E-Z-HOOK**—A convenient reference sheet titled, "How to Build the Five Most Useful Scope Probes," with schematic, mechanical component layout, etc. *See ad page 72.*

ANTENNA DISTRIBUTION

- 3R. **BLONDER-TONGUE**—New catalog sheet, Form No. TS-28, describes B-23 two-set booster which boosts the signal on 1 or 2 sets and couples 2 or 3 TV sets to one antenna. *See ad page 26.*
- 4R. **CHARLES ENGR.**—Complete description of new conductive capacitance TV set coupler and how it's used for coupling 2, 5, 10, 20 or more sets to one antenna without amplification. *See ad page 66.*
- 5R. **JERROLD**—New 8-page illustrated catalog on equipment for improving home TV reception, simplifying TV distribution systems and improving TV servicing.

BOOKS

- 6R. **GERNSBACK**—Descriptive literature on Gernsback Library books. *See ad page 63.*

BUYING GUIDES

- 7R. **UCP**—Complete descriptive literature on Radio-Electronic Master, 1584-page buying guide for the industry. *See ad page 70.*

CAPACITORS

- 8R. **CORNELL-DUBILIER**—Motor start-run capacitors, Bulletin XTR-MOT.
- 9R. **SPRAGUE**—"ABC's of Ceramic Capacitors," comprehensive brochure on the theory and applications of ceramic capacitors. *See ad page 2.*

CARTRIDGES & NEEDLES

- 10R. **DUOTONE**—Specification sheets on new "Acos Hi-g" stereo and manual phono cartridges, microphones, and tone arms. *See ads pages 46, 71.*
- 11R. **RECOTON**—Simplified replacement needle guide; inventory and re-order form; gift premium catalog. *See ad page 63.*
- 12R. **SONOTONE**—Phonograph modernization manual gives data on ceramic cartridges and their installation. *See ad page 55.*

CHEMICALS

- 13R. **KRYLON**—Catalog pages describing crystal-clear rust release, dulling spray, spray enamels, varnish sprays, and metal primers. *See ad page 24.*

CONTROLS

- 14R. **IRC**—Form SO67A, new merchandising guide. *See ad 2nd cover.*

FUSES

- 15R. **BUSSMANN**—Complete TV Fuse Guide shows types and ampere ratings of fuses used in various TV sets. *See ad page 25.*

HI-FI ENCLOSURES

- 16R. **BRITISH INDUSTRIES**—High Fidelity Plan Book and River Edge Cabinet Catalog. *See ad page 72.*

PICTURE TUBES

- 17R. **DUMONT**—Picture tube data chart. *See ad page 9.*
- 18R. **RAYTHEON**—Revised 14-page Television Picture Tube Characteristics Booklet includes data on aluminized black and white and color tubes, face plate deflection angle, bulb dimension, ion trap information, and basing diagrams. *See ads pages 14, 42.*

POWER SUPPLIES

- 19R. **ACME**—Variable Voltage Adjustor Catalog VA-312. *See ad page 36.*
- 20R. **PERMA-POWER**—Complete new catalog describing and illustrating several new products in company's lines. *See ad page 71.*

RECTIFIERS

- 21R. **SARKES TARZIAN**—Completely revised Silicon Rectifier Handbook No. 67—40 pages of technical data on complete line of silicon units.

RESISTORS & CONTROLS

- 22R. **CLAROSTAT**—"C Line" composition element and wire-wound potentiometers for lab and prototype work; 2, 3, and 4 watts. Form No. 753394. *See ad page 33.*
- 23R. **MILWAUKEE RESISTOR**—Catalog of servicemen's replacement items—fuse resistors, auto resistors, "W" series resistors. *See ad page 75.*

SERVICE CASE

- 24R. **MASTRA**—Complete data on "Tote-master," a new convertible master tube and tool tote box with room for over 360 tubes plus tools and equipment. *See ad page 69.*

SALES PROMOTION

- 25R. **CBS-HYTRON**—New 4th edition, CBS Tube Business Builders Catalog PA-37, describes over 90 items especially designed for the independent service dealer. *See ad page 35.*
- 26R. **VIS-U-ALL**—Auto radio service merchandising manual. *See ad page 61.*
- 27R. **WESTINGHOUSE**—"Dress Up Your Store" folder, Form No. 7ET-0505, describes Westinghouse identification materials, signs, decals, etc.

TECHNICAL PUBLICATIONS

- 28R. **HOWARD W. SAMs**—Complete details on new free file cabinet program. *See ads pages 29, 47, 56.*
- 29R. **SYLVANIA**—Information on black and white servicing course, "New Shortcuts to TV Servicing."

TEST EQUIPMENT

- 30R. **B&K**—Bulletin AP12 gives helpful information on new point-to-point signal-injection techniques with Model 1075 TV "Analyst"; other bulletins describe B&K "Dyna-Quick" models 500B, 650, and automatic 675 portable dynamic mutual conductance tube and transistor testers plus B&K model 400 CRT cathode ray-juvenator tester. *See ads pages 5, 38.*
- 31R. **DOSS**—Details on D-100 "Sweep Analyzer," D-200 "Video Master" and D-500 "Slave Oscillator." *See ad page 73.*
- 32R. **EICO**—New 16-page, 2-color catalog describes 55 models of test instruments and hi-fi equipment in both kit and factory-wired form; shows how you can save 50%. *See ad page 64.*
- 33R. **SERVICE INSTRUMENTS**—Catalog-size folder of entire Sencore line of time savers. *See ads pages 48, 54, 58, 62, 70, 75.*
- 34R. **TRIPLETT**—Transistor tester circular. *See ad pages 10-11.*
- 35R. **WINSTON**—One-page flyer on full line of equipment. *See ad page 43.*

TOOLS

- 36R. **ANCHOR PRODUCTS**—Information sheet on SL-10 light soldering instrument, the handy "Pee Wee" iron that does a giant-size job.
- 37R. **VACO**—Catalog on special free tool hanger board. *See ad page 78.*
- 38R. **WALSCO**—Form FR 3383, an illustrated brochure on the usage of Walco "C" ring tool for removing C-ring washers.
- 39R. **YEATS**—4-page catalog describing appliance dolly and padded covers for delivering TV sets. *See ad page 78.*
- 40R. **XCELITE**—Illustrated catalog on full line plus literature on new products. *See ad page 27.*

TRANSFORMERS

- 41R. **CHICAGO STANDARD**—100-page TV Transformer Replacement Guide, cross-referenced for over 7,000 chassis of 98 manufacturers. *See ad page 68.*



SUPPLEMENT TO SAMS FEBRUARY 1958 MASTER INDEX

Covers PHOTOFAC Set Numbers 390 through 400 Released

MARCH through MAY

This Supplement is your index to new models covered by PHOTOFAC since March 1958. For model coverage prior to this date see the Sams Master Index dated February 1958. Use this Supplement with the Sams Master Index—together they are your complete Index to PHOTOFAC coverage of over 30,000 receiver models.

Set No.	Folder No.	Model
ADMIRAL		
(Also See Record Changer Listing)		
Chassis 3J1	392-5	
Chassis 3K1	398-6	
Chassis 8G1 (TV Remote Control Unit)	394-1	
Chassis 16A81, 16A81C	394-1	
Chassis 16AD1, 16AD1C, 16AE1, 16AE1C	394-1	
Chassis 16AF1	395-1	
Chassis 16AG1, 16AG1C	394-1	
Chassis 16AL1, 16AL1C	394-1	
Chassis 16B1, 16B1C	394-1	
Chassis 16D1, 16D1C, 16E1, 16E1C	394-1	
Chassis 16F1	395-1	
Chassis 16G1, 16G1C	394-1	
Chassis 16J1, 16J1C, 16K1, 16K1C, 16L1, 16L1C	394-1	
Chassis 17AC1, 17AG1	397-1	
Chassis 17C1, B	397-1	
Chassis 17F1	367-13-5	
Chassis 17G1, B	397-1	
Chassis 20AZ4EF (See Photofact Servicer)	399	
Chassis 20SZ4EF (See Photofact Servicer)	399	
B1A21F1	397-1	
B121F1	397-1	
C21E2, C21E3	394-1	
C21E6, C21E7	394-1	
C21E12, C21E13, C21E14, C21E16, C21E17	394-1	
C21E22, C21E23, C21E24	394-1	
C21F42, C21F43, C21F46, C21F48	397-1	
CA21E2, CA21E3	394-1	
CA21E12, CA21E13, CA21E14	394-1	
CA21E22, CA21E23, CA21E24	394-1	
CA21F42, CA21F43	397-1	
CR21E12, CR21E13, CR21E14	394-1	
HT2236, HT2237	398-6	
L21E22, L21E23	394-1	
LA21E22, LA21E23	394-1	
P17D21, P17D22, P17D23, P17D24	395-1	
PA17D21, PA17D22, PA17D23, PA17D24	395-1	
T18A11, T18A12, T18A13	367-13-5	
T21E1, T21E2, T21E3	394-1	
T21E21, T21E22, T21E23	394-1	
T21F32, T21F33	397-1	
TA21E1, TA21E2, TA21E3	394-1	
TA21E21, TA21E22, TA21E23	394-1	
TA21F32, TA21F33	397-1	
TR21E21, TR21E22, TR21E23	394-1	
J114, J316	392-5	
AIRLINE		
GAA-2642B, GAA-2643B	384-6	
GRX-4019A (PCB 395-4)	345-2	
GRX-4020B (PCB 396-5)	347-1	
GRX-4023A, GRX-4025A (PCB 395-4)	345-2	
GSL-4019A, GSL-4023A (PCB 395-4)	345-2	
GTM-1109A	392-6	
GTM-4200A, GTM-4300A	391-16-5	
WG-4041A	394-2	
WG-4042A	396-1	
WG-4051A	394-2	
WG-4052A	396-1	
WG-4141A	394-2	
WG-4142A, WG-4143A	396-1	
WG-4151A	394-2	
WG-4152A, WG-4153A	396-1	
WG-5040A, WG-5041A	394-2	
WG-5042A	396-1	
WG-5047A	396-1	
WG-5051A	394-2	
WG-5052A	396-1	
WG-5140A, WG-5141A	394-2	
WG-5142A, WG-5143A	396-1	
WG-5147A	396-1	
WG-5151A	394-2	
WG-5152A, WG-5153A	396-1	
AMC (AIMCEE)		
A17P11 (Similar to Chassis)	379-3	
AMERICAN MOTORS		
(See Auto Radio Listing)		

Set No.	Folder No.	Model
ARTONE		
14TS78T, 14TS78TA	400-1	
17T161MA	399-1	
21CT64MA	399-1	
21TT61MA	399-1	
ARVIN		
956T1 (Ch. 1.42400)	391-5	
5578 (Ch. 1.43500)	393-6	
8565 (Ch. 1.41200)	300-2	
8571, 8572, 8573 (Ch. 1.41100, 1.41300)	394-7	
8576 (Ch. 1.41400)	395-5	
Ch. 1.41100	394-7	
Ch. 1.41200	300-2	
Ch. 1.41300	394-7	
Ch. 1.41400	395-5	
Ch. 1.42400	391-5	
Ch. 1.43500	393-6	
CROSLLEY		
F-24PDB, PDBU, PDMH, PDMU (TV Ch. 414, 414-1 and Radio Ch. 362-3) (See Photofact Servicer)	390	
F-25BE, BK, GN, MN (Ch. 25F) (See Photofact Servicer)	397	
G-200BD, EY, MY, WT (Ch. 200GA, GT) (See Photofact Servicer)	391	
H-21LPKBF, H-21LPKBU (Ch. 468, 469) (See Photofact Servicer)	391	
H-21LPKMF, H-21PKMU (Ch. 468, 469) (See Photofact Servicer)	391	
Ch. 25F (See Photofact Servicer)	397	
Ch. 200GA, 200GT (See Photofact Servicer)	392	
AYRES		
(L. S. Ayres & Co. Dept. Stores)		
SV721 (Similar to Chassis)	375-3	
SV725R (Similar to Chassis)	375-3	
BECKER		
(See Auto Radio Listing)		
BELL SOUND SYSTEMS		
2315	397-6	
2325	395-6	
5615	399-5	
BLAUPUNKT		
(See Auto Radio Listing)		
BUICK		
(See Auto Radio Listing)		
CADILLAC		
(See Auto Radio Listing)		
CHALLENGER		
CHA20, Y	394-9	
CHA33, Y	391-6	
CHA75	395-7	
CHEVROLET		
(See Auto Radio Listing)		
COLUMBIA RECORDS		
513	287-4	
CORONADO		
PH7-4095A	395-8	
RA48-8158A	394-10	
RA48-8159A	400-6	
TV3-9402A	385-13-5	
TV3-9450A	396-2	
TV3-9455A, TV3-9456A	396-2	
TV3-9460A, TV3-9461A	396-2	
TV2-9465A, TV2-9466A	384-17-5	
TV2-9470A, TV2-9471A	384-17-5	
TV2-9475A, TV2-9476A	384-17-5	
TV2-9480, TV2-9481A	384-17-5	
TV2-9485A, TV2-9486A	380-12-5	
TV3-9402A	398-1	
CRESCENT		
A-640A, B	391-7	

Set No.	Folder No.	Model
EMERSON-Cont.		
1034D (Ch. 120220D) (PCB 291-1)	275-7	
1036D (Ch. 120206D) (PCB 249-1, 269-1)	235-5	
1037D (Ch. 120208D) (PCB 249-1, 269-1)	235-5	
1037H (Ch. 120238D)	304-7	
1038F (Ch. 120225D) (PCB 249-1, 269-1)	235-5	
1041J (Ch. 120238H)	304-7	
1042F (Ch. 120206D) (PCB 249-1, 269-1)	235-5	
1044H, 1046F, 1048F (Ch. 120225D) (PCB 249-1, 269-1)	235-5	
1054F (Ch. 120225D) (PCB 249-1, 269-1)	235-5	
1060H, 1062J (Ch. 120245D) (PCB 318-1)	299-4	
EMERSON-Cont.		
1064F (Ch. 120239F) (PCB 291-1)	275-7	
1066F, 1070F, 1072F (Ch. 120223D) (PCB 249-1, 269-1)	235-5	
1073F (Ch. 120237D)	304-7	
1074H (Ch. 120225D) (PCB 249-1, 269-1)	235-5	
1084F (Ch. 120225F) (PCB 249-1, 269-1)	235-5	
1084H (Ch. 120235D)	304-7	
1086F, 1088F (Ch. 120225D) (PCB 249-1, 269-1)	235-5	
1090F, H, 1092F (Ch. 120225D, F) (PCB 249-1, 269-1)	235-5	
1094D (Ch. 120253) (PCB 291-1)	275-7	
1096A (Ch. 120257D) (PCB 308-1, 319-1)	296-6	
1096D (Ch. 120247D)	304-7	
1097A (Ch. 120258D) (PCB 308-1, 319-1)	296-6	
1110F, 1112F, 1116F, 1120F (Ch. 120257P) (PCB 308-1, 319-1)	296-6	
1122 (Ch. 120286P) (PCB 319-1)	296-6	
1139 (Ch. 120285T) (PCB 319-1)	296-6	
1148H (Ch. 120259H)	304-7	
1160 (Ch. 120286P) (PCB 319-1)	296-6	
1236 (Ch. 120245Z) (PCB 322-1)	299-4	
1237 (Ch. 120289R) (PCB 322-1)	299-4	
1240 (Ch. 120331H)	354-7	
1270 (Ch. 120331H)	354-7	
1276, 1277 (Ch. 120382H, HC, 120383M, MC)	389-16-5	
1282 (Ch. 120380H)	386-15-5	
1283 (Ch. 120381M)	386-15-5	
1284 (Ch. 120380H)	386-15-5	
1285 (Ch. 120381M)	386-15-5	
1286 (Ch. 120388H)	386-15-5	
1287 (Ch. 120389M)	386-15-5	
1288, 1289 (Ch. 120390H, HC, 120391M, MC)	389-16-5	
1290, 1291 (Ch. 120386H, HC, 120387M, MC)	389-16-5	

Set No.	Folder No.	Model
EMERSON-Cont.		
1404 (Ch. 120400S)	400-2	
1405 (Ch. 120401U)	400-2	
1418 (Ch. 120403S)	400-2	
1419 (Ch. 120404U)	400-2	
1420 (Ch. 120377C)	400-2	
1421 (Ch. 120370G)	400-2	
1424 (Ch. 120377C)	400-2	
1425 (Ch. 120370G)	400-2	
1426 (Ch. 120369C)	400-2	
1428 (Ch. 120369C)	400-2	
2007E (Ch. 120225D) (PCB 249-1, 269-1)	235-5	
Ch. 120206D, 120208D (PCB 249-1, 269-1)	235-5	
Ch. 120210D (PCB 291-1)	275-7	
Ch. 120220D (PCB 291-1)	275-7	
Ch. 120223D, 120225D, F (PCB 249-1, 269-1)	235-5	
Ch. 120331H	354-7	
Ch. 120233F, 120235D, 120236D, 120237D, 120238D, H	304-7	
Ch. 120239F (PCB 291-1)	275-7	
Ch. 120245D (PCB 318-1)	299-4	
Ch. 120247D	304-7	
Ch. 120253 (PCB 291-1)	275-7	
Ch. 120257D, 120258D (PCB 308-1, 319-1)	296-6	
Ch. 120259H (PCB 318-1)	299-4	
Ch. 120285T, 120286P (PCB 319-1)	296-6	
Ch. 120289R (PCB 322-1)	299-4	
Ch. 120369C, 120370G	400-2	
Ch. 120377C (PCB 318-1)	299-4	
Ch. 120380H, 120381M, 386-15-5		
Ch. 120382H, HC, 120383M, MC, 389-16-5		
Ch. 120386H, HC, 120387M, MC, 389-16-5		
Ch. 120388H, 120389M, 386-15-5		
Ch. 120390H, HC, 120391M, MC, 389-16-5		
Ch. 120397B	400-2	
Ch. 120400S, 120401U, 120403S, 120404U	400-2	
FIRESTONE		
4-A-167 (Code 382-7-41900)	394-11	
4-A-174	393-8	
FISHER		
PR-6	398-8	
TR-1	391-9	
500	400-7	
FORD		
(See Auto Radio Listing)		
GENERAL ELECTRIC		
14P1208 ("Q3" Line)	397-19-5	
14P1215, 14P1216 ("Q3" Line)	397-19-5	
17P1326, 17P1327 ("M3" Line)	383-3	
17P1332, 17P1334, 17P1335 ("M3" Line)	383-3	
21C1545, -UHF, 21C1547, -UHF, 21C1548, -UHF, 21C1549, -UHF, 21C1550, -UHF, 21C1551, -UHF, 21C1552, -UHF, 21C1553, -UHF, 21C1554, -UHF, 21C1555, -UHF, 21C1556, -UHF, 21C1560, -UHF, 21C1562, -UHF, 21C1564, -UHF ("U2" Line)	391-1	
21T1539, -UHF, 21T1540, -UHF, 21T1541, -UHF, 21T1542, -UHF, 21T1543, -UHF, 21T1544, -UHF ("U2" Line)	391-1	
24C1660, -UHF, 24C1661, -UHF ("U2" Line)	391-1	
24C1670, -UHF, 24C1671, -UHF ("U2" Line)	391-1	
HOFFMAN		
B1227, U (Ch. 327, U)	398-2	
B1231, U (Ch. 332, U)	393-1	
B1241, U (Ch. 332, U)	393-1	
B1251, U (Ch. 332U, 333)	393-1	
B1261, U (Ch. 334, U)	400-3	
B3081 (Ch. 419)	321-15-5	
B3311, U (Ch. 332, U)	393-1	
B3321, U (Ch. 332U, 333)	393-1	
B3331, U (Ch. 334, U)	400-3	
B3341, U (Ch. 334, U)	400-3	
B3351, U (Ch. 422, U)	393-1	
B3364, U (Ch. 332, U)	393-1	
B3374, U (Ch. 334, U)	400-3	
K1231, U (Ch. 332, U)	393-1	
K1241, U (Ch. 332, U)	393-1	
K3341, U (Ch. 334, U)	400-3	

NOTE: PCB Denotes Production Change Bulletin. • Denotes Television Receiver. S Denotes Schematic Coverage Only.

Set No.	Folder No.	Part No.
HOFFMAN—Cont.		
●M1227, U (Ch. 327, U)	398-2	
●M1231, U (Ch. 332, U)	393-1	
●M1241, U (Ch. 332, U)	393-1	
●M1251, U (Ch. 332U, 333)	393-1	
●M1261, U (Ch. 334, U)	400-3	
●M3081 (Ch. 419)	321-15-5	
●M3311, U (Ch. 332, U)	393-1	
●M3321, U (Ch. 332U, 333)	393-1	
●M3331, U (Ch. 334, U)	400-3	
●M3341, U (Ch. 334, U)	400-3	
●M3351, U (Ch. 422, U)	393-1	
●M3364, U (Ch. 332, U)	393-1	
●P1227, U (Ch. 327, U)	398-2	
●P1231, U (Ch. 332, U)	393-1	
●P1251, U (Ch. 332U, 333)	393-1	
●P1261, U (Ch. 334, U)	400-3	
●P3081 (Ch. 419)	321-15-5	
●P3311, U (Ch. 332, U)	393-1	
●P3321, U (Ch. 332U, 333)	393-1	
●P3364, U (Ch. 332, U)	400-3	
●P3374, U (Ch. 334, U)	400-3	
●SP3331, U (Ch. 334, U)	400-3	
●SP3341, U (Ch. 334, U)	400-3	
●SP3351, U (Ch. 422, U)	393-1	
●W1227, U (Ch. 327, U)	398-2	
●W1251, U (Ch. 332U, 333)	393-1	
●W3081 (Ch. 419)	321-15-5	
●W3311, U (Ch. 332, U)	393-1	
●W3321, U (Ch. 332U, 333)	393-1	
●X3341, U (Ch. 334, U)	400-3	
Ch. 327, U	398-2	
Ch. 332, U	393-1	
Ch. 334, U	400-3	
Ch. 419	321-15-5	
Ch. 422, U (PCB 398-5)	378-3	
HOTPOINT		
●175305, 175306 ("M3" Line)	390-1	
●215400 ("M3" Line)	390-1	
●215405 ("M3" Line)	390-1	
●215505, 215506 ("M3" Line)	390-1	
LAFAYETTE		
LA-69	397-8	
LINCOLN		
(See Auto Radio Listing)		
MADISON FIELDING		
A15	395-9	
FM-15	393-9	
MAGNAVOX		
●24 Series	392-1	
●25 Series	383-14-5	
●26 Series	391-16-5	
Chassis AMP-1488B, CB	340-10	
Chassis AMP-1518B, CB	343-6	
Chassis AMP-1644A, BA	395-10	
Chassis AMP-1664A, BA	399-8	
●Chassis U24-01AA, U24-02AA, U24-03AA, U24-04AA, U24-06AA	392-1	
●Chassis U25-01AA, U25-02AA, U25-03AA, U25-04AA, U25-05AA, U25-06AA, U25-07AA, U25-08AA, U25-09AA, U25-10AA, U25-11AA	383-14-5	
●Chassis U26-01AA, U26-02AA, U26-03AA, U26-04AA, U26-06AA	391-16-5	
●Chassis V24-01AA, V24-02AA, V24-03AA, V24-04AA, V24-06AA	392-1	
●Chassis V25-01AA, V25-02AA, V25-03AA, V25-04AA, V25-05AA, V25-06AA, V25-07AA, V25-08AA, V25-09AA, V25-10AA, V25-11AA	383-14-5	
●Chassis V26-01AA, V26-02AA, V26-03AA, V26-04AA	391-16-5	
MERCURY		
(See Auto Radio Listing)		
METEOR		
●7144 (Ch. 528.50060, 62, 63, 64, 65, 66, 67)	389-3	
●7145 (Ch. 528.50070, 71, 73, 74, 75)	389-3	
●7146 (Ch. 528.50060, 62, 63, 64, 65, 66, 67)	389-3	
●7147 (Ch. 528.50070, 71, 73, 74, 75)	389-3	
●7180 (Ch. 528.50060, 62, 63, 64, 65, 66, 67)	389-3	
●7181 (Ch. 528.50070, 71, 73, 74, 75)	389-3	
Ch. 528.50060, 528.50062, 528.50063, 528.50064, 528.50065, 528.50066, 528.50067, 528.50070, 528.50071, 528.50073, 528.50074, 528.50075	389-3	
MOPAR		
(See Auto Radio Listing)		
MOTOROLA		
TR-89R, T (Remote Control Unit)	393-2	
●Y14P3-1, -2, Y14P4-1, Y14P6-1, Y14P7-1, -2, Y14P8-1, -2 (Ch. TS, TTS, VTS, WTS-423Y)	366-7	
●Y21C6BG, MG (Ch. TS-537Y)	345-9	
●Y21F8B, BA, W, WA (Ch. TS-544Y)	393-2	

Set No.	Folder No.	Part No.
MOTOROLA—Cont.		
●Y21K53B, BA, M, MA, Y21K55B, BA, M, MA (Ch. TS-537Y, TTS-537Y)	345-9	
●Y21K64B, M, Y21K65B, M, Y21K66B, M, Y21K68B, M (Ch. QTS-537Y, TS-537Y, WTS-537Y)	345-9	
●Y21K73B, BA, M, MA, Y21K75B, BA, CW, CWA, M, MA, Y21K77B, BA, CW, CWA, M, MA, Y21K78B, M, Y21K80B, CW, CWA (Ch. TS-544Y)	393-2	
●Y21K81B, M (Ch. WTS-544Y)	393-2	
●Y21T32B, BA, CH, CHA, MGA, Y21T34B, BA, M, MA (Ch. TS-537Y, TTS-537Y)	345-9	
●Y21T40BG, BGA, MG, MGA, Y21T42B, BA, M, MA (Ch. TS-544Y)	393-2	
●Y21T47MO (Ch. MTS-537Y)	345-9	
●Y21V1W, WA (Ch. TS-544Y)	393-2	
●Y24C1B, M (PTS-537Y)	345-9	
●Y24K13B, M, Y24K18B, M (Ch. PTS-537Y, WTS-537Y)	345-9	
●Y24T5BG, MG (Ch. WTS-537Y)	345-9	
●14P3-1, -2, 14P4-1, 14P5-1, -2, -3, 14P6-1, 14P6A-1, 14P7-1, -2, 14P8-1, -2 (Ch. TS, TTS, VTS, WTS-423, A, Y) (PCB 399-4)	366-7	
●21C6BG, MG (Ch. TS-537)	345-9	
●21F8B, BA, W, WA (Ch. TS-544)	393-2	
●21K53B, BA, M, MA, 21K55B, BA, M, MA (Ch. TS-537, TTS-537)	345-9	
●21K64B, M, 21K65B, M, 21K66B, M, 21K68B, M (Ch. QTS-537, TS-537, WTS-537)	345-9	
●21K73B, BA, M, MA, 21K75B, CW, M, 21K77B, M, 21K78B, M, 21K80B, CW, CWA (Ch. TS-544)	393-2	
●21K81B, M (Ch. WTS-544)	393-2	
●21T32B, BA, CH, CHA, MGA, Y21T34B, BA, M, MA (Ch. TS-537, TTS-537)	345-9	
●21T40BG, MG, 21T42B, M (Ch. TS-544)	393-2	
●21T47MO (Ch. MTS-537)	345-9	
●21V1W, WA (Ch. TS-544)	393-2	
●24C1B, M (Ch. PTS-537)	345-9	
●24K13B, M, 24K18B, M (Ch. PTS-537, WTS-537)	345-9	
●24T5BG, MG (Ch. WTS-537)	345-9	
54L1A, 54L2A, 54L3A, 54L4A, 54L5A, 54L6A (Ch. HS-468)	266-9	
Ch. HS-468	266-9	
Ch. MTS-537, Y, PTS-537, Y, QTS-537, Y (PCB 397-4)	345-9	
Ch. TS-423, A, Y (PCB 399-4)	366-7	
Ch. TS-537, Y (PCB 397-4)	345-9	
Ch. TS-544, Y (PCB 399-4)	366-7	
Ch. TTS-423, Y (PCB 399-4)	366-7	
Ch. VTS-423, Y (PCB 397-4)	345-9	
Ch. WTS-423, Y (PCB 399-4)	366-7	
Ch. WTS-537, Y (PCB 397-4)	345-9	
Ch. WTS-544, Y (PCB 399-4)	366-7	
MUNTZ		
●724 Series	352-12	
●727 Series	352-12	
NEWCOMB		
E-50	394-12	
H-25	390-7	
H-50	391-10	
KX-25	393-10	
OLDSMOBILE		
(See Auto Radio Listing)		
OLYMPIC		
"Domino" 5806 T/W	398-9	
"Kobald" 5720W	390-8	
"Meteor" 5781W	392-9	
"Meridian" 5783W	392-9	
●CD108, U, CD109, U, CD110P, PU (Ch. GD, GDU)	397-2	
●KH402, U (Ch. GH, GHU)	397-2	
●KD118, U, KD119, U, KD120, U (Ch. GD, GDU)	397-2	
●KH406, U, KH407, U (Ch. GH, GHU)	397-2	
●TD102, U (Ch. GD, GDU)	397-2	
●11Y951 (Ch. DY)	391-2	
●11Y951, U, 14T192, U (Ch. GT, GTU)	395-2	
●14TU93, U, 14TU94, B, BU, M, MU, U (Ch. GU, GUU)	395-2	
Ch. DY	391-2	
Ch. GD, GDU	397-2	
Ch. GH, GHU	397-2	
Ch. GT, GTU	395-2	
Ch. GU, GUU	395-2	

Set No.	Folder No.	Part No.
PACEMAKER		
PM10, PM10S	394-13	
PM20	397-9	
2285	399-9	
PACKARD		
(See Auto Radio Listing)		
PACKARD-BELL		
RM-200 (TV Remote Control)	393-3	
3T3	392-2	
●21DC5, 21DC6, 21DC7 (Ch. 98D3)	393-3	
●21DK1, -U (Ch. 98D1)	318-9	
(PCB 400-5)	318-9	
●21SC6, 21SC7, 21SC8 (Ch. 8853)	392-2	
●21SK3 (Ch. 8853 and AM Tunes 3T3)	392-2	
●21ST3 (Ch. 8853)	392-2	
●21VT2 (Ch. 8853)	392-2	
●24DC4 (Ch. 98D3)	393-3	
●24DK1, -U (Ch. 98D1)	318-9	
(PCB 400-5)	318-9	
●24SC2 (Ch. 8853)	392-2	
●24VT1 (Ch. 8853)	392-2	
Ch. 8853	392-2	
●Y18C1 (PCB 400-5)	318-9	
Ch. 98D3	374-17-5	
PHILCO		
F-760	396-6	
F-963	396-6	
F-1500	362-5	
●F3042F, G, F3044A (Ch. 8H25)	387-17-5	
●F3202C, F3204B, L, M (Ch. 8H25)	387-17-5	
●F4210, E, L (Ch. 8L41)	399-2	
●F4210X (Ch. 8L41B)	399-2	
●F4212, L (Ch. 8L41)	399-2	
●F42145TM, STN (Ch. 8L42)	399-2	
●F4216, L (Ch. 8L71)	381-17-5	
●F4618, L, F4620SL, SM (Ch. 8L41)	399-2	
●F4621S, SL, F4622, L, F4624, F4625SL, SL (Ch. 8L43)	399-2	
●F4626, L (Ch. 8L73)	381-17-5	
●F4628, L (Ch. 8L41)	399-2	
●F4630, L, F4632, F4634, L, F4636, L (Ch. 8L43)	399-2	
●F6206SL, SM (Ch. 8P51, A)	399-2	
●F6205SL, SM (Ch. 8P51, A)	399-2	
●F6624T, TL (Ch. 8L72)	381-17-5	
●UF4618, L (Ch. 8L41U)	399-2	
●UF3042F, G, UF3044A (Ch. 8H25U)	387-17-5	
●UF3202C, UF3204B, L, M (Ch. 8H25U)	387-17-5	
●UF4210, E, L (Ch. 8L41U)	399-2	
●UF4210X (Ch. 8L41BU)	399-2	
●UF4212, L (Ch. 8L41U)	399-2	
●UF42145TM, STN (Ch. 8L42U)	399-2	
●UF4216, L (Ch. 8L71U)	381-17-5	
●UF4618, L, UF4620, SL, SM (Ch. 8L41U)	399-2	
●UF4621S, SL, UF4622, L, UF4624, UF4625SL, SL (Ch. 8L43U)	399-2	
●UF4626, L (Ch. 8L73U)	381-17-5	
●UF4628, L (Ch. 8L41U)	399-2	
●UF4630, L, UF4632, UF4634, L, UF4636, L (Ch. 8L43U)	399-2	
●UF6206SL, SM (Ch. 8P51U)	399-2	
●UF6205SL, SM (Ch. 8P51U)	399-2	
●UF6624T, TL (Ch. 8L72U)	381-17-5	
Ch. 8E11, U, 8E13	370-16-5	
Ch. 8H20, U, 8H22	370-16-5	
Ch. 8H25, U	387-17-5	
Ch. 8L41, B, BU, U, 8L42, U, 8L43, U	399-2	
Ch. 8L71, U, 8L72, U, 8L73, U	381-17-5	
Ch. 8P51, A, U	399-2	
PHONOLA		
1057, 1057W	399-10	
PONTIAC		
(See Auto Radio Listing)		
RCA VICTOR		
(Also See Record Changer & Recorder Listing)		
HFP (Ch. RS-164B)	395-11	
HRD-2 (Ch. RS-158J)	346-10	
SHF3, SHF3D (Ch. RC-1168A)	396-7	
SHF6, SHF7 (Ch. RS-164, A)	395-11	
8EY31HE, KE (Ch. RS-165 (2nd Prod.))	383-11	
8HFF1 (Ch. RS-158B)	346-10	
8RF13 (Ch. RC-1168A)	390-9	
9C7FE, FE, LE, 9C8FE, J, ME (Ch. RC-1166B)	394-14	
9ED1HE, JF (Ch. RS-170C)	398-10	
9ED2KF, LE (Ch. RS-170A)	400-9	
9ED31K, L (Ch. RS-170A)	400-9	
9ED32H, LJ (Ch. RS-170)	400-9	
9E5SH, FE, LE, 9C170B, 400-9	400-9	
9INT1, 9INT2 (Ch. RC-1172)	399-11	
9U5SH, KE (Ch. RC-1170A)	395-12	
9X10FE, JE, ME (Ch. RC-66A)	394-14	
RCA VICTOR—Cont.		
●14PD8053, U, 14PD8054, U, 14PD8055, U, 14PD8057, U (Ch. KCS111C, D)	396-3	
●14PT8021, U, 14PT8022, U (Ch. KCS111A, B)	396-3	
●14VT8155, U, 14VT8157, U (Ch. KCS111F, H)	396-3	
●17D8185, U, 17D8186, U, 17D8187, U (Ch. KCS109C, D)	392-3	
●17PD8093, U, 17PD8094, U, 17PD8096, U, 17PD8099, U (Ch. KCS-109C, D)	392-3	
●17PT8071, U, 17PT8072, U (Ch. KCS 109A, B)	392-3	
●21CD8725, U, 21CD8727, U (Ch. CTC7A, B)	399-3	
●21CD8775, U, 21CD8776, U, 21CD8777, U (Ch. CTC7A, B)	399-3	
●21CD8865, U, 21CD8866, U, 21CD8867, U (Ch. CTC7C, D)	399-3	
●21CD8885, U, 21CD8886, U, 21CD8888, U (CTC7C, D)	399-3	
●21CD8906, U, 21CD8907, U (Ch. CTC7C, D)	399-3	
●21CD8926, U, 21CD8927, U (Ch. CTC7E, F)	399-3	
●21CD8949, U (Ch. CTC7E, F)	399-3	
●21CS7815, U, 21CS7817, U (Ch. CTC5, A)	353-11	
●21CT7835, U, 21CT7837, U (Ch. CTC5B, C)	353-11	
●21CT7855, U, 21CT7857, U (Ch. CTC5D, E)	353-11	
●21CT7865, U, 21CT7866, U, 21CT7867, U (Ch. CTC5D, E)	353-11	
●21CT8785, U, 21CT8787, U (Ch. CTC5F, H)	353-11	
●21D8281, U, 21D8282, U (Ch. KCS116A, B)	400-4	


Set No.	Folder No.	Model
SILVERTONE—Cont.		
8116	(Ch. 528.51106, 107, 160, 161, 163, 164, 165, 166, 168)	397-3
8117	(Ch. 528.51110, 112, 113)	390-3
8117	(Ch. 528.51170, 171, 172, 173, 175)	397-3
8150	(Ch. 528.50144)	389-3
8151	(Ch. 528.50150, 152, 153, 154, 155) (PCB 400-5)	389-3
8152	(Ch. 528.50144)	389-3
8153	(Ch. 528.50150, 152, 153, 154, 155)	(PCB 400-5) 389-3
8154	(Ch. 528.51100, 102, 104)	390-3
8154	(Ch. 528.51106, 107, 160, 161, 163, 164, 165, 166, 168)	397-3
8155	(Ch. 528.51110, 112, 113)	390-3
8155	(Ch. 528.51170, 171, 172, 173, 175)	397-3
8156	(Ch. 528.51100, 102, 104)	390-3
8156	(Ch. 528.51106, 107, 160, 161, 163, 164, 165, 166, 168)	397-3
8157	(Ch. 528.51110, 112, 113)	390-3
8157	(Ch. 528.51170, 171, 172, 173, 175)	397-3
8158	(Ch. 528.51100, 102, 104)	390-3
8158	(Ch. 528.51106, 107, 160, 161, 163, 164, 165, 166, 168)	397-3
8160	(Ch. 528.51140, 142, 143)	390-3
8160	(Ch. 528.51180, 181, 182, 183, 184, 185, 187)	397-3
8161	(Ch. 528.51150, 152, 153)	390-3
8161	(Ch. 528.51190, 191, 193, 194)	397-3
8162	(Ch. 528.51140, 142, 143)	390-3
8162	(Ch. 528.51180, 181, 182, 183, 184, 185, 187)	397-3
8163	(Ch. 528.51150, 152, 153)	390-3
8163	(Ch. 528.51190, 191, 193, 194)	397-3
8182	(Ch. 528.51100, 102, 104)	390-3
8182	(Ch. 528.51106, 107, 160, 161, 163, 164, 165, 166, 168)	397-3
8183	(Ch. 528.51110, 112, 113)	390-3
8183	(Ch. 528.51170, 171, 172, 173, 175)	397-3
8184	(Ch. 528.51104, 140, 142, 143)	390-3
8184	(Ch. 528.51161, 162, 163, 180, 181, 182, 183, 184, 185, 187)	397-3
8185	(Ch. 528.51150, 152, 153)	390-3
8185	(Ch. 528.51190, 191, 193, 194)	397-3
8186	(Ch. 528.51104, 140, 142, 143)	390-3
8186	(Ch. 528.51161, 162, 163, 180, 181, 182, 183, 184, 185, 187)	397-3
8187	(Ch. 528.51150, 152, 153)	390-3
8187	(Ch. 528.51190, 191, 193, 194)	397-3
8188	(Ch. 528.51140, 142, 143)	390-3
8188	(Ch. 528.51180, 181, 182, 183, 184, 185, 187)	397-3
8190, 8190A	(TV Ch. 528.52100, 101, 102 and Radio Ch. 528.53190)	391-3
8191, 8191A	(TV Ch. 528.52110, 111, 112 and Radio Ch. 528.53190)	391-3
8192, 8192A	(TV Ch. 528.52100, 101, 102 and Radio Ch. 528.53190)	391-3
8193, 8193A	(TV Ch. 528.52110, 111, 112 and Radio Ch. 528.53190)	391-3
8196	(Ch. 528.51240, 241, 242, 245)	397-3
8197	(Ch. 528.51250, 251, 253)	397-3
8198	(Ch. 528.51240, 241, 242, 245)	397-3
8199	(Ch. 528.51250, 251, 253)	397-3
8200, 8202	(Ch. 132.43200, 201)	398-11
8236, 8238	(Ch. 528.59030, 567, 59030)	398-12
8239, 8242	(Ch. 528.59020, 567, 59020)	400-10
8244, 8245, 8246, 8247, 8248	(Ch. 528.59010)	400-10
9118, 9119	(Ch. 528.51220, 230)	400-14-5
9224	(Ch. 528.46400)	382-11
Ch. 132.42700		395-14
Ch. 132.42800		391-12
Ch. 132.42900		396-10
Ch. 132.43200, 132.43201		398-11

Set No.	Folder No.	Model
SILVERTONE—Cont.		
528.46300, 528.46301		388-1
(PCB 400-5)		382-11
528.46400		382-11
528.50125		389-3
528.50144		389-3
528.50150, 528.50152, 528.50153, 528.50154, 528.50155	(PCB 400-5)	389-3
528.51040	(See Photofact Servicer)	393
528.51050	(See Photofact Servicer)	394
528.51100, 528.51102, 528.51104		390-3
528.51106, 528.51107, 528.51108		397-3
528.51110, 528.51112, 528.51113		390-3
528.51140, 528.51142, 528.51143		390-3
528.51150, 528.51152, 528.51153		390-3
528.51160, 528.51161, 528.51163, 528.51164, 528.51165, 528.51166, 528.51167, 528.51168, 528.51170, 528.51171, 528.51172, 528.51173, 528.51175		397-3
528.51180, 528.51181, 528.51182, 528.51183, 528.51184, 528.51185, 528.51187, 528.51190, 528.51191, 528.51193, 528.51194		397-3
528.51220		400-14-5
528.51230		400-14-5
528.51240, 528.51241, 528.51242, 528.51245, 528.51251, 528.51253		397-3
528.52040		396
(See Photofact Servicer)		396
528.52050	(See Photofact Servicer)	398
528.52100, 528.52101, 528.52102		391-3
528.52110, 528.52111, 528.52112		391-3
528.53030		397-12
528.53040		392-10
528.53150		394-15
528.53190		391-3
528.53200		397-12
528.59010, 528.59020		400-10
528.59030		398-12
567.59020		400-10
567.59030		398-12
SONIC		
410		397-13
465		390-11
SPARTAN		
24 Series		398-4
25 Series		384-17-5
Chassis AMP-158AA		390-12
Chassis CR-729AA, BA		395-15
Chassis U24-01AA, U24-02AA, U24-03AA, U24-04AA, U24-06AA		398-4
Chassis U25-01AA, U25-02AA, U25-03AA, U25-04AA, U25-05AA, U25-06AA, U25-07AA, U25-08AA, U25-09AA, U25-10AA, U25-11AA		384-17-5
Chassis V24-01AA, V24-02AA, V24-03AA, V24-04AA, V24-06AA		398-4
Chassis V25-01AA, V25-02AA, V25-03AA, V25-04AA, V25-05AA, V25-06AA, V25-07AA, V25-08AA, V25-09AA, V25-10AA, V25-11AA		384-17-5
STEELMAN		
1A19-2		398-13
3A14-3		400-11
358		397-14
4A21, 4A22		397-15
4D15, 4D17, 4D18		395-16
STROMBERG-CARLSON		
AU-62		391-13
SR-402		395-17
SR-403B		400-12
STUDEBAKER		
(See Auto Radio Listing)		
SYLVANIA		
31C606 Series (Ch. 1-534-1, -2)		391-4
31T304 Series (Ch. 1-534-1, -2)		391-4
4401 (Ch. 1-608-1)		396-11
Ch. 1-534-1, -2		391-4
Ch. 1-608-1		396-11
TECH-MASTER		
FM-18		398-14
16A		396-12
21		391-14
630-5, 630-5T		388-2
(PCB 400-5)		390-4
1930N		390-4
2430N		390-4

Set No.	Folder No.	Model
TELEFUNKEN		
"Gavotte 7"		399-12
TONFUNK		
7046M		399-13
TRAV-LER		
TR-250-A, TR-251-A		392-11
617-33U, 617-34U (Ch. 628A6)		337-14
621-30U, 621-31U, 621-32U, (Ch. 628A6)		337-14
621-74U, 621-75U (Ch. 628A6)		337-14
717-MT-500 (Ch. 775-37)		371-13
721-K-610 (Ch. 718-17, 775-17)		371-13
721-K-611, U, 721-K-612, 721-K-613 (Ch. 736-47, 737-47)		371-13
721-LP-650 (Ch. 718-17, 775-17)		371-13
721-LP-651, U (Ch. 736-47, 737-47)		371-13
721-MT-600 (Ch. 718-17, 775-17)		371-13
721-MT-601, U (Ch. 736-47, 737-47)		371-13
721-T-602 (Ch. 736-47)		371-13
724-K-772 (Ch. 776-17)		371-13
1710, A (Ch. 72917, A, 775-27)		371-13
1715, U (Ch. 72916, 72917, 73016)		371-13
1720, U (Ch. 72916, 72917, 73016)		371-13
1722, 1723, 1725 (Ch. 740-17)		371-13
1730 (Ch. 729-26)		399-15-5
1731 (Ch. 775-57)		399-15-5
Ch. 628A6, (PCB 399-4)		337-14
Ch. 718-17, (PCB 394-5)		371-13
Ch. 729-26		399-15-5
Ch. 736-47, 737-47		371-13
Ch. 740-17, (PCB 394-5)		371-13
Ch. 775-17, -27, -37, 776-17		371-13
Ch. 775-57		399-15-5
Ch. 72916, 72917, 72917A, 73016		(PCB 394-5) 371-13
TRUETONE (Also See Auto Radio Listing)		
D2832B, D2834B		384-16
D5736A		386-12
D5770B, D5771B, D5772B		399-14
D5842A, D5844A		397-14
D5892, A, D5894, A		397-17
2D1824A, B, 2D1825A, B, 2D1826A, B, 2D1827A, B		394-3
2D1840A, 2D1841A, 2D1842A, 2D1843A, 2D1844A, 2D1845A		395-3
2D2720C, (PCB 398-5)		357-10
2D2728A, B, (PCB 396-5)		375-5
2D2840A, 2D2841A, 2D2842A, 2D2843A		395-3
V-M (Also See Record Changer and Recorder Listing)		
155A		393-11
991		398-15
1276		391-15
1290		392-12
WEBCOR		
(See Webster-Chicago)		
WEBSTER-CHICAGO		
1853		356-17
WELLS-GARDNER		
321AM54-A-436 (See Photofact Servicer)		400
321AM54-A-470 (See Photofact Servicer)		400
2321AM54-A-438 (See Photofact Servicer)		400
2321AM54-A-494 (See Photofact Servicer)		400
WESTINGHOUSE		
H-17T241, H-17T242, H-17T243, H-17T244, H-17T245 (Ch. V-2373-1)		392-4
H-17T241, H-17T242, H-17T243, H-17T244, H-17T245 (Ch. V-2383-1)		392-4
H-21K210, A, H-21K211, A (Ch. V-2364-1, -3)		399-15-5
H-21K226B (Ch. V-2372)		388-3
H-21K2256, H-21K2257 (Ch. 2371)		387-4
H-21KU210, A, H-21KU211, A (Ch. V-2364-2, -4)		399-15-5
H-21KU256, H-21KU257 (Ch. V-2381)		387-4
H-21T206, A, H-21T207, A (Ch. V-2364-1, -3)		399-15-5
H-21T219B, H-21T221B, H-21T222B (Ch. V-2372)		388-3
H-21T206, A, H-21T207, A (Ch. V-2364-2, -4)		399-15-5

Set No.	Folder No.	Model
WESTINGHOUSE—Cont.		
H-580T5, H-581T5, H-583T5, (Ch. V-2259-3)		392-13
H-621P6, H-622P6 (Ch. V-2296-1)		396-14
Ch. V-2259-3		392-13
Ch. V-2296-1		396-14
Ch. V-2364-1, -2, -3, -4		399-15-5
Ch. V-2373-1		392-4
Ch. V-2383-1		392-4
ZENITH (Also See Record Changer Listing)		
A512W, Y (Ch. 5A02)		397-18
A723F, R, W, A724G, L, Y, A730E, R, (Ch. 7A02, 7A04, 7A05)		398-16
A1410L, A1411P, A1412G (Ch. 15A26)		390-13-5
A1716L, A1717G, A1718B, A1719 (Ch. 15A26)		390-13-5
A1815P, PU (Ch. 15Z31, U)		376-5
A2001L (Ch. 15A26Q)		390-13-5
A2221J, JU, Y, YU, A2223E, EU, H, HU, R, RU, Y, YU, (Ch. 17A20, U)		393-4
A2221L, R, A2223E, R, Y, (Ch. 17A30)		390-13-5
A2245E, EU, R, RU (Ch. 17A20, U)		393-4
A2245E, R, A2246E, R (Ch. 17A30)		390-13-5
A2250M, MU, R, RU, A2251E, EU, R, RU, (Ch. 17A20, U)		393-4
A2252R, A2253E, R (Ch. 17A30)		390-13-5
A2282E, EU, R, RU, (Ch. 17A20, U)		393-4
A229E, R (Ch. 17A30)		390-13-5
A2329J, JU, A2330E, EU, H, HU, R, RU (Ch. 19A20, U)		394-4
A2358E, EU, R, RU, A2359E, EU, H, HU, R, RU, A2362M, MU, R, RU (Ch. 19A20, U)		394-4
A2673E, EU, R, RU, (Ch. 17A20, U)		393-4
A2673E, R (Ch. 17A30)		390-13-5
A3000E, R (Ch. 17A21Q)		393-4
A3000E, R (Ch. 17A31Q)		390-13-5
A3001E, H, R, (Ch. 17A20Q)		393-4
A3001E, R (Ch. 17A30Q)		390-13-5
A3004, E, R (Ch. 17A21Q)		393-4
A3004, E, R (Ch. 17A31Q)		390-13-5
A3006E, H, R (Ch. 17		

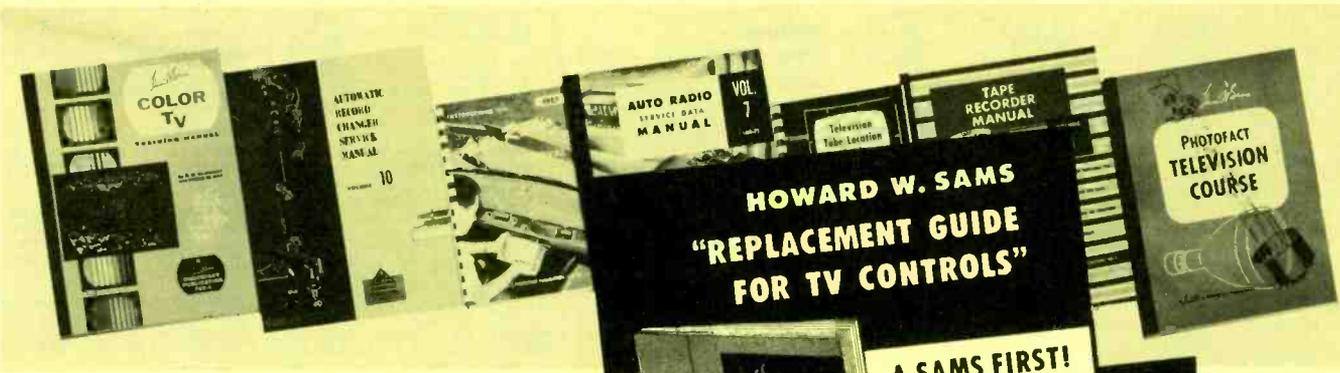DON'T MISS THIS IMPORTANT SAMS PUBLICATION !



IMPORTANT

**REPLACEMENT CONTROL DATA
FOR 18,000 TV SET MODELS!**

The four manufacturers (Centralab, Clarostat, IRC and Mallory) will not publish an individual replacement control guide for 1958. This guide was published at their suggestion and with their full cooperation. All replacement control listings have been checked and approved by the manufacturer of the replacement control.

**at your SAMS
distributors now!**

only \$1.00

**HOWARD W. SAMS
"REPLACEMENT GUIDE
FOR TV CONTROLS"**



A SAMS FIRST!

Lists recommended replacement TV controls of these manufacturers:


**CENTRALAB
CLAROSTAT
IRC
MALLORY**

NOTHING ELSE LIKE IT!

- The most complete replacement guide for TV Controls ever published—replacements for 18,000 TV models—covers virtually every TV set produced from 1947 to 1958!
- Every replacement control is *currently available* and recommended by the manufacturer to meet "Industry Part Number" specifications!
- Exclusive "Industry Part Number" system gives you quick, easy selection of all four manufacturers' recommended replacements!
- "Industry Part Number" listing helps you maintain inventory of most-needed controls for your service work—avoids needless duplication!
- Saves you time in selecting proper replacement controls—saves ordering time too. Guide actually pays for itself the first time you use it on a control repair job!

QUICK AND EASY!

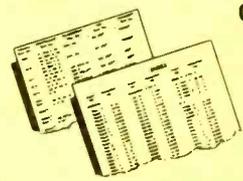Exclusive new "Industry Part Number" System locates recommended control replacements in just seconds.



A "MUST" IF YOU SERVICE TV!

8 1/2 x 11"
**BELONGS ON
YOUR BENCH**


Only \$1.00

**ORDER TODAY FROM YOUR SAMS
DISTRIBUTOR**

HOWARD W. SAMS & CO., INC.



anatomy
of the
tube...
LESSON #1

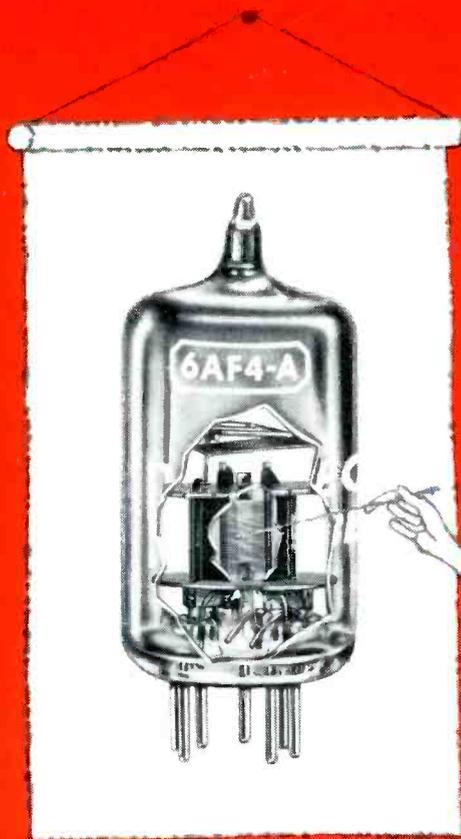

GRID

How RCA builds special
prescription grids...extends 6AF4-A life!

RCA's redesign of the 6AF4-A has resulted in minimized slump, product uniformity, and projected average life of 4,000 hours or more!

Here are some of the materials RCA "prescribes" in manufacturing the new 6AF4-A. The grid is plated with Palladium, a rare metal capable of withstanding high temperatures. The use of this grid structure minimizes interelectrode leakage, prevents grid loading, and as a result, provides stable tube performance. The cathode, a nickel alloy, is specially selected to reduce interface resistance and thus minimizes slump. The use of pins which are silver-plated reduces skin effect at ultra high frequencies and improves tuner performance.

All these features, in addition to dynamic life tests, help to assure long and dependable performance. No wonder RCA's 6AF4-A is tops!

So, here's the #1 lesson in radio, phonograph, and TV service—when ordering tubes for replacement, specify "RCA Tubes only."



RADIO CORPORATION OF AMERICA

Electron Tube Division

Harrison, N. J.

day
and
night
protection
with

L
I
T
T
L
E
F
U
S
E

Inc., Des Plaines, Illinois

