

SEPTEMBER, 1959 35 CENTS



PHOTOFACT REPORTER®

Including **Electronic Servicing**

REGISTER NOW!
 CHILDREN'S ENROLLMENT OFFICE
 Grades 1-9
 SOUTH DOOR ←
 ADULT BUSINESS EVENING CLASSES
 NORTH DOOR →




This Month's Highlights

- Selecting the Proper Scope Probe
-
- Crosshatch Marks Chroma Phase
-
- Vertical Sweep Systems Part 2
-
- Short-Lived TV Tubes

WM M DAVIS
118 RIVERSIDE AVE
CANON CITY COLO

IA 9H 635 1260E

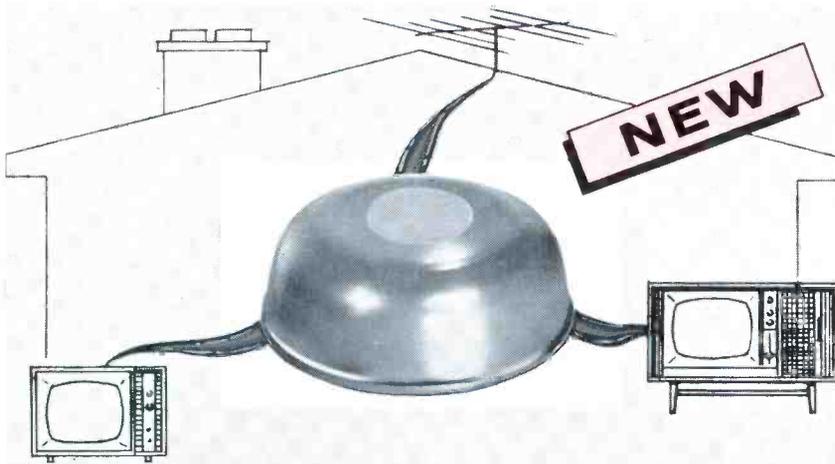

Walsco 2-Set TV-FM Couplers

A Walsco Exclusive . . . both these couplers can be mounted on wall or mast before attaching leads. Standard Model for strong signal areas; Low Loss Model for fringe areas.

No. 1600 Standard List \$2.50
 1602 Low Loss 3.50




WALSCO STRIP-ER CLIP

New precision tool with accurate dial for stripping each wire size. Clips all wires from 12 to 26 gauge. Ground cutting edges, insulated grip.
 No. 595-X List \$2.30



WALSCO LONG NECK OILER

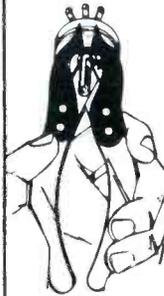Reach all those hard-to-get oil cups, etc. All plastic container and nozzle; telescoping extension reaches 7 inches. Contains high quality all-purpose oil.
 No. 985 List \$1.50



WALSCO C-RING TOOL


Specially designed to remove and insert "C" washers and retaining rings on tuners, control shafts, etc. High grade steel, nickel plated.
 No. 585 . . . List \$3.15



WALSCO STICKLEBABY

The only hand tool that drills and saws in any direction. Excellent for veneer work and fine carpentry. Combination drill, saw and rasp.
 No. 586-00 . . . List \$1.63

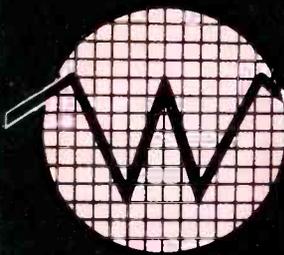More For You . . . And The Price Is Right!



WALSCO ELECTRONIC PRODUCTS

Everything You Need For Better Servicing



WALSCO CHASSIS PUNCHES

Make better chassis holes faster with Walsco's "Low-Torque" Punches. Specially hardened, precision ground tool steel; easy to use. Complete line of sizes and styles.



KEYED



SQUARE



"D"



WALSCO HEX & SPLINE KIT

Contains 11 of the most popular size hex and spline wrenches in durable plastic snap case. High grade alloy steel.
 No. 560 List \$2.25



WALSCO 100-PAK HARDWARE

All the quality electronic hardware items you need in convenient 100-to-a-box packages. Look for the Walsco Display at your jobber.



WALSCO PHONO DRIVES

The only complete line of replacement phono and recorder drives and belts on the market. Includes all the new model turntables and changers.


FREE! Write for your Walsco Catalog. Send postcard today.



WALSCO ELECTRONICS MFG. CO.

Division of Textron Inc.
 West Plant: Los Angeles 18, California Main Plant: ROCKFORD, ILLINOIS, U.S.A.
 Canada: Atlas Radio Corp., Ltd., Toronto 19

YOU CAN GET WHAT YOU WANT FROM WALSCO!

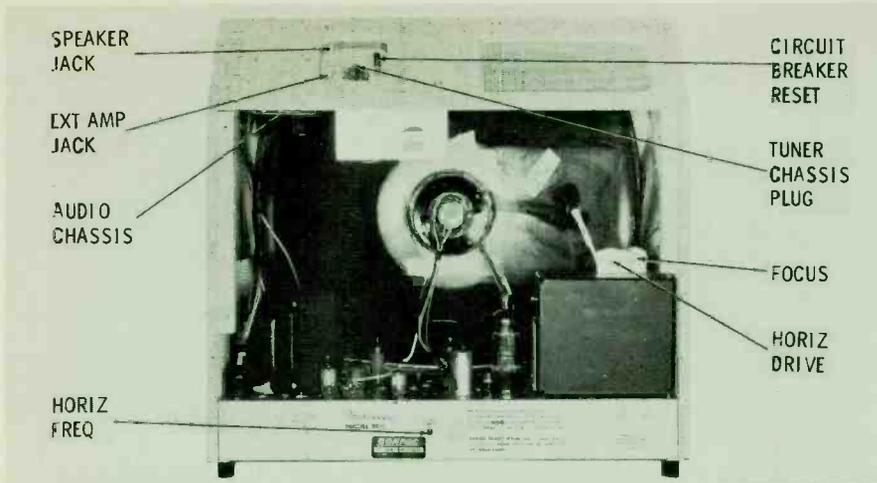

**Fleetwood Model 900
with tuner Chassis 870**

You may find this custom receiver installed in a bookcase, wall, or just about anywhere in a customer's home. The tuner chassis, including RF, IF, and sync stages, can be located in a remote position from the picture tube and sweep chassis. The complete outfit has a complement of 25 tubes in the tuner, audio, and sweep chassis, plus a 21ERP4 110° CRT.





Taking a peek at the back of the Model 900 chassis (shown here mounted in a utility cabinet), you can see its horizontally-mounted and transformer-powered. A two-tube audio chassis, incorporating an AF amplifier and output stage, is positioned under a sloping section at the top of the cabinet. This subchassis includes a 6-volt relay and switch that automatically applies power to the main sweep chassis whenever the tuner is energized. The drive adjustment shown on the rear of the cabinet is a 50K-ohm pot located in the output plate circuit of the horizontal multivibrator.


You'll also find several features on the "topside" of this chassis. For example, horizontal linearity and width coils are located behind the high-voltage cage, and a .3-amp slow-blow fuse mounts right next to the 6CD6 horizontal output tube. A pair of plug-in silicon rectifiers positioned near the power transformer are used to develop 300 volts B+.

On the front of the tuner chassis, you'll find one of the control knobs labeled DEFINITION. This should be set to give the most pleasing picture to the customer. Rotating the knob in one direction produces a softer tone, while picture elements appear much sharper at the other end of rotation. From the circuit diagram, you'll note that this control is a 3-position switch located in the plate circuit of the first video-IF amplifier. Capacitor C26 or C27 is switched across the tuned primary, and thereby varies the extent of high-frequency response.

Before making a call to fix this set, check your caddy for #14 dial lamps. The tuner uses 14 of these little rascals across the channel-indicating panel. Two audio-output jacks can be found on the rear apron of the tuner—one for a low-level output straight from the detector, and the other from a cathode-follower stage which includes the volume control.

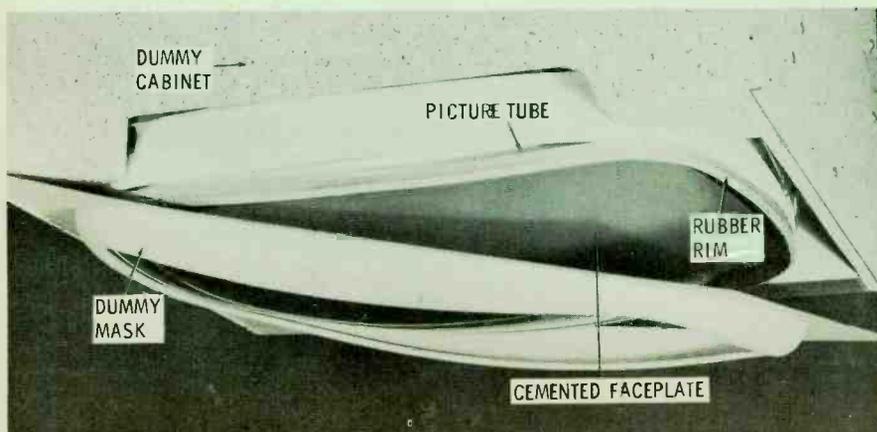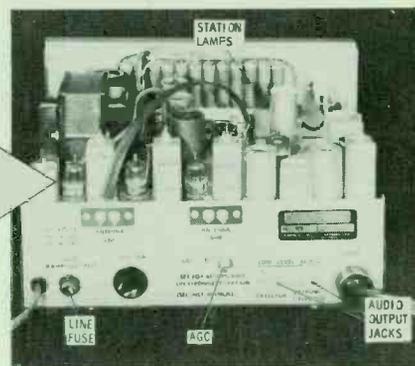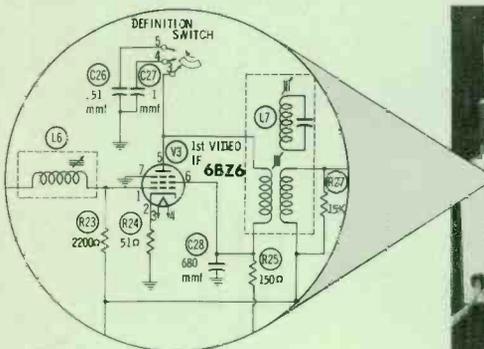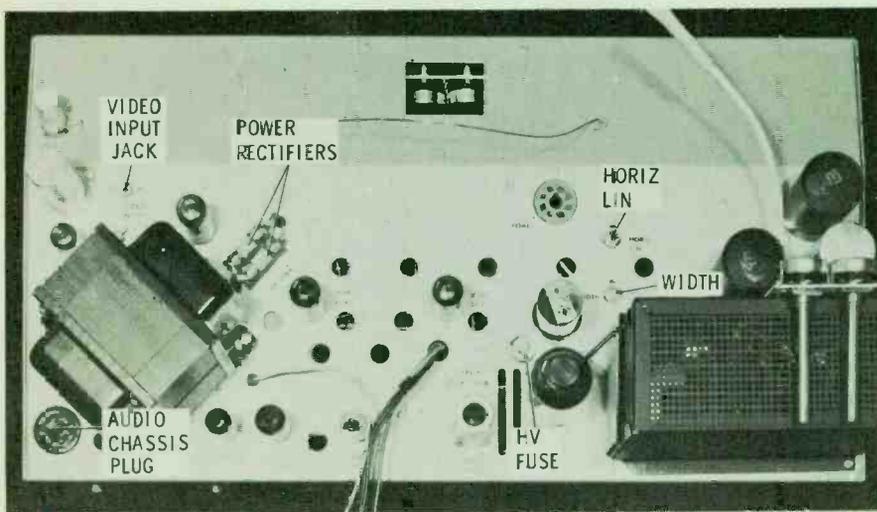Don't try to pry the safety glass from the front of the picture tube on this receiver. The front protective glass is sealed to the surface of the tube, and this laminated integral panel should not require cleaning.



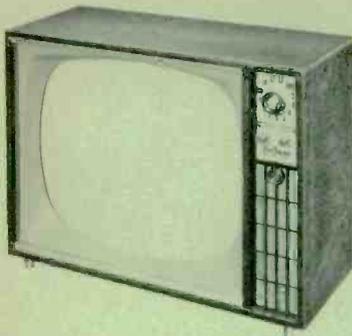

**Hoffman Model K1331
Chassis 344**

This receiver is one of a *Spanette* line featuring a 21" 110° picture tube housed in a cabinet only 10 7/8" deep. It's basically a table model, but is light enough to double for a large-screen portable. To remove the safety glass for cleaning, merely take out the Phillips-head screws holding the top retaining strip, tilt the glass outward at the top, and lift the glass up and out.





With the cabinet back removed, you'll find a transformer-powered, vertically-mounted hand-wired chassis. Notice, too, that a single 5U4 rectifier fits snugly in a chassis cutout on the right side. This tube, as well as the others, however, is in easy reach from the back. The *Hot Rod* tuner, employing 6CY5 and 6CG8 tubes, is positioned with the operating controls and the speaker on a narrow vertical panel at the opposite side of the cabinet. This panel is not attached to the main chassis, but is separately mounted to the cabinet. It need not be removed to work on the wiring side of the chassis; the pan can be pivoted outward and the panel left in place for many repairs.


Taking a closer look at the chassis, you'll see that the ringing coil for the horizontal multivibrator, and a pigtail line fuse, are located at the left and above the high-voltage cage. The 3.2-amp fuse is a slow-blow type in the primary circuit of the power transformer. About the latest tube types you'll run across in this chassis are a 6DT5 in the vertical output stage and a 6DA4 in the damper circuit.

If it's necessary to pull the chassis for bench service, you'll find that the main pan has only a tongue-and-groove fitting at the top of the cabinet near the service adjustments, and a couple of bolts at the bottom. Service adjustments across the top of the pan include AGC, horizontal drive, vertical linearity, and height.

To remove the panel incorporating the tuner, front controls, and speaker, you must first remove the push-on type knobs from the front and the Phillips-head screw pointed out in the photo.

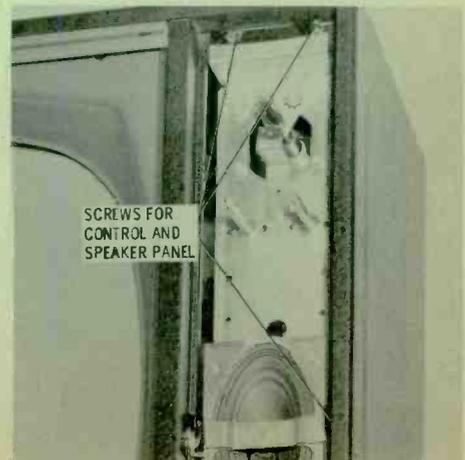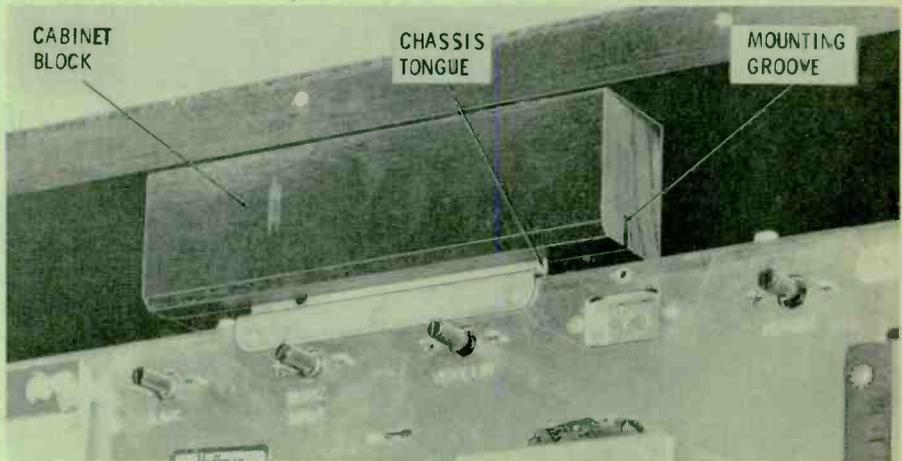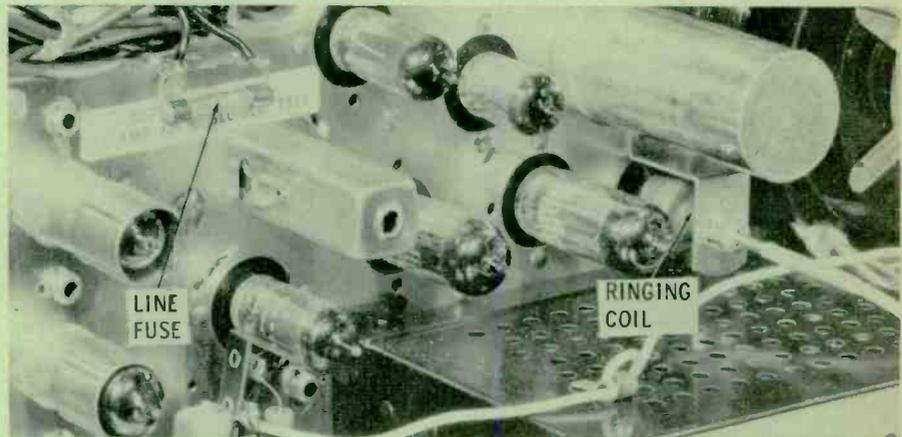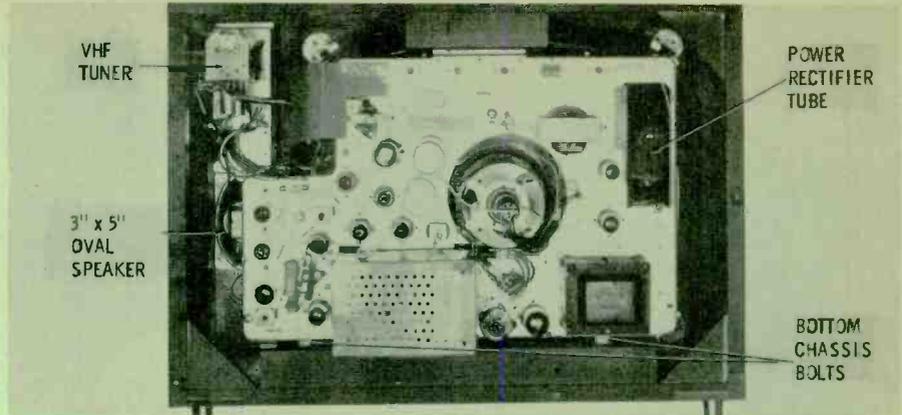After taking off the front decorative section, remove four Phillips-head screws under strips of tape at the top and bottom of the panel. This will free the panel, and the entire chassis can be removed by disconnecting the picture tube socket, yoke plug, and high-voltage lead.



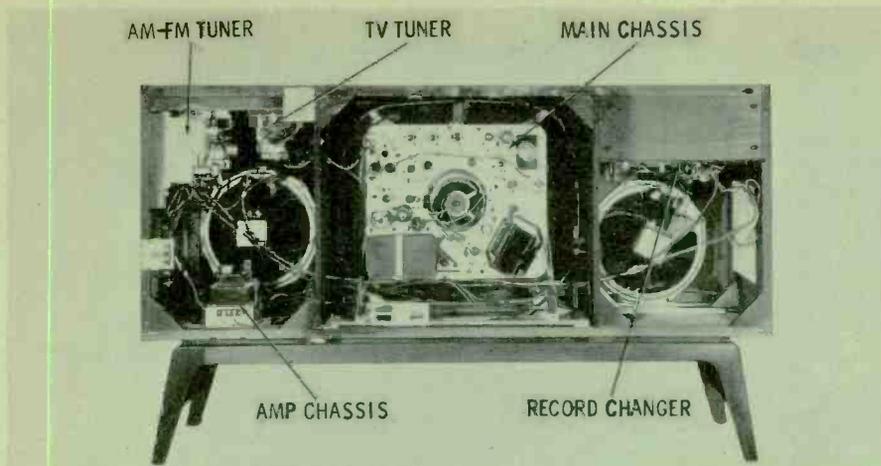

Magnavox Model IU 354R TV Chassis U30-15-00

This combination includes a 24" TV receiver, AM-FM radio, and stereo automatic phonograph. The 24AHP4 110° picture tube is featured in the center of the all wood cabinet, while sliding panel doors on the top expose the operating controls on the right and a record-changer compartment on the left.




You can see the layout of the combination from the rear cabinet view. The stereo reproduction system consists of six separate speakers—a 12" woofer and two 5" units on each side of the cabinet. In addition to the main TV chassis (designated as the 30-series), the instrument also employs an AM-FM tuner chassis 59-00 and an audio-amplifier chassis 196-00.

You'll find most of the TV service adjustments in a close group between the high-voltage cage and the power transformer at the bottom of the vertically-mounted chassis. The AFC dual-diode is a plug-in unit that feeds a special component combination network on the wiring side of the chassis.

You might take note of the AC line tap pointed out below the 5U4 rectifier. This small device is a special shorting plug located in the primary circuit of the power transformer to compensate for high line voltage. It has "117V" marked on one side and "127V" marked on the other. Under normal line conditions, the 117V mark should be up. If line voltage is higher than normal, the plug should be reversed in its socket.

The clip-in fuse is a 1/4-amp slow-blow type which protects the flyback system. The 6DQ6A horizontal-output tube is also located in this area of the chassis. Around the glass envelope of this tube, you'll note an ion trap magnet which serves to counteract Barkhausen oscillation. Speaking of tubes, a 6BF6 serves as half of a vertical multivibrator and as a diode clamper for both AGC and blanking. The AGC-keyer and sound-IF stages employ EF94's, which are merely foreign-made 6AU6's. You might also care to know that a 6V6GT is used as a voltage regulator for the power supply.

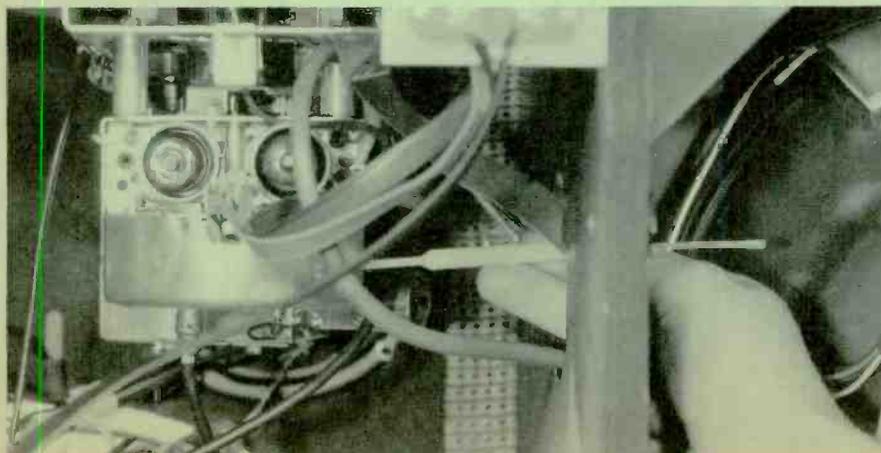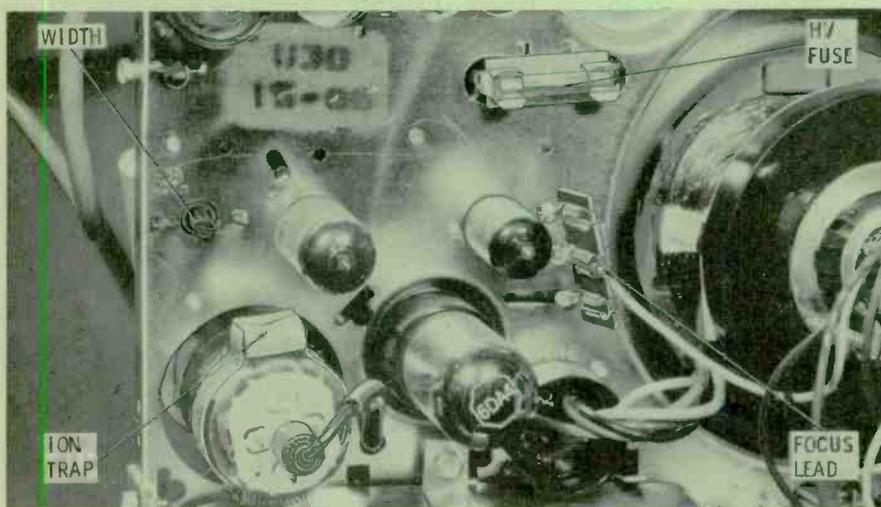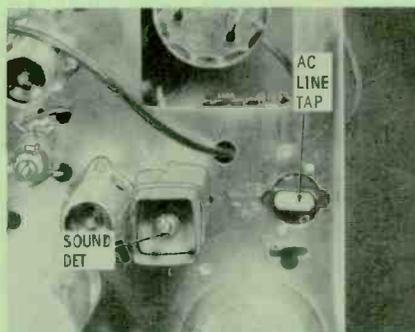The VHF-UHF tuner, located some distance from the TV chassis, makes use of three tubes—a 6BN4 RF amplifier, 6CG8 converter, and 6AF4A UHF oscillator. Access to the VHF oscillator adjustments is provided for as illustrated in the photo.





**RCA Model 210CK855
Chassis CTC9A**

This color console employs a 21CYP22 picture tube, VHF tuner, and 6" x 9" PM speaker. The color tube and safety glass can be cleaned from the front by first prying the top and bottom trim strips off, starting at the ends with a small screw-driver or soldering aid. This will expose two glass retainers at both the top and bottom. Remove the retainers by sliding them to the right, and the glass may then be lifted out.

The chassis is of conventional style, but mounts vertically along one side of the cabinet. The AGC control has been moved to the rear apron of the chassis, and no adjustment is provided for horizontal drive. The B+ fuse located on the top edge of the chassis near the tuner is a 3.5-amp "C" type. Newcomers to the tube lineup for RCA color sets include four 6EA8's and one 6EW6.






Although isolated from the line by a power transformer, the chassis employs two silicon rectifiers in the low-voltage supply. The pigtail fuse positioned directly in front of these is a 3/4-amp unit protecting the sweep and high-voltage circuits. The main chassis incorporates five separate printed boards; an additional board is used for the convergence panel. Each board features the new *Phantom Wiring*, which identifies each part and maps all connections on the component side for ease in circuit tracing.

You can reach the two tubes in the regulated high-voltage supply by removing one screw from the side of the cage and sliding the round panel door upward as shown. You'll find the horizontal linearity control in the cage, while the high-voltage adjustment and horizontal-waveform coil are positioned on the chassis in front of the cage.

You might note that the width adjustment on this receiver consists of a lead-and-plug arrangement on the yoke assembly. To increase width, remove the lead plugged into the dummy terminal on the left and insert it into the terminal identified as No. 2.

The hairpin clips attached to a plastic ring on the bell of the picture tube a few inches from the yoke are edge-purity magnets. Maximum correction is obtained with the open ends 180° apart. Neutral position is with both magnets in perfect alignment with each other.


For convenience, the dynamic-convergence adjustments are located on a separate panel which can be removed from the inside of the cabinet and positioned on the two mounting screws pointed out in the photo.

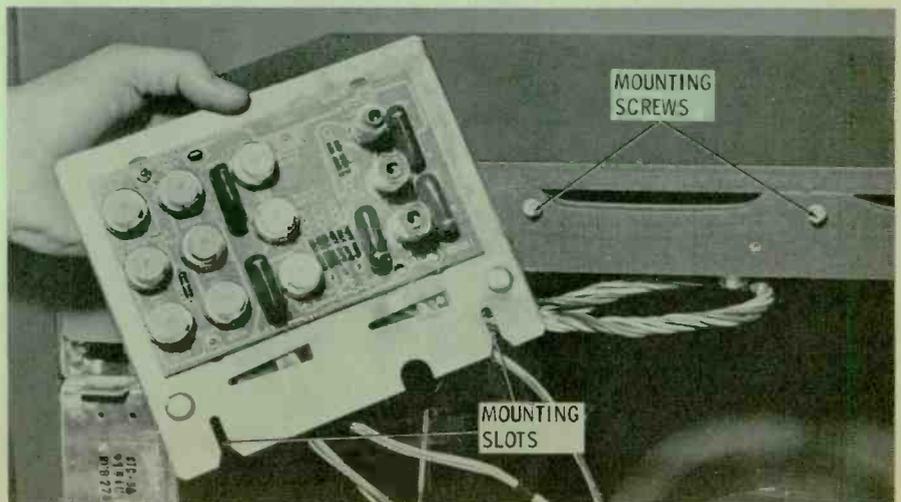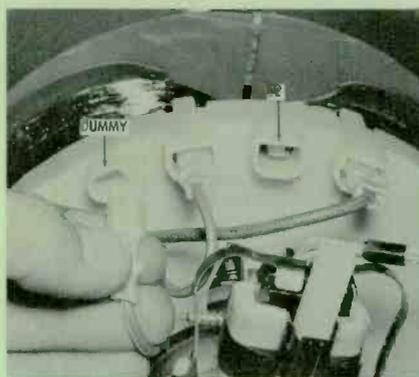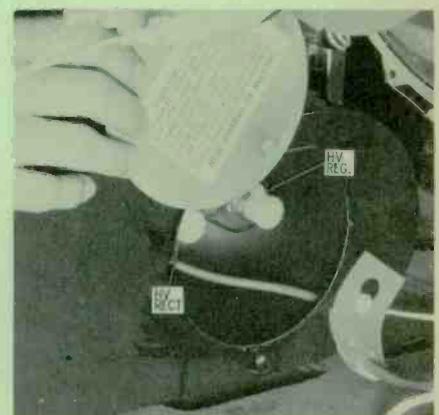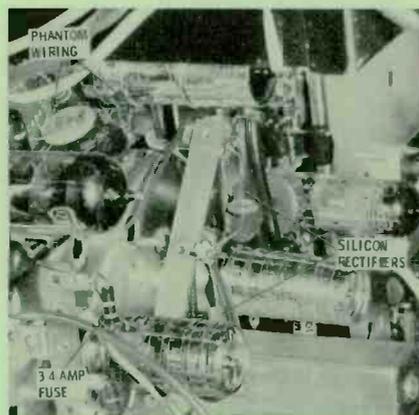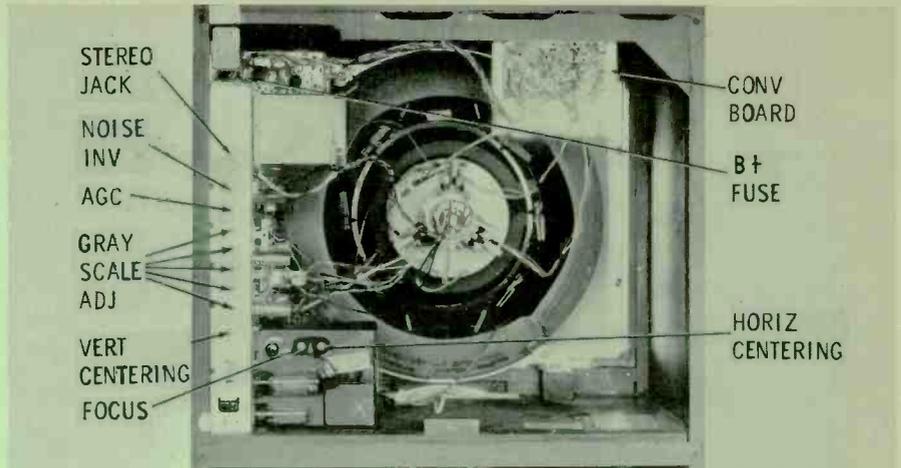

ASTATIC 77

DYNAMIC CARDIOID MICROPHONE

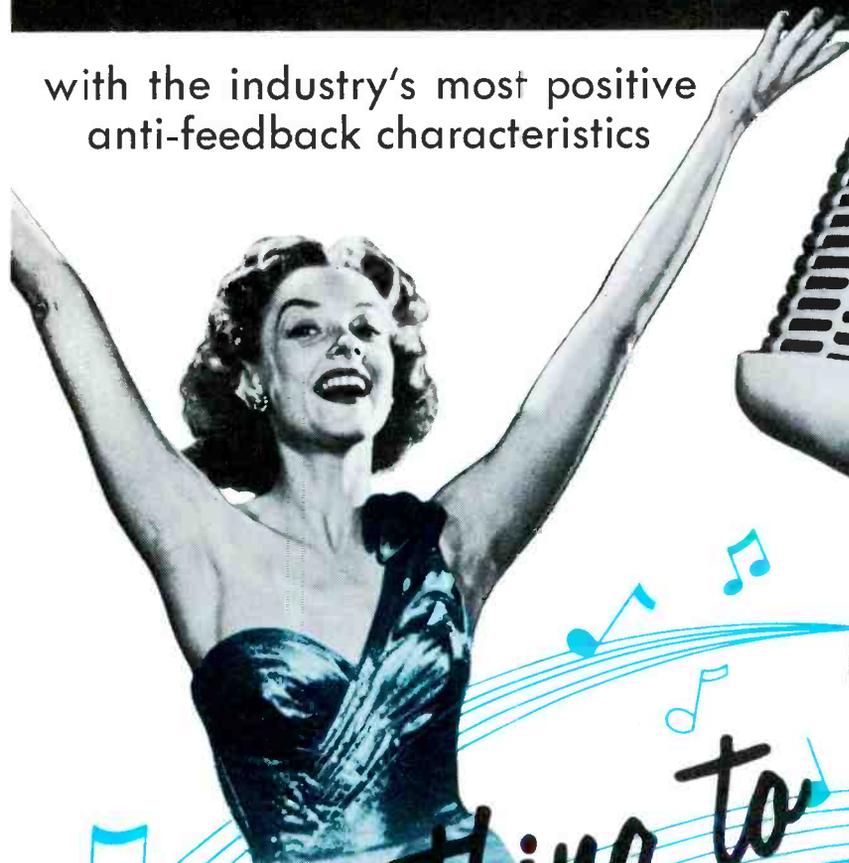with the industry's most positive anti-feedback characteristics



Something to Sing about

When you're looking for the ultimate in cardioid microphones, consider these advanced features of Astatic's Model 77 and see if you don't agree that no other manufacturer has SO MUCH TO SING ABOUT—the most positive anti-feedback characteristics ever achieved, -18 db; exclusive Mylar diaphragm that is pop-proof and blast-proof, retains like-new flex properties for more years; an exclusive sintered bronze method of acoustic phase shifting that creates the industry's top directional characteristics; -52 db output and exceptionally flat response through 30 to 15,000 cps.

Do one thing for your own satisfaction. On your next installation, make a direct comparison of the Astatic 77 with any other cardioid. We'll guarantee —when anyone mentions the word "cardioid" again, you'll sing the praises of this incomparable Astatic instrument.

LIST PRICES

Model 77 (Illustrated)

- Chrome Finish, \$82.50;
- Gold Finish, \$92.50.
- Model 77L (Head only),
- Chrome Finish, \$72.50;
- Gold Finish, \$82.50.
- Model G-77 (Complete with G-Stand),
- Chrome Finish, \$97.45.

**GO BY BRAND
—GO BUY ASTATIC**

THE **Astatic** CORPORATION, CONNEAUT, OHIO

IN CANADA: CANADIAN ASTATIC LIMITED, TORONTO, ONTARIO
EXPORT SALES: ROBURN AGENCIES INC. 431 GREENWICH ST., N. Y. 13, N. Y., U.S.A

**FROM What
You HEAR**

SINGING SOUNDS BETTER WHEN THERE'S AN ASTATIC MICROPHONE ABOUT

NEW DIFILM[®] BLACK BEAUTY[®] MOLDED CAPACITORS

BEAT THE HEAT AND HUMIDITY!

Now Sprague's new DIFILM BLACK BEAUTY MOLDED CAPACITORS have taken the steam out of heat and humidity problems. These capacitors are so good you can *boil 'em* for 24 hours without affecting their performance.


Unlike straight polyester film tubulars, these capacitors operate in a 105°C environment *without derating*.

And the heart of these new DIFILM capacitors can't be beat. It's a dual dielectric which *combines the best advantages of both Mylar* polyester film and the highest grade of paper dielectric*. A rock-hard solid impregnant fills every void and pinhole in the film.

Talk about *reliability!* . . . these capacitors have it. DIFILM capacitors are actually low cost versions of the Sprague capacitors now being used in every modern military missile. The basic reliability and outstanding performance of missile-type Sprague capacitors are all yours in this outstanding new development. Why take chances when you can get the best—DIFILM BLACK BEAUTY MOLDED TUBULARS . . . at regular prices.

For the complete DIFILM BLACK BEAUTY story, write for Bulletin M-759 to Sprague Products Company, 105 Marshall St., North Adams, Mass.

*DuPont trademark

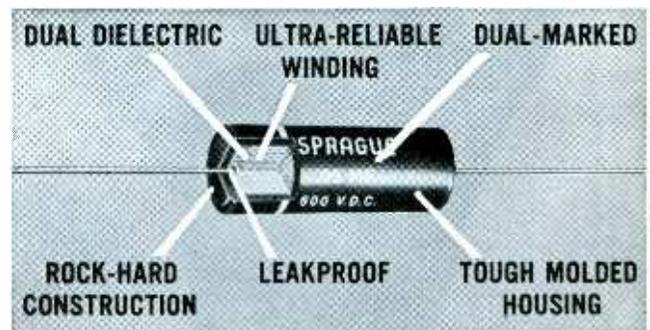

DIFILM BLACK BEAUTY CAPACITORS are now packed in reusable, rigid plastic Klee-Pak[®] boxes at no extra charge.

The major capacitor improvements come from

SPRAGUE[®]

world's largest capacitor manufacturer

SPRAGUE RESEARCH IS CONSTANTLY PRODUCING NEW AND BETTER CAPACITORS FOR YOU

publisher
Howard W. Sams

general manager
Mal Parks, Jr.

editor
Verne M. Ray

associate editors
Leslie D. Deane
Thomas A. Lesh
Calvin C. Young, Jr.

consulting editors
William E. Burke
Robert B. Dunham
George B. Mann
C. P. Oliphant
Paul C. Smith

art director
Don W. Bradley

advertising & editorial assistants
Georgeanna Caldwell
Paula Distelhorst
Monteen Johnson

production manager
Robert N. Rippy

circulation fulfillment
Pat Tidd, Mgr.
Ann Mathews, Ass't.
Constance McCawley, Ass't.

photography
Robert W. Reed

advertising sales offices
Midwestern
John Groce, PF REPORTER
2201 East 46th Street, Indianapolis 6, Ind.
Clifford 3-6441

Eastern
Cliff Landis
Corning Glass Building,
717 Fifth Ave., New York 22, N. Y.
MUrray Hill 8-6350

Western
The Maurice A. Kimball Co., Inc.
2550 Beverly Blvd., Los Angeles 57, Calif.
Dunkirk 8-6178; and 681 Market Street,
San Francisco 5, Calif. Exbrook 2-3365

Address all correspondence relating to circulation and editorial to PF REPORTER, 2201 East 46th Street, Indianapolis 6, Indiana



Copyright © 1959 by Howard W. Sams & Co., Inc. No part of the PF REPORTER may be reproduced without written permission. No patent liability is assumed with respect to use of information herein. Acceptance of advertising does not in any manner signify the products, policies and services so advertised have been approved, endorsed, or recommended by this magazine.



PF PHOTOFACT REPORTER®

including Electronic Servicing

VOLUME 9, No. 9

SEPTEMBER, 1959


CONTENTS

Previews of New Sets	1
In-the-home servicing data on four new sets.	
Video Speed Servicing	5
Trouble solutions for Admiral and Philco chassis.	
Letters to the Editor	16
Developing a Modus Operandi	24
Shop Talk—A basic method of operation for troubleshooting all types of TV circuits.	
Looking Over G.E.s 1960 Remote Unit	26
Servicing New Designs—A preview of the latest in TV remote controls and how it works.	
Selecting the Proper Scope Probe	28
How to determine which probe to use in viewing TV waveforms.	
Running Down AGC Trouble	34
Quicker Servicing—A case history report that may save you time and trouble on the very next job.	
Dollar & Sense Servicing	42
Crosshatch Marks Chroma Phase	44
Using a crosshatch generator to identify chroma demodulator phasing.	
Let's Talk About Vertical Sweep Circuits	48
The second half of a "meaty" servicing coverage.	
Short-Lived TV Tubes	54
How to put your finger on the real cause of repeated premature tube failures.	
Electronic Heater Circuits and How They Work	62
Servicing Industrial Electronics—Part 17	
Notes on Test Equipment	68
Lab reports on the use of Arkay VTVM, Jackson capacitor tester, and Seco transistor checker.	
Tips for Techs	74
The Troubleshooter	76
Product Report	85
Coming Next Month	86
Free Catalog & Literature Service	88

ABOUT THE COVER

Hi-ho, hi-ho, it's back to school we go . . . although Junior seems a little reluctant. Daddy's older and wiser, of course, and realizes the value of a good education. As a matter of fact, he's on his way to register, too—for an adult class that will better equip him to handle his servicing business.

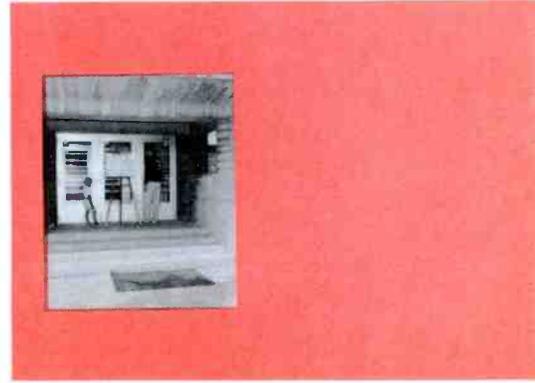As you can see from the later photo at right, Dad has been able to get his offspring to take the first step, although we have our doubts as to what his attendance record will be like.



mart service are using...



GET ARCO dp "5 PAKS" AT YOUR DISTRIBUTOR FROM THIS HANDY BLUE AND YELLOW MERCHANDISE DISPLAY RACK!

NOW AVAILABLE
IN THE HANDY ARCO



5 PAK

MOISTURE PROOF
TRANSPARENT BAG

Individually packed 5 dp
capacitors to a "5 Pak"



the revolutionary low cost quality capacitor
that puts an end to "CALL BACKS!"



Exclusive Features

- **MINIATURIZED**
50% Smaller than other brands
- **MOISTURE PROOF**
Designed to withstand 4 times more humidity than the best molded capacitors used in the past
- **CONSTANT HIGH TEMPERATURE OPERATION** at 110°C at full rated voltage
- **RELIABILITY** that meets computer and missile requirements
- **LONG TERM STABILITY**
no drift, no shift
- **ALL VALUES ±10% TOLERANCE**
- **PRINTED CIRCUIT and TRANSISTOR application**

SPECIFICATIONS	
VOLTAGE RATINGS:	100VDCW, 200VDCW, 400VDCW, 600VDCW, 1600VDCW,
INSULATION RESISTANCE:	@25°C.: 5000 megohm-microfarads or 100,000 megohms minimum, whichever is the lesser. @110°C.: 70 megohm-microfarads or 1400 megohms minimum, whichever is the lesser.
POWER FACTOR:	1.0% maximum at 1kc.
TEMPERATURE RANGE:	-55°C. to +110°C. with no voltage derating.
CAPACITANCE CHANGE VS. TEMPERATURE:	From 25°C. to -55°C. [- 9.0% max.] From 25°C. to +110°C. [+10.0% max.]
LONG TERM OPERATING STABILITY AT FULL RATED VOLTAGE AND RATED TEMPERATURE EXTREMES IS ±2% MAXIMUM.	



ARCO

electronics inc.

64 White St., New York 13, N. Y.

Branches: Dallas 19 • Los Angeles 35

technicians everywhere

ELMENCO



**DIPPED
MYLAR* - PAPER
CAPACITORS**

ARCO dp "5 PAKS" are available at your nearest distributor listed below:

ALABAMA
BIRMINGHAM—Mitchell Electronics Supply Co.
MOBILE—Forbes Electronic Dist., Inc.
MONTGOMERY—Stuart F. Graydon Co., Inc.
OPELIKE—Southern Electronics Corp.

ARIZONA
PHOENIX—Radio Specialties & Appliances
TUCSON—Inland Electronic Supply Co.

ARKANSAS
FORT SMITH—Carter Electronic Supply Co.
Wise TV & Radio Supply
NO. LITTLE ROCK—Lavender Radio & TV Supply Co.
PINE BLUFF—Lavender Radio & TV Supply, Inc.
SPRINGDALE—Springdale Radio & TV Supply
TEXARKANA—Lavender Radio & TV Supply, Inc.

CALIFORNIA
ALHAMBRA—Grossman & Reynolds
CULVER CITY—Electronic Trading Post
ENCINO—J. F. A. Associates
GLENDALE—Western Electronic Supply Corp.
INGLEWOOD—Grossman & Reynolds
LA MESA—La Mesa TV Supply Co.
LONG BEACH—Electronic Supply Co.
Kiesub Corporation
Mission Electronics Supply
Scott Radio Supply Inc.
LOS ANGELES—Atlas Radio & TV Parts Co.
Hamilton Electronics Supply Co.
Radio TV Supply Co.
Shelley Radio Co. Inc.
ONTARIO—Pomona Valley Electronics
PARAMOUNT—Elwyn W. Ley
SACRAMENTO—Faust & Co.
Nrcal Electronics
SAN DIEGO—Radio Parts Co.
SAN FRANCISCO—Edisco Electronic Dist. Co.
SAN JOSE—United Radio & TV Supply Co.
SANTA ANA—Hurley Electronics
SANTA MONICA—S. M. Radio
SUNNYVALE—Sunnyvale Electronics, Inc.
VAN NUYS—Capitol Electronics
Thrifty Electronic Supply Co.
Kiesub Corp.
WILMINGTON—Stratton Supply

COLORADO
COLORADO SPRINGS—D. & M. Electronics Supply
DENVER—Fistell's Electronics Supply
Inter-State Radio & Supply Co.

DELAWARE
WILMINGTON—Wholesale Electronic Supply

DISTRICT OF COLUMBIA
WASHINGTON, D. C.—Rucker Electronic Prods. Co.

FLORIDA
BRADENTON—Thurow Distributors, Inc.
CLEARWATER—Thurow Distributors, Inc.
COCOA—Thurow Distributors, Inc.
DAYTONA BEACH—Thurow Distributors, Inc.
FT. LAUDERDALE—Thurow Distributors, Inc.
Vance Baldwin, Inc.
FT. MYERS—Thurow Distributors, Inc.
FORT PIERCE—McNees Radio Supply, Inc.
JACKSONVILLE—Peard Electronics Supply Co.
Thurow Distributors, Inc.
LAKELAND—Thurow Distributors, Inc.
MIAMI—East Coast Radio & TV Co.
Herman Radio Supply Co.
Thurow Distributors, Inc.
Vance Baldwin, Inc.
ORLANDO—Radio Accessories Co.
Thurow Distributors, Inc.
PANAMA CITY—Thurow Distributors, Inc.
PENSACOLA—Thurow Distributors, Inc.

SARASOTA—Radio Accessories Co.
ST. PETERSBURG—Thurow Distributors, Inc.
TALLAHASSEE—Peard Electronics Supply Co.
Thurow Distributors, Inc.

TAMPA—Radio Accessories Co.
Thurow Distributors, Inc.

WEST PALM BEACH—Thurow Distributors, Inc.

GEORGIA
ATLANTA—Southeastern Radio Parts Co.
AUGUSTA—Prestwood Electronics Co., Inc.
MACON—Peard Electronics Supply Co.
SAVANNAH—Kings Appliance & Electronics

ILLINOIS
CHICAGO—Nationwide Radio Co.
Stolz-Wicks, Inc.
Walker-Jimieson, Inc.
MATTOON—Mattoon Radio & TV Supply Co.
PEORIA—Klaus Radio & Elec. Co.
ROCKFORD—J. & M. Radio & TV Supply

INDIANA
HAMMOND—Nationwide Radio Corp.
SOUTH BEND—Colfax Co., Inc.

KENTUCKY
LOUISVILLE—R & K Dist. Co.

LOUISIANA
LAFAYETTE—Lafayette Radio Equipment, Inc.
NEW ORLEANS—Bell Radio Supply Co.
Crescent Radio Supply, Inc.

MARYLAND
BALTIMORE—Kann-Ellert Electronics, Inc.
Revacto of Maryland, Inc.
COLLEGE PARK—Rucker Electronic Prods. Co.
HAGERSTOWN—Stoddard Supply Co.
SILVER SPRINGS—Rucker Electronic Prods. Co.

MASSACHUSETTS
BOSTON—O'Donnell Electronics Supply Co.
Yankee Electronics
LAWRENCE—Alco Electronics Mfg. Co.
LOWELL—Frank P. McCartin, Inc.
PEABODY—Tee-Vee Supply Co.

MICHIGAN
DEARBORN—Westside Radio Supply
MUSKEGON—Mutual Radio Supply Co.

NEW JERSEY
BERGENFIELD—County Dist. Co.
BLOOMFIELD—Variety Electronics Corp.
CAMDEN—General Radio Supply Co., Inc.
LONG BRANCH—Vi-Van Electronics, Inc.
UNION CITY—Pyramid Supply Co.

NEW MEXICO
ALBUQUERQUE—Tele-Radio Supply Co.
SANTA FE—A-1 Communications Supply Co.

NEW YORK
ALBANY—Boyers Electronic-Radio Dist. Corp.
BROOKLYN—Bay Electronics Distributors
Sam Buchman Dist. Co.
FLUSHING—Bay Electronics Distributors
NEWARK—Top Distributing Co.
SYRACUSE—Goldcrest Electronic Supply Co.
WHITE PLAINS—Melville Radio Corp.

NORTH CAROLINA
CHARLOTTE—Dixie Radio Supply Co., Inc.
GASTONIA—Dixie Radio Supply Co., Inc.
GOLDSBORO—Womack Electronics, Inc.
HICKORY—Industrial Electronics

OHIO
AKRON—Main TV Supply Co.
CLEVELAND—Radio & Electronics Parts Corp.
COLUMBUS—Ace Radio Supply, Inc.
DAYTON—The Stotts-Friedman Co.

TOLEDO—Lifetime Electronics

OKLAHOMA
MUSKOGEE—Sooner Radio & TV Supply
OKLAHOMA CITY—Radio Supply, Inc.

PENNSYLVANIA
ALLENTOWN—A. A. Peters, Inc.
BETHLEHEM—Buss Radio Elec. Supply
ELKINS PARK—A. G. Radio Parts Co.
HARRISBURG—D. & H. Distributing Co., Inc.
Electronic Wholesalers Inc.
Radio Distributing Co.
JOHNSTOWN—Cambria Equipment Co., Inc.
LANCASTER—George D. Barbey Co., Inc.
LEBANON—George D. Barbey Co., Inc.
NEW KENSINGTON—R. P. C. Electronics Co.
PHILADELPHIA—A. G. Radio Parts Co.
Almo Radio Co.
Raymond Rosen & Co., Inc.
POTTSTOWN—George D. Barbey Co., Inc.
POTTSVILLE—Moyer Electronic Supply Co.
READING—A. G. Radio Parts Co.
George D. Barbey Co., Inc.
ROCHESTER—Radio Parts Co.
SCRANTON—Fred P. Purcell
STATE COLLEGE—Alvo Electronics Dist., Inc.
UNIONTOWN—Radio Parts Co., Inc.
WEST YORK—York TV Supply Co.
WILLIAMSPORT—Alvo Electronics Dist., Inc.
Electric Appliance Dist., Inc.
YORK—Wholesale Radio Parts Co., Inc.

SOUTH CAROLINA
ANDERSON—Dixie Radio Supply, Inc.
COLUMBIA—Dixie Radio Supply, Inc.
FLORENCE—Dixie Radio Supply, Inc.
GREENVILLE—Dixie Radio Supply, Inc.
SPARTANSBURG—Dixie Radio Supply, Inc.

TEXAS
ABILENE—Radio Communications Supply Co.
AUSTIN—Standard Radio Supply
DALLAS—All-State Distributing Co.
FORT WORTH—Electronic Equipment Co., Inc.
United Electronic Supply Co.
HOUSTON—Angie Radio & TV Supply Co.
City Electronic Supply
LUBBOCK—Amarillo Hardware Co.
PORT ARTHUR—Diehl Radio & TV Supply
SAN ANTONIO—Olsen Radio Supply
Perry Shankle Co.
Radio & TV Parts Co.
WICHITA FALLS—Gose Radio Supply

UTAH
SALT LAKE CITY—Flint Distributing Co.
Strevell-Paterson Hardware Co.

VIRGINIA
ARLINGTON—Rucker Electronic Prods. Co.
DANVILLE—Womack Radio Supply Co., Inc.
FALLS CHURCH—Television Craftsman Wholesalers
LYNCHBURG—Eastern Electric Co.
NORFOLK—Southern Television Corp.
RICHMOND—E. A. Holsten, Inc.
ROANOKE—Dixie Appliance Co.
E. A. Holsten, Inc.

WEST VIRGINIA
WHEELING—Radio Parts Co.

WISCONSIN
FOND DU LAC—Harris Radio Corp.
KENOSHA—Chester Electronics Supply Co.
MILWAUKEE—A & F Electro Mart
Marsh Radio Supply Co.

HAWAII
HONOLULU—Radio Television Corp.

*DuPont Trademark


ARCO ELECTRONICS INC. 64 White Street, New York 13, New York

GET BEHIND THE

SYLVANIA

\$2. Combination

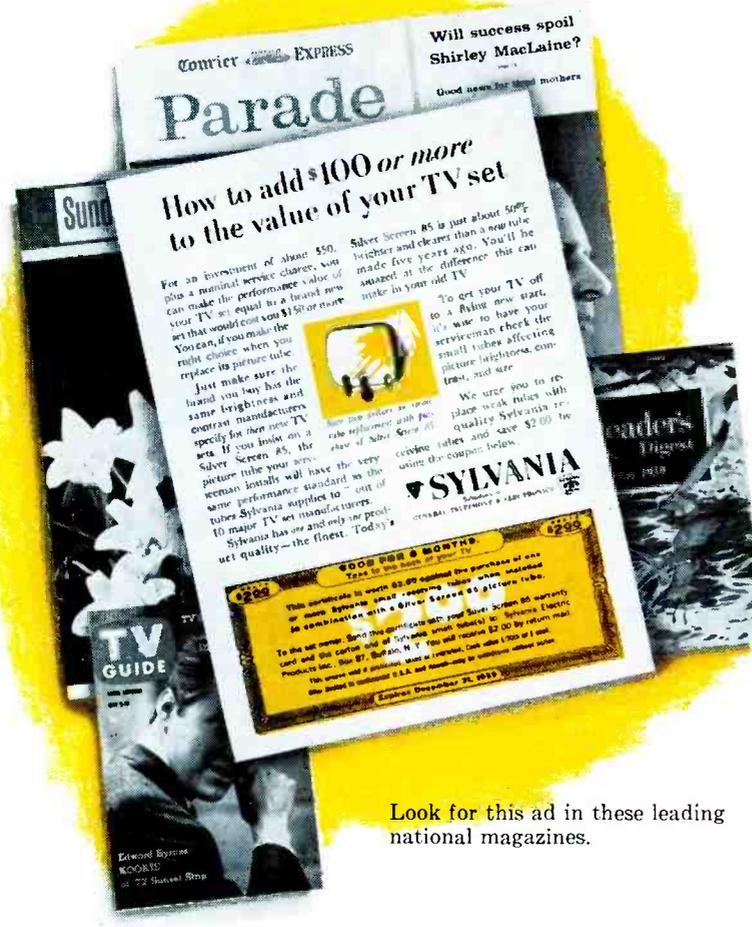**America's biggest magazines deliver
this business-building offer to over
100 million readers!**




On June 20th Sylvania launched the dramatic combination coupon offer appearing in America's biggest weekly magazine, *TV Guide*, and America's biggest monthly magazine, *Reader's Digest*—plus *Sunday* and *Parade* newspaper supplement magazines.

Your Service shares the spotlight with top-quality Sylvania picture tubes and receiving tubes in a three-point program to make your customer's old TV set *better than when it was new*.

Month after month, more set owners will be saving the \$2.00 coupon. Many will attach it to the back of their TV set so it's there for you to see.

You can identify yourself with this program by featuring Silver Screen 85 and Sylvania receiving tubes. Get behind the biggest, most practical, business-building offer ever made to the Service industry.

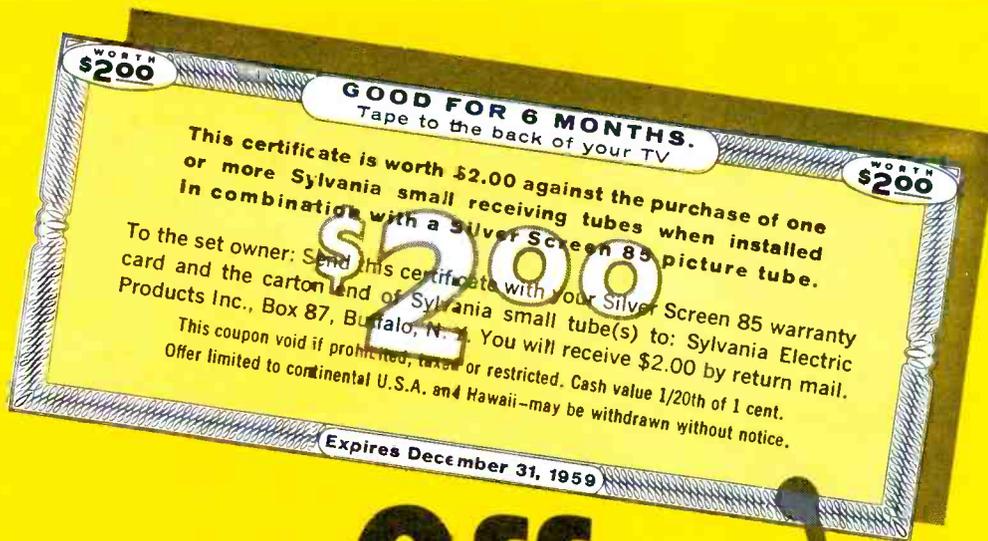Look for this ad in these leading national magazines.



Coupon Offer

Sells your service and Sylvania receiving tubes in combination with every Silver Screen 85 you install

Here's an action-packed offer that can add an average of \$3.00 to \$6.00 in receiving tube business every time you install a Silver Screen 85 picture tube.

Sylvania urges your customers to have their receiving tubes checked to make sure they get full performance from their new Silver Screen 85. And, to emphasize the importance of replacing weak tubes, Sylvania offers to pay \$2.00 toward the cost of Sylvania receiving tubes installed in combination with a Silver Screen 85.

Your customers mail the \$2.00 certificate directly to Sylvania with the picture-tube warranty card and receiving-tube carton end. Nothing for you to sign or send.

Stock up on Sylvania. Be prepared for greater-than-ever consumer demand for America's Number One picture tube and receiving tubes.



SYLVANIA
 Subsidiary of
 GENERAL TELEPHONE & ELECTRONICS




Introducing ATR CUSTOMIZED Karadio



Can be installed
in dash or under
dash as desired!

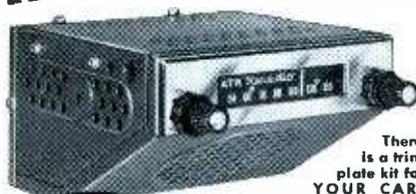for
small import cars
and
compact U.S. cars




There
is a trim
plate kit for
YOUR CAR!

ATR CUSTOMIZED Karadio

• VIBRATOR-OPERATED with Tone Control

The ATR Customized Karadio is a compact, new, self-contained airplane-styled radio for small import and compact American cars. This economical unit is perfect for all small cars because it can be easily and inexpensively installed in-dash or under-dash on most any make or model automobile—and its powerful 8-tube performance provides remarkable freedom from engine, static, and road noises. ATR Karadios are built to look and fit like original equipment with sleek, modern styling and solid, single-unit construction. They offer many customized features and provide highest quality fidelity—yet cost far less than comparably designed units. The ATR Customized Karadio comes complete with speaker and ready to install... and is the ideal way to add fun and value to your small import or American automobile!

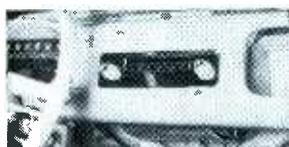

ATR KARADIO
... is ideal
for small import
cars or com-
pact American
cars! Unit is
completely self-contained—extremely compact!
Can be mounted in-dash or under-dash—where-
ever space permits! For 6 volt or 12 volt!

SEE YOUR JOBBER OR WRITE FACTORY

• "A" Battery Eliminators • DC-AC Inverters • Auto Radio Vibrators



AMERICAN TELEVISION & RADIO CO.
Quality Products Since 1931
SAINT PAUL 1, MINNESOTA, U. S. A.

Letters to the EDITOR

Dear Editor:

Since we have to stand for TV advertising as a necessary evil, the FCC should not permit TV stations to increase their audio power while transmitting commercials, as they often seem to do.

THOMAS LANE

Los Angeles, Calif.

Actually, they are not increasing their RF carrier output; the FCC sees to it that this is rigidly held to a certain maximum value. Here's what is probably happening: During certain types of program material — for example, old movies — somewhat less than 100% modulation may be impressed on the sound carrier. The modulation level suddenly jumps up to virtually 100% when a commercial comes along, thus giving the effect of a power increase. As far as we know, there are no regulations to prohibit this sort of operation. Unfortunately, too, there seems to be nothing you can do about the fact that an announcer's strident voice is much more irritating than an equally loud musical score or occasional POW! of a six-shooter.—Ed.

Dear Editor:

We have a Schaub radio which has two tubes, a UCH71 and a UEL71. We would like to restore it, but are having trouble finding tube replacements or interchanges. Could you be of any help?

GENE'S TV & RADIO

Eldridge, Iowa

None of our reference sources list any American tubes which bear even a remote resemblance to either of these two European types. Their basic specifications, determined from the type numbers, will give you some idea of what you're up against.

Both tubes are dual-section units with 8-pin miniature sockets and 100-ma heaters. The UCH71 is a heptode-triode, probably being used as a converter and 1F stage. The UEL71 is a combination of a tetrode and a power pentode, presumably employed in a two-stage audio section.

I doubt if these tubes are being regularly imported into the United States, but you might be able to order them from Europe. This is just about your only alternative other than extensively rebuilding the radio. We're sorry to break the bad news, but this sort of situation often arises when you're dealing with older-model or seldom-imported foreign equipment.—Ed.

Dear Editor:

I have just finished reading the item about the tip saver for miniature soldering irons (page 36, May issue). It's a good idea; however, I notice that Mr. Farmer used a double-pole, double-throw switch in the circuit. Wouldn't it work

equally well with only a single-pole, single-throw unit, as shown in the attached diagram?

JOHN FRENO, JR.

Brooklyn, N. Y.

Yep.—Ed.

Dear Editor:

Is there a practical way to cut down tube-caddy inventory of similar tube types (for example, the 6BK7, 6BQ7A, 6BZ8, 6BC8, 6BS8, etc.)?

R. G. MALCOM

Tulsa, Okla.

The experts say not. Top servicemen are trying to maintain as complete a tube stock as possible, even though this means using TWO caddies—one with common types to bring into the house, the other with rarer types to leave in the truck.

The trouble with cutting down on tube inventory is that substitute types are different enough from the originals to be ineffective as permanent replacements in a great percentage of cases. They sometimes fail to give sure-fire results in substitution tests, and they give very little insurance against callbacks.

But, as we all know, the problems of maintaining a really complete tube stock have become just about insurmountable. You're bound to be caught short every now and then, and a substitute tube is far better than none in such cases. For this reason, we periodically present features such as our Tube Substitution Guide. The substitutes we recommend are intended to be temporary, however. When you must install any tube other than the original type (or its improved version), it's good business to go back and install the right type as soon as practical.—Ed.

Dear Editor:

With the advent of hi-fi, I am getting into difficulty with the portable radio fans on the question of frequency response and tone quality. What can we expect from these \$80 transistorized jobs?

C. E. LIVINGWAY

New Baltimore, Mich.

Even though these radios are quite expensive, they have room for only a small speaker (usually from 2½" to 3½" in diameter). In addition, the power output available for driving the speaker is on the order of milliwatts. These limitations prevent you from getting any semblance of high fidelity out of a compact transistorized portable.

Actually, this isn't what they are designed to do. Essentially, they are a "go anywhere" type of radio, intended to provide the user with music of a sort as well as sports and news programs when away from a source of AC power. When used as such, they are excellent; however, it's unreasonable to compare them with high-fidelity sound equipment.—Ed.

Dear Editor:

In Figs. 7 and 8 of the "P's and Q's of Transistors" article (page 62 of the July issue), there seems to be a mix-up in the

• Please turn to page 22



**Really dresses up
your service work**

Reliable Tung-Sol tubes add real class to every service job — radio, tv, or hi-fi. Made to set manufacturers most exacting specifications, Tung-Sol Tubes are best for all replacements. Reduce your callbacks to new lows and keep your profitable new business rolling in high style. Tung-Sol Electric Inc., Newark 4, N. J.

Tell your jobber you'd rather have

ts TUNG-SOL®

Blue Chip Quality TUBES • TRANSISTORS • DIODES

September, 1959/PF REPORTER 17

**IRC
CARBON
COMPOSITION
RESISTOR
HANDY-PAKS ARE
TAKING AMERICA
BY STORM!**




NOW this exciting

HANDY-

is ready to keep

NEW!

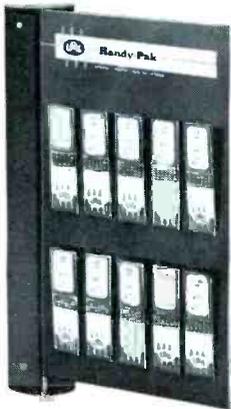

RESIST-O-PANEL

Easy-to-select, easy-to-inventory swing panel takes no bench space at all!

Wonderful space saver! Visible resistor stock on handy swing panel attaches to wall . . . can be used singly or in sets. All-metal—7" wide x 12 1/4" high—slotted to hold Handy-Paks—wall brackets included. Contains the 10 most popular resistor values, with room for 10 more Handy-Paks on back of panel. FREE with any of 4 popular assortments.

Dealer Net

Assortment # 64	60 1/2-watt, 10% resistors, 10 values	\$7.20
Assortment # 68	40 1-watt, 10% resistors, 10 values	7.20
Assortment # 72	60 1/2-watt, 5% resistors, 10 values	14.40
Assortment # 76	40 1-watt, 5% resistors, 10 values	14.40

NEW!



RESIST-O-ROUND

Unique revolving stock kit keeps IRC Handy-Paks at your fingertips!

Instant visual inventory within easy reach . . . in minimum bench space. Two tiers of Handy-Paks spin at the flick of a finger for fast, easy selection. This revolutionary metal kit is only 7" diameter, 6 1/4" high. Includes the 20 most popular resistor values. FREE with any of 4 assortments.

Dealer Net

Assortment # 65	120 1/2-watt, 10% resistors, 20 values	\$14.40
Assortment # 69	80 1-watt, 10% resistors, 20 values	14.40
Assortment # 73	120 1/2-watt, 5% resistors, 20 values	28.80
Assortment # 77	80 1-watt, 5% resistors, 20 values	28.80

MORE IRC HANDY-PAK STOCKERS FAVORED BY SERVICEMEN EVERYWHERE

Included
FREE
with any of 5
Handy-Pak stock
assortments.



IRC RESIST-O-PEDIA

Attractive hardback binder has 3-ring "fingered" inserts for Handy-Paks. Indexed stock saves searching . . . speeds servicing. Identification always visible. 9" x 8 1/4" x 2 3/4". Five popular assortments.

Assort. No.	No. of Resistors	Wattage	No. of Values	Tolerance	Dealer Net
44	462	1/2	77	10%	\$55.44
48	308	1	77	10%	55.44
51	195	2	65	10%	46.80
59	462	1/2	77	5%	110.88
63	308	1	77	5%	110.88



FREE
with any of
4 assortments.

IRC RESIST-O-CHEST

Ends "elgar box confusion". All-metal covered file in 10 Handy-Pak assortments. Compact 5 1/2" x 3 3/8" x 6 1/4" size . . . takes little bench space. Identification clearly visible.

Assort. No.	No. of Resistors	Wattage	No. of Values	Tolerance	Dealer Net
42	204	1/2	34	10%	\$24.48
43	462	1/2	77	10%	55.44
46	136	1	34	10%	24.48
47	308	1	77	10%	55.44
49	102	2	34	10%	24.48
50	195	2	65	10%	46.80
57	204	1/2	34	5%	48.96
58	462	1/2	77	5%	110.88
61	136	1	34	5%	48.96
62	308	1	77	5%	110.88



Included
FREE with
any of these
10 assortments.

IRC RESIST-O-CADDY

Ideal for in-home servicing. Plastic pouch folds to 6 3/4" x 3 3/8" x 1 1/2" . . . fits in tube caddy or tool chest. Individual Handy-Pak pockets.

Assort. No.	No. of Resistors	Wattage	No. of Values	Tolerance	Dealer Net
41	120	1/2	20	10%	\$14.40
45	80	1	20	10%	14.40
56	120	1/2	20	5%	28.80
60	80	1	20	5%	28.80

quartet of brand new

PAK* RESISTOR KITS

your resistor stocks at your fingertips

*Patent Pending

NEW!

RESIST-O-BIN



Easy-to-use
IRC
Handy-Pak
Stocker
with 36
identified
compartments!

Just what busy servicemen need for compact, convenient stocking of Handy-Paks. 36 compartments in recessed tiers are identified for easy access to resistors . . . and quick, accurate inventory. All-metal—6¾" wide x 4¼" deep x 4½" high. FREE with any of 4 assortments.

	Dealer Net	
Assortment # 66	204 ½-watt, 10% resistors, 34 values	\$24.48
Assortment # 70	136 1-watt, 10% resistors, 34 values	24.48
Assortment # 74	204 ½-watt, 5% resistors, 34 values	48.96
Assortment # 78	136 1-watt, 5% resistors, 34 values	48.96

NEW!

RESIST-O-RACK



Orderly, neat
IRC
Handy-Pak
file for
complete stocks
of resistors!

The perfect answer to maintaining an orderly, complete inventory of Handy-Paks. Individual compartments separate stock by resistance values . . . with identification always visible. Metal rack is 11¾" wide x 5½" deep x 8" high. Key-hole slotted for wall mounting, if desired. FREE with any of 4 assortments.

	Dealer Net	
Assortment # 67	462 ½-watt, 10% resistors, 77 values	\$55.44
Assortment # 71	308 1-watt, 10% resistors, 77 values	55.44
Assortment # 75	462 ½-watt, 5% resistors, 77 values	110.88
Assortment # 79	308 1-watt, 5% resistors, 77 values	110.88



3 TYPES

½ watt, 1 watt
and 2 watts*

10% tolerance **72¢** ea.
5% tolerance \$1.44 each
Dealer Net

Each IRC Handy-Pak contains several carbon composition resistors of one type and resistance value . . . to save you unnecessary shopping. Three types include: 6 ½-watt resistors; 4 1-watt resistors; 3 2-watt resistors.
*2-watt Handy-Paks available in 10% tolerance only.

IRC HANDY-PAKS

Smartest idea yet for
packaging carbon
composition resistors!

Servicemen from coast to coast praise IRC Handy-Paks as the neatest, most compact, most convenient resistor package in the industry. Resistance value and power rating are clearly visible on every Handy-Pak. They're handier to use . . . open at either end; close to hold remaining resistors. IRC Handy-Paks keep leads straight; resistors are always factory-clean.

Choose the
Handy-Pak deal
that suits you best!

Order today from your
IRC Distributor!



INTERNATIONAL RESISTANCE CO.

414 N. 13th St., Philadelphia 8, Pa.
In Canada: International Resistance Co., Ltd.
Toronto, Licensee

**SELL
THE ANTENNA LINE
THAT HELPS YOU
SELL!**

Cash in on . . .

Winegard's

... the Industry's Greatest

SEE the big-name TV stars such as ★ Ward Bond of "Wagon Train" ★ Walter Brennan of "The Real McCoy's" and other TV stars promoting Winegard Color'Ceptors!

SEE Winegard's advertising in a non-stop, big-space schedule in LIFE, Better Homes & Gardens, others, **ALL YEAR LONG!**



GET FREE PROFIT-MAKING SALES AIDS

GET Winegard's new "PROMOTION BUCKS"! Given to you free with every Color'Ceptor you buy. You use them for getting your own choice of the finest sales promotion aids anyone has ever offered — knock-out sales helps that hitch your business to the giant national sweep of Winegard's **BIG TV SHOW TIME!**

Sell the Winegard Color'Ceptor, the only antenna that's GUARANTEED to give your customers the BEST reception — In the rare event, a customer of yours is not satisfied — Winegard will refund the list price of the antenna and YOU KEEP YOUR FULL PROFIT.

Talk to your Distributor or send coupon for the whole story.
FEATURE THE LEADER AND BE ONE!



SEND THIS COUPON TODAY!

WINEGARD CO.
3009-9 Scotten, Burlington, Iowa

- RUSH full color brochure showing Winegard's new antenna dealer sales aids . . . and tell me how I can get them free!
- Send literature on Winegard's complete line of FM and TV antennas.

FIRM NAME _____

ADDRESS _____



Winegard Co.

3009-9 Scotten, Burlington, Iowa

As Advertised in

OUT WHERE THE SALES BEGIN



Color'Ceptor full-color mailing piece and full-color postcards for your direct mail program.



Special window deals.




DEALER'S NAME & ADDRESS GO HERE

Giant 6 foot 3-color metal road sign imprinted with your name.



Year-round big-space national advertising featuring big name TV stars.

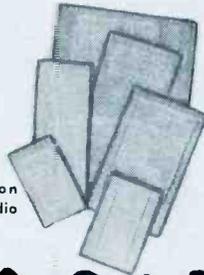Unlimited 50-50 co-op on local newspaper and radio advertising.



For best TV reception Winegard Gold Antennas

Big gold balloons for the kiddies.

BIG TV SHOW TIME!

All-Out Antenna Profit Drive!

INSIDE YOUR STORE



Colorful window streamers.




"Antenna Specialists" Shirt Emblems.



Attractive silk wall banners.



Antenna check-up sheets.

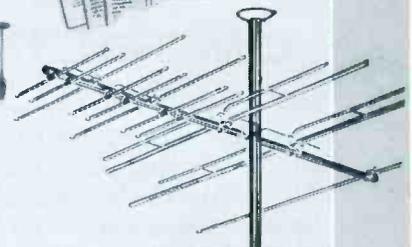

Gold anodized sample to hand out on service calls.



Illuminated plastic window sign.

New Color'Ceptor display with gold anodized mast.



OUTSIDE YOUR STORE

Eye-catching metal flange sign.



Special truck decals.



Hanging store front sign imprinted with your name.

ALL THESE SALES AIDS FREE - Ask Your Distributor



**"IT'S A WEBSTER CARTRIDGE, SIR
— EVEN BOWSER
CAN TELL THE DIFFERENCE"**

Well... it only goes to prove Websters give customers a lot more than they expect from a phonograph cartridge. You can tell a convincing performance story — no need to get technical either. Take the Webster Stereo-Ceramic, for example. It plays the new stereo discs with exceptional brilliance and depth — standard LP's and 78's with higher fidelity than ever before! And, that's just one... all Webster cartridges are star performers. Recommend and install them every time. It pays!



**look for it at your jobber —
NEW WEBSTER SERVICE CENTER**

When you see this modern cartridge merchandiser, you know you'll get fast, efficient service. Quick-reference chart assures accurate replacement for nearly every phono cartridge.

**ELECTRONICS DIVISION
WEBSTER ELECTRIC**
our **50**th year **RACINE · WIS**

franklin adv. Y-137

LETTERS

(Continued from page 16)

transistor symbols — or is it in the "NPN" and "PNP" labels on the schematics?

LYNN D. PEPPERMAN

General Electric Co.
Utica, N. Y.

In the second part of each figure, the arrow symbol for the emitter of the transistor was inadvertently turned end for end when the schematics were drawn. All the labels and voltage readings on these illustrations are correct.—Ed.

Dear Editor:

The mixed-up *Video Speed Servicing* in the June issue was an unexpected help to me. I was working on an Admiral Model C21-E2 with an intermittent video overload and loss of sync. While taking a break after a long bench session, I happened to glance at *Speed Servicing*; noticing the error, I decided to unscramble the cards. The words on the ZE 15B20-5 card seemed familiar, and it dawned on me that here was the same trouble I had in the Admiral. I resoldered the ground connection on its horizontal output transformer, and my problem was solved.

If it hadn't been for the mix-up, I probably would not have noticed the similarity in symptoms; so I would have wasted a good deal of time checking in the wrong places. To the editor I say, "May you edit for a long time to come."

EDWARD W. ATKINSON

Detroit, Mich.

Wish the publisher felt the same way. In case you missed out, we're still offering corrected reprints for those who request them. Also, Volume 3 of "*Video Speed Servicing*" is now available from your distributor.—Ed.

Dear Editor:

As an ardent reader of and subscriber to *PF REPORTER*, I have been meaning for some time to write and thank you for giving TV servicemen such a wonderful magazine. I find it good not only for filling in the gaps left open by the TV servicing course I took, but also for keeping up to date on the newest things in electronics. It certainly is worth every penny of the subscription cost — and much more. You perform a real service for the industry, and I (for one) surely do appreciate it.

TONY ACAR

Tulsa, Okla.

Dear Editor:

We appreciate your putting the proper *PHOTOFACT* Folder number on each *Video Speed Servicing* sheet, since we catalog all information about a particular TV or radio chassis under the good old "PF" number.

JUNIUS D. DEBONIS

East Hartford, Conn.

This is just one of several features we've recently added to *VSS* to make it more useful. By the way, have you noticed that component numbers referred to in the *Speed Servicing* sheets correspond to those listed in *PHOTOFACT*?—Ed.

Sign up now

The industry's only national program for quality independent service dealers

Finally, one company, Raytheon, gives you the kind of program you've asked for — the *new* Raytheon Bonded Dealer Program. It's the logical way, the *only* way, for *quality independent dealers* to unite into one strong network. It's the plan that builds customer confidence in *your* service, that builds repeat business for *you*.

Raytheon's ALL-STAR sales team will work for you all year 'round, telling families in your area about your Bonded Service. Join the Raytheon Bonded Dealer Program now, as *your* answer to increased profit.

Here's what you get: Free 90-day Repair Bonds

- Complete local back-up program
- National ads with Dealer Listings
- Free merchandising kit

Mail this coupon today



Mr. William Grey, Dept. 241,
Raytheon Company, 55 Chapel St., Newton 58, Mass.

Yes—I'm interested in taking part in the nationally advertised Raytheon Bonded Dealer Program. I understand that there are no dues or fees involved. I am a full-time, independent TV-Radio service dealer.

Firm Name: _____

Business Address: _____

City: _____ Zone: _____ State: _____

Telephone No.: _____

Your Signature and Title: _____

COMMON TV TROUBLES AND THEIR CAUSES

POSSIBLE DEFECT LOCATION SYMPTOM	TUNER	VIDEO IF	VIDEO DET & AMPS	SOUND IF	FM DET	AUDIO	AGC	CRT CIRCUITS	CRT COMPONENTS	SYNC SYSTEM	VERT DEFL. SYSTEM	HORIZ DEFL. SYSTEM	LOW VOLTAGE POWER SUPPLY	HIGH VOLTAGE POWER SUPPLY
SOUND OK, NO RASTER								✓	✓			✓		✓
PIX OK, NO SOUND				✓	✓	✓								
SOUND OK, NO PIX, RASTER OK			✓											
(SOUND NO) PIX RASTER													✓	
NO SOUND, NO PIX, RASTER OK	✓	✓	✓				✓							
PIX OK, DIST. SOUND		ALGN ✓		✓	✓	✓								
SOUND OK, PIX DISTORTED		ALGN ✓	✓				✓			✓	✓	✓		
PIX FOLDED OVER TOP OR BOTTOM											✓			
PIX NON-LINEAR VERT											✓			
PIX NON-LINEAR HORIZ												✓		
PIX FOLDED OVER HORIZ												✓		
HORIZ LINE											✓			
VERT KEYSTONING									✓					
HORIZ KEYSTONING									✓					
NO VERT SYNC										✓	✓			
NO HORIZ SYNC										✓		✓		
NO VERT OR HORIZ SYNC										✓				
SHADOWS ON EDGE OF RASTER								✓	✓					
AUDIO BUZZ		ALGN ✓		✓	✓									
BEND OR HOOK IN PIX	✓	✓	✓				✓			✓		✓		
BLOOMING								✓						✓
CORONA														✓
HORIZ PULLING		✓					✓			✓		✓		
INSUFFICIENT HEIGHT											✓		✓	
INSUFFICIENT WIDTH												✓	✓	
NEGATIVE PIX	✓	✓	✓				✓	✓						
WEAK PIX (LOW CONTRAST)	✓	✓	✓				✓	✓						
POOR FOCUS								✓	✓					✓
PIX SNOWY	✓						✓							
VERT RIPPLES IN PIX									✓			✓		
PINCUSHION EFFECT									✓					

Developing a MODUS OPERANDI

Television receivers, even though simplified to the point where they require only 13 tubes to produce both picture and sound, are still complex mechanisms. When something does go wrong with a television receiver, there are a host of circuits to consider; and it is the rare individual, no matter how experienced he may be, who can unfailingly put his finger on the trouble right away.

Is there an orderly troubleshooting process one can follow to save time and temper — a process that can be applied to all sets irrespective of the number of tubes they contain, the types of circuits they utilize, or the symptoms they display?

The answer to this question is an unqualified *yes*, and yet it is surprising how few servicemen (experienced or otherwise) consistently attack each servicing problem by following a systematic procedure. Most men, when you examine the way they operate, employ a fairly haphazard approach — perhaps using several proved shortcuts, but aside from these, generally improvising as they go along. If these men would add a systematic procedure to the experience which they possess, they would be pleasantly surprised at how much quicker they could proceed with their analysis and discover the trouble.

The goal of this article (and those to follow) is to establish a general *modus operandi*, or a servicing approach which can be applied in all instances to all types of receivers,

irrespective of the symptoms they exhibit. As the procedure unfolds, it will be seen to be quite flexible, enabling you to modify the technique as required. At all times, however, the over-all approach will remain the same.

As a start, let's assume a defective set is called to your attention, either in the home or in the shop. What do you do first? Begin by obtaining as much information as you can from the owner of the set—even before turning it on. Find out what peculiar trouble symptoms resulted in the service call. Here are some important points to check:

When did the symptoms first appear? Did they develop gradually, or was the change abrupt?

Has the set ever acted this way before?

Does this trouble occur on all channels or only one?

Is there any particular time of day when this trouble occurs, or is it always present?

This is an indication of the type of information that will assist you in cutting down on service time. Once you know the history and background leading up to the trouble, the next step is to place the set in operation and note the symptoms firsthand.

Symptoms which may appear in any television receiver can be grouped into two categories—those readily identifiable by the type of picture and/or sound they produce, and those which do not give any initial clear-cut clue as to the loca-

tion of the components causing them. Let us discuss the identifiable symptoms first, because the operating procedure we will develop in tracking down these troubles can then be expanded to include those that are more obscure.

An identifiable trouble is one which will enable the serviceman to proceed directly to either the defective component or the section of the receiver containing the component. For example, the picture may come through sharp and clear—but sound may be absent. In this case, there is obviously no reason to check through the RF or IF sections of the video system or the video amplifiers themselves. Attention should be concentrated on the sound system, from the take-off point to the loudspeaker. Another easily identifiable difficulty is the similar but opposite case where the sound comes through clearly, but no picture is obtained. A raster, however, is present. Here again, it is generally best to begin checking the circuits between the sound take-off point and the picture tube. Initially, there would be no reason to go into the RF or video IF stages.

Other easily identifiable symptoms are those which produce fairly characteristic picture distortions. In Fig. 1, for example, the picture is vertically keystoneed, a condition generally attributed to one or more shorted turns in the vertical windings of the deflection yoke. A comparable difficulty in the horizon-

• Please turn to page 83

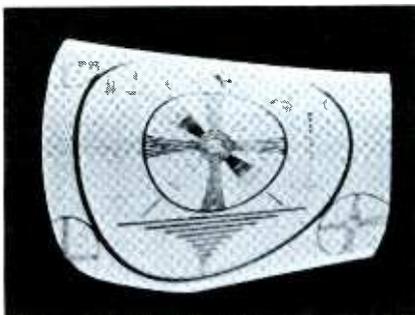


Fig. 1. A raster with unequal sides is due to shorted vertical yoke windings.



Fig. 2. When raster width is nonlinear, suspect a shorted horizontal yoke.

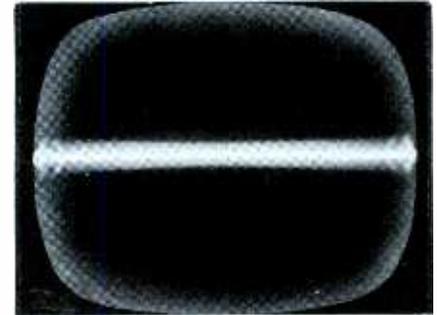



Fig. 3. A thin horizontal line indicates trouble in the vertical sweep system.

Looking Over

G.E.'s 1960

REMOTE-CONTROL UNIT

by Thomas A. Lesh

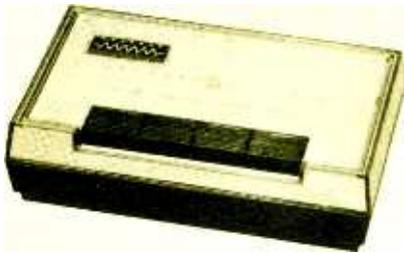

Remember when Studebaker first introduced an automatic shift for their cars? They must have thought enough different kinds of “---omatics” and “Power---s” were already on the market, for they christened their product just plain “Studebaker Automatic Transmission.”

General Electric apparently followed a similar line of reasoning in choosing a name for their new wireless remote control for TV sets. This unit, which is making its first appearance this fall in the U4 and M5 chassis, is called simply the “G-E Wireless Remote Control System.”

While this new device has some characteristics in common with other types of wireless remote units, it also employs several design features not previously used in the TV field. Basic specifications of the G-E system are as follows:

Medium of transmission: Radio waves (RF).

Operating frequency: 322.7 kc, modulated by four different audio frequencies corresponding to the four push buttons on the transmitter case.

Control functions and frequencies: Receiver on-off, 405 cps; channel-selector, 375 cps; reduce volume, 345 cps; increase volume, 315 cps.

Transmitter features: One 2N319 PNP transistor operating as a self-modulating RF oscillator; 9-volt mercury battery.

Receiver features: Movable ferrite-core antenna; two tubes (6EW6 and 6EA8); self-contained half-wave B+ rectifier using a germanium diode; a total of six relays to perform control functions.

Since the control receivers used in other types of four-button wireless remote systems generally have from six to eight tubes, you may be wondering how the G-E receiver can operate with only two tubes. Here's the answer: It doesn't have a separate electronic circuit for each

relay-control function, as do most other remote receivers. All control signals are fed through a single channel consisting of an RF amplifier, a common detector stage, and one audio amplifier. The different signals are separated from each other in the plate circuit of the final stage by means of a frequency-sensitive *reed relay*. In place of ordinary contacts, this unit has four flexible reeds which are mechanically resonant to the audio frequencies generated by the remote transmitter. Each incoming control signal produces an alternating magnetic field in the relay coil, thus causing one of the reeds to vibrate. When this occurs, the reed intermittently touches a stationary contact and completes a low-current circuit through the coil of another relay. The contacts of this secondary or “sensitive” relay then close, and the desired action is accomplished—turning the set on or off, changing channels, or varying the volume.

Fig. 1 is a schematic of one of the four identical reed circuits, and Fig. 2 is an interior view of the control receiver showing the location of all relays.

Let's trace out the circuits which connect the control receiver to the TV set, using the simplified sche-

matic in Fig. 3 as a guide. When the *remote on-off* switch on the rear of the TV set is closed, power is supplied to the control receiver from the AC line through pins 2 and 5 of the octal plug. The remote system is then ready to use, regardless of whether the main power switch on the TV set is in the *on* or *off* position.

As shown on the schematic, one side of the TV power-transformer primary is connected through this local on-off switch to either pin 3 or pin 4 of the remote plug. One of these pins—it doesn't matter which one—must be tied to pin 2 of the plug in order to place the transformer across the AC line. The required connection is made through the on-off latching relay in the remote receiver. The contacts of this toggle-type unit are switched back and forth between two different resting positions, alternately making pin 3 and pin 4 “hot” with AC. To turn on the TV set, it is only necessary to line up the contacts in the local and remote sections of the transformer-primary circuit to provide continuity through one of the two possible AC-return paths.

As a safety feature, the latching relay is equipped with a thermal protector which automatically opens the relay-coil circuit in case of excessive current flow through the coil.

When the sensitive relay in the channel-selector circuit is actuated, its contacts complete the power-return circuit of the power-tuning motor and thus cause it to rotate. It draws current from a special 24-volt winding on the TV power transformer, not shown in Fig. 3. The power-tuning mechanism is generally similar to the one in G-E's Chas-

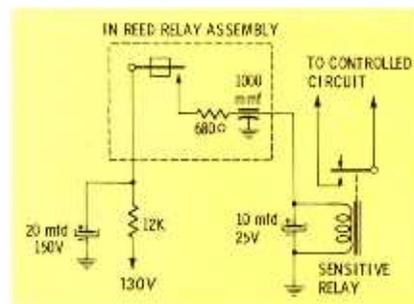


Fig. 1. Incoming signal makes reed vibrate, thus applying power to relay.

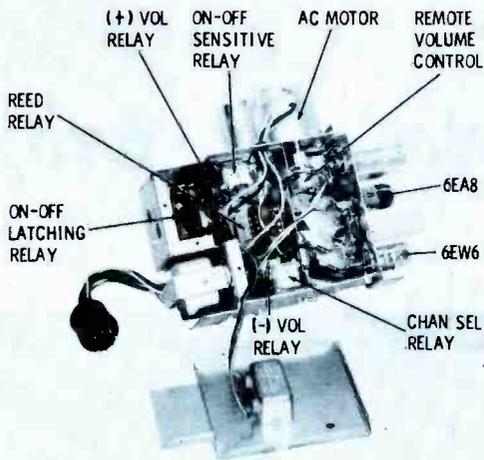


Fig. 2. Remote-control receiver has two tubes, six relays, and remote volume control operated by a small motor.

sis U3, which was described in this column last May. However, the newer unit features a different arrangement for presetting the fine tuning, as well as a "trip-proof" switch to protect the tuning mechanism from damage which fine tuning is being adjusted.

When either the "plus" or "minus" volume relay is operated, one of the windings of a special reversible motor is connected across the AC line terminals via pins 2 and 5 of the remote plug. This motor turns the shaft of a potentiometer, which regulates the audio volume by varying the DC screen voltage of the sound IF tube. Since the G-E remote system uses RF transmission instead of acoustic waves, the control signal can be transmitted as long as necessary—and then cut off at any desired instant. This enables the user to adjust the remote volume control with a great deal of precision.

The motor turns the potentiometer all the way through its range in a matter of a few seconds. At the end of rotation, the slider strikes against a mechanical stop. This is sufficient to stall the motor; no clutches, limit switches, or similar devices are needed. In order to turn the control back in the opposite direction, the user must press the other volume button on the remote transmitter.

The control receiver is a relatively simple device as far as its electronic circuits are concerned. The plug-in

antenna assembly functions as a tuned tank in the grid circuit of the 6EW6 RF amplifier. Output of this stage is coupled to the detector (triode section of the 6EA8) by a double-tuned transformer. Since the detector develops a high level of grid bias when a signal is present, the triode conducts only on positive half-cycles of the input signal. The resulting rectified output is coupled from the plate of the detector to the grid of the audio amplifier (6EA8 pentode section). Included in the RC coupling network is a sensitivity potentiometer which serves as a sort of "drive adjustment" for the audio stage.

The single transistorized stage in

the transmitter (Fig. 4) is a common-emitter circuit including tuned elements for both RF and audio frequencies. An isolated tuned circuit, including the secondary windings of collector transformers T1 and T2, is resonant at 322.7 kc. A signal of this frequency is fed back to the transistor's base circuit through a tickler winding on T1, thus sustaining RF oscillation. The ferrite-core transformers T1 and T2 (long rods in Fig. 5) function also as a transmitting antenna.

The audio oscillator is a Hartley type; in Fig. 4, note that the emitter is returned through the battery circuit to an intermediate tap on the

• Please turn to page 81

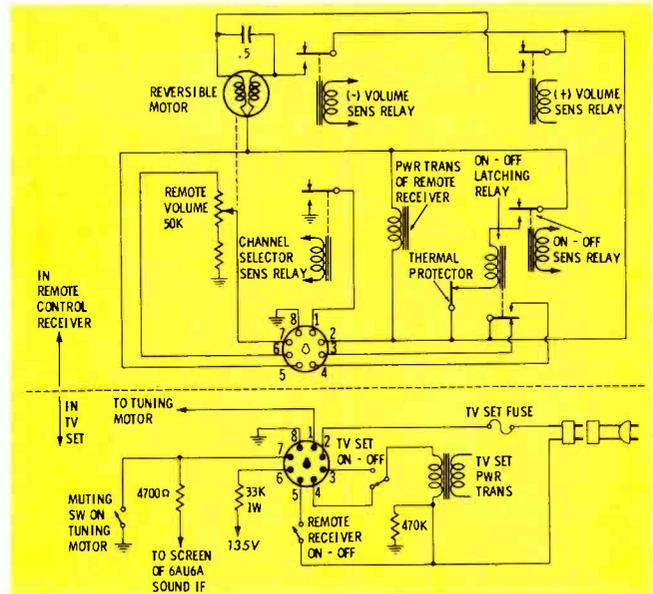


Fig. 3. Circuits associated with octal plug which connects General Electric wireless remote receiver to TV set.


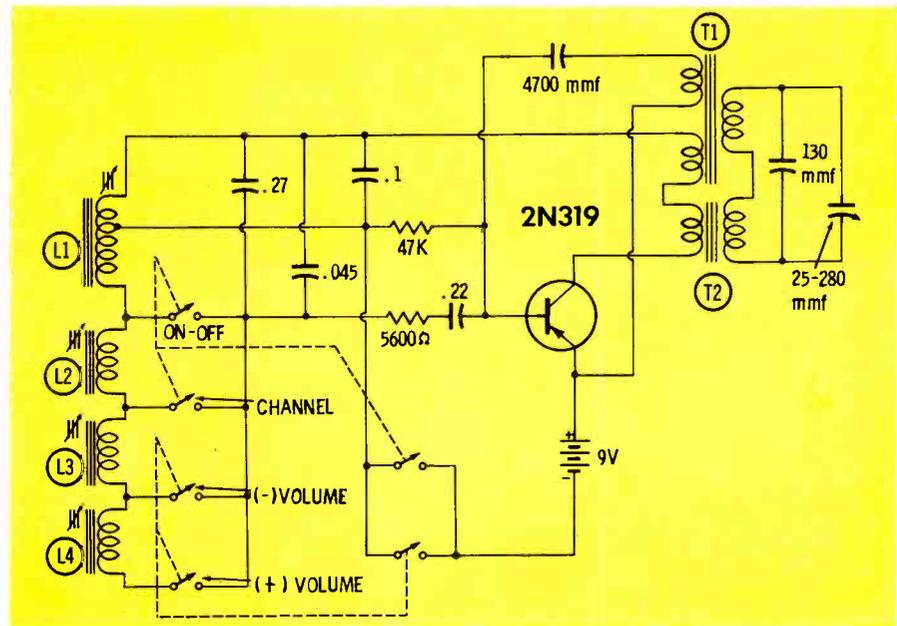


Fig. 4. Transistor circuit in transmitter is combination RF and AF oscillator.



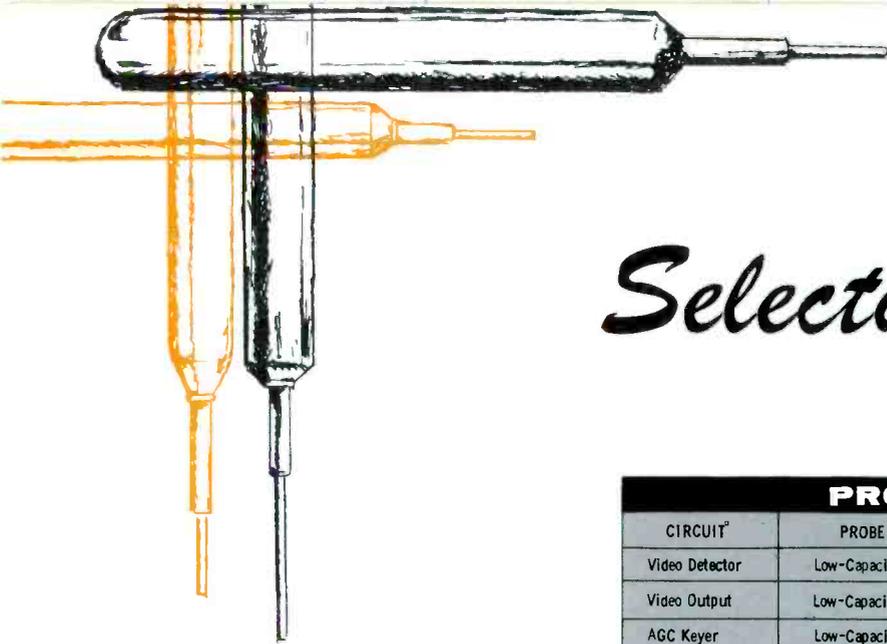


Selecting the proper

The scope is a valuable instrument in electronic service work, especially if it is used correctly. A large part of correct usage depends on the choice of accessory probes. Proper construction of probes is important, too; for example, every probe should be fitted with a coaxial lead no more than 3' to 4' in length. If you have trouble remembering which probe to use in various applications, the probe-usage chart given here will be a valuable asset.

PROBE USAGE CHART		
CIRCUIT*	PROBE	WHY
Video Detector	Low-Capacity	To eliminate capacitive loading and the resultant signal distortion.
Video Output	Low-Capacity	as above
AGC Keyer	Low-Capacity	To prevent circuit loading and introduction of signal phase shift.
Sync.	Low-Capacity	To eliminate instability that might be introduced by probe loading.
Noise Inverter	Low-Capacity	To eliminate phase shift caused by capacitance of direct probe.
Vert. Output	Low Capacity	To divide signal and avoid scope being overdriven.
Vert. Oscillator	Low-Capacity	To prevent probe capacitance from shifting frequency.
Horiz. AFC	Low-Capacity	as above
Horiz Oscillator	Low-Capacity	To prevent circuit loading and oscillator detuning.
Horiz. Output	Low-Capacity	(grid only) To prevent circuit loading and reduced grid drive.
Low-Voltage	Direct	Low-impedance, low-frequency circuit best handled with direct probe.
Video IF	Demodulator	Detect IF signal and provide a response within scope's bandpass.
Tuner	Isolation	Reduce noise pickup and make marker pulse easier to see (alignment)
Video Detector	Isolation	as above
Color Sync.	Demodulator	(single ended type) To provide a signal within scope's bandpass.

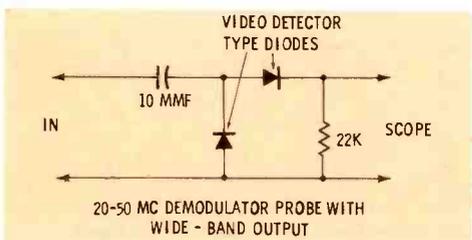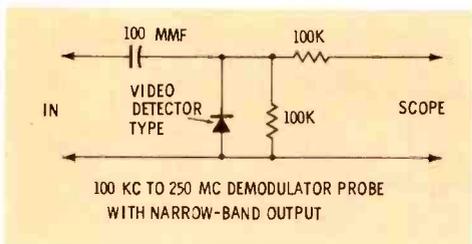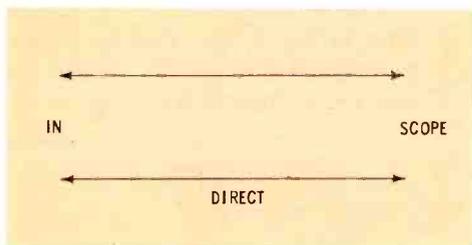Caution 1. Never apply any of these probes to points in the circuit that have AC, DC, or pulse voltages in excess of the rating of the probe's input component.



THE SIMPLEST PROBE

The DIRECT PROBE is the simplest of them all, and may be constructed in one of several different ways. It may consist solely of a piece of shielded cable with spade lugs on the scope end and alligator clips on the other—or, you may need co-axial or banana-plug connectors on the scope end. A dummy probe tip and a 10" wire complete with alligator clip terminating the braided shield makes a very good direct probe.



100-kc to 250-mc DEMODULATOR

This DEMODULATOR PROBE can be used at frequencies between 100 kc and 250 mc, and the demodulated output can be any frequency between 60 cps and about 8 kc. The unit is useful in signal-tracing video-IF stages and TV tuners, as well as in checking bandwidth in the chrominance sections of a color receiver.

20-50-mc DOUBLER-TYPE PROBE

This DOUBLER-TYPE DEMODULATOR PROBE has a much narrower bandpass than the single-ended type, but it offers about twice the signal output. It is excellent for all forms of troubleshooting in video IF and other circuits in the 20- to 50-mc range.

SCOPE PROBE

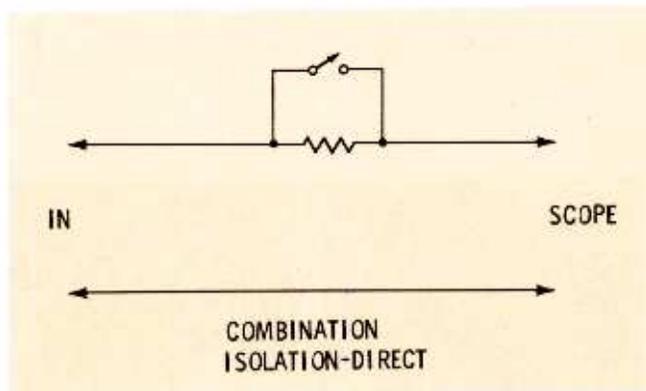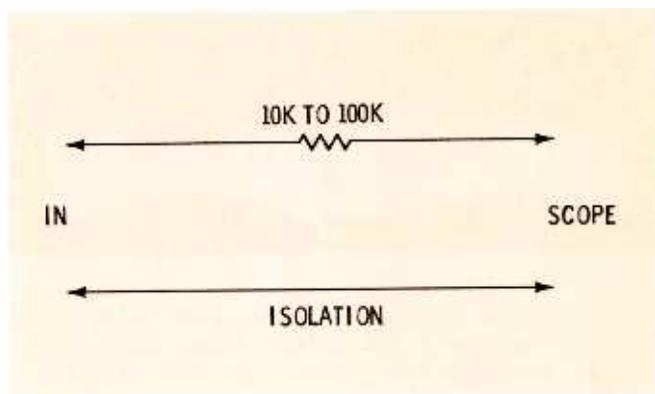

ISOLATION PROBE

This is also a direct probe with a 10K to 100K resistor in series with the "hot" lead. It is usually specified for RF and IF sweep alignment. A VTVM probe of the "Uniprobe" type would permit both DIRECT and ISOLATION probes to be contained in a single unit. The desired probe type could then be obtained with a simple turn of the tip, or a flip of a switch.


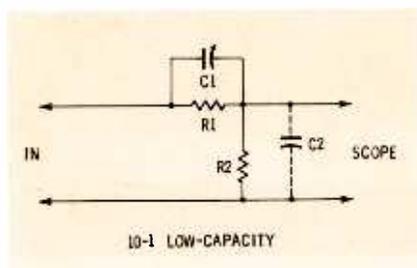


TABLE OF VALUES FOR LOW-CAPACITY PROBES			
SCOPE IMPEDANCE	R1	C1	R2
1 MEGOHM	1 MEG	3 - 13 NWF	110K
2 MEGOHMS	2 MEG	3 - 13 NWF	220K
3 MEGOHMS	3 MEG	5 - 20 MMF	330K

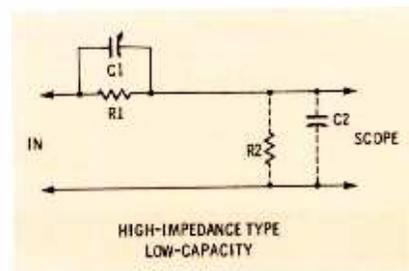


THE MOST USEFUL PROBE

The LOW-CAPACITY PROBE (with 10:1 attenuation ratio) is the most important accessory you can have for your scope. Its design is such that the output signal is one-tenth of the input, and thus it offers only one-tenth as much circuit loading as a direct probe. This is desirable even at the expense of a 90% signal loss.


Low-capacity probes have two general configurations. The simpler design offers higher impedance and correspondingly less circuit loading, but may have an attenuation factor other than 10 to 1, making it more difficult to calculate peak-to-peak signal measurements.

In either probe circuit, R1-C1 should equal R2-C2, and the value of R1 should be ten times that of R2. The combination of R2-C2 in the simpler circuit matches the impedance of the cable and scope. For the more elaborate probe, R2 always equals 1/9 of the scope's input resistance, and C2 is the total of the cable and scope input capacitances (no physical capacitor is used). The most common values for R1, C1, and R2 used in 10:1 probes are given in the table. Choose the values to match scope input impedance.

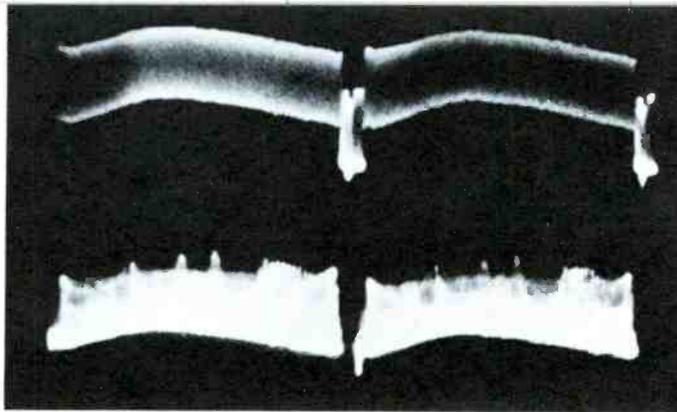


Vertical sync compression in this video-detector waveform was caused by circuit loading with a direct probe. Using this type of probe to monitor the video signal could cause you to erroneously assume there is trouble in the tuner or video-IF strip.

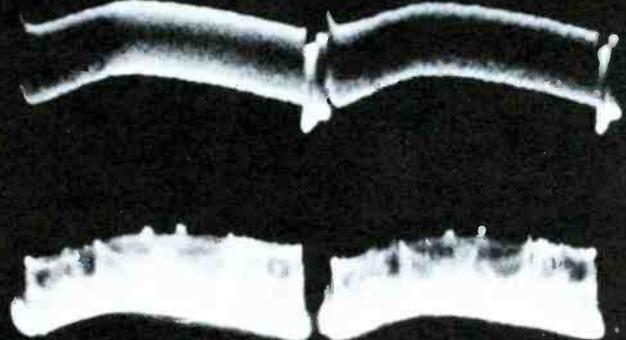
When a low-capacity probe is used to view the signal at the video detector, there is no circuit loading and you therefore get a true picture of tuner and IF operation.



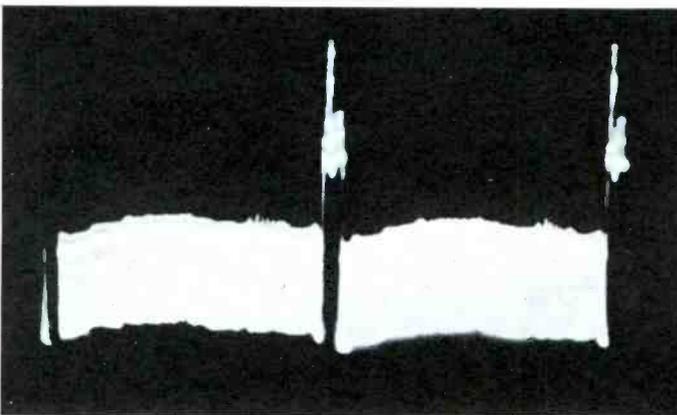
The detected IF signal, when using the single-ended demodulator probe, shows very prominent low-frequency response. High-frequency portions of the signal are greatly attenuated; thus, this type of probe is useful only when the modulating frequency is low.



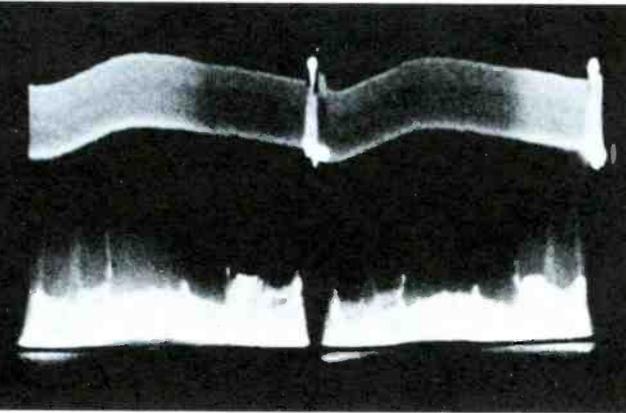
When using the doubler-type probe, the detected IF signal is very nearly identical to the video-detector output. Naturally, it is smaller by a degree, depending on the stage being examined. A small loss of high-frequency information is indicated by the lower relative amplitude of the horizontal sync pulses when compared to the vertical pulses.



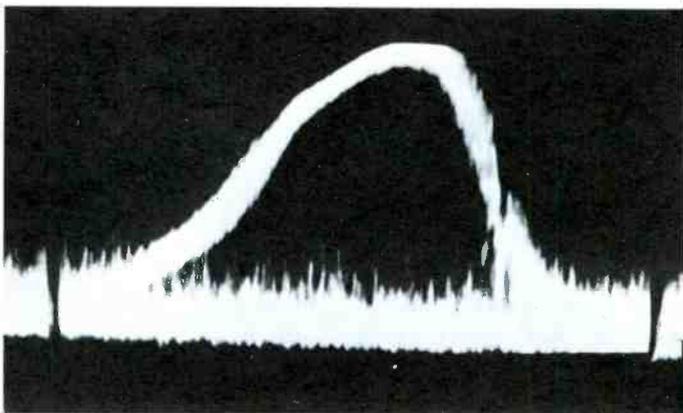A small marker pip or dip would be very difficult, if not impossible, to locate among the "grass" on this video-IF response curve. The grass is due to pickup of the 15,750-cps energy radiated by the horizontal-output and high-voltage circuits.



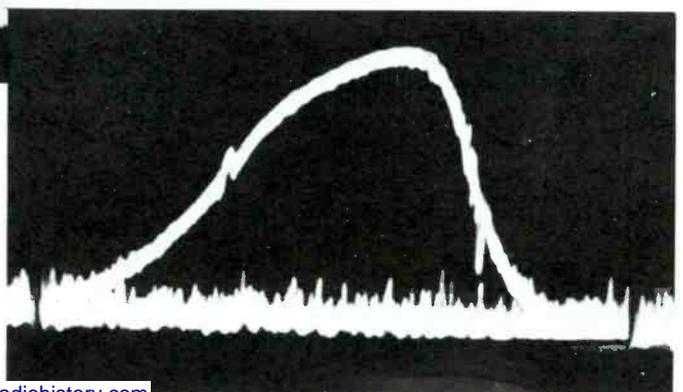This video-IF curve has much less "grass" because an isolation probe was used. The series resistance in the probe is frequency-discriminating, and affects high frequencies without disturbing low frequencies.



GET *more!* DO *more!* MAKE *more!*

PROFIT PROFESSIONALLY ON EVERY CALL WITH

NEW **B&K**

**LOW-COST PROFESSIONAL
Model 550 DYNA-QUIK
DYNAMIC MUTUAL CONDUCTANCE TUBE TESTER**



Model 550

NET **\$119⁹⁵**

Every service-technician now can easily check tubes the B&K professional way! Only with a *genuine dynamic mutual conductance tube tester* can you make a complete and accurate test under the actual dynamic operating conditions of the TV set. The compact new "550" is not just an emission checker. *It completely checks more tubes faster—with laboratory accuracy.* And the cost is so amazingly low, it pays its way over and over again! Take a tip from thousands of professional servicemen—use *B&K Dyna-Quik*. There is nothing like it.



Get More for Your Money

—IN SPEED, ACCURACY, AND VALUE



Save Customers

—SAVE CALL-BACKS, SAVE COST



Sell More Tubes

—MAKE MORE MONEY PER CALL

MODEL 550 DYNA-QUIK TUBE TESTER

Tests Each Section of Dual-Section Tubes Separately

Great new value in professional quick-check at small cost. Provides more tube sockets to test more tubes faster. Accurately checks most of the TV and radio tubes usually encountered in everyday service work. Tests each section of dual-section tubes separately. Measures true dynamic mutual conductance. Checks tubes for shorts, grid emission, gas content, and leakage. Completely tests each tube in seconds, checks average TV set in a few minutes, in home or shop. One switch tests everything. Fast, convenient reference listings on socket panel. Patented circuit provides automatic line voltage compensation. 7-pin and 9-pin straighteners on panel. Handsome, luggage-type carrying case. Net, **\$119⁹⁵**

MODEL 650 DELUXE DYNA-QUIK

Today's Finest Portable Tube and Transistor Tester

Accurately checks over 99% of the tubes most widely used in television receivers, plus popular home and portable radio tubes. Tests over 600 tube types. Lists over 125 most popular tube types, with settings, on socket panels for maximum operating speed. Complete listing in fast, index-type selector. Measures true dynamic mutual conductance. Tests each section of multiple tubes separately for GM, Shorts, Grid Emission, Gas Content and Life. Includes 16 spare sockets and ample filament voltages for future new tube types. Transistor Section checks transistors, diodes, and selenium rectifiers. Luggage-type carrying case. Net, **\$169⁹⁵**



Model 650

B&K


B & K MANUFACTURING CO.
3726 N. Southport Ave. • Chicago 13, Illinois

Canada: Atlas Radio Corp., 50 Wingold, Toronto 10, Ont.
Export: Empire Exporters, 277 Broadway, New York 7, U.S.A.

See Your Distributor or Send Now for Bulletin ST24-R

Dealer JOHN G. ALTMeyer Says...

"Mallory Components are Best

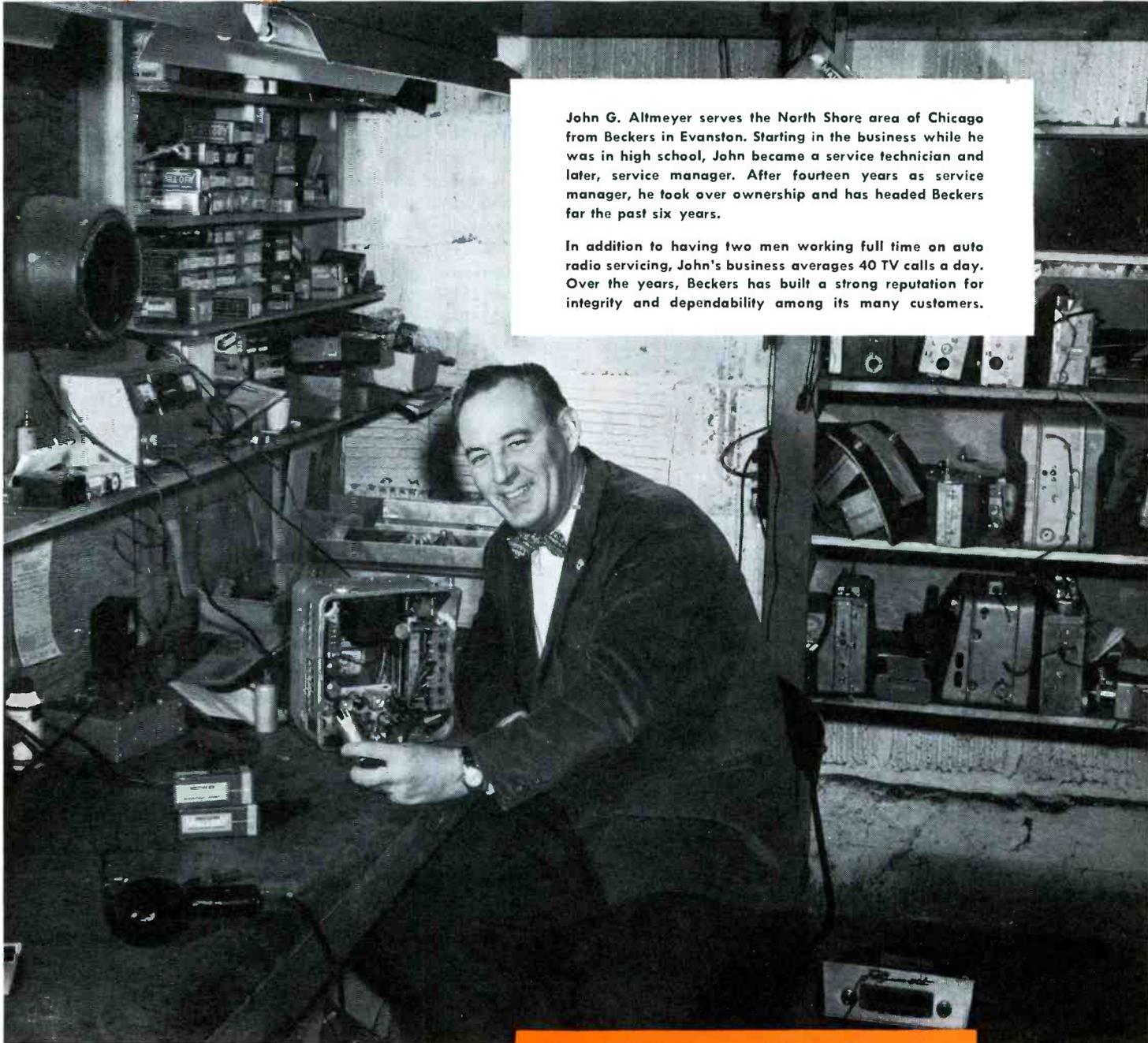

John G. Altmeyer serves the North Shore area of Chicago from Beckers in Evanston. Starting in the business while he was in high school, John became a service technician and later, service manager. After fourteen years as service manager, he took over ownership and has headed Beckers for the past six years.

In addition to having two men working full time on auto radio servicing, John's business averages 40 TV calls a day. Over the years, Beckers has built a strong reputation for integrity and dependability among its many customers.

P. R. MALLORY & CO. Inc.
MALLORY

P. R. MALLORY & CO. Inc., INDIANAPOLIS 6, INDIANA

for Modern Equipment 'Trouble Spots'”

“Modern car radios—for example—need quiet vibrators . . . that’s why we replace with Mallory.

Today’s automobiles are engineered for a quieter, more pleasurable ride. A noisy vibrator in a car radio stands out immediately. Our servicemen use Mallory Vibrators for all replacements. We’ve found that they’re quieter and more dependable. The Mallory buttonless contact design adds to their longer, trouble-free life.”

Whatever component you need for servicing—capacitors, controls, resistors, silicon rectifiers or batteries—you get the highest quality at sensible prices from Mallory. It’s the widest line of parts in the industry . . . and every model is service-engineered to assure you that each job is right the first time, every time.

Stop Callbacks with These Quality Mallory Products . . .



Gems—5 rugged, moistureproof, Mallory “Gem” tubular capacitors in an easy-to-use dispenser that keeps your stock fresh and clean—easy to find—no more kinks in lead wires. They’re your best bet for outstanding service in buffer, bypass or coupling applications.




RMC Discaps®—are a product of the world’s largest producer of ceramic disc capacitors. Long the original equipment standard, Mallory RMC Discaps are now available for replacement. They come in a handy 3” x 5” file card package . . . easy to stock, simple to use.

® Trade Mark of Radio Materials Company, a division of P. R. Mallory & Co. Inc.



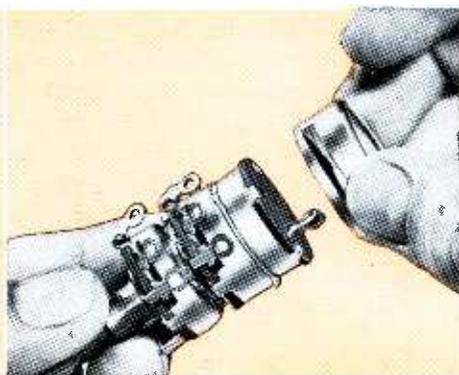FP Electrolytics—The Mallory FP—the original 85°C capacitor—now has improved shock-resistant construction and leakproof seal. Its etched cathode construction—standard in all FP’s—assures hum-free performance. High ripple current ratings fit the toughest filter circuits.




Sta-Loc* Controls—New Sta-Loc design enables your distributor to custom build, in just 30 seconds, over 38,000 combinations—eliminates waiting for out-of-stock controls. You can replace the line switch by itself, without unsoldering control connections.



Gold Label* Vibrators—On critical auto radio servicing, use the Mallory Gold Label Vibrator. It gives longer, trouble-free service life. Mallory Gold Label Vibrators feature Mallory exclusive buttonless contact design.

*Trade Mark

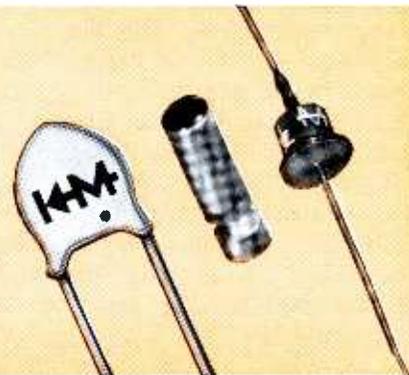

Silicon Rectifiers—New Mallory design gives far longer life, lower forward voltage drop, and reverse leakage current than conventional types . . . exceed the requirements of military humidity tests. In convenient kits for replacement of selenium rectifiers in radio and TV.



HAVE A CLEAR PICTURE EVERY TIME!

Install General Electric Service-Designed 6BZ6's and 6CB6-A's for optimum AGC performance in all signal areas!

Strong signal or weak, these General Electric video IF-amplifier tubes do the same fine job. Grid characteristics are closely controlled over the full operating curve, in order that the 6BZ6 and 6CB6-A may show proper response to widely varying AGC voltages. Give your customers real-life TV whether reception is strong, intermediate, or fringe-area!

Goodwill grows, callbacks are less when you replace with Service-Designed 6BZ6's and 6CB6-A's—built and tested to perform efficiently under *all* conditions! These improved pentodes pay off in better TV that brings new business to your door. See your G-E tube distributor! *Distributor Sales, Electronic Components Division, General Electric Company, Owensboro, Kentucky.*

Progress Is Our Most Important Product

GENERAL  ELECTRIC

3-111-207



No. 8666 6 oz. Dealer Price 99c



FASTER ACTING TV TUNER CLEANER

NEW AND IMPROVED FORMULA

Stop radio and television control noises with the easiest-to-use, greatest time and money saver ever developed for the serviceman. Cleans and lubricates with one lasting p-o-o-f. It's the genuine and original G-C SPRA-KLEEN, sold by jobbers everywhere.

Best and Easiest-To-Use Control Cleaner!

GENERAL CEMENT MFG. CO.

division of GC—Textron Inc.

West Plant: Los Angeles 18, California

Main Plant: **ROCKFORD, ILL., U.S.A.**

the curve back to normal (see Fig. 3).

Just to be on the safe side, I also checked tuner alignment. Since the response curve was tilted on low-band channels, I made a few touch-up adjustments. The small amount of adjusting required on the tuner ruled out twiddling, so I reasoned that tube replacement had affected tuner alignment slightly.

To test the repair, I then connected the set to the outside antenna system and tuned in the strongest local station. The AGC and fringe-lock controls now produced normal changes in picture and sound when they were adjusted; i.e., the AGC control range would white out the picture at one extreme, vary the degree of picture contrast in the center portion, and black out the picture at the other extreme setting. The fringe-lock control caused the picture to bend when adjusted toward the fringe position. The sound developed a trace of buzz at AGC-control settings which produced excessive contrast, which is the normal condition.

While we have just dealt with a case wherein alignment cured a very nasty AGC trouble, let's not get the idea that this will always be the case. The real story is not that the trouble was repaired, but how the serviceman went about locating its cause. If he hadn't checked things in an orderly and calculating manner, he might never have reached the conclusion that alignment was the source of his trouble.

For those who feel that the standard procedure of clamping the AGC line was overlooked, let's say briefly that this test wasn't tried since the voltage on the control grid of the first video-IF stage was positive. After the set was repaired, however, I did a little checking and found that, after disconnecting the coupling capacitor (C24 in Fig. 1) from the AGC-keyer plate, a negative voltage could be applied to the plate of the keyer tube to effectively clamp the AGC line. The voltage required was quite high, though; I used a 67.5-volt battery and a 1-meg potentiometer for the bias pack.

Grille Cloth Installation

Installing a strip of one of the new plastic grille-cloth materials can make a very noticeable improve-



To Assure You Safe, Trouble-Free Electrical Protection

every BUSS Fuse is electronically tested!



Before a BUSS or FUSETRON fuse ever leaves the plant, it must meet our high quality control standards.

Each fuse is tested in a sensitive electronic device that automatically rejects any fuse not correctly calibrated, properly constructed and right in all physical dimensions.

Thus . . . by selling and installing BUSS and FUSETRON fuses you have one more way to help safeguard your reputation for service and reliability.

Complete Line For All Your Fuse Needs

Single-element fuses for circuits where quick-blowing is needed.

Single-element fuses for normal circuit protection.

Dual-element, slow-blowing fuses for circuits where harmless current surges occur.

Indicating fuses where signals must be given when fuses open.

BUSS fuses range in size from 1/500 amperes up — and there's a companion BUSS line of fuse clips, blocks and holders.

Your customers Know and prefer BUSS fuses

The ready acceptance of BUSS fuses is built on the millions upon millions of BUSS fuses used in homes and industry over the past 44 years. When you furnish BUSS, your customers instantly recognize that you are providing them with the finest electrical protection possible.

For more information, write for BUSS bulletin SFB.

BUSSMANN MFG. DIVISION,
McGraw-Edison Co.
University at Jefferson, St. Louis 7, Mo.

859

BUSS fuses are made to protect - not to blow, needlessly.
BUSS makes a complete line of fuses for home, farm, commercial, electronic, electrical, automotive and industrial use.

MORE PICTURE POWER

new
BLONDER-TONGUE


B-24 POW-R BOOSTER



\$24⁹⁵
list

*it's a powerful booster
...or an amplified coupler!*

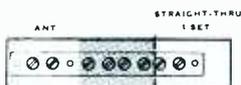
**provides sharp, clear TV pictures on
1, 2 or more TV sets with only 1 antenna**



'straight-thru' circuit provides up to 10 db gain as a powerful one-set booster



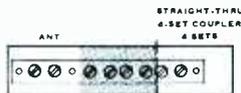'couple-two' circuit provides up to 5 db gain (per set) as an amplified two-set coupler



'straight-thru' circuit and B-T 4-set coupler provide no-loss 4-set distribution system

Employs new frame-grid tube 6DJ8 new circuitry to achieve highest signal gain and "lower-than-cascade" noise factor. Provides full broadband amplification covering low and high VHF channels. May also be used as FM-TV coupler. Features "NO-STRIP" 300 ohm terminals for positive, electrical contact in seconds. Has "on/off" switch.

Improve TV reception today on 1, 2 or more TV sets with a single antenna.



Available at parts distributors. For details write: PF-9

BLONDER-TONGUE LABORATORIES, INC.

9 Alling Street • Newark 2, N. J.

In Canada: Teleequipment Mfg. Co., Ltd., London, Ont. Export: Morhan Export Corp., N. Y. 13, N. Y. hi-fi components • UHF converters • master TV systems • industrial TV cameras • FM-AM radios

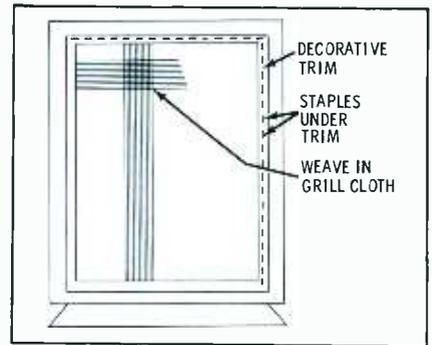


Fig. 4. Use decorative trim to hide staples used for installing grille cloth.

ment in the appearance of an older model TV, radio or hi-fi set. The actual installation is a relatively simple process, although it varies somewhat with the particular job. If speaker-board mounting permits, remove it, pull the cloth around all four sides, and staple it in place from the rear. Make sure to get the weave straight for appearance's sake. If the speaker board can't be removed, staple the cloth to the front at the outer edges, and install a narrow decorative trim strip to hide the staples as shown in Fig. 4.

One pitfall to avoid: think twice before you install light colored cloth over a light colored board. If you don't, the speakers will stick out like a sore thumb, as they do in Fig. 5. The remedy is simple; merely paint the speaker board with a flat black paint before installing the grille cloth.

Battery Lives Forever

Old soldiers aren't the only things that never die; Sonotone's new rechargeable flashlight pack is reported to have a useful life of 15 to 20 years in normal service.

This battery pack (Fig. 6) should be a boon to the TV serviceman. If

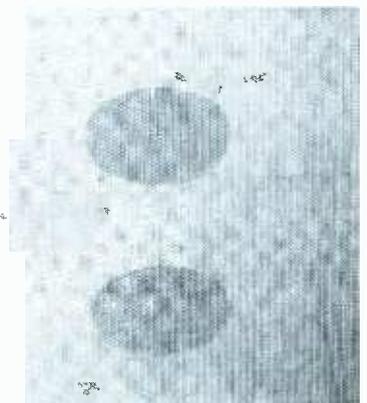


Fig. 5. Paint speaker board black when installing a light-colored grille cloth.

YOU SHOULD KNOW
THERE IS SOMETHING BETTER

DF-1

Duetto

2-WAY HI-FI LOUDSPEAKER SYSTEM

ONLY \$79⁵⁰

WITH
NEW
"FLEXAIR"
WOOFER



BURTON BROWNE ADVERTISING

Here is Jensen's latest "bookshelf" size speaker, an economically priced full two-way system featuring wide frequency range and exceptional, clean bass response down to 36 cycles due to the new FLEXAIR* woofer in tube-vented BASS-SUPERFLEX* enclosure. New direct radiator tweeter with crossover at 2,000 cycles carries the response smoothly out to 14,000 cycles. Enclosure is fine furniture crafted of rigid 3/4" selected veneer plywood

in choice of Walnut, Tawny Ash or Mahogany finished on four sides for horizontal or vertical placement. Genuine matching hardwood front frame with sculptured, curved lines and choice fabric grille cloth provide a graceful, distinguished appearance. Use a single DF-1 as an excellent monophonic system or low cost stereo add-on, or a pair for your stereo system. Speaker system also available in kit form. Write for Brochure KP

*TM



Illustrated with ST-972
Accessory Floor Base
(order separately).



jensen

DIVISION OF THE MUTER COMPANY

MANUFACTURING COMPANY

6601 S. Laramie Avenue • Chicago 38, Illinois

In Canada: J. R. Longstaffe Co., Ltd., Toronto

In Mexico: Radios Y Television, S. A., Mexico, D. F.

IMPORTANT NEW SAMS BOOKS



"101 Ways to Use Your Signal Generator"



by Bob Middleton

The most practical and complete guide to the fullest use of your signal generator. Covers all common and many uncommon applications. Each use is clearly described, with full data on connections required, additional equipment needed, proper test procedure and evaluation

of results. Specific sections cover uses of the signal generator for antenna tests, AM-FM receiver tests, TV set tests, component tests, etc. Over 100 illustrations. Invaluable for technicians, engineers, students and experimenters. 128 pages. 5½ x 8½". Only **\$2.00**

"How to Save Time Analyzing and Tracing TV Circuits"

by Milton S. Kiver



All-new second edition of Kiver's popular book describing his famous proved methods for fast, accurate diagnosis and solution of TV service problems. Chapters cover: Differences between Schematics and Sets; Following the DC Power Lines of a Set; Where the Boost Voltage Fits In; The AGC System; In and Around the Deflection Systems; First Things

First; What to Do When You Meet an Unfamiliar Circuit; How to Find Your Way Around Printed Circuits. This practical book belongs in the reference library of every technician and student. 160 pages; 8½ x 11". Only **\$3.50**

"Electronics Reference Data"



New Volume 2. Valuable reference compilation covering dozens of important subjects. Includes sections on: antennas and transmission lines; UHF television; circuit design (magnetic, dielectric and tubeless amplifiers); audio measurements; radar; meters and measurements; specialized application and development (microwave tubes, RF transistors, traveling wave amplifier,

etc). A profitable reference book for technicians, engineers, Hams and students. 128 pages; 8½ x 11". Only **\$2.50**

HOWARD W. SAMS & CO., INC.

Order from your Sams Distributor today, or mail to Howard W. Sams & Co., Inc., Dept. 3-J9 2201 E. 46th St., Indianapolis 6, Ind.

Send me the following books:

- "101 Ways to Use Your Signal Generator" (TEM-4)
 "How to Save Time Analyzing TV Circuits" (JA-2)
 "Electronics Reference Data—Vol. 2" (ERA-2)

\$_____ enclosed. Send Free Book List

Name _____

Address _____

City _____ Zone _____ State _____

(outside U.S.A. priced slightly higher)



Fig. 6. Sonotone rechargeable 3-volt pack compared to 2-cell flashlight.

you've ever been on a home call and needed your flashlight to locate the keyway on a 9-pin tube socket, only to find the batteries "shot," the rechargeable feature is sure to be of prime interest to you. With the new Sonotone battery, you just unscrew the cap, and insert the exposed male plug (Fig. 7) into the nearest AC outlet. In about 5 minutes or so, the battery will be recharged enough to complete the job. You could use this waiting time to clean the CRT screen or tuner contacts, or perform other small necessary jobs, thereby eliminating lost time.

To completely recharge the battery, leave it plugged into an AC outlet overnight. A six to eight hour charging period is usually sufficient to restore the battery to full charge, although longer charging periods won't damage it.

You dealers that feature walk-in sales items should be interested in stocking these rechargeable batteries for resale to your customers. As a matter of fact, you can sell them while making home calls without half trying. They are both shock-proof and leakproof, and have a recommended consumer price of \$7.95. ▲




Fig. 7. Simply plug the Sonotone battery into a 110-volt outlet to recharge it.

A Profitable New Field!

INDUSTRIAL ELECTRONIC SERVICING

with
OHMITE[®]
QUALITY
Components

Industrial electronic servicing is profitable new business for you. Especially when you stock and replace with dependable Ohmite components . . . the line your industrial customers know and prefer. Service such industrial equipment as mobile radio, aircraft and marine radar and radio, electronic controls for factory processes and automation, industrial P.A. and intercom systems, and—medical and dental electronics.

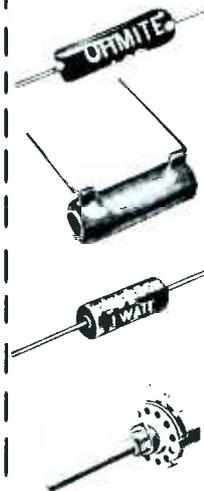

AXIAL-LEAD RESISTORS

Vitreous-enamelled, power-type units designed to withstand high temperatures. In 3, 5, and 10-watt sizes.

BROWN DEVIL[®] RESISTORS

Vitreous-enamelled. In 5, 10, and 20-watt sizes.

LITTLE DEVIL[®] COMPOSITION RESISTORS

Meet all MIL-R-11A requirements. Available in ¼, ½, 1, and 2-watt sizes in all standard EIA values.

MOLDED COMPOSITION POTENTIOMETERS TYPE AB

Resistance material is solid-molded, noise-free. Rated at 2 watts.

Write for Stock Catalog 28

OHMITE[®]

DEPENDABLE
RESISTANCE
UNITS

OHMITE MANUFACTURING COMPANY
3644 Howard Street, Skokie, Illinois

ready, willing and able



"TAB-MOUNT" CARBON POTS
SERIES B-47

Designed to meet the fast-growing tab-mounted carbon pot replacement needs. A wide selection of the most popular resistance values. Rated at 1/2 watt. Universal-type phenolic knurled shaft, slotted, 1" long. Easily cut or altered to suit individual needs.



MINIATURIZED CARBON POTS
SERIES 44 & 44S

The right replacement for transistorized circuits, portable radios, hearing aids, and other miniaturized applications. 0.2 watt. 2 1/2" diameter. Available with or without switch. Made in most popular values and tapers. 1/8" diameter shaft, 1/2" long.



more good reasons for
always saying:



CLAROSTAT MFG. CO., INC., DOVER, NEW HAMPSHIRE

Dynamic! NEW ADVANCEMENT IN TV SERVICING

See the Latest
Most Up-to-Date Method
of Servicing TV Horizontal
Sweep Troubles

The Pioneer 250 HORIZONTAL SWEEP QUANTALYST... by


DOSS



Only \$109⁰⁰ net

- ▲ FEATURES NEVER BEFORE OFFERED IN ANY INSTRUMENT
- ▲ TESTS THE ENTIRE SWEEP SYSTEM IN-CIRCUIT (RECEIVER ON)
- ▲ NO NEED FOR CHASSIS REMOVAL
- ▲ SIMPLY PLUG INTO DAMPER AND HORIZONTAL AMP. TUBE SOCKETS

Now BEING SHIPPED
TO YOUR DISTRIBUTOR

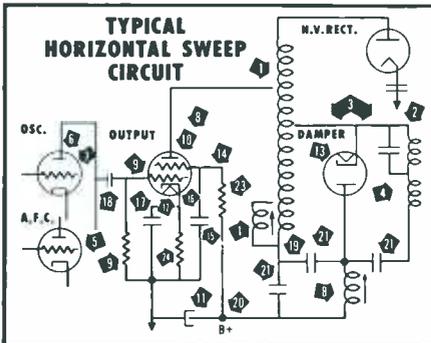

DYNAMIC IN-CIRCUIT TESTS . . . (RECEIVER ON)


- | | |
|--|--|
| 1. Flyback Transformer (Shorted Turns) | 10. Amplifier Gas Condition (Screen Re-emission) |
| 2. Yoke (Shorted Turns) | 11. Amplifier B+ Ripple |
| 3. Flyback-Yoke Match | 12. Amplifier Heater Voltage |
| 4. Yoke Inductance (mh) | 13. Damper Heater Voltage |
| 5. A.F.C. Sync. Range | 14. Amplifier Screen Voltage |
| 6. Oscillator Frequency (cps) | 15. Amplifier Screen Condenser |
| 7. Oscillator A.C. Output | 16. Amplifier Cathode Voltage |
| 8. Amplifier Cathode Current | 17. Amplifier Cathode Condenser |
| 9. Amplifier Grid Condition | 18. Oscillator Coupling Condenser |
| | 19. Boost Voltage |
| | 20. B+ Voltage |

STATIC CIRCUIT TESTS (RECEIVER OFF)

- | | |
|--------------------------------|------------------------|
| 21. Boost to B+ Resistance | 23. Screen Resistance |
| 22. Boost to Common Resistance | 24. Cathode Resistance |

DOSS Write Dept. PF-9
ELECTRONIC RESEARCH, INC.
820 BALTIMORE • KANSAS CITY 5, MO.

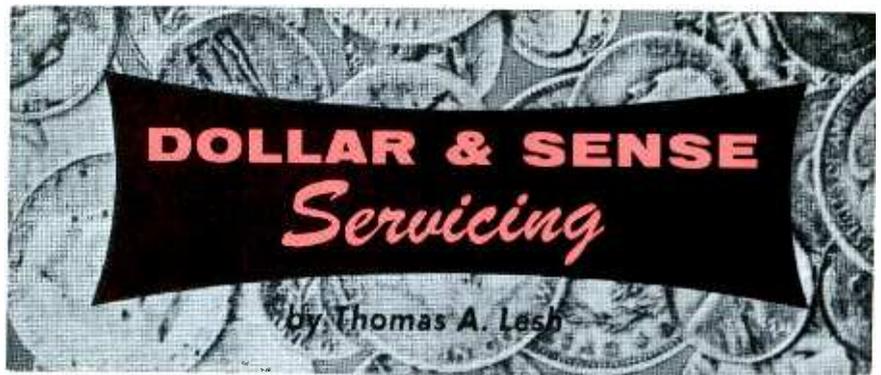For complete information including
FREE Quantalyst Trouble-Shooting
Chart—Please request Folder MP2



by Thomas A. Lash

What—Me Sell? If you shy away from the thought of performing a sales function, you have plenty of company. There aren't many good technical men who enjoy (or have the aptitude for) the aggressive, persuasive type of selling. In fact, TV-appliance stores frequently discourage their service employees from this kind of activity. If an outside technician sees an opportunity for sale of an appliance, he's often asked to pass along this lead to the regular sales force instead of handling it himself.

But this doesn't slam the door on all selling efforts by technical men. The low-pressure type of salesmanship, known as "suggestion," lends itself beautifully to use on service calls. Mr. C. W. Dunlap, a parts distributor in Stockton, Calif., has pointed this out very aptly in a newsletter he sends to his service-dealer customers:

"Your right foot and your left foot as you approach a customer's door enjoy a unique selling situation. You have no barrier to break down, nor must you resort to "fast talk" to gain your customer's attention. Quite to the contrary, the customer awaits your arrival. Your technical background and "know how" has been requested by the owner of a radio or TV set. This immediately places you in the role of the expert. Take one moment to analyze the situation.

1. You are called into the home as an expert because of your specialized knowledge.
2. Your customer will listen to what you suggest.
3. Pre-selling and promotion of a product by the brand-name manufacturer has already occurred, and the technician, by reminding his customers of the brand-name products he represents, has gained a unique selling situation. "Suggestion selling" calls for initiative, and it is a great profit power potential and a valuable

assist for increased profits."

Note one point: You have to take the initiative in order to reap the advantages of selling by suggestion.

\$ & C

Direct Mail — To Where? The other morning, I took in my mail as usual. With a well-practiced gesture, I deftly dropped the supermarket coupons, "Occupant" items, etc., into the wastebasket; then I settled down to read the "real" mail. Among the envelopes was a neat white one addressed in a precise, old-fashioned hand. A letter from some dear old aunt back East? Nope—it turned out to be an elegantly-printed invitation to the grand opening of a new golf driving range!


This was somewhat of a letdown, but the important point is that the letter got through my hard-shelled defenses and captured my attention.

Now let's talk about *your* direct-mail advertisements. If I had received your latest mailing piece, would I have taken a look at it, or shooed it into the trash bin? That would have depended upon a split-second impression. The item would have had to look worthy of consideration, or I (in my role of a skeptical, ad-weary householder) wouldn't have bothered to rip open the envelope.

To coax the addressee into looking at the mail you send, put his name on the envelope and get it *right* to the best of your ability. Perhaps you'd like to add a real personal touch with handwritten addresses, as the driving-range owner did. If so, the writing should be done in a reasonably careful hand in order to get the desired effect. Some retired or shut-in person in your neighborhood would probably be glad to turn out a meticulous job, and the expense is small. You might even pay (or persuade) members of your family to help you out.

CBS TELEVISION SHOWS TOP-RATED BY RATING SERVICES

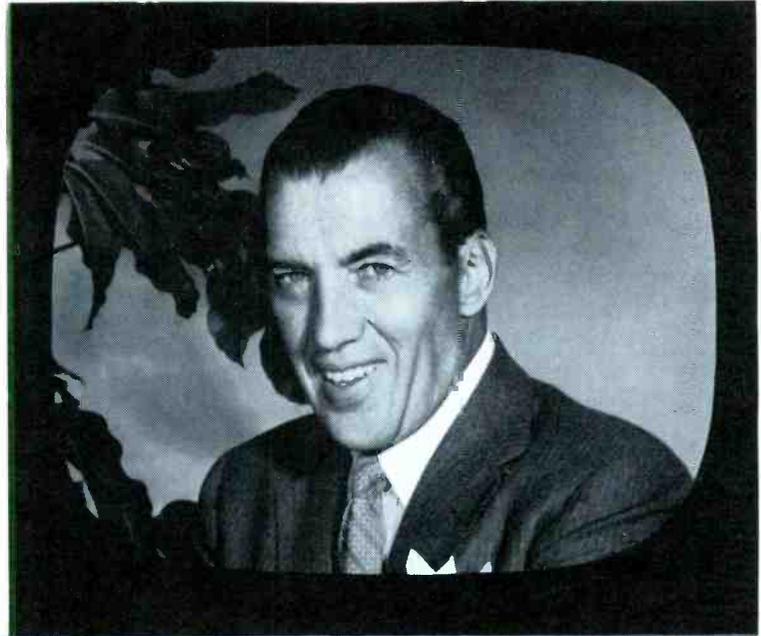This year, 20 out of the top 40 television shows were CBS. And 18% more people watched CBS Television Network programs than those of its nearest competitor. Typical is the ED SULLIVAN SHOW, top-rated program for over eleven years.



CBS TUBES TOP-RATED BY LEADING SET MANUFACTURERS

Leading set manufacturers constantly rate and re-rate receiving tubes for quality . . . brand by brand, type by type. We are proud to report that month after month CBS tubes consistently earn top ratings from these manufacturers, and maintain this approval.



TO YOU, this is unquestionable proof that when you choose CBS tubes, you choose top-rated quality . . . quality you can depend upon to cut your call-backs to the bone. Always ask for CBS . . . the top-rated name all your customers know and trust.

Receiving, industrial and picture tubes • transistors and diodes • audio components • and phonographs

CBS ELECTRONICS

Danvers, Massachusetts

Manufacturing division of Columbia Broadcasting System, Inc.

CROSSHATCH MARKS Chroma PHASE

how a crosshatch signal can be used to determine chroma phase

by Robert G Middleton

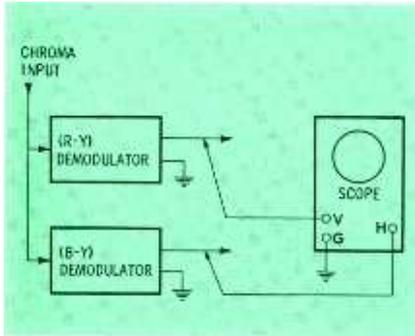


Fig. 1. Scope connections used for check of quadrature transformer adjustment.

Faithful color reproduction is possible only if the chrominance section of the receiver is properly aligned. Chrominance circuit alignment can be checked with even the inexpensive rainbow-type signal generator if the proper test procedure is employed. In making such a test, the rainbow signal is applied to the antenna-input terminals of the receiver, and the outputs from the R-Y and B-Y demodulators are fed to the vertical- and horizontal-input terminals of the scope as shown in Fig. 1.

The quadrature transformer is driven by the subcarrier oscillator, and supplies 3.58-mc reference signals to the chroma demodulators as indicated in Fig. 2. The quadrature

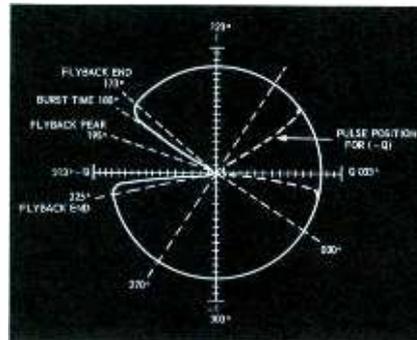


Fig. 3. Correct pattern obtained at quadrature transformer of I-Q color set.

transformer is slug-tuned, and when correctly adjusted, supplies the chroma demodulators with 3.58-mc voltages which differ in phase by 90°.

To check the adjustment of the quadrature transformer, observe the pattern on the scope screen while adjusting the transformer slug. Correct adjustment is indicated by a perfectly circular pattern; incorrect adjustment by a slanting ellipse which cannot be made into a circle by adjusting the vertical and horizontal gain controls of the scope.

This test method also works well with an I-Q demodulator system. Output from the Q demodulator is applied to the horizontal-input terminals of the scope, and output from

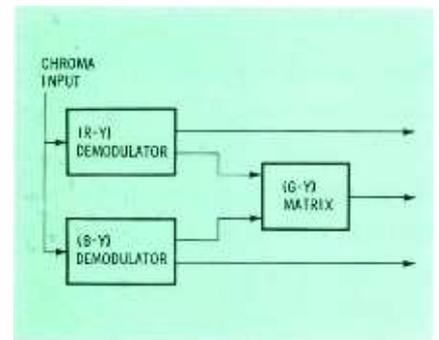


Fig. 4. Block diagram showing how R-Y and B-Y demodulators drive G-Y matrix.

the I demodulator is applied to the vertical-input terminals. As before, correct quadrature - transformer adjustment is indicated by a circular pattern, as illustrated in Fig. 3.

The G-Y Matrix

The R-Y and B-Y demodulators are followed by the G-Y matrix, as shown in Fig. 4. To test for proper matrixing with a rainbow signal, connect a scope to the output of any chroma channel, such as the B-Y demodulator indicated in Fig. 5. A sine-wave pattern should appear on the scope screen.

The pulse that appears on the sine-wave is a gating pulse. It marks the BY demodulator contributes the color-phasing control is correctly adjusted, this pulse appears at the bottom of the sine-wave, as shown in Fig. 5.

When the scope is connected at the output of the G-Y demodulator, the pulse should shift to the position illustrated in Fig. 6. The reason for this will be understood after looking at Fig. 7, which shows the basic phases of a rainbow signal. The G-Y matrix operates by mixing $-(R-Y)$ and $-(B-Y)$ voltages in a specific ratio. The burst occurs at $-(B-Y)$, and maximum negative output from the B-Y demodulator contributes maximum positive output to the G-Y matrix. The G-Y matrix obtains a negative output from the R-Y

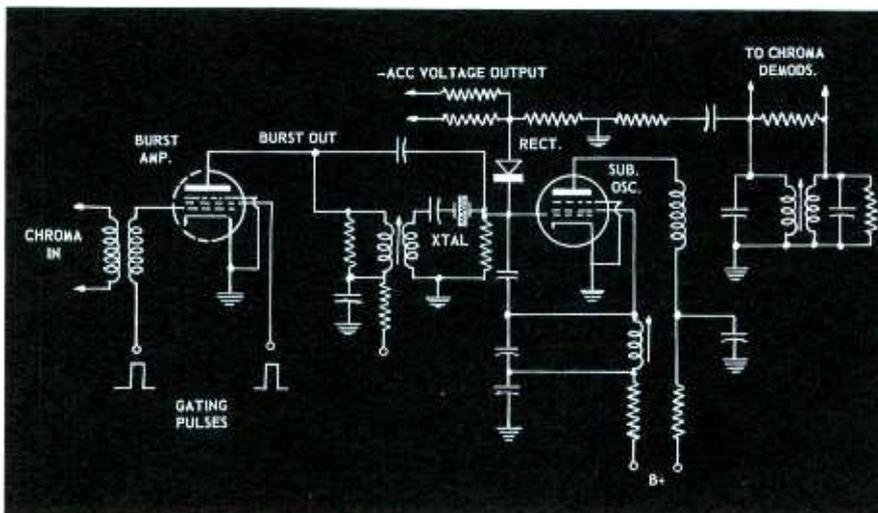


Fig. 2. The quadrature transformer supplies the demodulator reference signals.



Electronic Wire for Every Application

Service Rated—Quality Controlled
Every Electronic Wire you need
in easy-to-use packages.

- | | |
|------------------------------|--------------------------|
| Aircraft and Auto Radio Wire | Magnet Wire |
| Antenna Rotor Cables | Microphone Cables |
| Broadcast Audio Cables | Mil-Spec Hook-Up Wires |
| Bus Bar Wire | RG/U Cables |
| Community TV Cables | Shielded Power Cables |
| Cords | Shielding |
| Hi-Fi and Phono Cables | Sound and PA Cables |
| Hook-Up Wires | Strain Gauge Cables |
| Intercom Cables | Transmission Line Cables |
| | TV Camera Cables |

Ask Your Belden Jobber

One Wire Source for Everything
Electrical and Electronic



Magnet Wire • Lead Wire • Power Supply Cords,
Cord Sets and Portable Cord • Aircraft Wires
Electrical Household Cords • Electronic Wires
Welding Cable • Automotive Wire and Cable

8-3-8

PROFESSIONAL technicians
 use *Dave Rice's*
OFFICIAL ORDER BOOKS
 for every **TV-RADIO**
 service call



This is the businesslike approach to service record keeping. Triplicate forms serve as order form, invoice and office record, with spaces for complete information on every job. Separate listings for receiving tubes, pix tube, parts, serial numbers, labor and tax charges, signatures, etc. 75c a book, \$6.50 for dust-proof box of 10. In stock at your distributor. Write for your free folder describing Dave Rice's OFFICIAL ORDER BOOKS, including an actual size sample copy of the handy order form.

For customer's prices on every replacement part, plus flat rate and hourly service charge data, regional and national, Dave Rice's OFFICIAL PRICING DIGEST, listing over 63,000 items. \$2.50.

ELECTRONIC PUBLISHING CO., INC.
 180 N. WACKER DRIVE
 CHICAGO 6, ILLINOIS



FROM ONE WHO LEARNED

This enlargement shows a diamond-chip needle sent us by a disappointed user, who learned all diamond needles are not O.K. Shows what happens if a heat bubble forms when a chip is welded on. Can't happen with a Duotone Needle that uses only the whole diamond set deep in the metal shank.



Insist on Duotone. Be sure. Duotone's whole diamond can't break off.

DUOTONE DIAMOND NEEDLE

"that remembers"
 Keyport, N. J.

In Canada: Chas. W. Pointon, Ltd., Toronto

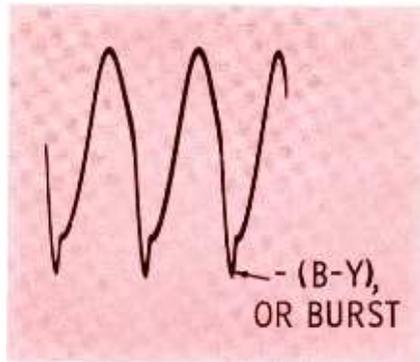


Fig. 5. Signal obtained when scope is connected to B-Y demodulator output.

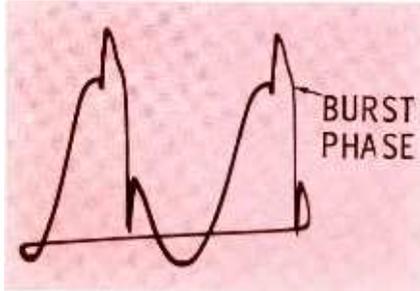


Fig. 6. Signal obtained when scope is connected to the output of G-Y matrix.

demodulator, which also contributes the the burst-phase pulse observed on the G-Y waveform.

Using Crosshatch Markers

Since the burst pulse lacks pinpoint sharpness, it is somewhat of an indefinite phase indicator; thus, a more accurate means is required to check matrix operation. One method is to use a keyed rainbow generator. Since many shops have simple rainbow generators instead of the keyed variety, however, a crosshatch pattern can be used to mark chroma phases.

Some instruments provide a crystal-controlled unkeyed rainbow signal, as well as a crosshatch signal. By taking advantage of the rainbow signal that feeds through while operating the crosshatch function, a simultaneous crosshatch and rainbow pattern will be displayed on the picture-tube screen. Operating in this manner, you will observe that the vertical bars of the crosshatch signal appear along the base line of the pattern when the scope is connected to the output of a chroma demodulator. As shown in Fig. 8, the fifth pip provided by a sample generator is very close to R-Y, the eighth pip is very close to -(G-Y), the tenth marks B-Y, the fifteenth -(R-Y), and the seventeenth G-Y. With the chroma gain control ad-

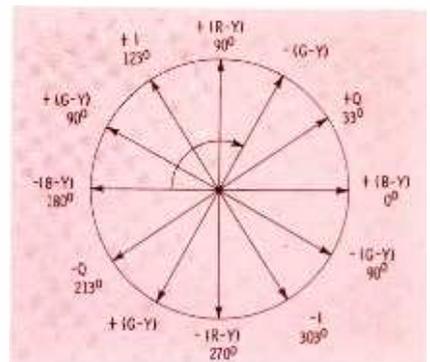


Fig. 7. Phases of a rainbow signal most often used in practical service work.

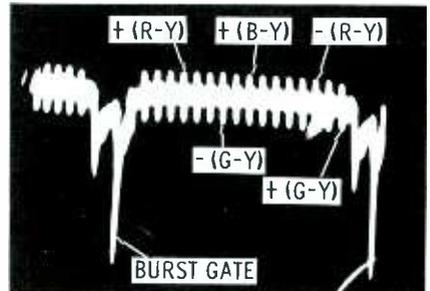


Fig. 8. Crosshatch pattern produces 17 pips along baseline for chroma check.

vanced, the pips appear along the sinewave output from the chroma demodulator, as seen in Fig. 9. As the color phasing control is rotated, the pips change positions or "slide" along the sine wave. Adjustment of the quadrature transformer also causes the pips to "slide." Thus, we have a ready means of checking the G-Y matrix; it is operating properly if we find the 17th pip at the positive G-Y peak (Fig. 9), and the eighth pip at the -(G-Y) peak. Appearance of these pips elsewhere than at the peaks of the sine wave (scope connected at the G-Y matrix output) is an indication of matrix trouble.

Many modern color receivers use R-Y and G-Y demodulators with a B-Y matrix. Principles of test are similar—the same sine-wave pattern, marked in the same manner, will be obtained whether the G-Y section is a demodulator or a matrix. ▲

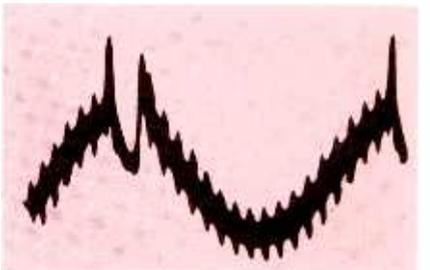


Fig. 9. Turning up chroma gain control produces marked sine-wave pattern.

ElectroVoice[®]

Power Point[®] PLUG-IN CARTRIDGES

are on the move!



Look
for the
E-V
trademark


***Opening Gun in the
Biggest Sales Push Yet!***

**There's PROFIT in E-V Stereo Power Point Cartridges! NEW,
IMPROVED MODELS—USED IN MORE AND MORE PHONOS.
PERFECT FOR CONVERSION TO STEREO NOW—LOW COST!**

These new, improved Stereo Power Points are a gold mine. They out-perform by far the old-style replaceable-needle cartridges. More and more of them are being installed daily in tone arms by manufacturers. Yet they cost the same, or less, than old-style needles alone! Everybody's selling E-V Stereo Power Points for STEREO CONVERSION, too. They're replacing old-style monaural cartridges or inferior cartridges—with one of these new E-V Stereo Power Points. It's easy, it's inexpensive, and each conversion assures a steady stream of replacement sales and PROFITS!

SO—GO E-V, the Power Point way—and listen to the music of your cash register! And remember, this is only the first of a series of promotions in this, E-V's biggest cartridge year!

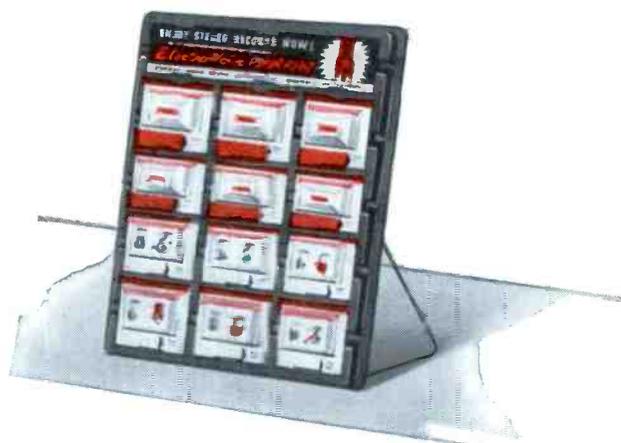**STEREO NOW – BIG PROFITS NOW!
All-Diamond–All-Stereo Rack Makes
Sales–Cash in on E-V Advertising
and Promotion!**



This special, all-diamond, all-stereo promotion is only the beginning!

This marks the start of the biggest year Electro-Voice has ever had for big merchandising—big product news—all good news for you!

Now—if you don't have the details on this opening gun promotion—write Electro-Voice or ask your E-V Rep. You'll get good news!



*Power Point plug-in cartridges are an exclusive development of Electro-Voice, Inc., made under one or more of the following patents: 170,347; 2,793,254; 2,851,541; 2,842,610.

ELECTRO-VOICE, INC., BUCHANAN, MICHIGAN

Let's talk about

VERTICAL SWEEP SYSTEMS

Part 2—Causes and cures for vertical bounce, poor interlace, and various types of sweep distortion— by Allan F. Kinckiner

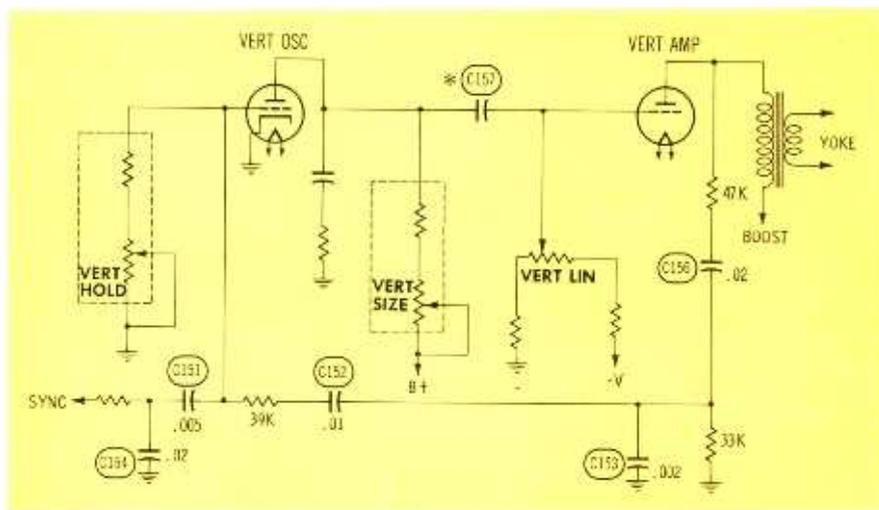


Fig. 7. Replacing C157 cured vertical bounce in an RCA KCS100B portable.

Vertical Bounce and Jitter

Every experienced serviceman is familiar with the vertical bounce found in many of the early Admiral sets. This bounce may often be cured by replacing the vertical-output transformer. Sometimes shunting of the transformer primary with a .05-mfd capacitor does the trick.

Recently, I traced the source of vertical bounce in an RCA KCS47 to the installation of an unpotted blocking-oscillator transformer. This case was resolved by replacement of the unpotted unit with the potted

type used in the original design.

One of the earliest RCA's to use a rectangular glass picture tube developed bounce when someone failed to replace the vertical-oscillator tube shield. The bounce only occurred when the set was in the cabinet, and we nearly lost our minds before this simple omission was discovered.

In an RCA KSC100B, vertical bounce was due to a somewhat different defect. The customer brought in this small portable himself, complaining that it would not hold vertically after it warmed up. Previous experience on this model had taught the serviceman that capacitors C152, C153, and C156 (Fig. 7) were prone to defects. These parts were changed, and the set was wrapped in a blanket to build up heat for a test run. After about 20 minutes, the set developed a most dis-

agreeable vertical bounce. C157, a .033-mfd unit, was temporarily replaced with a .047 unit because a .033 was not in stock. The set was again tested and operated perfectly.

The next day a .033-mfd capacitor was installed, but since the set had better linearity with a .047-mfd unit, a capacitor of that value was finally left in the set. A later job confirmed this observation, and it is now standard practice in our shop to use .047's in this application for all KCS100B's.

When an Admiral 22A2 exhibited vertical bounce, I first thought that it, too, was due to a change in vertical-output transformer characteristics; however, a new transformer did not help. After considerable testing, a waveform check at the video detector showed the pattern in Fig. 8. Note how the blanking level drops into the video area. This distortion was cured by increasing AGC filtering. (A 2-mfd capacitor was installed—negative end to the AGC line and positive end to chassis.) The improvement shown in Fig. 9 was equalled by the improvement in set performance.

Similar results have been obtained by the same means in RCA, Emerson, and other sets that employ

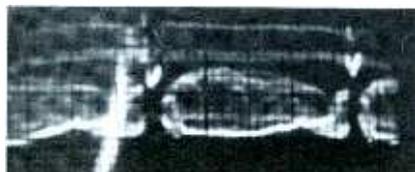


Fig. 8. Inadequate AGC filtering can distort sync and cause vertical bounce.



Fig. 9. Improved video-output waveform after installing 2-mfd AGC filter.

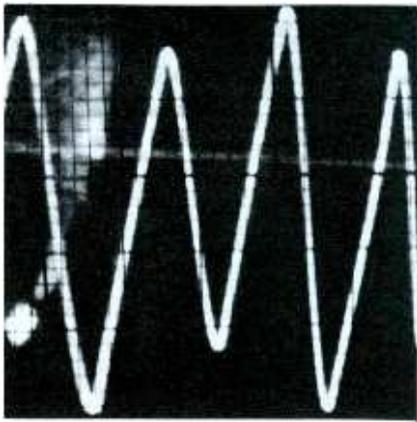


Fig. 10. Unbalanced ripple output of rectifier caused by defective 5U4 tube.

keyed AGC. Occasionally, the added filtering also rids the receiver of bends.

Poor Vertical Interlace

In early model receivers using 10" or 12" picture tubes, less than good interlace was acceptable, since the spaces between scanning lines were not easily noticed. In late model receivers using 21" and larger screens, there is more space between the lines. Should this be further compounded by line pairing, picture detail becomes seriously impaired.

Poor interlace presents itself in two conditions: a steady state where alternate fields are paired at all times, and a fluctuating state where alternate fields pair and interleave rapidly. Both types are difficult to correct, but some suggestions are offered here.

Poor Interlace, Steady

Line pairing is caused when the vertical oscillator is triggered one-half line too early. This type of defect is often due to insufficient high-frequency filtering in the integrator network, permitting the


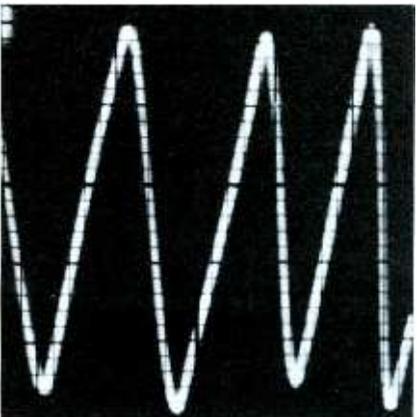


Fig. 11. Improved ripple waveform obtained when 5U4 tube was replaced.

Here's a 2-WAY PROFIT PROPOSITION

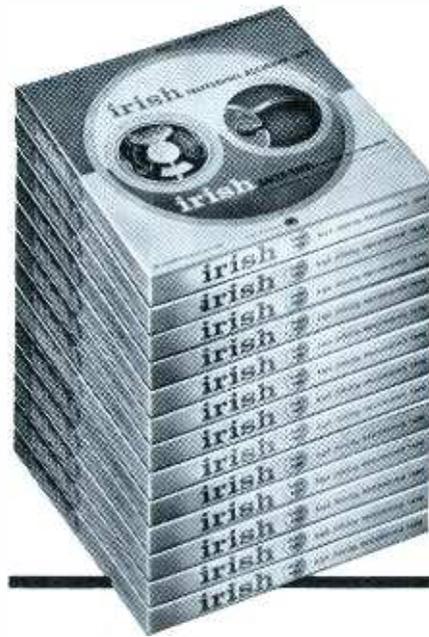from **irish** BRAND
1000 Service Dealers



Over 2½ million tape recorders and 35 million reels of recording tape have been purchased by your customers during the past five years. If you qualify for this special 2-way profit proposition, these expanding sales figures will mean a big additional source of income for you.

With your new **irish** Service Sales Tape Pak, you can confidently take over the servicing of every popular brand of tape recorder in your area and you can supply your customers with magnetic recording tape—in their homes, in your shop—at the moment when sales acceptance and demand are at their highest peak. In short, for an extremely modest investment, you can profitably establish yourself in your community as the expert tape recorder serviceman and franchised dealer of famous **irish** brand recording tape.

To Assure You A Handsome Profit Your **irish** Sales Service Tape Pak Will Include:

- **A COMPLETE TAPE ASSORTMENT—12 REELS \$44.40**
Four each of the three fastest selling items in the **irish** line. You pay only our FULLY DISCOUNTED DEALER PRICE of \$44.40 for the entire twelve reels. *Your profit is \$29.60.*
- **A COMPREHENSIVE TAPE RECORDER SERVICE-MAINTENANCE MANUAL—YOURS FREE**
Prepared specifically for radio and TV service dealers by Howard W. Sams and ORRadio Industries. Complete, detailed, easy-to-follow mechanical and electronic schematics, exploded views and trouble shooting charts on every one of the most popular tape recorders. 208 pages—worth \$4.95!
- **NEWSPAPER MATS—YOURS FREE**
Mats of proven, small-space (2" x 3", 2" x 2") newspaper ads to immediately establish your NEW line of business on a sure-fire profit basis.
- **A 3-COLOR BANNER—YOURS FREE**
This banner (22" x 26") for wall or window, immediately identifies you as a franchised dealer of **irish** brand Recording Tape and expert tape recorder technician!
- **NATIONAL ADVERTISING**
In addition to the items in your Service Sales Tape Pak, you receive the influential support of the consistent national advertising campaign reaching tape, recorder owners in every important market including: the general consumer, the hi-fi bug, the clergy, the schools, professional musicians, etc.



That's our proposition—the rest is up to you!



Dept. N-1, ORRadio Industries, Opelika, Alabama
Your 2-way profit proposition sounds interesting.

- my check for \$44.40 is enclosed
- have your representative call
- send me name of your distributor

FIRM NAME _____
 ADDRESS _____
 CITY _____ ZONE _____ STATE _____
 YOUR NAME _____

THE BIG NEWS FOR 1960

SYLVANIA 23-INCH TV



*Viewing area 275 square inches. 23-inch picture tube measured diagonally.

Big 23-inch* picture is the sensation of 1960 that *changes the face of television . . .* and Sylvania scoops the industry with the first complete line.

- Square corners of the 23-inch* bonded shield picture tube pioneered by Sylvania presents more of the TV picture as the camera sees it. New squared shape is closer to the 3 x 4 ratio of the true TV camera raster.
- The 23-inch* tube flattens the TV screen. "Bonded shield" face-panel eliminates the dust trap, cuts reflections in half, and improves brightness and contrast.
- ◆ New Super HaloLight® is bigger and better than ever. It's a Sylvania exclusive that adds eye comfort to eye appeal.

**SYLVANIA 23"* TV OFFERS THE NEWEST AND
FINEST FEATURES YOU CAN RECOMMEND**

SYLVANIA
Subsidiary of
GENERAL TELEPHONE & ELECTRONICS




Fig. 12. Unequal ripple in Philco set caused by defective selenium rectifiers.



Fig. 13. Improved ripple waveform observed with new seleniums installed.

equalizing pulses to reach the oscillator grid. If the integrator is not defective, its action can be improved by adding a series resistor at the input and a small capacitor to ground at the output. Nominal values for these additions are 22K ohms and .005 mfd.

Another cause of poor interlace is the presence of horizontal pulses at the vertical-oscillator input, a condition due to poor lead dress, poor B+ decoupling, etc. Rerouting all wiring capable of causing such unwanted interstage coupling, plus increasing filter values on lines common to both sweep oscillator circuits may be the only solution.

Poor Interlace, Fluctuating

This is usually more objectionable than the steady type because it also adds a small amount of bounce to the picture. Receivers having troubles similar to that discussed in connection with Fig. 8 are often subject to fluctuating interlace. The cure is the same—increased AGC filtering, particularly on the bias line to the tuner. There are also numerous cases of fluctuating interlace caused by a poorly-balanced full-wave rectifier system. Fig. 10 shows unbalance at the output of a 5U4 rectifier tube with a weak section. Fig. 11 shows the improvement after the 5U4 was replaced. Figs. 12 and 13 were obtained at the same point

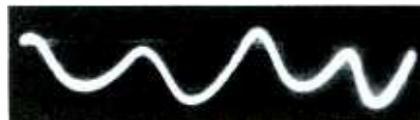



Fig. 14. Cathode signal when both B+ and bypass filters are in the same can.



Fig. 15. Normal signal at the output cathode restored by new bypass filter.

ownership of a **PHOTOFACT** SERVICE DATA LIBRARY SPELLS SUCCESS FOR SERVICE TECHNICIANS

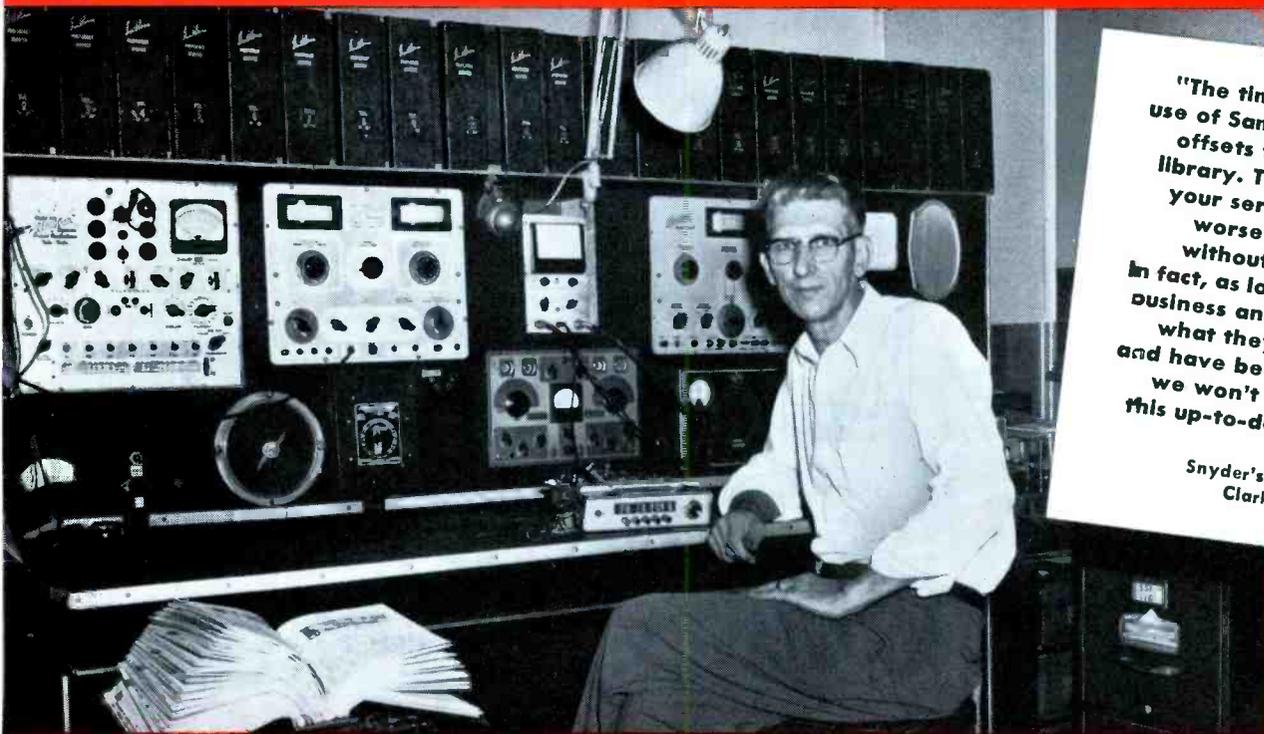here's actual proof from the men who know



"The time saved by the use of Sams more than offsets the cost of the library. To do without your service would be worse than operating without a V.T.V.M. In fact, as long as we are in business and Sams remain what they are today and have been in the past, we won't be without this up-to-date service."

—Frank Snyder,
Snyder's Sales & Service,
Clarksburg, West Va.

HERE'S MORE PROOF...FROM COAST-TO-COAST

ARIZONA

"I would not take anything for my valuable collection of Sams PHOTOFACT."

—Charles S. Cook,
Winslow, Arizona

IDAHO

"My PHOTOFACT library is an indispensable source of service information on the...TV sets serviced in our shop. Without this information, the time required to complete many repair jobs would be prohibitive."

—Richard Huntley,
Craigmont, Idaho

WISCONSIN

"With the PHOTOFACT file to back us, we have complete confidence that we can handle any service problem brought to the shop."

—Howard R. Olds,
Darlington, Wis.

TEXAS

"I don't see how anyone can run a shop without a set of PHOTOFACT. I would be lost without mine. They are a must on any bench job. You can do a faster job with the information in PHOTOFACT."

—T. A. Hopkins,
Quanah, Texas

OHIO

"PHOTOFACT speeds up my service on repairs and the file cabinets help dress up the shop."

—Ed Rahm, Toledo, Ohio

SOUTH CAROLINA

"(With PHOTOFACT) I have a lot less time on the bench and I can do a more complete repair job on a customer's set and have less come-backs because of a perfect repair job."

—Glen Stewart,
Pickens, S. Car.

MASSACHUSETTS

"PHOTOFACT has been one of the mainstays in my service business. The PHOTOFACT library has cut my service time well in half and has more than paid for itself already. In the best words—PHOTOFACT kept my new business in the black."

—Benjamin L. Hall,
Edgarton, Mass.

PENNSYLVANIA

"They are just great. Cuts service time to a minimum."

—Virgil Franceschin,
Barnesboro, Pa.

These are just a few of the hundreds of "Success with PHOTOFACT" letters in our files. Service Technicians everywhere are enjoying the profit-making advantages of a

complete PHOTOFACT Library. If you're not among them, see your Sams Distributor today, or write direct to Howard W. Sams for full details. Use coupon below.


NEW EASY-BUY PLAN! It's the money-saving way to build your complete profit-making PHOTOFACT Library! NO INTEREST—NO CARRYING CHARGE—AS LITTLE AS \$10 DOWN
FREE! Valuable steel file cabinets for PHOTOFACT monthly subscribers and Library purchasers.



Valuable booklet shows you how PHOTOFACT boosts your profit-capacity

FREE!

Send for it!

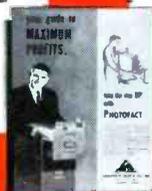

HOWARD W. SAMS & CO., INC.

2201 E. 46th St., Indianapolis 6, Ind.



- Send me Free booklet "Your Guide To Maximum Profits"
 I'm a Service Technician: full-time; part-time

My Distributor is: _____

Shop Name _____

Attn. _____

Address _____

City _____ Zone _____ State _____

FIRST TIME ... a versatile

DUAL

HEAT

SOLDERING GUN

FOR ONLY
\$795
 LIST
 Model 8200K

...and best of all,
 it's a new

Weller[®]

Here from Weller, long time leader in the soldering field, is the newest and finest soldering gun value on the market.

WELLER DUAL HEAT FEATURE saves time, gives greater convenience and greatly increases tip life. A touch of your finger on the Triggermatic control switches heat to high (125 watts) or low (90 watts) as your job requires. It adapts instantly to varying needs, and you use high heat only when necessary.

HIGH EFFICIENCY WELLERTIP utilizes copper for superior heat transfer and soldering efficiency, plus iron plating for durability. Flat cross-section design gives added strength and rigidity.

NEWEST DESIGN with sturdy plastic housing that resists hard knocks. Compact "feel" and comfortable balance aid precision soldering. Like all other Weller guns, this new model features instant heat, and a spotlight illuminates your work.



KIT INCLUDED

In addition to the Dual Heat Soldering Gun you get:

- Wire Bristle Cleaning Brush
- Soldering Aid for opening old joints, twisting wires
- All-purpose Solder

On sale now at your
 Electronic Parts Distributor

WELLER ELECTRIC CORP. • 601 Stone's Crossing Rd., Easton, Pa.



Fig. 16. Vertical-sweep distortion when video signal reaches the output grid.

in a Philco set using two 5U4's. Fig. 12 was the result of one tube being weak; Fig. 13 was taken with two new tubes in the set. In both these cases, the B+ voltage drop was not sufficient to cause symptoms other than the fluctuating interlace.

Distorted Sweep

While the poor linearity discussed at the beginning of the article can be classified as distorted sweep, this writer prefers to consider the following to be more truly representative of the term.

A DuMont RA340, after being serviced for other troubles, displayed a raster with two light horizontal stripes or bars. Close inspection revealed that they appeared to be the result of line bunching. The vertical section used a circuit similar to Fig. 4, except that the linearity control was in the cathode circuit of the amplifier and was bypassed with a 100-mfd, 50-volt electrolytic. Being an avid scope user, the serviceman used it to check this filter and observed the waveform in Fig. 14. The one he should have seen is shown in Fig. 15. Since the waveforms were taken with sweep at 30 cycles, he knew he should have only two peaks and not four. Checking further, he discovered that the cathode filter was housed in a can that also contained the high B+ filter. From this, he figured that coupling was taking place within the can. Replacing the cathode-bypass unit with a separate electrolytic of the correct value cured the condition. This symptom has also been found in Crosley and Emerson receivers using a vertical-amplifier cathode filter en-



Fig. 17. Video feedback from picture tube causes distorted vertical sweep.



Fig. 18. Clean picture after the retrace-blanking network had been modified.

cased in the same can as the B+ input filter.

Another type of sweep distortion is caused by defects in the vertical-retrace blanking network. Usually, defects in this network cause all sorts of strange conditions, such as raster shading, etc. The picture on a Motorola TS-418 with a slightly weak picture tube appeared as shown in Fig. 16. This set uses a negative pulse from the sawtooth-peaking resistor for vertical-retrace blanking. Use of a scope showed that a small amount of video was being fed back to the grid of the vertical-output tube. Fig. 17 shows the waveform on the retrace-blanking line; the encircled pulses are for blanking, and the smaller signals are due to video pickup by the picture tube grid. The retrace-blanking pulse is taken off as shown in Fig. 4, and thus signals fed back along this line will reach the grid of the vertical amplifier. By changing the retrace-elimination circuit to that shown in Fig. 18, the customer was spared the expense of picture tube replacement, and the picture came out as clear as that shown in Fig. 19.

This modification has been made in many different receivers (Muntz, Zenith, and Westinghouse to name

a few), and in every case has worked out superbly. Only one bit of advice is needed: Be sure the pulse taken from the vertical transformer is a negative-going spike.

In conclusion, I'd like to point out that vertical-sweep troubles need not be your nemesis. Pattern your approach after the doctor who tries not to operate before he knows what's wrong; i.e., don't start changing parts indiscriminately just because they *might* be defective. Instead, take a little time to analyze the symptoms and make conclusive tests before you operate. You'll find

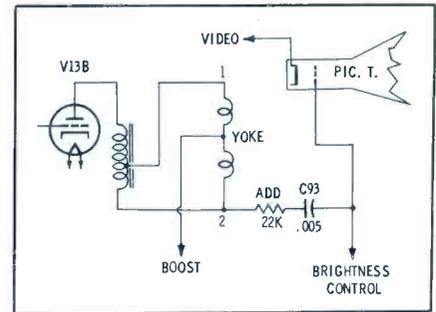


Fig. 19. Modified retrace-blanking network used to cure sweep distortion.

the trouble more quickly, I'm sure, and your disposition will be better, too. ▲

HICKOK

TWICE AS MANY IN USE AS ALL OTHER MAKES COMBINED

World's Leader in Tube Testers!

MODEL 820
\$99⁵⁵ NET
TUBE Caddy-Pal

COMBINATION TUBE-TRANSISTOR-CRT TESTER AND VTVM-OHMMETER

- An innovation in test equipment, designed for radio-TV home service.
- Replaceable 11-socket tube panel for most popular radio-TV—hi-fi tubes.
- Tests low-signal and power transistors, with special high-current test for power transistors.
- Reads Beta gain and reverse current collector leakage.
- Four voltage and three resistance ranges specifically designed for radio-TV service.

MODEL 121
\$299⁵⁰ NET
HIGH-SPEED CARDMATIC®

- A truly modern tube tester—specifically developed for today's critical tube applications.
- Now, you can not only make critical "fringe" tests, but you actually can test such types as 6SN7 and 6BQ6 for pulse operation.
- Its exclusive card-programmed switch, developed and patented by HICKOK, which positively and automatically sets up exact conditions, is the key to the 121's rapid and automatic tests.

MODEL 800
\$159⁵⁰ NET
LOW-COST DYNAMIC MUTUAL CONDUCTANCE


- Dynamic Mutual Conductance tube and transistor-diode checker.
- New leakage and shorts test and new grid current (gas) test feature.
- Lowest cost tester available in its completeness and accuracy range.

MODEL 6000
\$189²⁵ NET
HIGH-SPEED DYNAMIC MUTUAL CONDUCTANCE

- Features the original HICKOK-patented Dynamic Mutual Conductance circuit—the G_m method that has long been accepted as standard in the industry.
- Snap-in master socket panel, easily removable to accommodate future adapters, to prevent obsolescence.
- Reserve cathode capacity test, filament continuity test, extra sensitive shorts test, new gas test.



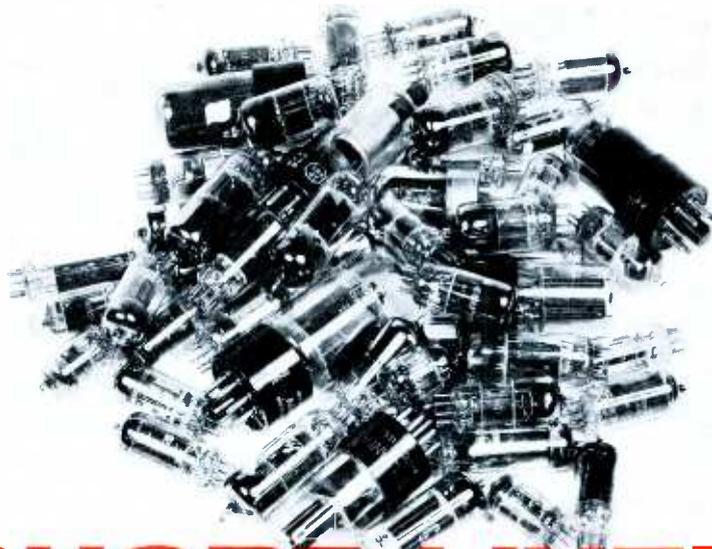THE HICKOK ELECTRICAL INSTRUMENT CO.
10514 Dupont Avenue • Cleveland 8, Ohio



SHORT-LIVED TV TUBES

by Allan F. Kinckiner

While the life span of tubes used in TV receivers varies considerably, a *minimum* figure can be set up as a standard. Depending on the tube type and the use to which it is put, a TV tube may provide trouble-free performance for 3500 hours or more, but a minimum life-expectancy figure should be between 1500 and 2000 hours. This equals approximately one year of operation for the average set. Shorter tube life than this is considered as premature failure, and where a tube repeatedly fails in less than a year's time, a defective circuit component is most likely to be the cause.

Certain runs of tubes do fail in shorter time; however, these failures are most often due to open filaments or interelectrode shorts. It is a credit

to the manufacturers that such defective runs are becoming scarcer. Other types of failures, such as lowered conduction and grid emission or gassy conditions, should definitely be considered symptomatic of circuit defects when they occur prematurely.

Premature failure is not always recognizable; tube appearance is an unreliable indicator (tubes that have been in a set several years often *look* better than others only a few months old). Then, too, you might replace a tube that another serviceman installed a few months previously. Even if you are one of those rare individuals who can translate all the code-dating systems, you would still fail to recognize a recently-installed tube if it had been

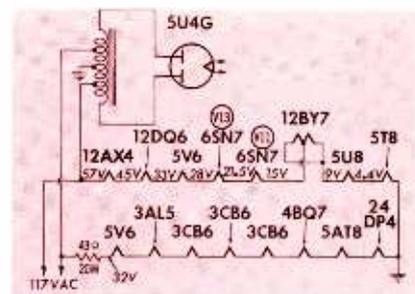


Fig. 2. Filament-string hookup in the case of the short-lived damper tube.

in the other fellow's stock a long time.

Customers can be helpful, but the frequent attitude of set owners is that the tube you just replaced is the same one the other man installed. When an itemized receipt or other evidence backs this contention, you have two alternatives. One is to replace the tube and attempt to get the customer's promise to call you the next time he needs service so you can follow up on the present job. (Leaving a piece of advertising literature with your phone number on it will induce the customer to keep this promise.) The other alternative is to suggest that the customer allow you to take the set in for a bench check; you'll be surprised at the number of times this suggestion will be accepted. More surprising is the number of times a customer himself will suggest a set be taken in, especially if he thinks he has had too much tube trouble lately. Most surprising is that a number of servicemen never make this suggestion, or belittle it when made by the set owner. Customer-serviceman relationships in such cases are discussed in some of the following instances of short-lived tubes.

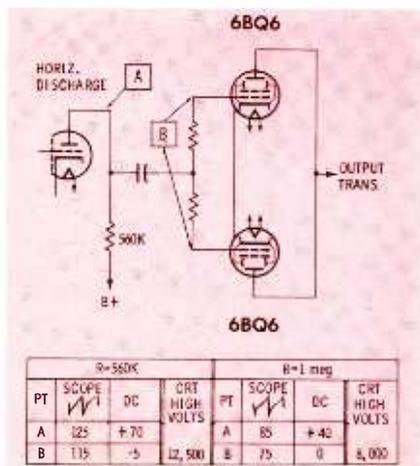


Fig. 1. Repeated burnout of the 6BQ6's was due to an off-value plate resistor.

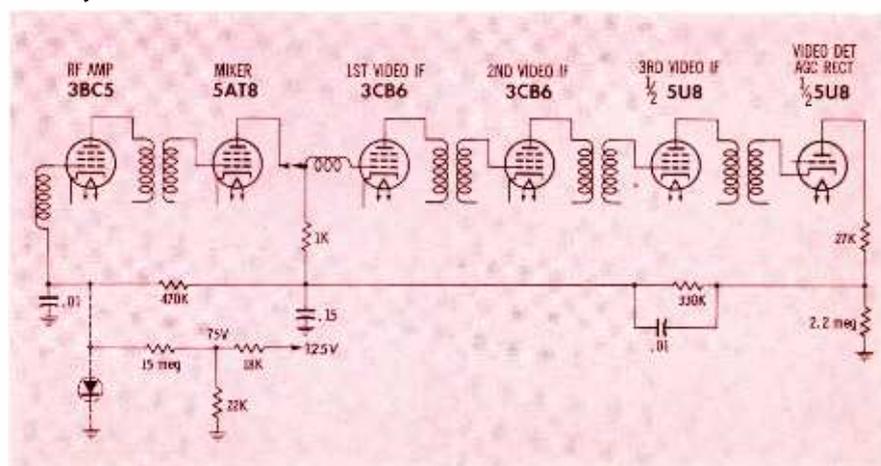


Fig. 3. AGC delay voltage at the RF amplifier grid caused the tube to draw grid current when a clamp wasn't used.

The Case of the Narrow Raster


The first set involved a Zenith 24G26 chassis belonging to one of our newer customers. The raster was narrow by about one inch on both sides. In the home, our man first tried a new 5U4 low-voltage rectifier without any result. Next, he replaced the two 6BQ6 horizontal-sweep amplifiers, and the width became fully adequate—so much so that he had to reduce the width-control setting (which was at maximum). Along about this time, the man of the house came in and told the serviceman that the set required a new pair of 6BQ6 tubes every six or seven months. He wondered if the previous servicemen were using inferior or old tubes. Our man assured him that such was not the case; the tubes just replaced were of good quality and reasonably recent date. Suspecting circuit troubles, the serviceman checked the 6SN7 horizontal oscillator-discharge tube. It also bore a recent code date, and the tube checker declared it to be in first class condition. The serviceman suggested taking the set to the shop for a complete bench check, and the customer readily agreed. He even expressed some enthusiasm over the idea. Here was a serviceman who didn't only change tubes; he tried to determine why the tubes required frequent replacing.

When he brought the set in, he related all the facts to the bench man, and started to hook up the set to demonstrate. He was abruptly stopped by the bench technician who, turning the set on its side, took a reading with the ohmmeter. Only then did he turn the set on, drawing a rough schematic like that in Fig. 1 as he waited for it to warm up. Using a voltmeter and scope, he obtained the figures shown in the table headed "R=1 MEG." The set was turned off, and after replacing the resistor shown in the schematic as 560K (the part he had first measured with the ohmmeter and found to read 1 megohm), the set was again turned on. Scope and voltmeter readings now became those shown in the table headed "R=560K."

Our outside serviceman was impressed with the differences in the readings, but wondered if noting them was really necessary. "Not

"Far better than advertised"

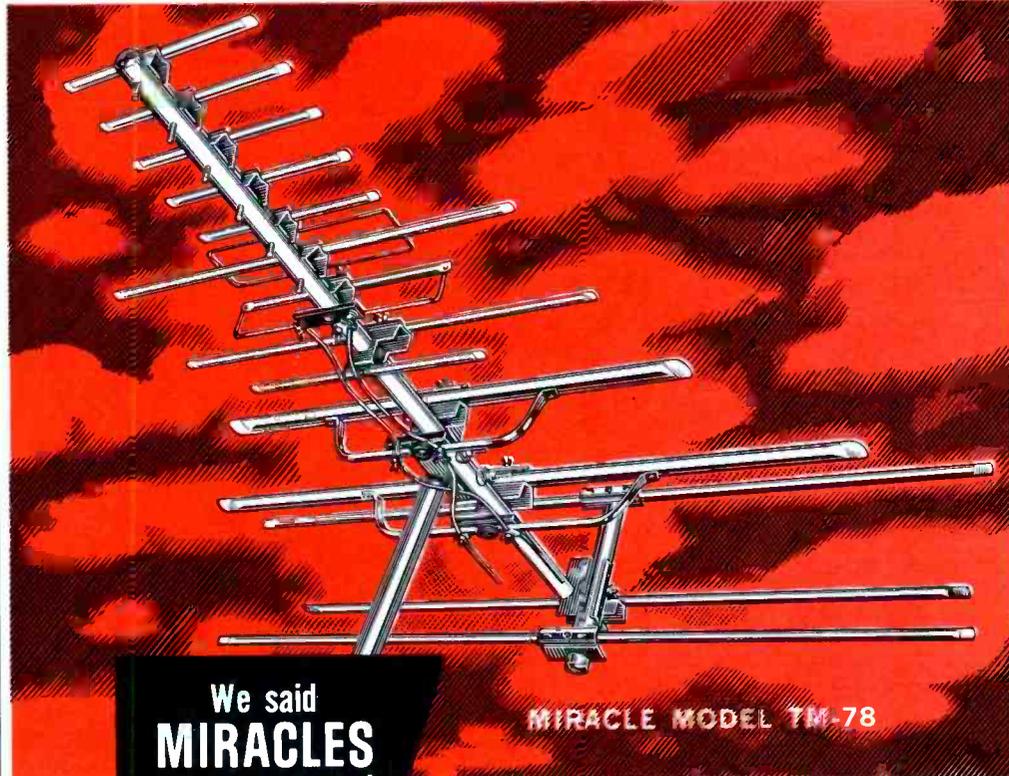...so say Miracle distributors, Miracle dealers and Miracle users!



We said
MIRACLES
are unsurpassed,
they say
MIRACLES
are unequalled

MIRACLE MODEL TM-78

By wire from a
Distributor in Illinois

By phone from a
dealer in Georgia

By letter from a
user in Ohio

Only four months since the new Miracle Antenna with marvelous Miracle Reflector System was first dealer-sold and dealer-tested . . . and already dozens of wires, calls and letters have been received stating that the Miracle far surpasses the claims made in Miracle advertising.

"Front to Back Ratio highest of any antenna ever sold or tested by us".

"After testing Miracle TM-78 with two other popular makes, we are discontinuing (Blank) line and will sell only Miracles in the future".

"Miracles are terrific! Your descriptive literature does not do full justice to model TM-57. It's a wonderful antenna . . . all our friends now envy our picture".

Such unsolicited and unbiased testimony is your assurance of Super Satisfaction when you, too, change to Miracles. Miracles are destined to become America's greatest seller, so be fair to yourself and to your future customers by investigating the Miracle Line of Antennas at once. Write, wire or phone collect for full particulars. Do it now, today . . . you'll always be glad you did!

THE TENNA MANUFACTURING CO. • CLEVELAND 25, OHIO
PHONE VULCAN 3-8080

As "The Man on the Roof" you would Prefer *South River* for making better television antenna installations



Take CHIMNEY BANDING for instance...



Why take this?

The troublesome watchspring effect—Some servicemen have to put up with banding that has a tight spiral "set". Bands of this kind can easily be spotted by their reluctance to stay put. Placement around the chimney is difficult and time consuming.



You can have this

This is the "free-opening" South River Band. Remove the retaining tape and you'll see it naturally unwinds for easy placement around the chimney. That's South River's way of making things easier for the man-on-the-roof.



Make It Easy for Yourself . . . Better for Your Customer


Insist on mountings and accessories made by

South River METAL PRODUCTS CO., INC.
South River, New Jersey

PIONEER MANUFACTURER AND OUTSTANDING PRODUCER OF THE FINEST LINE OF ANTENNA MOUNTING ACCESSORIES

CANADA: LEN FINKLER & CO., TORONTO

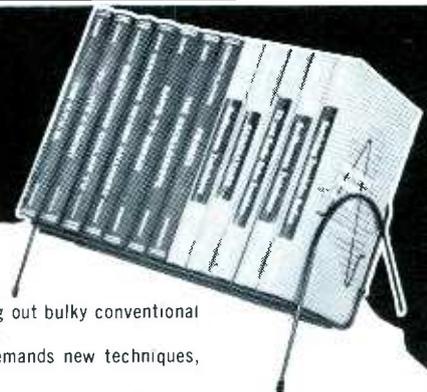YES, you can be an expert on PRINTED CIRCUITS



Printed circuits with their flat, slim look are elbowing out bulky conventional chassis in home and industrial electronic equipment.

But this circuit-shrinking brings in new problems, demands new techniques, requires new knowledge.

Where to get it?—read this new Gernsback book. It takes all the mystery out of printed circuits. Shows you how they developed, how they're made, how to make your own. Describes the special resistors, capacitors, subminiature tubes and semiconductors and other components used with them. Tells you how to work with them, repair them, and finally how to use them in advanced applications. It's practically an encyclopedia on printed circuits. The future of printed circuits is as limitless as space. Learn all you can about them now. It's easy to be an expert. This new deluxe cloth-bound G/L book shows you how. Get it today and see.

HOW TO GET THIS BOOK FOR ONLY \$3.35

Through the G/L Technicians' Book Club you can get this book and others equally valuable for only \$3.35—a 27% saving!

PRINTED CIRCUITS

By Morris Moses
224 pages, Deluxe gold-stamped hard cover.
List price \$4.60

HOW TO JOIN

- Fill in this coupon.
- SEND NO MONEY — we send you the book on approval.
- If you like it, send your remittance; if not, return the book.
- You receive a new book every three months on the NO-RISK approval plan.
- You need take only four books during the entire membership period. No time limit.
- You may cancel any time after that.

NO-RISK COUPON

Gernsback Library Inc. PR-99
154 West 14th St., New York 11, N. Y.

- Enroll me in the G/L Technicians' Book Club. Send me my copy of PRINTED CIRCUITS.
- Send me more information on the G/L Technicians' Book Club.

Name please print

Street

City Zone State

necessary, but it explains the tube-failure mystery," the bench man explained. "I'd be afraid to let the set go back without being sure in my own mind that the discrepancies we found were wholly responsible for the trouble."

"Wouldn't a voltage check across the grid resistor be enough of a check?" the outside man asked.

"The voltage reading on the grid of the horizontal amplifier is the result of the oscillator signal, and since its shape is as important as its amplitude, I prefer to observe the signal with a scope," replied the bench man. "Besides—there's a lot of resistance in the dual 6BQ6 cathode return, and the voltage across the grid resistor only runs a few volts as compared with the 30 or more volts found in sets with low-value or no cathode resistor." The bench man further explained that he had found this condition about thirty times in the past year, which was why he had checked the resistor first. He admitted that the tables were merely for the other man's benefit.

After slight adjustments of the buzz control and quadrature coil, set operation was top-flight. When it was returned to the customer, the increased brightness was readily noted by him. But his crowning comment was, "You made the sound clearer, too!"

The Case of the Troublesome 12AX4

An Emerson chassis #120286 was brought in at the customer's insistence because it had a habit of burning out the 12AX4 damper tube. The circuit in Fig. 2 shows that the set uses a power autotransformer with center tap grounded to the chassis. Tube filaments are series-connected in two strings between opposite sides of the power line and the chassis.

The serviceman suspected that pulse voltages at the 12AX4 cathode were responsible for the breakdowns but, before exploring this possibility, decided to take filament-voltage readings for all the tubes. Measurement across the 12AX4 filament was over 16 volts; all others were close to normal except those across the two 6SN7 tubes V11 and V13. They read only about four

volts each. The 6SN7's both bore the same code date and were of the same make. Replacing them with new tubes restored correct filament voltages all around.

Tube filaments that change resistance with age have never been explained to my satisfaction, and I'm only one of many servicemen who have been puzzled by the condition. Even more puzzling in this instance is why all the surplus voltage appeared across the 12AX4 filament, rather than distributing itself across the entire filament string.

The Case of the 12-Second Warm-Up

An Emerson chassis 120245D was brought in primarily because of a defective filter, but the set owner also complained about having to replace the RF amplifier every eight months or so, when the picture got too dark or would not hold sync. After replacement of the filter, the set was further checked, uncovering the fact that the AGC-controlled tubes were drawing grid current. Allowing the set to become stone cold, new tubes were installed in the RF and the first IF stages, but before turning the set on, a VTVM was connected across the AGC line. When the set was turned on, the meter swung violently positive. Quickly turning the set off, the meter polarity was reversed and the scale set at 60 volts. Now when the set was turned on, it was found that +20 volts was being applied to the grids of the AGC-controlled tubes. The voltage decreased slowly and fell to zero after about twelve seconds, when the regular AGC bias took over.

A study of the simplified circuit in Fig. 3 readily shows where the positive voltage comes from — the voltage divider formed by the 18K and the 22K resistors. It is counteracted in two ways — through DC conduction of the video detector and development of AGC voltage through rectification of the video signal.


It should be noted, though, that if any tube between the antenna and the video detector is slow in reaching its normal conduction level, the positive voltage will be impressed on the AGC-controlled stages even after they have reached full conduc-



**PERFORMANCEWISE,
QUALITYWISE,
and PRICEWISE,**

You can't beat the TARZIAN "HOT ROD" TUNER

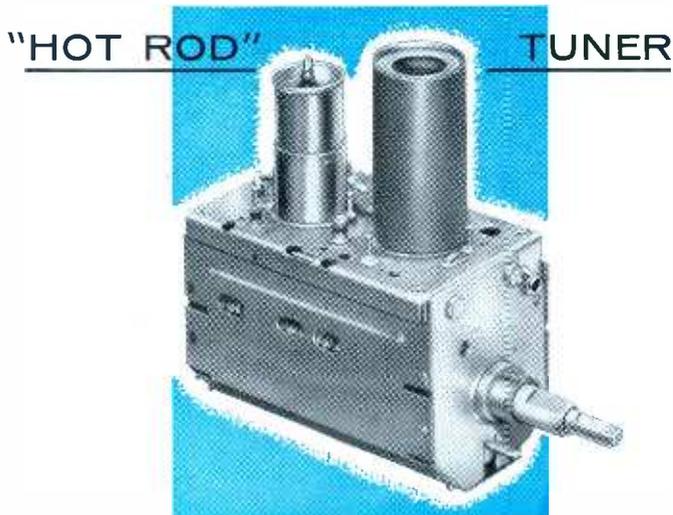Hailed as an engineering triumph, the "HOT ROD" is backed up by 15 years of Tarzian experience in the design . . . development . . . and manufacture of television tuners. This Tarzian "know-how"—coupled with new, automated production methods—brings you the



Engineers like its performance and purchasing agents like the LOW COST. Look at these features:

Tetrode R.F. stage . . . high gain . . . low noise . . . 13 permanent positions . . . easily converted to UHF . . . very low oscillator drift . . . individual oscillator front adjustment . . . small in size . . . good resetability . . . I.F. output tunable from the front . . . and it's adaptable for remote control operation.



Call or write for information

SARKES TARZIAN, INC.

Sales Department, Tuner Division
East Hillside Drive • Bloomington, Indiana

RCA's Top Three for Electronics Technicians!



NEW: RCA WO-33A SUPER-PORTABLE OSCILLOSCOPE

only \$129.95* (complete with Low-Cap Direct Input Probe and Shielded Cable). (Also available as easily assembled kit WO-33A (K) only \$79.95*, incl. above accessories)

Here is your rugged, compact, super-portable scope for those "in the home" color-TV and black-and-white TV servicing jobs! Enough bandwidth and gain for any "tough dog" service job—FEATURING: cable and power cord storage bracket on carrying handle • combination direct/low-cap probe and shielded input cable assembly • voltage calibrated, frequency-compensated 3-to-1 step attenuator • scaled graph screen and calibrating voltage source for direct reading of peak-to-peak voltages • "plus-minus" internal sync holds sync to 4.5 Mc • weight only 14 pounds!



NEW RCA WV-38A VOLT-OHM-MILLIAMMETER

only \$43.95* (complete with batteries, probe and cable with slip-on assembly, and operating instruction). (Also available as easily assembled kit WV-38A (K) only \$29.95*, including above accessories)

You'll get a world of use from this very essential piece of test equipment—FEATURING: extra 1-volt and 0.25-volt ranges for transistor servicing applications • fuse-protected ohms-divider network • polarity reversal switch • full-wave bridge rectifier circuit with excellent frequency response and low circuit loading on the ac ranges • extra large 5½-inch meter with easy-to-read standard ranges • standard dbm ranges.



NEW RCA WV-77E VOLT OHMYST

only \$49.95* (also available as easily assembled kit WV-77E (K) only \$29.95*)

The latest in the famous RCA VoltOhmyst quality line—FEATURING: fuse-protected ohms-divider network • ultra-slim probes and flexible leads • sleeve attachment on handle stores probes, leads, power cord • separate 1½-volt rms and 4-volt peak-to-peak scales for accuracy on low ac measurements • front panel lettering acid-etched for long life!

*User Price (Optional)

See the "top three" plus RCA's complete professional Test Equipment line at your Authorized RCA Test Equipment Distributor!



RADIO CORPORATION OF AMERICA
Electron Tube Division
Harrison, N. J.

tion. This condition can easily lead to a rapid lowering of tube transconductance, or give rise to grid emission and "gassy" operation.

The circuit is almost as old as those for AGC control, and is incorporated for the purpose of keeping bias on the RF stage slightly lower than IF bias. When it was used in earlier receivers, an unused diode section was available—either in a 6AT6, 6T8, or some similar type—for use as a clamp on this delay voltage. Diode sections are at a premium in later sets using -BN6 or -DT6 type audio demodulators, and thus the fact that AGC-controlled tubes are driven pretty hard on initial warm-ups is simply ignored.

We modified this circuit merely by adding a germanium diode as shown in Fig. 3. We used a 1N38, connecting the cathode to ground and the anode to the tuner AGC line. Semiconductors have other advantages; they don't have the warm-up time lag of tube-type diodes, they don't affect normal AGC action, and they have a tendency to flatten the vertical blanking pedestal in some sets. Where this latter improvement has been noted, vertical interlace was slightly better as a result.

The Case of the Self-Service Addict

The frequent need for replacement of 6BQ7's and similar types used as cascode RF amplifiers has led many servicemen to believe such tubes are inherently short-lived. Actually, the short life span of these tubes stems from the same condition noted in the previous case. While their early failure has been noted in receivers of virtually every make, using every type of AGC, it is more prevalent and severe in receivers employing keyed AGC.

A typical case recently involved a Motorola TS-553 which had an extremely snowy picture even though it was located in a prime signal area. On removing the back cover in preparation for replacing the 6BC8 RF amplifier, the serviceman was surprised to find five old 6BC8's lying in the chassis pan. The customer explained that he had been replacing these tubes ever since another serviceman had fixed the

best buys in custom hi-fi... **EICO**[®]

- praised by the experts
- beautifully styled
- priced right for you
- lifetime guarantee




FM Tuner HFT90
with precision "eye-tronic" tuning
Wired \$65.95* Kit \$39.95*
Cover \$3.95.
*Less Cover, FET included
"One of the best buys
you can get."—AUDIOCRAFT.



AM Tuner HFT94
with precision "eye-tronic" tuning
Wired \$65.95. Kit \$39.95.
Includes Cover & F.E.T.

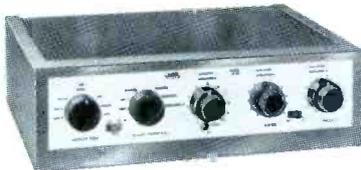**STEREO Dual Amplifier-
Preamplifier HF81**
Wired \$109.95 Kit \$69.95
"Excellent"—SATURDAY REVIEW;
and HI-FI MUSIC AT HOME.



STEREO Dual Preamplifier HF85
Wired \$64.95 Kit \$39.95

STEREO Dual Power Amplifier HF86
Wired \$74.95. Kit \$43.95.
70w STEREO Dual
Power Amplifier
Kit \$74.95
Wired \$114.95

Omni-directional Speaker System HFS2
completely factory-built: 36" h, 15 1/4" w, 11 1/2" d.
Mahogany or Walnut \$139.95. Blonde \$144.95
"Eminently musical"—HIGH FIDELITY
"Fine for stereo"—MODERN HI-FI

Also: **Bookshelf 2-Way Speaker System HFS1**
complete with factory-built cabinet, \$39.95
Other 2-Way and 3-Way Speaker System
Semi-kits, from \$47.50

Plus: POWER AMPLIFIERS (14, 22, 30, 35, 50 and 60-watts)
from \$23.50.
INTEGRATED AMPLIFIERS (12, 20, 32 and 50 watts)
from \$34.95.



best buys in test instruments... **EICO**[®]



**COLOR & Monochrome
DC to 5 MC Lab & TV
5" Oscilloscope #460**
Wired \$129.50
Kit \$79.95



**TV-FM Sweep Generator
& Marker #368**
Wired \$119.95
Kit \$69.95



**DYNAMIC CONDUCTANCE
Tube & Transistor Tester
#666**
Wired \$109.95
Kit \$69.95

IN STOCK at over 2000 neighborhood distributors coast to coast
Send for free catalog



**PEAK-to-PEAK VTVM
#232 & Unit-Probe**
Wired \$49.95
Kit \$29.95
(PAT. PEND.)

EICO, 33-00 Northern Blvd., L. I. C. 1, N. Y. PF-9

Show me how to save 50% on top-quality: Hi-Fi
 Test Instruments Ham Gear. Send free catalog
and name of neighborhood EICO supplier.
 Send free STEREO HI-FI Guide.

NAME _____
ADDRESS _____
CITY _____ ZONE _____ STATE _____

ADD 5% IN THE WEST

only, 1N38's have the low-forward, high-reverse resistance qualities needed for this application.

There are other, more readily apparent reasons for short tube life than those in the cases presented. The most common is premature horizontal sweep-amplifier failure due to excessive screen grid voltage, resulting from decreased resistance in the screen-grid dropping resistor. In sync stages, tubes have been found to fail prematurely because of slight leakage in coupling capacitors. Early loss of transconductance in 6U8 and 6X8 tubes used in video amplifier stages has not yet been pinned down to any circuit fault or component defect.

In addition to developing new types, tube manufacturers are also constantly engaged in improving the quality of commonly-used older types. Improved versions must retain essentially the same characteristics as the prototype so they can be used as replacements. Generally, this requirement is upheld, but our last case concerns a six-year old receiver in which a recently-manufactured tube would not operate properly.

To the serviceman, this call appeared to be simply a matter of replacing a tube. The set was a Zenith 20J22 with varying vertical size. The picture would stretch well beyond the mask outline and then alternately shrink so that it was about an inch short at both top and bottom. Tapping the 6BL7 indicated it was the culprit, so the serviceman stuck in a replacement and proceeded to make the necessary height and linearity adjustments. To his surprise, he could not obtain vertical lock-in, even after trying two other 6BL7's of different brands. Driving to several parts distributors (which luckily were not too far away) he purchased 6BL7's of makes different than those he had already tried. On returning to the job, he was quite chagrined to find that not one of the new tubes would permit vertical lock-in to be achieved. He gave up and brought the set in.

He presented the set and the above information to the bench technician, along with the new 6BL7's, which now included six different brands. Before working on

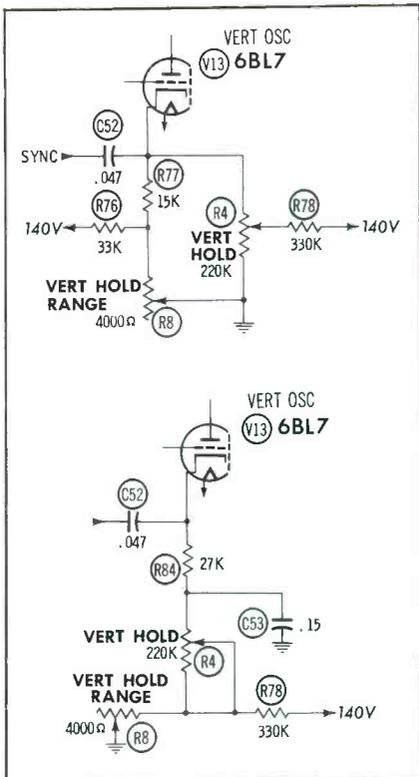


Fig. 5. Alternate vertical-hold control circuits for the Zenith Chassis 20J22.

the set, the bench man borrowed an old 6BL7 from one of the sets in the shop. Sure enough, the set worked perfectly. Delving into the circuit, he found that someone had previously replaced the 4000-ohm, vertical-hold range control with a 2000-ohm, 10-watt fixed resistor. The choice seemed logical enough, and because the set had worked, this type of repair could not be condemned. It also appeared logical that if a 4000-ohm control was now installed, vertical lock-in could be obtained with a new 6BL7 in use—but such was not the case. Further circuit checking turned up the fact that R78, a 330K-ohm unit, had increased in value. The bench man almost had apoplexy after the set still refused to hold vertically with the new resistor in place.

The PHOTOFAC folder indicated that two different circuits were used. The chassis under discussion contained the circuit in Fig. 5A. Since changeover to the alternate circuit shown in Fig. 5B seemed simple enough, the necessary work was done. Now the set would not only hold vertically, but it had that “snap into sync” characteristic so indicative of good vertical lock-in—and with each and every one of the six brands of tubes, too. ▲

THERE'S GOLD IN THIS C-D TREASURE CHEST




The modern way to stock and sell the world's most wanted capacitors. This efficient shop-chest tells you what's in stock and exactly where it is. No more digging for misplaced units. You get an assortment of the most popular C-D “Preferred” type twist-prongs, “Blue Beavers,” and Mylar Tubulars—in handsome metal cabinets. Makes you look more efficient...makes work efficient! Best of all they're FREE with your purchase of capacitors.

See the “Treasure Chest” at your C-D distributor or write for Bulletins to Cornell-Dubilier Electric Corporation, South Plainfield, N. J.



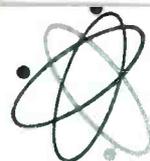Consistently Dependable
CORNELL-DUBILIER
SERVICE CAPACITORS



ELECTRONIC HEATER CIRCUITS

... and how they work

by Melvin Whitmer

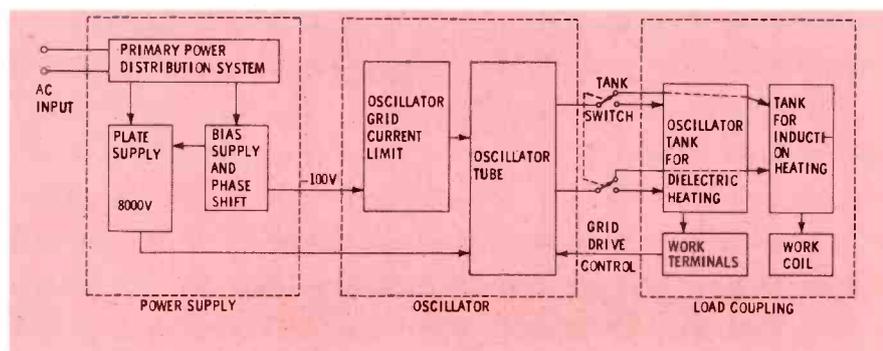


Fig. 1. Typical heater has power supply, oscillator and load-coupling sections.

tion quite often has facilities for controlling the amount of feedback.

Primary Power

AC power distribution for a typical 5-kw electronic heater is shown in Fig. 2. Closing MAIN POWER switch S1 applies AC power through fuses F1 and F2 to the fan, which operates continuously. Closing FIL ON switch S2 supplies primary power to relay K1 and lamp DS1. After S2 is closed, the normally-open contacts of relay K1 close and supply power to filament transformer T1 and bias transformer T4. One secondary winding on transformer T1 couples power to thermal time-delay switch S4, while the others supply filament power to the various tubes. It takes five minutes for S4 to close; thus, tube filaments are permitted to reach operating temperature before

In parts 15 and 16 of this series, dielectric and induction heating applications were described. You may recall a brief statement to the effect that the same heater may supply RF power for either of these applications. This versatility is made possible by simple changeover and load-coupling techniques.

shows how few circuits are really involved in an electronic heater. Note that the primary power distribution system contains protective devices required to save the equipment from self destruction, and that the oscillator section contains filters to prevent harmonic and other spurious oscillations from being radiated. In addition, the load-coupling sec-

The block diagram in Fig. 1

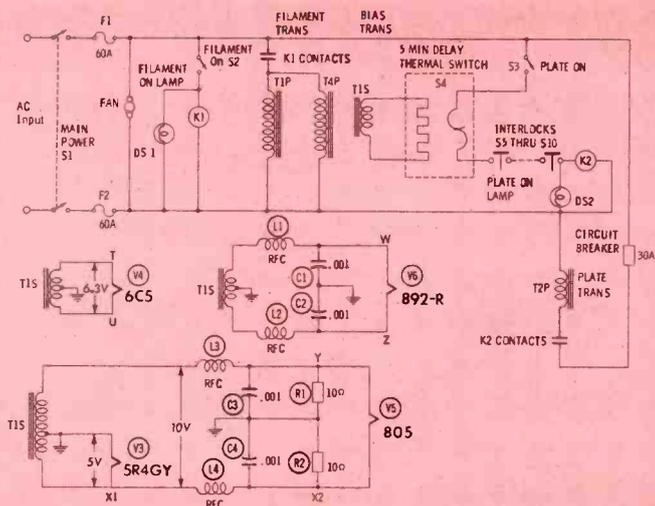


Fig. 2. AC power distribution for a typical electronic heater.

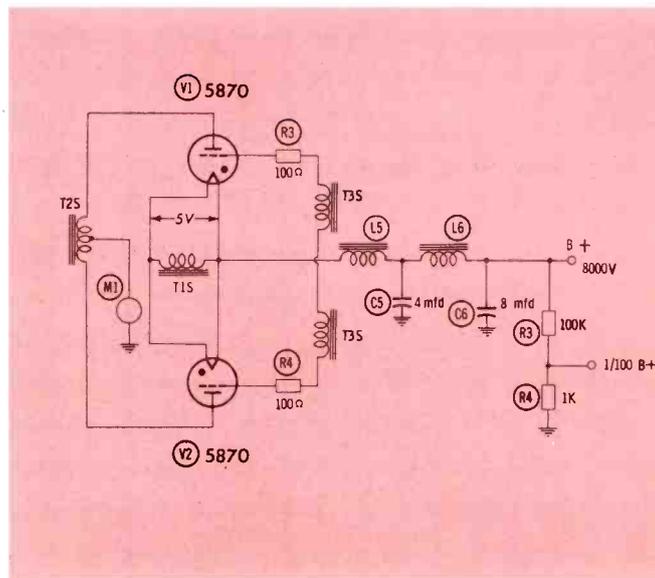


Fig. 3. Power supply uses grid-controlled thyratrons.

plate power is applied.

After the time-delay interval, actuating PLATE ON switch S3 will complete the primary power circuit for relay K2 and lamp DS2, provided all access doors are closed. Interlock switches S5 through S10 interrupt the primary power circuit for K2 when any one of the six access doors are opened, thereby eliminating shock hazards. When relay K2 energizes, its normally-open contacts close and supply power to plate transformer T2. Overload protection for the plate supply is provided by circuit breaker CB, which interrupts the T2P circuit when the plate transformer current exceeds 30 amps.


Plate Supply

The plate supply section is shown in Fig. 3. Transformer T2 supplies high voltage for mercury-vapor thyratrons V1 and V2. These tubes provide an output voltage which is continuously variable from 0 to 8000 volts. Their respective currents are controlled by a phase-controlled AC voltage coupled through T3S to their grids. The phase-shift network consists of T3, P1 and C7, all of which are shown in Fig. 4. Phase can be varied from 0° to 174° by adjustment of potentiometer P1. Fig. 5 shows how various resistance settings for P1 affect phase shift, thyratron conduction time, and output voltage. Conduction time is indicated by the shaded areas in the grid-plate voltage curves, which should help you visualize the control action. Output voltage is included only to indicate the reduction in voltage as phase shift is increased.

Referring again to Fig. 3, filter capacitor C5 charges to about 90% of the peak thyratron plate voltage with no load on the power supply. Power supply loading will decrease the value shown because output voltage is directly related to thyratron conduction time. For any given period of conduction, there is a corresponding value of available power. Since power is the product of voltage and current, an increase in current through the load must result in reduced output voltage.

Oscillator Bias

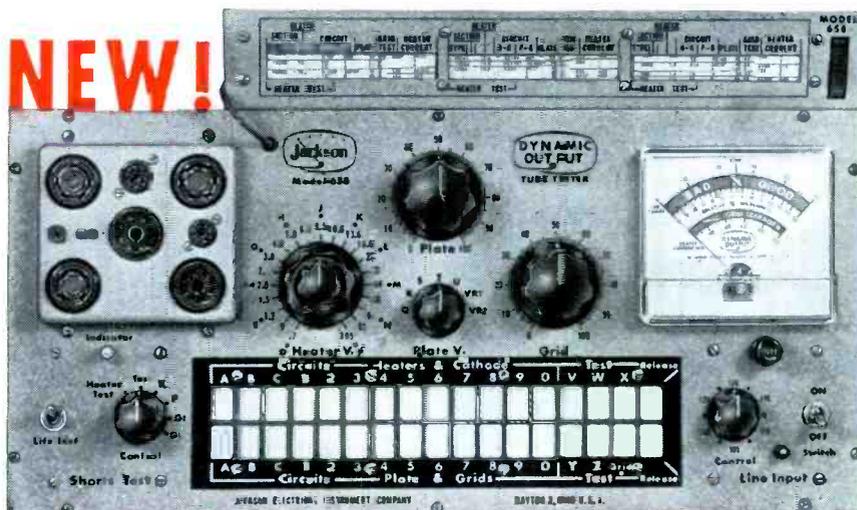Although oscillators generate self bias, large power oscillators are



DYNAMIC[®] OUTPUT 658 TUBE TESTER BY JACKSON

*Makes More . . . and more accurate tests
Than Any Service Tube Tester Ever Made!*

At last, here is a tube tester that will test practically every tube the average serviceman will ever encounter. Faster, more versatile, more accurate for more types, the new 658 is the ideal choice for service, laboratory, and engineering applications.

DYNAMIC OUTPUT PRINCIPLE—3 voltage positions for plate, screen and voltage regulators. Variable DC voltage, plus variable AC signal voltage is applied to control grid. The meter then reads only the AC component in the plate circuit. A much more valid test than mutual conductance, because it considers the entire output curve of the tube, not just a small portion.

TESTS NEW 12-VOLT PLATE HYBRID TUBES—Ample current capacity for even high current space charge grid tubes. The 658 is the only tester made with this capability.

TRUE RECTIFIER TESTS—AC voltages are applied to diodes and rectifiers. Meter then reads plate current—the only valid test for rectifiers. Easily handles even high current rectifiers up to 250 ma.

GRID LEAKAGE TESTS—Highly sensitive grid leakage test indicated directly on special meter scale. Sensitivity of 15 megohms.

TESTS "EYE" TUBES UNDER DYNAMIC CONDITIONS—Eye can be opened and closed to determine accurately its operating limits.

HEATER CURRENT TESTS ON SERIES STRING TUBES—Actual current is read directly on meter scale.

HEATER CONTINUITY CHECK WITHOUT WARM-UP—No wasted time if the heater is burned out.

TESTS ALL VOLTAGE REGULATOR AND REFERENCE TUBES—Actually indicates striking voltage and control voltage range.

PLUS THESE AND MANY MORE FEATURES

Famous Jackson Push-Button Sequence Switching
New Silicon-Rectifier Balanced double-bridge circuit
Triple Shorts Sensitivity Tests to suit each tube
231 Heater voltage combinations from 0.6 to 120 volts
Fused line for overload protection. Panel mounted fuse

Famous Jackson Life-Line Test
Grouped tube sockets for easy accessibility
Complete data for testing more than 1,200 types
Compact portable case—21" l. x 13 3/4" w. x 7" d.
Sockets for 4, 5, 6, 10ktal, octal, miniature 7 and 9 pin tubes plus two for sub-miniatures

SEE IT AT YOUR DISTRIBUTORS OR WRITE TODAY FOR LITERATURE

\$189.95



THE JACKSON ELECTRICAL
INSTRUMENT CO.
16-18 S. Patterson Blvd., Dayton 2, Ohio
In Canada: The Canadian Marconi Company


The Spotlight of Leadership is on...

arkay

Kits and Wired
TEST EQUIPMENT

TODAY'S BEST QUALITY BUY
Comparison proves... you get so much more with Arkay! Advanced engineering • exclusive new features • outstanding performance • truly hi-precision professional quality at amazing low cost. Prove it to yourself—at your distributor now.

EXTRA-LARGE Easier-to-Read 6" METER!

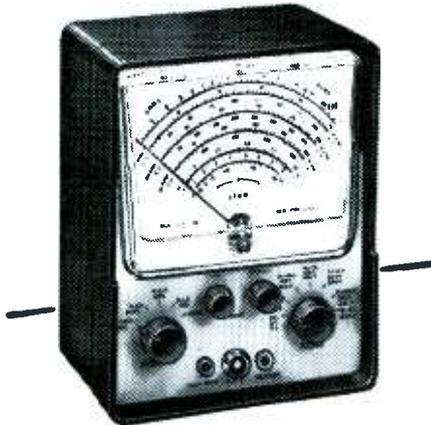

ARKAY VT-10 6-INCH MULTI-PURPOSE VACUUM TUBE VOLTMETER

For faster accurate servicing, the ARKAY VT-10 VTVM has exclusive larger 6-INCH meter, edge-lighted, for easier reading, 400 uA meter movement within 2% accuracy. 1% precision multiplier resistors are used throughout the range switch. There are 7 AC (RMS) and DC ranges, 0 to 1500 volts; also 7 AC (peak-to-peak) ranges, 0 to 2000 volts. Resistance of 0 to 1000 megohms, db and other essential ranges also included. Circuitry features 12AU7 for DC ranges, 6A15 for AC, meter diodes rectifiers, and transformer operated selenium rectifier. Handsome durable plastic case. A sensational quality buy, unmatched at this price!

Wired and tested \$47.95 Easy-to-build Kit **\$25.95**



ARKAY AV-20 6-INCH AUDIO VTVM PRE-AMPLIFIER

An Audio Vacuum Tube Voltmeter of extreme sensitivity, engineered for accurate measurements of RMS voltages.

Easy-to-build Kit **\$29.95**
Wired and tested \$49.95



ARKAY AW-30 6-INCH DIRECT READING AUDIO WATTMETER

Measures Audio Power Output with speed and precision. 0 to 500 watts in 6 ranges. For laboratory and general use.

Easy-to-build Kit **\$29.95**
Wired and tested \$49.95

ARKAY CA-40 6-INCH DIRECT READING CAPACITY METER

Easy-to-build Kit **\$29.95**
Wired and tested \$49.95

ARKAY MT-50 6-INCH 20,000 OHMS PER VOLT METER

Easy-to-build Kit **\$29.50**
Wired and tested \$42.95

All prices 5% higher west of Mississippi.

See ARKAY completely wired Test Instruments at your dealer. Write for detailed specifications and catalog. Write Dept. PF

arkay **PACE** **MEMO**

88-06 Van Wyck Expressway Richmond Hill 18, N.Y.

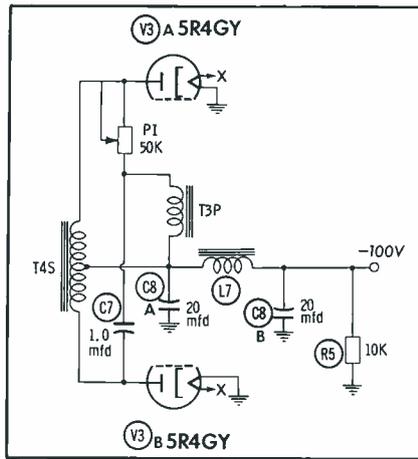


Fig. 4. Bias supply includes phase-shift network for controlling the thyratrons.

often protected by returning the control grid to a fixed negative voltage source. The normal operation of the oscillator remains unaffected because the fixed bias is much less than the self-generated bias. If oscillation ceases, however, the fixed bias limits oscillator plate current to a safe value. Transformer winding T4S (Fig. 4) supplies AC to bias rectifier V3 and the phase-shift circuit. The bias voltage of -100V is developed by the grounded-cathode (filament) rectifier and a pi-type filter located between the tap on T4S and ground. This voltage is applied to the oscillator grid through grid-current meter M2, R6, R7, R8, and radio-frequency choke L14 at the lower left in Fig. 6.

The bias voltage also acts as plate voltage (negative voltage to a cathode causes the same action as positive voltage to a plate) for current-control tube V4. Oscillator grid current through R6 develops bias for V4, and the plate current of V4 flows through R9 and develops bias for V5. The conduction level of V5 determines how much feedback signal will be applied to the grid of the power oscillator. Heavier conduction of V5 means less feedback and therefore less oscillator output power.

Power Oscillator

The power-oscillator circuit shown in Fig. 6 may be converted from a dielectric to an induction heating application simply by changing the tank circuits. Two separate oscillator coils provide a Colpitts-connected high-frequency circuit for dielectric work, or an Armstrong-connected low-frequency circuit for

TARZIAN Offers 48-Hour, Direct Factory Service on Tuner Repairs

only **\$7.50**

That's right. Net, \$7.50 per unit and \$15 for UV combinations, including ALL replacement parts. 90-day warranty against defective workmanship and parts failure. Tuners repaired on approved, open accounts. Replacements offered at these prices* on tuners not repairable:

- VHF 12 position tuner . . \$22.00
- VHF 13 or 16 position tuner 23.00
- VHF/UHF combination . . 25.00
- UHF only 15.50


*Subject to change



Tarzian-made tuners are easily identified by this stamping on the unit. When inquiring about replacements for other than Tarzian-made tuners, always give tube complement . . . shaft length . . . filament voltage . . . series or shunt heater . . . IF frequency and chassis identification. Use this address for fast, 48-hour service:

SARKES TARZIAN, Inc.

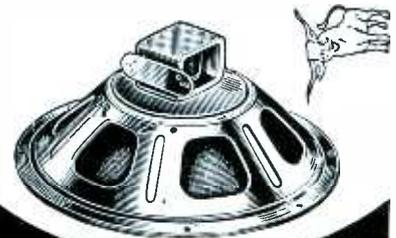Att.: Service Mgr., Tuner Division
East Hillside Drive
Bloomington, Indiana



SPEAKERS for SOUND INSTALLATION

Regardless of your application . . . P.A., inter-com, outdoor, extended range . . . OXFORD is the SPEAKER for you. Our very complete line includes speakers that will meet your every need . . . quality . . . delivery. Write for our new catalog today.

Leading distributors carry OXFORD COMPONENTS, INC.
556 West Monroe Street
Chicago 6, Illinois
Export: Roburn Agencies, New York
In Canada: Atlas Radio, Toronto

OXFORD
OXFORD BRANDS: Supreme Transformers, Hudson Lamps, Tempo Hi-Fi, Oxford Speakers & Rear Deck Kits.

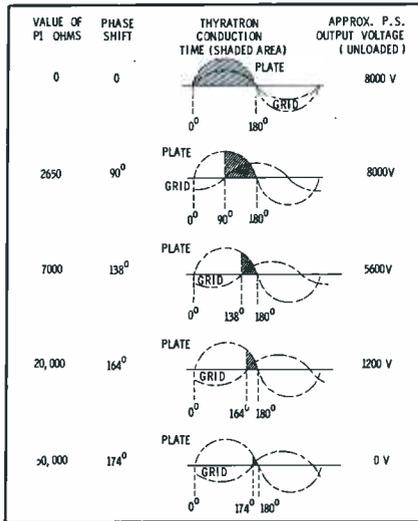


Fig. 5. How grid-signal phase affects conduction time and output voltage.

induction work. Copper connectors are bolted between the tube circuit and corresponding points on the desired oscillator coil. To change oscillator coils, the connectors are simply transferred from one oscillator coil to the other.

As an oscillator, this circuit differs from the local oscillator in a radio receiver and the variable-frequency oscillator in a transmitter in two respects. First, radio-frequency power is consumed by the load in large quantities. Second, tubes V4 and V5 limit the grid current. Neither of these features are encountered when the oscillator simply functions as an exact frequency source.

The first difference, that of power consumption, makes the oscillator change frequency. A normal frequency drift when changing from minimum to maximum load is 10% of the no-load oscillator frequency. Therefore, a dielectric heater operating at 27.3 mc without a load may



Here are two problems you won't have to face when you replace with Sylvania

Problem No. 1:

Which type replaces which?

Sylvania has the most complete line available. And your Sylvania distributor has them in stock. The full line listed here equips you to replace the output transistors of every major auto-radio make. To make your job easier, Sylvania has prepared an interchangeability chart—available from your Sylvania Distributor.

Sylvania's Auto-radio Transistor line

2N155	2N242	2N296	2N350	2N677
2N176	2N250	2N301	2N351	2N677A
2N235	2N255	2N301A	2N399	2N677B
2N235A	2N256	2N307	2N401	2N677C
2N235B	2N257	2N307A	2N419	2N678
2N236B	2N285A	2N326	2N420	2N678A

Problem No. 2:

The broken mica washer

More often than not the mica washer flakes when you remove the output transistor from the auto radio chassis. To save you time and money, Sylvania now packs a tight-fitting mica washer with every transistor. Next time you need an audio power transistor—get it from your Sylvania distributor and ask for Sylvania by name.

SYLVANIA
 Subsidiary of
 GENERAL TELEPHONE & ELECTRONICS



SYLVANIA ELECTRIC PRODUCTS INC.
 Semiconductor Division
 100 Sylvan Road, Woburn, Mass.

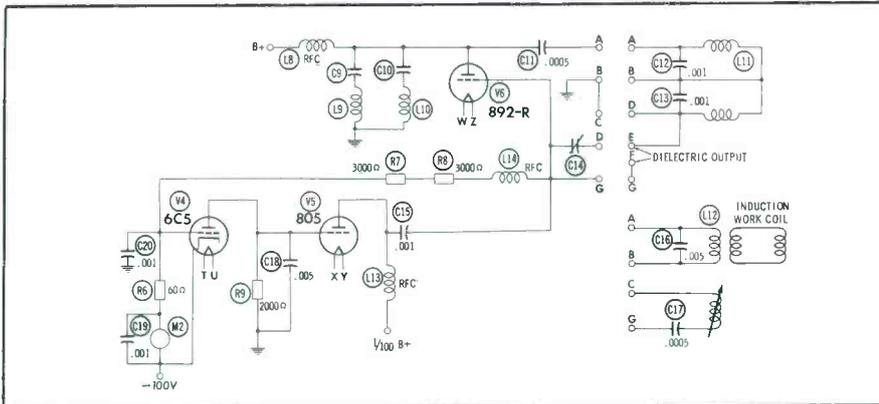


Fig. 6. This power oscillator circuit features automatic signal-feedback control and may be used for either dielectric or induction heating applications.


operate at 25 mc when loaded to capacity. For this reason, electronic heaters are usually operated within a shielded room or enclosure to prevent undesirable radiation.

The second difference, use of control tubes V4 and V5, guards against excessive grid current. When RF feedback drives the oscillator grid positive, it conducts to charge the feedback capacitor (C14 or C17). As the RF signal swings negative, capacitor discharge current flows through R8, R7 and R6. Voltage developed across R6 forms the input signal for V4, driving this tube toward cutoff. If the RF feedback voltage causes oscillator grid current of 165 ma or more to flow, the resultant voltage across R6 drives V4 to cutoff. This, in turn, removes the bias from V5 so that the next positive RF swing at the grid of V6 is clamped by the conduction of V5. Grid current for V6 is thus limited to a safe level.

Load Coupling

Any one of the four capacitors in the Colpitts oscillator network may be replaced by the work in a dielectric-heating application. Substituting the work for capacitor C11 provides increased coupling when the dielectric constant of the work is low. Thus, the tank circuit receives a greater push when the work is consuming the greatest amount of power. Using output terminals instead of tank capacitor C12 or C13 removes the DC plate voltage from one side of the output terminals, but does not provide compensation for changes in the dielectric constant of the work. The oscillator frequency changes more when the work replaces one of the tank capacitors than it does when the work replaces either of the output coupling capacitors. Replacing C14 with the work provides increased coupling for a material with a low dielectric constant. The regular output terminals shown in Fig. 6 have less DC voltage across them than plate-coupling capacitor C11. Making the grid-coupling capacitor C14 variable widens the dielectric-heating applications of the circuit because oscillator grid drive can be adjusted to compensate for different work properties.

Load coupling for induction heat-

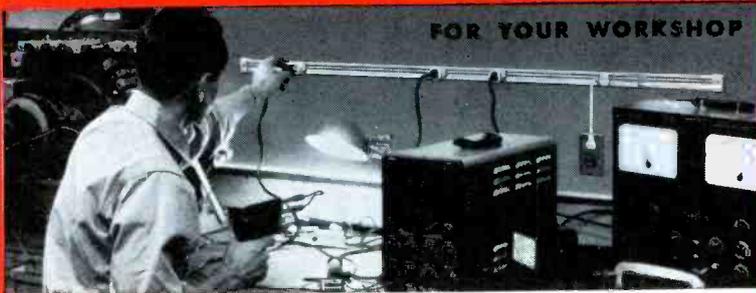

New electrical outlet convenience

Electrostrip

PATENTED [®]
"4-FOOTER" KIT \$2.95 →

Only five minutes to install it . . . then a twist of the wrist puts an electrical outlet right where you want it on Electrostrip! Here is ideal electrical convenience for your shop and for your displays. Electrostrip is the ideal solution to the problem of extra outlets in limited space . . . eliminates extension cords and "octopus" plugs. The "4-footer" Kit comes complete with 3 twist-in receptacle plugs, necessary screws, and handy polarized plug-in connector.

Write us for details on the Electrostrip "4-Footer" Kit, the "15-Footer" Kit, or the bulk rolls. Electrostrip is listed by Underwriters' Laboratories.



BULLDOG ELECTRIC PRODUCTS DIVISION
I-T-E CIRCUIT BREAKER COMPANY
 BOX 177 • DETROIT 32, MICHIGAN

In Canada: 80 Clayson Rd., Toronto 15, Ont. Export Division: 13 East 40th St., New York 16, N.Y.




ing must be based on generating a magnetic field around the work. Thus, a portion of the tank coil or a coupling loop must be used. Using an extension of the tank coil is usually difficult because of mechanical problems, in addition to maintaining the proper tank coil inductance. The most satisfactory method of coupling power to the load is through a low-impedance link. The link eliminates the above problems and permits low-impedance power transmission over considerable distances. Several applications described in the August issue used link coupling to facilitate impedance matching.

Harmonic Suppression

Lead inductance and stray capacitance are often large enough (due to the physical size and spacing between components) to resonate at points near the second harmonic of the power oscillator. The resultant spurious radiation not only wastes power, but also interferes with various radio services. To counteract this radiation, lumped elements that resonate at the same frequency are connected from the oscillator plate to ground. Two such networks (called suppressors) are shown in Fig. 6. The network of C9 and L9 passes one spurious frequency to ground, while C10 and L10 pass the second harmonic to ground.

This concludes the coverage on electronic heating units. In the next installment, we'll deal with open and closed loop recorders. A discussion on the three most popular types of electro-mechanical pen positioners will be included, along with service hints and typical troubles. ▲

Guess Who?

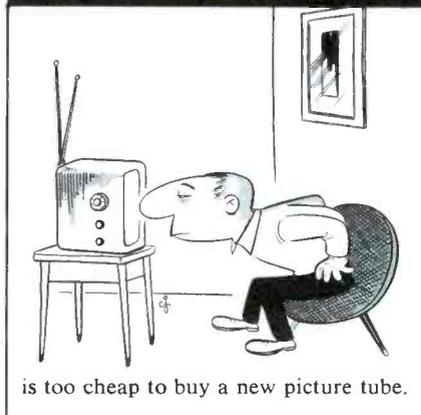

You can now **guarantee reliability** if you join Pyramid's

GOLD RUSH

BURTON BROWNE, New York

Pyramid's New "Gold Standard" $\pm 10\%$ Mylar® Capacitors

Imagine, capacitors that "absolutely guarantee reliability"! Pyramid's new "Gold Standard" capacitors, designed to give a critical tolerance of $\pm 10\%$ with non-hygroscopic Mylar dielectric, plus high resistance to moisture and high insulation resistance. Standard capacity values! Standard voltage ratings! Standard tolerance of $\pm 10\%$! Previously made only on special order and at premium prices, new "Gold Standard" capacitors are now available to servicemen at a price competitive with ordinary paper capacitors.

For reliability assurance, insist on Pyramid "Gold Standard" capacitors from your distributor. Catalog available.

PYRAMID

Pyramid Electric Company, North Bergen, N.J.



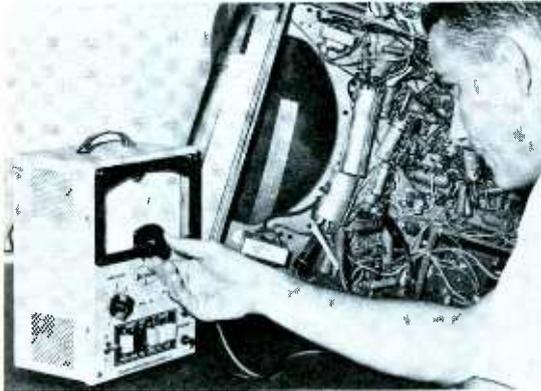


Fig. 1. Jackson's capacitance checker uses bridge circuit and tuning-eye tube.

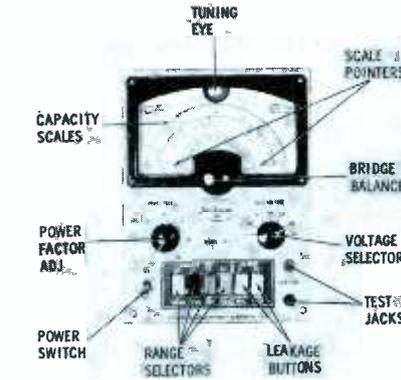


Fig. 2. Front-panel features of the Model 591. Push buttons are color-coded.

An "Eye" for Capacitors

When troubleshooting at the bench, why do we often suspect a capacitor is causing the trouble? Isn't it because we've been able to readily check the other components with tube tester and ohmmeter, saving the capacitors for last because we feel that they are difficult to test? Thus, the innocent looking capacitor often gives us our toughest "dogs," and we're prone to suspect it on every job that defies us longer than average.

I have emphasized this point to call your attention to the instrument being used in Fig. 1. Manufactured by the Jackson Electrical Instrument Co. of Dayton, Ohio, the Model 591 Capacitor Tester fulfills a wide range of applications, including tests for shorted, leaky, open, intermittent, value and power factor conditions.

Specifications are:

1. Power Requirements—117 volts, 60 cps; power consumption approximately 20 watts; transformer provides line isolation.
2. Capacitance Measurement—7 individual scales for 4 overlapping ranges covering from approximately 10 mmf to 1000 mfd; special scale for values above 30 mfd; open, shorted, or

intermittent conditions automatically indicated by tuning eye; push-button range selector and test leads provided.

3. Leakage Tests — measurements for both polarized and non-polarized capacitors made under 7 different working voltages up to 500 volts; special low-voltage range for transistor-circuit capacitors; conditions indicated by tuning eye; capacitor automatically discharged by releasing push buttons.
4. PF Check — power factor measurement for all electrolytic capacitors from .1 to 1000 mfd; tuning-eye indications provided by setting of separate 0 to 60% control on front panel.
5. Size and Weight—10" x 7½" x 5"; 10 lbs.

Examining and using the Model 591 on the bench, I checked a large quantity of capacitors ranging in value from 10 mmf to 350 mfd—those found in typical radio and television applications. I was most impressed by the simple, straightforward indications I was able to obtain. Since the unit is not designed for any kind of in-circuit testing, the results left no doubt as to the condition of each capacitor.

The instrument employs an impedance-bridge circuit which balances a known standard against the unknown with proper setting of a potentiometer on the front panel. A 6E5 tuning-eye tube serves as a bridge detector and indicating device for all tests. As pointed out in Fig. 2, the front panel also features a voltage selector for leakage tests, and a power factor control to determine the percentage directly.

The range-selector buttons are color-coded (green, red, black, and grey) to match corresponding arcs on the capacity scales. The bridge balance control has a rotation of only about 300°, but with two scale pointers attached to its shaft, its effective scale length is increased considerably. The dual pointers move in a

windmill-like fashion — the longer one indicating capacity on the outer scale arc, and the shorter on the two inner arcs. A complete test takes only two steps — one for leakage and one for measurement of capacitance.

When testing paper and mica capacitors, I first turned the instrument on and allowed it to warm up. Then, I connected the questionable component across the test jacks. Incidentally, the instruction manual mentions the fact that small-value mica capacitors must be connected directly to the test jacks in order to obtain an accurate reading. This, of course, eliminates any stray capacity introduced by the two test leads. Through actual trial and error, I found that the test leads seem to have little effect on units with values above 200 mmf, but a great deal on those below.

Getting back to the procedure, I next set the voltage selector to a position as high as possible without exceeding the rated value of the capacitor under test. (If the value of a paper type is above 1 mfd, however, the selector should be set to its 200 volt position.) To test for leakage, I pressed the leakage button labeled PAPER-MICA and took note of the eye tube at the top of the front panel. If the eye opens as pictured in Fig. 3A, the capacitor passes the test; if it remains closed as in Fig. 3B, the unit has excessive leakage and should therefore be discarded. For some capacitors, especially those of higher value, I found that it may be necessary to hold the leakage button in for 15 seconds or so before evaluating the test results.

Following instructions, I continued with the second step of the procedure and pressed one of the range-selector buttons covering the approximate value of the capacitor under test. Watching the tuning eye, I rotated the bridge balance knob until I obtained a circuit balance which produced the widest eye opening. I was then able to read capacity value on the scale corresponding to the range I had selected. If the capacitor is open, circuit balance will only occur at the far left end of the scale. With a shorted unit, on the other hand, a balanced indication will occur only at the far right end of the scale. These areas are labeled OPEN and SHORT, respectively. I also noted in this test that intermittent capacitors will show either open, shorted, or excessive change in capacity whenever they are tapped or slightly heated.

Electrolytic capacitors are tested in much the same manner; however, in the value range from .1 to 1000 mfd, the control marked POWER FACTOR is connected in the bridge circuit and must be adjusted in conjunction with the balance knob to obtain the widest eye opening. If a balance cannot be obtained at any setting of this control, the component undoubtedly has a power factor higher than 60% and should therefore be rejected. In testing electrolytics for leakage, I noticed in some cases that I had to wait for a minute or so before their plates would form sufficiently to produce an opening of the eye.

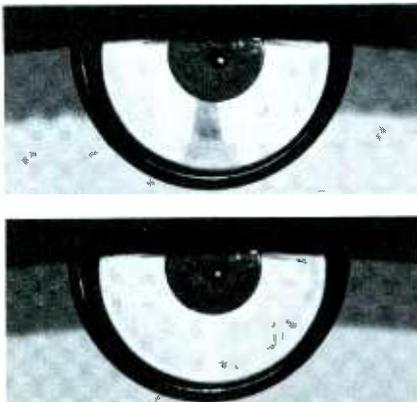


Fig. 3. Appearance of the indicating "eye" in open and closed positions.

A New VTVM

The piece of equipment shown in Fig. 4 is a Model VT-10 vacuum tube voltmeter by Arkay of Richmond Hill, New York. Housed in a black plastic case and featuring a wide-angle scale, it comes in either kit or factory-wired form with two test leads plus a DC probe and cable.

Specifications are:

1. *Power Requirements*—105/120 volts AC, 60 cps; power consumption about 7 watts; 1.5-volt battery supplied.
2. *DC Voltmeter*—ranges 0 to 3, 15, 75, 150, 300, 750, and 1500 volts; zero center-scale ranges 0 to 1.5, 7.5, 37.5, 75, 150, 375, and 750 volts; input resistance 11 megohms; both + and — positions on function switch; balance control provided for zero and center-scale adjustments; 1 megohm isolation provided in DC probe.
3. *AC Voltmeter*—rms ranges 0 to 3, 15, 75, 150, 300, 750, and 1500 volts; peak-to-peak ranges 0 to 8, 40, 200, 400, 800, and 2000 volts; peak-to-peak scales in red.
4. *Ohmmeter*—0 to 1000 megohms in 7 ranges of $R \times 1, 10, 100, 1K, 10K, 100K,$ and 1 meg; center-scale value 10; circuit powered by self-contained 1.5-volt battery; zero and ohms-adjust controls provided on panel.
5. *DB Meter*—3 ranges from -10 db to +58 db on AC voltage ranges of 15, 150, and 1500 volts; direct-scale reading from -10 db to +18 db; zero db=6 milliwatts across 500-ohm line.
6. *Panel Meter*—6", 400-ma movement with burnout protection; accuracy within 2%.
7. *Size and Weight* — $7\frac{3}{4}'' \times 6\frac{1}{2}'' \times 4\frac{1}{2}''$; 3½ lbs.

Examining one of the factory-assembled units in the lab recently, I found it possessed all the versatility one could want for radio and TV troubleshooting. Since the manufacturer made no direct mention of the instrument's accuracy,

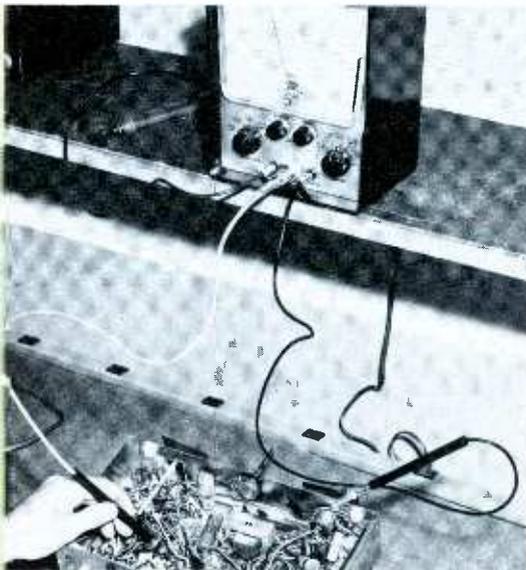


Fig. 4. Model VT-10 AC-powered VTVM is designed for both lab and bench use.

Hit any target



with
Centralab
Universal Shaft
Model B
Radiohm® Controls



If you're aiming for faster servicing and greater profits, ask for CENTRALAB Model B Controls. These are the only replacement carbon controls with a truly universal shaft that adapts to any application.


For any shaft target—split knurl, shallow flat, deep flat, half round, round, etc.—the Model B hits the bulls-eye. Its universal fluted, knurled-type shaft adapts to all knobs perfectly. AC Line switches snap right on, trigger-quick, to convert the control to a switch type unit.

Shoot right over to your CENTRALAB distributor and stock up on Model B Controls . . . and while you're there, be sure to Tell him you want your free copy of the brand-new CENTRALAB catalog.

Centralab
B-5957

A DIVISION OF GLOBE-UNION INC.
 942 I. EAST KEEFE AVE. • MILWAUKEE 1, WIS.
 IN CANADA: 669 Bayview Ave. • Toronto 17, Ont.

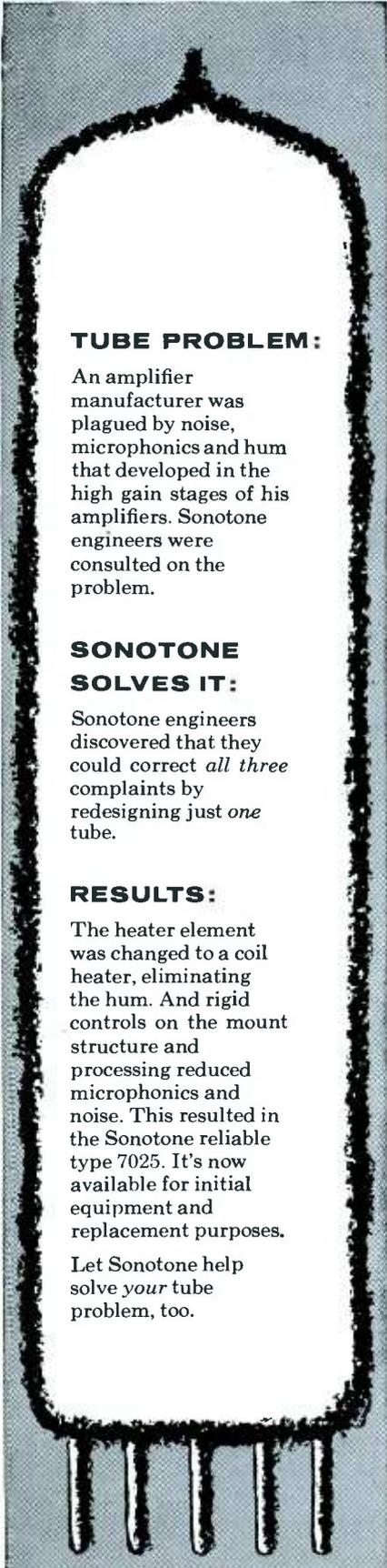CONTROLS • ROTARY SWITCHES • CERAMIC CAPACITORS
PACKAGED ELECTRONIC CIRCUITS • ENGINEERED CERAMICS



TUBE PROBLEM:

An amplifier manufacturer was plagued by noise, microphonics and hum that developed in the high gain stages of his amplifiers. Sonotone engineers were consulted on the problem.

SONOTONE SOLVES IT:

Sonotone engineers discovered that they could correct *all three* complaints by redesigning just *one* tube.

RESULTS:

The heater element was changed to a coil heater, eliminating the hum. And rigid controls on the mount structure and processing reduced microphonics and noise. This resulted in the Sonotone reliable type 7025. It's now available for initial equipment and replacement purposes.

Let Sonotone help solve *your* tube problem, too.

Sonotone UNION

Electronic Applications Division, Dept. TP-99

ELMSFORD, NEW YORK

Leading makers of fine ceramic cartridges, speakers, microphones, tape heads, electron tubes.

In Canada, contact Atlas Radio Corp., Ltd., Toronto

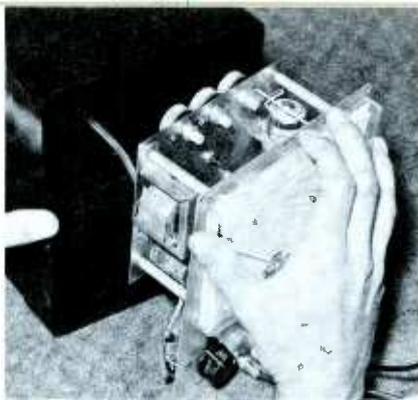


Fig. 5. Arkay meter slips out of its case after removal of four panel screws.

however, I thought that I might check out this all-important characteristic against our laboratory standards.

My first step was to recalibrate the meter by following instructions in the manual. I found the calibration adjustments located across the top chassis frame as pictured in Fig. 5. After calibrating the DC function using standards for 12, 60 and 120 volts, I made what is called a "diode adjustment" to balance out any contact potential introduced by the 6AL5 or 12AU7 tubes employed in the VTVM circuit. For the AC calibration, I used a recommended 75-volt standard, and also two others at 100 and 140 volts.

On completing the calibration, I measured a number of known AC and DC voltages as well as several precision resistors. My findings were favorable. I made spot checks at 1, 10, and 100 marks on the ohms scale for all resistance ranges and found that the readings were only off a hair from the lowest value to the highest. To me this meant that the ohmmeter accuracy was satisfactory for many laboratory applications and certainly adequate for the service bench.

Voltage-wise, I found the AC accuracy within $\pm 5\%$ and DC readings within $\pm 3\%$ of full-scale deflection. Actually, the few DC checks I made were closer than this rating indicates, but to be conservative, I'm quoting this percentage since it is generally accepted by the industry and is more than required for practical servicing applications.

Another function of a VTVM often ignored by the service technician, is its capability of expressing power loss and gain in terms of decibels. Since the meter is provided with a special db scale, I thought you might be interested in its "whys and whatfors."

Decibel indications have a relationship to the response of the human ear; i.e., a db ratio is roughly proportional to an

POWER LEVEL (DB)	POWER (mW)	VOLTAGE (V)	POWER LEVEL (DB)	POWER (mW)	VOLTAGE (V)
-10	0.0001	0.01	0	0.001	0.0316
-9	0.000126	0.0112	1	0.00126	0.0355
-8	0.000158	0.0126	2	0.00158	0.0398
-7	0.000199	0.0141	3	0.00199	0.0447
-6	0.000251	0.0158	4	0.00251	0.0501
-5	0.000316	0.0178	5	0.00316	0.0562
-4	0.000398	0.0200	6	0.00398	0.0631
-3	0.000501	0.0224	7	0.00501	0.0708
-2	0.000631	0.0251	8	0.00631	0.0794
-1	0.000794	0.0282	9	0.00794	0.0891
0	0.001	0.0316	10	0.01	0.1
1	0.00126	0.0355	11	0.0126	0.112
2	0.00158	0.0398	12	0.0158	0.126
3	0.00199	0.0447	13	0.0199	0.141
4	0.00251	0.0501	14	0.0251	0.158
5	0.00316	0.0562	15	0.0316	0.178
6	0.00398	0.0631	16	0.0398	0.200
7	0.00501	0.0708	17	0.0501	0.224
8	0.00631	0.0794	18	0.0631	0.251
9	0.00794	0.0891	19	0.0794	0.282
10	0.01	0.1	20	0.1	0.316
11	0.0126	0.112	21	0.126	0.355
12	0.0158	0.126	22	0.158	0.398
13	0.0199	0.141	23	0.199	0.447
14	0.0251	0.158	24	0.251	0.501
15	0.0316	0.178	25	0.316	0.562
16	0.0398	0.200	26	0.398	0.631
17	0.0501	0.224	27	0.501	0.708
18	0.0631	0.251	28	0.631	0.794
19	0.0794	0.282	29	0.794	0.891
20	0.1	0.316	30	1.0	1.0

Fig. 6. The chart in the Arkay manual lists db levels in both watts and volts.

increase or decrease in loudness or acoustical power as detected by a listener. Db values (based on power levels) may also be added or subtracted algebraically, and are therefore simple terms to use when expressing audio gain or loss.

In looking over the manual for the Model VT-10, I found a full page db chart which is reproduced in Fig. 6. This chart involves three factors: In the first column, db power level; in the second, corresponding power in watts; and in the third, an equivalent voltage value. When using this chart and/or the db scale of the meter, you must remember that all values and readings are accurate only if the load impedance you are working with matches that at which the instrument has been calibrated. In this instance, zero db equals 6 milliwatts of power measured across a 500-ohm load.

Using this function in a practical application, I tested an AF amplifier by using an audio oscillator as a signal source, and compared the input and output power levels in decibels. To take measurements across the input and output loads, I set the meter up to read AC voltage and balanced the pointer to zero on the db scale.

Provided my load impedances were 500 ohms, I could read directly any db level from -10 to +18 with the range switch in the 15-volt position. With the range switch in the 150-volt position, 20 db must be added to the reading indicated by the pointer. In this case, the range was from +10 db to +38 db. In the 1500-volt position, 40 db is added to make the range +30 db to +58 db.

I noted in this experiment, however, that as long as both input and output load impedances are equal, they need not have a value of 500 ohms to obtain an accurate indication of gain or loss. The individual db readings taken across input and output will not be a true representation of power, but their difference represents the change in power.

Dynamic Transistor Tester

Seco Mfg. Co., Minneapolis, Minn., has developed a new transistor checker that operates on a dynamic testing principle employing a pulse signal generator. Shown in Fig. 7, the Model 100 is a lightweight portable instrument and is completely self-powered.

Specifications are:

1. Power Requirements — one self-con-

tained 1.5-volt battery, universal replacements available.

2. Transistor Tests — checks PNP and NPN types in or out of circuit for opens, shorts, and gain; neon indicating lamp on front panel; special GO-NO GO quick check and gain-comparison test provided.

3. Panel Features — ON-OFF switch for

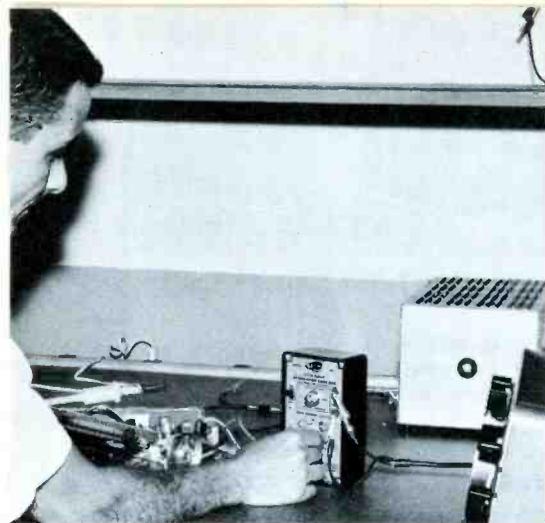


Fig. 7. Scope is used with Seco 100 to view the transistor-developed signal.

neon lamp; output jacks for voltmeter or scope indications; base current control and test selector switch; PNP-OFF-NPN selector switch; one 4-element transistor socket plus separate emitter, base, and collector test leads.

4. Size and Weight—6¼" x 3¾" x 2"; 1¼ lbs.

When I used the Seco Model 100 to test a number of known good and bad transistors, I immediately wanted to find out what made it tick. The instrument does not measure current or resistance on a meter, but indicates the condition of a transistor by placing it in a current-amplifying circuit. Its output is then evaluated by the glow of a built-in neon bulb, or by monitoring the output with an AC voltmeter or oscilloscope. Special output jacks are provided on the front panel for this purpose.


So that you will better understand its theory of operation, I have shown a schematic of the tester in Fig. 8. The transistor under test is connected as a grounded-emitter stage in a pulse generator circuit. This network functions as a simple blocking oscillator, driving the transistor into saturation and thereby generating a pulse signal with a repetition rate of approximately 150 to 12,000 cps.

A single 1.5-volt cell supplies operating bias for the transistor, while correct polarity is selected by the PNP-OFF-NPN switch located on the front panel. The 5K-ohm pot shown in the schematic permits the operator to vary base current and thereby establish a conduction range for the transistor. I found that the higher you set this control before the transistor cuts out, the higher the representative gain will be. You'll find this feature useful when comparing operating characteristics of like or unlike transistors.

When a satisfactorily operating transistor is connected to the tester, the AC signal developed in the primary winding of the transformer is stepped up in the secondary to fire the NE51 indicator. Brightness of the neon glow will be directly proportional to the amplitude of the output signal. When using the output jacks to monitor the signal, the lamp switch should be placed in its off position to prevent any limiting or clipping

XCELITE PLIERS

have a ...

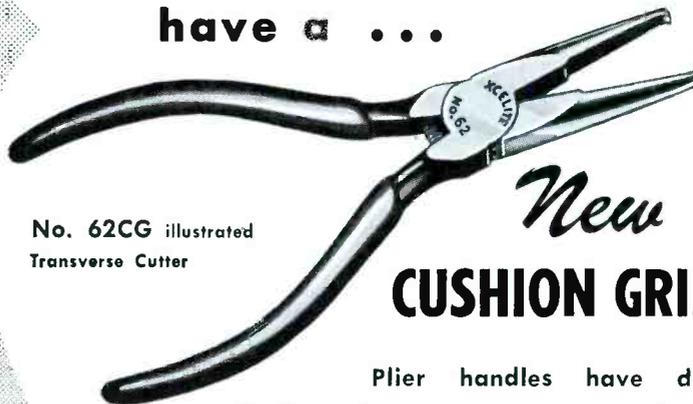

No. 62CG illustrated
Transverse Cutter

New
CUSHION GRIP!

Plier handles have dipped plastic coating . . . permanent, comfortable.

Heads polished and buffed to a "mirror finish".

All pliers available . . . See Your Distributor!

Gives pliers a "Feel" that inspires Craftsmanship!

XCELITE, INCORPORATED
ORCHARD PARK, NEW YORK
Canada: Charles W. Pointon, Ltd., Toronto

XCELITE
Quality Hand Tools
PREFERRED BY THE EXPERTS

VIS-U-ALL
BUSINESS BUILDING TEST EQUIPMENT FOR SERVICE DEALERS

NOW,
TEST & REACTIVATE
ANY PICTURE TUBE
monochrome or color,
short or long neck!



**V200 DYNAMIC
TESTER-REACTIVATOR**

and new CA-200
color tube adapter

Here's the only equipment on the market that dynamically tests all picture tubes . . . color and black-and-white, including 110° types with new 2.34v, 2.68v and 8.4 filaments. Each gun of color tubes tested separately and dynamically . . . the only accurate way. Exclusive "Magic Eye" makes reactivation safe and sure.

V200 only \$64.00 plus
CA200 adapter, \$13.50

Write
for
Details

VIS - U - ALL
PRODUCTS CO.
640 EASTERN, S. E.
GRAND RAPIDS 6,
MICHIGAN

SAMS PHOTOFAC INDEX



sent direct
to your shop

FREE

SEND FOR IT!

Yes, now you can have the valuable SAMS MASTER INDEX TO PHOTOFAC FOLDERS and Index Supplements sent direct to your shop at no cost to you! Just mail coupon below and you'll be sure to receive regularly your handy guide to the world's finest service data covering over 33,000 TV, Radio, Amplifier, Tuner Tape Recorder and Changer models. Send for it—it's FREE!

**MAIL
COUPON**

Howard W. Sams & Co., Inc.
2201 East 46th St., Indianapolis 6, Ind.

Put me on your mailing list to receive the Sams Photofact Master Index and Supplements

I'm a Service Technician: _____ full time; _____ part time

My Distributor is:

Shop Name: _____

Attn: _____

Address: _____

City _____ Zone _____ State _____

INCREDIBLE

THE SIZE • THE SOUND • THE POWER



1960

ALL-TRANSISTOR
RADIOs from
GRAND PRIX
AWARD WINNING

HITACHI



Finest and most complete line of imported personal radios in America. Created by Hitachi, Ltd., world-renowned leaders in advanced electronics design and manufacture . . . honored with the Grand Prix gold medal, for scientific equipment, at the Brussels World's Fair. *EACH SET GIFT BOXED* with leather carrying cases and accessories. And *power-promoted* all the way, nationally and locally.

For the authorized Hitachi distributor nearest you, write or phone:

THE SAMPSON COMPANY

ESTABLISHED 1921
ELECTRONICS DIVISION, 2244 S. Western Ave.,
Chicago 8, Illinois • Virginia 7-6363

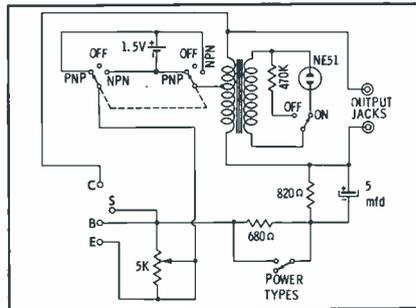


Fig. 8. Dynamic testing circuit used in Seco Model 100 transistor checker.

action by the bulb itself. With this switch in its off position, a 470K-ohm resistor loads the secondary of the transformer.

The switch shunting the 680-ohm resistor in the base network is used to change the amount of feedback present in the test circuit. Thus, the instrument can be set up to test a wide range of transistors from small signal types to power units. With this switch in its POWER TYPES position and the resistor in the circuit to reduce feedback, power transistors can be tested at currents up to 50 ma or more. To give you an idea of the actual test procedures involved, here are the motions I went through to test several different transistors in our lab.

For a straightforward "go-no go" indication, I first adjusted the base current control to its zero mark and turned on the neon lamp switch. Next, I pushed the slide-type selector switch to either its PNP or NPN position, depending on the type I was testing. I noted, however, that if you couldn't determine the type and switch setting, no damage would occur to the transistor or the instruments as long as the base current knob pointed to "0". This proved very interesting; if the bulb didn't glow after connecting the transistor and placing the switch in one position, I merely switched it to the other, got an indication, and thus identified the type automatically. Of course, if the unit under test is defective, the bulb will not glow in either position.

In each test I either inserted the transistor into the panel socket or attached the coded clip leads to the proper elements. Once the transistor is connected to the tester, its condition is indicated immediately by the glow of the neon bulb. The bulb will glow if the transistor is functioning in the oscillator circuit, which means it isn't open, shorted, or excessively weak. At this point, you may also increase the base current control, which is calibrated from 0 to 100, until a point is reached where the glow of the neon can no longer be detected. This is the drop-out or cut-off point of the transistor in the oscillator circuit, and the reading on the control may be used to indicate relative gain.


When monitoring the output of the Model 100 with a scope, I found that a normal signal generally produced a pattern like that pictured in Fig. 9A. This particular example was obtained using an NPN type 2N172 transistor. The pulse frequency was about 450 cps, and the

BERNS PERFECT
PIN-CRIMPER

Picture-Tube Repair Tool

Eliminates that hard
soldering job.

only \$1.25

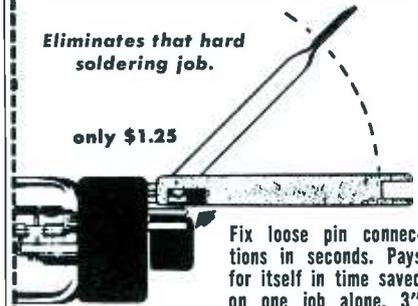

Fix loose pin connections in seconds. Pays for itself in time saved on one job alone. 3" long.

Patent 2,878,698

Intermittent operation of picture tubes due to defective solder connections at socket pins is easily corrected through the use of the Berns Perfect Pin Crimper. Actually a 3-in-1 tool that can also be used as a channel-selector wrench and screwdriver, it serves to notch pins and element leads to provide solid electrical connections. Pin keeps its original form.

IT'S DANDY . . . IT'S HANDY
"you'll like it"

Available at your parts distributor.
Another fine product from:

BERNS Mfg. Co.
9853 Chalmers,
Detroit 13, Mich



SANDY SAYS.
"The key to easy
Hi-Fi changeover"

3 ADAPTERS

HERE are the 3 KEYS to your CUSTOM Hi Fi installations . . . adapt existing connecting cables to your needs!

SD-12 
PHONO PLUG TO PHONO PIN CONNECTOR
. . . use to extend phono plug cables in new or revised Hi-Fi or Stereo installations.

DP-22 
DOUBLE PHONO PIN JACK ADAPTER . . .
invaluable for extending existing cable connections when converting Hi-Fi, etc.

SP-11 
PHONO PIN TO PHONO PLUG ADAPTER
. . . handy way to convert existing phono pin to phono plug connecting cables.

anchor products co.
ELECTRONIC COMPONENTS
2712 W. Montrose • Chicago 18, Ill.


Tarzian

*Offers You
A Complete Range
of Silicon Rectifier
Mounting Types*

THIS...



M-500

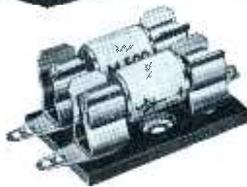

The cartridge-type Tarzian M-500 (500 ma) snaps into popular fuse holder brackets.

OR THIS...



40H



Standard top-hat Tarzian 40H (750 ma) is directly interchangeable where a metal case is required.

OR THIS...



F4

Tarzian F4 (750 ma) insulated case tucks in out of the way against chassis. Leads are solder type.

Write for complete information

SARKES, TARZIAN, INC.
RECTIFIER DIVISION

DEPT. PF-7, 415 NORTH COLLEGE AVENUE
BLOOMINGTON, INDIANA

In Canada: 700 Weston Rd., Toronto 9. Tel. Roger 2-7535
Export: Ad Auriema, Inc., New York City

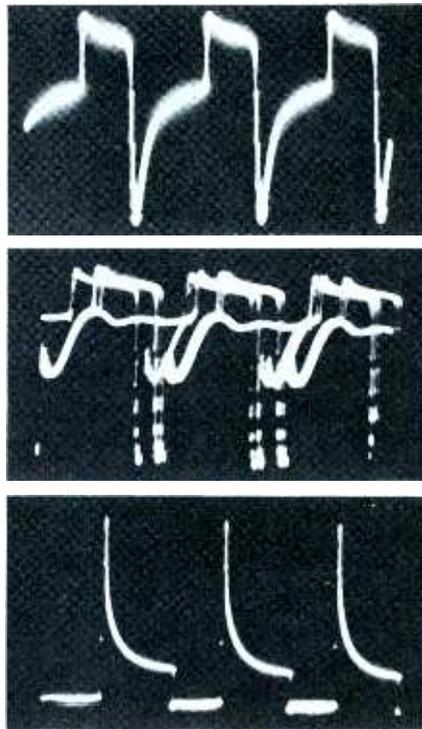


Fig. 9. Scope waveforms obtained at the output jacks of the Seco tester.

signal had an amplitude of 6 volts peak-to-peak. With the lamp switch turned on, this same output became distorted as shown in Fig. 9B. Here, I noted some clipping and a few unusual oscillations.


Checking a 2N44, which is a PNP type, I found the polarity of the signal reverses from that obtained with an NPN unit (see Fig. 9C). The pulse frequency was about the same, but the amplitude tripled. I could also reverse scope-lead connections and the pattern would revert back to the polarity of Fig. 9A. When I tested a CK721 known to be defective, I found it would not light the neon bulb nor produce any indication on the scope. Trying to out-fox the instrument, I also checked a 2N35 unit which had a good gain characteristic but excessive leakage. As it turned out, however, I couldn't fool the tester; an output just couldn't be obtained.

One of the most important test features of the Model 100 is its ability to check transistors in-circuit. This is a real timesaver, especially since so many transistors are now soldered to printed wiring boards. The impedance of the circuitry in most transistorized equipment is such that the tester is capable of generating a signal — provided, of course, the transistor itself is operative.

When troubleshooting portable radios, I found it's best to advance the volume control to maximum in order to minimize base circuit loading for an in-circuit test. To increase the instrument's utility, I noted that an external battery connected in series with the collector circuit would provide a higher operating potential for certain in-circuit test requirements. In addition, a 500-ohm control may be placed across the output jacks to extend the current range of the unit when checking power-type transistors. ▲

QUALITY

OF INTERNATIONAL REPUTATION

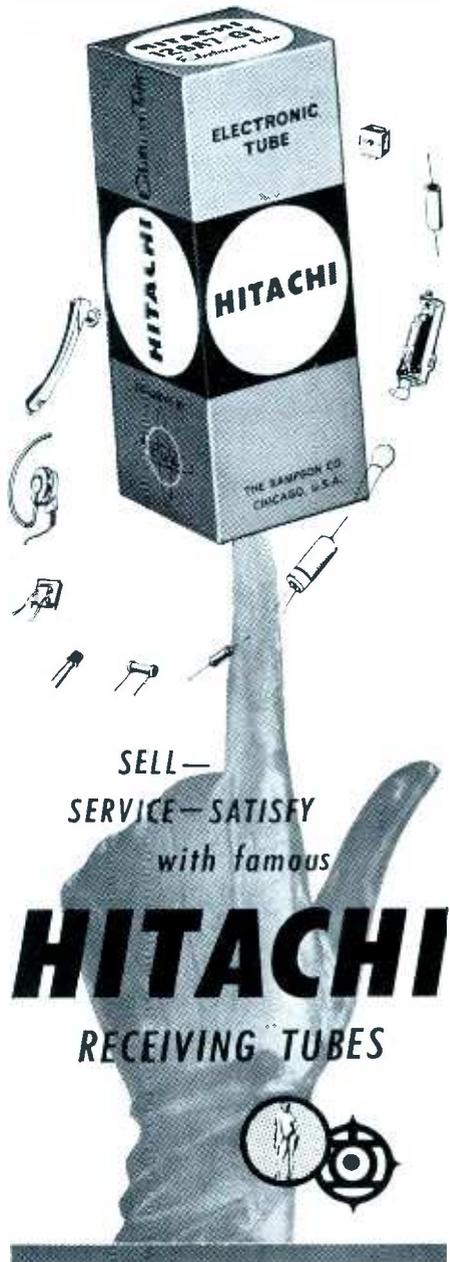

SELL—

SERVICE—SATISFY

with famous

HITACHI
RECEIVING TUBES

**Choice as original equipment by
manufacturers in the U.S. and abroad**

Performance-proved around the world. Made the quality-controlled American way to fully meet top American standards. Yet, important cost savings assure you profits not normally obtainable with tubes of such high calibre.

A complete line of quality electronic components. For CATALOG NO. 558-R, and the name of your nearest Hitachi distributor, write or phone:

THE SAMPSON COMPANY

ESTABLISHED 1921
ELECTRONICS DIVISION, 2244 S. Western Ave.,
Chicago 8, Illinois • Virginia 7-6363

NEW FROM SECO DYNAMIC TRANSISTOR CHECKER



MODEL 100

DYNAMICALLY CHECKS WIDE RANGE OF TRANSISTOR TYPES EITHER "IN OR OUT" OF CIRCUIT!

This new low-cost checker uses an entirely new approach but a proven DYNAMIC principle for checking transistors. safely tests PNP and NPN transistors either "in or out" of the circuit. Covers wide range of types: small signal including "drift" types, medium power; and power types. Provides positive check for "opens," shorts, and gain—condition indicated by means of a visual indicator plus jacks for meter or scope. Also provides GO-NO-GO test at practical currents—and permits matching of similar transistor types. No set-up required—no further leakage tests necessary. Model 100 is compact, lightweight, complete, and ready-to-use . . . helps you cash-in on the big profits in the fast growing transistorized equipment servicing field!

MODEL 100—Wired and factory tested . . . \$19.95 NET

NEW FROM SECO LOW COST, COMPLETE TUBE TESTER



MODEL 78

GRID CIRCUIT and TUBE MERIT TESTER

Complete test coverage of all modern TV tube types as well as all heater type radio tubes including hybrid types, using only 5 sockets. Incorporates patented Seco GRID CIRCUIT TEST plus a reliable CATHODE EMISSION test using new low impedance low test voltage circuit—also checks filament continuity and provides open element test. One easy-to-read meter indicates results for both Grid Circuit and Tube Merit Tests. Two-stage dc amplifier isolates meter from tube under test to protect meter—and makes it possible to achieve a wide range of load currents and test conditions. Complete with portable carrying case, pin straighteners, and flip-chart for quick set-up data.

MODEL 78—Wired and factory tested . . . \$69.50 NET



outstanding reliability, accuracy

Provides 3 important tests: amplifier types tested for gain by Dynamic Mutual Conductance method—power types tested for cathode current by Cathode Emission method—all types tested for shorts and grid error by Grid Circuit Test developed and patented by Seco. Dynamic Mutual Conductance Test pre-wired to eliminate elaborate set-up. Cathode Emission Test done by free point pin-selector method—will not be obsolete. Completely self-contained in portable carrying case.

MODEL 107—Wired and factory tested \$139.50 NET



MODEL HC-6
IN-CIRCUIT
CURRENT
CHECKER

positive, on-the-spot check of horizontal output current!

This new, low-cost current checker provides simple means for making a positive on-the-spot check of TV horizontal circuits. Can be placed into the circuit in seconds—no unsoldering of circuit wiring—immediately indicates whether horizontal tube cathode current is within manufacturer's recommended limits. Valuable as a fast, accurate indicating device when adjusting horizontal drive and linearity. Eliminates one of the most common causes of callbacks. Compact, inexpensive, easy to use.

MODEL HC-6—Wired and factory tested \$12.95 NET



MODEL GCT-8
GRID CIRCUIT
TESTER

fast check of critical "control grid" conditions

Model GCT-8 checks "control grid" condition of vacuum tubes faster, more accurately than any other tester! As many as eleven simultaneous checks—automatically! Quickly spots grid errors and leakage—stops guessing, substitution checking, and costly rechecks. Electron-Eye tube indicates faults at a glance. Truly portable. The perfect companion to any tester that employs only conventional gas and shorts test. Carry it on all calls.

MODEL GCT-8 Complete kit . . . \$19.95 NET

MODEL GCT-8 Wired and tested . . . \$29.95 NET

TIPS for TECHS



Soldering Gun Repairs Knobs

Ever pull the knob off the front of a set and have the metal insert either fall to the floor or stay on the control shaft? If you cement it back in place, you have to wait quite a while for the cement to set. Next time you encounter this trouble, use the tip of your soldering gun to fuse some plastic around the insert to hold it in place.



Handy Tool Bag

If those sets of interchangeable screwdriver bits or socket-wrench tips aren't kept together in a case, you probably have to paw around among the other tools in your box to find the one you need. You can keep all of these tools "rounded up" by putting them in a plastic or leather tobacco pouch of the type available at stores for a few cents.

Tube Removal Time-Saver

When a tube caddy is jam-packed with tubes in their cartons, it's not easy to take hold of the one you need and lift it out. In fact, it's possible to waste several minutes trying to fish out the tube you want. You can lick this problem by carrying a nailfile in your tube kit. Bend over one end of the file at a 90° angle so that you can slip it under the end flap of a carton to lift it out. Keep your "nail-file tube lifter" wedged in between cartons when it isn't in use.

SEND FOR
COMPLETE SECO
STORY ON . . .

- | | |
|---|--|
| <input type="checkbox"/> Three Tube Testers | <input type="checkbox"/> In-Circuit Current Checker |
| <input type="checkbox"/> VTVM | <input type="checkbox"/> 100% Accurate Flyback Checker |
| <input type="checkbox"/> Dynamic Transistor Checker | <input type="checkbox"/> Battery Eliminator |

Sold Only Thru Electronics Parts Distributors

OUTSTANDING RELIABILITY—TOP DOLLAR VALUE!




SECO MANUFACTURING CO.
5015 Penn Ave. So., Minneapolis, Minn.

NAME _____


ADDRESS _____

CITY _____ ZONE _____ STATE _____

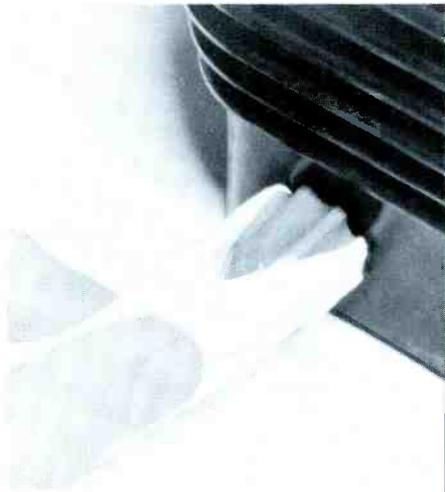

Handkerchief Frees Knob

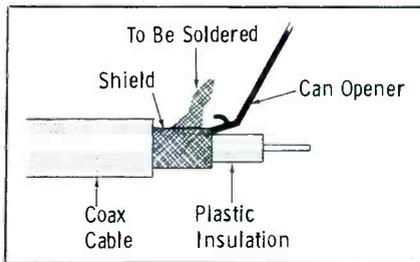If you ever encounter a stubborn radio or TV knob that just won't come loose no matter how hard you tug away at it, don't damage the set's cabinet by trying to pry the knob loose with a screwdriver. Instead, take a piece of cloth or a handkerchief, slip one edge down behind the knob, and pull outward. This will usually do the trick.




Opener Used As Heat Shunt

When you're soldering or tinning a braided shield on a piece of coax cable, the heat from the iron causes melting of the plastic insulation underneath. To prevent this, place the pointed end of a puncture-type can opener under the braid as shown. The opener will absorb most of the excess heat and thereby prevent melting of the underlying insulation.

A Sponge Will Do The Trick

What TV serviceman hasn't carried a heavy TV chassis and felt the discomfort of its sharp edges? Gloves make the task a bit easier, but a couple of those rectangular-shaped plastic kitchen sponges work even better. Next time you have a chassis to carry, try using them to pad the edges. You'll want them in your tool kit not only for this purpose, but also for padding a CRT when the chassis is rested on its side and for cleaning the tube face.

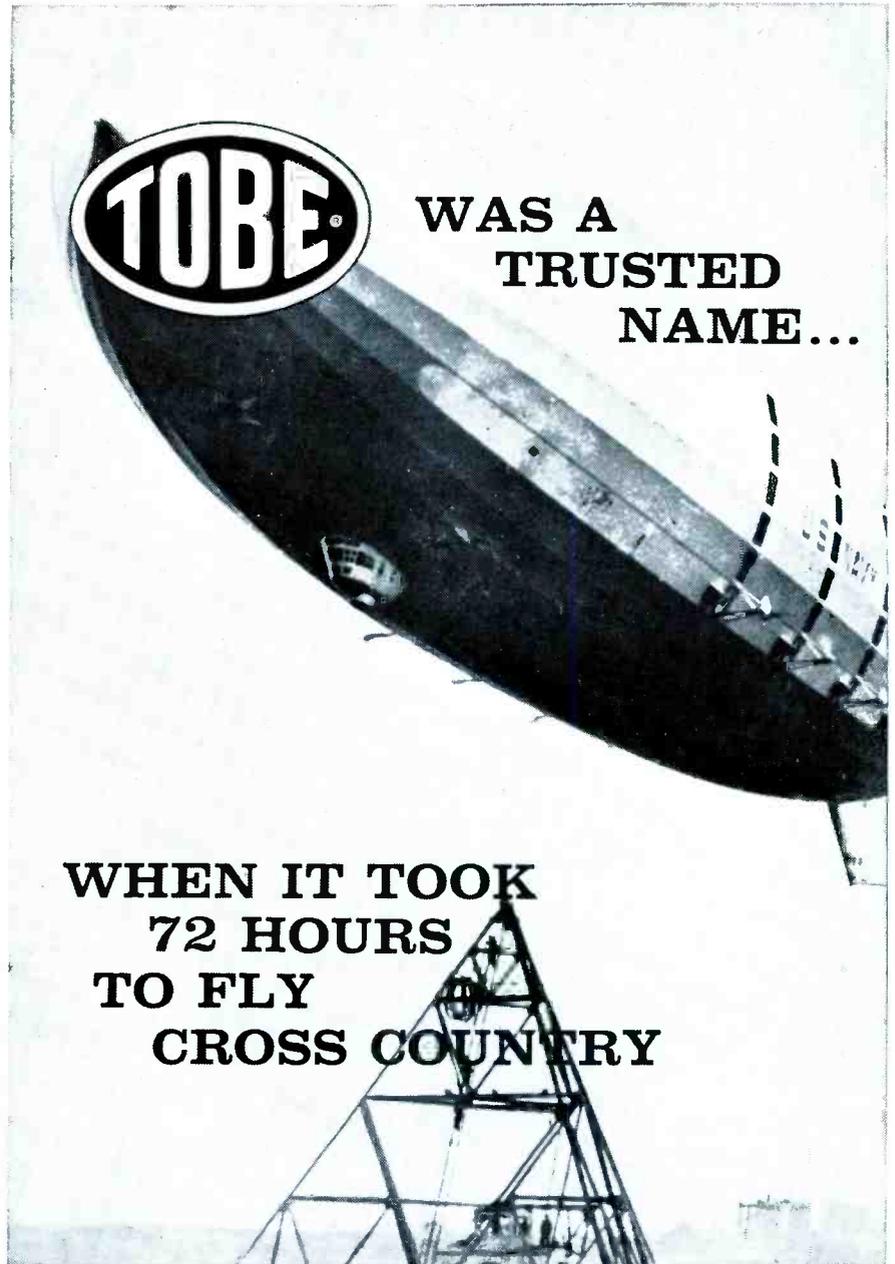

TOBE WAS A TRUSTED NAME...

WHEN IT TOOK 72 HOURS TO FLY CROSS COUNTRY

Back in 1924, when it took the dirigible *Shenandoah* 72 hours to fly from Lakehurst, N. J. to San Diego, TOBE had already built a reputation for dependable replacement capacitors. Today, Boeing 707's cross the continent in 5½ hours (and TOBE makes thermionic as well as replacement capacitors), but nothing has ever replaced TOBE dependability.

Yes, dirigibles are a thing of the past. So are worries over service call-backs, when you use dependable TOBE replacement capacitors. Install 'em. Forget 'em. Here's a typical TOBE long-life capacitor:

THE "JET" ELECTROLYTIC



- Hermetically sealed into aluminum containers with exclusive plastic sleeves.
- Compact construction; self-supported by means of rigged tinned leads.
- Capacities from 1 to 2000 mfd. Voltages from 3 to 700 vdcw.
- Temperature range to +85°C.

See your Tobe Distributor!

TOBE DEUTSCHMANN CORPORATION, INDIANAPOLIS, INDIANA

THE TROUBLESHOOTER

ANSWERS YOUR SERVICE PROBLEMS

A Lot of Pull

Several of my regular customers own General Electric Model 16C113 receivers. As these sets age, they have an increasing tendency to develop horizontal pulling when the contrast control is advanced. In one particular set, horizontal sync is completely lost at maximum contrast. I would appreciate any advice you can offer to help me eliminate this symptom.


E. J. STREBLER

St. Louis, Mo.

Horizontal pulling in this model is usually caused by some malfunction which interferes with normal operation of the sync stages. The grid of the sync amplifier is connected to the AGC system through the contrast control (see schematic); therefore, trouble in the sync section will affect AGC and vice versa. Resetting the contrast control will naturally produce a change in the observed symptoms.

Begin this repair job by installing new tubes in all tuner, IF, video, and sync sockets to eliminate the possibility of sync-signal distortion due to gas or leakage in tubes. In a set this old, you'd also be smart to replace tubular capacitors C35, C48, C75, and C77, which frequently become leaky and cause sync trouble.

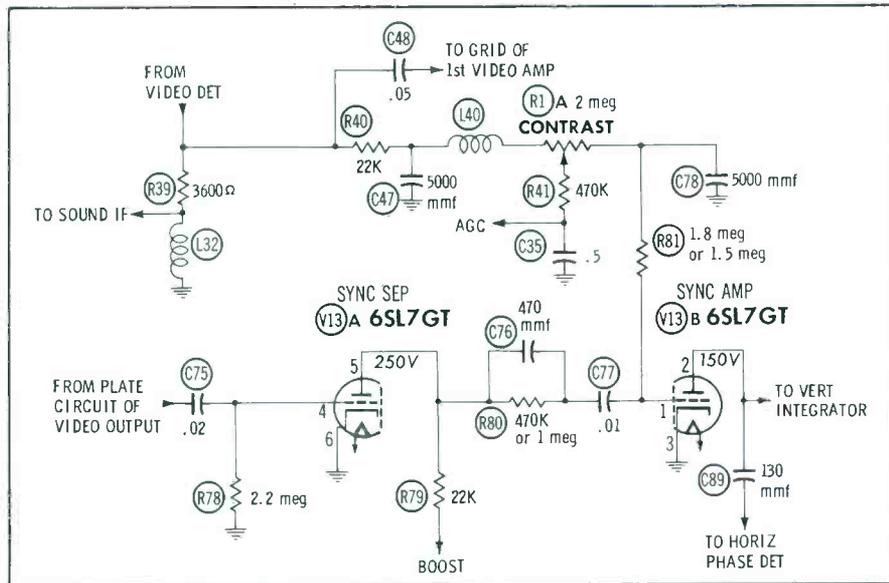If these efforts don't bring the pulling to a halt, check tube-pin voltages in the video and sync stages. Keep in mind that all grid voltages should measure slightly



Don't Miss This...

Big Contest by WORKMAN TV INC.

Contest ends Oct. 15, 1959

THE BEST ENTRY
IN THE OPINION
OF THE JUDGES
WILL...



Win

This Brand New 1959 Volkswagen Truck!
Equipped with...

- JACKSON TEST EQUIPMENT (Service Engineered, Selected for Quality)
 - 5" Scope Model #CRO-2
 - DYNAMIC Tube Tester Model #648P
 - ALL NEW 7" VTVM Model #590
 - Wide Range Capacitance Checker
- 500 WATT GASOLINE DRIVEN A.C. GENERATOR

In 10 words or less tell why you like WORKMAN TV INC. products.

ENTRY BLANKS are in...

- GLOBAL #051 (200HOT) 5 PACK
- ALL FUSED RESISTORS 10 PACK
- BELMETER 5 PACK
- 7F5-5 PACK (special 7 watt RCA & SYLVANIA fused resistor)



Ask your Distributor for Complete Information on this "Chance of a Lifetime Contest!"

The more entries you submit, the better are your chances of WINNING!

WORKMAN TV PRODUCTS, INC. Sarasota, Florida

TRY

"WISSH"

Contact Cleaner and Lubricant

by

WORKMAN TV PRODUCTS, INC.

IN THE NEW ECONOMY SIZE
16OZ. AEROSOL CAN..... only \$1.95

Model no. H14

Stocked by leading parts jobbers.

dealer net

negative with respect to the associated cathodes when no input signal is present. To prevent random noise from entering the receiver and causing inaccurate readings, short the VHF antenna terminals together.

The pulling symptom should yield to the above treatment. If not, check the output waveform of the video detector at a scope sweep frequency of 30 cps. If the sync pulses in this signal have a mashed-down appearance at high settings of the contrast control, RF or IF overloading is indicated; on the other hand, a clean waveform at the detector means the preceding stages are working normally, and you can confine your trouble search to the video and sync circuits.

TV Through Hi-Fi?

Is it practical to connect a TV set to an external hi-fi amplifier and speaker system to obtain better sound quality?


FRED W. BROWN

Los Angeles, Calif.

If it has a power transformer, a TV may safely be connected to an external audio amplifier with a minimum of trouble. If the connecting lead is going to be short (not over 6' of shielded cable), you can use the simple arrangement shown in part A of the schematic. Install a phono jack at the rear of the TV chassis; then unsolder the lead from the top of the volume control and run it to the center terminal of the jack by way of a .01-mfd coupling capacitor.

This high-impedance connection won't be satisfactory if the TV and hi-fi units are some distance apart. However, a long interconnecting lead can be used if you rewire the first audio amplifier of the TV set to convert it to a cathode follower. A suitable circuit is given in part B of the schematic. Try different values of resistance in the plate circuit, then finally install whatever value is necessary to deliver 100 volts at the plate of the 6T8.

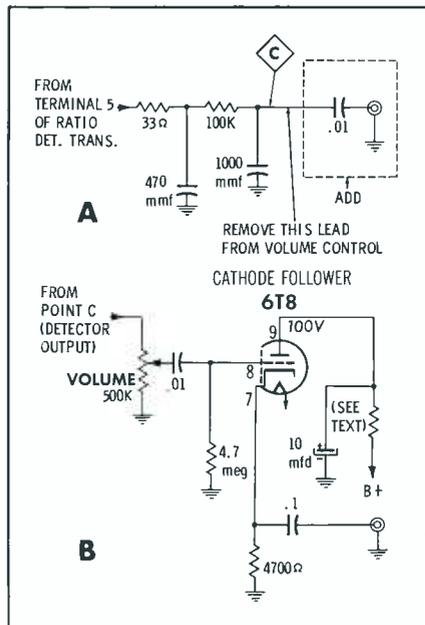Don't disable the audio output circuit of the set if it is an essential part of the B+ supply network (tube acting as



a dropping resistor between the high and low B+ lines). The output stage may be isolated from the first audio amplifier by removal of the coupling capacitor, and you can silence the TV set's speaker by replacing it with a dummy load consisting of three 10-ohm, 1/2-watt resistors in parallel. If you don't want to leave the audio output tube operating, you'll have to substitute a power resistor for it. This will require some figuring or experimentation to determine the resistance value which will establish the correct voltage level on the 135-volt B+ line.

Frybacks

I have had to replace the flyback transformer in a Magnavox 107 Series receiver several times during the past few years.

The transformer gets warm enough to melt the wax, and I've also had trouble with corona discharge. By placing sheets of polystyrene between the flyback and the chassis, I eliminated a great deal of the corona—but not the overheating. All components in the circuit seem to check normal. Could the high-voltage circuit be drawing too much current for some reason?

C. D. MAYSENT

Harlan, Iowa

Repeated flyback failure, when not accompanied by severe arcing, is generally the result of excessive current through the transformer. As a rule, the high-voltage rectifier circuit is not at fault. More probable causes of this condition are improper drive signal to the grid of

Transistor Radio Servicing CAN be Highly Profitable



The ONLY Complete Transistor Radio Service Lab

Everything you need for less than \$50



Check Transistors, Diodes, Rectifiers . . .

SENCORE TRC4 TRANSISTOR CHECKER

Accurately checks all transistors in hearing aids, radios and power transistors in auto radios. Tests for opens, shorts, leakage, current gain. Measures forward-reverse current ratio on all crystal diodes. Measures forward and reverse currents on selenium rectifiers. With set-up chart for accurate checking of each transistor. Size, 5x4 1/2 x 2 1/2". With batteries. DEALER NET..... **17 95**






Replace Batteries During Repair . . .

SENCORE PS103 BATTERY ELIMINATOR

All-new "Transi-Pak," twin to TRC4 Checker above. Provides variable DC voltage to 24 volts; 1.5-volt biasing tap (a "must" for servicing Philco and Sylvania radios). Metered current output, to 100 ma. Handles 200-ma peaks. Two 200-mfd electrolytics provide proper filtering and low output impedance. No hum or feedback problems. Ideal for alignment using station signal; adjust IF slugs for max. current, also ideal for charging nickel-cadmium batteries. Size, 5x4 1/2 x 2 1/2". DEALER NET..... **17 95**

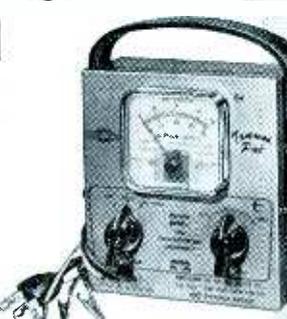



Find Defective Stage in a Minute . . .

SENCORE HG104 HARMONIC GENERATOR

New signal generator designed primarily for fast signal-tracing of transistor radio circuits. No need to unsolder all transistors. Provides RF, IF and audio signals *simultaneously*, drastically cutting service time. Traces from speaker to antenna. Clear 1000 cycle note signal is heard in speaker from all good stages. Signal weakens or stops at defective stage. Equally as effective for testing TV, hi-fi and other audio circuits also. Size, 3 1/2 x 4 1/2 x 1 3/4". With batteries. DEALER NET..... **9 95**



Turn page for other

SENCORE


Time Savers

S E N C O R E

ADDISON 2, ILLINOIS

See your Parts
Distributor
NOW!

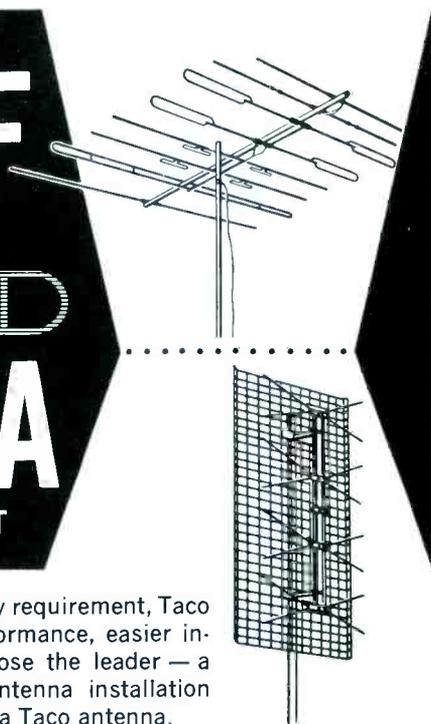FOR
UHF OR VHF
 THERE'S A
TACO
ANTENNA
 FOR EVERY REQUIREMENT




Best by field test! In every area, for every requirement, Taco antennas top them all! For better performance, easier installation, greater dependability — choose the leader — a Taco antenna. VHF or UHF, every antenna installation becomes more profitable when you use a Taco antenna.

TOPLINERS — TRAPPERS — EXPLORERS — BOWTIES
 —everyone a winner in its class, and everyone a Taco quality product.



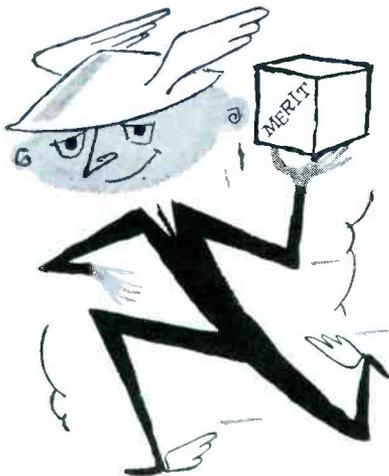WRITE FOR COMPLETE CATALOG ...
TECHNICAL APPLIANCE CORPORATION • SHERBURNE, NEW YORK
 In Canada: Hackbusch Electronics, Toronto 4, Ont.



**QUICK-SILVER FOR YOU ...
 MERCURY FOR US**

Merit shipments to all parts of the United States are jet-fast, and sure as sunrise. Mercury, the mythical god, would be pleased.

MERIT CONSISTENT QUALITY PLUS FAST DELIVERY MEANS QUICK-SILVER FOR YOU ... EXTRA DOLLARS AND BIGGER PROFITS.



COMPARE IT WITH
MERIT
 MERIT COIL AND TRANSFORMER CORP
 MERIT PLAZA . HOLLYWOOD, FLORIDA

ANOTHER HUNTER FIRST!

THE ATOM

3 NUT DRIVERS in 1
 IN 3 POPULAR SIZES
 1/4" • 5/16" • 3/8"

FREE!
 32 PAGE TOOL CATALOG

SLUG RETRIEVERS...

Magic-Tip SCREW HOLDING SCREWDRIVERS

NOW IN 14 PROVEN SIZES!

9851 ALBURTIS AVE.
 SANTA FE SPRINGS, CALIFORNIA

HUNTER TOOLS

the horizontal output tube, incorrect screen voltage on this tube, or misadjustment of the width and linearity controls. When these slugs are properly adjusted, the cathode current of the 6CD6 output tube should not exceed approximately 120 ma.

Sound Bars

I am working on a Packard-Bell Chassis 98D1 which has a beautiful picture (resolution better than 325 lines) until the fine-tuning control is adjusted for clear sound; then the picture is full of interference and barely usable.

ORVIL L. PAYNE

Santa Rosa, Calif.

There are only two things which cause sound bars and related interference patterns in the TV picture. One is lack of decoupling between the audio output stage and the rest of the receiver, while the other is incorrect alignment of the RF, IF or video circuits.

In the former case, bridging new units across the filter and decoupling capacitors in the audio output circuit will quickly reveal the culprit. Should you suspect misalignment, the first adjustments to check are the sound traps—one in the video amplifier (tuned to 4.5 mc) and another in the IF strip, usually adjusted for minimum response at 41.25 mc. In case these traps seem to be working properly, but you still cannot remove the sound bars from the picture, then you will probably have to perform further alignment of the video IF and possibly the tuner.

"Pleated" Raster

The enclosed photograph is of an Arvin Model 21-551TM. The combined keystone and foldover effect was caused by an open high-voltage winding on the horizontal-output transformer.

ROBERT E. REDD

Union Furnace, Ohio

It's a wonder you had any raster at all! According to the usual behavior of open circuits, you should have no input to the high-voltage rectifier and thus no screen brightness. Evidently, however, the gap in the transformer winding is narrow enough that the high-voltage pulses can arc across it and still reach the plate of the rectifier. This could happen even though the winding might give an "open" indication on an ohmmeter. At the same time, the open place



in the winding would probably cause enough detuning of the flyback circuit to produce the weird "pleated" effect in the raster.

Vertical Roll

An Olympic Chassis DD, used in a weak-signal area, has had poor vertical hold from the time it was installed. I have checked all components and voltages from the sync take-off point to the vertical output stage, but all check normal.

JOHN SCHLECHT

Baker, Mont.

If anyone ever needed a scope, you need one now! The key to your whole problem is the waveform at the output of the integrator. This should be viewed with the vertical output tube removed from its socket, and clean 60-cps pulses with an amplitude of about 5 volts p-p should appear. Unfortunately, the signal in your area may be so weak that you are not obtaining a good, noise-free vertical sync waveform of adequate height. In that case, make sure that the sync stages are all working at peak efficiency. You might increase stage gain or noise immunity by making slight changes in component values. If you attempt this, keep checking your results with the scope to see if the desired improvement is being produced; also consider whether or not the proposed changes would cause shortened tube life or circuit instability.

In case your integrated pulse waveform looks normal, the most likely trouble is that the natural frequency of the vertical oscillator is either too fast or too slow. For a quick check of this possibility, see if the oscillator tends to fall into sync at one end of the hold control range.

Behind Bars

A Motorola Chassis TS-52 has a number of vertical bars in the picture; the darkest ones are toward the left side of the screen. The set has shown the same symptoms to a slight degree since the date of purchase, but the bars have recently become strong enough to be objectionable. They change in intensity from day to day, and the defect is much more noticeable after two or three hours of operation. Various minor repairs in the past have temporarily reduced the bar effect but never completely cured it.

We suspect CRT cathode modulation of an intermittent thermal nature, and we wonder if a slight circuit change might not be in order—for example, connecting a bypass capacitor from the center arm of the brightness control to ground.

OSCAR VAN KAN

Cleveland, Ohio

Five or six vertical black lines appear in the left half of the raster on an Admiral Chassis 18Y4B. New horizontal sweep tubes and yoke-circuit capacitors have not helped matters, nor have I been able to eliminate the lines by putting a

magnet on the horizontal output tube. Since I can remove the lines by pulling the 6AW8 video output tube or bypassing the cathode of the picture tube, I suspect trouble in this area. However, I've been unable to eliminate the lines by rerouting the picture-tube base leads or shielding them with aluminum foil grounded to chassis.

"DURK" DURKIN

New York, N. Y.

Apparently, you're both experiencing the same trouble. The electron beam of the CRT is evidently being modulated by an unwanted signal originating in the horizontal sweep system. To confirm this suspicion, check the waveform on the driven element (cathode or grid) of the

picture tube, using a scope sweep frequency of 7,875 cps. The video signal input will have a "wrinkled" or "roller coaster" appearance if it contains enough horizontal sweep energy to produce noticeable bars in the picture. When a sweep signal is mixed with the video in this way, it is usually entering the tuner or IF strip by means of radiation from some horizontal sweep component. Judging from the patterns you describe, I doubt if your trouble is Barkhausen effect (radiation from the horizontal output tube); but there are several other possible sources of stray signals for you to check. Make sure the outer aquadag coating on the picture tube is grounded to chassis. In addition, you might try shielding the yoke and its leads. Also consider the pos-

Servicemen! SAVE TIME...SUBSTITUTE THE SENCORE WAY

The Fastest, Surest Method Known!

Substitute for Capacitors, Resistors
SENCORE H-36—THE "HANDY 36"
 36 most-often-needed resistors and capacitors, for fast, easy, direct substitution in all circuits. ● Eliminates searching for replacement components for test purposes. ● Avoids unnecessary unsoldering and soldering—no more solder mess. ● Pays for itself the first month in time saved. ● Flick of a switch instantly selects any one of —
 24 RESISTORS from 10 ohms to 5.6 megohms
 10 CAPACITORS from 100 mmfd to .5 mfd
 2 ELECTROLYTICS, 10 mfd and 40 mfd
DEALER NET 12⁷⁵

Substitute for Electrolytic Capacitors
SENCORE ES102 ELECTRO-SUB
 Usable from 2 to 450 volts, D.C.
 Contains 10 electrolytics from 4 to 350 mfd. Select the correct value with the flick of a switch. Features automatic discharge, surge protector circuit. Prevents accidental "healing" of capacitor being bridged. Completely safe—no arc or spark when connecting or disconnecting. **DEALER NET 15⁹⁵**

Substitute for Fuse Resistors During Repair
SENCORE FS3 "FUSE-SAFE" CIRCUIT TESTER
 Instantly tells you whether or not it is safe to replace fuse resistors, fuses, or circuit breakers. Separate red and green scale for each commercially available fuse resistor used in radio and TV. Eliminates guesswork and wasted time. Also handy for wattage checks up to 1100 watts. **DEALER NET 8⁹⁵**

Substitute for Bias Batteries During Repair
SENCORE BE3 "ALIGN-O-PAK"
 Completely isolated DC supply, with less than 0.1% ripple. Eliminates messy batteries in TV service work. Handy for alignment, AGC trouble-shooting, or checking gated sync circuits. Just dial the voltage you need, 0-18 volts, positive or negative. Covers all voltages recommended by TV set manufacturers. Size, 3 1/2 x 4 1/2 x 1 3/4". For 110-120 volts, 60 cycle AC. **DEALER NET 7⁸⁵**

UNIVERSAL TV JUMPER CORD
 Fits any set from back to chassis. Box has male and female plugs for additional power source, soldering, etc. **DEALER NET 1⁹⁵**






Turn page for other



See your Parts Distributor Now!

SENCORE

ADDISON 2, ILLINOIS

sibility of parasitic oscillation in the horizontal output or damper circuit. The most commonly-used remedy for the latter condition is to insert low-value resistors (under 100 ohms) in series with the various signal leads to the output and damper tubes. Connect the resistors directly to the socket pins and attach the leads to the outer ends of the resistors.

Grip of Death

Here is a hint regarding failure of 6CD6GA horizontal output tubes in General Electric Model 21C225 and similar sets. The tube is held in its socket by a spring-steel retainer having two jutting prongs. They grip the old-type 6CD6G tubes at the top of the Bakelite base;

however, the design of the newer-type 6CD6GA is such that the retainer contacts the glass envelope directly opposite the lower supporting disc for the tube elements. The high pulse voltages within the tube eat pinholes through the glass where the prongs touch it, thereby admitting air into the tube. The retaining device is easily removed, being held in place by only a single #8 x 1/4" sheet-metal screw.

JOHN H. BLOODGOOD

Anaheim, Calif.

Be on guard for this kind of trouble whenever "modernized" tube types seem to be suffering from a high failure rate. The 6BQ6GTB, 5U4GB, 1G3GT, 6L6GC, and similar tubes can be sub-

stituted for older types in most cases with no trouble; however, some design peculiarity of a certain chassis occasionally results in a bothersome problem involving nothing more than an improper physical clearance between parts.

Broadcast Interference

Would you give some practical solutions to various cases of interference with radio reception due to TV oscillations, stoker motors, heat blowers, electric razors, mixers, etc? This is a problem that everyone is up against to some degree, but I can't find sufficient information about what can be done with unwanted frequencies arriving at the radio—through the air, from the power line, or both. It's often impossible to correct the interference at its source.

JOHN J. HANCOCK

Keokuk, Iowa

The radio interference you describe is still one of servicing's nastiest problems. Most sources of interference radiate harmonics or noise pulses that cover the same frequency range as the standard broadcast band, so "wave traps" are powerless to filter out the objectionable signals.

If the spurious radiation is principally being fed in through the power line, as is often the case with household appliances, you're relatively well off. A line filter, inserted between the receiver and the AC line plug, will often reduce the interference to a bearable level.

Airborne interference is most efficiently attacked by increasing the radio's sensitivity to desired signals, or by improving its selectivity. An amazing improvement can often be made by adjusting the receiver for proper tracking—not in the sense of bringing in all stations at the correct places on the dial, but in the manner described in "Tracking Superhets" in our December, 1957 issue. If you make sure that the difference frequency between the RF and oscillator signals is always precisely equal to the center frequency of the IF, then the desired signals will receive more IF gain and will be better able to override noise.

Reception of a particular "favorite station" can be cleaned up to some degree by replacement of the standard radio antenna with a high-Q, ferrite-core antenna. This unit can be adjusted for peak antenna sensitivity in the desired portion of the broadcast band, with a resulting increase in signal-to-noise ratio.

Some desperate cases have been improved by installation of an outside radio antenna, as far removed as possible from interference sources. This may have to be connected to the receiver by a shielded cable to avoid picking up unwanted radiation on the lead-in. Unfortunately, an outside antenna isn't much help if the interference is coming from a neighbor's TV set and radiating from a roof antenna. In this instance, about your only recourse is to visit the owner of the offending TV receiver and politely seek to correct the cause of any excessive radiation.

"Simplifying Flyback Transformer Servicing"

is the subject of "Stan Cor's Corner"
... a new publication that is

FREE FROM STANCOR

This is the first in a series of publications loaded with service tips to make your job easier. This issue covers such subjects as

Symptoms due to defective flyback transformers

Symptoms due to other causes but frequently attributed to defective flyback transformers

Physically checking the flyback

Electrically checking the flyback

Repairing broken flyback leads

Little known facts about the horizontal output system

Ask your STANCOR distributor for your free copy. It is available only through him.

CHICAGO STANDARD TRANSFORMER CORPORATION
3503 ADDISON STREET • CHICAGO 18, ILLINOIS

G.E. 1960 REMOTE UNIT

(Continued from page 27)

basic oscillator coil L1. Incremental coils L2, L3 and L4 can be switched in series with L1 to provide more inductance and thus tune the oscillator to various lower frequencies. The transmitter's push buttons operate the coil switches as indicated in the schematic; at the same time, they close a battery switch and energize the transistor circuit.

Servicing

For a quick operational check of the transmitter, key it while holding it within several feet of an ordinary AM radio tuned to 640 kc. (In recent models, this corresponds to the *Conelrad* marking near the low end of the dial.) Since 640 is approximately the second harmonic of the 322.7-kc transmitter frequency, the control signals will normally be heard on the radio as a "do-re-mi-fa" series of audio tones. If you suspect that the transmitter's output is weak, remove the back of the case and check the base-emitter voltage of the transistor. (Proper test points are indicated in Fig. 5.) You should get a DC reading of -1.5 to -2 volts whenever you press one of the buttons; any lesser reading means insufficient output.

If necessary, the control receiver can be serviced without being connected to the TV set. Merely apply 117 volts AC between pins 2 and 5 of the octal plug, and observe the operation of various relays as indicators of system performance. It's advisable to keep the receiver in an "upright" position (with tubes sideways!) to insure free operation of the relays.

Two test points are provided outside the case of the receiver (near the 6EA8) to simplify alignment and testing. One of them, 2" above the antenna jack, is connected through a 5000-mmf capacitor to the plate of the audio amplifier. When this point is monitored with a VTVM (set on a low AC scale), a reading of about 15 volts rms should be obtained between test point and ground when the transmitter is held near the receiver and keyed.

If this reading seems abnormal, try moving the meter lead to the amplifier-grid test point on the other side of the 6EA8 socket. When the transmitter is keyed, you should ob-

tain an AC reading of about 1 volt rms—or a DC indication of as much as -2 volts. Exact values of voltage will depend upon several factors such as the sensitivity-control setting.

The grid of the detector (pin 9 of the 6EA8) is an excellent place to check for the presence of an input signal; unfortunately, you have to take off the side panel of the receiver to reach it. This point is a fraction of a volt negative with respect to ground, until a signal arrives from the transmitter; then the voltage should shift to some value from -5 to -12 volts, depending on

the strength of the input signal.

If a signal from a normally-operating transmitter does not produce the expected voltage shift at the input side of the detector, then trouble probably exists in the antenna, RF amplifier, or power supply of the receiver. Realignment might even be needed.

Adjustments

The General Electric remote unit, like most other electronic equipment, is not likely to need realignment for at least several years. However, it may be necessary to

Check **TUBES, VIBRATORS**
THE SENCORE WAY

EASY
ACCURATE
TROUBLE
SHOOTING

America's Most Popular Tube Tester
more than 25,000 now in use

SENCORE LC3 LEAKAGE CHECKER

Whips those "tough dog" tube troubles . . .

Ask any serviceman who owns one . . . or try one for just one day of servicing in your shop. You'll see for yourself how much time the LC3 can save *you*. Checks for leakage between all elements, whether caused by gas, grid emission or foreign particles. Also checks leakage on all capacitors with voltage applied—including electrolytics. Provides instant filament checks in "Fil-Check" position—no need for a second filament checker. One spare pre-heating socket and new roll chart prevent obsolescence. New charts provided—no charge. Leakage sensitivity; 100 megohms, control grid to all other elements; 50,000 ohms, heater to cathode. Size, 7x6x3½". Wt., 3 lbs. For 110-120 volts, 60 cycle AC. DEALER NET **28⁹⁵**



NOW . . . checks 172 tube types—more than any other checker of this type.

NEW . . . replaceable Roll Chart prevents obsolescence.

Check Filaments of All Receiving Tubes and Picture Tubes



FC4 FILAMENT CHECKER

For fast, easy checking of all tube filaments, without pulling chassis. Neon light goes out if tube filament is good. Also acts as continuity and voltage tester. Neon lamp glows when 115 v. AC is applied by heater cord, providing a check on power to TV set. Size, 3½x4x1". **2⁹⁵** With leads. DEALER NET.....

Check 3- and 4-Prong Vibrators . . . Faster, Easier



VB2 "VIBRA-DAPTOR"

Plugs into any tube checker; ideal for use with LC3 above. To check 6-v. vibrators, set for 6AX4 or 6SN7; for 12-v. vibrators, set for 12AX4 or 12SN7. Two No. 51 lamps indicate whether vibrator needs replacing. Instructions on front panel. Steel case. Size, 1½x1½x3". **2⁷⁵** DEALER NET.....

See your Parts Distributor NOW!



SENCORE
ADDISON 2, ILLINOIS

check the adjustment of the receiver antenna and the sensitivity control from time to time. Being RF-operated, the remote system is subject to some interference due to radiation of horizontal-sweep energy. This effect has been minimized by choosing an operating frequency midway between harmonics of the horizontal-oscillator frequency; even so, the remote-receiver antenna sometimes must be relocated to insure minimum pickup of sweep interference. The procedure is as follows: (1) Throw the horizontal oscillator out of sync in order to produce maximum interference; (2) use a VTVM to monitor the AC voltage at the audio-output test point; and (3) orient the antenna for a *minimum* reading.

While you're at it, check the sensitivity-control setting. With the horizontal oscillator still out of sync, turn the control until the VTVM reads 3 volts rms. The sensitivity of the receiver should then be high enough to permit normal operation of all relays, but not sufficiently high to let interfering signals cause spurious triggering. In locations where

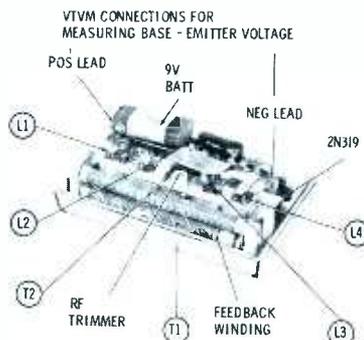


Fig. 5. Remove back of case for access to all coils, battery and transistor. considerable RF noise is present, you may have to cut down the sensitivity of the remote receiver. Although this will reduce the effective operating range of the transmitter, it will increase the reliability of the system.

Further alignment of the receiver consists of adjusting the double-tuned RF output transformer and touching up the antenna trimmer. If a known good remote transmitter is not available, an ordinary RF signal generator (tuned to 322.7 kc and modulated with audio) makes a satisfactory signal source.

If a transmitter must be aligned,

use a normally-operating receiver as an indicator; the job is much easier that way. The RF trimmer (Fig. 5) is adjusted for maximum AC voltage at the audio-output test point, and the reed relay is used as an indicator while the slugs in the audio coils are being retuned. Watch the shortest reed when adjusting the highest-frequency coil—and so on down the line. When you're on the right frequency, the reed will vibrate and energize its associated relay.

It's unlikely that two receivers using this same remote-tuning system will be installed close enough together to produce mutual interference; but if they ever do, provisions have been made for solving the problem by tuning one of the systems to a different frequency. The RF circuits have been designed for satisfactory operation at either 291.2 or 354.2 kc, should the need arise. (These particular frequencies are specified because they are subject to minimum interference from horizontal sweep.) Retuning is done just like regular alignment—adjust the receiver first, then the transmitter. ▲

YOU CAN ALSO DO THE BIG JOBS WITH WIZARDS



HOME - 7 Outlets - One Antenna - No Amplification: Residence of Bob Barker, MC of the popular daytime NBC show Truth Or Consequences.



HOTEL - 120 Outlets - One Antenna - One Amplifier: The Montecito - 6650 Franklin, Hollywood, California.



THE WIZARD 300*

ELECTRO-MAGNETIC COUPLER FOR ALL SINGLE ANTENNA MULTIPLE-OUTLET SYSTEMS IN TV FLAT LINE

*Pat. Pend

\$1.95
LIST PRICE

The high electrical efficiency of the Wizard 300 is proven in many installations where more than thirty receivers are being operated from a single antenna without amplification.

Information on any of the above jobs and a brochure covering Wizard System installations is available. Write Dept. PF99.

CHARLES ENGINEERING, INC.
6053 Melrose Avenue • Los Angeles, California



HOUSING PROJECT - 2,549 Wizards Installed To Date: L.A. Housing Authority, Los Angeles, California.



APARTMENT - 39 Outlets - One Antenna - No Amplification: The Del Rio - 10236 Old River School Road, Downey, Calif



APARTMENT - 48 Outlets - Two Antennas (24 Outlets each) - No Amplification: The Paramount Riviera - 12447 Paramount Blvd., Downey, California.

Shop Talk

(Continued from page 25)

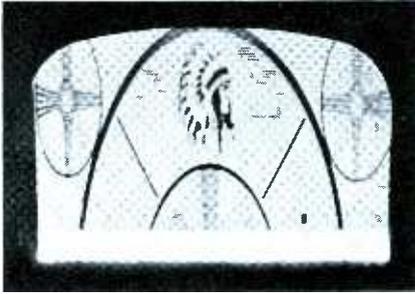


Fig. 4. Vertical foldover indicates that vertical yoke current is nonlinear.

tal windings will produce the distorted image shown in Fig. 2. When either of these two illustrations are encountered, your first action should be to change the yoke. No series of grueling tests are needed.

In Fig. 3, the complete absence of any vertical deflection (resulting in a brilliant, thin horizontal line) indicates that the trouble is in the vertical deflection system. Consequently, that section of the receiver is the place to look. Another type of trouble in the vertical system might lead to the distorted indication shown in Fig. 4. The picture is folded over at the bottom, indicating that vertical sweep is not linear. This trouble is generally caused by some defect in the vertical output stage, although the oscillator circuit is at fault on occasion. The final illustration, Fig. 5, illustrates a severe loss of horizontal synchronization. This symptom, known as the "Christmas-tree effect," produces a completely jumbled picture; its cause is highly erratic operation of the horizontal oscillator.

The foregoing symptoms are fairly specific in their origin, and should guide any reasonably experienced service technician directly to the stage or section where the trouble is being developed. There are quite a number of other trouble indicators

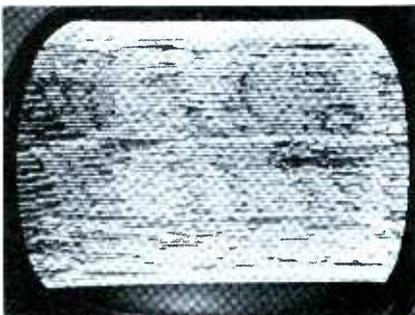


Fig. 5. Severe sync loss with ragged edges is called "Christmas-tree effect."

which fall into the same category; the most common are listed in Table 1. Possible sources of trouble have been broken down into 13 categories, which encompass every section of a television receiver, including the deflection components mounted on (and associated with) the picture tube. A check in the latter column does not necessarily mean that a component is defective, although it can be. Much more likely, it means the component (yoke, ion trap, focus magnet, etc.) is out of position and should be repositioned. In sim-

ilar fashion, a check in the "FM Detector" column more often indicates a need for readjustment of the input transformer rather than for changing any component.

In the chart, all possible stages in which a defect can produce the indicated symptom have been checked. However, it stands to reason that the trouble would normally be found in only one stage, not in all those checked.

Once a trouble has been narrowed down to a certain section of the receiver, the next step is to

SENCORE SS105 SWEEP CIRCUIT TROUBLE SHOOTER

IT'S A ...

UNIVERSAL HORIZONTAL OSCILLATOR. For direct substitution. No wires to disconnect in most cases. Traces trouble right down to the defective component. Variable output from 0-200 volts, peak-to-peak.

HORIZONTAL OUTPUT CATHODE CURRENT CHECKER. A proven method that quickly checks the condition of the horizontal output tube and associated components. Adaptor socket prevents breaking wires. Easily replaceable Roll Chart gives all necessary pin, current and voltage data.

UNIVERSAL DEFLECTION YOKE. A new, simple way to determine yoke failure accurately—without removing yoke from picture tube. Merely disconnect one yoke lead and substitute. If high voltage (also bright vertical line) is restored, TV yoke is defective.

DYNAMIC FLYBACK TRANSFORMER CHECKER. Merely flip switch to "Flyback Check" and meter will indicate condition of flyback transformer, in degrees of horizontal deflection. Extremely sensitive and accurate; even shows up one shorted turn on flyback.

VOLTMETER. For testing bootstrap, screen and other voltages. Direct-reading voltmeter, 0-1000 volts.

UNIVERSAL VERTICAL OSCILLATOR. Checks oscillator, output transformer and yoke. Merely touch lead to component and check picture on screen.

Size, 7x6x3½". Wt. 4 lbs.
For 110-120 volts, 60 cycle AC.

DEALER NET **39⁵⁰**



HORIZ. OSC.	VERT. OSC.
HORIZ. O.P. STAGE	VERT. O.P. STAGE
HORIZ. FLYBACK XFORMER	VERT. O.P. XFORMER
HORIZ. DEFLEC. YOKE	VERT. DEFLEC. YOKE

See Your Parts
Distributor
NOW!


SENCORE
ADDISON 2, ILLINOIS

SUBSTITUTE PARTS WITH-OUT SOLDERING

Quickly with E-Z-Hook "SUB" Connectors Easily Has 1001 Uses!

NEW
E-Z-Hook
"SUB"
Connectors

Connect a
speaker, or

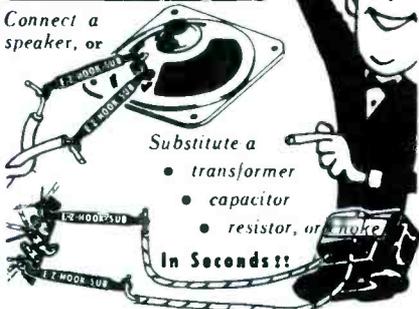

Substitute a
• transformer
• capacitor
• resistor, or choke
In Seconds!!

- ★ Makes connections instantly!
- ★ Won't pull off!
- ★ Insures positive contact!

Saves time, money and parts in servicing, experimenting, instructing and production.

E-Z-HOOK SUB

No. 71-1-1 SUB Only 69¢

Six Colors! - for Easy Lead Identification
Canadian Rep.: Len Finkler & Co., Toronto, Ontario



ORDER THROUGH YOUR
PARTS DISTRIBUTOR
E-Z-HOOK TEST PRODUCTS
Dept. F, 1536 Woodburn Ave.
Covington, Ky.

check the tubes in that section. It may be desirable, after the defect has been located and the set is operating normally again, to check all the tubes as "callback insurance." With the quick-test checkers now available, this can be done in 15 minutes or less. From a systematic point of view, it is seldom desirable to check all the tubes as the first step; it is better to wait until the defect has been localized and corrected.

An important feature of tube testing is the ability of the test instrument to reveal gas and high-resistance leakages. These are subtle defects that can play all sorts of havoc with receiver operation, and experience has demonstrated repeatedly that you will have less trouble with a tube possessing weak emission than one with gas or leakage.

There is one situation where the initial step might be to check all the tubes—when a receiver is brought into the shop and none of the tubes light up. This is a fairly common trouble, particularly since many receivers now being designed have all the tube filaments connected in series. Under these circumstances, checking the tubes to locate the one with the open filament would be a logical step; however, when all the tubes are lit, your best bet is to localize the trouble before testing them.

To summarize, here's a brief recap of the troubleshooting approach thus far:

1. Find out all you can about set behavior from the set user before any service work is done.
2. From the way the set operates, determine the section of the receiver where the defective component is likely to be located.
3. After the section in question has been located, check tubes in this section as a first step.

The systematic approach to troubleshooting can do more than just lead you to the defective section in a receiver. It can also help you find out which stage in the section is not functioning normally, and sometimes it even permits you to locate the exact component which is causing trouble. The next article in this series will take you a step farther in the technique of "analyzing trouble analysis."

TV TUNERS REBUILT

All MAKES & MODELS

VHF
or
UHF

EXCHANGED
OR
OVERHAULED
\$9.95
NET



90 DAYS
WARRANTY

COMBINATION
UHF/VHF
UNITS
\$19.90

ALIGNED TO ORIGINAL STANDARDS

Price includes labor and minor parts only, defective tubes and damaged major parts are extra at net prices.

Forward tuner complete with tubes, shield cover and any damaged parts.

QUOTE MAKE AND MODEL

F.O.B. CHICAGO OR TORONTO
We will ship C.O.D.

CASTLE TV TUNER SERVICE

5710 N. WESTERN
CHICAGO 45, ILL.

152 MAIN ST.
TORONTO 13

U.S.A.

CANADA

\$100.00 CASH REWARD

... to the first serviceman who reports the location of any of the following stolen receivers:

AMC, serial 6210857; Emerson, serial 151428; GE, serial 179594 and 284055; Motorola, serial 627880; Muntz, serial 31238; Olympic, serial R454175 and R473427; Philco, serial nos. DD98415, 188687, SR11019, F3044, S.O.H. 68747, A.D. 58146, A.D. 84616, and A.C. 40544; RCA, serial nos. 919673, 1801877, B5388102, 1837008, 1786520, 4613730, 1786697, 180076, 902650, 894108, A88460, and A4657299; Sentinal, serial 10793; Sylvania, serial nos. 537309-183-4334 and 537309-124-4108.

These receivers were stolen from various service dealers in the Indianapolis area. Investigation indicates they are being disposed of in several large midwestern cities.

Contact by phone or wire, Carl C. Schmidt, Inspector of Detectives, Indianapolis Police Dept., Indianapolis, Ind.

**IF YOU
MUST SPEND
YOUR MONEY**

Why not get
Something for it?
get
QUIETROLE




IN BOTTLES
2 oz. with
Dropper
4 & 8 oz.
Dropper with
6 oz. SPRAY-
PACK
"CAN"

QUIETROLE

TRADE MARK REG. U.S. PAT. OFF.

Costs little more than the poorest substitutes. Why take less than the BEST...

No Product can match its merit...
None can equal its quality...

It's the answer to noisy controls
and switches

QUIETROLE is the original product of its kind

MFG BY **QUIETROLE** Company


SPARTANBURG, South Carolina

IN CANADA: ACTIVE RADIO and TV DISTRIBUTORS
58 Spadina Ave., Toronto 2B, Ontario

PRODUCT report


For further information on any of the following items, circle the associated number on the Catalog & Literature Card.

Hex Drivers (41H)

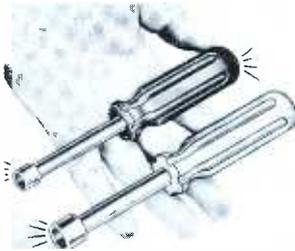


Extra-hard tempered sockets discourage "rounding out," and color-coded handles indicate socket size, in two new series of Vaco hex nut drivers. The *Chrome-Tone* line, with chrome-finished solid shafts drilled 1½" deep, comprises 13 different tools in standard, "stubby," and "extra small" sizes. The 18 nut drivers in the deluxe *Gold-Tone* line are equipped with gold-colored, hollow shafts.

Insulating Dope (42H)

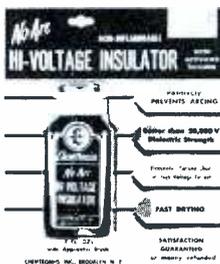

A nonflammable, clear fluid—Chemtronics *No-Arc Hi-Voltage Insulator*—can be brushed onto yokes, horizontal output transformers, and other components to repair damaged insulation or to serve as corona dope. It dries quickly to form a coating with a dielectric strength on the order of 20 kv. A 2-oz. bottle, with brush attached inside cap, has a net price of 89c.

High-Voltage Silicon Diodes (43H)

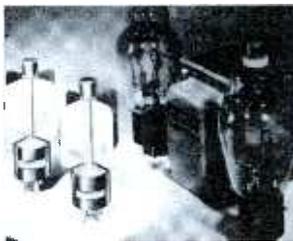

A pair of International Rectifier Corp. Type ST-7 silicon rectifiers can replace two Type 866 mercury-vapor rectifier tubes and their filament transformer for broadcast and communications radio applications where PIV does not exceed 6,400 volts. The silicon diodes and their cooling fins are mounted on tube bases to permit plug-in installation.

Knob Stems (44H)



Flatted shafts of ¼", 3/16" and .202" diameter, in addition to ¼" slotted and knurled shafts, can be fitted with Colman universal-type knobs by use of *Radio Knob Stems* as a coupling device. The selection of stems includes a total of 13 different types having various lengths.

Crystal Mike (45H)



A clip-on desk stand and a lavalier cord are furnished with the American Microphone Model X-206 portable tape-recorder microphone. Its response pattern is omnidirectional, frequency response is 65 to 10,000 cps, output level is -55 db, over-all length is 5 11/16", and list price is \$7.95.

More PROFITS from stereo conversions with ERIE...

NEW STERIEO CERAMIC CARTRIDGE



This high quality single-element stereophonic cartridge is ideal for converting monaural record players to stereo. Dual stylus—sapphire-sapphire. Frequency response: 20 to 16,000 cps. Tracking force: 5 grams. Output: 0.5V, each channel. Channel separation: 20 DB. **\$8⁹⁵**
Regular list price...

Plus Audio Amplifier Kit!

A complete-in-one-box ERIE "PAC" kit. Printed circuit board and plug-in components require little assembly time to build this high-quality, four-tube push-pull audio amplifier. Just right for profitable stereo conversions.

Regular list price . . .

\$12⁹⁵



BOTH


FOR ONLY

\$14⁹⁵
NET

Here's a special profit-making stereo conversion offer you can't afford to pass up—a full \$21.90 value for only \$14.95. Offer expires November 15, so order from your nearby Erie distributor now and cash in on high-profit conversion business.

For name of your nearest Erie Distributor write to:

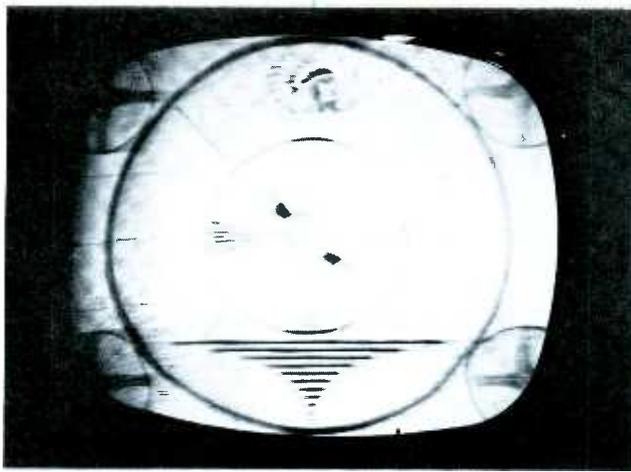ERIE Electronics Distributor Division
ERIE RESISTOR CORPORATION
Erie, Pennsylvania



COMING IN OCTOBER

Curing Brightness and Contrast Problems

The quality of a TV picture depends on accurate control of CRT phosphor illumination. You'll like the refreshing treatment of this subject, describing troubles that rob sets of that extra oomph.

Isolating Color TV Troubles by Symptoms

If you want to be proficient in locating and correcting color TV circuit troubles, you must know which section to suspect when confronted with a specific set of conditions. With the information included in this article, you'll take one giant step forward in the servicing profession.

Stock Guide for TV Tubes

A completely revised list of the 200 most popular TV tubes, with usage figures to guide you with regard to your inventory requirements. Of particular interest is that, for the first time, the chart will also include a suggested stock list for a typical tube-caddy inventory of 350 tubes.

Other helpful and informative articles include:

- Why Test Tubes in the Home?
- Using a Scope for TV Troubleshooting
- Previews of New Sets
- Video Speed Servicing
- Notes on Test Equipment
- How to Choose and Use Microphones—Part 2
- Servicing Medical Amplifiers

... plus all the other regular PF REPORTER departments, to make it the ONE magazine especially prepared for the palates of electronic servicemen.

TO ENTER A NEW OR RENEWAL SUBSCRIPTION, SIMPLY FILL IN AND MAIL THE COUPON BELOW.

Please enter my subscription to PF REPORTER for:

- 1 Year \$4.00 2 Years \$7.00 3 Years \$9.00

Above rates apply only in U.S.A., its possessions, and Canada, All other countries: 1 year \$5.00, 2 years \$9.00, 3 years \$12.00

- Bill Me Remittance Enclosed Extend Present Subscription

Give to your parts distributor or mail to PF REPORTER, 2201 E. 46th St., Indianapolis 6, Ind.

Please Check Your Business Classification

- Independent Radio, TV Serviceman Owner, Mgr.
- Retailer with Service Department Service Mgr.
- Industrial Electronics Service Employee
- Other (Specify occupation and title)

Name _____

Firm _____

Address _____

City _____ Zone _____ State _____

959

Two-Set Couplers (46H)

Two new Walsco antenna couplers are designed to be mounted on the mast (or wall) before the leads are attached. Connections are protected from the weather by a snap-on cap. The *Standard* coupler (No. 1600; \$2.50) is a resistive divider for use in areas where moderate RF power loss can be tolerated. The *Ultra Low Loss* unit (No. 1602; \$3.50) is recommended for fringe areas.



Stereo Stylus-Cartridge Combination (47H)

The standard version of the Sonotone Model 10T unitized stylus-cartridge assembly has both .07- and 3-mil sapphire tips, is designed to mount in a snap-in bracket, and has plug-in leads. Output is 1/2 volt, frequency response is 20-15,000 cps, tracking pressure is 6 to 8 gm., and compliance is 1.5 x 10⁻⁶ cm/dyne. Price is \$6.45 complete with mounting hardware.




Palm-Size Meters (48H)

Two new members of the "Little Triplet" line of hand-sized test instruments are the Model 307 AC ammeter (shown) and the Model 308 Lo-Ohmmeter. The former, used for measuring 60-cps current, has four ranges from 0-1 to 0-25 amps; the latter, for such jobs as motor testing and tracing shorts in wiring, accurately measures resistances as low as .1 ohm or as high as 5,000 ohms.



Tape Recorder Accessories (49H)

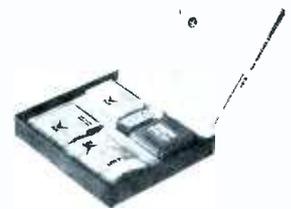The following items are contained in the V-M No. K-82 *Tape Editing Kit*: T-131 *Junior Tape Splicer*, T-132 *Klenz-A-Tape* cloth (for cleaning and lubricating tape), T-134 *Self-Timing Leader Tape* (marked at one-second intervals), T-136 *Recording Head Cleaner*, and a 150" x 1/2" roll of splicing tape. Inside the cover are adhesive reel labels and a "Guide to Better Tape Programming" booklet.



Bidirectional PA Speaker (50H)

The two-way sound-dispersion pattern of the Atlas TW-9 speaker enclosure enables it to "cover" long narrow areas such as corridors from a central location. This enclosure is designed for 8" cone-type speakers and comes equipped with a mounting plate which permits attachment to either a plain wall surface or an electrical outlet box. The case is finished in beige enamel.




Power Tools (51H)



Two new portable power tools have been announced by Drake Electric. A 1/4" drill, Model D74, operates at 2,000 rpm and draws 2.6 amps. Weight is 3 1/4 lbs. Its two-part aluminum housing is designed to provide easy accessibility to the motor for maintenance. Another item, the Model D58 jigsaw, is suggested for work on hi-fi cabinetry.

Tubular Capacitors (52H)

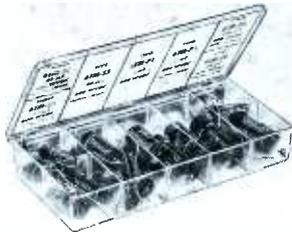

Sprague *Difilm Black Beauty* capacitors have a dual dielectric—both paper and Mylar polyester film—and are impregnated with a synthetic hydrocarbon which solidifies after being injected. The humidity-resistant molded phenolic case is black with red markings. A TK-1 kit of 20 units (in five often-used values) is \$14.46.

Record Player Adjustment Kit (53H)



Two phono servicing aids are packaged together in the Clevite "Walco" *Balanced Sound Kit* (list price \$2.50). One tool is a leveling gauge which indicates any variations from a true level condition when laid on a turntable, and the other device is the *Microgram Stylus Pressure Gauge*, a balance scale calibrated in 1-gm. steps.

Fringe-Area TV Antenna (54H)



The new Winegard Model SCL-4 *Super Color 'Ceptor'* TV antenna (\$38.95 list) has higher gain than the standard Model CL-4. The two driven elements, which have been redesigned into a modified folded-dipole configuration, are pre-assembled to the boom and "fold out" into operating position. The boom is reinforced with a short parallel brace and dual "wrap-around" mast clamps.

Filament Dropping Resistor (55H)



A 41-ohm fixed resistor, designed as an exact replacement for General Electric part RRR-148, has been added to the Clarostat P25K line of 25-watt wire-wound resistors. This new P25K-41 unit is suitable for use as a voltage dropping resistor in the filament circuit of certain models of TV sets.

Mobile Radio Base Station (56H)




An AC-powered base-station unit has been introduced for use with COMCO 580/582 *Fleetcom* Series VHF mobile radio gear (described in this column in December, 1958). Its transmitter receiver chassis is directly interchangeable with that of the DC-operated mobile unit. The base station, designed for desk mounting, weighs 30 lbs., measures 15 1/4" x 11 1/2" x 10", and costs about \$450.

The NEW YEATS "Shorty" STATION WAGON & PANEL PICK-UP appliance dolly



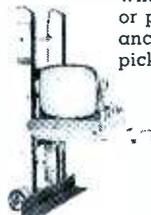YEATS Model No. 5
Aluminum alloy
Height 47"
Weight 32 lbs.



Folding platform is 13 1/2" x 24 1/2" —attaches instantly. (Platform only) \$9.95.




Furniture Pad

SEND postcard for full information on our complete line TODAY!

YEATS appliance dolly

2103 N. 12th St.

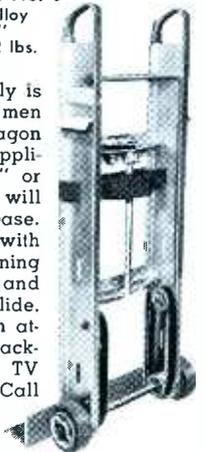

Only 47" tall, this new YEATS dolly is designed for TV and appliance men who make deliveries by station wagon or panel truck. No need to detach appliance for loading into the "wagon" or pick-up . . . the YEATS "Shorty" will slide into your vehicle with ease. Has aluminum alloy frame with padded felt front, quick fastening (30 second) strap step glide, and endless, rubber belt set glide. New YEATS folding platform attachment, at left, saves back-breaking work handling TV chassis or table models. Call your YEATS dealer today!

"Everlast" COVERS & PADS

YEATS semi-fitted covers are made of tough water repellant fabric with adjustable web straps and soft, scratchless white flannel liners. All shapes and sizes—Write.



TV Cover

sales co.

Milwaukee, Wis.

Here's a Bargain!

SPECIAL OFFER!

VACO

Nut Driver—

Voltage Checker & Probe Utility Set

you get

Two New Design VACO Nut Drivers (1/4" and 11/32") Plus Brand New Voltage Checker & Probe

A \$2.50 Value for \$1.79 NET
You Save 71¢



No. SP 3

You'll find a hundred uses for this probe. It's a voltage checker, electric tester, etc. Full instructions included.

GET ACQUAINTED OFFER: We make this unique offer for a LIMITED time only to acquaint you with VACO'S beautiful new line of Nut Drivers with full polished chrome shafts, colored-for-size handles and extra hard sockets that WON'T round out. Get your set, today!

See Your Parts Jobber or Write

VACO PRODUCTS COMPANY, 317 E. Ontario St. Chicago 11, Illinois
In Canada: Atlas Radio Corp., Toronto 19, Ontario

September, 1959

Anchor Products Co. 72
 American Television & Radio Co. (ATR) 16
 Arco Electronics, Inc. 12-13
 Arkay Radio Kits, Inc. 64
 Astatic Corp. 9
 B & K Mfg. Co. 31
 Belden Mfg. Co. 45
 Berns Mfg. Co. 72
 Blonder-Tongue Labs 38
 Bulldog Electric Products Div., I-T-E Circuit Breaker Co. 66
 Bussmann Mfg. Co. 37
 CBS Electronics 43
 Castle TV Tuner Service 84
 Centralab, A Div. of Globe-Union, Inc. 69
 Charles Engineering, Inc. 82
 Chicago Standard Transformer Corp. 80
 Clarostat Mfg. Co., Inc. 41
 Cornell-Dubilier Electric Corp. 61
 Doss Electronic Research, Inc. 42
 Duotone Co., Inc. 46
 EICO 60
 E-Z-Hook Test Products 84
 Electro-Voice, Inc. 47
 Electronic Publishing Co. 46
 Erie Resistor Corp. 85
 General Cement Mfg. Co. 36, 2nd Cover
 General Electric Co. Receiving Tube Dept. 35
 Gernsback Library, Inc. 56
 Hickok Electrical Instrument Co. 53
 Hunter Tool Co. 78
 International Resistance Co. 18-19
 Jackson Electrical Instrument Co. 63, 88
 Jensen Mfg. Co. 39
 Littelfuse, Inc. 4th Cover
 Mallory & Co., Inc., P. R. 32-33
 Merit Coil & Transformer Corp. 78
 Ohmite Mfg. Co. 40
 ORRadio Industries, Inc. 49
 Oxford Components, Inc. 64
 Perma-Power Co. 59
 Pyramid Electric Co. 67
 Quietrole Co. 84
 RCA Electron Tube Div. 58, 3rd cover
 Raytheon Co. 23
 Sampson Co. Electronic Utilities Div. 72, 73
 Sams & Co., Inc., Howard W. 40, 51, 71
 Sarkes Tarzian, Inc. Rectifier Div. 73
 Tuner Div. 57, 64
 Seco Mfg. Co. 74
 Service Instruments Corp. 77, 79, 81, 83
 Sonotone Corp. 70
 South River Metal Products Co. 56
 Sprague Products Co. 10
 Sylvia Electric Products, Inc. Semiconductor Div. 65
 Television Receiver Div. 50
 Tube Div. 14-15
 Technical Appliance Corp. (TACO) 78
 Tenna Mfg. Co. 55
 Tobe Deutschmann Corp. 75
 Tung-Sol Electric, Inc. 17
 Vaco Products Co. 87
 Vis-U-All Products Co. 71
 Webster Electric Co. 22
 Weller Electric Corp. 52
 Winegard Co. 20-21
 Workman TV, Inc. 76
 Xcelite, Inc. 71
 Yeats Appliance Dolly Sales Co. 87

ANTENNA SYSTEMS

- 1H. **BLONDER-TONGUE**—"Master TV systems Bidder's Guide," compiled from a series of catalog sheets and specification folders. See ad page 38.
 2H. **JERROLD**—Free subscription to *Technical Reporter*, which keeps you up-to-date on equipment for multiple antenna systems.
 3H. **SOUTH RIVER**—Illustrated material with information on the "free-opening" chimney mount banding. See ad page 56.
 4H. **TACO**—Revised price list and catalog sheets on antennas, accessories, and FM promotion kit. See ad page 78.

AUDIO & HI-FI

- 5H. **ARKAY**—Literature including specifications for the new Harting MS-5 stereo tape deck, dual-track record playpack. See ad page 64.
 6H. **ASTATIC**—Catalog 33-3 listing microphones, cartridges, and other radio equipment. Includes list prices. See ad page 9.
 7H. **ELECTRO-VOICE**—Bulletin No. 255, "How to Choose and Place Stereo Sound Equipment for the Home," explains what you should know about stereo. See ad page 47.
 8H. **RCA**—"Microphone-Select-a-Guide," with information to help you choose the right unit for any job. See ads page 58 and 3rd cover.
 9H. **TURNER**—New microphone catalog plus specification sheets with descriptions, specifications, and prices on various microphones in company's line.

CAPACITORS

- 10H. **CORNELL-DUBILIER**—Bulletins on the *Treasure Chest* twins and the new service bench capacitor kits. See ad page 61.
 11H. **SPRAGUE**—M-773 *Difilm* Mylar-paper capacitor catalog sheet. See ad page 10.

CARTRIDGES & NEEDLES

- 12H. **SONOTONE**—Cartridge reference chart, cartridge replacement manual, hi-fi products catalog, and rechargeable flashlight battery flyer. See ad page 70.

COMPONENTS (MISC.)

- 13H. **CENTRALAB**—New 24-page catalog listing over 1700 composition and wire-wound controls, ceramic capacitors, switches, and packaged circuits available through distributors. See ad page 69.
 14H. **RADIART**—1959 Vibrator Replacement Supplement.

FUSES

- 15H. **BUSSMANN**—Completely new television fuse chart describing proper fuses to use, how they are mounted, and which circuits they protect. See ad page 37.

SEMICONDUCTORS

- 16H. **PYRAMID**—Specification sheet on the S1-500 silicon power rectifier for radio and TV replacements. See ad page 67.
 17H. **RAYTHEON**—16-page "Transistor Entertainment Equipment Guide," providing interchangeability data for transistor radios. See ad page 23.
 18H. **SYLVANIA**—20-page booklet with up-to-date information on line of semiconductor diodes, including characteristics and interchangeability; also a replacement guide, form no. SD-10. See ads pages 14-15, 50, 65.

SERVICE AIDS

- 19H. **BULLDOG**—Catalog #EH-100 describes *Electrostrip* multiple AC outlet assembly. See ad page 66.
 20H. **CLAROSTAT**—Form 755259 describes 225-watt, power-resistor decade box with ranges from 1 to 999,999 ohms in 1-ohm steps. See ad page 41.
 21H. **E-Z-HOOK**—Convenient reference sheet titled, "How to Build the Five Most Useful Scope Probes," with schematics, mechanical component layouts, etc. See ad page 84.

- 22H. **SERVICE INSTRUMENTS**—4-page brochure on all company's time-saver instruments. See ads pages 77, 79, 81, 83.
 23H. **YEATS**—Data sheets on appliance dollies, hand trucks, and padded appliance covers. See ad page 87.

SPECIAL EQUIPMENT

- 24H. **ATR**—New **KARADIO** catalog sheet describing auto radios for both imported and small U.S. cars. See ad page 16.
 25H. **MONITORADIO**—Catalog page describing two new tunable FM communications receivers for the 30-50 mc and 152-174 mc bands.

TECHNICAL PUBLICATIONS

- 26H. **CBS**—The latest issue of *Tech Tips* by Bud Tomer, entitled "How to Test Transistors." See ad page 43.
 27H. **GERNSBACK**—Descriptive literature on Gernsbeck Library books. See ad page 56.
 28H. **HOWARD W. SAMS**—Descriptive literature on all Howard W. Sams publications covering servicing of radio, TV, hi-fi, etc. Includes data on latest books, "Television Antenna Handbook," "101 Ways to Use Your Signal Generator," the new revised edition of "PHOTOFACT Television Course," Volume 3 of "Video Speed Servicing," and Volume 2 of "Electronics Reference Data Handbook." See ads pages 40, 51, 71.

TEST EQUIPMENT

- 29H. **B & K**—Bulletin ST21-R gives helpful information on new point-to-point signal-injection technique with Model 1075 *TV Analyst*; other bulletins describe *Dyna-Quik* Models 500B, 650, and automatic 675 portable dynamic mutual-conductance tube and transistor tester, plus Model 400 CRT cathode-rejuvenator tester. See ad page 31.
 30H. **DOSS**—Information on the latest in test equipment, including the *Pioneer 250* Horizontal Systems *Quantalyst*. See ad page 42.
 31H. **EICO**—20-page 1959 2-color catalog describes 65 models of professional test instruments, hi-fi, and "ham" gear in both kit and factory-wired form. Shows how to save 50%. Also, 4-page 2-color stereo hi-fi guide. See ad page 60.
 32H. **JACKSON**—Data sheets describing Models 598 and 658 low-cost dynamic tube testers. See ads pages 63, 88.
 33H. **RCA**—Pocket-sized folders on the WV-38A(K) volt-ohm-milliammeter and WO-33A(K) super-portable oscilloscope kits. See ads page 58 and 3rd cover.
 34H. **SECO**—Literature describing the new Model 100 dynamic transistor checker and Model 78 grid-circuit and tube-merit tester; also 8-page 2-color folder on company's other equipment, plus servicing information. See ad page 74.
 35H. **VIS-U-ALL**—Tube-testing equipment catalog describing new quick-type portable and caddy tube testers and CRT tester-rejuvenator. See ad page 71.
 36H. **WINSTON**—Flyers describing complete line of instruments, including an AGC circuit analyzer, intermittent condition analyzer, induced waveform analyzer, rainbow generator, dot generator, sweep circuit analyzer, and audio system analyzer.

TOOLS

- 37H. **BERNS**—Data on the 3-in-1 picture tube repair tool that crimps pin and element lead to make a solid electrical connection; can also be used as screwdriver and channel selector. See ad page 72.
 38H. **HUNTER**—Catalog on subminiature tools for printed board work, etc. See ad page 78.
 39H. **XCELITE**—Catalog sheet on the latest in servicing tools. See ad page 71.

TUBES

- 40H. **TUNG-SOL**—Pocket price list for approximately 1000 receiving and picture tube types; also, order form and catalog sheet for newly-published "Tube Base Connections" and "Tube Characteristics" books. See ad page 17.




MODEL 648		MODEL 49		CATH. SHORTS	
TUBE TYPE	PLATE TEST	TUBE TYPE	PLATE TEST	TUBE TYPE	PLATE TEST
6A1	AC126	6A1	AC126	6A1	AC126
6A2	AC126	6A2	AC126	6A2	AC126
6A3	AC126	6A3	AC126	6A3	AC126
6A4	AC126	6A4	AC126	6A4	AC126
6A5	AC126	6A5	AC126	6A5	AC126
6A6	AC126	6A6	AC126	6A6	AC126
6A7	AC126	6A7	AC126	6A7	AC126
6A8	AC126	6A8	AC126	6A8	AC126
6A9	AC126	6A9	AC126	6A9	AC126
6A10	AC126	6A10	AC126	6A10	AC126
6A11	AC126	6A11	AC126	6A11	AC126
6A12	AC126	6A12	AC126	6A12	AC126
6A13	AC126	6A13	AC126	6A13	AC126
6A14	AC126	6A14	AC126	6A14	AC126
6A15	AC126	6A15	AC126	6A15	AC126
6A16	AC126	6A16	AC126	6A16	AC126
6A17	AC126	6A17	AC126	6A17	AC126
6A18	AC126	6A18	AC126	6A18	AC126
6A19	AC126	6A19	AC126	6A19	AC126
6A20	AC126	6A20	AC126	6A20	AC126
6A21	AC126	6A21	AC126	6A21	AC126
6A22	AC126	6A22	AC126	6A22	AC126
6A23	AC126	6A23	AC126	6A23	AC126
6A24	AC126	6A24	AC126	6A24	AC126
6A25	AC126	6A25	AC126	6A25	AC126
6A26	AC126	6A26	AC126	6A26	AC126
6A27	AC126	6A27	AC126	6A27	AC126
6A28	AC126	6A28	AC126	6A28	AC126
6A29	AC126	6A29	AC126	6A29	AC126
6A30	AC126	6A30	AC126	6A30	AC126
6A31	AC126	6A31	AC126	6A31	AC126
6A32	AC126	6A32	AC126	6A32	AC126
6A33	AC126	6A33	AC126	6A33	AC126
6A34	AC126	6A34	AC126	6A34	AC126
6A35	AC126	6A35	AC126	6A35	AC126
6A36	AC126	6A36	AC126	6A36	AC126
6A37	AC126	6A37	AC126	6A37	AC126
6A38	AC126	6A38	AC126	6A38	AC126
6A39	AC126	6A39	AC126	6A39	AC126
6A40	AC126	6A40	AC126	6A40	AC126
6A41	AC126	6A41	AC126	6A41	AC126
6A42	AC126	6A42	AC126	6A42	AC126
6A43	AC126	6A43	AC126	6A43	AC126
6A44	AC126	6A44	AC126	6A44	AC126
6A45	AC126	6A45	AC126	6A45	AC126
6A46	AC126	6A46	AC126	6A46	AC126
6A47	AC126	6A47	AC126	6A47	AC126
6A48	AC126	6A48	AC126	6A48	AC126
6A49	AC126	6A49	AC126	6A49	AC126
6A50	AC126	6A50	AC126	6A50	AC126
6A51	AC126	6A51	AC126	6A51	AC126
6A52	AC126	6A52	AC126	6A52	AC126

How to keep your profits from going to the "dogs"!

Another way
RCA helps you
improve your
business.


STOP PROFIT LEAKS!

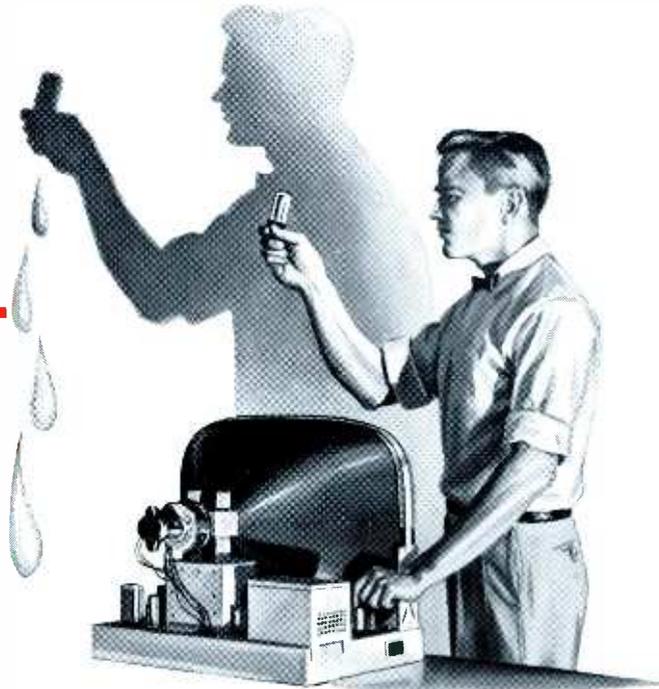


Review these important facts about heater-cathode leakage

Did that TV set come back? Same symptoms—60-cycle hum bars? You diagnosed the trouble correctly—a leaky tube.

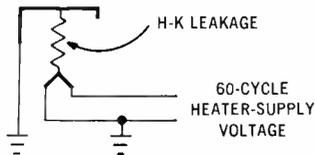Here's why a leaky tube can cause you a lot of trouble.



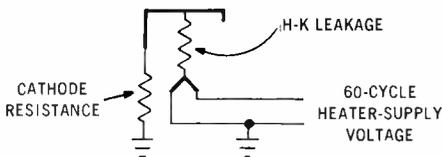H-K leakage provides a path for 60-cycle current to flow from the heater to the cathode. If there is no resistance or impedance in the cathode circuit, this leakage current usually causes no difficulty.




When there is resistance in the cathode circuit, the H-K leakage current develops a 60-cycle voltage across the cathode resistor. This voltage may produce visible and/or audible 60-cycle "hum".




H-K leakage in the RF, IF, or video stages of a TV receiver can produce 60-cycle horizontal pulling and "hum" bars.



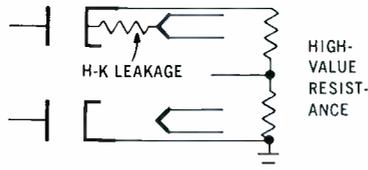
H-K leakage in the sync-separator tube or in the horizontal AFC, oscillator, or output tubes can produce 60-cycle horizontal pulling without "hum" bars.



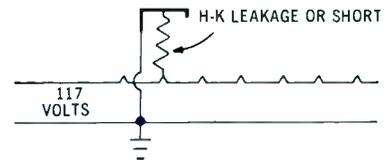In detector, discriminator, and AFC stages, which usually have relatively high values of resistance in the cathode circuit, even a slight amount of H-K leakage current can easily cause visible and/or audible 60-cycle "hum" symptoms.



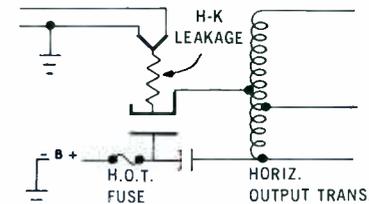An H-K short circuit, or low-resistance leakage, in a series-string tube, short-circuits part of the heater circuit. The resulting higher voltage across the remaining heaters may cause heater burnout.



H-K leakage in a damper tube which has its heater grounded may cause the H.O.T. fuse to blow.

RCA tubes help you beat these problems—drastically reduce heater-cathode leakage and shorts through such improvements as precise control of heater coatings to eliminate "thin spots"...better heater stem lead arrangements...new cathode materials and structures. Avoid callbacks caused by tubes that develop H-K leakage problems and keep your profits from "leaking" too. Remember to always ask your distributor for **RCA TUBES!**



RADIO CORPORATION OF AMERICA
Electron Tube Division

Harrison, N. J.



dealer-serviceman's fuse rack...


...for wall mounting

most needed



most wanted

... the FUSEMASTER!

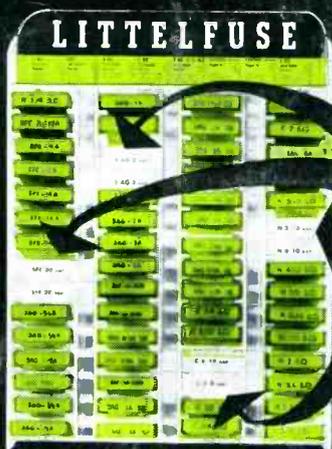

dealer-serviceman's fuse requirements at a glance