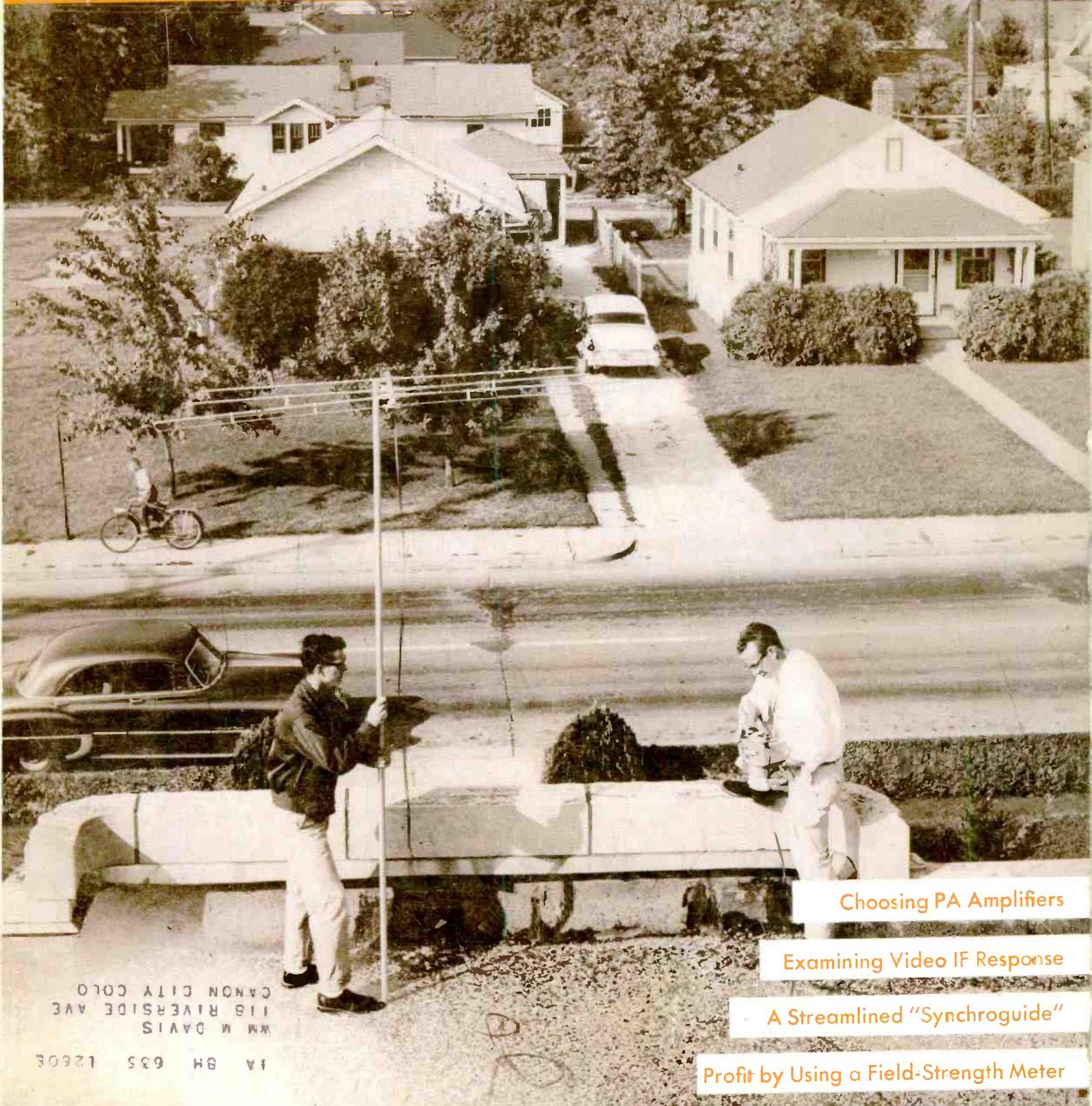


NOVEMBER, 1959 35 CENTS



PHOTOFACT REPORTER

Including **Electronic Servicing**



Choosing PA Amplifiers

Examining Video IF Response

A Streamlined "Synchroguide"

Profit by Using a Field-Strength Meter

1A 9H 635 1260E
WM M DAVIS
118 RIVERSIDE AVE
CANNON CITY COLO

now...


make your customers happy



...make more money!



with NEW G-C EXACT TV REPLACEMENT KNOBS

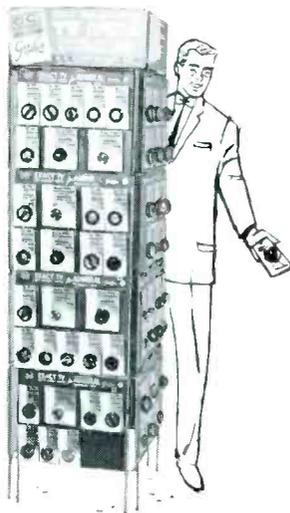

- 97 KNOBS TO CHOOSE FROM
- COVERS ALL 8 POPULAR TV MAKES
- REPLACEMENTS FOR ON-OFF, VOLUME, FINE TUNING, CHANNEL SELECTOR
- MODERN SKIN-PACK—PRICE-MARKED FOR YOUR TRADE

Whenever you run across a broken or missing knob on your TV service calls, you can supply an exact replacement that makes your customer happy, gives you extra money on that call. Your nearby G-C jobber is now showing the complete G-C TV Knob line . . . with each knob skin-packed, clearly identified, and marked with list price for the set owner's information. It's another great service for you from G-C and your G-C jobber.

WRITE today for your free G-C Catalog . . . other literature too.





G-C ELECTRONICS CO.

Division of Textron Inc.

West Plant: Los Angeles 18, California

Main Plant: ROCKFORD, ILLINOIS, U. S. A.

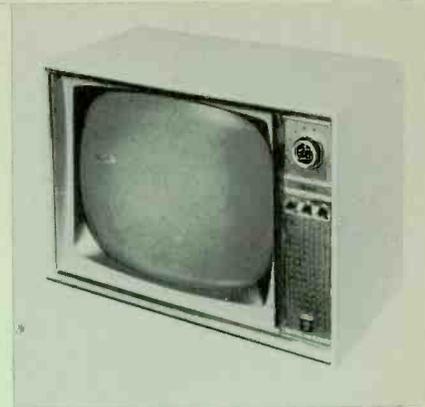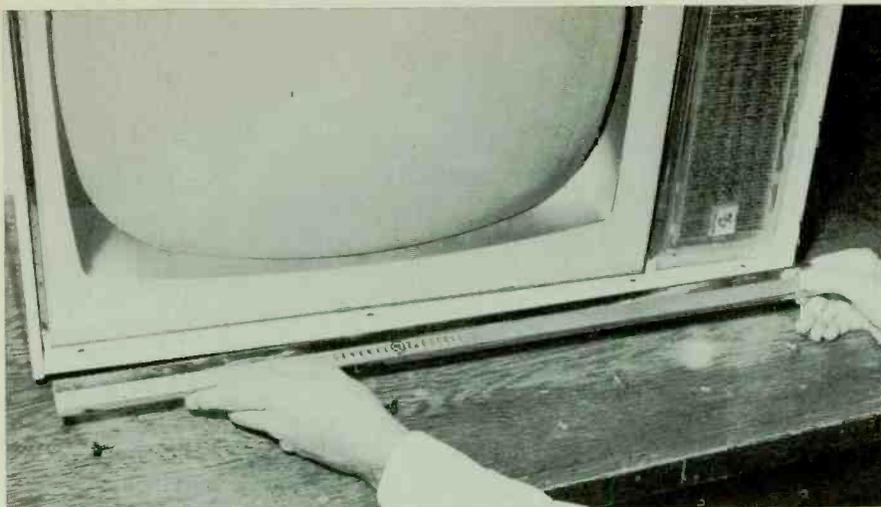

G. E. Model 21T3421 Chassis M5

The new *Designer* series includes this 21" table model with VHF tuner, short-neck 110° picture tube, and all-metal cabinet.





The front safety glass is well sealed, but slips out easily after removal of the bottom trim strip. This strip is held in place by four 1/4" hex-head screws located under the front part of the cabinet.

With the back off, you'll find a "U" shaped chassis which employs a power transformer and two printed boards. The VHF tuner mounts in the upper left corner directly above a single 4" PM speaker. As for new tube types, a 6FM8 is employed in the sound detector and AF amplifier stages, while a 6DN7 is used in the vertical sweep section.

From the back of the set, you can look down on the horizontally-positioned sweep-circuit board and see that all components are exposed and identified. A bright yellow tracing on the component side makes it easy to follow the printed wiring paths. The dual diode pointed out in the photo is soldered into the horizontal AFC circuit. Directly in front of a fat, stubby electrolytic mounted above the board, you'll find a pigtail fuse protecting the flyback system. This is a slow-blow unit rated at 375 ma. The printed board for the IF, video, and sound stages mounts vertically on the upright section of the chassis. This is on the left side of the cabinet as you view it from the rear.

Behind the antenna terminal bracket on this section, you'll find a separate line fuse. This is a 3.5-amp slow-blow unit which affords protection to the entire receiver. Although not shown here, the parallel filament circuit is also fused by a 2" length of #26 copper wire. This fuse link is soldered to the vertically-positioned board near the 6CX8.

An unusual circuit feature of this receiver is the horizontal and vertical blanking network. From the simplified schematic, you can see that a separate winding on the flyback is used to develop the horizontal pulses, while the vertical blanking signal is obtained from a tap on the vertical output transformer. The vertical pulses are shaped by an R-C network and then combined with horizontal pulses from the flyback winding. Both signals, of a negative polarity, are then coupled to the grid of the picture tube for blanking.

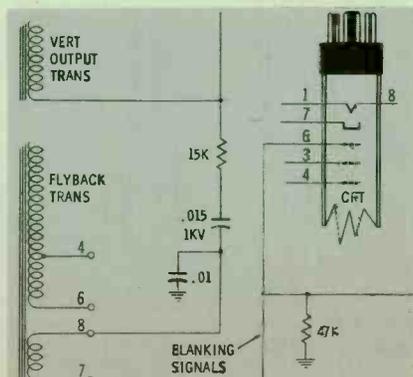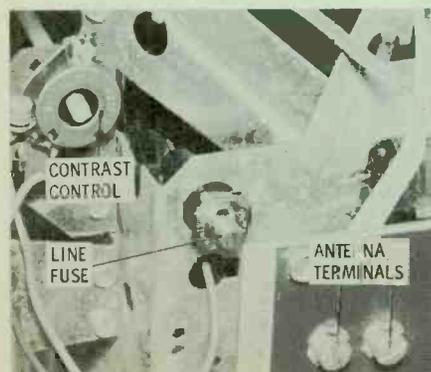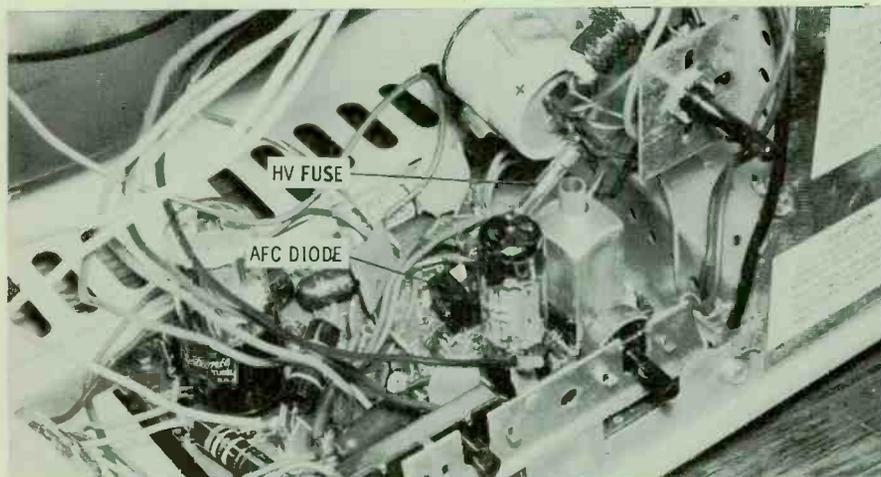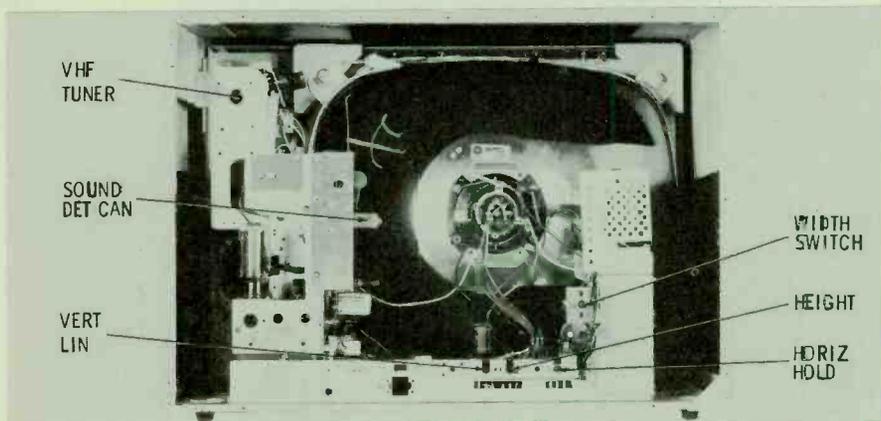



**Philco Model H-3412L
Chassis 10L43**

This new model in the *Predicta* line features a swivel-type 17" picture tube, telescoping antenna, and a clock which will turn the set on and off automatically.






The transformer-powered chassis (less CRT and yoke assembly) is confined to an oblong metal cabinet. The VHF switch-type tuner mounts separately on one side, and a 4" x 6" oval speaker is located up front on the other side. Brightness and hold controls are positioned at the top rear corner of the set, each with a plastic knob that extends through the back cover. All other service adjustments are on the rear of the chassis except the one for horizontal linearity, which is on the yoke assembly.



Some of the tubes in this set are a little difficult to get to, so you'll find it easier to service in some cases if you slide the chassis partially out of the cabinet. To accomplish this, remove the two 1/4" hex-head screws holding the interlock panel, unplug the clock power cord, and take off the vertical metal brace on the back of the cabinet. After removing the bolts from the bottom of the cabinet, the chassis can be pulled out far enough to make all tubes accessible.

Two printed boards are employed—one for the IF strip and the other for all other sections except the low and high voltage supplies. The only tube in the high-voltage cage is a 1G3GT rectifier. Other tubes of a more recent vintage include a 6BQ5 in the audio output stage, and a 6DR7 in the vertical sweep section. The damper circuit employs a 6DA4, and the video IF's are 6DE6's.

Directly in back of the power transformer is a fusible resistor which is series-connected in the B+ rectifier circuit. This *fusistor* is rated at 5.6 ohms and plugs into a small terminal strip. Although the chassis is isolated from the AC line by a power transformer, you'll find a pair of silicon rectifiers used in the low-voltage supply. These units are soldered in and are located just to the right of the *fusistor*.

Making a close examination of the printed board, you'll find the tube sockets employed are similar to regular test-socket adapters. This feature makes it convenient to take measurements from the component side of the board, and elevates the test points so that they are not spaced too closely to the conductors on the board. Wiring is traced out on the top side of the board, and all parts, stages, and test points are identified.

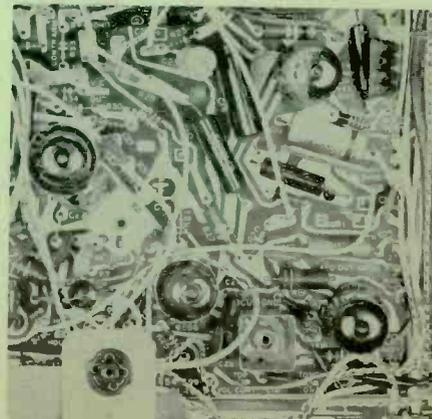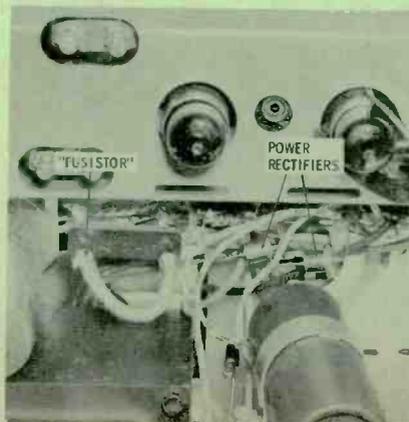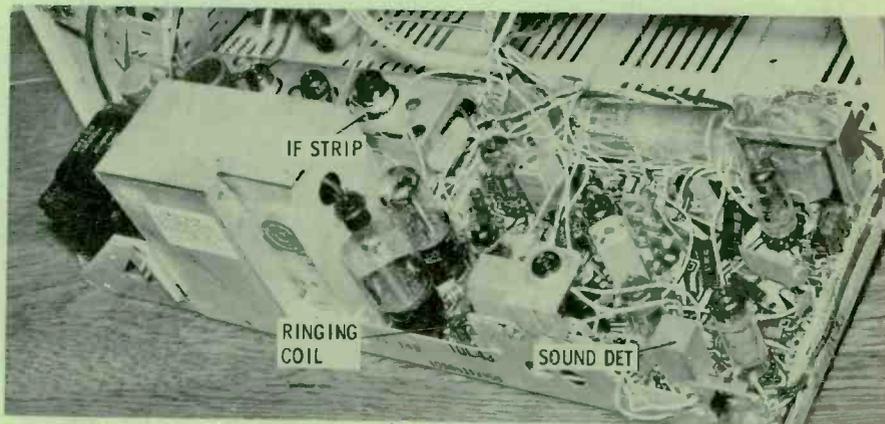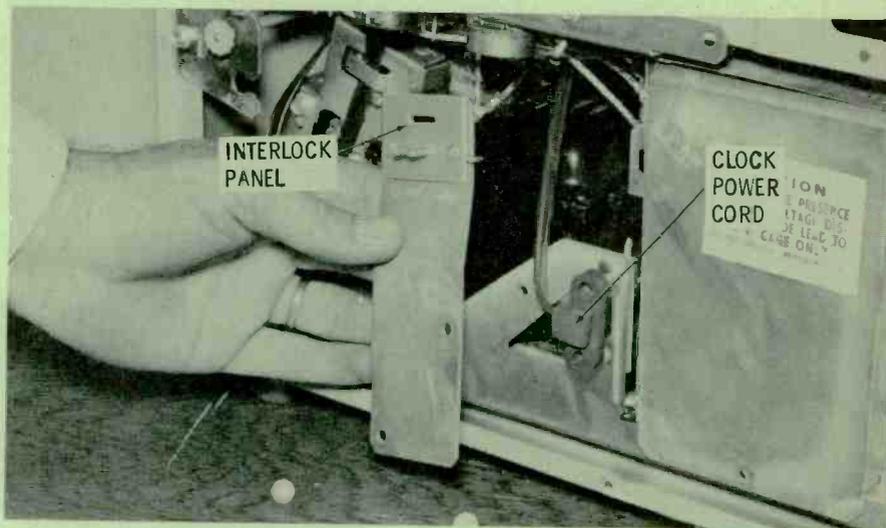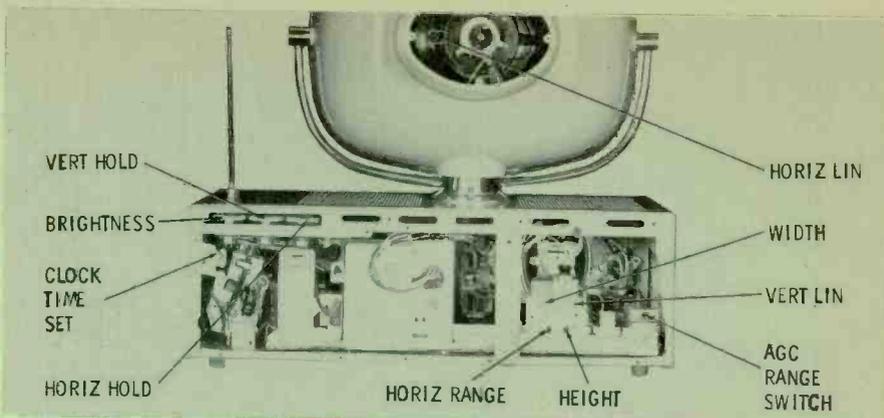

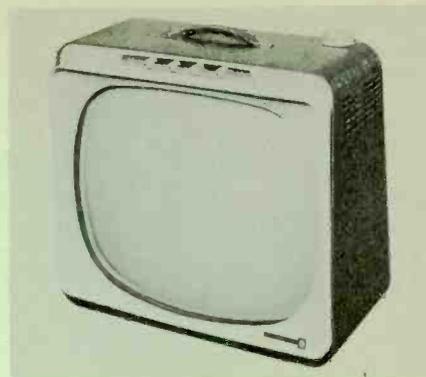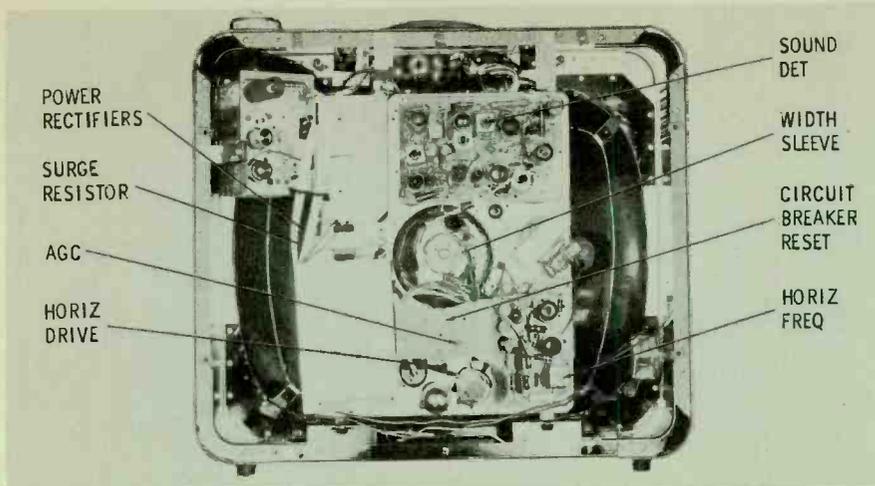

**Silvertone Model
118.5 CH-A
Chassis 528.51643**

The new *Medalist* line features this 21" portable with VHF-UHF tuner and a telescoping antenna built into the rear cover. Controls across the top front include volume control with on/off switch, brightness, contrast, and vertical hold. Station tuning knobs are in one rear corner.





The set employs a vertically-mounted chassis which bolts to both the top and bottom of the cabinet. To make it a little easier to pull the chassis, you'll find that the yoke and speaker have plug-in connections. Two printed boards are used—one for IF and sync stages, and the other for the sweep and oscillator circuits. All service adjustments are pointed out in the photo except height and vertical linearity. These are accessible through the shafts of the brightness and vertical hold controls, respectively.



Like previous Silvertone portables, this set employs 450-ma series-string tubes. Here's the lineup:

- | | |
|-------------------------|----------------------|
| 3CY5-RF amp | 6U8A-sound IF/sync |
| 6U8-conv. | 4DT6-sound det. |
| 3AR4-UHF osc. | 6AQ5A-audio out |
| 4BZ6-1st & 2nd video IF | 13DE7-vert. osc./out |
| 6AM8A-IF/vid. det. | 8CG7-horiz. AFC/osc. |
| 8BA8A-vid. out/sync | 17DQ6A-horiz. out |
| 4AU6-AGC keyer | 17D4-damper |
| | 1K3/1G3-HV rect. |

The *power monitor*, a circuit breaker positioned on a small panel next to the high-voltage cage, acts as a fuse in the input circuit to the low-voltage rectifiers. Since a momentary overload may cause the breaker to open, always check the reset button if tubes light up but raster and sound are not obtained. The "hot" chassis is powered by two silicon units located on the left side behind the chassis pan. You'll also find a 4.5-ohm, 10-watt surge resistor in this area. This component, too, is in series with the B+ rectifier circuit. If it becomes necessary to touch up RF oscillator frequency, you'll note from the photo that two adjustments are provided—one for the high band and one for the low band. Remember not to exert undue pressure on the slug or you may distort the shape of the coil.

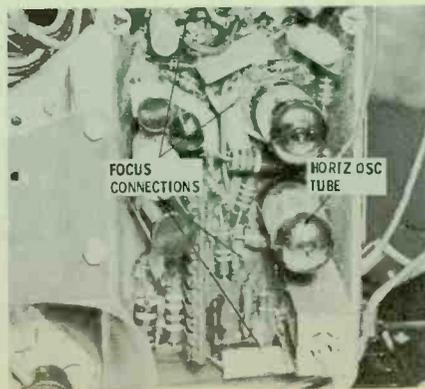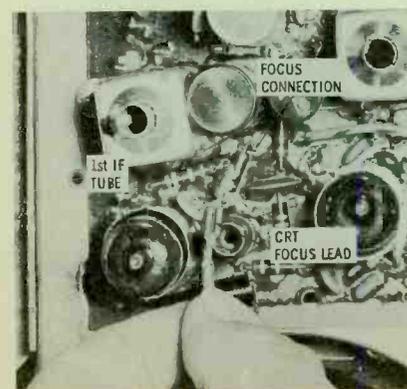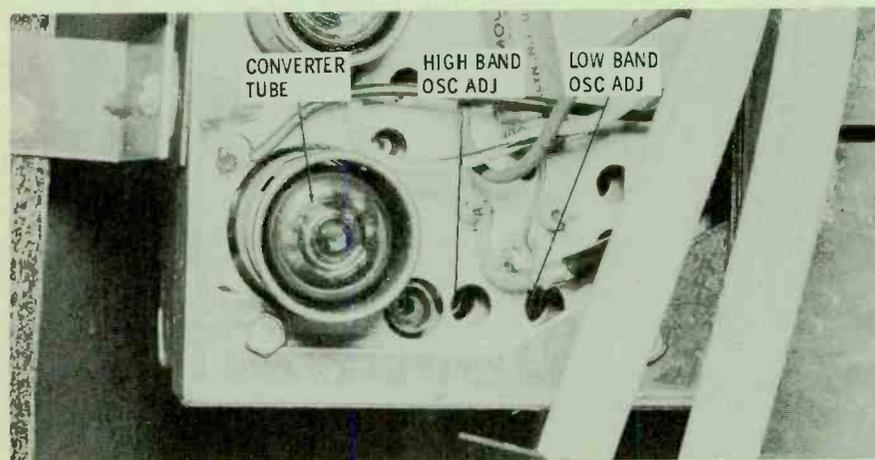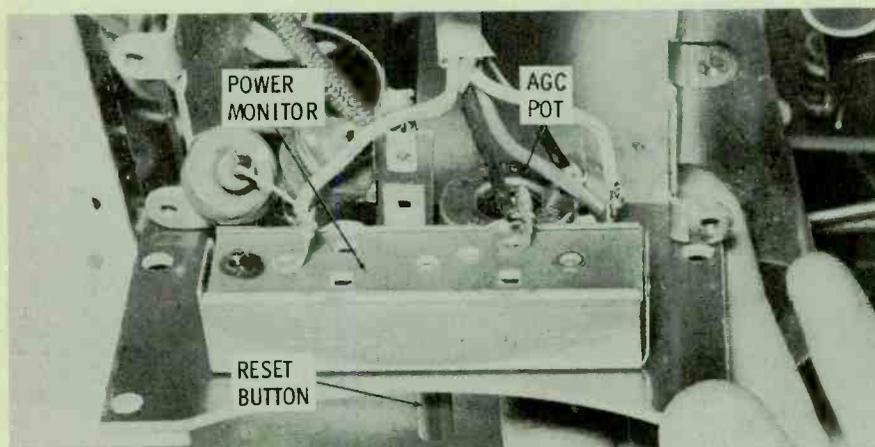Five individual terminals for picture tube focus voltage are provided on the chassis. One connection is located on the upper printed board, and four are on the lower board. These represent five different potentials ranging from chassis ground to 600 volts positive. The blue lead from pin 4 of the CRT should be permanently connected to the point that gives the sharpest focus at maximum brightness.



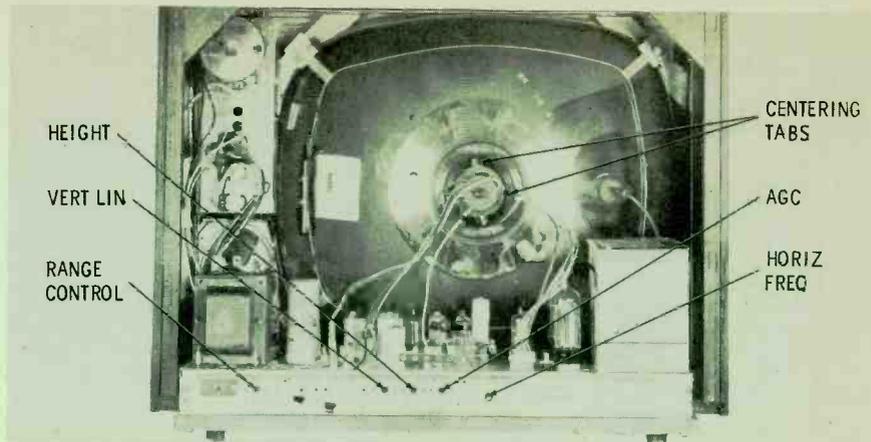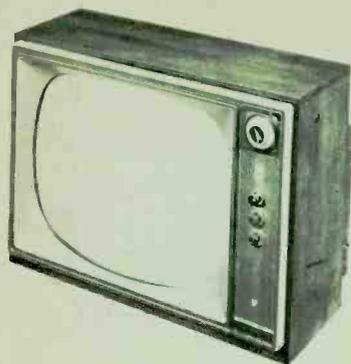

**Trav-Ler Model 821T901
Chassis 1051-19**

A 21" 110° short-neck picture tube and VHF tuner are incorporated in this set. Front operating controls are aligned along the right side, and include a *set-and-forget* volume control. If you're asked to clean the safety glass on this set, don't try to pry the mask off. The chassis and picture tube must be removed to perform this service.




You'll find that the chassis is a horizontal style which mounts across the bottom of the cabinet. It makes use of a power transformer and a parallel circuit for tube filaments; however, no printed wiring is used. The RANGE control located on the rear apron is used to improve sync in fringe areas. It should be set to the most counterclockwise point that provides good sync stability. The latest tube you'll run across in this receiver is a 6DB5 in the vertical sweep section. Incidentally, the 6AS5 audio output tube is used as a voltage divider in the B+ system, so don't forget that it can affect operation of other circuits.

On top of the chassis near the high-voltage cage, you'll find a B+ fuse connected in series with the ground return lead of the power transformer secondary. This "N" type unit is rated at 3/4 amp (slow-blow). The only other fuse in the set is a short length of #26 copper wire for the tube filament supply. It is soldered to a terminal board directly below the power transformer on the wiring side of the chassis.

To get to the high-voltage rectifier (1B3GT), remove only the screw on top of the cage and slide the lid back as shown. The only other major component in the cage is the horizontal output transformer.

A separate control and tuner panel is attached to the front of the cabinet as shown. This assembly comes out after removal of four screws. In this area, you'll also find a #47 dial lamp serving as a channel indicator in front of the *Fireball* tuner. A 4" x 6" oval speaker, with plug-in leads, mounts below the panel.

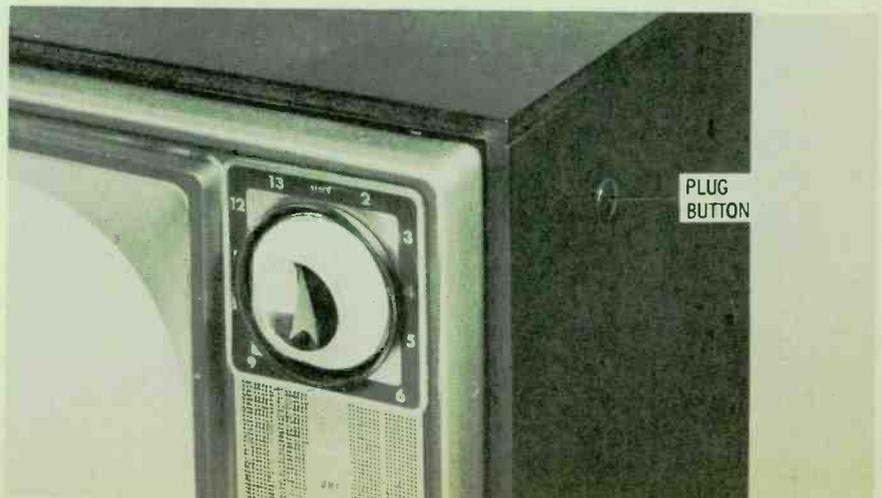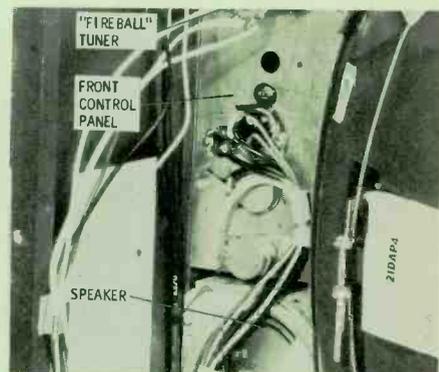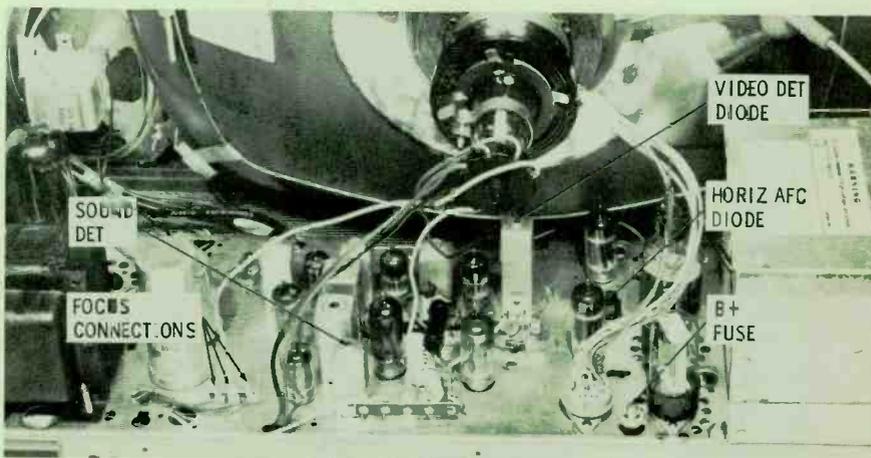To adjust the VHF oscillator of the tuner, remove the button plug located on the upper right side of the cabinet. The hole in the cabinet provides access to the oscillator slug for the channel indicated by the selector knob. The adjustment requires a nonmetallic tool with a tip no wider than 1/8", and no less than 4" in length.




THE WHOLE MULTI-MILLION DOLLAR MARKET HAS HEARD THAT

ASTATIC **PLUG-IN CARTRIDGES**



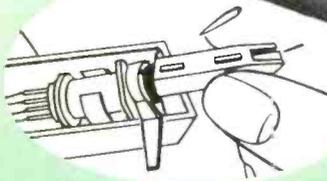ARE THE ONLY COMPLETE LINE THAT MEETS EVERY SALES OPPORTUNITY



AS EASY AS CHANGING A LIGHT BULB
... NO INSTALLATION OR SERVICE PROBLEMS

You've had the message by now—that millions of plug-in phono cartridges have already been sold . . . that Astatic Plug ins represent a tremendous multi-million dollar replacement market . . . and that **THE ONLY COMPLETE, SINGLE SOURCE PLUG-IN LINE ON THE MARKET IS ASTATIC'S!**

So why not use the message? Act now to cash in on this **RICH and SKY-ROCKETING MARKET**. Get into the plug-in business and get into it all the way—never missing a single sale—with **THE COMPLETE ASTATIC PLUG-IN LINE**.

**EASY, AUTOMATIC SALES WITH
ASTATIC MERCHANDISING PACKAGE**

You sell from this plastic display-merchandiser which is pilfer-proof, holds an assortment of a dozen cartridges. Information under each cartridge tells the customer which model he needs. Colorful, attractive window card—free of charge—tells 'em you've got 'em!



CALL YOUR DISTRIBUTOR OR WRITE FOR FULL DETAILS

THE **Astatic** CORPORATION, CONNEAUT, OHIO
KNOWN THE WORLD OVER 
IN CANADA: CANADIAN ASTATIC LIMITED,
TORONTO, ONTARIO
EXPORT SALES: ROBURN AGENCIES INC.,
431 GREENWICH ST., N. Y. 13, N. Y., U. S. A.

**GO BY BRAND
—GO BUY ASTATIC**



A MODEL FOR EVERY APPLICATION — STEREO OR MONAURAL — DIAMOND OR SAPPHIRE TIP

DIFILM[®]



BLACK BEAUTY[®] CAPACITORS BEAT HEAT AND HUMIDITY

New DIFILM Black Beauty Capacitors lead the way in tubulars! The operating temperature range of these new capacitors goes up to 105 C (221 F) *without voltage derating*. **Capacitance tolerance is held to $\pm 10\%$.***

- The new dual dielectric used in DIFILM Capacitors combines the proven long life of paper capacitors with the effective moisture resistance of polyester plastic film capacitors . . . to give you performance that can't be beat.
- Here's the kind of performance you can expect from DIFILM: very high insulation resistance, low power factor, moderate capacitance change with temperature,

excellent retrace under temperature cycling, and superior long-term stability . . . *all at regular prices!*

- This high performance is fully protected by HCX[®], an exclusive Sprague hydrocarbon material which impregnates the windings, filling all voids and pinholes before it polymerizes. The result is a solid rock-hard capacitor section. These capacitors are further protected by an outer molding of humidity-resistant, non-flammable phenolic.

For complete technical information on DIFILM Black Beauty Capacitors, write for Bulletin M-759 to Sprague Products Company, 105 Marshall St., North Adams, Mass.

*From .001 μ F up

The major capacitor improvements come from

SPRAGUE[®]

world's largest capacitor manufacturer

SPRAGUE RESEARCH IS CONSTANTLY PRODUCING NEW AND BETTER CAPACITORS FOR YOU

publisher
Howard W. Sams

general manager
Mal Parks, Jr.

editor
Verne M. Ray

associate editors
Leslie D. Deane
Thomas A. Lesh
Joe A. Groves

consulting editors
William E. Burke
Robert B. Dunham
George B. Mann
C. P. Oliphant
Paul C. Smith

art director
Don W. Bradley

advertising & editorial assistants
Georgeanna Caldwell
Paula Distelhorst

production manager
Robert N. Rippy

circulation fulfillment
Pat Tidd, Mgr.
Ann Mathews, Ass't.
Constance McCawley, Ass't.

photography
Robert W. Reed

advertising sales offices
Midwestern
John Grace, PF REPORTER
2201 East 46th Street, Indianapolis 6, Ind.
Clifford 3-6441

Eastern
Cliff Landis
Corning Glass Building,
717 Fifth Ave., New York 22, N. Y.
Murray Hill 8-6350

Western
The Maurice A. Kimball Co., Inc.
2550 Beverly Blvd., Los Angeles 57, Calif.
Dunkirk 8-6178; and 681 Market Street,
San Francisco 5, Calif. Exbrook 2-3365

Address all correspondence relating
to circulation and editorial to PF
REPORTER, 2201 East 46th Street,
Indianapolis 6, Indiana



Copyright © 1959 by Howard W. Sams & Co., Inc. PF REPORTER is a trademark of Howard W. Sams & Co., Inc. No part of PF REPORTER may be reproduced without written permission. No patent liability is assumed with respect to use of information herein. Acceptance of advertising does not in any manner signify the products, policies and services so advertised have been approved, endorsed or recommended by this magazine.



PF REPORTER®

including Electronic Servicing

VOLUME 9, No. 11

NOVEMBER, 1959

CONTENTS

Previews of New Sets	1
G.E. 21T3421, Philco H-34122, Silvertone 118.5CH-A, Trav-Ler 821T901.	
Video Speed Servicing	5
Hints on Emerson's 1204075, RCA's KCS120A & B chassis.	
Letters to the Editor	14
Tailoring Your Service Technique to the Circuit	24
Shop Talk — Time-saving steps for servicing various TV circuits.	
Examining Video IF Response	30
If IF bandpass circuits are your nemesis, you'll get a lot of help from this.	
Profit by Using a Field-Strength Meter	32
Paul Boller	
A Streamlined "Synchroguide"	34
Servicing New Designs — Here's how RCA's new circuit works, plus hints on service and adjustment.	
Choosing PA Amplifiers	36
Calvin C. Young, Jr. All the facts you need to select the right unit for the job.	
Dollar & Sense Servicing	42
Check that TEMPERATURE	48
Quicker Servicing — Adjusting color receiver gray-scale values requires skill and patience.	
The Troubleshooter	52
Class-A Amplifiers	58
Common circuits that often cause uncommon troubles.	
The Writing on the Wall	64
Industrial Electronics — Using electronically-controlled recorders as service aids.	
Notes on Test Equipment	68
Les Deane Lab reports on the Doss Pioneer 250, Jackson 648R tube tester, and Simpson 270 VOM.	
Coming Next Month	72
Tips for Techs	76
John A. Comstock	
Product Report	93
Free Catalog & Literature Service	96

ABOUT THE COVER

You could say our cameraman was "up in the air" the day he took this month's cover photo. The scene shows a field-strength meter being used to indicate the best position for a TV antenna. Additional uses for F-S meters are covered in the picture story on pages 32 and 33.



JFD HELPS THE SERVICE-DEALER GET BACK INTO PROFITABLE INDOOR ANTENNA BUSINESS. BEGINNING NEXT MONTH* JFD EXACT REPLACEMENT ANTENNAS WILL BE LISTED IN "SAMS PHOTOFAC" FOLDERS. THIS AUTHORITATIVE REFERENCE WILL NOW PROVIDE SERVICE-DEALERS WITH JFD EXACT FACTORY-SPEC REPLACEMENT ANTENNA DATA FOR ALL PORTABLE AND "TOTE-ABLE" TV SETS. AS A JFD EXACT REPLACEMENT ANTENNA SPECIALIST, THE SERVICE-DEALER (NOT THE LOCAL DISCOUNTER) MAKES A FULL PROFIT ON THE SALE AND THE INSTALLATION! . . . REMEMBER, NEXT TO RECEIVING TUBES, PORTABLE TV ANTENNAS REQUIRE THE MOST FREQUENT REPLACEMENT.

DISTRIBUTORS! THIS IS THE BRIGHT NEW FUTURE OF INDOOR ANTENNA BUSINESS. GET IN ON THIS GROWING MARKET. WRITE TODAY FOR PROFITABLE NEW JFD EXACT REPLACEMENT ANTENNA MERCHANDISING PLAN.


***Beginning with SAMS
PHOTOFAC set 467,
this December, 1959.**

JFD

**ELECTRONICS CORP.
BROOKLYN 4, N.Y.
DEWEY 1-1000**



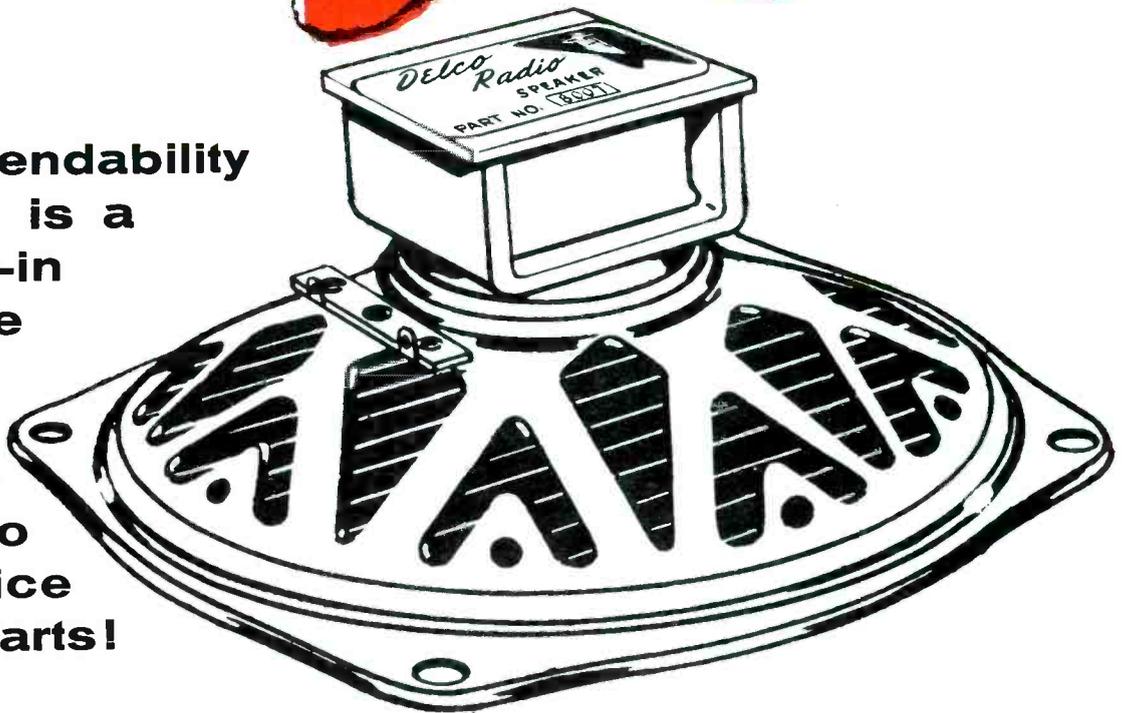**Dependability
is a
built-in
feature
of
all
Delco
Radio
Service
Parts!**



Take speakers, for instance. Delco electronic speakers are built rugged for long life and resistance to extreme weather conditions. You can rely on them for exceptional power handling and rich distortion-free tone.

Delco's popular 8-inch "Hi-Fi" speaker, No. 8007, provides the most power and tonal range for the money. Designed for replacement use and high fidelity audio systems, it's a good, fast seller with price and quality appeal.


For speakers, transistors, transformers and other fine parts for Delco and other radios, see your Delco Electronic Parts Distributor. He carries the complete line. Other extras you get with Delco are • Wide selection of special application parts • Complete technical training program • Effective warranties • Dealer identification signs.

Stock with Delco Electronic Parts—more dependability and reliability for your customers, more profit for you.

DELCO
DEPENDABILITY
RADIO
RELIABILITY

Division of General Motors • Kokomo, Indiana

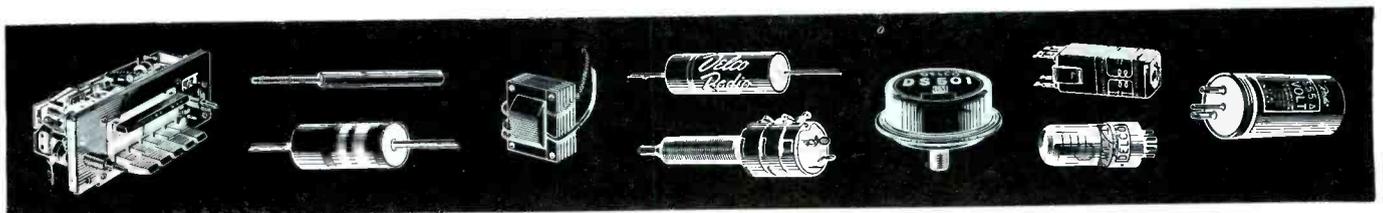Available everywhere through
Electronic Distributors
associated with




Introducing ATR CUSTOMIZED Karadio



Can be installed
in dash or under
dash as desired!

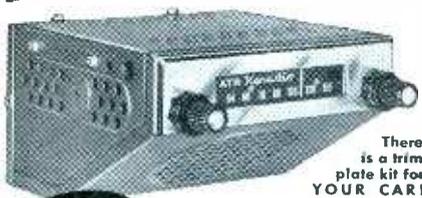for
small import cars
and
compact U.S. cars




There
is a trim
plate kit for
YOUR CAR!

ATR CUSTOMIZED Karadio

• VIBRATOR-OPERATED with Tone Control

The ATR Customized Karadio is a compact, new, self-contained airplane-styled radio for small import and compact American cars. This economical unit is perfect for all small cars because it can be easily and inexpensively installed in-dash or under-dash on most any make or model automobile—and its powerful 8-tube performance provides remarkable freedom from engine, static, and road noises. ATR Karadios are built to look and fit like original equipment with sleek, modern styling and solid, single-unit construction. They offer many customized features and provide highest quality fidelity—yet cost far less than comparably designed units. The ATR Customized Karadio comes complete with speaker and ready to install... and is the ideal way to add fun and value to your small import or American automobile!

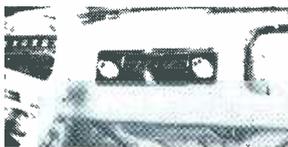

ATR KARADIO
... is ideal
for small import
cars or compact
American
cars! Unit is
completely self-contained—extremely compact!
Can be mounted in-dash or under-dash—where-
ever space permits! For 6 volt or 12 volt!

SEE YOUR JOBBER OR WRITE FACTORY

• "A" Battery Eliminators • DC-AC Inverters • Auto Radio Vibrators



AMERICAN TELEVISION & RADIO CO.
Quality Products Since 1931
SAINT PAUL 1, MINNESOTA, U. S. A.

Letters to the EDITOR

Dear Editor:

Since the lad on your August cover looks like a juvenile, I would suggest he be advised to lay off the ice cream, soda and candy, and avoid attracting bumblebees to his face.

As long as shops employ drugstore cowboys for servicing (which is a mature man's job), mishaps will be a daily occurrence.

Let's cut out the funnies and utilize the valuable cover space for something instructive and educational! Or at least don't create the impression that all servicemen are silly juveniles.

JERRY A. KOUTNIK

Bellaire, Mich.

Our cover man's three children cried when they read what you had to say about their daddy.

We subscribe to the belief that life these days tends to get too terribly serious—in the literal meaning of the word—and a little comic relief serves as good medicine. But we edit the magazine for ALL our readers. What say you, men, about our covers? Like the man says, tell us what you want and we'll give it to you.—Ed.

Dear Editor:

Please send me a corrected four-page reprint of *Video Speed Servicing* for June. I highly compliment you on your speedy correction of such mishaps, and thoroughly understand that any normal human being (editors included) has to make a mistake sometime.

I'm very much satisfied with the contents of your entire magazine, and consider it a strong crutch on which to lean when tackling complicated service jobs.


DAVID FULLER

Furman, Ala.

Sorry you had to run into a splinter in your "crutch." Dave. If anyone else wants reprints of the June VSS, they are still available on request.—Ed.

Dear Editor:

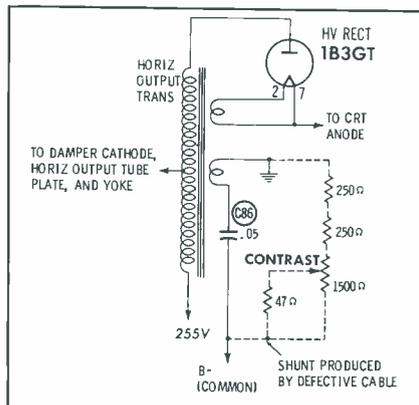I believe I have a possible solution for Oscar Van Kan's problem (*Troubleshooter*, September issue). The type of flyback used in the Motorola Chassis TS-



52 produces an induced voltage from B— to chassis ground, which modulates the video signal and causes an interfering vertical bar pattern in the picture.

To remedy this condition, a small winding is placed around the flyback core. One end is connected to chassis ground, and the other is returned to the B— (black-and-white) line through the .05-mfd capacitor C86. The special winding develops a pulse 180° out of phase with the undesirable induced voltage and equal to it in amplitude, thus resulting in cancellation. I suspect an open C86 or a poor solder connection to this component.

EARL A. HAMILTON

Oklahoma City, Okla.

Dear Editor:

Thanks for your helpful suggestions referring to my trouble with a Motorola TV set. You might like to know that the real source of trouble was the long shielded wire running from the contrast control to the cathode of the 6AH6 video output tube. Its rubber insulation had badly deteriorated, and a single strand of wire in the shield evidently made occasional contact with the center conductor—effectively grounding the 6AH6 cathode. Replacement of the wire cured the trouble.

OSCAR VAN KAN

Cleveland, Ohio

These seemingly unrelated bits of information have a very interesting connection with each other. It seems strange at first that vertical bars on the screen would be produced by grounding the cathode of the video output tube, but the situation is clearer in the light of Mr. Hamilton's logical assumption. The shield on the defective cable is connected to chassis ground, whereas the cathode circuit proper is returned to the common B— bus instead of the chassis. Therefore, the short in the cable would have produced a low-resistance shunt across C86 and the special transformer winding, upsetting the balance between the two out-of-phase pulse signals in the B— circuit. As a result, pulse interference found its way into the video output stage.

We suspected all along that the trouble was due to sweep interference, but we didn't realize it would take this route to reach the picture tube! In a set as old as this one (approaching 10 years), it would be a good idea to replace C86 as a matter of preventive maintenance, even though replacement of the cable seemed to cure the defect.—Ed.

Dear Editor:

In the August *Letters* column, your reply to a query on pay television did not include the latest news on the subject.

The world's first actual pay as you see TV system is now being installed in West Toronto, Canada. It will be on cable (rather than over the air) and will reach an immediate potential of 13,000 homes.

This service will be operated by Trans-


• Please turn to page 20



Ronette Cartridges

cut call-backs

...because they breathe

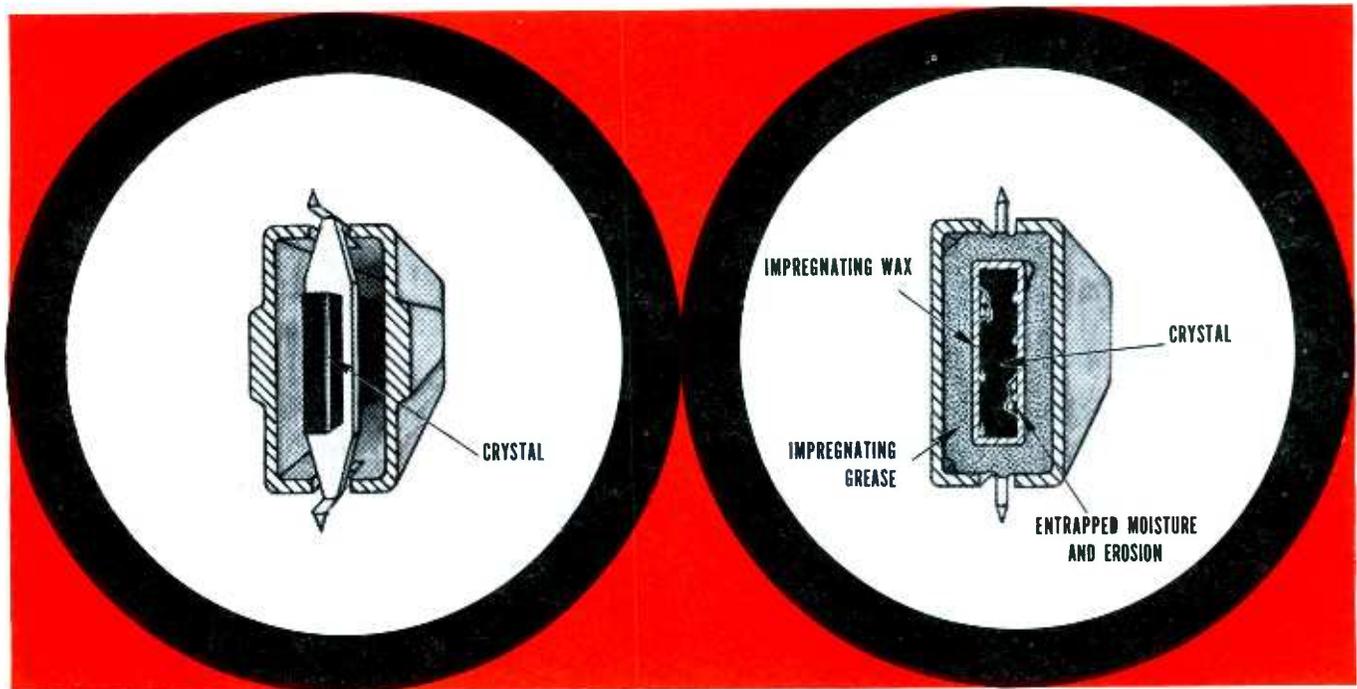

CBS-RONETTE CARTRIDGE

Specially grown crystal is unimpregnated, exposed to atmosphere, breathes, and remains intact.

OTHER CARTRIDGES

Ordinary crystal is not impervious to moisture, must be impregnated, is gradually destroyed by trapped moisture.



OTHER CBS-RONETTE ADVANCED ENGINEERING FEATURES.

- Easy-to-install clip-on styli with foolproof design assuring positive alignment.
- Precision-polished jeweled styli throughout line.
- Simplified line . . . 27 models replace 500.
- Exact replacements for over 6,000,000 cartridges.

An exclusive method of growing and processing Rochelle salt crystals protects CBS-Ronette stereo and monaural cartridges from adverse climatic conditions. These crystals, unlike all others, do not require water-proofing and impregnation . . . which actually traps moisture in the crystal and eventually dissolves it.

Because of its unique structure, the CBS-Ronette crystal can be directly exposed to the air. It *breathes* and does not retain destructive moisture that would dissolve it. This means dependable performance even in the tropics. And to you, it means freedom from irritating, costly call-backs due to shortened life of ordinary cartridges. Cut your cartridge call-backs . . . always ask for CBS-Ronette, the world's most popular cartridge.

CBS ELECTRONICS

Danvers, Massachusetts
A Division of Columbia Broadcasting System, Inc.

CBS FIRSTS IN TUBES



FIRST Bantam GT receiving tubes

FIRST Bantam Jr. subminiature tubes

FIRST rectangular picture tubes

FIRST receiving tubes designed especially for TV

FIRST receiving tubes rated for Continuous Television Service

FIRST practical color picture tube, CBS-Colortron

CBS FIRSTS IN COLUMBIA RECORDS



Leonard Bernstein, outstanding musical personality, is a Columbia Records star.

FIRST double-faced phonograph disc

FIRST (LP) long-playing record

FIRST complete symphony recording in U. S. A.

FIRST "360" hi-fi phonograph

FIRST major recording company with a record club

FIRST Stereo Seven — new seven-inch 33 $\frac{1}{3}$ rpm record



Receiving, industrial and picture tubes • transistors and diodes • audio components • and phonographs

WHAT THESE FIRSTS MEAN TO YOU

In records or tubes, the CBS family habit of being first helps guarantee you the quality of performance that only leadership can deliver. This leadership is your further assurance that:

- CBS tube quality cuts call-backs to the bone.
- CBS tube quality insures your customers of dependable performance.
- CBS tube quality offers built-in profits for you.

Ask for the leader with the top-rated name your customers know and trust. Ask first for CBS.

CBS ELECTRONICS

Danvers, Massachusetts

Electronic manufacturing division of Columbia Broadcasting System, Inc.

HARMONY CBS ELECTRONICS

Portable **Hi-Fi Stereo** with Console Sound

Independent
Service-Dealers!
This is Your line...

YOUR PROFIT OPPORTUNITY

Again CBS Electronics makes it possible for you to expand your business with a dependable product that fills a popular demand. Harmony Phonographs are engineered to uphold your position

in the community as an expert consultant on outstanding value in audio equipment. You can choose from three stereophonic and two monophonic portables, in decorator styles, and priced to sell under \$100.00.

**Suggested retail price. Slightly higher west of the Rockies.*

Identify yourself as a Harmony Phonograph dealer. Get your Harmony Phonographs, attractive consumer line folders and many other sales helps from your distributor.

Or, mail coupon today. 

CBS ELECTRONICS

Danvers, Massachusetts

A Division of Columbia Broadcasting System, Inc.



Model 208, Stereophonic Portable, \$39.95*

So much for so little... a value that you can recommend with confidence. Amazing realism! Has three-speed turntable, True-Track tone arm, and CBS-Ronette high compliance turnover cartridge with jeweled styli.



Model 224, Automatic Stereophonic Portable, \$99.95*

Big console performance. Has a modified simplex push-pull amplifier developed by CBS Laboratories, balanced woofers and tweeters, high fidelity Columbia CD cartridge with fool-proof single jeweled stylus, nonresonant tone arm, treble and bass gain controls, ten watts total peak output, and CBS tubes. Plays records of all speeds automatically.

CBS ELECTRONICS

Danvers, Massachusetts

Gentlemen:

Please send me the Harmony Phonograph consumer line folder, dealer helps booklet, and the name of my nearest distributor.

Name.....

Address.....

City..... Zone.....

State.....

... the smartest move you can make

is to **TRIPLETT VOMs**

*... the world's most complete
line of VOMs for every purpose!*

**639-N
CASE**

**MODEL
666-R**

**MODEL
666-
HH**

**MODEL
630**

**MODEL
630-A**

**MODEL
630-APL**

**MODEL
630-NA**

TRIPLETT

*Quality...
First to last*

**TRIPLETT ELECTRICAL INSTRUMENT COMPANY
BLUFFTON, OHIO**

TRIPLET

Quality...
First to last

**TESTER
STAND**



**HI-
VOLTAGE
PROBE**




**MODEL
625-NA**

**INTERIOR
VIEW
(630)**



**MODEL
630-PL**

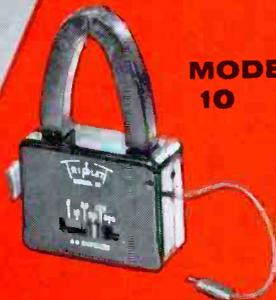

**MODEL
10**

**MODEL
631**



**MODEL
310**

Model 639-N Case \$9.50. Handsome, black cowhide leather. Center-cover flaps snap back for full view of scales and complete access to instrument without removal from case.

Model Pt. T-225-A-33 Tester Stand \$0.50. Metal, holds tester in approximately 45° angle; facilitates easy reading.

Probe for High Voltage Testing \$14.50. For models 630, 630-A, 630-PL, 630-APL, and 631. Completely insulated polystyrene; guard-type handle. 11 1/4" long; 48" hi-voltage wire lead with banana plug at tester end. Available in 0-12,000 AC or DC volts, and 0-30,000 AC or DC volts.

Model 630-T \$54.50. Specially designed for telephone maintenance. 2% accuracy on DC. Fused protected circuit protects resistors and meter in ohms ranges. Special neck strap holds instrument, freeing both hands. Banana jack connectors eliminate all shock hazard. Completely insulated case protects from ground.

Model 666-R Pocket VOM \$29.50. Hand size, ideal for electrical maintenance. With recessed range knob it fits easily into case. AC rectifier pre-calibrated unit for easy replacement. Banana jacks at panel top prevent leads falling over meter dial. Single king-size selector switch minimizes incorrect settings, burnouts. Molded case streamlined, fully insulated.

Model 666-HH Pocket VOM \$27.50. Compact, hand-size; 3" meter integral with panel, adjusted to 400 microamperes at 250 millivolts. Only 3 jacks necessary for all ranges. 19 ranges.

Model 625-NA \$54.50. Dual sensitivity for extra ranges; large mirror scale for super readability. 3-color meter scale 5" long. 6" instrument, 0-50 microamp. AC volts at 10,000 O/V for checking many audio and high impedance AC circuits usually requiring VTVM. 38 ranges. Molded insulated case.

Interior View showing advanced engineering features of all Triplet VOMs. Molded mounting for resistors and shunts allows direct connections without cabling. Eliminates shorts. Longer life.

Model 630 \$44.50. Popular, streamlined; long meter scales for easy reading. Outstanding linear ohm scale; low reading 1 ohm, high 100 megs. Single king-size selector-switch minimizes incorrect settings, burnouts. High sensitivity: 20,000 ohms per volt DC; 5,000 AC. Molded, fully insulated case.

Model 630-A \$54.50. Laboratory type; 1/2% resistors for greater accuracy. Long mirrored scale eliminates parallax. Banana jacks, low resistance connections; high flux magnet increases ruggedness. Single king-size selector switch minimizes incorrect settings, burnouts. Molded fully insulated case.

Model 630-PL \$44.50. Instant-vision, wider spread scales; streamlined case; handsome modern design. Unbreakable window. Outstanding linear ohm scale; low reading .1 ohm; high to 100 megs. Single king-size selector switch minimizes incorrect settings, burnouts. 5 to 500,000 cps frequency response in AC measurements. DC Polarity Reversing switch. High sensitivity: 5,000 ohms per volt AC; 20,000 ohms per volt DC.

Model 10 Clamp-On Adapter \$14.50. Checks line loads with model 310 (can also be used with 6 other models). Instant, accurate, safe. No circuit breaking or work interruption. Easy range switching. Available in 6 AC Ammeter ranges: 0-6-12-30-60-120-300. Clips around single wire to read AC Amperes direct. Use with adapter 101 to instantly divide 2-conductor cords. Molded case fully insulated, black plastic with engraved white markings.

Model 630-APL \$54.50. Laboratory type with 1/2% resistors, more accurate movement. Long mirrored scales eliminate parallax. Unbreakable window. Single king-size switch minimizes incorrect settings, burnouts. 5 to 500,000 cps frequency response in AC measurements. DC Polarity Reversing switch. High sensitivity: 5000 ohms per volt AC; 20,000 ohms per volt DC. Molded case fully insulated.

Model 630-NA \$74.50. Super DeLuxe with 70 ranges—nearly double conventional types. Frequency compensated from 35 cps to 20 kc. Temperature compensated. Accurate within 1 1/2% full scale reading on DC. Large open front meter easy to read. Unbreakable window. Mirrored scale. Meter protection against overloads. Molded fully insulated case.

Model 631 Combination VOM and VTVM \$64.50. Two fundamental units at the price of a single tester. The No. 1 instrument for all electronic men. Battery operation assures VTVM stability and long life. Sensitivity PLUS. 1.2 volt (VTVM) range is equal to more than nine million ohms per volt. Large easy to read meter with unbreakable face. Single king-size selector switch minimizes incorrect settings, burnouts. Molded case fully insulated.

Model 310 \$34.50. The only complete miniature VOM with 20,000 ohms per volt and selector range switch. Self-shielded against strong magnetic field. Rugged, high torque, bar-ring instrument. Unbreakable plastic meter window. Converts to common probe—frees one hand—by fitting interchangeable test prod into top. Standard sensitivity 20,000 ohms per volt DC, and 5,000 ohms per volt AC. Accuracy 3% DC. Molded fully insulated case.

BURTON BROWNE ADVERTISING

TUBE PROBLEM:

The Armed Forces needed a new version of the 6J4 reliable tube type which would provide a tube life of almost 1000 hours. Existing tubes of this type had an average life of only 250 hours. In addition, this new tube had to be produced under ultra-high quality control standards.

SONOTONE SOLVES IT:

By making improvements in the cathode alloy and setting up extremely tight controls in precision, manufacture and checking, Sonotone engineers produced a 6J4WA with a minimum life of 1000 hours... most running much longer.

RESULTS:

The Sonotone 6J4WA is one of three reliable tubes now being manufactured under U.S. Army Signal Corps RIQAP (Reduced Inspection Quality Assurance Program) monitored by the U.S. Army Signal Supply Agency. And the same rigid quality standards apply to Sonotone's entertainment type tubes as well.

Let Sonotone help solve your tube problems, too.

Sonotone

Electronic Applications Division, Dept. TP-119

ELMSFORD, NEW YORK

Leading makers of fine ceramic cartridges, speakers, microphones, tape heads, electron tubes

In Canada, contact Atlas Radio Corp., Ltd., Toronto

Letters

(Continued from page 14)

Canada Telemeter Ltd., a Division of Famous Players Canadian Corp. Ltd., the largest motion picture theater chain in the Dominion of Canada. The system will utilize Telemeter transmitters and home units developed by International Telemeter Co., a Division of Paramount Pictures.

Canadian Bell Telephone Co. is now installing 84 miles of overhead and underground cable to carry the three-channel program service to be offered. The system will begin operating before the end of this year.

WILL BALTIN

International Telemeter Co.
New York, N. Y.

This should help to settle the question once and for all as to whether people will pay to see television shows! We'll be watching with an interested eye for further developments.—Ed.

Dear Editor:

In July *Letters*, you mentioned that two volumes of *Video Speed Servicing* have already been published. I would like to know if they are made up like the sheets in PF REPORTER and where they can be purchased.

EARL W. WEHR

Barnesville, Ohio

Essentially, the information in these books is presented in the same manner as in PF REPORTER. The main difference is that the schematics in Volumes 1 and 2 use the manufacturer's component designations (R- and C- numbers), whereas PF REPORTER uses PHOTOFAC numbers. Volume 3 of VSS, just published as a Sams book, uses the same format employed by us.

Ask your parts distributor for the first two volumes; if he doesn't have them on hand, he can order them for you. Copies of Volume 1 (what few are left) sell for \$4.95 each; Volumes 2 and 3 are \$2.95 each.—Ed.

Dear Editor:

We expectantly await each month's issue of PF REPORTER, which is probably the most widely read magazine in our organization.

For your records, our new officers for 1959-60 are: Ralph Johonnot, president; Everett Pershing, vice-president; Gene Sheppard, secretary; Jimmie Scarborough, treasurer; and E. L. Bizzell, Felix Garrett, Winfield Howie, Ralph Singleton, and Walter Heuman, members of the board.

GENE SHEPPARD

Secretary, Society of Radio & Television Technicians, Inc.
Glendale, Calif.

Congratulations, gentlemen. Our best wishes for your success at the helm.—Ed.

Dear Editor:

I prize the information in *Video Speed Servicing* along with some of the most expensive data I have. While I'm at it, I want to thank you for such a wonderful magazine. I have stopped my subscription to two other publications because yours has everything I need.

Please keep PF REPORTER the high-class publication that it is, and don't ever cut down on any section—especially the *Troubleshooter* column. I'm not trying to flatter you; this is just the way I feel about your magazine.

JOSEPH J. MASARONE

New York, N. Y.

Thank you.

You're welcome.

Thanks again.

We'll do our best.

Thank you.—Ed.

Dear Editor:

In September *Letters*, Gene's Radio and TV Shop requested your assistance in securing information on European-made tubes UCH71 and UEL71 for a Schaub radio. As you stated, these tubes are probably difficult to find on the U.S. market. You suggested he should contact an European supplier, and perhaps he has done so by now. However, if he has not been able to correspond with a German firm, I should like to put him in touch with a good friend of mine who is a jobber for Lorenz/Schaub and might be able to help him. His address is:

E. Ruppert
c/o Radio Lorenz
284 Eckenheimerlandstr.
Frankfurt Main
W. Germany

Please mention my name in any correspondence.

Hoping this information will be a small sign of my appreciation for the nice job you do for us service people.

KARL H. PAQUEE

Stratford, Con.

Small sign? With an address like Ruppert's, it's more like a billboard! Many thanks for your help.—Ed.

Dear Editor:

Do you have a recommended tube stock list for radios only? I would like to stock a tube kit for radio servicing, so I won't have to lug along my big 400-tube TV caddy when I get a call to repair a radio.

A. G. HESHMATI

Carmel, Calif.

We haven't made up a stock guide for radio tubes, since only a small number of well-known types are used in most post-war radios. Now that you have called this matter to our attention, we are suddenly reminded that quite a few radios almost a generation old are still in service. Perhaps we'd be doing a useful service if we made up a chart of radio tubes, including the obsolescent types with which our younger readers are not well acquainted.

Speaking of tube stock requirements, our Stock Guide for TV Tubes appeared in the last issue. The later version has been expanded to include a new feature—a recommended tube-caddy stock comprising 350 tubes of approximately 200 types. You should find this listing helpful whenever you refill the 400-tube "whopper" you carry on TV calls.—Ed.

THIS SHOP IS MAKING MONEY



with **CLAROSTAT** RTV controls

Radio and television repair shops in all parts of the country are increasing their profits with Clarostat RTV controls—the controls that are *right* for the job, *right* from the carton.

RTV controls are manufactured as matched replacements under rigid quality control standards at the factory. Clarostat offers the direct replacement for practically every radio and TV set control ever produced. RTV controls can save you many hours per man per week, raising your output and multiplying your profits.

Always ask for CLAROSTAT!



GET THE COMPLETE DETAILS ON RTV CONTROLS FROM YOUR DISTRIBUTOR

CLAROSTAT MFG. CO., INC.

DOVER, NEW HAMPSHIRE

In Canada: CANADIAN MARCONI CO., LTD., Toronto 17, Ont.

"TUBE INVENTORY DOWN 30%,

... from using General Electric's **PROFIT*** Program. That's the dollar-saving, income-building record of Chicago partners Robert Knudsen and Harold Russell!



* Programmed Replenishment OF Inventory Turnover

"We're moving more tubes than ever, with a stock one-third less. Inventory turnover is that much higher, which shows in increased profits." The two busy partners of Tel-Rad TV Sales-with-Service, 5839 Belmont Ave., Chicago, name this as their principal benefit from General Electric's new PROFIT* Program.

Another big saving—space! The compactness of the General Electric Inventory Rack means that a service dealer can do away with 50 to 60 feet of shelving. Furthermore, the attractive, organized display of tubes gives the shop a modern and professional-looking appearance.

Knudsen and Russell add, "Now our tube stock's geared to our needs. And it stays that way—plenty of fast-selling types, a minimum of slow movers. The distributor's weekly re-order visit takes care of everything." No stock-taking or clerical work by the partners is involved. This saves them time for profitable repairwork.

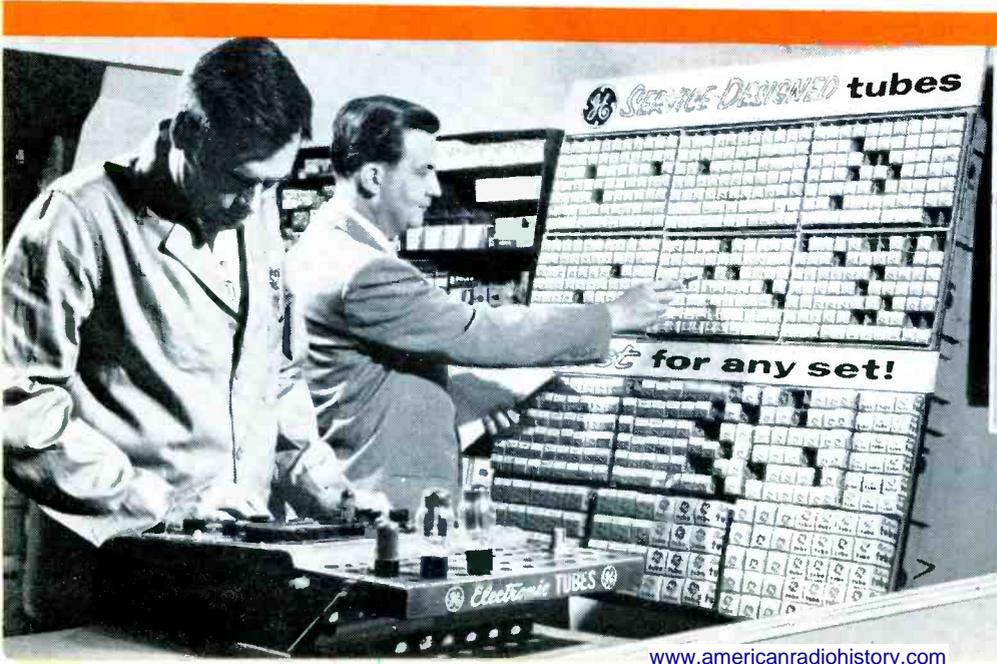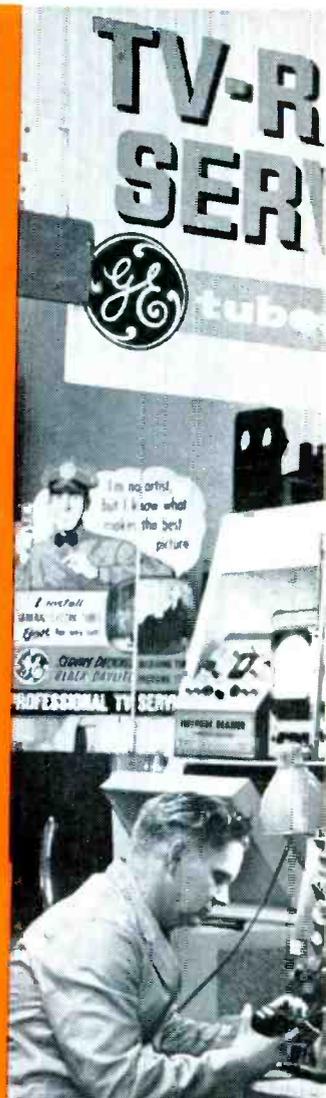You too can increase turnover and boost income with General Electric's new PROFIT* Program. Available with the purchase of tubes from your G-E tube distributor. See him today! *Distributor Sales, Electronic Components Division, General Electric Company, Owensboro, Kentucky.*



TEL-RAD'S SERVICE WORK

doesn't stop while tube stocks are being checked. Here Richard Schlueter (facing rack in picture at left), salesman for Melvin Electronics, General Electric tube distributor, inspects the PROFIT* tube inventory for types to re-order. Schlueter does this job weekly, handling all routine and paperwork—thus saving valuable time for Knudsen and Russell.

OUR SALES ON THE INCREASE!"



Progress Is Our Most Important Product

GENERAL  ELECTRIC

2-111-223

TAILORING YOUR SERVICE TECHNIQUE TO THE CIRCUIT

MILTON S. KIVER

In my last column, I outlined the preliminary steps in servicing a defective television receiver. This includes finding out all you could about the behavior of the set from the owner, noting which section appeared to contain the trouble, and then checking tubes in that section. Simple as this procedure is, it will uncover many of the troubles normally encountered.

Now the question is, "If none of the tubes are defective, what do you do next?" The answer depends on the section of the receiver suspected of harboring the trouble. For example, in the sync and sweep sections, waveform analysis will initially be of more value than voltage measurements. On the other hand, a VTVM generally proves more useful than a scope for checking AGC and power supply circuits. In signal-amplifying stages, a signal-injection procedure is more likely to yield faster results than any other.

Thus, we see that *different* sections of a TV receiver require *different* servicing approaches. And, if you are to gain any speed in your work at all, it is important that the difference in treatment be carefully learned. It is here that the experienced technician achieves his greatest advantage over the beginner. The man with experience knows which test instrument is best suited for certain jobs, and he uses it right from the start.

In the discussion to follow, it is assumed that the tubes associated with a section have been checked and found to be good.

The Power Supply

In some power-supply circuits, semiconductor diodes are employed in place of a rectifier tube. These components are prime suspects in the event B+ voltage is low. Here's the quickest way to locate trouble within a tubeless power supply:

First, check the DC output voltage as shown in Fig. 1. If it's low, measure the rectifier input voltage and then the AC line voltage. If the latter two measurements are normal, the semiconductor rectifiers should be tested by instrument or by direct substitution.

As for tube-type power supplies, the condition of the rectifier can readily be determined by simple substitution, but if a new tube fails to restore full B+, further tests (similar to those outlined above) should be tried. See Fig. 2.

In case none of the foregoing tests uncover the trouble, disconnect all the load lines from the power supply, and see if this brings the voltage back to normal (or above). If not, leaky filter capacitors may be pulling down the B+ voltage. If the output does return to normal, the trouble is due to excessive current drain resulting from low resistance

• Please turn to page 79

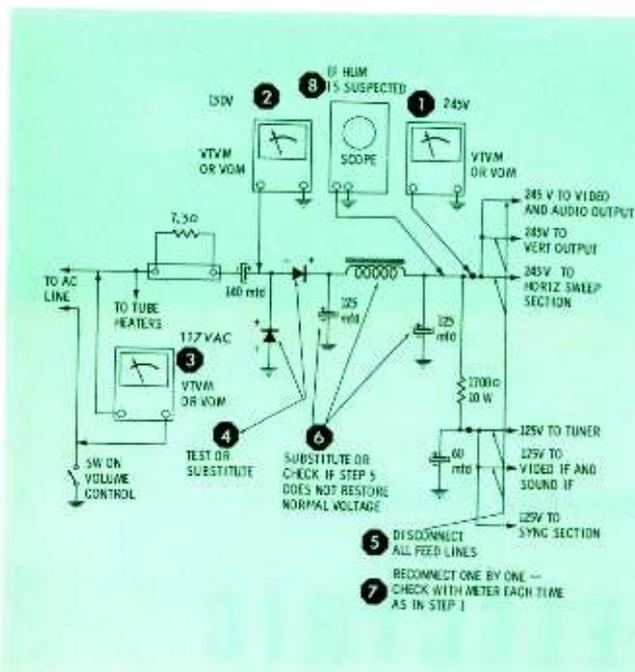


Fig. 1. Troubleshooting a semiconductor power supply.


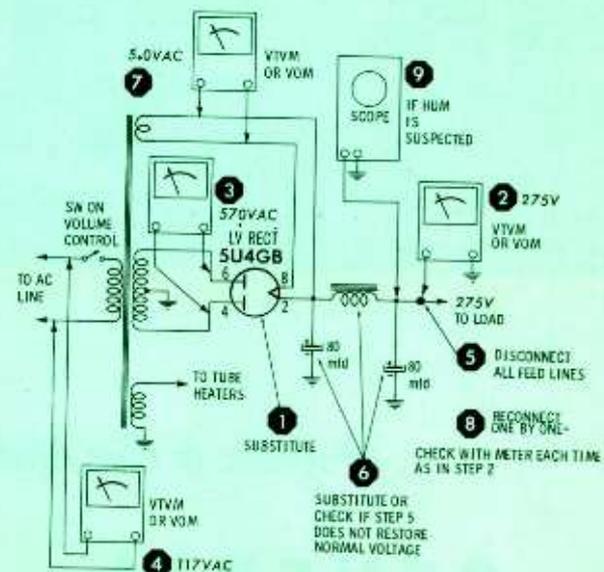


Fig. 2. Troubleshooting a tube-type power supply.

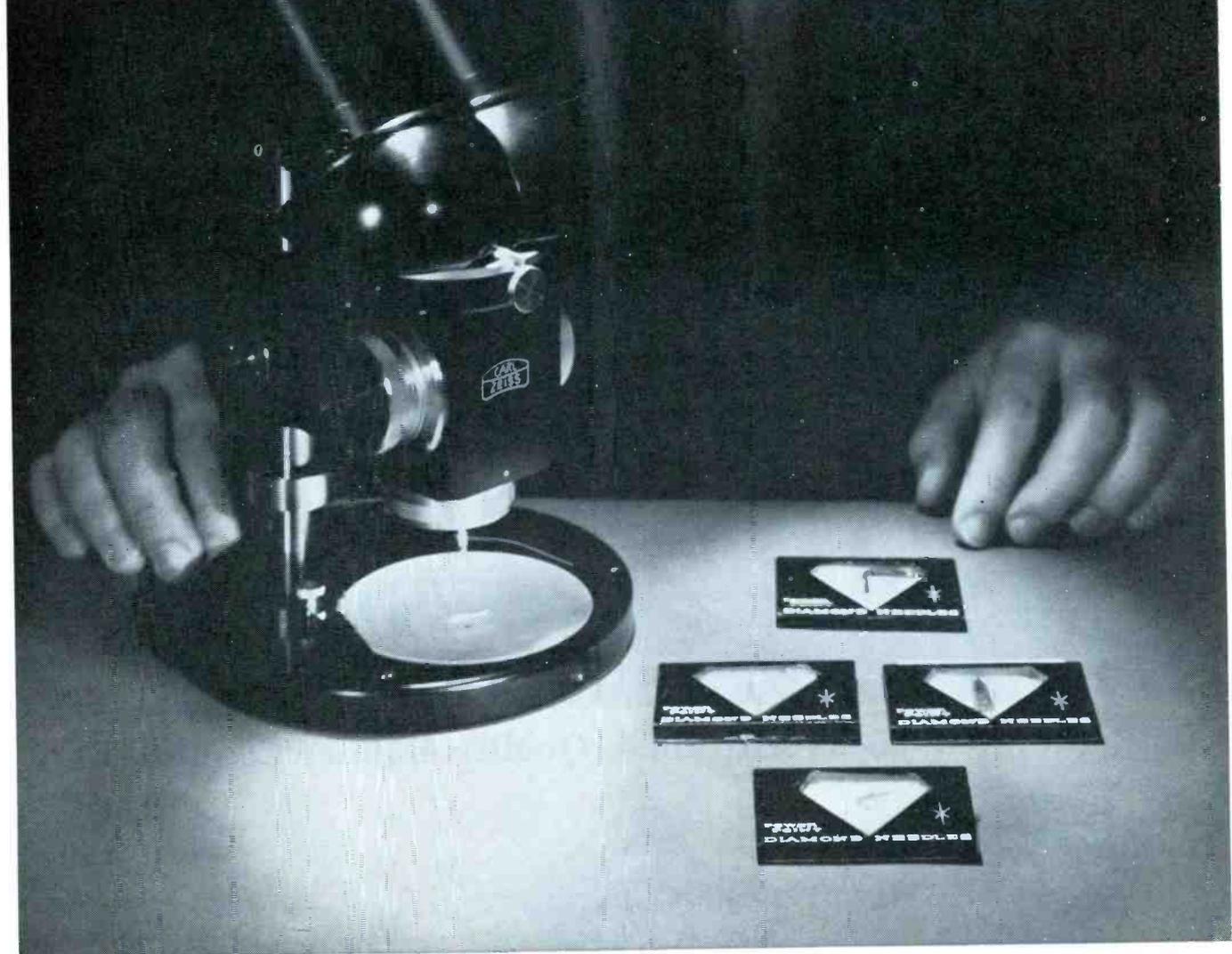ONLY A COMPANY INVOLVED IN ALL PHASES OF SOUND REPRODUCTION CAN PROVIDE REPLACEMENT NEEDLES MATCHED TO OVERALL SYSTEM REQUIREMENTS. ELECTRO-VOICE NOW OFFERS A COMPLETE REPLACEMENT LINE FOR EVERY CARTRIDGE



The great strides of recent years in the design and production of high-fidelity systems have been noticeably lacking in the area of replacement needles. Virtually every needle sold today was designed by a cartridge manufacturer. Few needle producers satisfy the rigid requirements of cartridge manufacturers. Now, E-V the leading cartridge manufacturer, with its large staff of engineers and trained personnel, offers you the opportunity to sell replacement needles that will produce the finest sound available.

Write for your copy of the new Electro-Voice Needle and Cartridge Replacement Guide

- Only from Electro-Voice, originator of the permanent needle cartridge would you expect to receive the high standards of quality and performance demanded by modern sets.

- Only from Electro-Voice, marketing and sales promotion innovator, would you expect to receive dynamic promotions that increase and safeguard profits.

- Only from Electro-Voice, with its vast facilities, would you expect to receive service and delivery which solve your inventory problems.

Electro-Voice INC., BUCHANAN, MICHIGAN—the complete quality replacement needle line

TV Technician TAYLOR THURMAN Explains . . .

"In Precision Circuitry,




Stop Call-backs with these Quality Mallory Components



Gems—5 rugged, moistureproof, Mallory "Gem" tubular capacitors in an easy-to-use dispenser that keeps your stock fresh and clean—easy to find—no more kinks in lead wires. They're your best bet for outstanding service in buffer, bypass or coupling applications.



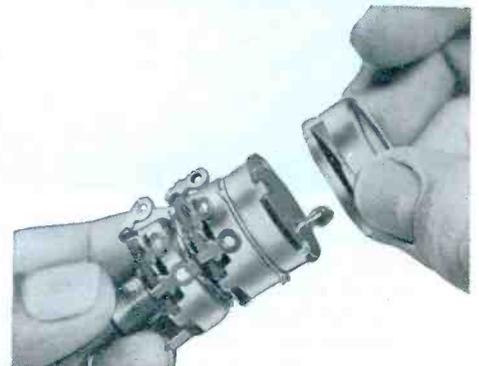FP Electrolytics—The Mallory FP—the original 85°C capacitor—now has improved shock-resistant construction and leakproof seal. Its etched cathode construction—standard in all FP's—assures hum-free performance.



Sta-Loc* Controls—New Sta-Loc design enables your distributor to custom build, in just 30 seconds, over 38,000 combinations—eliminates waiting for out-of-stock controls. You can replace the line switch by itself, without unsoldering control connections.

There's Nothing Like Mallory RMC Discaps[®]

"When it comes to replacing ceramic capacitors, we always use Mallory RMC Discaps. Time and again, they've proved dependable. For TV tuners and other precision circuitry the extra quality built into Mallory makes the difference between a satisfied customer and money losing call-backs."

When you're looking for high quality, sensibly priced components, check with Mallory. You get the widest selection of parts in the industry . . . and every Mallory component is service-engineered: your assurance that the parts you replace will be in service for a long, long time.

Taylor Thurman has operated his own TV repair service for more than 10 years. The Air Force gave him early training in electronics. At Scott Field, he became a Communications Chief. Later on, he attended the G.E. Television School in Syracuse. At his Richmond, Indiana, location, he now has two technicians helping him in radio and TV sales and service . . . operates two service trucks. Prompt attention to service calls and use of quality replacement parts are the chief factors to which Thurman attributes the steady growth of his business.



Get your RMC Discaps—in the handy 3 x 5 file card five-pack—from convenient display at your Mallory distributor's store.

©Trademark of Radio Materials Co.,
a Division of P. R. Mallory & Co. Inc.



TC Tubular Electrolytic Capacitors—economically priced electrolytic filter capacitors with a reputation for doing an excellent job. They have been proved in performance and are backed by years of Mallory experience. Also special TCX type available for -55°C .



Gold Label* Vibrators—On critical auto radio servicing, use the Mallory Gold Label Vibrator. It gives longer, trouble-free service life. Mallory Gold Label Vibrators feature Mallory exclusive buttonless contact design.

*Trademark



Silicon Rectifiers—New Mallory design gives far longer life, lower forward voltage drop, and reverse leakage current than conventional types . . . exceed the requirements of military humidity tests. In convenient kits for replacement of selenium rectifiers in radio and TV.



"It's good business to use this 90-day Repair Bond," says Ken Rodrigue. "We find it helps the customer feel, more than ever, that he has received full value from his service dollar."

“Most Constructive Step in the Industry”



“The new Raytheon Bonded Dealer Program is the best step yet towards identifying competent and reliable service organizations.

“It really goes a long way in assuring the public that its investment in qualified service is the best means—maybe the *only* means—

of enjoying trouble-free radio and TV.

“And this assurance is actually put right in their hands with the Raytheon 90-day Repair Bond.


“In addition, Raytheon backs the Bonded Dealer Program with national consumer advertising. And the Raytheon distributors supply local direct mail and advertising support. The average dealer couldn't afford this. Speaking for ourselves, we've tied into these programs with great success.

“Of course, we know that advertising promises have no value without quality products to back them up. Nine years of Raytheon tubes and CRT's have proved to us that a dealer can count on the Raytheon brand name.


“Congratulations on the whole Bonded Dealer Program—we know that it's helping us to increase profits.”

K. J. Rodrigue, President
Rodrigue's Radio & Television, Inc.
Milford, Conn.

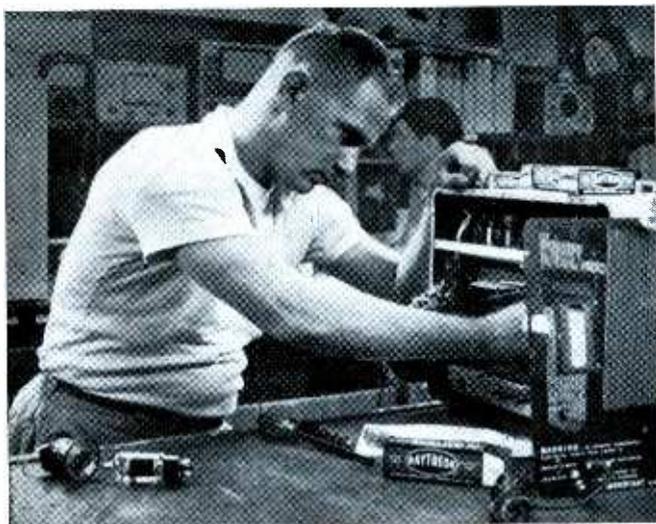Cash in! If you haven't signed up as a Raytheon Bonded Dealer, call your Raytheon Distributor today to march with the profit parade.



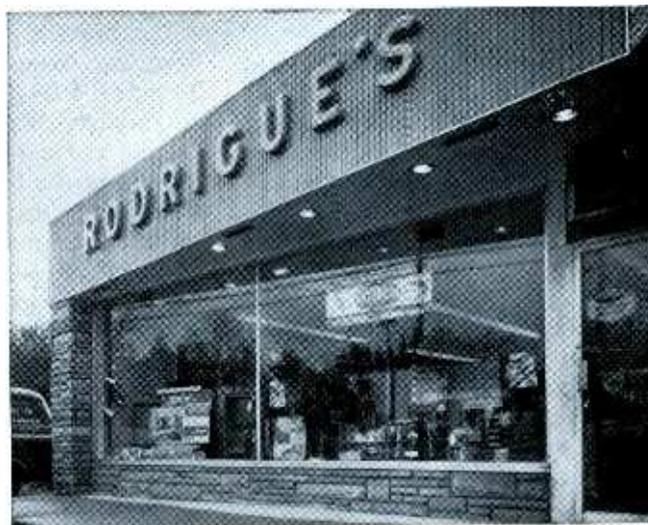
“We average over 6000 service jobs a year,” says Ken. “To achieve this kind of volume we depend on the skill and efficiency of our service technicians and top-quality Raytheon Tubes.”



“As Milford's largest servicing organization we have counted on Raytheon quality since the day we opened,” relates Ken. “In addition I like the 24 hour service I get from my Raytheon distributor.”

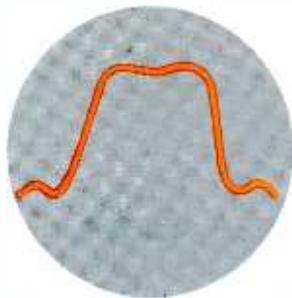RAYTHEON COMPANY • DISTRIBUTOR PRODUCTS DIVISION





EXAMINING

The bandwidth of a video IF amplifier system must be very broad, so that the wide range of modulating frequencies on the TV picture carrier (approximately 0-4 mc) will all be equally amplified. There is no getting around this fact, even though a technique called vestigial-sideband transmission is used to restrict bandwidth to a minimum.

If conventional double-sideband transmission were employed in TV, as it is in radio broadcasting, a video IF bandwidth of over 8 mc would be required. However, most of the lower sideband is filtered out of the TV signal, leaving only a small portion containing frequencies up to about 1.25 mc (see Fig. 1 for details). This arrangement permits a reduction in IF bandwidth to 6 mc or less with no loss of picture detail.

Vestigial-sideband transmission makes it necessary to tune the IF strip in an unconventional manner. Ordinary IF amplifiers of the type used in radios are designed to amplify frequencies on either side of the carrier equally. If the same procedure were followed in amplifying the video IF signal, the lower modulating frequencies (present in both the upper sideband and the remnant of the lower one) would produce twice as much power output as the higher modulating frequencies (which are present only in the upper sideband). This situation is illus-

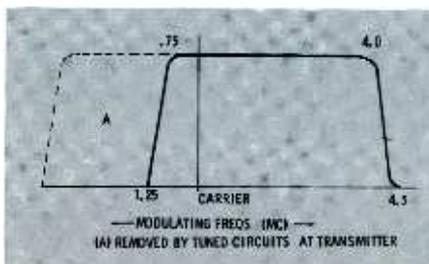


Fig. 1. Part of one sideband is omitted in vestigial-sideband transmission.

VIDEO-IF

RESPONSE

How circuit design affects bandpass characteristics by Irving Tepper

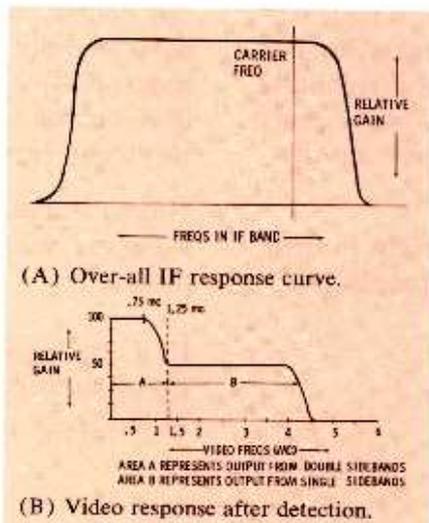


Fig. 2. Response curves when all sidebands receive 100% amplification.

trated in graph form in Fig. 2.

To prevent overemphasis of the low video frequencies, it is necessary to tune the IF strip so as to produce a specially-shaped gain-versus-frequency curve (Fig. 3). Placing the picture-carrier frequency at the midpoint along the sloping side of this curve (in other words, allowing only 50% of full gain at this frequency) serves to compensate for the presence of a vestigial sideband.

Fig. 3 demonstrates that dual sidebands are present for modulating frequencies between 0 and 0.75 mc, but that each sideband receives only partial amplification. The curve is shaped so that the total gain for any given frequency will be equal to 100%. For example, a modulating frequency represented by point A on the upper sideband will receive only 75% of full gain; but this same frequency on the lower sideband (falling at point B) will receive additional gain amounting to 25%. Due to partial amplification of the two sidebands at all frequencies from 0 to ± 0.75 mc (be-

tween points E and F in Fig. 3), the same results are obtained as for straight 100% amplification of a true single-sideband signal.

Response to Sound Carrier

While most TV receivers have similar over-all IF response curves, there are some differences between intercarrier and split-sound receivers with respect to curve shape. The major point of difference is that the intercarrier IF must amplify the sound carrier as well as the picture carrier. In the split-sound set, the sound carrier is excluded from the video IF amplifier strip by resonant trap circuits; thus, the sound-carrier frequency in the response curve of Fig. 4A appears to rest in a "notch" at virtually zero gain. On the other hand, a typical intercarrier IF curve (Fig. 4B) shows the sound-carrier frequency receiving about 5% to 10% of full gain.

Curve Formation

The over-all video response curve may be formed in one of several ways. The most generally-used method is known as *stagger tuning*. Each stage in a stagger-tuned IF strip is resonant to a slightly different frequency, and the response curves of all stages add together to produce a broad, flat-topped over-

• Please turn to page 83


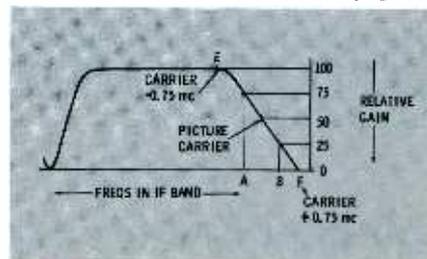


Fig. 3. Side of IF curve is sloped to compensate for vestigial sideband.

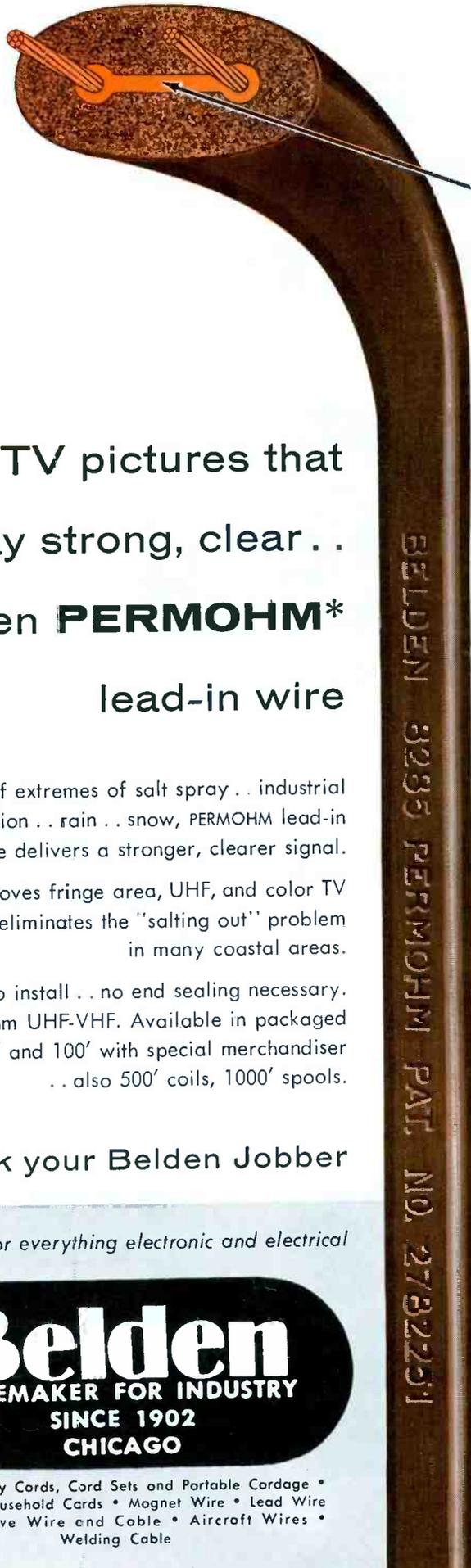

PERMOHM* means constant impedance . . . because its conductors are protected by encapsulation in cellular polyethylene.

for TV pictures that
stay strong, clear . .

NEW Belden PERMOHM* lead-in wire

In spite of extremes of salt spray . . industrial contamination . . rain . . snow, PERMOHM lead-in wire delivers a stronger, clearer signal.

PERMOHM improves fringe area, UHF, and color TV reception, and eliminates the "salting out" problem in many coastal areas.

PERMOHM is easy to install . . no end sealing necessary.
300 Ohm UHF-VHF. Available in packaged lengths of 50', 75' and 100' with special merchandiser . . also 500' coils, 1000' spools.

ask your Belden Jobber

one wire source for everything electronic and electrical



Power Supply Cards, Cord Sets and Portable Cordage •
Electrical Household Cards • Magnet Wire • Lead Wire
• Automotive Wire and Cable • Aircraft Wires •
Welding Cable

BELDEN 3235 PERMOHM PAT. NO. 2782251


*Belden Trademark and
Belden Patent . . U. S.
Patent No. 2782251

8-1-9

making use of the **FIELD STRENGTH METER**



High-gain tuners and increased station power have not obsoleted the field-strength meter as a valuable test instrument. On the contrary, it is more valuable than ever as a servicing aid and business-builder.

In slack work periods, a brief field-strength survey can be included on each home service call at no charge to the customer. The results can be used quite successfully to promote antenna sales or maintenance jobs. When suggesting antenna work, stress the importance of preventive maintenance in assuring your customers of uninterrupted service from their antenna systems. Even though these field-strength surveys may not immediately result in contracts for antenna service, they help to establish good will for you—thereby providing just the "push" required to get antenna jobs at a later date.


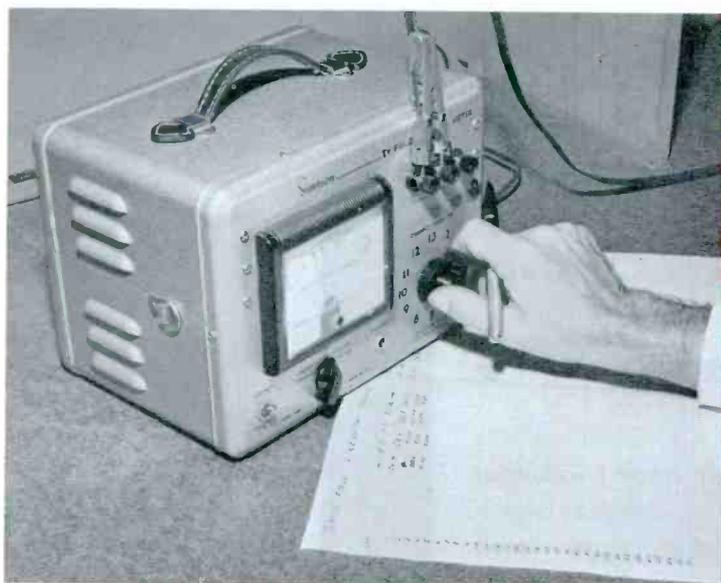


A daily reading and recording of signals at the shop will provide a reference against which other readings taken during the day can be compared.

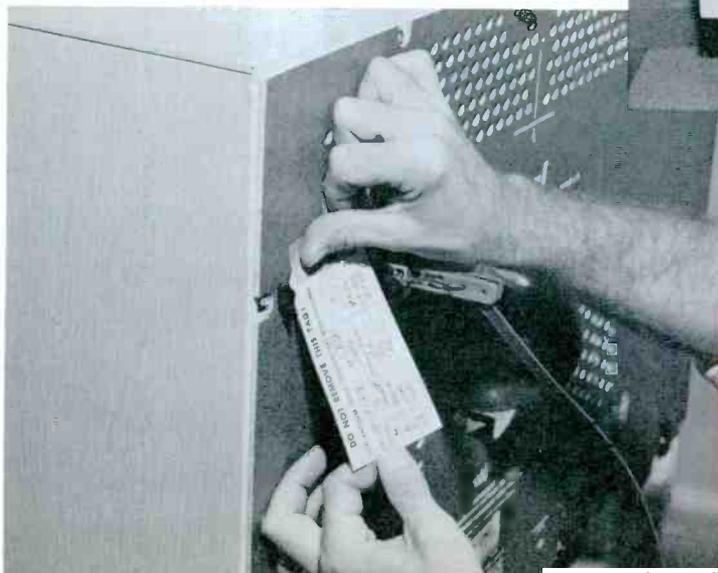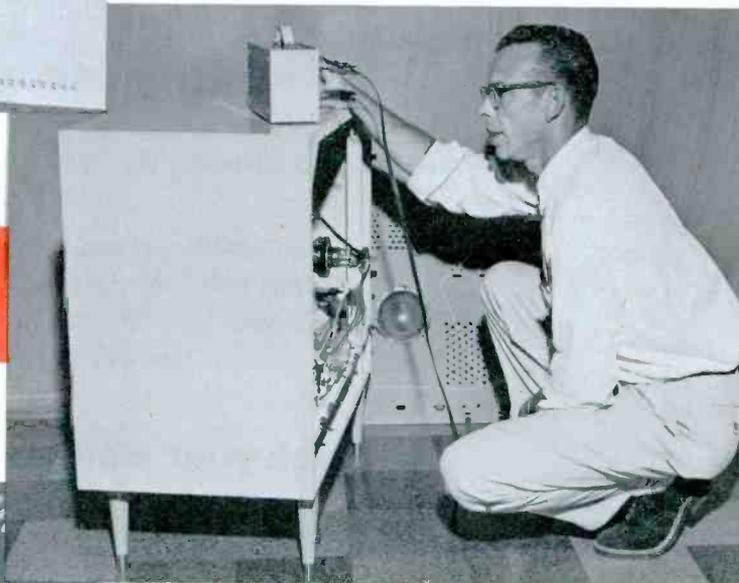At the customer's home, a field-strength meter can be used to check the ability of the antenna system to deliver a consistent signal of acceptable strength.




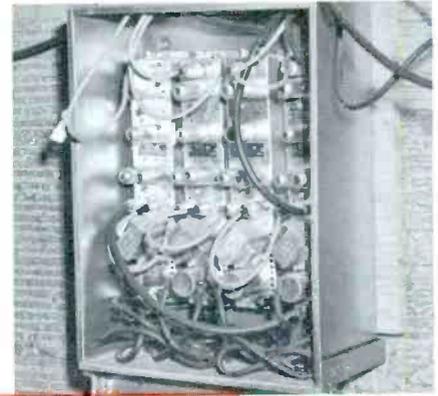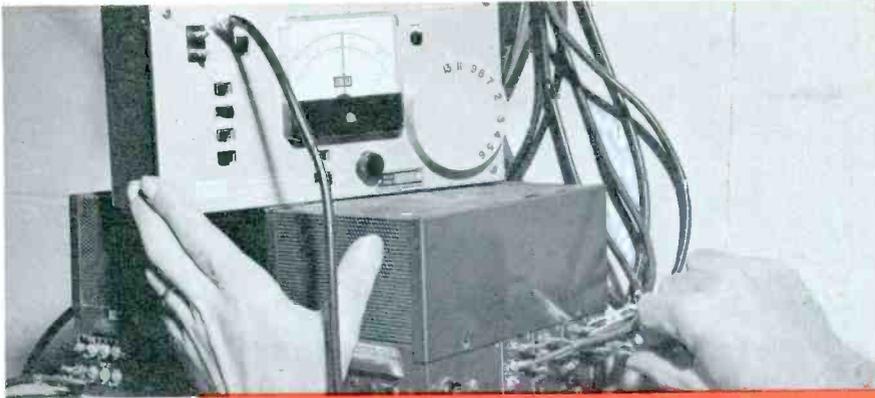A receiver tag containing the date, channel, signal level, shop reference reading, reception quality, and technician's initials proves very useful in isolating troubles on subsequent calls. If reception is poor, and a new reading shows serious loss of signal, you'll have definite proof that the installation requires replacement or repair.



When it has been definitely proved that the antenna system is at fault, the field-strength meter makes it easy to pinpoint the cause. Multiple antenna receptacles and master antenna systems are used extensively today—not only in hotels, motels, and apartments, but in homes as well. Point-to-point signal tracing is easily accomplished by use of the meter.

TYPE OF LINE	ATTEN. (db per 100 feet)	
	CHANNEL 2	CHANNEL 13
Open-wire (350 ohms)	0.13	0.25
Coaxial, air insulated	0.7	1.4
RG-8/U (53 ohms)	1.4	2.6
RG-58/U (53 ohms)	2.7	5.1
RG-11/U (75 ohms)	1.3	2.4
RG-59/U (75 ohms)	2.5	4.6
Twin-lead (300 ohms)	1.3	2.8
Twin-lead (150 ohms)	1.6	3.5
Twin-lead (75 ohms)	3.0	6.8

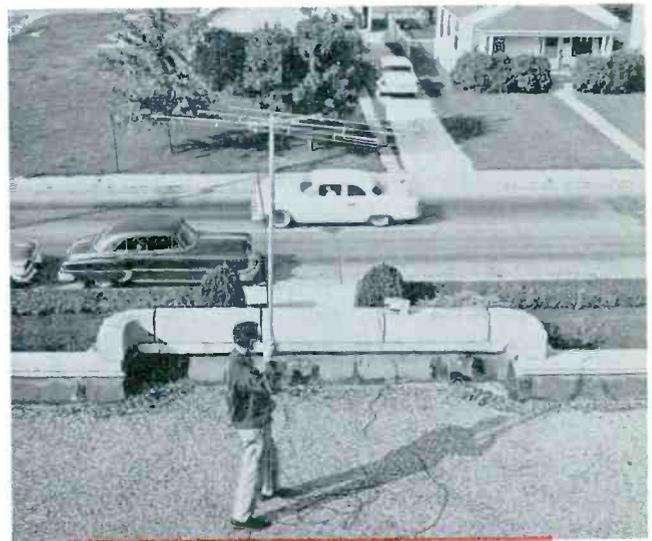

Another consideration important to the evaluation of signal readings is the natural line loss between antenna and receiver. This chart shows the line losses to expect under ideal conditions. Humidity, age, and other factors will result in increased losses. Becoming familiar with typical line losses will save you from looking for troubles that don't exist.

For determining antenna location and orientation, a field-strength meter is a great time-saver, eliminating the need for a communications setup between the receiver and the roof. In fact, one man can handle the entire job in many cases.



BLONDER-TONGUE
MODEL FSM-1—direct-reading
 Power Supply—battery-operated
 Frequency Range—54-216 mc continuous
 Range—10 uv to 3V
 Input impedance—75 ohms (300- to 75-ohm matching network supplied)
 Accuracy—±1 db full scale using 100-uv input
 Output jacks for video or sound
 Size and Weight—8½" x 12" x 9¼", 14 lbs. less batteries.



JERROLD
MODEL TMT—direct-reading
 Power Supply—Battery-operated—four 1.5V cells
 Frequency Range—Channels 2 through 6, 7 through 13 continuously
 Range—100 uv to 2V
 Input impedance—75 or 300 ohms
 Accuracy—±3 db
 Output jacks—none
 Size and Weight—10¼" x 5½" x 4½", 4½ lbs. less batteries



SIMPSON
Model 498A—direct-reading
 Power supply—117V, 60 cps or 6V rechargeable battery
 Frequency range—channels 2 through 83.
 Range—10 to 50,000 uv
 Input impedance—300 ohms
 Accuracy—±6 db VHF, ±3 db UHF
 Output jacks for 40-mc IF and audio modulation
 Size and Weight—11¾" x 7¾" x 9½", 14¾ lbs. less battery



A STREAMLINED

"SYNCHROGUIDE"

by THOMAS A. LESH

RCA has made some interesting changes in its time-honored *Synchroguide* horizontal oscillator circuit. Although the basic layout still consists of a triode-type AFC tube and a blocking oscillator, a number of important details have been altered enough to have a marked effect on troubleshooting. Oscillator waveforms and voltages are noticeably different from those in older *Synchroguide*-equipped sets, and horizontal-sweep alignment is simpler.

The revised circuit (Fig. 1) is found in the RCA Chassis KCS122 and all higher-numbered series, as well as last year's KCS116 and -117. Note that the transformer is now located in the grid-cathode circuit of

the oscillator stage. In addition, the hold control has been moved from the plate of the AFC stage to the oscillator grid circuit, and a fixed-tuned horizontal-frequency coil is employed. (The latter two features are not brand-new, but were gradually adopted during the last few years as early steps in the evolution of the present circuit.)

Fig. 2 is a view of the area around the 6CG7 horizontal AFC-oscillator tube of the 17" *Sportable* receiver (Chassis KCS126), showing how the new circuitry fits into the compact printed-wiring arrangement of the latest models. The sweep-circuit printed board in this portable is identical to the one employed in 21"

models for 1960, but is mounted in a different position. It has several interesting physical features, including built-in test jacks in the tube sockets and a "road map" (white markings) to indicate the path of conductor strips on the opposite side of the board.

To make up for the absence of a horizontal-frequency slug, an unusually sensitive horizontal-hold adjustment is provided. The control (Fig. 3) is electrically a conventional 40K-ohm potentiometer, but it is equipped with a type of planetary drive which gives a vernier-tuning effect. The inner end of the control shaft, tapered into a slender pin, is surrounded by three ball bearings which are turned by the shaft when it rotates. Riding on the outer surfaces of the bearings is a plastic carriage attached to the potentiometer slider. Approximately 10 turns of the shaft are required to move the slider through its entire range; thus, hold-control rotation produces a very gradual resistance change. The picture remains in sync over only a small portion of the control's total range—usually less than one complete turn of the knob. Therefore, from the set user's point of view, the hold control appears to behave about the same as the one on his previous set.

Signal Waveforms

Let's turn on the scope and have a look at the signals in the horizontal circuit of the *Sportable*. We'll use a low-capacitance probe for this job, since some portions of the *Synchroguide* circuit would be severely loaded by a direct probe. The peak-to-

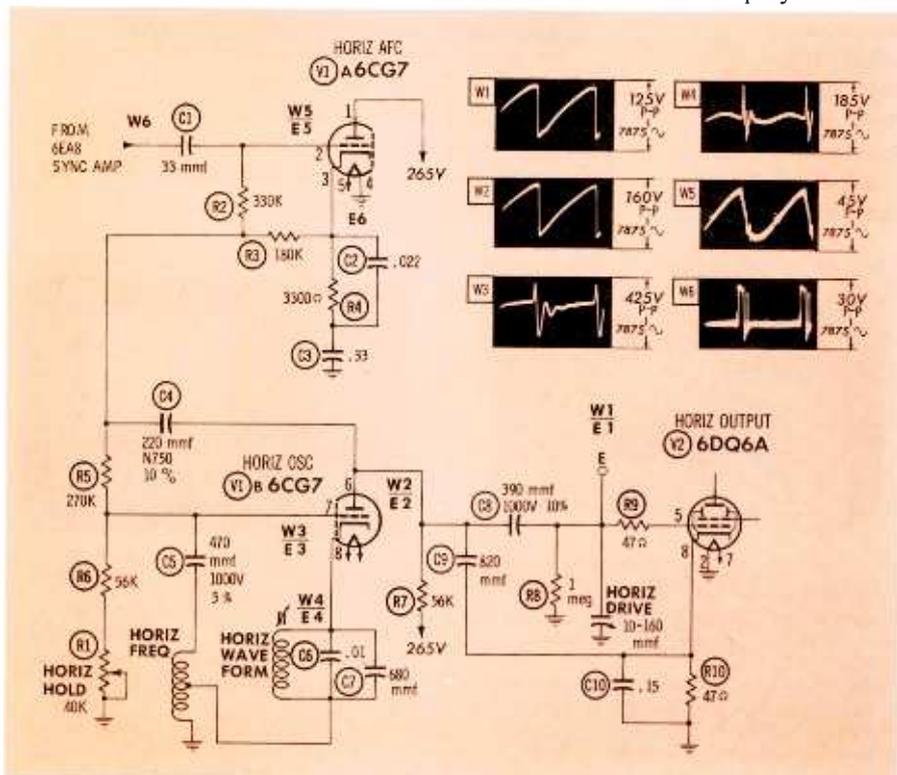


Fig. 1. Horizontal sweep circuits of the RCA Sportable (Chassis KCS126).

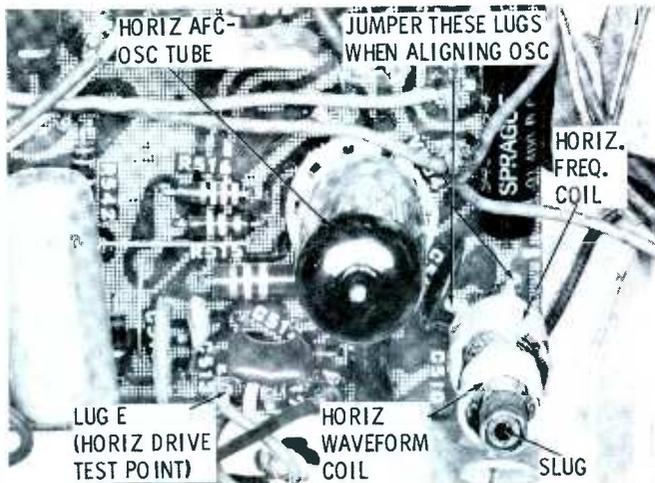


Fig. 2. Horizontal oscillator transformer is mounted on one corner of printed-wiring board next to 6CG7 tube.

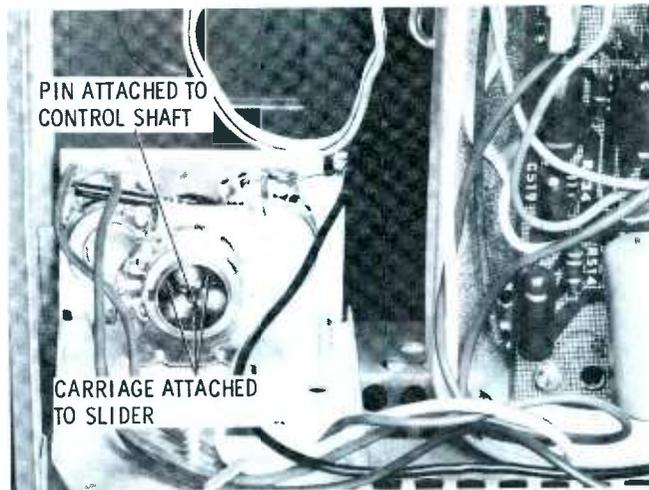


Fig. 3. Ball bearings serve to "gear down" horizontal hold control in order to permit more precise adjustment.

peak voltage readings obtained in our tests will be multiplied by the probe's attenuation factor to arrive at the true amplitude figures mentioned in this article; don't forget to do the same thing when using your own scope probe.

Let's begin by finding out what sort of output signal the modernized circuit produces. In an older-model set, we'd automatically touch the scope probe directly to the grid pin of the horizontal output tube in order to examine the drive signal. This approach doesn't work so well in the RCA KCS126, since the output-tube socket is a bit awkward to reach; so let's check the service data to see if we can find an easier way. How about the other side of the series grid resistor R9? As you can see in Fig. 2, this point in the circuit is right out in the open—at lug E near the bottom edge of the printed board. The green wire fastened to this lug will quickly steer you to it. Scoping this point, we find a conventional drive signal of modified sawtooth shape (W1 in Fig. 1). It has a lusty peak-to-peak amplitude (about 125 volts) for driving a 110° sweep system.

Moving back to the 6CG7 AFC-oscillator tube, we can easily obtain waveforms at the test point on the

tube socket. The oscillator plate waveform W2 (at pin 6) is a nearly pure sawtooth with a somewhat higher amplitude than W1. Do you wonder where the sine wave went? The sinusoidal hump which was a familiar feature of the standard *Synchroguide* plate waveform (Fig. 4) has disappeared, because the plate circuit no longer includes the oscillator transformer with its associated sine-wave coil. The shape of W2 is due almost entirely to the repeated charging and discharging of sawtooth-forming capacitor C9.

Oscillator grid waveform W3 (at pin 7) hasn't changed much as a result of the circuit revision. A moderate rise in grid voltage takes place during trace time (just as in all blocking oscillators); but, as Fig. 5 demonstrates, the resulting upward slope of the waveform is very difficult to see because it is dwarfed by the 425-volt pulses which occur during horizontal retrace.

When we check cathode waveform W4 at pin 8 (see Fig. 6), at last we find the sine-wave component which was missing from W2. (It appears in W4 because the cathode is returned to ground through the oscillator transformer.) This sine wave looks pretty puny in comparison with the 185-volt retrace pulses,

doesn't it? Since the regular "adjust for equal peaks" procedure is obviously impossible with W4, this waveform won't be of much help during alignment of the horizontal section. Nevertheless, it's useful as a trouble indicator; if the circuit cannot be satisfactorily aligned by the recommended method, you can try checking the shape of W4 to see if the waveform adjustment is correct. To interpret W4 properly, remember that its sinusoidal component is 180° out of phase with that of the plate waveform in the standard *Synchroguide* circuit. The new-style sine wave has just passed its positive peak, and is negative-going at the instant the oscillator reaches the end of the trace period. Since the cathode voltage is rapidly becoming less positive at the same time the grid voltage is becoming less negative, the bias quickly decreases to the critical point at which the oscillator tube can conduct and initiate retrace. If the cathode voltage does not "run down toward the grid voltage" in this manner, it furnishes less precise control over the exact time when tube conduction begins—and the oscillator is less stable.

You may recall that the sine-plus-sawtooth plate waveform in the old-

• Please turn to page 89

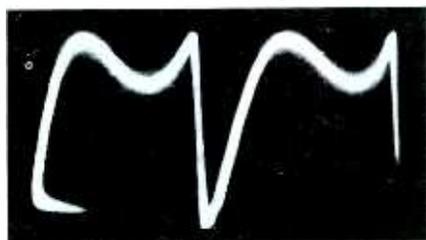


Fig. 4. "Adjust for equal peaks" plate waveform of older-type *Synchroguide*.

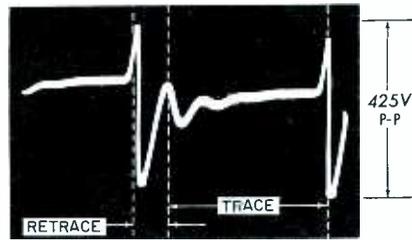


Fig. 5. Oscillator grid waveform actual-ly has upward slope during trace time.

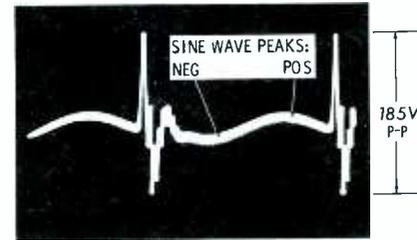


Fig. 6. Sine wave in cathode signal is of much lower amplitude than pulses.

Chart 2—Specifications for Various Brands of PA Amplifiers

MFR.	MODEL NO.	INPUTS		OUTPUTS				POWER OUTPUT	FREQUENCY RESPONSE	Facilities for Mobile Operation
		4	3	Impedances		Voltages	70			
				8	16					
Altec-Lansing	342B	4		8	16		70	35 at less than 5%	±1 db, 20-20,000	
	346A	3		8	16		70	20 at less than 2%	±2 db, 20-22,000	
Bell-Sound	5630	5		8	16		70	30 at less than 5%	±2 db, 30-20,000	operates on 6 or 12VDC, 117VAC
	5615	4		8	16	500	70	15 at less than 3%	+2 db, 30-20,000	
	5625-M3 ¹	4		8	16	500	70	25 at less than 3%	±2 db, 30-20,000	
	PM-33	3		8	16	500	70	33	±2 db, 30-15,000	
	PM-20	2		8	16		70	20	±2 db, 30-15,000	
	PM-212M3 ¹	2		8	16		70	20	±2 db, 30-15,000	
	PM-10	2		8	16		70	10	±2 db, 30-15,000	
Bogen-Presto	MX30	4		8	16		70	30 at less than 1%	±2 db, 35-20,000	operates on 12VDC, 117VAC
	MX60	4		8	16		70	60 at less than 1%	±2 db, 35-20,000	
	M330	3		8	16	25	70	30 at less than 1%	±2 db, 35-20,000	
	M60	3		8	16	25	70	60 at less than 1%	±2 db, 35-20,000	
Fanon	3310	2		8	16		70	10	30-20,000	operates on 6 or 12VDC
	3320	3		0	16		70	20	20-20,000	
	3340	3		8	16		70	40	20-20,000	
	3370	4		8	16		70	70	20-20,000	
	3525	2		8	16		70	25	30-15,000	
		6		8	16	250	70	25	±1 db, 20-20,000	
Newcomb	KX-25	6		8	16	500	70	25 at less than 3%	±1 db, 20-20,000	operates on 6VDC, 117VAC
	KX-50	6		8	16	500	70	50 at less than 3%	±1 db, 20-20,000	
	H-15	3		8	16	500	70	17 at less than 5%	±2 db, 20-20,000	
	H-25	4		8	16	500	70	25 at less than 5%	±2 db, 20-20,000	
	H-50	5		8	16	500	70	50 at less than 5%	±2 db, 20-20,000	
	E-25MP3 ¹	3		8	16	500	70	25 at less than 5%	±2 db, 20-20,000	
	10PA	2		8	16	500	70	10	±2 db, 70-10,000	
	20PA	2		8	16	500	70	20	±2 db, 30-15,000	
	30PA	3		8	16	250	70	30	±2 db, 30-15,000	
	30MPA	3		8	16	250	70	30	±2 db, 30-15,000	
Precision Electronics (Grommes)	60PA	3		8	16	250	70	60	±1 db, 30-15,000	operates on 6 or 12VDC, 117VAC
	G20	3		8	16	250	70	20 at less than 5%	±2 db, 50-10,000	
	G40	4		8	16	500	70	30 at less than 5%	±2 db, 50-10,000	
	G75	6		8	16	250	70	50 at less than 5%	±1 db, 50-10,000	
	1916	3		8	16	250	70	16 at less than 5%	±1 db, 40-20,000	
	1925 ¹	3		8	16	250	70	25 at less than 5%	±1 db, 30-15,000	
Rauland-Borg	1932	5		8	16	250	70	32 at less than 5%	±1 db, 40-20,000	operates from 6 or 12VDC, 117VAC
	1960	6		8	16	250	70	60 at less than 5%	±1 db, 40-15,000	
	TP10	3		8	16	500	70	10 at less than 5%	±1.3 db, 40-15,000	
	TP15	3		8	16	500	70	15 at less than 5%	+1.3 db, 40-15,000	
Webster Electric	TP25	4		8	16	125	70	25 at less than 5%	±1.5 db, 40-15,000	plugs into cigarette lighter receptacle for 12V operation plugs into cigarette lighter receptacle for 12V operation
	TP50	4		8	16	250	70	50 at less than 5%	±1.5 db, 30-15,000	
	TP90	5		8	16	250	70	90 at less than 2.5%	within 1.3 db, 35-20,000	
	TP20M	2		8	16	250	70	22.5	within 1.5 db, 30-10,000	
	TP20MP ¹	2		8	16	250	70	22.5	within 1.5 db, 30-10,000	
		2		8	16	250	70	22.5	within 1.5 db, 30-10,000	

¹ includes top-mounted, 3-speed phono

² 7 ranges from 6 to 392 ohms

³ 7 ranges from 4.5 to 343 ohms

CHOOSING PA AMPLIFIERS

In spite of the fact that the choice of a PA amplifier for any given installation is not difficult, several questions must be answered before any unit is decided upon. For example: How much area is to be covered? What is the ambient noise level? How many outlets are required? How many, and what kind of inputs are needed? Will use of the system be expanded or modified at a later date?

This article tells how the answers to these questions affect the selection of an amplifier.

Power Requirements

A number of methods can be used to determine the minimum power rating of the amplifier. The easiest and quickest way is to consult a chart where power requirements are cross-referenced with the area to be covered (see Chart I). If we consider, for example, that an auditorium is 30' wide and 100' long (3,000 sq. ft.), we can see that a 15-watt rating will suffice if the ambient noise level is average, but the amplifier would have to be continuously operated at maximum power. A 20-watt rating would provide a cushion, but a 25 or 30-watt unit would be more practical.

Type and Number of Inputs

Since one of the major functions of any PA system is voice distribution, microphone inputs will be required. For our 30' by 100' hall, three mike inputs is the minimum recommendation. This would allow one mike for each 10' of building width; any fewer would be inadequate for large panel discussions or civic events. Microphone inputs with facilities for accepting plug-in matching transformers (as shown in Fig. 1) will permit the use of any mike, regardless of impedance. You simply choose a plug-in transformer

that provides the proper match between microphone and amplifier input. If only one or two mikes are to be used at the outset, the amplifier need be equipped with only the matching transformers for those specific mikes. Whenever additional mikes are purchased, the needed transformers can also be obtained.

Each input circuit should have a gain control as shown in Fig. 1 so that the outputs can be balanced. In some units, the final output can be adjusted with a MASTER GAIN control. (Note: Not all PA amplifiers have such a control; some depend solely on the individual gain controls to regulate output, as well as the balance between the various inputs.)

In the event sound pickup points are not located more than a short distance (8' to 10') from the amplifier, high-impedance microphones can be used, thus eliminating the need for matching transformers. Further, if there is no foreseeable need for low-impedance inputs (for mikes located some distance away

from the amplifier), the amplifier chosen need not have plug-in transformer facilities.

Type and Number of Outputs

Basically, there are two types of

Chart I—Amplifier Power Required to Supply a Given Area.

AREA IN SQUARE FEET	AMPLIFIER RATING IN WATTS
50,000	100
40,000	100
15,000	30 to 50
10,000	30 to 50
8,000	30 to 50
5,000	30
4,000	15 to 30
3,000	15
2,000	15
1,000	10 to 15
500	10

NOTES: 1. Extremely noisy areas require a higher rating than shown.
2. Use lower wattage figure if noise level is below average.

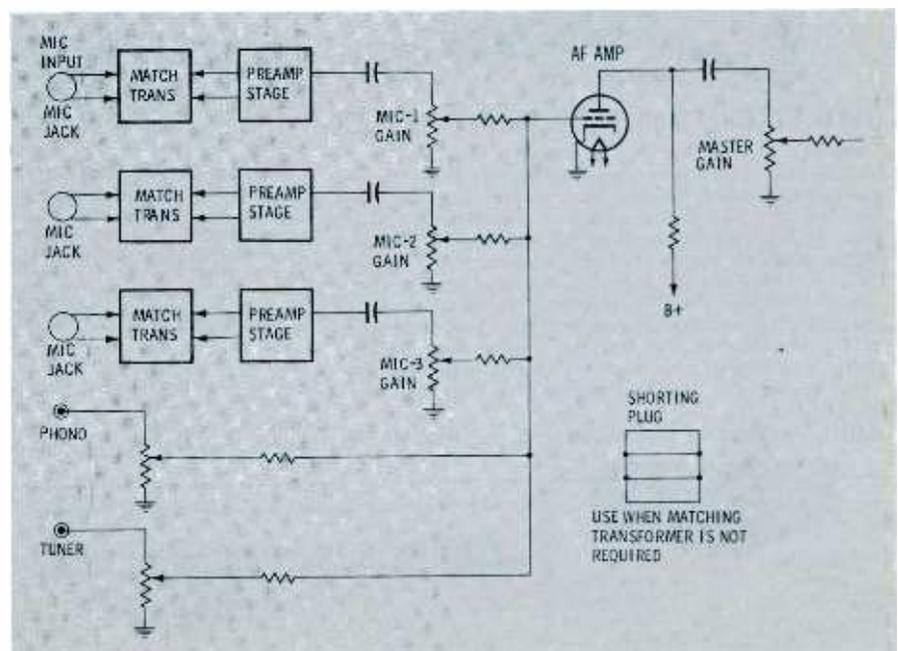


Fig. 1. Diagram of hook-up for multiple inputs and individual gain controls.

NEW FROM SECO DYNAMIC TRANSISTOR CHECKER



MODEL
100

DYNAMICALLY CHECKS WIDE RANGE OF TRANSISTOR TYPES EITHER "IN OR OUT" OF CIRCUIT!

This new low-cost checker uses an entirely new approach but a proven DYNAMIC principle for checking transistors, safely tests PNP and NPN transistors either "in or out" of the circuit. Covers wide range of types: small signal including "drift" types, medium power; and power types. Provides positive check for "opens," shorts, and gain—condition indicated by means of a visual indicator plus jacks for meter or scope. Also provides GO-NO-GO test at practical currents—and permits matching of similar transistor types. No set-up required—no further leakage tests necessary. Model 100 is compact, lightweight, complete, and ready-to-use . . . helps you cash-in on the big profits in the fast growing transistorized equipment servicing field!

MODEL 100—Wired and factory tested \$19.95 NET

NEW FROM SECO LOW COST, COMPLETE TUBE TESTER



MODEL 78

GRID CIRCUIT and TUBE MERIT TESTER

Complete test coverage of all modern TV tube types as well as all heater type radio tubes including hybrid types, using only 5 sockets. Incorporates patented Seco GRID CIRCUIT TEST plus a reliable CATHODE EMISSION test using new low impedance low test voltage circuit—also checks filament continuity and provides open element test. One easy-to-read meter indicates results for both Grid Circuit and Tube Merit Tests. Two-stage DC amplifier isolates meter from tube under test to protect meter—and makes it possible to achieve a wide range of load currents and test conditions. Complete with portable carrying case, pin straighteners, and flip-chart for quick set-up data.

MODEL 78—Wired and factory tested \$69.50 NET



MODEL 107
TUBE
TESTER

outstanding reliability, accuracy

Provides 3 important tests: amplifier types tested for gain by Dynamic Mutual Conductance method—power types tested for cathode current by Cathode Emission method—all types tested for shorts and grid error by Grid Circuit Test developed and patented by Seco. Dynamic Mutual Conductance Test pre-wired to eliminate elaborate set-up. Cathode Emission Test done by free point pin-selector method—will not be obsolete. Completely self-contained in portable carrying case.

MODEL 107—Wired and factory tested \$139.50 NET



MODEL HC-6
IN-CIRCUIT
CURRENT
CHECKER

positive, on-the-spot check of horizontal output current!

This new, low-cost current checker provides simple means for making a positive on-the-spot check of TV horizontal circuits. Can be placed into the circuit in seconds—no unsoldering of circuit wiring—immediately indicates whether horizontal tube cathode current is within manufacturer's recommended limits. Valuable as a fast, accurate indicating device when adjusting horizontal drive and linearity. Eliminates one of the most common causes of callbacks. Compact, inexpensive, easy to use.

MODEL HC-6—Wired and factory tested \$12.95 NET



MODEL GCT-8
GRID CIRCUIT
TESTER

fast check of critical "control grid" conditions

Model GCT-8 checks "control grid" condition of vacuum tubes faster, more accurately than any other tester! As many as eleven simultaneous checks—automatically! Quickly spots grid errors and leakage—stops guessing, substitution checking, and costly rechecks. Electron-Eye tube indicates faults at a glance. Truly portable. The perfect companion to any tester that employs only conventional gas and shorts test. Carry it on all calls.

MODEL GCT-8 Complete kit . . . \$19.95 NET

MODEL GCT-8 Wired and tested . \$29.95 NET

output circuits — constant impedance and constant voltage—but the number of output jacks may vary widely. Some amplifiers are equipped with several jacks so that a number of speakers, each equipped with the proper plug, may be connected directly into the amplifier. This is a valuable feature when the amplifier is to be used in a small system that employs only two or three speakers. It is also very useful in systems that require speaker cables to run in several directions.

If the proposed PA system requires adjustable output levels at one or more speaker locations, the amplifier chosen should have provisions for constant voltage output. This eliminates the power-consuming T and L pads which would otherwise be required.

When a tape recorder is to be included in a system, the PA amplifier should have some provision for supplying the recorder input with a suitable audio signal. Some amplifiers have an output jack for this purpose. If an otherwise acceptable amplifier does not have such a jack, one can be installed very easily. Simply mount a phone jack on the amplifier and run a shielded cable from it to the top of the volume or MASTER GAIN control as shown in Fig. 2. This places the input of the tape recorder in parallel with the volume control; however, the recorder input has a very high impedance and will not adversely affect amplifier operation.

Frequency Response and Distortion

Voice communication can be handled very nicely by an amplifier with frequency response limits of 200 to 3,000 cps. In fact, reducing amplifier response to this range is actually desirable for clarity in reproduction. Distortion is another

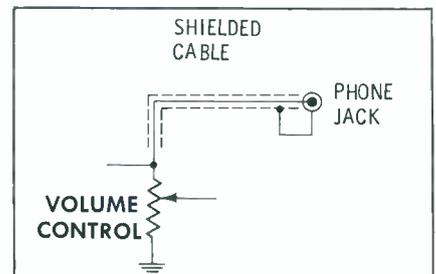


Fig. 2. Recorder jack connects to top of volume control via a shielded cable.

SEND FOR
COMPLETE SECO
STORY ON . . .

- Three Tube Testers
- VTVM
- Dynamic Transistor Checker
- In-Circuit Current Checker
- 100% Accurate Flyback Checker
- Battery Eliminator

Sold Only Thru Electronics Parts Distributors

OUTSTANDING RELIABILITY—TOP DOLLAR VALUE!



SECO MANUFACTURING CO.
5015 Penn Ave. So., Minneapolis, Minn.

NAME _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____

PLUS performance... PLUS value ...for a LIFETIME!

Jensen Hypex Horns and Lifetime Driver Units are way ahead in power rating . . . in efficiency . . . in dependability. They pack a terrific "punch" to penetrate high noise levels . . . to project sound over great distances. They are loaded with features that mean sturdiness, convenience and reliability. And you pay no more for all these PLUS values!

Jensen Hypex Horns and Lifetime Driver Units are standout members of the new Jensen Professional Series of loudspeakers especially designed for industrial commercial and institutional sound systems. Also included are Hypex Paging Projectors; Speech

Master speakers; High Fidelity Projector; 2-way coaxial and 3-way Triaxial* High Fidelity speakers; Extended Range speakers; Weather Master outdoor speakers; transformers, level controls and accessories.

*TM Reg.

We'd like to send you a copy of Catalog 1070. Send for copy today.

LIFETIME GUARANTEE

D-30; D-40 and DD-100 Lifetime Driver Units.

Every Lifetime Driver Unit is unconditionally guaranteed for life against failure when operated according to the instructions accompanying the unit.

Should any Lifetime Driver Unit become inoperative at anytime under these conditions, it will be repaired or replaced at our option entirely free from any service charge.

The instruction sheet supplements and is a part of the warranty under which the Lifetime Guarantee is extended.

JENSEN MANUFACTURING COMPANY

Jensen

DIVISION OF THE MUTER CO.

MANUFACTURING COMPANY

6601 South Laramie Avenue · Chicago 38, Illinois


In Canada: Renfrew Electric Co., Ltd., Toronto

In Mexico: Radios Y Television, S.A., Mexico D.F.

New and already famous!
Jensen RT-20

*Functional rectangular
horn of molded glass
reinforced polyester.*

BURTON BROWNE ADVERTISING

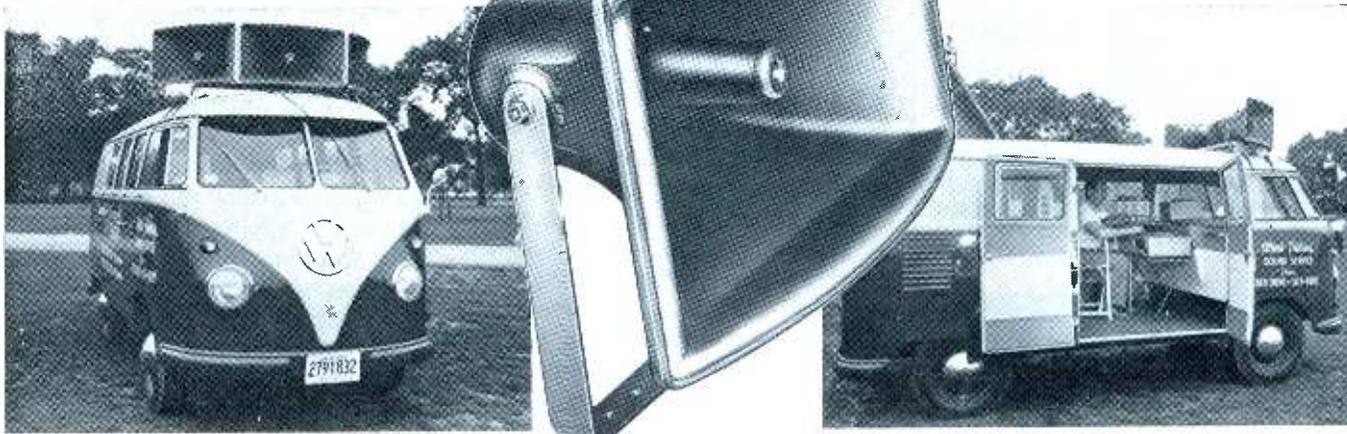

Jensen LIFETIME DRIVERS ARE GUARANTEED FOR A LIFETIME



D-30 New high rating for performance and dependability

30 WATTS



D-40 Higher efficiency and higher power rating


40 WATTS



DD-100 First Super Power Driver available

100 WATTS

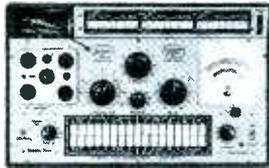NOW THERE ARE **3** JACKSON DYNAMIC® TUBE TESTERS




**DYNAMIC
OUTPUT
658**

Checks receiving tubes, voltage regulators, eye tubes. Shows heater continuity without warm-up. Reads heater current. Provides both shorts test and grid leakage test. Has 231 heater voltage combinations. An outstanding professional tube tester. **\$189.95**



**NEW
LOW
COST
DYNAMIC
598**

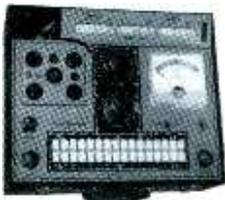Provides convenient lever switching and time-improved Jackson Dynamic test principle. Has variable plate voltage and load controls. Shorts test has variable sensitivity to 2 megohms. Convenient roll chart and grouped tube socket sub-assembly. **\$89.95**



**WORLD
FAMOUS
DYNAMIC
648R**

Features super-rapid sequence switching. The set-up time is less than the warm-up time of the tube. Twenty-three separate heater voltages. Line voltage control indicates actual line voltage. Famous for dependability the world over. **\$129.95**



POWER CHART ACCESSORY

Here's a new addition! The Jackson Power Roll Chart—available in all three tube testers for those who require the extra. Roll the chart from one end to the other in less than 25 seconds with the touch of a finger. **\$20.00 net**

SEE YOUR DISTRIBUTOR OR WRITE FOR LITERATURE.

Jackson
THE JACKSON
ELECTRICAL
INSTRUMENT
COMPANY
16-18 SOUTH PATTERSON BLVD.
DAYTON 2, OHIO
In Canada: The Canadian Marconi Company

matter. Even though this narrow band of frequencies is best for voice transmission, a small amount of hum or harmonic distortion can play havoc with understandability of speech.

An amplifier should have a minimum frequency response range of 50 to about 12,000 cps if it is to be used for music distribution. Response at frequencies above or below these limits is not required in PA work, since allied equipment normally used will limit the system to this range anyway. Again, distortion (either intermodulation or harmonic) must be kept low if best results are to be realized. Generally speaking, intermodulation and harmonic distortion should be less than 5% and 1%, respectively, at rated power output.

Normally, PA systems are used for both paging (voice transmission) and music distribution. The bass and treble controls can be adjusted to provide either the narrow response desired for voice work, or the wide response desired for music distribution. The controls should be set at minus-6 and minus-8 positions for voice amplification, or at plus-4 and minus-4 positions for music (see Fig. 3 for details).

Other Considerations

Naturally, all PA installations won't be in small auditoriums, nor will they all require multiple microphone inputs. The small office or business will probably need only one microphone input, and one other input for phono or tuner. Also, power requirements for small systems are fairly low. Generally, the PA amplifier that has single mike and phono inputs will have an output rating of 6 to 10 watts. Naturally, lower-powered units use single-ended power output stages, and often are rated at peak power rather than average power output. For permanent installations, a push-pull amplifier is desirable. Distortion levels in single-ended units are higher than is normally tolerable. The small low-power amplifier is most useful as a portable unit for occasional or emergency use.

A PA amplifier with only two inputs can serve systems that require microphone, phono and tuner inputs, provided the tuner used has a phono

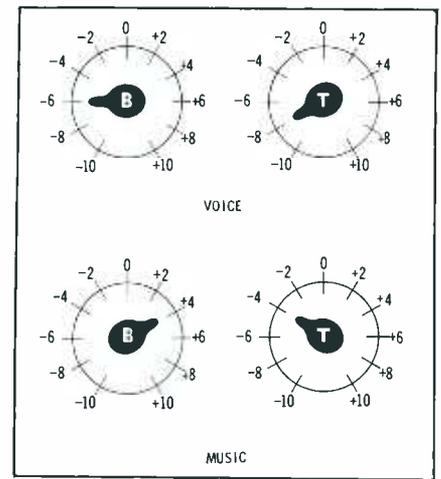


Fig. 3. Typical settings of tone controls for voice and music distribution.

input jack and facilities for selecting either phono or tuner operation. A system connected in this manner would appear as shown in the block diagram of Fig. 4. In fact, this system is the type most often employed in small offices or business places. Electrically, the amplifier mentioned above has controls for volume, bass and treble; high-impedance, high-gain mike inputs and additional inputs for phono or tuner; output impedances of 4, 8, 16, and 500 ohms; and a 10-watt push-pull output stage.

A final point to consider when choosing a PA amplifier is whether or not the unit will be used in mobile operation. Any amplifier that is to be powered from a low-voltage DC supply (6-, 12-, or 24-volt battery) should have either a built-in DC-to-AC converter, or else the necessary provisions for operation from an external converter. For most temporary mobile applications, a 10- to 20-watt amplifier will suffice. Frequency-response characteristics, number and type of input and output circuits, and other requirements will be generally similar to those of a fixed PA system of compact size. ▲

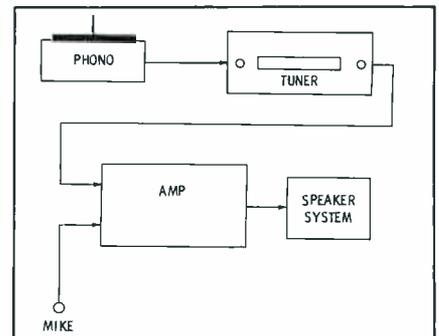


Fig. 4. How a phono, tuner, and mike can be used with dual-input amplifier.



SARKES TARZIAN

TUBE REPLACEMENT BULLETIN

WHERE RELIABILITY IS IMPORTANT Replace Rectifier Tubes with Tarzian Direct Replacement Silicon Rectifiers



S-5011A
1600 PIV
750 MA DC

Replacement for types 80, 82, 83, 83V, 5Z3
Max. RMS Voltage .1100 | Circuit F.W.
Max. Peak Current | Type Load Any
(ma)8000 | Max. Amb. Temp.. 100°C



S-5017
1600 PIV
750 MA DC

Replacement for types OZ4, 5X4, 5Y4, 6AX5, 6X5
Max. RMS Voltage .1100 | Circuit F.W.
Max. Peak Current | Type Load Any
(ma)8000 | Max. Amb. Temp.. 100°C



S-5018
1600 PIV
750 MA DC

Replacement for types 5AU4, 5AW4, 5AZ4, 5T4, 5U4,
5Y4, 5W4, 5Y3, 5Z4, 5931, 6087, 6106
Max. RMS Voltage .1100 | Circuit F.W.
Max. Peak Current | Type Load Any
(ma)8000 | Max. Amb. Temp.. 100°C



S-5019 or S-5162
2800 PIV
500 MA DC

Replacement for type 5R4
Max. RMS Voltage .1950 | Circuit F.W.
Max. Peak Current | Type Load Any
(ma)5000 | Max. Amb. Temp.. 100°C



S-5033
4500 PIV
250 MA DC

Replacement for types 6AU4, 6AX4, 6BL4, 6U4, 6W4,
12AX4, 17AX4, 25W4
Max. RMS Voltage *3200 | Type Load Res.-Ind.
Max. Peak Current | Max. Amb. Temp.. 100°C
(ma)2500 | * Input is 1600V Max.
Circuit H.W. | with Cap. load



S-5130
10400 PIV
300 MA DC

Replacement for types 866, 866A, 3B28
Max. RMS Voltage .7400 | Max. Amb. Temp.. 100°C
Max. Peak Current | For capacitive loads de-
(ma)3000 | rate input voltage 50%
Circuit H.W. | and current 20%
Type Load Res.-Ind.



S-5207
1600 PIV
500 MA DC

Replacement for types 6X4, 6063, 6202
Max. RMS Voltage .1100 | Circuit F.W.
Max. Peak Current | Type Load Any
(ma)5000 | Max. Amb. Temp.. 100°C



S-5251
1600 PIV
600 MA DC

Replacement for types 5AU4, 5AW4, 5AZ4, 5T4, 5U4,
5Y4, 5W4, 5Y3, 5Z4
Max. RMS Voltage .1100 | Circuit F.W.
Max. Peak Current | Type Load Any
(ma)6000 | Max. Amb. Temp.. 100°C



S-5343
7000 PIV
300 MA DC

Replacement for types 816, 836 or 3B28 and 866 at
reduced voltage
Max. RMS Voltage .5000 | Max. Amb. Temp.. 100°C
Max. Peak Current | Note: For capacitive
(ma)3000 | loads derate input volt-
Circuit H.W. | age 50% and current
Duty Continuous | 20%
Type Load Res.-Ind


Over 95% of all popular rectifier tube
types **can** be replaced with **Tarzian tube**
replacement silicon rectifiers.

SARKES TARZIAN INC. • RECTIFIER DIVISION

415 north college • bloomington, indiana • edison 2-1435

In Canada: 700 Weston Rd., Toronto 9. Tel. Roger 2-7535 • Export: Ad Auriema, Inc., New York City

Cornell-Dubilier Rotors

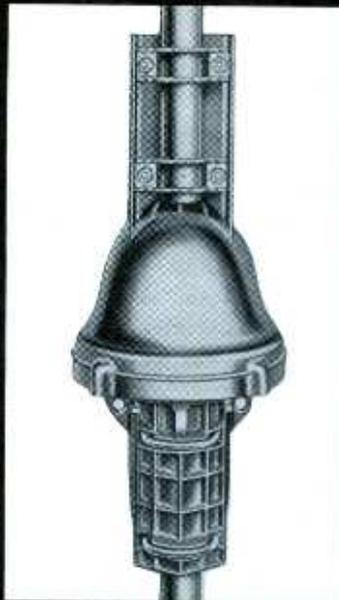


turn profits
your way

Whether you are after original installation business or replacement sales, you'll find the rotor best-suited for any job in the complete CDR line. Consider the heavy-duty TR-4 recommended for areas where ice-storms, heavy snowfalls and strong winds impair the efficiency of antennas turned by ordinary rotors. Your CD Rotor distributor is ready to show you why the TR-4 and other CD Rotor are the easiest to install...most satisfactory in the long run. Write for catalog TVR to Cornell-Dubilier Electric Corp., S. Plainfield, N. J.



**50 YEARS
OF
PROGRESS**

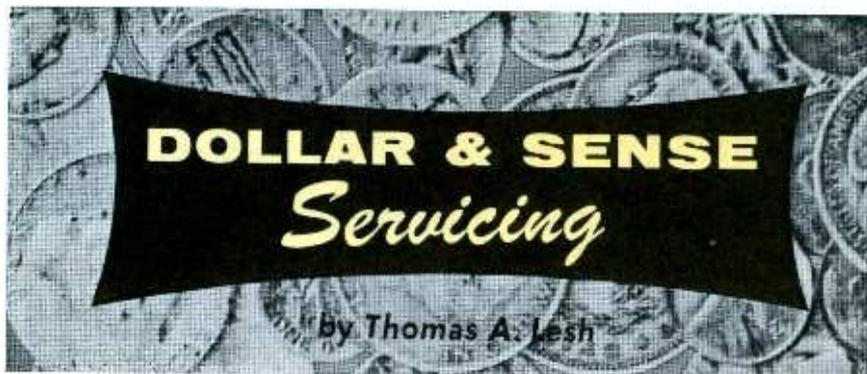

DOLLAR & SENSE *Servicing*

by Thomas A. Lesh

Santa's Helper. Christmas shoppers, always short on gift ideas, welcome suggestions for unusual and practical items to please their relatives and friends. As the holiday season gets into full swing, there is a tendency for people to buy almost anything (within reason) which strikes their eye.

All too many owners of "strictly service" shops pass up the chance to share in the business boom during this most generous spending season of the year. Perhaps it's because they don't realize what an excellent gift their stock in trade—service — can be. Taking a cue from the department stores, why not offer a Christmas gift certificate? It could be for a stated value to apply against the cost of service work as needed. One of the most appealing ideas along this line would be a "new picture tube for Christmas" theme.

Fulfilling these gift promises, by the way, would help keep business lively during the after-holiday period.

Some "gifts of service" can be performed beforehand and unveiled to the lucky one on Christmas morn. For example, a serviceman could install a personal, earpiece-type speaker for a hard-of-hearing or late-viewing member of the family, hiding it behind the set until the time arrives for it to be revealed. Or an old, neglected second set could be sneaked out of its dark corner during December, and restored to top condition—"for your own room, dear" — by Christmas-time.

If your shop now sells radios, TV sets, hi-fi and accessories, you are already loaded with gift opportunities. If your store window is not yet decorated with an appealing holiday display, your trucks aren't carrying bright signs offering gift suggestions, and your ads haven't adopted a holiday theme—it's time to "get with it!"

For the service specialist as well as the store owner, there are still more ways to spread the news about holiday gift ideas. For instance, the

serviceman on each home call can casually mention "service specials" being offered. The service bill itself can even carry a printed note: "Ask about our 'new picture tube for Christmas' gift plan," "Come in and see the latest portable stereo sets," or simply, "Smith's — Christmas gift headquarters."



Switcheroo. Want to attract attention to an outdoor or window sign while having it painted? Try the whimsical idea put to use on a new billboard by a local firm. When the first coat of paint was applied, one letter — the "R" in the word *fresh* — was painted in backwards. It was left this way for a few days, and then the painters came back and corrected the "R" — but this time reversed the "E" instead. After several more days during which the sign received hundreds of puzzled "double-takes" from passers-by, the painters finally straightened out the sign for good.

This type of crazy mixed-up sign should be professionally painted; if it looks homemade, prospective customers may miss the point and decide that you really don't know any better.



Skin Deep. Some TV dealers encourage their service technicians to insert the opening wedge for new set sales whenever the opportunity occurs. This often works out well, since the customer who asks a technician about TV sets expects to get an impartial, well-informed opinion instead of a sales talk.

Let's imagine that we're looking in on a serviceman in this situation. The customer has just asked in an offhand way, "What kind of set do you think is the best?" Our hero replies shrewdly, "Well, I've always liked a "Zapperino" because they give less trouble than any other brand I've worked on." (This just happens to be one of the major

GET *more!* DO *more!* MAKE *more!*

PROFIT PROFESSIONALLY ON EVERY CALL WITH

NEW **B&K**

**LOW-COST PROFESSIONAL
Model 550 DYNA-QUIK
DYNAMIC MUTUAL CONDUCTANCE TUBE TESTER**



Model 550

NET **\$119⁹⁵**

Every service-technician now can easily check tubes the B&K professional way! Only with a *genuine dynamic mutual conductance tube tester* can you make a complete and accurate test under the actual dynamic operating conditions of the TV set. The compact new "550" is not just an emission checker. *It completely checks more tubes faster—with laboratory accuracy.* And the cost is so amazingly low, it pays its way over and over again! Take a tip from thousands of professional servicemen—*use B&K Dyna-Quik.* There is nothing like it.



Get More for Your Money

—IN SPEED, ACCURACY, AND VALUE



Save Customers

—SAVE CALL-BACKS, SAVE COST



Sell More Tubes

—MAKE MORE MONEY PER CALL

MODEL 550 DYNA-QUIK TUBE TESTER

Tests Each Section of Dual-Section Tubes Separately

Great new value in professional quick-check at small cost. Provides **more tube sockets to test more tubes faster.** Accurately checks most of the TV and radio tubes usually encountered in everyday service work. Tests each section of dual-section tubes separately. **Measures true dynamic mutual conductance.** Checks tubes for shorts, grid emission, gas content, and leakage. Completely tests each tube in seconds, checks average TV set in a few minutes, in home or shop. One switch tests everything. Fast, convenient reference listings on socket panel. Patented circuit provides automatic line voltage compensation. 7-pin and 9-pin straighteners on panel. Handsome, luggage-type carrying case. Net, **\$119⁹⁵**

MODEL 650 DELUXE DYNA-QUIK

Today's Finest Portable Tube and Transistor Tester

Accurately checks over 99% of the tubes most widely used in television receivers, plus popular home and portable radio tubes. Tests over 600 tube types. Lists over 125 most popular tube types, with settings, on socket panels for maximum operating speed. Complete listing in fast, index-type selector. **Measures true dynamic mutual conductance.** Tests each section of multiple tubes separately for GM, Shorts, Grid Emission, Gas Content and Life. Includes 16 spare sockets and ample filament voltages for future new tube types. **Transistor Section** checks transistors, diodes, and selenium rectifiers. Luggage-type carrying case. Net, **\$169⁹⁵**



Model 650

B&K

B & K MANUFACTURING CO.
1801 W. BELLE PLAINE AVE • CHICAGO 13, ILL.

Canada: Atlas Radio Corp., 50 Wingold, Toronto 10, Ont.
Export: Empire Exporters, 277 Broadway, New York 7, U.S.A.

See Your Distributor or Send Now for Bulletin ST24-R

brands sold by his shop!) He goes on to brag a bit about the transformer-powered chassis in the latest "Zapperino" consoles.

Then, the customer, perking up at the thought of such a fine set, inquires, "Do they have any models that would look nice in this room?" Oh-oh! If the customer pursues this line of questioning, he'll have our technician friend out on a limb in no time. The poor guy is like most of us; he seldom pays any conscious attention to the outside of a TV receiver except when he's trying to get the cabinet out of the way of the

chassis. And here stands the customer, all set to drown him in a sea of questions such as, "Is there a '990' chassis in that neat lowboy with the wrought-iron legs that I saw in a magazine? Can I get it in blond wood? Would the top of it line up with my bookcase? And say, does their new glass fiber cabinet on the portable set resist cigarette burns?"

We don't recommend that all TV technicians take a course in interior decorating — but those who are seriously interested in promoting set sales would be smart to know plenty

about "appearance" features. The easiest solution is to be well-armed with illustrated brochures that will tell the prospective customer whatever he wants to know about styling features.



Big Brother. You don't have to be a Boy Scout leader to work with young people in your community. As an electronics expert, you have something special to contribute. You're right in the midst of a field which fascinates many youngsters, and you could do them a good turn by helping them pursue electronics as a hobby. Perhaps you could spend some spare time "coaching" them on construction projects; or, if you have the patience to answer a flood of questions, you could let them know they're welcome to drop in during your off hours for an occasional bull session.

When you carry on your own particular type of "youth activities," you do everyone a favor. Besides staying busy on something worth while, the kids also get an early start on the technical education which will help them hold down responsible jobs sometime in the future. Your efforts benefit the electronics industry as a whole, since you'll undoubtedly influence several capable young people to choose this field for their life's work. There's something in it for you, too. In addition to the deep satisfaction you get from helping others, you are building good will for your business and establishing yourself as an important member of your community. What's more, it could be part of the answer to your trained-help problem.



Ham Pals. When you promote cordial and friendly relations with your neighborhood radio amateurs, you are tapping an impressive source of immediate and potential business — particularly since hams are an ever-growing group.

For one thing, most hams (like other people) are TV set owners. And, while some of them may have sufficient electronic "know-how" to take care of minor and obvious troubles with their own sets, they more often have definite limitations in their shop equipment and special-

Mr. Service Dealer...


in CR Tubes Philco offers you

Double Protection

with Bond and Warranty

ALL NEW ... Electron Gun
 ALL NEW ... Exclusive Phosphor Coating
 ALL NEW ... Long Life Filaments
 ALL NEW ... Super Efficient Cathode
 ALL NEW ... Focusing Anodes
 ALL NEW ... Aquadag Shell Coating

Quality Tested—
 Life Tested

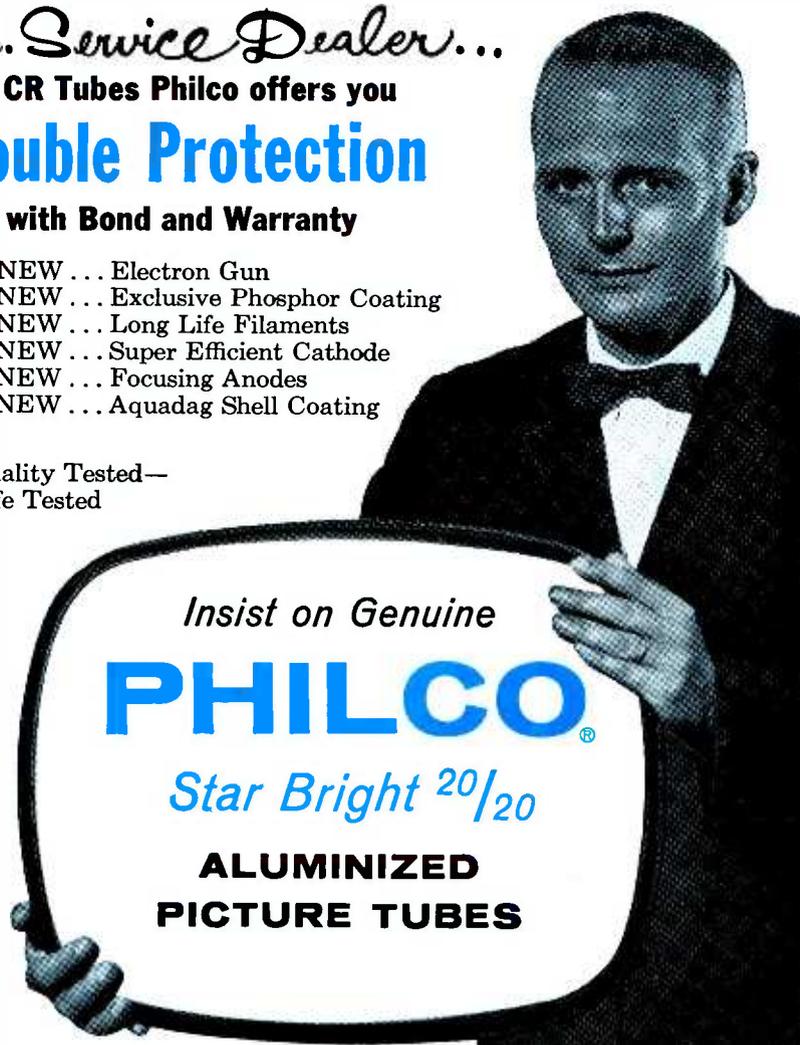

SENSATIONAL FREE OFFERS!

PHILCO PROFIT WHEEL PROGRAM

**Get All of the Details From Your
 Local Philco Distributor**

PHILCO ACCESSORY DIVISION
 WORLD-WIDE DISTRIBUTION

IS ONE OF THESE TYPICAL BLONDER-TONGUE AMPLIFIED INSTALLATIONS THE ANSWER TO BETTER TV RECEPTION IN YOUR AREA?


Blonder-Tongue reception improving TV products

NEW BLONDER-TONGUE B-24 POW-R BOOSTER



Powerful booster or amplified coupler provides sharp, clear pictures on 1, 2 or more TV sets with only one antenna. 10 db gain as 1-set booster, 5 db gain per set as amplified 2-set coupler. No-loss 4-set distribution system with B-T A-104 4-set coupler. New 6DJ8 frame-grid tube for highest signal gain. 24.95 list

NEW VHF ANTENNA BOOSTER, MODEL AB-2

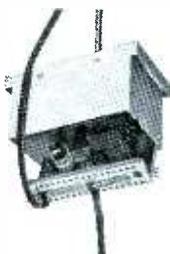

Brilliant, clear reception in fringe and weak signal areas — more than 10 db gain on all VHF channels. Utilizes advanced RF amplifier circuit with frame-grid tube for maximum signal-to-noise ratio. Can be mounted up to 500 feet from remote control unit. 53.95 list

Model AB-FM for superior FM reception. 53.95 list

'NO-STRIP' 2-SET COUPLER, MODEL A-102



300 ohm coupler provides low-loss, matched installation for superior two-set performance. Delivers more signal to each TV or FM set, with greater inter-set isolation than other couplers. No ghosts, no smears. Ideal for outside or indoor mounting, color TV, FM. 3.50 list

Model A-104 — 4 set coupler, list 4.50; Model A-105 high-low antenna list 3.50; A-107 UHF-VHF Mixer, list 3.50; A-100 Outdoor Mounting Kit, list 90¢

DISTRIBUTION AMPLIFIER, MODEL DA8-B




Powerful all-channel amplifier ideal for small TV systems (garden apartments, motels, TV showrooms), provides 8 isolated TV outlets from 75 or 300 ohm input and delivers more than 10 db gain on all VHF channels. Requires no tuning or other special accessories. 94.50 list

for every reception area — primary or fringe. for every type of installation — one set to 100


WEAK SIGNAL AREAS



INTERMEDIATE SIGNAL AREA

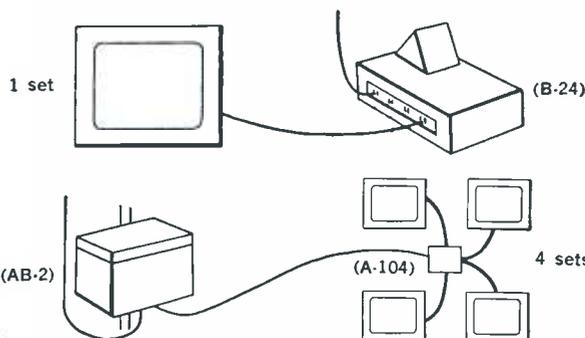


PRIME SIGNAL AREA

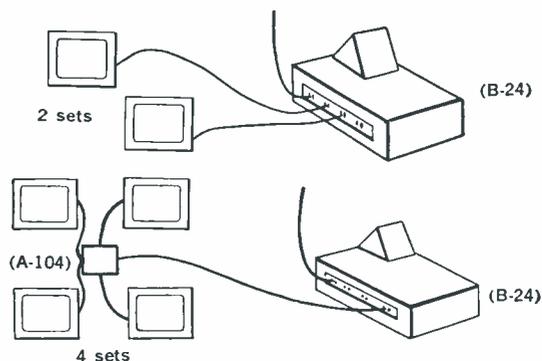

WEAK, INTERMEDIATE, PRIME SIGNAL AREAS

Small TV System — 8 sets

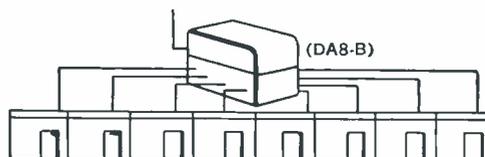

'NO-STRIP'— these Blonder-Tongue TV products feature exclusive B-T No-Strip terminals for speedy, secure positive installation.

More than 2,000,000 installations provide superior TV reception with B-T products.


Available at parts distributors. For further information write Dept. P-11

BLONDER-TONGUE LABORATORIES, INC.

9 Alling St., Newark 2, N. J.

In Canada: Telequipment Mfg. Co., Ltd., London, Ont. Export: Morhan Export Corp., N. Y. 13, N. Y.

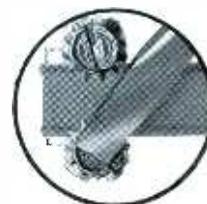hi-fi components • UHF converters • master TV systems • industrial TV cameras • FM-AM radios



ized knowledge. Thus, the average ham will more than likely seek professional TV service. Does he come to you? Not if he doesn't know you! Through contacts with other hams, he soon locates a TV man who has been a "good Joe" and has been doing a satisfactory job. Then business which could have been yours is taken elsewhere — perhaps even out of town.

Of course, TV sets aren't the whole story. Every ham worth his salt either *has* a good communications receiver or is feverishly hoarding his shekels to buy a better one.

He generally has the knowledge, ability and shop facilities to care for his receiver to the extent of replacing damaged components, but he is likely to need expert help in performing alignment and similar operations which call for more test equipment than the average ham shack boasts. If you can do such jobs, let your local hams know it; a few satisfied customers will spread the word. To save time and trouble, be sure to have hams bring factory instruction books for their communications radios along with the sets themselves. Another tip: encourage

their friendship by inviting them to participate in the work.

Your potential ham business does not end with the ham himself; almost invariably, his non-technical friends and neighbors will appeal to him for help in repairing their ailing radio and TV sets. Many hams hesitate to do more than "look at it"; in many cases, they will say they are not equipped to do the actual repairs, but will recommend an established shop. Will the shop they recommend be *yours*? It could be!

Make hams feel welcome; if you have the facilities, perhaps you could even offer them a place with a suitable "electronic atmosphere" to hold club meetings or training sessions. Your local hams would *like* to be your friends; *make* them so, to your mutual benefit.

A V R



the
NEW
PERMA-POWER

Model D-200

Automatic Voltage Regulator

will make you money and save you grief

It's easy to sell. There have been units similar to this on the market before—at prices upwards of \$75.00. The new PERMA-POWER Automatic Voltage Regulator has a list price of \$9.95—so *any* TV set owner can afford it . . . and any customer plagued by picture flutter, shrinking, flop-over, loss of brightness, and other similar disturbances will *want* it.

It's easy to use. This new unit insures top performance of TV sets by *automatically* returning full height and width to pictures when distorted by low line voltage. Whenever the line falls below 110 volts, it *automatically* boosts line voltage 10 volts—and it *automatically* feeds the line direct for normal voltages. *You don't have to worry about the customer's forgetting to switch the voltage regulator when the line is normal; this new PERMA-POWER unit switches automatically!*

It's easy to install. You plug it in, and it's ready to work; goes on and off with TV set. Compact and lightweight, it has no tubes, ballasts, relays, or other moving parts to fail; and it's fully guaranteed for one year. Can be used on any TV set or appliance rated up to 300 watts. See it at your distributor today.

Perma-Power COMPANY

3102 N. ELSTON AVE.
CHICAGO 18, ILLINOIS

S & C

Time Tip—IV. A TV set with an intermittent trouble is like a spoiled child; it tries to hog your attention and distract you from your other work.

Why not treat this type of receiver like the brat it is? Ignore it when it stubbornly refuses to act up—let it sulk in the corner until you can deal with it more effectively. Go ahead and do your regular work, rather than waste time on anything more than routine efforts to make the trouble appear. But watch the wayward set out of the corner of your eye, and pounce on it when it finally decides to cooperate.

You're probably thinking, "I'd like to let that intermittent sulk, but then how would I keep the *owner* of the set from sulking, too?" Well, that depends on the individual customer. If he is at all reasonable, be frank with him. Explain that the set can't be properly analyzed except when the trouble is actually present. Some of the public will understand your problem and will agree to let you take the time needed to complete the job.

If someone unreasonably insists on a quick repair of an intermittent trouble, we wouldn't blame you for turning down the job. Without adequate time to test the receiver thoroughly on that first trip to the shop, you'd be leaving yourself wide open for a series of embarrassing and profitless callbacks.


NEAT
NEW!

UNBREAKABLE

PRACTICAL

COMPACT

Picture shows actual size →

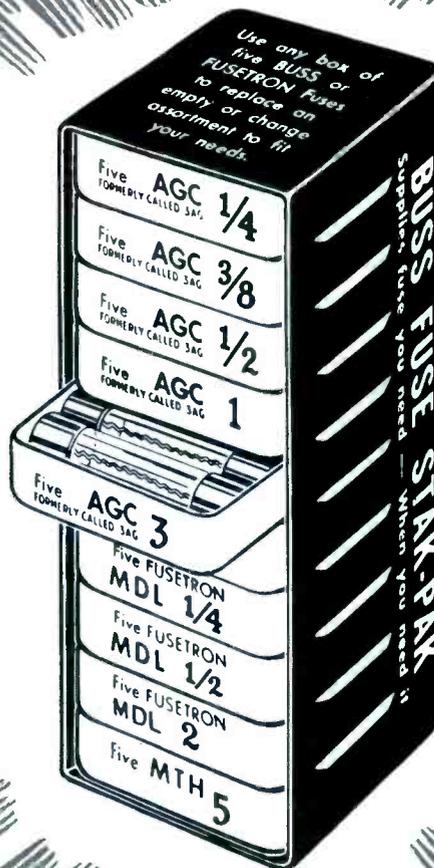

BUSS Fuse STAK-PAK

*An On-the-Job Fuse Assortment
Supplies the Right Fuse When You Need It*

The BUSS Fuse STAK-PAK offers the service man a new, convenient way to carry fuses.

It contains fifty of the most popular fuses, in ten different sizes and types. Five fuses to a box, ten boxes in all.

It's NEAT — no loose fuses scattered about in the tool box.

It's COMPACT — the most fuses in the smallest space — takes less space than any other type of assortment.

It's UNBREAKABLE — sturdy metal — not fragile plastic.

It's PRACTICAL — to replace fuses or to change assortments just slide in

tray of any BUSS or FUSETRON five-in box.

Serviceman can make assortment fit his local needs

The beauty of the STAK-PAK is that empty boxes can be replaced with same fuses — or assortment can be changed to fit the service-man's local needs.

Never any need for the serviceman to carry a lot of "slow-moving" fuses around with him.

If more fuses are needed the serviceman just picks up another STAK-PAK and arranges it to suit himself.

"PICK A PAIR OF STAK-PAKS"

Two Assortments Available to Supply Practically All Service Needs.

Standard Fuse Assortment supplies fuses most in use on popular TV sets. Order Number SP-1.

C & N Fuse Assortment supplies the popular sizes of these fuses that are especially designed for TV. Order Number SP-2.

While you think of it, make a note to "pick a pair of STAK-PAKS" at your distributor.

BUSSMANN MFG. DIVISION McGraw-Edison Co.
University at Jefferson, St. Louis 7, Mo.



1159

check that **TEMPER**ature

by Calvin C. Young, Jr.

When returning a color set that was recently in the shop for bench repairs, I checked color reproduction with a color-bar generator and found it to be satisfactory. At this time (the set was turned on for only a very short while), it seemed that color temperature and convergence were good, so no further adjustments were made. I collected for the repair and left. Needless to say, I was somewhat disturbed when the customer called the next day and complained that the colors were all wrong. In the customer's words, "the grass is blue and people's faces are murky." The customer requested that another call be made during a color transmission so I could see for myself. The next color program was at 7:30 that evening, and an appointment was made for that time. Arriving about 7:15, I began to make several preliminary tests. Operation of the various controls was checked, using the received black-and-white signal and the color-bar generator. It was noticed that a good black-and-white picture could be obtained if the brightness and contrast controls were judiciously adjusted. At low brightness settings, however, the picture took on a bluish hue. At higher settings, everything was tinged in green.

However, since it was time for the colorcast, the program was tuned in and the set adjusted for the best hue and color levels. Again, I found that by very careful adjustment of the brightness, contrast, hue, and color controls, an acceptable picture could be obtained on close-up scenes. But when a distant scene was shown, the grass appeared blue instead of green!

For the next 20 minutes, I carefully readjusted the color temperature controls for correct black-and-white balance. In simplified terms,

the procedure consisted of adjusting screen controls for gray values at normal brightness settings, and adjusting the background controls for gray values at low brightness settings (see Fig. 1). The procedure was repeated several times until the balance was maintained during normal variations in brightness and contrast control settings.

Now that this tedious task was over, I tuned in the station with the scheduled colorcast but, alas, the program had just ended. Fortunately, another was to start in a few minutes. While waiting, I couldn't help but worry and wonder, "Did the adjustments do the trick?" When the program came on, my worries were over. The picture was excellent, and, the customer was very pleased.

Needless to say, a thorough check of black-and-white balance is now a regular part of my color servicing procedure.

Home Call Can't Be Completed

On a recent call for a "no raster" condition, the customer insisted the set be fixed in the home. By asking the usual preliminary questions, I

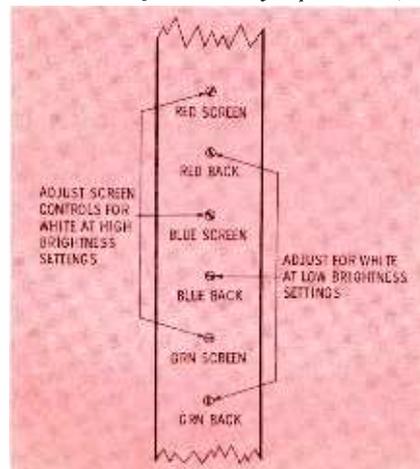


Fig. 1. Controls which are adjusted for proper black-and-white picture balance.

obtained an idea of how the set had failed. After removing the rear cover and plugging in my "cheater cord," I attempted to draw an arc from the 6BQ6 and 1X2B plate caps with a screwdriver. Getting nary a spark, I disconnected the power cord and tested the fuse. As suspected, it was open. After a VOM check of resistance from both sides of the fuse holder to chassis failed to reveal a short, I installed a new fuse.

When AC power was applied, the picture and sound both came on, but the picture wasn't too good. While I was checking the various horizontal sweep circuit adjustments, the picture started to shrink horizontally. Replacing the horizontal output tube cured this defect, and told me why the fuse had blown.

At this point, the set had been repaired for the defect the customer complained about — yet it wasn't *fully* repaired! The sound still had an annoying buzz, and the picture quality was poor. Touch-up adjustment of the ratio-detector transformer secondary had no effect on the buzz. Feeling that improper AGC action might be causing both the poor picture and the audio buzz, I decided to check the tuner, video IF, and video amplifier tubes for leakage and gas. Surprisingly enough, all of the tubes checked good — no leakage, no gas, good Gm.

Since the receiver was being operated on an outside antenna system, orientation of the antenna was checked. While some improvement was gained by turning the antenna slightly, picture and sound still weren't up to par.

Armed with all the facts—good tubes, proper antenna orientation, poor picture, and buzz in sound—I was convinced the set needed a trip

**Firefighting is for
firemen –
not servicemen**



Customers really burn when they have to call you back because of a premature failure. And while you're playing fireman, the profit on your next three service calls goes up in smoke. Tung-Sol tube quality is good insurance against callbacks. They're made to the highest specs of leading radio, tv and hi-fi set manufacturers. You'll find it good policy to keep that caddy full of Tung-Sol tubes. Tung-Sol Electric Inc., Newark 4, N. J.

Tell your jobber you'd rather have



TUNG-SOL®

Blue Chip Quality

TUBES • TRANSISTORS • DIODES

You can now **guarantee reliability** if you join Pyramid's

GOLD RUSH



BURTON BROWNE/New York

Pyramid's New "Gold Standard" $\pm 10\%$ Mylar® Capacitors

Imagine, capacitors that "absolutely guarantee reliability"! Pyramid's new "Gold Standard" capacitors, designed to give a critical tolerance of $\pm 10\%$ with non-hygroscopic Mylar dielectric, plus high resistance to moisture and high insulation resistance. Standard capacity values! Standard voltage ratings! Standard tolerance of $\pm 10\%$! Previously made only on special order and at premium prices, new "Gold Standard" capacitors are now available to servicemen at a price competitive with ordinary paper capacitors.

For reliability assurance, insist on Pyramid "Gold Standard" capacitors from your distributor. Catalog available.



PYRAMID

Pyramid Electric Company, North Bergen, N.J.

to the shop. Preparing myself for the worst, I simply told the customer exactly what I thought was wrong with the set and that it could only be repaired in the shop. To my surprise, the customer countered with, "Can you make the picture and sound good again if you take it into the shop?" Carefully explaining in layman's terms that the set required realignment, in addition to repairs to the AGC network, this customer was given my personal assurance that the job could be done. The customer okayed the shop repair without even a mention of price—and this was a brand-new customer, too!

Why? It's simple enough. My actions were convincing, and the customer quickly realized I had tried everything possible. Furthermore, the equipment I carried made it look as though I had every intention of fixing the set in the home. A brief explanation of the additional equipment needed for the job was the clincher. And payment for the job was made on delivery—with a smile and a thank you as well.

Printed Board Problem

A customer brought in a portable phonograph outfit and complained that it had suddenly gone completely dead. There were three tubes in the unit but, as luck would have it, they all checked good.

After visual examination failed to reveal any burnt resistors, etc., I applied AC power. Allowing a few seconds for warm-up, I turned up the volume control and touched my finger to the "hot" lead of the cart-ridge. Absolutely no sound came from the speaker.

A completely dead set usually means an open winding in the speaker or output transformer, so I next checked for plate and screen voltage on the output stage. Normal voltage at the screen and none at the plate



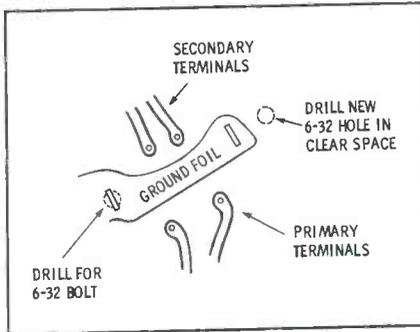


Fig. 2. Layout of printed board section modified to mount a new transformer.

meant only one thing—an open output primary. An ohmmeter test verified this and likewise eliminated the possibility that a short had caused the failure.


Now came the real problem. The service literature didn't list any standard replacement for this transformer. Furthermore, special spear lugs were used to mount the original to a printed board. Since I knew the customer would be unhappy at having to wait until an original replacement could be obtained, I decided to try my luck at installing a universal unit we had on hand.

Checking the printed board, I figured out how the new unit could be securely mounted. As shown in Fig. 2, I could drill out one of the original mounting holes so it would accommodate a 6-32 screw, and drill a new hole through a clear spot on the board. The flexible primary leads could be soldered to the original connection points without any problem. The secondary connections were another matter, however, since the replacement had several secondary lugs rather than wire leads. This matter was resolved by soldering wire leads from the proper lugs to the secondary terminal points on the board. Correct secondary impedance was determined from the specifications for the speaker in the replacement parts list, and by checking the speaker hook-up. Since, in this case, two four-ohm speakers were connected in series across the secondary of the output transformer, the replacement unit was connected to provide the necessary 8-ohm secondary impedance. A subsequent operating test confirmed the soundness of the repair.

The moral of this story is—don't get flustered because a part mounts to a printed board. Very often standard parts can be installed without too much trouble. ▲

Proved best in test after test!

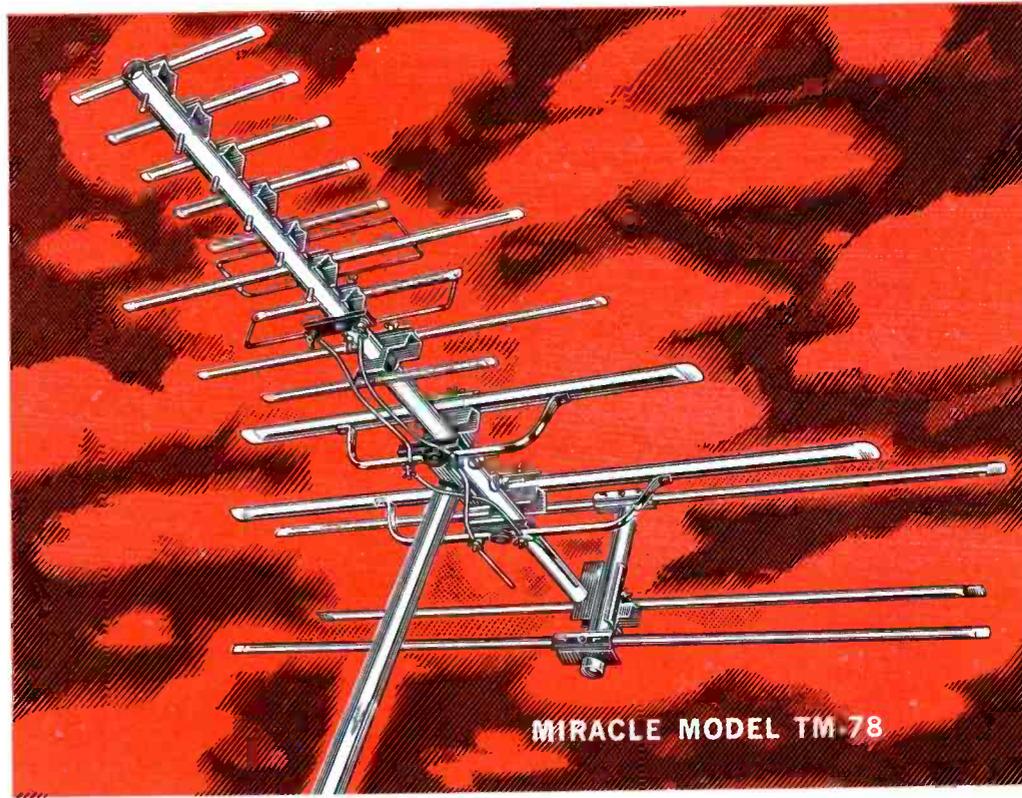
MIRACLE ANTENNA with MIRACLE REFLECTOR SYSTEM HAS YET TO MEET ITS PEER IN TV ANTENNAS!



HERE'S HOW TESTS WERE MADE...DO THE SAME AND CONVINCINGLY PROVE TO YOURSELF THAT THERE IS NO ANTENNA THE EQUAL OF MIRACLE

- TEST No. 1** Select location of tests in any tough reception area. Place any competitive "in-line" Yagi antenna on mast and point directly to desired station. Take reading and lower antenna as quickly as possible so as to assure same signal strength for all three tests.
- TEST No. 2** Add Miracle Reflector to same competitive Yagi, raise on mast, point directly to same station, take reading . . . and you'll be immensely pleased with its improved performance. The Miracle Reflector makes any "in-line" Yagi a better antenna.
- TEST No. 3** Now, lower Yagi and raise Miracle Antenna with Miracle Reflector System on mast. Point directly to same station and again take reading. You'll find that the Miracle with its amazing reflector, plus **tuned elements** gives you a **receiving combination** that has no equal among present day antennas. We invite YOU to make all three tests . . . why not do it at once and forever be convinced of Miracle superiority. Write, wire or phone collect today!

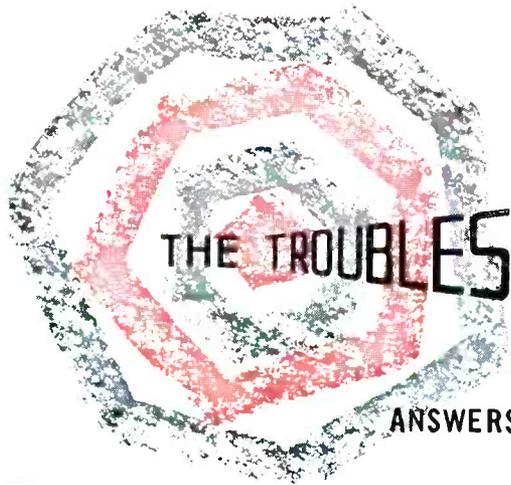THE TENNA MANUFACTURING CO. • CLEVELAND 25, OHIO
PHONE VULCAN 3-8080



THE TROUBLESHOOTER

ANSWERS YOUR SERVICE PROBLEMS

Skip-Mute

The muting switch on an RCA Model 3-HES-5 record changer is not working properly. It checks all right electrically, but its contacts never close during any part of the change cycle. How is this switch supposed to be tripped?

D. J. RECKTENWALD

Seattle, Wash.

An arm or projecting bar on the slide mechanism (under the turntable) is supposed to strike the muting switch during the change cycle, thereby grounding the output lead of the phono cartridge. Better check to see if any part of this mechanical linkage is bent or broken.

Sorry we couldn't send you a personal reply to your question, but you didn't furnish your complete address.

Juice Hog?

The owner of a Motorola Model 56T1 transistor radio complains that the battery runs down too fast, and only strong local stations can be picked up.

Checking voltages against those given in PHOTOFACT Folder 339-12, I find them all normal except on the converter transistor, a 2N172. The collector potential is normal; however, I measure .8 instead of 1.1 volts on the base and .7 instead of 1.1 volts on the emitter.

ALFRED WOODHAMS

Kalamazoo, Michigan


The 9-volt battery in this miniature set cannot be expected to last indefinitely. The receiver draws approximately 6 ma at full volume; according to battery specifications, only about 15 to 60 hours of actual operation should be anticipated at this level of current drain. (Service life varies according to several factors such as volume setting, operating temperature, and whether usage is continuous or only for short periods.) Thus, the receiver is probably normal unless a milliammeter in series with the positive lead of the battery indicates over 6 ma with the radio running "wide open." If you do find excessive current drain, look for such troubles as leaky filter capacitors across the power supply.

The slightly off-value voltages on the converter transistor are probably no cause for concern. DC potentials on the converter can be affected by several variables such as oscillator injection voltage, random noise fed in from the antenna, and differences between individual transistors.

You might be able to improve the sensitivity of the radio by slightly touching up the alignment.

Mysterious Fadeout

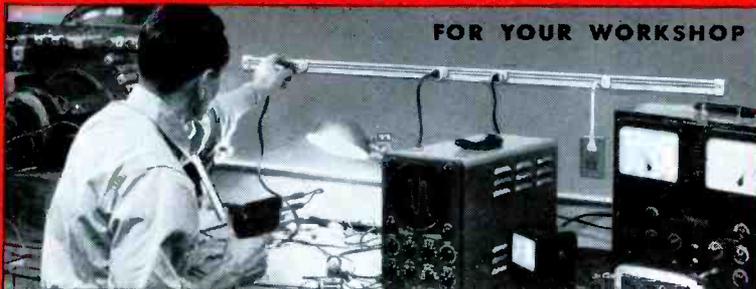A DuMont Model RA-162 is plagued with an intermittent loss of raster, accompanied by a slight loss of width on the right side just before the raster fades. The horizontal output tube evidently loses heater voltage, since it goes dark when the trouble occurs. At first, I thought the trouble was nothing more than an intermittently-open filament in the tube; however, replacement with a



FOR YOUR WORKSHOP

New electrical outlet convenience

Electrostrip

"4-FOOTER" KIT ^{PATENTED} \$2.95

Only five minutes to install it . . . then a twist of the wrist puts an electrical outlet right where you want it on Electrostrip! Here is ideal electrical convenience for your shop and for your displays. Electrostrip is the ideal solution to the problem of extra outlets in limited space . . . eliminates extension cords and "octopus" plugs. The "4-footer" Kit comes complete with 3 twist-in receptacle plugs, necessary screws, and handy polarized plug-in connector.

Write us for details on the Electrostrip "4-Footer" Kit, the "15-Footer" Kit, or the bulk rolls. Electrostrip is listed by Underwriters' Laboratories.



BULLDOG ELECTRIC PRODUCTS DIVISION
I-T-E CIRCUIT BREAKER COMPANY
BOX 177 • DETROIT 32, MICHIGAN


In Canada: 80 Clayson Rd., Toronto 15, Ont. Export Division: 13 East 40th St., New York 16, N.Y.



FOR YOUR DISPLAYS

INCREDIBLE HITACHI

THE SIZE • THE SOUND • THE POWER

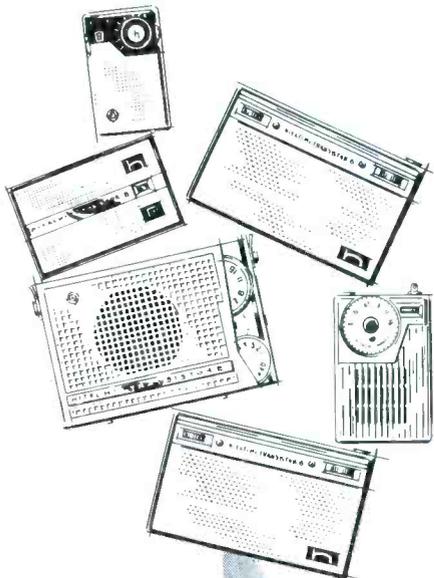

1960
ALL-TRANSISTOR
RADIOS from
GRAND PRIX
AWARD WINNING

HITACHI



Finest and most complete line of imported personal radios in America. Created by Hitachi, Ltd., world-renowned leaders in advanced electronics design and manufacture . . . honored with the Grand Prix gold medal, for scientific equipment, at the Brussels World's Fair. *EACH SET GIFT BOXED* with leather carrying cases and accessories. And *power-promoted* all the way, nationally and locally.

HITACHI

MEANS
ACTION FOR
PROFITABLE
CHRISTMAS
SALES!




It's the *fine line* that's nationally advertised and Pre-Sold to your customers now and all year round!

ACTION—count on it with
HITACHI

QUALITY

OF INTERNATIONAL REPUTATION

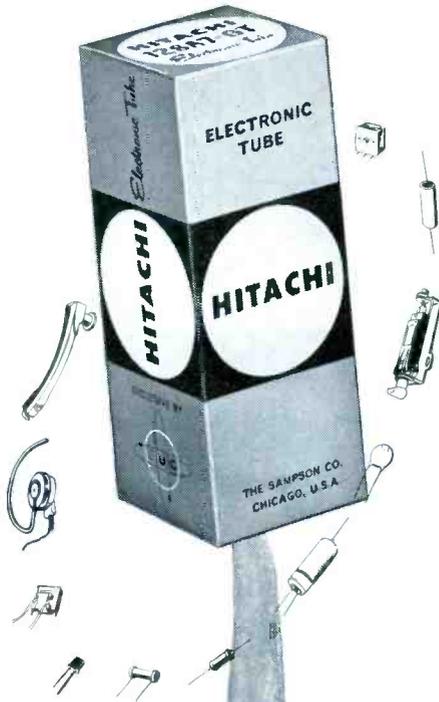

SELL—
SERVICE—SATISFY
with famous

HITACHI

RECEIVING TUBES




Choice as original equipment by manufacturers in the U.S. and abroad

Performance-proved around the world. Made the quality-controlled American way to fully meet *top American standards*. Yet, important cost savings assure you profits not normally obtainable with tubes of such high calibre.

A complete line of quality electronic components; send for Catalog No. 558-R.

For the name of the Hitachi distributor nearest you, write or phone:

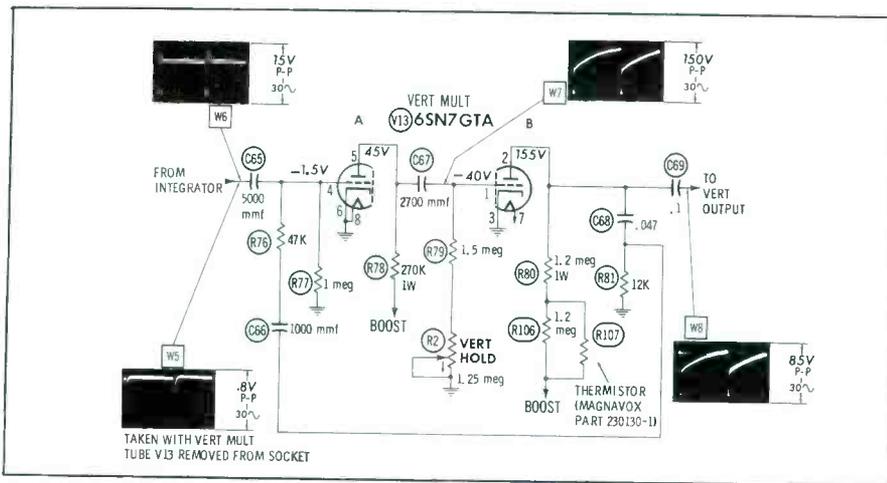THE SAMPSON COMPANY ESTABLISHED 1921
ELECTRONICS DIVISION • 2244 S. Western Avenue, Chicago 8 • Virginia 7-6363



new 6CD6 did not cure the defect. The power-transformer winding which supplies filament voltage to the output tube is apparently in good condition, since two other tubes connected in parallel across this same winding continue to receive voltage after the 6CD6 goes out. Measurement of filament voltage at the 6CD6 socket, with the defect present, showed that proper voltage was available. The socket was replaced, but the trouble still exists. Although the drive waveform on the grid is normal at all times, the DC voltage drops to about half of normal because no current is flowing in the output tube. Mechanical jarring of the ground and filament leads at the 6CD6 socket does not cause the symptom to appear.

ROBERT W. GREGWARE

Troy, N. Y.

You've made just about every possible test; offhand, I can think of only one more which you may not have attempted. This is to resolder the chassis ground connection of the lead going to the bottom side of the 6CD6 heater (pin 2 of socket). If this solder joint developed an intermittent high-resistance condition, filament voltage would be removed from the output tube; but you would still measure 6.3 volts AC from the high side of the 6CD6 filament to chassis ground.

Sync Almost Lets Go

Vertical sync in a Magnavox 250 Series receiver is critical; the picture slips a frame every now and then. Routine troubleshooting tests, including replacement of the integrator, have not improved operation. I don't fully understand this vertical oscillator circuit (which has a number of unusual features), and would appreciate a little explanation. For example, what is the purpose of C66 and R76?

M. J. MOLINA

Chicago, Illinois

This set has a modified type of plate-coupled multivibrator which operates independently of the vertical output tube. Although this arrangement is not employed too often, it is based on the first and simplest type of multivibrator circuit taught to students in TV training courses. The plate of each section of V13 is coupled to the grid of the opposite section through an RC network. This cross-coupling sets up a feedback action which causes the halves of V13 to "take turns" conducting; in other words, the circuit breaks into oscillation.

V13B remains cut off all through the vertical trace period, and sawtooth-forming capacitor C68 slowly charges from the B+ boost supply to develop the output drive waveform W8. The hold control serves to vary the discharging time constant of the RC network at the grid of V13B, thereby regulating the length of the trace period so as to control the frequency of oscillation.

At the end of trace time, V13B suddenly conducts and discharges C68. A negative going retrace pulse then appears in W8, and a spike of negative voltage is fed back through C66 and R76

Now Completely SELF-CONTAINED

For Testing & Rejuvenating

BLACK AND WHITE

and COLOR

including 110° TUBES

NEW CRT 440

CATHODE REJUVENATOR TESTER

B&K

TESTS AND REJUVENATES

all black & white and color picture tubes at correct filament voltage from 1 to 12 V.

TESTS AND REJUVENATES

110° tubes with 2.34, 2.68, 6.3 and 8.4 volt filaments.

TESTS AND REJUVENATES

color picture tubes. Checks each color gun separately same as black & white tubes.

Used by Thousands of Professional Servicemen

MAKES NEW PICTURE TUBE SALES EASIER

Gives you more value than ever—all-in-one. Quickly checks and corrects most TV picture tube troubles in a few minutes right in the home without removing tube from set. Gives new useful life to weak or inoperative tubes. Checks leakage. Restores emission and brightness. Repairs inter-element shorts and open circuits. Life test checks gas content and predicts remaining useful life of picture tube. Completely self-contained in leatherette-covered carrying case. Net, \$69⁹⁵

ACCESSORIES for USE ONLY with FORMER B&K Models 400 and 350 CRT



Model C40 Adapter. For use only with all previous B&K Model 400 and 350 CRT's. Tests and rejuvenates TV color picture tubes and 6.3 volt 110° picture tubes. Net, \$9.95

Model CR48 Adapter. For use only with all previous B&K Model 400 and 350 CRT's. Tests and rejuvenates 110° picture tubes with 2.34, 2.68, and 8.4 volt filaments. Net, \$4.95



See your B&K Distributor or Send now for Bulletin ST24-R



B & K MANUFACTURING CO.
1801 W. BELLE PLAINE AVE • CHICAGO 13, ILL.
Canada: Atlas Radio Corp., 50 Wingold, Toronto 10, Ont.
Export: Empire Exporters, 277 Broadway, New York 7, U.S.A.

to the grid of V13A in order to cut off the latter tube. V13A remains in the "off" state until its grid-circuit network becomes sufficiently discharged to let the tube resume conduction. At that time (the end of the retrace period), V13B is once again driven into cutoff.

Incoming sync pulse W5 is a negative spike which helps to achieve cutoff of V13A at the beginning of vertical retrace. Actually, cutoff occurs a little sooner than it would if no sync pulse were present. Therefore, if the sync signal is momentarily interrupted (as would happen during camera changes, between commercials, etc.), even a normally-operating vertical oscillator might temporarily slow down enough to cause one or two frames of vertical rolling.

If intermittent frame-slipping cannot be explained by fluctuations in the sync signal, you may assume that the oscillator is slightly unstable. This trouble is unlikely to be solved by voltage measurements or ordinary component-testing procedures; a better approach is to check resistors and capacitors (and the tube!) in the oscillator circuit by substitution.

There has been a production change in this chassis series, involving R80, R106 and R107. The schematic shows the most up-to-date version, which you might find advisable to install.

Pop Goes the Transistor

The output transistor in an auto radio sometimes becomes shorted because of a simple, easily overlooked defect in the radio or in the car's electrical system. We have recently heard several interesting reports of such troubles.

In a number of '58 Ford Model 84BF receivers, the cause of transistor burnout has been traced to the bias potentiometer in the audio output circuit. The case of this unit (which is grounded) has a hole on one side, and a terminal lug for the "high" end of the pot is brought out through the gap. In some receivers, there is insufficient slack in one of the leads attached to this lug. The lead thus exerts a constant sidewise pull on the lug, which eventually becomes shorted to the case. When this happens, the transistor's base is grounded—so it burns out. Next time you work on one of these radios, check the bias-pot leads



there's
a **C-D vibrator** for every
make and model

The C-D brand name on a vibrator is your guarantee of dependable performance, long trouble-free service. Because C-D vibrators are built to last, you can use them with full confidence. That's why it pays to reach for a C-D when a vibrator replacement is called for.


Remember, too, that there's a C-D vibrator type for every make and model car on the road. And the C-D VIBRATOR REPLACEMENT GUIDE makes it quick and easy for you to select the exact type required. Ask your local C-D distributor for a free copy of VIB-3, or write to Cornell-Dubilier Electric Corp., S. Plainfield, N. J.



**50 YEARS
OF
PROGRESS**

**CORNELL-DUBILIER
ELECTRIC CORP.**

THE BEST IN ELECTRONIC COMPONENTS

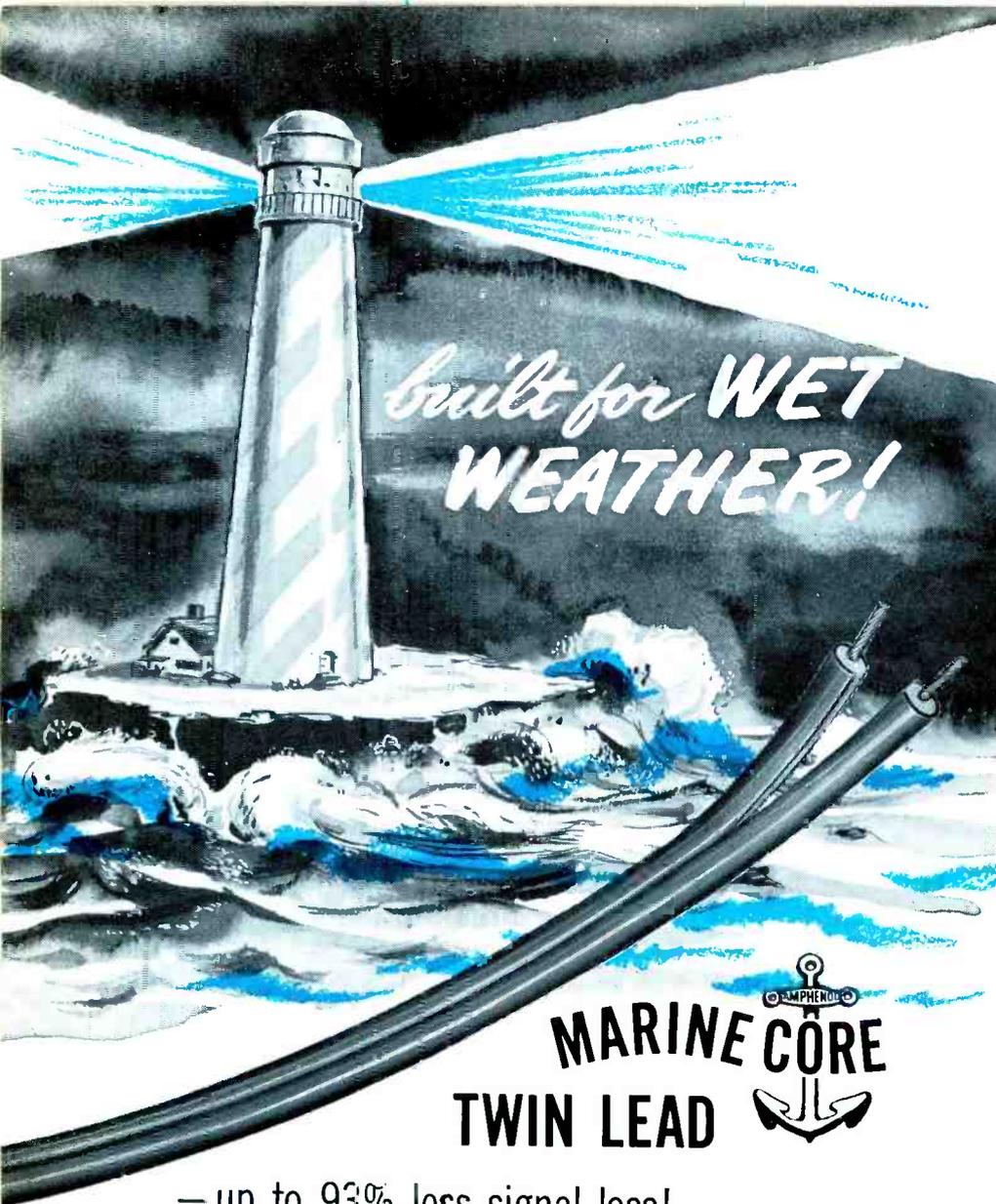

built for **WET
WEATHER!**

MARINE CORE
TWIN LEAD 

— up to 93% less signal loss!

In moisture, salt spray or areas of heavy industrial contamination, AMPHENOL's new 214-103 Marine Core Twin Lead provides amazing low-loss performance. Measured signal loss of polyfoam Marine Core *submerged* is 20% less than other foam type lines, 25% less than tubular lines, and up to 93% less than standard twin leads. Marine Core gives vital signal protection where other twin leads fail!

Extremely flexible, Marine Core's performance secret is simple: Proper spacing ratios between conductors and between conductors and line surface, a discovery of AMPHENOL engineers.

A tough, brown virgin polyethylene jacket protects Marine Core's double self-sealing cores of polyfoam. Conductors are 7/28 pure copper for longer life. Availability: Coils of 50, 75 and 100 ft., put-ups of 500 and 1000 ft.



AMPHENOL DISTRIBUTOR DIVISION
Amphenol-Borg Electronics Corporation
BROADVIEW, ILLINOIS

and lengthen them if necessary.
Another '58 Ford radio had similar trouble symptoms for an entirely different reason—strictly automotive this time. When the radio would not play in the car after being repaired, the battery polarity was checked and found to be reversed! Come to find out, the battery was incorrectly marked; the + sign was at the wrong end. For this reason, it had been installed backwards when the car was built. The glow of the red NOT CHARGING dash light caught the eye of the mechanic who inspected the car upon delivery. Deciding that the generator was incorrectly polarized, he "corrected" it. The generator then agreed in polarity with the battery; but, unfortunately, both were wrong.

Another case of wrong polarization, involving a '58 Oldsmobile, came to the serviceman's attention when he noticed that the blower motor of the heater was running backwards and sucking air out of the passenger compartment.

Polarization, which takes place during the manufacture of the generator, provides its field with enough residual magnetism to enable the unit to start charging as soon as it goes into service. Normally, repolarization is not necessary except when the generator field is rebuilt; but, if you ever have to perform this service, you can do so by disconnecting the FIELD and BATT wires from the voltage regulator (with engine off!) and momentarily connecting them together. This serves to remove the residual magnetism from the generator field and allow it to build up in the opposite direction.

Fuse Clues

In one of your early columns, we notice that Frank Szwaneck reported having trouble with repeated failures of the fusible resistor in an RCA Model 17D8185 for no apparent reason. We found that the original 5-watt resistor (RCA stock number 100151) overheats because of its closeness to the 17AX4 and 17DQ6. By replacing the original with a 100117B, rated at 7 watts, we found that we could eliminate the failures. We also understand that the 3/10-amp, L-type fuse should be replaced with the new chemical fuse, number 105042.

In regard to E. J. Carolan's trouble with fuse failure in a Model 21D8588, the vertical output tube current passes through this fuse and can cause repeated fuse failure if excessive. Even if the vertical circuit is OK, however, the original 3/10-amp fuse should be replaced with the number 105042 chemical fuse as mentioned above.

JOHN NOWAK,
Service Mgr.
Shelborne Electronics, Inc.


Wilkes-Barre, Pa.

I hadn't seen this field service information at the time I answered the above letters. Thank you for bringing us up to date.

Service Technicians! YOU EARN MORE... YOU RATE with the public when you own the **PHOTOFACT**® service data library!


"Time saved is the main reason we feel a real need for the PHOTOFACT Library. We could repair a set by trial and error but PHOTOFACT lays all the facts before us and reduces bench time to a minimum".

—William C. Dixey
Riverside, N.J.

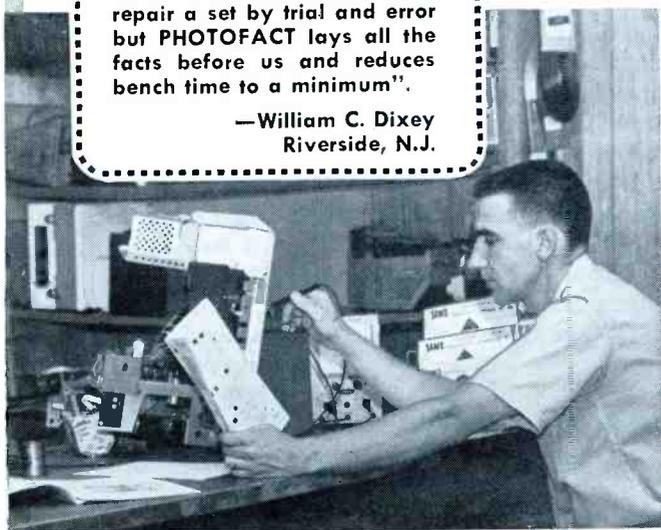

"PHOTOFACT gives us the best and latest information on part numbers, etc., as well as excellent schematics. Couldn't do without them".

—Johnny Wheeler
Mobile, Ala.

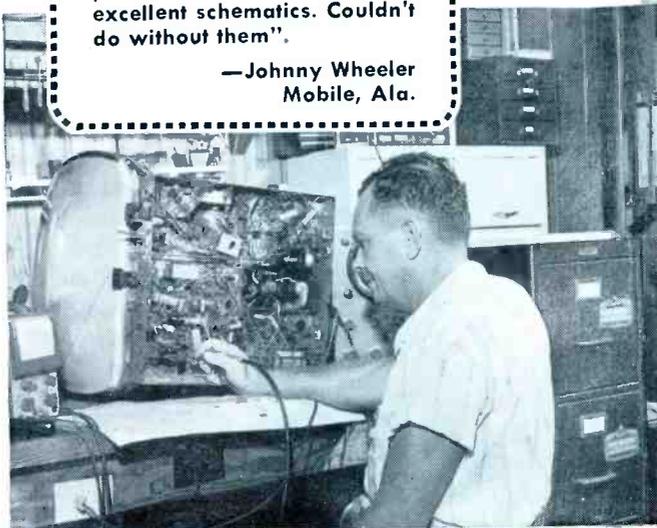

Yes, if you are one of the thousands of owners of a complete PHOTOFACT Service Data Library, you are enjoying maximum earnings. It's inevitable, because no matter how expert you are, you can always *save more time on any job, get more jobs done daily—EARN MORE, DAY IN AND DAY OUT...*

Moreover—as the owner of a complete PHOTOFACT Library, *you know your customers' sets best.* You can actually show each customer you have the PHOTOFACT Folder covering his very own set. Result: You command public respect and acceptance which paves the way to expanded business for you...

HERE'S HOW TO STAY AHEAD...

Today, the truly successful Service Technicians are those who own the complete PHOTOFACT Library, who can meet and solve any repair problem—faster and more profitably. And these men *keep ahead* because they're on a Standing Order Subscription with their Distributors to receive all new PHOTOFACTS as they are released monthly.

For PHOTOFACT Library Easy-Buy Plan details and Standing Order Subscription, see your Sams Distributor today, or write to Howard W. Sams...



BIG NEW PLUS

**"PEET"
PROGRAM**

If you now own a PHOTOFACT Library, you can apply at once for qualification in the powerful new "PEET" program. Designed to help you gain deserved recognition as a reputable businessman; develop and command public respect; justify better earnings warranted by your business investment and skill; pave the way to expanded business and increased profits for you. Ask your Sams Distributor about "PEET" or write to Howard W. Sams.

HOWARD W. SAMS & CO., INC.
2201 E. 46th St., Indianapolis 6, Ind.

- Send me full details on the new "PEET" Program, designed to build prestige and business for the Service Technician who qualifies. Include full information on the Easy-Buy Plan and Free File Cabinet deal.
- I'm a Service Technician: full-time: part-time

My Distributor is: _____

Shop Name _____

Attn: _____

Address _____

City _____ Zone _____ State _____

Class A AMPLIFIERS

Their use in power and voltage circuits accounts for over half the stages in a TV set.

Did you know that most of the circuits in a TV or radio receiver are class-A amplifiers? We have the RF amplifier in the tuner, video IF amplifiers, sync amplifiers, video amplifiers, the entire audio section (IF, amplifier and output), and the sweep amplifiers. Some of these are designed for voltage amplification, while others are power amplifiers. A better understanding of these two types of circuits will help you become master over a large percentage of the circuits in any TV or radio receiver.

Voltage Amplifiers

A class-A voltage amplifier stage generally employs a triode or a pentode biased so that the input signal never drives it into saturation or cutoff (See W1 of Fig. 1). The tube operates on the linear portion of its E_g - I_p curve (Fig. 2), and the signal is thus amplified without becoming distorted.

Class of operation is but one aspect of voltage amplifiers. Other factors are just as important; namely, supply voltage, applied signal voltage, plate- and grid-load impedances and characteristics of the tube itself. In order to explain how and why these factors are important, we'll use RC-coupled audio ampli-

fiers as examples; however, the principles outlined will also be applicable to other types of class-A amplifiers. Let's select a common audio amplifier tube, say the 12AX7, and use it in the standard circuit of Fig. 1. The values shown were taken from the circuit of an often-used circuit. Using these and the 12AX7 specifications listed in the tube manual, let's figure the gain furnished by this stage.

Incidentally, you may be wondering why the grid-load resistor of the 12AX7 is missing. Well, it's because its value has little or no effect on the gain of this stage. Voltage gain is a function of the mu and internal resistance of the tube, and load impedance. Load impedance of a voltage amplifier depends on the values of R_p , C and R_g . Consult the simplified diagram in Fig. 3 and note that C and R_g are in series, and they, in turn, parallel R_p . This combination makes up the total load impedance Z_o of this stage. (R_p does not actually connect to chassis ground but to signal ground via the B+ filters.)

The voltage gain of a triode at mid-audio frequencies may be found using the formula,

$$VG = \frac{\mu \times Z_o}{Z_o + R_i}$$

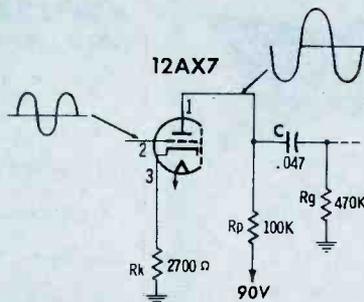


Fig. 1. Parallel combination of R_p and R_g form the total load impedance Z_o .

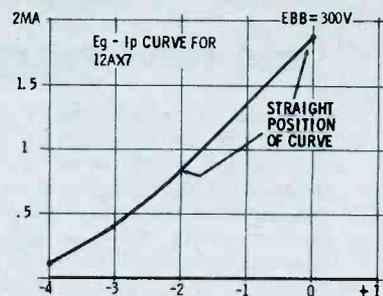


Fig. 2. Linear portion of E_g - I_p curve for 12AX7 tube with 300-volt plate E.

where R_i is the internal plate resistance of the tube, μ is the amplification factor of the tube, and Z_o is the equivalent output load impedance. The impedance of C is insignificant above a few hundred cps; thus, output impedance is the equivalent of R_p and R_g in parallel, or 80.5K ohms. The tube manual lists μ as 100 and internal plate resistance at 80,000 ohms. Substituting these into the formula, we find that $V_G = 50$.

Thus, using a tube with a theoretical gain factor (μ) of 100, we actually achieve a stage gain of 50. The full potential isn't realized because to do so would mean the tube would have to be driven from cutoff to saturation, and serious distortion would result.

Frequency Response

We mentioned that the impedance of C could be ignored for mid-audio frequencies; however, it cannot be ignored at very low frequencies. This follows since the signal voltage developed across R_p must be coupled through C to R_g , and if the impedance of C is high, an appreciable amount of signal will be developed across it, thereby reducing the signal across R_g .

High-frequency response is governed by the input capacity of the following tube, the output capacity of the amplifier tube, and the stray wiring capacity in the circuit, all of which effectively shunt the plate load (Fig. 4).

If we assume that the following stage uses a 6V6GT power amplifier and that there is about 10 mmf of stray wiring capacity, we find that the total shunt capacity is approximately 20 mmf. Its impedance at 20 kc is approximately 398K ohms. Being in parallel with R_p and R_g , it effectively lowers the plate-load impedance of the circuit at the higher frequencies. The mathematics required to calculate the exact load impedance at high audio frequencies is complex and will be omitted; it is only necessary that you understand the factors limiting the high-frequency response of a circuit.

Now let's apply this theory to a practical circuit—the audio section of a TV receiver. As is seen in Fig. 5, the high frequency response has been purposely limited by the installation of a 43-mmf capacitor

RCA's Top Three for Electronics Technicians!



NEW: RCA WO-33A SUPER-PORTABLE OSCILLOSCOPE

only \$129.95* (complete with Low-Cap Direct Input Probe and Shielded Cable). (Also available as easily assembled kit WO-33A (K) only \$79.95*, incl. above accessories)

Here is your rugged, compact, super-portable scope for those "in the home" color-TV and black-and-white TV servicing jobs! Enough bandwidth and gain for any "tough dog" service job—FEATURING: cable and power cord storage bracket on carrying handle • combination direct/low-cap probe and shielded input cable assembly • voltage calibrated, frequency-compensated 3-to-1 step attenuator • scaled graph screen and calibrating voltage source for direct reading of peak-to-peak voltages • "plus-minus" internal sync holds sync to 4.5 Mc • weight only 14 pounds!



NEW RCA WV-38A VOLT-OHM-MILLIAMMETER

only \$43.95* (complete with batteries, probe and cable with slip-on assembly, and operating instruction). (Also available as easily assembled kit WV-38A (K) only \$29.95*, including above accessories)

You'll get a world of use from this very essential piece of test equipment—FEATURING: extra 1-volt and 0.25-volt ranges for transistor servicing applications • fuse-protected ohms-divider network • polarity reversal switch • full-wave bridge rectifier circuit with excellent frequency response and low circuit loading on the ac ranges • extra large 5½-inch meter with easy-to-read standard ranges • standard dbm ranges.



NEW RCA WV-77E VOLT OHMYST

only \$49.95* (also available as easily assembled kit WV-77E (K) only \$29.95*)

The latest in the famous RCA VoltOhmyst quality line—FEATURING: fuse-protected ohms-divider network • ultra-slim probes and flexible leads • sleeve attachment on handle stores probes, leads, power cord • separate 1½-volt rms and 4-volt peak-to-peak scales for accuracy on low ac measurements • front panel lettering acid-etched for long life!

*User Price (Optional)

See the "top three" plus RCA's complete professional Test Equipment line at your Authorized RCA Test Equipment Distributor!



RADIO CORPORATION OF AMERICA
Electron Tube Division
Harrison, N. J.

from the plate of the 6T8 amplifier to ground. This capacity, added to the 20 mmf normally contributed by the tubes and the wiring, results in a total of 63 mmf, which has a reactance of about 170K ohms at 15 kc. Since the effective load impedance at mid-range is the parallel arrangement of R_p and R_g , or 235K ohms, it can be seen that the load has been effectively lowered at 15 kc by the shunting capacity. This lowering of load impedance means a reduction in the high-frequency gain of the stage. This is

desirable in this case since the low-frequency response of the speaker (a 5" or 6" unit) is very poor, and reduction of the high-frequency gain helps to equalize the ratio of "highs" to "lows." The listener is thereby given an illusion of better fidelity.

Driving Signal

It was previously stated that the grid signal couldn't be permitted to drive the grid into conduction or cutoff; and, as we continue, the reasons for this will become clear.

Let's get back to the Eg-Ip curve

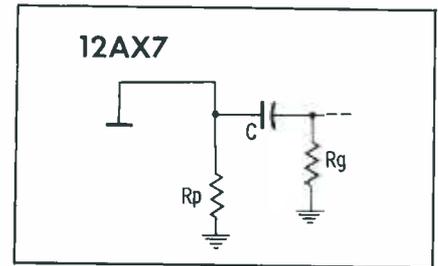


Fig. 3. Simplified load circuit class-A amplifier consists of R_p , C , and R_g . mentioned very briefly at the beginning of this article. You are probably wondering just where this curve was obtained, since it isn't given in the ordinary tube manual. Well, the data from the average plate-characteristic chart in a tube manual was transferred to graph paper as follows: Consult the curve in Fig. 2 and notice that plate current is plotted vertically, while grid voltage is plotted along the horizontal axis. Since zero bias will produce higher plate current than a more negative bias, the zero bias point is located toward the right side of the graph. At equally spaced points along the horizontal plane, graduations corresponding to the bias curves from the tube manual are marked. Since 300 volts is the value of $B+$ often used to supply a 12AX7 stage, follow straight up the 300-volt line in the tube manual chart and plot plate-current flow for each bias voltage. You should find that current is 1.9 ma with zero grid volts, 1.4 ma at -1 grid volts, .85 ma at -2 grid volts, .4 ma at -3 grid volts, and .1 ma at -4 grid volts. Connect the points thus obtained and you have the Eg-Ip curve, or transfer curve as it's often called. The curve between -2 volts and 0 volts is linear, since for a given vertical change along this portion there will be an identical horizontal change.

Practical Applications

The 6AT6 voltage amplifier, with a plate-load resistance of 100K ohms and a grid signal of 2 volts, can produce an output signal of 75

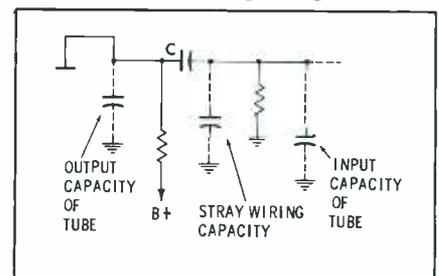


Fig. 4. Input, output, and stray capacitances limit high-frequency response.

The MONEY-MAKING Technicians are using

The Pioneer 250... by DOSS

HORIZONTAL SWEEP QUANTALYST

This is the **ONLY INSTRUMENT** to do the complete job of component failure isolation in the entire **HORIZONTAL SWEEP CIRCUIT**

Tests made in minutes with this new

PLUG-N-CIRCUIT DESIGN

\$12900 NET

TYPICAL HORIZONTAL SWEEP CIRCUIT

DYNAMIC IN-CIRCUIT TESTS (RECEIVER ON)

1. Flyback Transformer (Shorted Turns)
2. Yoke (Shorted Turns)
3. Flyback-Yoke Match
4. Yoke Inductance (mh)
5. A.F.C. Sync. Range
6. Oscillator Frequency (cps)
7. Oscillator A.C. Output
8. Amplifier Cathode Current
9. Amplifier Grid Condition
10. Amplifier Gas Condition (Screen Re-emission)
11. Amplifier B+ Ripple
12. Amplifier Heater Voltage
13. Damper Heater Voltage
14. Amplifier Screen Voltage
15. Amplifier Screen Condenser
16. Amplifier Cathode Voltage
17. Amplifier Cathode Condenser
18. Oscillator Coupling Condenser
19. Boost Voltage
20. B+ Voltage

STATIC CIRCUIT TESTS (RECEIVER OFF)

21. Boost to B+ Resistance
22. Boost to Common Resistance
23. Screen Resistance
24. Cathode Resistance

Tests the component you suspect, or the many you don't

New Features You Get Only from

DOSS

ELECTRONIC RESEARCH, INC.
820 Baltimore • Kansas City 5, Mo.

For complete information including FREE Quantalyst Trouble-Shooting Chart — Please request Folder MP3

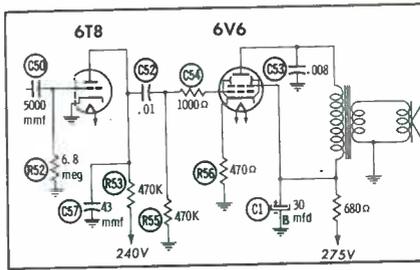


Fig. 5. Typical single-ended power amplifier circuit showing part values.

volts p-p if the DC supply is 250 volts and bias is -2 volts. From tube manual data, we can see that this exceeds the 8.5 to 12.5 volts p-p required to drive a single 6V6GT to full output. This explains why the sound on a TV receiver will distort when the volume control is turned to maximum.

Now, you may ask, "Why is this excess gain built into an amplifier?" It's possible to hold the output signal down to the required level by simply adjusting the volume control; however, there is no control to make up for lack of signal. This high gain factor is very useful in fringe areas where the signal at the grid of the audio amplifier is much less than 2 volts p-p.

Power Amplifiers

A few power-amplifier circuits will employ power triodes; but, because a pentode or beam-power tube has a much greater power sensitivity, most will employ one or the other of these. Power sensitivity is the ratio of signal power input to signal power output. Let's look at a couple of examples to emphasize this point. Using data from the tube manual, we find that 8.5 volts of audio signal is required to drive a 6V6GT to its full output of 2 watts. We know from experience that 470K ohms is a standard grid load for a 6V6, and we know from basic theory that power equal E^2/R , so we can readily determine that .154 milliwatts is sufficient to drive the tube to the limit.

Now let's look at a similar case with a 2A3 power triode. Again using data in the tube manual, we find that 45 volts of audio signal across a grid load of 500K ohms is needed to produce a maximum audio signal output of 3.5 watts. Thus, if we square 45 and divide by 500K we find that 4.05 milliwatts is required to drive this power triode to full output. Now if we divide the output power by the in-


put power in each case, we will have a comparison of the power sensitivities of these two tubes. For the 6V6GT, it is almost 13,000 while it is only 864 for the 2A3.

The chief advantage of the power pentode or beam-power types over the power triode is, therefore, much greater power sensitivity. Power pentodes have only slightly less power sensitivity than their beam-power equivalents.

We previously stated that voltage amplifiers employ plate-load impedances of fairly high values, (about 100K ohms) and that plate

current is normally on the order of a few ma. In power amplifier circuits, just the opposite is true; i.e., low-impedance plate loads are employed and plate current is high (on the order of 35 to 50 ma for a single-ended stage and higher for push-pull stages). With the exceptions of the low plate-load impedance, high plate current, and large grid signal, the single-ended power amplifier operates much the same as a voltage amplifier.

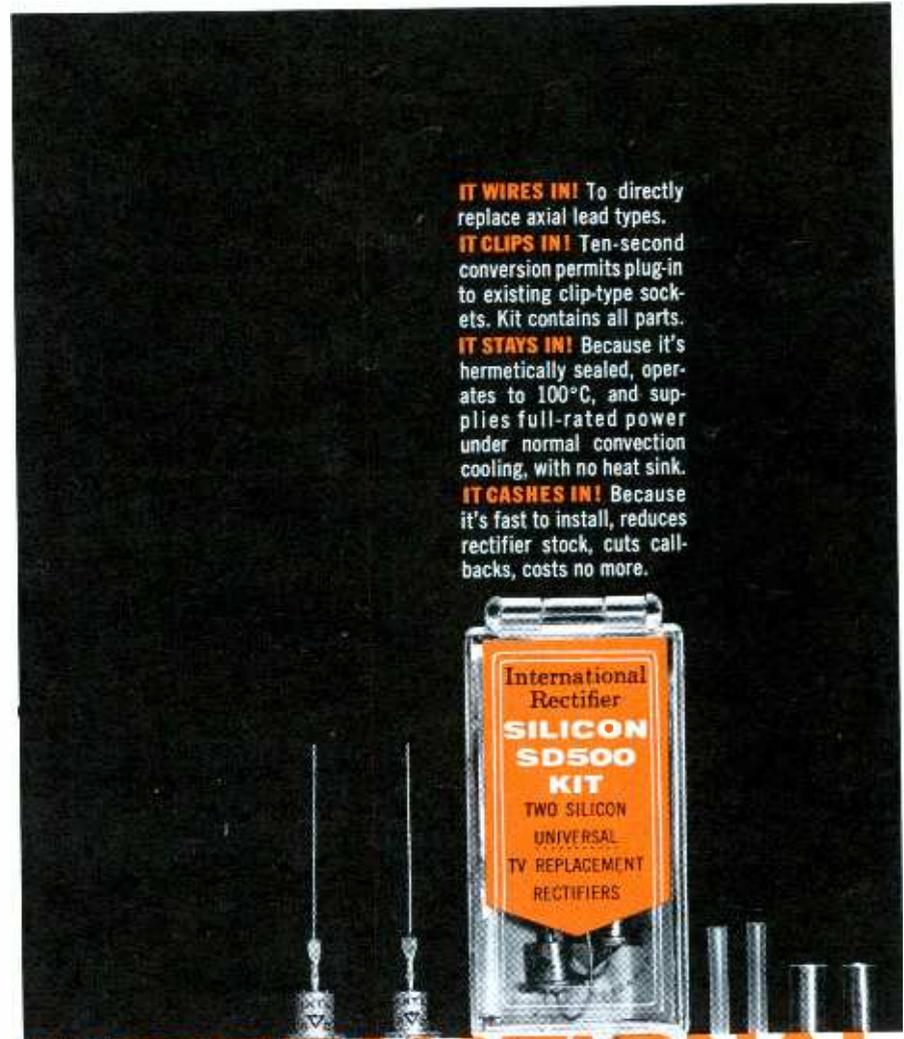There is one other point we should make about single-ended power amplifiers, and that has to



IT WIRES IN! To directly replace axial lead types.

IT CLIPS IN! Ten-second conversion permits plug-in to existing clip-type sockets. Kit contains all parts.

IT STAYS IN! Because it's hermetically sealed, operates to 100°C, and supplies full-rated power under normal convection cooling, with no heat sink.

IT CASHES IN! Because it's fast to install, reduces rectifier stock, cuts call-backs, costs no more.

INTERNATIONAL RECTIFIER

SD-500 KIT —The silicon radio-TV rectifier kit that replaces a drawerful!

INTERNATIONAL RECTIFIER CORPORATION

Distributor Sales Division: El Segundo, Calif.



Choose ... XCELITE[®] Hand Tools ... the Professionals do!

You need the BEST TOOLS to do the BEST JOB . .

Your Radio, TV and Electronic Parts Distributor has them!




Check the "SEIZER"

Provides the necessary "third hand" in so many tricky situations!



No. 42H

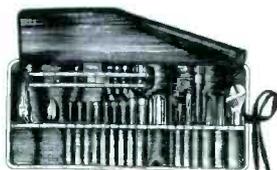- Clamps on as a Heat Sink.
- Holds wires etc. while soldering.
- Holds dial cords when stringing them.
- Retrieves small items from awkward places.
- Out-reaches and out-holds needle nose pliers.



Select from the Complete Line of Quality Tools and Handy Kits . . .

XCELITE, INCORPORATED
ORCHARD PARK, NEW YORK
Canada: Charles W. Pointon, Ltd., Toronto

XCELITE
Quality Hand Tools
PREFERRED BY THE EXPERTS

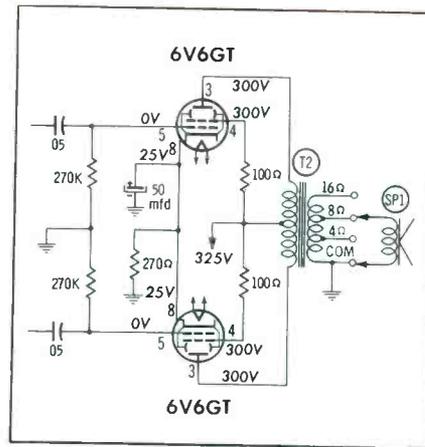


Fig. 6. Push-pull circuit provides three times the power of single-ended stage.

do with frequency response. The factors that affected frequency response in voltage-amplifier circuits also apply to power amplifiers; however, there are a couple of other factors which must also be considered. These are the frequency-response characteristics of the output-load impedance and the effect of the cathode load.

The audio-output transformer (the usual load impedance for an audio power stage) seriously affects the frequency response, and in all but expensive hi-fi units, the output transformer may actually limit the response to a range of 200 cycles to about 7 or 8 kc. This is considered adequate for voice and popular music and will be completely satisfactory to most customers.

Referring back to Fig. 5, you will notice that the cathode load resistor is not bypassed. The signal developed across it is 180° out of phase with the grid signal, reducing the gain of the stage slightly. At the same time, however, this helps improve frequency response since it tends to flatten the gain-versus-frequency curve.

Push-Pull Output Stages

The tube manual shows that only 5.5 watts, at 12% harmonic distortion, can be obtained from a single 6V6GT. However, two such tubes in a push-pull, class AB amplifier (Fig. 6) can deliver 14 watts with only 3.5% harmonic distortion. The reduced distortion is due to cancellation of even harmonics by the push-pull operation. Hum due to plate-voltage variations is also cancelled—a good reason why B+ to a push-pull amplifier may be obtained directly from the output of

PROFESSIONAL technicians use *Dave Rice's* OFFICIAL ORDER BOOKS for every TV-RADIO service call



This is the businesslike approach to service record keeping. TriPLICATE forms serve as order form, invoice and office record, with spaces for complete information on every job. Separate listings for receiving tubes, pix tube, parts, serial numbers, labor and tax charges, signatures, etc. 75c a book, \$6.50 for dust-proof box of 10. In stock at your distributor. Write for your free folder describing Dave Rice's OFFICIAL ORDER BOOKS, including an actual size sample copy of the handy order form.


For customer's prices on every replacement part, plus flat rate and hourly service charge data, regional and national, Dave Rice's OFFICIAL PRICING DIGEST, listing over 63,000 items. \$2.50.

ELECTRONIC PUBLISHING CO., INC.
180 N. WACKER DRIVE
CHICAGO 6, ILLINOIS



FROM ONE WHO LEARNED

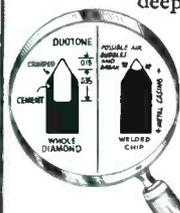This enlargement shows a diamond-chip needle sent us by a disappointed user, who learned all diamond needles are not O.K. Shows what happens if a heat bubble forms when a chip is welded on. Can't happen with a Duotone Needle that uses only the *whole diamond set* deep in the metal shank.



Insist on Duotone. Be sure. Duotone's whole diamond can't break off.

DUOTONE DIAMOND NEEDLE

"That remembers"
Keyport, N. J.

In Canada: Chas. W. Pointon, Ltd., Toronto


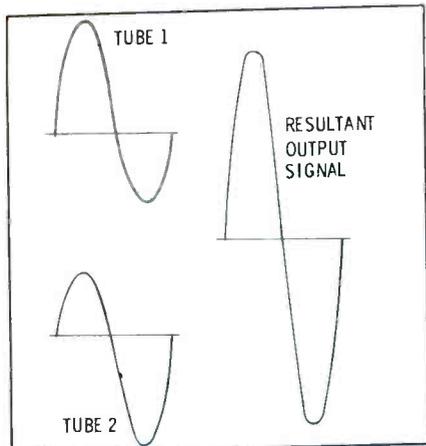


Fig. 7. How signals in push-pull, class-AB amplifier produce increased output.

the rectifier. In case you happen to be wondering just why it is desirable to connect the power amplifier directly to the output of the rectifier instead of to the filtered output, consider that the power-output stage draws more current than the remainder of the circuits in that unit. By not having its current pass through the filter resistor, the required wattage rating of this component is reduced. Then, too, the voltage at the output of the rectifier is higher, permitting higher output power to be obtained.

We mentioned briefly that a push-pull power amplifier using 6V6GT tubes operating class AB could produce 14 watts of audio signal power. This is almost three times the power that can be obtained from a single tube operated class A. To make this possible, the tubes are biased closer to cutoff so that each tube amplifies one-half of the signal more than the other. However, due to the driving arrangement, one tube amplifies the positive half of the signal more than it does the negative, while the other tube amplifies the negative half of the signal more than it does the positive. As shown in the drawing of Fig. 7, two power-amplifier tubes operating push-pull on a non-linear portion of the Eg- I_p curve can produce a linear (distortion-free) signal at relatively high output power.

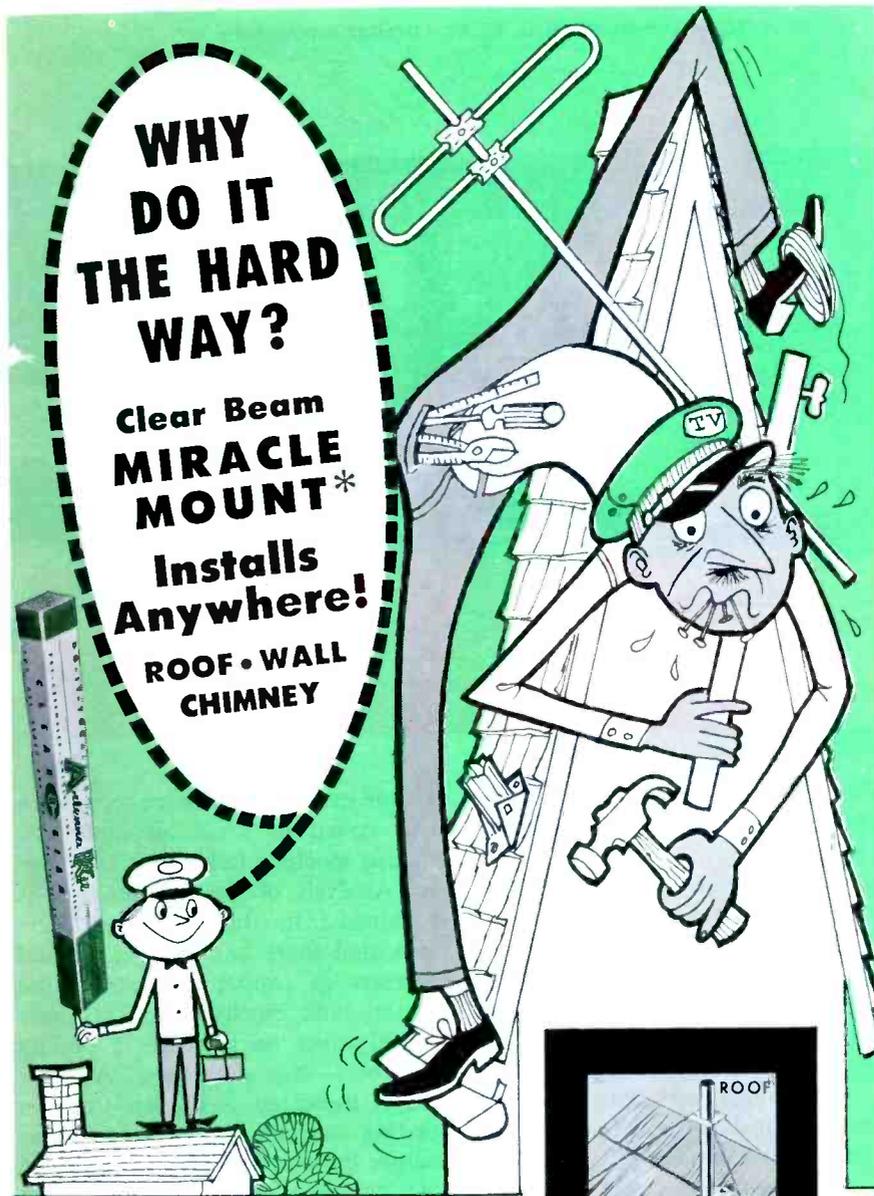If you thoroughly understand the major points of voltage- and power-amplifier operation presented here, you should have no trouble in locating and repairing any troubles that might be encountered in either circuit—providing you stop, analyze the symptoms, and think about how the circuit operates. ▲



***MIRACLE MOUNT COMPLETE ANTENNA KITS**


Clear Beam new Miracle Mount Antenna Kits install anywhere, allow you to pick the best, fastest and easiest to reach installation site on any home.

MOUNTS ON ROOF, WALL OR CHIMNEY

Everything you need for all types of installations in one complete low cost antenna kit which mounts anywhere... roof, wall or chimney.

LESS STOCK, MORE PROFIT

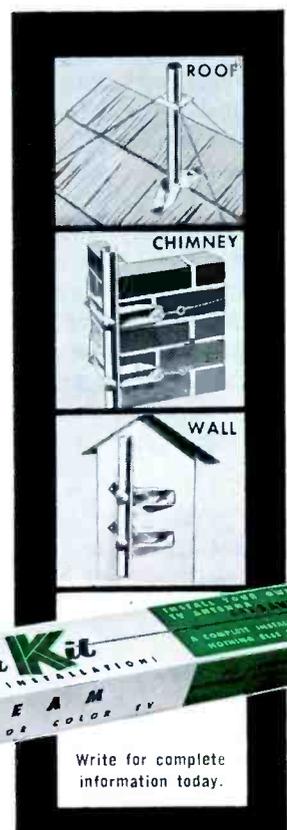Carry Clear Beam Miracle Mount Antenna Kits with you on all service calls and be ready for any type of installation job. Install as service or sell outright to Do-It-Yourselfers. You stock less, sell more with customer approved Clear Beam Kits.



Write for complete information today.

CLEAR BEAM ANTENNA CORPORATION
21341 Roscoe Boulevard • Canoga Park, California



The writing on the wall

"When did the pump stop?"
"What caused the improper chemical mixture?"
"How much does the temperature vary over an 8 hour period?"

The answers to these questions are vital to maintenance men in today's industrial plants, and are provided by the tireless vigilance of graphic recorders. Transducers which convert mechanical variations into an electrical signal are coupled to electro-mechanical devices that record the variations on ruled graph paper. Part of the value of graphic records is that they are always available for review; thus, a technician may determine the exact time of a breakdown. When several recorders are used to monitor different variable properties within one system, they may also be used to isolate the probable source of trouble.

For example, a service technician was called in when an automatic plating machine failed to plate evenly. Analysis of the various graphs obtained from the system recorders indicated there had been a gradual increase in copper sulphate in the plating-tank electrolyte. This alone would cause an increase in plating thickness—not a decrease. Another graph indicated a sudden drop in plating current about ten minutes before the inspector had stopped the plating operation. A graph from the voltage-monitoring recorder clearly established that the voltage had increased at the same time the current decreased. This information eliminated the power supply and electrolyte concentrate feeders as possible sources of trouble. Armed with the facts obtained from all the graphs, the technician checked the electrical connections leading from

the tank to the power supply. One high-resistance connection, caused by a loose bolt which led to subsequent corrosion, was found in the negative return cable. The technician cleaned the connection and replaced the bolt to complete the repair.

BY MELVIN WHITMER

Pen Positioners

Within each of the groups of pen-positioning mechanisms, there is a wide variety of specific devices. The technician should understand how the recorder operates because it is, for his purposes, a piece of test equipment. He is rarely called upon to service the recorders, but systems analysis is simplified by making use of the permanent records available from these instruments.

Electric Meter Positioners

The type of meter movement used in recorders depends on the input signal. Most DC recorders use a

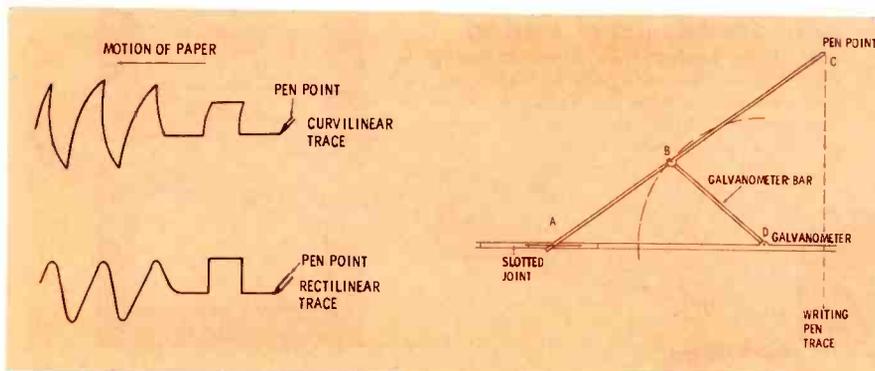


Fig. 1. Difference in appearance of curvilinear and rectilinear patterns.

Fig. 2. Mechanical linkage used to provide rectilinear recorder trace pattern.

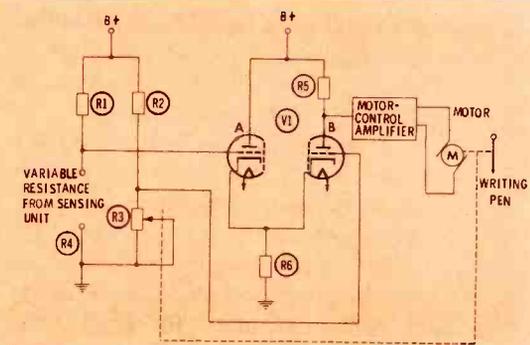


Fig. 3. Diagram of the potentiometer type DC null-balance recorder circuit.

galvanometer, while AC recorders use either vane-type meters for voltage readings or wattmeters as power indicators.

Galvanometers are more common, since most production variables can be readily converted into DC voltages; AC voltage measurements commonly pertain to power sources only. The galvanometer is a moving coil placed in the gap of a horseshoe magnet. Current in the coil generates a magnetic force which moves the coil, and therefore the pen, by pushing against the permanent magnetic field.

Recording is accomplished by a flow of ink, heating of temperature-sensitive paper, completing a circuit through electro-sensitive paper, scribing on blackened or pressure-sensitive paper, or applying pressure to the latter type of paper by means of an actuating bar.

Although the recording pen moves from side to side in response to input signals, it does not travel backward and forward over the paper. The trace is produced by moving the paper underneath the pen at a steady rate.

When the pen is connected directly to the moving coil, side-to-side motion produces a curved trace—as though the pen were the “business end” of a pair of compasses. The resulting *curvilinear* trace is shown in Fig. 1A. To produce a *rectilinear* pattern which is more nearly like a conventional oscilloscope trace (Fig. 1B), a mechanical linkage can be employed as illustrated in Fig. 2.

The outer end of the pen rides in a slotted joint at A. Attached to pivot point B on the pen shaft is a bar connected to the moving coil of galvanometer D. As the coil is turned, pen tip C is driven by the



"OFFHAND, MADAM, I'D SAY YOU NEED A NEW NEEDLE"

Farfetched? Well, perhaps. But what a worn-out needle can do to fine discs — to say nothing of those expensive stereo platters — shouldn't happen to a dog. So be a No. 1 Hero — tell the uninformed the Webster Stereo-Ceramic cartridge not only plays the new stereos but standard LP's and 78's as well . . . plays them better than they've ever heard before. Recommend and install Websters every chance you get. They're satisfying — and profitable, too.



see it at your jobber —
NEW WEBSTER SERVICE CENTER

A new way to serve you better. Quick-reference replacement chart and display-stock case mean faster service, accurate replacement for nearly every phono cartridge.

ELECTRONICS DIVISION
WEBSTER  ELECTRIC
our  th year RACINE · WIS

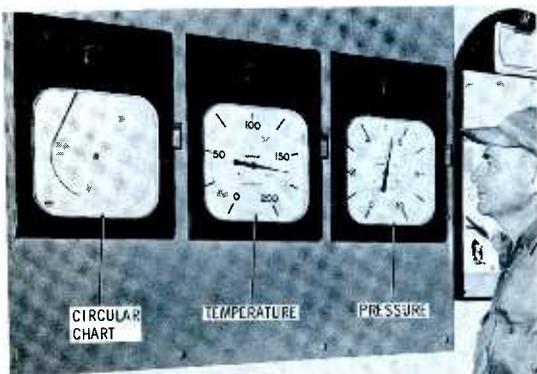


Fig. 4. Bristol recorder that indicates conditions at a station 30 miles away.

DON'T GUESS . . .

KNOW THE TEMPERATURE OF YOUR SOLDERING GUN BEFORE TOUCHING PRINTED CIRCUITS AND LAMINATED WIRING BOARDS!



ESICO GUNCHOKE®

REDUCES TEMPERATURE OF YOUR SOLDERING GUN TO TWO CONSTANT HEATS - 500° OR 600°

- Assures correct temperature for soldering printed circuits and laminated wiring boards.
- No need to wait for a slow-heating iron — and still have doubtful temperature.
- Just plug into GUNCHOKE and GUNCHOKE into outlet.
- Small, compact, to fit in your tool kit.

FOR ALL WIDELY USED GUNS
Get GUNCHOKE from your distributor

ESICO

LUGER GUN

Perfect balance permits delicate touch for most intricate work. Transformer built in handle eliminates tip heaviness. Long, thin tips simplify soldering connections inaccessible with other guns. LUGER is 150-watt capacity.

ELECTRIC SOLDERING IRON CO., INC.
559 W. Elm Street DEEP RIVER, CONN.

BERNS PERFECT PIN-CRIMPER

Picture-Tube Repair Tool

Eliminates that hard soldering job.

only \$1.25



Patent 2,878,698

Fix loose pin connections in seconds. Pays for itself in time saved on one job alone. 3" long.

Intermittent operation of picture tubes due to defective solder connections at socket pins is easily corrected through the use of the Berns Perfect Pin Crimper. Actually a 3-in-1 tool that can also be used as a channel-selector wrench and screwdriver, it serves to notch pins and element leads to provide solid electrical connections. Pin keeps its original form.

IT'S DANDY . . . IT'S HANDY
"you'll like it"

Available at your parts distributor.
Another fine product from:

BERNS Mfg. Co.
9853 Chalmers,
Detroit 13, Mich

action of the galvanometer bar and the writing arm.

Null-Balance Recorders

A second basic type of pen positioner, used in null-balance recorders, relies on a voltage-divider network, an amplifier, and a power-drive unit. Fig. 3 shows the potentiometer version of a DC system. The process variable to be recorded is transformed to a resistance change in a voltage divider (R_4 in Fig. 3). The resultant increase or decrease in the grid voltage of V_{1A} is cathode-coupled through V_{1B} to the motor-control amplifier. As the motor responds to the amplifier output voltage, it changes the position of the writing pen and also, through a mechanical linkage, the value of R_3 . Since resistors R_2 and R_3 form a voltage divider, the voltage at the grid of V_{1B} will increase or decrease until the current through V_{1B} is restored to the original value. The motor-control amplifier voltages will thus revert to normal, and the motor will stop, leaving the pen in a new position on the graph.

An AC bridge null-balance system is similar, except capacitors are used in the voltage dividers, and the amplifier is AC rather than DC coupled.

Other balance circuits use oscillator frequency changes and a discriminator, differential transformer, and photo-electric movements. However, these circuits are not as widely used as those in galvanometer or potentiometer-type recorders.

The null-balance system is particularly useful as a part of an automatically controlled process. Most power-drive units have enough torque to control other factors in addition to the positioning of the recorder pen—for example, corrective signals to compensate for process variations. Open and closed loop controls using null-balance recorders are the subject of a later installment, which will include a description of combination recorders and control units.

Recorder Charts

As mentioned previously, chart tracings are obtained in a number of ways. Ink is most frequently used on circular charts which, in operation, could be compared to phonograph records without grooves. The writing



Fig. 5. Strip-chart device that records and corrects temperature variations.

pen is positioned by a galvanometer, and contains enough ink to record during one revolution of the chart. One revolution may take 1, 4, 8, or 24 hours, depending on the expected rate of change in the factor to be recorded. On the 24-hour chart, radial divisions mark off 15-minute intervals, while circular divisions identify incremental changes in the sensed variable. Such a chart is useful for recording slowly-changing variables or maintaining day-to-day records, but greater accuracy is provided with faster revolution speeds.

In Fig. 4, a 24-hour circular recorder is shown as part of a remote indicating panel. Conditions at a pumping station 35 miles away are observed from this point. The recorder pinpoints the exact time of any changes, and in case of breakdown, assists in isolating the probable cause.

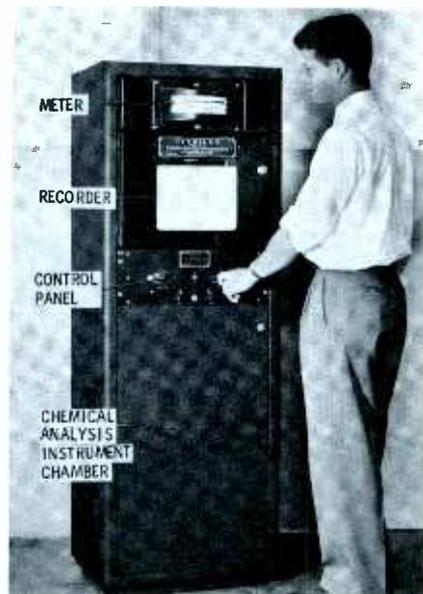


Fig. 6. This "Titrilog" recorder senses and controls chemical mixture balance.

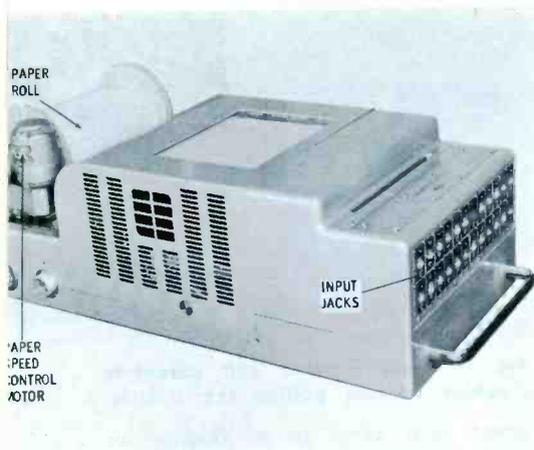


Fig. 7. Century Electrograph for airborne use handles 12 signals at a time.

Strip-chart recorders use rectangular graph paper, which moves under the recorder pen from a roll. Speed of the graph paper is measured in inches per second, and is usually adjustable to fit the input signal characteristics. The length of time a strip-chart recorder may operate unattended depends on paper speed and the size of the roll. Typical conditions allow four hours of continuous recording.

Application Examples

The actual means of recording on strip charts varies with application. Those most commonly used include pen and ink, current-sensitive paper and wire pen, light-sensitive paper and beam source, and temperature-sensitive paper and heated pen.

Fig. 5 shows a unit that records temperature deviations from a desired value. A thermocouple sensor provides an output voltage that changes with temperature. The desired temperature is preset by establishing a fixed reference voltage for comparison. The comparison-circuit output is applied to a galvanometer and controls the position of the pen.

Another use for a strip-chart recorder is shown in Fig. 6. Chemical solutions are often required to be neutral, i.e., neither caustic (like bleaches) nor acid. For instance, modern detergents and cleaners are advertised as being mild to hands, a factor that depends on the neutrality of the chemicals they contain. During the manufacturing of such products, the chemical neutrality is measured by devices like the one in Fig. 6. The recorder section is a

standard galvanometer strip-chart recorder.

Oscillographs

Oscillographs are wide-range instruments which use the strip-chart principle. Such units are not generally used in industrial process-control systems because chart speed and frequency response are not suitable. Fig. 7 shows an oscillograph designed for airborne operation. Notice that it has several input jacks, denoting multiple channels for recording many variables at one time. Galvanometer-type movements are most

often used because of their fast response characteristics.

The recorder is a precision instrument and should be calibrated by the manufacturer. Field service consists of cleaning and oiling (or other lubrication) or changing tubes. A recorder's usefulness as a means of rapid trouble analysis is of greatest importance to the technician.

Additional features of recorders, especially the null-balance system, will be described along with open and closed loop systems in the January issue. ▲

HICKOK

automatic tube tester,
transistor and diode checker

121

**EXCLUSIVE
UNIQUE
MODERN**

A new concept in tube testing . . .

Now, in 8 to 12 seconds you can make Tube Handbook tests on any tube, including pulse amplifiers, multi-vibrators, dampers and rectifiers. . . . Yes, for the first time you can accurately test such types as the 6BQ6 and 6SN7. This tester uses the time proven, Hickok-developed Gm test . . . plus, tube cut-off, saturation (zero bias) and the important and critical "fringe" evaluations for gas, grid emission, shorts and inter-element leakage. Never before has there been a tube tester so accurate, so complete and so easy to operate.

\$299.50

Ask your distributor for a "Hickok-demonstration".

The world's most complete line of quality tube testers.

Priced from \$99.50 to \$499.50.

THE HICKOK ELECTRICAL INSTRUMENT CO. 10514 Dupont Ave. Cleveland 8, Ohio

GREATEST NAME IN TESTERS

Dynamic Horizontal Sweep Tester

Have you ever stopped to wonder how many TV sets with horizontal sweep or high-voltage troubles cross the service bench each year? We don't know the exact figure, but it certainly must be a phenomenal number. Wouldn't it be simple in these cases if we could isolate trouble without pulling the chassis, removing a printed board, or unsoldering a slew of parts? The *Pioneer 250*, shown in use in Fig. 1, is designed expressly with this in mind. The instrument is manufactured by Doss Electronic Research, Inc., of Kansas City, Mo., and is identified as the Horizontal Sweep *Quantalyst*.

Specifications are:

1. *Power Requirements*—two self-contained 1.5-volt batteries for resistance measurements, replaceable with size AA penlight cells.
2. *Dynamic Tests*—checks of B+, boost, and output-tube screen and cathode voltages; substitution of output-tube screen and cathode bypass capacitors; measurement of output-and damper-tube heater voltages, horizontal AC drive, oscillator frequency, gas or grid emission in output tube, B+ ripple, cathode current of output tube; tests yoke and flyback for opens and shorts, yoke to flyback match, and yoke inductance.
3. *Static Tests*—ohmmeter measurements of output cathode and screen resistances, resistance between boost supply and common negative, and resistance between boost and B+.
4. *External Voltmeter*—two DC ranges 0 to 100 volts and 0 to 1000 volts, sensitivity 10,000 ohms/volt; AC range 0 to 150 volts (rms), sensitivity 2000 ohms/volt.
5. *External Ohmmeter* — three ranges 0 to 1000, 0 to 50K, and 0 to 500K; zero-ohms adjustment provided.
6. *Panel Features*—3" meter with

eight scales for ohms, DCV, ACV, AC drive, cathode ma, gas, and DC drive functions; six neon bulbs individually indicate presence of B+ or boost, open heaters, output-tube shorts, and flyback type; three test leads, two adapter cables, and plastic carrying bag supplied; accessory cables for uncommon tube types available.

7. *Size and Weight*—12½" x 7" x 4¾"; 7 lbs. complete.

From personal experiences in the lab, I found that this new Doss instrument can be used to troubleshoot a horizontal sweep circuit in "jig" time, and with very little effort on the part of the operator. The *Pioneer 250* automatically selects in-circuit test points, and indicates pertinent resistance, current, and voltage values on various scales of its built-in meter. Basically, it accomplishes all of this through the use of eight switches and three panel controls, plus a separate 17-position inductance selector.

The uniqueness of the instrument lies in the fact that it has special tube-socket adapters which plug into the horizontal output and damper stages of the set to be serviced (Fig. 2A). Two cables are supplied — each with a socket adapter on one end and a plug for connection to the instrument on the other (Fig. 2B).

The cables supplied can be used for all except output tubes of the 6AU5 and 6AV5 type, or miniature dampers such as the 6V3 and 6AF3. Adapter cables for these and other less common tube types are available from the manufacturer.

About the easiest way to understand the instrument's theory of operation is to follow through the step-by-step procedures discussed in the manual (also outlined in chart form inside the detachable lid). Before proceeding with the first step, however, a ground lead must be connected from the 250 to the chassis or common negative point of the set. (This connection is in addition to the regular cables.) The switch labeled

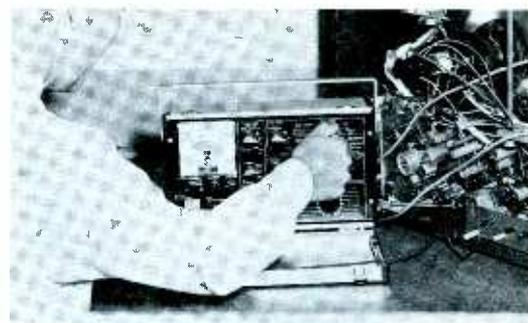


Fig. 1. Doss Pioneer 250 pinpoints troubles without pulling the chassis.

HORIZ. AMP. TYPE, located directly below the panel meter, must also be placed in its proper position. This switch has only two positions — one for tube types BQ6, CU6, DQ6, etc., and the other for types BG6, CD6, DN6, etc. In addition, the meter should be zeroed by pushing the OHMS CALIBRATE switch upward and adjusting the OHMS ZERO control.

The first four positions of the VOLTS/OHMS selector, found in the upper-right corner of the panel, are for ohmmeter measurements without power applied to the receiver. (See photo of front panel in Fig. 3.) In step number one, corresponding to selector-switch position #1, the resistance from the output-tube cathode to ground is automatically indicated on the 1K-ohm scale of the panel meter. If a resistor is used in the cathode circuit, its value is, of course, important to the proper operation of the sweep system.

In position #2, the screen resistor for the output tube is measured, and its ohms value shown on the 50K scale. I noticed that this check is made between output screen and plate of the damper tube (which is actually B+). In this step, one must make sure that the screen circuit returns to B+. If screen voltage is obtained from boost or any other source, this reading would be inconclusive. The test in position #7, however, will determine whether or not screen voltage is normal. Position #3 gives you a resistance reading between the boost supply line and common ground, while position #4 indicates any leakage path between boost and B+. These checks can quickly pinpoint a leaky boost filter, defective yoke, or shorted damper tube.

With the receiver turned on, the VOLTS/OHMS selector is then advanced to position #5, and B+ voltage is indicated on the 1000-volt DC scale. This measurement is made from damper plate to the cathode of the output tube. In selector position #6, boost voltage at the cathode of the damper tube is monitored, again using the output cathode as reference. It is interesting to note that a special stripping network is employed to protect the meter from any pulse voltages during both these tests.

In addition to measuring output screen voltage in position #7, the instrument simultaneously provides a substitute for the screen bypass capacitor. Position #8 measures output cathode voltage and also connects in a bypass substitute; therefore, if an original bypass is open, you


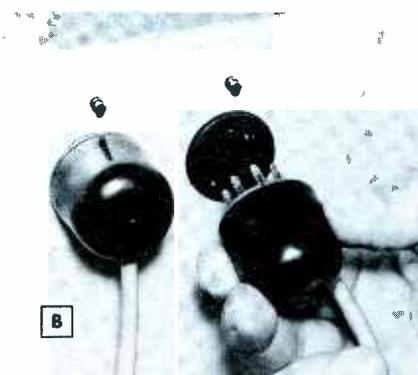


Fig. 2. Special adapter cables connect to (A) receiver, and (B) Doss unit.

CORNELL-DUBILIER CAPACITORS

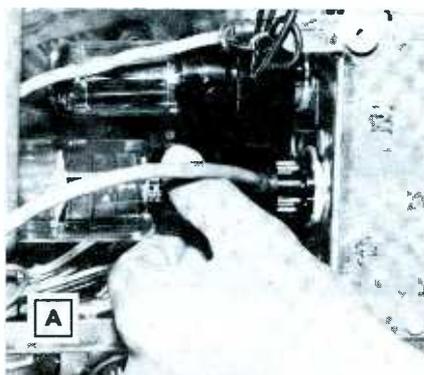

Fig 3. Model 250 switch positions follow a logical troubleshooting sequence.

should expect a change in set operation when the selector is moved to either of these two positions. Screen voltages are indicated on the 1000-volt scale, while cathode potentials are read on the 100-volt scale.

Voltage measurements are also obtained in positions #9 and #10, but from an rms scale calibrated with 6.3, 12.6, 17, 19, 25, and 30-volt markings. These two steps measure heater voltages for the horizontal output and damper tubes, respectively. An open heater is indicated by the glow of the neon bulb located directly below the associated number. You'll also find two positions not numbered on the selector switch. These are used for external voltage measurements and, incidentally, the selector should be placed in one of them for the remaining steps #11 through #19.

From Fig. 3, you can see that the middle section of the front panel is devoted to horizontal oscillator tests. If you move the switch in this section up to position #11, the panel meter will indicate the AC drive on the grid of the output tube. The meter scale for this function is graduated in steps representing sufficient drive for the various 50- to 110-degree sweep circuits. With this same switch in #12 position, the oscillator frequency can be measured in cps. The dial to the right of the switch is rotated until the meter peaks, and the frequency is read directly from the dial markings.

The switch section at the top left of the panel is employed for steps 13 through 16, which include a gas and grid-emission test of the output tube, a measurement of DC drive or grid bias on the output stage, a test for the presence of AC ripple on the B+ line, and a measurement of cathode current for the output tube. A separate 300-ma scale is provided for this latter test.

In the next step, the horizontal yoke leads are disconnected, and the switch found in the lower left section of the panel is flipped up to position #17. A variable inductor is automatically substituted as a load on the flyback and, by rotating the INDUCT-O-GRAPH switch and monitoring cathode current, one can determine whether the flyback or yoke is defective. In a similar manner, only with the switch in position #18 and the use of external test leads, you can check



The extra values are "on the house"

Want more capacitor for your dollar? Here's how: Cornell-Dubilier has originated a "preferred-type" program on twist-prong electrolytics. Now, a relatively few types fill over 90% of all replacement requirements. You need less - to do more. Fewer types means improved production efficiency, lowered costs - savings to you. How is it done? Instead of producing hundreds of types with odd and critical capacitance and voltage ratings, each "preferred type" carries the highest value and rating called for in each category. In most cases you get more capacitor at lower cost - plus added safety factor, improved performance and "call-back" protection. It's on the house! To get more capacitor for your dollar, ask your C-D Distributor about Preferred Type Twist-Prong Electrolytics or write Cornell-Dubilier Electric Corporation, South Plainfield, New Jersey.



CORNELL-DUBILIER CAPACITORS

Consistently Dependable

NEW!

Acme Electric
TRANSFORMERS

AUTOMATIC VOLTAGE STABILIZER



Compact in size, attractive in appearance. This unit rated at 200 va has capacity large enough to accommodate television receivers up to 24". Operation is noiseless and completely automatic. Fluctuation of incoming voltage over a range from 95 to 130 volts is automatically corrected ($\pm 2\%$) within 1/30th second when operated within its normal rated capacity of 200 va.

When TV set is turned off, a built-in relay automatically disconnects primary circuit, thus stopping coil magnetism. When TV set is turned on, relay automatically connects primary circuit.

Furnished complete with heavy duty primary cord and built in secondary receptacle.

Write for bulletin VA-322.

PO-3228

ACME ELECTRIC CORPORATION
9411 Water Street Cuba, N.Y.

the flyback-to-yoke inductance match. Step #19 is an actual measurement to determine yoke inductance. Here, too, the built-in variable inductor and peaking indications of the meter are used. This feature can also be of value in measuring other inductors as long as they fall within the 4- to 36-millihenry range of the INDUCT-O-GRAPH.

Although you may locate a trouble without going through the entire procedure, I found that I could complete all of the above tests in about ten minutes,

whereas a serviceman might normally take an hour or more by using conventional techniques. The nature of the trouble encountered may warrant variations in the order of test; however, you should find that this step-by-step procedure works very well for most practical cases. In the back of the Doss instruction manual, you'll find a list of normal and maximum cathode currents for most output tubes, as well as several hints on servicing the horizontal sweep system.

Push-Button Tube Checker

The Jackson Electrical Instrument Co. of Dayton, Ohio, is currently marketing the Model 648R Dynamic Tube Tester, featuring a keyboard switch bank and top-view roll chart (see Fig. 4). As can be seen in the photo, this portable instrument comes in a leatherette-covered case with a complete set of operating instructions inside the detachable lid.

Specifications are:

1. *Power Requirements* — 110/125 volts, 50/60 cps; power consumption less than 5 watts in stand-by condition; line calibration switch graduated in 2.5-volt steps.
2. *Shorts Tests*—shorts and leakage indicated by glow of NE-51 neon bulb; panel control determines leakage sensitivity from 250K to 2 megohms; element selector switch provided.
3. *Dynamic Test*—special plate conductance test indicated in relative micromhos on 4½" panel meter; voltages applied to each tube element by individual push buttons; roll chart supplies setup data.
4. *Life Test*—heater voltage automatically reduced with all other parameters remaining constant; life expectancy indicated by reduction in plate conductance; special switch provided.
5. *CRT Test*—pictures tubes tested under normal receiving tube procedures by using accessory adapters.
6. *Panel Features* — 9 test sockets grouped on 4" x 4½" elevated panel, wired replacement kit avail-

able; 3-column roll chart; filament selector providing 23 positions from .75 to 100 volts.

7. *Size and Weight*—16¾" x 6¾" x 13¾"; 18½ lbs.

When I first opened the lid of the Model 648R, I'll have to admit that the double bank of push buttons gave me the impression that the instrument was rather involved and probably complicated to operate. After reading the instructions and actually checking a few tubes, however, I found that first impressions don't mean a thing. The setup procedure is simple and straightforward. I noticed, too, that the roll chart is up out of the way where your hands and arms don't hide it. As the manufacturer puts it, "The setup time of the tester is less than the warm-up time of the tube."

To familiarize you with this particular instrument, let's run through the steps necessary for checking a tube. The first step, after turning the tester on and adjusting the LINE CONTROL to compensate for variations in line voltage, is to locate the tube type on the roll chart. By the way, this three-windowed chart is arranged so that when you reach the bottom of the first column, you merely refer to the middle column and the next numerical-alphabetical designation appears. This also applies when going from the second column to the third, which naturally eliminates a lot of unnecessary thumbing of the roller.

After you make sure that all push buttons are in a neutral position by pressing the two release keys at the right end of the switch bank, you proceed by setting up the filament selector and plugging the

the D-400 Hi Leak Analyzer

MADE BY THE
DESIGNERS
OF THE
Pioneer 250

SEE YOUR
DISTRIBUTOR



\$1295
NET

capacitor tester
SAVES YOU TIME

■ An extremely sensitive instrument designed to quick-check bypass condensers for leakage or open conditions.

The D-400 utilizes the relaxation oscillator principle and supplies 100 volts DC for the purpose of testing. A built-in neon indicator makes testing fast and simple.

Tests for leakage up to 500 megohms in any capacitor within the range of 0 to 1.0 MFD. Also ideal for testing filament continuity, etc.

DOSS

ELECTRONIC RESEARCH, Inc.—820 Baltimore • Kansas City, Mo.

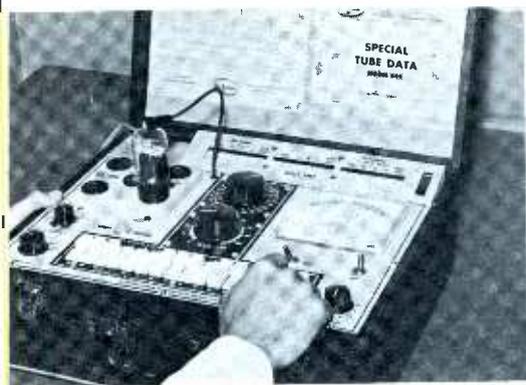


Fig. 4. Jackson 648R plate-conductance tester features special life test.

tube into the proper test socket. Incidentally, the 23 positions of the filament selector are not merely numbered or designated by alphabetical letters, but are identified by actual heater-voltage values.

In the next step, you set up the buttons in both top and bottom rows, which are referred to as circuits D and E. With this completed, the shorts-leakage test is next in order; however, I found it more convenient at this point to go ahead and adjust the PLATE control for the conductance test while the tube is still warming up.

The shorts test is performed by rotating the SHORTS TEST switch (located in the lower-left corner of the panel) through its four tube-element positions. During this check, the leakage control directly above the switch should be in the extreme clockwise position, thus making the circuit more sensitive to high-resistance shorts. Approximate leakage values can be determined by slowly rotating the control counterclockwise until the neon short bulb is extinguished. The leakage control is calibrated from 250K to 2 megohms.

If the tube passes this test, you can proceed with the quality test by placing the SHORTS TEST switch in its TEST position and then depressing the button or buttons designated on the roll chart under PLATE TEST. The panel meter will evaluate the tube immediately. Although the reading is considered to be a relative micromho indication, the meter is calibrated in bad, good, and questionable areas, as well as on a linear percentage scale (see Fig. 5).

An excessive reading classifies a tube as questionable, which indicates that it may be gassy, or have damaged or misplaced



Fig. 5. Note that the "Q" area is located at extreme right end of the scale.

the BIG SWITCH



is to **MINIATURIZED**

ELMENCO

dipped mylar*-paper capacitors

The revolutionary **LOW COST** capacitor that puts an end to "Call-Backs"

RELIABILITY . . . Elenco dp Mylar[®]-Paper Capacitors have achieved a reliability that meet missile and computer requirements. They are thoroughly and continually tested during production to insure outstanding performance. For example a 0.1 mfd. dp capacitor operated at full rated voltage and at 105° C will have a life expectancy of more than 5,000,000 unit hours.

MOISTURE-PROOF . . . Elenco dp Capacitors are specially processed and vacuum dipped to obtain solid impregnation and a rugged moisture-proof coat designed to withstand *4 times more humidity* than the best molded capacitors used in the past.

MINIATURIZED . . . These capacitors are 50% smaller than other brands and can be used in printed circuit and transistor application. Thousands of service technicians are switching to Elenco dp quality Capacitors. Why not see your Arco distributor today and get the best.

dp 5-PAKS . . . Look for the ARCO dp 5-PAK on the big blue and yellow display rack. Each value packed 5 to a 5-PAK in transparent bag for your convenience.

For full information write for Bulletin P-11

ARCO *electronics inc.*

* Dupont Trademark

64 White St., New York 13, N. Y. • Branches: Los Angeles 35 • Dallas 19

Sylvania Audio-Power Transistors



Here are two problems you won't have to face when you replace with Sylvania

Problem No. 1:

Which type replaces which?

Sylvania has the most complete line available. And your Sylvania distributor has them in stock. The full line listed here equips you to replace the output transistors of every major auto-radio make. To make your job easier, Sylvania has prepared an interchangeability chart—available from your Sylvania Distributor.

Sylvania's Auto-radio Transistor line

2N155	2N242	2N296	2N350	2N677
2N176	2N250	2N301	2N351	2N677A
2N235	2N255	2N301A	2N399	2N677B
2N235A	2N256	2N307	2N401	2N677C
2N235B	2N257	2N307A	2N419	2N678
2N236B	2N285A	2N326	2N420	2N678A

Problem No. 2:

The broken mica washer

More often than not the mica washer flakes when you remove the output transistor from the auto radio chassis. To save you time and money, Sylvania now packs a tight-fitting mica washer with every transistor. Next time you need an audio power transistor—get it from your Sylvania distributor and ask for Sylvania by name.



SYLVANIA ELECTRIC PRODUCTS INC.
Semiconductor Division
100 Sylvan Road, Woburn, Mass.



Fig. 6. To change roll chart, remove screw from back of case and lift out.

elements. (On the other hand, it may merely indicate an exceptionally "hot" tube.) By testing a number of known defective tubes in the Model 648R, I found that gassy amplifiers always produced readings somewhere above the 120% mark. In cases where the readings were between 120 and 130%, I discovered that the gas content was not necessarily sufficient to produce a trouble symptom. Tubes having enough gas to produce troubles, however, always registered in the questionable area.

If you can't seem to pinpoint an apparent tube trouble, yet suspect low line voltage as the basic cause, the special LIFE TEST afforded by the Jackson tester may help you solve the problem completely. To perform this test, you merely check plate conductance in the prescribed manner and, while holding down the test button or buttons, flip the LIFE TEST switch to its TEST position. The switch is a spring return type located directly below the panel meter; when held in its test position, filament or heater voltage is automatically reduced, while all other test voltages remain constant. Tubes with sufficient cathode coating will show little change in conductance under this condition; however, those on their last legs will cause the reading to drop considerably.

When I checked a 12BE6 converter tube that appeared to be causing drift in a radio, I noted that it passed both the shorts and quality tests of the Model 648R. However, in the life test, conductance of the pentode section dropped sharply from good to bad.

I also noticed that the gassy tubes I tested had more of a tendency to resist change in conductance under the life test. The best way to gain usable and concrete

information from the life test function of the Model 648R is to familiarize yourself with both the normal and abnormal readings obtained from known high quality tubes, and those that are weak or that you suspect are approaching the end of their useful life.

Another desirable feature of this instrument is its easy-to-remove roll chart. As shown in Fig. 6, the roller assembly can be taken out by removing only one screw located on the back of the case. Obsolete and seldom-used tubes have been omitted from the chart, but can be found in a tube data booklet which is stapled to the lid of the tester.

VOM Features Accuracy

Ohm's law involves only three inter-related terms—voltage, resistance, and current. In all fields from design to maintenance, all types of instruments have been developed for measuring their values.

A recent contribution to this category of instruments is the Model 270 VOM manufactured by Simpson Electric Co. of Chicago. Pictured in Fig. 7, the unit features a high degree of accuracy, is housed in a heavy black bakelite case, and comes complete with two 4' test leads and batteries.

Specifications are:

1. *Power Requirements* — five self-contained 1.5-volt batteries, one size D and four size Z flashlight cells.
2. *DC Voltmeter*—seven ranges of 0 to .25, 2.5, 10, 50, 250, 1000, and 5000 volts; sensitivity 20,000 ohms/volt; accuracy to 1000V $\pm 1.5\%$ of full scale at 77°F. $\pm 2\%$ within 10° variation; polarity switch provided.
3. *AC Voltmeter*—six rms ranges of 0 to 2.5, 10, 50, 250, 1000, and 5000 volts; sensitivity 5,000 ohms/volt; accuracy to 1000V $\pm 2\%$ of full scale at 77°F, $\pm 3\%$ within 10° variation; frequency response essentially flat to 30 kc, within 0.5 db to 200 kc on lower ranges.
4. *AF/db Meter*—AF output ranges

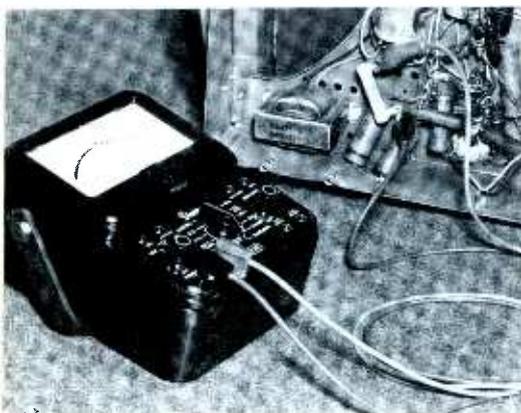


Fig. 7. Carrying handle supports 270 VOM in convenient sloping position.

Got a bee in your bonnet
about Ceramic Capacitors?

These **Centralab**

Hi-Kap® Kits

are real honeys!



You've got a real sweet deal with CENTRALAB Ceramic Capacitor Kits . . . and there's no sting to the prices—especially when you get the \$4.75 cabinet FREE with each kit!

So that you'll always "bee" prepared, these heavy gauge steel kits contain balanced inventories of the most frequently used values. Individual values are prominently and clearly labelled so you can locate the Hi-Kap you need, instantly. The rigid plastic package permanently separates and protects the units—yet is easily opened to remove a single capacitor.

So give your distributor a buzz right now, and ask him about these four honeys:

- DDK-200 kit—200 Standard Ceramic Disc Hi-Kaps—\$31.10 net
- TCK-80 kit—80 TC (Temperature Compensating) Hi-Kaps—\$26.90 net
- HVK-150 kit—150 High Voltage Disc Hi-Kaps—\$38.60 net
- D6K-200 kit—200 Tubular Ceramic BC Hi-Kaps—\$33.20 net

. . . and be sure to ask for a free copy of the new CENTRALAB catalog, or write direct to CENTRALAB for it.

Centralab
D-5952

A DIVISION OF GLOBE-UNION INC.
942K E. KEEFE AVE. • MILWAUKEE 1, WIS.
IN CANADA: 669 Bayview Ave. • Toronto 17, Ont.

CONTROLS • ROTARY SWITCHES • CERAMIC CAPACITORS
PACKAGED ELECTRONIC CIRCUITS • ENGINEERED CERAMICS



TACO TV ANTENNAS

...For your good! Nothing spells customer satisfaction as much as performance—and that's exactly what a Taco antenna provides. For more years than any other antenna manufacturer, Taco has provided the TV technician with the antennas best suited for all reception requirements. Try one on that next installation and see for yourself...

WRITE FOR COMPLETE TACO TV-FM-AMATEUR CATALOG.

TECHNICAL APPLIANCE CORPORATION, Sherburne, N. Y.

0 to 2.5, 10, 50, and 250 volts; power level ranges from -20 to +10 db, -8 to +22 db, +6 to +36 db, and +20 to +50 db, zero db = 1 milliwatt of AC power across a 600-ohm impedance; separate jack with blocking capacitor provided.

5. Ohmmeter—0 to 20 megohms in three ranges of R X 1 (center scale 12), R X 100, and R X 10,000; accuracy $\pm 1.5^\circ$ of scale arc at 77°F, $\pm 2^\circ$ within 10° variation; zero-ohms adjust provided on panel.

6. DC Ammeter—six ranges of 0 to 50 ua, 1 ma, 10 ma, 100 ma, and 10 amps; accuracy $\pm 1.5\%$ of full scale at 77°F, $\pm 2\%$ within 10° variation; separate panel jacks provided for 50-ua and 10-amp ranges.

7. Meter Accessories—two high-voltage probes for 25 kv and 50 kv measurements; leather or plastic carrying cases also available.

8. Size and Weight—5¼" x 7" x 3⅞"; 3¼ lbs.

This unit differs from its predecessor, the 260, in that it possesses greater accuracy, and features a mirrored wide-angle scale with a special knife-edged pointer. In the lab, I removed the meter chassis from its case, and surmised that its accuracy is directly related to the ½% precision resistors, a frictionless 50-ua meter movement, and the other high-quality components used in the construction of the instrument.

From the photo in Fig. 8, you can see that almost all chassis wiring is confined to a single printed board. The wirewound and deposited-carbon resistors positioned on top of the board are all identified by R numbers etched right on the board. These numbers correspond to the identification given in the instrument's parts list and on the schematic.

In the lower-right corner of the board, laying across the function switch, you'll find a pigtail fuse soldered in series with the common test jack. This 1-amp unit protects the instrument from damage due to misuse during ohmmeter and millimeter functions. The range switch, located in the center of the front panel, can be rotated in either direction through all twelve of its positions. Also on the front

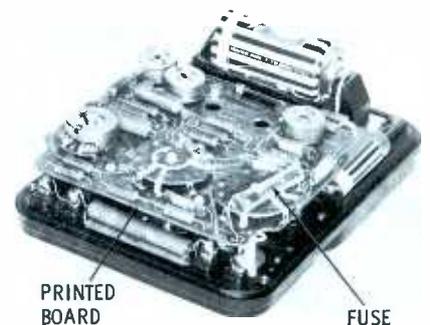


Fig. 8. Simpson 270 chassis comes out of case after removing only four screws.

ask the
"Man-on-the-Roof"
why he prefers
South River



TWO
TO A
SET

RATCHET TYPE CHIMNEY MOUNT


Model RT (Galv. Banding)
Model RT-ST
(Stainless Banding)

FASTEST, SIMPLEST, MOST
CONVENIENT EVER MANU-
FACTURED — Mounts in 2
simple steps. Completely fac-
tory assembled with no eye-
bolts, banding clips, nuts, etc.,
to handle. Furnished with
flat-lay, non-coiling banding,
heavy gauge embossed, welded
steel construction. Forged
heat treated Alum. ratchets.

SOUTH RIVER
METAL PRODUCTS CO., INC.
South River, New Jersey

pioneer &
outstanding
producer of
finest line
of antenna
mounts

Canada: Lea Finkler & Co., Toronto

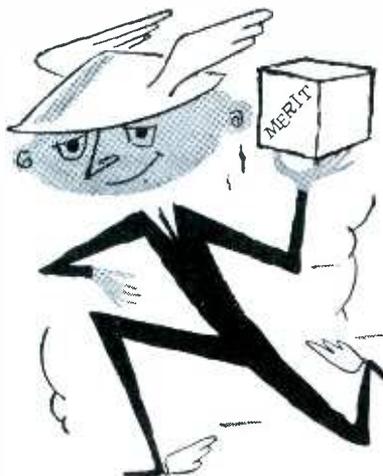

QUICK-SILVER FOR YOU... MERCURY FOR US

Merit shipments to all parts of the United States are jet-fast, and sure as sunrise. Mercury, the mythical god, would be pleased.

MERIT CONSISTENT QUALITY
PLUS FAST DELIVERY MEANS
QUICK-SILVER FOR YOU...
EXTRA-DOLLARS AND
BIGGER PROFITS.



COMPARE IT WITH
MERIT
MERIT COIL AND TRANSFORMER CORP
MERIT PLAZA . HOLLYWOOD, FLORIDA

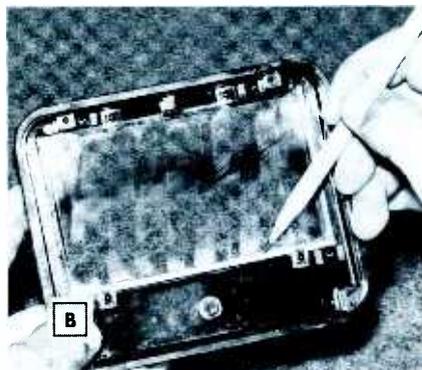
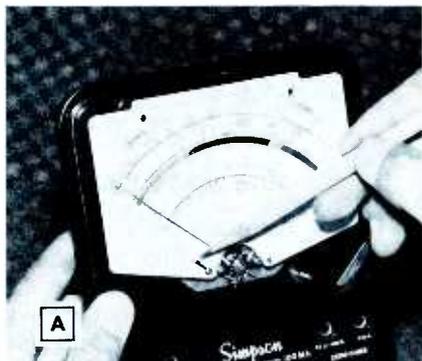


Fig. 9. This feature of the Simpson VOM presents static charge build-up.

panel, you'll find eight separate test jacks—two in each corner. Aside from the two labeled *COMMON* and *+*, these jacks are used for extended ranges or functions of the instrument.

The 4½" meter face has five calibrated arcs with a narrow mirror strip across the center. When I removed the protective frame from the front of the meter, I noticed a small piece of spring metal protruding from the base of the dial (see Fig. 9A). After examining the frame assembly, I found that this piece makes contact with the strip of metal foil pointed out in Fig. 9B. This effectively eliminates a buildup of any electrostatic charge on the glass or frame surrounding the pointer and meter movement.

Applications of a VOM are, of course, numerous; however, I found the Model 270 of particular value in checking current drain and bias potentials in transistor radios, measuring critical AGC voltages in TV receivers, and when looking for slight circuit changes in stubborn intermittent cases. I also found the unit's accuracy useful in the calibration and troubleshooting of other test instruments.

Speaking of accuracy, I'd like to point out some factors you might not know about. For example, accuracy of meter movements are affected by ambient temperature, operating position, and external magnetic or electrostatic fields. Even the use of steel-clad batteries in the case can change the instrument's sensitivity by forming a magnetic shunt in close proximity to the movement!

Like the 260 series, the 270 will accommodate the new Simpson *Add-A-Testers*. These adapters plug right in and convert the meter into a number of different test instruments. I'll be reporting on them in a forthcoming issue. ▲


NEW!

JERROLD ANTENNA MIXING NETWORKS

MODEL TX-(*)

Give Multi-Channel, All-Direction Reception Simultaneously...for FM, TV, UHF and Color!

Now multi-set families can have all-direction reception at the same time on *one common line!* No more rotators or switches... the versatile Jerrold Model TX-(*) can be used individually or in any combination to reject unwanted channels and to bring in weaker stations bright and clear. They will mix cut-to-channel antennas with a single broad band antenna... separate individual channels... mix or separate VHF and UHF... and mix or separate VHF TV and FM... *all without loss of signal.*

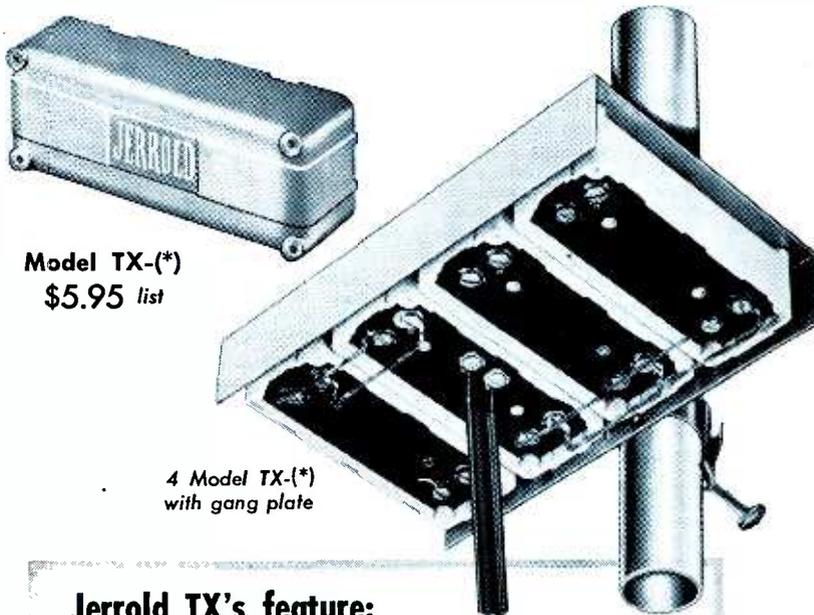

Model TX-(*)
\$5.95 list

4 Model TX-(*)
with gang plate

Jerrold TX's feature:

- up to 9 antennas on a single down lead
- high Q band-pass circuit for highest rejection
- negligible feed-thru loss... less than a knife switch
- matched mixing jumpers... for low VSWR
- unbreakable attractive housing, complete with hardware
- universal mounting... indoor or outdoor

*SPECIFY UNITS DESIRED: any TV channel from 2 through 13; FM; H-L (VHF high-low) or VHF-UHF

JERROLD

ELECTRONICS CORPORATION, Distributor Sales Division
Dept. PD 195, The Jerrold Building, Phila. 32, Pa.

Jerrold Electronics (Canada) Limited

Export Representative: CBS International, New York 22, N. Y.

LOOK TO JERROLD FOR AIDS TO BETTER TELEVIEWING

NEW IMPORTANT SAMS BOOKS



"Printed Circuit Diagnosis Made Easy"



Helps you become an expert in servicing printed circuit boards. Practical, simplified approach saves time troubleshooting all types of printed circuits. Explains correct way to interpret and use various styles of data shown in service literature. Describes best procedures to follow when only a schematic diagram is available.

Sample problems illustrate each phase of printed circuit troubleshooting. A "must" book for your service library. Illustrated; 64 pages; 5 1/2 x 8 1/2". Only..... **\$7.00**

"Radio Receiver Servicing"

ALL-NEW EDITION



Latest enlarged edition of John T. Frye's famous best-seller. Includes new chapter on how to service transistor radios and printed circuits. The most understandable and valuable guide to radio servicing; based on the author's 25 years of practical experience. Includes a separate chapter on each type

of trouble, such as the dead set; tubes light but no sound; noisy sets; weak sets; sets unable to separate stations, etc. 208 pages; 5 1/2 x 8 1/2". Only..... **\$2.95**

"Howard W. Sams Handbook of Electronic Tables and Formulas"

FOR ELECTRONIC TECHNICIANS

Specially prepared for electronic technicians, junior engineers and students. A valuable compilation of tables, charts, formulas and laws useful to all who work in electronics. Five comprehensive sections include: Formulas and Laws of Electronics; Constants, Standards, Symbols, Codes; Service and Installation Data; Mathematical Tables and Formulas; Miscellaneous.

Features full-color frequency spectrum chart based on latest 1959 FCC allocations. 134 pages; 5 1/2 x 8 1/2"; hard-cover. Only **\$2.95**

"Television Tube Location Guide" Vol. 9



Latest volume in this invaluable series. Gives tube location data for TV sets produced in 1958-1959. Shows position and function of tubes in over 250 receiver models—just find the trouble and replace defective tubes without removing chassis! Shows major component placement; signal path; pin orientation on socket;

series string filaments; fuse location. Includes tube failure check charts. 96 pages; 5 1/2 x 8 1/2"; comb binding. Only..... **\$1.25**

HOWARD W. SAMS & CO., INC.

Order from your Sams Distributor today, or mail to Howard W. Sams & Co., Inc., Dept. L-39 2201 E. 46th St., Indianapolis 6, Ind.

Send me the following books:

- "Printed Circuit Diagnosis Made Easy" (PC-1)
- "Radio Receiver Servicing" (RS-2)
- "Handbook of Electronic Tables" (HTF-1)
- "Television Tube Location Guide" Vol. 9 (TGL-9)

\$.....enclosed. Send Free Book List

Name.....

Address.....

City..... Zone..... State.....

(outside U.S.A. priced slightly higher)

TIPS

for TECHS




Put Flux in the Spool

Here's a handy hint for the radio-TV serviceman who likes to carry a can of paste flux in his tool kit. Instead of wasting valuable space, why not put the solder and flux into one container? After plugging one end of the solder spool with a cork, heat the can of flux in a pan of hot water and pour it into the core. When the flux cools, plug the open end with another cork. This arrangement is a space-saver, and you won't have to waste time hunting for your can of flux when it's needed.

Catch-All for Service Truck

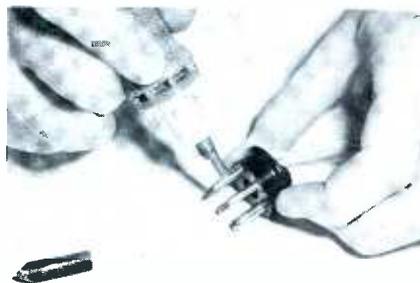A plastic shoe bag attached inside the service truck door comes in handy for holding a flashlight, often-used tools, parts, and other items. Fasten the bag in place with self-tapping screws and large round washers.



Sweat Soldering With Pencil Iron

When a pencil-type soldering iron is used for sweat soldering, you can convey more heat to the work by removing the tip and applying the end of the heating-element barrel directly to the work surface. This will result in maximum heat transmission and raise the work temperature in minimum time.

Hint for TV Line

If you maintain a TV line to subscribers, here is a hint you will find helpful. When you have to hunt down troubles at line amplifiers and line splitters after dark, it's often very hard to locate the poles on which these items are mounted. To make the task easier, put some automotive reflecting tape on each equipment housing. (You might even number the boxes in this way.) Just a dim flashlight beam will indicate the locations of the boxes, and let you hunt down troubles more speedily.

Fuse Inventory Control

Here's how you can keep track of fuses stored in "5-to-a-pack" boxes. You often find yourself pulling out empty boxes just when you badly need a fuse of some particular size. Prevent this by inverting nearly empty boxes in your caddy. The upside-down boxes will remind you to order a fresh supply of the values thus indicated.

Test For Speaker Rub

Ever wish for some quick and easy way to tell whether or not the distorted output from a speaker is due to voice-coil rub? Using your left hand, grasp the speaker by the edge of the field coil or PM magnet housing. Hold the speaker near your right ear and strike the back of the housing with your right hand. If the voice coil *isn't* making contact with the pole piece, you will hear a distinct *boing*. Otherwise, the speaker will give forth a muffled, rasping sound.

Bottles for Tool Kit Chemicals

Ask your wife to save you those sturdy glass nail polish bottles she usually discards. They make mighty handy service chemical containers for your tool box. One filled with solvent (or nail polish remover) will come in handy when you have to remove some enamel insulation from fine wire. A daub of the solvent or remover makes the job a cinch. Fill a second bottle with some extra soldering paste. Others filled with printed circuit paints will come in handy, too. They are practically unbreakable.



Keeping Test Leads Together

When several pairs of test leads are stored together, mates often become separated and much servicing time can be wasted sorting them out. To keep halves of a pair from becoming separated, fasten them together in the middle with a small compression spring as shown. This permits the leads to be separated quickly and easily should the need arise.



Sharpen Dull Screwdrivers!

Since Phillips screws are used almost universally in all kinds of electronics gear, it doesn't take long for one's Phillips screwdriver bits to become dull and develop burrs. Don't let these dull screwdrivers go unattended—dress the tip once in a while with a small triangular file. This will save time and temper in the long run, and will eliminate those unsightly, chewed-up screw heads that are the mark of an inexperienced serviceman.



Hook for Soldering Gun

A cup hook screwed into a small hole drilled into your soldering gun provides a convenient means of hanging it up when not in use. To insure that the hook doesn't pull loose, take the gun apart, and apply a blob of solder to the hook threads on the inside.

a vitally important message for every service technician

HOWARD W. SAMS
INDIANAPOLIS 6, INDIANA

Dear Friend:

Your Electronic Parts Distributor will soon present to you a remarkable new program designed to help you:

1. Gain deserved recognition as a reputable businessman in your community
2. Develop and command public respect and acceptance through favorable national and local publicity
3. Justify better earnings warranted by your business investment and skill
4. Pave the way to expanded business and increased profits for you

This program, known as "PEET", is made possible by a unique industry-wide relationship in which the Sams Company occupies a key position. Your Distributor will invite you to qualify for the program which has been planned solely in your behalf.

Please give your Distributor's representative the few minutes required for his presentation of "PEET." It may prove to be the most profitable time of your business career.

Some of you may already have been presented the "PEET" Program and you may be well on the way to qualify. I want to make certain *every* Service Technician is offered the opportunity—so—if you don't hear from your Distributor in the next few weeks, write to me personally. I will see to it you get the full details immediately.

Cordially,

**ASK YOUR ELECTRONIC
PARTS DISTRIBUTOR**

**QUALIFY FOR
"PEET"**

THE BIG NEWS FOR 1960

SYLVANIA 23-INCH TV




*Viewing area 275 square inches. 23-inch picture tube measured diagonally.

Big 23-inch* picture is the sensation of 1960 that *changes the face of television* . . . and Sylvania scoops the industry with the first complete line.

- Square corners of the 23-inch* bonded shield picture tube pioneered by Sylvania presents more of the TV picture as the camera sees it. New squared shape is closer to the 3 x 4 ratio of the true TV camera raster.
- The 23-inch* tube flattens the TV screen. "Bonded shield" face-panel eliminates the dust trap, cuts reflections in half, and improves brightness and contrast.
- ◆ New Super HaloLight® is bigger and better than ever. It's a Sylvania exclusive that adds eye comfort to eye appeal.

SYLVANIA 23" TV OFFERS THE NEWEST AND FINEST FEATURES YOU CAN RECOMMEND

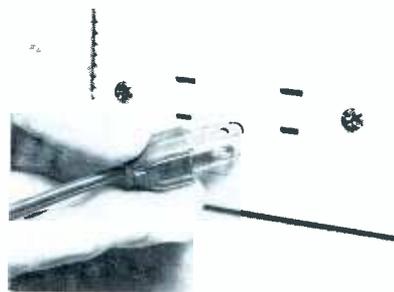SYLVANIA
Subsidiary of
GENERAL TELEPHONE & ELECTRONICS





Sure Way to Polarize a Plug

Modern receptacles for AC line plugs have one long and one short slot. The longer one is connected to the grounded side of the power line, if the receptacle has been correctly installed. (Double-check this by measuring voltage from each side of the line to the conduit box.) To take advantage of the safety features offered by this polarized receptacle, modify the line plug of AC-DC radios and other "shockable" equipment as shown. Solder a section of paper clip around the prong which connects to the common ground-return point (B— bus or chassis ground), as determined by actual measurement with an ohmmeter. (Thanks to Mr. Fred J. Ardalino, Brooklyn, N. Y., for this idea.)

Hang Test Leads on Tie Rack

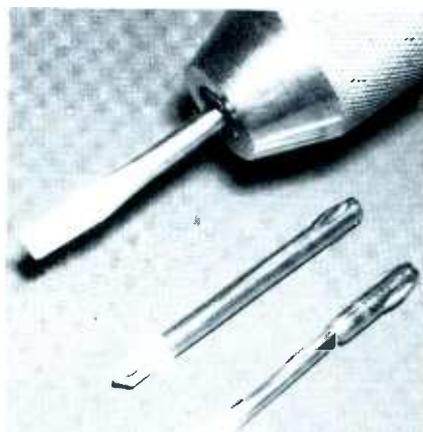Do you have a spare tie rack lying around the house somewhere? If so, hunt it up and convert it to a test-lead rack for the shop; it's practically made to order for the job. Attach it to the wall near your service bench.



Drill Overpowers Screw

Whenever you encounter a rusted screw that resists all efforts to remove it, just take the blade from an interchangeable screwdriver outfit and insert it into the chuck of your hand drill. You'll get more leverage, loosening the screw more quickly and with less effort.

Shop Talk

(Continued from page 24)

in one of the load circuits. Individual resistance measurements from each feed line to common ground may tell you which circuit is defective, or you can reconnect one line at a time and note the effect on B+ voltage. While each added line will cause the output voltage to drop slightly, a marked decrease will occur when the defective branch is hooked in. The procedure is slow, but there are no reliable shortcuts for this particular type of trouble. (However, if you are definitely sure the filter circuit is not leaky or shorted, you would save some time by disconnecting the load lines one by one, checking B+ voltages as you go.)

An interesting situation, low voltage in only *part* of the B+ system, can occur in those receivers where the audio output tube serves also as a voltage-dropping element (see Fig. 3). Voltage in the power supply itself may be normal, but the voltage on those stages which receive B+ from the cathode of the audio output tube can be low, or even nonexistent. If replacement of the tube fails to cure the low-voltage condition, one of the load circuits may be causing excessive current drain. Disconnect each one individually, check the audio-output cathode voltage, and reconnect the load circuit if the reading hasn't returned to normal. Don't forget the filter capacitors connected to the cathode! Avoid disconnecting several load circuits at once, since this will result in a misleadingly high cathode-voltage reading. If the load circuits all check normal, but the low-voltage condition persists, then make further tests of components in the audio output circuit itself. Low cathode voltage of this stage could be due to excessive bias, too much plate resistance, or related troubles.

The low-voltage power supply is a relatively simple circuit, and resistance and voltage checks are generally sufficient for most troubleshooting procedures. The only time an oscilloscope would be useful is when the hum level seems to be high. In that case, check the peak-to-peak value of the AC ripple. Ordinarily, it will be on the order

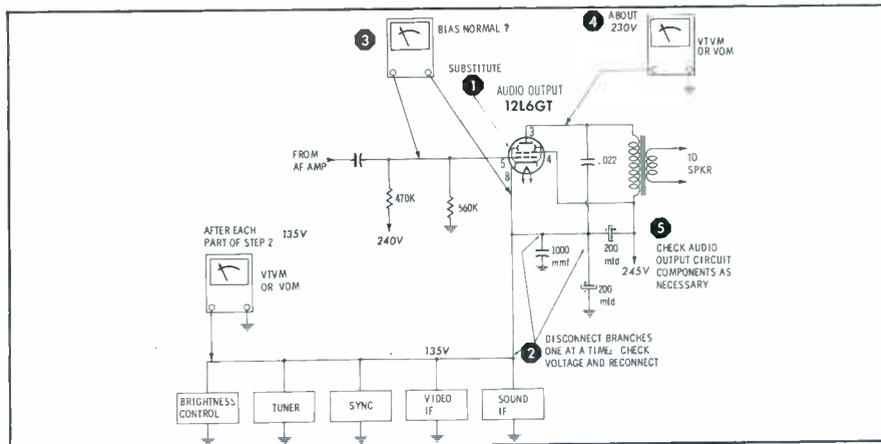


Fig. 3. Troubleshooting procedure to locate defects in a secondary B+ supply.

Transistor Radio Servicing CAN be Highly Profitable




The ONLY Complete Transistor Radio Service Lab
Everything you need for less than \$50

Check Transistors, Diodes, Rectifiers . . .



SENCORE TRC4 TRANSISTOR CHECKER

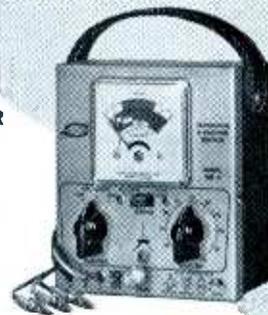Accurately checks all transistors in hearing aids, radios and power transistors in auto radios. Tests for opens, shorts, leakage, current gain. Measures forward-reverse current ratio on all crystal diodes. Measures forward and reverse currents on selenium rectifiers. With set-up chart for accurate checking of each transistor. Size, 5x4½x2½". With batteries. DEALER NET 17⁹⁵



Replace Batteries During Repair . . .



SENCORE PS103 BATTERY ELIMINATOR

All-new "Transi-Pak," twin to TRC4 Checker above. Provides variable DC voltage to 24 volts; 1.5-volt biasing tap (a "must" for servicing Philco and Sylvania radios). Metered current output, to 100 ma. Handles 200-ma peaks. Two 200-mfd electrolytics provide proper filtering and low output impedance. No hum or feedback problems. Ideal for alignment using station signal; adjust IF slugs for max. current, also ideal for charging nickel-cadmium batteries. Size, 5x4½x2½". DEALER NET 17⁹⁵



Find Defective Stage in a Minute . . .



SENCORE HG104 HARMONIC GENERATOR

New signal generator designed primarily for fast signal-tracing of transistor radio circuits. No need to unsolder all transistors. Provides RF, IF and audio signals *simultaneously*, drastically cutting service time. Traces from speaker to antenna. Clear 1000 cycle note signal is heard in speaker from all good stages. Signal weakens or stops at defective stage. Equally as effective for testing TV, hi-fi and other audio circuits also. Size, 3½x4½x1¾". With batteries. DEALER NET 9⁹⁵



Turn page for other

SENCORE
Time Savers

See your Parts
Distributor
NOW!

SENCORE
ADDISON 2, ILLINOIS

CHEMTRONICS' TUN-O-LUBE
 with MIRACLE ACTIVATED CLEANER TC-3
 cleans and lubricates all tuners and
 provides longer lasting protective film.
 FREE "Spray Aid" and "Wall Mount" with
 every 8 oz. can. See your distributor.
 CHEMTRONICS INC., Brooklyn 25, N. Y.

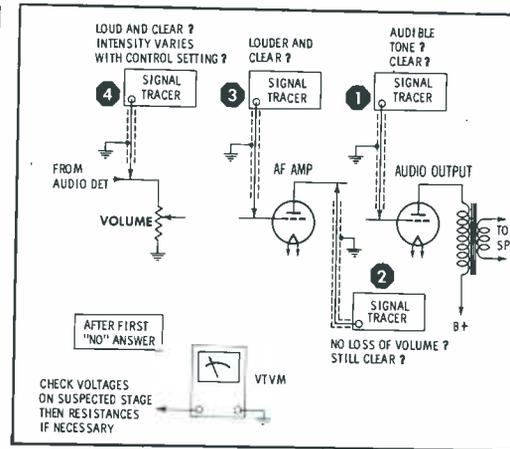



Fig. 4. How to use the signal-injection technique to isolate audio troubles.
 of 2 volts or less. If it possesses a substantially higher value, check or replace the filter capacitors.

The Audio Section

The audio section extends from the output of the FM detector to the loudspeaker. Trouble manifests itself here in the form of distortion, or in a complete lack of sound. The same symptoms can also be caused by a defect elsewhere in the sound channel, so your tests should quickly reveal whether or not the audio amplifiers are functioning normally. The quickest way is to use some form of signal injection (Fig. 4). The source can be an audio signal generator, 60-cycle AC taken directly from the filament line, or even your own finger. Apply the signal to the control grid of the audio output stage. A suitable sound should be heard in the speaker, even when you are using your finger. Of course, a signal generator will deliver a cleaner note and thus enable you to spot distortion more quickly. But when the trouble is low volume or none at all, any of the injection methods will work.

Work back from the speaker to the detector output and listen for the results. If sound increases appreciably as you change the injection point from the grid of one tube to the grid of a prior tube, the trouble is elsewhere and there is no point in spending any more time with the audio amplifiers. But, if you find that the sound distorts or disappears during the procedure, the next step is further localization. For example, is the output okay when the signal is injected at the plate of a stage, but distorted when it is applied at the grid? Assuming the tube to be

SAMS PHOTOFAC INDEX

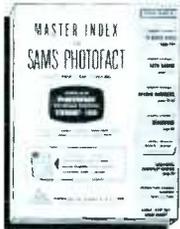

sent direct
to your shop

FREE

SEND FOR IT!

Yes, now you can have the valuable SAMS MASTER INDEX TO PHOTOFAC FOLDERS and Index Supplements sent direct to your shop at no cost to you! Just mail coupon below and you'll be sure to receive regularly your handy guide to the world's finest service data covering over 33,000 TV, Radio, Amplifier, Tuner Tape Recorder and Changer models. Send for it—it's FREE!

MAIL COUPON

Howard W. Sams & Co., Inc.
 2201 East 46th St., Indianapolis 6, Ind.

Put me on your mailing list to receive the Sams Photofact Master Index and Supplements

I'm a Service Technician: _____ full time; _____ part time

My Distributor is:

Shop Name: _____

Attn: _____

Address: _____

City _____ Zone _____ State _____

NEW SOUNDCRAFT VINYL



FOR EVERY
ELECTRICAL
TAPING JOB!

R92

Here's the electrical tape that's got everything!

**COMPLETE PROTECTION
AGAINST INSULATION FAILURE**

- Tremendous durability • Perfect conformability • High dielectric strength (10,000 volts) • Excellent adhesion and staying power • Non-combustible • Extreme resistance to aging • High resistance to temperature and humidity extremes and **remarkable adaptability to a wide variety of uses!**

REEVES SOUND CRAFT CORP. Great Pasture Road
 Danbury, Conn.

R76

manufacturers of the world's finest magnetic recording tapes

good, check voltages at its elements, particularly the plate and grid. If plate voltage is lower than it should be, follow the circuit to the B+ feed point, checking voltage as you cross each component. There is no point measuring plate load resistors or changing output transformers until you find a *normal* reference point. For instance, if B+ is normal and the plate voltage of a stage is low, we know the trouble is in this stage. But if the applied B+ is low, why look in the stage until the B+ is brought back to normal?

Low plate voltage can stem from the following causes:

1. Control grid less negative than it should be with respect to cathode.
2. Increased resistance in the plate circuit.
3. Decreased cathode circuit resistance.
4. Decreased screen grid resistance.


Conditions 2, 3, and 4 can be checked out in short order. With the power turned off, simply measure the resistance in each of these circuits with a VTVM or VOM. In order for a resistance change to produce noticeable results—such as distortion or lowered volume — it should be on the order of 50% or more. A 10 or 15% variation from rated value will hardly produce a significant change in amplifier operation. Note, too, that in conditions 3 and 4, a resistance decrease is indicated. In condition 3, the decrease will reduce stage bias and cause more plate current to flow. In condition 4, a lowered dropping resistor will increase screen grid voltage, which will have a greater effect on plate current flow than a

comparable rise in plate voltage. In condition 2, an increase in plate resistance is indicated. A decrease in resistance will result in a higher plate voltage.

Now let's consider condition No. 1, from the standpoint that the decrease in bias is not being caused by a decrease in cathode resistance (condition 2). The trouble could stem from the tube itself, for example, when gas is present. The preliminary tube check should reveal this, but only if you are sufficiently alerted to this possibility. If you are not, and the tube tester has no

simple check for gas, it may easily pass unnoticed. This was pointed out in my previous column, but is being mentioned again because of its importance.

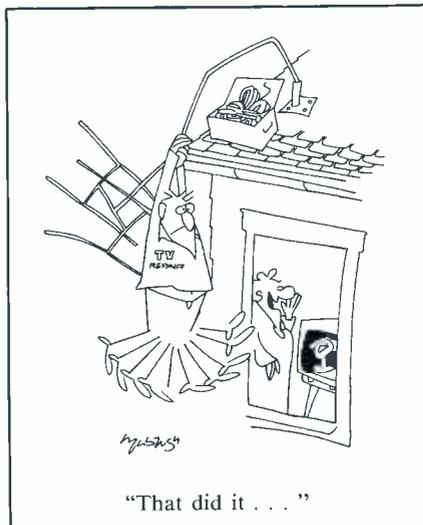Another reason for condition No. 1 is a leaky coupling capacitor. When the grid resistor has a high value, not much leakage is required to upset grid voltage. With a sensitive VTVM, check the voltage from grid to chassis (or to the low side of the resistor if it returns to a voltage source). The meter reading should be zero. Any slight positive voltage should be regarded with sus-



Servicemen! SAVE TIME...SUBSTITUTE THE SENCORE WAY

The Fastest, Surest Method Known!

Substitute for Capacitors, Resistors

SENCORE H-36—THE "HANDY 36"

36 most-often-needed resistors and capacitors, for fast, easy, direct substitution in all circuits. ● Eliminates searching for replacement components for test purposes. ● Avoids unnecessary unsoldering and soldering—no more solder mess. ● Pays for itself the first month in time saved. ● Flick of a switch instantly selects any one of...

24 RESISTORS from 10 ohms to 5.6 megohms
10 CAPACITORS from 100 mmfd to .5 mfd
2 ELECTROLYTICS, 10 mfd and 40 mfd

DEALER NET..... **1275**

Substitute for Electrolytic Capacitors

SENCORE ES102 ELECTRO-SUB

Usable from 2 to 450 volts, D.C.
Contains 10 electrolytics from 4 to 350 mfd. Select the correct value with the flick of a switch. Features automatic discharge, surge protector circuit. Prevents accidental "healing" of capacitor being bridged. Completely safe—no arc or spark when connecting or disconnecting. DEALER NET..... **1595**

Substitute for Fuse Resistors During Repair

SENCORE FS3 "FUSE-SAFE" CIRCUIT TESTER

Instantly tells you whether or not it is safe to replace fuse resistors, fuses, or circuit breakers. Separate red and green scale for each commercially available fuse resistor used in radio and TV. Eliminates guesswork and wasted time. Also handy for wattage checks up to 1100 watts. DEALER NET..... **895**

Substitute for Bias Batteries During Repair

SENCORE BE3 "ALIGN-O-PAK"

Completely isolated DC supply, with less than 0.1% ripple. Eliminates messy batteries in TV service work. Handy for alignment, AGC trouble-shooting, or checking gated sync circuits. Just dial the voltage you need, 0-18 volts, positive or negative. Covers all voltages recommended by TV set manufacturers. Size, 3½x4½x1¾". For 110-120 volts, 60 cycle AC. DEALER NET..... **785**

UNIVERSAL TV JUMPER CORD

Fits any set from back to chassis. Box has male and female plugs for additional power source, soldering, etc. DEALER NET **195**

Turn page for other
SENCORE
Time Savers

See your Parts Distributor Now!

SENCORE

ADDISON 2, ILLINOIS

picion, since the most likely reason is that the grid is drawing current. Use the lowest DC voltage range available — preferably one volt or less.

The opposite condition — plate voltage higher than normal — is another possible indication of distortion, or even complete loss of output. If the plate voltage is equal to the applied B+, no current is passing through the tube. Excessive negative voltage on the grid will cause this, as will an open in the cathode or screen circuits.

There is one additional defect

which will reduce the gain of an amplifier noticeably, and that is an open bypass capacitor in the screen grid circuit. (The extent of the decrease is proportional to the operating frequency, so an open screen bypass capacitor will have a greater effect in an IF stage than in an AF stage. In both instances, however, the amplification decrease is noticeable.) The fastest way to check for this condition is to bridge a good capacitor across the suspected unit. A return of normal volume indicates the original capacitor is defective. In this regard, do not overlook any

Table I—Instrument Selection for Troubleshooting a TV Receiver.

SECTION	PRIMARY TESTS	SECONDARY TESTS	
		1	2
POWER SUPPLY	VOM OR VTVM	SCOPE	—
AUDIO SECTION	SIGNAL GENERATOR	VOM OR VTVM	SCOPE

bypass capacitors in the plate circuit. These, too, can cause a similar difficulty.

The primary test instruments for troubleshooting the audio section are first, a signal generator and second, a VTVM or VOM. An oscilloscope can be useful, however, in isolating distortion. Use it to check input and output waveforms, and also to uncover the source of hum leakage. In printed circuits, the closeness of the conductors makes hum interference a not uncommon trouble. By checking control grids for the presence of AC voltage when no signal is being applied, you will discover any sneak paths. The cathode, too, can be another port of entry for AC voltages, either by leakage from the heater, across the socket terminals, or from the bypass capacitor shunted across the cathode resistor. The latter condition can arise when the capacitor is part of a multi-section filter which has leakage between sections.

To recapitulate, in troubleshooting the power supply, the primary test instrument is the VTVM or VOM. A secondary test instrument is the oscilloscope. To check the audio section, the signal-injection technique is the primary means, followed by use of the VTVM or VOM and then the oscilloscope. Table I lists this information, and as we examine additional sections in my next column, they will be added to the chart. ▲

2X NORMAL OPERATING VOLTAGE +1000 STANCOR TRANSFORMERS STAND UP!

Every STANCOR iron core transformer gets this breakdown test as a production line operation. To assure you of reliability and safety, each unit is tested for breakdown between windings and to ground—at twice its operating voltage *plus* 1000 volts! STANCOR'S thorough testing procedures protect you against failures and call-backs . . . one more reason why experienced technicians everywhere always specify STANCOR.



CHICAGO STANDARD TRANSFORMER CORPORATION
3503 ADDISON STREET • CHICAGO 18, ILLINOIS



Video IF Response

(Continued from page 30)

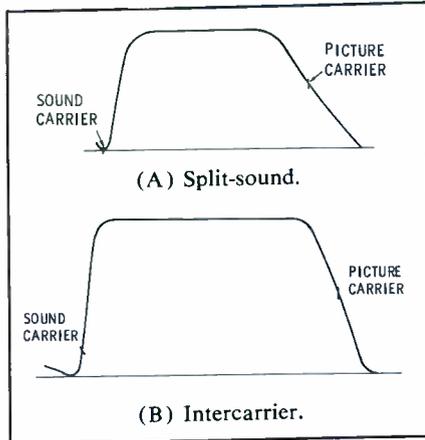


Fig. 4. Position of sound carrier on IF curve in different types of sets.

all response curve as shown in Fig. 5A. The shape of this final curve is determined by three factors—the resonant frequency of each stage, the Q of each tuned circuit, and the nature of the trap circuits.

The resonant frequency of each stage is determined by a combination of the interelectrode capacitance of the tube, the distributed capacitance of the coil, stray circuit capacitances, lead inductance, and the inductance of the coil. The core of each coil is adjustable for alignment purposes. The individual IF stages are impedance-coupled as shown in Fig. 5B. The value of grid resistor R1 will vary the effective Q of IF transformer L1, since its value determines the amount of coil loading. The lower the value of resistance, the greater the loading and the wider the bandwidth. A classic

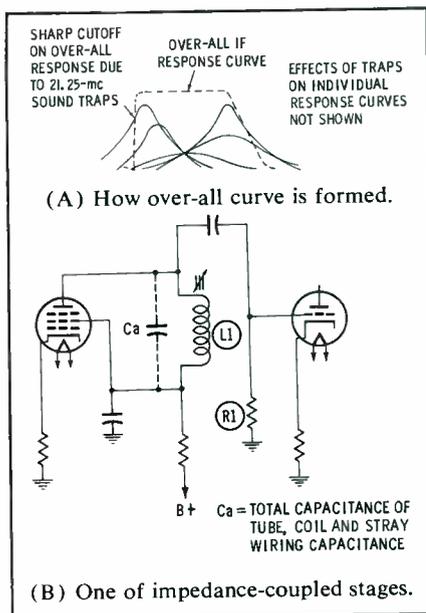


Fig. 5. Stagger-tuning of an IF strip.

example of this type of design is the IF strip in the RCA 630TS receiver (see Fig. 6).

Another method of shaping IF curves, sometimes referred to as *complex coupling*, illustrated in Fig. 7, is used in a number of earlier DuMont sets. Each interstage coupling network is a complete band-pass filter instead of being tuned to some specific frequency within the IF band. Fig. 7A shows the coupling circuit between the mixer plate and the grid of the first IF amplifier. Viewing this circuit in simplified form in Fig. 7B, you can see that it

is essentially a single-section, T-type, band-pass filter.

The over-all response curve is determined by the resonant frequencies of the various tuned circuits as well as the degree of coupling between stages. Traps are frequently included in some of the coupling circuits, as shown in Fig. 8. This circuit consists of a combination of band-pass and band-reject elements in a pi-type filter network. The combinations L1-C1 and L2-C2 are trap circuits tuned to 21.9 and 27.9 mc, respectively. The Q of the tuned grid and plate loads is lowered by

Check TUBES, VIBRATORS

THE SENCORE WAY

FAST
ACCURATE
TROUBLE
SHOOTING

America's Most Popular Tube Tester

more than 25,000 now in use

SENCORE LC3 LEAKAGE CHECKER

Whips those "tough dog" tube troubles . . .

Ask any serviceman who owns one . . . or try one for just one day of servicing in your shop. You'll see for yourself how much time the LC3 can save *you*. Checks for leakage between all elements, whether caused by gas, grid emission or foreign particles. Also checks leakage on all capacitors with voltage applied—including electrolytics. Provides instant filament checks in "Fil-Check" position—no need for a second filament checker. One spare pre-heating socket and new roll chart prevent obsolescence. New charts provided—no charge. Leakage sensitivity; 100 megohms, control grid to all other elements; 50,000 ohms, heater to cathode. Size, 7x6x3½". Wt., 3 lbs. For 110-120 volts, 60 cycle AC. DEALER NET **28⁹⁵**



NOW . . . checks 172 tube types—more than any other checker of this type.

NEW . . . replaceable Roll Chart prevents obsolescence.

Check Filaments of All Receiving Tubes and Picture Tubes



FC4 FILAMENT CHECKER

For fast, easy checking of all tube filaments, without pulling chassis. Neon light goes out if tube filament is good. Also acts as continuity and voltage tester. Neon lamp glows when 115 v. AC is applied by cheater cord, providing a check on power to TV set. Size, 3½x4x1". **2⁹⁵** With leads. DEALER NET

Check 3- and 4-Prong Vibrators . . . Faster, Easier



VB2 "VIBRA-DAPTOR"

Plugs into any tube checker; ideal for use with LC3 above. To check 6-v. vibrators, set for 6AX4 or 6SN7; for 12-v. vibrators, set for 12AX4 or 12SN7. Two No. 51 lamps indicate whether vibrator needs replacing. Instructions on front panel. Steel case. Size, 1½x1½x3". **2⁷⁵** DEALER NET

See your Parts Distributor NOW!

Turn page for other



SENCORE

ADDISON 2, ILLINOIS

Time Savers


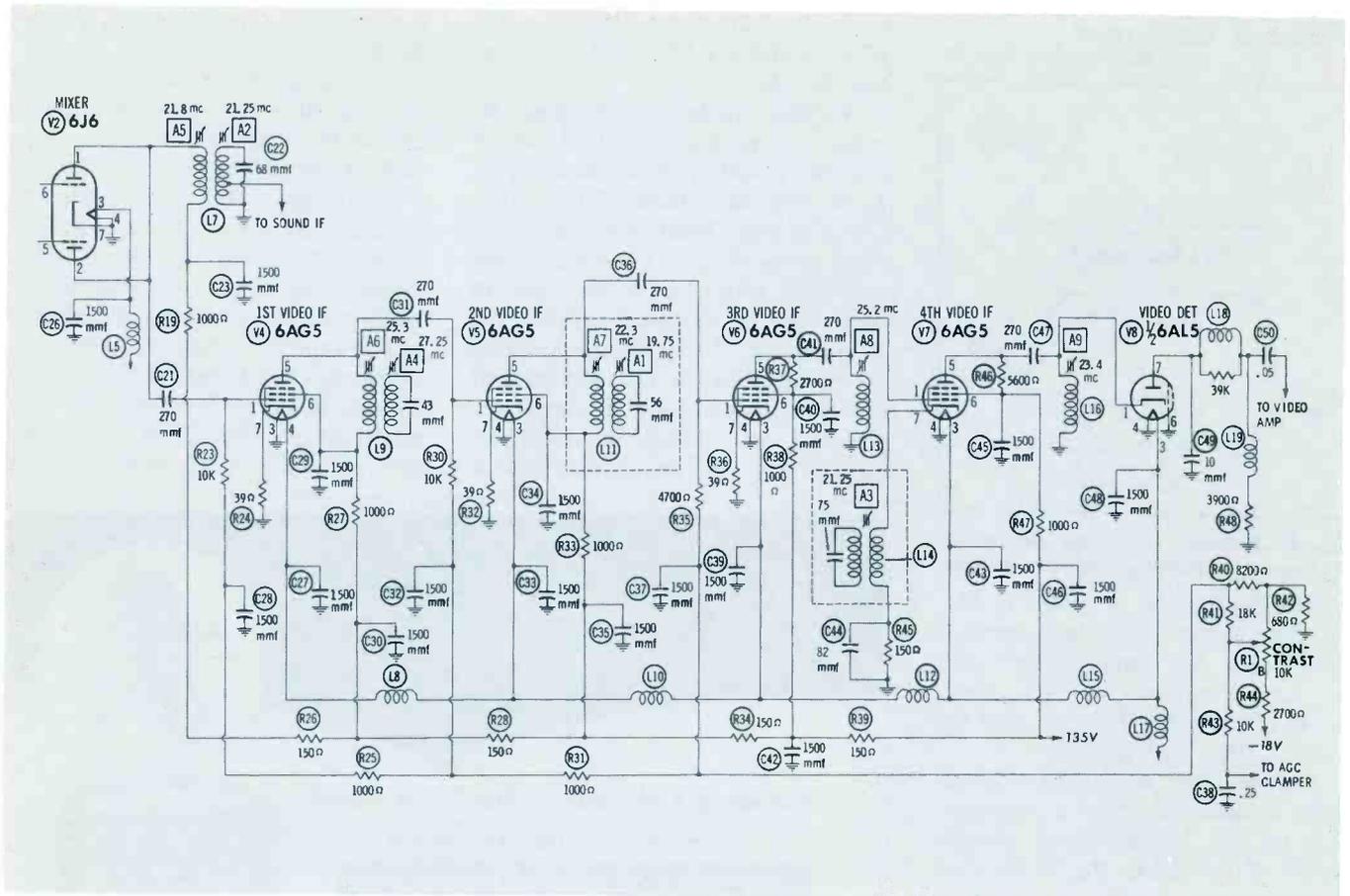


Fig. 6. RCA 630TS IF strip is an example of early stagger-tuned design.

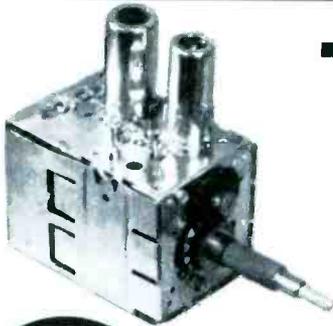

TV TUNERS OVERHAULED

VHF
OR
UHF

ALL

MAKES
AND
MODELS

90
DAYS
WARRANTY

FAST SERVICE

PRESENT DELIVERY IS
48 HRS. ON MANY TYPES

VHF OR UHF TUNER OVERHAULED

\$9.95 NET

Prices include labor and minor parts only, defective tubes and damaged major parts are extra at net prices.

UHF/VHF COMBINATION OVERHAULED

\$19.90 NET

Forward defective tuner complete with tubes, shield cover and any damaged parts. Quote make and model. We will ship C.O.D.—F.O.B. Chicago or Toronto.

Castle TV Tuner Service

5710 N. Western Ave. Chicago 45, Illinois

Suppliers of rebuilt TV Tuners to leading manufacturers, technicians & service dealers, coast to coast. Original and Only Complete TV Tuner Service covering the North American Continent.

In Canada: — 152 MAIN ST., TORONTO 13, ONT.

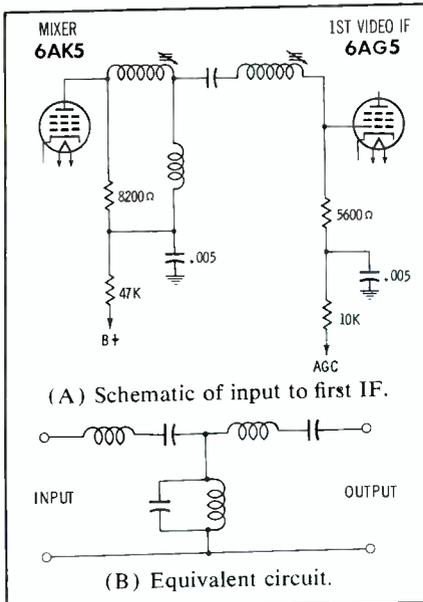


Fig. 7. Complex interstage coupling circuit employed in DuMont RA-105B. shunt resistors (R1 and R2), just as in the stagger-tuned circuits. The trap circuits are not shunted since they must have a high Q to insure that they will trap out only a very narrow band of frequencies.

The alignment of complex-type IF circuits is a difficult task if only a signal generator and VTVM are used, since the response of the tuned circuits is so broad that the center of the response curve is almost impossible to locate. A sweep alignment procedure must be employed to obtain best results.

An interesting variation of the stagger-tuning method involves use of a special type IF transformer known as a bifilar-wound coil. The primary and secondary windings of this component are interwound in the manner shown in Fig. 9. The coupling approximates unity; therefore, this circuit is the equivalent of the impedance-coupling network used in the previously-mentioned stagger-tuned circuit (Fig. 5B).

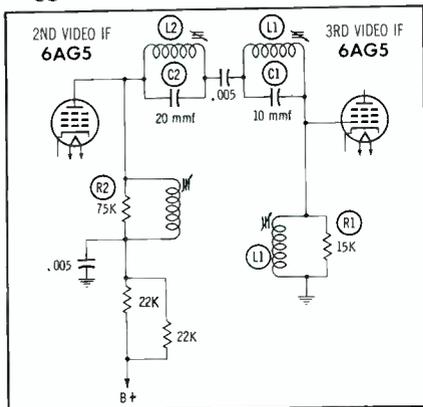


Fig. 8. Traps in second to third-IF coupling circuit, DuMont RA-105B.

Each transformer has only one tuning adjustment, and the resonant frequency of the individual stages is staggered in the conventional manner. Resistive loading is employed to reduce the Q and broaden the curve. An IF amplifier employing this type of transformer is shown in Fig. 10. The main advantages obtained from using bifilar transformers are better immunity to noise in the IF stages, and a reduced number of components.

Trap Circuits

Trap circuits used in video IF

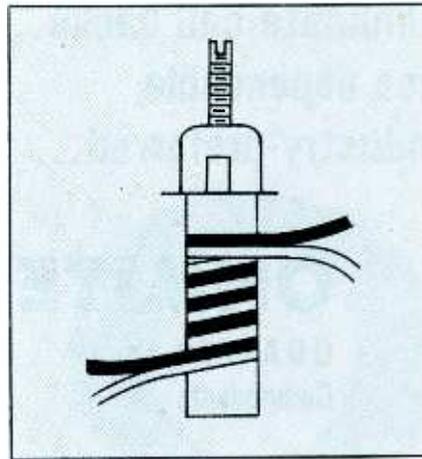


Fig. 9. Bifilar coils in IF transformer.

Pinpoint in Seconds...
HORIZONTAL & VERTICAL SWEEP TROUBLES

NEW
SENCORE
Time Saver

Sweep Circuit TROUBLE SHOOTER
MODEL 55105

PROVIDES:
- UNIVERSAL HORIZONTAL OSCILLATOR
- HORIZONTAL OUTPUT CATHODE CURRENT CHECKER
- UNIVERSAL DEFLECTION YOKE
- DYNAMIC FLYBACK TRANSFORMER CHECKER
- VOLT METER
- UNIVERSAL VERTICAL OSCILLATOR

DEFLECTION FORCE SURE

INTER SEL. HORIZ. OUTPUT CATH.

OSCILLATOR

OSC. OUTPUT

The missing link in TV service ...

SENCORE SS105 SWEEP CIRCUIT TROUBLE SHOOTER

IT'S A ...
UNIVERSAL HORIZONTAL OSCILLATOR. For direct substitution. No wires to disconnect in most cases. Traces trouble right down to the defective component. Variable output from 0-200 volts, peak-to-peak.

HORIZONTAL OUTPUT CATHODE CURRENT CHECKER. A proven method that quickly checks the condition of the horizontal output tube and associated components. Adaptor socket prevents breaking wires. Easily replaceable Roll Chart gives all necessary pin, current and voltage data.

UNIVERSAL DEFLECTION YOKE. A new, simple way to determine yoke failure accurately—without removing yoke from picture tube. Merely disconnect one yoke lead and substitute. If high voltage (also bright vertical line) is restored, TV yoke is defective.

DYNAMIC FLYBACK TRANSFORMER CHECKER. Merely flip switch to "Flyback Check" and meter will indicate condition of flyback transformer, in degrees of horizontal deflection. Extremely sensitive and accurate; even shows up one shorted turn on flyback.

VOLTMETER. For testing bootstrap, screen and other voltages. Direct-reading voltmeter, 0-1000 volts.

UNIVERSAL VERTICAL OSCILLATOR. Checks oscillator, output transformer and yoke. Merely touch lead to component and check picture on screen.

Size, 7x6x3½". Wt. 4 lbs.
For 110-120 volts, 60 cycle AC.

DEALER NET **39⁵⁰**

HORIZ. OSC.	VERT. OSC.
HORIZ. O.P. STAGE	VERT. O.P. STAGE
HORIZ. FLYBACK XFORMER	VERT. O.P. XFORMER
HORIZ. DEFLEC. YOKE	VERT. DEFLEC. YOKE

See Your Parts
Distributor
NOW!

SENCORE
ADDISON 2, ILLINOIS

Eliminate call backs...
use dependable,
industry-preferred...



3 WATT SIZE
5/16" x 1/4"

5 WATT SIZE
1 1/8" x 1/2"

AXIAL-LEAD RESISTORS
Vitreous-enamelled, power-type, axial-lead units designed to withstand high temperatures.

LITTLE DEVIL® COMPOSITION RESISTORS
Meet all MIL-R-11A requirements. Available in 1/10, 1/4, 1/2, 1, and 2-watt sizes in all standard EIA values.

BROWN DEVIL® RESISTORS
Vitreous-enamelled. In 5, 10, and 20-watt sizes.

TYPE AB POTENTIOMETERS
Resistance material is solid-molded, noise-free. Rated at 2 watts.

FR-7.5 FUSE RESISTOR
For easy replacement in many television receivers. 1 1/2" Tinned wire leads.

WRITE FOR STOCK CATALOG



OHMITE MANUFACTURING COMPANY
3644 Howard Street • Skokie, Illinois

amplifiers are designed to eliminate undesired signals, including co-channel sound, adjacent-channel sound, and adjacent-channel picture carriers. Generally, traps are constructed with very heavy gauge wire to attain the high Q necessary to trap out only the undesired signal. They may take one of the three forms shown in Fig. 11. The series-resonant trap L26 in Fig. 11A is connected from a point between the plate and grid circuit to ground. At its resonant frequency, the trap will have approximately zero impedance and will therefore conduct the signal to ground. At other frequencies, the trap has a very high impedance and therefore has little effect on the signal.

Fig. 11B typifies the design of a parallel resonant trap. It is always connected in series between the signal load, and either the grid or the plate of the amplifier tube. Since it has a high impedance at its resonant frequency, it will oppose the transfer of signal energy at this frequency.

Fig. 11C shows an absorption trap. Its operation is based on the fact that signals induced from L1 to L2 react as though L2-C2 formed a series resonant circuit. At resonance, XL2 will cancel XC2, and the circulating current will be at maximum. L2 and C2 will then absorb the greatest amount of energy from L1 at that frequency. At other frequencies, XL2 and XC2 don't cancel, and the trap absorbs little if any signal from L1.

Accompanying sound traps, besides being used to remove the sound signal from the video IF channel, may also be utilized to supply an input sound signal to the sound IF amplifier. Refer to Fig. 6 and note L7 in the plate circuit of the mixer tube. The secondary of this coil is an absorption-type trap; but, instead of dissipating the absorbed signal, it feeds it to the grid of the first sound IF. Thus, in addition to acting as a trap for the video IF channel, it functions as a first IF transformer for the sound channel.

Miller Effect

Designers of video IF stages must take into account a phenomenon known as Miller effect. Simply stated, this is the variation of the input capacitance in a tube as its grid bias is varied. Earlier, it was

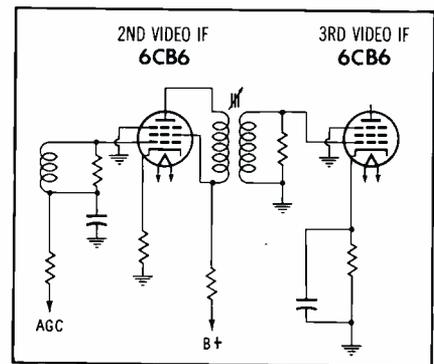


Fig. 10. Circuit using a bifilar transformer has a minimum of components.

pointed out that the resonant frequency of each IF stage was determined partly by the input capacitance of the tube. Since the amount of capacitance varies with bias changes, we may likewise expect the resonant frequency of the stage to vary. An IF stage controlled by AGC bias will change alignment when the strength of the received signal varies. In order to reduce this effect, a small amount of degeneration is inserted in each affected IF stage by inserting a low-value (39- to 47-ohm) unbypassed resistor in the cathode circuit.

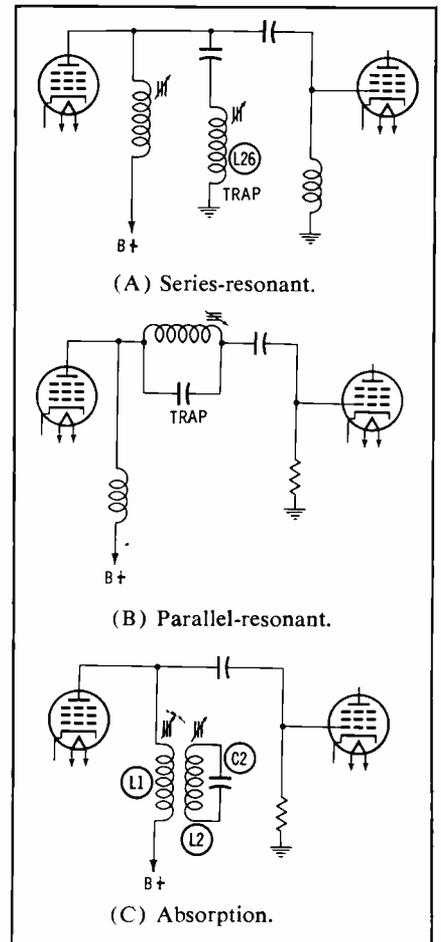


Fig. 11. Examples of the three basic types of trap circuits used in TV.

Some manufacturers make good use of the Miller effect by allowing the response curve to shift as Miller-effect capacitance varies. When low-amplitude signals are being received, the reduced AGC bias causes an increase in the input capacitance. This effect changes the IF response in such a manner that both carriers are moved up into a "higher-gain" position on the curve. Although some of the fine detail may be lost, snow is materially reduced. This reduction in snow content improves the picture more than a small loss of detail degrades it. DuMont employs this system in their RA-343 chassis, and so does Westinghouse in recent sets with "shifting IF."

Examples of Commercial IF Circuits

IF amplifiers in use today apply various combinations of the previously-described circuits to obtain the proper IF response curve. Fig. 12A shows part of the IF amplifier strip used in the Bendix T20 chassis. The input to V3 is through C26 and L20, which form a series-resonant circuit at 43 mc. A 12K resistor (R26) loads L20 to reduce the Q and broaden the response of the circuit. An absorption trap, resonant at 41.25 mc, is coupled to L20 to prevent excessive sound-carrier amplitude. Each successive stage is coupled with bifilar-wound coils which are stagger-tuned to produce the over-all response curve shown in Fig. 12B.

The same fundamental circuit is used in most types of recent-model sets, except for minor variations in resonant frequency, loading resistors, and trap circuits. The DuMont RA-365 differs only in the input to the first IF stage, as shown in Fig. 13. This set contains two traps which, at first glance, may appear to be parallel-resonant circuits and therefore not traps at all. However, careful analysis of the circuit reveals that, while the traps are parallel-resonant circuits at some frequency, each is effectively an inductance at either the sound IF or adjacent-channel sound frequency. Each inductance is in series with a small capacitor, thereby forming series resonant circuits at frequencies of 41.25 and 47.25 mc.

An interesting variation—in reality, an application of an early radio

best buys in custom hi-fi... **EICO**

- praised by the experts
- beautifully styled
- priced right for you
- lifetime guarantee



FM Tuner HFT90
with precision "eye-tronic" tuning
Wired \$65.95* Kit \$39.95*
Cover \$3.95.
*Less Cover, FET included
"One of the best buys you can get."—AUDIOCRAFT.

AM Tuner HFT94
with precision "eye-tronic" tuning
Wired \$65.95. Kit \$39.95.
Includes Cover & F.E.T.

STEREO Dual Amplifier-Preamplifier HF81

Wired \$109.95 Kit \$69.95
"Excellent"—SATURDAY REVIEW;
and HI-FI MUSIC AT HOME.



STEREO Dual Preamplifier HF85
Wired \$64.95 Kit \$39.95

STEREO Dual Power Amplifier HF86
Wired \$74.95. Kit \$43.95.
70w STEREO Dual Power Amplifier
Kit \$74.95
Wired \$114.95

Omni-directional Speaker System HFS2
completely factory-built: 36" h, 15 1/4" w, 11 1/2" d.
Mahogany or Walnut \$139.95. Blonde \$144.95
"Eminently musical"—HIGH FIDELITY
"Fine for stereo"—MODERN HI-FI

Also: **Bookshelf 2-Way Speaker System HFS1**
complete with factory-built cabinet, \$39.95
Other 2-Way and 3-Way Speaker System
Semi-kits, from \$47.50

Plus: POWER AMPLIFIERS (14, 22, 30, 35, 50 and 60-watts) from \$23.50.
INTEGRATED AMPLIFIERS (12, 20, 32 and 50 watts) from \$34.95.



best buys in test instruments... **EICO**



COLOR & Monochrome DC to 5 MC Lab & TV 5" Oscilloscope #460
Wired \$129.50
Kit \$79.95



TV-FM Sweep Generator & Marker #368
Wired \$119.95
Kit \$69.95



DYNAMIC CONDUCTANCE Tube & Transistor Tester #666
Wired \$109.95
Kit \$69.95



PEAK-to-PEAK VTVM #232 & Unit-Probe
Wired \$49.95
Kit \$29.95
(PAT. PEND.)

IN STOCK at over 2000 neighborhood distributors coast to coast
Send for free catalog

PF-11
EICO, 33-00 Northern Blvd., L. I. C. 1, N. Y.
Show me how to save 50% on top-quality: Hi-Fi
 Test Instruments Ham Gear. Send free catalog and name of neighborhood EICO supplier.
 Send free STEREO Hi-Fi Guide.
NAME _____
ADDRESS _____
CITY _____ ZONE _____ STATE _____

ADD 5% IN THE WEST



INJECTORALL

THE NEEDLE DOES THE JOB!



TUNER CLEANER AND LUBRICANT with... INJECTOR NEEDLE

The leak-proof steel Injectorall Needle lubricates where you need it... you can reach hard-to-get at Wafers without pulling Tuners apart, or even removing Chassis.

The BEST CLEANER on the market today!

INJECTORALL CO. Brooklyn 14, New York

High Fidelity 3 SPEAKER SYSTEMS

Here is a perfectly matched team with 3-way cross-over network. Kit includes 12" woofer; 8" midrange; 3 1/2" tweeter; hardware and network. Model 3W20... audiophile net \$39.00.

Beautiful cabinets available in variety of modern finishes and designs... write for FREE literature.

Leading distributors carry OXFORD COMPONENTS, INC., 556 West Monroe Street, Chicago 6, Illinois

OXFORD

Expert: Roburn Agencies, New York • In Canada: Atlas Radio, Toronto

OXFORD BRANDS: Supreme Transformers, Hudson Lamps, Tempo Hi-Fi, Oxford Speakers & Rear Deck Kits.

circuit—is used in the Emerson reflex IF amplifier shown in Fig. 14. The second video IF amplifier (V4) also serves as a sound IF amplifier in the following manner. The 4.5-mc sound output is taken from the secondary of a special transformer in the video-detector output circuit, and is fed back to the grid of V4 through L8 and the secondary of L7. The plate circuit of V4 has two resonant circuits, L9A (tuned to the conventional frequency of 42.6 mc for the picture and sound) and L9B (tuned to 4.5 mc for the sound IF). The signal developed across L9A, a bifilar IF transformer, is fed to the following video IF stage, while the signal across L9B is fed to the 5U8 sound limiter (which functions as a second sound IF stage). Since the signals are of widely different frequencies, there is no significant interaction between them.

A Word About IF Servicing

If a part failure in the IF strip brings about a complete loss of video and sound, the trouble can usually be located without too much difficulty. Techniques such as tube substitution, signal tracing (or injection), and voltage or resistance checks of suspected stages are especially helpful. It is often much harder to solve service problems involving only a moderate distortion of the IF signal, because the IF trouble is likely to masquerade as a sync, video, sound, or AGC defect. To add to the confusion, a faulty AGC system can make the IF strip behave as if it were defective. In case you suspect IF signal distortion, here are two tests which should be made immediately: Check all IF

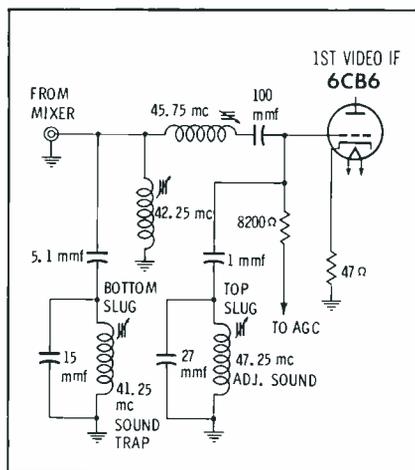


Fig. 13. Video IF input circuit in the DuMont RA-365 contains two traps.

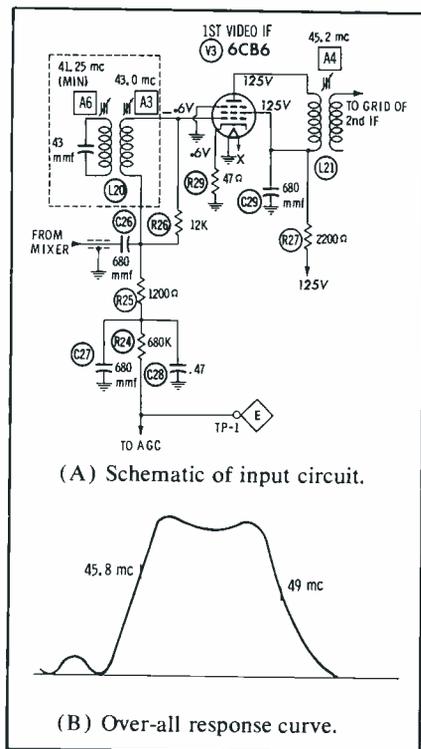


Fig. 12. Video IF strip of Bendix T20.

amplifier tubes for grid-circuit defects as well as for transconductance; and try connecting an adjustable DC voltage source (bias box) to the AGC line in an attempt to override any faulty action of the AGC system.

In some cases, you will finally come to the conclusion that the IF strip needs realignment. With a little practice, you can recognize a misaligned receiver by observing the picture as you turn the fine tuning control; however, for a really positive indication as to whether or not the IF strip is properly aligned, nothing beats a quick check of the over-all IF response curve with a scope and sweep generator. It's well worth the short time it takes. ▲

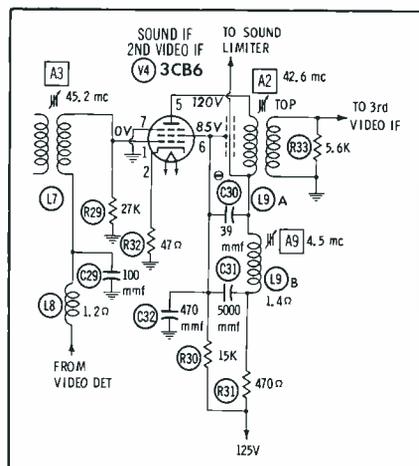


Fig. 14. Emerson 1138 employs a video IF stage also as a reflex sound IF.


Streamlined Synchroguide

(Continued from page 35)

er-type circuit works in just the opposite manner. Its sinusoidal portion has just passed the negative peak and is positive-going at the end of trace time. The resulting steep increase in plate voltage of the triode oscillator tube helps to regulate the time at which tube conduction begins during each cycle, in addition to preventing early triggering by noise pulses.

Going on to the AFC tube, we shouldn't expect to find any significant waveform at its cathode (pin 3) because of the bypassing action of C2 and C3. The plate (pin 1) will likewise be free of signals because it is tied directly to B+. However, a conventional "pulse-width AFC" waveform (W5) will be produced at the grid when the input sync pulse W6 combines with an integrated sawtooth wave fed back from the oscillator circuit.

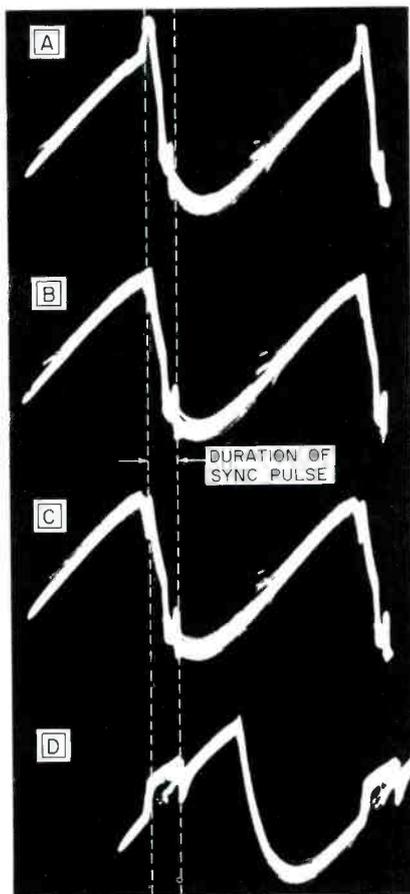The waveform sequence in Fig. 7 shows graphically what happens in



(A) Oscillator slow, but in sync.
 (B) Oscillator at correct frequency.
 (C) Oscillator fast, but in sync.
 (D) Out-of-sync condition.

Fig. 7. AFC grid waveforms (W5).

FIRST TIME . . . a versatile

DUAL HEAT

SOLDERING GUN

FOR ONLY
\$795
 LIST
 Model 8200K



...and best of all,
 it's a new

Weller®

Here from Weller, long time leader in the soldering field, is the newest and finest soldering gun value on the market.

WELLER DUAL HEAT FEATURE saves time, gives greater convenience and greatly increases tip life. A touch of your finger on the Triggermatic control switches heat to high (125 watts) or low (90 watts) as your job requires. It adapts instantly to varying needs, and you use high heat only when necessary.

HIGH EFFICIENCY WELLERTIP utilizes copper for superior heat transfer and soldering efficiency, plus iron plating for durability. Flat cross-section design gives added strength and rigidity.

NEWEST DESIGN with sturdy plastic housing that resists hard knocks. Compact "feel" and comfortable balance aid precision soldering. Like all other Weller guns, this new model features instant heat, and a spotlight illuminates your work.



KIT INCLUDED

In addition to the Dual Heat Soldering Gun you get:

- Wire Bristle Cleaning Brush
- Soldering Aid for opening old joints, twisting wires
- All-purpose Solder

On sale now at your
 Electronic Parts Distributor

WELLER ELECTRIC CORP. • 601 Stone's Crossing Rd., Easton, Pa.

**LATEST VOLUMES IN
POPULAR SAMS
SERIES BOOKS**

"Servicing Transistor Radios" Vol. 4



Complete analysis of popular transistor radios produced in 1958-59. Includes special section on "Techniques in Servicing Transistor Circuits." All data based on actual lab analysis. You get famous Sams Standard Notation schematics with Circuit-Trace; full photo views of each chassis; alignment data; parts replacement information — all you need for time-saving, profitable transistor radio servicing. Cumulative index covers all volumes in series. 160 pages; 8 1/2 x 11". Only.....\$2.95

"Record Changer Manual" Vol. 12



Complete analysis of 62 record changers produced in 1958-59 including: Dual, Fairchild, Garrard, Lesa, Miracord, Perpetuum - Ebner, Silverstone, V - M, Webcor, Westinghouse, Wum o. Provides general description, operating instructions, exploded views, change cycle data, adjustments, trouble chart, parts list, etc. Includes index for all volumes in series. 160 pages; 8 1/2 x 11". Only.....\$2.95

"Tape Recorder Manual" Vol. 4



Full analysis of 21 tape recorders produced in 1958-59. Covers Bell & Howell, Bell Sound, Grundig Majestic, Knight, RCA, Revere, Sylvania, Telectro, Tower. Includes general description, operation data, trouble shooting and maintenance facts, diagrams, parts lists, etc. With special editorial section on magnetic tape recording. Has cumulative index. 160 pages; 8 1/2 x 11". Only.....\$2.95

"Auto Radio Manual" Vol. 9



Covers scores of popular auto radios produced in 1958-59. Most complete data available: Schematics, chassis photos, voltages, resistance readings, parts lists and replacement data — everything you need to know for quicker, easier auto radio servicing. 160 pages; 8 1/2 x 11". Only.....\$2.95

HOWARD W. SAMS & CO., INC.

order from your Sams Distributor today, or mail to Howard W. Sams & Co., Inc., Dept. LL-39, 2201 E. 46th St., Indianapolis 6, Ind.

Send me the following books:

- "Servicing Transistor Radios" Vol. 4 (TSM-4)
- "Record Changer Manual" Vol. 12 (RC-12)
- "Tape Recorder Manual" Vol. 4 (TR-4)
- "Auto Radio Manual" Vol. 9 (AR-9)

\$_____ enclosed. Send Free Book List

Name _____

Address _____

City _____ Zone _____ State _____

(outside U.S.A. priced slightly higher)

the grid circuit when the feedback signal undergoes a phase shift with relation to the sync-pulse signal. Waveforms A, B, and C were taken with the receiver in sync and the oscillator running under the following conditions: (A) At the "slow" end of the hold-control range; (B) very close to the center of the range; (C) at the "fast" end of the range. Waveform D corresponds to a condition in which the picture slips out of sync and a horizontal-blanking bar appears in the center of the screen.

As you will note, the sync pulse normally arrives while the feedback signal is passing through the steep negative-going portion of its cycle. If the oscillator tends to run too slow, the pulse occurs relatively early in each cycle of the feedback signal. It then "rides high" on the crest of the modified sawtooth wave (as in waveform A) and drives the AFC tube into heavier-than-normal conduction. Cathode current of this tube, flowing through R3, R5, R6 and R1 in series, produces a positive bucking voltage which decreases the bias on the oscillator tube in order to speed up the operating frequency.

Whenever the oscillator tends to run too fast, the sync pulse arrives abnormally late in the feedback signal's cycle. It then serves to increase the negative voltage on the grid of the AFC tube—thereby slowing down the oscillator and keeping it in sync.

The AFC stage can maintain control over oscillator frequency only as long as the sync pulse occurs within the retrace period of the sawtooth wave. Sometimes, just past the end of the lock-in range, the picture tends to assume an out-of-phase condition in which a horizontal-blanking bar is displayed in mid-

screen. This symptom corresponds to D in Fig. 7, where the sync pulse occurs midway in the positive-going slope of the feedback signal.

Voltage Readings

Let's take a round of DC voltage measurements with a VTVM to see what the normal readings should be in this new *Synchroguide* circuit.

E1, the output-tube grid voltage, may be conveniently measured at lug E of the printed-wiring board. The reading between this point and ground will be about -25 to -35 volts, depending on drive-trimmer setting and condition of the receiver. Note that the total bias on the output tube will actually be greater than the grid-to-ground voltage, since a small positive potential will be developed across the cathode resistor of the 6DQ6A.

E2 (oscillator plate) remains constant at about 120 volts.

E3 (oscillator grid) varies by only a couple of volts over the entire range of the hold control. The nominal value is about -55 volts.

E4 (oscillator cathode) is only about a quarter of a volt above ground, since very little voltage is developed across the low resistance of the coils which form the ground-return path for the cathode.

E5 (AFC grid) is a tricky voltage to measure, since even a VTVM will load the circuit and may knock the oscillator out of sync. If it does this, E5 will be close to zero. At some settings of the hold control, an attempt to measure E5 will just cause the picture to shift slightly, and a reading of more than +5 volts will be obtained. By rotating the hold control while keeping the meter connected to the grid, you should be able to keep the picture synchro-

**Why Pay More . . . the D-600
Electrolytic Substitute
tests ALL radio and TV electrolytics!**

■ Technicians all over the country are reporting that this is one of the handiest tools on the bench.

A dual, split switch and built-in neon indicator allows you to shunt test in seconds without the danger of heating.

A fast, in-circuit method of testing
Two ranges . . . Low and High
(10-40 MFD 450V), (50 MFD up 450V)



**\$895
NET**

MADE BY THE
DESIGNERS
OF THE
Pioneer 250

SEE YOUR
DISTRIBUTOR

DOSS

ELECTRONIC RESEARCH, Inc.—820 Baltimore • Kansas City, Mo.

nized over a grid-voltage range of approximately -2 to +8 volts.

E6 (AFC cathode) is highly positive—much more so than in the older - type *Synchroguide* circuit. Therefore, the meter should be placed on the +75-volt or higher scale to check E6. Placing the test probe on the cathode may detune the oscillator, but this situation can be corrected with the hold control. You should be able to vary cathode voltage from about +45 to +65 volts between the "oscillator fast" and "oscillator slow" ends of the hold-in range.

Alignment and Adjustment

Now that the horizontal frequency slug has been eliminated, alignment of the *Synchroguide* oscillator consists mainly of adjusting the waveform slug for maximum picture stability. During this process, the horizontal hold control is placed within the correct portion of its range.

In the earlier-type circuit, proper setting of the waveform slug was determined by direct observation of the waveshape of the oscillator-plate signal (Fig. 4). Since none of the signals in the new circuit give such a clear-cut indication of proper alignment, the slug-adjustment procedure is now carried out by watching the effect on the picture. Since no scope is required, the horizontal section can be aligned without removal of the chassis from the cabinet.

Here is a quick run-down of the alignment sequence: Short out the waveform coil by placing a jumper between the two lugs indicated in Fig. 2. Disable the AFC stage by grounding its grid; the easiest way to do this is to stick a soldering-aid tool into the test jack at pin 2 of the 6CG7 socket, and then ground the tool to chassis with a clip lead. Next, adjust the hold control for a reasonably steady picture—or for a sort of "horizontal roll" effect with an absence of diagonal tearing. Disconnect the jumper from the waveform coil, and adjust the slug to restore the steady or "rolling" condition. Finally, remove the short from the AFC grid and lock in the picture by means of the hold control.

Of course, adjusting the drive trimmer is part of any good horizon-

SUBSTITUTE PARTS WITH-OUT SOLDERING
Quickly with E-Z-Hook "SUB" Connectors. Has 1001 Uses!

Connect a speaker, or
Substitute a
• transformer
• capacitor
• resistor, or
In Seconds!!

★ Makes connections instantly!
★ Won't pull off!
★ Insures positive contact!
Saves time, money and parts in servicing, experimenting, instructing and production.

E-Z-HOOK SUB
No. 71-1...SUB...Only 69¢ ea.
Six Colors! - for Easy Lead-Identification
Canadian Rep.: Len Finkler & Co., Toronto, Ontario

ORDER THROUGH YOUR PARTS DISTRIBUTOR
E-Z-HOOK TEST PRODUCTS
Dept. F, 1536 Woodburn Ave.
Covington, Ky.

ALL NEW BERNS
PERFECT Audio
"PIN-PLUG" CRIMPER

SLIP WIRE IN "PIN-PLUG", INSERT IN TOOL, AND SQUEEZE. JOB IS DONE.
USE END OF BLADE AS SCREWDRIVER.
USE END OF TOOL TO PUSH ON GROUND CONNECTOR.

Useful in making hi-fi, audio and sound, radio, phono, and TV equipment connections.

only **\$1.25**

Here's a handy new crimping tool for making audio pin-plug connections without soldering. The insulated conductor is simply inserted through the pin. A squeeze of the crimper finishes the job—provides a real solid electrical connection. Braided shield ground connections are easy, too. The other end of the crimping tool is used to push on a copper C-ring clamp, eliminating soldering that melts heat-sensitive inner insulation.

IT'S DANDY... IT'S HANDY
"you'll like it!"

Available at your parts distributor.
Another fine product from:

BERNS Mfg. Co.
9853 Chalmers,
Detroit 13, Mich

SERVICE RADIO and TV
FAST!
HANDLE MORE JOBS...
MAKE MORE MONEY

TIME and know-how are your two best servicing tools. Are you making the most of them? These two Gernsback Library books show you how. Now spot hundreds of tough TV and radio troubles in seconds. Fix them in minutes. With these handy alphabetized listings of symptoms, troubles and cures you can tame the toughest "dog." Complete, cross-referenced where necessary. Hundreds of helpful photos, schematics, and troubleshooting charts. Be the most successful technician in your neighborhood—keep these two books on your workbench. Watch your servicing time speed up and your income climb! **Get your copies today.**

RAPID TV REPAIR — G/L Book No. 60
RAPID RADIO REPAIR — G/L Book No. 78
By G. Warren Heath
Paper covered editions \$2.90 ea.
Deluxe hard-cover editions \$4.60 ea.

SEE YOUR DISTRIBUTOR OR
Mail this coupon today

GERNSBACK LIBRARY INC., Dept. 119, PF
154 West 14th St.
New York 11, N. Y.

Please send me the books
below postpaid

No. 60 hard cover paper cover
No. 78 hard cover paper cover

81 77 76 72
 68 65 62 59

Name _____ please print
Street _____
City _____ Zone _____ State _____

VIS-U-ALL

BUSINESS BUILDING TEST EQUIPMENT FOR SERVICE DEALERS

NOW, VIBRATORS
and PORTABLE
RADIO BATTERIES

also
self-
service
checked



on the
NEW
V13C TUBE TESTER

Now, profits on self-service testing multiply. New V13C tests car radio vibrators (6 and 12-volt) and portable radio batteries (1.5 to 90 volts) in addition to over 800 TV-radio receiving tubes! New 3-color panel makes tests easier than ever for customers. V13C Counter-Type, only \$159.50; V13 Floor-type with 5-drawer storage base, only \$199.50.



Model
V-13

Write
for
Details

VIS-U-ALL
PRODUCTS CO.
643 EASTERN, S.E.
GRAND RAPIDS 6,
MICHIGAN



QUIETROLE

the ANSWER TO
NOISY CONTROLS
and SWITCHES

over
12 YEARS OF
PROVEN SUPERIORITY

Costs Just Pennies more than
the poorest substitute . . .

Supplied in Spray can and 2, 4, 8 oz. bottles



MFG BY
QUIETROLE
COMPANY, INC.
SPARTANBURG, South Carolina

tal sweep alignment. Instructions usually tell you to tighten the trimmer until a "wrinkle" or vertical white line appears through the middle of the picture, and then to back off until this drive line just disappears. Sometimes, however, this indication is not sufficiently clear to let you make the drive adjustment with complete confidence. In such cases, try hooking up a scope and viewing W1 (Fig. 1) while you turn the trimmer. Tighten down the screw until the positive peaks of the waveform become noticeably more flattened; then back off until the distortion disappears. After completing this adjustment, check the cathode current of the output tube. A normal value for these 110° sets is 125 ma. If current seems excessive, try tightening the trimmer slightly. Suspect trouble if the trimmer adjustment does not bring the cathode current down to the prescribed level without putting a drive line in the picture.

Service Pointers

Since the revised *Synchroguide* circuit works fundamentally the same as the previous version, trouble-symptom analysis is similar for both designs. For example, the picture distortion known as "hunting" or "pie-crust effect" is most often produced by defective components in the AFC cathode circuit; random-frequency operation or "Christmas-tree effect" is commonly due to leaky or off-value capacitors in the oscillator stage; and drifting of oscillator frequency is usually caused by leakage or gas in the 6CG7 or by a heat-induced change in the value of some associated component.

Judging from the parts lists of the newest RCA receivers, the capacitors in the horizontal section have been chosen with an eye toward protecting the oscillator against frequency drift and other subtle defects. In the future, this should minimize the need for a serviceman to resort to the "shotgun blast" repair technique—wholesale replacement of all capacitors in the oscillator circuit.

The latter method can cause more trouble than it cures, if replacements are not selected with care. Here are a few capacitors which you may not have in stock, but should obtain if the need arises: A highly stable

.01-mfd tubular unit (C6) with Mylar and styrene dielectric; two 1000-volt types (C5 and C8) with 5% and 10% tolerance ratings; and an N750 ceramic disc capacitor (C4) with a negative temperature coefficient to counteract drifting of oscillator frequency during warm-up. ▲

STATEMENT REQUIRED BY THE ACT OF AUGUST 24, 1912, AS AMENDED BY THE ACTS OF MARCH 3, 1933, AND JULY 2, 1946 (Title 39, United States Code, Section 233) SHOWING THE OWNERSHIP, MANAGEMENT, AND CIRCULATION OF PF REPORTER published monthly at 2201 E. 46th St., Indianapolis 6, Ind. for October 1, 1959.

1. The names and addresses of the publisher, editor, managing editor, and business managers are:

Publisher: Howard W. Sams, 2201 E. 46th St., Indianapolis, Ind.; Editor: Verne M. Ray, 2201 E. 46th St., Indianapolis, Ind.; Managing Editor: None; Business Manager: Mal Parks, Jr., 2201 E. 46th St., Indianapolis, Ind.

2. The owner is: (If owned by a corporation, its name and address must be stated and also immediately thereunder the names and addresses of stockholders owning or holding 1 percent or more of total amount of stock. If not owned by a corporation, the names and addresses of the individual owners must be given. If owned by a partnership or other unincorporated firm, its name and address, as well as that of each individual member, must be given.)

Howard W. Sams & Co., Inc., 2201 E. 46th St., Indianapolis, Ind.; Alan S. Brengle, 28423 Kendallwood Dr., Farmington, Mich.; Jean B. Eldred, Redwood Drive, Franklin, Ky.; Paul F. Grubbs, 925 N. Audubon Rd., Indianapolis, Ind.; Edward D. James, 122 E. Michigan, Indianapolis, Ind.; Harold Knox, Zionsville, Ind.; J. A. Milling, 7905 Morningside Dr., Indianapolis, Ind.; Mrs. Lucile Overbay, 5768 Washington Blvd., Indianapolis, Ind.; Raffensperger, Hughes & Co., 20 N. Meridian, Indianapolis, Ind.; James R. Ronk, 6160 Primrose Ave., Indianapolis, Ind.; Howard W. Sams, 414 Kessler W. Dr., Indianapolis, Ind.; Donald B. Shaw, 3419 N. Pennsylvania, Indianapolis, Ind.; Benjamin T. White, 120 E. Market St., Indianapolis, Ind.

3. The known bondholders, mortgagees, and other security holders owning or holding 1 percent or more of total amount of bonds, mortgages, or other securities are: (If there are none, so state.)

Armer F. Ahlstrand, 335 Wilty Ave., Rockford, Ill.; Associates Life Insurance Co., 111 Monument Circle, Indianapolis, Ind.; Ad Auriema, 89 Broad Street, New York, N. Y.; Charles R. Barker, P.O. Box 384, Fredonia, N. Y.; John D. & Ruth E. Baur, 3239 Sutherland, Indianapolis, Ind.; Mary M. Benham, 215 N. Senate, Indianapolis, Ind.; Bertha & Frieda Binninger, 3510 Watson Rd., Indianapolis, Ind.; Ralph T. Brengle, Potter & Brumfield, Princeton, Ind.; Bruce & Lorraine Cumming, 6029 W. Belmont, Chicago, Ill.; Glen Dial, 812 Truman St., N. E., Albuquerque, N. M.; Herbert J. Farr, Jr., 3297 Enderby Rd., Cleveland 20, Ohio; Paul F. Grubbs, 925 N. Audubon, Indianapolis, Ind.; Elmer C. Hodges, 1100 Union St., San Francisco, Calif.; Joconat & Co.-Dept. 551, 3911 Prairie Lane, Prairie Village 15, Kansas; M. S. Kiver, 900 Fairview Rd., Highland Park, Ill.; Grace Knox, 505 W. Oak St., Zionsville, Ind.; Harold S. Knox, Zionsville, Ind.; Michelle Fern Koplow, 7035 N. Meridian, Indianapolis, Ind.; Robert J. Lewis, 5800 Lawrence Dr., Brendenwood, Indpls. 26, Ind.; Fernanda D. Milling, 7905 Morningside Dr., Indianapolis, Ind.; Margo Milling, 7905 Morningside Dr., Indianapolis, Ind.; Jack B. Moore, 128 W. Worth St., Worthington, Ohio; Melvin R. Moser, 864 McGill St., Orrville, Ohio; Frieda & Harold Neil, 5026 N. Hillside, Indianapolis, Ind.; Lucile Overbay, 5768 Washington Blvd., Indianapolis, Ind.; Mrs. Norman A. Perry, Sr., E. Shore Dr., Culver, Ind.; Edward E. Petri, Guaranty Bldg., Indianapolis, Ind.; James R. & Phylis M. Ronk, 6160 Primrose, Indianapolis, Ind.; O. T. Smith, W. 918 Long Point, Culver, Ind.; Kenneth Swan, 4243 Broadway, Indianapolis, Ind.; Typographic Service Co., Inc., 215 N. Senate St., Indianapolis, Ind.; Charles W. Vandenberg, P.O. Box 55266, Indianapolis, Ind.; The Estate of Lynne Ann Wavering, Continental-Illinois Bank & Trust Dept., 231 So. LaSalle, Chicago, Ill.; Benjamin T. White, 120 E. Market, Indianapolis, Ind.

4. Paragraphs 2 and 3 include, in cases where the stockholder or security holder appears upon the books of the company as trustee or in any other fiduciary relation, the name of the person or corporation for whom such trustee is acting; also the statements in the two paragraphs show the affiant's full knowledge and belief as to the circumstances and conditions under which stockholders and security holders who do not appear upon the books of the company as trustees, hold stock and securities in a capacity other than that of a bona fide owner.

(Signed) MAL PARKS, Jr., Bus. Mgr.
Sworn to and subscribed before me
this 30th day of September, 1959
(Seal) Mary Helen Whipp, Notary Public

PRODUCT report

For further information on any of the following items, circle the associated number on the Catalog & Literature Card.

Soldering-Gun Heat Control (43J)



Tip temperature of a soldering gun can be made low enough for safe use on printed wiring boards, if line current is fed to the gun through the *Gunchoke* manufactured by Electric Soldering Iron Co., Inc. The device can be adjusted to produce a tip temperature of either 500° or 600°. Models are available for use with all popular types of guns.

Tuner and Control Cleaner (44J)



A tuner and control cleaner called *Rx*, manufactured by Superex Electronics, contains a "detergent - lubricant" which coats the contact surfaces and provides a cleaning and lubricating action each time the contacts are actuated. The net price of \$1.19 per 6-oz. aerosol can includes a detachable injector-type applicator.

Portable Phonographs (45J)



CBS Electronics announces a new *Harmony* line of portable phonographs, to be marketed exclusively through the company's parts distributors. Model 220 (shown) is a stereo unit with four-speed changer and twin 5" speakers; its list price is \$79.95. Two other stereo and two monophonic models are also available in a price range of \$24.95 to \$99.95.

CRT Brightener Deal (46J)



A special promotional package offered by Perma-Power includes 12 *Vu-Brite* picture tube brighteners and a windproof cigarette lighter, all packed inside a bag made of heavy-gauge clear plastic. The cost is \$9.95—the regular net price of the 12 brighteners. The serviceman may choose units for either series-string or parallel-filament operation.


\$100.00 CASH REWARD

... for the location of any of the following stolen receivers:

Admiral, serial Nos. 7-147559, 7157997, 7211556, and 6-782330; General Electric, serial Nos. 256754, 256852, 256967, 257983, and 258239; Philco, serial Nos. BC-5008, 549813, and 7152708.

Contact by phone or wire, Carl C. Schmidt, Inspector of Detectives, Indianapolis Police Dept., Indianapolis, Ind.

Cartridge replacements ahead!

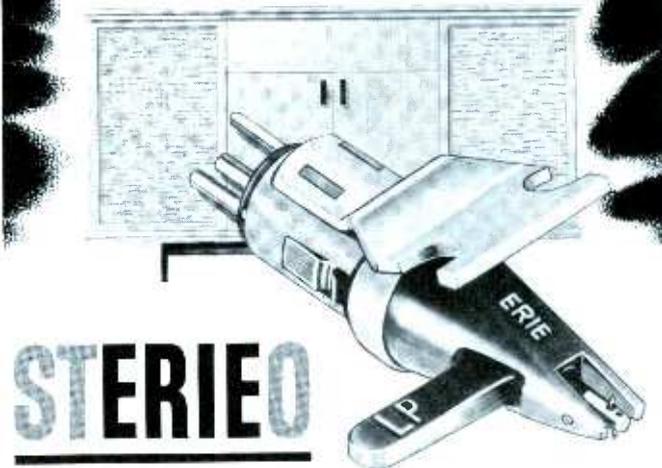

now original equipment on
leading **STERIEO** sets

The STERIEO single-element ceramic cartridge is now used as original equipment by a number of leading manufacturers of packaged stereo systems. The names of these O.E.M.s using STERIEO and the corresponding part numbers are available from your Erie distributor. He can also furnish you with complete stocks of this high-quality, high-profit cartridge.

Audio engineers specify STERIEO because it delivers the three most important qualities of stereo... balanced channel outputs, high channel separation, full frequency response.


But test STERIEO yourself. Compare its quality and compare its low price... dual stylus—sapphire/sapphire conversion kit only \$8.95 list; replacement unit, \$6.95 list. Then recommend STERIEO to your customers for all their stereo work—replacement and conversion.

STOCK UP NOW

For the name of your Erie distributor write to:


ERIE Electronics Distributor Division
ERIE RESISTOR CORPORATION
Erie, Pennsylvania

High-Value Ceramic Capacitors (47J)

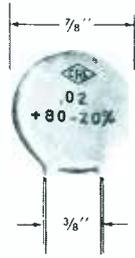

Centralab "DD" Series *Hi-Kaps* (ceramic disc capacitors for bypass, coupling and filter applications) are now being supplied in three new values of .03, .04 and .05 mfd, all rated at 600 WVDC. Measuring $\frac{7}{8}$ " in diameter and $\frac{3}{16}$ " thick, the new units are impregnated with high-melting-point wax, and are sealed in a coating of *Durez* resin.

Stereo Tape Deck (48J)

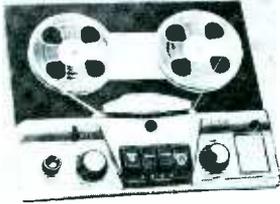

The Arkay/Harting MS-5 tape deck provides stereo recording and playback at either $3\frac{3}{4}$ " or $7\frac{1}{2}$ " per second. Metal guards prevent vertical movement of the tape as it passes over the heads. Other specifications include a $\frac{1}{2}$ " diameter capstan, push-button controls, dimensions of $12\frac{3}{8}$ " x $14\frac{1}{2}$ " x $6\frac{1}{4}$ ", and a price of \$129.95.

Miniature Electrolytics (49J)



Fifteen electrolytic capacitors, comprising five of the most popular values used in current models of transistor radios, are packaged in the Pyram No. 515 *Transistor Radio Maintenance Assortment*. Contents include four 6-mfd, four 12-mfd, three 25-mfd, two 50-mfd, and two 100-mfd units, all rated at 12 WVDC. Net price, complete with clear plastic box, is \$7.70.


Silicon Power Rectifiers (50J)

International Rectifier has introduced a new series of seven silicon rectifiers designed as exact plug-in replacements for vacuum-tube rectifiers. Of special interest to radio-TV servicemen are Type ST-1 (which replaces the 6X4 and 12X4); the ST-2 (which replaces the 5Y3GT, 5U4GB, 5AW4, etc.); and the ST-3 (which replaces the 6X5, 0Z4, and similar types).



Antenna Mounting Feature (51J)

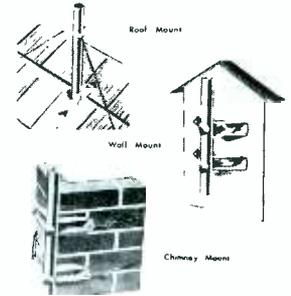All models in the Clear Beam line of do-it-yourself antenna kits are equipped with *Miracle Mount* brackets which are adaptable to many different types of installations. They may be used as a base for a roof-mounted antenna, fastened to a wall, or adjusted to form right-angle braces which serve as firm points of attachment for straps or cables in chimney-mount installations.



Phono Cartridge Display Rack (52J)

A dispenser rack with a gold, white and blue finish, accommodating 35 phono cartridges and 29 needles, is being offered to dealers by Sonotone. The unit can be employed as a free-standing counter display, or else mounted on a wall; in addition, two or more racks can readily be stacked to provide greater storage capacity. Furnished with the dispenser is a reference chart of Sonotone stereo cartridge replacement data.

YOU CAN ALSO DO THE BIG JOBS WITH WIZARDS



HOME - 7 Outlets - One Antenna - No Amplification; Residence of Bob Barker, MC of the popular daytime NBC show *Truth Or Consequences*.



HOTEL - 120 Outlets - One Antenna - One Amplifier; The Montecito - 6650 Franklin, Hollywood, California.



THE WIZARD 300*

ELECTRO-MAGNETIC COUPLER FOR ALL SINGLE ANTENNA MULTIPLE-OUTLET SYSTEMS IN TV FLAT LINE

*Pat. Pend

\$1.95
LIST PRICE

The high electrical efficiency of the Wizard 300 is proven in many installations where more than thirty receivers are being operated from a single antenna without amplification.

Information on any of the above jobs and a brochure covering Wizard System installations is available. Write Dept. PF119

CHARLES ENGINEERING, INC.
6053 Melrose Avenue • Los Angeles, California



HOUSING PROJECT - 2,549 Wizards Installed To Date; L.A. Housing Authority, Los Angeles, California.



APARTMENT - 39 Outlets - One Antenna - No Amplification; The Del Rio - 10236 Old River School Road, Downey, Calif



APARTMENT - 48 Outlets - Two Antennas (24 Outlets each) - No Amplification; The Paramount Riviera - 12447 Paramount Blvd., Downey, California.

Controlled Pickup Arm (53J)



The *Connoisseur* stereo tone arm, imported from Britain by Ercona, features "cushioned control"—a system in which the arm is gently lowered or raised by rotation of a knob. Arm length is 10 $\frac{1}{4}$ "; stylus force is 3 gm. The unit comes equipped with a ceramic pickup having a .6-mil diamond stylus and an output of 20 mv (into a 50K-ohm load). Price is \$59.50.

Rechargeable Batteries (54J)



Hermetically-sealed nickel-cadmium batteries, which can be repeatedly recharged, have been announced by Burgess Battery Co. Basic 1.25-volt cells are stacked together (using a conductive silver wax) to form various battery types. These "building block" cells are made in six sizes having different current capacities. Single-cell batteries are also available in Sizes AA and D.

Four-Track Tape Heads (55J)



A set of heads for conversion of dual-track tape recorders to four-track stereo operation is available from Robins. The new record-playback head, Model 5Q8, which is electrically and mechanically interchangeable with Robins M/M B&L Series heads, has a list price of \$30. A companion unit, the four-track Model 9QE3 erase head, is priced at \$14.

Parts Storage Cabinet (56J)



Akro-Mils storage cabinets for small parts are fitted with clear plastic drawers 2" high and 11" deep. Two drawer widths, 3" (M3 Series) and 4" (M4 Series) are available. Features of individual drawers include a stop tab at rear, full-length runners, label slots, and adjustable inner partitions. The welded steel cabinets are made in various sizes holding from 6 to 60 drawers.

Stereo Styli (57J)



An improved Mk II version of the Pickering *T-Guard* stylus, for Model 371 Stanton *Stereo Fluxvalve* cartridges, offers higher output (now 12 mv per channel) and thus a better signal-to-noise ratio. A built-in shock-absorbing feature also provides *controlled* (i.e., self-regulating) compliance. Model D3707A, with a tracking-force range of 2-5 gm for transcription arms, and D3707C, with a range of 3-7 gm for changers, have .7-mil diamond tips; Model S3727 MkII has a 3-mil sapphire.

Here's a Bargain!

SPECIAL OFFER!

VACO

Nut Driver—
Voltage Checker & Probe
Utility Set

you get

Two New Design VACO Nut Drivers (1/4" and 11/32")
Plus Brand New Voltage Checker & Probe

A \$2.50 Value

Only \$1.79 Net



You'll find a hundred uses for this probe. It's a voltage checker, electric tester, etc. Full instructions included.

GET ACQUAINTED OFFER: We make this unique offer for a LIMITED time only to acquaint you with VACO'S beautiful new line of Nut Drivers with full polished chrome shafts, colored-for-size handles and extra hard sockets that WON'T round out. Get your set, today!

See Your Parts Jobber or Write

VACO PRODUCTS COMPANY, 317 E. Ontario St. Chicago 11, Illinois
In Canada: Atlas Radio Corp., Toronto 19, Ontario

The NEW YEATS "Shorty" STATION WAGON & PANEL PICK-UP appliance dolly



YEATS Model No. 5

Aluminum alloy
Height 47"
Weight 32 lbs.

Only 47" tall, this new YEATS dolly is designed for TV and appliance men who make deliveries by station wagon or panel truck. No need to detach appliance for loading into the "wagon" or pick-up . . . the YEATS "Shorty" will slide into your vehicle with ease. Has aluminum alloy frame with padded felt front, quick fastening (30 second) strap ratchet, and endless, rubber belt step glide. New YEATS folding platform attachment, at left, saves back-breaking work handling TV chassis or table models. Call your YEATS dealer today!



Folding platform is 13 $\frac{1}{2}$ " x 24 $\frac{1}{2}$ " —attaches instantly. (Platform only) \$9.95.



Furniture Pad

SEND postcard for full information on our complete line TODAY!

YEATS appliance dolly

2103 N. 12th St.



TV Cover

sales co.

Milwaukee, Wis.

NOVEMBER, 1959

Acme Electric Corp. 70
 American Television & Radio Co. (ATR) 14
 Amphenol-Borg Electronic Corp. 56
 Arco Electronics, Inc. 71
 Astatic Corp. 9
 B & K Mfg. Co. 43, 54
 Belden Mfg. Co. 31
 Berns Mfg. Co. 66, 91
 Blonder-Tongue Labs 45
 Bulldog Electric Products Div. I-T-E Circuit Breaker Co. 52
 Bussmann Mfg. Co. 47
 CBS Electronics 15, 16-17
 Castle TV Tuner Service 84
 Centralab, A Div. of Globe-Union, Inc. 73
 Charles Engineering, Inc. 94
 Chemtronics, Inc. 80
 Chicago Standard Transformer Corp. 82
 Clarostat Mfg. Co., Inc. 21
 Clear Beam Antenna Corp. 63
 Cornell-Dubilier Electric Corp. 42, 55, 69
 Delco Radio Div., General Motors Corp. 13
 Doss Electronic Research, Inc. 60, 70, 90
 Duotone Co., Inc. 62
 EICO 87
 E-Z-Hook Test Products 91
 Electric Soldering Iron Co. 66
 Electro-Voice, Inc. 25
 Electronic Publishing Co. 62
 Erie Resistor Corp. 93
 General Cement Mfg. Co. 2nd Cover
 General Electric Co.—
 Electronic Components Div. 22-23
 Gernsback Library, Inc. 91
 Hickok Electrical Instrument Co. 67
 Injectorall Co. 88
 International Rectifier Corp. 61
 JFD Electronics Corp. 12
 Jackson Electrical Instrument Co. 40, 96
 Jensen Mfg. Co. 39
 Jerrold Electronics Corp. 75
 Littelfuse, Inc. 4th Cover
 Mallory & Co., Inc., P.R. 26-27
 Merit Coil & Transformer Corp. 74
 Ohmite Mfg. Co. 86
 Oxford Components, Inc. 88
 Perma-Power Co. 46
 Philco Corp.—Accessories Div. 44
 Pyramid Electric Co. 50
 Quietrol Co. 92
 RCA Electron Tube Div. 59, 3rd cover
 Raytheon Co.—
 Distributor Products Div. 28-29
 Reeves Soundcraft Corp. 80
 Sampson Co.—Electronic Utilities Div. 53
 Sams & Co., Inc.,
 Howard W. 57, 76, 77, 80, 90
 Sarkes Tarzian, Inc. (Rectifier Div.) 41
 Seco Mfg. Co. 38
 SENCORE 79, 81, 83, 85
 Sonotone Corp. 20
 South River Metal Products Co. 74
 Sprague Products Co. 10
 Sylvania Electric Products, Inc.—
 Semiconductor Div. 72
 Television Receiver Div. 78
 Technical Appliance Corp. (TACO) 74
 Tenna Mfg. Co. 51
 Triplett Electrical Instrument Co. 18-19
 Tung-Sol Electric, Inc. 49
 Vaco Products Co. 95
 Vis-U-All Products Co. 92
 Webster Electric Co. 65
 Weller Electric Corp. 89
 Xcelite, Inc. 62
 Yeates Appliance Dolly Sales Co. 95

ANTENNA SYSTEMS

- 1J. **ANTENNA SPECIALISTS** — 16-page catalog plus data sheets on complete line of communications antennas and accessories, including stationary, mobile, and portable types.
- 2J. **CLEAR BEAM**—Information on *Miracle Mount* "do-it-yourself" antenna kits. See ad page 63.
- 3J. **JFD** — New 24-page catalog of UHF, VHF, FM and indoor TV antennas and accessories, plus hi-fi speakers and TV accessories. See ad page 12.
- 4J. **JERROLD**—16-page booklet on the amplified TV-FM Home System shows how to obtain optimum TV and FM reception using a number of outlets throughout the home. See ad page 75.
- 5J. **TACO** — Revised price list and catalog sheets on antennas, accessories, and FM promotion kit. See ad page 74.

AUDIO & HI-FI

- 6J. **ASTATIC**—Catalog 33-3 containing complete listing and descriptions of cartridges, microphones, pickups, and needles. See ad page 9.
- 7J. **CLAROSTAT**—Form 75177301C, with data on line of sound system controls, including T- and L-pad combinations, constant-impedance attenuators, etc., plus diagrams showing typical applications and wiring instructions. See ad page 21.
- 8J. **ELECTRO-VOICE** — Catalog #136 for 1960 in a new two-section binding. Section one covers hi-fi products; section two describes microphones, commercial sound (public address), RME communications equipment, and replacement phono cartridges. See ad page 25.
- 9J. **PHILCO**—Catalog for full line of new speakers covering every application. See ad page 44.

CAPACITORS

- 10J. **MALLORY**—New 28-page capacitor catalog in step-down wall-chart form. See ad pages 26-27.
- 11J. **SPRAGUE** Large, 2-color *Ceramichart*, with circuit diagrams showing typical ceramic capacitor applications in radio and TV, plus color-code specifications for ceramic and molded mica capacitors. See ad page 10.

CARTRIDGES & NEEDLES

- 12J. **ERIE** — Brochure with description and full technical specifications on the *STEREIO* cartridge, plus literature on the "PAC" audio amplifier kit for converting any record player to stereo. See ad page 93.

SEMICONDUCTORS

- 13J. **INTERNATIONAL RECTIFIER**—Bulletin SR-208 describes 2E4 and 5E4 silicon diode rectifiers; also, Bulletin JB-510, which describes silicon TV replacement rectifiers and hi-density selenium stacks. See ad page 61.
- 14J. **SAMPSON** — Component catalog and transistor literature. See ad page 53.

FUSES

- 15J. **BUSSMANN**—Completely new television fuse chart describing proper fuses to use, how they are mounted, and which circuits they protect. See ad page 47.

SERVICE AIDS

- 16J. **CHEMTRONICS** — Flyers describing complete line of electronic servicing chemicals, including *No-Arc* high-voltage insulator. See ad page 80.
- 17J. **E-Z-HOOK**—Convenient reference sheet titled, "How to Build the Five Most Useful Scope Probes," with schematics, mechanical component layouts, etc. See ad page 91.
- 18J. **YEATES** — Literature describing aluminum-alloy appliance dollies and padded appliance delivery covers. See ad page 95.

SPECIAL EQUIPMENT

- 19J. **ACME**—New catalog entitled, "Variable Voltage Adjustors," discusses high and low line voltage problems, and tells you how to select the right Voltage Adjustor for the job. See ad page 70.
- 20J. **ANTRONIC CORP.**—Literature on Anchor *NEV-A-BREAK SOC-KIT*, the replacement socket for CRT testers.
- 21J. **ATR** — Brochure describing customized *Karadios* for small import cars and compact American cars. Eight models available. See ad page 14.

- 22J. **BULLDOG**—Literature on *Electrostrip*, the new multi-outlet assembly that lets you position AC line outlets as needed. See ad page 52.
- 23J. **PERMA-POWER** — New catalog sheet illustrating and describing the Automatic Voltage Regulator and its uses in eliminating picture flutter, shrinking, flop-over, loss of brightness and other similar TV troubles. See ad page 46.

TECHNICAL PUBLICATIONS

- 24J. **GERNSBACK**—Descriptive literature on Gernsback Library books. See ad page 91.
- 25J. **HOWARD W. SAMS** — Literature describing all Howard W. Sams publications covering servicing of radio, TV, hi-fi, etc. Includes data on "Tube Location Guide," "Printed Circuit Diagnosis Made Easy," "Servicing Transistor Radios, Volume 4," "101 Ways to Use Your Audio Test Equipment," and "Tape Recorder Manual, Volume 5." See ads pages 57, 76, 77, 80, 90.

TEST EQUIPMENT

- 26J. **B & K**—Bulletin ST24-R gives helpful information on how to save time and work, and make money with point-to-point, signal-injection, direct-viewing Model 1075 Television Analyst, Models 550 and 650 dynamic mutual-conductance tube testers, Model 675 automatic tube tester, and Model 440 CRT cathode-rejuvenator tester. See ads pages 43, 54.
- 27J. **DOSS**—Information on the latest in test equipment, including the *Pioneer 250* Horizontal Systems *Quantalyst*. See ads pages 60, 70, 90.
- 28J. **EICO**—20-page 1959 2-color catalog describes 65 models of professional test instruments, hi-fi, and "ham" gear in both kit and factory-wired form. Shows how to save 50%. Also, 4-page 2-color stereo hi-fi guide. See ad page 87.
- 29J. **HICKOK** — Literature describing new transistor checker, Model 850. See ad page 67.
- 30J. **JACKSON**—2-color folder showing complete line of "service-engineered" test equipment. See ads pages 40, 96.
- 31J. **SECO** — New 2-color folder describes latest low-priced tube tester Model 78, Dynamic Transistor Checker Model 100, and all other Seco test equipment. See ad page 38.
- 32J. **SENCORE**—4-page brochure on complete line of time-saver instruments. See ads pages 79, 81, 83, 85.
- 33J. **TRIPLETT**—New test equipment catalog No. 39-T describes and illustrates many VOM and VTVM models; signal, sweep, dot-bar, and color-bar generators; appliance, tube and transistor testers; plus wide-band, high-sensitivity 5" oscilloscope. See ad pages 18-19.
- 34J. **VIS-U-ALL** — Catalog #59A contains complete description of business-building test equipment. See ad page 92.

TOOLS

- 35J. **BERNS**—Data on the 3-in-1 picture tube repair tool that crimps pin and element lead to make a solid electrical connection and also serves as screwdriver and channel selector, plus data on the new "Audio Pin-Plug" crimper that lets you make pin-plug and ground connections for shielded cables. See ads pages 66, 91.
- 36J. **CHAMPION**—Folder on line of specially-designed *Channellock* pliers and cutters for electronic servicing.
- 37J. **ESICO** — Information on the *GUN-CHOKE*, a simple and inexpensive device that reduces tip temperature for soldering on printed-circuit or laminated boards. See ad page 66.
- 38J. **VACO**—Catalog pages on new insulated solderless terminals, plus special offer on new service tools. See ad page 95.
- 39J. **WELLER** — Catalog sheet describing complete line of soldering equipment and power tools. See ad page 89.
- 40J. **XCELITE**—Latest catalog on complete line of tools for radio, TV, and electronic servicemen. See ad page 62.

TRANSFORMERS

- 41J. **CHICAGO STANDARD** — New 36-page 1959-60 catalog containing detailed specifications on replacement transformers for radio, TV, industrial, and hi-fi equipment. See ad page 82.

TUBES

- 42J. **CBS**—New picture tube wall chart, PF-288, lists mechanical and electrical characteristics for more than 360 tubes and popular replacement types. See ad pages 15, 16-17.



MODEL 648		MODEL 49	
TUBE TYPE	PLATE CATH. TEST	SEC. A. B. C. D. SHORTS	GRID HEATER CURRENT
3EA5	3.0 A234 AC156 18XZ	P 3.0 3 2X 156 7 30	300
6DE4	6.3 234 6 14W	D 6.3 7 - 5 3 4	300
12BE6	12.6 AC1204 567- 15WY	P 12.6 3 X 1967 2 30	300
6095	12.6 123 4A5 25Y2	T 6.3 9 - 17 3 8	300
6086	6.3 A1236 B579 50WV	P 6.3 4 - 278 3 4	300

MODEL 658		GRID HEATER CURRENT	
TUBE TYPE	HEATER H-K P-G PLATE TEST	GRID HEATER CURRENT	HEATER CURRENT
3EA5	3.0K 124 ac356 32R 10WY	300	300
6DE4	6.4L 234 6 18U 10WY	300	300
6095	13.6E 1247 ac356 35R 15WY	300	300
6086	13.6G 127 48S 25Q 25WY	300	300
6086	13.6G 123 44S 25Q 25WY	300	300
6086	6.4J 1236 b579 45Q 20WY	300	300

Latest Chart Form 648-22, 49-5, 658-2

**For top customer value...
top dealer profits...
promote RCA Silverama Picture Tubes!**

Of the 3 largest-selling brands of replacement TV picture tubes...

**Only RCA
Guarantees you
an All-New Tube**




Let's face it—when you have to replace your TV picture tube, it means a sizeable investment. Doesn't it make sense, then, to be sure that the tube you get is *all-new*? That's why you should bear this in mind: Of the 3 largest-selling brands of replacement TV picture tubes, only 1... RCA... offers you a line of completely all-new tubes... RCA Silverama!

**With RCA Silverama,
you know what you're getting!**

RCA guarantees that each and every Silverama picture tube is all-new, totally new... new glass, new phosphor, new gun, new everything... and gives you the added assurance of a full-year warranty.

If your TV picture tube needs replacing, guarantee yourself the clearest, sharpest picture possible—insist on an RCA Silverama. There's one to fit virtually every make and model TV set. Ask your TV technician for complete information and prices.

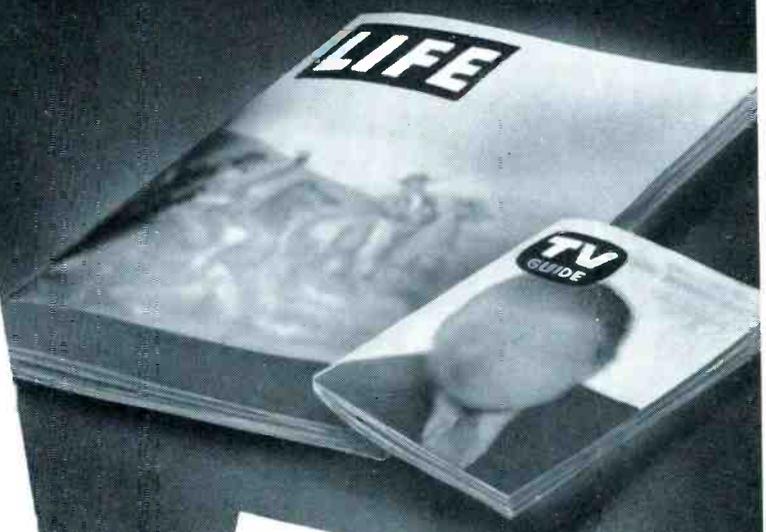 **RADIO CORPORATION OF AMERICA** - Electron Tube Division, Harrison, N. J.



Of the 3 largest-selling brands of replacement TV picture tubes...

**Only RCA
Guarantees you
an All-New Tube**

Let's face it—when you have to replace your TV picture tube, it means a sizeable investment. Doesn't it make sense, then, to be sure that the tube you get is *all-new*? That's why you should bear in mind: of the 3 largest-selling brands of replacement TV picture tubes, only 1... RCA... offers you a line of completely all-new tubes... RCA Silverama!

With RCA, you know what you're getting!

RCA guarantees that each and every Silverama picture tube is all-new, totally new... new glass, new phosphor, new gun, new everything... and gives you the added assurance of a full-year warranty.

If your TV picture tube needs replacing, guarantee yourself the clearest, sharpest picture possible—insist on an RCA Silverama. There's one to fit virtually every make and model TV set. Ask your TV technician for complete information and prices.

 **RADIO CORPORATION OF AMERICA** - Electron Tube Division, Harrison, N. J.

Ads like these in Life and TV Guide are pre-selling millions of TV-set owners on RCA Silverama Picture Tubes. Cash in!



RADIO CORPORATION OF AMERICA
Electron Tube Division
Harrison, N. J.

Silverama®

dealer-serviceman's fuse rack . . .

. . . for wall mounting

LITTELFUSE

most
needed



most
wanted

. . . the FUSEMASTER!



dealer-serviceman's fuse
requirements at a glance