

NOVEMBER, 1960

35 CENTS



# RF REPORTER

including **Electronic Servicing**

# SPOTLIGHTING

# the 1961

# TV LINES

Magnetic Amplifiers

The Expanding FM Radio Field

Direct Drive Sweep Troubles


Understanding Transistor Testers

12 OK 7456 1266  
WM. H. DAVIS  
RAD. & TV SERV.  
118 RIVERSIDE AVE.  
CANON CITY, COLO.



# BRIGHT NEW VIEW

for Multi-set TV-FM Home Operation...

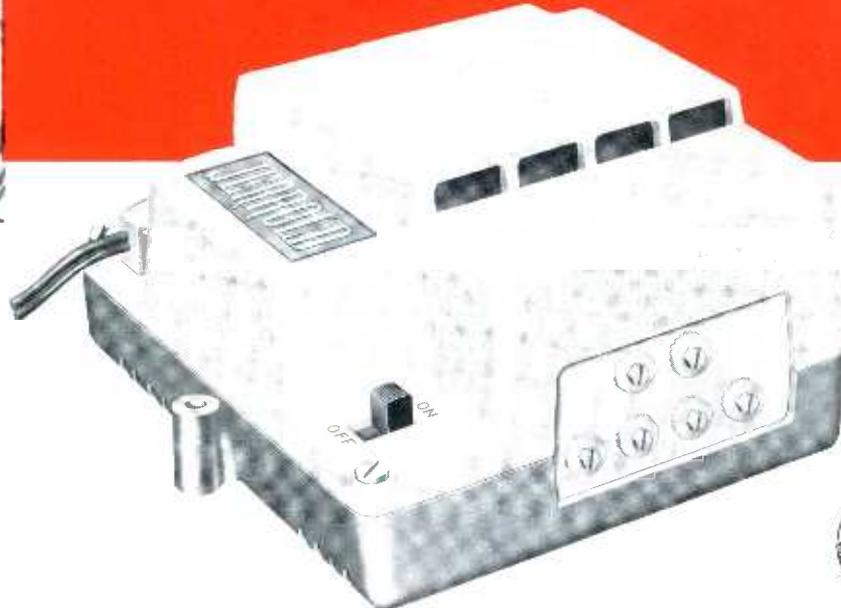

... and a

Bright Profit Outlook for YOU with

**NEW**

**JERROLD**


**HSA-43**

## Amplified 3 SET COUPLER

Here's a new precision-perfected amplifier that provides *5 DB min. gain across all TV-FM channels* on two outputs and no loss in the third output. Housed in a rugged, compact and handsome case. The HSA-43 features single tube operation (6DJ8), A.C. interlock and no-strip twin lead terminals. Its excellent isolation and match prevents set interaction and ghosting. IDEAL FOR FEEDING ONE FM AND TWO TV SETS FROM THE SAME ANTENNA.

**\$29.95 list**



### TYPICAL APPLICATIONS

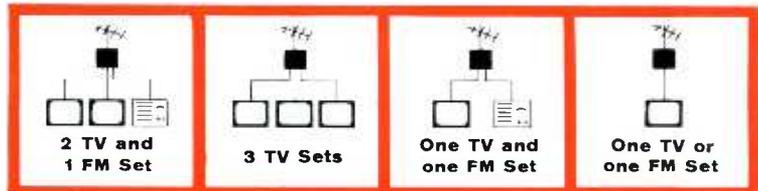

Write Jerrold today for full details on this new Profit Outlook!

**JERROLD** ELECTRONICS CORPORATION, Distributor Sales Division  
Dept. IDS-81, Philadelphia 32, Pa.  
Jerrold Electronics (Canada) Limited, Toronto  
Export Representative: CBS International, New York 22, N.Y.

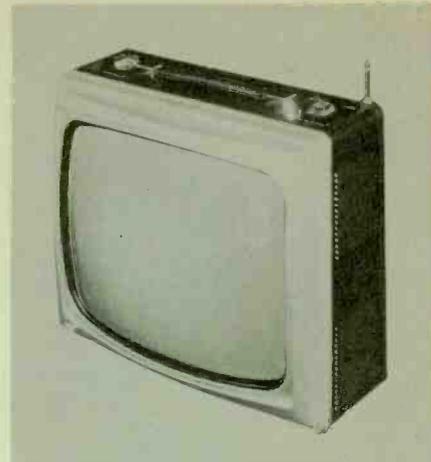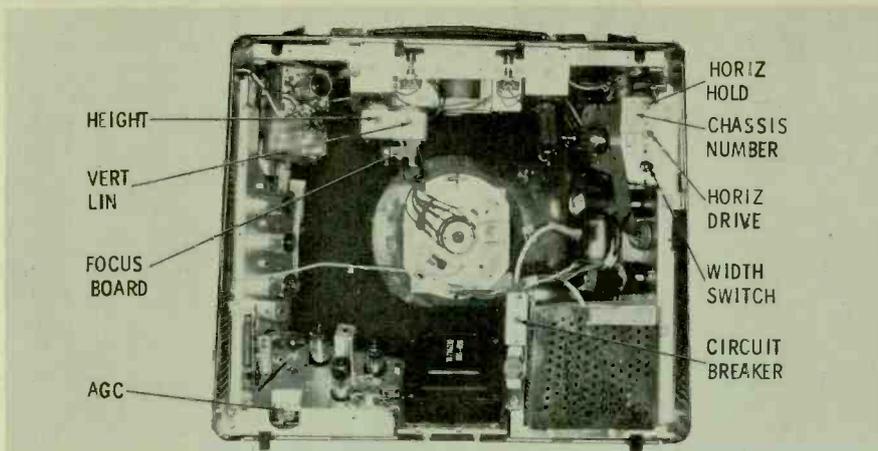LEADER AND LARGEST MANUFACTURER OF TV DISTRIBUTION SYSTEM EQUIPMENT



### Hoffman Model K1919 Chassis 355





Hoffman's 1961 portable line is represented by this 19", 110° model with bonded safety shield. Three different-colored cabinets of the same design make up the entire series. All are equipped with a monopole antenna, which is built into the rear cover along with a matching balun transformer. Operational controls are top-mounted; thumb-wheel knobs protruding through the upper part of the back cover control brightness and vertical hold.


The rather unusual 16-tube chassis nestles compactly around all four sides of the picture-tube bell. Conventionally wired, the component sides of the chassis are easily accessible after removal of the wrap-around cabinet (nine screws hold it in place). A strip of metal foil taped to the neck of the picture tube under the yoke provides proper horizontal linearity. When replacing the picture tube, be sure to tape the foil strip in the same location on the new tube. Also, be sure to use Mylar tape or the equivalent to prevent the possibility of arc-through.

The top part of the chassis carries the 6BQ5/EL84 audio output stage and a 6DE7 combined vertical multivibrator and output. Since the vertical circuits are supplied with boost voltage through the height control, and B+ through the output transformer, this part of the chassis is ideal for the location of the focus terminal board.

The left and right chassis contain the RF, IF, video, and horizontal sweep circuits. The subchassis with the 6CG7 horizontal oscillator circuit is mounted at a more extreme angle to provide room for the speaker. The yoke plug contains a jumper to complete the cathode circuit of the horizontal output tube. Since the phosphor of the picture tube may be damaged if the yoke plug or any tube in the horizontal circuit is removed while power is supplied to the set, be sure to disconnect the power before breaking these circuits.

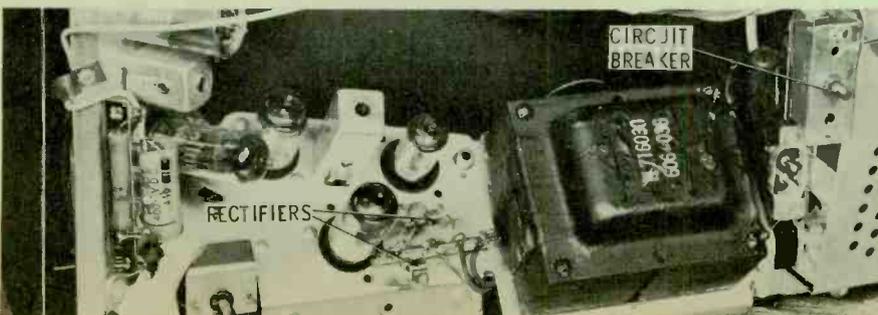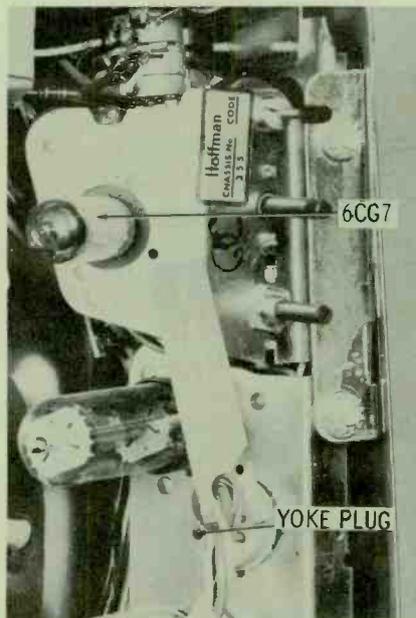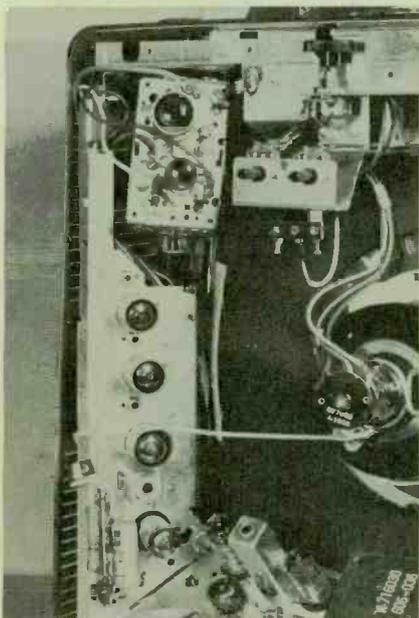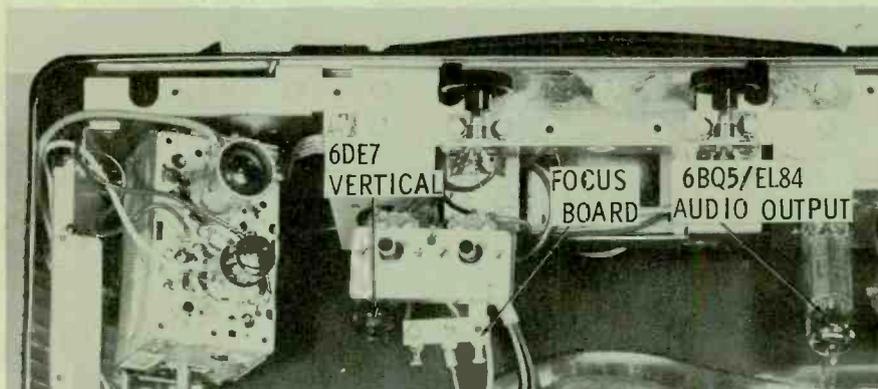On top of the base chassis, a pair of silicon rectifiers are connected in a full-wave, voltage-doubler configuration. There is a trend for manufacturers to employ this circuit in conjunction with a power transformer. However, it is unusual to find a transformer-powered chassis protected by a circuit breaker, as is the case in this Hoffman portable.



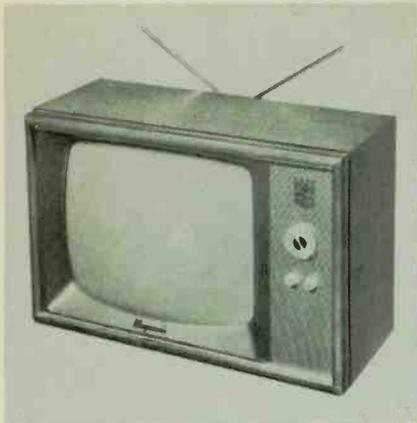

**Magnavox Model  
1MV139D  
Chassis V34-01-00**





This model from the 1961 Magnavox line sports a 19YP4, 110° picture tube. Other versions of this same chassis may use a 23MP4; neither tube type utilizes a bonded faceplate. A removable trim strip along the top of this model provides access to the face of the picture tube for cleaning. The only operational controls on the front are the push-pull off-on switch, volume, contrast, and tuning. (Some versions have remote control.)



Rear-mounted controls for horizontal hold, brightness, and vertical hold are equipped with thumb knobs which protrude through the rear cover. Setup controls are well labeled and easily accessible. The conventionally-wired, 18-tube, vertical chassis follows the same general layout used in previous years.

All of the signal-handling circuits are located along the upper half of the chassis. The 5U4GB B+ rectifier, in a rather unusual recessed mounting, is completely removed from the remainder of the power supply, so that the effects of its heat on other circuits is minimized. In the photo, the top cap has been removed from the video IF output transformer to show the soldered-in 1N64 video detector. The quadrature-coil adjustment is located on top of the "canned" coil in the locked-oscillator audio detector circuit, which uses a conventional 6DT6. Just to the right of the control panel, you'll find either a 6DG6 or 6W6 serving as the audio output. The tubes are used interchangeably and can be replaced with either type.

The remainder of the power supply and the vertical deflection circuits occupy the lower right part of the chassis. Magnavox has again reverted to the use of a 6BF6 as the first section of the vertical multivibrator circuit; the combined output and multivibrator stage incorporates a 6EM5. The transformer-powered chassis uses a 1½" length of #24 wire (located beneath the chassis) as a filament-protection device.

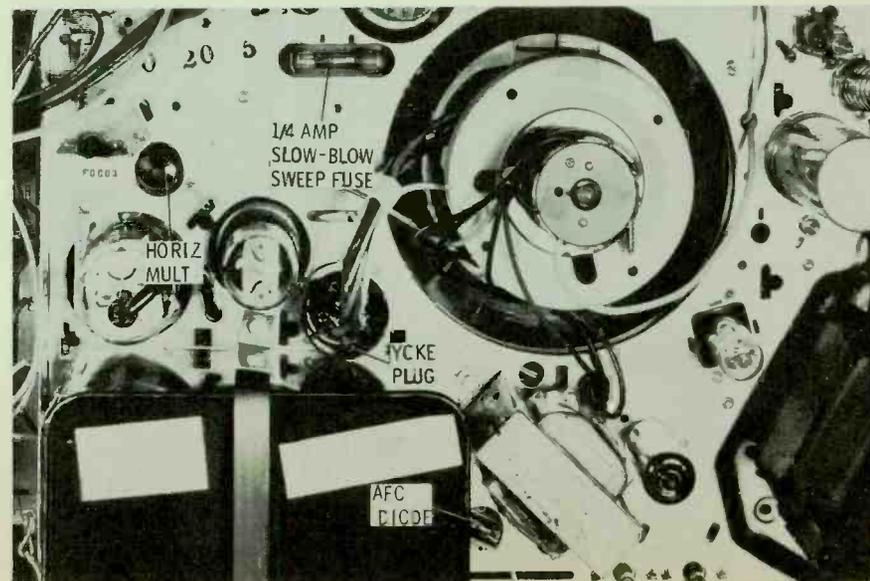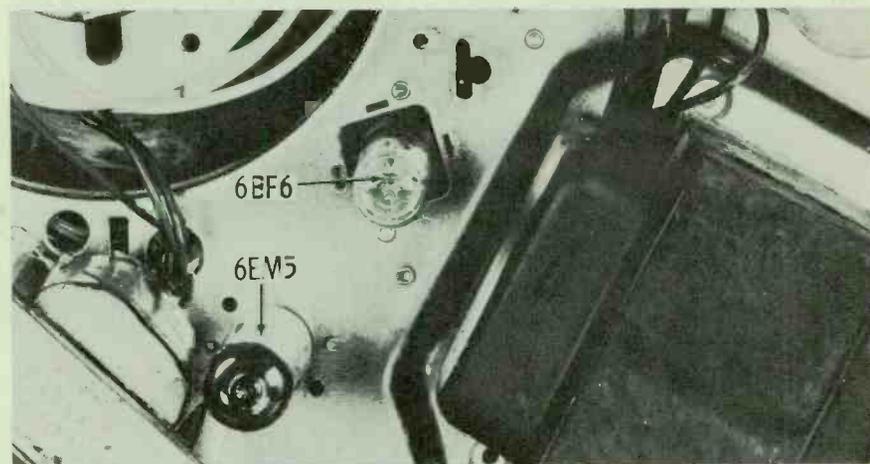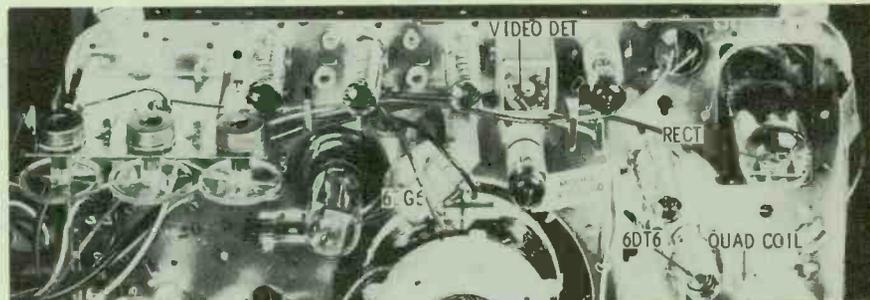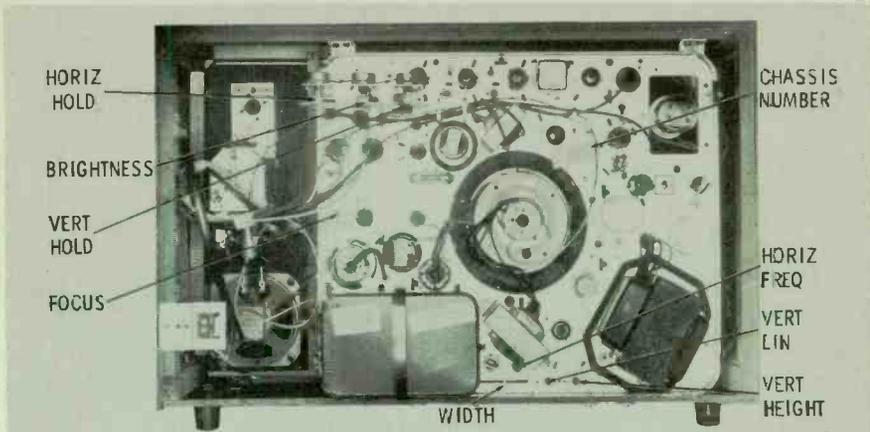A ¼-amp, slow-blow fuse provides sweep-circuit protection. As in previous years, the horizontal sweep circuits occupy the entire lower left-hand corner of the chassis. Also, the same circuit layout is employed, with the plug-in, dual-selenium horizontal AFC diode positioned along the right side of the high-voltage cage.



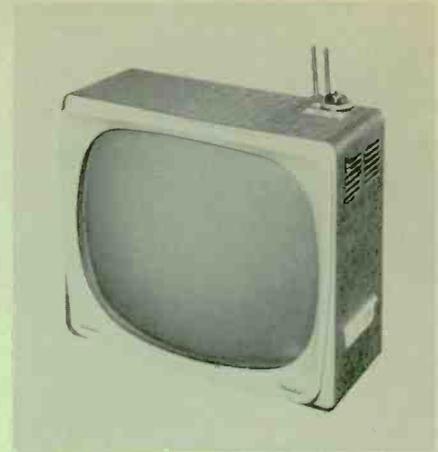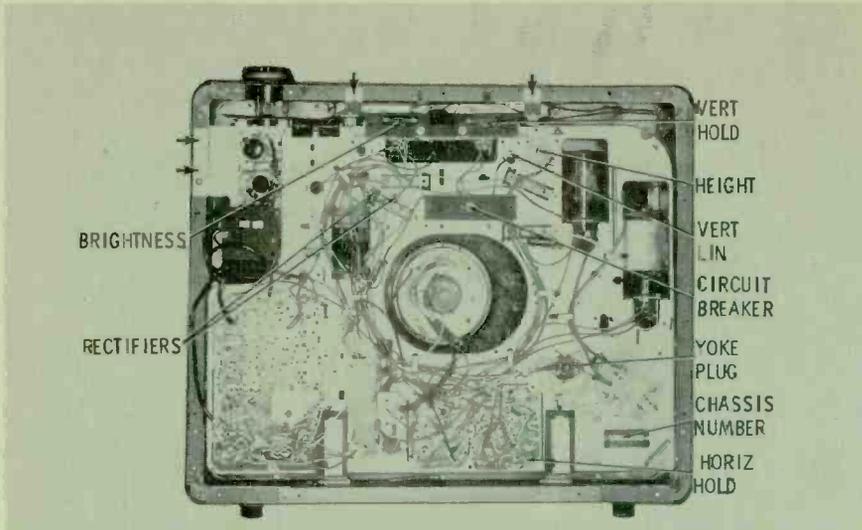

### Silvertone Model 1118CH Chassis 528.51680




Representing the *Medalist* series of 1961 Silvertones, this 21" portable has a west-coast twin with a PC prefix to the model number and a 456.51680 chassis. The series includes 12 basic models and 3 basic chassis (-680, -740, -760) used in 17", 21", and 23" versions. The 23" models have a bonded safety shield. In this model the mask is held in place with two screws in the cabinet bottom which, when removed, permit access to two springs holding the safety glass in place.


With the back removed, it's readily apparent how such a thin cabinet design is possible; the vertically-mounted chassis is turned around so the tube side faces forward. This feature is quite similar to some CBS chassis of days gone by. In order to gain access to the tubes, remove the knobs from the top-mounted controls and the four metal screws indicated by the heavy arrows. The top of the chassis will then tilt back. As you can see, most of the wiring is contained on two printed boards. The 15-tube chassis has a 450-ma series-filament circuit, and a pair of silicon diodes connected in a conventional half-wave doubler circuit. A circuit breaker provides protection for the B+ supply.

With the chassis tilted out at about a 45° angle, it's held in place by a beaded chain. All signal circuits are contained on the printed board on the right side. When compared to the '60 *Medalist* series, this board contains two major circuit changes. The third video IF and detector circuit uses a 3CB6 and crystal diode as opposed to last year's 6AM8 circuit, and a 4BU8 serves the keyed AGC and sync separator stages.

At the top of the chassis, the beaded chain is looped around and under a formed metal support so it can be released to lower the chassis to a horizontal position. The high-temperature horizontal output and damper stages are placed as far away from the remaining circuitry as possible, and are partially surrounded with heat sinks and radiation shields.

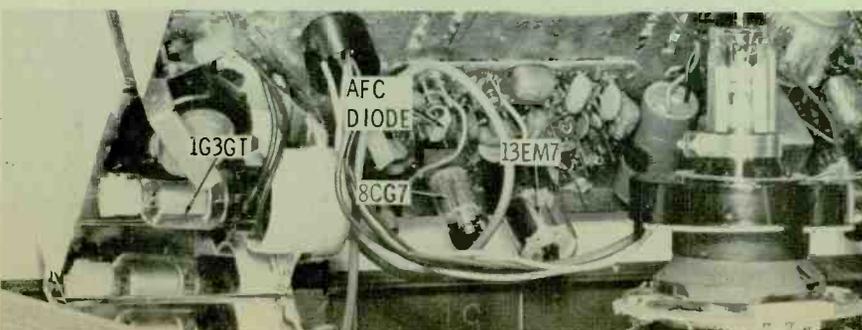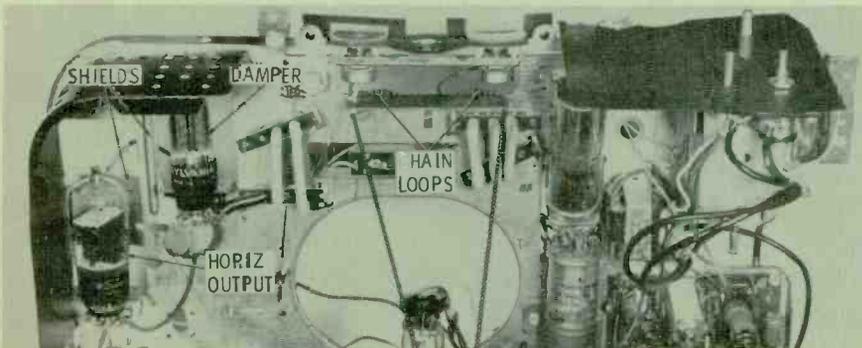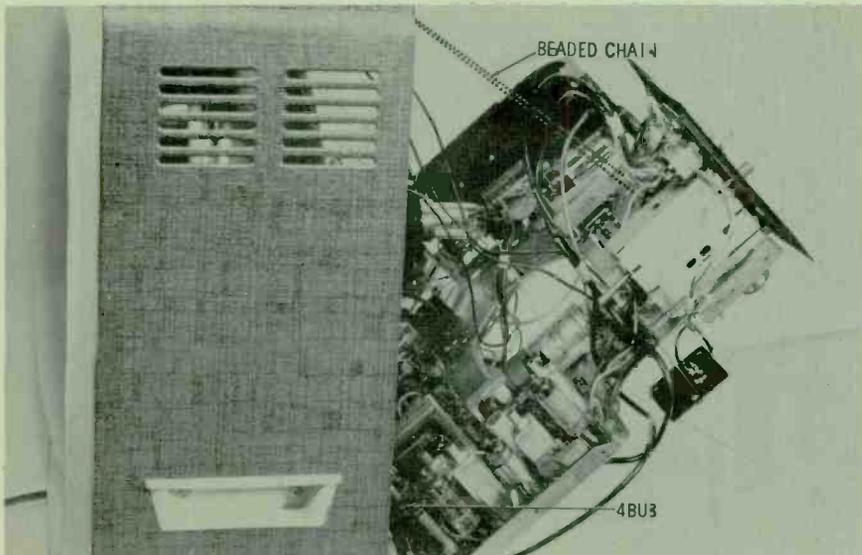As the chassis tilts out, it automatically exposes the flyback and 1G3GT. The printed board along the bottom edge contains the dual-triode 13EM7 used in combined vertical multivibrator and output stages, in addition to the horizontal AFC diode unit and 8CG7 horizontal multivibrator.



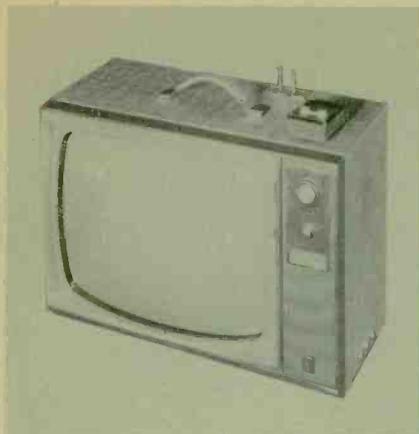

**Zenith Model F2215L  
Chassis 16F25Q**




Power and remote tuning are two specific features of this 19" portable. Other models using the same basic chassis employ conventional tuning, and some are equipped with a timer switch which functions much like the sleep switch of a clock-radio. Of the 38 models using 8 variations of this chassis, 13 use a 17DQP4 picture tube, while the other 25 use the 19ASP4 incorporated in this model. This 19" tube doesn't utilize a bonded faceplate; however, the mask easily pries out to provide access to the safety-glass retaining screws.

All service adjustments for the 16-tube, conventionally-wired chassis are labeled on the rear apron; the operational controls (other than off-on-volume and tuning) are mounted along the side. Either a 6EB8 or 6GN8 may be used in the video amplifier-sound IF application, and a 6EM7 or 6EA7 in the vertical deflection circuit. The manufacturer suggests using the original type when replacement is necessary. One of the major servicing features of these models is a removable plate held in place on the bottom of the cabinet by four metal screws. Removal of the plate provides access to all below-chassis wiring.

Mounted at the top of the cabinet, the *Space Command 300* remote-control chassis is a carryover from the 1960 line. It uses 6 tubes to provide unidirectional channel selection, power on-off, and volume control; a 3/4-amp, slow-blow fuse is connected in series with the AC line for protection. Programming adjustments are accessible without removing the back. Positioning the cams so they point toward the shaft causes the channel to be skipped, while a 90° turn in either direction causes the tuner to stop on the associated channel.


Resembling a piece of copper screen wire encased in plastic, the width sleeve used with this chassis looks a little unusual. A piece of tape firmly holds the sleeve in position. If the sleeve is adjusted or removed, the manufacturer specifies that its gap be positioned facing the high-voltage connector.

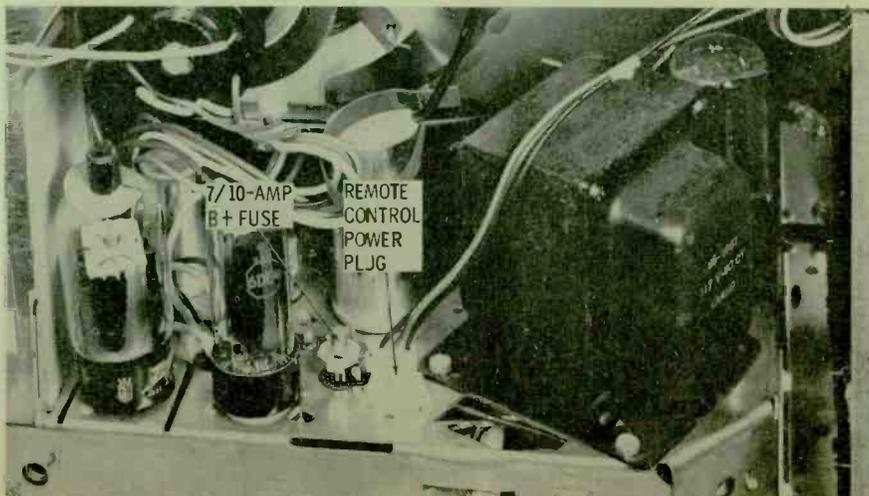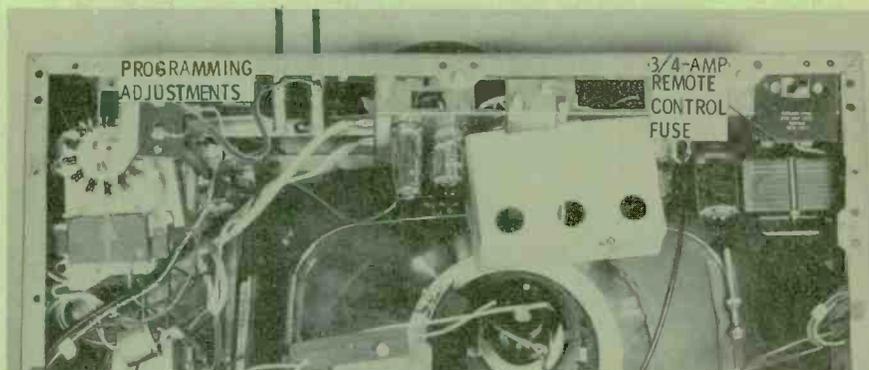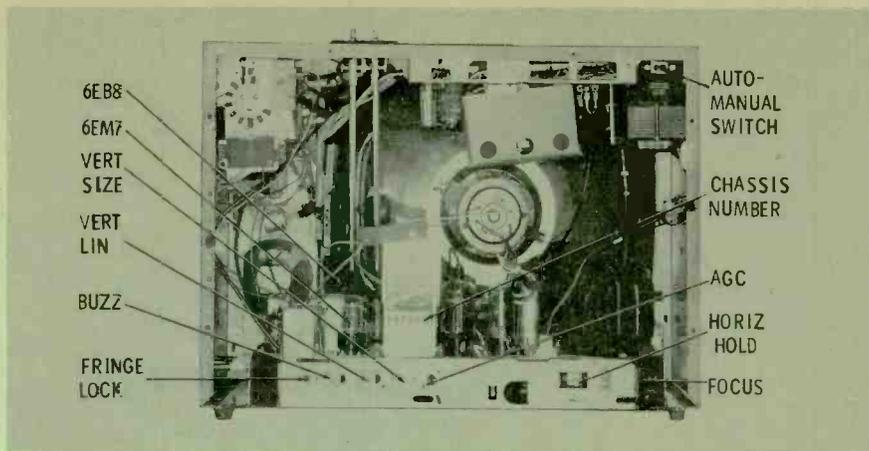The entire right side of the TV chassis is devoted to the power supply and horizontal deflection circuits. A 7/10-amp, type-N fuse is connected in the B-minus lead of the transformer to provide B+ protection, and a 1 1/2" length of #24 copper wire is used to protect tube filaments.




See PHOTOFAC Set 485, Folder 1

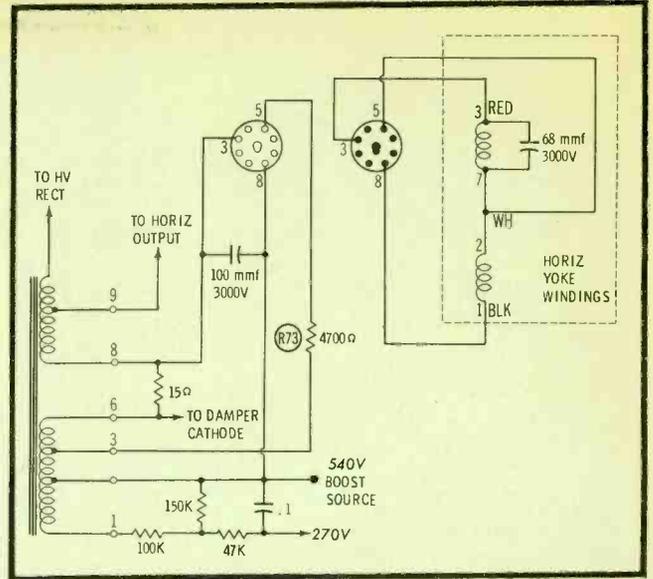
**Mfr:** Olympic **Chassis No. JA**  
**Card No:** OL JA-1  
**Section Affected:** Raster.  
**Symptoms:** Insufficient width; streaks in picture.  
**Cause:** Resistor in horizontal yoke circuit burned and reduced in value.  
**What To Do:** Replace R73 (4700 ohms).



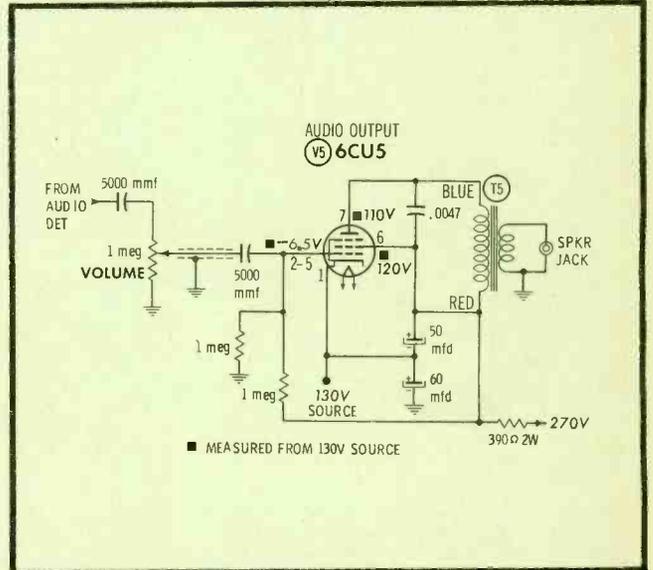**Mfr:** Olympic **Chassis No. JA**  
**Card No:** OL JA-2  
**Section Affected:** Sound and pix.  
**Symptoms:** No sound; no picture.  
**Cause:** Open audio output transformer.  
**What To Do:** Replace T5.



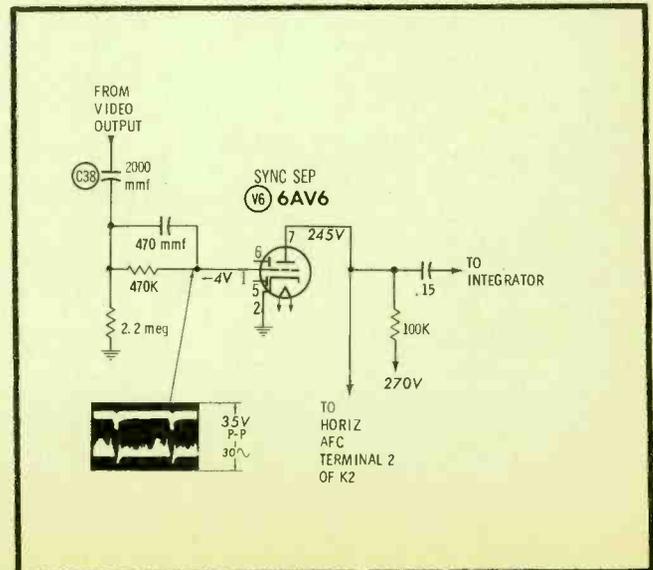**Mfr:** Olympic **Chassis No. JA**  
**Card No:** OL JA-3  
**Section Affected:** Sync.  
**Symptoms:** Vertical rolling; horizontal tearing.  
**Cause:** Leaky video-to-sync coupling capacitor.  
**What To Do:** Replace C38 (2000 mmf).



See PHOTOFAC Set 485, Folder 1



See PHOTOFACT Set 485, Folder 2

Mfr: Westinghouse Chassis No. V-2384-1


Card No: WE 2384-1-1

Section Affected: Raster.

Symptoms: Insufficient width.

Cause: Resistor in series with yoke center tap burned and decreased in value.

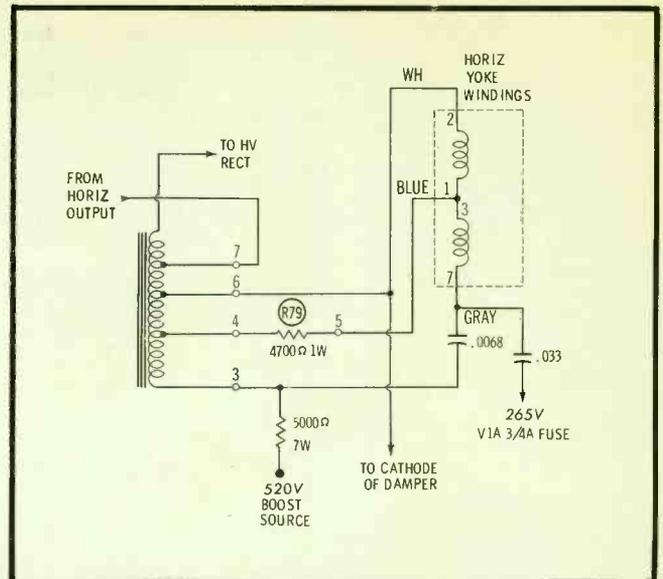What To Do: Replace R79 (4700 ohms — 1W).



Mfr: Westinghouse Chassis No. V-2384-1


Card No: WE 2384-1-2

Section Affected: Pix and sound.

Symptoms: Picture flashes on and off; sound disappears along with picture.

Cause: Intermittently open coupling capacitor between video detector and video output.

What To Do: Replace C29 (.033 mfd).

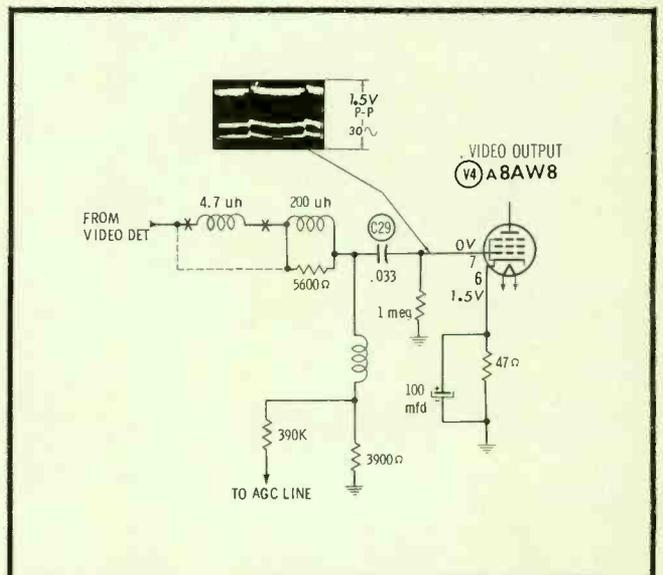

Mfr: Westinghouse Chassis No. V-2384-1


Card No: WE 2384-1-3

Section Affected: Raster.

Symptoms: As height control is adjusted, flashes and streaks appear in raster.

Cause: Open ground connection on height control.

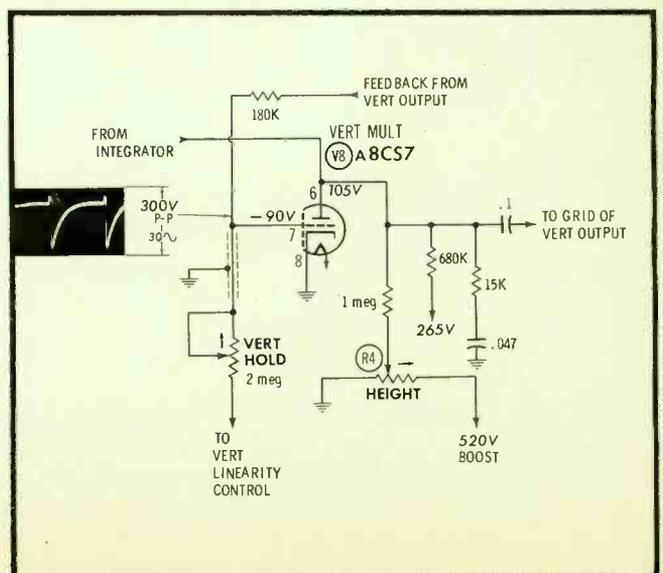
What To Do: Resolder ground connection on R4, and recheck action of control.



See PHOTOFACT Set 485, Folder 2

See PHOTOFACT Set 485, Folder 2

See PHOTOFACT Set 485, Folder 2

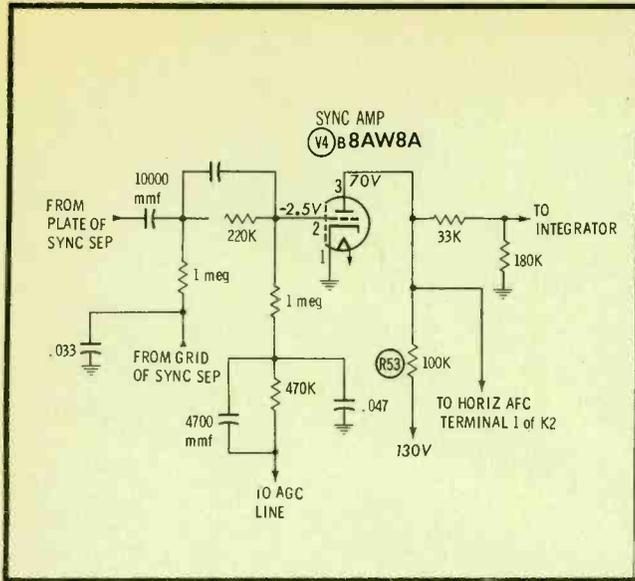

Mfr: Westinghouse Chassis No. V-2384-1


Card No: WE 2384-1-4

Section Affected: Sync.

Symptoms: Loss of vertical and horizontal hold, gradually developing as set plays.

Cause: Sync-amplifier plate-load resistor increases in value.

What To Do: Replace R53 (100K).

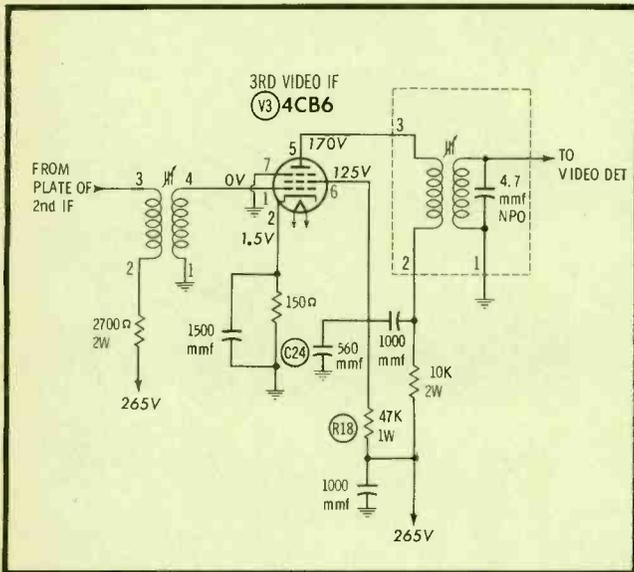

Mfr: Westinghouse Chassis No. V-2384-1


Card No: WE 2384-1-5

Section Affected: Pix and sound.

Symptoms: No picture or sound.

Cause: Shorted screen-bypass capacitor and open screen resistor in third IF stage.

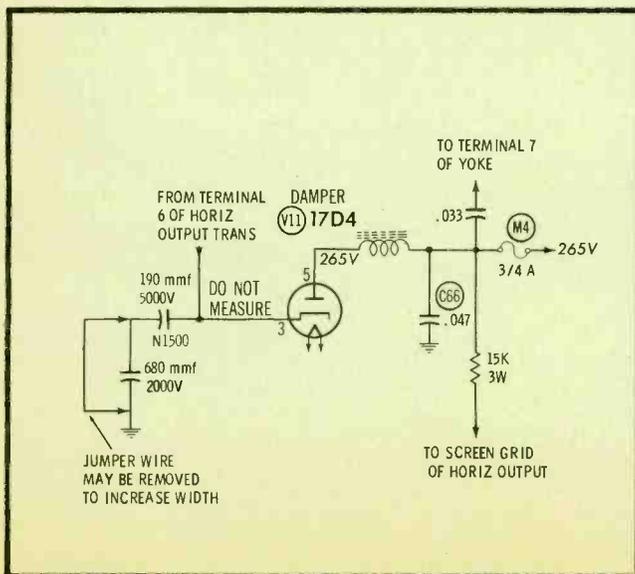What To Do: Replace R18 (47K—1W) and C24 (560 mmf).



Mfr: Westinghouse Chassis No. V-2384-1

Card No: WE 2384-1-6

Section Affected: Raster.

Symptoms: Sweep-circuit fuse blows frequently.

Cause: Leaky filter capacitor in plate circuit of damper.

What To Do: Replace C66 (.047 mfd) and M4 (3/4 amp—250V, slow-blow).



*universal  
acceptance!*

miniaturized  
**ELMENCO**

The exclusive Elmenco dip-coated Mylar-Paper capacitors (Arco type dp) represent a double breakthrough in capacitor design. They combine missile and computer quality and compare favorably in price with commercial general purpose units. The "dp" series is designed for universal use, from TV by-pass to critical industrial applications requiring stringent electrical and environmental characteristics. New high levels of ruggedness, stability and reliability have been achieved in a miniaturized body.

**54,745,000 SOLD  
IN LESS THAN 2 YEARS**

\* DuPont Reg. Trademark  
Write for catalog dp 110.



**ARCO** *electronics inc.*

64 White Street, New York 13, N. Y. • Branches: Dallas 19, Los Angeles 35



*Dipped  
Mylar\* - Paper  
Capacitors*

**NOW . . . OPERATING AT  
125° C WITHOUT DERATING**

**Reliability** Elmenco dp Mylar-Paper Capacitors have achieved a reliability that meet missile and computer requirements. They are thoroughly and continually tested during production to insure outstanding performance. For example a 0.1 mfd. dp capacitors operated at full rated voltage and at 105° C will have a life expectancy of more than 7,168,000 unit hours.

**Moisture-Proof** Elmenco dp Capacitors are specially processed and vacuum dipped to obtain solid impregnation and a rugged moisture-proof coat designed to withstand 4 times more humidity than the best molded capacitors used in the past.

**Miniaturized** These capacitors are up to 50% smaller than other types and can be used in printed circuit and transistor applications.

**±10% Standard Tolerance**

*the only one of its kind!*



NOW... THE *First* ANALYZER DESIGNED EXCLUSIVELY FOR TESTING TRANSISTOR CIRCUIT CAPACITORS!

## SPRAGUE MODEL TCA-1 TRANSFARAD\*

**THERE'S NOTHING LIKE IT ON THE MARKET ANYWHERE... AT ANY PRICE!**

Here, for the first time, is a precision-made instrument which is specifically designed to *safely* test low-voltage aluminum and tantalum electrolytic capacitors, film and paper capacitors, and ceramic capacitors. *No laboratory or shop working with transistor circuit capacitors can afford to be without one!*

**CAPACITANCE BRIDGE:** 1  $\mu\text{f}$  to 2,000  $\mu\text{f}$  in five overlapping ranges, with laboratory accuracy.

**INSULATION RESISTANCE:** 50 megohms to 20,000 megohms. Only 25v d-c is applied, permitting measurements on low-voltage ceramic, paper, mica, and film capacitors. For ceramics rated below 25 volts, IR may be calculated from leakage current measurements at exact rated voltage.

**POWER FACTOR:** Measured by Wien Bridge from 0 to 50%.

**LEAKAGE CURRENT:** 0.6  $\mu\text{a}$  to 600  $\mu\text{a}$  in 7 ranges. Measured directly on meter at exact rated d-c voltage of capacitor. No guessing on eye-width or counting lamp blinks!

**A-C BRIDGE VOLTAGE:** Only 0.5v is applied to the bridge. The voltage across the capacitor is less than this applied voltage, the amplitude depending upon capacitance being measured. No danger of overheating and ruining even a 1-volt electrolytic or a 3-volt ceramic.

**POLARIZING VOLTAGE:** Continuously adjustable, 0 to 150v.

**STABILITY:** Dual regulation of the power supply assures short-time reliability, while specially processed etched circuits and complete encapsulation of the critical meter amplifier insure long-time stability.

**MAGIC-EYE TUBE:** Simplifies bridge balancing for capacitance and power factor measurements.

**HIGH GAIN AMPLIFIER:** Sensitivity control for magic-eye null detector permits accurate measurements of small capacitances.

**CAPACITANCE DIAL:** Latest design jet black dial with brilliant white calibrations for quick, accurate readings from any position.

**BINDING POSTS:** Shielded for protection against pick-up of strays, assuring greater accuracy during low-capacitance measurements. 5-way connection feature for use with all types of test leads.

**SAFETY DEVICES:** Automatic discharge of capacitor after testing. Three-wire line cord grounds instrument case.

**OPERATING PROCEDURES:** Easy-to-follow operating procedures clearly shown on pull-out slide at base of instrument. Always handy for ready reference.

**MODERN CASE:** Handsome grey Hammerloid finish on heavy-gage steel. Measures 8 $\frac{1}{2}$ " high, 14 $\frac{1}{2}$ " wide, 9 $\frac{1}{2}$ " deep. Weighs only 21 pounds.

See the remarkable new TCA-1 TRANSFARAD at your Sprague distributor or write for descriptive folder M-792a to Sprague Products Company, 105 Marshall St., North Adams, Massachusetts.

ONLY  
**\$197 50**  
NET

\*Trademark

# SPRAGUE

world's largest capacitor manufacturer

**publisher**  
Howard W. Sams

**general manager**  
Mak Parks, Jr.

**editor**  
Verne M. Gray

**associate editors**  
Leslie D. Deane  
Thomas A. Lesh  
Joe A. Groves

**consulting editors**  
William E. Burke  
Robert B. Dunham  
George B. Mann  
C. P. Oliphant  
Paul C. Smith

**art director**  
Don W. Bradley

**advertising & editorial assistants**  
Georganna Caldwell  
Paula Hoffner  
Jean Sekulski

**production manager**  
Robert N. Rippey

**circulation fulfillment**  
Pat Todd, Mgr.  
Constance McCawley, Ass't.  
Katherine Smith, Ass't.

**photography**  
Robert W. Reed

**advertising sales offices**  
midwestern

John Groce, PF REPORTER  
2201 East 46th Street, Indianapolis 6, Ind.  
Clifford 3-6441

**eastern**

Howard W. Sams & Co., Inc.  
Corning Glass Building  
777 Fifth Ave., New York 22, N. Y.  
MUrray Hill 8-6350

**western**

The Maurice A. Kimball Co., Inc.  
2550 Beverly Blvd., Los Angeles 57, Calif.  
Dunkirk 8-6178; and 681 Market Street,  
San Francisco 5, Calif. Embarcadero 2-3365

Address all correspondence to  
PF REPORTER, 2201 East 46th Street,  
Indianapolis 6, Indiana



Copyright © 1960 by Howard W. Sams & Co., Inc. PF REPORTER is a trademark of Howard W. Sams & Co., Inc. No part of PF REPORTER may be reproduced without written permission. No patent liability is assumed with respect to use of information herein. Acceptance of advertising does not in any manner signify the products, policies and services so advertised have been approved, endorsed or recommended by this magazine.

Indexed in Electronic Guide and Literature.  
Printed by the Walden Press Div.  
of Howard W. Sams & Co., Inc.



# PF REPORTER

including **Electronic Servicing**

VOLUME 10, No. 11

NOVEMBER, 1960

## CONTENTS

<b>Previews of New Sets</b>	1
Hoffman Model K1919 (Chassis 355), Magnavox Model 1M139D (Chassis V34-01-00), Silvertone Model 1118CH (Chassis 528.51680), Zenith Model F2215L (Chassis 16F25Q).	
<b>Video Speed Servicing</b>	5
Service hints on the Olympic Chassis JA and Westinghouse Chassis V-2384-1.	
<b>Letters to the Editor</b>	12
<b>The Electronic Scanner</b>	20
<b>Understanding Transistor Testers—</b>	24
<b>Part 1</b>	
Shop Talk—An explanation of circuits used to check various transistor characteristics.	
<b>Applications of Magnetic Amplifiers</b>	26
Servicing Industrial Electronics—Details of motor-control and temperature-regulating circuits, including operating theory and servicing pointers.	
<b>The Expanding FM Radio Field</b>	28
Servicing New Designs—Zooming sales of inexpensive table model and FM auto radio receivers calls for this examination of their circuits.	
<b>Secondary TV Waveform Checks</b>	30
Your scope's usefulness doesn't end with viewing the waveforms given on service schematics . . . if you know how to interpret the patterns observed at other points.	
<b>Spotlighting the 1961 TV Lines</b>	32
An analysis of the newest receivers of 16 different manufacturers, pointing out their most pertinent features.	
<b>Dollar &amp; Sense Servicing</b>	46
<b>Fundamental Transistor Theory</b>	48
No "holes" in this story—just the plain facts about how a transistor works.	
<b>Direct-Drive Sweep Troubles</b>	56
Quicker Servicing—How to cope with an old-time horizontal deflection circuit that still haunts TV servicemen.	
<b>Notes on Test Equipment</b>	60
Lab reports on Motorola's new transistor tester, the PACO Model C-25 in-circuit capacitor tester, and the SENCORE "Mighty Mite" tube tester.	
<b>The Troubleshooter</b>	76
<b>Product Report</b>	85
<b>Free Catalog &amp; Literature Service</b>	88
<b>Monthly Index on free literature card</b>	

### ABOUT THE COVER

Along about this time every year, dealers and servicemen face a whole new crop of TV receivers. To serve the best interests of their customers (and their own, too, of course), they need to learn a little bit about a lot of sets—and fast!

A digest of all the pertinent facts you need to know about 16 major TV lines for 1961—utilizing all the space we could muster on 13 consecutive pages—begins on page 32 of this issue.



**ATR****PRODUCTS FOR MODERN LIVING****ATR UNIVERSAL INVERTERS**


A. C. Household Electricity Anywhere . . . in your own car!

- Tape Recorders • TV Sets
- Dictating Machines • Radios
- Public Address Systems

- Electric Shavers • Record Players • Food Mixers • and Emergency Lighting. . . . . NET

- 6U-RHG (6 V.) 125 to 150 W. Shp. Wt. 27 lbs. \$66.34
- 12U-RHG (12 V.) 150 to 175 W. Shp. Wt. 27 lbs. \$66.34

Auto Plug-in Home-type Portable

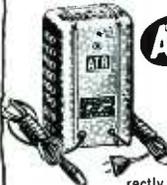**ATR BATTERY CHARGERS**

NO INSTALLATION . . . PLUG INTO CIGARETTE LIGHTER RECEPTACLE!

Keeps car battery fully charged in your own garage! Needed more now than ever before—makes motor starting easy! Operates directly from standard 110 volts A.C. current.

- 612CA4 (4 amp.) 6/12 V. Shp. Wt. 6 lbs. NET \$19.46
- 612CA6 (6 amp.) 6/12 V. Shp. Wt. 8 lbs. NET \$22.46
- 612CA10 (10 amp.) 6/12 V. Shp. Wt. 10 lbs. NET \$27.71

**ATR SHAV-PAKS**

Keep Clean-Shaved! Plugs into Cigarette Lighter Receptacle. Keep in Glove Compartment. Operates Standard A.C.

- ELECTRIC SHAVERS
- Small Timing Devices . . . . . In CARS, Buses, Trucks, Boats, or Planes.

- 6-SPB (6 V.) 15 W. Shp. Wt. 2½ lbs. NET \$7.97
- 12-SPB (12 V.) 15 W. Shp. Wt. 2½ lbs. NET \$7.97

**ATR****ELECTRONIC TUBE PROTECTORS**

Will Double or triple the life of all types of electronic tubes, including TV picture tube.

Automatic in operation, for use with any electronic equipment having input wattage of 100 to 300 watts. Fuse protected, enclosed in metal case for rugged construction and long life.



MODEL 250 (Wall Model) 115 V. A.C. Shp. Wt. 1 lb.

DEALER NET \$2.63

**ATR MODERN TABLE RADIOS**

Trim, modern clock radio in ebony or ivory plastic. Powerful 5 tubes including rectifier AM radio chassis with built-in "Magna-Plate" antenna. Full-toned 4" PM speaker. Popular features include: Musical Alarm—radio turns on automatically at any pre-set time; Sleep Selector—lulls user to sleep; Automatic Appliance Timer—outlet on back of radio times any electric appliance automatically (up to 1100 watts). Cabinet 10½ in. wide, 5 in. high, 5½ in. deep. Wt. approx. 8 lbs.

- Model T-91
- Clock Specifications:
- Genuine Telechron Movement.
  - Self-Starting . . . Never Needs Winding, Oiling, or Regulating.
  - Simplified Clock Controls for Radio and Sleep Switch.
  - 1100 Watt Controlled Outlet.
  - Automatic Buzzer Alarm.
  - Gold-Plated Bezel and Numerals on Large Bone-White Dial. UL Approved.

**ATR HAND WIRED—NO PRINTED CIRCUITRY "TILT-A-STAND" RADIO**

MOUNT ON THE WALL—UNDER A SHELF—OR SET ON A TABLE. PERFECT for every room in YOUR home.

Power-packed 5 tubes including rectifier chassis. Built-in loop antenna. Automatic volume control. Full 4" Alnico 5 speaker. Distinctive Roman numerals on dial. Size: 9½" W x 4" D x 5½" H. AC/DC. U.L. approved. Beautiful bakelite cabinet—Resists heat. Shipping Weight 5½ lbs.

- Model T-91 Clock Radio, Black . . . . . NET \$22.45
- Model T-91 Clock Radio, Ivory . . . . . NET 23.15
- Model T-87 (Tilt-A-Stand), Black . . . . . NET 17.47
- Model T-87 (Tilt-A-Stand), Red . . . . . NET 18.10

SEE YOUR ELECTRONIC PARTS DISTRIBUTOR WRITE FACTORY FOR FREE LITERATURE . . .

**ATR****AMERICAN TELEVISION & RADIO CO.**  
Quality Products Since 1931  
SAINT PAUL 1, MINNESOTA—U. S. A.*Letters to the***EDITOR**

Dear Editor:

We were somewhat surprised to note several errors in the text devoted to the Hoffman Model 3703 in the August *Previews of New Sets*. In the first paragraph, reference was made to the fact that this model contains a stereo amplifier, but no phono. Actually, this particular model is merchandised with an external matching stereo record changer. Since this fact is not contained in the information in our service notes, it's understandable that you missed it.

In the second paragraph, your copy states that only the right-channel amplifier is used for TV sound. On the first page of our Service Bulletin No. 1101, under the heading "Mark 5 Entertainment Selector," Item 1 says, "The sound from the TV receiver will play through both amplifiers and both speaker enclosures, thus producing the program through a total of six (6) loudspeakers and the dual channel stereo amplifier in your Mark 5 receiver." However, the third paragraph in your write-up ends with, "Another point you will want to keep in mind is that the right-channel speakers are the only ones used for TV."

There is also a statement in the third paragraph saying that "the usual tube placement chart is conspicuous by its absence." This really hurts, because we pay a premium to silk-screen the tube-location chart on our backboard—not only showing the tube types and locations, but also keying the tube pins.

E. J. GREANEY

National Service Manager  
Hoffman Electronics Corp.  
Los Angeles, Calif.

*Mr. Greaney wrote us just shortly before his untimely passing in September—news we received with deep regret.*

*We stand corrected on the use of both amplifiers for TV sound; however, the tube placement chart was not in evidence on the rear cover of the model we analyzed.—Ed.*

Dear Editor:

Your articles by Mr. Milton Kiver are so elucidating and to the point that I want to comment to the "editorial letter box" about same. They alone are worth the annual subscription fee, and are unequalled in any other electronic service magazine.

J. M. SCHILDZ

Lindenwood Radio & TV  
St. Louis, Mo.

Dear Editor:

I have just finished reading the last of the series of seven articles by Milton S. Kiver on servicing the basic circuits of a TV receiver. These were very good, and a round of applause is due him.

FRED DASI

(address not given)

*We heartily agree that Mr. Kiver is "the most." The first of his new series (2 parts), describing methods for testing transistors, begins on page 24 of this issue. His newest Howard W. Sams book, "Servicing Transistor TV Receivers," is now available from your local distributor.—Ed.*

Dear Editor:

The enclosed piece is being circulated by Airview Electronics of New York City. I'm passing it along with the idea that you might want to give your readers a chance to keep up with New York thinking on a most vexing problem.

Of course, this proposed calendar change is not something that will be accomplished overnight, or even in a fortnight of Sundays—but a beginning has to be made somewhere!

HARRY M. LAYDEN

Bronx, N. Y.

**ULCER-FREE CALENDAR**

Gen.	Fri.	Fri.	Thur.	Wed.	Tues.	Mon.
8	7	6	5	4	3	2
16	15	14	13	12	11	9
23	22	21	20	19	18	17
31	30	29	28	27	26	24
38	37	36	35	34	33	32

**ADVANTAGES**

1. Every job is a rush. Everyone wants his order delivered yesterday. With this calendar customers can order on the 7th and have delivery on the 3rd.
2. All customers want their deliveries on Friday, so there are two Fridays in each week.
3. There are seven extra days at the end of each month for those end of the month rushes.
4. There is no 1st, 10th, or 25th of the month; therefore, bills will not have to be paid.
5. There are no bothersome nonproductive Saturdays and Sundays.
6. A new "General Day" each week permits orders to be cancelled, style changes made, and other matters re-opened; for instance, a style change made on the 8th may reach you on the 5th, but you may make the change even though the goods were shipped on the 6th. Everybody will be happy, and we will soon have an ulcer-free industry.

*Thanks, Harry. It's just what we needed to get this issue published on time!—Ed.*


Dear Editor:

Looking back through your 1958 *Test Equipment Annual*, we noticed the following statement on page 47: "Marker injectors which maintain the size of a marker constant at any point on a response curve, out on the base line or in the bottom of traps, have been available for several years."

Our present alignment generator has an internal marker oscillator built into it, with the output mixed with that of the sweep signal. Would it be possible to modify or add to this unit so that it will perform as stated above? There are times when it is almost impossible to see the marker at all, no matter how the controls are manipulated and/or the generator output is coupled into the TV set.

• Please turn to page 16

# BREAKTHROUGH! BREAKTHROUGH!

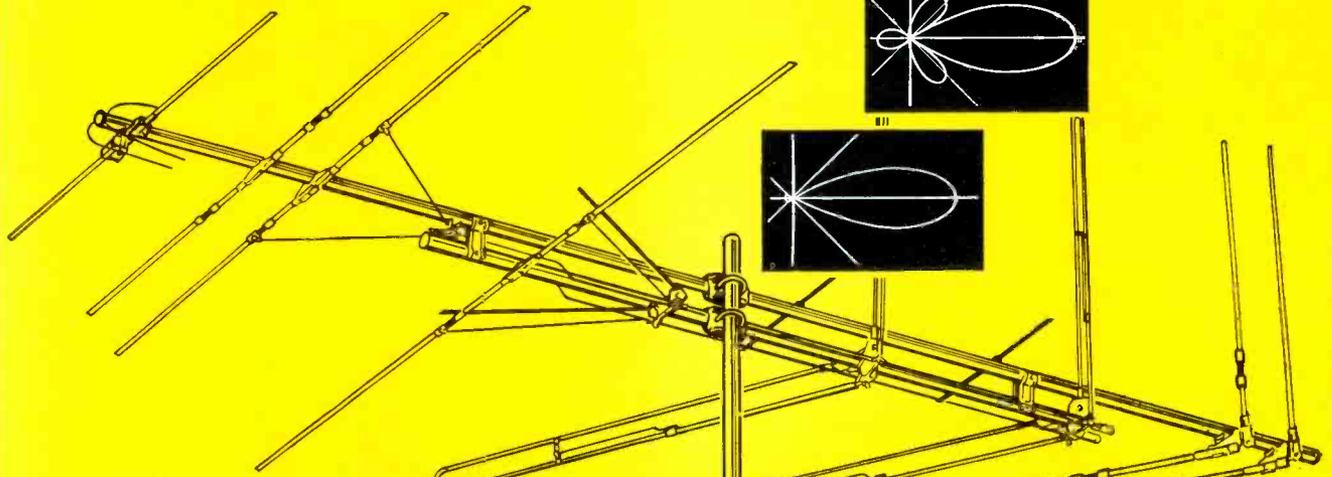


*Amazing antenna  
developments  
now make possible...*

**PEAK POWER** ON EVERY CHANNEL

*with the* **T-A-C-C-O**



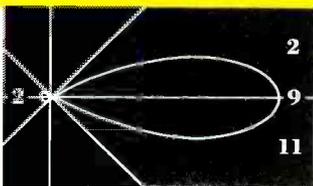Now—for the first time—Peakpower on every channel plus a directivity pattern clean as a whistle! Advanced antenna engineering on a specially-built test range by the most competent group of antenna engineers in the country now brings you the first high-gain, broad-band antenna with a single lobe—no side lobes—producing the sharpest pictures possible on any TV receiver . . .



A difference you can see on every TV screen! Elimination of side lobes ends displaced image (ghosts) to sharpen every channel. For the crispest, brightest pictures you ever sold—go T-Bird!

*Ask your distributor  
or write for complete details . . .*

**TECHNICAL APPLIANCE CORPORATION, SHERBURNE, NEW YORK.**


## PACKED WITH PROMOTION



The T-Bird is pre-sold by the most powerful promotion ever, spearheaded by Allie Scollon and her Injun Puppets on TV and radio. Point-of-sale, direct-mail, magazine and newspaper ads, giveaways, bus cards, and everything else to make everyone ask for a T-Bird . . .
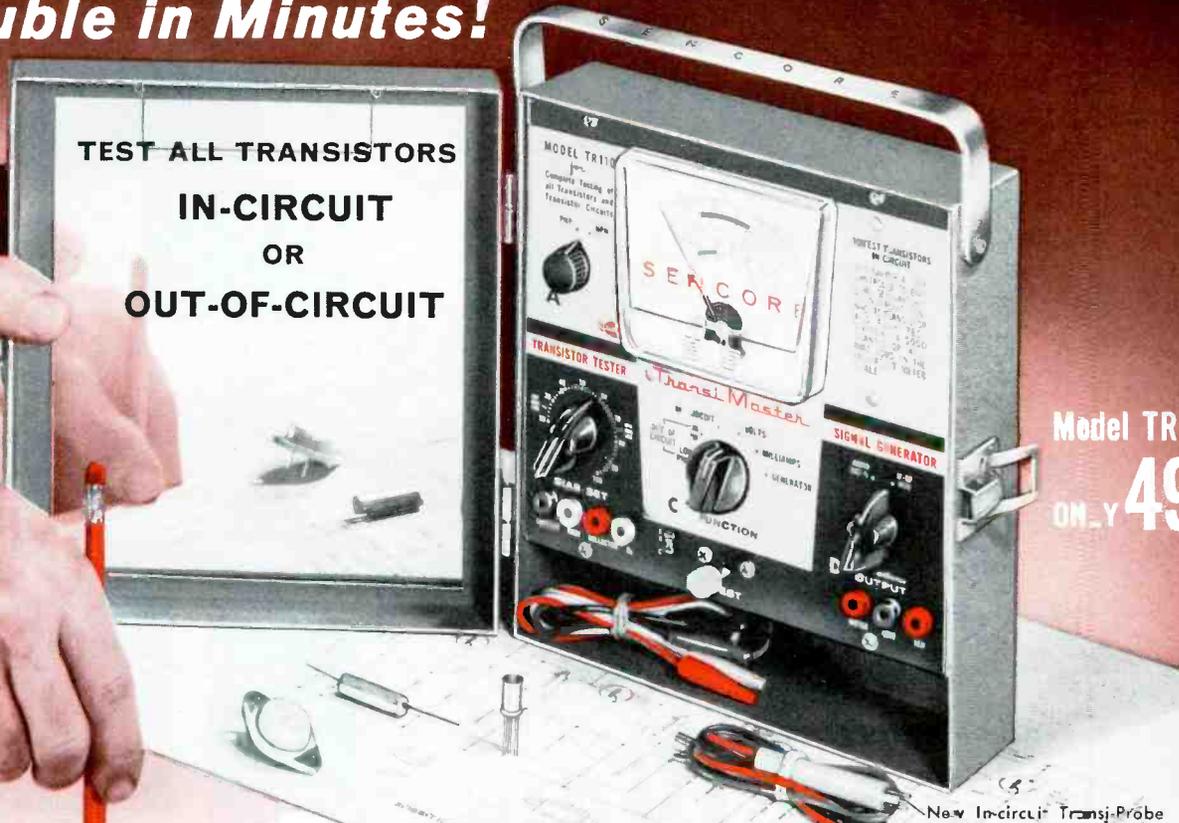
# NEW SENCORE Transi Master

**Analyze Every Transistor Circuit  
Trouble in Minutes!**



Model TR-110  
ONLY **49<sup>50</sup>**

**Now you can . . .**

**It's a . . . COMPLETE TRANSISTOR TESTER • SIGNAL TRACER  
VOLTMETER • BATTERY TESTER • MILLIAMETER**

Transistors are tested in-circuit with a new unique AC GAIN check and out of circuit with an accurate DC GAIN and LEAKAGE check. Set-up chart included for reference only.

- Test all transistors in-circuit with a new unique AC GAIN check. It works every time and without the use of the set-up booklet.
- Test all transistors out of circuit with the AC GAIN check or with a more accurate DC current gain and leakage check.
- Read current gain (beta) direct for experimental, engineering work or for matching transistors.
- Check diodes simply and accurately with a forward to backward ratio check.
- Signal trace from speaker to antenna with a special low impedance generator. No tuning, adjustments, or indicating device needed for transistor radio trouble shooting. Just touch output leads to transistor inputs and outputs until 2000 cycle note is no longer heard from speaker. (Generator output monitored by meter.) It's a harmonic generator for RF-IF trouble shooting and a sine wave generator for audio amplifier trouble shooting.
- Check batteries under operating conditions as well as the voltage dividers with a special 12 volt scale.
- Monitor current drawn by the entire transistor circuit or by individual stages with a 0 to 50 Ma current scale. A must for alignment and trouble shooting cracked boards.

## **Benefit from these Sencore extras**

- Lists Japanese equivalents.
- Automatically determines NPN or PNP.
- Mirror in detachable cover to reflect opposite side of printed board.
- Special clip to fit between batteries for current check.
- Transi-probe for making in-circuit transistor checks.

Color . . . . . modern two tone gray  
Size . . . . . 8" x 7<sup>5</sup>/<sub>8</sub>" x 3"  
Weight . . . . . only 5 lbs.  
Meter . . . . . 0 to 3 Ma, 3<sup>1</sup>/<sub>2</sub>", 5% tolerance,  
modern plastic  
Batteries . . . . . two size "C" cells

ALL PARTS ARE **SENCORE** MADE IN AMERICA

**SENCORE**  
ADDISON, ILLINOIS

Like to try it? Let Sencore Sam show you how and then see your Sencore Distributor. He has it in stock. . .



# SENCORE SAM

THE MINIT-MAN




**SHOWS YOU HOW TO USE THE SENCORE TRANSI-MASTER**

## A. TO TEST TRANSISTORS IN-CIRCUIT

**SAVE THE VALUABLE TIME YOU WASTE SOLDERING AND UNSOLDERING TRANSISTORS FOR SERVICE WORK ONLY!**

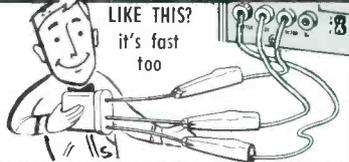1. Set to PNP or NPN
2. Set to Bias Line Transistor Radio
3. Set to in-circuit
4. Touch Special Probe to Transistor in-circuit
5. Push to Test
6. Read Meter

The in-circuit check can also be used for a quick check on transistors out of circuit



## B. TO TEST TRANSISTORS OUT OF CIRCUIT FOR GAIN, LEAKAGE, OPENS, SHORTS

**USE THIS DC CHECK FOR MOST ACCURATE TEST. USE SET-UP BOOKLET.**

1. Determine Transistor Type Set-up according to book
2. Connect to transistor. Use 4th leader for tetrode only.
3. Read Leakage and Compare to Chart
4. Push to test Gain
5. Normal Transistor will be in Green area of Gain Scale

Want to read Beta direct? Just set Bias Control to bias line and read meter. It's handy for engineers and when matching transistors.



For matching . . . pick the two transistors with closest Beta reading. The two transistors should also have approximately same leakage.

## C. TO SIGNAL TRACE TRANSISTOR CIRCUIT

**YOU CAN FIND THE DEFECT IN A JIFFY!**

1. Set Switch to Generator
2. Set according to stage
3. Meter will indicate when generator is putting out
4. Connect to common or ground
5. Touch to transistor inputs and outputs from speaker to antenna. 2000 cycle note from speaker will stop or decrease at trouble spot.

## D. TO CHECK CURRENT DRAIN BY COMPLETE SET OR INDIVIDUAL STAGE

**A REAL TIME SAVER FOR SPOTTING CRACKED BOARDS OR FOR ALIGNMENT. SEE SAM'S PF FOR AVERAGE CURRENT.**

1. Set to milliamp
2. Connect in circuit for reading current. Use special clip at end of battery.
3. Read current. Average Transistor Radio is 10 to 15 ma.


For alignment—just tune in any station and adjust slugs for maximum current.

## E. TO CHECK BATTERIES AND VOLTAGE DIVIDERS

**CHECK BATTERIES UNDER OPERATING CONDITIONS AND SEE THAT VOLTAGE IS DISTRIBUTED PROPERLY.**

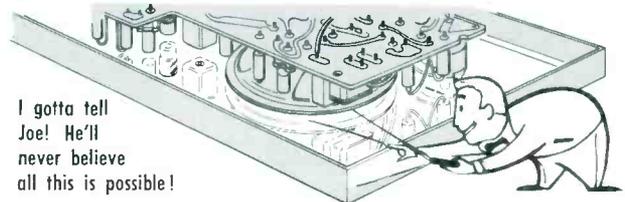1. Set to volts
2. Connect to batteries or across voltage dividers
3. Read voltage. Batteries should be within 10%

**AND LAST OF ALL . . .** the mirror in the detachable cover. Just place it under the printed board to see the other side as you work. Use pen light to see where you are.




ALSO FREE . . . Current transistor listings booklet, even has Japanese equivalents . . . just send in your warranty card and factory will keep you up to date!

Ask your distributor to show you the most useful equipment in servicing —



Transi Master  
by SENCORE  
ADDISON, ILLINOIS

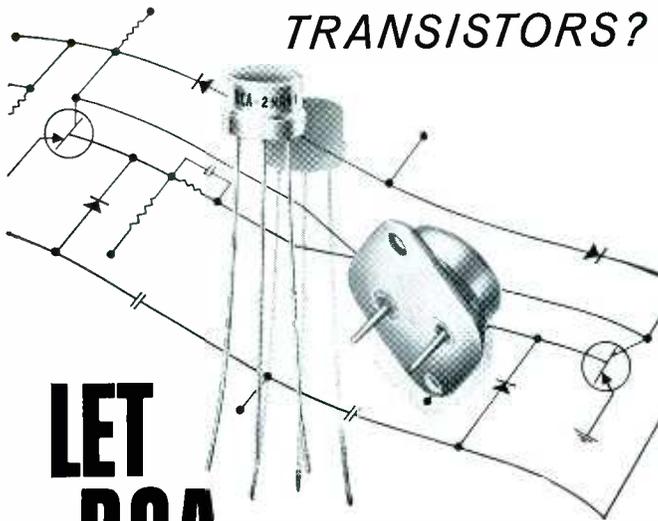Need to  
know more about  
**TRANSISTORS?**



# LET RCA TRAIN YOU AT HOME

in semiconductor physics  
and transistor applications

RCA Institutes Home Study School's new Transistor course is designed to meet the needs of men and women in the field of electronics who realize the growing importance of semiconductor technology. The course covers transistor characteristics and testing methods... prepares you to move up in your job as you increase your knowledge and skills. *No monthly installment payments.* Pay-as-you-learn using the most economical possible home study plan... you pay for your next study group only when you order it.

Courses also available in Electronic Fundamentals, TV Servicing, Color TV, and Electronics for Automation.

SEND FOR THIS FREE 64-PAGE CAREER BOOK TODAY!

**RCA INSTITUTES, INC.**  
A Service of Radio Corporation of America



The Most Trusted Name  
in Electronics



Licensed by the University of the State of New York

RCA Institutes, Inc., Home Study Dept. PF-NO  
350 West Fourth Street, New York 14, New York

Please rush me your FREE illustrated 64-page book "Your Career in Electronics," describing your home training programs, including complete information on the new Transistor course. No obligation. No salesman will call.

Name \_\_\_\_\_ Age \_\_\_\_\_  
(PLEASE PRINT)

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

Korean Vets: Enter discharge date \_\_\_\_\_

IN CANADA: No postage, no customs, no delay. Send coupon to:  
RCA Victor Company, Ltd., 5581 Royalmount Ave., Montreal 9, Que.

## Letters

(Continued from page 12)

At other times and frequencies, the marker generator swamps the curve, sometimes even without showing the marker pip.

A separately-controlled pip that could be placed anywhere on the response curve without causing distortion would be a serviceman's dream, and I am wondering if it could be secured without placing another mortgage on the property.

A. W. MCAULY

Oakmont, Pa.

*This type of equipment is known as a "marker adder" or "mixer adder." The only modification required for using such a unit with your present sweep and marker generator would be the removal of the marker-signal connection going to the sweep output jack, and the installation of a separate marker-output jack. Everyone ready for a new "Test Equipment Annual"?*—Ed.

Dear Editor:

In reference to the article, "That's the Way the Horizontal Sweeps" (May issue), I am interested in knowing how the yoke-current waveform W6 was obtained. The text stated that a 10-ohm resistor was placed in series with the low side of the yoke, and that the scope was connected directly across this resistor.

With the circuit as shown in Fig. 1 of this article, I should think the ground side of the scope probe would effectively short out the damper circuit. If you could clarify this point, it would be most helpful.

May I say that the entire article was very informative and interesting.

GEORGE OHANIAN

Lawrence, Mass.

*Obtaining the waveform is quite simple, the only requirements being those stated in the text. Any scope used for normal servicing can be used; it won't short out the damper circuit as long as the low side of the scope probe is not grounded to chassis. All you are doing is connecting the scope in parallel with the added resistor so you can view its voltage waveform. This calls for a little extra caution in measurement, since the entire scope chassis then assumes a high positive potential with respect to the TV chassis. Since the scope input has a very high impedance, it will not significantly load the yoke circuit or distort the sweep unless the test is attempted on the "high side" of the yoke.*—Ed.

Dear Editor:

Please send me two copies of the 1958 and 1959 *Subject Reference Indexes* to PF REPORTER. I have a copy of every issue to date and wouldn't take anything for them.

JOSEPH M. CATALONO

Crestwood, Mo.

*They're on the way, Joe. You'll find annual indexes for years prior to 1957 in the December issues (some still available—50c each). The 1960 index will be published this coming January, and will be supplied free on request. A monthly index now appears on the reverse side of the Catalog & Literature card in the back of each issue.*—Ed.

Dear Editor:

Enclosed herewith is my renewal order.

I, like many others, also find you have not only a very interesting but also an educational magazine, well worth the subscription price. I've weeded out my subscriptions to all other electronic magazines except PF REPORTER, since I find it covers about all the things in which I am interested.


The letters to the Editor are also very interesting and at times amusing.

HOWARD M. STANG

Elyria, Ohio

*We appreciate both the bouquets and the renewal order, Howard. But when all the letters are as nice as yours, we have a hard time making the answers as entertaining as we'd like!*—Ed.

# MAKE COMPLETE TUBE TEST FASTER, MORE ACCURATELY

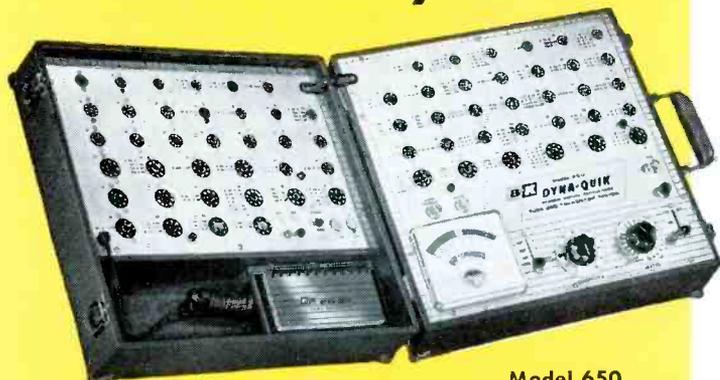

Model 650  
DYNA-QUIK

Simply by checking all the tubes in the set, and testing each tube completely the Dynamic Mutual Conductance way, you can

**SELL MORE TUBES PER CALL  
INCREASE YOUR INCOME\*  
SATISFY MORE CUSTOMERS  
SAVE COSTLY CALL-BACKS  
INSURE YOUR REPUTATION**

\*Actual experience shows TV servicemen average 2 extra tube sales per call. 5 calls per day in 5 days means as much as \$50.00 more income per week.

Widely Used and Preferred by Thousands of Professional Servicemen Everywhere



## Model 650 Dynamic Mutual Conductance PROFESSIONAL TUBE & TRANSISTOR TESTER

With multi-sockets and other B&K features, you can accurately quick-check most of the tubes widely used in television receivers, plus popular home and portable radio tubes. Includes spare sockets for new popular types. Tests each section of multiple tubes separately. Checks for Gm and all shorts. Makes highly sensitive grid emission and gas test. Checks for leakage and life. Shows true tube condition on "Good-Bad" scale and in micromhos. B&K patented bridge circuit. Also tests transistors.

Net, \$179<sup>95</sup>


## Model 550 Dynamic Mutual Conductance PROFESSIONAL TUBE TESTER

Real professional instrument for the limited budget. Provides 52 sockets to quick-check most of the TV and radio tubes usually encountered in everyday service work. Tests each section of dual-section tubes separately. Checks for Gm and all shorts. Makes highly sensitive grid emission, gas, and leakage test. Shows tube condition on "Good-Bad" scale and in micromhos. B&K patented bridge circuit.

Net, \$119<sup>95</sup>



Model 550  
DYNA-QUIK

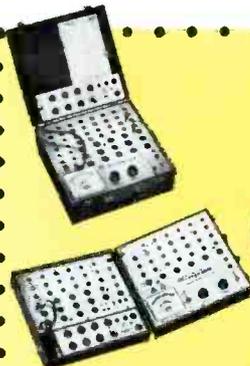

Shows how easily the new "610" fits into Models 550 and 650



Comes in 3 types:

Model 610-500 for use with Model 500 Tube Tester  
Model 610-550 for use with Model 550 Tube Tester  
Model 610-650 for use with Model 650 Tube Tester

## NEW Model 610 ACCESSORY TEST PANEL

Increases Capacity of Model 500, 550, or 650 Dyna-Quik

TO TEST BOTH OLD AND NEW TUBE TYPES

including New TV Types, Thyratrons, Voltage Regulators, Auto Radio Hybrid Tubes, Battery Radio Tubes, European Hi-Fi Tubes, and most Industrial Types

Simply by adding Model 610 to the Dyna-Quik, you have all the advantages of fast multi-socket testing, plus freedom from obsolescence. Enables you to test all present plus future TV, radio, and other tube types. Measures genuine dynamic mutual conductance.

Net, \$49<sup>95</sup>

## NEW TUBE INFORMATION SERVICE

Get test data on new tubes even before you encounter them in the field. Subscribe now to *New Tube Information Service* for owners of B&K tube testers. Issued every 3 months, at \$2.50 per year.



**B&K MANUFACTURING CO.**  
1801 W. BELLE PLAINE AVE • CHICAGO 13, ILL.  
Canada: Atlas Radio Corp., 50 Wingold, Toronto 19, Ont.  
Export: Empire Exporters, 277 Broadway, New York 7, U.S.A.

*"A new standard of perfection in television performance!"*


# SETCHELL-CARLSON

## UNIT-IZED



- Luxurious cabinet exteriors, all hardwood solids, and veneers in choice of African Mahogany, Fruitwood Cherry, Limed Oak or American Walnut.
- All Chassis are full transformer powered and feature supersensitive CASCODE tuners and 3 stages of inductively-coupled I.F. for superior fringe area, suburban and local reception.
- Nearly all models feature the new \*23" or \*\*19" overall diagonal "squared" tube face that lets you see all of the broadcast picture. (Viewable area: \*282 sq. in. or \*\*172 sq. in.)
- Most models are engineered with the exclusive Custom Unit-ized Chassis unequalled in performance, uniformity, and ease of modernization and maintenance, plus versatility.
- All models are equipped with Setchell-Carlson's exclusive Picture-Tube-Saver. (Patent applied for.)

EQUIPPED FOR STEREO

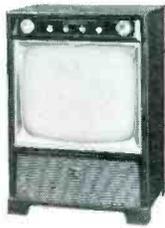

Custom Console 23C61

COMPLETE HOME STEREO CENTER



French Provincial 23L601 (also available in contemporary styling)

EQUIPPED FOR STEREO




Custom Lowboy 23L61

EQUIPPED FOR STEREO



Custom Console 24C61-27C61

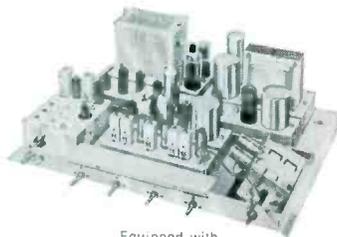

Equipped with Custom Unit-ized 159 Chassis

EQUIPPED FOR STEREO



Custom Lowboy 24L61-27L61

"without a doubt the finest PORTABLE manufactured today!"



Model P-67



Deluxe Console 61C\* (or 601C with X159 Unit-ized Chassis)


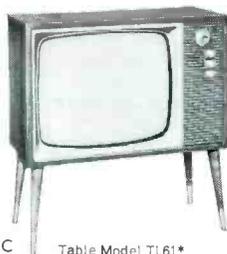


Table Model TL61\*

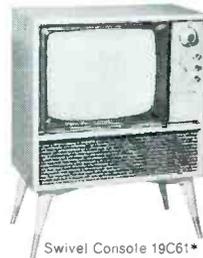

Swivel Console 19C61\*

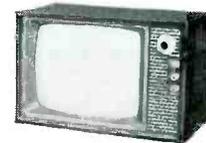



Table Model 19T61\*



RP91B



4814B

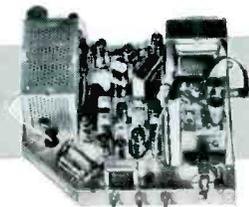

\*Equipped with Classic 361 Chassis



For Complete Information, Write, Wire or Phone:

### SETCHELL-CARLSON, INC.

New Brighton, St. Paul 12, Minnesota  
Telephone: MElrose 3-3131 — Wire FNW

# Why are more Service-Dealers Switching to

# JFD HI-FI TV ANTENNAS?



The Businessman in the Serviceman suit knows five million TV antennas are in need of replacement. For his installations he relies on the superior performance and quality of JFD Hi-Fi Colorennas to guarantee complete customer satisfaction, guard his reputation.

**JFD**

HI-FI HELIX HI-FI BANSHEE HI-FI FIREBALL



## because

they know 5 million antennas need replacement—that JFD HI-FI TV antennas assure them a *bigger* share of this profitable market.

## because

JFD all-out advertising *sells* for them in powerful national mass media—such as Look, TV Guide, Successful Farming, Farm Journal, Progressive Farmer.

## because


JFD is the *total* antenna line with the *right* model, at the *right* price for every location—does the *most* for them in mile-shrinking *performance* and customer *confidence*.

## because


JFD sales stimulators such as cloth patches, decals, mobiles, banners, displays and direct mail give them the *complete* package to *sell* new customers.

**HOW MUCH INSTALLATION BUSINESS ARE YOU LOSING BY NOT SWITCHING TO JFD? THE TV ANTENNA LINE AMERICA KNOWS BEST!**

HI-FI HELIX  
Silver or Gold Anodized

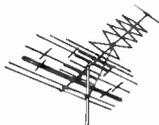

HI-FI BANSHEE  
Silver or Gold Anodized

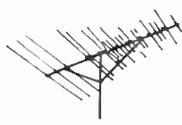

HI-FI FIREBALL  
Silver or Gold Anodized



THE BRAND THAT PUTS YOU

# JFD

IN COMMAND OF THE MARKET

JFD ELECTRONICS CORPORATION, Brooklyn 4, New York

JFD International, 15 Moore Street, New York, New York • JFD Canada, Ltd., 51 McCormack Street, Toronto, Ont., Canada

from **EICO**... a completely new  
CITIZENS BAND TRANSCEIVER

that meets  
FCC regulations\*



Model 760: 117 VAC  
Kit \$59.95 Wired \$89.95  
Model 761: 117 VAC & 6 VDC Kit \$69.95  
Model 762: 117 VAC & 12 VDC Kit \$99.95  
incl. mtg. bracket (Pat. Pend.)

\*EICO premounts, prewires, pretunes, and seals the ENTIRE transmitter oscillator circuit to conform with FCC regulations (Section 19.71 sub-division d). EICO thus gives you the transceiver in kit form that you can build and put on the air without the supervision of a Commercial Radio-Telephone Licensee!

Highly sensitive, selective SUPERHET (not regenerative) receiver with 5½ dual function tubes and RF stage. Continuous tuning over all 23 bands. Exclusive Super-Hush® noise limiter. AVC. 3" x 5" PM speaker. Detachable ceramic mike. 5-Watt crystal-controlled transmitter. Variable "pi" network matches most popular antennas. 12-position Posi-Lock® mounting bracket. 7 tubes and 1 crystal (extra xtals \$3.95 each). Covers up to 20 miles. License available to any citizen over 18—no exams or special skills required, application form supplied free. Antennas optional.

## YOU PROFIT WITH EICO

Everything in top-quality  
TEST EQUIPMENT for Shop  
and Field—at savings of 50%.



COLOR & Mono DC-5MC  
Lab & TV 5" Oscilloscope #460  
Kit \$79.95, Wired \$129.50  
5" Push-Pull Oscilloscope #425  
Kit \$44.95, Wired \$79.95



Peak-to-Peak VTVM #232 & \*UNI-PROBE®  
Kit \$29.95, Wired \$49.95  
\*U.S. Pat. No. 2,790,051  
Vacuum Tube Voltmeter #221  
Kit \$25.95, Wired \$39.95

More typical EICO values: Signal Generators from \$19.95, Tube Testers from \$34.95, Sweep Generators from \$34.95, Power Supplies from \$19.95, VOMs from \$12.90.

Everything in CUSTOM HI-FI:  
finest quality at 1/3 the cost.



FM Tuner HFT90  
Kit \$39.95, Wired \$65.95  
Cover \$3.95. Includes FET.  
AM Tuner HFT94  
Kit \$39.95, Wired \$65.95  
Includes Metal Cover and FET.  
FM/AM Tuner HFT92  
Kit \$59.95, Wired \$94.95  
Includes Metal Cover and FET.




Stereo Dual Amplifier-Preamp HF81  
Kit \$69.95, Wired \$109.95  
Includes Metal Cover.  
Stereo Dual Amplifier AF4  
Kit \$38.95, Wired \$64.95  
Includes Metal Cover.

Write for free catalog PF-11 and name of nearest distributor.

Most EICO distributors offer budget terms.

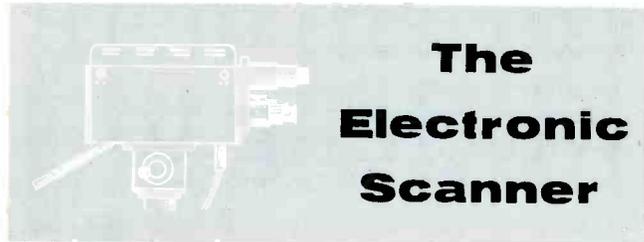**EICO**

3300 N. Blvd., L.I.C. 1, N. Y.  
Add 5% in the West



## The Electronic Scanner

### 1961 TV Training Sessions

Technical training sessions on the 1961 line of Westinghouse TV receivers will be conducted at hundreds of locations throughout the country this fall. Trained specialists will describe 1961 circuitry, placing special emphasis on new circuits and mechanical designs such as remote control systems. Troubleshooting techniques will be given a large share of attention, and each serviceman will receive a training manual plus a 1961 "Pocket Master." Contact your nearest Westinghouse distributor for details on meetings in your area.

### Test Equipment Development Center

Hickok's new research and development center in Cleveland, utilizing 1400 square feet and 52 engineering personnel, will be devoted to the development of new instruments for the electronic industry. Walter Cerveney, Chief Engineer for the company (far left) looks on as engineer J. D. Feher explains advantages of unique rack-mounting principle to Einar Carlson and P. H. Neville.



### Success Story

Among the servicemen groups who viewed the newest SENCORE slide film, "Old Tubes Seldom Die . . ." was this happy crew of Compton, Calif. Fred Bowerman, R.T.A. president, was host at his Mobile TV Service Lab. Other "Time-Saving Service Clinics" were also held recently at Denver, Colo. and Indianapolis and Richmond, Ind. Ed Flaxman, SENCORE v.p., presided at all four meetings. According to Herb Bowden, company president, the acceptance of SENCORE test instruments by servicemen has resulted in a 150% sales increase over last year. During the last 4½ of the 10 years it has been in operation, the company's net worth has increased more than ten times. Not bad, considering a start with less than \$1,000 capital and 1,000 feet of factory space!



### Which Tubes to Carry?

Inventory lists to guide servicemen in stocking tube caddies are now being provided with each of three service cases available through General Electric tube distributors. Stock guides of 162, 228, and 365 tubes are recommended for the three cases. Incidentally, one of the many helpful items noted in G-E's new dealer sales promotion catalog is a set of TV Service Shop Plans. Your G-E distributor can get them for you — only 50c.

### Opportunity Knocks

Fidelitone's nationwide "Fall Harvest" program, in which trade and consumer advertising is calculated to reach 2½ million readers every month, will feature the "Pyramid Point" diamond needle. Described as the first really new shape in a phonograph needle since its inception in 1887, the new concept in phono needles is named for its contour, which rides along the record "walls" without slipping into the "valleys."

# make your first move to **ROHN**




You Have the Greatest Sales Potential by Far With America's MOST COMPLETE LINE OF

## TOWERS—MASTS ROOF TOWERS Installation Accessories
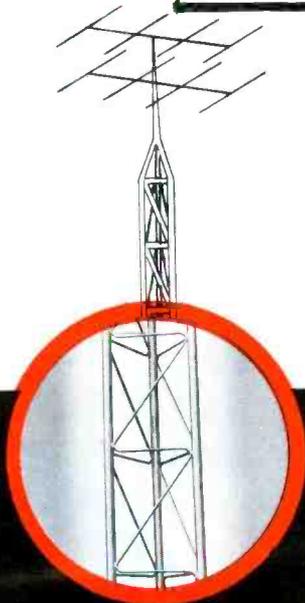
### ROHN TV TOWERS

ROHN makes the finest towers available for television reception! Illustrated is the No. 25 with amazing "zig-zag" cross bracing design. The entire tower is rated 33% stronger than other similar sized towers. Yes, sell and install the No. 25 up to 50 feet self-supporting or, properly guyed, up to 360 feet!

Or if you prefer, sell the popular ROHN No. 6 tower with the famous "Magic Triangle" cross-bracing. Both are fully HOT DIPPED GALVANIZED AFTER FABRICATION! Sections in easy-to-handle 10 ft. lengths.



From every standpoint, ROHN Towers offer you MORE . . . more quality, more variety, more advanced design, more sales features, more service, more total sales and more PROFITS! Move forward with these ROHN items!



### ROHN COMMUNICATION TOWERS

Here you have FIVE complete lines of heavy-duty, FULLY ENGINEERED communication towers to fulfill any communications requirement. Shown is the ROHN "SS" tower which is self-supporting up to 130 feet. Other models — (30-40-50-60) are available in heights up to 630 feet when guyed! Handle these towers for the demand in your area. There's a complete NEW catalog on this line. Get a copy so you'll have it on hand.


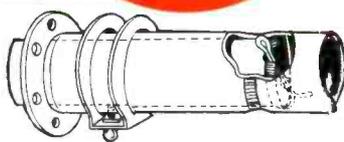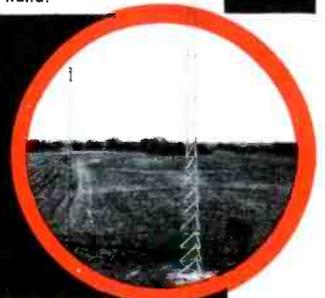
### AMATEUR "FOLD-OVER" TOWERS


Specially designed "fold-over" towers are the best ever designed for amateur radio and experimentation. They are the most desired because they "fold-over" completely so you work on the ground for ease and safety. Three sizes, including heavy-duty type to handle any needs. All hot dipped galvanized.




### TELESCOPING MASTS

Unexcelled in design, structural strength, and sales appeal. All popular sizes, heights, and weights available. Also, mast tubing in exact specifications that's demanded today.

### ROOF TOWERS . . .

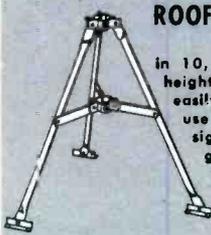

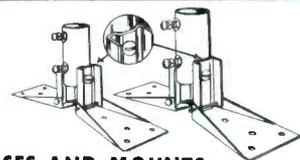in 10, 5, 3, and 2½ feet heights — very popular — easily shipped — ideal in use — the best ever designed — in hot-dipped galvanized finish — truly a big profit item for you!



### BASES AND MOUNTS

Wide variety of bases and mounts. Special features include "locking" device — also cast aluminum roof mounts — and a host of other installation items . . . get full details.



### TV SERVICE TABLE

For holding TV sets while servicing, or storing, or for mobile use of set in such places as motels, hospitals, etc. Ideal for dozens of uses — thousands sold. Large casters — a real work-saver.

# ROHN

Manufacturing  
Company

116 Limestone, Bellevue  
Peoria, Illinois

Get complete catalog from your ROHN representative or jobber or MAIL THIS COUPON!

Gentlemen: Please send me literature on ROHN Towers and Accessories.


Firm \_\_\_\_\_  
Name \_\_\_\_\_ Title \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_

# PHILCO LANDSLIDE

ALL OFFERS GOOD  
UNTIL DEC. 10th

Wonderful  
GIFTS FOR  
CHRISTMAS

SERVICE AIDS  
for your business

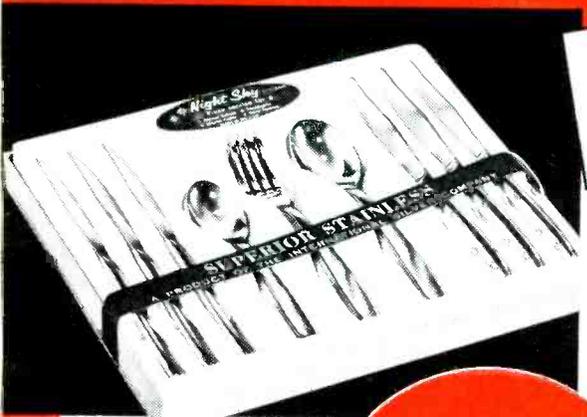

## 24-Piece Stainless

SERVICE FOR SIX  
INTERNATIONAL  
SILVER COMPANY  
new "Night Sky"  
pattern

**FREE**  
with your purchase of  
75 PHILCO  
TUBES

## Brunswick Black Beauty Bowling Ball

CUSTOM DRILLED AND  
PERSONALIZED WITH  
YOUR INITIALS



The most popular  
bowling ball in America!

## Argus C-3 35mm Color Slide Camera



**FREE** with your purchase of  
500 PHILCO TUBES  
Also, FREE offers on other famous cameras!

**FREE**  
with your purchase of  
375  
PHILCO TUBES



## 7 x 35 Center Focus Binoculars & Case



**FREE** with your purchase of  
400 PHILCO TUBES

## Million Miler Bowling Bag

UNMATCHED FOR  
RUGGED DURABILITY

Popular triangle style. Moulded of genuine  
U. S. Royalite—scuff proof . . . everlasting!



**FREE**  
with your  
purchase of  
150  
PHILCO TUBES

## Faribo Orlon Pak-A-Robe

In Vinyl  
Carrying  
Case



**FREE** with your purchase of  
150 PHILCO TUBES

## "Glolite" Electric TV-Lamp Clock

\$1195  
value



**FREE** with your purchase of  
100 PHILCO TUBES

## 6-Piece Flint Cutlery Set

**FREE**

with your  
purchase of  
200 PHILCO  
TUBES



\$1995  
value

## \$10.00 Value Airguide Barometer



**FREE** with your purchase of  
100 PHILCO TUBES


# OF FREE OFFERS!

with your purchases of

## PHILCO TUBES

There's something for everybody! All are FREE with your purchases of Philco Receiving Tubes you use every day!
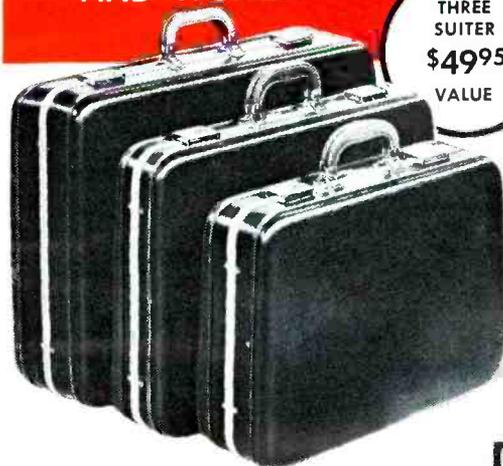
### Million Miler LUGGAGE FOR MEN AND WOMEN



THREE  
SUITER  
\$4995  
VALUE

Wide selection, including the 26" three-suiter, 24" two-suiter and 21" companion for men, shown above. The last word in durability and modern styling!

### FREE!

3-Suiter with 400 PHILCO TUBES  
2-Suiter with 350 PHILCO TUBES  
Companion with 225 PHILCO TUBES  
Similar offers on women's luggage

### Hamilton Cosco Folding Table and Chair Set

TABLE ONLY, **FREE**  
with your purchase of  
100 PHILCO TUBES

TWO CHAIRS, **FREE**  
with your purchase of  
150 PHILCO TUBES

### FREE

Complete 5-Piece  
Set of Table and  
Four Chairs  
with your purchase of  
400 PHILCO TUBES

\$4675  
value



### Famous Waltham & Hamilton Watches

For Men—  
WALTHAM  
"SENATOR"  
**FREE**

with your purchase of  
300 PHILCO TUBES

Also: Free Offer on Hamilton "Gardner" for Men

For Ladies—  
HAMILTON  
"TRIXIE"  
**FREE**

with your purchase of  
400 PHILCO TUBES



### Choose from these Free Business Aids



TV TOTER  
**FREE**  
with your purchase of  
100  
PHILCO TUBES


LUXO  
Magnifier-Lamp for  
Difficult Service Jobs

**FREE**  
with your purchase of  
500 PHILCO TUBES


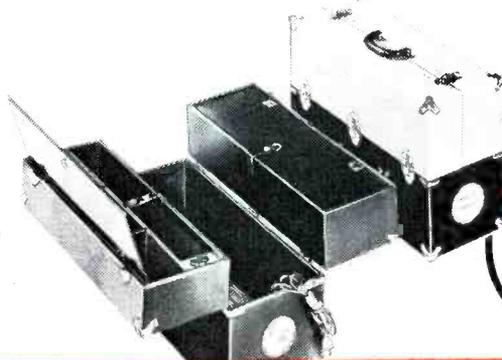
### TUBE CADDY

with built-in "Cheater Cord"  
and Pin Straightener  
Choice of two finishes



EITHER  
CADDY

**FREE**  
with your purchase of  
175 PHILCO  
TUBES

### "Big Eight" FOLDING POKER TABLE



Natural Harvest  
or Mahogany  
frame finish

Felt top—padded  
and upholstered with  
100% virgin wool green felt

**FREE** with your purchase of  
400 PHILCO TUBES

## SEE YOUR PHILCO DISTRIBUTOR



## understanding TRANSISTOR TESTERS

While experience tends to prove, on the whole, that transistors fail less often than vacuum tubes, a considerable number of transistors *do* fail. Therefore, anyone working on transistorized circuitry—whether it be in radio or television receivers, or in industrial equipment—must become familiar with the various ways in which transistors can be tested, together with the reasoning behind these tests.

While a number of tests can be performed on a transistor, just as a number of tests can be performed on a vacuum tube, servicemen will find that the test equipment designed for their use is capable of performing three primary tests. These include checks for shorts, leakage and gain.

### Short Test

The basic short test employs the circuit shown in Fig. 1. Here, the base and emitter elements are tied together and connected to one side of a battery. The other side of the battery connects to the collector through a suitable milliammeter and a current-limiting resistor. The transistor is back-biased, so very little current should flow. If this is found to be true, no internal shorts

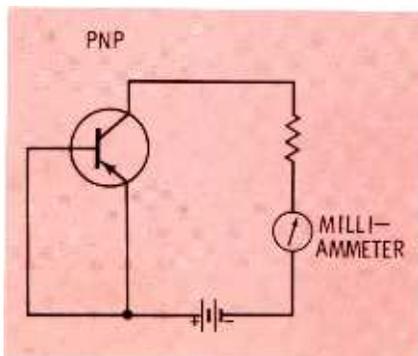


Fig. 1. With reverse bias on transistor, any sizable current indicates short.

exist in the transistor. However, if a sizable current is produced, the resistance between the collector and one or both of the other two elements is too low. (Note: This is not a test for leakage current, which we will discuss in a moment. This test simply determines if there are any short circuits within the unit.)

Most transistor testers do not incorporate a short test because the leakage test, which is normally part of all test procedures, will usually detect short circuits by an indication of excessive current flow. However, a few instruments do perform the short test, and the instructions state that transistors should be subjected to this test first. It is interesting to note that the short test has a direct counterpart in tube testing, where a similar test is always made prior to the check for gain.

### Leakage Test

One of two leakage tests is almost always performed by transistor testers, and some instruments perform them both. The most common leakage test uses the circuit in Fig. 2. The emitter is connected to one side of the battery and the collector to the other side, while the base element is left unconnected.

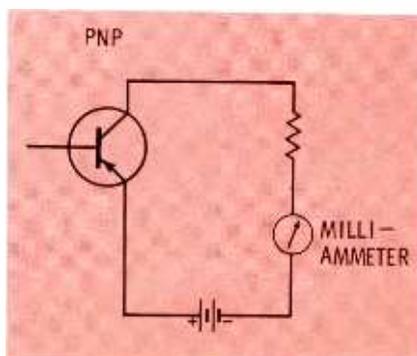


Fig. 2. Open-base circuit for checking leakage between emitter and collector.

A small milliammeter and a suitable current-limiting resistor are included in the hook-up. The amount of current in the circuit depends on the temperature at which the transistor is being checked, the resistivity of the germanium or silicon, and the applied voltage. If there is a short circuit within the device, or if there is any contamination on the transistor surface which would enable a sizable current to flow, the meter reading will be abnormally high. It is desirable for this reading to be as low as possible.

In most instances, the meter dial has a special leakage scale divided into different-colored segments, or marked off into separate regions, bearing such notations as high, medium, and low (or poor, fair, and good). As long as the transistor does not test in the poor or high regions, it can be considered usable. Some leakage is to be expected however, and will almost always be encountered. As a general rule, small signal transistors have considerably less leakage than power transistors. Also, germanium transistors have more leakage than silicon transistors. In all cases, any short circuit or low-resistance path through the

• Please turn to page 68


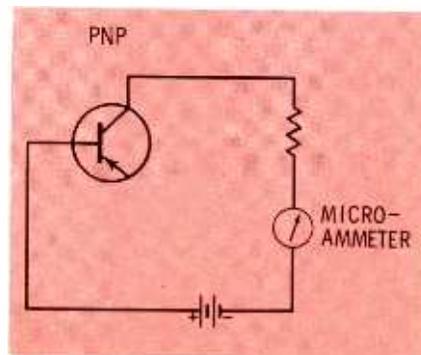
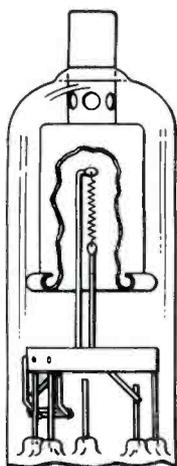


Fig. 3. Open-emitter circuit for measuring minute base-collector leakage.

at my  
 .....  
 expense  
 .....  
 try the  
 CBS  
 1G3GT/1B3GT

(LET IT CUT YOUR CALL-BACKS)

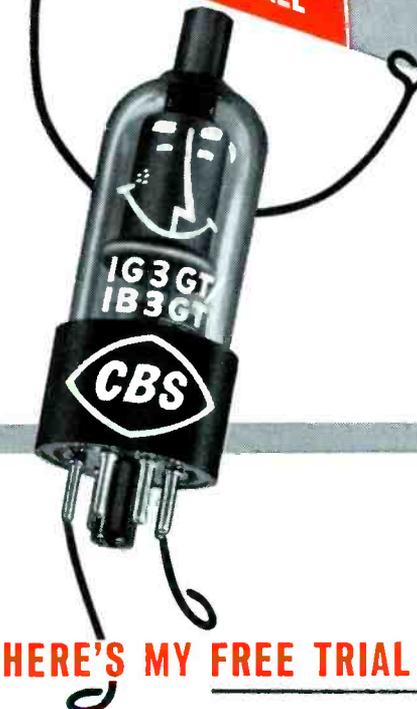


Yes, cut your call-backs four ways:  
 1. With the solid four-point suspension of my Bantet stem. 2. With my simplified two-weld filament support. 3. With my sagproof-flakeproof stretched filament coil (possible only with my costly catapnoetic coating applied *after* filament weld assembly). 4. With the permanent positioning of my anode with respect to my filament.

These four features keep me clean as a whistle inside . . . with no loose particles to make me get grouchy and sputter. My filament coating stays put. My filament and anode keep a respectful and arcproof distance. And you can stop worrying about arcs and burn-outs . . . because I like high voltage!

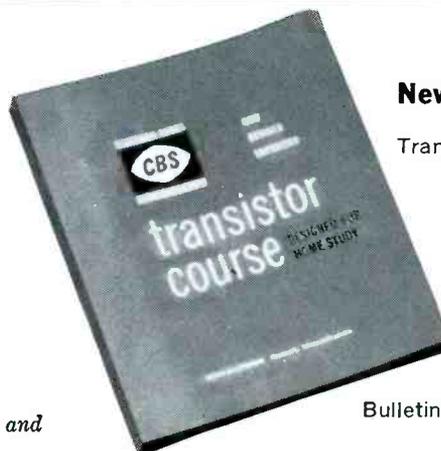**HERE'S MY FREE TRIAL OFFER**

Get one CBS 1G3GT/1B3GT FREE with your purchase of nine from your distributor of CBS Electronics products. Let me prove to *you*, at my expense, CBS TOTAL RELIABILITY . . . proved in performance year in, year out by leading TV and radio set manufacturers. Act now . . . this offer ends November 30.



**New . . . Revised . . . Expanded**

1961 Edition of the popular CBS Transistor Home-Study Course is now available. Many added pages of important transistor information make this easy-to-understand, proven course a timely "must" for service technicians with an eye to the future. Join the thousands upon thousands of engineers and technicians who are already profiting from this practical course. Write today for Bulletin PFF-276 giving complete details.

**CBS ELECTRONICS**

Danvers, Massachusetts

A Division of Columbia Broadcasting System, Inc.

Receiving, industrial and picture tubes • transistors and diodes • audio components • and phonographs

# APPLICATIONS of MAGNETIC AMPLIFIERS



Magnetic amplifiers are taking over many industrial jobs from vacuum-tube amplifiers, especially where high power is required. These rugged devices are used in lighting, power, heating, and motor-control circuits, as well as in servo systems, voltage regulators, timers, counters, computing circuits, and many other applications.

Their basic principle of operation consists of placing a variable inductive reactance in series with a load across a power supply, so that the current through the load can be varied. In Fig. 1 (a simplified diagram of a typical magnetic amplifier), two load windings on a common core pass current on alternate half-cycles of the AC supply voltage. A control winding on the same core receives direct current which can be varied to increase or decrease the degree of magnetic saturation of the core. In turn, this varies the reactance in the load circuit. Since only a small amount of power in the control winding can regulate a much larger load current, the device is classified as an amplifier.

To understand how the reactance is affected by core saturation, let's take a short excursion into the operating theory of inductive components. The permeability of the

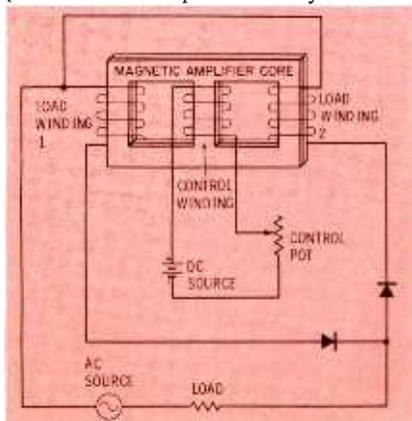


Fig. 1. Simplified diagram of self-saturating magnetic amplifier circuit.

core, or its ability to conduct magnetic flux, is closely proportional to the applied magnetizing force—until point 1 in Fig. 2 is reached. After this point, the permeability drops sharply, so that further increases in magnetizing force do not produce proportional increases in the amount of core magnetism. The portion of Fig. 2 between points 1 and 3 represents the region where the core approaches full saturation.

The key point in this discussion hinges on the steepness of the permeability curve from point 1 to point 3. The inductance and inductive reactance also follow an identical curve; therefore, when the core is just barely saturated, a relatively slight addition or subtraction of magnetizing force causes a large change in reactance. This explains why the current in the control winding of a magnetic amplifier need not be large.

Increasing the control current drives the core farther into saturation; from the permeability curve in Fig. 2, we can see that the reactance of the load windings will decrease, and the load current will increase. On the other hand, a decrease in control current will tend to desaturate the core, thereby increasing the series reactance and reducing the current delivered to the load.

Fig. 1 is a combination of a pictorial and schematic diagram, used primarily to illustrate circuit action. In practice, a saturable reactor may be shown on schematic diagrams in a number of different ways. Several of these appear in Fig. 3. Although only two coil sections are shown in

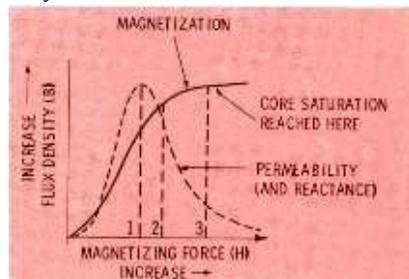


Fig. 2. Inductive reactance sharply drops as saturation point is reached.

each case, more would probably be used in actual practice. Fig. 3A is somewhat pictorial, while 3B is a conventional transformer diagram. The letters SR (for saturable reactor) may not always be included. The diagram of Fig. 3C has been adopted by several interested groups and seems to be making some headway toward becoming the standard symbol. Many manufacturers, however, still use some other symbol.

## Bias and Feedback

An AC control current is often desired instead of DC, but the application of pure AC to the control winding would introduce problems. For instance, if the applied control voltage periodically reversed in direction, the changes in magnetic flux would lag the voltage changes by a time interval determined by the core material. This lagging effect, called *hysteresis*, would greatly reduce the degree of control which could be obtained. Core materials are chosen for their low hysteresis ratings, but this condition cannot be eliminated entirely.

Here's another problem that discourages the use of a pure AC control input: If the flux continually changes direction, the core will be saturated during only a small portion of each control alternation; thus, control will be obtained over only a portion of the input signal.

To make it possible to feed an AC input to the control winding, a DC current, called *bias*, is added. Its effect on circuit operation is shown in Fig. 4. With the bias current added, the operating point is shifted to the right as indicated by

• Please turn to page 71

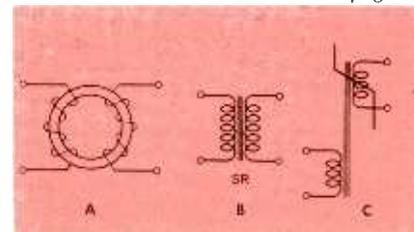


Fig. 3. All these symbols have been used to represent magnetic amplifiers.

# GOING "BROKE" ON FILAMENT "BREAKS"?



**NEW SYLVANIA 1G3/1B3 HAS  
BUILT-IN "PROFIT PROTECTION."**

**I**T'S HARD to make a dollar in this TV service business. And call-backs on tubes make it even tougher. That's why Sylvania concentrates on making tubes that perform better and last longer.

Take the new Sylvania 1G3/1B3, for example. The improved filament has increased life span and operates at reduced temperature. Plate is extra-big. Volume of space between it and the filament is enlarged. (That adds to "cooler" filament operation without lowering emission capabilities, and cuts probability of plate-to-filament arc-over.) Glass envelope has extraordinarily high electrical resistivity. This reduces electrolysis and the development of gas and leakage.

Further, every new Sylvania 1G3/1B3 is tested for emission, for arcing and electrical stability at maximum ratings, and arc-over-proofed at higher-than-rated plate voltages to give extra assurance of long tube life.

So, give yourself a break. Replace defective 1G3/1B3 high-voltage rectifier tubes with the new long-life SYLVANIA 1G3/1B3. Available from your distributor . . . now! Electronic Tubes Division, Sylvania Electric Products Inc., 1740 Broadway, New York 19, N. Y.



# SYLVANIA

Subsidiary of **GENERAL TELEPHONE & ELECTRONICS** 

# the expanding

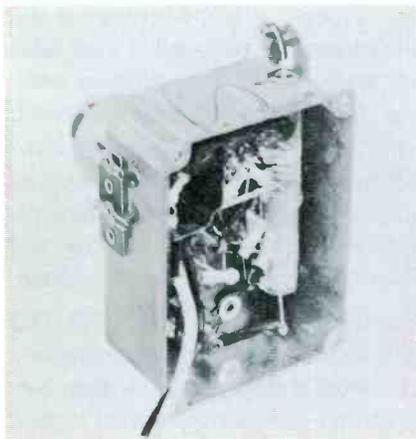


Fig. 1. Two different styles of one-tube FM tuners made in Western Germany.

Just a few years ago, when the hi-fi boom first began to pump new life into FM radio broadcasting, practically all receiving equipment was designed to please the serious audiophile. The prospective buyer had a wide choice of deluxe FM tuners for use in high-fidelity systems, but he had to hunt awhile if he wanted a small, self-contained radio that would pick up FM stations.

The market has changed greatly since then. A sizable demand for inexpensive FM radios has arisen among people who are more attracted by FM's high-quality programming than by its technical features—and this need is now being met by most of the major radio manufacturers. In addition, domestic production of FM car radios has begun in earnest.

### Table Radios

Since table FM receivers have been practically absent from the market for such a long time, the new models are almost complete strangers.

The simplest AC-DC radios in the FM field are following a consistent circuit pattern. FM-only sets typically have five tubes, plus a silicon or selenium rectifier to supply B+ voltage; for FM-AM combinations, a 12BE6 is added to serve as an AM converter. The FM lineup is usually as follows: 12DT8 dual-triode RF amplifier and converter; a pair of 12BA6 IF stages; a 19T8 as ratio detector and AF amplifier; and any one of the popular miniature beam-power tubes (35- or 50C5, 35- or 50EH5) in the audio output stage.

### RF Tuner

The most interesting innovation in the new crop of FM receivers is the "front end," which currently tends to be mounted on a small subchassis (somewhat like a TV tuner) containing all RF and frequency-converting circuits. This trend began with units of the type shown in Fig. 1, made in Western Germany. Some models are of hand-wired construction, as in Fig. 1A, while others of recent vintage contain a printed wiring board (Fig. 1B). The single tube is generally a 6DT8 or 6AQ8/ECC85, or a series-string counterpart of one of these types. In this dual triode, the RF section usually operates as a grounded-grid amplifier, while the second section is an *autodyne* converter—combining the functions of oscillator and mixer.

In the autodyne stage, oscillation is maintained by feedback from a plate-circuit tickler coil to a tuned tank in the grid circuit (see Fig. 2). In some other tuners of generally similar design, the tank is in the plate circuit and the feedback coil is at the grid—but the mode of operation is still basically the same.


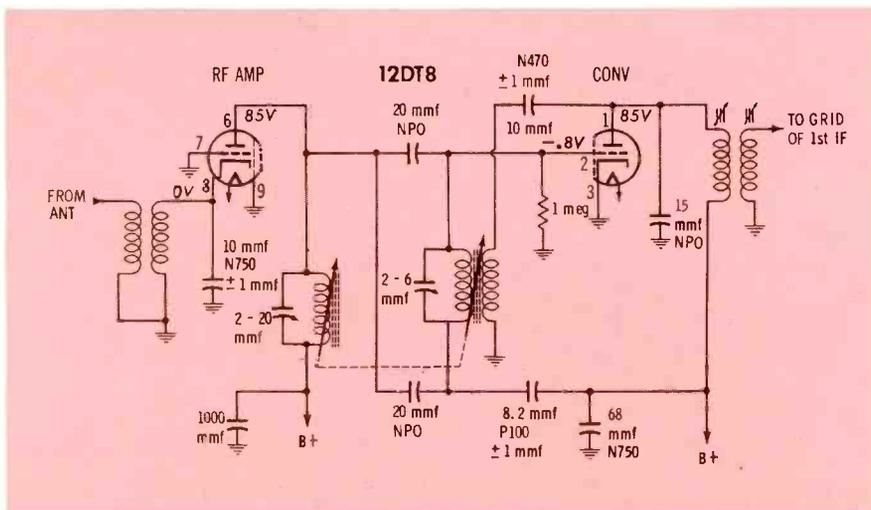


Fig. 2. Schematic of unit in Fig. 1A; note temperature-compensating capacitors.

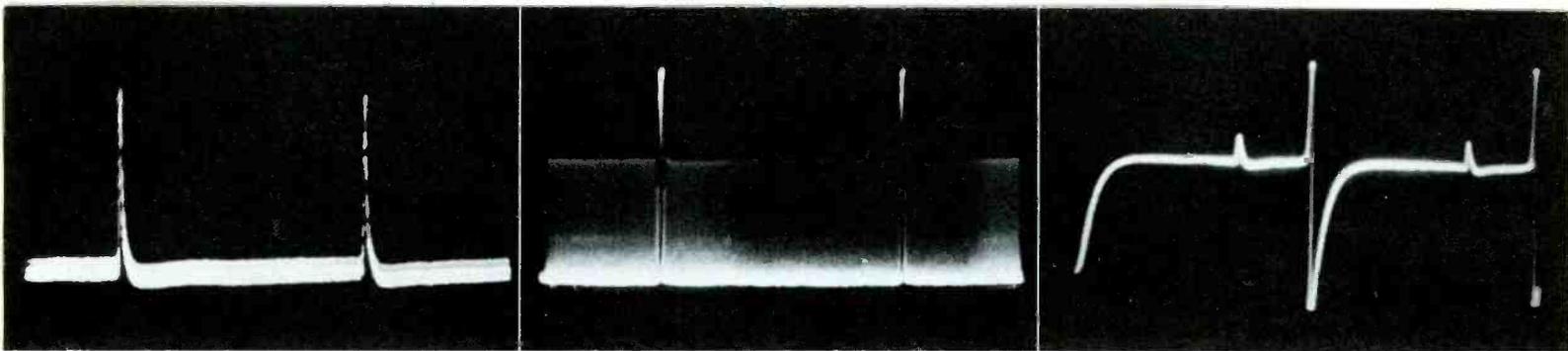



The waveform showing the 60-cps sync-pulse output of the vertical integrator is helpful in dealing with cases of unstable vertical sync. While you have the oscillator disabled to prevent its feedback signal from obscuring the sync pulses, use the opportunity to view the *input* waveform of the integrator. (See middle photo.) In many sets using a conventional vertical multivibrator, it is normal for the vertical sync pulses at this point to have a somewhat greater amplitude than the horizontal pulses (represented by the hazy area in the waveform). Equal heights




for the two sets of pulses many also be considered normal in some circuits, but noticeably smaller vertical pulses may well be the underlying cause of jittery vertical hold.

For a quick check to establish the presence of sync pulses at the integrator output, don't disable the oscillator—merely use the hold control to induce a slight vertical rolling of the picture. The sync pulses should then appear as small "traveling" positive pips, as shown in the third waveform.

*Key waveforms normally shown on schematics become familiar through constant "re-view," and it doesn't take long to become skilled at recognizing deviations from the normal patterns. However, once you recognize a fault at one of these key check points, you are apt to lay down the scope probe and rely on other means of further isolating the cause of the trouble.*

*But why change horses in midstream? In many cases, you can save time by checking other waveforms in search of further clues about the trouble at hand. Although these waveforms are not generally shown in service data, many of their patterns are fairly consistent from one set to another, and radical departures from the norm will pinpoint the trouble to a few specific components.*

## SECONDARY

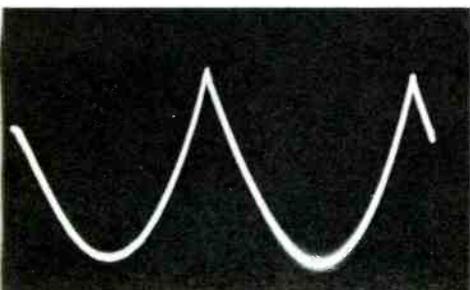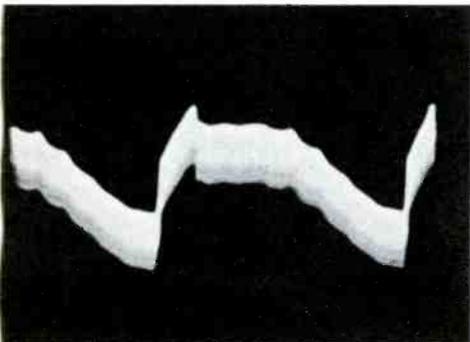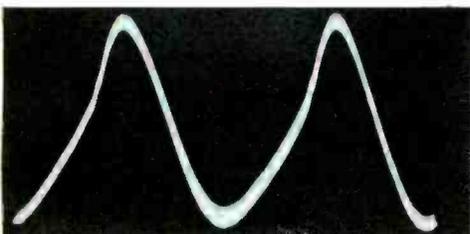



Theoretically, there should be pure DC on the AGC line of a normally operating receiver. In actual practice, you're more likely to encounter a slight amount of either sync, vertical, or video energy at this point. The signal will seldom exceed 1 volt peak to peak under normal conditions—and it may be much weaker. However, with an AGC filter capacitor open, you can expect this signal to increase in amplitude by 10 or 20 times. Excessive modulation on the AGC line can produce a number of different trouble symptoms including complete loss of video, negative picture, hum bars, or poor synchronization.

When the boost B+ is used to supply plate and bias potentials for several other circuits in a receiver, the boost source is usually well filtered. Although you'll normally find a certain amount of ripple modulation along this line, the AC component should be relatively minute compared to the DC voltage. If the signal at the boost source is viewed at one-half the horizontal sweep rate, or 7875 cycles, you will probably note a waveform similar to that shown. In most cases, however, you'll also find an equal amount of vertical energy when viewing the pattern at a 30-cycle scope-sweep rate. If a decoupling or filter capacitor associated with the boost supply is open, horizontal energy may reach the vertical section and cause unusual blanking symptoms or poor vertical sync. On the other hand, if vertical energy reaches the horizontal section, it can produce raster bends, poor horizontal linearity, or erratic horizontal sync.

The signal on the cathode of a vertical output tube normally varies with the setting of the linearity and height controls, and the deflection angle also has some bearing on the amplitude. Typical values are .5 to 3 volts peak to peak in circuits which employ a linearity control in the cathode circuit. With an open electrolytic cathode-bypass capacitor, the waveform takes on a sawtooth shape, and its amplitude increases to about 25 volts peak to peak. This fault generally causes vertical shrinkage of the raster, with distorted linearity and possibly foldover; however, the serviceman may not notice these symptoms because they can often be corrected by resetting height and linearity.


When you're confronted with a problem that involves loss of horizontal sweep, and you find a satisfactory drive signal on the grid of the output stage, how can you quickly check to see if the output tube is conducting? One of the simplest ways is to look at the waveform on the cathode. This may come as somewhat of a surprise, but even if this pin is grounded, you should still be able to detect a horizontal pulse in the neighborhood of .01 to .05 volts peak to peak (or higher)—provided the tube is conducting. You need only connect the "hot" scope lead directly to the cathode pin of the tube socket and attach the ground lead to the chassis a few inches away. Sensitivity of the scope must, of course, be adequate to produce at least a slight indication.

Scoping the screen of the horizontal output stage can often pinpoint the cause of raster bending, poor linearity, or a ringing condition. Here, we have pictured a typical waveform obtained at this point. Normal amplitudes may vary from 4 to 40 volts peak to peak, depending on how well the screen is bypassed to ground or cathode. Should you ever encounter a signal with an amplitude of from 100 to 200 volts, check for an open screen-bypass capacitor. It also pays to check this point for any unwanted vertical-sweep or power-line modulation by setting your scope at a 30-cycle sweep rate.

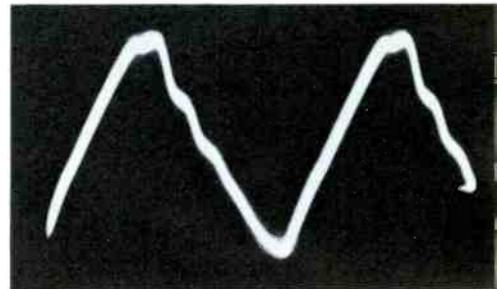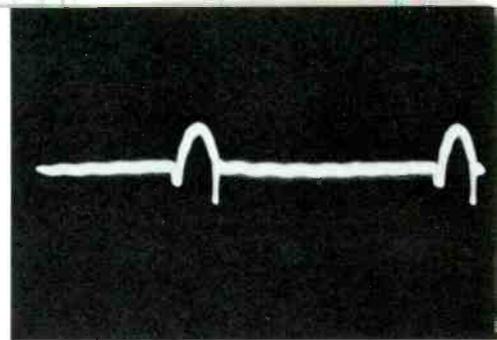

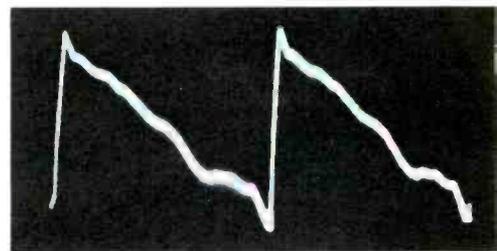
## TV WAVEFORM CHECKS


You'll also find a certain amount of normal signal voltage at the screen of the video amplifier or output tube. Even with this point well bypassed by an electrolytic, you'll generally be able to observe either a composite video signal or a damped pulse resembling that shown here. The set may function properly with a signal as strong as 10 volts peak to peak at this point; however, when the amplitude shoots up to 40 or 50 volts, be on the lookout for an open bypass. Symptoms resulting from this fault include a dark and smeared picture, excessive contrast, hum modulation bars, and unstable sync.



When troubleshooting to find the source of 60-cycle modulation, picture ringing, or similar interference problems, you may find it advantageous to check the cathodes of the video IF stages for any unusual or excessive waveshapes. Normally, there will be a small positive DC potential on the cathode pin, but no detectable AC signal will be developed across the cathode resistor. In a few receivers, however, you may notice a slight 60-cycle or video component at these points. The amplitude of this waveform should be considerably less than 1 volt peak to peak; if it isn't, check for defects such as heater-to-cathode leakage within the tube itself. This procedure can actually be quicker than substituting or testing the IF tubes.

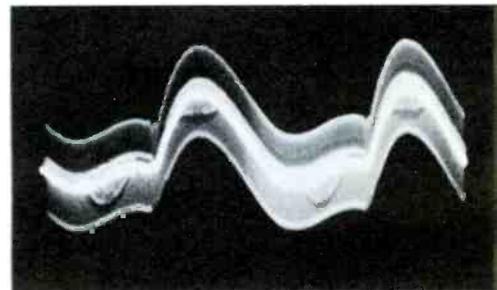

If any signal can be detected at the screen grid of a video IF tube, it will most likely consist of a 60-cycle pulse with a peak to peak value of less than 1 volt. When isolating the cause of picture ringing or hum modulation, you may suspect that one of the IF stages is oscillating, or that a stray AC voltage is modulating the video signal via the screen-grid circuit. Any unusual signal on the screen grid should prompt you to check for poor B+ filtering, leakage in the tube, or an open bypass capacitor. Sometimes, however, it is normal for a weak, distorted composite video signal to appear on the screen of the final video IF stage—especially if this element is connected directly to the bottom of the detector-transformer primary without the use of a decoupling network.

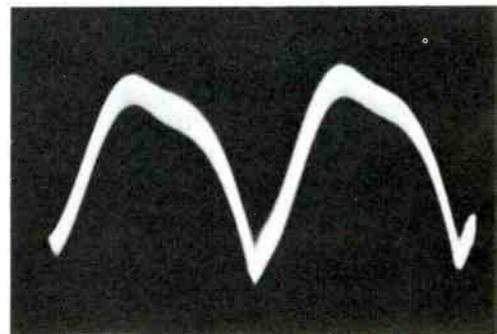

# Spotlighting the 1961 TV-lines

*Highlights of circuit features in all the new fall TV lines.—by Joe A. Groves*

What do the new 1961 TV's hold in store for the serviceman? Do the "old standard" circuits predominate, or is there a whole flock of new ones to contend with? What has the swing to 19" and 23" picture tubes done to the sweep, video, and high voltage circuits? These are only a few of the questions servicemen have as new models begin to flood into the field.

If you're a service dealer, you've no doubt been briefed on the selling points of some of the new lines—but what about the "insides" of those fancy cabinets and cases, and how do they compare with others on the market? You need this intimate knowledge to talk intelligently about your product.


If you've confined yourself strictly to servicing, you too will be called upon to discuss the new crop of sets by many of your customers. Remember, they look to you as authority, and in order to maintain a "well informed" status in their eyes, you must have some concept of what the new sets are like.

Here, after spending several weeks actually examining many of the sets, and studying hundreds of schematics, is a condensation of our findings—confined to the pertinent facts on the lines of sixteen manufacturers.
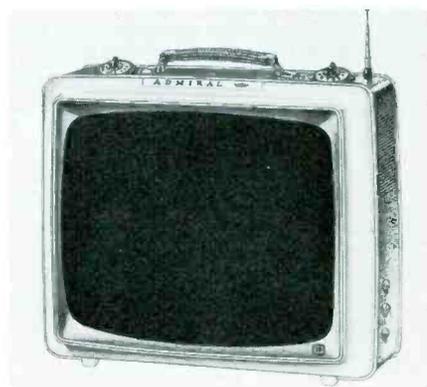
## Admiral

Three basic chassis series form the nucleus of Admiral's 1961 black-and-white TV line, which ranges all the way from a 14-tube, transformerless *Thinman* portable, to an 18-tube, transformer-powered console that includes a stereo amplifier in the audio section. Sweep circuits vary to accommodate picture tubes with deflection angles from 92° to 114°. All picture tubes feature the new square-cornered shape, and are of two sizes—23" with the bonded safety shield, and 19" without. Some chassis are equipped with a 7-transistor *Son-R* remote control receiver which operates at the command of mechanically-produced supersonic signals.

Circuits common to all chassis in the line include a BU8 keyed AGC-sync separator, cathode-coupled horizontal multivibrator with dual-diode horizontal AFC, combined vertical multivibrator and output circuit, crystal-diode video




detector, 'DT6 quadrature-grid sound detector, and circuit-breaker protection.

Three 19" chassis—all using a 114° CRT, the 19XP4—form the "low end" of the line. The smallest of these, the 15G1B, is a 600-ma series-filament version using two silicon rectifiers in a half-wave doubler circuit. The 15E1 and 15F1 are transformer-powered, 5U4-equipped units used in the higher-priced portables and 19" consoles. Remote control is an added feature of the 15F1 only. Two video IF stages and a 6AW8A video amplifier develop an output signal of 80 or 95 volts peak to peak (depending on chassis). A single printed board carries all of the signal circuits.



"Leader" models in the 23" *Presidential* line use a 92° picture tube, the 23AHP4, and either the 16-tube 20K7 or the 18-tube 20L7. The audio circuits mark the difference between the two groups. The 20K7 uses a single 6AS5 for the output, while the 20L7 employs a three-tube stereo circuit with a pair of EL86/6CW5's. Both chassis have a power transformer and 5U4 rectifier, a 6DE7 dual triode in the vertical circuit, and a three-stage video IF section which helps raise the signal output of the video amplifier to 125 volts. Two printed boards contain most of the wiring in this series.

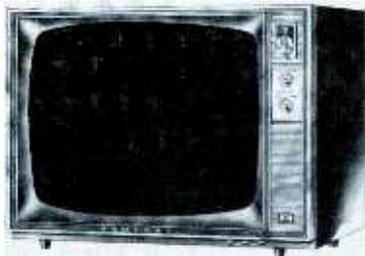


The big *Imperial* series uses the 20A7, 20B7, or 20C7 chassis with a 110° picture tube—either a 23CP4, -GP4, or -HP4. The basic 20A7 layout contains one more tube than the 20K7, using a 6FM5 pentode and half of a 6CG7 to replace the 6DE7 in the vertical circuit. The remaining half of the 6CG7 is put to use as an added sync phase inverter. The 20B7 chassis is equipped for remote control, while the 20C7 goes "all out" and includes a stereo amplifier with two EL86/6CW5 output tubes. A phono and a three-tube AM or seven-tube AM-FM tuner are also included in the 20C7 series.

## DuMont

New models introduced in DuMont's 1961 line, all members of the 700 series, use Chassis 120602 through 120605. The 90° picture tube is the same for all versions—a 23YP4 with bonded shield. The 120603 and -5 chassis differ from the others in the sound circuits, omitting the output stage and using a separate stereo amplifier with two pairs of push-pull EL84/6BQ5's. These are found in combination models that also have an AM-FM tuner, a phono, and a supersonic remote control device using an electronically-generated signal—the same system used in the '60 line. All versions are equipped with *DuMatic* power tuning and *Perma-Tune* "do-it-yourself" preset fine-tuning adjustment, also carried over into all the new chassis.

Other than the differences noted above, the chassis are identical. Conventionally-wired and transformer-powered, these units have their power supplies mounted on a separate subchassis. Three video IF stages are employed ahead of the single 12BY7A video amplifier. In the sound circuits, a 6T8 functions as a ratio detector, AF amplifier, and AGC clamper. (This was conventional just a few years ago, but today it's a rarity).

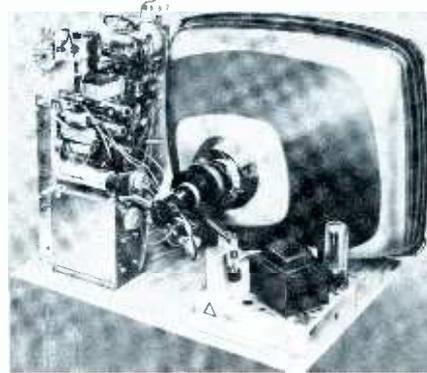Another old standby, a 6AL5, is used as an AFC detector to control the catho-



de-coupled multivibrator in the horizontal sweep circuit. Vertical sweep comes from a 6EM7 dual triode in a combined multivibrator and output circuit. One-half of a 6BU8 provides amplified AGC in a non-keyed arrangement; the other half serves as the only sync stage in the receiver.

## Emerson

The 1961 Emerson line centers around one basic chassis design even though 10 chassis numbers prevail. The predominant differences are in the choice of tuner, and in circuit variations to permit the use of additional radio, amplifier, and remote control chassis. The remote system, a supersonic version carried over from the '60 line, operates by means of an electronically-produced signal. Chassis 120530C, -552E, -553F, -554E, -556F, and -557E all use a 114° 19AXP4 without bonded shield, while the 120-549C, -550D, and -551C utilize a 110° 23CP4 with shield. The horizontal circuit comes in for considerable revision in the 114° series, because of the increased deflection-current demand. Output-tube screen voltage is increased 10 volts, the flyback and yoke are changed, boost filters are increased in value, and higher values of anti-ringing components are required.


All of the chassis have a single printed



board that contains most of the circuits except for the power supply, audio output, and sweep output stages. The complement of 17 tubes includes a 5U4 in the transformer-type power supply. The audio output tube, a 6CU5, doubles as a voltage divider in the B+ circuit. A 6AS8 pentode-diode, serving as a third video IF amplifier and video detector, feeds the pentode section of a 6AW8A, which amplifies the video signal to 115 volts peak to peak. These chassis provide a LOCAL-DISTANCE control for adjustment of the voltage divider that furnishes delayed AGC bias to the tuner from the 6BU8 AGC keyer. Horizontal sweep is controlled by a conventional multivibrator with dual-selenium-diode AFC, and vertical sweep comes from a 6AW8A triode section and a 6EM5 pentode in the familiar combined multivibrator-output circuit.
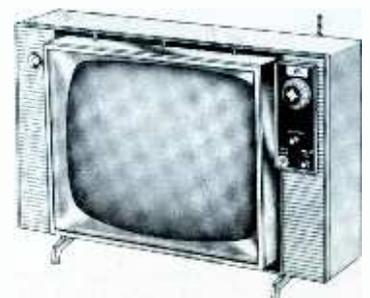
## General Electric


As in previous years, G-E's line is made up of two basic chassis; for '61, they're numbered M6 and U5. These are refined versions of the 1960 designs, following the same structural pattern. This year marks G-E's entry into the combination field, so minor circuit modifications have been made to accommodate additional radio tuners, amplifiers, and remote control units. Remote-equipped models will use either an improved version of 1960's four-button RF system, or a new, three-tube supersonic type that uses two transistors to generate the signal. Some models are equipped with "do-it-yourself" preset fine tuning, which has been termed *Automatic Fine Tuning* by G-E. Picture-tube options include the 17DLP4, 19ZP4, 21ESP4, and 23KP4—all 110° or 114° designs without a bonded shield. A three-stage video IF, a horizontal multivibrator controlled by dual-diode AFC, and a 6AU6 sound IF stage feeding a 6FM8 or 6T8 ratio




detector-AF amplifier are among the major features common to both chassis.

The smaller M6 chassis, used in the *Designer* series, incorporates a power transformer and 5U4 rectifier in its power supply. The 135-volt "low B+" potential is derived from the 6CU5 audio output stage. AGC bias is obtained by blending and filtering a combination of two signals—the output of the video detector and the grid signal of the triode-type sync separator. The single video amplifier is the pentode section of a 6CX8, and the combined vertical multi-vibrator and output circuit uses a 6DN7 dual triode.

"Big brother" U5 offers two stages of

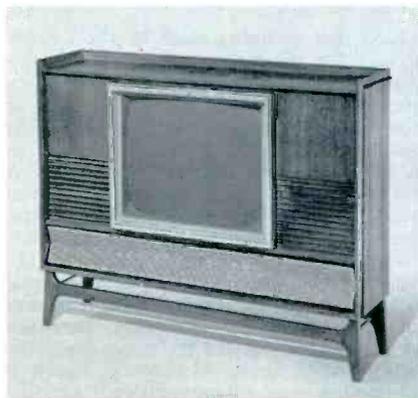

video amplification, a 6AW8 pentode section and a 6AQ5, designed to furnish a 160-volt peak-to-peak drive signal to the grid of the CRT. (High voltage in this chassis, by the way, is 18 kv.) AGC is developed by the keyed triode section of the 6AW8; the RF branch of the AGC line is clamped by an extra diode in the 6T8 ratio-detector tube. A new high-gain 6EW6 pentode appears in the final IF stage. The audio output tube is a 6BQ5, with the cathode circuit returned to ground instead of acting as a low B+ source. A 6DN7 vertical sweep tube is found in the U5, as well as in the M6; this time, however, it is wired as a blocking oscillator for feeding an independent output stage. Instead of teaming a 5U4 with its power transformer, the larger G-E chassis uses a pair of germanium rectifiers in a full-wave voltage-doubler circuit (see schematic). This reflects a growing trend in many '61 lines.

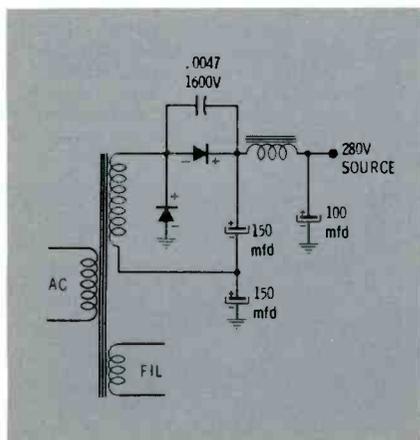


### Hoffman

Five chassis, numbered 355 through 359, constitute Hoffman's 1961 line. Bonded-shield 110° picture tubes (19-AFP4 or 23CP4) are used in all models.

The transformer-type power supply includes a 5U4 tube in every chassis except the 355, which uses silicon rectifiers. Hand-wired construction is used throughout the line. Covering a range from portables to combinations, the various chassis carry many minor variations. Two super-sonic remote control units are used—a two-button system producing mechanically-generated signals, and a four-button unit using a transistorized oscillator to generate four different signal frequencies.

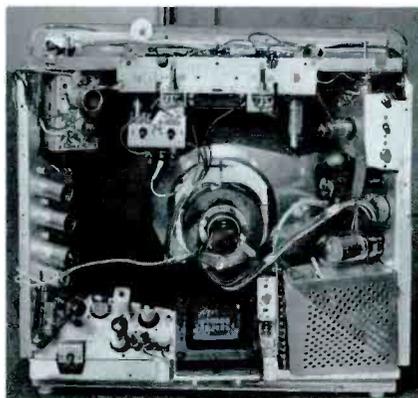
A 6AW8A serves as the video output and keyed AGC circuits in all chassis. The 6DT6 quadrature detector is unusual in that an AM REJECTION control is con-




nected in the cathode circuit. Three-stage video IF strips, horizontal multivibrators, and 6BQ5-equipped audio output stages are common to the full line.

Physical layout is the prime difference between the *Nine-teen* series (Chassis 355) and the rest of the line. Employed in 19" sets, this chassis is shaped like a picture frame mounted vertically inside the cabinet, with circuits on all four sides. Electrically, this 16-tube chassis is set apart from all other Hoffmans by the above-mentioned use of silicon B+ rectifiers, and by the employment of a 6DE7 in a combined vertical multi-vibrator and output circuit.

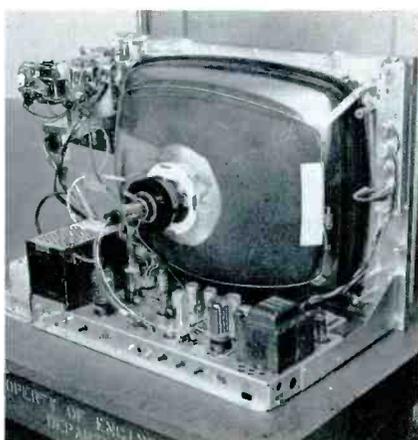Chassis 356, 357, 358, and 359, comprising the *Continental* series, are all basically the same. These 18-tube units offer a feature seldom seen these days—a 6CG7 in a cathode-coupled vertical multivibrator feeding an independent 6DT5 output stage. "Do-it-yourself" fine tuning is available in all members of



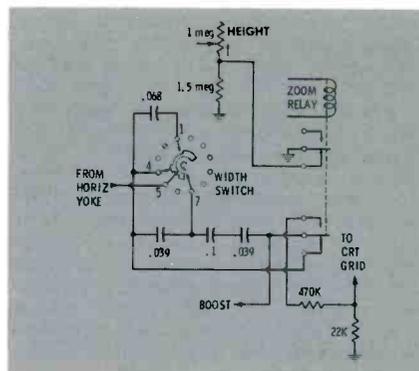this series except the 356. Chassis 357 and 359 carry over an interesting feature from the 1960 line—a *Lite Scope* circuit which varies the resistance in the brightness-control circuit in direct proportion to changes in ambient light. In addition,



the 359 chassis has a ZOOM or PICTURE MAGNIFIER circuit that increases the size of the image appearing on the screen. This is accomplished by increasing the amplitude of the vertical drive signal and adding two capacitors in series with the width-switch connection to boost. Also, a slight positive voltage is applied to the CRT control grid to increase beam current (see schematic).

### Magnavox


Magnavox's '61 TV line is made up of two new chassis and a revamped version of the existing 30 Series. The new 33 and 34 Series form the middle and low ends of the line, respectively, while the revised group of chassis (30-20 through 30-24) retains its position at the top. Picture tubes come in all available sizes from 19" through 27", and employ deflection angles of 90° to 114°. As in previous years, a wide range of models are developed by combining each of these basic TV chassis with various additional equipment (such as AM-FM tuners, stereo amplifiers, and phonos) in numerous arrangements.

All these chassis are transformer-powered (with 5U4 rectifier), conventionally wired, and mounted vertically. The single video output stage is a 6EB8 pentode section in the two newer series, or a 12BY7 in the 30 Series. Sound detection is performed by a 6DT6 in all cases, and the audio output tube is put to use as a B+ voltage divider. In some versions which use an external audio amplifier chassis, the set's own output tube is relieved of its duties as an amplifier; but it is retained in the chassis so it can continue its voltage-dividing job. Keyed AGC and two triode



sync stages are used throughout. While the 30 Series stays with the "old reliable" 6AU6 in the AGC function, the 33 and 34 Series have changed over to the pentode section of a 6GH8.

The 33 and 34 Series chassis are

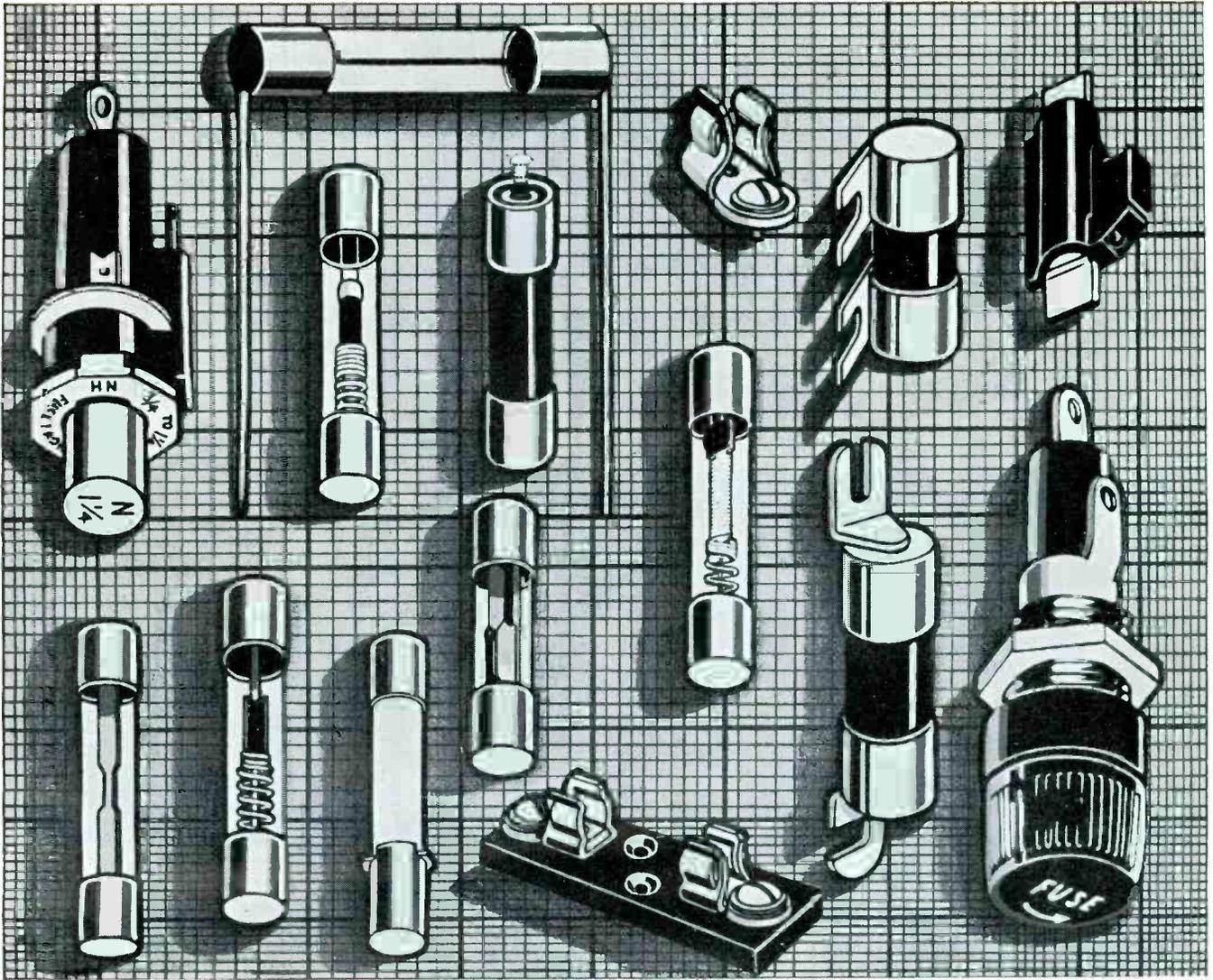

# BUSS fuses can help protect *your profits and your reputation for service*

You get double protection when you install BUSS fuses.

**First**, BUSS fuses are designed and manufactured to give maximum electrical protection.

But it doesn't stop there.

Every BUSS fuse is carefully tested in a sensitive electronic device that automatically rejects any fuse not correctly calibrated, properly constructed and right in all physical dimensions.

This is your assurance that BUSS fuses will operate as intended.

**Second**, BUSS fuses help protect your reputation for quality service. A fuse that opens prematurely causes a needless shutdown. Likewise, one that doesn't function properly may cause other components to burn out or be damaged. In either case, it's an annoying headache for your customer and it may cost you his confidence. More often than not, he will blame you for his trouble.

With dependable BUSS fuses, you need have no worries that faulty fuses will threaten your profits or your reputation. That's why it makes good sense to install BUSS fuses.

*For more information on BUSS and FUSETRON small dimension fuses and fuseholders . . . Write for bulletin SFB.*

**BUSSMANN MFG. DIVISION**

McGraw-Edison Co.

University at Jefferson, St. Louis 7, Mo.

1160

**BUSS FUSES ARE MADE TO PROTECT -  
NOT TO BLOW NEEDLESSLY**



BUSS MAKES A COMPLETE LINE OF FUSES FOR HOME, FARM, COMMERCIAL, ELECTRONIC, ELECTRICAL, AUTOMOTIVE AND INDUSTRIAL USE.

quite similar to each other, except for the following major points: The vertical circuit of the 33 Series uses a 6CM7 as a blocking oscillator and separate output stage, while the 34 Series has the familiar combined multivibrator and output circuit including a 6BF6 and a 6EM5. The diode sections of the 6BF6 are utilized as clampers for the AGC and horizontal-blanking circuits—another special feature of the 34 Series.

The 30-20 to -24 series chassis have many minor variations in control-panel layout and cabling arrangements, in order to accommodate different combinations of accessory equipment found in combination TV-radio-phono and similar units. The circuits are very much like those of the 34 Series, but individual tubes replace some of the dual-section types, thus accounting for the higher number of tubes encountered in the 30




Series. Chassis coded 30-20, -22, and -23 all use the 6DG6GT "audio output" tube only as a voltage divider, and feed the output of the sound detector to an external amplifier. In the 30-21 and -24 Series, a 6AT6 stage of audio amplification is added to drive a self-contained output circuit.
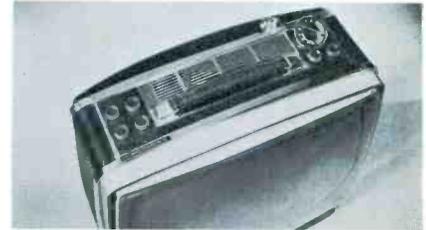
## Motorola

The most interesting innovation in Motorola's new line is the 19" transistorized portable. However, there are also eight other basic chassis that cover the field from 14" portables through 23" combinations. In all, 10 different CRT's are employed, with deflection angles ranging from 90° to 114°. Motorola favors the bonded safety shield for all the 19" and 23" types, excluding the one in the transistor set.

Although the different chassis groups vary greatly in tube types used, as well as in wiring methods and physical arrangements, the tubed chassis are consistent enough in basic design so that we can classify them into three broad groups. Furthermore, some design features are common to every chassis in this line. All have three stages of video IF and a single video output stage. With the exception of the TS-574 chassis, all have a single sound IF, a 'DT6 sound detector, and a simple one-stage audio output circuit. Keyed AGC, noise-immune sync, and the combined vertical multivibrator-output circuit are also used throughout, although the exact design of these circuits does vary a great deal.



Chassis TS-432 is used in the *Astronaut* transistorized portable set. Since there are far too many unique features of this chassis to allow adequate coverage in this review, we'll concentrate on the points we think you'll be most interested in knowing. All told, there are 25 transistors—22 PNP and 3 NPN types. The only tubes in the set are the CRT and a 1S2A high-voltage rectifier. (The latter delivers a 15-kv output.) In addition, there's an assortment of 12 semiconductor diodes and rectifiers serving various functions. Some of their applications are truly unique; for example, one of the diodes replaces a conventional integrator network, while others rectify pulse voltages from the flyback to obtain higher B+ voltages for the video output stage and the picture tube. The main power supply is a full-wave type with a regulated output of 19.5 volts; besides acting as a B+ source, it also charges the battery when the switch is in the off position and the TV is plugged into the AC line.

One of the very few 14" portables still available on the American market is the set using Chassis TS-434, carried over from last year's line. A similar chassis, the latest revision of the TS-430, is found in 17", 90° portables of the type shown. Both series are 16-tube, conventionally-wired chassis with 600-ma series-string tubes. Here's a brief run-down of differences between them: The 430 uses a pair of selenium rectifiers in a half-wave doubler circuit, while the 434 uses a single silicon rectifier to supply B+ voltage. The horizontal AFC stage in the 17" chassis takes in both diode sections of a 6CN7, whereas a dual selenium diode is found in the 14" version. Three triodes in the 430 perform the respective jobs of keyed AGC tube, noise limiter, and sync separator; on the

**FIND TUBE TROUBLES OTHERS MISS!**

**A New Dynamic Approach**

Check over 1300 tubes for

- Cathode Emission
- Grid Emission
- Leakage
- Shorts
- Gas

## SENCORE "MIGHTY MITE" TUBE CHECKER


Answers the needs of the fast moving, profit minded serviceman who hates time consuming call backs. A "mite" to carry but a whale of a performer that spots bad tubes missed by large mutual conductance testers.

New unique "stethoscope" approach tests for grid emission and leakage as high as 100 megohms, yet checks cathode current at operating levels. Special short test checks for shorts between all elements. The MIGHTY MITE will test every radio and TV tube that you encounter (over 1300!) plus picture tubes, foreign, five star and auto radio tubes (without damage). As easy to set up as a "speedy tester" from easy to follow tube booklet. New tube charts free of charge.

AND check these added Sencore servicing features: • Meter glows in dark for easy reading behind TV set • Stainless steel mirror in cover for TV adjustments • Rugged, all steel carrying case and easy grip handle • Smallest complete tester made.

Model TC109.....DEALER NET **59<sup>50</sup>**

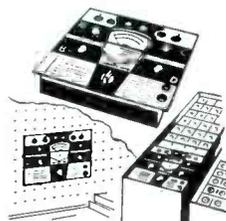Ask your distributor for the "MIGHTY MITE" with the mirror in the cover



Use it everyday in every way. Especially designed so you can transfer inner chassis to your tube caddy, bench or counter. Only 9" x 8" x 2 1/2".


ALL PARTS

**SENCORE**

MADE IN AMERICA


**SENCORE**

ADDISON 2, ILLINOIS

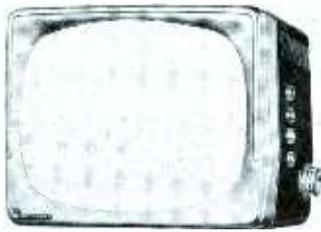

other hand, the 434 uses a single 3BU8 to serve all these functions.


Sharing the next higher step on the ladder are Chassis TS-433 and -435—used in 17" and 19" sets, respectively. Both series feature slim portable models with 110° picture tubes, and the 435 finds further use in the *Harbinger* line of 19" consoles and table models. The RTS-435 has a *Golden Satellite* two-function remote control—a supersonic system using a mechanically-generated signal. One all-inclusive "plug-in" printed board with color-coded conductors characterizes these 15-tube, series-filament chassis. A couple of familiar features in this design are a half-wave doubler (with two silicon rectifiers) and a 3BU8 keyed AGC-sync separator stage. Either an 8EB8 or an improved similar type, the 8GN8, serves

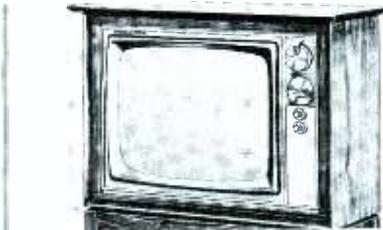

as a video output tube and as the first section of the vertical multivibrator. A plug-in dual selenium diode is used as a phase detector to control a 5GH8 sine-wave horizontal oscillator. Modules appear in the sweep circuits, and printed component combinations are found in many applications.

"Full-size" (21" and 23") sets use four distinct chassis types—the TS-567 in 21" receivers, the TS-568 in most 23" units, the VTS-569 in the 23" *Drexel* "fine-furniture" line, and finally the TS-574 in stereo combination sets.

The lowest-priced chassis of the group (the 567) has a 15-tube series filament string, while all others have a transformer-type power supply with 5U4 rectifier. (The 569 adds a supplementary 5Y3.) A couple of features common to all 23" sets, but not shared by the 567, are a new high-transconductance 6GK6 pentode in the video output circuit, and a sync phase-inverter stage following the 3BU8 sync separator. In the horizontal sweep section, the features follow a different lineup; the 568 and 574 employ a multivibrator circuit, while the 567 and 569 both have the newer sine-wave type of oscillator. All chassis use 90° or 92° picture tubes except the 569, which drives a 110° 23GP4. To supply the increased sweep power demanded by the

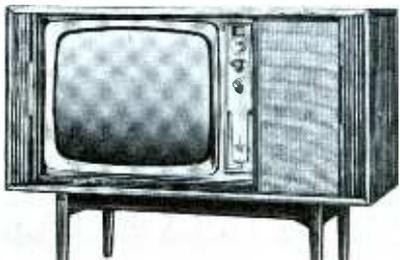

greater deflection angle, the 569 employs a 6EZ5 vertical output tube in place of the 5- or 6AQ5 found in other chassis.

Modules and component combinations find their way into all but the 569. In the 574 only, the audio output circuit is omitted, and a separate stereo amplifier serves as the audio section.


## Olympic

This year's selection of Olympic models leans heavily toward combination sets, with such diversified extras as AM radios, standard AM-FM tuners, "dual-channel" AM-FM tuners (for receiving stereo simulcast transmissions), stereo phonos, and remote control. There's a wide variety of picture-tube sizes, ranging from 17" to 24".

The line is a long one, comprising 14

chassis (not counting UHF versions); however, the various designs all have an underlying family resemblance. All but the KF chassis have two video IF stages and use the audio output tube as a B+ voltage divider; the KF chassis, on the other hand, has three IF's, and its EL84/6BQ5 audio output tube is not tied in with the low B+ network. Most chassis use the new 6EJ7/EF184 pentode—a high-gm, frame-grid tube—in the second IF spot. Quadrature FM detection, a cathode-coupled horizontal multivibrator with dual-diode AFC, and a combined vertical multivibrator-output circuit are common to all designs.

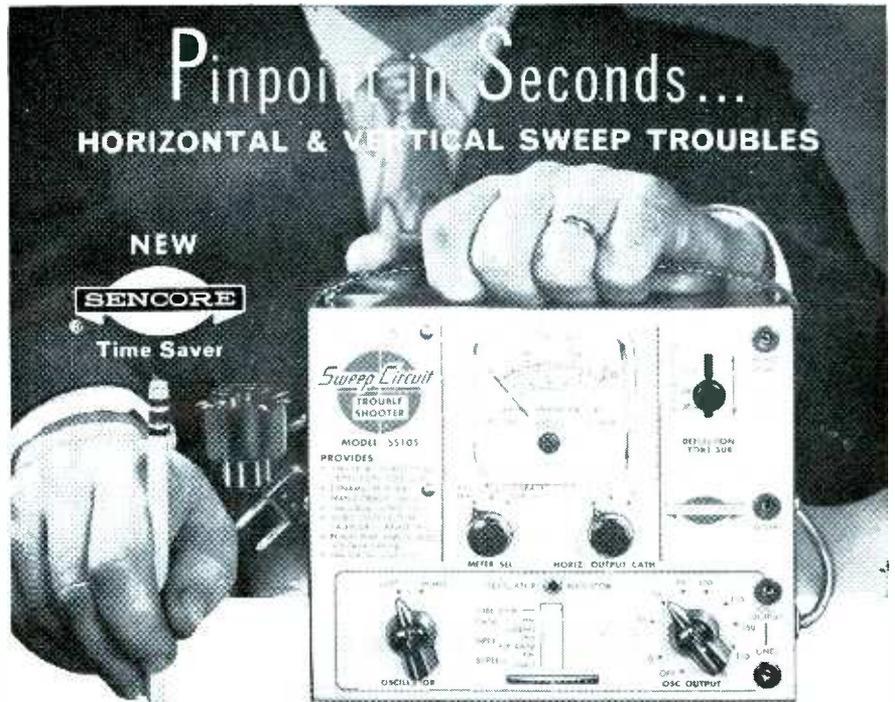Chassis KU is the smallest of the line. It's an 11-tube, series-filament version with two silicon rectifiers wired in a conventional half-wave doubler circuit. AGC voltage is obtained by filtering the output of the video detector, and the



The missing link in TV service...

## SENCORE SS105 SWEEP CIRCUIT TROUBLE SHOOTER



HORIZ. OSC.	VERT. OSC.
HORIZ. O.P. STAGE	VERT. O.P. STAGE
HORIZ. FLYBACK XFORMER	VERT. O.P. XFORMER
HORIZ. DEFLEC. YOKE	VERT. DEFLEC. YOKE

**IT'S A ... UNIVERSAL HORIZONTAL OSCILLATOR.** For direct substitution. No wires to disconnect in most cases. Traces trouble right down to the defective component. Variable output from 0-200 volts, peak-to-peak. Oscillator will sync to TV sync signal giving check on sync circuits.

**HORIZONTAL OUTPUT CATHODE CURRENT CHECKER.** A proven method that quickly checks the condition of the horizontal output tube and associated components. Adaptor socket prevents breaking wires. Easily replaceable Roll Chart gives all necessary pin, current and voltage data. New Roll Charts are Free.

**UNIVERSAL DEFLECTION YOKE.** A new, simple way to determine yoke failure accurately—without removing yoke from picture tube. Merely disconnect one yoke lead and substitute. If high voltage (also bright vertical line) is restored, TV yoke is defective.

**DYNAMIC FLYBACK TRANSFORMER CHECKER.** Merely flip switch to "Flyback Check" and meter will indicate condition of flyback transformer, in degrees of horizontal deflection. Extremely sensitive and accurate; even shows up one shorted turn on flyback.

**VOLTMETER.** For testing bootstrap, screen and other voltages. Direct-reading voltmeter, 0-1000 volts.

**UNIVERSAL VERTICAL OSCILLATOR.** Checks oscillator, output transformer and yoke. Merely touch lead to component and check picture on screen.

**SS105 is completely self-contained, nothing else is needed. New Improved Circuit... DEALER NET 42<sup>95</sup>**


ALL PARTS  
SENCORE  
MADE IN AMERICA

SENCORE  
ADDISON 2, ILLINOIS



only sync stage is a triode section of a 5B8 acting as a separator.

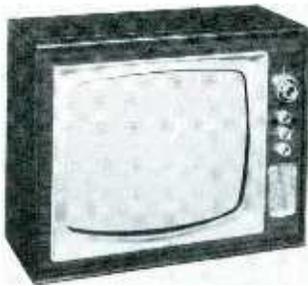The remaining chassis can be sorted into two groups, depending on deflection angle and type of low-voltage rectifier used. (All are transformer-powered.) Chassis JV, KRZ, KW, KV, and KZ are 110° or 114° units with a pair of silicon



diodes in a full-wave voltage-doubler configuration. On the other hand, the KA, KB, KC, KD, KE, KRB, and KRD are 90° chassis using a 5U4.

Olympic has joined the roster of manufacturers using a 6BU8 as an AGC keying tube and sync separator; this feature appears in all transformer-type


chassis except the JV, KA, and KV. The exceptions use the filtered video-detector output as AGC bias and employ the triode section of a 6AV6 for sync separation. (The diode sections of the 6AV6 are unused.) These sets also employ the pentode section of a 6AW8 in the video output stage, whereas the 6BU8-equipped chassis have changed over to a higher-gain 6GN8 or 6EB8 video tube. The sound section in the KC, KD, KE, and KW offers a 3D feature—a system of tone compensation achieved by degenerative feedback.

## Packard-Bell

To gain a comprehensive understanding of Packard-Bell's 1961 line, three groups of chassis need be considered—although there are at least two variations of each chassis. The line ranges all the way from 17" portables, through an assortment of 19" and 21" types, to 23" consoles and combinations. Neither 19" nor 23" picture tubes are equipped with bonded safety shields. Optional extras include AM-FM tuners capable of receiving simulcast transmissions, stereo amplifiers, and even connections for future installation of reverberation units. Wired remote controls are currently offered, with wireless units scheduled for introduction later in the year.

All chassis are conventionally wired. Among their standard features are three video IF's, a cathode-coupled horizontal multivibrator, and a combined vertical multivibrator and output circuit.

Only a handful of '61 designs use 450-ma series-string tubes, but Packard-Bell's *Custom* series (Chassis V8-8) is one of these. On the other hand, the *Compact* series (Chassis V8-7 and -9) have 600-ma strings. Both groups have a complement of 15 tubes, along with a half-wave doubler power supply using silicon rectifiers. Other design features common to both series are individual horizontal AFC diodes instead of a potted dual assembly; 'DT6 audio detection; an 'AS8 pentode-diode serving as a third IF amplifier and

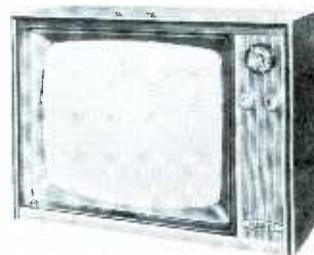

video detector; AGC derived from the detector output; and a single 'EA8 triode-pentode constituting the entire video and sync section.

There are three *Decorator* groups utilizing versions of the 88 Series chassis. All are equipped with a power transformer and 5U4. The basic 17-tube 88-8 chassis employs a crystal-diode video detector, a 6EB8 as a video output and noise inverter, and a dual-diode unit for horizontal AFC; it also differs from the smaller chassis series in that keyed AGC and a 6BN8 ratio detector-AF amplifier circuit are added. The 88-10 is the same as the 88-8 except for circuit variations made necessary by the addition of wired remote control. The 88-11 has a different audio circuit that uses a 6AL5 as a ratio detector and feeds the demodulated signal to an accessory AM-FM stereo

## Transistor Radio Servicing CAN be Highly Profitable



The ONLY Complete Transistor Radio Service Lab  
Everything you need for less than \$50

### Check Transistors, Diodes, Rectifiers . . .



#### SCENCORE TRC4 TRANSISTOR CHECKER

Accurately checks all transistors in hearing aids, radios and power transistors in auto radios. Tests for opens, shorts, leakage, current gain. Measures forward-reverse current ratio on all crystal diodes. Measures forward and reverse currents on selenium rectifiers. With set-up chart for accurate checking of each transistor. Size, 5x4½x2½". With batteries. DEALER NET..... 19<sup>95</sup>



### Replace Batteries During Repair . . .



#### SCENCORE PS103 BATTERY ELIMINATOR

All-new "Transi-Pak," twin to TRC4 Checker above. Provides variable DC voltage to 24 volts; 1.5-volt biasing tap (a "must" for servicing Philco and Sylvania radios). Metered current output, to 100 ma. Handles 200-ma peaks. Two 200-mfd electrolytics provide proper filtering and low output impedance. No hum or feedback problems. Ideal for alignment using station signal; adjust IF slugs for max. current, also ideal for charging nickel-cadmium batteries. Size, 5x4½x2½". 19<sup>95</sup> DEALER NET.....



### Find Defective Stage in a Minute . . .



#### SCENCORE HG104 HARMONIC GENERATOR

New signal generator designed primarily for fast signal-tracing of transistor radio circuits. No need to unsolder all transistors. Provides RF, IF and audio signals *simultaneously*, drastically cutting service time. Traces from speaker to antenna. Clear 1000 cycle note signal is heard in speaker from all good stages. Signal weakens or stops at defective stage. Equally as effective for testing TV, hi-fi and other audio circuits also. Size, 3½x4½x1¾". 9<sup>95</sup> With batteries. DEALER NET.....



Turn page for other

SCENCORE

Time Savers


ALL PARTS

SCENCORE

MADE IN AMERICA


SCENCORE

ADDISON 2, ILLINOIS

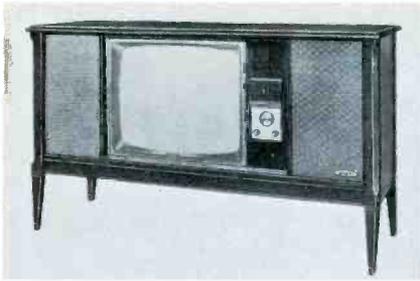

chassis. The latter, in turn, feeds the signal back to a three-tube stereo output circuit on the TV chassis.

The 98D10 and 98D11 *Signature* chassis are 20-tube, transformer-powered units using a 5V3 rectifier. A 6AM8 serves as third IF and video detector; a two-stage video amplifier (using a 6CB6 and 6CX8 pentode section) includes a PICTURE FIDELITY control to permit varying its high-frequency response. Keyed AGC and noise inversion circuits are again employed, but this time they use a 6AN8 pentode section and half of a 12AX7. An additional stage of sync amplification puts the triode section of the 6AN8 to use, and two diodes of a 6BN8 provide a horizontal AFC. Sound circuits vary from

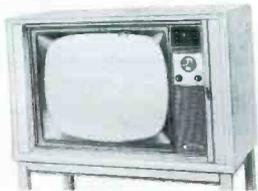

the 88 Series in that the remaining half of the 12AX7 noise inverter serves as an additional IF stage. Wired remote controls are included in both versions. The AF amplifier and audio output circuits of the 98D11 feed only an auxiliary speaker in the chairside remote-control box, while the output from the TV cabinet itself comes from an added stereo amplifier with push-pull pairs of EL84/6BQ5 output stages.

### Philco


A new supersonic remote control, using mechanically-generated signals, can be field-installed in some '61 Philco sets by service dealers—or it may be installed at the factory. The line includes nine different chassis, with one basic design for compact portables and another for the larger models. A variety of 17" to 23" picture tubes are used; only one of these, the 23CP4, has a bonded shield. Minor circuit variations provide for adding an AM-FM tuner, phono, or reverberation unit.

A new 6HJ8 is used as a third IF and video detector tube, except in the 11H25 chassis (which uses a 6AM8A). The audio detector circuit is a carry-over of Philco's special quadrature type utilizing a 'CS6 tube. Triode-type noise inverters and sync separators are used throughout; so is the combined vertical multivibrator and output circuit, which includes a tube of the 'DR7 type. Dual selenium diodes in the horizontal AFC circuit control a cathode-coupled multivibrator in all chassis.

The 11H25 and 11J27 chassis, found in compact 19" portables, contain two printed boards and a 15-tube, 450-ma series filament circuit. The usual half-wave voltage doubler, with two silicon




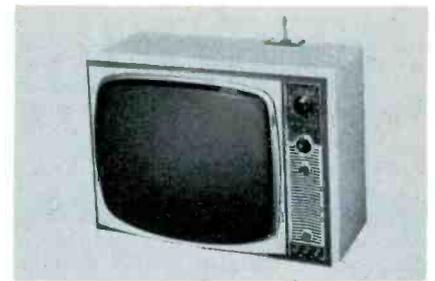rectifiers, is also used. The AGC circuit in this series is reminiscent of a design which gained some popularity in the early '50s; the contrast control provides a variable voltage for AGC to the IF's. Optional *New-Matic II* remote control is available for use with these chassis. This is an air-operated unit with a



hollow, flexible tube connecting the chassis to a control plunger.

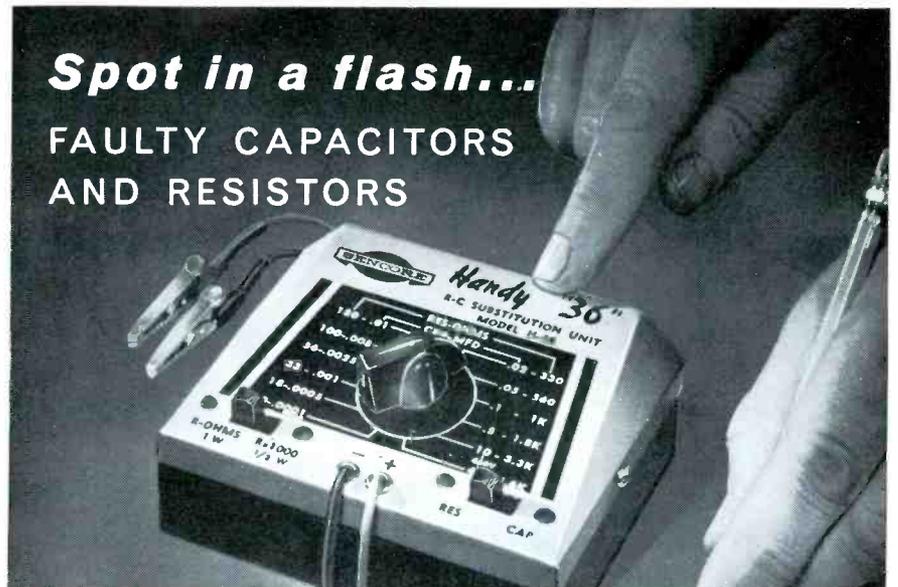The basis for the *Mark II Cool-Chassis* line is the 16-tube 11N51 and its variations, the 11N51A, -52, -52A, -53, -54, and -55. These units drive a 23CP4 CRT and have provisions for remote control and various other accessories. Trans-



## Spot in a flash... FAULTY CAPACITORS AND RESISTORS

A complete range of capacitors  
and resistors at your command.

### SENCORE HANDY 36 SUBSTITUTION UNIT


Serviceman... Engineer... Experimentor... here's a unit that really saves you time. The Handy 36 provides the 36 most often needed capacitors and resistors for fast, on the spot substitution. The 12 position, 3 wafer switch individually selects one of the 36 components. You simply dial the value you want to the exact or closest reading. Substitution is still the only time tested method for determining whether or not a component is faulty while operating in circuit.

Eliminate time wasted in hunting for parts to use in testing. Say goodbye to the soldering mess created by substituting individual components. Put an end to the twisted wires and messy parts you've tossed in parts drawers.

The Handy 36 is simple to use. If a component is suspected of being shorted, open one end and substitute the Handy 36. Or, merely parallel any capacitor or resistor you think is open.

Model H36.....DEALER NET 1275

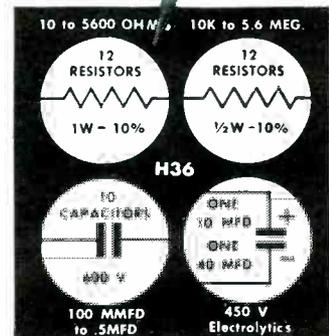Ask any parts distributor for the "Handy 36", accept no substitute.



The Handy 36, with new improved circuitry, pays for itself in the first month by saving you those valuable minutes. The parts alone in the H36 would cost you more than the completed unit.



# SENCORE

ADDISON 2, ILLINOIS

former-powered, they use a pair of silicon rectifiers in a full-wave doubler circuit. A 6BY8 is employed in a keyed and clamped AGC circuit—a feature seldom seen these days.

### RCA Victor

Six styles of picture tubes—ranging in size from 17" to 23", and having deflection angles of 90°, 110°, and 114°—are used in the five chassis series of RCA's 1961 lineup. All 23" versions use a 23EP4 with bonded shield, while the only 19" to have this feature is the 19AFP4 used with the KCS134 chassis. A wide variety of additional items such as AM-FM tuners, two- or three-section stereo amplifiers, and phonos, are used in conjunction with various chassis. In addition, there is a choice of two remote

controls. Both are supersonic systems; however, the control signals are mechanically-generated in the two-button version, and electronically-produced in the three-button type.


All chassis are transformer-powered and contain two printed boards. The IF strip includes a new 6GM6 pentode (with semiremote cutoff and high transconductance) in the second stage, and continues the use of a sharp-cutoff, high-gm 6EW6 in the third stage. Other circuits carried over into all the new chassis are a 6EB8 pentode section in a one-stage video amplifier, and also a 6DT6 quadrature detector feeding a 6BQ5 audio output stage. The KCS131 and -2 use a 5U4 low-voltage rectifier; all others are equipped with a pair of silicon rectifiers in a full-wave doubler circuit. A new concept in RF-tube design, the



6CW4 Navistor, is introduced in some models.


The KCS130 chassis used in 17", 110° thin-line portables, and the KCS134 employed in 19", 114° veri-thin table and "totable" models, have essentially the same circuits, but differ in layout. The separator is a 6EB8 triode section, and a 6EA8 operates as a sync amplifier and keyed AGC tube. A combined vertical multivibrator-output circuit, conventional in design, makes use of a 6DR7. The horizontal circuit is the same type of modified *Synchroguide* system as last year's RCA design—a blocking oscillator with a transformer in the grid-cathode circuit, preceded by a triode AFC stage.

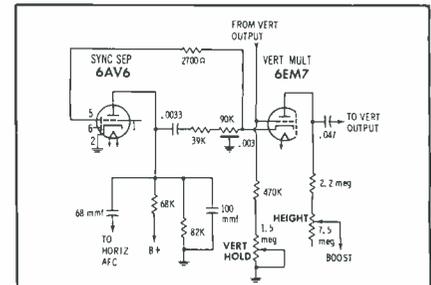"Full-size" table models, consoles, and combinations are divided into 21", 90° types (using Chassis KCS131) and 23", 110° types (outfitted with Chassis



KCS132). These two series, in addition to the KCS133 used in 19", 114° portables, are electrically very similar to each other except for differences in certain sweep components and in the low-voltage rectifiers. In these 18-tube chassis, the 6DT6 tube has been adapted to the keyed AGC function—marking the first time it has ever been used as anything but a sound detector. Other notable features are AGC clamping, noise inversion (by the triode section of the 6EB8), and the use of a 6AV6 triode as a sync separator. A dual-diode phase detector, preceding the triode AFC stage, increases the stability of the modified *Synchroguide* horizontal sweep circuit.

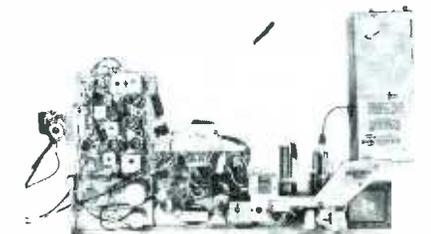An unusual feature of the combined vertical multivibrator and output circuit (see schematic) is that negative sync pulses are applied to the cathode of the first stage—which, in turn, is connected to the plate of a diode section in the 6AV6 sync separator tube. The diode is normally nonconducting, so the vertical stage has a high impedance in its cathode



**Substitutes FOR ALL ELECTROLYTICS**  
*without Arc or Spark!*

Complete range of electrolytics—4 to 350 MFD. Connect in any circuit from 2 to 450 V.

### SENCORE ES102

### ELECTRO-SUB

- What more can you ask for? The Electro-Sub not only saves time for any serviceman, engineer or experimenter but insures maximum protection too. Simply select the electrolytic, connect test leads and push surge protector switch.
- How many times have you reached for an electrolytic for substitution to find that value or voltage rating missing?
- How many times have you wanted a value just a little higher to see if you could knock out annoying hum?
- How many times have you had sets that blow fuses, fuse resistors or rectifiers and you did not check all electrolytics because it was too time consuming?
- Have you ever healed a suspected electrolytic by "bridging" it and made a call back that same week on the same trouble?
- Have you ever grabbed an electrolytic that you thought was discharged or watched a customer's dismay as you discharge one?
- Well, here is your answer . . . from the smallest electrolytics used in transistor radios to the largest used in costly Hi-Fi amplifiers . . . complete, safe substitution.

ES102 . . . DEALER NET **15<sup>95</sup>**

**AUTOMATIC SURGE PROTECTOR**  
for you and the circuit

DISCHARGE CHARGE SUBSTITUTE

It does all this by merely pushing surge protector switch. Move it as fast as you want; it is smooth and returns automatically.

You'd pay more for just the parts than you would for the complete ES102 . . . amazed? See your parts distributor.



**SENCORE**

ADDISON 2, ILLINOIS

circuit. However, when a sync pulse arrives, the vertical-sweep tube immediately begins conducting, and its cathode voltage rises. This causes the diode to conduct, thereby providing a low-impedance shunt across the cathode circuit so that the multivibrator tube can draw sufficient current for rapid discharge of the vertical sawtooth-forming network.

### Setchell-Carlson


Again in 1961, Setchell-Carlson's line includes some conventional and some *Unit-Ized* chassis; both types are hand-wired. Picture-tube sizes of 17", 19", 23", 24", and 27" are used with four chassis designs. A wide assortment of combinations can be assembled by adding supplementary plug-in units such as AM and FM tuners, mono and stereo amplifiers, and phonos, to the *Unit-Ized* chassis.

All receivers employ an unusual combination of a power transformer and a half-wave silicon-rectifier voltage doubler. Another feature, the *Picture Tube Saver*, consists of an 8-volt filament source, series dropping resistor, and provisions to short across the resistor when the CRT has weakened. A three-stage video IF strip and a 6CS6 sync separator are found throughout the line. The vertical sweep circuit in all chassis consists of a 12AU7 cathode-coupled multivibrator followed by a separate 6EM5 pentode output stage.



Two similar 17-tube chassis, the C106A and 361, do not employ the *Unit-Ized* feature. The former is mounted only in 17" (110°) portables, while the latter is used in 19" (114°) as well as in 23" (110°) receivers. Both designs incorporate a 6EB8 as a video amplifier and AGC keyer, and also a sound circuit consisting of one 6AU6 IF, a 6BN8 ratio detector-AF amplifier, and a single 6AQ5 output tube.

The *Unit-Ized* chassis for the *Custom* line is made in two alternate versions—the 159 (for 90°-92° sweep) and the 159X (for 110° sweep). Both types use 23" picture tubes with bonded safety shield. The 159 has six plug-in subchassis, and its power supply is mounted on the main chassis—whereas that of the 159X is on a seventh plug-in unit. The 23 tubes used in this series include two video amplifiers, a 6CB6 and a 6AQ5; a 6CL8A as a keyed AGC and sync phase-inverter tube; and a 6AL5 phase detector to control a 12AU7 horizontal

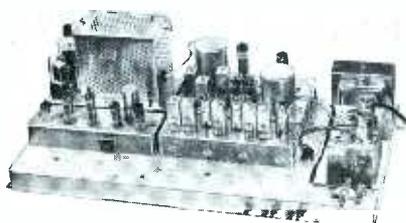

multivibrator. The sound circuit is well supplied with tubes, including two 6AU6 IF's, a 6AL5 ratio detector, an audio amplifier and phase inverter section utilizing both sections of a 6CL8, and finally a push-pull pair of 6AQ5's.

### Sylvania


The 1961 Sylvania line uses refined versions of the same basic chassis which is now in its fourth year of production. Known as the *Super S-110* chassis, the '61 revision is installed in a variety of 17", 19", and 23" sets—all "strictly TV." To form combination outfits, the TV receivers are used together with other pieces of equipment housed in matching *modular furniture* cabinetry. Initial-production 23" models used a CRT with a plain bonded safety shield. However, this

has been changed to a 23ATP4 (earlier designated as an AR23ANP4/23ATP4), in which the shield has been given an anti-reflection treatment. The same type of shield is used on the 19AUP4 CRT serving the 19" models.

Only minor circuit variations appear from model to model, in the form of *Halolight*, *Picture Prompter* (do-it-yourself preset fine tuning), *Magic Touch* remote control, etc. The basic circuitry remains essentially unchanged, even when picture-tube size considerations and cabinet shapes dictate changes in physical layout.

Chassis numbers for '61 include the following series: 546, 547, 548, 549, 550, and 552. In case you're not too familiar with Sylvania's basic *S-110* design, here's a quick rundown on the circuitry—including all the latest fea-
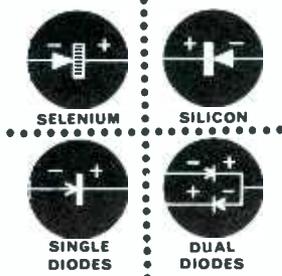
### SENCORE RS106 RECTIFIER TROUBLE-SHOOTER



Instant, Direct Substitution for . . .

**SELENIUM RECTIFIERS.** Substitutes for all types used in Radio, TV and other electronic devices up to 500 ma.

**SILICON RECTIFIERS.** Types found in many new TV sets.

**SINGLE DIODES.** With exception of some used in high frequency circuits.

**DUAL DIODES.** Types used in sync Discriminator circuits. Third test lead is provided for center connection.

Sencore has simplified trouble shooting rectifiers and diodes with this unique substitution unit. The RS106 gives you a positive check everytime . . . Substitute for suspected rectifier or diode . . . watch picture or listen to sound and you'll know in seconds whether or not the rectifier or diode should be replaced. No guess work, no soldering mess, no time lost. The RS106 actually costs less than having loose rectifiers and diodes in the shop for testing and is worth many times more.


- Rectifiers & Diodes at your finger tips for fast substitution

- Protected by 1/2 amp. Slow Blow Fuse.

RS 106  
DEALER NET. . . 1275

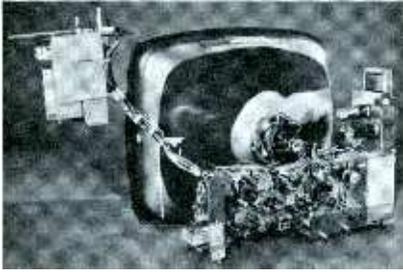Ask your Distributor to show you the RS106.





tures. A 16-tube, series-filament unit, the chassis uses silicon diodes in a half-wave doubler circuit. Printed wiring predominates. A video IF strip containing three 3BZ6's feeds a 1N295 connected in a shunt detector circuit. The video output and horizontal AFC circuits of the '61 chassis share a new 8ET7 pentode-dual diode. The triode section of a 5BR8

serves as a keyed AGC tube, while the pentode section is used in the sound IF spot to drive a 6BN8 ratio detector and AF amplifier. Single-stage audio output, 3CS6 sync separator, and conventional horizontal multivibrator circuits are employed. The 10DE7 used in the combined vertical multivibrator-output circuit of earlier models has been replaced with a new octal-based 10EG7 dual triode. Another change involves the width-control circuit; a voltage-dividing potentiometer in the screen-grid circuit of the horizontal output stage is now used in place of a width coil. Furthermore, a horizontal linearity coil has been added to the damper circuit.

### Trav-Ler

All of the '61 Trav-Ler chassis center

around one basic design, and only 19" and 23" tubes are employed. The 23AHP4 is a 92° type found in Chassis 1051-90, a 20-tube combination that incorporates an AM tuner, phono, and stereo amplifier. 23MP4's and 19XP4's (both 114° tubes) are used in Chassis 1051-60 and 1160-140, respectively. None of Trav-Ler's CRT's are equipped with a bonded shield.

All chassis are conventionally-wired and transformer-powered. Circuits common to all versions include a 1N87 video detector, 6AW8A video output, keyed AGC and sync separation from a 6BU8, and a stage for sync phase inversion. Dual selenium diodes control a cathode-coupled horizontal multivibrator. The combined vertical multivibrator and output circuit always uses half of a 6CG7 for the first stage; however, the output section varies, with a 12B4A serving the 92° version and a 6DT5 sweeping the 114° tubes.

## An open letter to George W. Riggle

**QUAM-NICHOLS Co**  
 MANUFACTURERS OF  
 LOUDSPEAKERS AND TELEVISION  
 MARQUETTE ROAD AND PRAIRIE  
 CHICAGO 37, ILLINOIS

Mr. George W. Riggle  
 Ace Radio & Television  
 Service  
 Jacksonville, Florida



Dear Mr. Riggle:

I have just received a report from our laboratory on the Quam speaker you recently sent back to us.

You are absolutely right; this speaker, which you installed more than 25 years ago, is still in perfect operating condition.

As proud as we are to have this evidence of the quality of materials and workmanship of Quam speakers, we are prouder still that you took the time and trouble to tell us about it.

It's nice to know we have such good friends in the service profession—men like yourself, dedicated to quality, dedicated to thirty year, not thirty day, installations. It affirms our policy of manufacturing only the finest possible product.

Very Cordially,  
 QUAM-NICHOLS COMPANY


*Helen S. Quam*  
 Helen S. Quam



UNRETOUCHED PHOTOGRAPH

P.S. We, also, agree with you that an ad with a picture of this unit would speak "loud" for Quam.

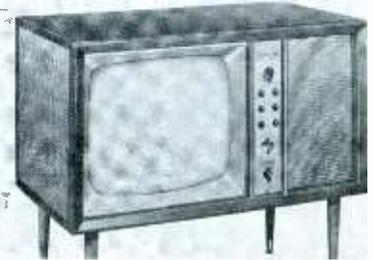**QUAM-NICHOLS COMPANY** 234 East Marquette Road  
 Chicago, Illinois




Instead of having an ordinary audio output stage following the 6DT6 quadrature detector, Chassis 1051-90 uses a three-tube stereo circuit. Among this set's other features are a 5V3 rectifier, two video IF stages, and a two-tube AM receiver. The other 23" chassis, the 1051-60, is the same except for the omission of the AM radio, a single-ended audio output stage, a 5U4 rectifier, and the 114° CRT requirements noted earlier for the vertical circuits—plus differences in the flyback, yoke, and boost filters. The 1160-140, a 19" version, duplicates the 1051-60 except for the change in CRT and the addition of a third video IF stage.

### Westinghouse

Two different remote control units are available with some 1961 Westinghouse models. Both operate on the supersonic principle, with the two-button version mechanically producing the signal, and the four-button unit doing it electronically by means of a transistorized circuit. The line features five chassis, used in an assortment of 17", 19", and 23" models—all straight TV sets, with no combinations being offered at this writing.

Printed wiring is used for most of the circuitry in all chassis. Three stages of video IF and single-stage video amplification are found in every member of the line. The sound circuits consistently have one IF (a triode section of a 6FV8), a DT6 quadrature detector, and a single output stage. The conventional combined vertical multivibrator-output circuit, dual horizontal AFC diodes, and cathode-coupled horizontal multivibrator, are also used.

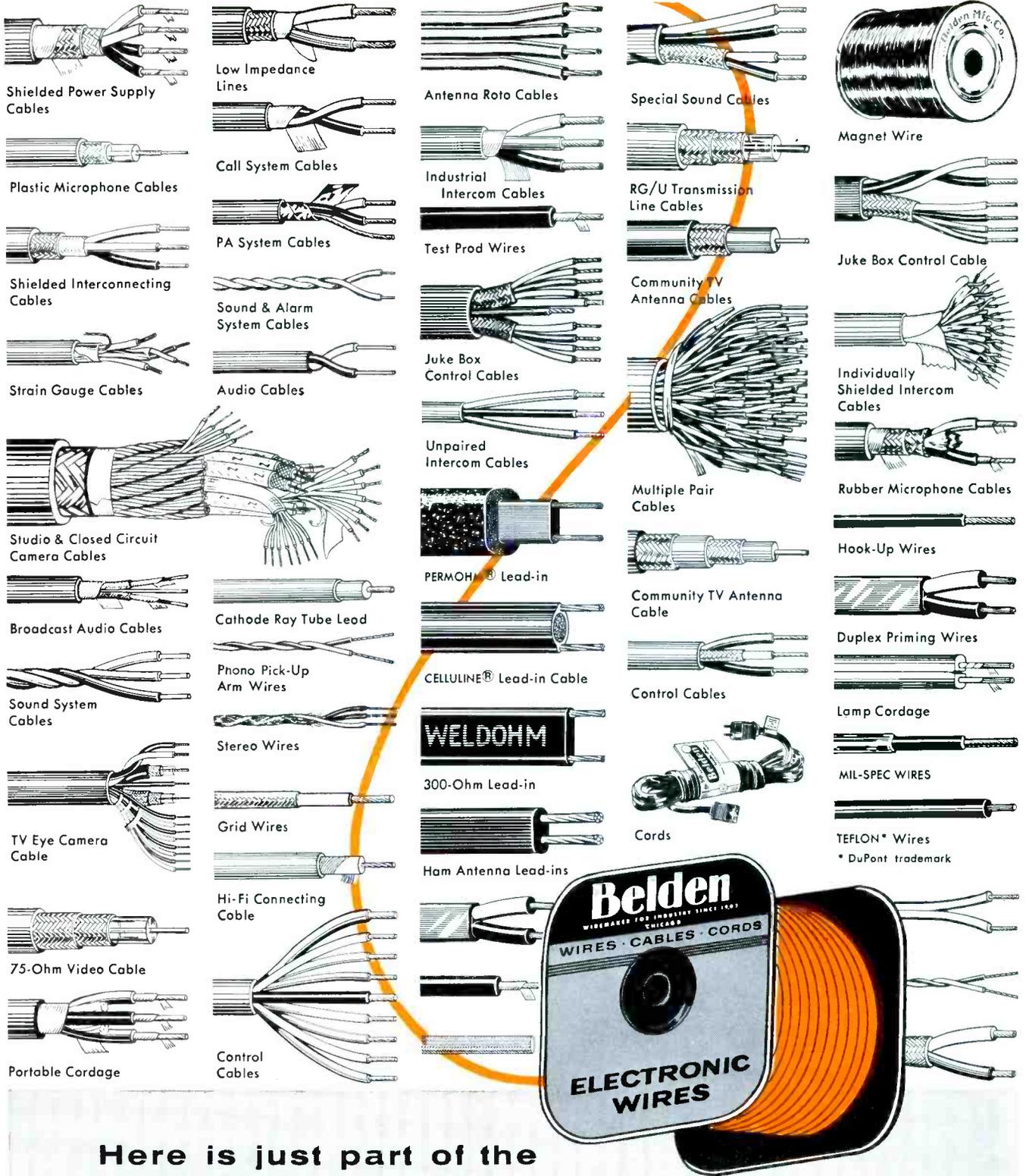Three chassis serving the 17" and 19" group are the V-2384, V-2409, and V-2412. The first and last of these are 15-tube chassis with 450-ma series filaments and a pair of silicon diodes in a half-wave doubler configuration. The 19" Decorator series uses the V-2409, a 16-tube chassis equipped with a power trans-



Here is just part of the  
**WORLD'S MOST COMPLETE LINE**  
of Electronic Wire and Cable!



**Available from Stock**


*One Wire Source for Everything  
Electronic and Electrical*

magnet wire • lead wire • power supply cords • cord sets • portable cordage • electronic wire  
• automotive replacement wire and cable • aircraft wire • electrical household replacement cards

8-3-9
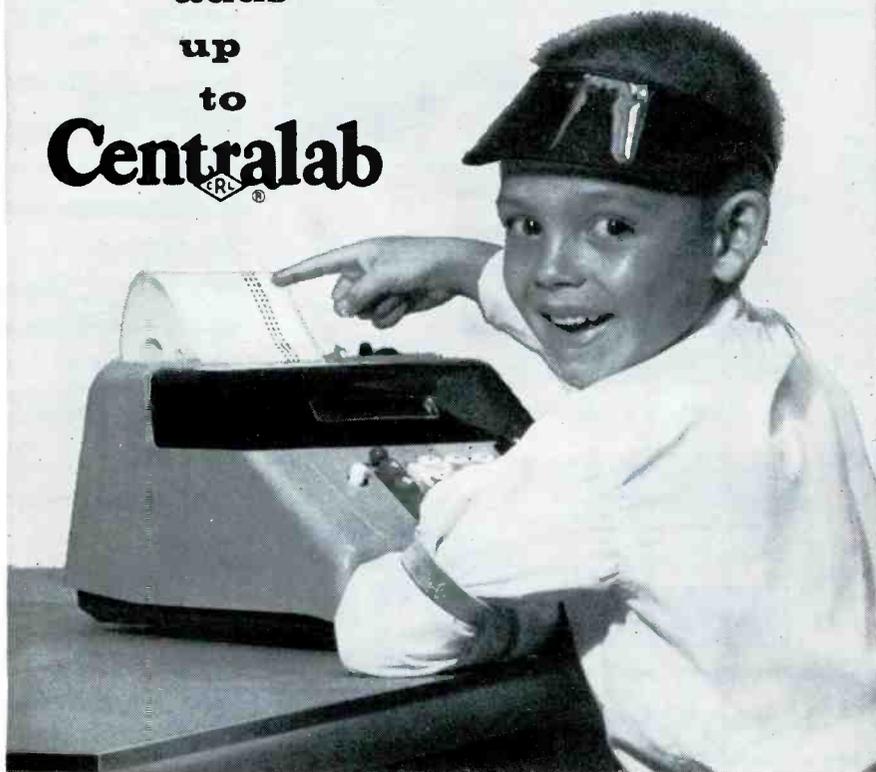
## For Push-Pull AND Push-Push Switch Type Controls

it  
all  
adds  
up  
to  
**Centralab**  
ERL®




Look at the figures—78% of the TV, radio and hi-fi sets now being produced utilize push-pull or push-push controls! Only CENTRALAB gives you a *complete* line of replacements for them—35 push-pulls, plus the *only* push-push units available! To multiply your choice, these CENTRALAB switch-type controls are divided into 4 types—Adashaft, Universal Shaft, Fastatch or dual concentrics, and Twin types for stereo. Whatever kind you need, you can be sure your CENTRALAB distributor has it. For a complete accounting on these push-pull and push-push controls, ask your distributor for Bulletin 42-936 or write us for your free copy.

# Centralab

B-6034 ERL®


THE ELECTRONICS DIVISION OF GLOBE-UNION INC.  
942L EAST KEEFE AVENUE • MILWAUKEE 1, WIS.  
CENTRALAB CANADA LIMITED—AJAX, ONTARIO

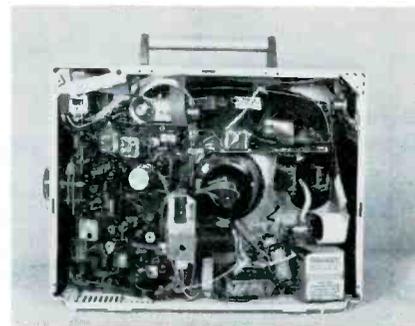ELECTRONIC SWITCHES • VARIABLE RESISTORS • CERAMIC CAPACITORS  
PACKAGED ELECTRONIC CIRCUITS • ENGINEERED CERAMICS



former and a 5U4. Some models in this group employ the two-button remote control system. In all the above chassis, AGC is derived from the video-detector output and sync-separator input signals. Separate triode sections serve as sync separator and sync noise inverter, and the vertical sweep tube is a 'CS7 dual triode.

The 17-tube V-2411 series of 23" chassis are very similar to the 19" V-2409 except for the addition of a 6AU6 in a keyed AGC circuit, the use of a higher-gain 6EB8 video output tube in place of a 6AW8A, and the substitution of a 6EM7 vertical sweep tube for a 6CS7. In the V-2389 chassis, largest in the line, the tube total is brought up to 18 by replacement of the dual-triode vertical multivibrator-output tube with a 12DT5 pentode and the triode section of an

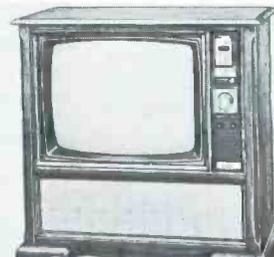

extra 6FV8. The pentode section of the latter tube is put to work amplifying the video-detector output signal and feeding it directly to the sync separator. A center-tapped 12-volt filament winding on the power transformer allows the use of three 12-volt tubes (12DT5, 12AX4-GTB, and 12DQ6B) alongside the regular 6-volt types. The above chassis also switch from a 6AQ5 audio output tube to a 6BQ5.

### Zenith

One basic circuit design underlies the entire 1961 Zenith line, although many optional features such as remote control, AM-FM tuners, stereo amplifiers, and timers are offered. The timers turn the set off, as is done by the "sleep" switch on a clock-radio. Three superpersonic remotes, dependent upon mechanically-generated signals, provide various control functions. Picture-tube sizes range from 17" through 23". The 17" and 19" versions require 110° and 114° deflection circuits, while all 21" and 23" chassis have only 90° or 92° sweep.

Two different physical layouts of the hand-wired chassis are used to accommodate it to large and small cabinets. The 16F25 and -6 series use the smaller of the two versions in the 17" and 19" sets. Chassis 16F24Q, using the largest remote system, an AM-FM tuner, and a stereo amplifier, omits the audio output stage from the TV chassis; this is the greatest deviation of any set from the standardized circuit pattern.




The '61 chassis are designated 16E23, 16E24Q, 16F21, 16F23, 16F24Q, 16F25, and 16F28. Additional suffixes of U, Q, and T indicate UHF, remote control, or timer options. Three stages of video IF, a crystal-diode video detector, and a 6EB8 or 6GN8 video output tube constitute the video-signal chain. The audio circuits retain the 6BN6 detector which has been used for a number of years. There are considerable variations in the tube used as a low-voltage rectifier; 5U4's, 5V3's, and recently-introduced 3DG4's find their way into various chassis. A 6BU8 serves in the keyed AGC and sync separator circuits, with no assistance from any sync-amplifier or phase-inverter stages. In the sweep circuits, vertical deflection is obtained from a 6EM7 or 6EA7 dual triode in a combined multivibrator and output circuit, while the horizontal section uses the modified "Gruen circuit" (sine-wave oscillator, reactance tube, and phase detector) carried over from last year's line.
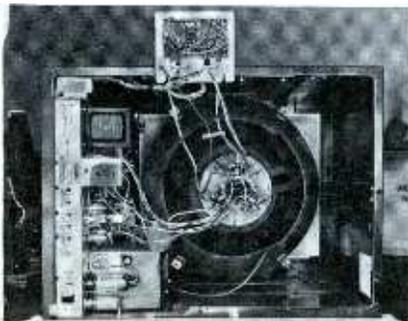
### Color

The 1961 color sets show signs of progress in the process of evolution. No major, industry-shaking breakthroughs have occurred; however, there's no doubt that the '61 lines carrying color receivers are offering the best units yet made available. At present, information is available on only the Admiral, Packard-Bell, and RCA Victor models; but Olympic has announced a color set that should be available soon.

Minor variations in numerous circuits, introduction of new tube types to achieve greater stability and reliability in already-existing circuitry, and new approaches to old problems are to be found in all chassis. Higher-gain tubes, revised AGC and noise-limiting circuitry, replacement of potentiometer-type focus circuits by variable-inductance circuits, and convergence-circuit variations are the predominant areas of redesign in the different chassis. Because of the complexity of color circuits, space does not permit a detailed explanation of all circuit changes at this time; however, these will be further explored in a later coverage.



### TUBE TESTER

Model 658 Dynamic® Output Type  
Faster, more versatile, more accurate.  
Makes more tests than any other tube  
tester. Meets the needs of every engi-  
neer, lab technician and serviceman.

\$189.95 Net

### OSCILLOSCOPE

Model 600 Laboratory type, wide  
band/high sensitivity operation  
for every industrial, scientific and  
service application. Has every per-  
formance feature of higher priced  
scopes.

\$335.00 Net



## ALL-NEW

# JACKSON INSTRUMENTS

for profit-minded service technicians



### SINE/SQUARE WAVE OSCILLATOR

Model 605 Precision unit gives both  
sine and square wave output for accu-  
rate amplifier circuit checks in hi-fi,  
stereo, video and industrial lab appli-  
cations. 20 to 200,000 cycle range.

\$129.95 Net

### POWER SUPPLY

Model 607 Laboratory unit provides  
heater, Negative and regulated vari-  
able B voltages in one compact  
package.



\$79.95 Net

*Investigate these new Jackson instruments. See your  
electronic distributor... or write for literature.*



## ELECTRICAL INSTRUMENT COMPANY

124 McDonough St., Dayton, Ohio

In Canada: The Canadian Marconi Co.

*More Signal  
Power with Winegard  
TV Amplifiers and  
Booster Couplers!*



**New Precision Amplifier A-400** drives 1 to 30 TV sets. You get up to 26db gain on TV and FM bands with the Winegard A-400. Has four 6FY5 neutroelectrode tubes with extremely low noise characteristics. Dual 75 ohm outputs—300 ohm balanced input with no-strip disconnect plug and 75 ohm coaxial input. Unit completely fused. Finest amplifier in its class—\$79.95.

**Booster Coupler WBC4**—operates 1 to 4 TV and FM sets. Delivers up to 12.5 db gain all channels on one set. Operates 2, 3 or 4 sets with up to 6 db gain for each set. Powerful 6DJ8 tube, shielded and protected. 4 sets of no-strip lead-in terminals—quick disconnect plug for antenna lead-in—\$27.50.



Write today for full information  
on Winegard TV distribution systems  
and famous Winegard TV antennas.



**Winegard Co.**

3009-11 Scotten Blvd. Burlington, Iowa  
Antenna Systems

Everything from the  
antenna to the set



**Gift Time.** We begin to get that "Christmas is around the corner" feeling about the time we're on our final helping of Thanksgiving turkey. In the midst of preparing for the Holiday mood, we turn our thoughts toward providing something special for our own customers. However, promotion plans for the Christmas season should be finalized long before Thanksgiving . . . if they are to pay off.

What part of your advertising budget in this season will be used for gifts? Who'll get them, and how will they be distributed? Think about your proposed gift: will it fill a need for your customers in their homes? Will it stay in sight and be used? You want your "morsel of remembrance" working for you as long as possible.

Don't forget the kids. A little gift, such as a toy glider or a package of balloons, will give you more word-of-mouth advertising than you'd think. It's amazing, but kids don't forget such favors—and they won't let their parents forget, either!

To show what can be done in the way of Christmas promotions, William Dufer, Jr., of Binghamton, N. Y., has written to tell us what several shops in his area are planning for the holiday season. He reports for instance, that Colonial TV of Johnson City will equip its home-call men with comic books and bags of crunchy candy to present to the small fry. Personalized greeting cards, carrying a photo of the crew and signed by every man, will also be sent to all customers. Tucked inside each card will be a \$1 credit memo that can be applied to the first 1961 transaction reaching a minimum of \$7.50.

Haloway-Cooper of Binghamton will make a personal telephone call to every customer, wishing him a happy holiday season and asking if his set is performing well. In addition, newspaper ads will offer *Christmas Radio-TV Service Bonds* in \$10 to \$50 denominations at a 10% discount, stressing their practicality as gifts for friends and neighbors, and especially for senior citizens who depend greatly upon radio and TV for entertainment.


Ang's TV Shop of Endicott will promote service by advertising a "pre-Christmas physical" for radio or TV sets, to keep them in top shape during the peak of the winter season. This shop's ads in local papers will offer a free Christmas tree with every new picture tube sold between the 5th and 20th of December.

Lange's TV in Vestal will install a gift-wrapping bar presided over by a group of housewives working four-hour shifts. The public will be invited to come in and have gifts wrapped for a token charge of four for a quarter—just about enough to cover the cost of the materials. It's hoped that many who come in to have their gifts wrapped will watch the bench men at work, will be favorably impressed, and will call on Lange's whenever they need service in the future.

This, then, is a sample of the Christmas plans already worked out by forward-thinking radio-TV servicemen. Within a single trading area, we find a variety of ways and means to reach one common goal—the garnering of both business and good will.

# Rebuild Tube Sales Volume
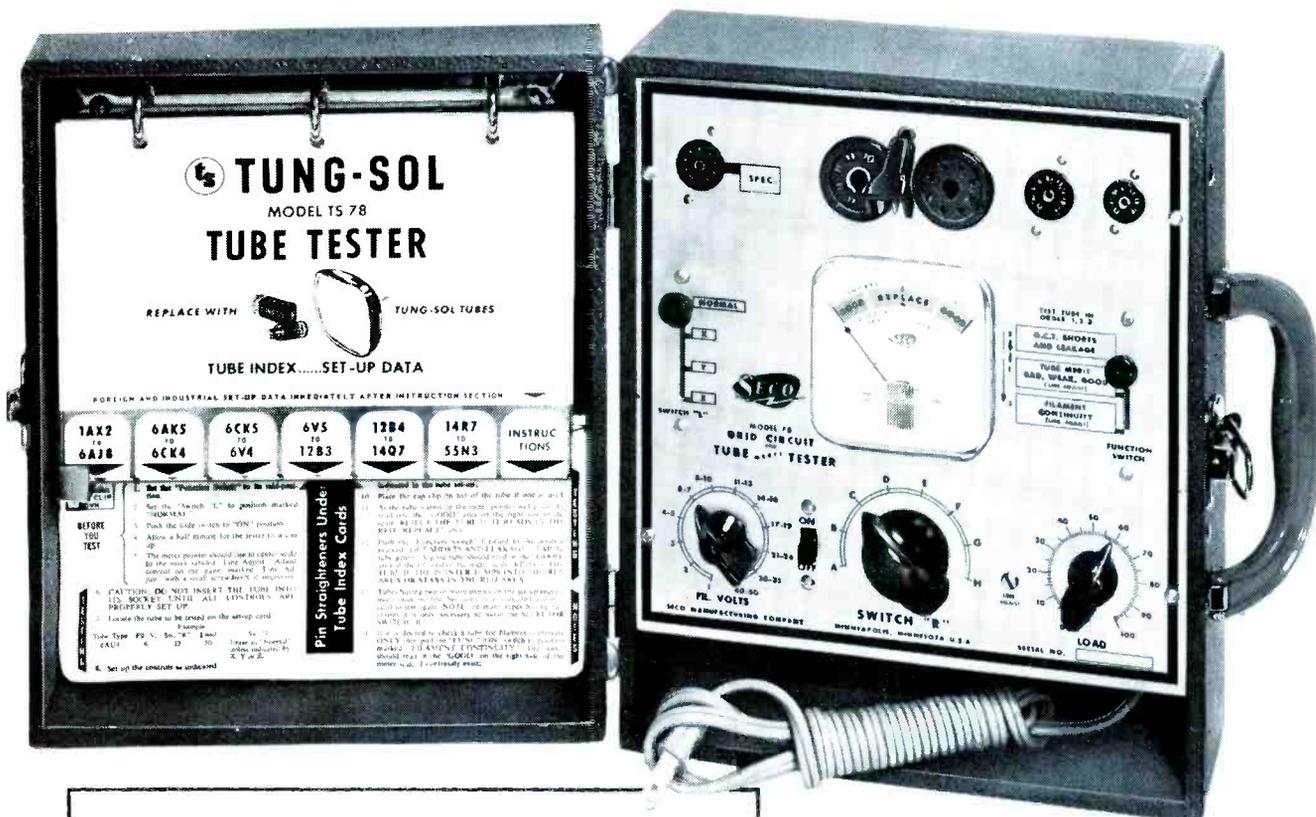
## With the Tung-Sol "take home" tube tester plan



The Model TS-78 Tube Tester is a precision instrument, exceptionally fast and easy to use. Five sockets accommodate all tubes.

Gives results for both grid circuit and tube merit tests. Comes equipped with all instructions and complete tube reference guide.

**TV servicemen** now can accommodate "do-it-yourself" customers who like to test their own tubes—and at the same time regain tube sales that have been slipping away.

The low-cost Tung-Sol "Take Home" Tube Tester enables you to provide a lending service that lets customers test their radio and TV tubes right in their own home.

Here's how it works! Customer borrows the tube tester. Checks all his tubes at home.

Returns the tester and buys the new tubes he needs from you.


In addition to boosting tube sales, the Tung-Sol plan will increase traffic to your place of business. You'll gain new service customers and increase in-store sales of other products.

Your Tung-Sol tube supplier has the whole story about the Tung-Sol "take home" Tube Tester plan. Get the information at once and begin to get back the tube sales you've lost. Tung-Sol Electric Inc., Newark 4, N. J.



**TUNG-SOL**<sup>®</sup>  
ELECTRON TUBES • SEMICONDUCTORS

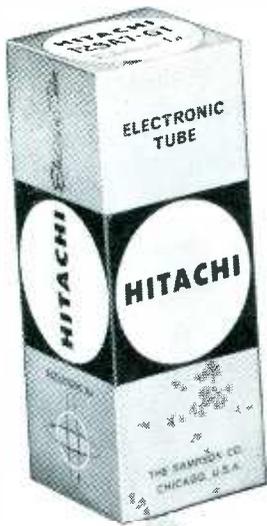**MORE PROFIT**  
per call... satisfaction for all!



SELL—SERVICE—SATISFY

**RECEIVING TUBES**  
MADE BY  
GRAND PRIX AWARD-WINNING  
**HITACHI**



Choice as original equipment by manufacturers in the U. S. & abroad

From all points come good words about Hitachi tubes produced by one of the world's largest manufacturers—Hitachi, Ltd., Tokyo, Japan. Tubes that can't be beat for performance and reliability. Most popular types are available . . . each made with strict quality-control to fully meet top American standards. Yet important cost savings guarantee you extra profits. And distribution is on a localized prompt-delivery basis.

**THE SAMPSON COMPANY**  
ELECTRONICS DIVISION, 2244 S. Western Ave., Chicago 8, ILL.

See your HITACHI Distributor  
— or write for CATALOG  
CT400-A

A COMPLETE LINE  
OF QUALITY ELECTRONIC  
COMPONENTS

## Fundamental Transistor Theory

by William C. Caldwell

Here's a treatment that goes straight to the heart of the subject without getting lost in the deep woods of atomic physics.

The simple diode, which has long been used to detect or rectify signals, is the backbone of the transistor. A short review on how diodes work will help in understanding transistors.

A typical modern diode may be of germanium, silicon, or a similar material. These materials, in pure crystalline form, make extremely good insulators; if no other materials were added, the diode would be unable to pass any current, and would therefore be useless. However, the diode is actually divided into two sections (*di* meaning two), and a certain amount of "impurity" is added to each section. The impurity is simply a different type of material which supplies current carriers (Fig. 1) of either negative or positive polarity, depending on the material added in the manufacturing process. One type of impurity will produce N-type carriers, which are negative; and another impurity will provide P-type carriers, which are positive.

The presence of these free current carriers allows the diode to become a fairly good conductor under the conditions shown in Fig. 2. When a battery is connected as shown, the junction between the N and P sections is literally flooded with current carriers. This means the resistance of the diode to current flow is very low. The reason the diode allows current to pass is

that there are plenty of free current carriers at the junction of the two diode sections.

To more clearly understand the principle of conduction through a diode, refer to Fig. 2 again. The negative battery terminal is connected to the N section of the diode, which contains free, movable electrons. Since like polarities repel each other, the negative field of the battery pushes the electrons toward the junction. Likewise, the positive pole of the battery repels the positive carriers toward the junction. It takes only a small voltage to give the charged carriers sufficient energy to cross the junction, and once they start moving, a constant exchange takes place. As negative carriers move into the P region, positive carriers cross into the N region (a fact which will become important later on). For the moment, however, the main thing to remember is that current carriers move through the diode and back into the battery. An ammeter placed in the circuit, as in Fig. 2, will indicate current is flowing.

### The Nonconducting Diode

But let's suppose the same diode is connected to the same battery, except that the polarity is reversed as shown in Fig. 3. The negative electrons in the N section are now attracted by the charge at the positive terminal of the battery, and the positive current carriers in the P region are attracted by the charge

Editor's Note: Material in this article has been excerpted from the new Howard W. Sams book, *Practical Transistor Servicing*, by William C. Caldwell.

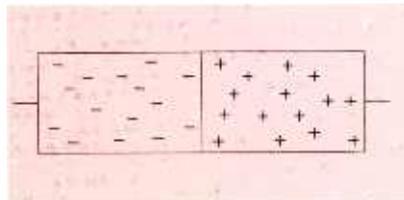


Fig. 1. Adding impurities to crystal material produces charged carriers.


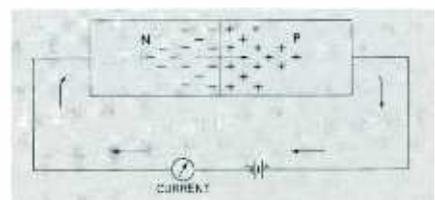


Fig. 2. Diode current will flow when battery voltage has proper polarity.

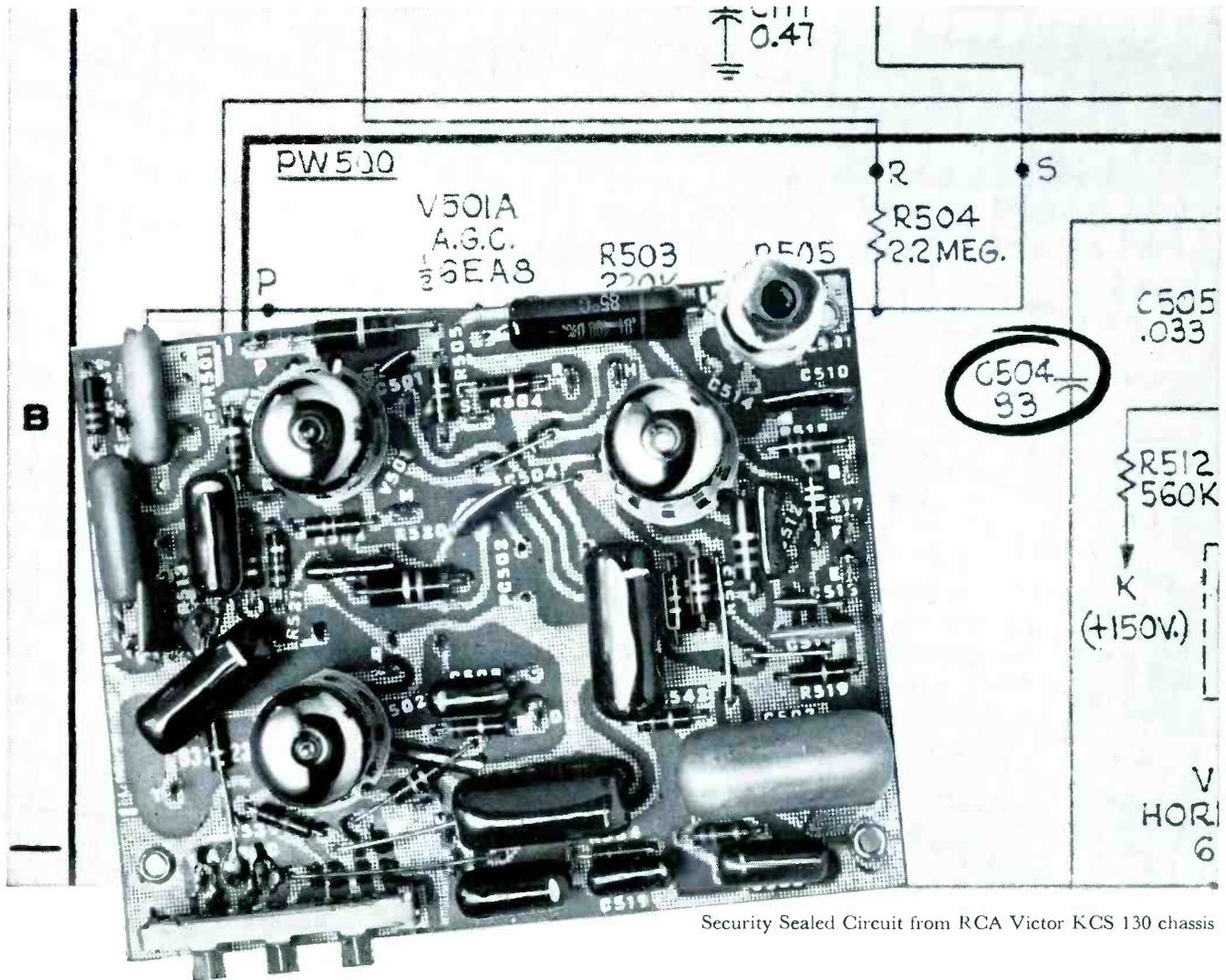

Security Sealed Circuit from RCA Victor KCS 130 chassis

## How fast can you find C 504? (Average time—10 seconds)

You know how valuable minutes are in TV servicing! Every one you save means money in your pocket.

With this all-important fact in mind, take a good look at the RCA Security Sealed Circuit in the picture above. All components are plainly marked. So are meter and scope take-off points and signal injection points. RCA Security Sealed Circuits take the *guesswork* out of servicing. That's for sure!

Now compare the RCA Security Sealed Circuit with any old-fashioned point-to-point wired chassis you have on your bench. Which do you vote for as a timesaver and error eliminator? If you vote for the printed circuit, you

are voting along with the nation's top missile, satellite and computer engineers! *Long ago, they chose printed circuits because printed circuits alone offer the maximum dependability.*

But, you may be thinking, how about parts replacement? Do printed circuits make this easier or tougher? The answer is—*easier!* All you need is a light, low wattage iron or gun, which is a good thing to have around the shop anyway. No special techniques are needed . . . just plain common-sense methods.

Next time a customer asks, explain that printed circuitry is the mark of modern, dependable, easy-to-service home entertainment equipment—such as RCA Victor!

TMK'S®



The Most Trusted Name in Television

RADIO CORPORATION OF AMERICA



**NEW! REPAIR SHAFTS FOR BROKEN STUDS**



PERFECT FOR ALL 1949-61 TV SETS

MODEL AGC DEALER NET ONLY 79c (Package of 6 most needed)

Servicemen everywhere are now repairing broken studs this easy, inexpensive way! Used on I.F. Transformers A.G.C. • Width • Horizontal Osc. and Linearity Coils. Also used as extension shaft for easier adjustment. 4-40 and 6-30 threads.



**Rx—TUNERS  
Rx—CONTROLS  
Rx—CONTACTS  
Rx—SWITCHES**

New formula Detergent-Lubricant Silicon oil

FREE INJECTOR

A must for all servicemen kits! Rx works wonders with tuners and controls, eliminates noise, retards corrosion, lasts longer. Recleans and lubricates with each rotation of tuner or control... simple to use... features a long-lasting detergent-lubricant. You can't afford to use less than the best. Insist on Rx.


Net \$1.19  
Giant 6 oz. can.



**REPLACEMENT FLAT LOOPSTICK for Japanese Transistor radios Model 2FT-397 List 2.35**

Make more money with this fabulous Flat Transistor Loopstick. Actually improves set performance by virtue of its extremely high "Q" is adjustable to match Japanese variable capacitor. Peps up weak stations. Supplied with illustrated, installation instructions.

**NEW! SUPEREX SET SAVER**

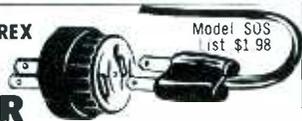

STOPS HARMFUL VOLTAGE SURGE... TRIPLES TUBE LIFE

MINIMIZE CALL-BACKS due to tubes popping, and make more money, too! SELL SET SAVER. Amazing SET SAVER eliminates harmful initial voltage surge that shortens life of tubes and parts. This is the same surge that often BLOWS OUT ELECTRIC BULBS just as you switch it on! SELL SET SAVER on all your calls!

ADDS LIFE TO TV SETS, RADIOS & HI-FI  
PROLONGS LIFE OF tubes (incl. picture tube), capacitors, rectifiers, transformers, other parts.

At your parts jobber. If not available, write for name of nearest supplier.

6 Radford Pl. Yonkers, N.Y.

at the negative terminal. The result is that both varieties of current carriers in the diode are pulled away from the junction, instead of toward it. This leaves no free carriers in the center of the diode, so this area again becomes an insulator, just as it was before the N- and P-forming materials were added to the pure crystal. The battery current is now blocked, and current flow ceases. Even if the battery voltage is increased, practically no current will flow. We say "practically" because a very minute "leakage" current (due to heat or moisture) does exist.

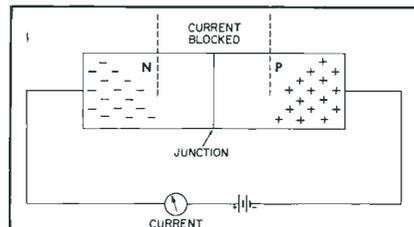


Fig. 3. Reversing battery connections will block current through the diode.

**Ohmmeter Causes Diode Action**

When an ohmmeter is placed across a diode, the resistance shown will be low or very high, depending on which way the leads are connected. The reason is that the ohmmeter is really just a milliammeter connected in series with a battery. (See Fig. 4.)

The negative lead of the ohmmeter in Fig. 4A is connected to the N side, and the positive lead to the P side, of the diode. This forces N and P current carriers across the junction, creating a low internal resistance. Current from the ohmmeter battery can now flow through the circuit, and the meter indicates a fairly low resistance (usually under 100 ohms). This reading is

actually a result of the current flow through the conducting diode and the meter, but the meter face is marked in ohms. In other words, a lower ohms reading indicates a greater current flow through the meter.

Now examine the circuit in Fig. 4B. The only difference between it and the one in Fig. 4A is that the ohmmeter has been turned so the positive lead is connected to the N side of the diode, and the negative lead to the P side. The polarity of the internal battery is such that the free current carriers are attracted away from the center of the diode. This creates an insulated area in the diode, making it void of all current carriers, both positive and negative. Battery current is now blocked, so nothing flows through the meter. The ohmmeter reading is thus very high; it theoretically should read infinite resistance, but there is always a very slight leakage current which causes the meter pointer to deflect to some degree.


**TV TUNERS OVERHAULED**

ONE PRICE . . . \$9.95 NET ALL MAKES AND MODELS

INCLUDING ALL VHF, UHF AND UV COMBINATIONS\*

\*UV combination tuner must be one piece construction. Separate UHF and VHF tuners with cord or gear drives must be dismantled and the defective unit only sent for overhaul.

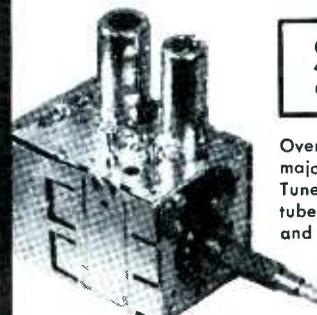**SAME DAY SERVICE ON POPULAR TYPES—48 HOURS MOST OTHERS**



Overhaul charge includes labor and minor parts; tubes and major parts are extra at net prices. Written 90 days warranty. Tuner to be overhauled should be shipped complete; include tubes, shield cover and any damaged parts. Quote model and state complaint. Pack well and insure.

WRITE FOR SPECIAL QUANTITY RATES & DISCOUNTS

Castle TV Tuner Service

5710 N. WESTERN CHICAGO 45, ILL.

U.S.A.

136 MAIN ST. TORONTO 13

CANADA

Suppliers of rebuilt TV Tuners to manufacturers, technicians & service dealers, coast to coast. Original and Only Complete TV Tuner Service covering the North American Continent.

Having now proved that diode resistance can be high or low, depending on the polarity of the voltage connected to it, let's see what this means as far as a transistor is concerned.

### The NPN Transistor

A curious and interesting effect occurs when three instead of two diode sections are placed together. Fig. 5A shows a P-type section, containing free positive current carriers, positioned between two N-type sections. Actually, two diodes have been formed, but diodes 1 and 2 both use a common P section in the middle. The schematic symbol for this arrangement is shown in Fig. 5B.

The first question that arises is, "What happens when a battery is connected across this structure?" Fig. 6A shows the battery connected in one direction, and Fig. 6B shows it connected in the other direction. In both examples, one of the diodes is biased in the high-resistance direction, causing free current carriers to be pulled away from the junction and leaving a blank area which blocks the flow of current. The reason is that the positive pole of the battery is always connected to one of the N sections, attracting negative car-

riers toward the outside edge and away from the junction.

If the battery and meter shown in Fig. 6 were both part of an ohmmeter, a similar action would take place. The current through the circuit would be quite small and the resistance would be fairly high. This reading is called the *leakage resistance*.

The battery voltage in Fig. 6 can be increased to several volts, and still very little current will flow. With increased battery voltage, however, there is a good source of current — but the blocked area

must be unblocked before carriers can cross the junction. The simple method used to unblock the insulated area is the secret of transistor action.

### Adding "Forward" Bias

The easiest way to make current flow through an area where there are no free current carriers is to send some current carriers into the area. This is done very simply in Fig. 7. A small voltage is connected across diode 1 only. The battery is connected so the polarity is in the forward, or low-resistance, direc-

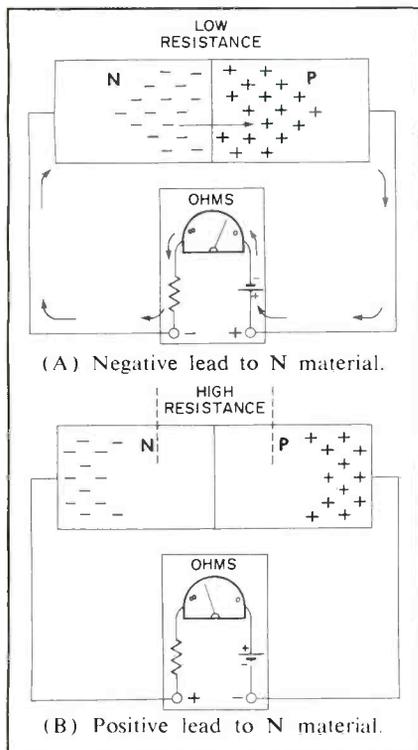



Fig. 4. Action of carriers when an ohmmeter is connected across the diode.

## Now Completely SELF-CONTAINED

For Testing & Rejuvenating  
BLACK AND WHITE and COLOR including 110° TUBES

# NEW CRT 440

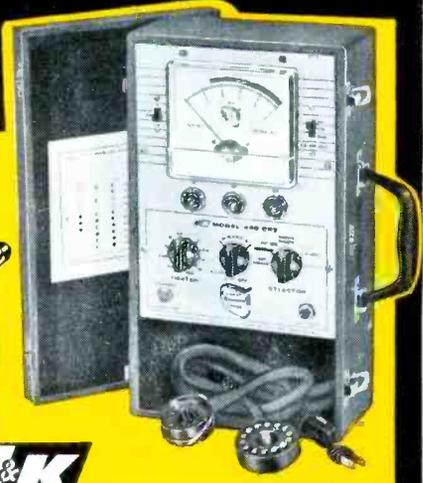

**TESTS AND REJUVENATES**  
all black & white and color picture tubes at correct filament voltage from 1 to 12 V.

**TESTS AND REJUVENATES**  
110° tubes with 2.34, 2.68, 6.3 and 8.4 volt filaments.

**TESTS AND REJUVENATES**  
color picture tubes. Checks each color gun separately same as black & white tubes.

*Used by Thousands of Professional Servicemen*  
**MAKES NEW PICTURE TUBE SALES EASIER**

Gives you more value than ever—all-in-one. Quickly checks and corrects most TV picture tube troubles in a few minutes right in the home without removing tube from set. Gives new useful life to weak or inoperative tubes. Checks leakage. Restores emission and brightness. Repairs inter-element shorts and open circuits. Life test checks gas content and predicts remaining useful life of picture tube. Completely self-contained in leatherette-covered carrying case. Net, **\$74.95**

**ACCESSORIES for USE ONLY with FORMER B&K Models 400 and 350 CRT**



**Model C40 Adapter.** For use only with all previous B&K Model 400 and 350 CRT's. Tests and rejuvenates TV color picture tubes and 6.3 volt 110° picture tubes. Net, **\$9.95**

**Model CR48 Adapter.** For use only with all previous B&K Model 400 and 350 CRT's. Tests and rejuvenates 110° picture tubes with 2.34, 2.68, and 8.4 volt filaments. Net, **\$4.95**

See your B&K Distributor or Send now for Bulletin AP16-R

## B&K


**B & K MANUFACTURING CO.**  
 1801 W. BELLE PLAINE AVE • CHICAGO 13, ILL.  
 Canada: Atlas Radio Corp., 50 Wingold, Toronto 10, Ont.  
 Export: Empire Exporters, 277 Broadway, New York 7, U.S.A.



Replace  
with  
the  
best...

**RCA POWER  
TUBES**

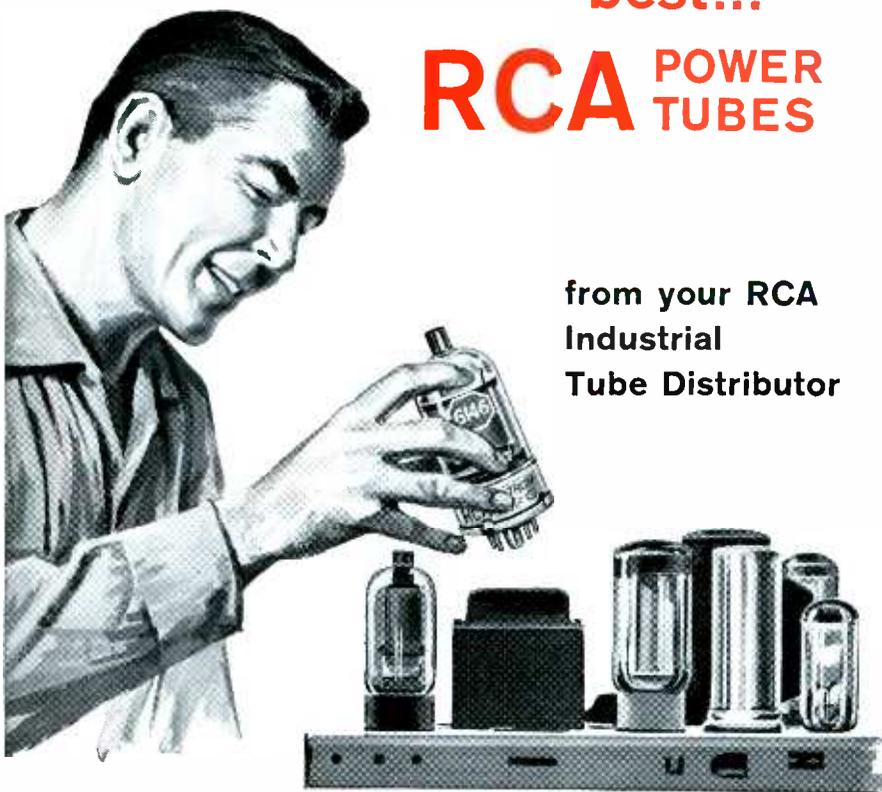from your **RCA  
Industrial  
Tube Distributor**



For reliable 2-way radio communications, always replace with RCA Power Tubes from your local RCA Industrial Tube Distributor. For more than a quarter-century RCA Power Tubes have been the standard of quality in communications equipment. Wherever you look in commercial radio, the military services or industry, you'll find RCA Power Tubes doing the critical jobs...delivering top performance. It makes sound business sense to invest in the long-life economy of RCA Power Tubes in your essential 2-way radio equipment.

Your RCA Industrial Tube Distributor carries a complete line of RCA tubes for fixed and mobile communications equipment. Give him a call whenever you need replacement tubes. He'll always give you fast, efficient service.



ANOTHER WAY RCA SERVES YOU THROUGH ELECTRONICS  
**RADIO CORPORATION OF AMERICA**  
Electron Tube Division Harrison, N. J.

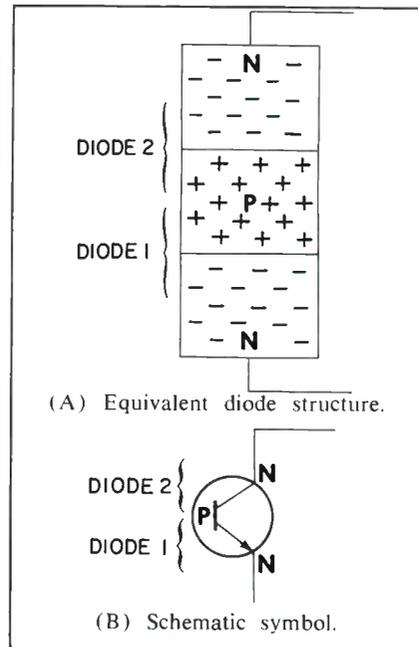


Fig. 5. Inside an NPN transistor.

tion (negative pole connected to the N material, and positive pole to the P material). This causes negative carriers to be pushed upward and into the P area. Most of these carriers will travel on through the narrow P area and enter the formerly blocked area of diode 2. Once the carriers have filled the upper N area, the larger battery keeps them moving into the output circuit, as indicated by meter M2 in Fig. 7A. The electrons continue to flow through the larger battery and back into the bottom N region, their point of origin.

A very small current will also flow in the input circuit (see meter M1), but it is much less than the M2 current because the input voltage is less. Thus, introduction of a small current has caused a much larger current to flow — which can be termed *current gain*. In Fig. 7B, the same circuit is redrawn to show the use of a transistor symbol. There are several reasons why this NPN transistor has gain when used in the basic circuit just shown:

1. The P area is made much narrower than the N areas, allowing negative carriers to cross it easily once they are started.
2. The negative carriers are easily pushed out of the bottom N area because the small battery is connected across diode 1 in the forward, or low-resistance, direction — the direction which makes cur-

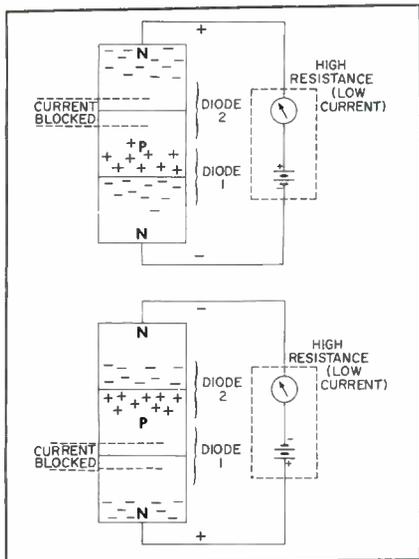


Fig. 6. Carrier action when battery is connected across an NPN structure.

rent flow easily.

3. The output battery, being larger than the input battery, is able to draw more current once the transistor has been unblocked by the smaller battery.

#### The PNP Transistor

The PNP transistor is similar to the NPN unit, except that the diode sections are arranged as shown in Fig. 8. An N section is sandwiched between two P sections, and the positive current carriers now become more important.

Again, regardless of in which direction the battery is connected, one of the diodes will be biased in the high-resistance direction—that is, the positive carriers will be attracted away from the center, and battery current will be blocked. However, if a small battery is con-

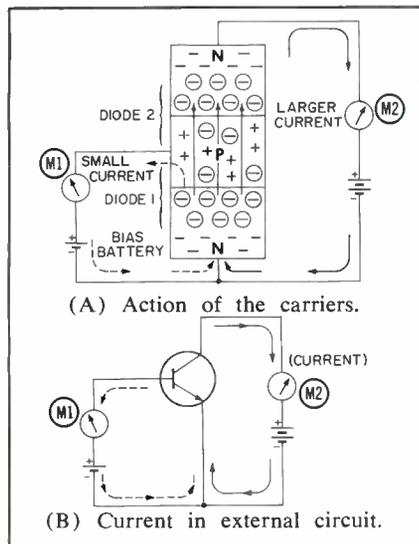



Fig. 7. Forward-biasing an NPN unit.

nected across diode 1 in the forward direction, as shown in Fig. 9, that diode will start conducting slightly. (Notice that the positive battery terminal is connected to the P section and the negative terminal to the N section.) Even a small voltage in the forward direction will force positive current carriers out of the lower P section.

Most of the positive carriers pushed out of the lower P section travel upward and through the narrow N section. This means they will flood the upper P section and unblock the transistor. With cur-

rent carriers available at all points in the transistor, the larger battery can now send its own current through the transistor and into the output circuit, as evidenced by meter M2.

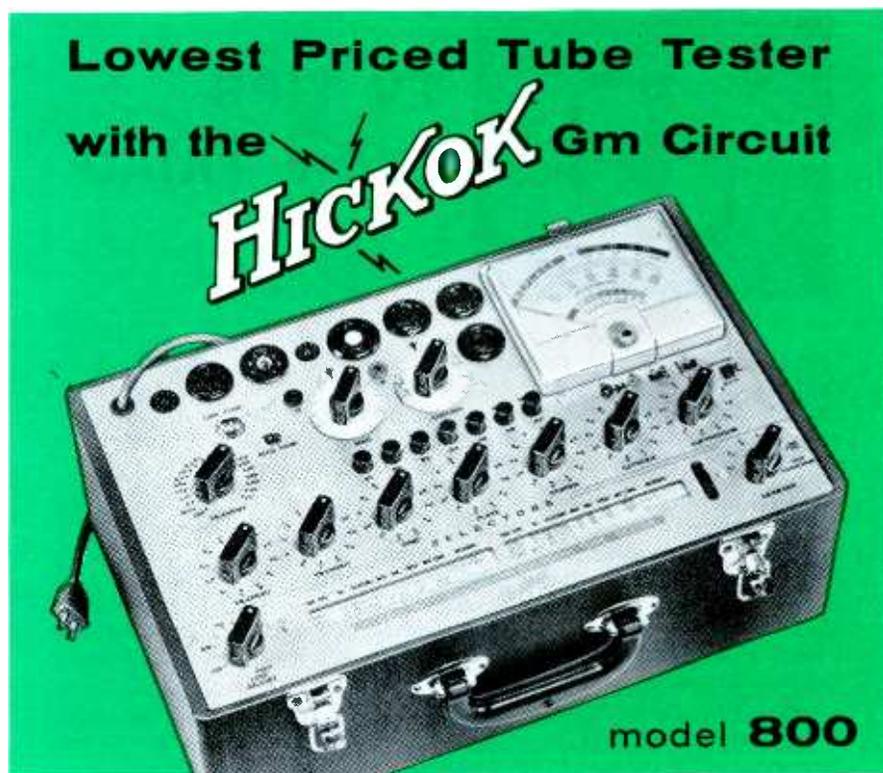As with the NPN transistor, the output current is larger than the input current because the voltage required in the input is extremely small. Since diode 1 is biased in the low-resistance direction, carriers are easily sent upward from the lower P area, even though the small battery may be only 0.1 or 0.2 volt. These carriers unblock diode 2 so



### Service Technician's Portable Tube Tester, Transistor and Diode Checker

- Built-in roll chart contains test data on latest tubes, including NUVIDISTORS
- Inter-element leakage and shorts read directly on the meter
- New filament continuity test speeds checking series-string tubes
- Cathode reserve measurement provided
- Only HICKOK offers roll chart subscription service

See Your Distributor, Ask for a Demonstration!  
\$169.50 net

The Hickok Electrical Instrument Co.


10566 DUPONT AVENUE • CLEVELAND 8, OHIO

current from the larger battery can flow through.

Since the diode sections were reversed to make the PNP transistor, the batteries were also turned around when they were connected to the PNP transistor. This is the reason the arrows depicting input and output current are reversed in Fig. 9A, as compared with Fig. 7A; electrons always leave the negative pole of a battery and enter the positive pole. (The arrows show electron flow from the batteries and through the circuit *outside* the transistor.)
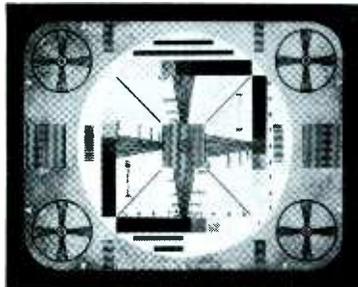
### Identifying Transistor Elements

The bottom section of the input diode is called the *emitter* because it supplies the current carriers which permit transistor operation. It is often compared to the cathode of a tube, which produces the electrons for tube operation. The opposite end of the transistor, to which the output circuit is usually connected, is known as the *collector* because it collects the carriers which come out of the emitter; this simulates the plate of a tube. The middle section is known as the *base* because, in the manufacture of the



## TV TIPS FROM TRIAD

NO. 10 IN A SERIES

"What gives with the schnorkel?," asked Bill as he examined the receiver on the bench. A four inch line of vent tubing angled up crazily and appeared to originate in the lower portion of the cabinet. A slight whirring sound suggested some kind of motor operating in the nether recesses.

"You are looking at the second power transformer I've installed in that set," answered Joe. "With everything normal it still smells after running for a couple of hours with the cabinet buttoned up. I thought the little fan on the phono motor might move enough air if I had the vent to direct it out of the cabinet. Well, it seems to help, but I can't put the back on, and you can hear the motor when the room is quiet. Looks like I need a power transformer that will give more watts without being one iota larger."

Neither Bill nor Joe had noticed Al, the parts salesman, enter, which was unusual, because Al was usually very noticeable, and today he was still exhibiting effects of the weekly sales meeting brainwashing.

"Just happen to have exactly what you want," said Al, "I looked over the shipment of new Triad power transformers with Triple X Steel," —he shifted smoothly into high gear— "and these transformers use the same size iron, so they fit, but because they're made of fine grade audio steel, we can design them to operate at a higher flux density and in many cases do not need heat dissipating fins to maintain safe temperatures—"

"Send me one," said Joe.

"—and since the efficiency of the steel is higher we do not require as large a stack, so our copper losses are lower—"

"I'm sold," said Joe.

"—and by utilizing a simple type of mounting bracket you can adapt the new series, even where the original had an unusual configuration —Oh, you'll take one? So soon? What's the matter? Don't want to learn anything?"

\* \* \*

**MORAL:** Sometimes a little "extra" in a replacement part will help make up for the effects of ageing in the receivers you service. If you would like to see for yourself how "Triple X" differs from the old "one grade better than stovepipe iron" drop us a line and we will be pleased to send you a sample. We will also include information on the new "Triple X" units. Write to **Triad Transformer Corporation**, 4055 Redwood Ave., Venice, California.

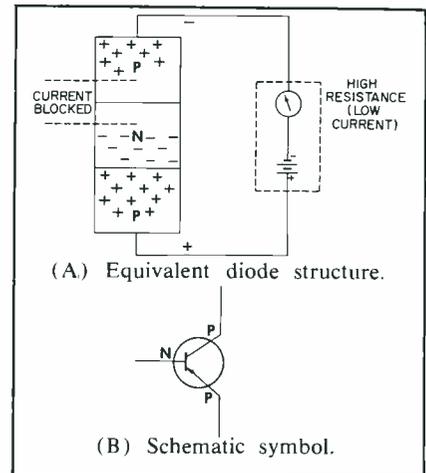


Fig. 8. Inside a PNP transistor.

transistor, it is usually made first, forming a base for the other two elements. The base in some ways acts like the grid in a vacuum tube, in that it controls the flow of current through the transistor.

In some schematics the emitter, base, and collector are labeled E, B, and C; in others, no letters are used. The emitter always has an arrow; the base is in the middle; and the collector is always at the end opposite the emitter, but contains no arrow.

When the emitter arrow points toward the base, the transistor is a PNP unit; when it points away from the base, it is an NPN unit.

### Conclusion

All things considered, transistors are really much more simple than vacuum tubes. Once you understand the basic principles, as outlined in this article, transistor circuit servicing should be a snap. ▲

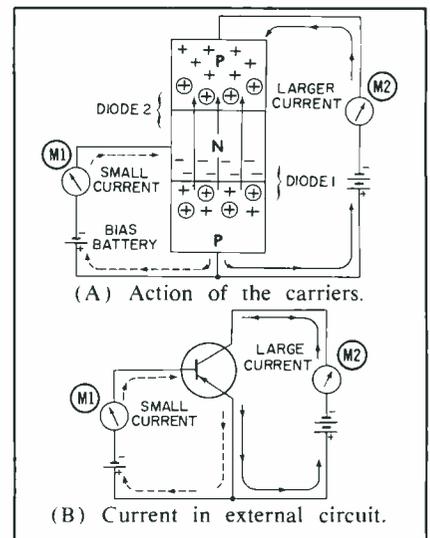


Fig. 9. Forward-biasing a PNP unit.

# ask YOURSELF

\* \* \* \* \*

## THESE Four QUESTIONS ABOUT BUYING OFF-BRAND SPEAKERS

### Can I Tell My Customers The Name Of The Speaker I've Installed?

Jensen is a name you can mention with pride and confidence. Jensen Viking and Weathermaster speakers benefit from the tremendous prestige of Jensen's HiFi lines.

\* \* \* \* \*

### Do I Pay More For Jensen?

No. You may find an off-brand "deal" occasionally, but you get consistent competitive year-round lowest cost and highest quality when you concentrate on Jensen.

### Can Off-Brands Give Me Proof Of Performance?

Jensen has designed every type of speaker for the military. Jensen speakers have been under the pole... and around the world—*outside* submarines. This know-how is a bonus extra in every Jensen speaker.

\* \* \* \* \*

### How About Availability?

Jensen speakers are stocked by fine jobbers and distributors everywhere. You can depend on replacements being available.



COMPARE OFF-BRAND ANSWERS TO JENSEN ANSWERS . . .

*. . . you'll find once again that there is something better from . . .*

**jensen** / MANUFACTURING COMPANY  
DIVISION OF THE MUTER CO. / 6601 S. Laramie Avenue, Chicago 38, Illinois

IN CANADA: RENFREW ELECTRIC CO., LTD., TORONTO • IN MEXICO: UNIVERSAL DE MEXICO, S.A., MEXICO D.F.





TAXICABS



CITIZEN'S AVIATION



BUSINESS



HIGHWAY PATROL



MARINE

# 5 NEW SOURCES OF SERVICE BUSINESS

You can qualify for them with new **Raytheon Communications Technician's Course**

There are over two million transmitters in the Safety and Special Radio Services now—and the number is expected to double each year. The opportunity for extra service business is endless, but . . .

Federal law requires an FCC license to service transmitting equipment. The Raytheon course assists in preparing you with the necessary technical background to take the FCC license examination through the following studies:

1. A review of electronic fundamentals
2. Typical circuits of two-way radio communications equipment
3. FCC rules covering laws and operating practices
4. Theory, operation, installation and maintenance of citizen's band equipment
5. Citizen's band frequency allocations, limitations, etc.
6. Frequency modulation theory
7. F/M techniques, detectors/discriminators, circuits

This is not a "cram" course just for the FCC examination but also includes exhaustive technical training that equips you to service two-way communications and allied industrial equipment as a practicing specialist.

Enrollment applications for this course necessarily involve an entrance examination to determine those qualified. On completion of course, you become a Raytheon Bonded Communications Technician, with diploma and merchandising aids to help you attract this new flourishing market.

Free Brochure and Application Papers—Mail Today

Send this coupon now for a booklet describing course and application for your entrance examination. Entrance exams will be graded as soon as received.

RAYTHEON COMPANY  
 DISTRIBUTOR PRODUCTS DIVISION  
 411 Providence Turnpike  
 Westwood, Mass.  
 Box No. 43

**GENTLEMEN:** Please send me your brochure describing the Raytheon Communication Technician's Course.

NAME \_\_\_\_\_ COMPANY NAME \_\_\_\_\_

ADDRESS OF DEALER \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_

DISTRIBUTOR'S NAME \_\_\_\_\_ ADDRESS \_\_\_\_\_



# RAYTHEON COMPANY

## DISTRIBUTOR PRODUCTS DIVISION

# Check the TECHNICAL ADVANTAGES you get in the RCA V-O-M with the Extras



- 20,000 ohms-per-volt meter movement
- Clearly marked db scales; no squinting to read results
- Special 1-volt and 0.25 volt (full-scale) ranges dc
- 3% accuracy on dc
- 5% accuracy on ac

See page 61 for the full story on this superlative value at only \$43.95\* \*User Price (Optional)

RCA Electron Tube Division, Harrison, N.J.



The Most Trusted Name  
in Electronics

RADIO CORPORATION OF AMERICA

the yoke and transformer primary.

3. The linearity coil is in series with the yoke and the damper tube between boost and B+.
4. The width potentiometer varies the voltage to the screen of the output tube and to the horizontal hold control.
5. The screen grid is bypassed to B+ through an .047-mfd capacitor and a portion of the width control, and also to the cathode through 100 mmf.

With these factors in mind, let's analyze the circuit from a servicing standpoint. The width control affects over-all picture width, since screen potential directly controls output tube conduction. If the tube's plate current increases, a stronger current pulse is passed through the yoke, and more scanning energy is developed. A defect in the screen-grid circuit will result in a narrow picture with acceptable linearity.

The linearity coil, being in the damper circuit, affects the left side of the picture. A defect in the linearity-coil circuit, therefore, usually results in distortion of the left side of the raster. An inactive linearity coil (its adjustment produces no significant changes in the picture) is almost always caused by shorted turns in the coil itself. A loss of capacitance in either of the .018 capacitors can reduce the effect of the coil.

The 4.7-mmf capacitor from the transformer tap to the yoke is a special high-voltage unit which should be replaced only with an identical part. Loss of capacitance in this unit can result in a loss of width, generally in such a way that normal width with good linearity cannot be achieved.

The oscillator circuit is affected by any changes in its load—which, in part, includes the output stage. Adjusting the width control produces a change in load, but this effect is compensated since the voltage to the oscillator-control (AFC) tube is obtained from the width control. Thus, adjusting the width control automatically changes oscillator conditions slightly to make up for the change in load.

Adjusting the drive trimmer also changes the load on the oscillator, and often makes it necessary to re-

adjust the horizontal frequency and waveform coils of the oscillator.

Since the screen grid is bypassed to B+ through part of the width control, a small amount of degeneration is built into the circuit. This is limited by the 100-mmf capacitor that bypasses the screen to the cathode. Slight blooming conditions that cannot be otherwise explained may be the result of a loss of capacitance in the 100-mmf component.

The yoke is a special unit which has low horizontal coil inductance (3 mh) and is subject to proportionately high pulse voltages. For this reason, extreme care must be exercised not to scrape or otherwise damage the insulation on the horizontal windings. Time, moisture, and the ravages of 3500-volt pulses will cause periodic failures in these yokes, but as a rule, they last for 6 to 8 years if ambient operating temperatures are reasonably low.

Any complete loss of sweep not due to a readily-detected open or short circuit condition (assuming correct functioning of the oscillator) may be caused by the boost capac-

## BERNS PERFECT PIN-CRIMPER

### Picture-Tube Repair Tool

*Eliminates that hard soldering job.*

**only \$1.25**



**Fix loose pin connections in seconds. Pays for itself in time saved on one job alone. 3" long.**


U. S. Pat. 2,878,698  
Canadian Pat. 592,702

Intermittent operation of picture tubes due to defective solder connections at socket pins is easily corrected through the use of the Berns Perfect Pin Crimper. Actually a 3-in-1 tool that can also be used as a channel-selector wrench and screwdriver, it serves to notch pins and element leads to provide solid electrical connections. Pin keeps its original form.

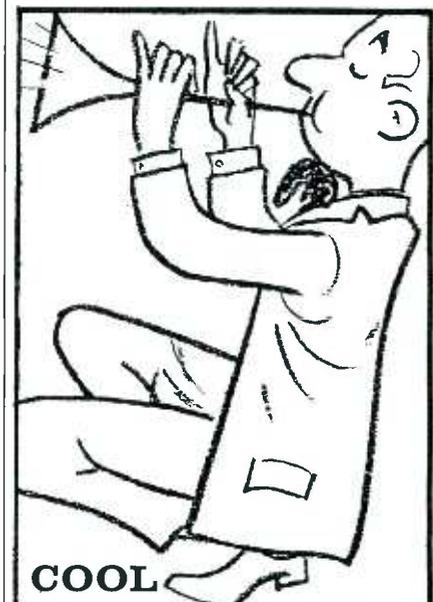**3 models: PT-1 for 3/32" pin diameter; AU-2 for 1/8" pin diameter and installing C rings; LC-3 for 5/32" pin diameter.**

Available at your parts distributor.  
Another fine product from:

**BERNS** Mfg. Co.  
9853 Chalmers,  
Detroit 13, Mich



**COOL**

**HEARD BY 13,798,831**

Duotone ads month after month in  
**NEW YORKER. THIS WEEK.**

Get the message? Customers right there in your home town do. Means more profits—more cool cash for you from

**DUOTONE** DIAMOND & SAPPHIRE NEEDLES  
KEYPORT NEW JERSEY

Makers of the first commercial diamond needle guaranteeing a natural whole gem every time

itors (.018-mfd, 1000-volt units). If you find it necessary to replace the boost filters, be sure the new ones have at least a 1000-volt rating to prevent callbacks.

### Portable CRT

Why is it that fate always picks your busiest day to make every set a shop job? And, wouldn't you know it, practically every chassis you pull has a cabinet-mounted CRT! You figure you can do without the picture tube, but to play it safe, you have to pull the yoke to operate the set on the bench.

If this is one of your problems, you'll be happy to hear about the *Tele-Check* now available from I.H. Mfg. Co., Inc.—a case-mounted 8" CRT complete with yoke and test leads. (The Model CR-168S, shown here, also has a universal test speaker and audio output transformer.)


While it uses a 110° check tube and yoke, it's versatile enough to work with sets having deflection angles from 90° to 114°. Of course, you'll run the gamut of picture sizes and distortions as you connect the unit to first one TV and then another. However, as long as you're interested only in whether or not you get raster and picture, it fills the bill nicely.

The unit is ruggedly constructed and flexible in application, so it's a handy thing to have along on "no-raster" home calls. If the trouble centers in something other than a tube or fuse, it's a simple matter to substitute the *Tele-Check* for the set's CRT and yoke. This will tell you if the yoke or CRT might be the cause of your trouble—thus saving you from pulling the chassis and then finding you've left the culprit in the cabinet!



# SEE
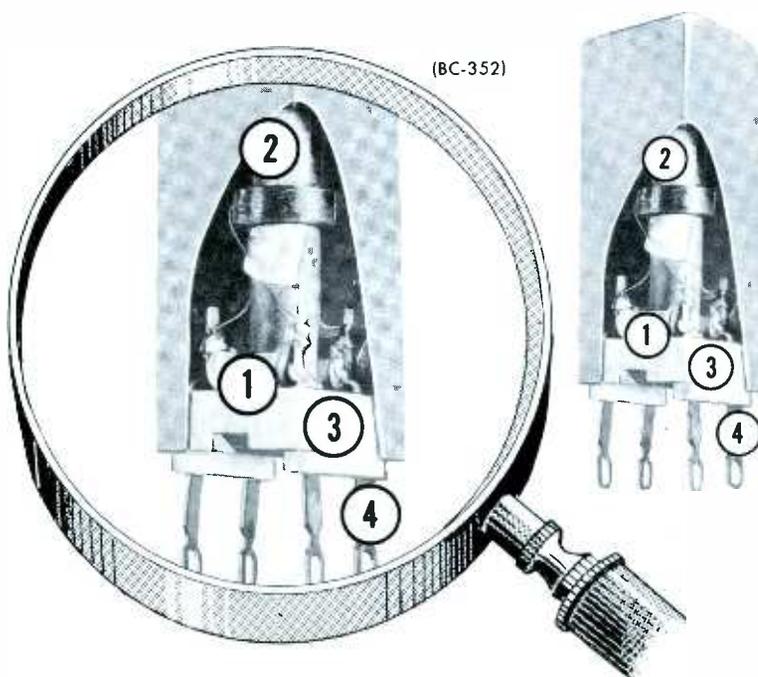
## Merit Quality! Look inside this I. F. Transformer!



1. Standard tubular capacitor instead of usual plate type. Assures optimum temperature stability—keeps Merit transformers within very close temperature drift limits. (Thermal coefficient over an extreme temperature range maintains stable capacity.)
2. Mylar tape for highest degree of insulation.
3. Ceramic base for high dielectric strength and minimum moisture absorption.
4. Printed-circuit lugs available.
5. Individually tested and pre-tuned to proper frequency under actual use conditions to assure many years of operation without failure.


**Merit**

COIL AND TRANSFORMER CORP.  
MERIT PLAZA • HOLLYWOOD, FLORIDA

You can ...

## PICK UP A HUMAN HAIR

with these  
precision-machined points

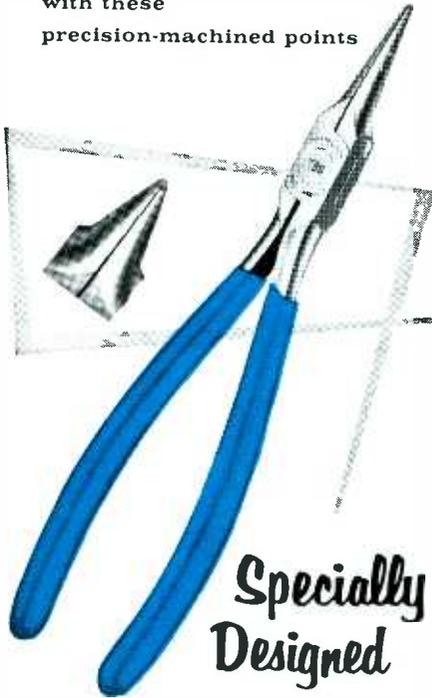

Specially  
Designed

**CHANNEL LOCK**<sup>®</sup>

No. 738 Long-reach

### Round-Nose Plier

A precision gripping tool for precision work . . . the CHANNELLOCK No. 738 Round-Nose Plier. Gives you a long slim, firm grip in tight places you can't reach with other pliers. Hundreds of uses on electrical, radio, TV, Hi-Fi and all other types of electronic work. Comfortable, blue-plastic grips. Top quality, polished forged steel. Ask your tool supplier for a CHANNELLOCK No. 738 Round-Nose Plier. If he's out of them, ask him to order one for you.



Write for Catalog of  
Complete Line of Pliers



#718 LONG-REACH FLAT-NOSE PLIER




#728 LONG-REACH DIAGONAL CUTTER


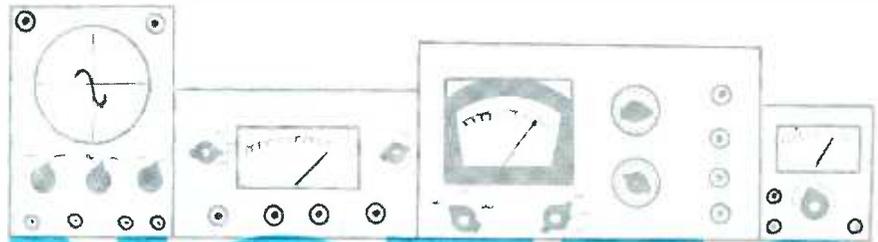
#748 LONG-REACH END CUTTER

Channellock Pliers are made only by

**CHAMPION DeARMENT TOOL COMPANY**  
Meadville, Pennsylvania



# NOTES ON TEST EQUIPMENT

by Les Deane

## Transistors Sound Off

The Parts & Accessories Div. of Motorola, Inc., Franklin Park, Ill. has recently introduced a new transistor tester. Pictured in Fig. 1, the instrument is completely self-powered and uses a built-in speaker as an indicator. It operates on a dynamic testing principle whereby an audible output quickly tells you whether a transistor is good or bad.

Specifications are:

1. *Power Requirements* — two self-contained 6-volt batteries (not supplied).
2. *Transistor Tests* — detects shorts, opens, or excessive leakage and measures relative gain of either power or small-signal types of PNP and NPN transistors; test results determined by output of audio oscillator circuit.
3. *Panel Features*—PNP-NPN selector switch, relative gain control, and 4-element transistor test socket plus separate plug-in test leads provided.
4. *Size and Weight* — 3" x 5 1/4" x 4"; 1 lb., 6 ozs. less batteries.

The instrument is housed in a small steel case with a metallic green finish. To install the necessary batteries, you merely remove six metal screws and separate the two "U" sections of the case. In addition to a standard transistor test socket, the front panel has three individual test jacks coded C, B, and E — corresponding to collector, base, and emitter. Test leads terminated with miniature alligator clips plug into these jacks and make it a simple matter to check transistors which cannot be plugged into the test socket.

To test a transistor, you simply flip the PNP-NPN switch to its proper position and, with the panel control fully counterclockwise, listen for an audio tone from the instrument's speaker. If a tone is clearly heard, the transistor is probably good—or at least is not shorted or open. To test for relative gain, the control is rotated slowly clockwise until a tone is no longer perceptible. The higher the setting reached, the higher the transistor's gain.

A leakage check is performed with

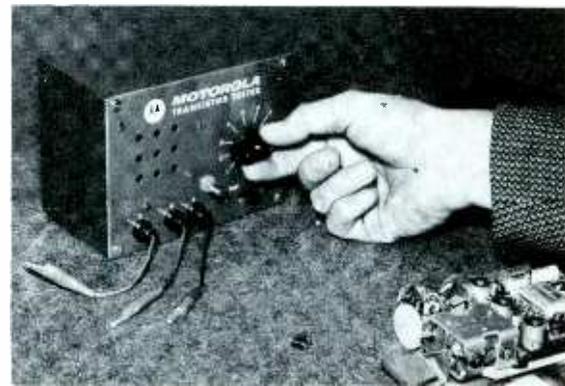


Fig. 1. Motorola's tester uses audio circuit for checking transistors.

the panel control in the maximum position that will still produce an audio indication. Position of the PNP-NPN switch is reversed for approximately ten seconds and then returned to normal. If you notice a change in pitch, or if a tone is no longer produced, the transistor is likely to have excessive leakage current.

I'm sure you'd like to know what makes the transistor under test "sound off," so let's take a look at the Motorola circuit in Fig. 2. The instrument evaluates the condition of a transistor by placing it in an audio oscillator stage. Variable control R1 permits manual adjustment of the oscillator feedback, and since the amount of feedback

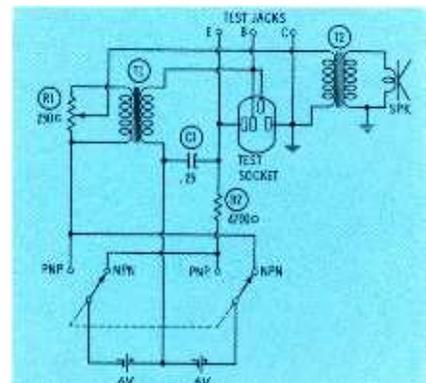


Fig. 2. Schematic of Motorola tester. Unit is powered by two 6-volt cells.

# RCA ELECTRONIC INSTRUMENTS

"PREFERRED BY PROFESSIONALS"

## METERS and TUBE TESTERS



### WV-38A VOLT-OHM-MILLIAMMETER THE V-O-M WITH THE EXTRAS!

Compare this superlative RCA V-O-M against the model you may have been thinking of buying. See if it doesn't check out better in these extra features:

- EXTRA! 1.0 volt and 0.25 volt ranges DC!
- EXTRA! Big easy-to-read 5 1/4" meter!
- EXTRA! Non-breakable plastic case; no glass to crack or shatter!
- EXTRA! Smart attractive modern styling—the V-O-M of the future!
- EXTRA! Red test lead has probe and slip-on alligator clip for added versatility!
- EXTRA! Orderly location of jacks below switches keeps leads out of the way!
- EXTRA! Spring clips on handle to hold test leads!

- EXTRA! DB scales clearly marked: no squinting!
- EXTRA! Rugged, scuff-proof, stain-resistant laminated vinyl carrying case, only \$4.95\* extra!

Only \$43.95\* complete with batteries, instruction book and all probes, clips and cables. (RCA V-O-M Kit only \$29.95\*.)



### NEW! WV-77E VOLTOHMYST®



Measures AC and DC voltages to 1500 volts; resistance from 0.2 ohm to 1,000 megohms. Separate scales, 1 1/2 volts rms and 4 volts peak-to-peak for low AC measurements.

Only \$43.95\* complete with probes, leads, instructions. (RCA VoltOhmyst Kit only \$29.95\*.)



### NEW! WV-98B SENIOR VOLTOHMYST®

Measures AC and DC voltages (3% accuracy); resistance from 0 to 1,000 megohms. Measures peak-to-peak values of complex waveforms. Rugged cast aluminum case, field-tested printed circuits. Big 6 1/2" meter.

Only \$79.50\* with leads, clips, instructions.



### WT-110A AUTOMATIC ELECTRON TUBE TESTER

Especially designed for TV and general service testing of electron tubes. Uses automatic punched-card selection of correct test conditions on wide variety of tubes. Checks vacuum-tube rectifiers under high-current conditions.

\$199.50\* complete with 263 punched cards, 24 blank cards, card punch; instruction book.


## SCOPES


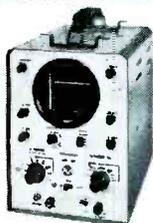
### WO-91A 5-INCH COLOR-TV OSCILLOSCOPE

High-performance, wide-band oscilloscope ideally suited for color-TV, black-and-white TV, and other electronic applications. Dual bandwidth (4.5 Mc, 0.053 volts rms/in. and 1.5 Mc, 0.018 volts rms/in.). Internal calibrating voltage and calibrated graph screen. Includes special direct/low-cap shielded probe and cable.

Only \$239.50\* complete with ground cable, insulated clip, instruction book.



### NEW! WO-33A SUPER-PORTABLE OSCILLOSCOPE

A low-cost all-purpose scope you can carry anywhere—only 14 pounds—ideal for in-the-home servicing of black-and-white and color-TV, audio and ultrasonic equipment. High gain and wide bandwidth to handle the tough jobs! Rugged and compact—scaled 3" graph screen.

Only \$129.95\* complete with low-cap direct input probe, cable, power cord, cord-carrying brackets, instructions. (RCA Super-Portable Oscilloscope Kit, only \$9.95\*.)

## GENERATORS



### NEW! WA-44C AUDIO GENERATOR

Generates sine and square wave signals for testing audio systems. Frequency range: 20 cps to 200 Kc. Used to measure intermodulation distortion, frequency response, input and output impedances, speaker resonance, speed of recording and playback mechanisms, transient response and phase shift.

Only \$98.50\* with cable and instructions.



### WR-69A TELEVISION/FM SWEEP GENERATOR

For visual alignment and troubleshooting of TV rf/lf/vf circuits and other electronic equipment. IF/video frequency ranges 50 Kc to 50 Mc, TV channels 2 to 13, plus FM range—88-108 Mc. Sweep width continuously adjustable to 12 Mc or more.

Only \$295.00\* with cables, instruction book.



### WR-99A CRYSTAL-CALIBRATED MARKER GENERATOR

To supply a fundamental frequency rf carrier of crystal accuracy for aligning and troubleshooting color-TV, black-and-white TV, FM receivers and other electronic equipment operating in 19 Mc to 260 Mc range.

Only \$242.50\* complete with output cable, two phone tips, instruction book.



### WR-49B SIGNAL GENERATOR

For alignment and signal tracing of AM/FM receivers, low-frequency signal tracing and alignment of TV vf/lf amplifiers. Six ranges—85 Kc to 30 Mc. Internal 400 cps modulation. Low rf signal leakage!

Only \$79.50\* complete with shielded cable for rf and af output, instruction book.



### WR-70A RF/IF/VF MARKER ADDER

To be used with WR-69A or similar electronic equipment. Eliminates waveform distortion due to receiver overloading during visual alignment by adding markers after the rf signal is demodulated.

Only \$74.50\* with cables, instruction book.

There's an RCA test instrument to help you do every job better, and easier—and to save you valuable time. A comprehensive line of test accessories: video multi-markers, TV isotaps and bias supplies, probes and cables. See your Authorized RCA Electronic Instrument Distributor for complete information.

RCA Electron Tube Division, Harrison, N.J.

\*User Price (Optional)



The Most Trusted Name in Electronics  
RADIO CORPORATION OF AMERICA

# WHICH of these 4 new books will help you most?



## INSTALLING HI-FI SYSTEMS

By Jeff Markell and Jay Stanton

Ideal for the technician who's in hi-fi professionally or as a hobby. Considers the various types of systems, tells how to avoid booby traps in setting them up. Discusses all the elements of a component system from an acoustic, esthetic as well as electronic view point. Valuable chapters on client relations, legal and insurance considerations. No. 86 - 224 pages. Paper bound. \$3.20



## PRACTICAL AUTO RADIO SERVICE & INSTALLATION—Transistor, Hybrid, FM & AM. By Jack Greenfield.

Covers all types. Tells you what equipment you need to set up a shop. Shows you how to install and remove sets, rear seat speakers, troubleshoot and repair speakers, tuners, power supplies. Covers FM, hybrids, all-transistor sets, auto phonographs. This one will help you build your business, increase your earnings. No. 87 - 160 pages. Paper bound. \$2.95



## PRACTICAL TV TROUBLESHOOTING

Some hot hints on how to get those piled-up tough ones off the bench. Work-tested techniques of some of the best technicians in the business on how to handle intermittents, ghosts, horizontal oscillator troubles, foldover, jitter and many other common and uncommon tough ones. A compilation of the best on TV servicing from the pages of *Radio-Electronics Magazine*. No. 102 - 128 pages. Paper bound. \$2.35



## TUBES AND CIRCUITS

By George Christ

An excellent book on the theory of electron tubes and their application in circuits. Considers basic electron theory, characteristics of simple and multiple element tubes, various tube types, gas tubes, photoelectric emission, and industrial applications. In helping the technician understand the fundamentals behind tube and circuit operation, this book enables him to analyze circuit troubles intelligently and correct them quickly and efficiently. No. 82 - 192 pages. Paper bound. \$3.45



On sale at distributors now — or buy direct. Order all four books.

GERNSBACK LIBRARY, INC. DEPT. PF 154 West 14th St., New York 11, N. Y.

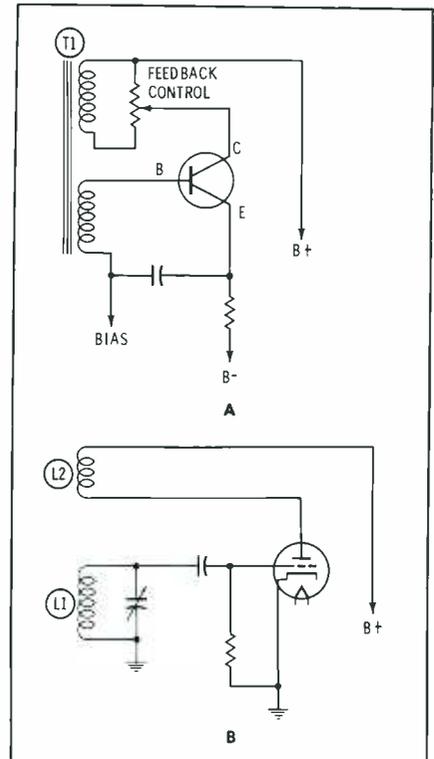


Fig. 3. Tester's basic oscillator circuit and comparable vacuum-tube stage.

necessary to sustain oscillation depends on the gain characteristic of the transistor, a relative indication is obtained by the control's setting. An output of the oscillator is sampled at T2 and reproduced by a 2" PM speaker.

A simplified schematic of the tester's oscillator circuit for an NPN transistor is shown in Fig. 3A. This common-emitter configuration might be compared to the more familiar oscillator stage of Fig. 3B. In the vacuum tube example, the amount of oscillator feedback is governed by the degree of inductive coupling between coils L1 and L2. This in turn depends on their physical proximity and the number of turns in each coil. The stage is tuned, of course, by adjustment of the variable capacitor in parallel with grid coil L1.

In the transistor circuit, feedback is made adjustable by a variable resistance that shunts the feedback winding of T1. Basically, both circuits of Fig. 3 are Armstrong oscillators; but in the untuned transistor stage, adjustment of the feedback control also causes the oscillator frequency to change. In a few cases where the feedback is reduced, the increase in frequency or pitch of the output tone may make it somewhat difficult to determine the setting at which oscillations cease. For example, I found that certain transistors may continue to produce oscillations, but at frequencies beyond normal hearing.

To check cutoff frequencies precisely, I monitored the tester's output on a scope; employing an audio generator as a reference, I used Lissajous patterns as a means of determining frequency. Cutoff frequencies for known good transistors I tested ranged from 5 to 20 kc. However, those of you unable to

HAMILTON

## RESISTORS YOU CAN'T RESIST!

Hamilton electronic components are supercharged with "SELL." When you think of resistors, think of Hamilton first because of:

- Quality Controlled Engineering
- Highest Grade Materials
- All Products 100% Guaranteed
- Sure-Fire Profits!

**FIXED COMPOSITION RESISTORS**

½ Watt  
1 Watt  
2 Watt

From 10 Ohms to 22 Megohms  
Made in U.S.A. Sold Bulk or Kits

**HAMILTON-HALL, INC.**  
227 N. Water Street, Milwaukee 2, Wis. BR 3-6460

## POWER TRANSISTORS

FOR GENERAL REPLACEMENT PURPOSES IN AUTO RADIOS, POWER AMPLIFIERS, FARM RADIOS, MARINE RADIOS, ETC.

*Individually packaged in a plastic see-thru box with instructions and cross-reference information.*

3 TYPES OF POWER TRANSISTORS THAT WILL REPLACE A LARGE MAJORITY OF TRANSISTORS IN USE TODAY

V176 LOW WATTAGE TYPE

V155 MEDIUM WATTAGE

V40 HIGH WATTAGE TYPE

---

## SILICON RECTIFIERS

FOR GENERAL REPLACEMENT PURPOSES

For use in radios, television sets, amplifiers or any electronic equipment presently using a tube, selenium or silicon rectifier.

*INDIVIDUALLY PACKAGED IN A PLASTIC SEE-THRU BOX*

500 MA  
200 P.I.V. TYPE  
PART No. SR-52

For use in all radios, phono amplifiers and electronic equipment where an RMS voltage of 140 volts or less is applied

500 MA  
400 P.I.V. TYPE  
PART No. SR-54

For use in all TV sets and electronic equipment where an RMS voltage of 280 volts or less is applied

**Vidair ELECTRONICS MFG. CORP.**  
365 BABYLON TPKE. — ROOSEVELT, N. Y.

detect tones above 13 or 14 kc needn't be concerned; the indications obtained are relative, and as long as only one person's hearing range is involved, they are suitable for all practical purposes.

When I compared a few of the tester's gain indications with actual beta measurements, I came up with the following:

Known Beta	Tester Setting
20	8
38	8.5
60	9
100+	9.5

The feature that impressed me most

about this unit was the simplicity of its test procedure. Even if you don't know whether the transistor to be tested is PNP or NPN, you won't damage either the transistor or the tester if you accidentally place the type switch in the wrong position. If you obtain no output on the first try, simply reverse the switch; an output should then be heard if the transistor is good. The switch position automatically identifies the class of transistor you are testing. The only thing you really have to know to operate the Motorola tester is the correct arrangement of element connections for different styles of transistors.



Fig. 4. In-circuit tester detects bad capacitors with low shunt resistance.

## A "Wink" at Faulty Caps

The piece of equipment shown in Fig. 4 is manufactured by the PACO Electronics Div. of PACOTRONICS, Inc., Glendale, Long Island. Designed to speed radio and TV troubleshooting, the Model C-25 In-Circuit Capacitor Tester has a built-in eye that "winks" whenever it encounters a shorted or open capacitor. The instrument is available in either kit or factory-wired form.

Specifications are:

1. Power Requirements — 105/125 volts, 60 cps; power consumption approximately 13 watts; transformer provides line isolation.
2. Shorts Test — detects shorted capacitors of all types "in-circuit"; positive indication obtained with

shunt resistances as low as 10 ohms.

3. Open Test—detects open capacitors "in-circuit" for all values down to approximately 7 mmf; special oscillator test circuit provided.
4. Value Test — approximate value of electrolytics measured "in-circuit"; capacitances of from 2 to 400 mfd tested in two ranges; accuracy determined by circuit's shunt resistance.
5. Size and Weight—7½" x 5¾" x 4¼", 6 lbs.

Trying out a Model C-25 in the lab recently, I found it exceptionally useful in isolating troubles caused by defective

capacitors—especially electrolytics. The instrument's most outstanding feature is that it permits you to check bypass, coupling, blocking, and filter capacitors without disconnecting them from the circuit, and with a relatively high degree of accuracy.

Reading over the test procedure in the PACO manual, I found the unit very simple to operate. After a brief warm-up period, you merely connect the clip leads of the shielded input cable across the suspected capacitor, place the function switch in the SHORT TEST position, and observe the tuning-eye indicator on the front panel. (By the way, the tuning indicator is one of the new rectangular-type eye tubes—an EM84.) If the capacitor is shorted, the eye will close. If the capacitor is not shorted, the eye will remain open—that is, provided the


*They're new! They're blue!*

MALLORY

**PVC**

MYLAR\*

CAPACITORS

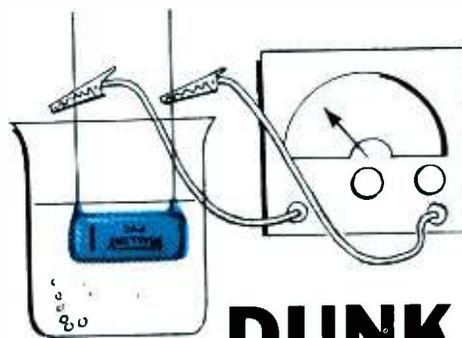

**DUNK 'EM**

The Mallory PVC stays moisture-proof. Dunk it . . . soak it . . . boil it . . . bend the leads or solder them . . . the flexible blue vinyl jacket never cracks or shrinks, never loses its moisture protection. It's truly a PLUS VALUE CAPACITOR.

Test-proved at 105°C at double voltage, the Mallory PVC is perfect for those tough jobs. It will never let you down. See your Mallory distributor for PVC five-packs . . . they're priced to please . . . 100, 200, 400 and 600 volt ratings in a wide range of capacities.

Distributor  
Division  
Indianapolis 6,  
Indiana



\*Registered Trademark of E. I. du Pont de Nemours & Co., Inc.

# electronic chemical

new formula

## EC-44

Economical! A little does a lot!

6 oz. spray can **\$3.50**

with 5" Plastic Extender Push Button Assembly FREE

lubricates conditions cleans all **ELECTRICAL CONTACTS**

Sold To Distributors Only

**ELECTRONIC CHEMICAL CORP.**  
813 Communipaw Avenue Jersey City 4, N. J.

## "Eliminates Soldering"

PERFECT *Audio*

# "PIN-PLUG" CRIMPER

SLIP WIRE IN "PIN-PLUG" INSERT IN TOOL AND SQUEEZE JOB IS DONE

USE END OF BLADE AS SCREWDRIVER

U. S. Pat. 2,878,698  
Canadian Pat. 592,702

USE END OF TOOL TO PUSH ON GROUND CONNECTOR

Useful in making hi-fi, audio and sound, radio, phone, and TV equipment connections.

only **\$1.25** C-rings 1c each

Get the tool that makes solid electrical pin-plug connections without soldering or destroying pin form. Use one end for pin crimping, the other to push on C-ring clamp for braided-shield ground connection. Nothing like it anywhere.

3 models: PT-1 for 3/32" pin diameter; AU-2 for 1/8" pin diameter and installing C rings; LC-3 for 5/32" pin diameter.

Available at your parts distributor.  
Another fine product from:

**BERNS** Mfg. Co.  
9853 Chalmers,  
Detroit 13, Mich

shunt or parallel resistance of the entire circuit is 10 ohms or above.

Incidentally, before making any of the in-circuit checks, you must remove power from the equipment and properly discharge the capacitor or capacitors to be tested. This protects the Model C-25 as well as yourself.

The block diagram of Fig. 5A illustrates the basic operation of the instrument during a shorts test. The 6.3 volts AC derived from the internal power supply develops a predetermined grid and plate potential on the 6C4 amplifier. The plate voltage of this stage, in turn, controls the potential on the input grid of the eye tube. Under normal conditions (with test leads either open or connected across a good capacitor), the tuning-eye remains open.

When a capacitor with a short of 10 ohms or less is connected across the test leads, the grid potential on the 6C4 will drop to zero. This causes the 6C4 current to decrease, and its plate voltage to rise. Since the plate circuit of the amplifier is connected to the input of the following stage, grid voltage on the eye tube increases, thus increasing its plate current and closing the eye. Experimenting with this test, I found that a capacitor with a short as high as 50 ohms will cause the eye to close partially. Therefore, whenever the eye starts to close in a circuit with fairly high shunt resistance, the capacitor may be leaky.

To check for an open condition in a capacitor, the test leads are again connected across the component in question, and the function switch is advanced to the OPEN TEST position. Provided the unit under test has a value of at least 7 mmf, the eye will remain open if the unit is good. If the capacitor is open, the eye will close.

The open test is illustrated in Fig. 5B. In this application, the 6C4 functions as a high-frequency oscillator. Its circuit employs an inductive feedback arrangement which takes into account the standing-wave properties of the input test cable. The cable leads effectively shunt the oscillator feedback coil, but when the ends of the cable are shorted (or connected across any good capacitor with a value not less than 7 mmf), feedback in the circuit is sufficient to sustain oscillations. Under these

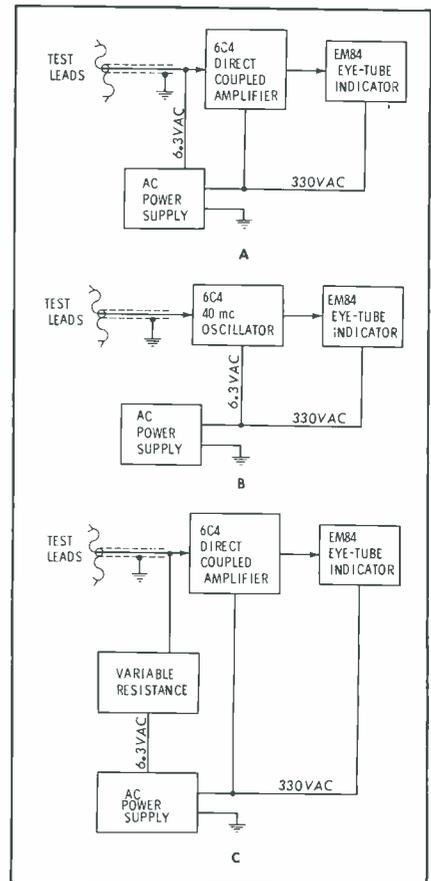


Fig. 5. Functional diagrams for the basic capacitor tests of Model C-25.

conditions, oscillator plate voltage holds the eye open.

When an open capacitor is connected across the end of the cable, the open line acts as a short across the feedback coils; this is because the length of the cable represents exactly one-quarter wave at the oscillator frequency of 40 mc. The resulting voltage-cancellation effect reduces feedback and, in turn, lowers oscillator grid voltage. As described in the shorts test, a drop in grid voltage and corresponding increase in plate voltage causes the eye to close.

The special test for electrolytics is intended only to reveal approximate in-circuit capacitance. The function switch is placed in either its third or last position, depending on the coded value of the capacitor tested. With the test leads

# TV TUNERS

\* REBUILT OR EXCHANGED

ALL TYPES

**\$9.95** including parts and labor  
(broken parts at our cost)

- Normally shipped same day received
- 90 day full guarantee
- U/V combinations \$17.95

FREE—!! Mailing carton sent to you on request

Phone REpublic 3-9189

**L. A. TUNER EXCHANGE**  
4611 West Jefferson Blvd.  
Los Angeles 16, California

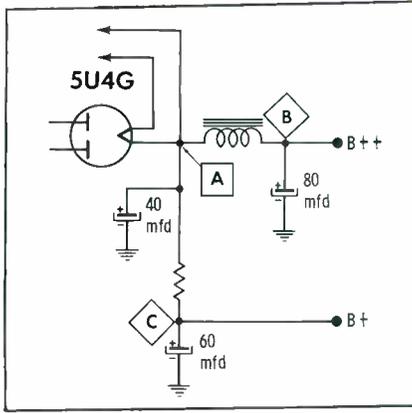


Fig. 6. Circuit used to check tester's ability to indicate capacitance values.

connected to the capacitor terminals, the capacitance dial on the front panel is adjusted for a minimum eye opening. The control dial is calibrated in mfd, and its setting indicates the in-circuit value of the electrolytic tested. Accuracy of these readings is determined mainly by the shunt resistance involved. Satisfactory shunt values for all capacitance ranges are listed in the instrument manual.

A block diagram of the electrolytic-measuring circuit is shown in Fig. 5C. Here, the 6C4 is again employed as a direct-coupled amplifier; its grid potential is determined by a divider network composed of a variable resistance and the capacitor under test. The 6.3 volts

from the power supply is developed across this network to ground. Voltage appearing across the capacitor is applied to the grid of the 6C4; since the voltage increases as capacitance decreases, the variable resistance (capacitance dial) must be increased to maintain the grid at a level which closes the eye. The variable resistance, which is a dual potentiometer, is calibrated in capacitance. On the lower electrolytic scale (2-40 mfd), both resistive elements are employed; on the higher scale (40-400 mfd), one dual section is

shorted out to compensate for the lower impedances offered by the capacitors in this range.

When I used this measuring technique on some actual equipment, I was truly amazed at the results. In the typical TV power supply circuit of Fig. 6, for example, I obtained a reading of 40 mfd at point A; 70 mfd at B; and slightly over 60 mfd at point C. Quick and easy measurements such as this can certainly help save a lot of time in pinpointing electrolytics which have drastically changed in value.

## "Mighty Mite"

The "Mite" in this title refers to the compact, lightweight tube tester in the photograph of Fig. 7. The unit is "mighty" handy for the radio and TV serviceman, because it offers all of the basic tube tests with a simple and speedy setup procedure. The Model TC109, nicknamed the *Mighty Mite*, is one of the newest in the line of time-saving instruments produced by SENCORE of Addison, Ill. The tester features a removable chassis which can be permanently or temporarily mounted as desired.


Specifications are:

1. Power Requirements — 110/120 volts, 60 cps; power consumption less than 5 watts in standby.
2. Tube Tests — checks over 1300 types, including 12-volt auto-radio tubes, for shorts, cathode emission, gas, grid emission, and grid leak-

age; results indicated on two GOOD?-BAD scales and a relative numerical scale, plus a neon panel lamp; heater-to-cathode leakage sensitivity 50K ohms; questionable grid leakage represents somewhat less than 200 megohms.

3. CRT Test—picture tubes checked for shorts and emission; standard test socket and cable supplied.
4. Other Features—3½" D'Arsonval panel meter; six panel-mounted test sockets; 12-position selector provides heater potentials from 1 to 50 volts AC; two pin straighteners for miniature tubes; special enclosed inner chassis; stainless steel mirror in lid.
5. Size and Weight — case, 9½" x 8¾" x 3½", 8 lbs.; removable chassis only, 9" x 7½" x 2¾", 4 lbs. (approx.).

All new...all blue...

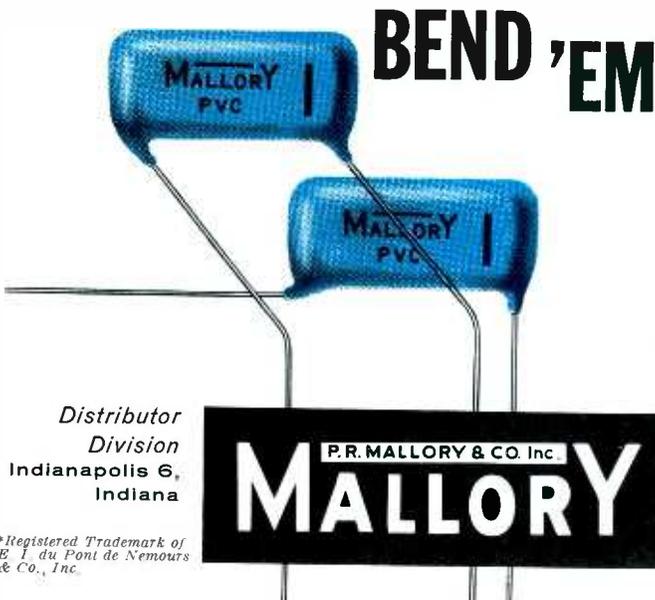

Bend those Mallory PVC leads to fit that tight spot . . . go ahead, the flexible, moisture-proof blue vinyl jacket won't crack . . . never loses its perfect seal. The PVC is a PLUS VALUE CAPACITOR . . . never lets you down.

Ideal for printed circuits, the PVC is test-proved for 105°C operation at double voltage. Popular-priced PVC's are available from Mallory distributors in handy five-packs . . . in a wide range of capacities and ratings of 100, 200, 400 and 600 volts.

★ INCREASE YOUR EARNINGS

★ ASSURE YOUR FUTURE

# NOW you can learn 2-way radio servicing at home from Motorola

NOW, for the first time, a home study course devoted exclusively to 2-way FM radio servicing.

The MOTOROLA TRAINING INSTITUTE trains you for a professional career with unlimited potential. The booming 2-way radio market should triple in the next 10 years. Qualified servicemen are urgently needed!

The Motorola Training Institute course of 38 lessons covers the entire field from basic principles to the more complex components and circuitry. Even the newest transistorized equipment is covered in detail.

## HERE'S WHAT STUDENTS SAY ABOUT THE MOTOROLA TRAINING INSTITUTE COURSE

"Even with a past background in 2-way radio servicing as a service station operator, I find the course has already been a definite help." (R.M.—Maine)

"Although I have an FCC license and some experience as a technician, I did not have a good working knowledge of the squelch circuit. Now, through my Motorola Training Institute training, I am able to do a decent troubleshooting job." (P.C.—Indiana)

"Personally, I think any technician that does not sign up for this course is missing a good opportunity to ease his servicing problems." (N.V.—New Jersey)

**Not for beginners, but for students with a background of basic electronics, the Motorola Training Institute course costs only \$95.00 including texts.**

Write today for complete information plus FREE text lesson taken from course.

**MOTOROLA**  
TRAINING INSTITUTE

4501 Augusta Blvd., Chicago 51, Ill.

Please send me complete information on the MOTOROLA TRAINING INSTITUTE No. PF-149.  
(please print)

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ ZONE \_\_\_\_\_ STATE \_\_\_\_\_



**NEW TECHNICIANS:** Learn in just a few months what could take years. Course prepared by experienced faculty and highly skilled technicians. Easy-to-grasp lessons—reference library—individualized instruction.



**RADIO SERVICE MANAGERS:** The Motorola Training Institute home study course is your answer to the problem of qualified servicemen. Add new efficiency to your staff by teaching them the right way to perform vital 2-way radio maintenance.



**EXPERIENCED TECHNICIANS:** Learn advanced servicing techniques and technological improvements. Get new information and know how on all the new transistorized equipment. An excellent "brush-up" course.



**SERVICE STATION OPERATORS:** Cut down on valuable time you spend training inexperienced technicians by enrolling them with Motorola Training Institute . . . key experienced technicians also benefit greatly.



Fig. 7. SENCORE'S Model TC109 features a highly sensitive grid-leak test.

Experimenting with the *Mighty Mite* and employing it in some practical applications, I found it quite useful in catching tubes having hard-to-detect faults. The first thing I noticed when I fired up the tester was a special pilot lamp that illuminates the test sockets, controls, and meter. This feature is convenient when troubleshooting in dimly lit areas such as behind a TV set in a customer's home.

Aside from the function selector which enables you to choose the test desired, there are only four setup knobs on the front panel. These are labeled A, B, C, and D; each is positioned in accordance with the listings in the accompanying data charts. Since there are two octal and two miniature test sockets provided, the charts also designate the socket to be used for each tube.

Several accessory or auxiliary features of the Model TC109 are pointed out in Fig. 8. The tube data booklet, together with a test socket for picture tubes and a top cap lead, is housed in a small dual compartment at the top of the panel. The setup data is contained in a small ring-type binder to permit the addition of new pages. (SENCORE provides free listings of new tube types to purchasers of the TC109.)

Ease of operation and portability make the instrument ideal for rental to do-it-yourself fans. In addition, since the chassis and control panel is, in itself, a complete assembly (see Fig. 9), it can be used for custom installations in tube caddies, service bench panels, sales counters, etc.

When putting the Model TC109 to work in the lab, I tried to "trip up"



Fig. 8. A number of "extras" are found on the new *Mighty Mite* tube tester.

the tester by throwing a few curves at it. Using my prized collection of rejected tubes that have mostly "tough dog" defects, I proceeded with the tests given in the SENCORE instructions. Results are as follows:

*Tube:* 6BG6G with known good emission, no gas, but intermittent short.

*TC109:* Emission, grid leakage, and shorts tests all checked out good; however, when I tapped on the tube and rotated the element-selector switch, a momentary short was revealed by the neon indicator on position H-K. This immediately pointed to an intermittent heater-to-cathode short.

*Tube:* 50C5 which was known to be gassy.

*TC109:* Emission tested good, and no shorts were indicated. In the grid leakage test, however, the meter needle registered in the BAD area. This test apparently detects leakage resistance, grid emission, or gas.

*Tube:* 1B3GT known to be weak (low emission).

*TC109:* After the tube passed the shorts test, which incidentally may differ for various brands, I made sure the meter was calibrated and performed the emission test. The needle came to rest right on the line dividing the question mark area and the region labeled GOOD.

*Tube:* 6BZ7 with grid-to-cathode leakage in one triode section.

*TC109:* Emission checked okay, no shorts were indicated, and the grid



**Fig. 9. Mighty Mite chassis slips out after four screws have been removed.**

leakage test produced a good reading—for the first few moments of the test. After checking leakage in the faulty section for about 30 seconds, the meter reading slowly crept into the BAD area.

*Tube:* 6AU6 known to develop excessive gas when sufficiently heated.

*TC109:* Initial tests revealed the tube to have good emission, no shorts, and also a satisfactory leakage reading. Since I knew the *Mighty Mite* could detect gas, I accelerated warm-up time by advancing the heater-selector switch one position. It would normally take this tube about four minutes to develop trouble in its original circuit. After only two minutes, however, I noted that the meter needle started to climb up the grid-leakage scale. Returning heater voltage to normal, I found that the reading reached almost full


scale after 6 minutes of operation. This one is tough to spot, for even after the gas develops, the tube will still pass the emission and shorts tests of many instruments.

*Tube:* 35Z5 with one section of its filament open.

*TC109:* The test circuit failed to light the tube at all, immediately tagging it as bad. I have found that some testers, even elaborate types, will check this tube as good in an emission test. The only clue is that in a shorts test, a short will not be indicated on pin 2 as it should be. This can be easily overlooked, especially if emission is measured first.

To me, these experimental tests proved some points many of us fail to realize. It boils down to the fact that there's "tube checking" and there's "tube testing." When merely checking a tube, one may go through the mechanics of operating the instrument and then rely on immediate results without question.

When properly testing a tube, however, one should consider the trouble symptoms involved and how they might affect testing techniques. Most of us do this subconsciously. If we're out to find possible causes for an intermittent condition, a slow warm-up problem, or a trouble that could stem from excessive gas, we perform various tests accordingly. There's more to using a tube tester than meets the eye, and this is where the competent technician has it all over the do-it-yourselfer. ▲

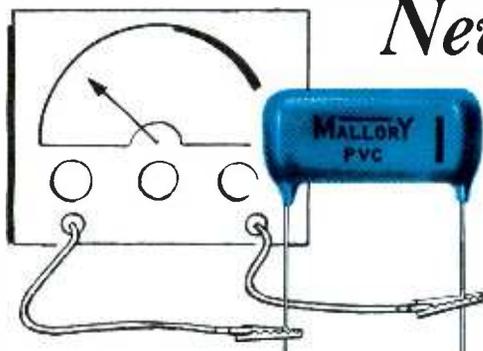

## OVERLOAD 'EM

The rugged, all-new Mallory PVC will operate at 105°C and twice its rated voltage—without de-rating. This test-proved, no-sacrifice performance is typical of the PVC. It's drift-free, too . . . and tolerance is  $\pm 10\%$ .

Flexible vinyl encapsulation keeps the PVC moisture-proof. Dunking won't change its perfect seal; neither will sharp bending of the leads for mounting in tight spots. See your Mallory distributor for this *Plus Value Capacitor* . . . popularly priced . . . in the handy five-pack. 100, 200, 400 and 600-volt ratings.

## New... Blue...

MALLORY

PVC

MYLAR\*

CAPACITORS


Distributor Division  
Indianapolis 6, Indiana

P. R. MALLORY & CO. Inc.

MALLORY

\*Registered Trademark of E. I. du Pont de Nemours & Co., Inc.

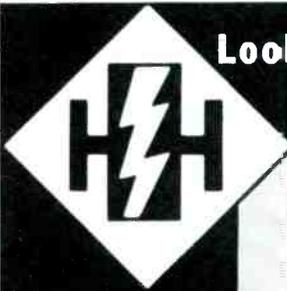
\*Registered Trademark of E. I. du Pont de Nemours & Co., Inc.



**Look for the I. H. Mark of Quality**

**IT MEANS "DOUBLE ASSURANCE" FOR YOU!**

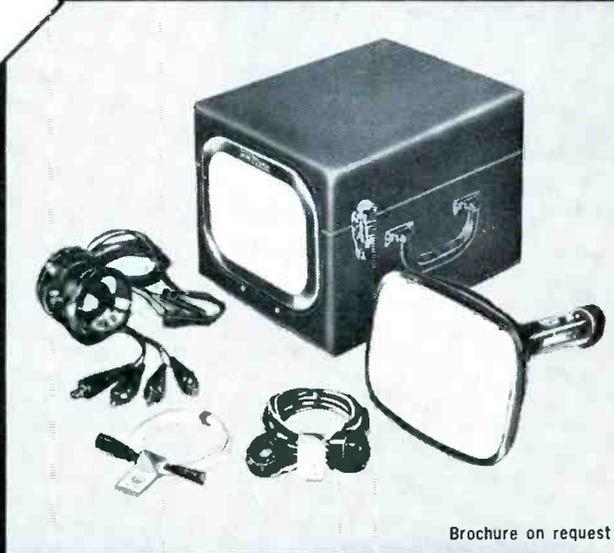I. H. Mfg., with its resources as the subsidiary of one of the leading manufacturers of OEM hardware — now makes a natural progression into the electronics distribution industry, with the assets and know-how of the former TELEMATIC line. It's your double assurance of superb product precision, tested performance, and "long" profits — down the line.



Brochure on request

## 8" TELE-CHECK

Now available for Both 90° and 110°

CRT Test Tubes

**I. H. MFG. CO.** — "the mark of quality"

Subsidiary of Industrial Electronic Hardware Corp.  
121 Greene Street — New York 12, N. Y. • ORegon 7-1881

Export: Roburn Agencies, 431 Greenwich St., N.Y. 13 • Canada: Active Radio & TV, 58 Spadina Ave., Toronto

## CLOSE INSPECTION

*Made Easy*

with the INSPECTOR



New magnifying lamp designed for miniature assembly work, quality control inspection, bench work, etc.

- Shadow free fluorescent light
- 5" precision polished magnifying glass
- On-the-arm action
- Choice of colors and mounts
- Exclusive electric base outlet (optional extra)
- Other models available

**DEALER AND DISTRIBUTOR INQUIRIES INVITED**

For free literature on the complete line of lamps for professional and industrial uses, write to:

Model M1  
**\$3600** List  
(45" arm reach)  
Less Bulb

**Swing-O-Lite**  
INCORPORATED  
13 MOONACHIE ROAD HACKENSACK, N. J.

## all new edition

up-to-date  
component prices

**PLUS**  
the quick easy way  
to figure service charges  
**EQUALS**



*Dave Rice's*

## OFFICIAL PRICING DIGEST

VOL. 4, NO. 1




Flat rate and hourly service charges, based on and showing regional and national averages, plus up-to-date list or resale prices on over 63,000 components. Arranged alphabetically by manufacturers and products, numerically by part number. Compact, convenient size fits in tube caddy, toolbox or pocket. \$2.50 per copy from your distributor.

**ELECTRONIC PUBLISHING COMPANY, INC.**  
180 N. WACKER DRIVE, CHICAGO 6, ILL.

## Transistor Testers

(Continued from page 24)

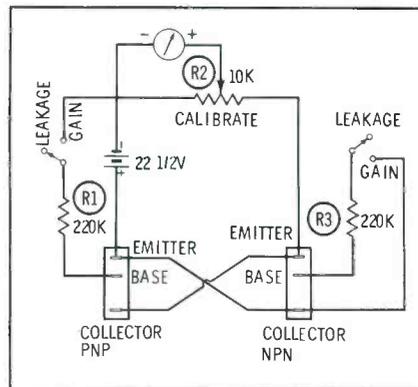

**Fig. 4. Simple circuit gives relative readings of gain and leakage currents.**

device will be revealed by an excessive flow of current.

The leakage current measured by the circuit of Fig. 2 is identified as  $I_{CEO}$ . The first two subordinate letters indicate that the powering circuit is connected between collector and emitter, while the letter o means that the remaining element (in this case, the base) is open. The amount of current normally produced in the  $I_{CEO}$  measurement is sufficient to actuate a milliammeter, which is convenient because it permits a relatively inexpensive movement to be used.

The second leakage test is the  $I_{CBO}$  measurement, which involves use of the circuit in Fig. 3. The battery, meter, and current-limiting resistor are connected between base and collector, and the emitter is left open. Since the base-collector diode is reverse-biased, only a very small current should flow—considerably less than obtained in the  $I_{CEO}$  measurement. To measure  $I_{CBO}$  properly, a microammeter is required; because these are considerably more expensive than milliammeters, the more economical testers skip this measurement and perform only the  $I_{CEO}$  test. This is generally acceptable, because the two quantities are related.

### Gain Tests

If the transistor passes the leakage test, it is ready for the gain test. For this purpose, nearly all transistor testers utilize the beta test, in which a small current is introduced into the base circuit and the corresponding effect on the collector current is indicated. This gain test is preferred because most

transistor applications use a common-emitter arrangement, with the incoming signal applied to the base, and the output signal obtained from the collector. While it is also possible to apply the incoming signal to the emitter and obtain the output signal at the collector, considerably higher current and power gains can be obtained with the first arrangement.

There are a variety of ways to perform the gain test. One of the simplest involves use of the circuit in Fig. 4. It performs two tests, leakage (ICEO) and gain. With a transistor in the appropriate socket, the LEAKAGE-GAIN slide switch is moved to the GAIN position, and the calibration control is rotated until the meter indicator is at full scale. The slide switch is then permitted to return to the LEAKAGE position, and the meter reading is noted. If the reading is less than full scale, it can be assumed that the transistor is satisfactory; the greater the difference between the LEAKAGE and GAIN reading, the better the transistor.

Let's examine what is being done here in more detail. When a transistor is inserted in the test socket

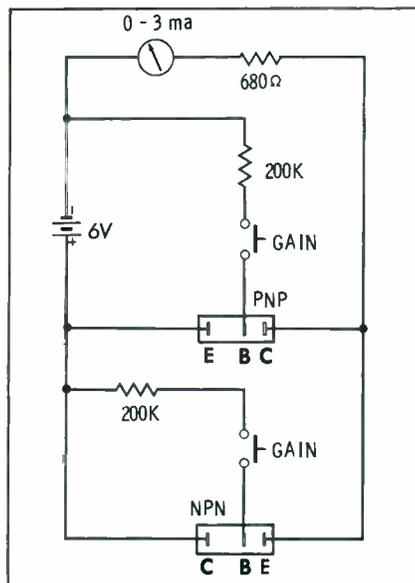


Fig. 5. Approximate value of beta can be computed from the meter reading.


and the LEAKAGE-GAIN switch is moved to the GAIN position, the calibration control arbitrarily sets this gain at full scale. This is done for all transistors, irrespective of what their true gain may be. When the circuit is returned to the LEAKAGE position, the base circuit of the transistor is opened and only the circuit between emitter and col-

lector is complete. In other words, ICEO leakage current is being measured as a percentage of gain current. Note that this circuit does not directly measure beta, but indicates the difference between beta and leakage.

A similar approach with a slight variation is employed in the circuit of Fig. 5. Separate push buttons are used for NPN and PNP transistors. With a PNP unit in the proper socket, leakage is measured with the base open; a positive voltage is applied to the emitter and a negative voltage to the collector through a suitable meter and current-limiting resistor. This duplicates the hookup in Fig. 2, which measures ICEO. If the leakage current is within limits, as indicated on the leakage scale, then the gain button is depressed. This connects a 200K-ohm resistor between the negative terminal of the battery and the base, supplying approximately 30 ua to this element. If the transistor can provide any gain at all, a larger current should flow in the collector circuit and be indicated by the meter. If we provide ten divisions on the gain scale, and use a 3-ma
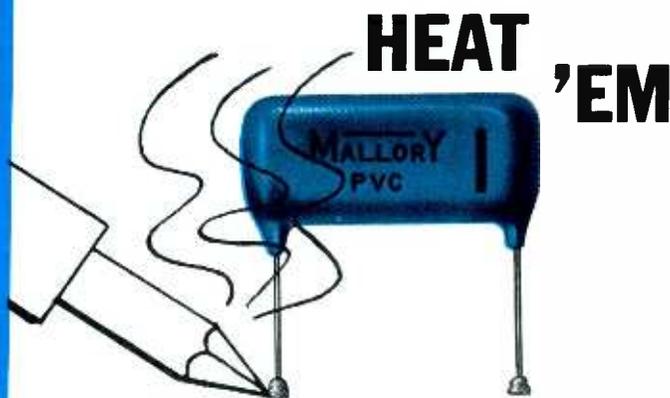
## New and Blue

**MALLORY**  
**PVC**  
**MYLAR\***  
**CAPACITORS**



P.R. MALLORY & CO. Inc.  
**MALLORY**

Distributor  
 Division  
 Indianapolis 6,  
 Indiana

\*Registered Trademark of E. I. du Pont de Nemours & Co., Inc.

Soldering heat won't damage the moisture protection of the all-new Mallory PVC—the Plus Value Capacitor. Its bright blue vinyl jacket actually tightens its grip when leads are soldered . . . stays flexible in high heat or below freezing . . . never cracks when leads are

sharply bent for mounting in tight, hard-to-reach spots. Your Mallory distributor carries the new, blue PVC . . . at popular prices . . . in a wide range of capacities at 100, 200, 400 and 600-volt ratings. Handy five-pack keeps leads free from kinks.

Eliminate call backs...  
use dependable,  
industry-preferred...



**3 WATT SIZE**  
5/16" x 1/4"

**5 WATT SIZE**  
1 1/16" x 1 1/32"

**AXIAL-LEAD RESISTORS**  
Vitreous-enameled, power-type, axial-lead units designed to withstand high temperatures.

**LITTLE DEVIL® COMPOSITION RESISTORS**  
Meet all MIL-R-11A requirements. Available in 1/10, 1/4, 1/2, 1, and 2-watt sizes in all standard EIA values.

**BROWN DEVIL® RESISTORS**  
Vitreous-enameled. In 5, 10, and 20-watt sizes.

**TYPE AB POTENTIOMETERS**  
Resistance material is solid-molded, noise-free. Rated at 2 watts.

**FR-75 FUSE RESISTOR**  
For easy replacement in many television receivers. 1 1/2" Tinned wire leads.

WRITE FOR STOCK CATALOG



OHMITE MANUFACTURING COMPANY  
3644 Howard Street • Skokie, Illinois

movement, one division will be equivalent to 300 ua. If we divide this 300 ua by the 30 ua fed to the base, a gain figure of 10 is obtained.

While the actual beta value of the transistor under test may not be indicated directly, knowing how this circuit operates makes it possible to arrive at the approximate value of this characteristic. This, however, is up to the ingenuity of the instrument user. Most inexpensive testers provide only an approximate indication of the beta value, which usually narrows down to whether or not leakage is within acceptable limits and gain is obtainable.

Fig. 6 uses the same basic circuit for checking ICEO leakage current, but another approach is taken in obtaining the gain measurement. A 6-volt battery is connected between emitter and collector. (A panel switch reverses polarity according to the transistor type.) Potentiometer R1 is connected across the battery, its center arm going to the base through 47K-ohm resistor R2. R1 is calibrated from 0 to 100 on the control panel, and the instructions specify settings which provide a mid-scale meter reading for all common transistor types. Thus, for any given normal transistor, R1 is set so that 1.5 ma flows in the collector circuit, deflecting the needle to the midpoint on the scale. If a transistor brings the needle to rest within the middle third of the scale, its gain can be considered satisfactory. However, a reading below center indicates lower-than-normal gain, and a reading above the center line indicates higher-than-normal gain.

Any transistor falling below the middle third of the range should probably be replaced. Any transis-

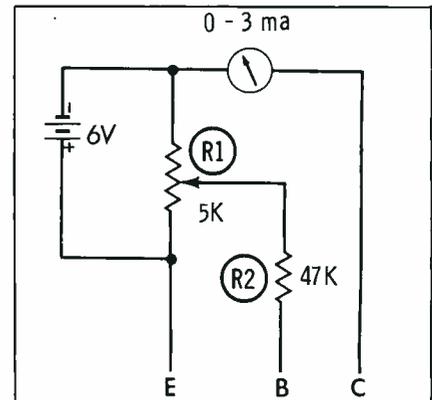


Fig. 6. Transistor's gain is checked against average value for same type. tor which moves the needle above the middle third is obviously better than normal, provided its leakage is acceptable.

Notice that the test circuit of Fig. 6 does not actually indicate the beta value of the transistor under test. It does, however, provide a means of comparing the tested transistor's performance in accordance with predetermined average values. Thus, the information is somewhat more specific than that obtained with the other two circuits. In the circuit of Fig. 4, only a general indication of performance capabilities is determined. The circuit of Fig. 5 gives a somewhat closer indication of leakage and gain. In this case, if the needle moves only one division in the gain test, a beta of 10 is indicated. If the normal beta for the transistor is 50, obviously 10 is not very good. Using the circuit of Fig. 6, evaluation is possible without the necessity for mathematical computation.

In the January column, we will delve into several of the more complex transistor test circuits. In addition, a chart listing the currently available commercial testers will be included. ▲

PHONE ED 9-9653

**\$7.50**  
plus parts,  
C.O.D. and postage charges

**90 DAY WARRANTY**

**Precision Tuner Service**


ALL TYPES T.V. TUNERS REPAIRED AND ALIGNED TO FACTORY SPECIFICATIONS ON CRYSTAL-CONTROLLED SWEEP GENERATORS  
24-HOUR SERVICE ON MOST TUNERS  
UHF - VHF COMBINATIONS — \$13.50

See your local distributor or send to:  
P.O. Box 272, 601 N. College  
BLOOMINGTON, INDIANA

State make and model. Send all parts, tubes and shields

## Magnetic Amplifiers

(Continued from page 26)

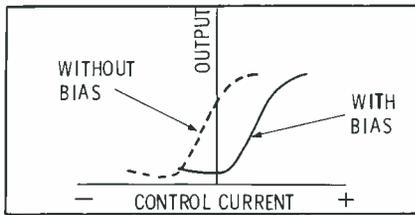

**Fig. 4.** To keep flux unidirectional, bias is added to AC control current. the solid-line curve. Then, even when an AC control current is added to the bias, the direction of the flux does not change — only its magnitude. The effect is similar to that of vacuum-tube bias, which keeps the control grid negative even with an AC signal applied. The use of bias in magnetic amplifiers is called *flux reset*. If desired, the bias could be applied in the opposite direction to move the curve of Fig. 4 to the left instead of the right. Operation would be the same in either case, except that the control magnetization would be in the opposite direction.

Bias may be applied to the control circuit by means of a separate winding on the control leg of the core, or directly to the control coil along with the AC signal.

Feedback windings may also be wound on the control leg of the core to alter certain amplifier characteristics. The feedback signal is obtained from the output, just as in tube circuits. Positive or in-phase feedback causes the stage to be more sensitive, giving higher gain. However, in some cases, instability and nonlinearity may result, and the time lag of the unit is increased. (The latter occurs because feedback alters the L/R time constant which determines the degree of time lag.) Negative or out-of-phase feedback produces the opposite effects. Gain and time lag are both decreased, while stability and linearity are improved.

### A Motor Control

Magnetic amplifiers are often used in the control of motors, as in the example illustrated by Fig. 5. This unit employs a push-pull type of circuit, designed so that the motor can be made to run in either direction. The two-phase motor is supplied with AC from the line through phase-shifting capacitors C1 and C2, and the resulting current

# all BOGEN "M" Series PA amplifiers give you a real sound proposition

Now, a complete new line of PA profit-makers bearing the most famous name in the industry. It's the Bogen "M" Series of PA amplifiers offering all that's new in amplifier design, yet retaining the world-renowned styling which won the Milan Triennial Gold Medal Award. The "M" Series provides better performance and reliability than ever before. Additional refinements such as variable level markers and versatile installation accessories make these amplifiers easier to use...easier to sell. Check the specs on this outstanding model for a sound proposition.



**NEW MX60, DELUXE 60-WATT PA AMPLIFIER WITH 4 MIKE INPUTS**—Power Output: 60 watts at less than 1% distortion. Power Consumption: 270 watts. Frequency Response:  $\pm 2$  db, 35 to 20,000 cycles. Gain: Microphone: 125 db; Tuner: 85 db; Magnetic Phono: 115 db. Hum: (below rated output): Microphone: -60 db. Output Impedances: 4, 8, 16 and 83 ohms, balanced 25-volt line, 70-volt line. Tubes: 10. Tone Controls: Treble (10 kc): +10 db to -10 db; Bass (60 c): +10 db to -10 db. Overall Dimensions: 16 $\frac{1}{4}$ " x 13" x 5 $\frac{3}{4}$ ". Shipping Weight: 37 lbs.

Never before such easy installation, easy service in PA systems...



Just loosen thumb-screws and the lid is off. Provides easy access for fast servicing.



Easy-sliding accessory wall-mount bracket permits amplifier to fold back when not used.

Accessory record player attaches to amplifier. Special mount takes just 4 thumb-screws.



Locking plate available to guard against tampering with control panel. All models are light, easily portable.



**BOGEN GIVES YOU MORE.** Bogen, maker of over one million high-fidelity and sound-distribution components in its 27-year history, gives you more engineering help with installations, more value, more performance, more features to sell. Find out more today about the new "M" Series of PA amplifiers, mixer-preamplifiers and booster amplifiers. Call your Bogen rep or write for full details to : Dept. PF-11. BOGEN-PRESTO, P.O. Box 500, Paramus, New Jersey. A Division of the Siegler Corporation.



the sound way  
to better business

# BOGEN

through L12 is called the reference field. Operation of the motor depends on the *control field* produced by L13; if there is no current through this winding, the motor does not turn.

The control field should be about 90° out of phase with the reference field in order for rotation to occur. Motor speed is determined by the magnitude of the current through L13. (The current in L12 is constant). If the control field leads the reference, the rotation will be in a one direction; if it lags, rotation will be in the opposite direction.

The DC control voltage is applied to four series-connected control coils, L1, L2, L3, and L4. Two of these coils are used in each magnetic amplifier section, as compared to only one in the circuit of Fig. 1. Each control coil is coupled to a load coil, and four rectifiers are connected in the load circuits. The actual load in this arrangement is L13, the control field of the AC motor.

To circuit-trace the load circuit, we can assume the polarities shown across L9 and L10, since they serve as AC sources for the load circuit.

Current travels from the negative end of L9, through the control field L13, diode M1, and coil L5, back to the positive end of L9. For the other circuit the current path is from the negative end of L10, in the opposite direction through L13, and then through M4 and L8 back to L10. For the next alternation L6, M2, L7, and M3 are conductive, but two currents still oppose each other in L13. As long as there is no DC control input, the load currents are equal and opposite, so there is no rotation of the rotor.

With a DC input of the polarity shown in Fig. 5, the control-current path through coils L1 and L4 is in the direction indicated by the arrows. The load coil currents are the same as previously given, but the values change. As shown, the arrows of L1 and L5 are in the same direction, so the magnetic fields of these coils reinforce each other and drive the core into saturation. This causes the L5 current to increase. In L4 and L8 the arrows are opposite, indicating a tendency to desaturate the core and decrease the current through L8. This means that the load current for the left circuit is greater than that of the right circuit, with the amount of difference determined by the magnitude of the DC control current. On the succeeding alternation L6 and L7 become conductive, with the L6 current the larger of the two.

If the DC control-input polarity were reversed, the motor would


# Neatest Tool Trick In Years!

It's

# VACO'S®

## "PIGGY-BACK" SCREW DRIVER OFFER

Look What You Get!

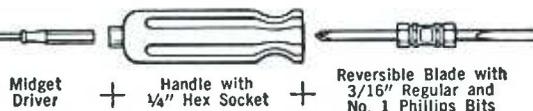


Only \$1.28 complete (Dealer Net)

A regular Vaco instrument-type screw driver is included FREE in this deal with the purchase of a quality VACO DU-11 Reversible with dual purpose regular and Phillips bits and 1/4" hex socket on dome of handle.
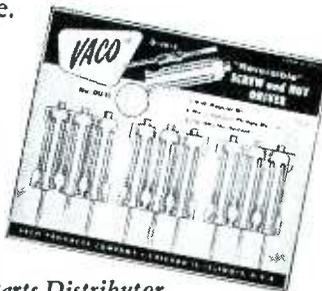
### Midget Driver FREE!

The midget driver handle, as illustrated, fits "piggy-back" into the hex socket of the DU-11 handle dome. This gives extra length and precision control when working in hard-to-get-at places.

Look for this display or ask your Parts Distributor for the VACO DU-11 "Piggy-Back" offer.



**VACO PRODUCTS COMPANY**  
317 East Ontario Street, Chicago 11, Illinois

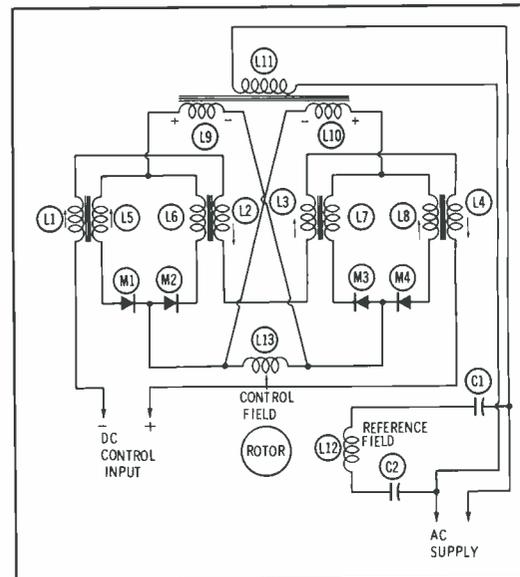


Fig. 5. Four-section magnetic amplifier controls motor speed and direction.

rotate in the opposite direction because the L13 current would be changed in phase by 180°.


### Temperature Control

Magnetic amplifiers can also be used for temperature control, as in the circuit of Fig. 6. Thermistor R1 and the heating element are both located in the oven whose temperature is to be controlled. A DC control input is used, and AC is used for the heating element—which in this case is the load. Two separate windings control the saturation level. The bias winding, in series with manual control R2 across the DC source, provides a means of presetting the temperature. The control winding is in series with the thermistor across the DC source, with the resistance of the thermistor determining the control current. These two windings are connected oppositely, so that they will have opposite effects on the saturation level.

The potential existing across the heating element determines the current through it, and therefore governs the heat produced. On each alternation of the AC input, the heating element is in series with one load winding and two diodes. The impedance of the load windings varies according to changes in the control circuit, thus regulating the potential across the heating element.

With very low current through the control winding, the saturation level is determined primarily by the bias-winding current. Saturation is then high, causing the load windings to have low reactance. Only a small portion of the AC is then dropped across the load windings; thus, a large voltage appears across the heating element, and the temperature increases.

As furnace temperature rises, the resistance of the thermistor decreases, allowing more current to flow through the control winding. This opposes the flux produced by the bias winding, thereby decreasing the saturation level. The impedance of the load windings then increases, making less voltage available across the heating elements. As the temperature begins to decrease, the opposite effects occur. The entire process keeps accurate

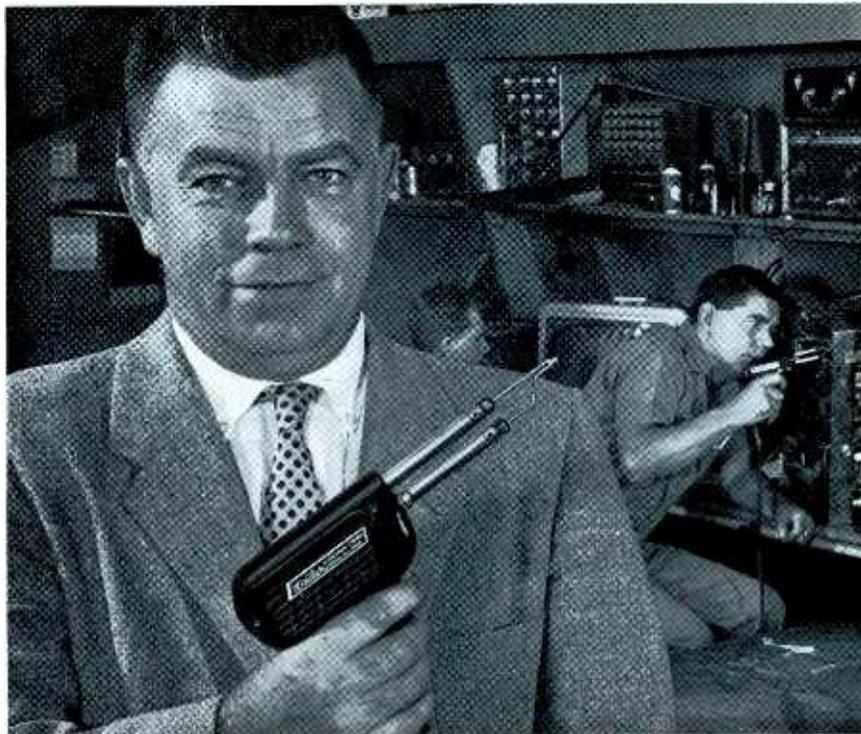

JOSEPH WHELAN, VICE PRESIDENT OF GERHARD'S, SAYS:

**"Gerhard's averages 70 service jobs a day**

**... and we do the work faster with**

**Weller® DUAL HEAT  
SOLDERING  
GUNS"**

Brand Name Retailer of the Year in 1959, Gerhard's of Glenside, Pa., is one of the largest TV, radio and hi-fi dealers in the nation. A major reason for this is dependable service. And this service is speeded by 23 service technicians—each with his own Weller Dual Heat Soldering Gun. The combination of instant heat and 2 soldering temperatures saves many man hours and results in more reliable soldered connections. Weller's exclusive Dual Heat feature permits instant switching to high or low heat as the job requires. Get these benefits in *your* service operation.

#### WELLER DUAL HEAT SOLDERING GUN model 8200K

90 and 125 watt heat. High efficiency, long-life tip has long reach. Instant heat. Prefocused spotlight.

**\$795**  
list



**Weller Single and Dual Heat Soldering Guns from 90 to 275 watts available at Electronic Parts Distributors.**

**WELLER ELECTRIC CORP. EASTON, PA.**

# CUT BACK on CALL BACKS



## AEROVOX MICA CAPACITORS

Why risk call backs when dependable Aerovox Mica Capacitors insure a stay-put repair job. Smart servicemen and technicians everywhere use and depend on Aerovox mica capacitors for "trouble-free" operation.

**POSTAGE STAMP MICAS . . .** for all those applications where only the smallest axial lead units will do. Perfect for horizontal and vertical oscillator requirements. All units color-coded and stamped.

**HIGH VOLTAGE MICAS . . .** designed especially for TV and low power transmitters. You'll find the highest voltages available in these small case sizes. Every unit is tested at twice the rated voltage to insure long-life. Units color-coded and stamped.

**DIPPED-MICAS . . .** superior in many cases to conventional molded units. High operating temperatures, excellent long-life characteristics. Perfect for printed-wiring assemblies. Smallest physical sizes with unsurpassed performance and stability features.

For "off-the-shelf" delivery on all your capacitor requirements see your local Aerovox Distributor.

**AEROVOX CORPORATION**  
DISTRIBUTOR DIVISION  
NEW BEDFORD, MASS.

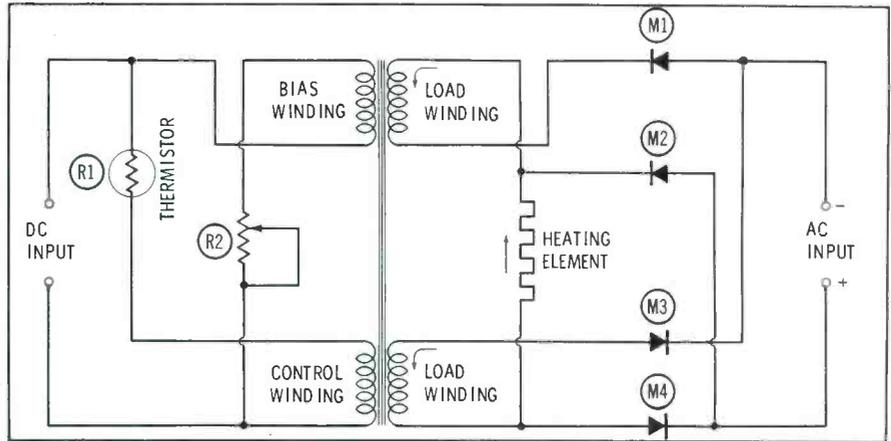


Fig. 6. Voltage across heating element is regulated to control temperature.

control over oven temperature.

Four diodes, used for self-saturation of the magnetic amplifier, are connected in the form of a bridge. With the AC polarity as indicated in Fig. 6, there is current through M3, the lower load winding, the heating element, and M2, back to the line. For the opposite alternation, there is current through M4, the heating element, the upper load winding, and M1, back to the other line terminal. In this way, current is always passed through the element in the same direction, and the load circuit is prevented from altering the core saturation level.

### Servicing

The primary advantages of magnetic amplifiers are ruggedness and long life, and because of this the servicing and maintenance problems are minimized. Usually a preventive maintenance program or regular replacement procedure is not needed. The majority of the servicing problems encountered result from faults in some of the associated components such as relays or rectifiers, rather than in the magnetic amplifier. As to the in-

## Check the MODERN STYLING you get in the RCA V-O-M with the Extras



- Big attractive 5 1/4" meter for better readability and visibility.
- Non-breakable plastic case and meter faceplate; no glass to crack or shatter.
- Orderly location of jacks below the switches keeps test leads out of the way.

See page 61 for the full story on this superlative value at only \$43.95\* \*User Price (Optional)

RCA Electron Tube Division, Harrison, N.J.



The Most Trusted Name in Electronics

RADIO CORPORATION OF AMERICA



## QUIETROLE LUBRI-CLEANER

The first of its kind and still best for silencing noisy controls and switches in TV, Radio & all Electronic Equipment.

### Spray it or Drop it

Just Press and whoosh . . . aerosol QUIETROLE quickly and easily cleans as it lubricates.

- Or, if you prefer, use this handy eye-dropper and just a drop or two of quality QUIETROLE does the job perfectly.

Either way, make sure it's QUIETROLE

**QUIETROLE** Company, Inc.

Spartanburg, South Carolina



In Canada:  
CROSS CANADA ELECTRONICS  
67 Ontario St., S., Kitchener, Ont.

ductors themselves, when operated safely within ratings, they are virtually indestructible. However, if the current rating is exceeded, one or more of the coils may open. Exceeding the voltage rating may produce shorts within the coil, or from coil to core, through breakdown of the insulation.


Operating at an incorrect frequency may also adversely affect operation. If the frequency of the AC load-circuit current is too high, the additional inductive reactance developed may decrease the load current so as to render the device inoperable. If the frequency is much lower than the rated value, excessive coil currents may damage the amplifier and possibly the load device as well. Changes of supply voltage cause changes of amplifier output, just as in other types of circuits. A decrease of frequency has the same effect as an increase of supply voltage. Decreased frequency also increases the L/R time delay because the theoretical minimum delay is the time of one half-cycle of the operating frequency.

In extreme cases, or over very long periods of time, it is possible that the characteristics of the core material may change. The saturation level and the shape of the hysteresis loop are two of these characteristics. However, in most cases we can dismiss this as being an unlikely trouble possibility. If it did occur, complete replacement of the reactor section would then be necessary.

The rectifiers used with the reactors are sometimes a source of trouble. One of the deterrents to earlier development of magnetic amplifiers was the lack of suitable rectifiers. Then, when improved versions were introduced (along with better core materials), high-quality magnetic amplifiers became feasible. Silicon rectifiers are quite often used because of the high front-to-back ratios of these units. Ordinary seleniums are usually not suitable; those used with magnetic amplifiers have front-to-back ratios better than 1000 to 1.

The saturable reactors in many magnetic amplifiers are potted, thus making the coils inaccessible. And while many circuit changes can be made theoretically, they cannot be made in a practical sense. ▲
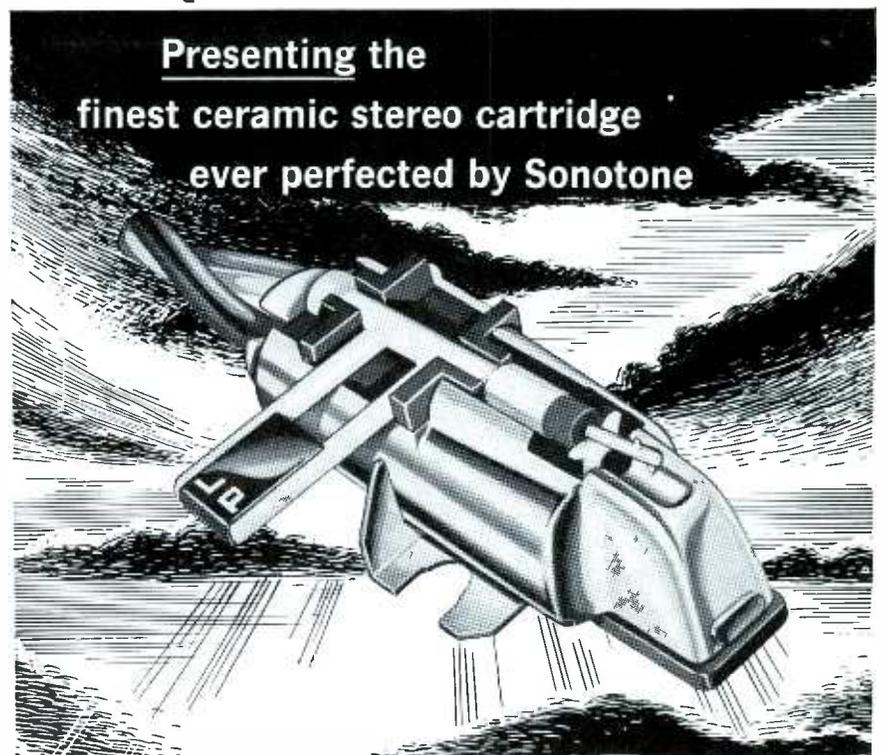
## STEREO QUALITY SOARS TO NEW HEIGHTS...



## THE "PROFESSIONAL QUALITY" 9T!

Now, the ceramic cartridge proved in independent A-B listening tests to perform as well as the highest-priced "professional" types. It's Sonotone's revolutionary new 9T. So superior, you can expect faithful reproduction from the most robust musical passages to the most subtle overtones. Sonotone's new 9T series stereo cartridge:

**GUARANTEES** performance equal to cartridges costing up to 3 times as much—as proven in A-B listening tests.

**GUARANTEES** highest compliance—allows major reduction of tracking force.

**GUARANTEES** more than adequate channel separation.

**GUARANTEES** crisp definition.

**GUARANTEES** superior, more compact mechanical design—including revolu-

tionary new needle design with instant "snap-in, snap-out" replacement needle feature and built-in jewel tip protector.

**ELIMINATES** distortion—incidentally flat response of  $\pm 1$  db from 20 to 17,000 cps—cuts listening fatigue.

**ELIMINATES** dust pile-up—at recent trade show the 9T ran 4 straight hours, collected no dust.

**ELIMINATES** most record groove noise or hiss—no "needle talk".

Imagine, the 9T boasts all these "professional" features...yet sells for less than half the price of the least expensive "professional" cartridge. Simplify your inventory...cut call-backs—increase sales and profits—with Sonotone's great new 9T cartridge...unsurpassed for performance—and for value.


LIST PRICE:	9T-S...\$16.50 (0.7-mil and 3-mil sapphires)	9T-S77...\$16.50 (Two 0.7-mil sapphires)	9T-SD...\$19.50 (Sapphire-Diamond)
-------------	---	---	---------------------------------------

# Sonotone<sup>®</sup>

ELECTRONIC APPLICATIONS DIVISION, ELMSFORD, N. Y. DEPT. C10-110

IN CANADA, CONTACT ATLAS RADIO CORP., LTD., TORONTO

LEADING MAKERS OF

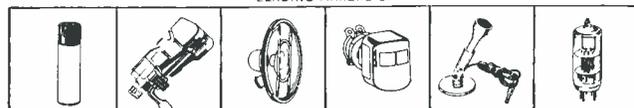

BATTERIES • CARTRIDGES • SPEAKERS • TAPE HEADS • MIKES • ELECTRONIC TUBES

# IMPORTANT NEW SAMS BOOKS

## Electronic Organ Handbook

by H. Emerson Anderson

**ONLY BOOK OF ITS KIND  
ON THIS IMPORTANT SUBJECT**



Here's all the information you need to get into this brand-new servicing market! Over 1,000,000 electronic organs are now in use. With your radio-TV servicing experience, plus the wealth of schematics, detailed operating data and troubleshooting information in this book, you'll be ready for

profitable service work in this big new field. Twelve comprehensive chapters cover these popular organs: Baldwin, Conn, Gulbransen, Hammond, Kinsman, Lowrey, Thomas and Wurlitzer. First chapter explains general operation of the electronic organ. Also includes data on the Leslie organ speaker, the Conn Strobotuner and Peterson Chromatic Tuner. The book you've been waiting for! Over 140 illustrations. 272 pages; 5½ x 8½". Only..... **\$4.95**

## Video Speed Servicing

NEW VOLUME 5

Latest volume in Sam Marshall's very useful series. Consists of 456 more practical troubleshooting hints for solving hard-to-find faults in major makes of 1959-60 TV receivers. All models are indexed by brand name, model and chassis number for quick reference. Each hint is accompanied by an explanatory diagram or schematic. An invaluable, time-saving shop reference. 160 pages; 8½ x 11". Only **\$2.95**



## TV Tube Location Guide

NEW VOLUME 10



Latest in this invaluable series. Gives tube location data for TV sets produced in 1959-1960. Shows position and function of tubes in hundreds of models—just find the trouble and replace defective tubes without removing chassis! Shows major component placement; signal path; pin orientation on socket; series string filaments; fuse location. Includes tube failure check charts. 96 pages; 5½ x 8½"; spiral bound. Only..... **\$1.25**

### HOWARD W. SAMS REPLACEMENT GUIDE FOR TV & AUTO RADIO CONTROLS

Vol. 3. Greatly expanded—covers 27,000 TV and over 1,000 auto radio models. Lists recommended replacement controls of Centralab, Clarostat, IRC and Mallory. **\$1.00**  
8½ x 11". Only.....



### HOWARD W. SAMS & CO., INC.

Order from your Sams Distributor today, or mail to Howard W. Sams & Co., Inc., Dept. L-30 1720 E. 38th St., Indianapolis 6, Ind.

Send me the following books:

- "Electronic Organ Handbook" (EOA-1)
- "Video Speed Servicing" Vol. 5 (VSM-5)
- "Television Tube Location Guide" Vol. 10 (TGL-10)
- "Replacement Control Guide" (RGC-3)

\$..... enclosed.  Send Free Book List

Name.....

Address.....

City..... Zone..... State.....

(Outside U.S.A. priced slightly higher)

# THE TROUBLESHOOTER

answers your service problems

## Impedance Ups and Downs

I've a question I can't seem to find the answer for. The situation is this: I'm using RG-59/U coax to feed a TV located across the room from a UHF converter. This way, I can use a short UHF transmission line to keep its losses at a minimum while still keeping the receiver in a better viewing location. I'm using matching transformers at the set and at the converter to match the input and output of my 72-ohm connecting cable; these are rated at 6 db gain from 72-ohm line to 300-ohm line. My question is: What gain or loss am I getting when the line goes from 300-ohm to 72-ohm?

EDWARD V. PELISSER

Hermiston, Ore.

*The 6-db gain you mention is voltage gain, but at the same time you get a 6-db current loss. The power available (watts) remains the same except for line and transformer losses, which are only a few per cent. At the cable-input transformer, you get a current step-up and voltage step-down; but, once again, there is no significant loss in RF power. You can assume a total loss of 1.5 db in the transformers and 3.5 db per 100' of RG-59/U.*

*Your system is superior to twin-lead for one reason: The coax cable is immune to losses caused by its environment, whereas twin-lead is peculiarly prone to this kind of loss.*

## Trapezoid

An RCA Chassis KCS49A has a somewhat trapezoidal raster, with the left side compressed vertically. Substituting the yoke didn't fix it. What else could cause this symptom?

PAUL SHOFFLER

Springfield, Va.

*You were quite right in anticipating*

*yoke trouble as the probable cause of this symptom. However, this chassis does incorporate a rather unusual vertical sweep circuit, and the most likely suspects in your case are the two capacitors C99 and C100 from the secondary of the vertical output transformer to ground. Substituting for these components should solve your problem.*


## Did-It-Themselves


I just took in a Bendix Model 21K3 that has poor sound, a washed-out picture, poor focus, and a raster that won't fill out on the right side. The 470-ohm resistor R21 feeding the 360-volt source was burned and arcing to a nearby filter, and I thought I had an easy job until I checked C2A (the filter in the 360-volt line) and found it to be OK. I went ahead and tried replacing R21. With C2A disconnected, the new resistor didn't burn; but reconnecting the filter brought the resistor to a boil. I can stop the overheating by disconnecting the flyback circuit from B+; yet, when I checked the current through the sweep-circuit fuse M1, there was no hint of excessive current drain in this circuit. Help, please!

CHARLES E. KESTER

Clearfield, Pa.

*Disconnecting the B+ line to the deflection circuits takes the load off a resistor in series with the 360-volt source? Let's have another look at the schematic! The sweep-circuit fuse M1 is shown connected to the 320-volt source; the 360-volt branch is supposed to feed only the video IF and tuner stages. Someone has evidently been there ahead of you, and has connected the lead from M1 to the wrong B+ source point. The heavy current drain of the sweep circuits through the 470-ohm, half-watt resistor is enough to*

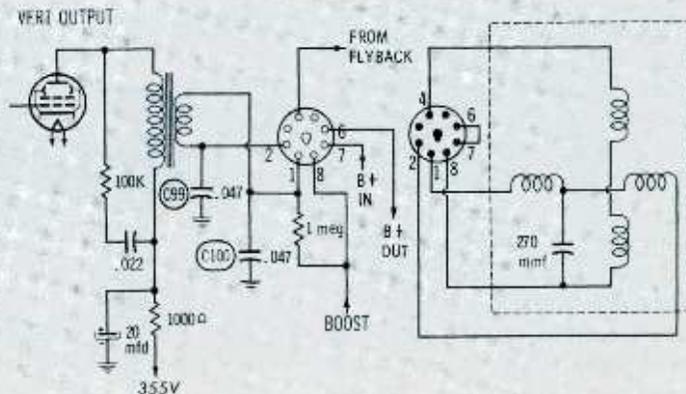

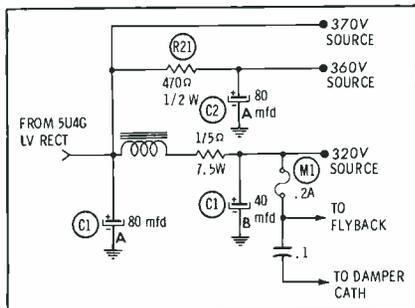

roast it, and incidentally to account for all your trouble symptoms. Trace out the B+ wiring and see if M1 hasn't been connected to C2A rather than C1B. Corrected wiring and another new resistor should solve this one for you.

### Sympathetic Vibration

An Admiral radio-phono Model 6S12N sounds good on radio unless the volume and bass controls are turned up high. Then the whole case starts vibrating, and some way the oscillation becomes amplified. In phono position, the vibration is so bad that its interfering hum and buzz override even maximum volume.

Squeezing the case reduces vibration to almost nothing. Also, removing the chassis stops the condition completely. I'll sure appreciate any help you can give.

CURT BENTHAM

Willsboro, N. Y.

*It seems the best answer is to eliminate the vibration. Make a close examination of the positioning of the radio chassis and the leads connected to it. Originally, a foam-rubber pad was positioned between the loudspeaker and the cabinet; be sure it isn't missing.*

*If you have not already done so, by all means try substituting for all the tubes. Heater-to-cathode leakage or a vibrating grid may be the source of your trouble. Make certain that none of the power leads are lying close to the audio output tube, or that an unshielded glass tube hasn't been "subbed" for any of the metal ones. Be sure the record-changer assembly is not screwed down tight to the chassis, but floating on the suspension springs provided to shock-mount it. Most important of all, make sure there is nothing loose on the case itself.*

### Electronic Organ Problem

I've just encountered a problem in servicing a Thomas organ, Model G, that's entirely new to me. When one of six or more keys in the upper two octaves is pressed, it continues to play until a note is struck in the lower half of the keyboard. Nothing I've tried so far has helped; anything you can suggest will be greatly appreciated.

EDWIN C. MYHRE

Mahtowa, Minn.

*The condition you describe is known as "cipher." It's a problem peculiar to the Thomas keying system. In all probability, it can be corrected by bending the leaves of the key switches. Details are contained in Chapter 8 of the recently-released Howard W. Sams book, "Electronic Organ Handbook."*

**"My Photofact Library is the most important tool in my daily servicing. With my Photofacts I am able to complete a job in just half the time it would take without them . . . Membership in the PEET program is the best thing that could happen to any Electronic Technician. I believe I speak from experience as this is my 19th year of full-time servicing."**

—A. Kish, Jr.  
AI's Radio & Television  
Carteret, N. J.



## Service Technicians! YOU EARN MORE... YOU RATE with the public when you own the PHOTOFACT® service data library!

You enjoy maximum earnings as the owner of a complete PHOTOFACT Service Data Library! It's inevitable, because no matter how expert you are, you can always *save more time on any job, get more jobs done daily*—EARN MORE, DAY IN AND DAY OUT...

What's more—as the owner of a complete PHOTOFACT Library, you know your customers' sets *best*. You can actually show each customer you have the PHOTOFACT Folder covering his very own set. Result: You command public respect and acceptance which paves the way to more business and earnings for you.

### HOW TO STAY AHEAD...

Yes, the truly successful Service Technicians are those who own the complete PHOTOFACT Library, who can meet and solve any repair problem—faster and more profitably. And these men keep ahead because they're on a Standing Order Subscription with their Distributors to receive all new PHOTOFACTS as they are released monthly. (They're eligible for the benefits of membership in PEET, too—see below!)

**ONLY \$10 DOWN** puts the complete PHOTOFACT Library in your shop—and you have up to 30 months to pay. See your Sams Distributor today, or write to Howard W. Sams

NOW IS THE TIME TO JOIN

**"PEET"**

### THE POWERFUL NEW PROGRAM FOR QUALIFIED TECHNICIANS

If you now own a PHOTOFACT Library or plan to own one, you can apply for membership in "PEET." It's the first industry program really designed to build powerful public acceptance for the Service Technician who qualifies. Builds enviable prestige and business for its members. Benefits cost you absolutely nothing if you qualify. Ask your Sams Distributor for the "PEET" details, or mail coupon today.

HOWARD W. SAMS & CO., INC.  
1728 E. 38th St., Indianapolis 6, Ind.

- Send me full details on the new "PEET" Program.
- Send full information on the Easy-Buy Plan and Free File Cabinet deal.
- I'm interested in a Standing Order Subscription.
  - I'm a Service Technician  full-time;  part-time

My distributor is \_\_\_\_\_

Shop Name \_\_\_\_\_

Attn: \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

# The VTVM with The 2-way Probe Tip

# Simpson

## MODEL 311 VTVM



### Compare these features before you buy!

- 22 MEGOHM Input Impedance
- Peak-to-Peak Readings of Complex AC Voltages
- Accessory RF Probe with High Frequency Response and Accuracy
- New "TIMESAVER" Probe Tip
- Unbreakable Metal Case
- AC Balance Adjustment

HANGS ON WIRE FOR CONTINUOUS READINGS

PROVIDES QUICK, NO-SLIP CONTACT

This new Simpson VTVM has all the capabilities you need to run highly accurate tests on practically any job. Note its timesaving features, too—slimline probe; special two-way probe tip; and Adjust-A-Vue Handle. You might expect Model 311 to cost a good deal more than it does, but the price complete with probe, lead, ground cable, clips, and Operator's Manual is a sensible . . . . .

**\$69<sup>95</sup>**

DC VOLTS: 0-1.5, 5, 15, 50, 150, 500, 1500  
(±3% accuracy)

AC VOLTS: 0-1.5, 5, 15, 50, 150, 500, 1500  
(±5% accuracy)

AC PEAK-TO-PEAK: 0-4, 14, 40, 140, 400, 1400, 4000 volts  
(±5% accuracy)

OHMS: X1; X10; X100; X1000; X10,000; X100,000; X1 megohm (meter can be set for center zero for FM alignment)

AC FREQUENCY RANGE: 30 to 100,000 cycles per second

INPUT IMPEDANCE: 22 Megohms

SIZE: 7½" x 5⅝" x 4½" deep

WEIGHT: 4½ lbs.


RF PROBE: 50 cycles to 100 megacycles, ±5%; 0-150 volts maximum, RMS. Input capacitance, 10 mmf . . . . . \$11.50

HIGH VOLTAGE PROBE: Gives measurements from 0-30,000 volts, DC . . . . . \$11.50

SEE YOUR ELECTRONIC PARTS DISTRIBUTOR, OR WRITE

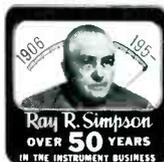**SIMPSON ELECTRIC COMPANY**

World's Largest Manufacturer of Electronic Test Equipment



5209 West Kinzie Street  
Chicago 44, Illinois  
Phone: EStebrook 9-1121  
In Canada:  
Bach-Simpson Ltd.  
London, Ontario

### FM Radio Field

(Continued from page 29)

of the Standard Coil tuner (Fig. 4B) illustrates how AFC can be applied to the autodyne converter. Certain types of semiconductor diodes, when reverse-biased, will act as variable capacitors. (The necessary bias in the circuit of Fig. 4B is supplied by a positive voltage fed to the diode cathode.) A change in the potential applied across the diode terminals will cause a corresponding change in capacitance; thus, if the diode is connected in series with the oscillator tank, a variable AFC voltage can be employed to control the oscillator frequency.

Although popular, these one-tube tuners are not universally used in FM table radios. For example, Zenith's current models have a 6BJ6 pentode RF amplifier, and use the two separate sections of a 12AT7 as oscillator and mixer on both FM and AM. The Blonder-Tongue Model R-20 (FM only) uses a 12BA6 followed by a 12AT7.

Sarkes Tarzian's Model 723-502 table radio employs the pentode section of a 19CL8A as an RF stage and the triode section as an autodyne converter. Another out-of-the-ordinary feature of the latter receiver is the DC "stacking" of the converter and the first IF stage across the B+ supply (Fig. 5)—an arrangement often seen in the first and second video IF's of TV sets, but seldom in radios.

### IF Circuits

The majority of other FM table radios use two 12BA6 pentodes as transformer-coupled IF amplifiers. In most AM-FM combination units, 455-kc IF transformers for the AM signal are connected in series with some of the 10.7-mc FM-IF transformers—thus allowing at least the second IF stage to function on both bands.

Unlike most high-fidelity FM tuners, small table radios do not ordinarily have extra IF stages designed specifically as limiters. However, the regular IF amplifiers of these receivers are generally fed a rather low plate voltage of 85 to 95 volts, which causes these stages to accomplish some limiting as well as amplification of the signal.

Furthermore, many of these units

have no AVC system at all; the IF stages are deliberately overloaded by strong input signals in order to clip off noise and keep the IF output-signal amplitude relatively constant.

Where AVC is provided in a combination AM-FM unit, the AVC line may be grounded in the FM position of the selector switch; or delayed AVC may be employed, as it is in TV tuners.

#### Detector

The ratio-detector circuit is predominant in small FM radios because it has better noise-limiting characteristics than the discriminator. However, certain receivers do use a discriminator circuit, preceded by a third IF or limiter stage. The quadrature-grid or "gated-beam" detector, now almost universally used in TV sound circuits, has not made much headway in the FM radio field—although one receiver, the above-mentioned Sarks Tarzian model, does use a 12BN6 gated-beam detector.

#### Servicing

In FM table models, as in other radios, signal injection is a speedy and effective method of localizing trouble. However, the techniques are different from those generally used in AM receivers, although not necessarily more difficult to apply. It is not really necessary to use a frequency-modulated signal generator for testing, since a certain amount of AM can be passed through even a ratio detector—provided the input-signal level is low enough to avoid limiting action in the IF stages. Consequently, an AM signal generator covering the 10.7-



"Well, if you don't pay that bill by tomorrow, I'm afraid I'll have to take drastic measures . . . and rest assured, this is no idle threat. Of course, you realize there's nothing personal in this, Mother."



## replace with **RCA** **BEAM POWER TUBES** *for reliable radio communications*

For long life and dependable performance in your two-way radio equipment, always replace with RCA beam power tubes. RCA pioneered beam power, and continues to pace advances in the art. RCA-6883 shown above, for instance, is the 12.6-volt version of RCA-6146—probably the most popular power tube in radio communications.

Your local RCA Industrial Tube Distributor carries a complete line of tubes for your fixed and mobile communications equipment. He also stocks tubes for just about every industrial application. Call him for immediate service on all replacement tube needs. *RCA Electron Tube Division, Harrison, N. J.*



The Most Trusted Name in Electronics  
RADIO CORPORATION OF AMERICA

## SAMS BOOKS

give you know-how on  
**TRANSISTORS**

available from your Sams Distributor



### ABC's of Transistors

by George B. Mann



Takes the mystery out of transistors. Explains principles, physical construction, basic circuits, temperature considerations, practical testing and servicing procedures. Written simply and clearly for easy understanding. Invaluable for electronic technicians, students and hobbyists. 96 pages; 5 1/2 x 8 1/2"; illustrated. No. TRA-1.

Only.....\$1.25

### Practical Transistor Servicing

by William C. Caldwell



The latest word on how transistors and transistor circuits operate—shows how to signal-trace and diagnose portable and auto-radio troubles. Tried and tested procedures are based on the premise that "time saved is money earned." Concentrates on the practical in 8 fact-filled chapters; tells clearly how transistors work; describes circuit components and their functions; shows how to isolate troubles; indicates normal transistor voltages and explains meanings of improper voltages; tells how to test transistors; shows how to troubleshoot auto radios; gives actual case histories. Profusely illustrated; 5 1/2 x 8 1/2". No. PTC-1.

Only.....\$2.95

### Servicing Transistor TV Receivers

by Milton S. Kiver  
and Charles R. Gray



Only book of its kind on this subject, timed with the appearance of the first transistor TV models. The authors introduce you to the transistor and to basic transistor circuits. Then, you are shown, one by one, how transistors are used in the tuner, video-IF amplifier, video-detector, video-amplifier, AGC, sound, sync-separator, and horizontal and vertical deflection sections. Includes data on the application of tube-set techniques; servicing differences between tube and transistor TV's; handling, testing and replacement of transistors; checking operating points, shorted and open transistors; plus special servicing pointers on specific sections, emphasizing horizontal-deflection systems. Illustrated; 272 pages; 5 1/2 x 8 1/2". No. KST-1.

Only.....\$4.50

### Servicing Transistor Radios Series



Complete Photofact® analysis of transistor radios produced from 1956 to the present. Includes famous Sams Standard Notation Schematics with exclusive CircuiTrace®; chassis photos; alignment data; servicing tips; complete replacement parts lists. Each volume 160 pages, 8 1/2 x 11".

Only.....\$2.95

- Vol. 1. 70 models (1956-1958) No. TSM-1.
- Vol. 2. 60 models (1956-1958) No. TSM-2.
- Vol. 3. 64 models (1957-1959) No. TSM-3.
- Vol. 4. 60 models (1958-1959) No. TSM-4.
- Vol. 5. 52 models (1958-1959) No. TSM-5.
- Vol. 6. 62 models (1959-1960) No. TSM-6.

FREE SAMS BOOKLIST AVAILABLE—ask your Distributor or write us direct

Available from your Sams Distributor  
**HOWARD W. SAMS & CO., INC.**  
1720 E. 38th St., Indianapolis 6, Ind.

mc IF and the 88-108 mc RF band can be used to advantage.

In order to introduce signals of sufficiently low strength, it is often desirable *not* to couple the generator directly to the RF or IF circuit being tested. Because of the high frequencies and high-gain circuits involved, it is often possible to radiate adequate signals into the various stages for troubleshooting purposes. The easiest way of doing this does not even require removal of the chassis from the cabinet. Simply remove or retract the tube shields, tune the generator to 10.7 mc, set it up for a strong RF output, and place the RF output connector against the glass envelopes of the second IF, first IF, and converter tubes in succession. You should be able to hear an audio tone from the speaker, increasing in volume as you move back toward the converter. A little practice will enable you to set the generator controls for best results. Of course, you should use a shielded RF cable with a small tip in order to pinpoint the radiation to a small area. Connecting the generator directly to the various grid and plate leads is also possible if the signal level can be kept low enough to prevent overloading.

Simplified generator units such as pencil-type "injectors" are excellent for signal-tracing the audio section, and are usually adequate for checking continuity through the IF's; however, it is not usually possible to adjust their output accurately enough for stage gain to be checked.

Naturally, if you have a sweep generator that can be tuned to 10.7 mc, its FM output is ideal for obtaining maximum accuracy in signal-tracing.


#### Alignment

Touching up the RF-IF alignment is highly advisable after you have finished repairing an FM radio. Many customers will expect even the humble table model to perform like "hi-fi," so the unit should be given a chance to do its best. Balancing the detector will minimize distortion in the audio, and peaking the RF-IF slugs will help the radio to separate stations clearly and to reject noise.

The quick, simple alignment method using an unmodulated RF generator and a VTVM is ordinarily adequate for small FM radios. The

## SWITCHCRAFT ADAPTERS

are  
your  
answer

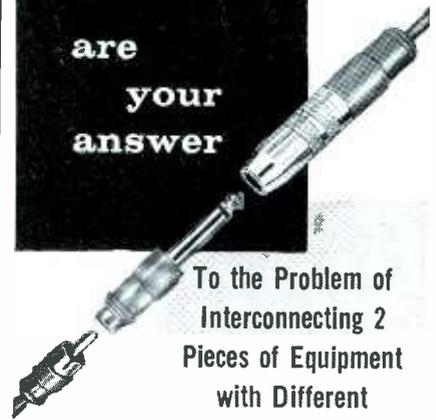

To the Problem of  
Interconnecting 2  
Pieces of Equipment  
with Different  
Type Connectors

Save Time—No Soldering—Eliminate Make-shift Connections—Provide a Neat Job.

Over 65 different types. Low cost.

Send for Catalog S-590.

**SWITCHCRAFT®**

5573 N. Elston Ave., Chicago 30, Ill.  
Canadian Rep.: Atlas Radio Corp., Ltd.,  
50 Wingold Ave., Toronto, Ontario  
Stocked by leading Electronic Distributors

Start the New Year . . .

# RIGHT!

with the OELRICH  
**"PROFIT-GUARD"**



**BOOKKEEPING  
SYSTEM FOR TV &  
APPLIANCE SHOPS**

An accurate, simplified system designed to enable you to do your own accounting expertly without previous experience. WRITE for information on the "Profit-Guard" and

many other fine aids designed for your better business.

**OELRICH PUBLICATIONS**  
4308 N. Milwaukee Ave.  
Chicago 41, Illinois

Dear Sirs:  
Please send complete information to:

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

detector - transformer secondary is adjusted for zero output from the detector at 10.7 mc, and all other adjustments are peaked for maximum voltage across the detector at the same frequency. Many, but not all, radios have double-tuned IF cans. Most of the one-tube tuners have trimmers in the oscillator and RF plate circuits, which may be adjusted as needed to improve sensitivity and tracking.

Of course, the sweep method of alignment gives more exact results, if you are properly set up for it. Certain types of troubles, such as a "lopsided" detector response or RF-IF regeneration, are much easier to handle with a sweep generator and scope.

### Auto Radios and Converters

FM receiving equipment for automobiles is just now entering the volume-production stage. The customers for these units are "pioneers" who need expert technical advice on getting the most satisfaction out of their purchases. FM reception in cars is definitely practical, but we must understand *how* and *why* it is different from AM reception.

A special antenna is usually not needed, since the existing AM whip antenna can operate as a quarter-wave (resonant) device at 88-108 mc when retracted to a length of slightly over 30'.

Especially in heavy traffic or in built-up areas of cities, the auto FM installation receives a constantly changing pattern of signal reflections. While these would cause intolerable ghosts in TV, they do not produce any noticeable distortion of FM sound. Their chief effect is a rapid raising and lowering of RF signal strength. In metropolitan areas, this seldom creates a problem, since even the signal "nulls" resulting from out-of-phase wave reflections are usually strong enough to provide adequate output from the radio. The use of very effective limiter circuits serves to keep the audio level practically constant in spite of wide fluctuations in RF field strength.

As the car is driven away from the FM transmitter, a point is eventually reached where the signal during "nulls" is not strong enough to rise above the background noise

# 5 GOOD REASONS WHY Shell OUTSELLS THEM ALL!

- TEST-O-MATIC**
- DEPENDABLE
  - ACCURATE
  - TIME SAVING
  - PROFIT MAKING
  - TOP QUALITY
- A  
TUBE TESTER  
TO FIT EVERY NEED



### DELUXE 102 SELF-SERVICE VOLUME TUBE SALES

Profit from list price sales of tubes at remote locations. The Test-O-Matic display is a permanent ad for your professional services. Units sell your tubes and services for you. The 102 lists and checks more tubes than any other self-service tube tester.

- Checks 6 and 12 volt vibrators • one knob control • complete emission tester • checks each section of multi-purpose tubes

**\$199.95** dealer net price



### S-18 SELF-SERVICE CREATES REPEAT SALES

The most consistent, dependable tester on the market. Suitable for placement in any high traffic location. Takes only 19" x 15" floor space. Storage capacity of up to 400 tubes. Tumbler lock steel cabinet allows easy stock control from compartmentalized sliding shelves.

- tests each side of multi-purpose tubes • Emission tests all tubes • New sockets conform to MIL spec • Tests more than 800 tube types

dealer net price **\$149.95**



### TM-18 TABLE MODEL SERVICE SHOP MONEY MAKER

Designed especially for the Service Shop the TM-18 is also available with legs. Same panel and performing qualities as the S-18 and attractively priced.

**\$91.95** dealer net price



### V-18 PORTABLE HANDY PORTABLE

Compact, yet tests more than 800 tube types. Ruggedly constructed, increases "on-the-job" tube sales. Panel and specs same as the S-18.

dealer net price **\$59.60**

### TC-18 TUBE CADI-TESTER TUBE TESTER AND AMPLE STORAGE

The Tube Cadi-Tester is a complete service outfit. A handy, convenient serviceman's dream with its accurate, dependable, built-in Test-O-Matic tube tester. "On-the-job" tube sales soar. Will stand up under constant use. Covering is black vinyl with reinforced outside trim. Uses just 18 sockets to test all tube types. Easy-to-use controls and fool-proof test meter.




dealer net price **\$69.95**

and our **NEW BATTERY TESTER** at **\$14.95**

# Shell

ELECTRONICS MFG. CORP.

112 STATE ST.  
WESTBURY, N. Y.

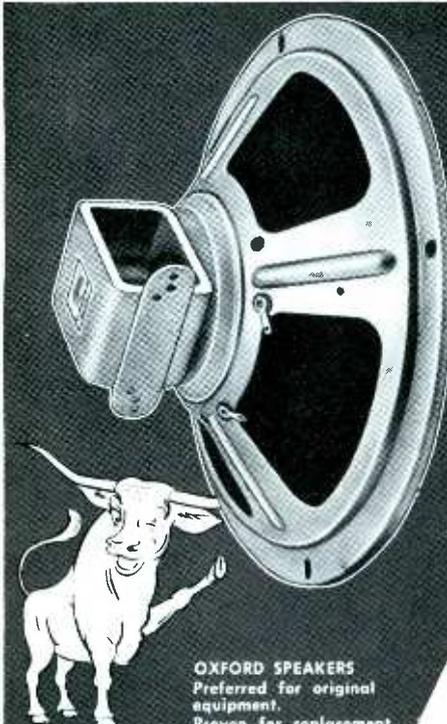

# OXFORD

*-the Leader*

**Largest exclusive SPEAKER manufacturer in the world**  
**6 factories located throughout the U.S.A.**

ONCE MORE UNTO THE BREACH, DEAR FRIENDS! When you are looking for replacement speakers on a par with original equipment, the prime source is Oxford. Oxford is the foremost name in original equipment speakers specified by manufacturers. We can supply you with exact replacement speakers which will be of the same high quality as that originally supplied. Oxford has a complete line for any and every application.

OXFORD SPEAKERS Preferred for original equipment. Proven for replacement.

Our catalog is available upon request.

**OXFORD Components,**  
 A Division of Oxford Electric Corp.  
 556 West Monroe St., Chicago 6, Illinois

Oxford Speakers are available from recognized electronic parts distributors.



level. "Picket-fencing," an effect in which the sound is broken up by signal fluctuations, then occurs. If you're familiar with the way a TV set behaves when the signal is disturbed by airplane flutter, you already know what "picket-fencing" is like. By the time this symptom appears, the car is out near the limits of the station's fringe area—so it's time to tune in another station if one is available. Unfortunately, the country isn't completely blanketed by FM radio signals, and sizable "white" areas will be found in less thickly populated regions. (Customers must be prepared to accept this fact.)

FM auto radios are highly sensitive, and make the most of available signals, but competition from electrical noise can become a serious problem in obtaining clear reception on weak stations. To add to the difficulty, much of the interference generated by the car's ignition system falls in the same frequency band as the FM radio signals; therefore, effective suppression of this noise is extremely important.

Conventional suppressor capacitors are often ineffective on FM because they have too much inductance. To get around this problem, special coaxial-type units are available for bypassing various points in the ignition system to ground. Besides the usual suppression measures, it is sometimes necessary in stubborn cases to bypass the battery lead of the ignition coil, and also to bond the ground terminal of the battery directly to the car body as well as to the engine block.

#### Typical Circuits

Several manufacturers have marketed *converters* which receive, amplify, and detect the FM radio signal. The recovered audio is then used to modulate an 800-kc oscillator which feeds its output to the antenna jack of the regular AM receiver. From this point, the signal is handled exactly like a conventional AM input. The only connections needed for attaching the converter are a 12-volt DC power lead and an antenna cable.

The Gonset converter, introduced a couple of years ago, is an example of this design. Another unit built along similar lines is the Granco

## SAMS PHOTOFAC INDEX

sent direct to your shop

**FREE**

SEND FOR IT!

Yes, now you can have the valuable SAMS MASTER INDEX TO PHOTOFAC FOLDERS and Index Supplements sent direct to your shop at no cost to you! Just mail coupon below and you'll be sure to receive regularly your handy guide to the world's finest service data covering over 33,000 TV, Radio, Amplifier, Tuner Tape Recorder and Changer models. Send for it—it's FREE!

**MAIL COUPON**

**Howard W. Sams & Co., Inc.**  
 1720 E. 38th St., Indianapolis 6, Ind.

Put me on your mailing list to receive the Sams Photofact Master Index and Supplements

I'm a Service Technician: \_\_\_\_\_ full time; \_\_\_\_\_ part time

My Distributor is: \_\_\_\_\_

Shop Name: \_\_\_\_\_

Attn: \_\_\_\_\_

Address: \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

## Check the EXTRA CONVENIENCE you get in the RCA V-O-M with the Extras



- Rugged, scuff-proof, stain-resistant laminated vinyl carrying case: only \$4.95 extra. Special receptacle for test leads!
- Spring clips on handle hold leads when instrument is not in carrying case.
- Red test probe supplied with slip-on alligator clip for added versatility.

See page 61 for the full story on this superlative value at only \$43.95\* \*User Price (Optional)



RCA Electron Tube Division, Harrison, N.J.

The Most Trusted Name in Electronics

RADIO CORPORATION OF AMERICA



the 12-volt supply; instead, a 108-volt DC plate potential is developed by a small, separate inverter/rectifier chassis which includes a 2N176 transistor as a power oscillator. Two more 2N176's are found in the push-pull audio output stage. The tuner uses the popular 12DT8 tube, with a semiconductor-diode AFC circuit that includes a neon-bulb voltage regulator to compensate for normal variations in supply voltage. Two 12AU6 IF stages, each with 100-volt plate voltage, are followed

by two more 12AU6's operating as limiters with 54 and 70 volts on their respective plates. A 12AL5 ratio detector feeds its output to a two-stage audio driver circuit employing both halves of a 12AU7—which in turn feeds the transistorized output stage. Delayed AVC voltage is developed across an RC grid-leak network in the grid circuit of the first limiter, and is fed back to the RF amplifier. (A similar feature is also used in converter-type units to minimize the problem of

signal fluctuations in auto installations.)

The speaker circuit of the FM-900 contains a built-in fader potentiometer, plus provisions for connecting both front and rear speakers. In addition, the circuit can be wired so that either or both of the speakers can be used on AM or FM at the flick of a switch—more evidence that convenience of operation has been one of the foremost aims in designing FM auto receivers. ▲

STATEMENT REQUIRED BY THE ACT OF AUGUST 24, 1912, AS AMENDED BY THE ACTS OF MARCH 3, 1933, AND JULY 2, 1946 (Title 39, United States Code, Section 233) SHOWING THE OWNERSHIP, MANAGEMENT, AND CIRCULATION OF PF REPORTER published monthly at Indianapolis, Indiana, for October 1, 1960.

1. The names and addresses of the publisher, editor, managing editor, and business managers are: Publisher: Howard W. Sams, 2201 E. 46th St., Indianapolis, Ind.; Editor: Verne Ray, 2201 E. 46th St., Indianapolis, Ind.; Managing editor: None; Business manager: Mal Parks, Jr., 2201 E. 46th St., Indianapolis, Ind.

2. The owner is: (If owned by a corporation, its name and address must be stated and also immediately thereunder the names and addresses of stockholders owning or holding 1 percent or more of total amount of stock. If not owned by a corporation, the names and addresses of the individual owners must be given. If owned by a partnership or other unincorporated firm, its name and address, as well as that of each individual member, must be given.)

Howard W. Sams & Co., Inc., 2201 E. 46th St., Indianapolis, Ind.; Alan S. Brengle, 28423 Kendallwood Drive, Farmington, Mich.; Cas & Co., c/o Brown Brothers Harriman & Co., 10 Post Office Square, Boston 9, Mass.; Lorraine G. Cumming, R. F. D. No. 1, Elburn, Illinois; Donaldson, Lufkin & Jenrette, Inc., 51 Broad Street, New York, New York; Jean B. Eldred, Redwood Drive, Franklin, Ky.; Genoy & Co., P.O. Box 491, Church Street Station, c/o Morgan

Guaranty Trust Co., New York 15, N. Y.; Griffin & Co., c/o Colorado National Bank, P.O. Box 5168, Denver 17, Colo.; Carl M. Loeb, Rhoads & Co., 42 Wall Street, New York, N. Y.; J. A. Milling, 7905 Morningside Drive, Indianapolis, Ind.; J. C. Orr & Co., Box 1368, Church Street Station, New York 8, N. Y.; Howard W. Sams, 414 Kessler Blvd., W. Drive, Indianapolis 8, Ind.; Donald B. Shaw, 3419 N. Pennsylvania, Apt. E-4, Indianapolis 5, Ind.

3. The known bondholders, mortgagees, and other security holders owning or holding 1 percent or more of total amount of bonds, mortgages, or other securities are: (If there are none, so state.)

Armer F. Ahlstrand, 335 Wilty Avenue, Rockford, Ill.; John D. Baur and Ruth E. Baur, 3239 Sutherland Ave., Indianapolis, Ind.; Mary M. Benham, 215 N. Senate, Indianapolis, Ind.; McFarland Benham, 601 Lemcke Building, Indianapolis, Ind.; Bertha Binninger and Frieda Binninger, 3510 Watson Road, Indianapolis, Ind.; Frieda Binninger and Bertha Binninger, 3510 Watson Road, Indianapolis, Ind.; A. W. Brayton, Jr., 3943 N. Illinois St., Indianapolis, Ind.; Lucile Lee Brayton, 3943 N. Illinois Street, Indianapolis, Ind.; R. M. Brotherson and Mary H. Brotherson, 2819 Grand Avenue, Joplin, Missouri; Wayne Burns, Jr., 7600 N. Meridian St., Indianapolis, Ind.; Edward D. James, 122 East Michigan, Indianapolis, Ind.; Edward D. James, Architect, Inc., 122 East Michigan Street, Indianapolis 4, Ind.; Grace Knox, 505 W. Oak Street, Zionsville, Ind.; John B. Kolling and Helma G. Kolling, 515 W. South Street, Crown Point, Ind.; Florence T. Lewis, 523 E. 51st Street, Indianapolis, Ind.; Katherine B. Lewis and Robert J. Lewis, 3640

Watson Road, Indianapolis, Ind.; Jack B. Moore, 128 W. North Street, Worthington, Ohio; Melvin R. Moser, 864 McGill Street, Orrville, Ohio; Frieda Neil and Harold Neil, 5247 32nd Terrace, North, St. Petersburg, Fla.; Edward E. Petri, c/o Petri Jewelry Company, Guaranty Bldg., Indianapolis, Ind.; Helen N. Sams, 3305 N. Meridian St., Indianapolis, Ind.; Howard W. Sams & Co., Inc., 2201 East 46th Street, Indianapolis, Ind.; Kenneth Swan, 4243 Broadway, Indianapolis, Ind.; Benjamin T. White, c/o Indianapolis Bond & Share Corp., 120 East Market Street, Indianapolis, Ind.

4. Paragraphs 2 and 3 include, in cases where the stockholder or security holder appears upon the books of the company as trustee or in any other fiduciary relation, the name of the person or corporation for whom such trustee is acting; also the statements in the two paragraphs show the affiant's full knowledge and belief as to the circumstances and conditions under which stockholders and security holders who do not appear upon the books of the company as trustees, hold stock and securities in a capacity other than that of a bona fide owner.

5. The average number of copies of each issue of this publication sold or distributed, through the mails or otherwise, to paid subscribers during the 12 months preceding the date shown above was: 75,046.

(Signed) MAL PARKS, JR., Bus. Mgr.  
Sworn to and subscribed before me  
this 28 day of September, 1960  
(Seal) Marian F. Newman, Notary Public

**NEW!**  
Only  
Grid Circuit  
Tube Tester  
with Full TV  
tube coverage!

**SECO GRID CIRCUIT TUBE TESTER**

Introducing the new Seco GCT-9—the first and only Grid Circuit Tester that offers you complete coverage of all TV tube types—including voltage amplifiers, power output and heater-type diodes, hundreds of Foreign and Industrial types as well as types with Grid, Plate or Cathode caps. Quickly lets you test for Grid Emission, Leakage, Shorts and Gas in one operation—indicates results instantly, visually on a 6AF6 "Eye" Indicator. In addition to conventional tests, the GCT-9 also offers two exclusive new testing features not found on any other tester: 1. Cathode Continuity Check; and 2. Complete Inter-Element Short Test, with shorts identified to pin numbers.

The new Seco GCT-9 is available in a sturdy metal case with exposed panel (GCT-9S): or mounted in a compact, portable carrying case (GCT-9W)—complete with easy to read tube set-up data. Equipped with new "Piggy-Back" adapter so you can mount either unit right to your tube caddy—unit may be removed for use in seconds! Wired and factory tested.

MODEL \$3295 NET GCT-9S MODEL \$3495 NET GCT-9W

WRITE TODAY! New literature available on all Seco test equipment.

**SECO SECO ELECTRONICS, INC.**  
5015 Penn Ave. So. • Minneapolis 19, Minn.

EAST CANADA: Daveco Agencies, Ltd., Montreal, Quebec  
WEST CANADA: Ron Merritt Co., Vancouver 1, B.C.

**SAVES your back... SAVES your time...**

**YEATS SHORTY DOLLY**  
for RADIO and TV

just 47 inches high for STATION WAGONS and PANEL PICK-UPS

Designed for TV, radio and appliance men who make deliveries by station wagon or panel truck... the short 47 inch length saves detaching the set for loading into the "wagon" or pick up. Tough, yet featherlight aluminum alloy frame has padded felt front, fast (30 second) web strap ratchet fastener and two endless rubber belt step glides. New folding platform attachment, at left, saves your back handling large TV chassis or table models. Call your YEATS dealer or write direct today!

**FOLDING PLATFORM**  
15 1/4" x 24 1/2" top.  
Snaps on or off.  
(Platform only)  
\$11.95

**FURNITURE PAD**

**"Everlast" COVER AND PADS**  
YEATS semi fitted covers are made of tough water repellent fabric with adjustable web straps and soft, scratchless white flannel liners. All shapes and sizes — Write

**TV COVER**

**YEATS APPLIANCE DOLLY SALES COMPANY**  
2103 N. 12th STREET MILWAUKEE, WISCONSIN

# PRODUCT REPORT

For further information on any of the following items, circle the associated number on the Catalog & Literature Card.

## Christmas-Tree Fuses (41V)



Ready for the holiday season, Littelfuse is offering a special fuse caddy containing replacements for the Type 8AG, 5-amp fuses used to protect strings of Christmas-tree lights. (The fuse holders are located in the AC line plug.) Dealer cost for the caddy (including 90 fuses, packaged in 18 metal boxes of 5 each) is \$3.13; the fuses are priced for resale at 29c per box.

## Reference Voltage Source (42V)



The eight outputs of the Malloy "Voltage Reference Battery" are 1.35, 2.70, 4.05, 5.40, 6.75, 8.10, 9.45, and 10.80 volts—all accurate within  $\pm 1/2\%$  throughout the life of the unit (normally at least three years). This mercury battery is useful as a reference source in instrument calibration, voltage measurement, thermistor bridges, bias circuits, pH testing, and other applications requiring a stable low-voltage DC output. Price is \$39.50, including carrying case.


urement, thermistor bridges, bias circuits, pH testing, and other applications requiring a stable low-voltage DC output. Price is \$39.50, including carrying case.

## Lamp-Magnifier Combination (43V)



The Swing-O-Lite "Inspector" features a 5" diameter magnifying glass with 13" focus, surrounded by a 22-watt ring-type fluorescent lamp. Three different sizes, with free-swiveling arms reaching 24", 33", and 45", are respectively priced at \$33, \$34.50, and \$36. Optional accessories include a convenience outlet in the base, a higher-power magnifying lens, and special colors besides standard grey, brown, or desert tan.

## Repairs for Tuning Studs (44V)

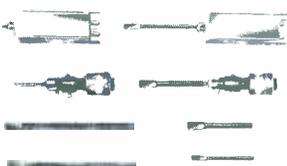


When you find the slotted tip broken off the threaded adjustment stud of a width or horizontal linearity coil, horizontal oscillator transformer, IF can, etc., attaching a Superex Model A.G.C. Repair Shaft will provide a convenient means of rotating the stud—thereby eliminating the need for replacing the coil. A repair shaft assortment, priced at 79c, contains both 4-40 and 6-32 sizes in six lengths.
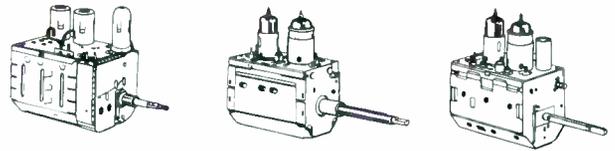
## Yoke Loosener (45V)



A spray application of Walsco "Ez-Off Frozen Yoke Remover" will free a deflection yoke which has become stuck to the neck of a TV picture tube. After the solvent has been allowed to penetrate the windings for a few minutes, the yoke can be slipped off with only slight pressure. This chemical (Catalog No. 215-03) is priced at 99c per aerosol spray can.



## TUNERS REPAIRED \$8.50

24-Hour Service 6-Month Warranty  
Repair Charge includes  
**ALL Replacement Parts**

SARKES TARZIAN, INC., pioneer in the Tuner Manufacturing business, offers fast, dependable, factory repair service on all makes and models. Cost—\$8.50 per unit. \$15 for UV combinations. Now offering 6-month warranty against defective workmanship and parts failure due to normal usage. Tuners repaired on approved, open accounts. Replacements available at low cost on tuners beyond practical repair.

Tarzian-made tuners easily identified by this stamping. When inquiring about service or replacements for other than Tarzian-made tuners, always give tube complement . . . shaft length . . . filament voltage . . . series or shunt heater . . . IF frequency, chassis identification. And, allow a little more time for service on these tuners. See your distributor, or use this address for fast, factory repair service:

SERVICE MANAGER • TUNER DIVISION  
DEPT. A



# SARKES TARZIAN INC

east hillside drive • bloomington, indiana  
edison 2-7251

Mfgs. of Tuners, Semiconductors, Air Trimmers, FM Radios, Audio Tape, and Broadcast Equipment

**MOST COMPLETE TESTER AVAILABLE!**

## WON'T BE OBSOLETE—OFFERS EVERY IMPORTANT TEST YOU NEED!

Finest, fastest tester at a popular price—and here's why! Dynamic Mutual Conductance Test on pre-wired chassis—best method for testing high transconductance amplifiers! Cathode Emission Test by free point selector system—best method for testing power output, pulse amplifiers, and damper tubes! Nationally accepted Grid Circuit Test patented by Seco—up to 11 simultaneous checks for leakage, shorts and grid emission. In carrying case with handy flip chart for tube set-up data.

**MODEL 107—Wired and Tested . . . \$139.50 NET**



Check output tube cathode current fast!  
Safeguard against horizontal output tube overload. Place in circuit in seconds—no unsoldering. Front panel lists essential information.  
**MODEL HC-6 . . . \$12.95 NET**

WRITE TODAY! New literature available on all Seco test equipment.

**SECO SECO ELECTRONICS, INC.**  
5015 Penn Ave. So. • Minneapolis 19, Minn.

**EAST CANADA: Davaco Agencies, Ltd., Montreal, Quebec**  
**WEST CANADA: Ron Merritt Co., Vancouver 1, B.C.**

# BUY PYRAMID! GET MORE!




Only Pyramid offers you so much! Only Pyramid gives you highest quality capacitors plus so many "all new" extras.

### THE VU-PAK

An entirely new way to package capacitors . . . clear plastic tubes, plainly labeled and packed with the highest quality electrolytic twist-mount capacitors. Each re-usable Vu-Pak comes with a blank label, ideal for storing small parts and tools on your bench or in your tool kit.
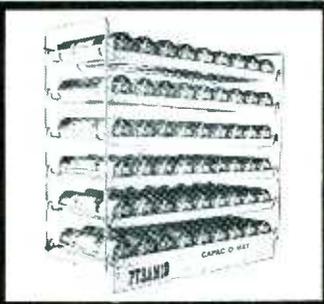
### EXTRA OFFER!

Save 50 Vu-Pak labels and get the fabulous new Pyramid storage rack the Capac-o-mat, at tremendous savings from your authorized Pyramid distributor. The Capac-o-mat fits right on your shelf, is dust-free and holds 54 Vu-Paks.



### JEWEL BOX


Handsome tan plastic, high impact cabinet with 9 drawers, contains 45 assorted Mylar\* paper Gold Dip capacitors, type 151. Practical . . . convenient . . . for storage in your shop, or home. Actual value of the Jewel Box with 45 Gold Dip capacitors—\$19.50, dealer net only \$9.25.



Gold Dip capacitors are also available in Clear-Vu paks . . . 5 to a package. Find them on Pyramid's new Whirl-o-mat on your favorite parts distributor counter.
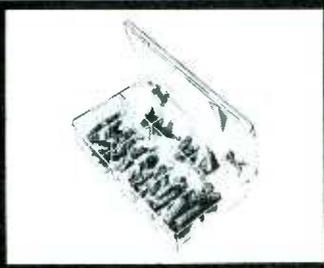
### "GOLD STANDARD" 111 KIT

Clear lucite hinged box containing 75 Pyramid's popular assorted Gold Standard Mylar\* capacitors. You'll find so many uses for the Gold Standard 111 Kit. Actual value is \$26.00, dealer net only \$13.00.



### 515 LYTIC-KIT

Hinged cover, clear lucite box with 15 assorted miniature low voltage electrolytic capacitors for transistorized circuit replacements, type MLV. This Kit is a constant companion to any busy serviceman. Actual value, \$20.60, dealer net only \$10.30.




## PYRAMID ELECTRIC COMPANY

DISTRIBUTOR DIVISION: UNION CITY, NEW JERSEY  
Factories: Gastonia, North Carolina • Darlington, South Carolina  
In Canada: Wm. Cohen, Limited, 8900 Tanguay Street, Montreal  
Export: Morhan Exporting Co., 485 Broadway, New York 13, N. Y.
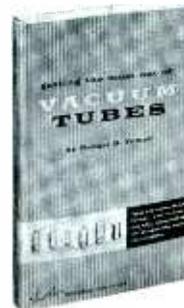
### Book on Tube Usage (46V)

"Getting the Most Out of Vacuum Tubes"—a new book written by Bud Tomer and published by **Howard W. Sams & Co., Inc.**—describes and classifies various types of tube failures, points out possible causes, and suggests ways of lengthening tube life by proper application and maintenance. The author also explains why so many different tube types are in use, goes into detail about the capabilities and limitations of tube testers, and answers the question, "Can a tube's future life span be predicted?"




### Heavy-Duty Communication Tower (47V)

The **Rohn No. 55** communication antenna tower can be erected to a maximum height of 450', allowing for a wind load of 30 lbs. per sq. ft., and an antenna size of approximately 12 sq. ft. Sections 10' long, which fit together with sleeve joints, have an 18½" equilateral-triangle cross-section and electrically-welded "zig-zag" bracing. The entire section is hot-dipped galvanized after fabrication.


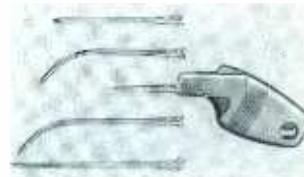
### Solder Feeder (48V)

The "Kormat" wire-solder dispensing tool, manufactured by **International Electronic Research Corp.**, eliminates the acid and oil contamination of solder joints which sometimes occurs when solder is hand-held. The probe tip is fastened to the body of the dispenser with a bayonet connector to permit quick interchange of various straight and curved tips for different jobs. Enough solder to last many hours is wound on a spool inside the handle. The unit is priced at \$5.95, complete with one standard-style tip.



### Sound Projector (49V)

Designed for use in churches, hotel lobbies, and other locations where an attractive appearance is important, the **Atlas DC-5 "DeCor"** sound projector has an exterior finish of brushed natural aluminum. The bell can be swiveled both horizontally and vertically. A 5" cone speaker provides low-level sound reinforcement with low-frequency response extending down to 120 cps. Suggested retail price is \$22.00.




### New Panel for Tube Testers (50V)

To enable **B & K** multiple-socket tube testers to check a greater number of tube types, the manufacturer has designed a Model 610 Test Panel which can be installed to provide expanded testing facilities for radio-TV tubes, hybrid auto-radio types, popular European designs, and most industrial tubes. The unit comes in three versions, for use with the Model 500, 550, and 650 tube testers. Net price is \$49.95.




### Wall-Mounted Speaker (51V)

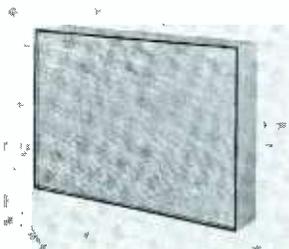

3" deep, 12" high, and 18" wide, the Utah PT-2 extension-speaker baffle contains a 6" x 9" inverted speaker, a 3" x 5" tweeter, and a bass-relief port. A choice of blonde or mahogany finish is offered, and "S" hooks for wall mounting are furnished. Over-all impedance is 8 ohms; power-handling capacity is 8 watts; retail price is \$32.50.

### Staple Gun (52V)

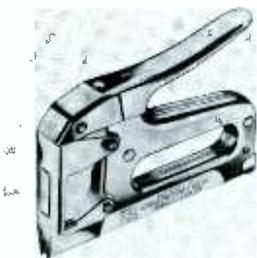


The tapered striking edge of the Arrow T-25 staple gun enables it to drive staples in tight places such as corners and narrow grooves. This gun uses a new type of round-top staple which fits snugly over low-voltage wires and cables without mashing the insulation. Staples of two different leg sizes, 7/16" and 9/16", are accepted by the same machine.

### Component Substitution Box (53V)



The Mercury Model 500 "Component Substitutor" (price: \$29.95) offers 10 values of capacitance from 100 mmf to .5 mfd, plus 10 electrolytics from 4 to 330 mfd; 20 values of resistance ranging from 33 ohms to 10 megohms; a power resistor, continuously variable up to 5000 ohms; and continuously variable bias voltages up to  $\pm 15$  volts. Substitutes are also furnished for crystal diodes and power rectifiers with ratings up to 55 ma.

### Wire-Wound Resistors (54V)

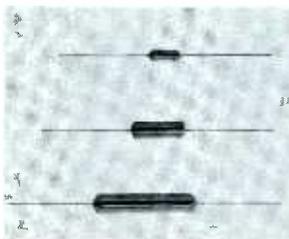

Axial-lead "Greenohm V" power resistors, in which the conventional terminal lugs have been omitted to save space, are newly available from Clarostat. There are three series, the VC3D, VC5E, and VC10F, with power ratings of 3, 5, and 10 watts (in that order). Standard resistance tolerance is  $\pm 5\%$  for values of 1 ohm or higher, and  $\pm 10\%$  for values under 1 ohm.

### Surge Protectors (55V)



Damaging current surges, which occur when equipment is first turned on, are limited with the ATR "Electronic Tube Protector." Unit is available in two types — Model 250 (shown; \$3.95) for plugging directly into an AC wall outlet, and Model 300 (with extension cord; \$4.95)

for mounting anywhere up to 6' away from the outlet. Both are fuse-protected and can be used with 100- to 300-watt loads.

### Component Price Information (56V)

A new edition of "Dave Rice's Official Pricing Digest" (Vol. 4, No. 1) has been announced by Electronic Publishing Co. List or suggested retail prices are given for more than 63,000 components; also provided is a table of national and regional average TV service charges. The 300-page book is corner-punched so it can be suspended from a cord; its 3 3/4" x 9 13/16" size also makes it suitable for carrying in tube caddy or toolbox. Price is \$2.50 per copy.

**CORRECT  
OVER VOLTAGE**

**CORRECT  
LOW VOLTAGE**



## and get BETTER PERFORMANCE with this ACME ELECTRIC VOLTAGE ADJUSTOR


TV sets, hi-fi's and other electronic equipment operate best when voltage holds closely to the normal 115-117 volts for which they were designed. Over-voltage and/or under-voltage affects the performance of the tubes and the life expectancy of all other components. Why fight an off-standard voltage condition? Correct it with an Acme Electric T-8394M Voltage Adjustor.

Corrects voltage over a range from 95 to 125 volts to normal 115/117 volts, simply by turning a regulating switch. Includes voltmeter which indicates output voltage; cord and plug and built-in, plug-in receptacle. Tell your supply dealer you want the Acme Electric T-8394M Voltage Adjustor. No other so compact, complete, practical, inexpensive.

SA 3402-1849

**ACME ELECTRIC CORPORATION**  
9411 WATER STREET CUBA, N. Y.

**Acme Electric**

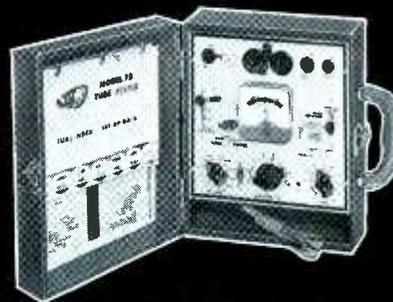

**SPOTS  
TUBE  
FAULTS  
FAST!**

### LOW COST... HIGHLY ACCURATE... COMPLETE TV TUBE COVERAGE!

Faster, handier than any other tester! Checks all modern TV tubes and heater type radio tubes, including hybrid types. Incorporates patented Seco Grid Circuit Test—reliable Cathode Emission Test—also checks filament continuity and provides open element test. Complete in rugged carrying case, with flip chart for quick set-up data.

**MODEL 78—Wired and tested.....\$69.50 NET**



Troubleshoots TV deflection circuits fast!

Checks complete horizontal circuit—quick "yes" or "no" answer on condition of flyback transformer and yoke—100% accuracy.

**MODEL FB-4.....\$38.95 NET**

**WRITE TODAY!** New literature available on all Seco test equipment.



**SECO ELECTRONICS, INC.**  
5015 Penn Ave. So. • Minneapolis 19, Minn.

**EAST CANADA: Daveco Agencies, Ltd., Montreal, Quebec**  
**WEST CANADA: Ron Merritt Co., Vancouver 1, B.C.**

November, 1960

Acme Electric Corp. .... 87  
 Aerovox Corp. .... 74  
 American Television & Radio Co. (ATR) ..... 12  
 Arco Electronics ..... 9  
 B & K Mfg. Co. .... 17, 51  
 Belden Mfg. Co. .... 43  
 Berns Mfg. Co. .... 58, 64  
 Bogen-Presto ..... 71  
 Bussmann Mfg. Co. .... 35  
 CBS Electronics ..... 25  
 Castle TV Tuner Service ..... 50  
 Centralab, A Div. of Globe-Union, Inc. .... 44  
 Champion DeArment Tool Co. .... 60  
 Duotone Co., Inc. .... 58  
 EICO ..... 20  
 Electronic Chemical Corp. .... 64  
 Electronic Publishing Co. .... 68  
 Gernsback Publications ..... 62  
 Hamilton-Hall, Inc. .... 52  
 Hickok Electrical Instrument Co. .... 63  
 I. H. Mfg. Co. .... 68  
 JFD Electronics Corp. .... 19  
 Jackson Electrical Instrument Co. .... 45, 88  
 Jensen Mfg. Co. .... 55  
 Jerrold Electronics Corp. .... 2nd cover  
 Littelfuse, Inc. .... 4th cover  
 Los Angeles Tuner Exchange ..... 64  
 Mallory & Co. Inc., P. R. .... 63, 65, 67, 69  
 Merit Coil & Transformer Corp. .... 59  
 Motorola Training Institute ..... 66  
 Oelrich Publications ..... 80  
 Ohmite Mfg. Co. .... 70  
 Oxford Components, Inc. .... 82  
 Philco Corp. — Accessories Div. .... 22-23  
 Precision Tuner Service ..... 70  
 Pyramid Electric Co. .... 86  
 Quam-Nichols Co. .... 42  
 Quietrole Co. .... 74  
 RCA Electron Tube Div. ... 52, 58, 61, 74, 79, 82, 3rd cover  
 RCA Institutes, Inc. .... 16  
 RCA Sales Corp. .... 49  
 Raytheon Co. .... 57  
 Rohn Mfg. Co. .... 21  
 Sampson Co., The ..... 48  
 Sams & Co., Inc., ..... 76, 77, 80, 82  
 Howard W. ....  
 Sarkes Tarzian, Inc. .... 85  
 Tuner Div. ....  
 Seco Electronics, Inc. .... 84, 85, 87  
 SENCORE ..... 14-15, 36, 37, 38, 39, 40, 41  
 Setchell-Carlson, Inc. .... 18  
 Shell Electronics Mfg. Co. .... 81  
 Simpson Electric Co. .... 78  
 Sonotone Corp. .... 75  
 Sprague Products Co. .... 10  
 Superex Electronics Corp. .... 50  
 Swing-O-Lite Inc. .... 68  
 Switchcraft, Inc. .... 80  
 Sylvania Electric Products, Inc. ....  
 Electronic Tube Div. .... 27  
 Technical Appliance Corp. (TACO) ..... 13  
 Telex, Inc. .... 56  
 Triad Transformer Corp. .... 54  
 Tung-Sol Electric, Inc. .... 47  
 Vaco Products Co. .... 72  
 Vidair Electronics Mfg. Corp. .... 62  
 Walsco Electronics Mfg. Co. .... 83  
 Weller Electric Corp. .... 73  
 Winegard Co. .... 46  
 Yeats Appliance Dolly Sales Co. .... 84

ANTENNAS & ACCESSORIES

- 1V. JFD — 1960 Exact-Replacement Antenna Guide for Portable and Toteable TV sets (20 pages), compiled and edited by Howard W. Sams & Co., Inc. Gives TV receiver model number, manufacturer's antenna part number, and model number of corresponding JFD exact-replacement antenna. Also Form 940 dealer catalog illustrating and describing 1960 line of natural silver and gold anodized Hi-Fi TV antennas, mounts, masts, and accessories. See ad page 19.  
 2V. JERROLD—"Products For Better Television," a 12-page catalog of home TV reception aids, TV distribution systems, antenna system test equipment and accessories. See ad 2nd cover.  
 3V. ROHN — New folder describing complete line of antenna towers and allied accessories; also descriptive literature on heavy-duty communications towers. See ad page 21.  
 4V. WINEGARD — Descriptive catalog on new A-400 distribution amplifier, including a schematic and specifications for the unit. See ad page 46.

AUDIO & HI-FI

- 5V. ATR — Literature on Universal Inverters, ideal for operating standard 110-volt AC public-address systems in mobile applications. See ad page 12.  
 6V. DUOTONE — "How-to—" booklet on identifying and replacing phono needles; wall chart of replacement-needle data; needle identification and replacement catalog to bona fide dealers and repairmen. See ad page 58.  
 7V. ERCONA — Illustrated brochure and price list on Mark III Reslo studio-type ribbon microphones featuring replaceable ribbon cartridges.  
 8V. SONOTONE — New cost sheet covering all products; specification sheet with color illustration of CM-17 Flex-Mike for language labs; new catalog sheet on 9T series of ceramic stereo cartridges. See ad page 75.  
 9V. SWITCHCRAFT — New-product bulletin No. 101 on ultra-miniature Micro-Jax for use as phone jacks on transistor radios. See ad page 80.  
 10V. TELEX — Literature on stereo and monophonic headsets and accessories for communications, educational, and entertainment use; also catalog sheets and hook-up information on under-pillow speakers. See ad page 56.

COMPONENTS

- 11V. CORNELL-DUBILIER — Substitution cross-index of twist-prong capacitors, listing recommended C-D replacements for Aerovox, Mallory, Pyramid, Sangamo, and Sprague types.  
 12V. SPRAGUE — Distributor Stock Catalog C-613 on line of capacitors, resistors, printed-circuit networks, and test equipment. See ad page 10.

FUSES

- 13V. BUSSMANN — 24-page booklet giving detailed information on complete line of BUSS and FUSETRON Small Dimension fuses and fuse holders — the ones most used in protecting electronic equipment. See ad page 35.  
 14V. LITTELFUSE — Information on caddy of fuses for Christmas-tree lights. See ad 4th cover.

PROMOTIONAL AIDS

- 15V. SYLVANIA — Booklet No. 1028, "Can Local Sylvania Advertising Really Help My Business?" with true case histories telling how other dealers have made money. Points the way for every service dealer to multiply business with local ads. See ad page 27.

SEMICONDUCTORS

- 16V. CBS ELECTRONICS — Reference Chart PF-384 for semiconductors, giving basic data on CBS transistors and diodes. See ad page 25.

SERVICE AIDS

- 17V. CASTLE TUNER — Leaflet describing fast overhauling service on television tuners of all makes and models. See ad page 50.  
 18V. INJECTORALL — 1960 catalog of electronic chemicals.  
 19V. PRECISION TV TUNER — Information on repair and alignment service available for any type of TV tuner. See ad page 70.  
 20V. SWING-O-LITE — Flyer on Inspector bench light with built-in 5" diameter magnifying glass surrounded by 22-watt shadow-free fluorescent tube and mounted on omnidirectional swivel arm. See ad page 68.  
 21V. YEATS — Information about dolly for delivering TV and hi-fi sets or appliances, and about padded TV, radio, and appliance covers. See ad page 84.

SPECIAL EQUIPMENT

- 22V. ACME ELECTRIC — Catalog 091-BL01 giving detailed information on automatic voltage stabilizers and manual voltage adjusters for TV receivers and other electronic applications. See ad page 87.  
 23V. DIALIGHT CORP. — Brochures, "Lights That Enlighten" and "Data-lites," describing a variety of applications for Dialco pilot lights as read-out indicators in data processing, instrumentation, and automation. Legend-bearing lights are presented, as well as Data Strip and Data Matrix multiple-light assemblies.  
 24V. SCHOBER — Catalog of electronic-organ kits; also descriptive sheet on AT-1 Autotuner and OT-1 Organ Tester for use in electronic organ maintenance.

TECHNICAL PUBLICATIONS

- 25V. ELECTRONIC PUBLISHING — Brochure describing all-new edition of Dave Rice's Official Pricing Digest, including list prices on over 63,000 components, plus national and regional average service charges. See ad page 68.  
 26V. GERNSBACK—Descriptions of Gernsback Library books. See ad page 62.  
 27V. MOTOROLA — Complete brochure describing Motorola Institute training course on two-way radio communications; sample lesson SA-7 on transistorized receiver circuits. See ad page 66.  
 28V. RCA INSTITUTES — Complete catalog of home-study training in radio and electronic fundamentals, TV servicing, automation, and transistors; also comprehensive electronic course selection at Resident Schools in New York City and Los Angeles. See ad page 16.  
 29V. HOWARD W. SAMS — Literature describing all current publications on radio, TV, communications, audio and hi-fi, and industrial electronics servicing. See ads pages 76, 77, 80, 82.

TELEVISION RECEIVERS

- 30V. SETCHELL-CARLSON — Attractive folder designed for distribution to customers, with photographs and descriptions of 11 basic models in current TV line — including combinations formed by adding some or all of the following plug-in components: AM radio, FM radio, phono, stereo amplifier, and remote stereo speaker cabinet. Plug-in principle is also used in series of separate stereo and monophonic hi-fi systems. See ad page 18.

TEST EQUIPMENT

- 31V. B & K — Bulletin AP16-R gives information on new Model 1076 Television Analyst, Models 1070 and A107 Dyna-Sweep Circuit Analyzers, Models 550, 650, 675, and new 685 Dyna-Quik dynamic mutual conductance tube testers, new Model 610 Test Panel, new Model 160 Transistor Tester, and Model 440 CRT rejuvenator-tester. See ads pages 17, 51.  
 32V. ELECTRO PRODUCTS LABS — Catalog sheet giving data on complete line of DC power supplies, including kits and regulated transistorized units.  
 33V. HICKOK — Folders describing Model 209A VTVM, plus line of tube testers, oscilloscopes, transistor testers, VOM's, and signal generators. See ad page 53.  
 34V. MERCURY — Master catalog on complete test-equipment line, plus information on new service aids.  
 35V. SECO — New 16-page booklet illustrating tube testers, dynamic transistor checker, two-way radio test set, and several time-saving service aids. See ads pages 84, 85, 87.  
 36V. SENCORE — New booklet, How to Use the SS105 Sweep Circuit Troubleshooter, plus brochure on complete line of time-saver instruments. See ads pages 14-15, 36, 37, 38, 39, 40, 41.  
 37V. SIMPSON — Brochure describing VOM's, DC VTVM, color-bar generator, and many other types of radio and TV test equipment. See ad page 78.

TOOLS

- 38V. BERNS — Data on 3-in-1 picture-tube repair tool, Audio Pin-Plug Crimper, and Ion adjustable beam bender. See ads pages 58, 64.  
 39V. L.I. ELECTRO-LABS — Catalog sheet on the Model A-1000 Solder-Pen, a 30-watt pencil-type soldering iron. When not in use, the removable handle fits over the tip, thus allowing the iron to be carried around while still hot.  
 40V. VACO — New 8-page catalog on specialty tools, entitled "Choose Your Cards," illustrating 34 different carded displays of tools. See ad page 72.




MODEL 598											
Tube Type	File	D.	E	File Test	A	B.	C.	H.I. D.	E	F	G
6BT5	6-3	123	AS7	17	XZ	63	31*	7	3	4	31
6BE6	6-4	123	AS7	17	XZ	63	31*	7	3	4	31
15BW6	15	AC123	567	45	XZ	15	31*	4	5	5	60
17BW6	17	123	445	15	XZ	17	4	5	1	22	15
34GD5	34	C123	467	15	VW	35	32	2	4	7	5
34GD5	34	C123	467	15	VW	35	32	2	4	7	5

SUPPLEMENT LATEST ROL CHART MARZIC

SUPPLEMENT LATEST ROL CHART MARZIC

MODEL 658									
Tube Type	Sec	Heater	H-K	p-G	Plate	Grid	Test	Heater	Current
6BT5	T	6.4J	123	457	17R	10W*	—	—	—
6BE6	P	10.6F	123	455	210	80V*	A15.6L	1.000	—
15BW6	T	18.6L	123	457	17R	20W*	—	—	—
17BW6	T	18.6L	123	455	190	20W*	—	—	—
34GD5	P	35E	123	467	35E	70V*	—	—	—

SUPPLEMENT LATEST ROL CHART 658

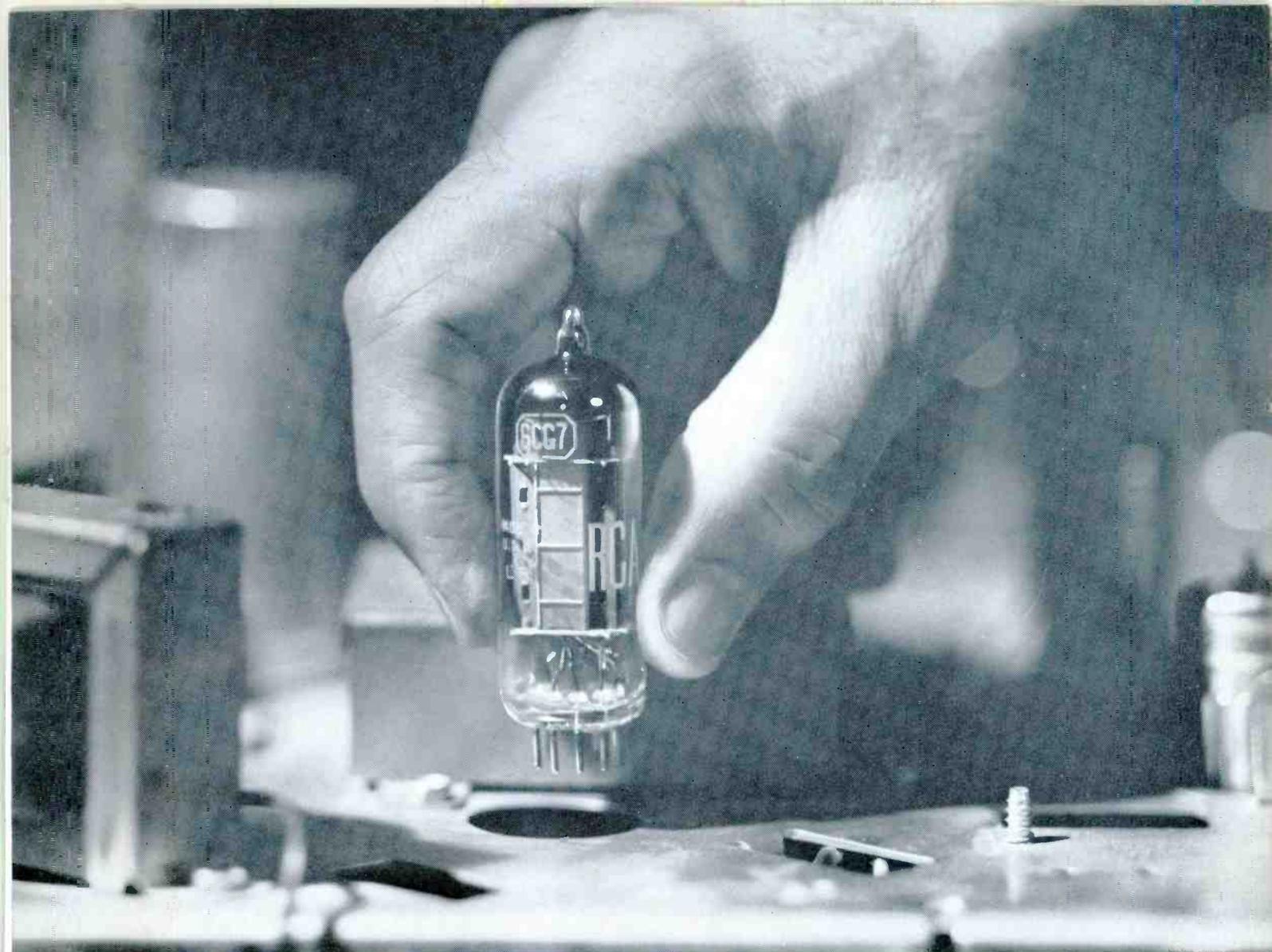

## WHEN YOU REPLACE A TUBE . . .

You have a lot at stake each time you replace a receiving tube in a customer's set. Your professional reputation, your customer's confidence, your day's profits—even future business—all depend on the quality of that replacement tube.

It is RCA's constant aim to provide receiving tubes you can install with confidence. To this end, RCA carefully controls every step of the tube making process from initial design to final test.

**QUALITY BY DESIGN**—Some of the foremost tube experts in the industry collaborate on each new RCA tube design. Engineers, chemists, physicists, metallurgists, production specialists, field representatives, all contribute their own skills and knowledge before a new RCA tube design ever leaves the drafting board.

**IMPROVED QUALITY FROM NEW AND IMPROVED MATERIALS**—All parts and materials in RCA tubes are either *produced* or *processed* by RCA under strictest quality control. Moreover, RCA scientists search constantly for new and better materials which will still further improve performance of RCA tubes. Many tube types you install today benefit from new cathode and plate materials developed in RCA labs.

**QUALITY IN MANUFACTURING**—Because tube construction is just as important as design and materials, RCA maintains a system of supervisory microscopic inspection at key points on every production line to detect any flaw in assembly. And to minimize the chance of human error, RCA has automated certain critical steps in tube production.

**QUALITY BY TESTING AND CONTROL**—Before shipment, *every single RCA receiving tube* is factory-tested for every significant characteristic. *A tube that fails one single test is rejected and destroyed. So there is no such thing as a "second" when you buy RCA.* In addition, thorough aging of tubes and rating-lab tests assure strict adherence to performance specifications.

This is why YOU CAN REPLACE WITH CONFIDENCE with RCA tubes . . . and why RCA tubes give you an extra advantage on every service job. Electron Tube Division, Harrison, N. J.



The Most Trusted Name in Electronics  
RADIO CORPORATION OF AMERICA

