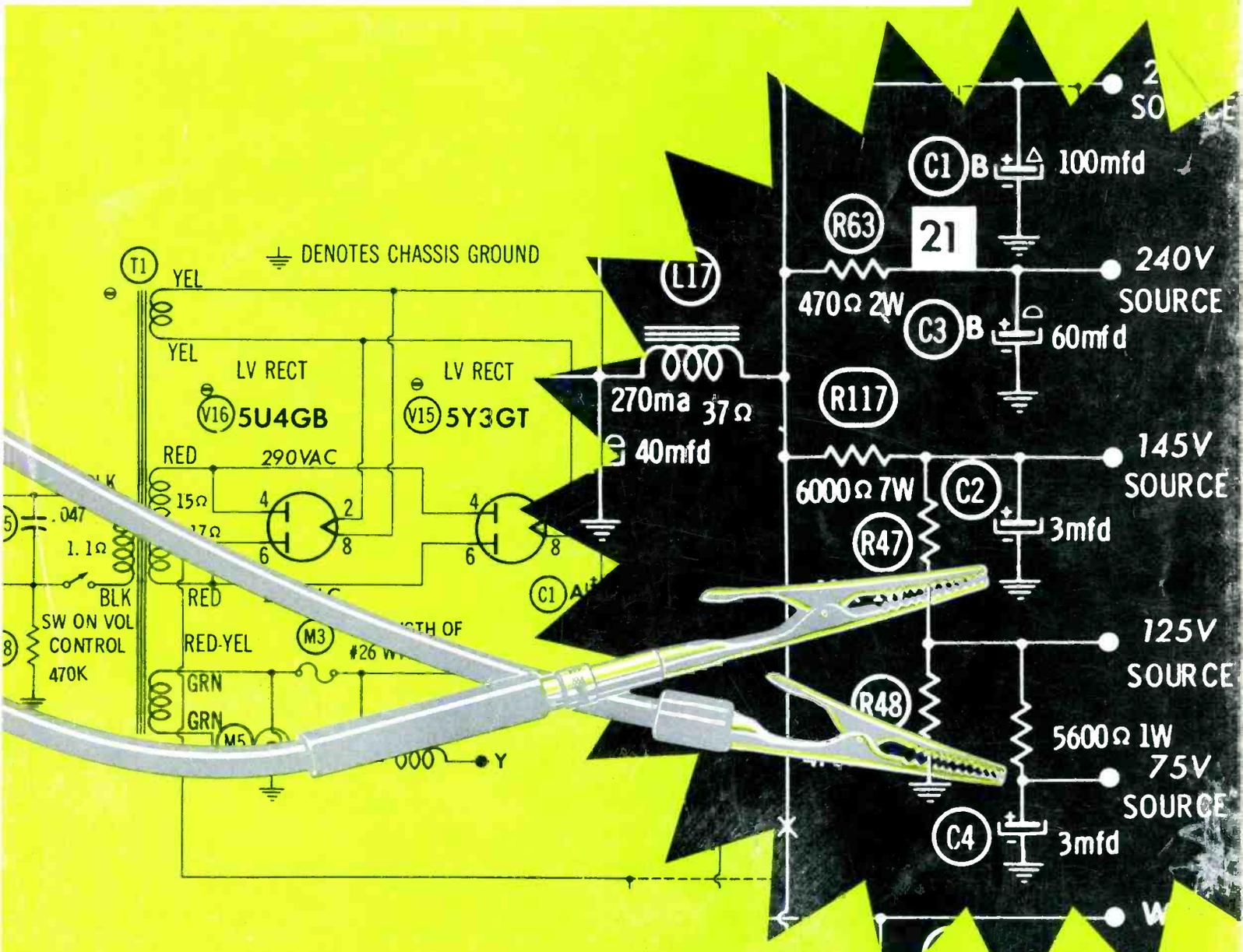




# PHOTOFACT REPORTER

## including Electronic Servicing




### Debugging B+

Transformer Tactics

- A Good Generator Sweeps Clean
- Colors Adrift? Check Color Sync
- Calibrate Your Own Voltmeters
- "Symfact" Charts

LA OK 7456 1264  
 WM. M. DAVIS  
 RAC. & TV SERV.  
 118 RIVERSIDE AVE.  
 CARON CITY, COLO.

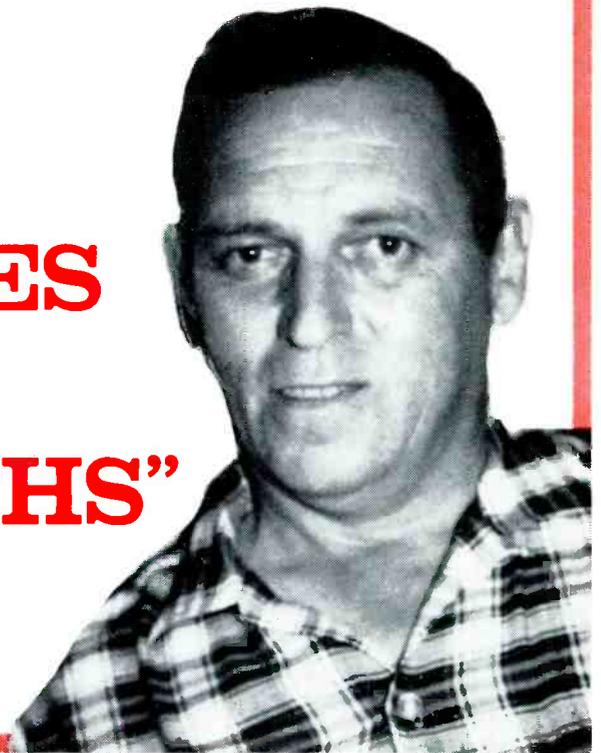**"WE SOLD  
\$3000  
WORTH OF  
POWERMATES  
DURING THE  
'SLOW' MONTHS"**



**CHRIS MARCOTTE**

Capeway TV Service Co., Harwich Port, Mass.


**POWERMATE's unexcelled performance plus Jerrold's powerful LOCAL promotions achieved this for Chris...**

Chris Marcotte worked closely with his Jerrold distributor on a powerful promotion program that appealed *directly* to his Cape Cod customers. Jerrold newspaper mats pre-sold the POWERMATE where it would do the most good—in Chris's service area. Jerrold also supplied store banners, counter displays, envelope stuffers—in short, a complete package that helped Chris tell the POWERMATE story most effectively to his neighbor-customers. This well-

planned LOCAL promotion, plus an unbeatable product, turned the trick for Chris.

Here's what Chris says: "The Jerrold POWERMATE outperforms all other transistorized antenna amplifiers we've tested under actual reception conditions. Boston and Providence, both 70 air miles away, come in free from any snow 90% of the time. We're watching Portland, Maine, a distance of 180 miles . . . in *COLOR*—very acceptable."

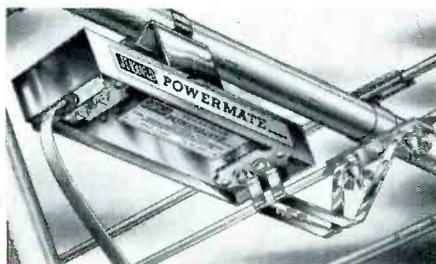Chris Marcotte's success story is being repeated over and over throughout the country. So get on the POWERMATE bandwagon now! Let Jerrold set up your LOCAL promotion. Write now for the name of your nearest Jerrold distributor.



**TRANSISTOR  
POWERMATE  
ANTENNA AMPLIFIER**

**\$3995**  
LIST

**JERROLD ELECTRONICS CORPORATION**  
A subsidiary of THE JERROLD CORPORATION  
Philadelphia 32, Pa.



Jerrold Electronics Corporation  
Distributor Sales Division, Dept. IDS-255  
Philadelphia 32, Pa.

I want Jerrold to promote the POWERMATE in my LOCAL area. Send me the name of my nearest distributor.

Name \_\_\_\_\_

Address \_\_\_\_\_

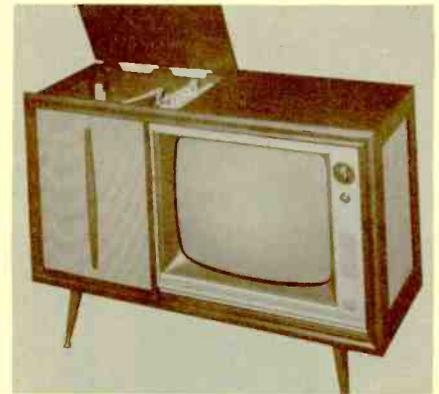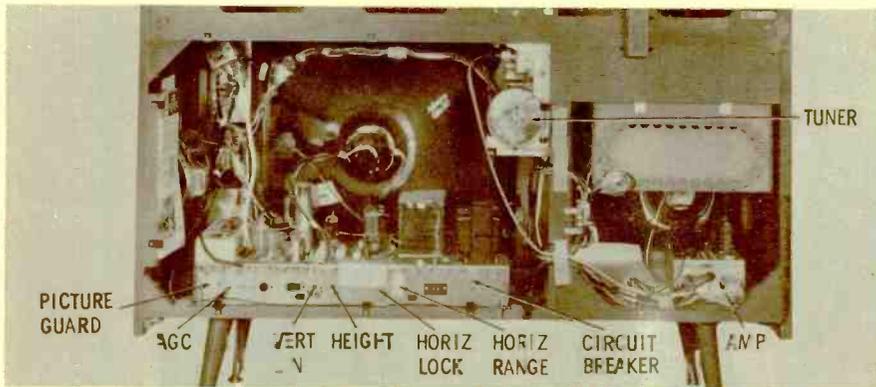City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_



**Admiral Model STF351**  
**TV Chassis 19C8B**  
**FM-AM Chassis 6S3C**  
**Amplifier Chassis 2PA5**




This combination model makes use of an FM-AM tuner, a stereo amplifier, and a 23" TV chassis. All operating voltages for the tuner are furnished by the power supply (5U4GB rectifier) on the TV chassis. The amplifier obtains B+ from the TV, but has its own filament supply. The B+ rectifier circuit is protected by a circuit-breaker mounted on the rear of the chassis, while the TV filament circuit includes a wire-link fuse (note physical location shown in the photo).

Plugs and sockets are plentiful in this set, and you should take note of where they are connected, before you start unplugging. The TV chassis can be operated independently of the tuner or amplifier, but if trouble develops in either of these latter chassis, operational checks will require that they be connected to the TV chassis.



Like the other TV sets in Admiral's '62 line, this receiver uses a 6K11 compactron as the AGC keying tube, sync separator, and noise limiter. A 6EW7 (a 9-pin miniature tube with an oversized glass envelope) is used in the vertical multivibrator-output stage, and the horizontal multivibrator is a 6CG7 (alternate 6FQ7). AFC voltage for the horizontal stage is developed by a selenium dual diode. Replacement of this unit is quick and easy; the diode (see photo) plugs into a socket mounted on one of the two printed circuit boards used in this set. A 1G3GT high-voltage rectifier and a 6AX4GTB damper round out the tube complement of the horizontal sweep section. (Some chassis may come equipped with a 6DE4 in the damper stage, rather than a 6AX4.)

Controls for on-off-volume, channel selection, fine tuning, brightness, and vertical hold are all mounted on the front. The contrast control is mounted on the underside of the chassis, but connects to a front operating knob via a plastic extension shaft. Controls mounted on the rear include PICTURE GUARD (noise), AGC, vertical linearity, height, horizontal lock (frequency coil), and horizontal range. The width is controlled by a metal sleeve placed between the yoke and the CRT.

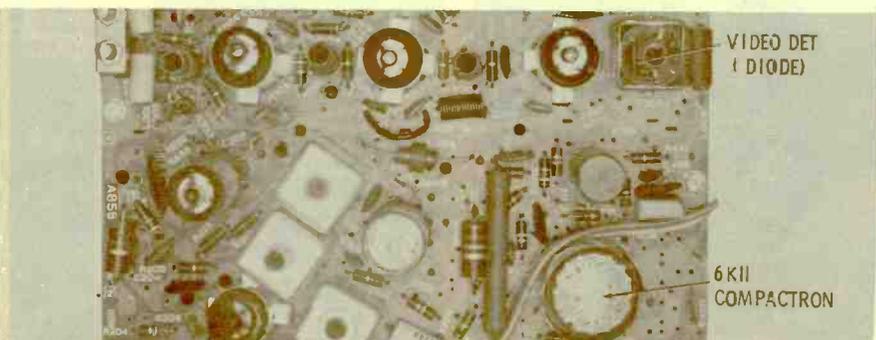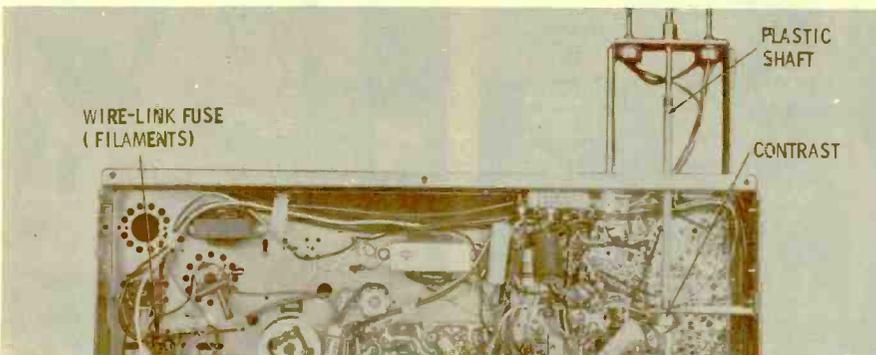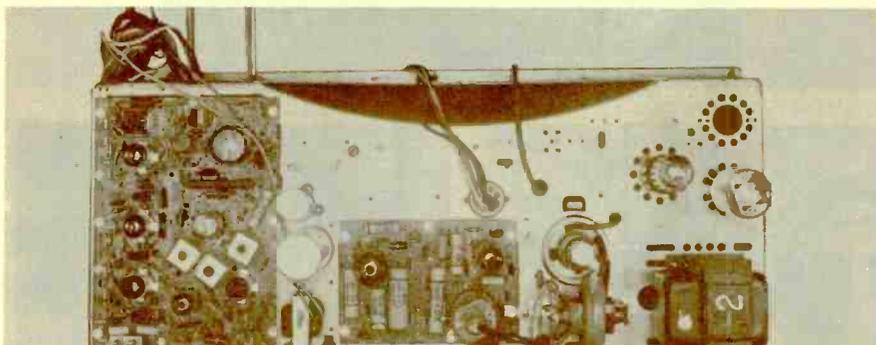The picture tube (a 92° 23AUP4) and the chassis can be removed, as a single assembly, from the front of the cabinet.



PF REPORTER for September, 1962, Vol. 12, No. 9. PF REPORTER is published monthly by Howard W. Sams & Co., Inc., 4300 W. 62nd St., Indianapolis 6, Indiana. Second-class postage paid at Indianapolis, Indiana. 1, 2 & 3 year subscription prices: U.S.A., its possessions, and Canada: \$4.00, \$7.00, \$9.00. All other countries: \$1.00, \$9.00, \$12.00. Current single issues 35c each; back issues 50c each.

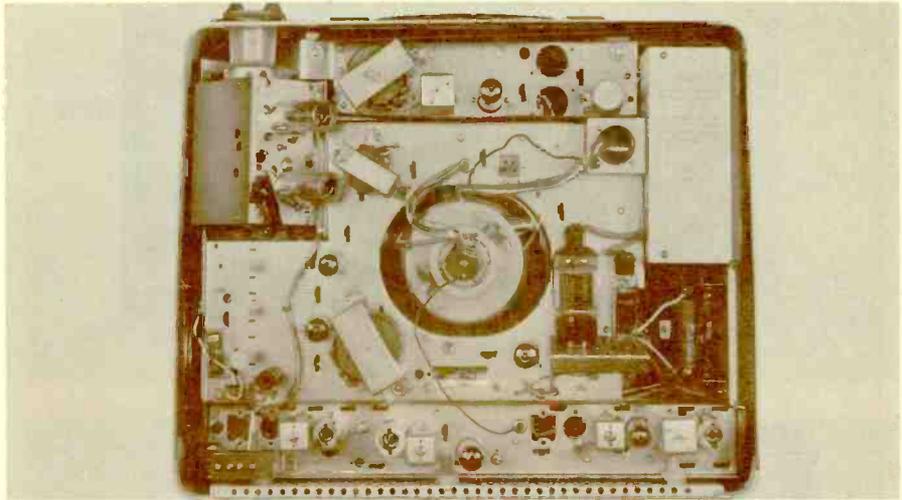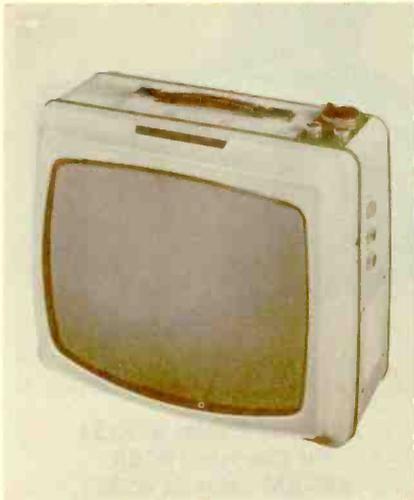

**Delmonico Model PTV-M3U**

One of the newest portable TV's introduced by Delmonico, this 19" receiver uses a 19YP4 114° picture tube and is equipped with a monopole antenna. If you elect to use an external antenna instead, loosen the thumb screws on the antenna terminal board (located on the rear cover), and remove the shorting bars from the upper terminals. Then, connect the external antenna leads to these upper two terminals. The connection from this terminal board to the tuner input proper is made via a plug and socket. The tuner, by the way, is a switch type that uses a 4BQ7A as the RF amplifier and a 5EA8 in the oscillator-mixer stage.





The tubes used in this receiver are 600-ma types, wired in a series string. The horizontal multivibrator is a 12-BH7A—unusual for this application. The 50-ohm, 10-watt filament-dropping resistor may be replaced without pulling the chassis.

A 2-amp fuse, mounted under a plastic cover on the rear side of the chassis, protects the entire receiver from overload. Electrically, this fuse is wired between one side of the AC input line and chassis. Make sure you use normal *hot-chassis* servicing procedures when working on this set.

Two silicon rectifiers, wired to double the input voltage, develop the B+ in this set. To replace either of these units, you must first pull the chassis.



Operating controls for brightness, vertical hold, and horizontal hold are all mounted on the right side of the cabinet; those for channel selection, fine tuning, contrast, and on-off-volume are located on the top. Service-adjustment controls (AGC, vertical linearity and height) have plastic extension shafts and are adjustable through holes in the rear cover. Other servicing adjustments in this set include one for width (a jumper wire in the screen circuit of the horizontal output stage), and one for focus. Any of three focus voltages may be selected with the plug and socket arrangement shown in the photo.

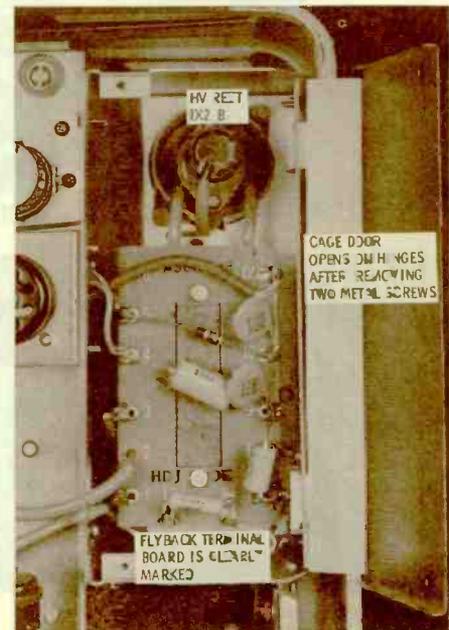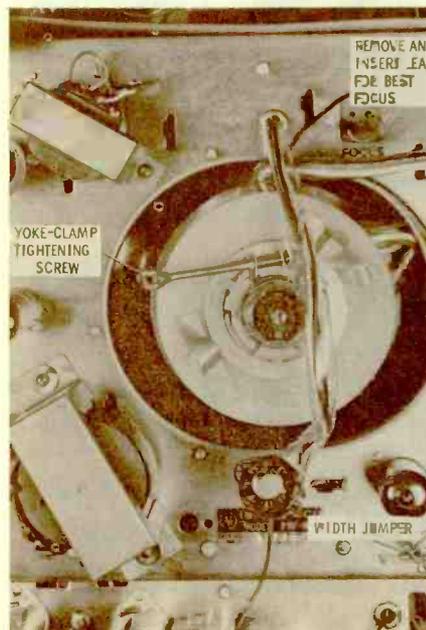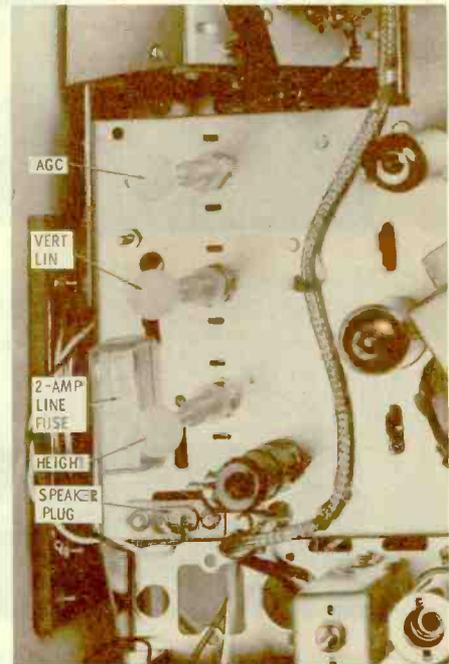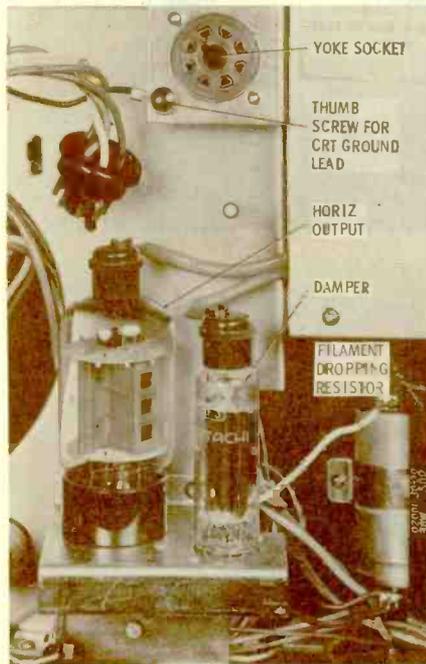Safety-window removal is fairly simple: Take out the five metal screws located on the front mask assembly, and lift this unit from the cabinet. Clean the window with mild soap and water only.



# PREVIEWS of new sets

RCA

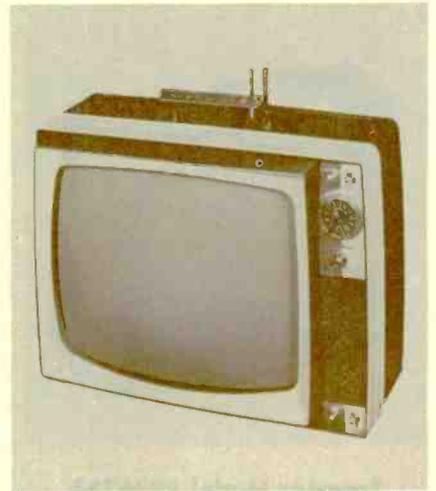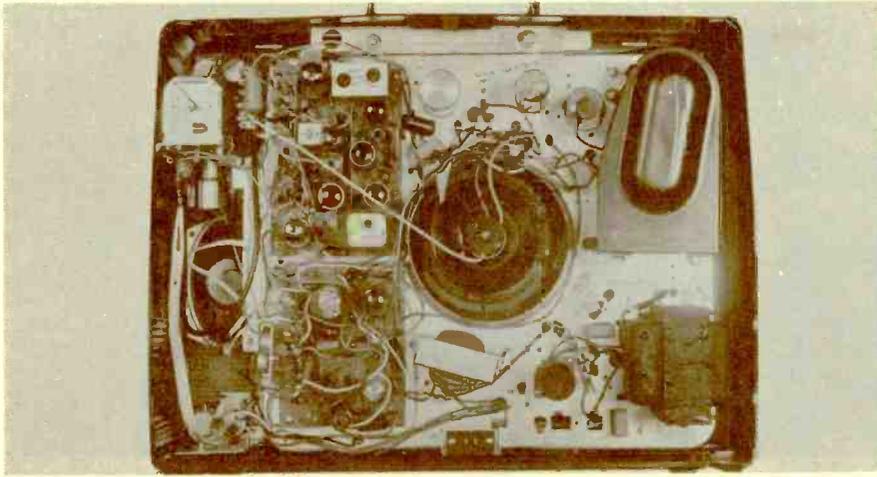

**RCA Model 193-A-542-MV  
Chassis KCS140A**

Pictured here is RCA's newest entry in its *Sportabout* line. Designated as the *Stylist*, this receiver uses a 114° picture tube (a 19AYP4), and has a built-in rabbit-ear antenna.

The RF amplifier in this set is the now-familiar 6CW4 nuvistor. A 6EA8 is used as the mixer-oscillator. This model is equipped to receive VHF channels only, but other models in this line, containing both a UHF and a VHF tuner, are available.




The deflection yoke (shown in the close-up) is wound in an unconventional manner. In place of the usual saddle-shaped windings, it has pairs of separate coils which are wound around the core in a *toroid* pattern.

Two plug-in *chemical* fuses are located near the power transformer. One is a 3-amp line fuse in the primary winding of the transformer; the other is a 4/10-amp fuse protecting the B+ circuit. The low-voltage supply uses two 1N1763 silicon rectifiers, wired in a voltage-doubler circuit. The 6.3-volt filament supply is split into two branches, with a #28 wire-link fuse protecting each branch.

Two *novar* tubes, the first to be employed in this company's portable-TV line, are used in this set. A 6GJ5 functions as the horizontal output tube, while a 6AY3 (removed from the socket to show its profile in the photo) is found in the damper slot. Other tubes in the receiver include a 6HF8 video output-sync separator and a 6GY6 used for keyed AGC.

The AGC, noise stability, height, and vertical linearity controls are adjustable through holes in the left side of the rear cover. To change the setting of the width coil, you must first remove the rear cover. To replace the video detector (crystal diode), remove the snap-on shield from the final IF can.

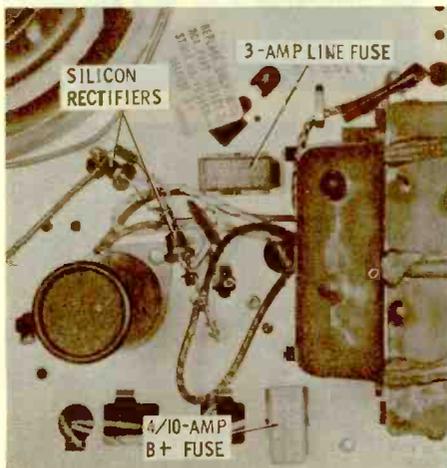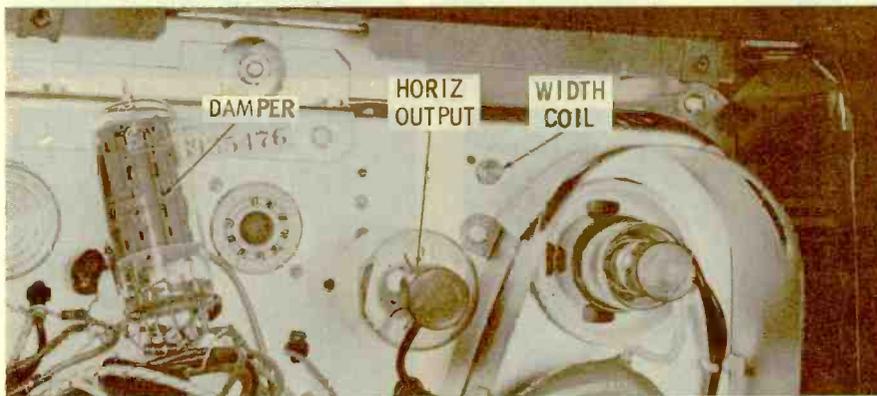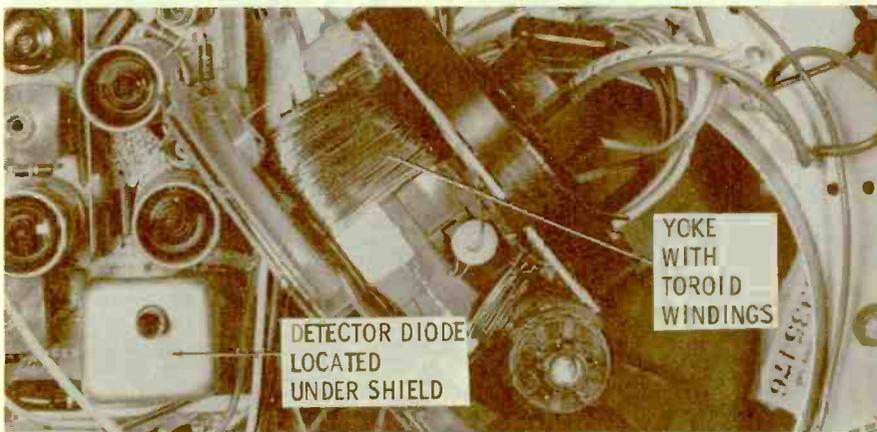The safety window, which should be cleaned with mild soap and water only, is held in place by three bottom screws outside the cabinet and two additional screws located on the inside. These inside screws can be reached by removing the rear cover. After removing those five screws and the front operating knobs, you can snap off the mask and safety window as a single unit.





**Trav-Ler Model 19P6233  
Chassis 1180-12**

Shown here is one of the 19" portable TV's available from Trav-Ler, using a 19XP4 aluminized 114° picture tube. Focusing is adjustable by changing the connection between pin 4 of the CRT socket and the focus terminal board on the chassis. Two of the plugs on this board are connected to different DC-voltage sources, and the third plug is grounded. Connect the lead to the plug which gives the best over-all focus on the screen.






The low-voltage circuit, a half-wave doubler using two silicon rectifiers, is protected by a circuit breaker and an 8-ohm, 10-watt surge resistor. As shown in the photos, all these components are located on top of the chassis and are easily accessible for replacement without removing the chassis from the cabinet. A 35-ohm, 10-watt resistor wired in series with the tube-heater string is similarly easy to replace.

Two semiconductors are used in this set: a 1N87 germanium diode as the video detector and a dual selenium diode in the horizontal AFC stage. The AFC diode (shown in the photo) plugs in, making replacement easy. The 1N87 is not replaced quite so simply; it's located inside the third IF can, and before it can be changed, the can must be unsoldered and removed from the chassis.

Some of the tubes used in this receiver are: a 6AW8 for the video output and sound-IF amplifier circuits; a 12CU5 for audio output (serving also as a B+ voltage divider); and a 3BU8 for the three functions of AGC keying, noise limiting, and sync separation.

The operating controls for on-off-volume, contrast, and vertical hold are mounted on the side of the cabinet. The vertical linearity control is attached to the rear of the contrast pot, and can be adjusted through the hollow shaft of the latter unit. In a similar manner, the height control is located directly behind the vertical hold. Controls for AGC, brightness, and horizontal hold are mounted on the rear apron of the chassis, and all are adjustable without removing the rear cover.

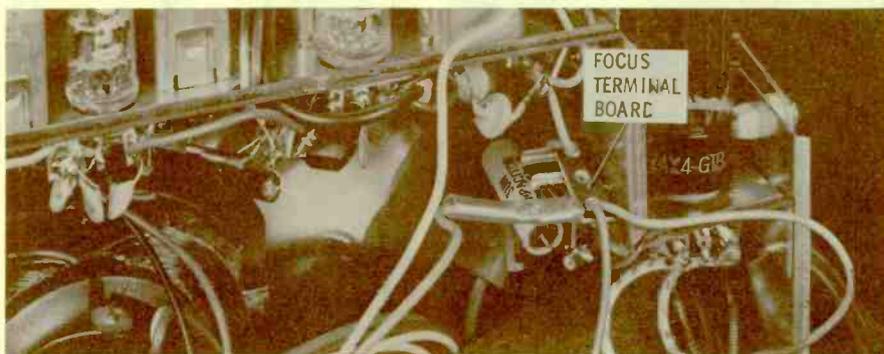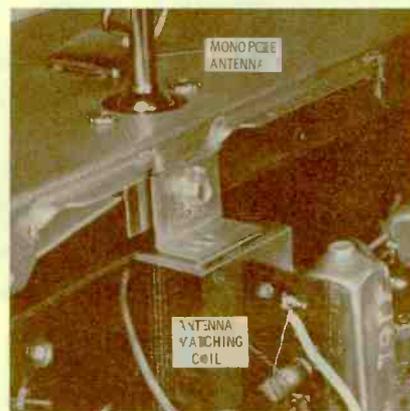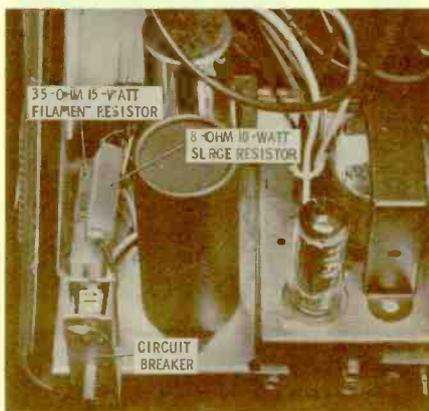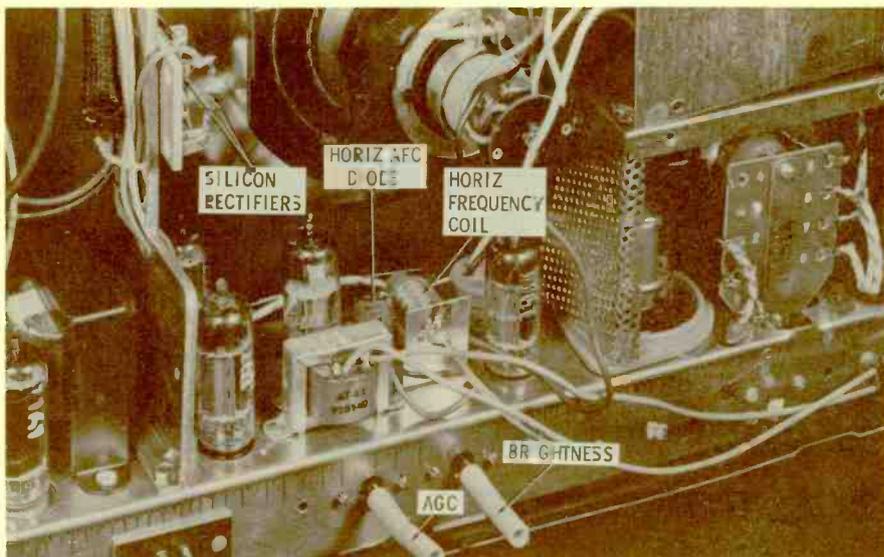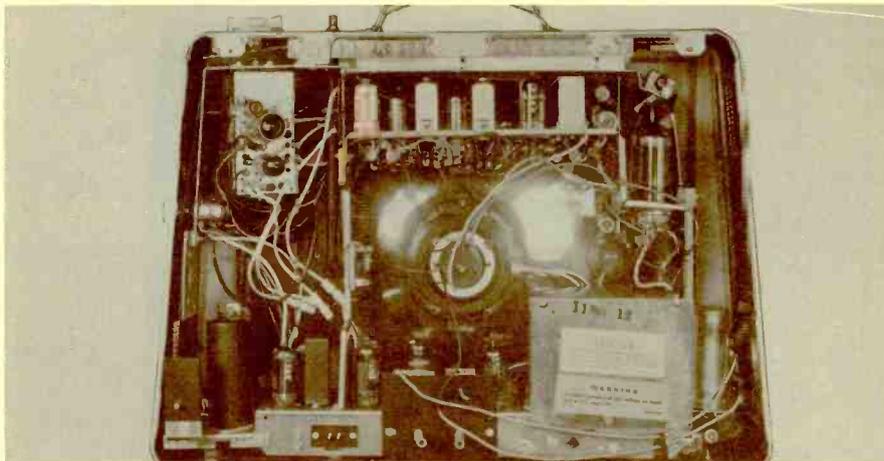The safety glass can be removed for cleaning after you remove the seven metal screws from around the front of the cabinet (three on the bottom and two on each side):



See PHOTOFACT Set 515, Folder 1

Mfr: Motorola Chassis No. TS-568


Card No: MO 568-1

Section Affected: Raster.

Symptoms: Flashes and streaks in raster; fluctuating voltage at screen grid (pin 4) of V12 (6DQ6).

Cause: Defective horizontal size control.

What To Do: Replace R9 (5000 ohms—2W).

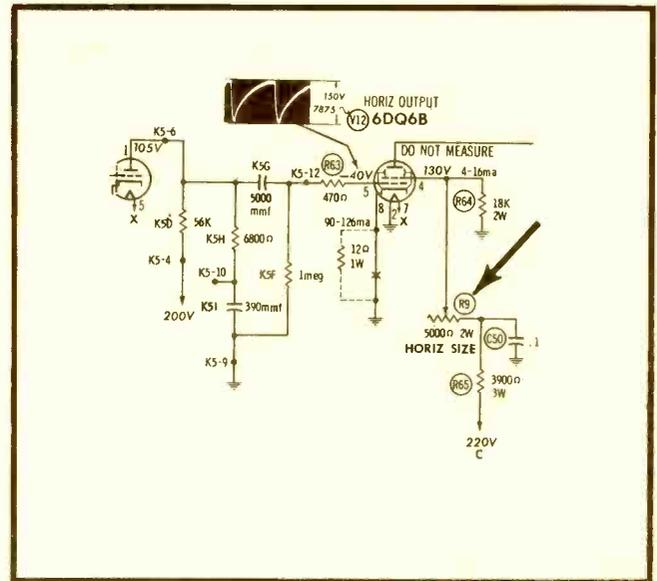

Mfr: Motorola Chassis No. TS-568


Card No: MO 568-2

Section Affected: Raster.

Symptoms: Insufficient vertical sweep; low boost voltage.

Cause: Leaky filter capacitor on boost line.

What To Do: Replace C52 (.1 mfd).

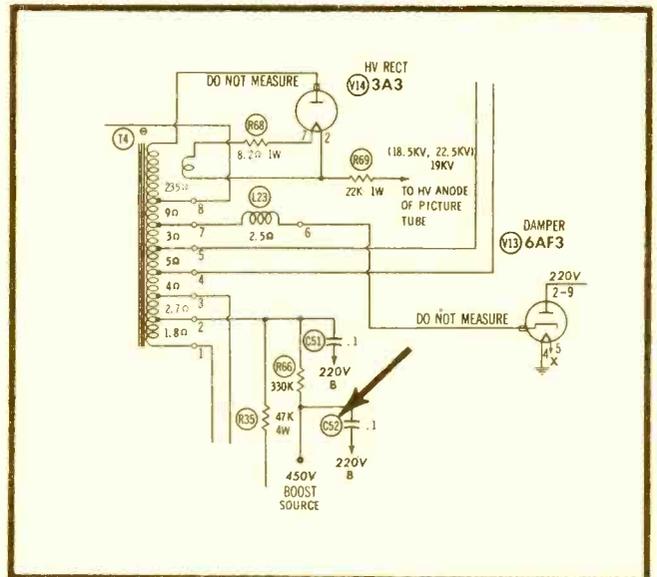

Mfr: Motorola Chassis No. TS-568


Card No: MO 568-3

Section Affected: Pix.

Symptoms: Smeared, weak picture.


Cause: Plate-load resistor in video output stage has decreased in value.

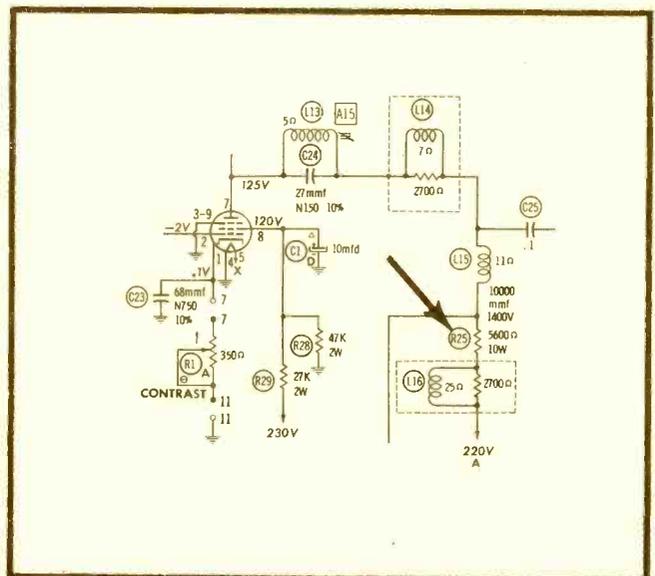What To Do: Replace R25 (5600 ohms—10W). Check V4 (6GK6) for shorts.



See PHOTOFACT Set 515, Folder 1

See PHOTOFACT Set 515, Folder 1

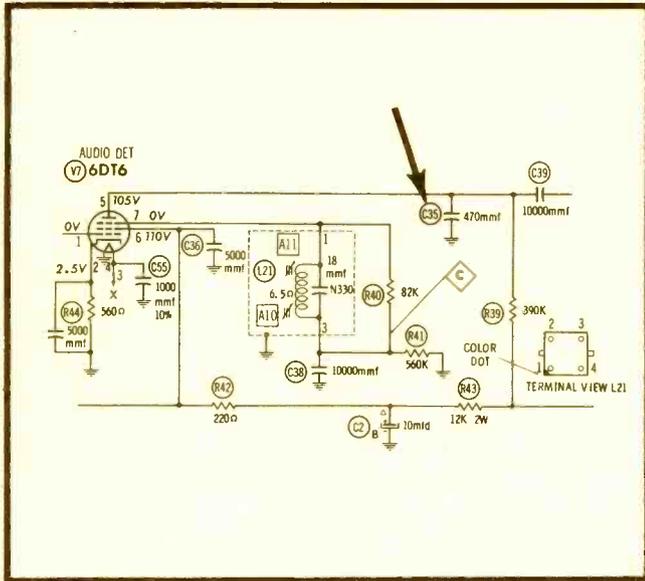

See PHOTOFACT Set 515, Folder 1

Mfr: Motorola Chassis No. TS-568


Card No: MO 568-4

Section Affected: Sound.

Symptoms: No sound. Zero voltage at plate (pin 5) of V7 (6DT6).

Cause: Shorted plate-bypass capacitor.

What To Do: Replace C35 (470 mmf).

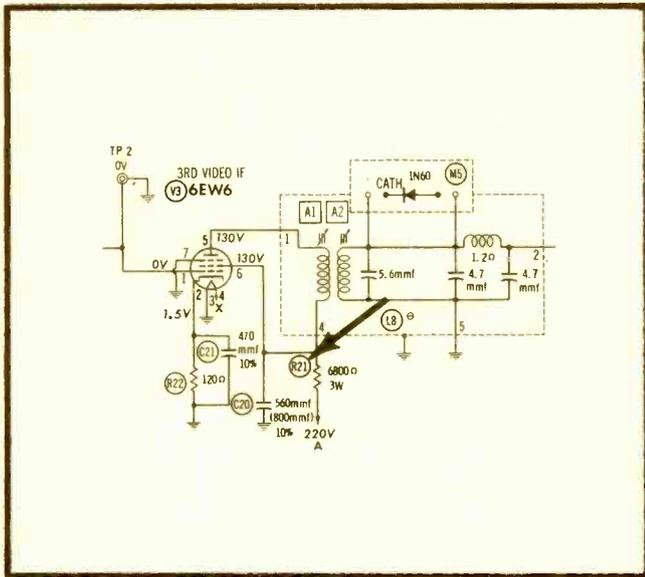

Mfr: Motorola Chassis No. TS-568


Card No: MO 568-5

Section Affected: Pix and sound.

Symptoms: Video and sound fade intermittently; when trouble occurs, voltage disappears at plate (pin 5) of V3 (6EW6).

Cause: Plate-decoupling resistor opens intermittently.

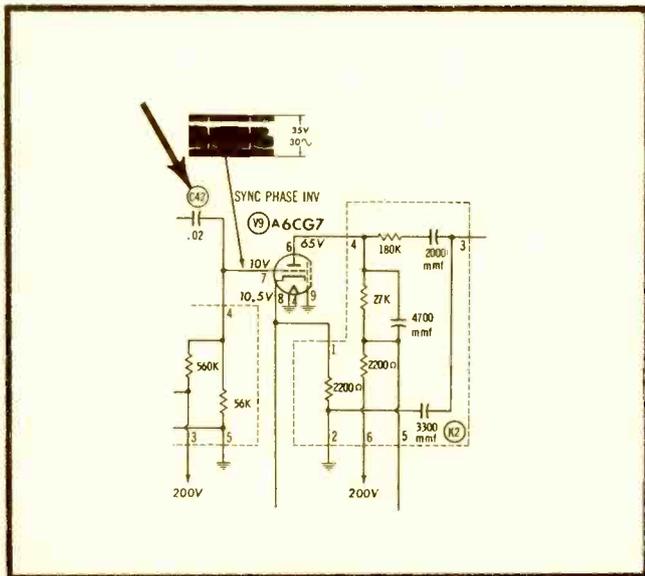What To Do: Replace R21 (6800 ohms — 3W).



Mfr: Motorola Chassis No. TS-568

Card No: MO 568-6

Section Affected: Sync.

Symptoms: Poor vertical and horizontal hold; voltage is too positive at grid (pin 7) of V9A (6CG7).


Cause: Shorted coupling capacitor between sync separator and sync phase inverter.

What To Do: Replace C42 (.02 mfd).



See PHOTOFACT Folder 539-2; PCB 588-3

See PHOTOFACT Folder 539-2; PCB 588-3

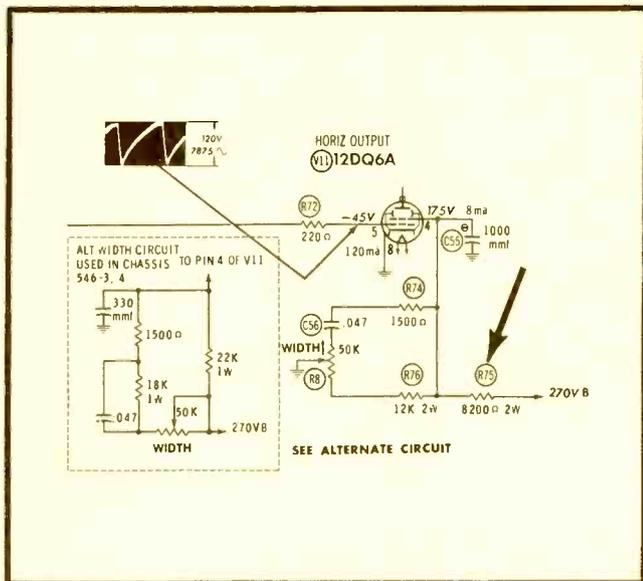

Mfr: Sylvania Chassis No. 546-1


Card No: SY 546-1-4

Section Affected: Raster.

Symptoms: Insufficient width.

Cause: Resistor in screen-grid circuit of horizontal output stage has increased in value.

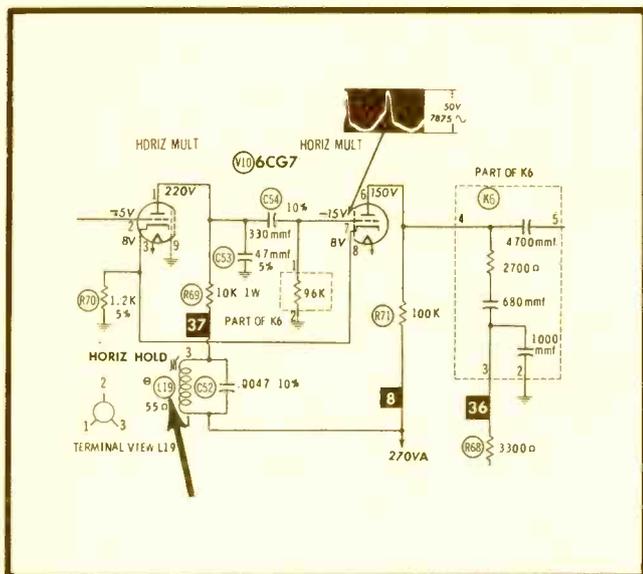What To Do: Replace R75 (8200 ohms — 2W).



Mfr: Sylvania Chassis No. 546-1


Card No: SY 546-1-5

Section Affected: Sync.

Symptoms: Poor horizontal hold.

Cause: Horizontal ringing coil has developed shorted turns.

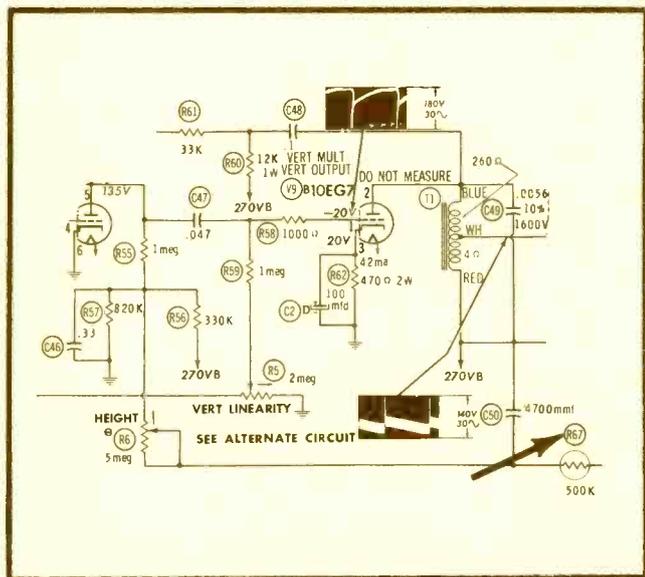What To Do: Replace L19, and check V10 (6CG7) for shorts.



Mfr: Sylvania Chassis No. 546-1

Card No: SY 546-1-6

Section Affected: Raster.

Symptoms: Insufficient vertical sweep; low voltage at grid (pin 1) of V9A (10EG7).

Cause: Defect in thermistor wired between height control and boost source.

What To Do: Replace R67 (Sylvania part no. 189-0081).

# TOP

**Higher Gain**

**Lower Noise**

# OF THE HEAP

85% of all TV servicemen prefer Standard turret type replacement TV tuners.

1 year guarantee backed by the world's largest TV tuner manufacturer.

Trade-in allowance for the defective tuner being replaced.

**In TV It's Standard**

See your local authorized Standard Coil Distributor

## **standard kollman**

**INDUSTRIES INC.**

FORMERLY STANDARD COIL PRODUCTS CO., INC., MELROSE PARK, ILLINOIS

## New Heavy Duty RFI Suppression Kit For Mobile Radio



**R**ADIO HAMS, fleet owners, and CB operators can now enjoy clearer, more readable, less tiring mobile communications at longer effective ranges.

Sprague's new Type SK-1 SUPPRESSIKIT provides effective R-F Interference suppression—at moderate cost—up through 400 megacycles. Designed for easy installation on automobile, truck, or boat engines with either 6-volt or 12-volt generators, the Suppressikit makes possible high frequency interference control by means of Sprague's new, extended range, Thru-pass® capacitors.

The components in the SK-1 Suppressikit are neatly marked and packaged, complete with easy-to-follow installation instructions. All capacitors are especially designed for quick, simple installation.

The generator capacitor is a heavy-duty unit rated at 60 amperes, and will operate at temperatures to 125°C (257°F). This means you'll have no trouble with an SK-1 installation in the terrific temperatures found "under the hood" on a hot summer's day. There's no chance of generator failures from capacitor "short outs," as with general purpose capacitors. The Thru-pass capacitors for use on voltage regulators are also rated at a full 60 amperes.

The Deluxe Suppressikit is furnished complete with an 8-foot shielded lead on the generator capacitor which can be trimmed to necessary length for any car or small truck, preventing R-F radiation from armature and field leads.

Containing only 5 easy-to-install capacitors, the Deluxe Suppressikit is a well-engineered kit. The net price is a little higher than that of many thrown-together kits, but it saves you so much time and aggravation it's well worth the slight extra cost.

For additional information on the Type SK-1 Suppressikit, see your Sprague Electronic Parts Distributor.

65-341 R2

**Sprague TWIST-LOK® Capacitors give you  
2 tremendous advantages over  
all other twist-prong electrolytics**



**1**

**The right size,  
the right rating, for  
EVERY replacement job**



**No need to compromise or  
improvise...the TWIST-LOK  
Line includes over 1690  
different capacitors . . . It's  
the industry's most complete  
selection of twist-prong  
type capacitors, bar none!**

**2**

**Exclusive, improved  
cover design for  
greater dependability**

**Type TVL Twist-Lok Capaci-  
tors are now more depend-  
able than ever! Sprague's  
new cover design provides  
a truly leak-proof seal and  
permits capacitors to with-  
stand higher ripple currents.**
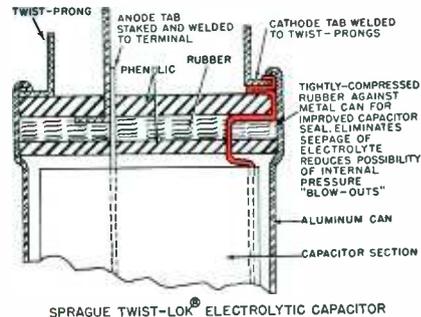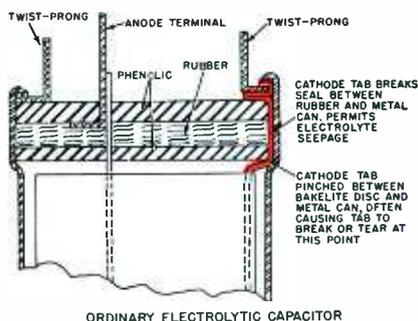
### Compare internal construction of TWIST-LOK to ordinary 'Lytic!



*Complete listings are shown in handy  
Wall Catalog C-457. Get your copy  
from any Sprague Distributor, or  
write to Sprague Products Company,  
105 Marshall St., North Adams, Mass.*

**WORLD'S LARGEST  
MANUFACTURER OF CAPACITORS**



**publisher**  
Howard W. Sams

**general manager**  
Mal Parks, Jr.

**editor**  
Verne M. Ray

**managing editor**  
Forest H. Belt

**ass't. managing editor**  
Thomas A. Lesh

**associate editors**  
James F. Galloway  
George F. Corne, Jr.

**consulting editors**  
William E. Burke  
Joe A. Groves  
C. P. Oliphant

**production manager**  
Robert N. Rippy

**circulation fulfillment**  
Pat Tidd, Mgr.  
Constance Bland, Ass't.  
Katherine Smith, Ass't.

**art director**  
Robert W. Reed

**advertising & editorial assistants**  
Ruth E. Bastin  
Paula Haffner  
Ellie Rother

**photography**  
John W. Smith  
Paul Cornelius, Jr.  
Joe Bretthauer

**advertising sales offices**  
John Groce, advertising sales manager

**midwestern**  
Hugh Wallace  
PF REPORTER  
4300 West 62nd Street,  
Indianapolis 6, Ind.  
AXminster 1-3100

**eastern**  
Charles Horner  
Howard W. Sams & Co., Inc.  
3 West 57th Street,  
New York, N. Y.  
MUrray Hill 8-6350

**western**  
The Maurice A. Kimball Co., Inc.  
2550 Beverly Blvd., Los Angeles 57, Calif.  
DUNKirk 8-6178; and 580 Market Street,  
Room 400, San Francisco 4, Calif. EXbrook 2-3365

**Address all correspondence to**  
PF REPORTER, 4300 W. 62nd Street,  
Indianapolis 6, Indiana



Copyright © 1962 by Howard W. Sams & Co., Inc. PF REPORTER is a trademark of Howard W. Sams & Co., Inc. No part of PF REPORTER may be reproduced without written permission. No patent liability is assumed with respect to use of information herein. Acceptance of advertising does not in any manner signify the products, policies and services so advertised have been approved, endorsed or recommended by this magazine.

Indexed in *Lectrodex*.

Printed by the Woldemar Press Div.  
of Howard W. Sams & Co., Inc.



# PF REPORTER

including **Electronic Servicing**

VOLUME 12, No. 9      **CONTENTS**      SEPTEMBER, 1962

<b>Previews of New Sets</b>	<b>3</b>
Admiral Model STF351 (Chassis 19C8B), Delmonica Model PTV-M3U, RCA Model 193-A-542-MV (Chassis KCS140A), Trav-Ler Model 19P6233 (Chassis 1180-12).	
<b>Video Speed Servicing</b>	<b>7</b>
Service hints on Motorola Chassis RTS-568 and Sylvania Chassis 546-1.	
<b>Letters to the Editor</b>	<b>14</b>
<b>Radio-TV Substitution Stock Guide</b>	<b>22</b>
<b>Debugging B+</b>	<b>24</b>
Quick ways to locate trouble in rectifier circuits and on B+ lines. <i>Wayne Lemons</i>	
<b>The Electronic Scanner</b>	<b>27</b>
<b>Calibrate Your Own Voltmeters</b>	<b>28</b>
You can finish the whole procedure in the time it takes to smoke one cigarette. <i>Len Buckwalter</i>	
<b>A Good Generator Sweeps Clean</b>	<b>30</b>
A well-marked response curve is useful for troubleshooting as well as alignment. <i>Denis A. Gentry</i>	
<b>Colors Adrift? Check Color Sync</b>	<b>32</b>
Quicker Servicing—Scope-tracing the burst signal is a short cut to isolating trouble. <i>George F. Corne, Jr.</i>	
<b>"Symfact" Charts</b>	<b>34</b>
See what happens to voltages and waveforms in a 6BU8 sync separator when troubles occur.	
<b>Does Your Customer Record File Cost or Pay?</b>	<b>38</b>
Dollar and Sense Servicing—A well-kept file makes it easier to settle callback disputes and plan direct-mail ads. <i>Art Margolis</i>	
<b>Transformer Tactics</b>	<b>44</b>
How to figure out what you can use as a replacement <i>Jim Galloway</i>	
<b>Servicing Is Fun!</b>	<b>50</b>
... There's something happening every minute. <i>Charles F. Lieder</i>	
<b>Servicing Tone-Coded Squelch</b>	<b>58</b>
Two-Way Talk—Do your part to help stamp out "channel chatter." <i>Patrick M. Craney</i>	
<b>Notes on Test Equipment</b>	<b>70</b>
Lab reports on the Precision Model E-450 Color Generator and RCA Model WO-91A Oscilloscope. <i>Forest H. Belt</i>	
<b>The Troubleshooter</b>	<b>80</b>
<b>Product Report</b>	<b>96</b>
<b>Free Catalog &amp; Literature Service</b>	<b>98</b>
<b>Monthly Index</b>	<b>on free literature card</b>

## ABOUT THE COVER

One of the things that "bug" TV service technicians is the job of tracing through the multiple branches of a B+ system to locate a short. This problem can be simplified, and wasted effort cut to a minimum, by means of the "thinking man's" approach outlined on page 24.



# ATR PRODUCTS FOR MODERN LIVING



## ATR PLUG-IN TYPE PORTABLE INVERTERS\*

**MODELS**  
 6-RMF (6 volts) 60 to 80 watts. Shipping weight 12 lbs. DEALER NET PRICE \$33.00  
 12T-RME (12 volts) 90 to 125 watts. Shipping weight 12 lbs. DEALER NET PRICE \$33.00  
 \*Additional Models Available

A. C. HOUSEHOLD ELECTRICITY anywhere in your own car, boat or plane Operates Standard A.C.  
 • Record Players  
 • Dictating Machines  
 • Small Radios  
 • Electric Shavers  
 • Heating Pads, etc.  
 In your own car or boat!



## ATR "A" BATTERY ELIMINATOR

For Demonstrating and Testing Auto Radios—TRANSISTOR or VIBRATOR OPERATED!

Designed for testing D.C. Electrical Apparatus on Regular A.C. Lines—Equipped with Full-Wave Dry Disc-Type Rectifier, assuring noiseless, interference-free operation and extreme long life and reliability.

MAY ALSO BE USED AS A BATTERY CHARGER  
 MODEL 610C-ELIF . . . 6 volts at 10 amps. or 12 volts at 6 amps. Shipping weight 22 lbs. DEALER NET PRICE \$49.95  
 MODEL 620C-ELIT . . . 6 volts at 20 amps. or 12 volts at 10 amps. Shipping weight 33 lbs. DEALER NET PRICE \$66.95

## ATR AUTO-RADIO VIBRATORS

By every test ATR Auto-Radio Vibrators are best! and feature Ceramic Stack Spacers, Instant Starting, Large Oversized Tungsten Contacts, Perforated Reed, plus Highest Precision Construction and Workmanship and Quiet Operation!

There is an ATR VIBRATOR for every make of car!

Ask your distributor for ATR's Low Priced type 1400, 6 volt 4-prong Vibrator, and 1843, 12 volt 3-prong or 1840, 12 volt 4-prong Vibrator. THE WORLD'S FINEST!



## ATR UNIVERSAL KARADIO MODEL 600 SERIES

Easily installed in-dash or under-dash. Amplifier power-supply chassis may be separated from tuner chassis for easy servicing. Utilizes 6-tube superheterodyne circuit (2 dual-purpose tubes). Supplied with separate 5" x 7" speaker. Neutral gray-tan baked enamel finish. Overall size 4" deep x 6 1/2" wide x 2" high. Tuner Chassis; with Amplifier Chassis, 2 3/8" deep x 6 1/2" wide x 3 7/8" high. Shipping weight 7 lbs. WILL OUT-PERFORM MOST SETS!

Model 612—12 Volt, Dealers Net Price \$31.96  
 Model 606—6 Volt, Dealers Net Price 31.96

## ATR TRUCK KARADIO

Airplane Style Overhead Mounting under Cab Roof NO PRINTS! CIRCUITRY

Excellent Tone, Volume, and Sensitivity!  
 Compact, yet powerful. Fits all trucks, station wagons, most cars and boats. Just drill a 3/8 inch hole in roof and suspend the one-piece unit (aerial, chassis and speaker) in minutes. Watertight mounting assembly holds antenna upright. Yoke-type bracket lets you tilt radio to any angle.

Extra-sensitive radio has 6 tubes (2 double-purpose), over-size Alnico 5 PM speaker for full, rich tone. Big, easy-to-read illuminated dial. Fingertip tuning control. Volume and tone controls. 33-in. stainless steel antenna. Neutral gray-tan enameled metal cabinet, 7 x 6 1/2 x 4 in. high over-all. Shipping weight 10 1/2 lbs.

Model TR-1279—12A for 12V Dealer Net Price \$41.96  
 Model TR-1279—6A for 6V Dealer Net Price \$41.96

See Your Electronic Parts Distributor Write Factory For Free Literature

# ATR ELECTRONICS, INC.

Formerly: American Television & Radio Co.  
 Quality Products Since 1931  
 ST. PAUL 1, MINNESOTA—U.S.A.

# LETTERS TO THE EDITOR

Dear Editor:  
 My curiosity is on the rampage, wondering what you mean in the August issue by the "new kind of aid for troubleshooting." Are you talking about an improvement in VSS? It very definitely is an aid to troubleshooting. Or will something completely new start in September? I can hardly wait to find out!

V. T. GARAMONDI  
 Boston, Mass.

You can relax, Mr. Garamondi, the time has come to reveal the new PF REPORTER "Symfact" feature. It will consist of facts about trouble symptoms in specific TV circuits. A complete explanation of the circuit is accompanied by tips on how to troubleshoot it. Then four common symptoms are analyzed in detail, and the components which cause trouble are pinpointed. But why take our word for it? See for yourself—it's on page 34! By the way, let us know how you like it.—Ed.

Dear Editor:  
 Fire the proofreader!! I guess he's already heard—there are a couple of mistakes in "Binary Numbers" (July PF REPORTER). The article was great, but don't add confusion to an already confusing subject. On page 28, Table II, Example B, the third binary digit (the 2' position) should be 1 instead of 0. Then, on page 63, Rule 6 should be restated; where it says  $1 \times 1 = 0$ , it should say  $0 \times 1 = 0$ . I'm in favor of more articles like you've been printing. Yours is one of the best magazines on the market today, but not if mistakes keep popping up.

JOHN B. PERKINS  
 Niles, Mich.

Do we dare point out just one more error, John? Table V on page 62 had a goof, too; in example D, the third decimal equivalent is 25 instead of 22. As for our proofreader, we've given him a light to read by, and I'm sur nohting like thsi will hapen agian.—Ed.

Dear Editor:  
 I'd like to pass along an idea I use for convincing customers that shop work on TV sets is worth the cost. Before I pull the chassis, I take a photo of the TV picture with my Polaroid camera, and give the snapshot to the customer for comparison with the improved performance after the repairs are finished.

T. J. WHITLEY  
 Dallas, Texas

You must get some interesting photos on symptoms such as no raster, garbled sounds, or no picture. Only kidding, T. J.

It sounds like a pretty good (and inexpensive) convincer, when you can use it.—Ed.

Dear Editor:  
 I think you're overlooking a good possibility by not running a series of articles on servicing electronic flash guns. Evidently, you're not in touch with enough fellows who have gotten their feet a bit wet in this line of work. This week, 55% of my total business was from repairing these units. They are shipped to me from six states, apparently because so many fellows don't quite see what a profitable service item this is. There must be a void somewhere.

M. G. GOLDBERG  
 St. Paul, Minn.  
 Got their feet wet, servicing flash guns? Must be a strange business! Anyone who'd like to find out more about this line of servicing? By the way, we're preparing a servicing article on darkroom equipment that is run and controlled by electronics; this is in somewhat the same field.—Ed.

Dear Editor:  
 On page 58 of your July issue, the Troubleshooter advised Mr. Leo Fruit of Macks Creek, Missouri, regarding a flyback replacement. If Mr. Fruit followed the diagram which accompanied the advice, he's probably still having trouble—the primary terminals are reversed! You'd better let him know, quick, before he burns up another flyback.

NAME WITHHELD  
 New Orleans, La.  
 Thanks, Mr. Withheld, and let's hope he reads this in time. Our apologies to both you and Mr. Fruit.—Ed.

Dear Editor:  
 A television dealer who services the sets he sells has one commodity with which to beat the discounter and price cutter . . . it is his service! We have competitors who don't care much for servicing; they take little responsibility for a set once it is sold, and don't mind "upping" a trade-in allowance several dollars above what is fair. When our customers say they've been approached with one of these "better offers," we agree to meet that price provided the customer will forego our usual full-year service warranty. This generally swings the deal our way, for few people want you to wash your hands of them after a sale.

JOHN A DEFREES  
 Durhamville, N. Y.



# Don't Compromise **INSTALL THE BEST!**

INSIST ON


# JFD



# transis-tenna<sup>®</sup>

REGISTERED TRADE MARK
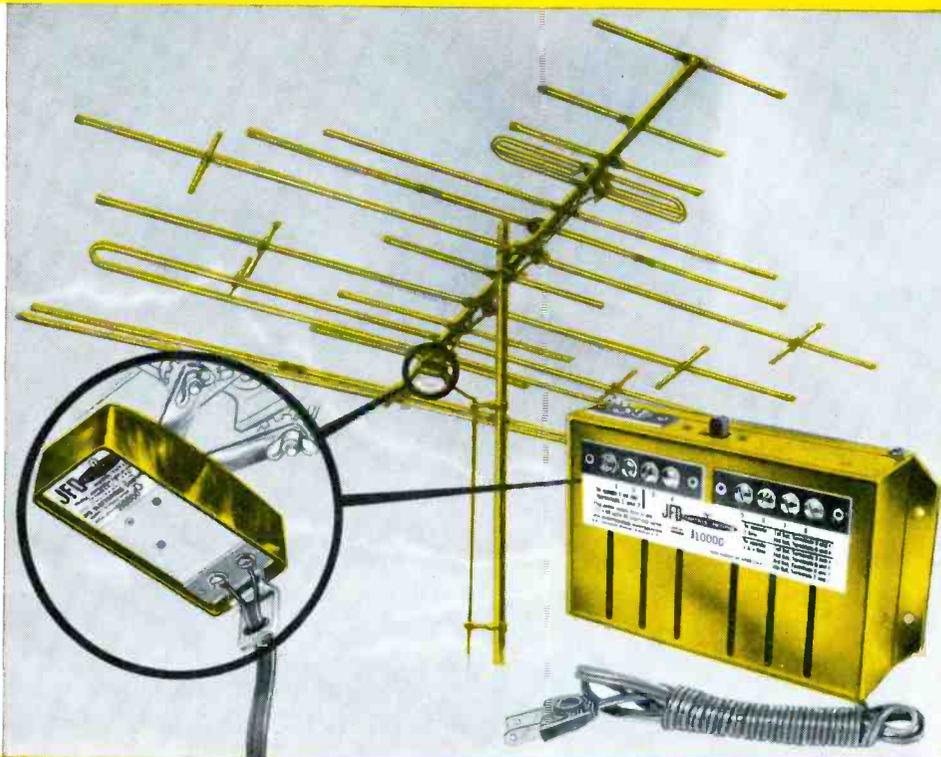
## ELECTRONIC TV ANTENNA-AMPLIFIER-DISTRIBUTION SYSTEM



and be **SURE** of **MAXIMUM** gain and **HIGHEST** signal-to-noise ratio—in black and white or color on 1, 2, 3 or 4 Sets!

### WHY QUALITY-CONSCIOUS, PERFORMANCE-CONSCIOUS, PROFIT-CONSCIOUS SERVICE DEALERS ARE SWITCHING TO THE JFD TRANSIS-TENNA




- PADS transistor circuitry provides higher gain, and superior saturation level and cross-modulation index characteristics. Up to 18 db gain on channels 2 to 6—15 db on channels 7 to 13 and 13 db on FM (gain above antenna). Proof of this superiority is the fact that competitive amplifier makers are switching to the same type PADS transistor.

- JFD amplifier is mounted directly on antenna terminals—the point of highest signal-to-noise ratio—the one and only right place. Result more clean signal on every VHF channel to each set in use—plus brilliant STEREO FM.

- Only the pure amplified TV signal gets through. "No picture tear-out" by unwanted amplified signals in the critical 130-160 mc frequency range. Specially designed circuit also eliminates interference from amateur, citizen's band, fire, police, aircraft and other commercial services.

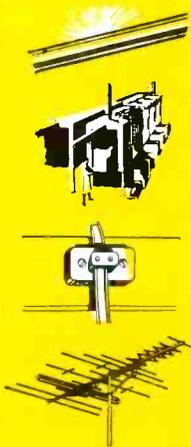- Linear frequency response... excellent impedance match... low VSWR at input and output (under 1.4 across VHF spectrum)—assures fidelity color.



- AAA\* Gold Bond Alodized aluminum keeps JFD Transis-tennas looking like new and working like new. This golden iridescent finish beautifies the antenna—protects it from corrosion or discoloration. And the electrically conductive coating will never flake, peel or chip—actually heals itself after damage. Conforms with requirements of MIL-C-5541 and MIL-S-5002 government specs for satellites and missiles. All at no extra cost to you.

(\*Attractive, Anti-Corrosive, Alodine-treated)

- Includes 300 ohm connectors for multi-set operation—provides up to four different locations where set can be plugged in.

- Only JFD provides you with the widest selection of electronic Transis-tenna antenna-amplifier-distribution systems for every location. Prices range from \$39.95 to \$76.95, retail, including antenna and amplifier system.

Call your JFD distributor today for Transis-tenna—or write for literature.

# JFD

THE BRAND THAT PUTS YOU IN COMMAND OF THE MARKET

**JFD ELECTRONICS CORPORATION**

6101 Sixteenth Avenue, Brooklyn 4, N. Y.

JFD Electronics-Southern, Inc., Oxford, North Carolina

JFD International, 15 Moore Street, New York, N. Y.

JFD Canada, Ltd., 51 McCormack Street, Toronto, Ontario, Canada

557 Richards Street, Vancouver 2, British Columbia

# Find it and Fix it in 1/2 the time!

EASILY SOLVES "TOUGH DOGS"... INTERMITTENTS... ANY TV TROUBLE



MODEL  
1076

## TELEVISION ANALYST

BLACK & WHITE AND COLOR

**By Easy Point-to-Point Signal Injection, You see the Trouble on the TV Screen and Correct it—Twice as Fast and Easy!**


Simplified technique stops lost hours never recovered on "tough dogs", intermittents, and general TV troubleshooting. This one instrument, with its complete, accurate diagnosis, enables any serviceman to cut servicing time in half... service more TV sets in less time... satisfy more customers... and make more money.

With the Analyst, you inject your own TV signals at any time, at any point, while you watch the generated test pattern on the picture tube of the television set itself. This makes it quick and easy to isolate, pinpoint, and correct TV trouble in any stage throughout the video, audio, r.f., i.f., sync and sweep sections of black & white and color television sets—including intermittents. No external scope or waveform interpretation is needed. Checks any and all circuits—solves any performance problem. Gives you today's most valuable instrument in TV servicing—proved by thousands of professional servicemen everywhere.

Available on Budget Terms. As low as \$30.00 down.

Net, \$29995

### SIMPLIFIES COLOR TV SERVICING, TOO

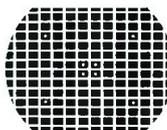

Enables you to troubleshoot and signal trace color circuits in color TV sets, or facilitate installation.



Generates white dot, crosshatch and color bar patterns on the TV screen for color TV convergence adjustments.



Generates full color rainbow display and color bar pattern to test color sync circuits, check range of hue control, align color demodulators. Demonstrates to customers correct color values.

### Time-Saving, Money-Making Instruments Used by Professional Servicemen Everywhere



Model 960 Transistor  
Radio Analyst



Model 360 V O Matic  
Automatic VOM



Model 375 Dynamatic  
Automatic VTVM



Model 700 Dyna-Quick  
Tube Tester



Model 440 CRT  
Rejuvenator Tester

See Your B&K Distributor  
or Write for Catalog AP20-R




### B & K MANUFACTURING CO.

Division of DYNASCAN CORPORATION

1801 W. BELLE PLAINE AVE. • CHICAGO 13, ILL.  
Canada: Atlas Radio Corp., 50 Wingold, Toronto 19, Ont.  
Export: Empire Exporters, 277 Broadway, New York 7, U.S.A.

See Only the Scale You Want...in the Exact Range You Want

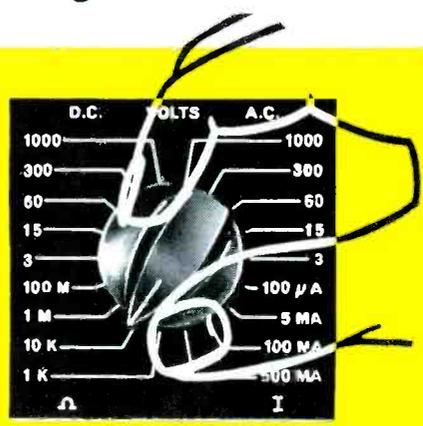**just set the range switch  
and the correct scale appears  
AUTOMATICALLY**



in the new **B&K**  
**VOM and VTVM**

**V O M A T I C 360**  
**AUTOMATIC VOLT-OHM MILLIAMMETER**

**WITH  
BURN-OUT PROOF  
METER**

Greatly simplifies your VOM use. Individual full-size scale for each range—and only one scale visible at any one time, automatically. Once you set the range switch, it is impossible to read the wrong scale. Reading in the range you want is amazingly easy—and direct. No reading difficulties, no multiplying, no errors.

**Sensitivity** 20,000 ohms per volt DC; 5000 ohms per volt AC. **Accuracy** ±3% DC; ±5% AC; (full scale). **DC Volts** in 6 ranges 0-6000. **AC Volts** in 6 ranges 0-6000. **AF (Output)** in 4 ranges 0-300 volts. **DC Current** in 5 ranges 0-10 amps. **Resistance** in 4 ranges 0-100 megohms. Supplemental ranges also provided on external overlay meter scales. Meter protected against extreme overload and burn-out. Polarity reversing switch. Automatic ohms-adjust control. Mirrored scale. Complete with 1½-volt and 9-volt batteries, test leads, and easy-viewing stand.

Net, \$5995



**DYNAMIC 375**  
**AUTOMATIC VACUUM-TUBE VOLTMETER**

Once you set the range switch, you automatically see only the scale you want and read the exact answer directly. Saves time, eliminates calculation, avoids errors. Individual full-size direct-reading scale for each range. Simplifies true reading of peak-to-peak voltages of complex wave forms in video, sync and deflection circuits, pulse circuits, radar systems, etc. Includes DC current ranges, too.

**Accuracy** ±3% full scale AC and DC. **Sensitive** 100 microampere meter movement. **DC Volts** in 7 ranges 0-1500. **AC Volts (rms)** in 7 ranges 0-1500. **AC Volts (peak-to-peak)** in 7 ranges 0-1500. **DC Current** in 3 ranges 0-500 ma. **Ohms** in 7 ranges 0-1000 megohms. Utilizes single DA-AC ohms probe and anti-parallax mirror. Swivel stand converts to carry-handle. Includes 1½ volt battery. Operates on 117 volts 50-60 cycle AC.


Net, \$8995

Ask Your B&K Distributor  
for Demonstration, or  
Write for Catalog AP20-R



**B & K MANUFACTURING CO.**  
Division of DYNASCAN CORPORATION  
1801 W. BELLE PLAINE AVE. • CHICAGO 13, ILL.  
Canada: Atlas Radio Corp., 50 Wingold, Toronto 19, Ont.  
Export: Empire Exporters, 277 Broadway, New York 7, U.S.A.

# Big Wheels in tv service

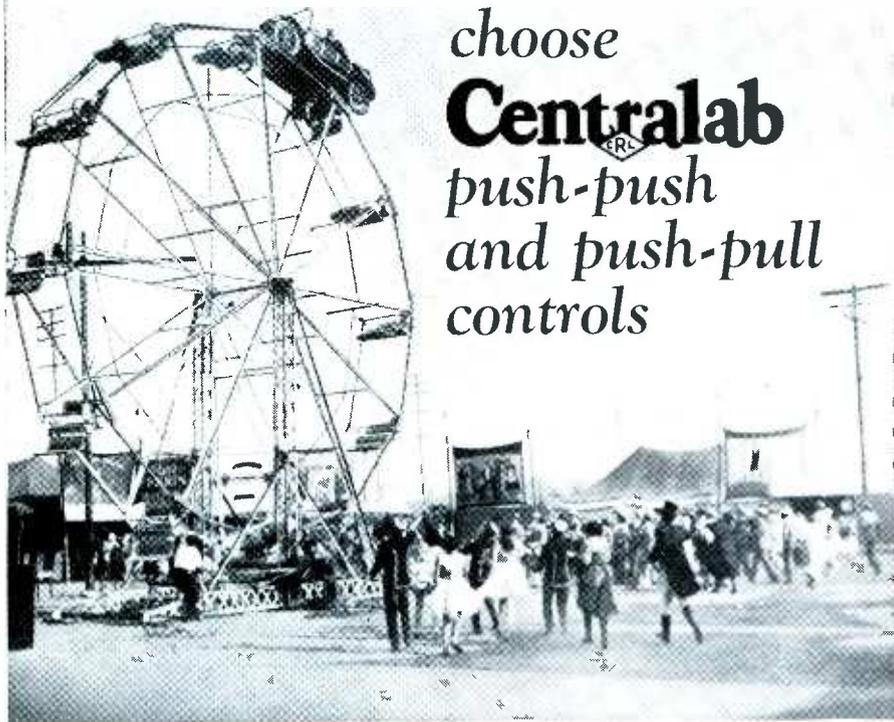

choose  
**Centralab**  
push-push  
and push-pull  
controls



ACTUAL SIZE

No need to go round in circles looking for push-push and push-pull switch-type replacement controls. Centralab has them—in 4 different types: Adashaft, Universal Shaft, Fastatch (for dual concentrics); twin types (for stereo).

As you know, controls of this type are original equipment in the vast majority of recent TV, radio, and hi-fi sets—and only Centralab has a complete line of replacements.

Incidentally, these easy-to-use units can also be used to replace any switch-type volume controls.

So get down to earth, and get over to your Centralab distributor for push-push and push-pull controls.

B-6204 S

**Centralab**

THE ELECTRONICS DIVISION OF GLOBE-UNION INC.  
942J EAST KEEFE AVENUE • MILWAUKEE 1, WISCONSIN  
In Canada: Centralab Canada Ltd., P.O. Box 400, Ajax, Ontario

ELECTRONIC SWITCHES • VARIABLE RESISTORS • CERAMIC CAPACITORS  
PACKAGED ELECTRONIC CIRCUITS • ENGINEERED CERAMICS

*That's undercutting the undercutters! But what do you do with the customer who buys on credit, and then dares you to refuse him service?—Ed.*

Dear Editor:

I would like to know why some brands of small receiving tubes test much higher than others in a mutual conductance type of tube tester. Do you have any comments on this?

WALTER J. WILLIAMS

St. Clair, Mich.

*In the usual emission tester, all elements except the cathode and heater are connected together for the test, and the instrument measures the ability of the cathode to emit electrons. In a mutual conductance tester, however, a signal is applied and the tester indicates how much control the grid has on the plate current. Since the effectiveness of the grid is somewhat dependent on the spacing between it and the cathode, slight differences in manufacturing tolerances may cause varied spacings among various brands—leading to different Gm readings, even in tubes of the same type. This does not necessarily mean they differ widely in performance, for the spacing of other elements within the tube also contributes to the overall performance.—Ed.*

Dear Editor:

In the July issue, your VSS card WE 2378-1-11 describes a symptom I've encountered often. My remedy consists of hooking a voltmeter to the plate (pin 5) of the 6DT6 and tuning L21 (A9) for maximum DC voltage. This always clears up my problem. Another thing: I'd like to see another issue like November, 1961—nothing but color.

HUGH O. BUTTS

Des Moines, Iowa

*Your wish is our command. Presto—and the November issue will be piled high with color-TV servicing goodies. Thanks, Hugh, for the service tip, although I doubt that tuning L21 will compensate for the defective resistor indicated on the VSS card. And if tuning did cure the symptom in such a case, the trouble would be likely to recur as the resistor further changed in value.—Ed.*


## Moving to a New Location?

If so, notify us by the 15th of the month to assure uninterrupted delivery of PF REPORTER.

Please be sure to give us both your old and new address, including your postal zone number. (Or better yet, enclose a current mailing label with your new address.) Send to:
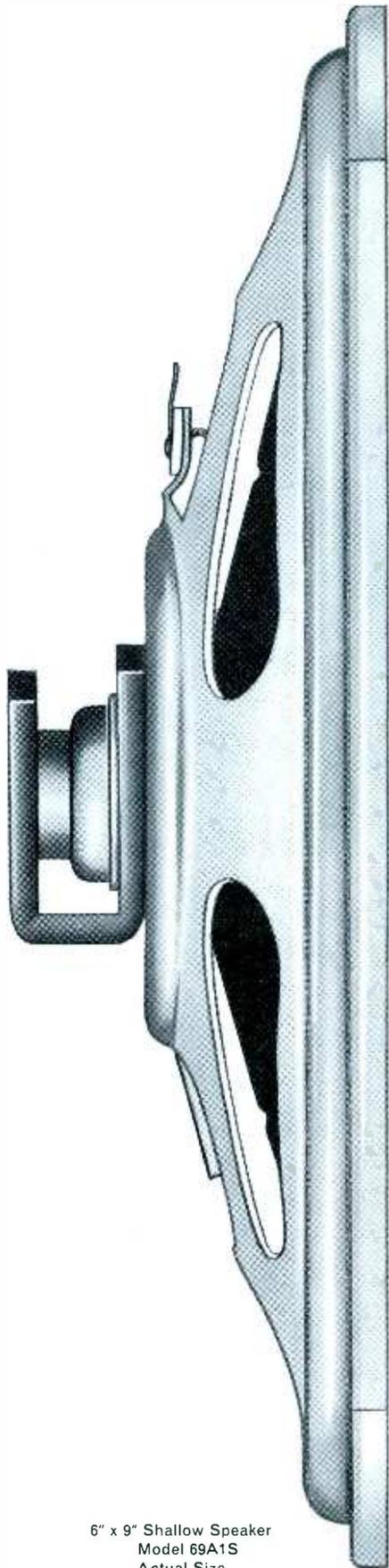
### PF REPORTER

Circulation Dept.  
4300 W. 62nd Street  
Indianapolis 6, Ind.



6" x 9" Shallow Speaker  
Model 69A1S  
Actual Size

# For those special applications choose a Quam speaker

When you need a 2¼" unit for a transistor radio—or a shallow 6" x 9" for a Thunderbird replacement—Quam has it!

When you need a special voice coil impedance or special field resistance—Quam has it!

Quam gives you the widest selection and the highest quality in the entire speaker industry! Ask for Quam, the Quality line, for all your speaker needs.



2¼" Transistor Radio Speaker  
Model 22A06Z8  
Actual Size

# QUAM

QUAM-NICHOLS COMPANY  
234 East Marquette Road  
Chicago 37, Illinois

- DESIGNED FOR COLOR TV
- PERFORMANCE GUARANTEE IN WRITING
- 100 MPH WIND TESTED

**SUNFAST GOLD ANODIZED**

\*Pat. Nos. U.S. 2,700,105; 2,955,289 • Canada 511,934 • Others pending.

# NEW FOR COLOR Winegard COLORTRON

**EVOLUTIONARY** — The finest TV antenna design ever engineered is the time-proven Electro-Lens all channel Yagi. This patented basic design, with its cross-phased driven elements and intermixed director system, was introduced by Winegard to the industry in 1954 and has never been surpassed. Now, through continuous research and product development, a new, improved Electro-Lens Yagi has evolved—the NEW WINEGARD COLORTRON—bringing this acknowledged design to a new peak of perfection.

**4 COLORTRON MODELS \$24.95 to \$64.95**  
There are 4 new COLORTRON yagis to cover every reception need, from suburbs to distant fringe areas . . . setting new industry standards for reception results and mechanical construction. They are


the only outside antennas that carry a *written factory guarantee of performance* with full factory back-up of consumer satisfaction.

**PERFECT COLOR ANTENNA** — COLORTRONS have an almost flat frequency response (plus or minus ½ DB across any 6 MC channel), no “suck-outs” or “roll-off” on end of bands . . . accurate 300 ohm impedance match, (VSWR 1.5 to 1 or better) . . . unilobe directivity for maximum ghost and interference rejection. They deliver today’s finest TV reception—COLOR or BLACK AND WHITE.


**RUGGED CONSTRUCTION** — **SUNFAST GOLD ANODIZED**—COLORTRONS are *built to last* . . . made of high tensile aluminum

tubing for rigidity and stability. New locking devices keep the elements aligned—straight as a die. This quality of construction will satisfy a perfectionist! Insulators have a triple moisture barrier to insure top performance, rain or shine. Every COLORTRON is GOLD ANODIZED the WINEGARD way for the best looking, most corrosion-proof and permanent Gold finish known for aluminum.

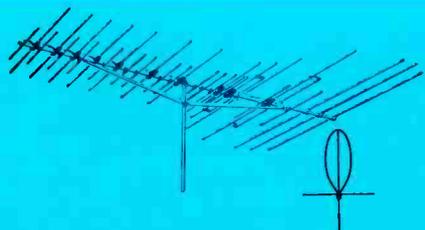
**POWERFUL ELECTRONIC ANTENNA** — Because the COLORTRON and the NUVISTOR amplifier were designed to match each other perfectly, electronically and mechanically, together they make the most efficient electronic TV antenna yet devised.




**MODEL C-44**  
GOLD ANODIZED \$64.95

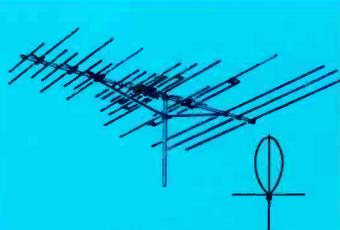


**MODEL C-43**  
GOLD ANODIZED \$51.90

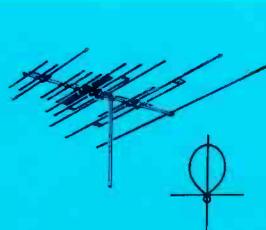

**MODEL C-42**  
GOLD ANODIZED \$34.95

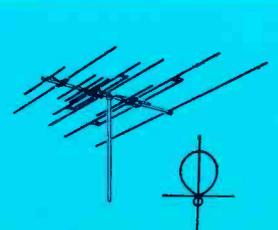

**MODEL C-41**  
GOLD ANODIZED \$24.95

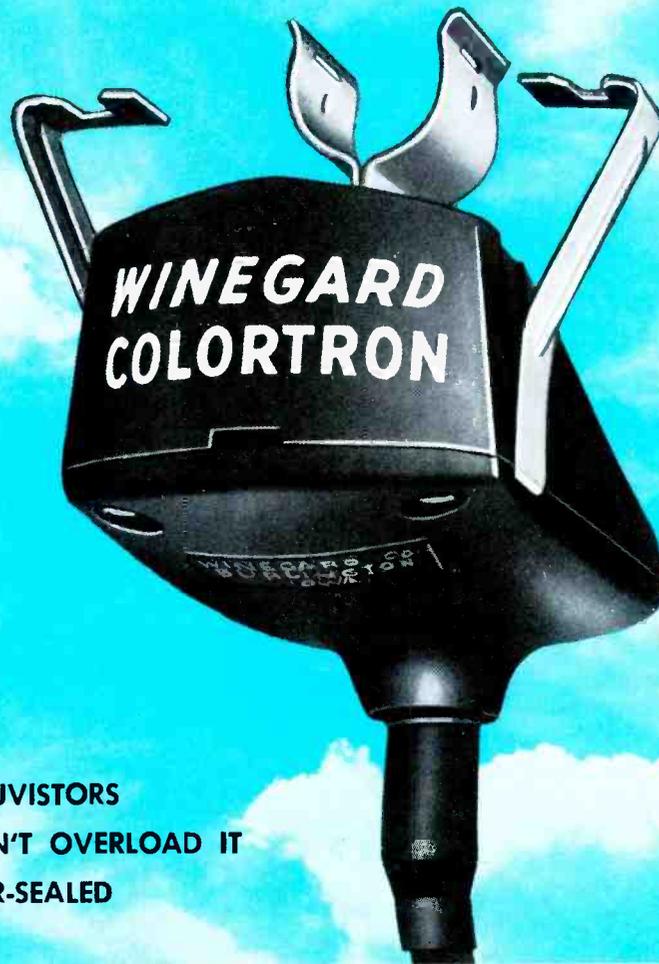

**USES 2 LONG LIFE NUVISTORS**

- **STRONG SIGNALS CAN'T OVERLOAD IT**
- **COMPLETELY WEATHER-SEALED**

# ANTENNA and COLORTRON AMPLIFIER

**REVOLUTIONARY**—Now a revolutionary new circuit, using two NUVISTORS enables the WINEGARD COLORTRON amplifier to overcome the limitations of other antenna amplifiers. For instance, oscillations, strong signal overloading and cross modulation picture interference are not problems with a COLORTRON AMPLIFIER because it will take up to 400,000 microvolts of signal input, 20 times more signal than other antenna amplifiers. *You can use it to amplify weak signals from far-away stations even though you have strong local signals from TV and FM stations. The COLORTRON NUVISTOR Amplifier is the only antenna amplifier that can do this!*

**"LIFESAVER" CIRCUIT GIVES NUVISTORS 4 TIMES THE LIFE OF ORDINARY TUBES**—A special "LIFESAVER" circuit has been designed to give the rugged LONG LIFE NUVISTORS an operating life many times

that of tubes, and superior to transistors in similar use. The COLORTRON NUVISTORS will operate perfectly for years.

**PERFECT COLOR TV AMPLIFIER**—The COLORTRON amplifier *has what it takes* to give CLEAN, CLEAR COLOR PICTURES, sharp and bright without smear. On weak signals, it will effectively reduce snow and interference, often making the difference between a very good picture and a poor one. It has an ultra low noise circuit... high amplification... flat frequency response... accurate impedance match (VSWR 1.5 to 1 or better, input and output)... and no phase distortion. You can be confident it will improve color and black and white TV reception in any location. This amplifier is so powerful, it can easily drive 6 sets at once with gain to spare!

**WEATHER-SEALED POLYSTYRENE CASE ... CORROSION-PROOF**—The COLORTRON

NUVISTOR amplifier is completely weather-sealed! Nothing is exposed to corrode and cause trouble—even the terminals are protected. A rubber boot over the twin-leac keeps moisture out. A built-in heat sink controls temperature of NUVISTORS. Everything possible has been done to eliminate maintenance problems. It comes complete with an all AC power supply with built-in 2 set coupler. (Mod. No. AN-220, \$39.95). The COLORTRON amplifier will give trouble-free performance for years. Install it and forget it!

#### OTHER ANTENNA AMPLIFIERS

FOR TV—2 Transistor (Mod. No. AT-220, \$39.95) also available. Will take up to 80,000 microvolts of signal input without overload. This is 3 times the input of other transistor antenna amplifiers.

FOR FM—Super sensitive 2 Nuvistor, 200,000 Microvolts Input—\$39.95.


Write for information.



**AMPLIFIER WORKS ON ANY ANTENNA.**



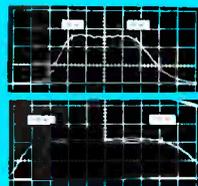**SPECIALLY DESIGNED AMPLIFIER CLAMP SNAPS ON COLORTRON ANTENNA IN SECONDS.**



**UNRETOUCHED PHOTO OF AMPLIFIER GAIN CURVE—FLAT RESPONSE ALL CHANNELS.**



**COLORTRON POWER UNIT WITH BUILT-IN 2 SET COUPLER.**



Write for technical bulletins

## Winegard

**ANTENNA SYSTEMS**

3009-9 KIRKWOOD • BURLINGTON, IOWA

# RADIO-TV

# Substitution

Keeping this inventory  
of major parts on hand will  
help you service faster and better

## STOCK GUIDE

What is the surest way to find out if a specific part is causing trouble? By substituting a known-good equivalent in its place. To do this, every radio-TV service shop needs a basic stock of replacement components. Naturally, you'll stock such small items as tubes, resistors, capacitors, fuses, fusible resistors, dial lamps, connectors, and other inexpensive parts. Suitable assortments of these components are readily available—often in kit form—but what about major components?

You have three alternatives when it comes to more expensive replacements: 1. Run down to the distributor and buy a part every time you want a substitute, 2. equip your shop with a complete assortment of component-substitution test equipment, or 3. maintain a basic stock of replacement items. A mixture of the last two is the most-favored choice. However, if you have limited finances, patient customers, and lots of time, the first alternative is okay. Even so, there is a definite disadvantage to this practice. If you guess wrong about the part, and the replacement didn't solve the problem, it means another trip. Also, you'll have to replace the original substitute instead of leaving the new part in the set and charging the customer for it—unnecessary billing is unethical and should be avoided.

To point out the most-often-needed major components, we've compiled the accompanying list. Notice the vertical integrator listed under the heading "Component Combination;" although this unit is an inexpensive part, it has been listed because it is difficult to test or substitute for in any other way.

The list doesn't show flybacks, picture tubes, power transformers, and other specialized components. Flybacks demand "exact replacement" types for substitution, and other parts are so easy to check that there is no need for substitution. The parts shown in bold type are the "must" items for all shops, and those in light-face type are "nice to have." Obviously, larger shops will want to stock one or more of all the items to have a readily available stock of replacements. However, you must be able to sell an item at least four times a year to make it profitable to stock more than the one test component. Therefore, watch the turnover of your stock to see exactly what you need. ▲

<b>Coils</b>					
Linearity—2-18 mh			Horiz. Ring—15,750 cps		
Width—.05-3 mh			"Synchroguide"—15,750 cps		
Width—4-30 mh			Motorola, RCA (modified),		
and 2-8 mh			and Zenith Horiz. Osc.		
Ratio Detector—4.5 mc			Universal Osc.—BC Band		
Quadrature—4.5 mc			Ferrite Loop Antenna		
<b>Component Combinations</b>					
Vertical Integrator			AC Isolation		
2200 mmf, two 4700 mmf,			470 mmf,		
two 8200 ohm, 22K			.3-1 meg		
<b>Electrolytics</b>			<b>Speakers</b>		
4/10/50/100/200 mfd @			4" square—3-4 ohms		
450V for test—assorted			6" x 9"—3-4 ohms		
voltages and combinations			Assorted sizes		
for stock					
<b>Transformers</b>					
Audio Output—3-4 ohm sec.			Vert. Osc.—1:4.2 (turns ratio)		
5000 ohms, 50 ma			Vert. Output—70°-90°		
2500 ohms, 50 ma			Universal 5:1 - 50:1		
7500 ohms, 50 ma			Vert. Output—1°0°		
10K ohms CT, 30 ma			12-13:1		
<b>Yokes</b>					
Degree	H	V	Degree	H	V
110°	18 mh	12 mh	90°	12 mh	33 mh
90°	20 mh	40 mh	70°	10 mh	45 mh
<b>Previous Articles About Stock</b>					
CRT's—May, 1961			Tubes—May, 1961		
Diodes, Rectifiers—July, 1961			Transistors—Aug., 1961		
Tuners—see article in this issue					

Tarzian offers

# FAST, DEPENDABLE TUNER REPAIR SERVICE

ALL  
MAKES



It just makes sense that a manufacturer of tuners should be better-qualified, better-equipped to offer the most dependable tuner repair and overhaul service.

Sarkes Tarzian, Inc., pioneer in the tuner business, maintains a complete, well-equipped Factory Service Dept.—assisted by Engineering personnel—and staffed by specialized technicians who handle ONLY tuner repairs . . . on ALL makes and models.

Tarzian-made tuners received one day will be shipped out the next. There is a 12-month guarantee against defective workmanship and parts failure due to normal usage. And compare our cost of \$8.50 and \$15 for UV combinations. There is absolutely no additional, hidden charge for ANY parts except tubes. Replacements available at low cost on tuners beyond practical repair.

Ⓢ Tarzian-made tuners are identified by this stamping. When inquiring about service on other tuners, always give tube complement . . . shaft length . . . filament . . . voltage . . . series or shunt heater . . . IF frequency . . . chassis identification. All tuners repaired on approved, open accounts. Check with your local distributor for Sarkes Tarzian replacement tuners, replacement parts, or repair service.

SERVICE MANAGER • TUNER DIVISION • DEPT. 3A



## SARKES TARZIAN INC

east hillside drive • bloomington, indiana  
edison 2-7251

MANUFACTURERS OF TUNERS . . . SEMICONDUCTORS . . . AIR TRIMMERS . . . FM RADIOS . . . AM-FM RADIOS . . . AUDIO TAPE . . . BROADCAST EQUIPMENT

ONLY

# \$8.50

INCLUDING

## ALL PARTS (EXCEPT TUBES) and LABOR

## 24-HOUR SERVICE 1-YEAR WARRANTY

## Tuners Repaired on Approved, Open Accounts

See your distributor, or  
use this address for fast,  
factory repair service

# DEBUGGING B+

by Wayne Lemons

Since troubles in B+ supplies can affect any TV circuit—sound, picture, sync, sweep or AGC—it's little wonder so many real "dogs" result from faults in the B+. Maybe we can refine our approach to B+ troubleshooting by analyzing a few power supplies and their load circuits.

## The Voltage Doubler

A circuit often used in transformerless sets—and occasionally in transformer-powered sets—is the voltage doubler, with either selenium or silicon rectifiers. A representative circuit is shown in Fig. 1.

While silicon rectifiers are now used almost exclusively, for many years the selenium was the only type available. The silicon unit has certain advantages in its generally small physical size; and because it has a low forward resistance, it develops from 5 to 10% more output voltage than the selenium. Silicon rectifiers almost never cause low B+ voltage from increased internal resistance—a common occurrence with seleniums. Silicons are, on the other hand, more susceptible to internal short circuits—their most common defect.

Fig. 2 will help you understand just how this circuit actually doubles the input voltage. M1 and M2

Here's a logical way to troubleshoot low-voltage supply networks . . .

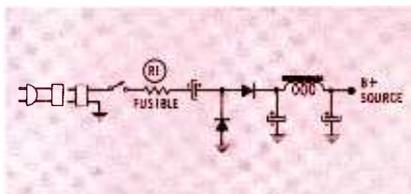


Fig. 1. Silicon rectifiers are commonly used in half-wave doubler circuit.

each act as a simple half-wave rectifier during one-half of the input-voltage cycle. On the negative half-cycle, M1 conducts as shown in Fig. 2A, charging C1 to almost the peak value of the input voltage; M2 cannot conduct, since it is connected in the opposite polarity. However, during the positive excursion of the input voltage, M2 does conduct as shown in Fig. 2B, charging C2; during this half-cycle, M1 has no effect in the circuit.

As the positive half of the input voltage is applied to C2 through M2, you will notice it is in series with the voltage charge already held by C1. This potential, then, combines with the input voltage and charges C2 to a level equal to the sum of both. Thus, the circuit effectively doubles the input voltage value.

The charge time of C1 and C2, the discharge time of the B+ load, and the internal resistance of the rectifiers, combine to prevent the DC output voltage from reaching

twice the peak input voltage; however, the output level is well over two times the rms input voltage.

## Doubler Troubles

The most common trouble in this circuit is either low voltage or none at all. Low voltage can be caused by an open or partially open C1 or C2, or by a defective rectifier. (Low voltage is seldom a problem with silicons, for the reason explained above.) The simplest and quickest way to check either of these parts is by shunting the suspected part with a known good one of the same general type.

In a case of no voltage at all, we naturally suspect the fusible resistor (R1) first. This resistor will open if a selenium or silicon shorts, or if a short develops on the B+ line. (Occasionally, one opens just to be an aggravation—see "What To Do When the Fuse Blows" in the July issue.)

If the customer complains of having no picture—and perhaps little or no sound—until after the set has been on for 30 minutes or so, you will be justified in suspecting either C1 or C2. Causing this symptom is a favorite trick of input filters. In radios, we notice it readily because of the excessive hum when the set is turned on; with TV, however,

• Please turn to page 88


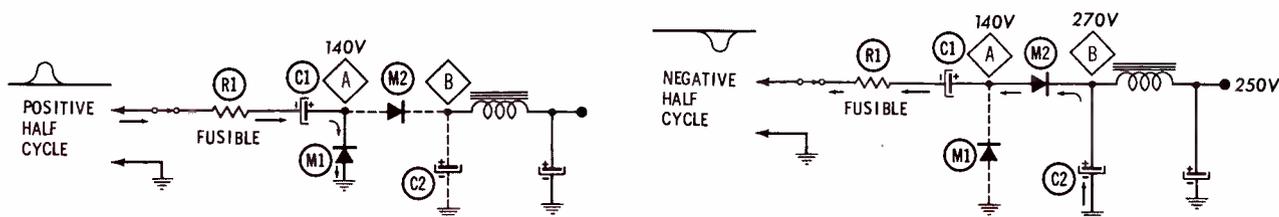


Fig. 2. DC output voltage of half-wave doubler is over twice the rms input.

FROM THE LEADING NAME IN WORLD-WIDE COMMUNICATIONS

*Electronic  
Elegance*

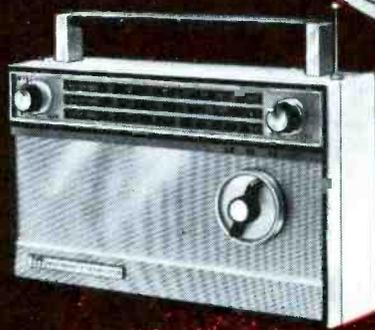

## NEW TRANSISTOR RADIO LINE

### PLEASURE-STYLING AT BETTER THAN COMPETITIVE PRICES

Here are some highlights which make the ITT Transistor Radio Package more than just another transistor radio line • Coast-to-coast service centers stocked with original parts • Recognized and accepted ITT prestige label on a quality product • Dealer-oriented sales program backed by national advertising and merchandising • Better than competitive pricing • 90-day warranty on all material • National network of warehouses • Sold through ITT franchised electronic distributors.

You can increase your radio department profits with ITT's complete line — ranging from the rugged AM/FM portable to the petite wrist strap model. See them at an ITT franchised electronic distributor or write direct.

**ITT**  
DISTRIBUTOR PRODUCTS DIVISION  
INTERNATIONAL TELEPHONE AND TELEGRAPH CORPORATION  
P. O. BOX 99, LODI, NEW JERSEY

# EVERYTHING IS A-OK--GO!



## PHILCO STAR BRIGHT 20/20 PICTURE TUBES

Starlight, STAR BRIGHT . . . here's the finest tube you'll see tonight! Philco Star Bright 20/20 Picture Tubes are not exactly intended to sail through space to the moon, but we couldn't be more particular about how they are made if our lives depended on them.


Everything that goes into\* a Philco Star Bright 20/20 Picture Tube is new! That means you need only open the carton . . . and install. Everything will be A-OK . . . no need to worry about checking, testing . . . or callbacks, either. Each Philco Star Bright 20/20 Picture Tube gets the same careful attention that we at Philco give to everything we make or sell . . . whether it is Philco equipment that rides the rockets to the moon . . . or Philco Star Bright 20/20 Picture Tubes to help you make more satisfied customers for your business.

\*Except the envelope which, prior to re-use, is inspected and tested to the same standards as a new envelope.



**PHILCO**  
Long Life Tested  
Receiving Tubes

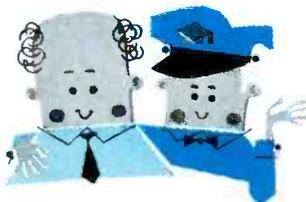A complete line of receiving tubes and numbers, manufactured under exacting quality standards, thoroughly tested and inspected. And each one bears the name PHILCO . . . a name your customers know and trust.




**Depend on Your PHILCO Distributor  
for Quality Replacements that  
Match Original Parts.**

PARTS & SERVICE OPERATIONS

# PHILCO®

A SUBSIDIARY OF *Ford Motor Company*

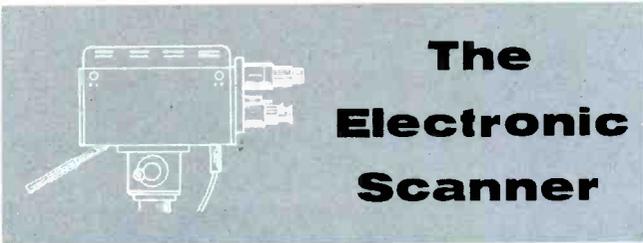

## The Electronic Scanner

### Microphone Given "Torture" Test



A newly developed Model 551 Industrial Microphone was recently subjected to a punishing torture test by Astatic. In an effort to prove the unit's durability, a company sales team attached the microphone to an auto bumper and dragged it 450 miles along the highway. The Model 551 worked perfectly at the end of the trip; the only damage was a missing front grill and some scuffed corners.

### To Change Company Name

Stockholders of Jerrold Electronics Corp., at their annual meeting, approved a proposal to reorganize the corporate structure of the company and to change its name to **The Jerrold Corporation**. "The new organization plan more fully reflects the diversified character of the company," according to president Sidney Harman. He further pointed out that, through recent acquisitions, Jerrold is now engaged in many phases of electronic communications, control, and display.

### Color Meeting At Channel Radio



A group of progressive dealers and technicians recently attended a color-TV meeting at **Channel Radio Supply**, Santa Barbara, California. The complete **Howard W. Sams** color-TV slide series was shown, providing those in attendance with a review of color principles as well as bringing them up to date on recent developments.

### Chicago-Area Firms Merge

B & K Manufacturing Company, Mark Mobile, Inc., and all subsidiaries of both companies, recently merged to form **Dynascan Corporation**. Carl Korn, former head of B & K, is president of the new concern. Dynascan Corp. will continue with the former activities of both companies—developing, designing, manufacturing, and selling electronic test apparatus, antennas, and microwave equipment.

### Cartridge Replacement Manual



A new manual released by **Sonotone** lists 1,200 models of phono cartridges made by 33 leading manufacturers. All are cross-referenced so the proper Sonotone replacement can be located easily. The "Phonograph Cartridge Replacement Manual" can be obtained by writing Electronics Application Div., Sonotone Corp., Elmsford, N. Y.

### CRT Data Offered

Three technical-aid publications on picture tubes and industrial CRT's are being offered by **Sylvania Electric Products, Inc.**, 1100 Main St., Buffalo 9, New York. The "Picture Tube Comparison Chart" and "Tube Selector Guide" are ten cents each, while "Characteristics of Cathode Ray Tubes" sells for 15 cents.

### Replacement Transistor Program Announced



The "Transistor Replacement Assistance Program" devised by **Semitronics** was planned to provide the products and sales aids necessary for high-volume transistor sales. More important, the program seeks to overcome the technician's too-prevalent fear of making incorrect replacement substitutions. Semitronics has assembled an assortment of 35 transistors that will replace 2000 original types.

## Your PHILCO Distributor—One-Stop Center for Every Servicing Need


Part No. 326-5029  
Part No. 326-5029-1  
with volume control.



FREE—2 attractive card displays with every dozen.

Speakers of molded plastic in streamlined design. 8 ohm voice coil impedance with .68 oz. Alnico magnet. Coaxial connector socket, cable connection.

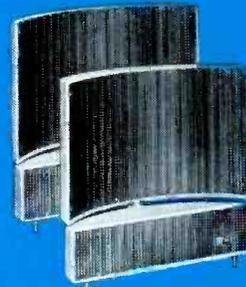
### PHILCO Deluxe PF 65 Stereo-Phone Swivel Speakers



A truly deluxe speaker set for the most particular stereo customer. Exclusive with Philco, these speakers use the famous Philco Fidelitron curved push-pull electrostatic reproducer. Unit on each Stereo-Phone swivels for tonal direction. Installs in minutes in any 8 ohm amplifier system. Glowing gold finish. 2" x 10" oval speaker.

Part No. 423-1003-1

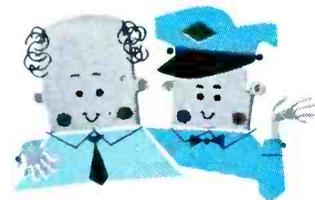PHILCO  
Direct-Pay Plans Totaled  
Over \$1 Million to  
"Independents" Last Year



Thousands of independent service businessmen are registered members of Philco Factory-Supervised Service Association. You, too, can be factory-trained; enjoy special benefits plus extra income. Ask your Philco Distributor about joining PFSS today!



**PHILCO**  
A SUBSIDIARY OF *Ford Motor Company*

MAIL THIS COUPON TODAY

Philco Parts & Service Operations, Dept. C-9  
"C" and Westmoreland Sts., Phila. 34, Pa.

Please send me FREE, the Philco Calculator. (Saves hours of time figuring out net costs and selling prices.)

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

Retailer with Service Dept.  Service Only.

Few things in a serviceman's daily experience bring the assurance that comes from smoothly-operating, accurately-calibrated test equipment. Working with a meter of questionable accuracy is as futile as trying to build a foundation on quicksand—the results are inconclusive and time-consuming. The price of accuracy does not run high; it merely involves periodic checks against standards that are easily acquired or already available in the shop.

Among the easy-to-obtain calibration standards are mercury batteries, 1% precision resistors, FM or AM broadcast stations, 60-cps line voltage, and certain crystals. Also, reasonable accuracy can be accomplished by first calibrating one piece of test gear, and then using it as a standard for setting up another. If, for example, a VOM is known to provide accurate voltage readings, this knowledge can be used in checking the milliammeter section. Lastly, there are commercially made instruments for calibration purposes, in case extremely close tolerances are desired.

### Why The Need

Over a period of time, a variety of factors tend to upset the accuracy originally built into test equipment by the manufacturer. Instruments undergo the same upsetting forces as the equipment they help troubleshoot—and sometimes more. Components age, internal heating alters values, and wear affects mechanical linkages. These add up to a condition which is often worse than outright failure—a progressive, almost imperceptible deterioration of precious accuracy. How far this shift in performance is permitted to go shows up in the service work.

The best way to keep instruments accurate is to follow a regular

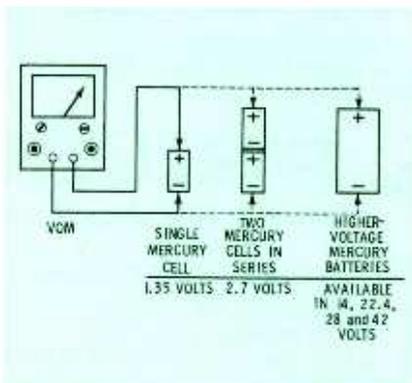


Fig. 1. Mercury cells are reliable as standards for DC voltage calibration.

# calibrate your own

# VOLT

by Len Buckwalter

schedule of calibration. This can often expose a defect before it becomes serious enough to cause trouble during routine measurements. A general rule of thumb for a calibration schedule could be: The more accurate the instrument, the more frequently it should be calibrated. A 1% instrument should be checked about once every three months. In the service shop, most test gear falls into the 1% to 5% category, and a checkup at least once every six months is advisable. Less accurate instruments, including such passive, nonpowered units as substitution boxes, may be checked on a yearly basis. The schedule should be accelerated for any instrument which is subjected to rough handling away from the shop. A chart, notebook, or other method of record-keeping should be used to record the date of calibration for future reference.

Some instruments cannot be calibrated very easily; a VOM, for example, seldom has internal calibrating controls. In cases like this, one workable solution is to find how inaccurate the unit is, and note the amount it deviates from the standard on a small chart which can be pasted directly on the case of the instrument. Then, when readings are taken, the chart can be consulted for corrections.

While it is possible to troubleshoot and repair minor inaccuracies in a VOM, this may be tricky unless one or two components have radically changed value. More often the problem develops from an accumulation of small errors which would require a major overhaul to correct.

Before considering specific calibration techniques, let's review some preliminary considerations applicable to most equipment:

1. *Physical Position* — Gravity affects the mechanical portions of any instrument, including the meter movement; therefore, it's a good idea to perform any calibrating adjustments with the unit in the same position used during routine operation. If your VOM or VTVM ordinarily sits vertically on a bench or shelf, don't lay it flat on the workbench during calibration.
2. *Mechanical Zero* — To compensate for small deviations, most meters have a screw slot just below the face for mechanically zeroing the pointer. This is adjusted with no power applied. The adjustment is most accurate if you gently tap the meter face with a fingertip to offset friction in the meter movement.
3. *Electrostatic Charge* — An accumulated electrical charge on a plastic meter face can affect accuracy. You can neutralize this during calibration, with a cloth wetted in household detergent. A few swipes across the meter face will remove the "static."
4. *Tube Aging*—If a new tube is being replaced at the time of calibration, it should be

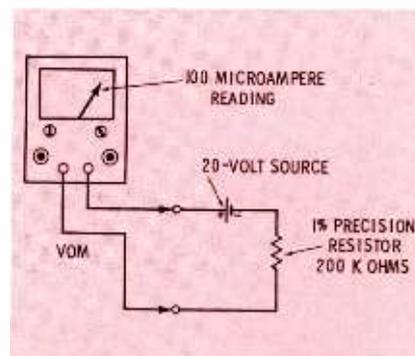


Fig. 2. Current through precision resistor is measured in milliammeter test.

# METERS

Keep instruments accurate by checking against readily-available standards.

"cooked" for at least 48 hours to prevent serious changes in instrument accuracy after a period of use—since new tubes initially display high emission which soon tapers down to stable levels. This aging can be done in the instrument itself, or in a tube checker.

5. *Operating Temperature* — If the unit contains tubes, permit them to warm up for at least an hour before attempting calibration.
6. *Mechanical Parts* — Tighten all set screws, knobs, and other mechanical parts which might have loosened during previous use.

## VOM Procedures

Probably the best reference source for calibrating the voltage scales of the VOM (or VTVM) is the mercury cell. (These batteries, nominally rated at 1.35 volts, can age for many months and still retain their original voltage characteristics.) However, the usefulness of zinc-carbon flashlight cells should not be disregarded completely. Although their voltage tends to drop off over a period of time, a fresh, unused dry cell may be expected to measure 1.55 volts.

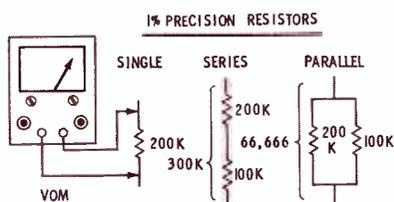


Fig. 3. Combination of precision resistors check accuracy of an ohmmeter.

Single cells of any type offer direct calibration points for low scales only. Yet this limitation is not severe, since any error in the instrument is likely to be uniform throughout all its ranges. Once the error on the lowest scale is known, the same deviation factor is generally applicable to higher scales, too. Direct calibration of the higher ranges is possible by placing cells in series, or by using batteries with higher voltage ratings (cells already placed in series by the manufacturer).

As you compare the voltmeter readings with the known voltage of the calibrating battery, it is important to interpret the results carefully. Manufacturers rate the accuracy of an instrument in a percentage of the *full-scale* reading. If you select a calibrating voltage which is less than full scale, you will have to calculate the permissible voltage error for that particular scale and note whether the reading falls within this limit.

As an example, assume that a 1.35-volt battery is connected to a 3% meter which is set to its 1.5-volt range. The pointer can be "off" by as much as  $\pm .045$  volts (3% of 1.5) and still be within tolerance. However, on the 15-volt scale, the permissible error is far greater;  $\pm .45$  volts (3% of 15). Even a significant error wouldn't show up if only a low-voltage calibrating battery were used.

Some typical voltage calibration setups are illustrated in Fig. 1. Once the voltage scales of a VOM are known to be accurate (or its calibration error has been noted), the milliammeter function can be checked by the use of Ohm's law

and some precision resistors. The test setup for this is shown in Fig. 2.

The choice of the resistor hinges on two key factors. First, it must be of known accuracy — easily solved by securing a 1% precision resistor. These are both inexpensive and readily available. The other factor is the value in ohms. The internal resistance of the meter, which will vary slightly from one VOM to the next, ultimately affects the amount of current through the meter. However, this factor can be eliminated by choosing a calibrating resistor of rather high value. If calibration is to be checked on the lowest current scale, the resistor value should be at least 200,000 ohms. On higher scales, the internal resistance is less significant and lower resistance values are usable.

Fig. 2 shows a typical setup for checking out the 100-microampere scale of a VOM. With 20 volts applied, the current through the resistor will be 100 microamperes.

Other current ranges are checked by using other applied voltages and/or resistance values. Ohm's law calculations can be worked out for the precision resistors on hand and the information noted for future reference.

Determining the accuracy of the resistance scales is the simplest of all the procedures, since you need only the precision resistors. The meter is first zeroed by touching the ohmmeter probes together and adjusting the ZERO knob. (Inability to zero the needle calls for battery replacement.) Readings are taken across suitable resistors and the results recorded. The total number of resistors needed to calibrate all ranges can be reduced by using series and parallel arrangements. Fig. 3 suggests some test setups for checking ohmmeter accuracy.

\* Please turn to page 92

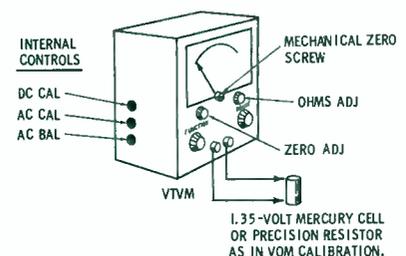


Fig. 4. These are the most important calibration points for typical VTVM.

# A GOOD GENERATOR SWEEPS

Alec was fiddling with the knobs on his sweep generator when Gene walked in, so he didn't realize at once that he had company. As he reached over to adjust his scope, he turned a little, and spotted the younger fellow. "Hi, Gene," he called. "The parts your boss sent you for are right over there on the counter. Tell him not to pay me; I'd rather he just replace them sometime soon. My stock sheet shows me they're running low."

Gene picked up the package. "The chief appreciates this," he said. Then, turning toward Alec's bench, he added, "I see you're wrestling with a dog there."

Alec looked surprised. "What makes you think so? As a matter of fact, this job was an easy one, and it's all but wrapped up. The customer complained about interference on all channels. He had an oscillating IF stage, but a new screen-bypass capacitor took care of that. I'm just giving it a final check."

"I wouldn't call an oscillating IF an easy job," Gene offered. "But the reason I thought it was a real brain-buster is the fact that you're using a sweep generator. We have one at our place, but I've never gotten into the habit of using it. I figure a bench man might hook one up if he has tried everything else and is still stuck."

"Too bad," Alec told the young technician. "A lot of other service

people have the same false notion about sweepers. Matter of fact, they're easy to use and can save you time on a lot of jobs. We automatically make a sweep check on many sets that come in with certain symptoms. An acquaintance of mine on the east side faithfully makes a sweep check of every completed job before it leaves the bench. What have you got against the instrument?"

"Lots of things," Gene began. "The sweep setup wastes a lot of time. I've seen ridiculous-looking response curves taken from sets that were working very well. On the other hand, I've seen others aligned to produce gorgeous curves, and yet they wouldn't deliver a decent picture until they were realigned with an ordinary RF generator and meter, or even by eye and ear! Besides, everyone knows that modern TV receivers seldom need alignment unless a component in a tuned circuit conks out. I've been warned about being alignment-happy."

Alec scratched his chin, and then said, "You know, that point about sets seldom needing alignment has real merit. But even so, the need for realignment is far from being the only reason for using a sweep generator. It's one of the fastest ways of giving tuned circuits and RF sections an over-all check. As a troubleshooting instrument, it can put the finger right on certain faults

that are hard to pin down with other methods. A darned good example is the oscillation I found in this set right here."

He continued, "What is it that bugs you about using a sweep generator? Have you really tried? Did you carefully follow instructions in the manual, and check the recommendations in the service notes for the set?"

Gene nodded positively to each of these questions. "After all that," he said, "I still get distorted curves that change shape every time I sneeze; markers will either get so big they wreck the curve or else will disappear even when I beef them up. It's just about impossible to work with multiple markers—and the whole business is far too time-consuming."

## Seeing Is Believing

Instead of answering immediately, Alec busied himself with firing up the equipment on the bench and making an adjustment or two. The IF response curve of the set soon stretched across the face of the scope (Fig. 1). Gene looked surprised. "You told me you were all finished with that one," he said, "and I just saw it putting out a sharp picture. How could it be, if the response really looks like that?"

Alec took one of the jumpers from the wall hook over his bench and, without a word, clipped one end to a ground post on the sweep generator, and the other to the receiver chassis. The curve on the scope flicked and assumed a shape (Fig. 2) similar to that shown in the service data spread out on the bench.

"What happened?" Gene queried. "One side of the sweep cable was already grounded to the TV set . . . oh, I get it! The manuals always talk about good grounds at these higher frequencies. In fact, some tell

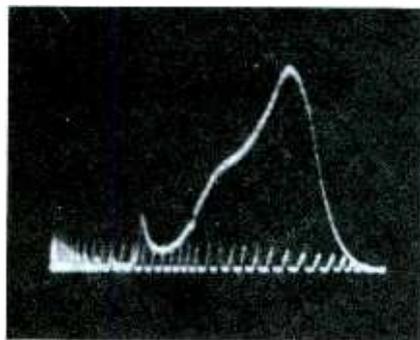


Fig. 1. Receiver is normal; distortion of curve is due to poor test setup.

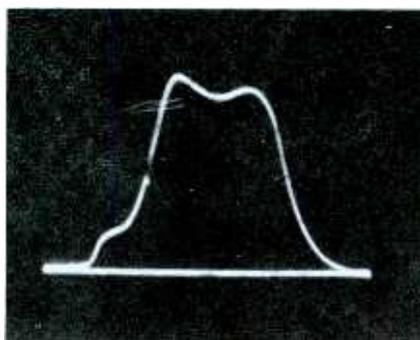


Fig. 2. Better ground connection from generator to receiver cured distortion.

# CLEAN

you that you should have a metal sheet across the top of your bench to insure good bonding and grounding during sweep alignment. And that's another nuisance. I wouldn't go to the trouble and expense of rearranging a good working setup to play with a new toy."

Alec finally spoke: "You don't need a metal top. First of all, try to clip the ground side of your sweep-generator cable as close to the injection point as possible. Then simply add another grounding jumper or two. That's all it should take to get an honest curve that won't be changed in shape by additional grounding or by grasping the output cable. I pulled off that jumper a moment ago when you weren't looking, to prove a point.

"Here's another thing to watch out for, as far as curve distortion is concerned." Alec pointed to the output-amplitude control on the sweep generator, which was set nearly to its minimum position. He cranked it up only slightly, and the curve changed (Fig. 3).

"That last curve was fine," Gene said, "but this one's a beauty. I didn't know they make sets like that. Look at that flat-topped response!"

"I'm looking," Alec countered. "What I did was to overload the set with too much signal. It's clipping. This is one of those cases where it's hard to get anything but a good curve, no matter what you do. But it'll never show up in performance."

"Why should the generator have so much output available, then?" Gene asked. "You had to turn it all the way down to get an honest display."

"Remember," Alec answered, "I'm going through three full stages of IF with good gain. You'll need lots more output when you're feeding the signal through a single, low-gain stage. But you should never use

more than you need. Start turning your control up from its minimum position. If you want a bigger display, use your scope's gain controls. Let me show you a few other things that can wreck a curve."

First he nudged the phasing control on the generator. This cut off a portion of the curve, making it unrecognizable. He explained that the sweep generator he was using had automatic blanking, which was now out of phase with the displayed signal. Before Gene could express his disapproval of this feature, Alec reminded him, "The blanking gives you the important zero-reference base line you need in many cases. Besides, it's extremely simple to get the phase adjusted right. The generator's instruction manual details a brief procedure for displaying the generator output without blanking, and for making the proper phase adjustment. Once you've done this, you use the same setting all the time; in fact, I've marked this spot on the front panel so I won't lose my place. Furthermore, I take the horizontal sweep from the binding posts provided on the generator to feed into my scope, not even using the internal scope sweep."

Alec then removed a jumper he'd been using to disable the tuner oscillator, and the curve changed shape immediately. Operating the fine-tuning control or the channel switch produced other alterations. Killing that oscillator obviously

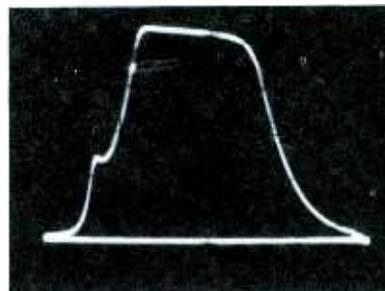


Fig. 3. Flat top on curve is too good to be true; the receiver is overloaded.

Response curves can be as neat as those shown in service data . . .

by Denis A. Gentry

avoided a lot of trouble.

Finally, he turned on his RF signal generator, which was connected to the sweep generator, and made a few adjustments. Soon he had a neat marker pip (Fig. 4) cleanly spotting his curve.

"I guess I should applaud," Gene grinned. "I know I'm not the only poor devil who has unsuccessfully struggled to get a clean marker, let alone getting one right away."

Alec reached over to his scope's vertical-input terminals and pulled away a small tubular capacitor. "Is this the sort of junk you get?" he wanted to know, pointing to the scope screen (Fig. 5).

"That's it, but what happened?" asked Gene.

Alec restored the capacitor—and the neat marker—then expanded the vertical and horizontal gain on the scope to show just the region near the marker on the curve (Fig. 6). "Let's consider what a marker is. You're sweeping a whole band of frequencies. The fixed generator is set to only one frequency—the one you want to mark. As the sweep passes through this particular frequency, its output zero-beats with that from the single-frequency generator. The wiggles you see are heterodyne products on each side of exact zero-beat. It's these low-frequency heterodyne signals that show up so well.

• Please turn to page 93

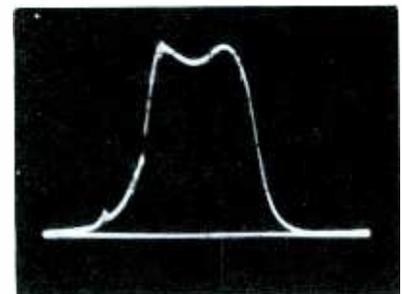


Fig. 4. The marker pip should be small and neat for best visibility on curve.



QUICKER SERVICING  
by George F. Corne, Jr.

# COLORS ADRIFT?

check color sync!

In my own experience, and that of other technicians I know, color-sync defects have been few and far between. However, those we did encounter were tough ones. Now that we're receiving more frequent calls to service color receivers, we've decided we had better acquaint ourselves more thoroughly with color-sync functions and adopt a workable technique for locating defects in these stages.

## What's Color Sync?

The color-sync signal transmitted during color telecasts is a short burst (approximately eight cycles) of a 3.58-mc subcarrier reference signal. The main purpose of this burst signal is to synchronize the local 3.58-mc oscillator within the receiver so it will operate in step (in phase and on frequency) with the subcarrier oscillator at the transmitter. Don't confuse the color-sync signal with the deflection sync signals; color sync is used by the chroma stages only and has no effect on the vertical or horizontal circuits.

The operational theory of color sync circuits was explained in the article "Understanding Color Sync" in the November, 1961 PF REPORTER. You may want to review that article in conjunction with studying the servicing procedures given here.

The circuits shown in the schematic diagram are typical of the color-sync stages found in late-model color receivers—the burst amplifier, sync-phase detector, ref-

erence oscillator, and oscillator-control circuit. They are found in nearly all color receivers, with occasionally a few variations, such as an extra burst stage, an automatic color-control stage (ACC), or a different sync-takeoff point. Whatever the circuit arrangement may be, the stages must still perform the same function — keeping the local 3.58-mc oscillator exactly on frequency, so the proper colors are reproduced on the screen.


## Waveform Checks

Signal tracing the color-sync signals with a scope is perhaps the fastest method to locate a defective stage—provided you know what to expect. The waveforms which illustrate this article were taken using the color-bar output of a keyed-rainbow generator. The RF-type generator was connected to the antenna terminals of the receiver, while the scope was connected through a direct probe to the points indicated on the diagram. Connecting the scope in this manner may cause a slight shift in the hue of the color bars on the receiver screen, but this will not affect your troubleshooting. If you use a low-capacitance probe, it will minimize the loading effect of the scope—just be sure you take the attenuation factor (usually 10:1) of the probe into account when you measure the amplitude of the signal.

Let's explore the color-sync circuits according to the numbered points circled on the schematic,

and see what signals should appear at each point. Also, we can discuss some symptoms which might occur when a signal is missing or weak.


### Point 1

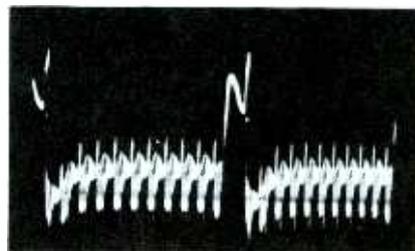

The output of the video amplifier stage is fed from this point to the chroma-bandpass and burst-amplifier stages. The waveform here shows us that the color signal is passing through the front-end stages in good shape. Loss of this signal, of course, would result in a "no-color" condition.

The keyed-rainbow signal at Point 1 contains the horizontal sync pulse, the burst signal (which can be seen as a high peak sitting on the back porch of the horizontal pulse), and ten wide pips, representing the color bars. The dark areas between each of the pips correspond to the spacing bars in the keyed-rainbow pattern.

### Point 2

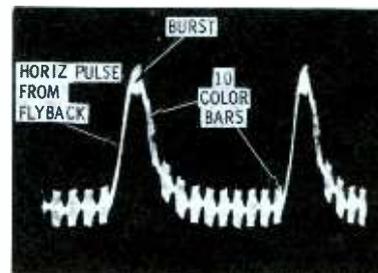

Look here for the presence of an incoming burst-and-color-bar signal combined with a keying pulse from a winding on the flyback. The burst signal can be seen sitting on the peak of the positive-going horizontal pulse, right where it belongs. The ten color bars produced by the generator are also well-defined.



If the horizontal keying pulse is absent at this point, the picture may be out of color sync, with the colors actually drifting around the screen; or perhaps it is in sync but with colors of the wrong hue.

Chances are that the burst signal will pass through the amplifier, even with the keying pulse missing, but the output signal will not be the good, clean burst waveform we need.

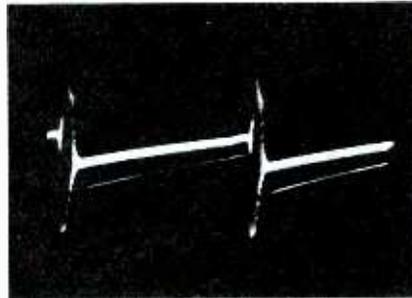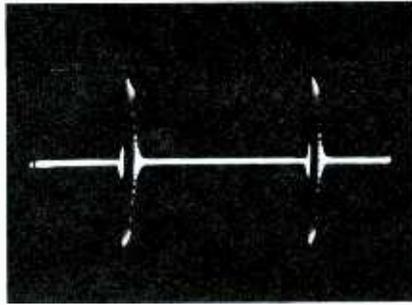**Points 3, 4, 5, and 6**

What you're checking for at these points is the *presence* of a clean *burst* signal. As mentioned before: At the grid of the burst amplifier the burst signal rides on the peak of the flyback pulse. This pulse appears during horizontal retrace time, and keys the burst amplifier into conduction. Since the burst signal arrives at the same time, it will appear in the output of the tube. On the other hand, the color bars arrive during active horizontal scanning time, and will not be developed in the output because the tube is cut off during that time.

Check for a good, clean burst signal at both ends of the burst-transformer secondary windings (Points 3 and 4), and be sure it



is getting through the coupling capacitors (Points 5 and 6). If trouble develops anywhere in this secondary circuit, it can cause a complete loss of color, wrong colors, or a loss of color sync.


The reason complete loss of color can occur is that the burst-

takeoff point for the color-killer stage is in this circuit. Remember, the chroma bandpass stage is biased into cutoff by the color-killer stage *unless* the burst signal is present to disable the killer. With the killer tube operating, due to the lack of a burst signal (or for any other reason), no color can appear on the screen.








When you have a loss of color sync (color bars display a "barber-pole" effect, with different colors floating horizontally or vertically), try rotating the TINT control through its range while watching the CRT screen. This control affects the phase of the burst signal fed into the phase detector. If the color bars sync into place during this test, the trouble is probably in the balance or filter networks of the phase-detector circuit.

If the output of the burst amplifier is good, you obviously have a defect in either the phase detector, the oscillator control circuit, or the oscillator itself. The

• Please turn to page 84

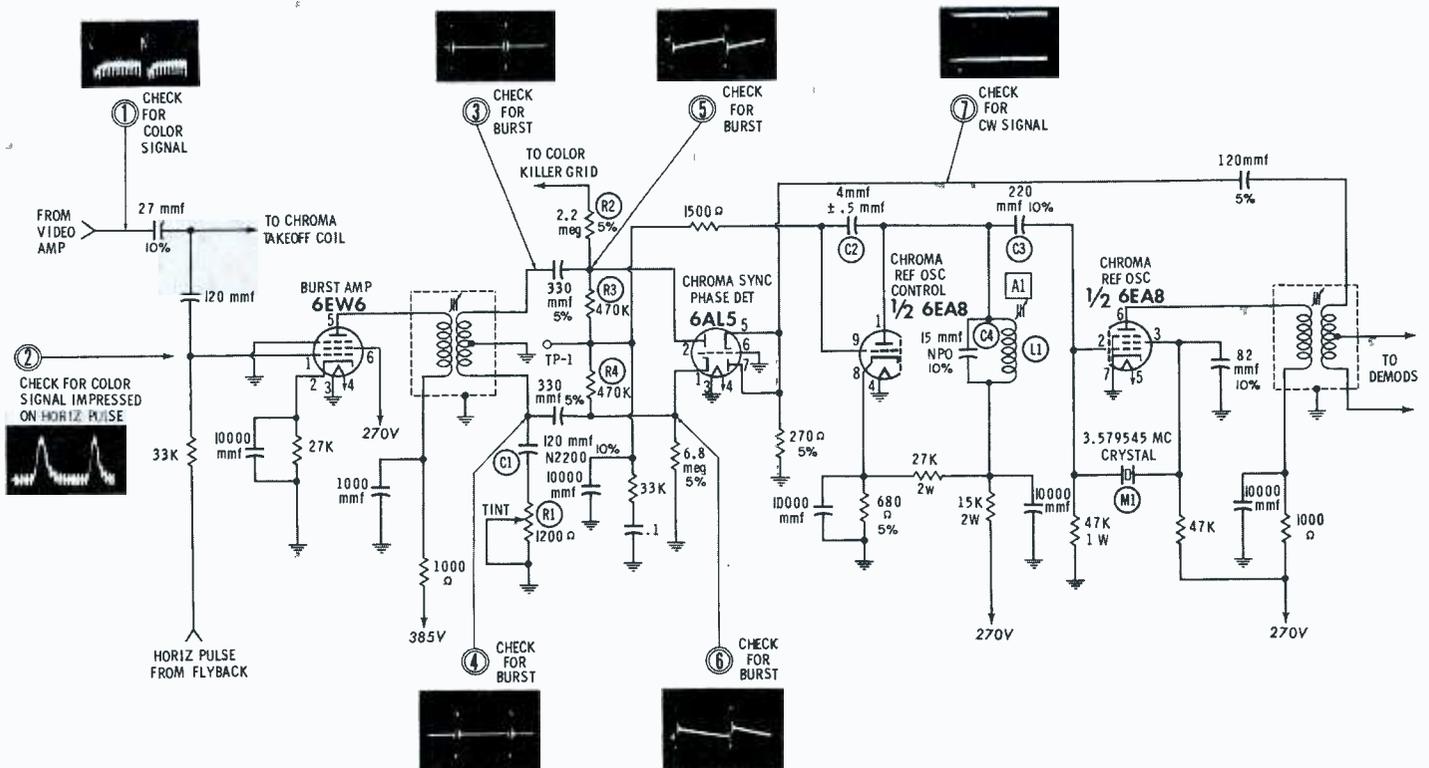

The transmitted color-TV signal contains a *color burst* (a sample of the chroma subcarrier) in addition to video, chroma, and deflection-sync modulation. In the receiver stages shown, the burst is amplified and compared with the 3.58-mc reference-oscillator signal. Any frequency error causes the chroma sync phase detector to apply a correction voltage to the grid of the oscillator-control tube, and the change in conduction of this tube makes the needed oscillator-frequency adjustment.

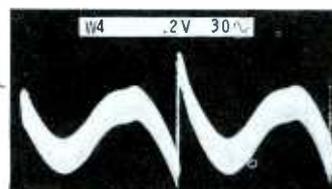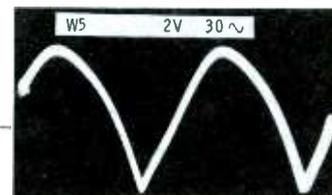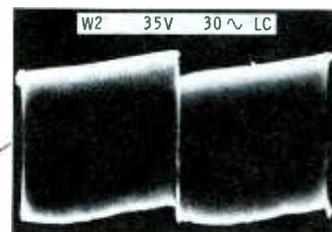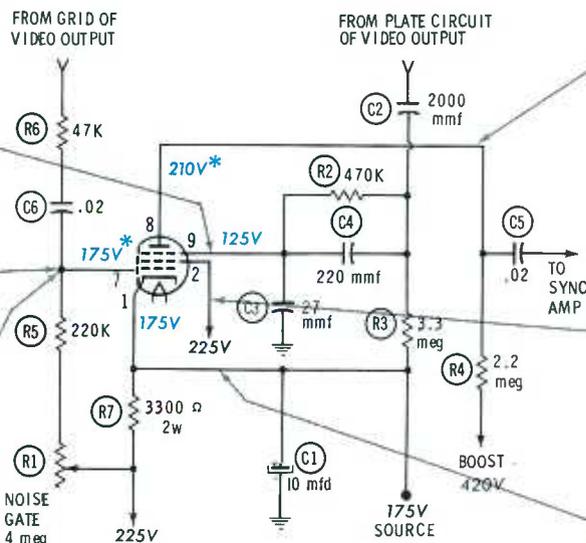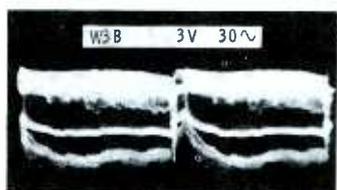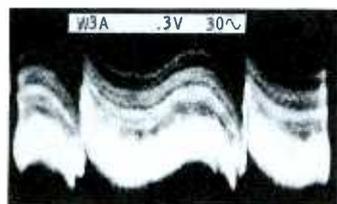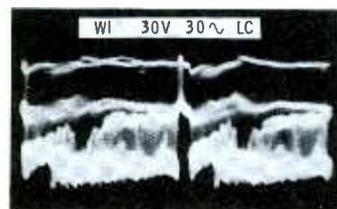

DC VOLTAGES taken with VTVM, on inactive channel, with antenna terminals shorted. \*means voltage will vary when signal is applied or control is adjusted. See "Variations."

WAVEFORMS taken with wide-band scope; receiver controls set for 50-volt p-p video to CRT. Low-cap probe (LC) used where direct probe might distort waveshape or amplitude.

### Normal Operation

Half of a 3-, 4- or 6BU8 tube operates as sync separator with built-in noise-limiting feature. Composite video input (W1) is fed to pin 9, and only sync pulses (W2) appear in output at pin 8. A much weaker composite-video signal, with polarity opposite to that of W1, is applied to pin 7. Normally, it has little effect on 'BU8 conduction; however, strong negative pulses of noise interference in video signal can momentarily increase bias at pin 7 enough to cut off the 'BU8 and clip noise out of W2. Noise-limiting action also affects AGC-keying section of tube (pins 1, 7, and 2, plus a separate grid—pin 6—and plate—pin 3). Circuit shown here, used in Motorola Chassis TS-570, typifies BU8 sync-stage designs in most major respects.

### General Troubleshooting

Usually, the first sign of trouble developing in a 'BU8 sync circuit is critical vertical hold. Slight horizontal instability appears in some cases. If scope checks of the sync separator indicate a distorted output signal and reasonably normal input, check voltages *with* and *without* signal to help to localize the fault.

### Operating Variations

#### PIN 9

DC voltage almost constant under all signal conditions—unlike triode sync separators. Waveform amplitude will change greatly with contrast adjustment, but only slightly with RF signal variations. This high-impedance circuit will be loaded even by low-capacitance probe, so rough, jittery appearance of W1 is normal. Use of direct probe decreases over-all signal amplitude and attenuates horizontal pulses.

#### PIN 8

DC voltage should rise to about 225 volts when strong station signal is applied. W2 maintains nearly constant amplitude. Direct probe distorts waveshape only slightly, but reduces amplitude.



#### PIN 7

At minimum-resistance setting of R1, positive voltage maintains zero bias between pins 1 and 7, swamping out waveform (see W3A). This setting is correct unless noise interference is a problem; then R1 should be adjusted to allow a few (not more than 10) volts of bias at pin 7. Waveform then appears as in W3B, and noise peaks in signal can cut off tube. With too much bias, negative sync tips in W3B can produce cutoff.


## Vertical Sync Critical

Slight Horizontal Bend  
at Top of Picture


C5 Slightly Leaky

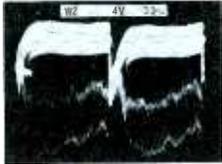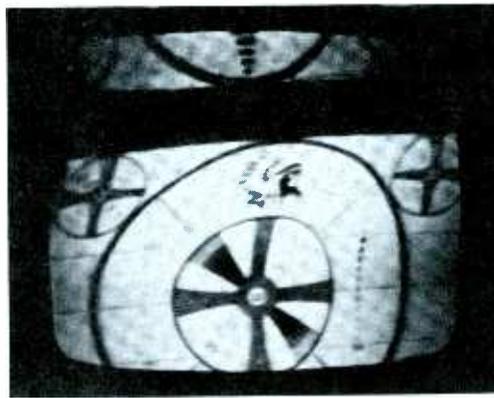

Waveform  
Analysis

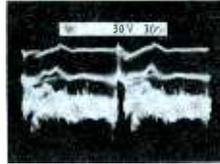

Voltage and  
Component Analysis

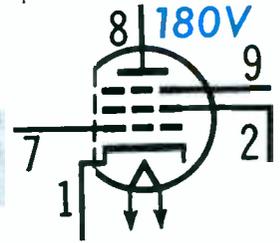



Only abnormal waveform is W2. Most important discrepancy here is low amplitude of only 4 volts p-p—too weak for solid vertical lock-in. Also note distortion in signal for short interval just after each vertical sync pulse—base line pulled down from top, and horizontal sync pulses practically lost. This accounts for bending at top of picture. During rest of time, horizontal sync-pulse amplitude is sufficiently constant for reasonably good synchronization of stable horizontal oscillator used in this receiver. W1 is normal; two jagged pips at top, which travel through waveform as picture rolls, are simply due to stray pickup of vertical retrace pulses.

All DC voltages are okay except on plate, where reading is 15% below normal. Slight leakage through C5 increases DC voltage drop across R4, thus reducing plate voltage of 'BU8. With plate at a DC level only a few volts higher than cathode, 'BU8 passes very little current, and only a weak signal voltage is developed across R4. Since there are no other discrepancies in DC or signal voltages, abnormal reading at pin 8 definitely indicates trouble in plate circuit. Similar symptoms and test indications would have been observed if R4 had greatly increased in value (to over 10 megohms). Leakage in C5 showed up in test with 200 volts applied.

## Vertical Sync Critical

Horizontal Sync  
Appears Normal

C6 Moderately Leaky

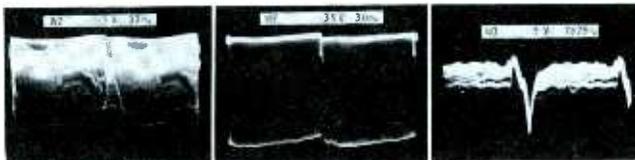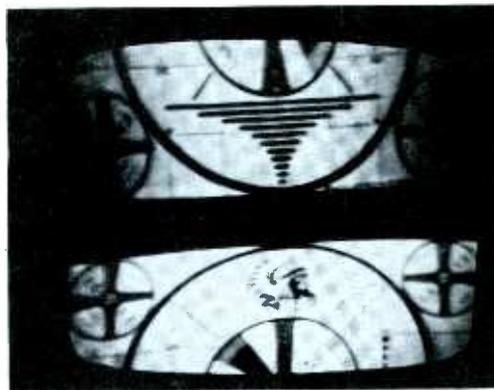


Waveform Analysis

W3 looks clean, but amplitude is 5V p-p—far greater than normal. Output waveform W2 contains normal horizontal pulses; but note virtual absence of vertical pulses (white dots near bottom of normal waveform). No wonder vertical sync is poor! Another look at W3, at scope sweep frequency of 7875 cps, gives clue to why horizontal hold seems unaffected. Horizontal sync pulses build up only gradually to negative peak, and limiter grid is driven into cutoff too late to prevent horizontal pulses in W1 from passing through 'BU8.

## Symptom Analysis

Picture will not "snap" into vertical sync, indicating deficient sync-pulse amplitude. Check of horizontal-hold action indicates good stability, so trouble is evidently affecting only vertical sync. NOISE GATE control must be set at minimum-resistance position to prevent losing all sync, indicating noise-limiter trouble.

Voltage and  
Component Analysis

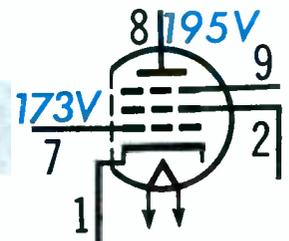


With NOISE GATE at minimum, 2-volt bias exists between pins 1 and 7; normal condition is zero bias. Even though this error seems small, it is strong evidence of trouble at pin 7. Plate voltage is low, but not significantly so; with signal applied, it rises to 225 volts, the same as in normal operation. More severe leakage in C6 would have been diagnosed as AGC trouble, but sync disturbance would be noticed first if defect developed gradually. Another fault that would cause similar symptoms is loss of capacitance in cathode bypass C1.

## Vertical Sync Critical

Horizontal Sync Critical  
With Slight Phasing Error

R3 Open

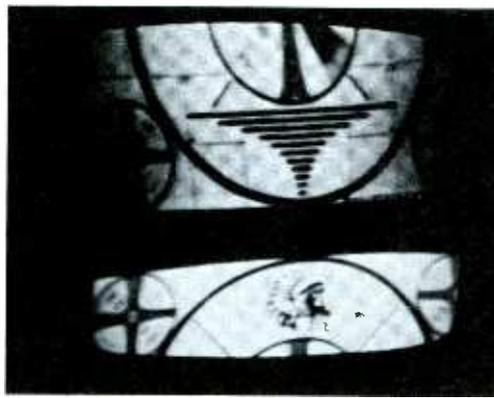

Waveform Analysis

Amplitude of W1 is normal, except vertical sync pulses rise higher than horizontal pulses even when low-cap probe is used. W2 is virtually absent, consisting only of video and hash with amplitude of less than 1 volt p-p. At scope-sweep rate of 30 cps, slight notches along bottom edge of waveform mark remnant of vertical pulses. Different view of W2, at 7875 cps, shows stubs of horizontal pulses. These waveforms might seem to indicate plate-circuit trouble, but it would be wise to check DC voltages before jumping to this conclusion.

## Voltage and Component Analysis


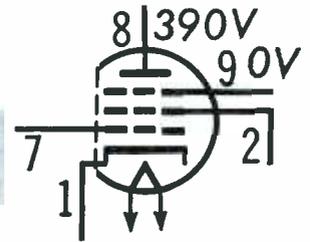
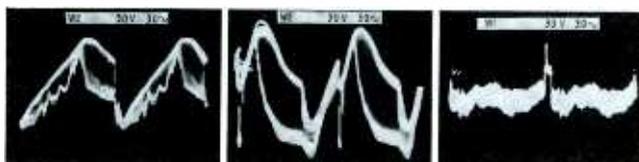


Plate voltage rises to 390 volts—almost the full value of boost. This drastic reduction in voltage drop across R4 is due to almost complete loss of plate current in sync section of 'BU8. Reason for cutoff is apparent when pin 9 is checked; DC voltage is missing, and resultant bias between this grid and cathode is 175 volts! Since connection to pin 1 via R3 is only DC path through which normal operating potential can be applied to pin 9, this connection is obviously broken. Defect does not prevent input signal from reaching grid.

## Horizontal Sync Extremely Unstable

Vertical Sync Normal

C4 Open

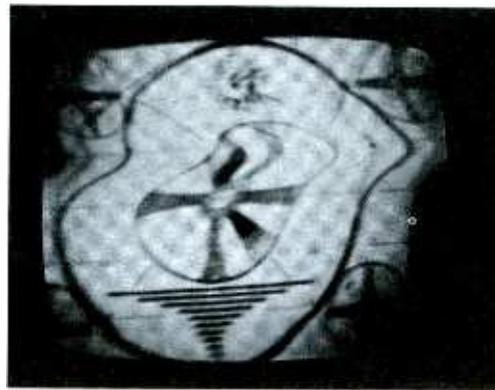


Waveform Analysis

Steep "cliff" in W2 is formed by leading edge of vertical sync pulse, which has normal amplitude. However, base line along top of waveform is distorted into hump-back shape, and amplitude of horizontal pulses varies erratically from zero to slightly over one-half of normal. (Note "scalloped" appearance of line traced by pulse tips.) W2 is shown twice to demonstrate changes in shape and amplitude caused by fluctuations in video program material. In W1, vertical sync pulses look okay, but horizontal sync pulses appear to be missing.

## Symptom Analysis

Horizontal hold is very critical, varying amounts of picture bending or pulling are noted, and sync is usually lost when station signal is interrupted. Either horizontal-AFC or sync circuits could be at fault. Checks of operating controls are inconclusive; bench testing is necessary to localize trouble.

## Voltage and Component Analysis

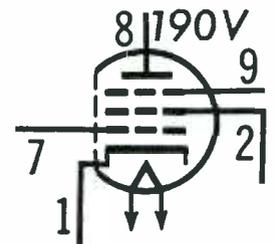

DC voltage readings give very meager clues to this trouble, and can even be misleading. Although plate voltage is slightly reduced, it is still "within tolerance," so change can easily be overlooked. If a technician *did* spot this abnormality, he would waste time looking for plate-circuit trouble. Condition of C4 has very little effect on DC grid voltage; its functions are merely to help stabilize grid voltage against momentary signal fluctuations, and to bypass high-frequency signal components (including horizontal pulses) around R2.



## are you replacing top quality tubes with identical top quality tubes?

You can, now! You can carry the identical tubes that you find in most of the quality TV sets you're servicing. Chances are, you were not aware that these sets were designed around special "Ampliframe" tubes originated by Amperex.

For some time now, designers have been using many Ampliframe tubes in their quality TV receivers and we can tell you now that even more Amperex tubes are being designed into the sets you'll be handling in the future.

Compare, if you will, the performance of Amperex Ampliframes with conventional IF tubes: They provide 55% higher gain-bandwidth, increase TV set reliability by simplifying circuits and they make your servicing easier, faster and more profitable because their extraordinary uniformity virtually

eliminates time-consuming realignment when you replace tubes.

About the only way, then, that you can be sure of optimum satisfaction for your customers and maximum profit operation for yourself is to make room in your caddy right now for the identical, matchless-quality tubes that are being designed into the original sets... now available to you from your local distributor with the brand of the originator — the Amperex brand.

Next time you visit your distributor, look for the green and yellow box and ask about Ampliframe tubes for TV and other entertainment replacement applications. Amperex Electronic Corporation, 230 Duffy Avenue, Hicksville, L. I., N. Y.

In Canada: Philips Electron Devices Ltd., 116 Vanderhoof Ave., Toronto 17.



ANOTHER **PRECISION** SERVICE TIP FOR YOU.

# PRECISION PETE

## "CHECKING OUT AT A HOTEL"

SECRETARIES' CONVENTION JUST ARRIVED, PETE. NEED EVERY TV AND RADIO SET IN TIP-TOP CONDITION RIGHT AWAY.

RITZ HOTEL WELCOMES SECRETARIES OF AMERICA

AT LEAST 80% OF ALL SERVICE PROBLEMS ORIGINATE WITH THE TUBES. AND THE FASTEST WAY TO TEST ALL YOUR SETS IS WITH MY **PRECISION 650 TUBE TESTER**. LET'S START CHECKING "SHORTS" MAX.

I'M WAY AHEAD OF YOU, PETE!

I MEAN "SHORTS" IN RECEIVING TUBES—LIKE THE **MINIATURES, COMPACTRONS, NUVISTORS, NOVARS AND OCTALS** THAT CAN BE TESTED WITH THIS **650**. IT ALSO ANALYZES **CONTROL GRIDS** FOR **LEAKAGE, EMISSION AND GAS CONTENT**.

YES, AND, WITH THIS **AD-65 ADAPTER**, YOU CAN EVEN TEST **PICTURE TUBES** FOR **SHORTS AND CATHODE EMISSION**.

THERE'S NO CATHODE SHORT OR LEAKAGE IN THIS TUBE. I'LL ROTATE THE "D" SWITCH THROUGH ITS TWELVE POSITIONS AND CHECK THE OTHER ELEMENTS.

BETTER CHECK CATHODE EMISSION. I'LL JUST PRESS THIS BUTTON AND SEE.

THERE, THAT'S THE LAST ONE. TWENTY-FOUR SETS CHECKED OUT IN JUST THREE HOURS, THANKS TO MY **PRECISION 650 GRID ANALYZER TUBE TESTER**.

WITH ALL THE NEW BUSINESS WE'VE BEEN GETTING SINCE WE SIGNED AS **REGISTERED PRECISION SERVICEMEN**, DON'T YOU THINK WE NEED MORE HELP...LIKE A SECRETARY FOR INSTANCE?

MMMM. THIS SET JUST CAME OUT LAST MONTH. DO WE HAVE A **DATA CARD** ON IT, MAX?

SURE DO, PETE. **PRECISION'S DATA SERVICE** KEEPS THE **650** FROM BECOMING OBSOLETE. LOOK HERE.

### FREE SERVICE BULLETIN

SERVICEMEN: THE **PRECISION 650** (DEALER NET: \$69.95; AD-65: \$5.95) LETS YOU FULLY TEST ALL POPULAR RADIO, TV AND COMMUNICATIONS TUBES FAST. WANT TO KNOW MORE? WRITE FOR FREE BULLETIN #102.

# PRECISION APPARATUS CO. INC.

70-31 84 ST. GLENDALE 27, NEW YORK

ALL **PRECISION** TEST EQUIPMENT IS GUARANTEED FOR ONE FULL YEAR.



WHEN IT COMES TO SECRETARIES, I DON'T NEED ANY HELP.

# GOLDMINE OF PRACTICAL INFORMATION

helps you get the most  
out of test equipment

It's easy to use  
**ELECTRONIC  
TEST  
EQUIPMENT**

by LARRY KLEIN and  
KEN GILMORE

192-page goldmine of practical information on electronic test equipment shows you how to select and use this equipment to the best advantage in many many applications. Only up-to-date book covering all the basic test instruments. Of benefit to both the newcomer to servicing and the old "pro".

- ① Saves you money on the purchase of new equipment because you'll know what features to look for. You avoid buying equipment you don't need.
- ② Saves you money in keeping your own test equipment in top condition because you're more familiar with what makes it tick. No more sending equipment back to the factory for adjustment or repair when you can do the job yourself.
- ③ Makes your present equipment more valuable by showing you new ways to use it.
- ④ Opens new fields of servicing profit because it makes you familiar with instruments used for radio and TV servicing, and industrial and audio.

Equipment covered is from simple VOM's and VTVM's through signal generators, oscilloscopes and other test equipment and helpful accessories. #308, \$4.00.

### NEW! FOR EVERY SERVICEMAN

**REPAIRING TV REMOTE CONTROLS** by Leon Cantor & Harry Horstmann. Here's how TV servicemen can successfully meet the challenge of repairing different types of TV remote control systems! This single volume offers servicemen a comprehensive repair guide for every popular TV remote control system. Includes detailed descriptions of each type's circuit operation, repair methods and alignment techniques. Covers one, two, three and four button transmitters; power-line, lights, vacuum tube and transistor-operated types, and their respective remote receivers. Armed with this book, professional TV servicemen can turn "dogs" into simple house calls. #303, \$2.50.

**INTERNATIONAL TRANSISTOR SUBSTITUTION GUIDEBOOK** by Keats A. Pullen, Jr. Eng. D. (Scientific Staff, Ballistics Research Labs., Aberdeen Proving Grounds) direct substitutions only "possible substitutions deemed doubtful", that is they work only in some cases, were omitted. . . . thus, substitution guide is a "safe" guide." — INDUSTRIAL ELECTRONIC ENGINEERING AND MAINTENANCE. #276 — \$1.50.

At your bookstore, parts distributor or direct

### 10 DAY MONEY-BACK GUARANTEE

John F. Rider Publisher, Inc. PF-9  
A Division of Hayden Publishing Co., Inc.  
116 West 14th Street, New York 11, N. Y.

Enclosed is \$\_\_\_\_\_ Please send:

- It's Easy to Use Electronic Test Equipment, #308, \$4.00  
 Repairing TV Remote Controls, #303, \$2.50  
 International Transistor Substitution Guidebook, #276, \$1.50

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

about 1000 ohms. I replaced the resistor, and the 6BQ6 plate stayed black this time. Since the shop repair, the set has operated normally for over a year with the same 6BQ6. Without checking the record file, we might have been changing 6BQ6's ad infinitum.

Another handy use for case histories on file is to help us settle recall disputes diplomatically with customers.

It's either difficult for people to remember, or easy for them *not* to remember, what you did on the previous call — especially within 90 days afterward. There was one freeloader who barged into our shop with a portable TV. I was working the counter. He blurted, "Had the TV here a few weeks ago. You fixed it, but it still ain't right."

Instead of playing it by ear, I pulled his file card and laid it alongside his TV. Then I turned it on. There was snow in the picture. I jiggled the built-in antenna, and the picture changed from clear to snowy, coinciding with my jiggling. I said, "You need a new built-in antenna."

"So," he snorted, "put it in, but I'm not paying for it. It should have been done when I had it here about ten days ago."

I picked up his file card and, scanning it, politely said, "According to our files, Mr. Jones, the last service call on your TV was about four months ago."

"Well," he bluffed, "time goes fast."

"It says here we repaired a vertical sweep trouble. There was too much vertical sweep, and a capacitor in the plate circuit of the vertical oscillator had opened up."

He tried to bluff a bit more: "Well, the antenna was supposed to be changed, too."

Then I clinched it: "It says here we told you about the antenna and you told us not to do the job. Here's your signature verifying it."

He smiled weakly, "Funny thing how a guy forgets. Yeh, I remember now. Fix it up, will ya?"

"Yessir," I answered, and installed a new built-in antenna.

### Perpetual Mailing List

Your customer mailing list is a vital organ of your TV service business. Without it, you are helpless when business falls off due to a sea-

sonal slump or when your competitors get aggressive.

With it, you can spark up business and compete more successfully. The uses of the mailing list are almost limitless. Besides giving free rein to your own imagination, you can read up on promotions (see "Summer Service Promotions" in July PF REPORTER) or get someone to help you think up ideas. As an aid, most of the manufacturers and publishers have professional advertising programs you can adopt.

The main thing is to have a completely up-to-date file. There are many ways to compile the list and to keep it up to date. The best way is to work on it regularly; a half hour a day is enough. Either you or your appointed assistant must take your completed service-call forms and convert the information into file-card form. If you do it daily, the effort is small and the list is always fresh. If you let it pile up for weeks or months, you have a massive project on your hands, and your file is partly out of date most of the time.

A well-maintained file is ready to use as soon as business slacks off. You can sift through it and compile lists of customers who would be particularly interested in various special offers. To the people who use rabbit ears, you can sell outdoor antennas. To the customers with outdoor antennas, you can suggest rotators and high-gain replacements. To set owners who have more than one TV, the installation of a two-set coupler is easy to sell.


The customers whose TV's have removable safety glass can be tempted with an inexpensive clean-up special. When you're able to make a good buy on a particular type of CRT, you can send out a



NEW, MODERN, PORTABLE... FOR THE MAN ON THE GO...

as easy to use as a voltmeter

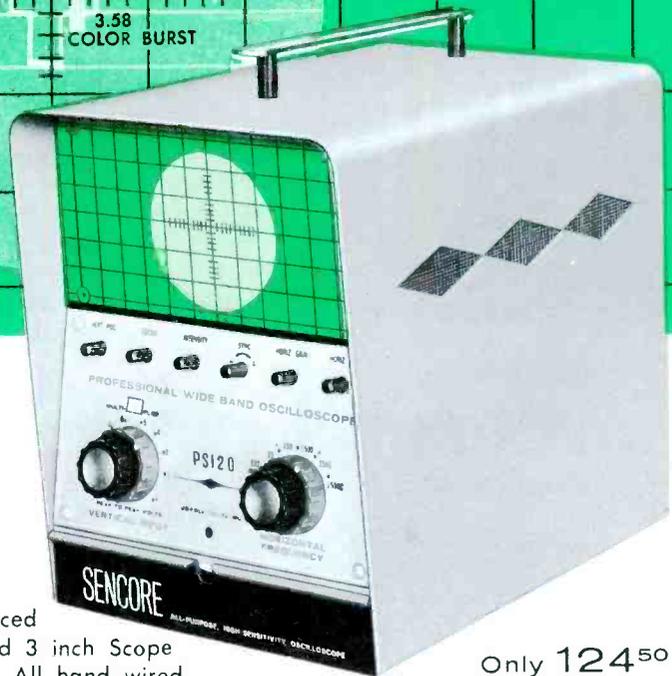- A new 3 inch Extended View Portable Scope with New Features and Performance Unmatched by even the most Costly 5 inch Oscilloscopes



NEW

## SENCORE PS120 PROFESSIONAL WIDE BAND OSCILLOSCOPE

Lowest priced Wide Band 3 inch Scope anywhere. All hand wired.

Only 124<sup>50</sup> net

Here it is, the scope that technicians, engineers and servicemen from coast to coast have been demanding. A portable wide band scope that can be used on the job anywhere, yet has the highest laboratory specifications for shop or lab. Cumbersome color TV sets, remote audio and organ installations and computers are just a few of the jobs that make owning a scope of this type so essential. Why consider a narrow band scope, when for only a few dollars more, this professional wide band sensitive scope equips you for any job.

- The PS120 provides features never before offered. Only two major controls make the PS120 as easy to use as a voltmeter. Even its smart good looks were designed for functional efficiency. New forward thrust design, creating its own shadow mask, and full width calibrated graph increase sharpness of wave form patterns. A permanent chromed steel carrying handle instead of untidy leather strap and a concealed compartment under panel for leads, jacks and AC

line cord make the PS120 the first truly portable scope combining neatness with top efficiency.

- Electrical specifications and operational ease will surpass your fondest expectations. Imagine a wide band scope that accurately reproduces any waveform from 20 cycles to 12 megacycles. And the PS120 is as sensitive as narrow band scopes... all the way. Vertical amplifier sensitivity is .035 volts RMS. The PS120 has no narrow band positions which cause other scopes to register erroneous waveforms unexpectedly. Another Sencore first is the Automatic Range Indication on Vertical Input Control which enables the direct reading of peak-to-peak voltages. Simply adjust to one inch height and read P-to-P volts present. Standby position on power switch, another first, adds hours of life to CRT and other tubes. A sensitive wide band oscilloscope like the PS120 has become an absolute necessity for trouble shooting Color TV and other modern circuits and no other scope is as fast or easy to use.

### SPECIFICATIONS

#### WIDE FREQUENCY RESPONSE:

Vertical Amplifier—flat within 1/2 DB from 20 cycles to 5.5 MC, down —3 DB at 7.5 MC, usable up to 12 MC.  
Horizontal Amplifier—flat within —3 DB from 45 cycles to 330 KC, flat within —6 DB from 20 cycles to 500 KC.

#### HIGH DEFLECTION SENSITIVITY:

	RMS	P/P
Vertical Amplifier—Vert. input cable	.035V/IN.	0.1V/IN.
Aux. vert. jack	.035V/IN.	0.1V/IN.
Through Lo-Cap probe	.35V/IN.	1.0V/IN.
Horizontal Amplifier—	.51V/IN.	1.44V/IN.

#### HIGH INPUT RESISTANCE AND LOW CAPACITY:

Vert. input cable	2.7 Meg. shunted by approx. 85 MMF
Aux. vert. input jack	2.7 Meg. shunted by approx. 20 MMF
Through Lo-Cap probe	27 Meg. shunted by 8.6 MMF
Horiz. input jack	330 K to 4 Meg.

#### HORIZONTAL SWEEP OSCILLATOR:

Frequency range— 4 ranges, 15 cycles—150 KC  
Sync Range— 15 cycles to 8 MC—usable to 12 MC

#### MAXIMUM AC INPUT VOLTAGE:

Vertical input cable—	} 1000 VPP (in presence of 600 VDC)
Aux. vert. jack—	
Lo-Cap probe—	
Horiz. input jack—	

#### POWER REQUIREMENTS:


Voltage— 105-125 volts, 50-60 cycle  
On pos. 82 watts  
Stby. pos. 10 watts

SIZE: 7" wide x 9" high x 11 1/4" deep—weight 12 lbs.




The PS120 is a must for color TV servicing. For example, with its extended vertical amplifier frequency response, 3.58 MC signals can be seen individually.

**SENCORE**  
ADDISON 2, ILLINOIS

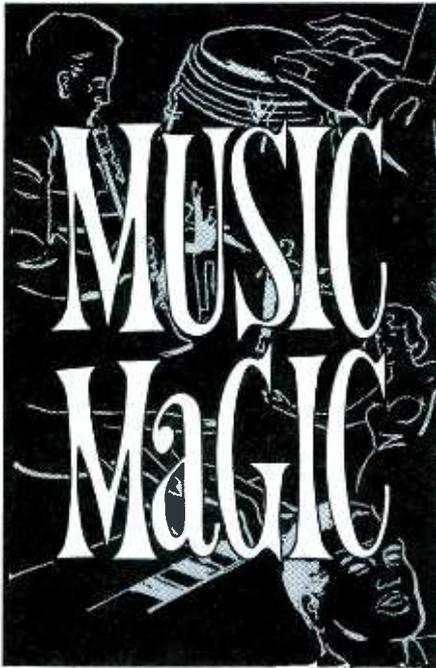

*utah*  
**Sorcerer**  
 SPEAKER SYSTEM

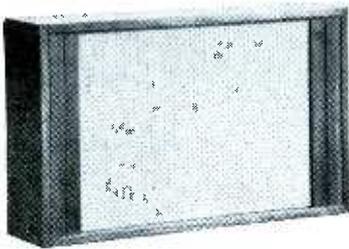


*with a flick of the wrist...*

and like *Magic*, your room fills with bewitching, beguiling sound which could only come from Utah's Sorcerer. Only the magic of Utah's electronic ingenuity produces the big, the full, distortion-less sound from such a *compact*, complete speaker cabinet.

- Styling—fits Early American through Modern decor.
- Components—Two Utah Speakers, an 8" Woofer, 5" Tweeter.
- Cabinet—Hand-rubbed, oiled walnut veneer, applied to 1/2" plywood, a standard for fine furniture.
- Location—Wall, bookshelf, floor, table-top.
- Dimensions—20" in length, 12" high, 5" deep.
- Power rating—12 watts.
- Uses—Hi-Fi or Stereo, as extension speakers for record player, radio or TV.

MODEL SH-4W—Finished Walnut Veneer

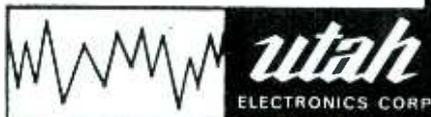

HUNTINGTON, INDIANA

mailing to people whose sets use that type, quoting a special replacement price. For the portable-TV owners, a "bring-in" deal can be arranged. Word of radio or record-player repair specials can be sent directly to owners of three-way combos. The things you can do are infinite as long as you own a good customer list.

I'll never forget one popular TV model that was built with a remote-control motor and attachments on the tuner — the only accessory not included was a simple plug-in control box. Yet, when these sets were sold, there was no mention of any remote attachments; so the people didn't know their TV's were set up for remote control! All they needed was the external attachment and hand grip. However, these were not available from dealers handling this brand.

One day, on my rounds, I ran into about 50 of these external units. I bought them for a few pennies each. Then I had the girl go through our file and address a letter to all those people who owned that model. (There were about 75 of them.) Yes, I turned a nice profit and made fifty customers happy by converting their TV's to remotes for a ridiculously low price. This doesn't happen often, but you will run into similar situations you can turn to your advantage if you have a good customer file.

#### Surveys

No matter what size your business may be, you must appraise its growth periodically. Then you can adjust your policies accordingly, to keep its growth healthy. If you don't do this, you can't stay in business for long.

With a good customer file you can tell approximately how many customers you're losing, how many you're gaining, in what areas you're losing, and in what areas you're gaining. This permits you to delve into losses and gains to take remedial action.

To illustrate this point, there's a gigantic apartment house where we have many service calls. During a periodic file-card survey, I noticed our volume there was dropping off. Since there are a thousand apartments in the building, I didn't like the idea of losing out in that spot. I went around and spoke to the

superintendent, who's a friend of mine, to find the reason for the drop off. He told me the general manager forbade him to recommend us as he had been doing. There was nothing he could do — it was policy. The remedial action was easy. I obtained a list of the tenants from an advertising company, listed them in a special file, and bombarded the tenants with a few TV-service mail specials. As it turned out, we did service work for the general manager, who also was a tenant, and he told the super it was okay to recommend us again.

#### Summary

One last little story about the customer file: I discovered that an area about twelve miles away was becoming harder and harder to serve conveniently, because of increased traffic on the roads in that area. When I first serviced there ten years ago, it was a profitable venture.

By means of my file, I counted the number of calls we received there per week; then I figured the gross income and the cost of doing business. Due to the increased traveling time, the profit margin was no longer worth the effort.

I hated to just give it up, so I dropped over there, and found a young fellow doing service in the area. I sized him up and found he was quite competent; so I asked him whether he'd like to purchase our business in his town. He was receptive, and I accepted his bid. I turned over the files for that district, and made up a mimeographed letter in which I bid farewell to our old customers and told them this excellent young serviceman would take over in our place. He's been doing well there ever since, as I knew he would.

Your customer record file is a strong limb on the body of your TV business. However, it will wither from disuse unless it is treated and used as a living thing. When kept up-to-date, it will give you a good service-call history that will help you stop customer arguments before they start; it will permit you to keep up a constant stream of mail that will keep old customers interested and spark new business; lastly, it will enable you to keep your finger on the pulse of your business so you can swim along with or against the tide. ▲

# Wake Up



A new day is dawning in electronics.

Transistors are here to stay... they are now being used everywhere; in radio, television, Hi-Fi, intercom, and in nearly all new electronic equipment...

Why put off transistor circuit servicing any longer... there's gold in them thar hills. But you must be equipped to do the job fast and efficiently. Here are the tools that you will need.



## NEW SENCORE TRANSI-MASTER

This Tester will analyze the entire circuit in minutes and test transistors in-circuit or out of circuit. Here is how you can pin point troubles step by step with the TR110.

First, check the batteries with the 0 to 12 volt meter. If the batteries are O.K., check the current drain with the 0 to 50 milliamp meter. A special probe is provided so that you do not need to break the circuit. Excessive current indicates a short; low current indicates an open stage or cracked board. All PF schematics indicate average current.

If trouble is not located by now, isolate the trouble to a specific stage by touching the output of the harmonic generator to the base of each transistor and note spot where sound from speaker (or scope where no speaker is used) stops or becomes weak. The generator becomes a sine wave generator for audio stages to help find distortion.

If trouble points to a transistor, check it in a jiffy with the exclusive in-circuit power oscillator check provided by the TR110. A special probe is also provided for this.

If the transistor checks bad in-circuit, remove it and give it an out of circuit check with the oscillator check or the more accurate DC check.

The DC check is provided for comparison reasons, experimental or engineering work and to match transistors in audio output stages. Beta (current gain) is read direct or on a good-bad scale for service work.

DEALER NET. ONLY **\$59.50**



Tests all transistors in-circuit or out-of-circuit

### Model TR110

It's a COMPLETE TRANSISTOR TESTER

- SIGNAL TRACER • VOLTMETER
- BATTERY TESTER • MILLIAMMETER



## NEW SENCORE TRANSISTOR AND DIODE CHECKER

Here is a low cost tester that has become America's favorite. The TR115 provides the same DC out of circuit checks as the TR110; leakage and current gain. Beta (circuit gain) can also be read direct or as good or bad. Opens or shorts in the transistor are spotted in a minute. The TR115 checks them all from power transistors to the small hearing aid type. Japanese equivalents are listed also. This famous tester is used by such companies as Sears Roebuck, Bell Telephone and Commonwealth Edison. New circuits enable you to make service checks without set-up charts even though charts are provided for critical checks.



Model TR115  
Dealer Net  
Wired  
**\$24.95**  
Kit.....\$15.95



## SENCORE BATTERY ELIMINATOR AND TROUBLE SHOOTER

For replacing batteries during repair.

Many servicemen say that they wouldn't service transistor circuits without this power supply. The tried and proven PS103 is a sure fire answer. It can be used to charge the nickel cadmium batteries as well. Dial the desired output from 0 to 24 volts DC and read on meter. Low ripple insures no hum or feedback. Total current drawn can also be read on the PS103 by merely flicking the function switch to milliamps. The PS103 is the only supply that will operate radios with tapped battery supplies such as Philco, Sylvania and Motorola. No other supply has a third lead.



Model PS103  
Dealer Net  
**\$24.95**

Now in stock at  
your Authorized  
Sencore Distributor



# SENCORE

ADDISON, ILLINOIS

# Transformer Tactics

by Jim Galloway

## When you can find an exact replacement—what then?

Transformer replacement can be very easy or it can be difficult. If you find that a set has a defective transformer and you can obtain an exact replacement, it is a simple matter to unsolder the leads, swap the units, and connect the new one. However, if the chassis happens to be out of date or an unfamiliar imported type, you may not always be able to locate an exact replacement.

In the case of most iron-core transformers—such as seen in Fig. 1—lack of a suitable replacement can create difficult problems indeed. Information about electrical ratings is not often marked on the defective unit; so, in addition to solving mechanical mounting problems, you must determine what operating characteristics a new transformer should have.

Sometimes, too, you will be working on a piece of equipment for which you cannot obtain part numbers; or perhaps your distributor doesn't have the correct part in stock. This latter situation is much less of a problem than not having the servicing information, since you can usually take the part number to your distributor and he will help you find a near-equivalent

transformer which will work in the equipment.

### Choosing a Replacement

Let's say you have an old radio-phonograph in the shop of such a vintage that you can't find service data for it. After picking your way through dirt accumulated over a period of years, you discover that the power transformer has given up. There are no identification numbers of any kind on the transformer and the customer is in a hurry to have the unit back. How can you find out what the proper replacement for the transformer should be?

The most logical method for attacking this problem is to make a few simple calculations which will allow you to choose a replacement with an adequate safety factor, but still not too large for convenient mounting.

Power transformers are usually given two ratings: The voltage of the secondaries and the maximum current that can be safely drawn from each. Of course, there are other considerations such as operating temperature and case insulation, but these factors are of concern only in certain special equipment.

The problem reduces to a matter of figuring out the voltage and current requirements of the set and finding a replacement that will safely meet them. One way to find the needs of a particular set is to locate service data for a piece of similar equipment. In the case of the radio-phonograph mentioned before, we could use the schematic and parts list for any radio-phonograph which used approximately the same types of tubes. Chances are good that a transformer which fits one would fit the other, even though holes might

have to be drilled in the chassis to accommodate the replacement unit.

If this method is impractical because you can't find data for a similar unit, the alternative is to figure approximately how much current and voltage is necessary to power the set. Then you can purchase a replacement on the basis of these calculations, made as follows:

1. List all the tubes in the unit and determine the operating requirements for each. A tube manual will give a lot of help, and you can also draw on your servicing experience for this information.
2. Using the "Typical Operation" data in your tube manual, find and list the plate and screen voltage for each tube. Next, note the plate and screen currents. Also write in the filament voltage and current ratings.
3. Add the plate and screen currents obtained in step 2; this will be a close approximation of the total B+ current requirements.
4. Trace the B+ line from the rectifier to see if there are any dropping resistors in series. If there are, calculate the voltage drop across them ( $E = I \times R$ ). Determine the value of I by figuring what portion of the total cur-

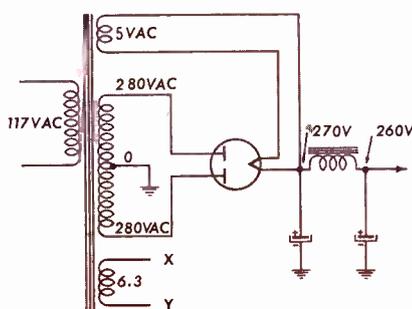


Fig. 1. Typical iron-core transformers.

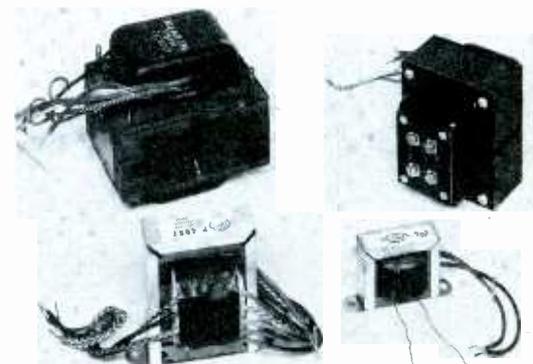


Fig. 2. DC output voltages are usually only slightly less than the rms values.

# Can you afford to guess

AT SWEEP, SYNC OR HIGH VOLTAGE TROUBLES?

WHEN IT'S SO EASY TO WALK THE TROUBLE  
RIGHT OUT OF THESE TIME CONSUMING  
CIRCUITS..... STEP BY STEP.....



SYNC. CIR. & H. SYNC. DISCRIM.	VERT. OSC.	VERT. OUTPUT	VERT. OUTPUT XFORMER	VERT. DEFLEC. YOKE
--------------------------------------	---------------	-----------------	----------------------------	--------------------------

HORIZ. OSC.	HORIZ. OUTPUT	HORIZ. FLYBACK XFORMER	2nd ANODE VOLTAGE CIRCUIT	HORIZ. DEFLEC. YOKE
----------------	------------------	------------------------------	---------------------------------	---------------------------



## NEW, IMPROVED SENCORE SWEEP CIRCUIT ANALYZER MODEL SS117

How many times do you ask, "Why do I take so long finding that sweep trouble?" How often have you wondered whether weak horizontal sync was caused by defective sync circuit, horizontal oscillator, or sync discriminator? Can you quickly isolate inadequate width or low 2nd anode voltage to the oscillator, output, flyback transformer, or yoke? How many times have you changed a good yoke by mistake?

The SS117 will pinpoint troubles like these in minutes with tried and proven signal injection, plus yoke substitution for dynamic in-circuit tests. Error proof push button testing enables you to make all tests from the top of the chassis without removal from cabinet for maximum speed and profit on every job.

Here are the checks the SS117 makes . . .

- Horizontal Oscillator: Checked by substituting 15,750 variable output universal oscillator from SS117. Signal can be injected at any spot from horizontal output grid to horizontal oscillator to determine defective component.
- Horizontal Output Stage: Checked by reliable cathode current and screen voltage checks made with adapter socket and two push buttons.
- Horizontal Output Transformer: Checked for power transfer in circuit and read as good or bad on meter.
- Horizontal Deflection Yoke: Checked by direct substitution with adjustable universal yoke on SS117.

- Vertical Oscillator: Checked by substituting 60 cycle synchronized oscillator.
- Vertical Output Transformer: By simple signal injection for full height on picture tube.
- Vertical Deflection Yoke: By signal substitution for full height on picture tube.
- Sync Stages: Checked by synchronizing triggered horizontal SS117 oscillator from any stage. If oscillator synchronizes, sync is O.K.
- 2nd Anode Voltage: A new dynamic check using simulated picture tube load. C.R.T. does not need to be operating for current tests. No interpretations—read direct from 0 to 30 KV.
- External Circuit Measurements: By applying from 0 to 1000 volts AC or DC to external meter jacks. Meter will read DC or peak-to-peak volts. 0 to 300 milliamp scale also provided for measuring horizontal fuse current.
- New features include: Large 0 to 300 microamp meter for minimum circuit loading; all-steel carrying case with full mirror in adjustable cover; two 115 volt AC outlets in cable compartment.

Size: 10¼" x 9¼" x 3½". Wt. 10 lbs.

Model SS117

Dealer Net **\$89<sup>50</sup>**

SEE YOUR AUTHORIZED SENCORE DISTRIBUTOR

# SENCORE

ADDISON, ILLINOIS



Sencore Sam says . . . How can you miss . . .

EACH PACKAGED UNIT CONTAINS:

- An Easy to Follow Instruction Book Especially Prepared and Edited by H. W. Sams.
- A complete 33 RPM, 10 inch Permanent Record on "How to Simplify Sweep Circuit Trouble Shooting."

# NEW SAMS BOOKS



## Troubleshooting with the VOM-VTVM

Robert G. Middleton describes the operation of VOM's and VTVM's; shows in detail how to use these instruments for troubleshooting TV circuits. Tells how to check and interpret voltages; gives step-by-step procedures for analyzing every type of TV circuit. Also describes measurement and analysis of both AC and DC voltages, resistance, capacitance, and RF signals. Includes measurement and analysis of transistorized circuits. 160 pages; 5 1/2 x 8 1/2". \$2.50  
Order TWV-1, only.

## Howard W. Sams PHOTOFACT Guide to TV Troubles

By Herrington and Oliphant. Causes of more than 90% of TV troubles can be isolated in minutes by following the procedures described in this book. Presents numerous actual picture screen photos showing which defective components cause the trouble. The many schematics included are accompanied by check charts showing troubles likely to be caused by various defective components. Outlines symptoms, analysis checks and where to look for trouble causes. 160 p.; 5 1/2 x 8 1/2". Order PFG-1, only... \$2.95

## Fundamentals of Magnetic Amplifiers

Barron Kemp has written a practical, easy-to-understand text for everyone working with saturable-core devices, such as those used in missiles, computers, industrial equipment and lab instruments. Describes basic reactors and reactor core materials; covers theory and operation of magnetic amplifier devices. Using a "building-block" approach, succeeding chapters provide a wealth of detail on design, applications and testing. 128 p.; 5 1/2 x 8 1/2". Order FMA-1, only... \$2.95

## ABC's of Radiotelephony

By Leo G. Sands. Here are all the basic principles of wireless communication, clearly explaining how radio signals are developed and transmitted and how they are received and converted into intelligible sounds. Block diagrams and basic circuit descriptions explain operation of both FM and AM transmitters and receivers. Chapters cover basic principles, carrier signal generation, carrier modulation, carrier radiation, carrier reception and demodulation, types of radiotelephone systems. 96 pages; 5 1/2 x 8 1/2". Order ABT-1, only... \$1.95



## Servicing Transistorized Two-Way Radio

This is the first complete volume describing servicing techniques for the modern transistorized 2-way designs used by major manufacturers, such as GE, Motorola, RCA and others. Chapters cover: Transistors; The Transistorized 2-Way Receiver; Troubleshooting and Receiver Alignment;

Transistorized Mobile Power Supplies; The Transistorized Mobile Transmitter; Tone-Coded Squelch Systems. 128 p.; 5 1/2 x 8 1/2". TRT-1, only \$2.95



## TV Diagnosis and Repair

By the Editors of PF Reporter. Practical servicing procedures and cures for typical TV circuit troubles, adapted from PF Reporter articles. Covers important tube problems (repeat burn-outs, unusual tube troubles, and tube changing). Special sections on sync and horizontal sweep problems (pie-

crusting, Christmas-treeing, yoke and flyback troubles). Also covers source-voltage and audio troubles. 96 p.; 5 1/2 x 8 1/2". Order TDR-1, only. \$1.50

**JUST OUT—TUBE LOCATION GUIDE, VOL. 12**  
Latest edition covering 1959 through 1961 receivers. Shows tube location and series-filament diagrams. 96 pages, 5 1/2 x 8 1/2". Order TGL-12, only... \$1.25

## HOWARD W. SAMS & CO., INC.

Order from your Sams Distributor today, or mail to Howard W. Sams & Co., Inc., Dept. J-32 4300 W. 62nd St., Indianapolis 6, Ind.

Send me the following books:

TWV-1  FMA-1  TRT-1  TGL-12  
 PFG-1  ABT-1  TDR-1

\$.....enclosed.  Send Free Book List

Name.....

Address.....

City.....Zone.....State.....

IN CANADA: A. C. Simmonds & Sons, Ltd., Toronto 7

rent (step 3) flows through the resistor in question.

5. Use the highest typical plate (or screen) voltage in the set as a standard, and add to it whatever voltage drops were found in step 4. The result should be the voltage required for B+ in this set. (If the equipment contains an audio-output tube, you can check your figures by comparing the value you obtained with the voltage expected at the screen of this tube; usually, the audio-output screen grid is run at full B+ voltage.)

6. Add all the filament currents to obtain the total filament current required from the transformer.

Now, you can take the data you have accumulated and turn it into some useful transformer ratings. Transformer voltage ratings are always in rms values; when this voltage is rectified and filtered, the resulting DC will be slightly more than the rms value of the secondary AC voltage. Therefore, if the radio-phonograph in our example were found to require approximately 270 volts of B+, a power transformer with a secondary rating of 250-0-250 volts rms would give approximately the required value of B+. In the secondary, it is best to allow about a 50% safety margin. If, from your calculations, you decide the B+ current will be 70 ma, choose a transformer that will supply at least 100 ma. Fig. 2 shows some of the input-output relationships in a typical transformer power supply.

Filament windings should also be protected by a safety factor. If the total drain on the filament supply is calculated to be 2 amps, at least

Typical Transformer Ratings		
Type of Equip.	B+ Current	B+ Voltage
10 watt Hi-Fi Amp	100 ma	260
TV Set	270 ma	260
25 watt Hi-Fi Amp	200 ma	350
Tape Recorder	100 ma	250
AM-FM Receiver	140 ma	115
Two-Way Base Station	250 ma	200
(two windings)	250 ma	200

Note: Each rating includes a safety factor.

Fig. 3. Chart showing approximate B+ voltage and current requirements.

a 2.5-amp filament winding should be used.

The procedure outlined above may seem complicated at first, but with a little practice you will be able to estimate the power requirements for a particular piece of equipment with satisfactory accuracy. In order to save you time, we have included a chart (Fig. 3) listing typical current and voltage requirements for various types of equipment you might be called on to service. Bear in mind that individual items differ, and this chart should be used only as a guide and not as an absolute authority.

## Output Transformers

The procedure for choosing replacements for audio-output transformers is no more difficult than for power transformers. The steps are:

1. Note the type of tube employed in the output stage.
2. Locate this tube in the tube manual and find its plate current and impedance. Remember, these characteristics vary according to the class of operation, so be sure to find the correct figures. Most single-ended output stages are operated as class A, while push-pull circuits are AB1, AB2, or class B — the tube manual tells which.



# PROFITS IN BACKGROUND MUSIC

Used in HOTELS, MOTELS, BANKS, OFFICES, RESTAURANTS AND ANY OTHER BUSINESS ESTABLISHMENTS.

Become a distributor in your locality for the newest field of background music on tape in cartridges.

Build up an INCOME selling the instrument and leasing continuous play music

Send for circular and catalog of the largest and finest library of Programmed Music.

**CINE-SONIC SOUND, INC.**  
485 EIGHTH AVENUE, NEW YORK 1, N. Y.



15,000,000 MULTIPLE-SET OWNERS NEED

# TRANSCEPTOR®

THE HOUSEHOLD SET COUPLER

ANYONE CAN INSTALL IN SECONDS



- improves reception for additional TV, color TV, FM, stereo FM
- provides most efficient signal delivery
- automatically matches impedance
- proved in more than 50,000 installations
- snaps on without tools
- eliminates extra antennas, rabbit ears
- packaged and designed for consumer appeal
- more than 2 million new customers annually

Foolproof, simple, rugged TRANSCEPTOR was designed especially for the fifteen million multiple-set owners in this country. Now, with easy-to-install TRANSCEPTOR, they can run any combination of TV and FM sets — two or more, one at a time or all at once — *off one antenna* without amplification in normal signal areas. And, because TRANSCEPTOR uses electro-magnetic pick-up instead of resistance splitting of the signal, the line is not cut, there is minimum signal loss, and better set-to-set isolation.

**Result: More customer satisfaction. More sales. More profits.**

\*\*\* INDIVIDUALLY PACKAGED ON SELF-MERCHANDISING COUNTER DISPLAY CARDS. AVAILABLE FROM YOUR LOCAL DISTRIBUTOR

**\$ 2.98**  
RETAIL



**AEROGAP** CORPORATION  
1680 VINE STREET  
LOS ANGELES 28, CALIF.

**INSTALL  
IN  
SECONDS**



1. slide apart



2. slide on line



3. connect to set



## **STEP ONE FOR COLOR TV SERVICING: THE NEW PRECISION E-450 COLOR BAR/WHITE DOT GENERATOR.**

Simple to use, crystal controlled and voltage regulated, the PRECISION E-450 is a must for the busy serviceman. It combines the facilities to test and adjust the phasing, matrixing, linearity and convergence circuits in all color receivers. Three front panel controls and one simple antenna cable connection to the receiver under test afford a new high in ease of operation. The PRECISION E-450 is furnished complete with output cable and technical manual for only \$189.95 net. For complete details on this and other models, see your jobber or write today.

**Patterns:** Color bars, White dots, Crosshatch, V bars, H bars. **RF Output and Sound Carrier:** Available on channel 3 or 4; field adjustable. RF output 50 mv max. Sound 10% of picture carrier. **Simple 300-Ohm Connection** to antenna input terminals of receiver. **No External Sync.** Signals required to lock in test patterns. **Master Voltage-Regulated, Crystal-Controlled Oscillator** operating on 189 kc assures stability of displayed patterns. **Easier Convergence Set-Ups:** Separate vertical and horizontal bar patterns. **Optimum Convergence Adjustments:** Extremely fine, well-defined dot pattern. **Color Bars:** A reference test signal, precisely controlled, produces 10 equally spaced color bars across face of TV receiver under test. Included are the color bars corresponding to R-Y, G-Y, E-Y, I and Q signals.

PRECISION APPARATUS CO., INC., GLENDALE 27, NEW YORK

**PRECISION** SUBSIDIARY OF  
PRECISION  
All Precision Test Equipment is Guaranteed For One Full Year

## STEP TWO. VISUAL ALIGNMENT AND WAVEFORM ANALYSIS.



ES-150 Wide Band Oscilloscope with DC to 5 mc Response. VERTICAL CHANNEL: 3-stage push-pull, balanced DC amplifier. Sensitivity: DC: 70 mv/in.; AC: 25 mv RMS/in. Frequency Response: DC: within 3 db to 4.5 mc, within 5 db at 5 mc; AC: within 3 db from 1 cps to 4.5 mc, within 5 db at 5 mc. Rise Time: better than .08  $\mu$ s. Input Impedance: 1.5 megohms shunted by 23 mmfd. 4-Step Frequency-Compensated Vertical Input Attenuator; Frequency compensated. Vertical

Polarity Reversal Switch: Simplifies pattern reversal. HORIZONTAL CHANNEL: Push-pull output amplifier; sensitivity: 0.6 v RMS/in. Frequency Response: Within 3 db from 1 cps to 400 kc. Input Impedance: 5 megohms shunted by 23 mmfd. Cathode-Follower Horizontal Input Circuit: Linear time base 10 cps. to 100 kc. Provisions for external capacitor sweep to 1 cps. Net Price: \$149.95. Also available in kit form as PACO S-55: \$95.95.



## STEP THREE. VISUAL SWEEP RESPONSE WITH ES-150.

E-410 Sweep Generator And Marker Adder. Frequency Coverage: 3 mc to 1080 mc in 6 bands (to 216 mc on fundamental). Continuously Variable Sweep Width: 0-3 mc on Band A to 0-30 mc on Band D. Band E varies from 0-16 mc. Output Impedance: 50 ohms terminated. Internal Blanking: Eliminates return trace. Automatic Gain Control: Regulates voltage amplitude on any band. Marker Adder: Superimposes marker "pips" on response curve; variable in size and width. Internal Phasing Control: Corrects phase shift between RF and horizontal scope outputs. Fixed Frequency Markers: Crystal circuit for accurate marking (one 4.5 mc crystal supplied). External Marker Input Connector: Permits use of external marker such as E-200C to provide variable marker "pips." Separate Line Filter: Minimum line cord radiation. Continuously Variable Attenuators: Control sweep width and vertical scope pattern. Net Price: \$159.95. Also available in kit form as PACO G-32: \$85.95.



## STEP FOUR. ALIGNMENT AND VARIABLE MARKER.

E-200C Multi-Band RF Signal and Marking Generator. Frequency Range: 88 kc to 440 mc (to 110 mc on fundamental). Direct reading in 10 bands up to 440 mc; within 1% accuracy on all bands. 0-1000 Point Vernier Dial: Ideal for hand calibration and frequency spotting. Dual-Shielded RF Attenuators. Smooth, stepless RF control. Four Types of Signals: Unmodulated RF; modulated RF (400 cps); externally modulated RF; 400 cps output. Direct Reading Variable Modulation Control 0-100%: Triples signal utility as against obsolete fixed or stepped modulation of only 30% or 40%. Built-In AVC-AGC Bias Substitution: Overcomes alignment troubles arising from varying receiver AVC and AGC. Net Price: \$109.95.

3. Determine the output impedance from the type of speaker used. If you are unable to find this information, use a transformer with a "universal" secondary and choose a tap that results in the greatest measurable output power.

4. From the data obtained in step 2, your distributor should be able to help you choose a replacement that will work in the circuit.

Vertical-output transformer replacements are seldom as difficult to locate. However, when the need arises, similar principles will help you choose a suitable unit. The information which will help you is the tube type, the output configuration (autoformer, isolated secondary, etc.), and the yoke characteristics. Transformer catalogs are usually very complete in the matter of describing the operating conditions for the replacement units they list.

### Replacement Hints

Normal replacement of transformers gives no trouble; however, there are instances when problems arise. Here are a few tips that may help you when you have to troubleshoot and replace transformers.

If ohmmeter checks and visual inspections have not shown why a transformer failed, and you have to check the circuit under operating conditions, a fuse should be employed to protect the new transformer. Most sets have power-line fuses, but if the set you're servicing hasn't, it is a good practice to install one. The owner will seldom object to the cost when it is compared to the repair bill for transformer replacement. Whenever you install a fuse in the primary circuit, place it between the off-on switch and the power line, so all portions of the circuit are protected.

Be particularly careful when installing a power transformer—other than an exact replacement—on hi-fi equipment. If the new unit is not adequately shielded or properly placed, it could cause objectionable hum due to its magnetic field interacting with some other transformer. Hook it up without bolting it to the chassis and, with the power on, try orienting the transformer to a position that results in the least hum.

Next, check to see that the

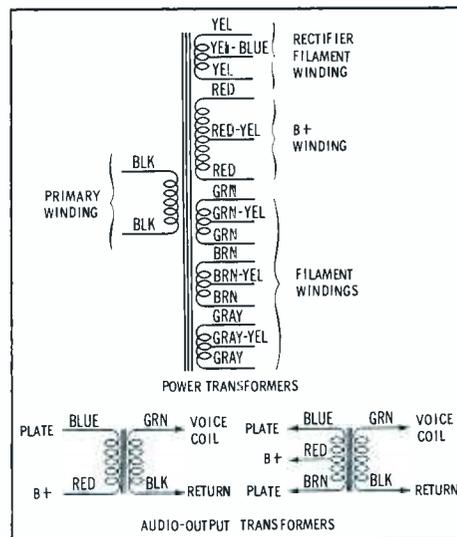


Fig. 4. EIA standard color codes for power and audio-output transformers.


equipment operates properly. If it does, let it cook for a while, placing your hand on the transformer occasionally to see if it is getting too hot. After 15 minutes of operation, it should be quite warm to the touch, but not hot enough to cause a burn.

Fig. 4 shows the EIA transformer color code. If you should happen to lose the wiring data which comes with a transformer, this chart will help you identify the leads.
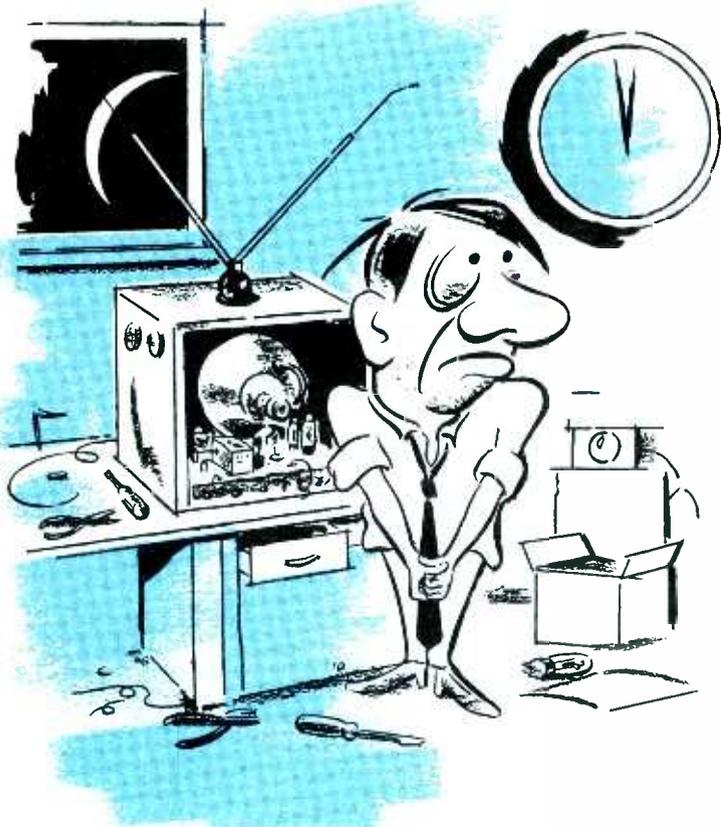
### Summary

Most transformer replacements are extremely simple. Occasionally, however, you will have to call on your ingenuity to either guess or calculate what characteristics a replacement unit should have. You don't have to shoot in the dark, though, for the aids in this article will help you choose the correct one. ▲





# and they say SERVICING is **FUN?**

"It works better than it ever has!"

These words are almost as much music to the ears of a TV technician as the words, "I've come to pay my bill."

Like other servicemen, I get a great deal of satisfaction from working over some rundown set, finding the causes of its aches and pains, and curing them. It's a real thrill to attempt what appears to be a difficult job and, after studying the symptoms, come up with a diagnosis of the trouble. Then, after taking a few scope checks to localize the trouble and a few voltage or resistance measurements to pin down the defective part, I enjoy verifying the diagnosis and effecting the proper cure.

I replace the defective parts, touch up the alignment, and finish with a set so perfect the waveforms on the service data seem distorted by comparison. The picture looks like a photograph and the audio section is so good that both the deep tones of a foghorn and the high-pitched hiss of a disgruntled studio audience come through perfectly. No king could feel better than a serviceman who has just turned out such a job!

Unfortunately, there are days (about six a week) when my jobs turn out something less than perfect—if I get anything done at all. Take yesterday, for instance, or the day before. I received a call from a new

customer who, like my other customers, wanted his set repaired immediately, or even sooner. Quickly winding up the job I was working on, I loaded my caddy and testers in the truck and drove to his home.

Inside, he led the way to the living room where, partly hidden behind a large chair, the TV set stood—nearly buried under an odd-shaped TV lamp, several photos, and a pile of magazines. Knowing from experience that quizzing a customer about the symptoms often gives valuable clues to the cause of the trouble, I tried to do so immediately. After we had discussed war experiences and the world situation for half an hour, he said the first trouble that had shown up was a vertical failure. "There was just a bright line across the middle of it."

He had played the set that way for a few days, just listening to it. Then the sound failed, and he spent an evening or two just watching the little line and hoping something would happen. It did—the bright line went out. As a last resort, he finally called me.

From these answers to my probing questions I surmised the set now had three trouble spots: the vertical stages, the audio section and a high-voltage failure. Taking the last one first, I found I was wrong on one count—the high voltage was fine, but the picture-tube filament had


burned out. The owner was quite shaken when I informed him he needed a new CRT, but when I assured him it wouldn't cost much more to fix the set than to buy a new one, he consented to let me do the job.

Back at the shop, I was eager to get started on the set since it looked like money in the cash register. I shoveled out the dirt (plus two bobby pins, a cheap ball-point pen, and a nickel) and pulled the chassis. Then I set it up on the bench, using my small test CRT in place of the bad picture tube. I turned it on and, after a few minutes, the vertical output tube started showing a purple glow. "Either a gassy tube or too much current—shorted maybe," I mused. I shut the set off, grabbed the tube to pull it, and heard something sizzle—the skin on my fingers. As I fished in the tool tray for a tube puller, I wondered if I'd ever remember that tubes get hot so quickly.

I replaced the vertical output tube, and another in the sound section. Turning on the set again, I got a roar of sound, but still only a thin bright line. There was still trouble in the vertical section, so I fired up the scope; did a good job, too, for it started smoking! Having no alternative but to fix it first, I hauled it out on the bench and started taking it out of the case.

FROM THE LEADING NAME IN WORLD-WIDE COMMUNICATIONS

**BUILD  
PROFITS  
WITH**

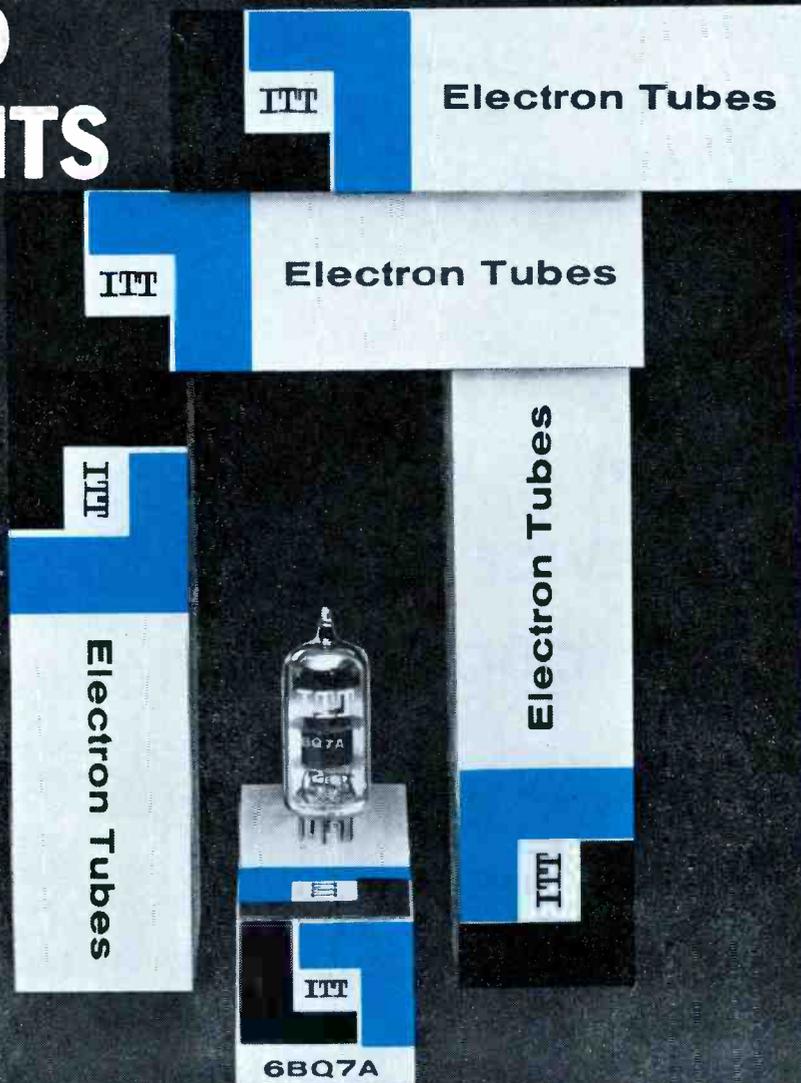

**QUALITY PRODUCTS**

Let's face it — you're the professional. Your customers rely on your judgement — if they don't, you're just working, not **building**. When your customers see you use the familiar and accepted ITT-labeled tube, they know you're a friend. **You** know it's a profitable friendship, and that's the kind that lasts. For over 25 years ITT has been advancing the state of the art in tube design and manufacture. This traditional quality is the stuff your reputation is made of . . . use it well. We can help you with a

confidence-builder, "**the ITT TUBE STORY**", pamphlet. Give one to your customers — they may give one to you (a customer, that is).



The next time you pick up ITT TUBES, ask your distributor to tell you the details of our Partnership in Prestige and Progress program — you can participate in this Dealer Award Plan.



**DISTRIBUTOR PRODUCTS DIVISION**

P. O. BOX 99, LODI, NEW JERSEY

TEL. HUBBARD 9-7800 • CABLE DISTRIBUTOR • TWX HKK 1586

INTERNATIONAL TELEPHONE AND TELEGRAPH CORPORATION

September, 1962/PF REPORTER 51

# A SALUTE TO



## FROM A VETERAN SERVICE MAN, WE QUOTE.....

'YOUR NEW CATALOG AND REPLACEMENT GUIDE, FORM 820, IS TERRIFIC. YOUR LISTING OF MANUFACTURERS' PART NUMBERS FOR CB, PA AND HI-FI EQUIPMENT AS WELL AS AUTO RADIOS, HOME RADIOS, TAPE RECORDERS AND RECORD CHANGERS HAS LONG BEEN NEEDED. KEEP UP THE GOOD WORK.'



At that point, a teen-age boy came in and set a paper sack on the counter, so I walked over.

"Do you think you can fix this?" he asked, hopefully. He reached into the sack and carefully pulled out the tangled wreckage of a transistor radio.

"I dropped it," he explained.

"From an airplane or a space ship?" I couldn't help asking.

My remark didn't get a laugh, but he did manage a sickly grin as I started pawing over the parts. The case was broken into several pieces, the antenna was damaged and the printed board was cracked in several places. I didn't know quite what to say, since most youngsters don't have a lot of money. (I often wonder if they ever will, considering the way they can swiftly make junk out of brand-new products.)

I finally told him I could probably patch it up at a reasonable cost but couldn't make it like new for much less than a new one would cost. He went for the patch job.

After he left, I turned back to my repair job on the TV, then remembered the scope had to be fixed. I upended it and a well-cooked resistor glared out at me like a black eye. I followed one lead to a tube-socket terminal; when I tested the tube, I found it shorted.

Just then the phone rang. As I lifted the receiver, the door opened and two ladies walked in. I nodded a greeting to them, then announced into the phone, "Cheerful Charlie's TV Repair Shop."

A girl's voice asked, "Do you fix TV's?"

One of the ladies in the shop said, "I want a tube for my radio."

"I try to," I answered into the phone.

"Have you a number?" I asked the woman.

"Fairview 2-3254," said the voice on the phone. "But I'm not home now, I'm at a friend's house. Her number is —"

"I'm sorry," I interrupted, "I was talking to another person." The phone clicked, and the dial tone came on.

"I just wanted one tube," answered the lady in the shop; "this one wouldn't light up." She produced a tube, which I checked, and

Again **B&K** Makes Servicing  
Easier... More Profitable!

NEW!  
**3-IN-1**  
DYNA-TESTER



Model 625

- 1** TUBE TESTER      **2** VOM      **3** CRT

Unique new B&K design now simplifies servicing in the home or in the shop. Combines Tube Tester, Volt-Ohm-Milliammeter, and Cathode Rejuvenator Tester in one compact, professional quality instrument—at low cost!

**1** **TUBE TESTER SECTION** is fast and accurate. Tests the *newest* tube types as well as all of the *old* commonly used tubes in TV and radio sets. Tests the Nuvisors and Novars, the new 10-pin tubes and 12-pin Compactrons. Tests voltage regulators, thyratrons, auto radio hybrid tubes, European hi-fi tubes, and most industrial types. Checks for *all* shorts, grid emission, leakage and gas. Provides *adjustable* grid emission check with exceptional sensitivity to over 100 megohms. *Checks each section* of multi-section tubes separately. Checks tube quality and capability of cathode emission under current loads simulating actual operating conditions.

**2** **VOM SECTION** provides the 7 most-used ranges for convenient TV testing:  
3 DC Ranges: 0-10, 100, 1000 volts  
3 AC Ranges: 0-10, 100, 1000 volts  
1 Resistance Range: 3 k center scale

**3** **CRT SECTION** spots picture tube trouble and corrects it in a few minutes right in the home, without removing tube from set. Tests and rejuvenates picture tubes at correct filament voltage from 1 to 50 volts. Checks for leakage, shorts, and emission. Removes inter-element shorts and leakage. Restores emission and brightness. (Checks and repairs color picture tubes with B&K Accessory C40 Adapter.)

Model 625 Dyna-Tester complete in handsome, lightweight, leatherette-covered carry-case. Size: 11 3/4" x 15" x 4 1/2". Net, \$139<sup>95</sup>

See your B&K Distributor, or Write for Catalog AP20-R

Time-Saving, Money-Making Instruments Used by Professional Servicemen Everywhere



Model 960 Transistor Radio Analyst



Model 360 V O Matic Automatic VOM



Model 375 Dynamatic Automatic VTVM



Model 1076 Television Analyst



Model 440 CRT Rejuvenator Tester

See Your B&K Distributor  
or Write for Catalog AP20-R




**B & K MANUFACTURING CO.**

Division of DYNASCAN CORPORATION

1801 W. BELLE PLAINE AVE. • CHICAGO 13, ILL.  
Canada: Atlas Radio Corp., 50 Wingold, Toronto 19, Ont.  
Export: Empire Exporters, 277 Broadway, New York 7, U.S.A.

# Heat absorbing

## "THIRD HAND"

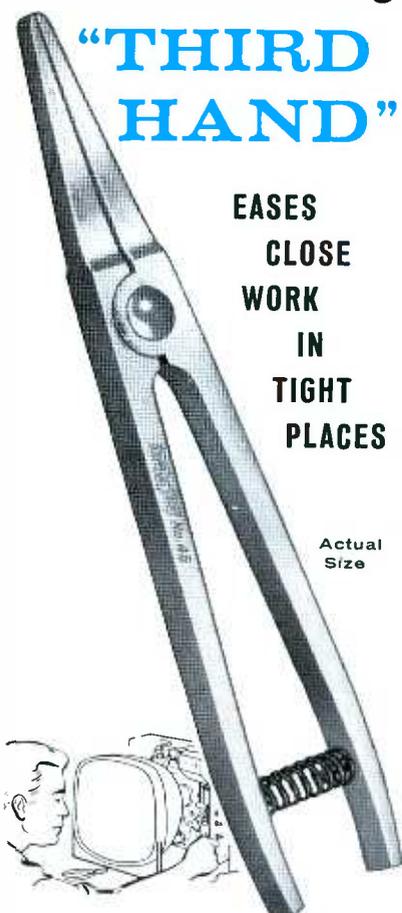

EASES  
CLOSE  
WORK  
IN  
TIGHT  
PLACES

Actual  
Size

SELF-GRIPPING

**CHAN NEL LOCK**

No. 46

**HEATSORB CLAMP**

(HEAT SINK)

A specially designed "heat sink" that prevents heat damage to electronic components during soldering operations. Also serves as handy, self-gripping "third hand" that holds and retrieves small parts in close work. Precision-made of light weight aluminum . . . easy to handle . . . cannot rust . . . Best of all, it's reasonably priced. *Be sure it's a genuine Channel-lock. Look for the trademark on the handle. Write for catalog showing complete line of pliers. Made Only By Champion DeArment Tool Company, Meadville, Pennsylvania.*

—wonder of wonders—found to be bad. I sold her a new one, then turned to the other lady who had been waiting patiently.

She showed me a transistor radio from which a small piece near a corner of the case had been chipped.

"Our cat knocked it off the table and made this hole in it," she explained. "After that, it got weaker and weaker until we could just barely hear it. My husband read someplace that the electrons in transistors go through holes and he thinks they've all leaked out of our radio. Can you do anything about that?"

I explained that transistors were only a part of the radio. Also, that they were made so the electrons could go only where they were supposed to. Then I put in a new battery, which restored the radio to life, and the lady departed, happy.

I decided to check the scope more thoroughly while I had it apart, and was busily engaged in this task when the phone rang. The woman's voice sounded familiar. When she asked if I was coming home for supper, I realized it was my wife. I also discovered it was past closing time—the day was done. Now I could go home and, after a satisfying meal, relax and enjoy myself—for about half an hour. I still had that TV on my bench; it wasn't fixed and more would come in tomorrow, so back to the shop I went for an evening session.

As most servicemen (particularly those with small shops) have found out, evenings are the only times one can work without interruption. Therefore, I was not-too-pleasantly surprised to find a man standing at my shop door with a portable television set in his hand.

He greeted me with, "Figured if you didn't show up pretty soon, I'd come on up to your house."

In the course of my business, I always present a smiling and cheerful face to my customers—that is, until closing time. I gave this one the sour look of a man who is not at all pleased. It didn't seem to affect him, so I unlocked the door and let him in.

His set was a series-string rig, and dead. Since I have found it quicker to test the tubes in these sets than to trace with an ohmmeter, I started on them. The job paid off; I found one tube burned out and another shorted. Two tubes restored the set to working order and, evidently anxious to spend the rest of the evening watching it, my customer paid up and hurried out. Locking the door and pulling the blinds, I sealed myself in for the evening.

Once more I turned to the TV on the bench. The bright line was still there. I turned the brightness down and studied it while I got my thinking back on the track. Then I remembered I hadn't yet put the scope back together. Muttering under my breath, I left the TV set long enough to reassemble the scope, without bothering to "check it more thoroughly."

I turned it on, and it seemed okay; so, for the umpteenth time, I fixed my attention on the TV set. I made a few scope checks which showed me that the vertical section wasn't working. This revelation didn't raise my eyebrows any; I'd figured that out already.

Using a low-capacity probe to keep from upsetting the circuit, I touched one scope lead to the grid of the vertical output tube. Getting

# TV TUNERS \* REBUILT OR EXCHANGED

ALL TYPES

**\$9.95** Including all parts and labor  
(except broken wafers—billed at cost)

- Normally shipped same day received
- 90 day full guarantee
- U/V combinations \$17.95

FREE—If Mailing carton sent to you on request

Phone REpublic 3-9189

## L. A. TUNER EXCHANGE

4611 West Jefferson Blvd.  
Los Angeles 16, California

Look for these signs at your participating Distributor

**YOU GET**  
**S&H**  
**GREEN STAMPS**  
**WHEN YOU**  
**BUY**  
**SYLVANIA**  
**RECEIVING**  
**TUBES**

**HUNDREDS OF GIFTS FOR YOU AND YOUR FAMILY WHEN YOU BUY SYLVANIA RECEIVING TUBES**

**FOR THE S&H CATALOG BUY SYLVANIA RECEIVING TUBES**

**SYLVANIA ELECTRONIC TUBE**

Get in on

## Sylvania's big, new Service 'n Save Stamp Plan

S&H Green Stamps add up in a hurry when you buy Sylvania tubes. So does customer good will when you stay with Sylvania quality.

That's why we say you can profit and save at the same time through the many Sylvania distributors offering S&H Green Stamps with Sylvania Receiving Tubes.

Select gifts from a big, new 144-page S&H Catalogue. Ask your Distributor for a copy.

**SYLVANIA**  
SUBSIDIARY OF  
**GENERAL TELEPHONE & ELECTRONICS**



# MAKE **COLOR** TV SERVICING

EASY AND PROFITABLE!

MODEL  
CA-378



KINECOLOR CIRCUIT ANALYZER

**\$19<sup>95</sup>** DLR. NET

... INSTANT HOOK-UP FOR ANALYZING, TESTING AND ADJUSTING **COLOR** CRT'S AND ASSOCIATED CIRCUITRY UNDER ACTUAL OPERATING CONDITIONS . . . WITHOUT CUTTING OR SOLDERING LEADS!

★ **CA-378 makes it easy to:**

- Adjust Purity
- Adjust Convergence
- Adjust Gray Scale and Tracking
- Measure Current
- Test Voltage
- Observe Signal Waveforms
- Connect All Test Equipment by Using Pin Jacks
- Use with Complete and Detailed Procedure Booklet

WRITE FOR LITERATURE TODAY!




**ANTRONIC CORPORATION**

2712 W. MONTROSE / CHICAGO 18 / ILLINOIS

DESIGNERS AND MANUFACTURERS OF ELECTRONIC COMPONENTS
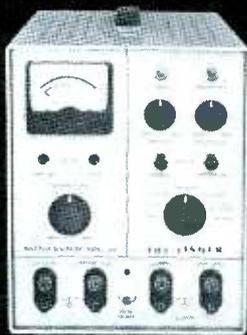
## Who says Multiplex servicing is complex? All you need besides your 'scope is this!



The Fisher Model 300 all-in-one Multiplex Generator with built-in FM Signal Generator.

Only Fisher could have designed this unique instrument—because only Fisher has the engineering depth in FM Stereo Multiplex tuners and receivers to create the ideal test equipment for servicing them. The future of high-fidelity radio unquestionably belongs to FM Stereo and the Model 300 is the instrument for the service technician in search of new business. It is compact, fully portable and completely self-contained. It has its own built-in FM signal generator. In addition to a composite MPX signal, it also generates low-distortion, stable audio signals. Thus it requires no companion instrument other than an oscilloscope for professional alignment of Multiplex equipment. Best of all, **THE FISHER** it costs only \$495.

USE THIS COUPON FOR DETAILED INFORMATION

FISHER RADIO CORPORATION

21-24 44th Drive, Long Island City 1, N. Y.

Please send me complete data and technical specifications on the Fisher Model 300.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

0917

no indication on the scope face, I decided the first stage of the multi-vibrator probably wasn't "vibrating."

I mentally listed the things that might keep it from operating, such as a bad tube (or a tube left out of the socket), little or no voltage (due to trouble on the B+ line), an open coupling capacitor (or one that had been cut out for checking and not resoldered), cold solder joints, solder slopped all over the socket terminals, or right wires connected to wrong terminals (or vice versa).

Since I hadn't started testing parts yet, I could rule out any mistakes I might have made, so I decided to take a few voltage readings. The plate voltage was higher than normal and the grid bias was next to nothing. Since this stage used plate feedback from the output tube, I checked components in the feedback loop and found an open capacitor. A new one brought the stage to life and a full picture to the face of the CRT.

I breathed a short sigh of relief; now all I had to do was install a new picture tube, put the set back together, clean the safety glass, and polish the cabinet. With a little luck I could get home early! . . . I left the shop at midnight.

The next day, as I rang the doorbell of my new customer's home, I could visualize his delight at seeing his set in such good condition. He helped me carry it in, and we quickly set it up and turned it on. My customer studied it thoughtfully for a few minutes, and then said, "Works pretty good, but the people look funny. Their legs are longer than usual and their bodies aren't tall enough. Before the set went bad, the actors' legs were short and their heads were long. Somehow, you've changed them."


I gave him a short explanation about vertical height and linearity controls and how they were used. I also told him I had adjusted his set for equal linearity, top and bottom, but he was still dubious. I asked him if the chorus girls had short legs and long heads at any musical show he had ever seen. That did it. "Gosh, no!" he exclaimed, looking at his TV with new understanding. "Yes, I guess it looks okay after all. I'll come over and pay the bill, in a week or so. . . ."
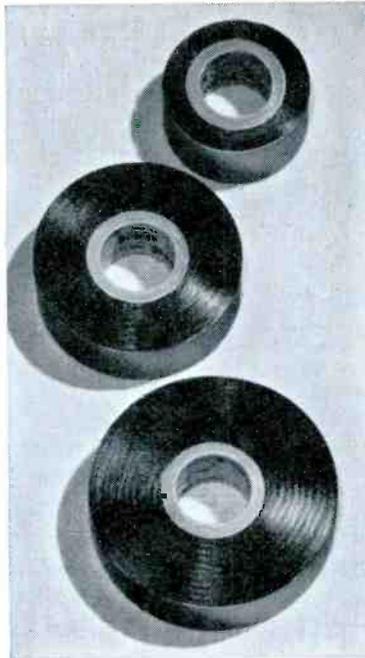
# COM-PAK

PACKAGES · ASSORTMENTS  
 PRICES: New tape buying  
 convenience from **3M** COMPANY!




**new** COM-PAK  
 QUANTITIES  
 Ten rolls to a carton. Ten  
 cartons to a case.  
 Buy the new convenient, economical, 100-roll case.



**new** COM-PAK  
 ASSORTMENTS  
 Job-rated roll-sizes:  
 66-foot... 20-foot...  
 New 44-foot. Makes  
 case-buying easier.



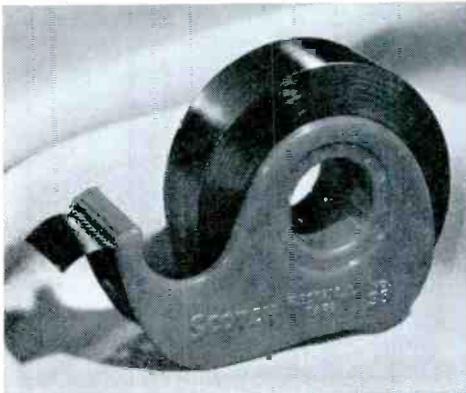**new** LOW  
 PRICES  
 Highest quality at new  
 low prices. Buy the 100-  
 roll case for fullest value, greatest savings.



**new** COM-PAK  
 DISPENSERS  
 FREE Taping Dispensers.  
 Mounted on 44-foot and 66-  
 foot rolls of No. 33 Tape.  
 Get a case, specify No. 33 D for Dispenser Pack.



**new** COM-PAK SINGLE  
 ROLL PACKS  
 Easy to identify...  
 say, "You're using the  
 best." Each roll  
 "protectively packed" in 100-roll cases.



**same** HIGH  
 QUALITY  
 Consistent perform-  
 ance. Right balance of  
 needed properties.  
 Get a whole case of electrical tape quality.

Nobody can give you tape satisfaction like **Scotch**<sup>®</sup>  
 BRAND

**3M** MINNESOTA MINING & MANUFACTURING CO. 2501 HUDSON ROAD, ST. PAUL 19, MINN.

"SCOTCH" AND THE PLAID DESIGN ARE REGISTERED TRADEMARKS OF 3M CO., ST. PAUL 19, MINN.

# SERVICING

## tone-coded

# SQUELCH

In the early days of radiocommunications, two-way radio users had relative privacy. When a frequency was assigned, little thought was given to sharing the channel, for there generally was no need to do so. In fact, a person could just pick up his microphone and transmit without worry of interfering with any other radio system.

However, as more commercial two-way radio stations were placed on the air, it became necessary for several systems to share an individual channel. Needless to say, this was quite annoying—all stations were forced to listen to the chatter from other stations on the channel, and when one was on the air the others could not transmit. The Federal Communications Commission (FCC) tried to help by decreasing the width of each channel, making room for more stations in the same frequency space. However, this solution was only temporary; an ever-increasing number of new users intensified the old problem, until today there are many channels on which

more than one licensed station must operate.

### The Push For Privacy

Naturally, many stations in the business services don't desire to be bothered by "chatter" from stations with which they share a channel, so they have sought a means by which they might hear only those messages intended for themselves—and no others. Commercial two-way-radio manufacturers have met this need with devices known variously as *Quiet Channel*, *Quiet Line*, *Private Line*, and *Channel Guard*. Since these all achieve the same purpose by essentially the same method, we can accurately describe them all as *tone-coded squelch systems*.

### How It Works

In a tone-coded squelch system, the receiver audio stages are blocked, or "squelched," much the same as with a carrier-squelch system (see "The Imperfect Squelch" in the June, 1962 PF REPORTER). The transmitter (Fig. 1) applies a low-frequency audio tone to the carrier during modulation. In the receiver (Fig. 2), the tone is taken from the discriminator output, amplified, and fed to a reed relay which opens the squelch circuit of the receiver so the message can be heard. If the receiver picks up a signal which *doesn't* contain this specific audio tone, the audio stays squelched, and the message isn't heard.

In order to understand more clearly, suppose that on a partic-

ular channel (say 155.25 mc) there are three systems operating in a single area—each system having one base and several mobiles. The stations whose receivers aren't tone-actuated will have to listen to messages not only from their own units, but also from those of both their "neighbors." However, if one of the systems has tone-coded facilities, the only messages received by that system will be its own. If all three are tone-equipped, each can operate in relative privacy.

### A Transistorized Unit

In keeping with today's trend towards use of transistorized circuits, we will first analyze a typical transistorized system. All systems use an audio tone, and except for their manner of generating the tone at the transmitter and utilizing it at the receiver, the systems are basically the same. For example, if the tones are the same, a *Quiet Channel* transmitter can actuate a *Private Line* receiver (or vice versa).

Since the purpose of the continuous audio tone is to operate the squelch circuit in the receiver, the transmitter must produce a tone of very exact frequency. The transmitter in Fig. 1 uses a mechanical resonant-reed device to generate the tone. The reed is located in the electrical field of a coil, through which the transistor base current flows (see Fig. 3). While the vibrating reed itself is not shown in the schematic, it is a functional part of the oscillator circuit because it controls the frequency. The initial flow of base current flowing in the coil energizes the reed, causing it to vibrate at its natural frequency (in the low audio range). The vibrating reed induces an audio voltage

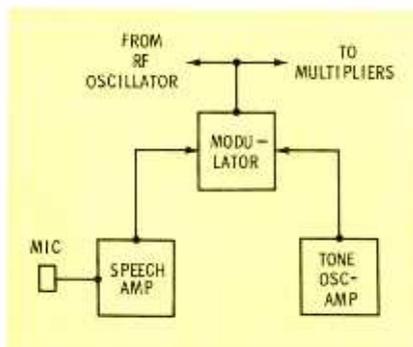


Fig. 1. Audio-frequency tone is applied to modulator stage in transmitter.


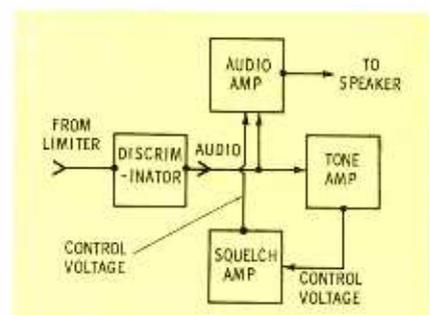


Fig. 2. In receiver, the tone circuit obtains its input from discriminator.

# Pack up your troubles

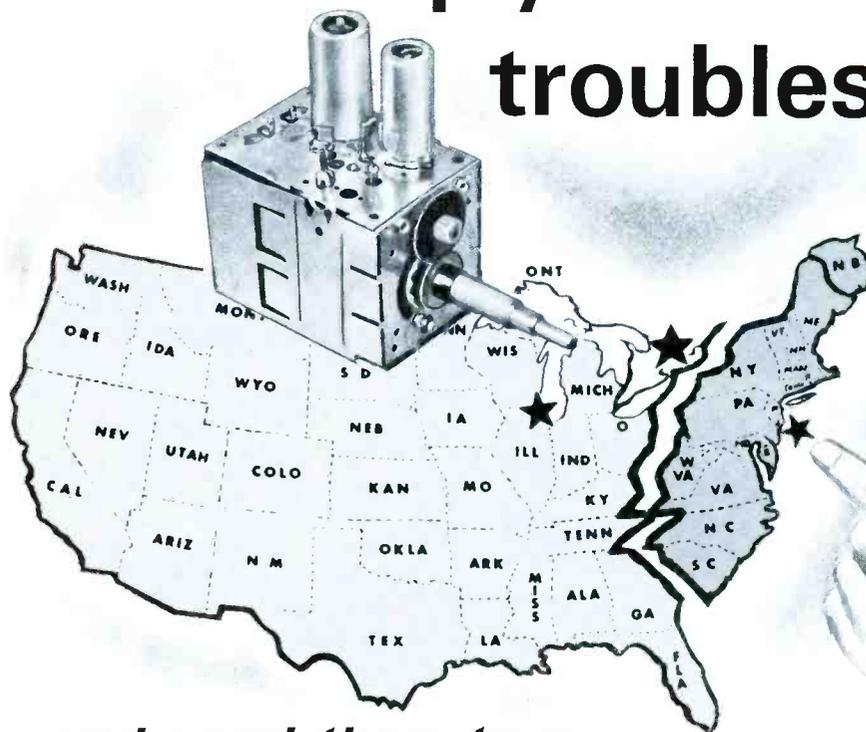

## and send them to a CASTLE TV TUNER SERVICE CENTER

*Ask yourself*

- ... do you have the time to fool around drilling, sawing, filing ... trying to make a "Universal" replacement tuner fit in place of the original?
- ... do you have all the expensive instruments and equipment to complete the alignment so essential after each tuner repair or replacement?
- ... can you spare the time repairing and adjusting your own TV tuners and can you charge enough to justify the time spent?

**A Castle Overhaul eliminates every one of these problems.**

Castle replaces all defective parts, (tubes and major parts are extra at net prices) and then aligns your tuner to the exact, original specifications.

Simply send us your defective tuner complete; include tubes, shield cover and any damaged parts with model number and complaint.

**A Castle Overhaul assures you of the best Service available . . .** because overhauling your TV Tuner is our only business . . . behind every Castle overhaul there is more than a decade of this highly specialized experience. We are proud of the work we do and at today's values our overhaul charge is a real bargain.

"Tough dog" TV Tuner troubles . . . difficult or impossible for the serviceman . . . are routine at Castle.

Send for **FREE** Mailing Kit and complete details.

**ONE PRICE**

**9<sup>95</sup>**

**ALL MAKES**

**VHF TUNERS  
UHF TUNERS  
UV COMBINATIONS\***

\*UV combination tuner must be of one piece construction. Separate UHF and VHF tuners with cord or gear drives must be dismantled and the defective unit sent in.

90 Day Warranty

**CHECK MAP FOR THE  
CASTLE CENTER  
SERVING YOU**




**CASTLE**  
**TV TUNER SERVICE, INC.**

Pioneers in TV Tuner Overhauling

5701 N. WESTERN AVE., CHICAGO 45, ILLINOIS  
653 S. PALISADE AVE., CLIFFSIDE PARK, NEW JERSEY  
IN CANADA: 136 MAIN ST., TORONTO 13, ONTARIO

# For Big Profits Doing This...

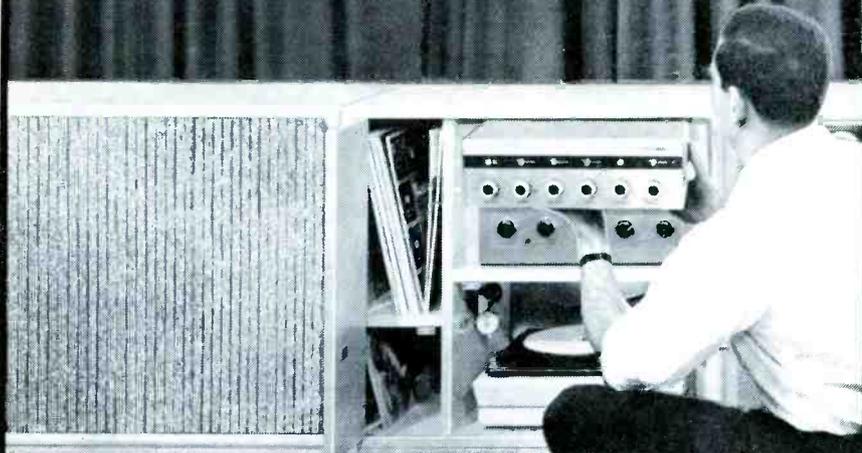

## ...Use These:

Whether it's hi-fi in the home, or CB in car, boat, truck, or taxi, custom installation jobs jump into the big-profit category when you deliver high quality at low cost.


And especially with EICO kits, which average 40% less than our own, low, wired prices. Wire 'em up yourself and pocket the difference—with your customer's blessing, because if you build the components yourself, it's custom-made all the way through!

But kit or wired, EICO's all-out, no-compromise engineering, EICO's strikingly dramatic beauty, and EICO's fantastically low prices provide all the ingredients necessary for big profits on custom jobs. To put it simply: *You Profit from EICO Excellence.*



Deluxe Citizens Band Transceivers

	Kit	Wired
#770: 117 VAC only	\$79.95	\$109.95
#771: 117 VAC and 6 VDC	89.95	119.95
#772: 117 VAC and 12 VDC	89.95	119.95

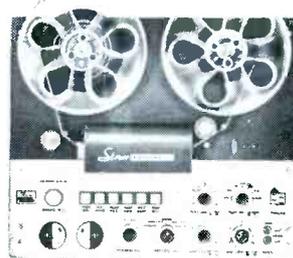

**NEW TRANSISTORIZED STEREO/MONO 4-TRACK TAPE DECK RP100**

Semikit \$299.95    Wired \$399.95  
Luggage-type Carrying Case \$29.95  
Standard 19-inch Rack Mount \$9.95



**STEREO FM MULTIPLEX TUNER ST97**  
Semi-Kit \$99.95    Wired \$149.95  
Includes metal cover and FET.



**FM/AM STEREO TUNER ST96**  
Kit \$89.95    Wired \$129.95  
Includes metal cover and FET.



**70-WATT INTEGRATED STEREO AMPLIFIER ST70**  
Kit \$99.95    Wired \$149.95  
Includes metal cover and FET.



**40-WATT INTEGRATED STEREO AMPLIFIER ST40**  
Kit \$79.95    Wired \$129.95  
Includes metal cover and FET.

Rely on EICO Excellence for your test equipment too:



**AC VTVM & AMPLIFIER #250**  
Kit \$49.95  
Wired \$79.95



**TRANSISTOR AND CIRCUIT TESTER #680**  
Kit \$25.95  
Wired \$39.95




**IN-CIRCUIT CAPACITOR TESTER #955**  
Kit \$19.95  
Wired \$39.95



ADD 5% IN THE WEST

For complete catalog of over 106 EICO kits and wired units—hi-fi, test equipment, citizens radio, ham gear—plus name of nearest distributor, write to dept PF-9 EICO ELECTRONIC INSTRUMENT CO., INC., 3300 Northern Blvd., L.I.C. 1, N.Y. Export Dept., Roburn Agencies Inc., 431 Greenwich Street, New York 13, N.Y.

VISIT EICO ROOMS 518 & 522, NEW YORK HI-FI & MUSIC SHOW, OCT. 2-7

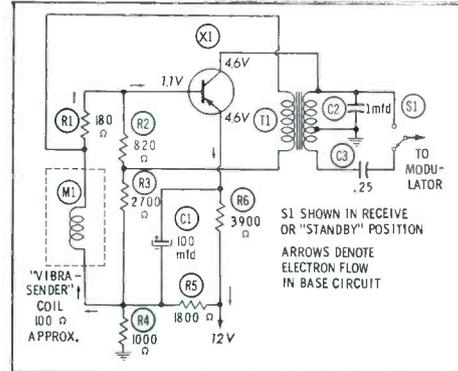

**Fig. 3. This transistorized oscillator drives a resonant-reed tone generator in the coil and thereby controls the operating frequency of the oscillator.**

The reed is a very high-Q device, with a frequency stability of .15% over a temperature range of  $-20^{\circ}$  to  $+80^{\circ}$  C. Because of its high Q, the reed is slow in starting; thus, after the transmitter carrier is keyed, there might be considerable delay before the amplitude of the tone is sufficient to modulate it. To prevent this lag, the tone oscillator is kept operating continuously, and the tone is applied to the modulator circuit by relay contacts when the microphone push-to-talk button is depressed. There is no delay in coding the carrier with this arrangement; therefore, the receiver for which the message is intended will be instantly actuated and none of the message spoken into the mike will be lost.

The oscillator in Fig. 3 is of the common-emitter type, with collector-to-base feedback through transformer T1. The voltage-divider network consisting of R1, R2, and R3 maintains just the right amount of feedback voltage on the base to sustain oscillations. For the sake of illustration, arrows are drawn in the base-to-emitter circuit to indicate the main electron flow. As you can see from the component values, the path of least resistance is through the *Vibrasender* coil rather than the feedback divider network. This current, of course, starts and sustains the vibrations of the resonant reed.

When the transmitter is keyed, the oscillator tone is injected via S1 into the modulator along with voice information from the speech amplifier. Together, they fre-



WILL THE REPLACEMENT ANTENNA YOU ARE NOW USING, COVER THIS HOLE? IF NOT, YOU ARE LOSING PROFITS, BIG PROFITS!

1 1/8"



**TENNA EXACT REPLACEMENTS**

GIVE YOU THE EXACT ANTENNA FOR EVERY CAR AND HOLE . . . EVEN FOR THOSE HARD TO FIT 1 1/8" HOLES!

OVER 100 DIFFERENT CAR MODELS REQUIRE BASES TO COVER 1 1/8" HOLES!

Chryslers, DeSotos, and Plymouths '57 thru '60 and 1960 Darts. Mercurys and Fords '52 thru '56, Thunderbirds '55 thru '57 and Buicks '61 and '62 all require large bases. You cannot afford to overlook such a huge market.



YOU LOSE PROFITS, BIG PROFITS WHEN YOU LOSE BIG HOLE SALES!

TENNA *Exact* REPLACEMENTS FIT ALL HOLES. NO SOLDERING, NO CEMENTING!

No matter how large the hole, you never have to solder, weld or cement rings around the hole before installing a Tenna Exact Replacement. Tenna Exacts save you countless hours of installation time.



YOU LOSE PROFITS, BIG PROFITS WHEN YOU TRY TO COVER BIG HOLES WITH SMALL MOUNTING BASES!

TENNA *Exact* REPLACEMENTS ARE FULLY ASSEMBLED, READY TO INSTALL!

To install a Tenna Exact Replacement all you have to do is remove from skin-wrapped package. Every part, everything you need is in the package.



YOU LOSE PROFITS, BIG PROFITS WHEN YOU MUST COLLECT PARTS AND THEN ASSEMBLE ANTENNAS!

TENNA *Exact* REPLACEMENTS WILL MULTIPLY YOUR ANTENNA PROFITS!

When you sell Tenna Exacts you have a replacement antenna for every car and every hole. You serve your customer in a more satisfactory manner . . . and make 3 times the profit or even more in so doing. It pays to sell Exacts.



YOU LOSE PROFITS, BIG PROFITS WHEN YOU SELL A UNIVERSAL INSTEAD OF AN EXACT REPLACEMENT!

WHEN YOU DISPLAY AND SELL

**TENNA EXACT REPLACEMENTS**

YOU ARE ASSURED OF BIGGER, BETTER, MORE BANKABLE PROFITS!



DEAL YOURSELF IN ON THE BIG **TENNA** FREE DEAL . . . and start making bigger profits at once!



**FREE!**

HANDSOME, GOLD FINISHED, REVOLVING COUNTER DISPLAY STAND AND TENNA ANTENNA GUIDE WITH THE PURCHASE OF 12 TENNA EXACT REPLACEMENTS

Tenna has not pre-selected or pre-packed the 12 antennas for you. You select the 12 Exact Replacements of your own choosing, the models best suited to your own local needs. Order your Tenna Exacts now and start enjoying bigger and better profits at once.

**TENNA CORPORATION, CLEVELAND, OHIO**

**WHERE PROGRESS IS A HABIT AND SALES LEADERSHIP AN ESTABLISHED FACT!**






## Tips for Technicians

Distributor Division, P. R. Mallory & Co. Inc.  
P. O. Box 1558, Indianapolis 6, Indiana

# Hints on Reducing Hum . . .

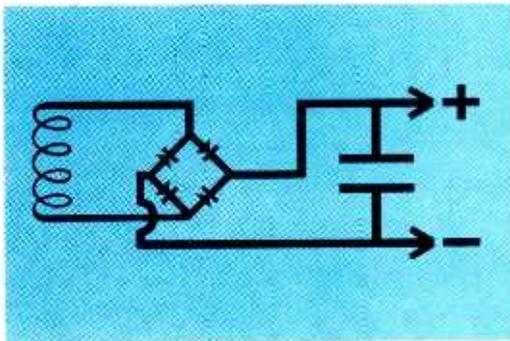

In high fidelity sound systems . . . and in many kinds of commercial and industrial electronic equipment . . . reduction of 60-cycle hum is one of the toughest problems that a technician has to tackle. Most hum comes from 60-cycle voltage sneaking into the signal circuit. There are, of course, many well-known precautions that should be observed . . . using shielded or coax cable between major components, keeping cables short especially in the low-level portion of the system, making sure connectors are tight. Here are some other thoughts that may be useful.

Power supplies in sound systems . . . hi-fi or commercial . . . generally operate at higher temperatures than those encountered in radio or TV. So it pays to be particular about filter capacitors. It pays to use electrolytics rated at 85° C. Those rated at only 65° C start to run into trouble. Then too, because of the added heat, the vent construction is important. In other words, "How good is the seal?" Our tip is to always use Mallory FP-WP electrolytics . . . voltage ratings are conservative and dependable . . . they have excellent stability at high temperature . . . and they all have *etched cathode* construction. This latter is extremely important in avoiding hum. We covered the reasons in a previous TIP (remember?).

Here's another source of hum . . . filament circuits. Many of the highest quality sound systems use a DC filament supply in the preamplifier. It's easy to add this refinement to any system. All you'll need is a Mallory FW-50 "packaged" silicon rectifier circuit. It's encapsulated in a tiny plastic block and takes up very little space. Simply connect the FW-50 to the circuit, add a WP-042 electrolytic and filament hum disappears permanently. If you want more specific information, write and ask us.

Another tip: call on your Mallory Franchised Distributor for prompt service, at sensible prices, on Mallory capacitors, switches, silicon rectifiers, controls, and batteries . . . and for any other parts you may need.

which is almost always below 300 cps. The combination of R1, R2, C1, and C2 presents a sufficiently long time constant to keep the voltage applied to the base of X3 fairly steady.

When switch S1 is closed, the voltage-divider network in the base circuit of X3 is complete. In this condition, audio amplifier X4 is directly controlled by X3, since the emitters of these two transistors are tied together. Normally, 6 volts DC is developed at the base of X3; at this value of base-bias voltage, X3 conducts, holding the voltage on its emitter to a value low enough to keep X4 cut off.

When the *Vibrasponder* reed is actuated by the incoming tone, the base voltage of X3 is raised to 12.8 volts. This causes PNP transistor X3 to cut off, increasing the emitter voltage from 6 volts to approximately 9.5 volts. The result is an increased emitter voltage on X4, which allows that transistor to conduct and permits the incoming message to be heard.

As previously explained, the tone squelch system prevents the radio operator from hearing sta-

tions other than his own. However, when he desires to transmit, he must first be sure the channel is not occupied; otherwise, he may interfere with someone's conversation. To provide for monitoring, a toggle switch (S1) is included in the control panel. When open, this switch disables X4, which in turn allows the audio amplifier to conduct. Any message on the channel can then be heard in the speaker, even if no tone is present.

### An Add-On System

The tone-coded squelch system shown in Fig. 5 is similar in most ways to the one just discussed; they both work on the principle of a resonant-reed relay. There are differences in the circuitry of various systems, but they all produce and receive a tone—the common denominator of them all. Therefore, if you understand the transistorized system just presented, you will have no trouble understanding any other system, even the few which do not use resonant reeds.

The unit shown in Fig. 5 is an

“add-on” device, consisting of the tone-squelch control circuit (V1), a filter (F2) which extracts the tone from the receiver audio and removes voice components, and an audio oscillator (V2) which supplies the tone for the transmitter. A unit such as this can be added to almost any existing equipment.


The squelch-control circuit consists of low-pass filter F1, audio amplifier V1, and resonant-reed relay M1. The output of the discriminator is fed to the input of filter F1. This filter rejects frequencies in the voice range and allows only the signalling tone to reach the two-stage tone amplifier, V1. The output of V1 is fed through transformer T1 to the coil of relay M1. The relay operates only if the tone frequency is the same as the resonant frequency of the reed.

The action of the squelch circuit (not shown) can be described as follows: Normally, the squelch gate tube in the receiver is cut off by a negative bias applied to its grid. When a signal containing the required tone is received, a relay M1 operates and applies a posi-

## MAKE BIG PROFITS!

with 25 to 50 MC. Industrial

# 2-WAY RADIO

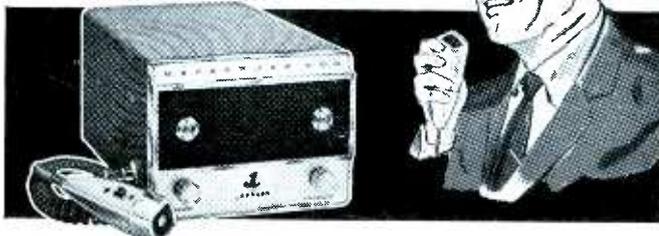

THE “MESSENGER 202” DELIVERS THE PEP AND PERFORMANCE NEEDED FOR SOLID COMMUNICATIONS—COMPLETE DEALER AID PROGRAM PUTS YOU INTO THIS PROFITABLE FIELD OVERNIGHT!


The “Messenger 202” sells for less than \$200.00—is priced within easy reach of any business! A complete 10-tube (including rectifier) crystal-controlled AM transceiver, the “202” is F.C.C. type accepted for use in the Industrial, Public Safety, and Land Transportation service. The “202” practically sells itself when you point out the savings that almost any business or municipal organization can make with this top performing, low cost industrial equipment! Highly selective and sensitive superheterodyne receiver, built-in “Squelch,” and AVC, ANL circuits. Designed for easy operation—fast, smooth installation—and simplified maintenance. Available nationally from E. F. Johnson Company distributors. Powerful dealer aid program shows you how to make big money in sales and service in this highly profitable field—gives you everything you need to handle your own line of industrial 2-way radio equipment!

CONTACT YOUR DISTRIBUTOR OR WRITE TODAY for Full Details



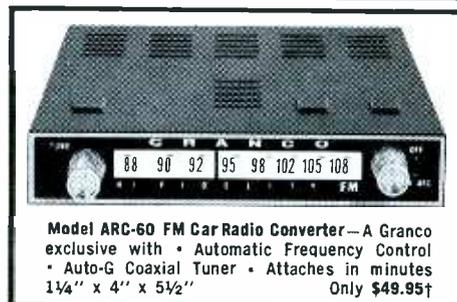**E. F. JOHNSON CO.**  
5607 Tenth Ave. S.W. • Waseca, Minn.

Manufacturers of World's Most Widely Used Personal Communications Transmitters



Model ARC-60 FM Car Radio Converter—A Granco exclusive with • Automatic Frequency Control • Auto-G Coaxial Tuner • Attaches in minutes 1¼" x 4" x 5½" Only \$49.95†

## ADDS INSTANT FM EVERYWHERE

# GRANCO

BY *Emerson Radio*



Model T-300 FM Tuner-Adapter — Exclusive Coaxial Tuner • 2-Knob Operation • So versatile it plugs into any home sound system • 6¼" x 4" x 4½" Only \$19.95†

Add exciting FM sound to any phonograph, TV set, hi-fi system, or car radio. Exclusive features plus advanced, hand-wired circuitry assure superb performance. Write for money-making facts on complete line of FM, FM/AM and new Stereo FM receivers.

†Suggested list. Slightly higher in some areas.



**GRANCO**  
Division of Emerson Radio Inc.

America's Leading Specialist in Stereophonic FM

680 FIFTH AVENUE N.Y. 19

RCA—PIONEER OF COLOR TV—BRINGS YOU

ALL YOU  
NEED FOR

# COLOR-TV SERVICING



WR-64A



WO-91A



WR-70A



WR-69A



WR-99A

## RCA Color-Bar/Dot/ Crosshatch Generator

Low-cost, lightweight, portable instrument that provides all essential Color-TV test patterns. Simple to operate: only 3 controls. RF output leads connect directly to antenna terminals of receiver; no external sync leads required. Crystal-controlled signals assure rock-steady patterns, free from "jitter" and "crawl." Extra-wide-range chroma control. Generates:

- **Color-bar pattern:** ten bars of color, including R-Y, B-Y, G-Y, I and Q signals spaced at 30° phase intervals for checking phase and matrixing, and for automatic frequency and phase alignment. Permits accurate alignment of the "X" and "Z" demodulators which are used extensively in RCA Victor and many other makes of color TV receivers
- **Crosshatch pattern:** a grid-like pattern of thin sharp lines for adjusting vertical and horizontal linearity, raster size, and overscan
- **Dot pattern:** a pattern of small sized dots facilitating accurate color convergence adjustments

\$189.50\* with output cables.

## RCA 5-Inch Oscilloscope for Color-TV

A wideband scope excellent for checking colorburst signals and general troubleshooting of wideband color circuits and other electronic equipment. Multi-scale calibrated graph screen makes measurement of peak-to-peak voltage as easy as with a VTVM.

- New 2-stage sync separator assures stable horizontal sweep lock-in on composite TV signals
- Dual bandwidth: 4.5 Mc at 0.053 volt rms/in. sensitivity. 1.5 Mc at 0.018 volt rms/in. sensitivity
- Continuously adjustable sweep frequency range: 10 cps to 100 Kc
- 3-to-1 voltage-calibrated, frequency-compensated step attenuator for "V" amplifier
- Simplified, semi-automatic voltage calibration for simultaneous voltage measurement and wave-shape display
- Vertical-polarity reversal switch for "upright" or "inverted" trace display

\$249.50\*, including direct/low capacitance probe and cable, ground cable, and insulated clip.

## RCA Television FM Sweep Generator

Specifically designed for visual alignment and troubleshooting of color and black-and-white TV receivers, and FM receivers. The RCA WR-69A has pre-set switch positions for all VHF TV channels, FM broadcast band, and TV video, chrominance, and IF frequencies. The WR-69A has these important features:

- IF/Video output frequency continuously tunable from 50 Kc to 50 Mc
- Sweep-frequency bandwidth continuously adjustable from 50 Kc to 20 Mc on IF/Video and FM; 12 Mc on TV channels
- Output level—0.1 volt or more
- Attenuation range: TV channels, 60 db IF/Video, 70 db FM, 60 db
- Return-trace blanking
- Two adjustable bias voltages on front panel

\$295.00\* including all necessary cables.

## RCA RF/VF/IF Marker Adder

Designed for use with a marker generator (such as RCA's WR-99A) and a sweep generator (such as RCA's WR-69A), this instrument is used for RF, IF, and VF sweep alignment in both color and black-and-white TV receivers. In visual alignment techniques, it eliminates distortion of sweep response pattern.

Important features:

- Choice of four different marker shapes provided by front panel switch for different types of sweep-response curves and for positive and negative sweep traces
- Provides very high-Q markers of high-amplitude and narrow bandwidth
- Complete front panel control of marker shape, marker amplitude, marker polarity, sweep amplitude, and sweep-trace polarity

\$74.50\* complete with cables.

## RCA Crystal-Calibrated Marker Generator

Supplies a fundamental frequency RF carrier of crystal accuracy for aligning and troubleshooting color and B&W TV receivers, FM receivers and other electronic equipment in the 19-260 Mc range. Combines functions of multiple-marker generator, re-broadcast transmitter, and heterodyne frequency meter.

- Highly stable output
- May be calibrated at 240 separate crystal check points—accurate calibration provided at 1-Mc and 10-Mc intervals
- Matched-impedance pad-type attenuator and double shielding of the oscillator provide effective attenuation of all frequencies
- Most-used IF and RF frequencies are specially indicated on the dial scale
- Sound and picture carrier markers available simultaneously

\$242.50\* complete with output cable and phone tip.

RCA ELECTRON TUBE DIVISION, Harrison, N. J.



The Most Trusted Name in Electronics

\*User Price (Optional)

# Arcolytic<sup>®</sup>

Available from all authorized ARCO distributors



## 1401 Values... The largest selection of exact replacement twist-mount & tubular electrolytics

■ 99.99% high purity aluminum foil electrolytics at no extra cost! ■ Choose from stock any single, dual, triple or quadruple capacitance-voltage combination for replacement in television, radio, and other electronic equipment ■ Made to withstand high ripple and high surge voltages ■ Designed for 85°C high temperature operation ■ Greater shelf and operating life because only premium grade ingredients are used ■ Built and tested to meet EIA Specification RS-154 ■ Individually packaged with mounting plates for your convenience ■ Unconditionally Guaranteed.

Manufactured by

# ARCO electronics inc.

Community Drive, Great Neck, New York • HUinter 7-0500

ELECTROLYTIC DIVISION

Branches:  
Dallas 7  
Los Angeles 35

tive voltage to the gate tube, thus causing it to conduct, and permitting the message to be heard in the speaker.


To provide for monitoring the channel before transmitting, a microphone hang-up switch is wired so that, when the microphone is lifted, the receiver audio section is restored to regular (carrier-actuated) squelch operation. Any signal strong enough to actuate the regular squelch circuit will then be audible even though it may not contain the required tone.

Like the audio-oscillator transistor in the other unit, this audio oscillator (V2) uses a resonant-reed drive-and-control coil to set the frequency of oscillation. The output of V2 is fed, through a modulation control and a low-pass filter (F3) which attenuates harmonics, to the second stage of the speech amplifier in the transmitter. Here, it is mixed with any voice modulation from the mic, and both signals go directly to the modulator.
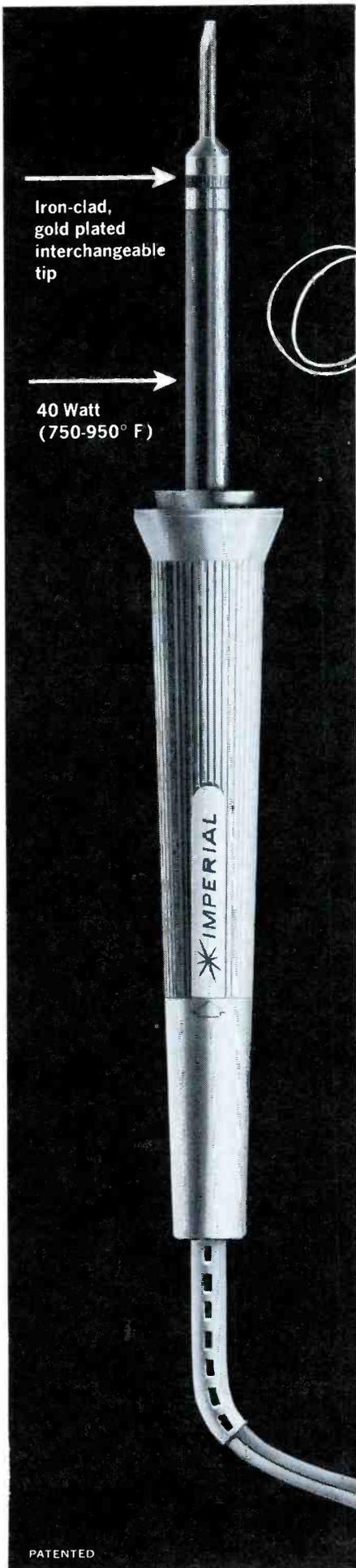
### Maintenance And Service

The tone-coded squelch portion of any transmitter or receiver seldom gives trouble. When it does occur, however, a malfunction in these circuits can be a real "dog." Sometimes, just replacing the resonant-reed relay (which is a plug-in unit) will cure the trouble. This, and changing the tubes (or the transistors) is about the easiest and quickest method of arriving at a decision as to the extent of trouble.

The wise serviceman will take voltmeter and scope readings in a couple of units he knows to be working, just to have a good reference in case of trouble. When readings are taken with a scope, it is not so important to obtain a perfect sine wave as it is to find the correct amount of amplification. Distortion of the waveform can become most severe before it will adversely affect the system, just as long as the frequency remains constant and the amplitude sufficient. In fact, when comparing the waveforms of units in the same system, you may find quite a variation from set to set. Ignore it!



Iron-clad,  
gold plated  
interchangeable  
tip

40 Watt  
(750-950° F)

# Special!

ONLY \$4.99

NOW...SAVE \$1.77



#6060 SOLDERING IRON

**SAVE** when you buy the

IMPERIAL... SAVE every time you use it on the bench or for on-the-spot servicing. The #6060 IMPERIAL... designed specially for printed circuitry and miniature soldering applications... reduces costly customer callbacks, damage to circuits, time spent on servicing.



The IMPERIAL features complete interchangeability of components, comes with two of the most-used tips (44 are available), and a 40 Watt high heat, long-life heat cartridge. See for yourself why the new IMPERIAL is the most preferred iron in the electronics field today!

115v AC-DC



components



**ASK FOR THIS SPECIAL  
OFFER AT YOUR UNGAR  
DISTRIBUTOR TODAY!**

PATENTED

# NEW SECO "TRI-TESTER"

With Seco's Patented Grid  
Circuit Test—copied  
by many, equalled  
by none



Model  
107A

ONLY  
\$14950  
NET



Tests all tubes including the new  
Nu-Vistors, Novars, Compactrons and 10-pin types

©1961 Seco Electronics, Inc.

The Seco 107A "Tri-Tester" is the finest, fastest, most complete tester on the market—and at a popular price. Extremely accurate and easy-to-use, this deluxe model provides *all* essential tests for a wide range of Radio-TV, Industrial and Foreign tube types including sub-miniature types.

Eye and Line Adjustments are set up only once—not individually for each tube. Handy new "FLIP-CHART" tube index lists complete tube data set-up information. Cards on new tube types are issued to registered owners, keeping your unit up-to-date. The

107A "Tri-Tester" is compact, portable and completely self-contained in a handsome, vinyl plastic carrying case.

Seco is a pioneer in the field of modern tube testing research—the originator and exclusive patent holder of the nationally accepted Grid Circuit Test. The "Tri-Tester" is well accepted as a standard by both industry and government agencies. It meets specifications for: FEDERAL STOCK CLASSIFICATION, Tube Tester Type 107-FSN-6625-713-9075. Make your next purchase a Seco product.

ONLY SECO GIVES YOU ALL THESE TESTS IN ONE TESTER

GCT

### GRID CIRCUIT TEST:

All tubes get 11 positive, simultaneous checks for leaks, shorts and grid emission. This Seco designed and patented "Electron-Eye" test detects "hard to find" faults passed up by conventional short tests.

DMCT

### DYNAMIC MUTUAL CONDUCTANCE TEST:

Pre-wired chassis for effective testing of voltage amplifier and similar tube types. "Fil. Sel." and "Load" are the only settings required. "Good-?-Bad" meter indicates relative trans-conductance.

CET

### CATHODE EMISSION TEST:

The best method for testing pulse amplifier, power output and damper type tubes. Number of set-up operations is kept to a minimum. This test is provided by the free point selector system.

See your distributor for complete details on the Seco Model 107A Tube Tester. He has a complete line of quality Seco units for testing electronic equipment.



**SECO ELECTRONICS, INC.**

1221 South Clover Drive, Minneapolis 20, Minn.

Please send Free...  Model 107A Operating Instructions and Schematic

"How to Test Tubes" Chart

Complete Seco Electronic Equipment Line Folder

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_

STATE \_\_\_\_\_

The shape of the signal is of little importance.

In the unit of Fig. 3, relay switch S1 gives trouble. Also, the disabling switch (S1 in Fig. 4) occasionally goes bad. More common is trouble in the resonant-reed devices in transmitters and receivers.


In some units there are no adjustments to be made. In Fig. 5, modulation control R1 is set at the factory and will require adjustment only when the oscillator tube or reed relay has been replaced—in which case the following adjustments must be made:

1. Disconnect the output cable of the tone unit from the jack on the transmitter.
2. Connect a signal generator (adjusted to provide a 1-volt, 1000-cps tone) to the mic-in-pup terminals.
3. While observing a frequency-deviation meter, key the transmitter on and adjust the transmitter modulation control for 80% of maximum deviation ( $\pm 4$  kc deviation for narrow-band or  $\pm 12$  kc for wide-band stations).
4. Reconnect the oscillator output cable to the transmitter. Leave the signal generator connected, also.
5. Adjust modulation control R1 in Fig. 5 until the modulation meter indicates 100% modulation ( $\pm 5$  kc for narrow-band or  $\pm 15$  kc for wide-band stations). The modulation now produced by the tone will not exceed  $\pm 1$  kc on narrow-band or  $\pm 3$  kc on wide-band units.

### Conclusion

The user can't have 100% privacy on a particular channel anymore, but a tone-coded squelch system can provide relief from incessant channel chatter. Whether the tone unit is an add-on type such as in Fig. 5, or a built-in unit, servicing consists simply of being sure the correct tone is being generated, and the received tone is properly actuating the squelch-control circuits. With a working knowledge of these circuits, you will find no problem in troubleshooting them. ▲
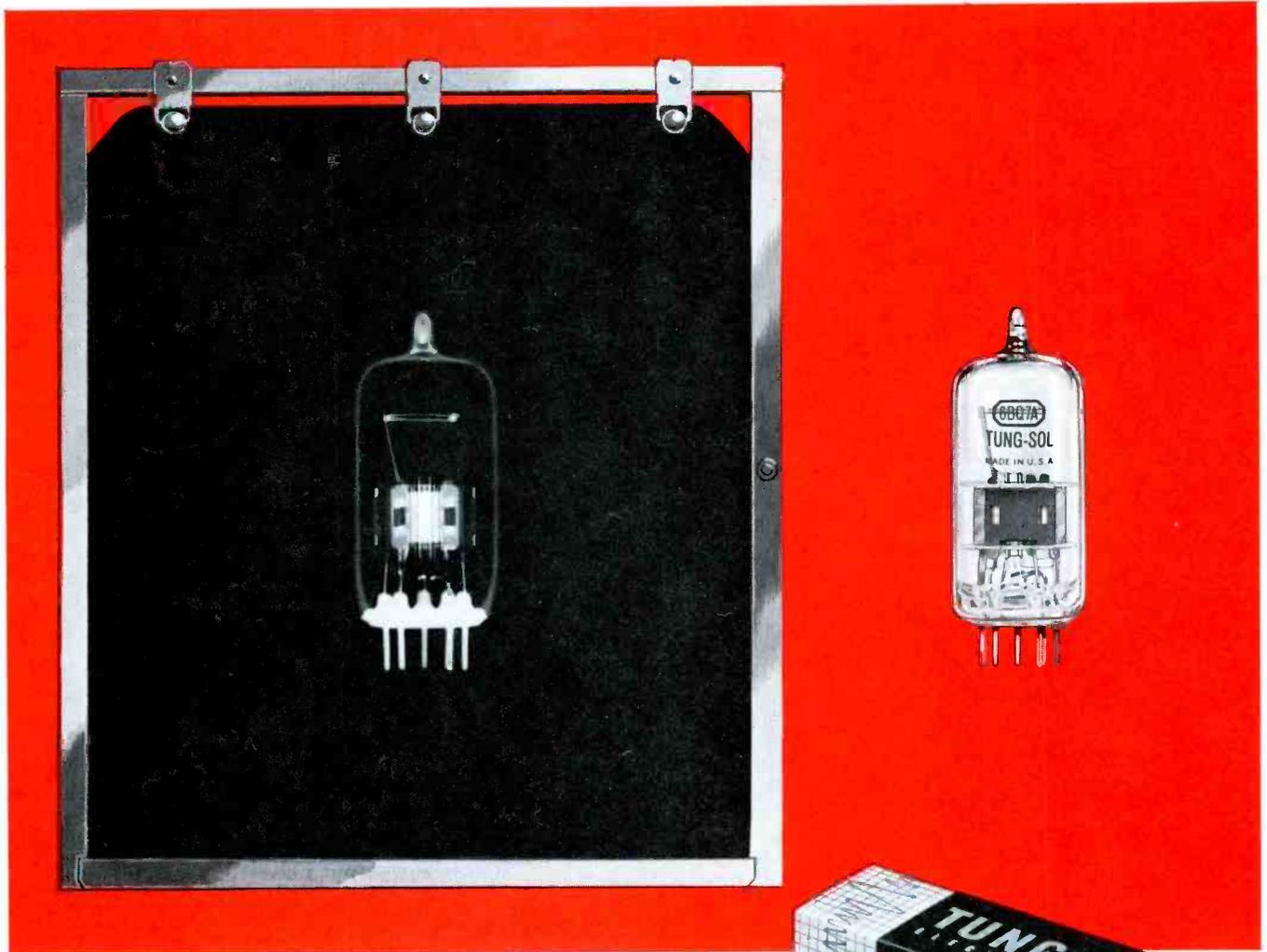
## HIGH GAIN AND LOW CAPACITANCE OF FRONT END TRIODES EXPLAIN ABSENCE OF SNOW ON PICTURE TUBES




**S**NOWY or hazy pictures are symptomatic of tv front ends that transmit input noise infections to the video stages. The wideband RF amplifier triodes manufactured by Tung-Sol for tv tuner service are immunized against this disease by abnormally close spacing of grids and cathodes, boosting power gain and allowing transconductance to increase faster than input capacitance. Isolation of tube elements is maintained by three-part formula: clear mica spacers and rigidized construction to prevent thermal warping and microphonics; high-purity materials prevent gas generation and the formation of leakage paths; extreme cleanliness during every step of manufacture avoids contaminants. Shot noise caused by uneven cathode emission is prevented by using finely dispersed cathode materials.

### PRESCRIPTION FOR PROFIT

Customers appreciate fair weather tv pictures. To keep customers and their sets sunny, specify Tung-Sol front end tubes.

 **TUNG-SOL**<sup>®</sup>  
RF AMPLIFIER TUBES

TUNG-SOL ELECTRIC INC., NEWARK 4, N. J.

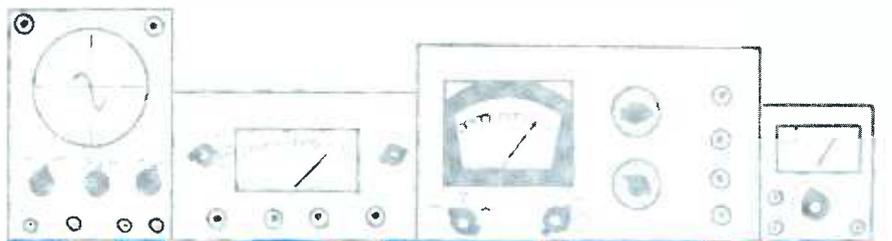

# NOTES

## ON TEST EQUIPMENT

by Forest H. Belt

### Unlimited Scope

The Model WO-91A Oscilloscope (Fig. 1), manufactured by RCA, is a wide-band, high-sensitivity instrument which is capable of handling color-TV troubleshooting requirements as well as the day-to-day needs of regular radio and TV servicing. In addition, it has many industrial uses.

Its specifications are:

1. **Power Required**—105-125 volts; 50-60 cps; 70 watts.
2. **Vertical Amplifier**—Frequency response, within  $\pm 1$  db from 3 cps to .5 mc (high sensitivity), within  $\pm 1$  db from 3 cps to 4.5 mc (wide band); sensitivity, 150 mv peak to peak for 1" deflection (wide band), 50 mv peak to peak for 1" deflection (high sensitivity); input loading 1 megohm shunted by 40 mmf (57 mmf with direct probe attached); maximum input voltage, 600 volts peak to peak (in presence of not more than 400 volts DC).
3. **Horizontal Amplifier**—Frequency response, within  $-6$  db from 3 cps to .5 mc; sensitivity, 180 mv rms for 1" deflection; input loading, 2.2 megohms shunted by 30 mmf; phase-control range from  $0^\circ$  to  $160^\circ$ .
4. **Z-Axis Input**—Frequency response,

within  $-6$  db from 3 cps to .5 mc; sensitivity, 12 volts rms for blanking.

5. **Sweep Ranges**—Continuously adjustable from 10 cps to 100 kc; preset positions, 30 cps (TV vertical) and 7875 cps (TV horizontal).
6. **Controls and Terminals**—Nine potentiometers: INTENSITY (ganged with ON-OFF switch), FOCUS, V CENTERING, H CENTERING, SWEEP VERNIER, H GAIN, SYNC ADJ, V CAL and PHASE; five rotary switches: 4.5 MC-CAL-1.5 MC, V POLARITY, V RANGE, SWEEP, and SYNC-H SEL; four combination-type terminals: GND, Z-AXIS, SYNC, and H INPUT; one coaxial V INPUT connector; pilot lamp.
7. **Size, Weight, Price**— $13\frac{1}{2}$ " x 9" x  $16\frac{1}{2}$ "; 30 lbs; \$239.50.

The Model WO-91A is a successor to the well-known Model WO-91 and incorporates a number of the features which made the earlier instrument popular. But the WO-91A has characteristics which are a definite forward step in scope design.

The WO-91A incorporates a green-trace, 5" CRT—the 5U1. A calibrated graticule, combined with internal compensation of the vertical attenuator, permits exact measurement of peak-to-peak voltages as they appear on the CRT screen. The high sensitivity of the instrument makes it useful for tracing voltages and signals in almost any type of entertainment-electronics equipment, from transistor radios to color television sets. By the turning of a switch, the unit can be changed to a wide-band scope, enabling the service technician to see highly accurate presentations of such complex waveforms as horizontal sync pulses, color bursts in a composite video waveform, and high-frequency square waves.

A special multipurpose probe—the Model WG-300B—is included with the scope. This probe is a combination direct-reading and low-capacitance unit, enabling the user to choose either function at the flick of a self-contained switch. The attenuation ratio of the low-cap probe is 10:1—standard with most such probes. This merely means that, when using the

probe, you must multiply any signal measurement by 10 to find its true value, since the waveform will be reduced on the scope screen by a factor of 10.

Probably the most unusual feature of the WO-91A is its choice of bandwidths for the vertical amplifier. This is accomplished by switching alternate values of certain components into the vertical amplifier circuits and adding or removing extra decoupling components. The result is a choice of either narrow bandpass with high sensitivity (.018 volts rms/inch) or wide bandpass with lowered sensitivity (.053 volts rms/inch). The practical high-frequency limit is 500 kc for the narrow-band position, and 4.5 mc for the wide-band position; the lower limit for both modes of operation is 3 cps—low, indeed.

The vertical input circuit incorporates a calibrated, frequency-compensated attenuator. The component values are chosen to control an input signal according to marked values, so the scope graticule can be used to measure the peak-to-peak value of an applied signal.

To use this measuring function of the WO-91A, first switch the bandwidth selector to CAL; this automatically switches the vertical attenuator to the 5-volt scale and applies a 3-volt peak-to-peak 60-cps signal to the vertical input. Then, adjust the V CAL control so the waveform on the screen fits between the "Cal" lines on the graticule. (We found this to be easiest when we used a SWEEP-control setting between 1000 and 10K, and adjusted the H GAIN for a scope trace about 2" wide.)

Having thus calibrated the vertical attenuator, you can use the V RANGE switch and graticule the same as the range switch and meter of any VTVM. For example, if a video waveform of unknown value were applied to the scope vertical input—using the *direct* probe—and the V RANGE switch had to be set to 15 (on the wide-band setting) to keep the pattern "on screen," the graticule marking would represent 15 volts, full scale. If the waveform filled only  $\frac{2}{3}$  of the vertical space in the graticule, its value would be 10 volts. To make readings more accurate, the graticule divisions are marked in volts; by use of these markings, very accurate peak-to-peak voltage measurements can be made.

Keeping the WO-91A in good operating shape is no problem. The only adjustment which may need to be made periodically—the *astigmatism* control—is accessible through a hole in the left side of the cabinet, as shown in Fig. 2. To adjust it, set the SYNC-H SEL switch to LINE and set the bandwidth control to CAL. Adjust the PHASE, V CAL, and H GAIN controls for a perfectly circular trace on the CRT. Set the FOCUS control for best focus around the entire circle. If the trace line is exactly the same thickness all the way around the circle, the astigmatism control is already set properly; however, if the thickness of the line varies, adjust the control with a screwdriver. It may be necessary to readjust the FOCUS control each time a slight adjustment is made to the astigmatism potentiometer; alternate



Fig. 1. New version of an old standby.



## Where you gonna get it?

From the distributor that stocks the "exact replacement" line? Too bad. Chances are 8 to 1 he can't fill your order. (This really shouldn't surprise you. There are more than 10,000 different values of electrolytics used in electronic equipment today. How can any line of 1600 exact ratings possibly include the exact replacement every time?)

Or maybe you hope to get it from the distributor who stocks the "service-designed 300." Pity. By the manufacturer's own admission, you'll be out of luck 3 times out of 10. You then have to "double up" (assuming you have the space, the time, the patience and the customer's consent) or you high-tail it to another distributor who has the right value (made by somebody else, probably us).

Smart technicians get their electrolytics from their Cornell-Dubilier distributor. Even though CDE


manufactures and stocks well over 1,000 different standard values, CDE distributors, by stocking only 425 Preferred units, have a replacement for you every time you call. Each and every CDE Preferred unit conforms to EIA Standard RS-154 (revised) for electrolytic capacitors, so you know they're right.

Next time you need an electrolytic, check your copy of the CDE Service Selector Catalog. Pick out the Preferred unit you need (they're starred in the listings). Call your CDE distributor. He'll have it for you! And ask him for a copy of "Truth of the Matter," Cornell-Dubilier's bulletin on electrolytic capacitors.

CORNELL-DUBILIER ELECTRONICS, DIV. OF FEDERAL PACIFIC, 50 PARIS ST., NEWARK 1, N. J.

**CDE** **CORNELL-DUBILIER**  
the only Company that makes them all

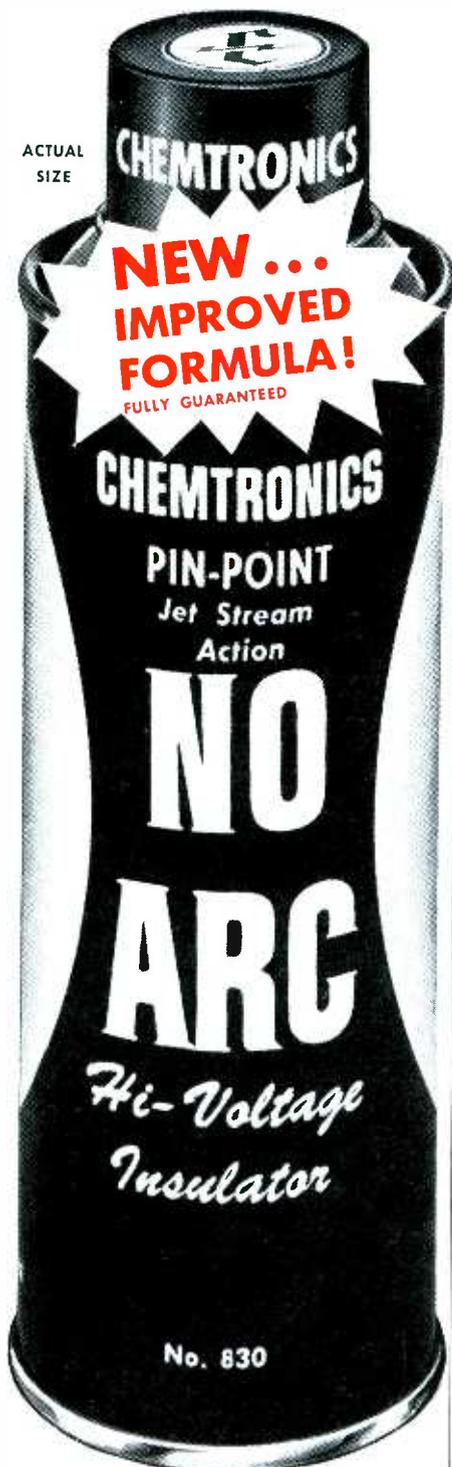**20,000  
VOLTS  
DIELECTRIC  
STRENGTH**



USES THE NEW PRINCIPLE OF

**JET-ACTION**  
**NOT A SPRAY!**

WRITE FOR LITERATURE



**CHEMTRONICS Inc.**  
870 East 52nd Street, Brooklyn, New York

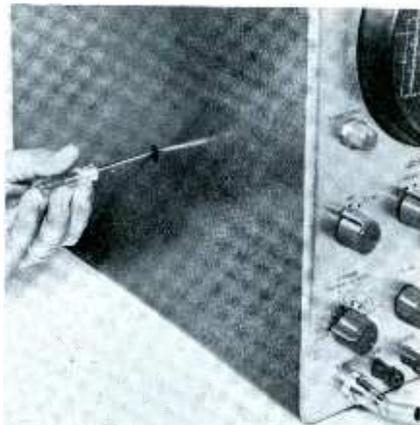


Fig. 2. Simple astigmatism adjustment.

between adjusting and refocusing until the trace forms a perfectly even, well-focused circle.

Other maintenance adjustments, which are best made with the proper test equipment, are fully described in the comprehensive manual which accompanies the WO-91A. These adjustments include vertical-amplifier alignment (which, incidentally, will very seldom be needed), plus compensation and calibration of the sweep oscillator.

We used the WO-91A scope in our lab for quite some time. The only annoyance we found with the instrument was a "bounce" of the trace (sometimes clear off-screen) when we connected the probe into a DC-carrying circuit. This is most noticeable when you're using the low-cap probe, and is caused by the large input capacitor used. This large-value component takes a bit of time to charge through the resistors in the vertical attenuator, and since the remainder of the vertical amplifier is DC coupled, the charging lag results in displacement of the trace. The large resistor in the low-cap probe makes the charging time even longer than when a direct probe is used, and the trace is much slower in returning to the center of the scope screen. We found we could hasten this "return time" by momentarily flipping the V RANGE switch to its highest position; this caused the capacitor to charge faster, and the trace returned more rapidly.

With its wide-band, high-sensitivity characteristics, Z-axis modulation capability, quick-change probe, line-phase control, external-sync facilities, and easy-reading calibration, the Model WO-91A is a very useful instrument for industrial applications, communications troubleshooting, and, of course, radio-television servicing. It is one of the better servicing scopes available today.

### Behind The Bars

A newly announced item of color-TV test equipment is shown in Fig. 3—the Model E-450 Color Generator introduced by Precision Apparatus Co., Inc.

Its specifications are:

1. Power Required—105-125 volts AC; 60 cps; 60 watts.

**Sy**   
**says:**

### Microphones — Part 1

There are four types of microphones commonly used in commercial/industrial applications — ceramic, crystal, dynamic and carbon. The technician should understand each of these, since they are not readily interchangeable.

The carbon microphone is the least understood, although it's actually the forerunner of all microphones. It consists of tightly packed carbon granules and a diaphragm which alternately compresses and loosens the carbon granules, varying the resistance of the carbon "button" in accordance with the sound pressure variations.

A carbon microphone requires a voltage source and a low-impedance input circuit. In high-impedance tube circuits, an input transformer must be provided to match the low microphone impedance to the grid-circuit.


Carbon microphones are characterized by their ruggedness, high output, and usually limited frequency range. All these characteristics have made it a favorite in the past on communication equipment, however, there are undesirable traits in all carbon type microphones such as carbon noise (hiss), granule coherence, non-linear response (distortion) and possible affects on carbon granules by excessive temperature or humidity. Because of these common faults and the fact that a carbon type microphone cannot be directly replaced by standard dynamic, crystal or ceramic units, Astatic is developing a transistor amplifier for use in our new mobile microphones which then will directly replace the carbon unit. In the meantime, we will still offer our 10M5A carbon microphone as we have for over 10 years.



THE ASTATIC CORP.

CONNEAUT, OHIO • U.S.A.

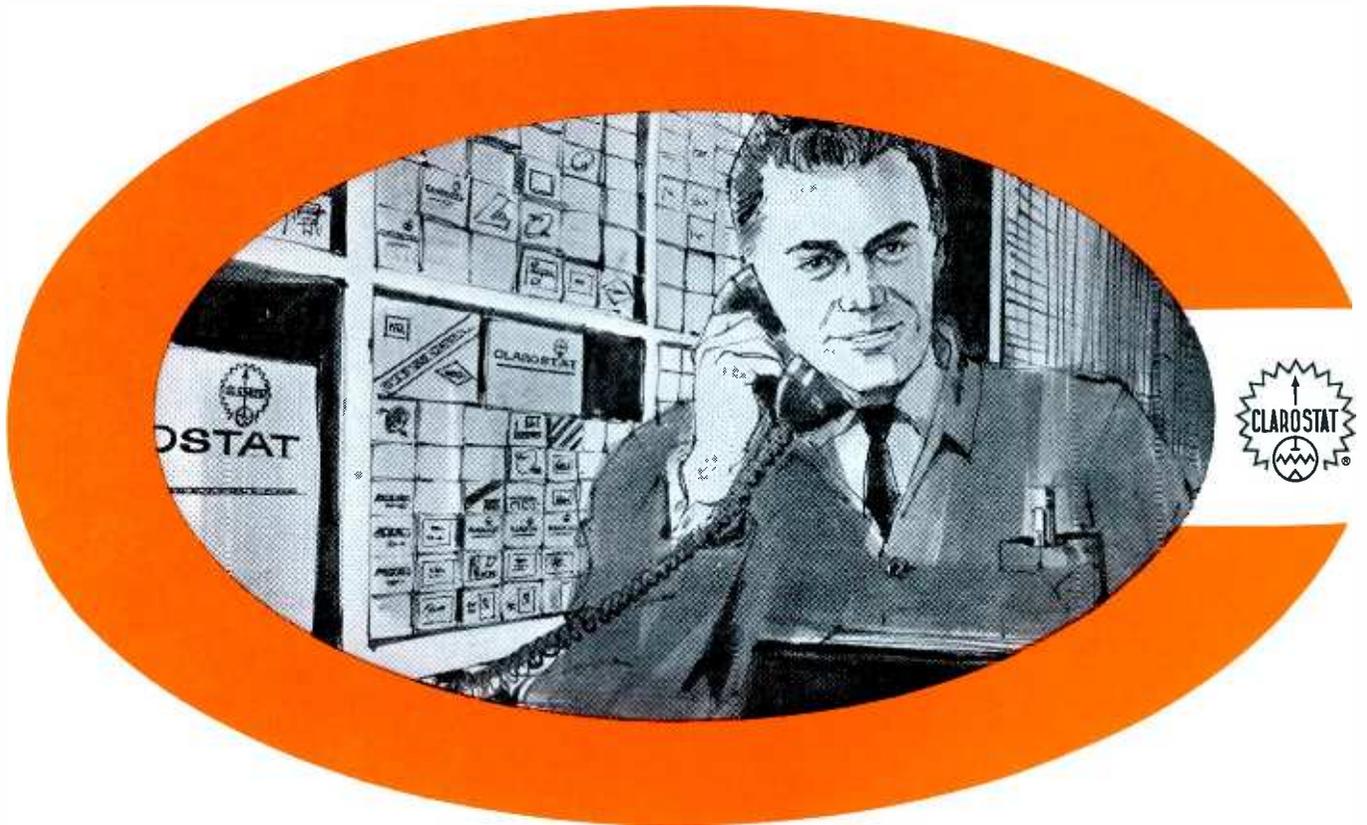MANUFACTURERS OF  
PHONOGRAPH CARTRIDGES • PICKUPS  
• NEEDLES • MICROPHONES • RECORDING TAPE



# A SALUTE TO A KEY MAN

The distributor counterman—fountainhead of information, aids to servicing, new products. At his fingertips is a wealth of information on the latest replacement parts, cross references to currently available components and older equipment. Ask your counterman—he'll steer you right every time.


**CLAROSTAT SERVICE COMPONENTS** Your counterman knows the completeness of the Clarostat line of potentiometers and resistors. Clarostat keeps him fully informed of all new Clarostat products, as well as where they go. With your counterman and Clarostat you're on the winning team of successful servicing...

DISTRIBUTOR SALES DIVISION


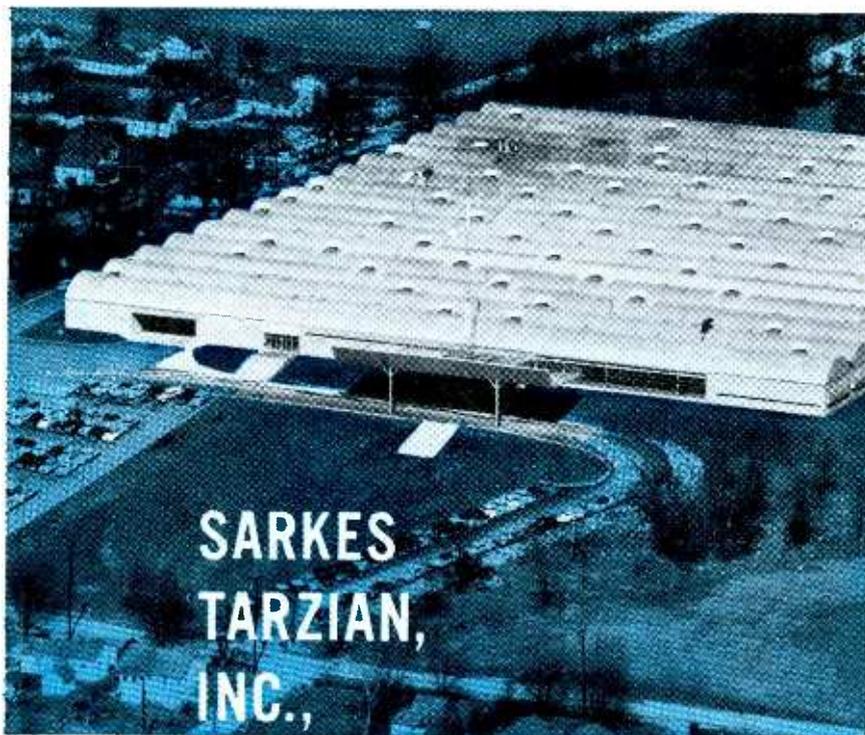
# CLAROSTAT

CLAROSTAT MFG. CO., INC. DOVER, NEW HAMPSHIRE



the home of  
**PRACTICAL INGENUITY  
 IN ELECTRONICS**

This modern 250,000 square foot plant is a far cry from the Company's modest beginning in 1944. Today, in this main plant, in Bloomington, Indiana, modern manufacturing methods—with an abundance of technical know-how—combine to produce the world's finest TV Tuners and FM Tuners.

Here, and elsewhere throughout the Tarzian industrial complex, some 2000 employees produce such diversified electronic products as:

**TV TUNERS**      **FM TUNERS**      **SEMICONDUCTORS**  
**BROADCAST EQUIPMENT**      **AIR TRIMMERS**  
**MAGNETIC TAPE**      **FM RADIOS and AM/FM RADIOS**

(In addition to the extensive manufacturing facilities, Sarkes Tarzian, Inc. owns and operates six full-time radio and TV stations in Indiana.)

The engineering excellence, reliability and sensible pricing of ALL Tarzian products are a part of the approach to "Practical Ingenuity in Electronics." Our reputation for customer satisfaction has been built on this philosophy. We intend to keep it that way.

*Electronic Products of Tomorrow—Today*



**SARKES TARZIAN INC**

east hillside drive • bloomington, indiana      edison 2-7251

2. *RF Output—Pretuned to Channel 3; video carrier, 20,000 uv; 4.5-mc sound carrier, 2000 uv; 300 ohms, balanced.*
3. *Video Patterns—Horizontal bars, vertical bars, crosshatch, dots, keyed color bars.*
4. *Controls and Terminals—Rotary DISPLAY switch for choice of video pattern; rotary SELECTOR switch, controlling output functions and AC power; CHROMA potentiometer, controlling percentage of saturation in color-bar display; coaxial RF output jack; pilot lamp.*
5. *Size, Weight, Price—13" x 12" x 8"; 14 lbs; \$189.95.*

The Model E-450 is a keyed-rainbow type of color-bar generator. Its operating panel is especially designed for simplicity of operation, having only three controls—one to choose the type of RF output, one to select the video display, and a saturation control for the color bars. In addition to the color display, the Model E-450 also supplies the signals needed for other color-set adjustments, such as convergence and deflection linearity.

The rainbow signal is produced in the generator by a crystal-controlled 3.563795-mc signal. Notice this signal is displaced from the 3.579545-mc reference oscillator in color receivers by 15,750 cps—a difference which represents a 360° phase shift during each horizontal scanning line. This precise phase variation will create a continuous color change during each scanning line, resulting in a complete color spectrum or *rainbow* display on the CRT screen.

To furnish a reference for the various portions of the rainbow pattern, the signal is "broken up" into sections, or bars, by keying the 3.563795-mc rainbow signal on and off. The periodic interruptions of the signal cause the display on the CRT screen to appear as *bars* of color. This "on-off" characteristic of the color signal gives rise to the name *keyed-rainbow*.

A series of oscillators and dividers initiate the various video patterns, as diagrammed in Fig. 4. The main timing action is controlled by a 189-kc crystal oscillator—a Pierce circuit which uses one section of a 12AU7. The frequency dividers are actually triggered blocking oscillators (a very stable arrangement)



**Fig. 3. Newly developed keyed-rainbow signal generator for color servicing.**

# THE FINEST STEREO HEADPHONES YOU'VE EVER HEARD



**jensen** MANUFACTURING COMPANY  
Division of The Muter Co.

Jensen's new HS-1 Stereo Headphones are ready for you. We think you will agree with the experts who say they are the finest ever. Reasons? They cover the frequency range with extra smoothness because they have new fluid-damped transducers developed by Jensen. And they are good to look at, easy to adjust, comfortable to wear. Cord comes out one side . . . you don't get tangled up. Impedance 8 ohms. Complete with Jackbox for connecting to any stereo amplifier. Write for Brochure MH.

HS-1 With 3 conductor plug and accessory jack box . . . . . Net \$24.95  
HS-1L With 4 spade lug terminals . . . . . Net 22.50

Jensen Manufacturing Co., 6601 S. Laramie Ave., Chicago 38, Ill. / Canada: Radio Speakers of Canada, Ltd., Toronto

# FOR ALL YOUR SERVICE NEEDS

## Speco Universal Replacement Kits

For all Domestic and Imported Transistor Radios and Equipment



**4-SPEAKER KIT #SPK-4**  
Each kit consists of one each of the following:  
U-260 2" U-261 2 1/4"  
U-265 2 1/2" G-208 2 3/4"  
All kit speakers are also sold individually.



**SUB MINIATURE ELECTROLYTIC KITS**  
MK-1—Master kit consists of 12 axial and 12 upright capacitors.  
AK-1—Axial kit consists of 12 asstd axial capacitors.  
UK-1—Upright kit consists of 12 asstd upright capacitors.



**SUB MINIATURE POLY-CARBONATE KIT PC-1**  
Consists of 21 Poly-Carbonate capacitors from .001 to .05 rated at 75 Volts.



**SUB MINIATURE CERAMIC-DISC CAPACITOR KIT CD-1**  
Each kit contains 35 ceramic disc capacitors from .001 to .05 rated at 25 volts.



**MINIATURE VOLUME CONTROL KIT VC-1**  
Consists of 6 miniature volume controls—3 with switches and 3 less switches at 2.5K, 5K and 10K. All controls have linear tapers.



**SUB MINIATURE RESISTOR KIT R-1**  
Contains 100 upright type RETMA color-coded resistors. 2 each of 50 assorted values. 5 ohms to 250 K. 1/20 watt



**UNIVERSAL REPLACEMENT EARPHONE KIT**  
Replaces 100% of earphones required in transistor radios and miniature tape recorders. Each earphone is individually packaged and marked. A replacement guide comes with each kit.



**MINIATURE TRANSFORMER KIT TR 1**  
Contains 2 input and 2 output transformers. Used in single or push-pull circuits.

All Speco Products Available at Your Local Distributor  
**Components Specialties, Inc.**

9 Kees Place • Merrick, L. I., N. Y.

each of which is controlled by the stage preceding it. Looking at Fig. 4—the 31.5-kc divider is a blocking oscillator which is triggered by every sixth positive-going pulse from the 189-kc master oscillator. A shaping stage gives the 189-kc output signal the correct characteristic to perform this triggering action properly.

The various black-and-white video pattern displays are developed by the chain of divider stages. For example, to create vertical bars, the 189-kc signal is used directly. It is fed to a keyer stage, turning that stage on and off some 12 times during each horizontal-scanning period. This keyed signal is fed through switch S1 to a vertical-bar shaping circuit which forms the pulse into a peaked waveshape; this vertical-bar signal is then applied to the video stage, where it can be passed on to the output circuits of the generator. Only 10 vertical lines appear on the CRT because two of the pulses are "lost" during horizontal blanking and retrace.


The horizontal-bar pattern is created by feeding a 900-cps signal into the video mixer. This signal is derived from the chain consisting of the 31.5-kc, 4500-cps, and 900-cps dividers. The 900-cps output is shaped into sharp pulses which occur 15 times during each vertical scan period; thus, on the CRT of a TV set, 15 horizontal lines will appear.

The crosshatch pattern is developed by simultaneously feeding the outputs of the vertical-bar shaper and the horizontal-bar shaper into the video mixer. This creates both vertical and horizontal bars on the CRT screen at the same time. A dot pattern is formed by incorporating a diode to eliminate the crosshatch lines, except at their junctions; the result is a presentation about 15 dots high by 10 dots wide on the CRT screen.

So the video display will be in synchronization with the sweep circuits in the set, the Model E-450 furnishes horizontal and vertical sync pulses along with the signal to the color receiver. The horizontal pulses are developed by a frequency-divider chain beginning with the 189-kc oscillator, and progressing through two other stages—the 31.5-kc and 15,750-cps dividers. The output of the 15,750-cps divider is formed into the correct shape for horizontal sync purposes, and is fed to the video-signal mixer.

The vertical sync signal follows a longer chain of dividers, progressing from the 189-kc oscillator through the 31.5-kc divider, then through the 4500-cps, 900-cps, 300-cps, and 60-cps divider stages. Each of these 6CG7 blocking oscillators is controlled by the preceding stage in the chain. The 60-cps output of the last divider is shaped into a vertical sync pulse and fed to the video mixer.

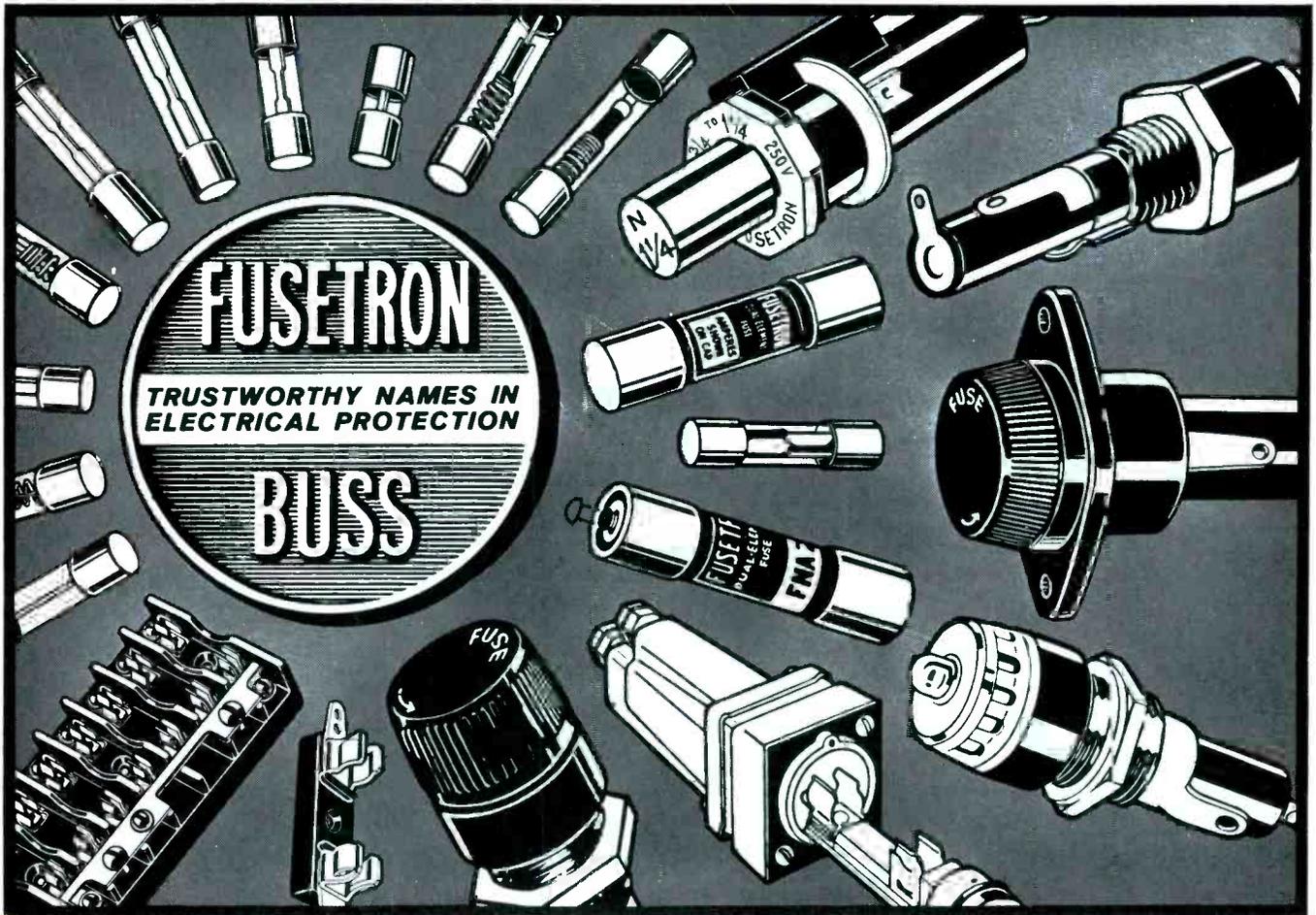For color-bar signals, the 3.56-mc oscillator is used. The shaped output from the 189-kc oscillator is mixed with the 3.56-mc chroma signal in the keyer stage. The keyer alternately turns the 3.56-mc signal on and off, causing *bursts* of the chroma signal to be fed—via S1—to the video mixer. Each burst contains ap-



## Save Time and Trouble by standardizing on BUSS Fuses—You'll find the right fuse every time...in the Complete BUSS Line!

By using BUSS as your source for fuses, you can quickly find the type and size fuse you need. The complete BUSS line of fuses includes: dual-element "slow-blowing", single-element "quick-acting", and signal or visual indicating types . . . in sizes from 1/500 amp. up—plus a companion line of fuse clips, blocks and holders.

### BUSS Trademark Is Your Assurance Of Fuses Of Unquestioned High Quality

For almost half a century, millions upon millions of BUSS fuses have operated properly under all service conditions.


To make sure this high standard of dependability is maintained . . . BUSS fuses are tested in a sensitive

electronic device. Any fuse not correctly calibrated, properly constructed and right in all physical dimensions is automatically rejected.

**Let BUSS Fuses Help Protect Your Profits . . .** The dependability of BUSS fuses helps you avoid "kicks" and complaints that the fuses you sold or installed failed to protect or blew needlessly. This safeguards you against costly adjustments and "call-backs". That's why it pays to refuse to take a chance with anything less than BUSS quality fuses.

For more information on the complete line of BUSS and FUSETRON Small Dimension Fuses and Fuse-holders, write for BUSS bulletin SFB.

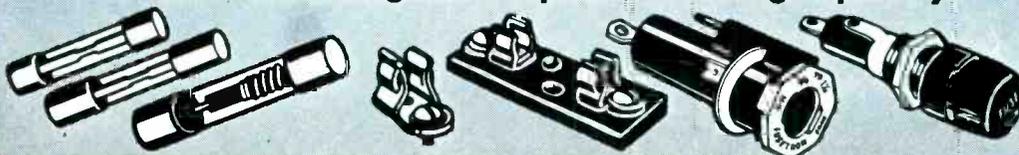**BUSS: The complete line of fuses and fuse mountings of unquestioned high quality.**



BUSSMANN MFG. DIVISION  
McGraw-Edison Co.  
St. Louis 7, Mo.





## YOU CAN BUY THAT NEW PANEL TRUCK WITH A FREE SIGNET SOUND CATALOG

Last year, several hundred electronic technicians earned enough spare-time income with their SIGNET SOUND Catalog to purchase new panel trucks...or new cars...or to make house improvements...or to take vacations. You can do the same. It's as easy as this. ■ First check your own neighborhood for prospects—places that could use top-quality, relatively low-cost sound components or complete sound packages. These you'll find in the SIGNET SOUND Series of STROMBERG-CARLSON® Communication Products, and you can sell them to churches, meeting halls, sports and social clubs, bowling alleys, taverns and restaurants. All you need to get started is the SIGNET SOUND Catalog, which is yours for the asking. ■ Selling SIGNET SOUND won't take up a lot of your time. There's no inventory for you to stock. You need no special knowledge or background to make the sale, and SIGNET SOUND is a cinch to install. Everything you need to make one extra-income sale after another is right in the catalog! Write for full details and your free SIGNET SOUND Catalog right now. You'll also receive a valuable booklet that shows how easy it is to install sound equipment. Write to General Dynamics/Electronics-Rochester, Box F, 1409 North Goodman Street, Rochester 1, N. Y.

# GENERAL DYNAMICS

**GENERAL DYNAMICS | ELECTRONICS — ROCHESTER**

# From ELECTRONIC DISTRIBUTORS EVERYWHERE!

## RESISTORS

Adjustable  
Axial Lead  
Composition  
Flat  
Lug Type

MIL Types  
Power  
Precision  
Vitreous Enameled  
Wire-Wound



## QUALITY POTS

1/2 and 2-Watt  
MIL Types  
Commercial Units  
Linear and Log



# QUALITY OHMITE COMPONENTS

## RHEOSTATS

12 1/2 to 1000 Watts  
Vitreous Enameled  
MIL Types  
Commercial



## RELAYS

Plug-In  
Enclosed  
General Purpose



## VARIABLE TRANSFORMERS

1.5, 3.5, 7.5, 20 Amps  
Cased, Uncased  
Portable  
Tandem



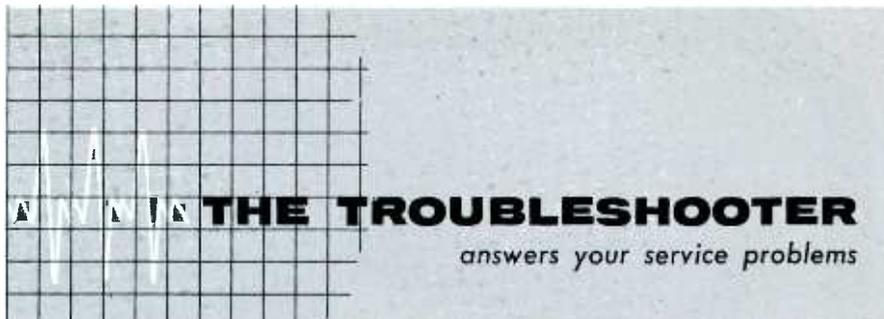
## TANTALUM CAPACITORS

Foil, Slug, and  
Wire Types



WRITE FOR STOCK CATALOG 30  
**OHMITE**  
MANUFACTURING COMPANY  
3644 Howard Street, Skokie, Illinois



### Depth Sounders

It appears I am going to become more and more involved in servicing depth finders in this small-lake area. The circuitry will not cause me much concern, but I don't understand how to test the transducers. How can I check these devices? Can I use an ohmmeter?

F & F TV & RADIO SERVICE

Bullhead City, Ariz.

*Yes, crystal-type transducers (most commonly used) can be checked with an ohmmeter. Any reading less than 2 megohms indicates leakage or a short in either the cable or the unit. If a good high reading is obtained, reverse the ohmmeter leads; you should notice a "kick" of the meter needle as the connection is made. If this deflection is absent, the cable or the transducer is open.*

*You can check operation of the entire system—transmitter, receiver, and transducer—by immersing the transducer in a water-filled tank of some sort. Some shops which do a volume of transducer work dig a hole with an auger (six feet deep will do), line it with pipe, and fill it with water. Others build a long, shallow testing tank; the suspect transducer is placed at one end, facing the other.*

*If it is absolutely necessary to test the unit without water, it can be done: Merely point the transducer at a nearby wall*

*and note the indicator. The reflection will appear at a calibration point about four times the actual distance, because sound is much slower in air than in water—1100 fps in air, as opposed to 4800 fps in water. Also, the sensitivity of the unit will be reduced when the transducer is not submerged.*


### Noisy Church

We are having trouble with a sound system in a local church—the amplifier is picking up noise. The church is heated with a thermostatically controlled hot-water system. The thermostats (in various parts of the building) control electric valves, and each time one of these valves closes or opens, a noise pops through the sound system like a gun going off. When we turn on light switches anywhere in the building, we have the same noise problem. We've tried grounding the amplifier, placing large capacitors across the AC line inside the amplifier, and installing a special AC filter at the power outlet; none of these have had any effect on the noise. The only way we can stop it is to turn down the gain on the amplifier, which makes it too weak to use. Do you have any suggestions?

CLYDE WILSON RAY

Lancaster, Ky.

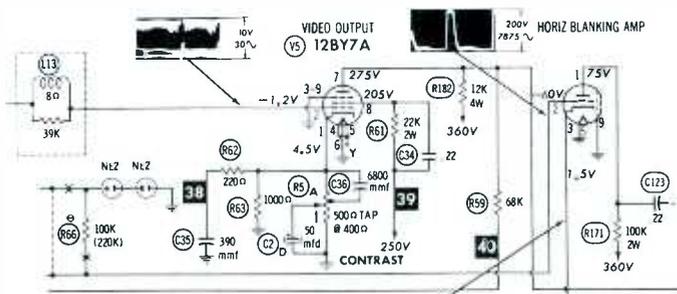*The noises you describe are not uncommon.*




### COLOR COUNTERMEASURES

Chassis: RCA CTC10

**Symptoms:** Picture intermittently loses contrast. It may jump rapidly back and forth from a weak, washed-out condition to normal operation, with lines or streaks appearing in the raster each time a change occurs. In some cases, the trouble may remain for several hours at a time.

**Tip:** Look for a defect in C2D, a 50-mfd electrolytic wired from the arm of the contrast control to chassis. The best way to check the capacitor for this particular trouble is to tap it with a screwdriver or other tool while watching the screen. If C2D is bad, the tapping will usually produce the symptoms.

# ONE UNIT for ALL C-B TESTS

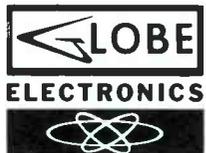

## SIGNAL OPTIMIZER 7 in 1 C-B TESTER

Be certain you're getting top performance from your C-B units and installation. Make servicing a snap. 7 pieces of test equipment in one handsome, portable, durable case.

1. **WATT METER**—measures direct transmitter power output to 10 watts, measures relative transmitter power output to 1000 watts.
2. **MODULATOR MONITOR**—tests for power robbing garbled modulation.
3. **FIELD STRENGTH METER**—measures radiated antenna power.
4. **TESTS OSCILLATOR**—to generate RF signals through use of 3rd overtone C-B Crystals.
5. **MEASURES SWR**—full power obtained only with correct standing wave ratio.
6. **TESTS HARMONICS**—fundamental frequency and overtones for correct C-B Crystals.
7. **MEASURES BASE STATION OR MOBILE ANTENNA EFFICIENCY**—adjusts directional antenna—secures optimum radiated power transfer.  
Only 8½" x 5" x 1⅞"—2 pounds.

### GC ELECTRONICS Co.

DIVISION OF TEXTRON ELECTRONICS, INC. · 400 SO. WYMAN ST. · ROCKFORD, ILL. · USA

Model No.  
65-518

# 47<sup>50</sup>

SUGGESTED  
NET

FREE  
CATALOG

- Send me a FREE copy of the latest Globe Catalog containing the most complete C-B product line available anywhere.
- SPECIAL—C-B Book—the whole C-B story—what you can and can't do—installation and testing information, noise control, tuning up gear—even a C-B lingo dictionary. Compiled by experts—regularly selling for 2.00—NOW FOR A LIMITED TIME ONLY 1.00 (Send Cash or Money Order to):  
GC ELECTRONICS CO., Dept. 16  
400 S. Wyman St., Rockford, Illinois, USA


NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_

Dept. 16
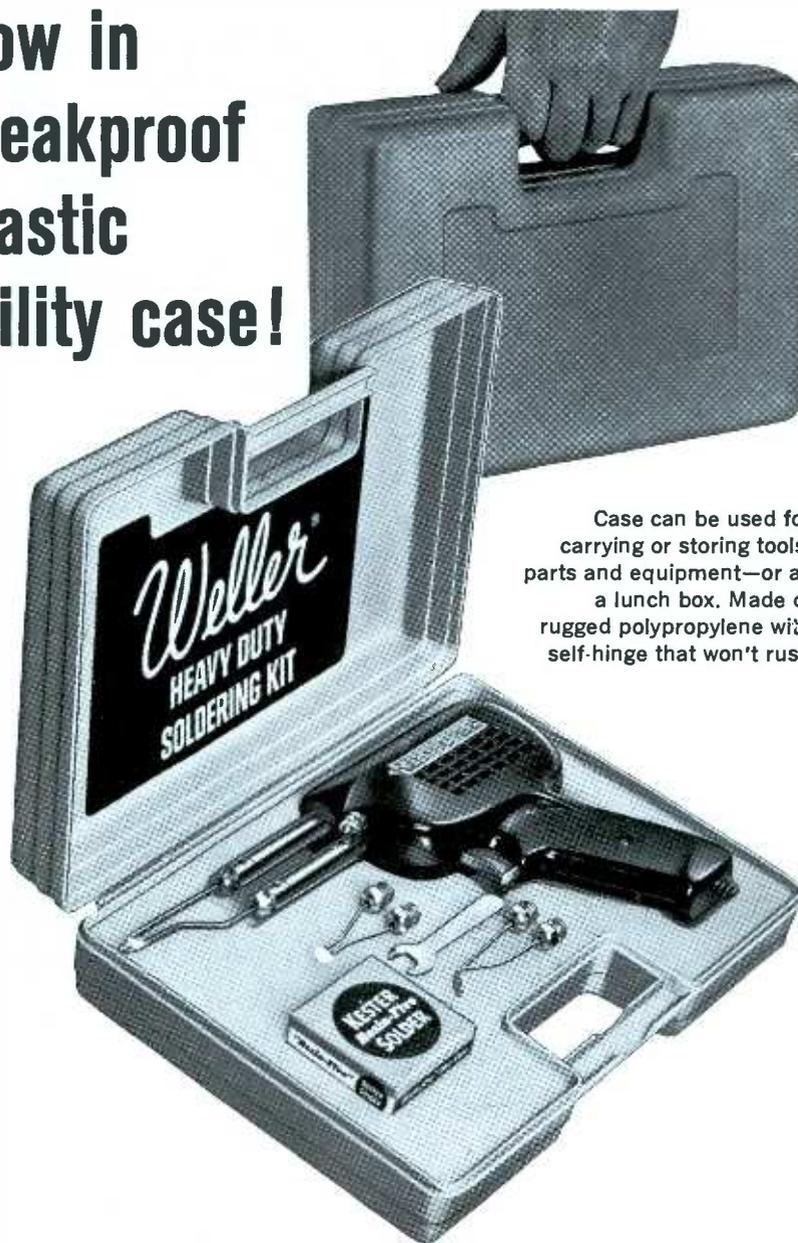
# Now in breakproof plastic utility case!



Case can be used for carrying or storing tools, parts and equipment—or as a lunch box. Made of rugged polypropylene with self-hinge that won't rust.

Weller adds greater value to the Heavy Duty Soldering Kit with a new utility case of miracle plastic that won't break. Kit features the Weller 275-watt Soldering Gun used by electronic service technicians the world over. Instant heat. Twin spot-lights. Long life, long reach tip—made of copper for superior heat transfer and iron plated for long life. Also included in this kit are smoothing tip, cutting tip, tip interchange wrench and supply of solder. Model 8250AK.

**\$14<sup>95</sup>**  
list



## Weller Hi-Speed Sabre Saw

For smooth, super-fast cutting of all kinds on speaker and record player mounting boards, cabinets, walls, etc. Makes its own starting hole for inside cuts. Never splinters or tears wood. Heavy duty, 4.8 amps. Model 88. **\$22<sup>95</sup>** list

On sale at your  
Electronic Parts Distributor

**WELLER ELECTRIC CORP. • EASTON, PA.**

mon in high-gain amplifier systems and must usually be suppressed at their source. For example, in the case of the thermostats, a .05-mfd, 600-volt capacitor across the points of each unit will usually eliminate the spark which causes noise in the amplifier system. The same thing is often needed across particularly noisy light switches.

However, the fact that the noise is so common, with almost every switch in the building affecting the problem, leads me to wonder about a couple of other possibilities: Is the building old? If so, perhaps a series of new switches (and thermostats) would solve the problem. Also, are you very sure the building electrical system is properly grounded? This last trouble can give rise to some very unusual effects, and the symptom you describe is one of them. Have a competent electrician check to make sure both sides of the service are properly returned to ground, and that the ground rod is correctly installed and effective.

Also, you can check a few points about the sound system itself. In areas where electrical noise is a problem, low-impedance microphones are best. Be sure the microphone is located as near the amplifier as possible, and properly shielded low-impedance mic cable is used. An improper impedance match between the mic and its cable, or between the cable and amplifier, can make the system unusually susceptible to noise.

## Width to Spare


A Hallicrafters Model 24T430B (covered in PHOTOFACT Folder 306-9) produces too much horizontal sweep, and the chassis has no width control. Voltages on the horizontal output tube check within tolerances. What can I do to reduce the width to normal?

J. E. CHAMBERS

Evanston, Ill.


If the screen voltage of the horizontal output tube is definitely not too high, and the drive waveform has the correct shape and amplitude, your best bet is to concentrate on the yoke.

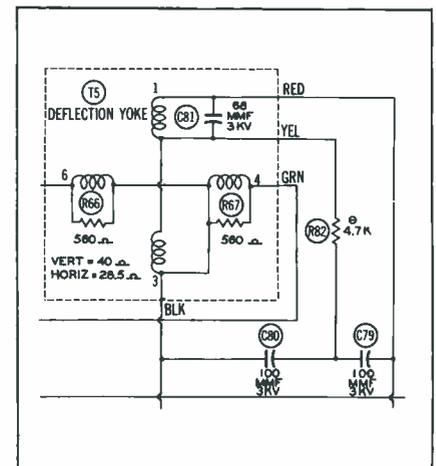You might try reducing the value of C79 and C80 in the yoke circuit, but keep their values equal so as not to upset the ringing balance set by C81.





Old

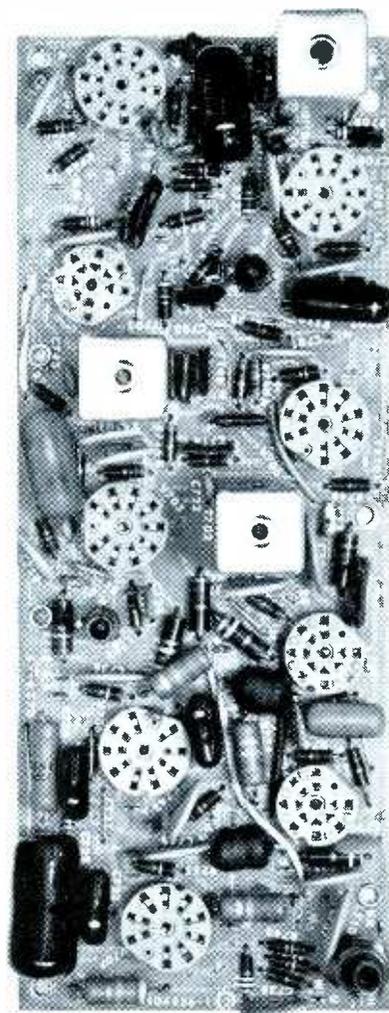

New

## Now, RCA VICTOR takes the tangle out of TV's toughest circuitry

 The advantages of the new RCA Security Sealed Chroma Circuits are plain to see. The simple fact that they're Precision Crafted Security Sealed boards tells you most of the good news . . . clean; easy to get at; "road-map" tracking, and just generally a cinch compared to their old, hand-wired counterparts.

This newly developed RCA chroma board sets many more benchmarks. For example, the color bandpass amplifier circuit

operates near Class "A," providing linear amplification of chroma signals. Color video amplifier outputs are 100% DC coupled to reduce drift in color temperature set-up.

The chroma circuit also features two new multi-grid pentode color demodulators to improve color with better matrixing. No "short cuts"—this is full-function circuitry...demodulators *plus* amplifiers for extra color brilliance and stability!

This circuit is very stable, and tube change has almost no effect on performance of matrixing.

The new Precision Crafted Security Sealed Chroma Circuit board is part of RCA's continuing program for faster, easier servicing of today's fastest-growing home entertainment medium . . . Color TV.

See Walt Disney's "Wonderful World of Color" Sunday's, NBC-TV Network.



The Most Trusted Name in Television

Tmk(s)<sup>®</sup>

**Mercury** offers you the **GREATEST VALUE**  
in **TUBE TESTERS**  
**TOP QUALITY • SPEED • ACCURACY • LOW PRICES**  
**...sell more tubes—earn more money**

a true DYNAMIC MUTUAL  
CONDUCTANCE TUBE TESTER  
for only **\$79.95**  
Net



**Model 1000**  
**MUTUAL CONDUCTANCE TUBE TESTER**

Tests for true dynamic mutual conductance (Gm)

Tests for shorts and leakage between any tube elements

Tests for gas and grid emission  
Sensitivity over 100 megohms

Tests picture tubes

Here, for the first time is a true dynamic mutual conductance tube tester to sell for less than a hundred dollars... in fact it bears a price tag of only \$79.95... truly, one of the greatest values in test equipment to come your way in a long time.

Size: 14x9½x4¾"

**Model 1100 TUBE TESTER**

... an outstanding tester—yet amazingly low in price!

Tests for shorts and leakage

Tests for dynamic cathode emission



Tests for grid leakage

Tests for gas content

**\$39.50**  
Net Size: only 10¼x8¼x3¼"

Here is the answer to technicians who seek a dependable, professional performing tube tester at a minimum cost. The Model 1100 has a range of operation that will outperform many, more expensive testers. It boasts an exclusive meter bridge circuit, found only in more expensive testers. Conveniently compact in size—a whale of a money-maker.

**ALL MERCURY Tube Testers have these features:**

- Also test the new tube types including Novars, Nuvisitors, Compactrons, new 10-pin tubes as well as battery type tubes, auto radio hybrid tubes, voltage regulators, foreign and hi-fi tubes, thyratrons and most industrial tube types.
- Check each section of multi-section tubes separately
- Handsome, two-tone long lasting etched aluminum panel
- Housed in sturdy carrying case with handsome leatherette finish.

**Model 1200**  
**MUTUAL CONDUCTANCE**  
**TUBE TESTER**

Tests for true dynamic mutual conductance (Gm)

Tests for shorts and leakage between any tube elements

Tests for gas and grid emission... sensitivity over 100 megohms

**\$119.95**  
Net

Here is a deluxe dynamic mutual conductance tube tester with a unique push-button set-up method that can be compared with the ease of selecting a record on a juke box. Push buttons provide complete flexibility in accommodating all present and new tube types and basing arrangements. The Model 1200 is the most versatile tube tester available today.



**Deluxe**  
**Dynamic Mutual Conductance Tube**  
**Tester with FAST PUSH BUTTON**  
**SETTINGS**

**TREMENDOUS**  
**VALUE!**

Also tests black and white and color picture tubes.

Also tests transistors.

Also tests batteries under load

Size: 18¼x10¼x4¾"

See your electronics parts distributor or write for complete Mercury catalog

**Mercury** **ELECTRONICS CORPORATION**  
manufacturers of quality electronic products

111 Roosevelt Avenue, Mineola, New York  
IN CANADA: Wm. Cohen, Ltd., 8900 Park Ave., Montreal

**Colors Adrift**

(Continued from page 33)

oscillator stage may be cleared of suspicion very easily; color on the screen, even though it may be out of sync, proves the 3.58 mc oscillator is running. But is it operating at the correct frequency?

One quick way to find out is to connect a clip lead from TP-1 to chassis. This just removes the phase-detector correction voltage from the control tube. (You've made this test before in horizontal-AFC circuits.) Now, try adjusting coil A1 in the control-tube plate circuit; if the shifting of hues in the color-bar pattern can be almost stopped, you may assume the oscillator to be working properly. If it is, you should concentrate your servicing efforts in the phase-detector circuit. Voltage and resistance checks should indicate the defective component.

If the color bars cannot be slowed to a "floating" condition (or even to a couple of slanted multicolor bars) by adjustment of A1, the reference oscillator and its control circuits are most likely the culprits. In this case, crystal M1 is a prime suspect; try a new one in its place. If this fails to correct the fault, the most expedient troubleshooting procedure is simply to replace L1, C2, C3, and C4 with exact-replacement components.

Here's a hint to keep in mind at this point:

If, after adjusting A1 and removing the clip lead from TP-1, you find that color-sync action has returned to normal, it's possible that aging components merely caused the oscillator to drift a slight amount. To check this, turn the receiver off and let it cool awhile; then, with the color-bar generator connected, turn the set back on and check for proper color sync. If it's good, let the set cook for a few hours, and then recheck for proper sync action—before you pronounce it cured.


**Point 7**

A waveform check here shows the reference signal which the phase detector is receiving from the demodulator transformer. It is a 3.58-mc CW signal, with only a slight trace of horizontal-sync pulse voltage mixed in. The phase of

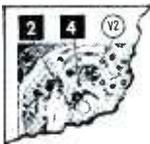
# why take hours to troubleshoot when PHOTOFACT® does it for you in minutes!

IF YOU'RE NOT NOW A PHOTOFACT LIBRARY OWNER, YOU'RE MORE THAN PAYING FOR IT IN THE TIME YOU LOSE

HERE ARE JUST A FEW OF THE DOZENS OF WAYS PHOTOFACT SAVES YOU TIME



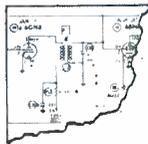**CircuiTrace®** saves countless hours of foil tracing time. This exclusive Sams system pin-points junctions and test points on schematic and printed board.



**Famous Standard Notation Schematic** saves valuable hours—always uniform, accurate, complete for every model.

COMPONENT CONNECTION	
VERTICAL OUTPUT	Original Connections
Blue Green	Red
Blue Yellow	Red
Blue White	Red
Blue Red	Blue


**Exact Terminal Connections** are indicated—no need for trial-and-error methods—a real time-saving feature.



**Field Servicing Notes** spell out locations of adjustments for speedy "in home" servicing. Saves time spent in hunting for hidden adjustments.



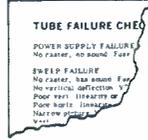
**Tube Location Guide** enables you to locate and replace proper tubes in seconds—a big time-saver on most repair jobs.




**Tube Failure Check Charts** spell out probable tubes responsible for failure—no need to waste time studying circuitry.



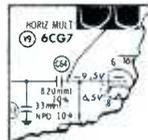
**Clear Parts Symbols** with values and associated information are shown plainly on the schematic—no time wasted in cross-reference "look-up."



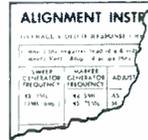
**Waveform** actual photos are shown on schematic for quick comparison of patterns on your scope. No time wasted in guesswork.



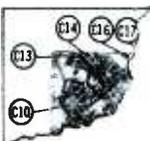
**Unique Alignment System** eliminates guessing; you get complete instructions with response curves, how to connect test equipment, proper adjustment sequence.



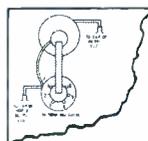
**Full Photo Coverage** of the actual equipment makes identification of all components and wiring easy—you can see everything.



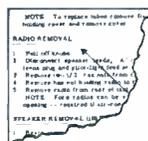**Terminal Identification** saves you time; transformer and coil terminals quickly identified by color code or basing diagram shown on schematic.



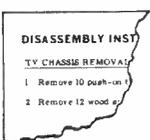
**Auto Radio Removal** instructions show you step-by-step procedure for removal of even the most complicated models—a big time-saver.



**Disassembly Instructions**, step-by-step, help you remove difficult chassis, subchassis, and assemblies in minutes.



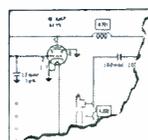**Dial Cord Stringing** instructions save you up to an hour or more of time and headaches on a single job.



**Alternate Tuner Data**—separate schematics, alignment data and parts lists are provided—no time wasted interpreting various tuner versions.

OWN THE TIME-SAVING, PROFIT-MAKING PHOTOFACT LIBRARY



**THIS EASY-BUY WAY**

The PHOTOFACT Library more than pays for itself from the first day you put it into your shop. It gives you instant time-saving help on more than 52,000 listings of TV, radio, hi-fi and other home-entertainment equipment—virtually any model made since 1946. You can own a PHOTOFACT Library this special Easy-Buy way:

- NO INTEREST
- NO CARRYING CHARGES
- ONLY \$10 DOWN
- UP TO 30 MONTHS TO PAY



You get FREE file cabinets with your PHOTOFACT Library—so you have all you need for time-saving, money-making service work right at your fingertips. Get the full PHOTOFACT Library details today.

You'll find dozens of other invaluable time-saving features in PHOTOFACT. Own the complete Library—so you can put your hands instantly on all the quick help you need for any job on your bench! Start a Standing Order Subscription today—keep up with current model output! See your Sams Distributor for full details or send coupon now.



**HOWARD W. SAMS & CO., INC.**

Howard W. Sams & Co., Inc., Dept. 7-J2  
4300 W. 62nd St., Indianapolis 6, Indiana

- Send full information on Easy-Buy Plan
- Enter my Photofact Standing Order Subscription


My Distributor is: \_\_\_\_\_

Shop Name \_\_\_\_\_

Attn. \_\_\_\_\_

Address \_\_\_\_\_

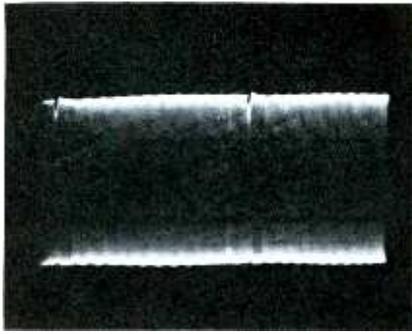City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_



this CW signal is determined by the oscillator, and the relationship between it and the incoming burst signal sets the conduction of the phase detector. Loss of this feedback signal could result in wrong colors or out-of-sync color bars.

### Summary

Color-sync servicing is no push-over, because the circuits contain close-tolerance components, and the operation of one circuit depends directly on the correct operation of another. However, you can be one step ahead if you will take a normally operating color receiver and run through the procedure outlined here, so you'll know exactly what the signals

should look like. This way, you'll be more able to locate and repair trouble in a defective color-sync stage, and you'll show more clear profit for your time. Don't wait until you *have* to fix one.



### "Spiked" Troubleshooter

The instrument pictured here — GC Electronics' Model 36-564 — is a simplified signal generator for troubleshooting transistor or tube radios. It is entirely portable, being powered by a small 6-volt battery contained within the unit.


The test signal is supplied by a two-transistor noise generator which develops a spike-shaped output — essentially a square-wave signal with

a fundamental frequency in the vicinity of 1200 cps. A switching arrangement permits adding an extra capacitor for greater differentiation of the output waveform, which sharpens the pulse and creates a greater harmonic content in the output signal. A "volume" control on the instrument has a similar effect on the signal — the shape of the pulses is altered, causing more signal to be passed through the stage being tested. The output level is constant, although it is somewhat dependent on the battery voltage; with a new battery, the unit will produce a signal of approximately 6 volts peak to peak.

Due to the choice of low or high harmonic content, the Model 36-564 is useful for signal tracing RF-IF as well as audio stages in small radios. Having no connection to the power line, it can be used on battery-powered, transformer-powered, or AC-DC equipment with equal safety. This device is handy to carry along on service calls, since it is compact, complete, and self-powered. The Model 36-564 sells for \$9.95. ▲

NO  
TEST BENCH  
IS  
COMPLETE

WITHOUT THIS  
AC TO DC  
POWER SUPPLY

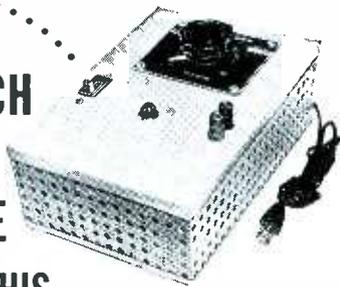

Plug this instrument into any 60 cps, 95/130 volt circuit and get a stabilized source of direct current, adjustable over a range from 0 to 45 volts DC, with current output 0/2.5 amperes, or 0-5 amperes. Filtered direct current output range 0/45 volts, current is continuously adjustable and stabilized  $\pm 1\%$  at any setting regardless of alternating current fluctuation. Voltage regulation is approximately 5% between full load and no load at full voltage setting.

This DC Power Supply instrument is ideal for use in transistor testing, circuit testing, to provide regulated voltage for light testing, eliminates the need of batteries by supplying exact DC voltage required.

Write for Bulletin 17 which gives full details and models available.

**ACME ELECTRIC CORPORATION**

949 WATER STREET

SAA 3581-2032

CUBA, N. Y.

In Canada: Acme Electric Corp. Ltd., 50 Northline Rd., Toronto, Ont.

**Acme Electric**

**Introducing an alligator clip with a "microscopic tip"!**  
*the Mueller* **MICRO-GATOR**

Here is the alligator clip you can now use where no other clip will do! On printed circuits, in tight spots and on tiny terminals too crowded for anything but its "microscopic" tip. Fully insulated right down to the nose. It offers all the speed, free-handed ease and convenience associated with other Mueller alligator clips.

Strong new type "keyed in" hinge. Traditionally snappy Mueller spring. Clinching ears for gripping wire.


Tough, Vinyl, skin-tight insulator. Lip-action tip-slot. A ringer for the popular "Mini-gator" insulator.

**INSULATORS SOLD SEPARATELY.** (Standard Red and Black colors. White, Blue, Yellow and Green also available.)


**FREE SAMPLE** of clip and insulator, on request to factory

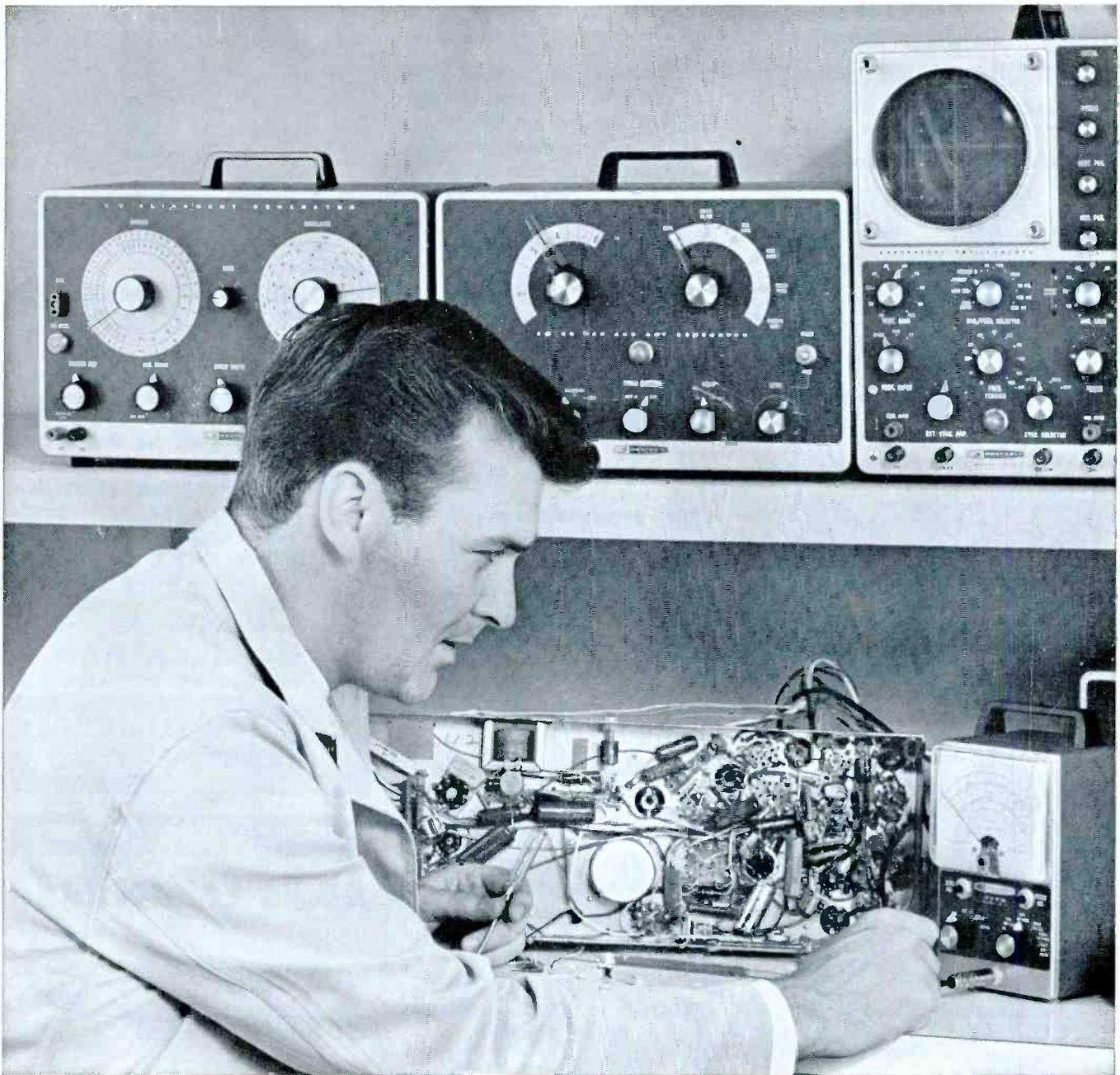**Mueller Electric Co.**

1561Y East 31st Street, Cleveland 14, Ohio



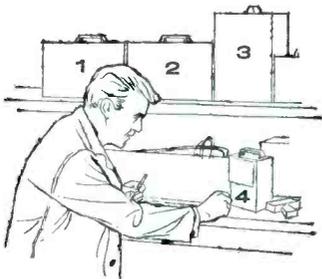**This Heathkit TV service group can be yours for only \$22 per mo.**



Only Heath, world's largest manufacturer of easy-to-build electronic kits, can offer test instruments with outstanding quality and performance, new professional styling and tremendous dollar savings! None other can match their great value. Equip your TV service bench with Heathkit Test Instruments as have so many other successful service technicians . . . enjoy far greater quality . . . at far less cost . . . by doing the easy assembly yourself!

Complete TV servicing facilities are yours with these new Heathkits: 1. Model IG-52 TV Sweep Alignment Generator, \$54.95; 2. Model IG-82 Color Bar & Dot Generator, \$64.95; 3. Model IO-12 Laboratory Oscilloscope, \$76.95; and 4. Model IM-11 Vacuum Tube Voltmeter, \$29.95. Use Heath's convenient time pay plan . . . pay only \$22 mo. while you enjoy the equipment you need now! See the complete new line of professional Heathkit test instruments in the 1963 Heathkit catalog or at your nearest Heathkit distributor.



**FREE 1963 HEATHKIT CATALOG**

If you are not already on our mailing list, fill in and mail this coupon right away to receive this new Fall & Winter edition of the world's biggest electronic kit catalog. More than 100 new electronic luxuries have been added since the last issue . . . more than 250 in all, completely described and illustrated. Send for your free copy today!



**HEATH COMPANY**

Benton Harbor 68, Michigan

Please send my FREE 100 page 1963 Heathkit Catalog

Name \_\_\_\_\_

Street \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

## SAMS BOOKS for

### PROFITABLE SERVICING

(available from your Sams Distributor)

#### TV Tube Symptoms & Troubles



Most TV troubles are caused by faulty tubes. This new Sams book shows over 150 actual photos of defective TV screens, arranged by trouble symptom (picture tube displays of picture, sync, size and linearity, raster and sound troubles). Tells you what each section of a TV set is supposed to do, what happens when it doesn't, and shows how to pinpoint troubles to specific sections and tubes. Special Tube Trouble Chart instantly relates troubles to specific tubes. No theory . . . just the practical photos and brief descriptions you need to locate most TV troubles in short order. 96 pages; \$1.50 5 1/2" x 8 1/2". No. TVT-1. Only.....

**Radio & TV Trouble Clues.** A collection of unusual "tough dog" troubles, based on actual field experiences with specific radio and TV sets. This handy reference will help you repair the tough ones more quickly and easily. 96 pages, 5 1/2" x 8 1/2". \$1.50 No. RTQ-1. Only.....

#### Bench Servicing Made Easy

Bob Middleton's new and really practical book on troubleshooting techniques. Here is a step-by-step guide to the location of defective components in any TV circuit you're likely to run across—the kind of help servicemen want but haven't found until now. Presents brand-new material based on the author's own workbench experience. Eleven big-help chapters. 160 pages; \$2.95 5 1/2" x 8 1/2". No. BSE-1. Only.....



#### Servicing TV Remote Controls

Sam Marshall helps you solve the pesky problem of servicing TV remote controls currently used with most new TV sets. Tells how the various systems work. Includes thorough analyses of transmitters, receivers, relay and motor control systems. Nine chapters include: Basic Principles of TV Remote Control Systems; Remote Control Transmitters (5 basic types); Remote Control Receivers (descriptions of all popular types). Outlines installation, adjustment, alignment and troubleshooting. 160 pages; \$2.95 5 1/2" x 8 1/2". No. REM-1. Only.....

**Rapid Printed Circuit Repair.** Describes and fully illustrates printed circuits and components used by various manufacturers; covers servicing and repair techniques; describes defects likely to be encountered. 128 pages; 5 1/2" x 8 1/2". \$1.95 No. PC-2. Only.....

#### Color TV Training Manual



A comprehensive manual prepared to train the technician in servicing Color TV receivers. Describes the science of color, the requirements and make-up of the composite color signal, color circuits, servicing procedures and many other subjects. Includes color blocks outlining the use of color test equipment. Over 300 illustrations with 40 pages in full color. 260 pages, \$6.95 8 1/2" x 11". No. TVC-1. Only.....

FREE SAMS BOOK LIST AVAILABLE

Ask Your Distributor or Write Us Direct

#### HOWARD W. SAMS & CO., INC.

4300 W. 62nd St., Indianapolis 6, Ind.  
In Canada: A. C. Simmonds & Sons, Ltd., Toronto 7

## Debugging B+

(Continued from page 24)

other electrolytics do a pretty good job of keeping the hum voltage down even though an input unit may be open. As a result, there are few telltale signs to lead us to the real trouble. A 100-mfd, 300-volt capacitor is a good size to use for checking the doubler electrolytics by substitution.

Output electrolytic C3 will not affect the DC output voltage even though it opens completely, but it will influence the ripple content and also affect decoupling between circuits on the B+ line.

#### Transformer Power Supplies

As we mentioned, a few transformer power supplies use semiconductor rectifiers and voltage-doubler circuits; the discussion above applies to these circuits as well. For tube-rectifier circuits, though, we want to consider another point or two.

Look at the circuit in Fig. 3—what would you expect the DC voltage to be at point A in a normally loaded circuit? The answer is: about 330 volts DC. This is a good rule of thumb, in case you can't find the service literature; the DC output voltage will approximate the rms voltage measured from one of the rectifier plates to ground. If the DC voltage is low, we suspect first the tube and then C1; C2, unless it becomes shorted, has no effect on the DC voltage.

#### Tracing B+ Faults

In any power supply, the output voltage is affected by the load; therefore, the B+ line must be free of leakage or shorts. If a trouble of this sort occurs in a hand-wired circuit, we can disconnect the various branches of the B+ supply line and check each for the component causing the overload. With printed circuits, however, disconnecting B+ lines indiscriminately can lead to a rather rough-looking service job; for these we need a troubleshooting method that doesn't involve too much brute force.

Fig. 4 shows a typical B+ circuit arrangement. We will use this circuit to demonstrate one method of locating the cause of an overloaded B+ line. Resistance readings are



**NEED A 110 V. A. C. OUTLET?**

**IN CAR, BOAT OR TRUCK, YOU HAVE IT WITH A**

**terado POWER INVERTER**

Actually gives you 110 volt, 60 cycle A.C. from your 6 or 12 volt D.C. battery! Plug inverter into cigarette lighter, and operate lights, electric shavers, record players, electric tools, portable TV, radios, testing equipment, etc.

See Your Electronics Parts Jobber, or Write:

Models from 15 to 300 watts, priced as low as **\$12.95 LIST**

**terado COMPANY**  
1073 RAYMOND AVE.  
ST. PAUL 8, MINN.

In Canada, ATLAS RADIO CORP. LTD. — Toronto, Ont.

#### SWITCHCRAFT AUDIO CONNECTORS

## Audio Connectors

With  
"CAPTIVE DESIGN"



INSERT SCREWS

Pat. Applied for

From Switchcraft!



Screws remain in inserts when removed for cable installation. EXCLUSIVE "GROUND TERMINALS" provide complete grounding provisions. Many other unique features in this 3-pin line.

**A3F—Female Plug—U.S.A. List—\$2.25**

**A3M—Male Plug—U.S.A. List—\$1.90**

**B3M—Male Single Hole Mount**

**Receptacle—U.S.A. List—\$2.90**

**C3M—Male Panel Mount**

**Receptacle—U.S.A. List—\$1.40**

Call Your Distributor Today!

**SWITCHCRAFT**  
INC.

5573 N. ELSTON AVE. • CHICAGO 30, ILLINOIS  
Canadian Rep: Atlas Radio Corp., Ltd.,  
50 Wingold Ave., Toronto, Ontario.



efficient voltage to overcome the "potential hill" of these rectifiers, in which case you won't encounter this possible difficulty.)

### Debugging "Stacked" B+

By "stacked" B+ circuits, we mean those in which B+ potentials are developed through voltage drops in normally operating tubes—for example: in stacked IF stages, cascade amplifiers, and circuits which derive B+ from the cathode of the audio output tube.

Fig. 5 shows a B+ circuit of the latter type wherein the tube takes the place of a large dropping resistor. The operation of this sort of circuit depends on the distribution of the various voltages. The grid must remain slightly negative with respect to the voltage expected at the cathode. In this circuit, the grid voltage is obtained at the junction of R1 and R2. Should R1 open or increase in value, the grid bias would become more negative—lowering conduction in the tube. As a

result, the "low B+" voltage at the cathode would decrease sharply.

In this type of supply circuit, a defect in the audio stage can often cause a seemingly unrelated symptom. For example, a common trouble in some color sets is a loss of AGC action. This fault has been traced several times to a grid resistor in the audio output circuit having changed value. This, in turn, lowered the B+ to the AGC keyer, causing the AGC voltage to be erratic.

Another typical case is a symptom of snow, caused by low gain in the cascade RF stage of a tuner. Grid bias for one of these "stacked" stages is nearly always developed by two fixed bleeder resistors from B+ to ground. When one of these resistors changes value, it causes one section of the tube to operate at reduced gain.

### B+ Filtering

Inadequate filtering of the B+ line is one of the most common causes of bending, jitter, tearing, and other similar instabilities. When this fault develops, the signal voltages of one circuit may get into another circuit and cause all sorts of weird troubles.

Without doubt, the oscilloscope is the most useful instrument for checking filtering on the B+ line, and its use is certainly not difficult. You don't even have to know the peak-to-peak value of the voltage, although this information is helpful at times.

When the problem is jitter or tearing, you will be most interested in whether or not the waveform you find on the B+ line shows any change as the picture content changes. If it does, there is video on the B+ line—a condition which can't be tolerated!

For "bending" problems that do not change with the content of the picture, you need to measure the peak-to-peak voltage of whatever waveform appears on the B+ line. This signal should not exceed 2 volts peak to peak, except at the input-filter electrolytic.

Now, the question might be asked: Why not just shunt the suspected B+ circuits with a good electrolytic rather than use a scope? The reason is that the sudden surge of charging the test electrolytic often heals the defective capacitor.

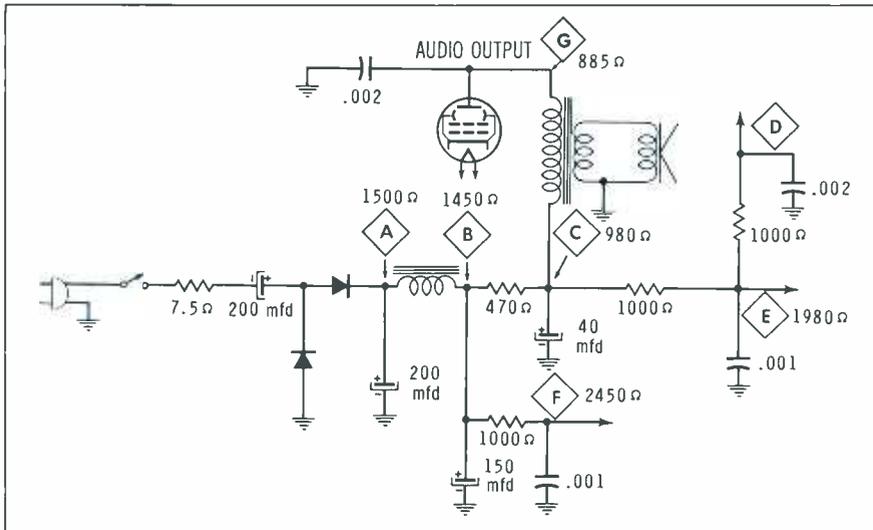


Fig. 4. Resistance method of localizing B+ shorts requires no unsoldering.

**Any of These Combinations  
PLUS 75¢ EXACT-O-SPRAY NEEDLE  
At Your Distributor for Only**

**\$1.96**

**Chem Spray**  
ELECTRONIC CHEMICAL KIT

2.71 VALUE  
\$1.96  
DEALER NET



1. TWO JETKLEAN TUNER CLEANER
2. TUNER CLEANER AND SUPER QUIK-FREEZE
3. TUNER CLEANER AND CONTROL CLEANER
4. TUNER CLEANER AND QUIKLEEN

Manufactured by

**CHEM SPRAY CORPORATION • HOUSTON, TEXAS**

unless you're using a substitution box which has an "anti-heal" test switch. If the faulty capacitor heals, you cannot really be sure you've found the trouble. And, unfortunately, a healed capacitor usually stays that way for only a limited time. If you accidentally "heal" a capacitor, you may have to keep the set for days or even weeks before the trouble will show up again. Using the scope eliminates this problem.

**Parts for B+ Circuits**

The values of electrolytics in B+

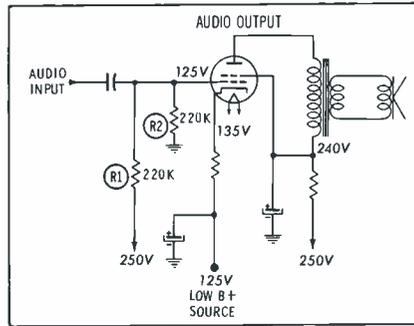


Fig. 5. Audio output tube serves as dropping resistor to develop low B+.

circuits are not usually too critical. If the voltage rating is ample, you can use a capacitor from 25% below to 100% above the original value with little noticeable difference in set performance.

Silicon rectifiers should not be used directly to replace seleniums unless you take into account the increased output voltage and the possible damage that might be done to other circuits in the set. Silicon rectifiers will sometimes "pep up" a set by increasing width, brightness and contrast, but this is somewhat like giving aspirin for fever—it cures the symptoms but not the disease! In addition, silicones require extra surge protection beyond that afforded by the fusible resistor; thus, conversion jobs usually require adding a wire-wound resistor (say, 10 to 22 ohms at 10 watts) in series with the fusible unit. Selenium rectifiers, of course, can't be used to replace silicones, since the B+ voltage would be too low.

The fusible resistor should not be changed in size from the original design; however, if you wish, you may install a slow-blow fuse and a resistor of the appropriate value and wattage in its place. Caution: Do not use only the fuse; the resistor is essential to prevent the surge damage mentioned before.

The information in this article should help you solve most B+ problems. When faced with a tough one, first be sure the supply itself is okay. If it is, then trace down any overload by means of resistance checks along the supply line. Lastly, reason out the probable cause of any abnormal voltage in a "stacked B+" system, taking into account the effects of the series tube or tubes. If you use this procedure, no B+ trouble need turn into a "tough dog" for you. ▲

**NEW**  
antenna specialists  
M-82 'Black Box'

**CB antenna amplifier**

an entirely new class of citizens band power accessory that gives you . . .

**FANTASTIC  
NEW  
PERFORMANCE  
INTO  
AND  
OUT OF  
YOUR  
PRESENT  
CB  
EQUIPMENT**



Forget everything you know about the "talk and hear" power of your present CB equipment. This remarkable new, self-powered device has changed the standards of "talk and hear" power! How? Produces a constant 100% legal power at the antenna. Result? 20 db gain (minimum) received . . . over 10 db transmit modulation gain (plus varying carrier gain) from base. Benefit! Clarity and volume never before possible at both ends. Drastic reduction of inherent mobile interference. It's like having another full turn on your volume control. Meets F.C.C. limitations, naturally.



**the antenna specialists co.**

12435 Euclid Avenue • Cleveland 6, Ohio  
Export Div., 15 Moore St., New York 4, N. Y.

**RMS ELECTRONICS, INC.**

Leader in indoor and outdoor antennas, intercoms and TV accessories, now introduces a complete line of wood wall baffles and speaker enclosures. Designed to give the best in sound reproduction and beautifully finished in Blonde, Mahogany and walnut, these units are amazingly low priced.

also available with speakers pre-mounted

**RMS WAVEBOOSTER**


*Quality Products*

**F-38K**

**DT-100**

For complete details write to  
**RMS - Dep't. "B"**  
2016 BRONXDALE AVE.  
BRONX 62, N. Y.

# NEW — from *Swing-O-Lite*

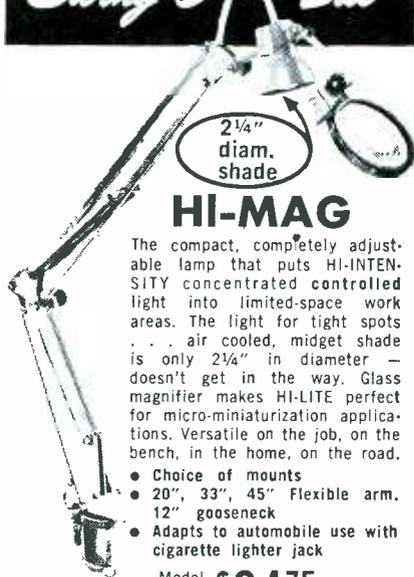

2 1/4" diam. shade

## HI-MAG

The compact, completely adjustable lamp that puts HI-INTENSITY concentrated controlled light into limited-space work areas. The light for tight spots . . . air cooled, midget shade is only 2 1/4" in diameter — doesn't get in the way. Glass magnifier makes HI-LITE perfect for micro-miniaturization applications. Versatile on the job, on the bench, in the home, on the road.

- Choice of mounts
- 20", 33", 45" Flexible arm. 12" gooseneck
- Adapts to automobile use with cigarette lighter jack

Model #HL-33C **\$2475** (without bulb) List magnifier

(as illust., 33" arm, with magnifier and bulb, \$36.00 list)

Brown, grey, or tan baked enamel finish.

## TWO OTHER GREAT SWING-O-LITE LAMPS!



## THE INSPECTOR

with built in magnifier

- Used with printed circuits, blueprints schematics, microminiatures, quality control inspection, etc.
- Shadow free fluorescent light
- 5" precision polished magnifying glass. Choice of mounts.
- 45" arm reach . . . adjusts to any position
- Exclusive convenience electric base outlet (optional)

Model M1 **\$3600** List Less Bulb

Baked enamel finish — brown, grey, or tan.

## THE SUPER ALL PURPOSE, INCANDESCENT LAMP



- Casts light over wider area
- Adjusts to any position
- Exclusive "Cool Aid" shade

Model SS-45  
45" arm reach

**\$2095** List Less Bulb

Brown, grey, or tan baked enamel finish. Choice of mounts.

It's SWING-O-LITE . . . where good lighting makes the big difference.

Write for free illustrated literature on the full line of lamps. UL seal on components.

Distributorships open in selected areas.

**Swing-O-Lite** INC.  
13 MOONACHIE ROAD HACKENSACK, N. J.

## Voltmeters

(Continued from page 29)

### VTVM Calibration

There is a great deal of similarity in techniques for calibrating the VOM and VTVM. The major difference is that the VTVM contains internal controls which can be adjusted to correct calibration errors. Also, the VTVM rarely has current scales. The general approach for setting up VTVM internal controls (which may or may not be accessible from outside the cabinet) can be followed by referring to Fig. 4.

The mechanical-zero set screw on the front panel is adjusted before turning the instrument on. Then, after sufficient warm-up time, the selector switch is rotated to DC+ for DC voltage calibration with a battery. The internal DC CALIBRATE control is turned until the needle reads the exact voltage of the calibrating battery. In Fig. 4, this is a 1.35-volt mercury cell, and the meter range is 1.5 volts. The meter should read accurately throughout its ranges after this step; otherwise, it will be necessary to resort to the technique used with the VOM—a calibration chart.

Next is the ohmmeter check. The calibrating controls for this are the two front-panel knobs for zeroing each end of the ohms scale. These are the same controls which are adjusted each time the meter is used for ohmmeter service. The precision resistors provide a calibration check and the information required to make up a correction chart, if needed.

The remaining internal controls have to do with the AC calibration of the meter. The adjustment pro-

cedure involves completely removing the AC test lead from the meter (to avoid stray pickup) and setting the range switch to its lowest scale (usually 1.5 volts, or thereabouts). The function switch is rotated from AC through DC- and DC+. Any tendency of the meter pointer to move off zero should be countered by adjusting the internal AC BALANCE control. After the needle remains stable, the AC test lead is reconnected and the VTVM set to measure some known AC voltage. The internal AC CALIBRATE control is adjusted to bring the needle to read the applied calibrating voltage.

An accurate AC voltage is not easily secured. However, this lack is not necessarily serious, for the intended accuracy of the instrument on AC is usually less than that for DC, due to the characteristics of the rectifiers used. If the meter is rated at 3% for DC, the AC tolerance may be 5%. This lesser accuracy for AC ranges is not a major disadvantage, since tolerances for AC measurements are not critical in most service work. Unless you are willing to invest in special calibrating devices, the AC section of the instrument may be calibrated against the power line for a nominal 117-volt reading. The internal AC CALIBRATE control should bring the meter needle to the correct point on the 150-volt scale.

The above steps are about all that's necessary to keep your VOM or VTVM reliable and accurate. In a later article, we'll consider calibration techniques which can be applied to other basic test instruments—the audio oscillator, oscilloscope, signal generator, and sweep generator. ▲

## PRECISION TUNER SERVICE

P. O. BOX 272

1200 S. WALNUT ST.

BLOOMINGTON, IND.

EDISON 99653

**7.50**  
V or U  
COMBO PLUS  
9.95 POSTAGE

6 MONTH WARRANTY



All Types T.V. Tuners Cleaned, Repaired and Aligned to Factory Specifications. Same day in shop service on most Tuners. Price Includes Minor Parts, Major Parts at Cost Price. We use Original Parts if possible. State Make Model and Enclose all Parts and Tubes. Pack Well and Insure.

ALSO HAVE LARGE STOCK OF EXCHANGE TUNERS, WRITE FOR TYPES AND PRICES.

## Generator Sweeps

(Continued from page 31)

"You see, one real trouble is that most of us have wide-band scopes these days, as we should. If you have a scope that can be switched to narrow-band operation, it will not pass higher-frequency heterodyne products, thus leaving only low frequencies grouped neatly around the zero point to give you a neat marker.

"My scope doesn't have a narrow-band position, so I shunt this .01-mfd capacitor across the vertical input to kill unwanted band-

width when I'm sweeping. Too high a value will make the marker too small to see; too low a value will leave too much smear. Incidentally, this trick will help keep out those spurious markers that sometimes crop up."

### More Than One Marker

"That's all right," Gene said, feeling a lot friendlier toward the whole business of sweep alignment. "But your mention of spurious markers brings up another point. They didn't really become a problem for me until I tried to use a simultaneous display of multiple markers. Then everything began beating with everything else, and I didn't know what I had. How do you get around that?"

"By not using multiple markers!" Alec countered. "I'm usually content to use one marker at a time, and tune the CW generator to run the marker over to any point I'm interested in at the moment. I can't imagine when I'd ever want more than two markers at the same time, and getting two is no problem at all—even though one may be invisible."

Before Gene could protest, Alec waved him to silence. He then adjusted the positioning controls so the marker on the curve fell right under the vertical center line on the calibrated grid over the face of the scope CRT. He then turned off the marker generator.

"That center line," he stated, "is now your marker for that frequency. As long as you don't change the sweep-width or phase-control settings on the generator—or the horizontal-gain or positioning controls on the scope—it will stay put. In-

**PROFESSIONAL**  
technicians

use

*Dave Rice's*

**OFFICIAL**  
**ORDER BOOKS**

for every

**TV-RADIO**

service

call

This is the businesslike approach to service record keeping. Triplicate forms serve as order form, invoice and office record, with spaces for complete information on every job. Separate listings for receiving tubes, pix tube, parts, serial numbers, labor and tax charges, signatures, etc. 75c a book, \$6.50 for dust-proof box of 10. In stock at your distributor.

\*\*\*\*\*

## FREE

Write for your free folder describing Dave Rice's OFFICIAL ORDER BOOKS, including an actual size sample copy of the handy order form.

**ELECTRONIC**  
PUBLISHING CO., INC.  
133 N. JEFFERSON ST.  
CHICAGO 6, ILLINOIS



**MY BACK IS KILLING ME!**  
I'VE LUGGED THIS STUFF ALL DAY  
AND STILL HAVE TWO CALL-  
BACKS TO GO! MY TUBE CHECKER  
LIED TO ME AND I  
RAN OUT OF  
TUBES FOR  
SUBSTITUTION!



**WISE UP OLD BUDDY! GET YOURSELF A MIGHTY MITE... NEVER LETS YOU DOWN AND IS AS EASY TO CARRY AS YOUR LUNCH BOX! I MADE 10 CALLS ALREADY AND SOLD FIVE EXTRA TUBES I WOULDN'T HAVE CAUGHT BY SUBSTITUTION!**



**"Finds 'em Fast... Checks 'em All!" SENCORE MIGHTY MITE**  
NOW CHECKS OVER 2,000 TUBES TUBE CHECKER



**RCA Sound Products**  
open new markets—  
bring you new business  
—increase your profits

There's a lot of money to be made in institutional sound systems for public address, paging, piped-in music, etc.

Now it's easier than ever to capture a profitable share. Complete sound systems—matched microphones, amplifiers, and speakers—all are available from a single source: RCA, the brand name that's easy to sell. No more time-consuming matching of components of different brands.

RCA sound products range from low-cost 12-watt paging networks to full-volume, auditorium-filling 100-watt installations... one for every customer requirement.

RCA sound components are available through your Authorized RCA Sound Products Distributor. If he is temporarily out of stock, please fill out and send us the coupon below.

RCA ELECTRON TUBE DIVISION  
Harrison, N. J.



The Most Trusted Name in Sound

Special Products Department  
RCA ELECTRON TUBE DIVISION  
Harrison, N. J.

Please send detailed information on:

- Complete line of RCA sound products  
 RCA microphones  RCA PA Amplifiers  
 RCA Speakers

Name \_\_\_\_\_ Title \_\_\_\_\_

Company \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_

creasing the sweep-generator amplitude or the scope's vertical gain will not budge it." He then reset the marker generator to produce a pip at another alignment frequency on the curve as recommended by the receiver manufacturer. "You now have two markers. No interaction, no confusion."

"You know," Gene said, "this has all been pretty impressive. It intrigues me enough that I'd like to give a sweep generator another try. I'm not sure the one in our shop will work the same way, but it's something to start on. I have to prove to myself that a sweep setup is worth the time it takes. To isolate troubles in the IF strip, I'd have to make a stage-by-stage check. In that case, I couldn't use the output of the video detector as an input to the scope, so I'd have to add a demodulator probe to the setup. Besides, I'd have a lot of connections to change around after checking every single stage."

"You know," said Alec, "I hate to deflate you, but you're not quite right about that. You *can* keep on using the detector in the set, so at

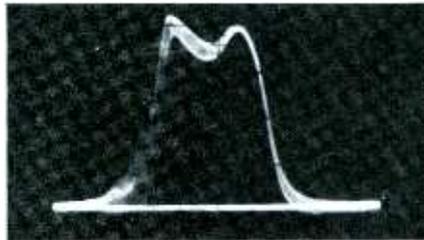


Fig. 5. Without capacitor, markers on wide-band scope may spread out.

least you won't have to switch the scope connection. That makes things a lot easier. Watch this—I'm going to feed sweep into the grid of the third IF through a capacitor—.001 is fine. Another capacitor, from the grid of the second IF to ground, shorts out stray signals and gives a cleaner curve. The response here depends mostly on the tuning of the last IF can. This double-tuned transformer gives a curve with twin peaks; here's a drawing in the service notes that shows the correct shape. The scope trace looks practically identical to it, and running a marker over the curve tells us the slopes occur at the right frequencies. So far, so good.

"Now I remove my bypass capacitor and move it to the grid of

the first IF; this allows me to feed the sweep signal into the grid of the second stage. Starting with this step, I'm also going to clamp the AGC line with a bias box, so I can control the effect of the grid bias on the curve. With the detector output now being influenced by the tuning of the second IF can, I can now set the marker to the resonant frequency of this single-tuned coil and peak the curve at this frequency. The scope shows me how the over-all curve is shaping up, too. If I need to touch up the previous adjustments, I can do this as I go along. By the time I've worked back to the input of the IF strip, the curve is all set. I don't know of any other method that's quicker or more reliable.

"If anything is interfering with proper tuning, it shows up right away. On this job I just finished, the curve broke up into wild oscillations as soon as I injected the signal ahead of the guilty stage. Sometimes the trouble won't be so obvious; perhaps you'll see just one high peak at a spot on the curve where it doesn't belong, or maybe one slug

**SAVES**  
your back...  
**SAVES**  
your time...

**YEATS** **SHORTY DOLLY**  
for RADIO and TV

just 47 inches high for STATION WAGONS and PANEL PICK-UPS

Designed for TV, radio and appliance men who make deliveries by station wagon or panel truck... the short 47 inch length saves detaching the set for loading into the "wagon" or pick up. Tough, yet featherlight aluminum alloy frame has padded felt front, fast (30 second) web strap ratchet fastener and two endless rubber belt step glides. New folding platform attachment, at left, saves your back handling large TV chassis or table models. Call your YEATS dealer or write direct today!

**FOLDING PLATFORM**  
15 1/4" x 24 1/2" top.  
Snaps on or off.  
(Platform only)  
\$11.95

**YEATS**  
Model No. 5  
Height 47"  
Weight 32 lbs.

**"Everlast" COVER AND PADS**

YEATS semi fitted covers are made of tough water repellent fabric with adjustable web straps and soft, scratchless white flannel liners. All shapes and sizes — Write

**FURNITURE PAD**

**TV COVER**

**YEATS** **APPLIANCE DOLLY SALES COMPANY**  
2103 N. 12th STREET MILWAUKEE, WISCONSIN

**LEARN FM 2-WAY RADIO SERVICING AT HOME**

- Earn More Money
- Build a Better Future

Advancement and increased earnings are waiting for you in the expanding communications field. The Motorola Training Institute's home study course in FM 2-way radio servicing can enable you to take advantage of these profitable opportunities now. Learn all about servicing the new transistorized equipment... learn advanced techniques for handling complex service problems easier and faster.

In addition to this wealth of practical application knowledge, you will also be preparing yourself for your 2nd Class FCC Radio-telephone License. For full details, send coupon today. There is no obligation and no salesman will call.

**MOTOROLA TRAINING INSTITUTE**  
4545 West Augusta Boulevard • Chicago 51, Illinois • Dept. ACX235

Please send me full details on the Motorola Training Institute's planned home study program on FM 2-Way Radio Servicing.

I now hold \_\_\_\_\_ FCC License.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_


New **BERNS** Perfect Pin Crimper

**Picture-Tube Repair Tool**

Also for—5U4, 6SN7, 6BQ6, etc.

Eliminates that hard soldering job

only \$1.25 each

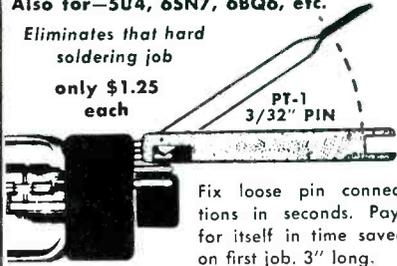

Fix loose pin connections in seconds. Pays for itself in time saved on first job. 3" long.

Patented


Intermittent operation of picture tubes due to defective solder connections easily corrected. Provides solid electrical connections, can also be used as channel-selector wrench and screwdriver. Pin keeps its original form. A 3-in-1 tool.

**3 MODELS**

**ELIMINATE SOLDERING**

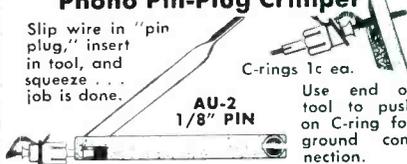**Makes Solid Electrical Connections Phono Pin-Plug Crimper**

Slip wire in "pin plug," insert in tool, and squeeze... job is done.



C-rings 1c ea. Use end of tool to push on C-ring for ground connection.

Ant. plugs, hi-fi, multiple plugs, public address, radio and TV tubes, radar, speakers, and loop connections. Many, many more uses.

**Model LC-3 for 5/32" pin diameter**

At your parts distributor or write us



Mfg. Co.  
9853 Chalmers,  
Detroit 13, Mich.



**INJECTORALL**

THE NEEDLE DOES THE JOB!



**TUNER CLEANER AND LUBRICANT with... INJECTOR NEEDLE**

The leak-proof steel Injectorall Needle lubricates where you need it... you can reach hard-to-get at Wafers without pulling Tuners apart, or even removing Chassis.

The **BEST CLEANER** on the market today!

**INJECTORALL CO.** Brooklyn 14, New York



Fig. 6. Pip is produced by heterodyning between the sweep and marker signals.

will fail to affect the curve. At other times, you'll have to back off on the AGC bias to make the trouble appear.

"Even so, you can sure save trouble by checking the IF curve. The other day, I had a case where a do-it-yourself whiz kid had knocked out one IF can, producing oscillation. He was too embarrassed to tell me what he had done. A turn of the alignment adjustment for that one stage took care of the problem. Later, I got a full confession from the owner.

"And that isn't all. I can show you a lot of other tricks. You can do a lot on an ordinary broadcast radio with a sweep generator if it sweeps down low enough, as this one does. But the main thing is that you're ready to reconsider the sweep method. We'll get together on this some other time. Right now, you'd better get back to your own shop before your boss thinks you've quit."

"Gee, that's right," Gene said, startled. He grabbed the package he had come for and took off, saying, "In the meantime, I'm going to try some of the stuff you showed me and let you know how I make out." Alec waved. ▲



"He's about got it. Start the fire."

**DEALERS HAVE BEEN ASKING ABOUT IT FOR YEARS...**

**NOW... you can handle tape head replacements quickly... easily... profitably!**

**MAKE BIG PROFITS WITH**

*Nortronics*

For years dealers have asked for an accurate, simplified method for handling the replacement of worn tape heads. NORTRONICS, supplier of original equipment heads to the top manufacturers who make more than 75% of the nation's tape recorders, has introduced a tape head replacement program which solves this problem *quickly, easily, and profitably!*

NORTRONICS offers the only tape head replacement program which is complete in all respects... heads are matched electrically and mechanically for more than 250 models of popular recorders... exclusive "Quik-Kit" mounting hardware simplifies installation and vastly increases flexibility of inventory... electrical components included when required... detailed drawings and instructions make work go faster... easier... giving more profit per job!

You can get into this profitable market NOW! Minimum, fast-moving stock required... and profits are high for both distributor and dealer!

Extensive national consumer advertising and publicity campaign is now building demand. NORTRONICS provides you with point-of-sale and counter displays, window streamers, consumer booklets and sales ammunition. Powerful packaging is designed to boost "impulse" sales; helps to move replacement heads fast!

Ask your distributor today about this new NORTRONICS tape head replacement program or write: Thor Johnson Distributor Sales Manager.

**MOST COMPLETE LINE OF CONVERSION KITS**

In addition, NORTRONICS provides the most complete line of kits for converting monophonic and 2 track stereo to 4 track stereo. Boosts sales of accessory equipment for completing stereo systems. Complete Jobber and Dealer information available—write today!



"Music Sounds Best on Tape — Tape Sounds Best on Nortronic Heads"

*Nortronics*

8119 West 10th Ave., North Minneapolis 27, Minnesota.

# Only 37¢ per watt output DC Power Supply

Unbeatable Performance and Price



D-612T... \$59<sup>95</sup>

► **Look at these exclusive features...**

- Lowest price per watt output.
- Full 10 ampere rating on V-12 volt range.
- Surplus power on 0-16 volt range.
- Full year warranty.
- Superior filtering over entire output.
- Large, easy-to-read plastic meters.
- Heavy overload capacity.

► **Compare with others...**

Brand	Voltage Output	Ampere Cont.	Output Interm.	Meters	Price/Watt Output**	Warranty	Terminals
EPL	0-8	10	20*	Large, clear plastic	\$.37	1 Year	Insulated binding posts
	0-16	10	20*				
A	6	10		Metal	.69	90 Days	Stud and wing nuts
	12	6					
C	0-8	10	20	Metal	.62	90 Days	Stud and wing nuts
	0-16	6	12				
E	0-8	10	20	Metal	.50	90 Days	Insulated binding posts
	0-16	6	10				
M	0-8	10	20	Metal	.62	1 Year	Stud and wing nuts
	0-16	6	14				
P	0-8	10	20	Metal	.68	90 Days	Metal binding posts
	0-16	6	12				

\*Best of all for operating signal seekers! \*\*Based on maximum continuous ratings.

17 Others from 6 to 125 VDC from \$19.95 up

Stocked at Your Electronic Distributor

FREE NEW CATALOG PS-562 on complete line



## ELECTRO PRODUCTS LABORATORIES

6125-T Howard, Chicago 48 (Niles), Ill.  
Phone: 647-6125

Canada: Atlas Radio Ltd., Toronto

Since 1936...Pioneers in Low Voltage DC Power Supplies

# PRODUCT report

For further information on any of the following items, circle the associated number on the Catalog & Literature Card.

### Replacement Diodes (43R)

300 diodes are contained in an assortment released by **Semiconics Corp.** More than 125 popular diodes can be replaced by the assortment, which is grouped into four basic types. A replacement chart is included with each display, listing the most popular diodes used in television and FM/AM radio.



The complete assortment, packed in a 6½" wide x 6½" deep x 4" high plastic display-storage case, sells for \$48.00.

### Tape Recorder (44R)

**NuTone's** new stereo tape recorder Model 2405 is built into the wall and matches the company's other built-in hi-fi components. Easily removed if a portable tape recorder is desired, the unit features two VU meters for accurate setting of recording levels and individual control of both record and playback channels. List price of the recorder, which will copy stereo tapes, is \$349.50.




### Inverter (45R)

A large-capacity unit has been added to **Terado's** line of power inverters. The "Dual Continental" Model 50-202 has a capacity of 550 to 600 watts, and allows operation of such equipment as drill presses, cash registers, and large appliances from a 12-volt car or truck battery. A remote control unit contains a variable-AC output switch and a signal light. The dealer net price of this transistorized inverter is \$232.68.
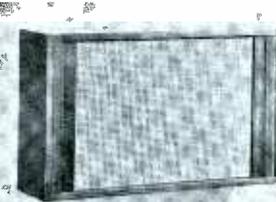
### Bookshelf Enclosures (46R)

An 8" woofer and a 3½" tweeter are contained in a new bookshelf system from **Utah.** Thinner than most rows of books, it can be used on a shelf, mantle, or table, or even hung on a wall. Keyhole slots in the back cover permit either vertical or horizontal mounting. The walnut-veneered surfaces of the "Sorcerer" Model SH4-W have a low-gloss oiled finish. An unfinished hardwood version is also available. Overall size of the unit, which will handle 12 watts of audio power, is 12" x 20" x 5".



### Loading Coils (47R)

A new line of epoxy-encapsulated loading coils for Citizens-band use is available from **Creative Products.** The LCF series permits owners of CB equipment to use shorter antennas and obtain increased efficiency. LCF-3 is used for antennas 96" and 102" in length, while Model LCF-4 is for those 92" long. The coils measure 1 15/16" in length by 1 3/16" in diameter and have 3/8-24 threads. A 3/4"-long mounting stud is also supplied.



### Transistorized CB (48R)



Receiver fine-tuning is provided for in the "Commaire" ED-276 transistorized Citizens-band transceiver manufactured by **Vocaline**. Other features of the unit include a signal-control squelch and RF gain, double-conversion receiver, and a three-stage AGC circuit. The ED-276 uses 22 transistors, 8 diodes,

and 3 tubes, and measures 5 3/8" high by 9 3/8" deep.

### Tube Tester (49R)



Two significant changes have been incorporated in all new **Sencore** Model TC114 "Mighty Mite" tube testers. An improved D'Arsonval meter is designed to provide increased reliability and damping. A large quick-setup chart, cemented inside the removable cover, eliminates the need to refer to the regular setup booklet for most-often-used tube types. Price of the Model TC114 is \$74.50 net.

### Stereo Attenuators (50R)

10 watts of audio can be handled by a new line of wirewound stereo attenuators by **Centralab**. The units, designed for installation in standard junction or switch boxes, are approximately half the depth of conventional four-section stereo L-pads. Measuring 1 1/8" in diameter and 1 5/32" deep, these attenuators feature anti-backlash construction and come with a gold anodized dial plate and a black set-screw knob.

### Heat-Sink Clips (51R)



Intended to protect semiconductors during soldering, **Aytron's** heat-sink clips (Part No. A1942) are made of aluminum. These clips fit around the lead between the semiconductor and the joint to be soldered, to absorb and dissipate the heat. Designed for use on any electronic equipment, the clips are spring-loaded, and are easily attached and detached. Price is \$19.80 per 100.

### TV/FM Couplers (52R)




No stripping, splicing, or soldering is necessary to install the "Transceptor" manufactured by **Aerogap Corp.** This two-set coupler snaps around the line and electromagnetically couples the signal from the main antenna line to the tap line. Insertion loss is only 1/2 db for low and 1/4 db for high channels. Useful for black-and-white TV, FM, and/or stereo FM, the device sells for \$2.98.

### Tab Twister (53R)



Quick twisting of tabs on electrolytic capacitors is easy with a new service aid from **General Electric**. Called a "Capacitor Tab Adjuster," the tool looks like a screwdriver, but has a slotted end instead of a blade. The slot fits over the capacitor mounting tabs, and a quick twist makes an easy job of removing and installing cantype capacitors. Price of the tool is \$1.00.
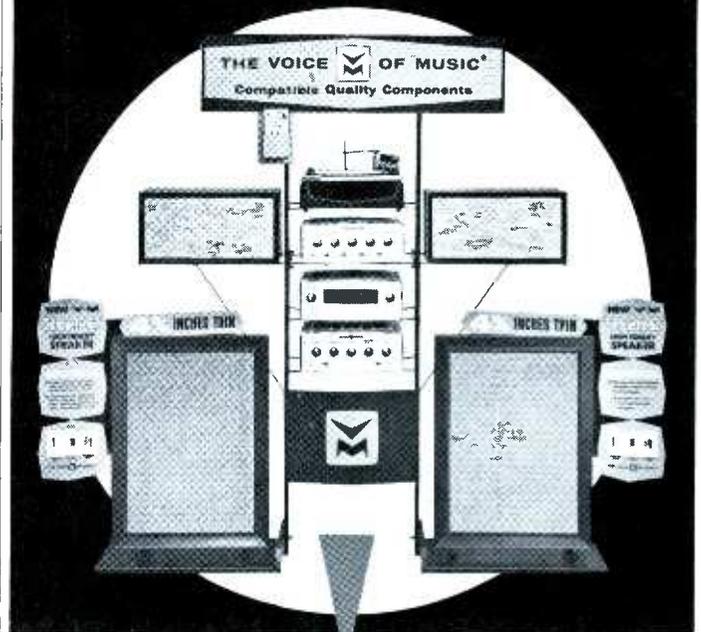
## ADD NEW PROFIT TO YOUR HI-FI COMPONENTS BUSINESS THE EASY V•M WAY!



- Priced to attract *new* customers, this complete line of quality components is effectively displayed and demonstrated in only 5 square feet.
- Convenient one-source buying . . . backed by V•M's national network of Service Centers.



The store display fixture is complete with literature dispenser and the "Silhouette 62" speaker feature posters. It actually displays nine V•M component products!



High-Fidelity FM Stereo, FM, AM Component Radio Tuner Model 1465.



'Stere-O-Matic'® 4-Speed Automatic Record Changer Model 1571 11" turntable. Automatic Manual-Play, Extra-long, dynamically balanced, non-resonant Tone Arm. Diamond Needle. Shadowlite stylus pressure.



Precision-Built AC Stereo Amplifier Model 1448. 40 watts (peak); 20 watts per channel. Frequency response, 40-25,000 cps.



Changer Base Model 1438. For 'Stere-O-Matic'® Changers. Pre-wired receptacles.



"Silhouette 62" High-Fidelity Component Speaker System. Three speakers: 10" woofer, 6" mid-range, 3.5" tweeter. Frequency response, 30-16,000 cps.



Stereophonic High-Fidelity Component Amplifier Model 1428. 60 watts (peak); 30 watts per channel. Frequency response, 20-30,000 cps.



High-Fidelity Component Speaker Model 32. Three speakers: Two 6" and one 3". Frequency response 60-12,000 cps.

YOUR V•M DISTRIBUTOR IS READY NOW TO GIVE YOU ALL THE DETAILS AND POINT OUT THE MANY ADVANTAGES OF THIS NEW V•M COMPONENTS LINE. CALL HIM TODAY!



V•M CORPORATION • BENTON HARBOR, MICHIGAN

KNOWN FOR THE FINEST IN RECORD CHANGERS, PHONOGRAPHS AND TAPE RECORDERS

September, 1962

Acme Electric Corp.	86
Aerogap Corp	47
Amperex Electronic Corp.	37
Anchor Electronic Products— Div. of Antronic Corp.	56
Antenna Specialists Co., The	91
Arco Electronics, Inc.	66
Astatic Corp.	72
Atlas Sound Corp.	78
ATR Electronics, Inc.	14
B & K Mfg. Co., Div. of Dynascan Corp.	16-17, 53
Berns Mfg. Co., The	95
Bussmann Mfg. Co.	77
Castle TV Tuner Service	59
Centralab, A Div. of Globe-Union, Inc.	18
Champion DeArment Tool Co.	54
Chem Spray Corp.	90
Chemtronics, Inc.	72
Cine-Sonic Sound, Inc.	46
Clarostat Mfg. Co., Inc.	73
Components Specialties Co.	76
Cornell-Dubilier Electric Corp.	71
EICO Electronic Instrument Co., Inc.	60
Electro Products Laboratories	96
Electro-Voice, Inc.	62
Electronic Publishing Co.	93
Emerson Radio (Granco Div.)	64
Fisher Radio Corp.	56
G-C Electronics	81
General Dynamics/Electronics—Rochester Heath Co.	79
Injectoral Co.	95
I.T.T. Distributor Products Div.	25, 51
Jackson Electrical Instrument Co.	1-2, 98
Jensen Mfg. Co.	75
Jerrold Corp.	Cover 2
JFD Electronics Corp.	15
Johnson Co., E. F.	64
Los Angeles Tuner Exchange	54
Littelfuse, Inc.	Cover 4
Mallory & Co., Inc., P. R.	63
Mercury Electronics Corp.	84
Merit Coil & Transformer Corp.	52
Minnesota Mining & Mfg. Co.	57
Motorola Training Institute	94
Mueller Electric Co.	86
Multicore Sales Corp.	78
Nortronics Co., Inc., The	95
Ohmite Mfg. Co.	80
Philco Corp.— Parts and Service Operations	26-27
Precision Apparatus Co., Inc.	39, 48-49
Precision Tuner Service	92
Quam-Nichols Co.	19
RCA Electron Tube Div.	65, Cover 3
RCA Industrial Electronic Products	93
RCA Sales Corp.	83
RMS Electronics, Inc.	91
Rider, John F., Publisher	40
Sams & Co., Inc., Howard W.	46, 85, 88
Sarkes Tarzian Inc., Tuner Division	74
Tuner Service	23
SENCORE, Inc.	41, 43, 45, 93
Seco Electronics, Inc.	68
Sonotone Corp.	89
Sprague Products Co.	12
Standard Kollsman Industries, Inc.	11
Swing-O-Lite, Inc.	92
Switchcraft, Inc.	88
Sylvania Electric Products, Inc.	55
Tenna Corp.	61
Terado Co.	88
Tung-Sol Electric, Inc.	69
Ungar Electric Tools	67
Utah Electronics Corp.	42
V-M Corp.	97
Weller Electric Co.	82
Winegard Co.	20-21
Yeats Appliance Dolly Sales Co.	94

Latest Jackson Tube Test Data

Tube Type	MODEL 648	MODEL 649	MODEL 650	MODEL 651	MODEL 652	MODEL 653	MODEL 654	MODEL 655
	W	A	B	C	D	E	F	G
6X4	12	12	12	12	12	12	12	12
6X5	12	12	12	12	12	12	12	12
6X6	12	12	12	12	12	12	12	12
6X100	12	12	12	12	12	12	12	12

ANTENNAS & ACCESSORIES

- 1R. COMMUNICATORS, INC. — 16-page guide containing information on master-antenna system installations for homes, showrooms, apartment houses, and motels.
- 2R. CUSH CRAFT—8-page catalog (No. 62) describing complete line of amateur communications antennas; both UHF and VHF types included.
- 3R. GAM — Catalog sheet giving specifications on miniaturized TG-2-R VHF mobile antenna designed to mount on top of vehicle or in other restricted spaces.
- 4R. JFD—Descriptive and promotional literature plus sales aids for new Transistennas; also complete set of specifications for outdoor and indoor TV antennas and accessories, including exact-replacement antenna data. See ad page 15.
- 5R. WINEGARD — New Factfinder bulletins on FM antennas, UHF antennas, and yagi couplers. See ads pages 20-21.

AUDIO & HI-FI

- 6R. ATLAS SOUND—Catalog No. 562 listing specifications on microphones and loudspeakers for public address, commercial and industrial use. See ad page 78.
- 7R. CINE-SONIC — Brochure describing background-music tapes available (hundreds of listings). See ad page 46.
- 8R. EICO—New 32-page catalog of kits and wired equipment for stereo and monophonic hi-fi, test equipment, Citizens-band transceivers, ham gear, and transistor radios. Also "Stereo Hi-Fi Guide" and "Short Course for Novice License." See ad page 60.
- 9R. HARMAN-KARDON — Revised catalogs on PA lines including Commander, Troubadour, and Galaxy series.
- 10R. NORELCO—Catalog NAP 1251 describing line of Continental tape recorders and other hi-fi components.
- 11R. QUAM-NICHOLS—Catalog sheet listing specifications and prices on complete line of wall baffles. See ad page 19.
- 12R. SWITCHCRAFT—Catalog E-508 illustrating and describing new series of 3-contact audio connectors. See ad page 88.

COMMUNICATIONS

- 13R. AMECO—Information describing Model SWB Standing Wave Ratio Bridge, for in-line use, and Model BIU Bridge Indicator Unit, for reading SWR. % power, and % voltage.
- 14R. CREATIVE PRODUCTS — Catalog sheets describing Citizens-band antennas for mobile use; also booklet listing antenna loading coils and discussing applications.
- 15R. DU MONT LABS — Information on Fairco Mark III Frequency Meter used to reduce WWV frequency standards to 5 kc for use throughout the amateur and Citizens bands.

COMPONENTS

- 16R. BUSSMANN — 24-page booklet (SFB) giving detailed information on complete line of BUSS and FUSETRON Small Dimension fuses and fuseholders used for protecting electronic equipment. See ad page 77.
- 17R. LITTELFUSE—Fuse Guide No. FG-62, giving up-to-date information and cross-reference data for auto-radio fuses. See ad 4th cover.
- 18R. PERMA-POWER—Latest Britener selector guide, showing the correct brightener to use with every type of picture tube in general use.
- 19R. SPRAGUE—Chart C-457 (designed to hang on wall) showing all popular TV-radio-hi-fi replacement components. See ad page 12.

SERVICE AIDS

- 20R. BERNs—Data on 3-in-1 picture-tube repair tools, on Audio Pin-Plug Crimper that lets you make pin-plug and ground connections for shielded cable without soldering, and on ION adjustable beam bender. See ad page 95.
- 21R. CASTLE—Leaflet describing fast overhaul service on television tuners of all makes and models; also illustrated lists describing universal and original-equipment tuners. See ad page 59.

- 22R. RCA (PARTS & ACCESSORIES DIV.) —Forms TK-306 describing Color Test Jig, and TK-310 describing Color Accessories and Color Parts Rack.
- 23R. SYLVANIA — Dealer shop equipment folder illustrating and describing workbenches, tube racks, and display counters. See ad page 55.
- 24R. YEATS—Literature describing the new Model 14 appliance dolly, featuring all-aluminum I-beam construction. See ad page 94.

SPECIAL EQUIPMENT & SERVICES

- 25R. EMCEE—12-page brochure describing complete line of TV rebroadcast translators and discussing their uses.
- 26R. ROTRON—Data sheet on Whisper fans for use in tape recorders, electronic instrumentation, and TV cameras.
- 27R. TERADO—Catalog sheet describing line of converters, battery chargers, and relays. See ad page 88.
- 28R. VOLKSWAGEN — 60-page illustrated booklet, "The Owner's Viewpoint," describing how various business enterprises use VW trucks in their operations; also booklet giving complete specifications on VW truck line.
- 29R. WABER — Sheet giving specifications and prices on various multiple-outlet boxes for use in service shop or home.
- 30R. WORKMAN — Catalog sheet describing fuse adapters used to adapt regular fuses for use in C and N type fuse holders; also information on 125-watt Transverter that allows 117-volt, 60-cps equipment to be operated in autos.

TECHNICAL PUBLICATIONS

- 31R. HOWARD W. SAMS — Literature describing all current publications on radio, TV, communications, audio and hi-fi, and industrial electronics, including brand-new Fall 1962 Book Catalog and descriptive flyer on 1962 Test Equipment Annual. See ads pages 46, 85, 88.

TEST EQUIPMENT

- 32R. B & K — Catalog AP20-R, giving data and information on Model 850 Color Analyst, Model 960 Transistor Radio Analyst, Model 1076 Television Analyst, Dynamatic 375 VTVM, V O Matic 360, new Model 625 3-in-1 Dyna-Tester, Models 600 and 700 Dyna-Quik tube testers, Models 440 and 420 CRT Tester-Reactivators, and Model 1070 Dyna-Sweep Circuit Analyzer. See ads pages 16-17, 53.
- 33R. ELECTRO PRODUCTS—Specifications on EC-3, a 20-volt, 150-ma

# SIGN UP

for more business



with colorful service signs from RCA

RCA signs for service technicians:

- Identify your business
- Call attention to your services
- Dress up your shop or truck
- Associate you with the prestige and customer acceptance of RCA—the most trusted name in electronics

*Another Way RCA Helps You in Your Business*

RCA ELECTRON TUBE DIVISION, HARRISON, N.J.



Metal Outdoor Hanging Sign—double-faced with hanging bracket, 40" x 28". (1A1275)



Metal Wall Sign—big 40" x 28" size. (1A1276)



All-Purpose Panel Sign Kit—for wall, truck, anyplace. Contains two 40" x 14" signs. (1A1278)



Metal Flange Sign—18" x 12"—for outdoor-indoor display. (1A1277)



Decal—12½" x 8½"—for wall, window, door, or truck. (1A1279)

All available from your Authorized RCA Tube Distributor. See him this week.



The Most Trusted Name in Electronics

# FASTER THAN A SHORT CIRCUIT



## SUB-MINIATURE MICROFUSES

and microfuse holders  
for internal connection  
and panel mounting.

1/500 AMP. thru 5 AMPS.  
@ 125 volts. Will  
interrupt 10,000 AMPS.  
DC short circuit.



## 8AG INSTRUMENT FUSES

1/500 AMP. thru 5 AMPS.

For instrument and meter protection, Littelfuse  
pioneered the design and  
development of reliable fast-acting fuses.

# LITTELFUSE

Des Plaines, Illinois