

OCTOBER, 1962

35 CENTS



RF REPORTER

PHOTOFACT

including **Electronic Servicing**

highlights of 1963 TV lines

JA OK 7498 1884
W.M. M. DAVIS
RAD. & TV SERV.
118 RIVERSIDE AVE.
CANNON CITY, COLO.

Standard Made It...



STANDARD CAN FIX IT BEST

\$11⁵⁰ Plus Parts . . . \$13.50 Maximum Total Cost

FREE Specially designed shipping cartons to prevent damage in transit

**6 Months
GUARANTEE**

Only BRAND NEW PARTS Used • 48 Hour
Service on All STANDARD Tuners • Latest
Testing Techniques Assure Proper Alignment •
\$3.00 Defective Tuner Trade-in Allowance
Against a New STANDARD Replacement Tuner
Carrying a 12 MONTH GUARANTEE

IN TV IT'S *Standard*

STANDARD has maintained uniform mounting centers for the last 13 years. Over 50% of the TV sets in existence today have STANDARD tuners—in the case of most other tuners one of the 8 STANDARD replacement models can be easily adapted or will fit directly in place of these units. All STANDARD replacement tuners carry a 12 Month Guarantee.

**SEE YOUR AUTHORIZED
STANDARD DISTRIBUTOR**

MORE PROFIT FOR THE SERVICE DEALER • GREATER CUSTOMER SATISFACTION
GUARANTEED BY THE WORLD'S LARGEST TV TUNER MANUFACTURER

standard kollman INDUSTRIES INC.

FORMERLY STANDARD COIL PRODUCTS CO., INC., MELROSE PARK, ILLINOIS

What's different about the new TV receivers now appearing on the American scene? You should know about these current trends:

Sales of 19" sets have climbed sharply. Two distinct types are found in most manufacturers' lines; "portables" tend toward slim briefcase styling and simplified circuitry, while "compacts" have more squarish lines and use circuits like those in big consoles.

The 21" and 24" screen sizes have just about disappeared. The 23" doesn't go unchallenged, however; 10 manufacturers now offer "king-size" sets with 27" screens. In some of these giants, 110° deflection helps reduce cabinet bulk.

Low-voltage rectifier tubes appear to be on their way out, as more and more manufacturers adopt silicon-rectifier voltage doublers even in transformer-powered sets.

The three-stage IF strip may also be on the wane. Super-high-gain tubes such as the frame-grid 6EH7 and 6EJ7, aided by "hot" RF-amplifier and video-output tubes, are making it possible to omit one IF stage without sacrificing performance. The swing back to DC-coupled video amplifiers is also gathering momentum.

Many wireless remote controls now have transistorized remote-receiver circuitry. For information on troubleshooting this equipment, see the article on page 32 of this issue.

The new color receivers will be described in the November PF REPORTER, which will be an "all-color" special issue again this year. For now, we'll concentrate on presenting thumbnail sketches of all the black-and-white TV lines.

Highlights of 1963 TV Lines



ADMIRAL

Few changes have been made from the '62 lineup. *Thinman* portables now use a 16A3B or -B3B chassis; remote-equipped versions, called *Sportsman* models (pictured here), use the 16C3U or 16D3U. Compact 19" sets are the manually-tuned *Spectator* (Chassis 16F3B) and remote-controlled *Viceroy* (Chassis 16G3U).

In both classes of 19" receivers, the models with remote control have a turret

tuner; others feature a new wafer-switch tuner with a 2- or 6FS5 shadow grid pentode in the RF stage. The latter tuner is also found in the 19E8B group of 23" sets, but all other 23's have a new DX-40 turret tuner with a 6DS4 RF amplifier (a remote-cutoff nuvistor). VHF models equipped with the DX-40 can be adapted to UHF by either adding from one to four channel strips, or installing an all-channel UHF tuner available as a conversion kit.


All chassis except the 16F3B and -G3U have a BU8 AGC-sync tube in place of the 6K11 compactron featured last year, but the octal damper used in '62 has been superseded by a 6- or 12AX3 compactron. Another new 12-pin type, the 12GE5, serves as a horizontal output tube in portables. In 23" models, picture-signal gain has been increased by substituting a 6DK6 for the 6CB6A, previously used as a third IF tube.

A special feature of the 21N3U chassis is a *Digital Tuning Control Center*, with 13 *Dialescent* (electroluminescent) panels providing illuminated channel numbers. Power is applied to one panel at a time through the switch shown in the schematic, which is ganged with the channel selector. To simplify circuit tracing, the wires to the panel are color-coded in the same color sequence as used on resistors.

Chassis used in combination sets, the 21S3U and -T3U, are like the other new 23" types except for differences in the audio circuits. The 20T8 in 27" models (covered in PHOTOFACT Folder 593-1) is similar to last year's 20A8 chassis. Color sets are also offered.

CURTIS MATHES

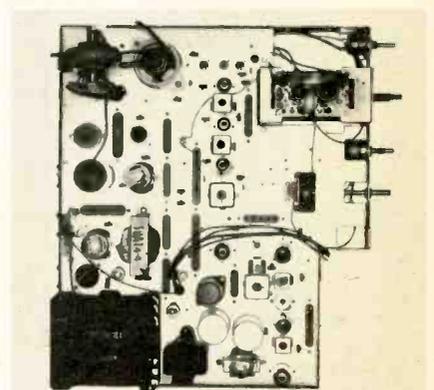Two differently-shaped chassis with almost identical circuits are now in production. The 10A is long, narrow, and horizontally mounted, like the Chassis 6D pictured in August, 1962 *Previews of New Sets*. On the other hand, the 9A shown



here is more nearly square in shape, and is mounted vertically on one side of the cabinet.


Several circuit changes have been introduced this season. The two-stage video amplifier (6U8 triode section and 12BY7) of past models has been replaced by a single-stage, high-gain circuit using a pentode section of a 6GN8. In the 9A, this stage drives a 23AWP4 picture tube, a low-Eg2 type which requires less video-signal input than its 23AHP4 predecessor.

Elsewhere in the new sets, an octal 6EM7 vertical output tube takes the place of the former 6DE7 or 6EW7. The combined functions of AGC keying, noise limiting, and sync separation have been taken over by a new 6KA8 triode-pentode. For a description of a similar 6KA8 circuit, turn to the RCA section of this article.

Some of the new Curtis Mathes chassis have a 6BQ5 audio output tube. Others, designed for use in combination models, feed audio through the high-fidelity phono amplifier circuits.

DU MONT


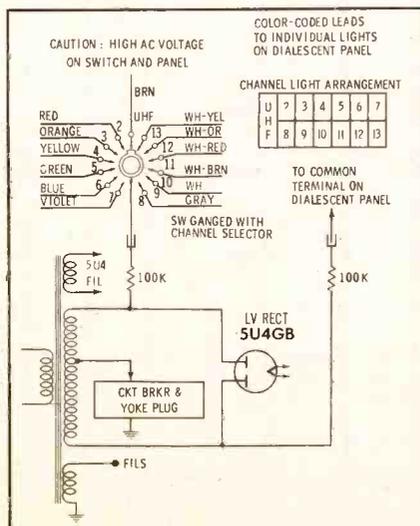
Chassis 120629 through -34, in the new "900" Series of 23" and 27" sets,



CHASSIS NO.	CRT TYPES	DEG DEF	BOND SHLD	PWR XFR	B + RECT	TUNER TYPE	DC CPL	NO. IF	HAF C TYPE	KEY AGC	NOI LIM	WIDTH CTRL	PROTECTED		CIRCUITS		REM AVL		
													PRI	SEC	SIL	FIL			
ADMIRAL 16A3B, -B3B, -C3U, -D3U 16F3B, -G3U 19E8B, -F8B, -G8B, -J8B 21K3U, -L3U, -M3U, -N3U	19XP4 19XP4 23BT4 23BT4	114 114 92 92			Sil dblr 5U4GB 5U4GB 5U4GB	* * SS TN		2 2 3 3	CC CC CC CC	BU Tr BU BU	BU Tr BU BU	sleeve sleeve sleeve sleeve			brkr brkr brkr	bkr	link link link	✓ ✓ ✓ ✓	
CURTIS MATHES 9A 10A	23AWP4 NA	92 92		✓	Sil dblr Sil dblr	SS SS		3 3	CC CC	P P	* *		fuse fuse		fuse fuse	link link			
DU MONT 120591, etc. 120629, etc.	17DKP4 19AVP4 23AFP4; 27ACP4	110 114 92		✓	5U4GB 3DG4	SG TG		3 3	CC T-D	BU BU	BU BU	coil coil		fuse *		link link		✓ ✓	
EMERSON 120619, etc.	17DKP4 19AVP4 23CP4; 27ADP4	110 114 110		✓	5U4GB	*		3	CC	BU	BU	coil		fuse		link		✓	
GENERAL ELECTRIC QX LX MX	16ATP4 19CFP4 19CKP4; 23DBP4	114 114 114	*	✓	Sil dblr 5U4GB Sil dblr	SS SS SG		3 3 3	T-D T-D CC	Tr Tr		coil coil coil	fuse	*	brkr	link link		✓	
MAGNAVOX 35 Series 36 Series 38 Series	23ASP4; 24AUP4; 27XP4 23MP4 24AHP4; 27ZP4 19BTP4	90 114 110 114		✓	Sil dblr Sil dblr Sil dblr	TG TG TG		3 3 3	S S S	P P P		coil coil coil	brkr		brkr	link link link		✓ ✓ ✓	
MOTOROLA TS-449 TS-578 TS-581 TS-584	19CHP4 23DAP4 19XP4 23AHP4 27YP4 19XP4; 23MP4 27ABP4 23AHP4 27YP4	114 94 114 92 90 114 110 92 90		✓	Sil HW Sil HW 5U4GB 5U4GB	SG SG SG SG		2H 2H 3 3	CA CA T-T T-T	P P BU BU	Tr Tr BU BU	jumper coil pot pot		brkr	brkr	brkr brkr		✓ ✓ ✓	
MUNTZ T36 ("19 Met") T37 ("J Series") 27"	19CLP4 23CP4 19XP4; 23MP4 NA	92 110 114 110		✓	Sil HW Sil HW 5BC3	SS TG NA		1 2 3	CC T-D T-D			*			brkr	FR FR	link		✓
OLYMPIC 10119 MM, MT MA MB ME	19XP4 19XP4 23AHP4 23AHP4 27XP4 23AHP4 27XP4	114 114 92 92 90 92 90		✓	Sil dblr Sil dblr 5U4GB 5U4GB 5U4GB	SG SG SS SG SG		3 2 2 2 3	T-D CC CC CC CC		BU BU	BU BU			brkr fuse	fuse brkr	link		
PACKARD BELL 88-14, -15 98D16, -C	19YP4; 23BTP4; 23MP4; 24AHP4 23CP4 23BTP4	* 114 92		✓	5U4GB 3DG4	TG TG		3 3	CC CC	Tr P	Tr Tr	coil coil		brkr brkr				✓ ✓	
PHILCO 13J27 13J28 13J41, -2, -3, -5 13N50 13N51, -2, -3	19ABP4 19ABP4 19BLP4 23BVP4 23BNP4	114 114 114 92 110		✓	Sil dblr Sil dblr Sil dblr Sil dblr Sil dblr	SG SG SG SG SG		2H 2H 2H 3 3	CC CC CC CC CC	Tr Tr P P P	Tr Tr Tr Tr Tr		jumper pot * * *			FR FR FR FR	link link link		✓ ✓ ✓
RCA KCS 140 KCS 141 KCS 136 Y	19AYP4 19AFP4; 19AUP4 23BKP4; 23BLP4	114 114 92		✓	Sil dblr Sil dblr Sil dblr	SN SN SN		3 3 3	* * *	P P P	* * *	coil coil coil	fuse fuse fuse		fuse fuse fuse	link link link		✓ ✓ ✓	

CHASSIS NO.	CRT TYPES	DEG DEF	BOND SHLD	PWR XFR	B+ RECT	TUNER TYPE	DC CPL	NO. IF	H AFC TYPE	KEY AGC	NOI LIM	WIDTH CTRL	PROTECTED CIRCUITS		REM AVL	
													PRI	SEC		SIL
SETCHELL-CARLSON																
463	19BRP4	114	✓	✓	Sil dblr	TN		2H	CC	Tr	*		fuse		FR	link
363	23CP4; 27ABP4	110	✓	✓	Sil dblr	TN		2H	CC	Tr	*		fuse		FR	link
163	23CP4	110	✓	✓	Sil dblr	TN		2H	CC	Tr	*		fuse		FR	link
X162	23CP4; 27ABP4	110	✓	✓	Sil dblr	TN		2H	CC	Tr	*		fuse		FR	link
SILVERTONE																
60000	19AYP4; 23BQP4	114			Sil dblr	SG		2	CC						brkr	✓
60100	23BDP4	92	✓		Sil dblr	SG		3	CC	BU	BU	sleeve			brkr	✓
61000	19AYP4	114			Sil dblr	SG		3	CC	BU	BU	sleeve			brkr	✓
	23CBP4	114	✓													
SYLVANIA																
563	19AFP4	114	✓		Sil dblr	SG		3	T-D	Tr	*	pot			brkr	link
565	23BGP4; 23BHP4	110	✓	✓	5U4GB	SG		3H	T-D	Tr	*	pot		brkr		link
TRAV-LER																
1188-12	17CFP4	90			Sil HW	*		2	CC						FR	
1181-42	19XP4	114			Sil dblr	SS		2	S	BU	BU				brkr	
1180-62	19XP4	114			Sil dblr	SS		3	S	BU	BU				brkr	
1179-22	19XP4	114		✓	5U4GB	SS		3	S	BU	BU		fuse			link
1082-162	23MP4	114		✓	5U4GB	SS		2	S	BU	BU		fuse			link
1073-152	23MP4	114		✓	5U4GB	*	✓	3	S	BU	BU		fuse			link
1090-253	27ZP4	110		✓	5U4GB	TG		3	S	BU	BU		fuse			link
WELLS-GARDNER																
19S26, -27	19CHP4	114			Sil HW	TS		2H	CA						FR	
19S18	19XP4	114			Sil dblr	TS		2H		BU	BU				FR	
23S330, -350	23AWP4	92			Sil HW	TS		2	CA						FR	
23S29, -31	23AHP4	92			Sil dblr	TS	✓	2H	T-T						FR	
23PS31	23AHP4	92		✓	Sil dblr	TS	✓	2H	T-T						FR	link
23PN30	23MP4	114		✓	Sil dblr	TN	✓	3	T-T	BU	BU				FR	link
WESTINGHOUSE																
V-2438	19CMP4	114			Sil HW	SG		2H	CC	Tr					fuse	
V-2437	19BWP4	114			Sil dblr	SG		3	CC	Te	Tr				fuse	
V-2435	19BWP4; 23CQP4	114			Sil dblr	TG	✓	3	CC	P	Tr	coil			fuse	
V-2436	19BWP4; 23CQP4	114		✓	3DG4	TG	✓	3	CC	P	Tr	coil	fuse			link
ZENITH																
16K20	19CRP4	92		✓	5BC3	SG		3	CC	BU	BU	sleeve		fuse		link
16K26	19CQP4	114		✓	5BC3	SG		3	CC	BU	BU	sleeve	fuse	fuse		link
16K27	19CQP4	114		✓	3DG4	TG		3	CC	BU	BU	sleeve	fuse	fuse		link
16K23	23ANP4	92	✓	✓	3DG4	TG		3H	CC	BU	BU	sleeve	fuse	fuse		link
16K22	23BTP4	92	✓	✓	3DG4	TG	✓	3H	CC	BU	BU	sleeve	fuse	fuse		link
16K28QS	23AFP4	92	✓	✓	3DG4	TG	✓	3H	CC	BU	BU	sleeve	fuse	fuse		link

Check mark indicates chassis has feature named; asterisk indicates "see text." Meanings of abbreviations and symbols: **TUNER TYPE** first letter T, turret; S, switch—second letter G, 6GK5 or similar type; N, nuvistor; S, shadow grid (6FS5). **DC CPL** means DC coupling from video amplifier to CRT. **NO. IF** means number of video IF stages; H indicates all IF tubes are high-gain type. **H AFC TYPE**—(selenium diodes) CC common cathode; CA common-anode; S series—(tube) T-T triode section; T-D dual diode section. **KEY AGC** and **NOI LIM** (noise limiter)—P, pentode; Tr, triode; Te, tetrode; BU, combination AGC-sync circuit (6BU8, 'GS8, or 'HS8). **PROTECTED CIRCUITS**—PRI and SEC, primary and secondary circuit of power transformer; SIL, in series with silicon B+ supply; FIL, filament. "FR" means fusible resistor; "link" means short piece of No. 24 to No. 28 wire. **REM AVL**—wireless remote control available.

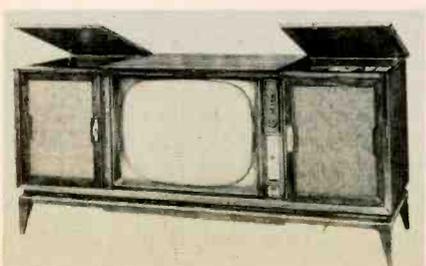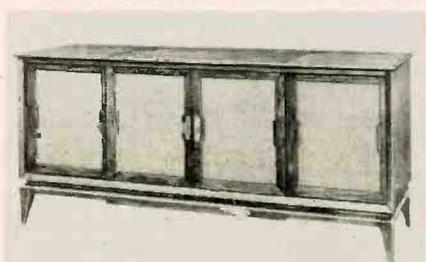

differ only slightly from the 120612 series introduced last fall. Several new tube types have been adopted: a 3DG4 B+ rectifier, a 3A3 high-voltage rectifier, a 6HS8 sync AGC tube, and the two new CRT's described in the chart. A damper-plate fuse gives additional protection to the flyback circuit besides that afforded by the circuit breaker on the primary side of the power transformer.

A half-dozen stereo combinations are included in the "900" series. One, the *Jameson* (see photo) has sliding doors; the panels are made of grille cloth, so the sound from the twin speaker systems can pass through them when they are pushed back for TV viewing.

Portable models for '63 are the 17" *Americana* and two 19" types, the *Sportsman* and *Bon Voyage*. Chassis numbers 120591, -2, -3, -644, -50, and -57 all are variations of the same basic design, a


transformer-powered, vertical chassis using mostly printed wiring.

Portables are available with clock timers, and 19", 23", and 27" sets with wireless remote control are offered. The line also incorporates color TV.

EMERSON

All chassis in '63 models are of the same general type, descended from last year's transformer-powered 120587-A and -93-A (covered in July *Previews of New Sets*). New chassis numbers are 120619 through -28, -44, -58, and -59. All of these are equipped with a width coil ('62 sets used a jumper for width adjustment). Some CRT's are new types. The 23" and 27" sets have turret tuners, while portables use switch tuners—but the RF amplifier is a 6GK5 in either case.

The photo depicts a remote-equipped

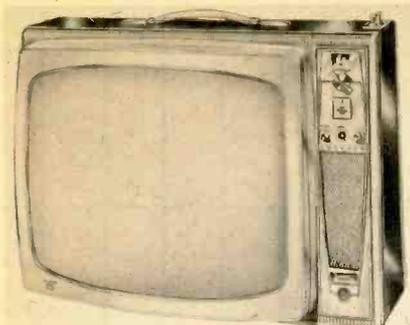

19" *Tru-Slim* portable, which also features an earphone jack. Another portable receiver has a clock timer. Safety windows used in these sets are glass rather than plastic.

At the top end of the Emerson line are several stereo combinations and color TVs.

GENERAL ELECTRIC

Every set in the G-E line (except color) contains from five to seven compactrons in addition to several conventional tubes.



The article, "TV Tube Trends," in the July PF REPORTER gave circuit functions and basing diagrams for all compactrons in the MX chassis (used in 19" compacts and 23" sets) and the LX (used in *Century* 19" portables). Since then, a third chassis (the QX) has been added. Its complement of compactrons is as follows: 11AR11, first and second IF; 15AF11, video output-sound IF-sync separator; 12AL11, audio detector and output; 15FY7, vertical sweep; 8B10, horizontal AFC-oscillator; 17GE5, horizontal output; and 17AX3, damper. The only other tubes outside the tuner are a 6GH8 third video IF-keyed AGC tube and a 1K3 high-voltage rectifier.

The QX chassis is found in the *Escort* (pictured), a 22-lb. portable with a new screen size: 16". The CRT has neither a bonded shield nor a separate safety glass; a thin film of *Lamilite* plastic over the CRT screen gives implosion protection.

Chassis LX, introduced early in the model year, was described in August *Previews of New Sets*. It has one feature which is rare in '63 models—a separate fuse protecting the horizontal sweep section.

The MX chassis includes several items not found in other recent "M" lines: keyed AGC, a DC-coupled video output stage, and a width coil. Some models are equipped with automatic brightness-contrast control; certain ones also have a wireless remote system. The MX line even boasts a


compact *Home Entertainment Center* with 19" TV, stereo phono, and AM-FM-stereo multiplex tuner, in a wood cabinet small enough to sit on a table or hang on the wall.

VHF versions of the QX and LX chassis have a switch-type *shadow grid* tuner, but UHF-VHF sets use a turret tuner with nuvistor RF amplifier.

MAGNAVOX


Large sets contain updated versions of the 35- and 36-series chassis—low-slung, U-shaped vertical types with "swing-out" mounting and three printed boards. Powering all 19" sets is a new 38-series chassis, with a more conventional "doughnut-type" vertical chassis pan, but with printed boards almost identical to those in the older series. All boards are marked with wiring paths on the component side, and with component symbols on the wiring side.

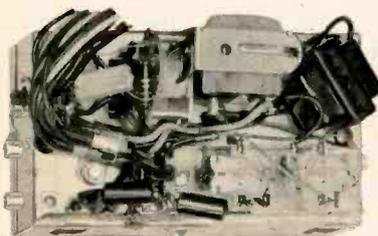A typical model from the 38 series will be described in December *Previews of New Sets*. Circuitwise, it is like the 36 series except that it has a 6GT5 (novar) horizontal output tube. Another new feature, found only in models with *Magnalux*



automatic brightness-contrast control, is the LDR RANGE adjustment shown in the schematic. This control can be used to set the accelerating-grid voltage of the CRT to any value between boost and B+, to maintain the correct brightness-contrast ratio over the widest possible range of ambient light. In the 35 and 36 chassis, the accelerating grid is simply connected to either boost or B+ by means of a jumper wire.

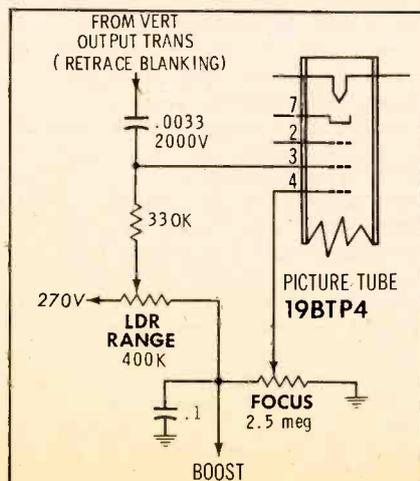Available with all chassis series is a new version of the *Phantom* wireless re-




mote system, incorporating a 6-transistor receiver section. As shown in the photo, the transistorized circuitry is not visible from the top of the remote-receiver chassis. The transmitter is a "tuned-port" (supersonic whistle) type, operating at the unusual frequencies of 22 and 28 kc.

The 37-series color receivers are still in the Magnavox line, but a new 41 series is scheduled for introduction in the near future.

MOTOROLA

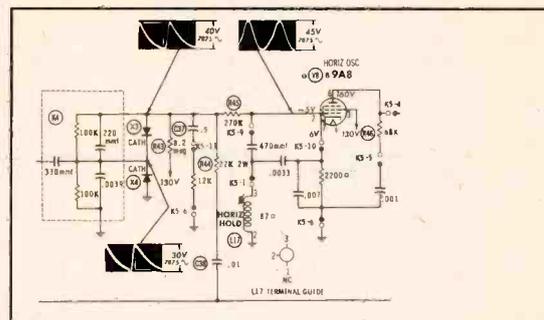The sets listed in the chart fall into two groups. The TS-449 and -578 are types that were introduced early this year for use in low-priced models, while the TS-581 and -584 series appear in the regular fall line.



Motorola has begun to standardize its chassis designs to the extent of no longer producing separate 400- and 500-series chassis types for 19" and 23" sets. Instead, "universal" chassis will be used (with only slight modifications) in sets ranging from 19" to 27". Chassis numbers have new letter prefixes to indicate CRT size—DTS for 19", ETS for 23", and GTS for 27". Any additional letters placed in front of these prefixes designates a change from the original chassis design.

The TS-449 and -578, almost alike except for sweep-circuit details and picture-tube type, use 300-ma series-string tubes wired in two parallel branches. Only the damper and picture tube are common to both heater strings. The unique horizontal oscillator (see schematic) is a simplified sine-wave circuit controlled directly by a dual selenium AFC phase detector. For further details on the TS-449, refer to February, 1962 *Previews of New Sets*.

All other new sets, in the TS-581 and -4 groups, are electrically almost the same as last year's TS-570 and -579. The main variations among sets within each chassis series involve sweep-circuit modifications to allow for different CRT sizes and deflection angles.


The most noticeable new physical feature is the use of solder-terminal boards mounted flush with the chassis. This type of construction is used throughout the '63 line, although not to as great an extent in the TS-581 as in the other chassis.

Included on some models is a fully transistorized remote unit which changes channels, and also operates a stepping relay for the on-off-volume function.

MUNTZ

Accounting for the bulk of present production is the J-shaped T37 chassis, which has been carried over from last year with no significant changes. The '63 models are all 19" or 23" sets with 110° or 114° deflection.


An interesting expansion has taken place at both ends of the Muntz line. A new *Metropolitan* 19" model (see photo) has a simpler chassis than the standard series, using six compactrons plus a 1K3 high-voltage rectifier, two tuner tubes, and a "low-drive" CRT. For compactron types and basing diagrams, refer to "TV Tube Trends" in the July issue. Don't look for boost in this receiver; since voltages above B+ (145 volts) are not needed by any circuits except the CRT anode, the boost source is omitted.

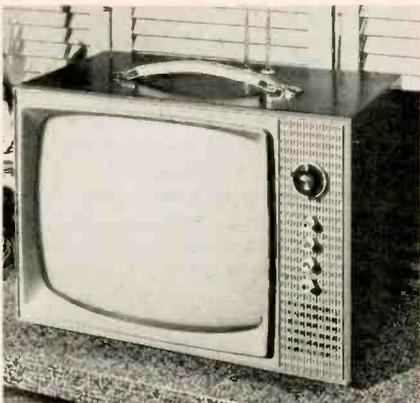

A deluxe transformer-powered chassis has also been designed for use in three new 27" models. The tube complement includes three novar types (6GT5 horizontal output, 6AY3 damper, and 5BC3 low-voltage rectifier); 6DT6 sound detector; 6BQ5 audio output; 6EM7 vertical sweep; and 6BY8 sound IF-AGC clamper. In addition, a 6KA8 is used in a keyed AGC-sync separator-noise inverter circuit similar to the one described in the RCA section of this article.

OLYMPIC

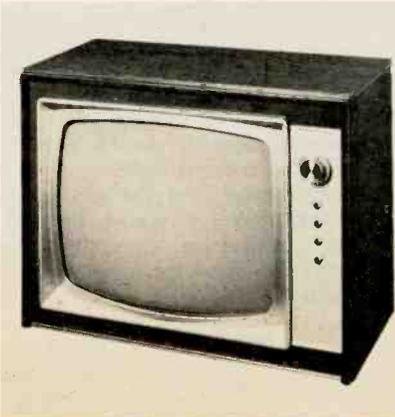TV-stereo combinations are still a specialty of this manufacturer. All except the lowest-priced models have AM-FM tuners capable of FM stereo reception. The three different transformer-powered chassis used in 23" and 27" combina-



tions, consoles, and table models closely follow previous designs.

Portables and 19" table sets are more prominent in the '63 line than in those of past years. One table model (Chassis 10119) is manufactured for Olympic in Japan; but all *super-slim* portables—and other sets like the one shown—are American made. Four different transformerless chassis—the MM, MT, LT, and LX—are found in recently-introduced models; there is also a transformer-powered portable (Chassis LV).

Rounding out the line are four color TV consoles.


PACKARD BELL

The newest editions of the *Rangefinder* chassis are the 88-14 and -15 (used in 19" *Astronaut* and 23" *Custom* models) and the 98D16 (for *Award* models).

Chassis 88-15 drives a 92° picture tube, the 23BTP4; the three other CRT's listed in the chart with this tube are 114° types used with the 88-14.

A few innovations have been made in the 88-series tube lineup. The damper is a 6BA3 or 6AY3 novar type, a 6CM8 serves as a third IF and noise limiter, and some sets use a 6GW6 horizontal output tube.

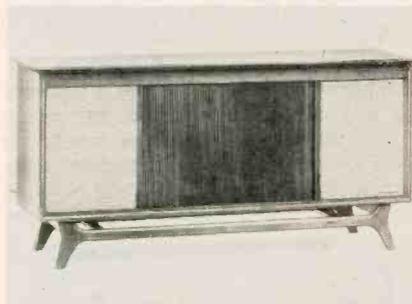The 98D16 chassis is designed to be used with a 114° CRT, except when a "C" suffix is added to the chassis number. In this case, the sweep circuitry has been modified for operation with a 92°, 23BTP4 tube.



A typical cabinet used with the 98-series chassis is shown on this page. Note the doors—a feature which seems to be gaining in popularity.


One 27" model is offered in the *Award* series, and a half-dozen color models are also available in this year's line. Some *Award* sets have an automatic brightness-control circuit. In addition, a wireless *Roto-Remote* unit is built into certain models (of both series) at the factory, and can be field-installed in other sets.

PHILCO

Acquisition of Philco by Ford Motor Company has not resulted in many drastic changes in the '63 TV chassis. For example, the 13J27 *Briefcase* is very similar to last year's 12J27, and the *Town and Country* 13J28 (in a tapered cabinet with rounded top) resembles the 12J28 *Black Beauty* described in July *Previews of New Sets*. However, some interesting changes have been made in the 19" compacts. A new styling idea appears in the *Town*


House model (see manufacturer's photo on this page), and a brand-new 13J41-series chassis has been introduced. In circuitry and general layout, it is similar to last year's 12N51 *Cool Chassis*, with one important exception: Using two frame-grid IF's in place of a three-stage IF strip has made it possible to reduce chassis size by consolidating all signal circuits on one large printed board.

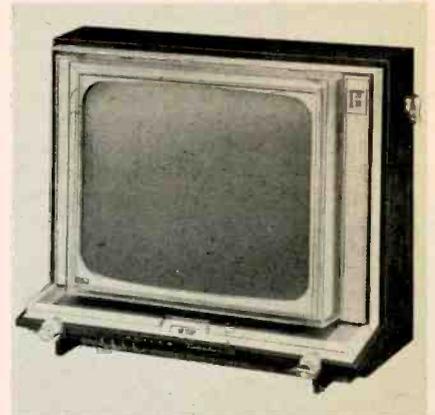The "N" group of chassis, now used only in 23" sets, have been slightly lengthened and rearranged for a more spacious



layout with fewer wire leads. The shield plate covering the underside of the IF printed board is removable, and the cut-outs in the plate underneath the main board have been enlarged.

All 110° *Custom Console* sets use the

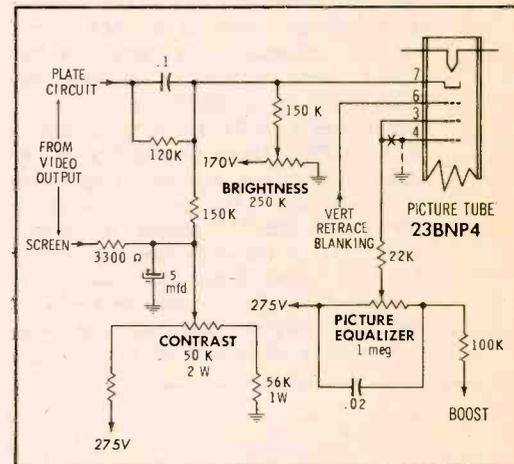

13N51 chassis series, which has several features in common with the 12N53 and -4 at the top end of the '62 line—for example, a 6HZ8 *Intensi-Tube* video amplifier, and horizontal retrace blanking.


In all 23" sets and compacts, a *varistor* furnishes automatic width control, and a *Picture Equalizer* (G2) potentiometer permits adjusting the accelerating-grid voltage of the CRT to obtain the best possible contrast range. The proper setting is obtained by applying a fixed bias of -1.5 volts to the grid of the video output tube, inserting a DC microammeter in the CRT cathode circuit, and turning the G2 control until the cathode current reads 220 ua (in compacts) or 250 ua (in 23" sets).

Two different types of *Directa* remote controls are available—one with tubes in the receiver, the other with transistors.


RCA VICTOR

All 23" black-and-white sets contain the KCS136Y chassis, a modification of last year's horizontally-mounted *Magic Monitor*. New features for '63 include silicon B+ rectifiers, a 6AY3 novar damper tube, and changes in the video output circuit to provide greater DC reinsertion. Automatic brightness-contrast control is available in some models.

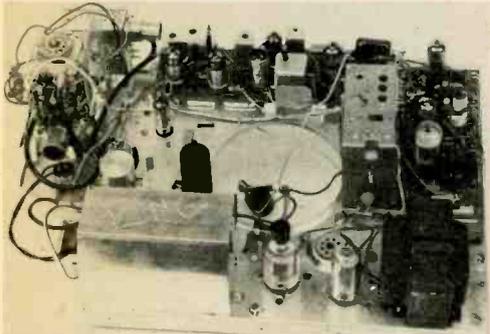The KCS130, -7, and -8 chassis have also been revamped for use in some portables; in addition, two new transformer-powered chassis have been introduced. One of these, the KCS140 used in *Stylist* models, was covered last month in *Previews of New Sets*. The other chassis is the KCS141 used in *Debonair* and remote-equipped *Fashionette* sets. A vertically-mounted type with a layout unlike



that of any previous chassis series, it is designed to stand upright without tipping over when removed for servicing. A 6KA8 triode-pentode serves as an AGC keyer and sync separator, in a rather complex circuit which includes a noise-limiting feature. (In the KCS136Y, a similar circuit utilizes a 6GY6 and a triode section of a 6HF8.) Noise interference in the video signal causes negative voltage spikes to be developed in the screen circuit of the keying tube; these are coupled to the suppressor grid of the same tube, and also to the input circuit of the sync separator, to counteract the effect of noise on the AGC and sync outputs. The noise-cancelling action can be varied with the SYNC STABIL-

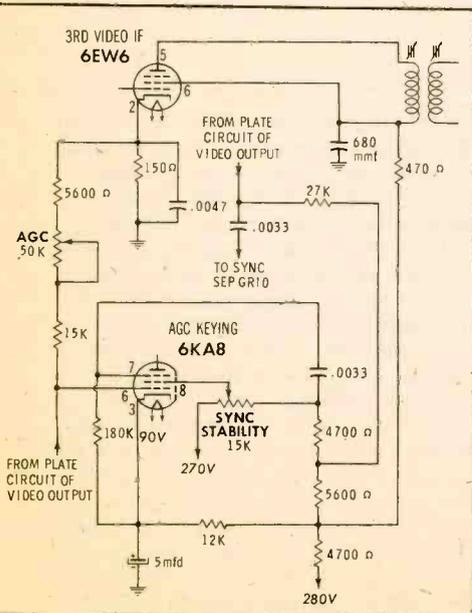

ITY control. Returning the grid of the AGC tube to ground through the cathode circuit of the third IF also contributes to noise cancellation.


In all the latest chassis, common-cathode selenium diodes develop a DC control voltage for a triode AFC stage, which in turn applies control voltage to a modified *Synchroguide* horizontal oscillator.

A new wireless remote receiver has transistors in all stages except the *Volume Up* and *Volume Down* relay-control circuits; these use sections of a 12BH7A tube.

The '63 color sets have an all-new, horizontally-mounted chassis—the CTC12—which will be covered next month in *Previews of New Sets*.


SETCHELL-CARLSON

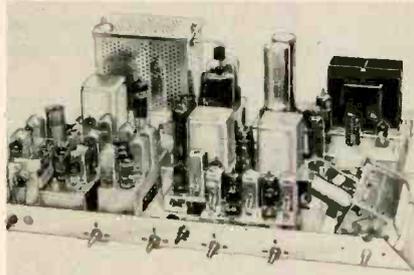New circuit features extending through the '63 line are a 6DS4 nuvistor RF amplifier, a two-stage video IF strip with 6EH7 and 6EJ7 frame-grid tubes, and two pentode stages in the video-amplifier section. As in previous models, the flyback is a plug-in type, and a 6CS6 operates as a sync separator and noise limiter.



The latest revision of the deluxe *unit-ized* chassis carries the same number (X162) as last year's version. All circuits except the low-voltage power supply are mounted on six plug-in subchassis units.

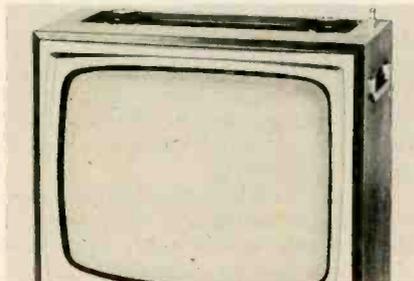A differently-arranged *unit-ized* chassis, the 163, is shown here. Used in combin-




ation sets, it has ten plug-in sections which accommodate all circuits including the B+ supply, twin high-fidelity audio amplifiers, an AM-FM tuner, and FM multiplex stages.

Two smaller chassis, the 363 and 463, use plug-in units only for the tuner, video IF, and 4.5-mc sound circuits. One of the 19" sets equipped with the 463 is a table model in a wood cabinet, with provisions for adding an AM radio tuner.

SILVERTONE

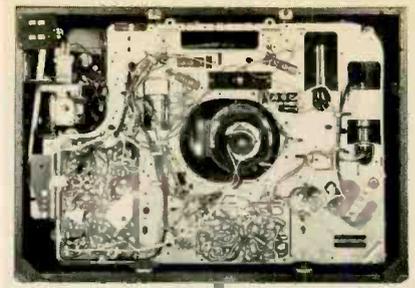
Chassis numbers above .60000 (following the usual 528 or 456 prefix) are applied to '63 sets. The first entry in the chart covers the majority of models. Sets



in this category use the "swing-out" style of vertical chassis shown in the photo, with tubes facing the CRT. The complement of 450-ma series-string tubes is the same as in last year's .51780 chassis, except that the new *shadow grid* tuner (equipped with a 3FS5 and a 6FG7) has been adopted in some models.

The .61000, .61020, and certain other chassis are constructed like the .60000, but have more elaborate circuits. A 4GS8 (an improvement on the 4BU8) is a combined AGC-keying, sync-separator, and noise-limiter tube; the last IF is a new high-gain 5EW6, replacing last year's 4CB6; and a 22BH3 novar damper is introduced in place of a 22DE4.

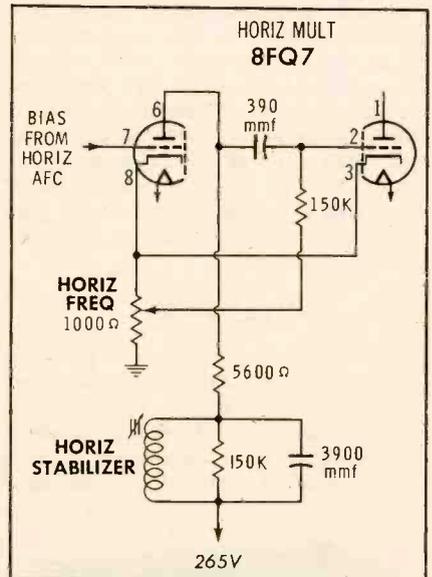A small group of models has a different style of vertical chassis, rather high and narrow, with tubes facing toward the rear. Although based on a design that has been in use for several years, this new .60100 chassis has modernized circuitry. Among the 600-ma series-string tubes are a 3GS8 keyed AGC-sync separator, 10EM7 vertical multivibrator-output tube, and 12AX4GTB damper.



All the new chassis afford a novel and interesting method of varying horizontal-multivibrator frequency. As shown in the schematic, the common cathode resistor is a potentiometer, and the ground return for the second section of the multivibrator is completed through the arm of this control—providing adjustable bias and feedback.

SYLVANIA

The GT-555 transformer-powered chassis used in 23" sets has been slightly revised for 1963; the newest chassis number

output; a 10JA8 video output-sync separator; and a 21GY5 compactron in the horizontal output stage. The yoke is a toroid type, and the AGC keying pulse is fed through a series trimmer so that the pulse amplitude can be varied to adjust the AGC bias.

Various models of all types have a *Mobil-Sound* circuit which rebroadcasts the TV sound so that it can be picked up on any nearby AM radio. All transformerless sets have polarized line plugs. An optional wireless remote control, with transistorized receiver circuitry, changes channels and performs a combined on-off-volume function.

For the first time in several years, color sets are available. A wide choice of cabinet styles is offered.

ZENITH

The "K"-series chassis listed in the chart were introduced this fall. Another complete series, bearing "J" numbers, were brought out last spring; they are closely related to the fall-1961 "H" group.

The greatest changes in the Zenith line are noted in 19" sets. In the 92° version (Chassis 16K20), several new tubes have been introduced—6KD8 horizontal oscillator, 6GE5 compactron horizontal output, 6AY3 novar damper, 6FM7 compactron vertical sweep, and 5BC4 novar B+ rectifier. A similar tube complement is found in the 114° Chassis 16K26, except for a 6GV5 compactron in the horizontal output stage, and a 6DX8 video output-sound IF tube. Incidentally, this chassis has no counterpart in earlier lines. The tube lineup in another 114° chassis, the 16K27, is practically the same as in 23" sets.

Portables feature tapered cabinet styling, as shown, while *Decorator* compacts have wider, more rectangular cabinet lines.

All 23" sets now have a *peak picture* control (video bandwidth adjustment) and frame-grid IF tubes. The following special features are found in the 16K22 and 16K28QS chassis: A 6JT8 frame-grid video output tube, *Dynamic Contrast* (DC-coupled video circuitry), a self-adjusting *FRINGE LOCK* circuit using a voltage-dependent resistor, and new *Super Sunshine* picture tubes. The 16K28QS is the *High Fidelity* chassis employed in the *Edgcombe* (pictured) and two other remote-equipped models in the deluxe *Decorator Group*.

Both versions of the *Space Command* wireless remote control are now fully transistorized.



Color sets have undergone only minor modifications since they were introduced last year; for the full story, see next month's PF REPORTER.

OTHER U. S. BRANDS

Andrea has just introduced two new chassis, the VTT-319 and -23, for 19" and 23" sets respectively. Newly-adopted features include a multivibrator-type horizontal oscillator, a quadrature sound detector, a circuit breaker, and silicon B+ rectifiers. Also newly announced are several color models using Chassis VCU-321.

The **Capchart** line includes two 19" portables, eight 23" console models (using two different chassis types), and four "Stereo Theaters" with 23" TV, phono, and AM-FM radio. All sets include a "Shadow Grid" tuner; each console has two speakers.

Sonora has a 17" portable, various 19" receivers (with at least three different chassis), and 23" receivers in a variety of cabinet styles.

Symphonic's 19" portable, Model H19, is covered in PHOTOFACT Folder 594-2. Also in this season's lineup are three upright consoles and two lowboys (all basically the same, except for cabinets and speakers), and two "Stereo Theater" combinations. All sets have bonded CRT's.

Transvision offers TV chassis in both kit and wired form; cabinets and accessories for custom installation are also available. The "Professional G" chassis, furnished with a 19", 23", or 27" picture tube, is equipped with either a push-pull audio output circuit or a cathode follower for feeding TV sound into a separate high-fidelity system. The "Economy B" chassis is suitable for 19" and 23" CRT's. There is a choice of two 21" color-TV kits—the CK-321 with push-pull audio output, or the CK-3A21 with an audio cathode follower.

FROM CANADA

Several companies are making their current lines available in the U.S. Although the emphasis is on elaborate 23" combination sets and TV consoles, smaller models are also offered.

Clairtone has three "stereo theatre" models with TV, phono, and AM-FM-stereo multiplex tuner. The TV audio circuits and speaker are independent of the stereo amplifier, and "silent listening" jacks are provided for stereo earphones. Model names are the "Duchess" (ST 853), "International" (ST 803), and "Viscount" (ST 703).

Electrohome sets use three different hand-wired chassis. The 17-tube "Centurion" appears in one 19" portable, two 23" consoles, and three 23" combinations; the Custom Duramatic, with 18 tubes, is used in another 19" portable, as well as in three consoles and a combination set of the 23" line; and the 21-tube Electromatic Imperial is found in five 23" consoles. All chassis include a "Power Pacer" (thermistor in the primary circuit of the power transformer) to reduce warmup surges.

Sparton's latest introductions are: three



19" compact sets using Chassis 19M1, -2, -3; five 23" consoles equipped with Chassis 23M1, -2, -7; and two stereo combinations (including the "Saguenay" model shown) using Chassis 23M4, -6. Another 23" console series uses Chassis 23L1, -2, -3, and the "Corona" (a 19" compact) has Chassis 19L1. The "Instant Reflex" chassis used in 23" sets is a hand-wired horizontal type with a bonded 110° CRT attached.

FROM JAPAN

The **Delmonico** line includes a 17-1b, 8" personal portable TV (Model 8PV-47U) with 14 tubes, three diodes, a cascade tuner, and a front-mounted speaker; three briefcase-styled portables, Models MTV-1U, -3U, and PTV-19U (for information on the latter, refer to PHOTOFACT Folder 538-1); two TV-AM/FM stereo combinations, Models CTV-237U and -350; and a color TV-stereo combination, Model CC-210.


Panasonic by Matsushita AN-14 is a 14" portable with 110° CRT. Chassis features include horizontal linearity and width coils, a 6DT6 audio detector, two earphone jacks, a cascade tuner, and an unusual vertical-linearity control (in addition to the usual size and linearity adjustments) which shapes the waveform of the feedback from the vertical output to the vertical multivibrator.

The **Star-Lite**, another 8" portable with tubes, includes a cascade tuner, three video IF's, and a crystal-diode ratio detector. Another set, expected to be added soon to this line, is a 16", 110° console in a wood cabinet with detachable legs.

Sony is offering a transistorized 8" personal portable (Model TV8-301W), described in PHOTOFACT Folder 588-2. An even smaller set, the "Micro TV" with square-cornered 5" CRT, has just been announced. This 8-lb. receiver can be operated from a rechargeable 12-volt battery pack, automobile battery, or AC line. The circuits utilize 24 transistors and 20 diodes.

Tarzian offers

FAST, DEPENDABLE TUNER REPAIR SERVICE

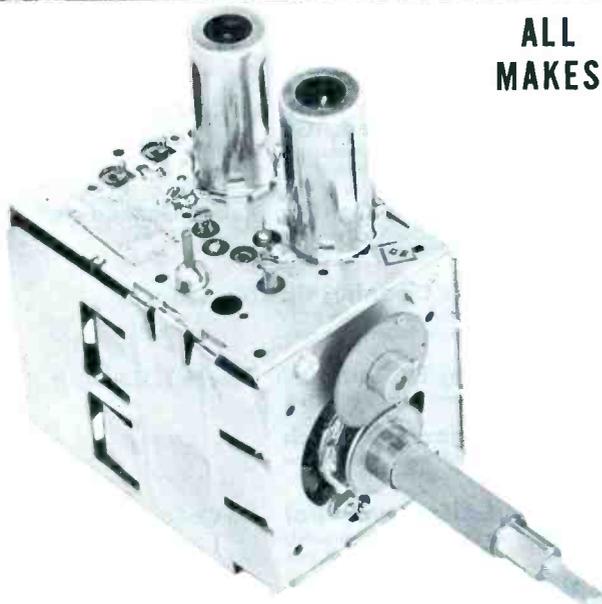

ALL
MAKES

It just makes sense that a manufacturer of tuners should be better-qualified, better-equipped to offer the most dependable tuner repair and overhaul service.

Sarkes Tarzian, Inc., pioneer in the tuner business, maintains a complete, well-equipped Factory Service Dept.—assisted by Engineering personnel—and staffed by specialized technicians who handle **ONLY** tuner repairs . . . on **ALL** makes and models.

Tarzian-made tuners received one day will be shipped out the next. There is a 12-month guarantee against defective workmanship and parts failure due to normal usage. And compare our cost of \$8.50 and \$15 for UV combinations. There is absolutely no additional, hidden charge for **ANY** parts except tubes. Replacements available at low cost on tuners beyond practical repair.

Ⓢ Tarzian-made tuners are identified by this stamping. When inquiring about service on other tuners, always give tube complement . . . shaft length . . . filament . . . voltage . . . series or shunt heater . . . IF frequency . . . chassis identification. All tuners repaired on approved, open accounts. Check with your local distributor for Sarkes Tarzian replacement tuners, replacement parts, or repair service.

SERVICE MANAGER • TUNER DIVISION • DEPT. 3A



SARKES TARZIAN INC

east hillside drive • bloomington, indiana
edison 2-7251

MANUFACTURERS OF TUNERS . . . SEMICONDUCTORS . . . AIR TRIMMERS . . . FM RADIOS . . . AM-FM RADIOS . . . AUDIO TAPE . . . BROADCAST EQUIPMENT

ONLY

\$8.50

INCLUDING

ALL PARTS (EXCEPT TUBES) and LABOR

24-HOUR SERVICE 1-YEAR WARRANTY

Tuners Repaired on Approved, Open Accounts

See your distributor, or
use this address for fast,
factory repair service

publisher
Howard W. Sams

general manager
Mal Parks, Jr.

editor
Verne M. Ray

managing editor
Forest H. Belt

ass't. managing editor
Thomas A. Lesh

associate editors
James F. Galloway
George F. Corne, Jr.

consulting editors
William E. Burke
Joe A. Groves
C. P. Oliphant

production manager
Robert N. Rippy

circulation fulfillment
Pat Tidd, Mgr.
Constance Bland, Ass't.
Katherine Smith, Ass't.

art directors
Dick Lovell
Robert W. Reed

advertising & editorial assistants
Georgeanna Caldwell
Ruth E. Bastin
Paula Haffner
Ellie Rother

photography
Paul Cornelius, Jr.

advertising sales offices
John Groce, advertising sales manager

midwestern
Hugh Wallace
PF REPORTER
4300 West 62nd Street,
Indianapolis 6, Ind.
AXminster 1-3100

eastern
Charles Horner
Howard W. Sams & Co., Inc.
3 West 57th Street,
New York, N. Y.
Murray Hill 8-6350

western
The Maurice A. Kimball Co., Inc.
2550 Beverly Blvd., Los Angeles 57, Calif.
DUnkirk 8-6178; and 580 Market Street,
Room 400, San Francisco 4, Calif. EXbrook 2-3365

Address all correspondence to
PF REPORTER, 4300 W. 62nd Street,
Indianapolis 6, Indiana



Copyright © 1962 by Howard W. Sams & Co., Inc. PF REPORTER is a trademark of Howard W. Sams & Co., Inc. No part of PF REPORTER may be reproduced without written permission. No patent liability is assumed with respect to use of information herein. Acceptance of advertising does not in any manner signify the products, policies and services so advertised have been approved, endorsed or recommended by this magazine.

Indexed in *Ictrodex*.
Printed by the Waldemar Press Div.
of Howard W. Sams & Co., Inc.



PF REPORTER


including **Electronic Servicing**

VOLUME 12, No. 10 **CONTENTS** OCTOBER, 1962

Highlights of '63 TV Lines A capsule review of all new chassis types now in production.	3
Letters to the Editor	16
The Electronic Scanner	19
Getting More Out of Resistance Measurements Quicker Servicing—How to avoid being fooled by "sneak circuits" and poor connections.	22 <i>George F. Corne, Jr.</i>
Symfact Charts: 6BU8 Keyed AGC See what happens to voltages and waveforms when troubles occur.	25
Weak, Washed-Out Pix Techniques for troubleshooting low gain in picture-signal circuits.	28 <i>Robert G. Middleton</i>
Closed-Circuit TV Is Opening Up Opportunities to install and service CCTV are multiplying faster than ever.	30 <i>Leo G. Sands</i>
They're Transistorizing TV Remotes In most '63 versions, tubes have been eliminated.	32 <i>George F. Corne, Jr.</i>
Fixing Record Changers Is a Cinch A new approach to isolating mechanical trouble by working backward from the adjustments.	38
Finding the Right Alignment Tool No more chewed-up slugs—if you're properly "tooled up" to align sets.	38 <i>Jim Galloway</i>
Stock Guide for TV Tubes	52
Synchroguide—From Squegs to Squeals Symptoms of frequency drift depend on the direction of error.	54 <i>Thomas A. Lesh</i>
Free Tube Testing—At a Profit? Dollar and Sense Servicing—Take the initiative and recapture tube sales from drugstore testers.	62 <i>Ernest Tricomi</i>
Notes on Test Equipment Lab reports on the Hickok Model 656XC Color-Bar Generator, EICO Model 955 In-Circuit Capacitor Checker, and Mercury Model 1200 Tube Tester.	68
Testing Magnetic Amplifiers Servicing Industrial Electronics—Here's how to determine what's going on in a "reactor."	81 <i>Barron Kemp</i>
The Troubleshooter	88
Product Report	103
Free Catalog & Literature Service	106
Monthly Index	on free literature card

ABOUT THE COVER

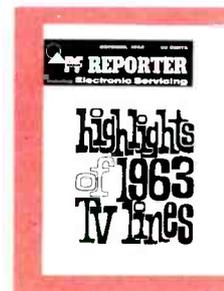If you're curious about what's inside the new TV receivers now on display in dealer's showrooms, just turn to page 3 and read our special feature article, "Highlights of '63 TV Lines"—which describes all the latest sets from a serviceman's point of view.



The **HIDDEN 500*** wrote these **6 SUCCESS STORIES**...

Service Technicians supply the happy endings!

Capacitor success stories are no novelty at Sprague. The "Hidden 500", Sprague's behind-the-scenes staff of 500 experienced researchers, have authored scores of them! And customers add new chapters every day. But none has proved more popular than the 6 best sellers shown here. Developed by the largest research organization in the capacitor industry, these 6 assure happy endings to service technicians' problems.

1 **DIFILM® BLACK BEAUTY® MOLDED TUBULAR CAPACITORS**



The world's most humidity-resistant molded capacitors. Dual dielectric—polyester film and special capacitor tissue—combines best features of both. Exclusive HCX® solid impregnant produces rock-hard section—nothing to leak. Tough case of non-flammable phenolic—cannot be damaged in handling.

2 **DIFILM® ORANGE DROP® DIPPED TUBULAR CAPACITORS**



Especially made for exact, original replacement of radial-lead tubulars. Dual dielectric combines the best features of both polyester film and special capacitor tissue. Exclusive HCX® solid impregnant—no oil to leak, no wax to drip. Double dipped in bright orange epoxy resin to beat heat and humidity.

3 **TWIST-LOK® ELECTROLYTIC CAPACITORS**



The most dependable capacitors of their type. Built to "take it" under torrid 185°F (85°C) temperatures—in crowded TV chassis, sizzling auto radios, portable and ac-dc table radios, radio-phono combinations, etc. Hermetically sealed in aluminum cases for exceptionally long life. Withstand high surge voltages. Ideal for high ripple selenium rectifier circuits.

4 **ATOM® ELECTROLYTIC CAPACITORS**



The smallest dependable electrolytics designed for 85°C operation in voltages to 450 WVDC. Small enough to fit anywhere, work anywhere. Low leakage and long shelf life. Will withstand high temperatures, high ripple currents, high surge voltages. Metal case construction with Kraft insulating sleeve.

5 **LITTL-LYTIC® ELECTROLYTIC CAPACITORS**



Ultra-tiny size for use in transistorized equipment. High degree of reliability at reasonable price. All-welded construction—no pressure joints to cause "open" circuits. Withstand temperatures to 85°C (185°F). Hermetically sealed. Extremely low leakage current. Designed for long shelf life—particularly important in sets used only part of the year.

6 **CERA-MITE® CERAMIC CAPACITORS**



Tiny, tough, dependable in practically every application. Low self-inductance of silvered flat-plate design gives improved by-pass action in TV r-f circuits. Higher self-resonant frequency than tubular ceramics or micas. Tough moisture-proof coating. Designed for 35°C operation.

*The "Hidden 500" are Sprague's 500 experienced researchers who staff the largest research organization in the electronic component industry and who back up the efforts of some 7,000 Sprague employees in 16 plants strategically located throughout the United States.

Handy Hanging Wall Catalog C-457 gives complete service part listings. Ask your Sprague Distributor for a copy, or write Sprague Products Co., 105 Marshall St., North Adams, Mass.





When is Big too Big?

When you "outgrow" your customers?

When you ration service according to their size?

When you put sales volume ahead of product quality?

When your service loses the *personal* touch?

When you become so self-important that you stop cooperating
with the service technicians who helped build your business?

In short, when you forget that your first and biggest job is satisfying your customers?

We've seen a lot of companies grow too big for their britches. Not so with Sprague!

In today's complex electronics industry, a company *must* be big! For only bigness—in research, production, and distribution—can bring you the technical services you need. But bigness

hasn't gone to our heads. We haven't lost the personal touch that helped us grow. Close attention to your needs is still primary with us.

You can depend on our faithful adherence to this policy—just as you can depend on the unmatched quality and selection of Sprague Capacitors.



WORLD'S LARGEST MANUFACTURER OF CAPACITORS

65-319 R1

**now
available
for custom
installation
and
replacement**


**two-way
protection
against
record wear**

1. Protects Against Spindle Wear. Smooth, precise dropping action minimizes wear on the record's center — eliminating a major cause of "wow."

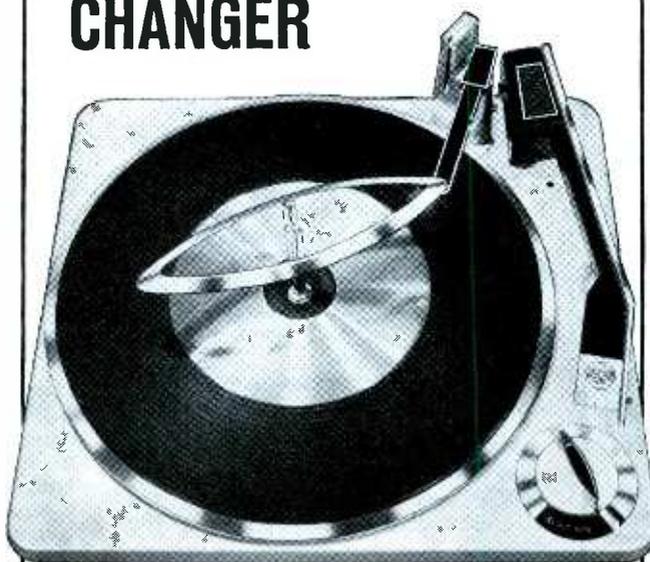2. Protects Against Groove Wear. Tracking is featherlight . . . true in the groove! Long record life and clean, vibrant sound are assured.

**available from your
local RCA outlet**

RCA VICTOR NEW STUDIOMATIC RECORD CHANGER



stock no. 12 B-100

**built for
endurance and
lasting
enjoyment**

Plays all size records with "Studio-like" precision.

Ultra-sensitive Living Stereo Ceramic Cartridge equipped with synthetic sapphire and diamond styli gives superb stereo separation plus all the brilliance of modern stereo.

'True-Track' Tone Arm is scientifically angled to insure optimum tracking from outer-edge to inner-most grooves.

RCA PARTS & ACCESSORIES, CAMDEN, N. J.

**styled for
beauty . . .
engineered
for precision**

■ Based on years of craftsmanship and millions of performance-proved Instruments.

■ A large turntable, almost 12" in diameter is scientifically balanced — cushioned to minimize rumble — supports record across entire playing surface.

■ Intermixes 7", 10", 12" records of the same speed.

■ Shuts off automatically — also has provision for amplifier shut-off.



**THE MOST
TRUSTED NAME
IN SOUND**

ATR

PRODUCTS FOR MODERN LIVING



ATR PLUG-IN TYPE PORTABLE INVERTERS*

A C HOUSEHOLD ELECTRICITY Anywhere in your own car, boat or plane

- Operates Standard A.C.
 - Record Players
 - Dictating Machines
 - Small Radios
 - Electric Shavers
 - Heating Pads, etc.
- In your own car or boat!

MODELS
 6-RMF (6 volts) 60 to 80 watts. Shipping weight 12 lbs. DEALER NET PRICE \$33.00
 12T-RME (12 volts) 90 to 125 watts. Shipping weight 12 lbs. DEALER NET PRICE \$33.00
 *Additional Models Available



ATR "A" Battery ELIMINATOR

For Demonstrating and Testing Auto Radios—TRANSISTOR or VIBRATOR OPERATED!

Designed for testing D.C. Electrical Apparatus on Regular A.C. Lines—Equipped with Full-Wave Dry Disc-Type Rectifier, assuring noiseless, interference-free operation and extreme long life and reliability.

MAY ALSO BE USED AS A BATTERY CHARGER
 MODEL 610C-ELIF... 6 volts at 10 amps. or 12 volts at 6 amps. Shipping weight 22 lbs.
 DEALER NET PRICE \$49.95
 MODEL 620C-ELIT... 6 volts at 20 amps. or 12 volts at 10 amps. Shipping weight 33 lbs.
 DEALER NET PRICE \$66.95


AUTO-RADIO VIBRATORS



By every test ATR Auto-Radio Vibrators are best and feature Ceramic Stack Spacers, Instant Starting, Large Oversized Tungsten Contacts, Perforated Reed, plus Highest Precision Construction and Workmanship and Quiet Operation!

There is an ATR VIBRATOR for every make of car!

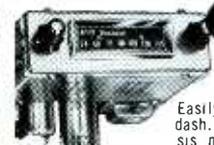Ask your distributor for ATR's Low Priced type 1400, 6 volt 4-prong Vibrator; and 1843, 12 volt 3-prong; or 1840, 12 volt 4-prong Vibrator. THE WORLD'S FINEST!



ATR UNIVERSAL KARADIO MODEL 600 SERIES


Easily installed in-dash or under-dash. Amplifier power-supply chassis may be separated from tuner chassis for easy servicing. Utilizes 6-tube superheterodyne circuit (2 dual-purpose tubes). Supplied with separate 5" x 7" speaker. Neutral gray-tan baked enamel finish. Overall size 4" deep x 6 1/2" wide x 2 1/2" high. Tuner Chassis; with Amplifier Chassis, 2 3/8" deep x 6 1/2" wide x 3 7/8" high. Shipping weight 7 lbs. WILL OUT-PERFORM MOST SETS!

Model 612—12 Volt, Dealers Net Price \$31.96
 Model 606—6 Volt, Dealers Net Price 31.96

Airplane Style Overhead Mounting under Cab Roof

NO PRINTED CIRCUITRY

ATR TRUCK KARADIO

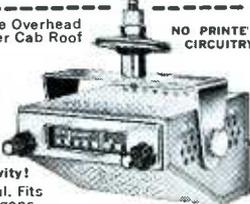

Excellent Tone, Volume, and Sensitivity!

Compact, yet powerful. Fits all trucks, station wagons, most cars and boats. Just drill a 1/8 inch hole in roof and suspend the one-piece unit (aerial, chassis and speaker) in minutes. Watertight mounting assembly holds antenna upright. Yoke-type bracket lets you tilt radio to any angle.

Extra-sensitive radio has 6 tubes (2 double-purpose), over-size Alnico 5 PM speaker for full, rich tone. Big, easy-to-read illuminated dial. Fingertip tuning control. Volume and tone controls. 33-in. stainless steel antenna. Neutral gray-tan enameled metal cabinet, 7 x 6 1/2 x 4 in. high over all. Shipping weight 10 1/2 lbs.
 Model TR-1279—12A for 12V Dealer Net Price \$41.96
 Model TR-1279—6A for 6V Dealer Net Price \$41.96

See Your Electronic Parts Distributor Write Factory For Free Literature

ATR ELECTRONICS, INC.

Formerly: American Television & Radio Co.



Quality Products Since 1931

ST. PAUL 1, MINNESOTA—U.S.A.

LETTERS TO THE EDITOR

Dear Editor:

I have been in the Navy for almost four years. In eight more months, I'll be on the outside once more.

Before enlisting, I was taking a radio-TV course, and also working part time in a local shop. When I entered service, I went to electronics schools and learned even more about troubleshooting.

Last fall, a friend who was a subscriber to PF REPORTER got me interested in it, and since then, I have regularly received and devoured the issues.

My main object in writing this is to let you know that PF REPORTER is actually a "course" in itself. It has brought much knowledge back to mind and added much, much more. I feel that with my past schooling and experience, and by keeping up to date through reading your magazine, I'll be ready for the outside. Thank you, and keep up the good work.

DUANE P. CULBERTSON, AT2, USN
Coronado, Calif.

What—not shipping over for another hitch? We sure hope the Navy doesn't hold it against us for influencing you in finding a satisfactory role in civilian life.—Ed.

Dear Editor:

We were pleased to note the special emphasis on Antenna Systems in your August issue. However, we were somewhat surprised to note that JFD was not listed in the "Distribution Accessories" category on page 31. As you know, they manufacture a complete line of outdoor and indoor multiset couplers, as well as the TNT105 Transistorized Distribution Amplifier. I trust you will correct this oversight.

JAMES SARAYIOTES

Delphi Advertising,
Agency for JFD Electronics, Inc.

PF REPORTER has been charged with the "Sin of Omission," and pleads guilty. If you readers filed the list, you may want to add JFD to this category.—Ed.

Dear Editor:

I must pare down my reading time; so I've decided to sacrifice my magazine subscriptions to the trend of the times... Who has time to read, "now-a-daze"?

You people should be first with a far-sighted idea to combat this problem. For instance, why don't you come out with a "Taped Tech Manual" recorded on magnetic tape at 3 3/4 ips? With each

"issue," includes a pamphlet consisting of photos and foldouts with figure numbers. Put in the photos that go with ads, but no printed matter—everything on the tape. Voices on the tape (male and female, and maybe even kids...) would give all references to the pamphlet.

I've time to listen, but reading is getting more time-consuming and tedious. Besides, I don't read too fast, but I listen very fast...

HENRY G. ZUK

Madison, Ill.

Yes, and our ads could be singing commercials... Still like the idea?—Ed.

Dear Editor:

I'm writing this note mainly in explanation of my failure to renew my subscription to your priceless monthly publication.

I have reached the age of 65 and, after many years of servicing radio and television equipment with the accurate guidance of PF REPORTER, I have retired. Although I am keeping my shop open for occasional service jobs, I find I must eliminate even the less expensive items to enjoy my remaining years working in electronics as a hobby.

But I want you to know that without your publication I would have run into a great many headaches, and I will miss the service helps and other information tremendously.

This magazine deserves the highest praise of any, and I strongly advise all servicemen (especially the up-and-coming younger generation) to be faithful to your advice, because it has been invaluable to me in the past.

Now, in my mellowing years, I wish you the best of success and hope your many subscribers will benefit from your information as much as I have.

WILLIAM L. JOYCE

Manager
Franklin Radio & Television Co.
Providence, R.I.

We are deeply and humbly gratified at such praise. If you find you just can't stay away from the ol' bench, Bill, we'll certainly be glad to welcome you back to the fold.—Ed.

Dear Editor:

Concerning the letter from I. & S Electronics published in your August issue, we in Venezuela are confronted with more or less the same problem on certain brands—with the additional aggravation that the parts never were imported.

To avoid embarrassing situations with my customers in connection with the repair of these sets, I very successfully follow the policy of repairing only American brands.

RAFAEL FEBRES ORTIN

Febres TV-Radio Servicio
Chacao, Venezuela


Slogan for today: "Buy Pan-American!" We're glad U.S. manufacturers are standing up to their obligation to make replacement parts available wherever needed.—Ed.

JFD **transis-tenna** the brand that puts you in command of your market—

brings you the *total* line of TV and FM electronic antennas and antenna amplifiers that is *ahead* in models, *ahead* in features, *ahead* in sell.


Why settle for less? Rely on JFD, the Antenna America knows best—and profit best!

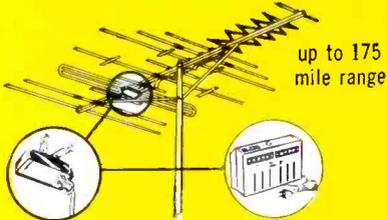JFD TRANSIS-TENNA ELECTRONIC TV ANTENNA-AMPLIFIER-DISTRIBUTION SYSTEM



up to 175 mile range

No. TNT1111G-AC \$76.95, list

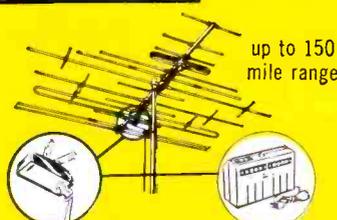


up to 150 mile range

No. TNT520G-AC \$66.95, list

ASSURE MAXIMUM GAIN AND HIGHEST SIGNAL-TO-NOISE RATIO—IN BLACK AND WHITE OR COLOR Super-gain PADT transistor circuit delivers up to 18 db gain on low-band, and 15 db gain on high band . . . exclusive direct-to-terminal mounting—the point of highest S/N ratio . . . a few of many reasons why you get more clean useable gain with Transis-tennas. Only JFD provides you with the broadest selection of electronic Transis-tenna systems—15 models—for every location and budget. Priced from \$39.95 to \$76.95, retail (antenna, amplifier and power supply included). Each antenna gleamingly AAA* gold bond alodized.


*Attractive, Anti-corrosive, Alodine-treated

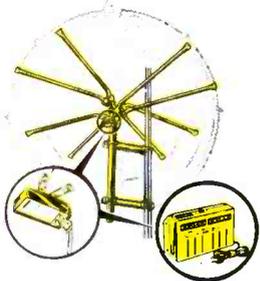100 MILE YAGI-SHARP RECEPTION FROM EVERY DIRECTION—WITHOUT A ROTATOR!



FM Stereo-Cone Transis-tenna No. TNTFM175G-AC \$47.95, list

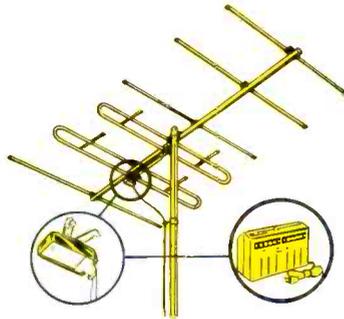200 MILE DEEP-FRinge HIGH FIDELITY RECEPTION



FM Stereo Yagi Transis-tenna No. TNTFM350G-AC \$54.95, list

JFD TRANSIS-TENNA ELECTRONIC FM ANTENNA-AMPLIFIER-DISTRIBUTION SYSTEMS

HIGH FIDELITY FM STEREO RECEPTION STARTS WITH A JFD FM STEREO-ENGINEERED ANTENNA. Whether you select an ultra-powerful JFD FM Stereo transistorized Transis-tenna or one of the 8 other quality-built JFD FM antenna kits, you step up to bright new profit opportunities in the growing FM market. You also get the extra sales boost of knowing that each JFD FM antenna is designed to overcome the power loss and range limitations of multiplexed FM stereo . . . receive distant stations crisply and clearly . . . add high fidelity quality to even budget-priced FM systems. Each antenna in lustrous AAA* gold bond alodized aluminum.

*Attractive, Anti-corrosive, Alodine-treated

JFD TRANSIS-TENNA TV/FM AMPLIFIER

THE ONLY "ADD-ON" TV/FM ANTENNA AMPLIFIER THAT MOUNTS ON EVERY TV ANTENNA AT THE RIGHT PLACE—DIRECTLY ON ANTENNA TERMINALS—THE POINT OF HIGHEST SIGNAL-TO-NOISE RATIO.

Only the JFD Transis-tenna mounts directly on the terminals of any antenna, regardless of its design—for maximum signal transfer. Exclusive PADT transistor circuitry provides superior gain—up to 18 db on low, 15 db on high band. Interference-proof circuit design rejects spurious amateur, CB, aircraft, fire, police and other interfering frequencies. Available with AC powered (TNT103) or battery-powered (TNT100) supply.



No. TNT103 AC-POWERED (shown above) \$36.95, list
No. TNT100 BATTERY-POWERED \$34.95, list

JFD "ALL-IN-ONE" HOME TRANSIS-TENNA TV AMPLIFIER

COMBINES AMPLIFIER AND AC-POWERED SUPPLY IN ONE HANDY UNIT that installs conveniently anywhere in home—yet operates 1, 2, 3 or 4 sets with amplified signal power. Average gain: low band, 18 db; high band, 15 db. Adjustable gain control . . . demonstrator shunt switch . . . optional 72 or 300 ohm connectors . . . courtesy AC outlet . . . AC-powered supply . . . 4-set coupler . . . all in one compact housing.

DEMONSTRATION SHUNT SWITCH

OPTIONAL 72-300 OHM CONNECTION

ADJUSTABLE GAIN CONTROL

No. TNT105 AC-POWERED \$29.95, list



JFD TRANSIS-TENNA FM AMPLIFIER

FOR THE ULTIMATE IN FM STEREO POWER, ADD THE NEW JFD FM TRANSIS-TENNA—THE ONLY FM ANTENNA AMPLIFIER THAT MOUNTS DIRECTLY ON THE TERMINALS OF ANY FM ANTENNA.

The best place for an amplifier is at the antenna terminals—and that's exactly where the JFD FM Transis-tenna goes . . . regardless of the antenna type. Increases gain of any FM antenna by 25 db. Complete with AC-powered supply—4 set distribution unit, 300 ohm connectors, and transistorized amplifier



No. TNT106FM AC-POWERED \$36.95, list

MAKE JFD—THE TOTAL TV/FM ANTENNA LINE—YOUR MAIN LINE TO PROFITS!
CALL YOUR JFD DISTRIBUTOR NOW.

JFD

THE BRAND THAT PUTS YOU IN COMMAND OF THE MARKET

JFD ELECTRONICS CORPORATION

6101 Sixteenth Avenue, Brooklyn 4, N Y

JFD Electronics Southern, Inc., Oxford, North Carolina


JFD International, 15 Moore Street, New York, N Y

JFD Canada, Ltd. 51 McCormack Street Toronto, Ontario, Canada

557 Richards Street, Vancouver 2, British Columbia

www.americanradiohistory.com

STANDOFF!

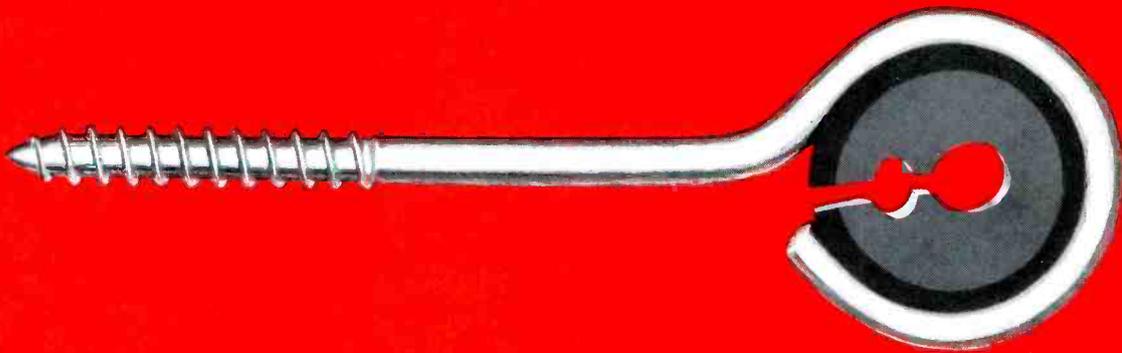


Most people think Standoff means "keep your distance" ■ Any good Service technician knows a Standoff as a gidget to hold the lead-in away from the house ■ So... ?

Just this. Philco talks your language, Mr. Serviceman. We practically eat and sleep parts and service day in, day out—just like you! We know your problems intimately. We know that unless you make a profit, this Philco operation can never make a profit, either. Everything we offer must be of value to you.

This Standoff, for instance. It has been tested for heat . . . for cold. It is hot galvanized to be rust resistant, tested for tensile strength, for shear . . .


dozens of individual tests and inspections. It's typical of the pains that are taken to insure the quality of every part Philco makes or sells.

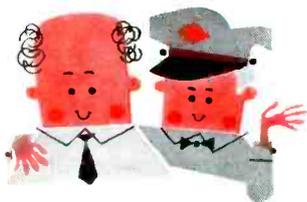Look to Philco for Sales helps, Training aids, Programs, to help keep you the expert in your field. And look to Philco for parts that replace quickly and stay replaced. This means Quality! Your profits will follow as day follows night—and so will ours! Standoffs, anyone?



YOUR PHILCO DISTRIBUTOR has a complete selection of Philco tubes, Philco and universal capacitors, batteries, parts and accessories . . . for every service need. See him today!

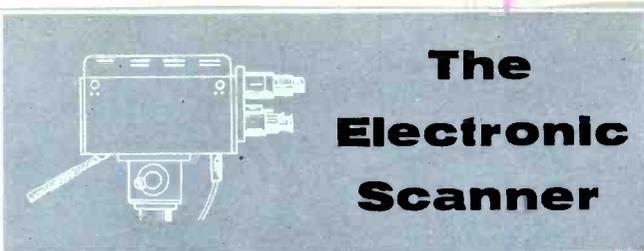PARTS & SERVICE OPERATIONS
PHILCO[®]
A SUBSIDIARY OF *Ford Motor Company*



The Electronic Scanner

Trading-Stamp Program Continues




Service dealers are now receiving "S & H Green Stamps" from their local distributors with purchases of Sylvania tubes. According to E. Bruce McEvoy (right), distributor sales manager for the company's receiving-tube division, "We are highly pleased at the increase in sales of receiving tubes for August. Our tube dealers are exceptionally enthusiastic over this program, since they're able to add the stamps they receive

from us to those they obtain through purchases of household goods, food, gasoline, and other products sold by thousands of merchants who give the stamps." Wyot Woods of Sperry and Hutchinson Co. is shown with Mr. McEvoy.

Recording-Tape Sales Campaign Initiated

The economical "Tartan" series of "Scotch" brand tapes, for home recordists, are being offered in specially priced three-reel packs by Minnesota Mining and Manufacturing Co. as part of their fall-winter sales campaign. Purchasers also will be given a special price on a gold-plated rack which will hold up to 40 boxes of tape.

Component-Display Stand Available

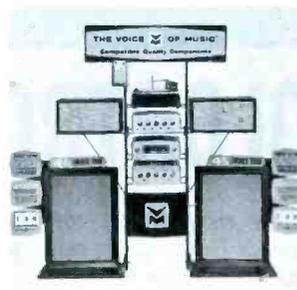

Entering the hi-fi components business is easy with the new metal "demonstration center" stand from the V-M Corp. Customers can get a look at the complete line of matching components, which includes the "Stere-O-Matic" record changer, standard and deluxe stereo amplifiers, Stereo/FM/AM tuner, and two sizes of speaker enclosures (with speakers). Also included with the display are a literature dispenser and promotional cards.

6-in-1 Knife-Tool Offered

With every "Universal Pak" of Anchor tube brighteners purchased, dealers will receive a knife that contains a cutting blade, screwdriver, bottle opener, Phillips screwdriver, wire scraper, and can opener. Each package contains ten "Brighteners" to take care of most TV sets in general use. Dealer net price of the entire package is \$11.95.

Come On In, The Water's Wet




"Operation: Service Aids"

Included in Motorola's new service-aids promotion are such items as complete service uniforms, tube totes, back-of-set stickers, door-knob hangers, and matchbooks. Service-men can obtain these service aids as premiums with the purchase of tubes or other replacement parts. Letterhead and bill-head stationery, business cards, and "want lists" are also included in the material offered.

Before long, a round-trip non-stop swim of the English Channel (never before accomplished) will be attempted by a lovely young lady of 24 named Mary Margaret Revell. University power hailers and loudspeakers will be used to relay information to her from the accompanying launch. These speakers are designed to operate continuously either in the water or out.

PHILCO® MEANS QUALITY

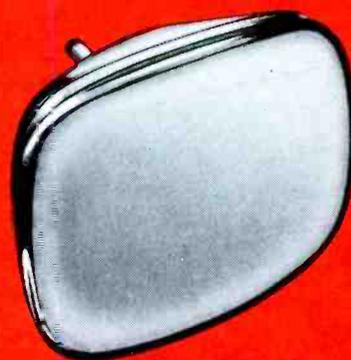

PHILCO Star Bright 20/20 Picture Tube

Everything that goes into a Philco Star Bright picture tube is new . . . to make TV sets sit up and act like new. New Electron gun, phosphor coating, filaments, cathode, focusing anodes . . . even new Aquadag Shell Coating.

PHILCO

Quality Tested Receiving Tubes

Just like the quality tubes in a brand new Philco television receiver. Safe, sure and sensible for every replacement, and they're engineered for long life.



4" Stereophonic Extension Speakers




Streamlined beige finished cabinet. 8 ohm voice coil impedance, .68 oz. Alnico magnet, Coaxial connector socket, cable connection plug included. With volume control (Part No. 326-5029-1) or without (Part No. 326-5029).

FREE 2 display cards with each dozen speakers.

For Over 30 Years... Providing a Better Future for America's Service Technicians

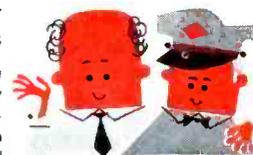Philco product data mailings—direct to you every month! Tangible benefits including low cost group insurance. Practical business building ideas. These advantages are yours when you enroll in the Philco Factory-Supervised Service Association. Ask your Distributor.



PARTS & SERVICE OPERATIONS

PHILCO®

A SUBSIDIARY OF Ford Motor Company

MAIL THIS COUPON TODAY TO:

PHILCO Parts & Service Operation, Dept. C10, "C" and Westmoreland Sts., Phila. 34, Pa.

Please send me FREE, the Philco Calculator. (Saves you hours of time figuring out net costs and selling prices.)

Name _____

Address _____

City _____ Zone _____ State _____

Service only Retailer with Service Dept.

- DESIGNED FOR COLOR TV
- PERFORMANCE GUARANTEE IN WRITING
- 100 MPH WIND TESTED



SUNFAST GOLD ANODIZED

*Pat. Nos. U.S. 2,700,105; 2,955,289 • Canada 511,934 • Others pending.

NEW FOR COLOR Winegard COLORTRON

EVOLUTIONARY — The finest TV antenna design ever engineered is the time-proven Electro-Lens all channel Yagi. This patented basic design, with its cross-phased driven elements and intermixed director system, was introduced by Winegard to the industry in 1954 and has never been surpassed. Now, through continuous research and product development, a new, improved Electro-Lens Yagi has evolved—the NEW WINEGARD COLORTRON—bringing this acknowledged design to a new peak of perfection.

4 COLORTRON MODELS \$24.95 to \$64.95
There are 4 new COLORTRON yagis to cover every reception need, from suburbs to distant fringe areas . . . setting new industry standards for reception results and mechanical construction. They are


the only outside antennas that carry a *written factory guarantee of performance* with full factory back-up of consumer satisfaction.

PERFECT COLOR ANTENNA — COLORTRONS have an almost flat frequency response (plus or minus ½ DB across any 6 MC channel), no “suck-outs” or “roll-off” on end of bands . . . accurate 300 ohm impedance match, (VSWR 1.5 to 1 or better) . . . unilobe directivity for maximum ghost and interference rejection. They deliver today’s finest TV reception—COLOR or BLACK AND WHITE.


RUGGED CONSTRUCTION — SUNFAST GOLD ANODIZED—COLORTRONS are *built to last* . . . made of high tensile aluminum

tubing for rigidity and stability. New locking devices keep the elements aligned—straight as a die. This quality of construction will satisfy a perfectionist! Insulators have a triple moisture barrier to insure top performance, rain or shine. Every COLORTRON is GOLD ANODIZED the WINEGARD way for the best looking, most corrosion-proof and permanent Gold finish known for aluminum.

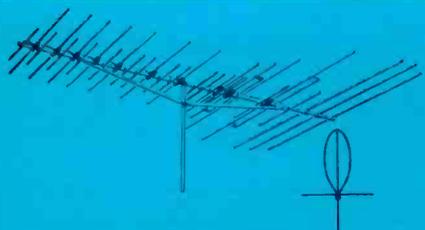
POWERFUL ELECTRONIC ANTENNA — Because the COLORTRON and the NUVISTOR amplifier were designed to match each other perfectly, electronically and mechanically, together they make the most efficient electronic TV antenna yet devised .




MODEL C-44
GOLD ANODIZED \$64.95

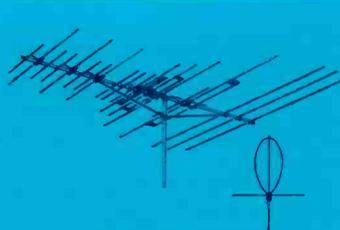

MODEL C-43
GOLD ANODIZED \$51.90

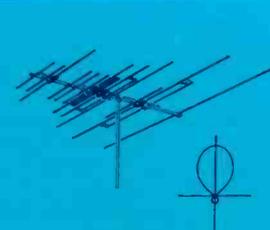

MODEL C-42
GOLD ANODIZED \$34.95

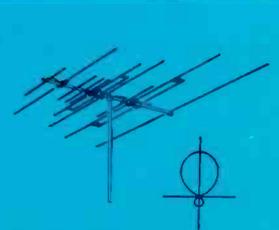

MODEL C-41
GOLD ANODIZED \$24.95



- USES 2 LONG LIFE NUVISTORS
- STRONG SIGNALS CAN'T OVERLOAD IT
- COMPLETELY WEATHER-SEALED

ANTENNA and COLORTRON AMPLIFIER

REVOLUTIONARY—Now a revolutionary new circuit, using two NUVISTORS enables the WINEGARD COLORTRON amplifier to overcome the limitations of other antenna amplifiers. For instance, oscillations, strong signal overloading and cross modulation picture interference are not problems with a COLORTRON AMPLIFIER because it will take up to 400,000 microvolts of signal input, 20 times more signal than other antenna amplifiers. *You can use it to amplify weak signals from far-away stations even though you have strong local signals from TV and FM stations. The COLORTRON NUVISTOR Amplifier is the only antenna amplifier that can do this!*

"LIFESAVER" CIRCUIT GIVES NUVISTORS 4 TIMES THE LIFE OF ORDINARY TUBES—A special "LIFESAVER" circuit has been designed to give the rugged LONG LIFE NUVISTORS an operating life many times

that of tubes, and superior to transistors in similar use. The COLORTRON NUVISTORS will operate perfectly for years.

PERFECT COLOR TV AMPLIFIER—The COLORTRON amplifier *has what it takes* to give CLEAN, CLEAR COLOR PICTURES, sharp and bright without smear. On weak signals, it will effectively reduce snow and interference, often making the difference between a very good picture and a poor one. It has an ultra low noise circuit... high amplification... flat frequency response... accurate impedance match (VSWR 1.5 to 1 or better, input and output)... and no phase distortion. You can be confident it will improve color and black and white TV reception in any location. This amplifier is so powerful, it can easily drive 6 sets at once with gain to spare!

WEATHER-SEALED POLYSTYRENE CASE ... CORROSION-PROOF—The COLORTRON

NUVISTOR amplifier is completely weather-sealed! Nothing is exposed to corrode and cause trouble—even the terminals are protected. A rubber boot over the twin-lead keeps moisture out. A built-in heat sink controls temperature of NUVISTORS. Everything possible has been done to eliminate maintenance problems. It comes complete with an all AC power supply with built-in 2 set coupler. (Mod. No. AN-220, \$39.95). The COLORTRON amplifier will give trouble-free performance for years. Install it and forget it!

OTHER ANTENNA AMPLIFIERS

FOR TV—2 Transistor (Mod. No. AT-220, \$39.95) also available. Will take up to 80,000 microvolts of signal input without overload. This is 3 times the input of other transistor antenna amplifiers.

FOR FM—Super sensitive 2 Nuvistor, 200,000 Microvolts Input—\$39.95.


Write for information.



AMPLIFIER WORKS ON ANY ANTENNA.



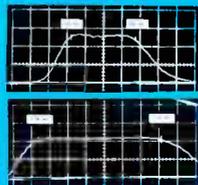SPECIALLY DESIGNED AMPLIFIER CLAMP SNAPS ON COLORTRON ANTENNA IN SECONDS.



UNRETOUCHED PHOTO OF AMPLIFIER GAIN CURVE—FLAT RESPONSE ALL CHANNELS.



COLORTRON POWER UNIT WITH BUILT-IN 2 SET COUPLER.



Write for technical bulletins

Winegard

ANTENNA SYSTEMS


3009-10 KIRKWOOD, BURLINGTON, IOWA



getting more out of

RESISTANCE

measurements

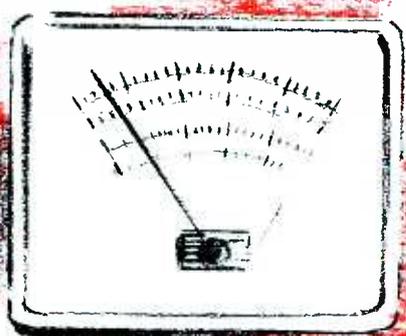

Visual checks, voltage measurements, and waveform analysis can generally clue the service technician to a troubled stage. After locating the defective circuit, he must find the individual component(s) which are causing the receiver to operate abnormally. His most useful instrument at this time will probably be his ohmmeter; in fact, his skill in using it and interpreting its readings may well determine his profit or loss on the job.

What methods or procedures will help increase the profit? Those mentioned in this article will be beneficial, if you'll start thinking about them and try putting them into practice.

Watch Your Test Points

You'll save yourself a lot of trouble by making resistance measurements as close as possible to the actual component you suspect of being defective. Placing the test probes on remote points, such as tube pins, may allow wiring defects to mislead you into replacing a perfectly good part.

To illustrate the importance of making direct measurements whenever you can, here's a case in which the initial measurements led to wrong conclusions and made some backtracking necessary. In a late-model TV set, intermittent pulling or loss of horizontal sync was the complaint. Rotating the fine-tuning

control (to mistune the RF oscillator a small amount) would sometimes cause the set to act up; at other times it wouldn't. A heat lamp was no help. The technician eliminated the AGC circuit (a keyed type) as a trouble spot, and started looking for defects in the noise-limiter and sync circuits (Fig. 1). Note that all connections between these stages are made through a printed-circuit component combination.

The resistance from the grid (pin 2) of the sync separator to chassis seemed normal enough—close to 1.4 meg—but the grid-to-chassis path from pin 9 of the noise limiter measured 22 megs. Connecting the ohmmeter leads between the grids of the two tubes indicated that R1, the 1-meg resistor inside the printed unit, was apparently defective. This could open the grid-return path for the noise limiter, causing intermittent operation.

The type of printed component board used in this receiver, shown in Fig. 2, provides for snap-in replacement of individual components; that is, any part may be replaced by first removing the defective item from the board and then snapping in a new one. Consequently, the technician was able to remove R1 and check it with his meter. To his surprise, it read 1 meg, just as it should. Rather than to put the old part back, he soldered in a new 1-meg resistor from his stock. However, on repeating the resistance check between the noise-limiter and sync-separator grids, he once more found the same

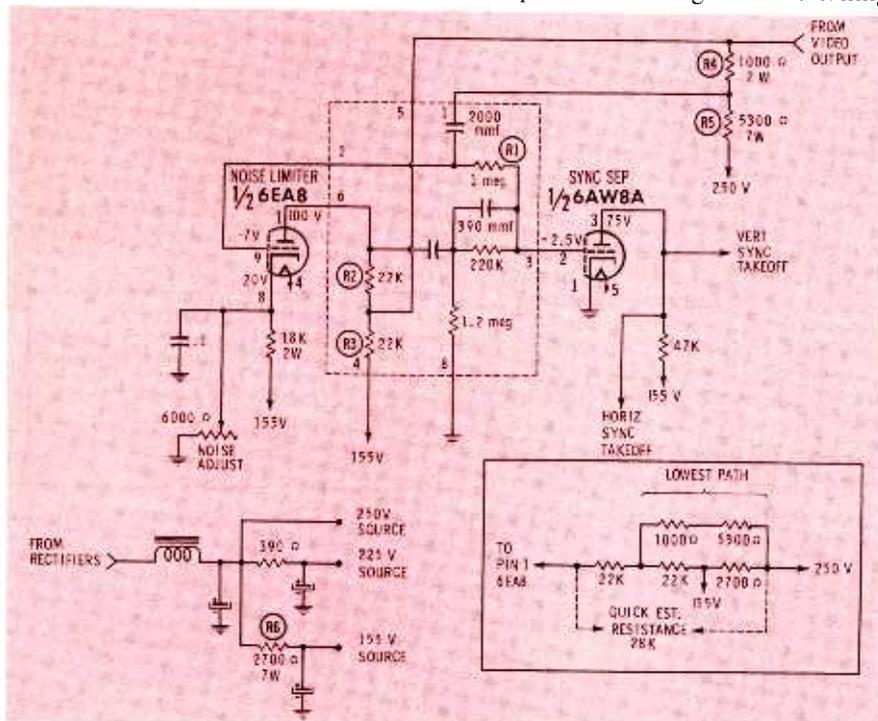


Fig. 1. Open path between the grid and ground caused pulling and poor sync.

• Please turn to page 98

FROM THE LEADING NAME IN WORLD-WIDE COMMUNICATIONS

*Electronic
Elegance*



NEW TRANSISTOR RADIO LINE


PLEASURE-STYLING AT BETTER THAN COMPETITIVE PRICES

Here are some highlights which make the ITT Transistor Radio Package more than just another transistor radio line • Coast-to-coast service centers stocked with original parts • Recognized and accepted ITT prestige label on a quality product • Dealer-oriented sales program backed by national advertising and merchandising • Better than competitive pricing • 90-day warranty on all material • National network of warehouses • Sold through ITT franchised electronic distributors.

You can increase your radio department profits with ITT's complete line — ranging from the rugged AM/FM portable to the petite wrist strap model. See them at an ITT franchised electronic distributor or write direct.

ITT
DISTRIBUTOR PRODUCTS DIVISION
INTERNATIONAL TELEPHONE AND TELEGRAPH CORPORATION
P. O. BOX 99, LODI, NEW JERSEY

TACO **T-BIRD** ELECTRA

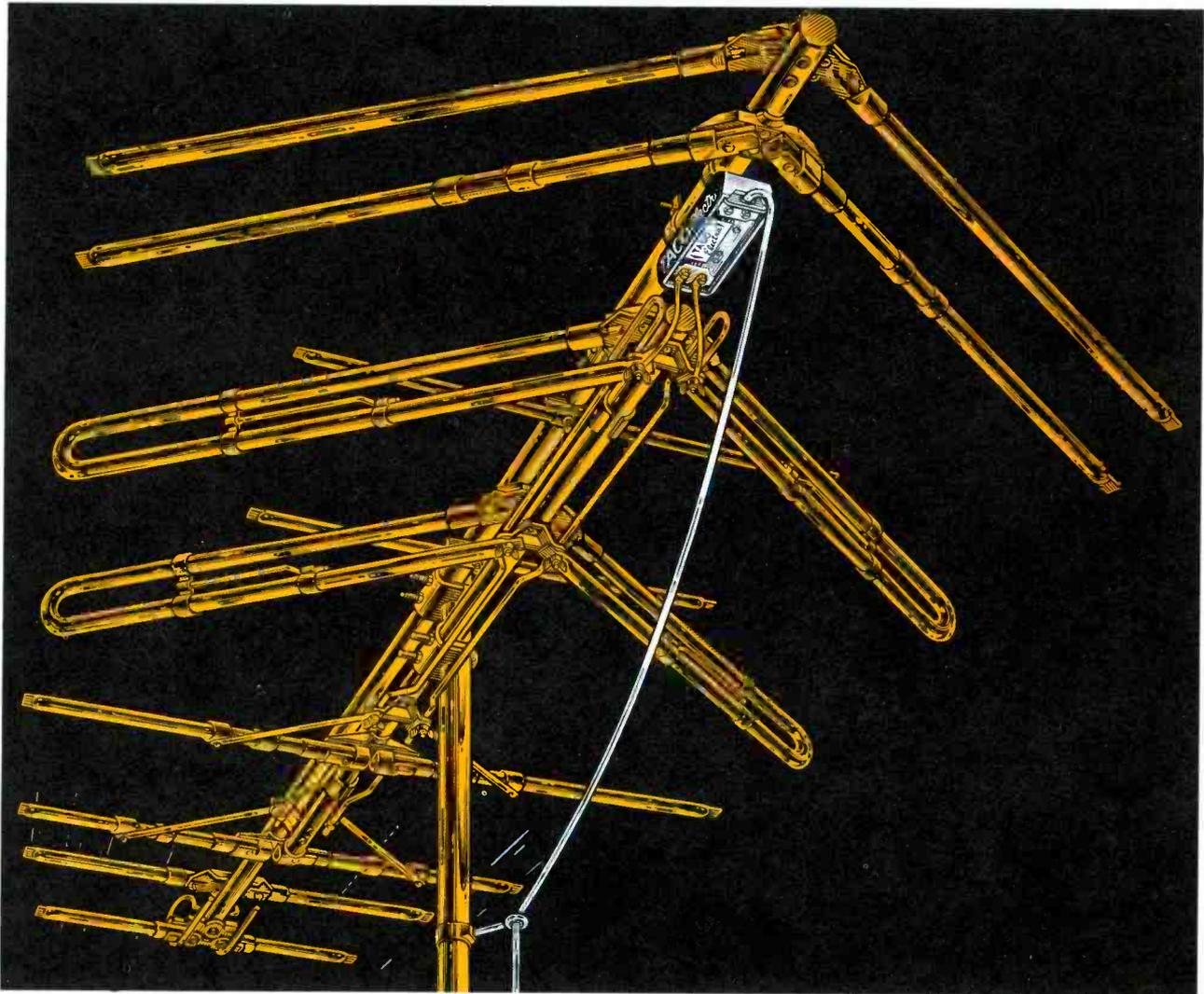

HOTTEST- and TOUGHEST

Compare and you'll see why! →


Besides being the most durable, note the almost flat response curve of the T-BIRD ELECTRA throughout the VHF band—no hills and valleys that cause smear and distortion in black-and-white, and disrupt optimum reproduction of color. T-BIRD ELECTRA delivers a strong, clean signal, free of element "junction noise" and gain flutter—a boon to black-and-white reception, a must for color!








Write for name of nearest distributor

TECHNICAL APPLIANCE CORPORATION

Dept. JTD54, Consumer Products Division
Sherburne, New York

A Subsidiary of
THE JERROLD CORPORATION

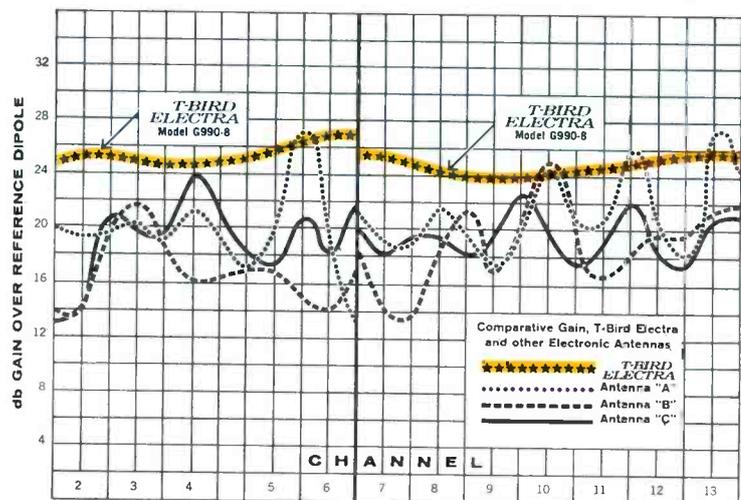

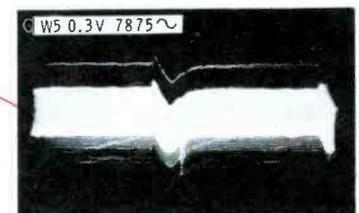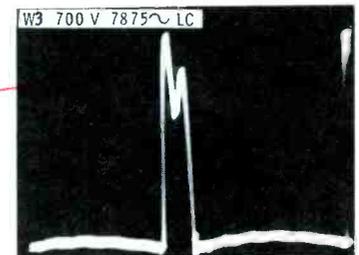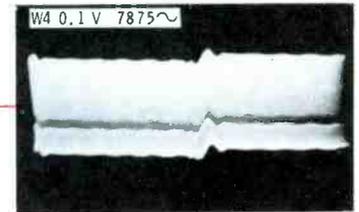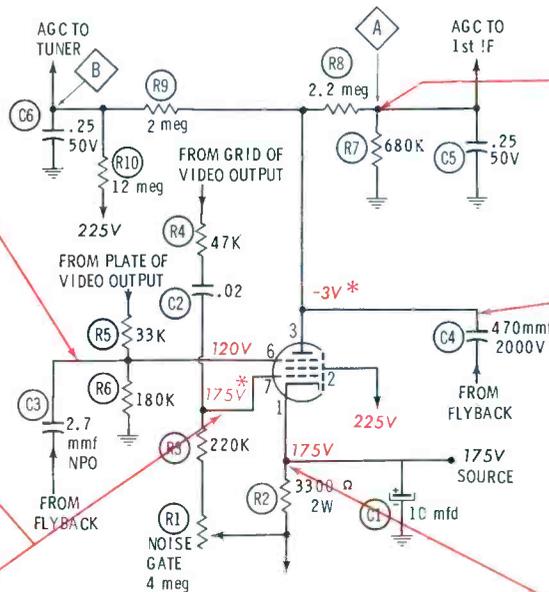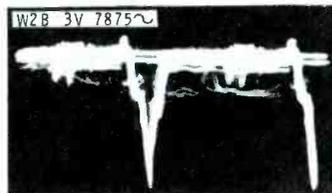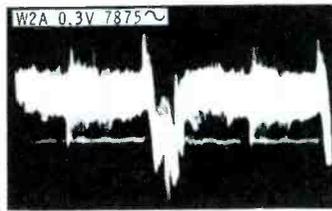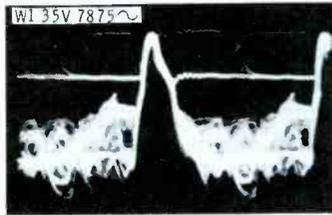

Normal Operation

One of two pentode sections in 'BU8 functions as AGC keying tube. (For description of other pentode section, refer to September, 1962 *Symfact* coverage on 6BU8 sync separator.) AGC portion of tube conducts only when positive keying pulse in W3—a sample of horizontal flyback pulse—is present on plate (pin 3). Strength of plate current is determined by DC voltage level on pin 6 at instant when keying pulse arrives. This element is direct-coupled to plate circuit of video output stage, making pin-6 voltage dependent on two factors: Amplitude of horizontal sync-pulse tips in W1, and DC plate voltage of video output tube. Both of these factors tend to raise voltage at pin 6 when RF input to receiver increases; 'BU8 then conducts harder and builds up additional charge on AGC filter networks in plate circuit. Pin-7 circuit combats noise interference in received signal, which tends to increase 'BU8 conduction and produces too much AGC bias. Sample of video waveform (W2) is fed to pin 7 in such a way that each incoming noise pulse can be made to block 'BU8 for an instant, and thus cancel itself. Unusual feature, small negative flyback pulse fed through C3, neutralizes positive-pulse feedback from pin 3 to 6 within tube.

Operating Variations

- PIN 3** Charging of AGC filter generates negative DC voltage proportional to video signal strength — usually -30 to -40 volts on strong stations. W3 overdrives some scopes, unless low-cap probe is used for its AC voltage-dividing action.
- PIN 6** Waveform amplitude and DC voltage both change according to contrast setting. DC range, from minimum to maximum contrast, is about 145-70 volts (no signal) or 155-130 (strong signal).
- PIN 7** Normally, R1 should be set for zero bias between pin 1 and 7, to swamp out waveform (W2A). Noise-suppression feature is activated by turning R1 so waveshape changes to W2B. Turning control too far disables AGC and sync.


About 1/5 of voltage at pin 3 appears at point A, because of voltage division across R8-R7. At point B, positive voltage fed through R10 opposes AGC bias, until pin-3 voltage reaches about -45 volts. This lets RF amplifier run at full gain under most signal conditions.

SYMPTOM 1

Vertical Roll Horizontal Pulling

Contrast Normal


C5 Open

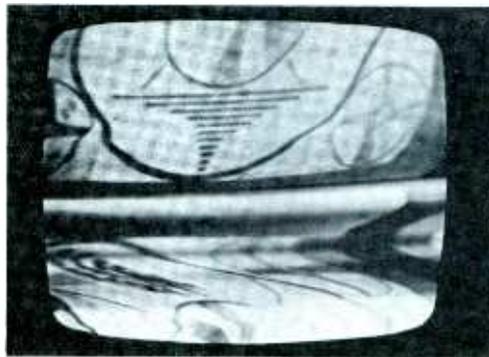

Symptom Analysis

Although complaint is sync trouble, strange white streak through vertical blanking bar points to video-circuit fault. Scope proves video signal is distorted (see below). As part of troubleshooting, fixed bias is substituted for AGC voltage. This removes symptoms, conclusively pin-pointing AGC as origin of distortion.

Voltage and Component Analysis

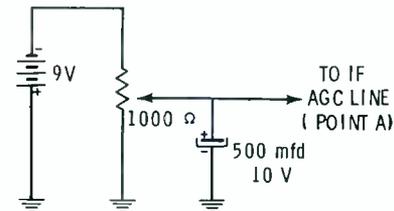

All DC voltages appear normal, whether or not signal is applied. But AGC trouble can be spotted by simple isolation test: *clamping*, or connecting low-impedance source of variable negative voltage to point A. This artificial bias substitutes for missing AGC voltage, or filters out ripple and hum—thus restoring normal video signal and simplifying troubleshooting. Once the isolation test is completed, bias pack may be left connected, to facilitate measurements; in other cases (like this one), AGC line must be unclamped for further attempts at troubleshooting.



Waveform Analysis


Cause of odd white bar in picture is negative pulse which cancels out most of vertical sync pulse in video signal. This pulse shows up plainly in W1 at scope frequency of 30 cps. Also note that horizontal sync pulses are nearly flattened. Naturally, all waveforms in sync circuits are poor. Tracing AGC circuit reveals ripple in W4 at 7875-cps scope frequency; when scope is switched to 30-cps sweep, negative spike is seen. This pulse, which is mixing with IF signal and causing distortion, should have been suppressed by AGC filter network including R5.

SYMPTOM 2

Video Weak or Absent (Except Fringe Reception)

Sound Fairly Normal


R1 Open

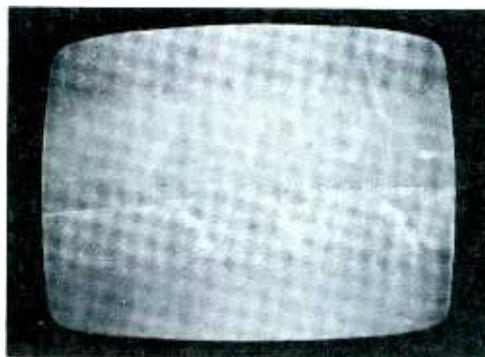


Symptom Analysis

Raster displays normal snow on vacant channels, but is nearly blank when local stations are tuned in. All evidence points to blocking of video output stage by incoming signals—a hint of AGC trouble. Clamping bias applied to point A restores picture, but sync remains critical at all settings of contrast control and R1.

Voltage and Component Analysis

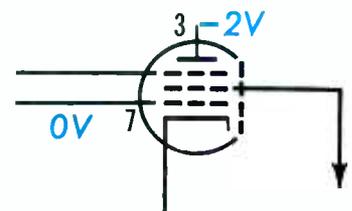

When voltages on 'BU8 are checked, complete loss of DC potential on pin 7 stands out like sore thumb, whether or not AGC line is clamped. Resulting 175-volt bias between pins 1 and 7 keeps both sections of tube solidly cut off. Thus, without clamping, voltage on pin 3 remains close to normal no-signal level of -2 to -3 volts at all times. Since incoming signal overloads video output tube almost to point of cutoff, its plate voltage rises—in turn forcing pin-6 voltage of 'BU8 up to abnormally high level. However, clamping restores correct voltage.

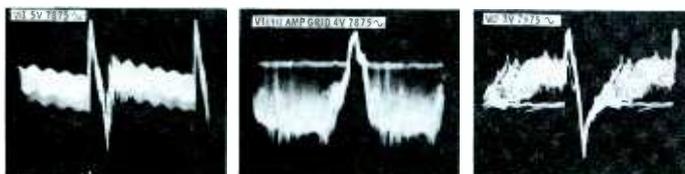

Waveform Analysis


W1 is present, but is misshapen; amplitude is far below normal. Although output signal of video detector is a bit stronger than normal value of 2 to 3 volts p-p, it is inverted; sync pulses in this waveform should be negative. When bias pack is connected, W1 and video waveforms regain proper appearance, but output from sync-separator section of 'BU8 is still almost nonexistent. Scope check at pin 7, in noise-limiter circuit common to both sections of tube, shows unusually large W2A which is unaffected by setting of NOISE GATE control, and is somewhat distorted.

SYMPTOM 3

Excessive Contrast

Horizontal Sync
May Be Unstable

R5 Increased in Value

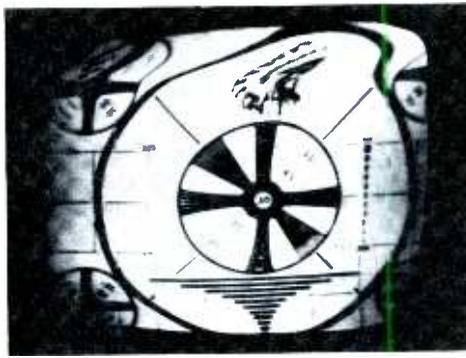

Symptom Analysis

Although slight horizontal pulling and sync buzz are intermittently present, main complaint is "picture too black." Symptoms suggest moderate overdriving of video amplifier by input signal, due to insufficient AGC voltage. Applying variable clamping bias to point A permits adjusting contrast to normal level.




Waveform Analysis

With no artificial bias applied, W1 viewed at either 7875 or 30 cps shows considerable distortion and compression of positive peaks. Output signal of video detector has good waveshape, but amplitude is 9 volts p-p (about three times normal). Clamping restores normal waveforms throughout set. Only scope clue to trouble is furnished by leaving AGC line clamped, setting CRT input at 50 volts p-p, and carefully measuring *amplitude* of W1. The result, 15-20 volts instead of normal 35-40 volts, reveals incorrect division of signal voltage across R5-R6.

Voltage and Component Analysis

DEPENDENT ON CONTRAST
75-125V

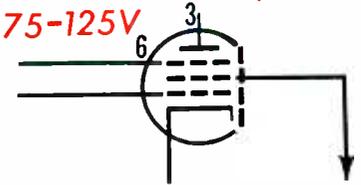


Obtaining usable voltage clues requires extra care in taking readings, plus good understanding of circuit behavior. Here's one pitfall of routine approach to voltage measurement: Although voltage at pin 6 should decrease as result of trouble, this change is likely to be cancelled out by unusually low setting of contrast control, which has effect of *increasing* pin-6 voltage. If R6 instead of R5 had gone up in value, conduction of AGC tube would be above normal, and overproduction of AGC bias would cause weak contrast or even snow in picture on local channels.

SYMPTOM 4

Video Overloading

"Muddy" Picture, Erratic
Sync, Noisy Sound

C4 Leaky

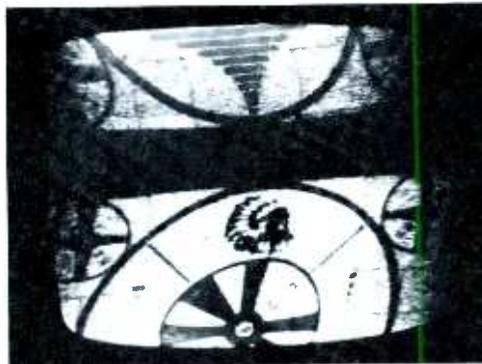

Symptom Analysis

All evidence indicates overdriven video output stage. Touchy sync and flat, dull appearance of picture are signs of clipping or compression in peaks of video waveform. Symptoms are worst on strongest channels—a characteristic indication of AGC trouble. Application of clamping bias to point A restores normal picture.




Waveform Analysis

Without clamping, appearance of W1 varies radically according to picture content of video signal. At times, sync pulses are completely flattened. Overall amplitude of waveform averages about 15-20 volts p-p at pin 6 of 7BU8, but may occasionally rise to 50 volts with severely compressed positive peaks. Abnormalities in this and other waveforms are effects rather than causes of trouble. To cite another example, unusual shape of W2A probably has very little influence on symptoms. Incidentally, W3 appears normal in spite of trouble in plate circuit.

Voltage and Component Analysis

AT ALL TIMES
WITH SIGNAL 170V

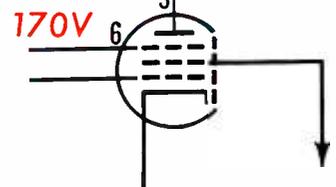

Clamping has drawback of restoring all voltages and waveforms to normal. Thus, it's necessary to disconnect bias pack to accomplish troubleshooting. Even then, voltages on AGC tube are no significant help unless signal is applied. Only exception is positive 1 volt on pin 3, which could easily be overlooked. With signal fed in, plate voltage fails to swing in negative direction—an important clue. Voltage at pin 6 is above normal for existing signal conditions, because plate voltage of video output tube is too high as consequence of this stage being overdriven.

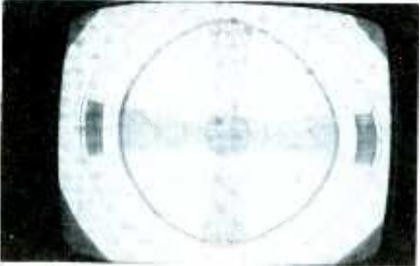
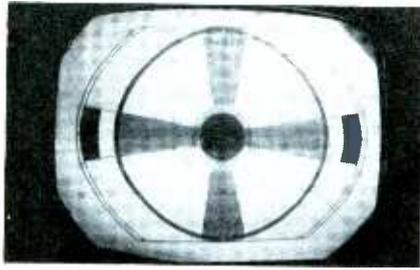


Fig. 1. Loss of contrast detracts greatly from the clarity of the TV picture.

Normal contrast (Fig. 1A) is taken for granted until the TV picture begins to look dull and lifeless. A pale image with no snow (Fig. 1B) makes the set owner begin to worry that his picture tube is going bad. The CRT could possibly be at fault in such cases, but poor contrast with good brightness is much more frequently due to insufficient video-signal input to the cathode or grid of the tube. There's a good chance that replacing the video amplifier (or possibly some other tube in the picture-signal section) will dispose of this problem. If tube changing doesn't help, though, the receiver needs an examination on the bench to find out which circuit is falling down on the job of providing video-signal gain.

In the shop, you may save considerable time by promptly check-

WEAK, WASHED-OUT PICTURES

ing the B+ and filament voltages fed to the CRT and picture-signal stages, and correcting any supply deficiencies before further analyzing the signal circuits. If "underpowering" doesn't account for the low video gain, signal tracing is the best way to proceed in isolating the trouble.

Detector Tests

The first circuit to check is the video detector, which joins the video IF strip to the video-amplifier section. The most important test to be made here is a measurement of signal amplitude at the detector output. A voltage-calibrated scope is the best instrument for this purpose, but a VTVM capable of indicating peak-to-peak AC values will also give usable results.

No hard-and-fast rule can be laid down regarding what is a "normal" video-detector output. Signal amplitude depends on many factors: the strength of the RF signal picked up

by the antenna, the gain available in the front end, the bandwidth utilized in both IF and video-amplifier sections, the design of the AGC circuit, and the tube complement throughout. Although signal values in different sets range all the way from 1 to 10 volts peak to peak, most receivers develop from 1.5 to 3 volts across the detector load.

During the past several years, most TV receivers have been equipped with a high-gain video-amplifier tube in an efficient single-stage circuit having modest input-signal requirements. Detector signals above 5 volts peak to peak, formerly seen in many economy-type sets, are seldom found today. Regardless of the age of a set, by the way, the number of video-amplifier stages it contains has little to do with the signal requirements: in fact, note that the one-stage circuit in Fig. 2 is fed a weaker input than the two-stage circuit in Fig. 3. The extra stage is likely to be included


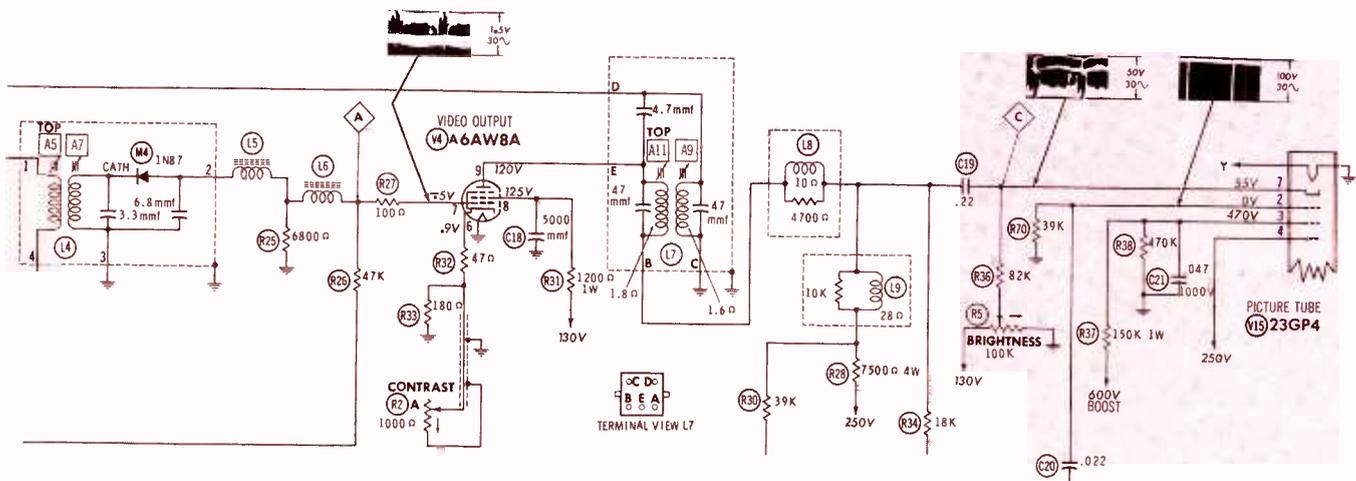


Fig. 2. Most TV receivers obtain adequate picture-signal gain from a one-stage video amplifier.

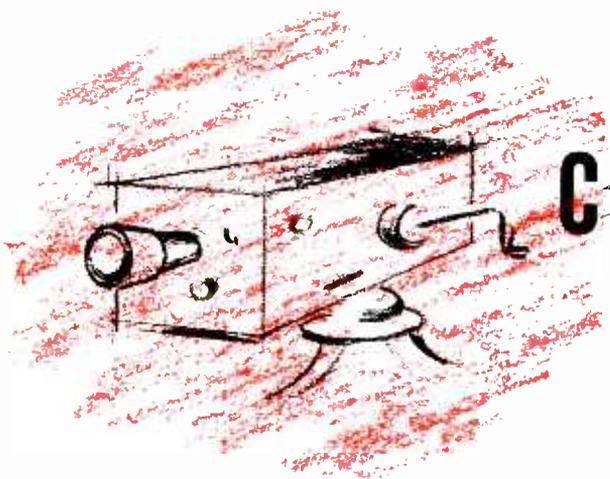

closed circuit TV is opening up!

Its growth rate is linked to the caliber of service available. — by Leo G. Sands

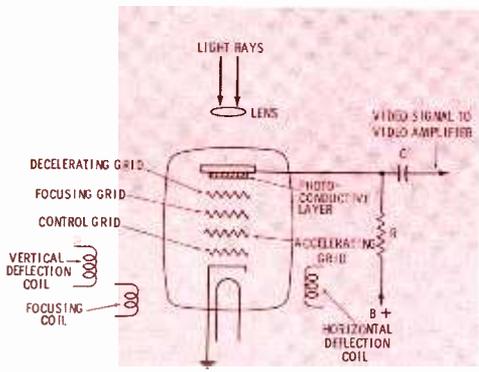


Fig. 1. Vidicon tube is very similar in general construction to ordinary CRT.

Servicing and installing closed-circuit TV systems can be a lucrative full-time or sideline activity for the service technician with TV-servicing experience. Sales of closed-circuit TV (CCTV) systems are rising, and they will be considerably greater when potential buyers are assured of readily available maintenance. The growth of this field, as

well as other branches of industrial electronics, is being retarded by the lack of service—when needed—at reasonable cost.

Who Uses Them?

Thousands of CCTV systems, sometimes called industrial television (ITV), are in use. At the world's busiest railroad station—Pennsylvania Station in New York—batteries of CCTV cameras are trained on Pullman-space diagrams. Each ticket window is equipped with a TV monitor on which the passenger may see the location of the Pullman space he is to occupy. At certain busy airports, a TV camera views the departure-arrival board, and the image is reproduced on numerous TV monitors in the airport terminal.

Banks use CCTV for remote viewing of checks and signature cards. In steel mills, machine oper-

ators can view and control dangerous operations from a point of complete safety.

A major automobile manufacturer plans to install closed-circuit cameras at infrequently used gates, which would otherwise have to be manned by guards at all times.

A wired-music-service operator plans to install CCTV monitors in bars and restaurants; printed announcements, filmed or taped programs, and special live broadcasts will be transmitted to these units.

All of these existing and planned CCTV installations must be serviced. This maintenance must be performed by employees of the system owners, by the CCTV distributor, or by independent service technicians.

CCTV opportunities will expand even more as soon as slow-scan TV systems become more readily available. Slow-scan systems can be used for transmission of documents, still scenes and (sometimes) slow-moving scenes. Instead of requiring coaxial cable or microwave, slow-scan TV signals can be transmitted over an ordinary voice-grade telephone line.

In one of these systems, the picture to be transmitted is mechanically scanned by a photoelectric cell, and the picture is built up on the screen of a monitor employing a long-persistence picture tube. Another slow-scan system prints the picture on photosensitive paper, leaving a permanent record of the scene. It can even be used to take a picture of a slow-moving train.

The market for CCTV service

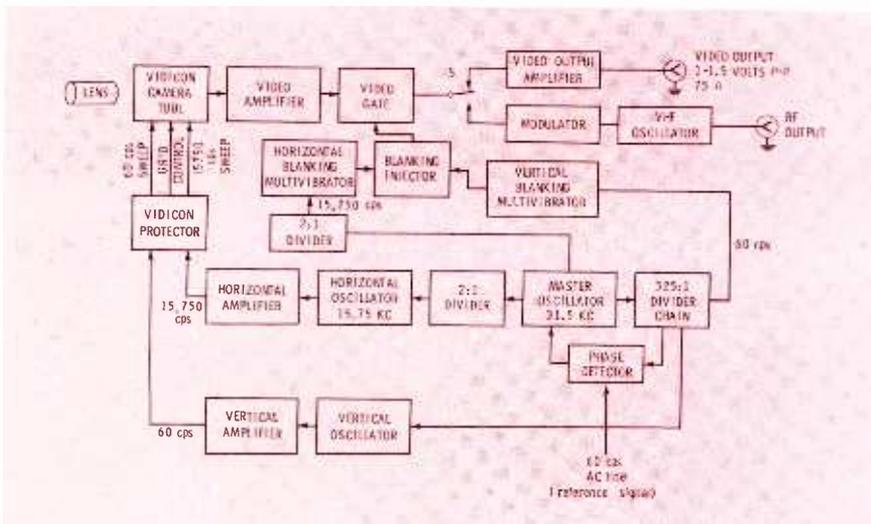


Fig. 2. Block diagram of camera using vidicon tube, showing circuit layout.

will grow quickly when educational institutions start taking advantage of federal ETV grants. Qualified schools will be eligible for matching funds for the purchase of educational TV equipment, including CCTV cameras, monitors, and transmission equipment.

A recent survey reveals that a large number of schools and colleges plan to use CCTV and that most of them will install facilities for transmitting TV programs between campus buildings and to off-campus points. One big-city university plans to transmit TV programs to 30 locations. Another major university plans to transmit TV—via wire lines—from its main campus to locations more than 100 miles away. Servicing these systems would be much less a problem if local maintenance were available for the CCTV equipment at each of the locations served.

The Equipment

A CCTV system may be very simple, consisting of a single camera and monitor, or it can be as complex as a network-TV facility. The basic equipment, however, is no more complex than an ordinary TV receiver. Some CCTV cameras deliver only a video signal and require the use of a special monitor or modified TV receiver. Others contain an RF signal generator, the output of which is modulated by the video signal; the modulated signal is then fed through coax or twin-lead—or sometimes an antenna distribution system—to the antenna terminals of regular home-type TV receiving sets.

To transmit TV programs from one building to another, coaxial cable or a microwave link is generally utilized. If the buildings are on the same parcel of property, and it is not necessary to cross public thoroughfares, a coaxial-cable system may be installed. But, if the buildings are separated by public thoroughfares, it is usually necessary

Partial List of CCTV Equipment Manufacturers

Adler Electronics, Inc. 1 Le Fevre, New Rochelle, N.Y.	Jerrold Electronics 15th & Lehigh, Philadelphia, Pa.
Avco Corp., Crosley Div. 1329 Arlington, Cincinnati, Ohio	Kay Electric Co. 14 Maple Ave., Pinebrook, N.J.
Bencix Aviation, Friez Instrument Div. 1400 Taylor, Baltimore, Md.	Miratel, Inc. 1st St. S.E. & Richardson, New Brighton 12, Minn.
Blonder-Tongue Labs 9 Alling St., Newark 2, N.J.	Motorola Comm. & Electronics, Inc. 4501 W. Augusta Blvd., Chicago 5, Ill.
Dage TV Division W. 10th St., Michigan City, Ind.	Packard Bell Electronics Corp. 12333 W. Olympic, Los Angeles 64, Calif.
DuMont Labs 750 Bloomfield Ave., Clifton, N.J.	Radio Corporation of America Camden 2, N.J.
Fairchild Camera & Instrument Corp. Rebbins Lane, Syosset, N.Y.	Setchell-Carlson, Inc. New Brighton 12, Minn.
General Precision, GPL Div. 63 Bedford Rd., Pleasantville, N.Y.	Sylvania Electric Products, Inc. 1100 Main St., Buffalo, N.Y.
General Electric, Comm. Products Div. Lynchburg, Va.	Thompson Ramo Wooldridge 23555 Euclid Ave., Cleveland, Ohio
Lear-Siegler, Inc., Hallamore Electronics Div. 714 N. Brookhurst, Anaheim, Cal.	Vicon Corporation 1369 Industrial, San Carlos, Calif.
ITT Federal Div. 100 Kingsland Rd., Clifton, N.J.	

that TV transmission lines be leased from the local telephone company.

Typically, the cost of leasing a CCTV transmission circuit runs around \$20 per quarter-mile per month for local service. For long runs, the rate may drop as low as \$45 per mile per month. In addition to rental charges, installation costs must be paid and a five- or ten-year contract is generally demanded. There is also a charge for rental of the equipment which connects the CCTV equipment to the facilities of the phone company. When a long, privately-owned coaxial cable is used, it may be necessary to install line amplifiers to make up for transmission losses, and equalizers to adapt the signal to cable characteristics.

How It All Works

CCTV systems employ cameras which utilize a vidicon tube for picking up images. A vidicon tube is small and costs only a fraction as much as the image orthicon used in most commercial TV broadcasting.

In a vidicon TV camera, the image is focused by a lens on a

photoconductive layer which is the anode signal element, and which is held at a positive potential (see Fig. 1). A beam of electrons emitted from the cathode passes through four grids on its way to the photoconductive signal anode. The beam is electromagnetically swept 15,750 times horizontally and 60 times vertically per second by deflection coils arranged around the neck.

Video and Sweep Signals

As the beam scans the photoconductive layer, anode current rises whenever the beam passes a point illuminated by the image. This causes current through load resistor R to vary, resulting in a video-signal voltage which is fed through the coupling capacitor to the video amplifier.

As illustrated in the block diagram (Fig. 2), this amplified video signal is fed to a video-gate or mixer stage, where blanking pulses are added. The composite signal is fed to a video output stage and thence to a TV monitor—sometimes directly or through a switching ar-

• Please turn to page 92

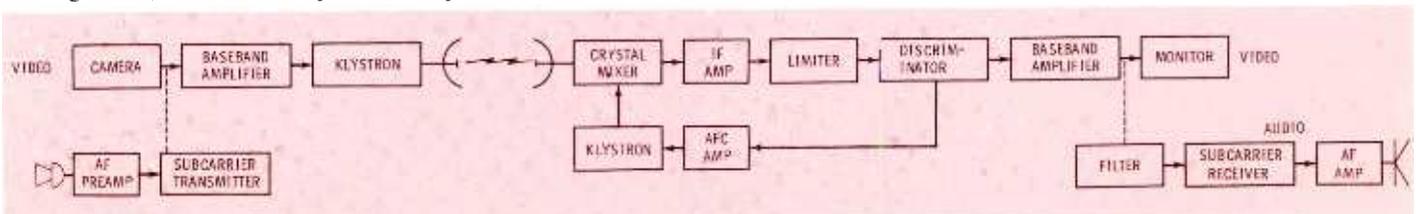


Fig. 3. Unidirectional microwave link which also includes a sound channel.



They're Transistorizing TV Remotes

New receiver units draw only a trickle of standby current... by George F. Corne Jr.

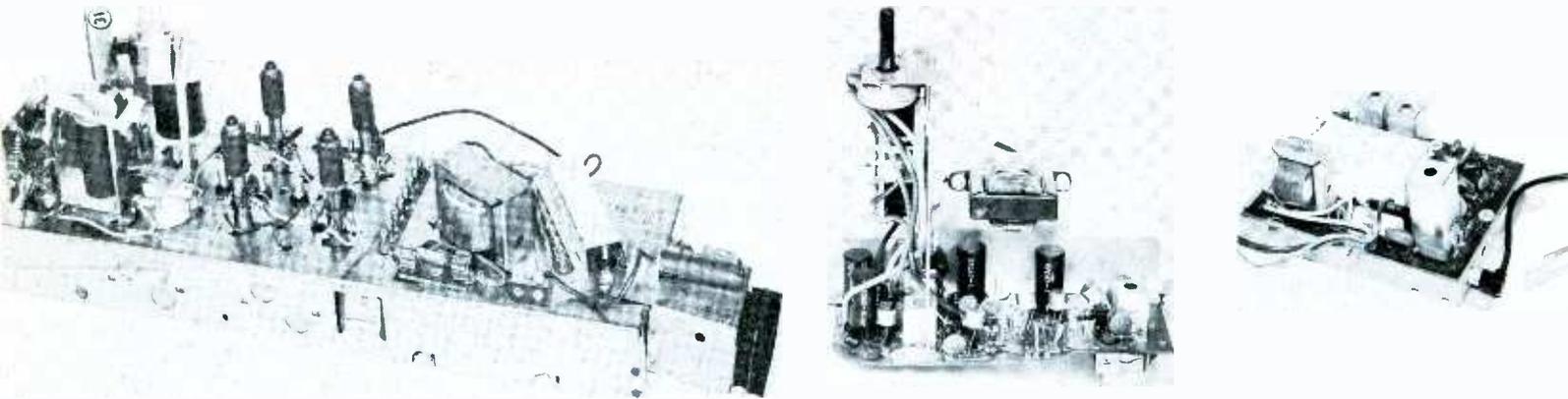


Fig. 1. Transistorized TV remote receivers of different shapes and sizes.

The majority of the remote control receivers in the latest TV models contain all-transistor circuitry. PNP transistors are the kind you'll find in most sets—generally from 6 to 8, depending on the number of remote operations the set is required to perform. Ordinarily, four transistors function as RF amplifiers in the

40-kc frequency region, and the remaining ones serve as driver or relay-control stages. As in tube-type remotes, various relays are energized by incoming signals to complete the electrical path for motors, volume switches, and similar components.

The design of remote transmitters

has not changed appreciably; the familiar transistor-oscillator types and mechanical tone generators are both still used. For this reason, we won't concern ourselves with transmitters in this article, but will direct our full attention to transistor receivers.

Fig. 1 shows some of the physical

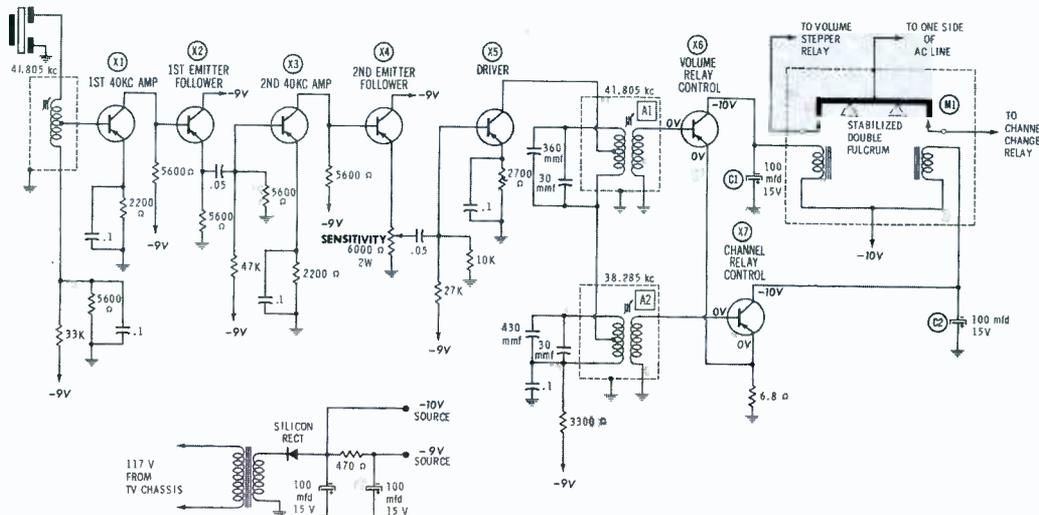


Fig. 2. Received signal is amplified to high enough level to drive relay-control transistors into conduction.

shapes and sizes of the transistorized remotes you'll be seeing in new TV sets.

Stage Functions

The actual circuits, as well as the functions, are basically no different from one transistorized remote to another. The unit shown schematically in Fig. 2 is representative of those being used at the present time. We'll first review some pertinent facts about circuit functions, and then suggest a few procedures to help you isolate a defective stage in any transistor remote.

Power for the remote receiver is normally obtained from the AC input circuit of the TV set, via a step-down transformer and half-wave silicon rectifier. These transistorized devices have low current requirements—an important advantage in a unit which is customarily left operating even when the rest of the TV set is turned off.

Methods used to couple the incoming signal to the base of the first amplifier vary in different models, but capacitive or direct coupling to a tuned input coil is found in the majority of sets. Some have an untuned input; in this case, a tuned circuit is located in one of the later amplifier stages.

In some receivers, certain RF stages are emitter followers. No gain is realized from these stages (X2 and X4 in Fig. 2), but this type of circuit results in good impedance matching between amplifiers.

Driver stage X5 has two tuned transformers in its collector load circuit—one tuned to 41.805 kc and the other to 38.285 kc. Through these, the incoming signal is coupled to relay-control transistors X6 and X7, which are biased at cutoff under no-signal conditions. The negative portion of the incoming signal causes one of these PNP transistors to conduct. Collector current then energizes one side of relay M1, completing the path for one of the remote-controlled functions. (Fig. 3 is a close-up photo of this bistable relay.)

Capacitors C1 and C2, wired in the collector circuits of the control transistors, smooth out the current through the relay to keep it from chattering. They also filter out noise pulses, which might otherwise cause

erroneous relay operation. Remember these components if you have a set which changes channels, or performs some other remote function, without a signal from the transmitter. Also, when a set is troubled by this *noise keying* effect, check to see if it includes a sensitivity control which can be used to vary the operational gain of the receiver. If such a control is used in the remote you're called on to service, adjust it for the least gain needed to obtain adequate remote operation. Seldom will it need to be set above the half-way point in its rotation; too high a setting could defeat its purpose.

Remote Control for Rotators

Circuits similar to those just described are also found in a transistorized remote control recently introduced for use with antenna rotator systems. In addition, the electro-mechanical sequence of relay operation in this unit is practically the same as in TV remotes. Much of the following description of rotator-control circuitry therefore applies equally well to TV-control functions such as remote adjustment of volume.

The "rotator remote" merely duplicates the electrical function of a three-position push-button switch located on the main rotator-control box. Spring loaded to the *off* position, this switch is used to start the rotor turning either clockwise or counterclockwise. Rotation will continue as long as this button is held down.

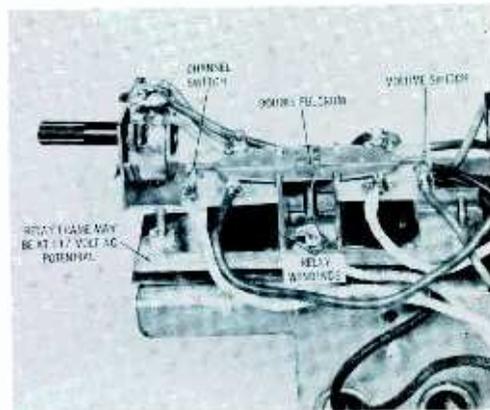


Fig. 3. Transistor collector current energizes one side of relay at a time.

In remote operation, a 46-kc pulse is transmitted by pressing a button on a hand-held *actuator* unit (a mechanical tone generator of the type used with TV's). Picked up by a transistorized receiver, this signal is first amplified and then used to energize relay M1 (Fig. 4) for the duration of the pulse. M1 closes switch S1, completing a current path for stepper relay M2. As M2 operates, the three cams on the actuating arm of this relay (see Fig. 5) cause the individual sections of S2 (A, B and C) to operate in the sequence shown in the chart in Fig. 4.

The A section is connected, via a plug and socket, in series with the motor-transformer in the rotator-control primary circuit. Sections B and C are likewise in series with the secondary of this transformer. The B section completes the circuit for

• Please turn to page 101


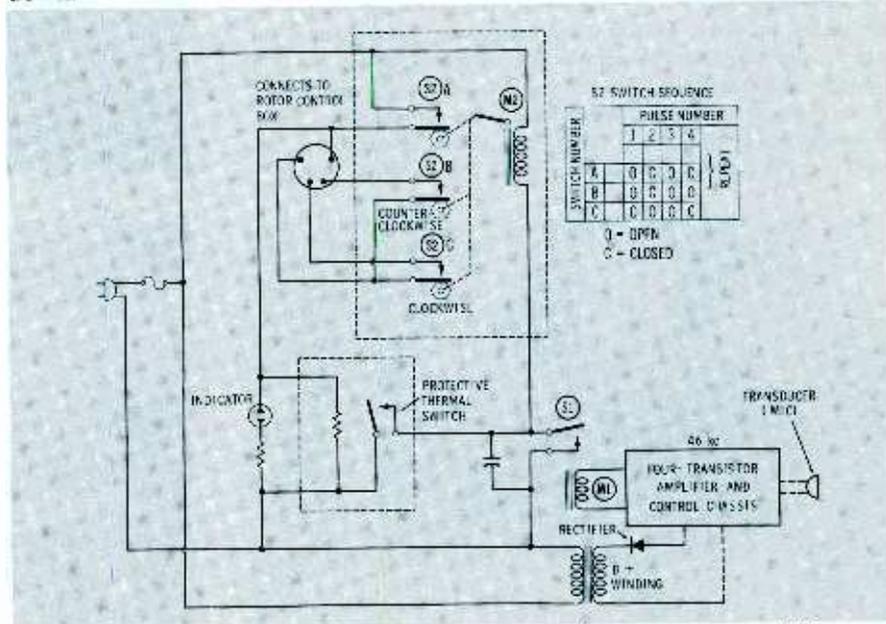




Fig. 4. Remote-control circuits used to start and stop antenna rotation.

fixing Record Changers *is a cinch!*

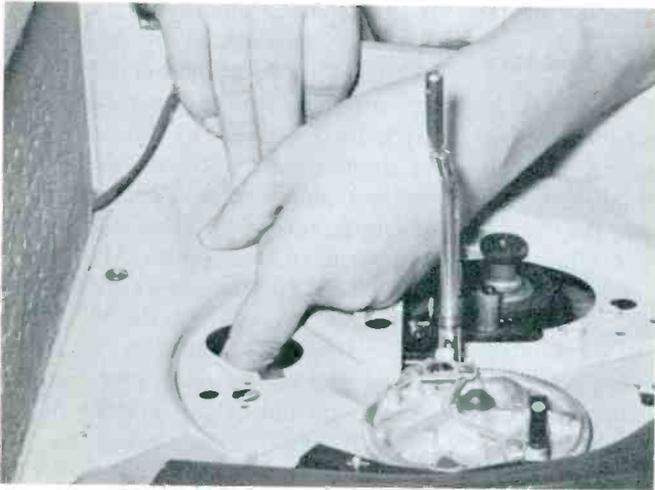


◀ To the uninitiated, getting the changer mechanism out of the cabinet for servicing occasionally presents something of a problem. The unit shown here is typical of changers with "hidden" hold-down clips. After first removing the turntable, you can release one clip by reaching through the access hole; one side of the changer platform can then be lifted and the unit slid sideways out of the mounting board. If you plan to take the mechanism completely out of the cabinet, be sure to disconnect the motor-power and cartridge cables.

One of the most common complaints with changers ▶ is improper set-down or landing of the tone arm; the needle either misses the record or lands past the beginning of the music grooves. Almost invariably, this adjustment is controlled by a spring-loaded screw at the base of the tone arm. Two typical screwdriver adjustments are shown here; not shown is a third type which can be reached from above, after lifting the tone arm to expose the adjusting screw. The small 45-rpm changer shown in the photo below is adjusted by loosening the tone-arm set screw, and placing the arm at its proper location on the spindle. Any inability to control the landing adjustment of a changer can be traced from the adjustment, back through the spindle, to the timing wheel or cam (or the slide) in the mechanism below, until the fault is found.

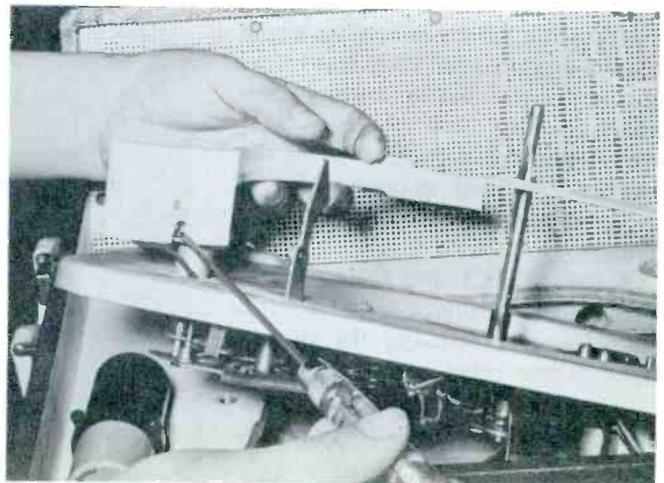
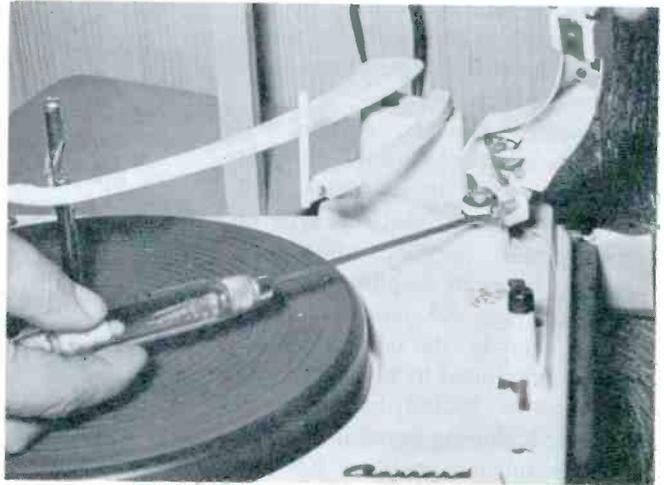



Any record-changing mechanism, although seemingly complex, actually goes through a "simple" series of inter-related actions. Various mechanical adjustments control these actions, setting the starting and finishing points of the different movements of certain slides, wheels, and/or cams. If you can understand the adjustments, and their locations, you will have little problem applying this knowledge to trace a changer-mechanism fault to its source. The photos show the various adjustment points, and the captions indicate how to apply this system of reasoning to changer troubleshooting.

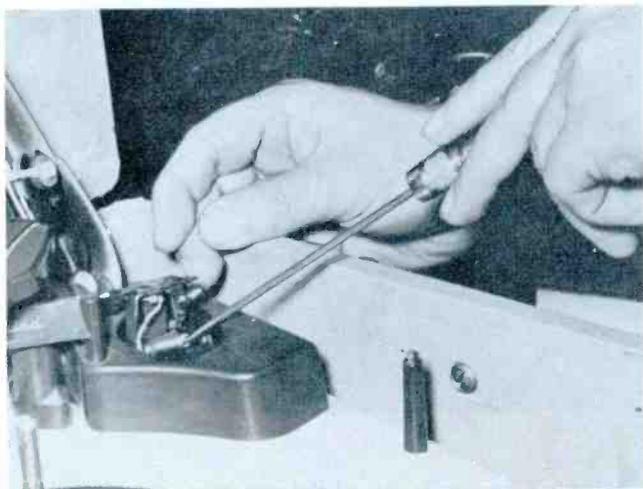

Needle-tracking pressure is important to modern changers. This is usually controlled by an adjustment at or near the base of the tone arm, as shown in the two photos. Some changers use a screwdriver adjustment to set the balance of the arm, while others use a simple spring arrangement (as shown in the photo to the right). Still other, more elaborate units have counterbalance weights somewhere on the base end of the tone arm. In any case, this is probably the simplest of the various adjustments. Since very little can go wrong with this portion of the mechanism, any fault involving needle pressure or tracking will be easy to trace. If a gram gauge indicates correct pressure at the needle end of the arm, any tracking fault (such as skipping) is probably caused by the needle or cartridge being improperly mounted. ▼



▲ During the change cycle, the arm may sometimes fail to clear a large stack of records. The arm height is controlled by an adjustment, usually in conjunction with a lift rod in the spindle. The adjustment, as indicated in the photos, may be reached from the top of the tone arm, from its underside, or at the base. The photo on the left shows a spring-and-drum arrangement, which can be adjusted with any small-diameter pointed instrument by merely inserting the point and revolving the drum. Faulty arm-height action can usually be traced through the lift rod (in the spindle) to the timing wheel or slide below. On the timing device—or associated with it—you will find some form of inclined plane which raises and lowers the tone arm as the changer goes through its cycle. Check these parts in the event of arm-height trouble.

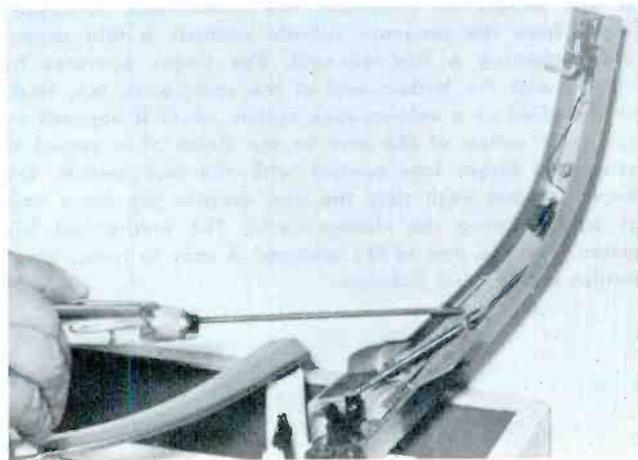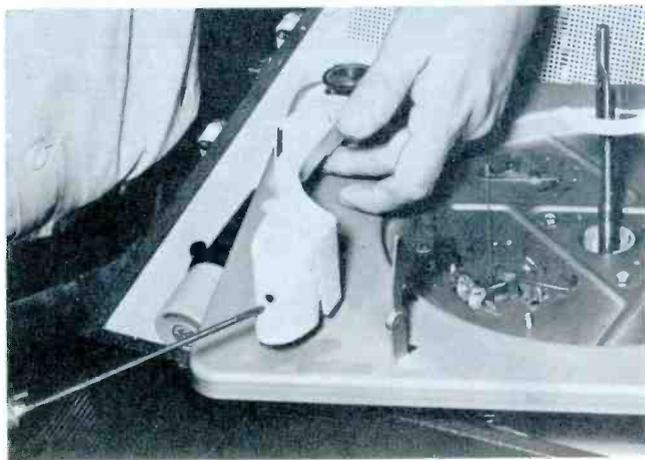

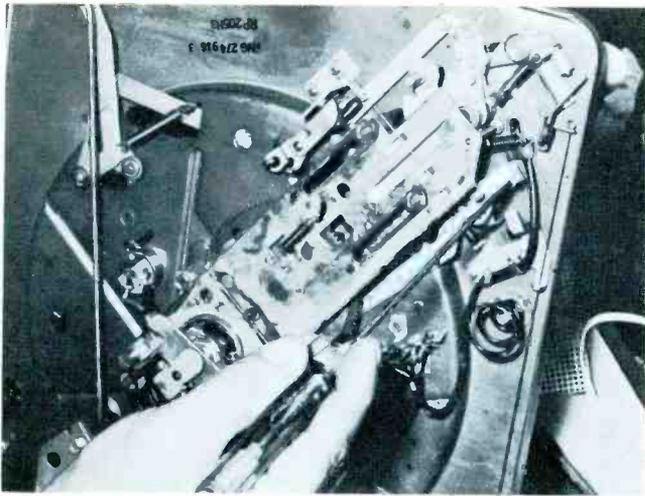


When a changer trips before completing a record, or fails to initiate the change cycle after the record is finished, the fault lies in the trip-mechanism adjustment (or its associated actions). The greatest differences you will find in record changer adjustments are in these mechanisms. In this photo, one of the more common trip mechanisms is depicted. The trip lever is adjusted to actuate the mechanism at just the proper tone-arm position by bending the tab indicated by the screwdriver. This tab is contacted by a finger from the tone arm, and is set to trip the mechanism when the needle reaches the inner groove of the recording.

There are a large number of variations in trip mechanisms, as well as in the method of adjusting the various linkages. This photo shows a changer whose trip lever has an action similar to the one described above, but the length of this lever can be adjusted by means of a set screw. This lever, too, is actuated by a finger from the tone-arm spindle. Both trip levers described actuate a mechanism which initiates the change cycle; therefore, any failure of the changer to properly begin or end a change cycle can be traced from the tone-arm finger, through the trip lever and its linkages, to the actual cycling mechanism (and its drive arrangement).

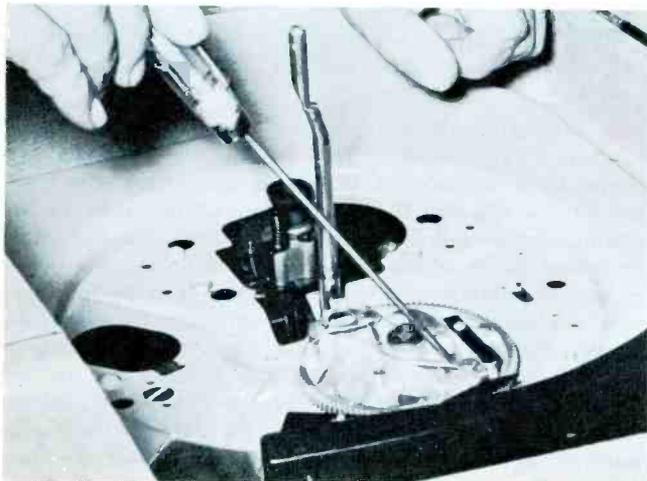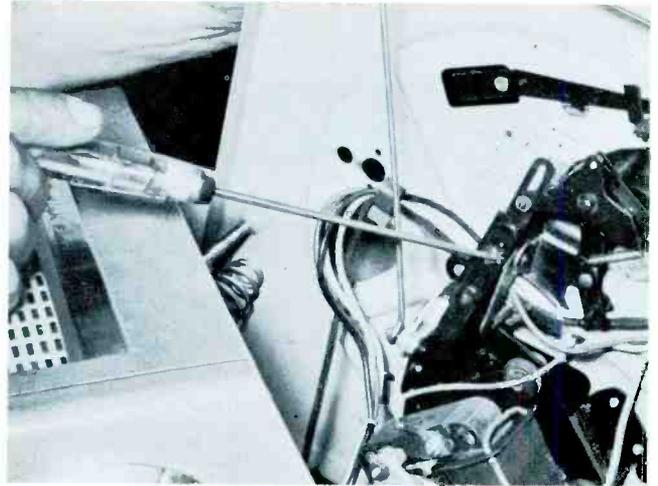

The mechanism in this photo represents a typical velocity-type trip arrangement. It depends on the quick movement of the tone arm as the needle enters the eccentric lead-out groove in the center of the recording. This system requires that each of the parts in the "chain" of action have absolute freedom of movement. They must, consequently, be kept very clean, and free from oil and dirt. (Alcohol is an excellent cleaning agent for these parts.) When a system of this type gets out of adjustment, it is usually very difficult to realign. Often, replacement of the entire assembly is more expedient, and less expensive, since the cost of parts is usually rather minimal.

A somewhat different type of trip device is shown in this picture—an electrical trip mechanism. A copper finger from the tone-arm spindle contacts a thin copper leaf, actuating a trip solenoid. The finger operates by friction with the bottom end of the spindle. It, too, could be classified as a velocity-type system, since it depends on the quick action of the arm at the finish of a record to bring the finger into contact with the leaf switch. The finger is reset each time the arm reaches the outer limit of travel during the change cycle. The mechanical trip action from the arm of the solenoid is easy to trace, being similar to other trip linkages.

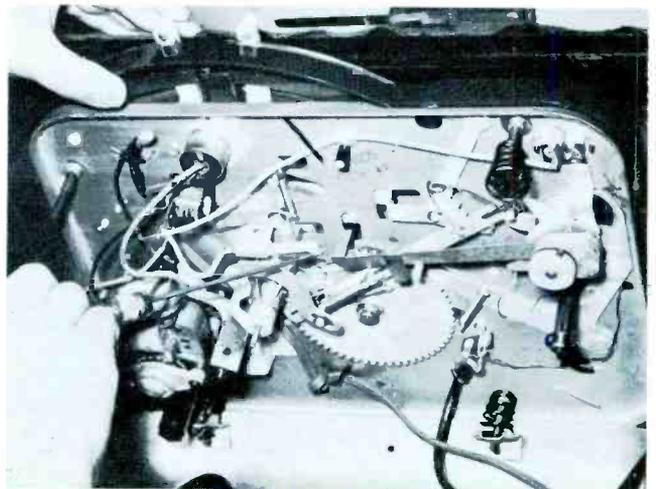



are you replacing top quality tubes with identical top quality tubes?

You can, now! You can carry the identical tubes that you find in most of the quality TV sets you're servicing. Chances are, you were not aware that these sets were designed around special Frame Grid tubes originated by Amperex.

For some time now designers have been using many Amperex Frame Grid tubes in their quality TV receivers and we can tell you now that even more Amperex tubes are being designed into the sets you'll be handling in the future.

Compare, if you will, the performance of Amperex Frame Grid tubes with conventional IF tubes: they provide 55% higher gain-bandwidth, increase TV set reliability by simplifying circuits and they make your servicing easier, faster and more profitable because their extraordinary uniformity virtually eliminates time-consuming realignment when you replace tubes. Technicians are finding Amperex THE line to carry.


Tubes introduced by Amperex and currently being used by major TV set makers include:

<i>Frame Grid</i>				<i>Others</i>	
2GK5	4GK5	6GK5	6EH7	6AL3	9A8
2ER5	4EH7	6ES8	6EJ7	6BL8	15CW5
3GK5	4EJ7	6ER5	6HG8	6BQ5	16AQ3
3EH7	4ES8	6FY5	7HG8	12AX7	27GB5


For optimum customer satisfaction and maximum profit operation for yourself, make room in your caddy right now for the identical, matchless-quality tubes designed into the original sets. Next time you visit your distributor look for the green-and-yellow box and ask about Frame Grid tubes for TV and other entertainment replacement applications. Amperex Electronic Corporation, 230 Duffy Ave., Hicksville, L. I., N. Y. In Canada: Philips Electron Devices Ltd., 116 Vanderhoof Ave., Toronto 17.

Finding the Right Alignment Tool

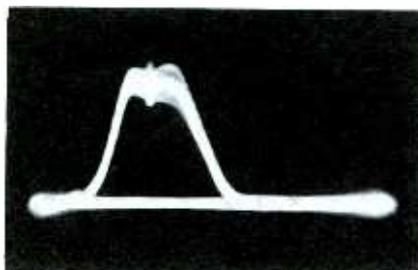
Be ready to align any equipment that comes to your shop . . . by Jim Galloway



(A) Normal response before tuning.

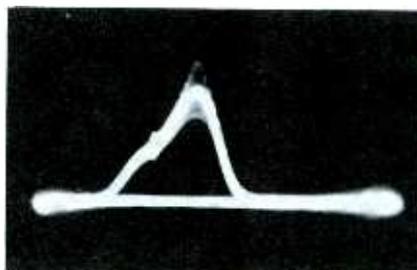

(B) Using metal screwdriver blade.

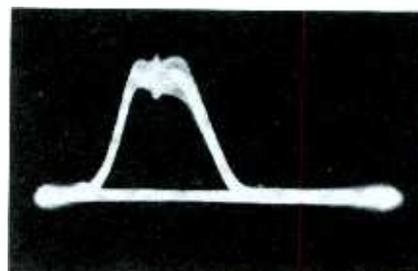

(C) Using plastic alignment tool.

Fig. 1. Effect on IF response when tip of tool is inserted in transformer.

Fig. 1 shows graphically how important it is to use proper alignment tools when you are adjusting tuned transformers. The waveform in part A is that of a normal IF response curve. Part B shows what happens to this curve while a steel-bladed screwdriver is being used to tune the transformer slug; Fig. 1C shows the same waveform when a non-magnetic alignment tool is used. You can see from these pictures that it's next to impossible to properly tune a transformer with a tool that distorts the frequency response.

Granted, you can get by with using an ordinary screwdriver, if you

turn the slug only slightly, and then withdraw the screwdriver blade to observe the change in tuning. After repeating this procedure several times, you might find the correct setting; however, this inefficient process wastes much time. Such makeshift techniques are seldom needed by the technician who makes a point of accumulating a good selection of alignment tools.

Literally dozens of special tool types are used in day-to-day servicing. Although the great majority of coil cores commonly found in home entertainment equipment can be adjusted with only a few basic tools,

many modifications of these general types have been made available for increased convenience in servicing. Tools with standard tip shapes are supplied in many different lengths, ranging from a little more than one inch to slightly over a foot and a half. They are also manufactured of several different materials, and to add further variety, there are many double-ended tools with different combinations of tips.

The roster of alignment tools also contains a number of special-purpose items with unusual tip styles. Almost every major innovation in electronics brings with it some new alignment-tool requirement. For example, the IF transformers in some portable transistor radios have square holes in the slugs, instead of the usual hexagonal or slotted arrangement.

Color TV has been another influence on the expansion of alignment-tool types. Most color sets have one or more concentric potentiometers; often two different sizes are found in the same set. Efficient adjustment of these controls requires the use of a special tool that allows simultaneous adjustment of inner and outer shafts. Many of these tools have facilities for adjusting both sides of concentric controls commonly encountered.

The assortment of tools shown in Fig. 2 gives some idea of how many

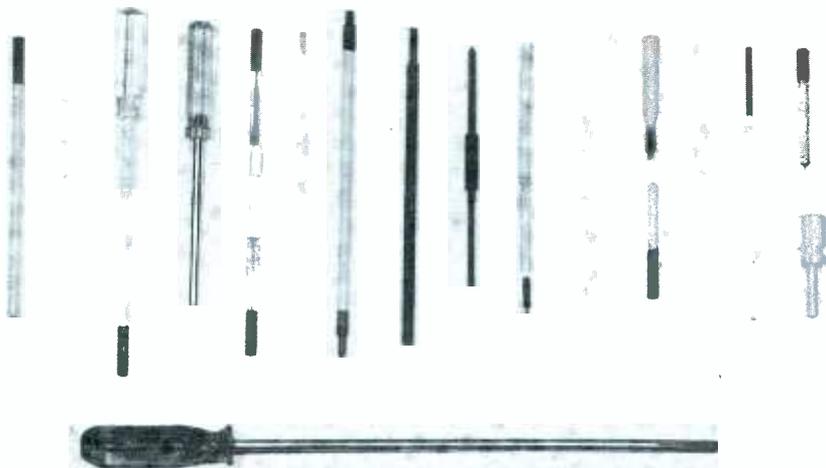


Fig. 2. Radio-TV service shops have uses for all these alignment tools.

What Does F. C. C. Mean To You?

What is the F. C. C.?

F. C. C. stands for Federal Communications Commission. This is an agency of the Federal Government, created by Congress to regulate all wire and radio communication and radio and television broadcasting in the United States.

What is an F. C. C. Operator License?

The F. C. C. requires that only qualified persons be allowed to install, maintain, and operate electronic communications equipment, including radio and television broadcast transmitters. To determine who is qualified to take on such responsibility, the F. C. C. gives technical examinations. Operator licenses are awarded to those who pass these examinations. There are different types and classes of operator licenses, based on the type and difficulty of the examination passed.

What are the Different Types of Operator Licenses?

The F. C. C. grants three different types (or groups) of operator licenses—commercial radiotelePHONE, commercial radioteleGRAPH, and amateur.

COMMERCIAL RADIOTELEPHONE operator licenses are those required of technicians and engineers responsible for the proper operation of electronic equipment involved in the transmission of voice, music, or pictures. For example, a person who installs or maintains two-way mobile radio systems or radio and television broadcast equipment must hold a radiotelePHONE license. (A knowledge of Morse code is NOT required to obtain such a license.)

COMMERCIAL RADIOTELEGRAPH operator licenses are those required of the operators and maintenance men working with communications equipment which involves the use of Morse code. For example, a radio operator on board a merchant ship must hold a radioteleGRAPH license. (The ability to send and receive Morse is required to obtain such a license.)

AMATEUR operator licenses are those required of radio "hams"—people who are radio hobbyists and experimenters. (A knowledge of Morse code is necessary to be a "ham".)

What are the Different Classes of RadiotelePHONE licenses?

Each type (or group) of license is divided into different classes. There are three classes of radiotelePHONE licenses, as follows:

(1) Third Class RadiotelePHONE License. No previous license or on-the-job experience is required to qualify for the examination for this license. The examination consists of F. C. C. Elements I and II covering radio laws, F. C. C. regulations, and basic operating practices.

(2) Second Class RadiotelePHONE License. No on-the-job experience is required for this examination. However, the applicant must have already passed examination Elements I and II. The second class radiotelePHONE examination consists of F. C. C. Element III. It is mostly technical and covers basic radiotelePHONE theory (including electrical calculations), vacuum tubes, transistors, amplifiers, oscillators, power supplies, amplitude modulation, frequency modulation, measuring instruments, transmitters, receivers, antennas and transmission lines, etc.

(3) First Class RadiotelePHONE License. No on-the-job experience is required to qualify for this examination. However, the applicant must have already passed examination Elements I, II, and III. (If the applicant wishes, he may take all four elements at the same sitting, but this is

not the general practice.) The first class radiotelePHONE examination consists of F. C. C. Element IV. It is mostly technical covering advanced radiotelePHONE theory and basic television theory. This examination covers generally the same subject matter as the second class examination, but the questions are more difficult and involve more mathematics.

Which License Qualifies for Which Jobs?

The THIRD CLASS radiotelePHONE license is of value primarily in that it qualifies you to take the second class examination. The scope of authority covered by a third class license is extremely limited.

The SECOND CLASS radiotelePHONE license qualifies you to install, maintain, and operate most all radiotelePHONE equipment except commercial broadcast station equipment.

The FIRST CLASS radiotelePHONE license qualifies you to install, maintain, and operate every type of radiotelePHONE equipment (except amateur, of course) including all radio and television stations in the United States, and in its Territories and Possessions. This is the highest class of radiotelePHONE license available.

How Long Does it Take to Prepare for F. C. C. Exams?

The time required to prepare for FCC examinations naturally varies with the individual, depending on his background and aptitude. Grantham training prepares the student to pass FCC exams in a minimum of time.

In the Grantham correspondence course, the average beginner should prepare for his second class radiotelePHONE license after from 300 to 350 hours of study. This same student should then prepare for his first class license in approximately 75 additional hours of study.

In the Grantham resident course, the time normally required to complete the course and get your license is as follows:

In the M thru F DAY course, you should get your first class radiotelePHONE license at the end of the 12th week of classes.

In the M-W-F EVENING course, you should get your first class radiotelePHONE license at the end of the 20th week of classes.

In the Tu-Th EVENING course, you should get your first class radiotelePHONE license at the end of the 30th week of classes.

The Grantham course is designed specifically to prepare you to pass FCC examinations. All the instruction is presented with the FCC examinations in mind. In every lesson test and pre-

examination you are given constant practice in answering FCC-type questions.

Why Choose Grantham Training?

The Grantham Communications Electronics Course is planned primarily to lead to an F. C. C. license, but it does this by TEACHING electronics. This course can prepare you quickly to pass F. C. C. examinations because it presents the necessary principles of electronics in a simple "easy to grasp" manner. Each new idea is tied in with familiar ideas. Each new principle is presented first in simple, everyday language. Then after you understand the "what and why" of a certain principle, you are taught the technical language associated with that principle. You learn more electronics in less time, because we make the subject easy and interesting.

Is the Grantham Course a "Memory Course"?

No doubt you've heard rumors about "memory courses" or "cram courses" offering "all the exact FCC questions". Ask anyone who has an FCC license if the necessary material can be memorized. Even if you had the exact exam questions and answers, it would be much more difficult to memorize this "meaningless" material than to learn to understand the subject. Choose the school that teaches you to thoroughly understand—choose Grantham School of Electronics.

Is the Grantham Course Merely a "Coaching Service"?

Some schools and individuals offer a "coaching service" in FCC license preparation. The weakness of the "coaching service" method is that it presumes the student already has a knowledge of technical radio and approaches the subject on a "question and answer" basis. On the other hand, the Grantham course "begins at the beginning" and progresses in logical order from one point to another. Every subject is covered simply and in detail. The emphasis is on making the subject easy to understand. With each lesson, you receive an FCC-type test so you can discover daily just which points you do not understand and clear them up as you go along.

Advanced Resident Training

The Grantham F. C. C. License Course is Section I of our Electronics Series. Successful completion of this course is a prerequisite for enrollment in Section II which deals with more advanced material. However, it is not necessary for the student to take Section II unless he wishes to advance beyond the level of a first class F. C. C. License.

Accredited by the National Home Study Council



What NHSC Membership Means:

Over the years, people have come to respect membership in the National Home Study Council as a hallmark of quality. No school can be a member of the Council unless it has met the rigid standards set up by the Council's Accrediting Commission. This means that all schools, such as Grantham Schools, Inc., which display the seal of the National Home Study Council have demonstrated their integrity and adherence to high ethical standards. It means that they offer quality instruction at reasonable tuition rates. It means that these schools believe in, and are specialists in, the home study method of instruction.

For further details concerning F. C. C. licenses and our training, send for our FREE booklet, "Grantham Training". Clip the coupon below and mail it to the School nearest you.

Get your First Class Commercial F. C. C. License Quickly by training at



GRANTHAM SCHOOL OF ELECTRONICS

1505 N. Western Ave. Los Angeles 27, Calif. (Phone: HO 7-7727)
408 Marion Street Seattle 4, Wash. (Phone: MA 2-7227)
3123 Gillham Road Kansas City 9, Mo. (Phone: JE 1-6320)
821-19th Street, N.W. Washington 6, D. C. (Phone: ST 3-3614)

MAIL COUPON NOW — NO SALESMAN WILL CALL →

(Mail in envelope or paste on postal card)

 **To: GRANTHAM SCHOOL OF ELECTRONICS
NATIONAL HEADQUARTERS OFFICE
1505 N. Western Ave., Hollywood 27, Calif.**


Gentlemen:
Please send me your free booklet telling how I can get my commercial F. C. C. license quickly. I understand there is no obligation and no salesman will call. **29-R**

Name _____ Age _____
Address: _____
City _____ State _____
I am interested in: Home Study, Resident Classes

AEROVOX ELECTROLYTIC CAPACITORS ARE YOUR BEST BUY FOR EVERY EXACT REPLACEMENT NEED



why use two when one will do?

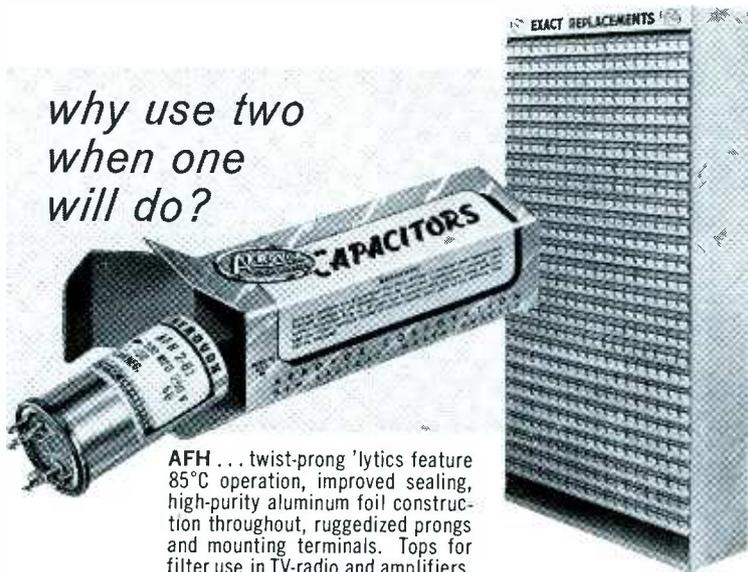

AFH... twist-prong 'lytics feature 85°C operation, improved sealing, high-purity aluminum foil construction throughout, ruggedized prongs and mounting terminals. Tops for filter use in TV-radio and amplifiers.

In addition to your technical skill and business integrity, your reputation and your profits depend on the performance of the replacement parts you use. When it comes to capacitors, you can depend on Aerovox because our continuous program of advanced product research and development has produced the most dependable and complete line of exact replacement 'lytics in the electronics industry, year after year! You see, we guard our reputation as zealously as you guard yours. Your local Aerovox Distributor stocks every rating you need, including the popular types featured here.



PR... wax-filled tubulars manufactured to same high standards as more expensive metal-cased units. Made for exact replacement in TV receivers. Available in singles, duals, triples, quads, and quints for 0-65° operation.



PTT-PWE... Miniaturized tubular 'lytics for repair of personal transistor radios, portable TV sets, and all space-tight requirements. Feature Polycap® plastic cases with exceptional humidity resistance.



PRS... compact "Dandee" units for trouble-free repair of series-string TV and AC-DC table radios. Aluminum cans with cardboard insulating sleeves. Made in singles, duals, and triples, as well as AC rated and non-polarized units.



XA... tubular 'lytics made especially for antenna rotors. Specify XA-4283 or XA-4098A* for 70 MMF capacity, 50 VAC and XA-10001 for 100 MMF, 50 VAC applications (*5" leads, no bracket).



SRE... "Bantam" metal tubular 'lytics hermetically-sealed in aluminum cans with cardboard insulating sleeves. Smaller than the PRS but capable of handling full size loads to 85°C.

NEW—TV Electrolytic Capacitor Replacement Guide AFG-462. Available direct from Aerovox for 50 cents or free from your Aerovox Distributor.



types are available to the modern serviceman. With this wide selection at hand, he can be reasonably sure of finding the right tool to do any job he might encounter.

It doesn't take a serviceman very long to assemble this large a complement of tools, even if he simply buys new types one by one as the occasion demands. However, waiting for the actual need to arise is likely to cause some headaches. If a serviceman doesn't have the correct tool for a particular job, he probably won't go out and buy it without first trying to make some other tool do the work. In too many cases, he finally has to make a trip to the distributor, after all—buying not only the alignment tool but perhaps also a new slug (or even a complete new transformer) to replace one damaged by use of the wrong tool.

A more systematic way for a serviceman to accumulate these tools is to anticipate his needs and buy an assortment of the more commonly-used ones. The chart included in this article will be of help in choosing the most useful types.

Actually, assortments well suited to the average serviceman's needs have already been planned by radio-TV accessory manufacturers, who offer several different kits of alignment tools. A well equipped service shop might have one kit containing tools for radio jobs, and another for TV alignment. There are different-sized kits available in several price ranges; thus, a serviceman's preparations for alignment work may be either as simple or as elaborate as necessary.

Unusual Alignment Tools

Certain items are of particular interest because they offer unique ac-

• Please turn to page 46

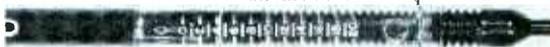


Fig. 3. Some tools have scale to count number of turns a slug is moved.



REMEMBER—it pays to use Aerovox!

AEROVOX CORPORATION
DISTRIBUTOR DIVISION NEW BEDFORD, MASS.

Technical Leadership — Manufacturing Excellence

SENCORE

SIMPLIFIES COLOR SERVICING

NEW! CA122

COLOR CIRCUIT ANALYZER

A simple approach to a complex problem

Here is an instrument that is designed to eliminate the guesswork in color TV servicing. A complete analyzer that provides all required test patterns and signals for testing from the tuner to the tri-color tube. Additional analyzing signals for injection at each stage including audio, video and sync, brings to life a truly portable and practical TV analyzer for on the spot service; virtually obsoleting other analyzers with the advent of color. Sencore's simplified approach requires no knowledge of I, Q, R-Y, B-Y, G-Y or other hard to remember formulas. The CA122 generates every signal normally received from the TV station plus convergence and color test patterns.

The CA122 offers more for less money:

TEN STANDARD COLOR BARS: The type and phase that is fast becoming the standard of the industry. Crystal controlled keyed bars, (RCA type) as explained in most service literature, offer a complete gamut of colors for every color circuit test.

WHITE DOTS: New stabilized dots, a must for convergence, are created by new Sencore counting circuits.

CROSS HATCH PATTERN: A basic requirement for fast CRT convergence.

VERTICAL AND HORIZONTAL BARS: An added feature to speed up convergence, not found on many other color generators.

SHADING BARS: Determines the ability of the video amplifier to produce shades (Y Signal) and to make color temperature adjustments. An important feature missing on other generators.

COLOR GUN INTERRUPTOR: For fast purity and convergence checks without upsetting color controls. Insures proper operation of tri-color guns, preventing wasted time in trouble shooting circuits when CRT is at fault.



A must for color . . .

a money maker for black and white TV servicing

ANALYZING SIGNALS: RF and IF signals modulated with any of the above patterns for injection into grid circuits from antenna to detector. IF attenuator is pre-set for minimum signal for each IF stage to produce pattern on CRT thus providing a check on individual stage gain. Sync and video, plus or minus from 0 to 30 volts peak to peak, have separate peak to peak calibrated controls for quick checks on all video and sync circuits. Crystal controlled 4.5 mc and 900 cycles audio simplify trouble shooting of audio circuits.

NEW ILLUMINATED PATTERN INDICATOR: A Sencore first, offering a rotating color film that exhibits the actual color patterns as they appear on color TV receivers. Locks in with pattern selector control.

You'll pay more for other color generators only.

Dealer Net. 187.50

NEW! PS120 PROFESSIONAL WIDE BAND OSCILLOSCOPE

A portable wide band 3 inch oscilloscope for fast, on-the-spot testing. An all new simplified design brings new meaning to the word portability . . . it's as easy to operate and carry as a VTVM. Though compact in size, the PS120 is powerful in performance: Vertical amplifier frequency response of 4 MC flat, only 3 DB down at 7.5 MC and usable to 12 MC, equips the technician for every color servicing job and the engineer with a scope for field and production line testing. AC coupled, with a low frequency response of 20 cycles insure accurate low frequency measurements without vertical bounce. Sensitive single band vertical amplifier; sensitivity of .035 volts RMS for one inch deflection saves band switching and guessing. Horizontal sweep frequency range of 15 cycles to 150 KC and sync range from 15 cycles to 8 MC (usable to 12 MC) results in positive "locking" on all signals. New exclusive Sencore features are direct reading peak-to-peak volts — no interpretation; dual controls to simplify tuning; lead compartment to conceal test leads, jacks and seldom used switches. Rear tilt adjustment angles scope "just right" for easy viewing on bench or production line.

Size: 7" w x 9" h x 11 1/4" d. Weight: 12 lbs.

Dealer Net. 124.50
(with low cap. probe)

Kit. 74.50



A must for servicing color TV in the home . . . lowest priced broad band scope. All hand wired — all American made

SENCORE

SIMPLIFIES SWEEP CIRCUIT TROUBLE SHOOTING

SS117 SWEEP CIRCUIT ANALYZER

For Color and Monochrome Testing

A professional trouble shooter that helps you methodically walk the trouble out of "tough-dog" sweep circuits in monochrome and color receivers. The SS117 provides a positive but simple push button test on all circuits indicated in the block diagrams. These time-consuming circuits are checked step-by-step with tried and proven signal injection and substitution methods. All checks can be made from the top of the chassis or from under the chassis when it is removed from the cabinet.

TV horizontal oscillator check is made by substituting a universal oscillator known to be good. Horizontal output check consists of a cathode current and screen voltage test. The TV horizontal yoke is checked by substituting a universal yoke from the SS117 and viewing brightness or restoration of 2nd anode voltage. Horizontal flyback is checked dynamically in circuit by measuring the power transfer to the yoke when TV is turned on. TV horizontal sync can be used to control the SS117 horizontal oscillator, providing a positive check on sync from the video amplifier to the TV oscillator. Vertical circuits are tested by simple signal injection from vertical yoke to oscillator for full height on CRT. The SS117 with the CA122 Color Analyzer provides a complete TV analyzer for virtually every stage in monochrome or color receivers.

External checks for AC, DC, peak to peak voltage readings and DC current in the upper right hand corner save using a separate VTVM. Accurate 2nd anode measurements up to 30,000 volts are made with a sensitive 300 microamp meter and the attached high voltage probe. AC outlets, all steel construction and mirror in the cover makes every servicing job easier.

Size: 10¼" x 9¼" x 3½". Wt. 10 lbs.

Dealer Net. **89.50**



The SS117 checks them all



FREE—A 33 RPM half hour permanent record packed with every unit explains each test.

FOR FASTER MORE ACCURATE TUBE TESTING

TC114 MIGHTY MITE TUBE CHECKER

This is the famous Mighty Mite, acclaimed by over 25,000 servicemen, maintenance men and engineers as "the best they've ever used." A complete tube tester that is smaller than a portable typewriter yet finds tubes that testers costing hundreds of dollars miss, thus selling more tubes and reducing call backs. A real money maker for the serviceman and a trusty companion for engineers, maintenance men and experimenters. The Mighty Mite has been acclaimed from coast to coast as the real answer for the man on the go. Even though the Mighty Mite weighs less than 8 pounds, new circuitry by Sencore enables you to use a meter to check grid leakage as high as 100 megohms and gas conditions that cause as little as one half microamp of grid current to flow. Thus, too, it checks for cathode current at operating levels and shorts or leakage up to 120,000 ohms between all elements. And it does all this by merely setting four controls labeled A, B, C, & D with new type easy grip knobs. Check these plus Sencore features... Meter glows in dark for easy reading behind TV set... The new Mighty Mite has large size Speedy-Setup Tube Chart inside of cover—cuts setup time for even faster servicing. New stick proof D' Arsonval meter will not burn out even with shorted tube... Rugged, all steel carrying case and easy grip handle.

The improved Mighty Mite will test virtually every radio and TV tube that you encounter, nearly 2000 in all, including foreign, five star, auto radio tubes plus the new Compactrons, Novars, Nuvisitors and 10 pin tubes. Has larger, easy-to-read type set-up booklet for faster testing.

Size: 10¼" x 9¼" x 3½". Weight: 8 lbs.

Dealer Net. **74.50**

TM116 TUBE TESTER MODERNIZING PANEL

New tube adapter for testing Compactrons, Novars, Nuvisitors and 10 pin tubes in any tube tester except cardomatic types. Plugs into octal socket of your tube tester enabling you to test these new tubes in the same manner



Fast, Accurate . . .
never lets
you down

A must for color



that your tester checks conventional tubes. Tube set-up chart included with each adapter.

Dealer Net. **24.95**

SENCORE

TRANSISTOR CIRCUIT TESTING MADE EASY & PROFITABLE

TR110 TRANSI-MASTER

A new transistor tester that will analyze the entire transistor circuit in minutes. Transistors can be checked in-circuit or out-of-circuit. Here is how it works:

First, check the batteries or power supply with the 0 to 12 volt voltmeter. Next, check the current drain with the 0 to 50 milliamp meter. A special probe is provided so that you do not need to break the circuit. Intermittents caused by cracked boards can be localized by the current check.

If trouble is not located by now, isolate the trouble to a specific stage by touching the output of the harmonic generator to the base of each transistor and note spot where sound from speaker (or scope where no speaker is used) stops or becomes weak. The generator becomes a sine wave generator for audio stages to help find distortion.

If trouble points to a transistor, check it in a jiffy with the exclusive in-circuit power oscillator check provided by the TR110. A special probe is also provided for this.

If the transistor checks bad in-circuit, remove it and give it an out-of-circuit check with the oscillator check or the more accurate DC check.

The DC check is provided for comparison reasons, experimental or engineering work and to match transistors in audio output stages. Beta (current gain) is read direct or on a good-bad scale for service work.

Dealer Net..... 59.50



- COMPLETE IN OR OUT-OF-CIRCUIT TRANSISTOR TESTER
- SIGNAL TRACER • VOLTMETER
- BATTERY TESTER • MILLIAMMETER

TR115 TRANSISTOR DIODE-CHECKER



Tests transistors for leakage, gain, opens and shorts. Reads gain as good or bad or directly in Beta. Checks diodes for forward to reverse ratios. Tests them all from the smallest transistors used in hearing aids to the power types used in auto radios. Also lists Japanese equivalents. This simple to operate, time tested checker can be used with or without set-up chart for both servicing, experimenting and lab work. The industry's most popular transistor tester, used by Bell Telephone, Sears Roebuck, Edison and many others.

Dealer Net..... 24.95

Kit 15.95

NEW! BE124 BATTERY ELIMINATOR



An easy to use power supply that replaces batteries during repair time of transistor radios. Tapped voltages at 1.5 volt DC intervals from 0 to 12 volts are on front panel for easy connection and to insure center tap and bias voltages when required. Function switch converts meter to a trouble shooting 0 to 50 Ma current reading device to monitor the current drain of the transistor radio. Improved regulation and voltage calibrate pot. guarantee accurate well filtered output. Also for charging nickel cadmium batteries.

Dealer Net..... 24.95

Kit 15.95

HG104 HARMONIC GENERATOR



Finds Defective Stage in a Minute . . . a real time saver. Just touch the output leads of the HG104 to inputs and outputs of transistors and a clear 1000 cycle note from speakers will tell you whether or not the stage is defective. It works every time from speaker to antenna. Two leads and calibrated output (not found on pencils) are a must for speaker connection, grounding to prevent RF spray and front end checks. With batteries.

Dealer Net..... 9.95

A NEW VERSATILE APPROACH TO CIRCUIT TESTING

SM112 SERVICE MASTER

A combination VTVM and VOM in one compact unit to simplify every testing need. The SM112 offers a conventional VTVM, operating from 115 volts AC for accurate bench or lab work . . . flip the function switch to VOM and two standard flashlight batteries power the unit as it is connected to a 5,000 ohms per volt meter. This Sencore first enables you to make voltage, resistance and current measures anywhere anytime. And to top this, indicating arrows located along the left side of the meter flash on and off as the controls are rotated to indicate the exact scale to read on any VTVM position or range. Hard to remember technical data is listed in the removable cover. One permanent probe is used for every test on VTVM or VOM. High voltage probe fits on end of permanent probe for measurements up to 30,000 volts DC. Standard specifications of 11 megohm input impedance on VTVM, 6 AC and DC voltage ranges from 0 to 1000 volts on both VTVM and VOM, 6 resistance ranges from 0 to 1000 megohms on VTVM, 2 ranges on VOM, and a 2 percent six inch meter provide all requirements for fast accurate measurements. Zero center scale and peak-to-peak measurements as added features create a truly great Sencore value.



Dealer Net..... only 79.95

SENCORE COMPONENT CHECKING MADE EASY BY SENCORE PARTS SUBSTITUTION

RC121 COMPONENT SUBSTITUTOR

A complete range of carbon resistors, capacitors, electrolytics and universal selenium and silicon rectifiers at your finger tips for on-the-spot substitution. Say goodbye to messy crumpled parts, unnecessary soldering and unsoldering when substituting components for test purposes only. Each section operates independently with a value close enough for every substitution need. Components in each section are isolated from chassis and from other sections. New electrolytic substitution section provides dual electrolytics as well as 25 single electrolytics. Exclusive surge protector prevents arcing, sparking or heating of single or dual capacitors being bridged. Electrolytics are automatically discharged when surge protector is released. Here are the values provided ...81 in all.

- 1. CARBON RESISTORS**...12 resistors, 1 watt from 10 ohms to 5600 ohms. 12 resistors, 1/2 watt from 10 K to 5.6 megohms.
- 2. POWER RESISTORS**...20 wire wound, 20 watts from 2.5 to 15,000 ohms.
- 3. CAPACITORS**...10 capacitors at 600 volts from 100 MMFD to .5 MFD.
- 4. RECTIFIERS**... Universal Selenium; .5 amps, 800 PIV. Universal Silicon; 5 amps, 800 PIV.



All your favorite Sencore Substitution time-savers in one compact unit.

- 5. ELECTROLYTICS**...10 dual electrolytics from 2 MFD to 250 MFD at 450 V DC can be used as singles or tie them together and double capacity to form up to 25 separate single values. Both sections protected by surge protector.

All hand wired, complete with four test leads.

RC121 Dealer Net **39.95**
RC121 (Kit) . . . Dealer Net **27.95**

H36 "HANDY 36"

Provides the 36 most often needed resistors and capacitors for experimenting, substituting and testing. 24 Resistors from 10 ohms to 5.6 megohms, 10 Capacitors from 100 mfd to .5 mfd, 2 Electrolytics 10 mfd and 40 mfd at 450 volts.

Dealer Net **12.75**

RS106 RECTIFIER TROUBLE SHOOTER

Substitutes for single and dual Selenium and silicon rectifiers, single and dual diodes. Gives you a positive check every time. A must for servicing voltage doubler circuits. Protected by a 1/2 amp. Slow Blow Fuse.

Dealer Net **12.75**



ES102 "ELECTRO-SUB"

Complete safe substitution for Electrolytic Capacitors from small transistor radio types to the largest used in Hi-Fi amplifiers. Contain 10 electrolytics from 4 to 350 mfd. Completely safe, has automatic discharge, surge protector circuit. Usable from 2 to 450 volts, DC.

Dealer Net **15.95**

PR11 "BIG 20" SUBSTITUTOR

For power resistor substitution from 2.5 to 15,000 ohms. Withstands up to 20 watts for normal testing time.

Dealer Net **12.75**

Time Saving Service Aids

BE113

DUAL TV BIAS SUPPLY

A single 0 to 20 volts DC bias supply or two separate 0 to 20 volts DC bias supplies—without interaction. Save time in AGC trouble shooting and aligning TV sets. Provides all TV biases recommended in photofact schematics and by all TV manufacturers. Well filtered—provides virtually pure DC with less than one tenth of one percent ripple. Calibration accuracy better than equivalent battery tolerance.

Dealer Net **12.75**

VB2 VIBRA-DAPTER

Checks 3 and 4 prong Vibrators faster and easier. Plugs into any tube checker; ideal for use with LC3 or the Mighty Mite. To check 6v. vibrators, set for 6AX4 or 6SN7; for 12v. vibrators, set for 12AX4 or 12SN7. Two No. 51 lamps indicate whether vibrator needs replacing.

Dealer Net **2.75**



FC123

FILAMENT CHECKER

Newly designed filament checker for continuity speed testing of all tube filaments including the new compactrons, novars, nuvistors and 10 pin tubes as used in new series TV receivers. Test leads are provided for CRT filament testing, continuity tests are AC or DC neon indicator voltage tests. TV cheater cord is used to power unit as a check on the cord to insure 115 volts AC on TV.

Dealer Net **3.95**

HM119 "HANDYMAN"

A Sencore time-saver to eliminate wasted time behind TV sets. Imagine, a cheater cord with on-off switch, dual extension cord, up to date filament checker, universal fuse checker, handy trouble light, neon voltage and continuity checker, pin straighteners and cord wrapper all in one complete unit.

Dealer Net **9.95**


ALL AMERICAN MADE
ALL HAND WIRED

SENCORE

ADDISON, ILLINOIS

FROM THE LEADING NAME IN WORLD-WIDE COMMUNICATIONS

**BUILD
PROFITS
WITH**

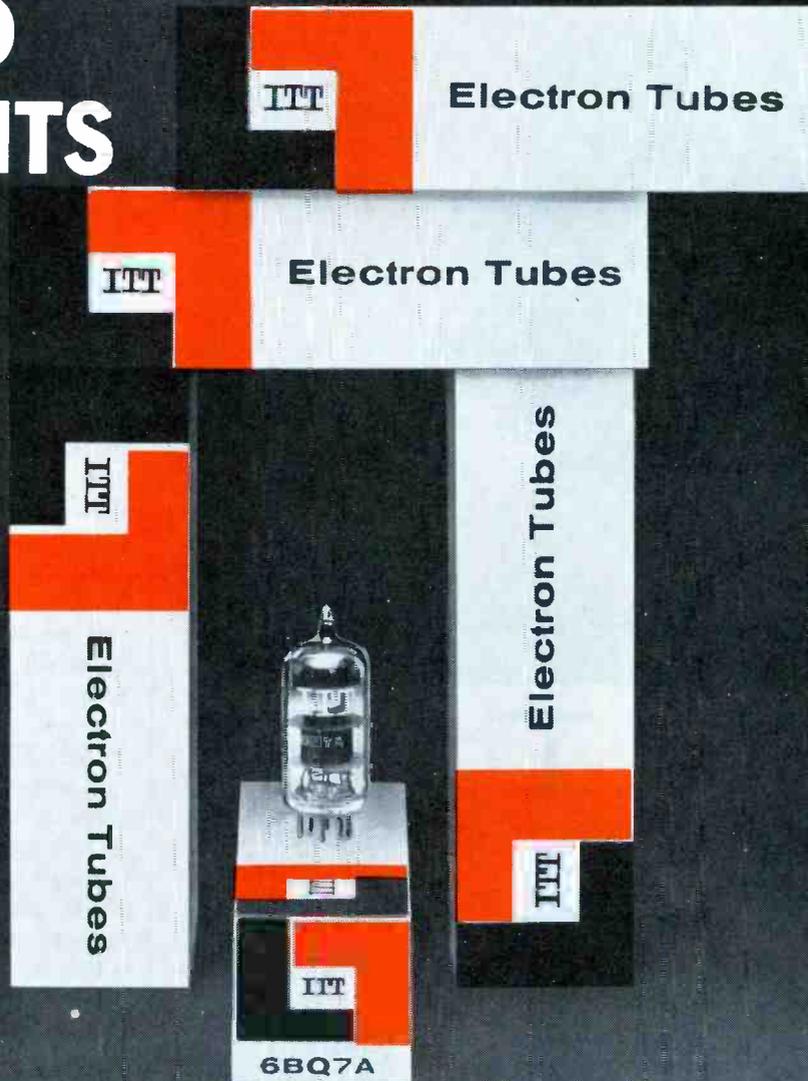

QUALITY PRODUCTS

Let's face it — you're the professional. Your customers rely on your judgement — if they don't, you're just working, not **building**. When your customers see you use the familiar and accepted ITT-labeled tube, they know you're a friend. **You** know it's a profitable friendship, and that's the kind that lasts. For over 25 years ITT has been advancing the state of the art in tube design and manufacture. This traditional quality is the stuff your reputation is made of . . . use it well. We can help you with a

confidence-builder, "**the ITT TUBE STORY**", pamphlet. Give one to your customers — they may give one to you (a customer, that is).



The next time you pick up ITT TUBES, ask your distributor to tell you the details of our Partnership in Prestige and Progress program — you can participate in this Dealer Award Plan.

ITT

DISTRIBUTOR PRODUCTS DIVISION

P. O. BOX 99, LODI, NEW JERSEY

TEL. HUBBARD 8-7800 • CABLE DISTRIBUTOR • TWX HKK 1586

INTERNATIONAL TELEPHONE AND TELEGRAPH CORPORATION

October, 1962/PF REPORTER 45

Put your TV Tuner Troubles



in Skilled Hands

CASTLE

TV TUNER SERVICE CENTERS

1. Compare the Quality

What price quality? We could "just repair" your tuner for less than \$9.95...but, the little extra you pay for a Castle Overhaul buys a lot of quality. Quality you can see when you examine the workmanship in a Castle Overhauled unit...Quality you can feel in dollars and cents saved in eliminated call backs...Quality you can hear in customer praise for a job well done...and, Quality that saves you time by giving you a quick solution to every tuner problem.

And don't forget the "Big Bonus" you get on a UV combination...a double portion of Castle quality for the same price.

Castle replaces all defective parts, (tubes and major parts are extra at net prices) and then aligns your tuner to the exact, original specifications.

Simply send us your defective tuner complete; include tubes, shield cover and any damaged parts with model number and complaint.

Send for **FREE Mailing Kit** and complete details.

See map for Castle Center Serving You



Pioneers in TV  Tuner Overhaling

CASTLE TV TUNER SERVICE, INC.

5701 N. Western Ave., Chicago 45, Illinois

653 S. Palisade Ave., Cliffside Park, New Jersey

In Canada: 136 Main St., Toronto 13, Ontario

Alignment Tools

(Continued from page 40)

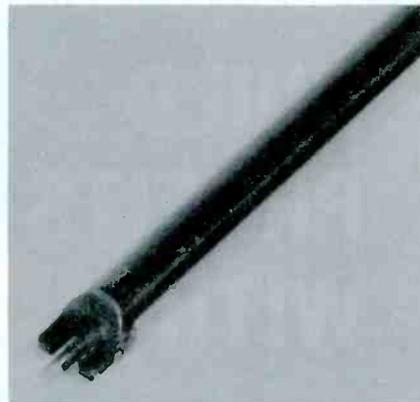


Fig. 4. Retrieving tool has pivoting blade section which grips slug tightly.

cessory features or are made of special materials. Some alignment tools are fitted with the device shown in Fig. 3, which enables the serviceman to count the number of turns (to the nearest quarter-turn) he has moved the slug from its original position. These tools come in especially handy for returning a slug to its original setting after you have checked to see if the coil is tuned to the right peak.

Another special device helps the serviceman overcome a problem sometimes encountered in aligning certain models of turret tuners. These are sometimes troublesome because they contain air-core coils which have a slug threaded directly into the coil wire. The coils are doped after the slug has been adjusted, and freeing the slug is likely to require more than normal pressure. If a slug is pushed too hard, it can slip out of contact with the windings. The special tool used to alleviate this problem has concentric shafts, as shown in Fig. 4. The center one, when turned, applies pressure against the sides of the slot, and allows the slug to be pulled as well as turned. In this way, its threads can be brought back into contact with the coil wires.

Although most modern alignment tools are made of some type of plastic, there are some special types made of other materials. For example, screwdrivers constructed of beryllium or some other nonmagnetic metal are useful when considerable torque is needed for loosening frozen slugs. Some older TV's also required this type of screwdriver for adjusting focus. Other ma-



Tips for Technicians

Mallory Distributor Products Company
P. O. Box 1558, Indianapolis 6, Indiana
a division of P. R. Mallory & Co. Inc.

Rectifier "packages" save time and space



When you're putting together a DC power supply, these little Mallory packaged rectifier circuits can spark a lot of time-saving, space-squeezing ideas.


Each package is a complete rectifier circuit . . . bridge, doubler or center-tap . . . that does the job of two or four separate rectifiers. So you've only got *one* component to wire in place. The individual rectifier cells are factory-connected in the package.

You can get the exact rectifier you want in this compact form. And we mean compact. Less than $\frac{3}{4}$ " by $\frac{1}{2}$ ", and $\frac{1}{4}$ " thick. Cold case design, too; you can mount 'em anywhere without worrying about case-to-ground shorts.

PRV ratings on all three types go as high as 600 volts. And there's plenty of current capacity. The FW full wave bridge models are rated 1.5 amps. DC at 50°C. ambient, 1.0 amp. at 100°C. Doubler Type VB and center tap Type CT are rated 0.75 amp. at 50°C., 0.5 amp. at 100°C.


If you need more current rating, you can parallel the two sides of the type CT package, using 0.5-ohm equalizing resistors in series with each leg. And you can get a high PRV unit at low cost by using a type VB double package as a series-connected half-wave rectifier, connecting a one-megohm resistor across each cell for voltage equalization.

As if all this weren't enough, you save money, too, because our packaged circuits cost less than individual rectifiers. Get them from your Mallory Franchised Distributor. He's a good man to call on for Mallory capacitors, switches, controls, batteries, resistors and vibrators . . . and for any other components you need.

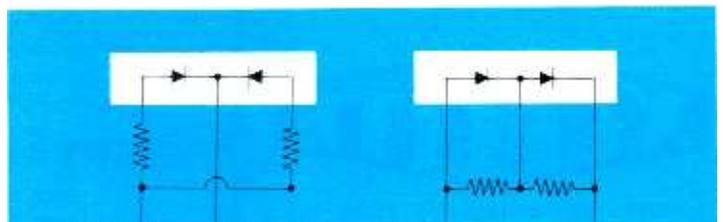

NEW 4-WAY POCKET TOOL

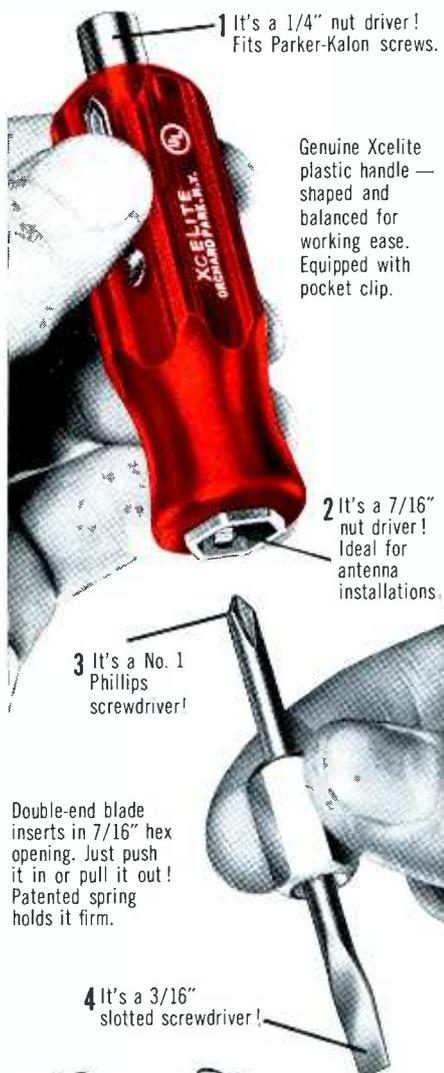a real "working partner"
for removing backs of TV sets
and installing antennas



1 It's a 1/4" nut driver!
Fits Parker-Kalon screws.

Genuine Xcelite plastic handle — shaped and balanced for working ease. Equipped with pocket clip.

2 It's a 7/16" nut driver!
Ideal for antenna installations.

3 It's a No. 1 Phillips screwdriver!

Double-end blade inserts in 7/16" hex opening. Just push it in or pull it out! Patented spring holds it firm.

4 It's a 3/16" slotted screwdriver!



Ask to see "No. 600" next time you pick up parts...

XCELITE

XCELITE, INC. • ORCHARD PARK, N.Y.
Canada: Charles W. Pointon, Ltd., Toronto, Ont.

materials that are occasionally used for making alignment tools are fiberglass and bone fiber. Tools made of these two materials have the advantage that they can be easily re-pointed on a bench grinder.

One highly useful tool, unlike the others mentioned above, is not intended for turning slugs. This device, the tuning wand, simply provides a convenient way to check a coil for proper alignment. It consists of a plastic rod with a powdered-iron tip on one end and a brass tip on the other. Inserting the powdered-iron core into a coil form raises the inductance of the coil, while inserting the brass core lowers the inductance.

Other Service Aids

A number of additional items, which are not alignment tools in the strict sense of the word, are nevertheless classified in the same general category. They are similar in construction to the special screwdrivers and wrenches used in alignment, and are equally handy to have in the shop.

Several interesting devices of this nature are shown in Fig. 5. At the left is a screw-holding screwdriver—a useful device indeed. Many minutes can be wasted trying to start a screw in a hard-to-get-at location. Few of us have the patience necessary to survive dropping a small screw in an inaccessible spot several times. With a captive screwdriver it is usually a simple matter to start the threads. The unit in the photo functions in the same manner as the slug-retrieving tool shown in Fig. 4—a rotating blade section, operated by an inner shaft, grips the screw by pressing against the slot.

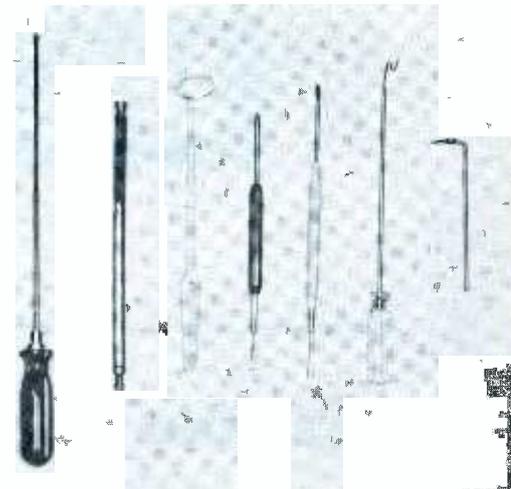


Fig. 5. Alignment-tool kits may also contain service aids, such as these.

A nut-starting tool (second from left) has coiled steel tips which fit over the heads of hex nuts and hold them steady to facilitate installing them in awkward spots.

Next in line is an inspection mirror, which comes in handy for jobs such as replacing a miniature tube located in a spot where the socket is difficult to see. These mirrors can also be used to examine resistors and other components hidden behind a transformer or electrolytic. Many different types are available, including nonmetallic and illuminated models.

To the right of the mirror are two different types of soldering aids. Both tools have a wire brush at one end for removing solder from connections, but the remaining tips have different purposes. One, a slotted probe, is useful for prying wires off terminals; the other, a sharp blade, can cut through foil conductors or pierce silicone-resin insulation on printed wiring boards.

The hooked probe, next in line, removes much of the exasperation

Western T.V. Tuner Rebuilders

VHF or UHF ALL MAKES


\$9.95 Including all parts and labor

major parts extra at (low) net price.

UHF-VHF COMB. \$17.50

90 Days Guarantee — 24 Hour Service

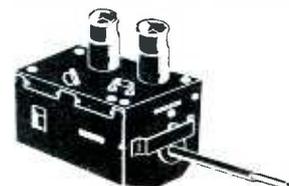All tuners are thoroughly cleaned, mechanically and electrically overhauled, aligned with crystal-controlled equipment, and finally given air check or sensitivity with TV transmitters.



WESTERN TUNER REBUILDERS

3040 W. Sunset Blvd., Los Angeles 26, Calif., NO 2-1397

4130 El Cajon Blvd., San Diego 5, Calif., AT 4-2733

ANOTHER **PRECISION** SERVICE TIP FOR YOU.

PRECISION PETE

"CHECKING OUT AT A HOTEL"

SECRETARIES' CONVENTION JUST ARRIVED, PETE. NEED EVERY TV AND RADIO SET IN TIP-TOP CONDITION RIGHT AWAY.

RITZ HOTEL WELCOMES SECRETARIES OF AMERICA

AT LEAST 80% OF ALL SERVICE PROBLEMS ORIGINATE WITH THE TUBES. AND THE FASTEST WAY TO TEST ALL YOUR SETS IS WITH MY **PRECISION 650 TUBE TESTER**. LET'S START CHECKING "SHORTS" MAX.

I'M 'WAY AHEAD OF YOU, PETE!

I MEAN "SHORTS" IN RECEIVING TUBES—LIKE THE **MINIATURES, COMPACTRONS, NUVISTORS, NOVARS AND OCTALS** THAT CAN BE TESTED WITH THIS **650**. IT ALSO ANALYZES **CONTROL GRIDS** FOR **LEAKAGE, EMISSION AND GAS CONTENT**.

YES, AND, WITH THIS **AD-65 ADAPTER**, YOU CAN EVEN TEST **PICTURE TUBES** FOR **SHORTS AND CATHODE EMISSION**.

THERE'S NO CATHODE SHORT OR LEAKAGE IN THIS TUBE. I'LL ROTATE THE "D" SWITCH THROUGH ITS TWELVE POSITIONS AND CHECK THE OTHER ELEMENTS.

BETTER CHECK CATHODE EMISSION. I'LL JUST PRESS THIS BUTTON AND SEE.

THERE, THAT'S THE LAST ONE. TWENTY-FOUR SETS CHECKED OUT IN JUST THREE HOURS, THANKS TO MY **PRECISION 650 GRID ANALYZER TUBE TESTER**.

WITH ALL THE NEW BUSINESS WE'VE BEEN GETTING SINCE WE SIGNED AS **REGISTERED PRECISION SERVICEMEN**, DON'T YOU THINK WE NEED MORE HELP...LIKE A SECRETARY FOR INSTANCE?

MMMM. THIS SET JUST CAME OUT LAST MONTH. DO WE HAVE A **DATA CARD** ON IT, MAX?

SURE DO, PETE. **PRECISION'S DATA SERVICE** KEEPS THE **650** FROM BECOMING OBSOLETE. LOOK HERE.

FREE SERVICE BULLETIN

SERVICEMEN: THE **PRECISION 650** (DEALER NET: \$69.95; AD-65: \$5.95) LETS YOU FULLY TEST ALL POPULAR RADIO, TV AND COMMUNICATIONS TUBES FAST. WANT TO KNOW MORE? WRITE FOR FREE BULLETIN #102.

PRECISION APPARATUS CO. INC.

70-31 84 ST. GLENDALE 27, NEW YORK

ALL **PRECISION** TEST EQUIPMENT IS GUARANTEED FOR ONE FULL YEAR.



WHEN IT COMES TO SECRETARIES, I DON'T NEED ANY HELP.



STEP ONE FOR COLOR TV SERVICING: THE NEW PRECISION E-450 COLOR BAR/WHITE DOT GENERATOR.

Simple to use, crystal controlled and voltage regulated, the PRECISION E-450 is a must for the busy serviceman. It combines the facilities to test and adjust the phasing, matrixing, linearity and convergence circuits in all color receivers. Three front panel controls and one simple antenna cable connection to the receiver under test afford a new high in ease of operation. The PRECISION E-450 is furnished complete with output cable and technical manual for only \$189.95 net. For complete details on this and other models, see your jobber or write today.

Patterns: Color bars, White dots, Crosshatch, V bars, H bars. **RF Output and Sound Carrier:** Available on channel 3 or 4; field adjustable. RF output 50 mv max. Sound 10% of picture carrier. **Simple 300-Ohm Connection** to antenna input terminals of receiver. **No External Sync.** Signals required to lock in test patterns. **Master Voltage-Regulated, Crystal-Controlled Oscillator** operating on 189 kc assures stability of displayed patterns. **Easier Convergence Set-Ups:** Separate vertical and horizontal bar patterns. **Optimum Convergence Adjustments:** Extremely fine, well-defined dot pattern. **Color Bars:** A reference test signal, precisely controlled, produces 10 equally spaced color bars across face of TV receiver under test. Included are the color bars corresponding to R-Y, G-Y, B-Y, I and Q signals.

PRECISION APPARATUS CO., INC., GLENDALE 27, NEW YORK

PRECISION 
All Precision Test Equipment is Guaranteed For One Full Year

STEP TWO. VISUAL ALIGNMENT AND WAVEFORM ANALYSIS.




ES-150 Wide Band Oscilloscope with DC to 5 mc Response. VERTICAL CHANNEL: 3-stage push-pull, balanced DC amplifier. Sensitivity: DC: 70 mv/in.; AC: 25 mv RMS/in. Frequency Response: DC: within 3 db to 4.5 mc, within 5 db at 5 mc; AC: within 3 db from 1 cps to 4.5 mc, within 5 db at 5 mc. Rise Time: better than .08 μ s. Input Impedance: 1.5 megohms shunted by 23 mmfd. 4-Step Frequency-Compensated Vertical Input Attenuator: Frequency compensated. Vertical

Polarity Reversal Switch: Simplifies pattern reversal. HORIZONTAL CHANNEL: Push-pull output amplifier; sensitivity: 0.6 v RMS/in. Frequency Response: Within 3 db from 1 cps to 400 kc. Input Impedance: 5 megohms shunted by 23 mmfd. Cathode-Follower Horizontal Input Circuit: Linear time base 10 cps. to 100 kc. Provisions for external capacitor sweep to 1 cps. Net Price: \$149.95. Also available in kit form as PACO S-55: \$95.95.



STEP THREE. VISUAL SWEEP RESPONSE WITH ES-150.

E-410 Sweep Generator And Marker Adder. Frequency Coverage: 3 mc to 1080 mc in 6 bands (to 216 mc on fundamental). Continuously Variable Sweep Width: 0-3 mc on Band A to 0-30 mc on Band D. Band E varies from 0-16 mc. Output Impedance: 50 ohms terminated. Internal Blanking: Eliminates return trace. Automatic Gain Control: Regulates voltage amplitude on any band. Marker Adder: Superimposes marker "pips" on response curve; variable in size and width. Internal Phasing Control: Corrects phase shift between RF and horizontal scope outputs. Fixed Frequency Markers: Crystal circuit for accurate marking (one 4.5 mc crystal supplied). External Marker Input Connector: Permits use of external marker such as E-200C to provide variable marker "pips." Separate Line Filter: Minimum line cord radiation. Continuously Variable Attenuators: Control sweep width and vertical scope pattern. Net Price: \$159.95. Also available in kit form as PACO G-32: \$85.95.

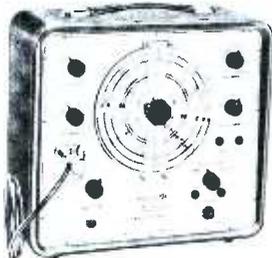

STEP FOUR. ALIGNMENT AND VARIABLE MARKER.

E-200C Multi-Band RF Signal and Marking Generator. Frequency Range: 88 kc to 440 mc (to 110 mc on fundamental). Direct reading in 10 bands up to 440 mc; within 1% accuracy on all bands. 0-1000 Point Vernier Dial: Ideal for hand calibration and frequency spotting. Dual-Shielded RF Attenuators. Smooth, stepless RF control. Four Types of Signals: Unmodulated RF; modulated RF (400 cps); externally modulated RF; 400 cps output. Direct Reading Variable Modulation Control 0-100%: Triples signal utility as against obsolete fixed or stepped modulation of only 30% or 40%. Built-in AVC-AGC Bias Substitution: Overcomes alignment troubles arising from varying receiver AVC and AGC. Net Price: \$109.95.

Alignment-Tool Requirements For Radio-TV Shops

Basic Tool Complement

1. Medium-length metal-tipped screwdriver
2. Medium-length plastic-tipped screwdriver
3. 2½" recessed-tip screwdriver
4. Flexible tuning wand
5. .100" - diameter tuning hexagonal tool used on Zenith TV's
6. .075"-diameter hexagonal tool
7. "K-Tran" IF-transformer tool with torque handle
8. 12" plastic screwdriver

Expanded Assortment

9. Short metal-tipped screwdriver
10. ⅜"-square socket driver
11. ⅜"-blade small-diameter screwdriver
12. Stud-core tool used on Stewart-Warner, Belmont, Motorola TV's

Service Aids

21. Inspection mirror
22. Contact-adjusting tool
23. Dial-cord stringing tool
24. Soldering aids
25. Screw-holding screwdriver
26. Nut-starting tool

from another tedious service job—the manipulation of dial cords and springs. Another hook (at far right) has slotted tips and is intended for straightening contacts on relays and switches.

Still another service aid, sometimes called "mechanical fingers" (not pictured), is designed to reach into small corners and other inaccessible places to retrieve small screws, nuts, and components. Several "fingers" are spring loaded in a housing; when the inner shaft is pushed from one end, these fingers extend from the housing and surround the object to be retrieved. When the inner shaft is released, the fingers clamp tightly around the object and allow it to be withdrawn.

Shop Hints

Here are some tips in connection with the use of alignment tools that might save some time on future jobs:

1. When working on older radios or TV sets, you might encounter a slug that is frozen in position, perhaps because it has never been adjusted during the life of the set. To loosen it, try a steady pressure first in one direction, then in the other. If the slug doesn't come free, don't force it; apply a couple of drops of alcohol directly to the slug. Other agents will also work, but be careful not to use anything that might dissolve the varnish which coats the turns of the coil.

13. 2½" recessed-tip tool used on Westinghouse and RCA TV's
14. Oscillator and IF-transformer tool used on RCA, G-E, Philco, and Admiral TV's
15. 9" tool with ⅜"-diameter shaft for "cup cores" (nested iron cores)
16. Recessed-tip screwdriver used on Zenith TV's
17. 7" metal-tipped screwdriver with torque handle
18. 10" beryllium screwdriver
19. Transistor-IF core-alignment tool
20. Concentric-shaft potentiometer tool used on color TV's.

2. If you should happen to strip the slot or hexagonal hole in the end of the slug, check the bottom side of the chassis; many slugs have adjustment slots on both ends.
3. Always examine a slug carefully before attempting to insert a tool. Many of the different recesses look similar, but unless the proper tool is used, the slug could be irreparably damaged.

Conclusion

A radio-TV technician needs many different alignment tools and related accessories in the course of his daily work, but since most of these are very reasonable in price, even the most elaborate collection of them will seldom cost him over \$25.00. This modest investment will spare him the great inconvenience and unnecessary damage to components that would result from using inadequate tools. ▲

Moving to a New Location?

If so, notify us by the 15th of the month to assure uninterrupted delivery of PF REPORTER.

Please be sure to give us both your old and new address, including your postal zone number. (Or better yet, enclose a current mailing label with your new address.) Send to:

PF REPORTER
Circulation Dept.
4300 W. 62nd Street
Indianapolis 6, Ind.

STOCK GUIDE

FOR
TV
TUBES...

This list omits over 50 of the rarest TV tube types, which many shops do not find it practical to keep in stock. To simplify the chart as much as possible, common radio and hi-fi tube types used in TV combinations are omitted; so are UHF types. Tubes marked* are primarily used in color sets.

The figures on a gray background suggest a stock of 350 tubes which should account for over 90% of your replacement needs, and should minimize your risk of being "caught short" even if you travel all day without refilling your tube caddy. However, if you prefer a more

limited caddy stock, the other set of figures (on white background) will help you decide which types to cull out. These figures indicate the number of tubes of each type you could expect to find in a random sample of 1000 tubes taken from all TV sets now in service. Where the usage is well below 1 per 1000, a dash is shown. To scale down your stock, you can omit many "dashed" types, and also reduce quantities of other types. In so doing, keep in mind three other factors besides usage rates which influence the demand for various tubes:

1. Relatively high failure rate of power

output and similar types.


2. Your specialization in certain makes of sets.
3. Average age of sets containing a particular tube type.

Temporary substitution of available types for rare types, as outlined in the Howard W. Sams book, **Tube Substitution Handbook, Vol. 5**, can also help you reduce stock requirements.

Another way to ease tube-stock headaches is to use only the latest -A or -B versions of various tubes. Types in common use are listed in the chart.

PER CADDY 1000 STOCK	TUBE TYPE																
25	3	1B3GT	—	1	5A54	14	3	6AW8A	1	1	6CS7	—	1	6FW5	—	1	10EM7
13	2	1G3GT	—	1	5A58	—	1	6AX3	3	1	6CU5	1	1	6FY5	—	1	10HF8
5	1	1J3	1	1	5AT8	23	3	6AX4GTB	1	1	6CU8	—	1	6GC5	1	1	12AF3
4	1	1K3	—	1	5AV8	3	1	6BA6	1	1	6CW4	—	1	6GE5	4	2	12AT7
1	1	1S2A	—	1	5AU4	1	1	6BA8A	—	1	6CW5	4	1	6GH8	16	3	12AU7
—	1	1V2*	1	1	5B8	3	2	6BC5	2	1	6CX8	1	1	6GK5	1	1	12AV5GA
6	2	1X2B	—	1	5BE8	2	1	6BC8	2	1	6CY5	2	1	6GK6	1	1	12AV7
2	1	2BN4	1	1	5BK7A	2	1	6BE6	2	1	6CY7	2	1	6GM6	7	2	12AX4GTB
—	1	2CW4	1	1	5BR8	—	1	6BF6	1	1	6CZ5	3	1	6GN8	4	2	12AX7
3	1	2CY5	—	1	5BW8	2	2	6BG6GA	2	1	6DA4	1	1	6GW6	2	1	12AZ7A*
—	1	2FH5	4	2	5CG8	2	1	6BH8	—	1	6DB5	1	1	6GX6	1	1	12B4A
—	1	2FS5	2	1	5CL8A	—	1	6BJ8	7	2	6DE4	1	1	6GY6	6	2	12BH7A
—	1	2GK5	1	1	5EA8	—	1	6BK4*	4	2	6DE6	—	1	6HF8	1	1	12BQ6GTB
4	1	3A3	—	1	5EW6	1	1	6BK5	1	1	6DE7	—	1	6HJ8	—	1	12BR7
1	1	3AL5	—	1	5GH8	5	2	6BK7B	1	1	6DG6GT	2	1	6HS8	—	1	12BV7
3	1	3AU6	—	1	5GM6	3	2	6BL7GT	5	2	6DK6	1	1	6J5	9	2	12BY7A
1	1	3BC5	—	1	5J6	2	1	6BL8	2	1	6DN7	10	3	6J6	3	1	12C/-CUS
3	2	3BN6	1	1	5T8	2	1	6BN4	—	1	6DQ5*	3	2	6K6GT	1	1	12CA5
3	2	3BU8	33	3	5U4GB	8	2	6BN6	20	2	6DQ6B	—	1	6K11	2	1	12D4
18	2	3BZ6	5	2	5U8	3	1	6BN8	2	1	6DR7	1	1	6S4A	1	1	12DB5
8	2	3CB6	2	1	5V3	6	2	6BQ5	—	1	6DS5	1	1	6SL7GT	8	2	12DQ6B
2	2	3CS6	1	1	5X8	10	3	6BQ6GTB	—	1	6DT5	31	3	6SN7GTB	—	1	12DQ7
1	1	3CY5	2	2	5Y3GT	9	2	6BQ7A	11	2	6DT6	1	1	6SQ7	—	1	12DT5
2	1	3DG4	1	1	6AB4	1	1	6BR8A	1	1	6EA7	8	2	6T8	—	1	12ED5
2	2	3DK6	2	1	6AC7	—	1	6BS8	9	2	6EA8	11	3	6U8A	—	1	12GC6
7	2	3DT6	1	1	6AF3	6	2	6BU8	5	1	6EB8	1	1	6V3A	2	1	12L6GT
—	1	3EA5	2	2	6AG5	—	1	6BW8	1	1	6EH7	8	2	6V6GT	1	1	12SN7GTA
—	1	3GK5	1	1	6AG7	1	1	6BX7GT	1	1	6EJ7	5	2	6W6GT	1	1	12W6GT
—	1	4AU6	1	1	6AH4GT	2	2	6BY6	1	1	6EM5	5	2	6X8A	1	1	13DE7
—	1	4AV6	3	2	6AH6	2	1	6BY8	5	2	6EM7	2	1	7AU7	—	1	13DR7
1	1	4BC8	1	1	6AK5	34	3	6BZ6	2	1	6ER5	—	1	7EY6	1	1	13EM7
—	1	4BN6	1	1	6AL3	2	1	6BZ7	2	1	6ES8	1	1	8AW8A	—	1	13FD7
1	1	4BQ7A	31	2	6AL5	3	2	6C4	—	1	6ET7	—	1	8BA8A	1	1	17AX4GT
—	1	4BU8	4	1	6AM8A	65	3	6CB6A	—	1	6EU8	2	2	8BQ5	1	1	17D4A
3	2	4BZ6	3	2	6AN8A	1	1	6CD6GA	5	1	6EW6	1	1	8CG7	—	1	17DE4
1	1	4CB6	20	3	6AQ5A	2	1	6CF6	—	1	6EZ5	—	1	8CX8	—	1	17DM4
1	1	4CS6	2	1	6AS5	33	3	6CG7	—	1	6FD7	—	1	8EB8	2	1	17DQ6B
—	1	4DE6	1	1	6AS8	11	2	6CG8A	2	1	6FH5	—	1	8EM5	—	1	17GW6
1	1	4DT6	1	1	6AT6	1	1	6CL6	—	1	6FG7	—	1	8ET7	2	1	19AU4GTA
—	1	4EH7	1	1	6AT8A	1	1	6CL8A	—	1	6FM8	—	1	8FQ7	—	1	22DE4
—	1	4EJ7	5	2	6AU4GTA	—	1	6CM6	—	1	6FQ5	1	1	8GN8	1	1	25AX4GT
—	1	4ES8	56	2	6AU6A	5	2	6CM7	1	1	6FQ7	1	1	9AU7	—	1	25BQ6GTB
2	1	5AM8	2	1	6AU8A	2	1	6CN7	—	1	6F55	—	1	9BR7	1	1	25CD6GB
1	1	5AN8	1	1	6AV5GTA	2	1	6CQ8	—	1	6FV6	2	2	10DE7	1	1	25DN6
5	2	5AQ5	9	2	6AV6	4	2	6CS6	—	1	6FV8	—	1	10EG7	2	1	25L6GT

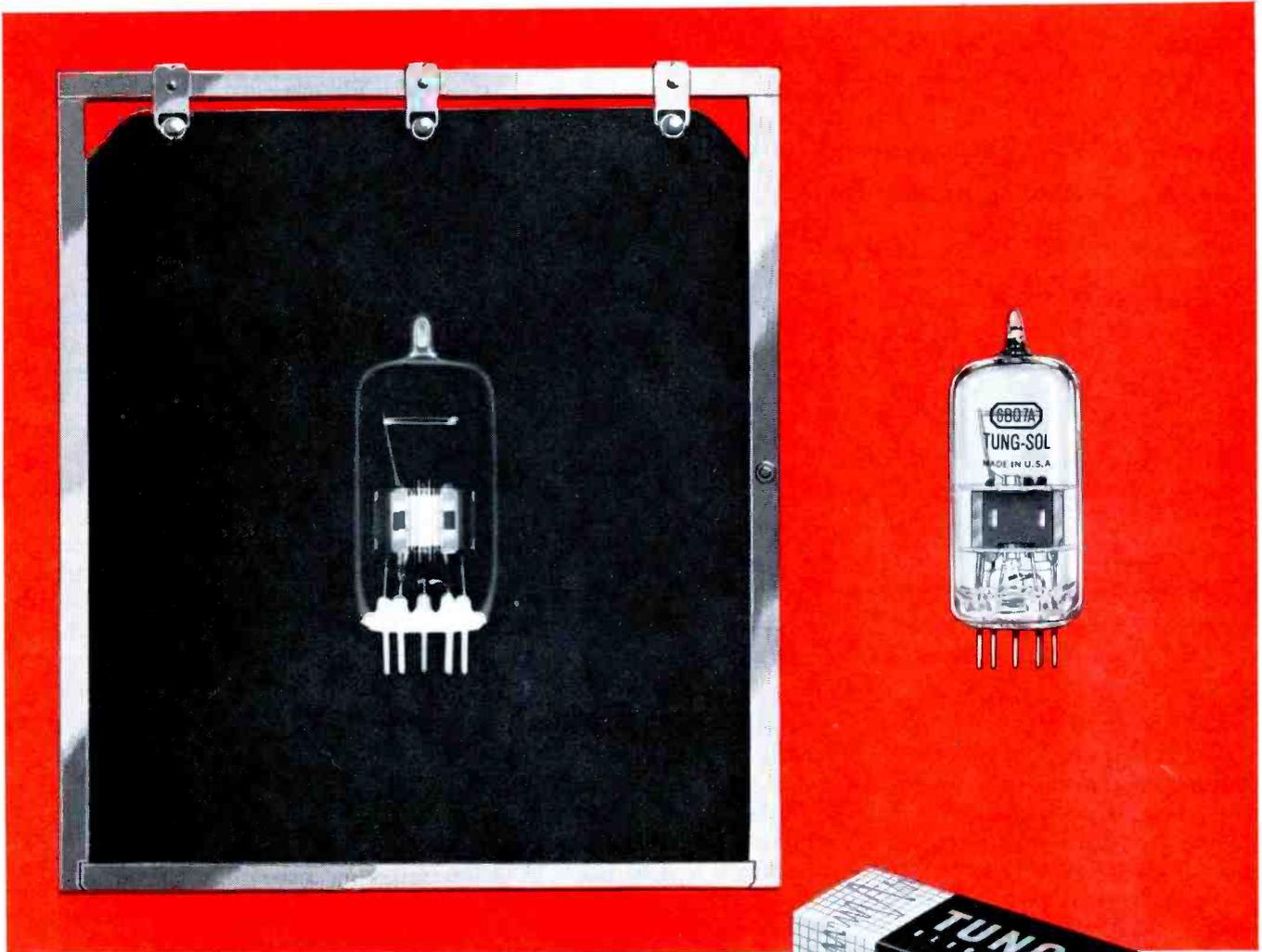HIGH GAIN AND LOW CAPACITANCE OF FRONT END TRIODES EXPLAIN ABSENCE OF SNOW ON PICTURE TUBES



SNOWY or hazy pictures are symptomatic of tv front ends that transmit input noise infections to the video stages. The wideband RF amplifier triodes manufactured by Tung-Sol for tv tuner service are immunized against this disease by abnormally close spacing of grids and cathodes, boosting power gain and allowing transconductance to increase faster than input capacitance. Isolation of tube elements is maintained by three-part formula: clear mica spacers and rigidized construction to prevent thermal warping and microphonics; high-purity materials prevent gas generation and the formation of leakage paths; extreme cleanliness during every step of manufacture avoids contaminants. Shot noise caused by uneven cathode emission is prevented by using finely dispersed cathode materials.

PRESCRIPTION FOR PROFIT


Customers appreciate fair weather tv pictures. To keep customers and their sets sunny, specify Tung-Sol front end tubes.

 **TUNG-SOL®**
RF AMPLIFIER TUBES


TUNG-SOL ELECTRIC INC., NEWARK 4, N. J.

SYNCHROGUIDE


From Squegs to Squeals

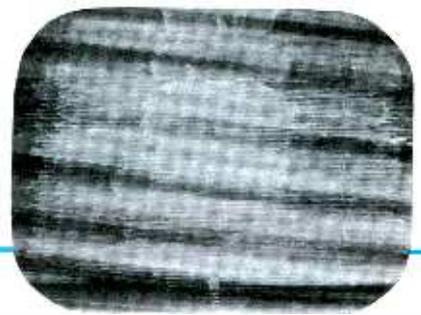

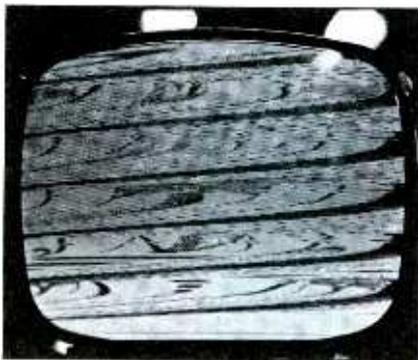What to do when a horizontal blocking oscillator strays off frequency . . . by Thomas A. Lesh



(A) Few cycles off frequency.

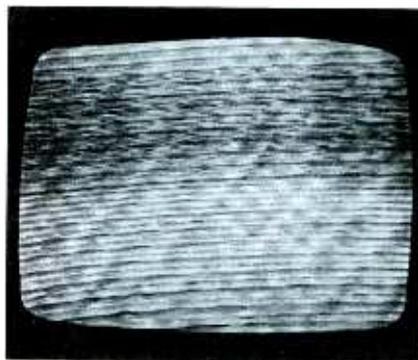

(B) Greater frequency error.

Fig. 1. Oscillator running too slow—mild case at left, severe case at right.

In many cases of horizontal-sync trouble, the sync pulses are perfectly normal, but the horizontal AFC circuit isn't responding to them by making the necessary corrections in horizontal-oscillator frequency.

The direction of the frequency error makes quite a difference in the trouble diagnosis, as we saw in "Horizontal Oscillator Running Wild" (August PF REPORTER). If the oscillator is running just

slightly slow, the picture will appear as in Fig. 1A, with diagonal bars slanting downward to the left. In worse cases (Fig. 1B), the bars will increase in number until they can no longer be distinctly seen; also, a loud squeal will be heard from the flyback. As a secondary effect, the boost voltage will usually decrease; this may cause a loss of height in sets which use boost as a source voltage for the vertical oscillator or


output stages.

On the other hand, too high an oscillator frequency will produce bars slanting downward to the right. If the frequency change is great enough, the horizontal drive signal will be weakened, causing a decrease in width and high voltage.

Another symptom of operation above normal frequency is peculiar to the blocking-oscillator and triode-AFC (*Synchroguide*) circuit, shown in Fig. 2. The frequency change causes distortion of the combined sine-sawtooth waveform developed in the oscillator plate circuit, producing the unstable form of oscillation called "squegging" or "Christmas-tree effect" (Fig. 3).

Several different faults in the oscillator or AFC stage can cause "above-frequency" operation. In addition, certain other troubles (especially in the AFC stage) can lower the oscillator frequency, while misadjustment of the tuned coils may create a frequency error in either direction.

Just as in a multivibrator, various conditions which cause a slight frequency shift are usually covered up by the action of the AFC circuit or by adjusting variable components. The front-panel horizontal hold control of a *Synchroguide*-equipped set usually has less range than in a set using a multivibrator, but the internal horizontal-frequency slug adjustment can be used to tune the oscillator over several thousand cycles of range. If this slug is periodically reset, a gradually worsening trouble will not be evident until the end of the slug's range is reached without locking in the picture. When the

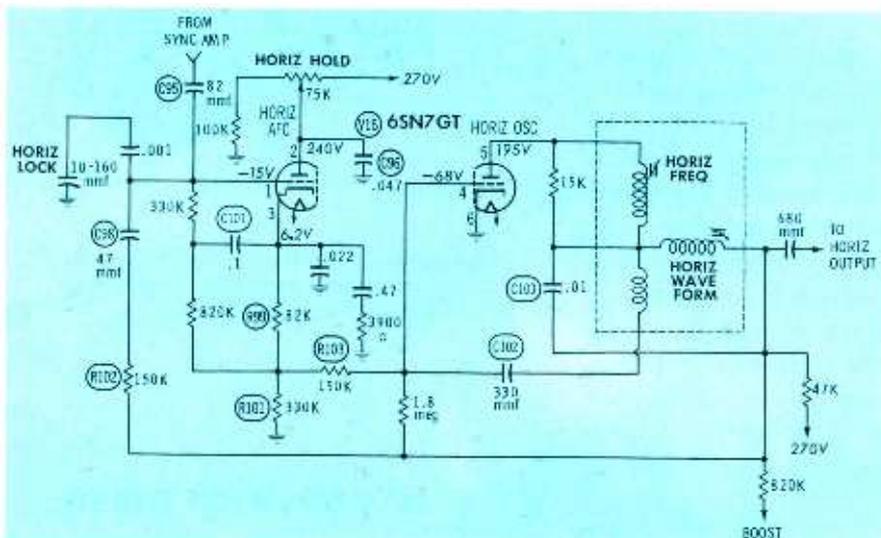

**FINEST
MONEY-MAKER
FOR
Professional
Servicemen**

Multiple-Socket Speed with Gm Accuracy

PLUS OBSOLESCENCE PROTECTION

TESTS
All TV and Radio Tubes
—Old and New

TESTS
European Hi-Fi Tubes,
Voltage Regulators, and
Most Industrial Types

TESTS
for True Dynamic
Mutual Conductance (Gm)

TESTS
Nuvistors and Novars

TESTS
the New 10-Pin Tubes

TESTS
New 12-Pin
Compactrons



Model 700 DYNA-QUIK DYNAMIC MUTUAL CONDUCTANCE TUBE TESTER

See your B&K Distributor
or Write for Catalog AP20-R

TESTS BOTH OLD AND NEW TUBE TYPES—SELLS MORE TUBES PER CALL

All over the nation, thousands of professional servicemen rely on the "700". Once you use it, you'll be as enthusiastic as they are. *Everyday use has proved its speed . . . its accuracy . . . its efficiency.* This up-to-date, obsolescence-proof tube tester is designed for maximum use *today and tomorrow.* Provides multiple-socket section to quick-check most of the TV and radio tube types the *true dynamic mutual conductance way—plus* simplified switch section to check new tube types in Dyna-Quik emission circuit. Also includes provision for future new sockets.

Makes test under set-operating conditions. Checks each section of multi-section tubes separately. Checks for *all* shorts, grid emission, leakage and gas. Makes quick "life" test. Exclusive *adjustable* grid emission test provides *sensitivity to over 100 megohms.*

Makes complete tube test in seconds. Checks average set in a few minutes. Discovers weak tubes that need replacement. *Satisfies more customers. Sells more tubes. Saves call-backs. Insures your reputation. Pays for itself over and over again.* Net, \$169⁹⁵

Time-Saving, Money-Making Instruments Used by Professional Servicemen Everywhere



Model 960 Transistor
Radio Analyst



Model 360 V O Matic
Automatic VOM



Model 375 Dynamic
Automatic VTVM



Model 1076
Television Analyst



Model 440 CRT
Rejuvenator Tester

NEW TUBE INFORMATION SERVICE
Available every 3 months, on subscription,
for all B&K Dyna-Quik Tube Testers



B & K MANUFACTURING CO.

Division of DYNASCAN CORPORATION

1801 W. BELLE PLAINE AVE. • CHICAGO 13, ILL.
Canada: Atlas Radio Corp., 50 Wingold, Toronto 19, Ont.
Export: Empire Exporters, 277 Broadway, New York 7, U.S.A.

COMPLETE SOLDERING OUTFIT IN PLASTIC CARRYING CASE

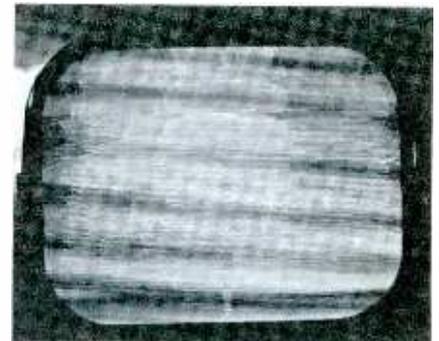


Fig. 3. "Christmas-tree effect" is a characteristic Synchroguide symptom. offending component is finally replaced, the out-of-sync condition may be as extreme as depicted in Fig. 1B, until the frequency slug is returned to a more normal setting.

Mild cases of frequency error may simply mean that a readjustment of the circuit is in order. But if the frequency slug has to be turned very far from the middle of its range to sync the picture, look out for incipient trouble which may become worse later, resulting in a callback.

When a raster full of coarse horizontal lines (and a piercing squeal from the flyback) tells you that the Synchroguide oscillator is running far below its normal frequency, you can usually assume that the trouble is in the AFC stage. You'll probably find that the cathode voltage of the AFC triode is more negative than normal; this usually indicates that its conduction is abnormally weak. With this stage failing to conduct properly, too much negative bias voltage is allowed to build up on the grid of the oscillator and each cycle of oscillation is lengthened—so the frequency is lowered.

Just by measuring the DC voltages on the AFC stage, you'll be able to tell that something's wrong, because malfunctions cause wild fluctuations in voltage on the elements in this tube. For instance, take note of what happened in one Philco that developed a shorted plate-bypass capacitor (equivalent to C96 in Fig. 2). Of course, the plate voltage dropped to virtually zero, effectively pinpointing the trouble spot; in addition, the grid voltage of the AFC triode dropped from the normal -10 volts to -42 volts, and the cathode voltage fell from +8 to -35 volts. The oscil-

All your soldering needs in a break-proof plastic utility case. Gun features dual heat. 2 trigger positions permit instant switching to low 100-watt or high 140-watt heat. Low heat prevents damage to heat sensitive components. By using high heat only when necessary, you prolong tip life and save current.

Plastic case can be used for carrying or storing tools, parts and equipment—also as a lunch or fishing tackle box. Model 8200PK.



Weller
Hi-Speed
Sabre Saw

For smooth, fast cutting of all kinds on speaker and record player mounting boards, cabinets, walls, etc. Makes its own starting hole for inside cuts. Never splinters or tears wood. 4.8 ampere, heavy-duty reciprocating motor. Model 88.

On sale at your Electronic Parts Distributor

WELLER ELECTRIC CORP., EASTON, PA.

Find it and Fix it in 1/2 the time!

EASILY SOLVES "TOUGH DOGS"... INTERMITTENTS... ANY TV TROUBLE



MODEL
1076

TELEVISION
BLACK & WHITE AND COLOR

ANALYST

By Easy Point-to-Point Signal Injection, You see the Trouble on the TV Screen and Correct it—Twice as Fast and Easy!


Simplified technique stops lost hours never recovered on "tough dogs", intermittents, and general TV troubleshooting. This one instrument, with its complete, accurate diagnosis, enables any serviceman to cut servicing time in half... service more TV sets in less time... satisfy more customers... and make more money.

With the Analyst, you inject your own TV signals at any time, at any point, while you watch the generated test pattern on the picture tube of the television set itself. This makes it quick and easy to isolate, pinpoint, and correct TV trouble in any stage throughout the video, audio, r.f., i.f., sync and sweep sections of black & white and color television sets—including intermittents. No external scope or waveform interpretation is needed. Checks any and all circuits—solves any performance problem. Gives you today's most valuable instrument in TV servicing—proved by thousands of professional servicemen everywhere.

Available on Budget Terms. As low as \$30.00 down.

Net, \$29995

SIMPLIFIES COLOR TV SERVICING, TOO

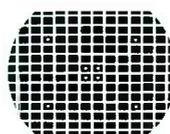

Enables you to troubleshoot and signal trace color circuits in color TV sets, or facilitate installation.



Generates white dot, crosshatch and color bar patterns on the TV screen for color TV convergence adjustments.



Generates full color rainbow display and color bar pattern to test color sync circuits, check range of hue control, align color demodulators. Demonstrates to customers correct color values.

Time-Saving, Money-Making Instruments Used by Professional Servicemen Everywhere



Model 960 Transistor
Radio Analyst



Model 360 V O Matic
Automatic VOM



Model 375 Dynamatic
Automatic VTVM



Model 700 Dyna-Quik
Tube Tester



Model 440 CRT
Rejuvenator Tester

See Your B&K Distributor
or Write for Catalog AP20-R



B & K MANUFACTURING CO.

Division of DYNASCAN CORPORATION

1801 W. BELLE PLAINE AVE. • CHICAGO 13, ILL.

Canada: Atlas Radio Corp., 50 Wingold, Toronto 19, Ont.

Export: Empire Exporters, 277 Broadway, New York 7, U.S.A.

lator grid voltage changed from -95 to -110 volts, causing about a 20% decrease in oscillator frequency.

Another possible reason for oscillator slowdown is a loss of one or both input signals to the grid of the AFC stage. In Fig. 2, an open C95 would remove the sync-pulse input, and an open C98 or R102 would eliminate the sawtooth signal which is supposed to be fed back from the oscillator plate circuit. In either case, the AFC tube would conduct less, and the reduced voltage drop across

R99 would make the cathode voltage of the AFC stage more negative than usual. The low-capacitance probe of your scope, touched to the AFC grid, will tell you if either component of the grid signal is missing. You're likely to have difficulty analyzing a grid-circuit defect in terms of DC voltages measured with a VTVM, since the conduction of the tube is not directly proportional to DC grid-cathode bias, but also takes into account the signal conditions in the grid circuit.

In a few instances, slow opera-

tion may be traced to the oscillator. (Perhaps someone previously installed too large a capacitor in place of C102, or too large a resistor for R103, trying to "fix" another defect by redesigning the circuit!) If this happened, you would recognize trouble in the oscillator by noting that the AFC cathode voltage was more *positive* than normal—this stage would be vainly trying to overcome an excess of bias generated by the oscillator.

Frequency Too High

When squegging and a loss of width tell you that the oscillator is running too *fast*, you'll save time by making a quick isolation check to see whether the fault is in the oscillator or in the AFC. The most satisfactory test procedure is to ground the cathode of the AFC section. This removes the variable element from the grid-leak bias circuit of the oscillator, allowing tests of the latter circuit by itself. In making this check, keep in mind that it lowers the over-all grid resistance of the oscillator circuit; thus, you can expect the oscillator to be slightly out of sync when "free-running" in this manner. A few turns of the frequency slug should be sufficient to pull in a picture, either "floating" across the screen or rolling horizontally. If not, the oscillator circuit is either badly misadjusted or defective.

When the customer complains of a sudden and severe loss of sync, the most likely troubles are that the horizontal frequency coil has developed shorted turns, or that C102 has just "sprung a leak." C103, across the waveform coil in the plate circuit, is likely to affect drive amplitude or to cause critical sync before it will force the oscillator very far off frequency.

If the oscillator seems normal when free-running, but goes wild with the AFC cathode ungrounded, several points in the AFC circuit should be checked. First of all, look for leakage in the sync and sawtooth coupling capacitors in the AFC grid circuit (C95 and C98), which would allow positive DC voltage to reach the grid circuit.

Faulty cathode-circuit capacitors are more likely to produce bending and "pie-crusting" than frequency

Solve Rough Sweep Output Problems

IN MINUTES
INSTEAD OF HOURS



B&K

Model 1070
DYNA-SWEEP
CIRCUIT ANALYZER

1. Provides composite synchronizing signals (negative or positive) to inject directly in each sync stage for trouble-shooting sync circuits.
2. Provides vertical plate drive signal to check complete vertical output circuit, including V.O. transformer.
3. Provides vertical grid drive signal to check vertical output stage.
4. Provides vertical yoke test signal to determine if vertical yoke windings are defective.
5. Provides horizontal plate driving signal to directly drive TV horizontal output transformer circuit.
6. Provides B+ boost indicator.
7. Provides unique high-voltage indicator.
8. Provides sensitive tests for each of the horizontal output components, including H.O. transformer and yoke. Immediately reveals their true condition, good or bad, before any replacement.

Quickly solves tough output servicing problems that have always plagued the TV service technician. Provides horizontal and vertical sync and driving pulses that make it easy to check out every stage in the sync and sweep sections of a television receiver. Tracks down troubles in the horizontal and vertical output circuit, including defective output transformer and yoke. Checks for shorted turns, leakage, opens, short circuits, and continuity. Gives unique high-voltage indication. Eliminates trial and error replacements. Saves many hours of service work. Pays for itself over and over again.

Completely self-contained, with its own driving pulses, for convenient use any time. **Net, \$74⁹⁵**

See Your B & K Distributor or Write for Catalog AP20-R

B & K MANUFACTURING CO.

Division of DYNASCAN CORPORATION

1801 W. BELLE PLAINE AVE • CHICAGO 13, ILL.

Canada: Atlas Radio Corp., 50 Wingold, Toronto 19, Ont. • Export: Empire Exporters, 277 Broadway, New York 7, U.S.A.



Manufacturing
 "know how" plus
Engineering skill
 plus
Reliability based on
Invaluable experience
Totals up to
Merit-orious products!

MERIT
 COIL and TRANSFORMER CORPORATION

Merit Plaza

Hollywood, Florida

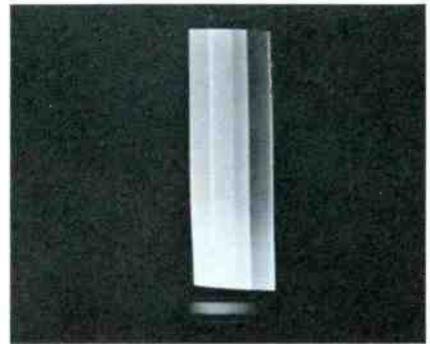


Fig. 4. Extreme loss of width caused by drastic rise in oscillator frequency.

errors. An important exception is C101 (not included in all versions of the *Synchroguide* circuit). If it becomes severely leaky or shorted, its frequency-raising effect will be almost as great as that of a leaky C95 or C98. In one RCA set where this capacitor became shorted, the AFC grid voltage climbed all the way from -26 to $+85$ volts; the cathode voltage went up from -9 to $+105$ volts; and the oscillator grid voltage shifted from -85 to only -55 volts. With such a great loss of bias on the oscillator, the frequency went so high that the raster was even narrower than shown in Fig. 4! The oscillator frequency was estimated (by counting cycles on the scope trace) as almost three times normal; drive amplitude fell from 100 to 60 volts peak to peak; and high voltage was only 8 kv. Oddly, the cathode current of the horizontal output tube did not noticeably increase, but a 50-volt drop in screen voltage showed that a greater proportion of cathode current was going to the screen circuit. That's rough on horizontal output tubes, as well as on screen resistors!

Conclusion

As we have mentioned, off-frequency operation of a *Synchroguide* horizontal oscillator can often be stopped by simply readjusting the tuned coils in the circuit. Nothing may have been wrong with the circuit in the first place, except for misalignment. However, there are certain danger signals that can warn you of oncoming trouble. If you notice frequency drift, have to set a slug toward the end of its range, or make a callback a short time later to correct the same symptom, you'd better check the trouble spots named in this article. ▲



TEST OVER 1750 TUBES

Test CRT too!

WITH ONE TESTER
that defies obsolescence

PORTABLE TUBE TESTER AND CRT REACTIVATOR

Small but powerful. Tests Compactrons, Nuvistors, Ten-Pin Sylvania, Novars, Foreign Tubes, Hybrid Auto Radio Tubes, some Industrial Tubes and Selenium Rectifiers. Tests and reactivates CRT Tubes; over 1,750 tubes, black and white or color—quickly and accurately.

Allows for future tubes, high sensitivity valuable in spotting border-line tubes, avoiding call backs.

Part No. 36-540

Suggested Dr. Net 67.50

SEE THE COMPLETE LINE OF GC HIGH QUALITY, LOW PRICED TEST EQUIPMENT



COMPONENT SELECTOR

Instant component substitution of 45 different Resistors, Capacitors and Electrolytics. Eliminates wasted time hunting for parts, determines the value of illegible capacitors and ends soldering mess created by individual substitution. Full electrolytic discharge protection.

Stretch repair shop budgets with the best equipment at the most reasonable prices.

Part No. 36-524 Suggested Dr. Net 24.95



TRANSISTOR TESTER

For testing PNP, NPN, power transistors, diodes and Rectifiers (Semi-conductors). The Tester's basic measurement capacities are Open Test, Short Test, Leakage—ICO, Gain—BETA, Out of Circuit. Operates on 2 penlite batteries which should last for life under normal operating conditions.

Part No. 36-560 Suggested Dr. Net 19.95



POWER SUPPLY AND BATTERY ELIMINATOR

Extended operation of units without batteries. Allows operation at higher or lower than normal output voltages, giving technicians better analysis of relative performance. Checks current drain; OPTIMUM FULL WAVE rectification through 2 heavy duty silicon rectifiers.

Part No. 36-562 Suggested Dr. Net 19.95



TRANSISTORIZED SIGNAL GENERATOR

For service repairs on Transistor, Auto, and conventional Radios and Hi-Fi Stereo sets. Makes trouble shooting quick, easy through signal injection method, isolating defects to a specific stage.

Part No. 36-564 Suggested Dr. Net 9.95



TRANSISTOR RADIO TROUBLE SHOOTER

Tests PNP, NPN, Power Transistors, diodes and rectifiers (semi-conductors). All transistors; operates as a SIGNAL GENERATOR of 400 CPS (approx.) audio signal; also acts as a POWER SUPPLY — BATTERY ELIMINATOR, gives an indirect battery test through substitution.

Part No. 36-568 Suggested Dr. Net 49.50



IN AND OUT OF CIRCUIT TRANSISTOR TESTER

Tests all common NPN, PNP transistors, provides an indication of collector to emitter shorts, collector to base shorts, condition of collector junction, DC current gain, crystal diodes and rectifiers. Provides an "In-Circuit" test to determine transistor's ability to oscillate as a blocking oscillator.

Part No. 36-570 Suggested Dr. Net 24.95



GC TEST "SIGNAL OPTIMIZER" 7-in-1 C-B Tester

"Wattmeter" measures antenna power in watts. "Modulation Monitor" Spot Garbled Modulation Field Strength Meter measures power radiated from antenna. Checks & tests the frequency and overtone of CB crystals. Measures standing wave ratio (SWR). It measures the "efficiency" of your base (or mobile) antenna.

Part No. 36-590 Suggested Dr. Net 47.50

FREE SUPPLEMENT CATALOG

Just off the press... GC Supplement Catalog No. FR-62-S. 48 pages of new test equipment, tools, antennas, phono drives, etc. Free with this coupon—Write: GC Electronics Co., Dept. No. 17, 400 So. Wyman St., Rockford, Illinois, USA.



NAME _____

ADDRESS _____

CITY _____

STATE _____ Dept., No. 17

GC ELECTRONICS CO.

DIVISION OF TEXTRON ELECTRONICS, INC. • 400 SOUTH WYMAN ST. • ROCKFORD, ILL., USA



Free Tube Testing

... *at a profit!*

by Ernest Tricomi

The do-it-yourself tube tester in the hardware store, drug store and gasoline station has, without question, dug deeply into the profits of television and radio service shops. In several areas of the country, however, machines have been installed to the point of saturation, and retailers report declining tube sales. It now appears that an energetic, determined service-shop owner can combat the competition from these machines, and stand a chance to win.

Back in the early 'fifties, manufacturers and distributors of the then-new self-service tube checkers approached many a service dealer with the proposition that he act as the franchised agent for the machines in his area, placing them in strategic locations in neighboring retail shops. The servicer wrongly supposed he could stem the tide by refusing to handle the checkers, and because he was not properly organized for selling and servicing them, he usually turned down the proposition.

Now, with the usual hindsight, many of these same service dealers could kick themselves for their lack of foresight and initiative. The business has gone to enterprising individuals, not always connected with the service business, who aggressively took up the idea and sold it to neighborhood retailers. The retailer was delighted. Not only did he make a profit from the sale of tubes, but the tube tester represented still another inducement to increase

his store traffic. Almost entirely self-service, the instruments did not require attendance by skilled help, and even inventory control was semi-automatic. The idea boomed, and today service shops are losing untold thousands of dollars which they might well have had for the asking a few years ago.

Know Your Competition

Never before has it been so true that, if you can't fight it, you should join it. Now that the idea of self-service testing has gone full cycle, service shops have a golden moment in which to turn the tide and win back most, if not all, of the tube sales that have been lost to the testing stations.

If you want to fight competition, you first need to learn all you can about it, just as the general in battle

tries to fathom his opponent's next move. There appear to be two plans in competition with the service technician—the ownership plan and the franchise plan.

Ownership Plan


In the ownership plan, the retailer actually purchases the tube tester, the stock cabinet, and an initial stock of tubes. The tester and cabinet cost about \$130, not a large investment for a moderate-sized retailer.


Most of the tube-testing stations sold to retailers under the ownership plan are made by manufacturers, who market the instruments under their own brand names. Selling is handled by the manufacturer's regular distributor organization, who have the responsibility for selling, installing, maintaining, and stocking the testers.

Franchise Plan

In the franchise plan, the retailer does not buy the instrument; it is owned and serviced by a franchised agent. The machines used in this type of plan are usually, but not always, made by small manufacturers who, in the absence of a regular distributor organization, turn to individuals for help in marketing the machine and the tubes.

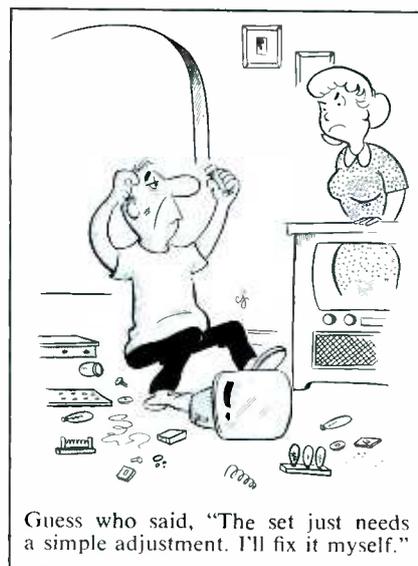The successful franchise agent can make a very comfortable living, indeed. A "string" of 20 or 30 machines in fair locations can gross as much as \$12,000 to \$15,000 annually. All the agent has to do is call on each of his stores once every



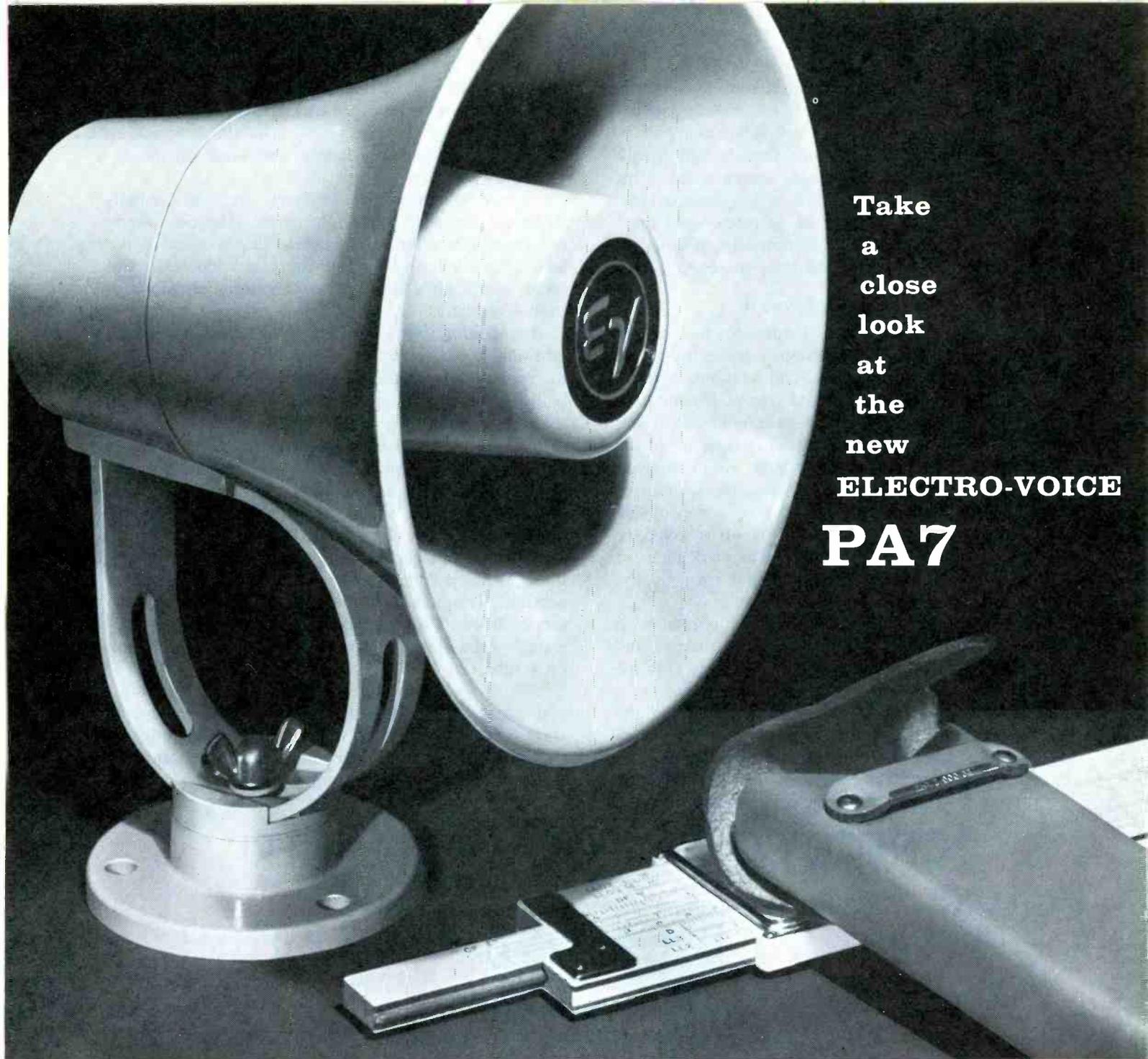

Take
a
close
look
at
the
new
ELECTRO-VOICE
PA7

A Bold Departure in Paging Speakers!

Look carefully at the new Electro-Voice PA7 paging speaker. The speaker that defies tradition to give you more value than any other paging unit on the market!

Even the horn is new! Molded of tough, unbreakable Cylolac* plastic, it outlasts metal yet doesn't "ring" like ordinary bells. And the color is molded in. Fading, peeling, rusting problems are gone forever!

Inside, a brand new ring-type diaphragm of fiberglass-reinforced Acoustalloy® provides the authoritative voice of the PA7. Unusually high efficiency is coupled with smoothly rising response and low distortion. Test it with voice—even music! This is crisp, commanding sound that puts even larger speakers to shame!

Although the PA7 is light in weight, the ingenious swivel mounting is strictly heavy-duty for quick, absolute positioning anywhere . . . mobile or fixed!

Every detail of design and performance of the PA7 reflects the refreshing, new ideas that have made E-V PA speakers the finest in the industry! Ideas that mean highest quality and reliability for you and your customers!

Measure this remarkable new paging speaker against your personal yardstick of quality. No matter how critically you judge the Electro-Voice PA7, you'll find it's better than you expected. Except the price. That's much better!

* T.M. Borg-Warner



SPECIFICATIONS: Frequency Response 400-13,000 cps, Sound Pressure Level 119 db (at 4' on axis, 7.5 watts Input, 2-4 kc), Power Handling Capacity 7.5 watts, Impedance 8 ohms, Dispersion 120°, Size 6 3/4" diameter x 6" deep, Weight 2 lbs.

\$27.00 LIST
(Normal trade discounts apply)

ELECTRO-VOICE, INC.
Commercial Products Div., Dept. 1026R,
Buchanan, Michigan



... THE SMART MOVE IS TO ELECTRO-VOICE!

Electro-Voice®

week or two, replenishing the stock and checking the performance of the instrument. Occasionally, it becomes necessary to dispatch a technician to repair it.

For his part, the retailer must provide four square feet of floor space somewhere near the entrance to his store, where customers can't fail to see the machine. He pays only for the initial stock of tubes—and these are sometimes provided on a guaranteed-sale basis, so the retailer risks nothing but the floor space.

The Customer Loves It

Now comes the part that is hardest for the service-shop owner to realize—the customer loves the whole idea! Far from being suspicious and cautious, Mr. Set Owner is enthusiastic. At the first sign of trouble with his set, he recklessly pulls out every tube he can reach, dumps them all in a paper sack, and charges off to the hardware store for a relaxing half-hour. And if they all test “good,” he’s disappointed! Nothing pleases him so much as to find a “bad” or “weak” tube in the lot. He cheerfully calls over the clerk, holds up a defective 6DQ6, and asks for a replacement. The clerk digs out a new 6DQ6, consults a price list, and rings up the sale on the cash register.

The customer returns home in triumph, tells his wife he just saved them five bucks in labor charges, and plugs in all the tubes. In far too many cases (for the service-shop owner’s welfare), the set works!

Where “name-brand” tubes are stocked, and the tester is in good condition, the do-it-yourself system is good business for the franchise operator, the distributor, the retailer, and the customer. The only one left

out in the cold is the serviceman—you!

But the news can't be all bad; let's look at the other side of the coin. Like anything else, the competition has some flaws and weaknesses, and these can be exploited by the alert servicer.

Weakness number one, of course, involves the limitations of the self-service tube tester. The do-it-yourself type of machine isn't built to detect some of the intermittent failures to which tubes are addicted. And some tubes, while inoperative in certain circuits, are usable in others.

In addition, some retailers have taken to stocking off-brand tubes, many of which are nearly impossible to trace to any well-known source. These tubes generally fail earlier than others (often as soon as they are installed), leading many formerly enthusiastic users of the tube testers to have some doubts.

Part of the reason self-service tube testers have enjoyed such great success can be traced back to the black eye suffered by the service business in the early days of television service. Exaggerated stories about the malpractices of unscrupulous operators certainly contributed to the tendency to avoid a service call whenever possible. The present-day revival of confidence in the service business should definitely help restore the technician as the man best qualified to judge the condition of a tube.

The best way to fight the competition of the do-it-yourself tester is to join it. Free tube testing is here to stay—and *you* might as well be the one to offer it. Customers can bring their tubes into your shop as easily as they can to the drugstore around the corner.

CHECK COLOR TV FASTER! EASIER!

COLOR
KEYED
for SPEED
and
PROFIT



JACKSON MODEL 800

COLOR BAR-DOT GENERATOR SIMPLIFIES
COLOR TV SERVICE WITH PUSH BUTTON EASE

PUSH
BUTTON
OPERATED

EXCLUSIVE PUSH BUTTON PANEL • CONVERGENCE SIMPLIFIED •
COLOR GUN KILLER • FRONT PANEL JACKS FOR VIDEO-SYNC-OR COLOR
DEMODULATOR SIGNALS • VIDEO LEVEL CONTROL • NEW MODERN FUNCTIONAL
STYLING • EASY TO SET UP • PILOT LIGHT • OPERATES ON TRANSFORMER ISOLATED 117 VAC

COLOR CLINICS TO BE HELD IN YOUR AREA SOON! WATCH FOR THEM.



MODEL CRO-3


5 inch wide-band, high sensitivity
sensitivity oscilloscope.

Laboratory quality scope with highly stable
circuitry and every feature for accurate TV work,
COLOR and BLACK and WHITE. Widely used, too,
in many laboratory and industrial applications.

MODEL 648-S

“Service Engineered”
Dynamic Tube Tester

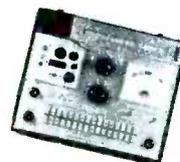
Tests all new tubes faster-easier to
use-more profit to the Dealer.
“See it to Believe it!”



"OVER \$12,000 WORTH OF POWERMATES SOLD...AND IT'S JUST THE BEGINNING!"

GEORGE MARKMILLER

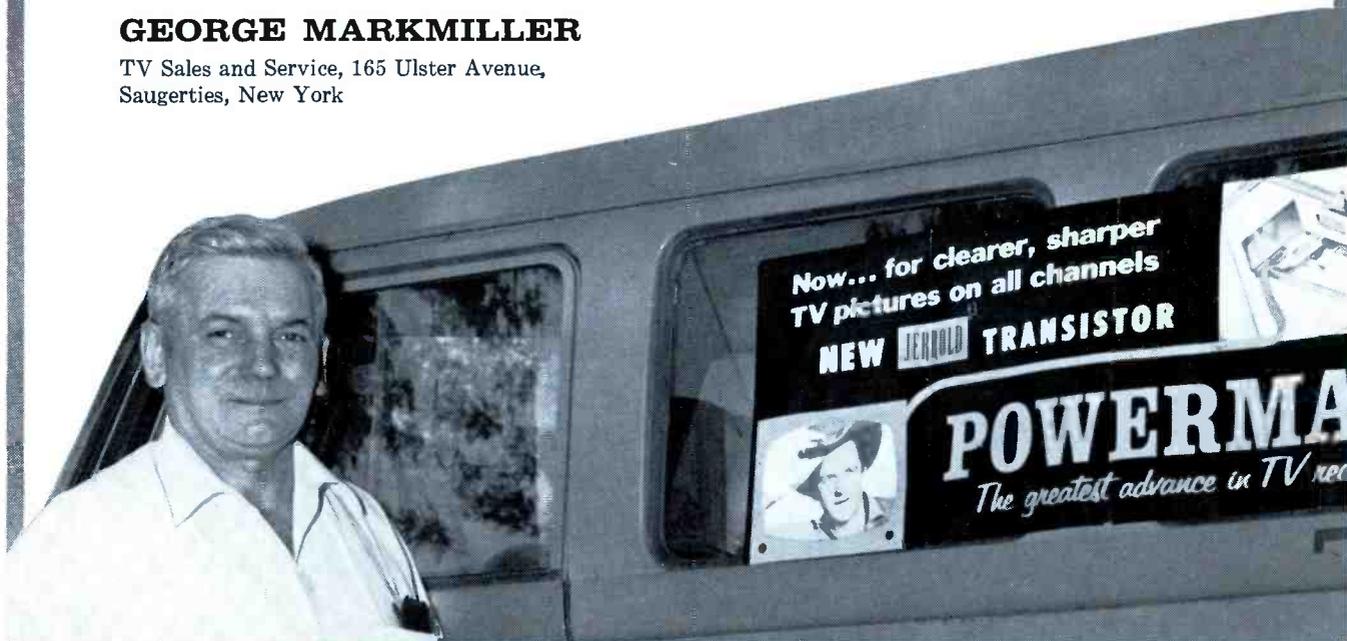TV Sales and Service, 165 Ulster Avenue,
Saugerties, New York




POWERMATE sells itself through its performance

George Markmiller's customers "were from Missouri" where TV reception was concerned. The products they had tried, in spite of high claims, had not produced snow-free TV from the distant New York stations. With the help of his Jerrold distributor, George used the potent promotional kit to tell his customers the POWERMATE performance story. Newspaper ads, truck banners, stuffers and store displays presold

POWERMATE because the promotion was *custom-designed* for his area.

The real clincher came after the demonstration when one customer began to tell the other about POWERMATE's amazing reception. The Saugerties area had never seen such clarity in black and white *and in color*. As George says, "The performance of this unit has been the best advertising that has helped to sell it."

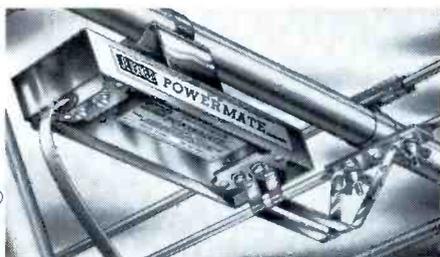Jerrold's ready to set up a POWERMATE promotion designed for *your local area*. You can repeat George Markmiller's success story as hundreds are doing—all over the country. Write for the name of your nearest Jerrold distributor.



**TRANSISTOR
POWERMATE
ANTENNA AMPLIFIER**

\$39⁹⁵
LIST

JERROLD ELECTRONICS CORPORATION
A subsidiary of THE JERROLD CORPORATION
Philadelphia 32, Pa.

Jerrold Electronics Corporation
Distributor Sales Division, Dept. IDS-266
Philadelphia 32, Pa.

I want Jerrold to promote the POWERMATE in my LOCAL area. Send me the name of my nearest distributor.


Name _____

Address _____

City _____ Zone _____ State _____

G-E reporter, Roland Kempton,
makes the rounds with
independent service dealers ...

 **ELECTRONICS**

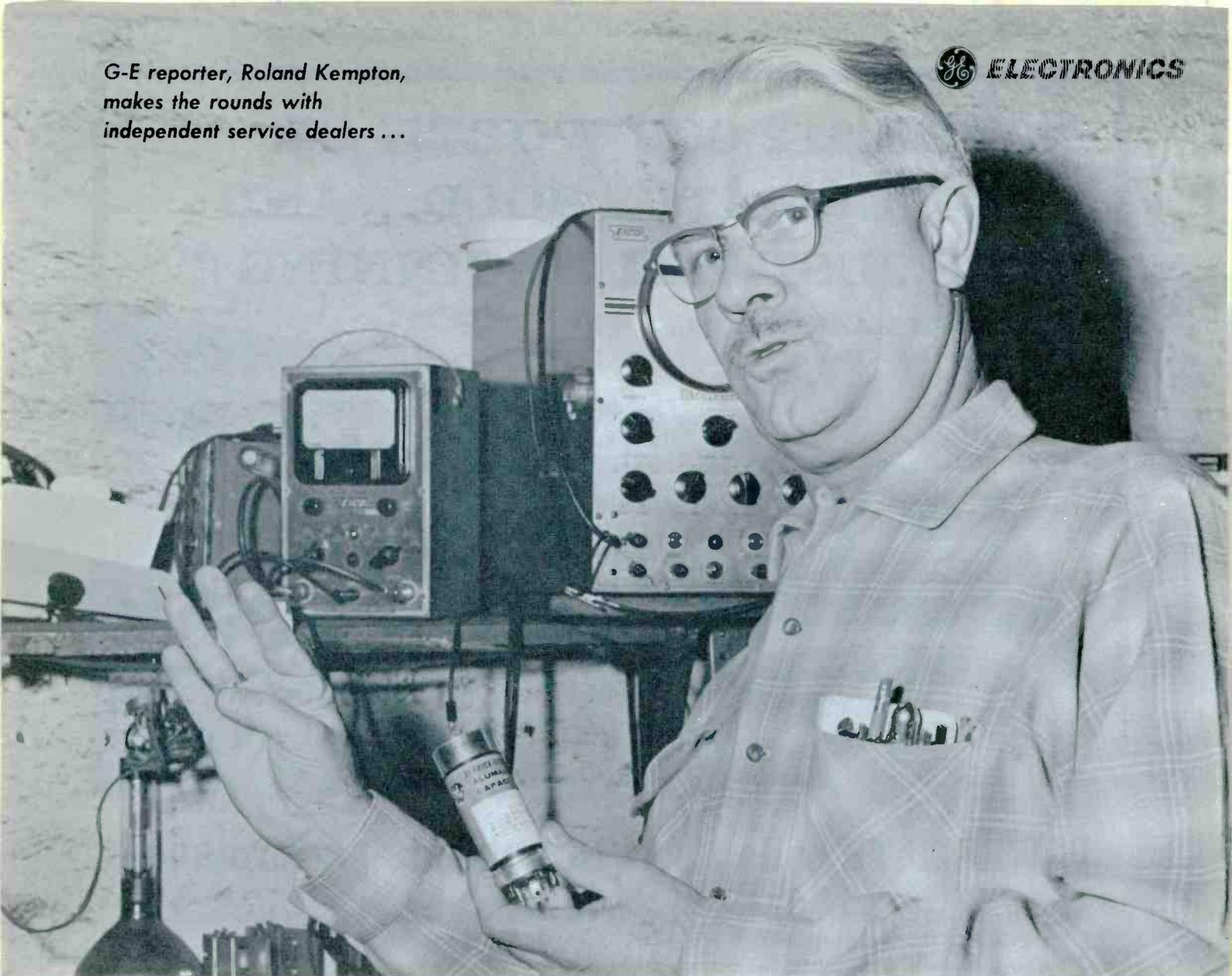

Ben Follrath says, "It's like having 4 capacitors in each box when you stock G-E *SERVICE-DESIGNED* capacitors"

Because one G-E Service-Designed capacitor takes the place of four ordinary types... Ben Follrath, owner of BEN'S TV, Alameda, Calif., can carry about 20 types in stock and still meet approximately 70% of his replacement needs. That's because G-E Service-Designed capacitors are designed for, and marked with, an "application range" of capacitance (i.e. "40-60 mfd"). One capacitor serves all values within this application range.

To Ben Follrath, and service dealers throughout the country, this means it pays to stock G-E Service-Designed capacitors. They save time, reduce costs

of single-unit ordering and pickup, speed customer service. Like having 4 capacitors in each box.

Get your complete capacitor catalog and replacement guide from your G-E Electronic Components distributor. Ask for ETR-2600, or write to: General Electric Company, Room 1774-A, 3800 N. Milwaukee Ave., Chicago 41, Illinois.

Progress Is Our Most Important Product

GENERAL  ELECTRIC



To get customers into your shop, you must work out a strategy in the form of convincing arguments, and then apply them to every possible situation in the form of advertising and promotion. Your copy themes should be:

First, bring out the fact that you offer *free* tube testing in your shop—and that *you* do the work, not the customer.

Second, educate the prospect that do-it-yourself instruments do not disclose every possible failure, that certain intermittent faults are not revealed at all.

Third, point out that a customer may replace a tube unnecessarily when he tests it himself. Often, a tube shows up as weak and gassy, but it will actually function satisfactorily in some circuits. These situations require the diagnosis of an expert.

Fourth, assure the customer that from your shop he will get brand-name tubes which are guaranteed by the manufacturer. While not all do-

it-yourself tube-testing stations are stocked with off-brand names, enough prospects will have been "stung" by unknown brands at one time or another to give your message a telling effect.

When you have worked out your message containing these four important points, be sure to exploit every medium at your disposal for disseminating your message.

Besides advertising your free tube-testing service, you can do these things:

1. Be sure to locate your own tube tester at or near your counter, so the customer can see for himself when a tube tests weak or bad. Place signs on your counter and in your window saying, "Tubes tested free by qualified technicians on high-grade testing instruments."
2. Print your message on product stickers, invoices, door-knob hangers, letterheads and business cards, your shop vehicles, job tickets, etc.
3. Get your local servicemen's association to sponsor a series of advertisements bearing the message.
4. Talk to your friends among the retailers who have tube testers in their establishments. Many of them may be on the verge of discontinuing this service, because competition has reached the saturation point; a timely word from you may be all that is needed to swing them over to your side.
5. Or, try another tack—check into the possibility of acting as agent for a "string" of tube-testing stations. A retailer who might otherwise be reluctant to install a tube tester may think better of the idea if he has an experienced service technician standing behind the instrument, and name-brand tubes to sell. Put a notice on the machines that *you* are the one to see if tube testing fails to solve the TV problem.

Competition from the do-it-yourself tube-testing station is similar to a one-sided fight—for several years now, the service shops have been taking all the punishment. But the opponent's arm is beginning to tire, and now is the time to bounce back with all you've got! ▲



Two Service Aids Included in New G-E Auto Radio Capacitor Kit

Kit K-202 contains 10 electrolytic twist-prong capacitors (8-most popular types) that will meet the majority of auto radio replacement needs. As a bonus, each kit contains a magnetic service light, tab adjuster and replacement guide... all at no additional charge.

The magnetic service light may be attached to auto dash or radio chassis and aimed where needed. The hollow-tip tab adjuster simplifies twist-prong servicing. Both Service Aids are included at no additional cost.

Get this extra-value kit now from your G-E Electronic Components distributor. Ask your distributor for a copy of the new General Electric Auto Radio Replacement Guide, ETR-3378, or mail coupon to Chicago warehouse address shown.

General Electric Company, Dept. 1774-A
3800 N. Milwaukee Ave., Chicago 41, Ill.


Please send me a copy of the new G-E Auto Radio Replacement Guide, ETR-3378.

Name _____

Address _____

City _____ Zone _____ State _____

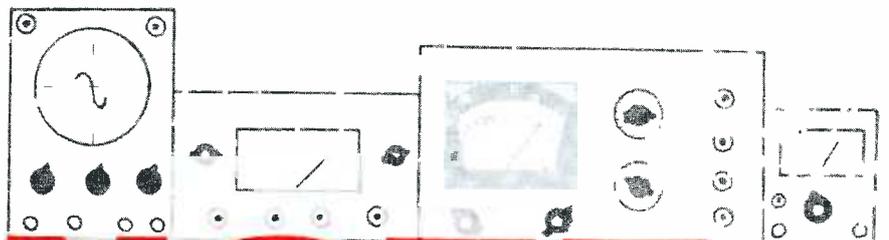**YOUR TUBES
TESTED
FREE
BY EXPERIENCED
TECHNICIANS
ABC Electronics**



NOTES

ON TEST EQUIPMENT

Color, Color Everywhere

Fig. 1 illustrates a completely self-contained NTSC-type color-bar generator, the Model 656XC by Hickok Electrical Instrument Co. of Cleveland—an accurate signal source for color television.

Specifications are:

1. Power Required—105-125 volts AC; 50-60 cps; 125 watts.
2. RF Output—Channels 2, 3, 4, 5, and 6, fixed-tuned; from 200 to 1000 uv available; 75, 90, or 300 ohms.
3. Video Output—Choice of: 15 horizontal bars, 20 vertical bars, crosshatch (consisting of 15 horizontal and 20 vertical bars), or approximately 300 dots; color-bar signals: choice of B-Y, R-Y, G-Y, or -G-Y signals, or 7-color display; approximately 2.5 volts peak to peak of signal available; 75, 90 or 300 ohms.
4. Sound-Channel Output — Frequency controlled by 4.5-mc crystal (supplied); VHF sound-channel crystal available as optional equipment.
5. Controls and Terminals—Four rotary switches: DOT-BAR-COLOR BAR selector, DOT-BAR selector, COLOR-BAR PATTERNS selector, and RF CHANNEL selector; seven toggle switches: VIDEO POLARITY, MODULATION ON-OFF, SOUND ON-OFF, Y-SIGNAL ON-OFF, CHROMA ON-OFF, B-Y/G-Y ON-OFF, and G-Y/R-Y ON-OFF; three crystal sockets: 3.579545-

mc crystal, sound-channel crystal, and 315-kc crystal; two potentiometers: VIDEO OUTPUT attenuator and RF OUTPUT attenuator; three coaxial connectors: VIDEO OUTPUT, RF OUTPUT, and 3.58-MC OUTPUT; one fuseholder; 19 potentiometers (under covers) for circuit adjustments.

6. Size, Weight, Price—18 $\frac{3}{8}$ " x 16 $\frac{3}{4}$ " x 7 $\frac{1}{2}$ "; 34 lbs; \$525.00.

The Model 656XC can be used by the color-service technician for all adjustments which must be made to the chroma-bandpass, color-sync, phase detector, demodulator, matrix, and convergence circuits in a color television receiver. The color-bar output of the generator is a standard NTSC (National Television Systems Committee) signal which contains the components of an actual color telecast. The unit directly generates three primary colors—red, blue, and green—and provides the three intermediate colors—yellow, magenta, and cyan—by using certain combinations of primary-color bars.

Fig. 2 shows how this is done: Equal-amplitude bars of Y-signal (brightness) information are fed into a mixing device, but the width of each bar is varied according to diagram A so they add as shown, creating the Y levels shown at B. This Y signal is mixed with the various amounts of chroma signal shown at C. The result is the video information included in D, an NTSC color signal.

The remainder of the composite NTSC color signal consists of a horizontal synchronizing pulse and a few cycles of the burst (3.58 mc) signal. The sync pulse synchronizes the set to the line rate of the generator, and the burst signal syncs the receiver circuits to the generator color signal. The entire color signal is shown at D in Fig. 2, with the various colors labeled: green, yellow, red, magenta, white, cyan, and blue—in that order.

In addition to the color signal, the Model 656XC also provides vertical and horizontal bars, dots, and a crosshatch pattern. The bars are developed by chains of blocking-oscillator dividers, using a crystal-controlled 315-kc oscillator as the master timer. The vertical bars are generated directly by the 315-kc oscil-

lator, and are shaped by a gating circuit into the thin line seen on the color-receiver CRT.

The horizontal bars result from a chain of dividers—a 31.5 kc blocking-oscillator divider, a 4500-cps divider, and a 900-cps divider. The output is fed to a gating circuit, where the pulses are shaped into thin horizontal lines. The crosshatch pattern is formed by mixing the two bar signals (horizontal and vertical) before they enter a special shaping circuit, while the dots are formed by eliminating the crosshatch bars and using only their junctions or crossover points.

Vertical and horizontal deflection-sync pulses are developed by other divider networks, but are keyed by the same 315-kc timer which controls the bar signals. A 15,750-cps divider follows the 31.5-kc oscillator-divider mentioned earlier; the 15,750-cps signal is fed through a pulse-shaping amplifier to a sync adder. Vertical sync signals come to the sync adder from a 60-cps divider stage, which follows the 900-cps divider in the horizontal-bar circuit.

The sync signal from the adder is combined with the bar signals in a video-mixing stage, and the composite signal is fed to a cathode follower. At this point in the circuit, the video signal is coupled to a VIDEO OUTPUT jack on the panel of the instrument, so it can be fed directly into the video amplifier of a color set, if desired. As an alternative, the MODULATION switch connects the video signal to a channel oscillator, and enables the signal to be fed into the antenna terminals. A channel switch allows the choice of any TV channel from 2 through 6.

A crystal-controlled 4.5-mc oscillator can be turned on by the SOUND ON-OFF switch. Its output is mixed with the channel-oscillator signal output to form a sound carrier 4.5 mc away from the video carrier.

The color signal is developed by a complex of shapers, dividers, adders, gate circuits, and delay lines. Fig. 3 shows a simplified block diagram of the sequence by which the NTSC signal is developed. The 15,750-cps signal is used to trigger the color multivibrators via a delay line, passing through a shaper for each multi-

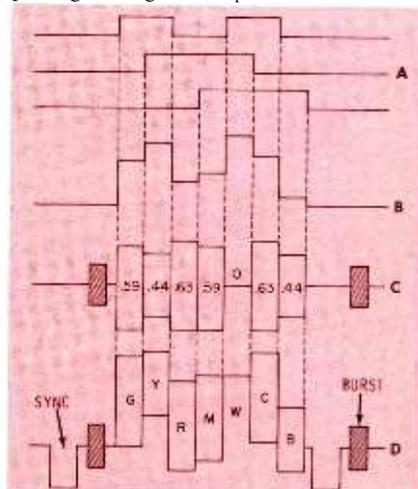


Fig. 2. Composite color signal consists of several components, pictured here.

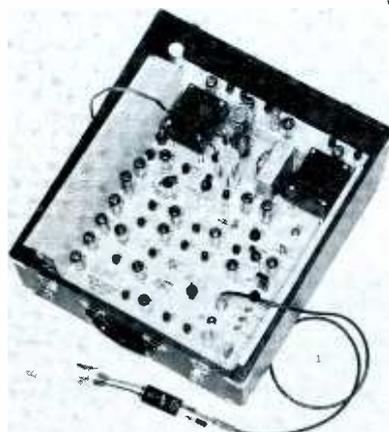


Fig. 1. Portable color generator is complex, with many tubes and adjustments.



Permohm^v and Celluline^v... TV lead-in cables give clearer, stronger color pictures



Here are two great Belden lead-in cables for color TV installations. Permohm 8285, which is encapsulated in cellular polyethylene, is specially designed for jobs where cables are exposed to salt spray, industrial contamination, and excessive ice, rain or snow. It improves fringe area reception and strengthens UHF and color TV reception.

Celluline 8275 eliminates all possible moisture between conductors . . . thus maintaining uniform electrical characteristics. The outer wall is of thick polyethylene which protects the cable from abrasion and sun damage. The result is a long lasting, efficient transmission line which gives you clearer color, and black and white images.

Order Permohm and Celluline from your Belden jobber. He also carries Weldohm†, standard 300-ohm line, and Belden's ivory colored decorator lead-in.



Be a Cartoon
Gag Writer

Win a \$25.00
Savings Bond

Send us your gag ideas for future cartoons. For each of your gag ideas used, we'll send you a \$25.00 Savings Bond. Write Belden Manufacturing Company. Attention: Mrs. Madelsa Allison, 415 S. Kilpatrick Avenue, Chicago 80, Illinois.

*This month's winner: Mr. Walter C. Downes, Jeannette, Pennsylvania.



^vBelden Trademarks and Patents—U. S. Patent No. 2782251 and 2814666

†Belden Trademark—Reg. U. S. Patent Office



For best results squeeze bulb from sides rather than up against handle

ENDECO DESOLDERING IRON

removes soldered connections quickly . . . easily . . . profitably

No need to send your printed circuit boards out to a specialist when you have an Endeco Desoldering Iron. You'll find it easy to remove transistors, transformers, condensers, resistors, diodes and even those difficult multiple pin or button type sockets with center posts. Endeco puts the profit margin back into your printed circuit work.

Any iron will melt solder; Endeco with its vacuum pickup completely removes melted solder . . . collects it in a non-breakable, stainless steel tube. The exclusive compact design lets you see the connection while you're desoldering. One hand operation.

No need to reach for another tool. Without even changing tips, you can resolder a clean, new connection. Worn tips are easily replaced, when it is necessary, even while iron is hot.

Endeco Desoldering Iron is not an attachment, but a complete desoldering/resoldering tool. The desoldering principle (pat. pending) is incorporated into the rugged Weller soldering iron with the exclusive Weller Magnastat sensing device in tip body which maintains constant temperature.

The new Model 100A Endeco Desoldering Iron is available at your electronic distributor or write direct.



ENTERPRISE
DEVELOPMENT
CORPORATION

917 Circle Tower Building
Indianapolis 4, Indiana

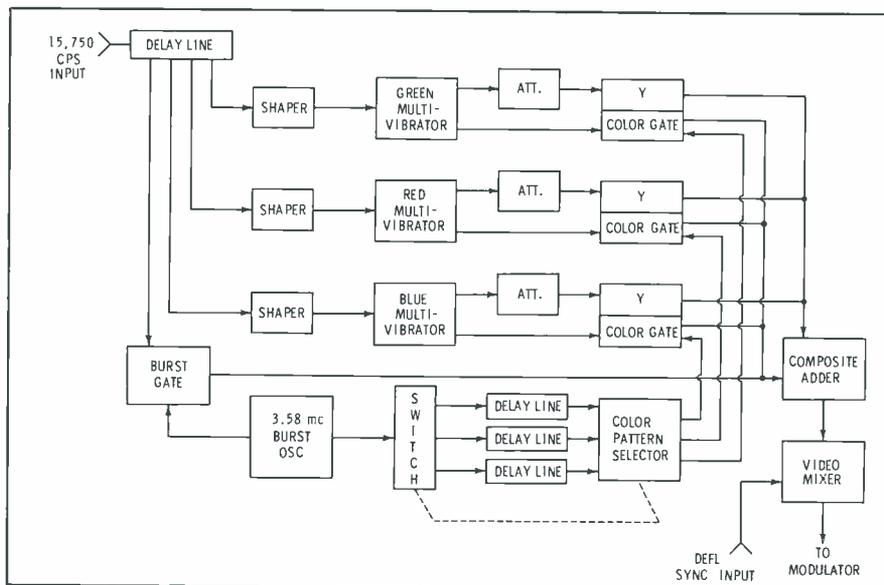


Fig. 3. Functional block diagram shows how the chroma signal is developed.

vibrator. The delay line is tapped at several points, to offer varying degrees of time lag to the trigger signals; as a result, each signal has a differing phase relationship with the beginning of each scanning line, and its position on the line is thus controlled. These positions are represented by the presentation in Fig. 2, which shows the beginning and end of each bar in the display.

The output of each multivibrator is split, and a portion is fed to a Y-signal adder. This circuit sets the height of the bars in A of Fig. 2; presentation B shows how these three bars appear when they are combined in the composite-adder circuit. This is the Y, or brightness, component of the color signal, representing the saturation of each bar.

The other portion of each color-multivibrator output is fed to a gating circuit.

Meanwhile, the 3.58-mc burst oscillator is fed to one or more of the color-gate stages, where it is mixed with the color-multivibrator signal. The outputs of these three stages are combined, resulting in the signal represented by C in Fig. 2, and fed to the composite adder.

The output of the composite adder contains the C and B signals. To this is added, in the video mixer, the deflection-sync pulse—resulting in the NTSC composite color-bar signal shown at D. This

is the signal fed to the modulator, for impression on the video carrier.

Using the Model 656XC was simple, with no problems such as jitter or bounce of the bar patterns. The blocking-oscillator-divider arrangement is extremely stable for frequency division, resulting in good pattern stability on the CRT screen. We tried convergence using all four patterns, and succeeded in adjusting our test receiver quite well.


Next, we undertook color-AFC alignment, refining the phase and AFC adjustments by using the color-bar presentation. For demodulator alignment, the Model 656XC offers another color presentation, which we haven't described as yet. It consists of either of two signal combinations—G-Y (90°) with -G-Y, or B-Y with R-Y. On the screen, either combination results in a special display which facilitates adjusting the demodulator or matrix circuits in the color chassis.

The tubes used in the 656XC are mainly 12AT7's, 12AX7's, 12AV7's, and 6U8's. A 12BH7, two 6BJ7's and three 5963's (the blocking oscillator-dividers) round out the complement of signal tubes. For the B+ supply, an OA2 regulator tube maintains a constant output from a type 83 mercury-vapor rectifier. Field adjustments appear uncomplicated, and

MERCURY TUNER SERVICE, INC.

890-1 River Ave., Bronx 51, N.Y.

"Largest in the East"

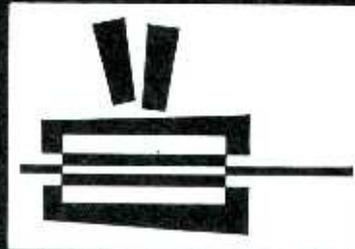

VHF-UHF TUNERS

One Year Warranty

Price Includes Labor & Minor Parts

TUBES & MAJOR PARTS
AT NET PRICES

When Shipping Tuner: Include Tubes,
Shields and Damaged Parts.
Give Model Number and State Complaint

PACK WELL AND INSURE
24 HOURS ON POPULAR TYPES

ALL MAKES
ONE PRICE!

\$9.50

REDUCE INVENTORY! INCREASE SALES!

**5 ADMIRAL
ENSIGNS REPLACE
43 TUBE TYPES**

**You save space, save dollars—
make more dollar profit per sale!**

...with the Admiral ENSIGN "Big 5" as your basic tube inventory. Less stock, more sales—and you make more profit! That's sweet music! Every Admiral ENSIGN tube is of fine/precision quality manufacture. All materials and parts used in the manufacture of these tubes are *new* except for the envelopes, which prior to reuse, have been inspected and tested to the same standard as new envelopes.



Call your ADMIRAL DISTRIBUTOR tomorrow... start cutting inventory cost, pocketing new profits right away!

BE WISE... STANDARDIZE ON

ADMIRAL[®]
ENSIGN

<p>ENSIGN 17BJP4 REPLACES</p>	<p>17ATP4 17AVP4A 17ATP4A 17BUP4 17AVP4 17CBP4</p>	<p>17CLP4</p>
<p>ENSIGN 21AMP4A REPLACES</p>	<p>21ACP4 21AQP4 21ACP4A 21AQP4A 21AMP4 21CUP4</p>	<p>21BSP4</p>
<p>ENSIGN 21CBP4A REPLACES</p>	<p>21FLP4 21ATP4 21CBP4B 21ALP4 21ATP4A 21CMP4 21ALP4A 21ATP4B 21CVP4 21ALP4B 21BAP4 21CWP4 21ANP4 21BNP4 21DNP4 21ANP4A 21BTP4 21CBP4</p>	
<p>ENSIGN 24CP4A REPLACES</p>	<p>24ADP4 24ATP4 24CP4 24AVP4 24QP4 24AVP4A</p>	<p>24XP4</p>
<p>ENSIGN 24AEP4 REPLACES</p>	<p>24DP4A 24ANP4 24YP4 24ZP4</p>	

REPLACEMENT PICTURE TUBES—ALWAYS FINE/PRECISION QUALITY

seldom will be required. If they are, the controls are easily accessible without disassembling the unit.

Checks Connected Capacitors

A new capacitor checker (Fig. 4) is available from EICO. The Model 955 is designed to perform in-circuit or out-of-circuit tests for shorts or opens, and to measure capacitance of large-value units. In-circuit measurements are possible even when the shunting resistance is comparatively low, due to the incorporation of a Wien bridge that balances out the circuit resistance.

Specifications are:

1. Power Required—117 volts AC; 60 cps.

2. Capacitor Tests—shorts, opens, and capacitance.
3. Capacitors Checked—shorts, all values up to 2,000 mfd (60-cps test signal); opens, checks values as low as 15 mmf (test signal, approximately 19 mc); capacitance, from .1 to 50 mfd.
4. Panel Indicator—EM84/6FG6 electron-ray tube (bright-bar pattern).
5. Controls and Terminals—TEST switch; LINE ADJ switch; RC RANGE switch; RC BALANCE potentiometer; CAPACITANCE dial; coaxial connector; special cable with two alligator clips on one end and microphone-type connector on the other.
6. Size, Weight, Price—8½" x 5¾" x 6"; 4 lbs; \$19.95 (kit), \$39.95 (wired).

The Model 955 uses a 6C4 and a



Fig. 4. The Model 955 measures capacitance and tests for shorts and opens.

special indicator tube to perform all checks. The TEST switch changes the circuit configuration to conform to the test desired. When the shorts test is being made (see Fig. 5), the capacitor under test is connected between J1 and ground. 330 volts AC is applied to the plate of V1 through R3, and 6.3 volts AC, of opposite phase, is applied to both the capacitor under test and the grid of V1 through R1 and C1. When the impedance across the test leads is greater than 10 ohms, the voltage appearing at the grid of V1 is sufficient to keep the tube near cutoff. This produces very little voltage drop across R3, allowing V2 to conduct heavily. This conduction causes a large voltage drop across R5 and keeps the indicator bars wide open (see Fig. 6A).

When the impedance at J1 is zero (such as when the test leads, or capacitors under test, are shorted), the 6.3 volts will all be developed across R1. The tube current increases, causing conduction in V2 to decrease. The voltage drop across R5 decreases and the bars close (see Fig. 6B). Impedances between 1 and 10 ohms are indicated by partially open bars (see Fig. 6C).

The instrument can also be used as a continuity checker in the SHORT position of the TEST switch. When the TEST selector is in the OPEN position, the circuit configuration shown in Fig. 7 is used; V1 is connected as a Hartley oscillator. Whenever the tank circuit comprised of C1 and L1 is oscillating, the grid voltage at V1 is slightly negative, and the bars will be open. Conversely, when there is no oscillation, the bars will close. The presence of oscillation depends on the impedance connected across the test leads



Service Technician's Portable Tube Tester, Transistor and Diode Checker

- Built-in roll chart contains test data on latest tubes, including NUVIDISTORS
- Inter-element leakage and shorts read directly on the meter
- New filament continuity test speeds checking series-string tubes
- Cathode reserve measurement provided
- Roll Chart Subscription Service assures up-to-date test data at all times

See Your Distributor, Ask for a Demonstration!
\$179.50 net

The Hickok Electrical Instrument Co.

10566 DUPONT AVENUE • CLEVELAND 8, OHIO

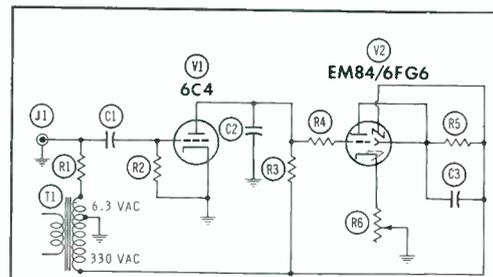


Fig. 5. Shorted capacitor across J1 removes cutoff voltage from grid of V1.



WITH A **PHOTOFACT**[®] LIBRARY YOU'RE THE MASTER

you troubleshoot in minutes any of the 53,000 TV, Home-Portable-Auto Radios, Hi-Fi and Phonographs, Record Changers and Tape Recorders, and CB Radios now on the market!

YOU EARN MORE DAILY when you have PHOTOFACT at your fingertips. It's your time-saving troubleshooting partner for everything that comes into your shop. Just reach for the easy-to-find PHOTOFACT Folder you need for any model. It provides *everything* you want—complete, uniform, authoritative.

You get: Famous Standard Notation Schematics packed with all the service details you need; full Photo Coverage of all chassis views; Complete Replace-

ment Parts Lists; Tube Placement Diagrams; full Alignment Instructions; actual Waveform Photos; CircuiTrace[®] for printed boards; Alternate Tuner data; Terminal Identification and Connections; Disassembly Instructions (including auto radio removal); Field-Servicing Notes; Dial Cord Stringing Diagrams; Changer and Recorder "Exploded Views"; Tube Test data—plus dozens of other great features.

Own the complete PHOTOFACT Li-

brary—so you can instantly put your hands on all the quick help you need for any job on your bench! If you're not now a PHOTOFACT Library owner, you're more than paying for it in the time you lose every day. So take the *right* step to time-saving, profit-building servicing—see your Sams Distributor for details on an Easy-Buy PHOTOFACT Library and Standing Order Subscription—or send coupon today!

SEND COUPON

**FREE
FILE
CABINETS**



OWN YOUR PHOTOFACT LIBRARY THIS EASY-BUY WAY

More than pays for itself from the first day you put it into your shop! Now available to you on a Special Easy-Buy Deal: • **NO INTEREST • NO CARRYING CHARGES • ONLY \$10 DOWN • UP TO 30 MONTHS TO PAY.** And you get FREE file cabinets with your PHOTOFACT Library—so you have all you need for time-saving, money-making service work right at your fingertips. Get the PHOTOFACT Library details today.

START A STANDING ORDER SUBSCRIPTION TODAY—Keep up with the rapidly-increasing current model output! See your Sams Distributor or send coupon now for full details.

HOWARD W. SAMS & CO., INC.

Howard W. Sams & Co., Inc., Dept. 7-K2
4300 W. 62nd St., Indianapolis 6, Indiana

- Send full information on Easy-Buy Plan
- Enter my Photofact Standing Order Subscription

My Distributor is: _____

Shop Name: _____

Attn: _____

Address: _____

City: _____ Zone: _____ State: _____

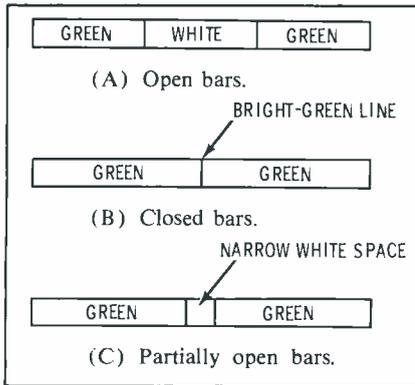


Fig. 6. Indicator-tube bar patterns. at J1. The test cable, together with L2, R1, and C3, is approximately one-quarter wavelength at 19 mc (the frequency of

the tank circuit). When there's an open circuit across the test-lead tips, a short is reflected at J1, because of the critical length of the test cable. This action shorts out a portion of L1 and causes the tank circuit to stop oscillating; therefore, the bars close. A capacitor greater than 15 mmf will represent an impedance of sufficient value to sustain oscillations and cause the bars to remain open.

Fig. 8 shows the circuit arrangement used when capacitance measurements are made. The circuitry ahead of C2 represents a comparison bridge. When this bridge is balanced, there is no voltage applied to the grid of V1 from the bridge; so the bars are closed. An unbalanced bridge causes the bars to open. The bridge is balanced by using R4A or R4B (depending on the position of S2) in

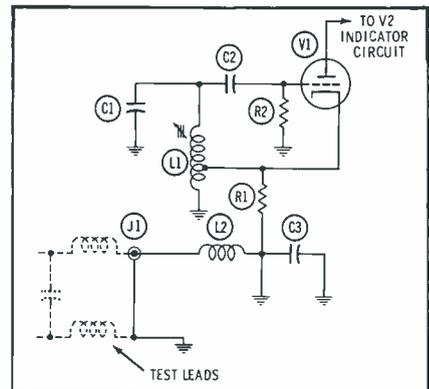


Fig. 7. An open circuit across the test leads causes V1 to stop oscillating.

series or in parallel with standard capacitor C1. When the impedance of the entire combination equals that of the capacitor under test (and its shunt resistance), the bridge is balanced.

Capacitance measurements with this instrument require more than usual care. The R-C product (the expected value of the capacitor under test multiplied by the shunt resistance) should be either calculated or estimated and set up on the RC RANGE or RC BALANCE controls. If this value cannot be determined, you should set both controls to infinity. Rotate the CAPACITANCE dial until the indicator bars reach the point of maximum closure; then, adjust the BALANCE control to improve the closure. The CAPACITANCE dial and BALANCE control are alternately adjusted until maximum closure is found; the dial then reads the value of the capacitor.

Another point to watch out for when measuring parallel capacitors: When the value of a capacitor is being measured in the circuit, the tester will indicate the total parallel capacitance. This could cause false indications, especially if the parallel unit is a large-value electrolytic filter.

We used several known-good and known-bad capacitors to put the Model 955 to work. Everything went fine, with the instrument spotting all opens and shorts both in and out of the circuit. We measured the values of several capacitors that were within the range of the instrument. The electrolytics all measured within 10% of their rated value, and the paper and Mylar tubulars above .1 mfd read within tolerance.

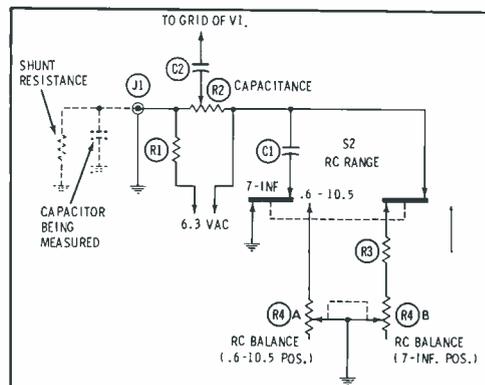


Fig. 8. When bridge circuit is balanced, capacitance is shown on the dial.

THE INDUSTRY'S STANDARD
Most Widely Used Today
by Professional Servicemen

SAVE
CUSTOMERS
MAKE
MONEY

CATHODE
REJUVENATOR
TESTER

FAMOUS DELUXE **B&K** CRT 440

For Black & White and Color

"Most valuable and useful" . . . "Wouldn't be without it" . . . "Pays for itself over and over again" . . . servicemen say. Quickly checks and corrects television picture tube troubles in a few minutes right in the home without removing tube from set. Gives new life to weak or inoperative tubes. Checks for leakage, shorts, open circuits and emission. Removes inter-element shorts and leakage. Repairs open circuits and low emission. Restores emission and brightness. Life Test checks gas content and predicts remaining useful life of picture tube. Makes new tube sales easier. Completely self-contained. Rich leatherette-covered carry-case. Net, \$74.95

TESTS AND REJUVENATES
all picture tubes at correct filament voltage from 1 to 12 volts

TESTS AND REJUVENATES
110° tubes and the new 19" and 23" tubes

TESTS AND REJUVENATES
color picture tubes. Checks each gun of color tube separately

UP-DATE YOUR B&K CRT WITH THESE ACCESSORIES


Model C40 Adapter. For use with previous Models 400 and 350 CRT's—to test and rejuvenate TV color picture tubes and 6.3 volt 110° picture tubes. **Net, \$9.95**

Model CR48 Adapter. For use with previous Models 400 and 350 CRT's—to test and rejuvenate 110° picture tubes with 2.34, 2.68, and 8.4 volt filaments. **Net, \$4.95**

Subscribe to New Picture Tube Information Service.

See Your B&K Distributor, or Write for Catalog AP20-R

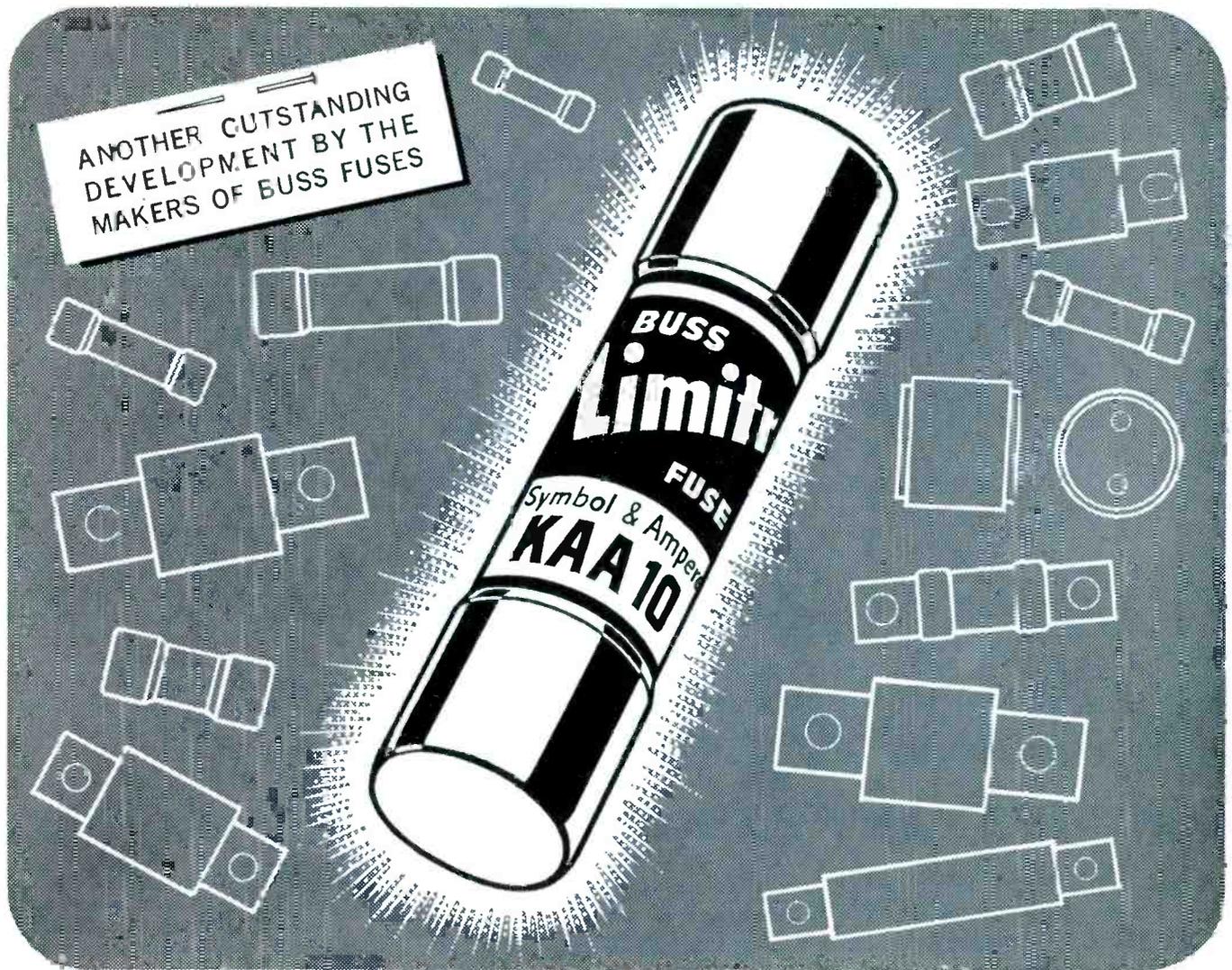B&K MANUFACTURING CO.
Division of DYNASCAN CORPORATION
1801 W. BELLE PLAINE AVE • CHICAGO 13, ILL.
Export: Empire Exporters, 277 Broadway, N.Y. 7, U.S.A.
Canada: Atlas Radio Corp., 50 Wingold, Toronto 19, Ont.



*For Protection of
Semi-Conductor Rectifiers—
BUSS designed special LIMITRON Fuses*

BUSS Limitron fuses are especially designed for the protection of semi-conductor rectifiers. They provide extremely fast opening on overload and fault currents, with a high degree of restriction of the let-thru current.

If each diode is protected by the proper size BUSS Limitron fuse, the fuse will open very quickly when the current drawn exceeds the rating of the diode.

Thus when a short-circuit occurs in a diode the fuse opens and takes that diode out of the circuit. This protects other good diodes in the rectifier which might otherwise be damaged.

For time-current characteristic charts ask for *BUSS Limitron fuse bulletin HLS*.

BUSS: one source for every electrical protection need

You can save time and trouble by relying on BUSS as your one source for fuses of unquestioned high quality. There is a complete line of BUSS fuses in sizes from 1/500 amperes up . . . plus a companion line of fuse clips, blocks, and holders.


BUSS fuses are electronically tested to assure proper operation under all service conditions

Every BUSS and FUSETRON fuse is tested in a sensitive electronic device that automatically rejects any fuse not correctly calibrated, properly constructed and right in all physical dimensions.

BUSS

BUSSMANN MFG. DIVISION
MAKERS OF THE COMPLETE LINE OF
FUSES OF UNQUESTIONED HIGH QUALITY

McGraw-Edison Co. • St. Louis 7, Mo.

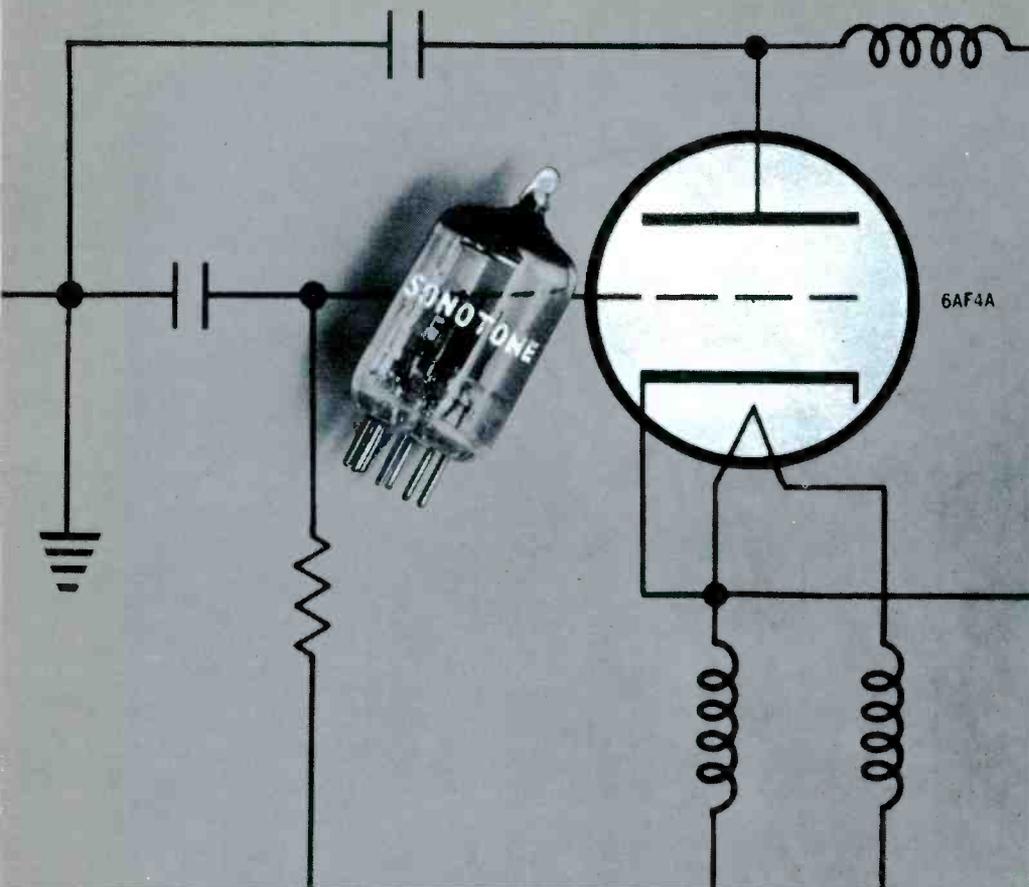

WON'T JUST ANY 6AF4A DO?

All 6AF4A tubes are designed for UHF applications — the Sonotone 6AF4A even more so! And when you're up around 800 megacycles, the extra stability you get with the Sonotone 6AF4A can make a world of difference in the performance of the unit.

There are any number of problems which the tube can introduce in a UHF oscillator circuit — drift, spurious oscillation, general instability and just plain malfunction. Whether or not they arise depends upon the tube you use. The Sonotone 6AF4A performs as it does because the manufacturer has taken unusual pains to maintain certain standards.

Every Sonotone 6AF4A is individually evacuated. A mechanically defective tube cannot contaminate the others. And any defective tube will be automatically rejected in the tests to which each tube is subjected.

More manufacturers of UHF tuners and converters specify the Sonotone 6AF4A than any other single make. Their engineers have learned that they can rely on the extra quality and performance which Sonotone engineers into its tubes. Next time you have to replace a 6AF4A, it makes sense to use a tube that will protect you from callbacks.

Just as in the 6AF4A — there's something extra engineered into all Sonotone tubes. It stands to reason that, as the first electron tube manufacturer to qualify for complete RIQAP (Reduced Inspection Quality Assurance Program) participation by the U. S. Army Signal Corps, Sonotone engineers a top quality tube. Sonotone offers more than 200 tube types; including many hard-to-get European types — home entertainment and industrial. All conform to the same high standards and are your key to replacement profits. Replace with Sonotone.

SONOTONE® CORPORATION

ELECTRONIC APPLICATIONS DIVISION • ELMSFORD, NEW YORK
Cartridges • Speakers • Tape Heads • Microphones • Electron Tubes • Batteries • Hearing Aids

We also discovered that with the instrument sitting upright on the workbench, it is very difficult to see the indicator bars. If you try to lay it on its back, you will find that the fuseholder protruding from the center of the back panel might become damaged. The best location for the 955 is on a shelf at or above eye level; with it in this position, you can look directly at the indicator tube.

In conclusion, we found the Model 955 to be a handy tester for checking opens and shorts, but its capacitance range limits its use to measuring only the larger values of capacitors.

Tube Tester—Plus

Facilities for testing picture tubes, batteries, and transistors are included in Mercury Electronics Corp.'s Model 1200 Mutual Conductance Tube Tester (Fig. 9).

Specifications are:


1. Power Required—117 volts AC; 60 cps.
2. Tests Performed—mutual conductance; cathode emission in diodes and CRT's; grid leakage and gas, sensitivity over 150 megohms; shorts; transistor beta (direct-reading); battery quality.
3. Tubes and Transistors Tested — all receiving types including novars, compactrons, 10-pin novals, and 5-pin nuvistors; monochrome and color CRT's; most popular transistors and diodes.
4. Panel Meter—face size 6"; sensitivity 1 ma; scales read mutual conductance in two ranges, emission, condition (BAD-WEAK-GOOD), beta, and gas.
5. Controls and Terminals—FUNCTION selector switch; filament SELECTOR switch; 26 push buttons (and two release buttons) for setting up tests and selecting elements; LOAD potentiometer; universal transistor socket; 13 sockets for various tubes; 7- and 9-pin straighteners; TRANSISTOR - BATTERY function rotary switch; BATTERY VOLTAGE rotary switch; LEAKAGE-GAIN slide switch; three pin jacks for testing batteries and transistors; neon SHORTS indicator; red POWER indicator; CRT test cable with sockets for monochrome and color tubes; various clip leads for connecting top caps, transistors, and batteries.
6. Size, Weight, Price—18¼" x 10¾" x 4¾"; 11½ lbs; \$119.95.

The tube-test portion of the Model 1200 is very similar, circuitwise, to the Model 1000 covered in August Notes. The same



Fig. 9. Tubes and transistors both can be tested on the Mercury Model 1200.

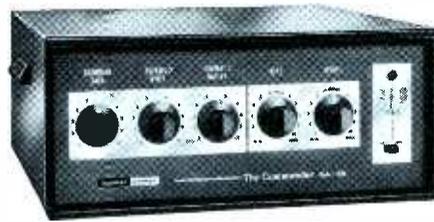For your next P.A. job, for every P.A. job,



Commander Series

Harman-Kardon gives you versatility,



Galaxy Series

top value and exclusive features



Troubador Series

in each of these complete lines!

Commander Series: Popular priced equipment with facilities and versatility seen only in "de luxe" amplifiers till now. 12, 35, and 100 watt amplifiers and a 4-channel mixer/preamplifier. Durable, continuous-duty equipment which opens a new range of applications that can now be serviced with popular priced p.a. units.

Get the full story!

Galaxy Series: A new concept in p.a.—modularized 40, 75, 150 watt amplifiers, boosters and 8 channel mixer, offering the quality of custom sound with installation ease of compact equipment. Pre-amp modules — give you precise equipment for any need, allows for expansion at any time at minimal cost; equipment never obsolesces.

Get the full story!

Troubador Series: Extra services and application flexibility unduplicated by any other transistorized equipment. A 15 watt mobile transistorized amplifier and a 30 watt portable transistorized DC or AC/DC amplifier. These amplifiers will find uses in police, fire, marine, construction, rental and other applications.

Get the full story!

Built by Sound Men for Sound-Men

harman kardon

For full details, write: Commercial Sound Div.

Desk H-10, Plainview, L.I., New York

BERNS PERFECT PIN-CRIMPER

Picture-Tube Repair Tool

Eliminates that hard soldering job.

only \$1.25

PT-1

Fix loose pin connections in seconds. Pays for itself in time saved on one job alone. 3" long.

U. S. Pat. 2,878,698
Canadian Pat. 592,702

Intermittent operation of picture tubes due to defective solder connections at socket pins is easily corrected through the use of the Berns Perfect Pin Crimper. Actually a 3-in-1 tool that can also be used as a channel-selector wrench and screwdriver, it serves to notch pins and element leads to provide solid electrical connections. Pin keeps its original form.

3 models: PT-1 for 3/32" pin diameter; AU-2 for 1/8" pin diameter and installing C rings; LC-3 for 5/32" pin diameter.

Available at your parts distributor.
Another fine product from:

BERNS Mfg. Co.
9853 Chalmers,
Detroit 13, Mich



Duotone needles, of course . . . tipped with genuine diamonds, synthetic sapphires or osmium.

Most people forget to change their styli or don't know how to change them. Why not suggest a Duotone diamond needle replacement for every phonograph that comes into your shop? It's the stylus with the diamond tip that's handset and hand polished. Your customers will appreciate the service and you'll appreciate the increase in business.

Write for Free 1962 Duotone Needle Wall Chart and see DUOTONE Distributor.

DUOTONE
COMPANY, INC. KEYPORT, N. J.

bridge circuit is used to measure mutual conductance; gas, emission, and shorts tests are also performed by similar circuitry. The most important differences are in the switching arrangements for connecting tube elements to the test circuits.

Each push button in the top row, when it is depressed, connects its corresponding socket pin to a source of B+ voltage (see Fig. 10). In the released position each is connected to the corresponding button in the lower row. These lower buttons connect to ground, in their normal position; when depressed, they connect to bias-and-signal voltages. Thus, any lower switch, which has been selected by an upper switch, ultimately either grounds the corresponding tube element or applies an operating voltage.

This arrangement simplifies the testing procedure and reduces the chance of setup errors; if a top button is depressed, its corresponding lower button is entirely disconnected from the circuit. This feature goes a long way toward preventing damage to either the tube or the tester.

In order for a tube to be tested, its identification number is first found in the setup booklet. The proper filament voltage is picked by the SELECTOR switch, and the LOAD potentiometer is set to the value listed in the chart. Next, the tube is inserted in the correct socket, and the FUNCTION switch is turned to the SHORTS position. The release button for the top row is held down and buttons "A" through "J" are pressed, one at a time, while the SHORTS indicator is watched; a steady glow indicates a short. Usually, when two elements are shorted together, the neon lamp will glow as either corresponding button is pressed. However, the lamp will go out if both buttons are held down at the same time.

For the mutual conductance (Gm) test, the FUNCTION switch is advanced to the GM-EM position and the buttons listed in the setup chart are depressed. The value of Gm indicated on the panel meter is compared to that listed under "Rated Gm" in the chart. If there is no Gm value listed (as in the case of diodes and CRT's), the tube is being given a dynamic emission test; emission quality is read on the BAD-WEAK-GOOD scale of the panel meter.

Gas tests are quick and simple with the Model 1200. The FUNCTION switch is advanced to the GAS-GRID LEAKAGE position and the listed buttons are pressed. A meter reading in the small green area of

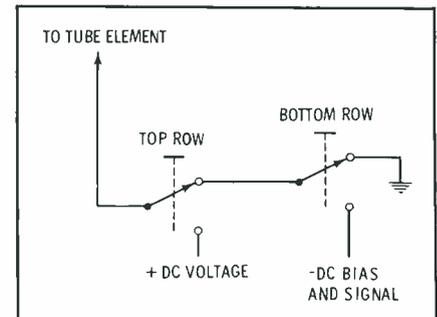


Fig. 10. Unique push-button arrangement provides DC to tube elements.

Complete Assortment

of EXACT REPLACEMENTS THERMAL CIRCUIT BREAKERS

17 MODEL NUMBERS

F2A SILVERTONE MOTOROLA G.E. WESTINGHOUSE WESTERN AUTO

F2A-B MOTOROLA 80C750604

F2A-C WESTINGHOUSE 753V006H01

F2.1A SILVERTONE 43-9-2

F2.2A MOTOROLA 80C66390A02

F2.2A-B ADMIRAL 84B17-4

F2.5A WARWICK 43-1-2

F2.6A RCA 945830-2

F2.75A SILVERTONE 43-12-2

F2.75A-B MOTOROLA 80C66390A01

F2.75A-C MOTOROLA 80K753396

F2.75A-D PHILCO 42-2136-1

F2.75A-E RCA 945830-1 G.E. ET10X32

F3A MAGNAVOX 180672-1

F3A-B MOTOROLA 80K647226

F4A PHILCO 42-2136-2

F4A-B EMERSON 808018

EXACT REPLACEMENT RESET THERMAL CIRCUIT BREAKERS

ADMIRAL MOTOROLA WESTERN AUTO G.E. WARWICK HUBSON PHILCO SILVERTONE WESTINGHOUSE

72¢ EA. DLR. NET

LOOK FOR THIS DISPLAY AT YOUR FAVORITE DISTRIBUTOR

WRITE FOR *Free* CROSS REFERENCE TO:

WORKMAN Electronic PRODUCTS, INC.
BOX 5397 SARASOTA, FLA.

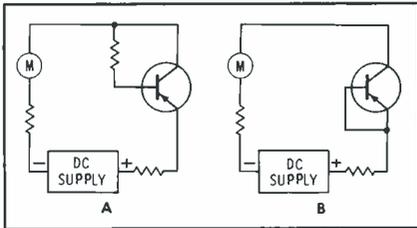


Fig. 11. Gain and leakage tests are performed by these simplified circuits.

the GAS scale indicates some gas is present in the tube, but not enough to impair its operation. If the meter reads in the large red BAD area, the tube should be rejected.

A meter indication will be obtained in the leakage test if the leakage resistance is 150 megohms or less. A resistance below 100 megohms will produce enough leakage current to deflect the meter into the BAD zone of the scale. Only in extremely critical circuits will a tube need to be replaced if the gas reading falls in the small green area at the left end of the scale.

A multiple-socket adapter is provided with the tester, to allow testing of both monochrome and color CRT's. These tubes are checked in a manner similar to that used with receiving tubes, except they are tested for emission rather than Gm. CRT's can also be tested for gas content and shorts.

The adapter also contains a COLOR GUN switch to check, individually, each gun of a color CRT. The switch is first set on the RED position and the tube tested the same as a monochrome type. Then, the green and blue guns are checked in like manner, with the switch set to their corresponding positions.

The transistor socket and battery jacks can be seen on the right side of the instrument. Transistors are checked for gain by the simplified circuit shown in Fig. 11A. A transistor is either plugged into the universal socket or connected to the three pin jacks on the front panel (clip leads are provided with the tester). No setup charts are used to test transistors; the value of DC beta is read



NEW SECO "TRI-TESTER"

With Seco's Patented Grid Circuit Test—copied by many, equalled by none



Model 107A

ONLY \$14950 NET



Tests all tubes including the new Nu-Vistors, Novars, Compactrons and 10-pin types.

©1961 Seco Electronics, Inc.

The Seco 107A "Tri-Tester" is the finest, fastest, most complete tester on the market—and at a popular price. Extremely accurate and easy-to-use, this deluxe model provides all essential tests for a wide range of Radio-TV, Industrial and Foreign tube types including sub-miniature types.

Eye and Line Adjustments are set up only once—not individually for each tube. Handy new "FLIP-CHART" tube index lists complete tube data set-up information. Cards on new tube types are issued to registered owners, keeping your unit up-to-date. The

107A "Tri-Tester" is compact, portable and completely self-contained in a handsome, vinyl plastic carrying case.

Seco is a pioneer in the field of modern tube testing research—the originator and exclusive patent holder of the nationally accepted Grid Circuit Test. The "Tri-Tester" is well accepted as a standard by both industry and government agencies. It meets specifications for: FEDERAL STOCK CLASSIFICATION, Tube Tester Type 107-FSN-6625-713-9075. Make your next purchase a Seco product.

ONLY SECO GIVES YOU ALL THESE TESTS IN ONE TESTER

GCT

DMCT

CET

GRID CIRCUIT TEST:

All tubes get 11 positive, simultaneous checks for leaks, shorts and grid emission. This Seco designed and patented "Electron-Eye" test detects "hard to find" faults passed up by conventional short tests.

DYNAMIC MUTUAL CONDUCTANCE TEST:

Pre-wired chassis for effective testing of voltage amplifier and similar tube types. "Fil. Sel." and "Load" are the only settings required. "Good?-Bad" meter indicates relative trans-conductance.

CATHODE EMISSION TEST:

The best method for testing pulse amplifier, power output and damper type tubes. Number of set-up operations is kept to a minimum. This test is provided by the free point selector system.

See your distributor for complete details on the Seco Model 107A Tube Tester. He has a complete line of quality Seco units for testing electronic equipment.



SECO ELECTRONICS, INC.

1221 South Clover Drive, Minneapolis 20, Minn.

- Please send Free... Model 107A Operating Instructions and Schematic
 "How to Test Tubes" Chart
 Complete Seco Electronic Equipment Line Folder

NAME _____
 ADDRESS _____
 CITY _____ STATE _____

why does
Blonder-Tongue
offer two new
indoor boosters?



Let's talk straight-from-the-shoulder about indoor boosters. Transistor boosters provide higher gain and are more rugged, but they have one problem—overload (windshield wiper effect, loss of sync, etc.). If you use a transistor booster in an area with one or more strong TV or FM signals — *you may be buying too much booster!* On the other hand, tubed boosters perform very well in these areas — and what's more, they cost less. That's why Blonder-Tongue has two new home indoor boosters — the transistor IT-4 Quadrabooster and the frame-grid tubed B-33 Amplicoupler.

The B-33 costs less than the transistor IT-4, \$19.95 as against \$29.95. In most cases, the extra cost of the IT-4 is more than justified by its remarkable performance and long life. However, if the B-33 can do the job, we don't want you to spend more than is necessary for the finest TV reception.

Which one is best for you? Try one, or both. They can be hooked up in seconds at the set terminals. Try them on all channels. With either an IT-4 or a B-33, you'll end up with the best TV reception possible.

BLONDER-TONGUE IT-4 TRANSISTOR QUADRABOOSTER • 4 to 8X increase of signal voltage for 1 set • improves reception on up to 4 TV or FM sets • long-life transistor • striplless terminals • exclusive neutralizing circuit minimizes overload. List **\$29.95**

BLONDER-TONGUE B-33 FRAME GRID AMPLICOUPLER • More than 2X increase of signal voltage for 1 set • Improves reception on up to 3 TV sets • Lowest price multi-set booster on the market. List **\$19.95**

indoor or outdoor • tubed or transistor • VHF or UHF • 1 set or 4 sets

BLONDER-TONGUE TV/FM BOOSTERS

MODEL AB-4-AC, Transistor Mast-Mounted TV/FM Booster w/remote AC power supply. Provides brilliant reception on up to 4 sets from a single antenna. Takes advantage of the optimum signal-to-noise ratio.List **\$34.95.**

MODEL AB-4 with remote battery power supply.List **\$29.95.**

MODEL B-24c, 4-set TV/FM Booster. Low cost home TV system uses rugged frame grid tube to power for as many as 4 TV or FM sets.List **\$24.95.**

MODEL BTA, TV Booster. Lowest cost booster on the market. Improves TV reception in prime or weak signal areas.List **\$15.50**

MODEL UB, UHF Booster. Brings in UHF where all other methods fail. 5 models cover all channels from 14 to 83.List **\$93.50.**

engineered and manufactured by

BLONDER-TONGUE
9 Alling St., Newark, 2 N. J.

PF-10

Canadian Div. Benco Television Assoc., Ltd., Toronto Export: Rocke Int'l, N. Y. 16, Cable: ARLAB
Home TV Accessories • UHF Converters • Master TV Systems • Closed Circuit TV Systems • CATV Systems

directly from the meter scale, and any indication between 20 and 100 indicates the transistor is conducting. Even though the unit conducts, leakage checks should be made in order to test the semiconductor completely. Fig. 11B shows the circuit employed for leakage tests. The slide switch is set to the LEAKAGE position, and the amount of leakage is indicated on the GAS TRANSISTOR-DIODE LEAKAGE scale of the meter.

Power transistors and diodes are given a forward-to-reverse current ratio test by reading reference values on the BETA scale. A small DC voltage is impressed across the component, and the current is measured by the meter.

Batteries are checked under full load current by the tester. The BATTERY VOLTAGE switch is set to the rating of the battery under test. This applies the correct load and allows the battery quality to be read on the GOOD-WEAK-BAD scale of the meter.

Using tubes and transistors of known quality, and batteries in various conditions, we tried out the Model 1200. The shorts tests not only showed up all known shorts in the tubes, but also indicated tube elements which were internally tied together. A notation in the setup booklet pointed out when to expect this indication of internal connections. As was mentioned previously, the gas test performed by this unit is extremely sensitive. Even those tubes which contained very slight amounts of gas were detected by the Model 1200. The Gm readings taken on amplifier tubes conformed closely to the known value for those tubes; tests performed on CRT's were accurate, too, and spotted the defective ones in our "library."

The transistor test, while it does not provide a complete analysis of semiconductors, does give a quick check to determine whether the unit is good or bad. The leakage test proved most dependable, quickly spotting our leaky and shorted samples.

Front-to-back tests were made on several diodes, and the results evaluated according to information contained in the instruction manual which accompanies the tester. Acceptable ratios are listed for all types of rectifiers, including silicon, germanium, and selenium units. The ratios obtained in our tests were crosschecked with a VOM and found to be reasonably accurate.

The Model 1200 tester is useful in the shop that services both tube and transistor equipment. Except for those rare cases where unusual transistor troubles require a complete analysis of the component, the Model 1200 provides the shop with complete testing facilities for tubes and transistors. ▲

now in our lab . . .

We're analyzing these test instruments for future Notes columns.

B & K Model 625 3-in-1 Tester
Electro Model EC-2 Power Supply
Paco Model G-34 Sine-Square Gen.
Seco Model 250A Transistor and Tunnel Diode Tester
Sencore Model PS120 Scope

TESTING MAGNETIC AMPLIFIERS

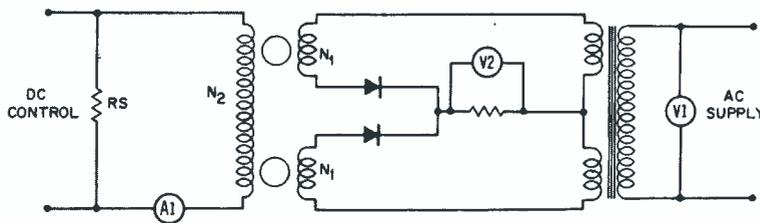


Fig. 1. Test arrangement for obtaining amplifier control characteristics.

Of all the unusual electronic devices which are enjoying increased popularity, magnetic amplifiers are probably the least understood. The reason seems to stem from the fact that they utilize certain principles which are unfamiliar to most electronic servicemen. Actually, many technicians don't even regard them as electronic devices. In reality, however, magnetic amplifiers use components which are familiar to every serviceman; the only difference between them and other elec-

The material used in the preparation of this article was taken from the Howard W. Sams book "Fundamentals of Magnetic Amplifiers" by Barron Kemp.

tronic circuits is the method of energy transfer, or (more accurately) controlling the energy transfer. (For a complete discussion of the operating principles of magnetic amplifiers, see PF REPORTER, November, 1960.)

Even relatively trouble-free equipment eventually needs routine maintenance and testing. The technician responsible for maintaining "mag-amps" should familiarize himself with the various methods of checking transfer characteristics, transient response and temperature rise.

Transfer Characteristics

The test circuit of Fig. 1 can be

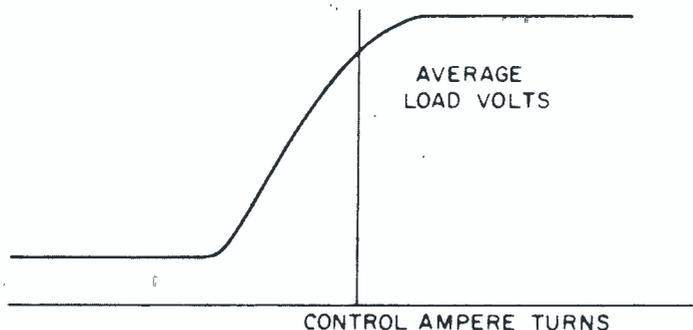


Fig. 2. Plotting load voltage vs control ampere-turns yields transfer curve.

NEW
antenna
specialists
brand

Black Beauty Fiberglas CB antennas

now you can whip two problems most common to fiberglas antenna performances!

First: through the "black magic" of exclusive Thermofit PVC process, brittleness and cracking are eliminated. Much more resistant to constant abrasions.

Second: The durable, black finish is inconspicuous yet gives an impressive, clean, classic look to your car. Looks good even after long, hard use. Center loaded and only 48" high. Choice of mounts. Available right now at your CB supplier or, for further information, write to


"Stripes of Quality"



the
antenna
specialists
co.

12435 Euclid Avenue
Cleveland 6, Ohio

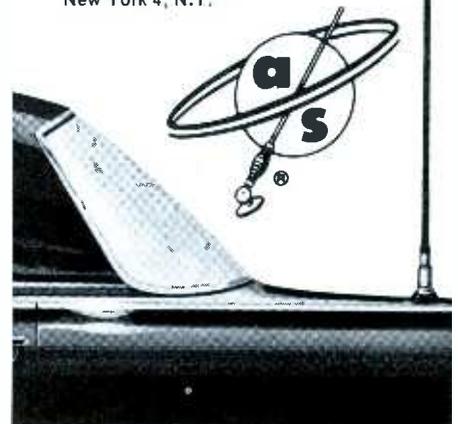Export Div., 15 Moore St.,
New York 4, N.Y.





Look!

... coming next month

COLOR TV special issue

Objective: Pure White

... shows the way to convergence without confusion.

Chroma Demodulator and Matrix Stages

... explains how red, green, and blue are recovered.

Aids to Color-TV Servicing

... describes accessories that save time and effort.

Answering Customers' Color Questions

... prepares you for almost anything they might ask.

A Look Inside a Color TV Station

... reveals the complexities of transmitting color.

Previews of New Sets

... covers the new RCA CTC12 and Zenith 27KC20 chassis.

Video Speed Servicing

... gives field-service tips for last year's color sets.

ALSO:

Interpreting Your Inventory

Corona—In the Cage and Out

Symfact Coverage of Vertical Multivibrator

Get Free Premium Books With Subscription

Enter my subscription to PF REPORTER and send me free book(s) checked.

3 Years \$9.00 2 Years \$7.00 1 Year \$4.00

The Troubleshooter's Handbook
 Servicing Industrial Electronics
 Servicing TV from Tuner to Picture Tube } Check one for each year you subscribe

Bill Me Remittance Enclosed Extend Present Subscription

Take this coupon to your distributor, or mail to:

Howard W. Sams & Co., Inc.

4300 W. 62nd St., Indianapolis 6, Ind.

Name _____

Firm _____

Address _____

City _____ Zone _____ State _____

Please Check Your Business Classification

- Independent Radio, TV Serviceman
- Retailer with Service Department
- Industrial Electronics Service
- Other (Specify occupation and title)
- Owner, Mgr.
- Service Mgr.
- Employee

used for obtaining data relating the load-circuit response with the control ampere-turns. The plot of average load-voltage versus control ampere-turns is called the control, or data, transfer-characteristics curve. A typical curve is shown in Fig. 2. The frequency, amplitude, and waveshape of the AC supply all affect amplifier characteristics. Hence, when obtaining data using the circuit of Fig. 1, care should be taken that the frequency does not vary, the supply voltage is maintained constant throughout the test, and the supply-voltage waveshape is not distorted.

For AC output-circuits, it may be desirable to plot rms output-current versus control ampere-turns. In this case, the average value of the AC load-current, or voltage, is obtained through bridge rectification. It is then multiplied by a form factor which allows for the use of rms rather than average voltage and current. Several magnetic amplifier manufacturers use a form factor of 1.1 (approaching a sinusoidal wave); however, it is only during maximum output that the waveshape is essentially sinusoidal. At other levels, the varying nonsinusoidal character of the output pulses causes the form factor to vary with the magnitude of the output voltage—in such cases, the form factor is greater than 1.1. As the output is decreased to near cutoff, the form factor may approach 1.5, the exact value depending on the type of core material among other factors. On the basis of 1.1, the rms value of output current would be equal to or greater than the rms value of the sine wave with the same average value as the output current. For these reasons, control characteristics based on rms values can only indicate comparative performance of magnetic amplifiers. For absolute comparison, average values should be employed.

The power gain of an amplifier is generally expressed as the average output power divided by the input control-power, although the heating power (I^2R) of the output differs from the average power due to the pulsating character of the output. The power gain is measured on an incremental basis; that is, the change

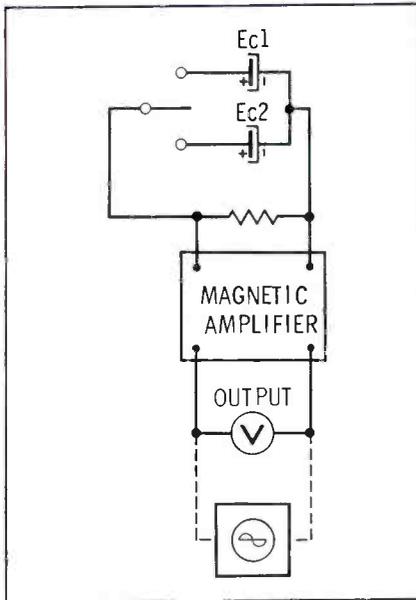


Fig. 3. Long time-constants are measured with a stop watch and indicator. in output brought about by a change in control current.

Transient Response

Measurements involving magnetic-amplifier response time may be accomplished by several methods. The measurement of time response involves determining the time that it takes for the output to change between two specified levels with a given step of control signal. (A step input-signal is a non-sinusoidal signal whose amplitude changes in discrete levels; it appears as a series of joined square-wave pulses each having greater amplitude than the preceding one and thus forming a composite signal resembling a stairway). Some manufacturers define the output swing to be 63% of the steady-state value, while others refer to 95% of static operation.



"Son, run see if daddy's got the TV set fixed yet,"

MAKING ROOM AT THE TOP



AC VTVM & AMPLIFIER #250

NEW EICO ENGINEERING ACHIEVEMENT Kit \$49.95 Wired \$79.95

Phenomenally good AC VTVM, bound to make room for itself at the top of the professional market. 12 ranges from 1 mv to 300 V full-scale, 10c-600kc ± 0 db response, 10 megohms input impedance, $\pm 3\%$ of full scale accuracy. At the flick of a switch, the internal wide-band amplifier is available for external use. Provides 8c-800kc ± 0 db response, 5 VRMS output, 5 kilohm output impedance, gain control, noise -40 db. Regulated power supply, frame grid tubes.

AC VTVM #255 Kit \$44.95 Wired \$72.95

All the precision VTVM facilities of the #250, less the external use of the wide-band amplifier.




ARMED TO THE TEST LEADS FOR THE TRANSISTOR GAME

TRANSISTOR AND CIRCUIT TESTER #680

Kit \$25.95 Wired \$39.95



Measure ICEO, ICBO & $dc\beta$ directly, $ac\beta$ indirectly, without charts or special settings—plus all dc volts, currents, and resistances needed to service transistor equipment. 50 μA , 3 1/2" face meter movement provides sensitivity and scale length necessary for accurate measurements. Built-in 20,000 ohms/volt VOM facilities let you work on transistor equipment with minimum equipment tie-up.

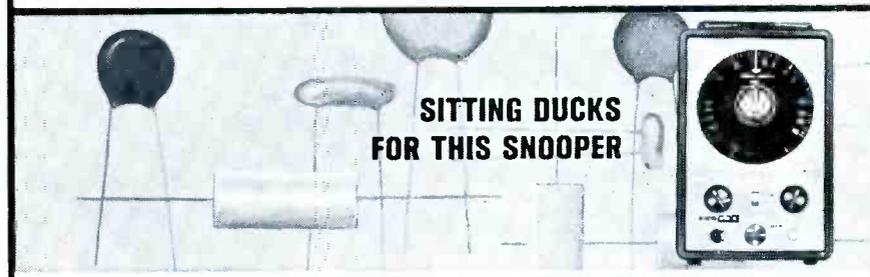

SITTING DUCKS FOR THIS SNOOPER

IN-CIRCUIT CAPACITOR TESTER #955

Kit \$19.95 Wired \$39.95



- Leave those capacitors where they are! Without unsoldering:
 - check for shorts (even in the presence of as little as 1 ohm shunt resistance)
 - check for opens (determine the presence of as little as 5mmf in the circuit), and to confirm open indication . . .
 - measure capacitance with $\pm 10\%$ accuracy between 0.1 mf and 50 mf
 - measure RC product, convertible into dissipation or power factor.

Also New From EICO:



Battery Eliminator and Charger #1064
Kit \$43.95
Wired \$52.95



AC Bench Supplies Model 1073—
Kit \$35.95
Wired \$47.95
Model 1078—
Kit \$42.95
Wired \$54.95



AC Volt-Watt Meter #261*
Kit \$49.95
Wired \$79.95

*Formerly designated as #260.



For complete catalog of over 106 EICO kits and wired units—hi-fi, test equipment, citizens radio, ham gear—plus name of nearest distributor, write to dept. PF-10
EICO ELECTRONIC INSTRUMENT CO., INC., 3300 NO. BOULEVARD, L.I.C. 1, N. Y.
Add 5% in the West Export Dept, Roburn Agencies Inc. • 431 Greenwich St., New York 13, N. Y.

Visit EICO Rooms 518 & 522, New York Hi-Fi & Music Show, October 2-7.

NEW SAMS BOOKS

JUST OUT! Enlarged 5th Edition
of the famous Howard W. Sams

Tube Substitution Handbook

Includes Over 1000
New Substitutions

Still Only \$1.50



More valuable than ever—now lists over 7,700 direct substitutions—1,078 more than in Vol. 4! Expanded Receiving Tube Directory now includes over 1,950 types, listing 4,162 substitutions. Subminiature Tube Section lists 359 types,

with 309 recommended substitutes. Other Sections list 263 industrial and 624 foreign substitutes for American receiving tubes, and 535 American receiving tube substitutes for foreign types. Picture Tube Section shows 520 types, with recommendations for 1,795 direct substitutions. A "must" for tube cad- dy and bench. 128 pages; 5 1/2 x 8 1/2". Still Only \$1.50



ABC's of Electronics

At last—a simple, easy to follow introduction to electronics. Basic principles are explained in terms of concepts familiar to anyone. In this major breakthrough to an understanding of electronics, Earl J. Waters covers principles of electricity, functions of atoms and electrons, magnetic forces relating to electronics, basic circuits and their applications, general applications of electronics. The right book for anyone wanting a basic understanding of electronics. 96 pages; 5 1/2 x 8 1/2". Only \$1.95

Electronic Test Instrument Handbook

Joseph A. Risse covers operating principles and proper use of: VTVM; Types of Tube Testers; Transistor & Diode Testers; Battery Testers; Signal Generators; Capacitance, Inductance, and Impedance Tests; Q Meters; Oscilloscopes; Frequency & Modulation Measurements; Communications System Testing; Specialized Test Instruments; Precision & Lab Test Instruments; Test Instruments for Industrial Electronics; TV and Radio Servicing Instruments. 256 pages; 5 1/2 x 8 1/2". Only \$4.95

Servicing Horizontal Sweep Circuits

Tells you how to solve the intricate and often obscure troubles which develop in horizontal oscillator-sweep circuits. Out of his long experience, Wayne Lemons reviews typical circuit designs, and draws on actual case histories to explain problems and their solution. Shows circuit adjustments you can make to help insure against callbacks; gives 50 service hints. 128 pages; 5 1/2 x 8 1/2". Only \$2.50

Automotive Electronics Test Equipment

Allan Lytel gives you the "why and how" of test equipment used in automotive servicing. Sections cover: timing lights; generator & voltage regulator testers; coil & condenser checkers; alternator testers; combustion analyzers; dwell-angle testers; tachometers; volt-ampere testers; distributor testers. Invaluable for service technicians and auto repair specialists. 128 pages; 5 1/2 x 8 1/2". Only \$2.50

Howard W. Sams Dictionary of Computer Terms

This modern, authoritative pocket dictionary defines over 850 terms and words used in computer technology. Covers analog, digital and hybrid computer system terminology; includes phrases, abbreviations and acronyms relating to coding and programming; memory-storage; logic and notation systems, and various electronic circuit categories. \$1.50 96 pages; handy 4 1/4 x 5 1/2" pocket size. Only \$1.50

HOWARD W. SAMS & CO., INC.

Order from your Sams Distributor today, or mail to Howard W. Sams & Co., Inc., Dept. K-32 4300 W. 62nd Street, Indianapolis 6, Ind.

Send me the following books:

- Tube Substitution Handbook, Vol. 5 (TUB-5)
- ABC's of Electronics (ELW-1)
- Electronic Test Instrument Handbook (ETI-1)
- Servicing Horizontal Sweep Circuits (HSL-1)
- Automotive Electronics Test Equipment (AEL-1)
- Dictionary of Computer Terms (DCT-1)

\$.....enclosed. Send Free Book List

Name _____

Address _____

City _____ Zone _____ State _____

IN CANADA: A. C. Simmonds & Sons, Ltd., Toronto 7

Stop Watch and Indicator Method

One of the simplest means for measuring a long time-constant is by use of a stop watch and an output indicator (voltmeter or oscilloscope). Once the input circuit has been adjusted for the proper swing with a simple switch arrangement (Fig. 3), the output indicator is calibrated for the starting point, and 63% or 95% of the transient. The average output is measured with the voltmeter. While using a scope, the change in the firing angle or peak voltage (when operating below half conduction) is observed. The step input-signal and the stop watch are activated simultaneously. The watch is stopped when the proper magnitude of output is achieved. Since great emphasis is placed on the ability of the operator, both in observation and in manual dexterity, the degree of accuracy available with this method varies. For time responses of one second or longer, this method is sufficiently accurate when several tests are averaged.

Recording Oscillograph Method

Another measuring method employs a recording oscillograph connected across the output as an indicating device (Fig. 4). This system yields more accurate data than the stop-watch technique because the entire transient can be recorded and the number of cycles carefully calculated. Two precautions must be heeded when using this method: the amplifier must not be loaded down by the recorder; and a sufficiently small output should be applied to avoid damage to the mechanism. One of the disadvantages of the recorder is its low carrier-frequency limit.

Square-Wave Generator Method

Another common measuring technique for response time employs a low-frequency square-wave generator of variable pulse width and phase, and a dual beam oscilloscope connected as shown in Fig. 5. The response time is determined by counting the number of cycles in the transient directly presented on the oscilloscope once the proper frequency, pulse width, and synchronization are achieved. This type of measurement is suitable for fast

Ask By Name For GENUINE

"NO NOISE" PRODUCTS

your assurance of brand name quality

No-Noise **VOLUME CONTROL** and Contact Restorer
- Cleans - Lubricates - Protects
Not a Carbon Tet Solution

2 oz. Bottle \$1.00
Net to Servicemen

6 oz. Spray Can \$2.25
Net to Servicemen

No-Noise **TUNER-TONIC** with PERMA-FILM
- Cleans, lubricates, restores all lenses, including water type
- Non-toxic, non-inflammable
- For TV, Radio and FM use.
- Economical—a little does a lot.

6 oz. Aerosol Can \$3.25
Net to Servicemen

FREE with each can of ELECTRONIC CHEMICAL products—5" PLASTIC EXTENDER

Push Button Assembly For Pin Point Applications—Does Not Cause Shorts

Electronic Chemical new formula **EC-44**
Lubricates, conditions, cleans all electrical contacts. Economical... a little does a lot!
6 oz. spray can \$3.50

ELECTRONIC CHEMICAL CORP.
813 Communipaw Avenue Jersey City 4, N. J.

EFFICIENT!

SAFE!

FAST!

ARROW'S T-25 Low Voltage Wire STAPLE GUN

For Fastening Any Inside or Outside Wire Up to 1/4" in Diameter

Takes 3 Staple Sizes:

- 3/8"
- 7/16"
- 9/16"

- Telephone wire
- Intercom wire
- Bell wire
- Thermostat wire
- Radiant heating wire
- Hi-Fi, Radio & TV wires

Tapered striking edge gets into close corners!

Available in: Brown, Ivory, Beige, Monel, Bronze, Natural

ARROW FASTENER CO., INC.
ONE JUNIUS STREET • BROOKLYN 12, N. Y.

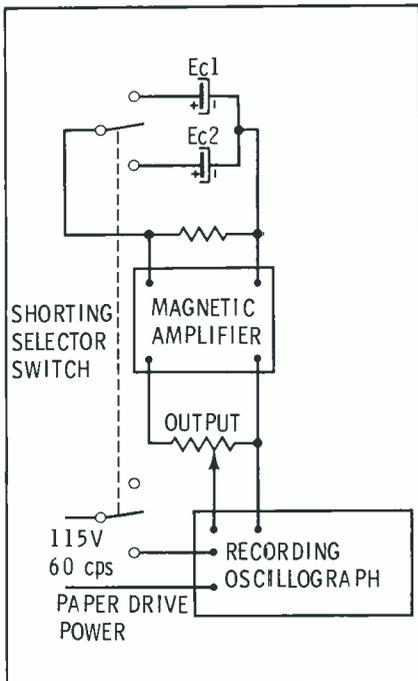


Fig. 4. A recording oscillograph is used to obtain an accurate measurement.

time-response values which are in the order of several cycles at the supply frequency.

Photographic Method

Time response measurements can also be made by photographing the transient waveform with an oscilloscope camera. Such a measurement is readily accomplished for fast responses in the order of 10 cycles or less. External synchronization of the scope sweep and the step impulse to the magnetic amplifier are actuated simultaneously. The system involves opening the camera shutter, initiating the transient, and closing the shutter. The photographic technique

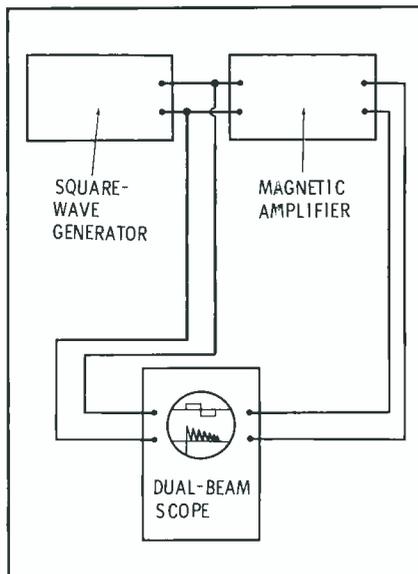


Fig. 5. This method uses a dual-beam scope and a square-wave generator.

I'd walk a mile...



for Centralab L & T Pad Attenuators



I'm not an ordinary camel—I'm a thinking man's camel—and I think highly of Centralab L & T Pad Attenuators.


These units work good—like an L & T Pad should—because of their small size, high wattage, and anti-backlash construction. Measuring less than 1 3/16" deep from the mounting surface, and with 1 3/32" diameter, they fit into any standard junction or switch box with room to spare.

In L & T Pads, though, it's what's in back that counts—and these Centralab units have exclusive "thermo-pass" insulation, which combines fast heat transfer with a high dielectric constant to achieve a conservative rating of 20 watts audio, 5 watts D.C., in a unit the size of conventional 2 watt controls.

Because of Centralab's anti-backlash construction, the "play" frequently found in dual controls is eliminated. The wiper contacts move in unison, so there's no alteration in frequency response due to variations in wiper position on the resistance tracks.

So hump down to your Centralab distributor and stock up on these L & T Pad attenuators. They satisfy!

B-6205S

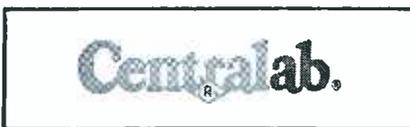


THE ELECTRONICS DIVISION OF GLOBE-UNION INC.
942K EAST KEEFE AVENUE, MILWAUKEE 1, WISCONSIN
In Canada: Centralab Canada Ltd., P.O. Box 400, Ajax, Ontario

ELECTRONIC SWITCHES • VARIABLE RESISTORS • CERAMIC CAPACITORS
PACKAGED ELECTRONIC CIRCUITS • ENGINEERED CERAMICS

TV TIPS FROM TRIAD

NO. 18 IN A SERIES

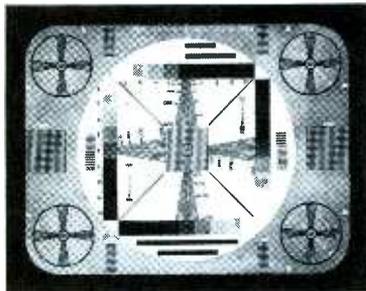

Joe stood frowning at the parade of Mr. 5 x 5 characters waddling across the screen. The raster was filled vertically, but the figures looked like they had been run over by a steam roller and only partially restored. "No width control on this one," he muttered.

Bill, the Senior PTM, glanced up from a rush job, "Hmm, looks like a new picture tube and yoke have been installed!"

"Correct," confirmed Joe. "Customer installed it himself. Said something about removing all the 'packing' and wants the set adjusted."

Bill squinted along the picture tube neck, then went over to the junk box. He pulled out a piece of impregnated paper and a small sheet of brass shim stock which he deftly wrapped around the neck and inserted into the yoke. The picture returned to normal. "Missing metal collar," he said. "The metallic sleeve absorbs some energy from the yoke, and width control results in proportion to insertion?"

"How come height is not affected?" queried Joe.

Bill explained, "The horizontal coils are always nearest the picture tube neck, so the metal collar absorbs more energy from the nearest coils. However, a word of caution. There's as much as 3500 peak-to-peak volts in the horizontal coils with only the varnish coating insulating it from the width collar. To reduce shock hazard, install an insulator between the yoke and the collar."

MORAL: Triad includes a special treated sleeve—the *Saf-T-Liner*—in yokes using this type of width control. Next time you go to your favorite Triad distributor, note the red and white boxes on his shelf. They contain highest-quality components engineered for the professional serviceman. For our helpful new catalog TV-62 and other literature, write Triad Distributor Division, 305 No. Briant St., Huntington, Indiana.

A DIVISION OF LITTON INDUSTRIES 

can be employed for a time constant longer than 10 cycles, but not long enough to be measured with a stop watch, by use of a slowly-driven calibrated sweep. Where the supply frequency of the amplifier is greater than 60 cps and a dual-beam oscilloscope is available, the sweep rate can be calibrated by applying the internal test voltage of the scope to the second channel while using a common control for the two channels.

Temperature Rise

Temperature rise is a very important factor in magnetic amplifier performance; however, the temperature rise measurement need not be too elaborate. Usually, the temperature is measured by mercury thermometers or thermocouples applied to the hottest accessible points on the reactor. A small amount of putty is used to shield the thermometer bulbs from the surrounding air, and care is taken to avoid external air currents, varying ambient temperature, or other factors which may introduce errors.

The preferred method of making a full-load temperature test is to maintain rated voltage, current, and frequency until the temperature becomes constant—readings are taken every half hour. The highest temperature reached at any time during the test is taken as the correct value.

For the totally-enclosed or electrically-insulated reactors, it is often preferable to determine the change in temperature by the rise of resistance method. In this case, the cold resistance of the windings is measured (usually after the reactor has been inoperative overnight) at uniform room temperature. The hot



Leader in indoor and outdoor antennas, intercoms and TV accessories, now introduces a complete line of wood wall baffles and speaker enclosures. Designed to give the best in sound reproduction and beautifully finished in Blonde, Mahogany and walnut, these units are amazingly low priced.



also available
with speakers pre-mounted



For complete details write to
RMS - Dep't. "B"
2016 BRONXDALE AVE.
BRONX 62, N.Y.

PRECISION TUNER SERVICE

P. O. BOX 272

1200 S. WALNUT ST.

BLOOMINGTON, IND.

EDISON 99653

7.50
V or U
COMBO PLUS
9.95 POSTAGE

6 MONTH WARRANTY



All Types T.V. Tuners Cleaned, Repaired and Aligned to Factory Specifications. Same day in shop service on most Tuners. Price Includes Minor Parts, Major Parts at Cost Price. We use Original Parts if possible. State Make Model and Enclose all Parts and Tubes. Pack Well and Insure.

ALSO HAVE LARGE STOCK OF EXCHANGE TUNERS, WRITE FOR TYPES AND PRICES.

resistance is at the highest value obtained during operation. Over moderate ranges of temperature, such as 100° C, the change in resistance is proportional to the temperature change. The temperature rise can therefore be calculated.

$$T = \frac{R_h - R_c}{234.5 - T_h}$$

where,

234.5 is the temperature for 100% conductivity in degrees C,

R_h is the hot resistance of the windings in ohms,

R_c is the cold resistance of the windings in ohms,

T_h is the winding temperature, when the cold resistance was measured in degrees C.

It is important that all tests be made under the same circuit conditions. For example, consider the case with a resistance in the control circuit to reduce the time response. Time-constant measurements of the circuit will yield an improved response, whereas the power gain will be reduced. Also, the control characteristics will be materially affected by a change in the circuit resistance.

Conclusion

Of course, there are other factors that determine the operation of magnetic amplifiers. However, the three characteristics covered above are those on which equipment design is usually based. Should these values change, the amplifier must necessarily deteriorate in efficiency. Any complete operating check of a unit should include tests in these areas.



NEWEST RCA SENIOR VOLTOHMYST®

NOW AVAILABLE AS A KIT FOR ONLY \$57.95*

NEW!
0.5-volt full-scale DC range for more accurate measurements of low voltages used in transistor circuits.

EXTRA!
Pre-assembled, factory tested probe (WG-299D) is included with every kit.

SAVE MONEY with this kit version of the RCA WV-98C, the newest improved model of the popular RCA SENIOR VOLTOHMYST. Even with its added features for extra versatility, this new kit still costs less than prior models.

This rugged precision instrument measures **AC voltages** (0.2 to 4200 volts peak-to-peak and 0.1 to 1500 volts rms); **DC voltages** (0.005 to 1500

volts DC); and **resistances** (0.2 ohms to 1000 megohms). Accurate to ± 3% full-scale on both AC and DC (± 5% on the 1.5 and 5-volt AC ranges). Less than 1% tracking error.

Scales are separately color-coded to differentiate peak-to-peak and rms voltage readings. Its big meter, 6½ inches wide—electronically protected against burnout—is one of the most readable ever designed into a VTVM.

RCA WV-98C

\$57.95*
KIT

\$79.50*
WIRED

For more information, ask your Authorized RCA Test Equipment Distributor.

*User Price (Optional)

RCA ELECTRON TUBE DIVISION, HARRISON, N. J.



THE MOST TRUSTED NAME IN ELECTRONICS

DEALERS HAVE
BEEN ASKING ABOUT
IT FOR YEARS...

NOW... you can
handle tape head
replacements
quickly... easily
... profitably!

MAKE BIG
PROFITS
WITH

Nortronics

For years dealers have asked for an accurate, simplified method for handling the replacement of worn tape heads. NORTRONICS, supplier of original equipment heads to the top manufacturers who make more than 75% of the nation's tape recorders, has introduced a tape head replacement program which solves this problem *quickly, easily, and profitably!*

NORTRONICS offers the only tape head replacement program which is complete in all respects... heads are matched electrically and mechanically for more than 250 models of popular recorders... exclusive "Quik-Kit" mounting hardware simplifies installation and vastly increases flexibility of inventory... electrical components included when required... detailed drawings and instructions make work go faster... easier... giving more profit per job!

You can get into this profitable market NOW! Minimum, fast-moving stock required... and profits are high for both distributor and dealer!

Extensive national consumer advertising and publicity campaign is now building demand. NORTRONICS provides you with point-of-sale and counter displays, window streamers, consumer booklets and sales ammunition. Powerful packaging is designed to boost "impulse" sales; helps to move replacement heads fast!

Ask your distributor today about this new NORTRONICS tape head replacement program or write: Thor Johnson, Distributor Sales Manager.

**MOST COMPLETE LINE
OF CONVERSION KITS**


In addition, NORTRONICS provides the most complete line of kits for converting monophonic and 2 track stereo to 4 track stereo. Boosts sales of accessory equipment for completing stereo systems. Complete Jobber and Dealer information available—write today!



"Music Sounds Best on Tape—
Tape Sounds Best on Nortronic Heads"


Nortronics

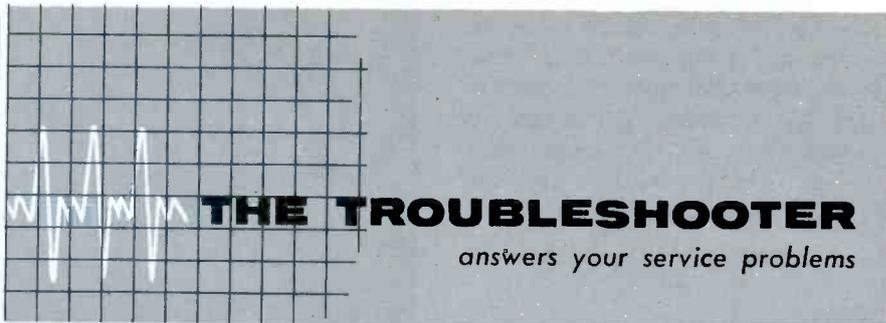8119 West 10th Ave., North
Minneapolis 27, Minnesota.



THE TROUBLESHOOTER

answers your service problems

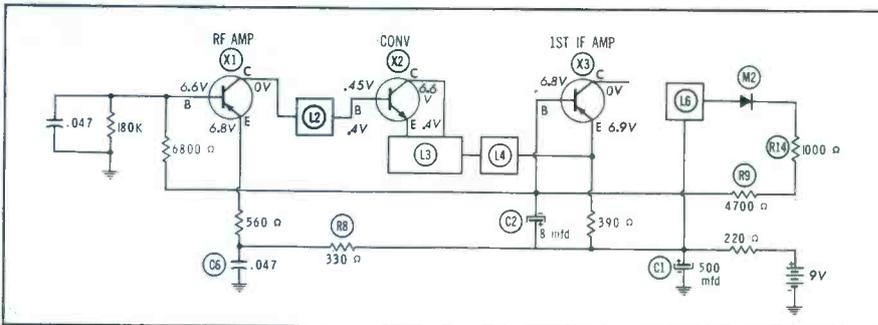

Transistor Stumper

I have been asked to repair a G-E Model P780A transistor radio (covered in PHOTOFACT Folder 485-10) which has me stumped. When it came in, it had static, much like an AC/DC set with a bad IF coil; since I started checking, it has gone completely dead. I can get a signal through the set from the collector of X1, but applying a signal to the base accomplishes nothing. This led me to change X1, but to no avail. By touching my finger to L3, I can get the set to pick up a few local stations, but I can't get X1 to amplify. Most of the voltages on the transistors read high. For example, on the bases of X1 and X3, the voltages

are considerably higher than normal; on their emitters the measurements are somewhat higher than usual, but not so much as on the bases. I hope you can get me on the right track.

BILL BANKS

Banks Radio & TV
Clarence, Iowa

The peculiar voltage symptoms you describe lead me to believe you have a short between the two power-supply lines in this receiver. You'll notice, in the simplified schematic, that M2, R9, and R14 form the decoupling resistances in this supply circuit—an unusual job for M2, I might add, since it is the detector diode. If M2 shorted, the circuit resistance would be lowered, as would be the case if


COLOR COUNTERMEASURES

Symptoms and service tips from actual shop experience

Chassis: RCA CTC7, -9, -10, and -11

Symptoms: Intermittent horizontal sweep.

Tip: Before checking voltages or waveforms in the horizontal circuits, press on the horizontal-oscillator printed board at different points, and see if horizontal sweep collapses. If it does, attach a clip lead to the chassis and touch the other end to each of the board-grounding points indicated in the photo. When one of these connections is defective, touching it with the clip lead will restore normal horizontal sweep. (This test must be made quickly; otherwise, lack of drive may damage the horizontal output tube.) These ground terminals often break contact with the chassis lugs to which they are soldered, thus causing the horizontal oscillator to cease functioning. In some cases, the open lug can be spotted visually when you apply pressure. While you're repairing one of these connections, it's a good idea to resolder the remaining ground lugs on this board.

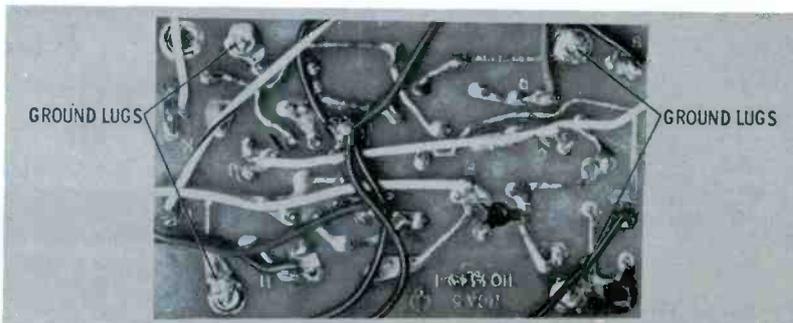

R9 or R14 decreased in value. The result would be a higher voltage on the transistor elements fed by this leg of the supply line—the bases of X1 and X3. Besides the parts already mentioned, C2 is connected between the two lines; if it became shorted, or even leaky, the same voltage symptoms would result. You'd better check its polarity, too, and make sure it hasn't been replaced and wired into the circuit backwards.

Another fault could cause the voltages to be upset in this manner: A short in either X1 or X3 could affect the voltages on the other of these two transistors, because each is connected between the two supply lines.

Lastly, it would be well to go over the printed-circuit board very carefully for any signs of leakage between conductors. This is a not-uncommon source of many troubles in electronic equipment using printed boards.

One caution, to prevent inadvertent damage to transistors: When using signal-injection troubleshooting procedures, be sure to use an isolating capacitor in series with the signal-source lead. Doing this will prevent an accidental ground connection from causing an overload which may burn out a transistor.

Restless Remote

I'm having trouble with the RC-50 wireless remote control used in a Philco Chassis 10L31 (PHOTOFACT Folder 479-1). After it has warmed up for about 10 minutes, it will take spells of tripping itself and changing channels. Sometimes it won't stop unless I turn off the TV.


L. D. PAYNE JR.

Port Lavaca, Texas

First, substitute for the 6BJ8 channel-selector relay tube, which may be developing gas or leakage after warm-up.

The grid voltage of this tube should be -22 volts when no signal is being applied. If it is less negative than this while the trouble is present, and a new tube doesn't help, try replacing C69; also check the bias-rectifier circuit (negative 20-volt source).

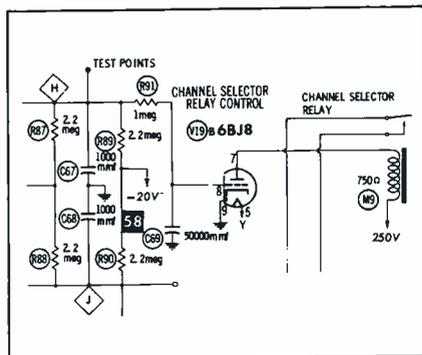There's a chance the trouble may be ahead of the discriminator. With the disturbance present, pull the 39-kc amplifier tubes one by one, starting at the head end. If the channel-changing stops, replace the tube you've just pulled. If you can restore normal operation only by disconnecting the input microphone, look for trouble outside the set.



Tarzian 400 and 600 volt F and H series units are available in handy Ten-Paks, in Doubler Replacement Kits, and in bulk; M150 and M500 units are available in Conversion Kits and in bulk. Nine standard tube replacement rectifiers replace over 95% of all popular

vacuum tube rectifiers; S5347 replaces 6BW4 or 12BW4 in Citizen's Band radios; your 50 to 500 ma requirements are covered by four "condensed stack" selenium rectifiers, which Sarkes Tarzian has made more efficient—and smaller—than before.

Sarkes Tarzian

...the preferred* silicon rectifiers that mean fewer call-backs

*by service technicians—again in '62

■ Tarzian silicon rectifier dependability virtually eliminates call-backs that waste your time and profits. Units are available immediately from distributors throughout the country... in the shapes, sizes, and specifications you need to do your work quickly and easily.

Tarzian's industry-wide reputation for high quality at a pace-setting low price is a basic reason why technicians like yourself prefer Sarkes Tarzian rectifiers by nearly as many votes as the next two brands combined.

That statement is based on the results of 1961 and 1962 mailings by Brand Name Survey, an independent research organization, to 23,000 service technicians in all major market areas of the United States, covering 36 states. You're in good company—and lots of it—when you make Tarzian rectifiers your first choice for replacement applications.

Free Tarzian "Distributor Line" Catalog is available now as your guide to replacement rectifier quality. Ask your nearest Tarzian distributor for your copy.



SARKES TARZIAN, Inc.

World's Leading Manufacturers of TV and FM Tuners • Closed Circuit TV Systems • Broadcast Equipment • Air Trimmers • FM Radios • Magnetic Recording Tape • Semiconductor Devices

SEMICONDUCTOR DIVISION • BLOOMINGTON, INDIANA
In Canada: 700 Weston Rd., Toronto 9 • Export: Ad Auriema, Inc., New York

SIMPLE OR ELABORATE

RCA has the INTERCOM SYSTEMS for virtually every requirement

Intercom systems—both sales and installation—are big business today. They can increase your business by getting you into entirely new markets. Today intercoms are more profitable than ever, because now you can offer a full range of systems from RCA—the name that enjoys the highest customer acceptance in electronics.

"SWITCHBOARD" INTERCOM SYSTEM. Master with up to 4 remote units. Master can be set up for remote-to-remote conversation, or speak with any one or all remote units.

"MASTERCOM" INTERCOM SYSTEM. Up to 6 units. With an all-master system, any unit can call any other unit direct; system permits 3 separate private conversations at once or conference between all 6.

WIRELESS INTERCOM SYSTEM. No connecting wires, no installation. Just plug unit into any 110-120 volt wall socket and talk with all other units on the same wiring system.

TRANSISTORIZED INTERCOM SYSTEM. Battery-operated (uses penlite cells), can be set up anywhere: parking lots, storerooms, etc.

"PARTYLINER" INTERCOM SYSTEM. Basic 2-station system. Additional remotes can be added. Very low cost. Ideal for paging; master calls all remote units at once. Any remote unit can call master.

For your convenience, all these systems are now available through your Authorized RCA Intercom Distributor. See him as soon as you can.

Find out how you can begin capitalizing on this new profit-making opportunity.

RCA Electron Tube Division, Harrison, N. J.



The Most Trusted Name in Electronics

Special Products Department
RCA ELECTRON TUBE DIVISION
Harrison, N. J.

Please send detailed information on the RCA INTERCOM SYSTEMS checked below:


- All systems Switchboard System
 Mastercom System Wireless System
 Transistorized System Partyline System

Name _____ Title _____

Company _____

Address _____

City _____ Zone _____ State _____

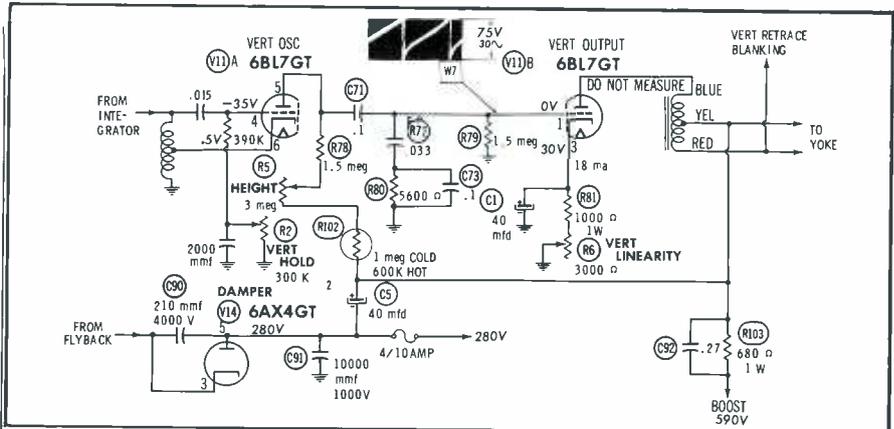

Elusive Height

I have a G-E Model 21C1552 receiver (covered in PHOTOFAC Folder 391-1) on the bench. The set performs fine for about 15 minutes, at which time the raster shrinks, pulling up from the bottom and developing nonlinearity. I've changed the output transformer, C5, C90, C91, C92, R102 and R103. The boost voltage is normal. I tried two different blocking-oscillator transformers; both of them make the lack of height worse. I have a 150-volt peak-to-peak drive signal at the grid of the output stage, but still not enough height. Can you help me find where the height has gone?

ROBERT RATELON

Westernport, Md.

From the fact that you mention finding an abnormally strong drive signal (150 volts) at the output grid, I'd surmise the output stage isn't doing its job. While you can't measure the voltage on the plate of the output tube, you can check it almost as effectively by touching the voltmeter probe to the yellow lead of the output transformer. Did you try a new capacitor in place of C1D, and measure the value of R81? Also, there's the possibility that the controls (R2 and R6) are changing value.

One thing which bothers me is the fact that the trouble affects the height more than the linearity. This effect hints at trouble in the oscillator stage—notwithstanding the apparently high drive signal. R102 is a special unit, and you should be sure to use the correct replacement. R78 and C71 will have a direct bearing on the height of the raster, as will ALL the components in the waveshaping network—R80, C72, and C73. Lastly, be sure R79 hasn't developed such a high resistance

that it is upsetting the bias on the output stage.

Pulling and Weaving


A Philco Model 52T2110 (covered in PHOTOFAC Folder 132-10) has come into my shop with what appears to be AGC or video trouble. After about 20 minutes, the picture begins to pull; it weaves all over the screen, but is worst at the top. I have eliminated the possibility of tube or filter trouble, and have checked the AGC circuit thoroughly.

A. DAMRON

Damron's Radio & TV
Pikeville, Ky.

You've a difficult trouble to pinpoint, because of possible interaction between various sections; this difficulty is common with AGC faults. However, in this particular model, the symptom you describe is often caused by a defective bypass capacitor (C51, C52, C53, or C54) or by a leaky sync-coupling capacitor C78. Besides these possibilities, the AGC filters—C37, C41, and C45—commonly cause weaving and bending such as you describe. If all of these are okay, check the components in the -17 volt supply—C5, R123, and R133.

The best method of troubleshooting this symptom would be to first clamp the AGC line with a bias supply having a low internal resistance. If the trouble clears up, you should look for a fault in the AGC system. Otherwise, use your scope to check all the way from the video detector through the sync separator circuits for any distortion of the horizontal sync pulses. Somewhere, you'll probably find that some of the horizontal pulses are being clipped or distorted. This should clue you right onto the point of trouble.

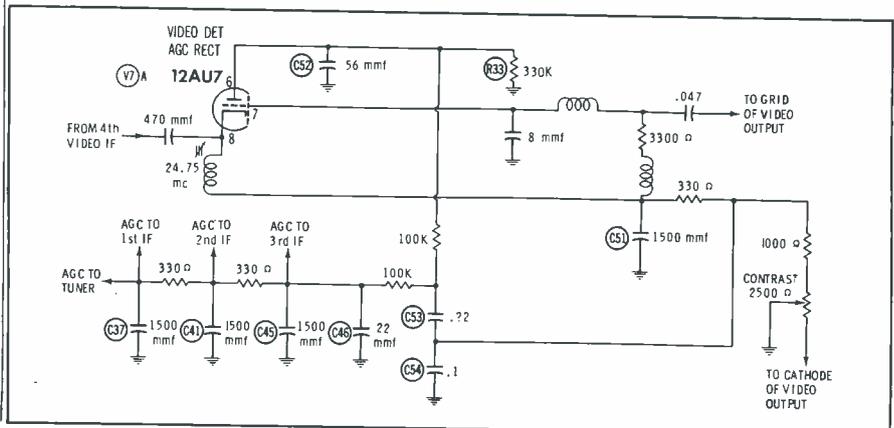

Solenoid Solution

I have a Bell & Howell tape recorder Model 300B, which has developed a loud hum. The volume control varies the hum level in the speaker. I've tried to locate the cause by several methods, with no luck. Also, when the PLAY or RECORD button is depressed, the solenoid (which I assume is DC-operated) fails to energize, and I can detect no voltage at the solenoid terminal or at the output of rectifier M1. Can you answer some questions for me? They are: What is the correct voltage across the solenoid, and how should I measure it? What is the DC resistance of the solenoid?


W. L. NELSON

Colton, Calif.

The hum problem you mentioned sounds like a poor ground. The bad connection is probably in the preamp section, since you can vary the hum level with the volume control. Have you carefully checked the preamplifier tube for cathode-to-heater leakage? Even a small amount can cause noticeable hum in the preamp stage. Check the leads and shields to the recording and playback head(s), check the head-lead disconnect socket, and check—by shorting across the pins—to be sure the head itself isn't picking up the hum.

I assume the solenoid you refer to is the capstan/pressure-roller solenoid; it is DC-operated, with a voltage (about 130 volts DC) developed by rectifier M1. To troubleshoot the absence of actuating voltage at the solenoid, check for AC input to the rectifier, and then trace the DC output voltage through resistor R1 and the contacts of switch M9 (in PLAY position) to the solenoid receptacle; from here, the voltage should go directly to one terminal of the solenoid itself. The ground, or return, side of this DC supply circuit is at the on-off switch, since the AC input for this supply circuit is taken off prior to the power transformer. Be very sure rectifier M1 and filter capacitor C1B are both connected with the polarity shown in the schematic.

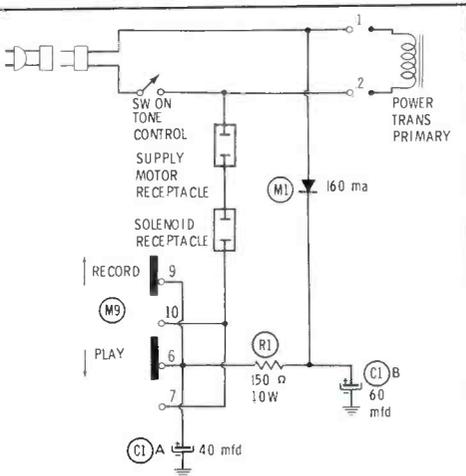To answer your other question: The DC resistance varies from coil to coil, but generally will measure only a few hundred ohms. ▲



SAVE VALUABLE MONEY-MAKING TIME with *Mercury* TEST INSTRUMENTS...

Model 500 COMPONENT SUBSTITUTOR

Now you can have all the substitutes for electronic components you want and need in your every day work in one compact unit. You'll find the 500 more convenient to take on calls . . . so much easier and faster to work with in the shop.

Handsome hammertone steel case



A complete range of components at your fingertips for fast substitution

SAVE MONEY! No need to buy many individual component substitutes . . . The Model 500 does all the jobs.

Substitutes for more components than any other instrument of its type!

\$3495 Net Size: 5 7/8" x 7 3/4" x 3 1/2"

- Substitutes for 20 values of resistors from 33 ohms to 10 megohms
- Substitutes for 10 values of condensers from .001 mfd. to .5 mfd.
- Substitutes for 10 values of electrolytics from 4 mfd. to 330 mfd.
- Substitutes for diodes • Substitutes for power rectifiers up to 500 ma.
- Substitutes for power resistors • Substitutes for bias voltages

Model 800 CRT TESTER-REACTIVATOR

- ✓ Also accommodates the new 8-pin, 7-pin and 14-pin base picture tubes
- ✓ Also provides the newer 2.35 and 8.4 filament voltages
- ✓ Tests and repairs the red, green and blue sections of color tubes separately

\$4995 Net

Sturdy case—leatherette finish



The Model 800 takes the guesswork out of the check, repair and reactivation of any black and white or color picture tube in the set or in the carton. It is a terrific money-maker . . . makes picture tube sales easier . . . builds customer confidence and goodwill.

... for ALL BLACK and WHITE and ALL COLOR picture tubes

CHECKS

- Emission • Inter-element leakage • Shorts • Opens • Life expectancy test estimates the remaining life of picture tube

REPAIRS

- Inter-element shorts • Open elements

REACTIVATES

- Low emission tubes to restore brightness • Meter indicates reactivation for proper control

Size: 11 1/8" x 9 1/2" x 4 1/2"

Model 300-A COMBINATION TESTER



Sturdy case—leatherette finish

\$10975 Net

The Model 300-A represents a new high in convenience for you . . . three instruments essential in your everyday work, combined into one compact, professional unit—available at an unbelievably low price.

Size: 17 1/2" x 13 1/8" x 4 1/2"

3 INSTRUMENTS IN 1

- 1 Tube Tester
- 2 CRT Tester-Reactivator
- 3 20,000 ohms per volt VOM

A complete portable service shop at your side wherever you go

AS A TUBE TESTER . . . will check emission, inter-element leakage and gas content of all tubes including Novars, Nuvisitors, Compactrons and the new 10-pin types.

AS A CRT TESTER-REACTIVATOR . . . will test, repair and reactivate all black and white and all color picture tubes.

AS A VOM . . . (20,000 ohms/volt)
DC VOLTAGE RANGES: 0 to 7500 volts
AC VOLTAGE RANGES: 0 to 1500 volts
OHMS RANGES: 0 to 10 megohms
DC CURRENT RANGES: 0 to 15 amps.
CAPACITY RANGES: .001 mfd. to 180 mfd.


See your electronics parts distributor or write for complete Mercury catalog

Mercury ELECTRONICS CORPORATION
manufacturers of quality electronic products

111 Roosevelt Avenue, Mineola, New York

IN CANADA: Wm. Cohen, Ltd., 8900 Park Ave., Montreal

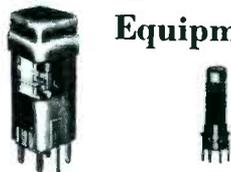**Exact Replacements
for Original T.V.
Equipment**



Cat. No.	Use	O.E.M. Part No.
----------	-----	-----------------

Admiral

1471-A	Sound Take-Off	72B185-2
1472-A	Sound Take-Off	72C132-19
6332	Horiz. Osc.	94C17-4

Crosley

7101	2nd Sound I.F.	157856-1
------	----------------	----------

Dumont

7103-DE	Discriminator	20004441
7104-DE	Sound I.F.	20004511

Emerson

6339-E	Width	708275
6340-E	Horiz. Osc.	716102
7112-E	4.5 Mc. Disc.	708276

General Electric and Hotpoint

6206-PC	TV Ratio Det.	RTD-026 (WT56X38)
6207-PC	TV Ratio Det.	RTD-025 (WT56X37)
6208-PC	TV Ratio Det.	RTD-020
6209-G1	TV Ratio Det.	RTD-024 (WT 56X36)
6334-G	Horiz. Phase	RLI-365
6335-G	Horiz. Osc.	WT36X402

Hallcrafters

1482 IFT	Sound I.F. and Trap	51B1996
7101	2nd Sound I.F.	51A1859

Muntz

7111-M	4.5 Mc. Disc.	10-0076
--------	---------------	---------

Phileo

6209-P1	TV Disc.	32-4721
6209-P2	TV Disc.	32-4689-1, 2
6209-P3	TV Disc.	32-4735-1, 2
7102-P	4.5 Mc. I.F. and Trap	32-4688-10

R.C.A.

1483 IF	Sound I.F.	76437
1484 RD	Sound Ratio Detector	102692
1485 RD	Sound Ratio Detector	102644
1486 RD	Sound Ratio Detector	102253
1487 RD	Sound Ratio Detector	100364
1488 RD	Sound Ratio Detector	79141
1489 RD	Sound Ratio Detector	101219
6333	Horiz. Osc.	103103
6336-R	Horiz. Osc. and Sync.	107284

Westinghouse

6204-W3	TV I.F.	V12128-1, 2, 3
---------	---------	----------------

Available through your local distributor

J. W. MILLER CO.



5917 S. Main St.
Los Angeles 3, Calif.



Closed Circuit TV

(Continued from page 31)

agement, and occasionally through line or distribution amplifiers.

Some CCTV cameras include a modulator and VHF oscillator. The modulated RF output signal can be fed to a conventional TV receiver or into a VHF distribution system. The RF oscillator in some cameras is adjustable to TV channels 2 through 6; in others, it is crystal-controlled at any one of the TV-channel frequencies.

Typically, the direct video signal is fed to video monitors at a level of 1 to 1.5 volts peak to peak, through 72-ohm coaxial cable. In RF cameras, the signal output is usually 50,000 to 100,000 microvolts. In a few camera types, video and RF outputs are available simultaneously.

The sweep and sync signals are generated by a master oscillator operating at 31,500 cps, which is phase-locked to the 60-cps AC line. Horizontal sweep and blanking signals at 15,750 cps are derived by dividing the master-oscillator frequency by two. The vertical sweep and blanking signals (at 60 cps) are developed by dividing the master oscillator signal by 525 through a chain of frequency dividers. The resulting 60-cps signal is compared with the AC line frequency in a phase detector which feeds an AFC correction voltage to the master oscillator.


Other Circuits

The vidicon tube is protected from burn damage by a circuit which cuts off the grid in the event of either horizontal or vertical deflection failure.

In some CCTV systems, the sweep and sync circuits are contained in the camera. In others, the camera housing contains only the vidicon tube and the video amplifiers; the sweep and sync signals, as well as supply voltages, are fed to the camera through a multiconductor cable from a remote unit.

While many cameras employ tubes, there are several transistorized cameras on the market, some of which can be operated from a 12-volt DC source as well as from AC.

Some cameras are equipped with

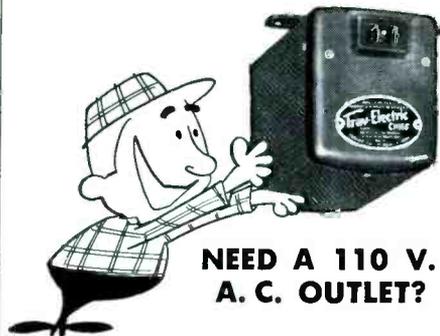

**NEED A 110 V.
A. C. OUTLET?**

**IN CAR, BOAT OR TRUCK,
YOU HAVE IT WITH A**

**terado POWER
INVERTER**

Actually gives you 110 volt, 60 cycle A.C. from your 6 or 12 volt D.C. battery! Plug inverter into cigarette lighter, and operate lights, electric shavers, record players, electric tools, portable TV, radios, testing equipment, etc.

Models from 15 to 300 watts, priced as low as **\$12.95** LIST

See Your Electronics Parts Jobber, or Write:

terado COMPANY
1073 RAYMOND AVE.
ST. PAUL 8, MINN.

In Canada, ATLAS RADIO CORP. LTD. — Toronto, Ont.

**DeSod System
PRINTED CIRCUIT
DESOLDERING
TOOLS**



COMPACTRON

Socket change done in one minute.

Tools available for most Multi-contact components of printed boards.

DeSod tools fit your present solder gun.

Available from your distributor.

EVERSOLE INDUSTRIES

2121 W. State St.
Fremont, Ohio



CCTV operator can observe any operation he desires, from remote location.

automatic light compensators which duplicate the performance of modern film cameras. Various types of lenses are available. Remote controls for lenses, and for the pan and tilt functions, are often employed.

A CCTV video monitor is similar to a TV set except for the omission of the RF, IF, and detector circuits. Generally, the monitor is designed for higher resolution and stability than a conventional TV set. When a professional TV monitor is used, picture resolution of 600 to 650 lines is possible with some cameras.

But, when a conventional TV receiver is used, with a VHF signal fed in, resolution is often limited to as little as 350 lines by the bandwidth of the RF-IF circuits.

Systems

The camera and monitor may be separated by any distance over which a suitable transmission path can be provided. The video transmission line must be capable of passing signals from near DC to several megacycles. Audio signals, if they are used, are generally run through a separate line. In a few systems, however, the audio signal from a microphone is fed through a preamplifier to a modulator unit and mixed with the video signal from the camera. The audio-video modulator unit produces an RF signal similar to that transmitted by a TV broadcasting station. The composite signal can then be applied to the antenna terminals of standard TV sets.

Microwave systems are being used, and will be used even more widely in the future, for CCTV transmission between buildings. These microwave stations must

operate in the 12,000-mc Business Radio Band—or in the proposed 17,000-mc Citizens band — if the system is licensed to commercial firms. Schools, whose microwave systems must also share these bands, may later be eligible to operate stations in the 2,000-mc ETV band.

In some systems, only the TV signal is transmitted via microwave; the audio channel (if used at all) is transmitted over a leased phone line. However, the audio may be transmitted along with the video, as illustrated in the typical microwave system shown in Fig. 3.

In such a system, the microphone signal is fed to a subcarrier transmitter—sometimes called the audio duplexer. The audio signal frequency-modulates a subcarrier at around 6 or 8 mc. The resulting FM signal is combined with the video information, and both are fed to the stages which modulate the microwave klystron.

At the microwave receiver, the FM subcarrier is separated from the video signal, and demodulated in a special FM-subcarrier receiver stage. The video signal is handled the same as if the sound were separate.

SOON!
**From the Antenna Research
 Laboratory of a Leading University
 a mathematical dream becomes
 an engineering reality**

LOG-PERIODIC

$$LPV \frac{L_{(n+1)}}{L_n} = \tau$$

**The space age antenna of tomorrow
 —and only JFD has it**

U.S. PATENT NUMBERS: 2,958,081—2,985,879—3,011,168 OTHER PATENTS PENDING

CHOICE OF OVER 250,000 SERVICEMEN



8 oz. ECONOMY SIZE... \$1.98
DEALER NET
FREE 12" SPRAY AID AND PREMIUM
3 oz. "CADDY SIZE"..... 98¢
DEALER NET
FREE SPRAY AID

CHEMTRONICS inc.
870 East 52nd Street, Brooklyn 3, New York
in Canada Contact: Active Radio & TV Distributors
431 King Street W. Toronto 2B, Canada

Opportunities

Most CCTV systems are sold by independent distributors who generally serve an extremely large area, making the service problem difficult. Many of these distributors would welcome the assistance of local service-shop owners who could take over installing and servicing CCTV systems located at distances too great for convenient handling by the distributor.

It is not likely that many industries, banks, or other users will employ electronics technicians on a full-time basis; the cost would be too great. Furthermore, it will seldom be practical to train plant electricians to handle CCTV maintenance.

Manufacturers and distributors of CCTV equipment can sometimes furnish maintenance service on a direct basis, but this is costly. The customer must be charged enough to cover direct labor costs and overhead, plus travel expenses. Generally, labor is charged for on a portal-to-portal basis. It would be much cheaper to engage a local service technician on an "as-required" basis, even at rates of \$10 per hour or more, if a competent man were available.

Tips On Servicing

The most essential test instruments for servicing CCTV equipment are an oscilloscope and a VTVM. Most service problems result from tube defects and aging components. Tubes with excessive leakage (which may pass muster on a simple tube tester) are a common cause of instability, especially in CCTV cameras. Trying new tubes or using a grid-leakage type of tube



Many new CCTV techniques are being devised—such as this portable unit.

tester is a quick way to determine if tubes are at fault, before checking other components.

Cable connections are another frequent cause of trouble. Connectors must be secure and free of faulty contacts to avoid hum, noise pickup, and erratic operation. Often, the trouble is caused by improper installation of cable connectors. Also, don't forget that coaxial cable can develop signal leakage from moisture absorption.

It is easy to get started in CCTV servicing. One way to become familiar with CCTV equipment is by studying the technical information provided by manufacturers. When you write to equipment manufacturers, you can also state your availability and describe your qualifications and facilities.

The CCTV business is still in its infancy. It is getting a real boost through federal subsidies for ETV, and, as business firms begin to grasp its money-saving values, CCTV will become one of the more important segments of the electronics industry. Now is the time to get ready to share in this rapidly expanding business. ▲

DON'T REPLACE CRYSTALLIZED RUBBER
PHONOGRAPH DRIVE WHEELS UNNECESSARILY

brush on **NEW FONO-MAGIC***

eliminate slipping...dragging
SAVES DRIVE WHEEL INVENTORY COSTS TOO!



*FONO-MAGIC is a NEW compound of special rubber and carbide particles. When FONOMAGIC is brushed on metal drive surfaces, it forms a coat of live, pliable non-slipping rubber .00065 inches thick. Carbide particles imbedded in the rubber coating will scratch slipping rubber idler wheels, exposing live rubber and prolonging the life of the idler wheel. Just one bottle of FONOMAGIC is equivalent to the replacement of 100 drive wheels. Only \$1.95 dealer net. Sold at Better Jobbers everywhere.

manufactured by R-COLUMBIA PRODUCTS CO., INC. Highland Park, Illinois

Weak Washed-Out Pix

(Continued from page 29)

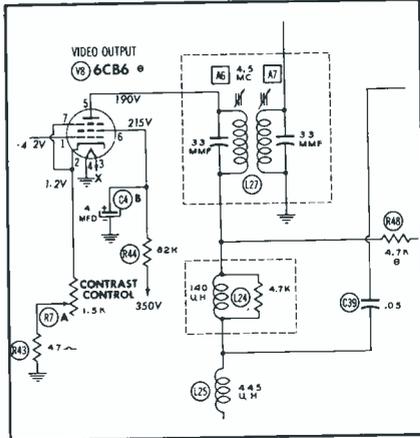


Fig. 4. Open C4B causes degeneration in video amplifier, lowering contrast.

control turned all the way up, forget about the picture tube—you almost certainly have video-amplifier trouble. This is a logical time to make DC voltage and resistance tests in the circuitry between the detector and the CRT.

In some situations, an extreme voltage error will lead you straight to the trouble. For instance, if the screen voltage of V4A in Fig. 2 measured 50% of its normal value, the appropriate action would be to check R31 for an increase in resistance, and C18 for leakage.

Sometimes, though, low screen or plate voltages are merely reflected symptoms. Consider the two-stage amplifier illustrated in Fig. 3; in case video-coupling capacitor C51 should become leaky, the control-grid voltage of V7 would be driven positive, and the plate voltage would fall as a result of the stepped-up DC plate current. The cathode voltage would also rise because of the abnormal flow of plate and screen current. However, among these three voltage errors, the one which actually holds the key to the problem is the grid voltage.

Worse leakage in the coupling capacitor would have a different re-

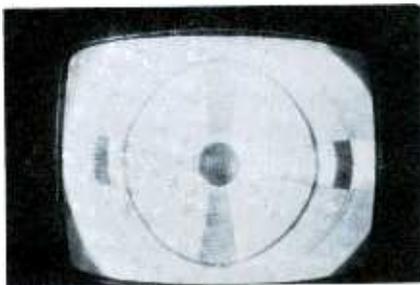


Fig. 5. Nearly open coupling capacitor causes this type of picture smearing.

flected effect on the plate voltage. If the grid voltage were positive enough to produce heavy grid-current flow, the grid would steal electrons from the stream intended for the screen and plate; then the voltages on the latter elements would be at a normal or higher level. Of course, the tube would run very hot and would be damaged.

There are occasional situations in which all DC voltages and resistances are within tolerance, but the picture cannot be brought up to full contrast. Excessive negative feedback is a suspect in this situation.

How can this occur? Refer to Fig. 4, which shows a circuit arrangement with an 82K-ohm screen resistor (R44) normally bypassed to ground by a 4-mfd electrolytic capacitor (C4B). When C4B loses a substantial amount of its capacitance, or becomes open, a signal is induced on the screen grid. The resulting degeneration considerably cuts down the picture contrast.

Another instance of poor contrast, with DC voltages and resistance values normal, is found when a coupling capacitor is nearly open. For example, if C51 in Fig. 3 loses

NOTICE

While they last, BACK ISSUES OF PF REPORTER are yours for just 50c. Send in your order today.

1956	1958	1960
all except Jan-Oct	all except Jan, Feb, Mar, Apr, and June	all except Jan and May
1957	1959	1961
all except Feb, Mar, Aug, Oct, Sept, Nov, and Dec	all except Sept, Nov and Dec	all except Apr
		1962
		all except March

Special!! Order 6 issues or more and save 10c a copy.

	JAN.	FEB.	MAR.	APR.	MAY	JUNE	JULY	AUG.	SEPT.	OCT.	NOV.	DEC.
1956												
1957												
1958												
1959												
1960												
1961												
1962												

Enclosed please find \$_____ for back issues checked above.

Mail to: Circulation Dept., PF REPORTER
4300 W. 62nd St., Indianapolis 6, Ind.

NAME _____

STREET _____

CITY _____ ZONE _____ STATE _____

1062



TYPE L . . . for long, long years of service life ask your distributor for PLANET LYTICAPS, the universal replacement type electrolytic capacitor. Available in a wide range of capacities in voltages from three to five hundred. The Planet listing carries many of the newer values required for adequate servicing of both TV and industrial electronic equipment. Planet LYTICAPS are called out on the blueprints of many blue chip equipment manufacturers because their engineers found that LYTICAPS are truly "Engineered for Quality".

Write today for complete information.

PLANET SALES CORPORATION
225 Belleville Avenue Bloomfield, New Jersey

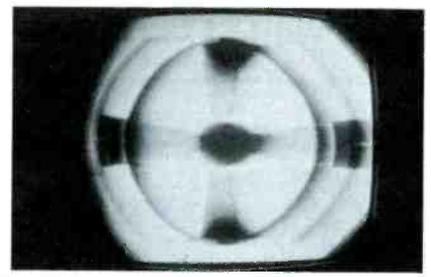


Fig. 6. Smear and loss of high frequencies, due to a defective peaking coil.

almost all its capacitance, it passes a greatly attenuated video signal containing only the higher frequencies. The lowest frequencies among those which get through are shifted in phase, and the result is a smeared picture in addition to low contrast (Fig. 5). In this situation, the picture symptoms are more distinctive than a simple "washed-out" appearance, and you can eliminate many circuit areas from suspicion at the outset.

High-Frequency Attenuation

A different type of smearing appears when a peaking coil such as L25 in Fig. 3 is open. In this case, the circuit is completed by the 12K damping resistor R53. The DC plate voltage of the video-output tube is reduced enough to cast suspicion on the open peaking coil, and even more conclusive evidence is obtained from symptom analysis. The picture (Fig. 6) is smeared and has low contrast, but differs from Fig. 5 in that high video frequencies have been eliminated. This effect results from the low-pass filter action of R53 and the shunt capacitance of the picture-tube input circuit.

Will sync lock be affected in these trouble situations? The answer depends upon where the sync-takeoff point is located in the signal channel. Properly evaluated, good sync lock (or the lack of it) can often help considerably in localizing the trouble area. For example, if the sync takeoff is between the first and second video-amplifier stages (as in Fig. 3), and sync lock is tight but the picture contrast is poor, the defect will probably be found in the second stage. The same general logic applies to keyed AGC systems—the AGC action will not be affected if the keying-tube input signal is taken off prior to the defective video circuit. Sound reproduction is a less clear-cut clue, because



Winegard TV-FM COUPLER



COUPLES ANTENNAS OR SETS

Couples TV and FM antennas OR couples TV-FM sets to an all-channel antenna. Exact 300-ohm match. No loss . . . no interaction. Can be mounted indoors or out. 300-ohm Model CA-FM, \$4.50 list. Also 75-ohm model. Write for Fact-Finder #231.

WINEGARD COMPANY
3009-10 Kirkwood Ave., Burlington, Iowa



Miniature
**I. F. TRANSFORMERS
OSCILLATOR COILS
and LOOP ANTENNAS**
for Transistor Sets

**GENERAL REPLACEMENTS FOR
IMPORTED and DOMESTIC SETS**

Size 3/8" x 3/8"		
PART NO.	OPERATION	
455-A1	INPUT	
455-A2	INTERSTAGE	
455-A3	OUTPUT	
455-OA	OSCILLATOR	
Size 1/4" x 1/4"		
PART NO.	OPERATION	
455-B1	INPUT	
455-B2	INTERSTAGE	
455-B3	OUTPUT	
455-OB	OSCILLATOR	

Packaged in Plastic See-Thru box in display carton with instruction.

MODEL LA-14 FOR USE WITH 148 MMFD. TUNING CONDENSER SIZE 1 1/16 x 1/16		MODEL LA-36 FOR USE WITH 365 MMFD. TUNING CONDENSER — SIZE 2-13/16 x 11/16
Packaged in plastic bag on display card		

Vidair ELECTRONICS MFG. CORP.
365 BABYLON TPKE. — ROOSEVELT, N. Y.

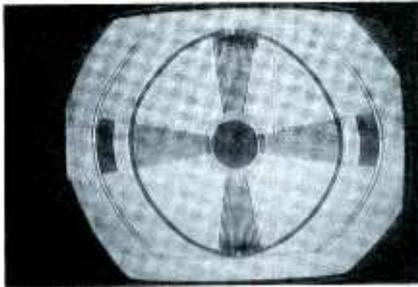


Fig. 7. Replacement of peaking coil with wrong value may cause ringing.

the sound often seems to remain about normal in spite of considerable attenuation.

Peaking-Coil Replacement


Beginners sometimes make the mistake of replacing a defective peaking coil with just any coil which happens to be handy. This practice can lead to ringing, as seen in Fig. 7, or to poor high-frequency response. Hence, always check the receiver service data for recommended values of peaking coils.

Summary

Complaints of poor picture contrast and associated symptoms can be run down in a short time by following the procedure just outlined, using proper test equipment. Here are some general rules:

1. Identify the receiver, and consult the service information so you will know what can reasonably be expected from the chassis.
2. Check the video-detector output to find out whether the video amplifier is receiving normal drive from the front-end circuits.
3. Restore a normal detector output, if necessary, before tackling the video amplifier.
4. Check with a calibrated scope to confirm the suspicion that the CRT is being fed insufficient video.
5. If the gain of the video amplifier is low, judging from a comparison of its input and output signals, make DC voltage and resistance measurements in this circuit.
6. If results of DC tests are inconclusive, use the scope to pinpoint any open coupling or bypass capacitors.
7. Replace any defective parts only with types recommended in service data. ▲

Winegard ULTRA LOW-LOSS* 2-SET COUPLER

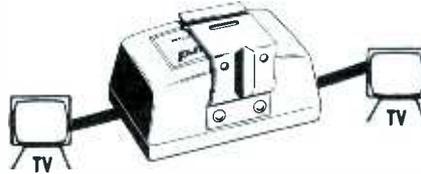

*20% LESS LOSS THAN
ANY OTHER COUPLER

Delivers equal signal to each of two TV sets. Ultra low loss. Exact 300-ohm impedance match. No smear. No interaction between sets. Highest quality. Model LS-23, \$3.75 list. Write for Fact-Finder #219.


WINEGARD COMPANY
3009-10 Kirkwood Ave., Burlington, Iowa

"Eliminates Soldering"

PERFECT *Audio*

"PIN-PLUG" CRIMPER

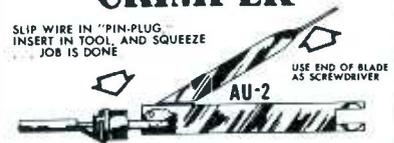SLIP WIRE IN "PIN-PLUG"
INSERT IN TOOL AND SQUEEZE
JOB IS DONE



U. S. Pat. 2,878,698

Canadian Pat. 592,702

Useful in making hi-fi, audio and sound, radio, phone, and TV equipment connections.

only **\$1.25**

C-rings 1c each

Get the tool that makes solid electrical pin-plug connections without soldering or destroying pin form. Use one end for pin crimping, the other to push on C-ring clamp for braided-shield ground connection. Nothing like it anywhere.

3 models: PT-1 for 3/32" pin diameter; AU-2 for 1/8" pin diameter and installing C rings; LC-3 for 5/32" pin diameter.


Available at your parts distributor.

Another fine product from:

BERNS

Mfg. Co.
9853 Chalmers,
Detroit 13, Mich

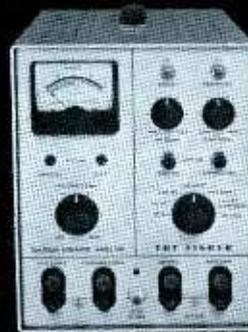Who says Multiplex servicing is complex?
All you need besides your 'scope
is this!



The Fisher Model 300 all-in-one Multiplex Generator with built-in FM Signal Generator.

Only Fisher could have designed this unique instrument — because only Fisher has the engineering depth in FM Stereo Multiplex tuners and receivers to create the ideal test equipment for servicing them. The future of high-fidelity radio unquestionably belongs to FM Stereo and the Model 300 is the instrument for the service technician in search of new business. It is compact, fully portable and completely self-contained. It has its own built-in FM signal generator. In addition to a composite MPX signal, it also generates low-distortion, stable audio signals. Thus it requires no companion instrument other than an oscilloscope for professional alignment of Multiplex equipment. Best of all, **THE FISHER** it costs only \$495.

USE THIS COUPON FOR DETAILED INFORMATION

FISHER RADIO CORPORATION
21-24 44th Drive, Long Island City 1, N. Y.

Please send me complete data and technical specifications on the Fisher Model 300.

Name _____

Address _____

City _____ Zone _____ State _____

09917

Resistance Measurements

(Continued from page 22)

22-meg reading!

Connecting his meter across pins 2 and 3 on the printed unit itself, he got the same indication, thus pinpointing the trouble within this unit. Referring again to Fig. 2, notice that printed foil conductors serve as the wiring paths for the individual parts. A close check of the unit in this case showed the copper foil was not soldered, as it is in the photo; neither were the small clips which retain the various components on

the board. The technician soon located a poor contact between the foil and the clip which held one end of the 1-meg resistor; this accounted for the high-resistance path and the intermittent trouble in the receiver.

Pressing on the clip, or moving the printed unit, established good contact and restored the correct resistance reading. (Take a tip from this experience: Don't move these combination units if you can help it, especially when you have an intermittent fault to deal with. You might temporarily cure it, and days

might pass before it would show up again.)

The technician scraped the copper foil and soldered the poor contact; as a preventive measure, he also cleaned and soldered all the other contacts on this unit. This finally solved his problem. If he had only checked the resistance across these pressure contacts before taking time to replace the resistor, he could have cured the trouble much more quickly.

Multipath Measurements

Some circuit points have several parallel DC paths back to the reference point from which resistance is to be measured. When you're looking for such paths, they're easily spotted, and the resistance readings you obtain will be easier to understand. Let's take an example of multiple parallel and series-parallel paths, using the same schematic (Fig. 1) we used for the "case of the poor contact."

If we have reason to measure the resistance from the plate (pin 1) of the 6EA8 to the output of the rectifier circuit (the 250-volt source), what resistance should we read? At first, there appears to be a "straight shoot" through the two 22K resistors and the 2700-ohm, 7-watt dropping resistor located in the power supply—a total of approximately 46K. But an ohmmeter will read only about 27K! Where's our low-

POINT OF POOR CONTACT (I WAS NOT SOLDERED)

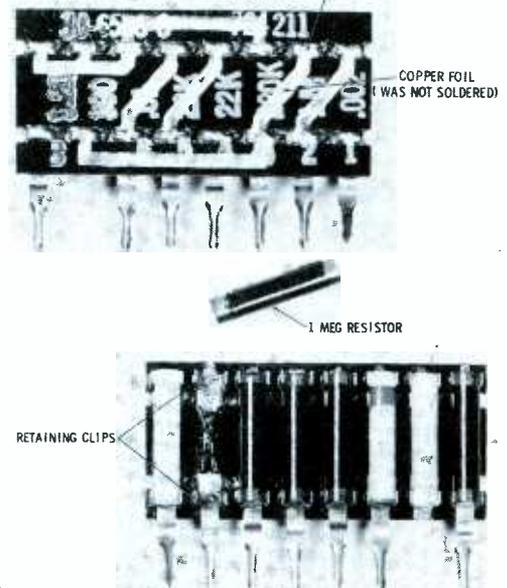



Fig. 2. Special printed component board used in noise-limiter and sync stage.

Build the finest professional color TV Set ever designed


WITH color

TV KITS

by TRANSVISION

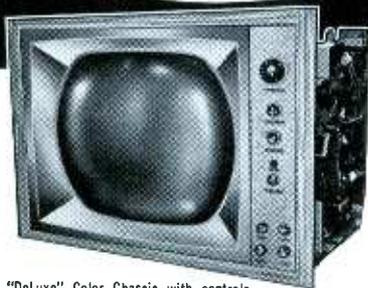

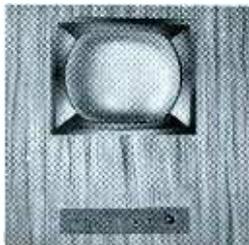"DeLuxe" Color Chassis with controls mounted on panel in a vertical position.



Custom wall installation of "DeLuxe" Color Chassis with horizontal controls separated from chassis.

LEARN AS YOU BUILD: Learn Color TV Theory, Practice, and Servicing. Complete course of study available for use in conjunction with the Kit—no technical background required to understand it.

INSTRUCTION MANUAL: Send \$5 for complete Assembly Manual, so that you can see how easy it is to build and service the Transvision TV Color Kit. Cost of manual refundable upon purchase of Kit.

This Color TV Kit is designed around the most expensive, thoroughly engineered and newest RCA TV Color Receiver.

Transvision has added improvements, features, and heavy-duty parts to this RCA licensed receiver in order to accommodate those who seek better quality than is commercially available.

WITH or WITHOUT REMOTE CONTROL

All critical circuitry is wired, aligned, and pre-tested by RCA.

Anyone Can Assemble—No Special Knowledge Required Buy Assembly Manual and See Easy, Complete Instructions.

Exclusive Features: All controls are mounted separately from chassis for flexibility in custom installation. . . . Only the finest quality oversized, extra heavy-duty parts are used for long, trouble-free use, and they are FULLY GUARANTEED for ONE FULL YEAR.

The 21" Color Tube is RCA's newest and best tube. The safety glass is bonded to the tube face to reduce reflections and eliminate dust accumulation. . . . NEVER OBSOLETE—Your Transvision TV Color Kit is always up-to-date because circuit improvements in Kit form are passed on to the Kit builder as they occur.

Buy on Installment Plan. **PAY AS YOU WIRE:** \$50 gets you started on this fascinating TV Color Kit project.

CHOICE OF MODELS: From \$394.00 Up

- With Hi-Fidelity Sound System, complete with Color Tube \$399.00 to \$439.00
- With Special Circuit (no audio) for connecting into your Hi-Fi System, with Color Tube \$394.00 to \$419.00
- Remote Control optional \$60.00 additional.

Also available as **WIRED CHASSIS** . . . Full line of Cabinets.

START NOW — MAIL THIS COUPON —

- Send FREE Catalog on Color TV Kits . . . I enclose \$5 for Assembly Manual, refundable on purchase of TV Color Kit.
- I enclose \$50 for Starting Package on pay-as-you-wire plan. (Complete Kits range from \$419 to \$499.) Dept. PFC-10

Name _____
Address _____
City _____ Zone _____ State _____

TRANSVISION ELECTRONICS, Inc.
Grey Oaks Avenue, Yonkers, N. Y. Dept. PFC-10
Telephone: (914) YONkers 5-6900

resistance path? The answer is simple, if not quick — through R2 (22K), R4 (1000 ohms), and R5 (5300 ohms) directly to the 250-volt source!

Remember one of the first rules you learned in electronics—the total resistance of a combination of resistors wired in parallel is always lower than the lowest one. The inset in Fig. 1 gives a plainer view of the path we just traced, but there's no need to redraw a circuit to this simple form unless it's very complex. The point is: no matter where you measure to or from, trace each path connected to the takeoff point until you reach a capacitor or some other DC-blocking component. If a multiple path *does* exist in any leg of the circuit, note the approximate resistance. Once you find the path having the least resistance, you can estimate the total value, and reasonably expect your estimate to come close to the actual reading you'll get with a meter.

Sometimes, during troubleshooting, you may find it necessary to simplify the task of resistance measurement by opening one or two legs of a circuit which has four or five different paths. When this occasion arises, don't just break the circuit at any old place; analyze it first, then open it where you can measure the largest number of resistors without an undue amount of unsoldering.

The use of printed wiring in a set doesn't necessarily restrict the use of this technique. Even when it isn't convenient to unsolder individual components, they can still be disconnected from the circuit by temporarily cutting one or more printed foil conductors with a sharp knife or razor blade. Afterwards, the cuts can be repaired by bridging with a short piece of wire and resoldering. (This and other hints for easier circuit-tracing and testing on PC boards will be more fully discussed in an upcoming issue.)

A good place to try disconnecting parts is in the complicated AGC circuits used in some TV sets. These circuits may have as many as 15 or 20 resistors (or more!), all working to develop and filter the AGC voltage and distribute it among the tuner and IF stages. But unsoldering a few strategic connections will al-

low you to break the circuit into sections for easier analysis.

Another place where judicious unsoldering will simplify resistance measurements is in circuits connected to B+ lines. If you can remove electrolytic capacitors from the circuit you're measuring, you'll eliminate a shunt path of uncertain resistance — thereby gaining accuracy. With an electrolytic in the circuit, you know the meter pointer is going to kick down to a low reading, and then slowly rise; but how do you know where it should come to rest? The answer to this question depends

on the size and condition of the B+ filters, as well as the amount of additional series resistance in the circuit being measured. A low-resistance shunt across a 'lytic can be measured without difficulty, but readings aren't reliable if the shunt resistance across the capacitor approaches the value of this unit's own final resistance reading.

Fortunately, many sets have a relatively low total DC resistance shunting the power supply, and you can obtain acceptably accurate readings from plate and screen circuits to ground. You only need patience




TWO-WAY RADIO
communications equipment

VHF-FM FOR: MOBILE AIRCRAFT MARINE MOTORCYCLE PORTABLE BASE	VHF-FM FOR: AIRPORT VEHICLES GROUND STATIONS POINT-TO-POINT	VHF ANTENNAS REMOTE CONTROLS ACCESSORIES
---	--	---




COMCO "ON GUARD" 24 HOURS A DAY

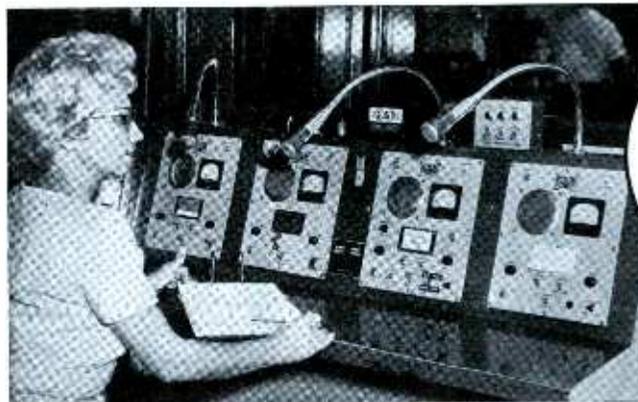

DEPENDABLE
COMCO
TWO-WAY RADIO
EQUIPMENT
USED EXCLUSIVELY
BY THE CITY OF
CORAL GABLES
FLORIDA FOR
PAST 15
YEARS

A SPECIALLY DESIGNED DISPATCHER'S CONSOLE PROVIDES EFFICIENT, INSTANT CONTROL OVER 4 RADIO CIRCUITS.

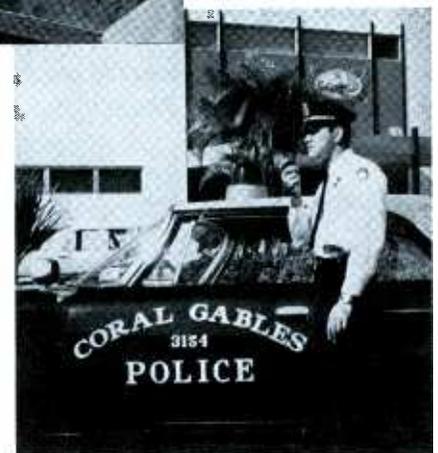- 1) Police messages are dispatched to patrol cars, motorcycles, police boats, and other vehicles over a 150 Mc mobile relay system of advanced design. A 310 ft. antenna height on relay transmitter provides 40 mile car-to-car communications. Two-way or three-way versatility by selection at control console.
- 2) A Local Government frequency for fire trucks, rescue squads, electrical trucks, and other maintenance and official vehicles.
- 3) The Inter-City circuit on 155.37 Mc has special relay provisions permitting messages from other communities in Dade County to be simultaneously re-transmitted to Gables police vehicles enabling each mobile unit to receive direct county-wide broadcast.
- 4) A completely independent stand-by base station for Police and Local Government frequencies is located several miles from main repeater station.



This high performance system includes four base stations, 80 mobile units, three portable base stations. Eleven new COMCO Model 900 mobiles with all-transistor receiver will soon be added.

For full details, write today!



DESIGNERS AND MANUFACTURERS OF **COMCO** RADIO COMMUNICATIONS EQUIPMENT

COMMUNICATIONS COMPANY, Inc.


FOUNDED 1938 CORAL GABLES, MIAMI 34, FLORIDA

to wait while the large electrolytic filters build up a charge from the ohmmeter battery. To avoid reverse leakage current which could produce an incorrect low reading, check the battery polarity of the ohmmeter to make sure it agrees with the polarity of the capacitor.

Summary

You might wonder why you need to worry about resistance measurements, or adopt measuring short-cuts—why not just unsolder each component and check it individually? To answer this question, take a close look at some of the sets you're servicing today. The advantages of avoiding unnecessary soldering on printed-circuit boards are obvious. Furthermore, certain components and subassemblies are designed and physically mounted in such a way that unsoldering can add hours to servicing time. For example, there are printed boards whose undersides are completely shielded; you can't gain access to the solder connections without first removing the board itself. Then, too, unusual chassis shapes often make removal of the

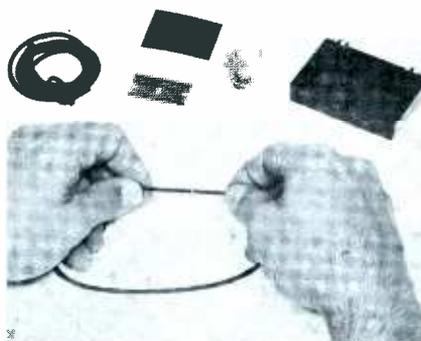picture tube imperative before you can locate or reach certain components. Think of all the places you can touch with an ohmmeter probe, but not with a soldering iron—and you'll readily see the advantages of knowing all you can about in-circuit resistance measurements!



Instant Drive Belts

The product shown above was originally part of a roll of ordinary-looking rubber material. In less time than it will take you to finish reading this article, a precise length was measured and cut from the roll, and the ends merged (by a special fluid) to create the endless belt shown.

The belt was fashioned from

materials contained in the *Mak-A-Belt Kit*, a new product developed by Techni-Parts Corp. of West Hempstead, New York. The kit includes several feet of rubber material, a vial of the special merging fluid, and a razor blade for cutting the belt.

For those who have taken the time to disassemble certain tape recorders for drive replacement, the *Mak-A-Belt Kit* will represent an unusual timesaver. The belt can be threaded around the wheels and into position without taking the recorder apart; the "weld" is made afterward. Besides saving repair time, the Kit is intended to cut down inventory. When you need a drive belt, you can simply measure the length of the old one, and make a new one from the Kit; there is no need to stock various sizes.

To make the belt shown in the picture, a length was cut from the roll, a drop of the merging fluid was applied to one end, and the other end was pressed firmly against it while we slowly counted to thirty. The result? The picture tells the story. ▲

FOR ALL YOUR SERVICE NEEDS

Speco UNIVERSAL REPLACEMENT KITS

For all Domestic and Imported Transistor Radios and Equipment

SUB MINIATURE ELECTROLYTIC KITS

MK-1—Master kit consists of 12 axial and 12 upright capacitors.

AK-1—Axial kit consists of 12 axial capacitors.

UK-1—Upright kit consists of 12 ass'd upright capacitors.

SUB MINIATURE CERAMIC-DISC CAPACITOR KIT CD-1

Each kit contains 35 ceramic disc capacitors from .001 to .05 rated at 25 volts.

SUB MINIATURE RESISTOR KIT R-1

Contains 100 upright type RETMA color coded resistors. 2 each of 50 assorted values. 5 ohms to 250 K, 1/20 watt.

MINIATURE TRANSFORMER KIT TR 1

Contains 2 input and 2 output transformers. Used in single or push-pull circuits.

All Speco Products Available at Your Local Distributor

COMPONENTS SPECIALTIES, INC.

9 Kees Place • Merrick, L. I., New York

ON OFF
Turn ON the QUIET
Turn OFF the NOISE

with **QUIETROLE...**

The quality, proved lubricant for effective silencing of noisy controls and switches on TV, radio and electronics instruments. And the FREE EXTENDER TUBE makes these once pesky places easy to reach. Put quality QUIETROLE in your repair kit and see how quickly and easily you satisfy more of your customers.

6 Oz. SPRAY PACK CAN
(with FREE Extender Tube)

2, 4, 8 oz. Bottles
(with Dropper)

Product of
QUIETROLE COMPANY

Spartanburg, South Carolina
in Canada: CROSS CANADA ELECTRONICS
12 Laurel Street, Waterloo, Ontario

TV Remotes

(Continued from page 33)
counterclockwise rotation, while section C causes clockwise rotation of the antenna.

As mentioned before, the three sections of S2 operate in a certain sequence. One complete cycle, starting from the *off* position, can be described as follows: Initiated by a press of the transmitter button, S2 operates; sections A and B close, and the rotator moves in a counterclockwise direction. When the rotator motor is actuated, it continues to run until the transmitter button is depressed again. Then S2 returns to the off position—all sections of the switch open—and the rotator stops. When the unit is pulsed once again, sections A and C close, moving the rotator in a clockwise direction. The next pulse again opens all sections of the switch and turns the rotator off. With the next series of four pulses, this sequence repeats itself.

Any time S2 is closed, the motor will be operating. If it is run continuously for too long a time, damage to the motor and transformer is possible. For this reason, some protective device is needed for these components, other than the line fuse in the input circuit. Shown in the schematic is a timed *thermal switch*, wired in parallel with S1. If this switch closes, due to thermal action (after four or five minutes of continuous operation), it will cause relay M2 to energize and move S2 to the next position—which will always be *off*. Remember, the off position occurs *every other* time the receiver is pulsed.

M2 will remain energized as long as the thermal switch is closed. In this state, M1 cannot cause S2 to move to the next position—even if M1 is keyed by the transmitter. After a few minutes, however, the thermal switch will cool and open; the system will then resume normal operation.

Trouble Isolation

Locating the cause of an inoperative remote system will be quicker and easier if you'll use the following outline as your guide:

First, manually close each set of relay contacts (using an insulated tool) and see if this initiates the expected action. If channel changing

and other functions occur as they should, proceed to check the remote receiver.

Apply a DC "unbiasing" voltage to the base of each relay-control transistor—that is, feed in a voltage which will counteract the fixed bias on the transistor and allow it to conduct. With the PNP transistors commonly used in these units, about -2 volts on the base should cause the relay to kick in.

You can use a bias box or a battery for this test. Don't short the base of any transistor to ground in

an effort to remove the bias. It probably won't harm a relay-control transistor, but it won't help, either. In any case, it's not a good habit to start, because using this type of test in some other circuits is likely to cause transistor damage.

If no relay action takes place during this test, check the output stages. If the relays do operate with the negative voltage applied, the next check is to see if a signal is being received from the remote transmitter. For this test, use another transmitter of the same type (if



Special!

ONLY \$4.99

NOW... SAVE \$1.77

IMPERIAL Ungar

#6060 SOLDERING IRON

SAVE

when you buy the IMPERIAL... SAVE every time you use it on the bench or for on-the-spot servicing. The #6060 IMPERIAL... designed especially for printed circuitry and miniature soldering applications... reduces costly customer callbacks, damage to circuits, time spent on servicing.

The IMPERIAL features complete interchangeability of parts, comes with two of the most-used tips (44 are available), and a 40 Watt high heat, long-life heat cartridge. See for yourself why the new IMPERIAL is the most preferred iron in the electronics field today!

115v AC-DC



ASK FOR THIS SPECIAL
OFFER AT YOUR UNGAR
DISTRIBUTOR TODAY!

available) or use the following hookup:

Take a CW signal generator that covers the 40-kc band, hook a small speaker to the output leads, and place the speaker near the input transducer of the receiver. With medium-low output from the generator, tune it through 40 kc and see if the relays operate. If so, the receiver is working properly, and the transmitter is probably faulty.

If the receiver doesn't operate, advance the generator output and again tune through 40 kc. If the relays still don't kick in, or require a very strong signal to react, the receiver has an open signal path or a weak stage.

Try signal injection with the generator to help isolate receiver faults. Tune the generator to some subharmonic of the desired frequency (such as 8 kc); this gives a more useful test than direct feed-in of the 40-kc signal, which tends to be hampered by stray pickup of signal radiated from the generator leads. Tuning to a subharmonic also allows the use of a higher output from the generator, which results in more accurate stage-gain checks.


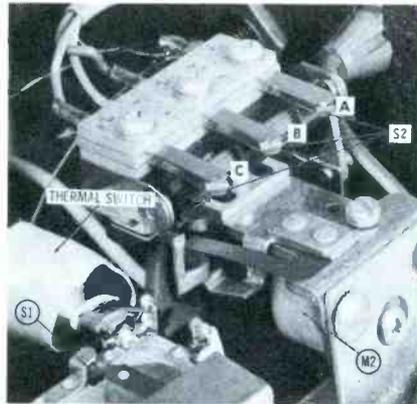


Fig. 5. Rotator control is self-contained unit equipped with stepper relay.

Start at the base of the last 40-kc amplifier stage, feeding in a signal through a coupling capacitor (approximately .05 mfd). Begin with a very low output from the generator, and tune through the frequency range where keying of the relays is expected. When a relay operates, remove the input signal, and note whether the relay *stays* closed. If it does, the test is inconclusive because the relay is being energized by stray signal pickup. Reduce the generator gain and try again. If the relay *did not* energize the first time around, *increase* the generator gain on the second try.

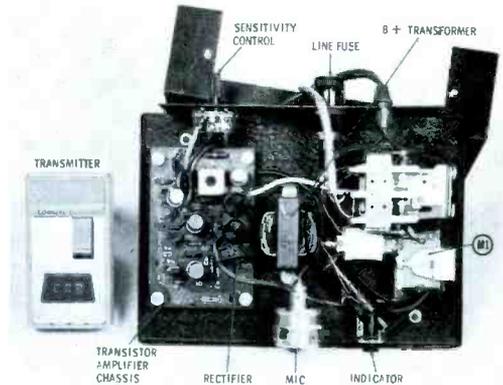

Repeat this injection test, working back toward the input of the receiver. Progressively less signal should be required to actuate the relays, except when the signal is fed into an emitter follower. If you note a lack of stage gain in an amplifier, or if one stage refuses to respond, carefully check the static DC operating voltages (with no signal input) in the suspected circuit—and check the transistor, too. Voltage and resistance checks should pinpoint the defective component. With a little practice, you can learn to check a receiver by this method in a matter of minutes. ▲

QUALITY PRODUCTS! . . . for High-Profit Sales and Year-Round Business!

2 NEW PRODUCTS FOR TAPE RECORDER MAINTENANCE

"SPOT" LUBRICATING OIL
For pin-point oiling of bearings, shafts and oil holes. "SPOT" is a high grade lubricant that reaches hard-to-get-at bearings with a concentrated spray.

TAPE RECORDER CLEANER
An approved chemical spray that washes accumulated iron oxide from tape recorder heads. The combination of the spray and pin-point applicator results in fast and efficient cleaning of tape recorder heads.

INJECTORALL
INJECTORALL COMPANY
Brooklyn 14, New York

MAKE BIG PROFITS!
with 25 to 50 MC. Industrial

2-WAY RADIO

THE "MESSENGER 202" DELIVERS THE PEP AND PERFORMANCE NEEDED FOR SOLID COMMUNICATIONS—COMPLETE DEALER AID PROGRAM PUTS YOU INTO THIS PROFITABLE FIELD OVERNIGHT!

The "Messenger 202" sells for less than \$200.00—is priced within easy reach of any business! A complete 10-tube (including rectifier) crystal-controlled AM transceiver, the "202" is F.C.C. type accepted for use in the Industrial, Public Safety, and Land Transportation service. The "202" practically sells itself when you point out the savings that almost any business or municipal organization can make with this top performing, low cost industrial equipment! Highly selective and sensitive superheterodyne receiver, built-in "Squelch," and AVC, ANL circuits. Designed for easy operation—fast, smooth installation—and simplified maintenance. Available nationally from E. F. Johnson Company distributors. Powerful dealer aid program shows you how to make big money in sales and service in this highly profitable field—gives you everything you need to handle your own line of industrial 2-way radio equipment!

CONTACT YOUR DISTRIBUTOR or WRITE TODAY for Full Details

E. F. JOHNSON CO.
5607 Tenth Ave. S.W. • Waseca, Minn.

Manufacturers of World's Most Widely Used Personal Communications Transmitters

PRODUCT REPORT

For further information on any of the following items, circle the associated number on the Catalog & Literature Card.

Tube-Tester Adapter (43S)



Five- and seven-pin nuvisitors, novars, compactrons, and 10-pin miniature tubes can be tested on any manually-operated tube tester that has an octal socket, when it is equipped with Hickok's CA-4 universal adapter. Each of 14 possible pin locations is controlled


by eight individual selector switches, thereby providing facilities for testing future tube types.

Soldering Tip (44S)



A new iron-clad thread-on soldering tip specifically designed for pin, tube-socket, and connector soldering work has been introduced by Ungar Electric Tools. This tip (No. 6481) is designed to thread onto any of three "Imperial" heat cartridges in approximate wattages (and tip temperatures) of 25W (690°), 30W (750°), and 40W (860°). A total of 44 different tips are currently available for "Imperial" irons.

Yagi Couplers (45S)

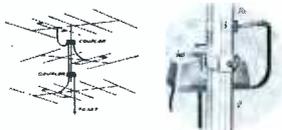

A new series of mast-mounted couplers by Winegard allow single-channel TV and FM yagis to be connected together so a single lead-in wire can be used to carry the signals into the building. These couplers are available in 12 VHF models and one FM model. The FM coupler can also be used inside the house as a signal splitter. Models CA-2 through CA-13 list at \$5.50 each; Model CA-FM sells for \$4.50.

CB Transceiver (46S)




An "S" meter and a transmitter-tuning meter are incorporated in Sonar's Model "G" Citizens-band transceiver. Eight crystal-controlled channels are featured in the unit, which weighs only nine pounds. Capable of five watts output, the transmitter employs high-level class-B modulation. The receiver is dual-conversion, tunable over 23 channels, with adjustable squelch and a crystal-spotting switch. Price is \$229.50.

Ceramic Cartridges (47S)



Two ceramic stereo cartridges, the Sonotone 16TA and 18TA, are designed to replace many existing original-equipment units. Output voltage of the 16TA is .65 volt, while the 18TA delivers 1 volt. Channel separation for both cartridges is 25 db, and frequency response is 20 to 10,000 cps ± 1 db; tracking force is from 4 to 7 grams. List price on each of these "turnover" units is \$6.00 with sapphire styli, and \$9.75 with a diamond-sapphire combination.

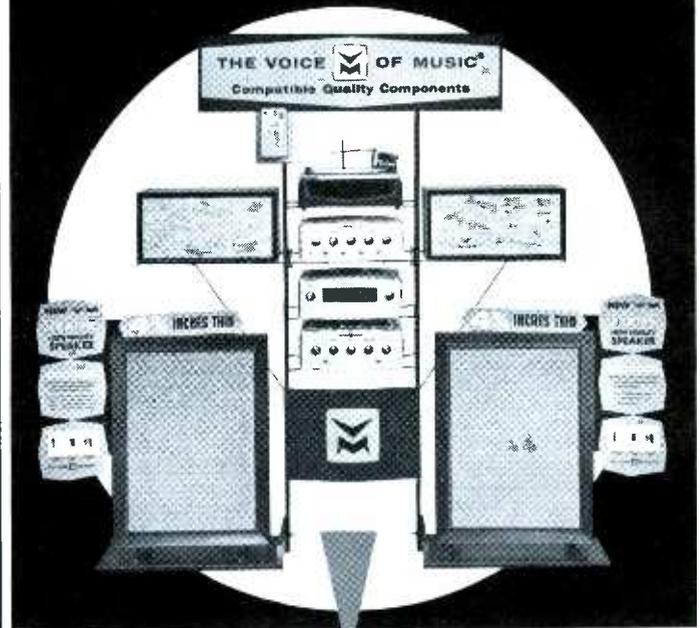ADD NEW PROFIT TO YOUR HI-FI COMPONENTS BUSINESS THE EASY V·M WAY!



- Priced to attract *new* customers, this complete line of quality components is effectively displayed and demonstrated in only 5 square feet.
- Convenient one-source buying . . . backed by V·M's national network of Service Centers.



The store display fixture is complete with literature dispenser and the "Silhouette 62" speaker feature posters. It actually displays nine V·M component products!



High-Fidelity FM Stereo, FM, AM Component Radio Tuner Model 1465.



"Stere-O-Matic"® 4-Speed Automatic Record Changer Model 1571 11" turntable.

Automatic Manual-Play, Extra-long, dynamically balanced, non-resonant Tone Arm. Diamond Needle. Shadowlite stylus pressure.



Precision-Built AC Stereo Amplifier Model 1448. 40 watts (peak); 20 watts per channel. Frequency response, 40-25,000 cps.



Changer Base Model 1438. For "Stere-O-Matic"® Changers. Pre-wired receptacles.



"Silhouette 62" High-Fidelity Component Speaker System. Three speakers: 10" woofer, 6" mid-range, 3.5" tweeter. Frequency response, 30-16,000 cps.



Stereophonic High-Fidelity Component Amplifier Model 1428. 60 watts (peak); 30 watts per channel. Frequency response, 20-30,000 cps.



High-Fidelity Component Speaker Model 32. Three speakers: Two 6" and one 3". Frequency response 60-12,000 cps.

YOUR V·M DISTRIBUTOR IS READY NOW TO GIVE YOU ALL THE DETAILS AND POINT OUT THE MANY ADVANTAGES OF THIS NEW V·M COMPONENTS LINE. CALL HIM TODAY!

THE VOICE OF MUSIC

V·M CORPORATION • BENTON HARBOR, MICHIGAN
KNOWN FOR THE FINEST IN RECORD CHANGERS, PHONOGRAPHS AND TAPE RECORDERS
October, 1962/PF REPORTER 103



a quick, inexpensive way to correct off-standard voltage

TV sets, hi-fi's and other electronic equipment operate best when voltage holds closely to the normal 115-120 volts for which they were designed. Over-voltage and/or under-voltage affects the performance of the tubes and the life expectancy of all other components. Why fight an off-standard voltage condition? Correct it with an Acme Electric T-8394M Voltage Adjustor.

Corrects voltage over a range from 95 to 125 volts to normal 115/120 volts, simply by turning a regulating switch. Includes voltmeter which indicates output voltage; cord and plug and plug-in receptacle. Tell your supply dealer you want the Acme Electric T-8394M 300 watt, Voltage Adjustor. No other so compact, complete, practical, inexpensive. Write for Bulletin 091.

ACME ELECTRIC CORPORATION

9410 Water St. SAA 3581-2033 Cuba, N. Y.
In Canada: Acme Electric Corp. Ltd., 50 Northline Rd., Toronto Ont.



LEARN FM 2-WAY RADIO SERVICING AT HOME

- Earn More Money
- Build a Better Future

Advancement and increased earnings are waiting for you in the expanding communications field. The Motorola Training Institute's home study course in FM 2-way radio servicing can enable you to take advantage of these profitable opportunities now. Learn all about servicing the new transistorized equipment . . . learn advanced techniques for handling complex service problems easier and faster.

In addition to this wealth of practical application knowledge, you will also be preparing yourself for your 2nd Class FCC Radio-telephone License. For full details, send coupon today. There is no obligation and no salesman will call.

MOTOROLA TRAINING INSTITUTE
4545 West Augusta Boulevard • Chicago 51, Illinois • Dept. ACX239

Please send me full details on the Motorola Training Institute's planned home study program on FM 2-Way Radio Servicing.
I now hold _____ FCC License.

Name _____
Address _____
City _____ Zone _____ State _____


PA Baffles (48S)

Two basic designs with identical styling make up a new line of ceiling or wall baffles from Argos Products. The surface-mounted units are 3½" deep and can be either permanently fastened to the wall or ceiling, or hung on the wall like a picture. The recessed model projects only 1½" from the surface; a 6" circular hole is required to accommodate the speaker. Six models are available in each version.



FM Antennas (49S)

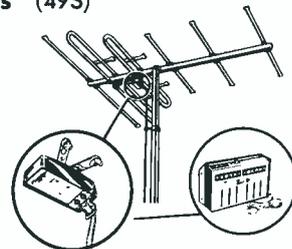A built-in transistorized amplifier is featured in JFD's Model TNTFM350-AC "Transis-Tenna" FM antenna. Twin-driven dipoles deliver 34-db gain to meet the stringent demands of stereo reception. The antenna can be purchased without the amplifier as Model AFM350, and the amplifier may also be bought separately as Model FM106. List price of the complete preassembled antenna is \$54.95.



Three-Way Pliers (50S)

Installation of electrical outlets is speeded up by the use of new electricians' pliers from Champion DeArment. This tool performs three separate jobs. Basically a diagonal cutter, the tool contains two wire-stripping notches which allow stripping of 12- and 14-gauge wire. The pliers are offered under the name "Channelock" No. 337-W.



Appliance Dolly (51S)

A deluxe model of the Yeats #7 appliance dolly is now available. Designated Model #14, the new type has two strap- and -ratchet assemblies. The second strap, located near the bottom of the dolly, keeps the appliance from shifting—especially when it is being moved up or down stairs. The Model #14 is constructed of aluminum and weighs 40 lb. Price is \$79.50.




Background Music (52S)

Plug-in tape cartridges are utilized in Cine-Sonic's new series of background-music players. Model ET #10 features a built-in paging system, while Model #40 is a tape-only machine. Continuous-tape cartridges allow completely unattended operation. Typical applications include systems in hotels, supermarkets, factories, stores, banks, and shopping centers. Three sizes of plug-in cartridges are available; the choice depends on the repetition requirements of the program.



Nutdriver Set (53S)

Ten pocket-size nutdrivers and a special "torque-amplifier" handle are contained in a new set from Xcelite. This special extension slips over the handle of any pocket nutdriver to give it a length and torque equivalent to a standard type. The drivers, which range in size from 3/32" to 3/8", are contained in a see-through plastic case which can be carried in a pocket or stood on a workbench. List price is \$8.25.

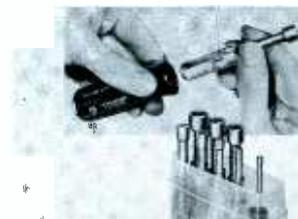

Soldering-Iron Handle (54S)



A new pencil-iron handle made from nylon is available from **Sidco**. The handle has vertical vents which keep it cool during use. The device, which will not break or crack in use, weighs 3 ounces with cord and is 6" long. A patented internal design keeps tips tight in the handle. List price is \$1.80.


CB Transceiver (55S)



A five-channel selector switch is featured in the "Globe Star" CB transceiver from **Globe Electronics**. Utilizing a dual-conversion superhet circuit, the unit contains 10 tubes plus rectifier, and has a squelch circuit that can be triggered by a .1-mv signal. Mobile-to-mobile range of the transceiver is up to five miles

depending on terrain and antenna location. User net price is \$159.95.


PA System (56S)

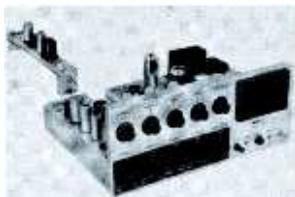

A new series of public address systems from **Harman-Kardon** utilizes modular construction to make them more versatile. The "Galaxy" series consists of three amplifiers, a preamplifier chassis, and three booster amplifiers. Various combinations can be made up from these basic components to suit

particular requirements. A wide choice of preamplifier input modules makes provision for almost every type of program source, including override and compression operation.


UHF Booster (57S)

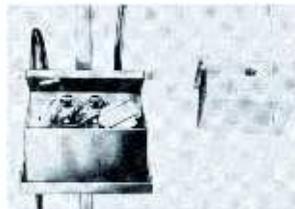

Five different boosters, each covering a portion of the UHF band, are included in the **Blonder-Tongue UB** series. These units have 300-ohm inputs and 75-ohm outputs, and are rated at 14-db gain. Designed for easy installation and servicing, the boosters have swing-down chassis and stripless connections. For MATV and CATV systems, a professional model

UBP is available.

Hi-Fi Baffles (58S)

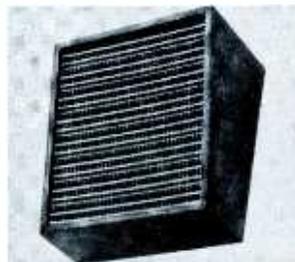

A new line of baffles and speaker-baffle combinations is announced by **RMS Electronics**. These wall-mount baffles are available with speakers (BS series) or without them (SB series), in sizes from 5" to 12". Cabinets are finished on four sides in mahogany, walnut or blonde. The decorator grille cloth is recessed 1/4" from the front face of each baffle.

Stereo Tuner (59S)



Both the front end and the four-stage IF board are pre-wired in **EICO's Model ST97 FM Multiplex Stereo Tuner** kit. No test or alignment instruments are needed to assemble the unit. Specifications include an audio-frequency response within ± 1 db from 20 cps to

15 kc, and 30 db of channel separation; full-limiting sensitivity is 10 uv. The unit weighs 17 pounds and measures 5 1/8" x 15 7/8" x 11 3/8". Price is \$99.95 (kit) or \$149.95 (wired).



...nothing cheap but the price!

Compare performance, filtering, quality, output



New DC Power Supplies

Guaranteed 1 Year

They'll sell you on sight. Never before has so much value and performance been packed into a completely assembled power supply.

Auto radio... Use EC-2 for all servicing needs. Use EC-1 for "warm-up" and "check-out" or as low cost power source for FM and AM demonstrations.

Transistor portable servicing... Ideal as a hum-free DC voltage source.

Research and development work... Reliable performance for wide application in industry and laboratory.



Save bench space. Only 10 3/4" x 4 3/4" x 6 1/2" ... use vertically or horizontally.

	EC-2	EC-1
DC VOLTAGE OUTPUT	0-16 VDC continuously adjustable	12 VDC (adjustable)
AMPERAGE OUTPUT	0-5 ADC	0-5 ADC
RIPPLE	0.5% at 5A	0.5% at 5A
REGULATION	1.8 V/A	1.4 V/A
METER	0-20 V/O - 10A
DC IMPEDANCE	1.8 ohms	1.4 ohms
PANEL FEATURES	On-off switch, pilot light, meter function switch, variable voltage control, insulated binding posts, fuse, 6' cord.	4-position voltage adjustment switch, pilot light, wing nut output terminals, 6' cord.

Write for Complete Line Catalog PS-561

Available Now at Your Electronic Distributor.



ELECTRO PRODUCTS LABORATORIES

6125-T Howard, Chicago 48 (Niles), Ill.

Phone: 647-6125

Canada: Atlas Radio Ltd., Toronto

Since 1936 . . . Pioneers in Low Voltage DC Power Supplies

October, 1962

Acme Electric Corp. 104
 Admiral Sales Corp. 71
 Aerovox Corp. 40
 Ampere Electronic Corp. 37
 Antenna Specialists Co., The 81
 Arrow Fastener Co., Inc. 84
 ATR Electronics, Inc. 16
 B & K Mfg. Co.,
 Div of Dynascan Corp. 55, 57-58, 74
 Belden Mfg. Co. 69
 Berns Mfg. Co., The 78, 97
 Blonder-Tongue Labs 80
 Bussmann Mfg. Co. 75
 Centralab, A Div. of Globe-Union, Inc. 85
 Castle TV Tuner Service 46
 Chemtronics, Inc. 94
 Communications Co., Inc. 99
 Components Specialties Co. 100
 DeSod Div. of Eversole Industries 92
 Duotone Co., Inc. 78
 EICO Electronic Inst. Co., Inc. 83
 Electronic Chemical Corp. 84
 Electro Products Laboratories 105
 Electro-Voice, Inc. 63
 Enterprise Development Corp. 97
 Fisher Radio Corp. 70
 G-C Electronics 61
 General Electric Co. 66, 67
 Harman-Kardon, Inc. 77
 Hickok Electrical Inst. Co. 72
 Injectorall Co. 102
 I.T.T. Distributor Products Div. 23, 45
 JFD Electronics Corp. 17, 93
 Jackson Electrical Inst. Co. 64, 106
 Jerrold Corp. 65
 Johnson Co., E. F. 102
 Littelfuse, Inc. 4th Cover
 Mallory & Co., Inc., P. R. 47
 Mercury Electronics Corp. 91
 Mercury Tuner Service, Inc. 70
 Merit Coil & Transformer Corp. 60
 Miller Co., J. W. 92
 Motorola Training Institute 104
 Nortronics Co., Inc., The 88
 Philco Corp.—Parts and
 Service Operations 18, 19
 Planet Sales Corp. 96
 Precision Apparatus Co., Inc. 49, 50, 51
 Precision Tuner Service 86
 Quietrol Co. 100
 RCA Electron Tube Div. 90, 3rd Cover
 RCA Parts & Accessories Div. 15
 RCA Test Equipment Div. 87
 R-Columbia Products Co. 94
 RMS Electronics, Inc. 86
 Sams & Co., Inc., Howard W. 73, 84
 Sarkes Tarzian, Inc.
 Semiconductor Div. 89
 Tuner Service 11
 Seco Electronics, Inc. 79
 SENCORE, Inc. 41-44
 Sonotone Corp. 76
 Sprague Products Co. 13-14
 Standard Kollsman Industries, Inc. 2nd Cover
 Sylvania Electric Products, Inc. 59
 Technical Appliance Corp. 24
 Terado Co. 92
 Transvision Electronics, Inc. 98
 Triad Distributor Division 86
 Triplett Electrical Instrument Co. 1-2
 Tung-Sol Electric, Inc. 53
 Ungar Electric Tools 101
 V-M Corp. 103
 Vidair Electronics Mfg. Corp. 96
 Weller Electric Corp. 56
 Western Tuner Rebuilders 48
 Winegard Co. 20-21, 96, 97
 Workman TV., Inc. 78
 Xcelite, Inc. 48

ANTENNAS & ACCESSORIES

- 15S. **BLONDER-TONGUE** — 15-page technician's guide, "Quick Reference Manual of Master TV Systems," containing diagrams for home, TV-shop, apartment-house, and motel systems. See ad page 80.
 25S. **CUSH CRAFT** — 8-page catalog (No. 62) describing complete line of amateur communications antennas; both UHF and VHF types included.
 35S. **GAM**—Catalog sheet giving specifications on miniaturized TG-2-R VHF mobile antenna designed to mount on top of vehicle or in other restricted spaces.
 45S. **JERROLD** — 4-page catalog containing information on APM-101 Powermate transistorized TV/FM preamp, and FMX Range Extender for FM use; also includes equipment for TV distribution systems. See ad page 65.
 55S. **JFD**—Descriptive and promotional literature plus sales aids for new Transis-Tennas; also complete set of specifications for outdoor and indoor TV antennas and accessories, including exact-replacement antenna data. See ads pages 17, 93.

AUDIO & HI-FI

- 65S. **ATLAS SOUND**—Catalog No. 562 listing specifications on microphones and loudspeakers for public address, commercial, and industrial use.
 75S. **EICO**—New 32-page catalog of kits and wired equipment for stereo and monophonic hi-fi, test equipment, Citizens-band transceivers, ham gear, and transistor radios. Also "Stereo Hi-Fi Guide" and "Short Course for Novice License." See ad page 83.
 85S. **FISHER**—1963 component catalog, 1963 handbook for custom installations, and complete information on Model 300 Multiplex Generator. See ad page 97.
 95S. **SONOTONE**—Sheet SAH-51 describing stereo and mono record/play and erase heads. See ad page 76.

COMMUNICATIONS

- 105S. **COMMUNICATIONS, INC.** — Data sheet on "Speak Easy" audio compressor/amplifier for use with Citizens-band mobile or base transceivers.
 115S. **CREATIVE PRODUCTS**—Complete information on LCF series of loading coils and other antenna accessories for CB use.
 125S. **MONITORADIO** — Catalog sheet describing complete line of FM receivers for both mobile and fixed-station use.
 135S. **SAMPSON**—Data on integrated components for complete CB base station; also sheet describing Model VM-12-120 modulator.
 145S. **SHURE** — 4-page catalog describing Model 488 noise-cancelling microphone; also lists microphones for both special- and general-purpose applications.

COMPONENTS

- 155S. **BUSSMANN** — 24-page booklet (SFB) giving detailed information on complete line of Buss and Fusetron Small Dimension fuses and fuseholders used for protecting electronic equipment. See ad page 75.
 165S. **BRITISH INDUSTRIES** — Sheet describing Multicore solder; discusses how Savbit Alloy extends tip life of soldering irons.
 175S. **CENTRALAB**—Brochure, "Modern Controls for Modern Equipment," describing push-pull and push-push switch controls. See ad page 85.
 185S. **LITTELFUSE** — Illustrated catalog showing prices and specifications on complete line of fuses, holders, and merchandising aids. See ad 4th cover.
 195S. **SARKES TARZIAN**—Catalog sheet listing silicon rectifier types used as plug-in replacements for rectifier tubes. See ad page 89.
 205S. **SPRAGUE**—Chart C-457 (designed to hang on wall) showing all popular TV-radio-hi-fi replacement components. See ad pages 13-14.

SERVICE AIDS

- 215S. **BERNS**—Data on 3-in-1 picture-tube repair tools, on Audio Pin-Plug Crimper that lets you make pin-plug and ground connections for shielded cable without soldering, and on ION adjustable beam bender. See ads pages 78, 97.
 225S. **CASTLE**—Leaflet describing fast over-

- haul service on television tuners of all makes and models; also illustrated lists describing universal and original-equipment tuners available. See ad page 46.
 235S. **GC ELECTRONICS**—Catalog FR-62-S, new products supplement for general catalog FR-62; lists replacement antennas, test equipment, and service aids. See ad page 61.
 245S. **INJECTORALL**—Catalog of electronic chemicals, including New No. 20 Lens Kleen (for removing scratches from plastic TV safety windows) and No. 30WC Renew Spray (for polishing cabinets and removing scratches); also pocket-sized catalog, "Open the Door." See ad page 102.
 255S. **PRECISION TUNER**—Information on repair and alignment service available for any TV tuner. See ad page 86.
 265S. **RCA (PARTS & ACCESSORIES DIV.)**—Form TK-331, "Color Cross Reference," and TK-310 "Color Accessories and Parts." See ad page 15.
 275S. **YEATS**—Literature describing the new Model 14 appliance dolly, featuring all-aluminum I-beam construction.

SPECIAL EQUIPMENT & SERVICES

- 285S. **ACME** — Illustrated catalog sheet 24-B01 giving specifications and listing applications for magnetic amplifiers designed for control uses; includes units with capacities from 5 to 1000 watts and voltage ranges from 24 to 160 volts. See ad page 104.
 295S. **ATR** — Literature on new series of Karadio models, including Series 600 tube-equipped types and Series 400 transistorized versions. All sets available as "universals" or customized. See ad page 16.
 305S. **INTERNATIONAL WIRE & CABLE** — 28-page catalog listing lead-in wire, coaxial cable, guy wire, and other wire and associated products.
 315S. **TELEPROMPTER CORP.**—Descriptive literature on Amphicon 190 large-screen television projector that provides 12-foot pictures for classrooms, clubs, etc.
 325S. **TRANSVISION ELECTRONICS** — 12-page catalog listing black-and-white TV kits and wired chassis for custom installation; also catalog of color-TV kits. See ad page 98.
 335S. **VOLKSWAGEN** — 60-page illustrated booklet, "The Owner's Viewpoint," describing how various business enterprises use VW trucks in their operations; also booklet giving complete specifications on VW truck line.

TECHNICAL PUBLICATIONS

- 345S. **MOTOROLA TRAINING INSTITUTE** — Literature describing two-way radio correspondence course available to qualified electronics technicians. See ad page 104.
 355S. **HOWARD W. SAMS** — Literature describing all current publications on radio, TV, communications, audio and hi-fi, and industrial electronics, including brand-new Fall-Winter 1962 Book Catalog and descriptive flyer on 1962 Test Equipment Annual. See ads pages 73, 84.

TEST EQUIPMENT

- 365S. **ANTRONICS**—Detailed information on the CA-378 Kine-Color Circuit Analyzer.
 375S. **MERCURY**—New master catalog showing complete line of test equipment and service aids. See ad page 91.
 385S. **SECO**—New folder describing complete line of tube and transistor testers and two-way radio test instruments. See ad page 79.
 395S. **SENCORE**—Latest catalog listing line of test equipment; includes information on new color analyzer, Model CA122. See ads pages 41-44.

TOOLS

- 405S. **EVERSOLE INDUSTRIES**—Sheets describing and listing prices on DeSod desoldering tools for removing and replacing parts on printed-circuit boards. See ad page 92.
 415S. **KEMODE MFG. CO.**—Descriptive literature on new cartridge-heated Quik-Shot soldering irons for use in remote locations where power is not available.

TUBES & TRANSISTORS

- 425S. **AMPEREX** — 15-page semiconductor handbook and 34-page tube reference book. See ad page 37.

Latest Jackson Tube Test Data

MODEL 448	MODEL 598	MODEL 658	MODEL 658
Tube Type	Tube Type	Tube Type	Tube Type
6X4	6X4	6X4	6X4
6X5	6X5	6X5	6X5
6X6	6X6	6X6	6X6
6X100	6X100	6X100	6X100

This many picture tubes from one box?



YES!

Because RCA Universal Silverama® Picture Tubes Make Possible Multiple Replacements!

78 Universal Silveramas replace virtually every type on the market

Every time you open an RCA Universal Silverama Picture Tube carton, you get the equivalent of *many* replacements—not just one!

RCA—pioneer of the Universal Picture Tube concept—has today achieved the greatest simplification of picture tube types.

First in the RCA Universal series—the 21CBP4A that replaces 19 industry types... or just about 25% of your replacement needs.

Next in the series, a family of four Universal Picture Tubes (the 21CBP4A, 21AMP4A, 21ZP4B, and 21YP4A) to replace 33 industry types—about half your replacement needs.

Every RCA Universal Silverama Picture Tube is made with an all-new electron gun, the finest parts and materials, and a glass envelope which, prior to reuse, has been thoroughly inspected, cleaned, and rescreened.

Now, 78 Universal Silveramas to replace 291 industry types—covering nearly any picture tube need.

This makes for an inventory simple enough that your RCA Distributor can easily keep a full stock. For you this means no more lost time hunting high and low for special, unusual, or infrequently-used types.

The whole story is conveniently set out for you in a handy slide-guide. Simply look up the Universal Silverama type you want and the guide shows you all the standard types it replaces. In addition, look up the industry type you find in your customer's set, and the guide shows you its RCA Universal counterpart. Be sure to get a Silverama slide-guide from your Authorized RCA Silverama Distributor.

RCA ELECTRON TUBE DIVISION, HARRISON, N. J.



The Most Trusted Name in Television

www.americanradiohistory.com

FASTER THAN A SHORT CIRCUIT



SUB-MINIATURE MICROFUSES

and microfuse holders
for internal connection
and panel mounting.

1/500AMP. thru 5 AMPS.
@ 125 volts. Will
interrupt 10,000 AMPS.
DC short circuit.



8AG INSTRUMENT FUSES

1/500 AMP. thru 5 AMPS.

For instrument and meter protection, Littelfuse
pioneered the design and
development of reliable fast-acting fuses.

LITTELFUSE

Des Plaines, Illinois