




NOVEMBER, 1962

35 CENTS






PHOTOFACT REPORTER


Including **Electronic Servicing**

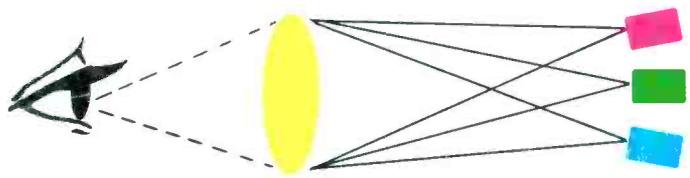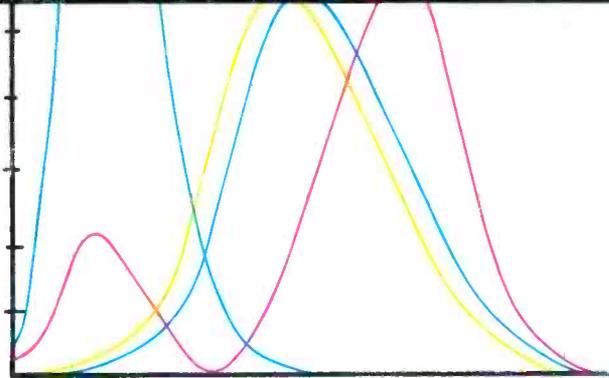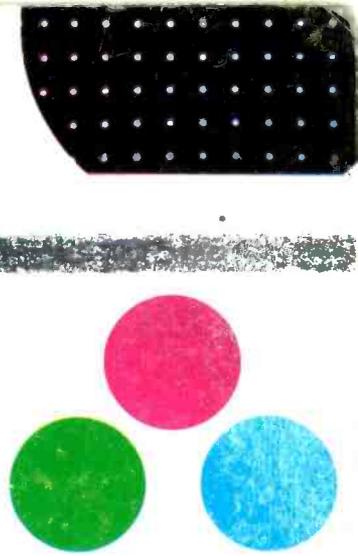


COLOR TV

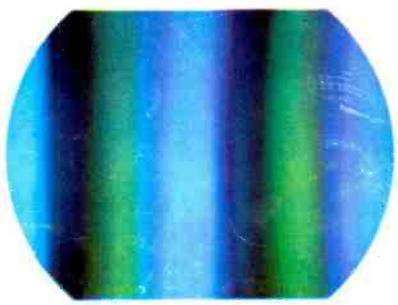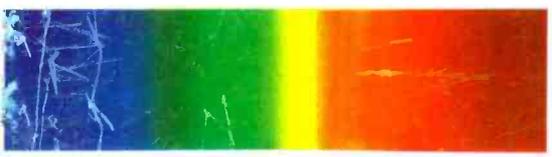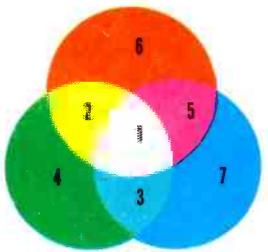

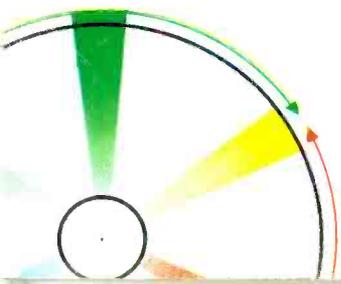
**Corona—In the Cage and Out
Objective: Pure White
A Look Inside a Color TV Station
Color TV Service Aids
Chroma Demodulator and
Matrix Stages**



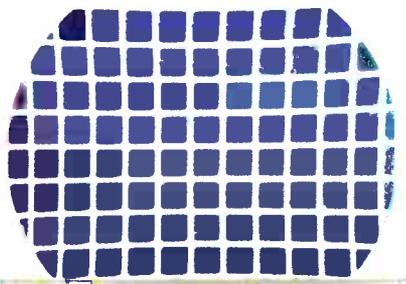PHOTOFACT REPORTER
Lester H. Davis
1400 N. Davis
St. Louis, Mo.
Radio & TV Serv.
111 Riverside Ave.
Cannon City, Colo.



TACO **T-BIRD** ELECTRA

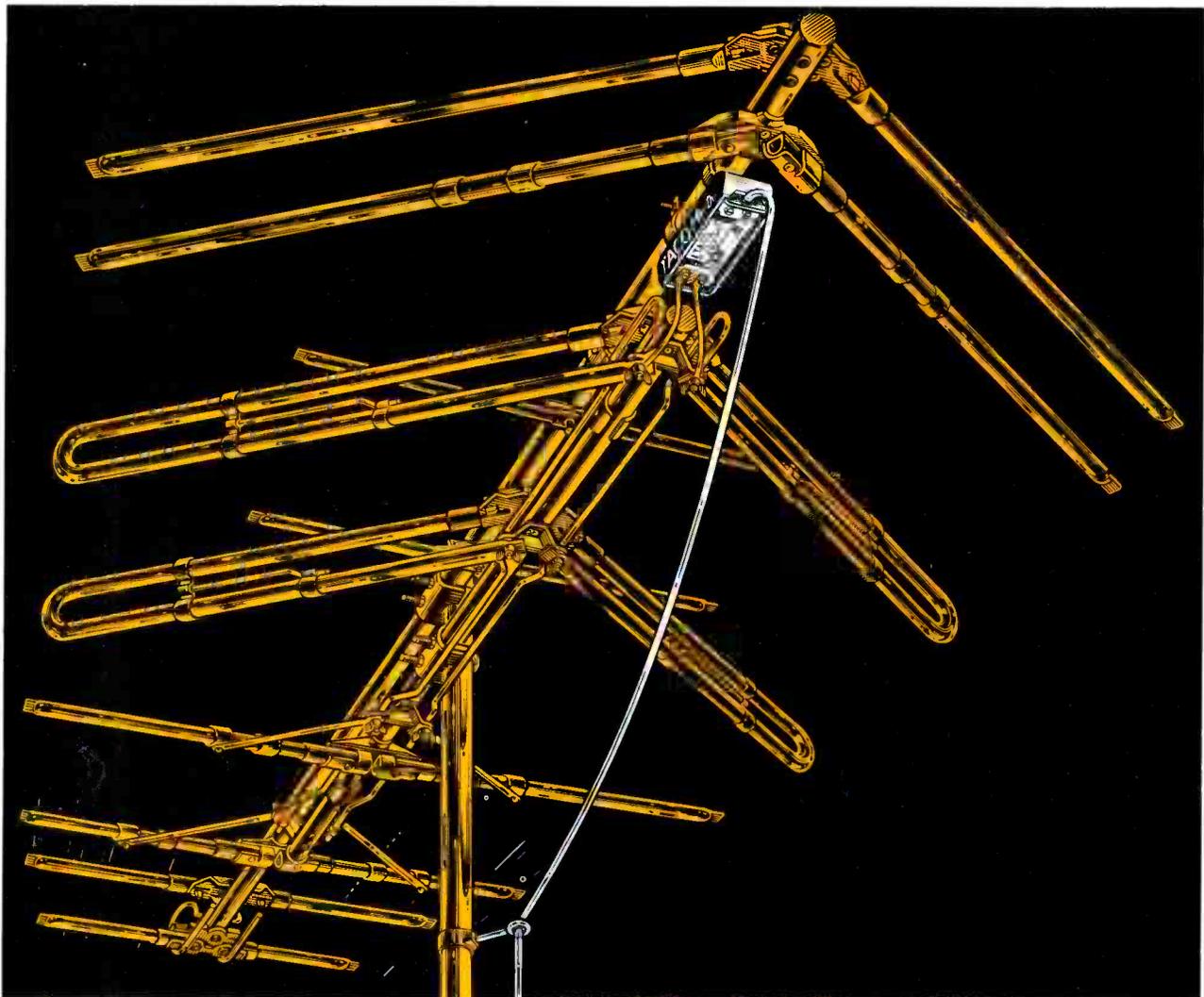

HOTTEST-and TOUGHEST

Compare and
you'll see why! →


Besides being the most durable, note the almost flat response curve of the T-BIRD ELECTRA throughout the VHF band—no hills and valleys that cause smear and distortion in black-and-white, and disrupt optimum reproduction of color. T-BIRD ELECTRA delivers a strong, clean signal, free of element "junction noise" and gain flutter—a boon to black-and-white reception, a must for color!

Write for name of nearest distributor

**TECHNICAL APPLIANCE
CORPORATION**

Dept. JDT-66, Consumer Products Division
Sherburne, New York

A Subsidiary of
THE JERROLD CORPORATION

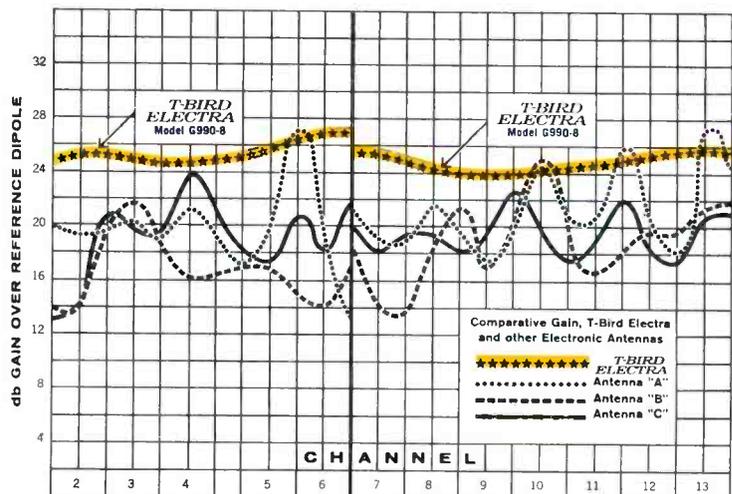



Delmonico

Model CC-210

This imported home entertainment center features a 21" color television (with 21FBP22 CRT), FM-AM tuner, four-speed phonograph, and stereo amplifier. Also included are provisions for adding an FM stereo adaptor.

The mode of operation (TV, FM, AM, PH) is selected by the four-position switch located on the radio control panel; other controls mounted on this panel include radio tuning, volume, tone, and on-off.

TV color, tint, brightness, contrast, vertical-hold, horizontal-hold, channel-selector, and fine-tuning controls are on a separate panel at the other side of the TV screen.






The switch-type tuner has a number of unusual features: electrical fine tuning, with an additional automatic-fine-tuning (AFT) control circuit to keep the oscillator on frequency; clearly marked channel numbers on the tuner face plate, to facilitate individual oscillator adjustment; a 7ES8 RF amplifier; and a 9A8 mixer-oscillator. The two tubes are wired in series, and their voltage is obtained from a separate winding on the power transformer—a point to remember if both of them fail to light.


B+ voltage is obtained from the power transformer and two silicon rectifiers; protection for this circuit is provided by a thermistor and 5-amp fuse, series-wired in the primary winding of the transformer.

The IF frequency used in this receiver is in the 26-mc range, with the picture carrier appearing at 26.75 mc. After three stages of IF amplification, the signal is detected by two OA70 diodes (one for sound, one for video).

The horizontal sweep circuits (protected by an 8/10-amp fuse) include a 12BH7A AFC/oscillator, 6DQ5 output, 6AU4GTA damper, 3A3 rectifier, 6BK4 regulator, and a 1X2B focus rectifier. The high-voltage circuits and adjustments are similar to those in American-made color receivers. Connections to measure the current through the horizontal output and regulator tubes are conveniently located on the top side of the chassis; merely open the appropriate jumpers (marked on the chassis), connect your meters, and monitor the currents. (Various other color test points are marked on one of the photos.)

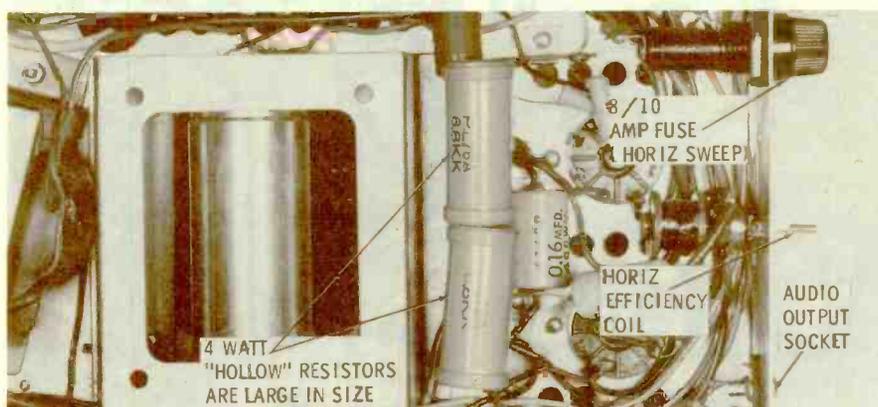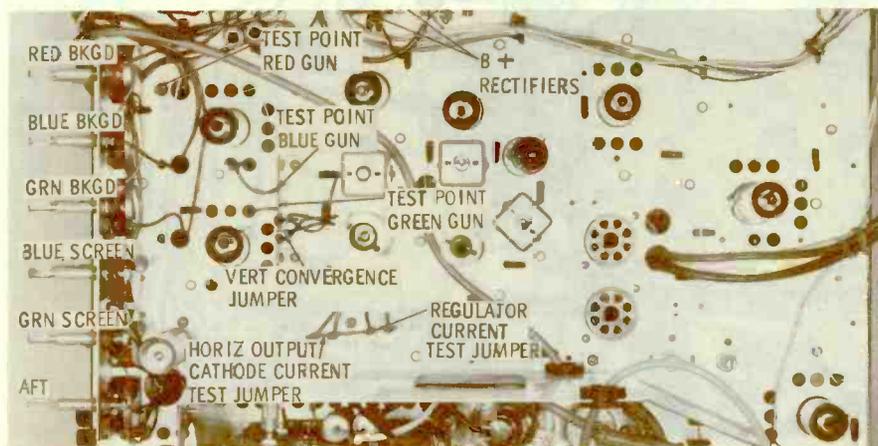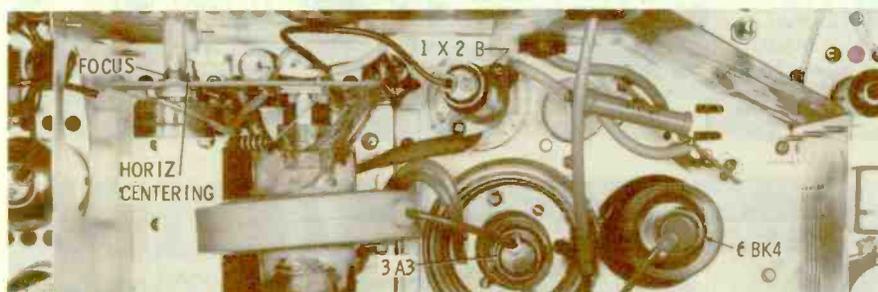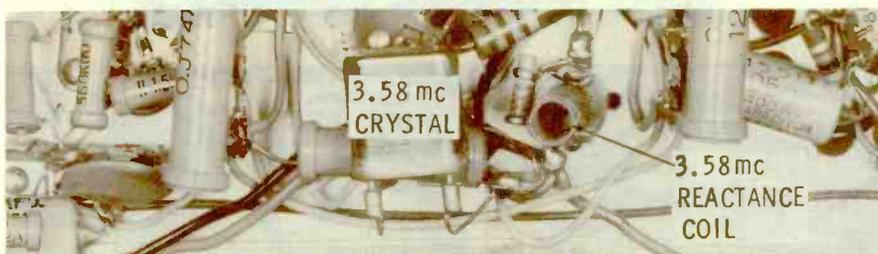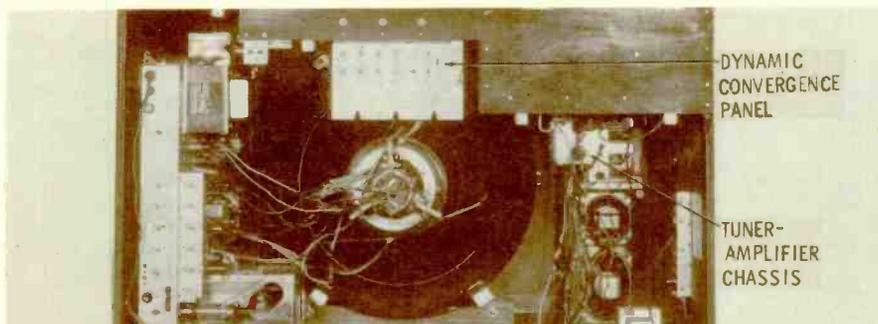The convergence procedures and components for this receiver are similar in every respect to those used in American equipment.



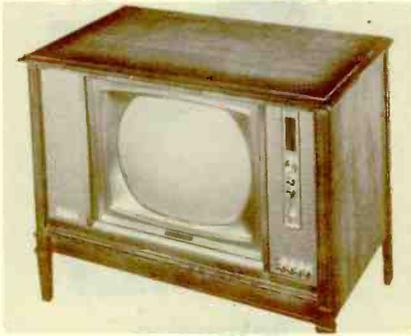

**Packard Bell Model 21CC4
Chassis 98C6**





This model comes equipped with a 21FBP22 color picture tube; others available in this line contain a bonded 21FJP22 CRT. The turret tuner utilizes a 6GK5 RF amplifier and a 6CG8A mixer-oscillator. A switch, mounted on the rear of the tuner shaft, completes an electrical path to the appropriate channel-indicator-light, each time the tuner is switched to a different channel. (The lamp panel is shown in one of the photos.)


An additional panel is mounted on the underside of the chassis to furnish a place for convenient field installation of a remote-control assembly. Two remote units, in kit form, are available for use in this set; mounting and wiring instructions are packed with the units.

B+ for this receiver is developed by a full-wave doubler circuit utilizing a power transformer and two silicon rectifiers. A thermistor protects the primary winding of the transformer, while a 3.5-amp fuse protects the B+ circuit from overload. Other protective devices in this chassis include a wire fuse for the main filament line (the CRT and voltage regulator tubes obtain filament voltage from a separate filament winding), and a 3/4-amp fuse for the horizontal sweep circuit.

The tube complement of the horizontal sweep stages is familiar: 6CG7 AFC/oscillator, 6DQ5 output, 6AU4 damper, 3A3 HV rectifier, 1V2 focus rectifier, and 6BK4 regulator. Tubes used in the color section are: 6U8A first chroma bandpass/color killer, 6AW8A second bandpass/burst amplifier, 6BN8 color sync phase detector/killer detector, 6GH8 chroma reference oscillator and control tube, 12AZ7 X demodulator/Z demodulator, 12BH7A B-Y/R-Y amplifier, and 12BH7A horizontal blanking/G-Y amplifier.

Operating controls for channel selection, fine tuning, brightness, color gain, hue, horizontal hold, vertical hold (killer threshold inside), contrast (vertical linearity inside), tone (height inside), and on-off-volume are mounted on the front of the cabinet. This set also has an internal brightness-range control mounted on the printed circuit board, under the 6AW8A video amplifier tube. Set this control in the following manner: Turn the brightness range full counterclockwise, turn up the external brightness to a point where the raster blooms, and then turn the range control clockwise to a point where blooming no longer exists; finally, return the brightness to a normal setting.

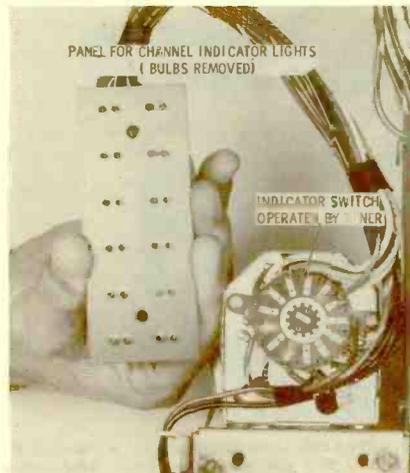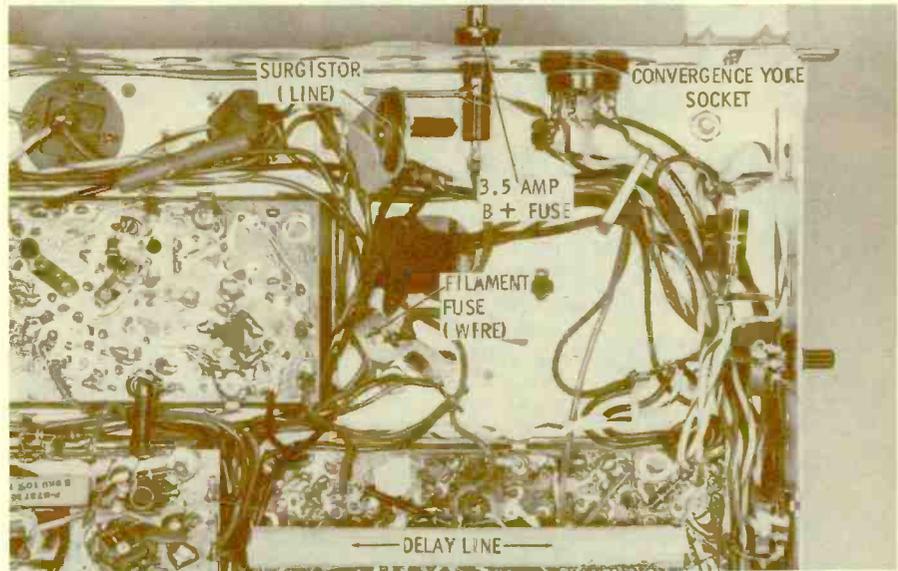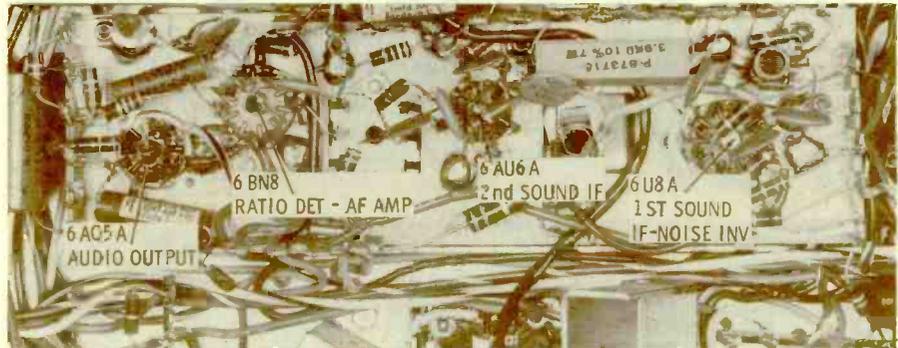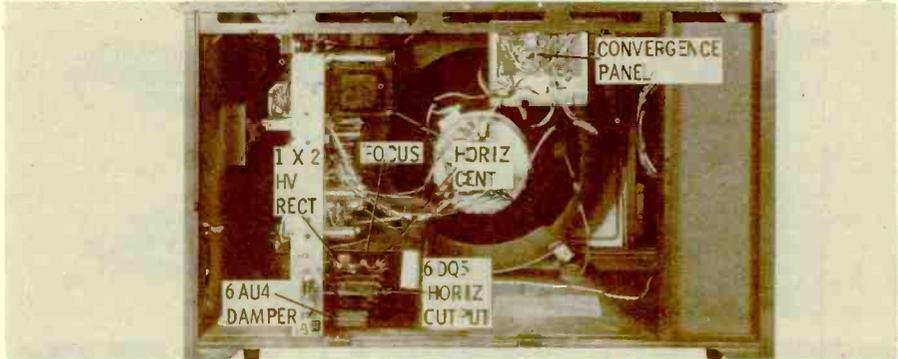

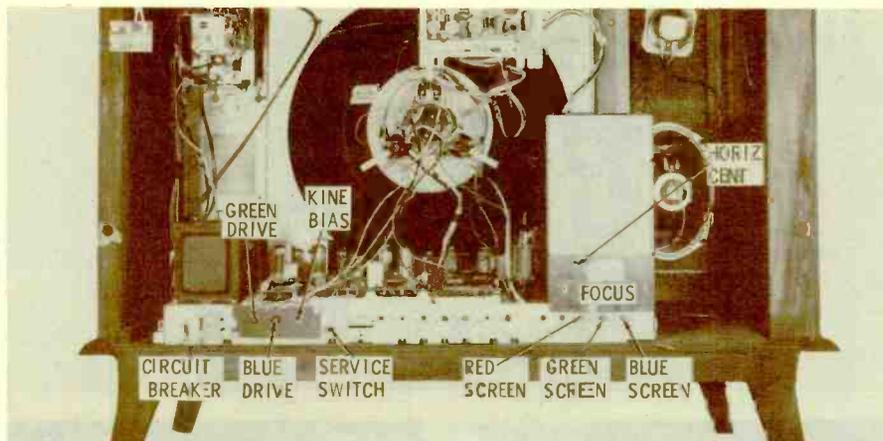

RCA Model 213G276MV Chassis CTC12A

All color receivers introduced by RCA for 1963 contain this new horizontally mounted chassis. A total of four printed-circuit boards hold the majority of the components in this set. The largest board contains all the color-signal stages, plus the video output tube (a 12BY7A).




This tube is the *third* amplifier following the video detector. The pentode section of a 6AW8A is used as the first video amplifier, and the triode section of this tube operates as a second amplifier stage for the luminance signal only; the chrominance and sync signals are taken off at the plate of the first video stage, as in previous RCA color sets.

A newly designed 6JU8 (containing four diode sections) is used as a chroma phase detector and killer detector; other color-circuit tubes which differ from those used in the CTC11 chassis include two 6GY6's as X and Z demodulators, a 6FQ7 R-Y/B-Y amplifier, and a 6FQ7 G-Y amplifier/blanker. The bandpass amplifier/color killer is a 6EA8.

B+ for this transformer-powered set is developed by two silicon rectifiers wired as a full-wave voltage doubler. Protection for this circuit is provided by a circuit breaker in series with the primary winding of the transformer. This winding has a 128-volt tap, to be used in areas of high line voltage. The main filament line is protected by a wire-link fuse; filament voltage for the picture tube and 6BK4 regulator is obtained from a separate winding on the transformer.

The width jumper which was connected to the yoke in this manufacturer's previous color receivers has been discontinued. Also, you'll find a new type of blue-lateral magnet mounted on the neck of the CRT (see photo). To position the blue beam horizontally, slide the magnet in or out of its sleeve.

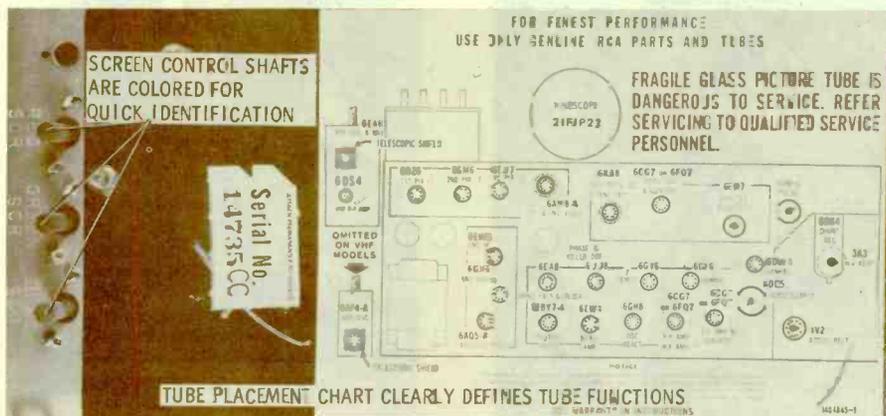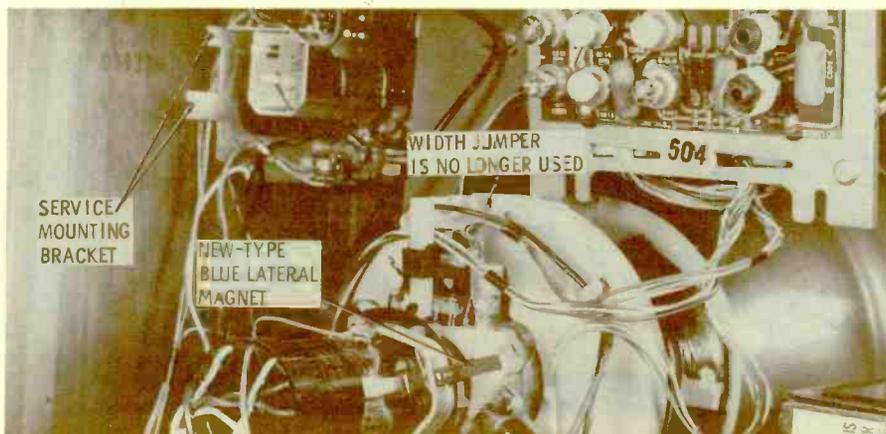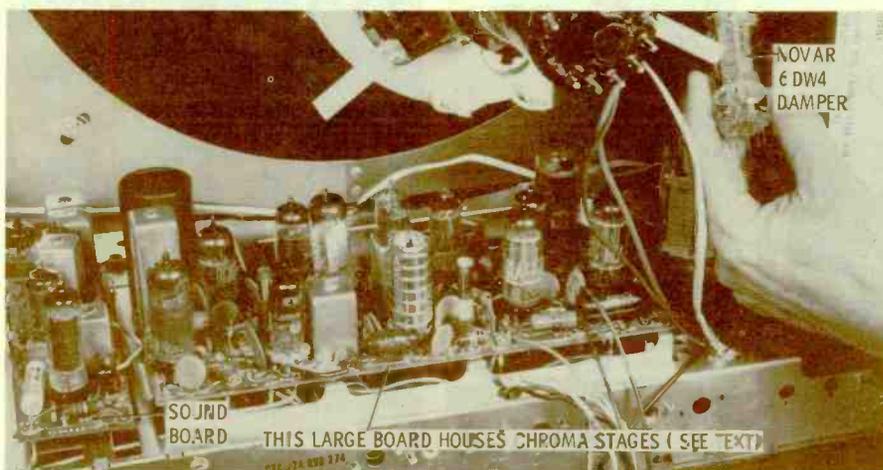The switch-type tuner makes use of a 6DS4 nuvistor (a new, remote-cutoff triode) and a 6EA8 mixer-oscillator. The tuner is mounted separately from the chassis in this receiver, but may be temporarily attached to a bracket on the left rear corner of the chassis to facilitate shop servicing.





Zenith Model 6015W

TV Chassis 27KC20Q

Remote Chassis S-56864

The metal-cabinet model shown here is one of the smallest sets available in the new color television line introduced by Zenith. It comes equipped with an all-transistor remote control having CHANNEL UP, CHANNEL DOWN, ON-OFF-VOLUME, and SOUND-MUTING functions. To prevent erroneous keying, the remote receiver is completely shielded; one of the pictures demonstrates removal of the shield.

The low voltage for this chassis is developed using a power transformer and a full-wave voltage doubler with two silicon rectifiers. Last year's chassis made use of two 3DG4's in this application. These rectifiers are mounted on the top side of the chassis, where they can easily be replaced without removing the chassis from the cabinet.

The receiver is protected by 3/10-amp B+ and 10-amp line fuses located on top of the chassis near the rectifiers, and a 5/10-amp horizontal-sweep fuse near the high-voltage cage.







A clamping diode, wired in the input to the Y amplifier, provides a controlled bias to this stage, and prevents picture blooming at high contrast and brightness settings.

The first color amplifier tube has been changed to a 6HL8, replacing the 6GH8 used in last year's models. This tube provides reserve gain for the color signals. In the vertical circuit you'll find a 6GL7, a cousin of the popular 6EM7 used in this circuit last year. Another new feature in the vertical circuit is the thermistor in the deflection yoke; it senses temperature changes and maintains vertical stability during warmup.

The width of the raster can be increased by moving the blue yoke lead (coming from the horizontal circuit) from the dummy connector on the chassis to the adjacent connector.

Auxiliary operating controls for brightness range and AGC are adjustable—with a screwdriver blade—through holes in the front control panel. A killer threshold control, new this year, is adjustable through the hollow shaft of the contrast control. Other controls adjustable through hollow control shafts on the front panel include the FRINGE-LOCK, inside the VERTICAL HOLD, and the HEIGHT, inside the BRIGHTNESS control.

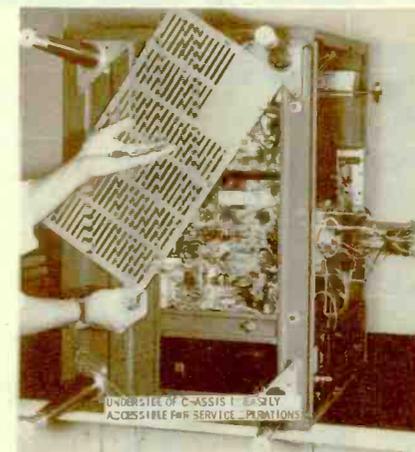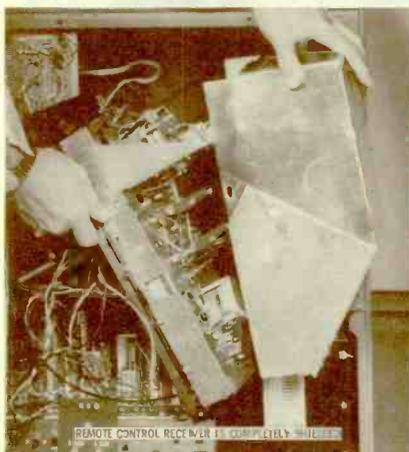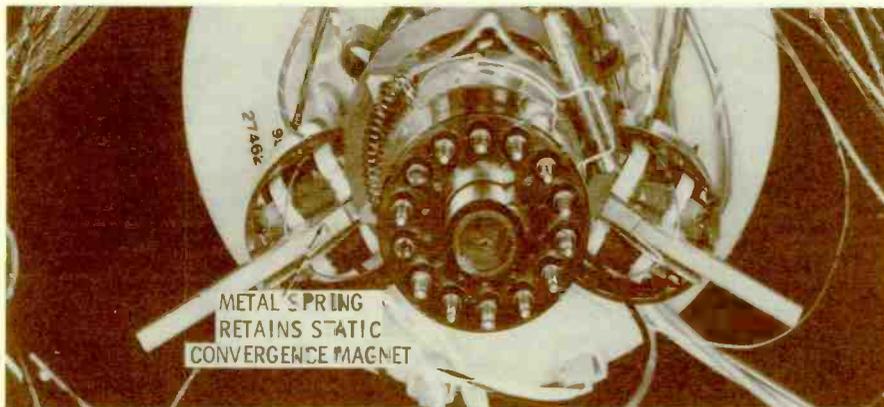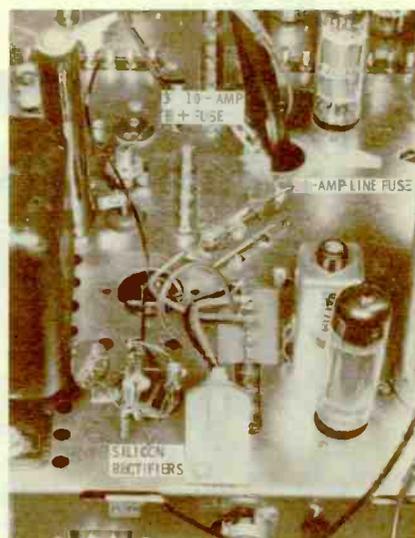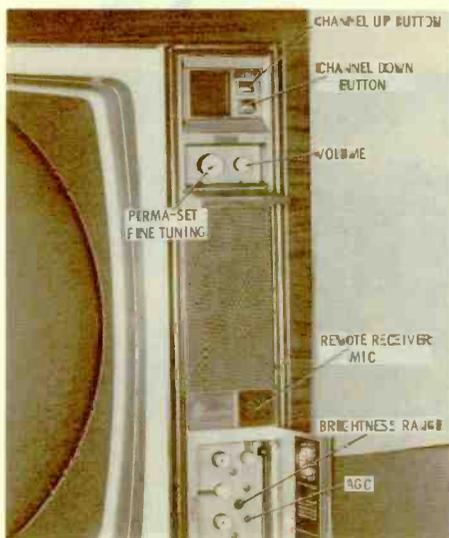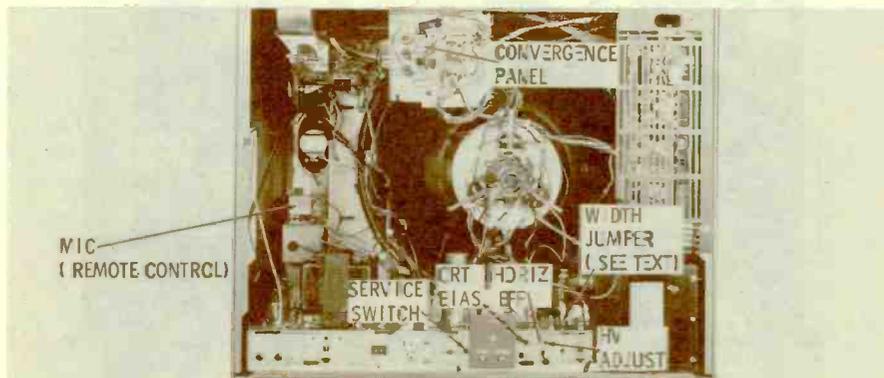The setup procedures for purity, convergence, gray-scale tracking and high voltage remain much the same in this chassis as in previous Zenith color receivers.



See PHOTOFACT Set 550, Folder 2

Mfr: RCA Chassis No. CTC11


Card No: RCA CTC11-1

Section Affected: Pix and Sync.

Symptoms: Excessive contrast and unstable sync—looks like video overloading due to AGC trouble.

Cause: Leaky screen-bypass capacitor in first video-amplifier stage.

What To Do: Replace C5 (2 mfd—350V).

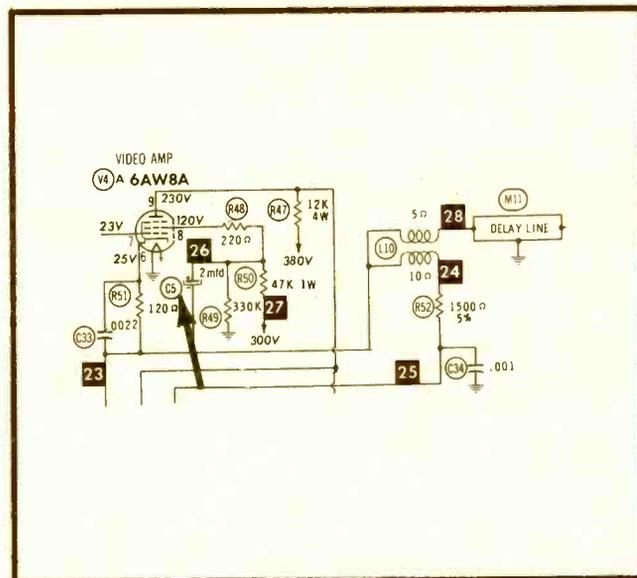

Mfr: RCA Chassis No. CTC11


Card No: RCA CTC11-2

Section Affected: Color.

Symptoms: Gradual loss of color.

Cause: Decrease in value of grid resistor in color-killer stage.

What To Do: Replace R131 (10 meg).

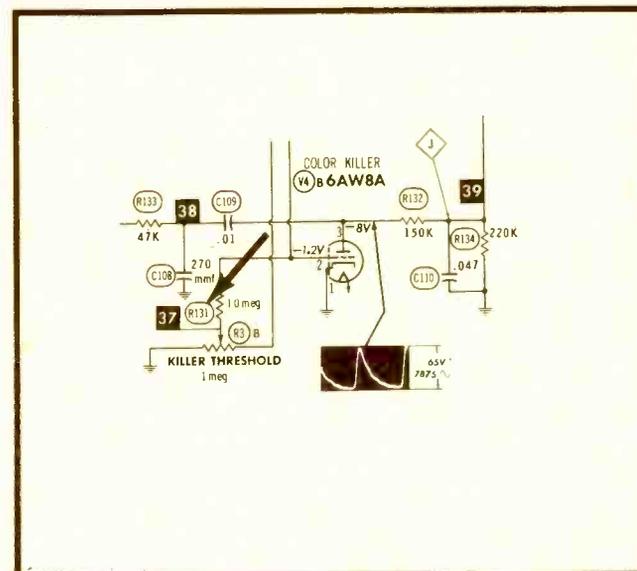

Mfr: RCA Chassis No. CTC11


Card No: RCA CTC11-3

Section Affected: Color.

Symptoms: Colors change during color program.


Cause: Color AFC circuits not properly adjusted.

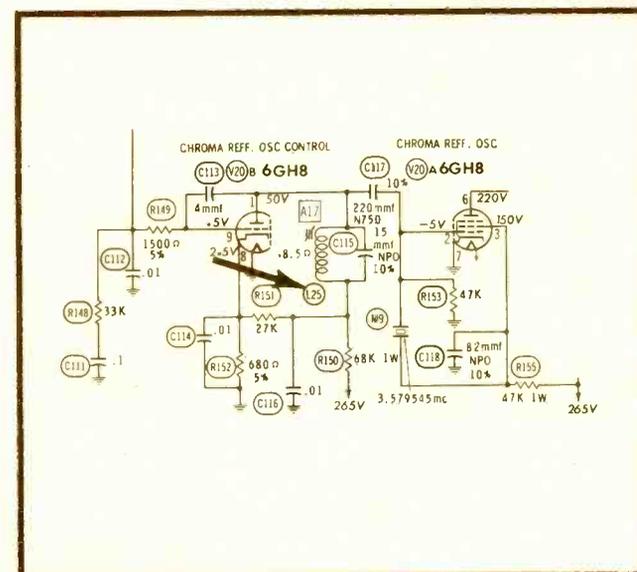What To Do: Ground TP1 (in chroma sync phase detector), and adjust reactance coil L25 for stable color presentation. Then unground TP1 and check tint control for proper setting. (This adjustment can be performed with chassis in cabinet.)



See PHOTOFACT Set 550, Folder 2

See PHOTOFACT Set 550, Folder 2

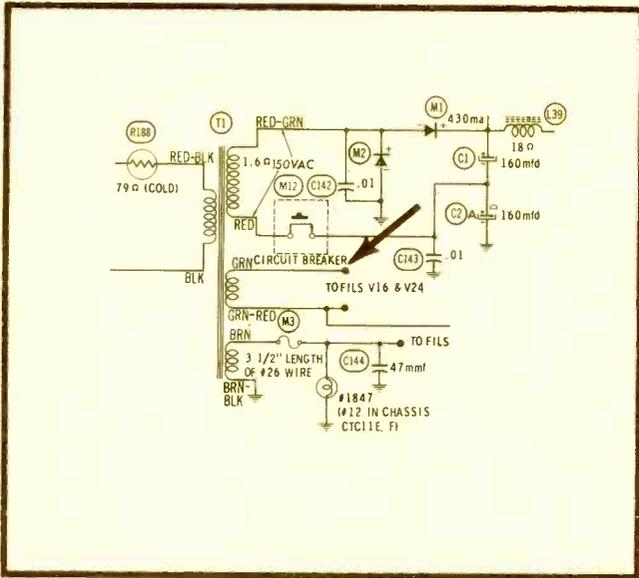

See PHOTOFACT Set 550, Folder 2

Mfr: RCA Chassis No. CTC11


Card No: RCA CTC11-4

Section Affected: Raster and Sound.

Symptoms: Circuit breaker opens at frequent intervals, interrupting B+ to all circuits. No shorts or arcing evident inside set.

Cause: Excessive voltage (steady-state or transient) on power line.

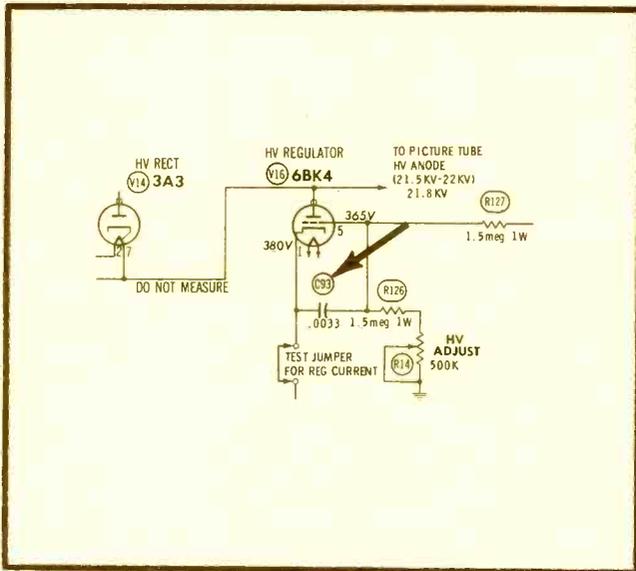What To Do: Check AC line for abnormally high supply voltage or sudden voltage fluctuations. In some cases, use of step-down line transformer is advisable.



Mfr: RCA Chassis No. CTC11


Card No: RCA CTC11-5

Section Affected: Raster.

Symptoms: Blooming and poor focus at high brightness settings. Horizontal-sweep and high-voltage tubes okay.

Cause: Intermittent short in capacitor connected between grid and cathode of HV shunt regulator.

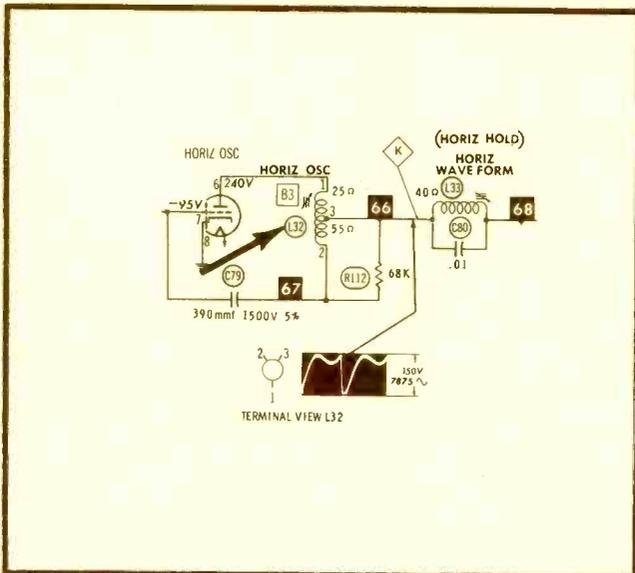What To Do: Check to see that leads of C93 (.0033 mfd) are not close enough together for a short to occur between them. If leads are not shorting, replace C93. Also replace V16 (6BK4).



Mfr: RCA Chassis No. CTC11

Card No: RCA CTC11-6

Section Affected: Raster.

Symptoms: Width decreases by 1" or 2" for short intervals, or rapidly jumps back and forth from normal to slightly narrow condition.

Cause: Intermittently shorted turns in horizontal oscillator coil.

What To Do: Replace L32.

See PHOTOFACT Set 599, Folder 2

Mfr: Zenith Chassis No. 29JC20,-Q


Card No: ZE 29JC20-1

Section Affected: Raster.

Symptoms: Insufficient width. Less than normal drive signal and DC bias voltage at grid of horizontal output tube.

Cause: Resistor in horizontal sawtooth-forming circuit changed in value.

What To Do: Replace R121 (33K).

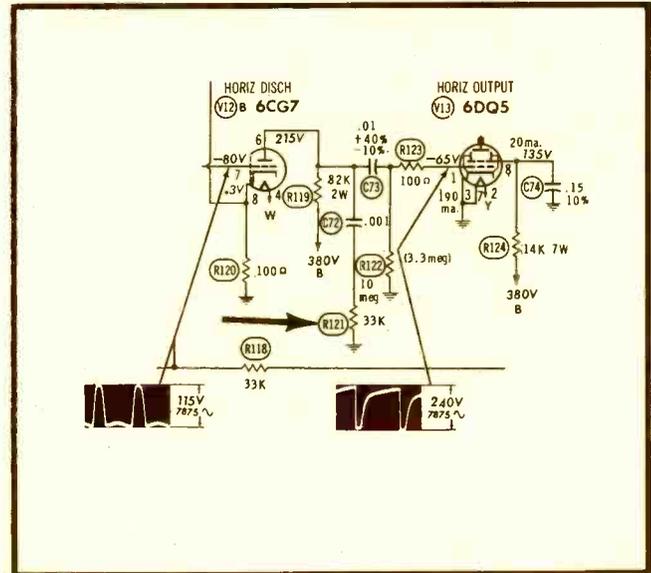

Mfr: Zenith Chassis No. 29JC20,-Q


Card No: ZE 29JC20-2

Section Affected: Color.

Symptoms: Loss of color. Low voltage at plate (pin 5) of burst amplifier V19 (6EW6); incorrect bias at grid (pin 8) of color-killer phase detector V20B (6BN8).

Cause: Leaky screen-bypass capacitor in burst amplifier.

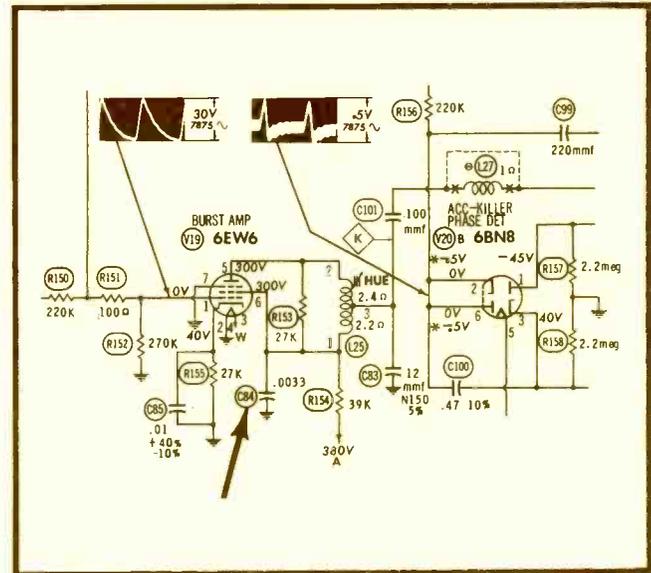What To Do: Replace C84 (.0033 mfd); also R154 (39K), which may have been damaged as a result of defect in C84.



Mfr: Zenith Chassis No. 29JC20,-Q


Card No: ZE 29JC20-3

Section Affected: Pix.

Symptoms: Picture tinted during black-and-white reception. Gray-scale tracking adjustments not effective. Tubes and voltages in video and chroma circuits all okay.


Cause: Defective 3.58-mc crystal.

What To Do: Replace M9.

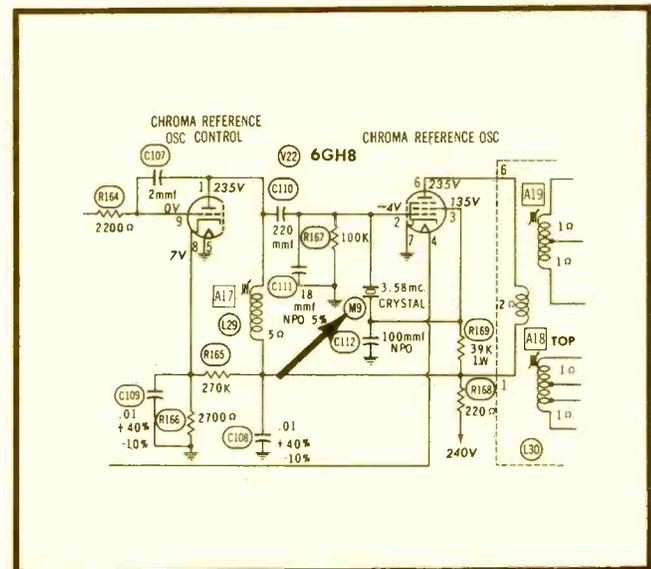

See PHOTOFACT Set 599, Folder 2

See PHOTOFACT Set 599, Folder 2

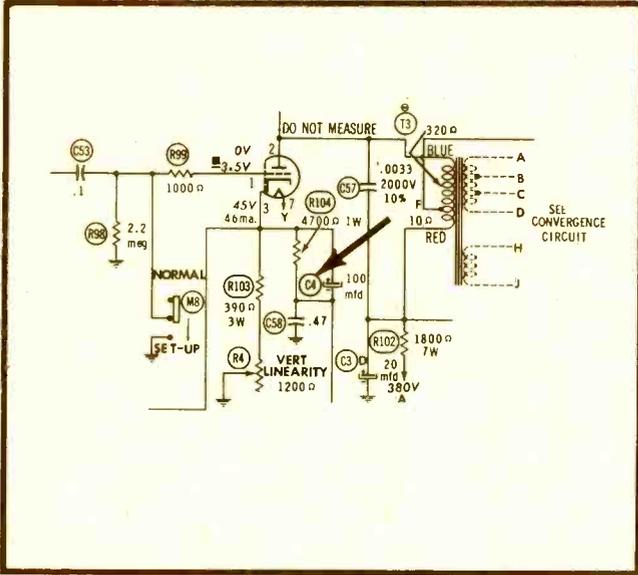

See PHOTOFACT Set 599, Folder 2

Mfr: Zenith Chassis No. 29JC20,-Q


Card No: ZE 29JC20-4

Section Affected: Raster.

Symptoms: Poor vertical linearity; also, in some cases, not enough vertical sweep.

Cause: Leaky cathode-bypass capacitor in vertical output stage.

What To Do: Replace C4 (100 mfd—50V).

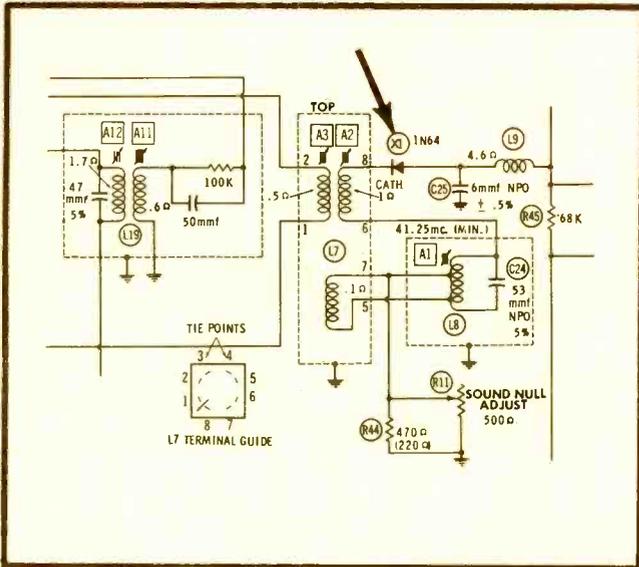

Mfr: Zenith Chassis No. 29JC20,-Q


Card No: ZE 29JC20-5

Section Affected: Pix.


Symptoms: Intermittent loss of picture—sound and raster not affected. All tubes and voltages okay; no loose connections.

Cause: Defective video-detector diode.

What To Do: Replace X1 (1N64).

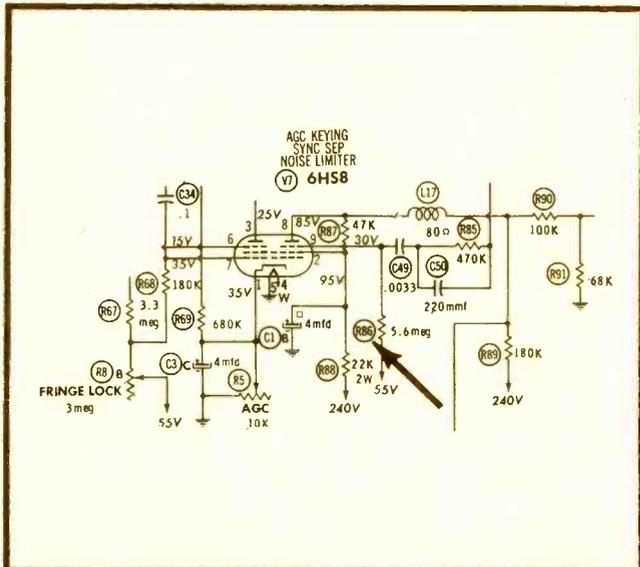

Standard Made It...

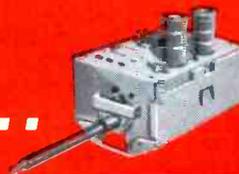

STANDARD CAN FIX IT BEST

\$11⁵⁰ Plus Parts . . . **\$13.50 Maximum Total Cost**

FREE Specially designed shipping cartons to prevent damage in transit

6 Months GUARANTEE

Only BRAND NEW PARTS Used • 48 Hour
Service on All STANDARD Tuners • Latest
Testing Techniques Assure Proper Alignment •
\$3.00 Defective Tuner Trade-in Allowance
Against a New STANDARD Replacement Tuner
Carrying a 12 MONTH GUARANTEE

IN TV IT'S *Standard*

STANDARD has maintained uniform mounting centers for the last 13 years. Over 50% of the TV sets in existence today have STANDARD tuners—in the case of most other tuners one of the 8 STANDARD replacement models can be easily adapted or will fit directly in place of these units. All STANDARD replacement tuners carry a 12 Month Guarantee.

**SEE YOUR AUTHORIZED
STANDARD DISTRIBUTOR**

MORE PROFIT FOR THE SERVICE DEALER • GREATER CUSTOMER SATISFACTION
GUARANTEED BY THE WORLD'S LARGEST TV TUNER MANUFACTURER

standard kollsman INDUSTRIES INC.

FORMERLY STANDARD COIL PRODUCTS CO., INC., MELROSE PARK, ILLINOIS

November, 1962/PF REPORTER 9



HOW TO BE SURE OF GOOD TV SERVICE...

1. Beware the Service "Bargain." If you shop around for cut-rate prices or extra-liberal service contracts, you're *asking* for trouble. A "something-for-nothing" offer usually means cut-rate parts and substandard service methods. The *reputable service dealer* spends years in study and training—thousands of dollars on test equipment, tools, and service manuals—countless hours in keeping up-to-date on new developments and service techniques. Because of this heavy investment, he can't *afford* to offer "bargains."

2. Rely on a Fully Qualified Independent Service Dealer. Well known and highly regarded by your friends and neighbors, his professional training and experience have made him a real technical expert. He takes pride in his work. He wants to stay in business. And he stakes his reputation and his future on satisfying *you*. So he'll use only component parts of the highest quality and latest design—plus his thorough knowledge and keen skills—to do the job right. Depend on him; he can't *afford* to let you down!

Your TV set provides you with a wealth of entertainment. Keep it in the best repair . . . at lowest cost . . . by calling your local TV-RADIO Service Dealer at the first sign of trouble!

THIS MESSAGE WAS PREPARED BY SPRAGUE PRODUCTS COMPANY,
DISTRIBUTORS' SUPPLY SUBSIDIARY OF SPRAGUE ELECTRIC COMPANY, NORTH ADAMS, MASSACHUSETTS FOR . . .

YOUR INDEPENDENT TV-RADIO SERVICE DEALER

68-342 R3

publisher
Howard W. Sams
general manager
Mal Parks, Jr.
editor
Verne M. Roy
managing editor
Forest H. Belt
ass't. managing editor
Thomas A. Lesh
associate editors
James F. Galloway
George F. Corne, Jr.
consulting editors
William E. Burke
Joe A. Groves
C. P. Oliphant

production manager
Robert N. Rippy
circulation fulfillment
Pat Tidd, Mgr.
Katherine Smith, Ass't.
Cora La Von Willord

art directors
Dick Lovell
Robert W. Reed

advertising & editorial assistants
Georgeanna Caldwell
Ruth E. Bastin
Paula Haffner
Ellie Rother

photography
Paul Cornelius, Jr.

advertising sales offices
John Groce, advertising sales manager

midwestern
Hugh Wallace
PF REPORTER
4300 West 62nd Street,
Indianapolis 6, Ind.
AXminster 1-3100

eastern
Charles Harner
Howard W. Sams & Co., Inc.
3 West 57th Street,
New York, N. Y.
MUrray Hill 8-6350

western
The Maurice A. Kimball Co., Inc.
2550 Beverly Blvd., Los Angeles 57, Calif.
DUmkirk 8-6178; and 580 Market Street,
Room 400, San Francisco 4, Calif. EXbrook 2-3365

Address all correspondence to
PF REPORTER, 4300 W. 62nd Street,
Indianapolis 6, Indiana



Copyright © 1962 by Howard W. Sams & Co., Inc.
PF REPORTER is a trademark of Howard W. Sams & Co., Inc. No part of PF REPORTER may be reproduced without written permission. No patent liability is assumed with respect to use of information herein. Acceptance of advertising does not in any manner signify the products, policies and services so advertised have been approved, endorsed or recommended by this magazine.
Subscription Prices: 1 year—\$4.00, 2 years—\$7.00, 3 years—\$9.00, in the U.S.A., its possessions and Canada.
All other foreign countries: 1 year—\$5.00, 2 years—\$9.00, 3 years—\$12.00. Single copy 35c; back copies 50c

Indexed in *Lectrodex*.
Printed by the Waldemar Press Div.
of Howard W. Sams & Co., Inc.



PF REPORTER

including **Electronic Servicing**

VOLUME 12, No. 11 **CONTENTS** NOVEMBER, 1962

Previews of New Sets	1
Delmonico Model CC-210 Packard Bell Model 21CC4 (Chassis 98C6) RCA Model 213G276MV (Chassis CTC12A) Zenith Model 6015W (Chassis 27KC20Q)	
Video Speed Servicing	5
Service hints on Zenith Chassis 29JC20 and RCA Chassis CTC11	
Letters to the Editor	12
The Electronic Scanner	20
Color-TV Service Aids	24
"Gadgets" that make the job easier and more accurate.	
Symfact Charts: Vertical Multivibrator—Control Circuits	29
See what happens to voltages and waveforms when troubles occur.	
Chroma Demodulator and Matrix Stages	32
Here's how you can signal-trace the circuits leading up to the CRT grids. <i>Thomas A. Lesh</i>	
Objective: Pure White	34
Quicker Servicing—A straightforward explanation that takes the hocus-pocus out of purity and convergence adjustments. <i>George F. Corne, Jr.</i>	
Meet a Color-TV Specialist	36
There is money to be made in color servicing. This man knows how.	
A Look Inside a Color-TV Station	38
A studio engineer prepares to put on a color show on the air. <i>Charles Guion</i>	
Interpreting Your Inventory	42
Dollar and Sense Servicing—Chart your needs and avoid piling up "dust-catchers." <i>Wayne Lemons</i>	
Color-TV Service-Charge Guide	50
Answering Customers' Color Questions	52
Lots of "troubles" can be fixed by conversation.	
How's Color TV Doing?	62
Read the facts concerning the rising tide of interest in color.	
Corona—In the Cage and Out	70
What is this strange wanderlust that sometimes possesses high voltage? <i>Stu Hoberman</i>	
Notes on Test Equipment	78
Lab Reports on the SENCORE Model PS120 Oscilloscope and the Electro Model EC-2 Power Supply. <i>Forest H. Belt</i>	
The Troubleshooter	84
Product Report	101
Free Catalog & Literature Service	104
Monthly Index	on free literature card

ABOUT THE COVER

There is no longer any doubt that color TV is alive and "on the move." Its progress in the past year has been substantial enough to make even the skeptics sit up and take notice. This issue, complementing last November's all-color special, contains valuable information for those already experienced in color work, as well as for those just beginning.



ATR PRODUCTS FOR MODERN LIVING



ATR PLUG-IN TYPE PORTABLE INVERTERS*

A. C. HOUSEHOLD ELECTRICITY Anywhere in your own car, boat or plane

Operates Standard A.C.
 • Record Players
 • Dictating Machines
 • Small Radios
 • Electric Shavers
 • Heating Pads, etc.
 In your own car or boat!

MODELS
 6-RMF (6 volts) 60 to 80 watts. Shipping weight 12 lbs. DEALER NET PRICE \$33.00
 12T-RME (12 volts) 90 to 125 watts. Shipping weight 12 lbs. DEALER NET PRICE \$33.00
 *Additional Models Available



ATR "A" Battery ELIMINATOR

For Demonstrating and Testing Auto Radios—TRANSISTOR or VIBRATOR OPERATED!
 Designed for testing D.C. Electrical Apparatus on Regular A.C. Lines—Equipped with Full-Wave Dry Disc-Type Rectifier, assuring noiseless, interference-free operation and extreme long life and reliability.

MAY ALSO BE USED AS A BATTERY CHARGER
 MODEL 610C-ELIF . . . 6 volts at 10 amps. or 12 volts at 6 amps. Shipping weight 22 lbs. DEALER NET PRICE \$49.95
 MODEL 620C-ELIT . . . 6 volts at 20 amps. or 12 volts at 10 amps. Shipping weight 33 lbs. DEALER NET PRICE \$66.95

AUTO-RADIO VIBRATORS



By every test ATR Auto-Radio Vibrators are best! and feature Ceramic Stack Spacers. Instant Starting, Large Oversized Tungsten Contacts, Perforated Reed, plus Highest Precision Construction and Workmanship and Quiet Operation!

There is an ATR VIBRATOR for every make of car!
 Ask your distributor for ATR's Low Priced type 1400, 6 volt 4-prong Vibrator; and 1843, 12 volt 3-prong; or 1840, 12 volt 4-prong Vibrator. THE WORLD'S FINEST!



ATR UNIVERSAL KARADIO MODEL 600 SERIES

Easily installed in-dash or under-dash. Amplifier power-supply chassis may be separated from tuner chassis for easy servicing. Utilizes 6-tube superheterodyne circuit (2 dual-purpose tubes). Supplied with separate 5" x 7" speaker. Neutral gray-tan baked enamel finish. Overall size 4" deep x 6 1/2" wide x 2 1/2" high. Tuner Chassis; with Amplifier Chassis, 2 9/8" deep x 6 3/4" wide x 3 7/8" high. Shipping weight 7 lbs. WILL OUT-PERFORM MOST SETS!
 Model 612—12 Volt, Dealers Net Price \$31.96
 Model 606—6 Volt, Dealers Net Price 31.96



Airplane Style Overhead Mounting under Cab Roof NO PRINTS/ CIRCUITRY

ATR TRUCK KARADIO

Excellent Tone, Volume, and Sensitivity!
 Compact, yet powerful. Fits all trucks, station wagons, most cars and boats. Just drill a 3/8 inch hole in roof and suspend the one-piece unit (aerial, chassis and speaker) in minutes. Watertight mounting assembly holds antenna upright. Yoke-type bracket lets you tilt radio to any angle.
 Extra-sensitive radio has 6 tubes (2 double-purpose), over-size Alnico 5 FM speaker for full, rich tone. Big, easy-to-read illuminated dial. Fingertip tuning control. Volume and tone controls. 33-in. stainless steel antenna. Neutral gray-tan enameled metal cabinet, 7 x 6 1/2 x 4 in. high over-all. Shipping weight 10 1/2 lbs.
 Model TR-1279—12A for 12V Dealer Net Price \$41.96
 Model TR-1279—6A for 6V Dealer Net Price \$41.96

See Your Electronic Parts Distributor Write Factory For Free Literature

ATR ELECTRONICS, INC.
 Formerly: American Television & Radio Co.
 Quality Products Since 1931
 ST. PAUL 1, MINNESOTA—U.S.A.

LETTERS TO THE EDITOR

Dear Editor:
 Your new *Symfact* is something I've wanted for years. I hope you enlarge on it, but it's a big help any way you look at it.

GERALD HESS
 Versailles, Ohio

Dear Editor:
 I'm pretty wild about your *Symfact* section on the 'BU8 in the September issue. I went through one of those circuits the hard way, just lately. Keep them coming!

M. P. WILLOUGHBY
 Olivehurst, Calif.

Dear Editor:
 I have just one word for *Symfact* — GREAT!

GERALD HOGAN
 Cleveland, Ohio

Dear Editor:
 Well done, on your *Symfact* feature. It's the best. I hope you carry through on all TV circuits. I'm going to save them and make a "Troubleshooter's Handbook" all my own.

FRANK D. MCCREERY
 Providence Forge, Va.

Dear Editor:
 I've just finished reading your *Symfact* on the 6BU8 sync separator. I think that is one of the best features you've had so far, although I find the entire magazine very good. I wouldn't be without it.

H. L. SMITH
 El Paso, Texas

Thanks, fellows. The response to *Symfact* has been overwhelming, and you'll be seeing one every month. Anything to please!—Ed.

Dear Editor:
 In the September article "Debugging B+," the center column on page 24 is doing battle with Fig. 2. It starts by saying, "On the negative half-cycle, M1 conducts as shown in Fig. 2A . . ." but the figure shows a positive half-cycle. Also, the arrows indicate electron flow, instead of current—I think. How about debugging the article?

BILL WHITE
 Princeton, Fla.

Simply exchange the input waveforms so that Fig. 2A shows the negative half-cycle, and Fig. 2B the positive one. Then all will be well. Incidentally, Bill, the arrows do indicate electron flow, since that's what happens when conduction takes place.—Ed.

Dear Editor:
 The September article "Calibrate Your Own Voltmeters" contains an error of omission. Mercury cells are available in two distinct voltages. In our line of batteries, single cells with an "R" suffix are 1.35 volts, while those without the "R" measure 1.4 volts. We make a mercury-type voltage-reference battery that has 1/2% accuracy. Also, the accuracy of any zinc-carbon is notoriously poor, because its voltage is radically affected by temperature, age, manufacturing tolerances, and all sorts of things. Even a brand-new one makes a poor voltage standard.

WM. F. MULLIN

Marketing Manager
 P. R. Mallory & Co., Inc.
 Indianapolis, Ind.

Thanks, Bill, for bringing these facts to our attention. This is the sort of information our readers can really use.—Ed.

Dear Editor:
 We enjoyed your "And They Say Servicing is Fun?" article. I read it aloud to my wife, and we laughed till tears came to our eyes. We especially liked the part about the man watching the little line and hoping something would happen. The lady with the transistor radio was comical, too.

KENNETH WAGNER

There is a lot of truth in the article about the headaches of a serviceman, but when you can read about them and laugh, the job seems a lot easier.

It's guys like "Charlie" who keep the service business alive, Ken. Glad you enjoyed the story.—Ed.

Dear Editor:
 I've been trying for some time to locate a couple of pieces of test equipment; perhaps your readers could help. I know they're not built any more, but I'd like to find a Chanalyst or a Hickok Traceometer—both are tunable signal tracers. Got any idea where I can find them?

MERTON JONES

Newark, N.J.



Tarzian offers

FAST, DEPENDABLE TUNER REPAIR SERVICE



ALL
MAKES

It just makes sense that a manufacturer of tuners should be better-qualified, better-equipped to offer the most dependable tuner repair and overhaul service.

Sarkes Tarzian, Inc., pioneer in the tuner business, maintains a complete, well-equipped Factory Service Dept.—assisted by Engineering personnel—and staffed by specialized technicians who handle ONLY tuner repairs . . . on ALL makes and models.

Tarzian-made tuners received one day will be shipped out the next. There is a 12-month guarantee against defective workmanship and parts failure due to normal usage. And compare our cost of \$8.50 and \$15 for UV combinations. There is absolutely no additional, hidden charge for ANY parts except tubes. Replacements available at low cost on tuners beyond practical repair.



Tarzian-made tuners are identified by this stamping. When inquiring about service on other tuners, always give tube complement . . . shaft length . . . filament . . . voltage . . . series or shunt heater . . . IF frequency . . . chassis identification. All tuners repaired on approved, open accounts. Check with your local distributor for Sarkes Tarzian replacement tuners, replacement parts, or repair service.

SERVICE MANAGER • TUNER DIVISION • DEPT. 3A



SARKES TARZIAN INC

east hillside drive • bloomington, indiana
edison 2-7251

MANUFACTURERS OF TUNERS . . . SEMICONDUCTORS . . . AIR TRIMMERS . . . FM RADIOS . . . AM-FM RADIOS . . . AUDIO TAPE . . . BROADCAST EQUIPMENT

ONLY
\$850
INCLUDING

ALL PARTS
(EXCEPT TUBES)
and LABOR

24-HOUR SERVICE
1-YEAR WARRANTY

**Tuners Repaired on
Approved, Open Accounts**

**See your distributor, or
use this address for fast,
factory repair service**

NEW ELECTRONIC NUVISTOR
FM ANTENNA FOR LONG-
DISTANCE FM AND STEREO!

World's
most powerful
FM Antenna—
positively improves
FM set
performance!

Winegard

STEREOTRON

WITH ELECTRONIC AMPLIFIER

Responds to Weakest Signals But Strong Signals Won't Overload It

(Takes Up to 200,000 Microvolts of Signal Input)

This is the world's most powerful antenna for FM or FM stereo. With the Stereotron and Stereotron amplifier, Winegard GUARANTEES unexcelled performance, GUARANTEES you will receive 85% of all FM stations in a 200 mile radius. The Stereotron, with powerful nuvistor amplifier, has a minimum gain of 26 DB over a folded dipole, with a flat frequency response of $\pm 1/4$ DB from 88 to 108 MC.

With nuvistor amplifier, Stereotron is so sensitive it will pull a 1 microvolt signal out of the noise, yet signals as strong as 200,000 microvolts will not overload the amplifier and cause it to cross modulate. This extraordinary performance is due to a unique amplifier circuit employing 2 RCA nuvistors.

Uppermost in the minds of the engineers in developing the Stereotron amplifier were two things—1. A new high in performance. 2. Long life and trouble-free operation. For example, the life of the 2 RCA nuvistors will be 5 to 8 years at top performance. This is possible because of a heat sink to control operating temperature and an automatic voltage control. A completely weather-sealed

case protects all amplifier parts from rust and corrosion. The antenna is beautifully gold anodized—100% corrosion proofed. Available both for 300 ohm or 75 ohm coax.

SF-8 Stereotron FM Antenna \$23.65

AP-320 Stereotron Nuvistor Amplifier \$39.95—amplifier can be purchased separately to use with any FM antenna.

READ WHAT USERS SAY—


"The results have been so outstanding under less than ideal conditions, I felt you might be interested. It was truly amazing how a previously blank dial sprang to life."

C. M. S. Elmira, New York

"I now get as strong a signal from out-of-town stations as I get from 'locals'. I told a radio and TV man in Hollister about my reception and invited him over to hear it!"

M. J. D. Hollister, Mo.

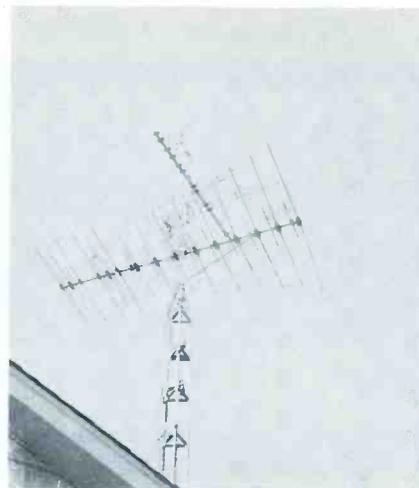Write for information or ask your dealer for spec sheets on Stereotron and other Winegard FM and TV antennas and accessories. Get FREE Station Log and FM map of U. S.




Dear Editor:

I thought you might be interested in this unusual antenna installation. We installed it for one of our customers who wanted to have a separate antenna for his children's set. He said he wanted it as compact as possible, and left the rest to us. The thing that complicated this problem was the fact that each antenna had to have its own rotator. The photo shows the arrangement we came up with. The topmost antenna is mounted on a 3/4" pipe, which runs through the pipe of the lower antenna and the upper rotator, and is turned by the lower rotator. The bottom antenna is mounted on a 1/4" pipe, large enough for the other to fit inside, and is turned by the top rotator.

J. EMBER

York, Pa.

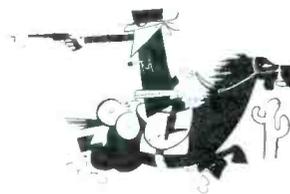Just goes to show what a little "Yankee" ingenuity can accomplish.—Ed.



Moving to a New Location?

If so, notify us by the 15th of the month to assure uninterrupted delivery of PF REPORTER.

Please be sure to give us both your old and new address, including your postal zone number. (Or better yet, enclose a current mailing label with your new address.)

Send to:

PF REPORTER

4300 W. 62nd St.
Indianapolis 6, Ind.



Winegard

ANTENNA
SYSTEMS

3009-11 Kirkwood Boulevard • Burlington, Iowa



are you replacing top quality tubes with identical top quality tubes?

You can, now! You can carry the identical tubes that you find in most of the quality TV sets you're servicing. Chances are, you were not aware that these sets were designed around special Frame Grid tubes originated by Amperex.

For some time now designers have been using many Amperex Frame Grid tubes in their quality TV receivers and we can tell you now that even more Amperex tubes are being designed into the sets you'll be handling in the future.


Compare, if you will, the performance of Amperex Frame Grid tubes with conventional IF tubes: they provide 55% higher gain-bandwidth, increase TV set reliability by simplifying circuits and they make your servicing easier, faster and more profitable because their extraordinary uniformity virtually eliminates time-consuming realignment when you replace tubes. Technicians are finding Amperex THE line to carry.

Tubes introduced by Amperex and currently being used by major TV set makers include:


—Frame Grid—				—Others—	
2GK5	4GK5	6GK5	6EH7	6AL3	9A8
2ER5	4EH7	6ES8	6EJ7	6BL8	15CW5
3GK5	4EJ7	6ER5	6HG8	6BQ5	16AQ3
3EH7	4ES8	6FY5	7HG8	12AX7	27GB5

For optimum customer satisfaction and maximum profit operation for yourself, make room in your caddy right now for the identical, matchless-quality tubes designed into the original sets. Next time you visit your distributor look for the green-and-yellow box and ask about Frame Grid tubes for TV and other entertainment replacement applications. Amperex Electronic Corporation, 230 Duffy Ave., Hicksville, L. I., N. Y. In Canada: Philips Electron Devices Ltd., 116 Vanderhoof Ave., Toronto 17.

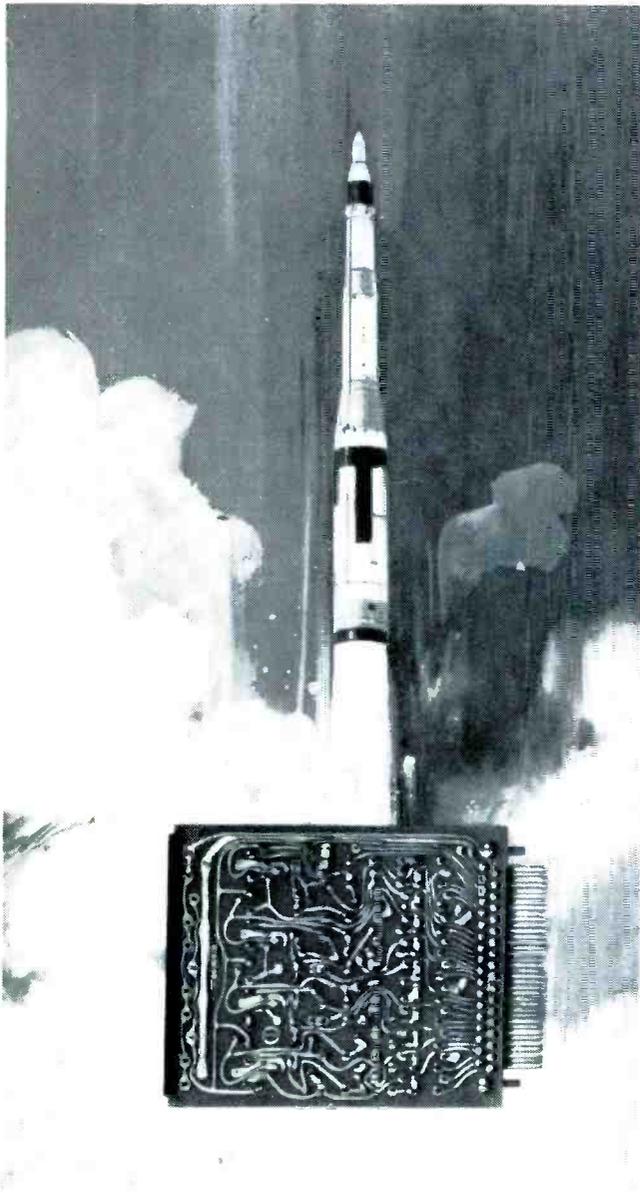This advertisement in the November Reader's Digest sealed circuits are the vital nerve systems for



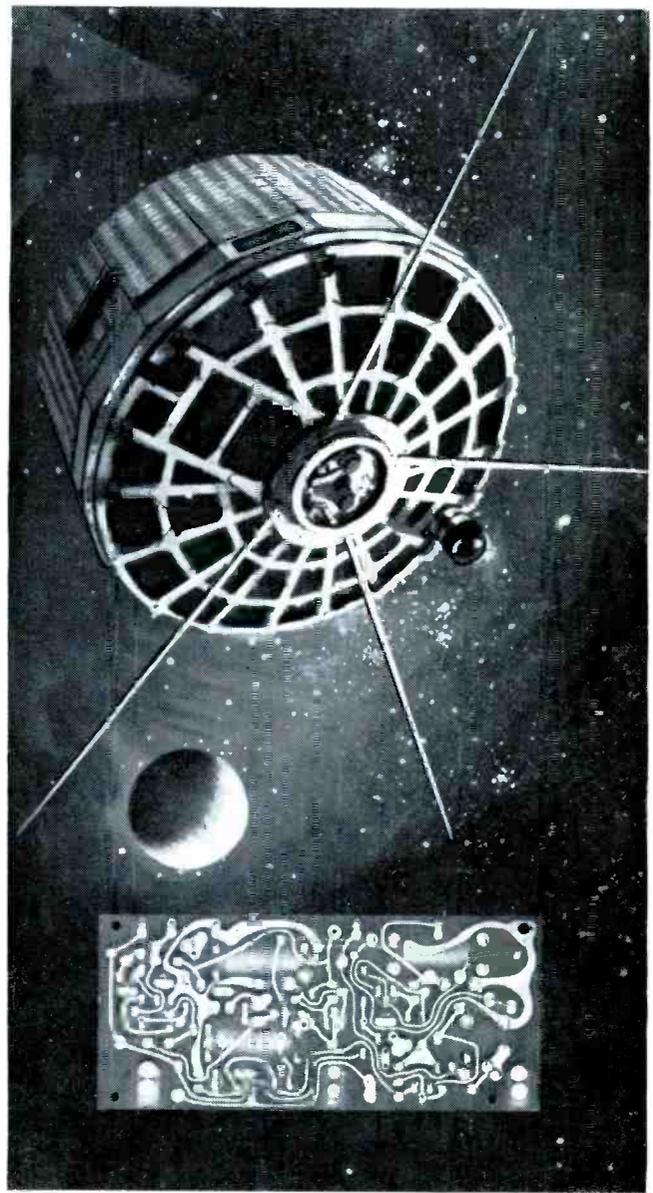RCA sealed circuit modules are used in the computer and communications of the U.S. Air Force Minuteman launching system, making possible high density of components, ease of maintenance, and rugged, reliable performance.



All five TIROS weather satellites, developed and built by RCA under the technical direction of Goddard Space Flight Center of NASA, have exceeded original goals; their lives enhanced by RCA-designed sealed circuitry.

How New Ideas in Sealed Circuitry

The circuit boards you see above are one of science's modern miracles used in satellites, space capsules, computers and TV sets. They differ in size—and design—and complexity—for their respective needs. But each one is the result of

science's search for the utmost in reliability and efficiency. Precision-crafted sealed circuit boards eliminate old-fashioned hand-wiring and hand-soldered connections that can come loose or short-circuit. These modern circuits are etched

shows millions of Americans why Precision-Crafted the marvels of the Space Age... and today's TV



Electronic Computers such as the RCA 301 calculate data at fantastic speed for American defense, and all phases of industry and communications. Their electronic hearts are sealed circuit boards



Color TV instructs, informs, as well as entertains millions. Here, the reliability of RCA Security Sealed Circuit Boards* has been proved for eight long years in homes like yours from coast to coast.

are Changing Our Daily Lives

in copper which is permanently bonded to boards, protecting them from heat and moisture.

**In the early days of television, RCA, like all other manufacturers, had to depend on all hand-wired circuitry. Today for greater pre-*

cision and reliability, two-thirds of RCA Victor TV circuitry is bonded on Security Sealed Circuit Boards.



The Most Trusted Name in Electronics
Tmk(s)®


Sylvania—first with the Sarong and Bikini cathodes—now announces a new development that significantly increases the reliability of Sylvania tubes. "LIFE-Boost Cathode" is the name... the secret is an ultra-pure, uniform alloy made possible by Sylvania's leadership in powder metal technology.

Contrasted to conventional melted alloys, the LIFE-Boost powder-metal alloy is so pure and uniform, with performance so predictable, that it eliminates any need for the usual "melt approval." Alloy uniformity inhibits the formation of leakage paths, which extends tube life. It also means

better-controlled electron emission and regulated barium release throughout life—tube performance stays within specifications. Further, the new cathodes have 25% greater mechanical strength, which significantly reduces equipment failure in the field.

Precise control of alloy composition is the key. The basic pure nickel powder plus carefully controlled powdered reducing agents are thoroughly blended and immediately rolled into thin-gauge strip. Because no critical temperatures are involved, no impurities are introduced from crucibles and con-

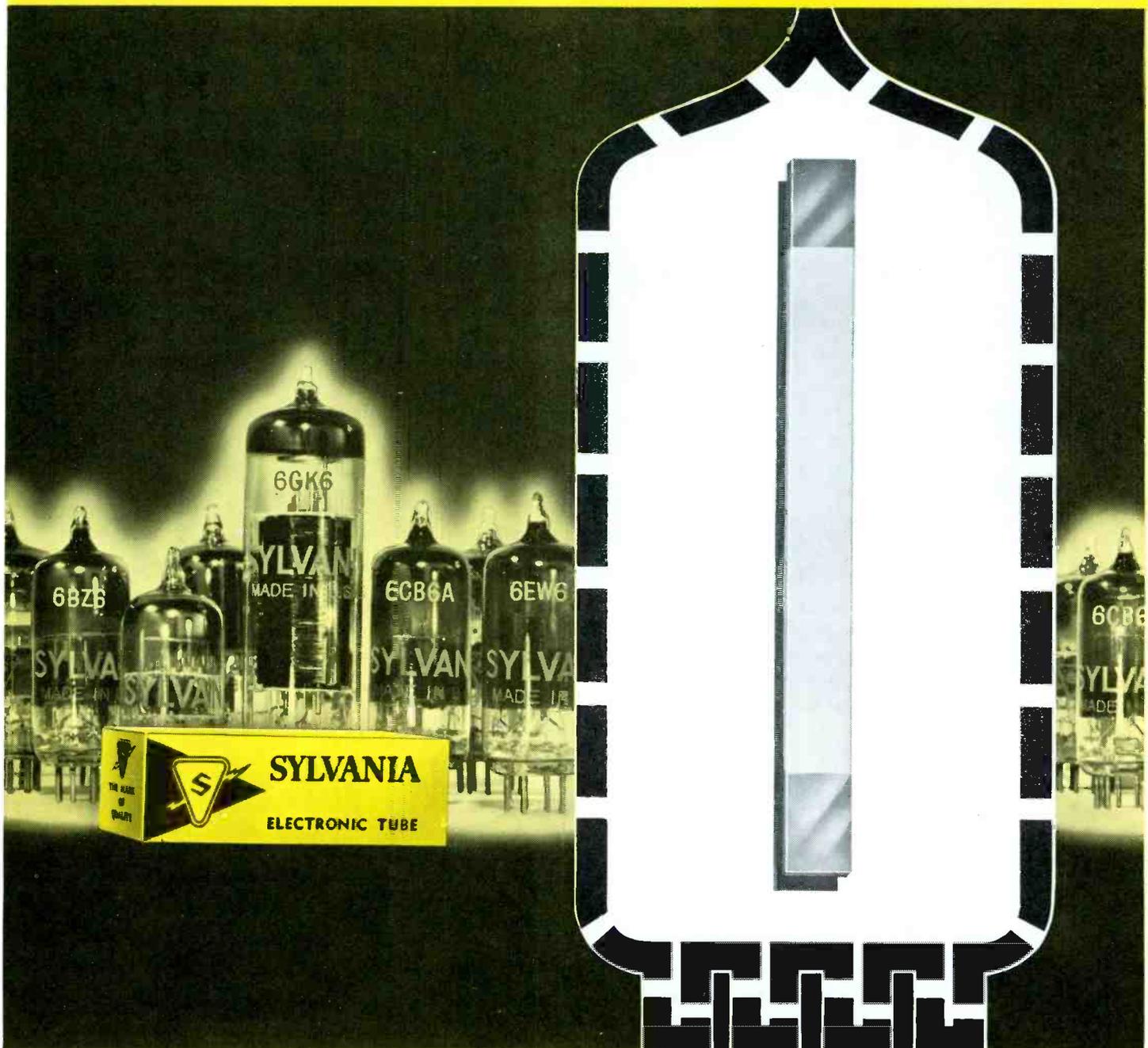
New Sylvania LIFE-BOOST* Cathode dependability—fewer callbacks, more



ainers, forging hammers or hot-rolling equipment. And the powder process permits previously impossible or hard-to-attain combinations of wanted properties, such as electrical passivity and mechanical strength at high temperature.

A planned conversion of Sylvania tubes to the LIFE-Boost Cathode is under way. See your distributor for dependable Sylvania tubes—the only ones with this new development that means fewer callbacks, more profitable servicing.

means greater profitable servicing

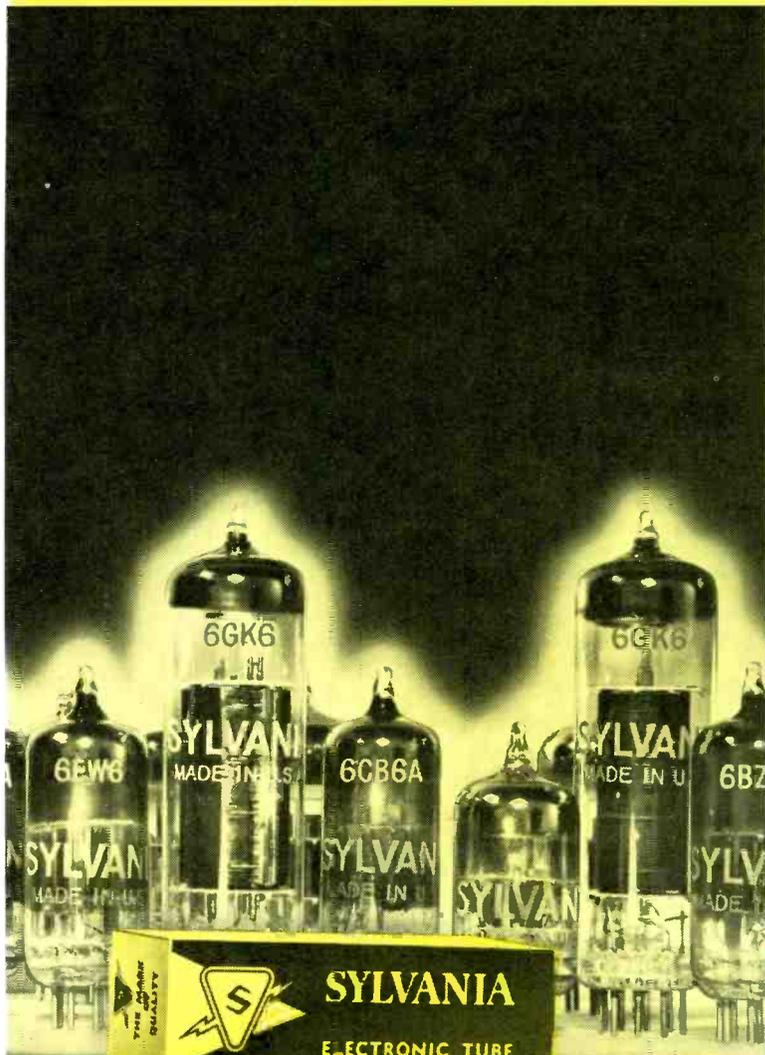

MORE THAN 80 TYPES already have the LIFE-BOOST Cathode. Here's evidence of what it can do:

...In 6DZ4 UHF oscillator:

No failures, greatly improved stability

Test: 40 tubes operated at 130 VAC for 1500 hours in 40 TV sets (4 models, 3 manufacturers represented).

Failures: None resulting in set failure. (Statistical estimate: 1% per 1000 hours at 130 V, or about 0.3% per 1000 hours at 117 V.) Failure rate for same tube made with conventionally prepared cathode material: 13.1%.

Oscillator Grid Current: After 1500 hours at 130 V, 90% of LIFE-Boost Cathode tubes had grid current between 550 and 950 μ A. Only about 38% of the tubes with conventional cathodes remained within these limits after period of test.

...in 6GK6, used for critical vertical output: TV set manufacturer reports improved stability

Test: More than 1000 hours at 135 VAC line.

Results: No leakage problems, no slump in characteristics; tube can be used in vertical socket as well as other sockets of customer's TV set line.

Sylvania tests show significantly reduced sublimation (formation of leakage paths), and improved plate current stability under accelerated life test and heater cycling conditions with over-voltages applied.

...in RF pentodes:

Reduced grid emission, no insulation breakdown

RF pentodes BZ6, CB6, EW6 and others, when subjected to life testing, showed reduced grid emission levels after conversion to the LIFE-Boost Cathode. Insulation levels during and at the completion of life showed little or no change—an indication of improved stability—and end-point failures due to breakdown were virtually nonexistent.

REMEMBER—many Sylvania Distributors give S&H Green Stamps when you purchase Sylvania Receiving Tubes. S&H Green Stamps are America's most valuable stamps and are exclusive with your participating Sylvania Distributor.

®Trademark


SYLVANIA

SUBSIDIARY OF

GENERAL TELEPHONE & ELECTRONICS



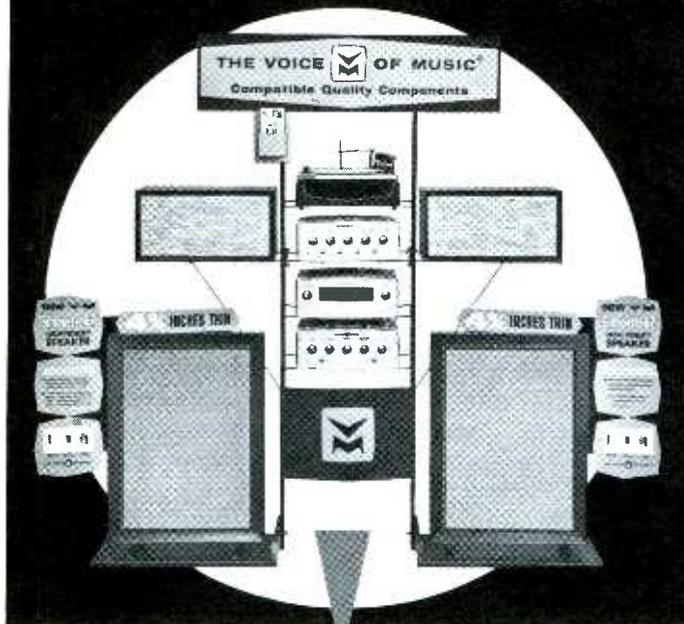ADD NEW PROFIT TO YOUR HI-FI COMPONENTS BUSINESS THE EASY V•M WAY!



- Priced to attract *new* customers, this complete line of quality components is effectively displayed and demonstrated in only 5 square feet.
- Convenient one-source buying . . . backed by V•M's national network of Service Centers.



The store display fixture is complete with literature dispenser and the "Silhouette 62" speaker feature posters. It actually displays nine V•M component products!



'Stere-O-Matic'® 4-Speed Automatic Record Changer Model 1571 11" turntable.

Automatic Manual-Play, Extra-long, dynamically balanced, non-resonant Tone Arm. Diamond Needle. Shadowlite stylus pressure.



Changer Base Model 1438. For 'Stere-O-Matic'® Changers. Pre-wired receptacles.



Stereophonic High-Fidelity Component Amplifier Model 1428. 60 watts (peak); 30 watts per channel, Frequency response, 20-30,000 cps.



High-Fidelity FM Stereo, FM, AM Component Radio Tuner Model 1465.



Precision-Built AC Stereo Amplifier Model 1448. 40 watts (peak); 20 watts per channel. Frequency response, 40-25,000 cps.



"Silhouette 62" High-Fidelity Component Speaker System. Three speakers: 10" woofer, 6" mid-range, 3.5" tweeter. Frequency response, 30-16,000 cps.




High-Fidelity Component Speaker Model 32. Three speakers: Two 6" and one 3". Frequency response 60-12,000 cps.

YOUR V•M DISTRIBUTOR IS READY NOW TO GIVE YOU ALL THE DETAILS AND POINT OUT THE MANY ADVANTAGES OF THIS NEW V•M COMPONENTS LINE. CALL HIM TODAY!



V•M CORPORATION • BENTON HARBOR, MICHIGAN

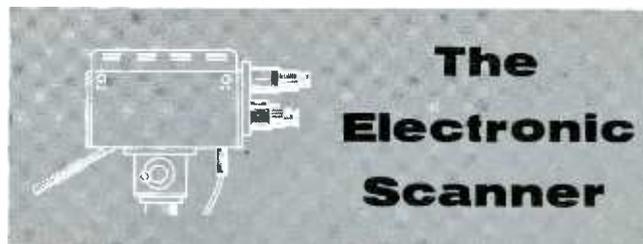KNOWN FOR THE FINEST IN RECORD CHANGERS, PHONOGRAPHS AND TAPE RECORDERS



The Electronic Scanner

"Time-Saving" Service Clinics



Touring the country for SENCORE these days is Wayne Lemons, shown here (center) with the firm's President Herb Bowden (right) and Chief Engineer Bob Baum. Some of the clinics Wayne will conduct this month, telling the SENCORE "Time-Saving Program" story, will be sponsored by National Radio Parts and Bay Electronic Distributors, Brooklyn (Nov. 12th); K-R Services, Inc., Newark (Nov. 13th); Slate and Company, Bronx (Nov. 14th); and H. L. Dalis, L.I.C., (Nov. 15th). Of course, you all recognize Wayne as author of two recent Sams books, "Transistor-Radio Servicing Made Easy" and "Servicing Horizontal Sweep Circuits."

Color Servicing Course



Color-TV servicing schools are now being held at local Admiral distributors throughout the country by factory Field Engineers and color specialists, under the direction of Mr. I. F. Johnston, National Electronic Service Manager. Mr. Willis Wood, General Manager of the National Service Division, pointed out that the Admiral Color Schools consist of approximately 3 hours of lecture and 5 hours of actual workshop. Arrangements for attendance can be made through the Admiral distributor in your area.

Tape-Head Replacement Program

To help dealers cut stock requirements, Nortronics has introduced "Quik-Kit" mounting hardware for their line of replacement tape-recorder heads. The new hardware kits include any electrical components needed, along with detailed installation instructions and drawings. Parts for more than 250 models of recorders are included in the program, and others will be added periodically. The company is now conducting an extensive national advertising campaign to build consumer demand for replacement heads.

Dynamic Service Demonstrator



Transistor-radio servicing and troubleshooting techniques can be demonstrated effectively with a new training aid from Motorola. This device is in a fold-open carrying case which, when opened, reveals a circuit diagram of a complete transistor radio with working components mounted on it. The large size makes possible demonstration, illustration, and direct application of service techniques to large groups. All components are removable and are identified by their functions and values. Training sessions, using the new aid, can be arranged through local Motorola distributors.

New Facilities for Color-TV Tube Production

A 45,000-square-foot addition, to be devoted to color-TV picture tube production, will soon be added to the Chicago plant of National Video Corp. The new addition should be completed in December of this year. As soon as rectangular glass envelopes become available, the company expects to produce rectangular color CRT's. They also plan to make 90° color tubes that will be 5" shorter than 70° types now in use.



©1962 VOLKSWAGEN OF AMERICA, INC. *SUGGESTED RETAIL PRICE.

Our truck is a big tool box.

You can load up a VW Truck with 1,000 lbs. of tools or parts or equipment. And still have room for 800 lbs. more.

Our truck will actually tote 1,830 pounds; 800 more than a half ton.

Yet, the VW is 3 feet shorter and weighs only half as much as a half ton.

It's our boxy shape that does it.

Outside, the VW doesn't have a long front hood. Because our engine's in the rear. For extra traction.

Inside, there's 170 cubic feet of usable space. With a 4-foot-wide side doorway. And double side doors. And a rear door. (And, if you want it, another side doorway in the far side for 80 bucks* more.)

Anderson & George Murray of Orleans, Mass., carry a big table saw over the engine in back of their VW.

They also carry so many tools and stuff that people have said: "It looks like you have the shop right in the truck."

They do.



RCA

invites you on


A JOURNEY

THRU TOYLAND

Get all these
wonderful
toys

FREE

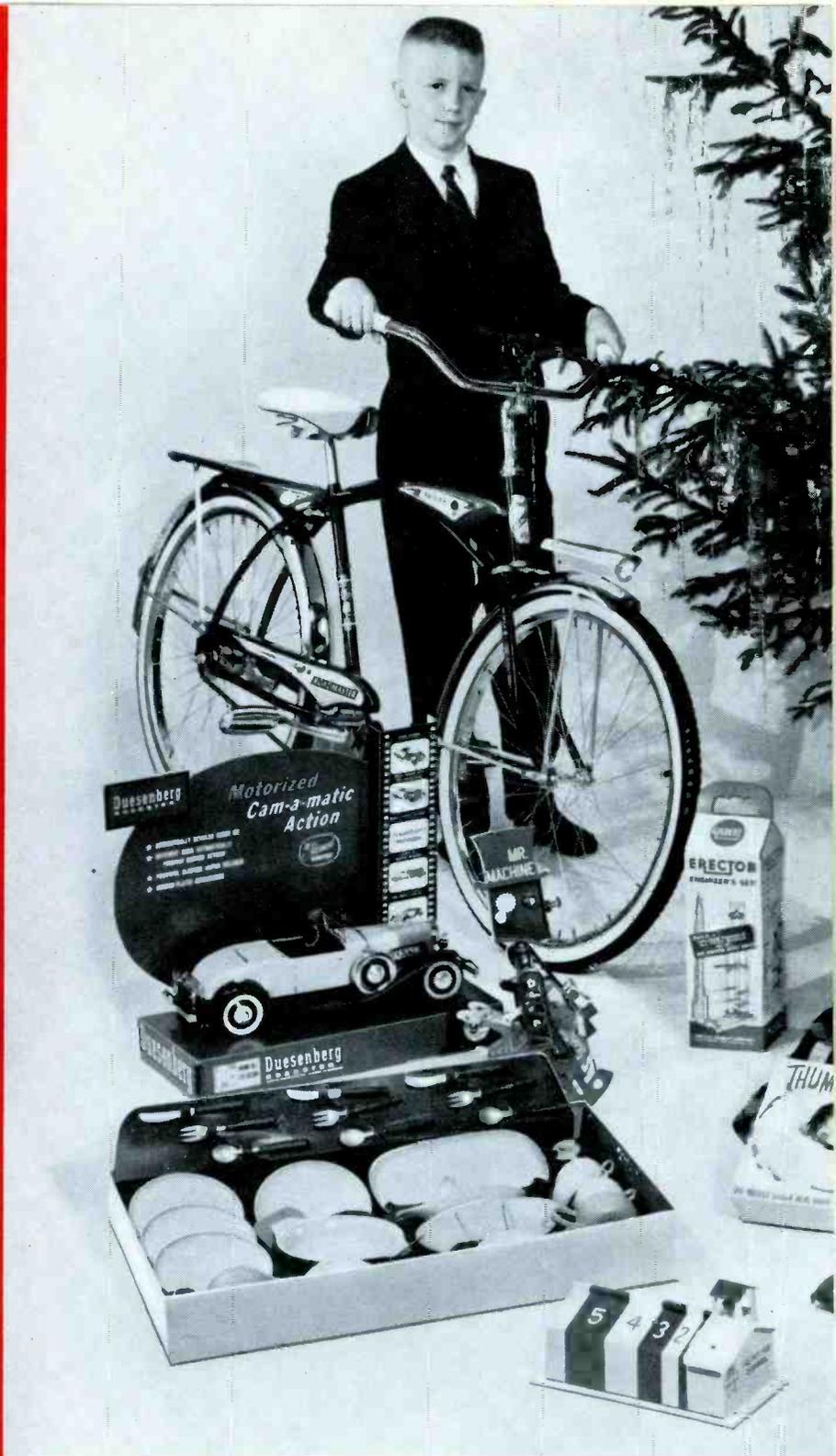with your
purchases
of RCA
receiving
tubes



Christmas is for children—and you can give any child a brighter, happier Christmas this year simply by buying the world's finest receiving tubes: RCA!

All the exciting, famous-name toys shown above are available FREE with the purchase of tubes through your participating RCA Distributor. See him right away to find out how your purchases of RCA receiving tubes entitle you to.....▶

RCA ELECTRON TUBE DIVISION, HARRISON, N. J.



The Most Trusted Name in Electronics


GILBERT

IDEAL


AMF



- | | | | |
|-----------------------------------|-----------|---|-----------|
| 1. Roadmaster
Boy's Bicycle | JTT 1675 | 10. Jumbo Gasoline
Truck | JTT 41277 |
| 2. Duesenberg Kit | JTT 36384 | 11. Smokey The Bear | JTT 78667 |
| 3. Mr. Machine | JTT 48447 | 12. Auto-Rama
Speedway Set | JTT 19083 |
| 4. Dinner Set | JTT 46375 | 13. Engineer's
Erector Set | JTT 10172 |
| 5. Rocket Launcher
Erector Set | JTT 10202 | 14. Electric Metal Zoom
Microscope and Lab | JTT 13099 |
| 6. Counting School
House | JTT 30973 | 15. Roadmaster
Girl's Bicycle | JTT 1685 |
| 7. Crying Thumbelina
Doll | JTT 05157 | 16. American Flyer
Sky Streak 7 | JTT 40006 |
| 8. Zipper Frog | JTT 71050 | 17. Astronaut
Helmet | JTT 42028 |
| 9. Chemistry
Lab | JTT 12152 | | |

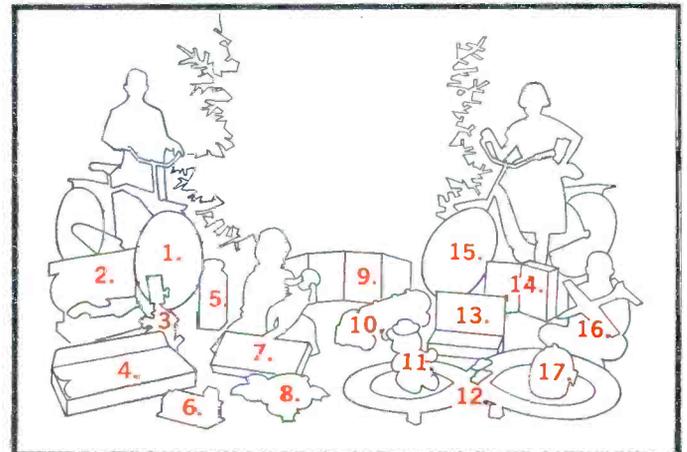

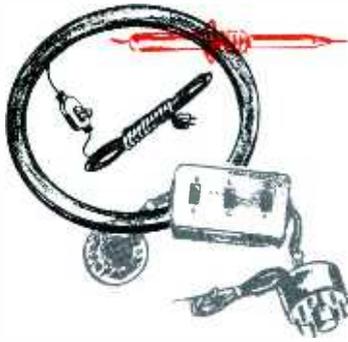It's RCA's way of wishing you and your entire family a Merry Christmas!



COLOR TV SERVICE AIDS

Tools and accessories to make color work go more smoothly.

Proper bench servicing of color receivers calls for the use of various inexpensive test accessories, which soon become indispensable to a shop handling any amount of color. More different types of service aids are needed than in black-and-white TV work, but the total number of units is not too great because of a high degree of standardization among color sets with respect to physical test arrangements. Here is a summary of the various types of color service aids, with pointers regarding their use. All are commercially available; in some cases, the serviceman can assemble suitable equipment himself.

Degaussing Coils

It has become standard procedure to demagnetize the color set as one of the first steps during the original installation, and thereafter as a preliminary to readjusting setup controls or checking for certain faults in the receiver. A "degaussing" coil has thus become a must item for color work. Excellent ones are available, but if you prefer to "roll your own," most specifications suggest winding a coil 12" in diameter, containing slightly over 400 turns of #20 enameled wire. The coil is then bound with plastic insulating tape, and the ends connected to a line cord.

Power-line current passing through the coil creates a strong AC magnetic field that neutralizes small amounts of residual magnetism in metal components of the TV set. After thoroughly going over the set, back away about 6' to 10' before disconnecting the coil; the idea is to

prevent remagnetizing the set with the collapsing lines of force that are produced when the line cord is pulled.

Not too much has been mentioned in the past about demagnetizing the *inside* of a color-TV cabinet in case of purity troubles. However, some interior components (especially CRT-mounting hardware) cannot be as effectively demagnetized from outside the receiver as from inside. If the technician works carefully, he can "degauss" stubborn magnetized spots without drawing the magnetization from the convergence or speaker magnets. An "inside job" is easier if done with a special coil, only 7" or 8" in diameter and wound with finer wire than the conventional coil.

CRT-Tester Adapters

Several regular TV test instruments can be utilized in color service work, if suitable accessories are added. One example is the CRT tester or reactivator. The only mechanical adaptation needed, to test each of the three guns in a color CRT individually, is to transpose connections to the proper pins of a standard 14-pin color CRT socket

so the color tube can be plugged into the 90° (duodecal) socket of the tester. Of course, the guns not actually being tested are left disconnected; a rotary switch or a set of toggle switches are provided for choosing the gun to be tested. Connections are shown in the chart.

Gun Disabler

One service aid which is very nice to have is simplicity itself—three 100K-ohm resistors with a common ground lead at one end, and individual clip leads at the other. Commercial units have refinements such as cases and individual slide switches, which make the resistors a great deal less awkward to handle.

What's it for? You don't *have* to use it at all, but you'll save a lot of time by doing so. It simply furnishes a means of biasing off one or more of the CRT guns as part of several routine service procedures. You can do the same thing by turning down the screen controls (or background pots, if used); but then you've upset the gray-scale adjustments and have to readjust these before you're through. In many instances, this wastes time because a complete re-setting may not have been necessary.

The most important use for the "gun-killer" is in making purity adjustments, where you want only the red gun operating during most of the procedure. It also comes in handy during convergence to remove the blue dots or crosshatch lines from the screen, so you can concentrate on the relationship between the green and red dots or lines. When

• Please turn to page 97

90° Black and White	Color (common to all guns)
Cathode — 11	Focus — 9
Grid — 2	Fil. — 1, 14
Accel. — 10	
Focus — 6	
Fil. — 1, 12	

Gun:	Red	Blue	Green
Cathode	4	13	5
Grid	2	12	6
Accel.	3	11	7

SENCORE

SIMPLIFIES COLOR SERVICING

NEW! CA122

COLOR CIRCUIT ANALYZER

A simple approach to a complex problem

Here is an instrument that is designed to eliminate the guesswork in color TV servicing. A complete analyzer that provides all required test patterns and signals for testing from the tuner to the tri-color tube. Additional analyzing signals for injection at each stage including audio, video and sync, brings to life a truly portable and practical TV analyzer for on the spot service; virtually obsoleting other analyzers with the advent of color. Sencore's simplified approach requires no knowledge of I, Q, R-Y, B-Y, G-Y or other hard to remember formulas. The CA122 generates every signal normally received from the TV station plus convergence and color test patterns.

The CA122 offers more for less money:

TEN STANDARD COLOR BARS: The type and phase that is fast becoming the standard of the industry. Crystal controlled keyed bars, (RCA type) as explained in most service literature, offer a complete gamut of colors for every color circuit test.

WHITE DOTS: New stabilized dots, a must for convergence, are created by new Sencore counting circuits.

CROSS HATCH PATTERN: A basic requirement for fast CRT convergence.

VERTICAL AND HORIZONTAL BARS: An added feature to speed up convergence, not found on many other color generators.

SHADING BARS: Determines the ability of the video amplifier to produce shades (Y Signal) and to make color temperature adjustments. An important feature missing on other generators.

COLOR GUN INTERRUPTOR: For fast purity and convergence checks without upsetting color controls. Insures proper operation of tri-color guns, preventing wasted time in trouble shooting circuits when CRT is at fault.



A must for color . . .
a money maker for black and white TV servicing

ANALYZING SIGNALS: RF and IF signals modulated with any of the above patterns for injection into grid circuits from antenna to detector. IF attenuator is pre-set for minimum signal for each IF stage to produce pattern on CRT thus providing a check on individual stage gain. Sync and video, plus or minus from 0 to 30 volts peak to peak, have separate peak to peak calibrated controls for quick checks on all video and sync circuits. Crystal controlled 4.5 mc and 900 cycles audio simplify trouble shooting of audio circuits.

NEW ILLUMINATED PATTERN INDICATOR: A Sencore first, offering a rotating color film that exhibits the actual color patterns as they appear on color TV receivers. Locks in with pattern selector control.

You'll pay more for other color generators only.

Dealer Net. 187.50

NEW! PS120 PROFESSIONAL WIDE BAND OSCILLOSCOPE

A portable wide band 3 inch oscilloscope for fast, on-the-spot testing. An all new simplified design brings new meaning to the word portability . . . it's as easy to operate and carry as a VTVM. Though compact in size, the PS120 is powerful in performance: Vertical amplifier frequency response of 4 MC flat, only 3 DB down at 7.5 MC and usable to 12 MC, equips the technician for every color servicing job and the engineer with a scope for field and production line testing. AC coupled, with a low frequency response of 20 cycles insure accurate low frequency measurements without vertical bounce. Sensitive single band vertical amplifier; sensitivity of .035 volts RMS for one inch deflection saves band switching and guessing. Horizontal sweep frequency range of 15 cycles to 150 KC and sync range from 15 cycles to 8 MC (usable to 12 MC) results in positive "locking" on all signals. New exclusive Sencore features are direct reading peak-to-peak volts —no interpretation; dual controls to simplify tuning; lead compartment to conceal test leads, jacks and seldom used switches. Rear tilt adjustment angles scope "just right" for easy viewing on bench or production line.

Size: 7" w x 9" h x 11 1/4" d. Weight: 12 lbs.

Dealer Net. 124.50
(with low cap. probe)

Kit. 74.50



A must for servicing color TV in the home . . . lowest priced broad band scope. All hand wired — all American made

SENCORE

SIMPLIFIES SWEEP CIRCUIT TROUBLE SHOOTING

SS117 SWEEP CIRCUIT ANALYZER

For Color and Monochrome Testing

A professional trouble shooter that helps you methodically walk the trouble out of "tough-dog" sweep circuits in monochrome and color receivers. The SS117 provides a positive but simple push button test on all circuits indicated in the block diagrams. These time-consuming circuits are checked step-by-step with tried and proven signal injection and substitution methods. All checks can be made from the top of the chassis or from under the chassis when it is removed from the cabinet.

TV horizontal oscillator check is made by substituting a universal oscillator known to be good. Horizontal output check consists of a cathode current and screen voltage test. The TV horizontal yoke is checked by substituting a universal yoke from the SS117 and viewing brightness or restoration of 2nd anode voltage. Horizontal flyback is checked dynamically in circuit by measuring the power transfer to the yoke when TV is turned on. TV horizontal sync can be used to control the SS117 horizontal oscillator, providing a positive check on sync from the video amplifier to the TV oscillator. Vertical circuits are tested by simple signal injection from vertical yoke to oscillator for full height on CRT. The SS117 with the CA122 Color Analyzer provides a complete TV analyzer for virtually every stage in monochrome or color receivers.

External checks for AC, DC, peak to peak voltage readings and DC current in the upper right hand corner save using a separate VTVM. Accurate 2nd anode measurements up to 30,000 volts are made with a sensitive 300 microamp meter and the attached high voltage probe. AC outlets, all steel construction and mirror in the cover makes every servicing job easier.

Size: 10 1/4" x 9 1/4" x 3 1/2". Wt. 10 lbs.

Dealer Net..... 89.50



The SS117 checks them all



FREE—A 33 RPM half hour permanent record packed with every unit explains each test.

FOR FASTER MORE ACCURATE TUBE TESTING

TC114 MIGHTY MITE TUBE CHECKER

This is the famous Mighty Mite, acclaimed by over 25,000 servicemen, maintenance men and engineers as "the best they've ever used." A complete tube tester that is smaller than a portable typewriter yet finds tubes that testers costing hundreds of dollars miss, thus selling more tubes and reducing call backs. A real money maker for the serviceman and a trusty companion for engineers, maintenance men and experimenters. The Mighty Mite has been acclaimed from coast to coast as the real answer for the man on the go. Even though the Mighty Mite weighs less than 8 pounds, new circuitry by Sencore enables you to use a meter to check grid leakage as high as 100 megohms and gas conditions that cause as little as one half microamp of grid current to flow. Thus, too, it checks for cathode current at operating levels and shorts or leakage up to 120,000 ohms between all elements. And it does all this by merely setting four controls labeled A, B, C, & D with new type easy grip knobs. Check these plus Sencore features... Meter glows in dark for easy reading behind TV set... The new Mighty Mite has large size Speedy-Setup Tube Chart inside of cover—cuts setup time for even faster servicing. New stick proof D' Arsonval meter will not burn out even with shorted tube... Rugged, all steel carrying case and easy grip handle.

The improved Mighty Mite will test virtually every radio and TV tube that you encounter, nearly 2000 in all, including foreign, five star, auto radio tubes plus the new Compactrons, Novars, Nuvistors and 10 pin tubes. Has larger, easy-to-read type set-up booklet for faster testing.

Size: 10 1/4" x 9 1/4" x 3 1/2". Weight: 8 lbs.

Dealer Net..... 74.50

TM116 TUBE TESTER MODERNIZING PANEL

New tube adapter for testing Compactrons, Novars, Nuvistors and 10 pin tubes in any tube tester except cardomatic types. Plugs into octal socket of your tube tester enabling you to test these new tubes in the same manner



Fast, Accurate...
never lets
you down



A must for color



that your tester checks conventional tubes. Tube set-up chart included with each adapter.

Dealer Net..... 24.95

SENCORE

TRANSISTOR CIRCUIT TESTING MADE EASY & PROFITABLE

TR110 TRANSI-MASTER

A new transistor tester that will analyze the entire transistor circuit in minutes. Transistors can be checked in-circuit or out-of-circuit. Here is how it works: First, check the batteries or power supply with the 0 to 12 volt voltmeter. Next, check the current drain with the 0 to 50 milliamp meter. A special probe is provided so that you do not need to break the circuit. Intermittents caused by cracked boards can be localized by the current check. If trouble is not located by now, isolate the trouble to a specific stage by touching the output of the harmonic generator to the base of each transistor and note spot where sound from speaker (or scope where no speaker is used) stops or becomes weak. The generator becomes a sine wave generator for audio stages to help find distortion. If trouble points to a transistor, check it in a jiffy with the exclusive in-circuit power oscillator check provided by the TR110. A special probe is also provided for this. If the transistor checks bad in-circuit, remove it and give it an out-of-circuit check with the oscillator check or the more accurate DC check. The DC check is provided for comparison reasons, experimental or engineering work and to match transistors in audio output stages. Beta (current gain) is read direct or on a good-bad scale for service work.

Dealer Net. **59.50**



- COMPLETE IN OR OUT-OF-CIRCUIT TRANSISTOR TESTER
- SIGNAL TRACER • VOLTMETER
- BATTERY TESTER • MILLIAMMETER


TR115 TRANSISTOR DIODE-CHECKER



Tests transistors for leakage, gain, opens and shorts. Reads gain as good or bad or directly in Beta. Checks diodes for forward to reverse ratios. Tests them all from the smallest transistors used in hearing aids to the power types used in auto radios. Also lists Japanese equivalents. This simple to operate, time tested checker can be used with or without set-up chart for all servicing, experimenting and lab work. The industry's most popular transistor tester, used by Bell Telephone, Sears Roebuck, Edison and many others.

Dealer Net. **24.95**
 Kit **15.95**

NEW! BE124 BATTERY ELIMINATOR

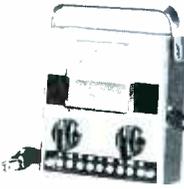

An easy to use power supply that replaces batteries during repair time of transistor radios. Tapped voltages at 1.5 volt DC intervals from 0 to 12 volts are on front panel for easy connection and to insure center tap and bias voltages when required. Function switch converts meter to a trouble shooting 0 to 50 Ma current reading device to monitor the current drain of the transistor radio. Improved regulation and voltage calibrate pot, guarantee accurate well filtered output. Also for charging nickel cadmium batteries.

Dealer Net. **24.95**
 Kit **15.95**

HG104 HARMONIC GENERATOR




Finds Defective Stage in a Minute . . . a real time saver. Just touch the output leads of the HG104 to inputs and outputs of transistors and a clear 1000 cycle note from speakers will tell you whether or not the stage is defective. It works every time from speaker to antenna. Two leads and calibrated output (not found on pencils) are a must for speaker connection, grounding to prevent RF spray and front end checks. With batteries.

Dealer Net. **9.95**

A NEW VERSATILE APPROACH TO CIRCUIT TESTING

SM112 SERVICE MASTER

A combination VTVM and VOM in one compact unit to simplify every testing need. The SM112 offers a conventional VTVM, operating from 115 volts AC for accurate bench or lab work . . . flip the function switch to VOM and two standard flashlight batteries power the unit as it is connected to a 5,000 ohms per volt meter. This Sencore first enables you to make voltage, resistance and current measurements anywhere anytime. And to top this, indicating arrows located along the left side of meter flash on and off as the controls are rotated to indicate the exact scale to read on any VTVM position or range. Hard to remember technical data is listed in the removable cover. One permanent probe is used for every test on VTVM or VOM. High voltage probe fits on end of permanent probe for measurements up to 30,000 volts DC. Standard specifications of 11 megohm input impedance on VTVM, 6 AC and DC voltage ranges from 0 to 1000 volts on both VTVM and VOM, 6 resistance ranges from 0 to 1000 megohms on VTVM, 2 ranges on VOM, and a 2 percent six inch meter provide all requirements for fast accurate measurements. Zero center scale and peak-to-peak measurements as added features create a truly great Sencore value.

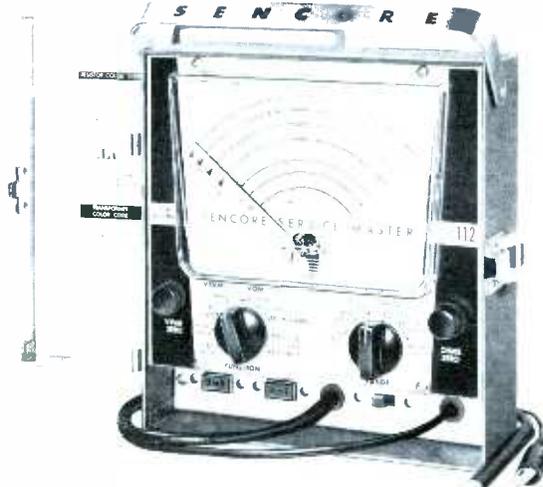

Dealer Net. **only 79.95**

SENCORE COMPONENT CHECKING MADE EASY BY SENCORE PARTS SUBSTITUTION

RC121 COMPONENT SUBSTITUTOR

A complete range of carbon resistors, capacitors, electrolytics and universal selenium and silicon rectifiers at your finger tips for on-the-spot substitution. Say goodbye to messy crumpled parts, unnecessary soldering and unsoldering when substituting components for test purposes only. Each section operates independently with a value close enough for every substitution need. Components in each section are isolated from chassis and from other sections. New electrolytic substitution section provides dual electrolytics as well as 25 single electrolytics. Exclusive surge protector prevents arcing, sparking or heating of single or dual capacitors being bridged. Electrolytics are automatically discharged when surge protector is released. Here are the values provided ... 81 in all.

- 1. CARBON RESISTORS** ... 12 resistors, 1 watt from 10 ohms to 5600 ohms. 12 resistors, 1/2 watt from 10 K to 5.6 megohms.
- 2. POWER RESISTORS** ... 20 wire wound, 20 watts from 2.5 to 15,000 ohms.
- 3. CAPACITORS** ... 10 capacitors at 600 volts from 100 MMFD to .5 MFD.
- 4. RECTIFIERS** ... Universal Selenium; .5 amps, 800 PIV. Universal Silicon; 5 amps, 800 PIV.



All your favorite

Sencore Substitution time-savers in one compact unit.

- 5. ELECTROLYTICS** ... 10 dual electrolytics from 2 MFD to 250 MFD at 450 V DC can be used as singles or tie them together and double capacity to form up to 25 separate single values. Both sections protected by surge protector.

All hand wired, complete with four test leads.

RC121 Dealer Net. **39.95**
RC121 (Kit) . . Dealer Net. **27.95**

H36 "HANDY 36"

Provides the 36 most often needed resistors and capacitors for experimenting, substituting and testing. 24 Resistors from 10 ohms to 5.6 megohms, 10 Capacitors from 100 mfd to .5 mfd, 2 Electrolytics 10 mfd and 40 mfd at 450 volts.

Dealer Net. **12.75**

RS106 RECTIFIER TROUBLE SHOOTER

Substitutes for single and dual Selenium and silicon rectifiers, single and dual diodes. Gives you a positive check every time. A must for servicing voltage doubler circuits. Protected by a 1/2 amp. Slow Blow Fuse.

Dealer Net. **12.75**



ES102 "ELECTRO-SUB"

Complete safe substitution for Electrolytic Capacitors from small transistor radio types to the largest used in Hi-Fi amplifiers. Contain 10 electrolytics from 4 to 350 mfd. Completely safe, has automatic discharge, surge protector circuit. Usable from 2 to 450 volts, DC.

Dealer Net. **15.95**

PR111 "BIG 20" SUBSTITUTOR

For power resistor substitution from 2.5 to 15,000 ohms. Withstands up to 20 watts for normal testing time.

Dealer Net. **12.75**

Time Saving Service Aids

BE113 DUAL TV BIAS SUPPLY

A single 0 to 20 volts DC bias supply or two separate 0 to 20 volts DC bias supplies—without interaction. Save time in AGC trouble shooting and aligning TV sets. Provides all TV biases recommended in photofact schematics and by all TV manufacturers. Well filtered—provides virtually pure DC with less than one tenth of one percent ripple. Calibration accuracy better than equivalent battery tolerance.

Dealer Net. **12.75**

VB2 VIBRA-DAPTER

Checks 3 and 4 prong Vibrators faster and easier. Plugs into any tube checker; ideal for use with LC3 or the Mighty Mite. To check 6v. vibrators, set for 6AX4 or 6SN7; for 12v. vibrators, set for 12AX4 or 12SN7. Two No. 51 lamps indicate whether vibrator needs replacing.

Dealer Net. **2.75**



FC123 FILAMENT CHECKER

Newly designed filament checker for continuity speed testing of all tube filaments including the new compactrons, novars, nuvistors and 10 pin tubes as used in new series TV receivers. Test leads are provided for CRT filament testing, continuity tests are AC or DC neon indicator voltage tests. TV cheater cord is used to power unit as a check on the cord to insure 115 volts AC on TV.

Dealer Net. **3.95**

HM119 "HANDYMAN"


A Sencore time-saver to eliminate wasted time behind TV sets. Imagine, a cheater cord with on-off switch, dual extension cord, up to date filament checker, universal fuse checker, handy trouble light, neon voltage and continuity checker, pin straighteners and cord wrapper all in one complete unit.

Dealer Net. **9.95**

ALL AMERICAN MADE
ALL HAND WIRED

SENCORE

ADDISON, ILLINOIS

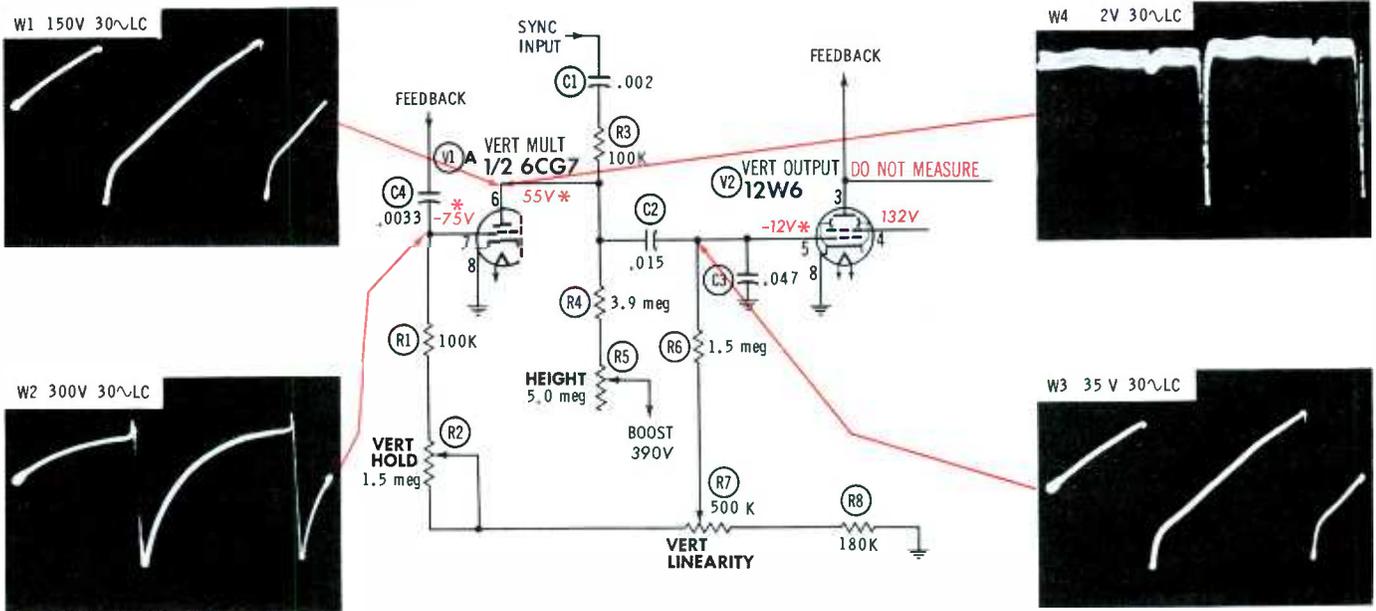

DC VOLTAGES taken with VTVM, on active channel. * means voltage will vary when signal is applied or control is adjusted. See "Variations."

WAVEFORMS taken with wide-band scope; receiver controls set for 50-volt p-p video to CRT. Low-cap probe (LC) used to obtain all waveforms.

Normal Operation

Triode and pentode form combined vertical multivibrator-output stage. Feedback from plate of V2 to grid of V1A sustains oscillation. Only the grid and control circuits are covered here; output transformer and feedback components will appear in December, 1962 *Symfact*. Circuit illustrated has feature common to many late-model sets: grounded cathode in output stage. Required operating bias is applied to grid via linearity control, which taps off portion of grid-leak bias developed by V1A across R1, hold control R2, and common ground resistor R8. Linearity and hold controls wired in series cause greater interaction between sections of multivibrator than in circuits using linearity control as cathode resistor. Vertical hold varies time constant of oscillator grid circuit, as in most other multivibrators. Sawtooth drive signal for output is developed in usual way, by charging capacitor from boost voltage through height circuit; but unusual here is inclusion of coupling capacitor C2 in sawtooth-forming network. Signal at plate of V1A is divided across C2, and C3, so W3 has much less amplitude than W1. Negative sync pulses (W4) are coupled via C2 to output grid, amplified, and fed back to grid of V1A to keep circuit in sync.

Operating Variations

PIN 6 DC voltage remains constant with or without sync signal, but can be varied from 35 to 65 volts by adjustment of height control; waveform amplitude ranges from 90 to 170 volts as control is turned.

PIN 7 DC voltage shifts to -60 volts under no-signal conditions, because loss of sync input signal causes minor change in output-tube operation which affects V1A through feedback network. Linearity adjustment causes bias change at pin 7 that induces vertical rolling.

PIN 5 DC voltage does not change when sync signal is removed; however, it varies from -9 to -17 volts with adjustment of linearity control. Waveform amplitude does not change, regardless of linearity and height settings.



W4 Sync-pulse waveform was taken with vertical sweep temporarily disabled by jumpering junction of R4 and R5 to chassis.

SYMPTOM 1

Severe Nonlinearity

Compression at Top—
Bottom Stretched


C3 Open

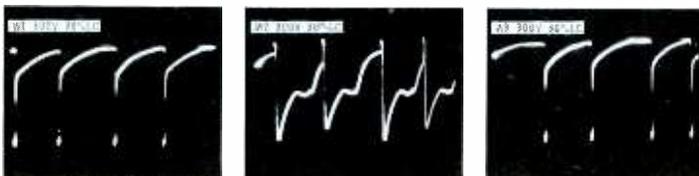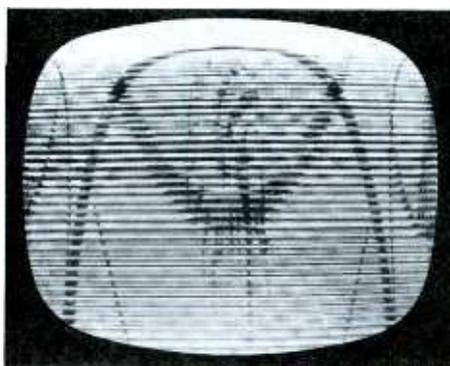

Waveform Analysis

W1 and W3 jump to 300 volts, and operating frequency changes to 120 cps—as evidenced by display of four cycles in all waveforms. W3 is developed across high resistance of R6-R7-R8 rather than relatively low reactance of C3. Therefore, its shape is more like square wave than sawtooth; in addition, virtually full value of W1 is placed on grid of V2. Contortions in positive-going slope of W2 are produced by faulty waveshape of feedback signal from plate of V2; “flat spots” correspond to most stretched-out areas of raster.

Voltage and Component Analysis

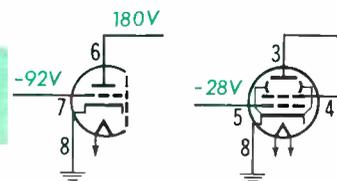


High plate voltage on V1A is incidental result of distortion in W1, which makes average value of this waveform more positive than normal. To help pinpoint reason why W1 fails to divide properly across C2 and C3, highly negative voltage on grid of V2 is most significant clue. C2 is obviously not leaky; if it were, grid voltage would shift in positive direction. Since more than twice normal bias is built up in grid circuit, great increase in impedance between grid and ground is evidently involved in trouble.

SYMPTOM 2

Bottom Foldover

Raster Stretched at Top

C2 Leaky

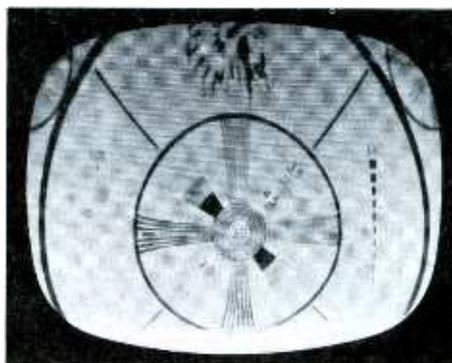


Waveform Analysis

W1, W2, and W3 all have slight waveshape distortion, but this might not be noticed except in side-by-side comparison with normal waveforms. Careful checking is also required to spot decrease in amplitude of W1 and W3, and increase in W2. Normal height is obtained with W3 amplitude less than normal—another sign of insufficient bias on V2. Lack of flat positive peaks on W3 indicates foldover being caused by saturation of output transformer rather than V2. This distorts feedback signal, producing “bump” near top of W2.

Symptom Analysis

Foldover indicates positive peaks of W3 are driving output stage into saturation. Most likely cause, other than faulty 12W6, is decrease of bias on this tube. Plenty of height is obtainable, but linearity is poor. Control adjustments only tend to aggravate condition. Foldover becomes worse during operation.

Voltage and Component Analysis

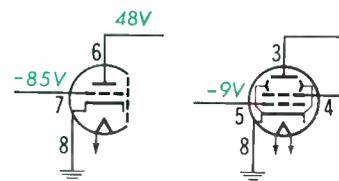


Grid voltage of V2 is -9 volts with linearity set near midpoint—confirming suspicion of not enough bias on output stage. Most probable trouble is leakage in C2, which would provide path from grid to positive DC source. Slightly low voltage on pin 6 could be due to leaky capacitor, or simply due to lower-than-usual setting of height control. Therefore, this measurement is not much help in troubleshooting minor faults. Defective capacitor which actually caused this symptom had 20-megohm leakage resistance in ohmmeter check.

SYMPTOM 3

Bottom Compression


Insufficient Height

R4 Increased in Value

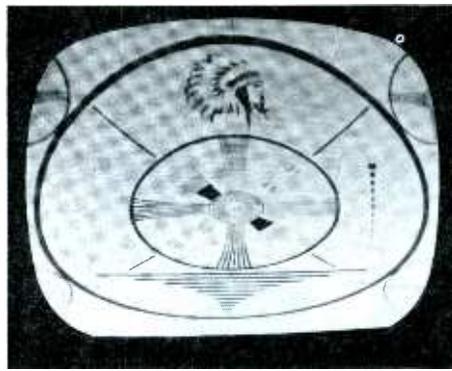


Symptom Analysis

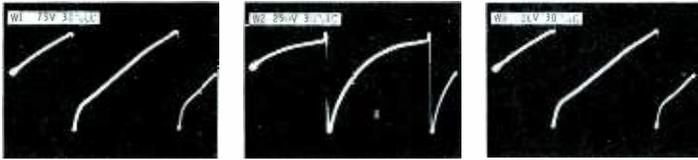Customer will probably put up with symptom until it reaches this condition. Screen cannot be filled by adjusting height control; only effect of increasing setting is to make linearity worse. Rotating linearity control for additional sweep causes vertical roll and extreme foldover at bottom of screen.



Voltage and Component Analysis

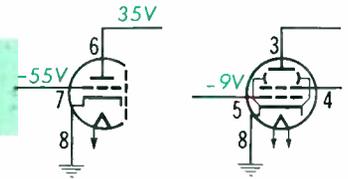

Waveform Analysis

All waveforms drop in amplitude, but shape is scarcely changed. W1 and W3 are more greatly affected by this trouble than W2, indicating fault in area of circuit between multivibrator and output stages. Since peak-to-peak values of W1 and W3 are in approximately same ratio as in normal circuit, C2 and C3 are correctly performing AC voltage division; thus, both capacitors are probably okay. Decrease of drive-signal amplitude could be caused by defect that results in slow charging of sawtooth-forming network through height control.


Voltage on pin 6 is far enough below normal to furnish useful clue. Expected value, 55 volts, is unobtainable at any setting of height control. Boost voltage at control arm checks normal, pinpointing trouble to circuit including control, series resistor R4, and C2. Resistance check of V1A plate circuit shows R4 has increased in value to 7 megohms. Defective control could cause similar symptom, plus "jumpy" sweep when control is turned. Bias on V2 is low, as in Symptom 2, but drive signal is too weak to produce foldover.

SYMPTOM 4

Nonlinearity


Moderate Foldover at Bottom

R7 Arm Open

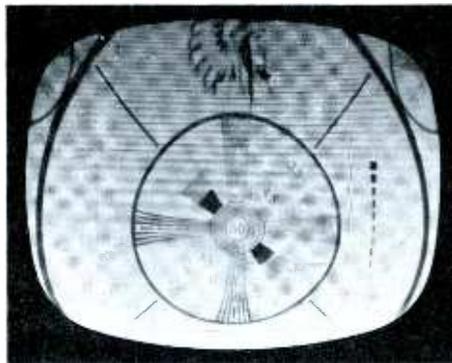


Symptom Analysis

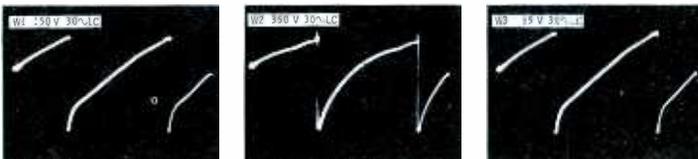Visual indication is similar to symptom 2, but milder—less foldover. One important clue quickly comes to light: Rotation of linearity control has no effect on vertical sweep. Trying to correct sweep by means of height control causes vertical roll, in addition to marked increase in foldover at bottom of screen.



Voltage and Component Analysis

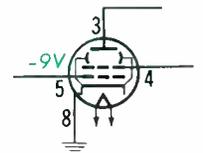


Waveform Analysis

W1 and W3 are normal in shape and amplitude, even though trouble is in grid circuit of V2—here's proof that waveforms in a troubled area do not always disclose presence of fault. Conversely, waveform distortion may not mean trouble close at hand; it may be byproduct of abnormal operation elsewhere in set. Example is small "bump" near positive peak of W2 (same as in Symptom 2). Normally, negative feedback voltage from V2 retards rise in V1A grid voltage. Saturation in V2 halts feedback, and W2 begins steep climb.

Only real clue is voltage on pin 5—it's not negative enough, and is unaffected by turning linearity control. Inability to adjust voltage ties trouble to grid-bias network; fault could be either poor contact on linearity-control arm or open R6. Incidentally, drift in value of R6 will cause gradual stretching at top of raster and compression at bottom; this is good point to remember if vertical linearity changes during warmup. Open resistor causes "floating grid" on V2, and symptoms may vary according to condition of rest of grid circuit.

Chroma Demodulator and Matrix Stages

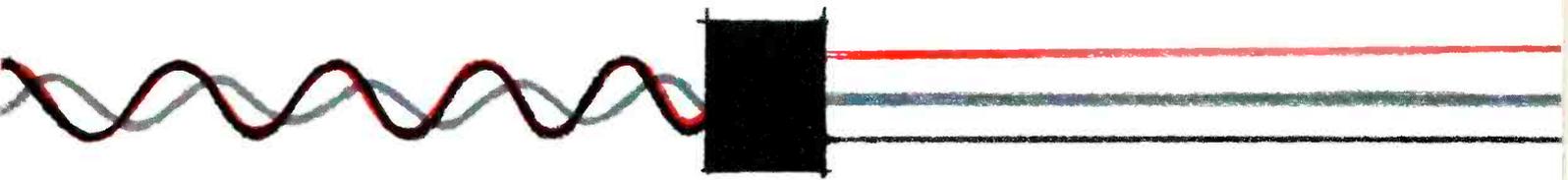

Finding out how red, blue, and green are recovered from the chroma signal . . . by Thomas A. Lesh

Occasionally a color-TV owner will complain that color pictures are deficient in certain hues — for instance, all shades of red appear as pastels, or all blue objects look too purplish or greenish. In certain other cases, both monochrome and color pictures will contain an overall tint of one hue, which cannot be removed by means of the color controls or setup adjustments (purity, convergence, and gray-scale tracking). The best way to solve prob-

lems such as these is to start at the grids of the color CRT and work back toward the chroma demodulators.

The average color-TV technician finds himself in somewhat unfamiliar territory when he delves into this portion of a color set. As yet, he hasn't had much opportunity to apply his theoretical knowledge of how signals are mixed to reproduce various colors. Even if he has had a fair amount of practice in making

chroma-sync and demodulator-phasing adjustments, he's likely to have followed the prescribed step-by-step procedures without much concern for understanding the principles involved. At this point, he needs to fill in the middle ground between these "school book" and "recipe book" approaches. By relating theory to actual practice, he will pave the way for intelligent analysis of troubles.

It's particularly important to learn

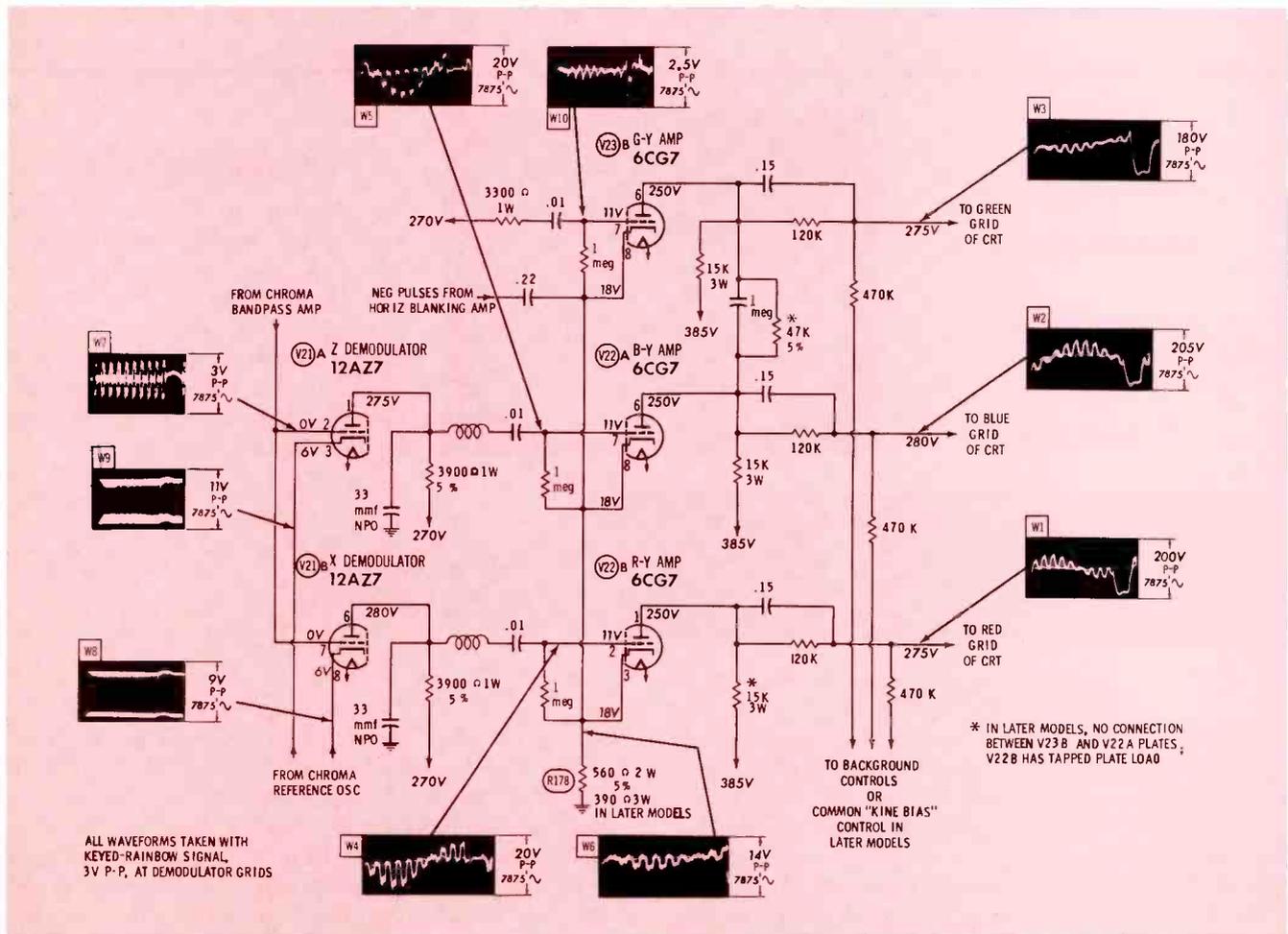



Fig. 1. Chroma demodulators and color-difference amplifiers of typical color TV (RCA Chassis CTC9).

more about the nature of typical test signals, because inaccurate color rendition is usually due to either *wrong proportions* or *incorrect timing* of signal inputs to the three guns of the color CRT.

Remember that each of the three outputs from the color-TV camera (red, green, and blue) is split in two before being transmitted. The portions corresponding to the relative brightness of different colors go to make up the equivalent of a black-and-white video signal. The remaining portions, called color-difference signals, are combined in specified amounts and then transmitted as chroma information.

At the receiver, the color demodulators must unscramble the chroma signal back into its original color-difference components; then these must be blended with each other and the video signal to recover the original colors. This final *matrixing* operation is done in the picture tube, by applying the video signal to the cathodes of all three electron guns and feeding separate color-difference signals to the individual control grids. The difference-signal voltages, by aiding or opposing the video-signal voltage in varying proportions, make the three guns conduct in the proper ratios to reproduce different hues.

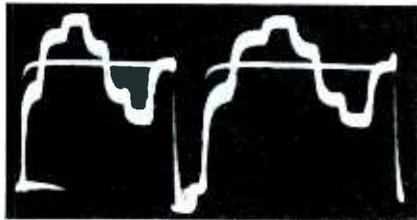Troubles which cause incorrect color mixing can develop in either the cathode or grid circuits of the picture tube. As a rule, faulty cathode operation is easily spotted by noting abnormal reactions to gray-



scale tracking adjustments; therefore, it is not usually necessary to analyze the cathode-signal waveforms in great detail. On the other hand, close attention to both the amplitude and the waveshape of the grid signals will often provide the key to locating trouble in the related circuits (Fig. 1).

A color-bar pattern is the best signal source for scope checks, because it provides a standard waveshape in which many important details can be readily identified. For example, the signals derived from an NTSC bar generator form "stair-step" patterns that show how the grid voltages fluctuate as various fully-saturated colors are transmitted. As demonstrated in Fig. 2, the waveform actually observed at the green grid bears a reasonably close resemblance to a graph of G-Y voltage based on mathematical color-difference formulas.

Note that the voltage is at a relatively low level during the first (red) bar, keeping the green gun cut off. The voltage rises above the zero reference line during the second bar, since the green gun (as well as the red gun) must conduct to produce yellow on the screen. The most positive point on the G-Y waveform naturally occurs during the third, or green, bar; if you scope the other two CRT grids, you'll find them both cut off by negative swings of voltage during this interval. The fourth bar (cyan) also requires some conduction of the green gun, so the signal level on the grid remains high. However, the blue bar causes a drop in grid voltage which interrupts the green beam. Magenta (the complement of green) accounts for the most negative signal peak in the bar presentation. During the white bar, no color-difference signals are produced, so the G-Y output is zero.

The other two grid signals can be similarly analyzed to find out which of the grid circuits is responsible for poor color mixing. Look for errors in overall waveform amplitude, or serious discrepancies in the relative amplitude of different signal elements; also see if any waveform "zigs" where it should "zag."

Keyed Rainbow Patterns

Obtaining color-difference signals

from a keyed rainbow generator makes it even easier to troubleshoot many matrixing faults. Although this type of generator doesn't supply the exact proportions of cathode and grid signals needed for presenting saturated color bars, it furnishes adequate color-difference signals for testing purposes. It also has the advantage of giving a very accurate indication of phase relationships between these signals. When the keyed-rainbow waveforms display proper phasing and correct amplitudes, it can generally be assumed that the grid circuits are able to do their part in accurately mixing all colors.

To make the most of keyed-rainbow signals, it's important to remember these basic facts about the generator that produces them: The RF output frequency is exactly 15,750 cps below that of the 3.58-mc chroma subcarrier. This slightly offset frequency gives the same effect as a 360° change in chroma

•Please turn to page 93

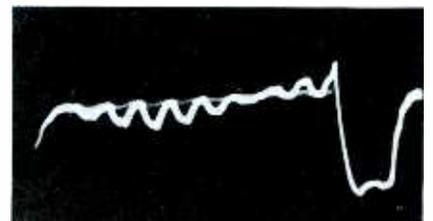
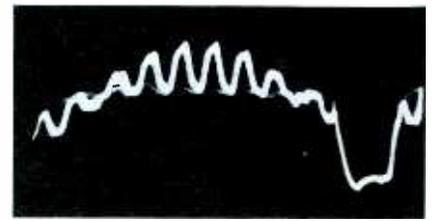
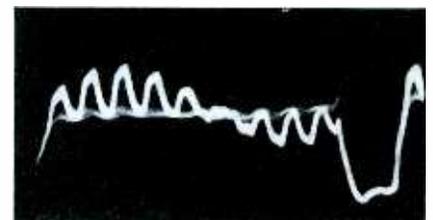


Fig. 3. Keyed rainbow with red, blue, and green grid inputs (W1, W2, W3).

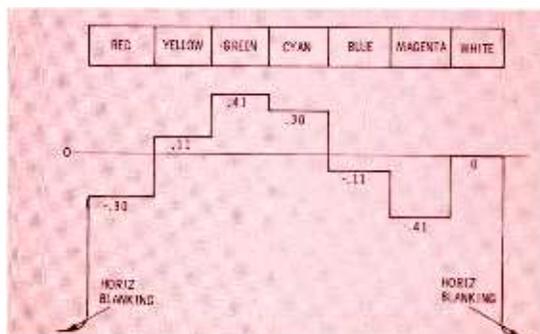


Fig. 2. Actual and theoretical G-Y waveforms of NTSC color-bar pattern.



QUICKER SERVICING
by George F. Corne, Jr.

OBJECTIVE

PURE
WHITE

One of the skills which a color-TV technician most urgently needs to develop is a well-practiced ability to make setup adjustments—static and dynamic convergence, purity, and gray-scale tracking. It's embarrassing, and sometimes frustrating, to be hesitant about what to do when you have a convergence job to perform in front of a customer. On the other hand, it's very satisfying to move controls and magnets with confidence, and know for sure which

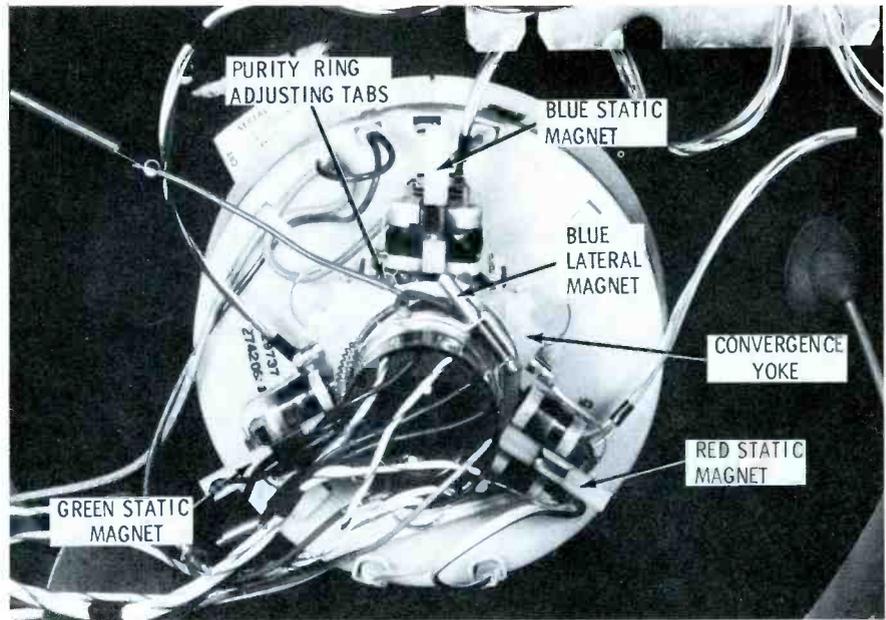


Fig. 1. Purity adjustments and convergence yoke are located on CRT neck.

adjustment you should make next.

You'll find frequent occasions to display your color-setup capabilities. A partial (and, in some cases, complete) convergence check is *always* necessary on new-set installations. It's also advisable after repair operations are completed, since a poorly converged screen can result from nothing more than circuits drifting out of adjustment — especially in older receivers.

Before you touch the setup controls, though, it's a wise move to stop and ponder the symptoms that appear on the screen. If you attempt setup before correcting other troubles, you can easily go off on a tangent and make conditions worse. To keep this from occurring, let's review a few of the symptoms and possible causes of incorrect purity and misconvergence. Then we'll discuss receiver procedures in detail.

Defining the Symptoms

If a limited area of the CRT screen shows background tinting, even without a picture present, one or more of the primary color fields—red, green, or blue—is contaminated. Before reaching for the static or dynamic convergence assemblies, try degaussing the receiver. This demagnetizing action, in the majority of cases, will result in a pure white screen; if it fails to do so, proceed to try the complete purity adjustment covered in this article.

A deep, overall tint of any one color is not normally caused by a

defect in purity or convergence; instead, it normally stems from a defect or misadjustment in the color demodulators, the CRT circuits, or even the chroma reference oscillator.

Color fringing on a black-and-white picture indicates convergence troubles, and the main thing to look for at this time is the extent or degree of fringing. You must also take into account the age of the set, how long since it was last converged, and other information you may obtain from the set owner. Evaluating this information will help you determine if you should attempt reconvergence in the home, or if you should pull the set.

In cases where fringing affects the entire screen, and touching up the static-convergence magnets will not cure it, you most likely have circuit troubles, and repair will be necessary before proper convergence can be obtained. This is a shop job, and even if your shop is equipped with a color test jig, it's best to pull the entire receiver. True, the defect could be in one of the circuits on the

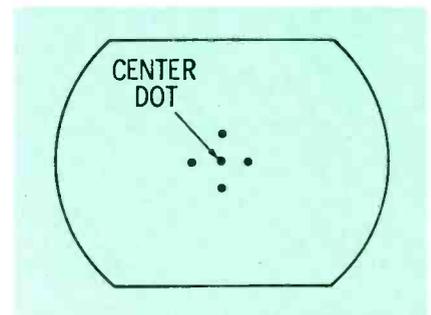


Fig. 2. Observe center dot while performing static convergence of beams.

STEP	PATTERN REF.	CONTROL NAME		FUNCTION	USE TO CONVERGE	REMARKS
		CHASSIS	CHASSIS	(Beam Displacement)	(or straighten)	
		CTC 10, 11, 12	29JC20 27KC20			

Vertical Convergence

1	Fig. 2					Perform Center Dot Static Convergence
2		R-G Master Tilt	R-G Vert Lines Top	Red and Green Vert Bars At Top of Screen	Red and Green Vert Bars, Pattern Area A-B	Touch Up Both Controls For Best Convergence, Pattern Area A-D
3		R-G Master Amp	R-G Vert Lines B't'm	Red and Green Vert Bars At Bottom of Screen	Red and Green Vert Bars, Pattern Area C-D	
4	Fig. 3	R-G Diff Tilt	R-G Horiz Lines Top	Red and Green Horiz Bars At Top of Screen	Red and Green Horiz Bars, Pattern Area A-B	Touch Up Both Controls For Best Convergence, Pattern Area A-D
5		R-G Diff Amp	R-G Horiz Lines B't'm	Red and Green Horiz Bars At Bottom of Screen	Red and Green Horiz Bars, Pattern Area C-D	
6		Blue Tilt	Blue Horiz Lines Top	Blue Horiz Bars At Top of Screen	Blue Horiz Bars with Red-Green Horiz Bars, Pattern Area A-B	Touch Up Both Controls For Best Convergence, Pattern Area A-D
7		Blue Amp	Blue Horiz Lines B't'm	Blue Horiz Bars At Bottom of Screen	Blue Horiz Bars with Red-Green Horiz Bars, Pattern Area A-B	
8	Fig. 2					Perform Center Dot Static Convergence

Horizontal Convergence

9	Fig. 4	B-1	Blue Horiz Lines Right Side	Blue Horiz Bars at Right Side of Screen	Make Blue Horiz Bar Straight, Pattern Area A-B	Touch Up Both Controls To Produce Straight Blue Line, Pattern Area A-D
10		B-2	Blue Horiz Lines Left Side	Blue Horiz Bars at Left Side of Screen	Make Blue Horiz Bar Straight, Pattern Area C-D	
11	Fig. 5	R/G-1	R-G Vert Lines Right Side	Red and Green Vert Bars At Right Side of Screen	Red and Green Vert Bars, Pattern Area A-B	Use Control as in Step 9 To Converge Blue Bar With Red-Green on Right Side
12		R/G-2	R-G Horiz Lines Right Side	Red and Green Horiz Bars At Right Side of Screen	Red and Green Horiz Bars, Pattern Area C-D	
13	Fig. 6	R/G-3	R-G Vert Lines Left Side	Red and Green Vert Bars At Left Side of Screen	Red and Green Vert Bars, Pattern Area A-B	Use Control as in Step 10 To Converge Blue Bar With Red-Green on Left Side
14		R/G-4	R-G Horiz Lines Left Side	Red and Green Horiz Bars At Left Side of Screen	Red and Green Horiz Bars, Pattern Area C-D	

chassis proper, but it could just as easily be in the convergence panel or the convergence yoke.

When fringing is only minor, chances are the convergence circuits are operating normally and all that's needed is a touch-up job. Before you perform this, try substituting new tubes in the horizontal and vertical circuits; then check the screen to see if fringing has decreased. Changes in sweep-circuit waveforms will often cause a small shift in convergence—perhaps back to normal.

During the touch-up job just mentioned, make sure an appro-

priate movement is evident on the CRT each time you adjust one of the controls on the convergence panel. If any of them fail to re-

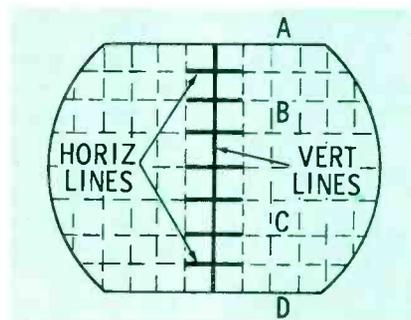


Fig. 3. Check for vertical dynamic convergence in this area of crosshatch.

spond, check the connecting wires to the convergence yoke, and make a visual check for loose or broken connections on the panel; these quick checks might keep you from unnecessarily pulling the set.

Black and White Setup

Perhaps you're not too familiar with the purpose or physical location of the different assemblies mounted on the CRT and used for purity and convergence adjustments. The physical arrangement is shown in Fig. 1; the purpose of the components in this photo will become

• Please turn to page 88



Meet a Color TV Specialist

How does a shop which specializes in color servicing appear—inside? What type of special equipment and test setups are required? What are some of the convenient little gimmicks used in color shop servicing? To find the answers to these questions (and others), we visited a color specialist who, in addition to servicing other electronic equipment, operates a profitable color-TV business.





Meet Leon Howland, of Indianapolis, Indiana. Leon has been actively engaged in home television repair since he first opened his shop in the spring of 1955, and active in color servicing since 1956. Prior to that he was a TV troubleshooter with a large electronics corporation. When questioned about color he readily admits, "I believe color is now being accepted by the public, and servicemen should keep abreast of its popularity."

Shown here is the color-service bench. Leon says this is a good workable setup, although the room area is small. Notice the position of the test equipment, neatly arranged on wooden shelves where it can be easily connected to any point on the color chassis. You'll see two color-CRT jigs in this photo, one stacked on top of the other. The upper one is used to "cook out" color chassis, after they are repaired.

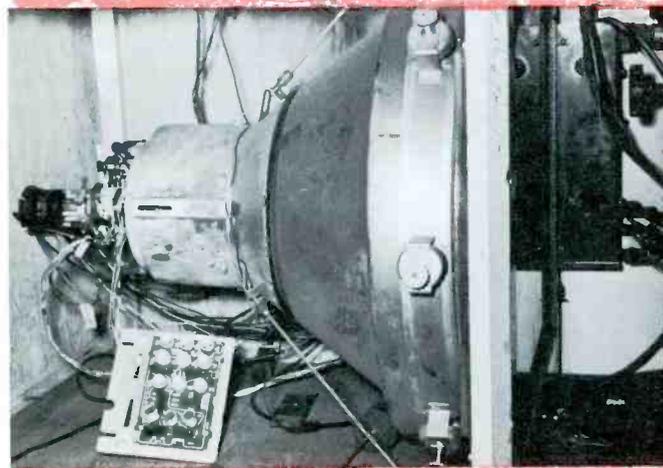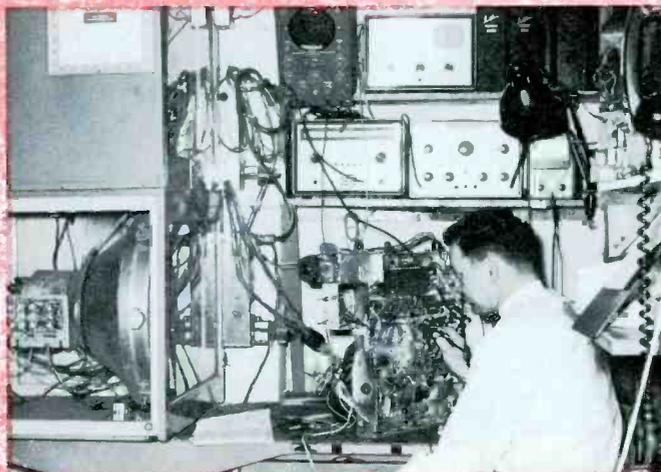


Cables for connecting the picture tube, the deflection and convergence yokes, and the CRT high voltage extend through a junction box to the front of the CRT-jig cabinet. The convergence yoke is installed on the neck of the test CRT. The convergence control panel (this type is used in late model receivers) is used to check convergence-current action quickly, without the panel from the set. Each control can be turned while the technician watches the CRT screen for the proper change in CRT beam displacement.

Leon explained what the technician is doing in these two photos. "On this special color jig, we can fire up any RCA color chassis, from the CTC5 through the CTC11, by merely changing the yokes. We've made our own adapters (one is shown connected to the yoke) which enable us to use our permanent test-extensions. To service a Zenith set, we need only to install its yoke on our CRT and connect the chassis."

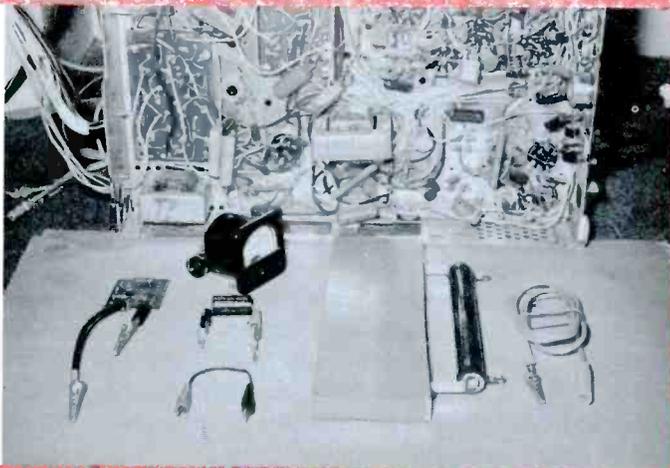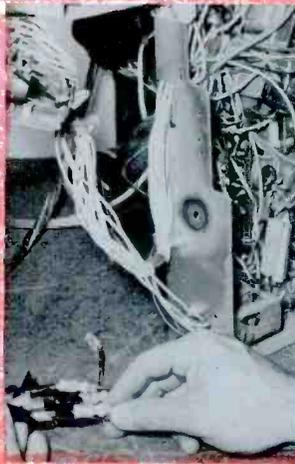


This display shows some ready-made aids for color servicing. A short clip lead, a resistor (in series with an electrolytic), and a detector probe (on the small terminal board) are all needed to perform chroma-bandpass alignment. The large 1500-ohm, 100-watt resistor is used to load the B+ supply, if horizontal sweep is disabled during alignment. The resistor is mounted on a wooden board because it runs "mighty hot" when connected. The anode cable has an alligator clip to facilitate connection to recent-model chassis.

The stock shelves shown here contain many replacement components for use in color chassis. Among them are two 3.58-mc crystals (chroma reference oscillator), a couple of plate coils for the same circuit, a thermal circuit-breaker, and a line thermistor (used in some color sets). Also, Leon mentioned he keeps one or two spares for any component which has a history of repeat failure in a particular color chassis. This special stock supply is located next to the color-test setup—there's real convenience!

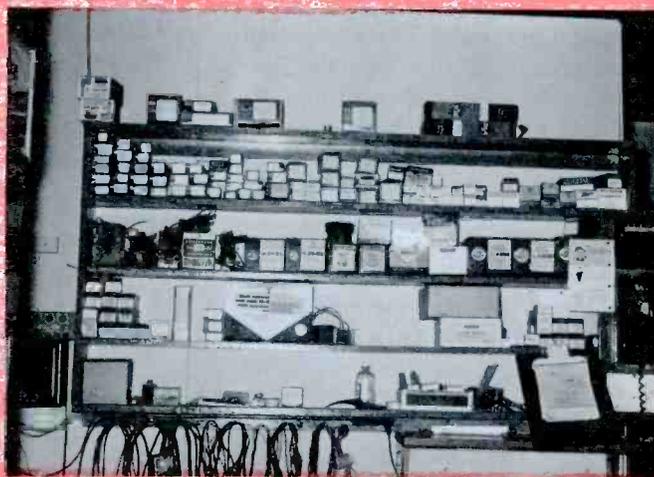

Leon also sells color television sets. Here we see his service manager, Owen Crew, making predelivery convergence adjustments to a new color receiver. He points out, "Prior to delivering a color set, we check its performance thoroughly, making any necessary convergence and operating adjustments in the shop. Usually all that's needed later, when we set the receiver in the customer's home, is degaussing and quick operational checks. Naturally, a few receivers still require touch-up in the customer's home."

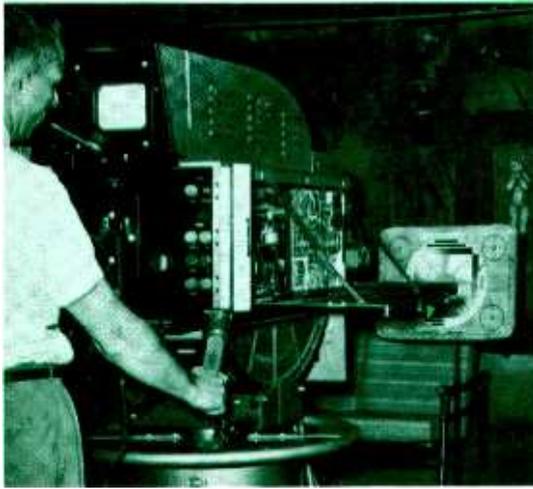

A LOOK INSIDE A COLOR TV STATION

Considerable effort goes into reproducing shows in natural color . . . by Charles Guion

Did you ever wonder what a television studio crew has to do to produce a live color picture? Just to think about it, you might imagine the engineer merely goes to the control panel and turns on a handful of switches, proceeds into the studio and lights up the set where the show will be televised, aims the camera in the general direction of the set, and awaits further instructions from the producer. On the surface, this is true—as far as it goes.

But just what switches does he turn on, and what are their functions and purposes? The first switch will probably turn on the tube filaments in the color camera. Next, the engineer will fire up the flag generator, the colorplexer, the color-bar generator, the color monitor, the black-and-white studio monitor, and the audio racks.

To help explain some of the equipment used in reproducing a color scene, let's take a brief look at the process used in color televising.

The Camera

The color camera is actually three separate cameras within a single



"Handful" of switches are important to color TV, but are only the beginning.

housing. It contains three separate *image orthicons* (similar to those used in black-and-white cameras), three video preamplifiers, and — until recent years — three separate camera cables.

However, the camera uses only one lens for all three orthicons. They are positioned so that, through the use of prisms and mirrors, the same scene strikes all three tubes. A color filter is placed in front of each tube. Each filter corresponds to one of the three basic colors used in the present color-TV system—red, blue, or green.

With the camera aimed in the direction of the scene to be televised, the orthicon with the green filter in front of it produces a signal voltage corresponding to the amount of green in the scene. In a like manner, the orthicons with the red and blue filters develop voltages in proportion to the amount of red and blue.

Colorplexer

The three color - signal voltages are then applied to the *colorplexer*. This unit, approximately 15" deep and 20" high, is usually mounted in a standard 19" equipment rack. The colorplexer contains the circuits which form a composite color signal by matrixing, or "cross-mixing," the green, red, and blue signal voltages from the color camera.


The colorplexer produces three output voltages: the luminance (Y) signal, and two chrominance signals (I and Q). These latter two are applied to a pair of balanced modulators within the colorplexer and combined with a 3.58-mc subcarrier. The balanced modulators suppress the carrier, so the modulators pro-

duce only the sidebands. The output signals from the modulators are 90° out of phase. When they are added (in another stage of the colorplexer), they produce a signal with an amplitude and phase which varies in accordance with the color saturation and hue in the scene being scanned. The I and Q signals are then added to the luminance signal, still within the colorplexer, and sent through switching relays and stabilizing amplifiers to the transmitter.

Preparing the Camera

Let's assume the camera chain has now been on for approximately thirty minutes. While the camera has been warming up, the studio engineer has been performing various routine tasks, such as checking the program log for upcoming color programs and shows that are to be put on television tape.

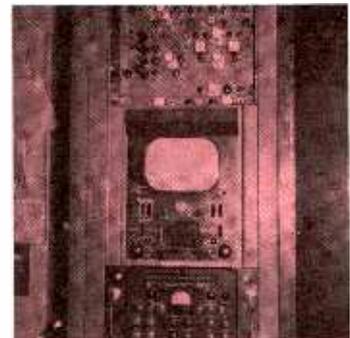He now switches on the camera B+, places a *resolution chart* in front of the camera, and (using a light meter) makes sure the chart is illuminated sufficiently. Next, at the control console, he makes sure the regulated power supplies are adjusted, and sets the focus current to



Colorplexer, monitor, and control board —a maze of tubes, controls, and knobs.

The new RCA MARK VIII 27-Mc 2-WAY RADIO



More Features • Improved Performance • AT A LOWER PRICE

Here is THE outstanding bargain today in a 2-way Citizens' Band radio: THE NEW RCA MARK VIII. Compact, dependable, simple to operate, it outperforms and offers more features than even the famous RCA Mark VII.

Look what this remarkable new unit offers you:

- 9 crystal-controlled transmit and receive channels
- Tunable receiver for reception of 23 C-B channels; dial marked in both channel numbers and frequency
- Exceptionally good voice reproduction—high intelligibility
- Maximum allowable transmitter input of 5 watts*—nominal output of 3 watts or more
- Highly selective superheterodyne receiver with one rf and two if amplifier stages
- Operates from standard 117 volt AC; separate DC power supply (optional) for mobile installations (you don't pay for unnecessary power supplies)
- Electronic switching—no relay noise or chatter
- Illuminated "working channel" feature
- Light and compact—only 3½ inches high, weighs only 8 pounds with mike; fits easily under the dashboard of even a compact car
- Improved Automatic Noise Limiter to reduce effects of ignition and similar interference

plus many more features to increase its usefulness and efficiency.

The new low Mark VIII price **\$149⁵⁰****
puts 2-way radio convenience within reach of everyone

GET THE FULL STORY; FILL OUT AND SEND IN THE COUPON BELOW

RCA Electron Tube Division, Commercial Engineering, Dept. X-33-R
415 South Fifth Street, Harrison, New Jersey

Please! Rush more information on the new RCA Mark VIII 2-way Citizens' Band Radio.

Name _____

Address _____

City _____ Zone _____ State _____

*Maximum plate input power to final radio-frequency amplifier stage; as defined by FCC regulations

**Optional list price



The Most Trusted Name in Electronics

the required value. Having taken care of these items, he is now ready to "set up" the color camera.

Beam Adjustments


With the camera lens covered, the engineer adjusts the green channel first, since the red and blue are registered with respect to the green. The beam current is first increased until the dot can be seen on the camera monitor. The green channel is then aligned by turning the focus control back and forth, meanwhile adjusting the two alignment controls until the focus dot remains stationary. The same procedure is then followed with the red and blue channels. The basic adjustments are similar to those of a black-and-white camera, except that three separate orthicons must be set up.

Now, with the green lens uncapped, the camera is positioned so that the resolution chart is centered in the camera's viewfinder monitor and the control-room monitor. The beam current is increased until the highlights (bright areas) of the chart are just on the verge of blooming. A test switch reduces the image on the viewfinder, and the target voltage is set to a point where the chart is barely visible; when the test switch is released, the picture of the chart is visible again. The same procedure is followed with the other two channels — the red and blue.


Registration

The resolution chart is now replaced by a registration chart. The engineer carefully checks the green channel for proper aspect ratio and adjusts the necessary controls.

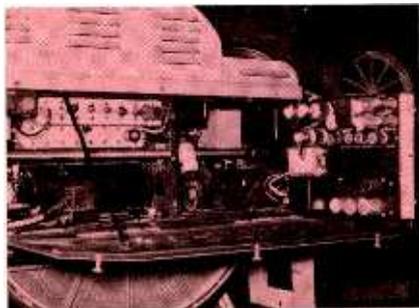Adjustment of the *gain* and *pedestal* controls to the prescribed levels in all three channels is necessary, before actual registration of the red and blue channels on the green can begin. By setting these



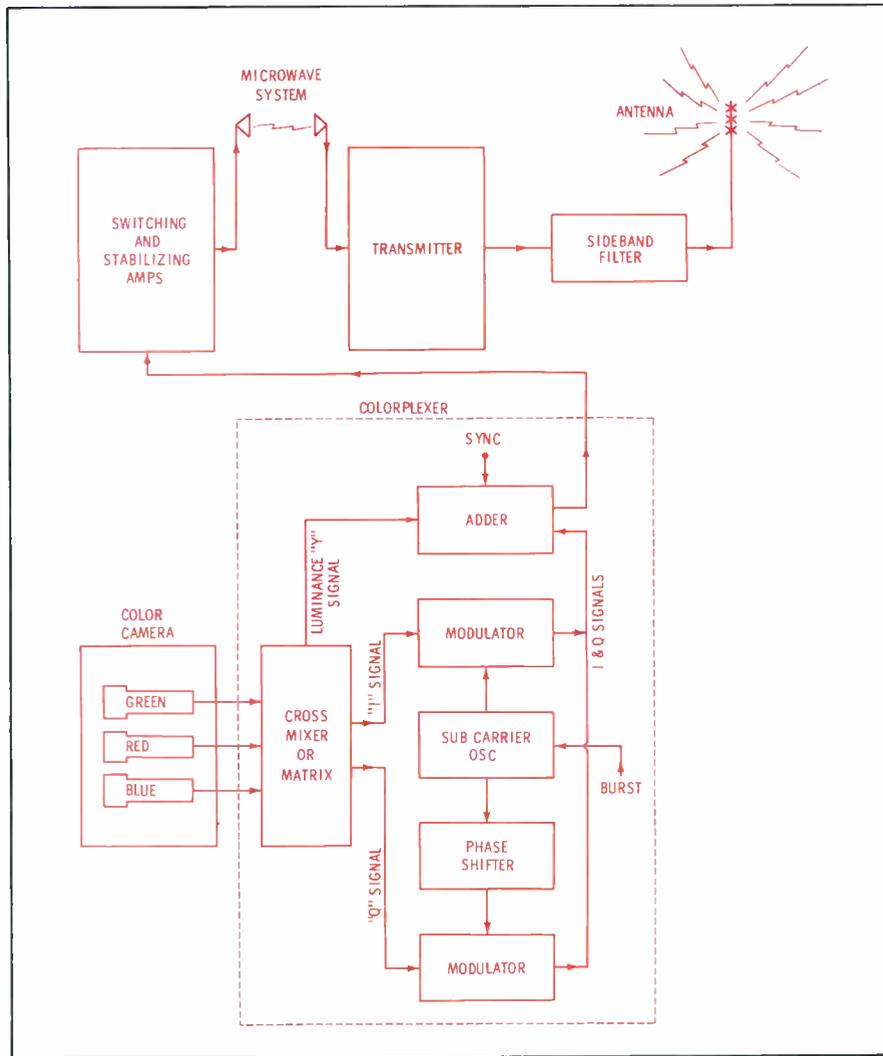Color camera with side panels down to reveal setup and maintenance controls.



Simplified block diagram shows relationships between components and signals.

controls, the engineer is attempting to achieve a good black and white picture, well focused, from each of the color channels in the camera.

Registration of the color cameras — similar to convergence in the color receiver — is one of the most intriguing, fascinating, and sometimes frustrating operations in the entire setup procedure. The procedure is briefly this: The red-green button on the processing amplifier is depressed, enabling the engineer to see two pictures on the camera monitor. The green channel is left strictly alone, and the red vertical centering control is turned to separate the two pictures of the chart. Thus, the engineer can check the height of the red channel image with respect to the green; they should be equal at the top and the bottom. When they are the same, he brings the displaced signals back together.

Next, the vertical lines of the chart must be checked to make sure that they are parallel in the two

rasters. To do this, the horizontal centering control of the red channel is turned just enough to offset the red-camera image. If the vertical lines are not quite parallel, the engineer can take care of this little problem with the *skew* control located on the camera.

Width is also checked, using this displacement technique; and even image displacement at the extreme left and right sides indicates equal widths. The chart images can now

• Please turn to page 100



Engineer uses resolution and registration charts to adjust color-TV camera.

NOW *EVERYONE* CAN QUICKLY Set up and Service Color TV



New! **B&K** Model 850 **COLOR GENERATOR**

*Most Complete, Most Versatile, Portable Instrument for Use in the Home and in the Shop
Makes Color TV Set-up and Service Easier, Faster than ever!*

Now every service technician can be ready to set-up and service color TV with amazing new ease and speed! New advanced design simplifies the entire operation, saves time and work in every installation. Eliminates difficult steps in digging into the color TV set. Gives you new confidence in handling color.

Produces Patterns, Burst, and Colors Individually—Provides dot pattern, crosshatch, vertical lines, horizontal lines, burst signal, and individual colors—one at a time—on the instrument panel as well as on the TV color set—for fastest, easiest check. Unique window-viewer on front of the instrument panel shows you each pattern and color as it should be—gives you an exclusive display standard to use as a sure guide for quick, visual comparison.

Provides Accurate, Individual Color Display—Produces Green, Cyan, Blue, B-Y, Q, Magenta, R-Y, Red, I, Yellow, and Burst—one at a time. All colors are crystal-controlled and are produced by a precision delay-line for maximum accuracy. Each color is individually switch-selected—no chance of error.

Provides Accurate NTSC-Type Signal—Color phase angles are maintained in accordance with NTSC specifications.

Makes Convergence and Linearity Adjustments Easy—Highly stable crystal-controlled system with

vertical and horizontal sync pulses, assures the ultimate in line and dot stability.

Simplifies Demodulator Alignment—The type of color display produced by this instrument provides the ultimate in simplicity for precise demodulator alignment.

Provides Automatic Deconvergence—Eliminates the necessity for continual static convergence adjustments. The instrument automatically deconverges a white into a color dot trio without digging into the color set to mis-adjust the convergence magnets. It also deconverges a white horizontal or vertical line into red, green and blue parallel lines. This greatly simplifies dynamic convergence adjustments.

Provides Exclusive Color Gun Killer—Front-panel switch control makes it easy to disable any combination of the three color guns. Eliminates continuous adjustment of the background or screen controls, or connection of a shorting clip inside the receiver. The switch also selects the individual grids of the color tube and connects to a front-panel jack to simplify demodulator alignment.

Provides Switch-Selected R.F. Signals—Factory-tuned, for channels 3, 4, and 5—for open channel use in your area.

Model 850 also includes other features that make it invaluable for home and shop use. Net, **\$199⁹⁵**

See Your B&K Distributor
or Write for Catalog AP20-R



B & K MANUFACTURING CO.

Division of DYNASCAN CORPORATION

1801 W. BELLE PLAINE AVE. • CHICAGO 13, ILL.

Canada: Atlas Radio Corp., 50 Wingold, Toronto 19, Ont.

Export: Empire Exporters, 277 Broadway, New York 7, U.S.A.

by Wayne Lemons



Interpreting Your Inventory

How much is your inventory really worth? If you were forced to close out your business tomorrow, could you get 20c on the dollar?

Maybe you're overstocked on obsolete items. For example, if you're still stocking as many 6SN7's or 6BQ7's as you were two or three years ago, you should get a rag and wipe them off, for they have been collecting dust sitting there undisturbed. Take a look at your shelves. If you're not on top of the inventory-control problem, you'll find a lot of boxes that are showing their age—a dead giveaway that some of your money tied up in parts is slowly but surely dissolving into the air.

What can you do about this very real problem of inventory obsoles-

cence? Unfortunately, there is no one pat answer, but even the smallest shop can take some highly effective stopgap measures. By far the most profitable of these is some sort of *simple, daily* inventory data sheet. This need not be elaborate; in fact, it should not be. Elaborate inventory controls are successful only for large companies—in small businesses they dig too deeply into the owner's productive time. Fortunately, even simple systems that take no longer than 15 or 20 minutes per day result in invaluable data relative to what you should or should not buy.

Fig. 1 shows a simple daily sheet you can use. All the information on it comes from your daily sales tick-

ets. It does double duty as a "want list" for reordering stock; also, by simply placing a check after the items listed, you can keep a record of parts ordered. This information, if you have a busy shop, can be transferred to a weekly tally sheet—or you may want to transfer the information only once each month onto a record chart something like that in Fig. 2. The monthly record then becomes your standard of buying; you rely on it, rather than on what you "feel" you need. For example, you may think you should stock ten 1X2's because this type seems like a good mover. A look at your monthly record, however, shows that you sold only ten 1X2's for the whole year. Obviously, then, since you never sold more than two in any month, two 1X2's should be an ample stock. You can use the money that would be tied up in eight more to provide you with some ready cash for improvements, to buy test equipment, or to purchase other, faster moving items for resale.

(Incidentally, many shops make up their monthly tube records using tube price lists furnished by the manufacturer—simply making tally marks alongside the tubes used. This saves you the trouble of having to list all tubes separately. The method you use is, of course, a personal preference.)

You will note that other, larger items are also listed in the monthly record: speakers, transformers, yokes, and the like. A great deal of money-saving information comes from keeping track of these comparatively expensive parts. In Fig. 2, for example, the record shows that only one 6" speaker was sold during the year. Thus, it would be folly for this shop owner to have more than one 6" speaker in stock. Actually, it is unlikely that even one should be stocked unless the shop happened to be in some remote area where two or three days would be required to obtain a replacement.

For the small shop in particular, it usually is not profitable to take the time necessary to list small items costing less than \$1, such as resistors and capacitors, on the record sheets. These are best kept in marked bins and reordered when the supply is low. These items usually

DAILY RECORD				No.	
DATE	PART	No. USED	DATE	PART	USED
			7/10/61	4CB6	
7/9/61	5U4			12BY7	
	6CB6			6CB6	
	6AU6			6T8	
	1B3			6AV6	
	6A55			6BQ5	
	6AQ5			5U4	
	3CB6			5CG8	
	5U8			6BQ7	
	12L6			6AX4	
	12BE6			17BQ6	
	Silicon Rect			21AUP4A	
	145 Vert Output XFMR			4" SPKR	
	6" x 9" SPKR			Y66 YOKE	
	100 MFD 150V			80MFD 450V	
	2-Set Coupler			10MFD 150V	

Fig. 1. Information from sales tickets is logged in a daily record sheet.

Find it and Fix it in 1/2 the time!

EASILY SOLVES "TOUGH DOGS"... INTERMITTENTS... ANY TV TROUBLE



MODEL
1076

TELEVISION ANALYST
BLACK & WHITE AND COLOR

ANALYST

By Easy Point-to-Point Signal Injection, You see the Trouble on the TV Screen and Correct it—Twice as Fast and Easy!


Simplified technique stops lost hours never recovered on "tough dogs", intermittents, and general TV troubleshooting. This one instrument, with its complete, accurate diagnosis, enables any serviceman to cut servicing time in half... service more TV sets in less time... satisfy more customers... and make more money.

With the Analyst, you inject your own TV signals at any time, at any point, while you watch the generated test pattern on the picture tube of the television set itself. This makes it quick and easy to isolate, pinpoint, and correct TV trouble in any stage throughout the video, audio, r.f., i.f., sync and sweep sections of black & white and color television sets—including intermittents. No external scope or waveform interpretation is needed. Checks any and all circuits—solves any performance problem. Gives you today's most valuable instrument in TV servicing—proved by thousands of professional servicemen everywhere.

Available on Budget Terms. As low as \$30.00 down.

Net, \$29995

SIMPLIFIES COLOR TV SERVICING, TOO

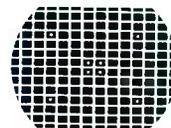

Enables you to troubleshoot and signal trace color circuits in color TV sets, or facilitate installation.



Generates white dot, crosshatch and color bar patterns on the TV screen for color TV convergence adjustments.



Generates full color rainbow display and color bar pattern to test color sync circuits, check range of hue control, align color demodulators. Demonstrates to customers correct color values.

Time-Saving, Money-Making Instruments Used by Professional Servicemen Everywhere



Model 960 Transistor
Radio Analyst



Model 360 V O Matic
Automatic VOM



Model 375 Dynamatic
Automatic VTVM



Model 700 Dyna-Quik
Tube Tester




Model 440 CRT
Rejuvenator Tester

See Your B&K Distributor
or Write for Catalog AP20-R



B & K MANUFACTURING CO.

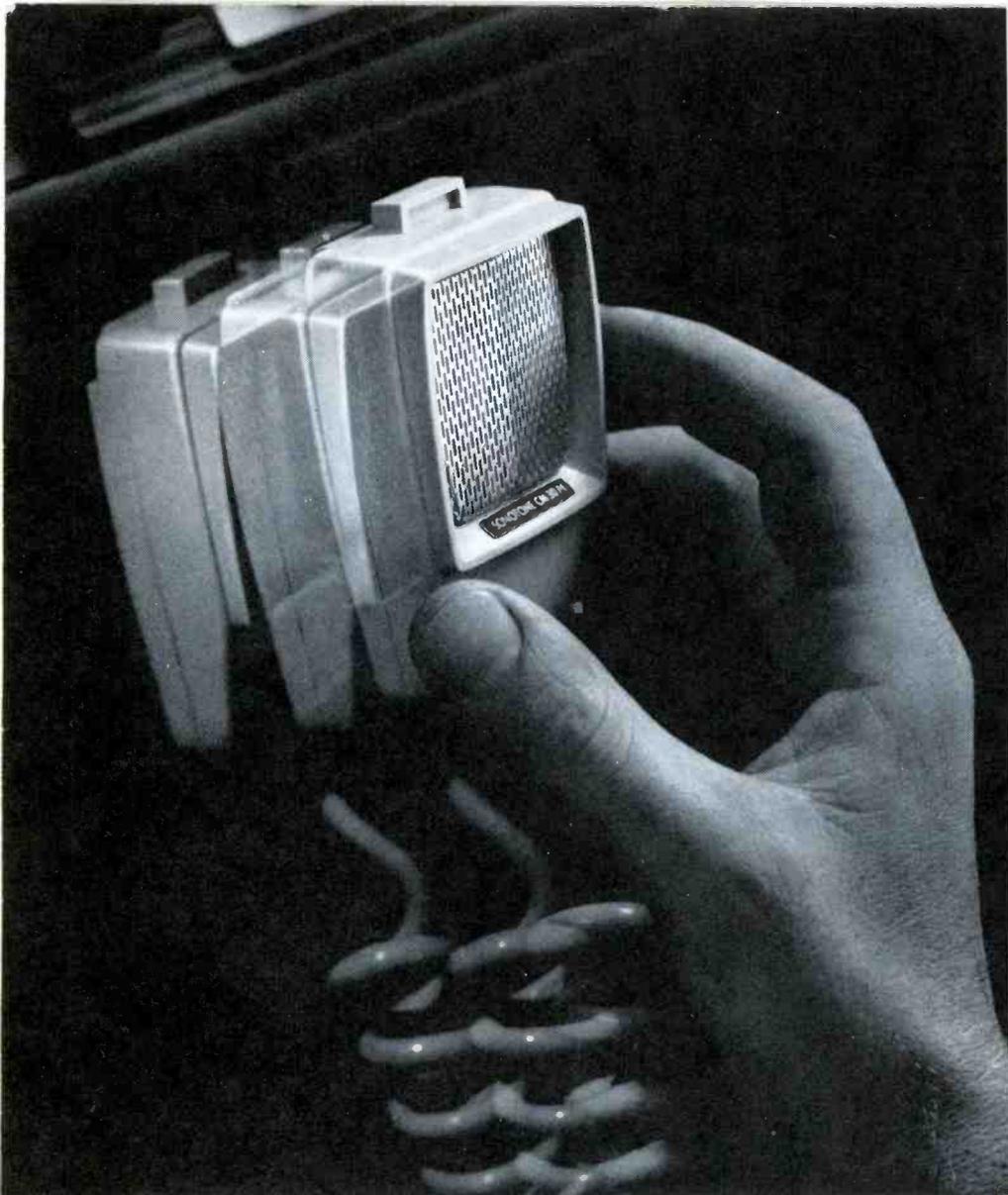Division of DYNASCAN CORPORATION
1801 W. BELLE PLAINE AVE. • CHICAGO 13, ILL.
Canada: Atlas Radio Corp., 50 Wingold, Toronto 19, Ont.
Export: Empire Exporters, 277 Broadway, New York 7, U.S.A.



Kerchunk! new sound of safety


Kerchunk is the sound made by the heavy duty magnet on the back of a Sonotone CB Ceramike as it mounts firmly, securely to your car's dashboard.

Kerchunk says: "Message to home base completed easily, safely."

Kerchunk means no more groping when you return your mike to its dashboard mounting bracket, no need to take your eyes off the road.

Responsible for this boon to those who rely on CB or mobile communication, from car or truck, is an important Sonotone development called "Magnet Mount." A heavy duty magnet on the back of Sonotone Ceramike mobile communications Models "CM-30M" and "CM-31M" lets you place the mike almost anywhere on or around the dashboard. Further, Magnet Mount eliminates the need to drill holes for dashboard mounting brackets.

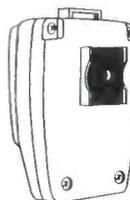The Ceramikes have far more to recommend them than just this amazing mounting device. The quality-engineered mobile communications models, "CM-30M" and "CM-31M," provide loud and clear reception. Inherently immune to extremes of temperature and



humidity, they will operate even if immersed in water. The ceramic transducer is neoprene encased, rendering it shock and impact-proof.

SONOTONE CERAMIKE "CM-30M" — Intelligibility unsurpassed. Sensitivity curve favors voice frequency range. High sensitivity from -49 db from 60 to 7000 cps. Ruggedly built to take the punishment of mobile use. Lightweight, shatterproof plastic case. So easy to handle and control with convenient "Push-to-Talk" button. Supplied with spring-spiraled, 4-conductor shielded cable — list \$16.50

With dashboard mounting bracket instead of Magnet Mount, Model "CM-30"— list \$14.00

SONOTONE CERAMIKE "CM-31M" — Budget-priced communications model in shatterproof plastic case features excellent intelligibility in 60 to 7000 cps frequency range at -49 db sensitivity. Mike has a 2-conductor coil cable, no switch—list \$16.00


Available with dashboard mounting bracket instead of Magnet Mount. Model "CM-31"—list \$13.50

Fixed communications or mobile, Sonotone Ceramikes provide topflight long-term, maintenance-free performance.

do not become obsolete; even if they did, they would hardly be a major factor in inventory control.

How to Reduce Your Stock

If you find that you are overstocked, what can you do about it? First, the obvious answer is not to reorder when you sell one of the surplus parts. Second, in the case of tubes, you may be able to substitute one type for another. (Turn to a tube substitution manual for help.) Larger components sometimes may be put to use as substitutes for others, but be sure that the time involved in making the substitution doesn't offset any profit gained by it. Third, if you are overstocked on items that may be sold across the counter, you should consider running a sale. Capital tied up in slow-moving merchandise is costing you money. Often it is better to break even, or sometimes take a slight loss, so you can put that money into other items that have faster turnover. Fourth, sometimes distributors have something like a "five-for-one" deal where they will give you full net price on an obsolete tube for every five of some other type you buy. Take advantage of these deals to get your money into fresh and fast-moving stock. Always try to maintain the money you have tied up in inventory at about the same level, if possible. Money in inventory is not like "money in the bank." The real value of your inventory is what you can turn it into —in the form of sales. In reality, a part sitting on the shelf has no

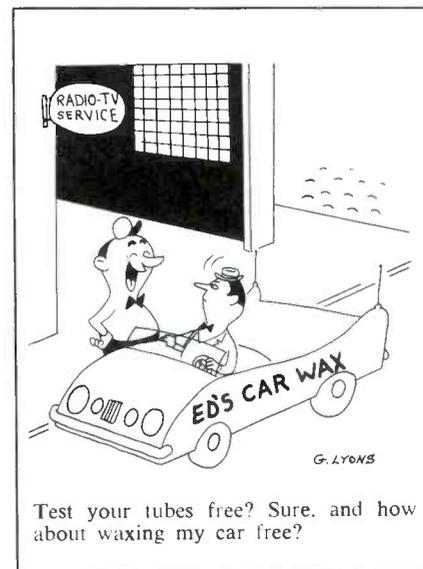


Test your tubes free? Sure, and how about waxing my car free?

SEE SONOTONE CB CERAMIKE WITH MAGNET MOUNT

Sonotone® Corp. • Electronic Applications Div. • Elmsford, N.Y. Canada: Atlas Radio Corp., Ltd., Toronto
Cartridges • Speakers • Tape Heads • Microphones • Electron Tubes
www.americanradiohistory.com

Again **B&K** Makes Servicing
Easier... More Profitable!

NEW! 3-IN-1 DYNA-TESTER

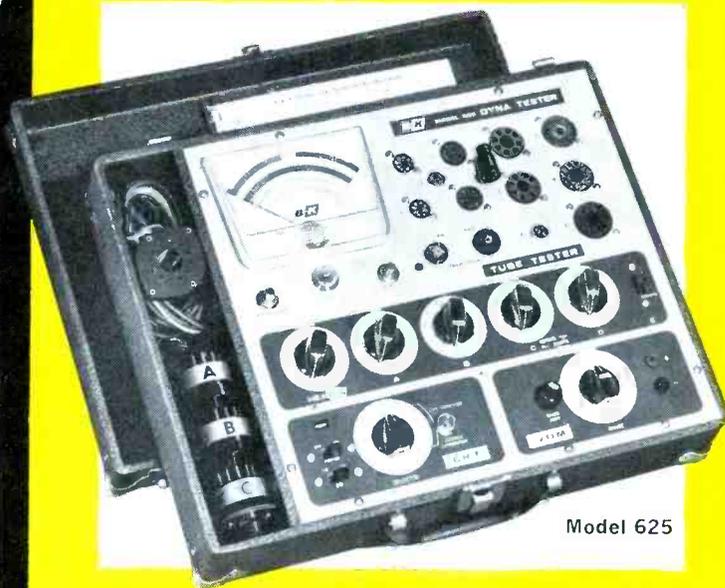

Model 625

- 1 TUBE TESTER 2 VOM 3 CRT

Unique new B&K design now simplifies servicing in the home or in the shop. Combines Tube Tester, Volt-Ohm-Milliammeter, and Cathode Rejuvenator Tester in one compact, professional quality instrument—at low cost!

1 TUBE TESTER SECTION is fast and accurate. Tests the *newest* tube types as well as all of the *old* commonly used tubes in TV and radio sets. Tests the Nuvistors and Novars, the new 10-pin tubes and 12-pin Compactrons. Tests voltage regulators, thyratrons, auto radio hybrid tubes, European hi-fi tubes, and most industrial types. Checks for *all* shorts, grid emission, leakage and gas. Provides *adjustable* grid emission check with exceptional sensitivity to over 100 megohms. *Checks each section* of multi-section tubes separately. Checks tube quality and capability of cathode emission under current loads simulating actual operating conditions.

2 VOM SECTION provides the 7 most-used ranges for convenient TV testing:
3 DC Ranges: 0-10, 100, 1000 volts
3 AC Ranges: 0-10, 100, 1000 volts
1 Resistance Range: 3 k center scale

3 CRT SECTION spots picture tube trouble and corrects it in a few minutes right in the home, without removing tube from set. Tests and rejuvenates picture tubes at correct filament voltage from 1 to 50 volts. Checks for leakage, shorts, and emission. Removes inter-element shorts and leakage. Restores emission and brightness. (Checks and repairs color picture tubes with B&K Accessory C40 Adapter.)

Model 625 Dyna-Tester complete in handsome, lightweight, leatherette-covered carry-case. Size: 11 3/4" x 15" x 4 1/2".

Net, \$139⁹⁵

See your B&K Distributor, or Write for Catalog AP20-R

Time-Saving, Money-Making Instruments Used by Professional Servicemen Everywhere



Model 960 Transistor
Radio Analyst



Model 360 V O Matic
Automatic VOM



Model 375 Dynamic
Automatic VTVM



Model 1076
Television Analyst



Model 440 CRT
Rejuvenator Tester

See Your B&K Distributor
or Write for Catalog AP20-R



B & K MANUFACTURING CO.

Division of DYNASCAN CORPORATION

1801 W. BELLE PLAINE AVE. • CHICAGO 13, ILL.
Canada: Atlas Radio Corp., 50 Wingold, Toronto 19, Ont.
Export: Empire Exporters, 277 Broadway, New York 7, U.S.A.

NEW! WINEGARD NUVISTOR ANTENNA AMPLIFIER



**ENGINEERED FOR TROUBLE-FREE,
LONG LIFE OPERATION...**

NO CALL BACKS!

INSTALL IT AND FORGET IT...USES 2 NUVISTORS THAT WILL LAST FOR YEARS... COMPLETELY WEATHER-SEALED, WON'T CORRODE... RESPONDS TO WEAKEST SIGNALS BUT STRONG SIGNALS WON'T OVERLOAD IT (TAKES UP TO 400,000 MICROVOLTS INPUT)... NOT AFFECTED BY HEAT OR COLD... DESIGNED FOR COLOR TV... FITS ANY ANTENNA... FULLY PROTECTED FROM LIGHTNING FLASHES, PRECIPITATION STATIC AND LINE SURGES ON 110 VOLT LINES.

Uppermost in the minds of Winegard engineers in developing the new Colortron amplifier were two things—1. A new high in performance. 2. Long life and trouble-free operation. For example, a special “lifesaver” circuit gives the two nuvistors an expected life of 5 to 8 years at top performance. This is possible because of a heat sink to control operating temperature and an automatic voltage control.

Winegard's revolutionary new circuit enables the Colortron to overcome the service problems and limitations of other antenna amplifiers. Colortron will not oscillate, overload or cross modulate because it takes up to 400,000 microvolts of signal input. *This is 20 times better than any single transistor amplifier.*

The Colortron amplifier will deliver clean, clear, color pictures or black and white, sharp and bright without smear. It can be used with any good TV antenna but will deliver unsurpassed reception when used with a Colortron antenna.

It has an ultra low noise circuit... high amplification... flat frequency response... accurate impedance match (VSWR 1.5 to 1 or better, input and output)... and no phase distortion. Can drive 6 sets or more easily.

Nothing on the amplifier is exposed to the elements—even the terminals are protected. A rubber boot over the twin-lead keeps moisture out. Colortron comes complete with an all AC power supply with built-in 2 set coupler. Colortron (model No. AP-220N) lists at \$39.95. Twin transistor model AP-220T also available. Input 80,000 microvolts without overload—\$39.95. For FM model, AP320 twin Nuvistor, 200,000 microvolts input—\$39.95.

Colortrons will be heavily promoted this fall with big ads in Life, Family Weekly, Parade and other consumer publications. Order now—ask your distributor or write for technical bulletin.

You get an extra bonus of quality and performance in all Winegard products.

value at all unless it can be sold. Basic as this obviously is, many technicians develop a false sense of prosperity when they take their physical inventory at the end of the year—counting each obsolete item at its full net price.

Where Should You Expand Inventory?

The admonition to maintain your inventory at a generally constant level is always wise unless you have a surplus of capital, or unless you can be reasonably sure that increasing your inventory will increase your profits. You might, for example, decide to take on transistor radios as a sales sideline. You should decide just how much money you are willing to spend. If you cannot spend enough money to put in a good selection of radios and to promote them through advertising, then you should forget about the whole thing. You might just as well put the money into a savings and loan association—you'd very likely make more money with a lot less effort. Or you'd be smarter to put it into some other item, such as a piece of test equipment, to speed up your work.

You must expand your tube inventory as new tubes come out; but by a careful check of your inventory records, you can usually do this without affecting your overall cost of inventory. You simply maintain a smaller stock of tubes that are being superseded by new types. For example, as you must buy more 6FQ7's, you can reduce your stock of 6CG7's. Likewise, you can buy fewer 6U8's as you stock up on 6EA8's and 6GH8's. You can keep up with new tube developments by studying articles on new set designs, and by checking the *Stock Guide for TV Tubes* which periodically appears in PF REPORTER.


Also remember that some tubes are used more in some areas than in others. For example, one make of set may be much more prevalent in your area than any other. This will help to determine what tubes you should stock, as well as other parts and components. It would be foolish, for instance, to stock 6BN8's if no sets sold in your area use them, or 6AF4's if you have no UHF tuners to service.



AMPLIFIER WORKS ON ANY ANTENNA.



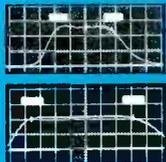SPECIALLY DESIGNED AMPLIFIER CLAMP SNAPS ON COLORTRON ANTENNA IN SECONDS.



UNRETOUCHED PHOTO OF AMPLIFIER GAIN CURVE—FLAT RESPONSE ALL CHANNELS.



COLORTRON POWER UNIT WITH BUILT-IN 2 SET COUPLER.



Winegard
ANTENNA SYSTEMS

3009-11 Kirkwood Boulevard

Burlington, Iowa
www.americanradiohistory.com

REDUCE INVENTORY! INCREASE SALES!

5 ADMIRAL ENSIGNS REPLACE 43 TUBE TYPES

**You save space, save dollars—
make more dollar profit per sale!**

...with the Admiral ENSIGN "Big 5" as your basic tube inventory. Less stock, more sales—and you make more profit! That's sweet music! Every Admiral ENSIGN tube is of fine/precision quality manufacture. All materials and parts used in the manufacture of these tubes are *new* except for the envelopes, which prior to reuse, have been inspected and tested to the same standard as new envelopes.



Call your ADMIRAL DISTRIBUTOR tomorrow... start cutting inventory cost, pocketing new profits right away!

BE WISE... STANDARDIZE ON


ADMIRAL ENSIGN

<p>ENSIGN 17BJP4 REPLACES</p>	<p>17ATP4 17AVP4A 17ATP4A 17BUP4 17CLP4 17AVP4 17CBP4</p>
<p>ENSIGN 21AMP4A REPLACES</p>	<p>21ACP4 21AQP4 21ACP4A 21AQP4A 21BSP4 21AMP4 21CUP4</p>
<p>ENSIGN 21CBP4A REPLACES</p>	<p>21FLP4 21ATP4 21CBP4B 21ALP4 21ATP4A 21CMP4 21ALP4A 21ATP4B 21CVP4 21ALP4B 21BAP4 21CWP4 21ANP4 21BNP4 21DNP4 21ANP4A 21BTP4 21CBP4</p>
<p>ENSIGN 24CP4A REPLACES</p>	<p>24ADP4 24ATP4 24CP4 24VP4 24XP4 24QP4 24VP4A</p>
<p>ENSIGN 24AEP4 REPLACES</p>	<p>24DP4A 24ANP4 24YP4 24ZP4</p>

REPLACEMENT PICTURE TUBES—ALWAYS FINE/PRECISION QUALITY

Heat absorbing

"THIRD HAND"

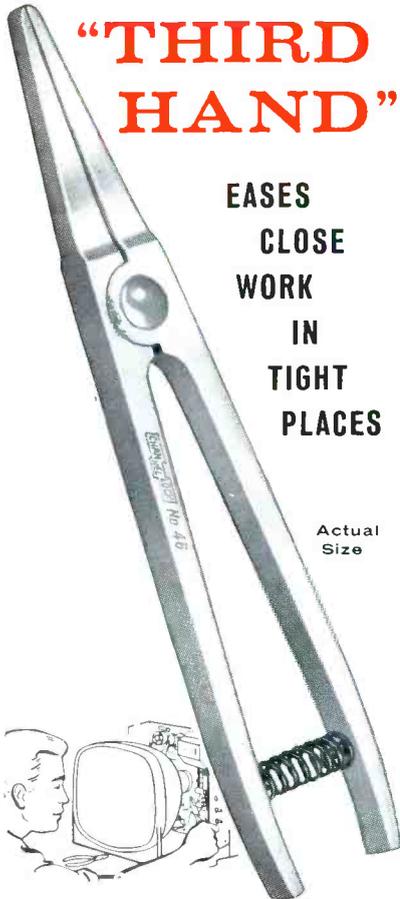

EASES
CLOSE
WORK
IN
TIGHT
PLACES

Actual
Size

SELF-GRIPPING

CHAN NEL LOCK

No. 46

HEATSORB CLAMP

(HEAT SINK)

A specially designed "heat sink" that prevents heat damage to electronic components during soldering operations. Also serves as handy, self-gripping "third hand" that holds and retrieves small parts in close work. Precision-made of light weight aluminum . . . easy to handle . . . cannot rust . . . Best of all, it's reasonably priced. *Be sure it's a genuine Channel-lock. Look for the trademark on the handle. Write for catalog showing complete line of pliers. Made Only By Champion DeArment Tool Company, Meadville, Pennsylvania.*

MONTHLY RECORD

PART USED	JAN.	FEB.	MAR.	APR.	MAY	JUNE	JULY	AUG.	SEP.	OCT.	NOV.	DEC.	TOTAL 1961
OZ4	1	2	0	0	3	4	2	3	0	1	0	0	16
1B3	11	10	6	9	7	3	9	12	6	1	5	4	83
1G3	4	2	3	4	1	2	2	0	1	4	4	3	30
1R5	0	0	0	0	1	0	1	0	0	0	0	0	2
1U5	0	0	0	0	1	0	0	1	0	0	0	0	2
1X2	2	1	1	1	0	0	0	1	1	0	2	1	10
2BN4	0	0	0	0	1	1	0	0	0	1	1	0	4
2CW4	0	0	0	0	1	0	0	1	1	0	0	2	5
2CY5	1	0	1	1	0	0	0	1	2	0	0	1	7
3A3	1	0	0	0	1	0	0	0	1	0	1	0	4
3AL5	0	0	1	0	0	0	0	0	0	1	0	0	2
3AU6	2	0	1	1	2	1	0	0	0	0	2	0	9
3AV6	1	0	0	0	0	1	0	0	0	0	2	0	4
3BN6	0	0	0	1	2	0	2	0	0	0	0	1	6
3BU8	0	0	0	2	0	0	0	0	1	0	0	3	6
3BZ6	5	3	2	6	4	8	4	3	1	7	10	9	62
Spkrs. 4"	1	0	2	0	3	3	0	2	4	0	0	1	16
Spkrs. 5"	2	2	0	0	0	0	2	0	0	1	0	1	8
Spkrs. 6"	0	0	0	0	0	0	0	1	0	0	0	0	1
Spkrs. 4" x 5"	0	0	1	0	0	0	0	1	0	0	0	0	2
Spkrs. 5" x 7"	0	0	0	0	2	0	0	1	0	0	1	0	4
Spkrs. 6" x 9"	0	0	0	2	0	3	4	1	0	0	2	0	12
Vert. Output XFMR	1	0	0	0	1	0	2	2	0	0	0	1	7

Fig. 2. Monthly record shows long-term inventory needs for various parts.

Let Salesman Figure Inventory?

Some shops have a favorite salesman do their inventory; he looks over the merchandise and brings it back up to the normal level. If the salesman is honest (and most are and have to be), this can save the shop owner a lot of time. But even the most honest salesman cannot protect you from creeping obsolescence unless he is really on the ball. *You* must still maintain your own inventory records if you are to stay on top of your business. You must know just how many of each item you should stock. You should have this information so that, even if the salesman does your inventory, your stocks will reflect the changing

trends in sales.


Also, if you do choose to have a salesman do your inventory, you can nearly always demand and get his agreement to replace slow-selling tubes with others that will move. Don't be afraid to ask for favors when you are extending him the privilege of an "automatic" order.

Summary

Inventory control can be simple or complex. For the small shop, keep it simple, but *keep it!* It will give you data that you can use to eliminate under- or overstocking, and can even help you to evaluate future sales trends. It can be the difference between making and losing money. ▲

TV TUNERS * REBUILT OR EXCHANGED

* ALL TYPES

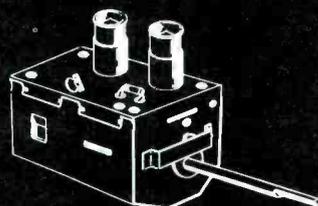

\$9.95 Including all parts and labor
(except broken wafers—billed at cost)

- Normally shipped same day received
- 90 day full guarantee
- U/V combinations \$17.95

FREE—!! Mailing carton sent to you on request

Phone Republic 3-9189

L. A. TUNER EXCHANGE

4611 West Jefferson Blvd.
Los Angeles 16, California

New TRANSISTOR RADIO ANALYST

makes it Easy and Profitable to Service all Transistor Radios



B&K Model 960

TRANSISTOR RADIO ANALYST
with Exclusive *DYNA-TRACE*
Single-Point Probe—and Built-in
Metered Power Supply and VTVM


**Complete Transistor Radio
Service Shop in One Instrument**

Signal-Generator, Power Supply, Milliammeter, VTVM, Battery Tester, Ohmmeter, and Both In-Circuit and Out-of-Circuit Transistor Tester—All in One

Also Speeds Servicing of Tube-Type Radios

Check all circuits - Pinpoint any trouble ... in minutes

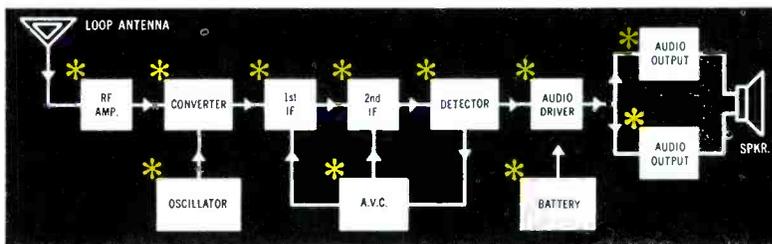Now you can profit from transistor radio servicing! This amazing new B&K "960" ANALYST gives you *everything* in one complete easy-to-use instrument. Makes transistor radio servicing *quick and easy*. Nothing else is needed except the transistor radios themselves waiting to be serviced. Brings you new customers for service, parts, and batteries. Makes this new business *yours*.



EASILY TROUBLE-SHOOT ANY STAGE BY UNIQUE POINT-TO-POINT SIGNAL INJECTION

The ANALYST gives you a complete signal-generating source for point-to-point signal injection. Easily enables you to trouble-shoot any transistor radio—check all circuits stage-by-stage—isolate and pinpoint the exact trouble in minutes.

Supplies modulated signals, with adjustable control, to check r.f., i.f., converter, and detector. Supplies audio signal to check audio driver and audio output. Provides unmodulated signal to test local oscillator. Provides separate audio low-impedance output for signal injection into loudspeaker voice coils to check speaker performance.

BUILT-IN METERED POWER SUPPLY FOR EASY SERVICING

Makes it easy to operate radio under test, while you inject your own signals. Provides from 1 to 12 volts in 1½ volt steps. Supplies all bias taps that may be required.

SIMPLIFIES IN-CIRCUIT TRANSISTOR TEST WITH NEW DYNA-TRACE SINGLE-POINT PROBE

Unique single-point probe needs only the one contact to transistor under test. No longer are three wires required to connect to emitter, base, and collector. Gives fast, positive meter indication. Saves time. Makes trouble-shooting simple and easy.

BUILT-IN VTVM

Includes high-input-impedance vacuum-tube voltmeter, which is so necessary for transistor radio servicing.

TESTS ALL TRANSISTORS OUT-OF-CIRCUIT

Meter has "Good-Bad" scale for *both* leakage and beta. Also has direct-reading Beta scale, calibrated 0-150. Assures quick, accurate test. Also automatically determines whether transistor is NPN or PNP. Meter is protected against accidental overload and burn-out.

Model 960. Net, \$99⁹⁵

Solve Every Service Problem and Profit with a Modern B&K Service Shop. See Your B&K Distributor or Write for Catalog AP20-R



B & K MANUFACTURING CO.

Division of Dynascan Corporation
1801 W. BELLE PLAINE AVE. • CHICAGO 13, ILL.
Canada: Atlas Radio Corp., 50 Wingold, Toronto 19, Ont.
Export: Empire Exporters, 277 Broadway, N.Y. 7, U.S.A.

COLOR TV

SERVICE CHARGE

GUIDE

Service shops are in business to make money. Some that service color sets, succeed in making a reasonable profit, while others don't. We made an investigation of current color-TV service charges, and came up with some facts and figures which should interest all servicemen.

Color-TV servicing, like many other types, is priced in one of several ways: by the hour, on a flat rate per job, at a rate based on parts which are replaced, service contract, and a service-call charge plus any bench service needed. In addition, prices vary among individual shops, and differ in various areas of the country.

For example, prices are higher in thickly populated areas than in rural areas. Much of this can be attributed to greater overhead costs; some in-

crease is dictated by the difference in labor costs in metropolitan centers. Western prices have a tendency to be higher than those in the East.

Color-TV calls and service are priced generally higher than for monochrome receivers. Partly, this is because more special test equipment is needed, and service charges must reflect this added cost. Another reason is the increased training and ability required of good color servicemen, thus raising their wage level.

Hourly rates are usually the basis for deciding by-the-part prices, although this method is used less than in former years. The time normally required to test and locate a defective part, plus the time needed to replace it, is determined; then the rate is computed from that. To these basic rates, most shops add a charge to cover disassembly, general clean-

ing, and adjustment.


Service calls usually cover the first half-hour of time in the home. Most shops then charge by the hour, for extra time needed. Some have come up with flat charges for standard jobs, such as a complete setup, where the time required is fairly well known in advance.

The accompanying chart reflects various methods of charging for color service. The prices shown are based on national averages, and may be more in some areas, or less in others. Your own service charges should be based on a realistic scale which takes into consideration your labor costs, overhead, and investment in special test instruments. With the chart as a guide, you can determine whether your charges are in line with the average. ▲

National Average Color-TV Service Charges

		for Color TV	for B-W TV
Hourly Rate		\$ 5.25	\$ 4.50
Home Service Call		6.25	4.25
Bench Charge—Min.		15.00	10.25
Bench Charge—Max.		27.50	21.50
Yearly Contract (incl. parts & CRT.)	1st yr.	72.00	55.00
	2nd yr.	120.00	75.00


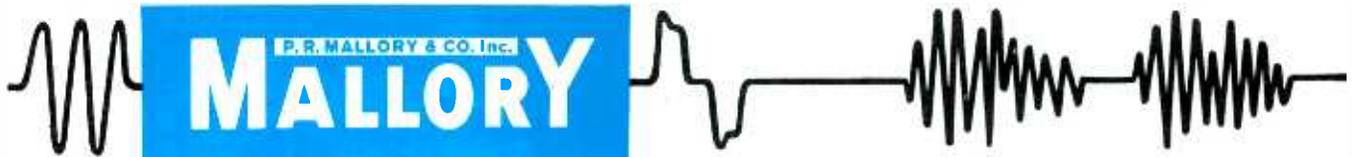
Note: The lowest prices charged centered around the northeastern section of the country, and are about 25% lower than the averages shown above. The highest prices, about 25% above the averages, are concentrated in the West Coast area.



Tips for Technicians

Mallory Distributor Products Company
P. O. Box 1558, Indianapolis 6, Indiana
a division of P. R. Mallory & Co. Inc.

Moisture and microfarads

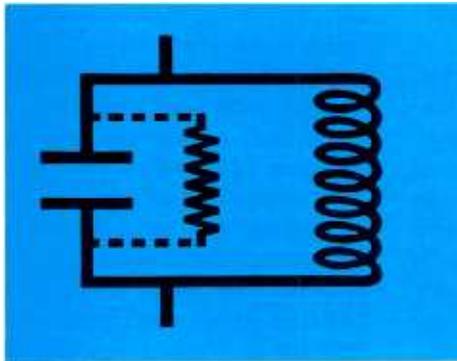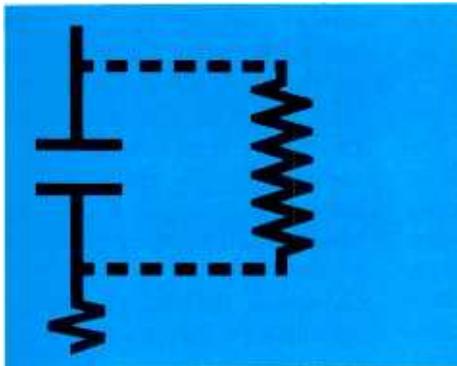

Humidity can cause serious troubles in capacitors used in many of the electronic circuits used today. Take a look at the equivalent circuit of a capacitor, and you can appreciate the source of these troubles. The D-C leakage path of a capacitor can be considered as a parallel resistance across the terminals. In a radio circuit, a capacitor with insulation resistance of as little as 25 megohms would give reasonable operation. But not in television and other sophisticated circuits.

Most television circuits have high impedance. Coupling, bypass and timing capacitors should have insulation resistance many times the circuit impedance. In a multivibrator circuit, for instance, capacitor leakage resistance alters the time constant of the timing network. In a ringing oscillator, frequency depends not only on inductance and capacitance, but also on the resistance of the capacitor leakage path.

What happens when ordinary capacitors are exposed to humidity? Sometimes there's an all-out failure. But even without a catastrophic short-out, a capacitor can begin to lose insulation resistance to the point where, in a television circuit, for instance, it's impossible to get the picture to lock in, verticals will be wavy, and the picture will bend at the top.

Our tip for the month: be sure of stable operation no matter how wet the weather, by using Mallory PVC capacitors. PVC stands for *plus value capacitor*. They're made with 100% Du Pont Mylar* dielectric. They contain no paper, no combinations of Mylar and paper, no substitutes for this most moisture-impervious of dielectrics.

PVC also stands for polyvinyl chloride . . . the flexible case on these new, blue capacitors that won't crack when you bend the leads. PVC's are exceptionally small for their ratings. You can squeeze 'em readily into crowded circuits. And they're even better in reliability, ruggedness and stability today than when we introduced them months ago.

Get Mallory PVC capacitors from your nearby Mallory distributor. He's the man to see for the best in capacitors, resistors, semiconductors, batteries . . . for *all* your component requirements.

* Reg. Trademark—E. I. du Pont de Nemours

How expensive are service calls?

Where can I get service?

When will color be cheaper?

What does warranty cover?

Why are the faces purple?

How many stations can I get?

answering customers' COLOR QUESTIONS

Be ready to stay one jump ahead of the anxious color-set owner . . .

Have you been stumped lately by inquisitive customers whose curiosity about color TV left you scratching your head for answers? If so, you're not alone; with the popularity of color TV growing by leaps and bounds, and with a large majority of TV stations transmitting either a little or a lot of color, this problem is cropping up among servicemen all over the country. To see what others are doing about it, let's peek in on a few scenes that have taken place at one or more shops in the past few months. These little bits of eavesdropping may prove very enlightening.

The scene is the color-TV showroom of a large midwestern TV dealer. Several color sets are sitting around the room, and even though the sun is bright outside, the light in the showroom is subdued. Two of the sets are playing—one, a table model, sitting on a decorative stand, and the other in a very fancy maple cabinet with doors.

A salesman and a customer are standing near the maple set, the customer with jacket unbuttoned and hand in pocket. The salesman has just extolled the virtues of this particular set, and the customer—with an all-wise look—continues the conversation something like this:

Customer: I'll agree, color-TV is much better than it used to be, but considering the price, I think I'll wait awhile. They're so expensive now, and later on they'll probably be as cheap as black-and-white.

Salesman: I appreciate your feel-

ings, but actually, the price of color sets has been pretty well stabilized for several years. Since they are already being mass-produced, there's little likelihood of savings in that area. Color-TV sets are more expensive than black-and-white simply because there's more in them. It just takes more circuits to process the more complex color signal than it does to handle a black-and-white signal. In spite of this, you *can* purchase a color set—for instance, this table model in the metal cabinet—for less money than some black-and-white models.

Customer: Sure, but that's still close to \$500, and I can buy a black-and-white set for one-third of that.

Salesman: But now you're talking about a portable, Mr. C, and the size of a color CRT alone dictates that a color set would not be easily portable. It is not likely that portable color sets will be a reality for several years, and when they are, the price will still be higher than that of a portable black-and-white TV, for the same reasons I mentioned before.

Customer: Okay, supposing I bought one? Could I use it on my screened-in patio in the summer time, like I do my black-and-white set?

Salesman: You could, but it wouldn't be advisable unless you have shades. You see, bright daylight "washes out" the colors, and would rob you of some of the enjoyment and benefits of your color picture. (Turning on several over-

head lights.) See? The colors were rather vivid on this set with the lighting lowered, but they appear a bit lifeless in the presence of bright light. (Turning the lights off again.)

Customer: Yes, I see now. It would be better in the living room. How about the antenna? Can I use the rabbit ears I've been using with my present set?

Salesman: Perhaps you can, but it wouldn't be wise for me to say for sure until we have a chance to use your particular antenna and actually see color shows from each of the stations you'll watch. Color sets require a more stable signal than monochrome sets, and faults (such as ghosts) which you can put up with on black-and-white will ruin your enjoyment of a color program. Occasionally, when stations are to be received from several directions, it is even necessary to install a rotator. In either case, you're sure to find the enjoyment you get from a color set worth the investment needed to get a proper picture.

Customer: What about service? I hear that will cost me more than for my black-and-white set.

Salesman: If and when your color set breaks down, the cost of repairs are usually a bit higher than with monochrome sets. A good color-TV serviceman will take more time to assure himself—and you—that the circuits in your color set are operating correctly. There is far more interaction among color circuits than is found in black-and-white sets, therefore they require special



6 NTSC
Standard Colors

Standard
Alignment Signals

Horizontal Bars

Vertical Bars

Crosshatch

White Dots

COLOR-APPROVED and NTSC for \$200 less!

Model 661—NTSC Bar-Dot Generator—\$349.50

Based on the same designs as Hickok's famous Model 656XC NTSC color bar generator, the NEW Model 661 is literally the answer for progressive service technicians who recognize the opportunities in color TV service but have been stopped by the cost of equipment. *The 661 is not a compromise—there are no short cuts—it's not "NTSC-like"; it is a complete instrument generating correct, 100% saturated, NTSC color signals complete with sync, blanking and burst at the right pedestal position and of the correct amplitude and phase, as well as demodulator alignment signals (R-Y, B-Y, -G-Y, G-Y 90°), plus dots and crosshatch.* In short, you

can expect the same kind of performance standards from the new 661 that have established Hickok's reputation with leading Color TV manufacturers as COLOR-APPROVED.

Compact, weighing just nine pounds, ideal for installation, convergence and in-the-home servicing, the new Model 661 provides everything needed for complete color service.

Ask your Hickok distributor to demonstrate the Model 661 for you . . . Write for our free booklet, "Why NTSC?" which explains why the NTSC standard tests are important. There is no obligation.

Equip your shop with these other Hickok Color-Approved instruments to provide your customers with complete color TV service:



615
Sweep &
Marker
Generator



CR33
Color
Picture Tube
Tester



656XC
NTSC Color
Bar Generator



660
White Dot-
Bar Generator




675A
Wide-Band
Oscilloscope



691
Marker
Adder

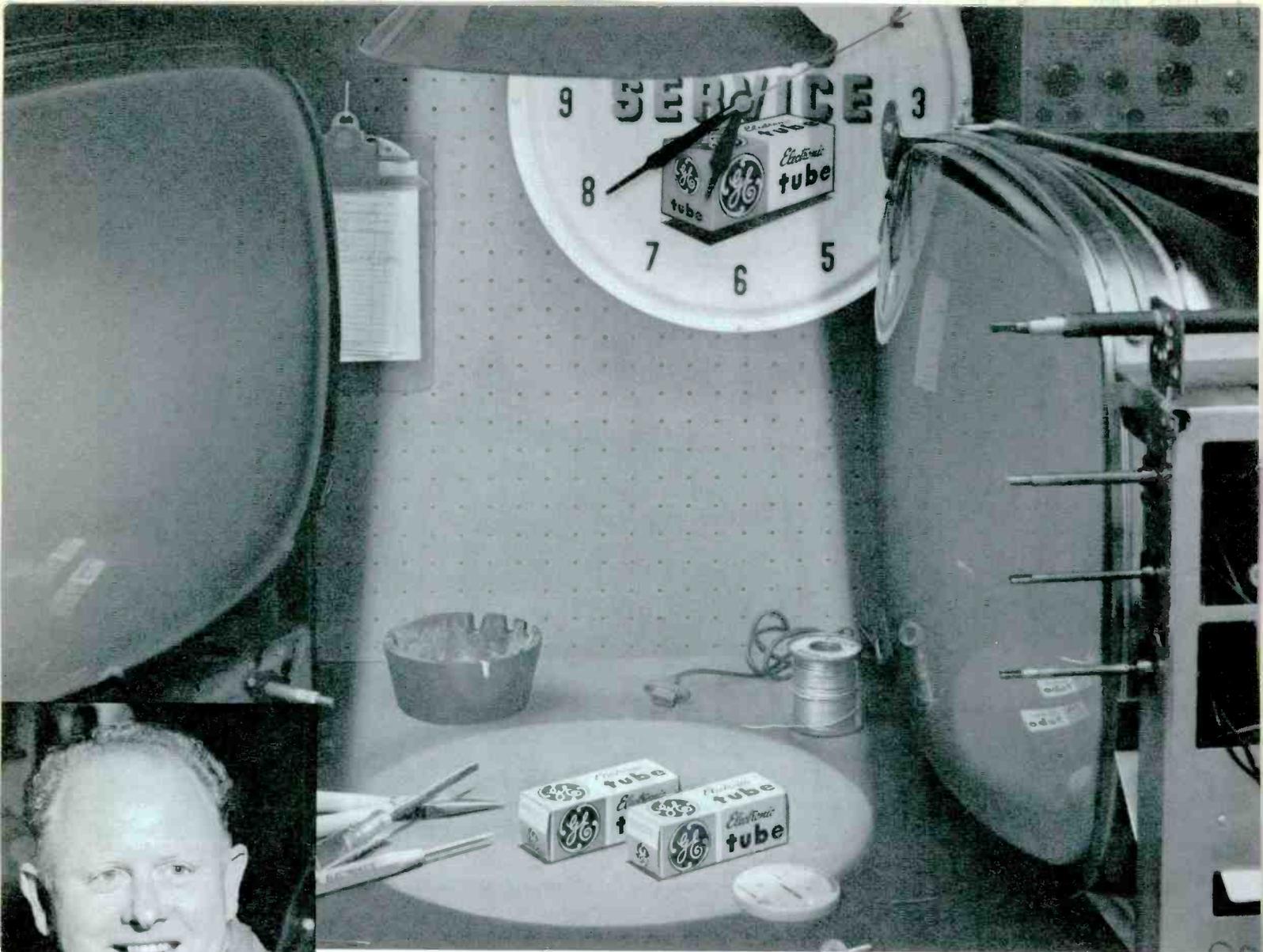THE **Hickok** ELECTRICAL INSTRUMENT CO.
10566 Dupont Avenue • Cleveland 8, Ohio



No callbacks tonight for Jim Liston, thanks to his in-warranty failure of less than 1% with G-E *SERVICE-DESIGNED* receiving tubes

"In this business, a reliable replacement tube can make you look like a hero . . . a callback due to in-warranty failure gives you a black eye, and wastes time and money. So, it's real simple, why I use G-E *SERVICE-DESIGNED* tubes in almost everything that comes into the shop. I can't afford callbacks."

Jim Liston is the owner of SOUTH CITY TV, South San Francisco, Calif. G-E *SERVICE-DESIGNED* "universal" replacement tubes help protect his profits—and his reputation. Here are just a few of their typical high-reliability features: (1) Rhenium-tungsten heaters increase tube reli-

ability up to 4½ times. (2) Three- and five-ply plate material provides uniform heat conduction and radiation. (3) Straight-sided bulbs give more uniform heat dissipation. (4) Tapered pins prevent socket damage; save time. (5) Tubes are interchangeable in all sets. General Electric Company, Distributor Sales, Electronic Components Division, Room 1743A, Owensboro, Kentucky.

Progress Is Our Most Important Product

GENERAL  ELECTRIC

care in servicing. However, the experience of recent years seems to indicate that color sets are built more soundly, since they must be precision instruments to handle color signals properly, and as a result, need less service.

Customer: But you still aren't telling me how much color-TV service is going to cost me.

Salesman: You can budget your service costs very accurately through the purchase of a service contract. For a specified amount, you can be assured of replacement of parts which become defective within the first year, and of any adjustment that become necessary.

Customer: Doesn't the warranty take care of that?

Salesman: The warranty provides for replacement of a defective color picture tube within one year's time, but you would normally have to pay for any service involved. Under a service contract, however, even the labor for replacing any of these parts is covered.

Customer: What happens after the first year? What do I do about service then?

Salesman: Many service establishments offer second- and third-year service contracts, at very reasonable cost. Our company offers a second-year service contract which covers all parts, all labor, and the color CRT. Some shops don't include the picture tube in second- or third-year contracts, and of course the price is somewhat less. Still another contract plan covers all labor, but you pay for parts at regular prices.

Customer: How do I know I can get competent service? Are there very many people who know how to fix color sets?

Salesman: Admittedly, color sets are more complicated than black-and-white. Recognizing this, certain leaders in the electronic industry have developed training courses and sessions which are available—sometimes at cost, sometimes free—to service groups, and to distributors for local showing to service people. Additionally, many forward-looking distributors are supplying training clinics of their own to familiarize servicemen with color sets, circuitry, and up-to-date techniques for troubleshooting them. Many test equip-

ment manufacturers are also offering local seminars stressing modern test equipment for servicing color sets. With all this effort being expended to train color servicemen, it is an unusual community that doesn't have at least one competent color-TV technician, and soon every shop will boast at least one color-TV serviceman.

... and so we step quietly out of the picture, leaving the color-TV salesman to consummate his sale, write up the order, and make arrangements for delivery. From the foregoing you can see, however, that simple factual answers are the best ammunition for combating doubts in the mind of a would-be color-TV customer.

Installing the Set


Mr. C bought the set. Deciding to go all the way, he picked the deluxe set in the French Provincial maple cabinet. The dealer's servicemen unpacked a new set from the crate, tested it thoroughly, let it "cook" a full day, and then delivered it to Mr. C's residence. Mr. C had decided to do without a new antenna system, so they had only to place the set in a corner of the living room, and connect the rabbit ears. With Mr. C as a very interested bystander (and occasional stumbling-block), one of the servicemen connected a dot-bar generator, demagnetized the set with a degaussing coil, and carefully touched up the convergence. Then, as the first color show began, Mr. C took over the operating controls of the new set. Let's listen:

Customer: I thought this show was in color. You said to turn up the color-control to get color, but it still doesn't work.

Serviceman: Perhaps you'd better recheck the fine-tuning control. To receive color, the tuner has to be carefully adjusted to the station frequency, at a point where the color part of the signal can get through.

Customer: Oh! There it is, but it sure looks gaudy; and how come the announcer's face looks so purplish?

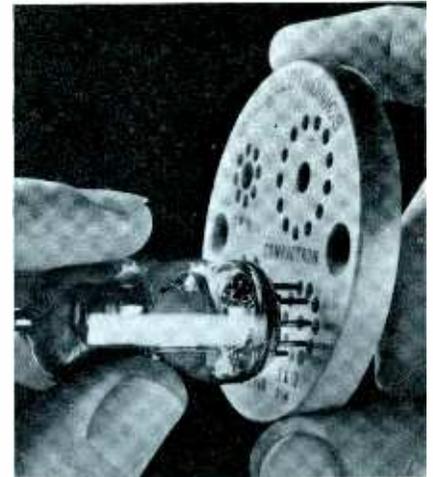
Serviceman: Well, the first thing to do is turn the COLOR TINT control down a little bit. If you overdo the color, it spoils the effect for you, while less color will give a nice



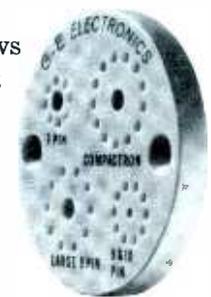 **ELECTRONICS**

New G-E Service Aid Provides Fast, New Way to Straighten Tube Pins

This original G-E Service Aid helps eliminate tube damage caused by bent pins; straightens pins on all 7-, 9- and 10-pin miniature tubes, large 9-pin and compactrons. Just insert tube pin base into pre-drilled bevelled holes and remove. Simple, fast, safe. This handy tool is small enough to carry in your pocket (2½" diameter), or mount it in your service case or on the bench with screws provided. Get it from your G-E tube distributor or mail coupon to Chicago warehouse address shown.



Progress Is Our Most Important Product

GENERAL  ELECTRIC

General Electric Company, Dept. 1743A
3800 N. Milwaukee Ave., Chicago 4, Ill.

Please ship prepaid:

____ ETR-3200 Multiple-Tube Pin Straightener,
60¢ each.

My check or money order is enclosed for the required amount plus any sales or use tax applicable in my area.

Name _____

Address _____

City _____

Zone _____ State _____

MAKE COLOR TV SERVICING

EASY AND PROFITABLE!

MODEL
CA-378



KINECOLOR CIRCUIT ANALYZER

\$19.95 DLR. NET

... INSTANT HOOK-UP FOR ANALYZING, TESTING AND ADJUSTING COLOR CRT'S AND ASSOCIATED CIRCUITRY UNDER ACTUAL OPERATING CONDITIONS ... WITHOUT CUTTING OR SOLDERING LEADS!

★ CA-378 makes it easy to:

- Adjust Purity
- Adjust Convergence
- Adjust Gray Scale and Tracking
- Measure Current
- Test Voltage
- Observe Signal Waveforms
- Connect All Test Equipment by Using Pin Jacks
- Use with Complete and Detailed Procedure Booklet

WRITE FOR LITERATURE TODAY!



ANTRONIC CORPORATION

2712 W. MONTROSE / CHICAGO 18 / ILLINOIS

DESIGNERS AND MANUFACTURERS OF ELECTRONIC COMPONENTS

Any of These Combinations
PLUS 75¢ EXACT-O-SPRAY NEEDLE
At Your Distributor for Only

\$196

1. TWO JETKLEEN TUNER CLEANER
2. TUNER CLEANER AND SUPER QUIK-FREEZE
3. TUNER CLEANER AND CONTROL CLEANER
4. TUNER CLEANER AND QUIKLEEN

Manufactured by

CHEM SPRAY CORPORATION • HOUSTON, TEXAS



pastel cast to the picture.

Customer: Okay, it's not so gaudy, but I still don't approve of a pastel purple announcer.

Serviceman: That's where the HUE control comes in. As you rotate it back and forth you'll notice the announcer's face changes from purple to green. You'll find a point between these two extremes where his face becomes a nice, soft flesh tone. Again, you'll want to be sure the color control is not too high.

Customer: You're right, it does look very nice now! But why must I adjust for flesh tone? Can't I use some other color? What would I do if there is no person on the screen to use as a guide?

Serviceman: Flesh tone is, generally speaking, the only color you can really depend on always being the same; that's why it makes a good reference. However, you can come pretty close, using an outdoor scene, if you adjust the hue control for a light blue sky and green grass. Then, if necessary, you can touch up the adjustment when there are scenes that involve people.

Customer: Well, I understand all that, so what's next?


Serviceman: If you mean, what else do you have to do to get color, there's nothing. The other controls operate just exactly as with a monochrome set. With a black-and-white program on the air, simply adjust the HOLD controls, BRIGHTNESS, and CONTRAST exactly as on your old set. Then, when a color show comes on, you have simply to turn up the color control, adjust the hue, sit back, and enjoy yourself.

Customer: Now, I'll just set this little lamp on top, and we'll be in business.

Serviceman: You'll want to be careful, Mr. C, about placing things on top of the color set. In some cases, metallic objects such as that lamp will affect the picture. See the pink tinge you now have at the top of the screen? That is caused by a slight magnetic field surrounding the lamp. Bring it over here to our degaussing coil and perhaps we can demagnetize it.

Customer: Gee, I had no idea these color sets were so sensitive. Do I have to be this careful all the time?

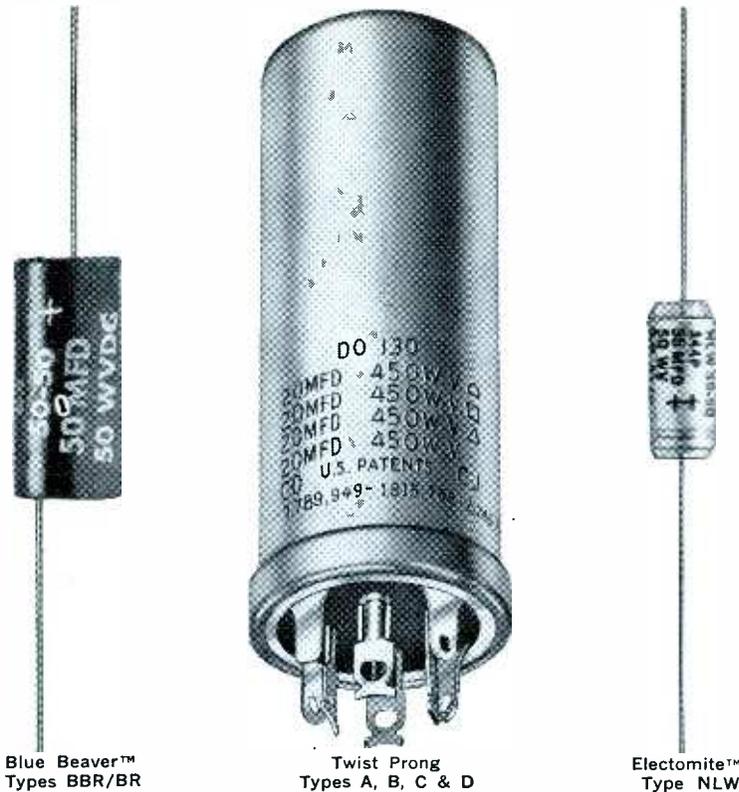Serviceman: Not necessarily, although if you suddenly notice some



so you think you know electrolytics!

(TAKE THIS QUIZ...RATE YOURSELF)

1. (True or False) In normal servicing, all 3 usually mount under the chassis.

Ans: FALSE. Twist Prongs, almost by definition, mount through the chassis. And the NLW is often mounted on printed circuit boards.

2. (True or False) The range of ratings of the 3 basic electrolytic types are clearly separate and distinct.

Ans: FALSE. Blue Beaver ratings are 3 to 300 V, 1 to 2000 mfd. NLW ratings overlap Blue Beaver ratings in many of the lower values. And Twist Prongs, as you know, are available in practically every rating imaginable.

3. (True or False) Although all 3 types are listed in the CDE Service Selector, the NLW is really a "special".

Ans: FALSE. All 3 are standard, stocked in depth by CDE distributors. In fact, the NLW has become such a favorite with technicians over the years Distributors tell us it's one of their fastest movers!

4. (True or False) Twist Prongs and Blue Beavers are designed for entertainment electronic replacements. The NLW, on the other hand, is so expensive that it should only be used in missiles.

Ans: FALSE. The NLW is designed for entertainment as well as in-

dustrial replacements. Use it where space is important (it gives your fingers "wiggle room") and whenever an extra margin of reliability is important. The price difference between the Blue Beaver and the NLW is actually only a few pennies.

5. (True or False) If you had the right answer to all these questions, you are, without doubt, an outstanding person with intelligence and wit far beyond your station. You are a credit to yourself, your family and your country. You are also a successful technician in your community.

Ans: TRUE.

CORNELL-DUBILIER ELECTRONICS, DIV. OF FEDERAL PACIFIC ELECTRIC CO., 50 PARIS ST., NEWARK 1, N. J.

CDE **CORNELL-DUBILIER**
the line that collects dollars, not dust!

GOLDMINE OF PRACTICAL INFORMATION

helps you get the most out of test equipment



192-page goldmine of practical information on electronic test equipment shows you how to select and use this equipment to the best advantage in many many applications. Only up-to-date book covering all the basic test instruments. Of benefit to both the newcomer to servicing and the old "pro".

- 1 Saves you money on the purchase of new equipment because you'll know what features to look for. You avoid buying equipment you don't need.
- 2 Saves you money in keeping your own test equipment in top condition because you're more familiar with what makes it tick. No more sending equipment back to the factory for adjustment or repair when you can do the job yourself.
- 3 Makes your present equipment more valuable by showing you new ways to use it.
- 4 Opens new fields of servicing profit because it makes you familiar with instruments used for radio and TV servicing, and industrial and audio.

Equipment covered is from simple VOM's and VTVM's through signal generators, oscilloscopes and other test equipment and helpful accessories. #308, \$4.00.

NEW! FOR EVERY SERVICEMAN

REPAIRING TV REMOTE CONTROLS by Leon Cantor & Harry Horstmann. Here's how TV servicemen can successfully meet the challenge of repairing different types of TV remote control systems! This single volume offers servicemen a comprehensive repair guide for every popular TV remote control system. Includes detailed descriptions of each type's circuit operation, repair methods and alignment techniques. Covers one, two, three and four button transmitters; power-line, lights, vacuum tube and transistor-operated types, and their respective remote receivers. Armed with this book, professional TV servicemen can turn "dogs" into simple house calls. #303, \$2.50.

INTERNATIONAL TRANSISTOR SUBSTITUTION GUIDEBOOK by Keats A. Pullen, Jr. Eng. D. (Scientific Staff, Ballistics Research Labs., Aberdeen Proving Grounds) direct substitutions only "possible substitutions deemed doubtful", that is they work only in some cases, were omitted. Thus, substitution guide is a 'safe' guide. — INDUSTRIAL ELECTRONIC ENGINEERING AND MAINTENANCE. #276 — \$1.50.

At your bookstore, parts distributor or direct

10 DAY MONEY-BACK GUARANTEE

John F. Rider Publisher, Inc. PF-11
A Division of Hayden Publishing Co., Inc.
116 West 14th Street, New York 11, N. Y.

Enclosed is \$_____ Please send:

- It's Easy To Use Electronic Test Equipment, #308, \$4.00
- Repairing TV Remote Controls, #303, \$2.50
- International Transistor Substitution Guidebook, #276, \$1.50

Name _____

Address _____

City _____ Zone _____ State _____

odd color effect in the picture, especially during black-and-white programs, check to make sure some magnetized object hasn't been placed near the set. Even moving the set to some other location will sometimes cause picture contamination, or color fringing. There, now the lamp doesn't affect the picture at all.

Customer: Yes, that's better, but what's this about moving the set? My wife will want to move it regularly, with the other furniture. Is there no way we can do it?

Serviceman: Yes, you can move it, but if there is any color contamination we may have to come out and, for a nominal charge, readjust the set to work properly in the new location.

Customer: Okay. If it's going to cost money, maybe we won't be moving furniture quite so often.

... and again we quietly withdraw and leave our installation technicians in full control of the situation. They have the answers to this customer's questions.

Servicing Color Sets

A few months later, Mr. C has settled into the routine of being a color-TV owner. But lately, the set doesn't seem to show as good a picture. So one bright morning, Mr. C picks up his phone and dials the number of his favorite service shop—those men who have always had the answers for him.

That afternoon, a neat, business-like serviceman is ushered into the presence of a somewhat sickly color set. Let's listen:

Customer: It's hard to say exactly what I think is wrong. The black except for those fringes around the

edges of everyone in the picture, but on color it just doesn't look right. What do you think?

Serviceman: Well, Mr. C, your set is obviously ready for a "tune-up." You've had it several months now, and parts have had time to age, resulting in a need for slight realignment. I'll get a pattern generator from my truck, and give the set a good checking over.

Customer: (when serviceman returns) How come you have to use special equipment?

Serviceman: I'll explain to you while I make some of the adjustments. Remember you mentioned the color slipping out of place? With this crosshatch pattern you see on the screen now, I can determine what sections of the picture need adjustment. For instance, up in this corner the red and green lines are both out of place. They should blend together with the blue line to make a white line, like it is in the center. With this pattern on the screen, I can see the result of my adjustments. There! Now we have white lines almost all over the screen, except for these little corners.

Customer: Why aren't the lines white all the way to the edges around the screen?

Serviceman: Manufacturing tolerances in the color picture tube and other circuits of the set make it well-nigh impossible to converge the lines all the way to the edge. However, when you're sitting at a correct viewing distance—say 12' or 14'—none of the action in the picture takes place in these corners, and any slight misconvergence is not noticeable.

Customer: What causes the screen

DON'T REPLACE CRYSTALLIZED RUBBER PHONOGRAPH DRIVE WHEELS UNNECESSARILY

brush on **NEW FONO-MAGIC***

eliminate slipping...dragging
SAVES DRIVE WHEEL INVENTORY COSTS TOO!



*FONO-MAGIC is a NEW compound of special rubber and carbide particles. When FONOMAGIC is brushed on metal drive surfaces, it forms a coat of live, pliable non-slipping rubber .000065 inches thick. Carbide particles imbedded in the rubber coating will scratch slipping rubber idler wheels, exposing live rubber and prolonging the life of the idler wheel. Just one bottle of FONOMAGIC is equivalent to the replacement of 100 drive wheels. Only \$1.95 dealer net. Sold at Better Jobbers everywhere.

manufactured by R-COLUMBIA PRODUCTS CO., INC. Highland Park, Illinois



HOW TO CUT THE COST OF POWER TRANSISTORS—WITHOUT CUTTING CORNERS:

simply say **Delco**

Now you can offer your customers inexpensive replacements for their Delco audio output transistor needs. The DS 520 and our new DS 525 can be used in place of the Delco DS 503 and DS 501 where low cost is a factor. Each of these low-priced transistors can produce 4 watts of output with top Delco reliability. They're ideal for the servicing of older car radios or for the experimenter or ham operator. The DS 520 and the new DS 525 will be a profitable addition to your basic line of Delco transistors: the DS 501 and DS 503—to restore full power audio output in all Delco

Radios; the DS 25 and DS 26 to cover small signal needs in Delco and just about every other auto radio or small portable on the market. How's that for a complete line of transistors? Oh, you need application and cross reference charts too? Look in the package. They come with all Delco transistors. All are available now through your United Delco electronics parts distributor.

Delco Radio automotive radio service parts and electro-mechanical devices are distributed nationally through **United Delco**.

DELCO RADIO, Division of General Motors, Kokomo, Indiana



to have that bluish look on black-and-white programs?

Serviceman: That is a function of certain other controls. I can set it up for what appears to be a pure white. You watch and tell me when I have it right.

Customer: Well-I-I, that's pretty close, but it still seems a little brownish. Could you make it more black?

Serviceman: There, I'll crank a little more blue into the picture. How's that look?

Customer: That's better. How come you didn't set it up like that in the

first place?

Serviceman: Well, everyone sees colors a little bit differently. The manufacturer provides these controls so we can make "custom" adjustments.

Customer: That reminds me—seems I have to adjust color controls several times an evening, to keep faces looking natural. What could be wrong with the set, to cause that?

Serviceman: Probably nothing is wrong with the set. Various shows are telecast under different lighting conditions; also, some of them are live, while others are on film or

video tape. All these things cause very subtle changes in the color. The stations and networks try to keep their studio lighting as consistent as possible, but its a hard job, and they have to keep working at it. Consequently, as you change from station to station and program to program, you'll find you must occasionally change the settings of the two color controls on your set. Now, a color show is on the air, so let's see what the colors look like. *Customer:* See the way those women in the picture have smeared lipstick? Can you do something to keep those colors from running together?

Serviceman: The trouble you see there is caused by ghosts, just like you had on black and white; the difference is, in color they are more noticeable. I'm sure we can clean up those ghosts, by putting up an antenna outside, or even in the attic. An attic antenna was installed for another customer of ours who lives only a few blocks away, and it works swell for them.

Customer: If I put up an antenna, could I get color shows from any other stations?

Serviceman: Yes, I can put up one of the latest-type antennas for you, and, in addition to helping clear up the ghost problems you have now, it will enable you to pick up color pictures from at least two other stations.

Customer: Won't that be pretty expensive? I've already got a lot of money tied up in this thing.

Serviceman: Not much at all, considering the added enjoyment you can get by receiving more programs in color. I think it would be a good investment.

Customer: Well, you may be right, I'll certainly give it some thought and let you know.

. . . and so we leave the scene.

The serviceman will pack up his pattern generator, pick up his tools, collect his service charge and leave.

By the way, Mr. C *did* buy a rather elaborate antenna installation, resulting in a greatly improved color picture. Because these people knew the answers to his color-TV questions, Mr. C became one of that dealer's best boosters, and convinced several of his friends to purchase color sets there. ▲

SAVE CUSTOMERS MAKE MONEY

THE INDUSTRY'S STANDARD
Most Widely Used Today by Professional Servicemen



FAMOUS DELUXE B&K CRT 440
CATHODE REJUVENATOR TESTER

For Black & White and Color

"Most valuable and useful" . . . "Wouldn't be without it" . . . "Pays for itself over and over again" . . . servicemen say. Quickly checks and corrects television picture tube troubles in a few minutes right in the home without removing tube from set. Gives new life to weak or inoperative tubes. Checks for leakage, shorts, open circuits and emission. Removes inter-element shorts and leakage. Repairs open circuits and low emission. Restores emission and brightness. Life Test checks gas content and predicts remaining useful life of picture tube. Makes new tube sales easier. Completely self-contained. Rich leatherette-covered carry-case. Net, \$74.95

TESTS AND REJUVENATES
all picture tubes at correct filament voltage from 1 to 12 volts

TESTS AND REJUVENATES
110° tubes and the new 19" and 23" tubes

TESTS AND REJUVENATES
color picture tubes. Checks each gun of color tube separately

Subscribe to New Picture Tube Information Service	UP-DATE YOUR B&K CRT WITH THESE ACCESSORIES
	Model C40 Adapter. For use with previous Models 400 and 350 CRT's—to test and rejuvenate TV color picture tubes and 6.3 volt 110° picture tubes. Net, \$9.95
See Your B&K Distributor, or Write for Catalog AP-20R	Model CR48 Adapter. For use with previous Models 400 and 350 CRT's—to test and rejuvenate 110° picture tubes with 2.34, 2.68, and 8.4 volt filaments. Net, \$4.95

B & K MANUFACTURING CO.
Division of DYNASCAN CORPORATION
1801 W. BELLE PLAINE AVE. CHICAGO 13, ILL.
Export: Empire Exporters, 277 Broadway, N.Y. 7, U.S.A.
Canada: Atlas Radio Corp., 50 Wingold, Toronto 19, Ont.




NEW AUDIO AMPLIFIER TUBE SUPPLIES FULL-RANGE TONE FIDELITY IN RECEIVERS

NEWEST addition to Tung-Sol's family of fine audio amplifier tubes is the type 4GZ5 pentode. Thorough exposure to realistic combinations of operating and environmental hazards during development shows this tube will lead its class in television, radio and high-fidelity service. Even after accelerated life testing, the subject remains full of pep, providing large power output with remarkably low distortion over the full audio range from

loud cry to subdued chortle.

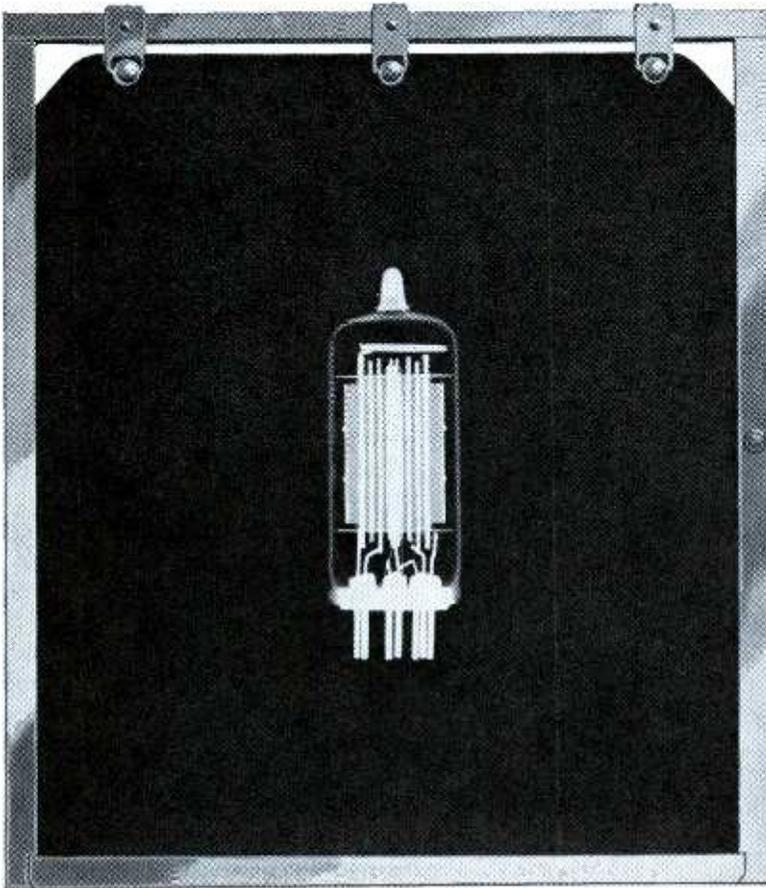Tung-Sol takes lavish parental care of this baby during its formative stages. Internal elements are welded and brazed on hospital-clean production lines after sterilization in bakeout ovens to prevent gas, leakage and spurious emission. Rigidized construction cures low-frequency rattles and other forms of tube distress. Alclad plates spread body heat evenly for efficient cooling.



FORMULA FOR GOODWILL

Customers will love the way this model tube makes stereo, radio and tv audio come alive. Foster good customer relations by adopting the 4GZ5 as your first choice in replacement tubes. Others in Tung-Sol's family of audio amplifiers are: 6CU5, 6BQ5, 12CU5, 6AQ5A, 6GK6.

 **TUNG-SOL**[®]
AUDIO AMPLIFIER TUBES

TUNG-SOL ELECTRIC INC., NEWARK 4, N. J.

Sy says:



Microphones—Part II

Last column we discussed the carbon microphone. This time we will discuss the crystal microphone and its cousin, the ceramic microphone.

Both the crystal and ceramic microphone are less expensive than the dynamic microphone which we will discuss in the next issue.

The crystal microphone has a high output and a good frequency response. The crystal unit consists of slabs of "Rochelle Salts" which are assembled and mounted so that the diaphragm will apply stress to the "crystal element" in accordance with the sound waves. The bending of the crystal element creates voltages on its surfaces, which are picked off by electrodes. It is a "capacitance" device having a value usually between 600 and 1,500 MMF. It is therefore, a high impedance device whose impedance varies with frequency.

The very similar ceramic microphone has most of the characteristics of the crystal unit, though the output voltage is slightly less. The ceramic unit will, on the other hand, withstand temperature and humidity ranges which might damage a crystal microphone.

Since the ceramic and crystal microphones are both high impedance devices, they can be connected directly to the grid circuit of a vacuum tube. For this reason, they are very popular for public address work, home recording and similar applications. Crystal or ceramic microphones can replace a high impedance dynamic type in most applications, although the performance may be a little different in response, range and level due partly to basic design and partly to any mismatch that might occur.

Ceramic units are not susceptible to nearby magnetic hum fields such as those from the amplifier chassis and this might favor the substitution.

In "exchanging" units, it is always important to compare the stated levels, response ranges and recommended load impedances. Don't go too far afield.

The Astatic Corporation offers a number of crystal and ceramic microphones. The newest being a ceramic mobile microphone Model 511 for Citizen Band application. The Astatic 330 Series units, which are widely used for tape recording and mobile installations, are available in either crystal or ceramic. The famous Astatic D-104, used by Ham operators the world over, is also manufactured as ceramic or crystal.



THE ASTATIC CORP.
CONNEAUT, OHIO • U.S.A.

IN CANADA: Canadian Astatic Ltd., Toronto
EXPORT: Roburn Agencies, N. Y. 13, N. Y.

MANUFACTURERS OF
PHONOGRAPH CARTRIDGES • NEEDLES

• PICKUPS • MICROPHONES • RECORDING TAPE

How's Color TV Doing?

Is its growth curve really taking an upturn?

by Forest H. Belt

A real bonanza is gaining momentum in the world of electronics—or is it? Some feel it is one of the biggest events in the consumer electronics field during recent years, while others feel it is a misfit, doomed forever to mediocrity. This would-be "boom" is Color TV!

Color TV was introduced several years ago with a large splash, and then sort of shuttled off to one side in favor of other things. Color had to share the limelight with such wonders as transistors and space-age electronics, so it's no wonder the "boom" never really came about. Let's examine the facts surrounding this unusual subject, and draw our own conclusions—are we going along with color TV, or not?

Strange Effects

Color TV has had some marked effects on more than one segment of the electronics industry, and these effects bear directly on feelings, today. Color has affected the manufacturer, the consumer, the broadcaster, and the serviceman.

The Manufacturer

When color first came along, a number of manufacturers plunged into the field, only to hastily withdraw when customer acceptance wasn't up to expectations. For several years, color television moved very slowly, with only one manufacturer—RCA—carrying the ball. A couple of years ago, several manufacturers decided color had reached a degree of acceptance, so they made color sets available in their line.

Next, Zenith culminated an ex-

tensive research program with a color chassis all their own. However, even their set used the tricolor CRT made by RCA, since it was the only such tube being produced.

Now, with color business picking up, other tube manufacturers are planning color CRT's—but more about that later.

The Consumer

Why did the consumer reject color TV for so long? There are a number of theories which have been advanced: One has it that color was given such a build-up, and then proved so poor, that no one wanted to pay the price for such disappointing results. Another idea is that people were already becoming used to large screens, and couldn't be satisfied with the masked-down picture on a 15" CRT. Some say the public was prediscouraged by the false starts that took place before a compatible system was developed. Others feel it could be because there just wasn't anything to watch in color—so why bother with it? Thus, the faults of color rejection are laid at the feet of almost anyone who had any connection with it; the circumstances just didn't seem right.

Now, all these faults have been overcome—is there anything left to hold color back? Price? Programming? Service? The sets? We'll see . . .

The Broadcaster

How has color affected the broadcaster? He is the one who provides the color-TV programs. Color productions are costly, and someone must pay the bill. Will it be the



15,000,000 MULTIPLE-SET OWNERS NEED

TRANSCEPTOR®

THE HOUSEHOLD SET COUPLER

ANYONE CAN INSTALL IN SECONDS



- improves reception for additional TV, color TV, FM, stereo FM
- provides most efficient signal delivery
- automatically matches impedance
- proved in more than 50,000 installations
- snaps on without tools
- eliminates extra antennas, rabbit ears
- packaged and designed for consumer appeal
- more than 2 million new customers annually

Foolproof, simple, rugged TRANSCEPTOR was designed especially for the fifteen million multiple-set owners in this country. Now, with easy-to-install TRANSCEPTOR, they can run any combination of TV and FM sets — two or more, one at a time or all at once — *off one antenna* without amplification in normal signal areas. And, because TRANSCEPTOR uses electro-magnetic pick-up instead of resistance splitting of the signal, the line is not cut, there is minimum signal loss, and better set-to-set isolation.

Result: More customer satisfaction. More sales. More profits.

*** INDIVIDUALLY PACKAGED ON SELF-MERCHANDISING COUNTER DISPLAY CARDS. AVAILABLE FROM YOUR LOCAL DISTRIBUTOR

\$2.98
RETAIL



AEROGAP CORPORATION
1680 VINE STREET
LOS ANGELES 28, CALIF.

**INSTALL
IN
SECONDS**



1. slide apart



2. slide on line




3. connect to set

MINIATURIZED
ELMENCO

Dipped Mylar*Paper Capacitors

New Low Prices!

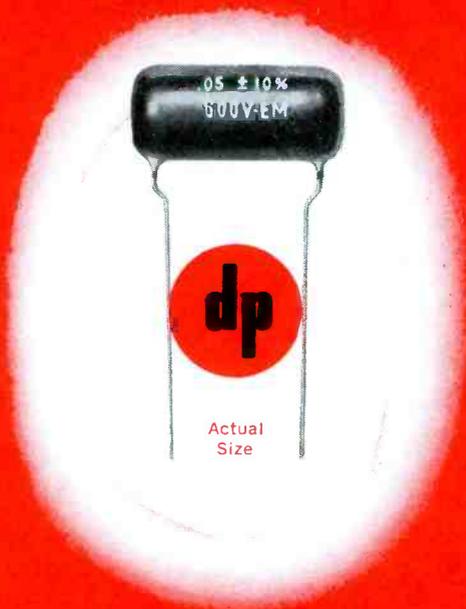

*DuPont Reg. Trademark

**First Choice with Service
Technicians Everywhere!
Over 89,754,000 Already Sold!**

Now being used in millions of television sets, radios, phonographs, electronic circuitry and military applications. ■ Operates at 125° C without derating. ■ Standard Tolerance $\pm 10\%$ ■ Missile Reliability ■ Completely moisture proof ■ Up to 50% smaller than other types.

DON'T ACCEPT SUBSTITUTES OR IMITATIONS!

Available at all authorized ARCO distributors in U.S.A.

ARCO

Community Drive, Great Neck, New York
Branches: Dallas 7, Los Angeles 35
electronics inc.

manufacturer, or perhaps the consumer? No, not directly, anyway. The broadcaster (network or local) must find *sponsors* who are willing to invest in the medium as a method of effective advertising.

This being the case, no wonder color telecasting was slow developing. The reasoning goes something like this: If the consumer hasn't a color set—no matter what the reason—he can't derive any benefit from watching a color show, so there is no special incentive to watch it. Without viewers, the program makes a poor advertising medium. If the sponsor can't get his money's worth, he simply will not pay the price for color shows. With no color shows, what's the use of owning a color set? . . . and we're back where we started.

It has been the job of progressive broadcasters to find and convince equally progressive advertisers that color-TV could and would become one of the more important and effective advertising mediums. We'll discuss the results in a moment.

The Serviceman

What has color TV done to and for the serviceman—you? For the serviceman who resists change, color has been a nemesis—something to be shunned, ignored, and discouraged. For more forward-looking technicians, color has presented a technical challenge, a chance for increased knowledge and prestige, and (not least) an opportunity for greater income.

Some shop owners tried (and still do) the old tack, "Leave it alone, and maybe it'll go away." It hasn't, nor does it appear that it ever will. Like it or not, color TV is real, and is growing by leaps and bounds. As the growth continues, those who accept and master the challenge are bound to profit. This has been the case in other parts of the electronics industry, and it can happen to you!


What Now?

No one can deny the existence of color TV, so let's look into some of the plans industry has for the future. By knowing what to expect from color, perhaps you can decide how your future will be affected. We'll see what's in store for that all-important four—manufacturer, con-

It used to take 2 men to pull
a color TV set into the shop...



BUT NO MORE

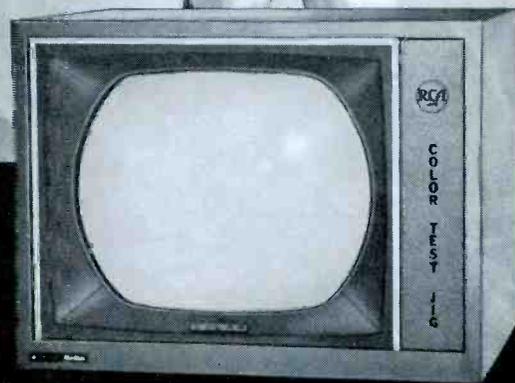

RCA COLOR TV TEST JIG

Cuts your manhours on Color-TV home service calls

Here is a real "must" for anyone servicing or planning to service color TV sets.

No longer must you send two men to a customer's home to pull in his entire color set. Now, one man can simply remove the chassis and bring it back to your shop for testing, troubleshooting and alignment in your RCA Color TV Test Jig.

Look at some of the extra advantages built into this money-saving unit:

- **Minimizes costly damage claims.** Pulling chassis eliminates possibility of scratching or damaging a customer's cabinet when transporting it to and from his home.
- **Saves time.** Eliminates need to reconverge a customer's set when chassis is returned. Convergence control panel on Test Jig provides static and dynamic convergence for CTC-10, CTC-11 and CTC-12 chassis.
- **Versatile.** Can be used with CTC-4, 5, 7, 9, 10, 11 and 12 chassis.
- **Safe.** Supplied with factory-installed safety glass and kine mask.
- **Complete components kit,** supplied with unit, provides all necessary service components and instructions for installing RCA Color Picture Tube.
- **Professional appearance.** Finish matches that of your other RCA test instruments.

The RCA Color TV Test Jig is available through your Authorized RCA Parts and Accessories Distributor. See him this week to find out how this versatile instrument can help you capitalize on the growing Color TV servicing market.

For information on where you may obtain the RCA Color Test Jig, and for additional specifications, fill out and mail the coupon below.

RCA PARTS AND ACCESSORIES, CAMDEN, N. J.



The Most Trusted Name in Electronics

RCA Parts and Accessories
P.O. Box 654, Camden, New Jersey

Please send me full specifications on the RCA Color TV Test Jig, and the name of the nearest distributor where I may obtain it.

Name _____

Company or Service Shop _____

Address _____

City _____ Zone _____ State _____



STEP ONE FOR COLOR TV SERVICING: THE NEW PRECISION E-450 COLOR BAR/WHITE DOT GENERATOR.

Simple to use, crystal controlled and voltage regulated, the PRECISION E-450 is a must for the busy serviceman. It combines the facilities to test and adjust the phasing, matrixing, linearity and convergence circuits in all color receivers. Three front panel controls and one simple antenna cable connection to the receiver under test afford a new high in ease of operation. The PRECISION E-450 is furnished complete with output cable and technical manual for only \$189.95 net. For complete details on this and other models, see your jobber or write today.

Patterns: Color bars, White dots, Crosshatch, V bars, H bars. **RF Output and Sound Carrier:** Available on channel 3 or 4; field adjustable. RF output 50 mv max. Sound 10% of picture carrier. **Simple 300-Ohm Connection** to antenna input terminals of receiver. **No External Sync.** Signals required to lock in test patterns. **Master Voltage-Regulated, Crystal-Controlled Oscillator** operating on 189 kc assures stability of displayed patterns. **Easier Convergence Set-Ups:** Separate vertical and horizontal bar patterns. **Optimum Convergence Adjustments:** Extremely fine, well-defined dot pattern. **Color Bars:** A reference test signal, precisely controlled, produces 10 equally spaced color bars across face of TV receiver under test. Included are the color bars corresponding to R-Y, G-Y, B-Y, I and Q signals.

PRECISION APPARATUS CO., INC., GLENDALE 27, NEW YORK

PRECISION SUBSIDIARY OF
RACAL ELECTRONICS
All Precision Test Equipment is Guaranteed For One Full Year

STEP TWO. VISUAL ALIGNMENT AND WAVEFORM ANALYSIS.



ES-150 Wide Band Oscilloscope with DC to 5 mc Response. VERTICAL CHANNEL: 3-stage push-pull, balanced DC amplifier. Sensitivity: DC: 70 mv/in.; AC: 25 mv RMS/in. Frequency Response: DC: within 3 db to 4.5 mc, within 5 db at 5 mc; AC: within 3 db from 1 cps to 4.5 mc, within 5 db at 5 mc. Rise Time: better than .08 μ s. Input Impedance: 1.5 megohms shunted by 23 mmfd. 4-Step Frequency-Compensated Vertical Input Attenuator; Frequency compensated. Vertical

Polarity Reversal Switch: Simplifies pattern reversal. HORIZONTAL CHANNEL: Push-pull output amplifier; sensitivity: 0.6 v RMS/in. Frequency Response: Within 3 db from 1 cps to 400 kc. Input Impedance: 5 megohms shunted by 23 mmfd. Cathode-Follower Horizontal Input Circuit: Linear time base 10 cps. to 100 kc. Provisions for external capacitor sweep to 1 cps. Net Price: \$149.95. Also available in kit form as PACO S-55: \$95.95.



STEP THREE. VISUAL SWEEP RESPONSE WITH ES-150.

E-410 Sweep Generator And Marker Adder. Frequency Coverage: 3 mc to 1080 mc in 6 bands (to 216 mc on fundamental). Continuously Variable Sweep Width: 0.3 mc on Band A to 0.30 mc on Band D. Band E varies from 0.16 mc. Output Impedance: 50 ohms terminated. Internal Blanking: Eliminates return trace. Automatic Gain Control: Regulates voltage amplitude on any band. Marker Adder: Superimposes marker "pips" on response curve; variable in size and width. Internal Phasing Control: Corrects phase shift between RF and horizontal scope outputs. Fixed Frequency Markers: Crystal circuit for accurate marking (one 4.5 mc crystal supplied). External Marker Input Connector: Permits use of external marker such as E-200C to provide variable marker "pips." Separate Line Filter: Minimum line cord radiation. Continuously Variable Attenuators: Control sweep width and vertical scope pattern. Net Price: \$159.95. Also available in kit form as PACO G-32: \$85.95.



STEP FOUR. ALIGNMENT AND VARIABLE MARKER.

E-200C Multi-Band RF Signal and Marking Generator. Frequency Range: 88 kc to 440 mc (to 110 mc on fundamental). Direct reading in 10 bands up to 440 mc; within 1% accuracy on all bands. 0-1000 Point Vernier Dial: Ideal for hand calibration and frequency spotting. Dual-Shielded RF Attenuators. Smooth, stepless RF control. Four Types of Signals: Unmodulated RF; modulated RF (400 cps); externally modulated RF; 400 cps output. Direct Reading Variable Modulation Control 0-100%: Triples signal utility as against obsolete fixed or stepped modulation of only 30% or 40%. Built-In AVC-AGC Bias Substitution: Overcomes alignment troubles arising from varying receiver AVG and AGC. Net Price: \$109.95.

sumer, broadcaster, and serviceman.

The Manufacturer

To begin with, the two current manufacturers have plans for better-than-ever circuits, with greater stability, greater dependability, and easier, more economical servicing. Production is at an all time high, although it is being curtailed by one problem—there are not enough color CRT's to go around.

RCA is the only builder of the tricolor picture tube that is now being used in all color sets. Those companies who are building sets under license can produce only as many sets as their numerical allotment of picture tubes. Zenith, too, is hampered by this shortage of CRT's.

The "drouth" is expected to end soon. Rauland, a subsidiary of Zenith, is tooling for color CRT's and hopes to be in production soon. Sylvania plans soon to produce a color picture tube, similar to the 21" round, shadow-mask, 70° tube being used now. National Video, on the other hand, is working on a 23" rectangular 90° CRT; this will be the first major change in color CRT's since the introduction of the 21" tube.

From overseas, a two-gun color CRT is being developed, which uses blue and red-orange phosphors. Exact plans for this tube, and its impact on the U.S. market, is not yet known. Time will tell.

Back home, there is discussion of a four-gun CRT, although no one has publicly committed themselves to produce or use it. The idea will be to use three guns for color, as is done now, and the beam from the fourth gun will fall on a regular black-and-white phosphor, to eliminate convergence problems for monochrome viewing. Once again, we'll see.

From all this you can see many things are in store for color TV. Other manufacturers are making plans for their own color chassis, and with more and improved CRT's available, this phase of color is well in hand.

The Consumer

Is the consumer going to buy color TV? All signs say, "Emphatically, yes." Even with the scarcity of CRT's slowing down some manufacturers, it now appears that sales

for this year alone will reach between 400,000 and one-half million. Planners are predicting sales in 1963 of 750,000. That's a lot of color sets!

In most of the major populations areas of the country, giant color promotions are taking place daily and weekly. The push is on to sell, sell, sell; and it is proving quite effective. Color sets in the New York and Los Angeles areas are moving at an all-time-high rate. If efforts mean anything, color sets will soon be almost as common as monochrome receivers.

Of course, much will depend on the consumer. Will he continue to buy durable goods? Will he accept the fact that color—real, true-to-life color—is here? Will the price tag hold him back? Those who claim to "know" answer "Yes, Yes, No," to these questions, in that order.

There is still a selling job to be done for color. The manufacturer, the broadcaster, and the serviceman are all going to have to assist in building the confidence the consumer has so far failed to feel toward color TV. It is not a feat any one of them is likely to accomplish alone. All are taking steps in this direction — the manufacturer through service-training programs, the broadcaster through more and better programming, and the serviceman through an enlightened viewpoint on the matter of customer relations. All are contributing to their future and that of color TV.

The Broadcaster

The season of telecasting which just began marks a milestone in the development of color TV. This season, all three major networks will be telecasting programs in color. NBC leads the way with a record high in color programming—much of it in prime night-time spots. Not including specials, NBC has devoted 68% of its prime time to color telecasts. ABC has joined the color parade with at least 3 regular weekly telecasts, and a number of specials. CBS is still holding out, but has indicated they have plans for this season, too.

On a more local basis, nearly 400 stations are now able to pass network colorcasts on to their viewers, while 150 local stations are equipped to originate color shows.

The latter requires quite an investment, and bespeaks the fact that these stations are sold on color. More are sure to follow.

Broadcasters are making concerted attempts to overcome one of the major consumer objections to color—that of constantly changing colors from program to program. Color is telecast by one of three methods: film, video tape, and live. Each has its problems.

Film made especially for color TV is produced under special conditions, and normally presents few problems; the colors are good, and

they stay that way. Older color films, adapted from movie films, are apt to have been less carefully produced, and may have certain color problems when rerun on TV.

Tape can be controlled rather closely, but trouble often occurs when parts of a show are taped at different times—sometimes even with different cameras. Cameras require extensive setup each time they're used, and it is very difficult to get them exactly the same two days in a row. Often, too, tape will be transferred to other tapes, and some quality is lost in the process.

The "tape of a tape of a tape" may leave much to be desired in the way of quality when viewed on a color receiver.

Live shows are probably most difficult to handle, from a standpoint of color. Lighting is very important, and must be controlled very carefully. Indoors, this can be done, but outdoor live shows are subject to the whims of weather, clouds, and other uncontrollable variations (even the humidity is a problem).

Great strides have been made in broadcasting, and more are yet to come.

The Serviceman

Surely by now you're wondering what's in store for you? The answer is—plenty! Plenty of work, plenty of learning, and for those who handle it right, plenty of profit.

Set makers are bending backward to provide information on color theory, color circuits, and practical troubleshooting methods. Test-equipment manufacturers are developing special instruments to simplify the task of keeping all those color sets working, and a number of them are providing free training clinics to help the serviceman better understand the test procedures necessary with color.

Other industry leaders are providing books, pamphlets, slide lectures, courses, and countless other aids, all aimed at helping the serviceman become a proficient color specialist.


Those servicemen who sell color-TV sets will be in on the spectacular rise in set sales that is anticipated. A boom in set sales is automatically followed by a boom in installations, and in sets which must be adjusted and regularly maintained. The opportunities are expected to abound.

Is It For You?

You're the only person who can answer this question. The opportunity has never been greater, and the means to carve yourself a slice of this melon are all around you.

You should be familiar with the trends, learn about the sets, study troubleshooting methods, and prepare to enter a new era in customer relations. We're launched on an era of Color TV, and I, for one, am going along. Are you? ▲

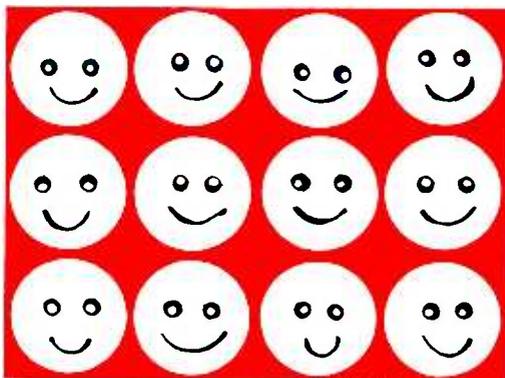look what happens when you
buy a
dozen
vu-brites...



You get the desk pen set free . . .

long-life easy-writing desk pen in a handsome satin-finished base for home or office use. Yours free with the purchase of 12 Vu-Brites.

You get twelve happy customers . . .

because 12 CRT's will be given an extra lease on life, 12 households will enjoy TV more, thanks to the brighter picture you (and Perma-Power's Vu-Brite) have provided.


what a deal!

For a limited time, Perma-Power is offering you this wonderful gift absolutely free with the purchase of 12 Vu-Brites at the regular price. Vu-Brites are the Briteners that really do a job—on parallel or series sets (Model C401 for parallel; Model C402 for series). They come colorfully packaged in individual boxes . . . and are priced at \$9.95 the dozen, net.


Perma-Power
COMPANY

3102 N. ELSTON AVENUE
CHICAGO 18, ILLINOIS

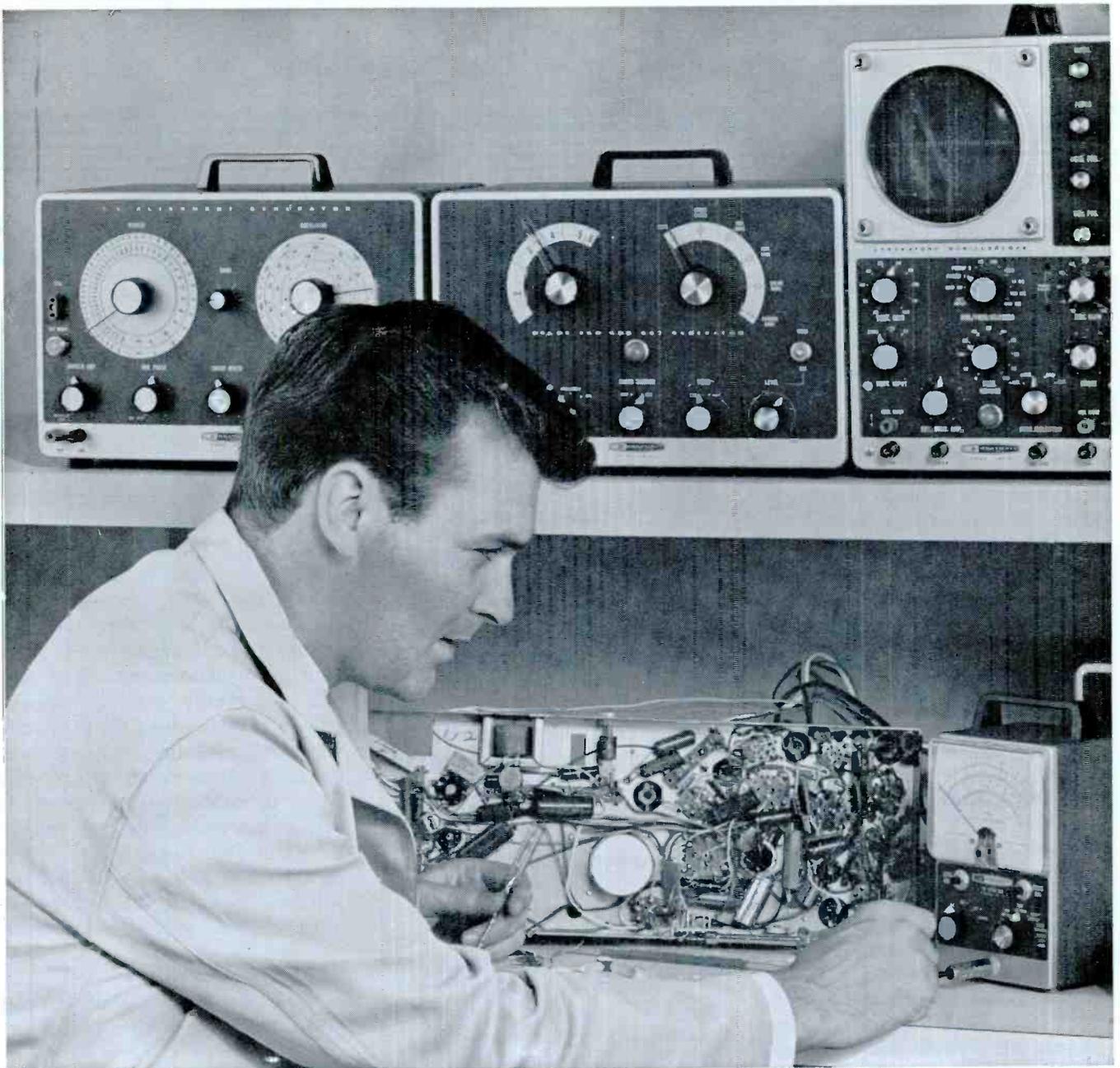*Hurry—this special gift offer will end when current stocks are gone.
Call your distributor today.*



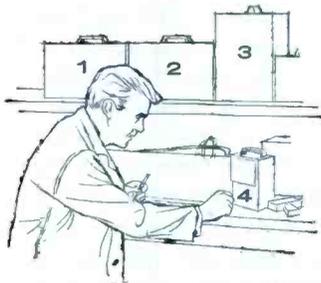This Heathkit TV service group can be yours for only \$22 per mo.



Only Heath, world's largest manufacturer of easy-to-build electronic kits, can offer test instruments with outstanding quality and performance, new professional styling and tremendous dollar savings! None other can match their great value. Equip your TV service bench with Heathkit Test Instruments as have so many other successful service technicians . . . enjoy far greater quality . . . at far less cost . . . by doing the easy assembly yourself!

Complete TV servicing facilities are yours with these new Heathkits: 1. Model IG-52 TV Sweep Alignment Generator, \$54.95; 2. Model IG-62 Color Bar & Dot Generator, \$64.95; 3. Model IQ-12 Laboratory Oscilloscope, \$76.95; and 4. Model IM-11 Vacuum Tube Voltmeter, \$29.95. Use Heath's convenient time pay plan . . . pay only \$22 mo. while you enjoy the equipment you need now! See the complete new line of professional Heathkit test instruments in the 1963 Heathkit catalog or at your nearest Heathkit distributor.



FREE 1963 HEATHKIT CATALOG

If you are not already on our mailing list, fill in and mail this coupon right away to receive this new Fall & Winter edition of the world's biggest electronic kit catalog. More than 100 new electronic luxuries have been added since the last issue . . . more than 250 in all, completely described and illustrated. Send for your free copy today!



HEATH COMPANY
Benton Harbor 68, Michigan

Please send my FREE 100 page 1963 Heathkit Catalog

Name

Street

City Zone State

CORONA

in the Cage and Out

A set that sizzles is cooking up trouble . . . by *Stu Hoberman*

Ask some technicians what to do about corona, and you may hear something like, "I simply spread dope over everything and hope for the best." Or perhaps, "There doesn't seem to be much you *can* do about it, except wait till the weather isn't so humid."

Feelings such as these are not really too surprising, because arcing and corona are the "plague" of the high-voltage cage. Some symptoms of corona are very difficult to understand; some are even difficult to spot. For example, a set was brought into a shop recently with a symptom of "wiggles all over the screen"—known to some old-timers as "waterfall effect," because the picture looks as if it is being seen through shimmering water. After much fruitless searching for sync trouble, or horizontal AFC trouble, the cause was finally traced to the high-voltage cage. There, with the shop darkened, a few spots of misty, blue "spray" could be seen sparkling between the flyback and the cage. This corona was radiating interference to the video circuits, causing the peculiar "waterfall" symptom. But what created this hard-to-locate phenomenon, anyway?

Corona (and arcing) generally occurs because the high voltage at some point has ionized the air gap between that point and ground. When air is the only insulator, moisture often contributes to the ionization. In television sets, however, high-voltage components are insulated with special dielectric materials, to supplement the safety afforded by physical separation. As a result, ionization—or corona discharge—can occur from deterioration of insulation, from improper repair techniques that damage insulation, or from actual breakdown

of certain high-voltage components. The greater high voltage used in color sets makes them even more susceptible to corona than monochrome receivers.

Three Types

You should understand that there are three distinct types of high-voltage breakdown. The first is symptomized by a hissing, sizzling sound, and is often accompanied by the sickly-sweet odor of *ozone*. This type of corona can be spotted only in a darkened place, as a rule, and very often continues undetected for quite some time, since it seldom bothers set operation.

The second type of breakdown is that described at the beginning of the article. You can see it in the light (not too bright a light) as it "sprays" itself from the high-voltage point to the surrounding ground areas, sometimes taking more than one path. This type of corona is commonly very bothersome to the set viewer, often disables the set completely, and can be very damaging to components under some conditions.

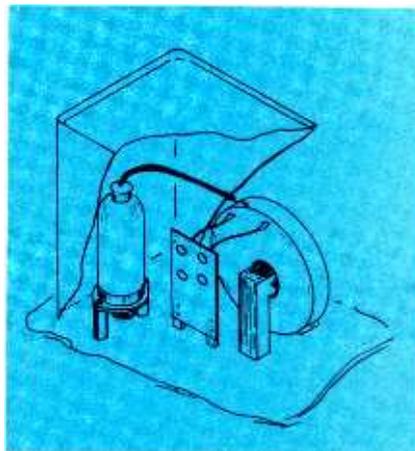


Fig. 1. Most common mounting for high-voltage sockets in older TV receivers.

The final, and worst, form of high-voltage breakdown is the loud cracking sound which occurs when high voltage completely breaks down the intervening insulation and air, and jumps viciously across the gap.

The important facts to remember about these three breakdowns are these: The latter type—the loud crack—occurs only when the high voltage is predominantly DC. The type of breakdown described second, the heavy corona, happens only in circuits where the high voltage is AC. The first type, the "unobtrusive" little corona spots, can occur in either type of circuit; it matters not whether the high voltage is AC or DC. But this type is the sneaky, easy-going one—the one you have to watch. Where it is, *the others are sure to follow*.

In the Cage

With these facts in mind, you can now identify the portion of the circuit which may cause a particular symptom. Since most corona and arcing problems appear inside the high-voltage cage, let's examine some of the possibilities for trouble.

One common symptom is that of DC arcing from the rectifier output to some nearby ground point. Modern tube sockets have done much to solve this problem in the immediate vicinity of the tube, but the filament leads still must be routed along the chassis, and must be wrapped around the core of the flyback transformer. If the insulation on the leads becomes aged or cracked, breakdown is likely to occur; the remedy is to replace the entire filament lead.

In sets without special sockets (see Fig. 1), arcing sometimes occurs from the socket terminals to the mounting hardware. An accumula-

What's the difference in loudspeakers that makes Quam so special?

All loudspeakers look pretty much alike, and may even sound pretty much alike—yet Quam speakers are different—in a way that's very important to you who use them!

the
difference
lies
in
**PERFORMANCE
RELIABILITY**

When it's a Quam speaker—you install it and forget it. Quam speakers are built to give long, trouble-free performance.

Quam's factory is a manufacturing plant, not merely an assembly shop. By making our own speaker parts, we can guarantee the quality of the materials that go into them. Our voice coils are centered precisely; each and every speaker is thoroughly tested; the product you get meets the standards we have insisted on for almost forty years.

Quam Quality Line speakers are enameled in gold—and while the color has no effect on performance characteristics, it symbolizes the quality and reliability that's built into every Quam speaker.

ASK FOR


QUAM

**THE QUALITY LINE—
for all your speaker needs**

QUAM-
NICHOLS
COMPANY

234 East Marquette Road
Chicago 37, Illinois

Put your TV Tuner Troubles

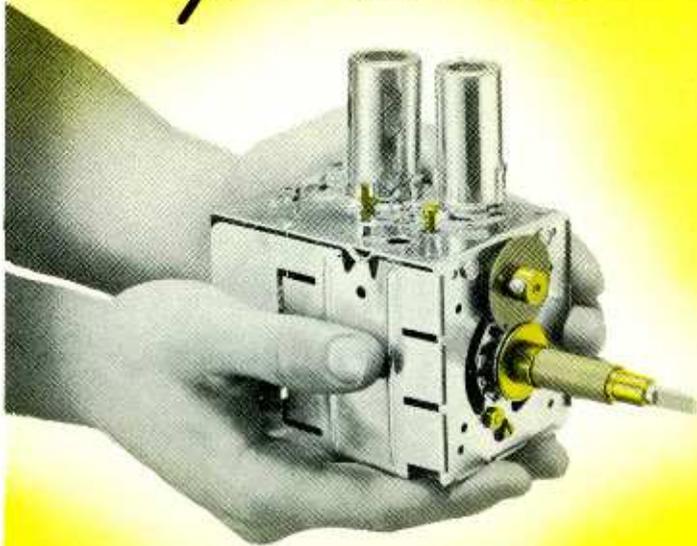

in Skilled Hands

CASTLE

TV TUNER SERVICE CENTERS

2. Compare the Value

Replacement tuners? Yes—we have them. But, even though we have the largest range, we give you top value by custom-overhauling your original tuner at the minimum cost for good performance and reliability. We offer a custom exchange replacement only when it is less costly than overhauling your original tuner. But remember, we have “universal” replacement tuners—priced from \$8.50 to \$15.95, with no exchange required. Send for lists.

For top value always, we recommend custom overhaul or exact original replacement over the so-called “universal” replacement tuners.

If you seek Value . . . you too will “Send it to Castle”.

Castle replaces all defective parts, (tubes and major parts are extra at net prices) and then aligns your tuner to the exact, original specifications.

Simply send us your defective tuner complete; include tubes, shield cover and any damaged parts with model number and complaint.

Send for **FREE** Mailing Kit and complete details.

See map for Castle Center Serving You



Pioneers in TV  Tuner Overhauling

CASTLE TV TUNER SERVICE, INC.

5701 N. Western Ave., Chicago 45, Illinois
 653 S. Palisade Ave., Cliffside Park, New Jersey
 In Canada: 136 Main St., Toronto 13, Ontario

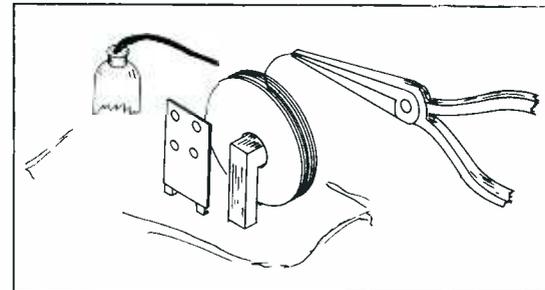


Fig. 2. Secondary winding of flyback transformer can sometimes be repaired.

tion of dirt or grease on the socket or its standoffs could furnish a path for first-stage corona, which would eventually build up to a complete arc-over.

Many times, the corona and arcing will result in carbonizing of the socket; this makes the condition worse, of course. Such carbonizing can be temporarily corrected by scraping the carbonized portion from the socket or supports, and coating the affected areas with corona dope. For a permanent cure, you must replace the socket and mounting.

Even more common than arcing in the cage is the problem of corona “spraying” from the flyback transformer to surrounding parts. This kind of corona (the damaging kind—remember?) can occur between any ground point and the high-voltage rectifier cap or lead, the windings of the flyback, the flyback terminals, or the horizontal output cap or lead. Extremely high-amplitude pulses of 15,750-cps energy exist all over these circuit components, just waiting for a break, a dust path, or a damp day to set them free.

Once the leakage point is located, it can sometimes be repaired simply by cleaning the surface with a good solvent, and then applying one or more coats of a good-quality corona dope. Evidence of this corona can be seen most plainly in a darkened room. A good method of detecting and locating breaks in the insulation of the flyback or the leads is to pass the blade of a screwdriver (well-insulated, for your own protection) over the suspected areas. Corona will become excessive around the blade when it is brought near the “weak spots”; even small breaks or pin-holes can be spotted by this method. Filling them with dope is easy.

If the flyback transformer be-

RCA—PIONEER OF COLOR TV—BRINGS YOU

ALL YOU
NEED FOR

COLOR-TV SERVICING



WR-64A



WO-91A



WR-69A



WR-70A



WR-99A

RCA Color-Bar/Dot/ Crosshatch Generator

Low-cost, lightweight, portable instrument that provides all essential Color-TV test patterns. Simple to operate: only 3 controls. RF output leads connect directly to antenna terminals of receiver; no external sync leads required. Crystal-controlled signals assure rock-steady patterns, free from "jitter" and "crawl." Extra-wide-range chroma control. Generates:

- **Color-bar pattern:** ten bars of color, including R-Y, B-Y, G-Y, I and Q signals spaced at 30° phase intervals for checking phase and matrixing, and for automatic frequency and phase alignment. Permits accurate alignment of the "X" and "Z" demodulators which are used extensively in RCA Victor and many other makes of color TV receivers
- **Crosshatch pattern:** a grid-like pattern of thin sharp lines for adjusting vertical and horizontal linearity, raster size, and overscan
- **Dot pattern:** a pattern of small sized dots facilitating accurate color convergence adjustments

\$189.50* with output cables.

RCA 5-Inch Oscilloscope for Color-TV

A wideband scope excellent for checking colorburst signals and general troubleshooting of wideband color circuits and other electronic equipment. Multiscale calibrated graph screen makes measurement of peak-to-peak voltage as easy as with a VTVM.

- New 2-stage sync separator assures stable horizontal sweep lock-in on composite TV signals
- Dual bandwidth: 4.5 Mc at 0.053 volt rms/in. sensitivity. 1.5 Mc at 0.018 volt rms/in. sensitivity
- Continuously adjustable sweep frequency range: 10 cps to 100 Kc
- 3-to-1 voltage-calibrated, frequency-compensated step attenuator for "V" amplifier
- Simplified, semi-automatic voltage calibration for simultaneous voltage measurement and wave-shape display
- Vertical-polarity reversal switch for "upright" or "inverted" trace display

\$249.50*, including direct/low capacitance probe and cable, ground cable, and insulated clip.

RCA Television FM Sweep Generator

Specifically designed for visual alignment and troubleshooting of color and black-and-white TV receivers, and FM receivers. The RCA WR-69A has pre-set switch positions for all VHF TV channels, FM broadcast band, and TV video, chrominance, and IF frequencies. The WR-69A has these important features:

- IF/Video output frequency continuously tunable from 50 Kc to 50 Mc
- Sweep-frequency bandwidth continuously adjustable from 50 Kc to 20 Mc on IF/Video and FM; 12 Mc on TV channels
- Output level—0.1 volt or more
- Attenuation range: TV channels, 60 db IF/Video, 70 db FM, 60 db
- Return-trace blanking
- Two adjustable bias voltages on front panel

\$295.00* including all necessary cables.

RCA RF/VF/IF Marker Adder

Designed for use with a marker generator (such as RCA's WR-99A) and a sweep generator (such as RCA's WR-69A), this instrument is used for RF, IF, and VF sweep alignment in both color and black-and-white TV receivers. In visual alignment techniques, it eliminates distortion of sweep response pattern. Important features:

- Choice of four different marker shapes provided by front panel switch for different types of sweep-response curves and for positive and negative sweep traces
- Provides very high-Q markers of high-amplitude and narrow bandwidth
- Complete front panel control of marker shape, marker amplitude, marker polarity, sweep amplitude, and sweep-trace polarity

\$74.50* complete with cables.

RCA Crystal-Calibrated Marker Generator

Supplies a fundamental frequency RF carrier of crystal accuracy for aligning and troubleshooting color and B&W TV receivers, FM receivers and other electronic equipment in the 19-260 Mc range. Combines functions of multiple-marker generator, re-broadcast transmitter, and heterodyne frequency meter.

- Highly stable output
- May be calibrated at 240 separate crystal check points—accurate calibration provided at 1-Mc and 10-Mc intervals
- Matched-impedance pad-type attenuator and double shielding of the oscillator provide effective attenuation of all frequencies
- Most-used IF and RF frequencies are specially indicated on the dial scale
- Sound and picture carrier markers available simultaneously

\$242.50* complete with output cable and phone tip.

RCA ELECTRON TUBE DIVISION, Harrison, N. J.



The Most Trusted Name in Electronics

*User Price (Optional)

From ELECTRONIC DISTRIBUTORS EVERYWHERE!

RESISTORS

Adjustable
Axial Lead
Composition
Flat
Lug Type

MIL Types
Power
Precision
Vitreous Enameled
Wire-Wound



QUALITY POTS

1/2 and 2-Watt
MIL Types
Commercial Units
Linear and Log



QUALITY

OHMITE COMPONENTS

RHEOSTATS

12 1/2 to 1000 Watts
Vitreous Enameled
MIL Types
Commercial



RELAYS

Plug-In
Enclosed
General Purpose



VARIABLE TRANSFORMERS

1.5, 3.5, 7.5, 20 Amps
Cased, Uncased
Portable
Tandem



TANTALUM CAPACITORS

Foil, Slug, and
Wire Types



WRITE FOR STOCK CATALOG 30
OHMITE
MANUFACTURING COMPANY
3644 Howard Street, Skokie, Illinois



comes defective as a result of the arcing problem just described, the defect will appear as an open circuit, in the secondary winding supplying the rectifier plate, or as shorted windings, which result in overheating of the unit. If a suitable replacement is not available, an emergency repair can be performed, as follows:

1. Unsolder the connections to the flyback transformer and remove it from the set.
2. Carefully remove the outer insulation to expose the first layer of windings. Unsolder the high-voltage lead.
3. Using a long-nose pliers, as shown in Fig. 2, carefully peel off the windings, layer by layer, until the break or short is uncovered. (To avoid impairing the efficiency of the transformer, do not remove an excessive amount of winding.)
4. Resolder the high-voltage lead and carefully tape it to the transformer with a good grade of plastic tape.
5. Using corona dope, paint the exposed windings evenly. Allow the dope to dry; then paint on a second coat before replacing the flyback in the receiver. However, it is wise to avoid excessive use of anti-corona preparations to eliminate arcing or corona.

Many high-voltage faults can be found by carefully inspecting the circuits for uneven or pointed solder connections, too-close component placement, or accumulated grease and dirt. Cleaning with a solvent and a touch-up with a soldering iron is often all that is needed to correct the trouble.

When soldering on or near the

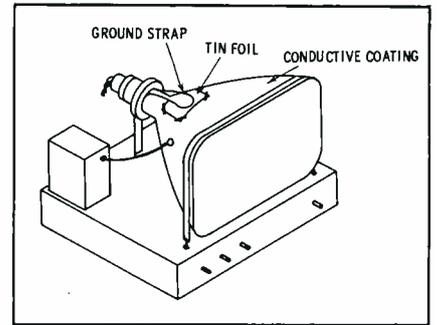


Fig. 3. Tin foil "patch" makes substitute for missing aquadag CRT coating.

socket terminals of the high voltage rectifier, be sure the soldered connection is round and smooth and no solder peaks are formed as the iron is lifted from the joint. Wire terminations should be cut very close to prevent possible arcing. You must also be careful that the hot solder tip doesn't accidentally touch a wire, or the flyback, leaving behind a melted opening where corona can develop.

Outside

Arcing and corona problems which develop outside the high voltage cage usually occur between the anode lead of the CRT and the chassis or mounting brackets, between the bell surface of the CRT and its grounding strap.

Arcing from the CRT anode lead is usually caused by deteriorated insulation, and is best remedied by complete lead replacement. This usually involves soldering inside the cage, where the precautions mentioned before should be taken.

Arcing from the anode socket to the CRT surface can result from an accumulation of grease and dirt. To correct this condition, remove the anode lead, being careful to discharge the CRT; then clean the area surrounding the anode socket with

QUICK and LASTING

When You Use

HUSH®

Chemically-Electronically, engineered for Tuners and Switching Mechanisms.

When New HUSH is applied it will wash-away that dirt, leaving clean and positive contacts protected by a lasting lubricant. New HUSH is made from the finest solvents and it contains Electro-Silicone oils.

6 oz. Spray can. Also available 2 oz., 8 oz., 32 oz. containers
FREE 6" Plastic Extender With Every Can


EVER-QUIET®

Since 1949

VOLUME CONTROL AND CONTACT RESTORER

EVER-QUIET is a free-flowing liquid that leaves no powder residue. Scientifically designed to seep around the shaft and penetrate the control or potentiometer, cleaning the contacts and leaving a safe protecting film. Harmless to metals, wire or carbon.

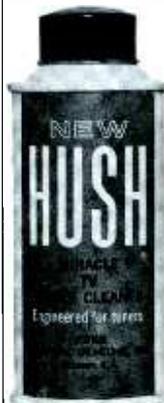2 oz. Bottle & dispenser. Also available—6 oz. Spray can



CHEMICAL ELECTRONIC ENGINEERING, INC., Matawan, New Jersey


Why take hours to troubleshoot when PHOTOFACT® does it for you in minutes!

IF YOU'RE NOT NOW A PHOTOFACT LIBRARY OWNER, YOU'RE MORE THAN PAYING FOR IT IN THE TIME YOU LOSE

HERE ARE JUST A FEW OF THE DOZENS OF WAYS PHOTOFACT SAVES YOU TIME



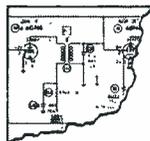CircuitTrace® saves countless hours of foil tracing time. This exclusive Sams system pinpoints junctions and test points on schematic and printed board.




Famous Standard Notation Schematic saves valuable hours—always uniform, accurate, complete for every model.

COMPONENT CONNECTION	
WIRE	VERTICAL OUTPUT
Original Connections	
Blue Green Red	
Blue Yellow Red	
Blue Green Red	
Blue Red Green	


Exact Terminal Connections are indicated—no need for trial-and-error methods—a real time-saving feature.



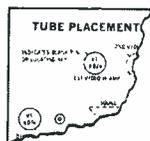
Field Servicing Notes spell out locations of adjustments for speedy "in home" servicing. Saves time spent in hunting for hidden adjustments.



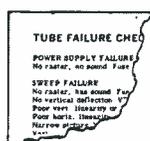
Tube Location Guide enables you to locate and replace proper tubes in seconds—a big time-saver on most repair jobs.



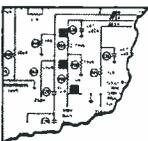
Tube Failure Check Charts spell out probable tubes responsible for failure—no need to waste time studying circuitry.



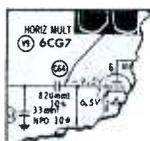
Clear Parts Symbols with values and associated information are shown plainly on the schematic—no time wasted in cross-reference "look-up."



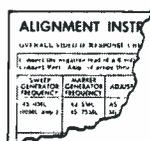
Waveform actual photos are shown on schematic for quick comparison of patterns on your scope. No time wasted in guesswork.



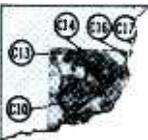Unique Alignment System eliminates guessing; you get complete instructions with response curves, how to connect test equipment, proper adjustment sequence.



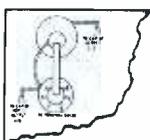
Full Photo Coverage of the actual equipment makes identification of all components and wiring easy—you can see everything.



Terminal Identification saves you time; transformer and coil terminals quickly identified by color code or basing diagram shown on schematic.



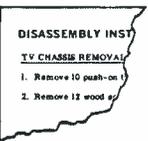
Auto Radio Removal instructions show you step-by-step procedure for removal of even the most complicated models—a big time-saver.



Disassembly Instructions, step-by-step, help you remove difficult chassis, sub-chassis, and assemblies in minutes.



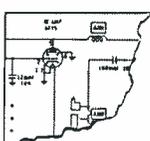Dial Cord Stringing instructions save you up to an hour or more of time and headaches on a single job.



Alternate Tuner Data—separate schematics, alignment data and parts lists are provided—no time wasted interpreting various tuner versions.

OWN THE TIME-SAVING, PROFIT-MAKING PHOTOFACT LIBRARY

FREE FILE CABINETS

THIS EASY-BUY WAY

The PHOTOFACT Library more than pays for itself from the first day you put it into your shop. It gives you instant time-saving help on more than 52,000 listings of TV, radio, hi-fi and other home-entertainment equipment—virtually any model made since 1946. You can own a PHOTOFACT Library this special Easy-Buy way:

- NO INTEREST
- NO CARRYING CHARGES
- ONLY \$10 DOWN
- UP TO 30 MONTHS TO PAY

You get FREE file cabinets with your PHOTOFACT Library—so you have all you need for time-saving, money-making service work right at your fingertips. Get the full PHOTOFACT Library details today.



You'll find dozens of other invaluable time-saving features in PHOTOFACT. Own the complete Library—so you can put your hands instantly on all the quick help you need for any job on your bench! Start a Standing Order Subscription today—keep up with current model output! See your Sams Distributor for full details or send coupon now.

SEND COUPON

HOWARD W. SAMS & CO., INC.

Howard W. Sams & Co., Inc., Dept. 7-L2
4300 W. 62nd St., Indianapolis 6, Indiana

- Send full information on Easy-Buy Plan
 Enter my Photofact Standing Order Subscription

My Distributor is: _____

Shop Name _____

Attn. _____

Address _____

City _____ Zone _____ State _____

NEW!
DUMONT
FAIRCO
MARK III
FREQUENCY METER



... a portable, low-cost, simply operated secondary frequency standard with accuracy exceeding FCC requirements! With one small unit you can now measure every frequency in the allocated FM spectrum—in central operations or in the field. A single cable connection allows exact adjustments of both transmitter and receiver in a matter of seconds. Settings are quickly and simply made for performance without error. A new "must" tool for 2-Way Radio service firms from the pioneer of communications. Write for details.

- Low price.
- Accuracy exceeding FCC requirements.
- Satisfies all allocated frequencies in FM band.
- Operates on 110 VAC, plus 6 or 12 VDC inverter.
- All circuits locked to a single temperature crystal standardized against WWV.

Price \$650.00

the servicing
do-all
TRANSISTORIZED
"FREQ" METER



FEATURES

- 24 r-f/i-f channels and an audio signal in one, pint-sized package.
- 25 to 470 Mc spectrum plus i-f channels in the 100 kc to 100 Mc range.
- Defies obsolescence—permits addition of new channels.
- Signal generator output for receiver servicing.
- Checks adjacent—or split-channel gear with excellent precision.
- Compact, transistorized, life-long battery powered—requires no a-c connection.

The most versatile servicing tool in the industry—now a standard. Lightweight—8 pounds, rugged construction for portability. The ideal Freq Meter to perform functions such as: Carrier frequency error indication, relative transmitter field strength, modulation deviation measurement, receiver r-f alignment generator, aural monitor of modulated signal and many others. Write for details.

Price \$435 with one RF Crystal

DUMONT REPRESENTATION FROM COAST TO COAST



ALLEN B. DUMONT LABORATORIES
 Divisions of
 Fairchild Camera and Instrument
 Corporation
 750 Bloomfield Ave., Clifton, N.J.

TABLE I

Symptom	Probable Cause	Remedy	
Arcing from high-voltage rectifier socket to cage, chassis, or mounting hardware.	Inside the Cage Accumulation of dirt on socket terminals, or on mounting hardware.	Clean socket terminals and mounting hardware with solvent; if necessary, apply corona dope. Cut leads close to terminals and smooth solder peaks with a hot iron.	
	Solder or wire "peaks" on socket terminals causing arcing between these points and ground. Socket mounting supports carbonized.	Scrape or sandpaper socket mountings to remove carbon; then clean with solvent, and paint with corona dope. Replace with equivalent resistor.	
	Filament limiter resistor or anode bleeder resistor breaking down.		
Internal arcing in high-voltage rectifier tube.	Tube elements shorting. Rectifier output shorting or arcing to ground.	Replace tube. Repair arcing as previously described.	
Internal arcing or burning in flyback transformer.	Open or shorted secondary windings.	Repair transformer (as previously described) or replace with equivalent.	
Arcing from filament winding to flyback core.	Outside the Cage Insulation on filament lead deteriorated.	Replace lead with equivalent.	
	Corona between CRT external conductive coating and ground.	External conductive CRT coating worn away.	a. Tape tin-foil square to CRT beneath ground strap. b. Use commercial aquadag to replace coating.
	Corona from anode socket to CRT surface.	Accumulation of dirt and grease.	Remove anode lead, discharge CRT; then use solvent to clean adjacent area.
Arcing from CRT anode lead to ground.	Lead insulation deteriorated.	Replace lead (and anode cap, if needed).	

a suitable solvent, and replace the lead.

Corona between the CRT surface and the ground strap (Fig. 3) results from erosion of the conductive external CRT coating (aquadag) or insufficient tension of the ground spring. As shown in Fig. 3, an emergency repair can be made by taping a sheet of tin foil to the CRT directly under the ground strap. Al-

ternatively, commercial aquadag solutions are available, which can be painted on to replace any defective portion of the coating.

Table I is a summarized listing of high-voltage problems, together with probable causes and cures. By using this chart and applying your knowledge of the facts behind corona, no high-voltage fault will be able to "throw" you! ▲

PRECISION TUNER SERVICE

P. O. BOX 272

1200 S. WALNUT ST.


BLOOMINGTON, IND.

EDISON 99653

7.50
 V or U


COMBO 9.95 PLUS POSTAGE

6 MONTH WARRANTY

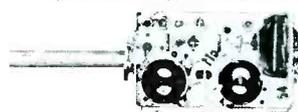

All Types T.V. Tuners Cleaned, Repaired and Aligned to Factory Specifications. Same day in shop service on most Tuners. Price Includes Minor Parts, Major Parts at Cost Price. We use Original Parts if possible. State Make Model and Enclose all Parts and Tubes. Pack Well and Insure.

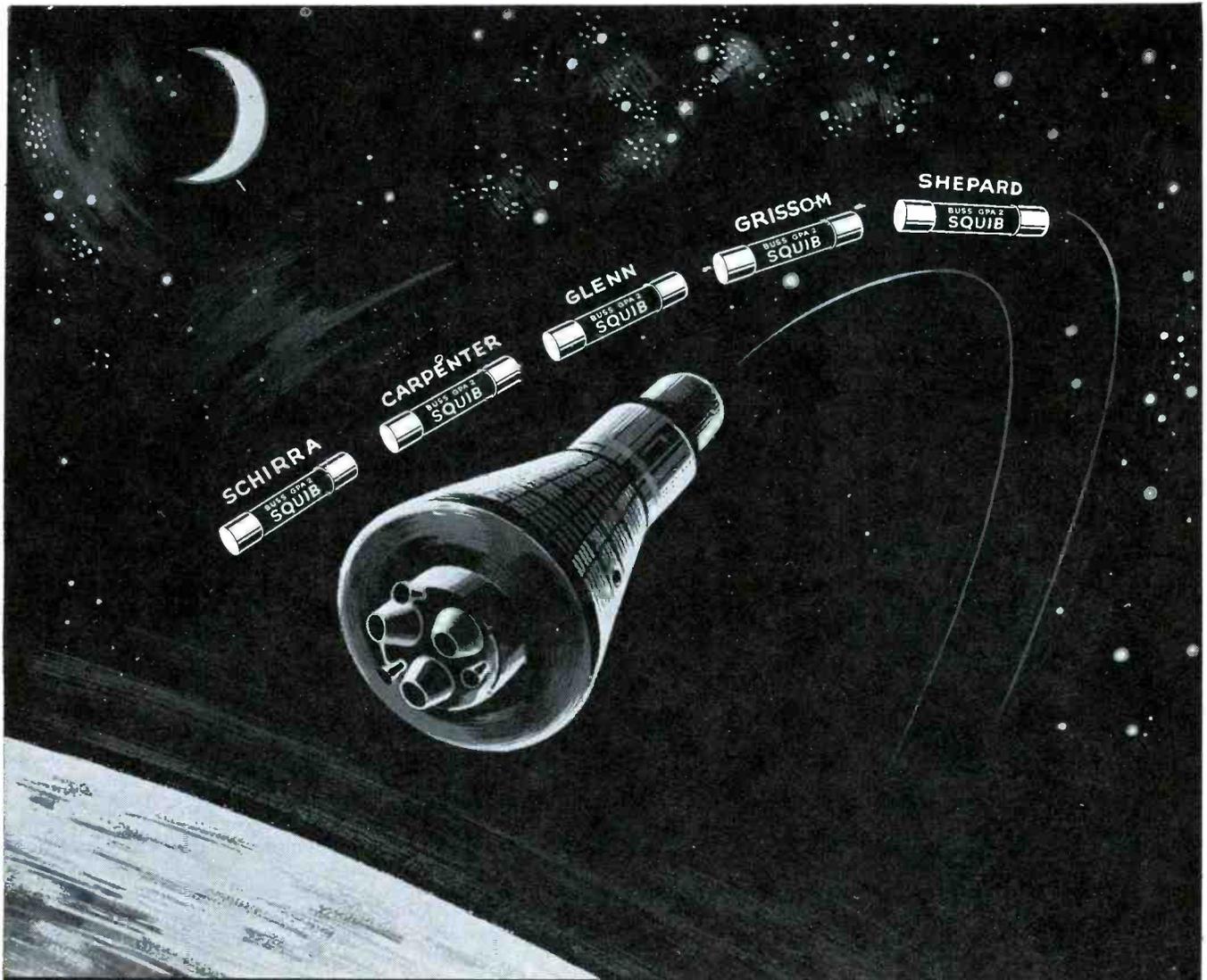ALSO HAVE LARGE STOCK OF EXCHANGE TUNERS, WRITE FOR TYPES AND PRICES.



**BUSS FUSES FLEW INTO SPACE WITH SCHIRRA AND ALL U. S. ASTRONAUTS—
and by proper functioning helped bring them back safely!**

When a man's life and scientific data relies on the accuracy and dependability of every component in a spacecraft,—chances with unknown or improperly engineered components cannot be tolerated.

That's why the Space Age engineers turned to BUSS for the fuses used to protect the electrical circuits in the spacecrafts.

This is not surprising when you consider that BUSS maintains the largest staff of fuse engineers and the largest fuse testing laboratory in the world.


Possibly, your fuse application is not as dramatic as America's manned space shots but you, too, can be sure of the finest, most dependable protection by standardizing on BUSS fuses.

To make sure BUSS fuses will operate as intended under all service conditions,—every BUSS fuse is individually tested in a sensitive electronic device that automatically rejects any fuse not correctly calibrated, properly constructed and right in all physical dimensions.

BUSS

BUSSMANN MFG. DIVISION
MAKERS OF THE COMPLETE LINE OF
FUSES OF UNQUESTIONED HIGH QUALITY

McGraw-Edison Co. • St. Louis 7, Mo.

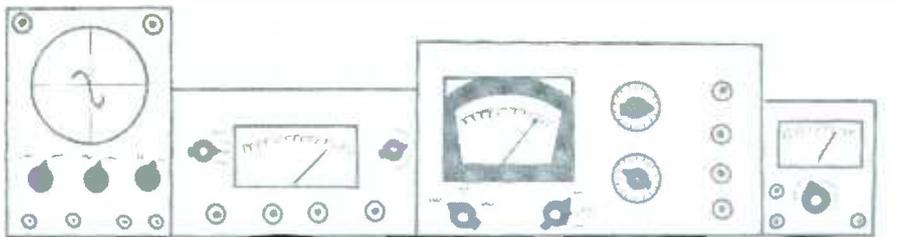

NOTES ON TEST EQUIPMENT

by Forest H. Belt

Extended Scope



Fig. 1. Extended-range oscilloscope will respond to frequencies beyond 7 mc.

Portability is one of the key features of SENCORE's new Model PS120 wide-band 3" oscilloscope. The unit, with its test probe, can be seen in Fig. 1.

Specifications are:

1. Power Required—105-125 volts, 50-60 cps, 82 watts (10 watts "Standby").



Fig. 2. Closeup of vertical attenuator showing multiplier reading in window.

2. Vertical Amplifier — Frequency response, within $\pm 1/2$ db from 20 cps to 6 mc, down 3 db at 7.5 mc; sensitivity, 35 mv rms for 1" deflection (350 mv rms through low-cap probe); input loading, 2.7 megohms shunted by 99 mmf, 27 megohms shunted by 9 mmf through low-cap probe, 2.7 megohms shunted by 27 mmf at auxiliary vertical input jack; maximum input voltage, 1,000 volts peak to peak in presence of 600 volts DC.
3. Horizontal Amplifier—Frequency response, within ± 3 db from 45 cps to 330 kc, within ± 6 db from 20 cps to 500 kc; sensitivity, .5 volts rms for 1" deflection; input loading, 40K-ohms to 200K-ohms shunted by 80 mmf; maximum input voltage, 15 volts peak to peak in presence of 400 volts DC.
4. Sweep Ranges—15 cps to 150 kc in five ranges; preset TV vertical and horizontal positions; adjustable automatic sync to 7.5 mc.
5. Cathode-Ray Tube — 3RP1, 3" face, green trace; covered by green graticule.
6. Controls and Terminals — Eight potentiometers: INTENSITY, VERT POS, FOCUS, SYNC, HORIZ GAIN, HORIZ POS, VERTICAL INPUT (gain), and HORIZONTAL FREQUENCY (vernier); two rotary switches: VERTICAL INPUT (multiplier) and HORIZONTAL FREQUENCY; two slide switches: OFF-STBY-ON and VERTICAL INPUT SELECTOR (both inside lower panel); HORIZ INPUT and AUX VERT INPUT pin jacks; pilot lamp; permanently connected cable with probe.
7. Size, Weight, Price — $8\frac{1}{2}$ " x 7" x 11"; 12 lbs.; \$125.50.

The Model PS120 provides the serviceman with a lightweight wide-band scope which he can use in both the shop and the home. The bandwidth of this unit is much wider than ordinarily found in a service-type scope, and enables the serviceman to see unusually detailed waveforms in both monochrome and color TV sets. The special probe, which is permanently connected to the unit, includes a detachable 10:1, low-capacitance tip for checking waveforms in sensitive circuits,

such as horizontal oscillator-AFC circuits.

The cabinet of the PS120, and the control-panel layout, represent something new in oscilloscope design. Two large concentric knob arrangements are used to control the vertical input voltage and the horizontal sweep frequency. Switches connected to the outer knobs serve for coarse voltage and frequency selection, while controls actuated by the inner knobs take care of fine adjustment. The four beam controls, which adjust the position of the display and the brightness and focus of the trace, are located in a row of controls spaced along the top edge of the control panel, just below the graticule. The synchronizing adjustment and the horizontal gain control are in the same row. None of these controls have knobs, but are fitted with black shafts which extend through the panel and serve the same purpose. The on-off switch (which also contains a standby position) is located in a lower compartment, one side of which provides space for storing the AC cord and the probe-and-cable assembly while the unit is being transported to or from a job.

The input sensitivity is controlled by turning the large knob on the left; a little window (Fig. 2) above the knob shows what multiplier to use with the calibrated control knob for measuring peak-to-peak voltages. There are four multiplier ranges: .1, 1, 10, 100. To use this arrangement, you first connect the probe to the point where the waveform is to be measured. Next, the vertical input coarse and fine controls are adjusted until the waveform display is 1" high on the graticule (which is ruled in 1" segments). By noting the setting of the control knob, and multiplying the setting by the figure shown in the little window, you can find the approximate peak-to-peak voltage of the waveform being picked up by the direct probe. If you're using the low-cap probe tip, you must also multiply the reading by 10, to allow for the 10:1 attenuation of the probe. The final result is the peak-to-peak voltage of the waveform being tested.

An auxiliary vertical input (connected through a switch inside the lower compartment) provides a means for using a direct probe for low-capacitance measurements, eliminating the 10:1 attenuation of the low-cap probe. The secret of this arrangement lies in the use of an unshielded lead, as short as possible. This introduces such problems as stray pickup, but these can be held to a minimum by careful routing of the lead during tests. Hand capacitance also affects this arrangement, and must be taken into consideration; the best means of eliminating this problem is to keep your hand away from the test lead or the circuit after making the connection.

The horizontal sawtooth frequency is controlled by the two large concentric knobs on the right of the panel. The output voltage is also available at the HORIZ

INPUT jack in the lower compartment; this makes an excellent source of sawtooth signal for other testing purposes.

When the horizontal frequency selector knob is in the EXT INPUT position, the HORIZ INPUT jack is connected to the horizontal amplifier, and any voltage applied to the jack will deflect the CRT beam horizontally. This is handy for special applications when other than sawtooth deflection is desired. The horizontal amplifier will handle external frequencies as high as 500 kc, although frequencies that high will be attenuated to about half the amplitude of frequencies in the 1,000-cps range. For horizontal deflection, however, this attenuation is of little importance, unless the source voltage is weak to begin with. As noted in the specifications, it takes .5 volt rms to sweep the beam at least 1".

The above-average frequency response of the PS120 is the result of careful design in the vertical amplifier. The input attenuator (Fig. 3) is thoroughly frequency compensated, which assures uniform response over the entire range of peak-to-peak voltages to be measured. Other important steps are taken throughout the vertical amplifier to attain the extra bandwidth.

In Fig. 4, the first stage in the vertical amplifier is cathode follower V1A, which effectively prevents loading of the input attenuator by the rest of the amplifier. The output is frequency compensated and fed to a potentiometer (the fine vertical attenuator). From the slider of this control, the signal is fed to amplifier V1B, which has a very low-resistance plate load to broaden the bandwidth at this point.

A high-gain pentode, a 6GM6, is used in the next stage. In addition to an un-bypassed cathode to insert a bit of degeneration, this circuit utilizes a peaking coil as part of the plate load; being a shunt coil, its effect is an extension of high-frequency response.

Final vertical amplifier V3 is a push-pull stage which drives the vertical deflection plates of the CRT. This is the stage where most of the peaking networks appear. Both series and shunt

COMPLETE SOLDERING OUTFIT IN PLASTIC CARRYING CASE



Weller[®] Expert Soldering Kit

All your soldering needs in a break-proof plastic utility case. Gun features dual heat. 2 trigger positions permit instant switching to low 100-watt or high 140-watt heat. Low heat prevents damage to heat sensitive components. By using high heat only when necessary, you prolong tip life and save current.

Plastic case can be used for carrying or storing tools, parts and equipment—also as a lunch or fishing tackle box. Model 8200PK.



Weller[®] Hi-Speed Sabre Saw

For smooth, fast cutting of all kinds on speaker and record player mounting boards, cabinets, walls, etc. Makes its own starting hole for inside cuts. Never splinters or tears wood. 4.8 ampere, heavy-duty reciprocating motor. Model 88.

On sale at your Electronic Parts Distributor

WELLER ELECTRIC CORP., EASTON, PA.


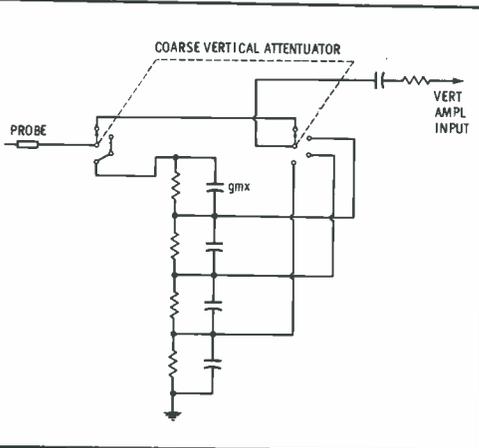


Fig. 3. Schematic showing compensation networks of vertical attenuator.

THE SPEAKER THAT SELLS ITSELF

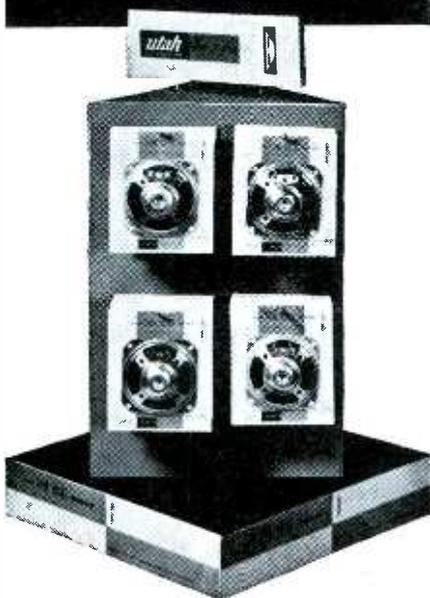

New Utah Thin-Drive Speakers in self service bubble pack display

Utah's radically new Thin-Drive Speaker is available in all popular sizes. It uses a completely new magnetic material (Lodex by G.E.). The "pot" is reduced in size and weight—efficiency and performance increased. The Thin-Drive is thinner in profile, allowing more knuckle room in tightly packed sets.

A beautiful combination!

Utah's new Thin-Drive speakers come individually carded—sealed in clear plastic bubbles for optimum protection and display.

Utah's attractive self service display rack offers fingertip convenience, self-merchandising—self-pricing. See your Utah distributor.

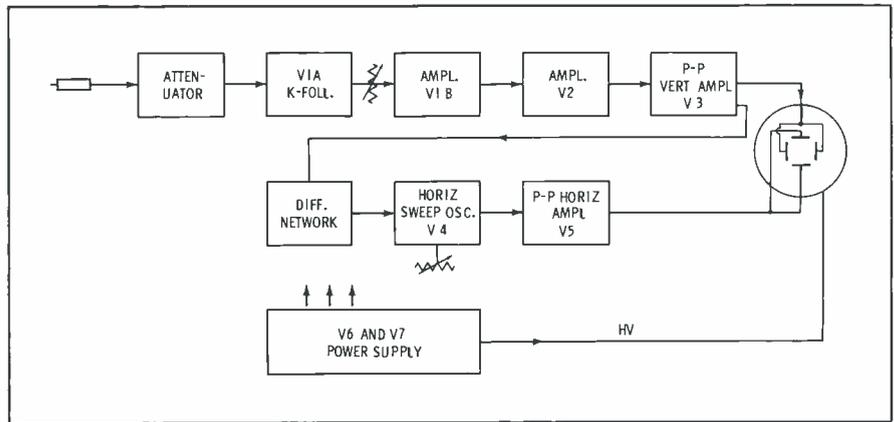


Fig. 4. Block diagram of PS120 scope.

peaking coils are used, to shape the response at both ends of the frequency spectrum. In addition, the cathodes are unbypassed, to smooth the overall response. This final stage is fed by a somewhat unbalanced phase-splitter arrangement in V2, which is compensated for in the design of the V3 stages. The result, however, is a balanced response for the entire amplifier.

A point worth mentioning is the use of low-value capacitors for coupling in the vertical amplifier. The PS120 vertical amplifier is AC-coupled throughout and the use of relatively small coupling capacitors minimizes the bounce often encountered when connecting a probe to a circuit. Using these low values demands that low-frequency response be restored in other sections of the amplifier, which has been done.

The horizontal sweep amplifier consists of a push-pull stage. AC-coupled to the CRT deflection plates. No special compensation is employed in this stage, except for a small amount of degeneration introduced by the unbypassed cathodes. As a result, the response is not nearly so broad as in the vertical amplifier, but bandwidth is not too important in the horizontal amplifier. This stage needs to pass without attenuation only the horizontal sweep frequencies of the scope; in this case, 150 kc is the maximum necessary bandwidth.

Horizontal sweep oscillator V4 is a cathode-coupled multivibrator, which feeds a sawtooth waveform to the horizontal amplifier. It is controlled by pulses from the output of the vertical amplifier, which synchronize the base line on the scope with the signal in the vertical amplifier. A differentiating network is inserted between the sync take-off point and the input to the multivibrator, to shape the synchronizing pulse into a spike that can more accurately control the sawtooth oscillator.

The power supply consists of a common full-wave rectifier, utilizing a 6V4 tube, and a 1V2 half-wave negative high-voltage circuit. The 6V4 develops approximately 340 volts DC of B+ for the scope stages, while the 1V2 develops minus 400 volts for the CRT.

We used the PS120 in our lab, for a number of different jobs. For one

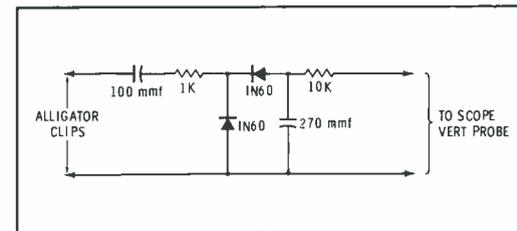


Fig. 5. Simple demodulator probe unit.

test, we checked waveforms all the way from the video detector of a color set to the CRT; we had nice, clean waveforms all the way. In using the PS120 for TV troubleshooting, we wished for an RF probe. So, we made up a small voltage-doubler demodulator probe similar to that shown in Fig. 5. By clipping this device into the IF circuits at various points, we used the PS120 for signal tracing all the way back to the tuner output. Of course, our indications were weak in the first IF stage, but they were sufficient to show that the stage was functioning.

Just to see how clean a waveform the PS120 would show, we used it as a waveform monitor for our color-TV transmitter. Chroma and horizontal waveforms showed up plainly, and the burst signal was easily spotted riding beside the horizontal pulse. For regular use in this application, however, a calibrated time-base would be very helpful.

Back in the lab, audio tests using square waves were a snap. The extended range of the PS120 is sufficient to test the most exacting audio or video amplifier. Our tests showed that rolloff began, for the instrument we used, around 6 mc. This is enough to satisfy the demands of any equipment likely to come into the average electronics service shop.

Not A Ripple

The Model EC-2, a DC Power Supply (Fig. 6) recently introduced by Electro Products Laboratories, is a well filtered, low-ripple unit housed in a small, portable case.

Specifications are:

1. Power Requirements—105/125 volts, 50/60 cps.
2. DC Output — continuously variable from 0 to 16 volts; 5 amps, continuous; 10 amps, intermittent.
3. Regulation — 1.8 volt/amp, no-load to full-load.
4. AC Ripple—less than .5%, at rated load.
5. Panel Meter—single meter monitors both voltage and current; switch selects meter function.
6. Controls and Terminals—ON-OFF slide switch; pilot light; meter function slide switch; fuse holder; voltage control; two insulated binding posts.
7. Size, Weight, Price—10¾" x 4¾" x 6½"; 9 lbs.; \$39.95.

The metal cabinet, designed for vertical use, has ventilation openings at the top, bottom, and both sides to provide heat dissipation when the unit is in operation. Provision is made for using the unit in a horizontal position by merely changing the rubber feet from the bottom to the left-hand panel. Access to the inside of the cabinet is by removing eight metal screws from one of the right-hand side panels. Fig. 7 shows the unit with the panel removed.

A carrying handle is included to make the unit easily portable. All operating controls are mounted on a gray panel and are clearly labelled. The output voltage binding posts, in addition to being color-coded (red and black), are labeled with positive and negative signs.

This power supply provides a well filtered DC source for servicing all types of low voltage electronic equipment, especially automobile radios, transistor radios, and Citizens-band transceivers. The output of the EC-2 (see schematic—Fig. 3) is smoothed by a pi-type network consisting of a dual 4000-mfd electrolytic capacitor and a heavy-duty filter choke. Two seleniums, wired as a full-wave bridge-type volt-



Fig. 6. Low-ripple DC supply can also be used for powering transistor radios.



BOOKS *for* ELECTRONIC TECHNICIANS

Gernsback Library

SERVICING

Radio Servicing Made Easy (2 Vols.)

by Leonard C. Lane

Get the latest servicing information on new radio types. Full instructions on how to fix FM, AM, AM-FM, Communications receivers, Marine Radios, transistor sets, Converters, etc. Books adapted from school course given at many times this price.

No. 107 2 Volumes \$7.20

Practical TV Troubleshooting

Trouble fixing TV sets? The experts let you in on their secrets to help you think your way through the toughest problems, quickly and efficiently. Add years to your technical knowledge.

No. 102 \$2.35

TV Trouble Analysis

by Harry Mileaf

Fix TV Troubles in any set fast, by knowing what symptoms look like and what causes them. Learn how and why components and circuits fail.

No. 101 \$3.20

How to Fix Transistor Radios & Printed Circuits (2 Vols.)

by Leonard C. Lane

Feel at home in the wonderland of semi-conductors. Learn improved transistor techniques and save time, handle more jobs and add to your income. Theory and practical applications with hundreds of diagrams. Originally published as an expensive school course.

No. 96 2 Volumes \$5.90

New Shortcuts to TV Servicing (2 Vols.)

by Leonard C. Lane

A practical servicing speed-up course. No theory or math, but heavy on test and repair techniques that save time and make money. Symptom analysis method helps you find troubles fast. Numerous handy check lists tell you how to find troubles easily and quickly.

No. 95 2 Volumes \$5.90

Practical Auto Radio Service & Installation

by Jack Greenfield

Newest servicing information on these specialized sets. For technicians, serious hobbyists interested in expanding their field of interest. Time-saving hints, speed servicing charts and check lists.

No. 87 \$2.95

Rapid Radio Repair

by G. Warren Heath

Put your finger on tough troubles in FM sets, transistor sets, hybrid auto sets and other modern radio receivers easily and quickly. Lists symptoms and cures alphabetically in four handy sections: Receivers, Techniques, Servicing, Charts.

No. 78 \$2.90

Servicing Transistor Radios

by Leonard D'Airo

Are you all thumbs handling tiny transistors? This book will show you that transistor sets are even simpler to fix than vacuum-tube counterparts. Learn the inside tips, the new techniques. Charts, diagrams provided.

No. 76 \$2.90

TEST INSTRUMENTS

How to Get the Most out of Your VOM

by Tom Jaski

Get more mileage out of this versatile instrument. A complete analysis, including theory and practical usage plus chapters on construction.

No. 85 \$2.90

Oscilloscope Techniques

by Alfred Haas

Use the scope in scores of new applications. Make tests and measurements, interpret patterns. Hundreds of photos of actual waveforms to help you.

No. 72 \$2.90

The VTVM

by Rhys Samuel

Get the most out of this electronic workhorse. Explains VTVM circuits and how and why they work. Gives many new time-saving uses.

No. 57 \$2.50

Sweep and Marker Generators for Television and Radio

by Robert G. Middleton

Tips and hints on how to use and understand this instrument. Includes major chapters on attenuation, signal calibration, receiver alignment, etc., and a terminology index.

No. 55 \$2.50

Buy these quality paperbacks, essential reading for your training, education, and reference shelf. Tax deductible if used for professional purposes.

BUY NOW FROM YOUR ELECTRONIC PARTS DISTRIBUTOR, or mail in the coupon below by checking matching book number with box number.

----- 10-Day Money-Back Guarantee -----

REMITTANCE MUST ACCOMPANY ORDER


107 102 101 Send books to: Name _____

96 95 87 Address _____

85 78 76 City _____ State _____ Enclosed is \$ _____

72 57 55 GERNSBACK LIBRARY, INC., DEPT. PF, 154 W. 14 St., New York 11, N.Y.

PLANET

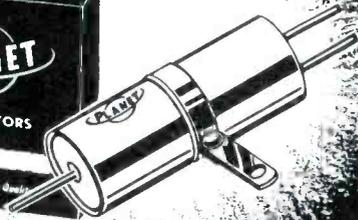

TYPE IL . . . why use old fashioned wax end-filled cardboard capacitors in radio repairs? Avoid call-backs with Planet type IL dual section tubular electrolytics . . . hermetically sealed in aluminum tubes with wax impregnated insulating jacket . . . U/L approved plastic covered leads . . . wrap-around mounting strap. Planet IL's are smaller and longer lasting. Planet IL's are also available in 450 volts for TV servicing. Ask for them by type number at your distributor.

Write today for complete information.

PLANET SALES CORPORATION
225 Belleville Avenue Bloomfield, New Jersey

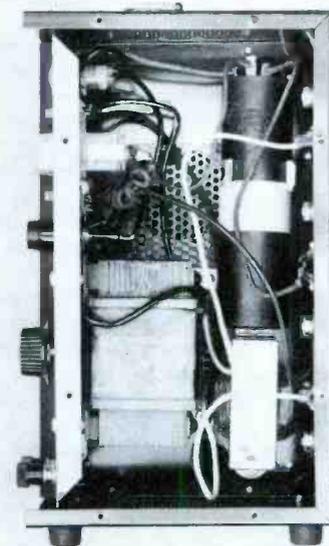


Fig. 7. Opened view of the Model EC-2.

age doubler, make up the rectifier circuit. Selenium rectifiers are used in this unit apparently because of their ability to withstand momentary overloads without being damaged. Thus, intermittent current as high as 10 amps can be drawn from the EC-2 without damaging the supply or its components.

The ON-OFF switch and a 3-amp fuse are in series with the primary winding of the power transformer. The output voltage is controlled by adjusting rotary contact assembly M1, which contacts the secondary winding of the power transformer, selecting a particular amount of the secondary AC voltage for the rectifier. This voltage is then rectified, filtered, and connected to the binding posts on the front panel.

The meter is used to measure either the voltage or the current of the supply. Current drawn by the load is developed across resistor R1 (approximately 13" of #20 copper wire) in the AMPS position of the selector switch; the meter is connected across R1, measuring the load current. In the VOLTS position, the switch connects the meter, in series with multiplier resistor R2, across the output terminals, and output voltage is indicated.

The EC-2 is designed to be used for battery charging in addition to its other applications. Before the instrument is used in this application, it is wise to remember certain important facts that apply to battery-charging in general.

For example, it is best to start with the voltage-control knob at minimum, and advance it slowly. The charging current is most important, while the voltage is relatively minor, so you should adjust the unit for proper charging current, and ignore the voltage. A maximum charging current of 5 amps seems best for a 6-volt battery and 3 amps for a 12-volt battery. Total charging time should not exceed 13 hours. Rely on the hydrometer to determine when the battery is fully charged, reading the specific gravity of all cells, not

DeSod System
**PRINTED CIRCUIT
DESOLDERING
TOOLS**



COMPACTRON

Socket change
done in one minute.

Tools available for most Multi-contact components of printed boards.

DeSod tools fit your present solder gun.

Available from your distributor.

EVERSOLE INDUSTRIES
2121 W. State St.
Fremont, Ohio

**A Revolutionary New
Signal Generator**

135 kc. to 240 mc.
TRANSISTORIZED
No Tube Troubles
BATTERY-POWERED
No Power Lines
CB CRYSTAL SOCKET
For Crystal Control

VALUE PRICED
Kit \$34.90 Assembled \$54.90

**NEW GRID
DIP METER**

Transistorized, Battery-Powered, Compact
Kit \$29.90 Assembled \$39.90

**At Better Dealers
Send For Technical Bulletins**

**PEL
ELECTRONICS**

214 MAIN STREET
HACKENSACK, NEW JERSEY

just one. The difference in the reading of any two cells should be no more than 50 points (.050); if it is greater, a defective cell is indicated.

Incidentally, you shouldn't rely on hydrometer readings for batteries other than the lead-acid type. Alkaline batteries use other methods of indicating the charge even though the method of charging is similar.

Never make or break the battery connections while the charger (in this case, the EC-2) is delivering current to the battery. The battery generates highly explosive hydrogen gas while being charged, and a very small spark can explode the battery, spraying battery acid over a wide area.

We lab-tested the EC-2 using it in several different applications. First, it was used to supply operating voltage for several transistor radios. The voltage meter came in handy to set the exact operating voltage for each transistor radio. The current meter, however, is not sensitive enough to read transistor-radio drain current. During this test, we also checked the meter by measuring the actual output voltage with an accurate VTVM. Within the operating range of the EC-2 — 0 to 16 volts — the meter readings were very close to those obtained with the VTVM.

An important point we might mention here, in connection with using the EC-2 as a transistor radio power supply: The ripple output is so small, and well filtered, that we could detect no hum whatsoever from the output of any of the transistor radios.

Automobile radios—older 6-volt, 12-volt hybrid, and all-transistor types—were "fired-up" with the EC-2. One of the advantages of the two-function meter was noticed in these applications: Since the meter reads both voltage and current, we were able to spot one of the radios that had a leaky output transistor; the defective component caused an abnormally high input-current reading on the meter, while the voltage control had to be set much higher than usual to get a normal output-voltage reading. Thus, we used the EC-2 as a troubleshooting device as well as for a power source. ▲

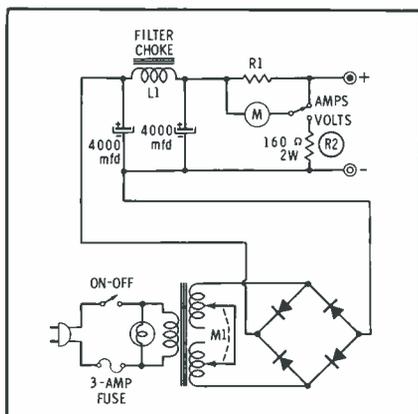


Fig. 8. Schematic showing straightforward circuit, special two-way meter.



It's an emergency!

I'm out of **Centralab**[®] Ceramic Capacitors!



There's no need to fly off the handle when you need a ceramic capacitor. Just taxi down the field to your nearest CENTRALAB distributor. He has the unit you need—whether it's plane or fancy.

CENTRALAB piloted the ceramic capacitor to its present importance in electronics, and today is flying high with the most complete line of discs, tubulars, buffers, trimmers, feed-thrus—for every standard or special application . . . and if you use CENTRALAB's handy capacitor kits you'll never be grounded by lack of parts.

You'll not only like CENTRALAB's complete selection of ceramic capacitors. You'll like the product quality—and you'll like the brand-new plastic box. Travel first class with CENTRALAB ceramic capacitors—in stock at your distributor.

Centralab[®]

THE ELECTRONICS DIVISION OF GLOBE-UNION INC.
942L EAST KEEFE AVENUE • MILWAUKEE 1, WISCONSIN
In Canada: Centralab Canada Ltd., P.O. Box 400, Ajax, Ontario

D-62115

ELECTRONIC SWITCHES • VARIABLE RESISTORS • CERAMIC CAPACITORS
PACKAGED ELECTRONIC CIRCUITS • ENGINEERED CERAMICS

NEW SAMS BOOKS

Modern Communications Course, Vol. 2 AM Modulation Systems

Provides a full understanding of amplitude modulation systems used in present-day transmitters. Many experiments are included to provide practical knowledge and skill. 8 chapters cover: AM Transmission Principles; Audio Systems & Modulators; Test Equipment & Adjustments; AM Modulation Methods; Transistor Modulators & Modulation Methods; Single-Sideband Generation; Single-Sideband Systems; Commercial AM Equipment. 272 pages; \$4.95
5 1/2 x 8 1/2". Order MCN-2 only. . . . \$4.95
Vol. 1, Radio Frequency Systems, MCN-1, . . . \$4.95

Electric Motor and Generator Repair

Details the operating principles and functions of electric motors and generators as well as repair and servicing techniques for each type. 10 complete chapters include: General Discussion; Introduction to AC Motors; Split-Phase Induction Motors; Capacitor Motors; Repulsion-Induction & Shaded-Pole Motors; Universal Motors; Polyphase Motors; DC Armatures; DC Motors; Generators. 256 pages; 5 1/2 x 8 1/2". Order MGR-1, only. . . . \$4.95

Solving TV Tough-Dogs

Bob Middleton's realistic approach to solving the really tough TV service problems, for both beginning and experienced technicians. Through examples drawn from actual practice, you learn how to analyze, localize and solve in minutes TV troubles which often take hours to find. 6 chapters include: What Makes a Tough-Dog?; No-Picture Troubles; Poor-Picture Troubles; Framing & Display Troubles; Raster Problems; Video-Sound Troubles. 128 pages; 5 1/2 x 8 1/2". Order TDM-1, only. . . . \$2.50

Small Engines Service Manual

All the knowledge you need for servicing virtually any small engine in operation today—covers over 1,250 models of 42 popular makes. Enables you to service engines used on lawn mowers and garden tractors, tillers, snow throwers, cycles, karts, scooters, elevators, grinders, mixers, portable electric units, etc. More than 850 pictures show internal construction and how to make tricky adjustments. 352 pages; 8 1/2 x 11 1/2". \$4.95
Order SES-1, only. . . . \$4.95

Outboard Motor Service Manual

Shows how to repair and maintain more than 750 models of 15 popular makes. Practical step-by-step instruction for every service procedure; disassembly and reassembly procedures; complete adjustment and repair of individual components; sections on lubrication, ignition, carburetion, power head and lower units. Over 600 how-to-do-it illustrations. 224 pages; 8 1/2 x 11 1/2". \$4.95
Order OUM-1, only. . . . \$4.95

ABC's of Tunnel Diodes

Teaches the basics of tunnel-diodes (TD's), important semiconductor devices used in thousands of electronic applications. Explains principles of TD operation, their characteristics and how they fulfill special needs in various circuits. 7 chapters include: Semiconductor Theory; Physics of Tunneling; Tunnel-Diode Amplifiers; Tunnel-Diode Oscillators; Tunnel-Diode Logic; Tunnel-Diode Computer Circuits; Measuring Tunnel-Diode Parameters. 96 pages; 5 1/2 x 8 1/2". \$1.95
Order TDK-1, only. . . . \$1.95

Interference Control Handbook

Analyzes all RF interference. Describes sources, types and effects of interference, as well as how to detect and control it. Chapters: Theory of RF Interference; Interference Measurements; Interference-Measuring Equipment; Measurement Problems; Electrical-Circuit Noise; Semiconductor Circuit Interference; Switches & Contactors; Suppression Techniques; Suppression in Rotating Machinery; Suppression in Ignition Systems; Suppression at the System Level. 256 pages; 5 1/2 x 8 1/2"; hardbound. \$6.95
Order RIC-1, only. . . . \$6.95

NEW: SERVICING TRANSISTOR RADIOS, VOL. 16
Just out—covers 42 important models produced in 1962. Complete PHOTOFACT® servicing data. 160 pages; 8 1/2 x 11". Order TSM-16, only. . . . \$2.95

HOWARD W. SAMS & CO., INC.

Order from your Sams Distributor today, or mail to Howard W. Sams & Co., Inc., Dept. L-32
4300 W. 62nd Street, Indianapolis 6, Ind.

Send me the following books:

MCN-1 MCN-2 MGR-1 TDM-1 SES-1
 OUM-1 TDK-1 RIC-1 TSM-16



\$ enclosed. Send FREE Booklist

Name _____

Address _____

City _____ Zone _____ State _____

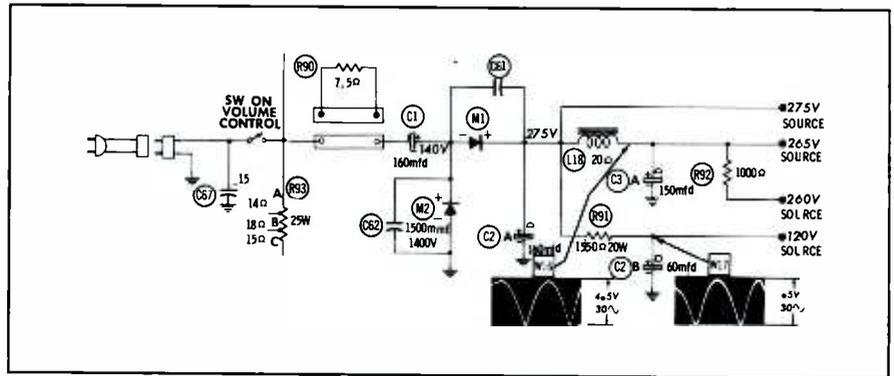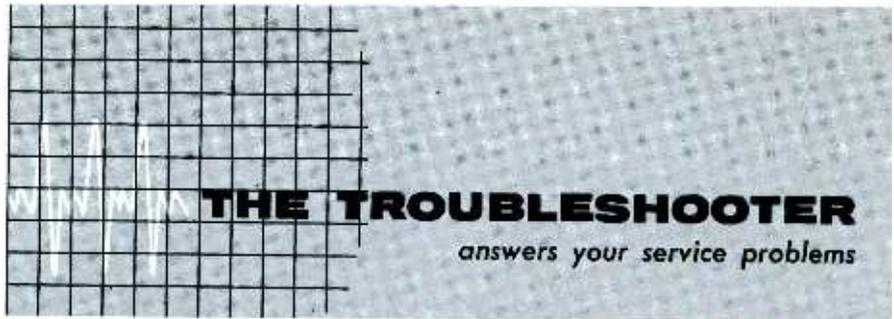IN CANADA: A. C. Simmonds & Sons, Ltd., Toronto 7



Smoker

I had a Westinghouse TV, Model H21K308 (covered in PHOTOFACT Folder 465-2), with an open 7.5-ohm fusible resistor. I replaced it with a 7.5-ohm universal type and got a perfect picture and sound. But, after five minutes or so the resistor started to overheat and smell—a thin trail of smoke rose from it.

The cathode current through the 12DQ6 horizontal output tube measured 110 ma and all of the B+ voltages were near normal. The current at the output

of rectifier M1 was 325 ma. All tubes checked good and I found no short circuits.

I then replaced the fusible resistor with a 5-ohm, 7-watt unit and made another operational check of the set. Everything appeared normal, so I returned it to the customer. What should the B+ current consumption be for this receiver? What kind of resistor should be used in this application?

S. YANCIS

Wilkes-Barre, Pa.

The first thought that enters my mind


COLOR COUNTERMEASURES

Symptoms and tips from actual shop experience

Chassis: Zenith 29JC20

Symptoms: No raster, smoke rolls out of set.

Tip: If burnt odor is in the area of the flyback cage, remove the cover and visually inspect L49, R126, and R127 (focus circuit). If all three of these components appear burnt, you'll find it necessary also to replace the flyback transformer. Replacement of C79, C78 and the 1V2 focus rectifier will not cure this defect, although it's a good idea to replace these components—especially the tube. As final callback insurance, make adjustments to the horizontal circuits as described in the service data—output current, regulator current, and high voltage.

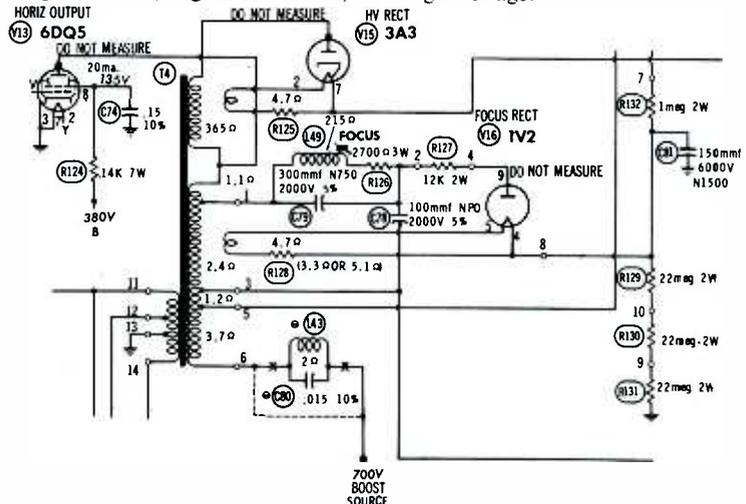

is: Did the new fusible resistor fail? You mentioned overheating, and smoke rising from the new resistor after a few minutes of operation, but failed to state the final results. This resistor runs pretty hot during normal operation, so the smoke you noticed could have resulted from the newness of the unit. Or, perhaps there was a small amount of oil from your hands—I've seen this happen a number of times.

The 325-ma reading you obtained at the output of rectifier M1 is probably normal for this receiver. The particular chassis analyzed for the PHOTOFAC T Folder drew a current of 310 ma. This information is usually listed directly on the schematic (at the output of the rectifier circuit); it was inadvertently left out of this Folder, but you'll find it in the parts list. The voltage rating of the rectifier is listed, along with the current through it.

In regard to the wattage rating of the 7.5-ohm fusible resistor used in this set, it's most likely a 5-watt unit; most of them are. You mentioned replacing this resistor with a 5-ohm, 7-watt unit, and I don't believe this will cause any noticeable difference in the circuit—just make sure the unit is a fusible type.


Dimly Lit

I have a problem with a Philco Model 51T2134. Referring to PHOTOFAC Folder 132-10, you do not state the amount of voltage applied to the second anode of the picture tube. In most sets, 14 kv, \pm 2 kv, will work; in this one, I measure only 9 kv. This is enough voltage to fire my small 5" test tube perfectly, but the CRT in the set will give only a very faint light. On pin 11 (cathode) of the CRT, I measure 20 volts with the brightness control at maximum and 70 volts when it's set to minimum. I have substituted a yoke, and several capacitors and resistors in the high-voltage rectifier circuit; the only thing I have not tried is replacing the flyback. Do you think 9 kv is enough high voltage for this tube?

B. REED

Limaville, Ohio

The 20DP4 picture tube used in this

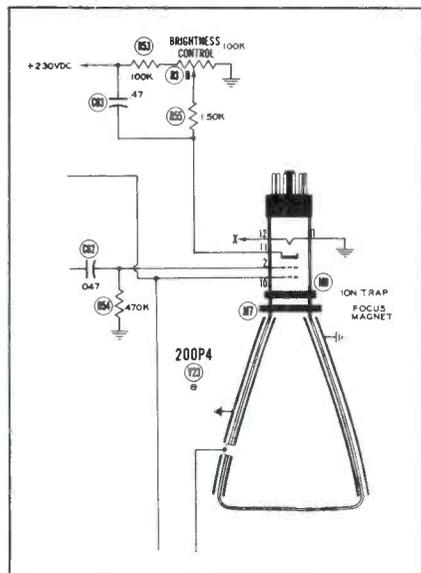

Mercury offers you the **GREATEST VALUE** in **TUBE TESTERS**

TOP QUALITY • SPEED • ACCURACY • LOW PRICES
...sell more tubes—earn more money

a true **DYNAMIC MUTUAL CONDUCTANCE TUBE TESTER**
 for only **\$79.95** Net

Model 1000
MUTUAL CONDUCTANCE TUBE TESTER

- Tests for true dynamic mutual conductance (Gm)
- Tests for shorts and leakage between any tube elements
- Tests for gas and grid emission sensitivity over 100 megohms
- Tests picture tubes

Here, for the first time is a true dynamic mutual conductance tube tester to sell for less than a hundred dollars... in fact it bears a price tag of only \$79.95... truly, one of the greatest values in test equipment to come your way in a long time.

Size: 14x9½x4¾"

Model 1100 TUBE TESTER
 ... an outstanding tester—yet amazingly low in price!

Tests for shorts and leakage

Tests for dynamic cathode emission

Tests for grid leakage

Tests for gas content

\$39.50 Net Size: only 10¼x8¼x3¼"

Here is the answer to technicians who seek a dependable, professional performing tube tester at a minimum cost. The Model 1100 has a range of operation that will outperform many, more expensive testers. It boasts an exclusive meter bridge circuit, found only in more expensive testers. Conveniently compact in size—a whale of a money-maker.

ALL MERCURY Tube Testers have these features:

- Also test the new tube types including Novars, Nuvisors, Compactrons, new 10-pin tubes as well as battery type tubes, auto radio hybrid tubes, voltage regulators, foreign and hi-fi tubes, thyratrons and most industrial tube types.
- Check each section of multi-section tubes separately
- Handsome, two-tone long lasting etched aluminum panel
- Housed in sturdy carrying case with handsome leatherette finish.

Model 1200

MUTUAL CONDUCTANCE TUBE TESTER

- Tests for true dynamic mutual conductance (Gm)
- Tests for shorts and leakage between any tube elements
- Tests for gas and grid emission... sensitivity over 100 megohms

\$119.95 Net

Here is a deluxe dynamic mutual conductance tube tester with a unique push-button set-up method that can be compared with the ease of selecting a record on a juke box. Push buttons provide complete flexibility in accommodating all present and new tube types and basing arrangements. The Model 1200 is the most versatile tube tester available today.

Deluxe
 Dynamic Mutual Conductance Tube Tester with **FAST PUSH BUTTON SETTINGS**

- TREMENDOUS VALUE!**
- Also tests black and white and color picture tubes.
 - Also tests transistors.
 - Also tests batteries under load
- Size: 18¼x10¾x4¾"

See your electronics parts distributor or write for complete Mercury catalog

Mercury ELECTRONICS CORPORATION

manufacturers of quality electronic products

111 Roosevelt Avenue, Mineola, New York
 EXPORT: EMEC Inc., 127 Grace St., Plainview, N. Y.

SOUND WAYS TO EXTRA PROFITS

Get into the all-year-round commercial sound trade and do away with seasonal repair work slumps! This steady-profit business—sales, installation and service—is available right in your own neighborhood! Factories, restaurants, schools, offices, bowling alleys... outdoors, athletic fields, swimming pools, etc... all are prospects for you.

Atlas Sound products, built to quality standards and backed by over 25 years of "know-how", are insurance for your reputation. Your Atlas Distributor can supply you with a complete line of performance-proven job-rated equipment: speakers, mike stands and related accessories for a professional sound installation.



Write for latest catalog and names of Atlas Distributors.

ATLAS SOUND DIVISION
American Trading and Production Corporation
1419-51 39th Street, Brooklyn 18, New York
In Canada: Atlas Radio Corporation, Toronto

receiver normally requires about 16 kv. As a general rule, you can get a pretty good picture with as little as 12 kv, but I agree that 9 kv seems pretty low. However, the symptom you describe, and the voltage readings you are getting, are commonly caused by a leaky C63. I would suggest that you change it, and check the value of R53. If a dim raster is still a problem, I suggest you look for high-voltage or horizontal-circuit trouble, either of which can cause poor high voltage.

Needed — Better Blanking


I want to eliminate vertical retrace lines in a Packard Bell TV, chassis V8-2 (covered in PHOTOFAC T Folder 387-3). I would appreciate any help you could send my way.

W. CZERVINSKI

SKI's TV Service
Fairchild, Washington.

This set already has a retrace-blanking circuit. Negative 75-volt pulses are coupled from the vertical output transformer through C83 (.01 mfd) to the accelerating grid of the picture tube. Perhaps blanking would be improved if you were to modify the circuit to conform with later versions of the V8 chassis, such as the V8-7 covered in PHOTOFAC T Folder 544-2.

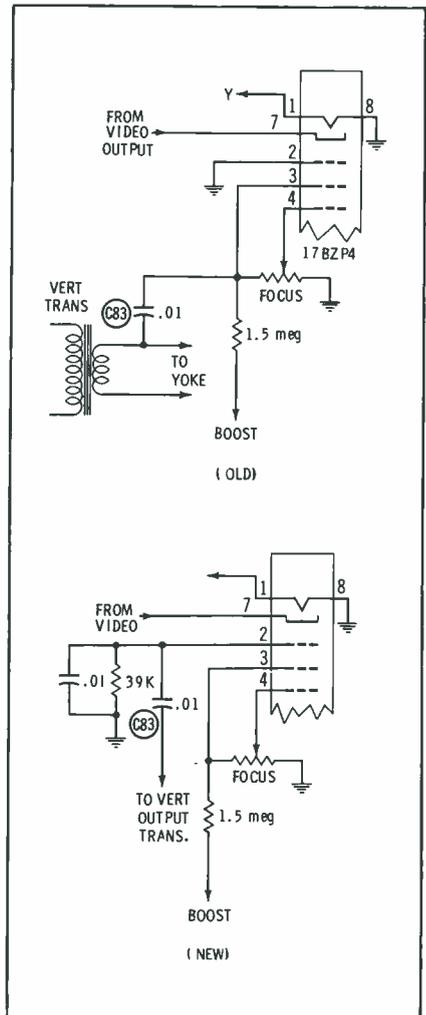The change (see schematic) involves transferring C83 from pin 3 to the control grid (pin 2). The existing ground connec-



Duotone needles, of course . . . tipped with genuine diamonds, synthetic sapphires or osmium.

Most people forget to change their styli or don't know how to change them. Why not suggest a Duotone diamond needle replacement for every phonograph that comes into your shop? It's the stylus with the diamond tip that's handset and hand polished. Your customers will appreciate the service and you'll appreciate the increase in business.

Write for Free 1962 Duotone Needle Wall Chart and see your DUOTONE Distributor.

DUOTONE
COMPANY INC. KEYPORT, N. J.

PROFESSIONAL
technicians

USE
Dave Rice's
OFFICIAL
ORDER BOOKS
for every
TV-RADIO
service
call



This is the businesslike approach to service record keeping. Triplicate forms serve as order form, invoice and office record, with spaces for complete information on every job. Separate listings for receiving tubes, pix tube, parts, serial numbers, labor and tax charges, signatures, etc. 75c a book, \$6.50 for dust-proof box of 10. In stock at your distributor.

FREE

Write for your free folder describing Dave Rice's OFFICIAL ORDER BOOKS, including an actual size sample copy of the handy order form.

ELECTRONIC PUBLISHING CO., INC.
133 N. JEFFERSON ST.
CHICAGO 6, ILLINOIS

tion to this grid should be broken, and a 39K resistor in parallel with .01-mfd capacitor inserted between pin 2 and ground.

This new arrangement should give more efficient blanking, since it applies vertical blanking pulses of approximately 35 volts peak to peak at the control grid. ▲

STATEMENT REQUIRED BY THE ACT OF AUGUST 24, 1912, AS AMENDED BY THE ACTS OF MARCH 3, 1933, JULY 2, 1946 AND JUNE 11, 1960 (74 STAT. 208) SHOWING THE OWNERSHIP, MANAGEMENT, AND CIRCULATION OF PF REPORTER published monthly at Indianapolis, Indiana for October 1, 1962.

1. The names and addresses of the publisher, editor, managing editor, and business managers are:
 Publisher: Howard W. Sams & Co., Inc., 4300 W. 62nd St., Indianapolis 6, Ind.; Editor: Verne M. Ray, 4300 W. 62nd St., Indianapolis 6, Ind.; Managing editor: Forest H. Belt, 4300 W. 62nd St., Indianapolis 6, Ind.; Business manager: Mal Parks, Jr., 4300 W. 62nd St., Indianapolis 6, Ind.

2. The owner is: (If owned by a corporation, its name and address must be stated and also immediately thereunder the names and addresses of stockholders owning or holding 1 percent or more of total amount of stock. If not owned by a corporation, the names and addresses of the individual owners must be given. If owned by a partnership or other unincorporated firm, its name and address, as well as that of each individual member, must be given.)

Howard W. Sams & Co., Inc., 4300 W. 62nd St., Indianapolis, Ind.; Chetco, 35 Congress St., Boston, Mass.; Jean B. Eldred, Redwood Dr., Franklin, Ky.; Genoy & Co., P.O. Box 491, c/o Morgan Guaranty Trust Co., New York, N.Y.; David H. Hertel, 30600 Salem Dr., Bay Village 40, Ohio; Robert E. Hertel, 1014 Wyandotte St., Kansas City 5, Mo.; Lehman Brothers, One William St., New York 4, N.Y.; Liorot & Co., c/o Manufacturers Hanover Tr. Co., Corporate Trust Dept., 55 Broad St., New York, N.Y.; James A. Milling, 7905 Morningside Dr., Indianapolis, Ind.; Mufun & Co., c/o Bankers Trust Co., P.O. Box 1371, New York 8, N.Y.; Reing & Co., Box 491, Church St. Sta., New York 15, N.Y.; Salkeld & Co., c/o Bankers Trust Co., P.O. Box 407, New York 8, N.Y.; Howard W. Sams, 414 Kessler Blvd., W. Dr., Indianapolis 8, Ind.; Sigler & Co., c/o The Hanover Bank, 70 Broadway, New York 15, N.Y.; Frank D. Smailey, 1285 W. 61 Terrace, Kansas City 13, Mo.

3. The known bondholders, mortgagees, and other security holders owning or holding 1 percent or more of total amount of bonds, mortgages, or other securities are: (If there are none, so state.)

John D. & Ruth E. Bauer, 3239 Sutherland Ave., Indianapolis, Ind.; Mary M. Benham, 215 N. Senate, Indianapolis, Ind.; McFarland Benham, 601 Lemcke Bldg., Indianapolis, Ind.; Bertha & Frieda Binnering, 3510 Watson Rd., Indianapolis, Ind.; Frieda & Bertha Binnering, 3510 Watson Rd., Indianapolis, Ind.; A. W. Brayton, Jr., 3943 N. Illinois, Indianapolis, Ind.; Lucile Lee Brayton, 3943 N. Illinois, Indianapolis, Ind.; R. M. & Mary H. Brotherson, 560 Princeton Ave., Des Plaines, Ill.; Hazel J. Earl, 5890 Compton Dr., Indianapolis, Ind.; Kenneth D. Earl, 5890 Compton Dr., Indianapolis, Ind.; Marguerite M. Edmonson, 19 S. Rebecca Dr., Indianapolis, Ind.; Edward D. James, 122 E. Michigan, Indianapolis, Ind.; Edward D. James, Architect, Inc., 122 E. Michigan St., Indianapolis, Ind.; Grace Knox, 505 W. Oak St., Zionsville, Ind.; John B. & Helma G. Kolling, 515 W. South St., Crown Point, Ind.; Florence T. Lewis, 523 E. 51st St., Indianapolis, Ind.; Katherine B. & Robert J. Lewis, 3640 Watson Rd., Indianapolis, Ind.; Melvin R. Moser, 864 McGill St., Orrville, Ohio; Crawford H. & Ruth Nangle, 6470 N. Rural St., Indianapolis, Ind.; Frieda & Harold Neil, 5247 32nd Terrace, N., St. Petersburg, Fla.; Edward E. Petri, c/o Petri Jewelry Co., Guaranty Bldg., Indianapolis, Ind.; Helen N. Sams, 5910 Primrose, Indianapolis, Ind.; Howard W. Sams & Co., Inc., 4300 W. 62nd St., Indianapolis, Ind.; Kenneth Swan, 4243 Broadway, Indianapolis, Ind.; William G. & Helen A. White, 4520 Marcy Lane Apt. 23, Indianapolis, Ind.

4. Paragraphs 2 and 3 include, in cases where the stockholder or security holder appears upon the books of the company as trustee or in any other fiduciary relation, the name of the person or corporation for whom such trustee is acting; also the statements in the two paragraphs show the affiant's full knowledge and belief as to the circumstances and conditions under which stockholders and security holders who do not appear upon the books of the company as trustees, hold stock and securities in a capacity other than that of a bona fide owner.

5. The average number of copies of each issue of this publication sold or distributed, through the mails or otherwise, to paid subscribers during the 12 months preceding the date shown above was: (This information is required by the act of June 11, 1960 to be included in all statements regardless of frequency of issue.) 80,631.

(Signed) MAL PARKS, JR., Bus. Mgr.
 Sworn to and subscribed before me
 this 3rd day of October, 1962
 (Seal) Billie S. Paul, Notary Public



THE **erit** MAN!


ELECTRONICS' FAMOUS TRADEMARK

symbolizes

SUPERLATIVE ENGINEERING

WORKMANSHIP OF HIGHEST QUALITY


CLEAN-CUT LEGITIMATE BUSINESS TACTICS

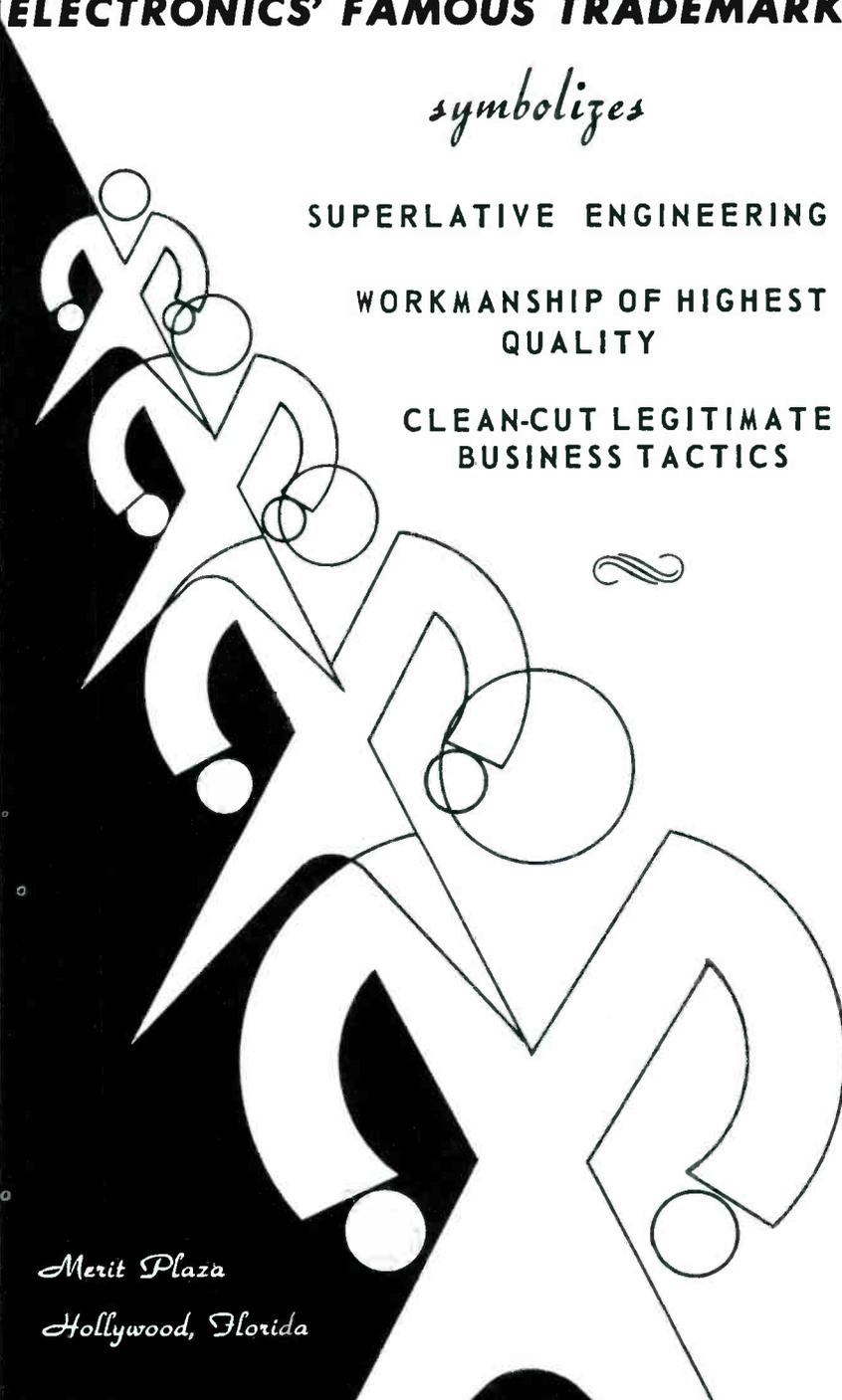

Merit Plaza
Hollywood, Florida

MERIT

COIL and TRANSFORMER CORPORATION

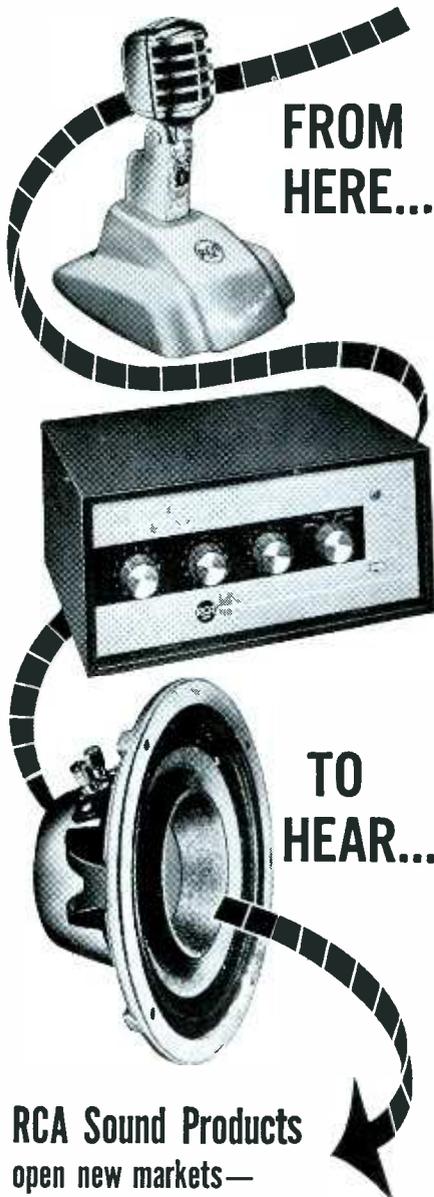

**FROM
HERE...**

**TO
HEAR...**

**RCA Sound Products
open new markets—
bring you new business
—increase your profits**

There's a lot of money to be made in institutional sound systems for public address, paging, piped-in music, etc.

Now it's easier than ever to capture a profitable share. Complete sound systems—matched microphones, amplifiers, and speakers—all are available from a single source: RCA, the brand name that's easy to sell. No more time-consuming matching of components of different brands.

RCA sound products range from low-cost 12-watt paging networks to full-volume, auditorium-filling 100-watt installations... one for every customer requirement.

RCA sound components are available through your Authorized RCA Sound Products Distributor. If he is temporarily out of stock, please fill out and send us the coupon below.

RCA ELECTRON TUBE DIVISION
Harrison, N. J.



The Most Trusted Name in Sound

Special Products Department
RCA ELECTRON TUBE DIVISION
Harrison, N. J.

Please send detailed information on:

- Complete line of RCA sound products
 RCA microphones RCA PA Amplifiers
 RCA Speakers

Name _____ Title _____

Company _____

Address _____

City _____ State _____

Objective: Pure White

(Continued from page 35)

evident as we describe the setup technique.

Purity checks are ordinarily made first, unless the convergence yoke or its magnets are known to be incorrectly positioned. To insure that each electron beam in the CRT will strike only the appropriate set of color dots on the screen, purity is adjusted by repositioning the deflection yoke and the purity rings. These rings are permanent magnets with projecting adjustment tabs; they look exactly like the centering rings used in monochrome receivers, even though they are not used for the same purpose. Rotating both rings at the same time moves the beams in a circular pattern on the screen, and spreading or closing the adjusting tabs causes radial movement of the beams. The purity rings are used to set the beam landing in the central area of the screen, while the yoke is used to set up correct purity on the outer edges of the CRT.

Some older receivers also had external edge-purity magnets (located around the perimeter of the CRT housing) to help remove color contamination on the outer edges of the tube; however, improvements in picture-tube tolerances have made these magnets unnecessary in newer sets.

Before attempting to adjust purity in a color receiver, give it and the color bar-dot generator a good 15 minutes to warm up; then degauss the receiver, and adjust operating controls for correct AGC, horizontal frequency, focus, vertical linearity, height, and centering (vertical and horizontal). If necessary, also make a rough adjustment of gray-scale tracking.

For the actual purity check, disable the green and blue guns —

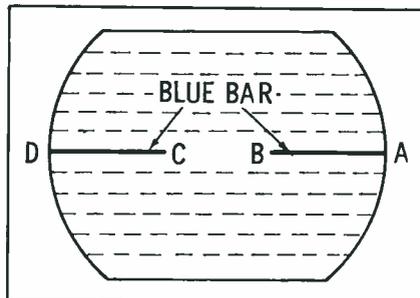


Fig. 4. Straightening the blue bar is first step of horizontal convergence.

**NEW — from
Swing-O-Lite**



HI-MAG

The compact, completely adjustable lamp that puts HI-INTENSITY concentrated controlled light into limited-space work areas. The light for tight spots — air cooled, midget shade is only 2 1/4" in diameter — doesn't get in the way. Glass magnifier makes HI-LITE perfect for micro-miniaturization applications. Versatile on the job, on the bench, in the home, on the road.

- Choice of mounts
- 20", 33", 45" Flexible arm. 12" gooseneck
- Adapts to automobile use with cigarette lighter jack

Model #HL-33C **\$2475** (without bulb) List magnifier

(as illust., 33" arm, with magnifier and bulb, \$36.00 list)

Brown, grey, or tan baked enamel finish.

TWO OTHER GREAT SWING-O-LITE LAMPS!



THE INSPECTOR

with built in magnifier

- Used with printed circuits, blueprints, schematics, microminiatures, quality control inspection, etc.
- Shadow free fluorescent light
- 5" precision polished magnifying glass. Choice of mounts.
- 45" arm reach — adjusts to any position
- Exclusive convenience electric base outlet (optional)

Model M1 **\$3600** List Less Bulb

Baked enamel finish — brown, grey, or tan.

THE SUPER ALL PURPOSE, INCANDESCENT LAMP



- Casts light over wider area
- Adjusts to any position
- Exclusive "Cool Aid" shade

Model SS-45
45" arm reach

\$2095 List Less Bulb

Brown, grey, or tan baked enamel finish. Choice of mounts.

It's SWING-O-LITE... where good lighting makes the big difference.

Write for free illustrated literature on the full line of lamps. UL seal on components.

Distributorships open in selected areas.

Swing-O-Lite INC.

13 MOONACHIE ROAD HACKENSACK, N. J.

either by turning down their screen controls, or by connecting the grid of each gun through a 100K resistor to chassis. Loosen the yoke-retaining clamp, and pull the yoke slightly rearward to scan only the center area of the screen. Now, adjust the purity ring to produce the purest (and brightest) red area in the center of the CRT. Slowly slide the yoke toward the bell of the tube, stopping at the point where the purest red field is evident over the entire screen. A more exact check of red purity can be obtained by looking through a magnifying glass or low-power microscope to see if the individual dots (especially near the edges of the screen) appear round. A circular area of illumination on a dot means that the beam is striking it correctly. Egg-shaped or oblong dots indicate that purity could stand some improvement—even though a good red field seems to be present on the screen. This check can also be made with the naked eye, if you look at the screen from an angle and focus on the dots in a single area.

If the red purity is good, proceed to activate the other two guns (one at a time) and check for a pure blue and green screen. When red is good, the other two colors will generally be just as good.

When purity is satisfactory—or in case the purity adjustments don't react as they should—the next step is to adjust four static-convergence components (blue lateral magnet, and red, blue, and green static magnets) so that the three CRT beams intersect at the center of the screen. Using the pattern from a dot generator, you should be able to make red, blue, and green dots coincide to form a white dot at this one point. Always remember to concentrate on the center dot, as shown in Fig. 2. (It's a good idea to circle this dot with a colored crayon or a grease pencil to facilitate the use of a mirror.)

When the red, blue and green magnet sleeves are slid inward or outward, the following actions should take place: The red and green dots should move diagonally in opposite directions on the screen, crossing through one another; and the blue dots should move up or

NEW SECO "TRI-TESTER"

With Seco's Patented Grid Circuit Test—copied by many, equalled by none



Model 107A

ONLY \$14950 NET



Tests all tubes including the new Nu-Vistors, Novars, Compactrons and 10-pin types.

©1961 Seco Electronics, Inc.

The Seco 107A "Tri-Tester" is the finest, fastest, most complete tester on the market—and at a popular price. Extremely accurate and easy-to-use, this deluxe model provides all essential tests for a wide range of Radio-TV, Industrial and Foreign tube types including sub-miniature types.

Eye and Line Adjustments are set up only once—not individually for each tube. Handy new "FLIP-CHART" tube index lists complete tube data set-up information. Cards on new tube types are issued to registered owners, keeping your unit up-to-date. The

107A "Tri-Tester" is compact, portable and completely self-contained in a handsome, vinyl plastic carrying case.

Seco is a pioneer in the field of modern tube testing research—the originator and exclusive patent holder of the nationally accepted Grid Circuit Test. The "Tri-Tester" is well accepted as a standard by both industry and government agencies. It meets specifications for: FEDERAL STOCK CLASSIFICATION, Tube Tester Type 107-FSN-6625-713-9075. Make your next purchase a Seco product.

ONLY SECO GIVES YOU ALL THESE TESTS IN ONE TESTER

GCT

DMCT

CET

GRID CIRCUIT TEST:

All tubes get 11 positive, simultaneous checks for leaks, shorts and grid emission. This Seco designed and patented "Electron-Eye" test detects "hard to find" faults passed up by conventional short tests.

DYNAMIC MUTUAL CONDUCTANCE TEST:

Pre-wired chassis for effective testing of voltage amplifier and similar tube types. "Fil. Sel." and "Load" are the only settings required. "Good-?-Bad" meter indicates relative transconductance.

CATHODE EMISSION TEST:

The best method for testing pulse amplifier, power output and damper type tubes. Number of set-up operations is kept to a minimum. This test is provided by the free point selector system.

See your distributor for complete details on the Seco Model 107A Tube Tester. He has a complete line of quality Seco units for testing electronic equipment.



SECO ELECTRONICS, INC.

1221 South Clover Drive, Minneapolis 20, Minn.

Please send Free... Model 107A Operating Instructions and Schematic
 "How to Test Tubes" Chart
 Complete Seco Electronic Equipment Line Folder

NAME _____

ADDRESS _____

CITY _____

STATE _____

DEALERS HAVE
BEEN ASKING ABOUT
IT FOR YEARS...

NOW... you can
handle tape head
replacements
quickly... easily
... profitably!

MAKE BIG
PROFITS
WITH

Nortronics®

For years dealers have asked for an accurate, simplified method for handling the replacement of worn tape heads. NORTRONICS, supplier of original equipment heads to the top manufacturers who make more than 75% of the nation's tape recorders, has introduced a tape head replacement program which solves this problem *quickly, easily, and profitably!*

NORTRONICS offers the only tape head replacement program which is complete in all respects... heads are matched electrically and mechanically for more than 250 models of popular recorders... exclusive "Quik-Kit" mounting hardware simplifies installation and vastly increases flexibility of inventory... electrical components included when required... detailed drawings and instructions make work go faster... easier... giving more profit per job!

You can get into this profitable market NOW! Minimum, fast-moving stock required... and profits are high for both distributor and dealer!

Extensive national consumer advertising and publicity campaign is now building demand. NORTRONICS provides you with point-of-sale and counter displays, window streamers, consumer booklets and sales ammunition. Powerful packaging is designed to boost "impulse" sales; helps to move replacement heads fast!

Ask your distributor today about this new NORTRONICS tape head replacement program or write: Thor Johnson, Distributor Sales Manager.

**MOST COMPLETE LINE
OF CONVERSION KITS**

In addition NORTRONICS provides the most complete line of kits for converting mono-phonics and 2 track stereo to 4 track stereo. Boosts sales of accessory equipment for completing stereo systems. Complete Jobber and Dealer information available—write today!



"Music Sounds Best on Tape—
Tape Sounds Best on Nortronic Heads"

Nortronics®

8125 West 10th Ave., North
Minneapolis 27, Minnesota.

down, intersecting with the red and green dots. If one of the color dots at the center cannot be moved far enough to reach the crossover point, remove the corresponding magnet sleeve, rotate it 180°, and reinsert. Also, in case the center blue dot falls to one side of the red-green dot junction, use the blue lateral magnet to move it horizontally. This adjustment will also tend to shift the position of the other two dots, making it necessary to retouch the red and green static-magnet adjustments.

When the static adjustments have been completed, the twelve dynamic controls are used to refine the convergence over the entire screen. The labeling of these adjustments varies from one receiver to another, but the resultant actions on the beams follow consistent patterns.

It will help you to think of the dynamic adjustments as being grouped into several "clusters," each of which is intended to have a specific effect on a certain small area of the screen. Remember—it becomes confusing to watch the entire screen during these adjustments, when you should be concentrating on one particular area.

To help you learn to converge a color receiver without constantly referring to a service manual, we've prepared the dynamic - convergence chart shown at the beginning of this article. It will serve to acquaint you with the convergence controls, their effects on the particular CRT beams, and the area affected by each group of controls. The chart is self-explanatory, as are the reference patterns chosen to demonstrate the screen areas. Under the heading *Control Name*, you'll find the control labels as they actually appear on the convergence panels of specific late-model receivers.

Looking back to the convergence

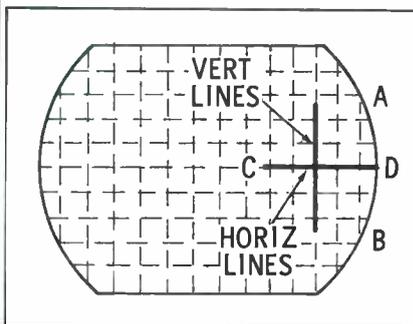


Fig. 5. Check convergence of both vertical and horizontal bars at right side.

circuits used in the RCA CTC7 and CTC9 chassis, we find few differences except in the vertical convergence adjustments. The red and green circuits have *separate* controls marked TILT and AMP, instead of the R-G MASTER TILT, MASTER AMP, DIFF TILT, and DIFF AMP controls used in the newer chassis; for all general purposes, however, the vertical-convergence action is much the same. In older sets, merely use the RED TILT and GREEN TILT controls to converge the center vertical lines at the top and bottom of the screen. Then, adjust the RED AMP and GREEN AMP controls to converge the center vertical lines all the way from the top to the bottom of the screen. Vertical convergence of the blue beam on older sets is the same as in steps 6 and 7 on the chart.

Previous adjustments, *including* static convergence, should be periodically retouched during the procedure. In fact, the complete convergence procedure may need to be repeated at least once, and in stubborn cases, a number of times. Remember, though, one of the most important facts to learn about converging a color receiver is *when to stop*. When the screen appears to have good convergence to within approximately 1½" to 2" of the CRT edges, stop — that's close enough! In cases where you need to leave one beam misconverged in a small area to obtain maximum convergence over the largest possible area of the screen, sacrifice blue; it will not be as noticeable, from a distance, as would red or green.

If acceptable convergence is unobtainable, check to see that the convergence assemblies are in their correct physical location on the neck of the tube, and that the magnets are properly seated in their mount-

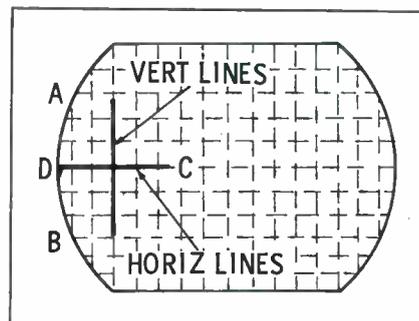


Fig. 6. Follow this pattern to adjust horizontal convergence at left side.

ings. Try relocating the convergence yoke; then reconverge.

Troubleshooting

If, during convergence, a control fails to produce the expected beam-shifting effect, a visual check of the convergence yoke and panel may locate the trouble. In case this fails, further troubleshooting in the vertical or horizontal convergence circuit is in order. By simple analysis of the action on the CRT, determine which convergence circuit is at fault—the vertical or horizontal. Are all three beams—red, green and blue—affected, or only one?

If it's all three, look for trouble in the vertical or horizontal sweep circuits, which supply currents to the convergence yoke. Troubleshoot by checking the input waveforms to the convergence assembly; these are shown in the service information covering the receiver.

If only one color beam fails to move when adjusted, chances are you'll locate a defect in the circuit pertaining to that particular color. Most likely suspects are a bad control, an open coil, or a broken connection on the convergence panel. (The majority of the convergence-circuit components are mounted on this panel.)

Gray-Scale Tracking

Gray-scale adjustments are rather simple in newer color sets, so we won't go through the complete adjustment sequence. Many technicians have their own procedure for gray-scale setup; some merely *feel* their way along until satisfactory reproduction is evident on the screen, while others follow the adjustments as stated in service information. No matter whether you "play it by ear" or "go by the book," keep in mind that the accelerating-grid controls (labeled SCREEN or G2) should be adjusted for the whitest possible highlight areas in a black-and-white picture at high brightness levels, whereas the other set of controls (variously marked DRIVE, GAIN, or BACKGROUND) need to be adjusted for true dark-gray tones in shadow areas. The end result you're after is to keep the raster free of color tinting throughout the brightness-con-

NOW! Profits for you bringing better TV to problem areas.




EMCEE VHF-UHF TRANSLATORS

Distributors, Servicemen... investigate the profits in selling, installing, servicing, the EMCEE Translator in areas that lack good direct TV reception.

You also profit from increased TV set sales, service customers and sales of replacement parts.

- **CONVERSION FLEXIBILITY**... any input channel to any non-adjacent output channel.
 - **FREEDOM FROM INTERFERENCE**... no internal signals which coincide with input to any other translators.
 - **EASY OPERATION UNDER FCC RULES**... simple control and identification unit minimizes maintenance and reduces cost... no operator required.
 - **EASY-INSTALLATION**... available for cabinet/rack mounting or in weatherproof housing.
- TRANSLATORS MAY BE RUN IN TANDEM TOO!

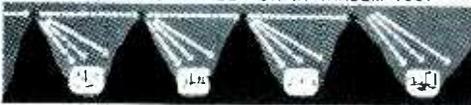

ELECTRONICS, MISSILES & COMMUNICATIONS, INC.
266 E. Third Street • Mount Vernon, New York

Gentlemen: PN

___ Please rush free planning package including data sheet, complete installation check list, coverage calculation form.

___ Please send free reprint of FCC rules covering translators.

NAME _____

ADDRESS _____

CITY _____ STATE _____

ELECTRONICS, MISSILES AND COMMUNICATIONS, INC.
266 E. Third Street • Mount Vernon, New York


THE INDUSTRY'S ONLY COMPLETE "LOOK-ALIKE" LINE

Exact Replacement Needles/Cartridges



Highest quality guaranteed! At your E-V distributor's or write for FREE replacement guide, today! Electro-Voice, Inc., Buchanan, Michigan. Dept. 1127R

ElectroVoice

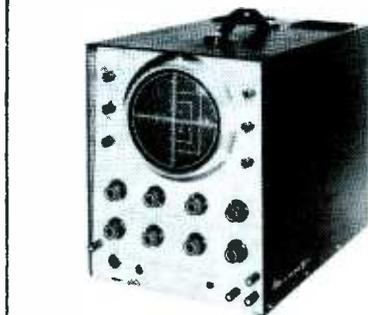

5 inch WIDE - BAND HIGH SENSITIVITY OSCILLOSCOPE

Laboratory quality scope with highly stable circuitry and every feature for accurate TV work, COLOR and BLACK and WHITE. Widely used, too, in many laboratory and industrial applications.

Jackson Electrical Instrument Co.
124 McDonough St. Dayton, Ohio

The New Way To Cut Drive Belt Inventory And Service Time



With instant MAKABELT* servicemen can "custom-make" exact replacement drive belts right on the job - in less time than it takes to read this ad!

The serviceman simply cuts a length of the rubber belting material supplied - threads it through the mechanism and joins the cut ends together with RUBRMERGE* - a unique bonding fluid. The joint is as strong as the rubber itself. You save as much as an hour or more in disassembly and reassembly time.

Instant MAKABELT* saves you time and money . . . and with less "down time" on your customer's equipment, you're sure to make extra profits.

Ask your distributor for MAKABELT* and other TPC products - "STROB-LOOP" and Self-Stick Felt Pressure Pads for tape recorders.

*T.M.

TECHNI PARTS CORP.
156 Hempstead Turnpike, W. Hempstead 9, L. I., N. Y.



OLD WAY



NEW MAKABELT* WAY

trol range. When you achieve this *final* setup, you'll have a good *black and white* picture on a *color* receiver.



Quicker Color Servicing

The Model CA-378 Kine-Color Circuit Analyzer, recently introduced by Antronic Corp. of Chicago, can be used to speed most color-TV servicing adjustments. By connecting the Analyzer between the color CRT and the chassis, the serviceman introduces a color-gun killer arrangement, a means for measuring the current in the circuit to any element of either color gun, and a way to measure the voltage between any CRT element and ground or between any two elements.

The color-gun killer is useful during convergence adjustments of a color set, as well as for controlling the guns during purity checks and gray-scale tracking adjustments. The panel switch (there is one for each gun) simply opens the lead from the chassis to the grid of the color gun, and grounds the corresponding CRT pin. Since the cathode remains at a positive potential, grounding the grid biases the gun enough to cut off that color.

Voltage tests for the Grid-3 pin and the heater "bias" are made at single pin jacks provided on the panel of the CA-378. One pin jack is connected to ground.

Cathode, control-grid, and screen-grid voltages and currents are brought to pin jacks on the front panel by a special switching arrangement that permits choosing one of the three color guns. This means that voltage and current can be measured in the circuit of any element of either color gun. In addition, voltage can be measured between the elements of any color gun. Complete instructions with the unit spell out how to make all measurements.

5 CORES

WETS FASTER **MELTS FASTER**

Solders Better

ERSIN Multicore

5-CORE SOLDER

WORLD'S FINEST

B.I.C. INDUSTRY QUALITY

Multicore Sales Corp. Port Washington, N.Y.

For information, write Department MS 942

BERNS PERFECT PIN-CRIMPER

Picture-Tube Repair Tool

Eliminates that hard soldering job.

only \$1.25

PT-1

Fix loose pin connections in seconds. Pays for itself in time saved on one job alone. 3" long.

U. S. Pat. 2,878,698
Canadian Pat. 592,702

Intermittent operation of picture tubes due to defective solder connections at socket pins is easily corrected through the use of the Berns Perfect Pin Crimper. Actually a 3-in-1 tool that can also be used as a channel-selector wrench and screwdriver, it serves to notch pins and element leads to provide solid electrical connections. Pin keeps its original form.

3 models: PT-1 for 3/32" pin diameter; AU-2 for 1/8" pin diameter and installing C rings; LC-3 for 5/32" pin diameter.

Available at your parts distributor.
Another fine product from:

BERNS Mfg. Co.
9853 Chalmers,
Detroit 13, Mich

Demodulator and Matrix

(Continued from page 33)

phase modulation during each horizontal scanning line; thus, the color circuits receive a signal that represents a continuous change in hue. This signal is alternately keyed on and off so the receiver will produce a series of bright vertical bars separated by dark strips. The chroma-signal phase advances by 30° with each succeeding color bar, resulting in the pattern diagrammed in Fig. 3. One of every 12 "keyed-on" intervals is overridden by a horizontal sync pulse, and the following bar serves as a reference burst signal. Since "burst phase" always corresponds to a greenish-yellow hue in a properly adjusted color set, the visible bars in a keyed-rainbow pattern normally progress from orange-yellow at the left end to green at the right.

If this sequence does not appear when the hue control is set near the middle of its range, the chroma-sync and demodulator - phasing adjustments should be checked as outlined in service data. The bars on the screen can serve as a fairly accurate indicator during this procedure, but more precise adjustments can be made by checking the effect on individual pips in the grid waveforms. These signals are best viewed with the aid of a low-capacitance probe at a scope-sweep rate of 7875 cps, and it's helpful to expand the trace horizontally (as in Fig. 3) for a better look at the series of pips corresponding to just one TV scanning line.

Note that all three waveforms include a wide, deep negative pulse for horizontal retrace blanking of the CRT. In addition, the "keyed-off" intervals between color bars form a convenient zero-reference line. The 10 active color-bar pips vary in height, setting up the proper combinations of grid voltages to produce the desired color sequence. For example, on the third pip following burst, the red-grid voltage (in W1) reaches its highest positive peak; the blue-grid voltage (in W2) stays down near the reference level; and the green-grid voltage (in W3) dips to a negative value. As a result, the color of the third bar on the screen is nearly pure red. On the



NEW VERSATILITY & COMPACTNESS in PROFESSIONAL TEST EQUIPMENT



AC VOLT-WATT METER #261


Formerly designated as #260
Kit \$49.95 Wired \$79.95



AC voltmeter and load-compensated audio-wattmeter of unique quality and accuracy. Measures AC voltage from 1 millivolt to 1000 volts in 11 ranges, and power from .015 milliwatt to 150 watts in 7 ranges, across standard loads from 4 to 600 ohms. The instrument incorporates a tapped power resistor load (4, 8, 16, and 600 ohms) to handle up to 80 watts of power on 8 ohms, and 40 watts on other taps. It may be switched to external load up to 150 watts. The meter is automatically compensated for any load selected, internal or external, to provide a single watt scale for all loads and ranges.

VOLTMETER: Ranges: .01, .03, .1, .3, 1, 3, 10, 30, 100, 300, 1000 RMS volts. Frequency Response: ± 0 db 10c to 150kc, -3 db at 500 kc. Input Impedance: 2 megohm shunted by 15mmf. Accuracy: $\pm 4\%$.

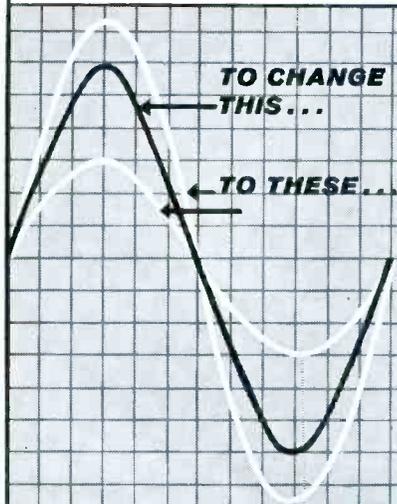WATTMETER: Ranges: 15mw, 1.5mw, 15mw, 150mw, 1.5W, 15W, 150W. Frequency Response: ± 0 db 10c to 100kc. Accuracy: $\pm 5\%$. Internal Loads: 4 (40W), 8 (80W), 16 (40W), 600 (40W). External Loads: 4, 8, 16, 600 (all to 150W).




...USE THESE!



METERED VARIABLE AUTO-TRANSFORMER AC BENCH SUPPLIES

1073 (3-amp rating)
Kit \$35.95 Wired \$47.95
1078 (7 1/2-amp rating)
Kit \$42.95 Wired \$54.95

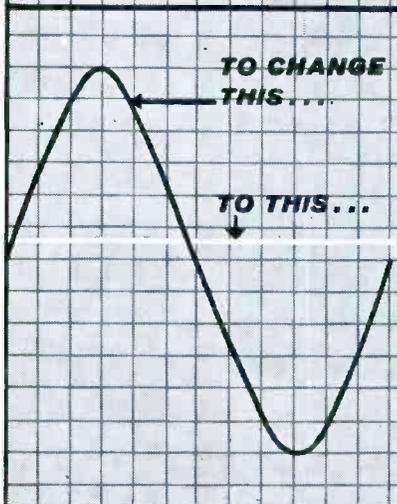Connect to 60 cycle, 120 volt line and obtain any desired voltage between 0 and 140 volts. Highly efficient variable auto-transformer of toroidal core design gives you continuously variable output, linear versus rotation, with excellent regulation and negligible waveform distortion. Model 1078 permits either 50 or 60 cycle operation.



...USE THIS!



Extra-Low-Ripple 6- and 12-Volt BATTERY ELIMINATOR AND CHARGER #1064

Kit \$43.95 Wired \$52.95

Connect to 60 cycle, 120 volt line and obtain highly filtered low dc voltage continuously variable over two ranges 0-8, 0-16 VDC. Heavy-duty pi-type LC filter is rated to take the full rated current output continuously (10 amps on 8V range, 6 amps on 16V range), reduces ripple as low as 0.3% at 2 amps on the 16V range. An essential instrument for servicing battery-operated equipment, including transistor or hybrid types, and an excellent battery charger.

Also New From EICO:



AC VTVM &
AMPLIFIER
#250
Kit \$49.95
Wired \$79.95



TRANSISTOR
AND CIRCUIT
TESTER #680
Kit \$25.95
Wired \$39.95



IN-CIRCUIT
CAPACITOR
TESTER #955
Kit \$19.95
Wired \$39.95

For complete catalog of over 106 EICO kits and wired units—hi-fi, test equipment, citizens radio, ham gear—plus name of nearest distributor, write to dept. PF-11



ELECTRONIC INSTRUMENT CO., INC.
3300 Northern Blvd., Long Island City 1, N. Y.

ADD 3% IN THE WEST Export Dept., Roburn Agencies Inc., 431 Greenwich St., New York 13, N. Y.

next pip, there is a little less red drive and a little more blue drive; thus, the fourth bar appears red with a definite bluish tinge.

During the sixth bar — when the input-signal phase has advanced 90° past the point of maximum red output — the voltage on the red grid remains at the background reference level (see W1). This and other “nulls” found in the three color-difference waveforms are the most reliable check points for setting up correct phase relationships in the chroma circuits. In a perfectly adjusted receiver, nulls should also appear at the third and ninth pips in W2 on the blue grid, and at the first and seventh pips in W3 on the green grid. Some leeway is permissible; for instance, W2 in Fig. 3 reaches a null somewhere between the second and third pips, but this slight displacement does not cause an obvious defect in the color-bar pattern on the screen of the test receiver.

If any greater phasing error is apparent in the waveforms, check to see if all the nulls are displaced

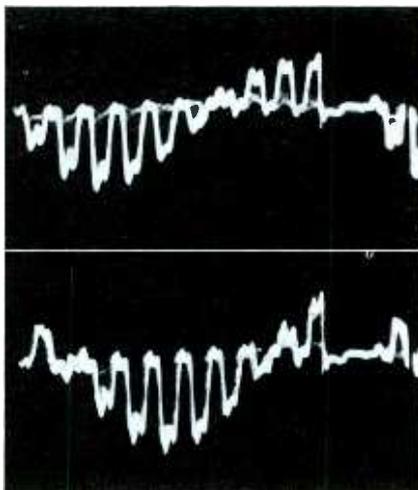


Fig. 4. Waveforms W4 and W5 applied to grids of R-Y and B-Y amplifiers.

equally in the same direction; if they are, they can usually be brought back to normal by readjusting the hue control or the burst-phase transformer. When only one or two nulls are out of place, the fault ordinarily lies in the demodulator-phasing adjustment or in one of the demodulator circuits.

Signal Amplitudes

Even when properly phased, the

CRT-grid waveforms will produce correct color mixtures only if the ratio of their amplitudes is normal. The red and blue signals should generally have about the same peak-to-peak value, but that of the green signal is likely to be somewhat lower. (This point is illustrated by the waveforms in Fig. 3, which were taken without resetting the vertical gain controls on the scope.)

In circuits of the type shown in Fig. 1, attenuation of a CRT-grid signal is often due to low gain in one of the color-difference amplifiers — V23B, V22A, or V22B. If this trouble involves a change in the DC plate voltage of the amplifier, the error will also be passed along to the associated CRT grid through the DC coupling circuit — resulting in a tinted raster. However, the technician may cover up a mild case of this symptom by readjusting the drive or background controls, before he realizes that a trouble is present.

Signal measurements will clear away any doubt about the relative gain of the color-difference circuits.

**LEARN FM
2-WAY RADIO
SERVICING
AT HOME**

- Earn More Money
- Build a Better Future

Advancement and increased earnings are waiting for you in the expanding communications field. The Motorola Training Institute's home study course in FM 2-way radio servicing can enable you to take advantage of these profitable opportunities now. Learn all about servicing the new transistorized equipment . . . learn advanced techniques for handling complex service problems easier and faster.

In addition to this wealth of practical application knowledge, you will also be preparing yourself for your 2nd Class FCC Radio-telephone License. For full details, send coupon today. There is no obligation and no salesman will call.

MOTOROLA TRAINING INSTITUTE
4545 West Augusta Boulevard • Chicago 51, Illinois • Dept. ACX243

Please send me full details on the Motorola Training Institute's planned home study program on FM 2-Way Radio Servicing.
I now hold _____ FCC License.

Name _____
Address _____
City _____ Zone _____ State _____

Complete Assortment of EXACT REPLACEMENTS THERMAL CIRCUIT BREAKERS

17 MODEL NUMBERS

- F2A SILVERTONE MOTOROLA G.E. WESTINGHOUSE, WESTERN AUTO
- F2A-B MOTOROLA 80C750604
- F2A-C WESTINGHOUSE 753V006H01
- F2 1A SILVERTONE 43-9-2
- F2 2A MOTOROLA 80C66390A02
- F2 2A-B ADMIRAL 84B17-4
- F2 5A WARWICK 43-1-2
- F2 6A RCA 945830-2
- F2 75A SILVERTONE 43-12-2
- F2 75A-B MOTOROLA 80C66390A01
- F2 75A-C MOTOROLA 80K753396
- F2 75A-D PHILCO 42-2136-1
- F2 75A-E RCA 945830-1 G.E. ET10X32
- F3A MAGNAVOX 180672-1
- F3A-B MOTOROLA 80K647226
- F4A PHILCO 42-2136-2
- F4A-B EMERSON 808018



LOOK FOR THIS DISPLAY AT
YOUR FAVORITE DISTRIBUTOR

WRITE FOR *Free*
CROSS REFERENCE TO:

WORKMAN *Electronic*
PRODUCTS, INC.
BOX 5397 SARASOTA, FLA.

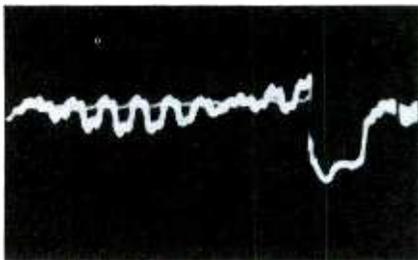


Fig. 5. W6 is developed across cathode resistor R178 in circuit of Fig. 1.

The overall peak-to-peak readings of the CRT-grid waveforms, including the horizontal blanking pulse, are valid indications of amplifier gain—since the pulse is fed into the common cathode circuit and amplified by all three color-difference stages.

If one or more of the CRT-grid inputs definitely seems weak, the next step in trouble isolation is to check the signals being fed to the R-Y and B-Y amplifier grids from the chroma demodulators. Both of these waveforms (W4 and W5—see Fig. 4) should have practically equal peak-to-peak values if the circuits ahead of the color-difference amplifiers are working properly.

The color-bar pips in W4 and W5 follow a pattern almost exactly opposite to those in W1 and W2, since the signals are inverted by the R-Y and B-Y amplifiers. However, the nulls are slightly displaced, indicating that the amplifiers introduce an approximate 20° phase shift in addition to a polarity reversal. The explanation of this slight phase alteration is tied in with the explanation of how an input signal is developed for the G-Y amplifier in the circuit of Fig. 1.

The cathodes of all three color-difference amplifiers are returned to ground through a common, unby-passed resistor R178. When W4 and W5 are applied to the red and blue amplifiers, replicas of both these signals are developed across the cathode resistor, and the resultant waveform (W6) is as shown in Fig. 5. This is a G-Y signal of the same polarity as W3. It is amplified by V23B, which operates as a cathode-driven, grounded-grid stage; however, it subtracts from the outputs of V22A and V22B.

This degenerative effect of the cathode circuit on the R-Y and B-Y signals is taken into account in the adjustment of demodulator phasing.



CADRE HAS A PLAN FOR YOU

CB means big business—and many service-technicians—particularly those who sell and service auto radios or who install P.A.—are equipped to enter this lucrative new field of communications equipment.

Cadre, leader in CB, offers you a sensible approach to selling this market—the most powerful all-transistor CB radio, backed up by sales aids that pave the way to big Citizens Band 2-way radio profits.

CADRE '510' ALL-TRANSISTOR 5-WATT CB 2-WAY RADIO

POWERFUL—Highest transmitter power authorized by FCC, 5-watts, provides maximum "talk" range—up to 20 miles (30 on water). Extra transmission punch through speech clipping. 5 crystal-controlled transmit/receive channels assure bull's-eye communications. Rugged microphone has "press-to-talk" switch and retractable cord. Audio power is a full 2.5 watts.

SELECTIVE—Dual-conversion superheterodyne receiver circuit with new tuned ceramic filters provides clear reception without adjacent channel interference. Automatic Noise Limiter suppresses external interferences. Adjustable squelch silences speaker for noise-free standby reception. Manually tunes in all 23 CB channels.

VERSATILITY—Built-in dual power supply, 12VDC/110-220VAC, for mobile or base station. Portable pack accessory with rechargeable batteries for field use.



RELIABLE—Negligible heat, no tubes to burn out because it's 100% transistorized—18 transistors, 8 diodes. Printed board, modular construction. Absorbs road shock without damage.

COMPACT—Slimmest, trimmest full-power unit takes up little leg room in car or truck. Fits conveniently on desk.

ECONOMICAL—Approximately 20% battery drain of a tube unit. Low current drain prolongs vehicle battery life. Also costs less to operate on AC.

CADRE PROMOTION SUPPORTS YOU



ADVERTISING—ads in all magazines reaching CB users, potential CB users—doctors, trucking companies, fleets, mariners.

DISPLAY—unique point-of-sale display '510' mounted on a simulated dashboard will attract customers to the Cadre display in your store, accommodates Cadre literature.

MAILINGS—Cadre supports you with an effective mailing program consisting of letters specially tailored to specific markets, imprinted on your letterhead if you wish.

STUFFERS—Cadre will supply you with descriptive, colorful line stuffers which you can give away or mail to your customers and prospects. Fit into point-of-sale display.

BOOKLET—Informative booklet of interest to everybody who owns CB equipment or is contemplating purchase of CB equipment will be featured in national advertising.

AD MATS—Effective ad mats for hard-hitting local newspaper advertising.

Wire . . . write today . . . phone for further information.



CADRE

INDUSTRIES CORP., COMMERCIAL PRODUCTS DIVISION, ENICOTT, N.Y. AREA CODE 607. 748-3373
Canada: Tri-Tel Assoc., Ltd., 81 Sheppard Ave. West, Willowdale, Ont. Export: Morhan Exporting Corp., 458 Broadway, N.Y. 13, N.Y.

Aside from this point, the X and Z demodulators are basically designed to recover the red and blue color-difference components of the signal coming from the chroma bandpass amplifier. A brief review of this process will make it easier to pinpoint troubles that result in phase or amplitude distortion of the demodulator outputs.

Demodulator Operation

The basic idea of demodulation is to combine the received chroma signal with a locally-generated 3.58-

mc signal in two different ways, to obtain a pair of waveforms from which the color-difference and matrixing circuits can reconstruct all hues. In most color receivers, the demodulators are respectively set up for maximum (or near-maximum) response to R-Y and B-Y phase modulation of the chroma signal. Since a 90° change in phase is what makes the difference between these two signal components, the desired waveforms can be recovered by feeding 3.58-mc reference signals approximately 90° out

of phase to the two demodulators.

Reference signal W8—fed to the cathode of the X demodulator—is nearly 180° out of phase with the chroma signal at the grid, when the latter is modulated at R-Y phase. The negative peaks of this cathode signal then coincide with the positive peaks of the grid signal, and this conduction causes maximum output from the demodulator. When the phase of the chroma signal changes, the demodulator-plate current decreases — reaching a minimum when the grid and cathode signals are in phase.

In the filtered output signal (W4), note that the strongest negative pulse, corresponding to maximum plate current in the X demodulator, is the third (red-bar) pip. The X output crosses the zero-reference line (equivalent to no chroma modulation) at a point between the sixth and seventh pips. W5 reaches its maximum negative value at about this time, since W9 (at the cathode of the Z demodulator) lags W8 by nearly 90°. Therefore, blue is the dominant output in this portion of the color-bar signal.

G-Y modulation in W7 reduces the plate current of both demodulators to minimum, as indicated by the positive value of the tenth pip in both W4 and W5. The R-Y and B-Y amplifiers invert this pip, developing negative outputs which cut off the red and blue CRT guns. At the same time, a positive pulse is developed in the common cathode circuit and amplified in the G-Y stage without inversion—driving the green gun into conduction.

Summary

Every change in chroma phase causes the demodulators to conduct in different proportions. As long as the circuits between the demodulators and the CRT grids are in correct balance, all three grid voltages will be varied in the exact amounts necessary for accurate reproduction of all colors. When some hues are poorly represented, troubleshooting is a matter of checking for faults in the sections of the circuit known to affect these hues. Analyzing the phase and amplitude of pertinent test signals is an excellent short cut to pinning down the trouble. ▲

interested in

Broadcasting - Communications

IF SO, YOU SHOULD BE RECEIVING
HOWARD W. SAMS

BROADCAST
ENGINEERING

The Technical Journal of Broadcasting-Communications—Increase your technical know-how by reading the only technical magazine that concentrates its coverage on the engineering aspects of broadcasting-communications. **BROADCAST ENGINEERING** features the practical side of everyday service, maintenance, and operation of radio-TV broadcasting-communications equipment.

Editorially, **BROADCAST ENGINEERING** covers a wide range of technical subjects, from microphone, camera, turntable, recorder and projector to transmitter and antenna. FM multiplexing, color TV, video recording, stereophonic broadcasting, automation and audio equipment are all covered, as are all other engineering subjects of interest to those responsible for station operation. Special editorial reports describe new station installations, remodeling and allied subjects, and each issue brings you all F.C.C. amendments affecting technical operations. Every significant facet of the technical phases of broadcasting is covered thoroughly.

BROADCAST ENGINEERING articles are designed to supplement your technical knowledge, and teach you the vital "how-to-do-it" information you need to be qualified in this rapidly expanding field. It will help you become authoritative on the technical and management aspects of broadcasting-communications.



YOUR GUARANTEE

If after reading your first issue of *BROADCAST ENGINEERING*, you are not completely satisfied with it, let us know and we will cancel your subscription and refund your full purchase amount immediately.

Use this handy order form to have **BROADCAST ENGINEERING** mailed to you every month

HOWARD W. SAMS & CO., INC., 4300 W. 62nd St., Indianapolis 6, Indiana

Please enter my subscription to *BROADCAST ENGINEERING* for the subscription period indicated.

3 years \$13.00 2 years \$10.00 1 year \$6.00

Check or money order enclosed Please bill me

Name _____

Firm _____

Address _____

City _____ Zone _____ State _____

112

Please check BOTH Your business and occupation

- | | |
|---|--|
| <input type="checkbox"/> AM Radio Station | <input type="checkbox"/> Owner, Manager, Officer |
| <input type="checkbox"/> FM Radio Station | <input type="checkbox"/> Engineer, Technician |
| <input type="checkbox"/> Television Station | <input type="checkbox"/> Other _____ |
| <input type="checkbox"/> Network | |
| <input type="checkbox"/> Consulting Engineer | |
| <input type="checkbox"/> Manufacturer or Distributor | |
| <input type="checkbox"/> Recording Studio | |
| <input type="checkbox"/> Government Agency, Library, School | |

Service Aids

(Continued from page 24)

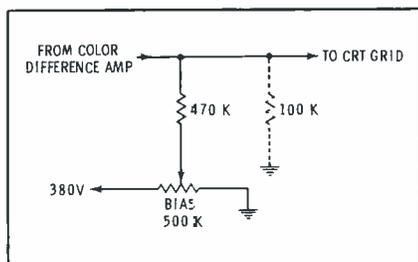


Fig. 1. 100K resistor disables CRT gun.

these are lined up to produce yellow, you can restore blue and converge it with the yellow lines.

Another time when you might want to disable guns is during in-the-home setup of color sync. Using a keyed-rainbow generator, you can remove two of the primary colors and adjust chroma phasing to remove all of the color from a certain bar in the pattern. (Exact instructions appear in service manuals.)

How does a 100K resistor disable a grid circuit? Fig. 1 gives the answer. By shunting from grid to ground, it alters the voltage division in the grid circuit so that the grid voltage is lowered. The decrease is enough to bias off the gun. A short from grid to ground would accomplish the same end, but would place too heavy a load on the circuit between B+ and the grid. At least one commercial unit disables the gun by disconnecting the grid from its divider network and grounding it. With the cathode highly positive, the grid is cut off, disabling the gun.

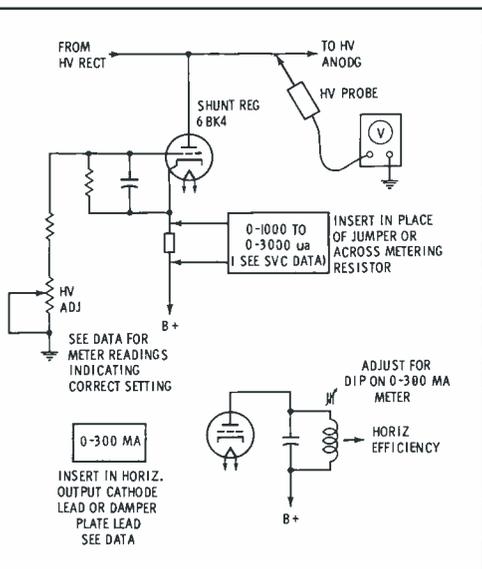


Fig. 2. Meters show the color-TV technician what's going on in HV circuits.

High-Voltage Accessories

In color TV, high voltage is not checked by just drawing a "zap" from the anode lead and estimating the strength of the arc. To maintain the voltage regulation necessary for proper sweep, focus, and convergence—and also to prevent overburdening the horizontal sweep system—a rather exacting procedure using meters is required to check the high-voltage system.

Fig. 2 shows a typical test setup. The high voltage is actually measured; a standard shop VOM or VTVM can be used, provided you

also use a HV multiplier probe rated at 30 kv or more. Two current meters indicate, respectively, the current drawn by the HV regulator cathode circuit and that drawn by the over-all horizontal sweep circuit. When the HV ADJUST pot is turned to adjust the anode voltage, both current meters must be monitored to see that regulator current is neither too high nor too low, and that the horizontal output and damper stages are not drawing excessive current.

A HORIZONTAL EFFICIENCY coil—same circuit location as the hori-

BE READY TO SERVICE COLOR TV



Walsco Repair Kit no. 2599x puts you in business . . . For Only \$21⁹⁰

The 5 essential Service Tools all in one kit . . .

CAT. NO.	TOOL	USE
2590	Degaussing Coil	eliminates stray magnetic fields for easy purity adjustment
2595	Grid Grounding Box	grounds kinescope control grids . . . each switch and cord color coded for quick connection
2548	Interlock Cheater	protects you from shock hazard . . . permits insertion of a voltage probe
2589	Alignment Tool	two-in-one tool for alignment of concentric controls . . . saves time
2596	Color Viewer	three viewing filters simplify phase and matrix adjustments, let you handle many service calls in-the-home

COLOR TV TUBE MICROSCOPE

Precision pocket-size scope that magnifies dots 25 times for SIMPLE and ACCURATE adjustment of purity magnet, yoke, and rim magnets

CATALOG NO. 2594
DEALER NET 19⁵⁰

and FREE! useful Color TV service book included with each kit

Zenith and other leading color TV set manufacturers recommend using Walsco Degaussing Coils and Color TV Accessory Tools in equipment servicing. And only Walsco is ready now to outfit you with all the tools you need.

For more information, write for Specification FR3554.

WALSCO ELECTRONICS CO.

a division of GC-Textron Electronics, Inc.

400 S. WYMAN ST., ROCKFORD, ILLINOIS

zontal linearity coil in black-and-white receivers—provides a means of “cooling down” the horizontal flyback current. Just as in some early monochrome receivers, sweep components will last a lot longer if the coil is tuned for a (minimum) dip in the milliammeter reading.

The low milliammeter range of a shop VOM can be used in place of a special current meter in some cases, but there are some instances where this introduces excessive resistance in the regulator circuit—thus lowering the readings. An ordinary meter may be used sometimes, if its shunting effect is allowed for; the set's service information will explain. However, it's a lot more convenient to have at least one special meter just for this purpose, so you can use two current meters at once to monitor all points involved in HV adjustment.

Bias Supplies

You may have heard that color-TV alignment often requires three or four separate clamping bias sources; perhaps you marveled at the statement, dismissed it as the complexity of color, and didn't even

find out what the various bias sources were for. The color sets of a few years ago required four bias sources for video-IF alignment. Two of these replace the RF and IF AGC bias, respectively; two others substitute for fixed negative bias normally obtained from the horizontal sweep circuit. (Specifically, the grid of the horizontal blanking amplifier and the bottom of the brightness control). These bias sources become necessary because the instructions call for disabling of horizontal sweep during alignment, to get rid of interference on the alignment curve and permit easy use of the multimarker.

By the way, this brings up another service accessory—a 2000 - ohm, 100 - watt resistor (1500 - ohm for some chassis) which is wired across B+ to take the place of the horizontal circuitry as a load. Removing a load of that size from the B+ circuit, without substituting for it, could raise the B+ voltage enough to affect IF frequency response and the accuracy of alignment!

In some of the more recent models, the IF-AGC bus can be

grounded to chassis, reducing the bias-pack requirements to three. In still others, no fixed bias is needed from the horizontal section, and one or two bias sources will suffice. None of the above-mentioned sets require a bias voltage greater than -15 volts at any of the points mentioned.

Test Extensions and Harness

Using test extensions with a color set produces the usual problems of cable capacitance—video smear in full color, possible cross-coupling effects between sweep leads (affecting convergence as well as sweep)—but these conditions can be taken into account during servicing. They can be somewhat alleviated by making extensions no longer than really necessary and by dressing leads of extension cables as far apart as practical (to discourage cross-talk). There's no question, however, that some type of extension setup is essential for servicing color receivers.

The necessary hookup includes the following: CRT base extension, HV extension, yoke leads, and convergence-yoke extension. CRT bases are the same (with 14 pins) on all



STOP  **Tape SQUEAL!**

NEW FORMULA!

... for Tape Recorder Heads
... cleans and lubricates to stop squeal and reduce wear!

Order...
Cat. Number 250

INJECTORALL'S "TAPE CLEANER," a three ounce aerosol spray with a wire cleaner, removes oxide coatings and leaves an anti-squeal lubricant that stops tape squeals and reduces wear on recording and playback heads.

Dealer Net..... **\$119**

INJECTORALL COMPANY
Brooklyn 14, New York
In Canada: Goldstein Agencies P.O. Box 187, Downsview, Ontario



NEED A 110 V. A. C. OUTLET?

IN CAR, BOAT OR TRUCK, YOU HAVE IT WITH A

terado POWER INVERTER

Actually gives you 110 volt, 60 cycle A.C. from your 6 or 12 volt D.C. battery! Plug inverter into cigarette lighter, and operate lights, electric shavers, record players, tape recorders, electric tools, portable TV, radios, testing equipment, etc. Frequency will not change with change in load or input voltage.

Models from 15 to 300 watts, priced as low as **\$12.95** LIST

See Your Electronics Parts Jobber. or Write:

terado CORPORATION
1073 RAYMOND AVE.
ST. PAUL 8, MINN.
In Canada: ATLAS RADIO CORP. LTD. — Toronto, Ont.

color sets, so one cable will take care of all. You'll need two basic types of heavy-duty HV leads—one for the older-style CRT's and another for the new sulfide tubes introduced last year.

Yokes are now standardized to connect to a bundle of four plug-in, color-coded leads—yellow and yellow/black for the vertical windings, red and blue for the horizontal. Special extensions are available for these. In addition, you'll find octal-plug yoke cables for some older sets.

The convergence plug in most sets is also octal. Notable exceptions are Zeniths, which use a square 9-pin plug, RCA Chassis CTC5, which has a 12-pin plug, and RCA CTC 4 which has a 6-prong plug.

Screen Inspectors

It seems you're always craning your neck to see the reflection of a color-TV screen, or squinting directly at the screen itself during set-up. Make it easy on yourself with a couple of optical accessories. One is a *good, large* mirror—one that will let you see the entire screen clearly while you're manipulating the yoke and purity magnets from behind the set. Another is a magnifying glass or pocket-size microscope that gives about 10-power magnification. It will let you look at a small sample of the phosphor dots on the screen to see if the beams are landing in the correct area of each dot.

Additional Aids

Countless other accessories are available to simplify the job of the color-TV technician. Color-CRT brighteners let him extend the life of weakening picture tubes. Special tools make it easier to adjust concentric controls, and other special alignment points. Some chassis even require special cheaters for the high-voltage interlock.

Special servicing aids are for a purpose—they are time-savers. The serviceman who has built his reputation for better, quicker service must make use of aids such as these to enable him to handle the increasing demands on his time. And better use of his time will help him build his reputation for better, quicker service. It just works that way! ▲

SPECIAL FEATURES for DECEMBER PF REPORTER

Profit from a Flat-Rate Service Call

It can be done, by careful planning, as shown in this article.

Got the Jitters?

New ways to troubleshoot one of the most elusive of service problems.

Analyzing Closed-Loop Systems

Explains how to understand these unusual control arrangements.

Stereo FM Report

Facts and figures on how stereo-FM is spreading throughout the country.


Signal vs Power Transistors

Describes in detail why each is better for certain applications.

Plus all the regular features:

- Notes on Test Equipment
- Symfact Charts—What happens in vertical multivibrators!
- The Troubleshooter
- Previews of New Sets
- Video Speed Servicing

And lots of other full-sized features!

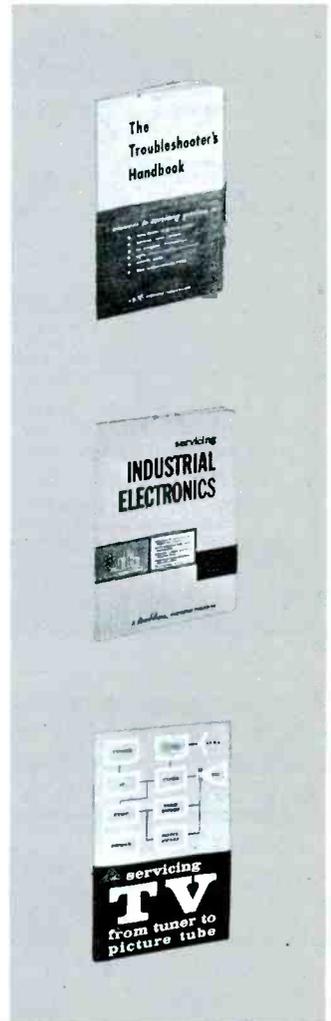

Get Free Premium Books With Subscription

Enter my subscription to PF REPORTER and send me free book(s) checked.

3 Years \$9.00 2 Years \$7.00 1 Year \$4.00

The Troubleshooter's Handbook
 Servicing Industrial Electronics
 Servicing TV from Tuner to Picture Tube } Check one for each year you subscribe

Bill Me Remittance Enclosed Extend Present Subscription

Take this coupon to your distributor, or mail to:
Howard W. Sams & Co., Inc.

4300 W. 62nd St., Indianapolis 6, Ind.

Name _____

Firm _____

Address _____

City _____ Zone _____ State _____

1062

Please Check Your Business Classification


- Independent Radio, TV Serviceman
- Retailer with Service Department
- Industrial Electronics Service
- Other (Specify occupation and title)
- Owner, Mgr.
- Service Mgr.
- Employee

"Eliminates Soldering"

PERFECT *Audio*

"PIN-PLUG" CRIMPER

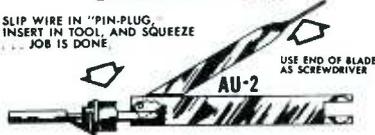SLIP WIRE IN "PIN-PLUG,"
INSERT IN TOOL, AND SQUEEZE
... JOB IS DONE.



U. S. Pat. 2,878,698

Canadian Pat. 592,702

USE END OF TOOL TO
PUSH ON GROUND CONNECTOR

Useful in making hi-fi, audio and sound, radio, phono, and TV equipment connections.

only

\$1.25

C-rings 1c each

Get the tool that makes solid electrical pin-plug connections without soldering or destroying pin form. Use one end for pin crimping, the other to push on C-ring clamp for braided-shield ground connection. Nothing like it anywhere.

3 models: PT-1 for 3/32" pin diameter; AU-2 for 1/8" pin diameter and installing C rings; LC-3 for 5/32" pin diameter.

Available at your parts distributor.

Another fine product from:

BERNS

Mfg. Co.

9853 Chalmers,
Detroit 13, Mich

POWER TRANSISTOR

POPULAR POWER TRANSISTOR FOR USE AS A REPLACEMENT IN MOST DELCO AUTO RADIOS




REPLACES
2N277, 2N278,
2N441, 2N442,
DS-501.

Individually packaged in a plastic see-thru box.

Cross reference and installation data included.

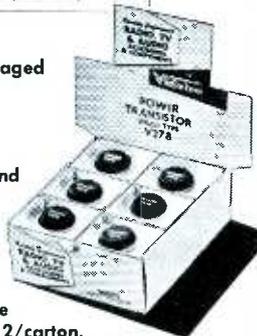Available in a compact attractive counter display, 12/carton.



Vidair ELECTRONICS MFG. CORP.
365 BABYLON TPKE. — ROOSEVELT, N. Y.

Color TV Station

(Continued from page 40)

be brought back together with the centering controls. With any luck at all, registration of the red and green channels is complete.

The same routine is followed in registering the blue channel over the green. Finally, the engineer looks at all three—the red and blue channels “supered” over the green. If registration is correct, only one chart will be seen.

Shooting

Now it's time for the engineer to look at the scene to be televised. First, he'll light the set. Many types of lights are used—spots and floods of all descriptions and power, from a single-candlepower light to a 5-kw monster mounted on wheels. “Lazy boys”—lights on scissors-like mountings—are pulled down, spotlights are zeroed in, and a dash of top light is added to highlight a good hairdo (and also add depth to the set). A basically flat light, between 250 and 500 foot-candles, is usually sufficient to light a set. The good engineer never uses more light than is necessary to get the desired results.

The engineer has now checked and rechecked the beam and target settings of the three orthicons, the three focus controls, and the pedestal and gain of each channel for the same output. Now it's time for him to take a look at the scene and make his final adjustments.

The equipment has now been on for probably two or three hours. The burst flag generator is working properly, sending keying pulses to the colorplexer to control the injection of the 3.58-mc burst into the composite signal. The colorplexer and the color monitor have been adjusted and balanced to the engineer's satisfaction, using signals from the bar generator. Now, he can switch the colorplexer from the bar generator to the camera. (It's embarrassing to have the switcher operator place the color signal on the air, only to see the color bars on the air monitor, instead of the desired stage scene. They are pretty, though.)

On the Air

With the test charts out of

the way, the cameraman dollies the camera back to a position from which he can get a good shot of the entire set to be televised. He then mechanically focuses the camera with the control handle. The camera controller (at the main control panel) makes any final adjustments necessary. The only adjustments left to be checked are the master gain, the iris control on the camera, and the master pedestal control, which maintains the proper blanking level in the three color channels. The controller may have to touch up the individual shading, both horizontal and vertical, as well as individual gain adjustments of the separate channels; often, he ends up painting, electronically, his own desired picture.

Once he is satisfied with the color-camera output, the engineer places the shield over the channel controls; only the master pedestal and gain controls are left for adjustment during the televising of the show. This eliminates the possibility of upsetting the registration or focus of one channel by turning the wrong knob.

All Done

After the show is over, and the studio lights are killed, the camera B+ is shut off; but filaments are left on so the camera will not cool down too quickly. Later all equipment is shut down, the camera is dollied back to its storage position, and the camera cables are coiled near the camera.

If there is any time left in the engineer's day, he'll do some maintenance on the camera or its associated equipment. There are always tubes to be checked and lenses, prisms, and mirrors to be cleaned. Blower motors need periodic lubrication. Many periodic checks are required so the gear will be ready to perform its duties at the desired time.

Finally, the last tube has cooled, the maintenance logs have been filled out, and the live-color shows for the day have been “put to bed.” The color-TV studio engineer can feel the satisfaction of a job well done, but he must also face the disquieting feeling of knowing it all has to be done over again tomorrow. ▲

PRODUCT REPORT

For further information on any of the following items, circle the associated number on the Catalog & Literature Card.


Transistor Protector (42T)



Littelfuse has developed a small device to protect transistors from both current and voltage overload. Known as "Transistor Protector," the unit can be mounted in printed-circuit boards or used with conventional-type wiring. The small cylindrical-shaped body houses a plug-in "Microfuse." The unit is presently available in the 20- to 200-volt range and for cur-


rents in the .05- to 1-amp range. Littelfuse expects to extend the line to other values at a later date.

Base-Station Antenna (43T)

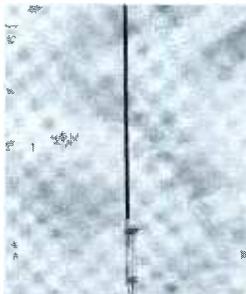

Taxi operators, police and fire departments, and commercial car fleets represent excellent markets for the new "Beacon" line of omnidirectional base-station antennas by Mark Products. Designed for use in the 150- and 450-mc ranges, these units have low VSWR and high strength-to-weight ratios. List prices range from \$75.00 for the eight-foot Model 4506 to \$175.00 for the 16-foot Model 4585. Longest unit in the line is the 21-foot Model 1506, priced at \$150.00.

UHF Antenna (44T)

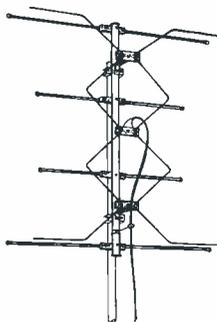

This new antenna by Antennacraft features all-aluminum, rust-proof construction and an anodized finish. It uses a multiresonant collinear reflector system and provides 37% more gain than previous chicken-wire-type antennas. Two models are available: SA-1483, for channels 14 to 83; SA-7083, peaked for channels 70 to 83. Each model, shipped preassembled, carries a price of \$10.95.

Wire Caddy (45T)



A combination container and reel, for shipping, holding, and dispensing certain types of wire, has been developed by South River Metal Products Co., Inc. This novel package is available with 300-ohm twin lead-in wire for antenna installation purposes. Each "Wire Caddy" (Model WC shown here) contains 1000 feet of wire. South River plans to furnish aluminum and steel guy wire, coaxial cable, and other products in the new type of package.

PRODUCT NEWS from EPL

...no one matches bias tap, regulation, filtering

Only supply with fully adjustable bias tap for servicing ALL transistor portables



0-20VDC at 150MA Power Supply Services Transistor Portables

Fully assembled EC-3.. \$19⁹⁵

Guaranteed 1 Year

Only Electro's EC-3 services all transistor portable radios... 1.5, 3.0, 2.8 or any other bias voltage, or center-tap arrangement

See how MUCH more EC-3 gives you for LESS money.

Brand	Output Voltage	Output Current	Meter	Bias Tap	Filtering	Rectifiers	Warranty
EPL	0-20V (0-24V)	150MA (100MA)	Edge Reading 0-24V/100MA (5% accuracy)	0-6V Fully Adjustable & Filtered	Condensers & Choke	Rugged Selenium Stack	1 Year
A	0-24V	100MA	0-24V/100MA (10% accuracy)	1.5V Fixed not Filtered	Condensers & Resistors	One Silicon Diode	90 Days
B	0-15V	100MA	None	None	Condensers	Silicon	90 Days
C	0-25V	100MA	0-25V/100MA (5% accuracy)	1.5V Fixed	Condensers	Silicon	90 Days
D	0-24V	100MA	0-24V/100MA (5% accuracy)	1.5V Fixed	Condensers	Silicon	90 Days

Available from Your Local Distributor
MOST COMPLETE LOW VOLTAGE LINE... 6 to 125 VDC
 Write for Complete Line Catalog PS-562



ELECTRO PRODUCTS LABORATORIES

6125-T Howard, Chicago 48 (Niles), Ill.
 Chicago Phone: 775-5220

2232

Canada: Atlas Radio Ltd., Toronto

Since 1936... Pioneers in Low Voltage DC Power Supplies

LUXO illuminated magnifiers for visual accuracy in electronics and industry.




Ultronix, Inc., ultra-precision resistors under Luxo magnification.

The new, versatile Luxo Illuminated Magnifier combines magnification, large viewing area, cool Circline fluorescent light and provisions to increase magnification from 3 to 11 diopters.

OUTSTANDING FEATURES:

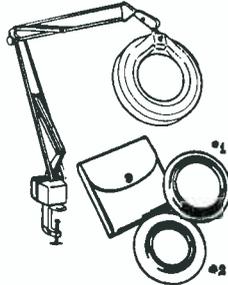- 3 Diopter, distortion-free Bausch & Lomb (5 inch dia.) glass lens.
- Lightest touch adjusts magnifier to any position . . . and the lamp STAYS PUT without tightening devices. Leaves both hands free for the job.
- Magnifier can be mounted anywhere and turned out of way when not in use.



EXCELLENT FOR:

- Inspection and quality control
- Assembling and servicing miniature components
- Reading small parts numbers and checking fine measurements.

There is a Luxo Lamp for every purpose. Contact your supply house or write for catalog #300.



LUXO LAMP CORPORATION
Chicago • Port Chester, N. Y. • San Francisco

FROM ONEIDA • A PRACTICAL SERVICE TOOL THAT QUICKLY AND EASILY ATTACHES TO YOUR PRESENT GUN FOR ONLY

\$7.95

CLEANS PRINTED
CIRCUIT
TERMINALS
IN SECONDS.
HERE ARE
A FEW
FEATURES
THAT
ONEIDA
OFFERS



- CLEANS TERMINALS FAST
- ATTACHES TO GUN QUICKLY
- PAYS FOR ITSELF IN A FEW DAYS
- WILL NOT BURN OR SMEAR CIRCUIT BOARDS
- COMPLETELY COVERED BY PATENTS— ONLY ONE ONEIDA
- ABSOLUTE GUARANTEE—COMPLETE SATISFACTION OR YOUR MONEY REFUNDED

Oneida is the line that SELLS ON SIGHT.

ALL ONEIDA PRECISION ELECTRONIC COMPONENTS AND ELECTRONIC CHEMICALS ARE AVAILABLE AT YOUR LOCAL DISTRIBUTORS. YOU WILL GET FURTHER WITH ONEIDA QUALITY PRODUCTS.
ALL AMERICAN MADE

Send for free catalog

Name _____
Address _____
City _____ State _____

Oneida

ELECTRONIC MFG. CO.
843 N. COTTAGE ST., MEADVILLE, PA.

New Microphone (46T)

"Big Mike" Mark 1, introduced by **Communications, Inc.**, Wilton, Conn., is primarily for use with CB transceivers or amateur transmitters. It has a built-in transistor amplifier, with adjustable controls for output level and tone. The mike is constructed of anodized aluminum. Power for the amplifier is obtained from a small, long-lasting mercury cell. Net price of the unit is \$29.95.




Antenna Coupler (47T)

A new special auto-antenna coupler has been introduced by **B & K Mfg. Corp.** Designated the CBC-1, the coupler permits the use of a single antenna for both CB and regular AM auto radios. Featuring an extremely low insertion loss — less than .3 db between transceiver and antenna — the coupler is recommended for use with any mobile CB antenna. Net price of the unit is \$8.95.



Clip Leads (48T)

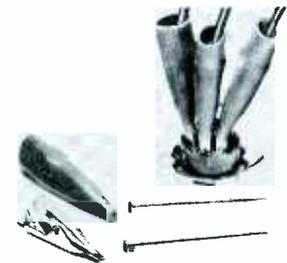The contact end of this tiny clip lead, new from **Mueller Electric**, is no larger than a pin head. The miniature size of this "Micro-gator" makes possible the connection of clip leads to the smallest terminals used in electronic equipment. Clips are available in both steel and copper. Various colored insulators, for use in multiple-lead applications, are also available.




Speaker Horn (49T)

Model IR-9 is a new two-way speaker or paging horn available from **Progress Webster**. The unit can be used with Webster intercom systems, Models W1-60 or W1-65. Especially suitable for areas of high noise level, the unit can be mounted on a wall or ceiling, indoors or out. The adjustable bracket provides directional flexibility. Power output is 7.5 watts. List price is \$24.50.



DC Supply (50T)

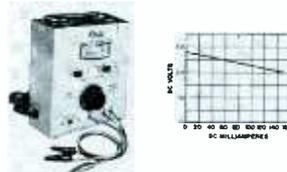The Model EC-3 transistor power supply, introduced by **Electro**, carries a full-year warranty. It has outputs of from 0 to 20 volts (adjustable) and delivers 150 ma at 20 volts. Also included is an adjustable bias tap for voltages of 0 to 6 volts. Sliding a handy switch connects the meter to read voltage or current. The unit, completely wired, sells for \$19.95.



Phonograph Aid (51T)

This new package from **Duo-tone** contains a turntable level indicator and needle cleaning brush. The level is 3" long and comes equipped with a handy pocket clip. The tiny brush may be used to remove dirt and grit from the needle tip. This complete package is available for immediate delivery and carries a suggested list price, for both items, of \$1.49.




Connectors (52T)



A new line of audio connectors—for microphones, tape recorders, amplifiers, and other electronic applications — has been announced by **Switchcraft, Inc.** Four new models are available: A3F, a female cord plug; A3M, a male cord plug; B3M, a panel-mount receptacle; and C3M, a wall-mount receptacle. In addition to three circuit contacts, each connector has a grounding contactor.

Stereo Amplifier (53T)

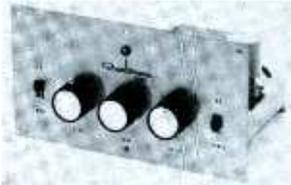

This low-priced stereo amplifier is now available from **Qualitone Industries, Inc.** Designated "Little Giant," this unit can be used for stereo conversion of portable phonographs or as a stereo tape recorder amplifier. Outputs (1½ watts per channel) are for 8-ohm speakers. Inputs to the amplifier can be from either a crystal or ceramic cartridge. This Model 26-01 retails for \$19.95.

Phonograph Accessory (54T)



A new "Disk-Whisk" kit, to clean records while they play, has been introduced by **Robins Industries.** The kit contains a pad and brush which, when attached to the tone arm, cleans the record grooves and deposits an antistatic coating on the record surface to prevent future dust gathering. The special antistatic fluid is included in the kit. List price is \$4.00. Refill kits (fluid and roller) are available for \$2.00.

Tube Tester (55T)



A new self-service tube tester, Model 203-LB, has just been introduced by **Mercury Electronics Corp.** The unit will test all tube types, including nuvistors, novars, compactrons, and new 10-pin tubes. In addition, it has provisions for testing vibrators, batteries, fuses, and pilot lights. New easy-to-read flip-type tube charts for the tester will be made available periodically. The unit is priced at \$254.50.

Recording Tape (56T)




"Scotch" brand 290 is an extra-long-play magnetic tape introduced by **Minnesota Mining and Manufacturing Co.** The tape is available in 600-foot lengths on 3¼" reels. Each reel provides a full hour of recording time on two tracks at 3¾ ips. List price is \$2.95 per reel.

Degaussing Coil (57T)

New from **Stancor** is this DGC-100 "Merchandiser," containing a total of five degaussing coils. Each features a convenient in-line power switch, and rugged construction. Easy-to-use instructions are packed with each unit. Dealer net price for each degaussing coil is \$12.75.

NO
TEST BENCH
IS
COMPLETE
WITHOUT THIS

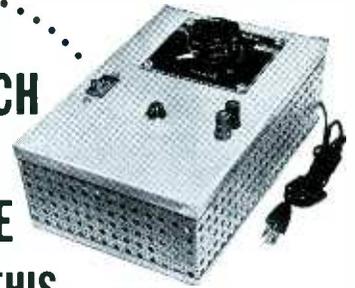

AC TO DC
POWER SUPPLY

Plug this instrument into any 60 cps, 95/130 volt circuit and get a stabilized source of direct current, adjustable over a range from 0 to 45 volts DC, with current output 0/2.5 amperes, or 0-5 amperes. Filtered direct current output range 0/45 volts, current is continuously adjustable and stabilized $\pm 1\%$ at any setting regardless of alternating current fluctuation. Voltage regulation is approximately 5% between full load and no load at full voltage setting.

This DC Power Supply instrument is ideal for use in transistor testing, circuit testing, to provide regulated voltage for light testing, eliminates the need of batteries by supplying exact DC voltage required.

Write for Bulletin 17 which gives full details and models available.

ACME ELECTRIC CORPORATION

9411 WATER STREET

SAA 3581-2032

CUBA, N. Y.

In Canada: Acme Electric Corp. Ltd., 50 Northline Rd., Toronto, Ont.

Acme  Electric

OBSOLESCENCE? none

COST? . . . the lowest

COVERAGE? fits

all popular tuners

ASSEMBLY TIME?

35 seconds



600
KNOBS
IN
ONE!

Available individually or in handy kit for shop or truck.

SEE YOUR JOBBER TODAY

COLMAN ELECTRONIC PRODUCTS, INC.

BOX 2965 ■ AMARILLO, TEXAS

EXPORT
CANADA

Singer Products, 95 Broad St., N.Y.C. 4
Wm. Cohen Ltd., 8900 Park Ave., Montreal

November, 1962

Acme Electric Corp.103
 Admiral Sales Corp. 47
 Aerogap Corporation 63
 Ampere Electric Corp. 15
 ATR Electronics, Inc. 12
 Antronic Corporation 56
 Arco Electronics, Inc. 64
 Astatic Corp., The 62
 Atlas Sound Corp. 86
 B & K Manufacturing Co. 41, 43, 45, 49, 60
 Berns Mfg. Co., Inc. 92, 100
 Broadcast Engineering 96
 Bussmann Mfg. Co. 77
 Cadre Industries 95
 Castle TV-Tuner Service 72
 Centralab, Division of Globe-Union, Inc. 83
 Champion DeArment Tool Co. 48
 Chemical Electronic Engineering, Inc. 74
 Chem Spray Corp. 56
 Colman Electronic Products 103
 Cornell-Dubilier Electric Corp. 57
 Delco Radio Division (GMC) 59
 DeSod Div. of Eversole Industries 82
 DuMont Labs, Allen B. 76
 Duetone Co., Inc. 86
 EICO Electronic Inst. Co. 93
 Electronics, Missiles & Communications 91
 Electronic Publishing Co., Inc. 86
 Electro Products Labs 101
 Electro-Voice, Inc. 91
 GC Electronics Co. 97
 General Electric Co.,
 Receiving Tube Dept. 54, 55
 Gernsback Library 81
 Heath Company 69
 Hickok Electrical Instrument Co. 53
 Injectorall Co. 98
 Jackson Electrical Instrument Co. 91, 104
 Los Angeles Tuner Exchange 48
 Littelfuse, Inc. 4th cover
 Luxo Lamp Corp. 102
 Mallory & Co., Inc., P. R. 51
 Mercury Electronics Corp. 85
 Merit Coil & Transformer Corp. 87
 Motorola Training Institute 94
 Multicore Sales Corp.
 Div. British Industries 92
 Nortronics Co., Inc., The 90
 Ohmite Mfg. Co. 74
 Oneida Electronic Mfg., Co. 102
 Pel Electronics 82
 Precision Apparatus Co 66, 67
 Perma-Power Co. 68
 Planet Sales Corp. 82
 Precision Tuner Service 76
 Quam-Nichols Co. 71
 R-Columbia Products Co. 58
 RCA Electron Tube Div. 3rd Cover, 22-23
 (Electronic Inst. Section) 73
 RCA Communications and
 Industrial Electronic Products 39, 88
 RCA Sales Corporation 16-17
 RCA Parts & Accessories Division 65
 Rider, John F., Publisher 58
 Sams & Co., Inc., Howard W. 75, 84
 Sarkes Tarzian, Inc. (Tuner Service) 13
 Seco Electronics, Inc. 89
 SENCORE, Inc. 25-28
 Sonotone Corp. 44
 Sprague Products Co. 10
 Standard Kollsman Industries, Inc. 9
 Swing-O-Lite, Inc. 88
 Sylvania Electric Products, Inc.
 (Electronic Tubes) 18-19
 Technical Appliance Corp. 2nd Cover
 Techni-Parts Corp. 92
 Terado Company 98
 Tung-Sol Electric Inc. 61
 Utah Electronics Corp. 80
 Vidaire Electronics Mfg. Corp. 100
 V-M Corp. 20
 Volkswagen of America 21
 Weller Electric Corp. 79
 Winegard Co. 14, 46
 Workman Electronic Products Inc. 94



MODEL 648										MODEL 598									
Tube Type	Pin	D	E	Plate	Y	A	B	C	Case	D	E	F	G	H	I	J	K	L	M
1AD9P	1-4																		
6A6L	4-3	A330	A234	4132	4-3	4V				7	3	42	47						
A334		A17	297																
6A6R	4-3	A128	479	4782	4-3	4V				3	9	7	82						
A128		A128	479	4782															
A311P	4-3	A378	C14*	495V															
A389		C14*	495V																
2280P	23	134	S	14W															

SUPPLEMENT LATEST ROLL CHART 448-24
 SUPPLEMENT LATEST ROLL CHART 282

MODEL 658									
Tube Type	Sec.	Model	H-D	P-D	Plate	Grid	Screen	Control	Current
1AD9P	D	1-37			3	3TU	VX		
6A6L	T	6-4K	218	4454	110	18XV			
A128	T	214	417	178	80V				
6A6R	T	6-4K	138	479	240	20VY			
A128	T	214	417	178	80V				
A311P	P	6-4J	876	1546	408	18VY			
A389	P	6-4J	876	1546	408	18VY			
2280P	D	22-24	134	Z	11W	Y			A35-K 2450

SUPPLEMENT LATEST ROLL CHART 658

ANTENNAS & ACCESSORIES

- 1T. JERROLD ELECTRONICS — Brochure describing how Jerrold's TX-FM coupler utilizes a TV antenna to provide FM signal to FM tuners.
 2T. JFD — Brochures on LPV log periodic TV antenna, FM stereo antenna; also catalog showing complete line of TV/FM indoor and outdoor antennas and antenna accessories.
 3T. TACO — Sheet giving specifications and performance information on Taco's T-Bird Electra antenna. See ad 2nd cover.

AUDIO & HI-FI

- 4T. ATLAS SOUND — Catalog No. 562 listing specifications on microphones and loudspeakers for public address, commercial, and industrial use. See ad page 86.
 5T. EICO — New 32-page catalog of kits and wired equipment for stereo and monophonic hi-fi, test equipment, Citizens-band transceivers, ham gear, and transistor radios. Also "Stereo Hi-Fi Guide" and "Short Course for Novice License." See ad page 93.
 6T. QUAM-NICHOLS — Catalog sheet listing specifications and prices on complete line of wall baffles. See ad page 71.

COMMUNICATIONS

- 7T. CADRE — 16-page booklet "Businessman's Guide to Citizens Band Two-Way Radio." See ad page 95.
 8T. COMMUNICATIONS COMPANY, INC. — Descriptive literature on VHF and UHF two-way radio communications equipment for airport vehicles and towers.
 9T. E. F. JOHNSON CO — Brochures describing complete CB equipment line, new Messenger "202" transceiver, and specifications on selective-calling system for CB equipment.
 10T. MIRATEL ELECTRONICS — Brochures containing information on Citizens-band equipment and CB Club membership.

COMPONENTS

- 11T. ADMIRAL (SALES DIVISION) — 1963 catalog listing parts and accessories, service and business aids, complete cross-reference on needles and cartridges, and complete antenna line.
 12T. BUSSMANN — Bulletin SFH-8 giving information on new GMW-HWA subminiature fuse-and-holder combination for use on panels or printed-circuit boards. See ad page 77.
 13T. CENTRALAB — Catalog No. 220, handy 6" x 9" 20-page catalog listing price and other information on more than 1,815 controls, switches, ceramic capacitors, and other electronic components. See ad page 83.
 14T. LITTELFUSE — Illustrated dealer-serviceman fuse and holder catalog (No. L-562) showing prices and specifications. See ad 4th cover.
 15T. SONOTONE — Sheet listing new dry-cell batteries for use with transistor radios, flashlights, photo units, and toys. Specification sheet No. SAH-58. See ad page 44.
 16T. SPRAGUE — Chart C-457 (designed to hang on wall) showing all popular TV-radio-hi-fi replacement components. See ad page 10.

SERVICE AIDS

- 17T. CASTLE — Leaflet describing fast overhaul service on television tuners of all makes and models; also illustrated lists describing universal and original-equipment tuners. See ad page 72.
 18T. ELECTRONIC CHEMICAL CORP. — Catalog and brochure listing electronic chemical line, including new formula EC-44 for lubricating and cleaning electrical contacts.
 19T. MINNEAPOLIS SPEAKER CO. — Brochure describing new "Mini-Speaker" specifications and applications.
 20T. PRECISION TUNER — Information on repair and alignment service available for any TV tuner. See ad page 76.
 21T. SWING-O-LITE INC. — Two brochures listing information on "The Inspector" and "Hi-Mag" lamps for servicing or office use. See ad page 88.

SPECIAL EQUIPMENT & SERVICES

- 22T. ACME — Illustrated catalog sheet 24-B01 giving specifications and listing applications for magnetic amplifiers de-

signed for control uses; includes units with capacities from 5 to 1000 watts and voltage ranges from 24 to 160 volts. See ad page 103.

- 23T. CINE-SONIC SOUND, INC. — Sheet listing cartridge tape repeaters for background music. Catalog of tape cartridges from the Largest Library of Music.
 24T. R-COLUMBIA PRODUCTS CO. INC. — Brochures No. 61 and 62, describing 7-oz dynamic headphones for language laboratories and stereo listening. See ad page 58.
 25T. TERADO CORP. — Catalog sheet 5978 showing Dual Continental and Continental inverters. See ad page 98.
 26T. TRANSVISION ELECTRONICS — 12-page catalog listing black-and-white TV kits and wired chassis for custom installation; also catalog of color-TV kits.
 27T. VOLKSWAGEN — 60-page illustrated booklet, "The Owner's Viewpoint," describing how various business enterprises use VW trucks in their operations; also booklet giving complete specifications on VW truck line. See ad page 21.

TECHNICAL PUBLICATIONS

- 28T. HOWARD W. SAMS — Literature describing all current publications on radio, TV, communications, audio and hi-fi, and industrial electronics, including brand-new Fall-Winter 1962 Book Catalog and descriptive flyer on 1962 Test Equipment Annual. See ads pages 75, 84.

TEST EQUIPMENT

- 29T. B & K — Catalog AP20-R, giving data and information on Model 850 Color Analyst, Model 960 Transistor Radio Analyst, Model 1076 Television Analyst, Dynamatic 375 VTVM, V O Matic 360, new Model 625 3-in-1 Dyna-Tester, Models 600 and 700 Dyna-Quik tube testers, Models 440 and 420 CRT Tester-Reactivators, and Model 1070 Dyna-Sweep Circuit Analyzer. See ads pages 41, 43, 45, 49 and 60.
 30T. HICKOK — Four-page brochure describing new Hickok Model 661 Chrom-Aligner NTSC Standard Color Bar Generator. See ad page 53.
 31T. MERCURY — Literature describing regular and self-service tube testers, component substitutor, CRT tester, and other service equipment. See ad page 85.
 32T. PRECISION — 7" x 10" two-color catalog containing specifications and prices of their complete test equipment line. See ads pages 66-67.
 33T. RCA — Pocket catalog covering complete line of test equipment; includes all color-TV instruments. See ad page 73.
 34T. SECO — Brochure describing new transistorized power supply, designed for high-powered transistorized equipment. See ad page 89.
 35T. SENCORE — Complete literature on the CA-122 color circuit analyzer and the PS-120 wide-band scope. See ads pages 25-28.
 36T. TRIPLETT — Catalog No. 44-T containing specifications of new test equipment.

TOOLS

- 37T. BERNs — Data on 3-in-1 picture-tube repair tools, on Audio Pin-Plug Crimper that lets you make pin-plug and ground connections for shielded cable without soldering, and on ION adjustable beam bender. See ads pages 92, 100.
 38T. ENTERPRISE DEVELOPMENT CORP. — Literature from Endeco on improved desoldering and resoldering techniques for use on PC boards.
 39T. ONEIDA ELECTRONIC MFG. CO. — Three brochures describing service chemicals, soldering-gun attachments, high-voltage caps (for color TV's) and other hard-to-find servicing accessories. See ad page 102.
 40T. UNGAR — Eight page, fully illustrated four-color catalog describing "Imperial" soldering iron and complete line of interchangeable Imperial components.

TUBES & TRANSISTORS

- 41T. AMPEREX — 16-page semiconductor handbook and 34-page tube reference book. See ad page 15.

COME PREPARED

to Every
Service Job



Tools and tubes are your bread and butter on home service calls. That's why, in addition to the finest electron tubes, RCA also provides you with special service-designed tool chests and tube caddies to increase your efficiency on every call. These valuable service aids...

- Save your time
- Simplify your job
- Organize your work
- Help you find the tool or tube you need readily and quickly
- Help assure that you have what you need when you need it—with nothing inadvertently left behind in the shop.

**ANOTHER WAY RCA HELPS
YOU IN YOUR BUSINESS.**

RCA ELECTRON TUBE DIVISION, HARRISON, N. J.


Ask your Authorized RCA Tube Distributor about obtaining these valuable service aids designed especially for your convenience.



NEW SERVICE-SPECIAL TOOL CHEST
(1A1280) Ample room for all basic tools, with a special compartment to hold your RCA WV-38A V-O-M or RCA Power Line Monitor.



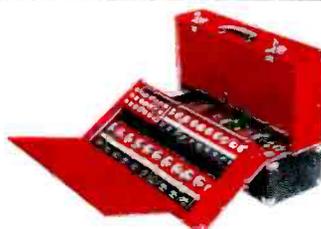RCA "QUICK CALL" TUBE CADDY
(1A1002) A handy tube caddy that holds 162 of the tube types you use most frequently on TV service calls.



RCA "TREASURE CHEST" TUBE CADDY
(1A1001) RCA's famous full-size caddy—holds over 260 receiving tubes.



RCA LITEWEIGHT TUBE CADDY
(1A1241) This lightweight, compact caddy holds up to 210 receiving tubes. Custom molded of plastic, its finish resists marring and staining, cleans with soap and water.



The Most Trusted Name in Electronics

www.americanradiohistory.com

In Electronic Circuits . . .

ALL AROUND PROTECTION

NEW MICROFUSE
 THE PIGTAIL VARIETY (278000) SERIES
 THE PLUG-IN VARIETY (272000) SERIES
 THE SUB-MINIATURE FUSE HOLDER (No. 281001)

New Indicating 3AG Fuse Posts

It GLOWS when the FUSE BLOWS

Labels around the circle:
 THROUGH PANEL MOUNTING, SCREW TERMINAL MOUNTING, SOLDER TERMINAL MOUNTING, 4AG FINGER OPERATED POST, TERMINAL CLIP, FUSE CLIP EARLESS, FUSE CLIP, LC FUSE HOLDERS, MOUNTINGS FOR RECTIFIERS, 3AG FUSES, 3AG SLO-BLO, 3AG MINI U/L, LC FUSES 25V TYPE C, LC FUSES 125V TYPE C, LC SLO-BLO 125V TYPE N, 8AG INSTRUMENT FUSES, 8AG U/L FUSES, AIRCRAFT FUSES, 4AG SLO-BLO, IN LINE FUSE RETAINERS, 3AG POST SCREWDRIVER OPERATED, 3AG POST FINGER OPERATED, 3AG POST MINIATURE, CAN COVER MOUNTING, THROUGH PANEL MOUNTING.

It's **LITTELFUSE** First!
 DES PLAINES, ILLINOIS