

# PF Reporter™

PHOTOFACT

*the magazine of electronic servicing*



1 A 3D 2036 265  
 SAMUEL SACHS  
 2244 NORTH 10TH ST.  
 PHILADELPHIA 33, PA.

- Find Profit in Small Tape Recorders
- Servicing Stereo Adapters
- The Knack of Filter Replacement
- Royal Road to Transistor Servicing
- Plus many more





## How to replace top quality tubes with identical top quality tubes

Most of the quality TV sets you are presently servicing were designed around special Frame Grid tubes originated by Amperex. More and more tube types originated by Amperex are going into the sets you'll be handling in the future.

Amperex Frame Grid tubes provide 55% higher gain-bandwidth, simplify TV circuitry and speed up your servicing because their extraordinary uniformity virtually eliminates need for realignment when you replace tubes.

Amperex Frame Grid Tubes currently used by the major TV set makers include:

2ER5	2GK5	2HA5	3EH7	3GK5	3HA5	4EH7	4EJ7	4ES8	4GK5	4HA5	5GJ7
	6EH7	6EJ7	6ER5	6ES8	6FY5	6GJ7	6GK5	6HA5	6HG8	7HG8	8GJ7

If your distributor does not yet have all the Amperex types you need, please be patient—in some areas the demand keeps gaining on the supply. Amperex Electronic Corporation, Hicksville, Long Island, New York 11802.



*Circle 1 on literature card*

# 1964

# SUBJECT REFERENCE INDEX

To increase the usefulness of this year's Subject Reference Index, we have expanded the code of symbols as follows to identify regular department locations in the subject page listings: CCM, Color Countermeasures; CS Communications Supplement; Sym, *Symfact*; Sym Jr, *Symfact Jr.*; TE, Notes on Test Equipment; TS, The Troubleshooter; and VSS, Video Speed Servicing.

- AFC**  
Horizontal  
—diode type  
  (Panasonic Mitey 5) ....Sym Sep 23  
—synchroguide .....Apr 32  
—synchroguide  
  (RCA KCS102B) .....Sym Jul 25  
—transistor circuits .....Jun 3
- RF**  
—defeat switch .....Feb 72  
—FM servicing chart .....Feb 74
- AGC**  
Checking with VTVM .....Mar 29  
Control voltage in IF .....TS Mar 16  
Delay resistor changes value .....Jan 54  
Flutter (Philco Chassis 444) ..TS Oct 54  
Intermittent component in .....Jan 52  
Keyed type .....Sep 28  
Limitations of .....Sep 28  
Peak type .....Sep 91  
Picture symptoms of  
  (Panasonic Mitey 5) ....Sym Jun 29  
Simple circuits .....Sep 29  
Transistor circuits .....Jun 7
- ALIGNMENT**  
AM radio .....Jul 58  
Color accessories for .....Aug 44  
Receiver, communications .....Apr 7  
Transmitter, Communications .....Apr 4  
TV-FM .....Jul 58  
Two-way radio .....Apr 1
- ANTENNAS**  
Amplifiers for .....Aug 23  
Communications types .....Jul 12  
  —guide to .....CS Apr 76  
Conductor separation .....Aug 39  
Couplers for .....Aug 32  
Distribution systems .....Aug 33  
Dummy-type .....Feb 54  
Equipment approval .....Aug 39  
Grounding practices .....Aug 39  
Indoor types  
  —TV and FM .....Aug 74  
  —UHF .....Oct 74  
Lead-in wire for .....Feb 20  
Lightning arrestors .....Aug 39  
Light-weight communications  
  type .....Jul 62  
Log-periodic type .....Aug 73  
Master system operations .....Aug 30  
Mobile types  
  —communications .....Sep 98  
  —omnidirectional .....Feb 79  
  —UHF .....Aug 75  
Mobile-home type .....May 95  
National Electrical Code,  
  as covered in .....Aug 39  
Rotor-booster .....May 94  
Safety .....Aug 39  
  —during installation .....Sep 56  
Sales techniques .....Aug 56  
SWR meter .....Feb 54  
SWR in two-way .....Mar 40  
SWR-versus-power chart .....Mar 44  
Tangent-paraboloid reflector  
  for UHF .....Oct 75  
UHF types .....Jan 62  
  —log-periodic .....Apr 69  
  —TV .....Apr 71
- AUDIO SYSTEMS**  
Booster amplifier for .....Aug 73  
Custom stereo types .....May 56  
Distortion in .....Sep 38  
Hum in .....May 62  
IM distortion in .....Mar 80  
Jacks, compact audio .....Jun 78  
Light-weight speakers for .....May 95  
Microphone-headset  
  combination for .....May 94  
Speaker installation in .....May 56  
Speaker phasing in .....May 60  
Transformer, extension speaker ..Apr 69  
Unitary speakers for .....May 88
- AUTOMATIC BRIGHTNESS CONTROL**  
DuMont Chassis 120692  
  —control ineffective .....Sym Feb 26  
  —picture defocused .....Sym Feb 26  
  —picture dull .....Sym Feb 28  
Magnavox .....Aug 1
- AUTO RADIOS**  
Audio output low (Chevrolet  
  Model 987727) .....TS Jun 18  
Buzzing in audio  
  (Ford Model 94BF) .....TS Jun 19  
Duplicating operating conditions  
  in servicing  
  —vibration .....Oct 42  
  —voltage variation .....Oct 42  
  —temperature variation .....Oct 44  
FM-AM transistor type,  
  intermittent .....TS Feb 18  
Fusible resistor in output stage ..Oct 14  
Portable transistorized  
  combination .....Nov 117  
Power supply in .....Apr 62  
Rear seat speakers for  
  —Delco car radio  
  Model 982136 .....TS Sep 21  
  —installation, general .....Aug 68  
Reverberation systems for .....Aug 73  
  .....Nov 116  
Specialization in servicing of .....Apr 34  
Stereo adapter for .....Nov 15  
Transistor truck type .....Jun 78  
Volume fades in (Chevrolet  
  Model 985432) .....TS Oct 21
- BATTERIES**  
Converter/charger .....Aug 64  
Eliminator for VTVM .....Jul 60  
Measuring voltages in mobiles .....Mar 44  
Rechargeable type .....Apr 69  
Transistorized inverter using .....Sep 99  
Transistor radios, for .....Jun 79
- BOOK REVIEWS**  
*Communication Satellites* .....Sep 47  
*Color TV Troubleshooting*  
  *Pict-O-Guide* .....Nov 117  
*Handbook of Electronic Tables*  
  & *Formulas, 2nd Ed.* .....Oct 78  
*Mathematics for Electronics*  
  and *Electricity* .....Dec 44  
*Two-Way Mobile Radio*  
  *Handbook* .....Oct 66
- BOOST**  
Blooming and HV loss .....May 36  
Checking procedure .....May 82  
Voltage absent, no raster (RCA  
  Chassis KCS137A) .....VSS Mar 5
- Voltage low, no raster (Admiral  
  Chassis 18B7) .....VSS Sep 5  
Weak voltage .....May 36
- BUSINESS**  
Audio servicing considerations ...Sep 72  
Callbacks, dealing with .....Dec 48  
Choosing new lines .....Jun 44  
Color questions and answers ....Nov 66  
Demonstrations, use of in sales ..Aug 61  
Employee theft .....Jul 42  
Expenses .....Apr 50  
Importers, guide to .....Jun 38  
Insurance .....Jan 68  
  .....Oct 52  
Management for profit .....Apr 48  
Modern methods .....Jan 44  
National Electrical Code .....Aug 39  
Office .....Jan 3  
Parts depot (Sylvania) .....Jun 16  
Phone conversations,  
  recording of .....Jun 14  
PL statement, sample .....Apr 48  
Promotion, sales .....Aug 61  
Protection against fraud .....May 66  
Radio amateurs, relations with ...Sep 78  
Records, analyzing .....Feb 46  
Salaries .....Apr 54  
Sales  
  —area facilities .....Jan 2  
  —breakdown charts ...Feb 48, 50, 52  
  —cost of .....Apr 48  
  —gross chart .....Feb 46  
Specialization .....Apr 34  
Tax deduction and  
  depreciation .....Oct 50  
Techniques for selling antennas ..Aug 56  
Test equipment, advantage  
  of quality .....Mar 50  
Transistor servicing .....Jun 32  
Transistors versus tubes .....Jun 70
- CAPACITORS**  
Facts about .....Apr 36  
Intermittent shorts or opens,  
  value changes .....Jan 50  
Metalized-paper type .....Apr 36  
Mica type .....Apr 37  
Multiplier designations .....Dec 13  
Paper-tubular type .....Apr 36  
Plastic-film type .....Apr 37  
Polarization of .....TS Aug 19  
Principles of electrolytics .....Feb 38  
Replacement of .....Dec 52  
Silvered mica .....Apr 37  
Substituter .....Feb 58  
Testing of filter types .....Feb 42  
Tubular bypass type .....Aug 75
- CAPACITOR TESTERS**  
Bridge, comparator .....Mar 92  
Cornell-Dubilier BF-71A  
  Analyzer .....TE Oct 58  
Decade .....Mar 86  
In-circuit tester .....Feb 44
- CARTRIDGES (PHONO)**  
Ceramic retractable .....Aug 74  
Snap-in replacement .....Nov 116  
Stereo ceramic .....Sep 99
- CHEMICALS**  
Aerosols .....Jul 36  
Plastic repair compound .....May 54  
Precautions in using .....Jul 38

**CITIZENS BAND**

Capital ND-309 transceiver	TS Mar 16
Class A stations	CS Apr 101
Class B stations	CS Apr 101
Class C stations	CS Apr 102
Frequency meter for	Apr 70
Frequency-synthesized transceiver	Jul 63
Industrial communications in	CS Apr 98
Industrial sales	CS Apr 104
Radiotelephones	Apr 69
—transistorized	Jul 63
Selective calling	CS Jul 74
Single-sideband transceiver	May 92
Station classes and channels	CS Apr 98
Transceivers	Oct 75
—AC or battery-operated	May 94
—modular	Jun 79
Transmitter and antenna tester	Feb 54

**COILS**

Measurements of low-Q types	Dec 32
Oscillator, TV	Jul 12

**COLOR COUNTERMEASURES**

Picture tube difficulties	CCM Nov 70
Zenith Chassis 25LC20, 25LC30 and 25MC30	
—Convergence, lack of CCM	Dec 64
Zenith Chassis 25LC20, 25LC 30 and 25MC30	
—impurity at outer edge of raster	CCM Nov 76
Zenith Chassis 25LC20, 25LC30, and 25MC30	
—S-hook or bend at top of raster	CCM Nov 74
Zenith Chassis 25LC20, 25LC30, 25MC30, 25MC33, and 26KC20	
—circuit breaker kicks out	CCM Nov 70
Zenith Chassis 25LC20, 26KC20, 27KC20, and 29JC20	
—purity errors and lack of convergence control	CCM Nov 72
Zenith Chassis 25LC20, 25LC30, 25MC30, 26KC20, and 29JC20	
—vertical sync poor	CCM Nov 74
Zenith Chassis 25LC20, 25LC30, 25MC30, 25MC33, 26KC20, and 29JC20	
—erratic CRT bias, misregistration of black and white	CCM Nov 72
Zenith Chassis 25LC20, 25LC30, 25MC30, 25MC33, 26KC20, 27KC20, and 29JC20	
—no high voltage, tubes check OK	CCM Nov 76

**COLOR GENERATORS**

B & K Model 1074 TV Analyst	TE Sep 82
Bar and dot type	May 70
Checking phase of	Nov 32
Heath Model IG-62	May 70
Hints for using	May 52
NTSC single bar type	Jul 12
Portable type	Nov 115
"Vectorscope" type	Oct 77

**COLOR TV**

Alignment accessories	Aug 44
Analyzer	Jun 78
Bar-dot generator	Jan 30
	May 70
Blue inoperative	May 46
Brightness low (Admiral Chassis 24F2)	Mar 68
Chassis or CRT troubles, how to distinguish between	Feb 36
Chroma alignment	
—AFPC circuits	Nov 38
—bench procedures	Nov 109
—procedures in the home	Nov 39
Chroma bandpass amplifier, single stage (Bradford Model	

WGEC-89946A) .....Sym Nov 27

Chroma reference and control circuits	
—phase detector	Nov 48
—reactance tube	Nov 50
—reference oscillator	Nov 52
Circuits for 1965	
—chroma bandpass stages	Nov 6
—color sync stages	Nov 6
—demodulator	Nov 7
—horizontal sweep & high voltage	Nov 7
—luminance channels	Nov 3
—power supply	Nov 8
Color-bar hints	May 52
Convergence	Sep 32
—lack of (Zenith)	CCM Dec 64
CRT tester-rejuvenator	TE Nov 96
Dot-bar generator	Mar 76
Green picture	May 46
Instruments for tough-dogs	Mar 68
Luminance channels	
—3-stage	Nov 41
—2-stage	Nov 103
Mercury Model 900 Color TV Analyzer	Dec 60
Phase and saturation	May 46
Raster, blinking	Mar 72
Registration poor (RCA)	May 52
Sales	Aug 56
Saturation and phase	May 46
Signal tracing	
—IF signals	Nov 36
—RF-IF overloading	Nov 36
—video detector output	Nov 36
—Y amplifier output	Nov 37
Ten Years of Color/a Report	Nov 99
Test equipment, for	Jan 30
	Nov 84
—CRT checkers	Nov 90
—oscilloscopes	Nov 93
—signal generators	Nov 90
Vertical arcing	Nov 58
White compression	Feb 36
<b>COMMUNICATIONS</b>	
Aircraft radio	Sep 34
	Dec 34
Alignment	
—generator	May 90
—techniques	Apr 1
Antennas	CS Apr 76
Aviation frequency assignment	Sep 96
Base-station microphone	Jul 63
CB transceiver, modular	Jun 79
Clipper, transistorized	CS Apr 92
Delay line	CS Jul 70
Direction finder, automatic	Dec 34
FM modulator operation	CS Jul 68
Frequency	
—adjustment	Apr 7
—meter, CB	Apr 70
—synthesis	CS Apr 86
Front end alignment	Apr 7
HF	
—aircraft radio	Sep 34
—transceivers	Nov 115
Industrial	
—CB applications	CS Apr 98
—radiotelephones	May 90
Instrument landing system	Dec 65
Light-weight fiberglass-encased antenna	Jul 62
Limiters, modulation	CS Apr 92
Low IF alignment	Apr 7
Midget transmitter	Dec 71
Mobile-base-portable, combination	Jul 60
Modulation	
—checks	Apr 4
—limiter action	CS Apr 92
—types of	CS Jul 68
Modulator, semiconductor junction	CS Jul 70
Multiplier alignment	Apr 5

Oscillator peaking	Apr 4
Over-modulation, preventing	CS Jul 68
PA alignment	Apr 5
Phase modulator	CS Jul 69
—transistorized	CS Jul 70
RF stage alignment	CS Apr 78
Radio paging	CS Jul 72
Radiotelephones	Apr 69
—marine	Jul 62
Receiver alignment	Apr 7
Selective calling	CS Jul 74
Single-sideband CB unit	May 92
Speech amplifier, transistorized	CS Jul 70
Test equipment for	Apr 1
Tone signal device, automatic	Nov 119
Tower maintenance	CS Oct 86
Transistorized microphones	CS Jul 66
Transmitter alignment	Apr 4
Transmitter and antenna tester	Feb 54
VHF	
—aircraft radio	Sep 35
—FM radios	Apr 70
—Omnirange receivers	Dec 34
—reception distances, aircraft radio	Sep 97

**DIODES**

AFC, FM	Feb 34
---------	--------

**FACILITIES**

Future shops	Jan 36
Modernization	Jan 44
Offices	Jan 3
Sales area	Jan 2
Service shop layout	Jan 1

**FILAMENT CIRCUITS**

Voltage low	
—RCA CTC11 (color)	TS Apr 22

**FM RADIO****AFC**

—defeat switch	Feb 72
—semiconductor diode	Feb 34
—servicing chart	Feb 74

Automatic multiplex tuner .....Jan 75

Stereo generator, for modern bench .....Jan 72

Stereo receiver .....Feb 78

Transistor, auto

—intermittent .....TS Feb 18

Tuning eyes .....May 32

**FUSES**

Circuit-breakers	Aug 75
Holder, miniature	Sep 99

Indicating type .....Jan 78

Miniature type .....May 93

Resistor, fusible (Philco Model UJ3702L) .....TS Jul 20

Importers .....Jun 38

Radio and Hi-Fi tubes, of .....Dec 20

Specifications of 1965 TV receivers .....Oct 2

Stock, TV tubes .....May 78

Test equipment

—accessories .....Jan 20

—specialized .....Oct 38

Wire and cable .....Feb 20

**HI-FI SYSTEMS**

Custom stereo type .....May 56

FM stereo receiver for .....Feb 78

Hum in .....May 62

Jacks, compact audio .....Jun 78

Matching equipment for .....May 62

New York Show report .....Dec 40

Old cabinets, using .....Oct 34

Speakers for

—installation .....May 56

—phasing .....May 60

Stereo conversions .....Oct 35

Transistorized stereo .....Oct 74

Unitary speakers .....May 88

**HIGH VOLTAGE**

Color circuits, 1965 .....Nov 7

Transistor circuits .....Jun 2

<b>HORIZONTAL OSCILLATOR</b>	Rolling, vertical not effected (RCA Chassis KCS102B) .....	Sym Jul 28	servicing .....	Aug 34
AFC and oscillator, isolation servicing procedure .....	Separator, single triode Wells-Gardner Chassis S37) .....	Sym Mar 23	Electronics at the World's Fair .....	Jul 1
Drifts during operation, caused by leaky coupling capacitor at output (Silver-tone Chassis 456.51800) .....	Sync unstable, caused by boost trouble .....	May 36	Electronics sliderule .....	Nov 115
Frequency incorrect (Panasonic Mitey 5) —high voltage low .....	Synchroguide .....	Apr 32	Magnifier .....	May 95
—unstable when synced with AFC control .....	Sync lost, width not effected (RCA Chassis KCS102B) .....	Sym Jul 26	New York Hi-Fi Show report .....	Dec 40
Multivibrator troubles (RCA Chassis KCS72) .....	Tearing —Silver-tone Chassis 456.51800 .....	VSS Mar 8	Radio amateurs aren't so bad .....	Sep 78
Sync inoperative, hold control has no effect (RCA Chassis KCS 72) .....	—vertical rolling (TraVler Chassis 23K6180F) .....	VSS May 8	WWV changes .....	Jun 16
Synchroguide AFC .....	Unstable, phasing bar in picture (Panasonic Mitey 5) .....	Sym Sep 24	<b>MULTIPLEX</b>	
Transistor circuits .....	<b>HUM</b>		Composite stereo signal .....	Dec 44
—Panasonic Mitey 5 .....	Audio system, in .....	May 62	Generator, stereo .....	Mar 94
<b>HORIZONTAL SWEEP</b>	Electronic musical instruments, in .....	Aug 72	Sencore Model MX 129 generator and analyzer .....	TE Aug 66
Bending, reduced video (Panasonic Model Mitey 5) .....	<b>IF SECTION OF TV</b>		Servicing adapters .....	Dec 42
Color circuits, 1965 .....	AGC control voltage .....	TS Mar 16	Stereo indicator .....	Dec 47
Components in, checking .....	Alignment of .....	Mar 64	Zenith Model SPTE-1 Multiplex generator .....	Jun 66
Drive lines .....	B+ in color circuit, stacked .....	TS Mar 16	<b>NOTES ON TEST EQUIPMENT</b>	
Insufficient width (Magnavox Chassis V38-01-00) .....	Transistor circuits .....	Jun 6	B & K Model 445 picture tube rejuvenator-tester .....	Apr 58
Intermittent loss of raster (Zenith Chassis 16V25,Q,U) .....	<b>INDUSTRIAL ELECTRONICS</b>		B & K Model 1074 TV analyst .....	TE Sep 82
Output current high (Spartan Chassis 23V5-2) .....	Darkroom equipment .....	Jan 32	Cornell-Dubilier Portapower Model 12PP14 power converter .....	Aug 64
Picture narrow with foldover, loss of sync (RCA Chassis KCS102B) .....	Electrostatic air cleaners .....	Aug 46	Cornell-Dubilier BF-71A Analyzer .....	TE Oct 58
Pulling, top of raster affected (Panasonic Mitey 5) .....	Radiotelephones .....	May 90	Delco Radio Model T-612 power supply .....	Apr 62
Screen resistor, changed value .....	Semiconductor applications .....	Jun 56	EICO 430 3" scope .....	Jul 46
Tearing —control critical (Admiral PL17F31B) .....	Solid-state rectifiers .....	Sep 36	EICO 667 dynamic conductance tube and transistor tester .....	Dec 59
—Coronado 515 .....	Thyratron circuits .....	Jan 32	EICO Model 902 distortion meter .....	Mar 80
Tearing and streaking, clicks in sound, caused by arcing transformer (Zenith Chassis 16V25,Q,U) .....	<b>INTERCOMS</b>		Electronic Measurement Corp. Model 501 AM signal generator .....	Apr 58
Transistor circuits .....	Remote amplifiers as .....	Jan 66	Electronics Communications, Inc. Port-A-Lab transmitter and antenna tester .....	Feb 54
Vertical bars, caused by radiation (RCA Chassis KCS72) .....	Scoping oscillators in .....	Dec 38	G-C Electronics 36-540 tube tester .....	May 70
Width decreased, sync OK (RCA Chassis KCS102B) .....	Wireless type .....	Jan 76	G-C Electronics 36-616 CRT tester-rejuvenator .....	TE Nov 96
Width decreases with time (RCA Chassis KCS137A) .....	<b>INTERFERENCE</b>		Heath Model IG-62 color bar and dot generator .....	May 70
Width & horizontal linearity .....	Hold critical, horizontal not affected .....	Sym Apr 30	Heath Model IT-12 signal tracer .....	Jul 48
Width reduced (Magnavox Chassis V38-01-00) .....	TV, cause, effect, cure .....	Mar 12	Hickok Model 470A VTVM .....	TE Oct 60
<b>HORIZONTAL SYNC</b>	<b>INTERMITTENT TROUBLES</b>		Hickok Model 209B VTVM .....	Aug 64
Absent, no hold control (RCA Chassis KCS137A) .....	Auto radio, transistor FM-AM .....	TS Feb 18	Jackson Model 805 VTVM .....	May 74
Bending, intermittent loss of sync (RCA Chassis KCS102B) .....	Capacitors .....	Jan 50	Mercury Model 301 tube tester/VOM .....	Jul 52
Flutter, frequency control critical (RCA Chassis KCS102B) .....	Horizontal tearing (Admiral PL17F31B) .....	TS May 21	Mercury Model 501, component substitutor .....	Feb 58
Frequency —drifts (Admiral Chassis 18B7) .....	Loss of horizontal sync (RCA Chassis KCS102B) .....	Sym Jul 28	Mercury Model 900 color TV analyzer .....	Dec 60
—out of range (TraVler Chassis 23K6180F) .....	Pull in picture, buzz in sound (Philco Chassis 12N51) .....	VSS May 5	RCA WR-50A signal generator .....	Jun 68
Hold (Airline Chassis WG-5218A) —erratic .....	Sound with occasional buzz (Zenith Chassis 16V25,Q,U) .....	VSS Aug 8	RCA WV-76A VTVM .....	Dec 62
—poor, vertical roll .....	Television receivers, in .....	Jan 50	Seco Model RPS 5 regulated power supplies .....	TE Sep 85
Inoperative (RCA Chassis KCS82) .....	Vertical symptoms —distortion (Muntz Chassis T37) .....	Sym Jan 27	SENCORE CG 126 color generator .....	Mar 76
Loss of (Magnavox Chassis V38-01-00) .....	—jitter (Muntz Chassis T37) .....	Sym Jan 28	SENCORE Model MX129 FM multiplex generator and analyzer .....	TE Aug 66
Pulling in raster —Wells-Gardner Chassis S37 .....	—roll —Panasonic Mitey 5 .....	Sym Jun 29	Standard-Kollsman VHF to UHF translator .....	TE Oct 61
—vertical jitter (Sylvania Chassis 571-1) .....	—Sylvania Chassis 571-1 .....	Sym Apr 29	Zenith Model SPTE-1 multiplex generator .....	Jun 66
	—Wells-Gardner Chassis S37 .....	Sym Mar 24	<b>OSCILLOSCOPES</b>	
	Volume varies .....	TS Apr 22	Advantages of using .....	Jan 31
	<b>MICROPHONES</b>		DC types .....	Mar 30
	Base station type .....	Jul 63	EICO 430 3" .....	Jul 46
	Cable for .....	Feb 20	Measuring inductance of low-Q coils, as used in .....	Dec 32
	Carbon type .....	CS Jul 67	Oscillator troubleshooting with .....	Dec 37
	Cardioid dynamic, shock mounted .....	Sep 98	Stereo servicing, as used in .....	Dec 42
	Dynamic and magnetic types .....	CS Jul 66	Transistor radios, as used in servicing .....	Jun 24
	High impedance type .....	CS Jul 66	Voltage measurements with .....	Jan 34
	Microphone-headset combination .....	May 94	Wideband types .....	Mar 90
	Noise-reducing type .....	Jul 61	<b>PA SYSTEMS</b>	
	Rebuilding carbon units .....	CS Oct 82	Battery-powered amplifier .....	Feb 78
	Transistorized types .....	CS Jul 66	Jacks, compact audio .....	Jun 78
	<b>MISCELLANEOUS</b>		Paging equipment .....	Apr 71
	Bleeder-circuit correction .....	Apr 14		
	Electronic musical instrument			

Portable amplifier .....	Sep 98	Solid-state inverter .....	Aug 73	Collapses on vacant channels	
Radio paging .....	CS Jul 72	Stabilized variable AC type .....	Sep 54	(Muntz Chassis T37) .....	Sym Jan 27
<b>PHONOGRAPHS</b>		Terado Model 50-204 .....	Jan 58	Compressed at bottom, stretched	
Record duster .....	Apr 70	Transistor TV, used in .....	Jun 1	at top (Magnavox Chassis	
Slide film viewer, with .....	Nov 115	Transistor circuits in two-way		V38-01-00) .....	VSS Feb 7
Speed too slow		equipment .....	CS Oct 88	<b>Dim</b>	
(RCA RP20502) .....	TS May 21	<b>PREVIEWS OF NEW SETS</b>		—Admiral 14VP3C .....	TS Jul 21
Tracking-error checker .....	Nov 115	Admiral Model UP1112C,		—blinker troubles .....	Mar 68
Wire, tone arm .....	Feb 20	Chassis C21A10-2C .....	Mar 1	—Silvertone Chassis	
<b>PICTURE SYMPTOMS</b>		Andrea Model VTT319 .....	May 1	528.50180 .....	TS Mar 17
AFC waveform coil bypassed .....	Feb 64	Arvin Model 63K19 .....	May 2	<b>Dim or absent (Silvertone</b>	
Bends, sync unstable (Admiral		Emerson Model U1840,		Chassis 528.50180) .....	TS Mar 17
Chassis 18B7) .....	VSS Sep 6	Chassis 120673-C .....	Mar 2	<b>Disappears</b>	
Boost poor .....	May 82	General Electric Model		—as set warms (Philco	
Brightness low (DuMont		M10YDG, Chassis SY .....	Feb 1	Chassis 12N51) .....	VSS May 6
Chassis 120692) .....	Sym Feb 27	Magnavox Model 1MR-303N,		—slowly, with brightness	
Brightness maximum, no control		Chassis C44-03-00 .....	Aug 1	and contrast control at	
(Silvertone Chassis		Motorola Model Y23CK38M-2,		maximum (RCA	
456.51800) .....	VSS Mar 7	Chassis TS908Y .....	Sept 1	CTC4A) .....	TS Nov 23
Color incorrect (Bradford		Motorola Model Y28K89,		Distortion, lines on left half .....	TS Jan 17
Model WGEC-		Chassis TS-586 .....	Feb 2	Foldover at bottom	
89946A) .....	Sym Nov 28, 29, 30	Packard Bell Model 19T22,		—Coronado S15 .....	VSS Feb 5
<b>Defocused at high</b>		Chassis 8814P .....	Mar 3	—Muntz Chassis T37 .....	Sym Jan 26
brightness (DuMont		Panasonic Mitey 9 .....	Feb 3	<b>Height insufficient</b>	
Chassis 120692) .....	Sym Feb 20	Philco Model M4504MR,		—TraVler Chassis	
Drive line, compress right side .....	Oct 65	Chassis 14N50A .....	Aug 2	23K6180F .....	VSS May 7
Fine tuning effects .....	Mar 62	RCA Model 64A030MU,		—Muntz Chassis T37 Sym	Jan 26, 28
Heavy snow, all channels		Chassis KCS146 .....	Feb 4	<b>High voltage weak (Magnavox</b>	
affected (Setchell-Carlson		Setchell-Carlson Model		Chassis V38-01-00) .....	VSS Feb 8
Chassis 400) .....	Sym Aug 26	3C64, Chassis U800 .....	Sept 2	<b>Horizontal bending and</b>	
Picture missing or very weak,		Silvertone Model 4101,		pulling (Wells-	
sound also missing (Setchell-		Chassis 528.60269 .....	Aug 3	Gardner Chassis S37) Sym	Mar 25
Carlson Chassis 400) .....	Sym Aug 27	Sonora Model S64K236W .....	Sept 3	<b>Horizontal pulling, top of</b>	
Screen blank (Setchell-Carlson		Sylvania Model 19P35,		raster effected (Panasonic	
Chassis 400) .....	Sym Aug 27	Chassis 571 .....	May 3	Model Mitey 5) .....	Sym Jun 28
Snow, no sound or picture (RCA		Truetime Model 2DC3416 .....	Aug 4	<b>Intermittent, critical</b>	
Chassis KCS143F) .....	Sym Dec 29	Westinghouse Model H-P3433,		horizontal sync (Panasonic	
Snowy picture, unstable sync		Chassis V-2443-3 .....	May 4	Model Mitey 5) .....	Sym Sep 26
(Setchell-Carlson		Zenith Model ML2784W3,		<b>Intermittent loss (Zenith Chassis</b>	
Chassis 400) .....	Sym Aug 26	Chassis 16L24 .....	Sept 4	16V25, Q, U) .....	VSS Aug 7
<b>Washed out</b>		Zenith Model T2203J,		<b>Modulation (120 cps, sound &amp;</b>	
—brightness normal (DuMont		Chassis 14L30 .....	Mar 4	picture okay (G-E MW	
Chassis 120692) .....	Sym Feb 27	<b>RADIO</b>		Compactron) .....	VSS Sep 7
—buzz in sound (Bradford		See also <b>AUTO</b> and <b>TRANSISTOR</b>		<b>Narrow</b>	
WGEC-91124A) .....	Sym Oct 28	Crystal-controlled tuners .....	Jan 77	—horizontal sync lost	
—1/3 rotation of contrast		FM, AFC .....	Feb 34	(Bradford WGEC-	
control, after (G-E		Low B+ missing (Truetime		91124A) .....	Sym Oct 29
MW Compactron) .....	VSS Sep 8	Model D2020 AM-FM) TS	Jun 18	—picture and sound normal	
—sound reduced (Muntz		Selenium rectifier burns		(Bradford WGEC-	
J-series) .....	Sym May 28	(Matsushita Model 748) TS	Oct 54	91124A) .....	Sym Oct 30
<b>Weak</b>		Signal generator for .....	June 68	—foldover, loss of horizontal	
—noise on all channels (RCA		Signal tracer for .....	Jul 48	sync (RCA Chassis	
Chassis KCS137A) .....	VSS Mar 5	Volume critical (Silvertone		KCS102B) .....	Sym Jul 27
—washed out, caused by poor		Chassis 132. 40100) .....	TS Apr 22	<b>Pulse sources for retrace</b>	
IF transformer connections		<b>RASTER (FAULTS)</b>		blinking .....	May 38
(Admiral Chassis 18B7) VSS	Sept 6	<b>Absent</b> .....	Feb 36	<b>Top stretched, bottom</b>	
<b>White compression</b> .....	Sept 28	—boost voltage low		folded over .....	Sym Jan 28
<b>PICTURE TUBES</b>		(Admiral Chassis 18B7) VSS	Sept 5	<b>Vertical deflection inoperative</b>	
Checker and reactivator .....	May 70	—boost voltage zero (RCA		—Magnavox Chassis	
<b>Color</b>		Chassis KCS137A) .....	VSS Mar 5	V38-01-00 .....	VSS Feb 8
—replacement of .....	Nov 42	—buzz in sound (Bradford		—Philco Chassis 12N51 .....	VSS May 6
—troubles in .....	Feb 36	WGEC-91124A) .....	Sym Oct 30	<b>Vertical foldover, insufficient</b>	
Implosion of .....	TS Dec 64	—Coronado S15 .....	VSS Feb 6	width & height (G-E	
Tester .....	Jun 76	—DuMont Chassis		MW Compactron) .....	VSS Sep 7
Tester-rejuvenator .....	Apr 58	120692 .....	Sym Feb 28	<b>Vertical linearity poor</b>	
Wire, HV .....	Feb 20	—high voltage zero, sound		—Coronado S15 .....	VSS Feb 5
<b>POWER SUPPLIES</b>		not affected (Panasonic		—Magnavox Chassis	
Color receivers, in .....	Nov 8	Mitey 5) .....	Sym Sep 24	V38-01-00 .....	VSS Feb 7
Converter, DC to DC .....	Mar 91	—sound normal (Panasonic		—Silvertone Chassis	
Cornell-Dubilier <i>Portapower</i>		Mitey 5) .....	Sym Sep 25	456.51800 .....	VSS Mar 8
Model 12PP14 power		Blinks (RCA), caused by open		<b>Vertical stretch</b> .....	Sym Jan 27
converter .....	Aug 64	ground .....	Mar 72	<b>Vertical sweep collapses</b>	
Delco Radio Model T-612		Blooming and HV loss .....	May 36	—Admiral Chassis 18B7 .....	VSS Sep 6
power supply .....	Apr 62	Brightness control has no		—Airline Chassis	
Dual-voltage type .....	Sep 98	effect (Zenith Chassis		WG-5218A .....	VSS Aug 6
Filters in .....	Feb 38	16V25, Q, U) .....	VSS Aug 8	—G-E MW Compactron .....	VSS Sep 8
Fusible resistor in (Philco		<b>Brightness insufficient</b>		—TraVler Chassis	
Model UJ3702L) .....	TS Jul 20	—G-E MW Compactron,		23K6180F .....	VSS May 7
Heath IP-22 isolation		defective spark gap .....	VSS Sep 8	<b>Vertical sweep inadequate on</b>	
transformer .....	Sept 54	—Magnavox Chassis		right side (Philco Model	
Regulator for mobile servicing .....	Mar 91	V38-01-00 .....	VSS Feb 7	AT1718) .....	TS Jun 19
Seco Model RPS 5 regulated		<b>Brightness low, becomes</b>		<b>Vertical white lines</b>	
power supply .....	TE Sep 85	normal as set warms		(Coronado S15) .....	VSS Feb 5
		(Philco Chassis 12N51) VSS	May 5	<b>Width and height reduced</b> .....	Oct 32

Width insufficient  
 —Magnavox Chassis  
 V38-01-00 ..... VSS Feb 8  
 —Bradford WGEC-  
 91124A ..... Sym Oct 28, 29  
 —RCA Chassis KCS102B Sym Jul 27

**RF SECTION**

Communications receiver,  
 alignment of ..... CS Apr 78  
 Transistor circuits ..... Jun 5

**RECTIFIERS**

Color TV focus type ..... Oct 75  
 Heavy-duty silicon type ..... Sep 98  
 Silicon-controlled type ..... Jun 62  
 Solid-state type ..... Sep 36

**RESISTORS**

Analyzer for ..... TE Oct 58  
 Bridge, comparative ..... Mar 92  
 Change in value ..... Jan 50  
 Decade ..... Mar 93  
 Fusible type ..... Sep 60  
 —Philco Model UJ3702L .. TS Jul 20  
 Heavy-duty potted type ..... Jan 77  
 Light-dependent type ..... Jun 62  
 Peak limiting, for ..... Sep 60  
 Steel-case, heavy-duty type ..... May 90  
 Substituter ..... Feb 58  
 Trimmer, subminiature ..... Feb 78

**SEMICONDUCTORS**

AFC diodes ..... Feb 34  
 AGC, as used in ..... Jun 7  
 Analyzer for ..... Mar 95  
 Diodes ..... June 56  
 —AFC, in FM ..... Feb 34  
 High voltage circuits, as used in ..... Jun 2  
 Horizontal AFC, as used in ..... Jun 3  
 Horizontal oscillator, as used in ..... Jun 3  
 Horizontal sweep, as used in ..... Jun 2  
 Hybrid circuits ..... Jun 64  
 Industrial applications ..... Jun 56  
 Light-dependent resistor ..... Jun 62  
 Packaging of ..... Jun 64  
 Power supply, in TV ..... Jun 1  
 Quad, diode ..... Jun 58  
 Replacements, general ..... Nov 118  
 Silicon-controlled rectifiers ..... Jun 62  
 Silicon-rectifier, replacement  
 for tubes ..... Jan 75  
 Sound circuits, as used in ..... Jun 8  
 Sync circuits, as used in ..... Jun 8  
 Tester, combination with tube ..... Mar 96  
 Thermistor ..... Jun 62  
 —protective devices, as ..... Sep 62  
 Thyrectors ..... Sep 94  
 Tuners, as used in ..... Jun 5  
 Tunnel diode ..... Jun 60  
 TV circuits, as used in ..... Jun 1  
 Varactor diode ..... Jun 58  
 Varistor ..... Jun 62  
 Vertical sweep circuits, as used in ..... Jun 4  
 Video detector and driver, as  
 used in ..... Jun 6  
 Video IF, as used in ..... Jun 6  
 Video output, as used in ..... Jun 7  
 Zener diode ..... Jun 58

**SHOP TALK**

AGC troubles and solutions ..... Sep 28  
 AM-RF generators, curing  
 troubles in ..... Mar 54  
 Oscilloscope troubleshooting  
 of transistor radios ..... Jun 24  
 Rasters, shrunken ..... Oct 32  
 Shortcuts that waste time ..... Jul 32  
 Synchronuide, operation of ..... Feb 32  
 Synchronuides, "tough dogs" in ..... Apr 32  
 Transistor radio servicing ..... Dec 36

**SERVICING AT BENCH**

Auto receiver, duplicating  
 operating conditions of ..... Oct 42  
 Filter replacement ..... Dec 52  
 Bench designs ..... Jan 1  
 Tape recorders, small portable ..... Dec 55  
 Transistor versus tubes ..... Jun 70  
 Wasted time ..... Jul 32

**SIGNAL GENERATORS, RF**

Aligning TV with ..... Mar 60  
 Attenuator, with ..... Mar 44  
 Communications equipment, for ..... Apr 3  
 Electronic Measurement Corp.  
 Model 501 AM signal  
 generator ..... Apr 58  
 Measuring low-Q-  
 inductance, as used in ..... Dec 33  
 RCA WR-50A signal generator ..... Jun 68  
 Six frequency ..... Mar 93  
 Sweep frequency ..... Mar 95  
 Troubles in ..... Mar 54

**SOUND DETECTORS, TV**

Buzz, caused by open quadrature  
 coil (Silver-tone Chassis  
 456.51800) ..... VSS Mar 7

**SOUND SECTION OF TV**

Alignment of IF in ..... Mar 66  
 Buzz

—G-E MW Compactron ..... VSS Sep 7  
 —Philco Chassis 12N51 ..... VSS May 5  
 —Silver-tone Chassis  
 456.51800 ..... VSS Mar 7  
 Distortion and/or low volume,  
 caused by frozen quadrature  
 coil (RCA Chassis  
 KCS137A) ..... VSS Mar 6

**Inoperative**

—Coronado S15 ..... VSS Feb 6  
 —Philco Chassis 12N51 ..... VSS May 5  
 —Muntz J-series ..... Sym May 27  
 —Setchell-Carlson Chassis  
 400 ..... Sym Aug 27

Intermittent operation (Zenith  
 Chassis 16V25, Q, U) ..... VSS Aug 8

Ratio-detector transformer  
 connections bad (Silver-tone  
 Model 7102S) ..... TS Oct 21

Smoothing filter shorted in  
 (G-E Model 21C138) ..... TS Jun 18

Sound weak, but without  
 distortion ..... Sym May 27

Transistor circuits used in ..... Jun 8

Volume low  
 —RCA Chassis KCS137A ..... VSS Mar 6  
 —Silver-tone Chassis  
 456.51800 ..... VSS Mar 7

**Weak output**

—distorted, contrast also  
 reduced (Muntz J-  
 series) ..... Sym May 26  
 —fades out completely  
 (TraVler Chassis  
 23K6180F) ..... VSS May 8

**SPEAKERS**

Display of ..... Dec 70  
 Dual-range type ..... May 88  
 Installation  
 —audio systems, in ..... May 56  
 —auto rear deck, in ..... Aug 68  
 Light-weight type ..... May 95  
 Matched extension systems ..... Oct 76  
 Phasing of ..... May 60  
 Weather proof type for paging  
 and talk back ..... Nov 118  
 Woofer 18" ..... May 93

**SPEAKER ENCLOSURES**

Construction of ..... May 56

**STEREO FM**

Alignment, principles ..... Jul 30  
 Automatic tuner ..... Jan 75  
 Bandpass, 38-kc ..... Jul 56  
 Composite signal ..... Dec 44  
 Decoder circuits, servicing of ..... Dec 42  
 Distortion (G-E RC1710  
 multiplex adapter) ..... TS Sep 20  
 Equipment requirements for  
 alignment ..... Jul 31  
 Generator  
 —alignment, for ..... Jul 30  
 —analyzer, and ..... Aug 66  
 —multiplex ..... Mar 94  
 Indicator ..... Dec 47

Pilot-channel adjustment ..... Jul 31  
 Transmitted signal ..... Dec 42  
 Trap adjustment, 67-kc ..... Jul 54

**SYMFACT**

Automatic brightness-contrast  
 control (Dumont Chassis  
 120692) ..... Feb 25  
 Converter stage, transistor ..... Jun 36  
 Horizontal AFC, synchronuide  
 (RCA Chassis KCS102B) ..... Jul 25  
 Horizontal output, grid as  
 bias source (Bradford  
 Model WGEC-  
 91124A) ..... Oct 27  
 Motorola Chassis TS-570 ..... Feb 12  
 Muntz Model 7310M (27") ..... Feb 12  
 One-stage vertical sweep  
 (Muntz Chassis T37) ..... Jan 25  
 Philco Chassis 13J42 ..... Feb 12  
 Reflex sound IF, video and  
 sound in one tube  
 (Muntz J-series) ..... May 25  
 Snow in fringe-channel  
 pictures (RCA Chassis  
 KCS143F) ..... Dec 29, 30  
 Switch tuner, nuvistor RF  
 amplifier ..... Dec 27  
 Sync separator (Sylvania  
 Chassis 571-1) ..... Apr 27  
 Sync separator, single triode  
 (Wells-Gardner Chassis  
 S37) ..... Sym Mar 23  
 Symphonic Model 19P2A ..... Feb 12  
 Transistor AGC circuit, keyed-  
 amplified (Panasonic  
 Model Mitey 5) ..... Sym Jun 27  
 Transistor horizontal oscillator,  
 blocking-type with diode  
 AFC (Panasonic Model  
 Mitey 5) ..... Sym Sep 23  
 TraVler Chassis 1906-242 ..... Feb 12  
 Turret tuner, frame grid RF  
 —Setchell-Carlson Chassis  
 400 ..... Sym Aug 25  
 Video amplifier with ABC (Du  
 Mont Chassis 120692) ..... Sym Feb 25  
 Wells-Gardner Chassis S17 ..... Feb 12  
 Zenith Chassis 14K20 ..... Feb 12  
 Zenith Chassis 16K26 ..... Feb 12

**SYNC**

See also HORIZONTAL and VERTICAL  
 Absent, horizontal and vertical  
 (Wells-Gardner Chassis  
 S37) ..... Sym Mar 24  
 Bending and pulling in  
 raster, horizontal  
 —Wells-Gardner Chassis  
 S37 ..... Sym Mar 25  
 Bending in picture, AGC  
 critical (Zenith Chassis  
 16V25, Q, U) ..... VSS Aug 8  
 Critical, video weak (Setchell-  
 Carlson Chassis 400) ..... Sym Aug 28  
 Hold critical ..... Sym Jan 27  
 Horizontal  
 —pulling, vertical jitter  
 (Sylvania Chassis  
 57101) ..... Sym Apr 28, 30  
 —vertical rolling (TraVler  
 Chassis 23K6180F) ..... VSS May 8  
 Separator  
 —4CS6 (Sylvania  
 Chassis 571-1) ..... Sym Apr 27  
 —single triode (Wells-  
 Gardner 537) ..... Sym Mar 23  
 Simplified approach to ..... Sep 30  
 Transistor circuits ..... Jun 8  
 Unstable  
 —picture bends (Admiral  
 Chassis 18B7) ..... VSS Sep 6  
 —snowy picture (Setchell-  
 Carlson Chassis 400) ..... Sym Aug 26  
 Vertical  
 —hold critical, horizontal

affected (Sylvania Chassis 571-1) .....Sym Apr 28  
 —hold poor, horizontal tearing (Silvertone Chassis 456.51800) .....VSS Mar 8  
 —roll intermittent, horizontal critical (Wells-Gardner Chassis S37) .....Sym Mar 24  
 —roll, poor horizontal hold (Airline Chassis WG-5218A) .....VSS Aug 6

#### TAPE RECORDERS

Adjustment and maintenance of heads .....May 86  
 Distortion and low volume .....Dec 58  
 Electrical characteristics of heads .....May 31  
 Erase circuit modification (Webcor) .....May 12  
 Head-gap correction .....Jun 14  
 Heads  
 —maintenance and selection .....May 30  
 —mounting .....May 84  
 —replacements .....Jun 78  
 Inspection and cleaning of heads .....May 86  
 Level-meter adjustment .....TS Apr 23  
 Magnetic heads, theory of .....May 30  
 Mounting of heads .....May 84  
 Recording of phone conversations .....Jun 14  
 Speed problems .....Dec 55  
 Stereo head for cartridges .....May 92  
 Stereo model .....Dec 70  
 Transistor portable .....Feb 79  
     Jun 78, 79  
     Dec 55

#### TELEVISION

Alignment with signal generator .....Mar 60  
 Circuit protection devices .....Sep 58  
 Conversion of standards .....Jul 34  
 Foreign systems .....Jul 34  
 Intermittents, servicing .....Jan 50  
 International standards, chart of .....Jul 34  
 Receivers for 1965 .....Oct 1  
 Ten Years of Color/a Report .....Nov 99  
 Transistorized circuits .....Jun 1  
 UHF  
 —converters .....Jan 62  
 —preparing for .....Jan 60  
 Waveforms save servicing time of .....May 34

#### TEST EQUIPMENT

Accessory guide .....Jan 20  
 Analyzer, transistor .....Mar 95  
 B & K Model 445 picture tube rejuvenator-tester .....Apr 58  
 B & K Model 1074  
   *TV Analyst* .....TE Sep 82  
 Bar-dot patterns .....Jan 30  
 C-R bridge, transistorized .....Aug 74  
 Capacitor testers .....Feb 42  
 Check list of .....Jan 31  
 Color  
 —adapter for tube testers .....Feb 36  
 —alignment accessories .....Aug 44  
 —bar-dot generator .....Jan 30  
 —pattern generator, solid-state .....Dec 69  
 “tough dogs,” for servicing .....Mar 68  
 TV, for servicing .....Nov 84  
 Color-bar hints .....May 52  
 Communications servicing, for .....Apr 1  
 —alignment generator .....May 90  
 Comparator, R-C-L .....Mar 92  
 Continuity testing .....Mar 88  
 Cornell-Dubilier BF-71A capacitance-resistance analyzer .....TE Oct 58  
 Cornell-Dubilier *Portapower* Model 12PP14 power converter .....Aug 64  
 DC scopes .....Mar 30  
 Decade  
 —capacitance .....Mar 86  
 —resistance .....Mar 93  
 Delco Radio Model T-612 power supply .....Apr 62

Distortion meter .....Mar 80  
 EICO 430 3" scope .....Jul 46  
 EICO 667 dynamic conductance tube and transistor tester .....Dec 59  
 Electronic Measurement Corp.  
   Model 501 AM signal generator .....Apr 58  
 Field strength meter .....Feb 56  
 —UHF type .....Mar 32  
 Frequency meter .....Apr 1  
 —CB type .....Apr 70  
 G-C Electronics 36-540 tube tester .....May 70  
 G-C Electronics 36-616 CRT tester-rejuvenator .....TE Nov 96  
 Generator  
 —color bar-dot .....Mar 76,86  
 —Pattern type, solid-state .....Dec 69  
 —RF signal type .....Mar 93  
 —sweep type .....Mar 95  
 —troubles in AM-RF types .....Mar 54  
 Good instruments, advantages of .....Mar 50  
 Heath Model IG-62 color bar and dot generator .....May 70  
 Heath Model IT-12 signal tracer .....Jul 48  
 Hickok Model 470A VTVM .....TE Oct 60  
 Hickok Model 209B VTVM .....Aug 64  
 In-circuit test adapter .....Jan 78  
 Jackson Model 805 VTVM .....May 74  
 Keyed rainbow adapter .....Apr 69  
 Magnavol adapter for tube tester (Seco) .....Jul 40  
 Mercury Model 301 tube tester/VOM .....Jul 52  
 Mercury Model 900  
   *Color TV Analyzer* .....Dec 60  
 Meter protection device .....May 94  
 Modern bench, for .....Jan 30  
 Modern business, in .....Jan 44  
 Modulation meter .....Apr 1  
 Oscilloscope, wide-band .....Mar 90  
*Port-A-Lab*, transmitter and antenna tester .....Feb 54  
 RCA WR-50A signal generator .....Jun 68  
 RCA WV-76A AC VTVM .....Dec 62  
 RF power meter .....Feb 56  
     Apr 3  
 RF signal generator, transistorized .....Aug 74  
 Seco Model RPS-5 regulated power supply .....TE Sep 85  
 SENCORE Model FC123 *Filcheck* .....Jun 76  
 SENCORE Model MX129 FM multiplex generator and analyzer .....Aug 66  
 Signal generator .....Apr 3  
 —alignment with .....Mar 60  
 Specialized instruments, guide to .....Oct 38  
 Standard-Kollsman VHF to UHF translator .....TE Oct 61  
 Stereo multiplex generator .....Jan 72  
     Mar 94  
 Substituter, component .....Feb 58  
 Sweep generator waveform .....Jan 31  
 Test-prod wire .....Feb 20  
 TV field-strength meter .....Dec 69  
 VOM in ignition system servicing .....Feb 30  
 VTVM  
 —distortion meter combination .....Mar 80  
 —FM AFC servicing, in .....Feb 74  
 —TV servicing, in .....Mar 29  
 Voltage measurements with scope .....Jan 34  
 Watt meter, RF .....Jul 61  
 Zenith Model SPTE-1 multiplex generator .....Jun 66  
 TOOLS  
 Chassis test jigs .....Apr 69  
 Combination wrench and

screwdriver .....Apr 69  
 Desoldering iron .....Oct 74  
 Electrical tape .....Nov 116  
 Fuse puller .....Jan 78  
 Magnifier .....May 95  
 Soldering pistol .....May 88  
     Oct 76  
 Wire stripper .....Oct 78

#### TRANSFORMERS AND COILS

Extension speaker transformer .....Apr 69  
 Horizontal flyback (Setchell-Carlson replacement) .....Apr 71

#### TRANSISTORS

AGC circuits, as used in .....Jun 7  
 Analyzer for .....Mar 95  
 Bias circuits .....Jun 33  
 Field-effect type .....Jun 52  
 High-voltage circuits, as used in .....June 2  
 Horizontal circuits, as used in .....June 3  
 Ignitions systems .....Feb 30  
 —circuit correction .....Jun 14  
 Lead recognition .....Jun 32  
 PNIP type in ignition system .....Feb 69  
 Power supply, TV .....Jun 1  
 Replacement type, general .....Dec 70  
 Sound, as used in .....Jun 8  
 Speech amplifier, using .....CS Jul 70  
 Sync circuits, as used in .....Jun 8  
 Terminology .....Jun 32  
 Tuners, as used in .....Jun 5  
 Vertical sweep circuits, as used in .....Jun 4  
 Video circuits, as used in .....Jun 6  
 Voltage polarity .....Jun 32

#### TRANSISTOR RADIO

Converter stage .....Sym Jr Jun 36  
 Dead receiver .....Sym Jr Jun 36  
 Distortion, distant stations missing .....Sym Jr Jun 37  
 FM-AM auto type .....TS Feb 18  
 Intermittent in FM-AM auto type, (Ford F3TBF) .....TS Feb 18  
 Intermittent operation, jarring set has effect .....Sym Jr Jun 37  
 Oscillation in .....Jun 70  
 —IF (G-E P-755-A) .....Feb 19  
 Sound  
 —fades .....Jun 35  
 —weak .....Jun 34  
 Troubleshooting methods .....Dec 36  
 —with a scope .....Jun 24

#### TRANSISTOR TESTERS

EICO 667 dynamic conductance tube and transistor tester .....Dec 59  
 Semiconductor, tube .....Mar 96

#### TROUBLESHOOTER, THE

Admiral Model 14VP3C, no picture .....TS Jul 21  
 Admiral Model PL17F31B, horizontal tearing .....TS May 20  
 Airline 35WG-3060B, oscillator waveform distorted .....TS Apr 68  
 Bendix Model PM21CS, vertical rolling .....Aug 68  
 Capital ND-309 .....TS Mar 16  
 Chevrolet car radio Model 985432, volume fades .....TS Oct 21  
 Chevrolet Model 987727 auto radio, audio output low .....TS Jun 18  
 Delco car radio Model 982136, rear seat speaker impedance problems .....TS Sep 21  
 Ford Model 94BF auto radio, buzzing sound .....TS Jun 19  
 Ford Model F3TBF, auto radio, intermittent .....TS Feb 18  
 General Electric Model 21C138, filter shorted .....TS Jun 18  
 General Electric Model P-755-A —transistor radio, squeals .....TS Feb 19  
 General Electric RC1710 multiplex adapter, distorted stereo .....TS Sep 20

Matsushita Model 748 table radio, selenium rectifier burns .....TS Oct 54  
 Philco Chassis 444, AGC flutter .....TS Oct 54  
 Philco Chassis 12H50A, fine tuning shaft broken .....TS Oct 55  
 Philco Chassis TV-330, vertical roll after warmup .....TS Jan 16  
 Philco Model AT1718, vertical sweep trouble .....TS Jun 19  
 Philco Model G4242M —vertical roll .....TS May 20  
 .....TS Sep 20  
 Philco Model UJ3702L, fusible resistor opens .....TS Jul 20  
 RCA RP20502 record changer, speed troubles .....TS May 21  
 RCA CTC4A —no raster at maximum brightness .....TS Nov 23  
 RCA CTC11 (color), filament voltage low .....TS Apr 22  
 RCA Chassis CTC15 —audio, video, and brightness loss; no convergence .....TS Nov 22  
 RA Chassis KCS72, horizontal oscillator out of sync .....TS Aug 18  
 RCA Chassis KCS82, horizontal sync lost .....TS Oct 20  
 RCA Chassis KCS128, picture rolls .....TS May 20  
 Radio volume critical (Silvertone) .....TS Apr 22  
 Silvertone Model 7102S, ratio detector transformer connections .....TS Oct 21  
 Spartan Model 52CM24, Chassis 23V5-2, horizontal output current high .....TS Jul 20  
 Sylvania Chassis 1-515-1, raster distorted .....TS Jan 17  
 Tape saturation, meter adjustment for .....TS Apr 23  
 Truetone Model D2020 AM-FM radio, low B+ missing .....TS Jun 18  
 Westinghouse Chassis 494306, noise in UHF video .....TS Jul 21  
 Westinghouse Chassis V-2436, severe tearing and excessive snow .....TS Oct 56

**TUBES**  
 Cabinet for .....May 92  
 Heat dissipating shield .....Apr 70  
 Stock guide for TV .....May 78

**TUBE TESTERS**  
 Automatic counter model .....Sep 98  
 B & K Model 445 picture tube rejuvenator-tester .....Apr 58  
 EICO 667 dynamic conductance tube and transistor tester .....Dec 59  
 G-C Electronics 36-540 tube tester .....May 70  
 G-C Electronics 36-616 CRT tester-rejuvenator .....TE Nov 96  
 In-circuit test adapter .....Jan 78  
 Laboratory and industrial type .....Nov 117  
 Magnoval adapter .....Jul 40  
 Mercury Model 301 tube tester/VOM .....Jul 52  
 SENCORE Model FC123 Filcheck .....Jun 76

**TUNERS, TV**  
 Balun coils open (RCA KCS137A) .....VSS Mar 5  
 Fine tuning insufficient. (Setchell-Carlson Chassis 400) .....Sym Aug 28  
 High channels lost .....Sym Dec 28  
 Mixer, UHF .....Mar 36  
 Oscillator, troubles in UHF .....Mar 35  
 Repairs of .....Jun 16  
 Transistor circuits .....Jun 5  
 .....Sep 64

—UHF .....Mar 1  
 Turret type, frame-grid RF Setchell-Carlson Chassis 400) .....Sym Aug 25  
 UHF type .....Jan 60  
 —noise in video (Westinghouse Chassis 494306) .....TS Jul 21  
 —oscillator faults .....Mar 25  
 —preliminary tests .....Mar 34

**TWO-WAY RADIO**  
 Call selector .....Sep 98  
 Field servicing of .....Mar 40  
 Power supply, regulated .....Mar 91  
 RF power and SWR .....Mar 40  
 Tone coding .....Jan 66  
 Transistor power supplies .....CS Oct 88  
*Two-Way Mobile Radio* .....Oct 66  
 Unusual complaints in .....Mar 48  
 Wire-line remote control .....Jan 64

**UHF TELEVISION**  
 AFC in .....Jul 15  
 Antenna and RF stages, tuner .....Mar 100  
 Antennas .....Jan 62  
 .....Apr 71  
 —sales of .....Aug 56  
 Converters .....Jan 62  
 .....Nov 119  
 —kit .....Dec 71  
 FSM's conversion of .....Mar 32  
 Legal check list .....Jan 61  
 Mobile antenna .....Aug 75  
 New station .....Oct 18  
 Noise in picture (Westinghouse Chassis 494306) .....TS Jul 20  
 Preparing for .....Jan 60  
 RF troubles in tuners .....Mar 36  
 Rules regarding .....Jan 61  
 Standard-Kollsman VHF to UHF translator .....TE Oct 61  
 Translator .....Mar 94  
 Tuners .....Mar 34  
 .....Jul 15  
 —transistorized .....Sep 64  
 VHF to UHF conversion .....Jun 16

**VERTICAL SWEEP**  
 Autotransformer as blanking pulse source .....May 40  
 Bottom foldover —Coronado S15 .....VSS Feb 5  
 —linearity normal (Muntz T-37) .....Sym Jan 26

**Collapses**  
 —Admiral Chassis 18B7 .....VSS Sep 6  
 —G-E MW Compactron .....VSS Sep 8  
 —streaks and flashes in raster (TraVler Chassis 23K6180F) .....VSS May 7

**Deflection inoperative**  
 —output transformer shorted Magnavox Chassis V38-01-00) .....VSS Feb 8  
 —Philco Chassis 12N51 .....VSS May 6

**Deflection poor, (RCA Chassis KCS128) .....TS May 20**  
 Drive circuit .....May 40  
 Excessive height, hold critical .....Sym Jan 27  
 Foldover .....May 36  
 Height insufficient, (TraVler Chassis 23K6180F) .....VSS May 7  
 Intermittent distortion, raster collapses .....Sym Jan 27  
 Output transformer as pulse source .....May 38

**Linearity poor**  
 —Coronado S15 .....VSS Feb 5  
 —Silvertone Chassis 456.51800 .....VSS Mar 8

**Multivibrator .....TS Mar 16**  
 Picture rolls (Philco Model G424M) .....TS May 20  
 Pulse sources for retrace blanking .....May 38

Reduced height —linearity good .....Sym Jan 28  
 —oscillator off frequency .....Sym Jan 26

**Right side of raster tapered, Philco Model AT1718) .....TS Jun 19**  
 Roll, (Coronado S15) .....VSS Feb 5  
 Single-stage type .....Sym Jan 25  
 Top stretch, intermittent jitter .....Sym Jan 28  
 Transistor circuits .....Jun 4

**VERTICAL SYNC**  
 Hold —critical, contrast poor, sound distorted (Muntz J-Series) .....Sym May 28  
 —critical, height excessive (Muntz T37) .....Sym Jan 27  
 —critical, horizontal affected slightly (Sylvania Chassis 571-1) .....Sym Apr 28  
 —drifts out of range (Airline Chassis WG-5218A) .....VSS Aug 5  
 —poor (Silvertone Chassis 456.51800) .....VSS Mar 8

**Intermittent roll**  
 —Panasonic Model Mitey 5 .....Sym Jun 29  
 —Wells-Gardner Chassis S37 .....Sym Mar 24

**Jitter (Sylvania Chassis S71-1) .....Sym Apr 30**  
 —horizontal normal (Wells-Gardner Chassis S37) .....Sym Mar 26  
 —horizontal pulling (Sylvania Chassis 571-1) .....Sym Apr 28

**Lost, horizontal pulling (Wells-Gardner Chassis S37) .....Sym Mar 26**  
 Roll —Bendix PM21CS .....Aug 68  
 —Coronado S15 .....VSS Feb 5  
 —hold control inoperative (Magnavox Chassis V38-01-00) .....VSS Feb 7  
 —hold control inoperative Philco TV-330) .....TS Jan 16  
 —horizontal hold poor Airline Chassis WG-5218A) .....VSS Aug 6  
 —intermittent, horizontal pulling (Wells-Gardner Chassis S37) .....Sym Mar 25  
 —Philco G4242M .....TS Sep 20  
 —tears horizontally (TraVler Chassis 23K6180F) .....VSS May 8

**Separator, single triode (Wells-Gardner Chassis S37) .....Sym Mar 23**  
 Unstable, horizontal OK Philco Chassis 12N51) .....VSS May 6

**VIDEO (FAULTS)**  
 ABC troubles (DuMont Chassis 120692) .....Sym Feb 25  
 Brightness low (DuMont Chassis 120692) .....Sym Feb 27  
 Color brightness dim, blanker trouble .....Mar 68

**Contrast**  
 —maximum, no control (TraVler Chassis 23K6180F) .....VSS May 7  
 —poor, sound distorted, vertical hold critical (Muntz J-Series) .....Sym May 28

**Horizontal bending, reduced video (Panasonic Model Mitey 5) .....Sym Jun 28**  
 Overload —sync okay (Airline Chassis WG-5218A) .....VSS Aug 6  
 —sync poor (Admiral Chassis 18B7) .....VSS Sep 5

Picture	
—absent (Admiral 14 VP3C)	TS Jul 21
—absent, sound also absent (Muntz J-Series)	Sym May 27
—dull, ABC on (DuMont Chassis 120692)	Sym Feb 27, 28
—overloaded, intermittent vertical roll (Panasonic Mitey 5)	SEym Jun 29
—washed out (Panasonic Mitey 5)	Sym Jun 29
—weak, audio slightly affected (Muntz J-Series)	Sym May 26
Smear (Airline Chassis WG-5218A)	VSS Aug 5
Weak, sync critical (Setchell-Carlson Chassis 400)	Sym Aug 28
<b>VIDEO AMPLIFIER AND OUTPUT</b>	
Automatic brightness - contrast control (DuMont chassis 120692)	Sym Feb 25
Brightness low, coupling capacitor leaking (DuMont Chassis 120692)	Sym Feb 27
Output-plate signal	May 44
Picture symptoms	
—absent, sound also absent, raster okay (Philco Chassis 12N51)	VSS May 5

—overload and pull (Philco Chassis 12N51)	VSS May 5
—washed out (DuMont Chassis 120692)	Sym Feb 27
Transistor circuits	Jun 7
<b>VIDEO DETECTOR</b>	
DC voltage in, measuring	Mar 64
Transistor circuits	Jun 6
<b>VIDEO SPEED SERVICING</b>	
Admiral Chassis 18B7	Sep 5
Airline Chassis WG-5218A	Aug 5
Coronado Chassis S15	Feb 5
General Electric MW Compactron	Sep 7
Magnavox Chassis V38-01-00	Feb 7
Philco Chassis 12N51	May 5
RCA Chassis KCS137A	Mar 5
Silvertone 456.51800	Mar 7
TraVler Chassis 23K6180F	May 7
Zenith Chassis 16V25,Q,U	Aug 7
<b>VOM'S</b>	
Ignition systems servicing with	Feb 30
Protection device for	May 94
TV servicing with	Mar 28
<b>VTVM'S</b>	
AC type, in distortion meter	Mar 80
Battery eliminator for	Jul 60
FM, AFC, servicing with	Feb 74
Hickok Model 470A	TE Oct 60
Hickok Model 209B	Aug 64

Horizontal oscillator, used in checking	TS Jan 17
Jackson Model 805	May 74
Limiters, used in checking	CS Apr 92
RCA Model WV-76A VTVM	Dec 62
Sensitive type	Mar 96
TV servicing with	Mar 28
UHF tuners, used in servicing	Mar 100
<b>WAVEFORMS</b>	
AFC	
—stage grid	Feb 64
—synchronguide	Feb 32
Blanking pulse	May 40
Blocking oscillator	Sym Jan 25
Difference amplifiers with blanker trouble	Mar 68
Horizontal sawtooth capacitor defective	Oct 63
Multiplex	Jul 54
RF generator	Mar 54
Sweep generator	Jan 31
Synchronguide	Apr 32
Video amplifier	
—ABC, and (DuMont Chassis 120692)	Sym Feb 25
—overdriven	Sep 28
Video output, blanker trouble	Mar 70
<b>WIRE AND CABLE</b>	
Coaxial cable	May 88
Stock guide	Feb 20

### INDEX OF TITLES

ABC's of Convergence	Sep 32
AGC Troubles and Solutions	Sep 28
Aerosols in Servicing Chemicals	Jul 36
Aligning TV With a Signal Generator	Mar 60
Alignment Techniques for Two-Way	Apr 1
Antenna Systems Can Be Safe	Aug 39
Applied reasoning for Auto Sets	Oct 42
Audio—Sideline or Main Line?	Sep 72
Blunderful World of Color	Nov 56
Boosting and Distributing UHF and VHF Signals	Aug 32
CB for Industrial Communication	CS Apr 98
Care and Choosing of Tape Heads	May 30
Case Book for Transistor Techs	Jun 34
Checking Phase of Color Bar Generators	Nov 32
Cheerful Charlie Foils the DIY's (Do-it-yourselfers)	Apr 40
Choosing New Lines of Business	Jun 44
Chroma Reference and Control Circuits	Nov 48
Color Instruments for 1964	Nov 90
Color Questions and Answers/Then and Now	Nov 66
Communications Tower Maintenance	CS Oct 86
Converting FSM's For UHF	Mar 32
Cures for Color Hue Troubles	May 46
Curing Aircraft Radio Problems, Part 1	Sep 34
Curing Aircraft Radio Problems, Part 2	Dec 34
Curing Blindness in FM Tuning Eyes	May 32
Curing Troubles in AM-RF Generators	Mar 54
Custom Stereo Simplified	May 56
DC Scope for Quick Analysis	Mar 30
Death Stalks the Rooftop	Sep 56
Electronics in the Darkroom	Jan 32
Field Effect Transistor	Jun 52
Field Servicing Two-Way Radio	Mar 40
Find Profit in Small Tape Recorders	Dec 55
Floor Plans for Service Shop	Jan 1
Fooled by Poor Boost	May 36
Foreign TV Systems	Jul 34
Frequency Synthesis	CS Apr 86
Getting Ready for UHF	Jan 60
Good Test Equipment Doesn't Cost . . . It Pays	Mar 50
Guide to Communications Antennas	CS Apr 76
Guide to Importers	Jun 38
Guide to Unusual Test Equipment	Oct 38
The High Cost of Employee Theft	Jul 42
Hi-Ho Come to the Fair	Jul 1
Highlights of 1965 TV Lines	Oct 1
Hot Roasted Intermittents	Jan 50
Improving Retrace Blanking	May 38
Industrial Semiconductors at Work	Jun 56
Instruments Simplify Color Tough-Dogs	Mar 68
Is Your Insurance Up to Date?	Jan 68
Key to Stereo Alignment	Jul 30
Kill Those Callbacks	Dec 48
The Knack of Filter Replacement	Dec 52
Know Your '65 Color Circuits	Nov 1
Make the Most of Your Attorney	Oct 48
Master Antenna Systems	Aug 30
Measuring Lo-Q Inductances	Dec 32
Me? Do Transistor Servicing?	Jun 32
Meet An Auto Radio Specialist	Apr 34
Misaligned RF Stage, The	CS Apr 78
Modulation Limiters for Two-Way	CS Apr 92
New Sound From Old Cabinets	Oct 34
Problem: Width & Horizontal Linearity	Oct 36
Quick Ways of Chroma Alignment	Nov 38
Radio Amateurs Aren't So Bad!	Sep 78
Radio Paging	CS Jul 72
Rebuilding Carbon Mics	CS Oct 82
Receiver Extraordinary	May 66
Removing the Mystery from Modulators	CS Jul 68
Replacing a Color CRT	Nov 42
Royal Road to Transistor Servicing	Dec 36
Scoping in Transistor Radios	Jun 24
Service Shop 1974	Jan 36
Servicing Electronic Musical Instruments	Aug 34
Servicing Electrostatic Air Cleaners	Aug 46
Servicing Stereo Adapters	Dec 42
Servicing TV With VTVM or VOM	Mar 28
"Shortcuts" That Waste Time	Jul 32
Shrunken Rasters	Oct 32
Sizes, Functions and Facts About Small Value Capacitors	Apr 36
Solid State Rectifier's Come of Age	Sep 36
Solid State TV Circuits From A to Z	Jun 1
Stock Guide for TV Tubes	May 78
Stock Guide to Radio Hi-Fi Tubes	Dec 20
Study of Luminance Channels, A	Nov 40
Sync Simplified	Sep 50
TV Circuit Protection Devices	Sep 58
TV Waveforms Save Analysis Time	May 34
Techniques For Selling Antennas	Aug 56
Techniques of Distortion Chasing	Sep 38
Ten Years of Color/A Report	Nov 99
Test Equipment Accessory Guide	Jan 20
Test Equipment for the Modern Bench	Jan 30
Test Equipment on Parade	Mar 86
Tips for Color Servicing	Nov 78
Tough Dogs in Synchronguides	Apr 32
Tracing Color Signals	Nov 36
Transistor Power Supplies for Two-Way	CS Oct 88
Transistorized Mikes for Mobiles	CS Jul 66
Transistorized UHF Tuners	Sep 64
UHF Tuners Inside and Out	Mar 34
Voltage Measurement With A Scope	Jan 34
Wire-Line Remotes For Two-Way	Jan 64
You Can Manage for Profit	Apr 48
You Can Modernize Your Service Business	Jan 44

Tarzian offers  
**FAST, DEPENDABLE  
 TUNER REPAIR  
 SERVICE (ALL  
 MAKES)**



It just makes sense that a manufacturer of tuners should be better-qualified, better-equipped to offer the most dependable tuner repair and overhaul service.

Sarkes Tarzian, Inc. pioneer in the tuner business, maintains two complete, well-equipped Factory Service Centers—assisted by Engineering personnel—and staffed by specialized technicians who handle **ONLY** tuner repairs on **ALL** makes and models.

Tarzian-made tuners received one day will be repaired and shipped out the next. Allow a little more time for service on other than Tarzian-made tuners.

Tarzian offers a 12-month guarantee against defective workmanship and parts failure due to normal usage. And, compare our cost of \$9.50 and \$15 for UV combinations. There is absolutely no additional, hidden charge, for **ANY** parts except tubes. You pay shipping costs. Replacements on tuners beyond practical repair are available at low cost.

Ⓢ Tarzian-made tuners are identified by this stamping.

When inquiring about service on other tuners, always give TV make, chassis and Model number. All tuners repaired on approved, open accounts. Check with your local distributor for Sarkes Tarzian replacement tuners, replacement parts, or repair service.

 **SARKES TARZIAN, INC.**  
 Bloomington, Indiana

MANUFACTURERS OF TUNERS . . . SEMICONDUCTORS . . . AIR TRIMMERS . . . FM RADIOS . . . AM/FM RADIOS . . . AUDIO TAPE . . . BROADCAST EQUIPMENT

**ONLY**  
**\$9.50**  
**INCLUDING**

**ALL PARTS**  
 (except tubes)  
**and LABOR**

**24-HOUR SERVICE  
 1-YEAR WARRANTY**

**TWO SERVICE CENTERS  
 TO SERVE YOU BETTER**

**See your distributor, or use the  
 address nearest you for fast fac-  
 tory repair service**

537 South Walnut St.  
 Bloomington, Indiana  
 Tel: 332-6055

10654 Magnolia Blvd.  
 North Hollywood, Calif.  
 Tel: 769-2720



A HOWARD W. SAMS PUBLICATION

**publisher**

Howard W. Sams

**editor**

Forest H. Belt

**managing editor**

George F. Carne, Jr.

**associate editors**

James M. Moore  
Allen B. Smith  
Stuart N. Sall  
Norman D. Tanner

**consulting editors**

William E. Burke  
Joe A. Groves  
C. P. Cliphont

**production manager**

Robert N. Rippy

**circulation manager**

Pat Tidd  
Katherine Krise, Ass't.  
Cara Lo Von Willard, Ass't.

**art directors**

Gene La Rue  
Robert W. Reed

**advertising & editorial assistants**

Hazel Boyer  
Rebecca Clingerman

**photography**

Paul Cornelius, Jr.

**advertising sales offices**

David L. Milling, advertising sales manager

**midwestern**

Hugh Wallace  
PF REPORTER  
4300 West 62nd Street,  
Indianapolis, Ind.  
AXminster 1-3100

**eastern**

Gregory C. Masefield  
Howard W. Sams & Co., Inc.  
3 West 57th Street,  
New York, N. Y.  
Murray Hill 8-6350

**western**

The Maurice A. Kimball Co., Inc.  
2550 Beverly Blvd., Los Angeles 57, Calif.  
DUmkirk 8-6178; and 580 Market Street,  
Room 400, San Francisco 4, Calif. EXbrook 2-3365

Address all correspondence to  
PF REPORTER, 4300 W. 62nd Street  
Indianapolis, Indiana 46206



Copyright © 1964 by Howard W. Sams & Co., Inc.  
PF REPORTER is a trademark of Howard W. Sams & Co., Inc. No part of PF REPORTER may be reproduced without written permission. No patent liability is assumed with respect to use of information herein. Acceptance of advertising does not in any manner signify the products, policies and services so advertised have been approved, endorsed or recommended by this magazine.

Subscription Prices: 1 year—\$5.00, 2 years—\$8.00, 3 years—\$10.00, in the U. S. A., its possessions and Canada. All other foreign countries: 1 year—\$6.00, 2 years—\$10.00, 3 years—\$13.00. Single copy 50¢; back copies 65¢.

Indexed in Lectrodex.  
Printed by the Waldemar Press Div.  
of Howard W. Sams & Co., Inc.

# PF Reporter™

PHOTOFACT

the magazine of electronic servicing

VOLUME 14, No. 12

DECEMBER, 1964

## CONTENTS

<b>1964 Annual Subject Reference Index</b>		<b>1</b>
<b>Letters to the Editor</b>		<b>13</b>
<b>The Electronic Scanner</b>		<b>18</b>
<b>Stock Guide for Radio and Hi-Fi Tubes</b>		<b>20</b>
<b>Symfact: Switch Tuner (Nuvisor RF Amplifier)</b>		<b>27</b>
See what happens to voltages and waveforms when troubles occur.		
<b>Measuring Low-Q Inductances</b>	Robert G. Middleton	<b>32</b>
Directions for using your scope to test large coils.		
<b>Curing Aircraft Radio Troubles—Part 2</b>	Keith Bose	<b>34</b>
Another installment to better acquaint you with aviation gear.		
<b>Royal Road to Transistor Servicing</b>	Allan F. Kinckiner	<b>36</b>
Shop Talk—Select the correct test instrument and you'll save time.		
<b>Report on New York Hi-Fi Show</b>		<b>40</b>
<b>Servicing Stereo Adapters</b>	Norman D. Tanner	<b>42</b>
Quicker Servicing—Here's how to troubleshoot multiplex circuits with your scope.		
<b>Book Review</b>		<b>44</b>
<b>Kill Those Callbacks</b>	Frank R. Perullo	<b>48</b>
Dollar and Sense Servicing—There are checkout procedures to prevent return trips—do you use them?		
<b>The Knack of Filter Replacement</b>	Jay F. Shane	<b>52</b>
Facts to help you select suitable electrolytics.		
<b>Find Profit in Small Tape Recorders</b>	Homer L. Davidson	<b>55</b>
Servicing methods to help you "cash-in" on the miniatures.		
<b>Notes on Test Equipment</b>	Allen B. Smith	<b>59</b>
Lab reports on the EICO Model 667 Tube and Transistor Tester, Mercury Model 900 Color TV Analyzer, and RCA Model WV-76A AC VTVM.		
<b>The Troubleshooter</b>		<b>64</b>
<b>Product Report</b>		<b>69</b>
<b>Free Catalog &amp; Literature Service</b>		<b>72</b>
<b>Monthly Index on free literature card</b>		

### ABOUT THE COVER

The small-sized tape recorders shown on this month's cover can be the source of large-sized profits. The holiday season will see a sharp increase in sales of personal portable recorders, each of which is a possible candidate for service. Join other successful technicians and follow the hints in the article on page 55.



**Q**UESTION: When it comes to electrolytic capacitors, why do more than half of the nation's Radio-TV Service Technicians prefer to do business with Sprague Distributors?

**A**NSWER: Because they don't want makeshift substitutions or multi-rating "fits-all" capacitors. They insist on exact replacements, which are always available through Sprague Distributors everywhere.

SPRAGUE **TWIST-LOK**<sup>®</sup> CAPACITORS...

1863 different ratings and sizes...

the world's most complete selection  
of **EXACT** replacements!



**Wouldn't you really rather have what the set manufacturer recommends? An exact replacement in capacitance, voltage, and size is easier to install and less expensive, in most cases, than substitutes!**

We don't have to tell you that it's easier to service with exact replacements. And we don't have to tell you that it's better, too. When sets are designed, specific capacitance values are used for peak operation, so it takes exact replacements to restore original set performance.

And who better than Sprague knows which values and sizes are needed in the replacement market? Sprague, the world's largest component manufacturer, has the most complete specification file on original set requirements. That's why you're always right when you service with Sprague TWIST-LOK exact replacements!

GET YOUR COPY of Sprague's comprehensive Electrolytic Capacitor Replacement Manual K-107 from your Sprague Distributor, or write Sprague Products Company, 105 Marshall Street, North Adams, Massachusetts.



WORLD'S LARGEST MANUFACTURER OF CAPACITORS

88-127-83 R2

Circle 3 on literature card

December, 1964/PF REPORTER 11

For window-size blow-ups of this message, send 10c to Sprague Products Co., 105 Marshall St., North Adams, Mass., to cover handling and mailing costs.



## Is "do-it-yourself" TV Service as dangerous as they say?

When a TV set starts "acting up," a tube is often involved. At least, that's where the trouble *appears* to be.

Some people will pull the back off the set, remove the tubes, and take them to the "do-it-yourself" tube tester at the neighborhood store. The test instrument shows which tubes are faulty (but not always—some faults do not show up on these testers). Replacements are purchased, then inserted into the set. Reception improves, and the trouble has been caught and corrected.

### BUT HAS IT?

The self-service test instrument checks *tubes*. It can't test the *more than 500 other parts* in

your set! It can't show you the *source* of the trouble that probably blew the tube. Neither can it show the damage often suffered by other parts due to the faulty tube.

Mere tube replacements do not always cure these trouble spots. Weak links continue to exist, *setting up chain reactions of damage, trouble, and expense!*

The total failure of many a good TV set can be traced directly to "do-it-yourself" tinkering.

Your TV set is the most complicated device you own—far more complex than even your automobile. When you need TV service, call an expert technician—your fully trained and experienced Independent Service Dealer.

**AFTER ALL, YOU WOULDN'T ENTRUST YOUR JOB TO AN AMATEUR, WOULD YOU?**

**THIS MESSAGE WAS PREPARED BY SPRAGUE PRODUCTS COMPANY,  
DISTRIBUTORS' SUPPLY SUBSIDIARY OF SPRAGUE ELECTRIC COMPANY, NORTH ADAMS, MASSACHUSETTS FOR . . .**

**YOUR INDEPENDENT TV-RADIO SERVICE DEALER**

Why doesn't  
everybody  
stock

# Jensen® SNAP-IN CARTRIDGES?



If you've been shying away from profitable cartridge replacement business because of the cost and conniptions of cumbersome inventories, let Jensen get you back on the right "track." Here's how:

- Less inventory
- Complete coverage
- Superior performance
- Respected, accepted brand name

Why doesn't everybody stock Jensen Snap-In Cartridges? Give 'em time. Soon they will.

### SPECIAL K-1964 DEAL

Write for details on special Dealer Starter Kit K-1964—12 brackets and 6 interchangeable cartridge bodies which will replace 80% of all basic cartridge requirements.

World's finest phonograph needles, cartridges, drives, accessories

**Jensen®**  
INDUSTRIES, INC.  
301 Interstate Rd., Addison, Ill.

In Canada: A. T. R. Armstrong,  
P.O. Box 244, Islington, Ontario

Circle 5 on literature card

## Letters to the Editor

Dear Editor:

I've noticed lately the capacitor value abbreviation "pf" (picofarad) is being used in place of mmf (micromicrofarad) on wiring schematics and other electronics literature. My latest PHOTOFACT Folders and PF REPORTER issues use the mmf, as previously. Does the Sams Co. plan to adopt the pf symbol on their service literature? If so, when?

LEON HOWLAND

Indianapolis, Ind.

The electronics industry has finally agreed to general use of the pf abbreviation; pico is a prefix meaning 10<sup>-12</sup> farad, which is equivalent to micromicrofarad. The mmf abbreviation has been phased out in favor of pf, starting with our January 1965 PF REPORTER and PHOTOFACT Folder.—Ed.

Dear Editor:

We were very surprised and disappointed to find that your July 1964 article "Aerosols In Servicing Chemicals" listed a great variety of cleaner-lubricant sprays but failed to make any mention of Channel Master Shield or Channel Master Lectro-Mist.

DANIEL S. ROHER

Advertising Manager  
Channel Master Corp.

Your sprays certainly should have been listed, Dan. The oversight is ours. We suggest all readers who saved the July article add these two sprays to those mentioned.—Ed.

Dear Editor:

This may happen frequently, but to me it was uncanny. The same day I got your August 1964 issue of PF REPORTER, I had in the shop a G-E Model 21C135 set which showed exactly the same symptoms described in Symptom 3 of SYMFACT; sure enough, the 4700-ohm oscillator supply resistor was at fault. Three days later, I worked on another G-E, this time a Model 14T106; the symptoms were like those in Symptom 4 of August SYMFACT. You guessed it—the trouble was an open mixer plate coil, just as SYMFACT said. In both the above sets, the voltages and everything were just exactly as shown. Keep up the good work in this feature and the rest of PF REPORTER.


JAY F. SMITH

Amory Radio & TV  
Chicago, Ill.

Very good, Jay. While circuit tolerances might cause slight variations from set to set and model to model, there is no guesswork in the preparation of SYMFACT. Every symptom is experienced and analyzed thoroughly in our lab. This special method of preparation has paid off, and resulted in a considerable number of letters relating experiences like your own.—Ed.



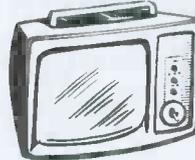**NOW...**  
THE FABULOUS  
\*G. E. COMBO



PLAYS ANYWHERE  
ON 110 AC OR 12V DC  
BATTERY CURRENT

For  
Auto • Boat • Plane  
Camps • Picnic • Trailer

ATR MODEL 12T-RME-1 INVERTER... \$39<sup>95</sup>  
\*G.E. MODEL M110Y 11" PORTABLE TV \$99<sup>95</sup>

\*Available at G.E. TV Dealers

Both Only \$139<sup>90</sup> Retail  
THE ATR MODEL 12T-RME-1 ONLY ONE  
OF A FAMILY OF FAMOUS DC-AC INVERTERS

### Also NOW...

HAND WIRED—  
NO PRINTED  
CIRCUITRY

ATR ALL-TRANSISTOR  
ULTRA COMPACT  
UNIVERSAL MODEL 707



Karadio  
IN DASH...  
UNDER DASH...

Complete with variable tone control... R. F. stage  
... Built-in speaker... and External speaker Jack.

ATR MODEL 707... \$29<sup>95</sup> Retail



ATR ALL-TRANSISTOR  
ROOF-MOUNT and  
IN-DASH MODELS

TRUCK

Karadio  
MODEL TR-720

FITS ALL TRUCKS • BOATS •  
STATION WAGONS  
INSTANT PLAY... POWERFUL

Complete with patented antenna-yoke assembly.  
(U.S. Patent No. 3,087,118. Canadian Reg. 575,567)

ATR MODEL TR-720... \$44<sup>95</sup> Retail



ATR "A" Battery  
ELIMINATOR

For Demonstrating and  
Testing Auto Radios—  
TRANSISTOR or VIBRATOR  
OPERATED!  
Designed for testing D.C.  
Electrical Apparatus on Reg-  
ular A.C. Lines.

MAY ALSO BE USED AS A BATTERY CHARGER  
MODEL 610C-ELIF... 6 volts at 10 amps. or 12 volts  
at 6 amps. Shipping weight 22 lbs.

USER NET PRICE... \$55<sup>00</sup>

ATR AUTO RADIO and  
COMMUNICATION

LONGER-LIFE  
VIBRATORS

"The Best by Test!"



SEE YOUR ELECTRONIC PARTS DISTRIBUTOR OR  
WRITE FACTORY FOR LITERATURE & DEALER PRICES

ATR ELECTRONICS, INC.



Quality Products Since 1931

St. Paul, Minnesota 55101—U.S.A.

Circle 6 on literature card

LICENSED UNDER ONE OR MORE OF U.S. PATENTS 2,988,081; 2,995,879; 3,011,189; 3,108,280; 3,150,376 AND ADDITIONAL PATENTS PENDING IN U.S.A. AND CANADA. PRODUCED BY JFD ELECTRONICS CORPORATION UNDER EXCLUSIVE LICENSE FROM THE UNIVERSITY OF ILLINOIS FOUNDATION.

ADVERTISED IN  
**LOOK** / *Sunset*

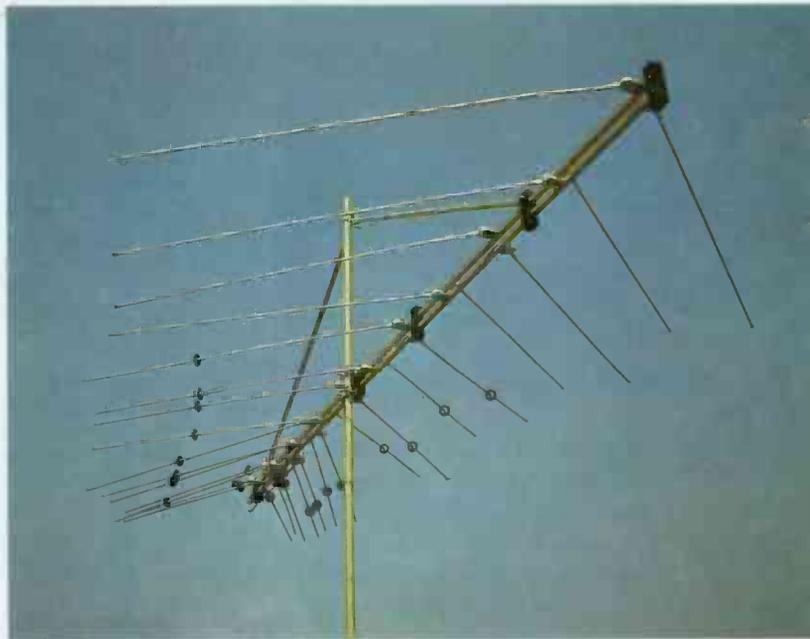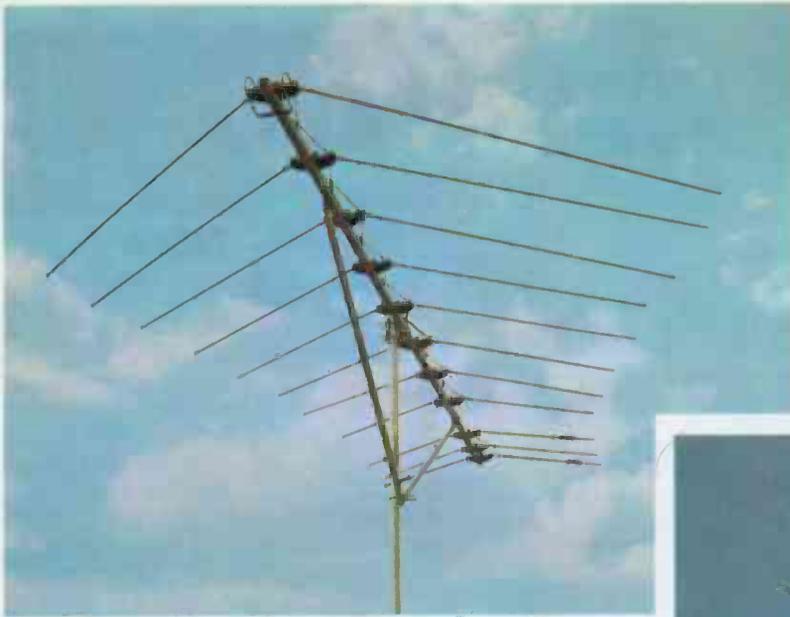

Model LPV-11

Model LPV-VU 15

Copyright JFD Electronics Corp. 1964

# You Can Rely on JFD Log-Periodic\* TV COLOR and

**NEW**—from the famous JFD R&D Laboratories in Champaign, Illinois — the authentic Log-Periodics with the engineering advances that outperform all others in **COLOR**, black and white—on VHF, UHF, VHF/UHF/FM!

**WHY MORE JFD LPV LOG-PERIODICS ARE BEING INSTALLED THAN ANY OTHER VHF ANTENNA . . .** The JFD Log-Periodic is a revolutionary new concept in antenna design. Its frequency-independent performance does not sacrifice gain, directivity, bandwidth or impedance match as other conventional antennas must on certain frequencies to achieve all-VHF-channel reception. Harmonically resonant V-elements operate on the patented Log-Periodic cellular formula  $\frac{L_{(n+1)}}{L_n} = \tau$  to provide the same superb performance on every VHF channel—color or black and white—plus FM/Stereo.

**STOUTLY BUILT OF HEAVY WALL GOLD ALODIZED ALUMINUM . . .** Inch for inch, ounce for ounce, JFD LPV Log-Periodics deliver more mechanical

strength in less mass. Gleaming gold alodizing (the same used by NASA and the military services) does not insulate vital contact points as does anodizing. Instead, electrically conductive gold alodizing improves signal continuity.

**DEVELOPED FROM RESEARCH PERFORMED AT THE UNIVERSITY OF ILLINOIS ANTENNA RESEARCH LABORATORIES . . .** The JFD Log-Periodic is the commercial end result of six years of electronic research. No other design has undergone such intensive research and development by leading antenna scientists.

**INSTALLED BY MORE WORLD'S FAIR PAVILIONS THAN ANY OTHER BRAND . . .** The New York World's Fair House of Good Taste, Formica House, New York City Pavilion, House of Japan, Eastman Kodak exhibit, Florida and Hawaii Pavilions installed JFD Log-Periodics to assure best possible performance of their color TV sets. Millions of Fair visitors will remember and ask for the JFD Log Periodic LPV, paving the way for more sales by you.



Manufactured and Sold by JFD Electronics Corp. 1964

**THE ONE AND ONLY ORIGINAL LPV LOG-PERIODIC FOR VHF CHANNELS 2 TO 13 & FM/STEREO**



model	description	list
LPV17	18 Cells Directors	\$59.95
LPV14	15 Cells Directors	49.95
LPV11	11 Cells Directors	39.95
LPV8	8 Cells Directors	29.95
LPV6	6 Cells	21.95
LPV4	4 Cells	14.95

**NEW! THE FIRST COMBINATION VHF/UHF/FM/STEREO —THE LOG PERIODIC "ALL-VU"—WITH SINGLE LEAD-IN**

model	description	list
LPV-VU18	18 Cells	\$69.95
LPV-VU15	15 Cells	\$59.95
LPV-VU12	12 Cells	\$49.95
LPV-VU9	9 Cells	\$39.95
LPV-VU6	6 Cells	\$27.50

**NEW! LOG PERIODIC ZIG-A-LOG FOR PROBLEM "UHF" AREAS**

model	description	list
LPV-ZU20	E-Plane Stacked	\$37.50
LPV-ZU10	1-Bay	\$17.95

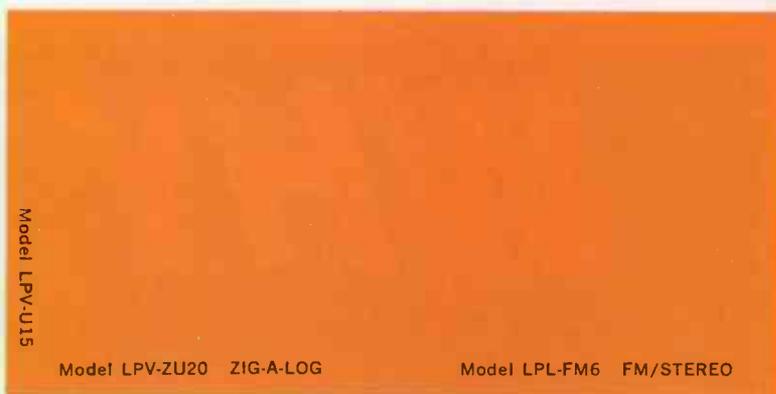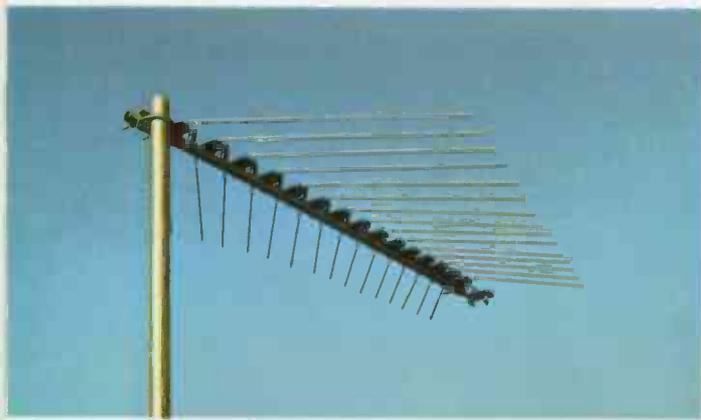

Model LPV-U15

Model LPV-ZU20 ZIG-A-LOG

Model LPL-FM6 FM/STEREO



# antennas for the Finest Pictures In Sight-Black/White!

## JFD FREQUENCY-INDEPENDENT LPV LOG-PERIODIC BREAKS THROUGH THE BANDWIDTH BARRIER FOR

**GAIN:** As high as 14 db (in model LPV17)—with extra gain on the high band where it is needed most.

**BANDWIDTH:** Frequency-independent log periodic design delivers broad band performance never before possible. Does not discriminate against any channel—or frequency.

**RESPONSE:** Consistently flat ( $\pm \frac{1}{2}$  db) across both low and high bands for the finest color reception.

**DIRECTIVITY:** No need to give up directivity to obtain bandwidth as other antennas do. Log-Periodic backfire horizontal radiation patterns, for example, are the narrowest of any all-channel antenna. Reject noise, ghosts, interference and other unwanted signals more effectively because: sharpness of beamwidth affects directivity more than any other factor.

**VSWR:** As low as 1.2 to 1 for maximum transfer of signal to line across the full bandwidth. Low VSWR's are typical of JFD LPV Log-Periodic antennas because of their constant 300 ohm impedance characteristic.

## EVERY LPV YOU BUY EARNS YOU VALUABLE FAIR FESTIVAL POINTS . . .

Each JFD Log-Periodic VHF, UHF, VHF/UHF/FM, or FM/STEREO you install includes Fair Festival certificates which you can trade in for FREE World's Fair tickets, trips or cash.

Whether it's VHF, UHF, VHF/UHF/FM, or FM/STEREO, JFD HAS THE LOG PERIODIC TO HELP YOU MAKE THE SALE OTHERS CAN'T!

## SEE WHY AT THE MOMENT OF TRUTH, THE PICTURE IS THE PROOF—THE JFD LPV LOG-PERIODIC WORKS BEST!

\*Don't gamble on Log-Periodic "look-alikes" and imitations! Insist on the genuine LPV by JFD—exclusive producers of the pace-setting Log-Periodic antenna developed from research performed by the Antenna Research Laboratories of the University of Illinois.

# JFD

## JFD ELECTRONICS CORPORATION

15th Avenue at 62nd Street, Brooklyn, N. Y. 11219

JFD Electronics-Southern Inc., Oxford, North Carolina

JFD International, 64-14 Woodside Ave., Woodside 77, N. Y.

JFD Canada, Ltd., 51 McCormack Street, Toronto, Ontario, Canada

### NEW! LOG PERIODIC LPV FOR UHF CHANNELS 14 TO 83 & VHF 7 TO 13



model	description	list
LPV-U21	21 Cells	\$27.95
LPV-U15	15 Cells	\$18.95
LPV-U9	9 Cells	\$12.50
LPV-U5	5 Cells	\$ 6.95

### NEW! LOG PERIODIC LPL-FM STEREO



model	description	list
LPL-FM10	10 Cells	\$49.95
LPL-FM8	8 Cells	\$39.95
LPL-FM6	6 Cells	\$29.95
LPL-FM4	4 Cells	\$19.95

### NEW! TELE-AMP ANTENNA AMPLIFIERS FOR VHF, UHF & FM



model	description	list
VUT-3	3-Transistor VHF/UHF/FM Amplifier	\$49.95
VN-2	2-Nuvistor VHF Amplifier	\$39.95
VT-2	2-Transistor VHF Amplifier	\$39.95
VT-1	1-Transistor VHF/FM Amplifier	\$34.95
UHT-1	1-Transistor UHF Amplifier	\$39.95
FT-1	1-Transistor FM Amplifier	\$34.95

Circle 7 on literature card

# WHY... SERVICE COLOR TV ?

**WHY WAIT?  
YOU CAN MAKE  
MONEY NOW!**

**...IF YOU'RE EQUIPPED - AND  
A WIDE BAND SCOPE IS A MUST**



**1,000,000 SETS IN 1964  
65% OF NBC PROGRAMMING\*  
IN COLOR  
NEW 25" SETS COMING  
THIS FALL  
2,000,000 ALREADY IN USE**

\*PRIME TIME

This Hickok-quality, full 5", wide-band scope - factory assembled, wired and calibrated can put you in color TV service... for less than \$200.00.

- Rise time—less than  $0.08 \mu\text{sec}$ .
- AC response—5 cycles to 4.5 MC within 3 db
- Vertical sensitivity—40 MV RMS/inch
- 5 times horizontal sweep expansion
- Sharp, bright (1600 volts anode potential)  
Trace with full astigmatic correction  
and, of course, it's...


Only  
**\$199.50**  
MODEL 677




THE COMPLETE COLOR LINE



MODEL 615

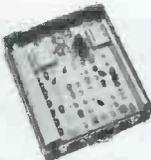

MODEL 656XC

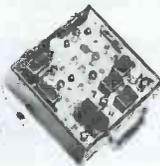

MODEL 660



MODEL 661



MODEL 675A

THE **Hickok**

**ELECTRICAL INSTRUMENT CO.**  
10566 DUPONT AVENUE • CLEVELAND 8, OHIO

Circle 8 on literature card

*makes other  
tube testers*

**OBSOLETE**

# HICKOK

## Model 800A



*Honest tests on today's tubes demand 14-position selector switches. Compactrons, novars, 5- and 7-pin nuvistors, 10-pin headers, transistors and diodes, along with the older type tubes, can all be checked out — completely and correctly — including high sensitivity leakage and gas tests, with the truly modern Hickok Model 800A. This quality tube tester includes these other recognized Hickok-quality features: Hickok-developed  $G_m$  test on all tubes • Sensitive, instantaneous inter-element leakage and shorts test • Filament continuity test — and the original HICKOK roll chart subscription service keeps it up-to-date!*

*Best of all, Hickok's low price for this portable do-it-all tester is only \$199.95. Available from stock at your franchised Hickok distributor. Let him give you a demonstration.*

**Ask to see  
these other  
Hickok  
instruments, too**



**677**  
Wide Band Oscilloscope



**470A**  
Uni-scale VTVM



**661**  
Color Bar Generator

**THE HICKOK ELECTRICAL INSTRUMENT CO. • 10566 Dupont Avenue • Cleveland, Ohio 44108**

*Circle 8 on literature card*

NOW, MORE THAN EVER...

# THE FINEST SERVICE IN TV TUNER OVERHAULING

## CASTLE TV TUNER-EAST HAS MOVED TO NEW LOCATION WITH IMPROVED FACILITIES

In Long Island City near Postal Concentration Center to provide faster service by mail.

All other U.S. and Canadian Servicemen will get the same fast service from CASTLE-CHICAGO and CASTLE-CANADA.



**ALL MAKES  
ALL LABOR  
AND PARTS  
(EXCEPT TUBES)\*  
ONE PRICE**

# 995

THIS ONE LOW PRICE INCLUDES ALL UHF, VHF AND UV COMBINATION\* TUNERS

Simply send us your defective tuner complete; include tubes, shield cover and any damaged parts with model number and complaint. 90 Day Warranty.

Exact Replacements are available for tuners unfit for overhaul. As low as \$12.95 exchange. (Replacements are new or rebuilt.)

\*UV combination tuner must be of one piece construction. Separate UHF and VHF tuners must be dismantled and the defective unit only sent in.

Pioneers in TV



Tuner Overhaling

# CASTLE TV TUNER SERVICE, INC.

EAST: 41-90 Vernon Blvd., Long Island City 1, N. Y.

MAIN PLANT: 5701 N. Western Ave., Chicago 45, Illinois

CANADA: 136 Main Street, Toronto 13, Ontario

\*Major Parts are additional in Canada

Circle 9 on literature card



## The Electronic Scanner

news of the servicing industry

### Plant to Open

An ultramodern production plant will open early next year at Glasgow, Ky., in order to meet increasing demand for Mallory electrolytic capacitors. In his announcement, Mr. Mallory said, "We are demonstrating our faith in the growth of the capacitor business, and our confidence that we will continue to expand our market position despite foreign and domestic competition, by making an investment at Glasgow which, including equipment, will total nearly \$2,000,000." The 85,000-square-foot Glasgow plant, scheduled for completion in April 1965, will be suitable for production of almost any kind of electrolytic capacitor. Employment may eventually reach 500.

### Technical School Progress

Plans for the fall-winter program at Sams Technical Institute, Inc., were detailed at the 111th Indiana State Teachers Convention. A new four-man advisory committee for the school will include the following prominent Indianapolis men: Edward D. James, president of Edward D. James & Associates; Albert L. Maillard, president and managing director of Electric League of Indianapolis; Leo H. Gans, vice-president and director, Education Division, The Bobbs-Merrill Company, Inc.; James A. Milling, president, Sams Division, and director, Howard W. Sams & Co., Inc. The committee will assist W. D. Renner, vice-president of vocational technical training, in overall future planning for the Institute. Also announced was the recent affiliation of STI with Indiana Northern University at Upland, Indiana. All work successfully completed at the Sams Technical Institute, Inc. can now be applied for credit toward a bachelor degree at the university. Enrollment at STI has climbed to over 600 this fall, equaling the enrollment of some colleges in the state. The Institute offers four separate two-year resident programs including Electronics Technology, Architectural Engineering, Tool Engineering, and Industrial Engineering. One current activity is an eight-week session of advanced training to keep practicing technicians informed of the most recent technological advancements in electronics. Courses on transistors and color television are available, with more to be added soon.

• Please turn to page 24



# YOU CAN WIN THIS GREAT SPORTS CAR!



## ENTER THE PHOTOFACT® "WIN-A-MUSTANG" CONTEST!

### A PRIZE FOR EVERYONE WHO ENTERS!

#### FIRST PRIZE

New 1965 Mustang Sports Car

#### SECOND PRIZE

Luxurious Mink Stole

#### THIRD PRIZE

Ladies Elgin Diamond Wrist Watch

All entrants will receive a special gift just for entering this PHOTOFACT contest...

Contest ends December 31, 1964. Entry forms are available from your Sams Distributor or from Howard W. Sams & Co., Inc. (only one entry per contestant accepted). All you do is fill out the entry form, and have it validated by your Distributor. Winners will be determined by a drawing. (Contest limited to U.S.A.; not valid where prohibited by State or local laws).

**DRAWING WILL BE HELD ON  
JANUARY 15, 1965**

*winners will be notified*

### *Get Your Entry Form Today!*

Enter this exciting contest now! Pick up your entry form at your Sams' Distributor, or send coupon below. Do it today! Everyone has an equal chance to win the drawing. All entries must be postmarked before January 1, 1965. Enter this worthwhile contest now!

CONTEST CLOSES DECEMBER 31, 1964

### GET YOUR ENTRY FORM

**DO IT TODAY!**

Available from your Sams Distributor or send coupon

HOWARD W. SAMS & CO., INC., Dept. PFF-12  
4300 W. 62nd St., Indianapolis, Indiana 46206

- Send my entry form for the "Win-A-Mustang" Contest
- I am presently a subscriber to a PHOTOFACT Service
- I am not a subscriber to a PHOTOFACT Service

Name \_\_\_\_\_

Shop \_\_\_\_\_

Address \_\_\_\_\_


City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

My Distributor is: \_\_\_\_\_



**HOWARD W. SAMS & CO., INC.**  
INDIANAPOLIS, INDIANA 46206

# STOCK GUIDE

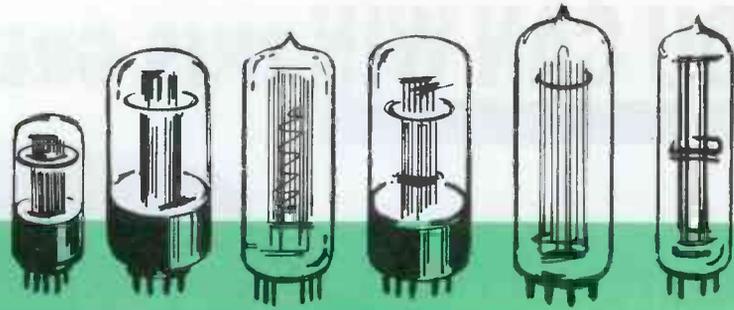

## for RADIO and Hi-Fi Tubes

The 30 tube types listed in the "Types Most Often Needed" column will handle the great bulk of your radio, phono, and tape-recorder replacement needs. However, the increasing popularity of FM radio, including stereo multiplex, has led to the use of several new tube types. These new types and those listed in the "Secondary Stock List" have appeared in enough models to be worth keeping in stock if you do a considerable volume of radio and audio servicing. The last

12 tubes listed in the secondary chart are found mainly in imported European equipment. American substitutes are listed where possible. Tubes used in both American and foreign equipment are listed according to the American type number, with the European designation also given. Tubes designated *MPX* are used in multiplex equipment; *MPX misc.* means a tube is used in more than one multiplex-circuit application.

Several special classes of tubes have been omitted from these listings:

1. Obsolescent radio tubes, used mainly in sets more than 10 years old or in portables.
2. Common TV tubes that are used only occasionally in radio and hi-fi circuits—for example, 6BN8, 6EW6, and 6EA8.
3. Tubes used exclusively in auto radios.
4. Tuning-eye indicator tubes.

### NEWLY INTRODUCED TYPES

5BC3	rectifier
6AJ8	IF amplifier
6AY11	Ratio detector and AF amplifier
6BC7	Ratio detector and AM detector
6BH6	MPX misc.
6BJ8	MPX misc.
6BN8	MPX misc.
6CW5/EL86	AF output
6D10	MPX misc.
6DT8	FM RF amplifier and converter
6EQ7	IF amplifier
6ER5	FM RF amplifier
6ER6	AF amplifier
6FQ7	AF amplifier
6GM5	AF output
6GQ7	MPX misc.
6GY8	FM mixer and oscillator
6HA5/EC900	FM RF amplifier
6HS6	IF amplifier
6J9	MPX misc.
6KL8	AM detector-AVC-FM limiter
6KV8	FM RF amplifier and converter
9EA8	MPX misc.
12JN8	FM RF amplifier and converter
12KL8	IF amplifier and AM detector
14JG8	FM detector and AF amplifier
18GD6	AM IF amplifier
19EA8	MPX misc.
19GQ7	FM detector and AM detector
19HR6	IF amplifier
19HV8	IF amplifier-AF amplifier-AM detector
19JN8	FM RF amplifier and converter
20EZ7	AF amplifier
25F5	AF output
25F6	AF output
35DZ8	AF output
45B5/UL84	AF output
50HK6	AF output
6973	AF output

### TYPES MOST OFTEN NEEDED

5Y3	rectifier
6AQ5	AF output
6AT6	AM detector-AF amplifier
6AU6	IF-AF amplifier
6AV6	AM detector-AF amplifier
6BA6	RF-IF amplifier
6BE6	AM converter
6BQ5/EL84	AF output
6L6	AF output
6V4/EZ80	rectifier
6V6	AF output
6X4/EZ90	rectifier
12AT6	AM detector-AF amplifier
12AT7/ECC81	AF amplifier
12AU6	IF-AF amplifier
12AU7/ECC82	AF amplifier
12AV6	AM detector-AF amplifier
12AX7/ECC83	AF preamp
12BA6	RF-IF amplifier
12BE6	AM converter
25C5	AF output
25EH5	AF output
25L6	AF output
35C5	AF output
35EH5	AF output
35L6	AF output
35W4	rectifier
50C5	AF output
50EH5	AF output
50L6	AF output

### SECONDARY STOCK LIST

5AR4/GZ34	rectifier
6AB4	FM oscillator
6AQ8/ECC85	FM RF amplifier and converter
6BJ6	FM RF or IF amplifier
6BL8/ECF80	MPX misc.
6BM8/ECL82	audio amplifier and output
6C9	FM RF amplifier and converter
6CA4/EZ81	rectifier

6EU7	AF preamp
6EZ8	FM mixer and oscillator
6GY8	FM mixer and oscillator
6JK8	FM RF amplifier and converter
12AL5	FM detector
12AQ5	AF output
12DT8	FM RF amplifier and converter
12EQ7	AM IF and detector
14GT8	FM detector and AF amplifier
17C9	FM RF amplifier and converter
17EW8/HCC85	FM RF amplifier and converter
18FW6	AM IF amplifier
18FX6	AM converter
18FY6	AM detector and AF amplifier
19T8	FM detector and AF amplifier
32E75	AF output
34GD5	AF output
36AM3	rectifier
50DC4	rectifier
60FX5	AF output
7025	AF preamp
7189A	AF output
7199	AF amplifier
7247	AF amplifier
7355	AF output
7408	AF output
7591	AF output
7695	AF output
EEA91	replace with 6AL5
EABC80/6AK8	AM-FM detector, AF amplifier
EBF89/6DC8	AM-FM IF, AM detector
EC92	replace with 6AB4
ECH81/6AJ8	AM converter, FM IF
ECL86/6GW8	AF amplifier and output
EF85/6BY7	IF amplifier
EF86/6Z67	AF preamp
EF89/6DA6	IF amplifier
EF94	replace with 6AU6
EL90	replace with 6AQ5
EL95/6DL5	AF output

# MISTER SERVICE DEALER:



## Make an Extra 12½% on your Replacement Speaker Purchases!

12½% EXTRA is a *big deal!* It's three times savings account interest . . . twice the yield of good bonds . . . more than the final net profit of many a business enterprise.

Worth while? You bet! And it's easy. Every time you install a JENSEN Viking replacement speaker you make not 40%, but 45% profit plus your labor charge. No extra cost to the customer—official list prices are very competitive . . . you benefit from a built-in better profit structure.

Quality? *Of course.* You and your customer know that the JENSEN label is synonymous with the best in hi-fi . . . with equipment on every fighting ship . . . major commercial aircraft . . . wherever the finest is important.

Can you afford *not* to use JENSEN Viking replacement speakers? Better see your distributor soon!

Write for Jensen Catalog 1090.


Nominal Size	Model No.	Magnet* Wt. Oz.	Imp. Ohms	List Price
3	3K7	.68	3.2	\$3.80
3½	35K7	.68	3.2	3.80
4	4K5	.55	3.2	2.90
4	4K7	.68	3.2	3.55
5	5K5	.55	3.2	3.25
5	5K7	.68	3.2	3.85
5¼	525K7	.68	3.2	4.35
6	6K7	.68	3.2	4.35
7	7W3	1.00	3.2	6.55
8	8W3	1.00	3.2	5.85
10	10J10	1.73	3.2	9.00
12	12J10	1.73	3.2	10.50

\*DP—Alnico 5 Magnets


Nominal Size	Model No.	Magnet* Wt. Oz.	Imp. Ohms	List Price
3x5	3X5K5	.55	3.2	\$4.10
4x6	4X6K7	.68	3.2	4.80
4x8	4X8W3	1.00	3.2	6.00
4x8	4X8W9	1.00	8-10	6.00
4x10	4X10W3	1.00	3.2	6.50
4x10	4X10W9	1.00	8-10	6.50
5x7	5X7W3	1.00	3.2	5.35
5x7	5X7W9	1.00	8-10	5.35
5x7	5X7V3	1.47	3.2	5.40
5x7	5X7V9	1.47	8-10	5.40
6x9	6X9W3	1.00	3.2	5.95
6x9	6X9W9	1.00	8-10	5.95
6x9	6X9V3	1.47	3.2	6.40
6x9	6X9V9	1.47	8-10	6.40

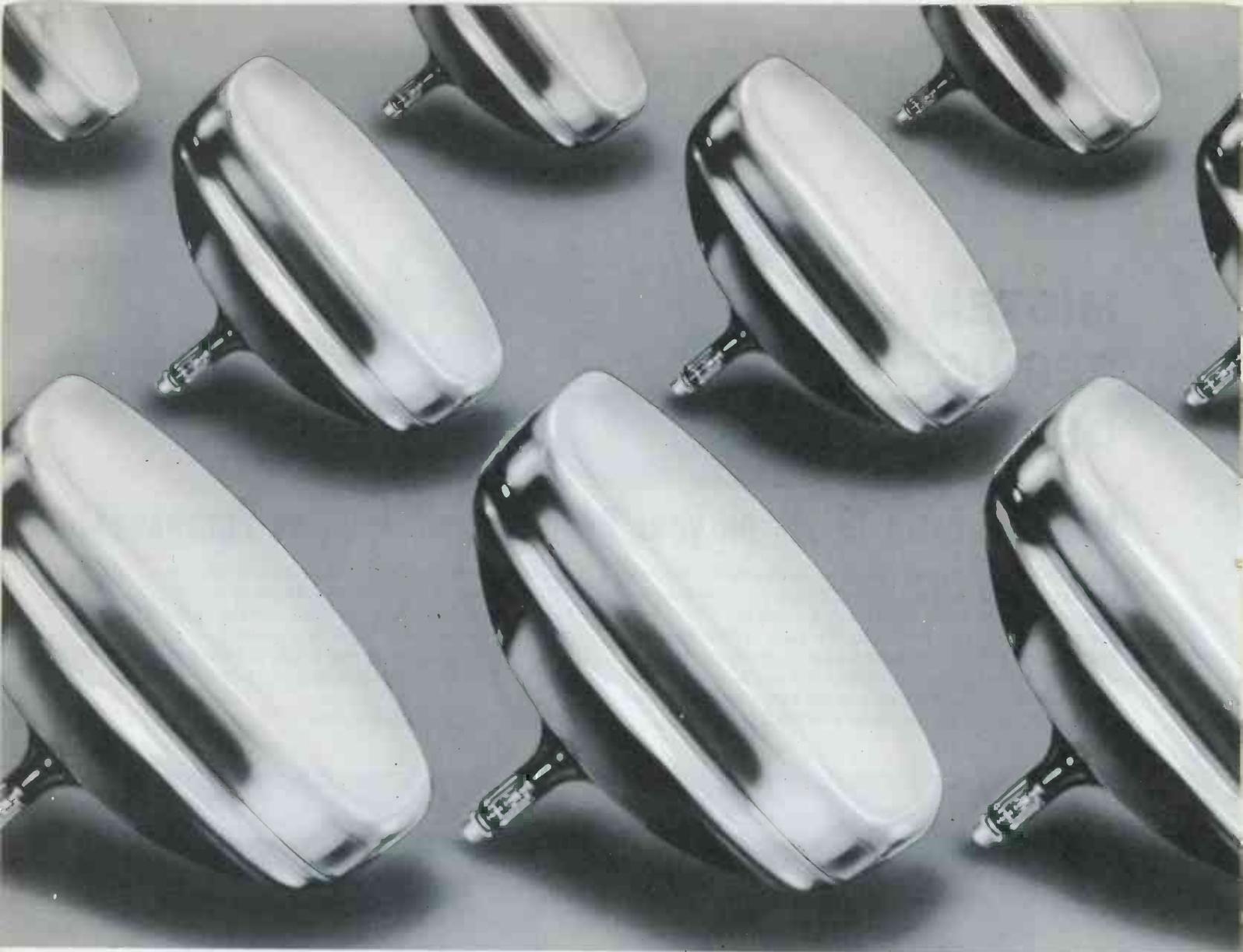JENSEN MANUFACTURING COMPANY / DIVISION OF THE MUTER COMPANY / 6601 SOUTH LARAMIE AVENUE, CHICAGO 38, ILLINOIS  
Canada: Radio Speakers of Canada, Ltd., Toronto • Argentina: Ucoa Radio, S. A., Buenos Aires • Mexico: Fapartel, S. A., Naucalpan, Mex.






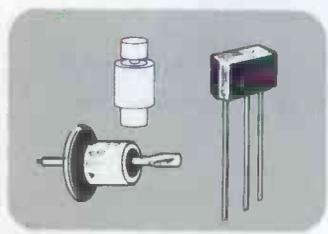
**THE QUALITY OF YOUR SERVICE DEPENDS ON THE PARTS YOU USE...DEPEND**



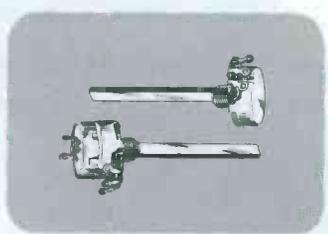
**Diodes, Rectifiers, Condensers and Resistors**  
Complete variety for all makes and models.



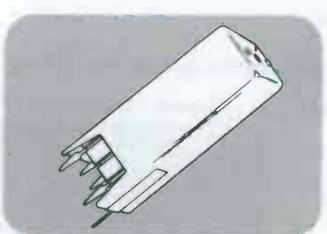**Universal Controls**  
With or without on-off switch. Standard taper, 3 inch shaft, half flat. 1 meg, 2 meg, 500 K. Complete selection. Fit Philco and other makes.



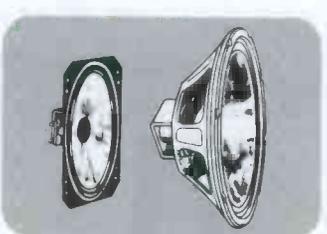**I.F. Transformers**  
For printed circuits, 4 lug, 5 lug or 6 lug types . . . to fit Philco or other makes. Dependable Philco Quality.



**Replacement Speakers**  
All sizes, round, oval or rectangular types. 3.2, 8, 16, 20 ohms. From tiny 1 3/4" to giant 15" sizes.



**Philco Receiving Tubes**  
To fit any make, any model TV or radio, manufactured to exact Philco standards, thoroughly inspected. Original factory cartons.



**Rotary Switch Antenna**  
High gain type with 6 position switch for best possible signal selectivity. 3 section brass dipoles. Padded cast iron base.



**Contact Cleaner**  
Philco TV and Radio Contact and Control Cleaner, Lubricant in self spray can, complete with protective cap and spray nozzle.



**Philco TV Yoke**  
Genuine Philco TV yokes, made to original factory specifications. Accurately wound and inspected. Packed in individual boxes, ready to install.

# There's a Philco Fully Stocked Parts Center Near You!

## IF YOU NEED A PHILCO PART...YOU CAN GET IT FAST...HERE'S WHY

1. Philco has a nationwide network of Parts distributors—THERE'S one in your area.
2. Philco distributors are backed up by Parts Warehouses with millions of dollars in Parts inventory.
3. NEW Parts for NEW Philco models are shipped automatically along with the NEW products.
4. All Parts orders are handled by experienced Parts specialists.
5. ALL EMERGENCY orders are transmitted over the nation's largest industrial communications system and processed within 24 hours.

Whatever you need—whenever you need it—if it's a Philco Part just dial your Philco distributor. He has thousands of Philco Parts right now on his shelves. If the item you need is temporarily out of stock—he can get it for you FAST. You may DEPEND on your Philco Parts distributor.


### Customer Confidence Begins When You Use Genuine Philco Star Bright 20/20 Picture Tubes

Every CR Tube you replace represents a high-dollar service sale for you . . . and your customer. Play it safe with a brand that's known for Quality . . . PHILCO. All material and parts used in the manufacture of Philco Star Bright 20/20 Picture Tubes are new except for the envelope, which prior to reuse, has been inspected and tested to the same standards as new envelopes.
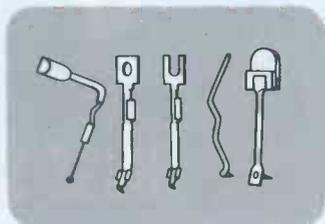
## ON YOUR PHILCO DISTRIBUTOR FOR ALL YOUR PARTS AND ACCESSORIES



**M62A 4-speed Record Changer**  
Intermixes all size records. Lightweight tone arm with retractable scratch protection assembly and famous Euphonics U8 cartridge. Changer ideal for built-in installations or "modernizing" record playing equipment. Template and instructions included.



**Philco Phono Needles**  
A complete selection of types and numbers for Philco and most all other makes. Carefully made, attractively-packaged. ALL TIP TYPES and sizes, including Diamond. Special now available—"THE BIG 18 KIT." This attractive compact metal case contains 18 of the industry's fastest selling needles.

### Your Philco Distributor Features These Famous Makes

PHILCO • PHILCO-Bendix • CROSLEY • EVEREADY Batteries and Flashlights • CAROL Cables • GOODRICH V-Belts • GC Products • AUDIOTEX • WALSCO Products • COLORMAGIC Antennas • PRECISION Test Equipment • SPRAGUE Capacitors

**Philco Parts are Available Through a nationwide network of Parts Distributors. Mail the Coupon Today for the Name of the One Nearest You.**



PARTS AND SERVICE OPERATIONS

# PHILCO®

A SUBSIDIARY OF *Ford Motor Company*

**Philco Parts & Service Operations**  
C & Tioga Streets, Phila. 34, Pa.

I am interested in receiving information about special Philco Parts offers, prices and facts. Please send me the name of the nearest Parts distributor.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

**VISUAL  
INDICATING**

**BODY SIZE  
ONLY  
.145 x .300  
INCHES**

## **BUSS Sub-Miniature PIGTAIL TRON FUSES**

For use on miniaturized devices,— or on gigantic multi-circuit electronic devices.

Glass tube construction permits visual inspection of element.

Smallest fuses available with wide ampere range. Twenty-three ampere sizes from 1/00 thru 15 amps.

Hermetically sealed for potting without danger of sealing material affecting operation. Extreme high resistance to shock or vibration. Operate without exterior venting.

# **BUSS**

Write for BUSS  
Bulletin SFB

BUSSMANN MFG. DIVISION, McGraw-Edison Co., St. Louis, Mo. 63107

### **Mustang Contest**



Gail S. Carter, executive secretary of National Electronic Distributors Assn. (NEDA), will draw the names of PHOTOFACT® "Win-A-Mustang" contest winners on January 15, 1965. Top prizes in the contest, sponsored by the Distributor

Div. of Howard W. Sams & Co., Inc., and which ends December 31, 1964, will be two new Ford Mustangs. Open to both distributors and PHOTOFACT users, the contest prizes also include two mink stoles and two ladies' diamond Elgin wristwatches.

### **NARDA School of Management**

Service managers and operators of service firms from 23 states met in September at Chicago's Allerton Hotel to concentrate on making their operations more efficient and more profitable. They spent at least two days studying financial statement analysis and productivity, how to set service rates and procure contract business, advertising, and record keeping. This group was participating in the 7th Annual NARDA School of Service Management.

The concern of good managers with productivity of their service technicians was covered by L. A. Porter, manager of field service, Whirlpool Corp. Porter related that experience shows an average of one hour is lost each day just in getting ready for the day's work—receiving work assignments, checking out parts, asking technical questions, or discussing bowling scores. Another area of lost time is in travel. With just ten minutes spent between calls, at least another hour a day is lost. Similarly, ten minutes lost because of lack of technical ability can amount to an hour or more a day. Among solutions proposed were careful assignment of work on the part of the manager, careful attention to the call-making procedure, and

## **BUSS: 1914-1964, Fifty years of Pioneering....**

### **Electronic Scanner**

*(Continued from Page 18)*

#### **UHF Seminar**



A special UHF-TV seminar for Ohio dealers was held by Gavin Instruments, Inc., to preview the introduction of Channel 22, WKEF-TV, to the Dayton market. According to Robert McDonald, Gavin sales manager, participating dealers were provided with a complete "UHF-TV Profile." This included technical data, programming material from WKEF-TV

director George Mitchell (right), and a training session on UHF equipment and installations. Additional seminars are planned by McDonald and his staff.

#### **Research Center**

Research and advanced development facilities are being established in the Ft. Lauderdale area by Astatic Corp. In announcing the move, James Ross, chairman, said, "Astatic fully realizes that, to maintain its leadership in the field of acoustics, it must reinforce its technical effort by establishing applied research and advanced development facilities. For this, Astatic needs more than ever to attract highly skilled and qualified technical personnel. Such people are concentrated in electronic centers, one of which is in the vicinity of Cape Kennedy, Florida. A location slightly removed from Cape Kennedy, to get away from the merry-go-round atmosphere prevailing at the Cape, appears most attractive to serious-minded research workers. After conducting an investigation of available facilities, Astatic has concluded that the Ft. Lauderdale area offers all that is required."



**Actual Size**  
Only 1-5/8 inches long...  
Extends just 29/32 inch  
behind front of panel

## **BUSS Space Saver Panel Mounted Fuseholder**

- Fuseholder takes 1/4 x 1 1/4 inch fuses. Converts to 5/32 x 1 1/4 inch fuses simply by changing screw type knob. Holder is rated at 30 ampere for any voltage up to 250.
- Also available in military type which meets all requirements of MIL-F-19207A.

# **BUSS**

Write for BUSS  
Bulletin SFH-10

BUSSMANN MFG. DIV., McGraw-Edison Co., ST. LOUIS, MO. 63107

Circle 12 on literature card

# BLOCKS for BUSS FUSES



**SOLDER  
TERMINALS**

**SCREW  
TERMINALS**

Above standard types available in any number of poles—  
From 1 to 12... plus other types for every application....

# BUSS

Write for BUSS  
Bulletin SFB

BUSSMANN MFG. DIV., McGraw-Edison Co., ST. LOUIS, MO. 63107

In discussing "What the Service Manager Should Know About Financial Statement Analysis," Jules Steinberg, executive vice president of NARDA, presented the A-C-O formula as a means of "guesstimating" the proper percentage of costs to be spent for advertising. "It is a simple rule of thumb," explained Steinberg. "The 'A' represents advertising, and 'C' the cost of selling, while 'O' represents cost of occupancy. These three expense factors should equal one-half your gross profit margin. If your gross margin is 25%, then rent, plus selling expense (salaries, commissions, promotions), plus advertising, should equal 12½% of total sales."

## "Sell Service" Campaign



Radio, television, and phonograph service dealers in the Indianapolis area have been asking customers "What else needs fixing?" during a local tryout of an Electronic Industries Assn.-sponsored program to promote servicing and boost sales of replacement parts. The

test run of the "sell service" program, brainchild of the EIA Distributor Products Div., involves Indianapolis distributors of replacement parts, who are urging service dealers to remind their customers that other radios, TV sets, or phonos lying unplayable about the house can be restored to working order through servicing. The distributor-dealer and dealer-customer persuasive efforts are backed by printed materials including lapel buttons and pocket protectors for salesmen and servicemen, self-sticking signs (photo) for shop windows, trucks, and tube caddies, and store banners for distributors. Based on weekly reports of the 13 distributors aiding in the Indianapolis test, EIA will decide shortly whether to extend the campaign nationwide. ▲

## ... New Developments in Electrical Protection

insuring that service trucks are equipped with the proper tools and parts to avoid costly callbacks.

"How To Establish Service Charges That Are Fair to the Consumer and Fair to Yourself," was the subject of an address by John Borlaug, national service manager, Sylvania Home and Commercial Products Corp. He explored advantages and disadvantages of pricing service by the hour and of flat-rate pricing. "Time spent in checking a circuit if you do not know what the circuit is supposed to do is time wasted. Don't charge your customer an hourly rate while your technician is learning how the circuit works—use flat rate charges tempered by local conditions. If you already know how the circuit works, your hourly rate applies and is fair to both you and your customer."

One of the more interesting facts learned at the School was that interest in service contracts is growing. More than twice as many of the attending service managers are now selling contracts, compared with those selling contracts last year and every man in the room except one expressed avid interest in the subject.

Through the years, recordkeeping has been a featured subject at the School of Service Management. This year, the subject was presented by dealer Ed Reich, president, Wholesale Television Service, Indianapolis, Ind. He pointed out that the key to efficiency is to know where everything is at all times. This is done basically with two forms, the job envelope and the order form. A 5" x 8" envelope is given to each serviceman in the morning, containing his assignments arranged in the order in which the calls are to be made. The front of the envelope provides space to list the job number, the name of the account, the time the call was made, the type of call (whether cash, charge, or contract), and the disposition of the call (whether customer-not-at-home, completed, or brought into shop). Finally, space is provided for listing the money collected. On the reverse side of the envelope, there is space for recording inventory usage during the day.

GMW FUSE  
and HWA  
FUSEHOLDER

FUSE SIZE  
ONLY .270 x .250  
INCHES

**BUSS**  
VISUAL  
INDICATING



## Sub-Miniature FUSE-HOLDER COMBINATION

For space-tight applications. Fuse has window for inspection of element. Fuse may be used with or without holder.

Fuse held tight in holder by beryllium copper contacts assuring low resistance.

Holder can be used with or without knob. Knob makes holder water-proof from front of panel.

Military type fuse FM01 meets all requirements of MIL-F-23419. Military type holder FHN42W meets all military requirements of MIL-F-19207A.

# BUSS

Write for BUSS  
Bulletin SFB

BUSSMANN MFG. DIVISION, McGraw-Edison Co., St. Louis, Mo. 63107

Circle 12 on literature card

**MAKES MORE . . . AND MORE  
ACCURATE TESTS THAN ANY SERVICE TUBE TESTER EVER BUILT.**

**TRIPLE SHORTS  
SENSITIVITY  
TESTS**

**TESTS  
HEATER CURRENT  
ON SERIES  
TUBES**

**TRUE  
RECTIFIER  
TEST**



**DYNAMIC  
TEST FOR  
EYE TUBES**

**TESTS  
REGULATOR &  
REFERENCE  
TUBES**

**231  
HEATER  
VOLTAGES**

**New Tube Test Data Issued Regularly - Keeps You Up To Date  
Between Roll Charts - No Charge !**

### **JACKSON MODEL 658A DYNAMIC OUTPUT TUBE TESTER**

*DYNAMIC OUTPUT PRINCIPLE* - A sensational improvement on the time tested Jackson principle. In the dynamic output test, variable D.C. bias voltage, plus variable A.C. signal voltages are applied to control grid. Variable D.C. voltage is applied to the plate and screen. The metering circuit a low impedance bridge type, then reads only the A.C. component of the plate current. Obviously this is the most valid kind of test for amplifiers, it considers the entire output curve of the tube, not just a small portion.

This principle coupled with the many Jackson features make this tester the biggest dollar value in the business.

DEALER NET **\$234<sup>95</sup>**

**See Your Franchised Distributor and See This One for Yourself -  
While You Are There, Ask About a Trade-In Deal**



### **Jackson model 805 Vacuum Tube Voltmeter**

Features Taut Band Suspension Meter, taut band suspension eliminates pivots and jewels, eliminating pivot friction and error due to pivot fall-over. No movement springs, spring set or hysteresis eliminated. May be operated in any position without degrading performance and is four times more sensitive than conventional movements. Also features static free face, burn out proof meter and direct probe.

DEALER NET **\$79<sup>95</sup>**


**"Service Engineered Electronic Test Equipment"**



The Jackson Electrical Instrument Company Dayton, Ohio

Circle 13 on literature card

Nuvistor RF Amplifier

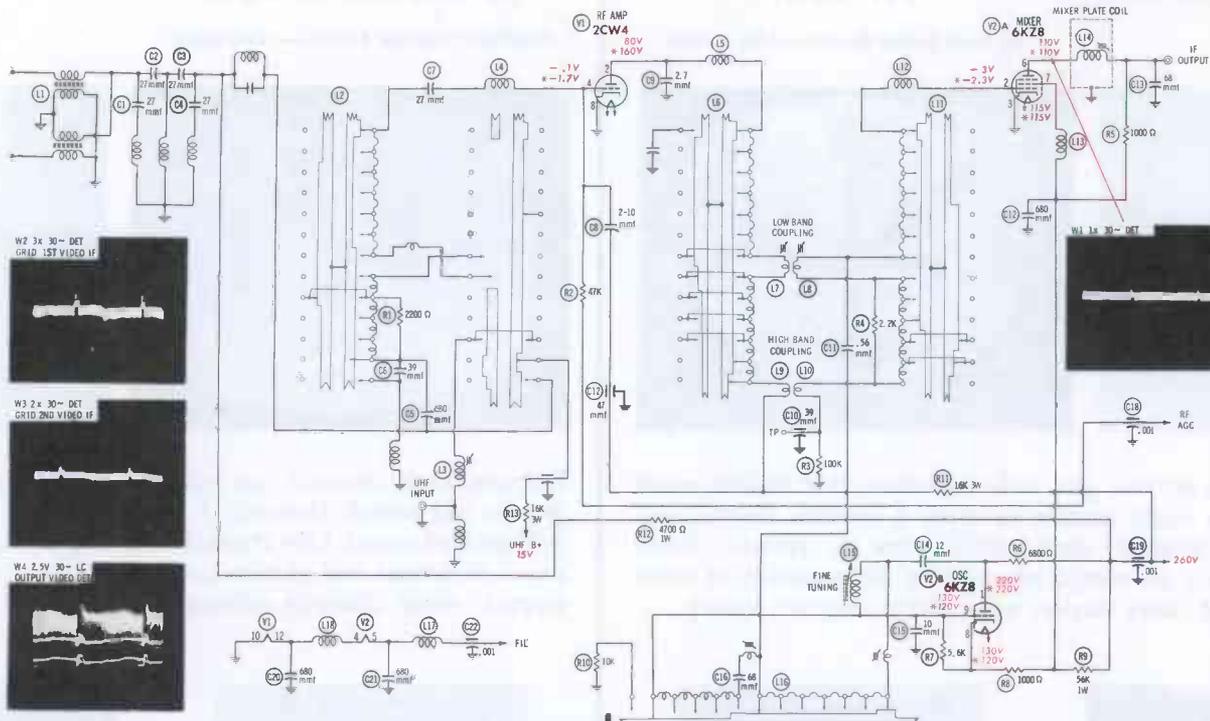

DC VOLTAGES taken with VTVM, on inactive channel; antenna terminals shorted. \*Indicates voltages taken with signal present—see "Operating Variations."

WAVEFORMS taken with wideband scope; TV controls set for normal picture. DET (detector), LC (low-cap), and DP (direct) probes are used where indicated.

Normal Operation

Switch tuner depicted above (from RCA Chassis KCS143F) features two improved tube types. A 2CW4 nuvistor functions as RF amplifier; its most notable improvement over other tube types is in signal-to-noise ratio. The 2CW4 has an all-metal case, very small heater and plate-power requirements, and controlled filament warmup time that especially suits it for series filament strings. Mixer-oscillator stage uses 6KZ8. Pentode section, used as mixer, has frame-grid construction and exceptionally high gain—approximately four times greater than that of 6EA8 or comparable type. Oscillator and mixer sections are connected in stacked B+ arrangement (leading to some unusual voltage symptoms); cathode voltage of oscillator section is applied directly to mixer plate and screen; R8-C12 decouple the two stages for RF signals. R9, between mixer supply and B+, helps compensate for any slight variation in oscillator cathode voltage, thus keeping voltage on mixer constant. Tuner is equipped for UHF reception; R10 disables VHF oscillator when channel selector is in UHF position. Signal path of this tuner is similar to turret tuner in August 1964 *Symfact*. Preset fine tuning is used here but does not mechanically adjust individual oscillator slugs; rather, it changes inductance of fine-tuning coil by sliding core in or out of coil form. Core in this arrangement is somewhat prone to break or become disconnected, disabling fine tuning; if this occurs, visual inspection of coil will reveal trouble.

Operating Variations

- PIN 4 V1** DC voltage is determined by AGC action and signal strength. Voltage varies from  $-0.1$  volt to  $-3.5$  volts, depending on AGC setting and strength of station signal.  $-1.7$  volts is typical.
- PIN 2 V1** Plate voltage changes as grid bias varies—goes more positive as bias goes negative. Without signal, voltage is 80 volts; with strong signal, increases to 200 volts. 160 volts is normal on plate of nuvistor.
- PIN 2 V2** Without signal, grid reads  $-3$  volts; with signal, varies from low of  $-2$  volts on strong station to high of  $-3$  volts on fringe stations. Reads  $-2.3$  volts with average signal.
- PIN 1, 8, 9 V2** Small difference in voltages with or without signal; practically no change on pin 1 (plate). Voltages on 8 and 9 decrease 10 volts with signal on mixer.
- WAVEFORMS** W1, W2, W3 are taken at mixer plate and in video-IF strip. Amplitude is small, but signal can be seen, evidenced by vertical sync pulses. Designation 2x, etc., indicates waveform amplitude compared with 1x amplitude of W1. W4 appears at video-detector output and amplitude depends on signal strength.

## Picture Snowy

Fringe Channels Missing

### SYMPTOM 1

#### R11 Open

(RF Plate Supply Resistor—16K, 3 watt)


#### Symptom Analysis




Strong stations give little indication that trouble exists—only slight amount of snow is present. Normal stations produce considerable snow in picture; fringe channels are completely missing. RF amplifier in tuner is most likely suspect when picture appears snowy.
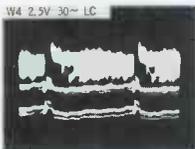
#### Waveform Analysis

Amplitude of signal at video-detector output (W4) is normal, but considerable snow ("grass") can be seen. Proves trouble is before video stages, in either IF strip or tuner. Loss of signal in W2 (first IF grid) proves trouble is prior to this point. Missing signal at mixer plate (W1) strongly indicates defect in tuner. Scope will not pinpoint defective component but is definite time-saver in isolating faulty tuner as most likely culprit.



#### Voltage and Component Analysis

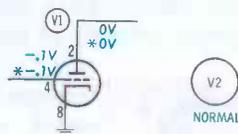

Grid voltage on RF amplifier remains same with or without signal—proves there is no AGC voltage developed. Loss of plate voltage on V1 explains snowy picture—RF amplifier can't conduct. Gain in mixer and IF amplifier stages is sufficient to produce picture on normal or strong stations. Loss of RF amplification lowers signal-to-noise ratio in later stages thus causing snow (noise) in picture. Noise generated in RF and mixer stages, with little signal to override it, is amplified in high-gain IF stages.

**Best Bet:** VTVM will locate trouble.

## High Channels Lost


Sound Also Missing

### SYMPTOM 2

#### R8 Increased in Value

(Oscillator Cathode Resistor—1000 ohms)



#### Symptom Analysis

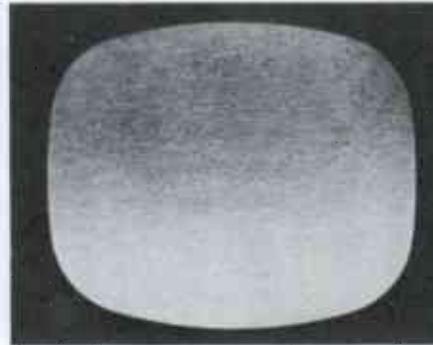


Extreme high channels are completely missing both picture and sound; channels 7, 8, and 9 very snowy with garbled sound. Low channels only slightly affected; sound is normal and picture has some snow. Tuner is suspect—some channels missing, some present.
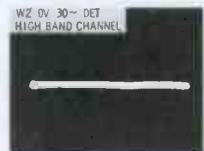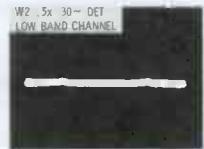
#### Waveform Analysis

With tuner on low channel, W2 shows some signal is passing tuner but amplitude is decreased considerably (compare to normal W2). With tuner on high band channels, W2 shows complete absence of signal. Scope is conclusive in isolating tuner. Oscillator stage is most logical point for voltage and resistance checks, as channels aren't affected equally. Oscillator defects are commonly more noticeable when tuned to high channels.



#### Voltage and Component Analysis

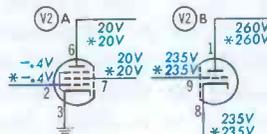

Voltages are incorrect on oscillator (V2B) with or without signal. All elements show increased readings, and there is only 25 volts between plate and cathode (normal is 100 volts), so oscillation has almost stopped. Plate and screen voltages on mixer stage (V2A) are greatly lowered, because resistance of their B+ supply path has increased—majority of small mixer current now flows through relatively high valve of R9 (56K). Lack of oscillator injection reduces mixer grid voltage enough to lower plate voltage even further to 20 volts.

**Best Bet:** VTVM for voltage and resistance.

## No Sound—No Pix


Only Slight Snow in Raster

R6 Increased in Value

(Oscillator Plate Supply Resistor—6800 ohms)

### SYMPTOM 3

#### Symptom Analysis

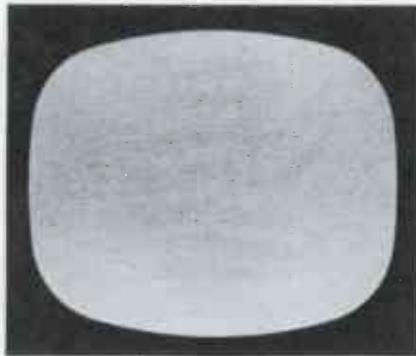


Only indication on screen is very slight amount of snow, whether tuned to active or inactive channel. Only sound heard from speaker is background noise. Clamping AGC line doesn't improve condition. Trouble could be in either IF amplifier stages or tuner.

#### Waveform Analysis

Trouble in stages following grid of second IF amplifier can be rapidly discounted by viewing waveform at grid (W3)—no signal is present. Further clue to tuner trouble is provided by W2 (first IF grid); no signal here, either. Absence of signal at mixer plate (W1) probably means tuner is defective. When symptoms indicate possibility of tuner trouble, this sequence of scope checks isolates tuner more rapidly than does VTVM.



#### Voltage and Component Analysis

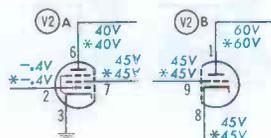

Oscillator plate voltage only 60 volts (normally 220) provides definite clue to trouble in oscillator supply circuit. Grid and cathode voltages on oscillator are also decreased, as are mixer plate and screen voltages. However, these are effect of trouble—not cause. With exceptionally high-gain 6KZ8 in mixer stage, it is possible and probable to get a picture with lowered voltages. Amount of increase in value of R6 determines exact symptoms—just a slight increase may produce snowy picture on some channels while others remain normal.

Best Bet: VTVM will find this one.

## Snow in Picture

Loss of Fringe Channels

L1 Open

(Antenna Coils—Balun)

### SYMPTOM 4

#### Symptom Analysis




Strong local stations show little evidence of trouble being present. Stations with mediocre signal strength are quite snowy; both picture and sound are missing on fringe channels. Symptom is typical of failure in RF amplifier stage or antenna input network.

#### Waveform Analysis

Observing signal at grid of first IF amplifier provides valuable assistance in locating trouble in tuner. W2 (taken on strong local station) shows signal is passing tuner but amplitude is reduced—compare to normal W2. With receiver on fringe channels, W2 shows complete loss of signal. Even with antenna coils open, strong stations appear normal because of excellent amplification and signal-to-noise ratio in nuvistor stage.



#### Voltage and Component Analysis

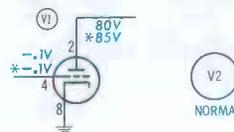

Pinpointing defective component from voltage readings is difficult. Without signal, all voltages are normal—thus eliminating suspicion of source voltage or plate supply resistor. Voltage stability also rules out probability of AGC defect. With information gained from above voltage measurements, it is logical to assume trouble is in signal path; best place to start looking is prior to grid of RF amplifier. If trouble is reported within few days after thunderstorm, antenna balun is certainly most likely suspect.


Best Bet: Ohmmeter and visual inspection.



*you get* **PRODUCT PLUS** *from your Sylvania Distributor*

# Suddenly

**COLOR TV  
HAS A NEW  
RED STANDARD**

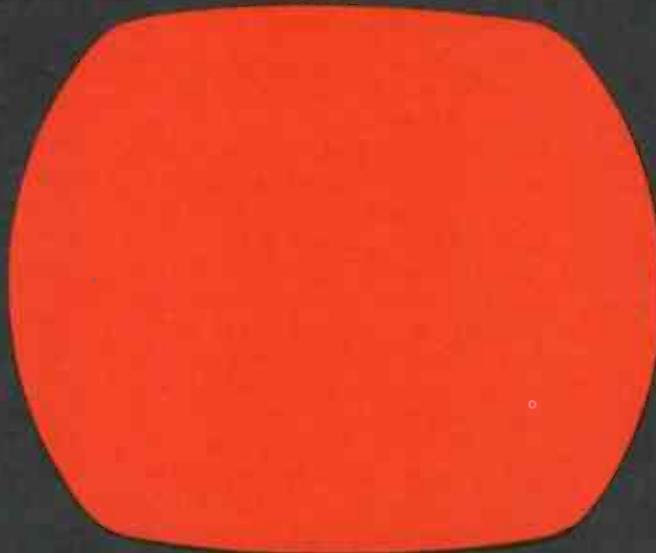

Sylvania's new **EUROPIUM RED**.

**New COLOR BRIGHT 85 picture tube brings more natural color to television and increases monochrome brightness 43%.\***

The startling news in the television industry is Sylvania's new picture tube, and its new, truer red phosphor.

EUROPIUM RED, developed at GT&E Laboratories, is the brightest red known to the industry. And, to match it, now the full brightness of blue and green is used. The result is a color picture tube that gives the entire television industry a boost.

Because the COLOR BRIGHT 85 tube is *really* bright, dealers can demonstrate color TV effectively in normally lighted showrooms. As the set's brightness is adjusted, the colors remain true—not shifting to unnatural tones in the highlights of the picture.

Another thing, black and white performance is far better than you've ever seen before in a color tube. Be-

sides the increased brightness, there's improved contrast in a sharp, vivid picture.

The new, exciting COLOR BRIGHT 85 picture tube is a product plus from Sylvania for the entire color television industry, and particularly for dealers. In color, as in black and white, you know it's good business to handle the Sylvania line.

**SYLVANIA**  
SUBSIDIARY OF  
**GENERAL TELEPHONE & ELECTRONICS** **GT&E**


NEW CAPABILITIES IN: ELECTRONIC TUBES • SEMICONDUCTORS • MICROWAVE DEVICES • SPECIAL COMPONENTS • DISPLAY DEVICES

\*Tests show the COLOR BRIGHT 85 tube is 43% brighter, on the average, than standard color picture tubes.

Circle 14 on literature card

December, 1964/PF REPORTER 31

# Measuring

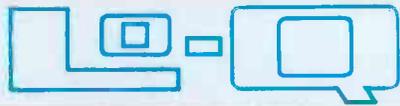

# INDUCTANCES

Another use for your bench scope.

by Robert G. Middleton

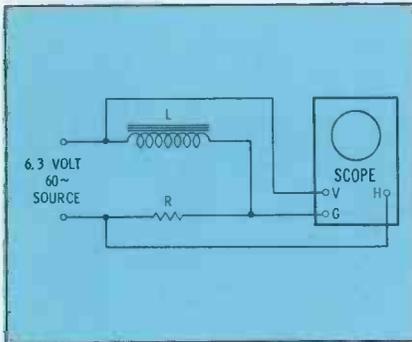


Fig. 1. Setup for impedance checks.

In a previous issue of PF REPORTER (March 1963), detailed information was given for testing medium- and high-Q inductors by "ringing." It was pointed out, however, that low-Q coils are often difficult to check with a scope, because the waveform is damped-out too quickly to be useful. Scope evaluation of low-Q inductors requires a different method.

## Low-Q Measurement

A suitable test setup for displaying an impedance waveform that can be used to check low-Q inductors is shown in Fig. 1. The inductor under test is seen at L; resistor R is any fixed-value resistor that provides ample horizontal deflection voltage. In general, high-impedance inductors should be tested using a high value of resistance, because less current will flow.

What do impedance patterns look like? Three basic types are illustrated in Fig. 2. If the inductor "looks like" a resistor at 60 cps, a diagonal line is displayed on the scope screen. On the other hand, an ideal inductor (with no winding resistance) would display a perfect circle when the vertical and horizontal gains are equalized. Most coils, of course, have appreciable inductance and resistance and display an elliptical impedance pattern.

### Reading the Pattern

Evaluate the impedance pattern using the procedure shown in Fig. 3. Center the waveform on the screen, using centering and gain controls, so it extends an equal number of squares up and down, and left and right, from the screen center-point. Any convenient settings of the scope's vertical and horizontal gain controls can be used. Now, count the number of squares from the center to the point at which the ellipse intersects the vertical axis—seven in Fig. 3. Also note the number of squares from the baseline to the top of the pattern—ten in Fig. 3. These two readings give the ratio of reactance to impedance. The ratio  $X_L/Z$  in Fig. 3 is  $7/10$ . ( $X_L$  = reactance, and  $Z$  = impedance.)

### Finding the Inductance in Henries

Of course, the information thus determined is comparatively useless

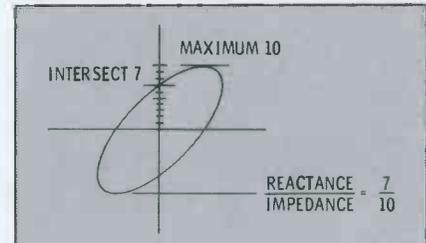


Fig. 3. Ratio of reactance-impedance.

from the servicing standpoint, because a technician generally desires to know the inductance of a particular coil. The inductance in henries is found by using an impedance triangle constructed as follows: First, draw a right angle on a sheet of paper, as shown in Fig. 4 (or linear graph paper could be used). Mark off seven units on the vertical axis. This leg corresponds to the seven squares (reactance) which were read on the scope screen. Next, mark off a 10-unit hypotenuse, as shown by the dotted line in Fig. 5. This is done most easily with a compass, although a ruler can be used. This completes the impedance triangle. The 10-unit leg corresponds to the 10 squares (impedance) which were read on the screen. The completed triangle shows the relative ohmic values of resistance, reactance, and impedance.

A numerical reference is obtained by measuring the winding resistance of the inductor with an ohmmeter. Since the resistance at zero fre-

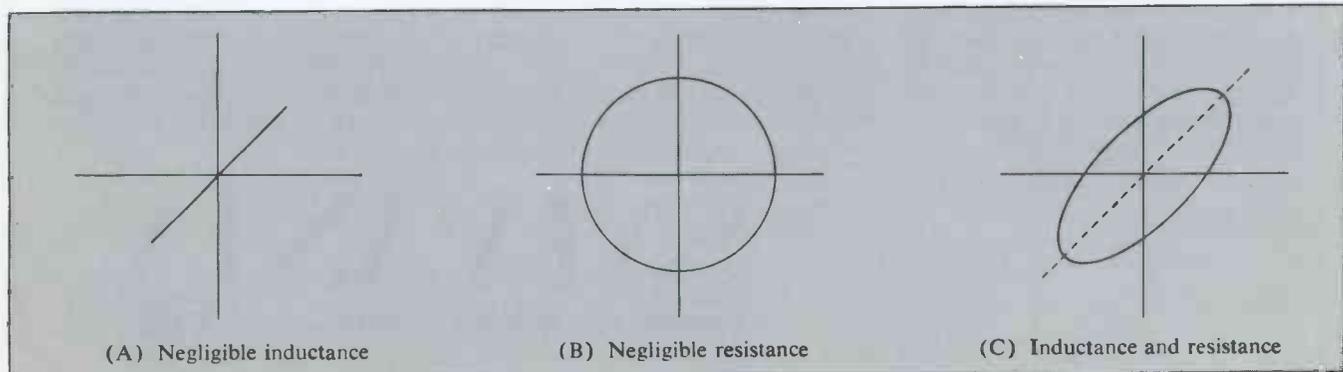


Fig. 2. Three basic types of impedance waveforms.

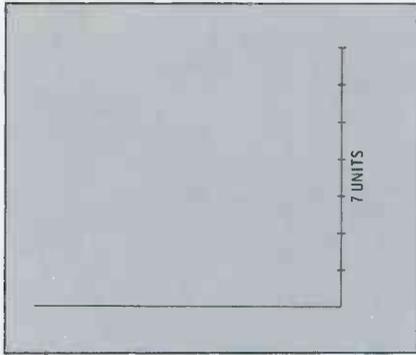


Fig. 4. Units indicate coil reactance.

quency is virtually the same as at the 60-cps frequency of the source voltage in the test setup, this is the easiest method of completing the data. If a value of 50 ohms is measured, assigning the value of 50 ohms to the base (resistance) leg of the triangle will establish the reference; the other values can then be determined. In this example, the reactance line has the same length as the resistance line—hence, the coil in question exhibits 50 ohms of inductive reactance. Since, in a right triangle, the hypotenuse squared equals the sum of the squares of the other two sides, the impedance line (hypotenuse) gives a value of 70.7 ohms. ( $50^2 + 50^2 = 2500 + 2500 = 5000$ ; therefore, the hypotenuse is  $\sqrt{5000}$ , or 70.7.)

The inductance of the coil can be determined from the reactance value of 50 ohms. Simply divide the inductive reactance by 377 ( $2\pi$ , or 6.28, times the 60-cps line frequency;  $X_L = 2\pi fL$  and  $L = X_L/2\pi f$  to find the inductance in henries;  $50/377 = .132$  hy, or 132 mh. With this straightforward procedure, it is easy to find the inductance, impedance, and reactance of any inductor using only its scope pattern.

#### Finding the Power Factor

The power factor of a coil is simply  $R/Z$ , or resistance divided by impedance. In the example of Fig. 6, the power factor is  $50/70.7$ , or .707. In general, the power factor will approach 1 if the inductance is negligible; on the other hand, the power factor will approach zero if the resistance is negligible.

#### Finding the Q Value

In case you wish to know the Q of the inductor, divide the reactance by the resistance ( $Q = X_L/R$ ). In the example of Fig. 6, Q is 1; in other words, this is a very low-Q

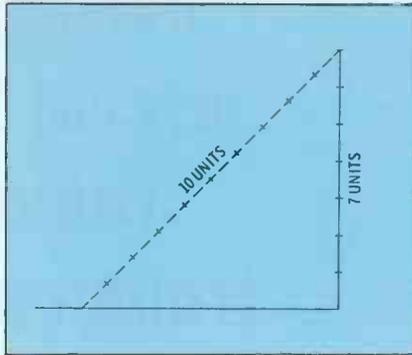


Fig. 5. Hypotenuse shows impedance.

coil. Different inductors have widely varying Q values. If the resistance is negligible, the Q will approach an infinite value. On the other hand, if the inductance is negligible, the value for Q will approach zero.

#### Practical Considerations

Returning to Fig. 1, note that the AC source must be ungrounded to apply voltage across the resistor to the horizontal-input terminals of the scope. Hence, it may be necessary to use the heater winding of a small power transformer as a voltage source. An audio oscillator with ungrounded (balanced) output will also provide a good test voltage. The chief advantage of an audio oscillator is that it can be expected to have a good waveform, while the 60-cps signal from the power line is not always a pure sine wave.

It is essential to drive the test setup with a uniform sine wave; otherwise, the pattern will have the "bends" seen in Fig. 7, and proper evaluation of the waveform will be difficult. Most inductors will display an undistorted pattern when the source voltage exhibits a good waveform. However, there are exceptions—sometimes the core material in the inductor under test is poor. For example, core laminations may induce excessive hysteresis losses that will introduce an odd-harmonic

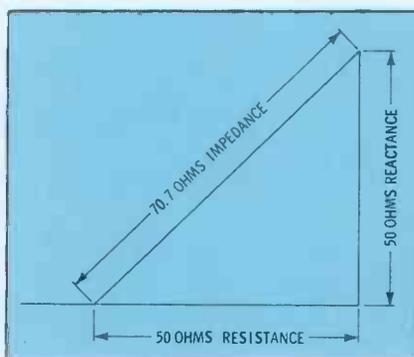


Fig. 6. Complete impedance triangle.

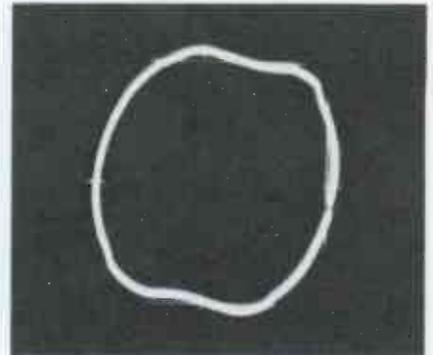


Fig. 7. Trace of distorted sine wave.

distortion into the current waveform (applied to the horizontal-input terminals of the scope). This distortion is commonly called an "iron third harmonic." Such inductors cannot be checked accurately by the method described earlier, if the iron third harmonic is large.

Technicians using a scope to check inductors for the first time may encounter distorted patterns due to overloading and clipping, as illustrated in Fig. 8. To avoid this difficulty, adjust the step attenuator to as low a setting as possible and operate the continuous attenuator at as high a setting as possible. This prevents overdriving the input cathode-follower stage of the scope. In case the horizontal channel in your scope does not have a step attenuator, avoid overload by not exceeding a reasonable input voltage to the horizontal-input terminals. Choose the value of R in Fig. 1 that permits operation of the horizontal-gain control at a fairly high setting.

Most scopes, barring circuit defects, have good 60-cps response in both vertical and horizontal amplifiers. To be sure, make the test depicted in Fig. 9; a straight diagonal line should be displayed. On the other hand, an elliptical pattern (as shown) indicates a phase shift between the scope amplifiers, which

• Please turn to page 68

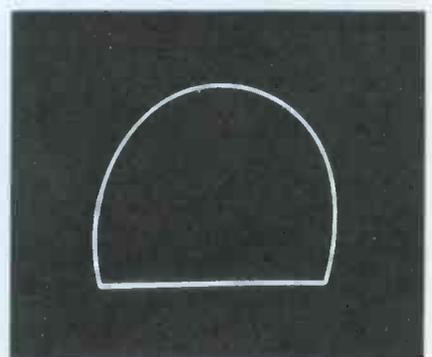


Fig. 8. Vertical amplifier overloaded.

In the first part of this series, aircraft communication systems were discussed. In this concluding part, the most widely used radio navigation systems will be described.

### Automatic Direction Finders

The primary airborne LF device today is the automatic direction finder, or ADF. Fig. 1 shows a typical ADF system such as might be found aboard a light business aircraft.

The ADF system shown consists of a carefully designed ferrite loop antenna and a sense antenna. Signals from these two antennas are combined in such a manner as to cause a servo to rotate the loop to a null. An indicator shows the direction of the loop, thus indicating the heading to any LF or broadcast station. Above the broadcast band, the reflection of sky waves makes ADF impractical. A great disadvantage of the low-frequency band is the presence of large amounts of atmospheric noise, particularly during electrical storms, and it is during stormy weather that aviation radio is most necessary.

### VHF Omni-range

At the close of World War II, the sudden increase in air traffic resulted in studies to originate more effective means of radio navigation. The four-course low-frequency range systems ("beams") in use at that time were inflexible and subject to atmospheric noise under adverse weather conditions.

Shortly after World War II, a radio navigation system utilizing VHF was developed. This modern system is called "very high frequency omnirange," sometimes termed "VOR" or just "omni." The system is used throughout the world

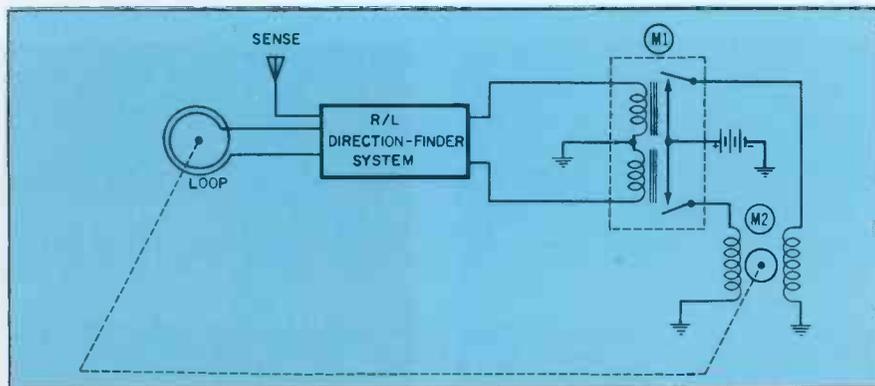


Fig. 1. Diagram of simple automatic direction finder system.

# curing aircraft radio troubles

Part 2



Fig. 2. VHF omnirange ground station.

except in the Iron Curtain countries. With this system, using a good omni receiver, a pilot may determine his bearing from an omni ground station within two degrees.

### Principles of Operation

To understand the principle of omnirange, imagine a beacon light arranged to rotate at constant speed. Another light is arranged to flash in all directions whenever the beacon points exactly north. By knowing the time required for a full rotation of the beacon and by observing flashes of the fixed light, an

observer can determine his direction relative to the beacon.

The same principle can be applied to radio emissions. An omni ground station consists of an antenna system arranged to rotate a directional beam at 1800 rpm, or 30 revolutions per second. Thus, an observer located at any point will receive from this antenna a signal that appears to be amplitude modulated by a 30-cps tone. Another antenna radiates a reference signal uniformly in all directions. This reference signal contains a 30-cps signal that is in phase with the signal from the rotating beam only when the directional antenna points north of the station. The phase relationship between the two signals is different for each other point of the compass.

The reference signal must be radiated in some manner which will not interfere with the rotating pattern signal. This is done by amplitude modulating the station carrier with an audio signal at a frequency of 9960 cps. This subcarrier is then frequency modulated by the 30-cps reference signal.

A VHF receiver in the airplane receives the sum of all modulation components from the ground station. Voice modulation is used for identifying the particular station, for weather broadcasting, and for communication with other airplanes; this voice modulation doesn't affect performance of the omni as a navigation device.

An omnirange ground station is shown in Fig. 2. These stations operate unattended and are located at points throughout the country to form airways. There are two types of ground stations, low-powered "terminal VOR" (TVOR) and

**Introduction to equipment used in airborne communications.**

by Keith Bose

higher-powered en-route stations. Terminal VOR is used near certain airports. Stations are normally operated by the FAA, although some states and private interests also provide omni service.

**Omnirange Receivers**

Omni stations operate between 112.0 and 117.9 mc. The sensitivity of a typical receiver for omnirange navigation is such that a 3-uv input signal modulated at 30% with a 1000-cps tone will develop 200 mw in a load, with a 6-db signal-to-noise ratio. AGC is incorporated to maintain not more than 3 db variation over an input range of 5 to 50,000 mv. Less expensive receivers are continuously tuned, but preferred types employ crystal-tuned channels.

Omnibearing instrumentation units are usually separate from the receivers. Fig. 3 shows the block diagram of a simple omnibearing instrument. Audio output from the detector of a receiver is fed to the unit. The detector output goes to two filters. One filter has a passband

of 9480 to 10,440 cps, which separates the FM reference signal from the other signal components. The other filter passes only the 30-cps signal resulting from the rotating pattern of the distant station. The FM audio reference signal is first limited, and then fed to a discriminator which recovers the 30-cps reference signal. The signal from the low-pass filter passes to a phase shifter potentiometer (usually a resolver), and then both 30-cps signals are applied to a phase-differential detector.

The detector drives a galvanometer-type meter movement which gives a visible indication to the pilot. When the needle is centered, the setting of the phase shifter (sometimes called omnibearing selector, or OBS) indicates the bearing of the omni station. To fly on this bearing, the pilot keeps the needle centered. An airplane at any location can be "homed" to an omni station by turning the resolver until the phase-detector needle is centered and then turning the airplane to the heading indicated by the resolver.

The resolver phase shifter is calibrated so the proper omnibearing is indicated when the needle of the phase detector meter is zeroed. However, there are two points 180° apart where a null can be reached. Thus, an airplane may be either on the bearing or its reciprocal when the omni needle has been centered. In one case, the reference voltage lags the bearing signal (when flying FROM the station), and in the other case its leads (when flying TO the station). It should be noted that omnibearings refer to the bearing *position* of the aircraft relative

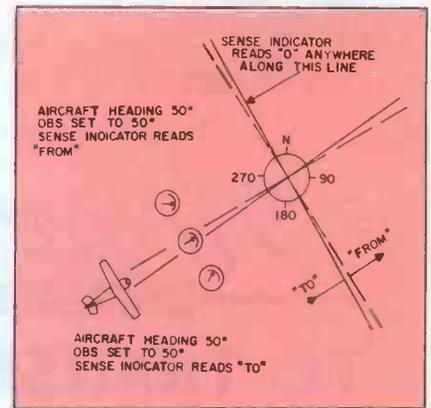


Fig. 4. TO-FROM indications in VOR.

to the station, *not* the heading of the airplane.

In order to determine if a bearing is TO or FROM a station, a fixed 90° phase shift may be applied to the reference voltage, and the resulting voltage is compared to the signal using another phase detector. Fig. 4 shows the phase relations arising from the TO-FROM bearings. The TO-FROM galvanometer movement is often arranged as a light metal "flag" moving behind a cutout on the face of the instrument.

A typical unit for light airplanes is the NARCO VHT-3 Superhomer. This unit, shown in Fig. 5, combines a continuously tuned VHF receiver, omni instrumentation circuitry, and a 12-channel transmitter, thus providing both communication and navigation in the same unit.

It is possible to arrange a servo loop to drive the phase-shift resolve of an omni indicator to null. Synchros can then be used to provide continuous readout on some suitable indicator. Fig. 6 shows an indicator known as a radio magnetic indicator (RMI). The rotating card of the

• Please turn to page 65

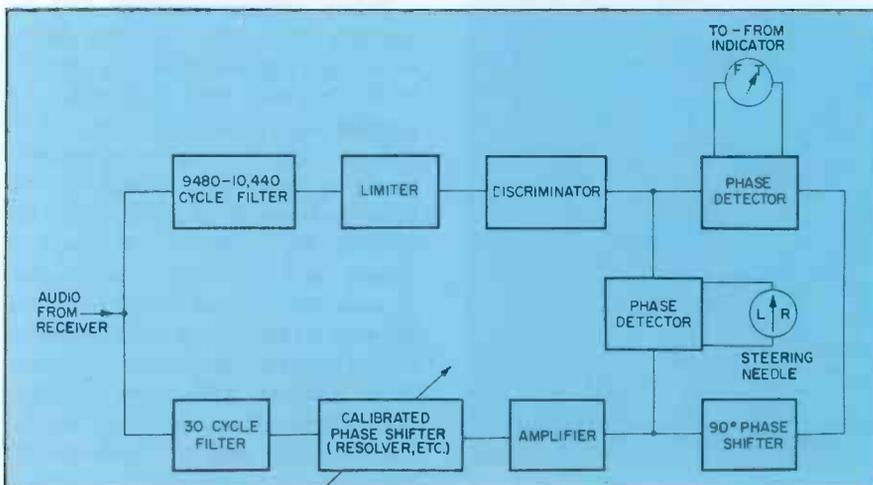



Fig. 3. Diagram of typical omnibearing instrument — called VOR device.



Fig. 5. Communication-navigation unit.

# Royal Road

## T TRANSISTOR SERVICING

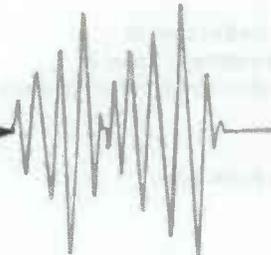

The ever increasing number of transistorized portable radios in need of servicing present technicians with a charge-rate problem in addition to some strictly technical difficulties. The low purchase price of these sets condition the owners to expect low repair charges also. However, small size and other design features are often not conducive to rapid repair; thus service charges are often larger than expected by the customers. In view of this, some technicians refuse to work on these sets—an attitude that dilutes customer confidence. “Why,” a customer might wonder, “should I trust my complex TV or hi-fi set to a shop that can’t repair a small radio?”

### Troubleshooting Methods

Rather than refuse to service transistor sets, a service-shop operator would do better to learn techniques that cut down troubleshooting time so that repair charges can result in profits and still be agreeable to set owners. While several troubleshooting techniques are useful, servicemen should recognize the limitations and advantages of each.

### Total-Current Measurement

One common troubleshooting procedure starts with measuring total current. A milliammeter is inserted in one of the battery leads to compare operating current with total-current norms usually noted on receiver schematics. The variation (higher or lower) of the abnormal reading from the prescribed value can often be analyzed to indicate the probable defect. When an audio circuit or another stage in a set having low-value emitter or collector resistors is at fault, current measuring is fairly reliable—a trouble in these sections will result in definitely erroneous readings. For example, an

open audio transistor will lower current demand by more than you might expect from disabling a single stage; conversely, a shorted transistor or one drawing too much current (in the audio stages) will be readily noted.

On the other hand, faults in stages where large-value resistors are used in the emitter or collector circuits will affect total current drain so little that the change cannot be detected by the total-current test. Fig. 1A shows the first IF stage of a Motorola 6X39A with normal operating voltages indicated. Normal current drain of the stage is computed from the voltage drop across R9 divided by the resistance of R9;  $I$  is 2.8 volts/2200 ohms = .0013 amps or

1.3 ma. When the transistor shorts, the battery voltage is impressed across R8 and R9 in series; current drain  $I$  is 6 volts/2420 ohms = .0025 amps, or 2.5 ma.

Thus with a shorted transistor an overdrain of slightly more than 1 ma results—very significant within the stage, but not too noticeable in a total-current reading that is perhaps 20 or 25 ma. This condition was actually experienced in the Motorola circuit shown, as was a similar condition in an Emerson 888 (Fig. 1B) in which the converter transistor shorted. The total stage current is that found by dividing the voltage drop across R5 by its resistance; normally this is 2 volts/2700 ohms, or .37 ma. With the transistor shorted, total supply voltage is impressed across R5. The resulting current through this resistor is 6 volts/2700 ohms, or 2.2 ma, again hardly noticeable when the reference point is at the power-supply input for the whole set. These examples clearly demonstrate one limitation of the total-current measuring technique.

### Voltage Measurement

While voltage readings will invariably be helpful (if not necessary) in pinning down a specific fault, they are often misleading for preliminary troubleshooting. It is even possible to develop the habit of rambling from one voltage to another in hope of stumbling onto the trouble. If, however, for want of clearer understanding, a serviceman is prompted to read voltages, he will be wise to limit such measurements to the drops across emitter resistors. These readings will supply considerable information concerning transistor operation and also indicate the input- and output-load condition of each stage.

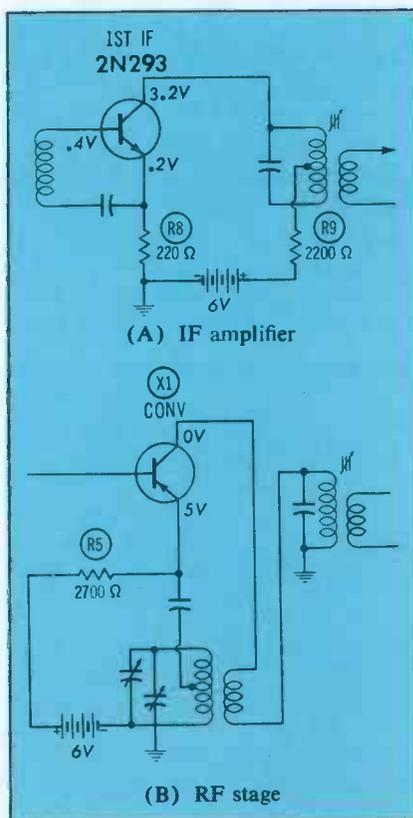


Fig. 1. Normal voltages in two typical RF and IF transistor circuits.

Even after the defect has been localized to one stage, voltage readings can be misleading. For example, consider the case of an RCA 1T4J (Fig. 2) in which the signal had been scope-traced to the first IF amplifier (X2) collector. There was no signal, however, on the base of second IF amplifier X3. The possibility of an open secondary in IF transformer L4 (my first suspicion) was sidetracked when a voltmeter reading showed an approximately correct voltage at the base of X3. Total loss of signal could result from a base-to-emitter short in X3; since such a transistor short would curtail current flow in the emitter resistor, a voltage reading was taken across R14. The subnormal voltage seemed to indicate such a base-to-emitter short, so the set was turned off in order to take resistance measurements. Resistance readings were perfectly normal—low resistance in one direction and high resistance in the other. If the transistor had been shorted, the resistance would have been low in both directions. Further resistance measurements did reveal, however, that the IF transformer secondary was indeed open. The approximately correct voltage found on the base, even with the source circuit open, is typical of the misleading indications frequently encountered in transistor-circuit voltage measurements. Similar conditions would be obtained should the emitter resistor open. Thus, with voltages measured at transistor elements, the source should be determined to avoid being misled by effects of shorted and open circuits.

#### Body Signal Injection

In troubleshooting vacuum-tube radios, it has become common practice to test the audio stages by touching the input grid with a screwdriver shaft or other instrument, while touching the metal with a finger. The resulting 60 cps hum from the speaker indicates signal continuity, while the loudness of the low-pitched noise suggests relative sensitivity of the audio stages. Applying this testing technique to the base of transistors, convenient as it is, has certain drawbacks. One limitation is imposed by the low input impedance of transistors, which may prevent manually induced hum from producing much sound from the

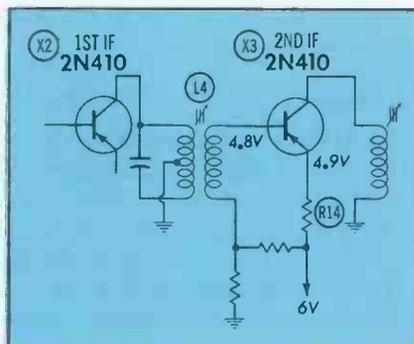


Fig. 2. Shorted IF transformer winding affects DC voltages only slightly.

speaker, even with good audio stages. In many cases, the noise produced from the speaker is too weak to serve as a dependable indication of relative sensitivity. There is another, more misleading limitation to the hum test in transistor circuits. Scratching the input (the transistor base or the hot end of the volume control) may generate noise more like RF static than like 60-cps hum. This noise can be detected by the ferrite loop, receive full amplification in the IF stages, and deceptively suggest normal audio performance.

#### Generator Signal Injection

Audio and RF generators provide more reliable signals for troubleshooting transistor circuits, and permit far better determination of stage amplification than does induced hum. The RF signal generator already owned by most shops can be used as the test source, but many shops specializing in transistor radio servicing have invested in small noise generators specifically developed for the purpose. These noise generators develop, without band-switching, a wide spectrum of signals from audio frequencies to more

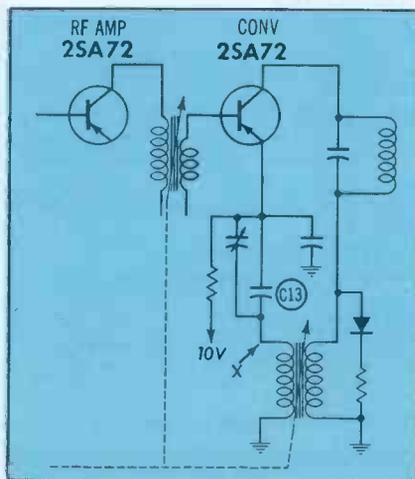


Fig. 3. A scoping point in typical auto radio transistor converter circuit.

than 2 mcs.

Although signal-injection is often helpful in localizing a defective stage, certain troubles that occur in transistor radios are susceptible to shock excitation by sharp pulses from a test generator. For example, applying a generator signal to the volume control of a dead RCA portable shocked the set into operation; and the radio worked perfectly for several days to follow. In another case, an inoperative Motorola set came alive when a test signal was applied to the base of an IF transistor; this set also had to be turned on many times afterward before the trouble returned. After experiencing this same shocking condition (no pun) several more times where resin joints were responsible, I gently packed up my signal generator and retired it from servicing transistor receivers.

These diabolical intermittents were all successfully analyzed by means of scope tracing (see "Scoping in Transistor Radios in PF REPORTER, June 1964), as were other troubles that conventional troubleshooting failed to uncover.

#### Scoping Oscillators

When scope tracing across the oscillator tank of a Westinghouse receiver indicated a nonfunctioning circuit, my next check was of the DC resistance in parallel with the tuning capacitor. This is a reasonable procedure because it quickly indicates continuity in the coil. In this specific case, I read a dead short; the cause: a tinkering customer had tightened the trimmer and punctured the mica.

#### Auto Radios

Checking oscillators with a scope is not necessarily limited to portable radios; the method is also applicable to a great many other devices, including transistorized automobile receivers. The circuit point to scope in radios is the hot end of the oscillator coil—identified as point X in Fig. 3, the oscillator schematic of a Motorola CTA61. One such receiver had every indication of a defective oscillator stage; the strongest local station came in at two points on the dial, and no other stations were received. In spite of this, a 5-volt signal (Fig. 4) was seen on the scope screen at point X,

contradicting the other clues.

Because the strong local station did crash through, I wondered if a freak demodulation was occurring in the RF stage. Voltage and resistance measurements subsequently indicated a shorted transistor. On replacing the transistor in the RF section, receiver operation was normal. A study of circuit conditions reveals the cause of demodulation in the RF section. The base voltage of the shorted transistor will remain close to 9 volts while the emitter drops to about 5 volts. With these voltages applied, the transistor will be

severely reverse-biased and become a class-B demodulator.

#### Intercoms

The General Electric W300A carrier-current transceiver found on the *Servicer* page of PHOTOFAC Folder 519 points up once again the value of scoping the oscillator tank signal. In a defective unit I was repairing, neither reception or transmission was possible. When I switched the unit to the transmit mode and scoped the oscillator tank circuit, no signal was found. This led to voltage measurement at the

oscillator stage, which revealed a shorted transistor.


This particular transistor, a type RS 2358, was used as an RF amplifier for reception and as an oscillator for transmitting. Since it was not listed in any transistor replacement guide, I replaced it temporarily with an RF type having a  $BV_{ce}$  rating of -20 volts. With this replacement, the intercom operated, but with considerable distortion. Scoping the oscillator tank signal revealed a severely clipped sine wave of over 20 volts. When the correct transistor was installed, normal operation was restored; and I found a 15-volt pure sine wave at the oscillator tank.

#### Summary

This article has pointed out how time-proven troubleshooting methods, used for years in vacuum-tube circuits, may prove misleading when applied to transistor-radio servicing. The low-impedance of semiconductor circuits can mask changes in voltage and rule out induced-hum signal tracing. The inherently small current drain of low-power transistors causes total current methods to defy evaluation. Thus, in many cases, the only sure-fire procedure for uncovering elusive defects in transistor-radio circuits calls for the use of an oscilloscope. Not only is scoping a practical method for checking oscillators, it comes through with flying colors in tracing RF, IF, and audio sections. So, don't throw away your VOM's and VTVM's, but move that scope a little closer to the transistor radio bench, and scope your way to profit! ▲



(A) Scope sweep at low frequency

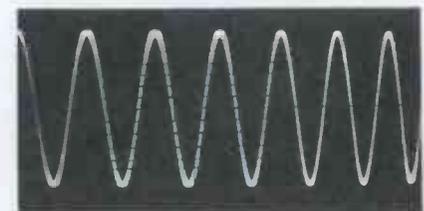

(B) Same signal swept rapidly

Fig. 4. Output waveform signals found in transistor radio oscillator circuit.

**ACCLAIMED  
BY SERVICEMEN**  
as one of the most  
useful instruments  
on the bench or  
on calls!

**Model 501 COMPONENT SUBSTITUTOR**

...places a complete range of  
components at your fingertips

**for fast  
substitution**

**only \$3750**  
Slightly higher in the West

Substitutes for  
any one of  
over 80  
component values

Will substitute  
up to 4 different  
components at  
the same time

A surge protector  
switch prevents arc-  
ing, sparking, or heal-  
ing of electrolytics

Electrolytics  
are  
discharged  
automatically

**SUBSTITUTES FOR:**

**CARBON RESISTORS**  
12 VALUES 1 watt: 10/18/33/56/100/180/330/560/1000/  
1800/3300/5600 ohms  
12 VALUES 1/2 watt: 10,000/18,000/33,000/56,000/  
100,000/180,000/330,000/560,000/1,000,000/1,800,000/  
3,300,000/5,600,000 ohms

**POWER RESISTORS (20 watt Wire Wound)**  
20 VALUE: 2.5/5/7.5/10/15/25/50/75/100/150/250/500/  
750/1,000/1,500/2,500/5,000/7,500/10,000/15,000 ohms

**CAPACITORS (600 volts)**  
12 VALUES: .0001/.0005/.001/.0025/.005/.01/.015/.02/  
.05/.1/.22/.5 mfd.

**ELECTROLYTICS (450 volts)**  
17 VALUES: 4/8/10/12/14/18/20/28/30/40/50/70/80  
130/150/200/230 mfd.

**RECTIFIERS (Universal)**  
**CRYSTAL DIODES**—all general purpose low voltage types  
**SELENIUM POWER RECTIFIERS**—up to 500 ma., 800 PIV  
**SILICON POWER RECTIFIERS**—up to 750 ma., 800 PIV

The Model 501 provides all the substitutes for electronic components you want and need in your every day work ... more than any other instrument of its type. No longer do you have to handle hard-to-manipulate crumpled parts ... solder and unsolder components as you trouble shoot a set. With a twist of a knob and a flip of a switch you can set the 501 to any one of over 80 component values ... substituting as many as four different components simultaneously. Smart, sturdy grey hammertone steel housing ... handy storage compartment accommodates the insulated test leads provided with the instrument. Size: 10" wide x 6 1/4" high x 4 1/2" deep.

See your electronics parts distributor or write for complete literature

**Mercury ELECTRONICS CORPORATION**  
manufacturers of quality electronic products

111 Roosevelt Avenue, Mineola, New York

# TWO NEW HIGH-PERFORMANCE CB TRANSCEIVERS FROM LAFAYETTE...*Leader In CB Equipment*

## NEW! LAFAYETTE 23-CHANNEL CRYSTAL-CONTROLLED DUAL CONVERSION 5-WATT CB TRANSCEIVER



Model HB-400  
**169<sup>50</sup>**

### With Advanced "Range-Boost"

- Ruggedly Built For Reliable 2-Way Radio Communication
- Easy To Use ... Easy To Maintain . With Every Feature CB Users Want!

- Frequency Synthesis Offers 23 Crystal Controlled Transmit/Receive Channels—No Extra Crystals Needed!
- "Range-Boost" Circuit for Increased Sideband Power . . . Greater Range!
- 17-Tube Performance With 13 Tubes
- Low Noise Nuvistor "Front End"
- 5 Double-Tuned IF Transformers
- Sensitive 3/10  $\mu$ V Dual Conversion Receiver
- Built-in 117V AC & 12V DC Power Supply
- Plug-in Facilities For Lafayette Selective Call Unit ■ Imported

## NEW! LAFAYETTE ALL-TRANSISTOR DUAL CONVERSION 5 WATT CB TRANSCEIVER With Mechanical Filter For Ultra-Sharp Selectivity

- 100% Solid-State ... Full 5-Watt Performance!
- 11 Rugged Silicon Mesa Transistors Used In Critical Areas
- Small, Compact—Only 3" High!
- Low Battery Drain—Less Than 350 ma on Receive, 850 ma on Transmit!

- 12 Crystal Transmit & Receive Positions
- 23 Channel Tunable Receiver with Spotting Switch
- 15 Transistors, 5 Diodes
- Sensitive 5/10  $\mu$ V Dual Conversion Receiver
- Variable Squelch, plus ANL
- For 12V DC, or 117V AC with Optional Solid State AC Power Supply ■ Imported



Model HB-500  
**139<sup>50</sup>**

**Dealerships  
Now Available for**

## LAFAYETTE'S NEW "HOT-LINE"

Lafayette Radio Electronics, "World's C.B. & Electronics Center" has available dealerships for its new "Hot Line" of Citizens Band equipment. A leader in the C.B. field, Lafayette equipment has been performance proven and customer accepted.

Lafayette is now introducing its new C.B. "Hot Line" etc. Engineered-designed, precision-crafted and field-tested to make Lafayette THE NAME in Citizens Band.

Be the first one to hook-up with Lafayette's  
**NEW "HOT-LINE."**  
Get complete information without obligation—mail the coupon today.

LAFAYETTE RADIO ELECTRONICS CORP.  
Dept. ASPFL-4  
111 Jericho Turnpike  
Syosset, L. I., N. Y. 11791

Mr. Robert Laub:  
Please send me full information on how I can become an exclusive Lafayette dealer. I understand there is no obligation.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_



Be a wise owl!

## How to cut call backs, increase profit on receiving tubes!



Engineered for peak performance . . . priced for extra profit! Every Admiral Supertron Electronic Tube must pass rigorous *super-quality* control tests and life tests to meet the high premium standards required for circuit approved tubes.

The remarkable Admiral price and volume discount helps you make *more dollar profit* on every service job! Reduce expensive call backs.

Order a complete supply of new Admiral Supertron Receiving Tubes today . . . start pocketing big profits tomorrow! Call your Admiral Distributor now!

Be wise . . . standardize on

# Admiral® SUPERTRON RECEIVING TUBES

Always Precision Crafted Quality  
Circle 19 on literature card

# NEW YORK HI-FI SHOW OPENS FALL SEASON

Transistorization and miniaturization were the key features of the equipment shown at the New York High-Fidelity Music Show in October. This annual affair is the national platform for launching new products by the many manufacturers who comprise the Institute of High Fidelity, Inc. Audiophiles and dealers await the unveiling of new trends and designs during the four-day showing. Two other Institute shows are held on the West coast at other dates, but the New York show annually introduces the greatest number of new products.

The trend toward miniaturization was apparent in the diminutive speaker cabinets and compact components and subassemblies displayed for 1965. Tape recorders were shown in greater numbers than ever before, with features that appeal more to the nonprofessional user than those of previous years. Here again, transistor applications offered important changes in operating efficiency, flexibility, and circuit reliability.

High-performance, portable phonographs, affording substantial power outputs never before supplied to the public, were exhibited by several manufacturers. These units are available in both wooden-cased types and luggage-styled portables. Transistor circuitry has permitted a substantial power increase in a far more compact package. In addition, new speakers and enclosures offer improved quality even with greatly reduced cubic content. Certain amplifier circuits have been redesigned to accent the characteristics of the new generation of speakers, with emphasis on good, clean bass response. The new compacts are in the \$200 price range, but should attract the serious audiophile who demands audio excellence in a small, easy-to-place speaker system.

Component amplifiers and tuners of more conventional size also employ transistors this season. Prices are still above the tube types in general, but increased reliability has been proved by the manufacturer and accepted by the public. The smaller component units should provide a comfortable starting place for the new high-fidelity component buyer of 1965 who has a limited budget.

Speakers also appeared in the guise of table or hanging lamps, as all-weather units for outdoor use, and in new shapes and sizes more likely to entice feminine interest. One small, high-performance speaker system measures 10½" x 5½" x 7¼". While small systems outnumbered larger designs, the impressive quality demonstrated by multispeaker systems in larger cabinets attracted many critical listeners.

Complete transistorization of tuners and amplifiers was evident in several new product lines. The overall chassis size of component equipment has not been reduced appreciably, except in the case of the compact amplifiers, but manufacturers claim cooler operation now permits less conspicuous installation in locations where ample ventilation space was required for tube types.

Industry estimates of more than \$100 million in sales for the next year were voiced by Walter O. Stanton, president of the Institute, and president of Pickering and Company, manufacturers of record-playing equipment. Mr. Stanton has watched the industry grow from annual sales of \$25 million in the 1950's to its present level. Virtually all of the industry growth has occurred since the end of World War II as a direct result of consumer demand for better sound.

According to Mr. Stanton, 75% of the urban homes having high fidelity installations are still not equipped for two-channel stereophonic sound, and this represents a major growth area for the industry in 1965. ▲



### MODEL 107B FEATURES "NO-SET-UP" TESTING

40 prewired sockets accommodate 63 basic pin arrangements for testing all modern TV, radio, industrial and foreign tubes. Also included is a plug-in chassis with 8 sockets wired to 14 lever type pin selectors for testing tubes circuit by circuit. To eliminate errors in reading, all information reads on *one* meter and *one* scale. Three comprehensive tests—Grid Circuit Test, Dynamic Mutual Conductance Test and Cathode Emission Test. Model 107B is always up to date—data book pages covering new tubes are mailed periodically to registered owners. ONLY \$189.50 net.

## SECO'S patented Grid Circuit Test detects "hard to find" tube faults

**GRID CIRCUIT TEST** makes up to 11 simultaneous checks for leaks, shorts and grid emission

### MODEL 98 FEATURES PICTURE TUBE TEST

Tests over 400 cathode ray picture tubes including 110° deflection types—has 12-pin picture tube socket. Also has replaceable plug-in chassis for receiving tubes—guaranteed up-to-date including novars, nuvistors, 10-pin types, compactrons and magnovals. This chassis can be replaced for new tubes or customized for special uses. Dial controls isolate or transpose tube circuits and select test current—Grid Circuit Test, Tube Merit Test and Heater Current Test. Removeable cover holds speed-indexed tube data cards, pin straighteners and condensed operating instructions. ONLY \$99.50 net.



### MODEL 88—COMPLETE TESTER AT LOW COST

Performs the same picture tube test as Model 98. Tests all receiving tubes including novars, nuvistors, 10-pin types, compactrons and magnovals. Grid Circuit Test, Tube Merit Test and Filament Continuity Test—you can find cathode emission, leaks, shorts, grid emission, gas error, filament continuity and cathode-to-heater emission. Stationary receiving tube chassis. Unit comes complete with speed-indexed setup data, pin straighteners and 12-pin picture tube socket on a 3-foot cable. ONLY \$74.50 net.



 For complete information on Seco test equipment, see your electronic supply distributor or write:  
**SECO ELECTRONICS, INC.** 1221 S. CLOVER DRIVE • MINNEAPOLIS, MINNESOTA 55420  
A DIVISION OF DI-ACRO CORPORATION

Circle 24 on literature card

December, 1964/PF REPORTER 41



FM stereo has been around for three and one-half years (the first broadcasts took place in June 1961), and has solidly caught hold of its market during 1964. What does this mean to the service technician? It means a good deal of equipment has been in use for some time now, and many additional units are being sold each and every day. So, get ready for more and more requests to service FM stereo receivers! The technician who best understands the operating principles of FM stereo reception is the one who will be able to repair these sets quickly, and consequently turn this activity into profit.

Several articles and books have been written dealing with the theory, operation, alignment, and other aspects of FM stereo receivers. It seems that in nearly all these writings, the importance of an FM stereo generator has been stressed. There is no doubt that such an instrument can often be mighty useful. However, *service* can be performed, and performed adequately, without a generator. A stereo transmission has all the signal components needed for checking stereo receiver operation. The main advantage of using a generator rather than a station transmission is the convenience of selecting specific components of the composite stereo sig-

nal. The remaining parts of a transmitted signal, of course, cannot be turned off. Therefore, to service stereo decoders without a multiplex generator, the technician must be able to recognize and concern himself with only the portions of the composite stereo signal which seem to be missing or improperly reproduced — a procedure quite similar to that of using video signals for servicing TV receivers.

### The Transmitted Signal

To best be able to recognize these individual components at the receiver, let's briefly review the signals transmitted during a stereo broad-

cast and the importance of each.

The stereo signal must serve two purposes. First, it must provide the stereo listeners with separate left and right audio. Secondly, those listeners having *monophonic* FM sets must not encounter any interference from the additional second-channel information, and must still enjoy good quality mono FM when stereo is transmitted. Both these requirements are accomplished in the following manner:

Three separate signals are transmitted during an FM stereo broadcast. The main channel (L + R) — that heard on standard FM receivers — consists of frequencies between 50 cps and 15 kc. The difference

# SERVICING STEREO ADAPTERS

by Norman D. Tanner

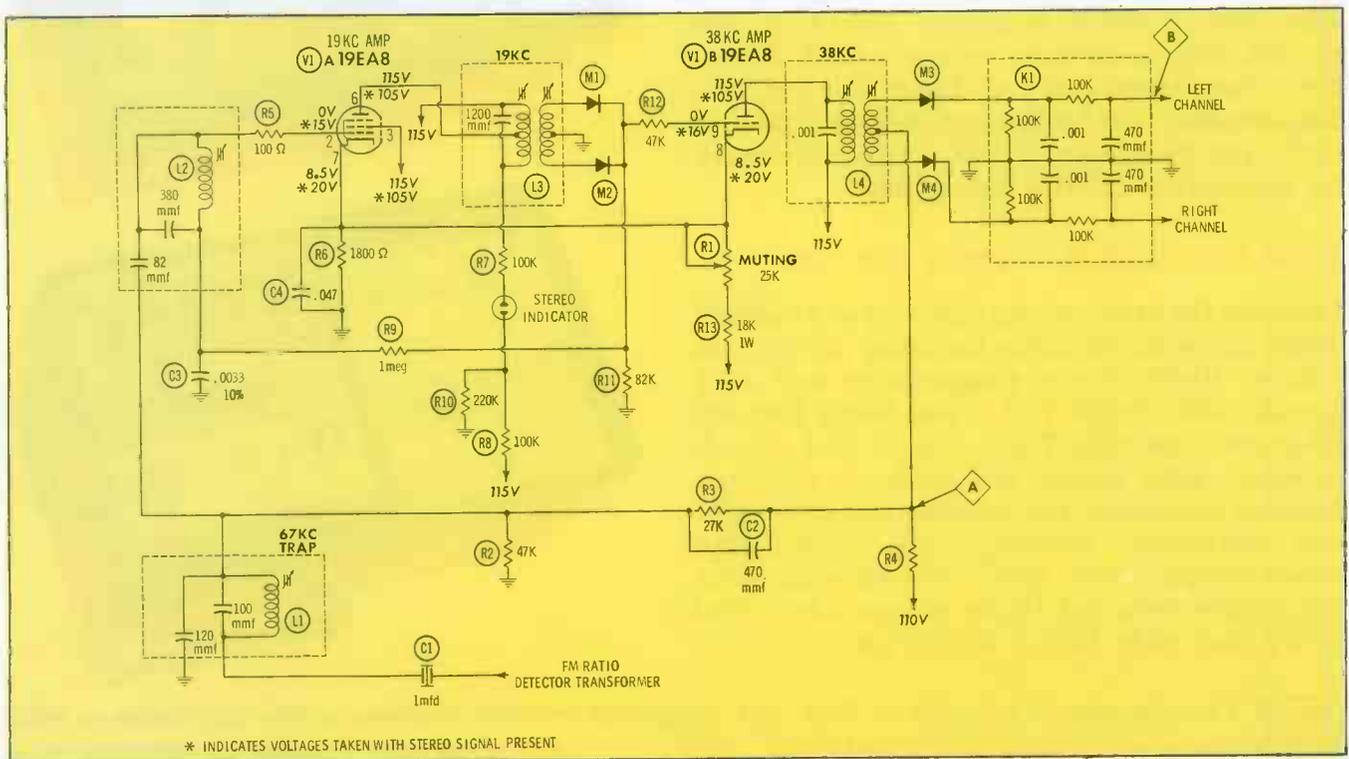


Fig. 1. Modern Stereo adapter circuit uses diodes to develop 38-kc carrier.

# NOW

*convergence and color adjustments  
are easier, faster, more accurate!*

## NEW B&K MODEL 1240 LOW PRICED PORTABLE COLOR GENERATOR

*with crystal-controlled keyed rainbow color display!*



**Thinnest Horizontal Lines! Smallest Visible Dots!**  
(Just one raster scanning line thick)

**Simplifies In-Home (or Shop)  
Color TV Set-Up and Servicing**

*only*  
**\$134<sup>95</sup>**<sub>NET</sub>

You're the color TV expert when you use the "1240." You have the advantage of B&K quality—with features not available before at such surprisingly low cost.

Provides crystal-controlled keyed rainbow color display on TV screen to test color sync circuits, range of hue control, and align color demodulators. Shows ability of TV receiver to display color values.

Provides dot pattern, crosshatch, horizontal and vertical lines. Highly stable crystal-controlled count circuit with small-step count assures greater reliability and stability of color, dots, and lines. All horizontal lines and

dots are just one raster scanning line thick. Lines begin off-screen and end off-screen, with no break in line. Dot brightness is adjustable with easily accessible control. Chroma Level Control simplifies color sync trouble-shooting.

Operates on channels 3, 4, and 5, and adjustable without removing cabinet. No connection inside TV set is needed. Power transformer operated and line isolated to prevent shock hazards. Operates reliably on 105-125 VAC, 60 cps. (Color Gun Killer is available as optional accessory.) Extreme lightness and portability (9 lbs.) make it ideal for in-home servicing.




*See it at your B&K Distributor  
or Write for Bulletin AP21-R*

**B & K MANUFACTURING CO.**  
DIVISION OF **DYNASCAN CORPORATION**  
**1801W. BELLE PLAINE AVE. • CHICAGO, ILL. 60613**  
Canada: Atlas Radio Corp., 50 Wingold, Toronto 19, Ont.  
Export: Empire Exporters, 123 Grand St., New York 13, U.S.A.

Circle 16 on literature card

December, 1964/PF REPORTER 43

## BOOK REVIEW

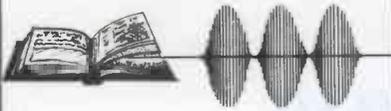

**Mathematics for Electronics and Electricity;** National Radio Institute Staff, John F. Rider Publisher, Inc., New York, New York; 250 pages, \$3.95. In its five chapters and 250 pages, this paperback volume covers the range of mathematics from counting in the decimal system to the fundamentals of Boolean algebra. The first chapter, "DC Circuit Calculations," is in reality a review of simple arithmetic—the basic operations of addition, subtraction, multiplication, and division as applied to whole numbers, fractions, and decimals. Simple electrical circuits are used as a basis for examples—a technique used throughout the book. The second chapter explains square roots, ratios, and positive and negative numbers. Phasors (vectors) are introduced in this chapter, also; solutions of problems by graphical means and by means of the theorem of Pythagoras are explained. Chapter three explains simple algebra and the operator  $j$ . The fourth chapter introduces elementary trigonometry, exponential numbers, significant figures, and the use of graphs. The last chapter is devoted to binary arithmetic and Boolean algebra. The explanations of the various topics are brief but adequate for the purpose. The experienced engineer or technician may have little need for such a text, but the beginner or the person whose knowledge of practical mathematics has grown "rusty" should find it useful.


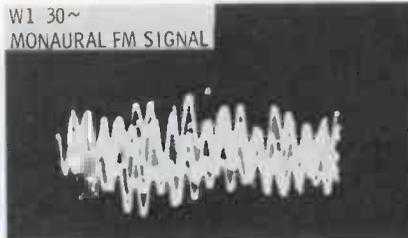


Fig. 2. Point A—monophonic FM signal.

signal ( $L-R$ ) amplitude modulates a 38-kc carrier which is then suppressed (not transmitted). Only sideband pairs 15 kc above and below 38 kc are transmitted. Therefore, in the stereo receiver this 38-kc carrier must be redeveloped. To produce a 38-kc carrier within frequency tolerance and in phase with the original suppressed carrier, a third signal — the 19-kc pilot — is transmitted. Special circuits in the transmitter combine these components and they appear together at the receiver as the composite stereo signal.

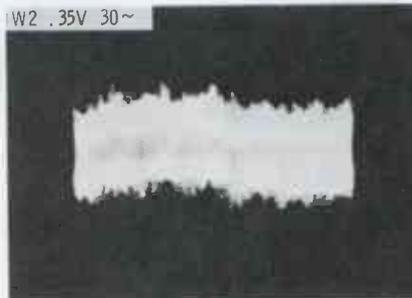Some stations also broadcast a third signal — background music service, or SCA — which ranges from 59 to 75 kc. Since this additional carrier is not suppressed at the transmitter, it must be removed by a filter network in the receiver to prevent "beat" interference with the  $L-R$  signal.



W2-scope set to 30 cps.


Enough on the signals that are transmitted. Now, let's see what happens to these signals in the stereo receiver.

### Tracing The Composite Signal

Fig. 1 shows a typical stereo adapter circuit. The composite signal is taken from the ratio detector transformer and coupled through C1 to the SCA filter. This trap is tuned to the center frequency of the SCA signal, 67 kc, and has a response sufficient to trap frequencies 5 kc above and below 67 kc. A defect in, or misalignment of, the 67-kc trap network will result in a "whistle" or other interfering noise from the speakers.

The output of network L1 (composite minus SCA subcarrier) is divided into two paths: The  $L+R$  (standard FM) and  $L-R$  signals are coupled to the center tap of the secondary winding of L4, while the 19-kc pilot is separated from the remainder of the composite signal and applied to the grid of V1A through tuned circuit L2.

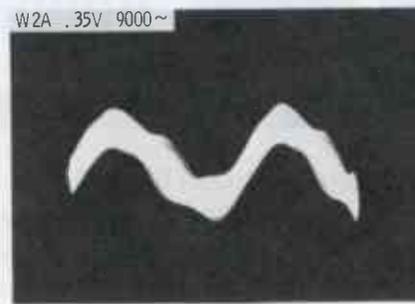Waveform W1 (Fig. 2), taken with the receiver tuned to a monophonic broadcast, shows the  $L+R$  signal present at point A. When a stereo signal is being received,



W2A-scope set to 9000 cps.

Fig. 3. 19-kc pilot signal at V1A grid.

# Season's Greetings

-To Our Many Good Friends!



Circle 17 on literature card

# MIRACLE WORKER

*in professional TV service shops*

**PINPOINTS ANY TV TROUBLE FAST! UPS YOUR PROFIT!**



**DELUXE B&K**

## MODEL 1076 B&W and COLOR TELEVISION ANALYST

*with Crystal-Controlled Keyed Rainbow Color Display  
and Highly-Stable Horizontal Oscillator Sync*

### **FLYING SPOT SCANNER**

*transmits B&K patterns or your own pictures onto TV screen*



It's like having your own TV station! You can inject your own TV signals at any time, at any point—and quickly solve tough dogs, intermittents, any TV trouble, as you watch the generated test pattern on the raster. Checks any and all circuits in any stage throughout the video, audio, r.f., i.f., sync and sweep sections of the TV set. No external scope or waveform interpretation is needed. And if you wish, you can transmit your own slide-pictures.

### **Makes Color TV Servicing Easy, Too.**

Generates white dot, crosshatch and color bar patterns for convergence. Generates crystal-controlled keyed rainbow color display to check color sync circuits, check range of hue control, align color demodulators. Demonstrates correct color values.

Saves time and work for the "pro." Makes servicing easier and faster for the beginner technician. Most valuable instrument in TV servicing.

Net, \$329.95

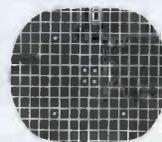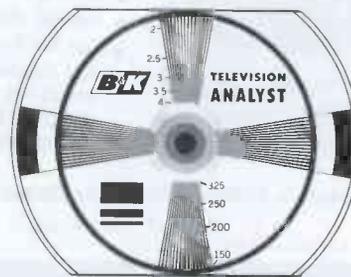

*Profit with a B&K Service Shop  
See your B&K Distributor  
or Write for Catalog AP21-R*

**B & K MANUFACTURING CO.**  
DIVISION OF **DYNASCAN CORPORATION**  
1801 W. BELLE PLAINE AVE. • CHICAGO, ILL. 60613  
Canada: Atlas Radio Corp., 50 Wingold, Toronto 19, Ont.  
Export: Empire Exporters, 123 Grand St., New York 13, U.S.A.

Circle 18 on literature card

W3 20V 9000~

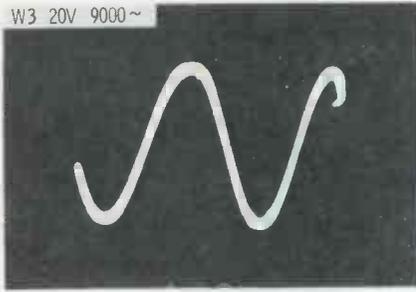


Fig. 4. Waveform at plate of 19 kc amp L+R is again present at A, but accompanied this time by the other components of the composite stereo signal.

The signal at the grid of V1A is depicted in Fig. 3. (These and all remaining waveforms were taken with the receiver tuned to a stereo broadcast.) W2 and W2A are photographs of the same signal; W2 was taken with the scope sweep set to 30 cps, W2A with the scope sweep set to 9000 cps. In both waveforms you can see the 19-kc pilot as well as audio. W2A, however, is most important at the grid of V1A, since L2 is tuned sharply to pass 19 kc. The transmitted 19-kc pilot signal is intentionally very low

W4 20V 9000~

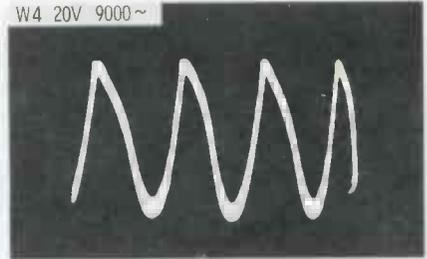


Fig. 5. Diode output — 38 kc sinewave. in amplitude to prevent interference in mono-only receivers.

The plate signal of V1A (W3), shown in Fig. 4, is the amplified 19-kc signal. Notice the audio information is much less pronounced at the plate; this is because plate transformer L3 is tuned to 19 kc. Each side of transformer L3 secondary feeds a diode, while the center tap is grounded. The diodes are connected in doubler fashion to produce an output of 38 kc.

The output of the doubling diodes (grid signal of V1B) is shown in Fig. 5. This waveform (W4) was observed with the scope sweep set to 9000 cps. Proper doubling action can be checked very easily. Set the scope for two cycles of the 19-kc signal at the doubler input and then, without changing the scope frequency, check the doubler output; four cycles (38 kc) should be displayed. A good indicator of diode condition is the amplitude of the four pulses, which should be constant under normal conditions.

Considerable amplification (about 19 db) takes place in the V1B stage, where plate transformer L4 is tuned to 38 kc. The signal amplitude at the grid is 20 volts peak-to-peak, while the plate signal (Fig. 6) is 175 volts.

The waveforms (W6 and W6A) in Fig. 7 show the signal that appears at the junction of L4 and M3, consisting of L+R, L-R, and the reinserted 38-kc carrier. The matrixing of the audio signals (L-R and L+R) begins at this point and the corresponding junction of L4 and M4.

W5 175V 9000~

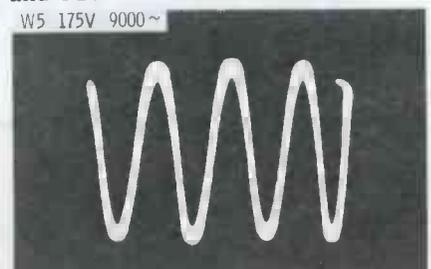


Fig. 6. Waveform at plate of 38 kc amp.

**R** FOR "DOCTORS OF SERVICING"



## Where there's a contact... or a relay...

**Service with Contact Shield! Protective! Corrective!** It not only cleans and safeguards contacts better on TV, radio, and hi-fi sets; on all **relay-operated** electrical equipment, regular protective maintenance with this versatile cleaner **prevents** sticky relays—while corrective servicing **unsticks** them... **in seconds.** Promotes greater conductivity, keeps relays working smoother, longer. Contact Shield—the professional service man's cleaner.

### APPLICATIONS INCLUDE:

- Bowling Alley Automatic Pin Spotters
- Vending Machines
- Slot Machines
- IBM Computers and other data processing equipment
- Industrial Equipment using relays, such as welding machines, etc.
- Pinball Machines
- Telephone Switchboards

For handy guidebook to better servicing, write Channel Master Corp., Ellenville, N.Y.

Circle 37 on literature card

## PRECISION TUNER SERVICE

P. O. BOX 272

1200 S. WALNUT ST.


BLOOMINGTON, IND.

EDISON 99653

**7.50**  
V or U

COMBO PLUS  
9.95 POSTAGE


6 MONTH WARRANTEE

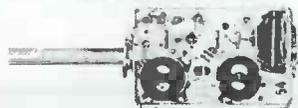


All Types T.V. Tuners Cleaned, Repaired and Aligned to Factory Specifications. Same day in shop service on most Tuners. Price Includes Minor Parts, Major Parts at Cost Price. We use Original Parts if possible. State Make Model and Enclose all Parts and Tubes. Pack Well and Insure.

ALSO HAVE LARGE STOCK OF EXCHANGE TUNERS, WRITE FOR TYPES AND PRICES.

Circle 20 on literature card

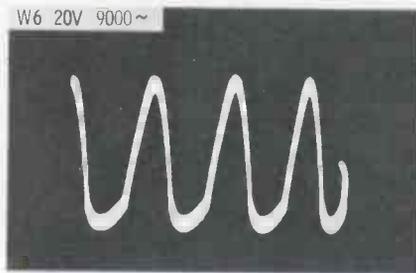

W6-scope set to 9000 cps.

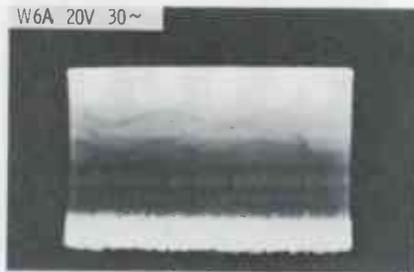

W6A-scope set to 30 cps.

Fig. 7. Signal input to detector diode.

The outputs of M3 and M4 consist of 38-kc pulses whose amplitudes vary at an audio rate; M3 recovers the left channel audio, M4 the right. The 38-kc carrier still present (W7 in Fig. 8) is filtered by K1, leaving only the audio signals for application to audio amplifier stages. The signal taken at point B is W8 in Fig. 9.

### Stereo Indicator

Many stereo receivers are equipped with a stereo indicator light. A popular version employs a neon lamp in the plate circuit of the 19-kc amplifier tube; a typical arrangement is shown in Fig. 1. The purpose of this indicator is to inform the listener when a stereo signal is being received—therefore, it should not light when the receiver is tuned to a monophonic signal.

One side of the lamp is connected to a fixed DC voltage, while the other side is connected to the plate of V1A through R7 and L3. When a stereo signal is received, a 19-kc pilot is present on L3. The peaks of this signal at the primary of L3 are sufficient to develop firing potential across the lamp circuit.

The muting control (R1) adjusts the cathode voltage and thus the bias on both V1A and V1B. Misadjustment of this control may prevent the neon lamp from firing (if the cathode voltage is too great), or allow it to fire when noise from an FM station is present (if the cathode voltage is too small).

Even with the muting control

properly adjusted, the indicator may not light on some stereo stations; this is usually caused by an improper antenna system.

### Summary

Once you have determined that a defect is present in the multiplex stages, isolating the defective circuit can be simplified by the signal tracing procedure we've given here. A waveform analysis of both plate and grid signals is a good starting point. Improper waveforms may be caused by either a defective component or misalignment of the associated coils. (A complete alignment procedure, and checks for individual coil alignment are given in PF REPORTER, July 1964.)

As was mentioned earlier, a station signal should prove adequate in servicing any FM stereo circuit. However, to assure proper separation of the audio signals a generator may be required; the varying levels of a broadcast just aren't suitable for this job.

The circuits in some receivers will not be identical to the one shown in Fig. 1. However, they all do the same basic job and their operation is similar. The most important circuit points to look for are the stage in which the 38-kc carrier is redeveloped and the network in which the L-R and L+R signals are matrixed. Once these have been recognized—and you know what the waveforms should look like—you're well on the way to faster stereo servicing. ▲

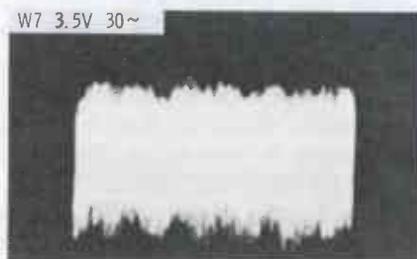


Fig. 8. Det output — 38 kc unfiltered.

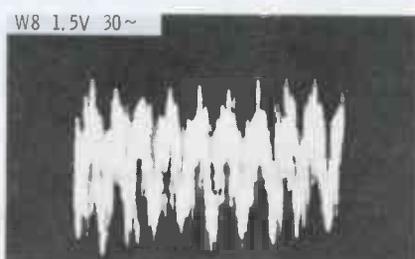


Fig. 9. Filtered output is pure audio.



## Can you service mobile radio and CB?

It's a big business . . . and getting bigger every day. There are thousands of mobile radio systems now in use plus thousands more marine and CB sets. **BUT . . . ONLY MEN WITH COMMERCIAL FCC LICENSES ARE LEGALLY AUTHORIZED TO SERVICE THEM.** Don't let this profitable new business get away from you. At home, in your spare time, a Cleveland Institute training program will prepare you for the tough new FCC License Exam . . . is backed by this remarkable offer: "If you complete the CIE program yet fail the FCC License Exam specified, all tuition will be refunded".

Get details. Send coupon for our book "How to Get a Commercial FCC License". There's no obligation.

Cleveland Institute also offers the following Electronics courses: Electronics Technology, Industrial Electronics, Broadcast Engineering, and Electronic Communications.

**ACT NOW . . . SEND COUPON FOR FREE BOOK**

### Cleveland Institute of Electronics

1776 E. 71th St., Dept. PF-19  
Cleveland, Ohio 44114

Please send me your free brochure "How to Get a Commercial FCC License".



Occupation \_\_\_\_\_ Age \_\_\_\_\_

Name \_\_\_\_\_  
(Please Print)

Address \_\_\_\_\_ County \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Now training over 15,500 students through Electronics Home Study.

For almost 14 years, I've been in and out of homes repairing TV, radio, and hi-fi sets. Probably one of the more demoralizing things that can happen is to remove, repair, and reinstall a 13-year-old *Whatzis*, which calls for enormous physical exertion (the people who own such sets invariably live on the third floor and ask you to use the back entrance), and then receive a phone call the day after saying the sound has a crackle in it every hour or so. You try to explain that the set was repaired for some other trouble entirely unrelated to sound, but that's like telling the local gendarme you didn't see him signal you to stop.

So, now what? You *could* go back with a tube checker, hoping to detect leakage or some other weakness in the audio tubes; you *could* then set up shop in the parlor, with the customer glaring over your shoulder and silently thinking, "Who does this guy think he's kidding, turning knobs, tapping tubes, and making a big deal out of nothing, when all any good TV man has to do is reach in and take out the bad tube?" Or, you *could* go quietly back and remove the chassis, explaining that it was all your fault and the job wasn't quite complete. What's best?

Having approached this problem for years from every angle, I find the ultimate answer to be: Completely check out the whole set while it's in the shop. By doing this, you may spend an hour longer, but in the long run you're 'way ahead.

#### A Procedure

First, check every tube—including the picture tube. Right here, 80% of your present and future troubles are eliminated; you not only protect yourself, but you capture tube sales that might otherwise go to drug and retail stores. You also increase your own profit and at the same time insure yourself to a degree against those time-consuming and costly callbacks.

Next, clean every control in the set with any good control cleaner. This procedure takes only five minutes and is invaluable. Then, using a high-quality tuner cleaner, care-

## KILL those CALLBACKS



by Frank R. Perullo

fully wash down the tuner contacts. You are then ready to find out what is wrong with the set. Check all components visually. The condition of many resistors and capacitors can be evaluated by sight—for instance, a capacitor with wax leaking out or a scorched resistor. Get them out! They are no good, and will quite possibly have you doing the job over again in a week or two, if they are not replaced. If either fails after the set is returned, and the job has to be done over, you can figure a loss as high as \$15 to \$20 worth of valuable time that could have been applied more profitably.

Look at those resistors. Any change in color means that either the value has changed or is soon likely to because some other component is drawing an overload through it. Change that resistor! And look for the cause of overload.

Get used to looking at every tie point, ground point, and—especially on printed circuit boards—every solder joint. With practice, you'll be able to pick out cold-soldered joints, cracks in PC boards, and other little things that competent eyes notice quickly.

#### After the Repair

Next, turn on the set and—with proper blend of mind, instruments, and experience—you should be able

then to locate the trouble and repair it. So the set is running and all you have to do is rush it back to the customer and collect. Whoops, not so fast! I'm quite sure most veteran servicemen have seen sets they've just repaired run beautifully for an hour or two, and then act worse than ever. The set should be run for a minimum of four hours. If you want to (although I don't think it necessary in all cases), operate the set at 100 volts AC for one half-hour and, if you suspect more hidden trouble, raise the input voltage to 125 volts AC for 10 minutes or so. (Of course, I'm assuming we all have variable transformers, which come in quite handy at times.)

After the "cooking" time is up, shut off the set for about 10 minutes and then turn it back on. If everything still looks good, you have an excellent chance of delivering the set and not seeing it again till it's due for another good going-over.

You now have done everything possible to eliminate unseen problems, and your customers will in the long run be glad they paid a few extra dollars for a *thorough* job; furthermore, you'll rest easier because you'll know you've given them a first-class job. At the same time, you've been building a reputation for being an expert television serviceman.

#### Philosophy of a TV Man

Television service is not like betting on a horse or like playing cards. We have thousands of different models to contend with, many of them designed by someone who never had to sweat out the humiliation we all experience at one time or another in our jobs.

For instance, you pry a tuner knob off the set and the pieces fall on the floor in front of the customer because it had a hidden setscrew you couldn't possibly see.

... Or a tube smothered by an immovable shield so that in trying to remove it you break the tube. Great for customer relations.

... Or the portable with a high-voltage lead that barely reaches the CRT, so when you reach in to re-

move it from the CRT your big paw has just enough room to squeeze that diabolic pincer-type connector that keeps slipping out of your grasp. You end up getting belted good and come out of the set with blood dripping off your hand.

... Or the 6AL5 that was cleverly put between the picture tube bracket and the high-voltage cable so that you have to put a mirror, a flashlight, and a tube holder all in the same spot while you spend ten precious minutes trying to replace the tube.

... Or the set with no name, model number, or tube layout, that bears no resemblance to any set you know of, but the customer will pay anything to have it fixed because it really is a *Whackeroo* built by *Whatzis* and designed by *Whichit*—or so his brother says, anyway.

... Or the set with an enormous sheet of boiler plate covering the back, so if you're not very careful it will slip out of your sweaty hands and shear off the CRT neck which extends three inches beyond the cabinet.

Yet try to explain any of these to poor Joan Doe. She not only won't but can't believe you. So, if you want to beat some of the odds against you on the next set you bring to the shop, do this:

1. Check all tubes and CRT.
2. Check all capacitors visually.
3. Check all resistors visually.
4. Check all solder joints.
5. Check and clean all controls.
6. If set is cranky, run it at high and low voltage by varying the voltage between 100 and 125 volts.
7. Also, don't forget to clean the CRT.

#### Experience Helps

I was working on a Sylvania portable that had already been toyed with by the customer's friend. Of course, I was a little apprehensive, but the customer pointed out that all the tubes had been checked and quite a few replaced. He was correct. There were about seven new tubes, but force of habit made me check the older ones. They were good.

After at least two solid hours of beating my brains, I finally decided my first impression was correct and the trouble was in the oscillator and

mixer section of the tuner. Both tubes in the tuner were new, but I checked them in the tube checker; they checked "good." I had an identical chassis in the shop, so I decided to swap tuners. Well, this *had* to do it, thought I.

After soldering the last wire, I turned on the set and . . . oh, my aching back, still nothing. Even though the 5U8 was brand new, I decided to get another from my tube caddy; I did, but still got no pix.

Now what? I sat back, carefully reviewed my efforts, and studied the schematic, which brought me right back to the tuner. There was another set on the bench and I noticed it used a 5U8. Like the drowning man who grabbed the straw, I pulled that 5U8 out and put it in the portable. Lo and behold, we were back in business!

I now had two *new* 5U8's that were bad and an *old* one that had put us back in business. I just had to know what was going on, so back to



- Tests TV and Radio Tubes—both old and new
- Tests all Novars
- Tests Nuvistors, 10-pin Tubes, and 12-pin Compactrons
- Tests Voltage Regulators, Thyratrons, Auto Radio Hybrid Tubes, European Hi-Fi Tubes, and Many Industrial Types

## **B&K** PROFESSIONAL QUALITY AT LOW COST

### Model 600 Compact Portable Dyna-Quik Makes Tube Testing Quick, Accurate, Profitable!

It's amazing how quickly you can accurately check out tubes on every call—sell more replacements, and make more money—with this up-to-date, low-cost professional quality tube tester. Checks for all shorts, grid emission, leakage, and gas. Checks each section of multi-section tubes separately. Checks tube capability under simulated load conditions. Rejects bad tubes, not good tubes. Quickly reveals tube condition, saves customers, stops call backs, increases servicing profit.

Exclusive adjustable grid emission test. Sensitivity to over 100 megohms. Phosphor-bronze socket contacts. Complete tube listing in handy reference index. Handsome, sturdy leatherette-covered carry-case.

Size 8½" x 11" x 4½". Net, \$74.95



#### QUICK, DIRECT, ERROR-FREE READINGS WITHOUT MULTIPLYING

Model 375  
VTVM  
Net, \$89.95

Model 360  
VO Matic  
Net, \$59.95



See Your B&K  
Distributor  
or Write for  
Catalog  
AP21-R



### **B & K MANUFACTURING CO.**

Division of DYNASCAN CORPORATION

1801 W. BELLE PLAINE • CHICAGO 13, ILL.

Canada: Atlas Radio Corp., 50 Wingold, Toronto 19, Ont.

Export: Empire Exporters, 253 Broadway, New York 7, U.S.A.

Circle 21 on literature card

December, 1964/PF REPORTER 49

# NOBODY CAN CHANGE THE WEATHER BUT OXFORD HAS CHANGED THE PUBLIC ADDRESS SPEAKER MARKET . . . with the introduction of the All New "Outdoor Specialist Series"

Oxford OP-8 and OP-6 Models represent the first major change in weather-proof paging and talk-back speakers in more than ten years. Not just a rehash of other speakers now on the market, but entirely new units incorporating new features, new materials and new design concepts throughout. □

**NEW BELL DESIGN:** Not a compromise, but a true "exponential flair" for maximum efficiency. Molded from *Implex*, a space age material that is practically indestructible and impervious to weather extremes. The ¼-inch bell sections guarantee vibrationless, resonance-free reproduction. □

**NEW COUPLING DESIGN:** Integral close coupled inner horn and diaphragm allows maximum energy transfer with minimum distortion. Heavy-duty slug magnets are used, not "gimmicked" or less efficient ring magnets. □

**NEW TRANSFORMER OPTION:** The OP-8 and OP-6 are available from stock with 25 or 70 volt transformers built in, or without any transformer. For those who wish to install their own transformers, a standard mounting bracket is provided. □




□ **NEW LEVER-LOCK\* MOUNTING BRACKET:** An Oxford exclusive that swivels 360° in the horizontal plane and 180° in the verticle with a flip of a single lever. The horn may be adjusted to any position without tools or disassembling . . . no thumbscrews to drop either! Stays locked until you unlock it. □

□ Oxford's OP Series is the first in a program that will bring many startling new speakers for public address applications . . . speakers that will meet and exceed the requirements of the dynamic sound industry. □

\*patent pending

**For Complete Information and Specifications,  
Write for Product Information Bulletin No. C-103**

**OXFORD  
TRANSDUCER  
CORPORATION**

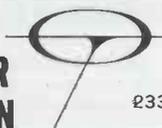

A Subsidiary of Oxford Electric Corporation

2331 North Washtenaw Avenue • Chicago 47, Illinois

Circle 22 on literature card

the tube checker. The first tube checked okay, but I was interrupted by a phone call and left it in the checker. When I got back, I pressed the check button and the needle dropped quite steadily till it reached an absolute "no good" indication. This tube evidently failed only after it warmed up.


About a week later, I repaired a GE Model 17C103. I had not checked all the tubes, but the pix was beautiful. I thought perhaps I should let just this one go by. However, bitter experience has taught me that tubes are devilishly two-faced and can cause all kinds of headaches. Consequently, I wheeled the chassis over to the tube checker and went to work. The tubes were all perfect except for an intermitently shorted 12AU7; out it came and in went a good one. I'm quite sure that if this set had gone back, I would have been back in the customer's house losing time, money, and prestige.

I recently repaired a changer for slippage in the 33-rpm position. The trouble was a worn shaft, so I talked the customer into changing the whole speed-shifting unit. The unit was replaced, and I played a stack of records on it and rushed it right back. I played a record for the customer and felt a little proud that this job was air-tight. Oh yeah? Next day, the customer phoned to complain that, on 45-rpm records, the arm landed in the wrong position. I had to go back and finish the job, because I didn't do it right the first time. If I had checked all speeds, I would have saved at least 1½ precious hours I could have spent more wisely elsewhere.

### Conclusion

We can't reeducate people to all our problems, so I've found a better way out of the callback problem: Make as complete a check as possible and charge a fair price for doing it. Yes, in the long run the public will gladly pay more for a complete, lasting repair, and will also tell their friends how, after having their set overhauled, it ran for months with no problems. I've found in my own business that I make more money, keep more friends (and customers), and save much more time by a complete overhaul. ▲

# SNOW COUNTRY!

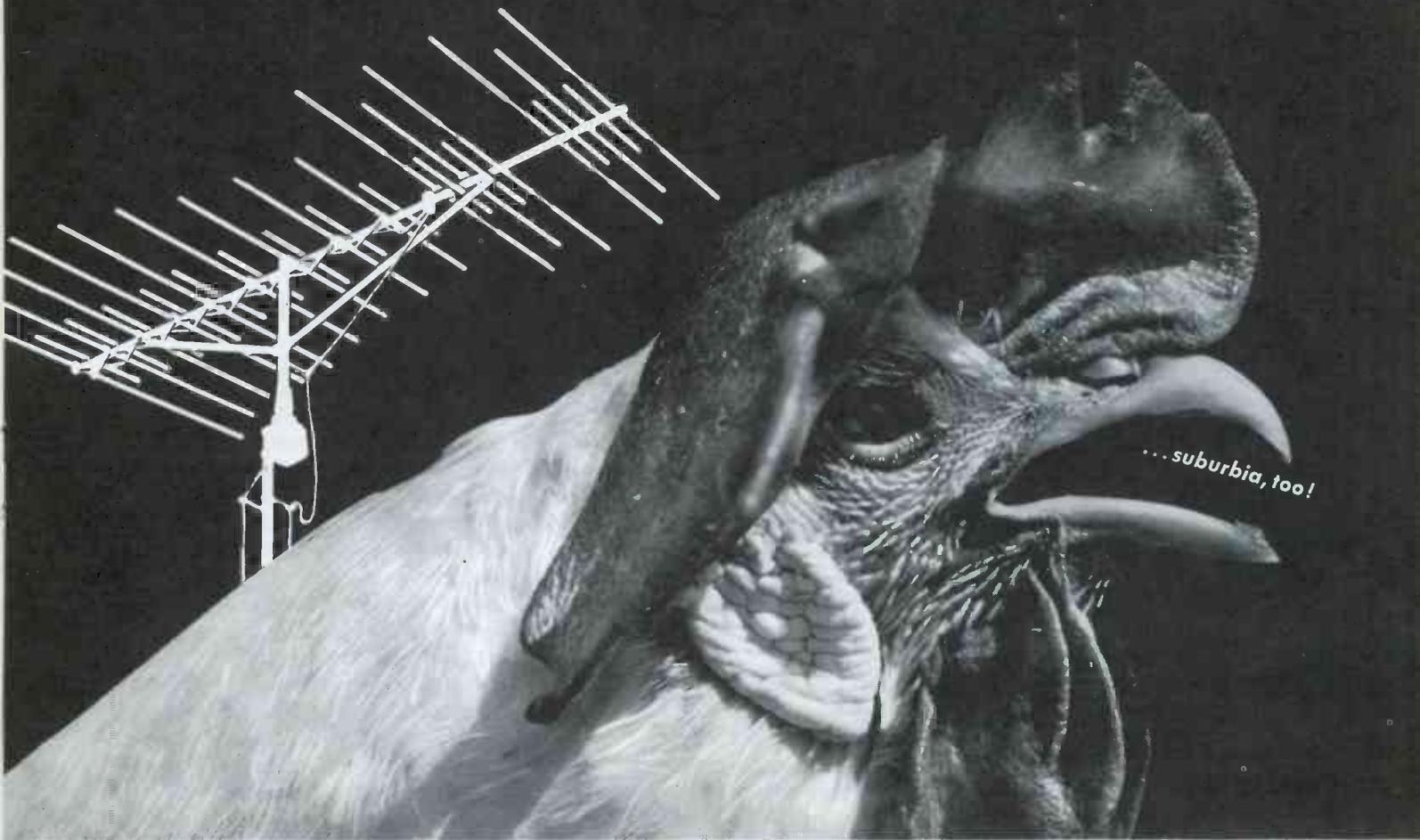

## Clean it up...take it over... with **CHANNEL MASTER CROSSFIRES**

The world's most powerful TV/FM antennas. Way-out farm country is snow country. Real weak signal. Without the right antenna, there's a good chance viewers are seeing "spots" on their TV screen. Near fringes and often suburbia are also weak signal. Smart watchers know what to do about this problem in all these areas. They get the right Crossfire.

**Top snow removal team!** The revolutionary Golden Crossfire alone works on the principle of Proportional Energy Absorption. Meaning? There are more driven elements working with greater efficiency on the Crossfire than in any other antenna. It actually delivers the highest antenna gain of all time. Cleanest, too. The unique transposed feed line cancels rear pick-up beautifully. Perfect for color. And exclusive E.P.C. "Golden Overcoat" protects against every type of corrosion.

8 rugged, handsome Crossfire models are available... 1 for every area and budget. Feature them and you've got the snow country, the near fringes, and the commuter belt... right where you want 'em! In your money belt. Shown above: 28-element Crossfire for deep-fringes. Model 3600.

### Now! Channel Master Reduces Booster Prices Up to \$10.


World's most effective antenna amplifiers.

... Because no boosters anywhere give you more extra signal power when and where you need it. Plus lowest possible noise figure. Built-in lightning resistance. Complete line covers model for every purpose and area... including an all-in-one rotator-TV amplifier. Write for catalog.

WAS \$39.95

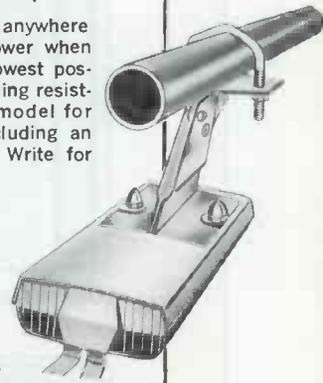**NOW! \$29<sup>95</sup>**

Transistorized Telstar TV/FM,  
with 4-set coupler. Model 0023B.



Model 3604, 11-element  
Crossfire Suburban  
... for high gain and  
top directivity.

**CHANNEL MASTER** hands you the keys to the snow country

ELLENVILLE, N.Y.

Circle 23 on literature card



# The Knack of FILTER REPLACEMENT

There is a right way —  
here's how to decide.

by Jay F. Shane

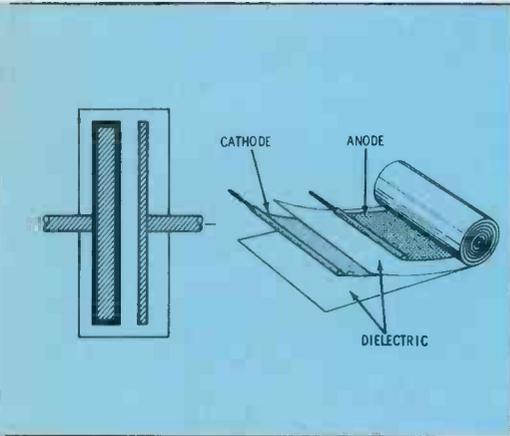


Fig. 1. Construction of an electrolytic.

Because of changing demands in the industry and the number of different circuit and chassis designs (despite the efforts of the EIA standards group) there is an almost unbelievable number of filter capacitor types. This multiplicity of types and values makes it practically impossible for even large distributors to stock a complete inventory of exact replacements. The televi-

*Note: Materials for a portion of this article was adapted from the Howard W. Sams book "Understanding Capacitors" by William Mullin.*

sion serviceman, therefore, is constantly plagued by not having a filter capacitor of the same size, type, and value as the defective component, especially for many older receivers. When this happens, a more specific knowledge of capacitor characteristics may help in selecting a suitable non-exact replacement.

A standard tubular capacitor consists of two metal-foil strips separated by mineral-oil- or wax-impregnated paper and rolled tightly into a tubular configuration. Anode (positive) and cathode (negative) contact terminals are bound into the unit, one to each metal strip. This typical manufacturing technique provides units that nominally range from .001 mfd to 1 or 2 mfd; many are also available with a variety of dielectric materials other than paper in the same nominal range.

The electrolytic capacitor used in filter sections is of a far different nature, however, because much higher capacitance values are required. And, although their number may seem overwhelming, they are alike in using a thin film of aluminum oxide as a dielectric (in some

electrolytics, tantalum oxide is the dielectric — the high price of these units, however, makes them seldom practical for replacement use). The standard electrolytic has an aluminum oxide film. The cathode of the electrolytic is actually a liquid electrolyte that consists of a solution of ammonium borate and boric acid, plus glycol to prevent freezing. A second aluminum conductor is embedded in the electrolytic to provide the cathodic connection. To ease manufacturing problems that would arise from using a free solution of the electrolyte, porous paper is impregnated with the solution so that the electrolytic is generally referred to as being "dry," although "damp" might be a more accurate word. Fig. 1 shows the theoretical symbol for and a simple assembly drawing of a typical electrolytic. The oxide film has a very high resistance to current in one direction and a very low resistance in the other. For voltage of one polarity, then, it acts as a dielectric and, in the other, acts as a conductor.

There are three basic electrolytic styles: polarized, semi-polarized and nonpolarized. Fig. 1 illustrates the first. Symbols for all three types are shown in Fig. 2. The semipolarized type has an oxide coating on the cathode as well as on the anode, but one that is much thinner. During polarity reversals of low current, the film prevents damage to the primary anode that would otherwise destroy the oxide film.

The nonpolarized type is actually double-polarized, with both plates being coated equally, thus providing immunity to polarity reversals. This type is often used in AC motor-starting circuits. These basic electrolytics must be replaced type-for-type; that is, polarized for polarized, etc.

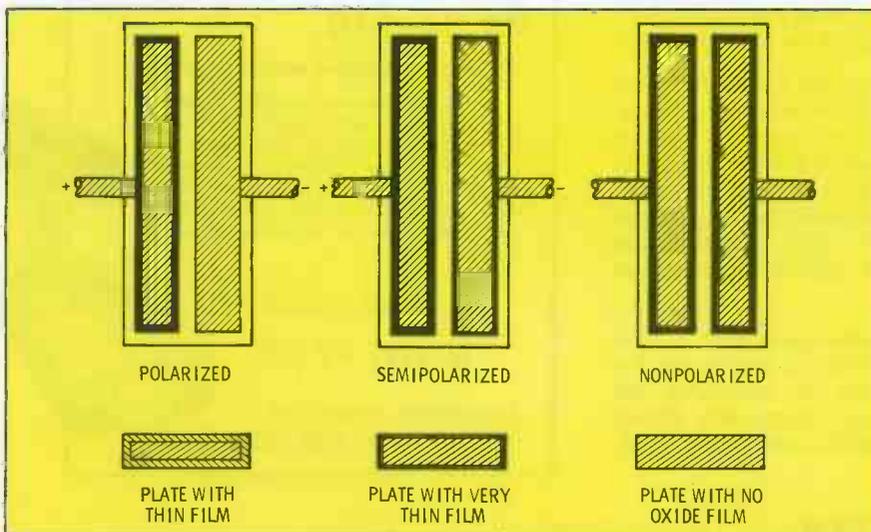


Fig. 2. The three basic electrolytic configurations.

Now, with an idea of how these devices are constructed, we can determine factors that control their use in circuits where direct replacements are unavailable. Tolerances for electrolytics are established at 25°C and may typically be -10% to +50% for medium-to-high-voltage units. By this, then, a 100-mfd capacitor could range from 90 to 150 mfd and provide replacement for an original-value capacitor within that range under normal room-temperature operation.

A second factor to be considered is that the electrolyte varies in chemical proportion for electrolytics of different working voltages. It is not a good idea to use a 450 VDC unit in a circuit where the voltage is far below that level, because the oxide film will "deform" and reduce the total capacitance.

Something else to remember is that electrolytics will deform spontaneously while idle, and a full application of rated voltage will often cause the film to break down, permanently ruining the unit. It is always a good idea to reform any capacitor, before installing it, to avoid callbacks. This can be done using a capacitor checker or by applying voltage (approximately the rated working voltage) to the unit through a 1000-ohm, 5-watt resistor, allowing the charge to build slowly over a period of a few minutes.

The factors to consider in non-exact replacement of electrolytics, in view of what we now know of these capacitors, are: The type of polarization; the value, considering the broad allowance for tolerances; the correct voltage rating; and, the operating temperature.

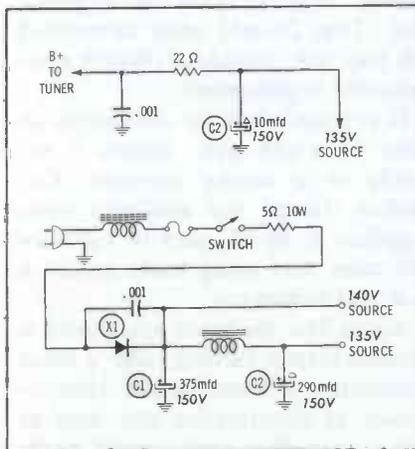


Fig. 3. Partial schematic of G-E chassis.



## NOW BETTER THAN EVER!

The famous RCA WV-38A Volt-Ohm-Milliammeter

### NEW FEATURES...

**COLOR-CODED FRONT PANEL MARKING** simplifies operation, reduces chance of error.

**METER MOVEMENT PROTECTED AGAINST BURNOUT.** Special silicon diodes guard meter against overload.

### PLUS...

**POLARITY REVERSAL SWITCH.** Reverses polarity of test leads without need for re-connecting. Handy for checking front-to-back resistance ratio of electrolytic capacitors and many types of semiconductor devices.

\*Optional distributor resale price. Prices subject to change without notice. Prices may be higher in Alaska, Hawaii and the west.

RCA ELECTRONIC COMPONENTS AND DEVICES, HARRISON, N.J.



The Most Trusted Name in Electronics

39 DIFFERENT MEASUREMENT RANGES.

MEASURES CURRENT from 50 microamps full scale to 10 amps full scale.

SPECIAL 0.25 volt and 1.0 volt (full-scale) DC ranges... useful in checking transistor circuits.

... and many additional features that have made this instrument the best V-O-M buy on the market today. **Only \$47.95\***. Kit version, WV-38A(K), only \$29.95\*.

See it at your Authorized RCA Electronic Instrument Distributor.

# new Allen type screwdrivers

work faster, easier ... reach where wrenches won't go



## fixed handle SCREWDRIVERS

11 hex sizes: .050" to 1/4"  
Precision formed, alloy steel blades  
Shockproof, breakproof, amber plastic (UL) handles

## detachable BLADES

8 hex sizes: 1/16" to 3/16"  
Fit all "99" Series handles  
Available singly — as a set of six in free plastic pouch — or in roll kit with handle

WRITE FOR BULLETIN N763

# XCELITE

XCELITE, INC., 18 BANK ST., ORCHARD PARK, N. Y.  
Canada: Charles W. Pointon, Ltd., Toronto, Ont.  
Circle 25 on literature card

## Case Histories

Fig. 3 shows the B+ supply of a GE Q2 chassis. The input filter (C1) is rated at 375 mfd at 150 VDC, required because of the 140-volt source developed by the rectifier. Several manufacturers show an exact replacement, but availability is often questionable at local distributor levels. Consulting a capacitor catalog, however, reveals several types you can substitute. There is, for example, a dual unit; 200-150 mfd at 150 volts DC. Tie the two sections together, and you get 350 mfd, well within tolerance. Or, select a second dual; 200-200 mfd at 150 volts DC. If dual-section electrolytics of this value are not available, then try a triple unit — 100-200-60 mfd at 300-150-150 volts DC, for example. This total value of 360 mfd is within acceptable tolerance.

The second filter of the Q2 chassis (C2) is a dual unit; 290-10 mfd at 150 VDC. The schematic (Fig. 3) shows the 10-mfd capacitor tied to the tuner B+ line which, in turn, is tied directly to the 290-mfd section for a total capacitance of 300 mfd in this filter. Here again, many other substitutes are available, using parallel arrangements.

Admiral's Chassis 16D9, 16E9, 16F9, 16UD9, or 16UF9 is about four years old and is very popular in motel installations. This receiver uses a 40-100-50 mfd unit at 350 volts DC. A replacement is listed, but, as we already know, listing and availability are often very different characteristics. The catalog shows at least three types, each of which can make an excellent replacement. There's a 40-80-40 mfd unit at 450-350-350 volts DC; a 40-40-80 mfd unit at 450-450-350 VDC, or a quad unit at 80-60-40-20 mfd and 350 VDC. The 20-mfd section can be tied to the 80-mfd section to total 100 mfd.

These chassis also use a "picture guard" circuit, Fig. 4. Experience has shown that any residual AC ripple component appearing on the B+ line will upset the "picture guard" circuit. The picture will usually be stable for a period from several minutes to a half hour long. It then gradually develops a slight curl, or wiggle, that may disturb the picture for a few minutes, then

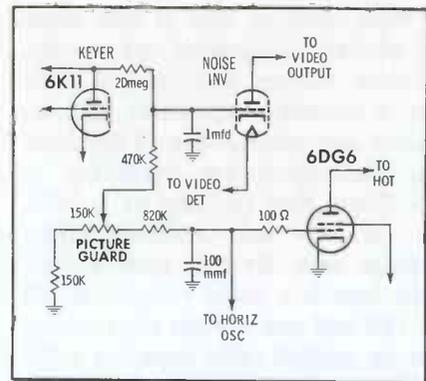


Fig. 4. "Picture guard" control circuit.

clear up. If tube substitution and checking the keyer, noise limiter, and sync-separator voltages shows them to be normal in all respects, don't fight the circuit; change the filter. The power factor has probably risen sky-high with increased temperature; or, perhaps, leakage has developed between sections.

## Points to Remember

A word of caution when servicing color receivers: Keep in mind that in chroma circuits electrolytics are often used as decouplers, and close tolerances are a prerequisite. The manufacturer uses optimum values, and he's well aware of the increase in capacitance due to ambient temperatures. He wants absolute filtering, excellent decoupling, and adequate bypassing to be maintained at all times. Changing values beyond a 10% tolerance in chroma circuits can and usually will affect color hue as well as color stability.


Remember, too: Do not substitute a polarized unit for a nonpolarized one. Disregarding this precept can cause a quick failure. You can make your own nonpolarized capacitors by tying two polarized units together, negative lead to negative lead. Two 20-mfd units connected this way will provide a 10-mfd nonpolarized replacement.

If you use a tubular electrolytic in place of a can type, anchor it securely to a nearby tie-point. Capacitor clamps are available from suppliers to fit all sizes of tubulars and cans, and using them makes a neat and secure job.

Just a few moments spent with a manufacturer's catalog, and a brief knowledge of some of the idiosyncrasies of electrolytics can help to make your filter replacement problems smaller and faster. ▲

# find PROFIT

in

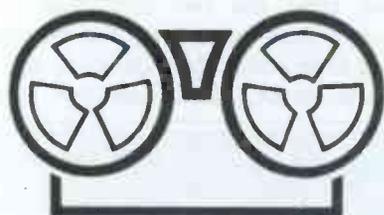

## SMALL TAPE RECORDERS

There's money in servicing these inexpensive machines.

by Homer L. Davidson

Low-cost tape recorders—those in the \$12.95 to \$49.95 price range—are considered by many service technicians as a no-profit item, to be tolerated if need be, but certainly not welcomed. This shouldn't be so for you, provided you have enough knowledge of these units to service them speedily. Waste just a little time, and you must settle for doing either a poor job or a non-profit job.

When the small transistorized tape recorder, like that in Fig. 1, comes into the shop for repairs, there is only a narrow range of possible symptoms—the recorder is running too slow, has low or no volume, or has plenty of distortion. Actually,

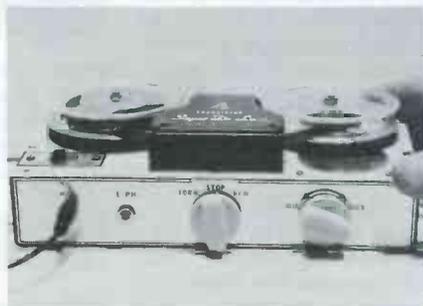


Fig. 1. Small recorders such as this are becoming fairly popular.

the small tape unit has only a handful of components. A transistor amplifier serves for both recording and playback, a small crystal mike and speaker are switched into the input and output of the amplifier, a small motor is operated from one or two flashlight cells to drive the tape reels, and one small recording head records and plays back the information on the tape.

Some faults in these little machines cause more than one symptom. If there is low volume and slow speed, for example, check *both* batteries. The 9-volt battery will cause low volume; most recorder amplifiers pull around 5 to 10 ma of battery current. There may be only one battery powering the small DC motor, although in those recorders that have two batteries in parallel (for motor power), batteries will last longer. The speed starts to drop when voltage on the flashlight cell drops to 1.25 volts, under normal load; most motors pull from 150 to 300 ma of current. Batteries are normally good for 30 to 50 hours of intermittent use.

### Speed Problems

Let's look a little closer at the symptom "slow or no speed." If the batteries are okay, check the motor and rubber-reel turntables. These rubber-wheel turntables are driven directly by shafts of a small motor, which is mounted horizontally as shown in Fig. 2. Each end of the motor shaft uses friction to drive the rubber wheels. Fig. 3 shows a vertically mounted motor, and the small pulley that pushes against the edge of the rubber wheels. The bar-handled switch actually moves the motor from one reel-edge to the other when it is switched from "play-record" to "rewind."

If you suspect slippage, check the edges of the rubber wheels and see



Fig. 2. Rubber-wheel turntables are driven directly from motor shafts.

if perhaps grease is making them slip. Clean the rubber edges with alcohol or some other good cleaning fluid. Remove the C-washers from the top of the spindles and pull the rubber wheels off. (Some manufacturers don't use C-washers.) Look for grease on the bearings at the bottom of the rubber wheels. If the bearing grease has become dirty and caked, remove the old grease and apply *Vaseline* or a light oil. Use grease and oil sparingly. Before reassembling, use the cleaning fluid to clean off the motor pulley.

Some manufacturers say not to oil the motor itself. You can tell if the bearings are dry by pulling the motor away from the rubber wheels and turn the switch to "forward" position. Dry bearings will make a dry, chattering noise. A drop of light machine oil will help. Be sure to wipe off any excess oil that might flow onto the drive shafts, and clean them again with cleaning fluid. Fig. 4 shows one way to oil the small motor.

Sometimes, after hard use, the motor pulleys become shiny and slick. As a last resort, to increase friction and reduce slippage, apply a light coat of phono-wheel dressing to these pulleys. Do not apply any to the rubber wheels.

Make sure the motor fits snugly into its carriage, and that the pulleys are in the correct position when the switch is flipped to record or rewind. Clean the tape guide pegs with cleaning fluid, so the tape will move freely over them. You can notice if there is a great deal of drag on the head and guide pegs. Also, check the unit out with no tape in position.

### The Recording Head

If the small recorder will not record or play back, first check the 9-volt battery. With the volume full on and the switch turned to play-

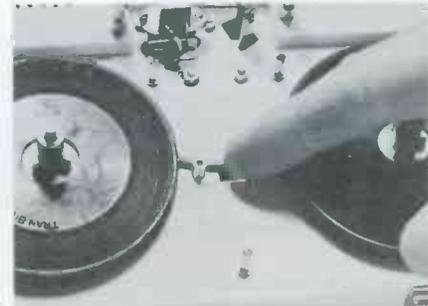


Fig. 3. Motor is mounted vertically in some miniature tape recorders.

back position, an audible pickup noise will be heard if the transistor amplifier is okay. If no noise is heard, the amplifier can be checked further by pulling the top guard piece off the recording head and touching a screwdriver to the unshielded side of the audio lead; a loud hum should be heard. An audio signal from a small harmonic generator, applied across the recording head leads, should be heard in the speaker. These tests should be made with the switch in playback position. The recording head is shown in Fig. 5. If a prerecorded tape is handy, place it on the rubber wheels


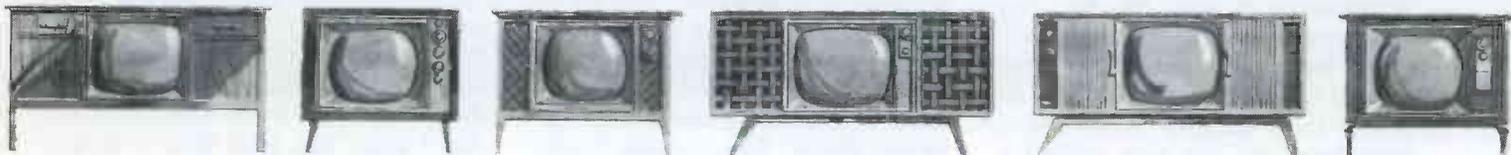


Fig. 4. Lubricants in pressure spray cans are handy for recorder service.

and switch to playback. Now there should be results.

Suppose the amplifier is okay, but

the unit still will not work. We already know the amplifier is good, so let's check the recording head itself. First, clean the front of the head with cleaning fluid. Next, measure it with your ohmmeter; its resistance should run from 450 to 900 ohms. Finally, make sure the tape moves past the correct portion of the head, in close contact. The pressure pad must hold the tape snugly against the head. Some small recorders do not use pressure pads; on units of this type, the two tape pegs are placed back far enough that the tape will drag across the face of the head. Furthermore, some recorders have

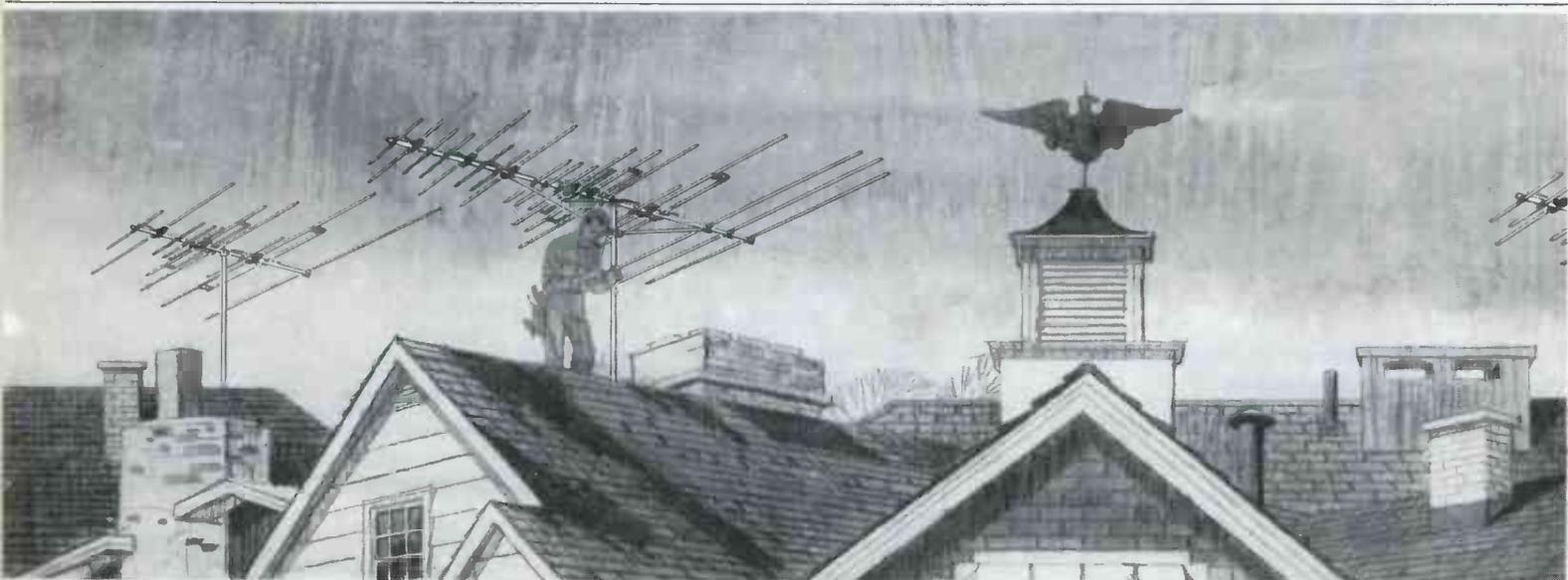

## Why are most **Color Television** Sets

**BECAUSE EXPERIENCED COLOR TV DEALERS KNOW THAT WINEGARD COLORTRONS ALWAYS DELIVER THE BEST COLOR PICTURES POSSIBLE!**

And it's just plain, common sense . . . when a man invests \$400-\$1000 or more in a color TV set, he expects—and deserves—the finest possible color reception!

Most people who demand the finest in color TV reception choose Winegard Colortron. Here's proof:

Look on top of the largest retail stores in the country . . . they demonstrate their sets connected to Winegard antennas; or look on the homes of the famous TV and movie stars in Hollywood; or on the studio buildings of all three major TV networks; even atop the Whitehouse in Washington. Wherever the best color is seen, you'll see a Winegard Colortron . . . it's the TV antenna made for color.


What's behind Colortron's Superior Performance? *Balanced Design!* Just what is Balanced Design? It's the perfect combination of high gain, accurate impedance match, complete band width, and pinpoint directivity . . . and only Colortron has it!

For example:

**Gain and Bandwidth**—A superior color antenna must have high gain and complete bandwidth. But the response must be flat if it is to be effective. Peaks and valleys in the curve of a high gain antenna can result in acceptable color on one channel and poor color on another. *No all-channel VHF-TV antenna has more gain with complete bandwidth across each and every channel than Colortron.* Look at the Colortron frequency response in this oscilloscope photo. Note the consistently high gain on all channels. Note the absence of suck-outs and roll-off on end channels. Note the flat portion of the curve . . . there is less than 1/2 DB variance over any channel.



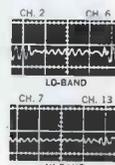**Impedance Match**—the two 300 ohm "T" matched Colortron driven elements have far better impedance match than any antenna using multiple 75 ohm driven elements. The Colortron transfers maximum signal to the line without loss or phase distortion through mismatch. The oscilloscope photo here shows the Colortron



rubber bumpers that lose shape and cause the head to tip, keeping it away from the tape. Some heads have an adjustment screw on one side that holds them in place.

If the tape doesn't move properly past the head, low volume will result, especially if the unit has a three-transistor amplifier. Either distortion or low or no volume may result from a defective recording-playback head. Fig. 5 also shows how to remove the head; merely remove two metal screws.

It is very possible that the recorder will not play back because the play-record switch was left in the

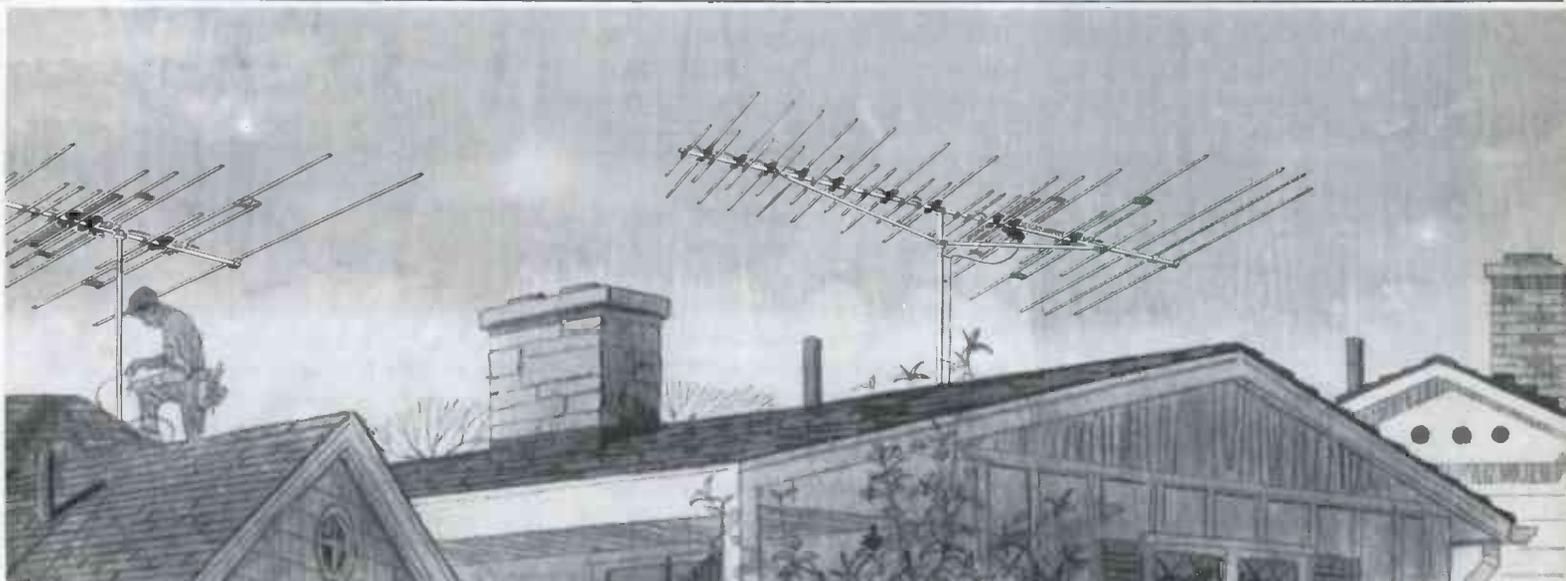


Fig. 5. Test amplifier section by touching metal to unshielded lead.

record position during rewind and the recording has been accidentally erased. This can be done on the

lower-priced units. On some models, you cannot rewind the recorder until the play-record switch is in the play position.

Many of the recording heads can be obtained from the distributor of small tape units, or substitute low-priced heads may be used. Be sure the new head has the correct impedance and that the mounting allows the tape to move past correctly. The new head may have to be raised or lowered with small fiber spacers. Check the resistance of a replacement head; it should match as closely as possible that of the original.



## connected to Winegard Antennas?

VSWR curve (impedance match). No current VHF-TV antenna compares with it across all 12 channels.

**Directivity**—An antenna with sharp directivity and good signal-to-noise characteristics is necessary for perfect color. Extraneous signals, picked up at the back and sides, produce objectionable noise and ghosts in black and white reception. But in color TV, they frequently ruin reception. *Winegard Colortron has the most ideal directivity pattern of any all-channel VHF antenna made.*

**The Unsurpassed Performance of Balanced Design is Matched Only by the Colortron's Unsurpassed Construction!**


Colortron has been engineered for maximum strength, minimum weight and minimum wind loading. The result is a streamlined,

lightweight antenna that stays stronger longer. Colortrons have even been wind tested to 100 m.p.h.

Advanced-design snap lock hardware makes Colortron the easiest antenna to install. Winegard Colortron also has the finest *Gold Anodized finish* of any TV antenna made.

**Winegard Helps You Sell . . .** With *More National Consumer Advertising Than All Other Brands Combined!* Look for Winegard . . . on AFL Football over ABC (over 1,500,000 viewers per game) . . . in Life Magazine (over 13,000,000 readers per issue) . . . in Parade (the big Sunday supplement with 21,000,000 readers per issue).

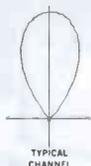This is the Season for TV buying . . . The season for you to stock up on Winegard Colortrons. Remember . . . over 2,000,000 Color TV Sets will be sold this year and the antenna made for color TV is Winegard Colortron. Order today!



COLORTRON ANTENNA  
Model C-44 • Gold Anodized • \$64.95



COLORTRON ANTENNA  
Model C-43 • Gold Anodized • \$51.90



COLORTRON ANTENNA  
Model C-42 • Gold Anodized • \$34.95



COLORTRON ANTENNA  
Model C-41 • Gold Anodized • \$24.95

 **Winegard Co.**

3009-L KIRKWOOD • BURLINGTON, IOWA

Circle 26 on literature card




**TYPE L . . .** for long, long years of service life ask your distributor for PLANET LYTICAPS, the universal replacement type electrolytic capacitor. Available in a wide range of capacities in voltages from three to five hundred. LYTICAPS are "Engineered for Quality".

## PLANET SALES CORP.

225 Belleville Ave.  
Bloomfield, New Jersey

Circle 27 on literature card

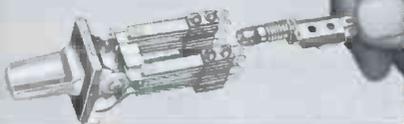takes the  
confusion out of  
switching circuits



### SWITCHCRAFT LEVER-LITE 3-COLOR SWITCHES



UP  
1st color



NEUTRAL  
2nd color



DOWN  
3rd color

One glance tells you what position the switch is in. Can be any one of six highly visible colors in each of the 3 positions. Specially designed for maximum visibility even in high ambient light. Remarkably small in size.

- 2 or 3 position models
- Locking or non-locking type
- From SPDT to 4PDT circuits
- Lamp assembly removes in seconds
- 6V or 28V lamps

WRITE FOR CATALOG S-309 OR SEE YOUR LOCAL SWITCHCRAFT DEALER.

## SWITCHCRAFT®

5573 Elston Ave., Chicago, Ill. 60630  
Canada: Atlas Radio Corp., Ltd.  
50 Wingold Ave., Toronto, Ontario

Circle 28 on literature card



Fig. 6. Amplifier circuits are usually found on small printed circuit board.

### Distortion and Low Volume

Distortion can be caused by a bad microphone, amplifier, or recording head, by poor speed regulation, or by low voltage. Improper speed will cause a form of distortion called wow and flutter. Be sure the slick and shiny side of the tape is not against the recording head; if the magnetic coating isn't directly against the head gap, low volume and distortion may result. The operator may have reversed the tape after it broke or when he started to rewind after the end of a reel.

Crosstalk distortion can occur when the erase magnet is not in place. This magnet should rest close to the tape when the switch is thrown to record. If the magnet is not in place, the messages will be recorded on top of one another. (One way to clear a tape is to unplug the microphone, switch the recorder to record, and run the whole tape through.)

Most of the amplifiers (Fig. 6) in these machines consist of three, four, or possibly five transistors. You need all the volume you can get on the three-transistor models, and every component must be up

to snuff. Distortion, low volume, and no sound are the most common troubles. (Generally, amplifiers cause few troubles in tape recorders.)

Low volume can be caused by defective transistors, coupling capacitors, or 9-volt battery. The output stages in the better amplifiers are push-pull, and one defective transistor can cause low volume or distortion. Electrolytic coupling capacitors may start to leak or dry out and produce distortion and low volume.

Apply an audio signal to the input of the volume control (Fig. 7), with the recorder in play position. Trace the signal through each transistor stage and notice the gain in each. Clip the signal lead to the ungrounded side of the playback head; you should notice additional audio gain. Each stage can be checked until the one that introduces the distortion or low volume is found.

### Conclusion

So you see, inexpensive transistor tape recorders are not so difficult to repair as your first impression might suggest. Only a few basic troubles are common, as has been shown. Using your sound understanding and your ordinary service equipment, you can turn these small units into large profits. ▲

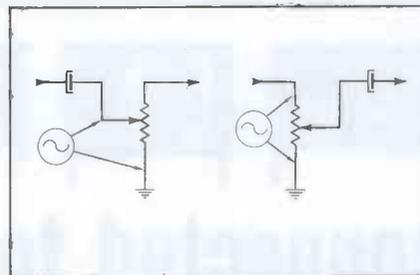


Fig. 7. Use audio signal generator to locate defective transistor stage.

**NEW!**



## ESCO DYNAMIC TRANSISTOR TESTER

**NO CHARTS—INSTANT TEST  
IN OR OUT OF CIRCUIT!**

Quickly tests ALL transistors: RF, Audio, Power, Switching, PNP, NPN, Unijunction types, etc.—under ACTUAL OPERATING CONDITIONS! Easy to use, accurate, rugged and compact. The perfect instrument for portable or bench use!

SEE it, TRY it, at your LOCAL DISTRIBUTOR

Model XT-1  
Dealer Net  
**\$1895**

Manufactured by

ESCO, 400 Hempstead Turnpike, West Hempstead, N. Y. — 516 IV 5-6068

Circle 29 on literature card



# Notes on Test Equipment

analysis of test instruments . . . operation . . . applications

by Allen B. Smith

## Versatile Tester



Fig. 1. Tube and transistor tester features pushbutton leakage test.

Many new home entertainment instruments (television sets, radios, and phonos) utilize transistorized circuits in whole or part. The EICO Model 667 Dynamic Conductance Tube and Transistor Tester shown in Fig. 1 enables the service technician to test both tubes and transistors in these units on the same portable test instrument. Ten different tube sockets accommodate most receiving tubes and a wide range of other types as well. A separate transistor socket will accept most replacement PNP and NPN transistors.

Tube types that can be tested by the Model 667 include: *novars*; 5- and 7-pin *nuvistors*; compactrons; 7-, 9-, and 10-pin miniatures; 5-, 6-, and 7-pin subminiatures; 8-pin submini-

atures; octals; and loctals. Many other special tubes — small transmitting types, voltage regulators, cold-cathode rectifiers, eye tubes, ballast tubes, and others—can also be checked on the unit.

Tests performed include: interelectrode leakage; merit — a combination of emission and dynamic conductance; and, for transistors, leakage measurement of collector current (emitter grounded, no base signal) and current-amplification factor (beta.) Fig. 2 shows the two circuits used to check transistors.

Operation of this tester is straightforward and quickly set up for each test, once the technician takes time to read the instruction manual. Detailed step-by-step instructions for testing all tube types and transistors are given in the manual. Lever and pushbutton switches seem positive in action and of good quality.

There are several levers and push-buttons whose operation will not be immediately apparent without reference to the manual. The v, c, and s levers, for example, determine voltage levels, cap connection, and variable meter sensitivity, respectively. In a second case, the roll-chart information for leakage tests (a series of several numbers) sometimes shows underlined figures; these are for testing heater-to-cathode leakage in indirectly heated tubes, and the H-K leak button must also be depressed during this test, or an inaccurate reading will be obtained. To obtain a high degree of flexibility, the manufacturer has chosen to use unfamiliar designations, but they are simple to understand if you have no aversion to reading instructions.

In the center of the *novar* socket is a second socket used to test miniature-base lamps (threaded or bayonet types). The inner wall of the socket is connected to ground, and the center contact is tied to the rotor of the filament-selector switch; the setting of that switch determines the voltage applied to the bulb. Testing several types of panel lights, and even a few Christmas-tree bulbs, showed us that faulty lamps can be quickly detected.

During evaluation in the field under

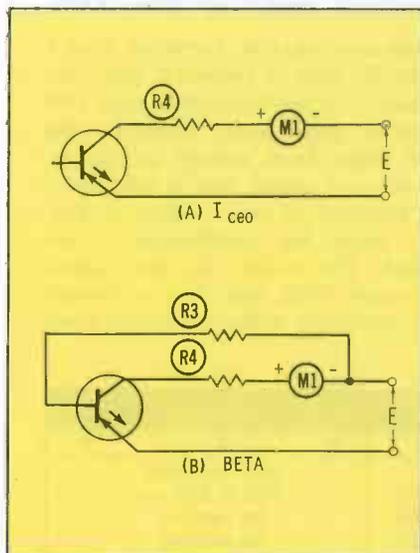


Fig. 2. Test circuits:  $I_{ce0}$  and Beta.

## NEW SAMS BOOKS

NOW AVAILABLE!

the famous HOWARD W. SAMS

### Tube Substitution Handbook in a special 2-in-1 package!




One copy for your bench...  
Compact copy for your caddy

Here's what you get in this amazingly low-priced package: 1. Latest 8th edition handbook, regular 5½ x 8½" size for bench use—lists over 11,000 direct substitutions; a complete and indispensable guide to substitutions for receiving, picture tube, subminiature, industrial, communications, and special-purpose types, including cross-reference of American and Foreign tubes. 2. Special pocket-size 3¼ x 8½" tube substitution guide for your caddy—lists American receiving tube and picture tube substitutions—all the tube substitution data you need for any outside call. Each handbook tells when and how to make proper substitutions. Both handbooks come to you in one vinyl-wrapped package. Order TUB-8P—get both of these in-<sup>valuable</sup> handbooks for only \$225

### Garage-Door Openers

by Jack Darr. This timely volume is the first complete and authoritative handbook on this increasingly important electronic device. Here are all the facts you need to know about how to install and maintain electronic garage-door openers. Provides step-by-step instructions for easy installation. Gives full, detailed procedures for troubleshooting, repair, and maintenance. A "must" book for everyone who installs and services garage-door openers, or who plans to enter this profitable field. 128 pages, 5½ x 8½". Order GDO-1, only \$295

### ONLY COURSE OF ITS KIND!

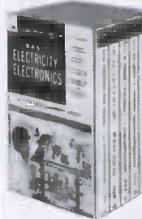

### New Hardbound Edition of the HOWARD W. SAMS Course

#### 5 Vol. Basic Electricity/Electronics

New, unique positive training worth hundreds of dollars. First completely new course to be published in the last 10 years... using the latest programmed method for quick, effective learning.

- Vol. 1. Basic Principles & Applications
- Vol. 2. How AC & DC Circuits Work
- Vol. 3. Understanding Tube & Transistor Circuits
- Vol. 4. Understanding & Using Test Instruments
- Vol. 5. Motors & Generators—How They Work

(Complete Set contains over 1300 pages; 1250 illustrations; 51 chapters; in sturdy slipcase)

Order ECS-50, hardbound edition, only \$2495  
Order ECY-50, softbound edition, only \$19.95

### Electronic Motor Control

by Allan Lytel. The field of motor control has been revolutionized by new requirements arising out of the development of new manufacturing methods and automated processes. This important new book describes the new control devices which have been developed, and the modifications of existing devices required today to provide precision control of the starting and speed of large and small motors. Thoroughly explains the new devices and the modifications of older types; covers thyratrons, ignitrons, and recent solid-state developments. An invaluable reference for electricians, engineers, and students. 224 pages; 5½ x 8½". Order MCL-1, only \$395

## HOWARD W. SAMS & CO., INC.

Order from your Sams Distributor today, or mail to Howard W. Sams & Co., Inc., Dept. PF-12, 4300 W. 62nd Street, Indianapolis, Ind. 46206

Send me the following books:

TUB-8P  GDO-1  ECS-50  ECY-50  MCL-1

\$\_\_\_\_\_ enclosed.  Send FREE Booklist

Name \_\_\_\_\_


Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

My Distributor is \_\_\_\_\_  
IN CANADA: A. C. Simmonds & Sons, Ltd., Toronto 7

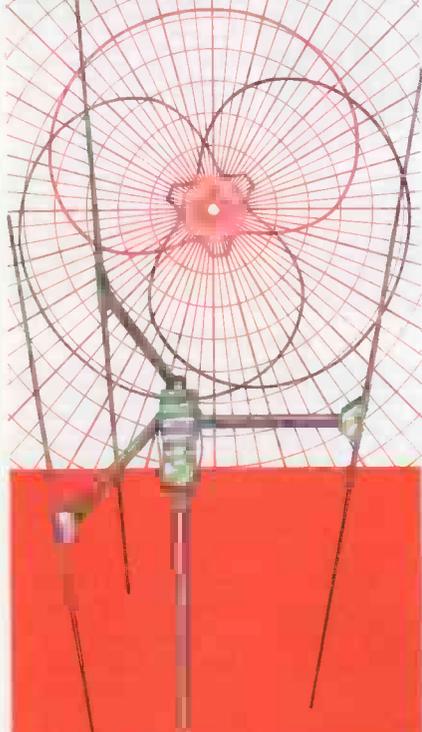**Revolutionary!**

**Change the Pattern  
of Your Whole  
Base Station Business**



The unique new all-electronic  
sector-phased Omni-Beam  
CB base antenna . . .



**THE SCANNER**  
Model **M-119**  
PAT. PENDING

**Available December 1st**

- Instantaneous scan
- All electronic three-sector beam—no mechanical rotator needed
- Extremely compact—easy to assemble
- 7.75 db directional gain—23 db front to back ratio
- Costs 30% less than old-fashioned rotator driven beam arrays

Contact your Antenna Specialists  
representative for full details.

**the  
antenna  
specialists co.**

12435 Euclid Ave., Cleveland, Ohio 44106

Stripes of Quality

Circle 30 on literature card



**EICO Model 667 Specifications**

**Tube types tested:**

5- & 7-pin *nuvistors*; *novars*; compactrons; 7-, 9-, & 10-pin miniatures; 5-, 6-, & 7-pin subminiatures; 8-pin subminiatures; octals; and loctals, plus other special types.

**Tube tests:**

1. Interelement leakage in ohms.  
2. Merit test: emission reading for rectifiers & diodes, and dynamic conductance for triodes, tetrodes, and pentodes.

**Transistor types tested:**

NPN and PNP.

**Transistor tests:**

1. Leakage of collector current.  
2. Beta (amplification factor).

**Size (HWD):**

6" x 15" x 12".

**Weight:**

20 lb.

**Power Source:**

105-130 volts AC, 60 cps; 10 watts (no tube), 50 watts (max).

**Price:**

\$129.95 (wired); \$79.95 (kit).

actual shop working conditions, the Model 667 tester was used by a technician in repairing various television receivers. Operation of the tester at first seemed a little cumbersome, but increased familiarity in setting the controls speeded the testing a great deal. More than 50 tubes (all known to be bad) were rechecked with the 667, and all were confirmed to be defective.

When analyzing the vertical-sweep circuits in a Philco chassis, he found

*For further information, circle 46 on literature card.*

roll-chart information on the output tube (12B4) was not listed, but was given in the supplement booklet. The manufacturer's manual, in a four-page procedure, gives a method for determining control settings to test unlisted types from manufacturers' specifications. The method is rather involved and would not normally be used; but, for emergency use, it does work. New roll charts are available from EICO at regular intervals, as new tubes come into common use.

**Bad Color CRT . . . or Circuit**

Often, it's advantageous for the service technician engaged in color work to have a fast means to make dynamic checks on the operation of the color picture tube—without needing several meters and/or making checks directly in wiring circuits. The Mercury Model 900 Color TV Analyzer shown in Fig. 3, is designed to meet these requirements.

The 900 is a self-contained unit, needing no power (internal or external) for its operation. The instrument connects in series with the picture tube, between the tube and the chassis; male and female plugs are included for this purpose. The only other connection necessary is to clip the ground lead from the unit to the TV chassis. Once connected, the instrument can be switch-operated to read voltage and current of each individual element, one color gun at a time. Operation of the test-set isn't difficult: A three-position COLOR GUN switch selects either the RED, GREEN, or BLUE gun to be tested. A six-position ELEMENT SELECTOR switch, with positions for



**Fig. 3. New Analyzer is used to make operational checks on color CRT's.**

METER OFF, HEATER, CATHODE, GRID 1 (control), GRID 2 (screen), and GRID 3 (focus). A spring-loaded PRESS FOR CURRENT pushbutton transfers the panel meter from voltage to current. The internal circuit, too, is automatically switched to read voltage or current, when the pushbutton is depressed. The meter has two scales; the upper black one is a combined volts-microamp scale, calibrated from

**Table 1**

Element	Voltage			Current		
	R	G	B	R	G	B
Filaments		180V		Not measured		
Cathodes	290V	290V	290V	200 to 250 $\mu$ a		
Grid 1	180V	180V	180V	No reading		
Grid 2	700V	640V	680V	No reading		
Grid 3		4.5KV		Not measured		

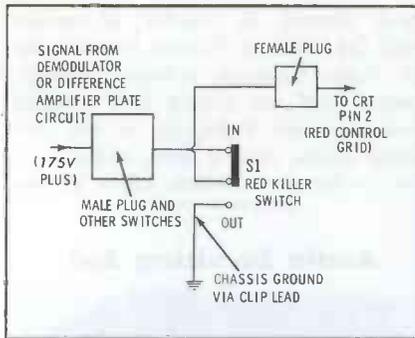


Fig. 4. Schematic of red killer circuit.

0 to 1000 volts or ua. Another scale — the lower red one — serves to indicate the focus voltage present on grid 3; it's calibrated from 0 to 7 kv. When the selector switch is in the METER OFF position, the meter movement is shunted to prevent possible damage during transportation of the unit.

An extra provision in the 900 is the inclusion of screen-killer switches. Three switches (RED, GREEN, and BLUE) are provided to bias off any single or combination of three color guns. Each slide switch has two positions — OUT, or IN — indicating the gun is off or on. We've shown a simplified schematic (Fig. 4) of the red killer circuit (the green and blue circuits are identical). With most color-killer switches, a 100K resistor is connected from the CRT grid to ground to bias off the gun; in this unit, the same thing is accomplished by a different method. The connection from the plate circuit of the demodulator (or color-difference amplifier) is DC coupled to the CRT grid; thus, B+ voltage on the plate (175 volts or more) is applied to the grid. As you'll notice in the schematic, the grid of the picture tube is connected to ground (via the clip lead) when the switch is in the OUT position; however, the switch simultaneously opens the B+ path, so the 100K resistors aren't needed.

We chose a new color receiver to give the unit a complete checkout in



"I figure I would save a little money by buying the antenna and putting it up myself."

our lab. During the process, we found the operation of the unit was uncomplicated — both in connection time and in operational checks of the color CRT. Table 1 contains the results from the particular tube we tested. We noticed that, when the unit was connected, a slight smear of the video information occurred. This was probably caused by the additional capacitance of the leads and sockets. Convergence was equally affected; final convergence adjustments with the unit connected seem unadvisable. However, this shouldn't overshadow the main purpose of the 900 — dynamic checks of the picture tube and associated cir-

cuits, while the set is in operation.

Our field report on the Model 900 proved it to be helpful in servicing symptoms of the CRT or associated circuit failure. For example, a Zenith 29JC20 chassis was being serviced for a no-raster condition. Sound was okay, high voltage was present, and the CRT filaments were lit. The tester was connected, and a quick voltage test of the picture tube elements made. The technician noticed that cathode and screen voltages were okay, but the focus voltage on pin 9 was only 1 kv. This immediately cleared the video and other CRT circuits and led to a quick conclusion of trouble in the

**Perma-Power HOLIDAY SPECIAL!**  
GENUINE  
**EVERSHARP**  
CARTRIDGE FOUNTAIN PEN  
in deluxe gift package  
**YOURS FREE**



**WITH EVERY VU-BRITE 12-PACK**

BRIGHTER TV PICTURES MEAN BRIGHTER SMILES ON YOUR CUSTOMERS' FACES!  
Bring fading, dull picture tubes back to original brilliance with Vu-Brite — the leading single-purpose britener. Model C-401 Parallel, C-402 Series.

This is not a cheap ball-point, or an advertising giveaway. It's the identical top-quality writing instrument (manufactured by Parker) you've seen in retail stores for \$2.95. It makes a perfect gift — and it's Perma-Power's gift to you when you buy 12 Vu-Brites.



**LOOK WHAT YOU SAVE!**

12 Vu-Brites—usual dealer net	<b>\$10.68</b>
Eversharp pen and cartridge	<b>2.95</b>
<b>TOTAL VALUE</b>	<b>\$13.63</b>
<b>SPECIAL OFFER</b>	<b>9.95</b>
<b>TOTAL SAVINGS</b>	<b>\$ 3.68</b>

**HURRY! DEAL ENDS DECEMBER 15, 1964**

**Perma-Power COMPANY** . 5740 N. TRIPP AVE. . CHICAGO, ILL. 60646

Circle 31 on literature card

December, 1964/PF REPORTER 61

**exciting new product!  
exciting new profits!**



**e.c.i. Courier 23**

## EASY TO SELL... EASY TO USE... EASY TO MAINTAIN 2-WAY RADIO FOR THE BOOMING CB MARKET!

Never before this performance breakthrough! Never before this big chance for you to cash in on the fast-growing 2-way radio market . . . for car, boat, home, business, office. The Courier 23 has unequalled performance with dollar for dollar value others can't match. It features dual conversion, transistor power supply, 23 crystal controlled channels and more features CB users want. It is priced at \$189.50 . . . and that includes all crystals, mounting brackets, power cords and noise-cancelling microphone. Best of all, the Courier 23 is "hot" . . . with wide acceptance everywhere!

### CAN YOUR FIRM QUALIFY AS AN AUTHORIZED **e.c.i.** DEALER?

A sound knowledge of radio and/or communications equipment . . . the desire to install and service this equipment . . . an established business reputation and a good credit rating . . . a real interest in a dynamic new product with dramatic profits. These are the requirements. Write today for details!

**e.c.i.** electronics communications inc., Dep't Q  
56 hamilton ave., white plains, n.y.

Please send full details on the Courier 23 and an e.c.i. dealership.

name .....

firm name .....

address .....

city ..... zone ..... state .....

focus circuit. A similar procedure could be used to isolate troubles to the video (cathode voltages wrong), control grid, or screen grid circuits (wrong screen voltages), if the occasion arises. And it does, often!

For further information, circle 47 on literature card.


### Audio Servicing Aid



**Fig. 5. High-sensitivity AC VTVM features switch operated LC probe.**

There is a steadily increasing flow of high-fidelity audio equipment from the consumer to the service technician. Many technicians now realize that conventional audio troubleshooting-techniques are marginally useful in restoring an expensive, high-performance system to original specifications, because a critical audiophile with several hundred dollars invested in a music system can be painfully demanding; and, his satisfaction is your source of profit. The RCA Model WV-76A high-sensitivity VTVM (Fig. 5) should prove to be useful in any shop that intends to accept a heavy volume of audio repairs.

The VTVM can be used for checking the overall frequency response of an entire system or a single stage, for signal tracing, power and gain measurements, balancing push-pull stages, and for general audio-voltage measurements. The instrument also can be

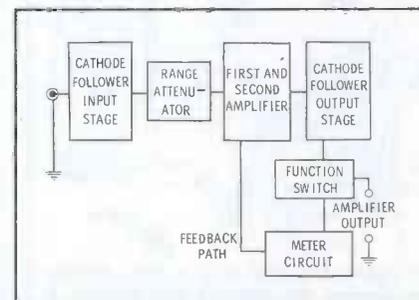

**Fig. 6. Block diagram of new VTVM.**

## RCA WV-76A Specifications

### Frequency Response:

WG-300B DIRECT  
 $\pm 1$  db 10 cps to 1.5 mc  
 WG-300B LO-CAP x10  
 $\pm 1$  db 10 cps to 500 kc

### AC-Voltage Measurements (WG-300B DIRECT):

Ranges 0 to 0.1, .03, .1, .3, 1 volt;  
 0 to 3, 10, 30, 100 volts  
 Accuracy  $\pm 5\%$  (full scale)

### DB Measurements

(0 db = 1 mw into 600 ohms):  
 Ranges -40, -30, -20, -10, 0, +10,  
 +20, +30, +40  
 Accuracy  $\pm 5\%$

### Input Characteristics:

At input connector  
 1 meg (shunted by 58 mmf)  
 WG-300B DIRECT  
 1 meg (shunted by 95 mmf)  
 WG-300B LO-CAP x10  
 10 meg (shunted by 13mmf)

### Preamplifier:

Output voltage  
 .8 volt output for .01 volt input  
 Output impedance  
 less than 400 ohms  
 Gain 38 db on 10-mv range

### Weight:

5 lb.

### Size (HWD):

7 $\frac{3}{8}$ " x 5 $\frac{3}{8}$ " x 4 $\frac{3}{4}$ ".

### Power Source:

105-125 volts AC, 50-400 cps; 35 watts.

### Price:

\$79.95.

used as a wide-range preamplifier with a gain of about 38 db. When used as an amplifier, the input signal is fed through the type WG-300B probe provided with the unit, and the output signal is taken from a terminal on the panel. Response is essentially flat from 20 cps to 500 kc. A block diagram of the WV-76A is shown in Fig. 6. The circuit is a simple, broadband voltage amplifier provided with a built-in meter-bridge circuit to read the established voltage.

The meter has two rms voltage scales (0-1 and 0-3) for voltage measurements and a separate scale for decibel measurements. A nine-position switch selects the proper range. A second switch selects the mode of operation: OFF, METER, or AMPLIFIER. Terminals are provided for amplifier-output and ground connections, and a screw-on connector accepts the probe.

Voltage measurements in AC circuits are straightforward using the WG-300B probe with its slide switch in the DIRECT position. With the probe switch in the LO-CAP x10 position, input resistance of the WV-76A is raised to 10 megohms, and the indicated scale reading must be multiplied by 10 to obtain the actual voltage.

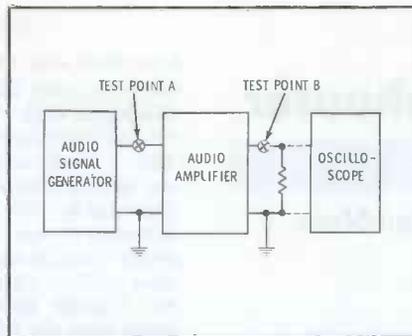


Fig. 7. Test setup for response checks.

When decibel readings are made, the actual scale value is valid only in the 0 db position of the range switch: In all other positions, the meter-scale reading must be added algebraically to the decibel figure indicated by the range-switch pointer. Relative decibel readings for a given voltage value can be read directly.

Accurate frequency-response evaluation of amplifiers, preamps, tone-control circuits, and other audio devices can be made using the test setup shown in Fig. 7. The input level measured at test point A with the WV-76A is maintained at a standard voltage level (by manual adjustment) regardless of the input frequency, and the voltage output measured at test point B is plotted graphically in decibel reference. The scope is not absolutely necessary, but it does provide a means for observing when distortion of the sine waveform occurs. Response measurements made with the WV-76A are valid only for pure sine-wave signals. Complete step-by-step procedures for this test and others are given in the manual which accompanies the instrument.

Our lab experience with this unit left us convinced that the scale is easy to read, the controls are positive in action, and the instrument itself is straightforward in design and easy to use. The action of the switch on the probe seemed less than positive, however, and easily slipped out of position unless care was taken to avoid touching it in use. ▲

For further information, circle 48 on literature card.

## now in our lab . . .

The latest test instruments being analyzed for future "Notes" columns:

- Lectrotech Model V7 Color Vectorscope
- RCA Model WT-115A Color CRT Tester
- SENCORE Model PS127 Oscilloscope
- Hickok Model 580 Tube Tester
- Heath Model IM-13 VTVM



# THE MAGIC OF COLORMAGIC TV ANTENNAS ADVANCED ENGINEERING DESIGN

BEST FOR COLOR AND BLACK AND WHITE



## Only Colormagic...

has been top-rated by independent consumer publication for broad band performance, gain, front/back ratio, beam width, impedance match, construction and ease of assembly.

## Only Colormagic...

has FHR which is the exclusive development of GC Electronics for process applied to all Colormagic series of antennas, to provide a resonating action within the elements of the fundamental harmonics of both the high and low bands.

## Only Colormagic...

has the outstanding Award Winning Carton Design in which all Colormagic series antennas are carefully packed.



## Only Colormagic...

has the endorsement from Philco, one of the leading manufacturers of TV receiving equipment. Colormagic antennas are recommended and approved for all Philco TV Color and black and white installations.



Write now for free four page color brochure which describes the entire Colormagic series of antennas.



**GC ELECTRONICS**  
 400 South Wyman Street Rockford, Illinois  
 Dept: BW

Circle 32 on literature card

December, 1964/PF REPORTER 63



# The Troubleshooter

answers your servicing problems

## It Blew Up

A customer had a 21AT4 picture tube which imploded spontaneously. He said, "It sounded like a bomb had gone off in the room." After seeing the set, with the wires in the yoke cut from the explosion, I shudder at the way some of these tubes are handled. Is there some information you can give me as to safety in handling and installing picture tubes? What could cause one to implode?

CLIFFORD TENNEY

Ronkonkoma, N. Y.

The implosion of a picture tube is a rare occurrence if correct handling precautions are observed. Of course, one will occasionally blow for unknown reasons, as in the case you mentioned. Usually, glass fatigue or a small, unnoticed scratch at a critical point on the tube is the cause.

Companies engaged in the manufacturing of picture tubes subject them to rigid tests of high temperature, air pressure, and many other severe stresses in an attempt to reveal any weakness that might cause the tube to implode.

A few simple rules to follow when handling, removing, or installing picture tubes are: Always wear safety glasses; don't set the tube down on a hard, rough surface; don't strain the neck of the tube; and, when you tighten the CRT mounting strap, tighten it for a snug fit but not so tight as to put a strain on the tube itself.


## COLOR COUNTERMEASURES

Symptoms and service tips from actual shop experience

Chassis: Zenith 26KC20, 25LC20, 25LC30

Symptom: Lack of convergence control during top and bottom vertical convergence adjustments.

Tip: A slight circuit modification will in most cases simplify top and bottom convergence adjustment. Referring to PHOTOFACT Folder 705-4 and the drawing below, change R102, the 220-ohm resistor connected to terminal "A" of the vertical output transformer, to a 330-ohm, 1-watt unit. Wire the 220-ohm resistor (just removed) in parallel with a silicon rectifier (Zenith part #212-27), and connect this network in series with the 330-ohm resistor—observing polarity as shown. Connect the other end to the junction of 100-mfd electrolytic C5, 4700-ohm resistor R101, and .47-mfd C51.

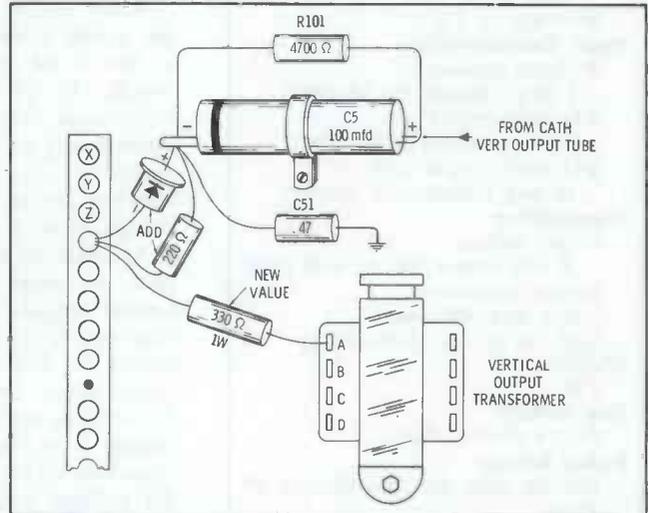

## Color TV Coil Exact Replacements

Cat. No.	Use	Mfr.	Part No.
6021	Chroma Bandpass Trans.	RCA	78887
6022	Chroma Bandpass Coil	RCA	78888
6023	Burst Transformer	RCA	100431/78886
6024	3.58 Mc. Output	RCA	78889
6025	Sync and Phase	RCA	78895
6026	Chroma Reference Osc.	RCA	78891
6027	3.58 Mc. Trap	RCA	78892
6028	3.58 Mc. Chroma Sync	RCA	78892
6029-R	First Chroma	RCA	1107853-1/105213
6030-R	Burst Amp	RCA	1107864-1/105214
6031-R	Video I.F.	RCA	106385
6032-R	Video I.F.	RCA	106386
6033-R	Video I.F.	RCA	106387
6034-R	Video I.F.	RCA	105292
6035-R	Video I.F.	RCA	105293
6036-R	Video I.F. and Trap	RCA	105294/1107858-1
6337-R	Horiz. Waveform	RCA	102195
6338-R	Horiz. Linearity	RCA	105196
7105-R	4.5 Mc. Sound I.F.	RCA	105286
7106-R	4.5 Mc. Sound I.F.	RCA	105287
7107-R	4.5 Mc. Quadrature	RCA	105288
7108-R	4.5 Mc. Sound I.F.	RCA	106381
7109-R	4.5 Mc. Sound I.F.	RCA	106382
7110-R	4.5 Mc. Quadrature	RCA	106383

Wide line of exact replacement coils for TV, radio, hi-fi—over 30,000 listings in Catalog 164 Cross Reference Guide—same day service on virtually all orders including special coils not listed.



## J. W. MILLER COMPANY

5917 South Main Street • Los Angeles, California 90003

See your local distributor for the full line of RF and IF coils, chokes, filters and transformers.

Circle 33 on literature card

## Save Time on PC Board Repairs!



Melted solder disappears up hollow tip into tube

### The ENDECO Desoldering Iron Removes Soldered Components in seconds... without damage!

Endeco melts solder, then removes it by vacuum • Leaves terminals and mounting holes clean • Resolders too • One-hand operation • Temperature controlled for continuous use • Ideal for use with shrinkable tubing • 4 tip sizes • Quickly pays for itself in time saved • Only \$18.75 net.

SMALLER SIZE AVAILABLE. SEE YOUR DISTRIBUTOR OR WRITE:




ENTERPRISE DEVELOPMENT CORPORATION

1102 E. 52ND • INDIANAPOLIS, IND. 46205

Circle 34 on literature card
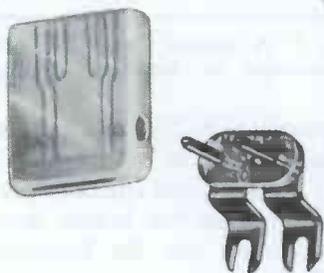
# ARE YOU IN THE TV SERVICE BUSINESS?

Here's a Calling Card that will guarantee customer satisfaction. While on your next service call, leave this MOSLEY calling card



## FAST \* SIMPLE \* SOLDERLESS

The MOSLEY 304 Input Adapter is an ideal connector for TV sets, boosters, etc. Just attach to the antenna terminal strip on chassis of TV and mate with the MOSLEY 311 Universal Transmission Line Socket.

## THE FINISHING TOUCH FOR A LASTING IMPRESSION

The installation provides a handy plug-in antenna line for Customer Convenience!

A moment of your time, at a cost of pennys, will buy you a Public Relations job that Pays Off In

- \* CUSTOMER SATISFACTION
- \* REPEAT CALLS
- \* REFERRALS

Send for your FREE **Mosley** Catalog. The one and only complete line of TV/FM accessories available on the market today!

Please send me your catalog containing the complete line of TV/FM installation accessories.

NAME .....  
 ADDRESS .....  
 CITY/STATE .....

**Mosley ELECTRONICS, INC.**  
 4610 NORTH LINDBERGH BOULEVARD  
 BRIDGETON, MISSOURI, 63044.

## Aircraft Radio

(Continued from page 35)



Fig. 6. Radio magnetic indicator gives all information on a single meter.

instrument is positioned by a gyro-stabilized compass, thus providing continuous heading. Radio direction (ADF) is provided on a wide needle, and omni bearing appears on the narrow needle. Hence, a pilot receives all navigation information on a single indicator.

## Instrument Landing System

The systems previously discussed allow an airplane to navigate point to point, but all-weather operations are impossible unless means are provided to facilitate a landing under conditions of minimum visibility. The instrument landing system (ILS) was adapted to worldwide standards after World War II. In this system, fixed beams which guide an airplane to the runway are radiated in two planes. It is usually unnecessary and undesirable for the aircraft to utilize the beams below a minimum ceiling of 200 feet; nevertheless, the fixed-beam system makes safe landings possible under almost all conditions.

The beam which allows the airplane to locate the runway laterally is called the localizer. The localizer ground antenna is usually located 1000 feet beyond the far end of the runway (opposite the approach end), and the center of the antenna array coincides with the center of the runway. The operating frequency is between 108 and 112 megacycles, and voice modulation is provided on the same frequency.

Vertical runway alignment is provided by a glide-slope beam lying in a plane usually inclined 3° from the runway. The glide-slope frequency is between 329.3 and 335 megacycles from an array located

# COMPARE Degaussing COILS

SAFE TO USE  
 NO EXPOSED  
 TAPE WINDINGS



**Walsco**  
 ELECTRONICS

No. 2590

# then buy WALSCO

- MOLDED HI-IMPACT CASE LASTS A SERVICE LIFETIME
- SAFE TO USE • NO EXPOSED TAPE WINDINGS
- MOMENTARY SWITCH ELIMINATES DANGER of "LEFT ON" CURRENT

Quality speaks for itself. See the only coil on the market with the hi-impact molded case, the case that eliminates any danger of electrical shorts or mal-function. Momentary switch couples convenience with safety. See it now. Ask your distributor about other WALSCO COLOR TV TOOLS and use the coupon to send for FREE literature on Walsco.....the Complete Line.

**WALSCO ELECTRONICS Co.**  
 DIVISION OF GC-TEXTRON ELECTRONICS, INC.  
 LOS ANGELES 18, CALIF., ROCKFORD, ILL., U.S.A.

Send to Walsco, Dept. 37, 400 S. Wyman, Rockford, Ill. Please send me the latest Walsco literature.

NAME .....  
 ADDRESS .....  
 CITY, STATE .....

**WE'RE EXPANDING!**

# MEN WANTED

**RF AMPLIFIER DESIGN ENGINEERS**

**ANTENNA ENGINEERS**

**MECHANICAL ENGINEERS**

**LABORATORY AND FIELD TECHNICIANS**

HERE IS AN OPPORTUNITY for qualified men to put their talent and abilities to use in a fast-growing corporation that is recognized as a leading manufacturer of TV and FM antennas and RF distribution systems. Expanded facilities and product lines require that we enlarge our engineering staff in the job categories outlined above. You will be working on exciting new products in one of the most modern, fully equipped electronics laboratories in the industry. (No military contracts.) Salaries are commensurate with experience and ability. There are numerous com-

pany benefits including a profit sharing plan, vacation plan and company-paid insurance. Our manufacturing plant and laboratory facilities are located in an attractive, friendly city on the beautiful Mississippi river where you and your family can really enjoy life to its fullest. Write stating your experience and an application form will be sent immediately to those persons who qualify. All inquiries will be held in strictest confidence. Address letter to: Personnel Dept., Winegard Company, 3000 Kirkwood, Burlington, Iowa.



WINEGARD COMPANY, 3000 KIRKWOOD, BURLINGTON, IOWA

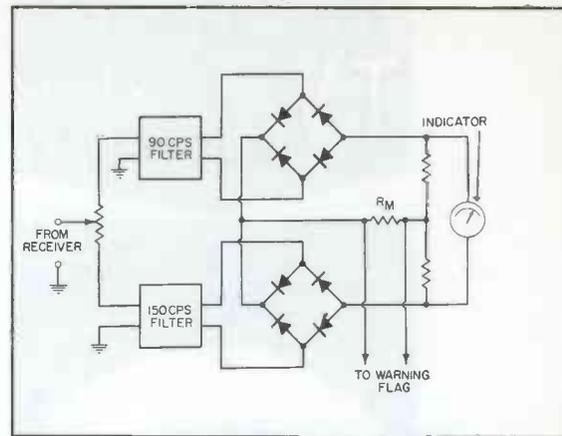


Fig. 7. A typical circuit for deriving glide-slope or localizer information.

approximately 750 feet beyond the approach end of the runway. Separate receivers and antennas are used to receive the two beams; however, to facilitate use, the localizer and glide-slope frequencies are paired together for any particular airport. In almost all cases, the same VHF receiver is used for omni and for ILS-localizer reception. When a pilot switches from one localizer frequency to another with a crystal-tuned VHF navigation receiver, relays are provided to also switch the glide-slope receiver to its correctly paired frequency.

Both the localizer and glide-slope beams appear as two narrow lobes which intersect on the correct course. One lobe in each beam is modulated with a 90-cps signal and the other with a 150-cps signal. The airplane flies along a path where the 90-cps and 150-cps signals are of equal strength.

A circuit for deriving glide-slope or localizer indication from a receiver is shown in Fig. 7. Audio output from the receiver is passed to two filters which separate the 90-cps and 150-cps components. The filtered signals are then rectified, and the resultant current energizes a galvanometer-type movement that provides the right-left or up-down indication to the pilot.

The presence of the 90-cps or 150-cps signal causes current flow in  $R_M$ , and this current is used as an indication to the pilot that the system is operative. A solenoid placed across  $R_M$  is energized when signal is present. A warning flag appears in a window cutout on the pilot's instrument when the solenoid is de-energized, indicating undependable signal reception.

**Table 1. Marker Indications**

Marker	Tone	Lamp Color
Airways (AM)	3000 cps	White
Outer (OM)	400 cps	Blue
Inner (IM)	1300 cps	Amber

**Marker Beacons**

The navigation systems discussed so far define paths along which an airplane may fly, but to complete a navigation system, a means must be provided to mark important points along the paths. Marker beacons operating on 75 mc are used for this purpose.


A marker beacon is simply a transmitter with an antenna array designed to radiate a sharply focused beam upward from the beacon location. Beacons placed along established airways (airway markers) are modulated with a 3000-cps tone. On an ILS system, one beacon (the outer marker) is placed about 4 miles from the runway on the localizer path and is modulated with a 400-cps tone. Another beacon (the inner marker) modulated by a 1300-cps tone is placed on the localizer path about 3500 feet from the touchdown point on the runway.

Marker equipment in the airplane consists of a 75-mc receiver and a means of converting the demodulated tone into sufficient power to light an indicator lamp—and provide aural output, if desired. A filter selects the particular tone, and a colored lamp lights (see Table 1).


Marker-beacon receivers are usually simple crystal-tuned superheterodynes, and good use can be made of solid-state devices. For example, the Narco MBT-2 marker receiver utilizes transistor circuitry, measures only 1½" x 3½" x 6", and weighs only 18 oz.

Marker-beacon, omnirange, and glide-slope receivers make it possible for an airplane to fly between two points and make a safe landing under almost all weather conditions. These three devices are the minimum required for all-weather flying. More elaborate installations also include automatic direction finder and weather radar.

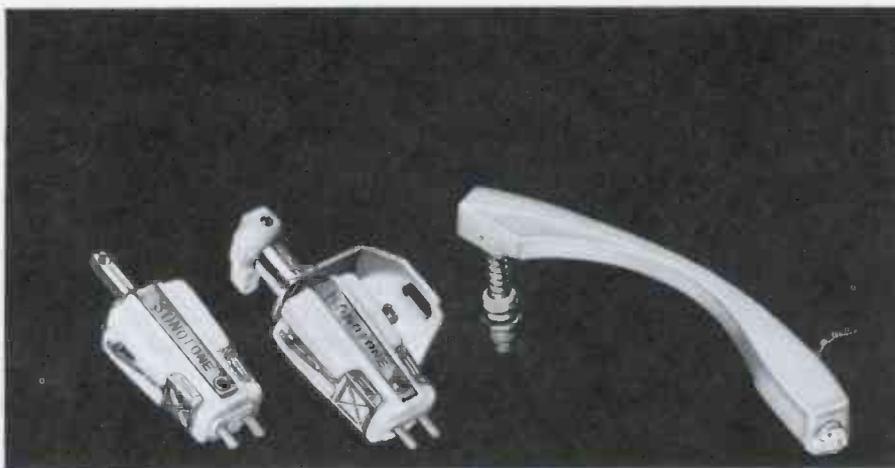As aviation becomes even more extensive, the use of electronics in aircraft communication and navigation will also grow. Therefore, it will become increasingly important that the progressive technician stay familiar with this subject. ▲



# How to turn crystal

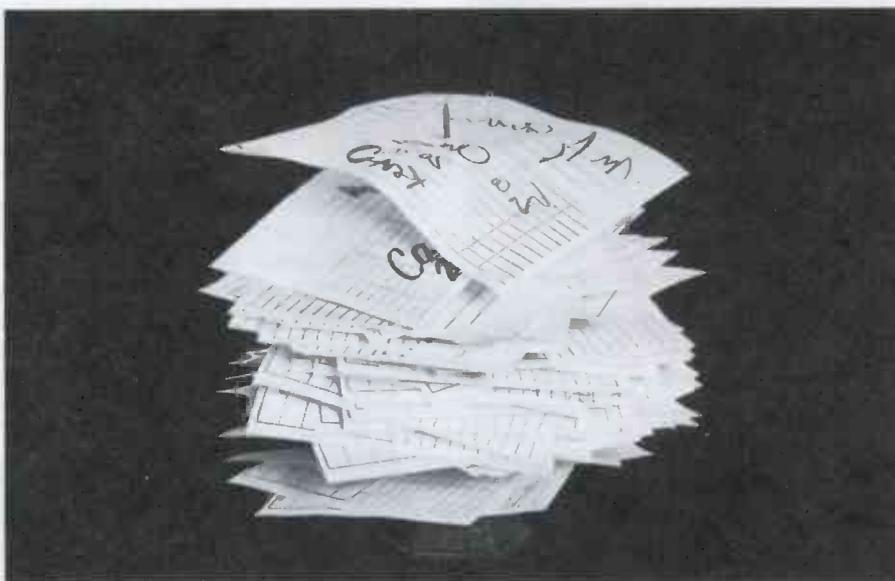

# into gold

You can strike it rich with the new Sonotone line of crystal cartridges. It offers direct replacements for "Ronette," "Vaco" and "BSR" models with typical Sonotone quality.

Here are the extras you get—New improved crystal elements for longer pickup life. Mono ("14T") and stereo ("20T") models. High output voltage. Modern turnover type for LP, 45 and 78 rpm records. Available with or without mounting brackets or turnover knobs to fit most arms.

Oh yes, they come in a slim, lightweight plastic tonearm, too. You have a choice of the mono ("14T") or stereo ("20T") cartridge. It's easy to install because it's prewired. It has a shielded cable, spring mounting post and a plated finger lift. It's complete with arm rest and all necessary hardware. Get details today. Write:


**SONOTONE**  
audio products

Sonotone Corp., Electronic Applications Div., Elmsford, New York  
Cartridges • Speakers • Microphones • Headphones • Hearing Aids • Batteries


Circle 38 on literature card

## Measuring Lo-Q

(Continued from page 33)

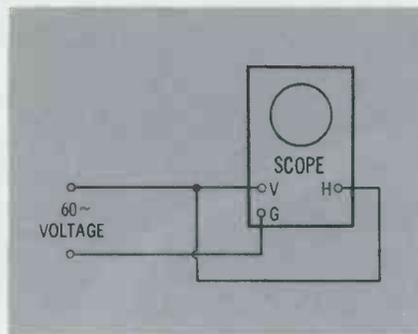

(A) Setup

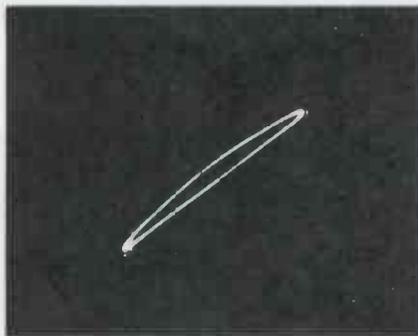

(B) Waveform

Fig. 9. Check scope for phase shift. will cause an error in pattern readings.

Phase shift in scope amplifiers at 60 cps is usually due to capacitor

trouble. Perhaps a grid-coupling capacitor has lost part of its capacitance; or, the trouble might be caused by a bad screen-bypass, cathode-by pass, or decoupling capacitor. Some scopes have a low-frequency boost circuit; check the boost capacitor in such a case.

Another type of amplifier distortion, without phase shift, is illustrated in Fig. 10. Note, however, the distorted diagonal line which points to nonlinear amplification. Try clearing up the distortion by reducing the test voltage used in the setup of Fig. 9. If the diagonal line is still curved at this point, there is trouble in the scope amplifiers. The cause may be a weak tube or low plate-supply voltage. Also check for bias or screen resistors that may have changed value.

### Conclusion

When properly performed, inductance checks using a scope are very useful in servicing work. Inductor measurements will show whether or not a unit is suitable for a given use. Tests made on inductors of known values will reveal shorted turns: Shorted turns *reduce* the inductance value and *increase* the

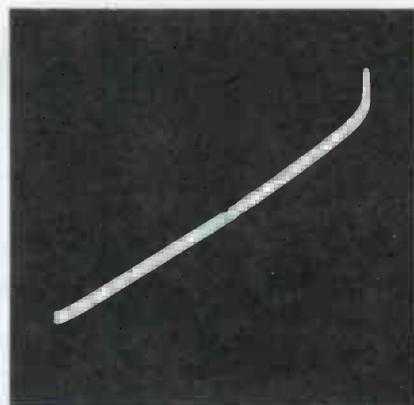


Fig. 10. Nonlinear amplifier pattern.

power factor. Remember that the test procedure discussed in this article is most suitable for low-Q inductors. In the case of high-Q inductors, a ringing test is preferred. The reason for this is that it's difficult to read the impedance pattern for a high-Q inductor—the two values indicated in Fig. 3 will fall so near the same figure that error in observation becomes serious.

There is a "twilight" area between low-Q and high-Q inductors in which both methods leave something to be desired. In such case, try both ringing and impedance patterns, choosing the method which affords the least error. ▲

Injectorall Super 100 tuner cleaner is...

**SAFE** for nylon shafts and plastics in tuners!

SUPER 100 is a fast drying spray cleaner and lubricant that is excellent for TV tuners. It cleans contacts sparkling clean and evaporates quickly leaving a lubricated coating.

**FREE!** 6 oz. spray can with 6 inch steel needle a \$1.95 value... when you buy a 16 oz. bench size SUPER 100 with steel needle.

Cat. No. 100-16-6—\$3.60 Net



cut out coupon and take to your distributor for

**FREE OFFER**

*You get FREE!*

1 Injectorall SUPER 100 (#100-6) 6 oz. size worth \$1.95 with the purchase of one 16 oz. SUPER 100.


Offer expires December 31, 1964.

Coupon void if taxed, prohibited or restricted by law. Cash value 1/20 of 1 cent.

INJECTORALL ELECTRONICS CORP.  
BROOKLYN 14, NEW YORK

## TV TUNERS

Rebuilt—Exchanged

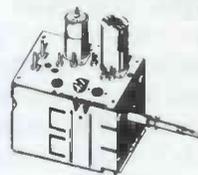

**\$950\***  
Plus Shipping Charges

All Makes—All Models

- Includes all parts except tubes
- 90 day full warranty
- All tuners cleaned, lubed, repaired and aligned with crystal controlled factory equipment to factory specifications, by factory trained technicians.
- 1 day service

Give model number of set and complaint. Include tubes, shields, cover and all parts, broken or not.

\*Practical Repairs


**VALLEY TV TUNER SERVICE**

5641 Cahuenga Blvd. PO 9-4730  
North Hollywood, California


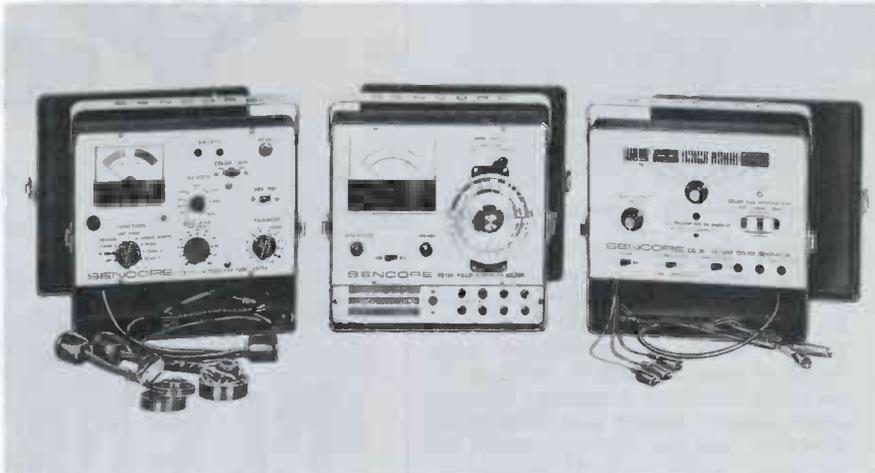
# Product Report

For further information on any of the following items, circle the associated number on the Catalog & Literature Card.



**Look-Alike Instruments (116)**

Three new testing units from **SENCORE, Inc.**, are housed in matched steel portable cases with removable covers. Covers are designed to be supported in an upright position (by the handles) when the instruments are placed on the bench; this permits easy viewing of operating instructions in the covers. The three new units are: an improved CRT tester, a solid-state all-channel TV field-strength meter, and a solid-state color pattern generator. None of the units requires warmup or stabilization time, and each has a compartment for storage of accessories and leads.



## New stick-on wiring system eliminates mechanical fasteners


New "Scotchflex" Brand Flat Cable System lets you install low-voltage hookups anywhere in seconds. Applies like tape to tile, concrete, brick, paneling, any surface. No stripping necessary . . . sharp "U" shaped prongs in the connectors pierce the insulation and establish firm contact with each of the round wire conductors. "Scotchflex" Cable saves installation time and provides better looking wiring on intercoms, call systems, hi-fi, and other low voltage systems. For details, write: 3M Co., St. Paul, Minn. 55119.

**3M** Electrical Products Division  
MINNESOTA MINING & MANUFACTURING CO.

"SCOTCHFLEX" IS A REGISTERED TRADEMARK OF 3M CO.

Circle 41 on literature card
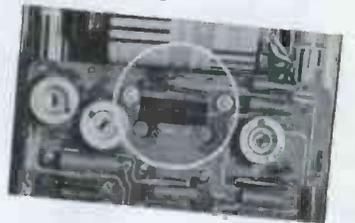
### Protects Meter Movements From All Overloads for LIFE!



## Metergard

For all VOMs and Voltmeters Installed in minutes on any meter, such as the Simpson 260 or Triplett 630, etc. Positively prevents meter movement burnout or damage regardless of overload. Accuracy not affected by more than 1/4 of 1%. No moving parts, nothing to wear out. End the time loss, expense and aggravation of meter movement repair due to damage or burnout.

ONLY **2<sup>95</sup>**

GUARANTEED

### Your VTVM will never need another battery for LIFE!



with

## Lectrocell

A miniaturized regulated power supply that replaces the battery in VTVM's. Furnishes 1.5 VDC for measuring resistance. Exact size and shape of battery it replaces. Installs in minutes . . . simply connect 3 wires and you're all set!

ONLY **3<sup>95</sup>**

GUARANTEED



See your distributor today; if he does not stock these units, send check or M.O. direct to DEPT. P-12


**LECTROTECH** INC.

1737 W. DEVON • CHICAGO, ILL. 60626

Circle 42 on literature card

December, 1964/PF REPORTER 69

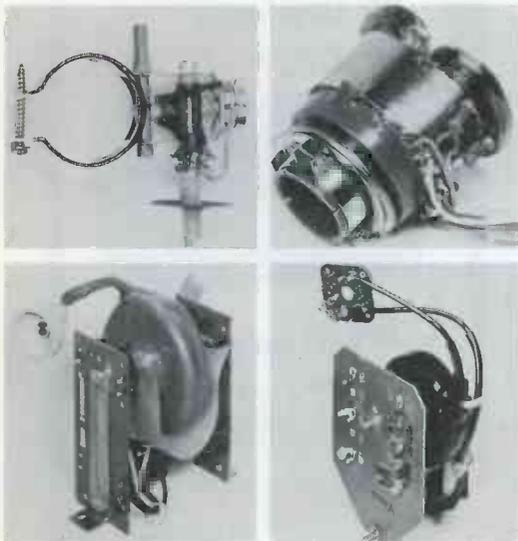Coming . . . in  
**PF REPORTER**  
next month



• **Horizontal Troubleshooting From A to Z**

8-Page Book Section: Update and consolidate your knowledge of horizontal sweep circuits.

• **Report on UHF Station Activity**

Learn what recent developments are taking place.

• **Servicing Auto Radio AGC**

Firm up your servicing techniques for solid-state receivers.

• **New Rules Spur Business Use of CB**

Recent FCC changes — do they affect your operation?

• **Symfact on 'BN6 Sound Detector**

... plus many more "meaty" servicing features, and of course . . .

**The Troubleshooter**  
**Notes on Test Equipment**  
**Dollar and Sense Servicing**




**Replacement Transistor (117)**

An exact replacement for the AR series power transistors, used in auto radios manufactured by Philco, is the Semitron Par 12 power transistor. The Semitronics Corp. transistor incorporates an extra length of insulated lead to facilitate installation, aluminum mounting clamps to insure positive contact with the external heat sink, and true hermetic sealing for reliability. List price is \$4.95; net is \$2.97.



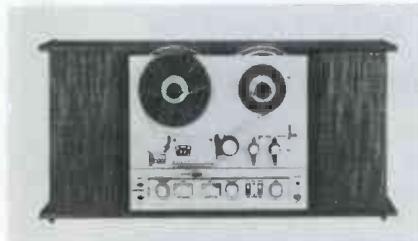**Speaker Display (118)**

Every "Celesta" series speaker is now being shipped in a box which converts into an attractive counter display. Both 8" and 12" Utah speakers are packed inside two-color cartons. The containers are only 1/2" larger than the speaker, requiring a minimum of counter space; also, the design techniques on both the inside and outside of the containers help to make the product sell itself.



**Stereo Recorder (119)**

The 1600 series of Designer tape recorders from Roberts have a frequency response of 30 to 18,000 cps at 7 1/2 ips and a signal-to-noise ratio of better than 45 db. The new table models feature fewer and more high styled controls than last year's line, giving a slim appearance. If desired, the recorders may be wall-mounted or recessed flush in a wall.

**CLEANS  
LUBRICATES  
PROTECTS**

**NEW!**

**FREE  
EXTENSION  
TUBE**



★ **NON-FLAMMABLE**  
★ **SAFE ON PLASTICS**

"CLEAN AND QUIET" CLEANS AWAY DUST, DIRT AND CORROSION..... on all electrical and electronic tuner controls, contacts and switches. A time saver for radio and TV servicemen. Just apply and work control. Part No. 94-06. net. \$1.49

WRITE FOR NEW SUPPLEMENT CATALOG NOW AVAILABLE. GC CATALOG FR-66-S.



**WALSCO ELECTRONICS**  
400 S. Wyman Street, Rockford, Illinois

Circle 43 on literature card

Enter my subscription to PF REPORTER 1264 and send me free book(s) checked.

- 3 Years \$10.00  2 Years \$8.00  1 Year \$5.00  
 The Troubleshooter's Handbook No. 2  
 Servicing Industrial Electronics  
 Servicing TV from Tuner to Picture Tube  
 Symfact Handbook

Check one of above for each year you subscribe

- Bill Me  Remittance Enclosed  
 Extend Present Subscription

Please Check Your Business Classification

- Owner, Mgr.  Employee  Service Mgr.  
 Independent Radio, TV Serviceman  Retailer with Service Department  
 Industrial Electronics Service  Other (Specify occupation and title)


Name \_\_\_\_\_

Firm \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip Code \_\_\_\_\_

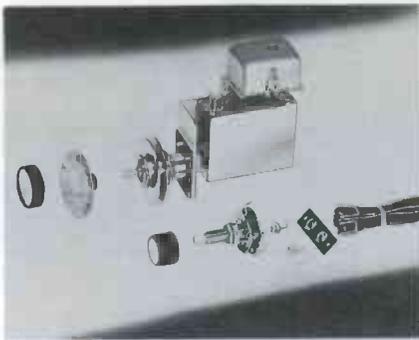Take this coupon to your distributor, or mail to: Howard W. Sams & Co., Inc., 4300 W. 62nd Street, Indianapolis, Indiana



**UHF Converter Kit (120)**

A compact, all-transistorized UHF television converter kit, UCT-051, permits customized in-set conversion of all console and table model (and most portable)

### INDEX TO ADVERTISERS

ATR Electronics, Inc. ....	13
Admiral Sales Corp. ....	46
Amperex Corp. ....	Cover 2
Antennacraft Co. ....	44
Antenna Specialists Co. ....	60
B & K Mfg. Co. ....	43, 45, 49
Div. of Dynascan Corp. ....	
Bussmann Mfg. Div. ....	24, 52
Castle TV Tuner Service ....	18
Channel Master Corp. ....	46, 51
Cleveland Institute of Electronics ....	47
ESCO Mfg. Co. ....	58
Electronics Communications, Inc. ....	62
Enterprise Development Co. ....	64
GC Electronics Co. ....	63, 70
Hickok Electrical Instrument Co. ....	16, 17
Injectorall Co. ....	68
JFD Electronics Corp. ....	14, 15
Jackson Electrical Instrument Co. ....	26
Jensen Industries ....	13
Jensen Mfg. Co. ....	21
Lafayette Radio Electronics Corp. ....	41
Lectrotech, Inc. ....	69
Littelfuse, Inc. ....	Cover 4
Mercury Electronics Corp. ....	40
Miller, J. W. Co. ....	64
Minnesota Mining and Mfg. Co. ....	69
Mosley Electronics, Inc. ....	65
Oxford Transducer Co. ....	50
Perma-Power Co. ....	61
Philco Corp. ....	22, 23
Planet Sales Corp. ....	58
Precision Tuner Service ....	46
RCA Electronic Components and Devices ....	53, Cover 3
Sams, Howard W. & Co., Inc. ....	19, 62
Sarkes Tarzian, Inc. ....	9
Seco Electronics, Inc. ....	51
Sonotone Corp. ....	67
Sprague Products Co. ....	11, 12
Switchcraft, Inc. ....	58
Sylvania Electric Products, Inc. ....	31
Valley TV Tuner Service ....	68
Walsco Electronics Co. ....	65
Winegard Co. ....	56, 57, 66, 71
Xcelite, Inc. ....	54

TV sets. The Standard Kollsman kit tunes all UHF channels and will operate with either series- or parallel-filament receivers. The UHF tuner is equipped with a transistorized IF amplifier which is tuned to feed channel 5 or channel 6 of the set's VHF tuner. The unit comes complete with installation instructions and mounting hardware.



**Midget Radio Transmitter (121)**

A shirt-pocket-size transmitter, capable of sending keyed signals across North America, weighs only 10 ounces including batteries. Developed by RCA, the transmitter operates on selected frequencies between 2 and 30 mc that are stabilized by body temperature. The user places a miniature metal container, linked to the transmitter, under his upper arm where a high degree of temperature stability exists. The crystal-controlled unit measures 2½" x 4" x 1½" and has a radiated power of 100 mw.



**Small-Screen Scope (122)**

A compact 3" wideband oscilloscope, suitable for servicing electronic equipment, including color and black-and-white television, is EICO's Model 435. The gun used in the flat-face CRT is the same as the one found in the 5" versions, thus giving greater sharpness and brightness to the smaller tube. This new instrument is priced at \$99.95 in kit form and \$149.95 in factory-wired versions. ▲

# Winegard

## Dealer of the month



### Pacific Antenna Service El Cajon, California

**Winegard Congratulates Pacific Antenna Service on their 15th year of continual growth and their distributor, Radio Parts Company, San Diego, Calif.**

How would you like to have a rig like L. G. Schlick, owner of Pacific Antenna Service? One of the largest antenna specialists in the country, Pacific Antenna Service sells and installs hundreds of antennas every month.

An exclusive Winegard dealer, Pacific constantly tests antennas both Winegard and competitive makes. Mr. L. G. Schlick recently wrote John Winegard as follows:

"Six years ago, after going from one antenna to another, we finally settled down with WINEGARD. Since that time we have never had a complaint against a WINEGARD antenna, and WINEGARD has doubled our business year after year.

"We have just completed tests with WINEGARDS against the new V type antennas, and also against a new \$79.00 antenna that was supposed to out-perform the new WINEGARD (Colortron model C44). We made the tests without amplifier and there was NO comparison. WINEGARD was out in front in every way—directivity, DB gain, front-to-back ratio, ease of assembly, and durability."

# Winegard Co.

Antenna Systems  
D3009L Kirkwood • Burlington, Iowa

Circle 44 on literature card

December, 1964/PF REPORTER 71



# FREE Catalog and Literature Service

\*Check "Index to Advertisers" for further information from these companies.

Please allow 60 to 90 days for delivery.

## ANTENNAS & ACCESSORIES

49. **ANTENNACRAFT**—Latest information on FM antennas, featuring new omnidirectional model for multiplex or monophonic broadcasts.\*
50. **CORNELL DUBILIER**—16-page instruction booklet on proper installation and usage of antennas, and rotors.
51. **FINNEY**—Catalog No. 20-291 gives information on single channel couplers.
52. **G. F. WRIGHT**—Catalog sheets on guy wire used with outside antenna installations.
53. **JERROLD**—16-page booklet describing latest TV-FM reception aids; includes antennas, antenna amplifiers, amplified couplers, UHF converters, and home distribution systems.
54. **JFD**—Literature on complete line of antennas for VHF, UHF, FM, and FM-stereo. Brochure showing converters, amplifiers, and accessories; also complete 64-65 dealer catalog.\*
55. **MOSLEY ELECTRONICS**—Illustrated catalog giving specifications and features on large line of antennas for Citizens band, amateur, and TV applications.\*
56. **MULTITRON**—Illustrated literature on FM stereo antenna No. MA-44.
57. **TRIO**—Brochure on installation and materials for improving UHF translator reception.
58. **ZENITH**—Informative bulletins on universal loudspeakers and a new line of log-periodic vee-type antennas for FM and monochrome or color TV.

## AUDIO & HI-FI

59. **ADMIRAL**—Folders describing line of '65 equipment; includes black-and-white TV, color TV, radio, and stereo hi-fi.
60. **ATLAS SOUND**—New 1964 catalog No. 564 contains illustrations and specifications on PA speakers, microphone stands for commercial and industrial installations, and other new products.
61. **BENJAMIN**—Brochure on *Miracord* record changers and *Elac* phono cartridges.
62. **DUOTONE**—Reference wall chart for replacement phonograph needles; also catalog on line of accessories.
63. **EUPHONICS**—Literature sheets on new low-mass phono cartridge and ceramic microphone.
64. **GIBBS SPECIAL PRODUCTS**—Folders describing principles of sound reverberation and *Stereo-Verb* reverberation units for automobiles.
65. **JENSEN**—New 24-page catalog No. 165-K illustrates and describes speakers and speaker system kits.\*
66. **NORTRONICS**—Engineering bulletins CEB No. 2 and CEB No. 9 give information on 3.75 ips tape operation and on silicon transistor recording amplifier.
67. **OAKTRON**—"The Blueprint to Better Sound" an 8-page catalog of loudspeakers and baffles giving detailed specifications and list prices.
68. **OXFORD TRANSDUCER**—Product information bulletin describing complete line of loudspeakers for all types of sound applications, including replacements for public address and intercom systems.\*
69. **PERMA-POWER**—New catalog sheet describing Ampli-Vox Model S-300 and Sound Crusier sound system Model S-310.\*
70. **QUALITONE**—Information on selling diamond needles and earning free gifts.
71. **QUAM-NICHOLS**—Catalog No. 64 listing over 30 speakers and transformers for sound system applications.
72. **ROBINS**—Form No. 163D describes self-merchandising display of tape accessories.

73. **SAMPSON**—Full-color catalog pages showing new line of Waltham transistor radios, tape recorders, and portable televisions.
74. **SONOTONE**—Colorful brochure on new *Sonomaster* Model RM-1 speaker system.\*
75. **SWITCHCRAFT**—New product bulletin No. 146 describing Q-G audio connectors.\*
76. **UNIVERSITY**—Public address catalog and information on various types of microphones.
77. **WATERS CONLEY**—Catalog sheet showing new line of stereophonic and hi-fidelity phonographs.

## COMMUNICATIONS

78. **AMECO**—New literature on 2 and 6 meter transmitter, and communications test equipment.
79. **PEARCE-SIMPSON**—Specification brochures on *Companion II* and *Escort* Citizens band transceivers.

## COMPONENTS

80. **BUSSMANN**—Bulletin SFB listing complete line of Buss and Fusetron small-dimension fuses by size and type; indicates proper fuse holders and gives list prices.\*
81. **ELECTRONIC DEVICES**—Bulletin on high-voltage selenium rectifiers for replacing rectifier tubes in color TV receivers.
82. **E-Z-HOOK**—Catalog sheets showing complete line of test connectors, cable harness binding posts, and test leads and clips.
83. **GC ELECTRONICS**—68-page industrial catalog FR-65-1 showing newly introduced products.\*
84. **INTERNATIONAL RECTIFIER**—Handbook with engineering data and specific applications for controlled rectifiers, zener diodes, and solar cells and photo cells.
85. **MUELLER**—Complete catalog No. 270 of electrical clips and insulators.
86. **ONEIDA**—Catalog on line of electronic components and replacement items.
87. **PERMACEL**—Bulletin describing line of plastic tape and plastic parts box.
88. **PRECISION RESISTOR**—Catalog No. 65 showing complete line of wire wound resistors.
89. **SARKES TARZIAN**—Handbook giving general descriptions of the construction, operation, and applications of silicon controlled rectifiers.\*
90. **SPRAGUE**—Latest catalog C-616 with complete listing of all stock parts for TV and radio replacement use, as well as *Transfarad* and *Tel-Ohmike* capacitor analyzers.\*
91. **TRW**—General catalog No. 164 covers all standard capacitors offered by company. Other technical information on tolerance, reliability, and other characteristics of capacitors.

## SERVICE AIDS

92. **CASTLE**—How to get fast overhaul service on all makes and models of television tuners is described in leaflet. Shipping instructions, labels, and tags are also included.\*
93. **OELRICH PUBLICATIONS**—16-page catalog of TV service order forms, service call tickets, phone message books, and many other items.
94. **PRECISION TUNER**—Literature supplying information on complete, low-cost repair and alignment services for any TV tuner.\*
95. **YEATS**—The new "back-saving" appliance dolly Model 7 is featured in a four-page booklet describing feather-weight aluminum construction.

## SPECIAL EQUIPMENT

96. **GREYHOUND**—The complete story of the speed, convenience and special service provided by the Greyhound Package Express method of shipping, with rates and routes.
97. **LECTROTECH**—Bulletins on new color TV test instrument, meter-protective devices, substitute for VTVM battery, and transistorized DC power supplies.\*
98. **VOLKSWAGEN**—Large, 60-page illustrated booklet, "The Owner's Viewpoint," describes how various VW trucks can be used to save time and money in business enterprises, including complete specifications on line of trucks.

## TECHNICAL PUBLICATIONS

99. **CLEVELAND INSTITUTE OF ELECTRONICS**—"Pocket Electronics Data Guides" with handy conversion factors, formulas, tables, and color codes. Additional folder, "Careers and Opportunities in Electronics," describes home-study electronic training program, including preparation for FCC license exam.\*
100. **RCA INSTITUTES**—64-page book, "Your Career in Electronics," detailing home study courses in TV servicing, communications, automation, drafting, and computer programming; for beginners and experienced technicians.\*
101. **HOWARD W. SAMS**—Literature describing popular and informative publications on radio and TV servicing, communications, audio, hi-fi, and industrial electronics, including special new 1964 catalog of technical books on every phase of electronics.\*

## TEST EQUIPMENT

102. **B & K**—Bulletin No. 124-R on new Model 1240 color generator. Catalog AP-21R describing uses for and specifications of Model 1076 Television Analyst, Model 1074 TV Analyst and Color Generator, Model 700 and 600 *Dyna-Quik* Tube testers, Model 445 CRT Tester-Rejuvenator, Model 960 Transistor Radio Analyst, Model 360 *V-O-Matic* VOM, Model 375 *Dynamic* VTVM, Model 1070 *Dyna-Sweep* Circuit Analyzer, and Model 230 Substitution Master.\*
103. **EICO**—New 32-page, 1964 catalog of test instruments, hi-fi components, tape recorders, and Citizens band and amateur radio equipment.
104. **LAFAYETTE**—New 516-page catalog featuring stereo hi-fi, Citizens band, test equipment, radio and TV tubes and accessories, and much more.\*
105. **HICKOK**—Complete description and specification information on newly introduced Model 662 installer's color generator, portable FM multiplex generator, Model 235A VHF-UHF field strength meter, and Model 800 tube tester.\*
106. **JACKSON**—Complete catalog describing all types of electronic test equipment for servicing and other applications.\*
107. **SECO**—New color folder describing complete line of test equipment, including color-bar generators, tube testers, and semiconductor testers.\*
108. **SENCORE**—New color catalog on complete line of company products; oscilloscopes, generators, testers, and many others.
109. **SIMPSON**—Complete 16-page brochure on entire line of electronic test equipment; also, catalog on line of panel meters.
110. **STANDARD KOLLSMAN**—Literature on VHF to UHF translator.
111. **TRIPLETT**—All new test equipment catalog No. 46-T showing complete line of VOM's, tube testers, transistor analyzers, and signal generators.\*

## TOOLS

112. **ADEL**—Literature on "Nibbling Tool" that cuts, notches, and trims round or irregular holes to any size over 7/16"; ideal for radio chassis, templates, or shims.
113. **ARROW FASTENERS**—Catalog page showing three wire and cable staple-gun tackers with grooved blade especially for fastening of wires and cables up to 1/2" in diameter.
114. **CHICAGO MINIATURE**—Complete miniature lamp catalog, including sections covering subminiature, ultra-miniature, and new line of T-2 type lamps.
115. **ENTERPRISE DEVELOPMENT**—Time-saving techniques in brochure from Endeco demonstrate improved desoldering and resoldering techniques for speeding up and simplifying operations on PC boards.\*

# USE THE HANDY CARD BELOW TO OBTAIN FREE CATALOGS & LITERATURE

As a service to its readers, PF REPORTER makes this postpaid card available for your convenience in obtaining current manufacturers' literature.

To use the card simply:

- Circle the numbers corresponding to the numbers of the items appearing either on page 72 or in the "Product Report" department.
- Print your name and address and check your occupation in the spaces provided.
- Tear out lower half of this insert and place in mailbox.

Note the deadline date — Requests received after this cannot be handled.

**Subject Index on Reverse Side**

**DECEMBER, 1964**

Please indicate number of items you have circled →

OFFER EXPIRES FEBRUARY 1, 1965

1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20	21	22
23	24	25	26	27	28	29	30	31	32	33	34	35	36	37	38	39	40	41	42	43	44
45	46	47	48	49	50	51	52	53	54	55	56	57	58	59	60	61	62	63	64	65	66
67	68	69	70	71	72	73	74	75	76	77	78	79	80	81	82	83	84	85	86	87	88
89	90	91	92	93	94	95	96	97	98	99	100	101	102	103	104	105	106	107	108	109	110
111	112	113	114	115	116	117	118	119	120	121	122	123	124	125							

Print plainly or type below

Name \_\_\_\_\_

Firm \_\_\_\_\_

Firm Address \_\_\_\_\_

City \_\_\_\_\_

Zone \_\_\_\_\_

State \_\_\_\_\_

Did you receive this issue through

Distributor

Subscription

Please check business classification:

Independent Radio, TV Serviceman

Full time  Part time

Retailer with Service Department

Industrial Electronics Service

Owner or Manager

Service Manager

Employee

Other (Specify occupation and title)

### Subscription Offer

Enter my subscription to PF REPORTER

3 Years \$10.00  2 Years \$8.00  1 Year \$5.00

Bill Me  Remittance Enclosed

Extend Present Subscription

FIRST CLASS

PERMIT No. 1076

Indianapolis, Ind.

**BUSINESS REPLY MAIL**

No Postage Necessary if Mailed in the United States

**POSTAGE WILL BE PAID BY—**

*Reader's Literature Service Dept.*

**PF REPORTER**

4300 WEST 62ND STREET

INDIANAPOLIS, IND. 46206

**BOOK REVIEW**

*Mathematics for Electronics and Electricity* .....44

**COMMUNICATIONS**

Aircraft Radio  
—curing problems in .....34  
—direction finders, automatic .....34  
—instrument landing systems .....35  
—marker beacons .....67  
—omnirange receivers, VHF .....34  
Transmitter, midget .....71

**FM STEREO**

Composite signal .....44  
Demodulator circuits, servicing .....42  
Indicator .....47  
Transmitted signal .....42

**GENERAL SERVICING**

Callbacks, preventing .....48  
Chemicals .....13  
Filter replacement .....52  
Measuring inductance of low-Q coils .....32  
Multiplier designations for capacitors .....13  
Replacement-type transistors .....70

**INDEX**

1964 Annual Subject Reference Index .....1

**INDUSTRY REPORT**

New York Hi-Fi Show .....40

**RADIO**

Guide to radio & hi-fi tubes .....20  
Troubleshooting methods for  
—body signal injection .....37  
—generator signal injection .....37  
—oscillators .....37  
—voltage measurement .....36  
—total-current measurement .....36

**TAPE RECORDERS**

Distortion and low volume in .....58  
Recording head .....55  
Servicing small portables .....55  
Speed problems in .....55

**TELEVISION**


Convergence, lack of .....CCM 64  
Implosion of picture tubes .....TS 64

**TEST EQUIPMENT**

Color TV analyzer, Mercury Model 900 ..60  
Tube and Transistor Tester, EICO Model 667 .....59  
VTVM, RCA Model WV-76A .....62  
(Note: Code letters TS and CCM indicate *The Troubleshooter and Color Counter* measures, respectively.)

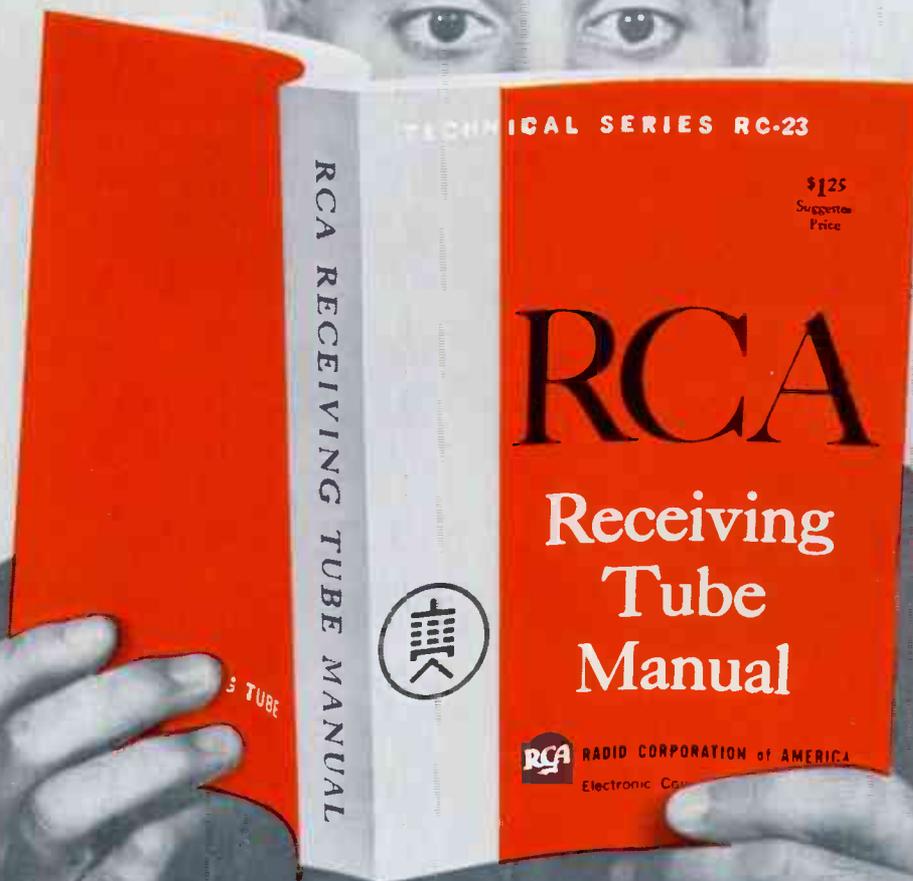**SYMFAC**

Switch tuner, nuvistor RF amplifier .....27



**You can't put it down!**

**THE BRAND NEW RC-23!**

**Latest and best edition of the famous RCA Receiving Tube Manual**

**Look at the great new features of the best selling tube manual in the industry:**

- ★ A record 608 data-packed pages
- ★ In addition to data on over 1,000 receiving tubes, the RC-23 includes data on color and B&W picture tubes, voltage-reference tubes, voltage-regulator tubes
- ★ New format, new type-face for easier reading
- ★ Popular circuit section with its many timely, practical tube applications
- ★ Revised and expanded Applications Guide covering 42 specific function classifications

**Now available from your local authorized RCA Tube Distributor**

RCA ELECTRONIC COMPONENTS AND DEVICES, HARRISON, N. J.



**The Most Trusted Name in Electronics**



# FUSE IMPULSE

**NEW FOR  
QUICK PROFIT ON  
YOUR COUNTER**



10 fuses  
Not 5—Not 6  
But 10 fuses  
in this assortment  
for widest coverage in fuse  
replacement  
in any auto!  
A vital necessity  
in every glove  
compartment

THESE NEW "SEE-THROUGH" EMERGENCY FUSE KITS COME PACKED 24 TO A CARTON—EACH CARTON INCLUDES WALL/COUNTER DISPLAY CARD. AVAILABLE FROM YOUR LITTELFUSE DISTRIBUTOR.

# LITTELFUSE

DES PLAINES, ILLINOIS

Circle 45 on literature card

[www.americanradiohistory.com](http://www.americanradiohistory.com)