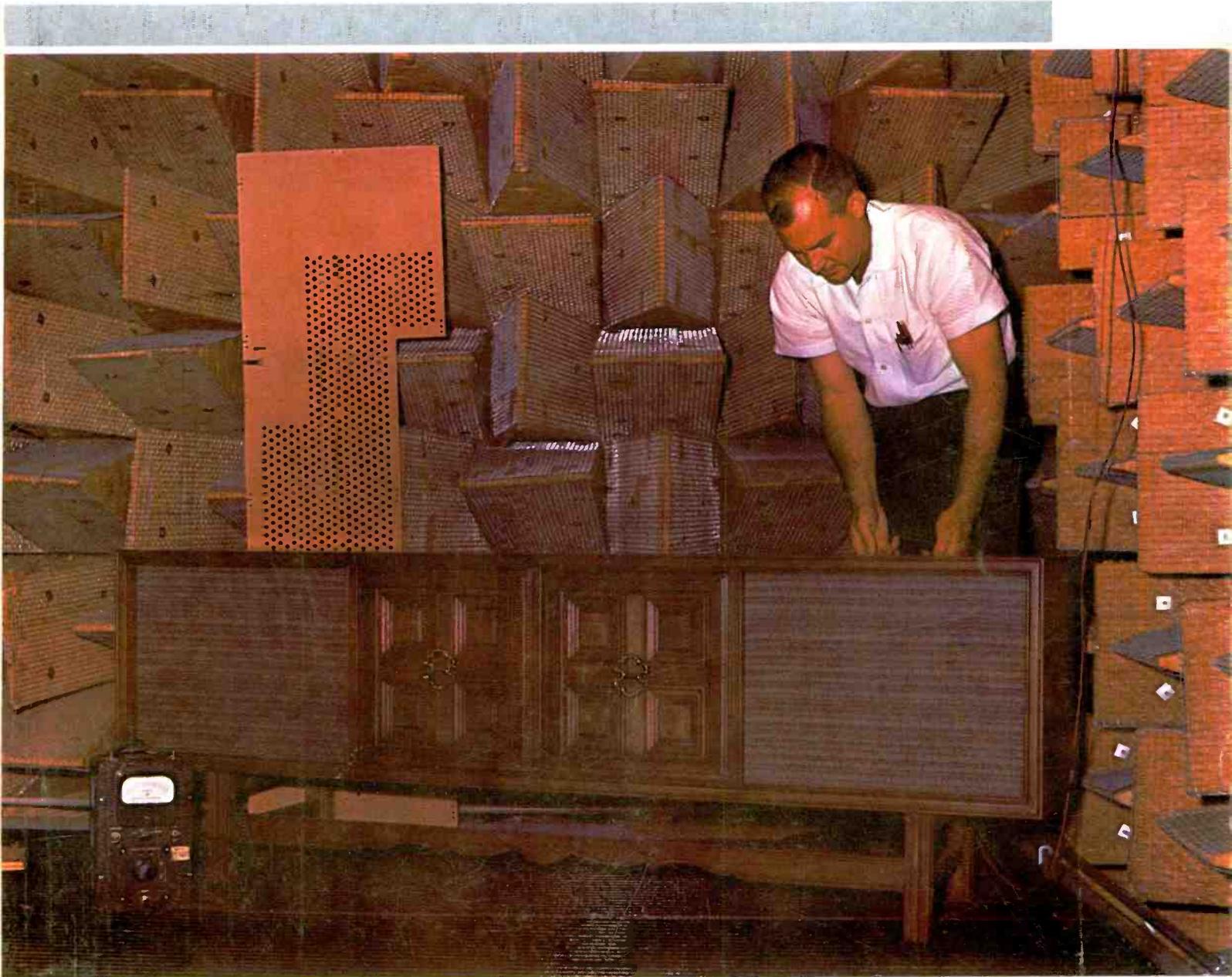




# PF Reporter™

PHOTOFACT

*the magazine of electronic servicing*



IA 2L 1104 1266  
WM. M. DAVIS  
RAD. & TV SERV.  
418 RIVERSIDE AVE.  
CANNON CITY, COLO.

### Special AUDIO Issue

- Audio Servicing From A to Z
- Make Money in Sales, Rentals, Leases
- Stereo With Transistors
- Acoustics Can Be Measured
- Plus other servicing features

# 9

*money-saving*

## NEW REASONS FOR BUYING EICO


UNCOMPROMISING ENGINEERING AT LOWEST COST ■



**1** New Model 965 - FaradOhm Bridge/Analyzer. 9-range, low-voltage capacitance-resistance bridge safely measures even 1-volt electrolytics. Metered bridge balance, leakage test voltage (6 DC VTVM ranges 1.5-500 V), leakage current (11 DC VTAM ranges 0.15 ua-15 ma). DC VTVM & VTAM externally usable. **\$129.95 wired.**



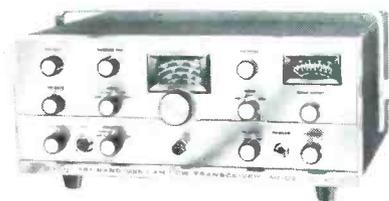**2** New Model 342 - FM Multiplex Signal Generator. Design lab quality. Both composite audio and FM RF outputs. Inputs for stereo audio source for store demonstrations, critical A/B listening tests. **\$149.95 wired.**



**3** New Model 753 - The one and only SSB/AM/CW Tri-Band Transceiver Kit. 200 watts PEP on 80, 40 and 20 meters. Receiver offset tuning, built in VOX, high level dynamic ALC. Unequaled performance, features and appearance. Sensionally priced at **\$179.95 kit, \$299.95 wired.**



**4** New model 3566 - All Solid-State Automatic FM MPX Stereo Tuner/Amplifier, kit or wired. No tubes, not even nuvistors. Delivers 112 watts IHF total to 4 ohms, 75 watts to 8 ohms. Completely pre-wired and pre-aligned RF, IF and MPX circuitry, plus plug-in transistor sockets. **\$219.95 kit (optional walnut cabinet \$14.95), \$325.00 wired including walnut cabinet. UL approved.**



**5** New Model 435 - D-C Wideband Scope. Top-quality DC-4. 5Mc scope with 3" flat-face CRT, Zener calibrator. Outperforms 5" scopes three times its size, facilitates on-location color TV and other servicing. **\$59.95 kit, \$149.95 wired.**



**6** New Model 779 - Sentinel 23 Dual Conversion 5-watt CB Transceiver. All crystals provided for 23 crystal-controlled transmit and receive channels. Delta tuning for receiving off-frequency transmissions. Panel switches for standby and use as 3.5 watt PA system. Transistorized 12VDC & 117VAC dual power supply. **\$169.95 wired only.**



**7** New Bendix NAVIGATOR 420 - BFO for CONSOLAN navigation, antenna post for pulling-in weak signals, illuminated dial for night navigation. Battery saver cord permits use of external 6 VDC sources. **\$99.95 complete.**



**8** New Doormatic 4000 - Automatic Garage Door Opener. Quick, dependable, silent radio-controlled operation of garage doors with exclusive TONECEIVER (audio modulated transmitter and receiver). System includes garage door mechanism, electronic control box with radio receiver, transistorized portable transmitter, and all mounting hardware. Furnished completely wired, UL approved. **\$59.95 mechanism only. Complete ready to install only \$159.95.**



**9** New Model 380 - Solid State NTSC Color Generator generates exact NTSC color signals individually and all required dot-bar patterns. Super-compact, 4 pounds light. Instant operation. **\$109.95 kit, \$159.95 wired.**

Over 3,000,000 EICO instruments now in use! Preferred by engineers, scientists, technicians and students. EICO equipment is available nation-wide through 2500 EICO dealers.

Send for FREE catalog describing the full EICO line of 200 best buys. EICO, 131-01 39th Ave., Flushing, N.Y. 11352.

1945-1965: TWENTY YEARS OF LEADERSHIP IN CREATIVE ELECTRONICS

Circle 1 on literature card

# audio servicing

## from A to Z

Circuits and how to troubleshoot them.

by David I. King

As stereophonic FM radios, record players, tape recorders, and massive solid-state home entertainment centers become increasingly popular, it is apparent that public interest in audio products is rapidly growing. Today, systems of types which once were owned by only the most sophisticated audiophile are becoming common in many homes.

To capitalize on the opportunity that servicing audio systems presents, the service technician needs only: the equipment that is normally used for servicing radio and TV audio circuits (which includes an audio signal generator), a basic understanding of audio theory (ranging from the oldest to the most modern circuits), and a knowledge of troubleshooting techniques which will produce rapid, efficient repairs.

### General Service Techniques

There are many techniques commonly used to isolate trouble in audio circuits. One of the most common methods is the "hum" or "click" test, which is accomplished by touching a finger or a screwdriver to the grid of the output stage. A loud "click" or "hum" from the speaker indicates the stage is operating. The serviceman then moves to each preceding stage in succession until the dead stage is found.

While this method is excellent for rapid service of table-model radios, it could prove disastrous if tried on the preamp of a powerful stereo amplifier using large speakers—the expensive woofers might be damaged by the transients and hum. When servicing transistor circuits, the low input impedance makes it difficult to induce significant hum in medium- and high-level stages. Too, in

a crowded printed circuit the possibility of shorting the transistor base to the collector with a screwdriver makes the "click" test inadvisable for transistor servicing.

With the high power and wide bandwidth common in modern high-quality vacuum-tube and solid-state audio equipment, certain precautions must be taken while servicing. Replacement of the speaker with a terminating resistor will not only protect the speaker (and the technician's ears) from loud transients accidentally introduced while troubleshooting, it will make frequency-response checks of the amplifier more accurate by eliminating phase shift caused by changes in loud-speaker impedance. For proper operation, the terminating resistor must be large enough to dissipate all the audio power produced by the amplifier, and it must match the output impedance. Most audio test equipment was designed originally for checking vacuum-tube equipment; special precautions must be taken to insure that, for example, signal-generator output voltage is not too high for low-level transistor

circuits. Unlike vacuum tubes, transistors can be destroyed by small overloads. To prevent damage from AC voltages introduced by ground loops, all equipment attached to transistor circuits must be properly grounded.

Either signal tracing or signal injection can be used to find defective stages; both methods require the same equipment, but the techniques are opposite. Signal tracing involves the use of a signal generator feeding the input of an audio amplifier. An oscilloscope is then used to trace the signal from the input toward the output until the defective stage is found. In contrast, signal injection involves the use of an oscilloscope tied to the output of the amplifier. Signal-generator output is injected first at the final stage; then, it is injected at preceding stages until the defective stage is found.

Although either type alone is quite useful, a combination of sine- and square-wave tests will give visible scope indications of most forms of distortion. Sine-wave checks will detect nonlinearity causing harmonic distortion, whereas square-

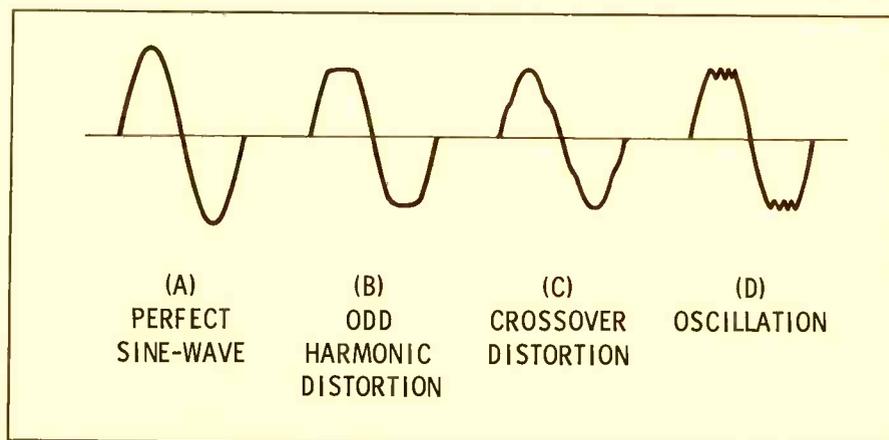


Fig. 1. Amplifier sine-wave outputs show various types of harmonic distortion.

wave checks will display phase shift causing frequency distortion.

Fig. 1 shows a normal sine wave compared to sine waves that have undergone various forms of distortion. In Fig. 2, a perfect square wave is compared to square waves that have been altered by phase shift. Circuit design will determine normal sine- and square-wave response of an amplifier. For example, while it is normal for a low-priced portable radio to display some harmonic distortion and degradation of a 1000-cps square wave, any sine-wave distortion for 20 to 20,000 cps or phase shift of square waves from 300 to 2000 cps would be an immediate indication of malfunction in a high-quality system.

If harmonic distortion is less than 10%, it is hard to detect with a normal sine-wave display. However, the test setup shown in Fig. 3 can be used to display as little as 1% harmonic distortion. With this arrangement, phase shift can be detected also.

The line in Fig. 3A will tilt to the left or right depending upon whether the output of the amplifier is in phase or 180° out of phase with the input. Care must be taken to insure that the scope introduces no distortion. Initially bypass the attenuator and amplifier to be certain that with the amplifier out of the circuit the line is straight and there is no phase shift. To prevent phase shift within the test setup, the attenuator and terminating resistor must be purely resistive—carbon or *noninductive* wirewound resistors must be used.

Nonlinearity within the amplifier will cause a change in the vertical-deflection rate. The horizontal-sweep

amplifier is fed directly by the sine-wave oscillator; hence, the horizontal-deflection rate will not be distorted and will exceed the vertical-deflection rate. The result is the deviations from a straight line shown in Figs. 3B and 3C.

If phase shift within the amplifier equalled 90°, the pattern produced would be circular; but phase shift seldom equals 90°, so the resulting pattern is elliptical. Phase shift (Fig. 3D) should not be noticeable except at the limits of the amplifier frequency-response characteristics. Any flattening of the elliptical trace is an indication of amplitude distortion. Kinks or curves within the ellipse indicate the presence of hum, noise, or oscillation.

All checks of amplifier frequency response must be made with tone controls set for flat response and all equalization (where used) switched out of the circuit. Otherwise the results of any test will be misleading.

After the stage causing trouble is found, checks are needed to isolate the defective component. An understanding of circuit function and characteristics is needed for troubleshooting individual stages. To cover the various audio circuits in use, the circuits have been classified as to the signal level at which they operate. The three divisions are: (1) Low-level circuits, which are the input stages; (2) medium-level circuits, which drive the final stages; and (3) high-level circuits, which supply power to the speaker. By analyzing common vacuum-tube circuits and comparing them to the newer transistor circuits, the serviceman can develop the basic knowledge of audio circuits that is essential for rapid troubleshooting.

## Low-Level Circuits

Fig. 4A shows a common-cathode amplifier. This circuit is often used as the preamplifier in high-quality audio circuits, because it has a high input impedance, high voltage gain, and low distortion. Input signal is developed across the 100K grid resistor (R1) and fed to the grid of V1. DC voltage drop across R2 develops negative grid bias by making the cathode positive with respect to the grid. R2 is sometimes unby-passed to introduce some degeneration which improves linearity. The output signal is developed across plate load resistor R3, then fed via C1 to the next stage. C2A and C2B together with R4 and R5 serve as a decoupling and voltage dropping network.

The circuit shown in Fig. 4B is primarily used as the first audio stage for AC-DC table radios. For small input signals this circuit is linear and has high gain. Bias is developed by electron emission from the cathode striking the control grid. A small negative voltage (.5 volts) results across the high-resistance (3.3 meg) grid resistor R1. In all other respects this circuit functions in exactly the same way as the circuit in Fig. 4A.

Grounded-grid amplifiers (Fig. 4C) are occasionally used instead of an input transformer to provide low input impedance and high output impedance. In the mobile radio circuit shown in Fig. 4C, variable resistor R1 is actually a carbon microphone; there is no need for an input transformer or separate carbon-microphone power supply. Often the signal is coupled by C1 and developed between grid and cathode by R1. In these cases R1 is a fixed resistor. As the cathode is normally positive with respect to the grid, bias circuitry is simplified. Instantaneous grid-to-cathode voltage still controls tube conduction, but the cathode voltage is varied instead of the grid voltage. The grid remains at ground potential. Also, there is no phase inversion; the amplified plate signal developed across load resistor R2 is in phase with the cathode signal. Again, C2 is the coupling capacitor to the next stage.

The transistor equivalent of the common-cathode amplifier, the common-emitter amplifier, is shown in Fig. 5A. This circuit is widely used

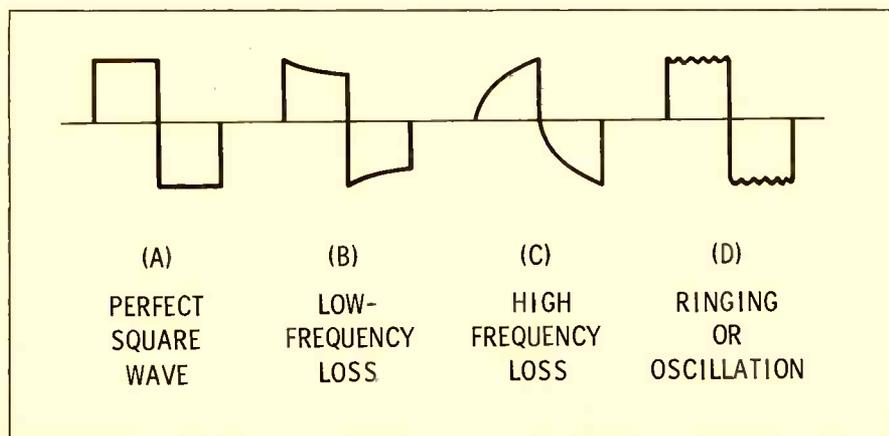


Fig. 2. Amplifier square-wave outputs show different types of phase distortion.

in low-level transistor circuits because of its flexibility, stability, and high gain. If circuit values such as coupling-capacitor size are noted, the low impedance common to transistor circuits become apparent. Input impedance for a typical common-emitter circuit ranges from 20 to 5000 ohms. Transistors are operated primarily as power amplifiers; gain for these circuits is expressed in db as power gain. In contrast, gain for low-level vacuum-tube amplifiers is usually expressed in db as voltage gain.

C1 (Fig. 5A) couples the input signal to the base of X1; the base is forward biased  $-.1$  volt by voltage divider R1-R2. Load resistor R4 develops the amplified and inverted output signal. C3, a 10-mfd electrolytic, then couples the output to the following stage. Protective biasing is provided by R3; C2 prevents degeneration.

Like its vacuum-tube counterpart, the grounded-grid amplifier, the common-base amplifier is used as a transformerless matching circuit. In Fig. 5B, the signal is coupled by C1 and developed across R1 to control base-emitter and, thus, collector-emitter current. C2 and C4 keep the base and emitter supply at AC ground; resistors R2 and R3 form a voltage divider to forward bias X1. The output signal, which is in phase with the input signal, is developed across R4 and coupled by C3 to the next stage.

### Servicing Low-Level Circuits

All defects in amplifier circuits can be classed as one or more of the following: (1) low gain, (2) hum, (3) distortion, (4) noise, and (5) oscillation. Often these defects occur in a combination, such as hum and distortion or noise and oscillation.

Low-level vacuum-tube amplifiers are particularly susceptible to hum and noise. Hum may be externally introduced by ground loops or can be caused internally by heater-cathode leakage or poor power-supply filtering. One rapid method of tracing hum is to bypass points in the signal path to ground with a 10-mfd capacitor. Bypassing pin 7 (the grid) of V1A in Fig. 4A will eliminate the hum if its source precedes this stage. Should the hum be caused by defects within this stage, it will

not decrease; if heater-cathode leakage in V1A is causing the hum, bypassing the grid will slightly increase hum output. Heater-cathode leakage should immediately be suspected when hum is found in a grounded-grid amplifier (Fig. 4C); the very low input impedance reduces the probability of externally induced hum.

The quickest test for open or dried-out filter electrolytics is to bridge them with a unit known to be good. Sometimes hum is introduced by leakage between sections of a multisection electrolytic; here, bridging will not cure the trouble.

Partial or complete loss of gain is usually caused by vacuum-tube defects. Voltage checks on the cathode, grid, and plate of V1A (Fig. 4A) should indicate a defective tube. With a plate-to-grid or plate-to-cathode short, the plate will be at a low voltage and cathode voltage will increase. A grid-to-cathode short will slightly increase cathode voltage (the grid will be at cathode potential) and decrease plate voltage. Open elements or complete loss of emission can be detected rapidly because the plate will be at B+ voltage.

Distortion is caused by operation outside the vacuum-tube's linear range. The most usual causes of non-linearity are grid current, grid cutoff, or plate saturation. Excessive drive can cause all of these and must be remedied. If the input signal is normal, nonlinearity in the grid circuit is a result of improper bias. A gassy tube is a common cause of grid current. Also, a leaky inter-stage coupling capacitor will place

a positive voltage on the grid and cause grid current.

Microphonic tubes, noisy controls, and poor connections are the most common causes of noise in vacuum-tube circuits. Watching for noise on the scope while tapping around the circuit with a pencil eraser will indicate most sources of noise.

Oscillation in an audio amplifier will not always be an audible howl. Sometimes the only audible evidence will be edginess and distortion; an oscilloscope will provide the most reliable detection—see Fig. 1D. Since oscillation usually involves several stages, if negative feedback is used check the feedback network first. Remove any input signal to prevent overload, then disconnect the feedback circuit; in Fig. 4A it is tied to the junction of R2 and the cathode of V1A. If oscillation ceases, a component in the feedback path has changed value. Should oscillation continue, check for an open bypass capacitor or ungrounded shield. When all else fails, try extra shielding. An increase in power supply impedance caused by the opening of an electrolytic will allow motorboating (low-frequency oscillation) to occur; as with searching for hum, bridging with a good electrolytic will usually pinpoint the defective component.

Transistor circuits are not subject to many of the malfunctions that occur in vacuum-tube circuits. There is no filament voltage required, and low impedances prevent electrostatic pickup; so, hum is almost nonexistent. Microphonics cannot be generated by transistors so all noise is

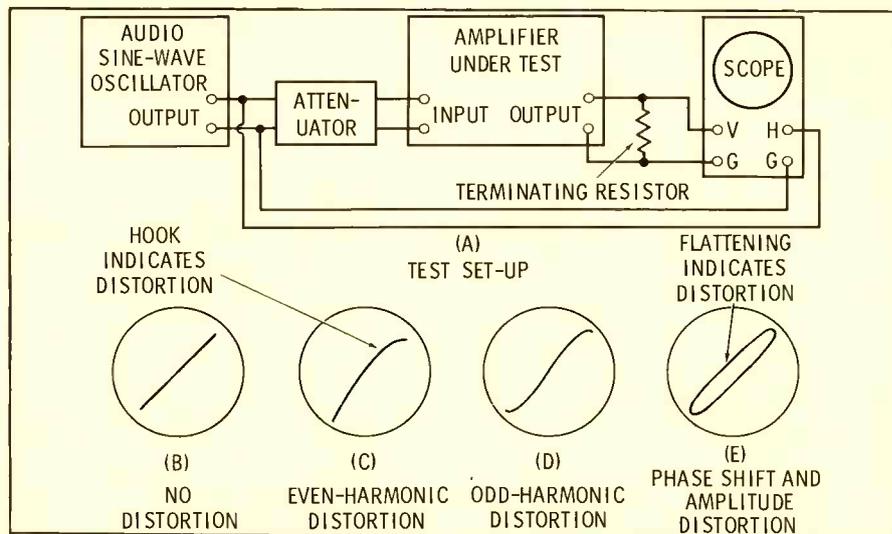


Fig. 3. Test setup will effectively show phase shift and amplitude distortion.

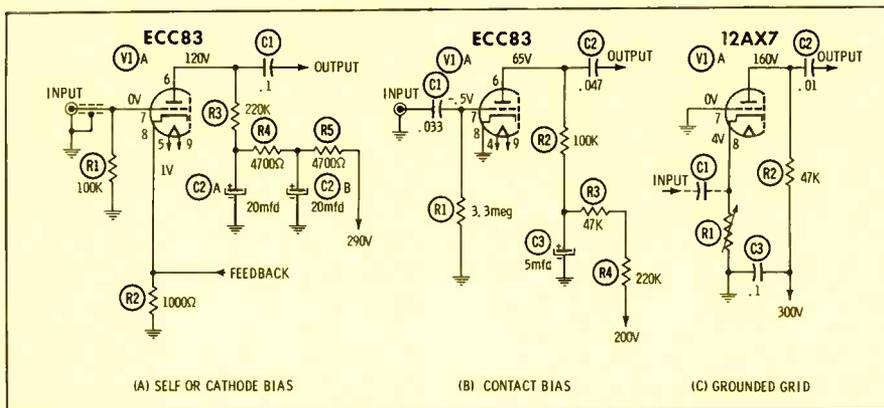


Fig. 4. Low-level tube circuits with different biasing and input arrangements.

limited to the surrounding circuitry.

Bias problems are the major cause of nonlinearity in transistor circuits. Leaky coupling capacitors will upset bias conditions and produce distortion. Good bantam electrolytics (which are commonly used for coupling) should have from 2 to 6 ua leakage—no more. Bias resistors should also be checked to insure that they have not changed value.

Motorboating in transistor circuits is a frequent trouble, especially in low-quality circuits. Defective electrolytics and weak batteries, where used, are the most common causes of motorboating. Bridging filter capacitors is a rapid way of finding the trouble; make sure the capacitor used for bridging is large enough. Since negative feedback is commonly used in transistor circuits, components associated with the feedback path can, if they change value, cause oscillation.

Low gain in transistor circuits is usually caused by defective coupling networks. Shorted interstage transformers, open coupling capacitors, and open collector load resistors can all cause low gain or complete loss of output. Shorted or open transistors are not as common, but these defects do occur. For example, in Fig. 5A, with the emitter open, the junction of the emitter and R3

would drop to 0 volts, and collector voltage would rise to the supply voltage (−12 volts). An open base, collector, or emitter will each produce almost the same symptoms, although there will be a slight emitter-base current with an open collector. A collector-to-emitter short will cause excessive emitter current and low collector voltage; collector and emitter voltages will be equal, but the base voltage will be normal. All three voltages (collector, base, and emitter) will be almost equal with a collector-to-base short; again, emitter current will be high. Base-to-emitter shorts are harder to detect, since the normal difference between base and emitter voltage is only .1 or .2 volt; usually, the transistor will be cut off and collector voltage will equal supply voltage. A base-to-emitter short can be found by connecting a VOM between the base and emitter and checking for the absence of bias voltage with the low-meter scale.

To determine rapidly if a transistor has an emitter-to-collector short, carefully short the base to the emitter. If the transistor is good, removing forward bias will cut it off, and collector voltage should equal source voltage.

A potentiometer between the power supply and ground can be

used to forward bias the base of a transistor. Carefully set the wiper arm for .1 to .2 volt of forward bias with respect to the emitter; connect the wiper arm to the base. As forward bias is slowly increased by the potentiometer, collector voltage should decrease; if not, the transistor is open.

### Medium-Level Circuits

The primary use for the cathode follower in Fig. 6A is as an impedance-matching circuit. Cathode followers are often used to provide a low-impedance output for cables to other equipment; occasionally they are also used as drivers for class AB output stages.

The cathode follows the grid signal. Since the signal developed across the cathode resistor is degenerative, it can never exceed the grid signal. Voltage gain in a cathode follower can never exceed one; however, owing to the high input and low output impedance, the cathode follower can produce power gain.

V1A's (Fig. 6A) grid signal is coupled in via C1 and developed across R1 and R3. DC through V1 produces a voltage drop across R2 for negative grid bias. The output signal is in phase with the input; it is coupled from the cathode of V1 by C2 to the load resistor, R4, and output jack, V1.

Fig. 6B shows a split-load paraphase amplifier. Note the similarity to the cathode follower (Fig. 6A); however, another output is taken from the plate. This circuit has a voltage gain of less than one for both outputs. Coupling capacitor C1 passes input signal to the grid of V1; bias is developed by R2. C3 couples the cathode signal appearing across R2 and R3 to the output stage. The plate signal developed by load resistor R4 is coupled to the output stage by C2. Outputs from C2 and C3 are of equal amplitude and 180° out of phase to provide drive for a class A push-pull output stage.

A cathode-coupled paraphase amplifier is shown in Fig. 6C; note that the bottom section is the grounded-grid amplifier previously discussed. DC coupling from the previous stage is often used in this circuit. V1A's grid (and cathode, due to R2) follow the input signal. The grid of V1B is held at AC ground by C1; but V1B's cathode follows the sig-

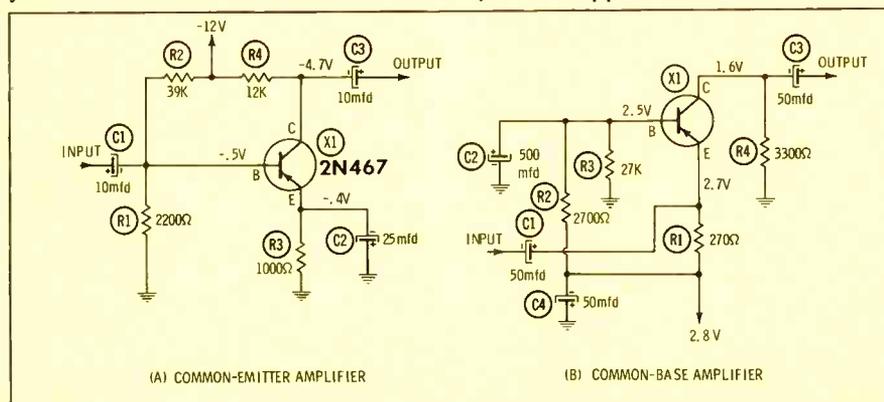


Fig. 5. Signal is coupled to emitter or base of low-level transistor circuits.

nal on R2, which in turn follows the signal of V1A's grid. The plate signal of V1A is 180° out of phase with the input signal, and the plate signal of V1B is in phase with the input signal. By proper selection of components, two signals of equal amplitude and 180° out of phase are coupled to the output stage.

Fig. 6D shows a floating paraphase amplifier. This circuit is composed of two cascaded common-cathode amplifiers with an output taken from each stage. Since phase inversion occurs in each stage, the output at the second stage is 180° out of phase with the output of the first stage. The input signal is coupled by C1 to V1A's grid; the inverted and amplified output is fed by C2 to one side of the output stage. Simultaneously, R2, R7, and C3 couple V1A's output to the grid of V1B. Plate signal from V1B is fed through two paths: via C4 to the output stage, and via R6, R7, and C3 back to the grid. Negative feedback is used to counteract the effects of aging tubes and slight changes in component values.

The transistor equivalent of the cathode follower, the emitter follower, is shown in Fig. 7A. Although this circuit has the lowest power gain of all three transistor amplifier configurations (common-emitter, common-base, and emitter-follower), it is quite popular as a coupling circuit. An emitter follower's high input impedance matches the common emitter's output impedance; while its low output impedance matches the common emitter's input impedance.

Also, because it produces current gain, the emitter follower is often used to drive a single-ended class A output stage. Forward bias for X1 is provided through R4, R1, and R2. Current flow through the transistor is controlled by the base signal, which has been coupled from the preceding stage by C1. The output signal is developed across R3 and direct coupled to the following stage.

Fig. 7B shows the transistor version of the split-load paraphase amplifier. This circuit, like its vacuum-tube counterpart, is used to drive a class A push-pull output stage. The push-pull output here drives a single-ended load. To help explain circuit action, the output stage has been included in the diagram. Input signal

is coupled by C1 to the base of X1; R1 and R2 provide forward bias. C3 couples the emitter signal, which follows the input signal, to the base of X3. Collector signal from X1, which is 180° out of phase with the input signal, is coupled by C2 to the base of X2. Since X2 is used in an emitter-follower configuration, the signal voltage appearing at the collector of X3 causes degeneration in X2. Feedback through C4 to the junction of R4 and R5 increases the signal applied to the base of X2 and decreases the signal applied to the base of X3. The circuit constants are chosen so that a balanced output signal results.

The third medium-level transistor circuit, in Fig. 7C, uses a class-A driver and a transformer to provide two outputs for push-pull operation. Because of its simplicity and high efficiency, this is the most common driver circuit. Operation is basically identical to that in Fig. 5A. Conduction of X1 controls current through the T1 primary; signal variations are coupled to the secondary windings. R4 provides a means of controlling the amount of high-frequency signal shunted to ground by C3; thus, it provides tone control.

## Servicing Medium-Level Circuits

Troubleshooting medium-level circuits involves the same basic principles used for low-level circuits, but, since these circuits have different functions, new techniques must be added.

Due to the great amount of degeneration within the cathode follower, malfunctions are not common. Aging tubes and small component value changes will have little effect on this circuit. Only major tube defects (open elements, internal shorts, and complete loss of emission) or component failures (open resistors or shorted capacitors) create trouble in this circuit.

Phase inverters should be subjected to both sine- and square-wave tests to insure that both outputs are of equal amplitude and have equal phase shift. Vacuum-tube aging is the usual cause of unbalance; changes in capacitors and resistors cause unequal phase shift. The cathodes of the phase inverter in Fig. 6C operate above ground, which makes this circuit susceptible to heater-cathode leakage. The circuit in Fig. 6D tends to become unbalanced as the tube ages.

Critical forward bias for X1 in

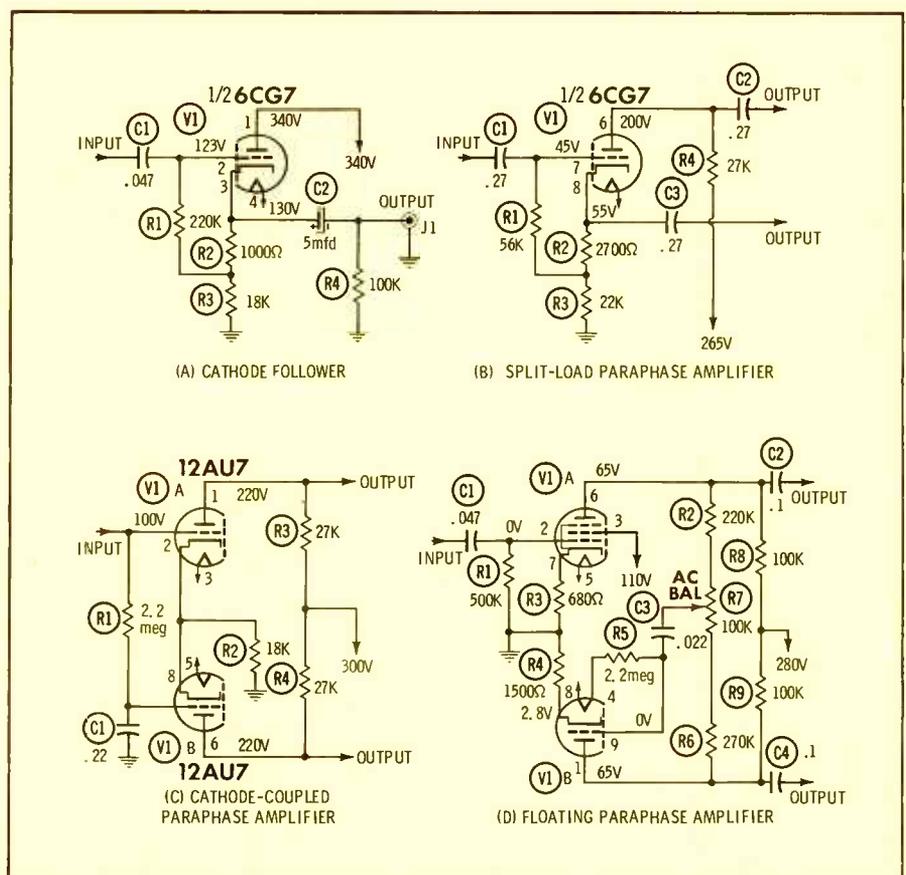


Fig. 6. Medium-level vacuum-tube circuits prepare signal for the output stage.

Fig. 7A makes the operation of the emitter follower more touchy than that of the cathode follower. Unbalanced output from T1 in the driver circuit of Fig. 7C can be caused by shorted turns in the secondary. Troubleshooting procedures for the emitter follower and the driver circuit are identical to those for low-level circuits.

Because of the circuit arrangement, scoping for unbalance in the paraphase amplifier of Fig. 7B can be difficult; here if unbalance is noted, individual component tests will be needed to find the trouble.

### High-Level Circuits

The most common output circuit used in AC-DC radios, low-priced phonographs, and television sets is shown in Fig. 8A. Use of a beam-power pentode gives the circuit relatively high efficiency, high power output, and high power sensitivity (which minimizes the number of preceding stages). With only 125 volts on the plate, this circuit can provide more than 2 watts output. Signal to the grid of V1 is coupled by C1; R1 is the grid resistor, and R2 provides cathode bias. The cathode is kept at AC ground by C2, and C3 suppresses transients produced by T1. V1 controls current flow through T1, which couples plate current variations to the speaker.

In Fig. 8B, the output stage is essentially the same as in Fig. 8A, but the cathode of V1 is used as the 135-volt supply point. R1, R2, and

R3 bias the grid, since the cathode is 135 volts above ground; C3 holds the cathode at AC ground. The output tube and the tubes supplied with 135 volts form a voltage divider.

Where higher power and greater fidelity is required, push-pull output circuits are used. Even harmonics and hum are cancelled in the push-pull arrangement, and the operating cycle is divided between both tubes. Hence, the push-pull circuit shown in Fig. 8C will operate in class A or class AB to provide high power with far greater fidelity than can be realized with single-ended output circuits.

Because the two sections are identical in operation, only the top section of the push-pull stage will be described. Input signal is coupled by C1 and developed across R1 and R4 to ground. From the bias supply -14 volts is applied to the DC BALANCE control; the bias for V1 is determined by the position of R2's wiper-arm. These circuits often use negative feedback, and phase shift at high frequencies can cause unstable operation; for this reason, parasitic suppressor R6 is inserted in series with the control grid of V1. Current flow through the T1 primary is controlled by V1 and V2. The secondary of T1 transforms the low impedance of the loudspeaker to the load impedance required by the tubes.

While vacuum-tube circuits have evolved into more-or-less standardized designs, it seems that today the flexibility of the transistor is being used to create as many design

variations as possible. Compare, for example, the two single-ended output circuits in Fig. 9.

In Fig. 9A, the input signal coupled to the secondary of T1 is connected to X1's base. R1, R2, R3, and R4 control forward bias to X1. As surrounding temperature increases, negative-temperature-coefficient resistor R4 decreases in resistance, and forward bias decreases. C1 and C2 reduce high-frequency response. The inverted signal at X1 collector is coupled by C1 back to the base, providing negative feedback, and C2 shunts high-frequency transients to ground. Both impedance matching for the 3-ohm speaker, and output transistor protection from shorts are provided by using output transformer T2.

Direct coupling is used in Fig. 9B for maximum simplicity and economy. Components associated with the emitter-follower driving X1 are selected to set proper bias at the base of X1. Part of the output from X1 collector is fed back to the preceding stages as DC stabilization and negative feedback—this arrangement prevents thermal runaway and reduces distortion. Inductor L1 aids impedance matching to the 35-ohm speaker.

OTL (output - transformerless) transistor circuits are one of the most important innovations in audio circuitry. Weight and space requirements for high-power output circuits are reduced, and elimination of the output transformer improves speaker damping.

To obtain maximum power in the

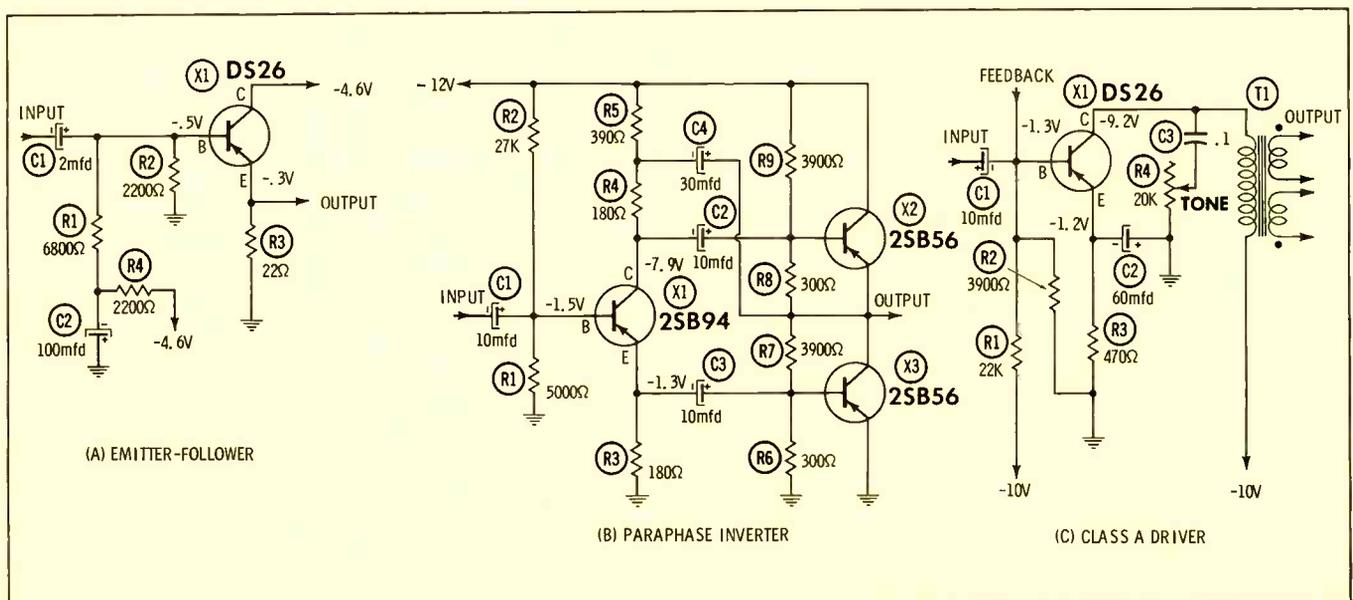


Fig. 7. Transistors in medium-level circuits use direct, RC, or transformer coupling to drive the power-output stage.

OTL circuit of Fig. 10A, the transistors are stacked in series. For one half of the input cycle, the top section (transistors X1 and X2) controls current flow from the -32 volt supply through the speaker to ground; for the alternate half-cycle, the lower section (X3 and X4) controls current flow from the +32 volt supply through the speaker to ground.

Since circuit action in the top and bottom sections is identical, only the top section will be explained. The signal from the driver is coupled by T1 and applied through R1 and R5 between the emitter and base of X1. Series resistors from -32 volts to ground provide forward bias for X1 at the junction of R1 and R2 and forward bias for X2 at the junction of R3 and R4. R5 is a stabilization resistor to prevent thermal runaway. Although the load (speaker) is in series with X1's emitter circuit, it is not tied between the emitter and base. Actually the load for X1 is grounded-base amplifier X2 (X2's base is tied to AC ground by C1). As the -32 volt power supply is considered to have no AC impedance, the speaker is effectively in series with the collector of X2. X1 and X2 form a compound circuit in which a common-emitter amplifier is directly coupled to a grounded-base amplifier with the speaker as a load.

There is no vacuum-tube equivalent for the circuit in Fig. 10B. The complementary-symmetry amplifier uses the opposing conduction char-

acteristics of NPN and PNP transistors to produce a single-ended push-pull amplifier that requires no phase inverter. Forward bias and input signal are directly coupled to the base of NPN transistor X2; the same input signal is coupled through R1 to the base of PNP transistor X1. Power-supply voltage is connected by R4 and R2 to the base of X1 for forward bias. With no input signal, both transistors are conducting slightly, and C3 charges to the voltage at the junction of R5 and R6. As the input signal goes positive, the base of X1—a PNP transistor—is reverse biased, and electron flow from the -9 volt supply ceases. Simultaneously the base of X2—a NPN transistor—is being forward biased, and electron flow through X2 increases as C3 discharges through R6, X2, and the speaker. When the input signal goes negative, X2 stops conducting. Electron flow through X1 (which is now forward-biased) charges C3 and returns through the speaker to the supply. To reduce crossover distortion and DC imbalance, negative feedback is taken from the junction of R5 and R6 and fed through R3 to the preceding stage.

In Fig. 10C the circuit is similar to vacuum-tube push-pull output circuits; however, a center-tapped speaker voice-coil replaces the output transformer. T1 couples the signal from the driver to the bases of X2 and X3. Voltage developed across the forward-biased PN junction of X1, a diode-connected transistor, is used to forward bias X2

and X3. If surrounding temperature increases, the voltage across X1 will decrease, and forward bias to X2 and X3 will drop. R2 provides more stabilization to prevent thermal runaway. Distortion is reduced by negative feedback from the collectors via C2, R3, C3, and R4. Transients developed across the speaker are suppressed by C1.

### Servicing High-Level Circuits

Single-ended output stages are quite susceptible to distortion, hum, and parasitic oscillation. Distortion is usually caused by a gassy tube or a leaky coupling capacitor. In Fig. 8B, the cathode is positive with respect to the filament, and the possibility of heater-cathode leakage and shorts is increased. Often, beam-power output circuits are operated so that the screen grid is more positive than the plate during part of the operating cycle; this sometimes causes Barkhausen oscillations. Bypassing the screen grid as is done in Fig. 8B will usually prevent distortion and RF interference created by these oscillations.

Push-pull output stages (Fig. 8C) create distortion when they become unbalanced. Static balance of push-pull stages is accomplished by inserting a milliammeter in each cathode lead and adjusting bias until the currents are equal. At times, it may be necessary to select tubes to balance cathode currents. To check rapidly for oscillation around the feedback loop, disconnect the feedback path; cathode current will decrease if the circuit is oscillating.

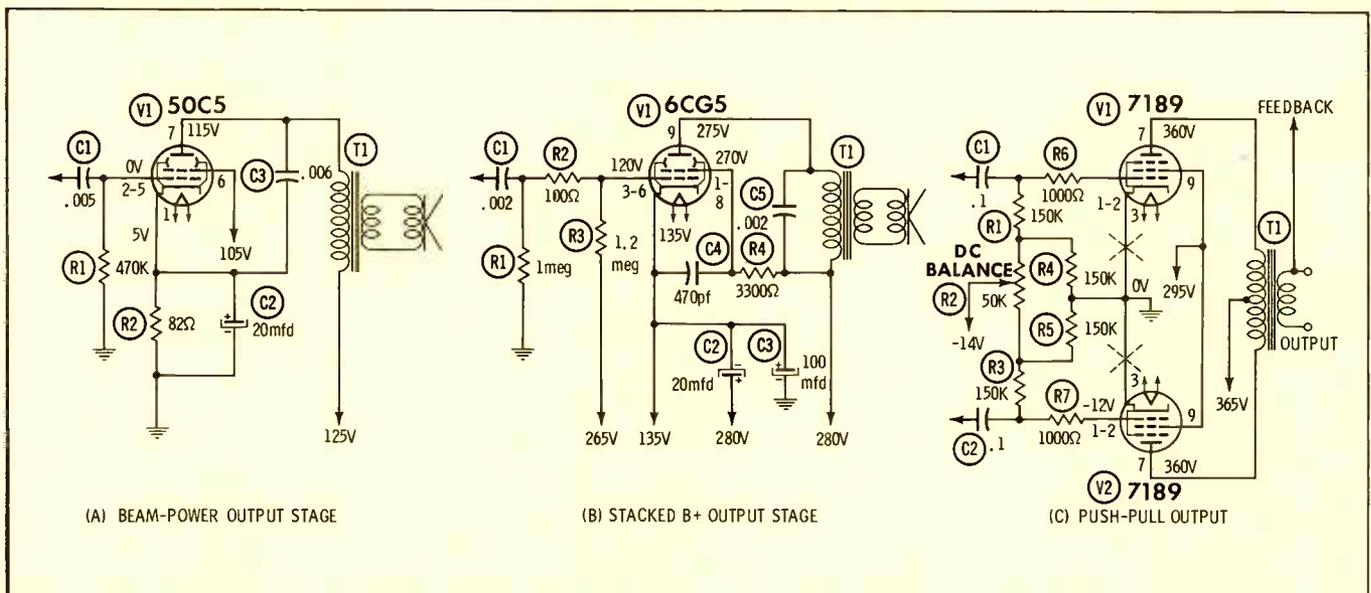


Fig. 8. Tube high-level output stages provide sufficient power to drive loudspeaker—output transformer matches impedances.

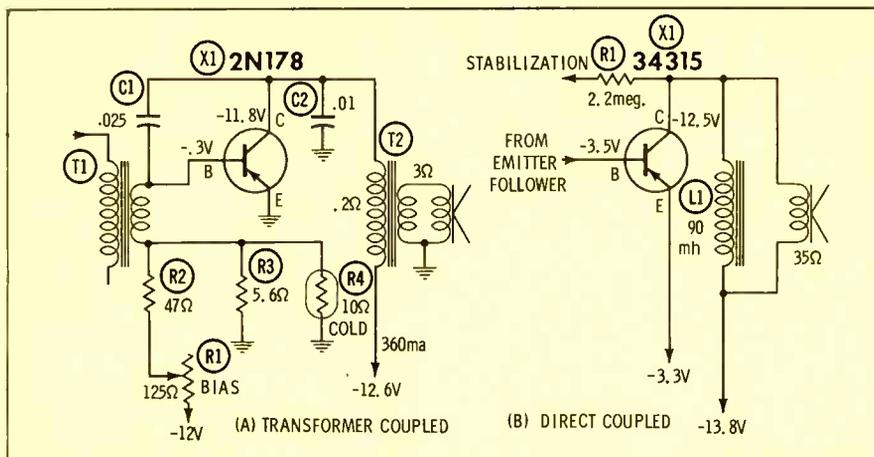


Fig. 9. Single transistor operates in class A for power to drive loudspeaker.

These push-pull stages will operate—with higher distortion and lower output—with only one side of the circuit functioning. Don't be surprised if the circuit works with one tube dead.

Transistor single-ended output circuits are critical as to bias adjustments for linear operation. Here, voltages are low, and much more information can be gained by using current checks to determine if the amount of current flow is normal. Excessive emitter current indicates that forward bias is too high or the transistor is shorted.

Insufficient emitter current indicates that forward bias is too low or the transistor is open. Components other than transistors are the most common cause of malfunctions;

however, the failure of an associated component often damages the transistor. Always be certain that the primary cause of transistor failure has been found. When servicing direct-coupled output circuits such as the one in Fig. 9B, make sure that the cause of trouble is not in the preceding stages.

Since, for maximum efficiency, transistor push-pull output stages are operated class B, proper biasing to prevent crossover distortion is important. This crossover distortion, as is shown in Fig. 1C, occurs if one half of a push-pull amplifier begins to cut off before the other half starts to conduct. Because the percentage of distortion is higher, crossover distortion is much more prominent at low output levels. If R4 in

Fig. 9A were to increase in value, or the voltage across X1 in Fig. 10C were to decrease, forward bias would decrease, and crossover distortion would occur. Because the transistors of the complementary-symmetry amplifier (Fig. 10B) are different types, it is difficult to match them. Care must be taken to insure a replacement complements the other transistor's characteristics. Oscillation at a low frequency (which can be mistaken from motorboating) will occur in the circuit of Fig. 10C if one half of the speaker voice coil opens. The feedback path consists of C1, the collector-base negative feedback network of the open side, and the T1 secondary. The same symptom can occur at a higher frequency if X2 or X3 opens. Here, as in single-ended transistor outputs, static current checks may, at times, be more useful than voltage checks; both should be used to get all possible clues as to the cause of trouble.

### Conclusion

Although a few different techniques are necessary for servicing the latest transistorized audio circuits, the same basic procedures used for all electronic troubleshooting still apply. A basic understanding of audio circuit theory and test equipment application will enable a service technician to troubleshoot the most difficult audio troubles. ▲


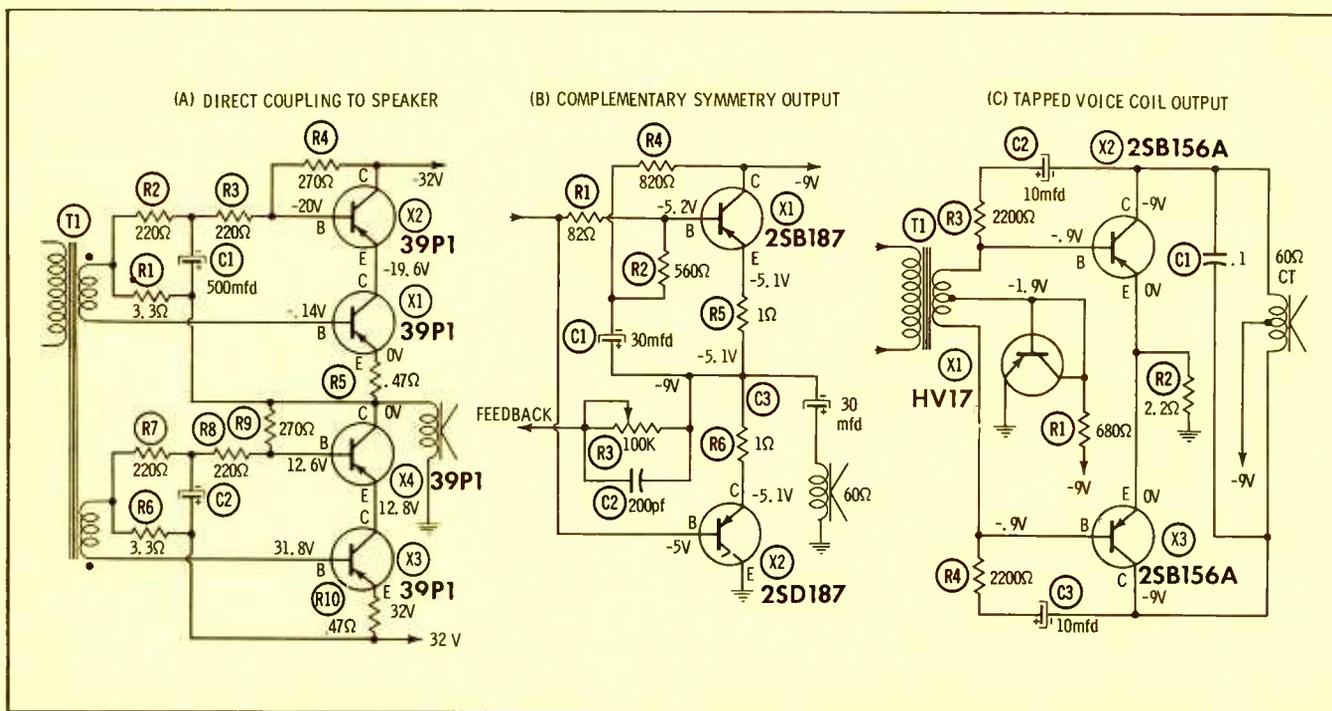


Fig. 10. Transistor OTL stages couple power to the speaker directly or use a capacitor; no output transformer is needed.

# TUNER REPAIRS

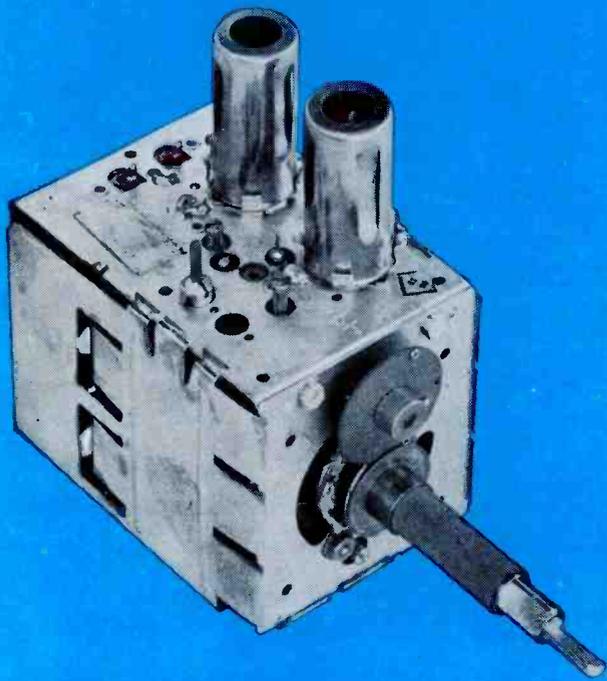

# \$9.50

**FOR COMPLETE OVERHAUL**

**Includes ALL parts (except tubes)  
ALL labor on ALL makes**

**24-HOUR SERVICE with  
FULL YEAR WARRANTY**

Sarkes Tarzian, Inc., largest manufacturer of TV and FM tuners, maintains two completely-equipped Service Centers to serve YOU. Both centers are staffed by well-trained technicians in this specialized field and are assisted by engineering personnel to assure you of FAST, DEPENDABLE service.

Ⓢ Tarzian-made tuners—identified by this stamping—received one day will be repaired and shipped out the next. A little more time may be required on other makes. Every channel is checked and re-aligned per manufacturer's specifications, not just the channels which might exist in any given area.

You get a 12-month guarantee against defective workmanship and parts failure due to normal usage. Cost to you is only \$9.50 and \$15 for UV combinations, including all labor and parts except tubes. No additional costs. No hidden charges. All tuners repaired on approved, open accounts. You pay shipping. Replacements on tuners beyond practical repair are available at low cost.

When inquiring about service on other than Tarzian-made tuners, always send TV make, chassis and Model number. Check with your local distributor for Sarkes Tarzian replacement tuners, parts, or repair service. Or, use the address nearest you for fast factory repair service.



**SARKES TARZIAN, INC.**

**TUNER SERVICE DIVISION**

*See your distributor, or use the address nearest you*

537 South Walnut St.,  
Bloomington, Indiana  
Tel: 332-6055

10654 Magnolia Blvd.,  
North Hollywood, Calif.  
Tel: 769-2720

Manufacturers of Tuners . . . Semiconductors . . . Air Trimmers . . . FM Radios . . . AM-FM Radios . . . Audio Tape . . . Broadcast Equipment

Circle 2 on literature card

August, 1965/PF REPORTER 9



A HOWARD W. SAMS PUBLICATION

# PF Reporter™

PHOTOFACT

the magazine of electronic servicing  
VOLUME 15, No. 8 AUGUST, 1965

## CONTENTS

<b>Audio Servicing From A to Z</b>	David I. King	1
How to understand and troubleshoot audio circuits from preamp to output.		
<b>Letters to the Editor</b>		13
<b>The Electronic Scanner</b>		16
<b>Make Money in Rentals, Sales, Leases</b>	Thomas R. Haskett	24
Some tips to help earn extra dollars by supplying audio equipment services.		
<b>Stereo With Transistors</b>	Leo G. Sands	26
Here's what you need to know about solid-state circuits used to add dimension to sound.		
<b>Keep It Clean!</b>	Steve P. Dow	29
Tape recorders and phonographs work best only when they're free from dirt.		
<b>AGC Filter and Distribution Faults</b>	Allan F. Kinckiner	31
Shop Talk—Case histories show how to conquer these problems.		
<b>Testing Three-Terminal Networks</b>	Robert G. Middleton	33
Advanced Servicing Techniques—Applying knowledge of resistance and capacitance to "black boxes" containing both.		
<b>Acoustics Can Be Measured</b>	Don Davis	36
You can determine quantitatively the audio "response" of a room or auditorium.		
<b>Notes on Test Equipment</b>	Major Henricks	39
Lab report on B & K Model 801 Capacitor Analyst and EICO Model 435 Oscilloscope.		
<b>ASCAP and BMI</b>	Paul Norman	50
The inside story on one of the important legal aspects of background-music operation.		
<b>PFR Bench Report</b>		57
<b>Symfact: Transistor Audio Output (Push-Pull With Driver)</b>		59
See what happens to voltages and waveforms when troubles occur.		
<b>The Troubleshooter</b>		64
<b>Color Countermeasures</b>		66
<b>Product Report</b>		68
<b>Free Catalog and Literature Service</b>		74
<b>Monthly Index</b>	on free literature card	

### **publisher**

Howard W. Sams

### **editor**

Forest H. Belt

### **managing editor**

James M. Moore

### **ass't to the editor**

Norman D. Tanner

### **associate editors**

Major Henricks

David I. King

Allen B. Smith

### **consulting editors**

William E. Burke

Joe A. Groves

C. P. Oliphant

### **research librarian**

M. D. Bishop

### **production manager**

Esther M. Rainey

Robert W. Pool, Ass't.

### **circulation manager**

Pat Tidd

Katherine Krise, Ass't.

Cora La Van Willard, Ass't.

### **art directors**

Louis J. Bas, Jr.

Robert W. Reed

### **advertising & editorial assistants**

Hazel Boyer

Rebecca Clingerman

### **photography**

Paut Cornelius, Jr.

### **advertising sales offices**

Hugh Wallace, advertising sales manager

#### **midwestern**

Paul N. Houston

PF REPORTER, 4300 West 62nd Street,

Indianapolis, Ind., AXminster 1-3100

#### **eastern**

Gregory C. Wisefield

Howard W. Sams & Co., Inc. 3 West 57th Street,

New York, N. Y., MUrray Hill 8-6350

#### **southwestern**

C. H. (Jake) Stackwell

C. H. Stackwell Co., 4916 West 64th St,

Mission, Kansas, RAndolph 2-4417

#### **western**

G R. Holtz

The Maurice A. Kimball Co., Inc.

Los Angeles area: 2008 West Carson Street,

Suites 203-204, Torrance, Calif. 90501,

320-2204; and 580 Market Street,

Room 400, San Francisco 4, Calif. EXbrook 2-3365

Address all correspondence to

PF REPORTER, 4300 W. 62nd Street

Indianapolis, Indiana 46206



Copyright© 1965 by Howard W. Sams & Co., Inc.  
PF REPORTER is a trademark of Howard W. Sams & Co., Inc. No part of PF REPORTER may be reproduced without written permission. No patent liability is assumed with respect to use of information herein. Acceptance of advertising does not in any manner signify the products, policies and services so advertised have been approved, endorsed or recommended by this magazine.

Subscription Prices: 1 year—\$5.00, 2 years—\$8.00.

3 years—\$10.00, in the U. S. A., its possessions and Canada.

All other foreign countries: 1 year—\$6.00, 2 years—

\$10.00, 3 years—\$13.00. Single copy 50¢; back copies 65¢.


Indexed in LECTRODEX.

Printed by the Waldemar Press Div.

of Howard W. Sams & Co., Inc.
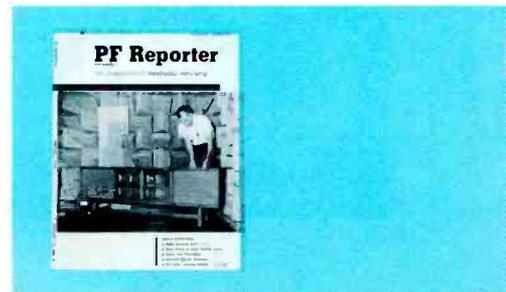
## ABOUT THE COVER

The interior of the anechoic room at RCA's Indianapolis plant sets the theme of this month's issue. Speaker tests, such as the one simulated in the cover scene, are but one aspect of the ever-growing field of audio technology.





# 1,863 reasons why Sprague Twist-Lok® Capacitors help you to protect your reputation


When you fool around with makeshift or "fits-all" capacitor replacements by substituting sizes and ratings, you leave yourself wide open for criticism of your work, you risk your reputation, and you stand to lose customers. With so much at stake, it just doesn't pay to use makeshifts when it's so easy to get exact replacement capacitors from your Sprague distributor.

With 1,863 different Sprague Twist-Lok Capacitors as standard catalog items, and more being added regularly, Sprague gives you the world's most complete selection of exact replacements.

We don't have to tell you that it's easier to service with exact replacements. And we don't have to tell you that it's better, too. When sets are designed, specific capacitance values are used for peak operation, so it takes exact replacements to restore original set performance.

And who better than Sprague knows which values and sizes are needed in the replacement market? Sprague, the world's largest component manufacturer, has the most complete specification file on original set requirements. That's why you're always right when you work with Sprague Twist-Lok exact replacements!

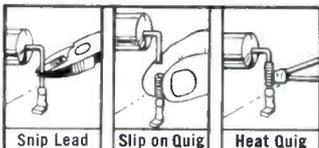GET YOUR COPY of Sprague's comprehensive Electrolytic Capacitor Replacement Manual K-107 from your Sprague Distributor.



## HAVE YOU TRIED QUIG® CONNECTORS?

Not just another wire spring connector! Copperweld wire inner core, a layer of flux, and an outer coating of solder . . . all you supply is heat! Now being packed with Sprague Atom® Capacitors at no extra cost to you! See your distributor!



WORLD'S LARGEST MANUFACTURER OF CAPACITORS

Circle 3 on literature card

Sprague Products Co., 105 Marshall St., North Adams, Mass. 01248

# ALL NEW FROM *HICKOK*

**100% G<sub>m</sub> TESTS...**  
*No Emission Tests,  
No Compromise!*

**OBSOLESCENCE PROTECTION**  
*Realistic, Practical  
No Compromise!*

**MULTI-SOCKET SPEED...**  
*No Compromise  
In Accuracy!*

**MORE PROFIT**  
*Because You'll Sell  
More Tubes...  
Sell Them  
Honestly!*

**NEW HIGH-SENSITIVITY  
LEAKAGE AND  
GAS TESTS!**

**MODEL 799**  
*Mustang*  
**\$199<sup>95</sup>**

From the laboratories of the world's leading tube tester manufacturer comes the model 799 "Mustang" — a completely new tube tester.

Multi-socket tube testers used to have two serious drawbacks: circuit limitations made them obsolete overnight and, at best, no more than 10% of their tests were actually mutual conductance. But the Hickok "Mustang" doesn't compromise; it delivers *honest* mutual conductance tests. And a unique circuit approach, together with an easily replaceable accessory socket panel, makes it "circuit ready" for

any possible new tube types.

A solid-state power supply gives increased accuracy and dependability. An all-transistorized gas and leakage test circuit sets a new standard of reliability for spotting "tricky" tube defects that can "chew up" your profit. You can actually read interelement leakage to 50 megohms; gas/grid leakage effects to 0.1  $\mu$ a!

We call it the "Mustang" because it uses fresh, new engineering ideas and because it gives you a real opportunity to break into new profits.

See it at your Hickok distributor or write for circular TT799.

Ask your distributor about the Hickok Credit Plan.

**THE HICKOK ELECTRICAL INSTRUMENT CO.**

10566 Dupont Avenue, Cleveland, Ohio 44108

Represented in Canada by Stark Electronics, Ajax, Ontario  
Internationally by Hughes International, Culver City, California

# *HICKOK*




Circle 4 on literature card



OHMITE  
1000 OHM  
1/2 WATT 10%  
RC20GF102K

Little Devil® Composition Resistors

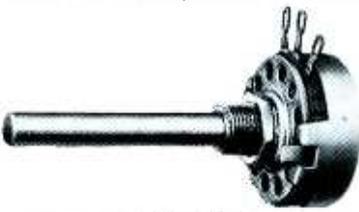

Type AB 2-Watt Molded Pots

## five ways to stop customer "static"



Gold-Bonded Germanium Diodes



OHMITE  
BROWN

Brown Devil® Wire-Wound Resistors



OHMITE  
995-5A

Series 99 Wire-Wound Resistors

Customer "static" is hard on the ears... hard on profit. But you're always safe with Ohmite quality replacements in your repair jobs. Order Little Devils in handy cabinet assortments or on Tally-Tape; all popular sizes and values. Select AB Pots from 50 ohms to 5 megohms in several shaft lengths. Choose from ninety 1N types of diodes. Get Brown Devils from 3 to 20 watts in 0.5-ohm to 100K-ohm values. Order Series 99 resistors in 1½, 2¼, 3¼, 5, 11 watt sizes from 1 to 51,000 ohms. Ask your distributor for the latest edition of Ohmite's Stock Catalog 30.

Be right with



# OHMITE

RHEOSTATS • RESISTORS • VARIABLE TRANSFORMERS • TAP SWITCHES  
TANTALUM CAPACITORS • RELAYS  
R.F. CHOKES • SEMICONDUCTOR DIODES


Circle 5 on literature card

## Letters to the Editor

Dear Editor:

In the April 1965 issue, I believe the tube-voltage schematics in SYMFACT Symptoms 3 and 4 should be exchanged. Also, the open connection you say is at terminal 2 of L2 should actually be at terminal 3 or 4. Correct me if I'm wrong. I enjoy SYMFACT, and it's very helpful. Sometimes, however, these errors (though not many) make me dig in to see what's wrong.

Johnson City, Tenn.  
ROSS SHIPLEY

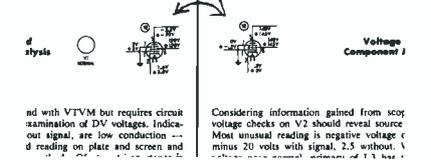

I wish we could say we drop in those errors to keep you on your toes, Ross; unfortunately, they slip in despite our best efforts to keep them out. Your discoveries are correct, and the figure herewith shows one way to mark your SYMFACT sheet and call attention to the switch of schematics. The other error is easily marked; the heading should read "Open Connection, Pin 3 of L2."—Ed.

Dear Editor:

I am interested in writing articles for PF REPORTER. What kind of training does this require? Do you demand special qualifications of your authors? I have been servicing electronics equipment for almost ten years, and feel as if I could pass along quite a bit of information that would be useful to other technicians—especially beginners. Can I write about anything I want to? Or do your articles have to be on specific subjects?

WOOD B. REITER  
Somewhere, U.S.A.

This is typical of several letters we've received recently. Qualifications for a PF REPORTER author include a thorough knowledge of electronic principles, experience in applying these principles and in troubleshooting, and the ability to put your experiences on paper in accurate, readable English. Most of the articles in PF REPORTER are staff-written and edited. Those that are prepared outside our staff are usually done on assignment only, and we recommend that you send us an outline of any proposed article before you work up a manuscript. This might save you time and effort because we can frequently give concrete suggestions concerning how to proceed with a particular subject. A letter stating your background and experience will get you a copy of our mechanical-requirements sheet. A sample manuscript would also allow us to offer suggestions on your writing.—Ed. ▲



## PRODUCTS FOR MODERN LIVING

### NEW ATR Golden Line

#### FREQUENCY-STABLE INVERTER\*



THIS ATR 12T-RME-1 INVERTER with automatically controlled "Frequency - Stability" will deliver 110-volt A.C. 60 cycle power for all popular make 11" to 13" portable TV Sets.

12 T-RME-1 (12V D. C.)  
Rated: 140 watts max.  
Shipping Wght., 14 lbs.  
Dealer Net **\$2916**  
Price,

A.C. HOUSEHOLD ELECTRICITY Anywhere... in your own car, boat or plane!  
Operates Standard A.C.  
• Portable TV Sets  
• Record Players  
• Small Tape Recorders  
• Dictating Machines  
• Small Radios  
• Electric Shavers  
• Heating Pads, etc.

\*Additional Models Available

### ATR UNIVERSAL INVERTERS

A. C. Household Electricity Anywhere... in your own car, boat, or plane!

- Tape Recorders • TV Sets
- Dictating Machines • Radios
- Public Address Systems
- Electric Shavers • Record Players • Food Mixers • and Emergency Lighting.

NET

12U-RHG (12 V.) 150 to 175 W. Shp. Wt. 27 lbs. **\$73.00**  
28U-RHG (28 V.) 150 to 175 W. Shp. Wt. 27 lbs. **\$87.50**

### ATR BATTERY CHARGERS

NO INSTALLATION... PLUG INTO CIGARETTE LIGHTER RECEPTACLE!

Keeps car battery fully charged in your own garage! Needed more now than ever before—makes motor starting easy! Operates directly from standard 110 volts A.C. current.

612CA4 (4 amp.) 6/12 V. Shp. Wt. 6 lbs. NET \$19.46  
612CA6 (6 amp.) 6/12 V. Shp. Wt. 8 lbs. NET \$22.46  
612CA10 (10 amp.) 6/12 V. Shp. Wt. 10 lbs. NET \$27.71

### ATR ALL-TRANSISTOR UNIVERSAL MODEL 707

HAND WIRED—NO PRINTED CIRCUITRY



Karadio  
IN DASH... UNDER DASH...

Complete with variable tone control... R. F. stage... Built-in speaker... and External speaker jack.

ATR MODEL 707N ..... **\$2597** Dealer Net

### ATR "A" Battery ELIMINATOR



For Demonstrating and Testing Auto Radios—TRANSISTOR or VIBRATOR OPERATED!

Designed for testing D.C. Electrical Apparatus on Regular A.C. Lines.

MAY ALSO BE USED AS A BATTERY CHARGER  
MODEL 610C-ELIF... 6 volts at 10 amps. or 12 volts at 6 amps. Shipping weight 22 lbs.

USER NET PRICE ..... **\$55.00**

### ATR AUTO RADIO and COMMUNICATION LONGER-LIFE VIBRATORS

"The Best by Test!"



SEE YOUR ELECTRONIC PARTS DISTRIBUTOR OR WRITE FACTORY FOR LITERATURE & DEALER PRICE

## ATR ELECTRONICS, INC.


Quality Products Since 1931  
St. Paul, Minnesota 55101—U.S.A.
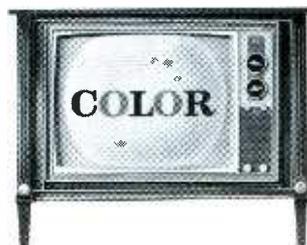
# RCA Solid Copper Circuits



replace old-fashioned  
"hand wiring"... RCA Solid  
Copper Circuits are the  
circuits of the space age

RCA Solid Copper Circuits are made by methods as modern as tomorrow. They give greater dependability . . . better TV performance. It's typical of the advanced design you'll find throughout every RCA Victor home instrument. It all adds up to sets that are easier to service so that owners are more satisfied with results.



The Most Trusted Name  
in Electronics

Trmk(s)®

More TV servicemen own RCA Victor Color TV than all other leading makes combined



# MIRACLE WORKER

*in professional TV service shops*

**PINPOINTS ANY TV TROUBLE FAST! UPS YOUR PROFIT!**



**DELUXE B&K**

## MODEL 1076 B&W and COLOR TELEVISION ANALYST

*with Crystal-Controlled Keyed Rainbow Color Display  
and Highly-Stable Horizontal Oscillator Sync*

### **FLYING SPOT SCANNER**

*transmits B&K patterns or your own  
pictures onto TV screen*

It's like having your own TV station! You can inject your own TV signals at any time, at any point—and quickly solve tough dogs, intermittents, any TV trouble, as you watch the generated test pattern on the raster. Checks any and all circuits in any stage throughout the video, audio, r.f., i.f., sync and sweep sections of the TV set. No external scope or waveform interpretation is needed. And if you wish, you can transmit your own slide-pictures.


### **Makes Color TV Servicing Easy, Too.**

Generates white dot, crosshatch and color bar patterns for convergence. Generates crystal-controlled keyed rainbow color display to check color sync circuits, check range of hue control, align color demodulators. Demonstrates correct color values.

Saves time and work for the "pro." Makes servicing easier and faster for the beginner technician.

Most valuable instrument in TV servicing.

Net, \$329.95

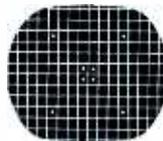

*Profit with a B&K Service Shop  
See your B&K Distributor  
or Write for Catalog AP21-R*

**B & K MANUFACTURING CO.**  
DIVISION OF **DYNASCAN CORPORATION**  
1801 W. BELLE PLAINE AVE. • CHICAGO, ILL. 60613  
Canada: Atlas Radio Corp., 50 Wingold, Toronto 19, Ont.  
Export: Empire Exporters, 123 Grand St., New York 13, U.S.A.

# COMPLETE TUNER OVERHAUL

ALL MAKES — ONE PRICE

995

ALL LABOR  
AND PARTS  
(EXCEPT TUBES  
& TRANSISTORS)\*




VHF



UHF



COLOR

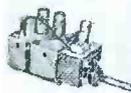

U-V



TRANSISTOR

## COLOR TUNERS

GUARANTEED COLOR  
ALIGNMENT — NO  
ADDITIONAL CHARGE

Simply send us the defective tuner complete; include tubes, shield cover and any damaged parts with model number and complaint. Your tuner will be expertly overhauled and returned promptly, performance restored, aligned to original standards and warranted for 90 days.

UV combination tuner must be single chassis type; dismantle tandem UHF and VHF tuners and send in the defective unit only.

Exact Replacements are available for tuners unfit for overhaul. As low as \$12.95 exchange. (Replacements are new or rebuilt.)

And remember—for over a decade Castle has been the leader in this specialized field . . . your assurance of the best in TV tuner overhauling.

Pioneers of TV



Tuner Overhauling

# CASTLE

TV TUNER SERVICE, INC.

MAIN PLANT: 5701 N. Western Ave., Chicago 45, Illinois

EAST: 41-90 Vernon Blvd., Long Island City 1, N.Y.

CANADA: 136 Main Street, Toronto 13, Ontario

\*Major Parts are additional in Canada

Circle 9 on literature card



## The Electronic Scanner

news of the servicing industry

### Winners of "500" Contest

Three PHOTOFACT 500 Mile Race Contest winners who received deluxe trips to the race in Indianapolis have been announced by Howard W. Sams & Co., Inc.

Winners were Harold Law (right) and Floyd Burch (left), both of Electronic Parts Company, of Denver, Colorado, and



Joe Taylor, (center) Tri-State Electronics, Greenville, Mississippi. These three top salesmen were named from 3000 entries in the national sales contest.

In a four-day trip to Indianapolis, the three winners and their wives participated in a series of race-week festivities that included the "500" festival parade, a VIP tour of the Speedway, and numerous parties and social events.

### Broadcasting and Communications

The 30th Annual Report of the Federal Communications Commission gives some idea of growth in the regulated branches of electronics.

Big news of course is Comsat (Communications Satellite Corporation) whose initial \$200-million stock issue was snapped up quickly at \$20 per share. Half was subscribed by communications carriers and half by the public. Their Early Bird satellite is in use, and by press time Comsat should have filed rate tariffs.

American Broadcasting Co. has already thrown a curve to Comsat and to AT & T; ABC proposes orbiting their own relay satellite for network programs, bypassing both Comsat's spaceborne relay station and AT & T's microwave and long-line facilities. FCC will decide whether or not to authorize this new idea.

Only one aired pay-TV test is in progress—in Hartford, Conn., and no applications are pending. WHCT, Channel 18, Hartford, has about 5000 subscribers and transmits about 30 hours of toll telecasts each week (plus regular free programs). Subscription service over cable, which isn't regulated by FCC, took a beating in California, but the upset has been overridden by a Federal Court Judge who ruled the new restriction unconstitutional. Unless an appeal is granted, pay TV may get a foothold there on the cable system installed expressly for the purpose.

There are 350 television channels now reserved for educational TV (ETV or ITV). At least 14 cities have two ETV channel allocations. About 80 ETV stations are now on the air, not counting translators. Airborne ETV (MPATI) is still underway in the Midwest, although their request for more channels (74, 78, 80, and 82) is still under consideration. MPATI presently uses channels 72 and 76.

Total commercial television stations authorized are 668, with only 582 of them in operation. Add 1913 translators to this (1415 in operation), and you find nearly 2000 operating and 584 (mostly translators) to come.

Every state has at least one commercial FM station. There are more than 1180 on the air, with 190 more authorized. About 400 of the stations carry subsidiary background music.



# Your ticket to a good job in electronics.

These men will tell you how to get it!



**Matt Stuczynski, Senior Transmitter Operator, Radio Station WBOE.**

"The Commercial FCC License is a 'must' for a career in broadcasting. I took Cleveland Institute's Home Study Electronics Course and, thanks to CIE's 'Auto-Programmed' teaching method, passed the First Class FCC License Exam on my first try! I now have a good job in studio operation, transmitting, proof of performance, equipment servicing."



**Chuck Hawkins, Chief Radio Technician, Division 12, Ohio Dept. of Highways.**

"My CIE Course enabled me to pass both the 2nd and 1st Class License Exams on my first attempt . . . even though I'd had no other electronics training. I'm now in charge of Division Communications and we service 119 mobile units and six base stations. It's an interesting, challenging and extremely rewarding job."



**Glenn Horning, Local Equipment Supervisor, Western Reserve Telephone Company.**

"I owe my 2nd Class FCC License to Cleveland Institute. Their FCC License Program really teaches you theory and fundamentals . . . is particularly strong on transistors, mobile radio, troubleshooting and math. Our Company has 10 other men enrolled with CIE and it's going to help every one of them just like it helped me."

How about you? If lack of an FCC License is holding you back, it's time you looked into Cleveland Institute of Electronics Home Study. All you have to do is send us the coupon . . . and in a few days, you'll have the complete story. And remember . . . Cleveland Institute backs their programs with this exclusive, money-back warranty: "A CIE License Course will quickly prepare you for a Commercial FCC License exam. If you complete the course but fail to pass the exam *on your first attempt*, CIE will refund all tuition."

**Get started now. Send coupon for free booklet "How To Get an FCC License." There's no obligation.**

## Cleveland Institute of Electronics

1776 E. 17th St., Dept. PF-24 • Cleveland, Ohio 44114



**CIE**  
Cleveland Institute of Electronics  
1776 E. 17th St., Dept. PF-24  
Cleveland, Ohio 44114

**HOW TO GET A COMMERCIAL FCC LICENSE**



Yes! I want to know how to get a Commercial FCC License. Please send me your FREE booklet . . . without obligation.

My Occupation is \_\_\_\_\_

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_ County \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

**A leader in Electronics Training . . . since 1934**

Circle 10 on literature card

# Delco Radio offers a new kind of volume control



This year you can get a Delco Radio Parts Kit for *each* 1966 General Motors car. You buy only what you need—no more. That controls the volume of parts you need to carry.

There's a separate kit for Chevrolets, Pontiacs, Oldsmobiles, Buicks,

and Cadillacs. Plus a Universal Kit with parts that are interchangeable on *all* GM cars.

All kits contain the fastest moving parts and information pinpointing the models they're meant for. There are no carryovers from previous years.

Now's the time to order your Delco Radio Parts Kits for the *Circle 11* on literature card

makes you service most. Just call your United Delco representative.



Delco Radio, Division of General Motors, Kokomo, Indiana


# The new Amphenol 860 Color Commander cuts alignment time in half!

Ever finish a convergence job to find the raster off center. Lose convergence when you re-centered? Can't happen with the Amphenol Color Commander, battery-powered, solid-state color generator. A special, single-crossbar pattern consists of one horizontal and one vertical line, crossing just where the center of the raster should be. No need to guess when centering the raster with this new pattern.

See dots before your eyes when you want only one to start static convergence? The 860 gives you that single dot, right at center screen. You'll be switching back to this important dot during dynamic adjustment to make sure you haven't gone off the track.

Even the old patterns offer something new. Line spacing in the cross-hatch pattern is rigidly maintained for the 4:3 aspect ratio. You can rely on it for linearity, height, and width adjustments. The pattern gives you finely etched line width at normal brightness levels. What good is perfect convergence at reduced brightness if you lose it when the set's readjusted for normal viewing? This special crosshatch also eliminates receiver fine-tuning error. Among the 860's nine (most generators have only 5 or 6) are: multiple-dot, single vertical line, single horizontal line, vertical lines only, and horizontal lines only.

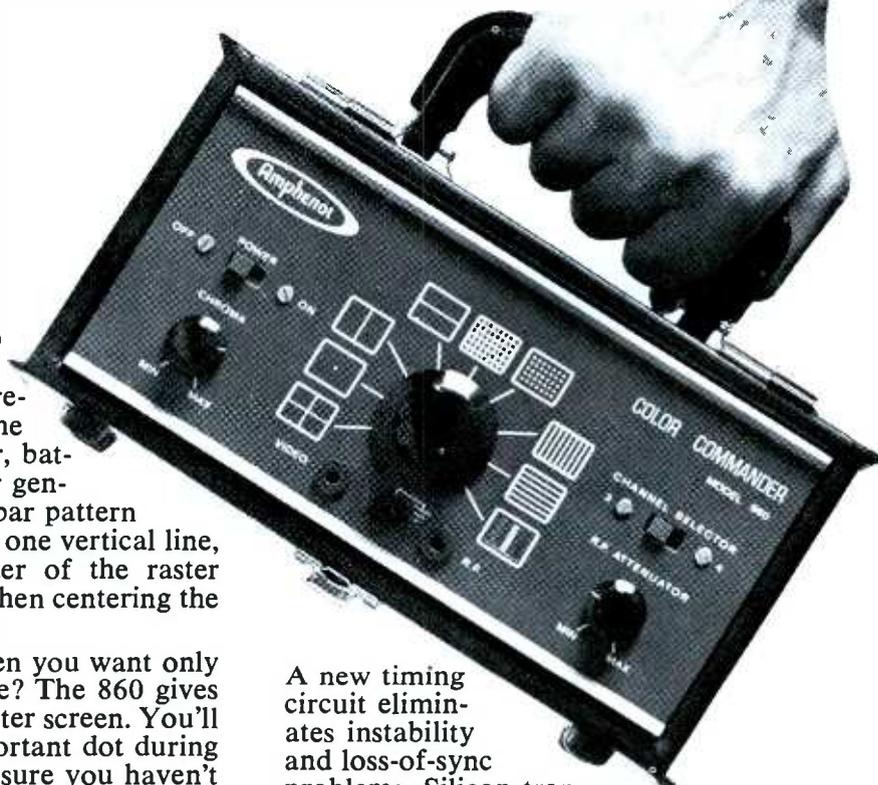Finally, the Color Commander's unique color bar pattern (just three bars: R-Y, B-Y and -R-Y) simplify color adjustments. You can get a rapid, overall check of color circuits. Then adjust color demodulator phase or pre-set the hue control and check its operating range. In each step, you know precisely how the color bars should look and how they should change during adjustment.



A new timing circuit eliminates instability and loss-of-sync problems. Silicon transistors maintain built-in precision and stability indefinitely. RF output is on channel 3 or 4, switch selected. An attenuator simulates weak-signal conditions. It has gun killer circuit. Uses 9 penlight cells. Weighs 3½ lbs. in compact leatherette carrying case. \$149.95. Optional AC power supply, \$19.95.

**AMPHENOL CRT COMMANDER, MODEL 855.** Solid-state. Checks all black-and-white or color CRT's with the same techniques used by tube manufacturers. Rejuvenates where others fail. Versatile 5-socket cable accommodates 7 different sockets. With CRT chart, \$89.95.


See the new Color Commander test instruments at your Amphenol distributor.

**Amphenol**  
DISTRIBUTOR DIVISION  
amphenol corporation  
2875 S. 25th Ave., Broadview, Ill. 60155



Circle 12 on literature card

# TRON SUB-MINIATURE PIGTAIL FUSES

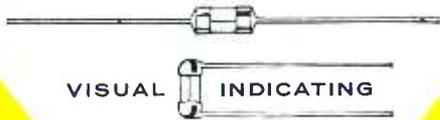

VISUAL INDICATING

**BODY SIZE ONLY**  
**.145 x .300**  
**INCHES**

For use on miniaturized devices, or on gigantic space tight multi-circuit electronic devices.

Glass tube construction permits visual inspection of element.

Smallest fuses available with wide ampere range. Twenty-three ampere sizes from 1/100 thru 15 amps.

Hermetically sealed for potting without danger of sealing material affecting operation. Extremely high resistance to shock or vibration. Operate without exterior venting.

**Insist On**  
**BUSS**

**QUALITY**  
Fuses

Write for  
BUSS  
Bulletin SFB

BUSSMANN MFG. DIVISION, McGraw-Edison Co., St. Louis, Mo. 63107

from the field a few years ago, is returning. Hoffman Electronics Corporation, which produced more than a million sets prior to withdrawal from the television industry in 1966, will be offering color television receivers and solid-state stereophonic phonographs to the public this Fall. The West Coast manufacturer will market its new products to the public through franchised dealers. Color receivers will be utilizing the shallow-depth, rectangular picture tube.

## New Building

Antennacraft Co. is now in operation in their newly completed modern factory building located just outside of Burlington, Iowa, on highway 34. It is a steel and concrete structure that



doubles the floor space of the former location. A matching building, now under construction, will again double their floor space.

## Color CRT's and Yokes

Color television picture tubes have been receiving a lot of attention lately among the manufacturers of sets. It seems no one can agree if there are too many or too few and of which size you're asking about.

Major companies building color CRT's are RCA, Rauland (Zenith), National Video, Sylvania, Philco, General Electric,

# BUSS: The Complete Line of Fuses and...

Nearly 300 are broadcasting multiplex stereo programs. Educational FM stations number 243, with another 14 due on the air this summer. There are 3976 AM stations on the air, with 85 more that are authorized but silent for one reason or another.

Safety and Special Radio Services have made spectacular growths. Here are some statistics of transmitters authorized:


Amateur	298,338
Aviation	172,663
Citizen's Band	2,197,302
Industrial Group	1,161,505
Land Transportation	396,211
Marine	195,670
Public Safety	509,800
<b>TOTAL</b>	<b>4,931,489</b>

On the not-so-sunny side, FCC pointed out that they received 27,135 complaints of TVI, 3,725 of BCI, and 7,381 others. Of this 38,241, they investigated 18,922, and received the help of 799 interference committees. They found 480 unlicensed stations and 47 cases of indecent language. There were 2772 violation notices issued to ship stations, 2596 to broadcast stations, 3915 to non-broadcast services, and an undisclosed number of amateurs. There was a net of 8401 new First- and Second-Class Radiotelephone Licenses granted, bringing the total to 145,767 (about 55% of them First's). First- and Second-Class Radiotelegraph Licenses number 15,390.

FCC has had a busy year. And this year will be busy for the licensed 160,000 technicians whose job it will be to maintain those 4,900,000 Safety & Special Services transmitters and the 7476 broadcast stations, not to mention installing the other 901 stations that are authorized.
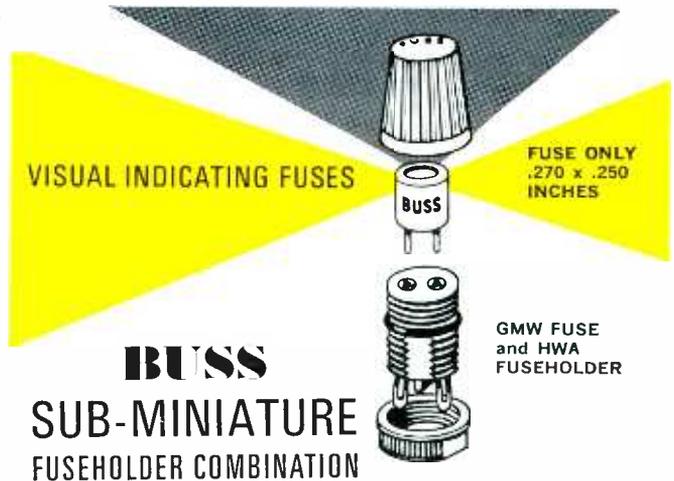
## Staging A Comeback

An old-timer in the television industry, a brand that withdrew



**BUSS**  
**SUB-MINIATURE**  
**FUSEHOLDER COMBINATION**

For space-tight applications. Fuse has window for inspection of element. Fuse may be used with or without holder.

Fuse held tight in holder by beryllium copper contacts assuring low resistance.

Holder can be used with or without knob. Knob makes holder water-proof from front of panel.

Military type fuse FM01 meets all requirements of MIL-F-23419. Military type holder FHN42W meets all military requirements of MIL-F-19207A.

**Insist On**  
**BUSS**

**QUALITY**  
Fuses and Fuseholders

Write for  
BUSS  
Bulletin SFB

BUSSMANN MFG. DIVISION, McGraw-Edison Co., St. Louis, Mo. 63107

Circle 13 on literature card



Screw type slotted knob that is recessed in holder body and requires use of screwdriver to remove or insert it.



Screw type knob designed for easy gripping, even with gloves. Has a "break-away" test prod hole in knob.

## BUSS Space Saver Panel Mounted Fuseholders

Fuseholder only 1 3/8 inches long, extends just 3/32 inch behind front of panel. Takes 1/4 x 1 1/4 inch fuses. Holder rated at 15 ampere for any voltage up to 250.

Military type available to meet all requirements of MIL-F-19207A.



Write for  
BUSS  
Bulletin SFH-10

BUSSMANN MFG. DIVISION, McGraw-Edison Co., St. Louis, Mo. 63107

some of RCA's output. Motorola, meanwhile is rolling along smoothly with their own supplier (National Video) of 23" rectangular color tubes, which they pioneered.

With color picture tubes in such short supply, it seems the replacement market may find itself working primarily with "re-built" color CRT's. These are generally tubes that have been regunned, since the phosphor-depositing process is expensive and complicated—approaching new-tube costs.

While color CRT's are in the limelight, over on the sidelines some observers are predicting a scramble for other color parts—particularly yokes, as was pointed out recently in **Television Digest**. Three manufacturers are the main source of yokes for color sets: Advance Ross Electronics, F. W. Sickles Div. of General Instruments, and of course RCA. In a not-too-veiled hint, RCA told color-set manufacturers that good purchasing procedure "includes the development of secondary sources of supply." This includes all types of parts, obviously, but copper scarcities have caused a "run" on suppliers of yokes, who can't seem to get enough raw material to meet the demand. The yoke builders, and their suppliers of copper wire, indicate that set manufacturers are ordering "an unreasonable and unrealistic" quantity of yokes—more, in fact, than they can use.

From all this controversy, however, one thing the service technician and dealer can be sure of: Color television is no longer the "baby" of RCA and the industry; it's big business!

### CATV School

Twenty-three CATV operators from all over the country became the 150th class to complete the one-week CATV course offered by the CATV Division of **Jerrold Electronics Corp.** The course covered CATV system design, maintenance, and troubleshooting. Emphasized were Jerrold transistor systems, microwave, and test equipment. Jerrold has been holding classes for the past 13 years. More classes are to be held soon. ▲

# Fuseholders of Unquestioned High Quality.

and soon Westinghouse. Some produce only for themselves, some only for others, some do both, all depending on what size you're asking about.

RCA, largest source of 21" round color tubes, has gone through several phases of rationing this popular commodity, sometimes amid cries of "overcharging." From a policy of "none to anyone," RCA has progressed through "limited quantities to others" to a "no-limit" supply. Recently, however, the word came out that RCA would again supply primarily its own needs and only limited quantities would be available to others. During the earlier "freeze," other tube makers started building 21" color CRT's but not sufficiently to supply every-

one. On the heels of this announcement was the news that RCA's new 19" rectangular 90° color tube would be available to manufacturers in "sample commercial quantities." This new tube contains a "rare-earth" (Europium and Yttrium) red phosphor of the type pioneered by Sylvania, and also includes improved blue and green sulphide phosphors. These improvements, which result in mainly brighter color pictures, are being incorporated in all RCA color CRT's; the new line is tagged "Hi-Lite." The Sylvania 19" tube, introduced earlier also contains rare-earth phosphors.

General Electric, meanwhile, has started producing what they call "an improved version" of the shadow-mask type—in a 12" size. This new three-gun tube incorporates the raster-brightening rare-earth phosphors already mentioned. G-E has tested the new tube in a variety of screen sizes, but production will be limited during 1965.

Sylvania plans to double its color-tube production this year. Admiral is tooling up for pilot production, Philco's plans for their own tubes are far along, and Westinghouse is working on developing their own color CRT's.

Most major set manufacturers are now on the 25" bandwagon, and the tubes for these may develop into a supply problem, since RCA is allocating only beyond their own needs. Rauland (Zenith) and Sylvania are both producing tubes in this size, but it is doubtful they can fill the demand without



For protection of all types of electronic and electric devices

The complete line of BUSS and "TRON Family" fuses includes quick-acting, slow-blowing, signal or visual indicating fuses in sizes from 1/500 amperes up.

All standard items are easily obtained through your BUSS distributor, but if you don't find what you want get in touch with us.




Write for  
BUSS  
Bulletin SFB

BUSSMANN MFG. DIVISION, McGraw-Edison Co., St. Louis, Mo. 63107

Circle 13 on literature card

August, 1965/PF REPORTER 21
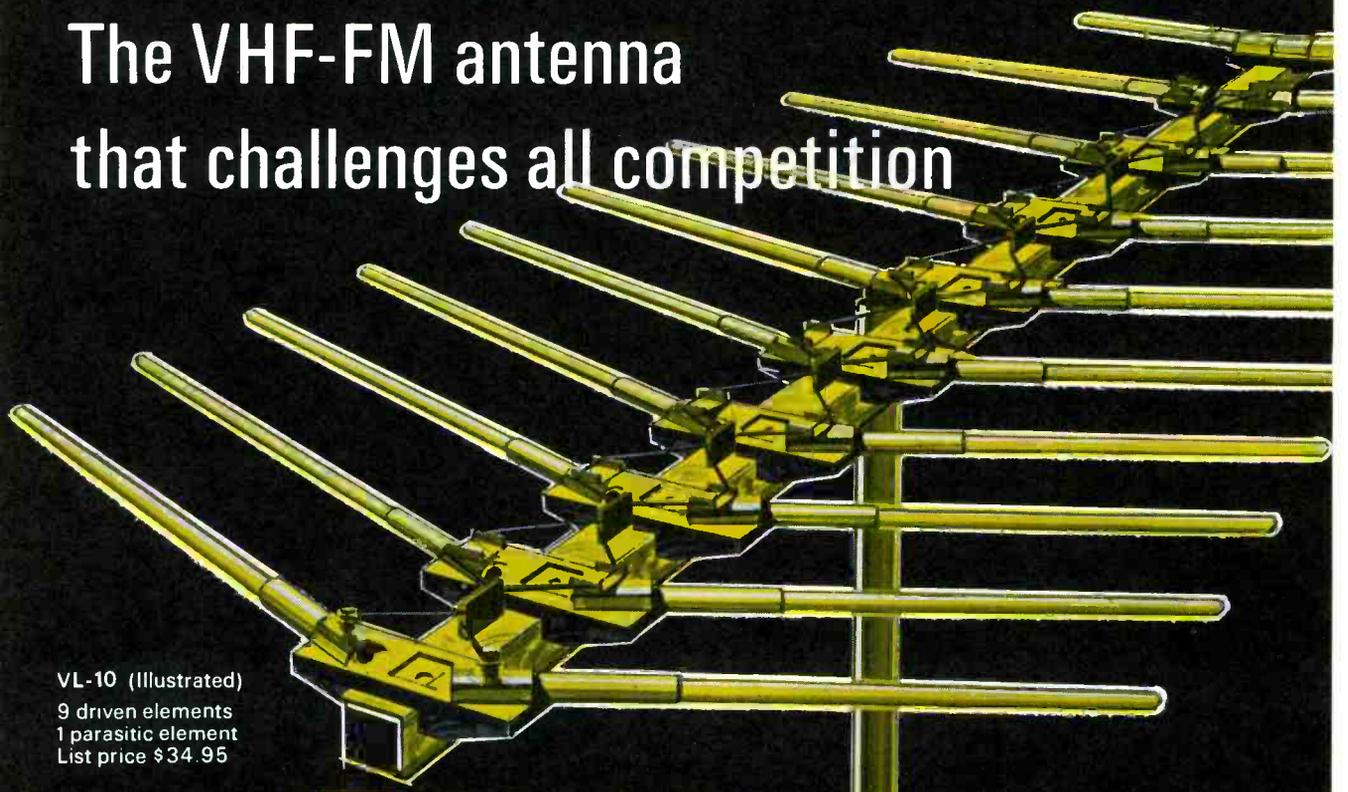
# The VHF-FM antenna that challenges all competition




VL-10 (Illustrated)  
9 driven elements  
1 parasitic element  
List price \$34.95
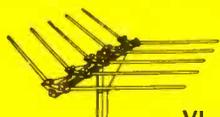
## NEW **FINCO**<sup>®</sup> *Swept Element* "COLOR-VE-LOG" VHF-FM ANTENNA


Finco's Color Ve-Log challenges all competition on color or black and white reception and stands behind this challenge with a "Guarantee of Supremacy". The swept element design assures the finest in brilliant color and sharply defined black and white television reception – as well as superb FM monaural and stereo quality. FINCO precision-engineered features make these advanced-design antennas indispensable to good home sight-and-sound systems. And, of course, they carry the famous unconditional guarantee from the leading manufacturer in the field – FINCO. Promote the Color Ve-Log Antennas with pride, sell them with confidence, and profit handsomely.

Featuring Finco's Exclusive Gold Corodizing



VL-5

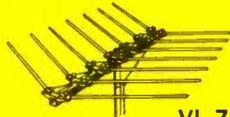5 element VHF-FM  
5 driven elements  
List price \$16.95



VL-7

7 element VHF-FM  
7 driven elements  
List price \$23.95



VL-15

15 element VHF-FM  
9 driven elements  
6 parasitic elements  
List price \$46.95



VL-18

18 element VHF-FM  
9 driven elements  
9 parasitic elements  
List price \$54.50

The FINNEY Company • 34 W. Interstate Street • Bedford, Ohio

Write for color brochure #20-307, Dept. 310

# What you should know about TV lead-in before you buy!



By Roland Miracle  
 Engineer, Electronics Division  
 Belden Manufacturing Company  
 Richmond, Indiana

There are four basic types of cable for TV lead-in on the market today—flat ribbon, tubular, encapsulated, and coaxial. The advantages and disadvantages of each type should be understood before making an installation.

Here, Roland Miracle, electronics engineer at Belden Manufacturing Company's Richmond plant, answers questions regarding the suitability of the 300-ohm twin-lead types and coaxial cable.

**Q.** What is the best TV lead-in for most applications?

**A.** The choice is not simply between coaxial cable and twin-lead. This is because there is a great deal of difference between old style 300-ohm line and encapsulated 300-ohm line. Ordinary ribbon lines will give troublesome and inconsistent performance in color or UHF installations.




**Q.** What are the differences in 300-ohm line?

**A.** Flat ribbon and tubular 300-ohm line perform well at UHF frequencies only when they are free from all traces of surface deposits. When these lines encounter dirt, rain, snow, salt, smog, fog or industrial deposits, problems arise. Impedance drops abruptly, and attenuation soars. Ghost pictures result.

Encapsulated 300-ohm line features a low loss cellular polyethylene protective jacket which keeps all surface deposits out of the critical conductor area—regardless of

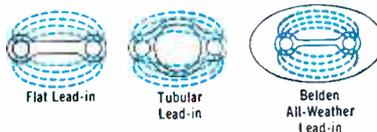weather conditions. This type of lead-in is made by Belden under the name of "Belden All-Weather Permohm\* Lead-In" and is highly recommended for UHF and color installations.



**Q.** When and where are coaxial cable installations best?

**A.** Coaxial cable systems are preferred where strong interference signals are present. This will usually be an urban location near a hospital, an industrial complex, or other such locations where extreme interference is radiated.

**Q.** Are the transmission characteristics of coaxial cable superior to 300-ohm twin-lead?

**A.** No! The attenuation of TV signals through coaxial cable is much greater than through 300-ohm twin-lead. This higher loss reduces the signal delivered to the TV receiver and makes booster amplifiers necessary at VHF frequencies in all but high strength areas. Coaxial cable systems also require two matching transformers—one at the set and one at the antenna—because all coaxial cables are unbalanced lines and normally have a 75-ohm impedance. TV antennas and receivers are normally designed to use balanced lines having 300-ohm impedance.

**Q.** How does the attenuation of Permohm compare with coaxial lead-in?

**A.** The chart in the next column compares the values of Belden Permohm (No. 8285) with a typical coaxial line (RG-59U) under similar conditions. Note, how even when enclosed in metal pipe, the encapsulated line delivers a stronger signal than an equal length of coaxial cable under the same circumstances. The difference is even more apparent at UHF frequencies.

## 300 MICROVOLT ANTENNA SIGNAL

Channel 6		
RG-59U	[Bar]	201
8285 in air	[Bar]	261
8285 in pipe	[Bar]	210

Channel 13		
RG-59U	[Bar]	153
8285 in air	[Bar]	231
8285 in pipe	[Bar]	172

Channel 20		
RG-59U	[Bar]	99
8285 in air	[Bar]	195
8285 in pipe	[Bar]	123

Channel 83		
RG-59U	[Bar]	69
8285 in air	[Bar]	162
8285 in pipe	[Bar]	100

**Q.** What about cost?

**A.** A coaxial cable installation is much more expensive. The cost of a typical 75-ft. coaxial lead-in installation is about \$20.00 compared to \$7.00 for the best encapsulated 300-ohm lead-in. This extra cost results from the higher cost of the coaxial cable plus the extra cost of the two matching transformers. Also, coaxial cable requires carefully made electrical connections which are time consuming and costly.

**Q.** Does Belden make all types?


**A.** Yes. Belden offers the most complete line of TV lead-in, including coaxial cable. However, because of the many superior transmission characteristics of Permohm 300-ohm line, it continues to be the best lead-in for 90% of all TV installations. Ask your distributor about Belden Permohm.

BETTER BUILT  
 BETTER BUY...



BELDEN MANUFACTURING COMPANY  
 P. O. Box 5070-A • Chicago, Illinois 60680  
 8-6-5 \*Belden Trademark Reg. U.S. Pat. Off.

Circle 15 on literature card

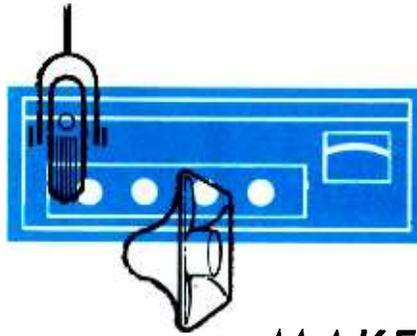

## MAKE MONEY IN

# RENTALS SALES LEASES

**A path to profits in audio systems.**

by Thomas R. Haskett

Lots of people—merchants, educators, political candidates, etc.—need to reach the public through sound and public-address systems. Providing the equipment for these requirements can be a profitable addition to a service business. There are three general ways that audio gear is handled by a service shop: short-term rental, long-term lease, and outright sale.

### **Rental**

It's likely that if a client is going to use your equipment for only a few days he will be renting it. Enterprises that are likely prospects for sound and public-address (PA) equipment rental include any activity of a temporary nature. For instance, church bazaars and bingo parties, company picnics and beach parties, jazz festivals, band concerts in the park, and religious revivals all are naturals for rental arrangements.

At a small company picnic where it is necessary only to provide music and a microphone for speeches and announcements, the client normally will request only that you deliver the equipment to the site, hook it up, assure him that it's working, and then pick it up when he's finished with it. If the equipment is relative-

ly uncomplicated, he will probably provide an operator. Your responsibility is merely to furnish working gear.

The situation is different, however, at a large political rally or an important commercial venture (such as an outdoor symphony concert). Here the client is not merely concerned that the equipment works; he wants his PA coverage to be handled properly. Thus, he will be glad to pay for the services of a technician to set up the gear and operate it to provide the best possible coverage of the event.

### **Leasing**

When a client desires the use of sound equipment for more than about a week, the arrangement is generally referred to as a lease. Most leases involve rather extended periods of time (months or years), but there is no rigid rule except that the longer the customer desires the equipment, the lower the lease rate is. A client may, for example, wish to install a background-music and paging system in a restaurant that he has leased and is operating. Since he doesn't own the restaurant, he may not want to buy the sound equipment.

It goes without saying that when

you rent equipment it must be kept in working condition. It is unlikely that an amplifier will develop trouble during a three-day period of use, although it's a good idea to have spare units on hand for immediate replacement in case trouble does arise. When it comes to a lease lasting several months, the spare equipment becomes mandatory, because part of your lease contract will include a provision that you service and maintain the equipment and insure continuity of service.

### **Sales**

When an audio shop rents and leases PA gear, it is natural that some customers will come to the shop when they are thinking of purchasing such equipment. Some dealers use the lease-purchase plan, which allows the client to apply a portion of his lease fees toward the eventual purchase of the item. If a new amplifier is purchased, it carries a manufacturer's guarantee; however, if the same amplifier is leased with an option to purchase, the guarantee may expire before the client actually buys the unit, and it's your duty to make this point clear to him. On-hand used equipment, which is leased and later purchased, carries no guarantee unless

you choose to guarantee it yourself. Some shops offer rebuilt and reconditioned amplifiers with a 30-day guarantee. This often encourages a sale, but yet isn't burdensome or expensive for the dealer.

Still other shops sell the equipment and a maintenance contract along with it. You should point out to the customer that in a commercial venture he may be losing money if his equipment fails and he can't get it repaired in a hurry. Your job will then be to check it out periodically and anticipate trouble, as well as to be on call for emergencies.

### Equipment Involved

To engage in audio rental, lease, and sales, you must maintain a certain amount of equipment on hand—ready to go at a moment's notice. For outdoor work, you'll need several horn-type radiators and their associated drivers. Matching transformers designed for use with 70-volt lines are necessary, and of course you'll need several rolls of speaker cable. You may find that indoor jobs can be done with horn speakers. However, if you are going to engage in musical concerts, sealed enclosures of the high-fidelity type are a much better investment, as they have a broader frequency response.

Two types of amplifiers are useful in sound and PA work. The first, and older, is the integrated amplifier with two or three built-in microphone preamplifiers. You can

obtain this type in power outputs from 12 to 150 watts, with 30 or 40 watts being the most useful size. These units include a phono input for a crystal or ceramic (high-level) phono cartridge; they have constant-voltage output and 4-, 8-, and 16-ohm taps.

The other type of amplifier consists of a mixer-preamplifier and a power amplifier. The preamplifier may have from three to six microphone inputs, a tape input, and a magnetic-phono input. A cathode-follower output stage provides about 2 volts RMS, and the unit sometimes is equipped with a VU meter. Along with the mixer-preamplifier, you'll need a power amplifier designed to work with the mixer. The amplifier generally has a single input, which requires about 1 or 2 volts RMS to drive it, and the various constant-voltage and low-impedance outputs for speakers.


The advantages of the preamplifier-amplifier arrangement are that the inputs are more flexible and as many power amplifiers as desired can be added. For instance, when installing the sound system for a jazz festival, it's not unusual to have six or eight microphones in use at various times. In such cases, two mixer-preamplifiers would be used, with their outputs connected in parallel across a buss feeding several parallel-connected power amplifiers. Each PA then drives its own bank of speakers. This parallel arrangement offers the additional advantage of redundancy: If

any single amplifier failed in service, the rest of the system would continue to function, and if necessary, you could use the remaining power amplifiers to drive the extra speakers (at a slight reduction in volume).

When the client desires music on location, some shops still rent or lease phonographs or turntables for use with PA amplifiers. But the cartridge-tape recorder is more practical, especially where nontechnical personnel must operate the system. You can buy prerecorded tapes and wind them on cartridges, or you can dub your own tapes from discs. Sometimes the customer will want a sales message recorded for use at a display; in this case a repeating cartridge is used.

Cartridge-type players are available for vehicular use, and this is another possibility for your service. Any type of truck or automobile which can be fitted with rooftop carriers and horn speakers can be used as a mobile sound truck. All that is required is the addition of a transistor amplifier and a cartridge-tape player, powered by the car battery. Such a vehicle is useful in political campaigns, sales promotion drives, and many other similar events. Movies are sometimes promoted prior to their local opening by such a truck displaying posters and playing a cartridge which contains a radio spot announcement or a portion of the sound track of the movie.

● Please turn to page 46

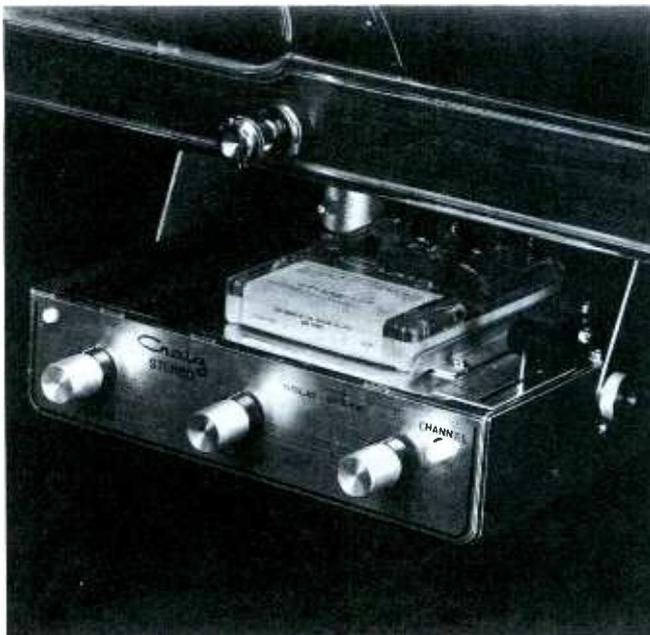

Cartridge-tape recorders are available for automobile use.



Company picnics are a good prospect for audio gear rentals.



lower than those required for tubes.

The highest voltage above chassis ground in a typical all-transistor unit is -43 volts. Since there are no DC voltages greater than 43 volts across any component, capacitor breakdown problems are minimized. Furthermore, because of the high efficiency of transistors, compared to tubes, very little heat is generated.

### All-Solid-State Stereo

The power-supply section for a completely solid-state unit is shown in Fig. 1. It consists of two power supplies sharing the same power-transformer core. Unregulated DC at +24.5 volts and -24.5 volts for the audio power amplifiers is obtained from a full-wave bridge rectifier. The transformer center tap is grounded in order to obtain voltages of equal but opposite polarity with respect to ground. Note that only half of the total bridge-rectifier output voltage is applied individually to filter capacitors C29 and C30.

Regulated +16 volts DC is fed from transistor X1 to the multiplex circuit, the IF amplifiers, and the front end of the receiver. The transistor regulator is referenced to zener diode M7.

A full-wave, center-tap rectifier (M5 and M6) applies 43 volts DC to the direct-coupled series transistor regulators (X2 and X3) which maintain a constant output voltage of -28 volts. This voltage is reduced slightly by decoupling networks prior to application to the preamplifier and audio amplifier stages.

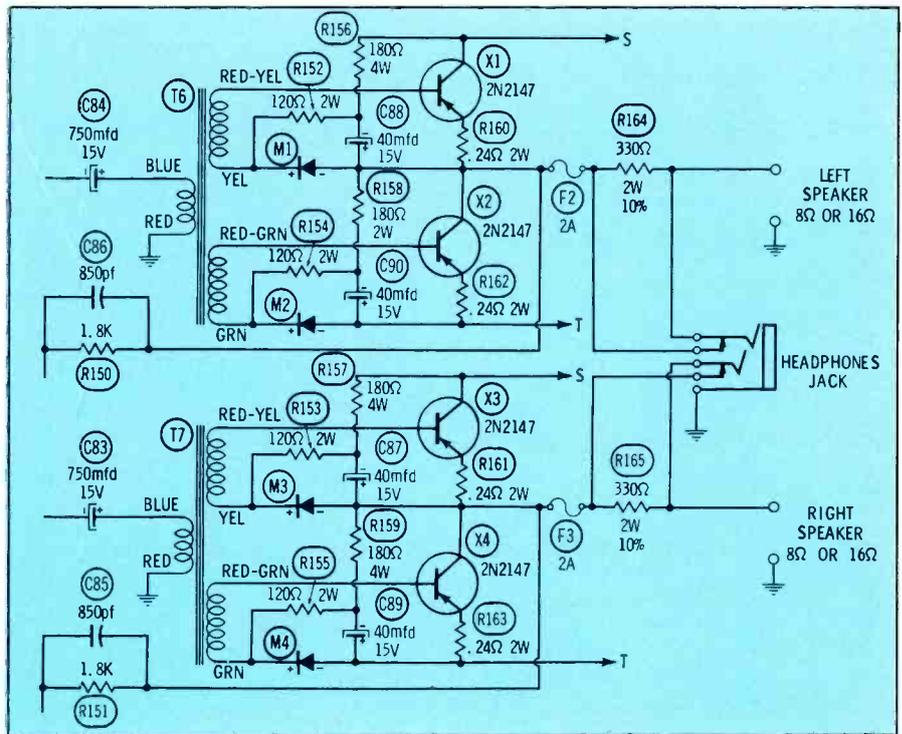


Fig. 2. Power output circuit uses four 2N2147 transistors, but no transformer.

Employing voltage regulators and separate rectifiers insures that heavy instantaneous current surges in the output stages have no effect on the operation of rest of the circuits.

Each audio channel employs a pair of 2N2147 power transistors in the output stages, as shown in Fig. 2. The two channels combined are capable of delivering 112 watts of IHF music power to 4-ohm speaker systems, or 75 watts to 8-ohm speakers. Who says transistors can't compete with tubes?

Notice in this circuit there is no output transformer, which has been somewhat of a bottleneck in hi-fi

systems until recently. Since the speakers are not isolated from the DC circuits each speaker network is fused to prevent damage due to inadvertent shorting of the speaker leads. A stereo headphone jack is provided which cuts off the speakers when the headphones are used.

The audio amplifier ahead of the output stages employs 18 transistors and provides ample gain: 3-millivolt sensitivity for magnetic phono cartridges and 180-millivolt sensitivity for tape and auxilliary inputs. Frequency response is  $\pm 1$  db from 5 to 10,000 cps at 25 watts output per channel, power band-

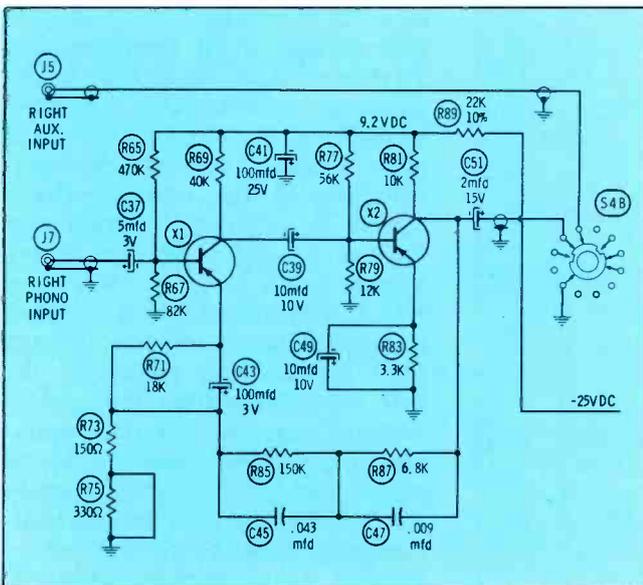


Fig. 3. Preamplifier uses electrolytics for impedance match.

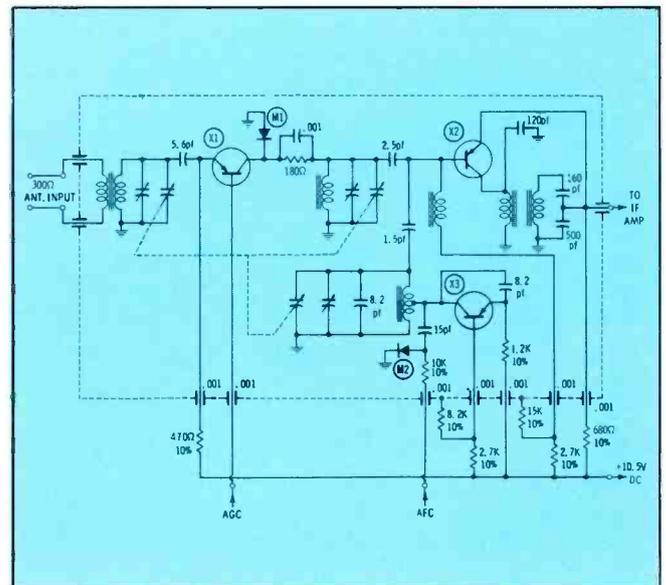


Fig. 4. Solid-state RF section uses three PNP transistors.

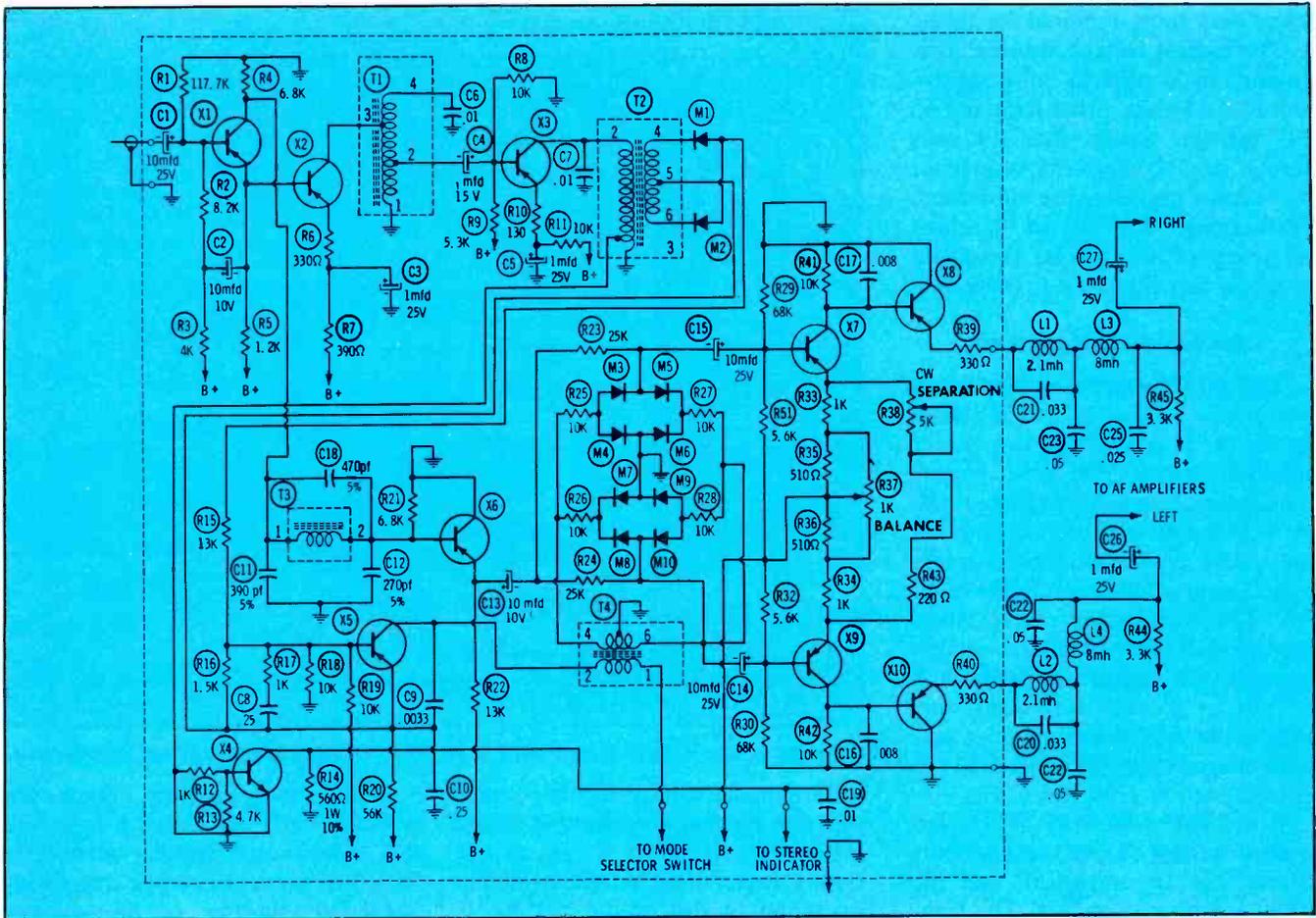


Fig. 5. Multiplex decoder uses a total of ten transistors and ten signal diodes.

width is 8-60,000 cps, and distortion is as low as or lower than that of most good quality tube amplifiers.

The stereo preamplifier uses a total of four transistors (two for each channel). Notice that the phono input is coupled to the base of X1 through a 5-mfd electrolytic capacitor to match the low input im-

pedance of the transistor. The circuit of the right-channel preamplifier is given in Fig. 3.

The front end, as shown in Fig. 4, employs three transistors and two diodes in the RF, mixer, and local oscillator stages. Front-end overloading, even on strong local signals, is prevented by AGC and a

shunt diode in the RF amplifier. Sensitivity, nevertheless, is 1.2 microvolts for 20 db quieting and 2.7 microvolts for full limiting and 40 db quieting.

The mixer drives a 4-stage IF amplifier, which in turn feeds a broadband ratio detector. The composite stereo signal from the detector is applied to a printed circuit board which contains the multiplex circuits. This multiplex (FM stereo) unit consists of 10 transistors and 10 diodes, as shown in Fig. 7. The sampling (time-sharing) technique is used for deriving the individual audio signals. The 19-kc pilot signal (part of the composite stereo signal) is amplified by transistors X1 and X2 and is doubled in frequency to 38 kc at the output of X3. This synchronized 38-kc signal is applied to diodes M3 through M10 and used in recovering the L-R information from the double-sideband, suppressed-carrier multiplex signal. The separated stereo signals are fed through transistors X7, X8, X9, and X10 through compensating networks to the corresponding audio amplifier channels.

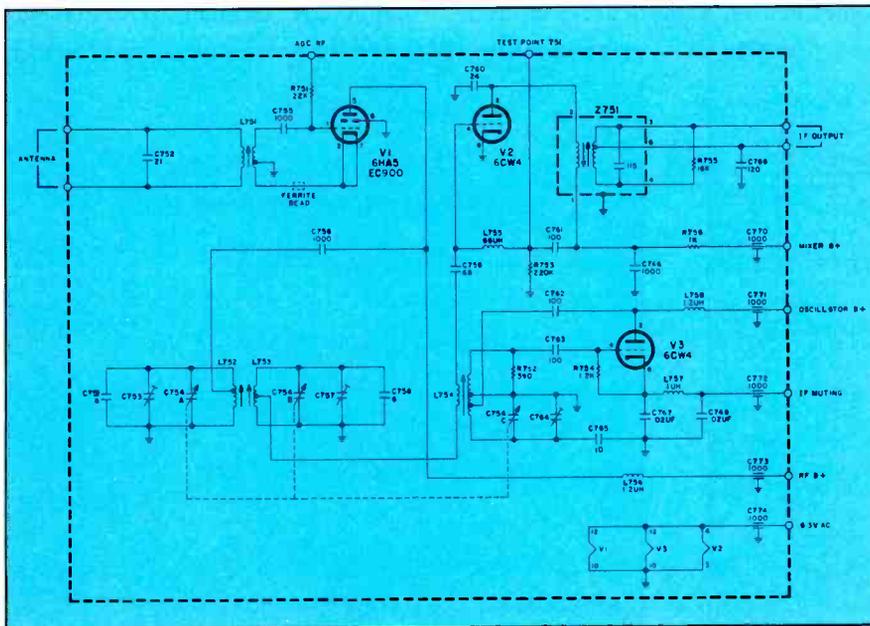


Fig. 6. This hybrid receiver employs tubes only in the FM front-end circuits.

• Please turn to page 47

**Dirt removal from tape  
and phono mechanisms.**

# *keep it clean!*



by Steve P. Dow

Cleaning tape-recorder and phono mechanisms is an important part of audio-equipment maintenance. As use of a machine increases, regular cleaning becomes all the more essential. Environment has much to do with the amount of dust and grime that accumulates; recorders with fans attached to motors draw in dust with the cooling air. Because dust and heat harden bearing lubrication in time, the motor torque needed to pull automatic record changers through their cycles and run tape recorders at stable speeds is lost. Dirty idlers and belts soon lose their traction and slip causing erratic operation. The critical tension involved in friction clutches is drastically altered as pads become saturated with dirt. Failure of brakes to control fast-moving spools of tape causes breakage and spills.

## **Tools and Materials**

Cotton swabs, available at any drugstore, are good for cleaning mechanisms, and a small wooden typewriter brush is handy for getting dirt out of small grooved pulleys and gears. (Don't use a plastic brush because solvents will melt it.) A supply of clean lint-free rags should also be kept on hand. Standard solvents for tape and phono work are carbon tetrachloride, acetone, wood alcohol, and benzene. Carbon tet is an excellent degreaser and a good rubber solvent. Acetone is a plastic and cement solvent and loosens sealing compounds used to lock mechanical preset adjustments; it also breaks down hard deposits of tape-oxide grime that collects on guides and tape lifters. Wood alcohol is a mild solvent and

can be applied to sensitive plastic parts that are attacked by carbon tet and acetone. Benzene is a rubber cleaner and traction surface reactivator.

Use caution with any solvent when cleaning plastic parts; most plastics are soluble in certain solvents. Whenever there is doubt about whether a solvent will melt a plastic, a simple test can be made by dipping a swab into the solvent and holding it against some unexposed area of the part until it dries. If the cotton adheres to the part, the solvent can damage it. Benzene, wood alcohol, and acetone are inflammable—don't keep a large supply on the bench! Work from a two-ounce bottle, and use an applicator; never pour a solvent onto a part or into a mechanism. Rags that have been used with solvents should be kept in a metal container. Whenever using acetone, or carbon tet avoid breathing the vapors. Keep a small fan on the bench to blow the fumes away from your face, and, if possible, keep a window open for adequate ventilation.

## **Idler Drive Maintenance**

Idlers couple motor shafts to flywheels and turntables. Slippage is caused when traction surfaces become hard and shiny after long periods of use; idlers with scarred surfaces or bumps must be replaced. Traction surfaces can be restored by rubbing them with benzene; work the benzene in well with a cloth until all the glaze is gone. A clear idler has a rich carbon-black color. Note the number of spacer washers above and below an idler when removing it; these are used

for positioning and changing the height, and could cause trouble if improperly replaced.

Stepped shafts on motors provide the speed selection on most changers and idler-driven recorders; clean these with carbon tet to remove rubber deposits and oil. Never clean motor shafts with the motor running. Threads from the swab or cloth may drape around the narrow sections causing them to bend and introducing flutter and speed problems. Shafts with coiled-spring diameter sections must be cleaned with care so the spring position won't be altered.

## **Cleaning Belt-Drive Mechanisms**

Belts used in recorders are of three types: rubber, rubber-backed fabric, and coil spring. Rubber belts are self tensioning and are made in four forms—grooved, square, and round (commonly called "O" rings). Oil and grease is picked up in minute quantities and absorbed by belts; this makes them soft and causes slippage. Belts can be degreased and cleaned by immersing them in benzene for a few seconds, then wiping them off with a cloth. Tacky, stretched, or cracked belts must be replaced. When a belt is cleaned or replaced, the pulley should be checked to make sure that no rubber deposit is left. Rubber-belt slippage causes small particles of rubber to peel off and adhere to the pulley; the replacement belt then has a tendency to vibrate or grab. Carbon tet cleans and degreases metal pulleys; nylon pulleys should be cleaned with benzene.

Fabric belts are used in machines as slipping clutch devices; they are

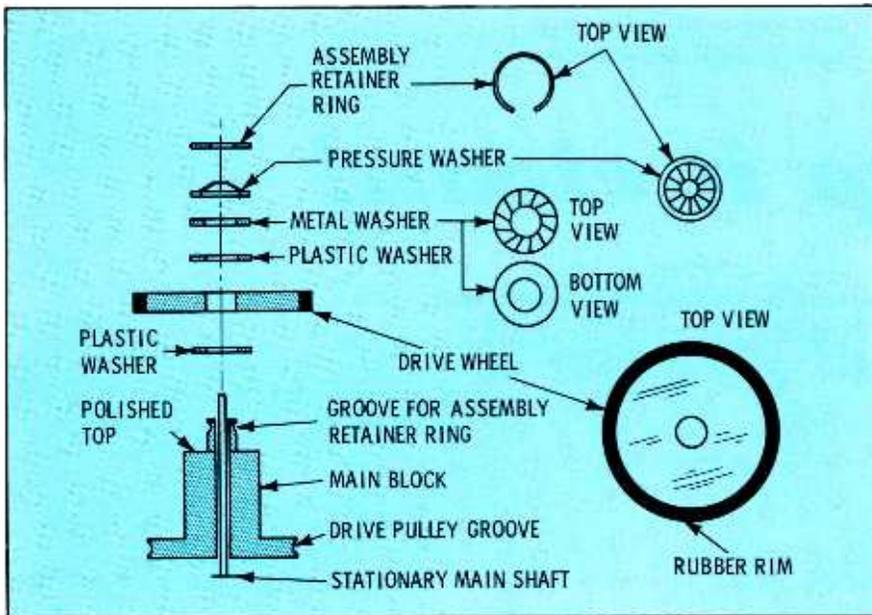


Fig. 1. Blown-up view showing parts of a typical surge-clutch assembly.

not elastic and require tensioning. By changing belt tension, the torque on a driven pulley can be altered. When rubber-backed fabric belts wear out, the rubber impregnates the fabric and slip qualities are lost. It's hard to clean fabric belts because the solvent dissolves the backing; without backing the fabric frays and the belt comes apart. When replacing fabric belts, be sure the pulleys and tension rollers are free of oil and dirt. If they are not, the new belt will soon fail.

Coil-spring belts are quite trouble free but do require cleaning to remove grease and oil. The spring should be dipped in carbon tet and allowed to dry.

### Cleaning Brake Mechanisms

Recorder brakes must stop the tape smoothly without spilling or tearing. Dirt and grease cause brakes to work erratically or fail completely. Cork is often used for recorder brakes because it provides smooth braking with little tendency to grab. Apply benzene carefully when cleaning cork brake surfaces so that the glue holding the pad won't be loosened. Some recorders use rubber drums and plastic shoes. Others use rubber shoes with tensioning devices to make braking smooth. Use benzene on metal brake drums; wood alcohol should be used on plastic drums and shoes. When rubber is used in a braking system, clean it with wood alcohol. If the alcohol doesn't restore the surface, use a bit of benzene; apply just

enough so that it evaporates in a second. Don't rub it in. Too much benzene will make the brakes grab.

Cord brakes are lengths of cord strung around drums attached to the feed and takeup spindles. The cords are fixed at one end, and the other end goes to spring-tension levers attached to the function-selector system. Metal cord drums are cleaned with benzene and plastic ones with alcohol. Solvents can weaken the cords; wipe them with a rag moistened in water.

Felt brake shoes absorb dirt and become hard. If no replacement pads are available, pry the old pad off and soak it in acetone. Squeeze it dry after a few minutes and then soak it in carbon tet. (The acetone removes the old cement, and the carbon tet removes the grease and dirt.) When the pad is dry, reglue it with a good plastic cement. Don't use a rubber adhesive.

### Servicing Clutches

Clutches are key parts of single-motor tape recorders; they drive the takeup reel and apply back tension

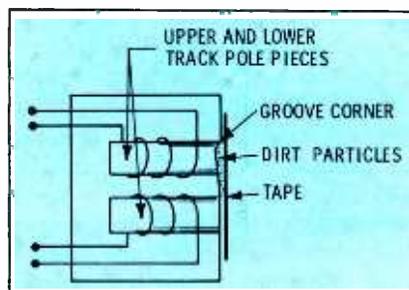


Fig. 2. Grime collection on undercut groove holds tape away from the gap.

to the feed reel. In some recorders clutches limit the surge force applied to the tape during winding and rewinding operations. Friction between two plates of a clutch depends upon the nature of the coupling surfaces, and torque transmitted through a clutch depends upon the force pushing the plates together. If the plates of a clutch get dirty or greasy, tape tension will be changed, and the tape reels will pull too hard or stop altogether.

Felt rings are used extensively in recorder clutches. They are glued to metal plates and rotate against flat metal, nylon, or plastic tables. Clean the metal or nylon clutch plates with benzene. Use wood alcohol on plastic plates. Soak the felt rings in acetone to remove all traces of the old cement; then soak them in carbon tet to remove oil and dirt deposits. When drying the rings don't twist or pull them to remove excess liquid; press them between two pieces of blotting paper. Twisting or pulling wet felt stretches it out of shape. Reglue the ring with a good plastic cement and allow it to set before reinstalling the clutch.

Surge-limiting clutches seldom seize; instead, oil gets inside and makes them slip. This causes tape to slow down near the end of reels during winding and rewinding. Surge clutches must be cleaned with care and reassembled in exactly the same way that they came apart. Clean plastic contact disks, found in some surge clutches, with wood alcohol. Fig. 1 shows the assembly of a typical surge clutch.

### Tape-Head Maintenance

Tapes are lubricated during manufacture to reduce friction. New tape has loose particles of oxide that come off and combine with the lubricant to form sticky deposits on the recorder heads and guides. These deposits greatly increase abrasion between the tape and the surface over which it passes. Deposits on the heads keep the tape away from the gap and cause loss of high frequency response. Quarter-track recorders are more prone to trouble from dirty heads than half- or full-track machines. Dirt on a quarter-track head that causes a 10db loss in playback level can prevent the machine from recording

• Please turn to page 49

# AGC Filter and Distribution Faults

Case histories of how some tough dogs were overcome.

In servicing TV sets, the technician encounters a great variety of resistor-capacitor filter networks used between the AGC source and the tubes controlled by AGC. Typical circuits for this application are shown in Fig. 1. In each circuit, resistors R1 and R2 serve two purposes: They serve as supply routes for the AGC voltage and also help filter out video signals from the AGC lines. The capacitors contribute to the filtering action and also serve as signal-return paths for the input loads of the IF and RF stages.

The RC time constants for any filter capacitor, both charge time and discharge time, must be considered. Charge time is obtained by multiplying C in mfd times R in megohms, where R is the total resistance between the AGC source and the capacitor. Discharge time is also obtained by multiplying C times R, but R is now the effective resistance between C and ground. Notice what an interesting effect this has on the RC discharge time constant on the RF filter in circuit F.

Another factor involved in the circuits is the magnitude and type of signal present at the AGC source. When AGC is derived from simple AGC, the source has a relatively small signal of detected video. With peak AGC, the video signal at the source is slightly larger. The two sources supplying supplemented AGC are out of phase, although both develop negative voltage; this out-of-phase combining makes for

a relatively clean source of AGC. When the source is keyed AGC, it not only has a greater amount of video signal, it has high-level horizontal pulses that must be filtered out.

Circuit G has a noteworthy oddity. As used in a mid-fifties Andrea, the resistor and capacitor shown in dashed lines cleaned up the horizontal keying pulse at the source, the plate of a keyed-AGC stage. Some recent RCA receivers with keyed AGC use a similar arrangement; the networks reduce harmonic hash that might be present on the keying pulse. The circuit shown in Fig. 1H is used in many models by Westinghouse, and in a few models by many different set makers. It also has a cleaner voltage at the AGC source.

Values of the resistors and capacitors in the filter networks are determined by a great number of variables. In general, the RC time constant should be large enough to filter out efficiently the lowest-frequency signals on the AGC lines, but the time constant must also be small enough to permit the DC charge on the capacitor to adjust to changing DC levels at the source without excessive time delay—the speed with which DC on the capacitor follows DC at the AGC source determines the ability of a receiver to maintain a reasonably constant signal at the video detector despite fluctuating or fading of received signals. However, if the RC time constant is too short, the network is inefficient at

filtering the lowest-frequency signals present at the AGC source. If these low-frequency signals, particularly the vertical-sync pulse trains, are impressed on the IF and RF stages, they cause, at worst, vertical-sync instability or, at least, raster shading.

Larger network RC time constants result in better pictures without raster shading and also improved vertical locking. But fading or fluctuating signals at the antenna will present contrast fluctuation at the picture tube; a prime example of this condition is the “airplane flutter” common to some early-model receivers.

It is interesting that if the charging time constant and the discharging time constant are nearly equal the picture flutter is worse than if there is considerable difference in the two time constants. For example, in early receivers using the network in Fig. 1A, the charging time constant of the IF AGC was R1 (1.5 meg) times C1 (.22 mfd), or .33 sec. The discharging time constant equalled C1 times the sum of R1 plus the resistance looking into the AGC source. Since the resistance of the source was only five thousand ohms, the discharge-time constant was practically equal to the charging time constant. With this network

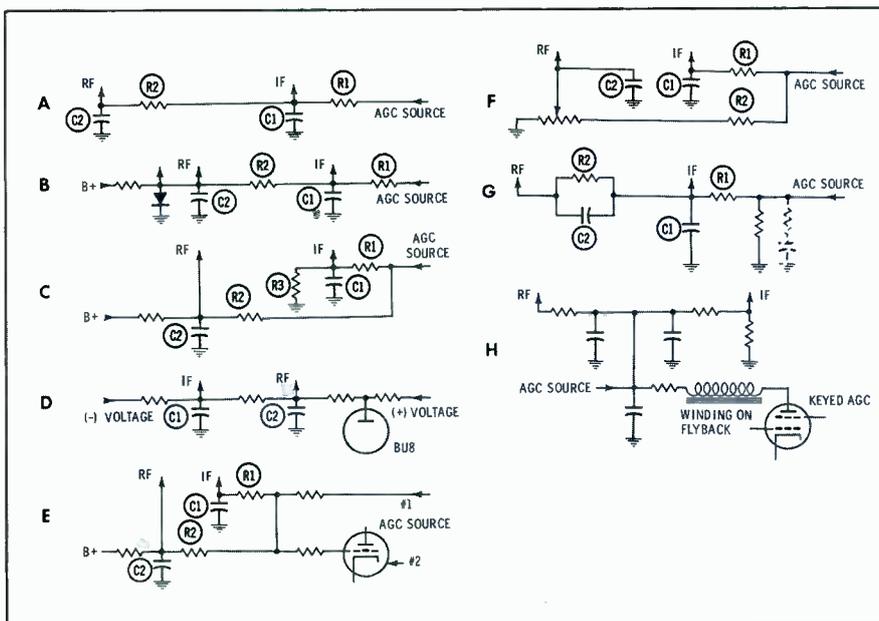


Fig. 1. Schematics of common AGC filter and voltage-distribution circuits.

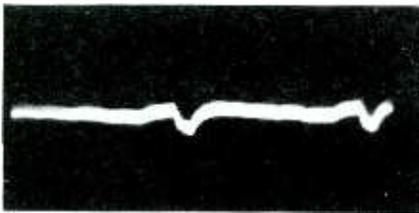


Fig. 2. One-and-one-half-volt unwanted signal on IF AGC line in Motorola set.

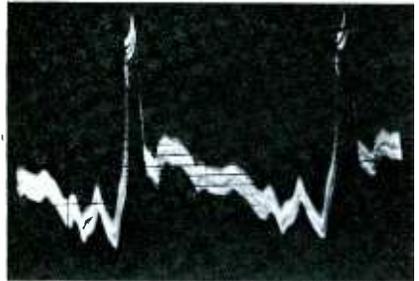


Fig. 3. One-volt unwanted signal was found on AGC line of Bendix receiver.

in a simple AGC circuit, annoying airplane flutter was invariably present. When the same network was used in a peak AGC circuit, the source resistance was increased to 1 meg. Under this condition the charge time remained the same as before, but the discharge time became .55 sec. With the discharge time greater than the charge time, the picture flutter was greatly reduced. In the circuit of Fig. 1C, R1 is 1.8 meg, C1 is 1 mfd, the charge time constant is 1.8 sec, and the discharge time is only .15 sec (since R3 is only .15 meg). With this circuit, used in many late-model Admirals, contrast flutter is negligible even in the face of fading signals.

It must be clarified that the time constant applying to an individual RC combination is not necessarily the time constant characteristic of

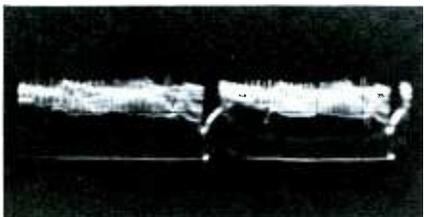


Fig. 4. Video-detector signal in Bendix; note distorted vertical back porch.

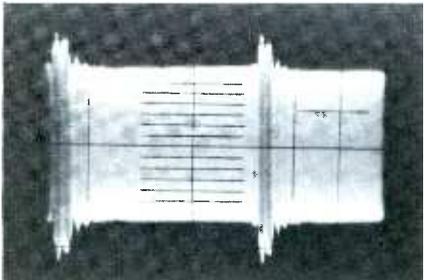


Fig. 5. Hash signal on AGC line during white-out due to open filter capacitor.

the AGC. The latter is a result of combining the time constants of all RC combinations in the circuit and is a measure of the speed with which overall sensitivity will respond to changes in received-signal level. Nonetheless, the preceding explanations should be helpful in understanding the effects of defective AGC filtering.

### Filter Troubles

Filtering of the AGC voltage will be impaired if any of the numbered resistors in the Fig. 1 circuits changes value severely, but the major cause of poor filtering is defects in the numbered capacitors. The effect of an open or low-capacitance defect naturally varies from case to case, depending on four factors: 1. type of AGC involved, 2. gain of IF stages, 3. location of open filter (on IF or RF line), and 4. amount of residual or other capacitance bypassing the open filter. In addition to symptoms on the screen, the open capacitor also causes distortion in sync and video waveforms and permits the presence of unwanted signals on the AGC line. In fact, some milder effects of filter troubles are more recognizable on scope traces than by the marginal trouble produced in the picture.

Critical vertical locking is probably the mildest trouble that can result from an open AGC filter. In one Motorola TS-292, the critical locking was accompanied by occasional vertical jitter. Scoping the AGC line—after almost everything else had been checked—revealed the signal shown in Fig. 2. This model uses a circuit similar to Fig. 1A, and the offending capacitor corresponds to C1 in that circuit. A Bendix with the same symptoms plus intermittent top hooking was found to have an intermittently open filter in the same location. This set uses the same Fig. 1A circuit with simple AGC, but the unwanted signal on the AGC line appeared as in Fig. 3. The big discrepancy between Fig. 2 and Fig. 3 is probably due to the isolation networks used at the return ends of the IF-transformer secondaries. The Bendix set also had distortion on the detected video signal as in Fig. 4; no corresponding distortion was noted on the Motorola video-detector signal. The



A



B

Fig. 6. Horizontal bars only appeared at top of picture in Westinghouse set.

distorted back porch of the vertical sync, apparent in Fig. 4, is one of several distortions found there in almost every case of open AGC filters.

Intermittent white-out on one Sylvania 518 was also traced to an open AGC filter. When the picture whited out, the scope indicated the signal disappeared at the video detector; this definitely localized the trouble to the IF and RF sections. The circuit fault was so touchy that

• Please turn to page 52




A



B

Fig. 7. More severe bar conditions appearing in some RCA TV receivers.

# Testing

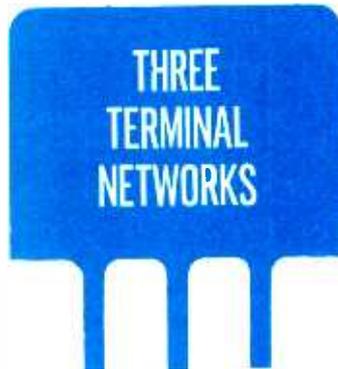

by Robert G. Middleton

Fourth in a series of square-wave-testing articles, this installment in our "Advanced Service Techniques" department takes up the analysis of RC combinations by square-wave testing procedures. Following an introductory article on the square wave itself (April 1965 PF REPORTER—"Advanced Techniques for Future Servicing"), the first three testing articles covered resistance, inductance, and capacitance. In articles that follow, you will learn how to use the knowledge gained from these first articles to analyze three-terminal networks that contain combinations of all three—resistance, inductance, and capacitance. When the only visible portion of a component pack is a set of three leads, these special tests are one of the few ways you can identify what's inside or what may be defective inside.

The techniques outlined can be carried out properly only with a triggered scope of the variety described in the March 1965 PF REPORTER article "Learning About Triggered-Sweep Scopes." Few service shops have such an instrument available; they are found mostly in television broadcast stations, electronic and research labs, and of course a few truly forward-thinking shops. If you can find any way to gain the use of such a scope, for even a few hours each month, take advantage of the opportunity to familiarize yourself with its operation and to practice the testing techniques we're outlining in this series. The time will come when much of your servicing work will require a scope like this; a lot of your present troubleshooting could be greatly simplified by a high-quality triggered scope on a rollabout cart in your shop. Future articles, in addition to showing you how to test component combinations of the ordinary and microcircuit variety, will teach you to use a triggered-sweep scope for regular troubleshooting in television and stereo receivers, where the ability of a fast-rise triggered scope to reproduce faithfully every "squiggle" in a waveform can speed your circuit analysis tremendously.—*The Editor.*

We have seen how various types of resistors, capacitors, and inductors respond to square-wave voltages. If the applied square wave has a long rise time, a wire-wound resistor responds in the same manner as a composition resistor. On the other hand, if the applied square wave has a short rise time, the reproduced wave shows the presence of inductance in a wire-wound resistor. Again, if the applied square wave has a long rise time, a high-capacitance potentiometer responds in the same way as a low-capacitance potentiometer; but if the applied square wave has a short rise time, the reproduced wave shows the presence of objectionable capacitance in a high-capacitance potentiometer.

We have also seen that when a square wave with a long rise time is applied, a paper capacitor will respond as a mica capacitor. However, when a square wave with a short rise time is applied, the reproduced wave shows the presence of inductance in a paper capacitor. In general, the larger the paper capacitor is, the more inductance is found by a square-wave test. Furthermore, test leads were seen to have appreciable inductance and capacitance in short-rise-time tests. Hence, it is necessary to keep test leads short when making a square-wave test of any component.

## RC Circuit Response

It is helpful to develop an understanding of square-wave testing by analyzing circuits which have "perfect" components. We will limit our tests at this time to circuits which comprise composition resistors and mica (or ceramic) capacitors. In turn, the reproduced square waves will show the response of simple circuits, in which the resistors and capacitors are "perfect" from a practical viewpoint. Accordingly, the shape of the reproduced square wave will obey simple theory, unless a capacitor or resistor is defective. We shall also see how departures in waveshape indicate which component is defective, and what the particular defect may be.

Before going any further, it's a good idea to review RC circuit theory. In Fig. 1, S is initially at contact 1. C is completely discharged, and there is no voltage

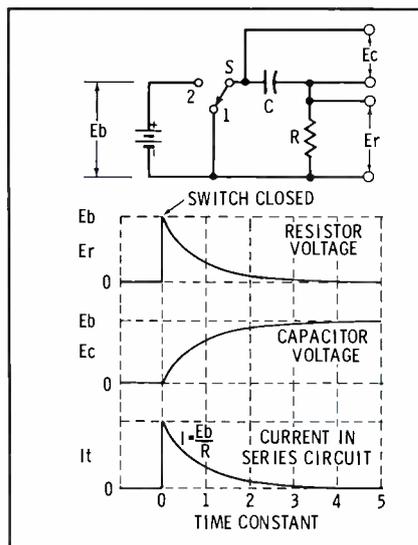


Fig. 1. RC circuit with charge waveforms across capacitor and resistor.

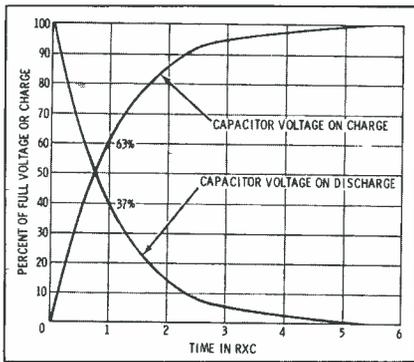


Fig. 2. Graph shows charge and discharge percentage vs time constant.

across R. S is then switched to contact 2; as the graph shows, current instantly increases to maximum value and is limited only by resistance R. As Fig. 2 shows, in one time constant (TC)—which is equal to resistance, in ohms, multiplied by capacitance, in farads—C will charge to 63.2% of voltage  $E_b$ . Consequently the voltage across R will decrease from  $E_b$  (at  $1TC$ ) to 36.8% of  $E_b$ .  $E_c$  will increase and  $E_r$  will decrease until, at 5 TC,  $E_c$  will for all practical purposes equal  $E_b$ .

The battery and switch form a very simple square-wave generator. To further explain RC circuit action let's use a conventional square-wave generator as is done in Fig. 3. Here the square wave switches symmetrically above and below zero voltage. Square-wave frequency has been selected for a value that allows C to charge to peak voltage during T (each half of the square-wave period). In other words, T equals 5 TC.

Voltage across C (Fig. 3) has a very rounded leading edge; in fact, the leading edge resembles that of a sine wave. If the voltage across C were used, the circuit would be called an *integrator*—to integrate means to unite. Since the capacitor

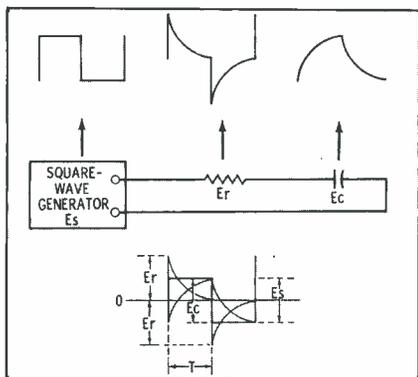


Fig. 3. Waveforms across resistor and capacitor with square wave applied.

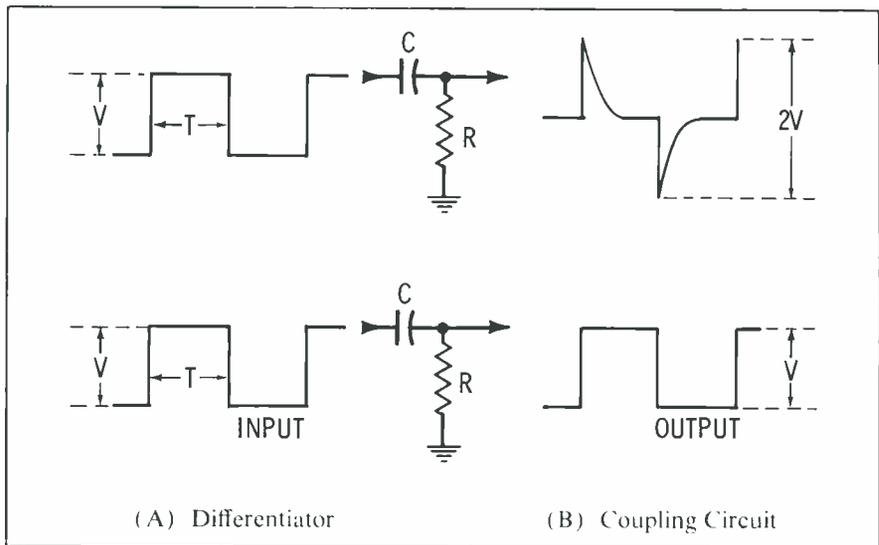


Fig. 4. Time-constant versus duration of waveform determines circuit function.

offers little impedance to the high-frequency elements of the square wave, they appear across R. Because C's impedance increases as frequency decreases, the low-frequency elements appear across C. As TC becomes longer with respect to T, the output of the integrator becomes closer to pure DC; the parts are summed. If the input waveform is AC, the alternate halves will cancel and there will be zero DC voltage remaining across C; but if the input is DC or has a DC component, C will charge to the DC voltage.

Because the highest-frequency elements appear across R the waveform has a very sharp leading edge. When the resistor voltage is considered as the output, differentiation—which means to break up into small parts—of the waveform takes place. In contrast to the integrator, the square wave is broken into a series of frequencies with maximum amplitude developed at the highest frequency elements. As Fig. 4A shows, the resulting waveform is a spike with the leading-edge rise time determined by the highest frequency, and the lagging edge determined by the circuit TC. Note the fact that the peak-to-peak voltage across R is twice the peak-to-peak square-wave voltage. Yet as was shown in Fig. 3, Kirchoff's law holds true; at any instant the sum of the voltages around this network equals zero.

Differentiation will not take place if the circuit TC is more than 10 times as long as T, because C will not have time to assume any significant charge. Instead, this circuit can

be used as a coupling circuit as Fig. 4B shows. Often compromises have to be made in circuit design, and some differentiation of low-frequency square waves occurs as is shown in Fig. 5.

#### Rise Time of Applied Square Wave

The preceding facts are comparatively well known. However, it is worthwhile to review these basic principles to reassure the beginner who is tackling square-wave testing for the first time. Next, we must ask how the *output voltage* from a differentiating circuit may depend upon the *rise time* of the applied square wave. We shall find that there are situations in which the applied square wave may be considered "perfect" (as in Fig. 3), but that there are other situations in which the output amplitude is lowered. If we do not understand how the output amplitude is related to the rise time in various practical situations, we will arrive at false conclusions.

• Please turn to page 55

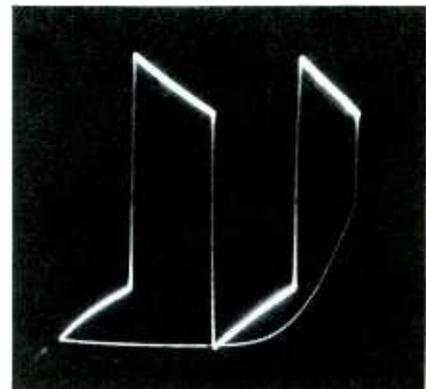


Fig. 5. Differentiation limits the low-frequency response of coupling network.



The quality goes in before the name goes on

**Choose from the complete line  
built to Zenith's high quality standards!**

## ZENITH FAMOUS QUALITY TUBES

Zenith replacement picture tubes and receiving tubes meet the famous quality standards set for Zenith "original" parts—your assurance of the

world's finest performance! Wherever you are located, there's a Zenith Distributor near you, who can supply you quickly on a day-to-day basis.

### ZENITH QUALITY TELEVISION PICTURE TUBES

Complete line of more than 180 top-quality picture tubes . . . color, black-and-white, special purpose. These picture tubes have the same standard of quality that goes into Zenith television sets as original Zenith equipment.



Zenith black-and-white replacement picture tubes are made only from new parts and material except for the envelope which prior to re-use, is inspected to the same standards as a new envelope. In color tubes the screen, aperture mask assembly and envelope are inspected and tested to meet Zenith's high quality standards prior to re-use. All electron guns are new.

### ZENITH QUALITY "ROYALTY CREST" RECEIVING TUBES




Complete line of more than 800 top-quality receiving tubes . . . made to the same quality standards as original equipment in Zenith products! More than 1,500,000 tube hours are accumulated every month by Zenith's life-testing under actual operating conditions. This insures that Zenith "Royalty Crest" tubes have greater reliability which reduces costly call-backs . . . and longer life which increases customer satisfaction!

Check the Yellow Pages for the Zenith Distributor nearest you.  
Or write to Zenith Sales Corporation, Parts & Accessories Division,  
5801 West Dickens Avenue, Chicago, Illinois 60639,  
for Distributor name and information on Zenith quality  
replacement picture tubes and receiving tubes.

Specifications subject to change without notice.

Circle 16 on literature card

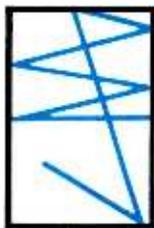

# ACOUSTICS can be measured

Quantitative ways to  
judge room "response".

by Don Davis

The two components of a sound system that normally remain untested are the speaker system and the acoustical properties of the environment. To fully engineer a sound system, the characteristics of the space where it will be used must be considered, and the system adjusted to give the best possible performance in that space. The characteristics of sound in a confined space are called *acoustics*.

## What to Measure

There are four basic conditions that need to be measured and subjected to reasonable control if good listening conditions are to be achieved. These are (1) quietness, (2) proper reverberation, (3) useful and adequate loudness, and (4) proper distribution.

### Quietness

You need to know two things about the noise present: its sound-pressure level (SPL) and its distribution by

frequency. Once these two factors are determined you can make an accurate engineering judgment regarding the potential of the noise for creating interference and the best solutions to apply in each situation.

At the Indianapolis Motor Speedway, a sound level of 125 db was present 85 feet or more from the track as a field of 33 cars raced by the grandstands. The majority of this energy was concentrated below 500 cps. This knowledge allowed us to concentrate our effort at reinforcement to the end of the spectrum where results were possible.

Noise level can vary from impossible, which would require a solution involving the quieting of the noise source itself, to ideal, which allows great freedom in planning a full-range low-distortion music reinforcement system.

### Proper Reverberation

Sounds must "hang on" long enough to allow music to sound natural, and yet not long enough to allow one word to blur the next word during normal speech. It is often desirable to have low frequencies reverberate longer than high frequencies in the same space.

Here again two factors need to be measured: how long it takes sound to decay in the room and how the decay time varies at different frequencies. It is good practice to measure the decay time at each 1/3-octave interval from 50 cps to 10,000 cps.

Reverberation times range from in excess of 18 seconds down to less than .4 second. The 18-second auditorium was accompanied by 38 echoes per sound. It was impossible to communicate prior to the survey, but subsequent improvements—based on the survey information—completely

changed this situation.

### Loudness

Loudness must be adequate and useful if the audience is to hear. A louder sound does not necessarily mean a clearer sound. Echos increase the total amount of sound but often at the expense of intelligibility. Far too many sound systems simply add to the ambient noise level with more-than-adequate but less-than-useful loudness. Failure to achieve useful loudness can be attributed to (1) nonuniform frequency response, (2) high distortion of the signal, (3) improper polar response characteristics, (4) incorrect high- and low-cutoff frequencies, or (5) improper equalization.

The recently developed pulse test measures the ratio of direct sound to reflected sound present at a point. With this test, any location can be measured and rated as to useful and adequate loudness. The test gives a clear picture of the relative amplitudes (in db) and the relative time differences (in milli-seconds). Also it clearly reveals when direct sound has failed to reach the seat or has failed to override ambient noise that is present at this location.

### Proper Distribution

The entire audience needs to hear clearly. Good listening in one seat must not be at the expense of marginal listening elsewhere. The graphic level recorder, random noise generator, and tunable 1/3-octave filter have made it possible to quickly and economically "search" the entire audience area for changes in acoustic level. There is no excuse left for individuals in an audience to discover that their particular seat in an auditorium is located in a "dead spot."



Fig. 1. Sound-level meter with mic.

## Specific Measurements

The basic environmental and system parameters that can be measured during an acoustical survey are:

1. The ambient noise level (in db) of the environment at 1/3-octave intervals from 50 cps to 10,000 cps.
2. The reverberation times of the environment (in number of seconds for 60 db of decay) taken at 1/3 octave intervals from 50 cps to 10,000 cps.
3. The distribution of sound, verified by a complete "level search" of the listening area at 1/3-octave band intervals throughout the spectrum incorporated in the system design.

In addition, the following measurements should be made at each listener's seat:

1. Frequency response.
2. Total harmonic distortion at each octave interval.
3. The relative direct-to-reflected-sound differences of amplitude (in db) and time (in milliseconds).

## Microphones

The basic instrument in any acoustical measuring system is a reliable, accurately calibrated microphone. Unfortunately, no one type of microphone possesses all the desired qualities, so the usual compromise is to use a calibrated ceramic microphone of the type shown on the sound-level meter in Fig. 1. They are more costly than their commercial sound counterparts, but are rugged in regard to temperature variations, moisture, and moderately rough treatment.

The usual measuring chain has as an alternate condenser microphone system for when (1) extended frequency response is needed, (2) high sound-pressure levels are encountered and/or (3) extremely smooth frequency response is required.

## Sound-Level Meter

The sound-level meter into which microphones operate is essentially a very sensitive audio-frequency voltmeter with a calibrated attenuator. It also includes the necessary isolation stages to drive recording devices and



Fig. 2. Band-rejection filter analyzer.

analyzers.

The sound-level meter contains within its own circuits a small amount of analyzing ability in its "weighting networks." The presence of sound pressure primarily low in frequency can be detected by going to the "A" scale and observing a drop in the meter reading.

For example, in a DC-7, the meter reading was over 90 db on the "C" scale. This normally indicates a noise level that would interfere with speech. Passengers had no difficulty conversing, however. On further investigation of the "A" and "B" scale readings, it immediately became apparent that most of the sound pressure indicated on the meter was concentrated at the frequency of the low-pitched throb of the four engines.

The decibel scale is the most convenient for expressing ratios between two sound pressures. Hearing responds logarithmically to stimuli. In measuring work, it is possible to run into SPL changes on the order of ten million ( $10^7$ ) to one. Since the decibel is merely a ratio indication until given a reference, there has been established a standard reference pressure called 0 db which is .0002 dyne per  $cm^2$ .

The inverse-square law states that the strength of a field decreases in proportion to the square of the distance from its source. As applied to acoustics, this means that the reading on a sound-level meter will decrease 6 db when the distance from the source is doubled, or it will increase 6 db when the distance is halved. Reflections especially on indoor systems, can change this considerably, but the foregoing serves as a rough planning guide to avoid inadequate coverage of a widespread audience. If this power of an amplifier driving a speaker is doubled, the sound-level meter will show a 3-db increase. Conversely, if the power is halved, the meter reading will drop 3 db. A knowledge of what to expect in advance, along with some understanding of reasonable readings, leads to a much more intelligent interpretation of the data.

Although the sound-level meter gives an accurate reading in decibels, it does not indicate directly how this pressure is distributed by frequency. For example, an audio oscillator putting out a 1000-tone over a speaker system could be adjusted to give a sound-level meter reading of 80 db. The entire 80 db would be concentrated at 1000 cps. If a random-noise source were substituted for the oscillator and adjusted so the sound-level meter again read 80 db, the amount



Fig. 3. Octave-band noise analyzer.

of 1000-cps energy would be considerably less. The 80 db of energy in the random noise would be distributed over all the frequencies present in the noise source.

## Wave Analyzer

Because few of the noises dealt with in acoustical measuring work are single-frequency in nature, a way is needed to determine how they are distributed over the frequency spectrum. A wave analyzer, connected to the output of the sound-level meter, indicates in detail the frequency distribution of any signal.

The three basic types of wave analyzers are (1) constant bandwidth, (2) band-rejection filter, and (3) constant-percentage bandwidth. Filters for four bandwidths are used with the constant-percentage-bandwidth type of wave analyzer: the octave filter, 1/2-octave filter, 1/3-octave filter, and narrowband (7%) filter.

The band-rejection filter analyzer (Fig. 2) also known as a distortion and noise meter, is the type most commonly seen on the test benches of commercial sound technicians. Although it is used widely to test electronic components for distortion, hum, and noise, it can also measure acoustical distortion.



Fig. 4. Sound and vibration analyzer.

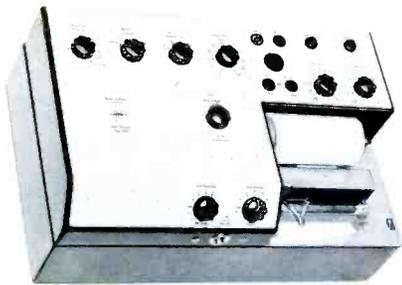


Fig. 5. A graphic level recorder.

The constant-percentage bandwidth analyzers are the most useful of all the types available for acoustical tests and measurements. The least detailed is the octave-band noise analyzer (Fig. 3). The unit shown breaks down the audio spectrum (approximately 20 to 20,000 cps) into 10 contiguous bands.

The most desirable instrument is a sound and vibration analyzer which combines the 1/3-octave band and 1/10-octave (7%) wave analyzer. A typical unit is shown in Fig. 4. In the 1/3-octave mode it provides 41 contiguous bands, and in its 1/10-octave mode, 135 contiguous bands. This instrument is essentially a continuously tunable audio voltmeter of extremely uniform frequency response and high sensitivity.

Once the frequency of a signal is known, the wavelength can be calcu-

lated since the speed of sound in air (at 68°F) is 1127 feet per second. The formula is:  $W=1127$  divided by  $f$ , where  $W$  is the wavelength in feet and  $f$  is the frequency in cps.

By the foregoing formula, the wavelength of a 1000 cps tone is 1.127 ft, 100 cps is 11.27 ft, and 30 cps is 37.56 ft.

### Graphic Level Recorder

Because of the tremendous amount of data desired for a thorough survey and because of the speed required, some form of automatic recorder is highly desirable if accuracy is to be maintained. In the case of reverberation-time measurements, automatic recording is mandatory. Servo-operated AC recording voltmeters suitable for acoustic work are called graphic level recorders. Fig. 5 illustrates one such recorder. A different unit can be mechanically interlinked with either an analyzer or a beat-frequency oscillator (BFO) for completely automatic chart tracing.

Charts are available for recorders to match the spacing of the dial calibrations of the various analyzers and oscillators. Special time-base charts are also available for reverberation-time measurements as well as level searches.

The graphic level recorder can be operated in either a forward or a reverse direction, thus allowing a resonance in a space to be approached from either direction frequencywise. This makes it possible to detect the contribution of a resonance to the readings after the resonance passes its fundamental frequency but before it decays.

### Oscilloscope

Amplitude, frequency, and time can be measured with more than adequate accuracy for acoustical work using the combination of a sound-level meter, a wave analyzer, and a graphic level recorder. With the addition of a calibrated oscilloscope, signal waveforms can be seen that are of too short a duration to be written down accurately by a graphic level recorder.

Such an oscilloscope should be of the x-y input variety, with a sensitivity of 1 mv/cm and sweep times from 5 sec/cm to 1 usec/cm. Both amplitude and time-base calibrations are most useful when they are stepped in a 5, 2, 1 configuration such as 5 sec/cm, 2 sec/cm, 1 sec/cm, .5 sec/cm, .2 sec/cm, .1 sec/cm, etc. A P2 phosphor is the most suitable for general audio and acoustical use, especially for photo-

• Please turn to page 44


**WHY**

**USE 11**

**WHEN**

**5**

**WILL DO IT BETTER?**

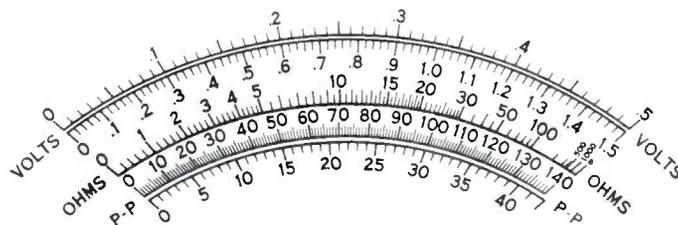

ASK YOUR DISTRIBUTOR ABOUT THE HICKOK CREDIT PLAN

**Hickok**

**The HICKOK Electrical Instrument Company**

10566 Dupont Avenue  
Cleveland, Ohio 44108

Represented in Canada by Stark Electronics, Ajax, Ontario  
Internationally by Hughes International, Culver City, California

Circle 17 on literature card

## Capacitance Analyzer

A handy addition to the test bench is the capacitor tester, of which several types are being manufactured. One type which, instead of measuring power factor for electrolytics, measures effective capacitance is the B & K Model 801 Capacitor Analyst. (Fig. 1).

Tests for shorts, opens, and leakage (except in electrolytics) may be made in circuit. Tests for capacitance value and leakage (for electrolytics) must be made out of circuit; that is, one capacitor lead must be discon-

### B & K Model 801 Specifications

#### Functions:

Tests for shorts, opens, leakage; measures capacitance value.

#### Capacitance Range:

25 pf to 100 mfd for nonelectrolytic, special *effective capacitance* scale for electrolytics. Eight ranges for capacitance measurement.

#### Leakages Ranges:

3 volts and 100 volts.

#### Other Ranges:

One open position, one short position, and one calibrate position.

#### Power Requirements:

117 volts AC, 60 cps, 14 watts.

#### Size (HWD):

5¾" x 12¾" x 7¼"

#### Weight:

8 lb.

#### Price:

\$99.95

nected. The capacitance-value test will measure the value of capacitors from 25 pf to 100 mfd for nonelectrolytics and up to 2000 mfd for electrolytic units. The two leakage ranges (3 volts and 100 volts) assure adequate



Fig. 1. Bridge-type analyst reads effective capacitance for electrolytics.



# Notes on Test Equipment

analysis of test instruments . . . operation . . . applications

by Major Henricks and David I. King

testing for both high-voltage types and low-voltage types (such as those used in transistor radios).

A simplified schematic of the circuit used to measure the effective capacitance of electrolytics is shown in Fig. 2. Without CX (the unknown capacitor), equal currents flow through both legs of the bridge; that is, the current through X1 and R1 is equal to the current through X2 and R2. Since the two diodes (X1 and X2) are alike and resistors R1 and R2 are equal in value, the potential difference between points A and B is zero. When CX is added to the circuit, it will charge through X2 during one half-cycle of the supply voltage. During the next half-cycle, CX appears as an equivalent battery connected in parallel with R2. Some of the charge is lost during the second half-cycle when the diodes are back biased. The amount of discharge depends on the resistance across the capacitor, which is made up of R2 and the leakage resistance of CX. If the capacitor contains a high amount of internal leakage, more of the charge will leak off. The amount of charge left will then appear in series opposing to the new charging half-cycle, and the potential at point B will be lower than normal.

Since a potential difference now exists between points A and B, the meter will indicate a current flow between the two points. Since the amount of potential difference between points A and B depends on the amount of charge that CX will hold, the meter can be calibrated in effective capacitance. If CX contains a high series resistance, the amount of charge will be lower and the meter will read less. If CX contains a high amount of leakage (low leakage resistance) the charge will not hold and the meter will still read less. In both cases the

charging ability is reflected in the meter reading. Since this is the same as actually changing the value of capacitance connected across R2, the meter can be calibrated in microfarads.

For further information circle 130 on literature card

## Wideband DC Scope

As color television becomes more popular, service technicians are becoming familiar with more sophisticated test equipment such as wideband oscilloscopes. To capitalize on the demand for more modern and complex devices, test-equipment manufacturers have recently begun to introduce wideband DC scopes with response characteristics which were originally common only in lab units.

There are many advantages to using a wideband DC scope. Although parallax error on the scope face limits accuracy, a DC scope can be used as a VTVM to determine DC voltage levels; this is particularly advantageous for servicing circuits where both the peak-to-peak waveform voltage and DC voltage level are critical for proper circuit operation. Also, the fact that a wideband scope is useful to signal trace a number of RF and IF circuits without having to use a modulated signal and demodulator probe. The low-frequency response of a DC scope is invaluable for servicing high-quality audio equipment. Too, DC response is sometimes needed to service industrial equipment. As an added advantage, DC coupling eliminates the annoying bounce which occurs when the input probe is attached to a circuit point that is at a DC potential.

The EICO 435 (Fig. 3) is a very portable wideband DC oscilloscope. In fact, it is not much larger or heavier than some VTVM's. Yet this unit seems to be quite sturdy and reliable. Since the top of the chassis is very open, convection cooling dissipates the heat generated by the tubes and resistors. Open, neat construction insures adequate cooling for all parts and prevents hot spots which can cause DC drift and rapid component deterioration. The cabinet is made of lightweight aluminum, and perforations in the top, bottom, and sides provide ventilation.

In a unit like this, space is at a

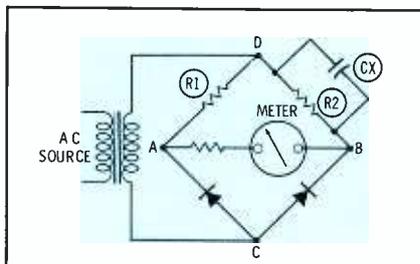


Fig. 2. Simplification of circuit which indicates effective capacitance value.

## EICO Model 435 Specifications

### Vertical Channel:

Sensitivity—Direct terminal, .018 volt rms per cm; response—+1, -3 db from DC to 4.5 mc; input impedance—1 megohm shunted by 35 pf.

### Horizontal Channel:

Sensitivity—Direct terminal, .7 volt rms per cm; response—+1, -3 db from 1 cps to 500 kc; input impedance—cathode follower input, 4 megohms shunted by 40 pf.

### Sweep Generator:

Range—10 cps to 100 kc in four ranges, continuously adjustable. TV horizontal (7875 cps) and vertical (30 cps) test frequencies for fast checks on TV sets. Synchronization—four positions: internal +, internal -, external, and 60 cps.

### Features:

AC-DC signal operation, retrace blanking, internal calibrator, Z-axis input, sawtooth output, edge-lit CRT screen.

### Power Requirements:

117 volts AC, 60 cps 110 watts.

### Size (HWD):

8½" x 5¾" x 15½"

### Weight:

15 lbs

### Price:

\$99.95 kit.

\$149.95 factory assembled.

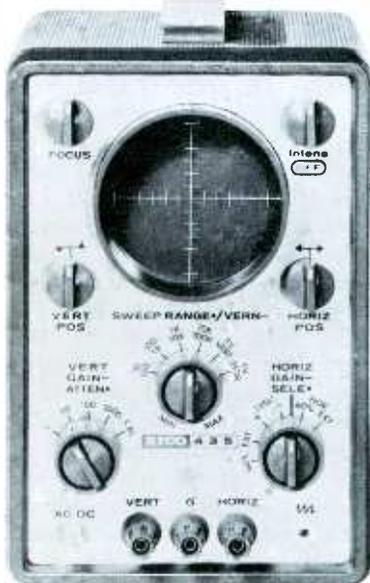


Fig. 3. Operating controls are fully accessible despite small scope size.

premium, but the controls most often used have been placed for easy use. The CRT controls—FOCUS, INTENS, VERT POS, and HORIZ POS—have been equally spaced around the 3" CRT, and a screwdriver adjustment to correct astigmatism is accessible through a hole in the left side of the cabinet. At the bottom left, vertical-amplifier gain is controlled by the concentric VERT GAIN-ATTEN switch and pot; below is an AC-DC switch that allows a choice of vertical amplifier operation. Selection of horizontal function and gain is accomplished with the HORIZ GAIN-SELE control. A sawtooth output from the horizontal cathode follower is available from a tip jack. Directly below the CRT is the SWEEP RANGE/VERN- control. Six range positions, 10-100, 100-1K, 1K-10K, 10K-100K, TV VERT (30 cps), and TV HOR (7875 cps), are included, and the concentric pot provides vernier control of sweep frequency from 10 cps to 100 KC. Across the bottom, 3 combination banana jack/binding posts, VERT, G (ground), and HORIZ, supply inputs for the vertical amplifiers and—depending on the position of the horizontal selector—the horizontal amplifier or external sync. On the back of the cabinet there is a tip jack which connects to the CRT grid for intensity modulation. Below this jack is a rheostat to control illumination of the edge-lit plexiglass CRT screen.

The block diagram in Fig. 4 can be divided into three main divisions: the vertical amplifier, the horizontal sweep generator, and the horizontal amplifier.

Vertical amplifier input is fed through the frequency-compensated vertical attenuator to the grid of V1A (Fig 5). Note the similarity of this circuit to a cathode-coupled paraphase amplifier. However the outputs of this circuit—although they are 180° out of phase—are not of equal amplitude. With R5 set for maximum resistance, there is very little signal output from V2's plate. As R5's resistance is decreased, the signal output from V2A increases until with

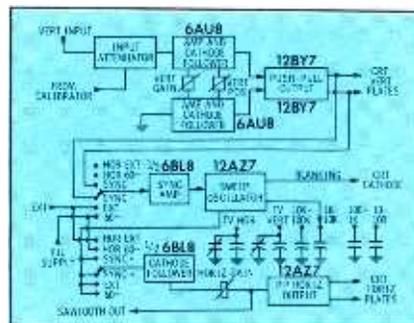


Fig. 4. Block diagram shows reliable design based upon simple circuitry.

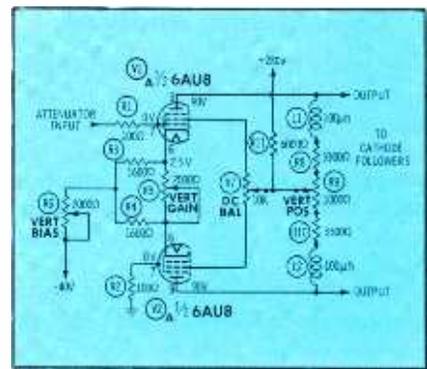


Fig. 5. Amplifier balances DC drift and rejects common-mode interference.


minimum resistance between the cathodes of V1A and V2A, the output on V2A is 80% of that from V1A. The output from V1A also increases as R5's resistance decreases because R4 then parallels R3, thus decreasing degeneration. Since V2A's grid is grounded, only the signal of V1A's grid will unbalance this circuit. V1A and V2A form a differential amplifier which rejects common-mode signals such as noise, hum, and DC drift caused by power-supply variations.

The outputs of V1A and V2A are fed to cathode followers V1B and V2B respectively; this simplifies DC coupling and extends high-frequency response by presenting low impedance inputs to the push-pull output stage. Because the cathodes of the two



FOR ONLY \$1.49 DEALER NET  
LESS BATTERIES

BATTERY OPERATED  
TESTS WITH POWER OFF

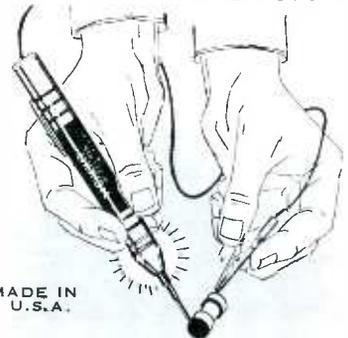

MADE IN U.S.A.

- CONTINUITY • FUSES • SWITCHES
- CHIMES • APPLIANCES • MOTORS
- BUZZERS • PUSH BUTTONS
- AUTO IGNITION and VOLTAGE REGULATORS, ETC.

ASK YOUR ELECTRONIC PARTS DISTRIBUTOR FOR

MODEL NO. BZ5

WORKMAN Electronic PRODUCTS INC.  
SARASOTA FLORIDA

Circle 19 on literature card

# GET IN ON THE **COLOR TV BOOM!**

EARN BIG SERVICING PROFITS *with the know-how you get in*

# PHOTOFACT® COLOR TV COVERAGE

## PHOTOFACT COLOR TV COVERAGE AVAILABLE ON FOLLOWING BRANDS:

ADMIRAL	MOTOROLA
AIRLINE	MUNTZ
AMC	OLYMPIC
ANDREA	PACKARD-BELL
ARVIN	PENNCREST
BRADFORD	PHILCO
CAPEHART	RAYTHEON
CATALINA	RCA VICTOR
CBS-COLUMBIA	SEARS
CORONADO	SENTINEL
CURTIS MATHES	SETCHELL-CARLSON
DELMONICO	SILVERTONE
DUMONT	SPARTON
ELECTROHOME	STROMBERG-CARLSON
EMERSON	SYLVANIA
GENERAL ELECTRIC	TRUETONE
HOFFMAN	WESTINGHOUSE
MAGNAVOX	ZENITH

FOR PHOTOFACT FOLDER COVERAGE OF SPECIFIC CHASSIS MODELS in the above brands, check your Photofact Master Index and latest Supplement.

An average of 3 Color TV chassis is now covered monthly in current PHOTOFACT



## HAVE EVERYTHING YOU NEED TO PERFORM EXPERT PROFITABLE COLOR TV SERVICING!

- Famous SAMS "Standard Notation" Detailed Schematics
- Chassis View Photos
- Disassembly Instructions
- Set-up Adjustments
- Full Alignment Data
- Resistance Charts
- Tuner Schematics
- Block Diagrams
- Waveform Diagrams
- Tube Placement Charts
- Complete Parts Lists

Plus dozens of other invaluable PHOTOFACT features

FOR THE COLOR TV COVERAGE YOU NEED, check your latest PHOTOFACT Master Index—the issue dated February, 1965 includes a special section listing all Color TV makes and models now covered in PHOTOFACT—so you can instantly locate the Color TV PHOTOFACT Folder you want.

See your Sams Distributor—he stocks all PHOTOFACT Sets to fill your requirements immediately.

## NOW MORE THAN EVER—PHOTOFACT OWNERSHIP PAYS OFF BIG!

### OWN A PHOTOFACT LIBRARY THE EASY-BUY WAY

Only \$10 down • 30 months to pay • No interest or carrying charges • Prepaid transportation • Add-on privilege of a year's advance subscription to current PHOTOFACT on the same Easy-Buy contract • Save 30¢ per Set—special \$1.95 price applies on Easy-Buy (instead of the regular \$2.25 price).



Deluxe new 4-drawer File Cabinet (full-drawer suspension)—available with your purchase of a PHOTOFACT LIBRARY consisting of 200 Sets (plus a selection of valuable Free extras!).

SEE YOUR SAMS DISTRIBUTOR FOR FULL DETAILS, OR MAIL COUPON

4 Ways to Select Your PHOTOFACT Library: 1. Complete your present Library. 2. Order a "Starter" Library. 3. Order by brand name and year. 4. Order a complete Library. See your Sams Distributor for full details, or send coupon below.

### HOWARD W. SAMS & CO., INC.

Howard W. Sams & Co., Inc. Dept. PFF-8  
4300 W. 62nd St., Indianapolis, Ind. 46206

- Send FREE Photofact Cumulative Index.  
 Send full details on Easy-Buy Plan.

My Distributor is: \_\_\_\_\_  
Shop Name \_\_\_\_\_  
Attn. \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

## PRECISION TUNER SERVICE

P. O. BOX 272

1210 S. WALNUT ST.

BLOOMINGTON, IND.

EDISON 99653

# 7.95

V or U

COMBO PLUS  
9.95 POSTAGE

6 MONTH WARRANTY



All Types T.V. Tuners Cleaned, Repaired and Aligned to Factory Specifications. Same day in shop service on most Tuners. Price Includes Minor Parts, Major Parts at Cost Price. We use Original Parts if possible. State Make Model and Enclose all Parts and Tubes. Pack Well and Insure.

ALSO HAVE LARGE STOCK OF EXCHANGE TUNERS, WRITE FOR TYPES AND PRICES.

Circle 21 on literature card

Choose the  
**RIGHT** wrench for your job...

Tools by


**CHAN NEL LOCK**

When You Buy CHANNELLOCK Adjustable Wrenches you buy the finest—at no extra cost. CHANNELLOCK wrenches are drop forged of special analysis steel . . . heat treated for maximum toughness and proper hardness of working surfaces . . . chrome plated . . . built to last. Available also with blue dipped plastic cushion grip handles. Specify CHANNELLOCK adjustable wrenches . . . you'll be glad you did.

**CHANNELLOCK, INC.** Meadville, Pennsylvania

Formerly Champion DeArment Tool Co.

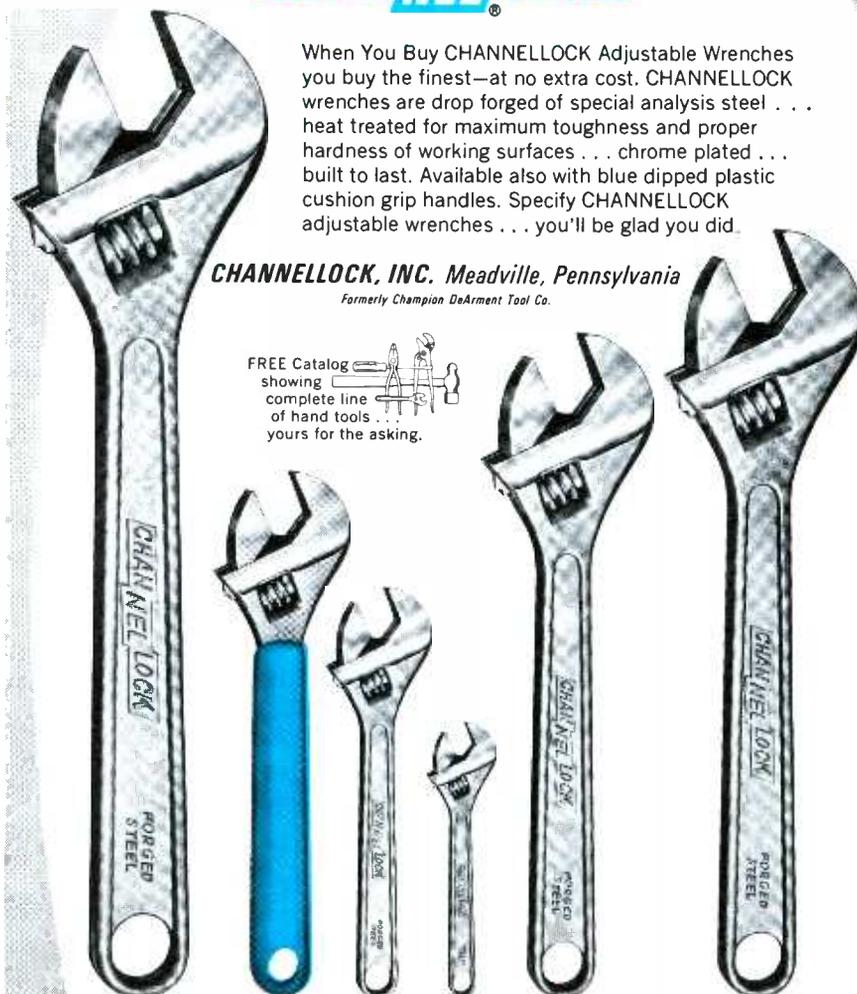FREE Catalog showing complete line of hand tools . . . yours for the asking.



Circle 20 on literature card

12BY7 output tubes are connected and a relatively large cathode resistor is used, the output stage functions as a paraphrase amplifier and feeds a push-pull signal to the CRT vertical-deflection plates. Common-mode signals arriving at the grids are of equal amplitude and in phase; hence, they are cancelled.

Despite its simplicity, the 12AZ7 cathode-coupled sweep multivibrator produces a linear sweep throughout its range. Also, retrace time is very short; using our lab scope we found that retrace time ranges from 400  $\mu$ s at 10 cps sweep rate to 1  $\mu$ s at 100 kc. A biased diode and coupling capacitor are used to select and feed the proper blanking voltage to the CRT cathode. The 6BL8 pentode section is used as a limiter amplifier to trigger the sweep oscillator.

Horizontal amplifier design is quite straightforward. The 6BL8 triode section is used as a cathode follower; its output is coupled by a 50-mfd capacitor to the horizontal output amp and the sawtooth-output jack. One 12AZ7 is connected as a paraphrase amplifier to develop push-pull output voltages for the horizontal-deflection plates of the CRT.

Both +360 and -40 volts are fed from the low-voltage power supply to allow DC operation of the vertical amplifier; the circuit uses an EX81 full-wave rectifier. A source of -1600 volts for the CRT cathode is produced by the high-voltage power supply which uses a 1V2 half-wave rectifier. AC from the power transformer is fed through a 150K dropping resistor to a 1N713 zener diode; a divider across the diode provides a 200 mv peak-to-peak square wave for calibration.

We connected our laboratory square-wave generator to the 435 and ran it over its entire range; the square waves displayed by the 435 showed little droop or overshoot. At 1 mc, the highest frequency available from our generator, the scope still could sync with no visible jitter or pulling. Using internal sync the scope will lock on with less than 1 cm peak-to-peak pulse displayed. Square-wave tests also showed that with AC operation low-frequency droop did not exceed 10% until the square-wave frequency went below 10 cps. We also displayed the output of a 5.35 mc marker generator; although it took 1.5 cm display for internal sync, the waveform was clear with little pulling.

Where a very portable scope which offers the advantages of wideband DC operation is required, the EICO 435 will do the job. ▲

For further information, circle 131 on literature card.

# Have you tried new **QUIG**<sup>®</sup> connectors?




**Not just another wire spring connector!**  
The 3-in-1 QUIG is brand new and different . . . Copperweld wire inner core, a layer of flux, and an outer jacket of solder . . . all you need is heat!  
**Makes one-handed soldering possible!**

Once again, Sprague helps the TV-radio service industry by solving two increasingly serious problems . . . parts replacement in those "inaccessible" chassis nooks, such as crowded tube sockets, as well as soldering onto the delicate circuitry of printed wiring boards.

Mechanically sturdy and electrically reliable, the revolutionary QUIG provides fast, expertly-soldered connections as easy as A-B-C!



Ten times actual size

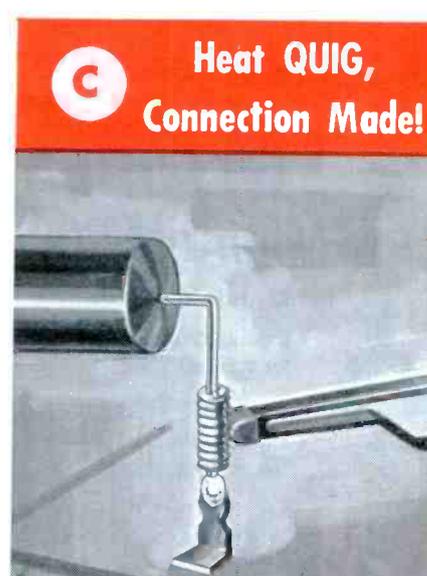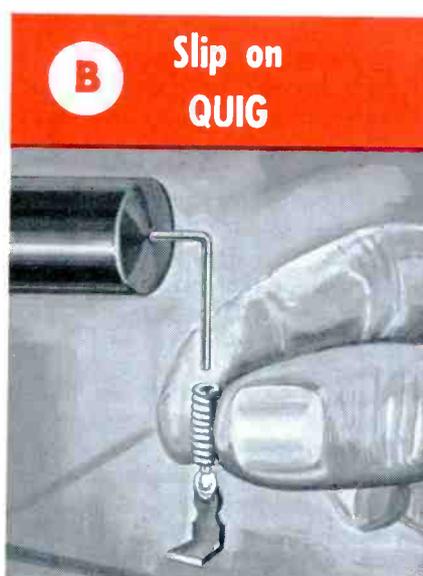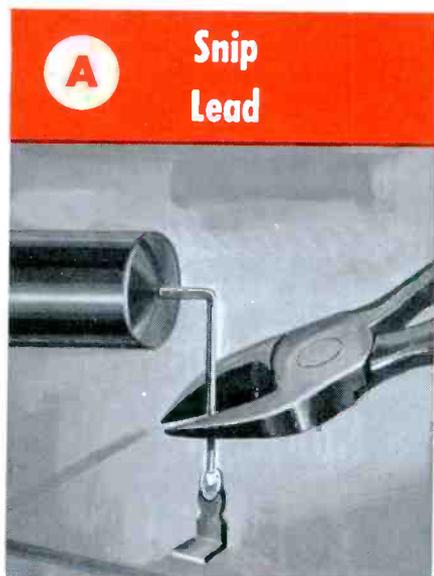

**NOBODY ELSE HAS QUIG CONNECTORS...  
YOU GET 'EM ONLY FROM SPRAGUE PRODUCTS!**

QUIGS are now being packed with Sprague Atom<sup>®</sup> Capacitors *at no extra cost to you!* Whenever you need tubular electrolytics, insist on pre-packaged Sprague Atoms from your parts distributor and you'll automatically get your QUIG component connectors . . . the biggest boon to the service technician since the soldering gun!



WORLD'S LARGEST MANUFACTURER OF CAPACITORS

85-4104

Circle 22 on literature card

August, 1965/PF REPORTER 43

Our CB story this month  
is short and sweet:



the  
beauty of  
this baby  
is its  
18" length!

## M-130

### "Mighty Mite"

18" Mobile CB antenna

- Capacity-matched to car body for excellent VSWR
- Fine-tuning adjustment
- Professional-type, 2½" stainless steel shock spring



#### M-130 "Mighty Mite"

¾" snap-in mount—  
no soldering



#### M-131 "Maggie Mite"

Gutter clip mount—  
hang it anywhere

the  
antenna  
specialists co.



12435 Euclid Ave., Cleveland, Ohio 44106  
A division of A/S Industries, Inc.

Export Div.:  
64-14 Woodside Ave.,  
Woodside 77, N.Y.

"stripes of quality" ©



Circle 23 on literature card

## Acoustics

(Continued from page 36)

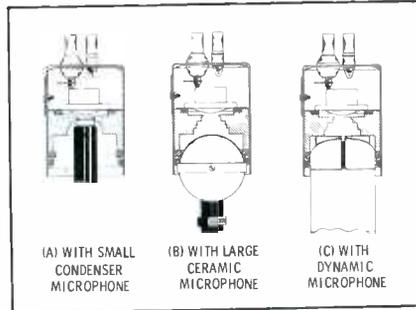


Fig. 6. One type sound-level calibrator.

graphic purposes. The oscilloscope must have a variable trigger with an adjustable threshold for amplitude sensitivity. An illuminated graticule is required which has a minimum viewing area of 8 x 10 cm, calibrated vertically and horizontally with five minor divisions per centimeter.

### Sound-Level Calibrator


In order to calibrate the entire chain of instruments some form of reliable and accurate acoustical signal is required. Fig. 6 shows one type of sound-level calibrator and its accompanying audio source.

Once a chain of acoustical measuring instruments has been set up, a known acoustical signal must be applied to bring all readings into agreement. The calibrator applies such a signal to the microphone of the sound-level meter so that the latter can be calibrated. This signal also appears at the output of the meter and can be used to calibrate the wave analyzer, graphic level recorder, oscilloscope, and tape recorder.

Microphone sensitivity is usually checked with a 120-db signal at 400 cps. (Data are supplied with the calibrator so that a wide range of frequencies at reduced levels can be used for calibration.) However, a microphone can usually be considered functioning properly if it sounds normal when listened to and meets its sensitivity figure of 400 cps. The sound-level calibrator can be used with microphones varying in size and shape.
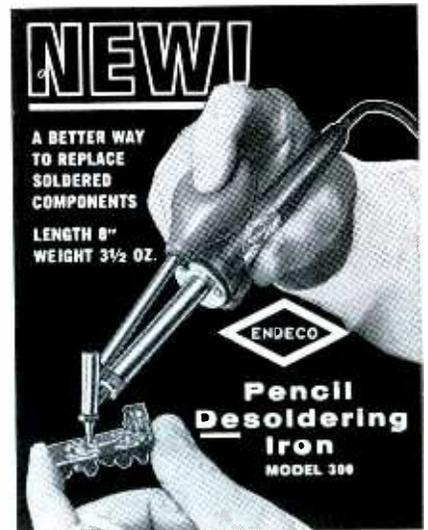
### Conclusion

Other, more specialized acoustical-measuring instruments are available to the sound technician. Special techniques, notably the time-pulse system, offer more acoustical information than ever before. When you're faced with a tough audience-coverage problem, therefore, don't hesitate to put these instruments and techniques to work for you. The result will be a truly professional job. ▲



Now—remove miniature soldered components in seconds—without damage

Hollow tip fits over connection; vacuums all solder for easy removal of component. Leaves terminals and mounting holes clean. Then, with 360° contact, it resolders even faster and better than regular irons. Handles miniature and standard components in printed circuit boards and conventional wiring. Self-cleaning. All parts replaceable. 40 watts, 115-v. 5 tip sizes. Pays for itself in time saved. \$9.95 net East of the Rockies.

Larger model available. See your distributor or write:

ENTERPRISE DEVELOPMENT CORPORATION  
1102 E. 52nd • INDIANAPOLIS, IND. 46205  
IN CANADA: A. C. Simonds & Sons, Ltd. 100  
Merton St., Toronto 7, Canada.  
Circle 18 on literature card

Every No-Noise Aerosol Product  
*Guaranteed*  
Non-Flammable  
Non-Toxic and  
Won't Affect Plastics

"NO NOISE"

PROVED BEST  
FOR COLOR TV

VOLUME CONTROL  
& CONTACT RESTORER

"TUNER-TONIC" WITH PERMA-FILM

EC-44 for all electrical contacts

FREE 5" plastic extender push-button assembly for pin-point application with all No-Noise products.

ELECTRONIC CHEMICAL CORP.  
813 Communipaw Avenue, Jersey City 4, N. J.

Circle 24 on literature card

# NOW! OVER 2700 REPLACEMENTS

with only 13 RCA Top-of-the-Line transistors

With RCA's "Top-of-the-Line" SK Replacement Series, you need only 13 transistors, including two matched pairs for ready replacement of more than 2700 types. In addition, RCA's two new SK-Series rectifiers—the SK3016 and SK3017—enable you to replace virtually any selenium or silicon rectifiers having comparable ratings.

Stock the complete SK-Series—13 transistors and 2 rectifiers. They will provide the answer to many of the replacement problems you face servicing auto radios, battery-operated portable radios, tape recorders, hi-fi equipment, phonographs, black and white and color TV, and other entertainment-type equipment using solid-state devices.

Accurate, comprehensive replacement information is given in the new 16-page RCA "Top-of-the-Line" Semiconductor Replacement Guide SPG-202. With it you have at your fingertips information on more than 2700 transistor types, including many of foreign manufacture—which the 13 RCA "Top-of-the-Line" types replace.

See your RCA Distributor about the RCA SK-Series, and be sure to ask for your copy of the RCA Semiconductor Replacement Guide.

RCA ELECTRONIC COMPONENTS AND DEVICES, HARRISON, N. J.



The Most Trusted Name in Electronics

## "Top-of-the-Line Replacement Transistors"

SK-3003	pn-p type, AF Driver and Output Stages (9 V Supply)	SK-3010	npn type, AF Driver and Output Stages of Broadcast Receivers
SK-3004	pn-p type, AF Driver and Output Stages (15 V Supply)	SK-3011	npn type, RF, IF, and Converter Stages of Broadcast Receivers
SK-3005	pn-p type, RF, IF, and Converter Stages of Broadcast Receivers	SK-3012	pn-p type, Audio Output Stages of Auto Radios
SK-3006	pn-p type, RF, IF, and Converter Stages of FM and AM/FM Receivers	SK-3013	Matched pair of SK-3009
SK-3007	pn-p type, RF, IF, and Converter Stages of All-Wave Receivers	SK-3014	Drift Field type for Output and Driver Stages of Hi-Fi equipment
SK-3008	pn-p type, RF, IF, and Converter Stages of Auto Radios	SK-3015	Matched pair of SK-3014
SK-3009	pn-p type, Audio Output Stages of Auto Radios	SK-3016	Silicon Rectifier for color, B/W TV, Radios, Phonographs
		SK-3017	Silicon Rectifier for color, B/W TV, Radios, Phonographs



Circle 53 on literature card

## Money in Rentals

(Continued from page 25)

At many outdoor events, 100-milliwatt transceivers (operating on CB frequencies) are useful adjuncts to outdoor events. At a bicycle race, for instance, the sponsoring organization could station spotters at strategic places around the track, and these spotters could then report the happenings back to the location of the PA microphone. Transceivers are also useful in wiring buildings; it then isn't necessary to tie up a telephone or string your own communication lines.

If you are going into sound and PA work, it would be worth your while to make arrangements with some manufacturers so that you can use and sell their amplifiers, speakers, etc. It's a good idea to have a display of their products in your shop, preferably one that can be demonstrated upon demand. Some shops try to buy one of each new item that hits the market.

### Fees


Naturally, your charges will depend on the amount of equipment used, how long it is used, and

whether or not you must furnish a technician to operate it. Your charges must be adequate to cover paying the technician, the use of the truck to deliver and pick up the gear, and the cost of purchase and maintenance of the equipment. You will also want insurance—liability insurance to protect yourself from a lawsuit resulting from an accident caused by your company, and some form of protective insurance to protect yourself against loss of equipment installed on the client's premises.

### Conclusion

Whether or not you should expand your present business to include an audio rental, lease, and sales department depends on many things. First of all, is there a demand for such services in your particular location? Secondly, do you have or can you hire a serviceman qualified to install and repair this equipment? If the answer to both of these questions is yes, your bank account can rise considerably from the income of this new venture. ▲

**a lot of good dealers here ...**

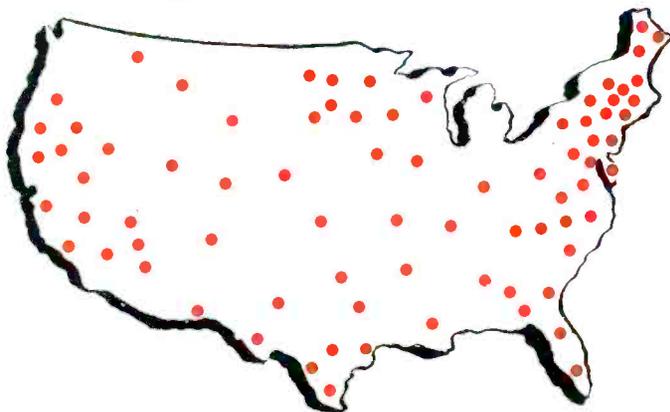

**but room for lots more**

Be an authorized  
e.c.i. dealer  
with the most  
profitable  
CB & BB 2-way  
radio line in the  
country!

### CAN YOU QUALIFY?

- Do you have a sound knowledge of radio and/or communications equipment?
- Have you the desire to install and service this unique equipment?
- Do you have an established business reputation? Good credit rating?
- Have you a real interest in dynamic new products?
- Do you want to make really big profits?

**MANY PRIME AREAS STILL OPEN . . .  
WRITE TODAY FOR FULL DETAILS!**

Name .....

Address .....

City ..... State .....

 **electronics communications, inc.**  
dept. PF 8, 56 hamilton ave., white plains, n. y.

Circle 25 on literature card



**RESTORES  
LINE "LOSS"  
FOR  
GREATER  
FREEDOM  
IN  
TAPING**

### SWITCHCRAFT

## "MIX-AMP"

MINIATURE TRANSISTORIZED  
LINE AMPLIFIER

Tied to short mike cables? Losing high frequencies? Insufficient signal when using a resistance-type mixer? Forget 'em . . . substitute gain for loss with a cigarette-pack size MIX-AMP. Up to 30 db gain with a 600 ohm mike—compensates for cable runs of 30 feet! Often used in place of line transformers. Overcomes usual "losses" from resistance mixers and provides 3 db output gain. 9V battery powers it. 20-20,000 cps. Virtually zero hum and noise.

write for Catalog A-401

**SWITCHCRAFT**  
INC.

5573 N. Elston Ave., Chicago, Illinois 60630

Circle 26 on literature card

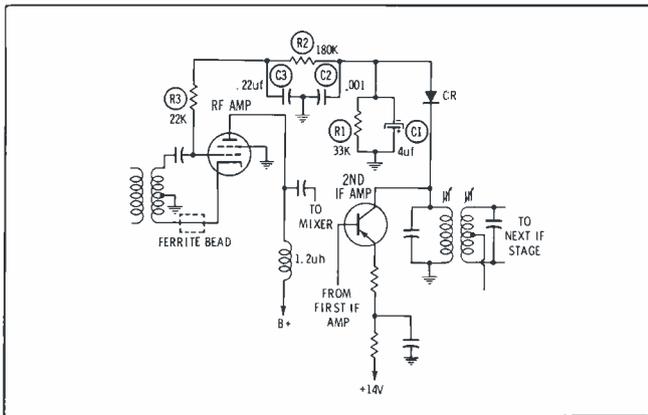


Fig. 7. RF amplifier is AGC controlled by signal from IF.

The filter consisting of C11, C12, C18, and T3 attenuates the 67-kc SCA signal to prevent interference when it is present on the carrier.

Hybrid Receivers

Most hybrid sets also are designed for operation from a 115-volt AC source. One winding on the power transformer furnishes 6.3 volts AC for the heaters of the three tubes and the dial lights. Other windings and their associated rectifiers supply regulated DC at up to -34 volts, unregulated DC at -36 volts and +36 volts, and +152 volts DC (for the plates of the tubes used in the front end). The FM tuner section, which employs all the tubes used in this receiver, is shown in Fig. 6.

AGC voltage for the RF amplifier tubes is obtained by rectifying the IF signal at the collector of the second IF amplifier transistor as shown in the simplified diagram, Fig. 7. The collector is at DC ground potential except for the small DC voltage drop in the primary of the IF transformer. The IF signal present here causes a DC voltage to be developed across R1 and C1. This voltage is then fed through an RC filter and isolating resistor R3 to the control grid of the RF amplifier tetrode. The amount of applied DC voltage is proportional to IF signal level, and its variations are delayed by C1—a 4-mfd capacitor.

The multiplex circuit, shown in Fig. 8, employs six transistors, two independent diodes, and a packaged ring demodulator (CR403) containing four diodes. There are two separate audio control amplifiers, one for each stereo channel.

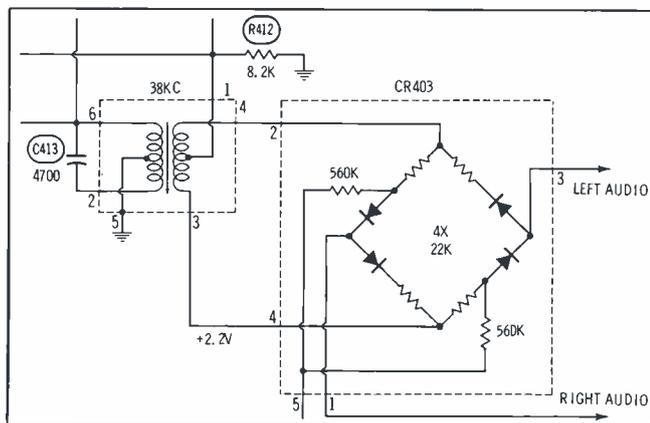


Fig. 8. Signal is detected by packaged-ring demodulator.

a new money-making,  
traffic-building tube tester

for you or your customer!



THE ALL NEW SENCORE TC131  
SEMI-AUTOMATIC TUBE CHECKER

After thousands of requests here is the "counter/bench" version of the famous Sencore Mighty Mite Tester; designed for the ultimate in tube checking thoroughness and operational simplicity! Designed for two-way use — as a professional shop tester and customer self-service unit. Tests over 2500 tubes — including Nuvistors, Compactrons, 10-pins, Novars, Magnovals and foreign tubes with a big 6-inch meter for easy reading. Semi-automatic; simply turn function control to any test and watch lighted arrow on meter automatically stop on right scale. User can't go wrong — no guess work — everything is read right on the meter (no tricky neon lights to misread); only 3 set-up controls. Easy to read, speed-indexed set-up cards make every test fast and sure. Like the famous Mighty Mite, the TC131 uses 100-megohm grid leakage sensitivity to spot those "tricky" tubes other testers miss; tests inter-element shorts and makes cathode emission tests under full operating levels. A real profit maker as a counter checker or self service tube seller in your shop . . . and it's only

\$129<sup>95</sup>

See your distributor about the big TC131 trade-in deal.


professional quality — that's the difference!

SENCORE

426 SOUTH WESTGATE DRIVE • ADDISON, ILLINOIS  
Circle 27 on literature card

**There's a tool right here  
for any soldering need.  
And you know it's best  
because it's from**

**Weller®**

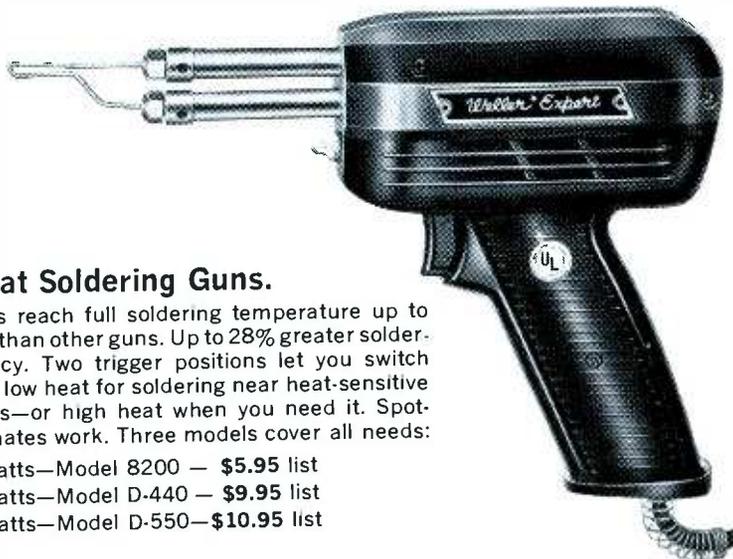

### Dual Heat Soldering Guns.

Weller guns reach full soldering temperature up to 40% faster than other guns. Up to 28% greater soldering efficiency. Two trigger positions let you switch instantly to low heat for soldering near heat-sensitive components—or high heat when you need it. Spotlight illuminates work. Three models cover all needs:

- 100/140 watts—Model 8200 — \$5.95 list
- 145/210 watts—Model D-440 — \$9.95 list
- 240/325 watts—Model D-550—\$10.95 list



### “Pencil” Soldering Iron. Small, lightweight, efficient.

A 25-watt, 115 volt iron that weighs only 1¾ ounces. Yet it does the work of irons that weigh twice as much and have much higher wattage. You can hold and maneuver it as easily as a pencil. Recovers heat rapidly. Maximum tip temperature 860°F. With ¼" screwdriver tip and cord. Model W-PS—\$5.20 list.



### Temperature-Controlled Low-Voltage Soldering Pencil.

New! For universal soldering including heavy-duty chassis work. Temperature control is in the tip. Interchangeable tips give a choice of 500°F, 600°F, 700°F and 800°F controlled temperatures. Operates on 24 volts. Small, lightweight, highly efficient. Complete with ⅜" 700°F tip and 60 watt, 120 volt, 50/60 cycle power unit which has stand for soldering pencil attached. Model W-TCP—\$26.00 list.

**AT YOUR ELECTRONIC PARTS DISTRIBUTOR  
WELLER ELECTRIC CORP., EASTON, PA.**

In Canada: Weller Electric Corp., 121 Counter Street, Kingston, Ontario

**WORLD LEADER IN SOLDERING TECHNOLOGY**

Circle 27 on literature card

The two stereo units described here typify the basic concepts used by equipment designers. One set uses diodes and transistors throughout, the other uses tubes, but only in the VHF circuits in the front end. In both, very little heat is generated compared to all-tube designs.

### Servicing Solid-State

Servicing solid state stereo is not much different from servicing tube-type equipment, except that the voltages are lower. To service FM/MPX stereo, a sweep generator and an oscilloscope are required for aligning the IF stages. A VOM and a VTVM are required for measuring DC and signal voltages, and an FM/MPX stereo signal generator is required for adjusting and checking the multiplex circuit. An in-circuit transistor checker facilitates testing of transistors without having to remove them from their circuits. Some receivers employ wired-in transistors; others use plug-in types.

In addition to complete receivers (tuner-amplifiers), separate solid-state stereo amplifiers are also available. Most FM/MPX stereo equipment is available in factory-wired form. However, some manufacturers offer kits and wired equipment.

### Antennas

Along with increased business for the service shop because of the growing number of transistor stereo sets, there will be a sharp rise in FM antenna sales. While the better stereo sets are unusually sensitive, a good antenna system will provide more satisfactory performance. Full limiting is required for stereo reproduction. A good antenna system provides a strong signal at the tuner input and minimizes distortion that might otherwise be caused by multipath propagation.

### Conclusion

We have given you a brief description of what's inside solid-state stereo receivers. Let's face it, solid-state receivers are here to stay! If you aren't prepared to service these units, you'll be missing an abundance of added work. The serviceman who can repair transistor sets is the one who is going to be in business longer and make more money. ▲

## Keep it Clean

(Continued from page 30)

entirely on that track. A badly worn head requires cleaning more often than a new one; Fig. 2 shows what happens when grime accumulates on a head that has a groove worn in it. The dirt pushes the tape out of the groove, and any slight vertical drift moves it away from the pole piece.

Pressure pads on tape heads soon accumulate dirt and harden. Stiff pads cannot hold the tape to the contour of the head. Dirty guide-posts increase the friction during winding and rewinding. In some cases the increased drag may stall the machine.

Clean the tape heads with wood alcohol; don't use stronger solvents, because they may damage spacers or other plastic parts in the face of the head. Use acetone to remove hard deposits of dirt from tape filters and guideposts. It may be necessary to use a small brush to get all the dirt out. Be careful not to splatter the acetone on plastic or painted surfaces. Stiff pressure pads should be replaced, but if none are available soak the pad in acetone and carbon tet. Reglue the pad with plastic cement, and position it so that the tape is pressed squarely against the head. Clean the pinch roller with wood alcohol to remove oxide particles. If the roller is glazed, wipe it with benzene to restore the surface. Remove all traces of rubber from the capstan with carbon tet.

## Finishing the Job

When a customer picks up his tape recorder or recorder player at your shop, the outside appearance of the machine counts more than all the careful craftsmanship that went into the repair job. Clean knobs and polished plastic trim plates stand out and are likely to be remembered when the machine needs service again.

Clean the imitation leather or plastic fabric covering with a small amount of liquid detergent on a damp rag. Use a brush dipped in soapy water to get dirt out of grooves in knobs and trim plates. Paper-covered cases must be cleaned with care; rubbing too hard may remove the pattern. Plastic faces over tape-counter dials are cleaned with a soft rag. Magic-eye tubes grow dim after long periods of use; replacing them adds a bit of sparkle to the job. Clean number drums on tape-footage counters with a cotton swab dipped in soapy water; don't rub too hard or the paint will come off the numbers. As a final touch, clean the line cord and wind it up neatly.

Attention to these final details is important. Because phonos and tape recorders require regular service, part of the job is making sure the customer returns to you the next time he needs work done. ▲



at last...  
instant color patterns  
at your finger tips...  
zero warm-up time



## THE ALL NEW SENCORE CG135 DELUXE TRANSISTORIZED COLOR GENERATOR

The big push is on in Color TV. Equip yourself now with the new, solid state Sencore CG135 and cash in on the zooming volume of new service business as Color-TV booms! Instant, service-ready RCA standard color bars, cross-hatch, white dots and individual vertical and horizontal bars enable you to set up or trouble-shoot more Color TV sets per day; earn top money in this fast growing service field. It's an analyzer too: Color gun interruptors, unmodulated video for chroma circuit trouble isolation and unmodulated sync pulses to keep Zenith receivers in sync for this test, make color trouble shooting a snap. Sturdy all-steel construction for rugged, heavy duty in the field or shop. Another Best Buy in profit-building service instruments from Sencore at **\$149<sup>95</sup>**

COMPARE THESE FEATURES: SEE WHY THE CG135 IS IN A CLASS BY ITSELF

- Solid state construction employs high priced GE "Unijunctions" to develop six "jump out proof counters" that guarantee stable patterns at all times with no warm-up
- Standard RCA licensed patterns as shown on schematics throughout the industry
- Handy universal color gun interruptors on front panel
- Lead piercing clips insure non-obsolescence
- CRT adaptors optional
- Crystal-Controlled 4.5mc Sound Carrier Analyzing Signal to insure correct setting of fine tuning control
- RF output on Channel 4 adjustable to Channel 3 or 5 from front of generator when Channel 4 is being used
- No batteries to run down; uses 115 V AC
- Less than one foot square, weighs only 8 lbs.

professional quality — that's the difference!


# SENCORE

426 SOUTH WESTGATE DRIVE • ADDISON, ILLINOIS

Circle 29 on literature card

August, 1965/PF REPORTER 49

by Paul Norman

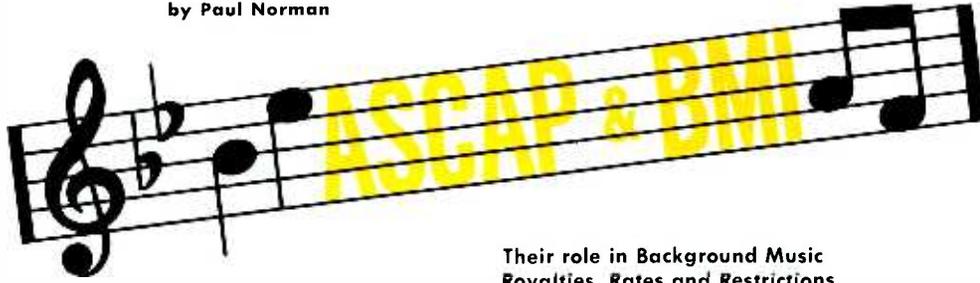

### Their role in Background Music Royalties, Rates and Restrictions.

Songwriters write songs to make a living. Obviously, if you want a copy of the sheet music of a song, or a recording of that song, you must pay for it; part of the purchase price goes to the writer of the song. If you use the sheet music or the recording only for your personal enjoyment or that of your friends, no one minds—this is the purpose for which you've made your purchase. But suppose you decide to hire a band and have them play the music, or set up a phonograph and play the recording, and then charge admission so that the public may enjoy the music for a price. Under the U.S. copyright law, you must pay the composer a fee for this additional use. Why? Because you are using his music to make a profit.

As a matter of fact, a series of court decisions has established that it makes no difference whether the public must pay admission or not and it doesn't matter whether the music is played by a live orchestra or reproduced by means of recordings, radio, or television. If the music is furnished by the operator of a commercial establishment (a restaurant or store, for instance) for the enjoyment of his customers, who pay him money for his goods and or services, then that operator is said to be using the copyrighted material for profit. He owes the songwriter a fee. It makes no difference that the music may be incidental, as in the case of background music; obviously, the presence of music enhances the attractiveness of the restaurant or makes working conditions more pleasant for factory or office employees—or else the management wouldn't spend money to install the equipment and lease the music service. The music is being performed for profit, and the courts have held that the user must pay the composer. (There is an exception for jukeboxes, but that doesn't concern us here.)

#### Music Licensing

There are several thousand songwriters in the U.S. alone. There are also several hundred thousand commercial establishments which use music to entertain their patrons. Obviously, it would be impossible for each composer to deal directly with each restaurant, night club, factory, and other place that might use his music. To perform this task, music-licensing organizations have been formed. In 1914, composer Victor Herbert found to his dismay that a restaurant in New York City was using his music to entertain its

patrons without paying him. As a result of the lawsuit which he pressed, a ruling was obtained which bestowed the songwriter's right to a performance fee. Herbert was then faced with the problem of licensing such performance, and he joined with others to form ASCAP, the American Society of Composers, Authors, and Publishers.

During the 1940's, there was a dispute between ASCAP and the radio broadcasting industry, and ASCAP refused to license stations to broadcast their music. Broadcasters then formed their own licensing organization, Broadcast Music, Inc., more commonly known as BMI. The dispute has long since been settled, and since that time both organizations issue licenses to radio and TV stations, as well as nearly all other establishments which perform music for profit. There are, of course, other groups which represent copyright holders, but ASCAP and BMI handle the bulk of the U.S. industry.

When songwriters affiliate with ASCAP or BMI, they simply authorize the particular agency to represent them in licensing or franchising commercial establishments to perform their music publicly for profit. While there are exceptions, in nearly all cases the restaurant, broadcaster, or background-music supplier obtains a *blanket license* from the society. This entitles the operator to perform any or all of the society's music which is *cleared*, that is, for which the composer has granted performance permission. (Sometimes the composer of a Broadway musical or TV show will withhold permission until his show has opened, fearing premature exposure will destroy his music's freshness.)

If you use music without paying a fee and without a license, you are infringing the copyright. You are liable to a lawsuit and, if found guilty in court, you may be fined \$250 for each unauthorized performance.

#### How Licensing is Accomplished

Night clubs using live musicians usually deal directly with a licensing society. Radio and TV stations and networks do the same, although the licenses are slightly different. Motion pictures are licensed through their producers, and recording companies have their own particular arrangements.

In the field of background music, the most common arrangement is for the supplier of the service to deal directly with a licensing body, paying such fees as may

be required and then passing this expense on to his clients or subscribers. Thus relatively few restaurants, etc., must go to the trouble of negotiating with ASCAP or BMI for the right to use background music—unless the restaurant owner himself assembles and reproduces music from an unlicensed source, such as the corner record shop. In this somewhat rare case, the owner must obtain his own license. Note that records and tapes sold in stores to the public are licensed only for private use, *not for profit*.

There are also noncommercial licenses available for cases where music is used by nonprofit organizations such as churches, schools, and the like. These do not require the payment of fees.

### Restrictions and Fees

The licensing organizations collect the fees from the users of the music. After deducting operating costs, they pass the money on to the composers and publishers. Money is apportioned to the various members on the basis of how frequently their music is performed.

When it comes to paying the license fees, it wouldn't be fair to charge the same rate for a small corner cafe as for a large hotel. Hence there are different rates for various commercial establishments, depending on such things as size of public area, seating capacity, number of speakers installed, type of establishment (industrial or entertainment), and whether or not admission is charged.

Generally the subscriber to background music is not permitted to make use of the music anywhere but on the premises specified in the license (or franchise or contract). He must make his books and records available (or else the supplier must) for inspection by the licensing society's representatives at any reasonable time, if necessary, to verify any agreements made under the license. From time to time, the subscriber or program supplier must furnish a sample log of musical selections transmitted to clients. The license may be terminated upon notice, which is often 30 days. There are various other minor technical restrictions.

If a franchise is granted for specific premises, such as a restaurant with a seating capacity of 50 persons, and the owner later remodels to seat 100, he must notify his music supplier and/or the licensing body.


### Conclusion

The preceding information is necessarily generalized, but should serve as an introduction to the subject. If you are entering the background-music field as an installer or franchiser, you should write directly to the headquarters of ASCAP and BMI (see below) for specific information concerning your particular application. While both firms are headquartered in New York City, they have regional offices around the U.S. ▲

ASCAP: American Society of Composers, Authors, & Publishers  
575 Madison Avenue  
New York New York 10022

BMI: Broadcast Music, Inc.  
589 Fifth Avenue  
New York, New York 10017

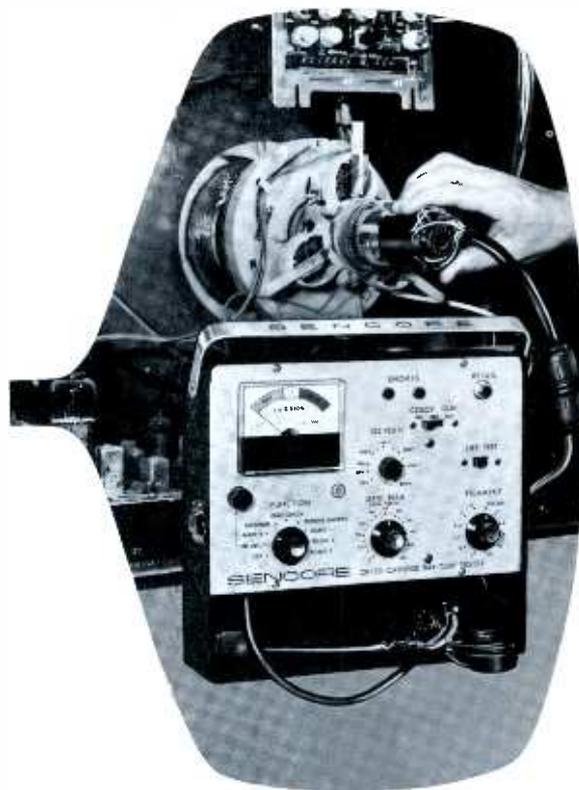**top money maker in  
the service business**



## NEW IMPROVED SENCORE CR133 CRT CHECKER & REJUVENATOR

The new, improved CR133 CRT Checker is designed to test all present picture tubes—and it's ready for future tubes too! Two plug-in replaceable cables contain all sockets required. The compact, 10 lb., CR133 checks CRT emission, inter-element shorts, control grid cut-off capabilities, gas and expected life. Checks all tubes: conventional B&W, new low drive B&W, round color tubes and new rectangular color picture tubes. Exclusive variable G2 Volts from 25 to 325 Volts insures non-obsolence when testing newly announced "semi-low" G2 CRT tubes. New Line Voltage Adjustment insures the most accurate tests possible. Uses well-filtered DC for all checks to avoid tube damage and reading errors. Color guns are individually tested as recommended by manufacturers. Exclusive automatically controlled rejuvenator applies rejuvenation (ACR) voltage as required by individual tube condition; precisely timed to prevent over-rejuvenation or tube damage. The ACR feature is most useful for color tube current equalization to insure proper tracking. Hand-wired and steel-encased for protection of meter and panel in truck or shop, the new improved CR133 is only . . . **\$89<sup>95</sup>**

The famous CR128 CRT Checker and Rejuvenator is similar to above, but with a three position G2 slide switch and without Line Voltage Adjustment at \$69.95

*professional quality — that's the difference!*

# SENCORE


426 SOUTH WESTGATE DRIVE • ADDISON, ILLINOIS

Circle 30 on literature card

August, 1965/PF REPORTER 51

# now there are 3 time & tool-saving double duty sets

New PS88 all-screwdriver set rounds out Xcelite's popular, compact convertible tool set line. Handy midgets do double duty when slipped into remarkable hollow "piggyback" torque amplifier handle which provides the grip, reach and power of standard drivers. Each set in a slim, trim, see-thru plastic pocket case, also usable as bench stand.

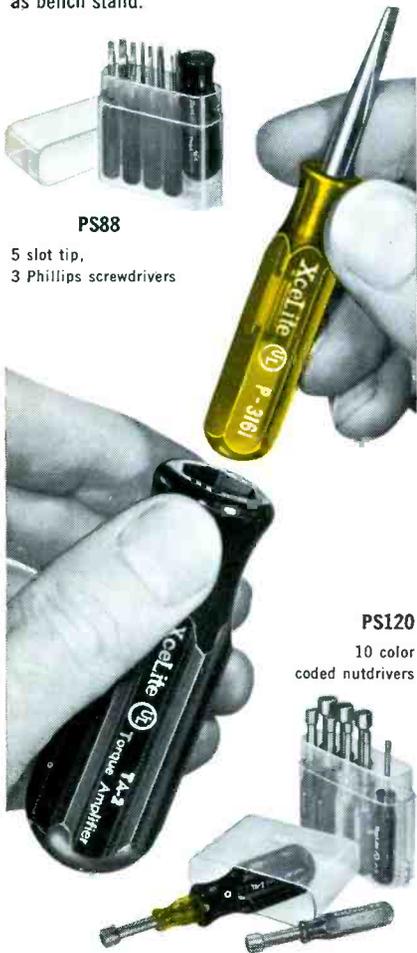

PS88

5 slot tip,  
3 Phillips screwdrivers

PS120

10 color  
coded nutdrivers

PS7

2 slot tip,  
2 Phillips screwdrivers,  
2 nutdrivers

WRITE FOR CATALOG SHEET N563



XCELITE, INC., 18 Bank St., Orchard Park, N.Y., U.S.A.  
Canada: Charles W. Pointon, Ltd., Toronto, Ont.

Circle 32 on literature card

52 PF REPORTER/August, 1965


## AGC Filter

(Continued from page 32)


when voltage readings were attempted, the trouble would immediately clear up, and it was necessary to wait until it reappeared before further checks could be made. The shop scope was then used because with its low-cap probe it produced less circuit disturbance than an 11-meg VTVM. The signal in Fig. 5 was observed on the IF AGC line; the 2-mfd capacitor on the AGC line was open. This set uses keyed AGC and a filter circuit similar to Fig. 1C; the open filter corresponded to C1.



(A) Picture

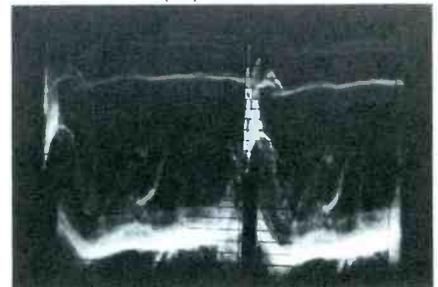

(B) Video signal

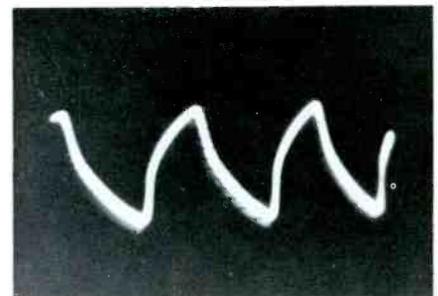

(C) Signal on AGC line

Fig. 8. Hard-to-lock-in pix in Motorola was due to an open AGC filter.

### Horizontal Line Interference

Horizontal-bar interference due to open AGC filters has been found in many makes and models using keyed AGC. This type of interference comes in many different variations. The condition shown in Fig. 6A occurred in a mid-fifties Westinghouse; the corresponding video signal is shown in Fig. 6B. Note that ringing in the trace and bars in the picture complement each other,

## New BERN'S Perfect Pin Crimper

### Picture-Tube Repair Tool

Also for—5U4, 6SN7, 6BQ6, etc.

Eliminates that hard  
soldering job  
only \$1.25  
each

Also for  
color pic  
tubes



Fix loose pin connections  
in seconds. Pays  
for itself in time saved  
on first job. 3\"/>

U.S. Pat. 2,878,698 CANADA Pat. 592,702

Intermittent operation of color, black and white picture tubes and other tubes due to defective solder connections easily corrected. Provides solid electrical connections, can also be used as channel-selector wrench and screwdriver. Pin keeps its original form. A 3-in-1 tool.

### 3 MODELS ELIMINATE SOLDERING

#### Makes Solid Electrical Connections Phono Pin-Plug Crimper

Slip wire in "pin  
plug," insert  
in tool, and  
squeeze  
job is done.

Crimps 1c ea.

Use end of  
tool to push  
on Crimp for  
ground  
connection.



Ant. plugs, hi-fi, multiple plugs, public address, radio and TV tubes, radar, speakers, and loop connections. Many, many more uses.

#### Model LC-3 for 5/32\"/>

The most wanted tools sold to and used by thousands of professional TV Service Technicians and School Trainees from coast to coast and foreign countries, also sold to U.S. Government. Nothing like it anywhere.

At your parts distributor. If not available have them order from us.

**BERN'S** Mfg. Co.

P.O. Box 7968  
14500 Kercheval  
Detroit, Mich. 48215

Circle 31 on literature card

950

ALL PARTS

(except tubes)

Plus Shipping Charge

QUALITY

TV TUNER

SERVICE

24 hrs.

Service

Most Makes

UHF - VHF - COLOR - (COMBOS. - 14.50)

15 YEARS OF TUNER EXPERIENCE

- 1 Year Warranty
- Tuners completely cleaned and checked
- Open Account on approved credit
- Dist. write for price structure



Pack Tuner Carefully  
— Insure Package —  
Include all parts  
(Broken or not)

QUALITY TUNER SERV.

5142 W. 25th St.  
CHICAGO, ILL. 60650

Circle 33 on literature card

being at the beginning of each vertical field and the top of the picture, respectively.

In some RCA's, KCS-68, 72, etc., the interference has been more severe. Two examples are the high-contrast condition with only 10 bars in Fig. 7A and the lower-contrast condition with about 16 bars in Fig. 7B. **More Effects**


Add two more troubles stemming from open AGC filters to those already covered. The trouble (on a Motorola TS-426) pictured in Fig. 8A gave every indication of sync trouble; lockin was attainable only with the most critical adjusting of hold controls, and then held only a few seconds. Presence of the distortion at the vertical sync and blanking segments of the video signal (Fig. 8B) suggested AGC-filter trouble, and the waveform (Fig. 8) on the IF AGC line verified that the capacitor was faulty.

A most unusual effect of an open AGC filter occurred intermittently in an Admiral portable, Model 15G1. The condition shown in Fig. 9A presented itself after about 15 minutes of warmup; it would clear up and then reappear at random intervals. It was learned that tapping the chassis also corrected or created the trouble. It was decided to find out as much as possible with scope tracing before removing the case, to avoid accidentally disturbing the defective component and making it that much harder to find.

The condition in Fig. 9A bears a resemblance to defective B—line filters discussed in previous Shop Talk articles. For this reason the easily accessible filter cans were scoped; their voltages were "hound's tooth" clean. Since there might have been other B—line filters than those in the cans, a scope check was made of the two B supplies (also accessible for scoping) feeding the tuner. Result — nothing. Finally a scope measurement at the feed-through connection for AGC to the tuner revealed the trouble—the 1½ volts of hash shown in Figs. 9B and 9C. Trace B was taken with a sweep frequency of 30 cps and a scope sensitivity of 10 volts per inch. Trace C shows the same signal with the



(A) Picture

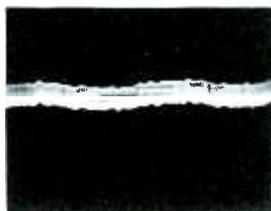


(B) Hash on line



(C) Trace B, different settings


Fig. 9. Condition due to an open AGC filter on the RF line.
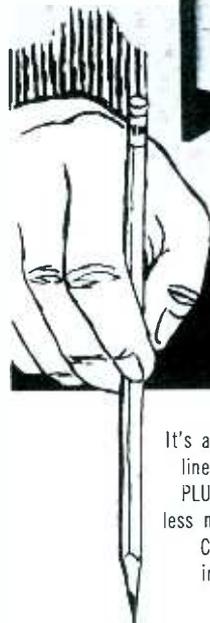
## PINPOINT COLOR TV TROUBLES IN SECONDS...


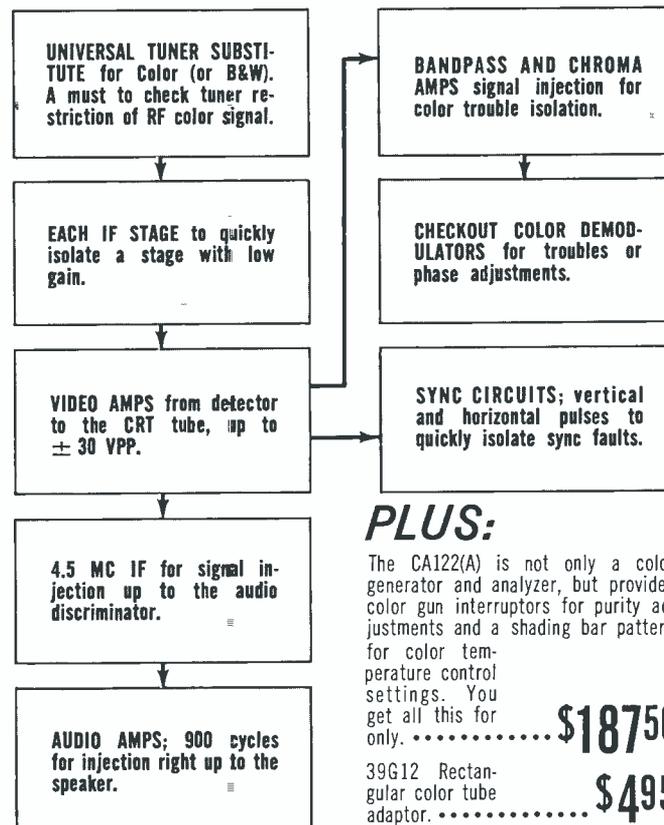
### WITH THE NEW IMPROVED SENCORE CA122(A) COLOR CIRCUIT ANALYZER

It's a standard ten color bar generator; produces vertical lines, horizontal lines, crosshatch, and adjustable dots, PLUS a complete TV analyzer for color and B&W—at less money than color generators only. Here is what the CA122(A) will do for you by tried and proven signal injection into these stages.



### PLUS:

The CA122(A) is not only a color generator and analyzer, but provides color gun interruptors for purity adjustments and a shading bar pattern for color temperature control settings. You get all this for only..... **\$18750**  
39G12 Rectangular color tube adaptor..... **\$495**

See your distributor today. He has the CA122(A) in stock now.

# SENCORE

426 SOUTH WESTGATE DRIVE

• ADDISON, ILLINOIS

Circle 34 on literature card

August, 1965/PF REPORTER 53

# great profits



(small inventory)

Imagine—just 6 Sonotone® crystal cartridges replace 146 models. In microminiatures, the Sonotone Micro-Ceramic® series updates to 1965 performance almost any phonograph using a ceramic cartridge produced within the past 20 years. Replacements in transistor phonographs? The "24T", "27T" and "35T" Micro-Ceramics are the answer. For the world's "safest cartridge," try the "21TR" with its fully retractable, hinged mounting bracket, bottoming button and Sono-Flex® stylus. Replacements in the top-end hi-fi models? The audiophile-accepted Sonotone "9T" series is your best bet. And from the standpoint of customer satisfaction, only Sonotone cartridges are equipped with the virtually indestructible Sono-Flex stylus. Now the clincher: Sonotone cartridges are direct replacements in more than 15 million phonographs in which they are original equipment.

These are just a few of the reasons you need stock fewer Sonotone cartridges than other brands—and still have the right replacement for just about every phonograph that comes into your shop. For comprehensive cartridge replacement guide, write:

## SONOTONE

audio products

Sonotone Corp., Electronic Applications Div., Emsford, N. Y.  
Export: Singer Prods. Co., Inc., P.O. Box 100, Yonkers, N. Y.

Circle 36 on literature card



Fig. 10. Receiver adjusted for normal vertical blanking bar at midscreen.

sweep at one-half horizontal frequency and one volt per inch scope sensitivity.

### Use the Vertical Blanking Bars

Inasmuch as defective AGC filters distort vertical sync signals, an indication of this defect can be obtained by looking at the vertical blanking bars. If the vertical-hold control is carefully adjusted so that the blanking bar can be seen, and brightness and contrast are also adjusted correctly, a normal bar will appear as in Fig. 10. Note that all portions of the blanking bar are darker than any picture content.

Fig. 11 shows the blanking bar in a set with an open AGC filter. In this case the equalizing pulses following the sync pulse dip into the



Fig. 11. Vertical blanking bar in set having an open AGC filter capacitor.

white levels of the video signal.

### Conclusion

There are various indicators present in AGC-filter troubles: critical vertical sync, vertical shading, horizontal bars, the telltale distortions in video signals, distortions of the vertical-blanking bar, the presence of abnormal signals on AGC lines. Using these indicators—and perhaps others of his own—the service technician should be able to make troubleshooting and curing AGC-filter troubles one of the easier tasks in keeping TV watchers happy. ▲

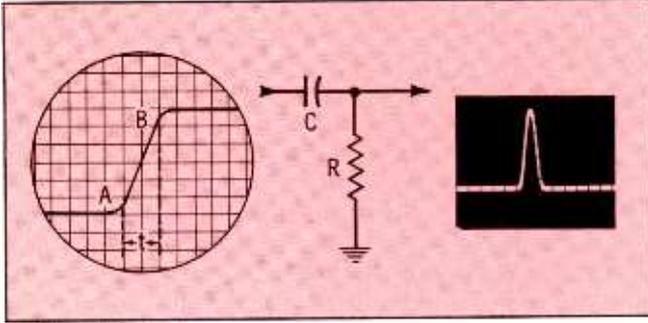


Fig. 6. Pulse amplitude is determined by both  $t$  and  $RC$ .

In Fig. 4A, the differentiating circuit produces an output pulse in which the leading edge has the same amplitude as the leading edge of the input square wave. In some practical situations, we will find this equality. On the other hand, consider the relations depicted in Fig. 6. Here, the amplitude of the output pulse is somewhat less than the square-wave amplitude. We will find by practical tests that as we make the time constant shorter, the amplitude of the output pulse becomes less; this results because the square wave does not have zero rise time. A square wave requires a certain time  $t$  to rise from A to B. In other words, we have a situation in which the square wave must be recognized as a trapezoidal wave.

Practical technicians do not concern themselves with the formula which relates  $t$  and  $RC$  in Fig. 6. Instead, they employ a handy rule-of-thumb, which states:

1. If  $RC$  is much greater than  $t$ , the pulse output has practically the same amplitude as the leading edge of the square wave.
2. If  $RC$  is about equal to  $t$ , the pulse output has approximately 53% of the amplitude of the leading edge of the square wave.
3. If  $RC$  is 30% or less of  $t$ , the pulse output will be approximately 30% or less of the amplitude of the leading edge of the square wave.

For example, if  $RC$  should be 10% of  $t$ , then the output pulse will have approximately 10% of the amplitude of the leading edge of the square wave. On the other hand, if  $RC$  should be 10 times  $t$ , then the output pulse will have approximately the same amplitude as the leading edge of the square wave. Note carefully that the rule-of-thumb we are discussing has *nothing whatsoever to do with the frequency of the square wave*. The rule-of-thumb concerns only the rise time of the square wave with respect to the amplitude of the output.

With these basic facts in mind, let's consider a practical application. Perhaps we suspect that  $C$  in Fig. 6 is open. A capacitor never becomes completely open, because there is a very small stray capacitance between its leads or terminals. If the capacitor is open, the time constant becomes very small. In turn, the amplitude of the output pulse becomes very small compared with the amplitude of the square-wave input. Observe the height of the output pulse. Then, short-circuit  $C$  temporarily. This feeds the input square wave directly to the scope. If the square-wave pattern jumps up to a much greater amplitude than the pulse, the suspicion that  $C$  is open is confirmed.

add an fm-stereo service center  
with this one new  
sencore unit!



## THE SENCORE MX129 FM STEREO MULTIPLEX GENERATOR & ANALYZER

FM-Stereo growth continues to mount and is fast becoming as big a field as Color TV. This means more FM-Stereo service business for you, now and in the future. Is your shop equipped? It can be — completely and economically — with the MX129, the FM-Stereo "Service Center in a Case." The instantly stable, 19-Transistor, crystal controlled MX129 is the most versatile, most portable (only 7½ pounds), most trouble free and efficient multiplex unit on the market — just like having your own FM-Stereo transmitter on your bench or in your truck. Powered by 115 volts AC, it produces all signals for trouble shooting and aligning the stereo section of the FM receiver . . . can be used to demonstrate stereo FM when no programs are being broadcast. Self-contained meter, calibrated in peak to peak volts and DB, is used to accurately set all MX129 controls and as an external meter to measure channel separator at the FM-Stereo speakers. **NO OTHER EQUIPMENT IS REQUIRED.** **\$169<sup>50</sup>** only

### SIGNALS AVAILABLE FOR ALIGNMENT, TROUBLE SHOOTING AND ANALYZING:

- FM-RF carrier with composite multiplex audio signal with 38kc suppressed carrier, 19kc pilot and 67kc SCA signals
- Multiplex signal formed by 60 or 1000 cycle internal tones or any external signal
- Full control over left and right channel amplitude (modulation)
- External 67kc SCA signal available for trap adjustment
- Composite signals available for signal injection FM detector

professional quality — that's the difference!

# SENCORE

426 SOUTH WESTGATE DRIVE • ADDISON, ILLINOIS

Circle 36 on literature card

August, 1965/PF REPORTER 55

Next, let's consider another type of practical application. Suppose that you are at the incoming-inspection station and are checking a shipment of capacitors for satisfactory tolerance. We know that if  $RC$  is much smaller than  $t$  in Fig. 6, then the height of the output pulse will be proportional to the value of  $C$ . If you provide a test jig to plug capacitors into the differentiating circuit of Fig. 6, the pulse height on the scope screen gives a relative measurement of capacitance. In other words, after choosing a suit-

able value of  $R$  to work with, the scope can be calibrated to read capacitance directly. Compared with measurements on a capacitor bridge, this test method is very rapid, because there is no adjustment required to find a null.

### Conclusion

Now that we have a basic understanding of how basic  $RC$  circuits respond to square waves, we are in a good position to proceed with square-wave tests of more elaborate  $RC$  "couplates" and complete stages

of printed circuits. These considerations will be explained in the following article. You will find that it is seldom necessary to disconnect a capacitor or resistor to localize a defect in any printed circuit. Square-wave tests give more information than ordinary waveforms when we tackle complex  $RC$  circuitry because the frequency and rise time of the applied square wave can be varied to assist in evaluation of results. On the other hand, if we use the waveform which happens to be present in the circuit, we are "stuck" with this waveform's frequency and rise time.

We will find that the output amplitude from complex  $RC$  circuits varies with the square-wave rise time and that this voltage-vs-rise-time response has considerable meaning with respect to defective components. Thus, we will be working with input amplitude, output amplitude, output amplitude variation, input frequency and rise time, output waveshape, and critical test conditions. In many cases, we will be concerned with waveform details which correspond to values of individual components. ▲

**CAN THIS PICTURE TUBE BE SAVED?**

Fading dull picture tubes bounce back pronto with **Perma-Power Briteners**

Give new life, new brightness to aging picture tubes—and watch your customer's confidence in you bounce back, too, when you sell a \$4.00 britener instead of a \$70.00 tube. (Then you're a cinch for the tube sale later.)

It's easy with Perma-Power's **Tu-Brite**. Handsomely packaged for instant acceptance, color-coded by base type for instant selection. The right voltage is assured. With Tu-Brite, *if the base is right, the boost is right*. Make sure you have all three models in stock.

- Model C-202** for duodecal base CRT's.
- Model C-212** for 110° button base CRT's.
- Model C-222** for 110° shell base CRT's. Net \$2.25 each.

Write for free **Britener Selector Chart**, your guide to the base type of every picture tube now in the field.

**YES!** Perma-Power Brightens Color Sets, Too. **Color-Brite** Model C-501, Net \$5.85 each.



**TYPE CTC . . .** cardboard tube electrolytics especially designed for exact placement in television sets . . . one end closed . . . long insulated leads out the other end . . . sealed with high melting point wax . . . guaranteed for one year . . . individually packaged.

**PLANET SALES CORP.**  
225 Belleville Ave.  
Bloomfield, New Jersey

**Perma-Power** COMPANY

5740 North Tripp Avenue • Chicago, Illinois 60646

Phone: 539-7171 (Area Code 312)

Circle 37 on literature card

Circle 38 on literature card

## PFR Bench Report



### Transistor Tester

Many times, in troubleshooting transistor circuitry, the technician is not concerned with anything about the transistor except whether it is good or bad. This transistor tester provides just that information: it tells the operator to either replace the transistor or go on looking for the real trouble.



Provisions are made for the testing of transistors (low- and high-wattage) in or out of the circuit. For in-circuit testing, color-coded leads which plug into labeled jacks are included to clip onto the transistor terminals. For out-of-circuit testing, two sockets are mounted on the tester; simply plug in the transistor.

To test the transistor, connect the leads or plug the transistor into the proper socket. Start with the variable control set to zero. A tone should be heard from the speaker; if it is not, reverse the PNP-NPN switch (the transistor will not be damaged). Advance the control until the tone stops, then turn it back until the tone just starts, and flip the PNP-NPN switch to the opposite position, then back again. The tone should start immediately if the transistor is good.

The pilot lamp indicates the relative amount of emitter current, and the control is calibrated in relative base current. If the light glows with the control set to zero, the transistor has an emitter-to-collector short. Leaky transistors cause the tone to "beep."

The Model XT-1 dynamic transistor tester is available from ESCO Manufacturing Company distributors at \$18.95. Test leads and instruction manual are included. ▲

*just in time for the  
fm and uhf boom!  
an all transistorized  
field strength meter.*



## THE ALL NEW SENCORE FS134 FIELD STRENGTH METER

Once again, you can turn to the roof tops for a fast dollar in antenna installations. But this time, you can do it the easy way. No more running up and down ladders, locating cumbersome AC extension cords, lugging heavy tube operated field strength meters on the roof, or worse yet, getting the shock of your life from the AC line as you hold onto a soil pipe. Here is a new portable field strength meter to fill your every need in VHF, UHF or FM antenna installations. Many customers want all antennas on one mast thus creating interaction. Here is where the FS134 goes to work. You can optimize antenna location and orientation in seconds. Just connect the antenna, tune in the station and adjust. Self-contained speaker blasts forth the sound from the TV or FM station to insure that you have the exact signal that you are looking for. The FS134 is so light weight (only 9 lbs.) that you can take it with you up the chimney if necessary. Get rid of the assistant at the other end of the transmission line and the needless "yelling" back and forth. Get the FS134 today . . .

only **\$199<sup>50</sup>**

COMPARE TO ANY OTHER FIELD STRENGTH METER  
AT TWICE THE MONEY

- Sensitivity . . . 5 microvolts on VHF and FM, 15 microvolts on UHF
- Input impedance . . . 300 ohms or 75 ohms with plug-in transformer
- 500 KC band width
- Powered by easy to get "C" cells
- 4 inch meter with 2 percent accuracy calibrated in DB and microvolts.

*professional quality — that's the difference!*


# SENCORE

426 SOUTH WESTGATE DRIVE • ADDISON, ILLINOIS

Circle 39 on literature card

August, 1965/PF REPORTER 57

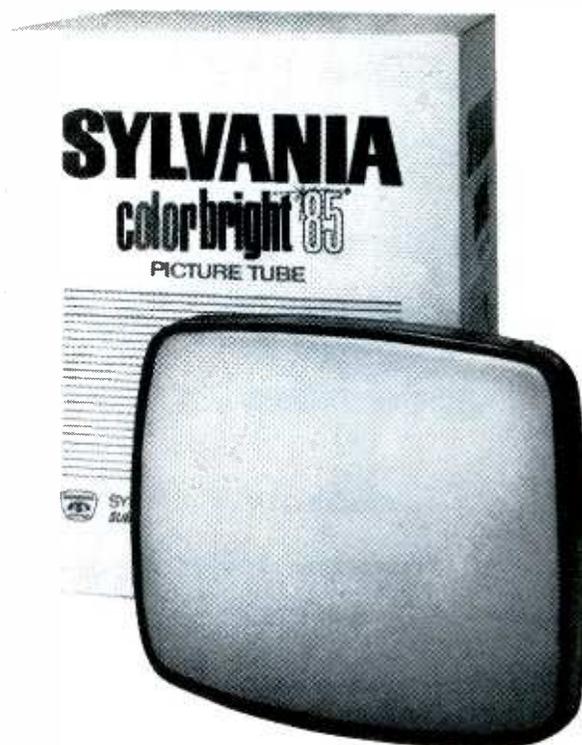YOU GET PRODUCT PLUS FROM YOUR SYLVANIA DISTRIBUTOR



# CONSUMERS' CHOICE

## Here's how.

	BRIGHTEST COLOR PICTURE	BEST OVERALL COLOR PERFORMANCE	CLEAREST COLOR PICTURE TO WATCH	BRIGHTEST BLACK AND WHITE PICTURES
Sylvania color bright 85 picture tube	76.1%	66.6%	68.0%	77.7%
Picture Tube A	6.9	9.8	8.9	7.4
Picture Tube B	9.5	13.7	13.4	7.1
Picture Tube C	7.5	9.9	9.7	7.8

Test made under supervision of John J. Henderson and Associates, N. Y. Note: Not all people answered all questions—votes tabulated for 100% of answers to each.

In six major cities from coast to coast, 9,789 consumers compared the new *color bright 85* picture tube to ordinary non-rare-earth color tubes in three leading brands of TV sets. Sylvania's new tube, the first with rare-earth phosphors, was the overwhelming choice.

## Here's why.

The vivid colors, derived from europium rare-earth compounds, are unexcelled for true color fidelity. In monochrome, the picture is noticeably brighter; there's better contrast too. And today this extraordinary tube is still the performance leader. Sylvania's new air-spun screening process gives *color bright 85* picture tubes the competitive difference in the sharpest images ever displayed.


The *color bright 85* tube is available to you now for today's growing color TV market. It is a product of Sylvania Electronic Tube Division, Electronic Components Group, Seneca Falls, N. Y.

**SYLVANIA**  
SUBSIDIARY OF  
GENERAL TELEPHONE & ELECTRONICS **GTE**

Circle 41 on literature card



## Push-Pull With Driver

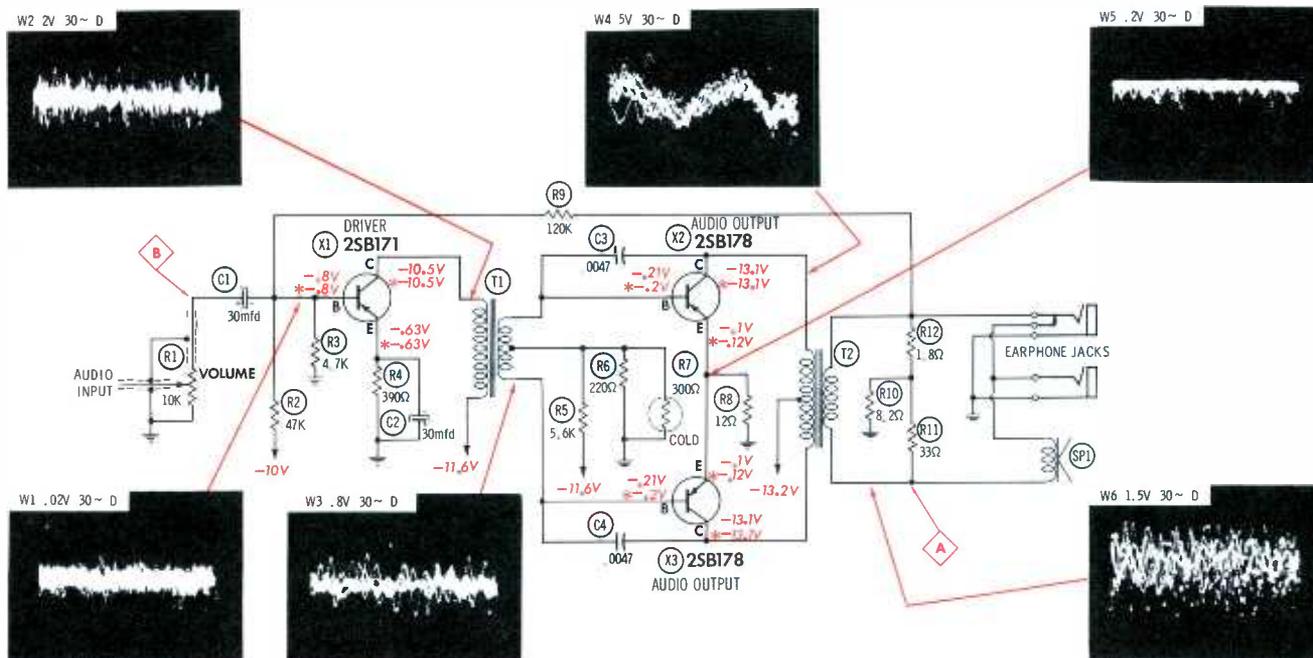

DC VOLTAGES taken with VTVM, on inactive channel; antenna terminals shorted. \*Indicates voltages taken with signal present—see "Operating Variation

WAVEFORMS taken with wideband scope; TV controls set to produce normal picture and sound. D (direct probe) usable at all points throughout circuit.

### Normal Operation

Push-pull audio output circuit preceded by driver is quite typical of audio sections in transistor TV's. Circuit is also used in many transistor radios. Operation of output and driver stages shown here (from Panasonic Model Mitey 9U) is exactly same as ones found in FM radios. Audio signal is coupled to base of driver through C1; signal level is determined by setting of volume control. X1 base voltage is derived from base voltage-divider network (R2 and R3). Base voltage is same as drop across R3. With PNP transistors and negative supply supply voltage, resistor from base to ground is always smaller value than resistor from base to source. With positive source, or negative source and NPN transistor, reverse is true—smaller resistor is from base to source. Audio signal is amplified by X1 and coupled to bases of output transistors through driver transformer (T1). Amplitude loss in coupling through T1 is due to step-down transformer, necessary for low-impedance input of output transistors. Base voltage on output transistors again is determined by voltage divider network (R5, R6, and R7). Resistance of R7 is 300 ohms cold but decreases as set reaches operating temperature. Resistance change in R7 permits stable operation of transistors from time set is first turned on until set reaches maximum operating temperature. Emitter resistor R8 is to prevent thermal runaway of output transistors, isn't actually bias resistor, although small voltage is developed across it. T2 is step-down type similar to those used in tube-type receivers.

### Operating Variations

#### X1

With or without signal present, DC voltages on all elements of driver transistor remain same. Waveform amplitude (peak-to-peak voltage) on base and collector is determined by setting of volume control. At maximum setting of control, (with normal program on local channel) audio signal at base increases to .07 volt; at collector to 10.

#### X2B, X3B

With signal present and normal volume, base voltage on output transistors decreases slightly. Decrease is even greater (to  $-1.15$  volt) with volume control at maximum.

#### X2E, X3E

Emitter voltage increases with signal, due to increased current in output stage. With volume control fully clockwise, voltage increases to  $-.3$  volt.

#### X2C, X3C

At normal volume, collector voltage remains constant with or without signal. However, with volume control set to maximum, increased collector current results in collector voltage decreasing to  $-12.8$  volts.

#### WAVEFORMS

Waveform amplitude throughout output stage is dependent upon content of audio signal and setting of volume control. At maximum volume W3 is 3 volts, W4 20 volts, W5 1 volt, and W6 is 1.5 volts.

## Audio Missing

No Hash or Noise Is Present

### Symptom 1

#### C1 Open

(Base Coupling Capacitor—30 mfd)




Symptom Analysis



Absolutely no sound is heard from speaker; not even hash or noise is present with receiver tuned to inactive channel; volume control has no effect. This suggests trouble in driver or output stages, because with defects in IF stages noise is usually audible.
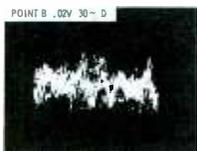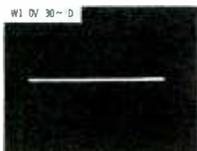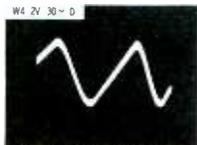
#### Waveform Analysis

Audio signal is completely missing in W4, only 2-volt ripple on supply voltage is present—evidenced by fact that waveform doesn't vary in amplitude as volume control is rotated. W1 eliminates driver and output stages, as signal is still missing at this point. Immediate area of trouble is pinpointed by scoping at point B. Audio signal is present here; thus open circuit exists somewhere between point B and base of driver transistor.



#### Voltage and Component Analysis

NO VOLTAGE CLUES

Open coupling capacitor from volume control to base of X1 has no effect on DC voltages—all remain normal with or without signal. Therefore, defect is impossible to locate with voltage measurements; however, trouble can be found quite easily and rapidly by scope or signal injection. Touching finger to soldering aid and making contact on X1 base produces buzz from speaker, indicating following stages are operating. Same procedure at high side of volume control results in no buzz; therefore open circuit is quickly isolated.

**Best Bet: Scope or signal injection.**

## Volume Reduced

Audio Not Garbled

### Symptom 2

#### R2 Increased in Value

(Base Bias Resistor—47K)



Symptom Analysis




Output level from speaker is reduced; normal volume can be obtained, but volume control must be fully clockwise (maximum). Sound isn't "fuzzy" or garbled. Without signal, only background noise is audible; no buzz or hum is present. Audio output stages are suspected.
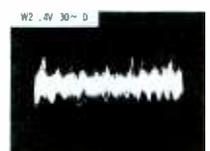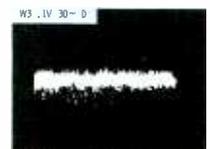
#### Waveform Analysis

Waveform (W3) on base of output transistor is reduced in amplitude—only .1 volt p-p (normal is .8 volt). This clears output stages as being responsible for trouble. All stages preceding driver are proven to be operating normally by fact that W1 is correct. Further isolation of defective area is obtained by viewing W2; amplitude is greatly reduced (it's only .4 volt p-p). Therefore, loss of amplification is occurring in driver stage.



#### Voltage and Component Analysis

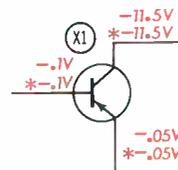

Faulty stage can be isolated with meter; however, scope checks will locate defective stage much more readily. Only three waveform checks are necessary, whereas more measurements are required when checking with meter first. Once stage is determined with scope, voltage measurements on X1 readily point to trouble. Since base voltage is reduced to .1 volt, increase in value of R2 or decrease of R3 (less likely) is suspected. Emitter voltage is decreased and collector voltage increased because of reduced emitter and collector current.

**Best Bet: Scope to isolate; then VTVM.**


## Volume Reduced

Audio Not Distorted


### SYMPTOM 3

#### R4 Increased in Value

(Emitter Resistor—390 ohms)


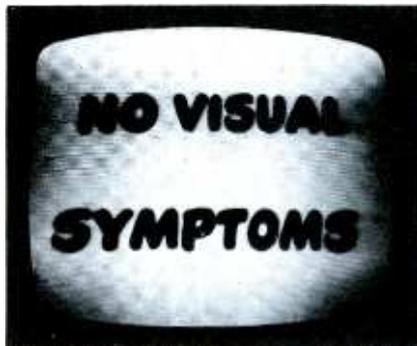


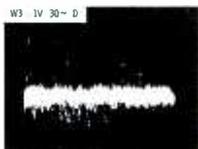Sound output level is greatly reduced. At normal setting of volume control, sound is barely audible. Even with volume control at maximum, sound level is only normal or slightly less than normal. Audio is free from any type of distortion.



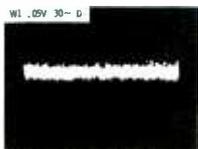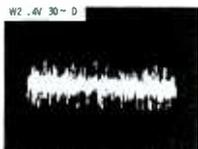
#### Waveform Analysis

Symptom suggests loss of gain in output or driver stage; thus, waveform check at base of output transistors (W3) is good place to begin troubleshooting. Signal level at this point is reduced to .1 volt, clearing output stage and suggesting next check should be in driver. W2 is also reduced—only .4 volt p-p. Tracing backward shows W1 is slightly increased; although not really indicative of trouble, it definitely isolates driver stage.



#### Voltage and Component Analysis

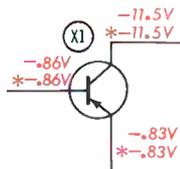

Based on information gained from scope analysis, voltage checks on elements of X1 should provide positive location of defective component—and they do. Emitter voltage is increased to  $-.83$  volt and base voltage has also increased, but only slightly (.06 volt). Collector voltage is increased to  $-11.5$  volts, suggesting decrease in collector current; however, emitter voltage indicates increased current. Analysis of voltage clues definitely points to increase in value of R4. Resistance measurement from emitter to ground isolates bad component.

Best Bet: Scope followed by voltage checks.


## Volume Reduced

Audio Is Distinct

### SYMPTOM 4

#### R8 Increased in Value

(Thermal-Runaway Resistor—12 ohms)

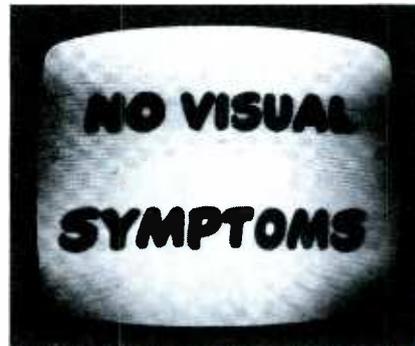


#### Symptom Analysis


Sound heard from speaker is reduced, even with volume control at maximum. Audio is distinct—no buzz or hum is present. Picture and raster are normal; therefore, stages handling both audio and video are probably okay. Symptom is indicative of defect in audio output.
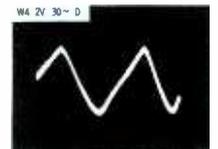
#### Waveform Analysis

Normal waveform (W3) on base of X3 and waveform on X2 base (not shown) prove previous stages are normal, and further substantiate that output circuit is responsible for trouble. Search for trouble is narrowed even further by W4; waveform is mostly 60-cps ripple which cancels in T2 primary. Emitter signal W5 is normal; scope proves only that loss of gain in output stage is reason for reduced volume, does not isolate defective component.



#### Voltage and Component Analysis

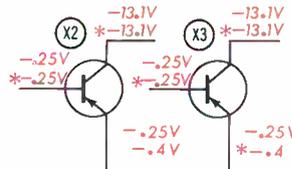

Following information gained from scope analysis and concentrating voltage checks on output stage proves helpful. Most drastic voltage change is on emitters of X2 and X3; reading has increased to  $-.4$  volt, but collector voltage is unchanged. Thus, increase in value of R8, rather than increased current, is responsible for loss of gain. Base voltages did change slightly, but not enough to be of any significance. When emitter resistor has changed value, be sure to check output transistors, as they may have been damaged.

Best Bet: Scope followed by voltage measurements.

## Volume Insufficient

Audio Is Distortion Free

### X2 Leaky

(Output Transistor—25B178)

#### Symptom 5


Symptom Analysis



With volume control at normal, sound volume from speaker is considerably less than adequate. Normal volume can be developed, but only with control near maximum. Sound is free of buzz and hum; thus, driver or output stage is suspected trouble spot.
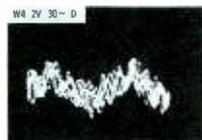
#### Waveform Analysis


Since symptom indicates trouble in output circuit, base of output transistor (W3) is logical point to begin scope checks. Preceding stages are proven to be okay by presence of normal W3. Reduced amplitude of W4 strongly suggests loss of amplification in output stage. W5 is increased in amplitude, and during pauses in transmitted audio, 60-cps ripple is present. Ripple present at emitter is definite clue to leakage in transistor.



#### Voltage and Component Analysis

Since symptom points to trouble in audio output circuit, voltage measurements on output transistors should prove helpful. This check does provide valuable information, since voltages on all elements of X2 and X3 are incorrect. X2 leakage is more likely since voltages on this transistor are considerably more abnormal than those on X3. Amount of leakage determines exact symptom. Slight leakage may be unnoticed, while excessive leakage results in severe loss of volume or, in some cases, complete absence of any audible signal.

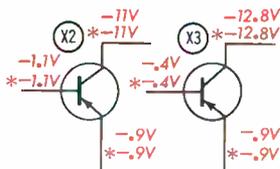**Best Bet: Voltage checks and circuit analysis.**



## No Audio

Picture and Raster Normal

### Open Connection in Earphone Jack

(Broken Contact)

#### Symptom 6

Symptom Analysis



Audio section of receiver is completely dead; absolutely no sound is heard from speaker. Raster and picture are both normal. Touching finger to base of driver or to base of output stages still results in no sound being heard from speaker.

#### Waveform Analysis

Audio signal at output of driver (W2) is normal, localizing trouble area to between this point and speaker. Normal W4 eliminates output transistors and associated components; thus, only output transformer and speaker circuitry remain as possible causes of trouble. Normal W6 (at input to speaker) proves transformer isn't responsible for loss of sound and points to open circuit somewhere between point A and speaker return to transformer.



NO VOLTAGE CLUES

#### Voltage and Component Analysis


Fault can be located with continuity check. Such checks can be misleading because of parallel paths. Here speaker lead was disconnected from point A and check made from speaker terminal to ground. Without lead disconnected meter shows continuity through secondary of T2. With troubles of this nature, visual inspection prior to removing chassis will often save considerable troubleshooting time. Dirty, broken, or corroded contacts on earphone jacks aren't uncommon occurrences, especially in small portable transistor radios.

**Best Bet: Visual inspection and resistance checks.**

**Your black and white skills**



**are not enough for Color TV**

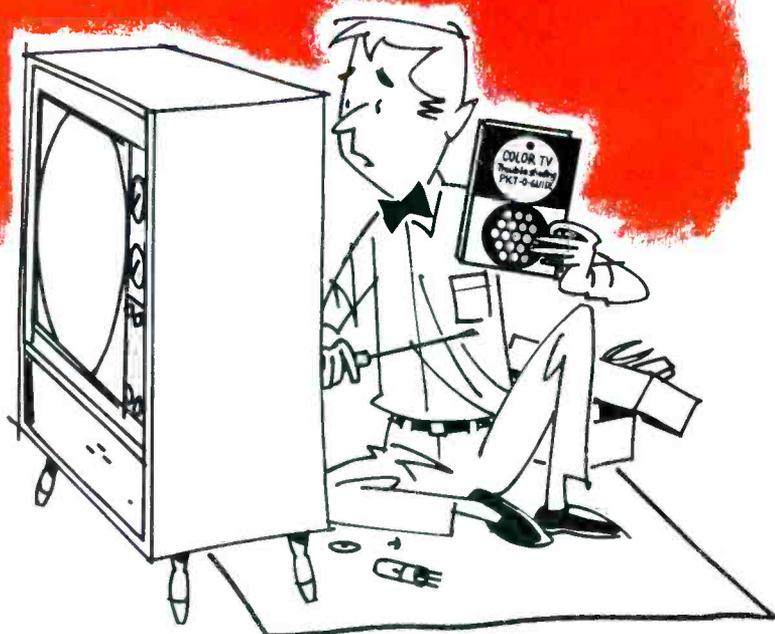


**You need this book  
to help you cash in  
on Color TV business**

NEW RCA COLOR TV TROUBLESHOOTING  
PICT-O-GUIDE, 1A1389

You're missing more and more chances for profit if you're not in color TV service. There are 3 million color sets in use now... and the total should be at least 5 million by the end of the year.

The new, completely revised RCA Color TV Pict-O-Guide, with its many color photos and illustrated step-by-step instructions makes it possible for you to recognize and understand the visible symptoms of troubles and maladjustments in color receivers. Use the Pict-O-Guide whenever you work on a color set.

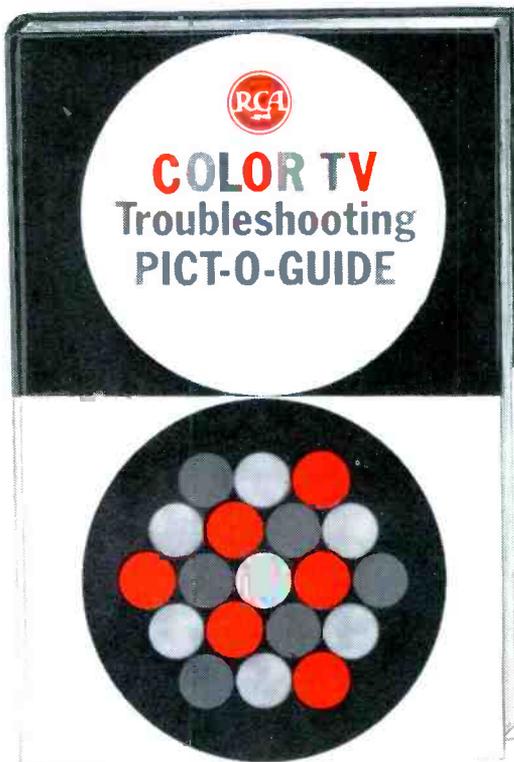RCA ELECTRONIC COMPONENTS AND DEVICES, HARRISON, N. J.



(For a complete course in the principles and practices of color TV you will find the 8 lesson Color TV Home Study Course by RCA Institutes, 1A1325, invaluable.)

WHAT THE  
RCA COLOR TV  
PICT-O-GUIDE  
GIVES YOU:

- Color Fundamentals
- Receiver Set-Up
- Functions of the Color Set Controls
- How to Use Color Test Equipment
- Troubleshooting Color and Black and White Sections of Receiver
- Servicing and Alignment Techniques


...and much, much more. 150 pages. *This book should more than pay for itself the first time you use it.*

**ORDER THROUGH  
YOUR LOCAL  
AUTHORIZED RCA  
TUBE DISTRIBUTOR**



**The Most Trusted Name in Electronics**




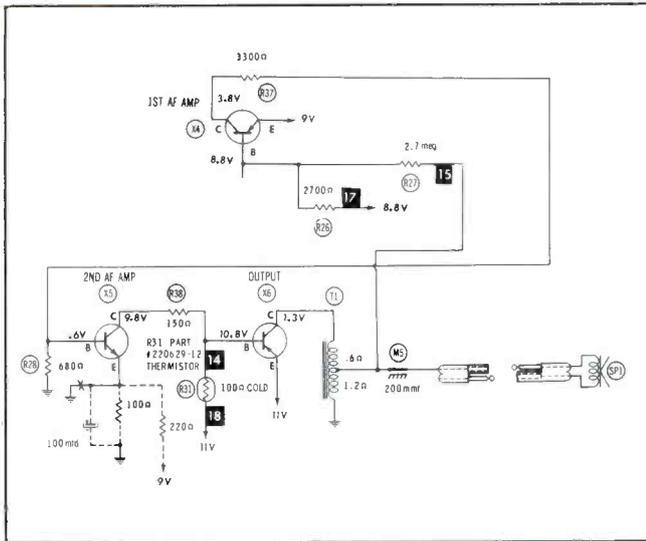

The driver stage of this receiver was changed in late production models. X5, Bendix part 2091260-3, was replaced with Bendix part 2092609-1; and the emitter of X5 was tied to ground. Check the circuit board to see if the emitter of X5 is connected to ground through a 100-ohm resistor to determine if this is an early- or late-production model.

Since X4, X5, and X6 are direct-coupled amplifiers, any drift in one stage would affect the DC levels in the following stages. Start the set; before fading begins, check base, collector, and emitter voltages of X4, X5, and X6. Apply concentrated heat around X4 and X5; note the first voltage that changes, and then check the associated resistors and the transistor. Don't overlook the possibility of thermistor R31 being defective. ▲
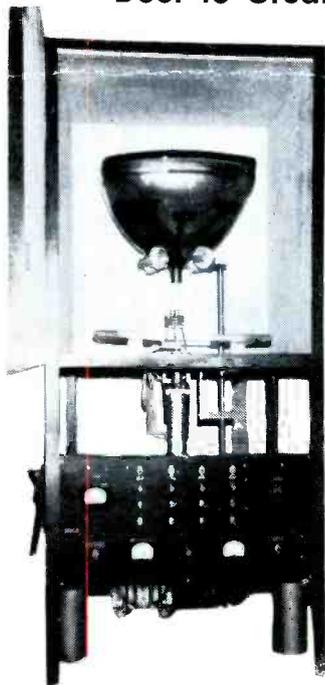
## TECHNICANS . . . Open the Door to Greater TV Profits



Rebuild Color — Black and White — Bonded Face Television Picture Tubes in

### YOUR OWN SHOP

Send today for 16 page brochure describing how you can capture the television picture tube rebuilding market in your area. Low investment of \$3,290.00 and up. Financing available. Training at our plant included in low price. Get started today toward greater profit tomorrow.

### VACATION BONUS

When on vacation plan to stop by and see a complete demonstration. If purchase is made while you are here Windsor will pay equivalent to your tourist rate plane fare from your U.S. home and back with the exception of Alaska and Hawaii.

## WINDSOR ELECTRONICS, INC.

Equipment Division  
999 N. Main St., Glen Ellyn, Illinois

Circle 40 on literature card



PICTURE TUBES, TOO

# SECO MODEL 88 TESTS ALL TUBES

Tests all receiving tubes including novars, nuvistors, 10 pin types, compactrons, magnovals—plus over 400 cathode ray picture tubes including 110° deflection types. Reveals cathode emission, leaks, shorts, grid emission, gas error, filament continuity and cathode-to-heater emission.

MODEL 88 TUBE TESTER \$74<sup>50</sup><sub>NET</sub>

## MODEL 98 HAS PLUG-IN CHASSIS

Plug-in socket chassis is easy to replace if it wears or if new tube types appear. Tests picture tubes and all receiving tubes (over 2500 types)—reveals same tube errors as Model 88 above.

MODEL 98 TUBE TESTER \$99<sup>50</sup><sub>NET</sub>

PICTURE TUBES, TOO




PICTURE TUBE ADAPTOR INCLUDED

This picture tube adaptor with a 12-pin socket fits over 400 cathode ray picture tubes including 110° deflection types. Comes with Model 88 and Model 98 Seco Tube Testers!
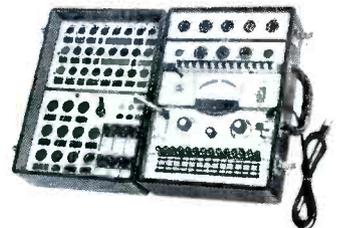
## MODEL 107B FOR NO SET-UP TESTING

40 prewired sockets fit 63 tube bases—plus a plug-in 8 socket chassis wired to 14 lever type pin selectors. Gives three comprehensive tests—finds faults quickly.



MODEL 107B TUBE TESTER \$189<sup>50</sup><sub>NET</sub>



Write for full information today

## SECO ELECTRONICS

1221 S. Clover Drive • Minneapolis, Minn. 55420

Circle 43 on literature card

August, 1965/PF REPORTER 65

the greatest—yet the smallest—  
price-and-performance package  
ever to hit commercial sound



INTRODUCING NEW  
COMPACT  
**MERCURY**  
PUBLIC-ADDRESS AMPLIFIERS  
10, 25, 40 watts

Harman-Kardon's new compact MERCURY p.a. amplifiers put out clean, fully usable rated power from a tiny package and at a low price. You'll find wide use for MERCURY in motels, restaurants, small apartment houses, and other low- to medium-power installations.

Trim, metal-enclosed package (4½" x 5½" x 9½" on all three models) fits easily on shelf, under counter—almost anywhere. Universal microphone input on all models allows use of either high- or low-impedance microphones—no matching transformers necessary. All input and output jacks conveniently located on rear apron. Reliable push-pull circuitry on all three models delivers clean, full-rated power output. Compact MERCURY amplifiers—10 watts, 25 watts, or 40 watts—meet or exceed their rated specifications.

Send for complete information on MERCURY—the best dollar-for-dollar value in its price and power category.



A subsidiary of The Jerrold Corporation.

Commercial Sound Division  
15th & Lehigh Avenue • Philadelphia Pa, 19132

Circle 44 on literature card


**COLOR COUNTERMEASURES**

Symptoms and service tips from actual shop experience

Chassis: Zenith 27KC20.

Symptom: Uncontrollable brightness.

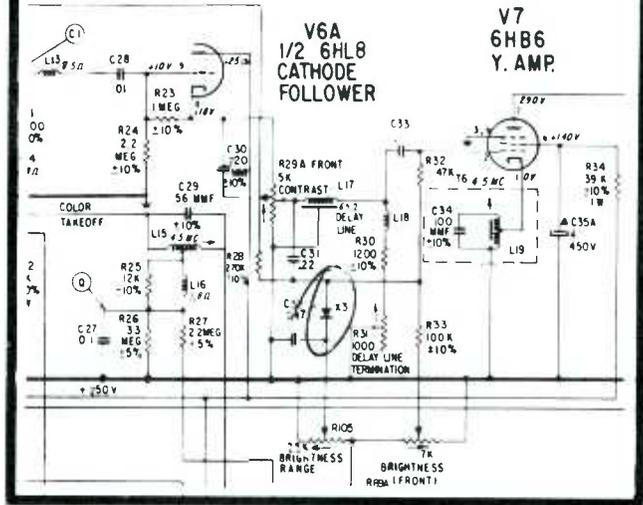Tips: Customer-operated brightness control on front panel is inoperative. Internal brightness-range control (located on the operating control-panel subchassis) is working normally. Check for a shorted crystal diode in the brightness circuit. Replace X3 (connected from center tap of brightness range control to junction of R28, R32, and C31) with Zenith part No. 103-23; be sure to observe polarity.



Distributors,  
THEY  
SELL  
LIKE  
HOTCAKES  
Dealers,



with mic, cord, & i ch

**Generals 24 Channel Super MC-8**

Once again General has produced a new and original design to set the pace for the entire Citizens Radio Industry. The new 24 Channel Super MC-8 with Turretuner is years ahead of the field. Its 30 watt construction and super sensitive dual conversion receiver are the result of many years of development and testing.

General CB equipment has long been recognized as the industry standard of engineering quality and performance. NEW TERRITORIES ARE OPEN. Write to Larry Larisan, Vice President and National Sales Manager at General, today.

**GENERAL RADIOTELEPHONE COMPANY**

3501 West Burbank Boulevard, Burbank, California  
Telephone: 849-6891, Area Code: 213

Circle 45 on literature card

# Want faster parts action? Mail this coupon.



Things move fast when you order parts from Philco. Your Philco Distributor's experienced parts specialists have only one job—to get that part out to you, and fast. Fast parts service means money to you, and your Philco Distributor never forgets it!

He stocks direct replacement parts for just about every model Philco TV, radio, phonograph and record-changer ever made—plus a wide range of national brand components and accessories for all makes and models such as Sprague Capacitors, Eveready Batteries, Rembrandt Antennas, G.C. Products, Semitron Transistors, Speco Components, Sencore Test Equipment, Colormagic Antennas.

If by chance he's out of a part you need, Philco's Lifeline Emergency Service goes into action. Your requirement is quickly transmitted to Philco's new National Parts Depot at Bedford, Indiana—and your part is on its way to you by air within 24 hours or less.

If you're not getting this kind of fast, complete parts service, don't you think you ought to be? Just mail the coupon and start doing business with your nearest Philco Parts Distributor.

YES, Philco, I want faster, complete parts service! Tell the nearest Philco Parts Distributor to send me information about special Philco Parts offers, prices and facts. And tell him to hurry!

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_

State \_\_\_\_\_

Mail to: Philco Parts & Service Department  
P. O. Box No. 3635  
Philadelphia, Pennsylvania 19134

P

PARTS & SERVICE DEPARTMENT  
**PHILCO**<sup>®</sup>  
A SUBSIDIARY OF *Ford Motor Company*

*you can't properly service  
color tv without these*

**I.E.H.**

## COLOR HARNESES & ADAPTORS

- For Efficient and Profitable Color TV Servicing.
- Fits All 19", 21", 23" and 25" Color Tubes.
- You Need No Others!
- Kit includes UNIVERSAL COLOR HARNESS FOR ALL 21", 23" and 25" Color Tubes, Yoke, Anode, Convergence Magnet Extensions and Adaptors.
- Look for the "slots in the socket."
- New From I.E.H., the only manufacturer producing a complete line of color harnesses and adaptors.



the slots  
make it universal

for all 21", 23"  
& 25" round  
and rectangular  
color tubes

### Convert, Adapt and Extend for Servicing any Color TV Set

Kinescope socket extension cable, 48" for all color sets with 21AXP22 CRT—CR-106

Deflection Yoke Extension Cable, 48" For RCA Color Chassis CTC7 to CTC 15, Motorola, Admiral, Zenith, etc. CR-502

Deflection Yoke Extension Cable, 48" For all 23" and 25" color sets. CR-504

Adaptor Socket converts 21AXP22 socket to 23" & 25" socket for test equipment. CR-505

Kinescope Extension, 48" for 23EGP22/25AP22 rectangular tubes. CR-506

Kinescope Adaptor Extension, 48" Converts 23" or 25" color sets for use in 21" color jig or test tube. CR-507

Anode Extension, 48" For extending anode lead when set is removed from chassis. CR-508

Convergence Magnet Extension / Deflection Yoke Extension, 48" Convergence magnet extension for RCA CTC7 to CTC15 chassis, Admiral, Motorola, Zenith, etc. Deflection yoke extension cable for RCA 600 and 700 series chassis. CR-509.

Color Convergence Grid Shunt Color Gun killer. AS-122




- Packaged in a see-thru plastic utility box!
- Don't miss out—see your I.E.H. distributor now!

**I.E.H. MFG. CO., INC.**


102 Prince St., New York, N. Y. 10012 • (212) 925-8500

Circle 47 on literature card

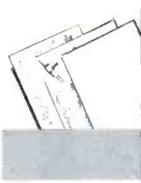
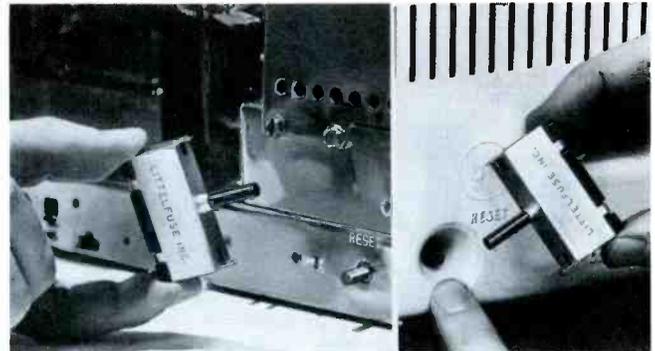
## Product Report

For further information on any of the following items, circle the associated number on the Catalog & Literature Card.



120

### Circuit Breakers for TV


The "Littelbreaker," a manual-reset circuit breaker by Littel-fuse, Inc., is of completely enclosed construction. Units are available for exact replacement in all television sets now made using this type of circuit interrupter. The circuit breakers measure 1 $\frac{3}{4}$ " x 1 $\frac{13}{16}$ " x  $\frac{1}{2}$ " with two solder terminals on the back for connection. The 815(000) Series thermally responsive breakers are dual-operated bimetallic devices providing temperature compensation over a wide range of ambient temperature variation. They are rated at 125 VAC with current-carrying capacities up to 3 amps. A built-in "trip-free" feature prevents the breaker from closing when dangerous overload currents are flowing through the breaker even if the plastic plunger is held fully depressed to restore a faulty circuit.



121

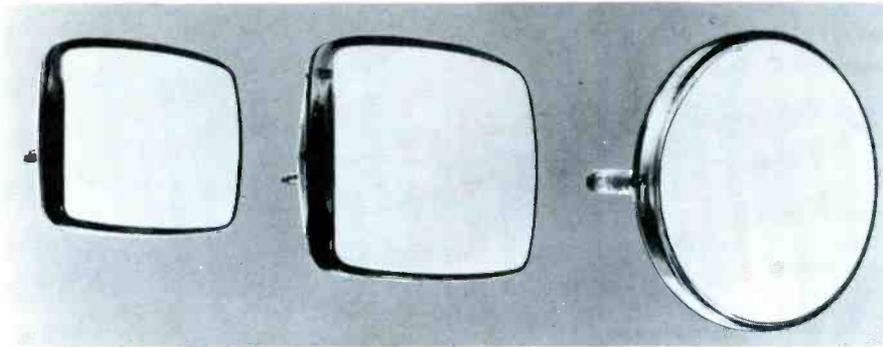
### Lightning Protection

A new capacitor/resistor spark-gap component, designed especially for antenna coupling devices, is now available from Centralab, the Electronics Division of Globe-Union, Inc. Called the "Type-L Tube-R-Cap" the miniature device carries the Underwriters' Laboratories yellow-card listing. Hollow tubular construction permits these units to be slipped over antenna-terminal pins of any TV, radio, or communications unit and soldered directly to the pins. According to the manufacturer, this assembly method results in a considerable reduction in production time. Attachment and soldering operations, except for the antenna leads themselves, are eliminated. The Type-L measures only 9/32" in diameter and is  $\frac{3}{8}$ " long. It is currently available as a .001-mfd/1-megohm combination. Voltage rating is 1.4 kv DC and 150 volts rms.



**Rare Earth 19" Color Tube**  
(122)


Sylvania Electric Products, Inc. has sent samples of its new 19", 90°, rectangular color-television picture tube to the nation's leading TV set manufacturers. The 19" tube uses Sylvania's exclusive red "rare earth" europium-activated yttrium-vanadate phosphor, plus improved green and blue phosphors. The phosphors are said to provide a substantially brighter picture than is obtainable with standard phosphors. The 19" color tube is the third color tube using rare earth elements for brighter pictures introduced by Sylvania in the past six months. Shown in the photo are Sylvania's 21" round, 25" rectangular, and 19", 90° rectangular tubes. The latter tube will be available in quantities during the second half of 1965.

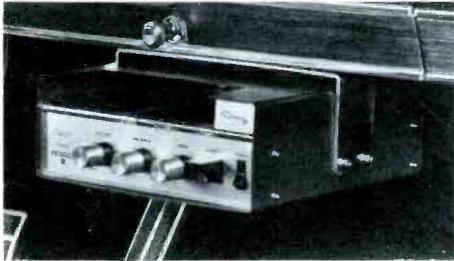

(123)
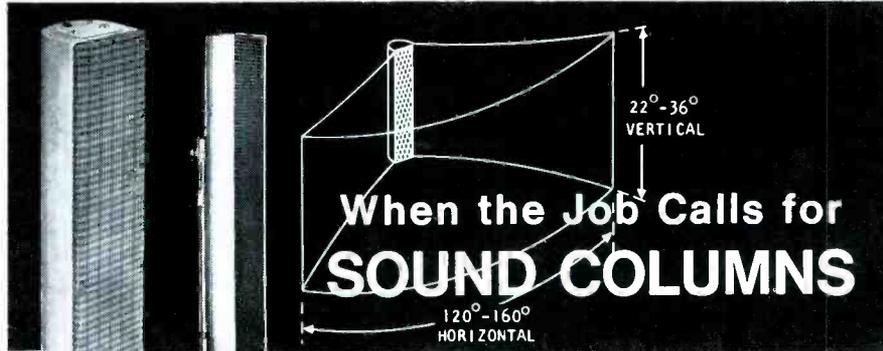
### Auto Tape Recorder

This new car-mounted stereo tape recorder has such features as solid-state amplifiers, dual-stereo playback heads, electronic track selection, push-pull output, and a self-activating cartridge system. The case is of all-steel construction with a brushed-aluminum face plate. The Model C-502, a product of the Auto Sound Division of Craig Panorama, Inc., is priced at \$119.



**When the Job Calls for  
SOUND COLUMNS**

### BE COLUMN RIGHT

When the job calls for columns—the controlled distribution of sound to cope with acoustic feedback—all the reasons add up to specifying "Columair" C-46 and C-66 columns by ATLAS SOUND.

**EFFECTIVENESS**—Feedback-generating low frequencies have been engineered out deliberately. Focused dispersion pattern controls "howl" in reverberant trouble spots by restricting coverage to audience.

**CONVENIENCE**—Compact design fits neatly anywhere with handling ease that king-size sound columns cannot match. Exclusive "EASY-MOUNT" brackets by ATLAS SOUND simplify installation and critical aiming for accurate coverage. Neutral-finish metal enclosure blends with decor. For special matching, grill cloth replacement and refinishing are easy. The SS-4 Stand and MK-1 Attachment Kit make child's play of portable applications and rental jobs.

**ECONOMY**—You can afford better coverage at "Columair" budget prices. C-46 (Six 4" speakers, 20 watts), \$37.50 Net. C-66 (Six 6" speakers, 40 watts), \$57.00 Net. SS-4 Stand, \$13.50 Net. MK-1 Kit, \$1.20 Net.

For full specifications on "Columair" sound columns—and for the ATLAS SOUND answer to all your needs in public address speakers and microphone stands—write for Catalog PFC-18



**ATLAS SOUND**, Division of  
AMERICAN TRADING AND PRODUCTION CORPORATION  
1419-51 39th Street, Brooklyn, New York 11218

Canada: Atlas Radio Corporation, Toronto



**THIRTY YEARS OF LEADERSHIP IN COMMERCIAL SOUND**

Circle 48 on literature card

# UPdate your present test equipment to UHF...



## with the new LECTROTECH U-75 UHF TRANSLATOR

*For Color and Black and White*

Instantly converts VHF signals from Channels 2 through 6 to UHF Channels 15 through 75 without wiring or modification. The only UHF translator with tuned VHF input for sharpest image... no unwanted signals. No existing test equipment provides a UHF signal for servicing UHF sections of TV sets or UHF converters. Now, the U-75 converts VHF signals from analyzers, color bar generators, test pattern and AM signal generators or regular VHF TV programs to UHF for test purposes. Connects in a flash... simply dial channel desired for color or black and white signal. A precision instrument in rugged steel case for shop and field servicing. 300 and 75 ohm impedance matched inputs. Less battery \$39.50 (9 volt). Only \$39.50

**One Year Warranty**




Manufacturers **V7**  
of the famous  
—the only complete  
Color TV Test In-  
strument. Complete... 18950

See your distributor or write Dept. PF-8  
**LECTROTECH, INC.**  
1377 Devon Avenue, Chicago, Illinois 60626

Circle 49 on literature card

August, 1965/PF REPORTER 69

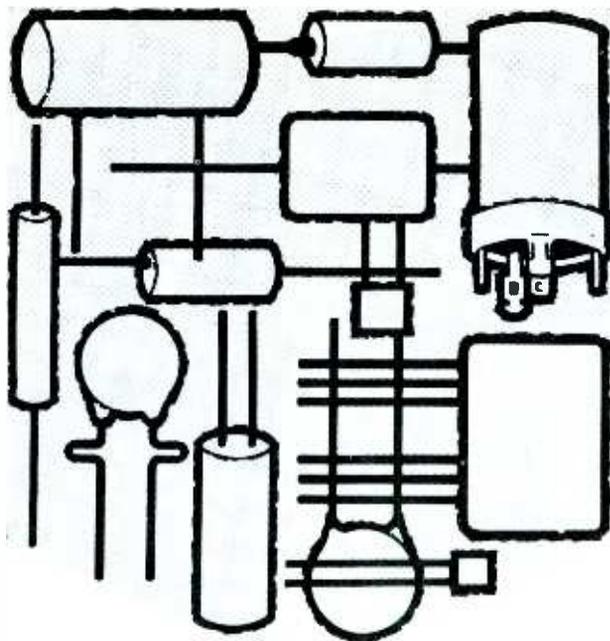

Whatever your replacement need...

CALL FOR  
**AEROVOX**  
CAPACITORS

Whatever the requirement, there is an Aerovox capacitor to satisfy it. Your Aerovox distributor can supply your every need with a complete line of in-stock capacitors that are designed and manufactured to meet the highest possible reliability standards.

And when we say "A COMPLETE LINE" we include:

**ELECTROLYTIC CAPACITORS**

Twist-Prong Cans  
Tubular  
Miniaturs  
Wax Filled

**BYPASS CAPACITORS**

Radial & Axial Leads  
Dual Dielectric  
Straight Mylar

**CERAMIC CAPACITORS**

High Voltage  
Temperature Compensating  
General Purpose Discs  
Tubulars

**MICA CAPACITORS**

Molded  
Axial Lead  
Dipped Radial Lead

Your local Aerovox distributor offers sure, one-stop service for all capacitor replacement. Buy the best—buy Aerovox.




**AEROVOX CORPORATION**

DISTRIBUTOR DIVISION NEW BEDFORD, MASS.

*Technical Leadership - Manufacturing Excellence*

*Circle 50 on literature card*

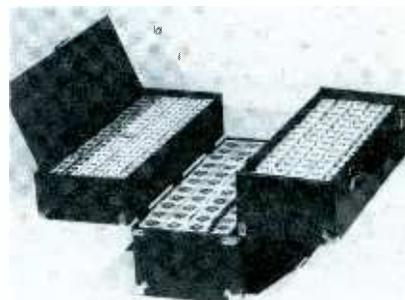

(124)

**New Caddy**

A rugged but attractive luggage-type service case capable of holding 365 tubes is available from **General Electric Co.** Covered in rust-brown armored vinyl, the ETR-3915 service case has a strong, durable Bakelite handle. "Egg-crate" separators hold tubes in position, while a flexible curtain holds job tickets, alignment tools, and a characteristics booklet. Tools are carried in a separate covered compartment. The case features heavy nickel-plated steel hardware and snap locks. It is priced at less than \$30.



(125)

**360° Speaker System**

The Model KSC-3 speaker system is designed to permit the mid- and high-frequency speakers to radiate in a 360° pattern. This **KCS Systems, Inc.** system contains three speakers made by **SEAS of Norway**: a 10" woofer, a 6" mid-range, and a 3½" tweeter. A three-way

crossover network is included, and there are two potentiometers for balancing the volume of the mid- and high-frequency speakers to suit individual preference and room acoustics. In the American built cabinet (patent applied for), the tweeter and mid-range section is completely separated from the woofer section; the 360° dispersion is confined to the high and mid-range area.

Impedance is 8 ohms, power-handling capacity is 30 watts, and the frequency range is 30 to 20,000 cps. The cabinet measures 13" x 13½" x 29¾" and is finished in oiled walnut. Price of the KSC-3 is \$185. It is available from franchised distributors only.



(126)  
**Transistorized Vibrator  
Eliminator**

This 12-volt vibrator eliminator is designed by GC Electronics for CB-mobile and car radios. No tools are required for installation. The unit has no moving parts and is housed in an aluminum case to keep out dust. It oscillates with battery voltages as low as 5 volts. The eliminator operates over a temperature range of -50° to +180°F; its power capacity is sufficient for the maximum CB transmitter output authorized by the FCC. The unit is supplied with installation instructions and a list of CB sets in which it can be used to replace original equipment.

#### Solid-State CB Transceiver

The 12-channel **Hallcrafters** CB-12 fully transistorized CB transceiver includes a three-stage transmitter rated for full authorized power. The receiver employs a dual-conversion superheterodyne circuit; sensitivity is less than 1.0 uv for 10 db S/N. Audio output is 3.5 watts. Battery



### New RCA WR-64B Color Bar / Dot / Crosshatch Generator



## THE ESSENTIAL COLOR-TV TEST INSTRUMENT

Now in a new model with more features for greater stability and versatility

- Crystal-controlled RF oscillator for stable picture carrier.
- Three additional crystal oscillators are used to produce the sound carrier, color sub-carrier signal and the three patterns.
- Convenient front-panel gun killing switches to aid individual gun testing as well as convergence and purity adjustments.
- Sound-carrier signal unmodulated for accurate adjustment of fine tuning control of TV receiver. . . accurate setting of the fine-tuning control is essential for checking the performance of the receiver.
- Generates all necessary test patterns: COLOR BARS for checking and aligning color circuits; CROSSHATCH for adjusting vertical and horizontal linearity and raster size; and DOTS for accurate convergence.
- Color-phasing adjustments may be made with this instrument in the home without a scope.
- The standard of the Color-TV servicing industry: much of the practical information available for trouble-shooting color circuits is based on the RCA Color Bar Generator. Only \$189.50\*

ASK TO SEE IT AT YOUR AUTHORIZED RCA TEST EQUIPMENT DISTRIBUTOR

\*Optional distributor resale price. All prices subject to change without notice. Prices may be slightly higher in Alaska, Hawaii and the West.

RCA Electronic Components and Devices, Harrison, N. J.



The Most Trusted Name in Electronics

meet the new  
**WINEGARD  
 HOT-SHOT**  
 Super Compact All-Band  
 (UHF, VHF, FM)  
 Color Antenna...

*Eliminates Ghosts  
 Better than any  
 other Metropolitan  
 Type Antenna*

Here's the antenna that replaces Conicals, Twin Vees, In-Lines and all Indoor antennas. It's Hot-Shot, the new antenna from Winegard that outperforms the others... yet lists for only \$8.80!

Designed specifically for all-band (UHF, VHF, FM) reception in metropolitan areas, Hot-Shot has a very high front to back and front to side ratio to eliminate ghosts more effectively than other antennas. Works on all bands to deliver life-like color, sharper black and white and distortion-free FM stereo. Easily installed, too, on roofs or in attics—you work with just one download. It even has Winegard's new Gold Vinylized finish to triple antenna life.

So don't give your customers the limited performance of an indoor or old fashioned outdoor antenna when for no more money than indoor types (\$8.80), you can give them the outstanding results of the all new Winegard Hot-Shot.

Ask your distributor or write today for Hot-Shot Fact-Finder #241. It's the hottest new all-band antenna for metropolitan and suburban reception areas.

## **Winegard Co.**

ANTENNA SYSTEMS

3000 Kirkwood • Burlington, Iowa

Circle 52 on literature card



(127)

drain is .2 amp on receive, 1 amp on transmit. Chassis dimensions are 2 $\frac{3}{8}$ " x 6" x 9 $\frac{1}{2}$ ".

The CB-12 is supplied complete with push-to-talk microphone, one set of crystals, and mobile-mounting kit. List price is \$179.95. A pedestal AC power supply, the P-12, is available at \$34.95 for base-station installations.



(128)

### **Desoldering Tool**

Solder may be melted and vacuumed away from connections of printed circuit boards in a one-hand operation with the Ungar Electric Tools "Hot-Vac." The complete assembly, Model No. 7800, includes the No. 777 Clean Room handle, a standard Ungar heating unit, the No. 7806 Hot-Vac tip, and a rubber aspirator bulb.

No tinning is necessary because the tip has a coating that resists solder and thus prevents clogging of the tip orifice. A stainless-steel check valve is provided in the tip to prevent molten solder from being drawn into the aspirator bulb. The tip is set at an angle so that the tool can be held as a pencil iron normally is held. After each desoldering operation, molten solder in the collector is discharged into a metal waste receptacle by depressing the rubber bulb.

# new SAMS BOOKS

## Know Your Signal Generator



by Robert G. Middleton. The newest book by this popular author offers, in his inimitably clear style, full and practical coverage of signal generators from A to Z—theory, operation, and applications. Explains basic principles of all types of signal generators; proceeds to explain generator accuracy, calibration, modulation, measurement of output voltages, harmonic amplitudes, and many other considerations. Includes dip meters, analyzers, radio test sets, and uhf and supersonic generators. Special

chapter on FM stereo multiplex signal generators. Invaluable for service technicians, apprentices, hams, and hobbyists. 144 pages; 5 1/2 x 8 1/2". \$250  
Order KOG-1, only

## Two-Way Mobile Radio Maintenance (New 2nd Ed.)

by Jack Darr. This newly revised and updated guidebook includes coverage of the latest transistorized 2-way equipment. Here is a complete and extremely practical field servicing handbook, a valuable guide to planning, installing, and maintaining all types of 2-way mobile radio systems. The author's own first-hand experience gets you right to the heart of how to do the job the quickest and best way. Written in easy-to-understand language; illustrated with many on-the-job photos of 2-way equipment. 256 pages; 5 1/2 x 8 1/2". Order TWD-2, only \$495

## Second Big Printing! Color TV Guidebook

A special Howard W. Sams publication—the most complete and authoritative guide to color TV, servicing techniques, equipment required, and related subjects. General information includes outlook for color TV manufacturers, broadcasting networks, and technicians. Specific sections deal with starting a color TV service business, troubleshooting and repair techniques, antennas, color tube stocking, transistorized color TV, small-town color TV problems, new circuits and developments; building a color TV kit, and much more. The biggest dollar's worth of useful, practical color TV data available. 8 1/2 x 11". Order PFR-1, only \$100

## Transistor Radio Servicing Made Easy (New 2nd Ed.)

by Wayne Lemons. Latest, completely updated edition of this practical how-to-do-it book. Explains only what you need to know to repair transistor radios (now including FM) with maximum profit. The on-the-job experience presented makes it the only book of its kind available. From the introductory chapter through the step-by-step explanations of bench-tested troubleshooting procedures, the text is written in servicemen's language. Explains how to find causes of noises, squeals, poor sensitivity and distortion; how to substitute transistors and check circuit performance; how to minimize "hard-to-find" parts problems. Includes a complete new chapter on FM transistor circuits. 144 pages; 5 1/2 x 8 1/2". Order TRE-2, only \$250

## Technical Speller & Definition Finder

by Aetna Miles. A practical reference, using an entirely new concept — gives the correct spelling, plus convenient sources for definitions and additional information on approximately 50,000 technical terms. Essential for secretaries, librarians, educators, authors, technicians, engineers, and others with scientific interests. Handy alphabetical listing has accurate spelling and definition key. Includes acronyms and their definitions. Trademarks are identified, and the proper spelling and typing form is shown. 288 pages; 5 1/2 x 8 1/2". Order SDH-1 (hardbound), only \$595  
Order SDS-1 (softbound), only 4.95

## HOWARD W. SAMS & CO., INC.

Order from your Sams Distributor today, or mail to Howard W. Sams & Co., Inc., Dept. PF-8  
4300 W. 62nd Street, Indianapolis, Ind. 46206

Send me the following books:

- KOG-1     PFR-1     SDH-1  
 TWD-2     TRE-2     SDS-1

Send FREE Sams Booklist. \$\_\_\_\_\_enclosed

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

My Distributor is \_\_\_\_\_

IN CANADA: A. C. Simmonds & Sons, Ltd., Toronto 7

## INDEX TO ADVERTISERS

AUGUST, 1965

ATR Electronics, Inc. ....	13
Aerovox Corp. ....	70
Amphenol-Borg Corp. ....	19
Antenna Specialists Co. ....	44
Atlas Sound ....	69
B & K Mfg. Co. ....	15
Div. of Dynascan Corp. ....	
Belden Mfg. Co. ....	23
Berns Mfg. Co., Inc., The ....	52
Bussmann Mfg. Div. ....	20, 21
Castle TV Tuner Service ....	16
Channellock, Inc. ....	42
Cleveland Institute of Electronics ....	17
Delco Radio Div. ....	18
EICO Electronic Instrument Co., Inc. ....	Cover 2
Electronic Chemical Corp. ....	44
Electronics Communications, Inc. ....	46
Enterprise Development Co. ....	44
Finney Co. ....	22
General Radiotelephone Co. ....	66
Harmon-Kardon ....	66
Hickok Electrical Instrument Co. ....	12, 38
IEH Mfg. Co., Inc. ....	68
Lectrotech, Inc. ....	69
Littelfuse, Inc. ....	Cover 4
Ohmite Mfg. Co. ....	13
Perma-Power Co. ....	56
Philco Corp. ....	67
Planet Sales Co. ....	56
Precision Tuner Service ....	42
Quality Tuner Service ....	52
RCA Electronic Components & Devices ....	45, 63, 71, Cover 3
RCA Sales Corp. ....	14
Sams, Howard W. & Co., Inc. ....	41, 73
Sarkes Tarzian, Inc. ....	9
Seco Electronics, Inc. ....	65
SENCORE, Inc. ....	47, 49, 51, 53, 55, 57
Sonotone Corp. ....	54
Sprague Products Co. ....	11, 43
Switchcraft, Inc. ....	46
Sylvania Electric Products, Inc. ....	58
Weller Electric Corp. ....	48
Windsor Electric Co. ....	65
Winegard Co. ....	64, 72, 73
Workman Electronic Products, Inc. ....	40
Xcelite, Inc. ....	52
Zenith Radio Corp. ....	35

# Winegard Dealer of the Month

No. 39 of a series

Don Shater says: "After many years of experimentation with the top lines of antennas, we've gone to Winegard exclusively."



Winegard salutes  
**RECEPTION UNLIMITED,**  
San Jose, California.

Don Shater is an old hand at TV antenna installations, and since going into business for himself early in 1963, he has carried Winegard antennas exclusively. "Our primary reason for choosing Winegard antennas was simply that they perform better... even under the most adverse conditions. In addition, the structural design lends itself to long life and good appearance. There was one more very important factor. To our knowledge, there has never been an instance when the Winegard Company did not back up its famous Gold Bond Guarantee."

When Reception Unlimited went into business, they decided to build a reputation for carrying only the finest products and delivering only outstanding workmanship. Winegard was part of that plan which, today, has become a reality. Says Don, "We are now privileged to install Winegard antennas exclusively on all the installations for Macy's of California and Breuner's Home Furnishers in San Jose and Campbell."

The confidence Don Shater has shown in Winegard comes from installing Winegard Products and seeing them in action. He is one more important Service Dealer who knows Winegard's standards of excellence first hand.

# Winegard Co.

Antenna Systems

3000 Kirkwood • Burlington, Iowa

Circle 54 on literature card

August, 1965/PF REPORTER 73



# FREE Catalog and Literature Service

\*Check "Index to Advertisers" for further information from these companies.

Please allow 60 to 90 days for delivery.

## ANTENNAS AND ACCESSORIES

- 56. **ALLIANCE** — Colorful 4-page brochure describing in detail all the features of *Tenna-Rotors*.
- 57. **ANTENNACRAFT** — Literature on new 75-ohm TV and FM antennas for use with RG-59/U coaxial cable.
- 58. **FINNEY**—Catalog 20-322 showing newest addition to the All-Band Color-Ve-Log series of UHF-VHF-FM antennas.\*
- 59. **JFD**—Literature on complete line of log-periodic antennas for VHF, UHF, FM, and FM stereo. Brochure showing converters, amplifiers, and accessories; also complete '64-'65 dealer catalog plus dealer wall chart of antenna selection by area.
- 60. **MOSLEY ELECTRONICS** — Illustrated catalog giving specifications and features on large line of antennas for Citizens band, amateur, and TV applications.
- 61. **MULTITRON** — Illustrated literature on FM-stereo antenna No. MA-44, multi tuner Model M-11, and Minitenna No. MINI-4T.
- 62. **PARKER**—Bulletin describes new *Da Vinci* indoor UHF antenna.
- 63. **TRIO**—Brochure on installation and materials for improving UHF transistor reception.
- 64. **WINEGARD**—Catalogs describing new: Conicals, UHF antennas, transistor pre-amplifiers, noise filter, transformer package, couplers, and Chroma-Tel line.\*
- 65. **ZENITH** — Information bulletins on antennas, rotors, batteries, tubes, loudspeakers, record changers, and wire and cable.\*

## AUDIO & HI-FI

- 66. **ADMIRAL** — Folders describing line of '65 equipment; includes black-and-white TV, color TV, radio, and stereo hi-fi.
- 67. **ACOUSTIC RESEARCH** — New products catalog including latest speakers.
- 68. **BENJAMIN** — Descriptive literature on Stereo 200, Stereo 200 FM, and Benjamin 208 speaker systems.
- 69. **EUPHONICS** — Jumbo 8-page 4-color brochure introducing Euphonics Mini-comic semiconductor stereo phono cartridge. This graphic presentation also covers principles and history of disc recording, stereo theory, cartridge design factors, and characteristics of different cartridges.
- 70. **GC ELECTRONICS** — New up-to-date phono wall chart, No. FR-250-G, including new drives and hundreds of newly cross-referenced models.\*
- 71. **KARG** — Data sheets for Model X-1 transistor stereo amplifier and Model T-9 stereo FM tuner.
- 72. **JENSEN** — 24-page catalog, No. 165-K, illustrates and describes speakers and speaker system kits.
- 73. **NUTONE**—Two full-color booklets illustrating built-in stereo music systems and intercom-radio systems. Includes specifications, installation ideas, and prizes.
- 74. **OAKTRON** — "The Blueprint to Better Sound," an 8-page catalog of loudspeakers and baffles giving detailed specifications and list prices.
- 75. **OXFORD TRANSDUCER**—Product information bulletin describing complete line of loudspeakers for all types of sound applications including replacements for public address and intercom systems.
- 76. **PERMA-POWER**—Literature describing Model S-2000 *The Diplomat* transistorized attache-case public address system which operates on flashlight batteries.\*

- 77. **QUAM-NICHOLS** — Catalog 65 listing replacement speakers for public address systems, hi-fi, auto radio, and radio-TV applications.
- 78. **RANGER**—Folder Form No. RA-65-13 describes under-dash mounted *Stereo-Magic* car radio reverberation unit.
- 79. **SAMPSON** — Full-color catalog pages showing new line of Waltham transistor radios, tape recorders, and portable televisions.
- 80. **SONOTONE**—Specification sheet SAH-97 on new RM-1 *Sonomaster* speaker system.\*
- 81. **TENATRONICS** — Descriptive literature on new line of solid-state 110 volt AC table model radios.

## COMMUNICATIONS

- 82. **EICO**—Data sheet on Model 753 *Tri-Band* transceiver and other ham gear, plus full-line catalog.\*
- 83. **LAFAYETTE**—New 512-page 1966 catalog 660 describing electronics equipment for home, hobby, and industry.
- 84. **PEARCE-SIMPSON** — Specification brochure on IBC 301 business-band two-way radio, *Companion II*, *Escort*, and *Guardian 23* Citizens-band transceivers.

## COMPONENTS

- 85. **BUSSMANN**—Bulletin SFUS, a 12-page booklet listing the complete line of BUSS and FUSELTON small dimension fuses by size, type, and list prices—also indicates proper fuseholder.\*
- 86. **CLAROSTAT** — 1965 full-line catalog covering switches, potentiometers, and resistors.
- 87. **J-B-T INSTRUMENTS**—General catalog 565; bulletins on reed relays, oscillator controls, toggle switches, and subminiature rotary-lever switches.
- 88. **RAWN** — Detailed instruction sheets on TV knob and plastic repairs with *Plas-T-Pair*.
- 89. **SWITCHCRAFT**—New product bulletin No. 152 describes: series H-100 and H-200 "HI-D" switch, and series D.A. "DATA-SWITCH".\*
- 90. **TRIAD**—1965 replacement catalog and television guide on transformers for television, hi-fi, home and auto radios.
- 91. **WORKMAN**—Coil catalog No. 109 and cross reference for replacement of antenna coils, IF transformers, RF chokes, linearity coils, and others for FM radios, tape recorders and color TV receivers.\*

## SERVICE AIDS

- 92. **CASTLE**—How to get fast overhaul service on all makes and models of television tuners is described in leaflets. Shipping instructions, labels, and tags are also included.\*
- 93. **CBC INDUSTRIES**—Literature describing power selector boxes Model SS-G1 (fused) and Model SS-GD-CB (with circuit breaker). Each outlet on box has control switch.
- 94. **INJECTORALL**—1965 catalog No. 65 on electronic chemicals.
- 95. **LUBRA CLEAN** — Information on new tuner cleaner.
- 96. **PRECISION TUNER**—Literature supplying information on complete, low-cost repair and alignment services for any TV tuner.\*
- 97. **YEATS** — The new "back-saving" appliance dolly Model 7 is featured in a four-page booklet describing feather-weight aluminum construction.

## SPECIAL EQUIPMENT

- 98. **ATR** — Descriptive literature on selling new, all-transistor *Karadio* Model 707, having retail price of \$29.95. Other literature on complete line of DC-AC inverters for operating 117-volt PA systems and other electronics gear.\*
- 99. **GREYHOUND** — The complete story of the speed, convenience, and special service provided by the Greyhound Package Express method of shipping with rates and routes.
- 100. **SPRAGUE** — Circular M-853 describes SK-1, SK-10, SK-20, and SK-30 *Sup-presskits* for vehicles with alternators or DC generators.\*
- 101. **VOLKSWAGEN** — Large, 60-page, illustrated booklet, "The Owner's Viewpoint," describes how various VW trucks can be used to save time and money in business enterprises, including complete specifications on line of trucks.

## TECHNICAL PUBLICATIONS

- 102. **CLEVELAND INSTITUTE OF ELECTRONICS**—Free illustrated brochure describes electronic slide rule with four lesson Instruction Course and grading service.\*
- 103. **RCA INSTITUTES** — 64-page book, "Your Career in Electronics" detailing home study courses in telecommunications, industrial electronics, TV servicing, solid-state electronics, and drafting. Preparation for FCC license, and courses in mobile communications and computer programming also available.\*
- 104. **HOWARD W. SAMS** — Literature describing popular and informative publications on radio and TV servicing, communications, audio, hi-fi, and industrial electronics, including special new 1965 catalog of technical books on every phase of electronics.\*

## TEST EQUIPMENT

- 105. **B & K**—Bulletin 108-R on Model 801 Capacitor Analyst. Bulletin No. 124-R on Model 1240 color generator. Catalog AP-21R describing uses for and specifications of Model 1076 Television Analyst, Model 1074 TV Analyst and Color Generator, Model 700 and 600 *Dyna-Quik* Tube testers, Model 445 CRT Tester-Rejuvenator, Model 960 Transistor Radio Analyst, Model 360 *V-O-Matic* VOM, Model 375 *Dynamic* VTVM and other test instruments.\*
- 106. **HICKOK**—Specification sheets on Model 662 installer's color generator. Model 677 wideband scope, Model 470A uni-scale VTVM, and Model 799 *Mustang* tube tester.\*
- 107. **JACKSON** — Complete catalog describing all types of electronic test equipment for servicing and other applications.
- 108. **LECTROTECH** — Bulletins on *Meter-gards*, *Lectrocels*, Models V-6 and V-7 color-bar generators, and Model T-100 horizontal-deflection circuit meter.\*
- 109. **MERCURY**—Catalog describing full line of electronic test equipment.
- 110. **PRECISE**—8-page catalog describing kit and factory-wired test equipment.
- 111. **SECO**—New colorful folder describing 20 test instruments including tube testers.\*
- 112. **SENCORE** — Information on all solid-state color generator Model CG135 plus full line catalog.\*
- 113. **SIMPSON** — Complete 16-page brochure on entire line of electronic test equipment; also, catalog on line of panel meters.
- 114. **TRIPLETT** — New catalog No. 47-T covering the company's entire line of test equipment.

## TOOLS

- 115. **ARROW** — Literature outlining "How, When, and Where" to use 3 staple gun tackers.
- 116. **ENTERPRISE DEVELOPMENT**—Time-saving techniques in brochure from Endeco demonstrate improved desoldering and resoldering techniques for speeding up and simplifying operations on PC boards.

## TUBES & TRANSISTORS

- 117. **SEMITRONICS** — Bulletins describing new No. TV1000 UHF transistor and No. CTV358 color crystal.

RCA announces a complete new line of color television picture tubes for the replacement market... **Hi-Lite.** RCA Hi-Lite tubes are all-new. Glass. Gun. The works! Rare-earth phosphors applied by RCA's advanced screening process create vivid, natural colors, and color picture brightness unsurpassed in the color TV industry! **Better black-and-white pictures, too!** RCA's Hi-Lite line includes 19-inch and 25-inch rectangular and 21-inch round tube types. **RCA Hi-Lite Color Tubes lead the color parade.**

**Join it!**


RCA ELECTRONIC COMPONENTS AND DEVICES, HARRISON, N. J.



**The Most Trusted Name in Electronics**


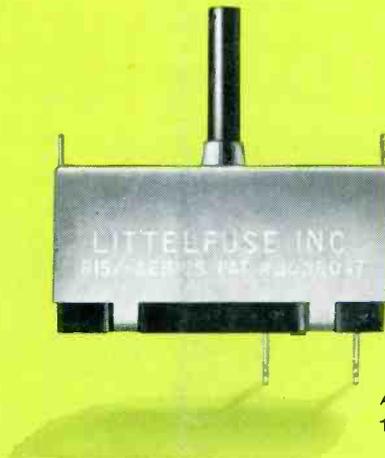
# Introducing a Complete Line of Littelfuse Quality Circuit Breakers



Actual Size  
1 $\frac{3}{4}$ " x 1 $\frac{7}{16}$ " x  $\frac{1}{2}$ "

## Exact replacement from factory to you

Designed for the protection of television receiver circuits, the Littelfuse Manual Reset Circuit Breaker is also ideally suited as a current overload protector for model railroads and power operated toy transformers, hair dryers, small household appliances, home workshop power tools, office machines, small fractional horsepower motors and all types of electronic or electrical control wiring.

# LITTELFUSE

DES PLAINES, ILLINOIS

Circle 55 on literature card