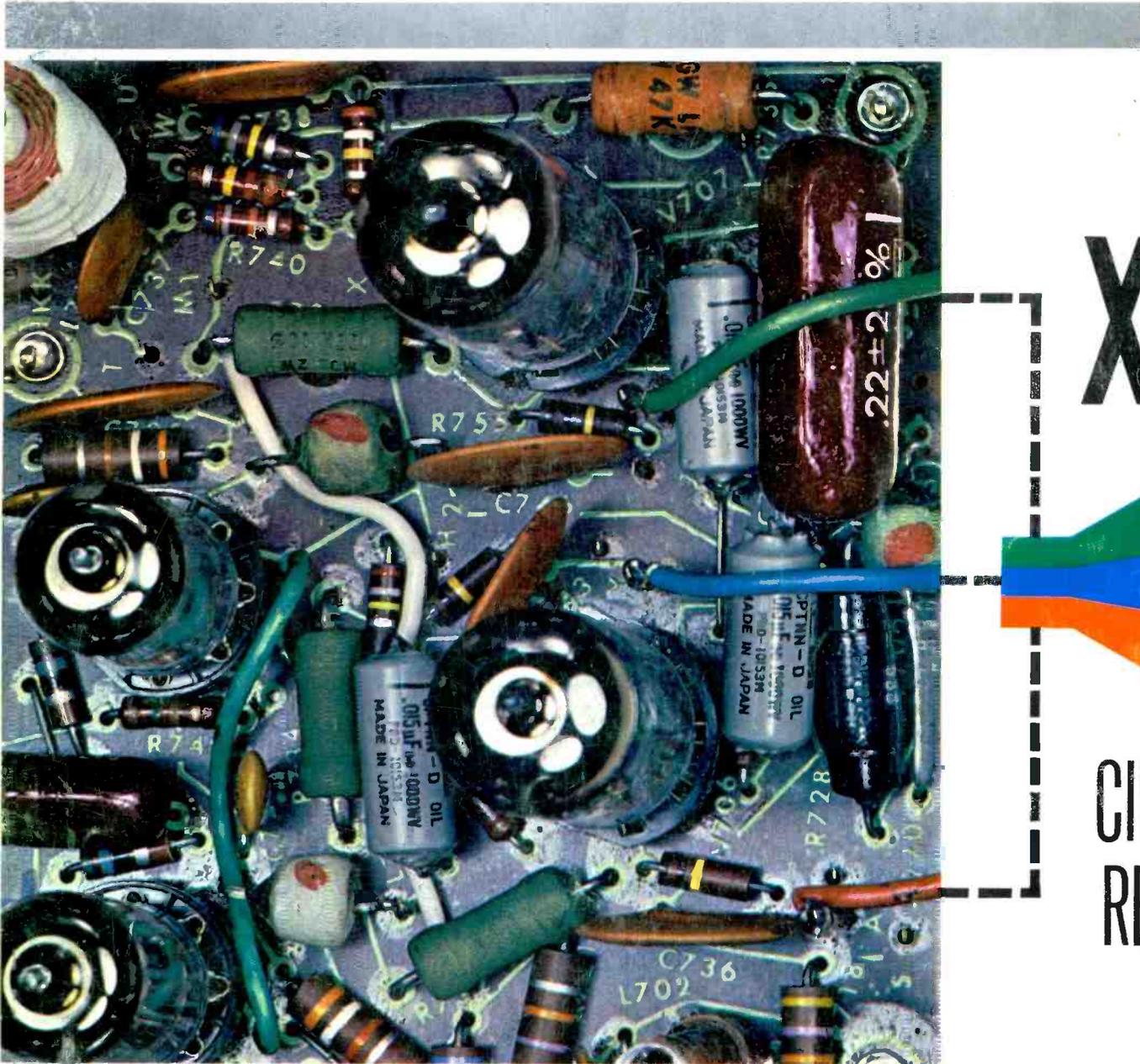



PF Reporter™

PHOTOFACT

the magazine of electronic servicing



XYZ

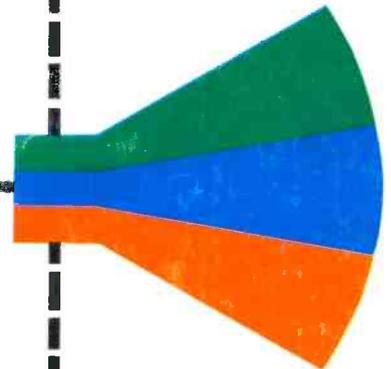

CIRCUIT REPAIR

1A SL 4279 1268
 WM. M. DAVIS
 RADIO & TV SERVICE
 118 RIVERSIDE AVE.
 CANON CITY, COLO.

- Chasing Troubles in Stereo-On Indicators
- Locus of the Focus
- Keyed AGC
- Leave Those Parts in the Circuit
- New Tube and Transistor Data
- Stereo-FM Station Guide





amazing new
engineering
achievement from
JERROLD!

82-CHANNEL Coloraxial™ Cable

**Delivers unheard-of low loss and
top 82-channel color performance**

At last, a TV transmission line that gives you the right answer to all-channel and color reception problems. Lets you install *TV studio quality* reception in homes, TV shops, appliance stores and MATV systems.

This remarkable, *low-loss* cable comes in ready-to-install, 50 and 75-foot sweep-tested coils with factory attached connectors. Saves you time and effort! In many areas you can use a smaller antenna because loss is so low. And 82-Channel Coloraxial Cable is actually less expensive than some twinlead.

If the *bugaboo* of coax loss has held you back—look for a new excuse. 82-Channel Coloraxial Cable causes *less loss* than shielded twinlead, and it's comparable to new twinlead in a typical home installation. What's more, twinlead losses increase with age—coax losses remain constant! And Coloraxial cable *lasts 10 times longer* than twinlead.

For full profit, easy installation *without* callback, try Jerrold's *low-loss* Coloraxial cable on your next antenna installation. For the best customer reception, offer the best TV reception with Coloraxial Cable.

JERROLD


JERROLD ELECTRONICS CORPORATION

Distributor Sales Division

401 Walnut Street, Philadelphia, Pa. 19106

See us at the NEW SHOW, Booth 2411-2413 ... enjoy our hospitality in Suite 1607, San Francisco, Hilton

Circle 1 on literature card

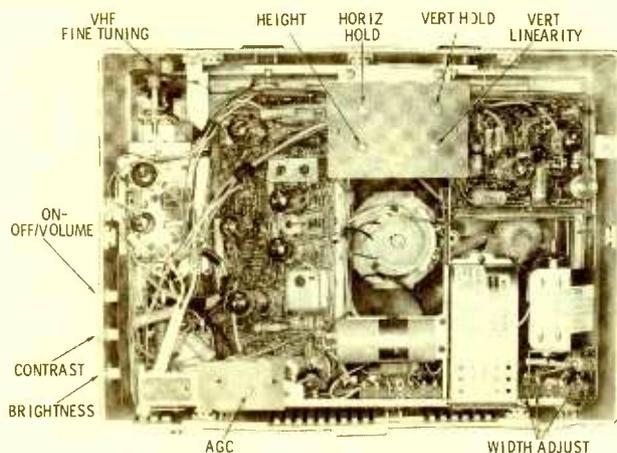

Arvin Model 65K28
Chassis—1.87803




Here is a late-production version of Arvin's 16" B-W portable. Manufactured in Japan by Matsushita, the set contains an AW40-12 picture tube and two vertically mounted circuit boards. A total of 12 tubes and 10 semiconductors are used including four transistors.

A horizontal oscillator circuit change has placed the horizontal frequency centering adjust in series with the horizontal hold control. Both controls are now connected between the AFC cathode and the oscillator grid.

The transformerless low-voltage supply uses two silicon rectifiers to develop B+. A 1.6-amp line fuse provides protection for the low-voltage supply and the series filament string. A 4.7-ohm fusible resistor provides additional surge protection for the rectifiers.

Focusing is accomplished by connecting the lead from pin 4 of the picture tube to one of four taps on the left side of the sweep circuit board. A jumper arrangement for adjusting the horizontal width is located on the lower right side at the rear of the set.

The VHF channel selector and fine tuning control are located on the left side of the cabinet top. The VHF fine tuning uses a separate control which adjusts the slug of each oscillator coil through a belt-driven gear shaft. The VHF tuning control is located on the front bottom left of the cabinet. Brightness, contrast and on-off/volume are situated on the bottom left side of the cabinet. Height, vertical hold, horizontal hold, and vertical linearity controls are grouped together at the top rear of the set. AGC control is also located on the rear of the set.

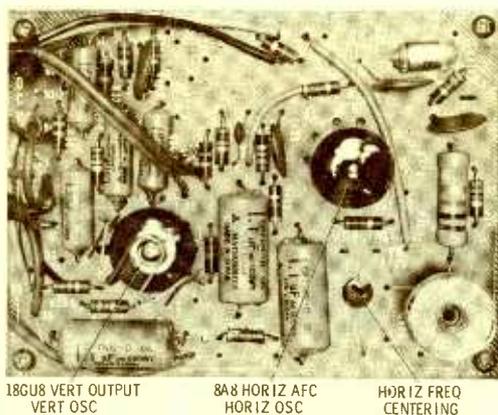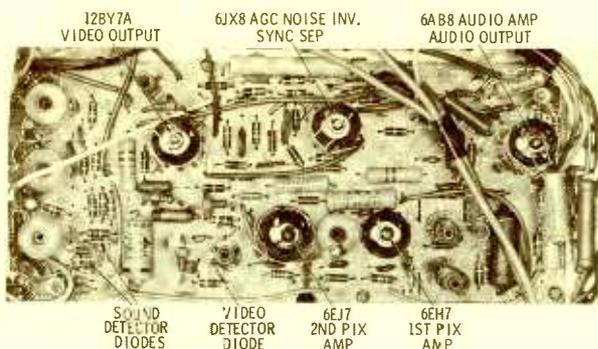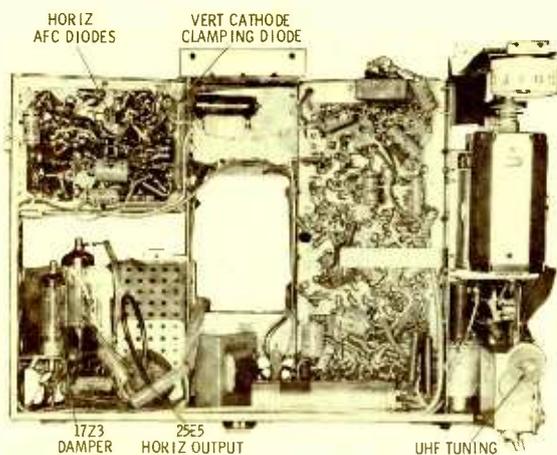



General Electric Model M1937ACL Chassis—CTCA428





The 21" color console pictured here employs a 21FJP22 picture tube and a transformer-powered chassis which has changed little from previous color chassis. The number of tubes used on the main chassis has been reduced to 20 by the use of five compactrons.

A 6BH11 double-triode-pentode compactron serves the horizontal oscillator, reactance, and discharge circuits. Another compactron, a double-pentode 6AL11, is used in the sound demodulator and audio-output stages. The vertical-oscillator and vertical-output stages share a double-triode 6FM7 compactron. Other compactrons used are a 3AT2 as the high-voltage rectifier and a 6BE3 diode in the damper circuit.

A 6LF8 triode-pentode is used in the first and second video amplifiers in place of a 6AW8A triode-pentode. The horizontal output tube has also been changed, with a 6JS6A pentode replacing the 6HF5 pentode previously used. The 6JS6A suppressor grid is grounded externally instead of connected internally to the cathode, as in the 6HF5.

A full-wave voltage doubler is used in the low-voltage power supply. A reset-type circuit breaker provides B+ overload protection. The main parallel filament string is protected by a fuse wire.

A zener diode, mixer diode, and transistor oscillator make up the solid-state UHF tuner. An all-channel tuning system provides illuminated channel indication for both VHF and UHF channels and in addition, features a single control for VHF fine tuning or UHF tuning. VHF fine tuning involves pulling the spring-loaded knob outward and turning it. The knob returns to its original position when released and is then used for UHF tuning.

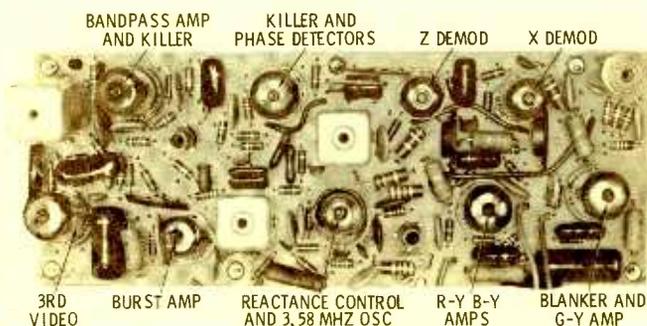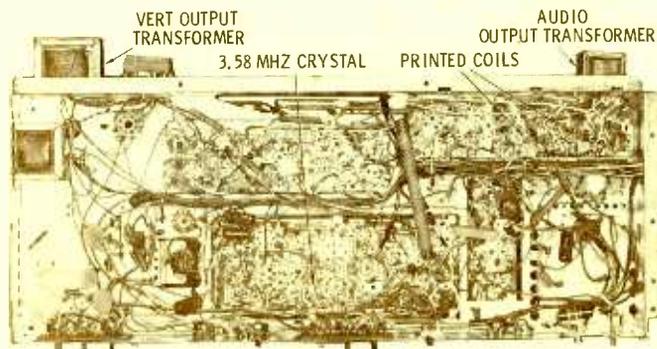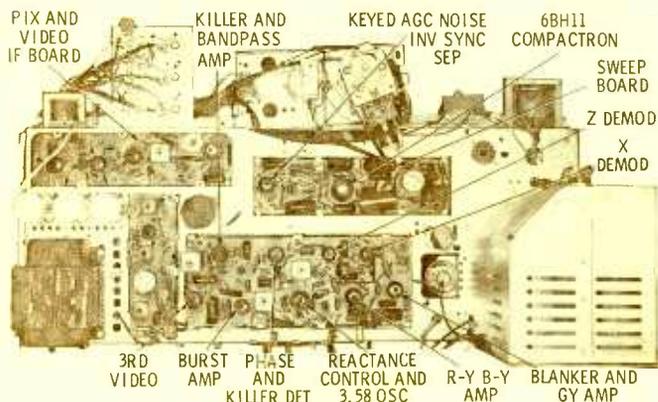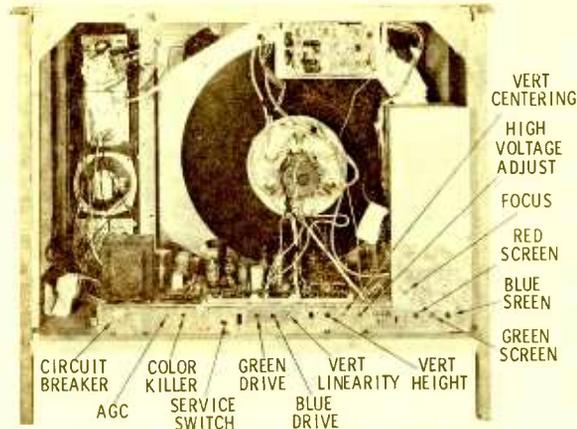



RCA Model—FG525E, W
Chassis—CTC19A


The 19" table model color set shown above is housed in a vinyl-covered metal cabinet and uses a 90° rectangular 19EYP22 picture tube. Two circuit boards and a total of 23 tubes are used in the new compact chassis.

6GH8A triode-pentodes are used exclusively for all functions in the chroma circuits. The triode section of one 6GH8A is used as the first video amplifier, with the color and sync signals taken off the grid/cathode circuit of this stage and fed to the pentode section of the same 6GH8A, which serves as the sync, AGC, and chroma amplifier.

A new tube type, a 6KM6 pentode, is used in the horizontal-output stage. Other tube changes involve the replacement of the 6EW6 pentode normally found in the sound IF with a 6JC6 pentode, and the use of a 2AV2 as the focus rectifier and a 6BS3 in the damper circuit.


The low-voltage power supply is a full-wave bridge circuit using four silicon rectifiers. A reset-type circuit breaker provides protection for the B+ line, and a wire-link fuse is used in the main filament line.

The VHF tuner has four stages and employs a 6DS4 *nuvistor* triode in the grounded-cathode RF stage. A 6KE8 triode-pentode serves as the mixer/oscillator. Two concentric tuning knobs operate both the VHF and transistorized UHF tuner. The VHF tuner has 13 detent positions, plus a UHF-IF position. VHF fine tuning is accomplished by pushing in on the large outer knob. The UHF tuner is mechanically linked to the VHF fine-tuning shaft and is engaged unless the tuning knob is pushed in.

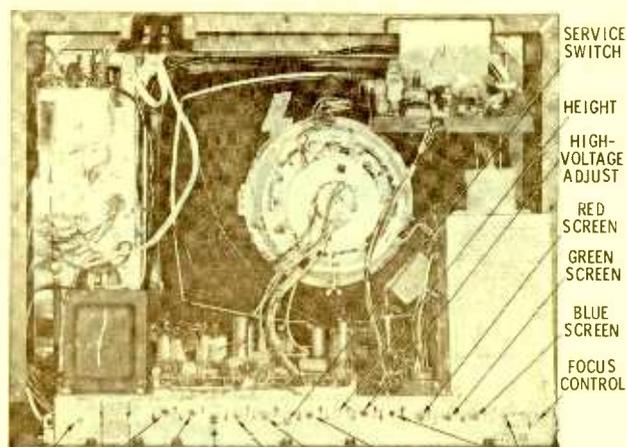


SERVICE SWITCH
HEIGHT
HIGH-VOLTAGE ADJUST
RED SCREEN
GREEN SCREEN
BLUE SCREEN
FOCUS CONTROL

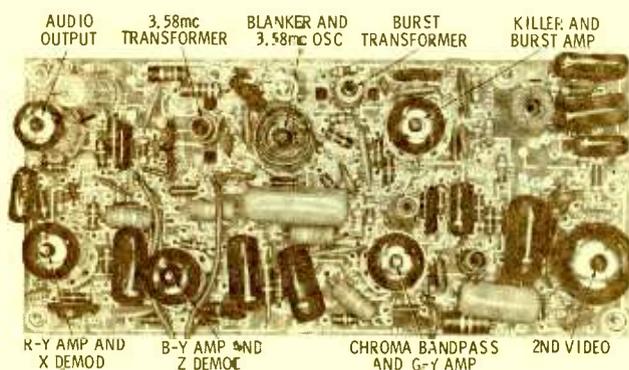CIRCUIT BREAKER AGC COLOR KILLER KINE BIAS GREEN DRIVE BLUE DRIVE VERT LINEARITY PINCUSHION ADJUST




AUDIO OUTPUT 3.58mc TRANSFORMER BLANKER AND 3.58mc OSC BURST TRANSFORMER KILLER AND BURST AMP

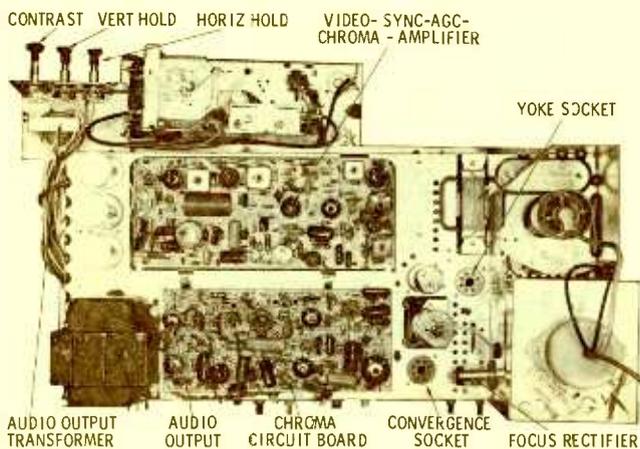R-Y AMP AND X DEMOD B-Y AMP AND Z DEMOD CHROMA BANDPASS AND G-Y AMP 2ND VIDEO




CONTRAST VERT HOLD HORIZ HOLD VIDEO- SYNC-AGC-CHROMA - AMPLIFIER YOKE SOCKET

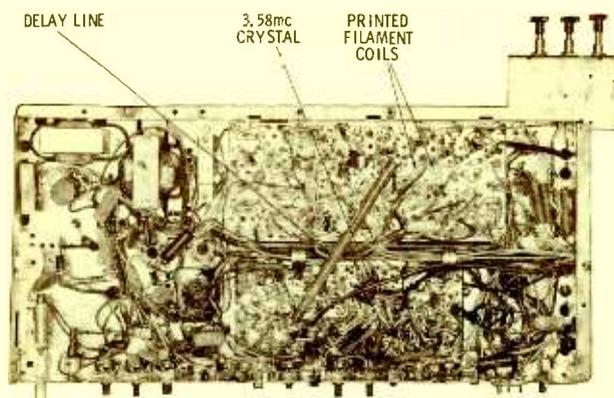AUDIO OUTPUT TRANSFORMER AUDIO OUTPUT CHROMA CIRCUIT BOARD CONVERGENCE SOCKET FOCUS RECTIFIER



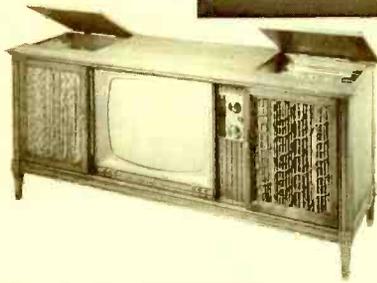DELAY LINE 3.58mc CRYSTAL PRINTED FILAMENT COILS



Sylvania Model 258C83
Chassis— DO2-6





The photo above shows Sylvania's 25" color model TV with AM-FM/-FM stereo radio/phono combination. Except for the larger picture tube, a rectangular RE25CP22, and a few circuit and tube changes, the TV chassis is not drastically changed from previous 21" color models.

One tube type has been changed: The vertical oscillator/vertical output stage now uses a 6LU8 triode-pentode in place of the 6GF7 dual-triode previously used. The pentode section is used in the vertical-output stage.

Two transistors and 16 solid-state diodes are used in the main TV chassis and UHF tuner. One transistor, a 2N306, is employed in the grounded emitter noise-gate circuit. The other transistor is used in the RF-oscillator stage of the UHF tuner.

The low-voltage power supply employs two silicon rectifiers in a full-wave voltage doubler. Overload protection is provided by a reset-type circuit breaker with the main filament string protected by a fuse wire.

The AM/FM tuner, stereo amplifier, and power supply circuits are transistorized and combined on one chassis. The tuner consists of a seven-stage FM circuit using a four-stage IF, and a four-stage AM circuit with two IF's. FM multiplex, AFC, and AVC facilities are also included. The stereo amplifier channels contain a preamp, driver, and power-output stages. Two separate transformer-powered rectifier circuits make up the power supply. One, a full-wave circuit, provides operating voltages for the tuner and power amplifier. The other, a half-wave circuit, produces 4.5 volts for the stereo-indicator circuit in the tuner.

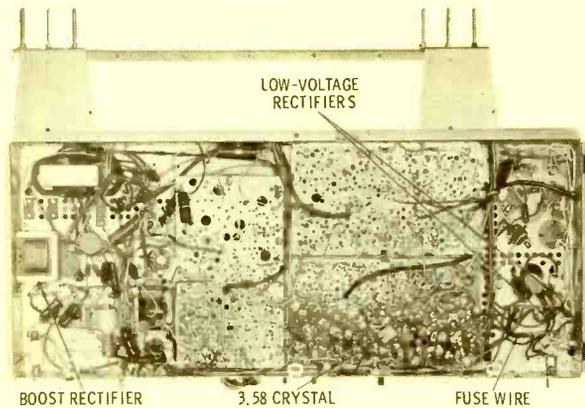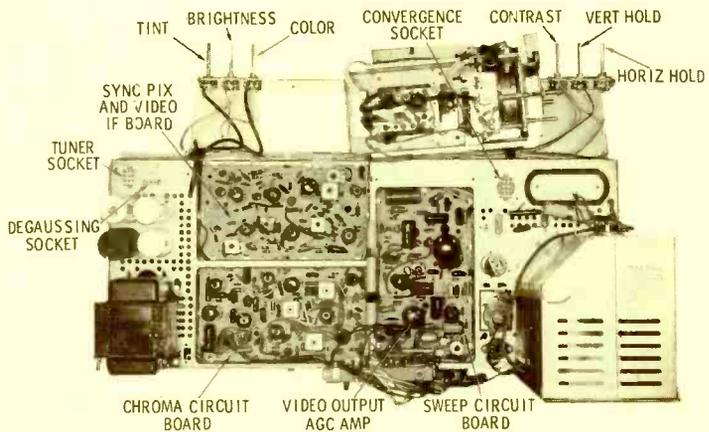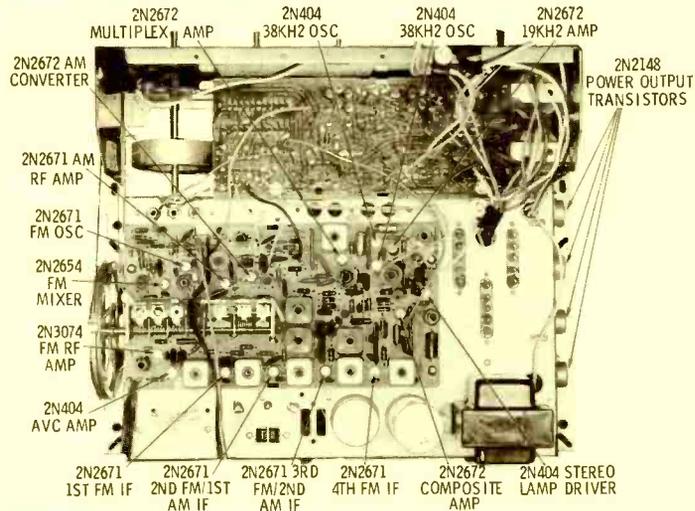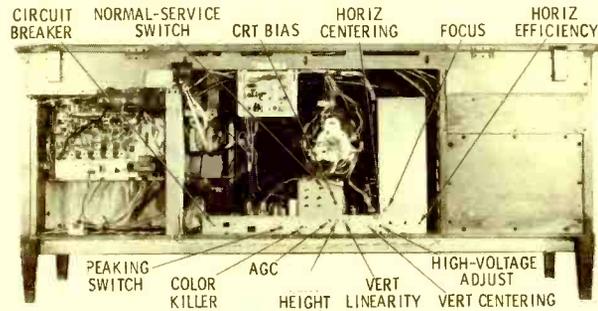

SEE PHOTOFACT Set 746, Folder 3

Mfr: Magnavox

Chassis No: C/U45-01-00 thru C/U45-04-00


Card No: MAG 45-1

Section Affected: Pix.

Symptoms: Video overload; cannot be remedied by reducing video signal with contrast control.

Cause: Defective video detector.

What To Do: Replace video detector X7.

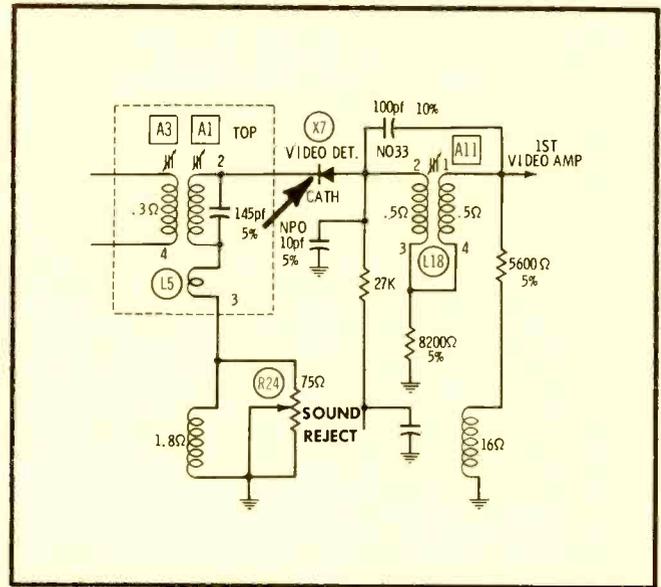

Mfr: Magnavox

Chassis No: C/U45-01-00 thru C/U45-04-00


Card No: MAG 45-2

Section Affected: Sync.

Symptoms: Unstable horizontal sync.

Cause: Defective or unmatched dual-diode section in horizontal-phase detector circuit.

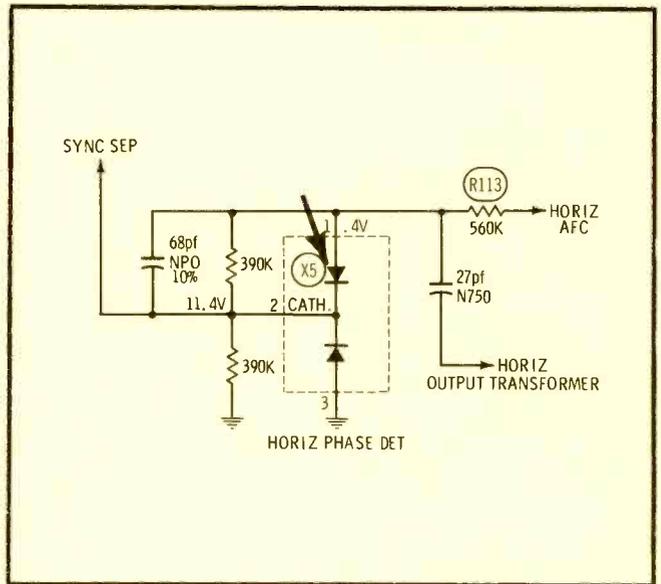What To Do: Replace horizontal-phase detector unit X5.



Mfr: Magnavox

Chassis No: C/U45-01-00 thru C/U45-04-00


Card No: MAG 45-3

Section Affected: Raster.


Symptoms: Raster out of focus.

Cause: Open focus rectifier.

What To Do: Replace focus rectifier X3.

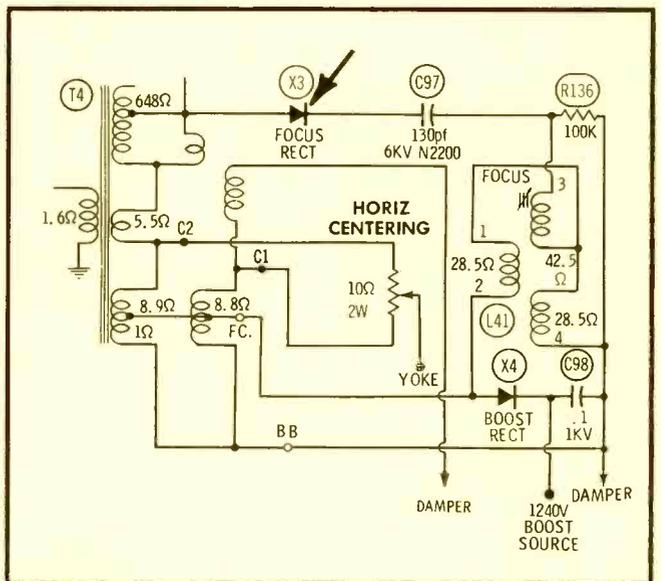

SEE PHOTOFACT Set 746, Folder 3

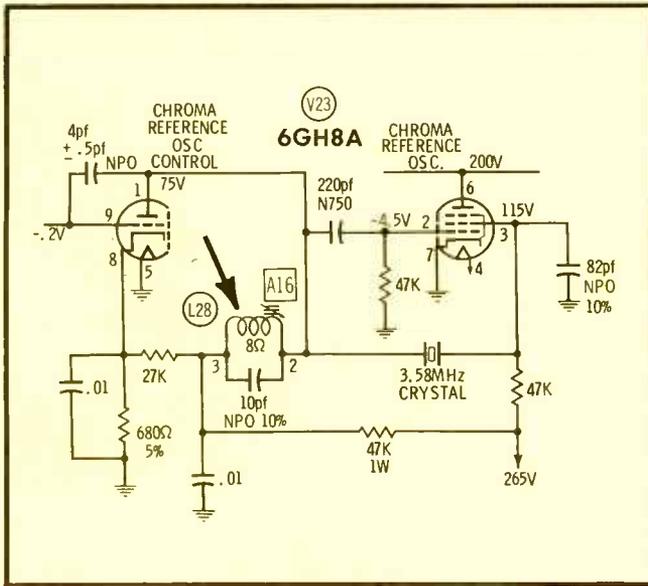

SEE PHOTOFACT Set 746, Folder 3

Mfr: Magnavox

Chassis No: C/U45-01-00 thru C/U45-04-00


Card No: MAG 45-4

Section Affected: Pix (color).

Symptoms: Color fades in and out; cannot be properly adjusted.

Cause: Poor soldered connections in reactance coil.

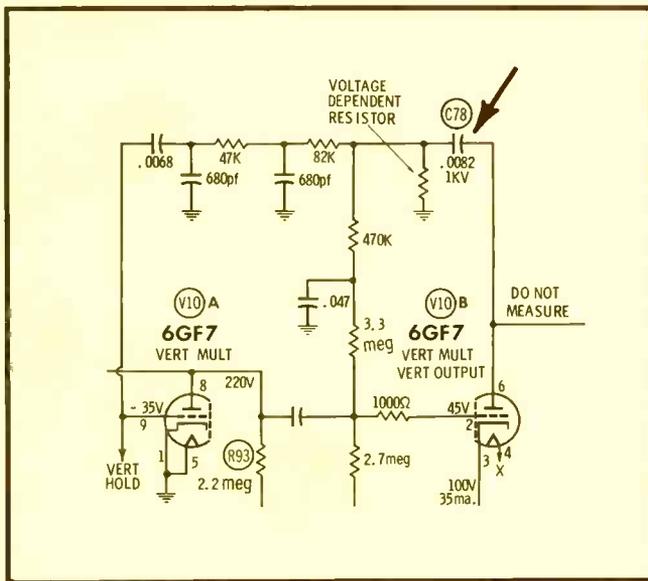What To Do: Resolder all leads in reactance coil L28.



Mfr: Magnavox

Chassis No: C/U45-01-00 thru C/U45-04-00


Card No: MAG 45-5

Section Affected: Raster.

Symptoms: No vertical sweep; low voltage at pin 8 of vertical multiplier.

Cause: Open feedback capacitor.

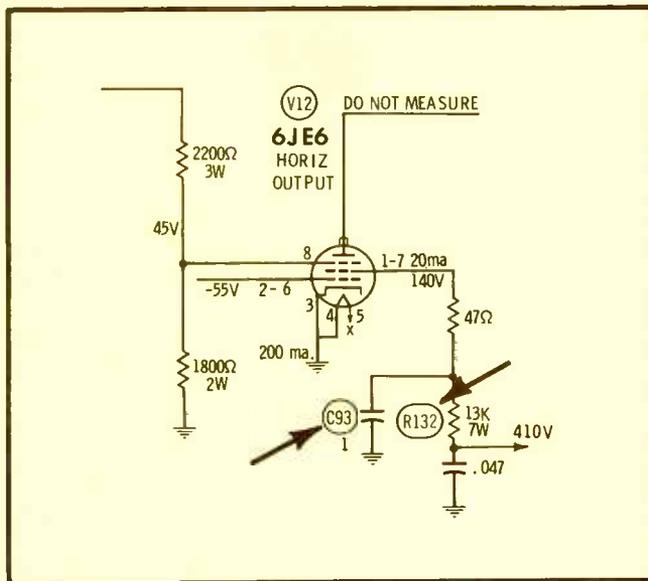What To Do: Replace C78 (.0082 mfd, 1KV).



Mfr: Magnavox

Chassis No: C/U45-01-00 thru C/U45-04-00

Card No: MAG 45-6

Symptoms: Narrow or reduced width.

Section Affected: Raster.

Cause: Screen-grid resistor in horizontal-output tube circuit has changed value.

What To Do: Replace R132 (13k, 7w), and C93 (.1 mfd).

SEE PHOTOFACT Set 640, Folder 3

Mfr: RCA Chassis No: CTC12A, B, etc.


Card No: RCA CTC12-1

Section Affected: Color.

Symptoms: B-W pix not affected; all channels operating; no color signals coming through. Normal color hash on screen when tuning off-channel not present.

Cause: Coupling capacitor to grid of burst amplifier open, causing color information to be lost at this point. Voltages on tube normal.

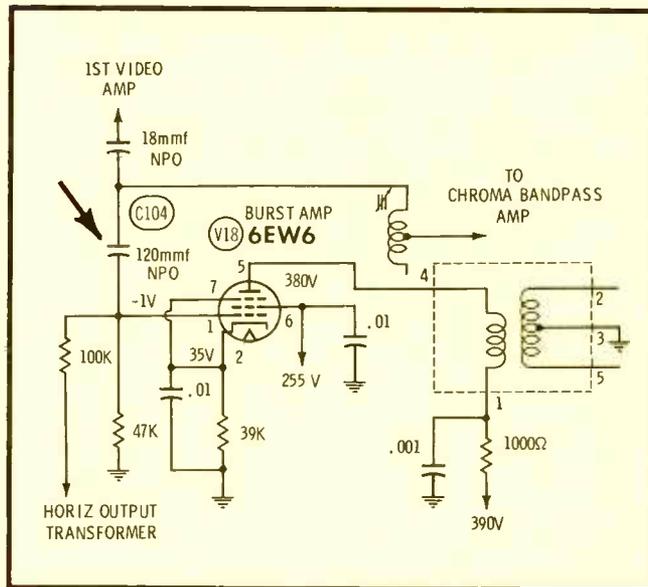What To Do: Using color-bar generator, signal trace back from chroma-bandpass amplifier to burst amplifier. Faulty stage will be localized when color signal is applied to first video amplifier. Replace C104 (120 mmf).



Mfr: RCA Chassis No: CTC12A, B, etc.


Card No: RCA CTC12-2

Section Affected: Pix.

Symptoms: When brightness is varied pix blooms and defocuses. Regulator tube burns out periodically. Excessive high voltage (correct value, 24KV). Cathode current in horizontal-output tube high (should be 210 ma). Cathode current in shunt regulator low (should be 850 μ a).

Cause: Incorrect high-voltage adjustments.

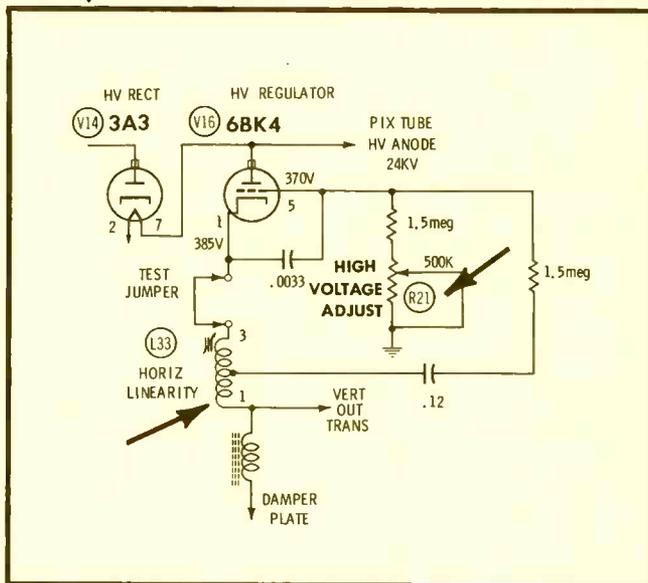What To Do: Perform high-voltage adjustment



Mfr: RCA Chassis No: CTC12A, B, etc.


Card No: RCA CTC12-3

Section Affected: Raster.


Symptoms: No raster. Boost B+ supply resistor R130 overheats; reads short to ground on one side.

Cause: Green screen control shorted to ground through case of control causing boost and B+ voltage to short to ground. Supply resistor R130 in boost B+ supply burning. Focus rectifier possibly damaged due to overload. Screen controls must be removed from circuit to find faulty control.

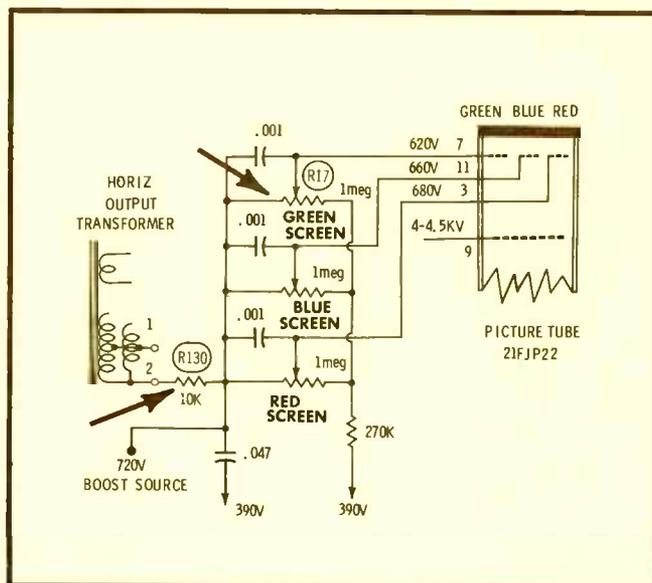What To Do: Replace shorted green screen control R17 and R130 (10K). Check focus rectifier and replace if necessary.



SEE PHOTOFACT Set 640, Folder 3

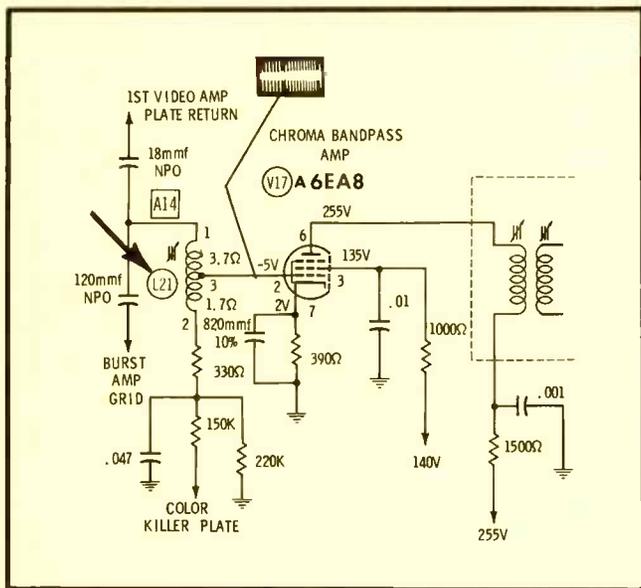

SEE PHOTOFACT Set 640, Folder 3

Mfr: RCA Chassis No: CTC12A, B, etc.


Card No: RCA CTC12-4

Section Affected: Color.

Symptoms: No color pix. B-W pix normal. All set functions are normal. Dot-bar color signal present at control grid of chroma-band-pass amplifier; signal does not appear at output of burst amplifier.

Cause: Open chroma-takeoff coil.

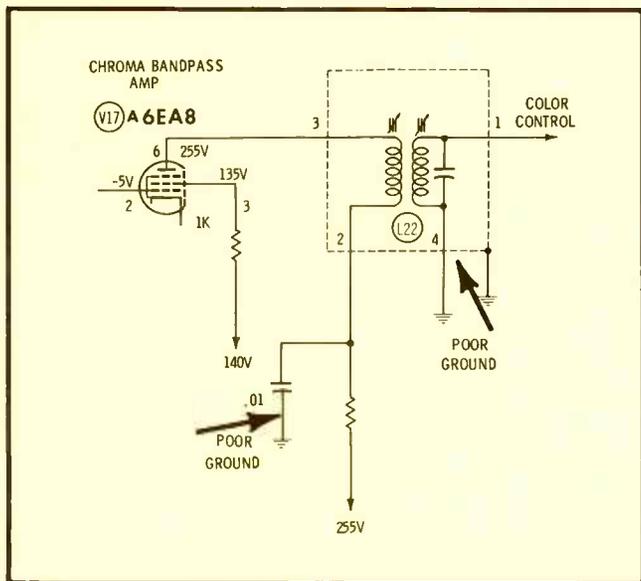What To Do: Check resistance of chroma-takeoff coil L21; if open, replace or resolder.



Mfr: RCA Chassis No: CTC12A, B, etc.


Card No: RCA CTC12-5

Section Affected: Color.

Symptoms: Color and B-W signals good, but become intermittent after set plays for 15 to 30 minutes.

Cause: Poorly soldered ground point on printed-circuit board.

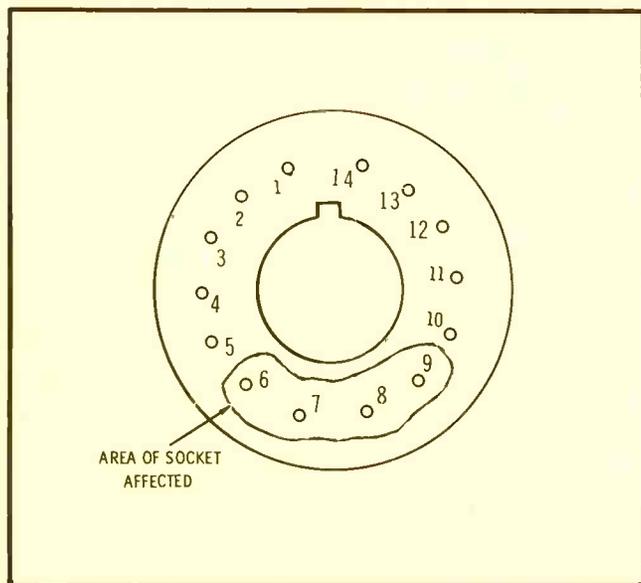What To Do: Let receiver heat up for one or two hours. A resistance check and mechanical stress of the printed-circuit board will reveal defective ground points; resolder.



Mfr: RCA Chassis No: CTC12A, B, etc.

Card No: RCA CTC12-6


Section Affected: Raster or Pix.

Symptoms: No raster, or poor focus when raster is present. Low focus voltage, reduced high voltage; when focus-supply voltage is disconnected from CRT socket, focus and high voltage return to normal.

Cause: High resistance leakage in CRT socket between pins 6, 7, and 9 causing low focus voltage and reduced high voltage.

What To Do: Replace CRT socket. Opening old socket will reveal carbonization.

Complete TUNER REPAIR for only

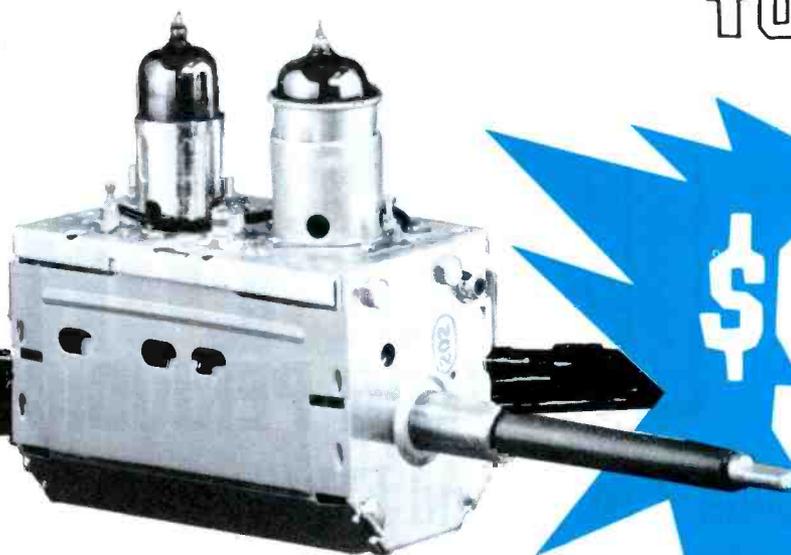

\$9.50

Sarkes Tarzian, Inc., largest manufacturer of TV and FM tuners, offers unexcelled tuner overhaul and factory-supervised repair service. Completely-equipped and conveniently-located Service Centers offer fast, dependable and factory-supervised repair service on all makes and models. Centers are staffed by well-trained technicians, assisted by engineering personnel.

Tarzian-made tuners received one day will be repaired and shipped out the next. More time may be required on other makes. Every channel—not just the channels existing in any given area—is checked and re-aligned per orig-

inal specifications. Exclusive cleaning method makes the tuner look—as well as operate—like new.

Cost, including ALL labor and parts (except tubes) is only \$9.50 and \$15 for UV combinations. No additional charge. No hidden costs. Too, you get a full, 12-month warranty against defective workmanship and parts failure due to normal usage.

Always send TV make, chassis and Model number with faulty tuner. Check with your local distributor for Sarkes Tarzian replacement tuners, parts or repair service. Or, use the address nearest you for fast, factory-supervised repair service.



TUNER SERVICE CORPORATION

(Factory-supervised tuner service authorized by Sarkes Tarzian)

MIDWEST—817 N. Pennsylvania St.,
Indianapolis, Ind. Box 1642
Tel: 317-632-3493

EAST —547-49 Tonnele Ave., Jersey City, N. J.
Tel: 201-792-3730

WEST—

SARKES TARZIAN, Inc.
Tuner Service Division

10654 Magnolia Blvd.,
N. Hollywood, Calif.
Tel: 213-769-2720



MANUFACTURERS OF TUNERS, SEMICONDUCTORS, AIR TRIMMERS, FM RADIOS, AM-FM RADIOS, AUDIO TAPE and BROADCAST EQUIPMENT

Circle 2 on literature card

May, 1966/PF REPORTER 9



Again from **JFD**[®]


the first major VHF antenna advance
since the invention of the JFD LPV Log Periodic!

Developed at the JFD Antenna-Research Laboratories, Champaign, Illinois under the
direction of Dr. Paul E. Mayes, co-inventor of the acclaimed LPV Log Periodic concept.

*the remarkable **new***

JFD[®] **LPV-TV**[®]
COLOR
LOG PERIODIC

for channels 2 to 13 and FM/Stereo

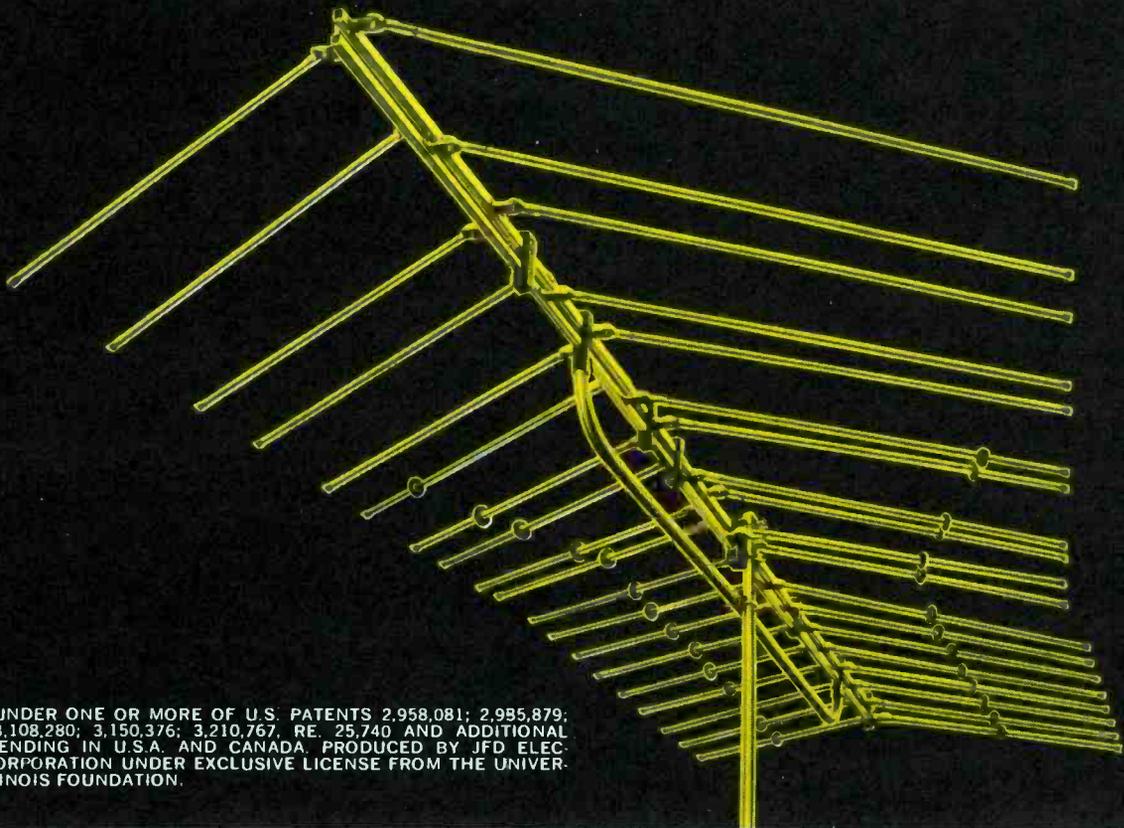

LICENSED UNDER ONE OR MORE OF U.S. PATENTS 2,958,081; 2,985,879;
3,011,168; 3,108,280; 3,150,376; 3,210,767, RE. 25,740 AND ADDITIONAL
PATENTS PENDING IN U.S.A. AND CANADA. PRODUCED BY JFD ELECTRONICS CORPORATION UNDER EXCLUSIVE LICENSE FROM THE UNIVERSITY OF ILLINOIS FOUNDATION.

Circle 3 on literature card

WIFIJECH

While our LPV-TV series was undergoing development in Champaign, Ill., it was assigned the code name: WIFIJECH.

For good reason.

Its performance objectives were to surpass every competitive make—model for equivalent model—in gain, directivity, response, V S W R, & F/B ratio.

Did the new LPV-TV come through?

—All the way! Its performance is the proof!

Now at your JFD LPV distributor.

Seven LPV-TV models to choose from — meet any location or budget needs!

Write for LPV-TV brochure 1039.



BY FAR—the best antenna for VHF COLOR performance because it combines...

- The electronic perfection of the patented frequency independent Log Periodic concept of the University of Illinois Antenna Research Laboratories.
- New capacitor-coupled Cap-Electronic elements that respond on the third harmonic mode for highest effective gain. More harmonically resonant elements mean higher signal-to-noise ratios, better ghost rejection, sharper directivity on high VHF band—where it's most needed, especially in color.*
- True dual-band directors separately tune to high and low bands for added gain and directivity on all channels.
- Flat frequency response ($\pm \frac{1}{2}$ db across entire channel) for studio-quality color regardless of channel tuned.

New LPV-TV Log Periodic antenna series incorporates new capacitor-coupled element concept for improved response, especially in color, on channels 2 to 13.

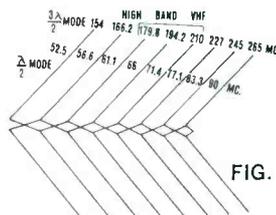


FIG. 1 (Note that only three dipoles resonate at frequencies in the high VHF band.)

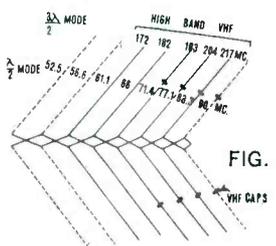


FIG. 2 However, by introducing parallel plate capacitors into the dipoles and by carefully adjusting the value of this capacitance and its position on the dipole, as shown in Figure 2, the resonant frequencies of the dipole can be shifted in the 3/2 wavelength mode. In this way, the dipole can be made to resonate at two desired frequencies: e.g., 88 and 216 mc.

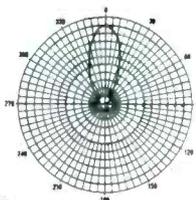


FIG. 3 Result: the active region in the high band extends over five of the eight original dipoles instead of three, as in Fig. 2, with a performance improvement of 66%. The new capacitor-coupled dipoles also present more capture area on the low band than ordinary dipoles. Thus LPV-TV antennas offer, on both bands, higher and more uniform gain, lower side-lobe levels, narrower beamwidths, for vastly improved ghost rejection (see Fig. 3).

 <p>VHF — up to 50 miles FM — up to 30 miles Model LPV-TV3 3 Cell System (single-crossarm) With electronic "ghost-killing" trap \$14.95 list</p>	 <p>VHF — up to 75 miles FM — up to 40 miles Model LPV-TV5 6 Active Cell & Director Cap-Electronic Element System \$23.95 list</p>	 <p>VHF — up to 100 miles FM — up to 50 miles Model LPV-TV7 8 Active Cell & Director Cap-Electronic Element System \$31.95 list</p>	
 <p>VHF — up to 125 miles FM — up to 50 miles Model LPV-TV10 10 Active Cell & Director Cap-Electronic Element System \$41.95 list</p>	 <p>VHF — up to 150 miles Model LPV-TV13 13 Active Cell & Director Cap-Electronic Element System \$49.95 list</p>	 <p>VHF — up to 175 miles Model LPV-TV16 16 Active Cell & Director Cap-Electronic Element System \$59.95 list</p>	 <p>VHF — up to 200 miles Model LPV-TV19 19 Active Cell & Director Cap-Electronic Element System \$79.95 list</p>

JFD ELECTRONICS CORPORATION
15th Avenue at 62nd Street, Brooklyn, N.Y. 11219
JFD International, 64-14 Woodside Ave., Woodside, N.Y. 11377

See what's NEW from JFD at BOOTH 2101 in San Francisco Parts Show June 3, 4, 5

PF Reporter™

PHOTOFACT

the magazine of electronic servicing

VOLUME 16, No. 5

MAY, 1966

CONTENTS

Previews of New Sets	1
Arvin Model 65K38, Chassis 1.87803; General Electric Model M937ACL, Chassis CA428; RCA Model FG525E, Chassis CTC19A; Sylvania Model 25HC83, Chassis D02-6.	
Video Speed Servicing	5
Service hints on Magnavox Chassis C/U45-01-00 thru C/U45-04-00 and RCA Chassis CTC12A,B etc.	
Letters to the Editor	16
The Electronic Scanner	17
Keyed AGC Allan F. Kinckiner	20
Shop Talk — Circuit analysis, troubles, and troubleshooting techniques.	
Locus of the Focus Jack Darr	23
The "Hot-Shot" encounters a focus problem but survives to tell the story.	
Repairing the XYZ Color Circuits Homer L. Davidson	25
A close look at these critical circuits reveals the cause of some typical troubles.	
New Tube and Transistor Data	27
Chasing Troubles in Stereo-On Indicators Jack Gamble	31
An analysis of indicator circuits and their troubles provides some good trouble-shooting hints.	
Leave Those Parts in the Circuit—Part I Larry Allen	34
The application of these troubleshooting tips will save you time and leave your soldering gun cold.	
Notes on Test Equipment T. T. Jones	38
Lab report on B & K Model 707 Tube Tester and Waterman OCA-11A Oscilloscope.	
Book Review	42
Stereo-FM Station Guide	44
Puzzler	70
The Troubleshooter	76
Color Countermeasures	80
Product Report	82
Free Catalog and Literature Service	88
Monthly Index on Free Literature Card	

publisher

Howard W. Sams

general manager

Danald W. Bradley

editor

William E. Burke

managing editor

James M. Moore

associate editors

Thomas T. Jones

J. Phipps

Ralph M. Scott

consulting editors

Joe A. Groves

C. P. Olliphant

research librarian

Bonny Howland

production manager

Esther M. Rainey

circulation manager

Pat Tidd

art directors

Louis J. Bos, Jr. & Robert W. Reed

photography

Paul Cornelius, Jr.

advertising sales offices

Hugh Wallace, advertising sales manager

midwestern

Roy Henry

Howard W. Sams & Co., Inc. 4300 West 62nd St.,

Indianapolis, Ind., 46206

291-3100

central

Paul Houston

Howard W. Sams & Co., Inc. 4300 West 62nd St.,

Indianapolis, Ind., 46206

291-3100

eastern

Gregory C. Mosefield

Howard W. Sams & Co., Inc. 3 West 57th St.

New York 19, New York

MU 8-6350

southwestern

C. H. (Jake) Stockwell

C. H. Stockwell Co., 4916 West 64th St.

Mission, Kansas, RA 2-4417

western

Los Angeles Office

G. R. (Jerry) Haltz

The Maurice A. Kimball Co., Inc.

2008 West Carson St., Suites 203-204

Torrance, Calif., 90501

320-2204

San Francisco Office

The Maurice A. Kimball Co., Inc.

580 Market St., Room 400

San Francisco 4, California

EX 2-3365

Address all correspondence to PF REPORTER,

4300 W. 62nd Street, Indianapolis, Indiana 46206



Copyright © 1966 by Howard W. Sams & Co., Inc. PF REPORTER is a trademark of Howard W. Sams & Co., Inc. No part of PF REPORTER may be reproduced without written permission. No patent liability is assumed with respect to use of information herein. Acceptance of advertising does not in any manner signify the products, policies and services so advertised have been approved, endorsed or recommended by this magazine.

Subscription Prices: 1 year—\$5.00, 2 years—\$8.00, 3 years—\$10.00, in the U. S. A., its possessions and Canada. All other foreign countries: 1 year—\$6.00, 2 years—\$10.00, 3 years—\$13.00. Single copy 50¢; back copies 65¢.

Indexed in LECTRODEX.

Printed by the Waldemar Press Div. of Howard W. Sams & Co., Inc.


About the Cover

Our cover this month simplifies the process which takes place in the color demodulators of a color receiver. Any service technician who has touched a chroma circuit board or viewed a cyan screen knows that color is not as easy as ABC, or XYZ for that matter. The article beginning on page 25 in this issue provides some valuable information on these critical circuits.




Did you ever...

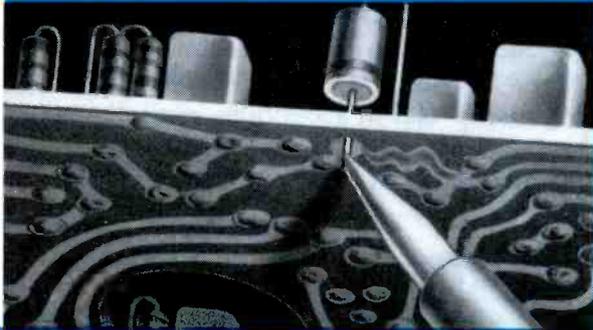... lift a wire-lead component from a printed wiring board for testing ?



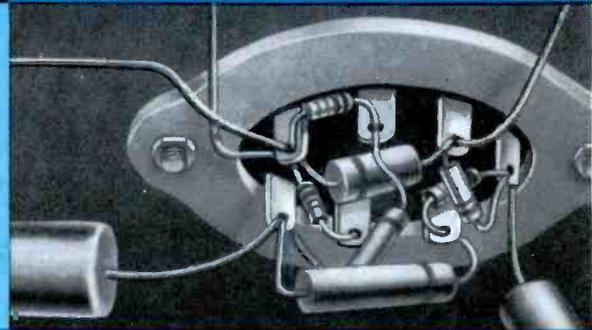... test or replace a capacitor or resistor on a crowded tube socket ?



CUT YOUR TIME IN HALF with **KWIKETTE** Soldering Aids ...the revolutionary

connectors that practically let you do "in-circuit" component testing!



(six times actual size)

WIRE FLUX SOLDER

The KWIKETTE SOLDERING AID is not just another wire spring connector! It has a Copperweld wire inner core, an intermediate layer of flux, and an outer jacket of solder . . . all you need is heat!


KWIKETTES are now being packed with Sprague Atom® Capacitors at no extra cost to you! Whenever you need tubular electrolytics, insist on pre-packaged Sprague Atoms from your parts distributor and you'll automatically get your KWIKETTE component connectors . . . the biggest boon to the service technician since the soldering gun!

FREE TRIAL PACKAGE!


10 free KWIKETTE Soldering Aids are yours for the asking! Simply send your postcard request to KWIKETTE Center, Sprague Products Co., 105 Marshall Street, North Adams, Mass. 01247. Don't forget to include the name of your Sprague Distributor.

* trademark


SNIP LEAD ...

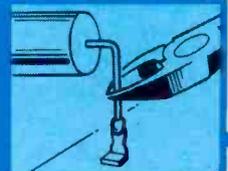


TEST ...

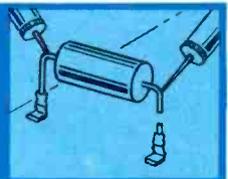

SLIP ON KWIKETTE ...

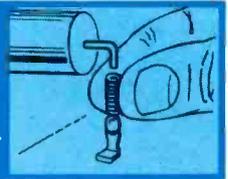

APPLY HEAT!

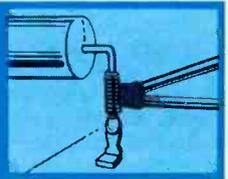

SPRAGUE
THE MARK OF RELIABILITY

WORLD'S LARGEST MANUFACTURER OF CAPACITORS



Circle 4 on literature card

www.americanradiohistory.com

THIS VOM WON'T FOOL YOU ON TRANSISTOR CIRCUIT CURRENT

Low 50-Millivolt drop on current ranges gives accurate measurements

Now, you can make transistor current measurements with a VOM . . . and with 0.05 volts or less change in operating conditions. ■ This new, self-shielded, taut band member of Simpson's famous 260® family of VOMs is made for use in transistor circuits. Regular VOMs often give wrong current readings because their high resistance actually changes the operating conditions by as much as 300 millivolts. ■ Model 250 also has provisions for using Simpson "Add-A-Tester" adapters and all other 260-family probes and accessories. Sensitivity is 20,000 ohms per volt DC, 5000 ohms per volt AC. Accessories include three DC high voltage probes, an AC high voltage probe, plus several styles of leads and carrying cases — eleven accessories in all. If your work includes checking current in transistor circuitry, call your electronic distributor for fast delivery of a Simpson Model 250. Complete with test leads and operator's manual **\$59⁹⁵**

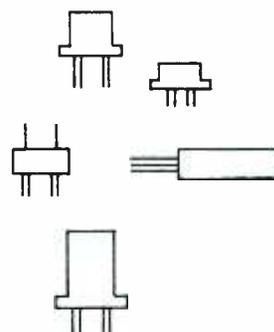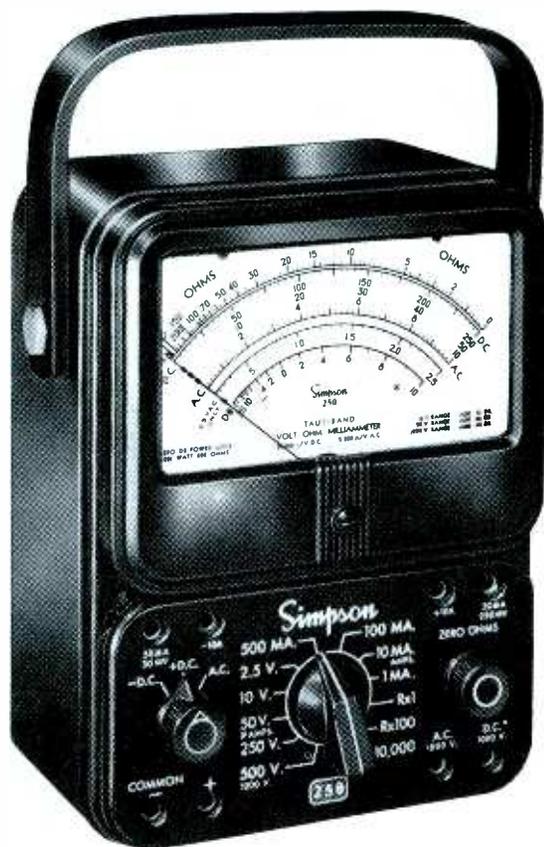

RANGES

DC VOLTS: 0-0.050; 0-0.250; 0-2.5; 0-10; 0-50; 0-250; 0-500; 0-1000
AC VOLTS: 0-2.5; 0-10; 0-50; 0-250; 0-500; 0-1000
DC MICROAMPERES: 0-50 (Both 50 and 250 MV Drop)
DC MILLIAMPERES: 0-1; 0-10; 0-100; 0-500 (50 MV Drop)
DC AMPERES: 0-10 (50 MV Drop)
DB SCALE (1MW-600Ω): -20 to +10; -8 to +22; +6 to +36; +20 to +50
RESISTANCE RANGES: R X 1 0-2000Ω (12Ω center); R X 100 0-200kΩ (1200Ω center);
 R X 10K 0-20 megΩ (120KΩ center)

ACCURACIES

0-50 MV; 0-250 MV; 0-2.5
 to 0-1000 V DC: ±2% F.S.
0-50 MICROAMPERES: ±1% F.S.
0-1 MA to 0-10 A DC: ±2% F.S.
RX1: ±2.5° of Arc
RX100, RX10,000: ±2.0° of Arc
0-2.5 to 0-1000 V AC: ±3% F.S.



SIMPSON ELECTRIC COMPANY


5205 W. Kinzie Street, Chicago, Ill. 60644 • Phone: (312) EStebrook 9-1121
 Representatives in Principal Cities . . . See Telephone Yellow Pages
 Export Dept.: 400 W. Madison St., Chicago, Ill. 60606 Cable, Simelco

In India: Ruttonsha-Simpson Private Ltd., Vikhroli, Bombay

WORLD'S LARGEST MANUFACTURERS OF ELECTRONIC TEST EQUIPMENT

Circle 5 on literature card

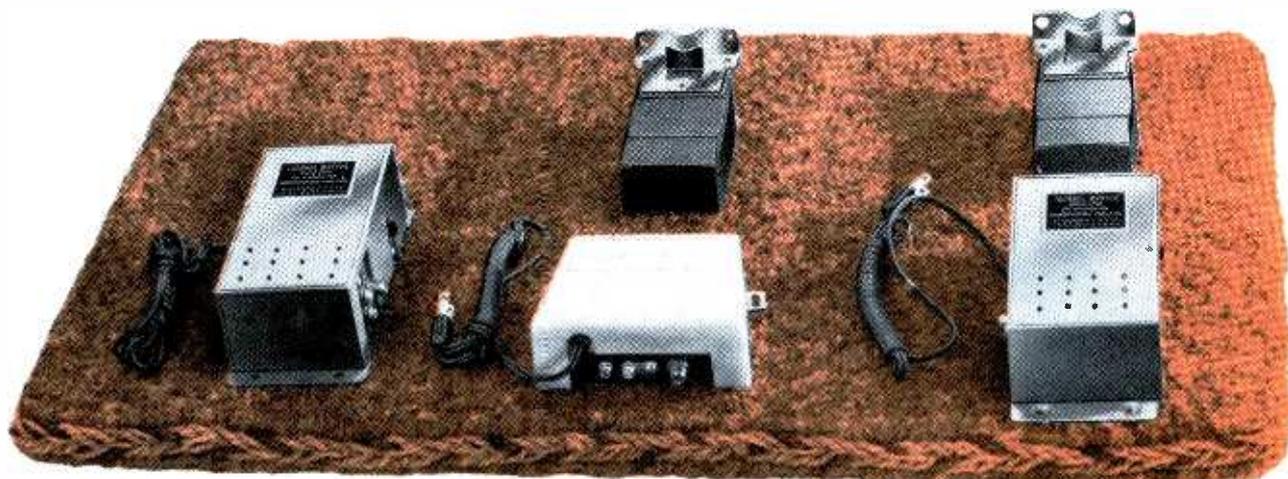Small homes are saying "Yes" to big MATV business.



Walk right in with one of our 5 brand-new Channel Master MATV Amplifiers*

(They're priced fantastically low).

The color explosion has given birth to a gigantic new market. One that's left the door to multi-set homes wide open for big business opportunities.

When a family buys a color set, they don't throw the old black-and-white console away. They keep it. Chances are they also own a portable and even an FM set or hi-fi.

All this means one thing: Every one in your neighborhood who has, or buys, a color set becomes a hot prospect for the unique room-to-room flexibility offered by a Master Antenna Home System.

Here's where you cash in with our big line of Channel Master MATV amplifiers. They let you accommodate the

exact need. For instance: Our new solid state VHF/FM Color Amplifier (Model 7035) provides 15 db across the entire band, flat color response, 1.5 volt output capability, plus a 75 ohm or 300 ohm input or output. It could be perfect for a home with a number of outlets in a weak to medium signal area.

Or the situation may call for one of our two new 75 ohm coaxial boosters: the single transistor Telstar VHF/FM (Model 0043); or the 2-transistor Twinstar VHF for areas with overload problems (Model 0041). Both models provide especially high gain (15 db) and low noise figures—and are the only coaxial amplifiers with both a 75

ohm and 300 ohm output.

Motels and garden apartments? Use our new outstanding 30 db VHF/FM Color Tandem Amps (Models 7041, 7043). Consists of mast-mounted pre-amps of models 0041 and 0043 cascaded with Model 7035 (contains power supply for pre-amps).

We have other amplifiers, including several for medium and large commercial systems. But the important thing is our flexibility. You're backed by the broadest MATV amplifier line in the business.


Like we said: The welcome mat is out. What are you waiting for?

Write for the facts!

* MODEL	GAIN	NOISE FIGURE		MAXIMUM INPUT SIGNAL IN MICROVOLTS		OUTPUT CAPABILITIES		LIST PRICE
		LOW BAND	HIGH BAND	LOW BAND	HIGH BAND	LOW BAND	HIGH BAND	
7035 Color Amp	15 db	2.5	5.4	300,000 total		1.5v total		Only \$34.95
0043 Telstar	15 db	2.2	3.0	15,000	30,000	100,000	135,000	Only \$34.95
7043 Color Tandem	30 db	2.2	3.0	15,000	30,000	1.5v total		Only \$64.95
0041 Twinstar	15 db	2.5	3.7	150,000	190,000	850,000	600,000	Only \$44.95
7041 Color Tandem	30 db	2.5	3.7	60,000	100,000	1.5v total		Only \$74.95

© Copyright 1966, Channel Master Corp., Ellenville, N.Y.

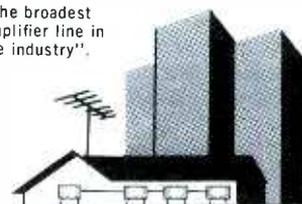"The broadest amplifier line in the industry".




CHANNEL MASTER

ELLENVILLE, NEW YORK

Circle 6 on literature card

May, 1966/PF REPORTER 15

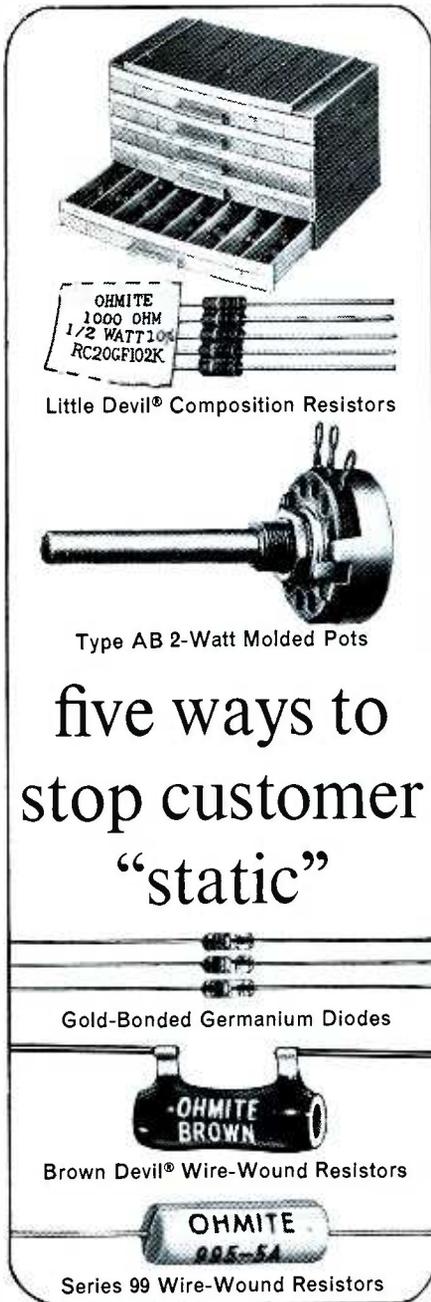

Little Devil® Composition Resistors

Type AB 2-Watt Molded Pots

five ways to stop customer "static"

Gold-Bonded Germanium Diodes

Brown Devil® Wire-Wound Resistors

Series 99 Wire-Wound Resistors

Customer "static" is hard on the ears . . . hard on profit. But you're always safe with Ohmite quality replacements in your repair jobs. Order Little Devils in handy cabinet assortments or on Tally-Tape; all popular sizes and values. Select AB Pots from 50 ohms to 5 megohms in several shaft lengths. Choose from ninety 1N types of diodes. Get Brown Devils from 3 to 20 watts in 0.5-ohm to 100K-ohm values. Order Series 99 resistors in 1½, 2¼, 3¼, 5, 11 watt sizes from 1 to 51,000 ohms. Ask your distributor for the latest edition of Ohmite's Stock Catalog 30.

Be right with



Circle 7 on literature card

Letters to the Editor

Dear Editor:

This for me is a first-writing to an editor. Only infrequently do I get a feeling of genuine personal, down-to-earth involvement in a magazine article. However, I must admit it occurs more and more frequently in your PF REPORTER.

The October '65 issue contains a letter from a name withheld about the merits of your publication (with which I agree) and also included two problems (page 14). I accepted the challenge but did not get very far with it. What caused my reaction to this is that I have always had much difficulty setting up equations that will be completely true to the facts on the situation. I sincerely am concerned about why I cannot clearly see through problems of this type.

The letter and your comments started some deeper than usual thinking for me; this occurs only occasionally and is in itself a high recommendation of the caliber of your magazine.

It is my earnest hope to learn more about why I have difficulty setting up (or seeing how to set up) basic equations. I have had basic and advanced algebra in high school and a review by correspondence course since. However, very little practice was given on how to set up a group of facts. Much necessary time and effort is spent on solutions of equations, and I believe I have a fair ability in solving them once they are set up. It seems to me that most courses stress the *how* without explaining the *why*. I have had much practice on how to solve $x + (x + 12) = 46$ but very little on where this originates. Your letter hits it right on the head and brings out why the equation was formed in the first place. I suspect a great deal of my trouble is due to not enough experience with math.

You close the solution to the problems with "why then don't these same intelligent technicians use such logic in their everyday work?" I do have difficulty almost daily in solving problems, as an electronic technician doing general repair. And I could not solve the two problems. "How well related are the two?" I asked myself.

You say logical procedure is the way to do it. I like to think I solve my electronic problems logically, yet I could not reason out how to do the problem. Thus, I may not understand this "logical procedure" thing. So I thought it out further and here is what I came up with:

Logic—

Electronic troubleshooting is basically the use of logic. To properly understand this the meaning of logic must be known.

Webster defines it as "a connection of facts, events, and inferences in a rational way leading to a conclusion that makes arguments useless." Thus if $2x + 12 = 46$, then $2x = 46 - 12$, $2x = 34$, and $x = 17$. There is no argument about this assortment of facts being true logical conclusions. Any procedure whereby a step-by-step gathering of facts leads to a positive conclusion may not always be completely true due to an unknown factor or an unknown result from a combination of factors. The percentage of true conclusions will be increased in proportion to a person's knowledge and experience in application.

Assume two people graduate from high school together. One goes immediately to work at a skilled trade and ceases to study. The other continues studying in college. The first becomes quite proficient at certain operations involving mechanical skills and has certain (usually quite definite opinions) in matters of intellect (natural from a narrower viewpoint). The second may not be much good at similar mechanical skills at first but will gain an intellectual ability enabling him to understand and reason out many more problems. Thus, in a short while, the second will be able to accomplish any task the first man can perform, with few exceptions, then easily go on to others. The second will have more ability to create, simplify, perfect, and enlarge upon more and more things as his knowledge increases. Of the two, one can see which should be the more logical thinker, or performer, in most situations. The first would be more the type to remember that the last repair of a "no-vertical-sweep" problem was made by replacing the vertical output transformer, therefore, the same repair should fix this one too. The second man would be more apt to understand and realize there are six or eight things other than the output transformer to cause this trouble. He would apply a logical approach to determining what area held the problem.

So I think I have answered my own questions—I'm sort of in the category

• Please turn to page 86



The Electronic Scanner

news of the servicing industry

Industry at New Peaks in 1965

Culminating a decade of growth, output of the home entertainment products of the electronics industry attained new peaks in 1965 with further gains forecast through 1970, the Electronic Industries Association's Marketing Services Department reported.

Color television leads the latest upward surge. EIA points out, but radical improvements have instilled a new life in the radio and phonograph markets as well. In addition, new electronic consumer products such as tape recorders and electronic organs have opened other fields for expansion.

The domestic market absorbed 11.6 million television receivers last year, including one million imported receivers.

Despite the soaring popularity of television, demand for radios reached an all-time high of 41 million sets in 1965 compared with 14 million in 1955. A sharp reduction in prices of portable radios, the introduction of stereophonic radio broadcasting during recent years, and the resurgence of FM no doubt contributed heavily to this phenomenal increase, according to EIA. One out of every four radios produced was for use in autos.

The market for phonographs reached a new record of 6.5 million sets in 1965—more than double the sales in 1955. Technological improvements, stereophonic sound reproduction and a new generation of portables were factors chiefly responsible for this growth in consumer demands.

Sales of tape recorders increased from a negligible amount in 1955 to 4 million units last year. Most of these were imported, but a number of U.S. manufacturers began production during the year, while others broadened their product lines and output.

The sale of color TV sets last year, according to EIA's final tabulations, practically doubled within one year to reach 2.7 million sets. The public demand for black-and-white TV, with a heavy accent on portables and small screen sizes, rose to 8.9 million during 1965—over a million more than in 1955.

EIA's Marketing Services Department foresees a continuing strong rise in color television sales during the next five years as the demand for black-and-white sets may begin to taper off.

The upsurge of electronic consumer products is expected to be accompanied by increased factory employment, as new plants open to supply the growing market, as well as by a corresponding expansion in retail and service operations throughout the United States, according to EIA.

Tuner Company Formed

An agreement has been reached between Electro-Netic Steel and Industrial Electronic Hardware Corp. to form a new company, **Electro-Netic Products Corporation**, which will purchase the present VHF Tuner Division of Electro-Netic Steel and the UHF Tuner Division of Raypar Electronics, Inc., a wholly-owned subsidiary of Industrial Electronic Hardware Corp.

The new company will produce and sell a complete line of TV tuners for black-and-white color sets.

New Labs

Hewlett-Packard Company has announced the consolidation of its advanced research and development activities into a new organization known as HP Laboratories.

Located in Stanford Industrial Park, the new organization is engaged in several advanced research activities.

HP now has 16 product divisions, each with its own line of instruments and supported by its own product-development group.

Experience for Sale.....45¢

Sure seems we started something!


Yes; over ten years ago, when we started overhauling tuners (all makes and models), we set a price of \$9.95 for this service.

Apparently there are those who would like to imitate our achievement—and for 45¢ less.

Maybe the special skills, special equipment and downright old fashioned experience we built up during these past years are worth that little extra.—You be the judge.

Remember; 45¢ buys you more than a quarter of a million man/hours of experience, plus true devotion to our business . . . our only business . . . overhauling your television tuners the best way we know how. And in over ten years we sure know how!

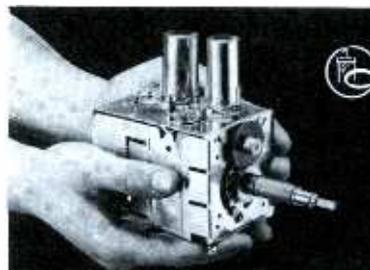Castle — The Pioneer of TV tuner overhauling
Not the cheapest — just the best.



For complete tuner overhaul we still charge only \$9.95. This includes all labor and parts; except tubes and transistors, which are charged extra at low net prices.

Simply send us the defective tuner complete; include tubes, shield cover and any damaged parts with model number and complaint. Your tuner will be expertly overhauled and returned promptly, performance restored, aligned to original standards and warranted for 90 days.

UV combination tuner must be single chassis type; dismantle tandem UHF and VHF tuners and send in the defective unit only.

Exact Replacements are available for tuners unfit for overhaul. As low as \$12.95 exchange. (Replacements are new or rebuilt.)

CASTLE

TV TUNER SERVICE, INC.


MAIN PLANT: 5701 N. Western Ave., Chicago 45, Illinois

EAST: 41-90 Vernon Blvd., Long Island City 1, N.Y.

CANADA: 136 Main Street, Toronto 13, Ontario

*Major Parts are additional in Canada

Circle 8 on literature card

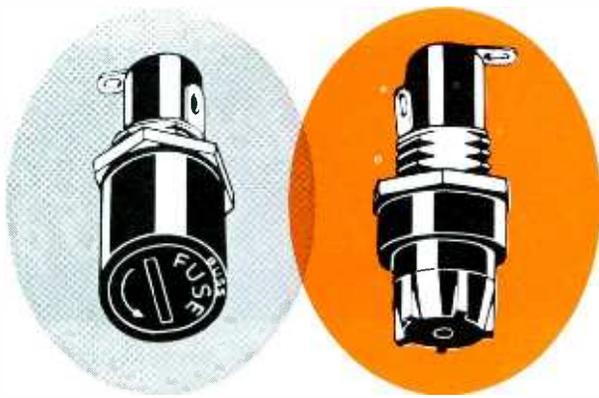

Screw type slotted knob that is recessed in holder body and requires use of screwdriver to remove or insert it.

Screw type knob designed for easy gripping, even with gloves. Has a "break-away" test prod hole in knob.

BUSS Space Saver Panel Mounted Fuseholders

Fuseholder only 1 1/8 inches long, extends just 3/32 inch behind front of panel. Takes 1/4 x 1 1/4 inch fuses. Holder rated at 15 ampere for any voltage up to 250.

Military type available to meet all requirements of MIL-F-19207A.

Write for BUSS Bulletin SFH-10

INSIST ON BUSS QUALITY

BUSSMANN MFG. DIVISION, McGraw-Edison Co., St. Louis, Mo. 63107

BUSS: The Complete Line of Fuses and

A primary objective of HP Laboratories is to provide these groups with a reservoir of advanced scientific knowledge and techniques.

When appropriate, HP Laboratories also will make its research capabilities available to outside agencies.

5.5 Million Color TV Receivers Forecast For 1966

The Radio Corporation of America raised its forecast of 1966 industry color television receiver sales by one million sets to a total of 5.5 million units, reflecting increases in both consumer demand and production capacity.

The new estimate, double last year's sales total, will result in retail sales of nearly \$3 billion, thus equaling for the first time the total consumer dollar volume of all other home entertainment products, according to Raymond W. Saxon, Vice President, RCA Victor Home Instruments Division.

Citing as an example of the speed with which the industry is building new facilities to meet the booming consumer demand, Mr. Saxon said their new television receiver plant in Memphis, Tenn., is expected to start turning out black-and-white receivers in May, fewer than five months from the start of construction. The \$20 million Memphis facility will free space at RCA's Bloomington, Ind., plant for more color production.

"Color television has stimulated the economy to such a degree that we now foresee a total consumer electronics industry dollar volume of more than \$6 billion this year," Mr. Saxon said. "This will be nearly twice the dollar volume of the entire home instruments industry as recently as 1964."

"Even with the revised production estimates, the snowballing consumer demand for color sets will continue to outstrip industry manufacturing capacities for some time to come."

The new Memphis TV receiver plant, which eventually will manufacture color as well as black-and-white sets, is part of a \$65.6 million expansion program. The first phase

of that program, a \$13.3 million expansion of existing plants in Bloomington and Indianapolis announced last June, is now nearing completion.

Mr. Saxon said industry color sales for the first eight weeks of 1966 are running 69 percent ahead of last year's rate. This rate is expected to climb as more sets become available through industry's new production facilities.

Supporting his optimistic outlook, RCA estimates place the average expenditure per household for home entertainment products at \$101 in 1966, compared with \$61 per household two years ago.


Sylvania Electric Products Inc. announced it is building a multimillion-dollar facility on a 125-acre site in Smithfield, N. C., to increase production space for color television sets and other electronic entertainment products.

Gene K. Beare, President of Sylvania, said construction would begin immediately on a 221,000-square-foot initial unit of the plant, and that the company will "substantially increase its output of color television sets in 1966 over 1965. This will be made possible partially by the transfer of stereo and radio production from the 430,000-square-foot Batavia plant to Smithfield to make room for increased color and black-and-white TV production at Batavia."

Westinghouse Electric Corporation has already completed major phases of a multimillion-dollar expansion program that will quadruple its color television manufacturing capacity by the third quarter of this year.

The program is based on an extensive expansion at the TV-Radio Division, Metuchen, N. J., coupled with the start-up of color TV tube production at the Electronic Tube Division, Elmira, N.Y. This tube production will cover part of the Company's requirement.

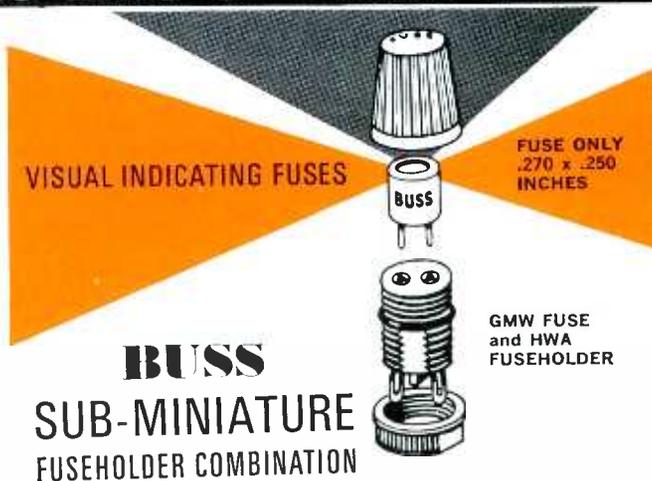Full production is expected to be achieved late this summer. Over the long term, the TV-Radio division will have a potential capacity of nearly 500,000 sets a year with the facilities that will be in operation this summer.



For space-tight applications. Fuse has window for inspection of element. Fuse may be used with or without holder.

Fuse held tight in holder by beryllium copper contacts assuring low resistance.

Holder can be used with or without knob. Knob makes holder water-proof from front of panel.

Military type fuse FM01 meets all requirements of MIL-F-23419. Military type holder FHN42W meets all military requirements of MIL-F-19207A.

Write for BUSS Bulletin SFB

INSIST ON BUSS QUALITY

BUSSMANN MFG. DIVISION, McGraw-Edison Co., ST. LOUIS, MO. 63107

Circle 9 on literature card



BLOCKS for BUSS FUSES

TYPES AVAILABLE
FOR ALL
APPLICATIONS

Single pole, multiple pole, small base, full base, molded base, laminated base, porcelain base for fuses from 1/4 x 3/8 inches up. Also signal type fuse blocks and special blocks of all types.

Tell us what you need or . . .

Write for BUSS Bulletin SFB

INSIST ON **BUSS**
QUALITY

BUSSMANN MFG. DIVISION McGraw-Edison Co., St. Louis, Mo. 63107

exchange of stock with Acme's shareholders.

Howard W. Sams, Chairman, commenting on this latest expansion move, stated, "This is our third technical school acquisition, the second within nine months. Negotiations with other schools are currently underway."

Present STI Centers are at peak enrollment with 1050 resident students at Indianapolis, 357 at Evansville, and 350 in Dayton by this Fall.

Sams also announced the introduction of a Home-Study Program in Electronics.

Move To Maryland

Polytronics Laboratories, Inc., a subsidiary of Vitro Corporation of America, will move to a new location adjacent to the Vitro Electronics Division's facility in Silver Spring, Maryland. The new location will give Polytronics access to the fabrication and assembly facilities contained at Vitro Electronics, enabling them to draw on the research, technical, and other staff facilities of the parent company when required.

Chip Production Up

To meet growing demand for integrated Circuits, **Raytheon Company** will expand production at Mountain View, Calif. and establish a new integrated-circuit production facility at Santa Ana, Calif.

The new integrated-circuit facility at Santa Ana will be in a 20,000-square-foot area of the Raytheon Computer Operation plant. This facility is expected to be operational early this summer. Some 200 persons now working on transistor assembly at Mountain View are also being trained for integrated-circuit work. ▲

.. Fuseholders of Unquestioned High Quality

Zenith Radio Corporation announced plans for a new \$3,000,000 manufacturing facility to be built in Sioux City, Iowa, by its subsidiary, the Wincharger Corporation.

The new Wincharger plant will total some 220,000 square feet for manufacturing, engineering, and general offices.

The new plant will permit Wincharger to increase production of Zenith radio receivers, and enable them to begin production of electronic components for Zenith consumer products.

Wincharger originally produced wind-driven generators ("Winchargers") that were a familiar sight on American farms 30 years ago. Because of declining demand as a result of Rural Electrification, production ended in 1958.

\$3,000,000


Setchell-Carlson, Inc., 32-year-old manufacturer of home-entertainment and communications equipment, has signed a purchase agreement for sale of all of the company's outstanding stock to Marquette Corporation of Minneapolis for \$3,000,000 in cash and notes.

Marquette, principally a manufacturer of battery chargers, welders and diagnostic engine analyzing equipment and a marketer of private brand major appliances, entered the entertainment field for the first time in 1965 with the introduction of a line of stereo and stereo-TV combination units manufactured by Setchell-Carlson.

Among Setchell-Carlson's contributions to electronic entertainment were the industry's first practical automobile radio, top-tuning television receivers, and a system to eliminate high current surges during the initial warm-up of a television picture tube, thus prolonging the life of the tube.

Acquires Dayton School

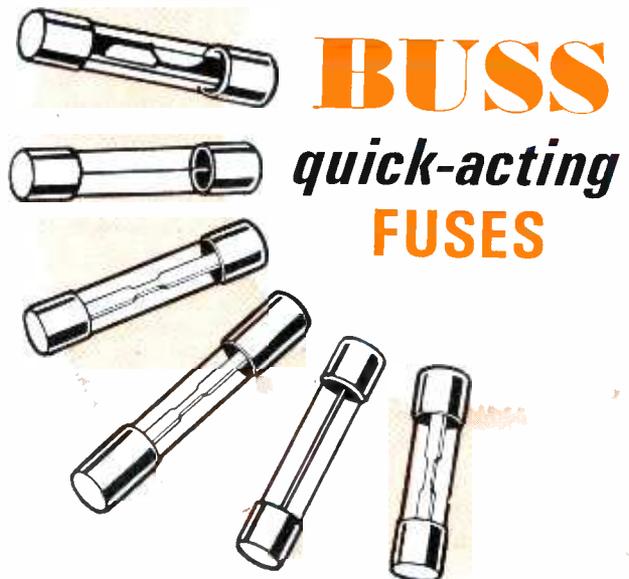Howard W. Sams & Co., Inc., announced the acquisition of Acme Institute of Technology, Inc., Dayton, Ohio, by



BUSS
quick-acting
FUSES

"Quick-Acting" fuses for protection of sensitive instruments or delicate apparatus;—or normal acting fuses for protection where circuit is not subject to current transients or surges.

Write for
BUSS
Bulletin SFB

INSIST ON **BUSS**
QUALITY

BUSSMANN MFG. DIVISION, McGraw-Edison Co., ST. LOUIS, MO. 63107

Circle 9 on literature card

by Allan F. Kinckiner

Find your way through these gain-control circuits

Keyed AGC is one of the most poorly understood circuits employed in TV receivers. It shouldn't be! Not only is the means by which the negative voltage develops less complicated than that in simple, peak, or supplemented AGC, but the method of controlling the magnitude of developed voltage is far less complex than that used in amplified AGC. By employing several analogies, circuit operation can be so simply explained that virtually every TV technician can understand it.

Analogy No. 1: Every TV technician is familiar with the circuit in Fig. 1A. It is the first stage of a half-wave voltage doubler used to supply B+ in many receivers. Even technicians not familiar with this rectifier circuit are aware of certain conditions normal to it; the circuit as shown will produce DC voltage at point A, but if X1 were removed (or open) no DC voltage would be measured at point A. If X1 were reversed, as in Fig. 1B, the DC voltage would also be reversed, now being negative (assume C1 is a non-polarized unit rather than the polarized electrolytic usually employed). If X1 in Fig. 1B is replaced by a vacuum tube, as in Fig. 1C, a negative voltage will be developed on the plate just as a negative voltage was developed on the anode of X1. If we change the type of voltage fed through capacitor C1, a negative voltage will still be produced on the plate of V1, although the amplitude will vary according to the make-up of the signal or voltage applied to C1. The value of C1 should also be changed as the frequency of the signal applied is changed. With the cir-

cuit in Fig. 1A operating at 60 Hz, C1 must be over 100 mfd for efficient operation. With the circuit in Fig. 1C used as a simulated keyed AGC stage fed by a high-frequency narrow pulse, little increase in DC plate voltage can be realized by increasing the value of C1 above .001 mfd. However, a sharp decrease in the value of C1 below .001 mfd will cause a proportional drop in the DC plate voltage.

A more theoretical analysis of these circuits indicates that the DC voltage is the result of the charge retained by C1. But a technician does not concern himself with this facet of operation of the keyed AGC stage, any more than he concerns himself with this facet of operation in the rectifier circuits. In summary, the analogy used with Figs. 1B and 1C answers the question, "Where does the minus voltage come from on the plate of a keyed AGC tube?"

The second most common question concerning keyed AGC is, "How is the amount of AGC voltage controlled?" There is no ready-made analogy to answer this question, but one can be manufactured.

Analogy No. 2: If the lead to ground in Fig. 1A, or preferably 1B, is opened and a variable resistor inserted, as is R1 in Fig. 2A, the magnitude of DC voltage developed will vary inversely with resistance. At higher values of R1, lower DC voltages will be produced; at lower values, higher DC voltages will result. Likewise, if the cathode return lead of V1 in Fig. 1C is opened and a variable resistor inserted, as is R2 in Fig. 2B, the DC plate voltage will also vary inversely with resistance. Increasing the resistance of R2 will

produce a lower DC voltage at the plate of V1; decreasing R2 will produce maximum DC voltage. It is no secret that introducing R2 into the circuit merely biases the tube. However, by showing that the similar use of a resistor in a diode circuit produces the same result, it becomes obvious that the conductance or internal resistance of the tube can also be controlled. The important thing is, however, that the magnitude of AGC voltage on the plate of any keyed AGC tube is determined by the amount of grid-to-cathode bias.

Control Circuits

Bias for controlling a keyed AGC tube is obtained from other receiver stages; most frequently a video amplifier is used. A typical early (and still very common) design is shown in Fig. 3. Here's how it operates: Under no-signal conditions, the cathode resistors R1 and R45 solely determine bias for V8 and set its plate current at approximately 10 ma. This plate current produces a drop of about 50 volts across R46, producing about 110 volts on the plate and also at the top of R46. This 110 volts is applied through isolation resistor R48 to the grid of V9, the AGC tube. With 110 volts on its grid and 160 volts on its cathode, V9 is so highly biased it does not conduct; no AGC voltage will be developed from the pulses applied to its plate.

Under signal conditions, the video detected by V7 consists of negative DC components at levels relative to the composite signal levels. These negative DC components form the grid signal of V8. Being of negative polarity and direct coupled to the grid, they decrease the plate current and reduce the voltage drop across R46. The resulting higher voltage at the plate end of R46 also places a higher voltage on the grid of V9; the bias applied to V9 is reduced, causing it to conduct and develop a negative AGC voltage (from pulses applied to its plate) in direct proportion to the bias.

The presence of a high DC potential on the cathode of the keyed

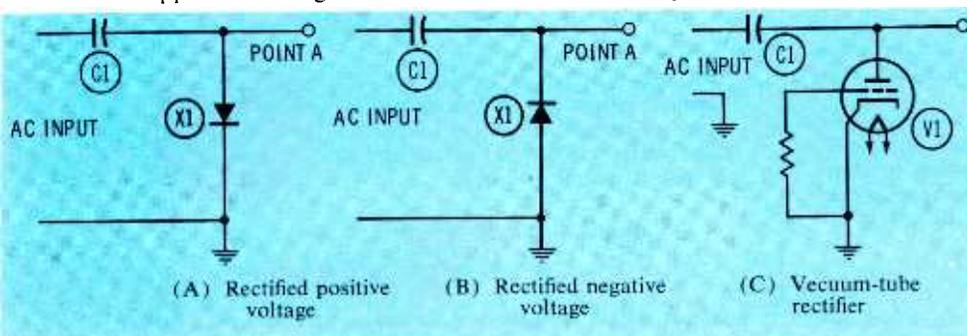


Fig. 1. Analogy of keyed AGC tube.

AGC tube is one of the major disadvantages of the circuit in Fig. 3. In many cases it necessitates the use of an ungrounded filament source connected to a B+ source to reduce the possibility of cathode-to-heater breakdown in the tube. Although many recent designs use circuits employing high DC voltages applied to the keyed AGC cathode, in most cases the tubes used have cathode-to-heater insulation capable of withstanding high DC voltage differences. Some manufacturers prefer, however, to use circuits in which the cathode operates at a reasonably low DC potential.

The circuit shown in Fig. 4 is a typical application in which the keyed AGC tube operates with a low DC potential on its cathode. The cathode voltage is adjustable from zero to a maximum of 65 volts. The voltage present at the plate end of R26, the video-amplifier load resistor, is coupled to the grid of V4B through a voltage divider network consisting of R60 and R61. Thus, the grid voltage will vary exactly as it did in Fig. 3, causing the AGC tube to conduct and develop AGC voltage in proportion to the strength of the received signal.

The circuit shown in Fig. 5 operates the cathode at ground potential to prevent cathode-to-heater breakdown. The conduction of the AGC tube is controlled by applying to its grid a negative voltage that is proportional to the negative potential present on the grid of the horizontal output. This negative voltage is fed to the AGC grid through voltage dividers R9 and R56 and opposes a positive voltage from the video-am-

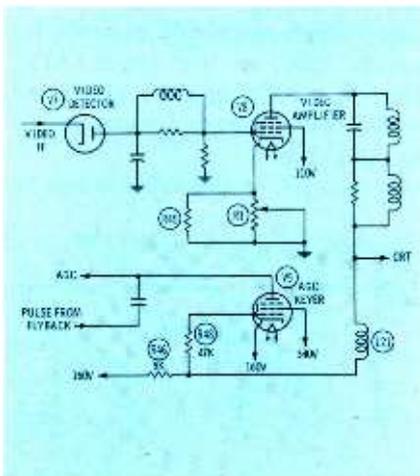


Fig. 3. Source of AGC tube bias.

plifier plate circuit applied through resistor R54.

A variation of the basic design is shown in Fig. 6. Operation is identical to that of the basic design with one exception. V6B is in the DC signal path between the video amplifier and the keyed AGC tube. V6B has two functions; it operates as a horizontal sync separator with sync pulses taken off at its plate. It also operates as a buffer between the video-amplifier plate and the grid of the keyed AGC stage. In the latter function, V6B operates as a cathode follower and any voltage variation at its grid produces a similar variation at the cathode. Therefore, the cathode voltage of V6B varies in step with the DC potential on the grid of the video amplifier. Since a portion of the cathode voltage of V6B is directly coupled through R7 and R49 to control conduction of V8B, AGC voltage will be developed in proportion to signal strength.

This circuit also has its share of cathode-to-heater shorts, this time in V6B. When a short occurs, it always results in a change in the resistance of R73. Thus, when a tube corresponding to V6B in these circuits is found to have a cathode-to-heater short, repair cannot be considered complete unless R73 or its equivalent is checked, even though replacing the shorted tube restores receiver operation.

Troubles

There are three distinct types of troubles common to keyed AGC systems: (1) Troubles due to poor filtering of the control voltage. (2) Troubles associated with incorrect distribution of the control voltage. (3) Troubles connected with incorrect levels of AC voltage. We will discuss only the third type.

In Fig. 7, a series of photos show the effects of incorrect AGC voltages. Fig. 7A is the result of extremely excessive AGC, Fig. 7B shows more than normal AGC, and Fig. 7C shows the absence of AGC. This range of various AGC voltage levels can be simulated in some sets by varying the AGC control. In many sets, however, the range of the AGC control is not this great. Actually, the more the contrast can be overloaded by adjustment of an

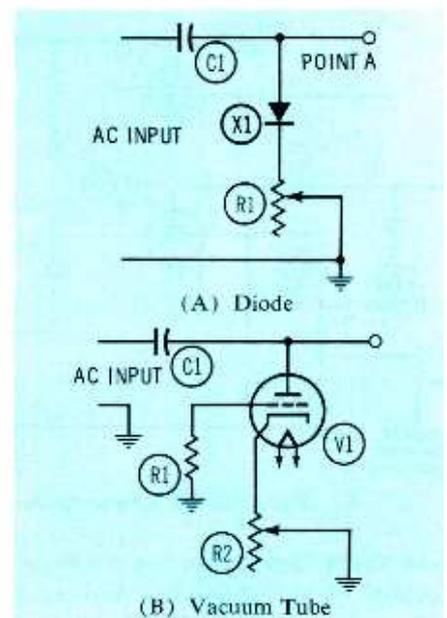


Fig. 2. Control of rectified voltage.

AGC control, the greater is the gain of the signal stages. If the more severe conditions (negative picture or whiteout) cannot be attained in some sets, a weak tube in the RF, IF, or video amplifier is indicated.

Because keyed AGC systems involve other stages in the receiver and depend upon the horizontal-deflection system, an AGC defect can produce abnormal operation in the associated stages. It is more probable that a defect in any of these stages will produce AGC troubles. The video amplifier is the stage most often responsible for improper operation of a keyed AGC circuit. Many AGC troubles would more accurately be called video-amplifier trouble if it were not true that it is easier to recognize abnormal AGC voltages than abnormal voltages on a video-amplifier stage.

Many cases of an open series-peaking coils, corresponding to L21 in Fig. 3, produce a dead, blanked-

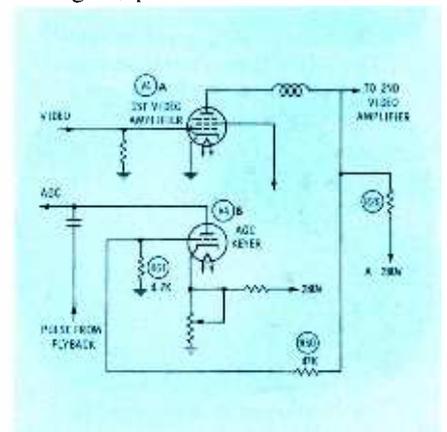


Fig. 4. Source of cathode voltage.

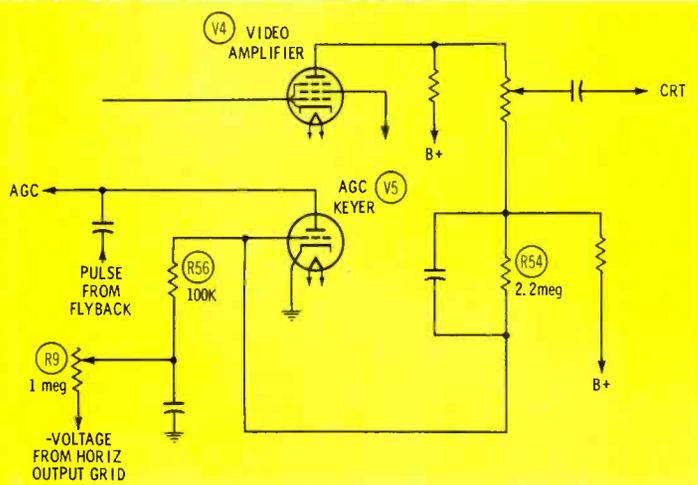


Fig. 5. Circuit with grounded cathode.

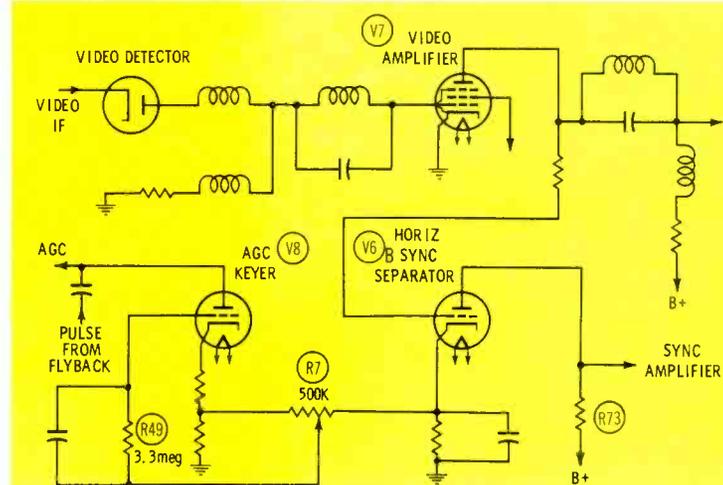


Fig. 6. Use of buffer and amplifier.

out raster identical to the condition caused by an excessively overbiased IF section. When a VTVM indicates about -50 volts on the AGC line, it is accepted as further proof of AGC trouble. But with additional checking, it will be found that the video-amplifier plate has zero volts while the plate end of the video-am-

plifier load resistor has as much voltage as is found at the B+ end. Furthermore, it will be found that both the grid and the cathode of the keyed AGC tube have identical voltages, thereby producing maximum conduction and maximum AGC voltage.


Just as common is the condition in which the contrast control, connected similarly to R1 of Fig. 3, opens. Symptoms are exactly like the preceding case; a blanked-out dead raster and excessive AGC voltage. Here again the excessive AGC is likely to be discovered before the open contrast control is pinpointed as being the trouble source.

Considering this last condition, a fairly recent circuit uses this principle in its motor-tuned channel-selector version (Fig. 8). While the station selector is in motion, the cathode of the video amplifier is ungrounded, muting sound and producing a blanked-out raster, because the AGC supplies excessive AGC to the IF and RF stages. When the selector stops on a station, the video cathode returns to ground, restoring normal AGC to IF and RF stages, and producing normal picture and sound.

One case of washed-out contrast with poor sync looked suspiciously like an AGC defect, and suspicions were stronger after it was found that the AGC voltage was about twice its normal value. When voltages on the AGC tube seemed about right for the amount of AGC voltage developed, the signals to the video amplifier were scoped. At the output of the video detector, point A in Fig. 9, excessive signal levels with clipped sync were found. But at the grid of the video amplifier, point B, the scope showed the same signals greatly diminished. An ohmmeter was used in the circuit to check L23 and R36. After the meter showed these components were good, V6 was replaced, eliminating the trouble. Obviously the control grid of V6 had some unusual characteristic, and if the picture had been merely washed out without the clipping it would have been suspected more quickly.

In addition to troubles originating from defects in the stage preceding and controlling the keyed AGC stage, which invariably produce incorrect bias on the keyed AGC tube, other AGC troubles are caused by the other voltage parameters of the AGC tube.

• Please turn to page 57

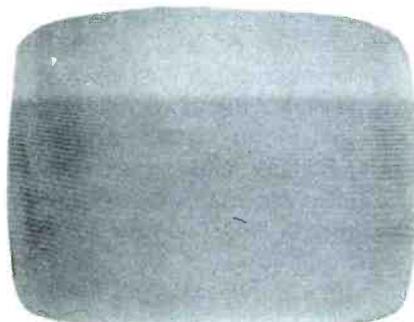

(A) Excessive AGC voltage



(B) More than normal voltage



(C) Absence of AGC voltage

Fig. 7. Visual AGC symptoms.

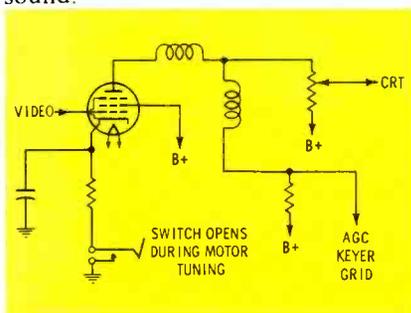


Fig. 8. Cathode lead opened during automatic tuning.

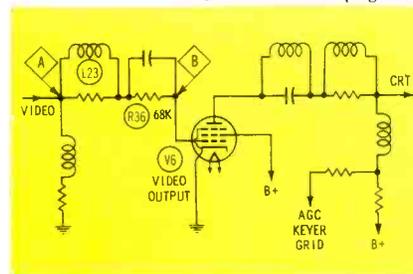


Fig. 9. Bad V6 produced odd symptom



The "Visiting Hot Shot" remembers some basic principles.

by Jack Darr

I walked into my Little Buddy's shop one afternoon, and right away he yelled, "Hey! I got one for you! It'll make a dandy article!" People are good to me, always bringing me things for material. (Actually, I get enough dogs in my own joint, but no matter.) Anyway, this was an Admiral 25H6 color chassis, and it had about the worst defocused picture I'd ever seen; nothing but great white blobs of light. Since they did move, you could tell they were parts of a picture, but that's all.

"O.K.," I said, in my best 'Visiting Hot-Shot' voice. "Check the focus rectifier tube."

"Did. It's O.K."

"Substitute a new one?"

"Yep. No difference." (End of Diagnosis No. 1. It was only a little Tentative Diagnosis anyhow. Now for No. 2.)

"How about the focus control?"

"Makes no difference at all." (Diagnosis No. 1 woke up, stirred, and waved for No. 2 to take over.)

"Well! Maybe it's open. How's the focus voltage?"

"Dunno. Didn't check it."

"Let's see. Gimme that meter. Aaah—pin 9 on this tube, isn't it?"

"Yeah. This is a 25FJP22."

I check on pin 9. Hmm. Nothing. We looked at one another, and Diagnosis No. 2 sat up and smiled heartily, feeling better all the time.

"Well, well. How's the high voltage?" This was on general principles; at this time I didn't think there was anything wrong with it. After all, I could see some fairly bright blobs on the screen.

"Didn't check it yet."

"Let's. Hand me that HV probe, huh?"

He had the doghouse open, so I touched the probe to the 3A3 socket-

cup. "Hey! Look at this! 15,000 volts."

"Well, that's good." said LB.

"Good? Whoa! This is a color set! How about getting it back up to 25,000 volts where it belongs?"

"Oh. I forgot."

"Well, stop forgetting. How about the regulator current? And the regulator tube?" (Diagnosis No. 2 sighed and sat down again. Diagnosis No. 3 got up, stretched and got ready to take over.)


"Pull the cap off that 6BK4, and turn the set on," I said, holding the HV probe where it was. He reached for the tube cap, hit the HV lead, used some simply shocking language, and finally managed to get the 6BK4 plate disconnected. He sat back on his heels and looked at me." "Hey, y' know what? I just remembered. When I turn this thing on, a picture comes on, just for a couple of seconds, then it goes all fuzzy like that!"

"Well, turn it on now and let's see what happens."

He did. The tubes warmed up, and sure enough, a fairly good,

slightly green picture came on. Then "Zap! Zap! Zap!" Big fat blue sparks shot back and forth everywhere in and around the flyback. We both grabbed at the cheater cord, and finally got it pulled out. In the midst of the melee, I noticed that the HV meter had slapped against the peg at 30,000 volts. (Diagnosis No. 3 brightened up and appeared to gain weight.)

We looked at one another. "Well, that takes care of the high voltage," I said. "Looks like that's high enough! OK, unhook the cathode of the 6BK4." He picked up the soldering iron and unhooked the yellow wire. We clipped the meter in the circuit, set on the 1.2-ma scale. (Diagnosis No. 3 tapped me on the shoulder and reminded me about vacuum tubes and their grid bias under certain conditions. So I reached over and set the meter up to the 12-ma scale, just in case. Of course, it was *his* meter, but I could never stand to see a grown man cry.) After clearing a good solid ground where one of the alligator clips had

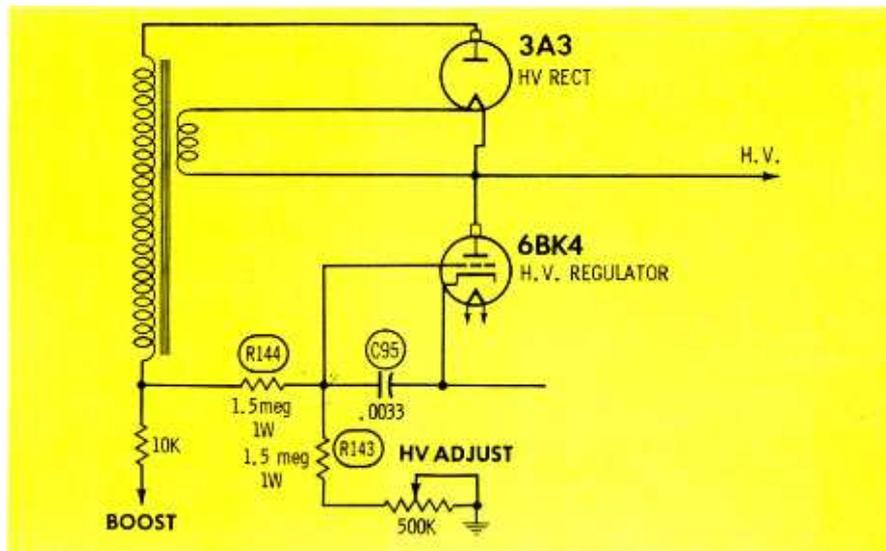

slipped and replacing the 6BK4 plate cap, we turned it on again. Oh, ho! Sure enough, the picture did come on for about 2 seconds, then went fuzzy. When it did, the 6BK4 plate current rose gently to about 3.0 ma!

"Turn the HV adjust control," I said. He did. Nothing happened. Diagnosis No. 3 thickened a little around the waistline. "Well, well, Turn it off and let's look underneath this thing."

He did this, and we located the bias resistors, a pair of one-watt 1.5-meg types on a terminal strip. "OK. Check 'em," I said, handing him the meter leads. "One of 'em ought to be open, or away off-value, or something." Diagnosis No. 3 nodded and smiled happily.

"O.K.," he said, turning the VOM to "Ohms X 100." "Hey R143 is open!"

"Good!" I said happily. Diagnosis No. 3 beamed approvingly over our shoulders. "Now check R144 just for luck."

He did. "Reads about a half-meg."

"Well, well. OK, pull 'em loose and let's see about putting in some that will be a little bit closer to the schematic value, huh? That's it. The bias is so far off that the regulator tube is pulling the HV way down." Diagnosis No. 3 patted me on the head.

He unhooked the junction of the two resistors. I handed him the meter probes again, and said "Let's check 'em again just to make sure we didn't have any parallel paths in there." Actually, I couldn't think of any in that circuit, but I felt like being sure. He touched the prods to the resistor, and then stood there with a very funny look on his face. "It's OK! Reads exactly 1.5 megs!"

"What? Are you sure?"

"Try it yourself," handing me the prods. I got down on the prayer bones and did. Sure enough, R143 now read a solid 1.5 meg, right on the nose. So did R144. Diagnosis No. 3 looked a bit sheepish.

"Check the ohmmeter!" I said, in desperation. He gave me a nasty grin, and handed me a 1% one-meg resistor I'd given him some time ago just for this purpose. I checked it, and sure enough, it was one meg right on the nose. Hmmm. The Visit-

ing Hot-Shot looked pretty bad at the moment. So, just to have something to do, I checked the resistors again. Oh, oh. "Hey! Now look. This reads completely open!"

"You got a bad connection," he said.

"Nope, look at it. Tight and firm. Now, let's try the other one." I moved the prods, and gulped; it read 1.5 meg. Back to the first one, which now also read 1.5 meg. Light dawned; I shorted the meter prods, and grinned. "Look, Maw—no continuity!"

When I wiggled the meter leads the reading 'came and went!' Investigation showed that not one but both test leads were broken inside the insulation! After some pungent comments, we pulled the wires out, trimmed them back and resoldered them. Now, back to work.

Both resistors read 1.5 meg-ohms, just as before. Diagnosis No. 3 gulped, and got a lot thinner and sort of airy-looking; in fact, you could see right through it in places. To look busy, I checked on the terminal board where the resistors had been hooked. There wasn't anything there but C95, a little ceramic capacitor with a piece of fishpaper on its leads. All of a sudden, Diagnosis No. 3 jumped up, and hit me smartly on the top of the head. I was getting a low reading from both ends of the thing! As it was now (cathode lead open, and all resistors taken loose) I shouldn't be getting *any* resistance readings!

Little Buddy looked at me inquiringly, as if he wanted to know why I had that funny look on my face. Pulling my diagonals out of my pocket, I haggled off the ends of the leads and took the capacitor completely out. Now, there wasn't any resistance at all on the terminal board!

Hooking the ohmmeter leads across C95, it turned out to be an RC network consisting of a capacitor in parallel with about a 5,000-ohm resistor! Since the schematic showed it differently, I felt better, and Diagnosis No. 3 was looking positively smug.

"Got a double-0-3 ceramic?" I asked.

"Sure," he said, scrabbling in a drawer. "Here." I stuck the resistors

back in place, then put the bit of fishpaper on the new capacitor leads. (This was put on there to space the leads so that they'd work as a spark gap in case of catastrophe.) Soldering it in place, I got up off my knees, painfully.

Turning the chassis down, we hooked the meter into the 6BK4 cathode again, leaving it on 12-ma scale just for luck. I sneered at Diagnosis No. 3, which was looking most insufferably smug, crossed my fingers behind my back, and turned the thing on.


The meter came up to about 2.0 ma as a fairly well focused raster and picture came on. Setting the HV adjust, we got just a bit over 1.0 ma for an average raster, and the HV now sat nicely at about 24,000 volts. Diagnosis No. 3 chortled happily in my ear. LB said, "Hey! That looks more like it! Thanks a lot!"

"Nothing to it," I said, in my most obnoxious 'nothing that any good high-grade genius couldn't have done' voice. I left, with Diagnosis No. 3 trailing after me, burbling in glee and ignoring my mental plea to 'Aw, shut up, willya?'

The moral to this story: make up a diagnosis on each job, based on the observed conditions (Notice I didn't say 'observed facts'? There aren't any facts at this stage of the game; not until you have made some tests.) Diagnosis No. 1, of course, was a bad focus rectifier tube. No. 2 was trouble in the focus circuitry, but it didn't last long after we found that taking the HV regulator tube out of the circuit brought back the high voltage with a bang (literally). So, No. 3 was the HV regulator drawing too much current and overloading the output. By upsetting the proportions between HV and focus voltage, we got the badly defocused raster. The first suspect was the bias resistors. This was complicated by the test leads being intermittent. Which, by the way, was the reason that we read no voltage on the focus connection on our first test.

So, check your diagnosis as you go, being ready to change them at any time the facts don't support them. Also, make a habit of checking your test equipment, to be sure that *it* isn't bad, instead of the set!

▲

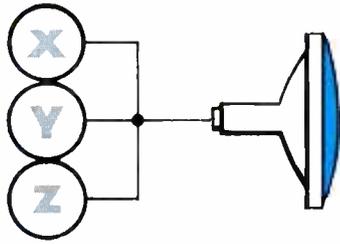

REPAIRING THE X-Y-Z color circuits

Typical troubles that can occur in these critical circuits.

by Homer L. Davidson

Have you ever had a color receiver screen change to a green or red color just five minutes before the set was to be delivered? You can bet that we have. So we like to fire up all of our new color sets for at least eight hours before delivery, though sometimes this plan doesn't work out. We also try to let a repaired set run for several hours before it is returned to the customer's home.

One new color set we recently worked on had a nice green cast to the black-and-white picture. Just about pea green. The back was taken off and a new R-Y amplifier tube inserted. We knew that the red was missing from the picture, so if it was tube trouble, the R-Y amplifier or X demodulator tube was at fault. We thought we were in luck as the original black - and - white picture popped in place.

The picture stayed white for about ten minutes and then turned to red. So we changed the G-Y and B-Y amplifier tubes, and the picture seemed to be good again.

At this moment a color broadcast was on the air so we switched to the local color station. The picture was predominantly blue and green with very little red, if any. Once in a while a light trace of red could be noticed with the tint control turned counter-clockwise.

It looked like the chassis would have to be pulled, but first a voltage check was made. We remembered when a CTC9 chassis gave us this trouble. Then the coupling capacitors from the plates of the X and Z demodulators to the output amplifier grid circuits had either shorted or had a high leakage. So the VTVM was placed on the grid of the R-Y amplifier of this new set, and sure

enough, a B+ voltage of 205 volts was present. The voltage at this point should be -1.5 volts with no signal.

All three .01 mfd coupling capacitors to the grids of the R-Y, B-Y, and G-Y amplifiers were replaced. Although this set was brand new, we couldn't risk this trouble recurring on a demonstration in the customer's home. The lack of red in

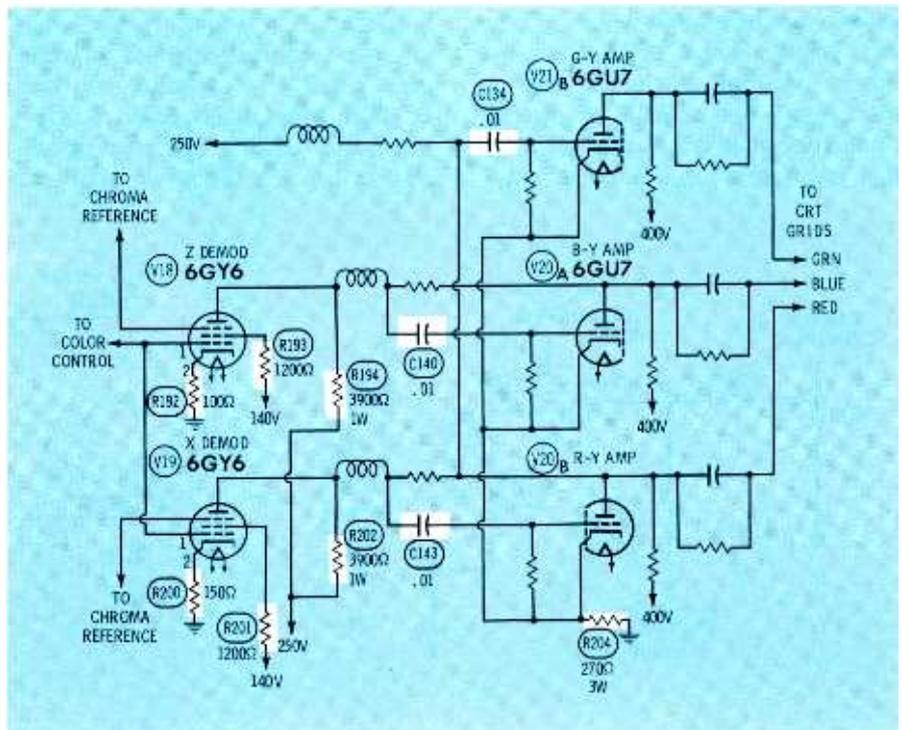


Fig. 1. RCA CTC17 circuit with most troublesome parts indicated.

the color program was due to a burned plate-load resistor, R202, in the X demodulator stage. The circuit is shown in Fig. 1. A heavy current had flowed through the resistor and the shorted coupling capacitor C143. As a result, there was no amplification in the X demodulator circuit and very little red on the screen.

The Black-and-White Picture

Let us take a new color set and actually see what happens when a few tubes are pulled in the XYZ circuits. Look at Fig. 1 and follow along. Disable the R-Y amplifier, V20B, by shorting the grid to the cathode. The screen turns cyan or bluish green. Put the R-Y amplifier back in operation and disable the B-Y amplifier tube, V20A. Of course, the blue is missing and the screen is close to chartreuse.

Now pull out the X demodulator then the Z demodulator tube, both type 6GY6. You will notice that the demodulator tubes affect only the color picture, not the black and white. This is good to remember when working on the XYZ stages.

The black-and-white picture may be upset by tubes, shorted capacitors or changing value of resistors in the R-Y, G-Y and B-Y circuits. Shorted or open elements in the color picture tube should also change the color of the black-and-white picture. When the color picture tube ages a few years, the black-and-white picture can change when the set is first turned on. This is due to one or more guns not coming up to full brightness when the set is cold. After the set warms up, the black-and-

white picture may not be too bad. A good color picture tube tester can be used to check the condition of the picture tube. If one of the guns is intermittent, generally a few light taps on the end of the picture tube cap will change the black-and-white picture.

Illustrative Cases

In an Admiral 24E2 color chassis there was very little blue in the color picture. The black-and-white picture was fairly good. So we pulled the Z demodulator tube, Fig. 2, and inserted a new one. Still there was no blue in the color picture. We checked the old 6GY6 demodulator tube and found it badly shorted. Just in case the new 6GY6 was defective, another was inserted in its place. Still no blue. R178, a 6,200-ohm resistor, had gotten quite warm and had decreased to 1000 ohms. Undoubtedly, when the 6GY6 had shorted, the increased current burned the plate-load resistor.

An RCA CTC10 chassis came in the shop with a completely red screen. Both grid coupling capacitors on the R-Y, B-Y amplifiers were shorted and the common cathode bias resistor was burned. The trouble cleared up when the R-Y, B-Y amp tube was replaced along with the defective parts. In the newer TV color chassis the common cathode resistor of the R-Y, G-Y, and B-Y amplifiers is a 3-watt type. Generally, this resistor will hold its value even if the grid capacitors do leak or short. Most newer color receivers have disc ceramic coupling capacitors as originals. These do not break

down as easily as molded ones.

In a brand new RCA CTC16XL chassis, the screen would become extremely red like an overdriven picture. This reddish color would still be in the picture when the tint control was turned to the extreme end of rotation. Another serviceman had changed the coupling capacitors and plate-load resistors in the X and Z demodulator circuits. We checked all previous wiring and parts replacements and everything seemed to be in place.

The capacitors, plate-load resistors, and X and Z tubes were all brand new. After voltage and resistance checks were made, we found the problem to be the cathode resistor of the X demodulator. This was supposed to be 150 ohms, but had decreased to 15 ohms. Replacing this cathode resistor returned the set to normal operation.

In Fig. 1, the XYZ circuits of a RCA CTC17 color chassis are shown with the most troublesome parts indicated. Good tube testers, VTVMs, and scopes are a must when servicing these circuits. When there is a loss of one color or a weak color, the scope will easily isolate the defective stage.

Color-Fidelity Circuits

In some of the newer color TV receivers a color-fidelity control has been installed to change the tint of the black-and-white picture. In many of these new receivers, the color-fidelity control is a potentiometer on the front of the TV receiver, while others use a switch to change the

• Please turn to page 74

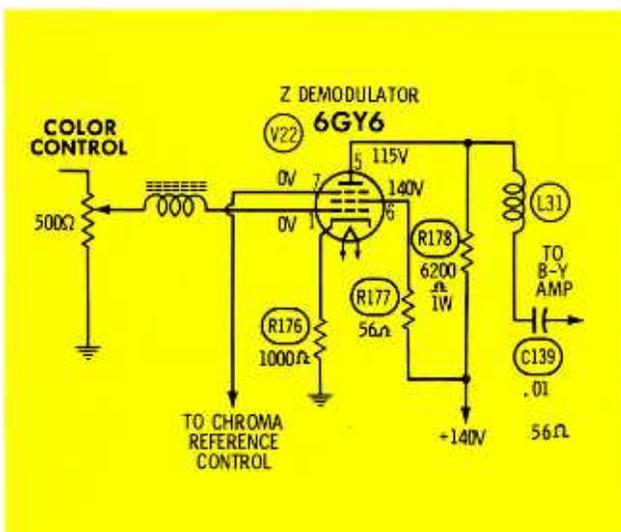


Fig. 2. Admiral 24E2 Z demodulator circuit.

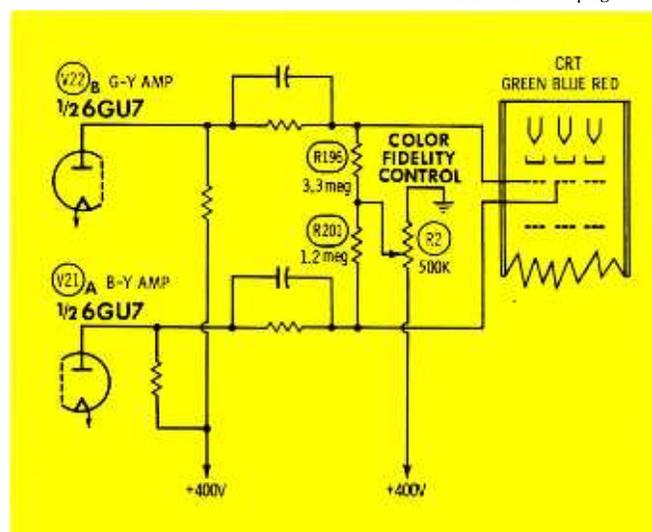



Fig. 3. Admiral G1263-1 color-fidelity circuit.

TUBE and TRANSISTOR DATA

RECEIVING TUBES

3AV2

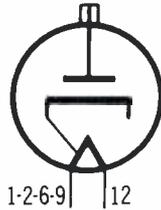High-Voltage Rectifier
 Fil.—3.15V @ 0.35A
 PIV.—38KV @ 2.2ma



12EW

2BJ2


High-Voltage Rectifier
 Fil.—2.3V @ 0.3A
 PIV.—20KV @ 1.0ma



9RT

8AR11

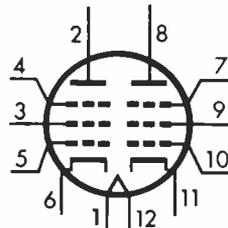
TV-IF Amplifiers
 Fil.—8.4V @ 0.6A (11 sec)



12DM

6BK4B

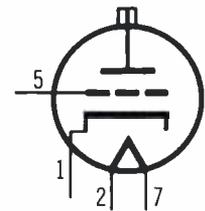
High Voltage Regulator
 Fil.—6.3V @ 0.2A
 Higher plate dissipation than 6BK4A



8GC

8BA11

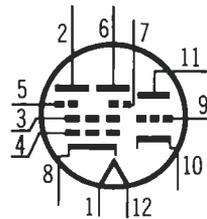
Pentode—Sync Separator
 Triode—Vertical Oscillator
 Fil.—8.4V @ 0.45A (11 sec)



12ER

14BL11

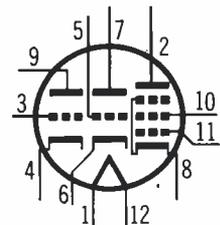Pentode—Video Amplifier
 Triodes—General Purpose
 Fil.—14.2V @ 0.45A (11 sec)



12GC

3BF2


High-Voltage Rectifier
 Fil.—3.6V @ 0.225A
 PIV.—35KV @ 2.2ma



12GQ

6BN11


TV-IF Amplifiers
 Fil.—6.3V @ 0.8A

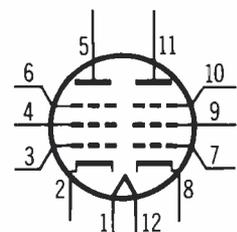

12GF

12BF11

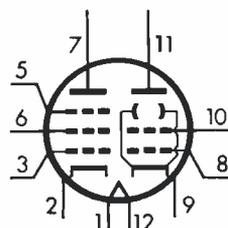
Pentode #1—Audio Output
 Pentode #2—Audio Detector
 Fil.—12.6V @ 0.6A (11 sec)



12EZ

14BR11

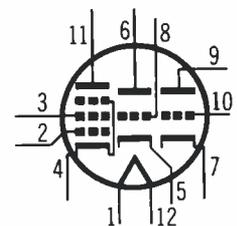
Pentode—Video Amplifier
 Triodes—General Purpose
 Fil.—14.2V @ 0.45A (11 sec)



12GL

11BT11

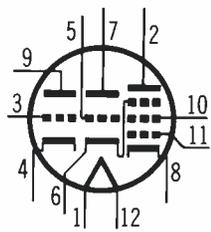
Pentode—Video Amplifier
Triodes—General Purpose
Fil.—10.7V @ 0.6A (11 sec)



12GS

6CH3


Damper
Fil.—6.3V @ 2.5A
PIV.—6KV @ 350ma

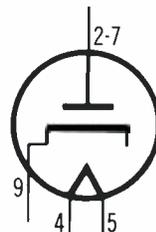

9HP

8BU11

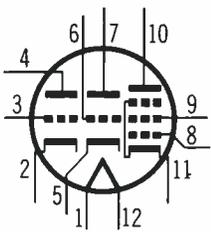
General Purpose
Fil.—7.8V @ 0.6A (11 sec)



12FP

11FY7

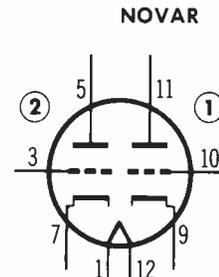
Triode #1—Vertical Oscillator
Triode #2—Vertical Output
Fil.—11.0V @ 0.6A (11 sec)



12EO

17BZ3

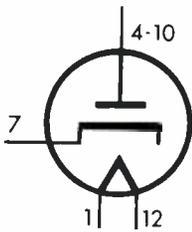
Damper
Fil.—16.8V @ 0.45A (11 sec)
PIV.—4.5KV @ 200ma



12FX

5GS7


VHF Converter
Fil.—5.4V @ 0.45A

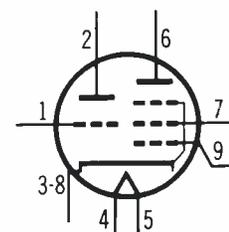

9GF

6CG3


Damper
Fil.—6.3V @ 1.8A
PV.—5KV @ 350ma

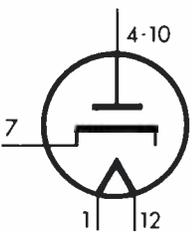

12FX

18GV8

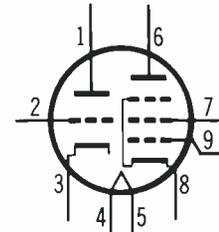Pentode—Vertical Output
Triode—Vertical Oscillator
Fil.—18.0V @ 0.3A




9LY

CATHODE-RAY TUBES

19ENP4A

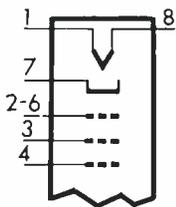
Protection—tension band
Deflection—114°
Filament—6.3V @ 0.45A (11 sec)
Grid 2—50V



8HR

19EUP4

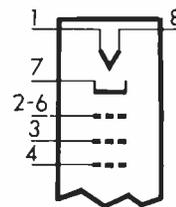
Protection—tension band
Deflection—114°
Filament—6.3V @ 0.6A (11 sec)
Grid 2—400V




8HR

19EXP22


Protection—none
 Deflection—90°
 Filament—6.3V @ 0.8A
 Grid 2—400V
 Rare-earth phosphor

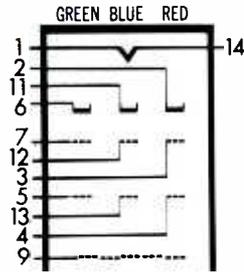**14BE****23EWP4A**


Protection—tension band
 Deflection—114°
 Filament—6.3V @ 0.45A (11 sec)
 Grid 2—400V

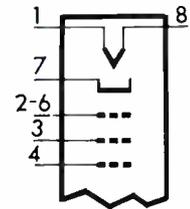**8HR****19EYP22**


Protection—bonded glass
 Deflection—90°
 Filament—6.3V @ 0.8A
 Grid 2—400V
 Rare-earth phosphor

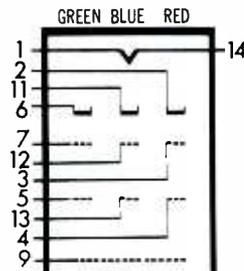**14BE****23FKP4**


Protection—bonded glass
 Deflection—94°
 Filament—6.3V @ 0.6A (11 sec)
 Grid 2—500V

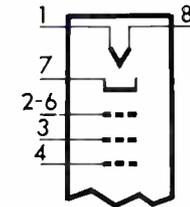**8HR****19FEP4A**


Protection—tension band
 Deflection—114°
 Filament—6.3V @ 0.45A (11 sec)
 Grid 2—30V

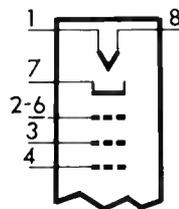**8HR****23GKP4**


Protection—filled rim
 Deflection—92°
 Filament—6.3V @ 0.6A (11 sec)
 Grid 2—300V

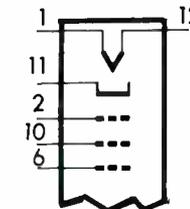**12L****19FTP4**


Protection—tension band
 Deflection—114°
 Filament—6.3V @ 0.45A (11 sec)
 Grid 2—400V

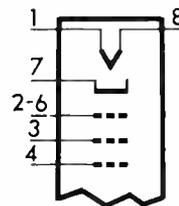**8HR****23GRP4**


Protection—filled rim
 Deflection—92°
 Filament—6.3V @ 0.45A (11 sec)
 Grid 2—300V

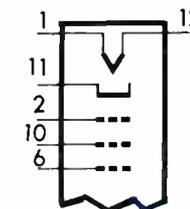**12L****21FZP4**

Protection—tension band
 Deflection—114°
 Filament—6.3V @ 0.45A (11 sec)
 Grid 2—400V

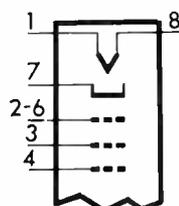
**8HR****23GSP4**

Protection—tension band
 Deflection—110°
 Filament—6.3V @ 0.6A (11 sec)
 Grid 2—300V

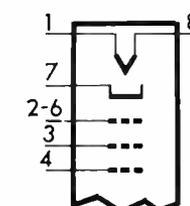
**8HR**

TRANSISTORS


2SB75B
Audio Amplifier
PNP—Germanium

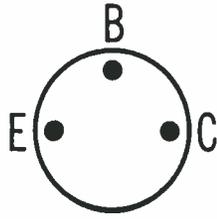


2SB185
Audio Amplifier
PNP—Germanium

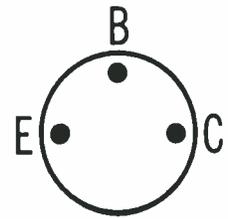


2SB77V
Horizontal Driver
PNP—Germanium

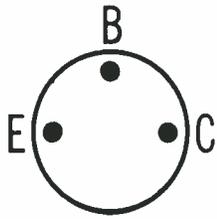


2SB187
Audio Amplifier
PNP—Germanium

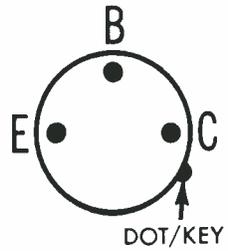


2SB135
Audio Amplifier
PNP—Germanium

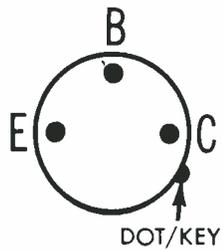


2SB217
Audio Amplifier
PNP—Germanium

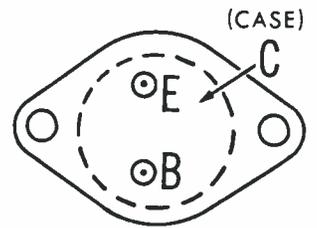


2SB171
Audio Amplifier
PNP—Germanium

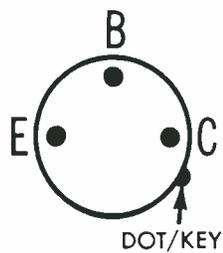


2SB274V
Vertical Output
PNP—Germanium

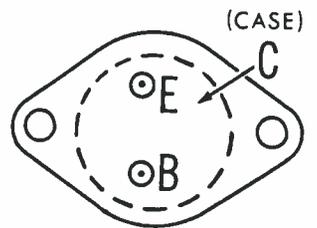


2SB176
Audio Amplifier
PNP—Silicon

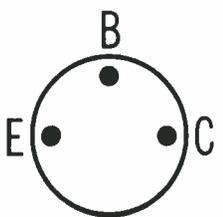

2SB365
Audio Amplifier
PNP—Germanium

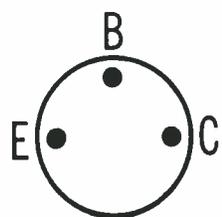

chasing troubles

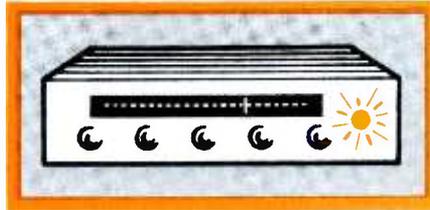

in stereo-on indicators

Repairing those troublesome indicators

by Jack Gamble

Modern FM stereo tuners employ various devices to indicate that the received signal is a stereo transmission. Neon bulbs, low-voltage AC pilot lamps, and meters are used as stereo-on indicators. Most of these devices are activated by the 19kHz pilot signal, which is a necessary part of the detected stereo signal. This article concerns the type of stereo-on indicator circuits in which a component failure will not effect stereo separation.

One circuit of this type utilizes a simple neon bulb and isolation network placed across the 19kHz or 38kHz tuned circuit in the decoding section of the receiver. The large AC

voltage across the parallel tuned tank is more than sufficient to ignite the bulb. Should the indicator fail to ignite, troubleshooting would be confined to the bulb or the resistive isolation network, provided stereo separation was not affected. Other components could prevent the bulb from igniting; however, they would also affect stereo separation.

There is one other possible trouble related to the neon bulb which should not be ignored. The ignition of the neon bulb can create noise. Since the neon indicator is normally mounted on the control panel, care should be taken to ensure that the leads to the bulb are not placed too close to the preamplifier circuits or

function switch. Lead dress could produce noise in one channel or both. Of course this source of noise would be present only when the indicator showed stereo-on. This trouble can be isolated by disconnecting the neon bulb while the noise is present.

The circuit shown in Fig. 1 is a popular, solid-state indicating circuit, using a No. 49 lamp as the stereo-on indicator. Transistor Q12 is employed as the 19kHz detector and transistor Q13 is a DC indicating amplifier. The supply voltage for both transistors is 6.3 VAC provided by a winding on the power transformer which is also used for the instrument pilot lamp. The 6.3 VAC is rectified by diode X10.

The desired result of the circuit is to forward bias Q13 when a stereo

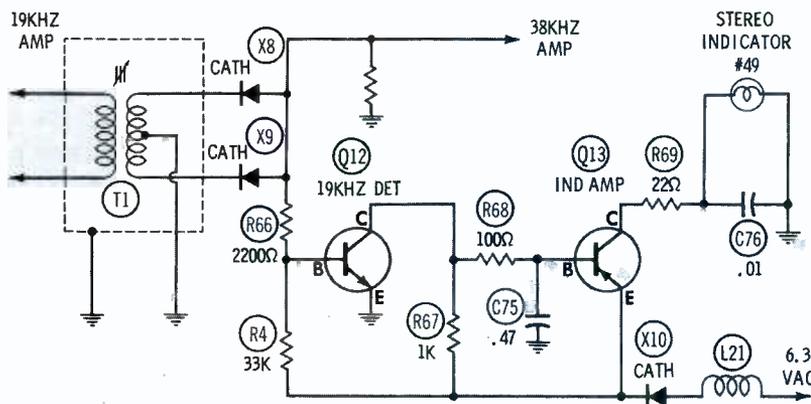


Fig. 1 Schematic Magnavox R204 EP chassis.

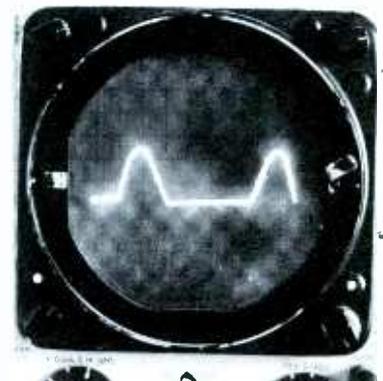


Fig. 2 Base waveform at Q2.

signal is being received. Stated another way, we want the base of Q13 to go less positive when the 19kHz pilot signal appears across the secondary of T1.

During monaural reception, both transistors offer high impedance through their emitter/collector circuits, limiting current flow to a negligible value. The 19kHz signal applied to the base of Q12 will cause current flow from emitter to collector through R67 to the power supply. The voltage drop across R67 causes the collector of Q12 to be less positive. This change causes the base of Q13 to become less positive, forward biasing it. With forward bias, the collector/emitter resistance of Q13 is lowered. Current will flow through the indicator lamp, resistor R69, transistor Q13, to the power supply.

Now for trouble analysis in this circuit: Suppose the indicator does not show stereo-on, and stereo separation is normal. Check the DC amplifier (Q13) portion of the circuit. An open component in the current path of the indicator lamp would prevent its working. The indicator lamp itself could be at fault; also resistor R69, transistor Q13, diode X10, or coil L21.

Here is a quick way of checking all components in the amplifier circuit: As you recall from our previous discussion, a decrease in collector/emitter resistance of Q12 forward biases Q13. We can simulate this condition with a resistor from the collector of Q12 to ground. Use a resistor about one fifth the value

of R67, or about 200 ohms. Another way to forward bias Q13 is to place a 100 ohm resistor across capacitor C75. If all components in the amplifier circuit are working the indicator will show stereo-on with Q13 forward biased.

Incidentally, this quick component check may be an answer to another possible service problem: A leaky C75 will keep the indicator reading stereo-on at all times.

The components most likely to open in the amplifier circuit are the indicator lamp and diode X10. The diode can be quickly checked by shunting a good diode across it. If the diode is shorted, the stereo-on indicator will be excessively bright on a stereo station. Keep in mind that a shorted diode may possibly cause repeated failure of the indicator lamp. In addition, with diode X10 shorted, the 6.3 VAC would approach 18 volts p-p and possibly damage the transistors.

The sensitivity and possible repeated failure of the indicator lamp are dependent on resistor R69. Initial production versions of this circuit used a 22 ohm resistor for R69. On later versions, the resistor was increased to 39 ohms. Approximately 50 mv of antenna signal are required for operation of the stereo-on indicator.

We mentioned previously that a leaky C75 could keep the stereo-on indicator glowing at all times. This capacitor is a necessary filter for the base voltage of transistor Q13. An open C75 could prevent the stereo-on indicator from working. Fig. 2

shows the normal scope pattern at the base of Q13 with the scope set to the line frequency. If C75 were open, 19kc would also be present at this point.

The base of Q12 has a positive .23 volts during monaural reception, and the collector has 6.3 volts. With a 19kHz signal of approximately 1.5 volts p-p on the base, the emitter/base junction acts as a diode detector. Thus, when 19kHz is present, the base voltage changes to zero and the collector to 1.9 volts. Resistor R4 is used to supply the base voltage and R67 supplies the collector voltage. While resistor failure in this circuit may affect its operation, the most likely component is the transistor itself.

Leakage between collector and base would lower the collector voltage during monaural reception and keep the stereo-on indicator operating. An emitter/base short of Q12 will prevent the stereo indicator from lighting during stereo operation. Should the emitter/base junction open, the voltage on the base would remain at .23 volts during stereo reception, and the indicator would not light. With the base/collector junction open, the base voltage will go to zero during stereo operation; however, the collector voltage will remain at 6.3 volts and the stereo indicator will not register stereo-on.

Fig. 3 shows another stereo-on indicator circuit. The 28 volt lamp is in parallel with Q2, the switch transistor. In this circuit Q2 is forward biased during monaural reception and reverse biased for stereo. During monaural reception the collector/emitter resistance of Q2 is low and acts as a shunt across the lamp. The collector voltage measures -3.6 volts and the emitter -3.39 volts. This leaves only about .3 volts across the lamp during monaural operation. When Q2 is reverse biased during stereo operation, the collector/emitter impedance is high; however, 20 to 25 ma. of current will now pass through R1, the indicator lamp, and R2. The voltage at the collector of Q2 changes to -18 volts, placing about 15 volts across the lamp—sufficient voltage for illumination.

Q2 is reverse biased by the con-

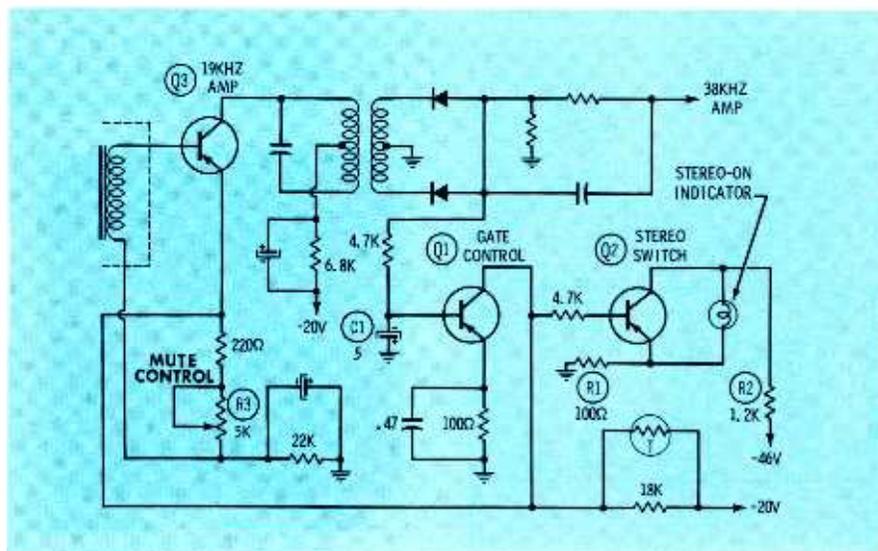


Fig. 3. Schematic Zenith 1N26T24.

duction of Q1, the gate-control transistor. Q1 is dependent on a 19kHz signal of sufficient amplitude to start Q3, the 19kHz amplifier, conducting. The sensitivity of Q3 is controlled by the setting of the mute control R3.

Both the collector and base of the gate-control transistor are driven negative by conduction of the 19kHz amplifier. The base control for the gate transistor is taken from the 38kHz doubler circuit. The 38kHz negative pulses are filtered by capacitor C1, a necessary filter for proper operation of the stereo-on indicator.

Summarizing the operation, Q2 is forward biased for monaural operation and reverse biased for stereo. This is in contrast to Q1, which is reverse biased for monaural and forward biased for stereo operation.

Let's look at Q2 and its circuit. Transistor problems such as open elements or base/emitter shorts would keep the stereo indicator on at all times, provided R1 and R2 have proper values. Difficulties within the transistor could be diagnosed effectively by checking voltages.

The stereo indicator switch-circuit can be checked by placing a 100 ohm resistor from base to ground. This will zero bias the transistor, and the indicator should light if collector circuit components are okay.

Q1, the gate-control transistor, must be forward biased in stereo operation. Approximately 1.7 volts p-p on the anodes of the 38-kHz doubler diodes is coupled to the base of Q1. The signal is filtered by C1, resulting in a $-.4$ volts on the base. Q1 base voltage measures zero for monaural operation. A shorted C1 would keep the base voltage at zero and prevent the stereo indicator from showing stereo-on.

If the base voltage of Q1 changes from zero to $-.4$ when tuning from monaural to stereo, the emitter voltage will change from zero to $-.2$ volts. If the emitter voltage does not follow this pattern, check the 100 ohm emitter resistor and bypass capacitor. If the resistor and capacitor are good, change the transistor. In the foregoing, we have assumed a negative voltage on the collector; otherwise the stereo indicator would be on.

Fig. 4 is the schematic of an indicator circuit using a 1K ohm meter movement. Even though this system is dependent on proper stereo separation before the meter reads stereo-on, several components can keep the meter indicating stereo-on during monaural reception.

Before discussing the possible trouble spots, let's have a quick review of circuit operation. A signal from the 19kHz amplifier stage is coupled through stereo-threshold adjustment R4 to the base of Q14, a 19kHz switching amplifier. From the collector of Q14, the 19kHz signal is R-C coupled to the base of Q15. Q15, another 19kHz switching transistor, is reverse biased for monaural operation and forward biased during stereo operation by a negative 19kHz voltage on its base.

The $-.7$ volts reverse-bias voltage for Q15 is developed by a voltage-divider network consisting of resistor R79 and diode X28. The diode is used to stabilize the voltage to a $-.7$ v.

During stereo operation the current through Q15 causes the voltage at point A to change from -20 volts to approximately -5 volts. The voltage at point A is also the collector supply for the 38kHz oscillator transistor. When the voltage at point A is lowered (or swings in a positive direction), the oscillator starts and injects a 38kHz signal to the demodulator circuits, resulting in stereo separation. The function switch on the control panel must be in the *FM Stereo* position to complete the emitter circuit of the os-

illator. The stereo-indicator meter functions at all FM positions of the function switch, and when Q15 is forward biased, the indicator will read stereo-on.

Shorted or leaky capacitors C15, C16, and C25 can cause the meter to show stereo-on at all times. If the guilty capacitor is C15, the base voltage of Q15 will read negative during monaural reception, as opposed to a normal reading of zero volts. If the voltage at the base of Q15 is zero, check voltages at points A and B. If these voltages are equal, C16 should be suspected. (Remember that the oscillator emitter circuit is disabled when the function switch is not in the FM Stereo position.) If the voltage at point B is less negative than point A, check capacitor C25.

A shorted diode X28 would change the meter sensitivity and cause it to indicate on noise pulses during monaural operation. Remember, the emitter voltage of Q15 should read $-.7$ v at all times. A shorted X28 could be found by a voltage check at this point. Of course an open R79 would also create the same problem. (Resistors are not mentioned too frequently because surveys show that they constitute less than 5% of the defective components in most solid-state products.)

If diode X28 were open, a high negative voltage would appear on the emitter of Q15, reverse biasing the stage to such a degree that the stereo meter would not work. An

• Please turn to page 65


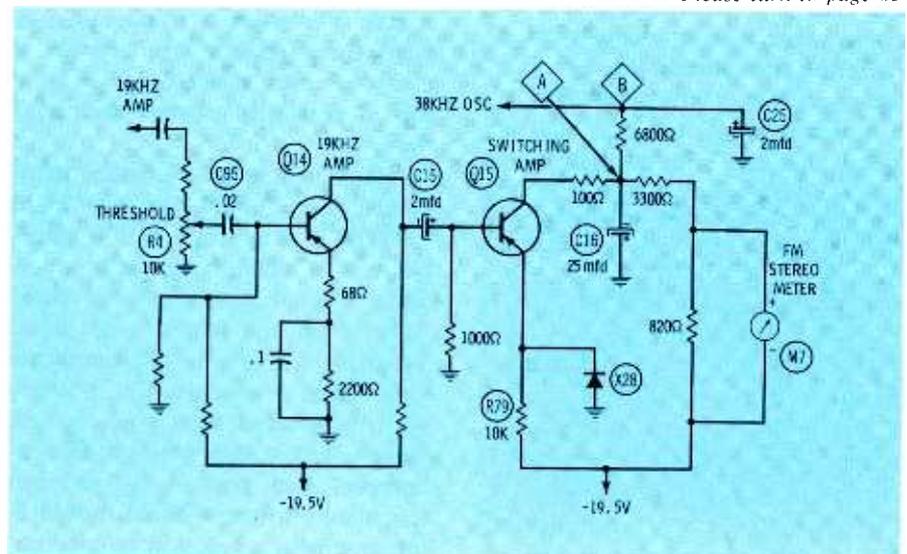


Fig. 4 Schematic Magnavox R201-05 chassis.

Leave those parts in the circuit

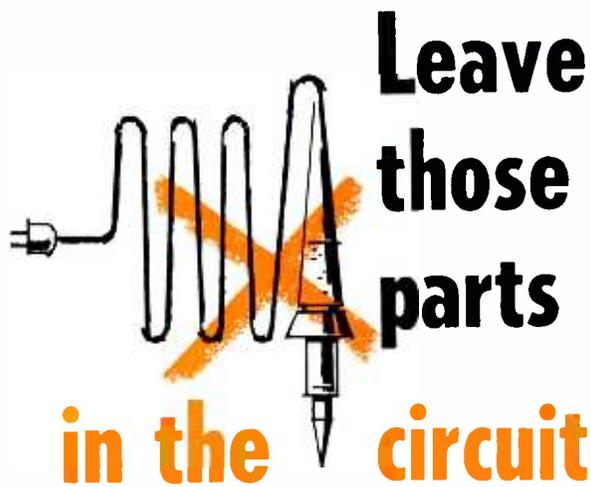

Forget that soldering iron for a while.

by Larry Allen

I had hardly settled down on the stool next to Jim when he suddenly grunted “Ouch!” and jerked his left hand away from the chassis he was working on. Stuck to the back of his hand were three small but painful splotches of solder—solder that had splattered there when a resistor lead finally responded to his heating and tugging.

Jim’s painful little accident brought to mind something I’ve seen in shop after shop: resistors, capacitors, coils, transformers—practically every kind of part—being needlessly clipped out or unsoldered from the circuit for testing. Since my reason for being at Jim’s shop was to teach him and his bench men some tough-dog troubleshooting tricks, I picked this occurrence as the starting point for a lengthy lecture on how to test components without doing so much soldering and unsoldering. You can’t test everything in the circuit, but it’s a good practice to test whatever parts you can without heating up

your soldering gun (and all the parts around it).

Importance of Test Equipment

Naturally, the more test equipment you have, the easier your troubleshooting should be. And it might presumably follow that much fancy test equipment would make it easier to test parts in the set, once you’ve pinned down the trouble to a specific area. That’s not necessarily so! Simple test instruments can give you a lot of information if you use them properly and know what they’re telling you.

You might think it is easier to clip parts out of the circuit, slap them on a component tester and then try to put the good ones back in where you found them, than it is to bother hooking up your basic test instruments. The truth is: You ought to have them hooked up anyway, if you’re serious about doing a good job in reasonable (and profitable) time.

What do I mean by basic instruments? You should have a VTVM (a VOM is okay if it’s 20,000-ohms-per-volt or better), an oscilloscope, and a signal generator—all three warmed up and ready at all times. To settle for less is to complicate your work unnecessarily, because with these three units you can test almost any component you’ll encounter. And, best of all, you can test many of them without unsoldering anything; a few will require unsoldering one lead.

It’s important to remember that you’ll often make two or three tests on a particular component. Use first the tests that require the least unsoldering, and whichever instrument is quickest or surest. Most of the tests will be conducted with your VTVM and scope. For some, you’ll need the signal generator.

Remember, too, that each of these tests is possible because of a component’s characteristics and the way it is used in the circuit. If you don’t know the principles of parts and their circuits, you may need to bone up a little before you can understand some of these tests. I’m going to show you the *what* and let you figure out the *why*. In every case, I’ll point out how to take shunt paths into consideration, for they are very important in evaluating the results of in-circuit parts testing.

Small-Value Capacitors

Think of capacitor testing in terms of the three faulty conditions you are most likely to encounter: open, leaky, or shorted. For Jim’s men, I divided my capacitor discussion among those three faults.

Seldom can you spot a faulty capacitor visually, unless a lead has broken off externally. You will use test instruments in one way or another. Depending on the capacitor value and type, the tests you make may be for all three possible conditions; sometimes a single test will suffice. Certain tests are good for

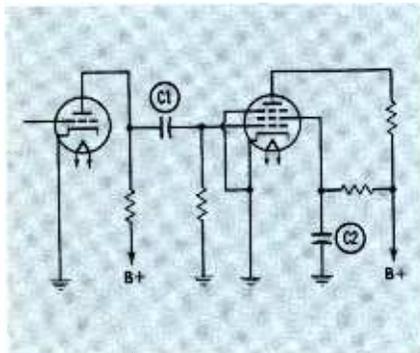


Fig. 1. Small-value coupling and bypass capacitors in a typical R-C amplifier.



Will the Amphenol Signal Commander spoil the TV serviceman?



The Signal Commander is shown here with the optional UHF plug-in and probe antenna in place, balun (left) and VHF plug-in.

You bet it will. You can count on Amphenol's new portable field strength meter to make light work of your color antenna selection, MATV and Stereo FM jobs.

Here's why:

1. **The Signal Commander gives new meaning to portability.** It runs on batteries, weighs only 3 1/2 lbs, fits easily into one hand. It's by far the most compact field strength meter you can use.
2. **You get laboratory quality,** including both relative and direct readings (in microvolts and db's with 2 scales).
3. **Modular construction includes VHF, UHF, FM.** We've designed the Signal Commander to grow with your business. To go with the VHF/UHF/FM modules already available, you'll soon be able to have communications plug-in modules for use without field adjustment.
4. **The Signal Commander costs less than any other meter on the market.**

Let the Signal Commander start making money for you. See your Amphenol salesman. Or write to Dan O'Connell, Market Manager for Service Products, 2875 South 25th Avenue, Broadview, Illinois 60153.



AMPHENOL

Circle 10 on literature card

one condition and certain component values, while another test may be more meaningful for that same condition with other component values.

Capacitors are connected either for coupling or for bypassing (decoupling). The latter units almost always have one end returned to ground or to B-, occasionally through a larger electrolytic. Certain tests prove more effective for particular circuit usages; pay attention to which test you should use for each circuit connection.

Open Capacitors

Probably the most difficult capacitor condition to diagnose is an open. Generally, one of the leads has separated from the foil inside the case of the capacitor. Testing isn't difficult or complicated, although there are several ways to find an open capacitor. First, let's consider coupling capacitors (C1 in Fig. 1).

If the capacitor is higher in value than .001 mfd, connect your ohmmeter leads (set turned off, of course) across the suspected unit. Unless there's a fairly low-resistance (5000 ohms or less) shunt path—through the grid resistor, ground, power-supply electrolytic, and plate resistor—you'll see a slight kick of the meter pointer; quickly reverse the ohmmeter leads and you should see another slightly greater kick. If the pointer remains at some resistance value, a shunt path is preventing your using this particular test. To eliminate this problem, unsolder one lead of the capacitor and make the test again. If there is absolutely no deflection with the ohmmeter connected either way, chances are the capacitor is open.

Another effective way to check a coupling capacitor for an open is by using the scope with a signal generator. You don't have to unsolder anything, and the test is effective for any value of capacitor, even below .001 mfd. The set is turned off and the generator connected to the input end of the capacitor. Generator frequency depends on the capacitor; Table 1 shows frequencies suitable for various values. Connect the scope directly to the generator lead and note the amplitude of the output waveform on the scope screen (the scope's sweep frequency is not important, since we are interested in signal amplitude). Next, move the scope probe to the other end of the capacitor. Unless the capacitor is open, there should be almost no reduction in the amplitude of the waveform. If the amplitude is reduced even half, the capacitor is bad.

A variation of this last test is possible without the generator. Leave the set turned on and check at both ends of the capacitor with your scope. If the normal signal going through the set is significantly reduced on the output end of the capacitor, the capacitor is faulty.

Testing for open bypass capacitors (C2 in Fig. 1) is slightly different. Connect the scope and generator leads together and note the amplitude of signal; then, with the set off, connect both leads—still connected together—across the bypass capacitor. If the capacitor is good, and the generator frequency is set according to Table 1, the amplitude will be reduced to half or less. If the amplitude on the scope screen remains the same, with or without the capacitor

Table 1.

10 pf	3kHz
100 pf	300 Hz
1000 pf	3 mHz
.01 mfd	300 kHz
.1 mfd	30 kHz
1 mfd	30 mHz

across the leads, the capacitor is open and the signal is not being bypassed. (A variation of this test is to check across the bypass capacitor with only the scope while the set is operating, but it is difficult to decide just how much signal is normal—some bypass capacitors aren't intended to bypass all signals that are present.)

Leaky Capacitors

Testing a leaky capacitor can be a bit difficult if the leakage is very slight or if the capacitor is used in a bypass configuration. Clipping an ohmmeter across the unit is not a good test. At the low voltage furnished by an ohmmeter, the capacitor may refuse to leak even slightly. On the other hand, your ohmmeter may not be sensitive enough to show slight amounts of leakage; you know how crowded most ohmmeter scales are at the high end.

Because of the nature of leakage, the best test is usually the open-end method, which requires unsoldering one end of the capacitor. Try this: If the capacitor is in a B+ circuit, such as C1 and C2 in Fig. 1, unsolder the end *not* connected to B+ (the grid end of C1 or the ground end of C2). With the set on use your VTVM (a VOM may not be sensitive enough) to measure DC voltage on the free lead. If any DC voltage is indicated at all, the capacitor is leaky. This open-end method is the most sensitive leakage test you'll ever need for a capacitor.

If the capacitor is not in a B+ circuit, you can still check it by this method if there is some DC voltage handy. If there is none, then leakage isn't likely to be much of a problem anyway; however, if you feel leakage might cause trouble in a critical application, you can break the don't-take-it-out rule and remove the capacitor from the circuit, tack one lead to a B+ source, and make the open-end test that way. The sensi-

• Please turn to page 68

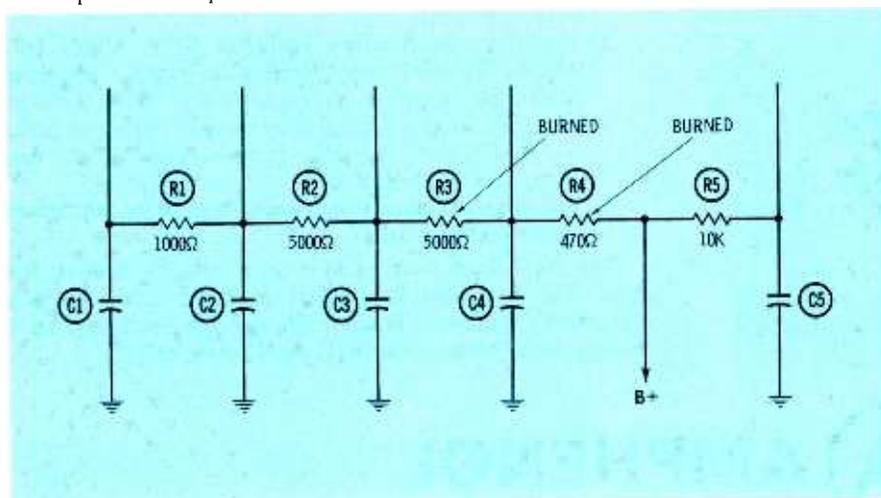


Fig. 2. Ohmmeter tests in this B+ feeder string quickly pinpoint exact fault.

Compare Color Generators

look at the rest... and you'll buy the best, new B&K model 1245

The all solid-state B&K Model 1245 Color Generator duplicates the waveforms transmitted by a color TV station.


Adherence to these waveforms makes it easy to converge the color tube, check sync and make other raster adjustments... and the color generator with station quality signal will be able to sync next year's sets. Generators with compromise waveforms do not give you this obsolescence protection.

Here are oscilloscope photographs from the outputs of two typical competitive color generators, one transistorized and one tube type, and the B&K Model 1245. The detailed analysis with each photograph shows a few of the reasons why you'll save time and effort with B&K.


COLOR

CROSSHATCH

STANDARD STATION SIGNAL

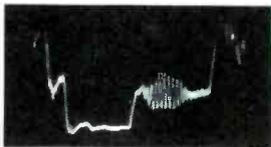


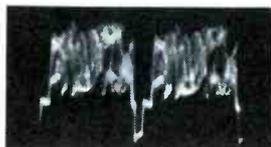One horizontal sync pulse with its color burst.




Two lines showing horizontal sync pulse with black and white TV signal.

TRANSISTORIZED B&K MODEL 1245

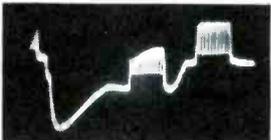


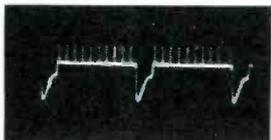Good duplication of station signal including back porch. If the set won't sync, the set is defective.




Well defined back porch on horizontal sync pulse permits accurately setting color killer and almost eliminates need to adjust brightness and contrast.

TRANSISTORIZED GENERATOR A

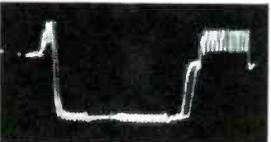


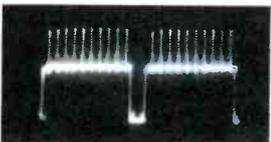No back porch causes unstable color sync. Burst amplitude compression may permit sync on wrong color bar.




Square wave horizontal sync pulse with no back porch and poor dc coupling forces adjustments of brightness, contrast & fine tuning to obtain usable pattern.

GENERATOR B

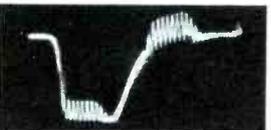


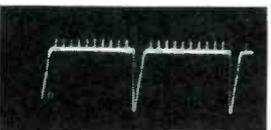No back porch; color information on top of sync-pulse makes sync difficult on some sets.



Complete absence of any back porch necessitates readjustment of brightness, contrast and fine tuning to obtain a usable pattern.

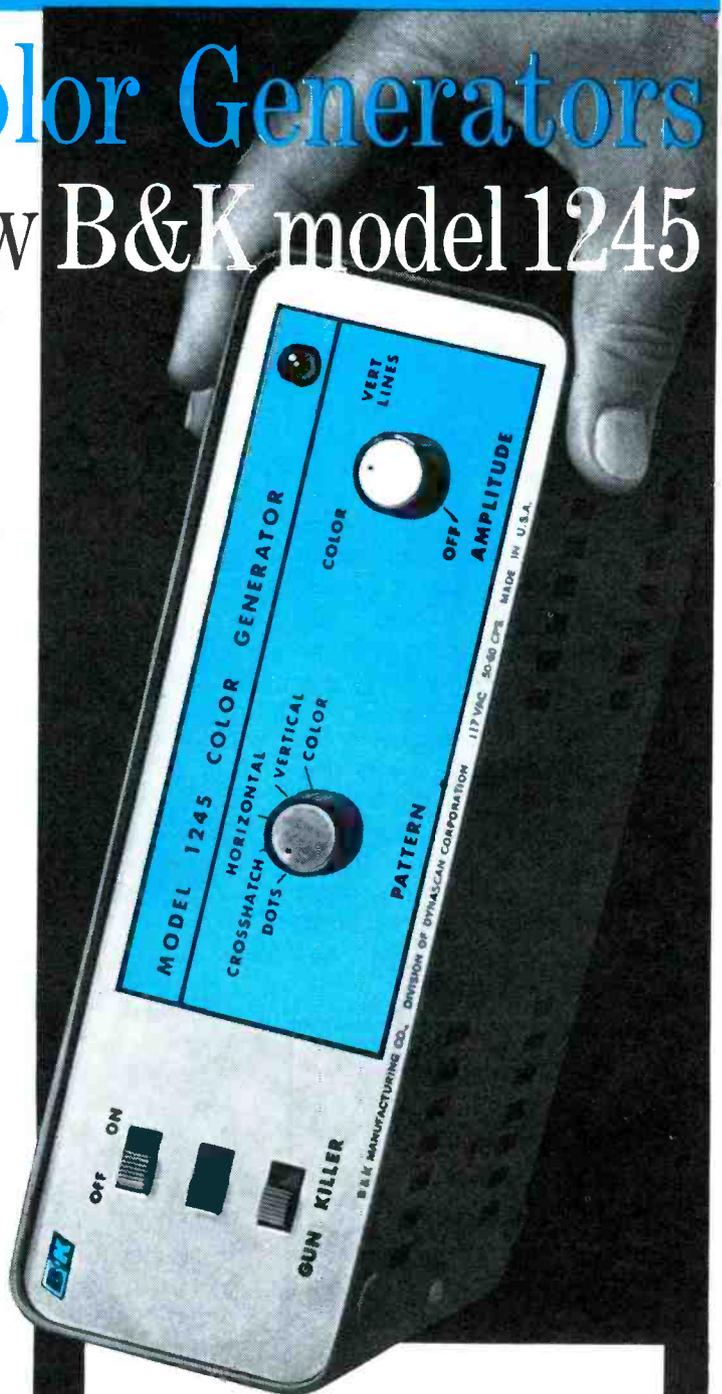See your B&K Distributor for a demonstration or write for Catalog AP22.



For the first time, with the no-compromise waveforms from the B&K Model 1245, it is possible to accurately set the color killer threshold control with a color generator.

The miniature size and convenience of the Model 1245 match its performance. It provides crystal-controlled keyed rainbow color bar display, and dot, crosshatch, horizontal line and vertical line patterns as well as gun killer controls that will work with any picture tube. Size only 2 7/8 x 8 1/2 x 8 7/8". Net \$134⁹⁵.



B & K MANUFACTURING CO.
DIVISION OF **DYNASCAN CORPORATION**
1801 W. BELLE PLAINE AVE. • CHICAGO, ILL. 60613

Export: Empire Exporters, 123 Grand St., New York 13, U.S.A.



Notes on Test Equipment

analysis of test instruments... operation... applications

by T. T. Jones

Industrial Scope

The instrument in Fig. 1 is a recent addition to Waterman Instrument Corporation's line of pocket-size oscilloscopes. Though very small in size, this is truly a professional instrument with full-size performance.

The scope has a frequency response which limits its use in television (see specs.). We did try it on a color set and found there were many tests we could make, though the horizontal pulses were somewhat rounded, and burst pulses completely missing on the back porch.



Fig. 1. Small and useful.

However, this scope was never designed for TV. It's an industrial scope, and in these applications it does very well. The triggered sweep is quite stable and locks down on very complex waveforms. In most industrial maintenance jobs, the equipment is so large that the repairman must bring his tools to the job. The OCA-11A is small and rugged enough to be carried anywhere. Some typical applications are shaker systems, welding equipment, servos, etc.

The internal construction of the scope is of very high quality. The display tube, type 3RP1 has an integral magnetic shield, and a viewing area $1\frac{3}{4} \times 2\frac{3}{8}$ inches. There are no vernier controls on the vertical and horizontal gain. However, the step attenuators have closely spaced steps which give adequate gain control. We measured the frequency response and found the scope to be flat within ± 1 db out to 22 kHz and 6 db at 70 kHz. Sine waves were visible at 600 kHz, though much attenuated. With the sweep rate at maximum and the

5 x horizontal expansion, it is possible to display one cycle of a 150 kHz waveform.

A companion model, the OCA-11B, has all of the features of the OCA-11A with exception of the time base which is continuously variable from 10 seconds to 1 millisecond.

For further information circle 72 on literature card.

Tube Tester

One piece of test equipment that gets a lot of mileage around the shop is the tube tester. Most of us hate to take it out of the shop though, because it is either too big, too heavy, or too fragile.

SENCORE has developed a fourth generation of their portable tube tester. Dubbed the "Mighty Mite IV," the model TC 136 continues the tradition of a small, rugged yet capable tester suitable for outside work as well as the bench.

The TC136 uses the proven circuits of the previous models, together with some refinements for added coverage of special type tubes. The index booklet has been revised and now has a latching device for one hand operation. The type is quite large and readable.

The Model TC136 checks all modern tube types from Nuvistors to Novars, including the new 10 pin types from Amperex and Mullard. The index gives data for the special tubes in

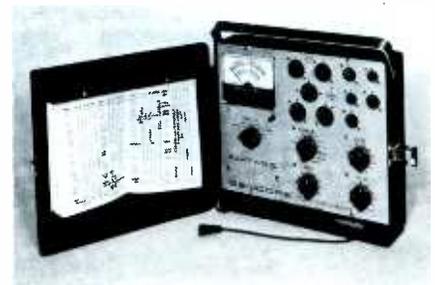


Fig. 2. Checks all modern tubes.

WATERMAN OCA-11A SPECIFICATIONS

VERTICAL CHANNEL:

Response; DC to 22 kHz \mp 1db usable trace to 200 kHz.

Sensitivity; compensated 12-step attenuator measures signal from 10 mv to 50 volts p/p per division. Impedance—1 megohm shunted by 30 pf.

HORIZONTAL CHANNEL:

Duplicate of vertical channel

Z—AXIS INPUT:

None

SYNC INPUT:

Automatic leveling, 1V to 50V. Impedance—1 megohm \mp 60 pf.

INTERNAL SWEEP:

4 decades plus vernier gives continuously variable sweep 3 Hz to 30 kHz, free-running or triggered.

OTHER FEATURES:

Horizontal expansion system 2.5 x and 5 x. Beam-deflection system swings beam off screen during retrace. Maximum input voltage above ground 600 V peak including DC component. Chassis ground may be isolated from signal ground with 10 megohms shunted by .47 mfd, 400 V cap.

SIZE:

(HWD) $7\frac{1}{4} \times 3\frac{1}{2} \times 13\frac{5}{32}$ "


WEIGHT:

9 lbs.

PRICE:

\$269.

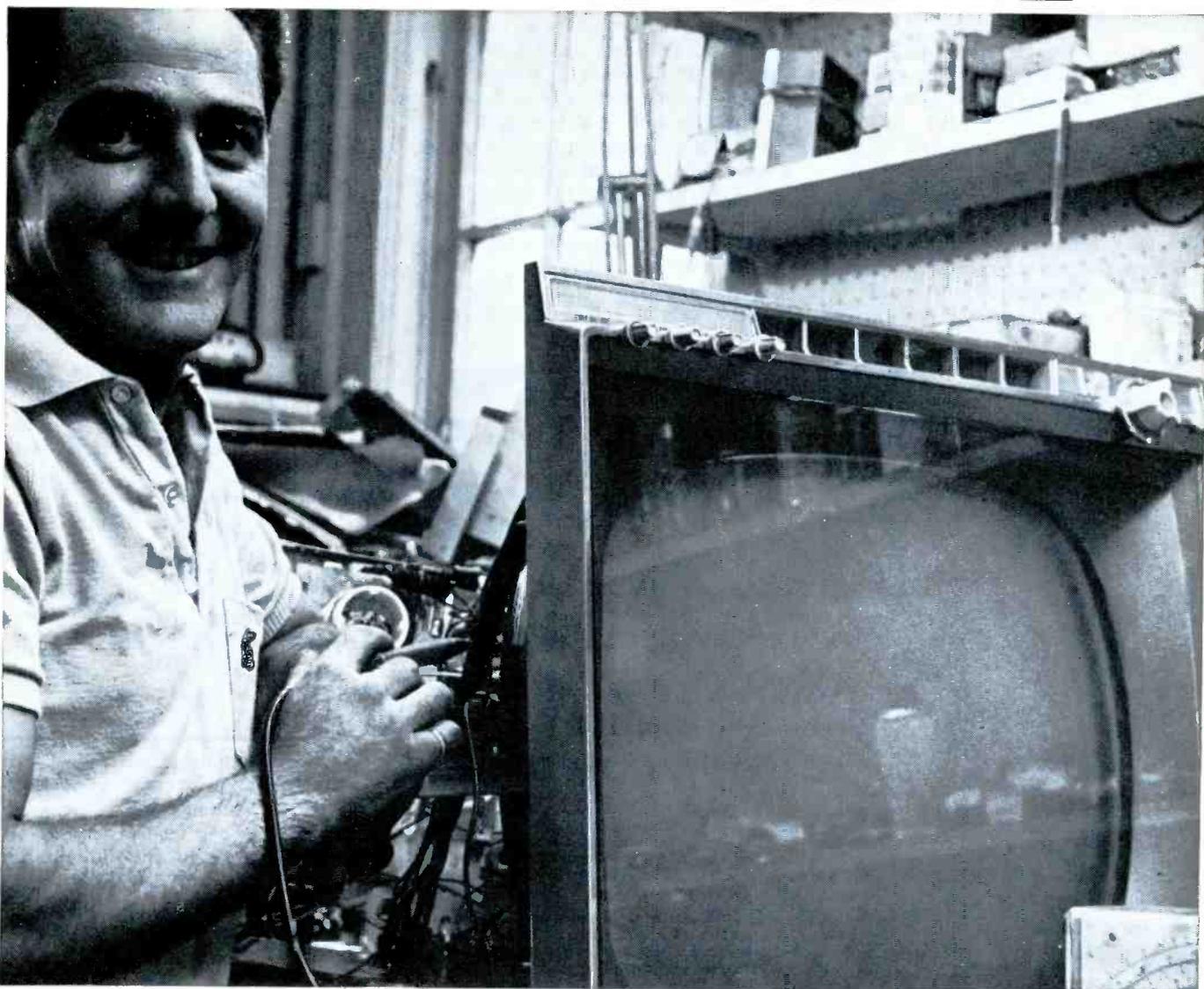Island-Wide gets the Action-People.* Do you?



"Yellow Pages made my business zoom," says Paul S. Fusco, Island-Wide Servicing, New Dorp, Staten Island, N.Y. "Before I started advertising in the Yellow Pages, my business was nothing. Now, I can barely keep up with it. I'm sold on Yellow Pages."

Advertise for action...



ISLAND-WIDE SERVICING

CALL **CAN-DO**
TV SERVICE

AUTO RADIO REPAIRS
Room Air Conditioning Service
351-3899
1694 RICHMOND RD. D.H.

HI-FI & STEREO CONVERSIONS
Color TV Service
Antennas & Repairing on

- RCA
- PHILCO
- ADMIRAL
- MOTOROLA
- G.E.
- ZENITH
- EMERSON
- PENNSYLVANIA
- SYLVANIA
- SILVERTONE
- WESTINGHOUSE

TV RENTALS



SERVICE

Same Day Service

Display ad (shown above reduced) runs under TELEVISION SERVICE. Call your Yellow Pages man to plan your program. Find him in the Yellow Pages under: ADVERTISING — DIRECTORY & GUIDE.

*The 3 out of 4 busy Americans who shop the Yellow Pages way.

Circle 12 on literature card

the 4-digit series and also foreign tubes, including Japanese.

The manual gives simple instructions how to use the tester for types too new to be covered by the index.

In use, the tester is fast and efficient. There are only four set-up switches.

The circuit is a type of VTVM. Cathode emission is measured by applying AC voltage to the grid of the tube under test, and measuring the pulsating DC at the cathode. The tubes are tested at or near their normal cathode current ratings.

The grid emission is measured by applying +40 volts to all elements of

the tube except the grid, which is tied to ground through a 10-meg resistor. Any voltage present across this resistor is measured by the VTVM circuit. Grid emission current of .5 μ a will produce a reading in the "bad" area of the meter. This is in the order of 100 megohms grid leakage.

Further information on the meter circuit can be found in the November, 1965 PF REPORTER. In that issue we tested the SENCORE TC131 bench-type tube tester, which has essentially the same metering circuit.

Like the earlier "Mighty Mite III," the new TC136 is housed in a sturdy

SENCORE Model TC136 Specifications

Tube sockets:

- 7, 9, and 10 pin miniature
- 8 pin octal
- 8 pin loctal
- 9 pin Novar
- 12 pin compactron
- Novistor

Tests performed:

- Cathode emission
- Grid leakage (sensitivity over 100 megohms)
- Shorts between elements (sensitivity up to 180-K ohms)

Test settings:

- Filament
 - 1 to 50 volts AC in 12 steps
- Load
 - 9 ranges of cathode current from less than .5ma to over 50ma.

Power Requirements:

- 105-125 volts AC, 50-60 cps, 7 watts.

Size: (HWD)

- 4" x 10 $\frac{3}{4}$ " x 10 $\frac{1}{2}$ " with cover installed

Weight:


- 9 lbs

Price:

- \$74.50

black wrinkle-finish steel cabinet with a detachable hinged cover. A compartment at the bottom contains the power cord and top cap lead. Throwing the function switch to the off position dampens the meter. These features and more add up to a rugged reliable instrument, equally capable in field or bench work.

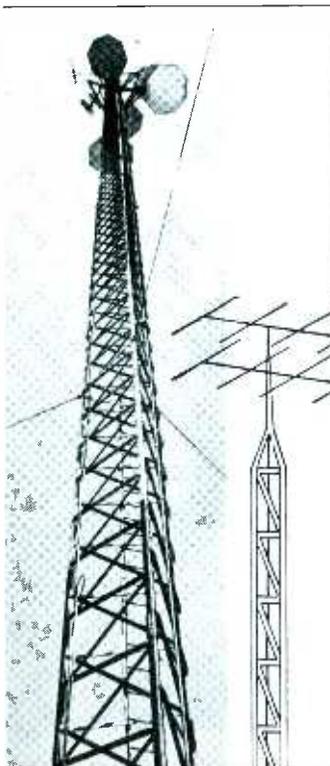For further information circle item 73 on literature card.



The most Famous Name in TOWERS of ALL KINDS!

Here are the advantages you get when you insist on ROHN TOWERS

LARGEST FULL RANGE OF TOWERS—you can get anything from home TV and amateur radio towers to heavy-duty communication and micro-wave towers. Included are 500 foot self-supporting towers, 1,000 foot guyed towers, "fold-over" and crank-up towers. Regardless of your needs, ROHN can supply it.


UNQUESTIONED LEADERSHIP IN DESIGN AND MANUFACTURE—you get the latest in advanced tower engineering. All communication towers are engineered to EIA specifications, and are proved by thousands of installations. No other manufacturer can surpass the quality and fine reputation of ROHN.

QUALITY MATERIALS AND WORKMANSHIP—Only highest quality steel is used which fully meets the specifications for the job. ROHN towers are hot-dipped galvanized after fabrication—a feature ROHN pioneered!

SERVICE WHEREVER YOU WANT IT—ROHN representatives are world-wide. Complete erection service for communication systems, broadcasting, micro-wave, and other needs is available; also competent engineering service to help you.

Settle for the BEST in TOWERS—ROHN—today the world's largest, exclusive manufacturer of towers of all kinds!

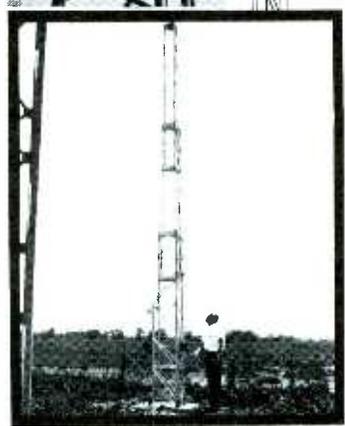For your needs, contact your local ROHN salesman, distributor or dealer; or write direct for information.



SEND THE HANDY COUPON INDICATING YOUR NEEDS


ROHN
Manufacturing Co.
BOX 2000
PEORIA, ILLINOIS

ROHN Manufacturing Co.
Box 2000
Peoria, Illinois

Send me complete literature on the following ROHN Products:

<input type="checkbox"/> Home TV Towers	<input type="checkbox"/> Amateur Towers
<input type="checkbox"/> Communication Towers	<input type="checkbox"/> AM-FM Broadcasting Towers
<input type="checkbox"/> Micro-Wave Towers	<input type="checkbox"/> Government

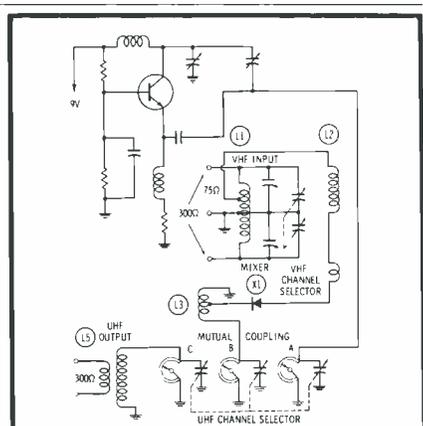
Name _____
Firm _____
Address _____
City _____ State _____



ERRATUM

In the April "Notes on Test Equipment" item describing the Lectrotech Model U-75 (page 46), the incorrect illustration was used for Fig. 2. The correct illustration appears above. Fig. 2. Complete schematic reveals method used in converting VHF to UHF.

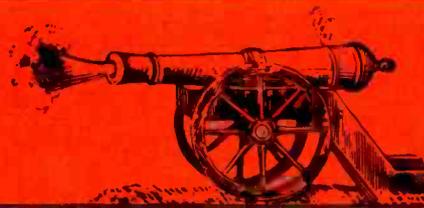For window-size blow-ups
of this message, send 10¢ to
Sprague Products Co.,
105 Marshall St., North Adams,
Mass., to cover handling
and mailing costs.



EVERY DAY IS ★ ★
INDEPENDENCE
DAY 
FOR YOU AND YOUR
★ **INDEPENDENT** ★ ★
TV SERVICE DEALER

Your independent TV Service Dealer is in business for himself because he too wants to exercise his independence just as you do. You purchased your TV or radio set where you wanted to . . . when you wanted to . . . and at the price you decided was right.

Your TV service dealer is also an independent in the things he buys in his day-to-day work. He buys repair parts where he can get the highest quality and the best service. And, he trained himself in his own way, on his own time, at his own expense, to be able to do the very best for YOU.

He stands or falls on what you think of him and his work. He has to do good work to keep your business . . . and he knows it!

We're lucky in these United States that every day is Independence Day. Independent buying, selling, and servicing is the very lifeblood of American business. Let's keep it that way.

**THIS MESSAGE WAS PREPARED BY SPRAGUE PRODUCTS COMPANY,
DISTRIBUTORS' SUPPLY SUBSIDIARY OF SPRAGUE ELECTRIC COMPANY, NORTH ADAMS, MASSACHUSETTS FOR . . .**

YOUR INDEPENDENT TV-RADIO SERVICE DEALER

9⁵⁰

ALL PARTS

(except tubes)

Plus Shipping Charge

QUALITY TV TUNER SERVICE

24 hrs. Service

Most Makes

UHF - VHF - COLOR - (COMBOS. - 14.50)

15 YEARS OF TUNER EXPERIENCE

- 1 Year Warranty
- Tuners completely cleaned and checked
- Open Account on approved credit
- Dist. write for price structure



Pack Tuner Carefully — Insure Package — Include all parts (Broken or not)

QUALITY TUNER SERV.

5142 W. 25th St. CHICAGO, ILL. 60650

Circle 15 on literature card

The difference in screwdrivers is spelled

CHANNEL LOCK



You'll do the job easier and faster, year after year with CHANNELLOCK drivers. Blades are forged from tough, chrome vanadium steel . . . won't twist or snap. Tips are ground lengthwise to assure greater "end" strength and snug fit in screw slot. Opaque blue plastic (UL) handles are shockproof, breakproof and locked to the blade. Specify CHANNELLOCK drivers . . . you'll be glad you did.

Tips are ground lengthwise for greater end strength.

SHOCKPROOF... BREAKPROOF

FREE Catalog showing complete line of hand tools . . . yours for the asking.

CHANNELLOCK, INC. Meadville, Pennsylvania
Formerly Champion DrArment Tool Co.

Circle 16 on literature card

BOOK REVIEW

Radioman's Guide (AUD-3A); Edwin P. Anderson. revision by David E. Hicks; Theodore Audel Co., Division of Howard W. Sams & Co., Inc., Indianapolis, Indiana, 1964; 448 pages, 6½" x 4½", hardbound; \$5.00.

This text is a complete revision, including new illustrations, of the previous edition which included television theory. The new edition covers component and radio theory only. Included in the coverage are: wave propagation, characteristics of sound, magnetism, structure of matter, electricity, resistance, inductance, capacitance, transformers, vacuum tubes, semiconductors (including transistors), speakers and microphones, electronic circuits (power supplies, amplifiers, oscillators), transmitters, receivers, antennas, and electrical measuring instruments. One complete chapter is devoted to the testing of radios, including repair and alignment. A separate final chapter contains trouble pointers in the form of questions and answers.

Throughout the text, the use of math has been kept to a minimum, but for interested readers appendices are included which contain tables, nomographs, and formulas. ▲

NEW!



ARROW'S T-18 Low Voltage Wire STAPLE GUN

For Fastening Any Inside or Outside Wire Up to 3/16" in Diameter

Takes a 3/8" leg staple with 3/16" crown.

- Telephone wire
 - Intercom wire
 - Bell wire
 - Thermostat wire
 - Radiant heating wire
 - Hi-Fi, Radio & TV wires
- Tapered striking edge gets into close corners!

Steel wire staples available in brown, ivory, beige or natural; bronze and monel staples also available.

ARROW
ARROW FASTENER CO., INC.
ONE JUNIUS STREET • BROOKLYN 12, N. Y.

Circle 63 on literature card



stereo FM station guide

The information in this directory was taken from the Howard W. Sam publication North American Radio-TV Station Guide, 3rd Edition (RSG-3), by Vane A. Jones.

Alabama

Birmingham	
WCRT-FM	96.5
WSFM	93.7
Dothan	
WOOF-FM	99.7
Huntsville	
WAHR	99.1
WNDA	95.1
Mobile	
WLPR-FM	96.1
Montgomery	
WAJM	103.3
WFMI-FM	98.9
Muscle Shoals	
WLAY-FM	105.5

Alaska

Anchorage	
KBYR-FM	102.1
KNIK-FM	105.5

Arizona

Phoenix	
KNEO	96.9
KNIX	102.5
KOOL-FM	94.5
KRFM	95.5
Sun City	
KTPM	106.3
Tucson	
KSOM	92.9

Arkansas

El Dorado	
KELD-FM	103.1
KRIL	99.3
Fort Smith	
KMAG	99.1

Jonesboro	
KBTM-FM	101.9
Little Rock	
KARK-FM	103.7

California

Alameda	
KJAZ	92.7
Bakersfield	
KGEE-FM	101.5
KIFM	96.5
Fresno	
KCIB	94.5
KXQR	102.7
Garden Grove	
KGGK	94.3
Lodi	
KCVR-FM	97.7
Long Beach	
KNOB	97.9
Los Angeles	
KCBH	98.7
KFAC-FM	92.3
KFMU	97.1
KFOX-FM	100.3
KPOL-FM	93.9
KRHM	102.7
Los Banos	
KARL-FM	95.9
Monterey	
KHFR	96.9
Riverside	
KDUO	97.5
Sacramento	
KFBK-FM	92.5
KHIQ	105.1
KSFM	96.9
San Diego	
KBBW	102.9
KFMX	96.5

KGB-FM	101.5
KLRO	94.9
KPRI	106.5
San Fernando	
KVFM	94.3
San Francisco	
KBRG	105.3
KFOG-FM	104.5
KMPX	106.9
KPEN	101.3
KSFR	94.9
San Jose	
KEEN-FM	100.3
KSJO-FM	92.3
San Luis Obispo	
KSBT-FM	93.3
Santa Barbara	
KGUD-FM	99.9
KMUZ	103.3
Santa Maria	
KXFM	99.1
Stockton	
KUOP	91.3
Turlock	
KHOM	93.1
Ventura	
KUDU-FM	95.1
Visalia	
KONG-FM	92.9
Walnut Creek	
KDFM	92.1
Woodland	
KATT	102.5

Colorado

Colorado Springs	
KLST	94.3
Denver	
KFML-FM	98.5
KLIR-FM	100.3
KTGM	105.1

Manitou Springs	
KCMS-FM	102.7

Connecticut

Brookfield	
WGHF	95.1
Hartford	
WTIC-FM	96.5
Meriden	
WBMI	95.7
New Haven	
WNHC-FM	99.1

Delaware

Wilmington	
WDEL-FM	93.7
WJBR	99.5

District of Columbia

Washington	
WASH	97.1
WGMS-FM	103.5
WMAL-FM	107.3

Florida

Belle Glade	
WSWN-FM	93.5
Bradenton	
WBRD-FM	103.3
Clearwater	
WTAN-FM	95.7
Cocoa	
WEZY-FM	99.3
Cocoa Beach	
WRKT-FM	104.1
WXBR	101.1
Coral Gables	
WVCG-FM	105.1
Ft. Lauderdale	
WFLM	105.9
WMJR-FM	100.7



B&K MODEL 970 RADIO ANALYST

SERVICE AM & FM AUTO AND TRANSISTOR RADIOS AT A PROFIT!

NEW!

Jobs that used to be unprofitable now go so quickly that you can make good money handling them! There are millions of auto radios and transistor radios in the field—portables, auto and table models, plus hi-fi and communications equipment. Instead of turning them away, you can turn them into money-makers with the B&K Model 970 Radio Analyst.

The 970 is effective because it's *accurate* and *complete*. Using the famous B&K signal injection technique, this all-in-one instrument provides the required dc power, lets you test power and signal transistors in and out of circuit; generates RF and audio signals, and includes a rugged, accurate VOM. Four functions in one compact package—with solid state reliability, B&K professional quality.

LOW INVESTMENT—QUICK RETURN

See your B&K Distributor or write for Catalog AP22-R

Net \$199⁹⁵



B & K MANUFACTURING CO.
DIVISION OF DYNASCAN CORPORATION
1801 W. BELLE PLAINE AVE. • CHICAGO, ILL. 60613

Export: Empire Exporters, 123 Grand St., New York 13, U.S.A.

FEATURES:

BUILT-IN POWER SUPPLY

Auto Radios—High current, low-ripple, for transistor, hybrid, and vibrator types.

Transistor Portables—1½ to 12 volts for battery substitution—plus separately variable voltage tap for bias.

QUICK AND ACCURATE TESTING OF POWER AND SIGNAL TRANSISTORS

In-Circuit—stage by stage DC signal injection and sensitive metering of power supply current.

Out-of-Circuit—Direct Beta and Leakage meter scale readings. Easy balancing or matching.

VERSATILE SIGNAL GENERATORS

RF Generators—provide broadcast and IF frequencies for both AM and FM bands.

Audio Generator—for AM or FM modulation of the RF signals, and for trouble-shooting audio circuits.

RUGGED VOM

Volt-OHM-Milliammeter—with rugged, taut band meter—provides correct ranges for easy, fast servicing of all home and auto radios, as well as transistor portables.

Ft. Myers
WINK-FM 96.9
Ft. Walton Beach
WFTW-FM 99.3
Gainesville
WRUF-FM 103.7
Jacksonville
WIVY-FM 102.9
WJAX-FM 95.1
WKTZ-FM 96.1
WQIK-FM 99.1
Marianna
WTOT-FM 100.9
Miami
WIOD-FM 97.3
WWPB 101.5
Miami Beach
WAEZ 94.9
Milton
WXBM-FM 102.3
Orlando
WHOO-FM 96.5
Palm Beach
WWOS 97.9
Panama City
WMAI-FM 107.9
Pensacola
WPEX-FM 94.1
St. Petersburg
WTCX 99.5
Sarasota
WYAK 102.5
Stuart
WMCF 92.7
Tallahassee
WBGW 98.9
WFSU-FM 91.5
Tampa
WFLA-FM 93.3
West Palm Beach
WPBF 107.9
Winter Haven
WINT-FM 97.5

Georgia

Albany
WGPC-FM 104.5
Americus
WDEC-FM 94.3
Athens
WGAU-FM 95.5
Atlanta
WKLS 96.1
WLTA-FM 99.7
WSB-FM 98.5
Carrollton
WLBB-FM 92.1
Columbus
WRBL-FM 102.9
Gainesville
WDUN-FM 106.7
La Grange
WLAG-FM 104.1
Moultrie
WMTM-FM 93.9
Rome
WROM-FM 97.7
Savannah
WTOC-FM 94.1

Hawaii

Honolulu
KAIM-FM 95.5

KPOI-FM 97.5

Illinois

Bloomington
WJBC-FM 101.5
Chicago
WEFM 99.5
WFMT 98.7
WKFM 103.5
WLS-FM 94.7
WMAQ-FM 101.1
WNUS-FM 107.5
WXRT 93.1
Crete
WTAS 102.3
Decatur
WSOY-FM 102.9
Elmwood Park
WXFM 105.9
Joliet
WJOL-FM 96.7
Loves Park
WLUV-FM 96.7
Mattoon
WLBH-FM 96.9
Quincy
WGEM-FM 105.1
Rock Island
WHBF-FM 98.9
Springfield
WFMB 104.5

Indiana

Columbus
WCSI-FM 101.5
Evansville
WIKY-FM 104.1
Ft. Wayne
WKJG-FM 97.3
WPTH 95.1
Greenfield
WSMJ 99.5
Hartford City
WWHC 104.9
Indianapolis
WFMS 95.5
WIFE-FM 107.9
Kendallville
WAWK-FM 93.3
Lafayette
WASK-FM 105.3
Peru
WARU-FM 98.3
Plainfield
WJMK 98.3
Richmond
WKBV-FM 101.3
South Bend
WNDU-FM 92.9
Terre Haute
WVTS 100.7
Vincennes
WAOV-FM 96.7

Iowa

Ames
WOI-FM 90.1
Des Moines
KWDM 93.7
KDMI 97.3
Sioux City
KDVR 97.9
Waterloo
KXEL-FM 105.7

Kansas

Lawrence
KANU 91.5
KLWN-FM 105.9
Leavenworth
KCLO-FM 98.9
Newton
KJRG-FM 92.3
Wichita
KCMB-FM 107.3
KQTY 101.3

Kentucky

Lexington
WVLK-FM 92.9
Owensboro
WSTO 96.1

Louisiana

Baton Rouge
WJBO-FM 102.5
De Ridder
KDLA-FM 101.7
Hammond
WGTI 107.1
Monroe
KMLB-FM 104.1
New Orleans
WDSU-FM 93.3
Shreveport
KBCL-FM 96.5

Maine

Brunswick
WCME-FM 98.9
Caribou
WFST-FM 97.7
Poland Spring
WMTW-FM 94.9

Maryland

Baltimore
WITH-FM 104.3
Bethesda
WHFS 102.3
WJMD 94.7
Halfway
WHAG-FM 96.7
Towson
WAQE-FM 101.9

Massachusetts

Boston
WBCN 104.1
WHDH-FM 94.5
Lynn
WLYN-FM 101.7
North Adams
WMNB-FM 100.1
Waltham
WCRB-FM 102.5
Worcester
WSRS 96.1

Michigan

Ann Arbor
WOIA-FM 102.9
Bay City
WBCM-FM 96.1
WNEM-FM 102.5
Detroit
WABX 99.5
WBFM 98.7
WDTM 106.7
WGPR 107.5
WJBK-FM 93.1
WLDM 95.5

WOMC 104.3
East Lansing
WSWM 99.1
WVIC-FM 94.9
Flint
WGMZ 107.9
Grand Rapids
WJFM 93.7
WOOD-FM 105.7
Holland
WHTC-FM 96.1
Interlochen
WIAA 88.3
Kalamazoo
WKMI-FM 106.5
WMUK 102.1
Midland
WQDC 99.7
Mt. Pleasant
WCEN-FM 94.5
Saginaw
WSAM-FM 98.1

Minnesota

Minneapolis
KWFM 97.1
WAYL 93.7
WPBC-FM 101.3
St. Louis Park
KRIS-FM 104.1

Mississippi

Greenwood
WSWG 99.1
Gulfport
WROA-FM 107.1
Hattiesburg
WFOR-FM 103.7
Jackson
WWHO 94.7
Pascagoula
WPMP-FM 99.1

Missouri

Crestwood
KSHE 94.7
Joplin
KSYN 92.5
Kansas City
KCMO-FM 94.9
KMBC-FM 99.7
St. Louis
KCFM 93.7
Sedalia
KSIK-FM 92.1
Springfield
KTXR 101.5

Montana

Great Falls
KOPR-FM 106.3

Nebraska

Omaha
KOWH-FM 94.1

Nevada

Las Vegas
KORK-FM 97.1
Reno
KNEV 95.5

New Hampshire

Mt. Washington
WMTW-FM 94.9

New Jersey

Atlantic City
WFPG-FM 96.9



new
8290
Shielded Permohm*
 Shown Actual Size




82 Channel TV lead-in

for the strongest, cleanest picture signal and best color... ever!

- Provides 82 channel color reception
- Less installation time and cost
- Eliminates transmission line pick-up of noise and ghost signals
- No expensive matching transformers required
- Can be installed anywhere

Photos courtesy of WGN-TV.

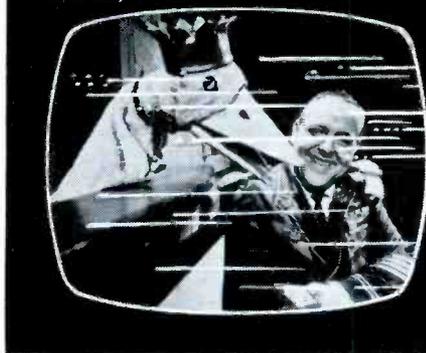

Unshielded twin-lead
 Severe picture disturbance
 due to ignition noise.



Coaxial Cable
 Ignition noise minimized—
 but not eliminated.



* Shielded Permohm
 Eliminates automobile
 ignition noise.

■ New 8290 Shielded Permohm TV Lead-in combines the strong signal strength of twin-lead with the clean signal protection of shielded cable. Because it is a balanced line for 300 Ohm TV antennas and receivers, *costly matching transformers and connectors are eliminated.*

8290 is specifically designed for superior color reception on all 82 channels. The twin-lead is encapsulated in low-loss cellular polyethylene insulation, Beldfoil** shielded against all outside disturbances, and protected with a weatherproof

*Belden Trademark—Reg. U.S. Pat. Off.

jacket. A drain wire is provided for grounding the shield. The need for stand-offs, twisting or routing of lead-in is eliminated. 8290 can be taped directly to a mast or tower, routed through metal pipe, buried underground, or even installed in rain filled gutters to reduce installation time and cost.

Ask your distributor about 8290 Shielded Permohm TV Lead-in cable, today! Or, write P. O. Box 5070-A for complete information.

**Belden U.S. Patent 2,782,251 and Patent Pending

B-9-5

BELDEN MANUFACTURING COMPANY

Belden

P.O. Box 5070-A • Chicago, Illinois 60680

Circle 19 on literature card

May, 1966/PF REPORTER 47

Dover	
WDHA-FM	105.5
Long Branch	
WRLB	107.1
Paterson	
WPAT-FM	93.1
Princeton	
WPRB	103.3
Trenton	
WBUD-FM	101.5

New Mexico

Albuquerque	
KHFM	96.3
Los Alamos	
KRSN-FM	98.5

Roswell	
KBIM-FM	94.9
University Park	
KRWG	91.7

New York

Babylon	
WGSM-FM	94.3
Binghamton	
WNBF-FM	98.1
Buffalo	
WADV	106.5
WDCX	99.5
De Pew	
WBLK-FM	93.7
Garden City	
WLIR	92.7

Jamestown	
WKSJ-FM	101.7
Lake Success	
WTFM	103.5
New York	
WKCR-FM	89.9
WNBC-FM	97.1
WQXR-FM	96.3
WRFM	105.1

North Carolina

Patchogue	
WPAC-FM	106.1
Riverhead	
WAPC-FM	103.9
Rochester	
WCMF	96.5
Schenectady	
WGFM	99.5
Syracuse	
WONO	107.9
WSYR-FM	94.5
Utica	
WUFM	107.3

North Dakota

Burlington	
WBBB-FM	101.1
Charlotte	
WBT-FM	107.9
WSOC-FM	103.7
Greensboro	
WMDE	98.7
WQMG	97.1
Greenville	
WNCT-FM	107.7
Hickory	
WHKY-FM	102.9
WIRC-FM	95.7
Leaksville	
WLOE-FM	94.5
Williamston	
WIAM-FM	103.7
Fargo	
WDAY-FM	93.7

Ohio

Cambridge	
WILE-FM	96.7
Canton	
WCNO	106.9
Cincinnati	
WAEF-FM	98.5
WKRC-FM	101.9
Cleveland	
WCLV	95.5
WDOK-FM	102.1
WNOB	107.9
WZAK	93.1
Columbus	
WBNS-FM	97.1
Fairfield	
WCNW-FM	94.9
Findlay	
WFIN-FM	100.5
Kettering	
WVUD-FM	99.9
Mansfield	
WVNO-FM	106.1
Medina	
WDBN	94.9
Middletown	
WPFB-FM	105.9
Pt. Clinton	
WRWR-FM	94.5

NEW B & K MODEL 606 DYNA-JET

TESTS LATEST TUBES QUICKLY AND ACCURATELY

PORTABLE/LOW COST/PROFESSIONAL

This new B&K Tube Tester provides the sockets and the features you need to test the latest color and compactron receiving tubes, as well as older types.

You can test for all shorts, grid emission, leakage and gas; and check cathode emission the accurate way—under simulated load conditions! Each section of a multiple section tube is checked. With the Model 606, you won't reject the good tubes, and you'll quickly find the bad ones, reducing call backs, selling more tubes, and increasing service profit.

You'll find "tough dogs" and weak tubes with the exclusive adjustable grid emission test, which has a sensitivity of over 100 megohms. Tube sockets have phosphor bronze contacts for long, trouble-free life. Complete tube listings are provided in a handy reference index.

This efficient instrument, in a small, handsome, leatherette covered carry case, will perform professionally on house calls or the service bench. Its low price will soon be paid for with increased profit. *Net \$79.95*



For additional information write for Catalog AP-22.



B & K MANUFACTURING CO.
 DIVISION OF **DYNASCAN CORPORATION**
 1801 W. BELLE PLAINE AVE. - CHICAGO, ILL. 60613
 Export: Empire Exporters, 123 Grand St., New York 13, U.S.A.

Circle 20 on literature card

A COMPLETE FAMILY OF QUALITY UHF-VHF-FM ANTENNAS


KAY-TOWNES

OVER 900 MODELS FOR EVERY AREA — EVERY PURPOSE

colorphase

WITH PIGGY BACK POWER PACK

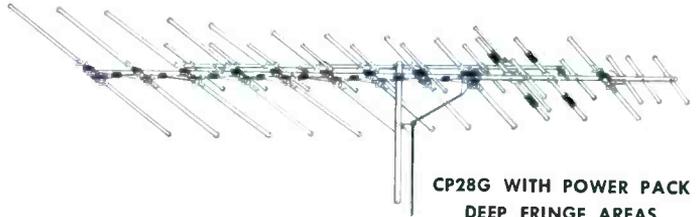Gives the EXTRA PUNCH needed to produce the best in color and improved black and white. High Gain, high front to back ratio. Double U-bolts and double cross-arms for rugged rigidity. 2-piece locking mast clamp. No boom braces needed.



VHF-FM

CP28G WITH POWER PACK
DEEP FRINGE AREAS
LIST \$53.75



CP23G WITH POWER PACK
FRINGE AREAS
LIST \$44.80



CP19G WITH POWER PACK
NEAR FRINGE-FRINGE
LIST \$35.05



CP15G WITH POWER PACK
SUBURBAN-NEAR FRINGE
LIST \$26.10



CP11G
SUBURBAN
LIST \$20.19




CP7G
CITY AREAS
LIST \$13.02


COLORDYNE

COMBINATION UHF-VHF-FM

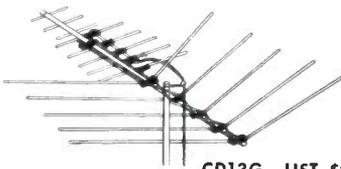An antenna for all channels 2 through 83. Simplicity of design permits high gain reception at low cost.



CD13G LIST \$21.92
SUBURBAN-NEAR FRINGE

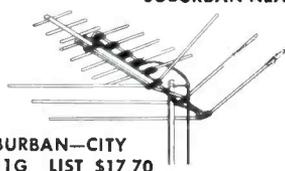

SUBURBAN-CITY
CD11G LIST \$17.70

All models include Free Band Splitter

Colorphase Combination

ALL-BAND UHF-VHF-FM
WITH PIGGY BACK POWER PACK


One antenna to cover all channels 2 through 83 with single down lead for all areas including FRINGE AREA.



FRINGE
CPC27G WITH POWER PACK LIST \$40.75



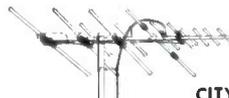SUBURBAN
NEAR FRINGE
CPC24G WITH POWER PACK LIST \$35.41




CITY AREAS
CPC12G LIST \$17.42

All models include Free Band Splitter


ALP MODELS

VHF-FM

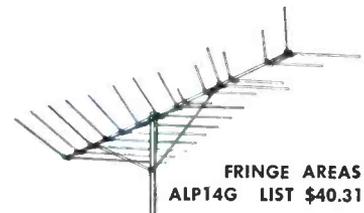
All channels 2 through 13. Simple swept-element permits low cost with high gain and excellent color as well as black and white and FM Stereo.



FRINGE AREAS
ALP14G LIST \$40.31

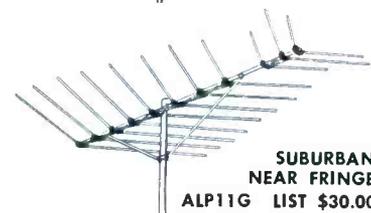

SUBURBAN-NEAR FRINGE
ALP11G LIST \$30.00

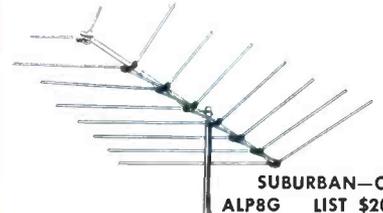

SUBURBAN-CITY
ALP8G LIST \$20.85

COLORVISTA UHF

Converts any existing VHF antenna to 82 channel reception with a single lead. Receives UHF in one direction and VHF in another with no rotor or coupler necessary.



CVU-13G LIST \$14.15



GENUINE
GOLD ANODIZED

Not a Spray to Wash Away!

SEE US AT THE SAN FRANCISCO SHOW — BOOTH 2606

SALES TERRITORIES OPEN IN SOME AREAS

QUALITY • PERFORMANCE • ECONOMY



KAY-TOWNES
antenna company

HEADQUARTERS OFFICE AND PLANT — 1511 DEAN AVE., ROME, GA., 30162

Circle 21 on literature card

FREE!



\$9.95



HIGHWAY EMERGENCY KIT

with the

AEROVOX AK600H CAPACITOR KIT

It's the biggest deal in town, and it's as legitimate as the United States Mint!

Your Authorized Aerovox Distributor will present you with an Electro-Lite Highway Emergency Kit FREE OF CHARGE with the purchase of the AK600H Capacitor kit.

Now get this!

...The capacitors alone list for more than forty dollars.

...The Highway Emergency Kit is a national best seller at \$9.95.

YOU GET BOTH FOR ONLY \$22.95... Save over twenty-seven dollars on a single purchase!

Look at the capacitors listed and you will see that there are no "dogs." You get 25 bypass tubulars, 8 tubular electrolytics, and 6 twist-prong electrolytics... including 7 red-hot color certified units!

Don't delay. Your distributor has these kits in stock *right now!* Get one for your truck, one for your car... and if your wife drives her own, one for her too. This is an item she'll really appreciate.

Order now while supply lasts.



Highway Emergency Kit contains:

- Tire Inflator
- Two-way flashlight
- Nite Glo S.O.S. Flag
- First Aid Kit
- Fire Extinguisher
- Magnetic Police-type red flasher

AK600H Capacitor Kit contains:

- | | |
|----------------|------------------|
| 5-DBE 6D1 | *1-AFH 2-57 |
| 5-DBE 6D5 | 1-PR 1-075 |
| 5-DBE 6S1 | *1-PRS 1360 |
| 5-DBE 6S5 | *1-PRS 1470 |
| 5-DBE 6P1 | *1-PRS 1735 |
| 1-AFH 1-22-05 | *1-PRS 1750 |
| 1-AFH 1-24 | *1-PRS 1780 |
| 1-AFH 1-24-75 | 1-PRS 2200 |
| 1-AFH 1-25-65 | 1-PRS 2240 |
| *1-AFH 1-37-25 | *Color Certified |



AEROVOX CORPORATION
DISTRIBUTOR DIVISION
NEW BEDFORD, MASS.

Technical Leadership - Manufacturing Excellence

Circle 22 on literature card


Portsmouth	WPAY-FM	104.1
Springfield	WBLY-FM	102.9
Toledo	WCWA-FM	104.7
Urbana	WCOM-FM	101.7
Youngstown	WBBW-FM	93.3
Oklahoma		
Lawton	KLAW	101.5
Midwest City	KTEA-FM	92.5
Oklahoma City	KFNB	101.9
Stillwater	KOSU-FM	91.7
Tulsa	KOCW	97.5
	KRAV	96.5
Oregon		
Eugene	KFMY	97.9
	KWFS-FM	96.1
Portland	KPFM	97.1
	KXL-FM	95.5
Pennsylvania		
Allentown	WFMZ	100.7
Altoona	WFBG-FM	98.1
Boyertown	WBYO-FM	107.5
Braddock	WLOA-FM	96.9
Chambersburg	WCHA-FM	95.1
Hanover	WYCR	98.5
Harrisburg	WTPA-FM	104.1
Johnstown	WJAC-FM	95.5
Oil City	WDJR	98.5
Philadelphia	WDVR	101.1
	WFIL-FM	102.1
	WFNL-FM	95.7
	WHAT-FM	96.5
	WIFI	92.5
	WIP-FM	93.3
	WQAL	106.1
Pittsburgh	WKJF	93.7
Red Lion	WGCB-FM	96.1
Scranton	WDDL-FM	104.9
Tyrone	WGMR-FM	101.1
Warren	WRRN	92.3
Wilkes-Barre	WYZZ	92.9
Puerto Rico		
Aguadilla	WABA-FM	100.3
Rio Piedras		

FINCO

COLOR-VE-LOG ANTENNAS

FOR UHF, VHF, FM RECEPTION

ALL-BAND UHF-VHF-FM ANTENNA

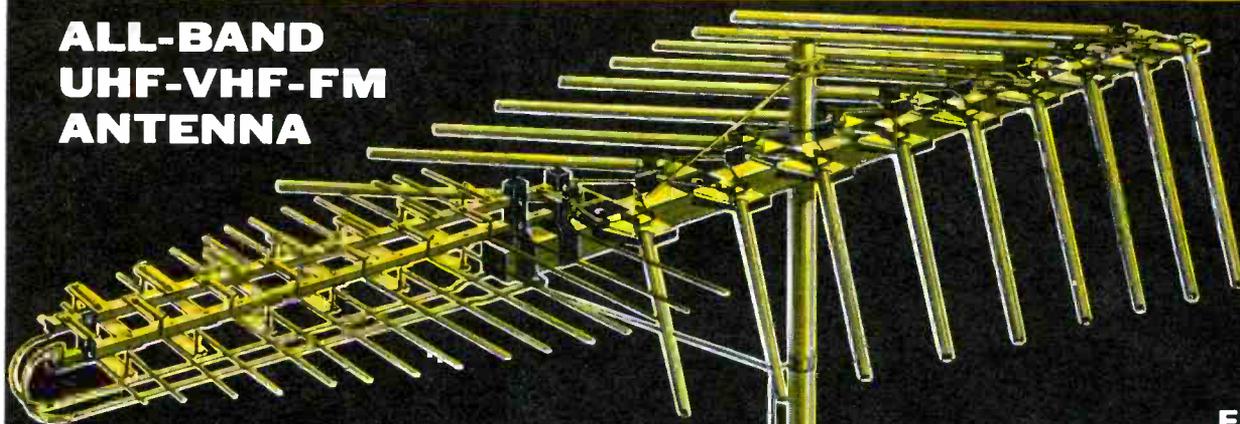


FINCO
Model UVF-24
\$59.95 list

The one antenna that does the work of 3! Gives startlingly clear black and white pictures and beautiful color on both UHF and VHF television channels — plus the finest in stereophonic and monophonic sound reproduction.

FINCO Model UVF-18 — \$42.50 list
FINCO Model UVF-16 — \$30.50 list
FINCO Model UVF-10 — \$18.50 list

SWEPT-ELEMENT VHF-FM ANTENNA

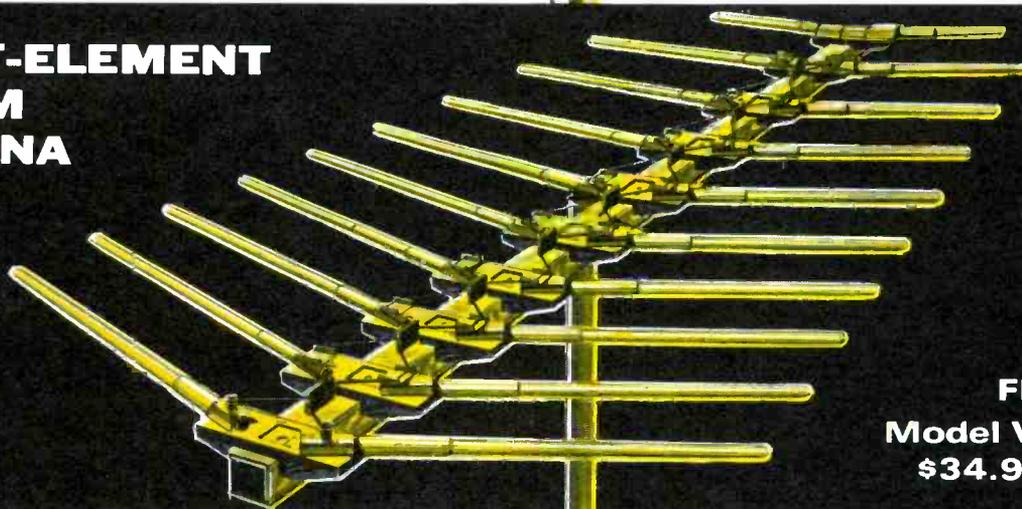

FINCO
Model VL-10
\$34.95 list

FINCO's Color-Ve-Log challenges all competition! Its swept-element design assures the finest in brilliant color and sharply defined black and white television reception — as well as superb FM monaural and stereo quality.

FINCO Model VL-18 — \$54.50 list
FINCO Model VL-15 — \$46.95 list
FINCO Model VL-7 — \$23.95 list
FINCO Model VL-5 — \$16.95 list

Featuring FINCO's exclusive Gold Corodizing

FINCO COLOR-VE-LOG

Prices and specifications subject to change without notice

THE FINNEY COMPANY • 34 W. Interstate Street • Bedford, Ohio

Write for beautiful color brochures Number 20-322, and 20-307, Dept. 310

Circle 23 on literature card

May, 1966/PF REPORTER 51



Look what's happened to the RCA WR-51A FM Stereo Signal Simulator

...it got to be the WR-52A...

NEW, REDESIGNED AND IMPROVED

Last year we decided to make a few improvements in our WR-51A Stereo FM Signal Simulator... for two years THE established test instrument for multiplex stereo servicing. We intended to call it the WR-51B. But one thing led to another and we made so many extensive improvements that we virtually had a new instrument on our hands. You're looking at it: the NEW RCA WR-52A STEREO FM SIGNAL SIMULATOR. We've added an RF Deviation Meter to measure the modulation level of both stereo and monaural FM signals. The meter is also used to accurately establish the level of the 19 Kc subcarrier.

We've included provisions for modulating left or right stereo signals with an external monaural source.

We've added a switch to disable the 19 Kc oscillator to provide a low-distortion monaural FM output.

We've added a new frequency (72 Kc)... required, along with the 67 Kc frequency, for trap alignment in some sets.

These features, together with numerous internal circuit design changes have resulted in a vastly improved, almost completely new instrument. And, the RCA WR-52A includes all those features that made its predecessor such a valuable servicing tool.

■ **COMPOSITE STEREO OUTPUT**—for direct connection to multiplex circuit

Choice of left stereo and right stereo signals

■ **RF OUTPUT**—for connection to receiver antenna terminals

100 Mc carrier, tuneable
Choice of FM signals—left stereo, right stereo, monaural FM, internal test and 60 cycle FM sweep
FM stereo deviation adjustable from 0-100%
100 Mc sweep signal adjustable from 0 to more than 750 Kc at a 60 cps rate

■ **CRYSTAL-CONTROLLED 19 Kc SUBCARRIER** ($\pm 0.01\%$)

■ **SINE WAVE FREQUENCIES**

Three low-distortion frequencies—400 cps, 1 Kc, 5 Kc
Two crystal-controlled frequencies—19 and 38 Kc
Additional frequencies—67 and 72 Kc for trap alignment

■ **READILY PORTABLE**—weighs only 12¾ pounds, measures 13½" by 10" by 8"

■ **COMPLETE WITH WIRED-IN CONNECTING CABLES**

We also raised the price... just 50 cents. The WR-52A is now \$250.00.* Ask to see it at your Authorized RCA Test Equipment Distributor.

*Optional distributor resale price, subject to change without notice. May be slightly higher in Hawaii and the West.

RCA ELECTRONIC COMPONENTS & DEVICES, HARRISON, N.J.

WFID 95.7

Rhode Island

Providence
WBRU 95.5
WCRQ 101.5

South Carolina

Beaufort
WBUE-FM 98.7
Greenville
WMUU-FM 94.5
North Charleston
WKTM 102.5
Spartanburg
WSPA-FM 98.9

South Dakota

Sioux Falls
KELO-FM 92.5

Tennessee

Chattanooga
WDOD-FM 96.5
Kingsport
WKPT-FM 98.5
McKenzie
WKTA 106.9
Morristown
WMTN-FM 95.9
Nashville
WLAC-FM 105.9
WNFO-FM 103.3
WSIX-FM 97.9
Sevierville
WSEV-FM 102.1
Tulahoma
WJIG-FM 93.3

Texas

Abilene
KWKC-FM 105.1
Amarillo
KVII-FM 94.1
Austin
KTBC-FM 93.7
Beaumont
KHGM 95.1
Clear Lake City
KMSC 102.1
Dallas
KIXL-FM 104.5
KVIL-FM 103.7
WRR-FM 101.1
El Paso
KTSM-FM 99.9
Fort Worth
KCUL-FM 93.9
WBAP-FM 96.3
Gainesville
KGAF-FM 94.5
Houston
KBNO 93.7
KFMK 97.9
KLEF 94.5
KODA-FM 99.1
KRBE 104.1
KXYZ-FM 96.5
Lubbock
KBFM 96.3
Port Arthur
KFMP 93.3
San Angelo
KWLW 93.9
San Antonio
KEEZ 97.3



The Most Trusted Name in Electronics

KITY 92.9	KLAY-FM 106.1	Wyoming	CHML-FM 95.3
Sinton		Cheyenne	London
KTOD-FM 101.3	West Virginia	KVWO-FM 106.3	CFPL-FM 95.9
Wichita Falls	Bluefield		Ottawa
KNTD 95.1	WHIS-FM 104.5	Canada	CFMO-FM 93.9
Utah	Charleston	Alberta	Sault Ste. Marie
Ogden	WKNA 98.5	Calgary	CJIC-FM 100.5
KBOC 101.9	WVAF 99.9	CHFM-FM 95.9	CKCY-FM 104.3
Salt Lake City	Martinsburg	Edmonton	Toronto
KSL-FM 100.3	WEPM-FM 97.5	CFRN-FM 100.3	CHFI-FM 98.1
KSOP-FM 104.3	Wisconsin	Red Deer	CHUM-FM 104.5
Virginia	Delafield	CKRD-FM 98.9	CJRT-FM 91.1
Harrisonburg	WHAD 90.7	British Columbia	CKFM-FM 99.9
WVSA-FM 100.7	Eau Claire	Kamloops	Windsor
Martinsville	WIAL 94.1	CFFM-FM 98.3	CKLW-FM 93.9
WMVA-FM 96.3	Green Bay	Penticton	Quebec
Norfolk	WBAY-FM 101.1	CKOK-FM 97.1	Montreal
WTAR-FM 95.7	Kenosha	Vancouver	CFCF-FM 92.5
WYFI-FM 99.7	WAXO 96.9	CHQM-FM 103.5	CJFM-FM 95.9
Richmond	WLIP-FM 95.1	CKLG-FM 99.3	CJMS-FM 94.3
WFMV 103.7	Madison	Victoria	CKGM-FM 97.7
Roanoke	WHA-FM 88.7	CFMS-FM 98.5	Quebec
WLSL-FM 99.1	WISM-FM 98.1	Manitoba	CHRC-FM 98.1
Washington	WMFM 104.1	Winnipeg	Rimouski
Aberdeen	WRVB-FM 102.5	CBW-FM 98.3	CJBR-FM 101.5
KDUX-FM 104.7	Milwaukee	CJOB-FM 97.5	Sherbrooke
Seattle	WFMR 96.5	CKY-FM 92.1	CHLT-FM 102.7
KBBX 98.9	WMKE 102.1	New Brunswick	Verdun
KETO-FM 101.5	WTMJ-FM 94.5	St. John	CKVL-FM 96.9
KISW 99.9	Tomah	CFBC-FM 98.9	Saskatchewan
KIXI-FM 95.7	WTMB-FM 98.9	Ontario	Saskatoon
KLSN 96.5	Wausau	Cobourg	CFMC-FM 103.9
KZAM 92.5	WSAU-FM 95.5	CHUC-FM 103.1	
Tacoma	West Bend	Hamilton	
	WBKV-FM 92.5		

FAMOUS ZENITH QUALITY TUBES for greater reliability, longer life



TV Picture Tubes

A complete line of more than 200 top-quality tubes. For color, black-and-white, or special purposes.

Zenith black & white replacement picture tubes are made only from new parts and materials except for the glass envelope in some tubes which, prior to reuse, is inspected and tested to the same high standards as a new envelope. In Color tubes the screen, aperture mask assembly and envelope are inspected and tested to meet Zenith's high quality standards prior to reuse. All electron guns are new.

"Royal Crest" Circuit Tubes

A full line of more than 875 tubes ... the same quality tubes as original Zenith equipment. Your assurance of the world's finest performance.

Order all genuine Zenith replacement parts and accessories from your Zenith distributor.



BUILT TO THE QUALITY STANDARDS OF ZENITH ORIGINAL PARTS

ZENITH

The quality goes in before the name goes on®

Circle 25 on literature card

NOW! ADD TO OR COMPLETE YOUR **PHOTOFACT® LIBRARY** AT PRESENT LOW PRICES!

UNTIL JULY 1, 1966—
SAVE
\$123⁷⁵
 on your purchase
 of a 225-Set
PHOTOFACT LIBRARY
ORDER NOW!



Until July 1, 1966, you can buy a PHOTOFACT LIBRARY (minimum of 60 Sets) at the present low Easy-Buy contract price of \$1.95 per Set—you save 55¢ per Set—
you save over \$120.00 on a 225-Set Library purchase!

(After July 1, 1966, PHOTOFACT prices go up: Single Sets 1 through 200 go to \$3.00 each; Single Sets 201 through current issues go to \$2.50 each)

ACT NOW! THERE'S NEVER BEEN A DEAL LIKE THIS:

NO INTEREST, NO CARRYING CHARGE

LIBRARY EASY-BUY PLAN

- Yes—no interest—no carrying charge—no other deal like it!
- Only \$10 down—30 months to pay while the Library earns for you!
- Prepaid transportation to your shop.
- Add-on privilege of a year's advance subscription to current PHOTOFACT Sets on same contract.

4 WAYS TO SELECT YOUR LIBRARY

1. Complete your present PHOTOFACT Library.
2. Order a "Starter" Library of 225 Sets. (Sets 451-675—coverage from 1959 to 1964—only \$14.29 per month).
3. Order by brand name and year—see the handy selection chart at your Sams distributor.
4. Order a *complete* PHOTOFACT Library.

FREE

the famous
14-volume

NEW STANDARD ENCYCLOPEDIA!

RETAIL
VALUE
\$149⁵⁰

FREE with the purchase of a
PHOTOFACT LIBRARY consisting
 of 225 or more Sets... an invaluable
 TREASURY OF KNOWLEDGE for your family—a complete, authoritative, indispensable reference library for your home!



ACT NOW!
 Offer ends
June 30, 1966

SAVE OVER \$120.00! Order your Photofact Library today!

Use the handy order form on opposite page—bring it to your
 Sams Distributor or mail to Howard W. Sams & Co., Inc.

PLEASE CUT ALONG DOTTED LINE

SAVE NOW—ORDER YOUR PHOTOFACT EASY-BUY LIBRARY!

ENTER YOUR ORDER BELOW—OFFER ENDS JUNE 30, 1966

I understand I may select and order a library of PHOTOFACT Sets (minimum 60 Sets) and receive bonuses as explained below. I also understand there will be no interest or carrying charges added to this contract and that all merchandise on the order will be shipped transportation charges PREPAID from Indianapolis, Indiana (Within continental limits of U.S.A.).

CHECK PHOTOFACT SETS TO BE ORDERED ON THIS PLAN

1966 MONTH OF PUBLICATION

1	31	61	91	121	151	181	211	241	271	301	331	361	391	421	451	481	511	541	571	601	631	661	691	721	751	781	811
2	32	62	92	122	152	182	212	242	272	302	332	362	392	422	452	482	512	542	572	602	632	662	692	722	752	782	812
3	33	63	93	123	153	183	213	243	273	303	333	363	393	423	453	483	513	543	573	603	633	663	693	723	753	783	813
4	34	64	94	124	154	184	214	244	274	304	334	364	394	424	454	484	514	544	574	604	634	664	694	724	754	784	814
5	35	65	95	125	155	185	215	245	275	305	335	365	395	425	455	485	515	545	575	605	635	665	695	725	755	785	815
6	36	66	96	126	156	186	216	246	276	306	336	366	396	426	456	486	516	546	576	606	636	666	696	726	756	786	816
7	37	67	97	127	157	187	217	247	277	307	337	367	397	427	457	487	517	547	577	607	637	667	697	727	757	787	817
8	38	68	98	128	158	188	218	248	278	308	338	368	398	428	458	488	518	548	578	608	638	668	698	728	758	788	818
9	39	69	99	129	159	189	219	249	279	309	339	369	399	429	459	489	519	549	579	609	639	669	699	729	759	789	819
10	40	70	100	130	160	190	220	250	280	310	340	370	400	430	460	490	520	550	580	610	640	670	700	730	760	790	820
11	41	71	101	131	161	191	221	251	281	311	341	371	401	431	461	491	521	551	581	611	641	671	701	731	761	791	821
12	42	72	102	132	162	192	222	252	282	312	342	372	402	432	462	492	522	552	582	612	642	672	702	732	762	792	822
13	43	73	103	133	163	193	223	253	283	313	343	373	403	433	463	493	523	553	583	613	643	673	703	733	763	793	823
14	44	74	104	134	164	194	224	254	284	314	344	374	404	434	464	494	524	554	584	614	644	674	704	734	764	794	824
15	45	75	105	135	165	195	225	255	285	315	345	375	405	435	465	495	525	555	585	615	645	675	705	735	765	795	825
16	46	76	106	136	166	196	226	256	286	316	346	376	406	436	466	496	526	556	586	616	646	676	706	736	766	796	826
17	47	77	107	137	167	197	227	257	287	317	347	377	407	437	467	497	527	557	587	617	647	677	707	737	767	797	827
18	48	78	108	138	168	198	228	258	288	318	348	378	408	438	468	498	528	558	588	618	648	678	708	738	768	798	828
19	49	79	109	139	169	199	229	259	289	319	349	379	409	439	469	499	529	559	589	619	649	679	709	739	769	799	829
20	50	80	110	140	170	200	230	260	290	320	350	380	410	440	470	500	530	560	590	620	650	680	710	740	770	800	830
21	51	81	111	141	171	201	231	261	291	321	351	381	411	441	471	501	531	561	591	621	651	681	711	741	771	801	831
22	52	82	112	142	172	202	232	262	292	322	352	382	412	442	472	502	532	562	592	622	652	682	712	742	772	802	832
23	53	83	113	143	173	203	233	263	293	323	353	383	413	443	473	503	533	563	593	623	653	683	713	743	773	803	833
24	54	84	114	144	174	204	234	264	294	324	354	384	414	444	474	504	534	564	594	624	654	684	714	744	774	804	834
25	55	85	115	145	175	205	235	265	295	325	355	385	415	445	475	505	535	565	595	625	655	685	715	745	775	805	835
26	56	86	116	146	176	206	236	266	296	326	356	386	416	446	476	506	536	566	596	626	656	686	716	746	776	806	836
27	57	87	117	147	177	207	237	267	297	327	357	387	417	447	477	507	537	567	597	627	657	687	717	747	777	807	837
28	58	88	118	148	178	208	238	268	298	328	358	388	418	448	478	508	538	568	598	628	658	688	718	748	778	808	838
29	59	89	119	149	179	209	239	269	299	329	359	389	419	449	479	509	539	569	599	629	659	689	719	749	779	809	839
30	60	90	120	150	180	210	240	270	300	330	360	390	420	450	480	510	540	570	600	630	660	690	720	750	780	810	840

Total Number of PHOTOFACT Sets _____ @ \$1.95 each (minimum order 60 Sets) Until July 1, 1966 \$ _____

PHOTOFACT BONUSES (SELECT ONE CATEGORY) ALTERNATE BONUS FOR PURCHASE OF LESS THAN 225 SETS

- 14 Volume Set New Standard Encyclopedia FREE _____ (one allowed with purchase of 225 sets)
- Single Drawer Cabinets to be shipped FREE _____ (one allowed with each purchase of 60 sets)
- Deluxe Four-Drawer Cabinets to be shipped FREE _____ (one allowed with purchase of 200 sets)
- Regular 4-Drawer Cabinets to be shipped FREE _____ (one allowed with purchase of 180 sets)

- Special 4-drawer Cabinet with extension drawer @ \$55.00 EACH _____ \$ _____
- Regular 4-drawer Cabinet @ \$38.95 each _____ \$ _____
- Number of single drawer file cabinets @ \$9.95 each _____ \$ _____
- Bases for single drawer file cabinets @ \$2.50 each _____ \$ _____

TOTAL COST SAMS BOOKS OR SPECIALIZED VOLUMES ADDED TO YOUR PHOTOFACT LIBRARY ORDER \$ _____

Cat. No.	Price	Cat. No.	Price	Cat. No.	Price	
_____	\$ _____	_____	\$ _____	_____	\$ _____	
_____	\$ _____	_____	\$ _____	_____	\$ _____	
_____	\$ _____	_____	\$ _____	_____	\$ _____	TOTAL COST . . . \$ _____

Please add this order to my present Easy Buy Contract. I understand you will adjust my payments, therefore, I am attaching my present Easy-Buy coupon payment book.

I enclose my down payment of \$10.00 and agree to pay the balance of \$ _____ in _____ equal monthly payments. I prefer to make my payments the _____ day of each month.

Until full payment is made, I agree that the title and right of possession of the merchandise shall remain in you, that I will not sell, remove or encumber the same without your written consent, that I assume and shall be responsible for all loss or damage to said goods, and that upon default of any payment or payments, you may, at your option, take back the merchandise or affirm the sale and hold me liable for the full unpaid balance.

Dated this _____ day of _____ 19____. Your Signature _____ (Purchaser)

MY SAMS DISTRIBUTOR IS:

Name _____
 Address _____
 City _____
 State _____ Zip _____

Please ship order to my business name and address shown below.

Name _____
 Address _____
 City _____ (Do Not Use P. O. Box Number)
 State _____ Zip _____

PER SALESMAN: _____ PFF-5

PLEASE CUT ALONG DOTTED LINE

HOWARD W. SAMS & CO., INC. 4300 W. 62ND STREET, INDIANAPOLIS, IND. 46206



RCA is the Mark of Quality in replacement parts, too

Genuine RCA replacement parts assure the quality performance
originally engineered into the equipment...use them to help eliminate costly call-backs

Why settle for substitutes, when genuine RCA precision engineered replacement parts are readily available? They're specifically designed and matched for optimum performance in RCA equipment. Many RCA parts also have universal application (wherever used, they assure RCA's high standard of quality). Your RCA Distributor stocks them for all your parts requirements, including those for:

- ... Color TV, Black and White TV, Radios, Hi-Fi's, and other Home Instruments
- ... RCA Audio-Visual equipment for schools, business and industry
- ... RCA Broadcast equipment for radio and TV stations
- ... RCA Radiomarine equipment

- ... RCA Microwave systems for local utility, turnpike, and other right-of-way communications
- ... RCA 2-Way Radio equipment for police, fire departments, taxicab and truck fleets
- ... RCA Servicemen's Test Equipment.

Avoid wasting profitable service time trying to make-do with substitutes. Your RCA Distributor can supply you with all the genuine RCA replacement parts you need, competitively priced—and readily available.

RCA PARTS & ACCESSORIES, DEPTFORD, NEW JERSEY

Get comprehensive literature—cross-reference and application data on replacement parts—available from your RCA Distributor.



The Most Trusted Name in Electronics

Keyed AGC

(Continued from page 22)

In earlier keyed AGC systems using a pentode, the screen voltage is usually higher than normal for the particular tube employed. In many models the high screen voltage is obtained from boost. Knowledge of this produced a quick analysis in one intermittent condition. Vertical deflection would shrink slowly while picture contrast increased rapidly to overloaded or blanked-out conditions. A look at the circuit revealed one component common to both vertical and AGC circuits; the resistor feeding voltage to the screen of the AGC tube also fed B+ to the plate of the vertical oscillator from the boost source. A visual examination of this resistor, a two-watt composition unit, showed it to be badly overheated; it was replaced with a five-watt wirewound unit and normal operation was restored.

The circuit in Fig. 10 also had an odd, but in this case, strictly AGC trouble. The set was dead and something was smoking—the 'something' was found to be R71, which was overheating due to a cathode-to-filament short in the AGC tube. Replacing the tube eliminated the overheating, but did not restore the picture as expected. Instead it produced an overloaded blanked-out condition resulting from no AGC. Using a VTVM, the AGC tube was found to have approximately normal voltage on the cathode, while the screen was only about twenty volts higher. Since the voltage difference between screen and cathode, in this set, is determined by the voltage drop across R71, it was checked and found to be about one-fourth its normal resistance. Replacing it restored normal operation. One observation is worth noting: the screen voltage of a 'BU8, 'HS8, and other related types is normally only about eighty volts with respect to the cathode, compared to the much higher values in pentode types used for AGC stages. In this case, the use of an override bias to check AGC would have been absolutely useless, inasmuch as the voltage checks would still be necessary and might not have been as conclusive.

The keying pulse applied to the plate of the keyed AGC tube will also produce AGC trouble. A unique trouble of this sort was found in one set. The AGC pot could be used as a contrast control on some stations but on other stations the picture would be either overloaded or blanked-out. In this set, the keying pulse was taken from the horizontal oscillator circuit and was quite different from the usual keying pulse. See Fig. 11. This keying pulse had an amplitude of only thirty volts as against the normal 120-150 volts. Shunting the pulse-coupling capacitor provided normal

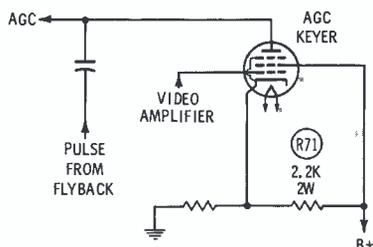


Fig. 10. Source of screen voltage.

Communications, mobile radio...

A First Class FCC License

...or Your Money Back!



Your key to future success in electronics is a First-Class FCC License. It will permit you to operate and maintain transmitting equipment used in aviation, broadcasting, marine, microwave, mobile communications, or Citizens-Band. Cleveland Institute home study is the ideal way to get your FCC License. Here's why:

Our training programs will quickly prepare you for a First-Class Commercial Radio Telephone License with a Radar Endorsement. Should you fail to pass the FCC examination after completing your course, you will get a full refund of all tuition payments. You get an FCC License... or your money back!

You owe it to yourself, your family, your future to get the complete details on our "proven effective" Cleveland Institute home study. Just send the coupon below TODAY. There's no obligation. Cleveland Institute of Electronics, 1776 E. 17th St., Dept. PF-29, Cleveland, Ohio 44114.

NEW in 1966

Only CIE offers new, up-to-the-minute lessons in all of these subjects:

- Logical Troubleshooting
- Laser Theory and Application
- Microminiaturization
- Single Sideband Techniques
- Pulse Theory and Application
- Boolean Algebra

Mail Coupon TODAY For FREE Catalog

Cleveland Institute of Electronics

1776 E. 17th St., Dept. PF-29
Cleveland, Ohio 44114

Please send FREE Booklet "HOW TO GET A COMMERCIAL FCC LICENSE," without obligation.

Your present occupation _____


Name _____ Age _____
(please print)

Address _____

City _____ State _____ Zip _____

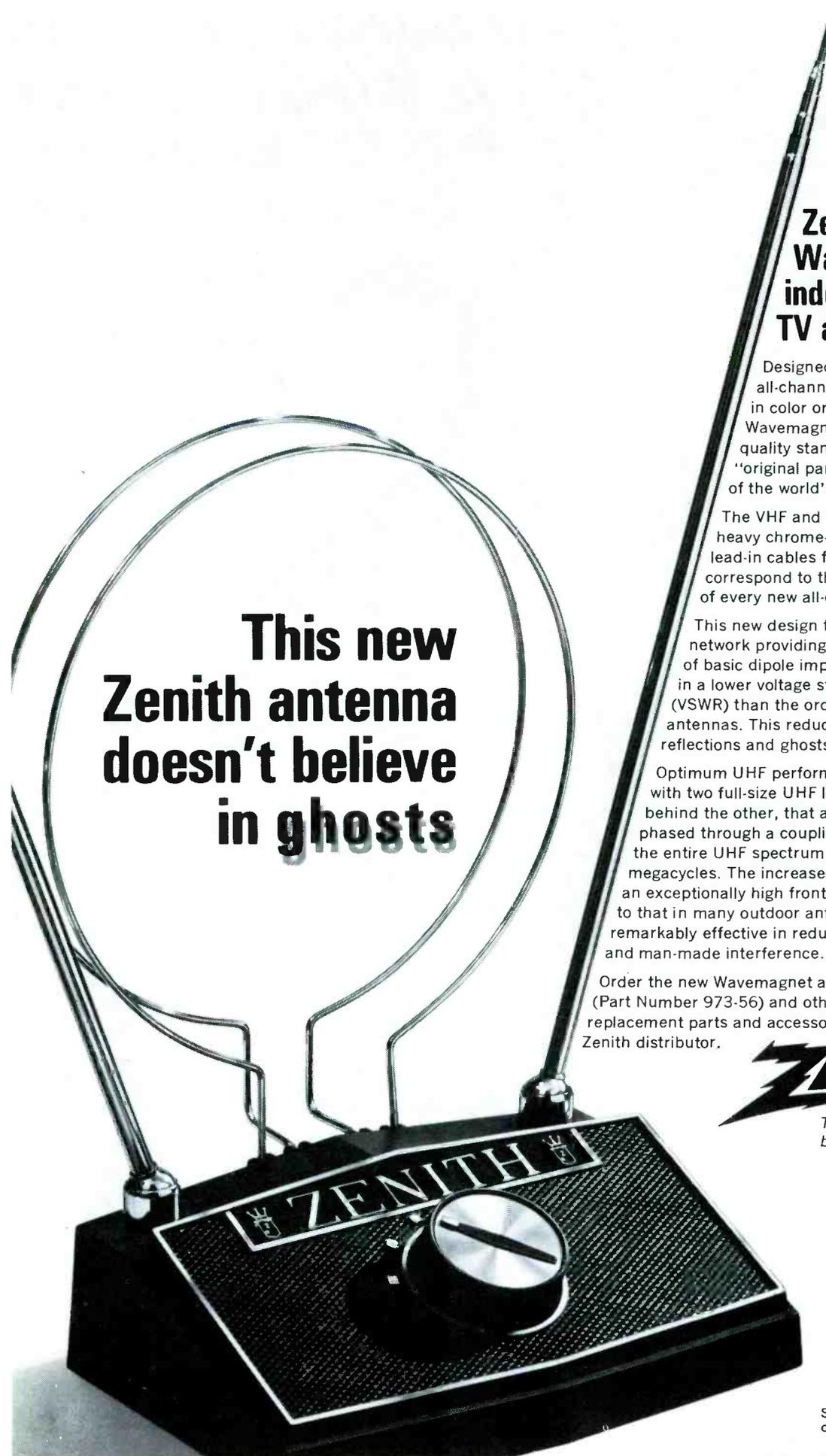A leader in Electronics Training... since 1934





**This new
Zenith antenna
doesn't believe
in ghosts**

**Zenith
Wavemagnet®
indoor
TV antenna**

Designed for clear, sharp, all-channel (2 to 83) reception in color or B&W, the Zenith Wavemagnet antenna meets the quality standards set for Zenith "original parts" . . . your assurance of the world's finest performance.

The VHF and UHF elements are heavy chrome-plated. Separate lead-in cables for UHF and VHF correspond to the input arrangement of every new all-channel TV receiver.

This new design features a special network providing substantial step-up of basic dipole impedance, resulting in a lower voltage standing wave ratio (VSWR) than the ordinary VHF indoor antennas. This reduces snow effect, reflections and ghosts.

Optimum UHF performance is achieved with two full-size UHF loops, arranged one behind the other, that are carefully phased through a coupling network through the entire UHF spectrum from 470 to 890 megacycles. The increased sensitivity develops an exceptionally high front-to-back ratio equal to that in many outdoor antennas. This is remarkably effective in reducing ghosts and man-made interference.

Order the new Wavemagnet antenna (Part Number 973-56) and other genuine Zenith replacement parts and accessories from your Zenith distributor.

ZENITH
®

*The quality goes in
before the name goes on®*

Specifications subject to
change without notice

amplitude. After the old unit was removed it was found to be cracked, a condition not noticeable while it was in the set.

Troubleshooting

Applying an override bias on the IF AGC line is a very common approach to AGC trouble. If its use clears up an overloaded condition, it shows that the AGC circuit is not developing the proper control voltage; however, the picture condition or a VTVM connected to the IF AGC line will tell you the same thing. If override bias restores a normal picture from the dead, blanked-out condition of Fig. 7A or the washed out condition of Fig. 7B, it indicates that the AGC is supplying excessive control voltage. Again either the picture or a VTVM will give the same information. Even after employing override bias to restore the picture, it is still necessary to use the VTVM, and invariably it will reveal voltage discrepancies in the circuit.

AGC troubles discussed in this article have been presented in the order of their possible occurrence, and the troubleshooting techniques that were applied to those cases are recommended in a similar order. For example, in the cases first discussed concerning open peaking coils that produce dead blanked-out rasters from excessive AGC (which a VTVM reading verifies), the initial step is to check the voltage drop across the load resistor of the tube that controls the AGC tube. While it was noted that open peaking coils in video amplifiers cause excessive conduction of a keyed AGC tube and excessive AGC, open cathode resistors or open screen circuits can also produce excessive AGC. In troubleshooting keyed AGC, first check voltages on the stage that controls the AGC tube.

Directly tied in with the voltage drop across the controlling tube's load resistor is the voltage difference between the control grid and cathode of the AGC tube. It is virtually impossible to know exactly what this voltage difference should be, but in normally operating receivers it will be found that it will range between 15 and 30 volts with strong signals. With no signal being received, the voltage difference will range above thirty. Because this voltage difference controls conduction of the AGC tube, some technicians have wondered how the AGC tube can be conducting at all with the heavy bias provided when strong signals are being received. A triple-exposure photo taken from a DC scope (Fig. 12) shows that VTVM readings do not tell the entire story when measuring this control-grid-to-cathode voltage difference. The lower line on Fig. 12 was exposed with the scope probe grounded; it

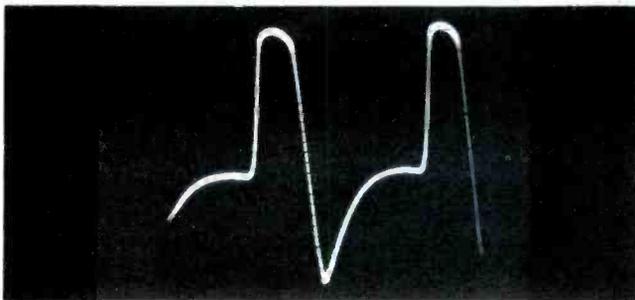


Fig. 11. Unusual keying pulse.

...now available in a **WIRE-IT-YOURSELF KIT!**



Model 1400K ...Kit **\$24.95** Net
 Model 1400 Wired **\$34.95** Net

The new Model 1400 is the only capacitor to do the whole job. It will quickly find whatever defects exist in a capacitor, no matter how elusive. It will also check electrolytics, by-pass, coupling, blocking, and filter capacitors, all without disconnecting them from the circuit.

SPECIFICATIONS	Tests	
	In-Circuit	Out-of-Circuit
SHORTS TEST —Detects shorted capacitors of all types in-circuit with shunt resistance as low as 6 ohms.	✓	✓
OPENS TEST —Detects open capacitors for all values in-circuit down to 7 mmfd., with shunt resistance as low as 15 ohms.	✓	✓
VALUE TEST —Indicates value of electrolytics in-circuit from 2 mfd. to 450 mfd.	✓	✓
HI-LEAK TEST —Detects those hard-to-find leaky capacitors out-of-circuit: Sensitive to 150 megohms...Tests made at 300V D.C.	✓	✓

See your parts distributor... or write for complete catalog

315 Roslyn Road, Mineola, N.Y. 11501
 Export: Morhan Exporting, 458 Broadway, N.Y.C. 10013

MERCURY ELECTRONICS CORP.

Model 1400 IN-CIRCUIT CAPACITOR TESTER...

eliminates the time consuming method of unsoldering and resoldering when checking capacitors

EXCLUSIVE — HI-LEAK TEST

Detects those hard-to-find leaky capacitors (out-of-circuit)... leakage sensitivity to 150 megohms.

EXCLUSIVE—Special low test voltage of 2.9 volts provided to prevent damage to the new low voltage electrolytics used in transistorized equipment.

MERCURY ELECTRONICS Corp. invites you to visit their exhibit at the NEW show June 3,4,5 Civic Auditorium, San Francisco... Booth 2422

Chuck Gravina just learned how to plan his profits the easy way.

It wasn't hard at all. Chuck took advantage of the all-new expanded Philco Tech-Data & Business Management Service. He received all the facts in the mail, liked what he read, subscribed and received Philco's Profit Planning kit *free*.

The kit contains a 24-page guide on profit planning, plus an accurate, easy-to-use profit calculator. Philco designed it especially for service-businessmen like you. You get practical, usable information that can help *you* make *your* business more profitable.

And Chuck's subscription means a wealth of factory-accurate new product manuals — mailed directly to him. So you'll know about the new products *before* they reach the retailers. You'll get monthly information on business management and customer relations. And, of course, you'll receive a full year's subscription to your Philco Service Businessman's magazine.

Chuck Gravina knew a good program when he saw it. And he subscribed. How about you? Shouldn't you subscribe right now and start planning your own profits for 1966? Philco is mailing all the details to thousands of service-businessmen right now. Watch your mail for all the information. And if you'd like any additional facts, talk to your Philco Distributor or contact Parts & Service Department, Philco Corporation, Tioga & "C" Streets, Philadelphia, Pa. 19134.

PHILCO
A SUBSIDIARY OF Ford Motor Company.



Circle 31 on literature card

Engineered for Professional Quality and savings up to 50%

Whether you want the creative pleasure and thrift of build-it-yourself, or factory-assembled professional quality equipment ready-to-use—you save up to 50% with EICO

no-compromise engineering. Be super-critical. Compare EICO with anybody else. The more critically you judge, the more you'll see for yourself that your best buy is EICO.

EICO
KITS & WIRED

COLOR TV LAB


Three compact portable instruments for shop or home Color TV servicing. Add one more and you're set for FM-MPX stereo.



New Model 380 Solid State NTSC Color Generator generates exact NTSC color signals individually and all required dot-bar patterns. Super-compact, 4 pounds light, instant operation. \$159.95 wired only.



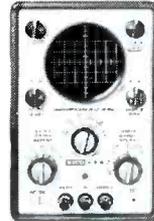Model 369 Sweep/Marker Generator for easiest, fastest visual alignment of color or B&W TV and FM RF and IF circuits. Five sweep ranges from 3-220mc. Four marker ranges from 2-225mc. Crystal marker oscillator. Post injection of markers. \$89.95 kit, \$139.95 wired.



New Model 435 Direct-Coupled Wideband Scope. Top-quality DC-4.5mc scope with 3" flat-face CRT. Zener calibrator: Outperforms 5" scopes three times its size. Facilitates on-location color TV and other servicing. \$99.95 kit, \$149.95 wired.



New Model 342 FM Multiplex Signal Generator. Design lab quality. Both composite audio and FM RF outputs. Inputs for stereo audio source for store demonstrations, critical A/B listening tests. \$149.95 wired.



New Model 1030 Regulated Power Supply. Speeds troubleshooting, design work, production line testing, electronics teaching. Variable bias and plate sources regulated to 1/3 of 1%: 0-150V @ 2ma; 0-400V @ up to 150ma. Ripple less than 3mv rms. Unregulated fil. volts of 6.3V & 12.6V, @3A. Switchable, monitoring milliammeter and voltmeter. \$59.95 kit, \$99.95 wired.



New Model 378 Audio Generator. Near-distortionless sine wave generator (<0.1% 20-20,000c) providing fast, convenient switch-selection of frequencies from 1c to 110kc (1c steps 1c-100c, 10c steps 100c-1kc, 100c steps 1kc-10kc, 1kc steps 10kc-110kc), 8-pos. 10db/step output attenuator & fine attenuator. Output meter (4 1/2" 200ua) with 8 voltage ranges & db scale. \$49.95 kit, \$69.95 wired.



New Model 965 FaradOhm Bridge/Analyzer. "Unusually versatile" — Electronics World. 9-range, low-voltage capacitance-resistance bridge safely measures even 1-volt electrolytics. Metered bridge balance, leakage test voltage (6 DC VTVM ranges 1.5-500V), leakage current (11 DC VTAM ranges 0.15ua-15ma). DC VTVM & VTAM externally usable. \$129.95 wired.



Model 460 Wideband Direct-Coupled 5" Oscilloscope. DC-4.5mc for color and B&W TV service and lab use. Push-pull DC vertical amp., bal. or unbal. input. Automatic sync limiter and amp. \$89.95 kit, \$129.50 wired.



Model 232 Peak-to-Peak VTVM. A must for color or B&W TV and industrial use. 7-non-skip ranges on all 4 functions. With Uni-Probe.® \$29.95 kit, \$49.95 wired.



New Model 779 Sentinel 23 CB Transceiver. 23-channel frequency synthesizer provides crystal-controlled transmit and receive on all 23 channels. No additional crystals to buy ever! Features include dual conversion, illuminated S/Rf meter, adjustable squelch and noise limiter, TVI filter, 117VAC and 12VDC transistorized dual power supply. Also serves as 3.5 watt P.A. system. \$169.95 wired.



New Model 3566 All Solid-State Automatic FM MPX Stereo Tuner/Amplifier. "Very satisfactory product, very attractive price" — Audio Magazine. No tubes, not even nuvistors. Delivers 112 watts IHF total to 4 ohms, 75 watts to 8 ohms. Completely pre-wired and pre-aligned RF, IF and MPX circuitry, plus plug-in transistor sockets. \$219.95 kit (optional walnut cabinet \$14.95), \$325.00 wired including walnut cabinet. UL approved.



New Model 753 The one and only SSB/AM/CW Tri-Band Transceiver Kit. "The best ham transceiver buy for 1966" — Radio TV Experimenter Magazine. 200 watts PEP on 80, 40 and 20 meters. Receiver offset tuning, built-in VOX, high level dynamic ALC. Unequaled performance, features and appearance. Sensationally priced at \$179.95 kit, \$299.95 wired.

FREE 1966 CATALOG

EICO Electronic Instrument Co., Inc.
131-01 39th Ave., Flushing, N.Y. 11352 PF-5

Send me **FREE** catalog describing the full EICO line of 200 best buys, and name of nearest dealer. I'm interested in:

- test equipment ham radio
 stereo/hi-fi Citizens Band radio

Name _____


Address _____

City _____

State _____

1945-1965: TWENTY YEARS OF LEADERSHIP IN CREATIVE ELECTRONICS

colorstar EXPANDS BY 3

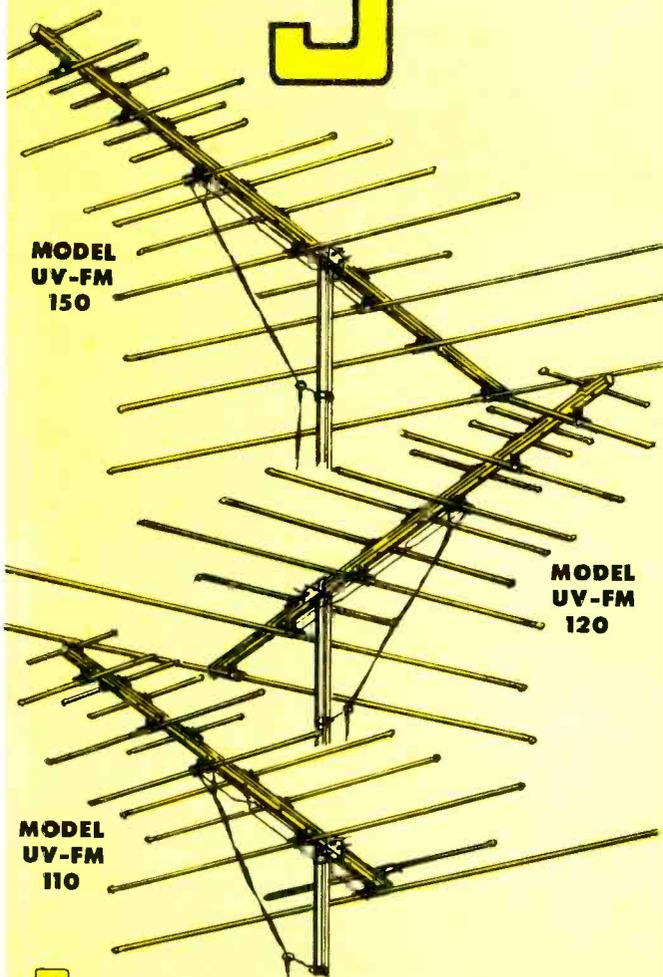

- 3** ANTENNA SIZES
(11 element - 12 element - 15 element)
- 3** POPULAR PRICE LEVELS
(\$14.95 - \$19.95 - \$24.95)
- 3** INSTALLATION APPLICATIONS
(suburban - fringe - medium fringe)
- 3** RECEPTION RANGES
(uhf - vhf - fm)



See us in Room 327 — San Francisco

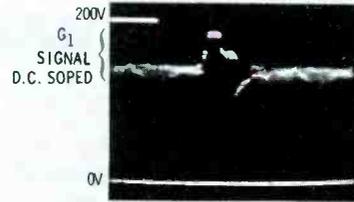


Fig. 12. DC levels at AGC grid.

represents zero volts, and the beam was positioned at the bottom of the screen. Next the scope probe was applied to the cathode of the AGC tube. It represents 200 volts, the same value as measured by a VTVM, and its trace line was shortened for the purpose of identification. The third exposure is the signal at the grid of the AGC tube. Note that its sync tip is very close to the 200 volt level. This third exposure shows that DC levels of the signal vary from a little less than two hundred volts to about 100 volts. A VTVM reading at the grid gave about 160 volts. Thus the bias as indicated by VTVM readings is far greater than the actual bias of the tube.

After it has been established that normal bias is present on the keyed AGC tube, the voltage should be measured between screen grid and cathode. For 'BU8 type tubes, the voltage is always between 65 and 90 volts; for other type pentodes the limits are considerably greater—in some designs as low as 150 volts, in others as much as 300 volts. The tighter limits in the 'BU8 types make this phase of testing a little easier, but the additional grid used for noise cancelling in these tubes is also capable of producing AGC trouble. Any effect of this noise-cancelling grid can be eliminated entirely by shorting it to the cathode.

If all these tests fail to reveal the cause of the AGC trouble, the keying pulse to the plate should be examined. The easiest and only sure way to check the pulse is with a scope. The amplitude ranges from as low as 250 volts to more than 600 volts in some models.

Conclusion

A thorough understanding of keyed AGC theory—knowing how the negative voltage is developed from a positive pulse, knowing how the magnitude of the voltage is controlled, and full awareness of the part played by the controlling stage—is the most important factor in solving AGC problems. Without a thorough understanding of the keyed AGC theory, the measurements or values indicated by test equipment have little meaning.

While there are 'quickie' checks that can in some instances help in troubleshooting keyed AGC, pinpointing the defect in most cases requires extensive, closely examined voltage measurements. It is somewhat ironic that as helpful as a scope can be for troubleshooting less complex circuits, it has definite limitations for troubleshooting this complex circuit. Your knowledge and your VTVM are your best tools in handling these circuits. ▲



"Rather powerful, I'd say."

No one has ever offered a line equivalent to this

IRC's VIDOR has done it again. They're here with the only high power battery line in America today.

Up to now you couldn't even get a high power battery line—from anybody. But now it's here. Only VIDOR has it. And the same great quality you expect from the British (you know about Garrard, Rolls-Royce and Wilkinson).

Talk about profits, listen to this. They'll last up to three times longer than other standard carbon zinc types, so you can sell VIDOR high power for those that want the best, which it is, and get *top dollar*.

Or you can discount and still get a bigger profit than you can selling any other battery.

VIDOR high power batteries have the kind of product-profit-quality story you haven't heard before. And VIDOR is here to stay (they're already here with transistor and general purpose battery lines).

If you haven't heard about VIDOR, you should. And quick. The quicker you do, the more money you'll make. Call your IRC representative for all the profitable details today.



Consumer & Distributor Products Division, IRC, Inc., Philadelphia, Pa. 19108.

See us at Booth 2501—Suite 375—Del Webb's Towne House

Circle 34 on literature card

STEP UP


TO WIDER RANGES
GREATER ACCURACY



Model 630-NA
VOLT-OHM-MILLIAMMETER
PRICE \$85.00



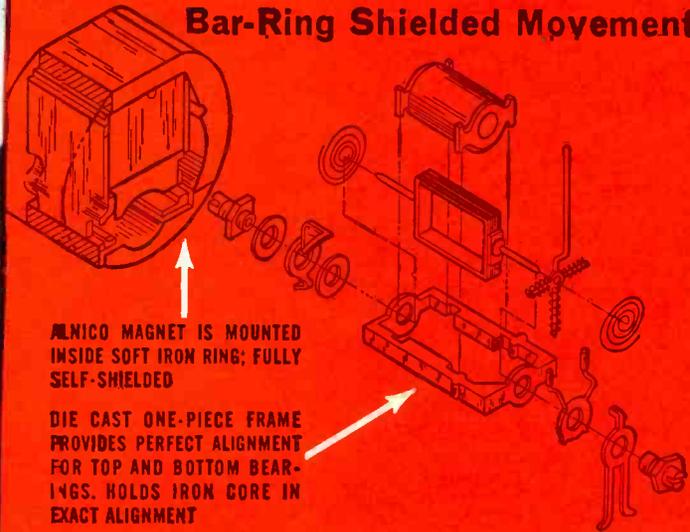EXCLUSIVE PATENTED
.....
Bar-Ring Shielded Movements



ALNICO MAGNET IS MOUNTED
INSIDE SOFT IRON RING; FULLY
SELF-SHIELDED

DIE CAST ONE-PIECE FRAME
PROVIDES PERFECT ALIGNMENT
FOR TOP AND BOTTOM BEAR-
INGS. HOLDS IRON CORE IN
EXACT ALIGNMENT

Uses Unlimited:


- FIELD ENGINEERS ■ APPLICATION ENGINEERS ■ ELECTRICAL, RADIO, TV, AND APPLIANCE SERVICEMEN
- ELECTRICAL CONTRACTORS ■ FACTORY MAINTENANCE MEN ■ INDUSTRIAL ELECTRONIC MAINTENANCE TECHNICIANS ■ HOME OWNERS, HOBBYISTS

FACTS MAKE FEATURES:

- 1** 70 RANGES—nearly double those of conventional testers. Un-breakable window. Mirror Scale.
- 2** HIGHEST ACCURACY—1½% DC to 1200 volts, 3% AC to 1200 volts; mirror scale and knife-edge pointer to eliminate parallax.
- 3** FREQUENCY COMPENSATED—Flat from 20 CPS to 100,000 CPS; varies from ¾ to 1¼ DB at 500,000 CPS. Temperature compensated. Meter protection against overloads.

THE TRIPLET ELECTRICAL INSTRUMENT COMPANY, BLUFFTON, OHIO

See Us in Booth 2001, San Francisco

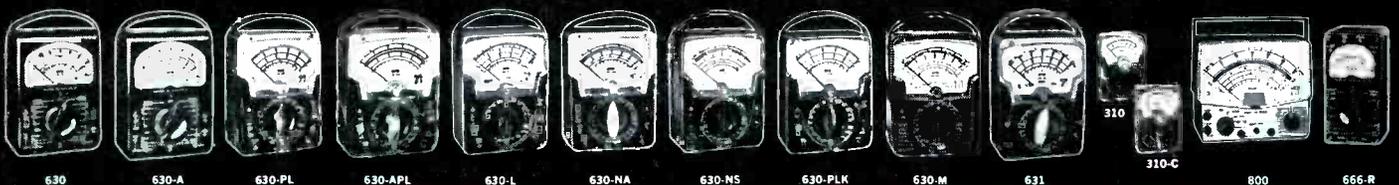

THE WORLD'S MOST COMPLETE LINE OF V-O-M'S. AVAILABLE FROM YOUR TRIPLET DISTRIBUTOR'S STOCK

Circle 35 on literature card

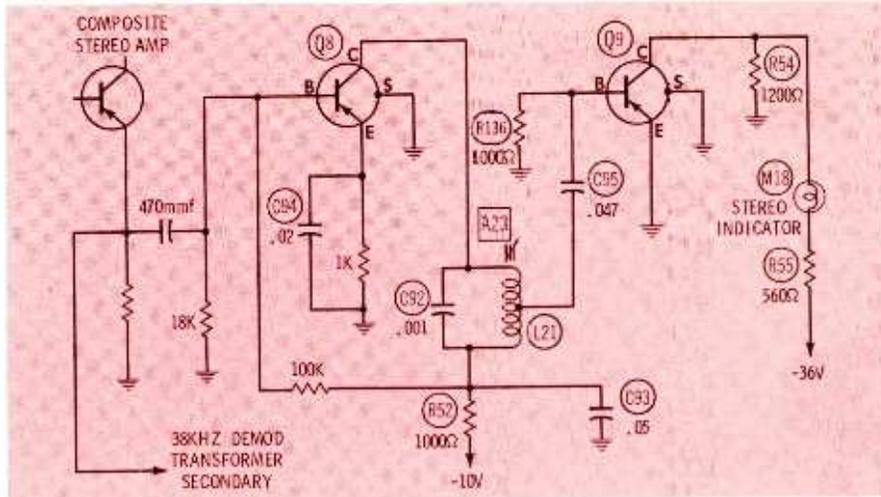


Fig. 5. Schematic Claritone TC-4 chassis.

open diode X28 would also prevent stereo separation.

A leaky or shorted capacitor C95 would reduce the sensitivity of the meter. In fact, if C95 shorts, the meter will not register at all unless the threshold control is turned fully clockwise and the received signal is strong. Capacitor C95 can be checked by measuring the negative voltage at the base of Q14 under a no-signal condition. The DC voltage at the base of Q14 should not change when R4 is rotated; if it does, C95 should be changed. The stereo-threshold setting will affect meter sensitivity.

Fig. 5 is another example of a separate stereo-indicating circuit. Two transistors are used to operate the stereo-on indicator. The signal coupled to the base of Q8 is the composite stereo signal and is developed on the emitter of the stereo-amplifier stage. The same signal is also coupled to the center tapped secondary of the 38kHz demodulation transformer. Q8 has a 19kHz tunable tank in the collector circuit. Adjustment of this tank (A23) will affect the sensitivity of the stereo-on indicator.

The 19kHz signal coupled to the base of Q9 provides forward biasing. The resultant collector/emitter current illuminates stereo indicator M18.

The arrangement of the collector circuit of Q9 makes voltage checking for open components very effective. An open R55 or lamp would result in zero collector voltage. Should R54 open, the collector voltage will increase above normal. This would make the indicator excessive-

ly bright with a faint glow possible in monaural operation.

If capacitor C95 is leaky, a negative voltage would be placed on the base of Q9. The negative base would keep this stage forward biased and the lamp would indicate stereo-on at all times. When the receiver is tuned to a monaural station, the base of Q9 should read zero.

A base/emitter short in Q9 would prevent the stereo-on indicator from working. The base/emitter junction

can be checked with an ohmmeter, just as a diode is checked. However, when checking by reversing the ohmmeter leads, remember that the highest reading will be the 1000 ohms of R136.

The components in the first amplifier can affect the sensitivity of the stereo-on indicator. A normal reading of -8.8 volts on the collector would indicate that R52 and tank coil L21 are not open. It would also indicate that decoupling capacitor C93 was not shorted. The emitter/-base junction of Q8 should read .2 volts with forward bias. It would be best to check this voltage by placing the voltmeter leads directly from emitter to base. (This is good procedure for checking emitter/base bias anytime the emitter is not grounded.)

The frequency determining components of L21 and C92 will affect the indicator operation. If the voltages on Q8 are normal you may check the tank-circuit components as follows: Insert a 19kHz signal on the collector of Q8. Reduce the amplitude of the generator so that the

CHEMTRONICS

**NON-DRIFT
COLOR LUBE**

**CLEANS TUNER
BETTER**

**SAFE FOR
PLASTICS**

**NON-
FLAMMABLE**

**TEST AFTER TEST HAS PROVEN
COLOR LUBE TO BE THE BEST
TUNER CLEANER
FOR ALL COLOR TV SETS!**

CHEMTRONICS inc. 1260 RALPH AVENUE
BROOKLYN, NEW YORK 11236

Circle 36 on literature card

Now an Atlas Sound speaker that can do more than any one speaker could do before...



SERIES AP-30
PATENTS PENDING

... and all you need is a screwdriver to mount, connect and adjust it.

New Series AP-30 install easier, faster and better with built-in transformers, screw-to-line terminals and watts/impedance switch. Very high efficiency is thrifty with amplifier power for low level reinforcement. The speakers are 30 watts rugged for penetration over distance and noise.

From solderless installation to quality performance on the job, four weather-sealed AP-30 models cover your requirements for most single and multiple installations.

From \$23.70 net.

For the complete Professional Series AP-30 story, ask for catalog PFH-15



ATLAS SOUND, Division of
American Trading and Production Corporation
1419-51 39th Street, Brooklyn, New York 11218
Canada: Atlas Radio Corporation, Toronto
THIRTY YEARS OF LEADERSHIP IN COMMERCIAL SOUND
Circle 38 on literature card

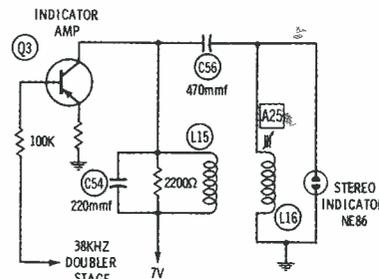
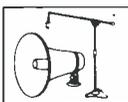


Fig. 6 Schematic Motorola HS 1128.

indicator just turns off. Move the generator lead to the base of the transistor. Assuming the transistor is okay, the indicator should show stereo-on if the tank circuit components are of proper value. If the indicator does come on, adjustment of A23 should control sensitivity. You may have to reduce the generator signal when checking the adjustment of A23. You can also observe C94, the emitter bypass capacitor: If the emitter voltage is normal, the capacitor is not shorted. However, an open C94 would cause degeneration and reduce the sensitivity of the stereo-on indicator.

A solid-state circuit using an NE-86 neon bulb is shown in Fig. 6. Transistor Q3 is the indicator amplifier and is forward biased by a positive voltage developed across a 100K resistor connected to the primary of the 38kHz transformer. The collector load, a parallel tank, develops an AC voltage when 19kHz is present in the received signal. The AC is also placed across a series-resonant circuit consisting of C56 and L16.

While the total AC across the series circuit may be small (considering the voltage across C56 is out of phase with that across L16), the voltage across the inductor is large and approaches 100 volts p-p. This voltage ignites the neon indicator.

Anything affecting the series-resonant circuit would reduce the ignition voltage developed across coil L16. The adjustment of A25 will change both the available ignition voltage and the sensitivity of the stereo-on indicator.

Troubleshooting of this circuit when the indicator fails to light should start with a check of the bulb, then the voltages at the emitter,



Two New Products FROM RAWN!



* THE TUNER-CONTACT CLEANER and FREEZE-IT CIRCUIT COOLER

The maker of Plas-T-Pair, famous for quick, effective plastic repair for anything from TV Sets to dentures, announces two great new products.

LCP TUNER AND CONTROL CLEANER is formulated of the finest materials. It contains the proper amount of silicon for lasting lubrication. The cleaning solvents have the highest rating for cleaning fats, tars, oils.
Six oz. can \$.99

FREEZE-IT COOLER provides pinpoint cooling for the smallest to largest component. Extremely fast acting, it requires a minimum of cooler. There is no overlap to other components.

Six oz. can \$.99



If you want the best for less, buy RAWN'S, for when a better tuner cleaner or circuit cooler is made, RAWN will make it.

RAWN MANUFACTURING CO.

Write for free detailed instruction sheets or see your local distributor.

Circle 37 on literature card

base, and collector of Q1. If the collector is low, check C56 for leakage and L15 for an open. If the collector voltage is high, a check of the transistor is called for. The emitter base junction should be tested by placing a voltmeter between the emitter and base.

When voltages on the transistor are normal, but the indicator does not show stereo-on, the component values in the two tank circuits may be at fault. Try this procedure for checking tank circuits: Insert a 19 kHz signal from the generator onto the collector of the transistor. If the bulb ignites, lower the amplitude of the generator as low as possible, keeping the bulb ignited. Check the adjustment of A25. If the adjustment affects bulb sensitivity, the circuit comprised of L16 and C56 is okay. Next, reduce the generator output to the point where the bulb goes out, and connect the generator signal to the base of Q3. The bulb should ignite if the tank-circuit components are of proper value. Remember that this check assumes the transistor is good.

Conclusion

It has been the purpose of this article not only to acquaint the servicemen with the various types of separate stereo-on indicator circuits, but to offer an effective system of troubleshooting such circuits. A good understanding of the normal operation of the circuit under test and an application of the troubleshooting techniques discussed should provide a speedy solution to most stereo-on indicator problems. ▲

TOPS



VACO AMBERYL® SCREW DRIVERS

The top-selling, top-quality screw driver with precision ground, nickel-chrome plated steel blade . . . distinctive Amberyl handle . . . topped by exclusive Comfordome® hand-ease design. Available in 200 types and sizes . . . your choice of attention getting displays . . . U/L tested and approved for safety. See 'em, try 'em at better stores everywhere!

The Most Powerful Name
in Hand Tools . . . Terminals • Screw Drivers • Nut Drivers • Pliers • Wrenches • Specialty Tools • Solderless Terminals

VACO®

PRODUCTS COMPANY
317 E. Ontario St., Chicago, Illinois 60611

Circle 40 on literature card

at last...
instant color patterns
at your finger tips...
zero warm-up time



THE ALL NEW SENCORE CG135 DELUXE TRANSISTORIZED COLOR GENERATOR

The big push is on in Color TV. Equip yourself now with the new, solid state Sencore CG135 and cash in on the zooming volume of new service business as Color-TV booms! Instant, service-ready RCA standard color bars, cross-hatch, white dots and individual vertical and horizontal bars enable you to set up or trouble-shoot more Color TV sets per day; earn top money in this fast growing service field. It's an analyzer too: Color gun interruptors, unmodulated video for chroma circuit trouble isolation and unmodulated sync pulses to keep Zenith receivers in sync for this test, make color trouble shooting a snap. Sturdy all-steel construction for rugged, heavy duty in the field or shop. Another Best Buy in profit-building service instruments **\$149⁹⁵** from Sencore at

COMPARE THESE FEATURES: SEE WHY THE CG135 IS IN A CLASS BY ITSELF

- Solid state construction employs high priced GE "Unijunctions" to develop six "jump out proof counters" that guarantee stable patterns at all times with no warm-up
- Standard RCA licensed patterns as shown on schematics throughout the industry
- Handy universal color gun interruptors on front panel
- Lead piercing clips insure non-obsolence
- CRT adaptors optional
- Crystal-Controlled 4.5mc Sound Carrier Analyzing Signal to insure correct setting of fine tuning control
- RF output on Channel 4 adjustable to Channel 3 or 5 from front of generator when Channel 4 is being used
- No batteries to run down; uses 115 V AC
- Less than one foot square, weighs only 8 lbs.

professional quality — that's the difference!

SENCORE

426 SOUTH WESTGATE DRIVE • ADDISON, ILLINOIS

Circle 39 on literature card

May, 1966/PF REPORTER 67

Gain to spare at the toughest location



JERROLD SOLID-STATE "DE-SNOWER" AMPLIFIERS MODELS SPC-132, SPC-103

The famous Jerrold 5-transistor Powermate "De-Snowor," Model SPC-132, shown above, and its 2-transistor companion model, SPC-103, give you a choice of antenna-mounting coaxial VHF amplifiers that can't be equalled for bringing bright, snow-free pictures to master-antenna systems.

Their high gain (SPC-132 up to 29 db, SPC-103 up to 16 db) and extremely low noise figure make these preamps ideal for the really tough system installation from custom home to motel or apartment house. Coaxial downlead is a *must* for good color reception, and belongs in any quality system for longtime interference-free reception.

Examine the "De-Snowor" at your Jerrold distributor's, or write for complete information. *Jerrold Electronics, Distributor Sales Division, 4th & Walnut Sts., Philadelphia, Pa. 19105.*



... the most experienced name
in TV signal distribution



Circle 40 on literature card

Leave Those Parts

(Continued from page 36)

tivity of this test may make it worthwhile to go to the extra trouble in critical circuits.

If you've figured out why the test is so sensitive, you'll also see how you can sometimes check coupling capacitors for leakage without unsoldering them at all. Just pull the following tube, and if the grid resistor is high enough in value, it stimulates the high input impedance of a VTVM and a positive voltage develops across it in proportion to leakage in the capacitor. If the resistor is below 500,000 ohms in value, it takes considerable leakage to build a measurable voltage; therefore, this version of the test may not be sensitive enough for critical circuits. If not, revert to the open-end test.

Shorted Capacitors

Shorted capacitors often leave a trail of burned resistors behind, making the short easier to track down: find which resistors are burned, trace from B+ through the last burned one, and the capacitor connected there is probably your culprit. However, that isn't always the case.

Suppose you found the trail of burned resistors shown in Fig. 2. Quick reasoning tells you C3 is the shorted one. If R1 and or R2 happens to be of a value or a wattage rating that won't easily develop an overdose of heat, the culprit could just as easily be C2 or even C1.

A trip down the line with your ohmmeter would tell quickly which is at fault. In an actual case that happened in Jim's shop, we found these measurements between ground and the junctions: R-C1, 1000 ohms; R1-R2, 10 ohms; R2-R3, 5000 ohms; R3-R4, infinity; R4-R5, 50 K; R5-C5, 60K. Analyzing: C2 is shorted. The R1-C1 reading is the value of R1 (the other end is grounded through C2). Similar situation for R2-R3. R3-R4, infinity because R3 and R4 are burned open. At R4-R5, 50K is the reading of leakage across the B+ glter, and 60K at R5-C5 has the 10K resistance added. As a result of our quick run down the string B+ filter, and 60K at R5-C5 has the 10K resistance and a single capacitor.

Shorted coupling capacitors such as C1 in Fig. 1 will ordinarily put a positive voltage on the grid of the following tube, no matter what the value of the grid resistor. It is even possible that the grid resistor and plate resistor will be damaged. In any case, a check with your VTVM will definitely pinpoint a shorted coupling capacitor.

Shorted bypass or decoupling capacitors on B+ lines (both the capacitors in Fig. 2 and C2 in Fig 1)

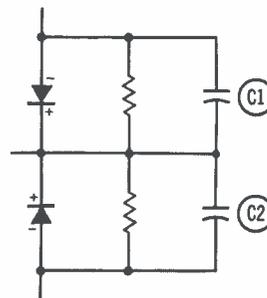


Fig. 3. Balanced diode circuit offers unusual problems.

are usually easy to find by this ohmmeter method, or they can be traced with a voltmeter—simply track down the overload by following the succeeding lower voltages until you reach the point on the B+ line where the voltage is virtually at ground potential.

Direct shorts in capacitors that aren't connected to B+ or other easily measured DC voltages are tough to spot. An ohmmeter is usually the best means; simply check across them with the ohmmeter leads. If they have unusual shunt paths, you may have to unsolder one end. In a circuit like Fig. 3, C1 (or C2) could be checked for a short by clipping the leads across the capacitor, then reversing them. In one direction, the diode will show a low resistance. In the other, the resistance should be that of the resistor. If the resistance is low in both directions, either the capacitor or the diode is shorted (usually the diode, so unsolder it first). You can use this type of reasoning to check small capacitors for shorts in other unusual and low-voltage circuits.

These and similar techniques can be used to test other types of capacitors as well as other components. I've started with small capacitors to introduce you to the techniques and the reasoning involved.

In the next installment, we'll apply these methods to electrolytic capacitors in both tube and transistor equipment and to coils and transformers. Be sure to save this issue so you can refer back to the methods and techniques introduced in this part. ▲

Look for the JUNE issue


- **The Transistor Amplifier**
- **Transistorized Automatic Tuning Auto Radios**
Servicing those automatic tuners.
- **Transducer Circuits in Industry**
Sensing devices and their uses.
- **Leave Those Parts in the Circuit**
Part 2 tells how to check electrolytic capacitors and transformers.
The Troubleshooter
Notes on Test Equipment
Color Countermeasures
New Tube and Transistor Data
- . . . and many more features.

PINPOINT COLOR TV TROUBLES IN SECONDS...



WITH THE NEW IMPROVED SENCORE CA122(A) COLOR CIRCUIT ANALYZER

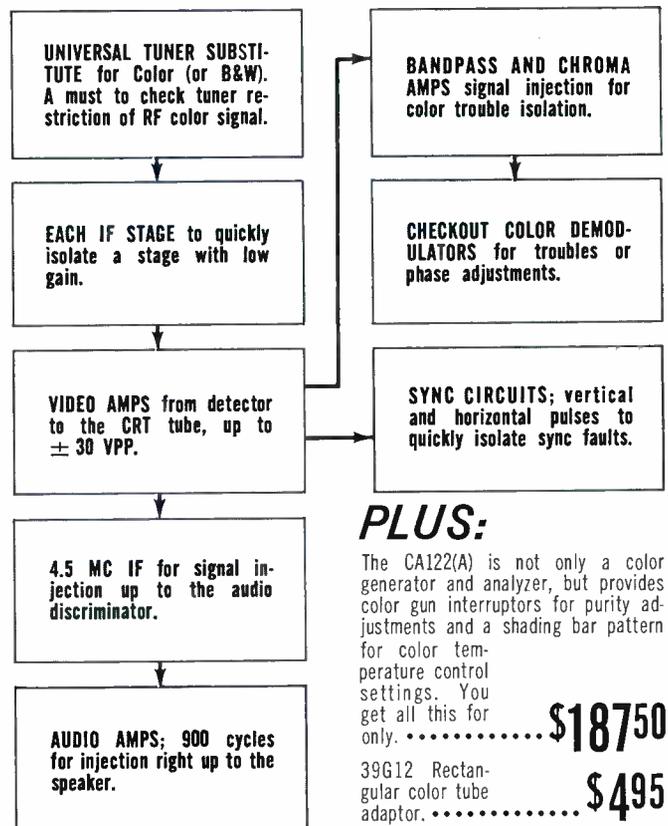It's a standard ten color bar generator; produces vertical lines, horizontal lines, crosshatch, and adjustable dots, PLUS a complete TV analyzer for color and B&W—at less money than color generators only. Here is what the CA122(A) will do for you by tried and proven signal injection into these stages.



PLUS:

The CA122(A) is not only a color generator and analyzer, but provides color gun interruptors for purity adjustments and a shading bar pattern for color temperature control settings. You get all this for only. **\$18750**
39G12 Rectangular color tube adaptor. **\$495**

See your distributor today. He has the CA122(A) in stock now.

SENCORE

426 SOUTH WESTGATE DRIVE

ADDISON, ILLINOIS

Circle 42 on literature card

May, 1966/PF REPORTER 69

VACUUM-TUBES

The puzzle below contains 25 words relating to vacuum-tube terminology. Some of these words are the actual names of tube types; others are related to tube construction. These words are scattered throughout the puzzle, some interlocking with another word. They may be discovered by reading left-to-right, right-to-left, up, down, or diagonally.

See how many of these vacuum-tube terms you can discover. The answers and a score sheet will appear in the June PF REPORTER.


Q	X	E	M	R	S	T	A	C	K	Y	B	E	L	U	Z	T	N	K	I	C	K	E	P	D	H	O	M	T	V	P
D	B	K	H	L	N	A	U	S	P	R	A	O	E	J	Z	C	H	A	S	I	S	L	O	V	Y	E	J	B	C	A
J	F	S	P	O	N	N	E	T	V	A	T	Z	L	S	R	T	R	A	E	J	I	E	X	Z	B	K	M	Q	T	C
S	T	P	L	A	T	E	C	C	A	H	M	N	K	T	V	O	B	K	J	R	E	C	W	C	H	D	O	Q	S	P
N	O	R	M	E	N	Z	V	O	Y	T	S	K	B	P	T	K	U	S	C	E	D	T	I	J	E	Y	M	T	N	O
S	I	M	D	N	U	G	M	R	V	Q	P	A	E	C	N	O	M	B	F	D	C	R	O	S	E	B	A	T	F	T
L	O	O	T	P	L	Z	A	X	X	T	U	V	E	M	N	O	R	P	A	E	F	O	G	N	Q	G	H	J	I	P
M	S	O	C	K	E	T	B	E	O	L	Y	T	F	M	E	P	S	A	R	F	L	D	U	G	W	M	T	Z	L	Y
G	R	T	L	O	R	X	T	B	E	H	E	M	R	S	C	J	K	V	O	R	T	E	M	P	P	Q	X	X	B	D
J	U	N	E	O	P	B	Q	S	X	D	E	L	L	I	F	S	A	G	V	W	A	T	T	A	R	G	E	T	P	Z
R	P	M	N	A	C	F	Q	Z	Y	L	T	A	V	M	T	C	R	U	Z	K	J	I	U	M	R	T	S	E	O	L
D	D	M	O	R	E	P	X	D	A	V	Q	T	X	R	U	A	B	F	H	H	J	T	N	A	X	Z	B	A	L	M
C	A	B	F	R	I	N	G	I	I	P	S	U	T	U	C	J	K	N	Q	Z	V	O	I	L	T	A	C	O	K	T
M	N	X	R	N	N	A	L	R	B	E	S	W	M	I	N	G	K	C	B	V	M	B	N	T	R	P	C	M	K	A
I	Z	T	O	W	F	B	E	G	S	Y	F	E	C	C	N	E	O	F	F	N	A	F	G	S	O	T	H	X	V	B
T	X	R	S	X	B	I	P	X	T	R	J	L	D	X	P	R	U	I	H	H	L	G	E	E	O	S	J	A	E	B
Z	B	Q	T	A	F	L	R	F	F	U	Q	C	I	V	Z	Q	L	J	A	A	K	T	Y	D	P	A	I	S	N	E
Q	F	P	P	I	B	O	Z	H	L	X	O	P	R	M	A	O	B	V	T	E	Z	L	E	X	X	L	B	Q	S	P
A	T	L	T	P	T	T	B	A	M	B	E	E	Q	E	I	V	Z	Q	T	K	V	L	P	H	B	P	R	M	G	B
X	O	C	E	Q	H	R	S	C	R	E	E	N	Z	A	L	T	Q	T	E	Z	E	Z	P	F	N	Y	G	F	J	H
B	E	P	N	N	G	E	P	D	O	L	C	V	V	T	T	A	E	R	R	M	S	X	A	L	Q	K	Q	I	I	J
R	N	H	Z	V	I	Z	H	W	O	C	O	N	V	E	R	T	E	R	E	S	T	Q	R	R	A	P	T	A	X	L
F	V	J	N	B	L	Y	M	N	F	A	P	A	H	O	U	H	N	N	M	Q	E	S	F	B	M	A	P	J	W	M
T	E	X	Q	H	M	R	O	B	I	T	M	X	J	R	N	M	T	A	P	Y	J	M	J	I	E	X	A	R	Z	T
M	L	T	R	T	M	E	B	E	N	H	B	P	I	T	Q	W	A	B	B	F	I	L	A	M	E	N	T	E	R	R
U	O	B	I	J	E	M	F	J	G	O	A	F	L	B	H	A	X	N	O	H	B	P	I	F	L	V	R	A	D	W
H	P	E	A	L	C	T	J	I	D	D	R	J	Q	I	J	F	Y	K	Y	J	A	A	S	Z	E	A	E	B	E	A
Y	E	M	B	Q	A	W	R	P	D	E	M	R	A	N	F	G	P	K	N	I	T	T	K	R	C	M	N	V	H	V
J	A	Q	H	P	E	N	T	O	D	E	T	O	Z	D	L	I	R	X	G	N	S	H	E	A	T	E	R	W	Y	Y
I	T	L	X	T	P	Z	A	L	D	O	N	H	M	E	V	R	E	U	T	O	K	V	T	E	R	S	A	X	Q	X
O	F	V	L	S	I	N	B	T	M	E	A	Y	N	R	E	A	Z	R	O	T	U	A	Q	B	O	P	V	T	S	A
L	U	Y	T	R	J	C	E	V	Z	B	A	L	L	A	T	R	Z	A	N	B	T	T	A	M	N	U	L	O	V	S

*the instrument with
endless uses...the all new
improved completely solid state
SENCORE FS134 FIELD STRENGTH METER*

HERE ARE JUST A FEW OF THE MANY USES...




A. Distribution Systems

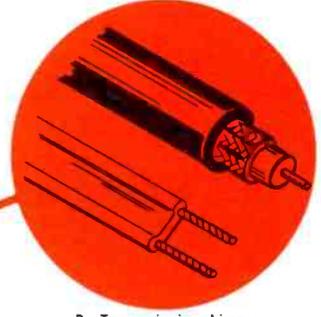


D. Transmission Lines



B. Antenna Installations

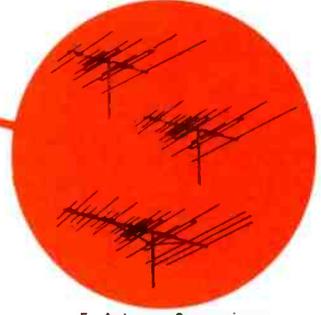

E. Antenna Comparisons

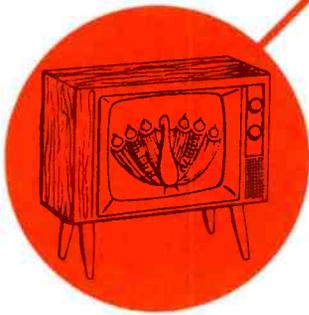

C. Color Insurance



F. Checking Generators

only
199.50
lowest price going

A. INSTALLING AND CHECKING OUT DISTRIBUTION SYSTEMS

Qualify for this multimillion dollar business in hotel, motel, and hospital installations.

B. INSTALLING UHF, VHF, AND FM ANTENNAS

Cut down installation time and pay for the FS134 in a short time on critical UHF as well as VHF and FM antennas.

C. COLOR INSURANCE

Be sure the signal is adequate on each channel for proper color TV operation.

D. CHECK TRANSMISSION LINES

For the first time read actual db loss in either 75 or 300 ohm transmission lines.

E. COMPARE ANTENNAS

For actual db gain; see which is best for each location, both VHF and UHF. Also excellent for

orienting "dishpans" for translator use at the high end of UHF band.


F. CHECK ANY GENERATOR OUTPUT

For correct frequency and output all the way up to a tenth of a volt RMS. What a time saver when you want to know if your generator is putting out.

PLUS: LOCALIZE NOISE AND INTERFERENCE

Find noise source fast; pick quiet locations for antenna installations or orient antenna away from noise when possible.

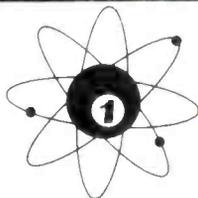These are only a few uses of this UHF-FM-VHF accurately microvolt calibrated field strength meter. You can start paying for the FS134 tomorrow in the time saved today — if you see your Sencore distributor now. Why not pick up the phone and ask him to show you the new FS134?



SENCORE

NO. 1 MANUFACTURER OF ELECTRONIC MAINTENANCE EQUIPMENT


426 SOUTH WESTGATE DRIVE, ADDISON, ILLINOIS 60101

Circle 43 on literature card

May, 1966/PF REPORTER 71



Blooming?

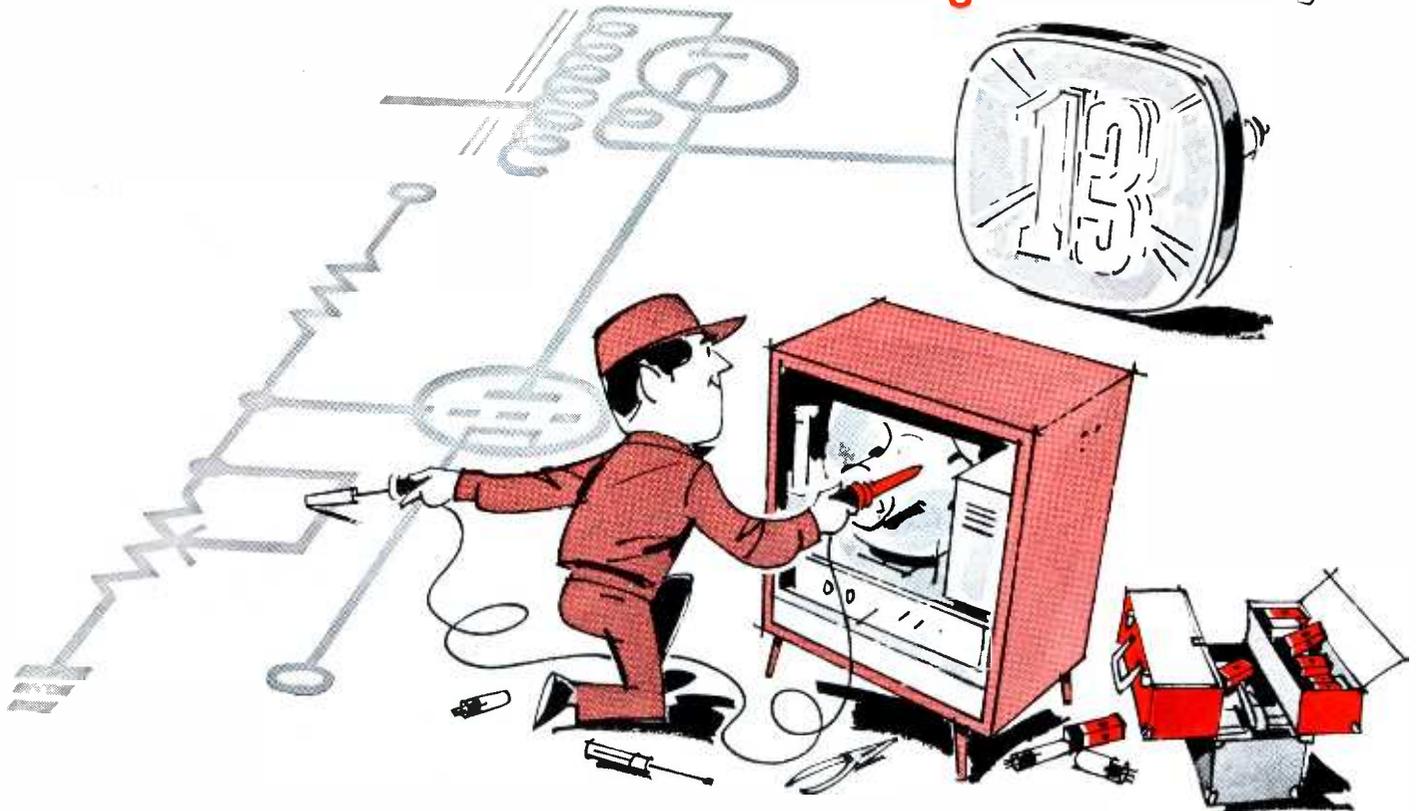

...Varying picture size? Misconvergence?

Check the high voltage regulator section

Poor high-voltage regulation in color sets can be the cause of many needless callbacks, and in some cases, the outright loss of a valued customer. Merely replacing tubes in the horizontal and high voltage sections could result in a premature tube failure brought about by improper high voltage regulator action. Follow these simple FAST-CHECKS and make your color set servicing life a little easier.

1. Determine the proper value for the high voltage by checking the service notes of the receiver. Measure the high voltage at the picture tube anode connection and adjust the high voltage control for the specified value.
2. Turn the brightness control back and forth. If during this adjustment you get blooming, varying picture size and misconvergence, measure the cathode current of the high voltage regulator tube with the brightness turned down. If the regulator tube cathode current is below the specified minimum when the correct high-voltage is attained, the high-voltage input to the regulator system is probably low.
3. To correct small errors in the high-voltage input to the regulator tube, measure cathode current in the horizontal deflection output tube and adjust the horizontal efficiency coil for the specified current.
4. If this adjustment does not increase the regulator tube cathode current to the specified value, check the horizontal output tube, the damper tube and the drive to the horizontal output tube.
5. After making any adjustments or changes required in step 4, rotate the brightness control. If the shunt regulator tube is in good operating condition and you have made the proper adjustments, the blooming, varying picture size, and misconvergence will disappear.

Before replacing a shunt regulator tube, always follow the procedure above. You'll save time and money and have a satisfied customer.

This color TV service hint is another in a series of service hints from RCA. When you order receiving tubes, always specify "RCA". You'll find your customers better satisfied and you'll have fewer callbacks.


RCA ELECTRONIC COMPONENTS AND DEVICES, HARRISON, N. J.



The Most Trusted Name in Electronics

First UHF/VHF/FM 2-83 antenna that really works in fringe areas

New Winegard Chroma-Tel CT-100

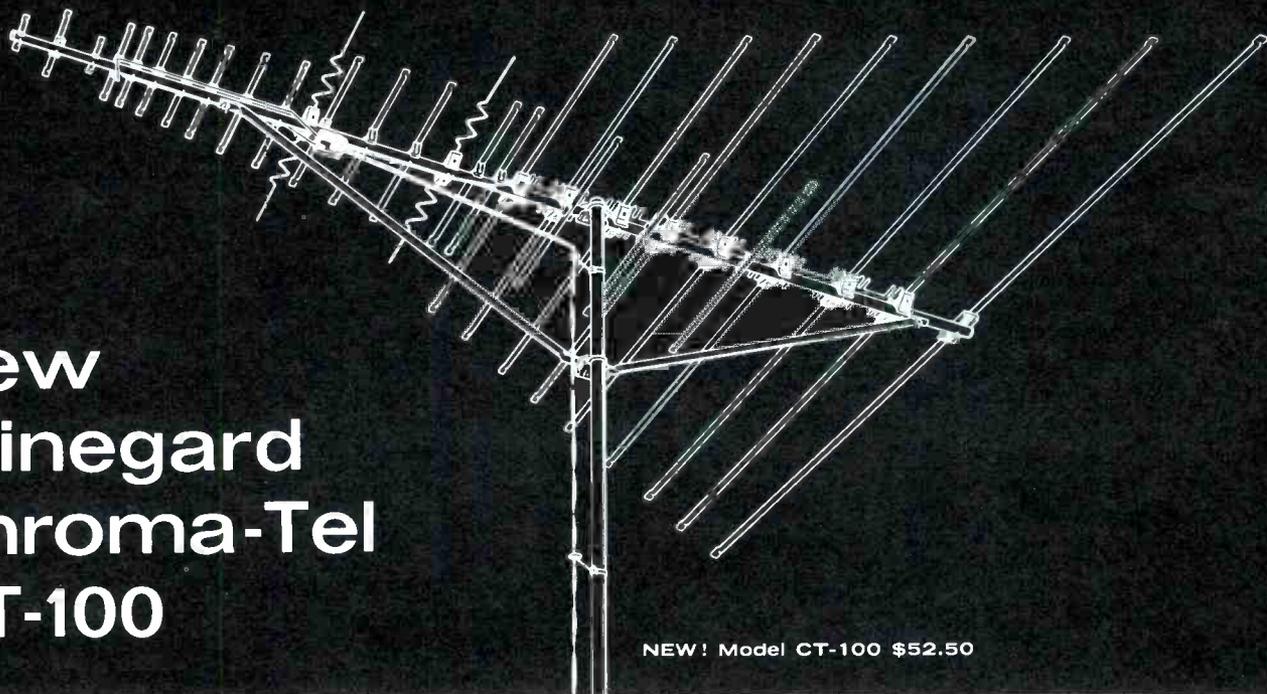

NEW! Model CT-100 \$52.50

Winegard's sensational new CT-100 Chroma-Tel has 29 elements in all. And they're all working to provide the finest all-band reception (UHF-VHF-FM) even in difficult fringe areas.


In addition to those 29 elements, the CT-100 incorporates a unique matching network that guarantees maximum signal transfer to the downlead—and on all channels 2-83 plus FM. Gives sharpest color and black & white reception.

And like all Chroma-Tels, it has Winegard's exclusive Chroma-Lens Director System (intermixes both VHF and UHF directors on the same linear plane without sacrificing


performance) . . . and our Impedance Correlators (special phasing wires that automatically increase the impedance of Chroma-Tel's elements to 300 ohms).

That's Winegard's new CT-100 Chroma-Tel. Bigger and better. But not too big. The full-line of Winegard Chroma-Tels still offers half the bulk; half the wind loading; half the truck space; and half the weight of all other all-band antennas—and at much lower prices. No wonder Winegard Chroma-Tels (now 4 models) are the hottest performing, hottest selling all-band antennas on the market! Better call your Winegard distributor or write for Chroma-Tel Fact Finder 242.



Model CT-40 \$17.50

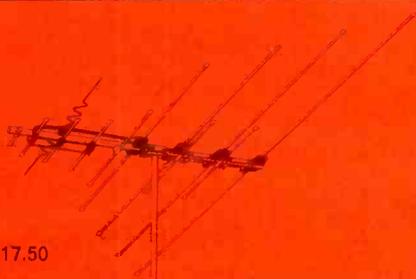

Model CT-80 \$27.50

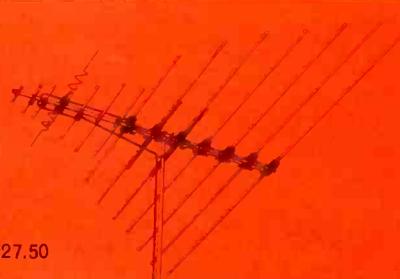

Model CT-90 \$37.50

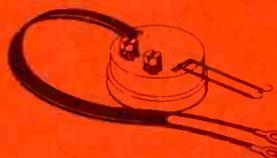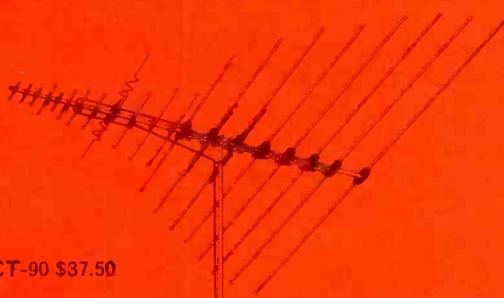

FREE!

Every Winegard Chroma-Tel, including the new CT-100, comes complete with free CS-283 UHF-VHF Signal Splitter. Hangs behind set and separates UHF and VHF signals coming from antenna to the two pairs of set terminals.

Winegard ANTENNA SYSTEMS Winegard Co. • 3000 Kirkwood • Burlington, Iowa 52602

Circle 43 on literature card

www.americanradiohistory.com



POWER BY PRECISE

Three great new electronic power instruments from Precise's exciting "Green Line"—the top quality line that's fast becoming the first choice of electronic technicians, servicemen, experimenters, hams. These "Green Line" power instruments have everything you want—sophisticated circuitry that's been thoroughly checked out for long-life reliability; advanced design that sets new standards of performance and accuracy; special panel layouts that make operation faster and easier than ever before; unique color panel arrangement featuring easy-on-the-eyes Green for improved appearance and readability.

**IF YOU'RE LOOKING FOR THE BEST IN POWER,
AT A POCKET-SOOTHING PRICE,
LOOK TO PRECISE!**

Model 780 REGULATED POWER SUPPLY


A compact two-in-one instrument. Provides a reliable source of variable regulated DC voltage from 0 to +400 volts and from 0 to -150 volts. Both voltages are available at the same time from separate front panel terminals. Also provides 6.3 and 12.6 volt AC heater supply. Includes separate meters on front panel for monitoring output current and voltage. Entire instrument is thoroughly fuse-protected.



\$99.95

Model 713A POWER LAB HIGH OUTPUT SUPPLY

An extremely versatile multi-function bench power supply, with low and high voltage AC and DC supplies. This one unit can operate an entire bench or shop. It provides: DC high current ammeter, DC voltmeter, high current line voltage variable transformer, AC line voltage meter, AC line ammeter, AC line wattmeter. Can be used as a battery eliminator and battery charger; as a variable AC line isolation transformer; as a complete hobby power pack; as an AGC bias box. Includes separate HI-LO indicator lights, plus many other functional features.

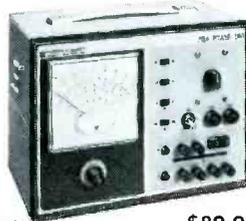

\$89.95

Model 707 ELECTRONIC BATTERY

A portable, low-ripple, high-current DC power supply and/or battery substitute, ideal for test and service work on modern transistorized, tube type, and battery-operated equipment. 8 volt and 16 volt DC ranges, both continuously variable. Up to 20 amperes current capacity. Two wide-visibility meters provide simultaneous monitoring of voltage and current. Use as power supply for auto radios, battery-operated transmitters, CB equipment; charging auto and boat batteries; operates model trains, relays, road-race sets, etc. All top-rated, quality-controlled components assure long life, reliable operation.



\$59.95

See the complete Green Line—power instruments, scopes, VTVM's, signal generators, tube testers, decade boxes, probes—at your local distributor, or write direct for full information and specs.

PRECISE ELECTRONICS

Division of Designatronics Incorporated
76 East Second Street, Mineola, L.I., New York
ENGINEERED EXCELLENCE IN TEST EQUIPMENT

Circle 46 on literature card

XYZ Color


(Continued from page 26)

rather from black and white to a blue or red tint. The new Admiral color receivers use a variable resistor in the CRT grid circuit to change the tint of the screen from blue through gray to sepia. This control also will vary the color picture when a color broadcast is on.

One example of the color-fidelity circuit is shown in Fig. 3. In this version, R2 controls the bias on the blue and green guns of the CRT. Advancing this control produces a higher positive voltage on the blue and green grids. Since R201 is smaller than R196, the blue grid voltage will be raised proportionally higher than the green. The result is a greenish blue tint on the raster. Reversing the action lowers the voltage on those grids, and since the red grid remains at a constant potential, the raster will take on a reddish tint. The fidelity control should be centered during initial gray-scale tracking adjustments.

There are advantages for this color-fidelity control for both the customer and for the serviceman. After the color receiver has been in use several months, the tubes and components in the XYZ circuits will age and change the picture tint. The color-fidelity control can be adjusted to compensate for this condition. Also, when we look at the color picture we do not all see alike, so the viewer can adjust the shade or tint to his own vision.

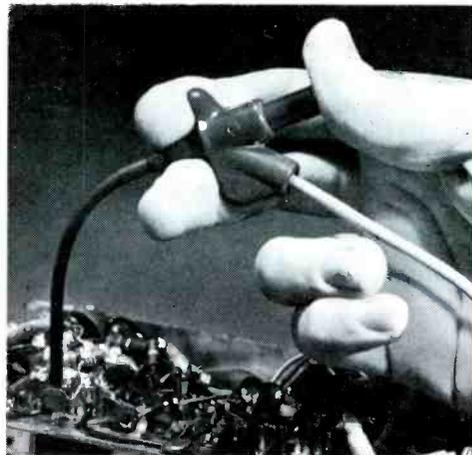The tint should be set to the customer's preference. He may want a little more red or blue put into the picture. With the color-fidelity control he can adjust the picture to suit himself. ▲



Clever Kleps 30

Push the plunger. A spring-steel forked tongue spreads out. Like this  Hang it onto a wire or terminal, let go the plunger, and Kleps 30 holds tight. Bend it, pull it, let it carry dc, sine waves, pulses to 5,000 volts peak. Not a chance of a short. The other end takes a banana plug or a bare wire test lead. Slip on a bit of shield braid to make a shielded probe. What more could you want in a test probe?

Available through your local distributor, or write to:

\$147





RYE INDUSTRIES INC.
120 Spencer Place, Mamaroneck, N.Y. 10543

Circle 47 on literature card

for the traffic outlet
that doesn't want to lose a sale...
RCA'S NEW LAZY SUSAN FULL-LINE BATTERY CENTER



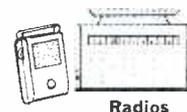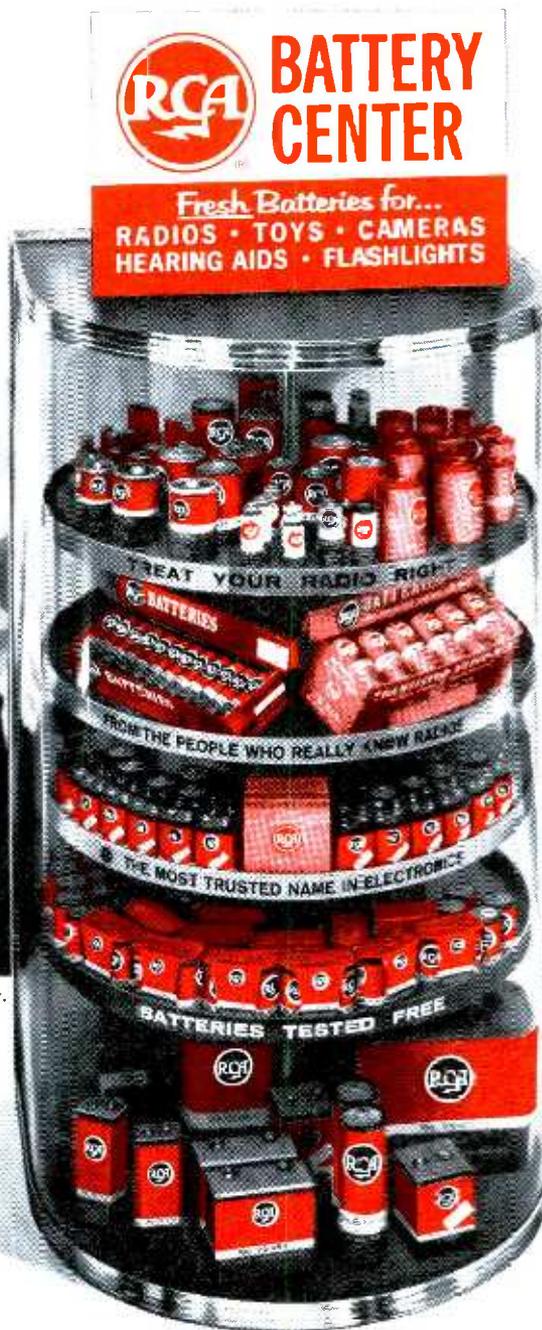
15" wide, 15" deep, 28" high, plus header.




Radios



Toys

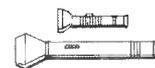

Flashlights

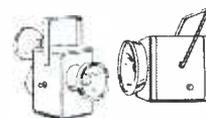


Lanterns



Hearing Aids



Cameras

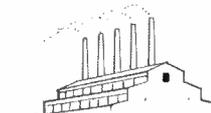

Industrial and Commercial Applications

The base section can also be used as a showcase for transistor radios and other battery-operated devices.

Now display *and* sell up to 40 different battery types for radios, toys, flashlights, hearing aids, cameras and industrial and commercial applications. Batteries can be grouped by application for faster service, easier inventory control. RCA's Lazy Susan Full Line Battery Center (1P1214) is a clear extruded vinyl plastic showcase with revolving shelves of high impact styrene. Solid brass trim adds strength to the unit. It's attractive, durable and convenient. Latched half doors in the rear allow easy access to battery stock. Don't let those potential sales walk by...contact your RCA Battery Distributor...and start making your battery business that much better.

RCA ELECTRONIC COMPONENTS AND DEVICES, HARRISON, N. J.



The Most Trusted Name in Electronics



The Troubleshooter

answers your servicing problems


Spurious Signal

I have recently run across a symptom in a General Electric TV model 21C1562 (PHOTOFACT Folder 391-1) which I have never seen in five years of servicing. After the set has played for about 40 minutes, a white streak appears on the right side of the screen. It moves up and down the right side of the screen, but does not pull in the picture or raster. The length of the white line varies from 2" to 4" and extends from the right side toward the center about 3". The streak is present even when the set is receiving no signal. The picture has a slight vertical jitter.

I have substituted all tubes but it has not helped. When I shunt C5 with another 40 mfd capacitor the streak disappears; however, after removing the original C5 and replacing it, the streak is still present.

RONALD STROUP

Deer Creek, Okla.

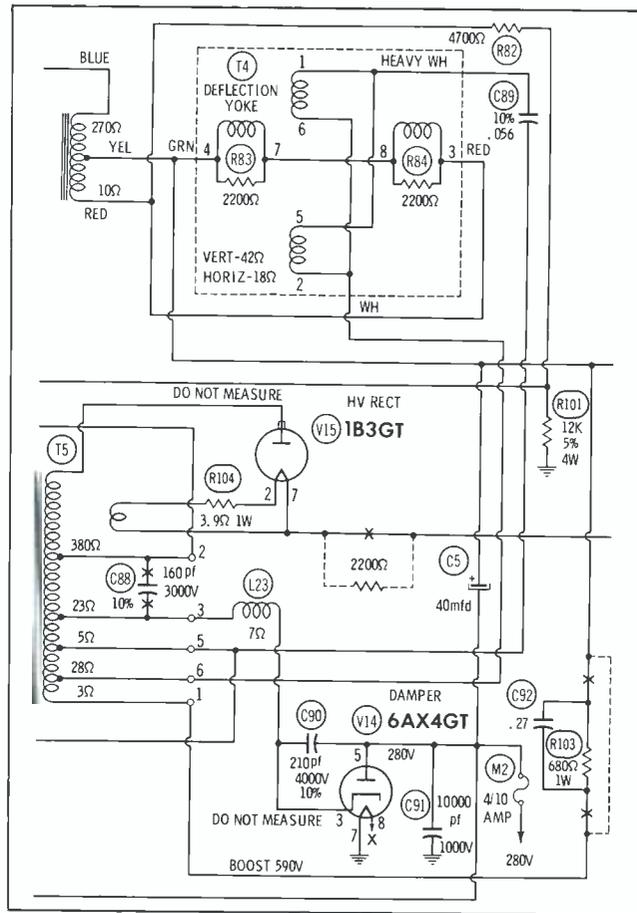

there's **EXTRA PROFIT** in **NOISECTOMIES***

QUIETROLE
IS HARMLESS TO PLASTICS

Harmless to metal... non-conductive, non-inflammable and non-corrosive. Zero effect on capacity and resistance.

* a simple quick operation performed by Doctors of Electronics with the aid of Quietrole to cure scratchy, noisy tuners and controls of TV and radio. Fast set recovery with no ill side effects assured. Saves time... makes money for servicemen.

At Your Distributor ... Ask for Quietrole by Name.
manufactured by **QUIETROLE CO.**
Spartanburg, South Carolina

Circle 50 on literature card

fat, ugly machine that can make you a lot* of money.

Just so you'll be sure it's an oven. Not for pies. Nor cakes. Not even for pizzas. It's for television picture tubes, and performs chores like tube evacuation, cathode bombarding, induction heating, and more. Most important, it is part of the exclusive Windsor System of picture tube rebuilding — your key to a business you can run (right along with what you're doing right now), and make extra money with in amounts you might not have thought possible (*like \$4,000, \$5,000, \$10,000 a year and more!)

Sound good? Then send for the full story. Write direct, or circle our number right away. Who knows, that happy guy in the picture could be you.

WINDSOR ELECTRONICS, INC.
999 North Main Street
Glen Ellyn, Illinois 60137

Circle 49 on literature card

Join our profit-sharing plan for color TV repair.


Here's how the plan works. First, Sylvania advertises you in TV Guide as the right TV serviceman for color repair—Mister Right. We make you a big name in a booming business.

We have all kinds of tie-in display pieces.

We supply you with our *color bright 85*TM picture tube and color receiving tubes that you can push or ignore, since you're independent.

And the payoff: you get the profits from all the new color TV repair business we send you. We get more profit because we make more replacement parts. No one else offers you a profit-sharing plan like this because no other major tube manufacturer deals exclusively with the

Independent Service Dealer.

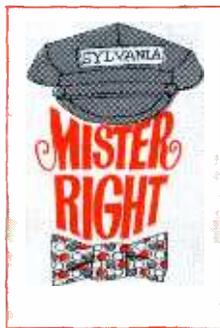

In the Mister Right part of the plan, your Independent Sylvania Distributor puts your name, town and phone number in up to four TV Guide ads this year. You're listed right next to our big, full-color ads that talk about you.

He also gives you up to nine Mister Right display pieces. Free banners, displays to spark up your windows, decals and cards. And, an illuminated Color TV Service sign for a slight charge.

So join our profit-sharing plan. There'll be a lot to share. See your Independent Sylvania Distributor.

Sylvania Electronic Tube Division, Electronic Components Group, Seneca Falls, New York 13148.



SYLVANIA
SUBSIDIARY OF
GENERAL TELEPHONE & ELECTRONICS **GTE**

Circle 51 on literature card

**before you buy any
color generator . . .
get all the facts**




**only one* has all
these features and
it's only 99⁵⁰**

LECTROTECH V6

Any comparison will prove that the Lectrotech V6 truly stands alone. Provides all of the time-tested standard features plus many Lectrotech exclusives for the fastest, most reliable color installation and servicing. The V6 gives you: Crystal-controlled keyed rainbow color display • All cross hatch, dots, vertical lines only, horizontal lines only • Red-blue-green gun killer (usually extra or not available on other color bar generators) • Exclusive Dial-A-Line feature (Horizontal adjustable 1 to 4 lines wide) • Exclusive solid state reliability • Exclusive voltage-regulated transistor and timer circuits • Exclusive simplified rapid calibration • Off-On Standby Switch • Adjustable dot size • Color level control • Connects to antenna terminals (no connections needed inside of set) • Power transformer—line isolated, to prevent shock hazard • Lightweight and portable, only 4½" H. x 7¾" W. x 10¾" D. Weight, 7½ lbs.

*Except our own V7

ONE YEAR WARRANTY

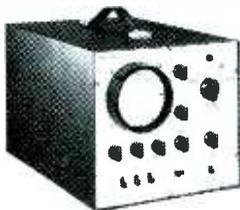

V7 Sensational new Lectrotech V7 — the only complete Color TV Test Instrument.

Has all the features and performance of the V6 PLUS Lectrotech's exclusive built-in Color Vectorscope for simplified visual color servicing.

Complete.....only **189⁵⁰**



See your distributor or write for details before you buy any color generator. Dept. PF-5
LECTROTECH, INC.
1221 Devon Avenue • Chicago, Illinois 60626

Circle 52 on literature card

What you have described appears to be a picture curl, although a picture curl normally runs the entire length of the raster. However, it is possible that only a portion of the curl is being displayed in this case.


General Electric Product Service Bulletin No. 8T (Oct '57) lists a production change to eliminate picture curl on the right side of the raster. It consists of a parallel combination of a 680 ohm, 1 watt resistor and a .25 mfd capacitor in series with terminal No. 1 of the horizontal output transformer (590 volt boost voltage). The chassis location of both components is shown in the "chassis top view" of PHOTOFACT.

Low Voltage Too Low

I have substituted every component in the audio-output stage of a Philco Chassis 8L41 (PHOTOFACT Folder 399-2), but have been unable to determine the reason for a 35 volt reading at the 145 volt source. The plate and screen voltages are normal and I have resoldered all connections to eliminate the possibility of a high-resistance connection. I have also substituted the 6CU5 several times, and have tried lowering the resistance of the plate circuit by placing a 150 ohm resistor across the primary of T5. What have I overlooked?


J. H. BARNETT

Freeport, Texas

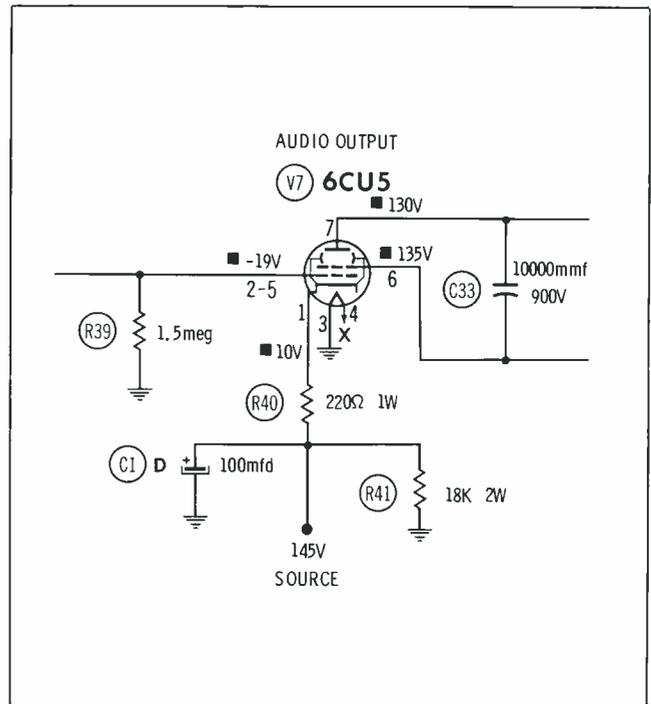

It should be remembered that a voltage source can be affected by the circuits to which it provides voltage. In this example, the 145 volt source provides plate and screen voltages to the 1st, 2nd and third video IFs, the sound IF and limiter, and to the remote control chassis (if the set you are servicing is so equipped). Suggest you check capacitors C10, C13, C16 and C27 in these circuits for a shorted condition. (Larry Allen's article "Leave Those parts In the Circuit!" in this issue provides some good tips on checking such components.) ▲

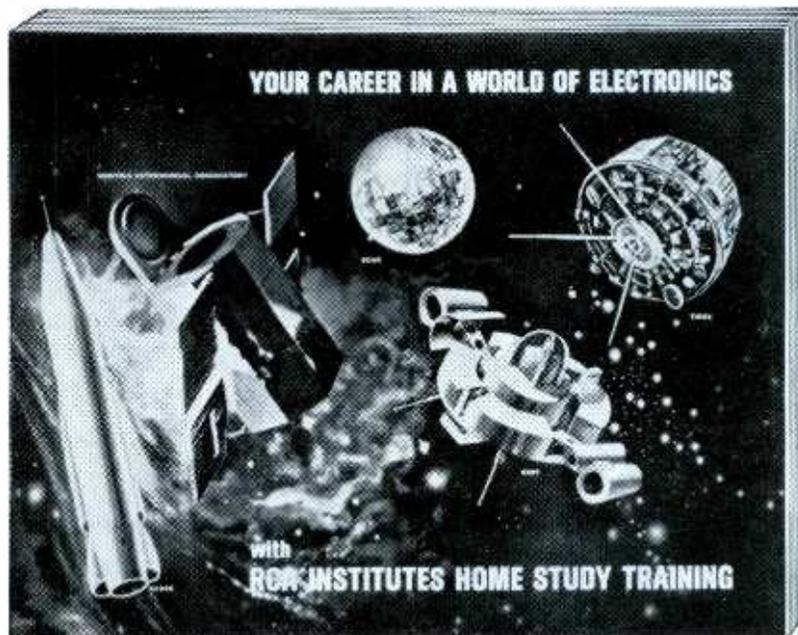SEND FOR RCA'S NEW 1966 HOME STUDY CAREER BOOK TODAY



• COLOR TV • COMMUNICATIONS ELECTRONICS • AUTOMATION ELECTRONICS • SOLID STATE ELECTRONICS

- Learn about the amazing "Autotext" programmed instruction method—the easier way to learn.
- Get the facts about the prime quality kits you get at no extra cost.
- Read about RCA Institutes' Liberal Tuition Plan—the most economical way for you to learn electronics now.
- Discover how RCA Institutes Home Training has helped its students enter profitable electronic careers.

Send coupon today, or write to RCA Institutes, Inc. 350 West 4th Street, New York, New York 10014.

RCA INSTITUTES, Inc. Dept. PF-56
A Service of Radio Corporation of America
350 West 4th Street, New York, New York 10014

NAME _____

ADDRESS _____

CITY _____ STATE _____ ZIP CODE _____

Veterans: Check Here

Classroom
Training
Also Available.
Check here for
free catalog



The Most Trusted Name in Electronics

it's here! most advanced
color TV test instrument
ever developed



- OBSOLETES ALL OTHERS
- ELIMINATES ALL GUESSWORK

LECTROTECH V7*

A sensational new color generator with 4 major Lectrotech exclusives . . . plus all of the time-proven standard features . . . in one compact, portable unit. For the first time, you can install and service color TV completely, accurately and faster! Here are the facts:

EXCLUSIVE—COLOR VECTORSCOPE—Until now, available only in \$1500 testers designed for broadcast. Accurately measures color demodulation to check R-Y and B-Y plus all 10 color bars for color phase angles and amplitude. A must for total color and those hard to get skin tones.

EXCLUSIVE—SELF-CALIBRATING — Adjust timing circuit without the use of external test equipment. No need to return unit to a factory for adjustment.

EXCLUSIVE—DIAL-A-LINE — Now, you can adjust horizontal line to any width desired from 1 to 4 lines wide.

EXCLUSIVE—SOLID STATE RELIABILITY — Only two tubes are used in combination with fully transistorized diode-rectifier circuit.

PLUS— the V7 produces all Crosshatch, Dots, Vertical only, Horizontal only and Keyed Rainbow Patterns. RF at channels 3, 4 or 5. Video Output (Pos. and Neg. adjustable) for signal injection trouble-shooting. Red-Blue-Green Gun Killer. All transistor and timer circuits are voltage regulated to operate under wide voltage ranges. Lightweight, compact — only 8¼" x 7½" x 12½". Net. **189.50**

ONE YEAR WARRANTY

For the full story on the V7, write for complete catalog or see your distributor.



V6 Complete color bar generator with all the features of the Lectrotech V7 except the Vectorscope. Only **99.50**

See your distributor or write Dept. PF-5

LECTROTECH, INC.

1221 Devon Ave. • Chicago, Ill. 60626 • Area 312 465-2622

Circle 55 on literature card




Color Countermeasures

Symtoms & Tips From Actual Shop Experience

Chassis: Zenith (All Chassis)

Symptoms: No separation between sound and picture during fine tuning with continuous buzz in sound. AGC control smears picture.

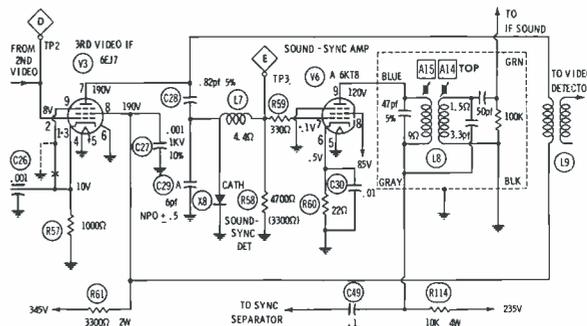Tips: Replace X8 Crystal Diode used as sound and sync detector.



What are you doing about car-stereo?

The 4-Track Market Is Here!

C-503 CUSTOM CRAIG CAR-STEREO



Craig Car-Stereo is your answer. Lots of consumer electronics people are picking up extra profits with the Craig line.

It's the best line on the market. Loaded with quality you can sell. Quality electronics you and your customers can count on.

Along with the 4-track, dual-head Car-Stereo line, you've got a huge tape cartridge music library that keeps the profits coming in.

Craig Car-Stereo is your answer. Drop us a line for the name of your nearest distributor.


The 4-track market is here and it's yours for the selling!

CRAIG PANORAMA, INC.

2302 East 15th Street • Los Angeles, Calif. 90021 • (213) 623-2421 • TLX 76-4116

Circle 56 on literature card

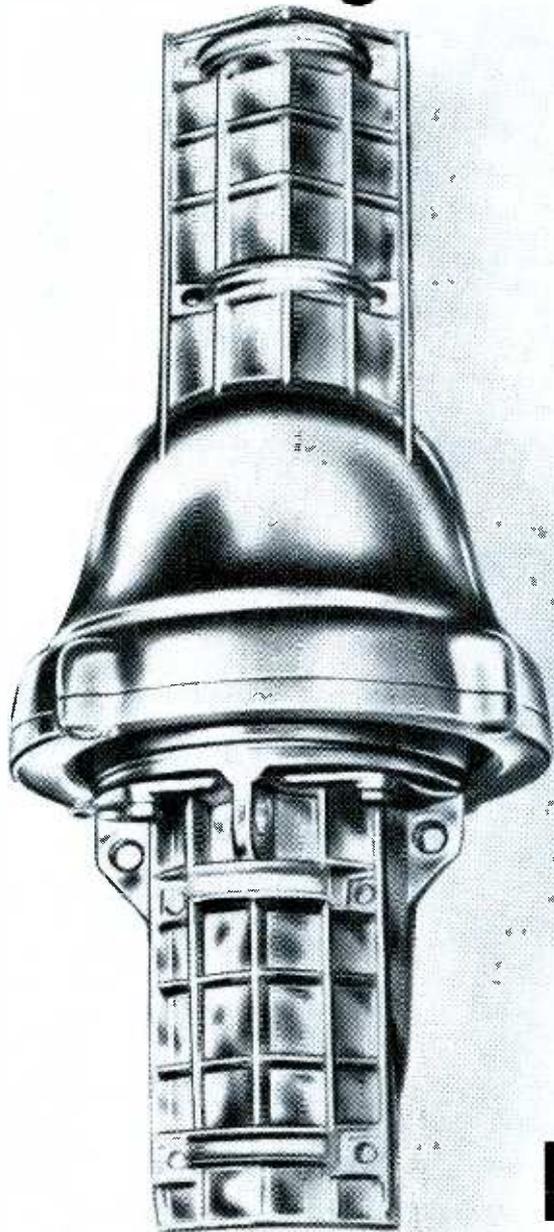Never ask a lightweight rotor to do a heavyweight's job.



Selling your customer a lightweight rotor when he has a large antenna array just doesn't make sense. Especially since you can offer him an alternative: the heavy-duty "Bell Series" rotor, from CDE.

Available in both automatic and manual forms, this rotor is designed specifically for large, heavy antenna arrays... designed specifically for unmatched fringe-area reception... designed to give your customers the finest color TV reception possible. In fact, this is the *only* heavy-duty rotor available.

We call it the Bell Series because of its completely weatherproof, die-cast aluminum housing. You'll call it rugged because it has 4 to 5 times the stalling and braking torque of any other rotor! This means *any* antenna will turn, even under the most adverse weather conditions... and that your customers will get terrific color or black and white reception despite high winds or heavy icing. Great FM reception too!

The Bell Series rotor: one-of-a-kind built for one-of-a-kind performance!

CDE CORNELL-
DUBILIER

Circle 57 on literature card



TYPE L . . . for long, long years of service life ask your distributor for **PLANET LYTICAPS**, the universal replacement type electrolytic capacitor. Available in a wide range of capacities in voltages from three to five hundred. LYTICAPS are "Engineered for Quality".

PLANET SALES CORP.

225 Belleville Ave.
Bloomfield, New Jersey

Circle 61 on literature card



Product Report

For further information on any of the following items, circle the associated number on the Catalog & Literature Card.



Paging and Talkback Speakers

A screwdriver is the only tool required to mount, connect and adjust the volume on the AP-30T (70 volt) and AP-30T-25 (25 volt) Professional Series, 30 watt, omnipurpose public-address speakers now available from Atlas Sound.

AP-30T and AP-30T-25 specifications: Power, continuous up to 30 watts; equalized to frequencies above horn cutoff, 40 watts. Frequency response 225 - 14,000 Hz. Sound level, 125 db measured 4' on axis at 30 watts input. Dispersion, 100°.

Time and cost saving features for installing and wiring both types of speaker include: built-in 70 volt or 25 volt line transformer; watts/impedance selector switch; screw terminals; and omnidirectional, three way adjustable mounting bracket.

The speakers are constructed of metal, using die castings and aluminum parts. Special corrosion proofing and enamel weather protection are also used.


The dimensions of both speaker models are 10" wide, 9½" high and 10½" deep. Price is \$48.50.

ZENITH QUALITY WIRE, CABLE AND ROTORS

Zenith's new heavy-duty rotor


can turn a 150-lb. antenna in a complete circle in only 45 seconds! Rugged, dependable Zenith quality throughout.

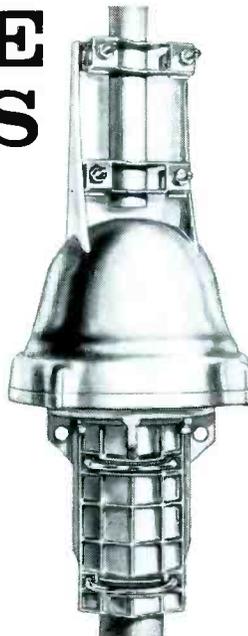You can couple it quickly to a mast or tower without using an adapter. Choose from two control units; one stops rotor automatically at preset position, the other is directly controlled by the operator.



New Zenith wire and cable

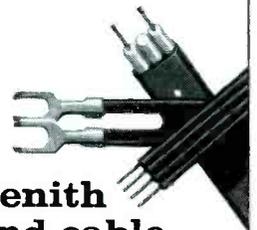assures exceptionally low loss and longer life. Designed to Zenith's exacting specifications for UHF and VHF reception, antenna rotors and other electronic uses. You'll find convenient lengths—from 50-foot coils to 1000-foot spools.



Order all genuine Zenith replacement parts and accessories from your Zenith distributor.

BUILT TO THE QUALITY STANDARDS OF ZENITH ORIGINAL PARTS

ZENITH The quality goes in before the name goes on®

Circle 58 on literature card



WHAT'S HAPPENING
TO **OAKTRON**

NEW
IDEAS

NEW
PRODUCTS

NEW
PACKAGING

NEW
PROMOTIONS

NEW
SALES RECORDS

STOP IN AT BOOTH #2507 CIVIC AUDITORIUM IN SAN FRANCISCO AND CHECK OAKTRON . . . WHERE EXCITING NEW THINGS ARE HAPPENING TO SPEAKERS AND BAFFLES.

YOUR BLUEPRINT TO BETTER SOUND
OAKTRON

OAKTRON INDUSTRIES, INC. MONROE, WISCONSIN
Circle 68 on literature card



Semiconductor Tester
(76)

A new in- or out-of-circuit semiconductor tester has been announced by **American Electronic Laboratories, Inc.** The Model 259 In-Circuit Semiconductor Tester provides a rapid and safe means of testing semiconductors. It measures both transistors and diodes, in-circuit, for reverse leakage down to 500 ohms of shunt loading. The Model 259 also measures field effect transistors for leakage and transconductance, and both low and high power transistors for 1000 cycle beta. Other measurements include the resistance across the emitter-to-base, collector-to-base, and collector-to-emitter electrodes.

The Model 259 is housed in a drip-proof, high-impact plastic case, with cover.




Scrulox Screwdriver
(77)

Because of increasing industry use of square recessed screws in the production of appliances and electronic instruments, **Upson** has added Scrulox drivers to their regular line. The 4" blades are aluminum with genuine Scrulox inserts to insure long life. Other features include shock-proof, breakproof handle construction which prevents blade drive through or

brand new
... and very important ...

QUAM COLOR TV REPLACEMENT SPEAKERS PREVENT COLOR PICTURE DISTORTION

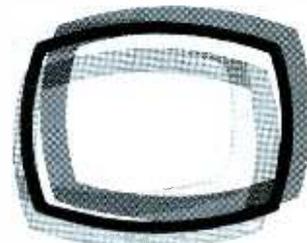OFTEN CAUSED BY STRAY
MAGNETIC FIELDS FROM
ORDINARY LOUDSPEAKERS



When you use an ordinary loudspeaker in a color TV set, you're looking for trouble . . . picture trouble. The external magnetic fields from standard loudspeakers will deflect the primary color beams, causing poor registration and distorted pictures.



QUAM RESEARCH SOLVES THIS PROBLEM

An entirely new construction technique, developed in the Quam laboratories, encases the magnet in steel, eliminating the possibility of stray magnetic fields and the problems they cause! These new Quam speakers have been eagerly adopted by leading color TV set manufacturers. Quam now takes pride in making them available for your replacement use. Five sizes (3" x 5", 4", 4" x 6", 5 1/4", 8") . . . in stock at your distributor.

QUAM

QUAM-NICHOLS COMPANY


234 E. Marquette Rd. • Chicago, Ill. 60637

Circle 60 on literature card

May, 1966/PF REPORTER 83

twisting. Handles are UL approved.

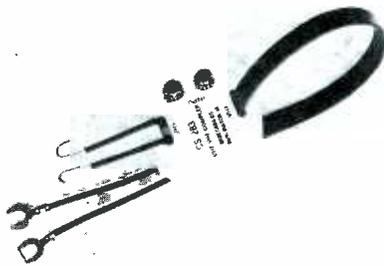The new Scrulox screwdrivers are color coded and are available in No. 0, 1, 2, and 3 tip sizes.



Signal Splitter
(78)

A printed circuit UHF-VHF back-of-

set signal splitter. Model CS-283 has been introduced by the **Winegard Company**. Use of a printed circuit provides low loss and high efficiency and eliminates capacitance between coils.

The CS-283, described as a "pigtail" splitter, is designed to separate UHF and VHF signals coming from a combination UHF-VHF antenna or antenna coupler. The pre-attached 300-ohm lead-in connects to the UHF and VHF antenna terminals on the set or UHF converter.

VHF bandpass is 0-235 mc. UHF bandpass is 400-1000 mc. UHF and VHF circuitry has 15 db minimum isolation to prevent interaction. The unit is completely assembled and lists at \$3.00.



Solid-State Regulated Power Supply
(79)

A solid-state power supply designed to supply fully regulated DC voltages for transistorized equipment, is announced by **Pace Communications Corp.**

The unit delivers from zero to 15 volts DC at up to 2.5 amperes—useful for servicing Citizens-band transceivers, auto radios, transistor radios, industrial-laboratory instruments, and production-line equipment.

Designated Model 5803, the power supply provides regulation better than 1% (line and load) at 13V, 1A continuous rating; ripple less than 1 millivolt, continuous. All silicon semiconductor construction assures good reliability and heat resistance.

The metered output may also be used to charge storage or Nicad batteries, as a source for low-power metal plating, or to power variable-speed DC motors.

The price is \$59.95.

Faulty, fragile, filament failures.

Phooey.


Yes, phooey to filament failures and costly tube replacements. CB radios should be solid state to take the bumps and knocks of mobile use.

That's why *all* Amphenol Citizens Radios are solid state. We don't believe in thin filaments that heat up and short or snap. Or in fragile glass enclosures. Or in tubes at all, when transistors have

more than ten times the life and warm up instantly. That's why Amphenol has the broadest line of solid state equipment available today.

Take the new Spokesman 650 for example. This ten crystal-controlled channel receiver is complete with spot button, S and RF meter, squelch control, 23 channel RF tuner, solid state switching (no relay, making it possible to provide communications even at 25°F below zero), and most important, Amphenol dependability.

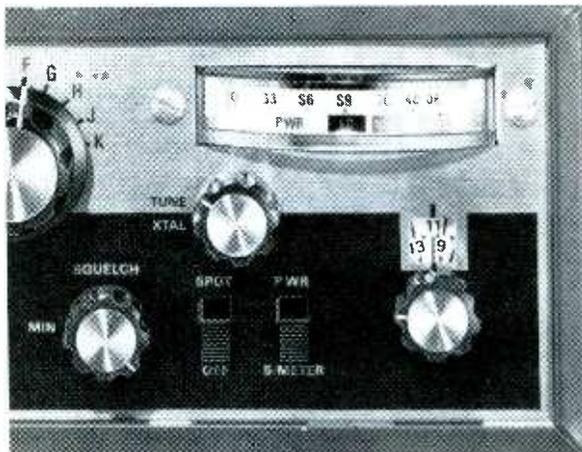Remember, when you want the reliability of solid state circuitry, think of the industry's broadest line, Amphenol. See your local Amphenol distributor for more information on Amphenol solid state, and the Spokesman 650, or write us direct.



AMPHENOL DISTRIBUTOR DIVISION

AMPHENOL CORPORATION
2875 South 25th Avenue, Broadview, Illinois 60153

Circle 62 on literature card

Every No-Noise Aerosol Product

Guaranteed

Non-Flammable

Non-Toxic and

Won't Affect Plastics

"NO NOISE"

Insist On This Trusted
NAME BRAND
Avoid Risky "Private Labels"

**"No Noise" PRODUCTS ARE
PERFECT FOR COLOR TV**

No need to stock special color TV LUBRICANTS. No-Noise is ideal for both color and black & white TV. FREE 5" plastic extender push-button assembly for pin-point application with all No-Noise products.

ELECTRONIC CHEMICAL CORP.
813 Communipaw Avenue, Jersey City 4, N. J.

Circle 59 on literature card



Stereo Headphones (80)

Stanford-MB headphones are the latest quality electronic products from West Germany, imported and distributed nationally by **Stanford International**.

Model MB-K64S stereo headphones feature exceptionally clean design and light weight (5 ozs.) to eliminate listener fatigue.


The single headband is made of plastic covered unbreakable steel. Air-cushioned oval earpads of foam rubber fit snugly and shut out ambient noise. The 17-ohm standard stereo model has an 8-foot cable with bright metal telephone plug, and has a frequency range of 20-17,000 cps. Retail price is \$17.95.




Transmatch (81)

A compact, portable, "laboratory" that indicates the status of the vital RF characteristics of equipment to help maintain optimum operation, the Model 715 Transmatch is manufactured by **EICO Electronic Instrument Co., Inc.** It is designed for both the professional and hobbyist in ham & CB work.

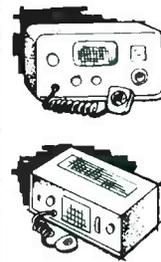At the flip of a switch, the 715 gives you fast, accurate readings of: standing wave ratio, true RF power, modulation percentage, modulation distortion, and relative field strength. Rugged, all solid-state, self-powered, and sensitive (with 100-ua meter), the 715 complements the EICO line of ham and CB transceivers. Kit is \$34.95. wired is \$44.95.



The Heart of your Radio is Its

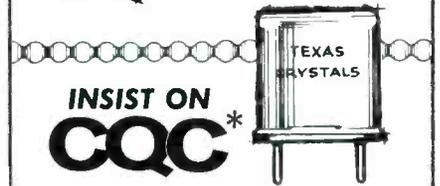

* Controlled Quality Crystals available only from Texas Crystals dealers. Extensive precision testing throughout manufacture enables Texas Crystals to unconditionally guarantee their frequency control crystals. Use of Texas Crystals in space program and by other governmental agencies is evidence of the quality you can count on.


If your dealer can't supply your needs, send his name with your request for catalog to our plant nearest you.



1000 Crystal Drive Fort Myers, Fla. 33901 4117 W. Jefferson Blvd. Los Angeles, Calif. 90016
Phone: 813-936-2109 Phone: 213-731-2258

Circle 65 on literature card


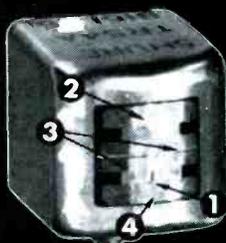
Know how to spot head wear? These unretouched photos show you how!



"LOOK"—Look for: (1) the gap; (2) depressions, gouges, score marks; or (3) angled wear lines on either side of pole pieces.

"TOUCH"—Run your fingernail across face of head vertically and horizontally in both directions. Can you feel (4) rough surfaces, sharp edges, or catch your nail on (5) a weargroove?

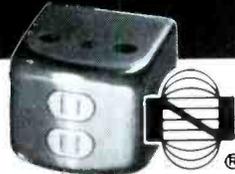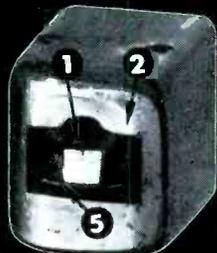OR "LISTEN"—Use our AT-100 Test Tape or play a pre-recorded tape with good "highs" as offered by Latin-type music or Violins. Do the "highs" sound flat, mushy or distorted?



**IF ANY OF THESE
CONDITIONS EXIST—
REPLACE THE HEAD!**

FOR VISUAL
COMPARISON...
take a look at this
new Nortronic head.

Your tape head wears every time you use your recorder, and as it wears, the brilliant realism of tape is lost! Pressure pads and the magnetic tape itself, both cause wear. The oxide coating used on the tape is an abrasive which slowly grinds away the face of the head—and pressure pads cause uneven wear. For top performance, intimate tape-to-gap contact is essential . . . and poor contact, due to wear, results in severe high frequency losses, erratic output, loss of output!

See your local Nortronic Dealer!
Protect your investment in tape and equipment by replacing worn heads with full-fidelity Nortronic precision replacements.

Nortronic


8167-A 10th Ave. No. • Minneapolis, Minn. 55427

Circle 64 on literature card

CHEK-IT CIRCUIT TESTER

FOR ONLY **\$1.49** DEALER NET
LESS BATTERIES

**BATTERY OPERATED
TESTS WITH POWER OFF**

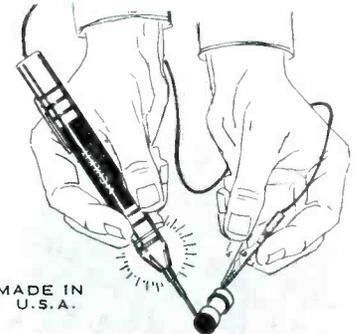

MADE IN
U.S.A.

- CONTINUITY • FUSES • SWITCHES
- CHIMES • APPLIANCES • MOTORS
- BUZZERS • PUSH BUTTONS
- AUTO IGNITION and VOLTAGE REGULATORS, ETC.


ASK YOUR ELECTRONIC PARTS DISTRIBUTOR FOR

W MODEL NO. BZ5

MANUFACTURED BY
WORKMAN Electronic PRODUCTS INC
SARASOTA FLORIDA

Circle 72 on literature card

May, 1966/PF REPORTER 85

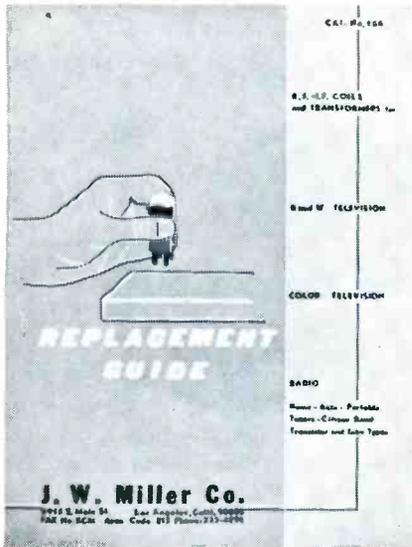

NEW Coil Catalog & Replacement Directory No. 166

New 168-page catalog gives specifications and prices for the most complete line of RF and IF coils. Replacement directory cross references coils for all known TV sets, radios and car radios.

For your free copy, call on your local distributor or write directly to:




J. W. MILLER COMPANY

5917 SO. MAIN STREET • LOS ANGELES, CALIFORNIA 90003

SEE YOUR LOCAL DISTRIBUTOR FOR THE FULL LINE OF RF AND IF COILS, CHOKES, FILTERS AND TRANSFORMERS.

Circle 67 on literature card

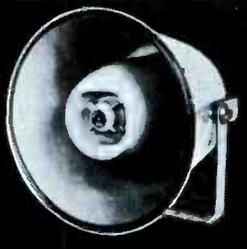YOU CAN SAFELY PUT ALL YOUR EGGS IN ONE BASKET



You profit more by using the same dependable brand of public address speakers and microphone stands for all your needs.

Your ATLAS SOUND distributor makes one-stop shopping easy with a wide selection of proven models...backed by our years of commercial sound experience...concern for product reliability...pricing for your profit.

Look for the ATLAS SOUND mark of quality on all paging and talkback speakers, trumpets, drivers, explosion-proof speakers, sound columns...floor, desk, boom stands...accessories for all. This trademark makes a world of difference. Write for catalog PFC-15

ATLAS SOUND, Division of
AMERICAN TRADING AND PRODUCTION CORPORATION
1419-51 39th Street, Brooklyn, New York 11218
Canada: Atlas Radio Corporation, Toronto



THIRTY YEARS OF LEADERSHIP IN COMMERCIAL SOUND

Circle 66 on literature card

Letters

(Continued from page 16)

of the first man and have a limited knowledge. The solution is to get more training, facts, and experience.

This probably answers your question "why then don't these same intelligent technicians use such logic in their everyday work?"

It is evident to me that you already knew the answer because of the quality, content, and accuracy of your publication. I shall continue to study your magazine—I say study on purpose—it is that type as well as being entertaining. I am also starting a review of mathematics!

I could not hope for a magazine to be more timely, more helpful with less chaff than yours. In a crew of 16 men with whom I work, none but myself believes in a trade magazine subscription out of their own pocket (strange?) yet, two besides me do subscribe to PF REPORTER because of my enthusiasm.

Sincerely,
WILL MORGAN

Citrus Heights, Calif.

Mr. Morgan's letter needs no answer from us. The answering should be done by all service technicians—to themselves. —Ed.

GET YOUR FIRST CLASS COMMERCIAL F.C.C. LICENSE

or Your Money Back!

The Grantham F. C. C. License Course by correspondence will prepare you to pass the F.C.C. examination for your first class radiotelephone license. We know this, but of course you do not really know if it is true. Therefore, we make this offer: After completing this course if you should fail to pass the F.C.C. exam for this license, Grantham will refund all of your tuition payments!

Read complete details in our new 1966 catalog of courses. For this free catalog, write:

Dept. 69-DE
Grantham School of Electronics
1505 N. Western Ave.
Hollywood, Calif. 90027

Card 69 on literature card

INDEX TO ADVERTISERS

MAY, 1966

Aeovox Corp.	50
Amphenol Borg Corp.	35, 84
Antennacraft Co.	62
Arrow Fastener	42
AT&T	39
Atlas Sound	66, 86
B&K Mfg. Co., Division of Dynacorp.	37, 45, 48
Belden Mfg.	47
Bussman Mfg. Div.	18, 19
Castle TV Tuner Service	17
Channellock, Inc.	42
Channel Master Corp.	15
Chemtronics, Inc.	65
Clarostat Mfg. Co., Inc.	43
Cleveland Institute of Electronics	57
Cornell Dubilier	81
Craig Panorama	80
Electronic Chemical Corp.	84
EICO	61
Finney Co.	51
General Electric Co.	87
Grantham School of Electronics	86
IRC, Inc.	63
JFD Electronics Corp.	10, 11
Jerrold Electronics	cover 2, 68
Kay-Townes Antenna Co.	49
Lectrotech, Inc.	78, 80
Littelfuse, Inc.	cover 4
Mercury Electronics Corp.	59
Miller, J. W. Co.	86
Nortronics Co., Inc.	85
Oaktron Industries, Inc.	83
Ohmite Mfg. Co.	16
Philco Corp.	60
Planet Sales Co.	82
Precise Electronics	74
Quality Tuner Service	42
Quam-Nichols Co.	83
Quietrol Co.	76
RCA Components & Devices	cover 3, 52, 56, 72, 75
RCA Institutes	79
Rawn	66
Rye Industries	74
Rohin Mfg. Co.	40
Sams, Howard W. & Co., Inc.	54, 55
Sarkes Tarzian, Inc.	9
SENCORE, Inc.	67, 69, 71
Simpson Electric Co.	14
Sprague Products Co.	13, 41
Sylvania Electronic Products, Inc.	77
Texas Crystal	85
Tripplett Electrical Instruments	64
Vaco Products Co.	67
Winegard Co.	73
Windsor Electronics, Inc.	76
Workman Electronic Products, Inc.	85
Zenith Radio Corp.	53, 58, 82

3 reasons why

it pays to use
General Electric
renewal parts



1 INCREASED CUSTOMER SATISFACTION

The best customer is a satisfied one—satisfied with your service and with the quality of the parts you use. Satisfy your customers with genuine G-E quality.

2 AVAILABILITY OF PARTS AND SERVICE CATALOGS

G.E.'s dependable distribution system makes it easy for any appliance technician to obtain genuine parts and required service information.



3

REDUCED INVENTORY AND SERVICE COST

With G.E.'s continuing parts standardization program you can stock fewer parts. Save time and money in everyday service operations.

BUILD PROFITS WITH THESE FAST MOVING TV AND PHONOGRAPH PARTS

			
Transistor EA15X25	Spindle EA97X174	Knob ET43X299	Polarized Extension Cord ET90X32

These are four samples of G-E renewal parts, parts that are factory engineered, precision-fitted, and designed for long-lasting performance. Call your nearby General Electric distributor and ask him for Genuine G-E Renewal Parts.

GENERAL ELECTRIC



830-40C

Circle 70 on literature card

May, 1966/PF REPORTER 87



FREE Catalog and Literature Service

*Check "Index to Advertisers" for further information from these companies.

Please allow 60 to 90 days for delivery.

ANTENNAS & ACCESSORIES

90. **ALLIANCE** — Colorful 4-page brochure describing in detail all the features of Tenna-Rotors.
91. **AMPHENOL CORPORATION** — New 28-page catalog aids selection of RF connectors and coaxial cable. Specifications are detailed for nearly 1400 items.*
92. **ANTENNACRAFT** — Four-color catalog sheet about the new "Big-Shot-8" VHF-UHF-FM antenna designed for city and suburban use.*
93. **BLONDER-TONGUE** — New products catalog, featuring all channel UHF-VHF-FM amplifiers, couplers, converters, etc.
94. **FINNEY** — Form 20-349 describes the new Finco-axial color matching transformer kit.*
95. **GC ELECTRONICS** — Catalog FR-3-CM is a 12-page catalog describing color-magic antennas, other antennas and accessories.
96. **JFD** — New 1966 dealer catalog covering complete line of log-periodic outdoor antennas, indoor antennas, rotators, converters, amplifiers, masting, splitter-couplers/combiners, matching transformers, lightning arrestors, antenna mounts, and hardware.*
97. **PARKER METAL GOODS CO.** — Catalog sheet illustrating ratchet type chimney mount.
98. **WINEGARD** — 12-page brochure "Color Spectacular" featuring antenna products designed for color TV use.*
99. **ZENITH** — Information bulletin on antennas, rotors, batteries, tubes, power converters, record changers, picture tubes, wire, and cable.*

AUDIO & HI-FI

100. **ADMIRAL** — Folders describing line of equipment; includes black-and-white TV, color TV, radio, and stereo hi-fi.
101. **BENJAMIN** — Product literature on Miracord 40A, 40H and 50H automatic turntables and associated accessories. Product literature on stereo 200 and stereo 200/FM compact systems.
102. **CLEVELAND ELECTRONICS INC.** — 3 multi-color flyer sheets describing Babe reverberation kit, Cathedral-Sonic self-contained reverberation kit, and Cletron TV camera components.
103. **JENSEN** — Multicolored 24-page catalog No. 165-L featuring speakers and headphones. Also, 22-page catalog No. 6801 supplying phono-cartridge list and cross-reference.
104. **NUTONE** — 16-page full-color booklet illustrating built-in stereo music system and intercom radio systems. Includes specifications, installing ideas and prices.
105. **OAKTRON** — "The Blueprint to Better Sound," an 8-page catalog of loudspeakers and baffles giving detailed specifications and list prices.*
106. **OXFORD TRANSDUCER** — 4-page catalog describing three lines of automobile rear-seat speaker kits.
107. **PHONOLA** — Full-color 18½" x 12" brochure depicting full line of phonographs, tape recorders, and consoles.
108. **SWITCHCRAFT** — Bulletin 159 about two new high-powered miniature pre-amps.

COMMUNICATIONS

109. **ACTION! COMMUNICATIONS SYSTEMS** — Form 715 depicts the new Touch/Dial multi-station communications system.

110. **COMCO** — Complete communications systems brochures available on request.
111. **MOSLEY ELECTRONICS** — Catalog covering complete 1966 line of Citizens-band equipment.
112. **PEARCE-SIMPSON** — Specification brochure on 1BC 301 business-band two-way radio, Companion II, Director, Escort II, Guardian 23, and Sentry Citizens-band transceivers. "The Modern Approach to Business Communications" concerning land mobile radio service for businessman.

COMPONENTS

113. **BUSSMAN** — New 1966, 16-page car and truck fuse list. Shows proper fuse to use and where it is located. Covers foreign as well as domestic cars and trucks. Buss form AWC.*
114. **CORNELL-DUBILIER** — 96-page reference catalog about Twist-prong Electrolytic capacitors.*
115. **OAK** — Catalog and supplement describes Oak line of rotary and lever switches.*
116. **SONOTONE** — Spec sheet on 19T and 1ST stereo and mono cartridges.
117. **SPRAGUE** — Catalog K-508 is a large 64-page replacement manual cross-referencing electrolytic capacitors from manufacturers part number to Sprague number. Covers TV, tape recorders, radios, etc. Includes list prices.*
118. **TRIAD** — 12-page replacement guide on transformers. Manufacturer's number to Triad number.
119. **WORKMAN** — Form X-47 describes noninductive ceramic resistors used in color TV sets.*

SERVICE AIDS

120. **CASTLE** — How to get fast overhaul service on all makes and models of television tuners is described in leaflet. Shipping instructions, labels, and tags are also included.*
121. **CLEVELAND INSTITUTE OF ELECTRONICS** — New pocket-sized, plastic "Electronics Data Guide" of formulas and tables, including frequency and wavelength, db formulas and table, antenna lengths, and color code.*
122. **ELECTRONIC CHEMICAL** — Brochure of aerosol chemicals for controls, tuners, and tape heads.*
123. **G.C.** — New 300-page catalog FR 67 covers GC, Walsco, Audiotex, Telco, and Electrocraft brands of service aids and components.
124. **PRECISION TUNER** — Literature supplying information on complete low-cost repair and alignment service for any TV tuner.
125. **RAWN** — Instruction bulletin on how to make knobs in minutes with Plas-T-Pair.*
126. **WALDOM NYLON AND BUTYRATE HARDWARE** — 4-page brochure about Nylon and Butyrate hardware.
127. **YEATS** — The new "back-saving" appliance dolly Model 7 is featured in a four-page booklet describing featherweight aluminum construction.

SPECIAL EQUIPMENT

128. **AMPROBE INSTRUMENT** — Catalog sheet REC 1007 about the Direct-O-Log strip-chart recorder.
129. **PERMA-POWER** — New catalog LCG-680 describes Electro-Lift garage door opener.

130. **SAMPSON** — Flyer sheet about the new Waltham Micro-8 vest pocket size transistor radio.
131. **TERADO CORPORATION** — Flyer sheet describes Model 50-160 portable 115VAC supply.

TECHNICAL PUBLICATIONS

132. **CLEVELAND INSTITUTE OF ELECTRONICS** — Free illustrated brochure describing electronics slide rule and four-lesson instruction course and grading service.*
133. **HAYDEN** — New, 64-page catalog listing books published by the Hayden Book Company, Inc. and John F. Rider Publisher, Inc. for the electronics service technician, student, and hobbyist.
134. **HOWARD W. SAMS** — Literature describing popular and informative publications on radio and TV servicing, communications, audio, hi-fi, and industrial electronics, including special new 1966 catalog of technical books on every phase of electronics.*

TEST EQUIPMENT

135. **B & K** — New 1966 catalog featuring test equipment for color TV, auto radio, and transistor radio servicing, including tube testers designed for testing latest receiving tube types.*
136. **EICO** — 1966 short-form catalog is 48 pages long. Describes a complete line of test instruments, CB and ham equipment, hi-fi components, and miscellaneous electronic equipment.*
137. **HICKOK** — New flyer detailing selected items of service test equipment.
138. **JACKSON** — New catalog of "Service Engineered" test equipment.
139. **MERCURY** — All new test-equipment catalog featuring time saving "Service-Man" equipment.*
140. **SECO** — Catalog sheet No. 90065 describing Model 900 color-bar generator and Models 88, 98, and 107B tube testers.
141. **SENCORE** — Latest 4-color catalog plus other information on new developments in the Econoline series of test equipment.*
142. **SIMPSON** — Flyer giving specifications of Model 604 Multicorder for measuring and recording volts, amps, milliamps, and microamps.*
143. **TRIPLETT** — New test equipment catalog D-66-1 with full line of panel and portable instruments and accessories.*

TOOLS

144. **ARROW** — Flyer sheet illustrating three staple guns and showing uses.*
145. **ENTERPRISE DEVELOPMENT** — Time-saving techniques in brochure from Endeco demonstrate improved desoldering and resoldering techniques for speeding and simplifying operations on PC boards.
146. **VACO** — New 4-page catalog on Vaco's line of Professional Pliers and wrenches.*

TUBES & TRANSISTORS

147. **GE** — New 18-page "Semiconductor Almanac" for use in servicing radio, TV, and audio sets.
148. **RCA** — 6-page brochure illustrating the full line of dealer aids and promotional material about replacement color picture tubes.*

RCA's REPLACEMENT COLOR PICTURE TUBE

POINT-OF-PURCHASE PROGRAM FOR '66

...will help you reap the profits from the long-awaited "color boom"


Identify with RCA... because RCA is identified with COLOR! Get ready... now! Color TV picture tube replacement sales are expected to increase sharply during '66. This Illuminated Window Display (ID 1227) is only one of the many attractive pieces available to help you get your share of this growing business. Others include counter cards, window decals and streamers, mailers, consumer folders, and promotional giveaways... all designed to help you advertise your color TV servicing capability.

Contact your RCA Color Picture Tube Distributor today!

RCA Electronic Components and Devices, Harrison, N. J.




The Most Trusted Name in Electronics

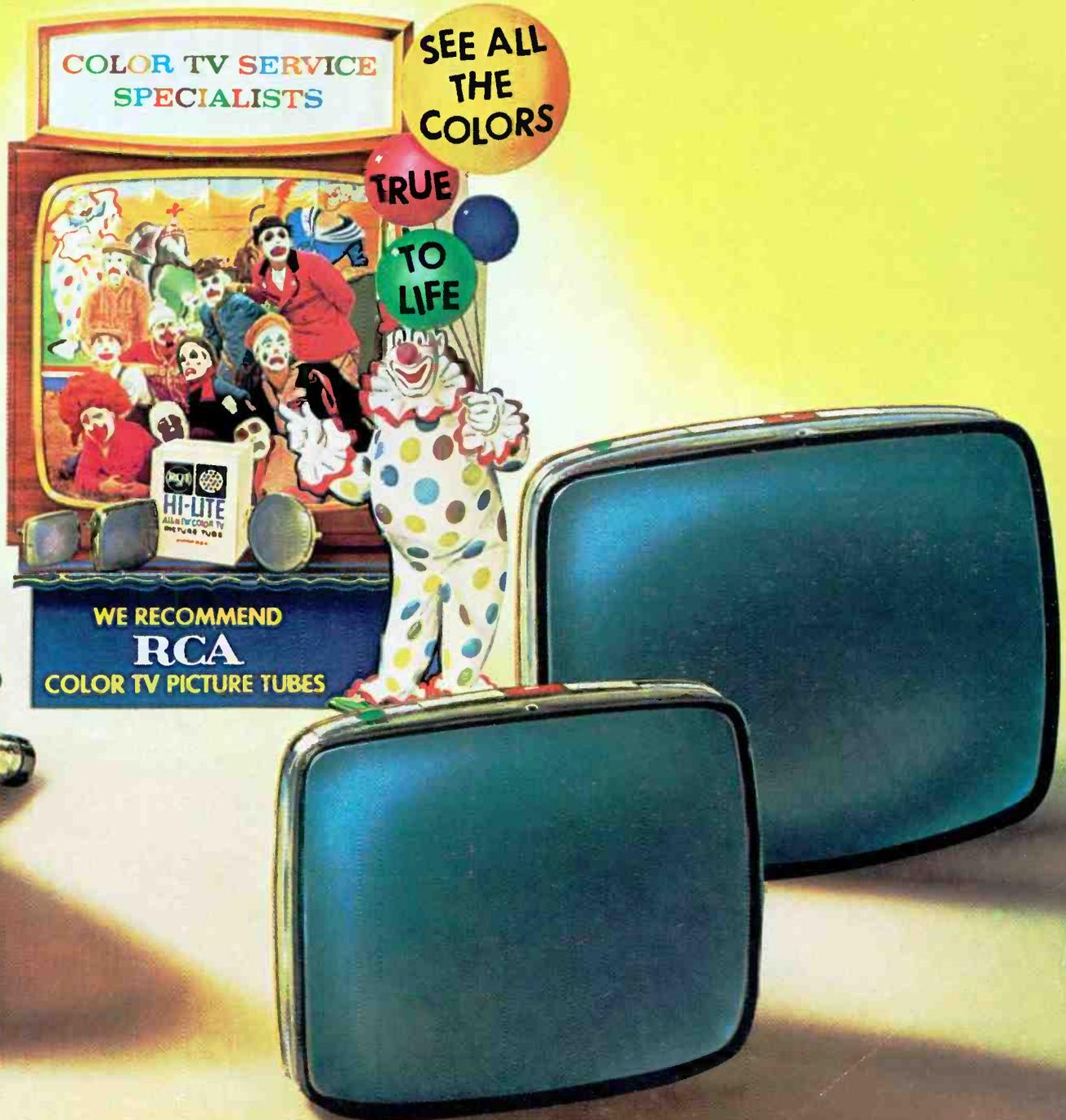




LOOK WHAT'S HATCHING IN **COLOR TV**

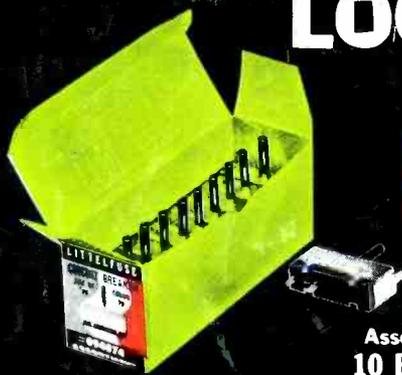

Assortment #094074
10 BULK BREAKERS



Assortment #094073
10 CARDED BREAKERS

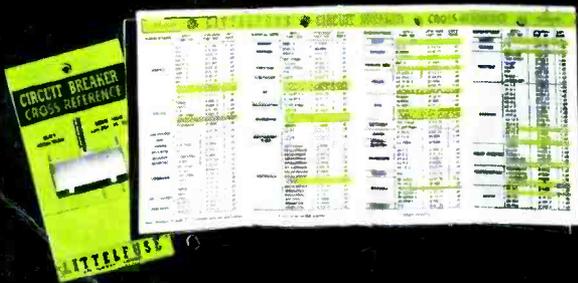

**A COMPLETE ASSORTMENT
OF CIRCUIT BREAKERS FOR
COLOR TV APPLICATIONS**

Ten breakers, seven ratings in one handy box for 100% replacement needs. Assortment available consisting of breakers on individual display cards or in bulk.

Included with each assortment: Pocket size cross-reference on color and black/white TV circuit breaker applications. Form No. CBCRP865H.

LITTELFUSE

DES PLAINES, ILLINOIS

Circle 71 on literature card