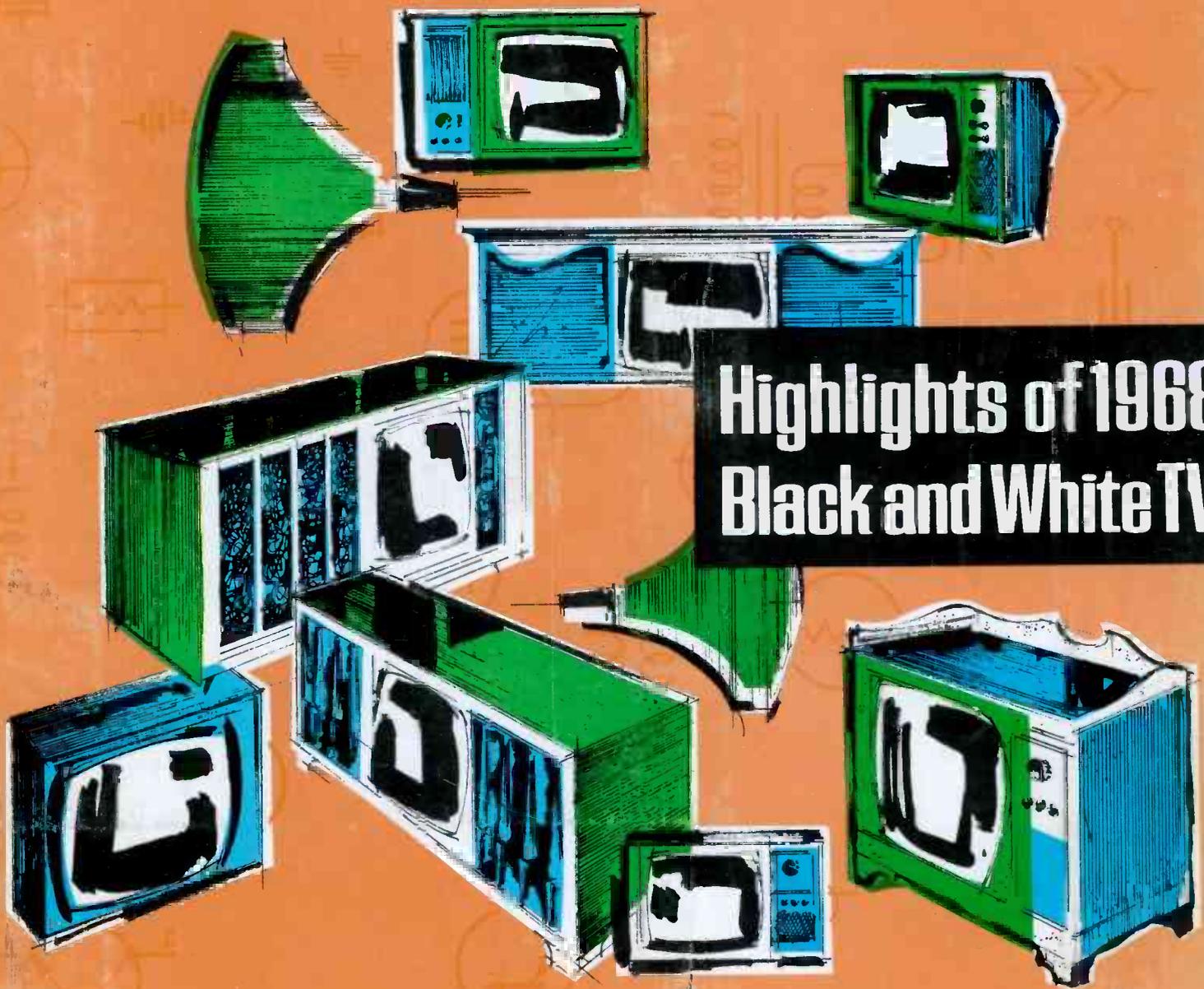


PF Reporter

PHOTOFACT


the magazine of electronic servicing



Highlights of 1968 Black and White TV

- Color TV Service Training
- Highlights of '68 TV Lines
- Repairing the Deluxe AM-FM Chassis
- Notes on Test Equipment
- The Troubleshooter

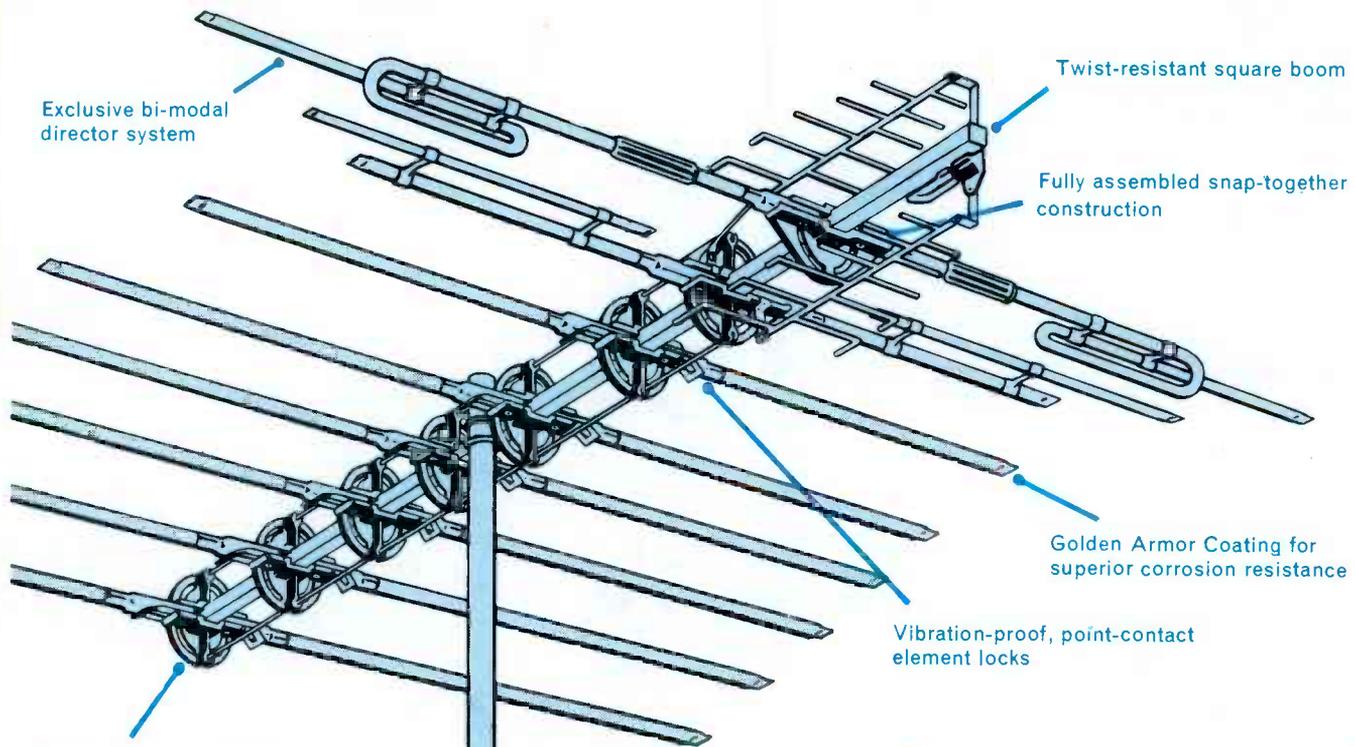SAVUEL SACHS
 2244 NORTH 10TH ST.
 PHILADELPHIA, PA. 19133



82-channel signal grabber

The Jerrold VUfinder® Antenna. The first 300-ohm UHF-VHF-FM antenna designed—from the ground up—for uncompromising color and black-and-white excellence across the entire TV spectrum. Models available for metropolitan to deepest fringe areas.

- Sharp directivity eliminates color ghosts
- Flat response (± 1 db per channel) for optimum color fidelity
- Exclusive bi-modal director system for extra gain

VUfinders are easy to put together, can't possibly fall apart. The quality that's built in stays in. Quickly convertible to 75-ohm Color-axial performance. VUfinders come in 5 models. Each is supplied with a UHF/VHF frequency splitter. And the list prices range from \$17.95 to \$79.95. There's no better performance per dollar than this—anywhere.

For the most efficient 300-ohm signal grabber in Jerrold's Spectrum '67, see your Jerrold Distributor *today* about the Jerrold VUfinder antenna.



Indoor antennas



Home pre-amplifiers



Distribution equipment



*Focusing on one thing...
better reception*


Circle 1 on literature card

PF Reporter[®]

PHOTOFACT

Tube Substitution Supplement

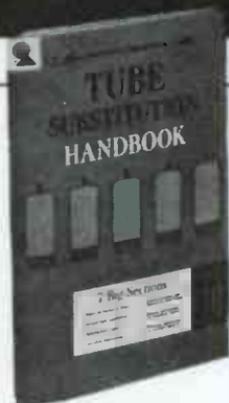This Supplement has been designed to provide you with the latest up-to-date information on new tubes. The format allows maximum use during a house call or at the bench.



REMOVE THIS
SUPPLEMENT FROM

PF Reporter[®]

and put it in
the back of your

**TUBE
SUBSTITUTION
HANDBOOK**

direct substitutes

Included are the older tubes that will substitute directly for the new tubes. This information supplements the sections in the Tube Substitution Handbook for American Receiving Tubes and Picture Tubes.

basing diagrams

The basing diagram for each new tube will help you in the servicing of new receivers when service literature is not available.

typical characteristics

The typical, or average, characteristics of each new tube can be of great help when troubleshooting new circuits.

easy reference

The direct substitution list will be cumulative each month. Thus, only the latest edition need be carried in the Tube Substitution Handbook.

Direct Substitutions

To Replace	Use	To Replace	Use
1BK2	1AX2 1S2A	4JH6	4BZ6
1BL2	*	5GH8A	5EA8 5GH8 5U8
2CN3A	*		
2EG4	*	6BY11	*
3BL2	3AT2 3BN2	6BW11	*
3BM2	3BN2	6CL3	6CJ3 6CK3 6DW4A 6DW4B
3BN2	3AT2 3BL2		
3BS2	3BS2A	6CM3	*
3BS2A	3BS2	6EJ4	*
3CN3A	3CN3	6JC6A	6HM6 6HT6 6JC6 6JD6
3JC6A	3HM6 3HT6 3JC6 3JD6		
4JC6A	4HM6 4HT6 4JC6 4JD6	6KT6	*
		6KV6	*
		6KY6	*

PF REPORTER October, 1967, Vol. 17, No. 10. PF REPORTER is published monthly by Howard W. Sams & Co., Inc., 4300 W. 62nd, Indianapolis, Indiana 46206. Second-class postage paid at Indianapolis, Indiana. 1, 2 & 3 year subscription prices; U.S.A., its possessions and Canada: \$5.00, \$8.00, \$10.00. Other countries: \$6.00, \$10.00, \$13.00. Current single issues 75¢ each; back issues \$1.00 each.

*To Replace**Use**To Replace**Use*

6LB6

*

11SP22

*

6LC6

*

11TP4

*

6LH6

*

12BQP4

12BKP4

6LJ6

*

12BUP4A

12BUP4

6ME8

*

12CBP4

*

6MF8

*

12CEP4

*

6MK8

*

12CNP4

12CFP4

7KY6

*

12CQP4

*

7KZ6

*

12CSP4

*

8GU7

*

12CTP4

*

9GH8A

9EA8

15KP22

*

9KX6

*

15LP22

*

9LA6

*

16CHP4A

16CHP4

12CL3

12CK3
12DW4A

16CSP22

*

12FQ7

*

17EQP4

*

17CL3

17CK3
17DW4A

19GBP4

19CZP4

19GJP4

19DAP4

17KV6

*

19GJP4A

19DQP4

22KM6

*

19GVP22

*

25CM3

*

19GWP22

*

29KQ6

*

19HAP4

*

30KD6

*

21FBP22A

*

34CM3

*

21FYP4

*

21GCP4

*

21GJP4

*

To Replace	To Replace	Use	Use
22JP22	*	23HUP4A	23HUP4
22KP22	*	23HWP4	*
23FLP4	*	23HWP4A	23HWP4
23GHP4	*	25TP4	*
23HBP4	*	25WP22	*
23HRP4	*	25XP22	*
23HUP4	23HUP4A	25YP22	*

*No replacement at present time. See future editions of Tube Substitution Handbook

General Specifications

High-Voltage Rectifier
Fil.—1.8V @ 0.9A
PIV—38KV @ 2.2ma


2CN3A



8MN

High-Voltage Rectifier
Fil.—3.0V @ 0.3A
PIV—30KV @ 1.7ma

3BM2

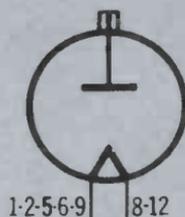

12HK

Suggested direct replacement: 3BN2

High-Voltage Rectifier
Fil.—3.15V @ 0.48A
PIV—38KV @ 2.2ma

3BS2



12EW

Suggested direct replacement: 3BS2A

High-Voltage Rectifier
 Fil.—3.15V @ 0.48A
 PIV—38KV @ 2.2ma

3BS2A




Suggested direct replacement: 3BS2

12EW

High-Voltage Rectifier
 Fil.—3.15V @ 0.48A
 PIV—38KV @ 2.2ma

3CN3A

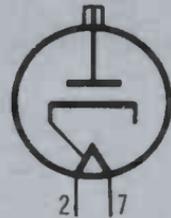


Suggested direct replacement: 3CN3

8MN

#1—Video Amplifier
 #2—General Purpose
 Fil.—6.3V @ 0.8A

	#1	#2
E_p	125	125V
E_{SG}	125	125V
R_K	56	56Ω
I_p	22	11ma
I_{SG}	4.8	3.8ma
G_m	8500	13,000 μmhos


6BW11

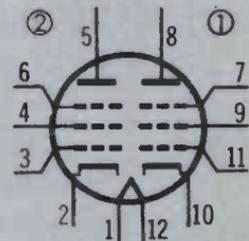

12HD

Protection—tension band
 Deflection—110°
 Filament—6.3V @ 0.45A (11 sec)
 Grid 2—50V

12BUP4A

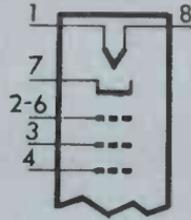


Suggested direct replacement: 12BUP4

8HR

Protection—None
 Deflection—90°
 Filament—6.3V @ 0.9A


15KP22

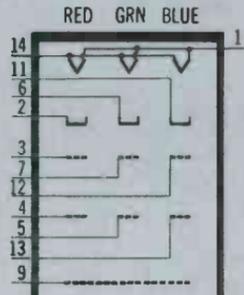

14BH

Protection—Bonded
 Deflection—90°
 Filament—6.3V @ 0.9A


15LP22

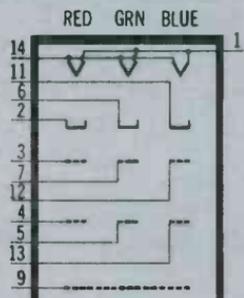

14BH

Protection—tension band
Deflection—114°
Filament—6.3V @ 0.45A (11 sec)
Grid 2—400V

19GJP4

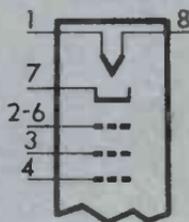


Suggested direct replacements: 19DQP4, 19DWP4,
19FCP4

8HR


Protection—tension band
Deflection—114°
Filament—6.3V @ .315A
Grid 2—50V

19HAP4

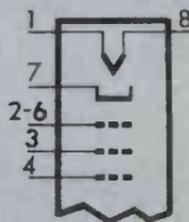

Protection—tension band
Deflection—94°
Filament—6.3V @ 0.45A (11 sec)
Grid 2—200V

23GHP4

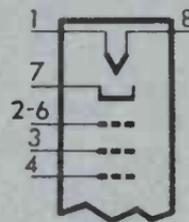

8HR

EICO Makes It Possible

You get 100% professional test equipment quality—and economy. EICO's uncompromising engineering-for-value makes it possible. Twenty-three years ago we started EICO to deliver "Laboratory Precision at Lowest Cost." Today, three million customers like us for it. Compare EICO products with *anybody's* at your local dealer. You'll see for yourself how you save up to 50% with EICO kits and wired equipment—and enjoy electronic excellence too!



- 1/2-volt Full-Scale DC Transistor Servicing Range. Accurate measurements down to 0.01 volts.
- Deluxe full-view 6" 200 microamp meter movement.
- Unique ease & speed by exclusive color coding of switches with meter scales.
- Dual purpose EICO exclusive AC/DC Uni-Probe.®
- Signal isolation floating ground.

NEW EICO 235 PROFESSIONAL VTVM

Feature-packed 6" professional VTVM brings you more in functional styling, convenience, and dependable performance for exacting measurements in solid state circuitry.

8 DC Ranges: 0-0.5-1.5-5-15-50-150-500-1500 (to 30,000 volts with optional high voltage probe). 7 AC Peak-to-Peak Ranges: 0-4-14-42-140-1400-4200. 7 AC RMS Ranges: 0-1.5-5-15-50-150-500-1500. 7 Resistance Ranges Covering: 0.2Ω to 1000MΩ. Frequency Response: 3 cps to 3Mc ±1db (up to 250Mc with optional PRF probe). Input Resistance: DC 11MΩ; AC 1M shunted by 60mmf. 1% precision multiplier resistors. 3% accuracy on AC and DC scales.

Kit 49.95
Wired \$69.95

Terrific time-saver! Only 1 probe performs all functions — a half-turn of probe-tip selects DC or AC-OHMS!

TRUVOHM PROFESSIONAL PORTABLE MULTIMETERS by EICO.

The industry's greatest V-O-M values. Designed & manufactured to Eico's high standards of professionalism. Each complete with batteries & test leads. Backed 100% by famous EICO warranty.

100,000 Ohms/Volt Model 100A4, \$34.95
optional carrying case \$5.95
The best buy in a bench-size multimeter. With AC sensitivity 12,500Ω/V, combines minimal circuit loading with wide-ranging functional utility. Double-jewelled ±2% D'Arsonval meter movement; full-view 4-inch mirror-back two-color scale eliminates reading parallax; matched pair of silicon diodes prevents accidental overload of meter movement. High-impact, custom-molded case protects against shock.



30,000 Ohms/Volts Model 30A4 \$19.95



30,000 Ohms/Volts Model 30A3 \$15.95



20,000 Ohms/Volts Model 20A3 \$12.95



4,000 Ohms/Volts Model 4A3, \$8.95



1,000 Ohms/Volts Model 1A1, \$5.95



Model 232 Peak-to-Peak VTVM. A must for color or B&W TV and industrial use. 7 non-skip ranges on all 4 functions. With exclusive Uni-Probe.® \$29.95 kit, \$49.95 wired.



New Model 567 VOM Kit \$34.95
Wired \$44.95

- 20,000 ohms-per-volt sensitivity
- 0.25 volt full-scale range
- Silicon diode meter protection circuit

DCV: 0-0.25, 2.5, 10, 50, 250, 1000, 5000V. ACV: 0-2.5, 10, 50, 250, 1000, 5000V. DCI: 0-50 uA, 1 mA, 10 mA, 100 mA, 500 mA, 10 amps. —12 to +55 db in 5 ranges. RES: 0-2KΩ, 200KΩ, 2MΩ.



laboratory precision at lowest cost.



and amp. \$109.95 kit, \$149.95 wired.

Model 460 Wideband Direct-Coupled 5" Oscilloscope. DC-4.5mc for color and B&W TV service and lab use. Push-pull DC vertical amp., bal. or unbal. input. Automatic sync limiter



Model 369 Sweep and Post-Injection Marker Generator. For easiest, fastest visual alignment of color B & W TV and FM RF and IF circuits. Five sweep ranges from 3-22C Mc/S. Four marker ranges from 2-225 Mc/S. Crystal marker oscillator. Post injection of markers. **Kit \$99.95. Wired \$149.95**

FREE 1968 CATALOG

PF 10

EICO Electronic Instrument Co., Inc.
131-01 39th Ave., Flushing, N.Y. 11352

Send me FREE catalog describing the full EICO line of 200 best buys, and name of nearest dealer.

Name _____
Address _____
City _____
State _____ Zip _____

PUBLISHER
HOWARD W. SAMS

GENERAL MANAGER
DONALD W. BRADLEY

EDITOR
WILLIAM E. BURKE

MANAGING EDITOR
JAMES M. MOORE

ASSOCIATE EDITORS CONSULTING EDITORS
Thomas T. Jones Joe A. Groves
J. W. Phipps C. P. Oliphant
Carl F. Moeller George B. Mann

PRODUCTION MANAGER RESEARCH LIBRARIAN
Esther M. Rainey Mrs. Bonny Howland

CIRCULATION MANAGER
Pat Osborne

ART DIRECTORS
Louis J. Bos, Jr. & Robert W. Reed

PHOTOGRAPHY
Paul Cornelius, Jr.

ADVERTISING SALES OFFICES

Midwestern Regional Sales Manager

ROY HENRY

Howard W. Sams & Co., Inc., 4300 W. 62nd St.
Indianapolis, Ind., 46206 • 317-291-3100

Eastern Regional Sales Manager

ALFRED A. MENEGUS

Howard W. Sams & Co., Inc., 3 W. 57th St.
New York, New York, 10019 • 212-688-6350

Southwestern Regional Sales Manager

MARTIN TAYLOR

P. O. Box 22025, Houston, Texas 77027
713-621-0000

western/Los Angeles

G. R. HOLTZ

The Maurice A. Kimball Co., Inc.
2008 W. Carson St., Suites 203-204
Torrance, Calif., 90501 • 213-320-2204

western/San Francisco

The Maurice A. Kimball Co., Inc.

580 Market St., Room 400
San Francisco, Calif., 94104 • 415-392-3365

Address all correspondence to PF REPORTER
4300 W. 62nd Street, Indianapolis, Indiana 46206



Copyright © 1967 by Howard W. Sams & Co., Inc. PF REPORTER is a trademark of Howard W. Sams & Co., Inc. No part of PF REPORTER may be reproduced without written permission. No patent liability is assumed with respect to use of information herein. Acceptance of advertising does not in any manner signify the products, policies and services so advertised have been approved, endorsed or recommended by this magazine.

Subscription Prices: 1 year—\$5.00, 2 years—\$8.00, 3 years—\$10.00, in the U. S. A., its possessions and Canada.

All other foreign countries: 1 year—\$6.00, 2 years—\$10.00, 3 years—\$13.00. Single copy 75¢; back copies \$1.

Indexed in Lectrodex. Printed by the Waldemar Press Div. of Howard W. Sams & Co., Inc.

PF Reporter®

PHOTOFACT

the magazine of electronic servicing

VOLUME 17, NO. 10


OCTOBER, 1967

CONTENTS

Tube Substitution Supplement		9
Highlights of 1968 B-W TV	<i>J. W. Phipps</i>	4
<small>Details of the new circuits and features found in the '68 models.</small>		
The Electronic Scanner		13
Color TV Service Training—Part III		16
Notes on Test Equipment	<i>T. T. Jones</i>	28
<small>Lab report on Amphenol's Model 870 FET Meter.</small>		
Repairing the Deluxe AM-FM Chassis	<i>David Held</i>	32
<small>Tips and techniques for quicker servicing —with case histories.</small>		
R-C Circuits		38
<small>How to compute the time constant in R-C coupling circuits.</small>		
Book Review		41
The Troubleshooter		45
Protect Your Business From These Credit Abuses	<i>Ernest W. Fair</i>	52
<small>How to keep accounts receivable in the assets column of the ledger.</small>		
Color Countermeasures		61
Product Report		63
Letters to the Editor		69
PHOTOFACT BULLETIN		70
Free Catalog and Literature Service		72
Monthly Index on Free Literature Card		

ABOUT THE COVER

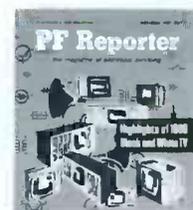This month's cover illustrates abstractly the many new monochrome TV receivers in the '68 lines. The symbols in the background point out that many of the new models are either hybrid or completely solid-state. For more information on the new sets see the article starting on page 4.



SOME SHOP OWNERS DO MORE BUSINESS THAN OTHERS BY DOING BASIC THINGS LIKE THESE:



1 Reading what's new in leading technical magazines.



2 Keeping their trucks ready to roll at a moment's notice.



3 Arranging to have their phones answered promptly.



4 Making sure their caddies are organized and properly stocked.



5 Keeping accurate track of their time on each job.



6 Smiling . . . often . . . both on and off the job.



DIFILM® ORANGE DROP® . . .
The world's finest radial-lead capacitor



DIFILM® BLACK BEAUTY® . . .
Ultimate in molded tubulars

7 INSTALLING SPRAGUE DIFILM® CAPACITORS

These two great Sprague capacitors are expressly made for men who are in the TV service business to do business . . . as it should be done. Both feature the ultimate in tubular capacitor construction to keep you out of call-back trouble:

- Dual dielectric . . . combine best properties of both polyester film and special capacitor tissue.
- Impregnated with HCX® to provide rock-hard capacitor section.
- Because impregnant is solid, there's no oil to leak, no wax to drip.
- Designed for 105° C (220° F) operation without voltage derating.

For complete listings, ask your Sprague distributor for Catalog C-617, or write to Sprague Products Company, 105 Marshall Street, North Adams, Massachusetts 01247.

DIFILM® ORANGE DROP® Dipped Tubular Capacitors

A "must" for applications where only radial-lead capacitors will fit. Perfect replacements for dipped capacitors used in most leading TV sets. No other dipped tubular capacitors can match them. Double-dipped in rugged epoxy resin for positive protection against extreme heat and humidity.

DIFILM® BLACK BEAUTY® Molded Tubular Capacitors


World's most humidity-resistant molded capacitors. Feature tough, protective outer case of non-flammable molded phenolic . . . which cannot be damaged in handling or installation. Will withstand the hottest temperatures of any radio or TV set . . . even in the hottest, most humid climates.

**DON'T FORGET TO ASK YOUR CUSTOMERS
"WHAT ELSE NEEDS FIXING?"**

Circle 3 on literature card



HIGHLIGHTS OF 1968 TV LINES

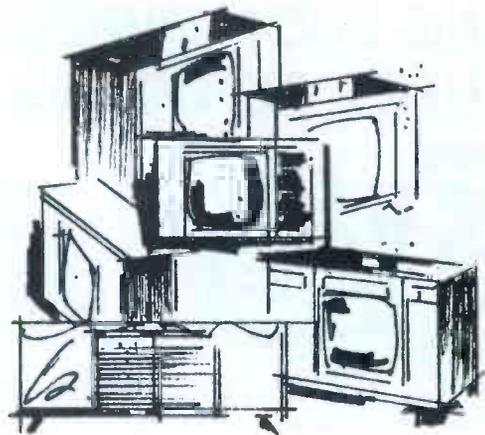

A preview of the black-and-white models offered for the coming year, including an analysis of new features and circuitry.

by J. W. Phipps

ADMIRAL

A wide variety of screen sizes and a new hybrid chassis are featured in this manufacturer's black-and-white lineup for '68. Although the majority of models are new, nearly all use carryover chassis.

Leading the lineup are two new 22" table models employing the previously introduced 3G5 chassis. Also offered is a 22" holdover table model using the 7G7 chassis. Eight consoles are included in the new line; four are new models using the 3G5 chassis, while the other four are carryovers that use chassis 7G7.

The portable grouping offers screen sizes ranging from 9" to 20". Two Playmate 9" models are available; one is a new deluxe version and the other is last year's introduction. Both use the recent MG2-1 chassis. The Playmate series has also been extended to the 12" models with the addition of four new portables using the familiar H1-1A and

H1-1A chassis. All four come with a sun shield (Fig. 1) that snaps on the front of the cabinet to provide improved contrast outdoors, or in brightly illuminated rooms.

Three new 14" models are also included in the extensive portable grouping. Each uses Chassis 1H2-1A. Two of the three 16" models are equipped with the new "Sun Shield." All use the H3-1A chassis and come equipped with "roll-about" stands.

Roll-about stands also come with all 18" and 20" portable models. Eight 18" models are available; five use the H4-1A chassis and the other three use a version of the new hybrid H5 chassis. The three 20" portables also use a version of this new chassis. One 20" set, the Jubilee (Model P2037C), is shown in Fig. 2.

The new H5 hybrid chassis uses five tubes (plus picture tube) and thirteen transistors. The tubes include the following: a double pentode 24BF11 used in the sound detector and sound output stages, a triode-pentode 24JZ8 employed in the vertical oscillator and vertical output circuits, and a twin diode-pentode 11LT8 serving the horizontal AFC and horizontal oscillator. Rounding out the tube complement are a diode-pentode 53HK7 functioning in the horizontal output and damper circuits and a 1AY2 high voltage rectifier. A 19HAP4 or 21GTP4 picture tube is used with the H5 chassis.

Three transistor video IF stages are included in the H5 design, along with two transistorized stages of video amplification. Sound is taken off the collector of the 1st video amplifier and fed to a PNP transistor sound IF circuit, which in turn feeds a conventional tube-type quadrature detector.

A forward, keyed AGC system (Fig. 3) is employed in the H5 chassis. The term "forward" describes the biasing effect the AGC voltage has on the transistors to which it is fed. With the exception of voltage polarities and values, Q1 operates like a tube-type keyed AGC stage. A negative-going video signal from the emitter circuit of the 1st video amplifier is applied to the base of Q1, while a horizontal pulse is fed through C1 to the collector. The simultaneous application of both signals (during horizontal retrace) causes Q1 to conduct, charging C1. The charge on C1 is added to an existing 3.3-volt charge on C2, producing approximately 8 volts of



Fig. 1. Sun shield used on Admiral's Playmate portable series.

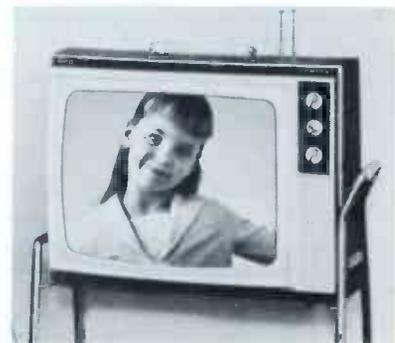


Fig. 2. Admiral's 20" Jubilee model.



\$975

EFFECTIVE 8/1/67

GUARANTEED

Nine-seventy-five buys you a complete tuner overhaul—including parts (except tubes or transistors)—and absolutely no hidden charges. All makes, color or black and white. UV combos only \$15.

Guaranteed means a full 12-month warranty against defective workmanship and parts failure due to normal usage. That's 9 months to a year better than others. And it's backed up by the only tuner repair service authorized and supervised by the world's largest tuner manufacturer—Sarkes Tarzian, Inc.

Four conveniently located service centers assure speedy in-and-out service. All tuners thoroughly cleaned, inside and out . . . needed repairs made . . . all channels aligned to factory specs, then rushed back to you. They look—and perform—like new.

Prefer a replacement? Sarkes Tarzian universal replacements are only \$10.45, customized replacements \$18.25. Shipped same day order received. Order custom tuners by TV make, chassis, and model number. Order universal replacement by part number:

Part #	Intermediata Frequency	AF Amp Tube	Osc. Mixer Tube	Heater
MFT-1	41.25 mc Sound 45.75 mc Video	6GK5	6LJ8	Parallel 6.3V
MFT-2	41.25 mc Sound 45.75 mc Video	3GK5	5LJ8	Series 450 MA
MFT-3	41.25 mc Sound 45.75 mc Video	2GK5	5CG8	Series 600 MA

Genuine Sarkes Tarzian universal replacement tuners with Memory Fine Tuning—UHF Plug In for 82-channel sets—Pre-set line tuning—13-position detent—HI gain—Lo noise—Universal mounting

FOR FASTEST SERVICE, SEND FAULTY TUNER WITH TV MAKE, CHASSIS, AND MODEL NUMBER, TO TUNER SERVICE CENTER NEAREST YOU



TUNER SERVICE CORPORATION FACTORY-SUPERVISED TUNER SERVICE

MIDWEST817 N. PENNSYLVANIA ST., Indianapolis, IndianaTEL: 317-632-3493
 EAST547-49 TONNELE AVE., Jersey City, New JerseyTEL: 201-792-3730
 SOUTH-EAST . . .938 GORDON ST., S. W., Atlanta, GeorgiaTEL: 404-758-2232
 WESTSARKES TARZIAN, Inc. TUNER SERVICE DIVISION
 10654 MAGNOLIA BLVD. North Hollywood, CaliforniaTEL: 213-769-2720

Circle 4 on literature card

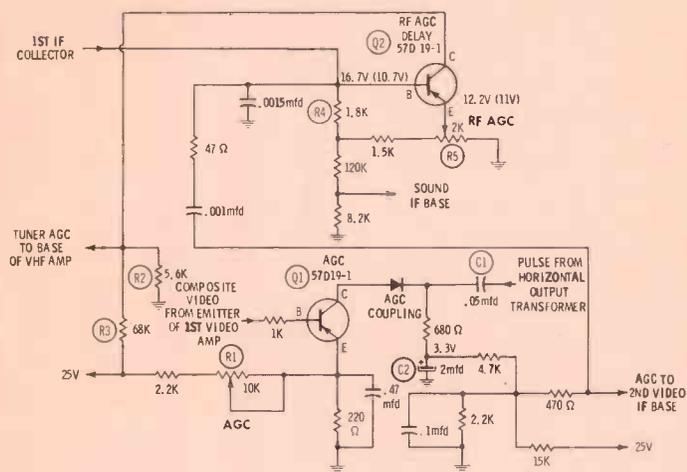


Fig. 3. Forward AGC system employed in Admiral's new H5 hybrid chassis.

positive AGC voltage. (The actual amount of AGC voltage produced is dependent on the level of the video signal applied to the base of Q1 and the setting of R1, the overall AGC control.)

The positive AGC voltage is then applied as forward bias to the base of Q4, the 2nd video IF (Fig. 4). Current through Q4 increases and, in turn, develops a larger voltage drop across R6. Since R6 is in series with Q4, the increased voltage drop across it detracts from the emitter-to-collector voltage of the transistor, thus decreasing the gain of the stage.

The 1st video IF also feels the effects of the forward AGC voltage. An increase in the voltage drop of R6 produces a more positive voltage at its ungrounded end. This increased positive voltage is applied to the base of Q3, increasing the forward bias on this stage and producing a reduction in gain in the same

manner as was described for the 2nd video IF.

To prevent reduced gain in the tuner during the reception of relatively weak signals, the AGC applied to the VHF amplifier is delayed by Q2 (Fig. 3). With low-level IF signals, Q2 is biased to cut-off. R5, the RF AGC control, determines the level of signal required to bring Q2 into conduction. When a high-level signal is received, the added voltage drop across R4 forward biases Q2 into conduction, which raises the voltage at the high side of R2 and adds to the forward bias applied to the VHF amplifier transistor. Increased forward bias reduces the gain of this stage exactly the way it does for the 1st and 2nd video IF amplifiers.

Other features of the H5 chassis include "Instant Play" and spot elimination circuits. Both are shown in Fig. 5. With the on-off switch in

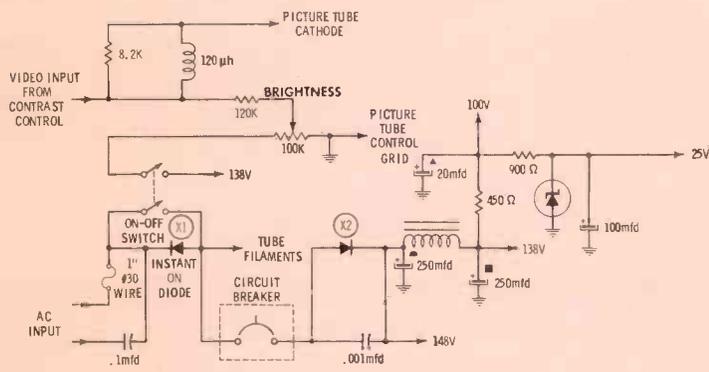


Fig. 5. Low-voltage power supply used in H5 chassis.

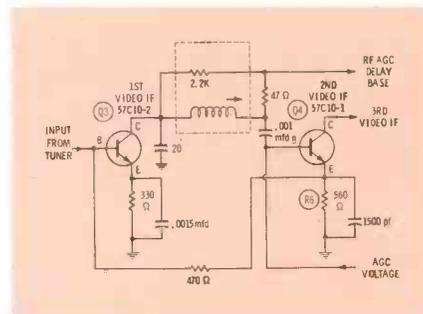


Fig. 4. Positive AGC voltage applied to base forward biases Q4.

the off position (as shown in Fig. 5), X1 provides all tube filaments with half-wave current instead of the normal full-wave current. No B+ is developed in the off position because X1 and X2 are back-to-back. The spot elimination circuit is ganged to the on-off switch and in the off position, removes B+ from the brightness control, causing the picture tube to draw increased current, thereby quickly discharging the aquadag coating and eliminating the spot on the screen.

Also shown in Fig. 5 is the half-wave low-voltage power supply. Four values of B+ are provided. The 25-volt source is regulated by a Zener diode and used in the transistor circuits.

ANDREA

An 18" and a 22" table model make up Andrea's b-w line for the coming year. Both models use the same transformer powered chassis that was introduced in last year's models. The 18" Courier model is shown in Fig. 6.

The big news this year from Andrea concerns the new 5-year consumer guarantee offered on all of their television chassis. The 5-year guarantee covers all parts except the picture and receiving tubes, which are covered by a separate 1-year guarantee.



Fig. 6. Andrea's 18" Courier model.

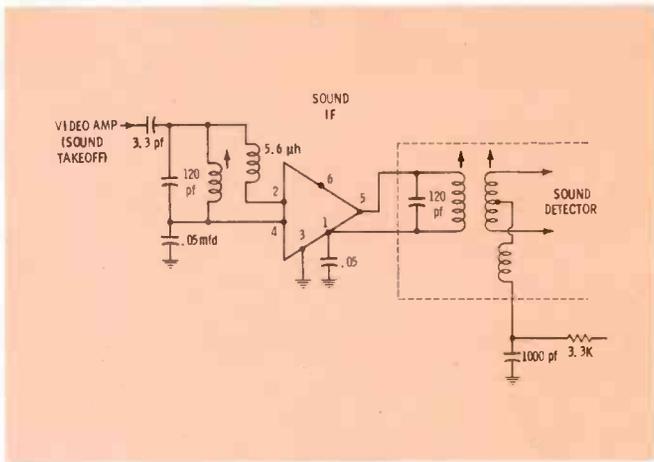


Fig. 10. Packard Bell's 88-21 chassis uses integrated circuit.

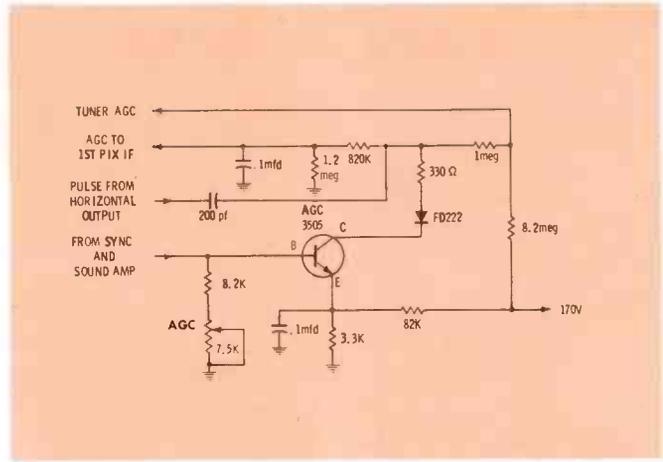


Fig. 12. Transistor AGC circuit used in RCA's KCS158.

the 18" receivers are equipped with a "quick-on" circuit, two have clock timers that provide automatic cut-off of the set after a selected period of operation, and two use Emerson's new VHF tuner featuring "Perm-Lok" fine tuning.

A 19" screen is available on two portable models. The 19P76 is shown in Fig. 9. Both use 20ADP4 picture tubes and chassis that are identical to the 120856, except for slight modifications of the CRT circuits. Both 19" models are equipped with the "quick-on" and clock-timer circuits, as well as the new "Perm-Lok" tuner.

Completing Emerson's '68 line are five 22" models. The chassis used in all five models are also identical to the 120856 chassis, except of course, for the CRT (a 23HWP4). Features common to all 22" models are "quick-on" and "Perm-Lok" fine tuning.

PACKARD BELL

Fourteen models with screen sizes ranging from 8" to 22" are available in this manufacturer's new b-w line. Heading up the small-



Fig. 11. Panasonic's 8" Model TR-238B.

screen portable sets are two 8" AC/DC models sharing the same solid-state chassis. Included in the chassis design are three stages of video IF, two video amplifier stages, a noise canceller circuit, and tripler-type high-voltage supply feeding the 9XP4 picture tube. A full-wave bridge rectifier is used for AC operation, together with an active power filter circuit which also serves during DC operation.

Tube-type chassis are used in the two 12" and two 15" AC-only models. Both chassis designs employ series filaments and a transformerless half-wave low-voltage supply. The only major difference in the chassis are the CRT's; the 12" models use a 12CUP4, while the 15" models use a 16CVP4.

Two new models and one carry-over are offered in the 18" portable grouping. Both new models use the transformer-powered tube-type 88-21 chassis. An integrated circuit, shown in Fig. 10, is featured in the sound IF stage of this chassis.

An 18" table model and two 22" consoles complete this manufacturer's '68 line. All three models use the 88-21 chassis.

PANASONIC

Three new models are included in Panasonic's '68 offerings. Model TR-205, the "Starstream", is a 5" solid-state AC/DC portable equipped with a new "dark-tint" screen. Three video IF stages and two video amplifier stages are used along with a noise canceller circuit, sync separator, and sync amplifier. Also used are three stages of audio amplification fed by a ratio sound detector and a single-stage sound IF. The

deflection circuits use drivers between the oscillator and output stages. A bridge-type rectifier supplies power for AC operation. For DC (battery) operation, the input is fed directly to an active power filter circuit.

Models TR-238B (Valley View) and TR-228D (Georgetown) use the same basic circuitry as the TR-205 described previously. The major electrical difference in the three designs involves the CRT sizes and the accessory circuits. Both the TR-238B (shown in Fig. 11) and TR-228D employ 9XP4 picture tubes and are therefore categorized as 8" portables. The TR-238B also employs a charging circuit for its "built-in" cartridge-type battery. An added feature of the TR-228D is an automatic timer which allows up to two hours of operation before automatically turning the set off. One other difference involves the high-voltage circuits; the 5" TR-205 uses a voltage tripler arrangement consisting of three semiconductor diodes, whereas the two 8" chassis use a 1X2B tube-type high-voltage rectifier circuit. Both the TR-238B and TR-228D are equipped with "dark-tint" screens.

Other solid-state models featured in Panasonic's new line are: An 8" AC/DC portable using a chassis similar to TR-205; one 8" AC/DC portable and one 8" AC/DC table model equipped with AM/FM radios; one 8" AC/DC table model with clock and timer; and one 9" AC/DC portable.

Tube-type and hybrid AC portables round out this manufacturer's line. Included are three 12" and one 15" all-tube receiver. The two hybrids offered have 18" screens.

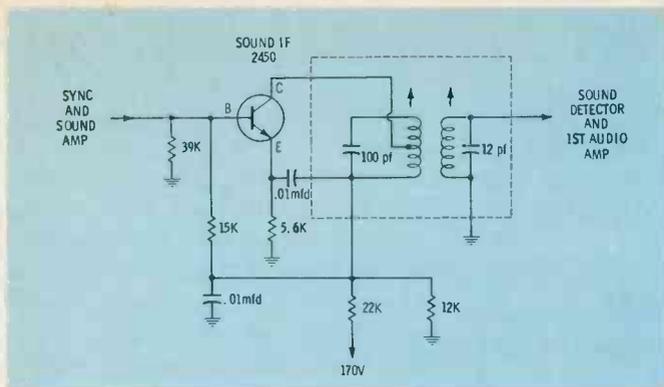


Fig. 13. Sound IF stage of Chassis KCS158 is solid-state.

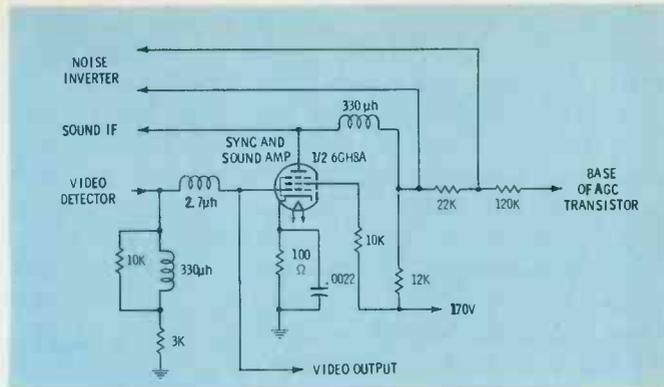


Fig. 14. Sync and sound amplifier employed in KCS158 and KCS159 chassis.

PHILCO

A variety of tube, hybrid, and all-transistor chassis are utilized in Philco's 37-model b-w "R" line for the coming year. A total of 13 chassis are used, including 7 carryovers and 6 recent designs. Screen sizes range from 8" to 22".

Offered in the 8" size is one transistorized AC/DC portable with a built-in battery charger. Three 12" models are included in the new line; all use the tube-type 17C21 carryover chassis. Three 16" portables also use carryover tube-type chassis (17H22 and 16H22).

Seven tube-type and three compact hybrid models comprise the 18" size group. Carryover 17J27 and 17J25 chassis are used in six of the tube-type 18" receivers. One hybrid 18" uses the previously introduced 17JT41 chassis, while the other two 18" hybrid receivers employ a newer version of the same chassis (18JT41). One 18" model features Philco's "Midnite Mask" black glass screen.

Two 19" compact models are available. One employs the new 18J32 chassis equipped with a 20RP4 picture tube. A remote control unit utilizing an integrated circuit is used with the chassis powering the other 19" receiver. This chassis is also equipped with the 20RP4 picture tube.

Chassis 18LT43, a transformer-powered hybrid chassis similar to last year's 17LT43, is used in two 20" compact models. A 21FYP4 picture tube is used in both models.

Three 22" table models and eight 22" consoles employ Chassis 18N35, which is nearly identical to the previously introduced 17N35 chassis except for a different VHF tuner

and minor circuit changes. Completing the "R" line are five 22" consoles powered by Chassis 18NT45, a newer version of the hybrid 17NT45 introduced last year. The UHF and VHF tuners employed with this chassis are solid state.

RCA

The 23 black-and-white models offered for 1968 by this manufacturer are designed around twelve chassis. Eight are continuing chassis employed in the 1967 line, two are recently introduced chassis, and the remaining two are new chassis.

Continuing chassis are the KCS-152, a tube-type vertical chassis used in one 15" model; KCS155, an autotransformer-powered vertical tube-type chassis employed in an 18" model; KCS156, a transformer-powered horizontal chassis used in another 18" model; and KCS161, a transformerless, vertically mounted chassis serving in one 20" receiver. Other continuing chassis are the transformer-powered KCS163, a horizontally mounted chassis used in one 18" set; KCS159, a horizontally mounted transformer-type chassis employed in three 22" consoles and one 22" table model; and KCS160, an autotransformer-powered, vertical chassis utilized in two 18" and one 19" model. Rounding out the continuing chassis list is the KCS-164, a chassis similar to KCS160. Two 18" and one 20" receiver use this chassis.

The four small-screen portables offered in RCA's '68 b-w line use the two recently introduced chassis. A completely solid-state chassis, the KCS157, functions in two personal 8" models, aptly named "Minikin Jr."

The other recently introduced

chassis, KCS165, is a compact tube-type employed in two 11" receivers. The design of this series-filament chassis includes two stages of video IF, a single video output stage, and a transformerless, half-wave, low-voltage supply. Two twelve-pin duodecar-type tubes are included in the complement of eleven tubes and four solid-state diodes. One is a 33GY7 diode-beam power pentode serving the horizontal output and damper stages. The other twelve-pin type is a 17BF11 double pentode used in the quadrature sound detector and audio output circuits. A 12CNP4 or 310AUB4 bonded-faceplate picture tube is used in this chassis.

The new KCS158 chassis (used in two 19" models) is electrically similar to the KCS159 mentioned previously, while the actual physical layout closely resembles KCS164. Similarities to the KCS159 include a transistor AGC circuit (Fig. 12) and a transistor sound IF stage (Fig. 13). In addition, both the KCS158 and KCS159 employ a separate sync and sound amplifier, shown in Fig. 14.

One major difference between the KCS158 and KCS159 involves the low-voltage power supply. The continuing KCS159 uses a conventional power transformer in a full-wave

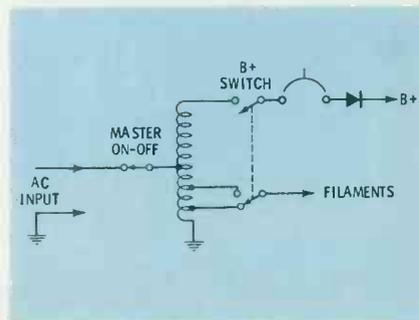


Fig. 15. KCS158 "Instant-Pic" circuit.

configuration, along with parallel filaments. The low-voltage supply of the KCS158 employs an auto-transformer, half-wave rectifier, and series filaments. Also, the KCS158 is equipped with an "Instant Pic" circuit, shown in Fig. 15. Two on-off switches are provided. One is labeled "Master on-off", and in the off position, completely removes power from the autotransformer. The other on-off switch serves two functions: In the off position it disables the B+ circuit and provides half of the normal voltage to the filaments, thereby keeping them warm and ready for instant use. In the on position it re-establishes the B+ circuit and switches the filaments to a tap that supplies full voltage to them. Either a 19DQP4 or 20TP4 picture tube is used with the KCS-158 chassis.

The other new chassis found in RCA's '68 line is the KCS168, used in two 15" receivers. One of these models, equipped with a clip-on dark filter, is shown in Fig. 16. The physical and electrical characteristics of this chassis are similar to those of the KCS165 described previously. However, the KCS168 uses a 16CHP4, whereas the KCS165 is equipped with a much smaller 12CNP4. This difference in CRT size necessitates slight differences in the deflection stages and CRT blanking and supply circuits. A twelve-pin 38HE7 diode-pentode is used in the horizontal output and damper circuits of the KCS168 in place of the twelve-pin 33GY7 diode-pentode employed in the same circuits of the KCS165. The only other tube difference is found in the AGC and video output stages; the KCS168 uses an 8JV8 triode-pentode in these stages, while the KCS165 uses an 11KV8. Other dif-



Fig. 16. RCA's Model AJ-058 is equipped with a clip-on dark filter.

ferences involve the vertical yoke windings; those employed in the KCS168 are supplied from a tap on the primary of the vertical output transformer, whereas the yoke windings of the KCS165 received their supply from the secondary of the same transformer.

SYLVANIA

Eight chassis are found in this manufacturer's '68 models. Three (A02, A06, A07) are solid-state carryover designs used in one 12" personal portable and two 18" "roll-about" portables. Other 18" roll-about portable models use either chassis B05 or B06 (tube-type carryovers).

Two new 19" models (the MY71K is shown in Fig. 17) use the recently introduced B09 chassis. This is a transformerless, series-filament chassis employing a full-wave voltage doubler in the power supply. Two transistors (in addition to the one in the UHF tuner) are included in the main chassis complement of the B09. Both are used in a two-stage noise suppression circuit consisting of a noise gate circuit in series with the cathode of the sync separator and a noise amplifier connected between the output of the video detector and the base of the noise gate. DC picture restoration and horizontal blanking are also included in this chassis, as well as all other chassis in Sylvania's new line. The CRT used in the B09 is a 110° 20ZP4.

Six models are offered in the 22" size group; two are table models and four are consoles. Powering these 22" receivers is Chassis B04, a tube-type carryover. One other chassis, the B07, is included in Sylvania's new line; however, no information concerning this new chassis is available at the present time.

WESTINGHOUSE

A total of 32 models comprise Westinghouse's '68 b-w line. Leading off the new line is the "Jet Set" grouping which offers eight models equipped with a no-glare black-tinted glass over the screen. One of the two 12" receivers included in this group is a combination TV/phonograph/clock-radio. Called the "Mini-Combo", the unit measures

15" high by 19" wide by 11" deep. The tube-type TV chassis (V2490-9) used in this model is a carryover and like all of this manufacturer's tube-type b-w chassis, is equipped with an instant-on circuit.

Other models and screen sizes available in the "Jet Set" grouping include three 18", two 20", and one 8" receiver. Chassis V2483, a solid-state design introduced last year, is used in one 18" and one 20" model. The only tube employed in this chassis, other than the CRT, is a 1K3 high-voltage rectifier.

The 8" "Jet Set" receiver is an AC/DC model equipped with the V2652 all-transistor chassis. A voltage tripler circuit provides 9.5 kv of high voltage to the 9XP4 picture tube used in this chassis. Also employed in this chassis is an active power filter circuit, shown in Fig. 18. The remaining 18" and 20" "Jet Set" models use carryover Chassis V2487. This is a transformerless tube-type chassis.

Thirteen additional portable receivers (not included in the Jet Set grouping) are also available. Four of these are 12" models utilizing the V2490 chassis. Eight portable models use the carryover V2486 chassis; six have 18" CRT's and two offer 20" screens. One 18" portable uses the all-transistor V-2483 chassis.

The table and console models included in Westinghouse's '68 b-w line all use 22" screens. One roll-about table model is offered, along with two receivers that can be used as either table or console models. The console grouping consists of eight models; five use Chassis V2487.

ZENITH

Two new chassis designs are in-

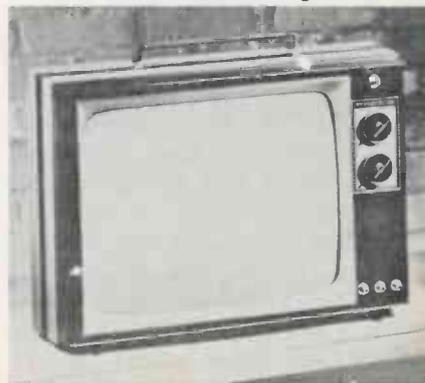


Fig. 17. Sylvania's new Model MY71K.



THE ELECTRONIC SCANNER

news of the servicing industry

Hugo Gernsback Dies

Hugo Gernsback, pioneer in electronic invention, author, publisher, and called the father of modern science fiction, died on Saturday, August 19, in New York City. He was 83 years old.

At his death Mr. Gernsback held 80 scientific patents. He was editor in chief of RADIO-ELECTRONICS, editor in chief and publisher of the magazine Sexology, and chairman of the board of Gernsback Publications, Inc.


During his long publishing career, he put out more than 50 magazines, including the first radio magazine, MODERN ELECTRONICS in 1908, and the first science fiction publication, AMAZING STORIES in 1927. Mr. Gernsback is widely credited with having written the first true science fiction story, and with coining the term itself. In his honor, science fiction writing awards are called "Hugos."

He is perhaps best-known as a "Prophet of Science," as Life called him in a 1963 article. His first science fiction story, published in 1911, accurately predicted radar, microfilm, stainless steel and numerous other now commonplace things, even including night baseball. His window into the future has been producing amazingly accurate predictions ever since. M.I.T. scientists, in announcing the first Venus probe, opened with the statement that it was first "proposed by Gernsback in 1927."

Mr. Gernsback sponsored New York's first television broadcast in 1928, and was honored by the radio industry in 1953 in recognition of his "first 50 years of inspiring leadership in radio-electronic art."


His awards and associations include: Marconi Memorial Wireless Pioneer Medal, Veteran Wireless Operators, 1950; Gold Medal of Luxembourg, Grand Order of Oaken Crown; Silver Jubilee Trophy, Belgian Society Helios, 1953. Member American Physics Society, A.A.A.S.; founder Wireless Association of America.

COMPLETE TUNER OVERHAUL

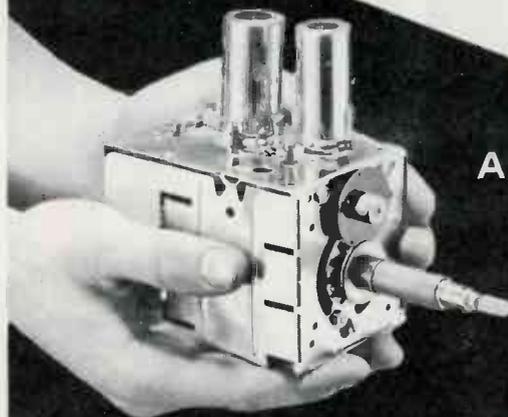

ALL MAKES —
ONE PRICE

9.95

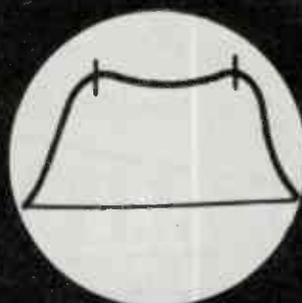

3.58

ALL LABOR
AND PARTS
(EXCEPT TUBES
& TRANSISTORS)*

COLOR TUNERS

GUARANTEED COLOR
ALIGNMENT — NO
ADDITIONAL CHARGE



VHF



UHF



COLOR



U-V



TRANSISTOR

Simply send us the defective tuner complete; include tubes, shield cover and any damaged parts with model number and complaint. Your tuner will be expertly overhauled and returned promptly, performance restored, aligned to original standards and warranted for 90 days.

UV combination tuner must be single chassis type; dismantle tandem UHF and VHF tuners and send in the defective unit only.

Exact Replacements are available for tuners unfit for overhaul. As low as \$12.95 exchange. (Replacements are new or rebuilt.)

And remember—for over a decade Castle has been the leader in this specialized field . . . your assurance of the best in TV tuner overhauling.

Pioneers of TV



Tuner Overhauling

CASTLE

TV TUNER SERVICE, INC.

MAIN PLANT: 5701 N. Western Ave., Chicago 45, Illinois
EAST: 41-90 Vernon Blvd., Long Island City 1, N.Y.

Get Trouble-Free Fuse Protection
in Wet Locations with a

TRON

IN-THE-LINE
WATERPROOF
Fuseholder



FOR USE ON:

- Electronic Components at Missile Sites
- Marine Equipment
- Mobile Power Supply Units
- Yard Lights
- Military Field Applications
- Communications Equipment
- Any circuit operating in exposed locations.

FOR PROTECTION OF CIRCUITS
OF 600 VOLTS OR LESS

Watertight construction; resistance to damage by weather, water, salt spray or corrosive fumes permit use of TRON fuseholders in exposed locations where safety and long life are of vital importance.

TRON fuseholders are available to take two sizes of fuses, $1\frac{1}{2}$ " x $1\frac{1}{2}$ " and $1\frac{3}{8}$ " x $1\frac{3}{8}$ "; and take many sizes of solid or stranded wire.

Write for BUSS Bulletin SFH-11

INSIST ON

BUSS QUALITY

BUSSMANN MFG. DIVISION, McGraw-Edison Co., ST. LOUIS, MO. 63107

Academy Avionics is a subsidiary of Ag Aviation Academy and is a resident, full-time aviation electronics school. VA approval means any of the courses may be pursued under the various G. I. Bill provisions.

Courses included in the certification are Basic Electronics, a 6-month course; Avionics (aviation electronics), 12 months; Advanced Avionics, 960 hours or approximately 6 months; and FCC License Course.

TV Next?

Philco-Ford announced price increases of 1 to 3%, effective September 22, on all of its appliance lines except air conditioners. The company said the move was taken "most reluctantly, but was forced upon us by the continuing increases in the costs of materials, labor and freight."

Products affected include refrigerators, freezers, ranges, dishwashers, automatic washers, dryers, combination washer-dryers and wringer washers.

The company pointed out that the industry price base for these products is substantially less now than it was in 1952, compared with an increase of more than 20% in all items on the Consumer Price Index. Average 1966 refrigerator prices, for example, were less than 55% of what they were in 1952.

BUSS: The Complete Line of Fuses and

\$5 Reward

In an effort to locate the few remaining sets which may have radiation levels above acceptable levels, **General Electric** is offering \$5 reward for turning in the obsolete HV regulator tubes from those sets. The tubes in question are: 6EA4, 6EF4, and certain 6LC6's. Contact your nearest GE distributor for details.

Microelectronic VR

An integrated microelectronic voltage regulator developed by **Delco Radio Division** will be introduced in some models of the 1968 Pontiacs. The miniaturized voltage regulator is so small that it can be included as a part of the Delcotron generator produced by Delco-Remy Division. In the past voltage regulators have been separate units about 3 x 3 x 4 inches in size.

The new Delco Radio unit has no moving parts. It is about the size of a man's wristwatch. Benefits derived from the new regulator include increased reliability because there are no moving parts, elimination of external wiring, and because electronic sensors are unaffected by moisture, aging, or vibration.

Courses Approved

Full Veterans Administration approval has been awarded **Academy Avionics** for electronics courses offered at Reno/Stead Airport, Reno, Nevada, the school has announced.


BUSS SUB-MINIATURE FUSEHOLDER COMBINATION

For space-tight applications. Fuse has window for inspection of element. Fuse may be used with or without holder.

Fuse held tight in holder by beryllium copper contacts assuring low resistance.

Holder can be used with or without knob. Knob makes holder water-proof from front of panel.

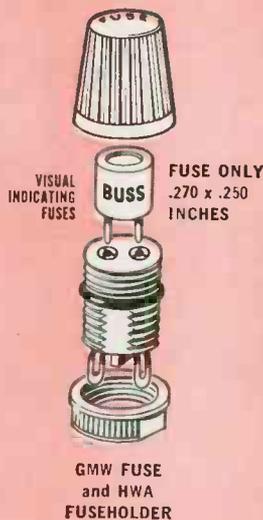Military type fuse FM01 meets all requirements of MIL-F-23419. Military type holder FHN42W meets all military requirements of MIL-F-19207B.



Write for PUSS Bulletin SFB

INSIST ON

BUSS QUALITY

BUSSMANN MFG. DIVISION, McGraw-Edison Co., ST. LOUIS, MO. 63107

Circle 6 on literature card

BUSS



Write for BUSS
Bulletin SFB.

QUICK-ACTING FUSES

"Quick-Acting" fuses for protection of sensitive instruments or delicate apparatus;—or normal acting fuses for protection where circuit is not subject to current transients or surges.

INSIST ON
BUSS QUALITY

BUSSMANN MFG. DIVISION, McGraw-Edison Co., St. Louis, Mo. 63107

Globe Battery and Centralab Electronics. Also located at the Glendale facility are Globe-Union's financial and data processing operations, a 30-thousand volume technical library, sales and purchasing organizations plus corporate and divisional administrative offices.

Perma-Power, a fast-growing Chicago-based electronics manufacturer, has occupied a second major facility on the city's Northwest side. The new facility, a modern two story brick structure, is directly adjacent to the company's main plant and provides Perma-Power with an additional 20,000 square feet of space. With the additional space, Perma-Power now occupies almost six times as much space as it did four years ago.

Texas Instruments and **Sprague** have entered into a non-exclusive, cross licensing agreement under their patents in the semiconductor field. Under this agreement, each is licensed to use the other's patents in the design and fabrication of semiconductor devices, including both integrated circuits and transistors. The rights exchanged are worldwide, except for Japan, and include TI's Kilby patents as well as Sprague's Lehovec patent.

The agreement further calls for dismissal without prejudice of TI's appeal from an adverse Patent Office decision and Sprague's counterclaim for infringement. The financial terms of the agreement were not disclosed. ▲

Fuseholders of Unquestioned High Quality

Mergers, Expansions, Etc.

Admiral announced that it has licensed Canadian General Electric Company and a European company to manufacture color picture tubes of Admiral design for television receivers, and to use Admiral-developed engineering and production equipment.


Vincent Barreca, president, said that the contracts also include provisions for technical assistance, and added that other discussions are being conducted with potential licensees in other parts of the world.

A new research and development center that will permit expansion of technical services to customers has been announced by **Belden**.

Robert W. Hawkinson, president of the Chicago-based manufacturer of wire, cable and cords, announced that Belden has purchased a 22,000-sq. ft. building near Geneva, Ill. "All research and development activities now being conducted at both our Chicago and Richmond, Ind., plants will be centralized in this modern new location," he said.

Globe-Union, manufacturer of electronic components, batteries and other packaged power units, has completed occupancy of its new Administrative and Research Park in Glendale, Wisconsin.

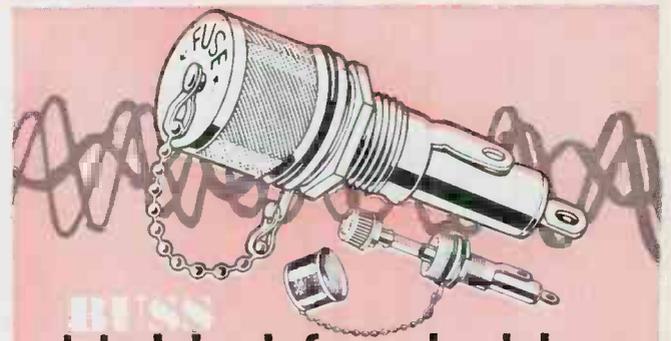The new 33-acre park houses executive offices for the firm, extensive research and engineering facilities plus headquarters for Globe-Union's two divisions,



shielded fuseholders

PREVENT RADIO
FREQUENCY INTERFERENCE

For use where fuse and fuseholder could pick up radio frequency radiation which interferes with circuit containing fuseholder — or other nearby circuits.

Fuseholder accomplishes both shielding and grounding. Available to take two sizes of fuses — $\frac{1}{4}$ x $1\frac{1}{4}$ " and $\frac{1}{4}$ x 1" fuses.

Meets performance specifications of both MIL-I-6181D and MIL-F-19207B.

INSIST ON
BUSS QUALITY

BUSSMANN MFG. DIVISION, McGraw-Edison Co., ST. LOUIS, MO. 63107

Circle 6 on literature card

COLOR TV

PART

3

service training



MASTERING

VERTICAL DEFLECTION

HORIZONTAL DEFLECTION

CIRCUITS

HIGH VOLTAGE

In lesson 2 of this series, the tuner, video IF amplifier, sound IF amplifier and output, luminance (or video) amplifier, and the sync and AGC circuits were discussed. All of these circuits are similar to circuits having the same functions in a black-and-white set.

The tuner and IF circuits are modified only slightly to increase the response near the upper edge of the video passband. Additional traps are required to prevent interaction between the 4.5-MHz sound carrier and the 3.58-MHz chroma information. The additional traps make it necessary to move the sound takeoff point "forward" and use a separate sound IF detector. Otherwise, the sound system is conventional. The

AGC and sync circuits are nearly identical to the ones found in monochrome receivers.

The luminance channel performs the same functions as the monochrome video amplifier and also it has some additional features. It provides for video delay, performs the retrace blanking, incorporates the brightness control, and, of course, it drives three CRT cathodes instead of one. The luminance channel is direct coupled and this can lead to service problems for the unwary technician.

Vertical Deflection Circuit

The circuit most frequently used to generate the vertical deflection

current is a modified free-running multivibrator. The modifications are incorporated to change the usual square-wave output into a waveform which produces a sawtooth current through the deflection coil or yoke. Since the impedance of the yoke is inductive, current lags the voltage; and so the multivibrator output waveform rises very steeply, decays steeply to about one-half its maximum, and then decays at an almost linear rate.

The circuit shown in Fig. 1 is from the Zenith 24MC32 chassis. This circuit is typical of many receivers although several sets examined used the old, familiar twin-triode configuration. We also noted that some circuits have the hold

not completely linear since it is a portion of the exponential charging curve of a capacitor; however, V9 is not linear either (gain is different at various bias levels). By proper adjustment of the linearity control, a level of bias is obtained that causes these two inherent nonlinearities to be equal and opposite.

The network consisting of C47, K2, R98, and C50 shapes the feedback pulse to the grid of V7. The shape of this pulse determines the conduction time of V7 and this determines the retrace time. M7 disables the multivibrator for color setup purposes. R102 and R103 are loading resistors across the deflection coils. They prevent the coils from oscillating at the end of the retrace interval. The resistance of R95 decreases with temperature rise to compensate for the increase in resistance of R96, R8, and R4 as the temperature rises.

Some sets use a vertical centering circuit to control a small DC current which flows through the vertical deflection coils. This current either aids or opposes the vertical deflection current to shift the entire raster up or down.

Horizontal Phase Detector

The horizontal oscillator and its synchronizing circuits used in color sets are no different than those used in b-w receivers. The schematic shown in Fig. 2 is the horizontal phase detector circuit used in the Philco 16QT85 chassis. The two inputs to the phase detector are compared to determine their relative timing and a correcting voltage (error signal) is developed to correct the oscillator frequency.

Negative sync pulses from the sync separator are applied to the junction of the cathodes of the phase detector diodes and both diodes conduct. This places a negative charge on the tops of C75 and C52. Between sync pulses, these capacitors discharge as follows: C75 discharges downward through R113 causing the anode of X20 to be negative with respect to ground. C52 discharges downward through R112 causing the bottom of R112 to be positive with respect to its top. Since the voltage at the bottom of R112 cannot be negative with respect to the top of R113 and the voltage drops across R112 and

R113 are nearly equal, the voltage measured from the top of R112 (or C52) to ground is nearly zero.

At about the same time that the sync pulse is applied to the junction of the diode cathodes, a negative pulse from the horizontal output transformer is supplied to the junction of C76 and C77. This drives electrons away from the top of C76 and down through R112 and R111. During the interval between pulses, the current flows back up through R111 and R112 producing a positive-going sawtooth at the top.

Now consider the interaction of the two separate actions which result from the sync pulse and the feedback pulse. Referring to Fig. 3A, we see the phase relation of the two voltages when the oscillator is operating at the correct frequency. The sync pulse arrives shortly after the start of the negative-going feedback pulse. Since X19 can conduct only until its anode becomes negative with respect to its cathode, only a portion of the electrons that could be supplied by the sync pulse actually get to the top of C52. During the long interval between sync

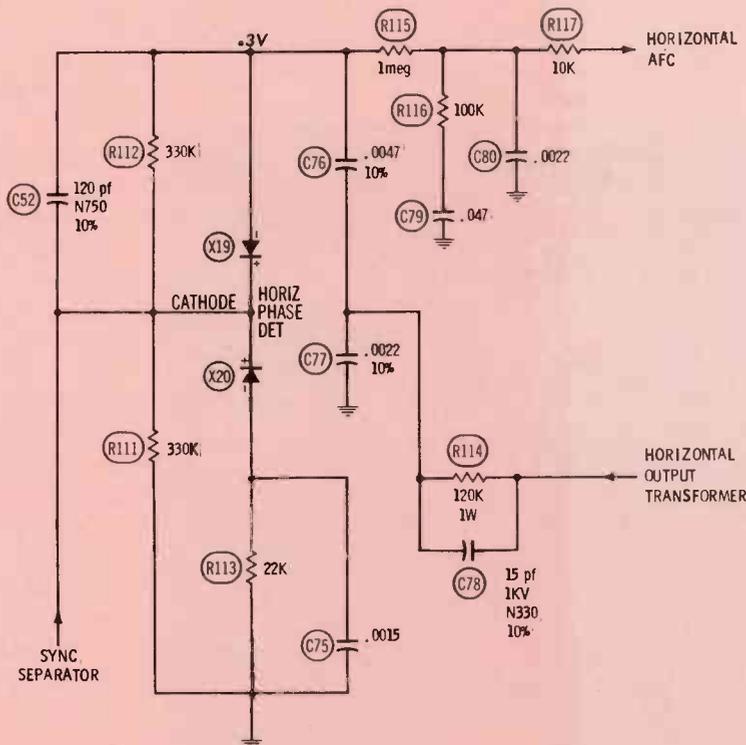


Fig. 2. Horizontal phase detector of the Philco 16QT85 chassis.

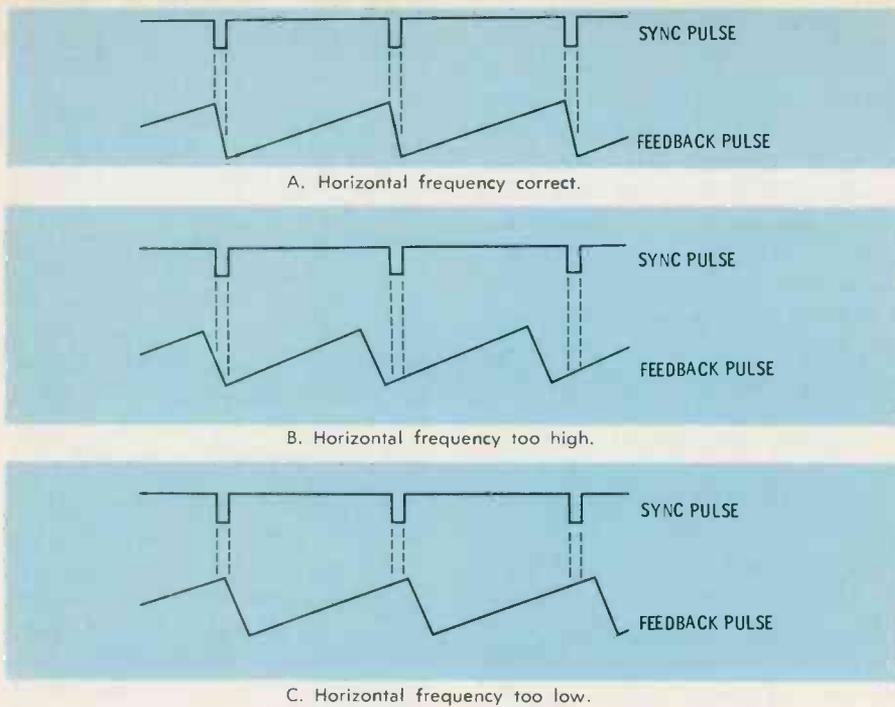


Fig. 3. Horizontal sync and feedback pulses.

pulses, some of the electrons required to recharge the top of C76 are supplied from C52 and the remainder flow upwards through R111 and R112. Since the total-current through R111 and R112 has been diminished by the action of the feedback pulse, the average-voltage at the top of C76 is less positive than it would be in the absence of the sync pulse.

Fig. 3B illustrates the action of the phase detector if the oscillator

frequency is too high. The feedback pulse is shifted to the left from its normal position and the anode of X19 is driven farther negative before the sync pulse arrives. As a result, fewer (or none) of the electrons supplied by the sync pulse are actually deposited on the top of C52. During the interpulse interval, all of the electrons must flow upwards through R111 and R112 and the voltage at the top of C76 is more positive.

Inspection of Fig. 3C shows that if the feedback pulse arrives too late (frequency low), a greater portion of the sync pulse electrons reach C52 and the average voltage at the top of C76 is less positive than before.

Referring once again to Fig. 2, R115, R116, R117, C79 and C80 form the anti-hunt network. This is essentially an integrating circuit which smooths the voltage at the top of C76 into an almost constant level. If the integrations are too great (time constants too long), horizontal pulling will result because the AFC tube will not correct the frequency quickly enough. On the other hand, too little integration will cause horizontal jitter because the AFC tube will tend to overcorrect the frequency (hunt).

From this discussion of the phase detector circuit, we learn that an increase in oscillator frequency results in a positive-going error signal at the grid of V7. While this is true of this specific circuit, some circuits are designed so that the exact opposite is true. That is, increased frequency produces a negative-going error signal in some receivers even though the circuit configuration is quite similar.

Horizontal AFC and Oscillator

Referring to Fig. 4 which is the schematic of the AFC and oscillator circuits of the same Philco 16QT85 chassis, the error signal is applied to pin 9 of V7. However, before attempting to understand the operation of the AFC tube, the operation of the oscillator must be thoroughly understood.

The oscillator is basically a Hartley type although the tank circuit capacity, as well as the inductance, is tapped. The waveshape of the oscillator output is modified by R124 and C88 before it is applied to the output tube. V7B is grid-leak biased by R122 and C84.

The frequency-determining circuits of the oscillator are L37, C85, C86, and the AFC tube. Insofar as an AC signal is concerned, the AFC tube is shunted across C86, and so the current through V7A is part of the total current of the tank circuit.

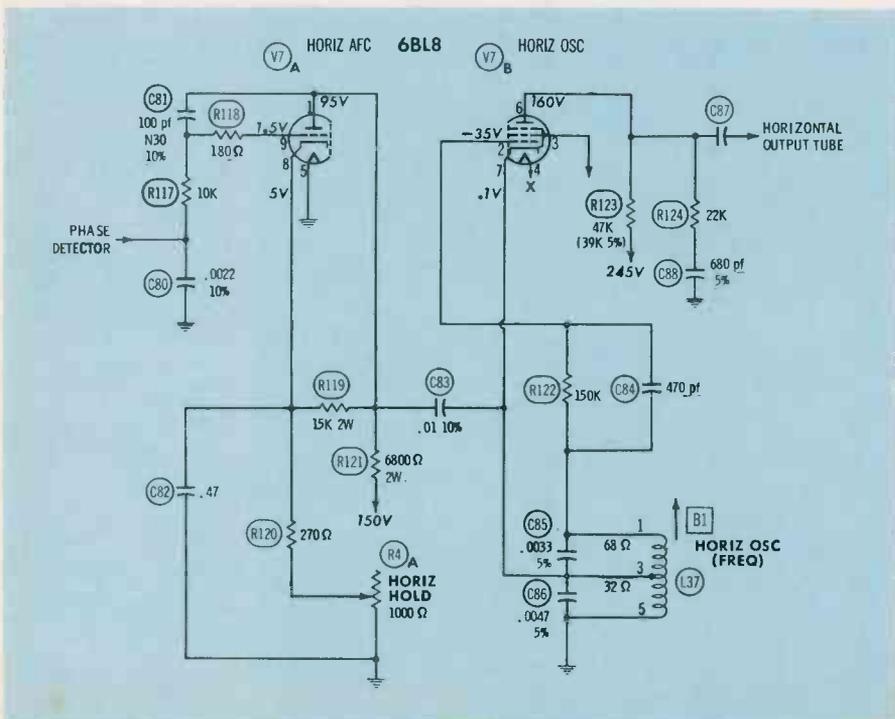


Fig. 4. Horizontal oscillator and AFC of the Philco 16QT85 chassis.

Compare Color Generators

look at the rest... and you'll buy the best, new B&K model 1245

The all solid-state B&K Model 1245 Color Generator duplicates the waveforms transmitted by a color TV station.


Adherence to these waveforms makes it easy to converge the color tube, check sync and make other raster adjustments... and the color generator with station quality signal will be able to sync next year's sets. Generators with compromise waveforms do not give you this obsolescence protection.

Here are oscilloscope photographs from the outputs of two typical competitive color generators, one transistorized and one tube type, and the B&K Model 1245. The detailed analysis with each photograph shows a few of the reasons why you'll save time and effort with B&K.

COLOR

CROSSHATCH

STANDARD STATION SIGNAL

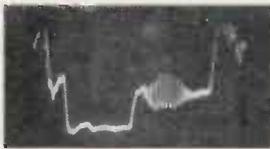


One horizontal sync pulse with its color burst.




Two lines showing horizontal sync pulse with black and white tv signal.

TRANSISTORIZED B&K MODEL 1245

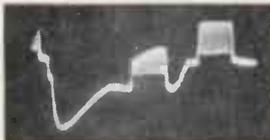

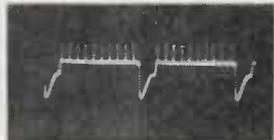Good duplication of station signal including back porch. If the set won't sync, the set is defective.




Well defined back porch on horizontal sync pulse permits accurately setting color killer and almost eliminates need to adjust brightness and contrast.

TRANSISTORIZED GENERATOR A



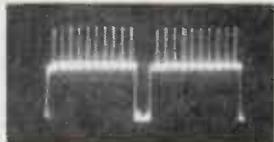No back porch causes unstable color sync. Burst amplitude compression may permit sync on wrong color bar.



Square wave horizontal sync pulse with no back porch and poor dc coupling forces adjustments of brightness, contrast & fine tuning to obtain usable pattern.


GENERATOR B



No back porch; color information on top of sync-pulse makes sync difficult on some sets.



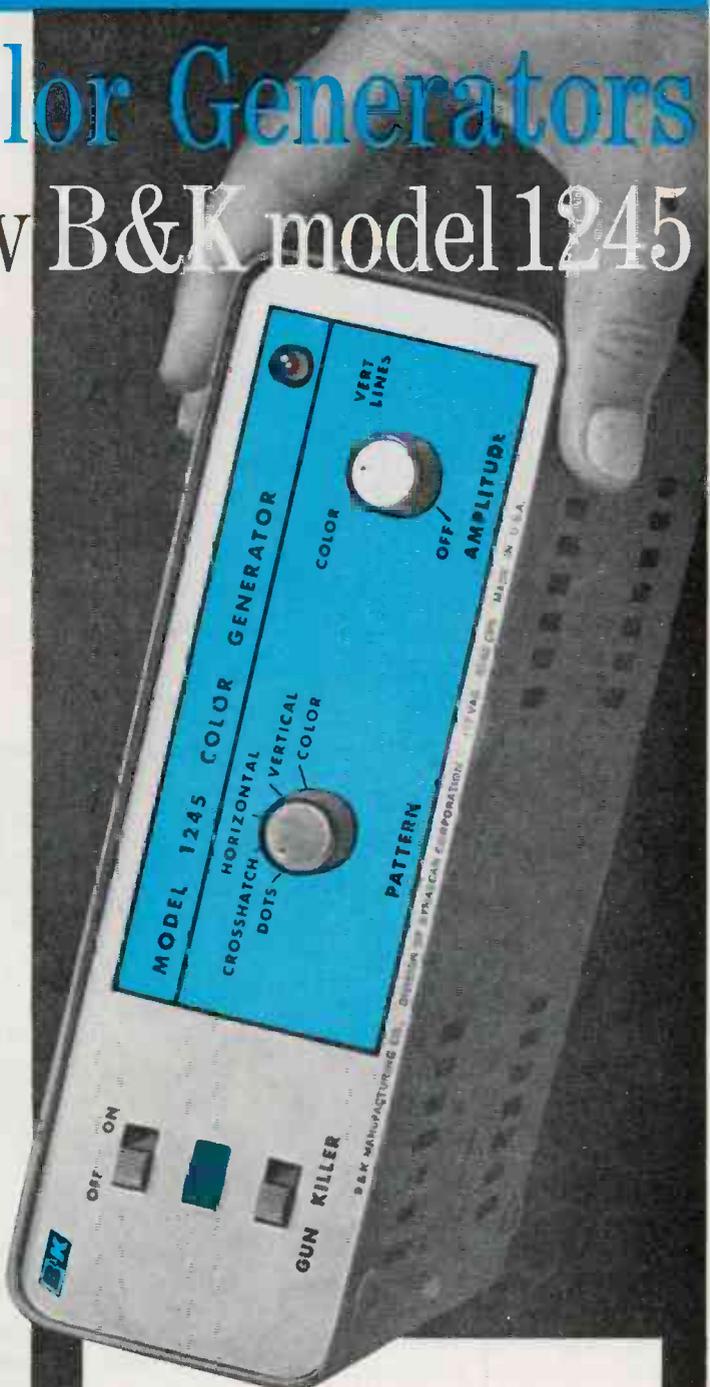Complete absence of any back porch necessitates readjustment of brightness, contrast and fine tuning to obtain a usable pattern.



For the first time, with the no-compromise waveforms from the B&K Model 1245, it is possible to accurately set the color killer threshold control with a color generator.

The miniature size and convenience of the Model 1245 match its performance. It provides crystal-controlled keyed rainbow color bar display, and dot, crosshatch, horizontal line and vertical line patterns as well as gun killer controls that will work with any picture tube. Size only 2 7/8 x 8 1/2 x 8 7/8". Net \$134⁹⁵.

See your B&K Distributor for a demonstration or write for Catalog AP22.



If you're looking for trouble,



you'll find it fast.

That's what Amphenol test equipment is all about. The CRT Commander. The Milivolt Commander. The Signal Commander. The Color Commander. The Stereo Commander. They're all time savers. With them you can test any TV, radio or stereo set. They let you find trouble, fix it, then get out of there. See your Amphenol distributor. Or write us direct. Amphenol Corporation, Department ET-107, 2875 South 25th Avenue, Broadview, Illinois 60153.



CRT



Milivolt



Stereo



Color



Signal




AMPHENOL

Circle 8 on literature card

www.americanradiohistory.com

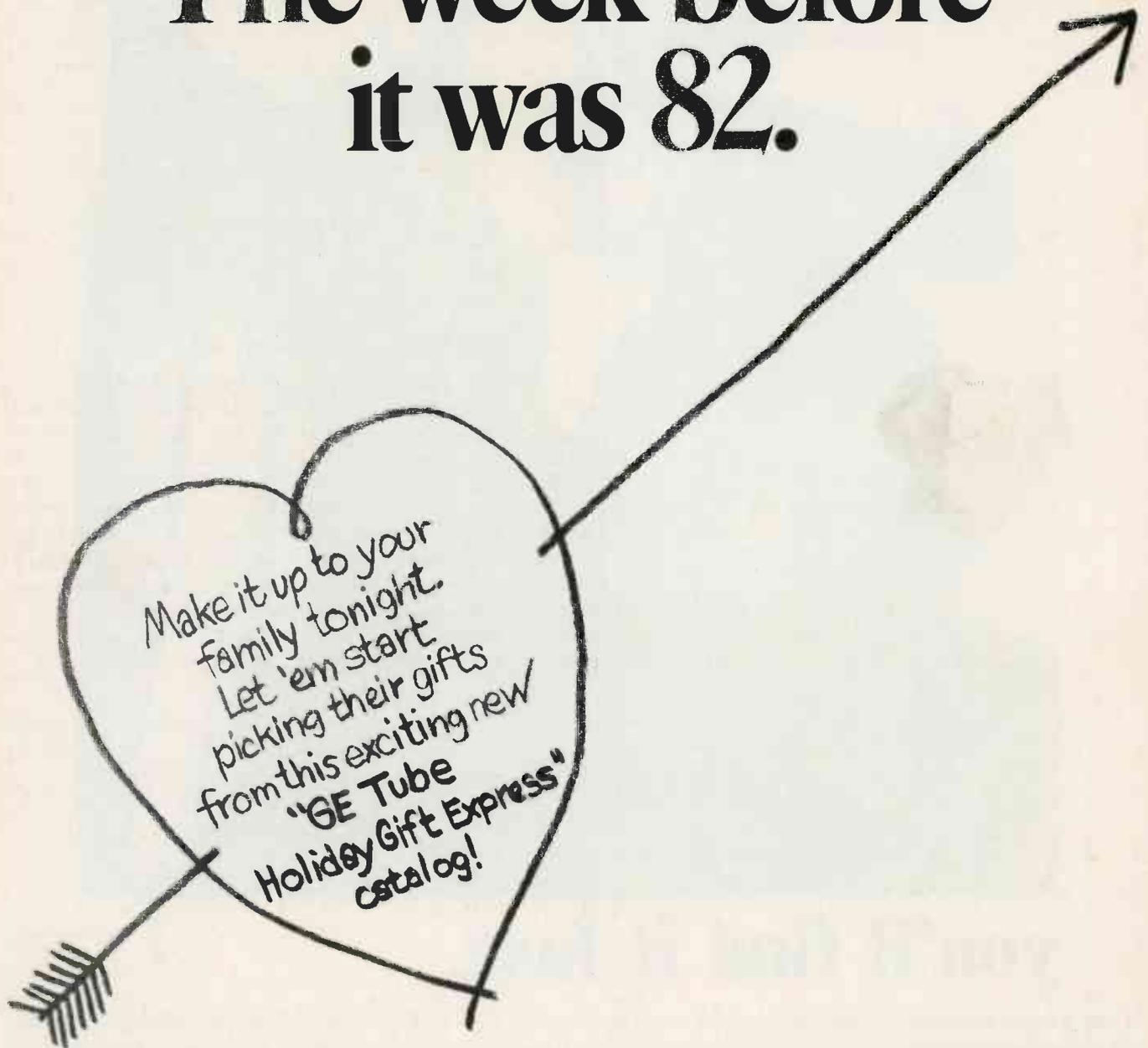Last week you worked
71 hours.
The week before
it was 82.



Make it up to your
family tonight.
Let 'em start
picking their gifts
from this exciting new
"GE Tube
Holiday Gift Express"
catalog!

Buy General Electric Entertainment Receiving
Tubes and earn valuable gifts for the whole
family. See your participating GE Tube Dis-
tributor today for complete information. 288-12

GENERAL  ELECTRIC

Earn these valuable gifts when you buy GE Tubes!



1. GILBERT PIONEER 600 MODEL TRAIN SET, Model 20811
57 Gift Points



2. GE CUSTOM ELECTRIC SLICING KNIFE, Model EK-9
46 Gift Points



3. GE PORTABLE TAPE RECORDER, Model M8021
66 Gift Points



4. GE HEAT 'N SERVE BABY DISH, Model D-2
26 Gift Points



5. GILBERT LAB 1 MICROSCOPE, Model 13301
18 Gift Points



7. REMCO KATRINA DOLL, Model 3046
21 Gift Points



6. GE AUTOMATIC 8-CUP COFFEE MAKER, Model P-12
36 Gift Points



8. GE ELECTRIC SHOE POLISHER KIT, Model SP-2
49 Gift Points



10. GE DELUXE AUTOMATIC CAN OPENER/KNIFE SHARPENER, Model CG 15, 40 Gift Points



9. GE AUTOMATIC TOOTHBRUSH SET, Model 5109
36 Gift Points



11. GE AUTOMATIC BLENDER, Model BL-1
70 Gift Points



12. GE CUSTOM PORTABLE MIXER, Model M-67
36 Gift Points



13. GE HEAT MASSAGER, Model MR-2
34 Gift Points



14. AMF VELOCIPEDE TRICYCLE, Model B-915
38 Gift Points



15. GE AUTOMATIC MANICURE SET, Model MS-1
50 Gift Points

MORE . . .

Get aboard!
GE Tube Holiday Gift Express



16. GE PORTABLE HAIR DRYER, Model HD-20
 41 Gift Points



17. GE SPRAY, STEAM & DRY IRON, Model I-81
 47 Gift Points



18. GE AUTOMATIC TOASTER, Model T-82
 46 Gift Points



19. REMCO WEATHER STATION, Model 437
 16 Gift Points



20. AURORA CUSTOM RACING SET, Model 1314
 48 Gift Points

Get valuable gift tickets when you purchase GE Tubes!



Select gifts for the whole family and redeem your gift tickets in time for the holidays

Allow 2-3 weeks for delivery. Orders must be postmarked by midnight, December 8, 1967 for Christmas delivery. This offer void where taxed or prohibited by law.

GE Tube Holiday Gift Express

GIFT ORDER FORM

Check Selections	Gift	Gift Points	Quantity	Points Enclosed
1.	Gilbert Train Set	57		
2.	GE Slicing Knife	46		
3.	GE Tape Recorder	66		
4.	GE Baby Dish	26		
5.	Gilbert Microscope	18		
6.	GE Coffee Maker	36		
7.	Remco Doll	21		
8.	GE Shoe Polisher	49		
9.	GE Toothbrush Set	36		
10.	GE Can Opener/ Knife Sharpener	48		
11.	GE Blender	70		
12.	GE Portable Mixer	36		
13.	GE Heat Massager	34		
14.	AMF Tricycle	38		
15.	GE Manicure Set	50		
16.	GE Hair Dryer	41		
17.	GE Iron	47		
18.	GE Toaster	46		
19.	Remco Weather Station	16		
20.	Aurora Racing Set	48		

MAILING LABEL

SHIP TO: NAME _____
 ADDRESS _____
 CITY _____
 STATE _____ ZIP _____

Mail this order form, along with the correct number of gift tickets to:

GE TUBE HOLIDAY GIFT EXPRESS DEPOT
 POST OFFICE BOX 300
 NEW YORK, NEW YORK 10008

See your GE Tube Distributor today for details.

GENERAL ELECTRIC
 ETR-4829

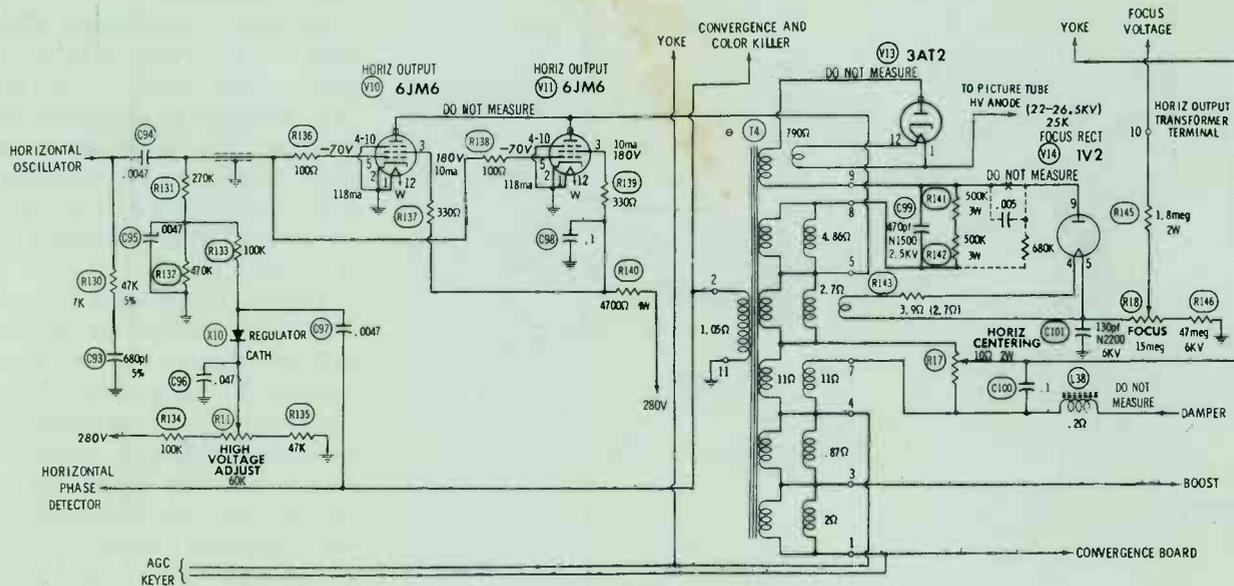


Fig. 6. Horizontal output and high-voltage circuit of the Admiral 1G1155-1 chassis.

are made black or gray, the CRT beam currents decrease and the ultor supply voltage tends to rise. The boosted B+ also rises and this positive-going voltage is used to decrease the bias on V16. Thus, V16 conducts more, the load on the ultor supply remains constant, and the ultor voltage is stabilized.

Some manufacturers use the average potential of the CRT cathodes as a control voltage for the ultor

regulator. A black picture is produced by a positive-going voltage at the CRT cathodes, and this voltage (in lieu of the boosted B+) is used to increase the conduction of the regulator tube.

A rather unique approach to the problem of high-voltage regulation is illustrated in Fig. 6. This is a schematic of the horizontal output and high-voltage section of the Admiral 1G1155-1 chassis. Notice that

no shunt regulator is used.

A feedback pulse from the secondary winding (terminals 1 and 2) of T4 is rectified by X10 and the resulting voltage is added to the bias supply for the horizontal output tubes. This total bias determines the amount of drive to the high-voltage transformer and, finally, the potential of the ultor supply.

As the CRT beam currents increase and load the supply, the am-

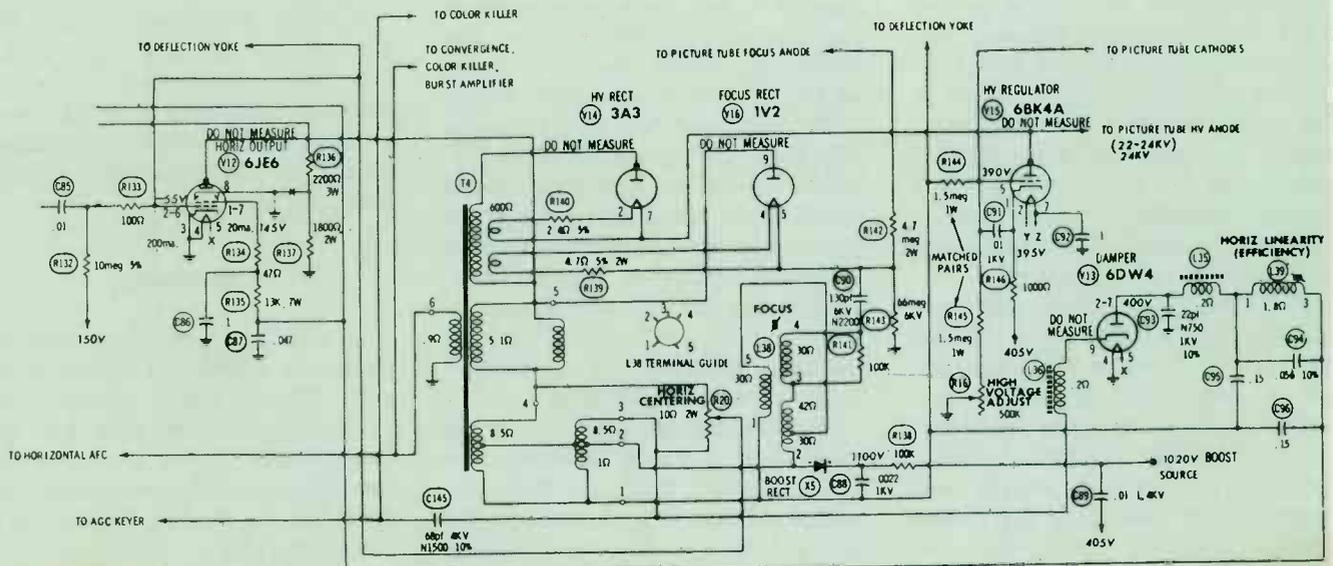


Fig. 7. Horizontal output and high-voltage circuit of the RCA CTC16 chassis.

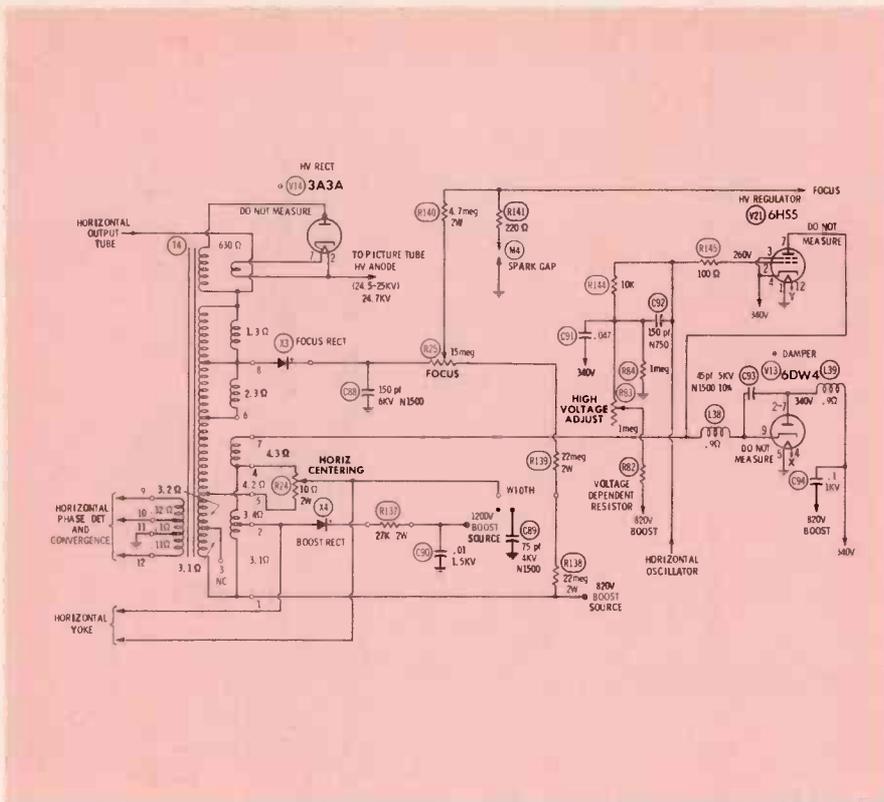


Fig. 8. Horizontal output circuit in Zenith 23XC38 chassis.

plitude of the feedback pulse is decreased and this results in a lesser bias voltage at the grids of V10 and V11. This causes V10 and V11 to conduct more heavily to increase the ultor voltage.

While this system is adequate, it does allow some variations in the high voltage. In order to maintain good focus over a range of ultor voltages, the focus voltage is made to "track" the ultor voltage. This is accomplished by R141 and R142 along with their filter, C99. As the CRT beam currents increase, the voltage across R141 and R142 increases and this voltage is added to the output of the focus rectifier to adjust the focus automatically for changes in CRT current. A slight change in width as the brightness control is rotated is normal in receivers using this circuit.

The horizontal output and high-voltage circuits of the RCA CTC16 chassis are shown in Fig. 7. In this circuit, the focus rectifier is connected to the plate of the horizontal output tube and develops 4 to 4.5 kv. The ultor voltage supply and regulator are similar to the Zenith chassis discussed earlier, but the regulator control voltage is derived from the CRT cathodes.

The horizontal-centering problem

is solved by driving the yoke with two identical windings of the high-voltage transformer. A 10-ohm potentiometer used as a centering control is connected between terminals 3 and 4, and a small DC potential exists across it. One end of the yoke is connected to the center arm of the control. Depending on the setting of the control, a small DC current can be caused to flow in the yoke to change the centering.

A third method of high voltage regulation has been developed in the Zenith 23XC38 chassis. The horizontal output circuit is shown in Fig. 8. This circuit uses a type 6H55 regulator (V21) whose cathode and plate are connected to B+ and a tap of the horizontal-output transformer, respectively. Since the tube is operating at potentials which are much lower than those encountered in the conventional shunt regulator circuit, there is no need for radiation shielding or a double-ended envelope for the tube.

The control signal for V21 is derived from a divider network consisting of R82, R83, and R84 connected between a portion of the boosted B+ supply and ground. R83 is used to set the bias level of V21 and this ultimately adjusts the ultor supply voltage. A second volt-

age is also applied to the grid of V21. This is a positive pulse taken from the cathode circuit of the horizontal oscillator.

Assume a white raster which results in maximum loading of the ultor power supply. The boosted B+ potential is minimum and the bias on V21 is maximum. Under these conditions, the conduction of V21 is minimum and the regulator has little effect on the output voltage of the ultor supply.

Under black-raster conditions, there is no load on the ultor supply and this voltage tends to rise. The boosted B+ also tends to rise and the bias of V21 is reduced. The horizontal-oscillator pulse causes V21 to conduct during the retrace interval and this conduction loads the horizontal output transformer. Stated another way, V21 clips the positive excursion of the "ringing" or flyback pulse of the horizontal-output transformer and this tends to reduce the ultor supply voltage. The amount of clipping (or loading) is determined by the boosted B+ potential which, in turn, is determined by the load on the ultor supply. As the raster changes from black to white, the conduction of V21 becomes progressively less and so the ultor supply voltage is stabilized.

The regulator tube is pulsed on only during horizontal retrace for two reasons:

1. Since V21 is cut off during the forward scan, it does not affect the width of the raster.
2. Since V21 conducts only during retrace, the duty cycle is low and only a minimum amount of power is extracted from the horizontal-output circuit. This also minimizes the plate-dissipation requirements for V21.

Summary

In this lesson, we have analyzed the power supply and deflection circuits. The principal difference between these circuits and their b-w counterparts is that greater power-handling capability and greater stability are required in the circuits of color receivers.

The next lesson in this series (Part 4) will begin the discussion of the chroma circuits. ▲

PROTECTS AGAINST • Bent Pointers • Burned-Out Resistors
 • Damaged Pivots • Overheated Springs • Burned-Out Meter
 • Changes in Accuracy Due to Overheating



Model 630-PLK

BURNOUT PROOF V-O-M

\$89.00
Suggested
U.S.A. User Net

USES UNLIMITED

School Classrooms • Field Engineers • Application Engineers
 • Electrical, Radio, TV, and Appliance Servicemen • Electrical
 Contractors • Factory Maintenance Men • Industrial Elec-
 tronic Maintenance Technicians • Home Owners, Hobbyists

FACTS MAKE FEATURES:

- 1** Comprehensive overload protection.
- 2** One selector switch minimizes chance of incorrect settings
- 3** Polarity reversing switch

Additional protection is provided by Model 630-PLK's new transistorized relay circuit. Transistorized overload sensing device does not load circuit under test, eliminating the possibility of damaging circuit components. A special meter shorting feature on "off" position offers high damping when moving tester. The exclusive patented Bar Ring Movement provides self-shielding and is not affected by stray magnetic fields. Wider spread scales, and unbreakable clear plastic window assure maximum readability. Diode network across meter protects against instantaneous transient voltage.

TRIPLETT ELECTRICAL INSTRUMENT COMPANY, BLUFFTON, OHIO


RANGES

DC Volts:	0-2.5-10-50-250-1,000-5,000 at 20,000 ohms/volt; 0-0.25 at 100 microamperes.
AC Volts:	0-3-10-50-250-1,000-5,000 at 5,000 ohms/volt.
Decibels:	-20 to +11, +21, +35, +49, +61, +75; "0" DB at 1 MW on 600 ohm line.
DC Microamperes:	0-100 at 250 Mv.
DC Milliampere:	0-10-100-1,000 at 250 Mv.
DC Amperes:	0-10 at 250 Mv.
Ohms:	0-1,000-10,000 (4.4-44 at center scale).
Megohms:	0-1-100 (4,400-440,000 at center scale).

Output Volts (AC): 0-3-10-50-250-1,000 at 5,000 ohms/volt; jack with condenser in series with AC ranges.

CARRYING CASE

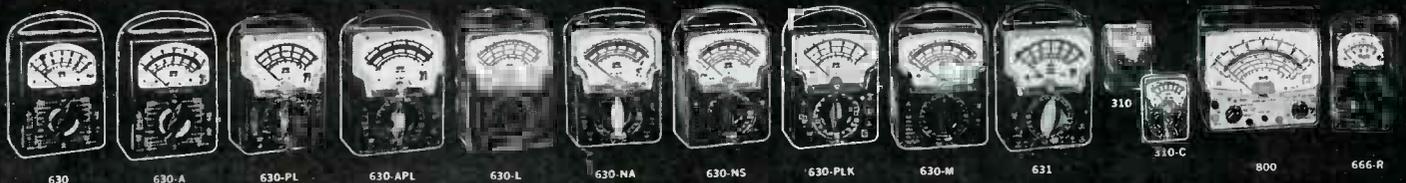Model 639-OS black leather carrying case, built-in stand, Flaps open to permit use of tester in the case. Suggested U.S.A. User Net.\$14.00



THE WORLD'S MOST COMPLETE LINE OF V-O-M'S. AVAILABLE FROM YOUR TRIPLETT DISTRIBUTOR'S STOCK.

Circle 10 on literature card

www.americanradiohistory.com

NOTES ON TEST EQUIPMENT

*analysis of test instruments
...operation...applications*

By T. T. Jones

FET VM

The new "Millivolt Commander" just released by Amphenol is about as close to the state of the art as you can get. It combines the feature of many different instruments into one package.

It functions as a VOM (sorry, no current scales) because it's completely portable — no line cord. It's a good substitute for a VTVM because it boasts 10.6-megohm input resistance on DC ranges and 10-megohm impedance on AC. It also has high-sensitivity ohms scales — 10 ohms to 10 megohms center scale. It even masquerades as an AC VTVM because it has the very sensitive AC ranges usually found only in AC VTVM's. And to top it off, the accuracy is $\pm 2\%$ DC and $\pm 3\%$ on AC ranges.

FET meters are popping up like spring tulips all over the industry. Nearly every test equipment manufacturer is either producing or developing one. Amphenol's Model 870 happens to be the first we've had an opportunity to analyze, but if others follow the pattern of desirable features per dollar, then the VTVM may be on the way out.

The basic metering circuit is shown in Fig. 2. Q1 is the FET. Just think of it as a conventional triode tube. It's purpose is impedance matching from the high-Z input to the low-Z second stage. It also provides amplification.

CR-1 is an overload protection diode. It's not a conventional zener, but acts as one in this circuit. Its purpose is to keep the applied voltage within the FET's gate ratings. Remember that even a momentary

overload can puncture the gate insulation and irreparably damage a FET.

Q2 is the second stage of amplification. This stage is a conventional PNP common emitter configuration and needs no explanation. Most of

Amphenol Model 870 Specifications

DC Voltmeter

Ranges:

0-.1 1-1000V in a 1-3 sequence. + DVC or - DVC.

Input resistance:

10.6 megohms all ranges.

AC rejection:

40 dB greater than full-scale affects reading less than 1%.

Accuracy:

$\pm 2\%$ of full scale.

AC Voltmeter

Ranges:

Input impedance:

0-. 01-300V in a 1-3 sequence. -40 to +50 dB in 10 dB steps.

.01 to 1V scales; 10 megohms shunted by 31 pf. All other scales; 10 megohms shunted by 20 pf.

Accuracy:

$\pm 3\%$ of full scale.

Ohmmeter

Ranges:

0-500 Ω —500M Ω with 10 center.

Voltage:

1.5V open circuit.

Accuracy:

$\pm 3^\circ$ arc.

Size (HWD):

5 $\frac{3}{4}$ " x 9 $\frac{1}{4}$ " x 6 $\frac{7}{8}$ " o.a.

Weight (with batteries)

5 pounds.

Power Source:

8 "AA" 1.35-to 1.5-volt cells, 2 AA 1.4-volt mercury cells. (Carbon cells may be used in all circuits if 1 mv per day zero drift can be tolerated.)


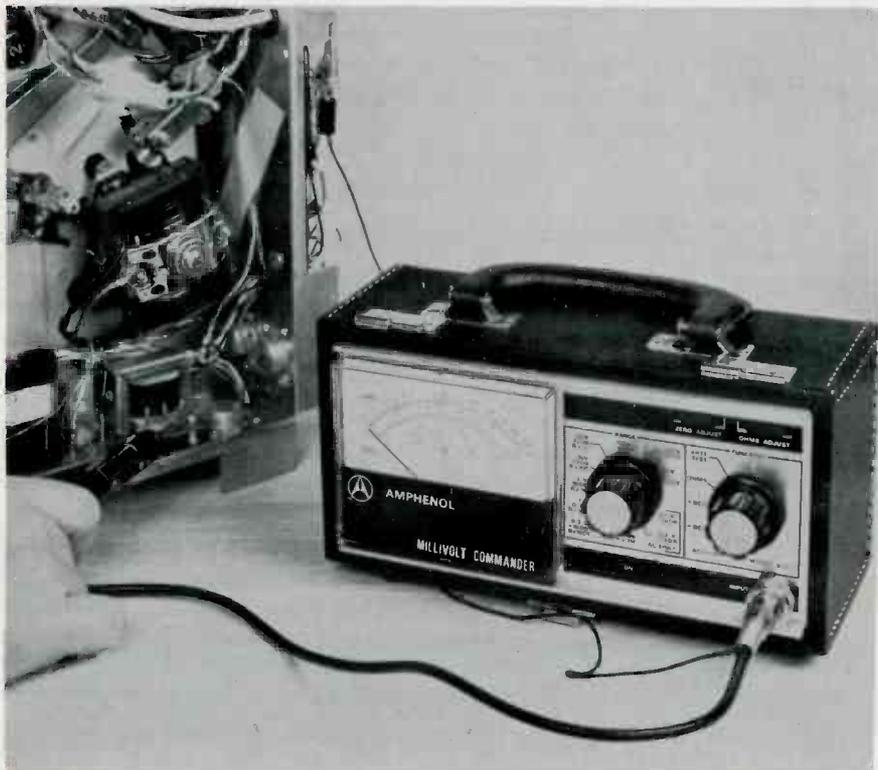


Fig. 1. New meter features field-effect transistor.

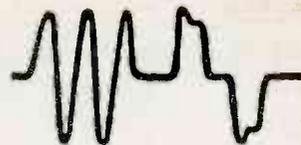

Which miniature electrolytics for transistorized AM-FM radios ?

COMPARATIVE SIZES
OF CAPACITORS ALL RATED
10 MFD., @ 25 WVDC
(shown actual size)



TT aluminum electrolytic



MTA aluminum electrolytic



TAS solid tantalum



TAP wet slug tantalum



TLS wet slug tantalum



MTP wet slug tantalum

The new portable AM-FM radios are so compact you wonder how they get all those components into that little box. You wonder even more when you have to replace some of the parts.

Electrolytic capacitors, for example. The original electrolytic usually turns out to be a tiny thing jammed in among a dozen other midget gadgets. Getting it out is a trick in itself. Getting a suitable replacement is even tougher! And unfortunately, you're apt to need replacements, because many of these tiny capacitors just aren't much good. They don't meet the quality specs of good domestic capacitor makers. But high quality domestic capacitors are often just a bit too big to fit in the space available.

What's the answer? Search the town for another "little-bitty" original capacitor? Tell your customer you can't finish the job?

Don't give up. We have a few suggestions.

First, try a Mallory TT aluminum electrolytic. This is a real quality capacitor, rated 85°C, and it's pretty doggone small. Or a Mallory MTA, a revolutionary molded case aluminum electrolytic with excellent quality at low price.

If neither of these will fit, try a Mallory tantalum capacitor. The TAS solid tantalum is about the same size as the TT, but it's rated 125°C. Need still smaller size? Take a look at the Mallory "wet slug" tantalum types TAP and TLS—and the super-miniature MTP, which gives you the most microfarads in the smallest size of anything on the market. The pictures at the left show you comparative sizes, all for a 10 mfd, 25 WVDC rating.

Sure, you'll pay a little more for the tantalum capacitor. But not as much as you might think. The TAP only costs 42¢ more than the TT, in the rating shown. And you get the utmost in reliability.

We certainly don't expect you to use a tantalum capacitor to replace every aluminum electrolytic. But they come in mighty handy sometimes. And you can get them when you need them from your Mallory Distributor. Ask him for our latest catalog, or write to Mallory Distributor Products Company, a division of P. R. Mallory & Co. Inc., Indianapolis, Indiana 46206.

DON'T FORGET TO ASK 'EM—*"What else needs fixing?"*

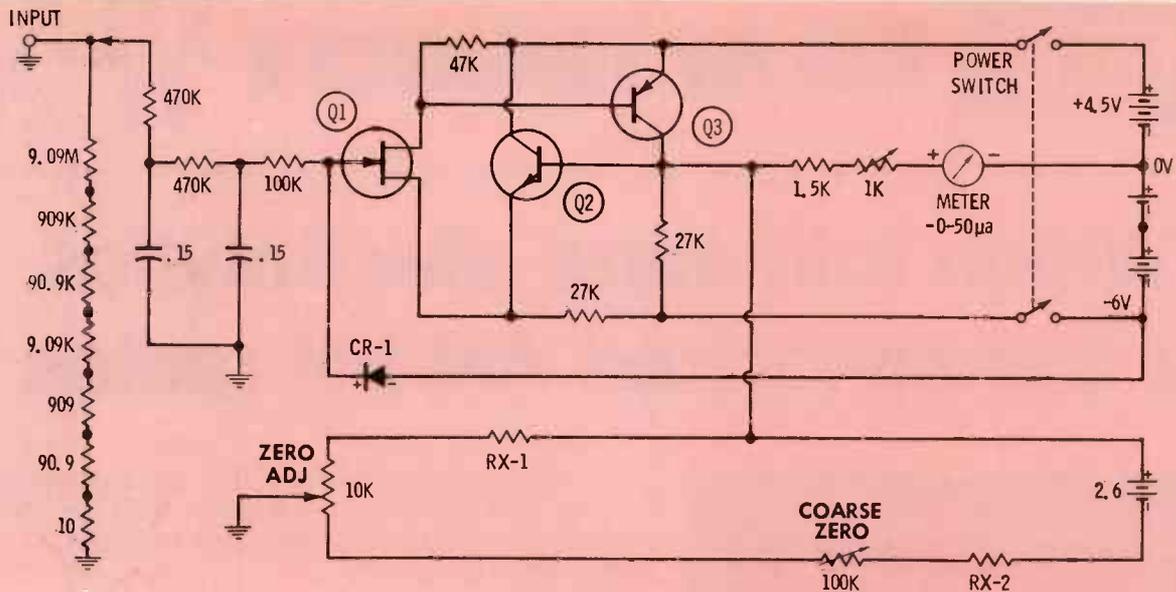


Fig. 2. Simplified schematic of the DC voltmeter.

the output is applied to the meter, but a portion of Q2's output is fed to Q3, the stabilizer. Similar stabilizing stages can be found in most high-quality VTVM's. It senses changes in the overall gain of the amplifier and compensates for these changes. Thermal drift, power supply voltage changes, and aging of components may cause a slight

drift in overall gain. Q3 acts on this through an inverse feedback arrangement and corrects the errors.

When measuring AC voltages, an additional two-stage amplifier is switched in between Q2 and the meter. There are also some frequency compensating components switched in at the input.

The Model 870 is housed in a

black leatherette-covered wood case which matches the other instruments in the Amphenol line. There's a large pocket in the cover for lead storage. To help conserve batteries, the instrument is automatically switched off when the cover is closed.

For further information circle 56 on literature card

Why not sell the best

Now...get
genuine Zenith parts
three ways faster—
with ZIP!

Your Zenith Distributor has a revolutionary new system to speed your replacement parts ordering. Called "ZIP" (Zenith Instant Parts), it gives you much improved service.



Easy-to-handle, space-saving microfilm cards in file 2" to 3" deep replace 10 feet of catalogs.

1. Looking up parts numbers is 100% quicker than before. Because parts lists and schematics for the past ten years are now microfilmed on compact, easily-handled filmcards.

2. "Out-of-stocks" are cut down. The new ZIP program helps your Zenith distributor keep tighter inventory controls and maintain a more complete stock.

3. Factory special orders are shipped faster. Under the new ZIP program, the Zenith factory is geared to ship orders without delay.

Order from your Zenith Distributor for "Zenith Instant Parts" service on all genuine Zenith replacement parts and accessories.


ZENITH®
The quality goes in before the name goes on

Circle 12 on literature card

Want a high-pay career in Electronics?

This free book may change your life

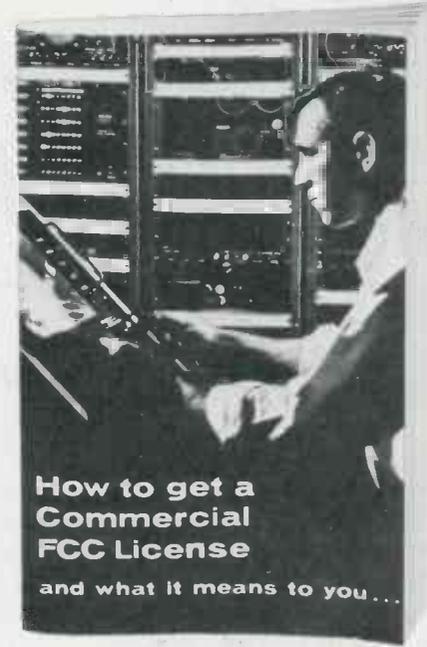It tells how to go about getting the key to job success in the growing electronics boom—a Government FCC License



THERE'S A BIG BOOM IN ELECTRONICS. And YOU can be part of it. You don't need a college education or any previous experience in electronics. The free book shown here tells you how.

In the last 15 years, the electronics manufacturing industry alone has grown from \$2.7 billion to \$17 billion, and is expected to hit \$24 billion by 1970.

Thousands of trained men are urgently needed to help design, manufacture, inspect, test, install, operate, and service electronics marvels that are making headlines. If you qualify, it means a secure, steady high-pay job with a real future to it.

Maybe you'd like to become a broadcast engineer . . . put famous radio disc jockeys and television entertainers "on the air." Or be your own boss servicing some of the more than a *million* two-way mobile radio systems in taxis, trucks, trains, etc. Or work alongside famous scientists developing and testing such electronics miracles as picture-frame TV, desk-top computers, pea-sized hearing aids, rocket guidance and control systems.

Regardless of which you choose, the secret of "getting your foot in the door" is getting a Government FCC (Federal Communications Commission) License. It's government-certified *proof*, respected by employers everywhere, that you have passed a standard Federal exam on the fundamentals of electronics—that you're not just an electronics handyman, but a real "pro." Many jobs legally require it.

Now, because of the importance of getting your FCC License, Cleveland Institute of Electronics has prepared a valuable 24-page book telling you how to go about it.

ENROLL UNDER NEW G. I. BILL

All CIE courses are available under the new G.I. Bill. If you served on active duty since January 31, 1965, OR are in service now, check box in coupon for G.I. Bill information.

You will find out why the Commercial FCC License is often called the "passport to success." You'll see how and why the Government issues these licenses. You'll learn how you can get your license . . . and qualify for top opportunities in Electronics.

With this book, you will receive a second free book, "How To Succeed In Electronics." It's the catalog of the Cleveland Institute of Electronics . . . first organization to offer an FCC License Warranty. (CIE will refund all of your tuition if you don't pass the FCC exam . . . on your first try . . . after completing the course designed to prepare you for it.) You will learn why better than 9 out of 10 men with CIE training get their FCC Licenses, even though 2 out of 3 without this training fail.

To receive both books without cost or obligation, just mail the coupon below. If coupon has been removed, write to: Cleveland Institute of Electronics, 1776 East 17th Street, Dept. PF-40 Cleveland, Ohio 44114. Do it now—it may change your whole life.

MAIL COUPON FOR 2 FREE BOOKS

CIE Cleveland Institute of Electronics
1776 East 17th Street, Cleveland, Ohio 44114

Please send me, without cost or obligation, your 24-page book, "How To Get A Commercial FCC License," together with your school catalog, "How To Succeed In Electronics," of license-preparation courses.

Name _____ (please print)

Address _____

City _____ State _____ Zip _____


Occupation _____ Age _____

Check here for GI Bill information.

Accredited Member National Home Study Council
A Leader in Electronics Training . . . Since 1934 PF-40

repairing the deluxe

AM-FM CHASSIS

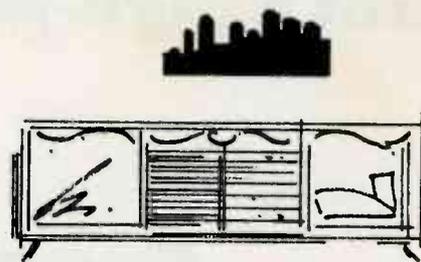

by David Held

Sophisticated circuitry doesn't necessarily require the most elaborate test equipment. The case histories and troubleshooting techniques discussed in the following paragraphs help clarify this point.

The size, shape, and audio power rating of high-quality AM-FM solid-state chassis is as varied as cabinet sizes and design. Shown in Fig. 1 is a block diagram of a typical solid-state AM-FM chassis. The most common model is the AM-FM stereo combination. The larger consoles provide 60 to 250 watts of audio power

and employ up to 44 transistors and 31 diodes. These large console units also employ up to eight speakers covering the 20 to 20,000-Hertz audio frequency range.

The circuitry of the solid-state AM-FM chassis is basically similar to the vacuum tube chassis, except for more stages. This is especially

true in the audio amplifier section.

One significant difference between the tube and transistor chassis is the low-voltage power supply. The tube chassis may have voltage requirements ranging up to 450 volts; however, the solid-state chassis seldom needs more than 70 volts maximum—typically, much less.

Most high-quality AM-FM receivers have an FM-RF amplifier stage followed by a converter or separate oscillator-mixer stage. In the AM section, we find an AM-RF stage and converter circuit. Three or more transistor IF stages are used for both AM and FM functions.

Troubleshooting

If I had to choose only three test instruments for troubleshooting AM-FM solid-state chassis they would be the noise signal generator, in-circuit transistor checker, and VTVM. With these test instruments, a service technician can uncover the cause of most troubles in AM-FM chassis. Of course, nearly all up to date service shops have a scope, capacitor analyzer, and signal and audio generator to round out the test equipment required for solid-state servicing.

Circuit Analysis

We had a Truetone Model 4DC-5665A come into the shop with only a hissing sound on FM. The local FM station could just barely be heard. Of course, the stereo indicator light would not come on. The AM stations and phonograph played perfectly.

Looking at the schematic diagram, we attempted to isolate the

Table I
Transistor Replacement

STAGE AND TYPE	RCA	General Electric	Delco
AM Converter or RF, PNP	SK 3005	GE-1	DS-25
FM-RF AMP, PNP	SK 3006	GE-9	DS-41
FM-IF AMP or FM-Converter, NPN	SK 3018	GE-11
AF Output or Driver, PNP	SK 3004	GE-2	DS-26
NPN	SK 3020	GE-10	DS-46
Audio Output	SK 3009	GE-3	DS-52
Audio Output Hi Fidelity AMP (Matched Pair)	SK 3014		

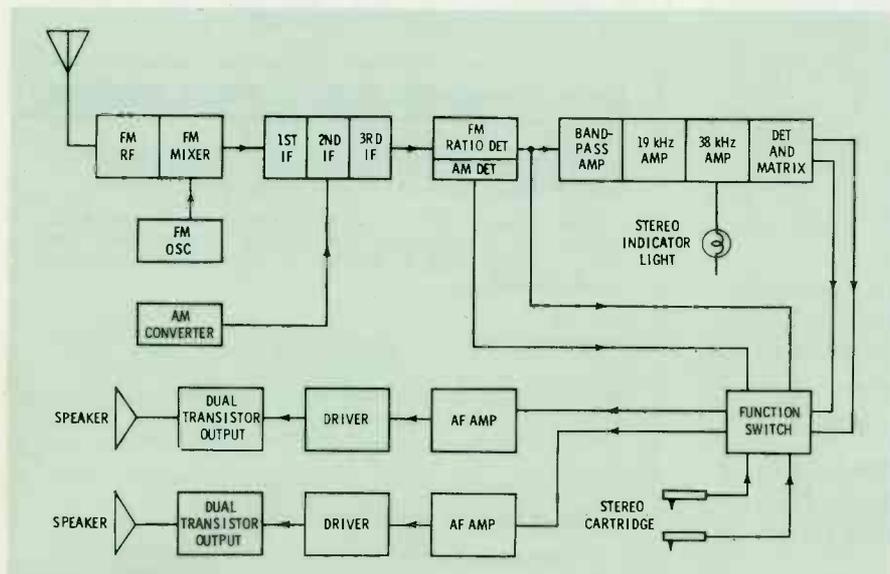


Fig. 1. Block diagram of a typical deluxe AM-FM Chassis.

circuit. Since the AM section worked perfectly, the trouble must be located between the first IF stage and the FM antenna. Another clue was a weak local FM station received at 93MHz.

This last clue told us that the FM oscillator and mixer stages were performing—although weak—so the trouble must be in the FM-RF stage. We clipped the in-circuit transistor tester to the three transistor terminals, as shown in Fig. 2. The absence of a beta or leakage reading indicated an open transistor. Once this defective RF transistor was replaced, the receiver returned to normal operation.

In many solid-state receivers, the circuitry is so compact that individual stages are difficult to get at. Be extra careful when unsoldering and pulling small transistors out of such tight places—unnoticed damage to surrounding components and circuitry can add hours to a simple thirty minute repair job. Also, check the replacement transistor before it is installed, and be sure it is installed in the exact spot as the original. Table 1 provides a list of common replacement transistors for solid-state AM-FM chassis.

Signal Injection

An RCA Chassis RC1223A had no AM or FM reception. The phonograph played normally. Using the output of a signal noise generator, and starting at the AM audio function switch, we progressed from the crystal detector to the IF stages. We reasoned that the trouble had to be in the IF stages since both AM and FM reception were dead. The schematic revealed that the AM converter was fed to the 1st FM-AM IF amplifier stage.

Applying the output of the noise signal generator to the base and collector of the 3rd and 2nd IF stages (in that order) localized the trouble to the base of the 2nd AM-FM IF amplifier. The signal was heard at the collector but not at the base. No signal was heard by injecting the signal at the emitter.

The in-circuit transistor checker indicated that the 2nd IF amplifier transistor was shorted. It is possible to have high microamp leakage in an in-circuit transistor tester, but usually a dead short or 2K- to 5K-

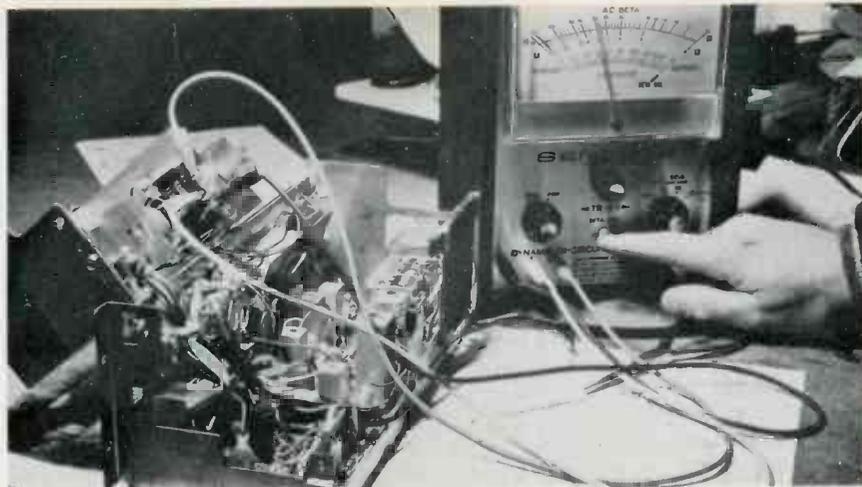


Fig. 2. Checking beta and leakage with an in-circuit transistor tester

ohm leakage will show up as a defective transistor. For an accurate leakage test, the suspected transistor should be removed from the circuit board. Many times a diode or directly driven transistor tied in the collector circuit will show up as a shorted transistor.

In-circuit transistor beta and leakage tests may produce readings that differ slightly from one chassis to another; however, the readings shown in Table 2 are typical and, therefore, can be used for comparison purposes.

In another solid-state AM-FM chassis, the high end of the AM band was completely dead. Below about 1000 kHz the radio operated normally. The FM band and phono were also normal.

If this trouble symptom was displayed by a tube-type chassis, the oscillator tube would be suspected and replaced. Why should the solid-state chassis be treated any differently—after all, the circuitry is basically the same.

The oscillator transistor was removed and checked on the high-beta scale. The beta reading was 50, with no sign of leakage. A couple of new transistors designed for the oscillator stage were selected and their beta readings checked. The RCA SK-

3008 had a beta of 70, the SK3005 checked in at 80, and the SK3007 produced a beta reading of 100.

According to the PHOTOFACT for this particular chassis, the oscillator required an RCA SK3005 transistor. Sure enough, the AM radio played perfectly across the entire AM band when the new oscillator transistor was installed. The defective transistor was checked in an older type transistor tester and produced a reading in the green scale.

The most common failure in solid-state circuitry is a shorted, weak, open, or noisy transistor. It is easy to locate a defective transistor stage by using a noise signal generator and proceeding from base to collector of each transistor until the defective stage is located. Then, an in-circuit transistor checker will show if the transistor is at fault. In the event the transistor checks good, voltage and resistance checks can be made to isolate the defect.

VTVM or VOM Tests

Solid-state servicing requires an accurate VTVM and a good ohmmeter to check the low resistances and voltages found in transistor circuits. Transistor emitter and base voltages range from .1 to 6 volts. Collector voltages vary from zero to

Table 2
Typical Transistor Readings In AM-FM Solid-State Chassis

STAGE	BETA READING	LEAKAGE (MICROAMPS)
RF Hi-scale	35	1K
OSC Hi-scale	25	2K
IF	45	225
AF	35-45	0 to 20
Power Hi-fidelity	30-500	5K

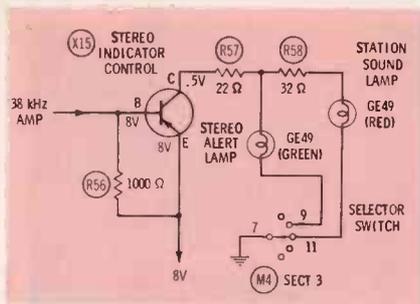


Fig. 3. Stereo and sound indicator circuit of Silvertone Chassis 528.63310.

60 volts. (The higher voltage is found in output stages.)

Along with low emitter and base voltages, transistor circuits also have low values of resistance. The emitter resistances of the RF and converter stages range from 330 to 4700 ohms. Emitter resistors in the IF stages vary from 330 to 1000 ohms, while the emitter resistance in the audio output stage may be as low as .39 ohms. With these low values of voltage and resistance, a VTVM or 20,000 ohms-per-volt meter should be used.

Multiplex Stages

The ratio detector circuit employed in most deluxe AM-FM chassis uses two crystal diodes. Only one diode is used in the detector stage of the AM band. The FM stereo signal is fed to the multiplex and doubler stages. A stereo indicator lamp is found in the matrix output stage.

The stereo FM indicator bulb will light only if a stereo multiplex signal is being received. The stereo indicator circuit of a tube-type FM receiver uses a neon bulb as the stereo indicator. Nearly all transistorized chassis use a pilot light in

the collector leg of a separate stereo indicator amplifier stage.

As a preliminary check of the multiplex section of the receiver, tune in a local FM stereo station and observe the stereo indicator light; it should come on. If not, remove and replace the pilot light. Also, check the pilot light socket and wiring associated with the stereo indicator circuit.

We had an unusual case of "no stereo reception" come in from a local TV shop. The receiver was a Silvertone 528.63310 chassis and we were told there was no FM stereo reception. The technician had checked the pilot light and made a few simple voltage checks. He also informed us that he had tried to make the stereo indicator light come on by adjusting the 19-KHz doubler and 38-KHz amplifier transformer slugs. Of course, he didn't have an FM stereo multiplex signal generator to correctly align the stages.

After we spent an hour aligning the multiplex section, the stereo indicator still failed to light. However, the station sound lamp was operating. (This chassis has, in addition to the stereo indicator, a station sound lamp that can be switched into the stereo indicator transistor circuit, as shown in Fig. 3.) In a few minutes the stereo indicator was repaired by resoldering a poor connection on pin 9 of the switch section.

Multiplex and IF transformers seldom change alignment by themselves. It is possible to have shunting capacitors change value and throw them off frequency, but such cases are very rare. Never try to

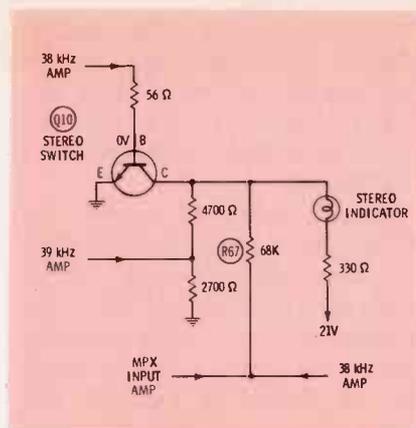


Fig. 4. Stereo indicator circuit employed in RCA tuner Chassis 1227B.

align a multiplex circuit until all tests have proven conclusively that alignment is the problem, and then follow the manufacturer's alignment procedure using proper equipment.

Another trouble involved a solid-state RCA RC-1227B tuner chassis that was noisy during FM reception. The popping and cracking noise was evident across the entire FM band. Reception on a local FM station was quite good, except for the noise. The AM and phonograph sections were quiet and played perfectly. This trouble was definitely a noisy transistor in the FM front end.

The IF transistors were checked, but nothing showed up. We unplugged all front end transistors and checked each individually. Often, a noisy transistor cannot be detected on a transistor checker, so we substituted all three transistors. Still no results. The local FM stereo station was tuned in once again and we noticed the stereo indicator light was out. We had not noticed this condition before, so we checked the indicator bulb. When the bulb checked good, we probed around in the indicator circuit (Fig. 4) and stumbled across the trouble: One of the stereo indicator light plugs had been pulled off and opened the circuit at the top of R67. Replacing the small plug brought life to the stereo indicator light and knocked out all popping and cracking.

While repairing the stereo indicator section of an RCA RC-1223A chassis (Fig. 5), a few voltage checks were made. We found that when a local FM stereo broadcast station was tuned in, the collector voltage of Q11 returned to zero. Of course, the stereo indicator light was on with the station tuned in properly.

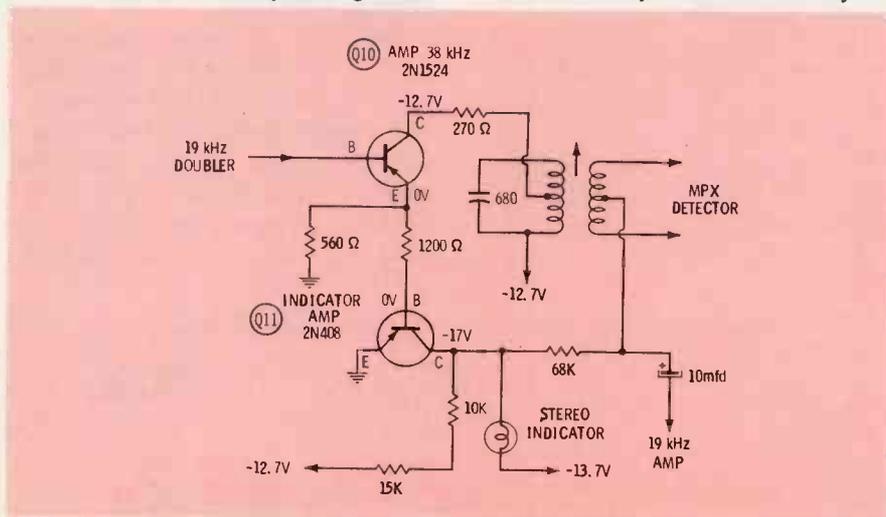


Fig. 5. RCA Chassis 1223A uses stereo indicator circuit shown here.

COLOR GENERATORS

FOR EVERY NEED

4 reasons why Sencore is your best buy
in professional test instruments

1

LOBOY CG10

America's lowest priced professional quality standard color bar generator. All solid state. Battery powered for maximum portability.

\$89.50



2

LOBOY CG12

AC operated version of the CG10. Also has 4.5 MHz crystal controlled signal for fine tuning adjustment.

\$109.50



3

COLOR KING CG141

Absolute stability assured by exclusive "Temp Control" and new timer circuitry. All standard patterns, plus new movable single dot and single cross. Analyzing features too.

\$149.95



4

COLOR ANALYZER CA122B

The complete analyzer for color and B&W—far more than just a color generator. Has variable RF and IF outputs, composite video, chroma, and horizontal and vertical sync pulses.

\$187.50



Whatever the need, Sencore has the color generator that is just right for you. Each has the built-in quality you expect from Sencore. Each has standard RCA licensed color bar patterns.

Each is triple tested for guaranteed accuracy. Each is steel encased with chrome panel. See your distributor for more reasons why Sencore is your best buy, always.



SENCORE


NO. 1 MANUFACTURER OF ELECTRONIC MAINTENANCE EQUIPMENT
426 SOUTH WESTGATE DRIVE, ADDISON, ILLINOIS 60101

Circle 14 on literature card

Plug in
with a
winner...

TV
SERVICE
CORDS by

Columbia

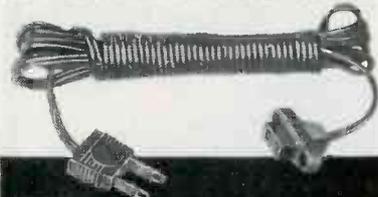

Match the requirements of most every TV set in use today from the broad selection of service cords Columbia produces and stocks to meet immediate needs.

Choose from a variety of non-polarized and polarized caps and connectors for safer operation, added customer protection against shock hazards. Available in standard 6 and 9-foot lengths, Columbia cords have durable vinyl or rubber insulation, are available in brown or white to meet color preferences.

All are quality built to give long, trouble-free service life, added customer satisfaction, and greater profits for you.

Order from
your
distributor today!

Columbia
WIRE PRODUCTS COMPANY
2850 Irving Park Road
Chicago 60618

Circle 15 on literature card

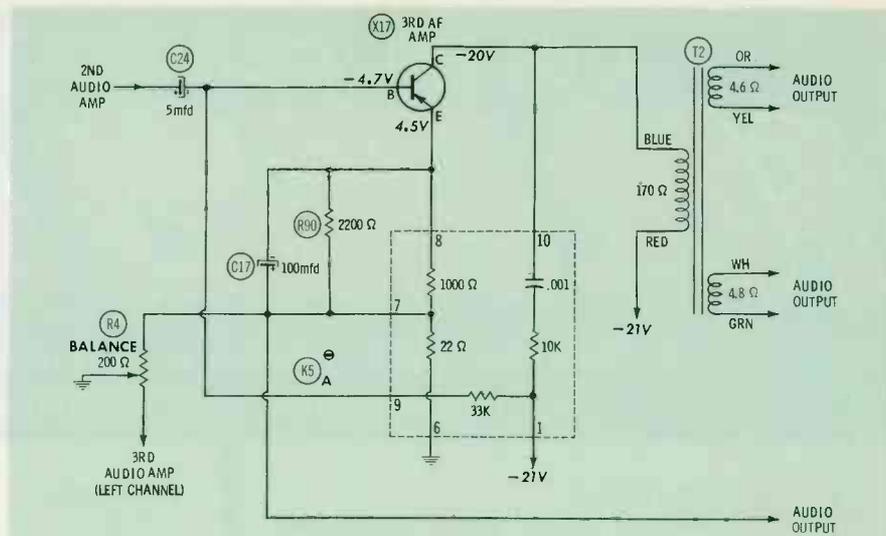


Fig. 6. Leaky coupling capacitor caused distortion in right channel of Magnavox Chassis R204-10.

With the receiver tuned slightly off station, the light went out and Q11 collector voltage returned to the value of the supply voltage. In this particular case, the collector voltage was -12.7 volts.

If the indicator light is not open, the voltage on the collector terminal of Q11 is zero; if the stereo indicator light is open, the voltage will

increase to -12.7 volts. The base voltage of Q11 is zero when a stereo station is not being received. On a local stereo station, the base voltage of the indicator transistor will increase to -1 volt.

Checking the Audio Stages

The noise signal generator can also be used to find a defective audio stage. From the base terminal of the final audio output stage proceed back toward the phono input jack. A reduction or complete loss of audio signal will be encountered at the defective stage. Use the VTVM or VOM to find the defective component.

With a small audio signal loss, or in case of extreme distortion, a scope and audio signal generator should be used. When the volume of one channel is extremely low and will not balance up properly, the noise signal generator will help locate the trouble. But when there is only a small loss of signal, the scope will quickly pinpoint the defective stage. For cases involving extreme distortion, a square-wave audio generator and scope will quickly locate the stage causing the distortion.

A Magnavox Chassis R204-10 had extreme distortion in the right channel. The crystal cartridge was checked by switching the phono input leads. For a sure check, the square-wave audio signal generator was attached to the phono input stage. The volume control was turned wide open, while the output of the square-wave generator was kept as low as possible at 2000 Hz.

EXTRA PROFIT! FOR COLOR TV TECH.

Now - you can bench service color TV as easy as black & white and convert usual lost time into an extra profit. Remove color chassis only - No truck or helper needed. No time lost carrying test equipment to customer's home BUY NOW - PREPARE FOR COLOR SERVICE RUSH

NEW! 21" COLOR TEST PEDESTAL WITH PANEL BRACKET



MODEL C21
TECH-NET 14.50
PAT. PEND.

FOUR RECTANGULAR TEST PEDESTALS AVAILABLE

This "EIGHT BALL" 21" color test pedestal, is designed to secure your test tube, deflection yoke and convergence panel in position for direct hookup, exactly as in customers cabinet and bench service of chassis in horizontal or vertical positions without cables; plus, full view of picture in service mirror. One man portable and perfect for use on all makes with 70 degree deflection. Costs less than set of extension cables - Pays for itself with time saved - Rectangular test pedestals available. Model R19" 14.50 - R21" 15.50 - R23" 16.50 - R25" 17.50 See your distributor or remit direct - Postpaid U.S.A.

8 EIGHT BALL COMPANY 8
1135 W. MAIN ASHLAND OHIO

Circle 16 on literature card

The scope probe was applied to the collector and base of each transistor and the scope readings compared with those in the normal left channel. Using this method, the distortion was quickly localized to the input of the 3rd AF amplifier. A 5-mfd electrolytic coupling capacitor, C24 in Fig. 6, was found to be leaky. Electrolytic capacitors, burned resistors, and leaky audio output transistors are the most common causes of distortion in AM-FM solid-state chassis. A good circuit capacitor tester will quickly locate a bad capacitor.

Intermittent audio stages can be caused by a cracked crystal cartridge or defective audio coupling capacitors. Many times a poor solder connection on a PC board will cause an intermittent condition. Twisting or pushing up and down on the PC board will usually uncover this source of intermittent trouble.

We had another case of extreme distortion with low, garbled volume in the left channel of an Electro-home Model TR30M. This trouble had to be in the final output stages. Using the PHOTOFAC schematic, we located the two final power output transistors and removed them from the chassis. One of the transistors had a dead short. A new RCA SK3009 power transistor was installed in its place.

We still had low volume with some distortion. Checking the circuit closer, we discovered that R93 and R89 (Fig. 7) were burned and had changed value. It is advisable to check for burned resistors in final output transistor circuits when a leaky or shorted transistor is found.

Conclusion

Repairing the solid-state deluxe AM-FM chassis is no more difficult than servicing tube-type chassis if proper test equipment is used. A good schematic is a must item. For extreme distortion or intermittent conditions, use the scope and capacitor analyzer. Use an in-circuit transistor checker to quickly check the transistor in the suspected section. If the transistor is not defective, check voltages and resistances with a VTVM or 20,000 ohms-per-volt (or better) VOM. ▲

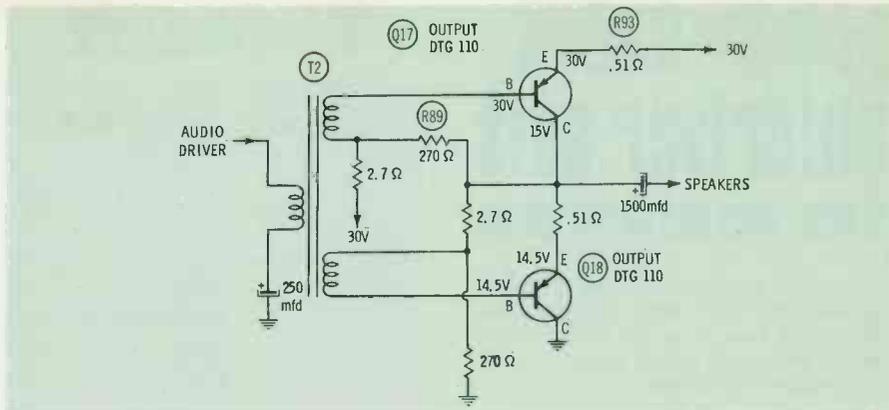


Fig. 7. Shorted transistor and burned resistors caused extreme distortion and low volume.



USERS CAN'T BE WRONG!

Technicians everywhere rely on famous Sencore Mighty Mites. Here's why.

- Grid Leakage Test with ultra-high sensitivity of 100 megohms
- Emission Test at full rated cathode current
- Shorts Test picks out interelement shorts of 180K ohms or less
- Mighty Mite accurately checks over 3,000 tubes, including foreign.



**NEW
MIGHTY
MITE
V
TC142**


Now, Sencore's new Mighty Mite V gives you the same reliability and accuracy, plus new features that make the "V" the most up-to-date tester of all.

- NEW—Magnoval socket so you check many more tubes.
- NEW—Horizontal in-line switch layout saves setup time.
- NEW—Rugged vinyl-clad steel case stays new longer.
- NEW—Brushed chrome panel; detachable cover.

The new TC142 is truly Sencore's mightiest Mighty Mite and it's still only

\$74.50

IN STOCK AT YOUR DISTRIBUTOR NOW.

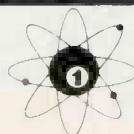

SENCORE

NO. 1 MANUFACTURER OF ELECTRONIC MAINTENANCE EQUIPMENT

426 SOUTH WESTGATE DRIVE, ADDISON, ILLINOIS 60101

Circle 17 on literature card

color coded nutdriver sets in new "keep and carry" cases

Sturdy plastic cases keep nutdrivers in order on the workbench. Tight fitting, snap-lock covers protect tools when not in use, permit carrying them on service calls without danger of spilling or becoming lost in tool box.



No. HS-6-18
HOLLOW SHAFT
NUTDRIVER SET

10 Hex Openings: $\frac{3}{16}$ ", $\frac{7}{32}$ ", $\frac{1}{4}$ ", $\frac{9}{32}$ ", $\frac{5}{16}$ ", $\frac{11}{32}$ ", $\frac{3}{8}$ ", $\frac{1}{2}$ ", $\frac{5}{8}$ ". Yellow, slipover cover case.



No. 77
DRILLED SHAFT
NUTDRIVER SET

7 Hex Openings: $\frac{3}{16}$ ", $\frac{7}{32}$ ", $\frac{1}{4}$ ", $\frac{9}{32}$ ", $\frac{5}{16}$ ", $\frac{11}{32}$ ", $\frac{3}{8}$ ". Hole depth $\frac{1}{4}$ ". Black, pebble grain, hinged cover case.

professional quality

Precision fit, case-hardened sockets, polished and plated steel shafts; shockproof, breakproof, color coded plastic (UL) handles.

WRITE FOR BULLETIN N567



XCELITE, INC., 18 Bank St., Orchard Park, N.Y. 14127
In Canada contact Charles W. Pointon, Ltd.

Circle 18 on literature card

RC CIRCUITS

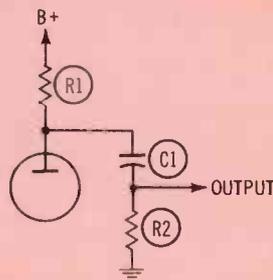


Fig. 1 shows a typical RC coupling circuit that might be used between almost any two audio or video amplifiers. In most cases, this circuit is designed to couple the signal with a minimum of distortion, although it may be designed to change the shape of the signal waveform in some applications. The effect of the circuit on the waveform is determined by the values of R2 and C1 so long as the impedance of these two components is great with respect to R1.

Let's assume that R1 is 20K ohms so that it is small with respect to R2 and will not affect the circuit. If C1 is .01mfd and R2 is 1 megohm, the RC time constant of the coupling circuit is .01 second. RC time = R (in ohms) X C (in farads) = time (in seconds). Assume the input to be a square wave whose width is more than 5RC. The voltage at the junction of R2 and C1 will be 37% of the applied voltage at the end of 1RC time.


At the end of 2RC time, the output will have dropped to 37% of its value at the end of 1RC time, or about 14% of the applied voltage. The output will continue to decay at this exponential rate, and it may be considered to have reached 0 at the end of 5RC time. In our example, the output would be 0 at the end of .05 second.

To couple without distortion, the RC time constant should be at least 10 times the duration of the widest pulse that has to be passed by the circuit. Thus, in our circuit, the maximum pulse width which can be coupled has a width of .001 second. At the end of 1/10 RC time, the output will have fallen to about 90.7% of the input level. ▲

Speedy TUNER REPAIR

FAST SERVICE

ONE YEAR WARRANTY

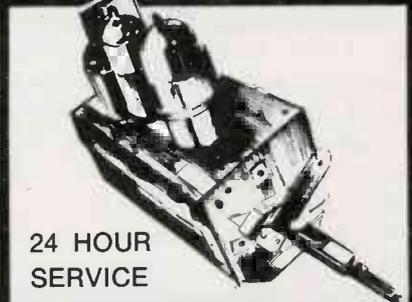

24 HOUR
SERVICE

COLOR • UHF • VHF

\$950 (\$14.50 COMBO)
COMPLETE

Includes all parts
(except Trans. & Tubes)

We are new in name only—
Behind every tuner repair is
15 yrs. of experience. Our base
price is compatible with other
companies, but the extra service
and high quality workman-
ship makes our service cheaper
in the long run. Send the defect-
ive tuner with all parts, in-
clude tubes, make, model No.
and complaint. Pack well and
insure. All tuners returned
C.O.D. unless accompanied by
an open check. (Dist. write for
price structure)



SUPERIOR TUNER SERVICE

1377 N. CURRY PIKE
BOX 368

Bloomington, Indiana 47401

Circle 19 on literature card

Industry Demanded - only Sencore delivered

AN ALL NEW IMPROVED COLOR CRT TEST



**Simple - Fast - Accurate • Automatic Color Tracking!
No Time-Wasting Logging and Computing!**


CRT manufacturers, set manufacturers, distributors, technicians — all demanded a better CRT tester than any available. This is it — the new Sencore CHAMPION — a winner on every count.

Separate G2 screen grid controls, just like the color circuit itself, enable you to set up each color gun, then automatically compare it with the others for tracking — exactly according to industry standards. This check is important when claiming credit for a defective color CRT. No time consuming logging of each color gun reading at every setting of the G2 control like competitive models. It's automatic with the CR143 Champion.

The CHAMPION also makes all the standard color and black and white CRT tests — shorts, emission, and life tests. Its Line Adjust control assures exceptional accuracy. Its exclusive three step Automatic Rejuvenation Circuit lets you save many a faulty black and white tube or equalize gun currents in color tubes.

The all-new CHAMPION is equipped with plug-in sockets for fast testing and easy updating. Rugged vinyl-clad steel case has spacious lead compartment.

For a sure thing, put your money on the champion — the Sencore CR143 CHAMPION.

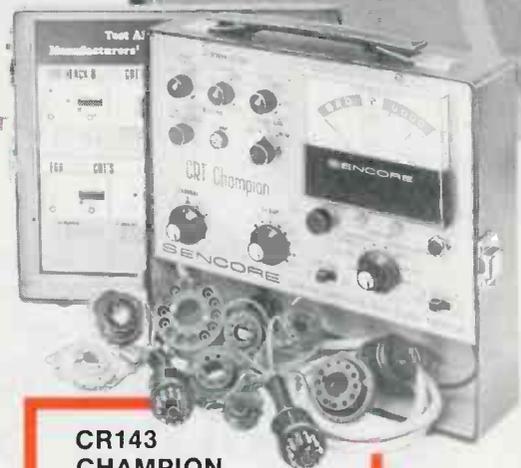

**CR143
CHAMPION**



\$9950




SENCORE

NO. 1 MANUFACTURER OF ELECTRONIC MAINTENANCE EQUIPMENT
426 SOUTH WESTGATE DRIVE, ADDISON, ILLINOIS 60101

Circle 20 on literature card

October, 1967/PF REPORTER 39

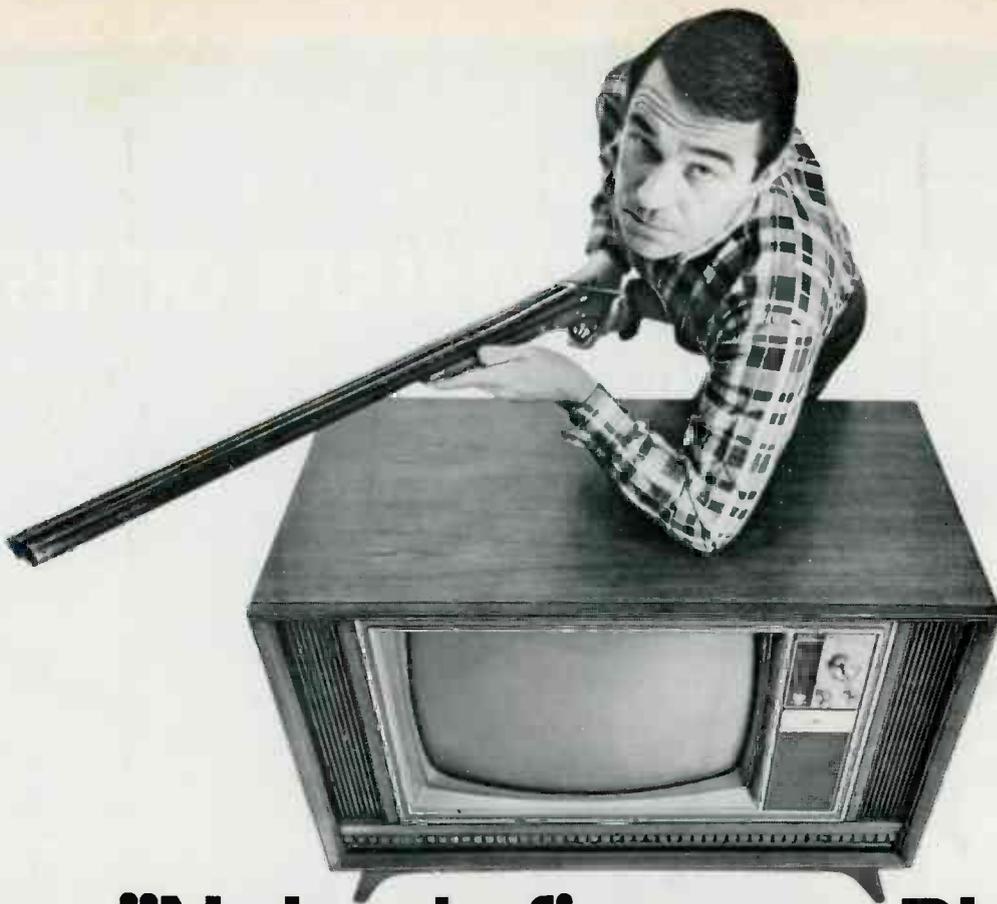

“Nobody fixes my Philco but a Philco technician!”

That color TV cost him \$500 and he wants a real specialist to fix it! Why don't you become the specialist? Give Philco Qualified Service and get the business.



Your service technicians can get all the training they need right there in your area. Local training meetings are held all over the country. Then, after the course, our Tech Data

Service keeps them tuned in to what's new. And you get the fastest parts delivery in the industry. Philco

Parts Distributors stock almost every part you'll ever need. Any part they don't have will be on its way to you by air within 24 hours through our Lifeline Emergency Service.

Get new customers — more business. Your shop can appear in our Yellow Pages listings, and you become your area headquarters for Philco Service. There's plenty of attractive identification material wherever your firm name is used.

Philco owners are sold on the idea of specialist service. Shouldn't you be? Your local Philco-Ford Distributor will give you all the details. Call him now and ask for the Service Manager.

Philco-Ford Corporation
Philadelphia, Pa. 19134



Circle 21 on literature card

BOOK REVIEW

Single Sideband: Theory and Practice: Harry D. Hooten, W6-TYH; Editors and Engineers, Ltd., New Augusta, Ind. 1967; 352 pages, 8¾" × 5¾", hard cover; \$6.95.

This text treats the subject of single sideband in a manner that will be easily understood by both the technician and engineer. Basic principles and circuitry are emphasized, while mathematics is used only when needed to clarify or expand a point. Wherever possible, specific commercial equipment of current design is used to explain theory and illustrate circuit applications.

The origin of single sideband is the first item discussed (Chapter 1) and is followed by an analysis of the single-sideband signal (Chapter 2). Chapters 3 through 6 examine the techniques and circuits involved in the actual development of the single-sideband signal. These include carrier generation, speech amplifiers and associated filters, carrier suppression, and sideband selection. After being examined on an individual basis, the circuits and techniques are combined in Chapter 7 to form the single-sideband generator. Both the filter and phase-shift type generators are discussed. The process of converting the low-frequency signal to the desired transmission frequency is found in Chapter 8.

The features and characteristics of specific low-power transmitters are analyzed in Chapter 9. The function and design considerations of linear RF power amplifiers are the subjects of Chapter 10. Specific models of receivers and transceivers are presented in Chapters 11 and 12. The final Chapter is concerned with tests and measurements. ▲

NO MORE GUESSWORK!




AMERICA'S MOST RELIABLE TUBE ANALYZER

You don't need three guesses to tell if a tube is bad — or why. With the new Sencore MU140 Continental, you know. Right now. And you simply can't go wrong. Because it's a complete tube analyzer for 4-way testing — true mutual conductance (using exclusive 5000 hertz square wave), full cathode emission, 100 megohm grid leakage, and internal shorts. Tests all tubes, including foreign — over 3000 in all. Obsolescent-proof, too — with "new socket" panel, and controls so standard the switch numbers correspond to the pin numbers in any tube manual.

If it's reliability you want — for years to come — you need the Continental. It's the best way to be sure —

for only
\$179⁵⁰

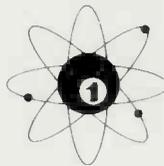See America's most complete line of professional test instruments — at your Distributor now.



SENCORE

NO. 1 MANUFACTURER OF ELECTRONIC MAINTENANCE EQUIPMENT

426 SOUTH WESTGATE DRIVE, ADDISON, ILLINOIS 60101

Circle 22 on literature card

MOVING?

Don't lose touch . . .
RECEIVE PFR AS USUAL
(INCLUDE OLD AND NEW ADDRESS)

PF REPORTER
CIRCULATION DEPT.
4300 W. 62nd St.,
Indianapolis, Ind. 46206



SYLVANIA

SYLVANIA
RADIO
TV
SERVICE

BRIGHT
GUY

Are you eligible for the Bright Guy Awards?

It's easy to get them—and to get all the business they'll bring you. New customers. More sales. More money.

The Bright Guy Awards is the big program Sylvania's running this year to boost your sales.

Your Sylvania distributor can put your name and address in TV Guide in your own area. These Sylvania ads will call you "the brightest serviceman in town"—and tell people in your town why they should call you.



You'll get into the Yellow Pages, too, under the heading "TV Service and Repairs."

Once again this year you'll be eligible for over



one hundred valuable, interesting SMB-Bright Guy gifts, just for buying the Sylvania TV replacement parts you normally buy anyway.

And you'll get window displays proclaiming you "the brightest"—the TV serviceman everyone's reading about.


You're eligible for the Bright Guy Awards just by buying Sylvania's famous *color bright 85*[®] color picture tube. And our other picture tubes, and our receiving tubes. So see your Sylvania distributor.



Sylvania Electronic Tube Division, Electronic Components Group, Seneca Falls, New York 13148.

SYLVANIA
SUBSIDIARY OF
GENERAL TELEPHONE & ELECTRONICS **GTE**

Circle 23 on literature card

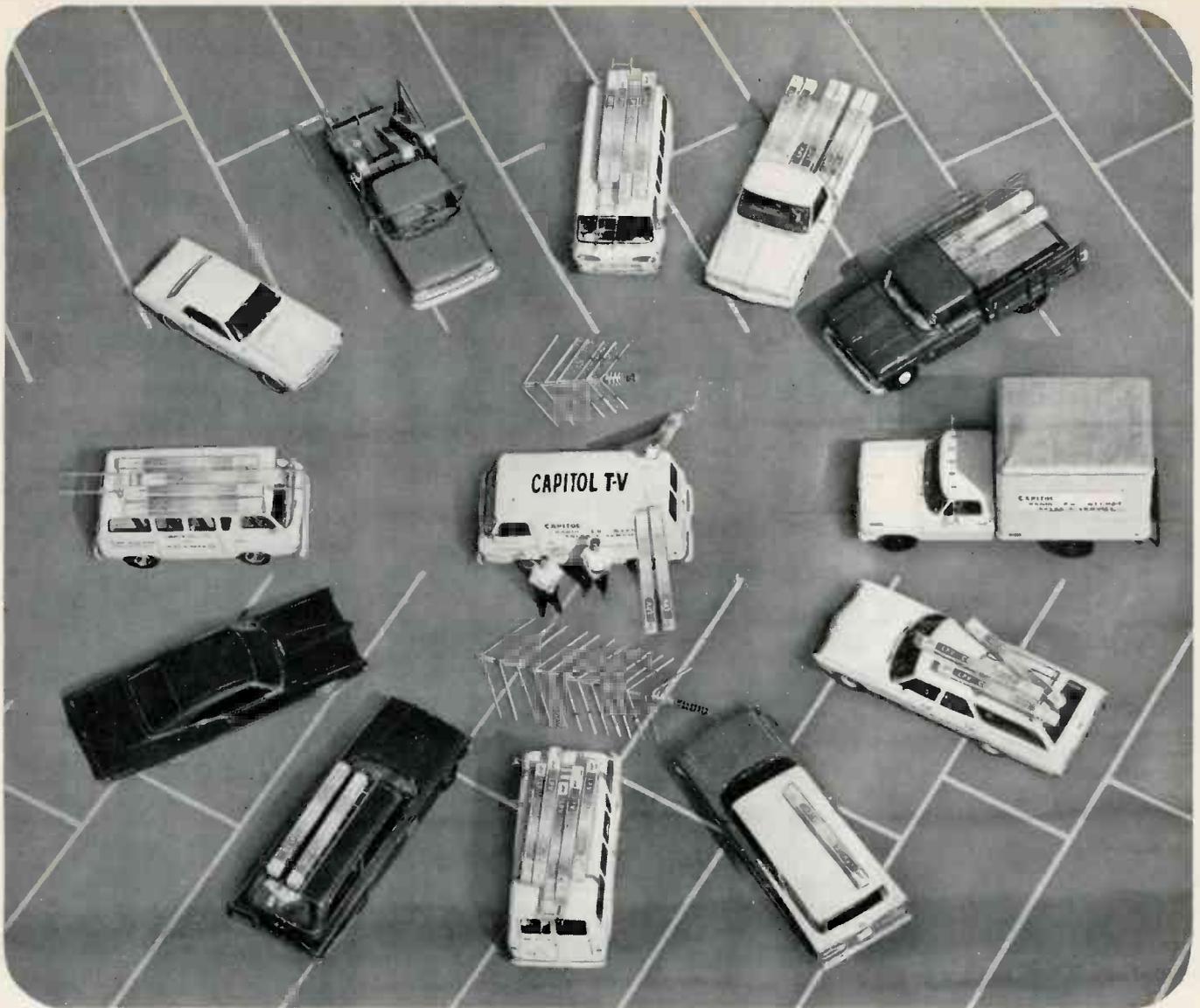


"When you guarantee finer color pictures...

... like we do, you *better* deliver!" says George Comer and Bob Garrison, of Capitol TV Sales and Service, Atlanta, Georgia.

"We install antennas for many dealers, retailers, chains and department stores here in the Atlanta area. They look to us to give their customers the fine color reception their customers were guaranteed when they bought their sets. We make sure we deliver the best possible color pictures by installing JFD Color Lasers.

"Before using Color Lasers, we installed VHF LPV Log Periodics. Frankly, we didn't think a combination 82-channel antenna would work so well across the VHF, UHF and FM bands. But the Color Laser is proving it to us where it counts — in happy customers and protected profits."

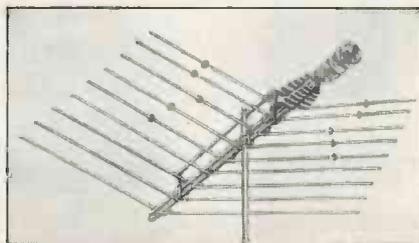George Comer and Bob Garrison know from experience—like other professionals



— that JFD Color Lasers come through with the superb reception people expect from a professional service company.

Only Color Lasers offer:

BRILLIANT COLOR — flat (frequency independent) response across each channel, free from suck-outs or roll-off. Keeps colors vivid and alive.

PATENTED W-I-D-E BAND LOG PERIODIC DESIGN — the most efficient ever developed — provides higher gain, better

signal-to-noise ratios, needle-sharp directivity. Eleven patents cover its revolutionary space-age design.

MORE DRIVEN ELEMENTS. Harmonically resonant capacitor coupled design makes dual-function elements work on both VHF and UHF frequencies. *Entire* antenna (not just part of it as in other log periodic imitations) responds on every channel.

LUSTROUS, ELECTRICALLY CONDUCTIVE GOLD ALODIZING promotes signal transfer, protects against corrosion, enhances appearance.

The Best Antenna for Color TV is The Color Laser by

JFD®

Now at your JFD distributor!

JFD ELECTRONICS CO. 15th Avenue at 62nd Street, Brooklyn, N.Y. 11219

JFD International, 64-14 Woodside Ave., Woodside, N.Y. 11377 JFD Canada, Ltd., Ontario, Canada

JFD de Venezuela, S.A., Avenida Los Haticos 125-97, Maracaibo, Venezuela

LICENSED UNDER ONE OR MORE OF U.S. PATENTS 2,958,081; 2,985,879; 3,011,168; 3,108,280; 3,150,376; 3,210,767, RE. 25,740 AND ADDITIONAL PATENTS PENDING IN U.S.A. AND CANADA. PRODUCED BY JFD ELECTRONICS CO. UNDER EXCLUSIVE LICENSE FROM THE UNIVERSITY OF ILLINOIS FOUNDATION. LICENSED UNDER ONE OR MORE OF U.S. PATENTS 2,955,287 AND 3,015,821 AND ADDITIONAL PATENTS PENDING.

Circle 24 on literature card

THE TROUBLE-SHOOTER

Poor Vertical Sync

We have a Zenith chassis 14M21/X (PHOTOFACT Folder 764-4) with poor vertical sync. I have measured the voltages at V5, the sync separator, AGC, and noise canceller tube. The table below shows the results and also the correct voltages taken from the PHOTOFACT Folder.


Pin No.	Measured	Correct
2	85	103
3	10	13
6	-10	-17
7	-.4	-.9
8	75	54
9	-35	-3

The resistance readings are normal except that the resistance from pin 3 to the B+ source is only 1.4 megohms. R13 was disconnected and it measures 6.8 megohms. With it disconnected, pin 3 to B+ reads 1.7 megohms.


I would appreciate any comments you can make concerning these voltage and resistance readings. Also, I would like to know if the voltage and resistance readings shown on the PHOTOFACT Folder are actual readings made by your technicians.

C. H. ALEXANDER

Ebensburg, Pa.

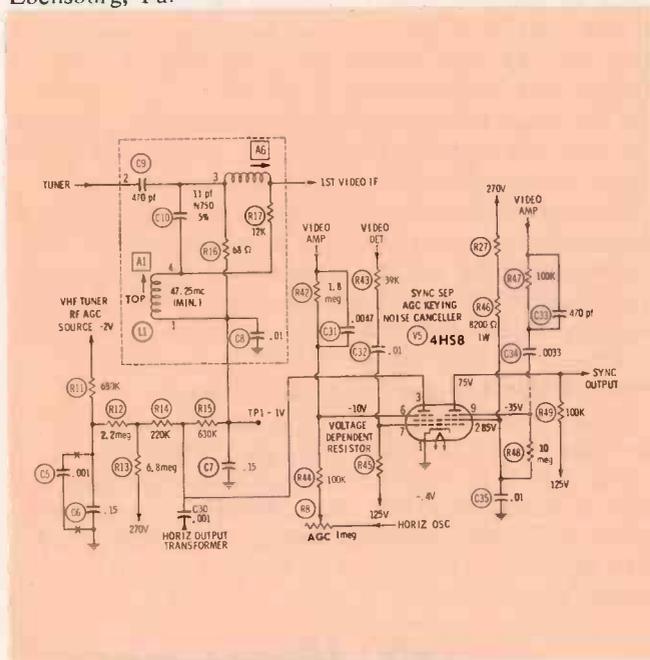

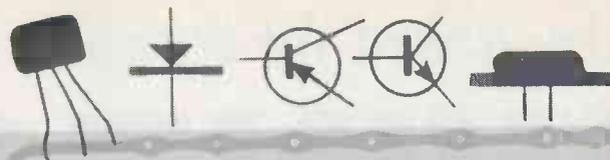You are correct in assuming that the resistance readings shown in the PHOTOFACT Folder are taken by our staff. Incidentally, the voltage, waveform, and alignment data are also derived from actual measurements and adjustments made by our technicians using accurately cali-



TEST TRANSISTORS IN SECONDS in circuit



Also check all transistors, diodes, and rectifiers out of circuit for true AC beta and Icbo leakage.

Your best answer for solid state servicing, production line testing, quality control and design.

Sencore has developed a new, dynamic in-circuit transistor tester that really works—the TR139—that lets you check any transistor or diode in-circuit without disconnecting a single lead. Nothing could be simpler, quicker or more accurate. Also checks all transistors, diodes and rectifiers out of circuit.

BETA MEASUREMENTS—Beta is the all-important gain factor of a transistor; compares to the gm of a tube. The Sencore TR139 actually measures the ratio of signal on the base to that on the collector. This ratio of signal in to signal out is true AC beta.

ICBO MEASUREMENTS—The TR139 also gives you the leakage current (Icbo) of any transistor in microamps directly on the meter.

DIODE TESTS—Checks both rectifiers and diodes either in or out of the circuit. Measures the actual front to back conduction in microamps.

COMPLETE PROTECTION—A special circuit protects even the most delicate transistors and diodes, even if the leads are accidentally hooked up to the wrong terminals.

NO SET-UP BOOK—Just hook up any unknown transistor to the TR139 and it will read true AC beta and Icbo leakage. Determines PNP or NPN types at the flick of a switch.

Compare to laboratory testers costing much more. . . . \$89.50

See America's Most Complete Line of Professional Test Instruments — At Your Distributor Now.


NO. 1 MANUFACTURER OF ELECTRONIC MAINTENANCE EQUIPMENT
SENCORE
 426 SOUTH WESTGATE DRIVE, ADDISON, ILLINOIS 60101

Circle 25 on literature card

You asked for it, waited for it and now here it is!


WINEGARD ULTRA-[®]PLEX

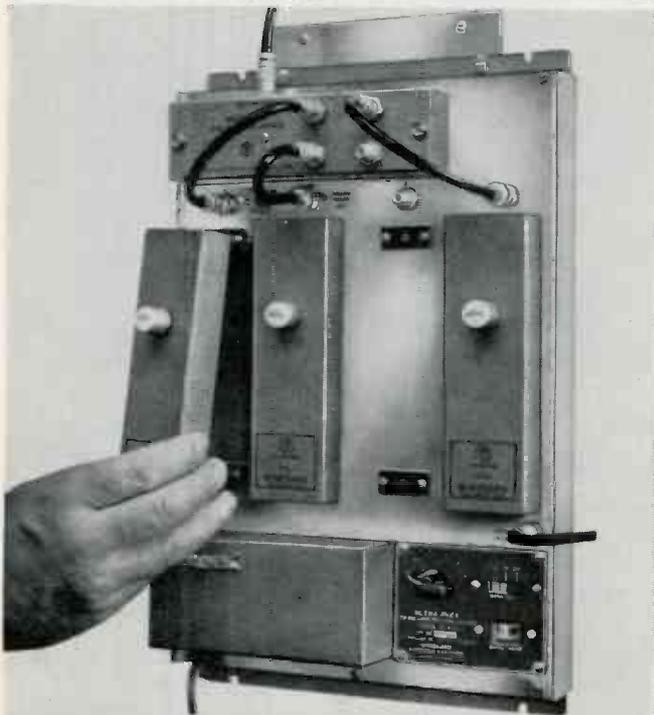The first 82-channel, solid state MATV color distribution system!



82-Channel Ultra-Plex System
using 10 band plug-in VHF amplifier
... hi band plug-in VHF amplifier...
and broad band UHF amplifier.

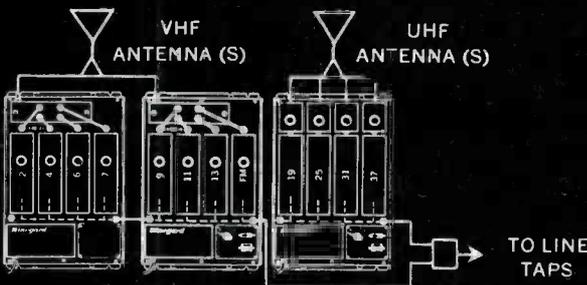82-Channel Ultra-Plex System
using single channel plug-in amplifiers.



Winegard Ultra-Plex is a unique 82-channel, modular plug-in distribution system with all components matched to work together perfectly. The system never becomes obsolete, because you can add new LHF or VHF channels quickly, easily and inexpensively whenever needed.

Now you can have complete signal control of each channel!

- Amplifies! ■ Equalizes!
- and Feeds any number of channels to any number of tv sets —with a minimum of labor and equipment—and at a cost that's actually lower than most "VHF ONLY" systems!

For use in homes, as well as in the largest apartment buildings, hotels & motels, hospitals, etc.

Sensational Winegard **Ultra-Plex** is the best thing to ever happen to MATV system installers. Because **Ultra-Plex** gives the installer unprecedented flexibility regardless of system size. Because **Ultra-Plex** covers the full range of UHF, VHF and FM frequencies.

And because **Ultra-Plex** is super compact...installs easier than old fashioned equipment...costs less...and operates inexpensively with little or no maintenance.

Plenty of other reasons, too. **Ultra-Plex** incorporates your choice of either single channel or broad band solid state amplifiers that plug into the modular power panel. **Ultra-Plex** is totally designed with all the components needed to solve every conceivable distribution system problem. And **Ultra-Plex** equipment is manufactured to the highest commercial standards of quality—second to none.

If you are now installing MATV systems, you'll want to know more about profitable Winegard **Ultra-Plex**. Or if you've wanted to get into the booming MATV business, but thought it too complicated, let us show you exactly how easy and profitable it is. Write for Fact Finder #246 today. It gives you all the facts on MATV systems in general, and **Ultra-Plex** in particular.

 **Winegard**
ANTENNA SYSTEMS

WINEGARD COMPANY • 3000 KIRKWOOD STREET
BURLINGTON, IOWA 52601

© Copyright 1967, Winegard Company, Burlington, Iowa

braided equipment.

There are several bleeders from B+ to ground and the total DC resistance is about 34K ohms. Thus, if either C7 or C8 were leaking, the resistance from pin 3 of V5 to B+ could drop to the value you measured. If C5 or C6 were leaking, the resistance would be somewhat higher unless, of course, R12 had changed value. C9 or C30 leaking also could cause a low-resistance path to B+.

The increase in voltage at pin 2 of V5 is probably caused by a decrease in value of either R46 or R27. After you have corrected this problem, you will probably find the voltage at pin 9 to be normal.

The increase in negative voltage at pin 7 indicates that R45 has increased in value. When you have corrected the two other faults, you may find that the set has good vertical sync. Even so, don't risk a call-back; change R45 if the voltage is abnormal.

Tuning Trouble

I have had the same problem with several Satchell-Carlson receivers which were manufactured about 10 years ago. When I adjust the fine tuning control, just as I tune from the "sound side" to where a clear picture should appear, a wavy pattern appears. This pattern changes as I adjust the fine tuning.

Originally, I thought this might be a fault in one make of tuner, but now I have had the same problem with two different makes of tuner. I sent one tuner to a repair service and it worked properly when it was returned. If you know a solution to this problem, I would appreciate your help.

LEONARD W. BAUMAN

Woodruff, Wis.

Since your problem is of a general nature, here are some suggestions which are also of a general nature.

1. Be sure the output of your sweep generator is properly terminated and also matched to the receiver input.
2. Keep the leads of this matching network as short as possible. The unshielded leads should be no more than 1 inch long.
3. Make sure the detector probe and cable is well shielded and keep the unshielded leads as short as possible.
4. Make sure the output of your sweep generator is flat. If it has a "notch" in its output, you may be peaking the tuner response during alignment to compensate for it.
5. Be certain that bias on the tubes is the same during alignment as it is in normal operation. Use a well-regulated, filtered bias supply.
6. Be careful of lead dress and lead positions both during alignment and after the set is put back in the cabinet. If lead position changes the response curve during alignment, find out why and correct the trouble.
7. Keep the shields in place to prevent a change in the response curve when you replace them.

Vertical Roll

A Zenith Chassis 14L20 (PHOTOFACT Folder 711-4) displays a vertical roll after about one hour of operation. I have recently replaced the yoke with a Triad Y-83-1. All scope patterns seem normal. The trouble has not been

Swingin'
Combo
for
Top
Performance!




NEW SENCORE SM112B SERVICE MASTER VTVM/VOM

Here it is—the third generation of Sencore's famous Service Master—the two-in-one professional instrument that saves your time, speeds your service work, puts extra profits in your pocket.

- Just one function switch, one range switch and one probe provide all functions of VTVM and VOM.
- Voltage, current and resistance in 33 ranges — for accurate measurements anywhere, anytime.
- VTVM operates from 115v AC for precise bench or lab work; battery powered VOM gives you a 5000 ohms per volt meter.
- Lighted arrows automatically indicate VTVM scales.
- Large, easy-to-read 6-inch two percent meter covers all measurements.
- Handsome new styling in tough, vinyl-clad steel case.
- Optional high voltage probe attaches for measuring up to 30,000 volts DC.

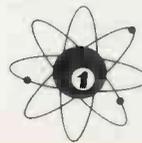So why use two when one will do—the new Sencore SM112B. Truly professional quality, and still only **\$89.95**
High Voltage Probe HP118 **\$7.95**



SENCORE

NO. 1 MANUFACTURER OF ELECTRONIC MAINTENANCE EQUIPMENT
426 SOUTH WESTGATE DRIVE, ADDISON, ILLINOIS 60101

Circle 27 on literature card

October, 1967/PF REPORTER 47

Don't let Money-Making Technical Advances Pass You By!

RCA Institutes offers these four comprehensive home study courses especially designed to help build your income immediately:

COLOR TV

Take advantage of the growing profit potential in this area. Add color TV to your skills with this home training course, newly revised to include information on the latest techniques, receiver circuitry and equipment. Train under the direction of RCA Institutes... experts in Color TV home study training.




SOLID STATE ELECTRONICS

You get the necessary background for semiconductor technology including characteristics of tunnel diodes, rectifiers and other solid state devices. Transistor trainer also available.



AUTOMATION & INDUSTRIAL ELECTRONICS

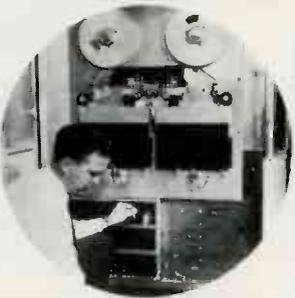Trains you for the many applications of automation electronics in industry and government including Photoelectronics, Digital Techniques, Synchros and Servomechanisms, Automatic Control Systems, Nuclear Instrumentation and many more!



COMMUNICATIONS

Trains you to service and maintain 2-way radio communications on land, sea and air! Gives you the technical foundation for space communications.

You have no long-term obligations with RCA Institutes Liberal Tuition Plan. You only pay for lessons you order. Licensed by New York State Education Department. Approved for veterans.



Send this coupon now for complete free information



RCA INSTITUTES, INC.

Home Study School, Dept. PF-07
350 West Fourth Street, N.Y., N.Y. 10014

Without obligation rush me free information on the following RCA Home Training Course: COLOR TV _____ SOLID STATE _____ COMMUNICATIONS _____ AUTOMATION & INDUSTRIAL ELECTRONICS _____

Name _____

Address _____


City _____ State _____

IN CANADA - The RCA Victor Company, Ltd.

cured by changing every resistor and capacitor in the vertical oscillator and output stages. The vertical blanking bar rolls within 2" of the bottom edge and stays there until the vertical hold is adjusted. It will lock back in sync for about 15 minutes and then the same symptom occurs again. The picture cannot be centered without a black area at the bottom of the screen. The vertical hold does not seem to have much variation. Could the new yoke be defective and if so, would it cause the trouble I have described.

EUGENE N. SPETTER

Rossville, Kans.

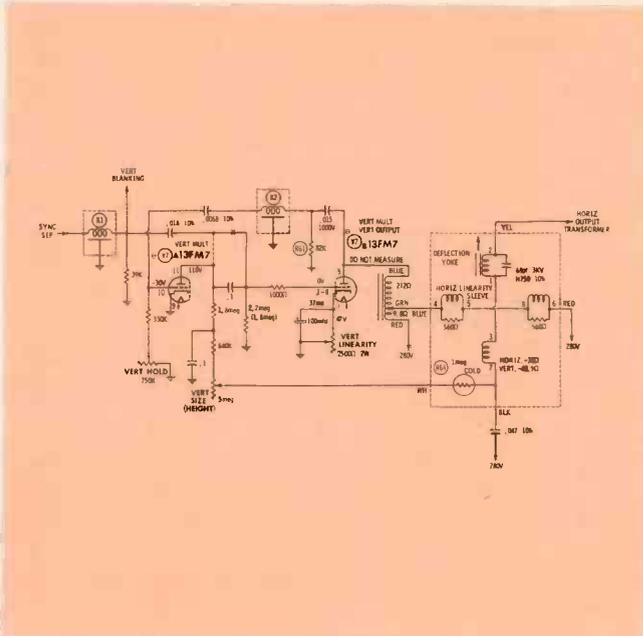

Weller®

**makes first class
soldering the easiest
part of any job**



NEW Weller
**BATTERY OPERATED
Iron for field servicing**

Now get controlled 700°F tip temperature from a battery! Lightweight TCP-12 iron features Weller's patented "Temperature Sensing" system, clips to any 12-volt battery or 12-14 volt AC/DC source. Also available for 24-28 volt operation (Model TCP-24). A must for mobile communications work.

**Efficient MARKSMAN Irons
for continuous-duty soldering**



Ideal for the bench or caddy, Marksman irons outperform others of the same size and weight. Five models feature long-reach, stainless steel barrels and replaceable tips.

- 1¼-oz, 25-watt Model SP-23
- 4-oz, 80-watt Model SP-80
- 2-oz, 40-watt Model SP-40
- 10-oz, 120-watt Model SP-120
- 16-oz, 175-watt Model SP-175



**Dual Heat
Soldering Guns for
dependable maintenance
and repair**

The most widely used gun in the electronics field. Available in three wattage sizes, each with Weller's exclusive trigger-controlled dual heat, pure copper tip, and spotlight.

- 100/140-watt Model 8200
- 145/210-watt Model D-440
- 240/325-watt Model D-550

**25-watt Technician's Iron
for intricate circuit work**




Industrial rated pencil iron weighs only 1¼ ounces, yet delivers tip temperatures to 860°F. Cool, impact-resistant handle. All parts readily replaceable. Model W-PS with ⅛-inch tapered tip.

Complete Weller Line at your Electronic Parts Distributor

WELLER ELECTRIC CORPORATION, Easton, Pa.
WORLD LEADER IN SOLDERING TECHNOLOGY

Circle 29 on literature card

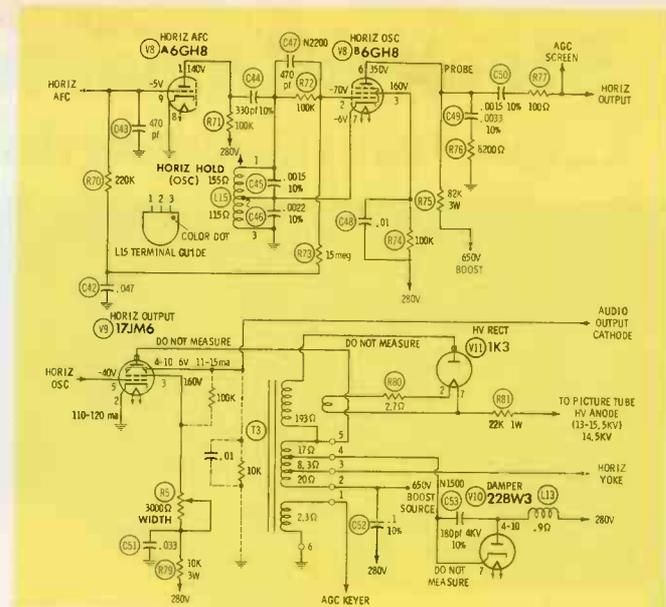

from another set, or some other source, inject a drive signal at the horizontal output grid. If high voltage, boost, and raster return, you can be fairly certain the trouble is in the horizontal AFC or horizontal oscillator. However, if high voltage, boost, and raster do not return, the trouble is probably in the horizontal output, high-voltage, or damper circuits.

If the foregoing procedure indicated trouble in the stages preceding the horizontal output grid, you can localize the trouble even further by grounding the grid of the horizontal AFC stage. High voltage, boost, and raster should return if the defect is in the AFC circuit. Once the trouble is localized to the AFC or horizontal oscillator circuit, voltage and resistance checks will isolate the actual defect.

If injecting a drive signal at the horizontal output grid did not restore high voltage, boost and raster, the trouble, as noted before, must be located in the horizontal output, high-voltage, or damper circuits. Although there are a number of sequences that can be followed in troubleshooting these circuits, probably the quickest is to first check the most logical suspects. Begin with the boost capacitor (C52). There are a couple of effective methods you can apply here, such as substitution or removing the damper tube (jumper across damper filament because of the series filament string), which should restore high voltage and a narrow rippled raster if C52 is shorted. If C52 is not defective, disconnect the yoke leads while monitoring the boost voltage. If boost is restored or greatly increased with the yoke disconnected, a defect in the yoke has been causing an excessive load on the system. Next, measure the screen grid voltage on the horizontal output tube. An open or increase of R79 could disable this stage.

Another possible cause of no high voltage is a defective CRT. Remove the high-voltage lead to the CRT anode and see if high voltage and raster are restored.

At this point you have eliminated nearly all suspects (it is assumed all tubes and B+ were checked as preliminary procedure) except the flyback itself. A flyback checker can be used to check this component; however, it cannot be considered an absolute indication of a good or bad flyback unless all other circuits have been previously tested or have been disconnected before the flyback is tested. Also, some flyback defects will show up only while the flyback is connected in the circuit and operating. It is generally conceded that the best check of a flyback is substitution after all other possible circuit defects have been eliminated. Of course, the foregoing is true only if there are no visible signs that the flyback is defective, (melted wax, etc.). ▲

Join the PHOTOFACT[®]-OF-THE-MONTH Club

and receive each and every month

THE WORLD'S FINEST TV-RADIO SERVICE DATA

Complete up-to-the-minute coverage • Save over \$60 per year!

Howard W. Sams now offers this great new monthly package exclusively for P.O.M. members!

You get your 6 new PHOTOFACT Sets every month in sturdy new file folders sealed in factory carton to insure perfect condition and completeness—easier-than-ever to file and use. Now—only \$10 per month and you get 20% MORE COVERAGE!

NOW! more current model coverage each month to keep you ahead earning more—
AND YOU SAVE OVER \$60 PER YEAR!

As a PHOTOFACT-OF-THE-MONTH CLUB member, you get 6 new PHOTOFACT Sets every month—the world's finest TV-radio service data—with all the time-saving, profit-boosting help you want!



AT LEAST 6 COLOR TV FOLDERS MONTHLY

NOW! ONLY \$10 PER MONTH brings you 20% MORE PHOTOFACT[®] coverage!

complete current coverage of at least 50 chassis each and every month for less than

20¢ per chassis model!

To stay ahead, to save money (individually purchased sets now sell for \$2.50 each)—join the PHOTOFACT-OF-THE-MONTH CLUB now!

see how PHOTOFACT boosts your earning power!

SUBSCRIBE TODAY THROUGH YOUR SAMS DISTRIBUTOR OR USE THIS HANDY ORDER FORM

TRY A THREE-MONTH P.O.M. SUBSCRIPTION

HOWARD W. SAMS & CO., INC. Dept. PFF-10
4300 W. 62nd St., Indianapolis, Ind. 46268

Enroll me for a 3-month membership in the Photofact-of-the-Month Club. I agree to pay \$10 per month, and understand I will receive 6 current Photofact Sets monthly for 3 months to be delivered by my Sams Distributor (named below).

Name _____


Shop Name _____

Address _____

City _____ State _____ Zip _____

My Sams Distributor is: _____

Signed: _____

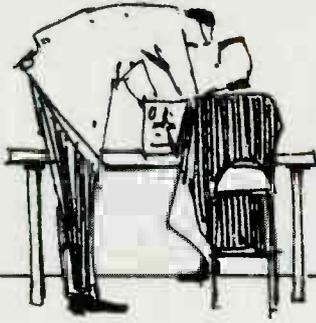

Protect your business from these credit abuses

by Ernest W. Fair

Proper handling can reduce the risks involved in extending credit. The following article outlines the correct procedures to follow, both before and after an account is opened.

Well over half of today's business is transacted on a credit basis. That percentage grows every year, and soon may be near universal. As credit expands, so do the hazards involved. The very life of any electronic service business may well depend on how adequately it is protected against abuse of this credit.

In past years, improper and hap-

azard operation of credit has accounted for as high as 65% of small business failures. While some losses can be attributed to lax procedures in granting credit, this problem has been decreasing during the past five years due to better education on procedure and greater availability of checking agencies. During the past year several surveys have re-

vealed this decline but also pointed up an alarming increase in losses through abuse of credit.

We've carefully studied several such reports, as well as surveys on the subject. In paragraphs to follow is a list of the top ranking credit abuses which were responsible for fully 90% of these losses. With each is shown recognized and proven


Why not sell the best

ZENITH TUBES built to the quality standards of Zenith original parts

"Royal Crest" Circuit Tubes

More than 875 tubes—a full line with the same quality as original Zenith equipment. Get Zenith tubes for greater dependability and finer performance.

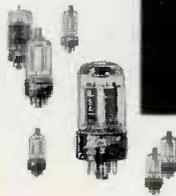Order all genuine Zenith replacement parts and accessories from your Zenith distributor.



TV Picture Tubes

For color TV, B&W TV or special purposes. A complete Zenith line of more than 200 tubes built for greater reliability, longer life.

Zenith B&W replacement picture tubes are made only from new parts and materials except for the glass envelope in some tubes which, prior to reuse, is inspected and tested to the same high standard as a new envelope. Some color picture tubes contain used material which, prior to reuse, is carefully inspected to meet Zenith's high quality standards.

ZENITH®

The quality goes in before the name goes on

Circle 31 on literature card

steps to avoid damage to the business. Following these steps should be a "must" procedure to assure a profitable year of business.

Changes in credit status. Yesterday's well-rated customer can, through all sorts of circumstances, become a dangerous risk tomorrow. Failure to watch over the continuing credit status of major customers is always a hazardous procedure.

Preventive: Periodically survey account status of all customers. Watch carefully any account which has become slower and slower in making payments over any past three-month period.

"Softness" in collection procedure. One is always tempted to grant the good credit account some extra concessions. Too often this leads to a major loss.

Preventive: Strict adherence to conventional credit terms at all times is a must. Extension of such terms in cases of genuine emergency are justified only on a short-term basis.

Mistakes or errors in bookkeeping. Failure to charge the proper account, and errors in transcription of invoice or sales slips to account ledgers are the two most common mistakes in this area.

Preventive: A well developed system for handling the paper work for all charges and a constant check of employees to see that this is being followed does the job. Avoid "hurry and rush" in handling these steps.

Laxity in follow-up on delinquent accounts. There should be no exceptions regardless of how good the customer involved may be. Carelessness in handling delinquent accounts invariably leads to greater delinquency.

Preventive: Establish a definite procedure to follow and use it on every account without exception. Never wait more than 30 days to put it into use.

**"I was TROUBLE-SHOOTING
in the DARK 'til Sencore's Scope
Showed Me What Color Waveforms
Really Look Like."**

Only
199⁵⁰



**PS 127 5" WIDE BAND
OSCILLOSCOPE**

Technicians everywhere are talking about the PS127 5" Wide Band Oscilloscope. Try one and you, too, will send us comments like these—

"So easy to use! With my Sencore scope I can read high or low frequency signals without band switching. As easy to use as a voltmeter."—R. L., Portland, Ore.

"I've only had my PS127 a couple of months, but it's more than paid for itself already with the extra jobs I've been able to handle."—S. O., New Orleans, La.

"With the direct peak-to-peak readout I can compare voltage readings to those on the schematic without wasting valuable time setting up my scope with comparison voltages."—J. M. F., Plymouth, Michigan.

"Those Sencore exclusives really sold me, like the extra 500KC Horizontal Sweep range and the free high voltage probe."—D. N., Brooklyn, N.Y.

You'd expect a wide band scope of this quality to cost at least double."—W. L., Chicago, Ill.

"With the PS127, I find I can trouble-shoot those tough ones twice as fast as before—especially color TV."—F. C., Burlingame, Calif.

"Once I compared the specs, I knew Sencore had the best buy in scopes. We now have three PS127's in our shop."—J. S., Ft. Lauderdale, Fla.

SPECIFICATIONS

Vert. Freq. Resp. 10 CPS to 4.5 MC \pm 1 db, — 3 db @ 6.2 MC • Rise Time .055 Microseconds • Vert. Sens. .017 Volts RMS/inch • Horiz. Freq. Resp. 10 CPS to 650 KC • Horiz. Sens. .6 Volts RMS/inch • Horiz. Sweep Ranges (10% overlap) 5 to 50 CPS, 50 to 500 CPS, 500 CPS to 5 KC, 5 to 50 KC, 50 to 500 KC • Input Impedance 2.7 megohms shunted by 99 MMF, 27 megohms shunted by 9 MMF thru low-cap. jack • High Voltage Probe 5000 Volts Max. • Dimensions 12"x9"x15½", Wt. 25 lbs. • Price Complete \$199.50



NO. 1 MANUFACTURER OF ELECTRONIC MAINTENANCE EQUIPMENT

SENCORE

426 SOUTH WESTGATE DRIVE, ADDISON, ILLINOIS 60101

Circle 32 on literature card

NEW

FINCO®

COLOR SPECTRUM™ ANTENNAS

are "signal customized"
for better color reception...



"the ANTENNA that captures the RAINBOW"

FINCO has developed the Color Spectrum Series of antennas — "Signal Customized" — to exactly fit the requirements of any given area.

There is a model scientifically designed and engineered for your area.

Check this chart for the FINCO "Signal Customized" Antenna best suited for your area.

STRENGTH OF UHF SIGNAL AT RECEIVING ANTENNA LOCATION	Strength of VHF Signal at Receiving Antenna Location				
	NO VHF	VHF SIGNAL STRONG	VHF SIGNAL MODERATE	VHF SIGNAL WEAK	VHF SIGNAL VERY WEAK
NO UHF →		 CS-V3 \$10.95	 CS-V5 \$17.50 CS-V7 \$24.95	 CS-V10 \$35.95	 CS-V15 \$48.50 CS-V18 \$56.50
UHF SIGNAL STRONG →	 CS-U1 \$9.95	 CS-A1 \$18.95	 CS-B1 \$29.95	 CS-C1 \$43.95	 CS-C1 \$43.95
UHF SIGNAL WEAK →	 CS-U2 \$14.95	 CS-A2 \$22.95	 CS-B3 \$49.95	 CS-C3 \$59.95	 CS-D3 \$69.95
UHF SIGNAL VERY WEAK →	 CS-U3 \$21.95	 CS-A3 \$30.95	 CS-B3 \$49.95	 CS-C3 \$59.95	 CS-D3 \$69.95



NOTE: In addition to the regular 300 ohm models (above), each model is available in a 75 ohm coaxial cable downlead where this type of installation is preferable. These models, designated "XCS", each come complete with a compact behind-the-set 75 ohm to 300 ohm balun-splitter to match the antenna system to the proper set terminals.

THE FINNEY COMPANY

34 West Interstate Street • Dept. 310 • Bedford, Ohio 44146

RCA TEST EQUIPMENT FALL COUPON CARNIVAL

Clip the coupons—take them to your participating RCA Test Equipment Distributor any time between now and October 31st. Take advantage of RCA's BIG Fall offer—*discounts on every test instrument listed!*

(Only one coupon will be accepted per instrument)



RCA Electronic Components and Devices, Harrison, N. J.

The Most Trusted Name in Electronics

PICK YOUR RCA INSTRUMENTS—ACT NOW!

\$10.00

TOWARD PURCHASE OF
3" OSCILLOSCOPE WO-33A



Mr. Distributor: Refer to RCA Fall Festival Announcement. Void where prohibited, taxed or restricted. Cash value 1/20¢. Offer expires October 31, 1967.

\$3.00

TOWARD PURCHASE OF
WV-38A V.O.M.



Mr. Distributor: Refer to RCA Fall Festival Announcement. Void where prohibited, taxed or restricted. Cash value 1/20¢. Offer expires October 31, 1967.

\$10.00

TOWARD PURCHASE OF
WA-44C SINE/SQUARE WAVE
AUDIO SIGNAL GENERATOR



Mr. Distributor: Refer to RCA Fall Festival Announcement. Void where prohibited, taxed or restricted. Cash value 1/20¢. Offer expires October 31, 1967.

\$3.00

TOWARD PURCHASE OF
WR-50B RF SIGNAL
GENERATOR



Mr. Distributor: Refer to RCA Fall Festival Announcement. Void where prohibited, taxed or restricted. Cash value 1/20¢. Offer expires October 31, 1967.

\$25.00

TOWARD PURCHASE OF
WR-64B COLOR BAR /DOT/
CROSSHATCH GENERATOR



Mr. Distributor: Refer to RCA Fall Festival Announcement. Void where prohibited, taxed or restricted. Cash value 1/20¢. Offer expires October 31, 1967.

\$20.00

TOWARD PURCHASE OF
WR-69A TV-FM
SWEEP GENERATOR



Mr. Distributor: Refer to RCA Fall Festival Announcement. Void where prohibited, taxed or restricted. Cash value 1/20¢. Offer expires October 31, 1967.

\$5.00

TOWARD PURCHASE OF
WR-70A RF-IF-VF
MARKER-ADDER



Mr. Distributor: Refer to RCA Fall Festival Announcement. Void where prohibited, taxed or restricted. Cash value 1/20¢. Offer expires October 31, 1967.

\$3.00

TOWARD PURCHASE OF
WV-77E VOLTOHMYST®



Mr. Distributor: Refer to RCA Fall Festival Announcement. Void where prohibited, taxed or restricted. Cash value 1/20¢. Offer expires October 31, 1967.

\$14.00

TOWARD PURCHASE OF
WO-91B 5" OSCILLOSCOPE



Mr. Distributor: Refer to RCA Fall Festival Announcement. Void where prohibited, taxed or restricted. Cash value 1/20¢. Offer expires October 31, 1967.

\$20.00

TOWARD PURCHASE OF
WR-99A MARKER-GENERATOR



Mr. Distributor: Refer to RCA Fall Festival Announcement. Void where prohibited, taxed or restricted. Cash value 1/20¢. Offer expires October 31, 1967.

\$10.00

TOWARD PURCHASE OF
WT-115A COLOR PICTURE
TUBE TESTER



Mr. Distributor: Refer to RCA Fall Festival Announcement. Void where prohibited, taxed or restricted. Cash value 1/20¢. Offer expires October 31, 1967.

**ALSO
SAVE ON
RCA
KITS!**

\$5.00

TOWARD PURCHASE OF
WO-33A(K) 3" SCOPE KIT

Mr. Distributor: Refer to RCA Fall Festival Announcement. Void where prohibited, taxed or restricted. Cash value 1/20¢. Offer expires October 31, 1967.

\$2.50

TOWARD PURCHASE OF
WV-38A(K) V.O.M.

Mr. Distributor: Refer to RCA Fall Festival Announcement. Void where prohibited, taxed or restricted. Cash value 1/20¢. Offer expires October 31, 1967.

\$4.50

TOWARD PURCHASE OF
WR-50B(K) RF SIGNAL
GENERATOR KIT

Mr. Distributor: Refer to RCA Fall Festival Announcement. Void where prohibited, taxed or restricted. Cash value 1/20¢. Offer expires October 31, 1967.


\$2.50

TOWARD PURCHASE OF
WV-77E(K) VOLTOHMYST

Mr. Distributor: Refer to RCA Fall Festival Announcement. Void where prohibited, taxed or restricted. Cash value 1/20¢. Offer expires October 31, 1967.

TUNE IN ON THE PERRY COMO HOLIDAY SPECIAL IN COLOR ON NBC-TV. THURSDAY, NOVEMBER 30, 7:30 - 8:30 P.M., E.S.T.

October, 1967/PF REPORTER 55

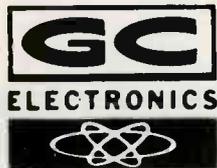

has
everything
in

TV hardware

GC-Telco, the world's largest basic manufacturer of TV antenna hardware, is your most complete single source for all TV antenna installation needs, indoor and outdoor antennas, and antenna accessories.

Choose from the largest selection of chimney, roof, wall or vent-type mounts, all available in attractively carded kits, antenna masts, lead-in and rotor wire, stand-offs, lightning arrestors, ground and guy wire needs . . . everything needed to make any installation easier, faster, more efficient.

For quality, versatility, and dependability, go with the leader . . . make GC-Telco your No. 1 source today.

Write for your Giant **FREE GC Catalog** today . . . over 12,000 items including TV Hardware, Phono Drives, Chemicals, Alignment Tools, Audio, Hi-Fi, Stereo & Tape Recorder Accessories, Nuts & Bolts, Plugs & Jacks, Service Aids, and Resistive Devices.



*only GC gives you
everything in electronics.
..... for almost 40 years!*

GC ELECTRONICS COMPANY

400 South Wyman Street
Rockford, Illinois 61101
A DIVISION OF HYDROMETALS, INC.


Circle 33 on literature card



Telco Snap-In
Chimney Mount
Cat. No. 8610



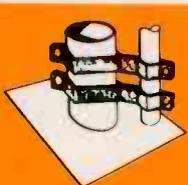Telco Ratchet Type
Chimney Mount
Cat. No. 8006



Telco Vent Mount
Cat. No. 8802



Telco E-Z Stand-Off
Cat. No. E-Z 8027
Wood Screw Stand-Off
Cat. No. 8028



Telco 3-Way Antenna Klip
Cat. No. 9015



Chronically slow accounts. Many a good credit customer has been permitted to down-grade into an undesirable one because of failure to insist on payment according to agreed terms.

Preventives: (a) Reduce the amount of credit allowed. (b) Keep in a separate file for closer attention. (c) Institute a 1% per-month service charge for failure to pay on the due date.

Carelessness in handling credit cards. More use of bank-type credit cards is a certainty for the future. Carelessness in handling the charge slips means sure loss.

Preventive: Make certain every item of basic data needed is clearly reproduced on the slip (particularly the account number of the customer).

Charges by unauthorized individuals. Members of the family or associates of an individual who charge to his account without permission are involved in this abuse.

Preventive: Make a matter of record names of those who can use the account and take time to check with the account in each instance before going ahead.

Too many returns for credit. Every such action does away with profit on the given sale and increases the chance for error in handling the transaction. Frequently credits are made for larger amounts than the original charges.

Preventive: Require original charge slip to accompany each such return. Exert more sales pressure to convince the customer to retain the item he purchased.

Partial payments on accounts month after month. This too often leads to a dangerously large balance the customer cannot pay and will then jeopardize his previously good credit rating.

Preventives: (a) An account charge of 1% per-month on the unpaid balance each time. (b) Reduce the limit of credit allowance as the practice continues. (c) Personal contact with the customer after the

There's a heckuva lot of VTVM units around.
Only the 177 "Professional"
has battery eliminator, mirrored scale,
half volt scale for transistor circuits
and—your name.



If you're one of the skeptics who think one VTVM is pretty much like another, the B&K 177 "Professional" will change your mind. This one stands out from the crowd.

A gigantic 7" mirrored scale reads faster, more accurately. An extra-sensitive 0.5 VDC range will check transistor circuits.

A zener diode regulated power supply insures reliable ohmmeter performance. No batteries required. A single probe ends cable fumbling. Transit switch position protects the meter on the road. The vinyl covered steel case is good-looking and tough. Its appearance symbolizes your professional status and, above all, it has B&K quality.

Any way you look at it, the 177 "Professional" is really different and it's all yours—the handle is personalized with your name. Cost? Just \$79.95.

B&K Division of Dynascan Corporation
1801 W. Belle Plaine • Chicago, Illinois 60613



Where Electronic Innovation Is A Way Of Life

Circle 34 on literature card

Supplements latest Model 658 and 648 Roll Charts

Type	Model 658						Model 648				
	Sec.	Heater	Circuit H&K	P&G	Plate	Grid Test	Heater Current	Fil.	D	E	Plate Test
1AY2	D	1.2J	16	0	14U	VX		1.4	16	9	35VX
	Insert leads into pins 4 & 9 of 9 pin min socket						Insert leads into pins, etc.				
2EG4	T	2.0G	123	a45	47S	10WY.		1.75	A123	A45	36V
3BL2	D	3.0P	—	7	15U	VX		3.0	—	9	30XZ
	Connect top cap to octal socket pin 1						NOR-S switch in S position				
4KT6	P	5.0F	1236	b579	27R	10WY.		4.2	A1256	B479*	22XZ
6BZ3	D	6.4L	C5	3	22U	V		6.3	C5	3	14W
6CF8	P	6.4J	1237	ab468	20R	15XY.		6.3	A1237	AB468	28XZ
17B-B14	P	18.6H	123	b480	22R	90VY.		17	123	B489	12WZ
	Adapter 9MNA required						Adapter 9MNA Required				


Complete low cost tube data subscription service available for Jackson and Mercury tube testers...write for information

JACKSON TUBE TEST DATA DIV. 1744 Rockaway Ave., Hewlett, N.Y. 11557

Circle 36 on literature card

THE BEST COLOR ANTENNAS!

RMS SUPER TRANS POWER'D

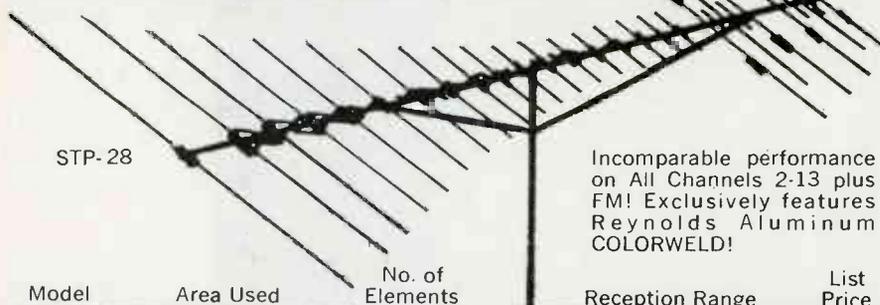


STP-28

Incomparable performance on All Channels 2-13 plus FM! Exclusively features Reynolds Aluminum COLORWELD!

Model	Area Used	No. of Elements	Reception Range	List Price
STP-7	Metropolitan	7	Up to 50 miles	\$13.45
STP-11	Suburban	11	Up to 75 miles	19.95
STP-15	Semi-Fringe	15	Up to 100 miles	26.95
STP-19	Fringe	19	Up to 125 miles	39.95
STP-23	Extreme Fringe	23	Up to 150 miles	44.95
STP-28	Extreme Fringe	28	Up to 175 miles	53.95

RMS DYNERGY

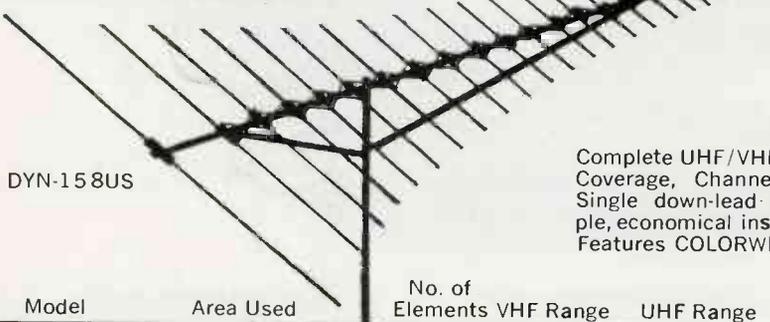

DYN-158US

Complete UHF/VHF and FM Coverage, Channels 2-83! Single down-lead for simple, economical installation! Features COLORWELD!

Model	Area Used	No. of Elements	VHF Range	UHF Range	List Price
DYN-33US	Metropolitan	6	to 35 miles	to 20 miles	\$19.95
DYN-54US	Suburban and Semi-Fringe	9	to 60 miles	to 30 miles	29.95
DYN-66US	Suburban and Semi-Fringe	12	to 75 miles	to 50 miles	34.95
DYN-88US	Semi-Fringe and Fringe	16	to 125 miles	to 75 miles	44.95
DYN-118US	Semi-Fringe and Fringe	19	to 125 miles	to 75 miles	44.95
DYN-158US	Fringe	23	to 150 miles	to 75 miles	49.95

Make your next installation profitable with these dependable RMS Antennas. Write for FREE Informative Catalog! . . . Dept. PFA

Dependable construction and performance for long-life installation!

RMS ELECTRONICS, INC.

50 ANTIN PLACE, BRONX, N. Y. 10462

Circle 35 on literature card

second or third such partial payment to help solve the problem before it grows larger.

Granting requests for larger than authorized amounts of credit. This is usually done for a good customer of long standing as a special favor.

Preventive: Without exception, granting the request should be delayed long enough to check on the reasons behind it, the ability of the customer to pay the larger sum, and any changes in financial capabilities of the account.

Checking only one credit reference. Many substantial losses were noted during the last year where only one reference was required on credit applications or only the first was checked if more were listed.

Preventive: Check all references and require at least three from every applicant. Questionable credit risks often make an excellent record with one account for just such a reason.

Urging customers to use credit. The drive for additional business can never be discouraged in any concern but when such business is obtained on a basis of credit where not justified, it usually costs much more than the profit made thereby.

Preventives: (a) Discourage use of high pressure methods which result in customer over-use of credit beyond ability to pay. (b) Hold fast to all credit rules in periods where special business promotion activities are underway. (c) Set up separate credit facilities for use at such times.

Too liberal concession to accounts during emergencies. This has generally been the granting of 90- to 120-day payment-free periods or extra credit allowances to customers on such occasions. This invariably results in laxity of responsibility by the customer in the future.

Preventives: (a) Set up special arrangements to cover partial payment of account during these periods (b) Arrange for financing at a

This part speaks for the whole radio.



This box speaks well of you.

To the listener, the speaker is the most important part of the radio. Reason enough that it be of the highest quality and reliability. And when it says Delco on the box you can be certain you've got it: genuine OEM quality.

Delco Radio Parts are designed by engineers who specialize in automotive radios. Delco Radio speakers, for example, provide greater efficiency and sensitivity per ounce of magnet than any other speakers built. And since nearly half the cars on the road



have Delco Radios as original equipment, you are assured of a vast pre-sold market.

Doesn't it make sense to stock the best for your customers?

They know Delco's reputation. So, the next time you reorder, remember your United Delco Supplier. He handles the most widely advertised, merchandised and recognized name in the parts business.

Why not let Delco Radio speakers say something nice about you?

Delco Radio, Division of General Motors, Kokomo, Indiana.



Circle 37 on literature card

**WORLD'S
FINEST
5-CORE
SOLDER**



**ERSIN
MULTICORE**

**NEW EASY
DISPENSER
PAK ONLY 69¢**

BUY IT AT RADIO-TV PARTS STORES
Multicore Sales Corp. Westbury, N.Y. 11591
Circle 38 on literature card

**We offer You
nothing but
finer, faster,
Precision
Tuner
Service!...**



(Period) **VHF-UHF**
\$7.95
+parts & shpg.

Why pay for parts you don't need?
Mail coupon now for free information!
PRECISION TUNER SERVICE
...one of the OLDEST and LARGEST TV tuner repair firms in the world!
Box 272P Bloomington Indiana 47401

Firm _____
Name _____
Title _____
Address _____
City _____ St. _____ Zip _____

bank or elsewhere to handle money needs created by the emergency. (c) Pay close attention to the account immediately at the end of the period in order to put it back into line as speedily as possible.

Assuming the good "cash customer" is automatically an excellent credit risk. This has been one of the leading reasons for credit losses among small business concerns everywhere for a number of years.

Preventive: A positive policy of complete investigation on every credit application.

Accepting recommendation of present customer for another. This is sometimes a good method of building new credit accounts but where all checking of such an applicant is waived it has often proven an unsound practice.

Preventive: Handle every such new account with the regular routine used for all credit applicants. Where offending the old customer cannot be risked, an immediate grant of small credit pending regular checking will usually handle the problem.

Failure to pursue collection steps for fear of losing a good customer. Almost every business failure during the last year revealed the presence of such procedure. An uncollectable account is certainly anything but that of a **good** customer.

Preventives: (a) Follow through on a standard policy of handling credits and collections with no variance for any but emergency considerations (b) Realize that the good customer whose account has become hazardous has lost his good status and handle it accordingly.

Finally, the **lack of proper credit and credit control records**, has always been a contributing factor where credit abuses have eaten heavily into the profits of the business. The system which fails to immediately point up existence of shaky credit conditions is an inadequate one. Without workable credit records and systems, all other safeguards the business may use will prove inadequate. ▲

NEW! from 

**"IN-CIRCUIT"
CURRENT CHECKER**

Eliminates most common cause of "callbacks" (unstable focus, shrinking pictures, etc.)! Should pay for itself on next months' calls alone!



Nothing else like the HC-8 available! Tune horizontal drive and linearity for "dip"—and in seconds—you've got best possible focus, width and stability at minimum cathode current. Makes convergence adjustments faster, easier—longer lasting!

Especially useful on color TV where a slight misadjustment of horizontal linearity or efficiency coils drives cathode currents sky high! 5 pre-wired sockets for all popular horizontal output tubes lets you plug into circuit fast—no clipping or unsoldering of leads! **\$34.50** Net

ASK YOUR DISTRIBUTOR
or write for full details.

 **SECO
ELECTRONICS CORP.**
1001 Second St. So. Hopkins, Minn. 55343
Circle 39 on literature card

COLOR

COUNTERMEASURES


SYMPTOMS AND TIPS FROM ACTUAL SHOP EXPERIENCE

Chassis: RCA CTC11

Symptom: Complete loss of contrast. Raster and color signals remain on screen.

Tip: Check for Heater-Cathode short in V24 (CRT).

Analysis: Heater of CRT is connected to B+. A heater-cathode short will place this B+ source on the cathode. The power supply filter will then filter out the luminance information normally present on the cathodes of the CRT. In addition, the +180 volts applied to the cathode will clamp the normal bias and in effect make the grids of the CRT positive with respect to cathode, allowing raster to remain on screen.

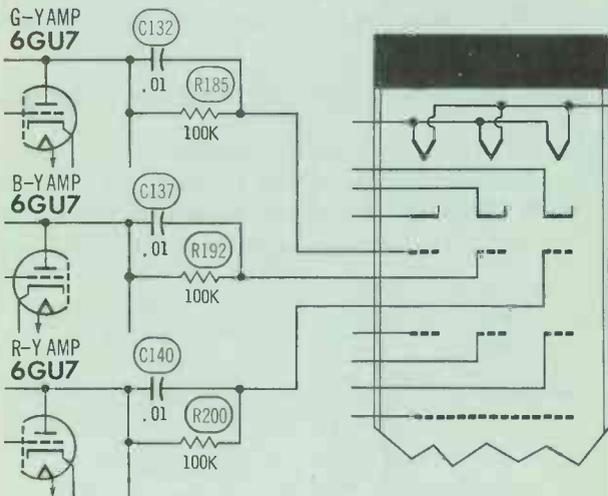

Chassis: Zenith 24NC312 and 25N38.

Symptom: Screen turns light green on color program; normal on black-and-white program.


Tip: Plug that connects hue and color level controls to the chassis is defective. Remove plug and connect wires directly—watch the color code of the wires, as they do not match.

LEADER

TEST INSTRUMENTS

Much in little

New!

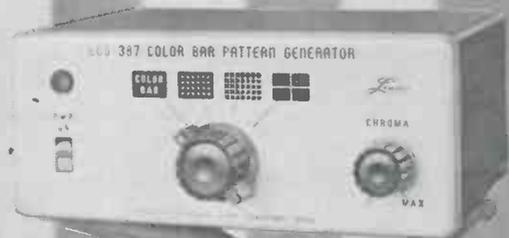

\$13450

LCG-387

COLOR BAR PATTERN GENERATOR

Here it is—LEADER's new color bar pattern generator which includes the keyed rainbow, SQUARE crosshatch, dots, AND the single cross bar. In fact, this cross pattern will speed up adjustments on raster centering, purity at the center and dynamic convergence. Sharp and clear lines, both vertical and horizontal, produced by return trace blanking. Two switchable channels, 5 and 6, with 10mV output. Solid state, of course, with voltage regulated supply. Compact and sturdy construction for field use—supplied with carrying bag for convenience. Size only 2 $\frac{3}{4}$ " H \times 6 $\frac{3}{4}$ " W \times 4 $\frac{3}{4}$ " D in., and weight 3.3 lbs approx.

LEADER ELECTRONICS CORP.

NEW YORK OFFICE

101-103 ROME ST., FARMINGDALE, L.I., N.Y. 11735

TEL (516) 694-1534 541-5373

Circle 40 on literature card

October, 1967/PF REPORTER 61

DELHI

68 FOOT SELF-SUPPORTING TV TOWERS



U.S. Patent applied for

are only part of our line of precision-built Towers, Masts and Accessories for domestic TV, amateur, CB and lighting installations.

- ★ **DMX Series Towers** — uniformly tapered, self-supporting with concrete bases, have channel legs and riveted "X" braces. Six models from 28 to 68 ft.
- ★ **DMX Series Towers** — but with steel cylinder bases, needs no concrete and can hinge-up. Five models from 20 to 52 ft.
- ★ **DMX Series Heavy Duty Towers** — with concrete bases for supporting amateur arrays. Three models from 32 to 48 ft. plus mast.
- ★ **DME Series Towers** — with parallel channel legs and riveted "X" braces. Six bracketed models from 16 to 52 ft. Guyed to 80 ft.
- ★ **Commercial Guyed Towers** — up to 120 ft.
- ★ **Golden Nugget Tubular Towers** — with rust proof welds, available in 10 foot sections in 18 or 16 gauge.
- ★ **Tripod Roof Mounts** — in 3, 5, 8 and 10 foot models.
- ★ **Pop-up Masts** — from 20 to 50 ft.
- ★ **Welded Galvanized Mastings** — in many lengths, diameters and gauges, swaged or plain.

Ten years of tower building experience plus careful engineering and modern, progressive manufacturing techniques assure your satisfaction.

Write for complete information on these value packed Delhi products.

DELHI

DELHI METAL PRODUCTS, INC.
SHERIDAN, INDIANA 46069

IN CANADA — DELHI METAL PRODUCTS LIMITED
DELHI, ONTARIO


Circle 41 on literature card

Chassis: Sylvania D01 and D02

Symptom: Poor color sync.

Tip: Check R168 and R169 for changed value.

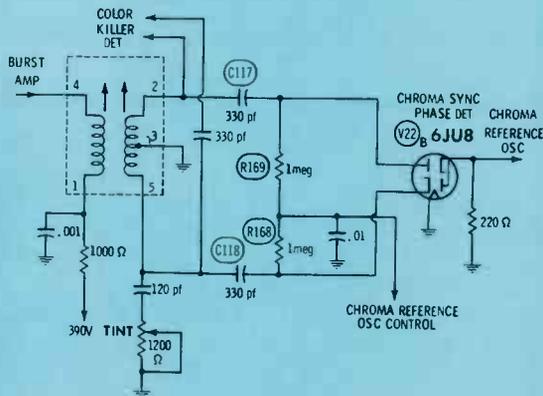If either is defective, replace both with a matched pair of 2% resistors. Also check C117 and C118 for a leakage or shorted condition.



Chassis: All.


Symptom: Evenly spaced, multiple ghosts in picture.

Tip: May be caused by reflected energy in an improperly terminated delay line. Check for an open terminating network at the output end of the delay line, or an ungrounded shield on the line. An open delay line would result in a complete loss of luminance signal.

Chassis: Zenith, all chassis using socket-type CRT grid leads.

Symptom: Hue control action reversed.

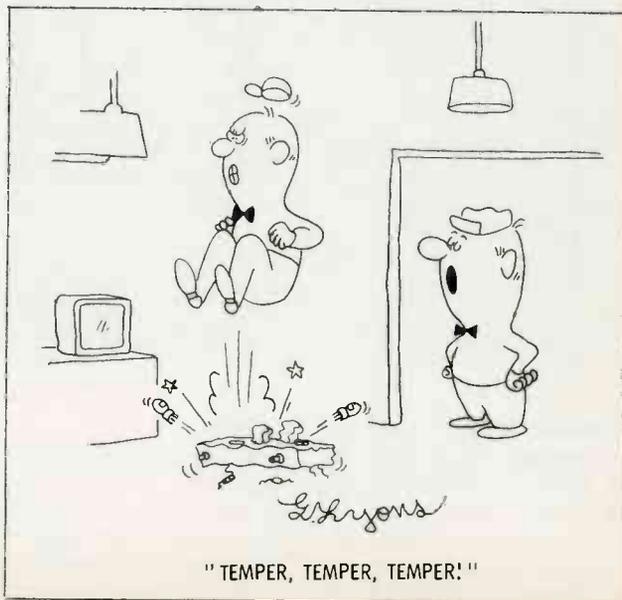Tip: May be caused by reversal of green and blue grid leads. Disconnect and change position of leads. ▲



"TEMPEM, TEMPEM, TEMPEM!"

PRODUCT REPORT

for further information on any of the following items, circle the associated number on the Catalog & Literature Card.




Transistor Analyzer
(57)

Transistors can be checked both in and out of circuit with Lectrotech's new Model TT-250 Transistor Analyzer. In-circuit AC gain tests indicate the condition of the transistor as either good or bad, with no numerical interpretation involved. Out-of-circuit tests measure beta or gain on two scales: 0-250 and 0-500. Biasing is automatic and no calibration is required.

The unit measures transistor leakage (I_{cbo}) directly in microamperes. It also measures reverse leakage and forward conduction of diodes and rectifiers to determine front-to-back ratios. Transistor classification—PNP or NPN—can be quickly determined without a set-up book. In addition, electrolytic capacitor leakage current can be checked using 6 volts, with the indication read directly in microamperes.

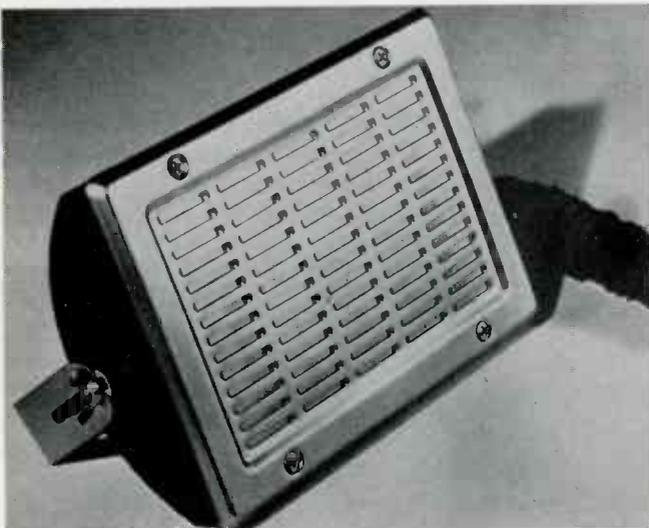
Other features of the analyzer include a 6" meter and all steel case. The unit measures 10½" × 7" × 4" and weighs 5½ lbs. Price is \$87.50.



Stereo Speaker
(58)

A new stereo speaker that can be used anywhere a stereo effect is desired has been announced by **Best Automotive**.

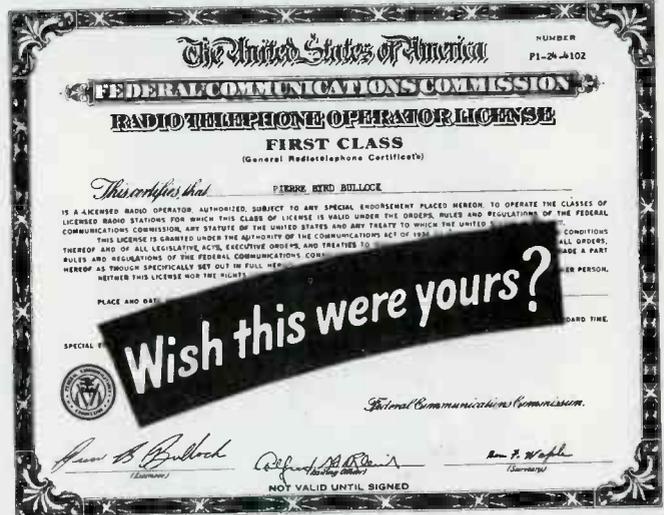YOU EARN YOUR FCC FIRST CLASS LICENSE or your money back!



5 NRI COMMUNICATIONS COURSES INCLUDE FCC LICENSE TRAINING

Earning an FCC License can be quick and easy the NRI way. You can concentrate on a short FCC License course—"specialize" by training in Mobile, Aviation, or Marine Communications—or go all-out with the job-simulated NRI course in Complete Communications. It is the only home-study training plan that includes professional lab equipment specifically designed to give you on-the-job, "hands on" experience as you train.

Whichever NRI Communications course you choose, with an FCC License you're ready to operate, service and install transmitting equipment used in broadcasting stations, aviation, on board ships, and in mobile and Citizens-Band radio. And you **MUST PASS** your FCC exams or *NRI refunds your tuition in full*. Can you do it? The NRI record of success is outstanding. 87% of NRI graduates pass their FCC exams.

Get full details today about five courses that include FCC License preparation, plus seven other training plans offered by NRI, the oldest and largest school of its kind. Mail coupon. No obligation. No salesman will call. **NATIONAL RADIO INSTITUTE**, Electronics Div., Washington, D.C.

APPROVED UNDER GI BILL. If you served since January 31, 1955, or are in service, check GI line in coupon.

MAIL NOW for FREE CATALOG



NATIONAL RADIO INSTITUTE 22-007
Electronics Division, Washington, D.C. 20016

Please send complete data about FCC License training, other NRI courses checked below. (No salesman will call.)

- | | |
|---|--|
| <input type="checkbox"/> FCC License | <input type="checkbox"/> TV-Radio Servicing (with color) |
| <input type="checkbox"/> Complete Communications | <input type="checkbox"/> Advanced Color TV |
| <input type="checkbox"/> Aviation Communications | <input type="checkbox"/> Industrial Electronics |
| <input type="checkbox"/> Marine Communications | <input type="checkbox"/> Basic Electronics |
| <input type="checkbox"/> Mobile Communications | <input type="checkbox"/> Electronics for Automation |
| <input type="checkbox"/> Math for Electronics | <input type="checkbox"/> Electrical Appliance Repair |
| <input type="checkbox"/> CHECK FOR FACTS ON NEW GI BILL | |

Name _____ Age _____

Address _____

City _____ State _____ Zip _____

ACCREDITED MEMBER NATIONAL HOME STUDY COUNCIL

**only picture tube analyzer
that tests all color tubes
as they should be tested!**

(THE WAY TUBE MANUFACTURERS DO)



**NEW LECTROTECH CRT-100
PICTURE TUBE ANALYZER
FOR COLOR AND BLACK AND WHITE**

Does everything . . . you would need all three units of the leading competitive brands to equal the performance of the Lectrotech CRT-100. No other brand has all the features . . .

- Line voltage adjustment (to insure all tube voltages are correct regardless of line voltage).
- Critical Grid-to-Cathode Leakage is read on sensitive meter for greatest accuracy.
- Leakages in all other elements are indicated on neon lamp.
- Tests all black and white and all color tubes for leakage, shorts and emissions.
- Tests each color gun separately.
- Tests each color gun to a standard set of test conditions. With variable G-2 voltage, each grid is normalized to a reference cut-off voltage. This method is used by tube manufacturers and simulates tube performance in color receiver.
- Rejuvenates and removes shorts on both color and black and white tubes for increased brightness.
- Life expectancy test, predicts remaining useful life of both color and black and white picture tubes.
- Continuously variable G-2 voltage for all tubes, present and future, including new 15 inch color tubes.
- Complete plug-in cables for easy replacement.
- Complete self-contained black and white socket assembly. No adapters to lose or cables to break.
- Including Pilot Light.

Only **89⁵⁰** net

ONE YEAR WARRANTY

See your distributor or write DEPT. PF-10

LECTROTECH, INC.

1221 Devon Ave., Chicago, Illinois 60626



Circle 42 on literature card

The Model ST46BC speaker comes assembled in an attractive 7¼" × 5" × 2½" metal housing with a black finish, complete with chrome grill and chrome mounting bracket. All necessary wire, hardware, and instructions are furnished. A versatile mounting bracket permits ease of installation. Price is \$7.25.



Batteries

(59)


A complete line of manganese alkaline batteries for toys and radios as well as photoflash and portable lighting equipment is announced by Ray-O-Vac. Available in open stock or on bubble pack cards, the line consists of five different size batteries: No. 813 Size "D", No. 814 Size "C", No. 815 Size "AA", No. 824 Size "AAA", and No. 810 Size "N". Also available is a battery display (No. MA30) housing the three most popular batteries—815, 814 and 813—on bubble pack cards. The display, which hangs from a pegboard or stands on a counter, is only 13" wide by 6¾" deep by 16½" high and is priced at \$23.70.

CRT Test Adapter

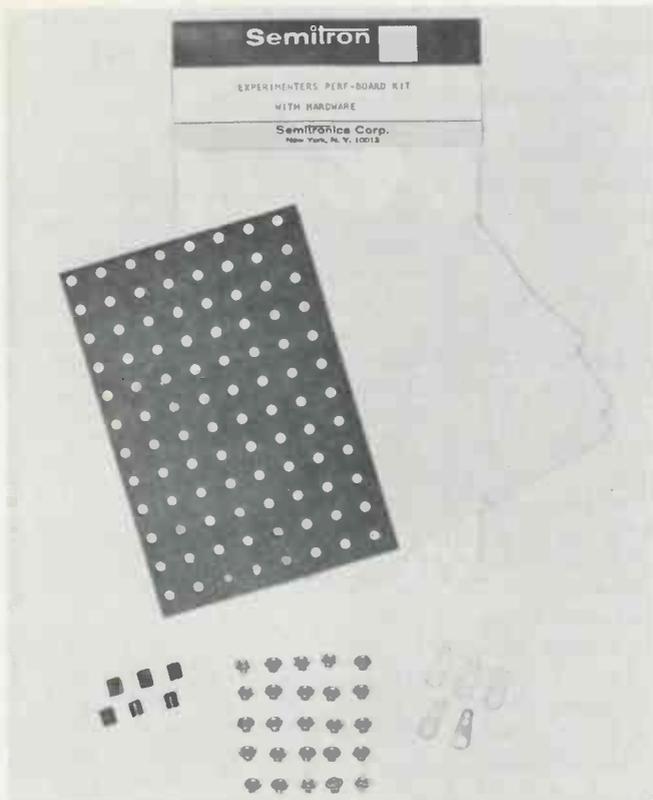(60)

Existing CRT test equipment can be converted to test the picture tubes used in small screen personal portable television sets through the use of a new tube socket test adapter introduced by Pomona Electronics, Inc. CRT's such as 9YP4, 11RP4, 12BEP4, 16BXP4, etc., fit the adapter.

The Model 2713 adapter socket accepts tubes using 7GR basing (E7-91 base), and plugs into the standard 12L Duo-Decal socket found on current tube testers. The unit features a clearance hole in the 7GR socket which accepts the CRT evacuation stem and prevents accidental breakage. Price is \$1.95.



Experimental Kit
(61)

A new line of experimenters perf-board kits with hardware is designed for experimenters, vocational school students, shop teachers, hobbyists, hams, technicians, and engineers who want a quick setup that can be assembled rapidly and efficiently. The Semitron Experimenter's Perf-Board Kit consists of 1/8" tempered board. The spacing of the holes on 1/2" centers helps prevent component crowding. Solid brass eyelets are supplied, permitting easy soldering and the insertion of a number of component leads through a single eyelet.

Cartesian coordinate graph paper also forms part of the kit, allowing spacing of components after prior planning using the graph. If solderless connections and maximum construction speed are desired, the spring connectors supplied with the kit can be used for making rapid and mechanically secure connections. Using several kits permits modular construction for the design and building of a large number of stages, arranged either horizontally or vertically. The kits are priced at 89c.



Studio Mixer
(62)

A new battery-operated studio mixer designed specifically for studio, remote, and home hi-fidelity use has

**You can pay more
but you buy less!**



**new Lectrotech V6-B
color bar generator**

99⁵⁰ brings you...

- **Guaranteed performance . . . full one year warranty.**
- **A.C. operated solid state generator . . . no batteries to buy . . . no failures when needed most.**
- **Most stable generator of all . . . sharper, brighter patterns.**

The V6-B provides crystal-controlled keyed rainbow color display, all cross hatch, dots, vertical lines only, horizontal lines only, Red-Blue-Green gun killer, exclusive Dial-A-Line feature (horizontal line width adjustable), voltage-regulated transistor and timer circuits, simplified rapid calibration. Supplies adjustable dot size, RF output more than 10,000 mv, operates on channels 3, 4 or 5, has color level control for color sync servicing. Connects to antenna terminals (no connection needed inside of set). Power transformer-line isolated. Stable operation under wide voltage ranges assured by fully voltage-regulated circuits. Hand-wired reliability . . . no printed circuits. Fully enclosed test lead compartment. Rugged, caddy size unit built to withstand rigors of field servicing. Size: 7⁵/₈"W, 3¹/₂"H, 9"D. **99⁵⁰**
Weight: 5¹/₂ lbs. Only

See your distributor or write for literature.

DEPT. PF-10

LECTROTECH, INC.

1221 W. Devon Ave., Chicago, Ill. 60626

Circle 43 on literature card

October, 1967/PF REPORTER 65

for PROFITABLE,
TIME-SAVING
SERVICING

OF: Black & White TV
Color TV

AM and FM, Tube or
Transistor Home, Portable
and Auto Radios

Communications
equipment &
Home
Appliances

Hi-Fi
Components

**B&K PROFESSIONAL
TEST EQUIPMENT**

WITH SIGNAL INJECTION AND IN-AND-OUT OF CIRCUIT
MEASURING TECHNIQUES

Send today for your free copy of Catalog AP22



DS:602

1801 WEST BELLE PLAINE AVENUE, CHICAGO, ILL. 60613
Telephone: (312) 327-7270 • Cable Address: BANDKCO

Circle 45 on literature card

been announced by **Switchcraft, Inc.** Called the "Studio MixMASTER" Model 307TR, it is a solid-state stereo-monaural audio frequency mixer/amplifier. The mixer can be used with phonographs, microphones, electronic instruments, and tape recorders. It permits recording sound on sound, fades music and voices, records voice over music, and mixes voice and program sources from several different locations.


Powered by standard "D" batteries, the unit requires no external power. Distortion is 1% maximum (0.5% typical) at 1.5 volts output. Frequency response is 20 Hz to 20,000 Hz with a minimum signal-to-noise ratio of 60 dB referred to 1-mv input.

The mixer accepts from one to four monaural input signals or up to two stereo input signals from any combination or type of program source. It is also equalized for magnetic phono cartridges. Each program input level is controlled individually by a separate gain control or simultaneously with the master gain control. These broadcast-type control knobs are numbered for easy reading and rapid error-free operation. Other controls include an on-off switch, phono equalization, and stereo-mono switches. Standard phone

and phono jacks are used for various inputs. Each input will handle a wide range of signals without overloading. The microphone inputs will accommodate both low- and high-impedance microphones without transformers.

Signals are mixed and amplified up to a 2-volt level in each channel, then fed to a single high-impedance output for distribution to recorders, public address, or musical instrument amplifiers. The unit measures 3½" high by 12" wide by 7¼" deep and is finished in satin black enamel with a brushed aluminum escutcheon plate. Protective rubber feet prevent scratches to fine surfaces. Price is \$145.00.

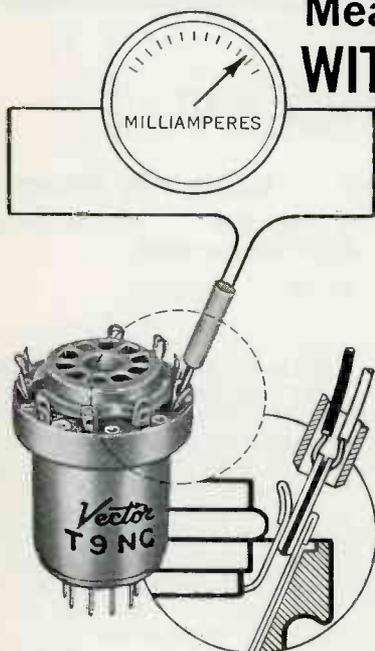**Measure current or voltage
WITHOUT CUTTING LEADS**



*Vector Current
Test Adapters . . .*

are designed to measure tube circuit current, voltage or waveform . . . without cutting leads, unsoldering or disconnecting circuit. Simply insert the Adapter between tube and tube socket and test with single or dual-sided probe.


TUBE SOCKET TEST ADAPTERS—Commercial and MIL-STD. Straight-thru adapters in nine different models for all tube types. Fit inside all tube shield bases. Recessed, shock-proof test tabs take probe or alligator clip across flange.

EXTENDED SHIELDED SOCKET TEST ADAPTERS—For voltage measurements in hard-to-reach locations; available in 3¼" or 4" lengths.

SOCKET CHANGE ADAPTERS save socket modification time; are stocked unwired in the most frequently used combinations of octal, 7 and 9 pin miniature units. Wired units to order.

SOCKET EXTENDERS eliminate wear of permanent tube sockets in expensive test equipment.


Send for complete literature

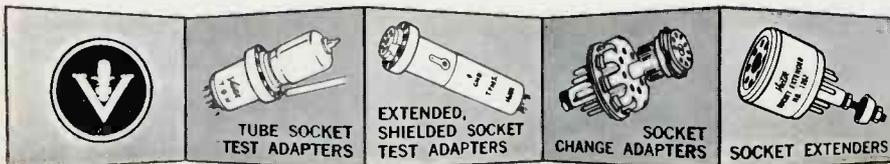

VECTOR ELECTRONIC CO., INC.

1100 Flower Street, Glendale 1, California • Phone: (213)245-8971

Circle 44 on literature card

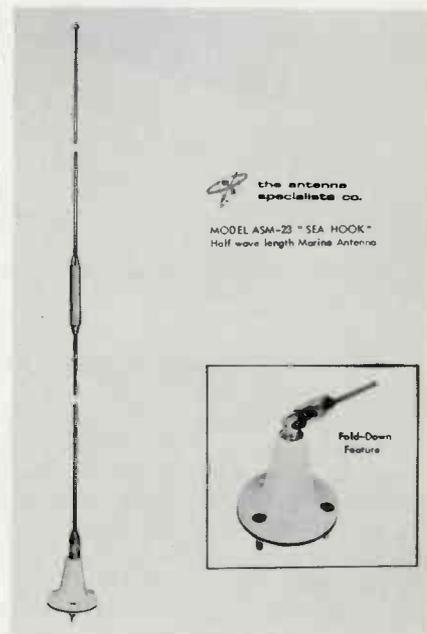

Marine CB Antenna
(63)

A new omni-directional marine CB radio antenna with a low angle of radiation for maximum "over-water" range has been announced by **The Antenna Specialists Co.** The new 27-MHz antenna, designated Sea-Hook Model ASM-23, is a full electrical half-wave radiator with an overall length of 97". A feature of special importance to boat owners is the pure-white Cocolac base with a built-in fold-over feature allowing instant "retraction" of the antenna when negotiating bridges.

No ground plate is required since link coupling is employed, thus simplifying installation. All critical parts are solid brass with chrome plating for additional protection. The loading coil is enclosed in white, weatherproof

plastic with chrome-plated end caps. The upper and lower whips are fabricated from stainless steel. The impedance of the unit is 50 ohms. VSWR is better than 1.5 to 1.0. The upper radiator can be easily adjusted for fine tuning. The antenna is priced at \$29.50.



Seven in One
(64)

The solid-state portable unit shown here incorporates seven instruments

for testing audio FM and multiplex. Four signal sources and three measuring instruments are contained in **Amphenol Corporation's** new Model 880 Stereo Commander.

Signal sources provided by the unit include:

- (1) An audio generator that supplies either sine or square wave signals used by other sections of the unit.
- (2) A multiplex simulator that generates or controls all signals necessary for complete and accurate alignment of an FM multiplex receiver.
- (3) RF/sweep oscillator that may be used as an FM source modulated by the signal present at the composite jack (monaural sine wave or square wave) or as a sweep generator with 60-Hz sweep rate for FM tuner alignment.
- (4) An oscillator that generates a crystal-controlled 10.7-MHz signal for use as a marker for aligning FM receivers.

Measuring instruments included in the instrument are:

- (1) An intermodulation distortion

analyzer which measures distortion to 100% using an SMPTE standard signal.

- (2) An impedance bridge capable of measuring largely resistive unknowns from 1 ohm to 20,000 ohms. Since the audio generator provides the signal used to drive the bridge, unknown impedance can be checked at any frequency within the generator range. This section may also be used to determine resonant frequencies.
- (3) A high-impedance AC voltmeter with a sensitivity of 100 mv full scale. The unit measures from 0.1 volt full scale to 1000 volts full scale in nine increments. The VTVM is also used as an indicator for the impedance bridge and intermodulation analyzer sections.

The Model 880 has a composite output of 5 volts p-p stereo, with 35-dB channel separation up to 10 KHz; 2.5-volts p-p L-R and 3-volts p-p monaural. A sine wave output of 5 volts p-p is available at 19, 38, and 67 KHz. The monaural audio output consists of a 3-volt p-p sine wave and

fat, ugly machine that can make you a lot* of money.

Just so you'll be sure . . . it's an oven. Not for pies. Nor cakes. Not even for pizzas. It's for television picture tubes, and performs chores like tube evacuation, cathode bombarding, induction heating, and more. Most important, it is part of the exclusive Windsor System of picture tube rebuilding — your key to a business you can run (right along with what you're doing right now), and make extra money with in amounts you might not have thought possible (like \$4,000, \$5,000, \$10,000 a year and more!).

Sound good? Then send for the full story. Write direct, or circle our number right away. Who knows, that happy guy in the picture could be you.

WINDSOR ELECTRONICS, INC.
999 North Main Street
Glen Ellyn, Illinois 60137

BOB LINDE
2228 N. W. 30th Ct.
FORT LAUDERDALE, FLA.
phone: 352-583-2240

BILL CHILDS
POST OFFICE BOX 135
PICKATELLO, IOWA 480
phone: 208-237-8329

Circle 46 on literature card

Discriminate Between Desired Signal and Unwanted Noise

with the

FREE SPACE STANDING WAVE MAGNETIC ANTENNA
UHF-VHF-FM-COLOR

Investigate now!

S&A Electronics Inc.
Manufacturers of the TARGET ANTENNA

Phone 419-693-0528

206 West Florence Street Toledo, Ohio 43605

Circle 47 on literature card

new Sams books

Servicing Closed-Circuit Television



by Melvin Whitmer. Teaches the fundamentals of servicing closed-circuit television systems which are coming into widespread use. Clearly explains the differences between closed-circuit and home-type television. Describes how to set up various systems and how to maintain and repair complete installations. Covers types of systems and their applications in general terms, and describes specific makes and models. Includes schematics and other detailed data to provide a complete understanding of closed-circuit TV. 192 pages; 8 1/2 x 11". Order 20574, only \$4.25

specific makes and models. Includes schematics and other detailed data to provide a complete understanding of closed-circuit TV. 192 pages; 8 1/2 x 11". Order 20574, only \$4.25



ABC's of Hi-Fi and Stereo (2nd Ed.)

by Hans Fantel. This newest revision gives you a full understanding of what high-fidelity and stereo are all about. Describes the basic principles of sound reproduction and what you should know to select, operate, and maintain equipment. Explains monaural and stereo sound and discusses the relative merits of consoles and component systems. Treats in detail the requirements of amplifiers, turntables, tone arms, cartridges, speakers, record changers, and tape recorders. Shows how to set up a sound system, how to get the most from it, and what to do in case trouble is encountered. 128 pages; 5 1/2 x 8 1/2". Order 20539, only \$2.25

ABC's of Vacuum Tubes

By Donald A. Smith. Gives you the basic understanding of the electron tube required for the study of electronics and modern circuitry. Explains the principles and operation of each basic tube type in language anyone can understand. Describes the factors affecting tube operation. Includes valuable formulas for the more serious student. 128 pages; 5 1/2 x 8 1/2". Order 20576, only \$2.25

Tape Recording for the Hobbyist (2nd Ed.)

by Art Zuckerman. While concerned with tape recording as a hobby, this revision of the book *Magnetic Recording for the Hobbyist*, also provides many ideas for important uses of the recorder in home and office. Describes special entertainment uses, ranging from party tricks and "detective-type" work to building a library of sound. Includes useful tips on microphones, special sound effects, candid recordings, correspondence recording, the versatile use of battery-powered portable recorders, tape editing, producing your own programs, synchronizing sound on tape, tape and recorder maintenance—plus home video tape recording. 160 pages; 5 1/2 x 8 1/2". Order 20583, only \$3.25

Controlled Guidance Systems



by Hal Hellman. This programmed text explains the fundamentals of guidance systems. Covers ballistic trajectory, hyperbolic guidance, motion, translation, proportional navigation, celestial navigation, and stellar inertial guidance. Explains the principles, operating characteristics, and construction of various systems, both active and passive. Describes the early history and development of missiles, from the V-2 bomb of World War

II to the far more sophisticated rockets and missiles used today. Topics and chapters end with test questions and answers to help reinforce learning; a final examination is included. 224 pages; 5 1/2 x 8 1/2". Order 20573, only \$4.95

These and over 300 other SAMS Books are available from your local Electronics Parts Distributor . . .

HOWARD W. SAMS & CO., INC.
4300 WEST 82nd ST. • INDIANAPOLIS, INDIANA 46268

Circle 48 on literature card

68 PF REPORTER/October, 1967

a 10-volt p-p square wave. Both sine and square wave are variable from 35 Hz to 18 KHz in two ranges with less than 1% distortion.

The unit measures 11 1/2" wide by 9 3/4" high by 6" deep and weighs slightly over 8 lbs. Price is \$329.95.



Nutdriver Set
(65)

A selection of hollow shaft nutdrivers in a new plastic case is offered by Xcelite, Inc. Identified as No. HS6-18, the set consists of ten color-coded nutdrivers with hex openings from 3/16" through 9/16" and clearance hole depths for long bolts and studs from 4 3/8" through 6". The tools are


packaged in a molded yellow plastic case. A tight-fitting cover with integral snap lock keeps the nutdrivers clean and dust-free when not in use. It also permits them to be carried on service calls without danger of spilling or becoming lost in the tool box. The nutdrivers are designed with precision fit, case-hardened sockets; polished, plated steel shafts; and shockproof, breakproof, color-coded plastic (UL) handles. Price of the set is \$18.50.



Color TV Control Kits
(66)

The two new compact kits pictured here offer the service technician a wide selection of exact replacement controls for color TV sets. Each Mal-lory kit is packaged in a reusable, metal, storage tray and includes a free Lampliter automatic photo electric light control. This device turns lights on at dusk and off at dawn.

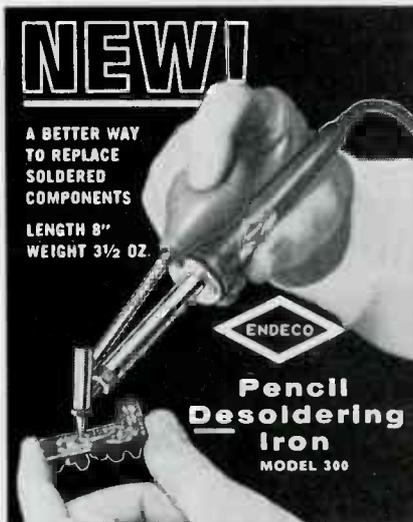The CCK-1 and CCK-2 kits contain a carefully selected assortment of trimmers, convergence controls, and high-voltage controls for virtually every color TV set on the market. Each kit, complete with Lampliter and metal storage tray, is \$12.50.



Now—remove miniature soldered components in seconds—without damage

Hollow tip fits over connection; vacuums all solder for easy removal of component. Leaves terminals and mounting holes clean. Then, with 360° contact, it resolders even faster and better than regular irons. Handles miniature and standard components in printed circuit boards and conventional wiring. Self-cleaning. All parts replaceable. 40 watts, 115-v. 5 tip sizes. Pays for itself in time saved. \$9.95 net East of the Rockies.

Larger model available. See your distributor or write:

ENTERPRISE DEVELOPMENT CORPORATION

5151 E. 65th St. • Indianapolis, Ind. 46220

Circle 49 on literature card

MOVING?

Don't lose touch . . .


RECEIVE PFR AS USUAL

(INCLUDE OLD AND NEW ADDRESS)

PF REPORTER
CIRCULATION DEPT.

4300 W. 62nd St.,

Indianapolis, Ind. 46206

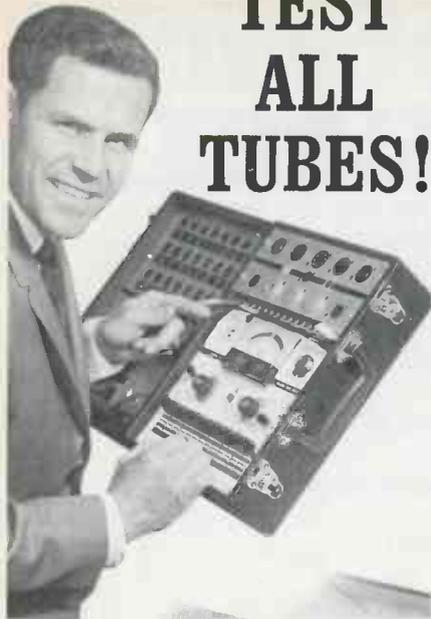

TEST ALL TUBES!


New Deluxe 107C Tester

Exclusive "eye" tube spots momentary shorts. Superior accuracy and stability from constant voltage transformer—no line adjust.

Now a portable tube tester unmatched in speed, sensitivity and reliability for all modern TV, radio, hi-fi, industrial and foreign tubes. Tests more than 1000 different tubes without setup, more than 3000 in total. Patented Grid Circuit Test; Dynamic Mutual Conductance and Cathode Emission Tests; many others.


\$198⁵⁰
NET

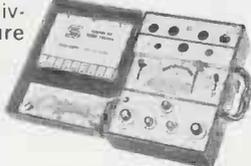MODEL 98. For comprehensive analysis of all modern TV and radio tubes. Includes patented Grid Circuit, Cathode Emission, Tube Merit, Heater Current tests for more than 2500 types of receiving and picture tubes.



\$109⁵⁰
NET

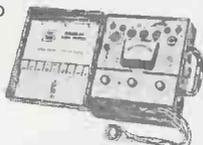MODEL 88. Popular, low cost Grid Circuit and Tube Merit Tester. Complete coverage of all popular receiving tubes plus adaptor for more than 400 picture tubes. Includes speed indexed setup data.



\$74⁵⁰
NET

ASK YOUR DISTRIBUTOR
or write for full details.

SECO ELECTRONICS CORP.
1001 Second St. So. • Hopkins, Minn. 55343

Circle 51 on literature card

LETTERS TO the EDITOR

Many readers have responded to Mr. A. DuBusley's request for an effective method of loosening adjustable iron cores that have been frozen in the core.

Dear Editor:

Try a drop or two of penetrating oil directly on the slug. Allow it to soak for a minute or two and then apply a steady pressure with the wrench. Once the slug is loose, remove it from the form and clean out the oil with alcohol and a cotton swab.

E. V. MAPPIN, JR.

Lower Burrell, Pa.

Dear Editor:

If the core is the type with hexagonal hole, insert an Allen setscrew wrench through the hole. Hook a soldering gun tip around the offset end of the Allen wrench and turn the gun on and off while applying slight turning force with the gun. Within about two minutes you can feel the slug turn. Do not apply nylon wrench until slug has cooled.

C. WALTER

Niagra Falls, N.Y.

Dear Editor:

I have had the problem of frozen cores many times, and I find it much cheaper and quicker to replace the coil. For the few times when a new replacement has been unavailable, I have used a similar coil from a junked set. I don't like to do this but it is sometimes necessary. I always notify the customer that I used an old part and that a new part is on order. The customer usually does not bring the set back when I notify him that the new part has arrived.

B. W. FOWLER

Lake View, Texas

FAST

COMPLETE OVERHAUL ON ALL MAKES OF TV TUNERS

Maximum Time In Shop 24 Hrs.

(WE SHIP C.O.D.)

\$9.50




Black & White or Color

VHF or UHF

UV Combo's \$15.00

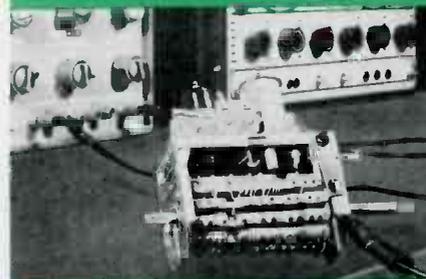Price includes all labor and parts except Tubes, Diodes & Transistors. If combo tuner needs only one unit repaired, disassemble and ship only defective unit. Otherwise there will be a charge for a combo tuner. Ship tuners to us complete with Tubes, Tube Shields, Tuner Cover and all parts (including) any broken parts. State chassis, model number and complaint.



All tuners are serviced by **FACTORY TRAINED TECHNICIANS** with years of experience in this specialized field. All tuners are **ALIGNED TO MANUFACTURERS SPECIFICATION** on crystal controlled equipment and air checked on monitor before shipping to assure that tuner is operating properly.

GEM CITY TUNER REPAIR SERVICE

Box 6C Dabel Station
2631 Mardon Drive
Dayton, Ohio 45420

Circle 50 on literature card

October, 1967/PF REPORTER 69

If You're Still Using A V.T.V.M. It's Time To Change ...Go Solid-State!

Kit
IM-16
\$44⁹⁵



Kit
IM-25
\$80⁰⁰
Wired
IMW-25
\$115⁰⁰

These New Heathkit® Solid-State Meters Feature State-Of-The-Art Performance At Prices You Can Afford

- Modern, stable, long-life solid-state circuitry
- New low-voltage ranges to accurately analyze modern transistor circuits
- Full capability to go "out on the job" . . . instant selection of internal battery power or 120/240 v. 50-60 Hz AC operation
- Exceptional accuracy . . . 3% on DC volts, plus a large, easy-to-read 6" meter face
- High impedance F.E.T. input for minimum circuit loading

A New! Deluxe Solid-State Volt-Ohm Meter
Features 8 DC and 8 AC voltage ranges from 0.5 v to 1500 v full scale; 7 ohmmeter ranges (10 ohms center scale) x1, x10, x100, x1k, x10k, x100k, & x1 megohm; 11 megohm input on DC ranges; 1 megohm on AC ranges; internal battery or 120/240 v 50-60 Hz AC power for portable or "in shop" use; large readable-across-the-bench 6" meter; separate switches for individual functions; single test probe for all measurements; modern, stable solid-state circuit-board construction.

Kit IM-16, 10 lbs. \$44.95

B New! Deluxe Solid-State Volt-Ohm-Milliammeter
All silicon transistors plus FET's. Features 9 AC and 9 DC voltage ranges from 150 mV to 1500 volts full scale; 7 ohmmeter ranges (10 ohms center scale) x1, x10, x100, x1k, x10k, x100k, & x1 megohm; 11 current ranges from 15 uA to 1.5 Amperes full scale; 11 megohm input on DC voltage ranges; 10 megohm input on AC voltage ranges; internal battery power or 120/240 v 50-60 Hz AC power for maximum versatility; easily readable 6" meter face; ±3% accuracy on DC volts; ±4% on DC current; ±5% accuracy on AC voltage and current; separate range switches "human engineered" for efficiency in actual use; modern circuit board construction; all solid-state components; easy to assemble.

Kit IM-25, 10 lbs. \$80.00
Wired IMW-25, 10 lbs. \$115.00



HEATH COMPANY, Dept. 25-10
Benton Harbor, Mich. 49022
In Canada, Daystrom Ltd.

Please send my FREE 1968 Heathkit Catalog.
 Enclosed is \$_____, plus postage.
Please send model(s) _____

Name _____
Address _____
City _____ State _____ Zip _____
Prices & Specifications subject to change without notice. TE-165

PHOTOFACT™ BULLETIN

PHOTOFACT BULLETIN lists new PHOTOFACT coverage issued during the last month for new TV Chassis. This is another way PF REPORTER brings you the very latest facts you need to keep fully informed between regular issues of PHOTOFACT Index Supplements issued in March, June, and September.

Admiral	Chassis H3-1A, H4-1A, 1H4-2A	909-1
Airline	GEN-8077A, GEN-8447A	907-1
Curtis Mathes	10M070	906-1
Motorola	Chassis 9TS-460A-09, C9TS-460A	911-1
	Chassis C/D18TS-594C/D, C22TS- 594/CD, D20TS-594C/D	910-1
Olympic	9P56, 9P57, 9P58	906-2
	9P59	908-1
Penncrest	4871B-48/72B-46/73B-46/74A-48/ 75A-46/76A-48/77A-48/78A-46, 4883A-48, 6881C-48, 6882C-49, 6882D-49, 6885A-46	906-3
RCA Victor	AJ005B, AJ009E/Y (Ch. KCS157A)	907-2
	Chassis CTC19C/D/U	909-2
Sharp	CN-32T	911-2
Sylvania	Chassis D02-7 thru D02-12	908-2
Symphonic	TCT195	910-2
Truetone	HFP3780A-76 (2DC3780)	910-3
Zenith	Chassis 20X1C36, 20X1C38	908-3
The following TV sets are given schematic coverage in the Extra Contents.		
Curtis Mathes	AG3223 (Ch. 12A8, 32)	906
RCA	Chassis CTC27A/B, CTC35A/B	907-9-S
Production Change Bulletins		
Airline	WG-4234B, WG-4334B	907-3
Coronado	TV2-9552B, TV2-9553B, TV2-9554B, TV2-9559B	907-3
Electrohome	A-092, AU-093, A-090, AU-019, A-094, AU-095	909-3
Olympic	Chassis NCP	909-3

BUY



ALL WEATHER
VINYL PLASTIC

ELECTRICAL TAPE

the first
all weather tape
at standard
tape prices

NOW at your
local
GE Distributor

Insulating Materials Dept.

GENERAL ELECTRIC

846-02

Circle 52 on literature card

INDEX TO ADVERTISERS

October, 1967

Amphenol Corp.	23
ATR Electronics Inc.	71
B & K Mfg. Co., Div. of Dynascan Corp.	21, 57, 66
Bussmann Mfg.	14, 15
Castle TV Tuner Service, Inc.	13
Cleveland Institute of Electronics	31
Columbia Wire Products Co.	36
Delco Radio Division	59
Delhi Metal Products, Inc.	62
Eico	1
Eight Ball Co.	36
Enterprise Development Corp.	68
The Finney Co.	54
G. C. Electronics	56
Gem City Tuner Repair Service	69
General Electric Co.	24, 24a, 71
Heath Co.	70
Jackson Electrical Instrument Co.	58
Jerrold Electronics Corp.	Cover 2
JFD Electronics Co.	44
Leader Electronics Corp.	61
Lectrotech, Inc.	64, 65
Litelfuse, Inc.	Cover 4
Mallory, P.R. & Co., Inc.	29
Multicore Sales Corp.	60
National Radio Institute	63
Phileo-Ford Co.	40
Precision Tuner Service	60
RCA Components & Devices (Entertainment Tubes)	Cover 3
RCA Components & Devices Test Equipment)	55
RCA Parts & Accessories	49
RCA Institutes, Inc.	48
RMS Electronics, Inc.	58
S & A Electronics, Inc.	67
Sams, Howard W. & Co., Inc.	51, 68
Sarkes Tarzian, Inc.	5
Seco Electronics Corp.	60, 69
SENCORE, Inc.	35, 37, 39, 41, 45, 47, 53
Sprague Products Co.	3
Superior Tuner Service	38
Sylvania Electric Products Corp.	42, 43
Tripplett Electrical Instrument Co.	27
Vector Electronic Co., Inc.	66
Weller Electric Corp.	50
Windso Electronics	67
Winegard Co.	46
Workman Electronic Products, Inc.	71
Xcelite, Inc.	38
Zenith Sales Corp.—Parts & Accessories	30, 52

ATR PRODUCTS FOR MODERN LIVING



ATR UNIVERSAL INVERTERS
A.C. Household Electricity Anywhere - in your own car, boat or plane!
- Tape Recorders - TV Sets
- Dictating Machines - Radios - Public Address Systems - Electric Shavers - Record Players - Food Mixers - and Emergency Lighting. **NET**
12U-RHG (12 V.) 150 to 175 W. Shp. Wt. 27 lbs. \$73.00
28U-RHG (28 V.) 150 to 175 W. Shp. Wt. 27 lbs. \$87.50



ATR "A" BATTERY ELIMINATOR

For Demonstrating and Testing Auto Radios—**TRANSISTOR or VIBRATOR OPERATED!**
Designed for testing D.C. Electrical Apparatus on Regular A.C. Lines.

MAY ALSO BE USED AS A BATTERY CHARGER
MODEL 610C-ELIF ... 6 volts at 10 amps. or 12 volts at 6 amps. Shipping weight 22 lbs.
USER NET PRICE \$55.00

ATR AUTO RADIO and COMMUNICATION

LONGER-LIFE VIBRATORS



"The Best by Test!"

SEE YOUR ELECTRONIC PARTS DISTRIBUTOR OR WRITE FACTORY FOR LITERATURE & DEALER PRICES

ATR ELECTRONICS, INC.

Quality Products Since 1931
St. Paul, Minnesota 55101—U.S.A.

Circle 54 on literature card

BUZIT TRANSISTORIZED SIGNAL TRACER

FOR ONLY **\$9.57** DEALER NET WITH BATTERIES



NO CLIPS
NO WIRES

MADE IN U.S.A.

USED FOR TROUBLE SHOOTING

- A.F. CIRCUITS • I.F. CIRCUITS
- R.F. CIRCUITS • CONTINUITY CHECKS • SPEAKERS, ETC.

EXCELLENT FOR TRANSISTOR RADIOS BECAUSE BUZIT USES ONLY A 3 VOLT POWER SUPPLY


ASK YOUR ELECTRONIC PARTS DISTRIBUTOR FOR

WEP MODEL NO. BZ-1

MANUFACTURED BY **WORKMAN Electronic PRODUCTS INC.**
TARASOTA FLORIDA

Circle 53 on literature card

October, 1967/PF REPORTER 71

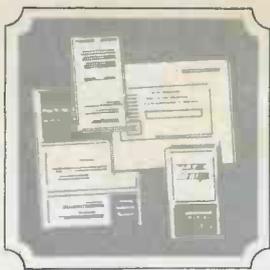

\$ FREE \$

CATALOG AND LITERATURE SERVICES

*CHECK "INDEX TO ADVERTISERS" FOR FURTHER INFORMATION FROM THESE COMPANIES

ANTENNAS

75. **ALLIANCE** — Colorful 4-page brochure describing in detail all the features of Tenna-Rotors.
76. **BLONDER-TONGUE** — Colorful new flyer describes line of solid-state UHF converters for adding channels 14-83 to VHF TV receivers.
77. **CORNELL-DUBILIER** — New 4-page brochure with instructions for installation of AR10B Skyline Series rotor.*
78. **DELHI**—Twelve-page catalog introducing a complete new line of home TV towers, ham towers, citizen's band towers, masts and telescoping masts.
79. **FINNEY** — 4-color brochure with description and technical details on new Finco color spectrum frequency dependent antennas for UHF-VHF-FM, and UHF. Form 20-413.
80. **JERROLD** — New 4-page full-color catalog describes the new Paralog Plus antennas.*
81. **JFD** — Color Laser and LPV antenna brochures. New 1967 dealer catalog covering complete line of log-periodic outdoor antennas, rotors, and accessories.
82. **MOSLEY** — Information on new Mosley MATV system for up to 8 TV/FM sets. Includes TV antenna, distribution system and outlets.
83. **RMS ELECTRONICS** — Color brochures describing Super Transpower'D and Dynergy VHF, UHF, FM antennas, Mystic and Mark indoor antennas, solid state antenna boosters, amplifier-4-set coupler, UHF converters, antenna replacement rods, splitters and couplers.
84. **SPAULDING** — Brochures about EP series economy-priced towers.
85. **WINEGARD** — New 40-page MATV catalog features Ultra-Plex amplifier system and installation instructions.

AUDIO

86. **ATLAS SOUND** — Catalog 567 illustrates complete line of speakers, horns, microphone stands and booms, transformers, patio speakers, and accessories.
87. **ELECTRO-VOICE**—Catalog 167 on microphones and PA equipment.
88. **OXFORD TRANSDUCER** — Bulletin A-109 features speaker installation in automobiles, hospitals, and recreation rooms.
89. **SHURE** — Catalogs AL310, AL314, and AL318 about microphones for mobile communications, PA, and special purposes.
90. **SWITCHCRAFT**—Bulletin 172 describes Model 307TR, a new battery operated mixer for studio, home, or remote use.
91. **UNIVERSITY SOUND** — PA, Hi-Fi, and microphone catalogs, plus "Technigram" with graph showing what size amplifier to use in a given area.

COMMUNICATIONS

92. **AMPHENOL** — 2-color spec sheets on new Model 650 CB transceivers and Model C-75 hand-held transceiver.
93. **GOLD LINE CONNECTORS** — Catalog 207 about connectors, antennas, and accessories for Ham and CB use.
94. **E. F. JOHNSON** — Catalogs of the complete line. Covers components, CB, business, and industrial radio.

95. **MOTOROLA** — New brochure tells how to reach people on-the-move through use of personal two-way radio.
96. **POLYTRONICS** — Brochures on several CB transceivers and accessories, including TC1 and TC7 selective tone callers.

COMPONENTS

97. **BELDEN** — Catalog 867, a 56-page catalog of the complete Belden line.
98. **BUSSMANN** — Small TV Fuse leaflet designed to fit pocket or tool kit, shows list prices of fuses most commonly used in TV sets. Ask for BUSS Leaflet TVLP.
99. **CENTRALAB**—24-page replacement parts catalog No. 33GL.
100. **CHICAGO MINIATURE LAMP WORKS** — Specifications of miniature lamps and barretters are included in catalog CM-1. Catalog CMT-2 lists specs of subminiature lamps.
101. **GC** — FR-029E wall chart of industrial electronic components.
102. **LITTELFUSE** — Pocket-sized TV circuit breaker cross-reference gives the following information at a glance. Manufacturer's part number, corresponding Littelfuse part number, price, color or b/w designation. A second glance gives trip ratings and acquaints you with a line of caddies. Ask for CBCRP.
103. **MALLORY** — Bulletin 4-82 describes radial and axial lead tantalum capacitors.
104. **MILLER** — 4-page cross-reference guide to color TV sweep, convergence, and linearity coils.
105. **QUAM-NICHOLS** — Complete replacement information on auto radio speakers 1955-1967.
106. **SPRAGUE** — C617, a complete catalog of the Sprague line.
107. **TEXAS CRYSTALS** — 12-page catalog of crystals including engineering data, specifications and prices.

SERVICE AIDS

108. **CASTLE TUNER** — How to get fast overhaul service on all makes and models of television tuners is described in leaflet. Shipping instructions, labels, and tags are also included.
109. **ELECTRONIC CHEMICAL** — Catalog sheets on aerosol sprays for servicemen.
110. **G.C.** — FR-67G flyer on color harnesses. FR-67A complete Audio-tex catalog.
111. **INJECTORALL** — New 1967 catalog of chemicals and alignment tools.
112. **MIDSTATE TUNER** — 24-hour service on any make tuner is described in a colorful brochure.
113. **PERMA-POWER** — Catalog sheet describes new isolation boosters for color TV.
114. **VECTOR** — Short-form catalog lists current measuring and socket change adaptors, Vectorboard, terminals and accessories.

SPECIAL EQUIPMENT

115. **ATR** — Literature about DC-AC inverters up to 600 watts load.
116. **CBC** — Catalog of power controls.
117. **PHILMORE** — Supplement No. 671 about tuners, kits, remote controls, etc.
118. **WINDSOR ELECTRONICS** — Booklet entitled "The Open Door to TV Profits."

TECHNICAL PUBLICATIONS

119. **ALCO ELECTRONICS**—28 design ideas for use with isolation relays.
120. **CLEVELAND INSTITUTE OF ELECTRONICS** — Free illustrated brochure describing electronics slide rule and four lesson instruction course.
121. **3 M COMPANY** — "Taping Tips for Electronic Servicing," a 32-page booklet for professionals and hobbyists.
122. **PHILCO** — Information about Tech Data & Business Management service. Also, free parts catalog.
123. **RCA INSTITUTES** — New 1967 career book describes home study programs and courses in television (monochrome and color), communications, transistors, industrial, and automation electronics.
124. **SAMS, HOWARD W.** — Literature describing popular and informative publications on radio and TV servicing, communications, audio, hi-fi, and industrial electronics, including special new 1967 catalog of technical books on every phase of electronics.

TEST EQUIPMENT

125. **B & K** — New 1967 catalog featuring test equipment for color TV, auto radio, and transistor radio servicing, including tube testers designed for testing latest receiving tube types.
126. **COLETRONICS** — Flyer sheet about a new tube-tester adaptor.
127. **EICO** — New spec sheet describes model 100M4 multimeter with DC sensitivity of 100K ohms per volt.
128. **HICKOK** — Quick reference catalog No. 67D gives brief descriptions and prices for complete test equipment line. Also, specification data on Models CR-35 CRT tester, GC-660 color generator, and 860 Injecto-Tracer.
129. **JACKSON** — New catalog showing 5 new "Service Engineered" test instruments.
130. **LECTROTECH**—Two-color catalog sheet on new Model V6-B color bar generator, the latest improved model of the V6. Gives all specs and is full illustrated.
131. **MERCURY** — All-new 16-page test instrument catalog.
132. **PRECISION APPARATUS**—Illustrated catalog describing signal generators, oscilloscopes, and meters.
133. **SECO** — Operating manual for the HC8 in-circuit current checker.
134. **SENCORE** — 8-page full color catalog plus a new 4-page supplement catalog.
135. **SIMPSON** — Catalog 2076 featuring a VOM with a temperature range and a 22-range VOM chart recorder.
136. **TRIPLETT** — Literature sheet on the new model 600 transistorized VOM.

TOOLS

137. **ARROW**—Catalog sheet showing 3 staple gun tackers designed for fastening wires and cables up to 1/2" diameter.
138. **BURNS** — Catalog sheet on pin crimpers for making repairs to picture tubes and installing cable on standard phono plugs.
139. **DIAMOND** — 16-page booklet, W-68, lists wrenches, pliers, snips, and electronic tools.
140. **ENTERPRISE DEVELOPMENT**—Time-saving techniques in brochure from Endeco demonstrate improved desoldering and resoldering methods for speeding and simplifying operations on PC boards.
141. **KRAEUTER** — Tool selection guide describes entire plier and wrench line.
142. **VACO** — Catalog SD-66X describes 5 tools available with imprinting for promotional use.
143. **XCELITE** — Bulletin N567 lists two sets of nut drivers with color coded handles and plastic cases.

TUBES AND TRANSISTORS

144. **RADIO CORP. OF AMERICA** — PUX 300, a 12-page product guide on RCA picture tubes, covering both color and black-and-white. Includes characteristics chart, terminal diagrams, industry replacement, and interchangeability.

USE THE HANDY CARD BELOW TO OBTAIN FREE CATALOGS & LITERATURE

As a service to its readers, PF REPORTER makes this postpaid card available for your convenience in obtaining current manufacturers' literature.

To use the card simply:

- a. Circle the numbers corresponding to the numbers of the items appearing either on page 72 or in the "Product Report" department.
- b. Print your name and address and check your occupation.
- c. Include ZIP code—requests may not be filled without it.
- d. Tear out lower half of this insert and place in mailbox.

Note the deadline date — Requests received after this cannot be handled.

Subject Index on Reverse Side

OCTOBER, 1967
OFFER EXPIRES JANUARY 1, 1968

1	2	3	4	5	6	7	8	9	10	11	12
23	24	25	26	27	28	29	30	31	32	33	34
45	46	47	48	49	50	51	52	53	54	55	56
67	68	69	70	71	72	73	74	75	76	77	78
89	90	91	92	93	94	95	96	97	98	99	100
111	112	113	114	115	116	117	118	119	120	121	122
133	134	135	136	137	138	139	140	141	142	143	144
155	156	157	158	159	160	161	162	163	164	165	166

Print plainly or type below

Name _____

Firm _____

Firm Address _____

City _____ State _____ Zip _____

Did you receive this issue through

Distributor Subscription

Subscription Offer

Enter my subscription to PF REPORTER

3 Years \$10.00 2 Years \$8.00 1 Year \$5.00

Bill Me Remittance Enclosed

Extend Present Subscription

BOOK REVIEW
 Single Sideband: Theory and Practice 41
B-W TELEVISION
 Highlight of 1968 TV Lines 4
BUSINESS
 Credit abuses, protecting against 52

COLOR TELEVISION
 Color sync poor, Sylvania
 Chassis D01 and D02 CCM 62
 Contrast lost, RCA Chassis CTC11 CCM 61
 Green screen on color program, Zenith
 Chassis 24NC312 and 25N38 CCM 61
 Hue control action reversed,
 Zenith Chassis CCM 62
 Multiple ghosts, unevenly spaced,
 all chassis CCM 62
 Service Training—Part 3
 —horizontal AFC and oscillator 20
 —horizontal output and high voltage 22
 —horizontal phase detector 19
 —vertical deflection 17

GUIDES:
 Tube Substitution Supplement a
PHOTOFAC BULLETIN
 906 through 911 70
 906 through 911 70
RADIO/PHONO
 AM-FM/ stereo 36
 —audio stages, checking 36
 —circuit analysis 32
 —distortion and low. garbled volume,

TELEVISION SERVICING
 Raster, boost, and high voltage missing,
 Zenith Chassis 14M20 TS 48
 Vertical roll, Zenith Chassis 14L20 TS 47
 Vertical sync poor,
 Zenith Chassis 14M21/X TS 45
 Wavy screen pattern,
 Satchell Carlson Chassis TS 47

TEST EQUIPMENT
 Amphenol Model 870 Voltohmmeter NTE 28

THEORY
 RC Circuits 38
 (Note: Code letters CCM, NTE, and TS
 indicate *Color Countermeasures, Notes on
 Test Equipment, and The Troubleshooter,*
 respectively.)

FIRST CLASS

PERMIT No. 1076

Indianapolis, Ind.

REPLY MAIL

Delivered in the United States

POSTAGE PAID BY—

PF Reporter Service Dept.


REPORTER

62ND STREET

INDIANAPOLIS, IND. 46206

Get on board RCA's Gift-Time Special for 71 valuable prizes

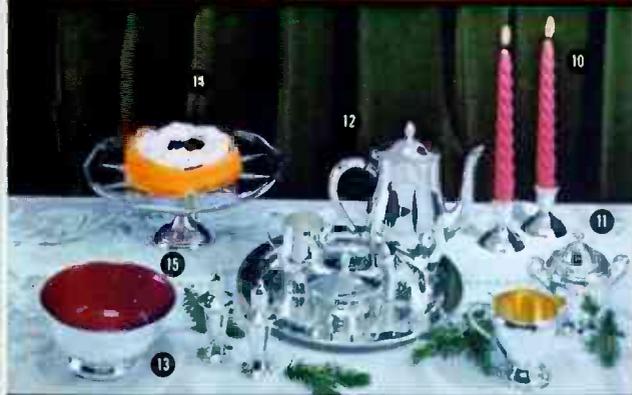FREE with your purchases of RCA receiving tubes



RCA's "Gift-time Special" certificates bring you great premiums for Christmas gift giving for the entire family. These valuable certificates are FREE WITH YOUR PURCHASES OF RCA RECEIVING TUBES from your participating RCA Tube Distributor. (Optional with RCA Tube Distributors.)

1. Argus Electromatic Slide Viewer. 51-126. 43 Cert. 2. Polaroid 215 Color-Pack Camera. 51-170. 155 Cert. 3. Polaroid Flash Gun Attachment. 51-174. 22 Cert. 4. Toastmaster "Sovereign" Automatic Toaster. 35-80. 51 Cert. 5. Rival Slimline Electric Knife. 35-141. 33 Cert. 6. West Bend 8-Cup Automatic Aluminum Percolator. 35-73. 27 Cert. 7. Man's Elgin "Armada" 17-jewel Watch. 53-80. 61 Cert. 8. Longines-Wittnauer Man's Watch. 53-11. 146 Cert. 9. Hickock Man's Alligator Belt. 20-765. 36 Cert. 10. Sterling Silver Candlesticks. 52-25. 15 Cert. 11. Star Rogers and Bros. Silverplate "Starlight" by The International Silver Company. 52-45. 37 Cert. 12. Oneida 4 pc. "Paul Revere" Coffee Service. 52-46. 81 Cert. 13. Sterling Silver Salt and Pepper Shakers. 52-26. 15 Cert. 14. Sterling Silver and Crystal Cake Plate. 52-75. 17 Cert. 15. Reed and Barton Color-Flared "Paul

Revere" Bowl. 52-96. 29 Cert. 16. Man's Alligator Raincoat. 20-568. 103 Cert. 17. Lady's Alligator Raincoat. 20-571. 103 Cert. 18. Lady's Twin-Pearl Ring. 49-147. 39 Cert. 19. Lady's Linde Star Ring. 49-149. 105 Cert. 20. Hamilton "Loralie" Lady's Watch. 53-65. 133 Cert. 21. "Buddy L" Aerial Ladder Fire Engine. 48-90. 18 Cert. 22. Toddler's "Tiger Trike". 47-51. 16 Cert. 23. "Buddy L" Sit N Ride Truck. 48-207. 19 Cert. 24. "Kiss Me" Doll. 48-137. 13 Cert. 25. Cosco Doll High Chair. 48-43. 10 Cert. 26. "Drink and Wet" Doll and Cradle. 48-139. 13 Cert.

AND THESE ARE JUST A FEW OF THE 71 EXCITING GIFT PREMIUMS AVAILABLE! Get RCA "Gift-time Special" certificates FREE with your purchases of RCA receiving tubes from your participating RCA Tube Distributor.

RCA Electronic Components and Devices, Harrison, N.J.



The Most Trusted Name in Electronics

See the caddy



See the fuse box
through the caddy



See the fuses
through the
fuse box
through the caddy



See more profits through

LITTELFUSE

DES PLAINES, ILLINOIS

Circle 55 on literature card