

# PF Reporter®

PHOTOFACT

*the magazine of electronic servicing*



## SEASONS GREETINGS




*The ring of the axe stings the cold silence as falling snow from shaking branches tingles against the cheek. When the tree is felled and loaded, we are homeward bound with snow crinkling beneath chilled steel and the foggy breath of spirited boys telling of their labor.*

- DC Voltage Distribution in Transistor Circuitry
- Installing Intercom & Music Distribution Systems
- Know Your '68 Color Circuits—Part 2
- Notes on Test Equipment
- Keyed AGC—a review

SAVUEL SACHS  
2244 NORTH 10TH ST.  
PHILADELPHIA, PA. 19133

IA 50 3879 568

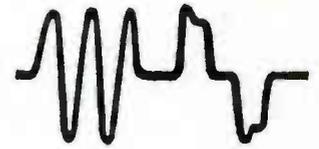

## Remember to ask—"What else needs fixing?"



That's the question to ask to add extra profit to every service call. It makes sense. Just about every customer who calls you for TV repair owns other electronic products that are excellent prospects for service. You've already invested your time getting to his home. So why not see what further service you can render?

Does it work? You bet! On a test program sponsored by Electronic Industries Association, in which Mallory is an active member, service men got 6% more profit from business they added just by asking that simple question.

Here are some tips that you can use to cash in on this idea.

Portable radios, for instance. Most homes have at least one. Ask 'em, "How about fresh batteries?" And then sell Mallory Duracell® batteries . . . best buy in long life and fade-free power. And don't forget cameras, flashlights and toys. They need batteries, too, and there's a Duracell type for every job.

Ask to check table radios . . . then listen for hum as the set warms up. Many people put up with hum because they've forgotten how well the radio sounded when new. But hum may be a sign that a filter capacitor is near the end of its life. Replace with a Mallory FP, WP, TC or MTA. Your Mallory Distributor can supply the exact size and rating you need.

How about hi-fi and stereo? Ask to turn them on, and see if you detect anything that calls for service. You can suggest adding remote speakers for a porch or family room. Be sure to include a Mallory balance control and remote volume controls, to make the installation complete. Record changers and electronic organs are good service opportunities, too.

Try this profit-building "What else needs fixing?" idea on the next calls you make. And for the quality components that make every job sure, see your Mallory Distributor. Mallory Distributor Products Company, a division of P. R. Mallory & Co. Inc., Indianapolis, Indiana 46206.

©Duracell is a registered trademark of P. R. Mallory & Co. Inc.



Circle 1 on literature card

# EICO Makes It Possible

You get 100% professional test equipment quality—and economy. EICO's uncompromising engineering-for-value makes it possible. Twenty-three years ago we started EICO to deliver "Laboratory Precision at Lowest Cost." Today, three million customers like us for it. Compare EICO products with *anybody's* at your local dealer. You'll see for yourself how you save up to 50% with EICO kits and wired equipment—and enjoy electronic excellence too!

- 1/2-volt Full-Scale DC Transistor Servicing Range. Accurate measurements down to 0.01 volts.
- Deluxe full-view 6" 200 microamp meter movement.
- Unique ease & speed by exclusive color coding of switches with meter scales.
- Dual purpose EICO exclusive AC/DC Uni-Probe.®
- Signal isolation floating ground.



## NEW EICO 235 PROFESSIONAL VTVM

Feature-packed 6" professional VTVM brings you more in functional styling, convenience, and dependable performance for exacting measurements in solid state circuitry.

8 DC Ranges: 0-0.5-1.5-5-15-50-150-500-1500 (to 30,000 volts with optional high voltage probe). 7 AC Peak-to-Peak Ranges: 0-4-14-42-140-1400-4200. 7 AC RMS Ranges: 0-1.5-5-15-50-150-500-1500. 7 Resistance Ranges Covering: 0.2Ω to 1000MΩ. Frequency Response: 3 cps to 3Mc ±1db (up to 250Mc with optional PRF probe). Input Resistance: DC 11MΩ; AC 1M shunted by 60mmf. 1% precision multiplier resistors. 3% accuracy on AC and DC scales.

**Kit 49.95**

Wired \$69.95

Terrific time-saver! Only 1 probe performs all functions — a half-turn of probe-tip selects DC or AC-OHMS!

## TRUVOHM PROFESSIONAL PORTABLE MULTIMETERS by EICO.

The industry's greatest V-O-M values. Designed & manufactured to Eico's high standards of professionalism. Each complete with batteries & test leads. Backed 100% by famous EICO warranty.

100,000 Ohms/Volt Model 100A4, \$34.95  
optional carrying case \$5.95  
The best buy in a bench-size multimeter. With AC sensitivity 12,500Ω/V, combines minimal circuit loading with wide-ranging functional utility. Double-jewelled ±2% D'Arsonval meter movement; full-view 4-inch mirror-back two-color scale eliminates reading parallax; matched pair of silicon diodes prevents accidental overload of meter movement. High-impact, custom-molded case protects against shock



30,000 Ohms/Volts Model 30A4 \$19.95



30,000 Ohms/Volts Model 30A3 \$15.95



20,000 Ohms/Volts Model 20A3 \$12.95



4,000 Ohms/Volts Model 4A3, \$8.95



1,000 Ohms/Volts Model 1A1, \$5.95

### ATTENTION EICO TUBE TESTER OWNERS:

NEW TUBE DATA AND SUBSCRIPTION PLAN NOW AVAILABLE FOR ALL MODELS. Write To: EICO Tube Data Division, 1744 Rockaway Ave., Hewlett, N. Y. 11557



Model 232 Peak-to-Peak VTVM. A must for color or B&W TV and industrial use. 7 non-skip ranges on all 4 functions. With exclusive Uni-Probe.® \$29.95 kit, \$49.95 wired.



New Model 567 VOM Kit \$34.95 Wired \$44.95

- 20,000 ohms-per-volt sensitivity
- 0.25 volt full-scale range
- Silicon diode meter protection circuit

DCV: 0-0.25, 2.5, 10, 50, 250, 1000, 5000V. ACV: 0-2.5, 10, 50, 250, 1000, 5000V. DCI: 0-50 uA, 1 mA, 10 mA, 100 mA, 500 mA, 10 amps. -12 to +55 db in 5 ranges. RES: 0-2KΩ, 200KΩ, 2MΩ.



laboratory precision at lowest cost.



Model 460 Wideband Direct-Coupled 5" Oscilloscope. DC-4.5mc for color and B&W TV service and lab use. Push-pull DC vertical amp., bal. or unbal. input. Automatic sync limiter and amp. \$109.95 kit, \$149.95 wired.



Model 369 Sweep and Post-Injection Marker Generator. For easiest, fastest visual alignment of color B & W TV and FM RF and IF circuits. Five sweep ranges from 3-220 Mc/S. Four marker ranges from 2-225 Mc/S. Crystal marker oscillator. Post injection of markers. Kit \$99.95. Wired \$149.95

### FREE 1968 CATALOG PFR-12

EICO Electronic Instrument Co., Inc. 283 Malta Street, Bklyn., N.Y. 11207

Send me FREE catalog describing the full EICO line of 200 best buys, and name of nearest dealer.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_  
State \_\_\_\_\_ Zip \_\_\_\_\_

PUBLISHER  
HOWARD W. SAMS

GENERAL MANAGER  
DONALD W. BRADLEY

EDITOR  
WILLIAM E. BURKE

MANAGING EDITOR  
JAMES M. MOORE

ASSOCIATE EDITORS      CONSULTING EDITORS  
Thomas T. Jones      Joe A. Groves  
J. W. Phipps      C. P. Oliphant  
Carl F. Moeller      George B. Mann

PRODUCTION MANAGER      RESEARCH LIBRARIAN  
Susan M. Hayes      Mrs. Bonny Howland

CIRCULATION MANAGER  
Pat Osborne

ART DIRECTORS  
Louis J. Bos, Jr. & Robert W. Reed

PHOTOGRAPHY  
Paul Cornelius, Jr.

ADVERTISING SALES OFFICES

*Midwestern Regional Sales Manager*

ROY HENRY

Howard W. Sams & Co., Inc., 4300 W. 62nd St.  
Indianapolis, Ind., 46206 • 317-291-3100

*Eastern Regional Sales Manager*

ALFRED A. MENEGUS

Howard W. Sams & Co., Inc., 3 W. 57th St.  
New York, New York, 10019 • 212-688-6350

*Southwestern Regional Sales Manager*

MARTIN TAYLOR

P. O. Box 22025, Houston, Texas 77027  
713-621-0000

*western/Los Angeles*

G. R. HOLTZ

The Maurice A. Kimball Co., Inc.  
2008 W. Carson St., Suites 203-204  
Torrance, Calif., 90501 • 213-320-2204

*western/San Francisco*

The Maurice A. Kimball Co., Inc.

580 Market St., Room 400  
San Francisco, Calif., 94104 • 415-392-3365

Address all correspondence to PF REPORTER  
4300 W. 62nd Street, Indianapolis, Indiana 46206



Copyright © 1967 by Howard W. Sams & Co., Inc. PF REPORTER is a trademark of Howard W. Sams & Co., Inc. No part of PF REPORTER may be reproduced without written permission. No patent liability is assumed with respect to use of information herein. Acceptance of advertising does not in any manner signify the products, policies and services so advertised have been approved, endorsed or recommended by this magazine.

Subscription Prices: 1 year—\$5.00, 2 years—\$8.00, 3 years—\$10.00, in the U. S. A., its possessions and Canada.

All other foreign countries: 1 year—\$6.00, 2 years—\$10.00, 3 years—\$13.00. Single copy 75¢; back copies \$1.

Indexed in Lectrodex. Printed by the Waldemar Press Div. of Howard W. Sams & Co., Inc.

# PF Reporter®

PHOTOFACT

*the magazine of electronic servicing*

VOLUME 17, NO. 12

DECEMBER, 1967

## CONTENTS

<b>Tube Substitution Supplement</b>		<b>a</b>
<b>DC Voltage Distribution in Transistor Circuitry</b>	Robert G. Middleton	<b>4</b>
<small>Quicker Servicing—In-circuit tests to evaluate transistor performance.</small>		
<b>Letters to the Editor</b>		<b>8</b>
<b>The Electronic Scanner</b>		<b>9</b>
<b>Know Your '68 Color Circuits—Part 2</b>	J. W. Phipps	<b>12</b>
<small>More details on the new circuits</small>		
<b>Installing Intercom and Music Distribution Systems</b>	Louis M. Dezettel	<b>24</b>
<small>A few tips to get you started in this lucrative business</small>		
<b>Keyed (Gated) AGC — a Review</b>	Ellsworth Ladyman	<b>30</b>
<small>A clear explanation of how these circuits function, with troubleshooting tips.</small>		
<b>Book Review</b>		<b>36, 62</b>
<b>Notes on Test Equipment</b>	T. T. Jones	<b>40</b>
<small>Lab report on the SENCORE CR13 CRT tester and the Triplett Model 600 FET meter.</small>		
<b>PHOTOFACT BULLETIN</b>		<b>52</b>
<b>Color Countermeasures</b>		<b>53</b>
<b>The Troubleshooter</b>		<b>55</b>
<b>Product Report</b>		<b>58</b>
<b>Free Catalog and Literature Service</b>		<b>64</b>
<b>Monthly Index on Free Literature Card</b>		

## ABOUT THE COVER

The scene depicted on this month's cover represents one of many traditions associated with the holiday season. Although the mode of transportation has changed and the tree purchased from a super market or tree lot, the significance of this and most other Yule traditions has not diminished. The editor and staff of PF REPORTER wish to extend to each of our readers and to every member of the electronics industry a Merry Christmas and prosperous New Year.



# SOME SHOP OWNERS DO MORE BUSINESS THAN OTHERS BY DOING BASIC THINGS LIKE THESE:




1 Reading what's new in leading technical magazines.



2 Keeping their trucks ready to roll at a moment's notice.



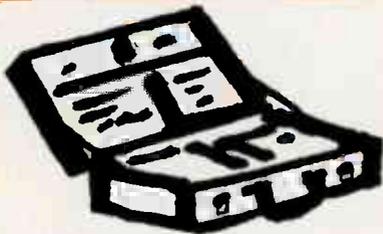
3 Arranging to have their phones answered promptly.



4 Making sure their caddies are organized and properly stocked.



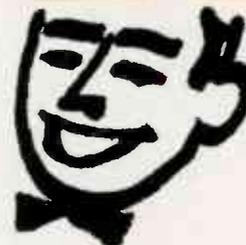5 Keeping accurate track of their time on each job.



6 Smiling . . . often . . . both on and off the job.



DIFILM® ORANGE DROP® . . .  
The world's finest  
radial-lead capacitor

DIFILM® BLACK BEAUTY® . . .  
Ultimate in molded tubulars



## 7 INSTALLING SPRAGUE DIFILM® CAPACITORS

These two great Sprague capacitors are expressly made for men who are in the TV service business to do business . . . as it should be done. Both feature the ultimate in tubular capacitor construction to keep you out of call-back trouble:

- Dual dielectric . . . combine best properties of both polyester film and special capacitor tissue.
- Impregnated with HCX® to provide rock-hard capacitor section.
- Because impregnant is solid, there's no oil to leak, no wax to drip.
- Designed for 105° C (220° F) operation without voltage derating.

For complete listings, ask your Sprague distributor for Catalog C-617, or write to Sprague Products Company, 105 Marshall Street, North Adams, Massachusetts 01247.

### DIFILM® ORANGE DROP® Dipped Tubular Capacitors

A "must" for applications where only radial-lead capacitors will fit. Perfect replacements for dipped capacitors used in most leading TV sets. No other dipped tubular capacitors can match them. Double-dipped in rugged epoxy resin for positive protection against extreme heat and humidity.

### DIFILM® BLACK BEAUTY® Molded Tubular Capacitors

World's most humidity-resistant molded capacitors. Feature tough, protective outer case of non-flammable molded phenolic . . . which cannot be damaged in handling or installation. Will withstand the hottest temperatures of any radio or TV set . . . even in the hottest, most humid climates.


**DON'T FORGET TO ASK YOUR CUSTOMERS  
"WHAT ELSE NEEDS FIXING?"**

Circle 3 on literature card



# UNDERSTANDING DC VOLTAGE DISTRIBUTION

## in TRANSISTOR CIRCUITRY

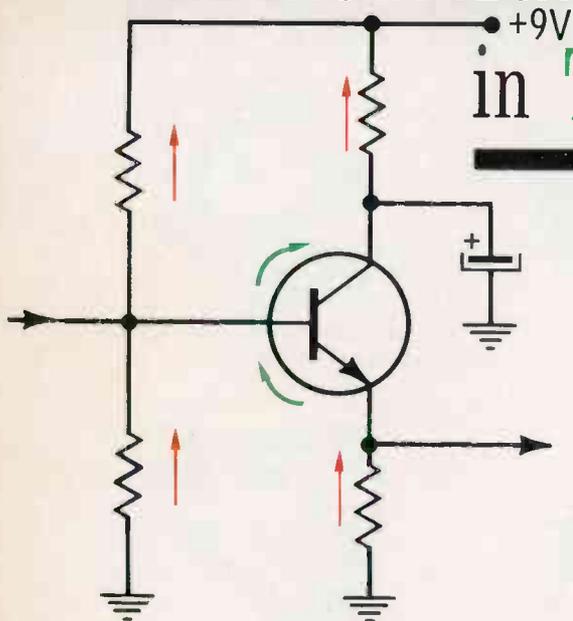

□ Defects within a transistor produce predictable changes in its electrode voltages.

This fact, when combined with an understanding of transistor action and proper testing methods, makes transistor servicing almost easy.

by Robert G. Middleton

DC voltage values in transistor circuits often seem to disobey ohm's law. However, when the circuit action is fully evaluated, we find that the voltages do follow the usual rules. It is essential to understand DC voltage distribution in transistor circuitry, to avoid unnecessary occurrence of "tough dog" jobs.

When a transistor becomes defective, its electrode voltages change. This is the most practical way to pinpoint a defective transistor. For example, Fig. 1A shows a typical NPN transistor in an IF stage. Insofar as DC voltage distribution is concerned, we may consider the circuit to be simplified, as depicted in Fig. 1B. The DC voltage distribution may be tabulated as follows:

Emitter-Ground .....	-4.5 volts
Base-Ground .....	-4.3 volts
Collector-Ground .....	0 volts
Emitter-Base .....	-0.2 volts
Collector-Base .....	-4.3 volts

### Collector Junction Leakage

One of the most common transistor defects is leakage from collector to base (leakage through the collector junction.) This leakage affects the circuit the same as if a resistor were connected between collector and base, as shown in Fig. 2. This leakage resistance draws current from the voltage divider that biases the base of the transistor, and the base voltage decreases. This base-voltage decrease also affects the emitter voltage as follows:

1. A decrease in base voltage increases the emitter-base bias voltage.
2. Increase in emitter-base bias voltage causes the collector current to increase.
3. Since the increased collector current flows through the emitter resistor, the drop across the emitter resistor increases.
4. Increased voltage drop across the emitter resistor causes the emitter voltage to decrease.

In the example of Fig. 2, the 100-k leakage between collector and base causes both the emitter voltage and the base voltage to decrease by 0.15 volt. Therefore, the emitter-base bias voltage has remained unchanged, although the transistor is drawing more current. If the leak-

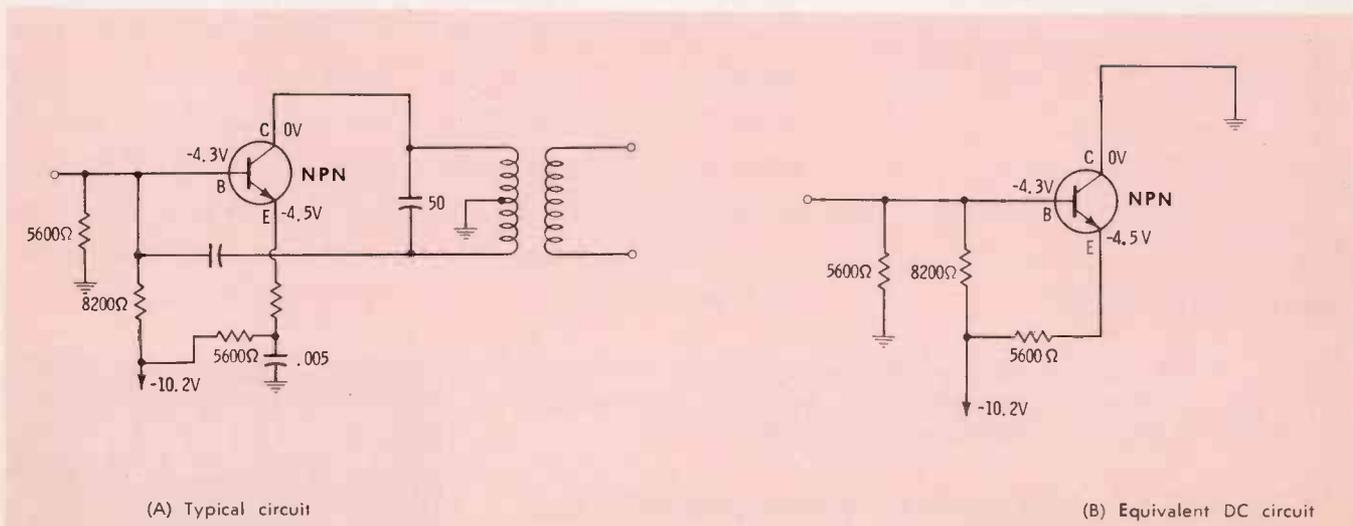


Fig. 1. Transistor IF circuit.

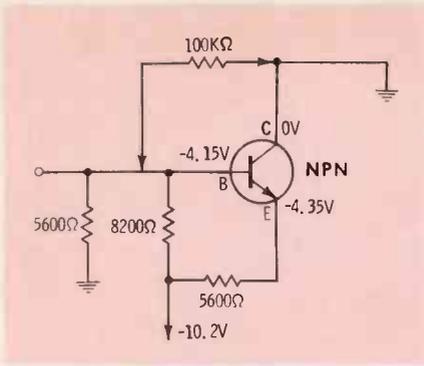


Fig. 2. The equivalent circuit with collector leakage.

age becomes excessive, the collector junction will overheat. The transistor then becomes open or shorted and the stage is dead. Moderate amounts of leakage usually cause gain reduction.

### Open and Shorted Collector Junctions

Let us consider the DC voltage distribution in our basic circuit in case the collector-base junction is short-circuited. In this case, the base voltage will be zero. Since the emitter-base junction has a very low forward resistance, the emitter current flow is practically equal to the supply voltage divided by the emitter resistance, or 1.8 ma in accordance with Ohm's law. The emitter-base bias voltage will rise somewhat above its normal value of 0.2 volt, but the emitter-base junction will not be damaged.

On the other hand, suppose that the collector-base junction is open. In such case, the collector circuit does not load the bias circuit, and the emitter voltage rises to -6.5 volts, while the base voltage rises to -6.3 volts. Accordingly, the

emitter-base bias voltage remains normal, and the emitter-base junction is not damaged.

In summary, collector leakage, or open or shorted collector junctions show up quite clearly as abnormal DC voltage distributions. As shown in the foregoing examples, when a collector-junction defect is present the emitter and base voltages may be either too high or too low.

### Cutoff Test

The cutoff test is very informative when the normal operating voltages of the transistor are unknown. This is also a useful supplementary test, even when the normal operating voltages are known. The test consists simply in cutting off the base-current flow, and checking the voltage drop across the emitter resistor. For example, let us consider a cutoff test of the transistor depicted in our basic circuit Fig. 1. If the 8200-ohm base resistor is short-circuited, we will expect the voltage drop across the emitter resistor to be practically zero. The reason for this is that the base is reverse-biased by the short-circuit, which will normally cut off both the base current and the collector current.

Fig. 3 illustrates the cutoff test. Before the short-circuit is applied, the voltage drop across the emitter resistor reads 5.7 volts. With the 8200-ohm base resistor short-circuited, only the very small saturation current flows through the emitter resistor, and the voltmeter reads practically zero. This test result shows that the transistor has normal control action. On the other hand, if the voltmeter reading does

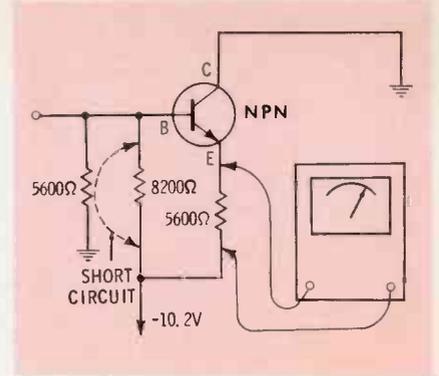


Fig. 3. The cutoff test.

not drop to zero, it indicates that the collector junction is leaky. Note that if the collector junction is leaky, the emitter will be less negative than the base in the short-circuit test—the emitter junction is therefore reverse-biased.

### Resistors in Collector Circuit

The circuit in Fig. 4A differs from that in Fig. 1A in that the collector is not grounded, but returns to ground through a 2200-ohm resistor. Fig. 4B shows the DC equivalent circuit. Note that the collector is normally -2.2 volts with respect to ground; the emitter-base bias is 0.2 volt; the collector-to-emitter voltage is 2.2 volts. Suppose that there is collector-to-base leakage in the transistor (Fig. 4B); then both the emitter and base voltages decrease, and the collector voltage increases.

The reason for this changed DC voltage distribution is seen in Fig. 5. Suppose that there is 10,000 ohms leakage from collector to base. This is the same situation as if a 10-k resistor were connected between collector and base. Obviously,

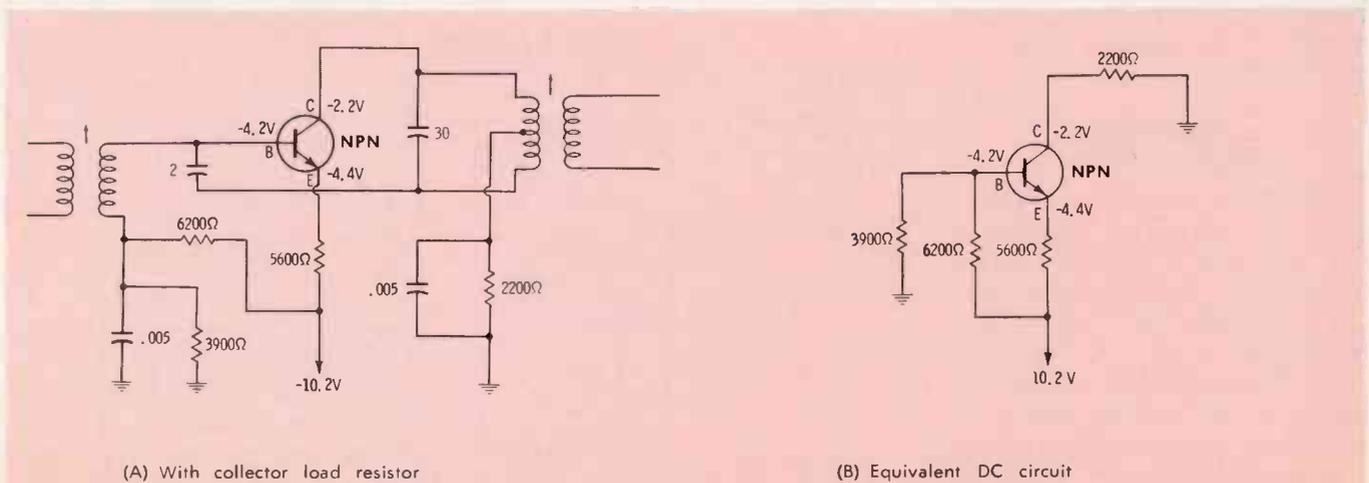


Fig. 4. Variation of the typical transistor IF circuit.

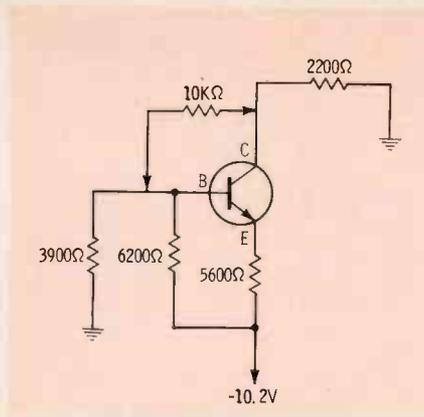


Fig. 5. Collector leakage upsets voltage on all resistors.

more current then flows through the 5600-, 6200-, and 2200-ohm resistors. Therefore, the voltage across each resistor increases. An increased voltage drop across the 2200-ohm resistor increases the collector voltage with respect to ground. Since the 10-K resistor increases the base-emitter current flow, we normally measure an increased voltage drop across the emitter resistor in this test.

Let us suppose that we wish to test for normal control action of the transistor in Fig. 4B, and for the presence of comparatively small leakage between collector and base. To do so, we connect a voltmeter across the collector resistor, and short-circuit the base to the emitter, as shown in Fig. 6. If the transistor is in good operating condition, the voltage drop across the collector resistor falls to practically zero. This action occurs because when the base and emitter are at the same voltage, the transistor is cut off; the only currents that flow through the collector resistor are the saturation current and the leakage current. Both of these currents are extremely small if the transistor is in normal condition.

### Comparative Voltage Indications

Some tests require a voltmeter with a low first range such as 0.5 volt full scale. A value of 0.01 or 0.02 volt can then be clearly read. Let us consider the control-action test depicted in Fig. 3. If the transistor is in first-class condition, we can barely see the pointer move off zero when the short-circuit is applied and the voltmeter is switched to its 0.5-volt range. On the other

hand, if there is objectionable collector-to-base leakage in the transistor, the voltmeter typically indicates 0.02 volt. This is two scale divisions on most meters. Thus, the up-scale deflection from zero is quite evident.

Next, let us consider the control-action test depicted in Fig. 6. If the transistor is in first-class condition, we must observe closely to see that the pointer moves off zero when the short-circuit is operated on its 0.5-volt range. On the other hand, if there is objectionable collector-to-base leakage in the transistor, the pointer typically moves up to 0.25 volt. Thus, a voltmeter with a first range of 2.5 volts full scale could be used in this situation.

The basic difference between the indications obtained in Fig. 3 and Fig. 6 is that there is only one path for leakage-current flow in Fig. 6; that is, all the leakage current flows through the collector resistor. On the other hand, there are two paths in parallel for the leakage-current measurement shown in Fig. 3. Part of the leakage current passes through the base resistance into the short-circuit path; the other part of the leakage current passes out of the emitter into the emitter resistor. In an approximate analysis, the transistor can be represented by an equivalent T circuit, as shown in Fig. 7. Observe that there are two paths for leakage-current flow.

In the equivalent circuit of Fig. 7, the collector junction ideally passes no current. However, with collector-junction leakage present, we may replace the junction by a high resistance; this resistance may

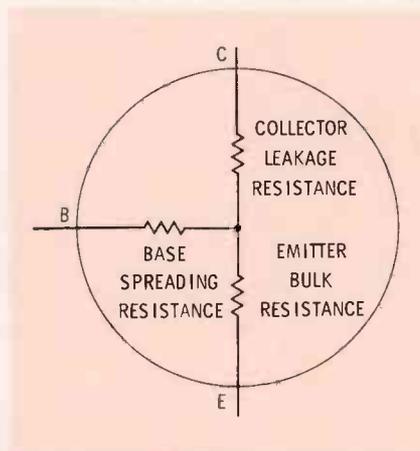


Fig. 7. Equivalent circuit for a transistor with collector-junction leakage.

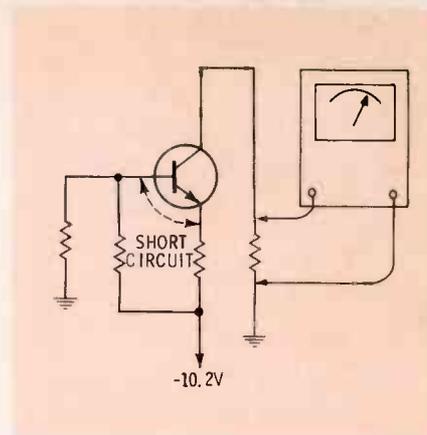


Fig. 6. The control-action test.

pass up to 1 ma of current in a very bad leakage situation. In effect, the base is connected to the lower end of this leakage resistance. The base has a certain resistance from this point to the base terminal, which is usually called the base spreading resistance. The emitter material also has resistance. Thus, neglecting some secondary semiconductor actions, the equivalent T circuit is as shown within the circle of Fig. 7.

Note carefully that the change in meter indication produced by collector-junction leakage in Fig. 3 is proportional to the change in meter indication produced by collector-junction leakage in Fig. 6. The basic distinction is that the meters are measuring a much lower voltage range in Fig. 3 than in Fig. 6. In other words, the control-action test depicted in Fig. 3 is just as sensitive as the control-action test depicted in Fig. 6, although we are working with a much smaller voltage value.

### Common-Base Circuits

Although less widely used than the common-emitter configuration, the common-base arrangement is often found in electronic circuitry. The resistive portion of a typical common-base amplifier is shown in Fig. 8. If the collector junction is leaky, both the emitter and base voltages increase. The collector voltage also increases because of the leakage current. Note that the base voltage increases when leakage is present because collector voltage is then bled into the base circuit. An increase in base voltage causes increased current flow in the emitter-base circuit. This produces more

• Please turn to page 56



# \$975

EFFECTIVE 8/1/67

## GUARANTEED

*Nine-seventy-five* buys you a complete tuner overhaul—including parts (except tubes or transistors)—and absolutely no hidden charges. All makes, color or black and white. UV combos only \$15.

*Guaranteed* means a full 12-month warranty against defective workmanship and parts failure due to normal usage. That's 9 months to a year better than others. And it's backed up by the only tuner repair service authorized and supervised by the world's largest tuner manufacturer—Sarkes Tarzian, Inc.

Four conveniently located service centers assure speedy in-and-out service. All tuners thoroughly cleaned, inside and out . . . needed repairs made . . . all channels aligned to factory specs, then rushed back to you. They look—and perform—like new.

*Prefer a replacement? Sarkes Tarzian universal replacements are only \$10.45, customized replacements \$18.25. Shipped same day order received. Order custom tuners by TV make, chassis, and model number. Order universal replacement by part number:*

Part #	Intermediate Frequency	AF Amp Tube	Osc. Mixer Tube	Heater
MFT-1	41.25 mc Sound 45.75 mc Video	6GK5	6LJ8	Parallel 6.3V
MFT-2	41.25 mc Sound 45.75 mc Video	3GK5	5LJ8	Series 450 MA
MFT-3	41.25 mc Sound 45.75 mc Video	2GK5	5CG8	Series 600 MA

*Genuine Sarkes Tarzian universal replacement tuners with Memory Fine Tuning—UHF Plug In for 82-channel sets—Pre-set fine tuning—13-position detent—Hi gain—Lo noise—Universal mounting*

FOR FASTEST SERVICE, SEND FAULTY TUNER WITH TV MAKE, CHASSIS, AND MODEL NUMBER, TO TUNER SERVICE CENTER NEAREST YOU



**TUNER SERVICE CORPORATION** FACTORY-SUPERVISED TUNER SERVICE

MIDWEST.....817 N. PENNSYLVANIA ST., Indianapolis, Indiana .....TEL: 317-632-3493  
 (Home Office)  
 EAST.....547-49 TONNELE AVE., Jersey City, New Jersey .....TEL: 201-792-3730  
 (Under New Management)  
 SOUTH-EAST.....938 GORDON ST., S. W., Atlanta, Georgia .....TEL: 404-758-2232  
 WEST.....SARKES TARZIAN, Inc. TUNER SERVICE DIVISION  
 10654 MAGNOLIA BLVD., North Hollywood, California .....TEL: 213-769-2720

Circle 4 on literature card

# FAST

## COMPLETE OVERHAUL ON ALL MAKES OF TV TUNERS

Maximum Time In Shop 24 Hrs.

(WE SHIP C.O.D.)

# \$9.50




Black &  
White  
or Color

VHF or  
UHF

UV Combo's \$15.00

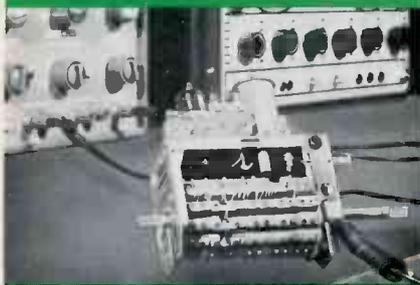Price includes all labor and parts except Tubes, Diodes & Transistors. If combo tuner needs only one unit repaired, disassemble and ship only defective unit. Otherwise there will be a charge for a combo tuner. Ship tuners to us complete with Tubes, Tube Shields, Tuner Cover and all parts (including) any broken parts. State chassis, model number and complaint.



All tuners are serviced by **FACTORY TRAINED TECHNICIANS** with years of experience in this specialized field. All tuners are **ALIGNED TO MANUFACTURERS SPECIFICATION** on crystal controlled equipment and air checked on monitor before shipping to assure that tuner is operating properly.

## GEM CITY TUNER REPAIR SERVICE

Box 6C Dabel Station  
2631 Mardon Drive  
Dayton, Ohio 45420

Circle 5 on literature card

## LETTERS to the editor

Dear Editor:

The latest PF REPORTER just arrived and I thought I would pass on my method of removing pages that I want to save, such as the Tube Substitution Supplement. I spray a little lighter fluid on the glue line and, within seconds, I can lift out the desired pages. By removing pages, I can make a very convenient data service for servicing some of the "dogs."

I have been a subscriber to PF REPORTER since it's inception and have a complete run of the publication. I locate many interesting articles in previous issues, and it is fun to examine the older issues.

H. D. WESTBROOK

Griffin, Ga.

Dear Editor:

I am writing in regard to a Capehart Model P4 AS 38 stereophonic record player I am repairing. Now that the company is no longer productive I have a tube problem. The set uses one 12AX7, one 35A3, and two 35D5's, and I have been unable to locate the last two types at any of the local distributors. I would like for you to determine substitutes for the 35A3 and 35D5 or send me information on where I may obtain original replacements. A stamped, self-addressed envelope is enclosed for your reply.

W. W. SMITH

Baltimore, Md.

*The 35A3 and 35D5 were introduced by Marconi of Italy and, so far as we can determine, are not stocked by the leading parts houses or distributors. You may be able to obtain them from a supplier specializing in imports, such as Euro Electronics, Inc., 4329 N. Western Ave., Chicago, Ill. 60618. We do have the specifications for these tubes and have determined that there are no suitable substitutes.*

# NOW

One of the world's  
largest manufacturers  
of OEM and Private  
Label Phono Needles...

## ENTERS THE DISTRIBUTOR MARKET



## Miller PHONOGRAPH NEEDLES

NOW for the first time Distributors and Dealers can sell the Famous Miller Phono Needles, Phono Drives and Record Care Accessories.

Now the famous long-wearing diamond and sapphire needles that have only been available to Manufacturers are now being offered to the Distributor and Dealer trade. In addition, we're offering a complete line of wheels, drives and belts and record care accessories. GET OUR NEW CATALOG—the latest most up-to-date in the industry. You can depend on Miller for the finest in phono needles and accessories.

**UNINTERRUPTED SERVICE — THESE  
OLD LINE SELLING ORGANIZATIONS  
FORMERLY REPRESENTED AND SOLD  
JENSEN NEEDLES.**

Represented Nationally by:

Stanely K. Wallace Lutz, Florida	EKP Associates, Inc. Easton, Pa.
Robert Tanner Co. Pittsburg, Pa.	George Petitt Co., Inc. River Forest, Ill.
T. H. Ellis Sales Co. Prairie Village, Kan.	ABM Sales Co. Detroit, Mich.
Lawrence B. Cole Co. Wellesley, Mass.	L. J. McTaggart Assoc. Buffalo, N.Y.
Mike Stobin Van Nuys, Calif.	Joseph V. Belusko Co. Portland, Ore.
Koether Cox Co. Denver, Colo.	HMR, Inc. Minneapolis, Min.

Write for complete catalog

## Miller MANUFACTURING CO.

4th & Church St. • Libertyville, Ill. 60048  
Circle 6 on literature card

2746



# THE ELECTRONIC SCANNER

*news of the servicing industry*

## Service Technician Program Announced by EIA


The Consumer Products Division of the **Electronic Industries Association** at its annual fall meeting approved a far-ranging program aimed at increasing the number of qualified service technicians for consumer electronic products. It was stated that the budget for the Service Technician Development Program will amount to \$100,000 in the 1967-68 fiscal year and over a half-million dollars over the next five years. The program follows a six-month exploratory effort, will encompass all phases of electronics service technician development, and will involve career guidance, teacher and student training, curricula upgrading, job placement and public relations.

Richard W. Tinnell, new director of education and training for the division, will be in charge of initiating the program. Mr. Tinnell outlined the career guidance effort which would be implemented by films, brochures and by working closely with career guidance teachers throughout the nation.

Production will start immediately on a 15-minute color film which is expected to be viewed by over a quarter of a million interested high school students each year. An effective brochure on the benefits of electronic servicing will be completed this year. Displays and seminars on a future in electronic servicing will be held at many vocational education conventions. The first of these seminars is scheduled to take place at the 61st annual American Vocational Association Convention in Cleveland in December.


Public image development will also be an important part of the program, and a good portion of the annual

# COMPLETE TUNER OVERHAUL

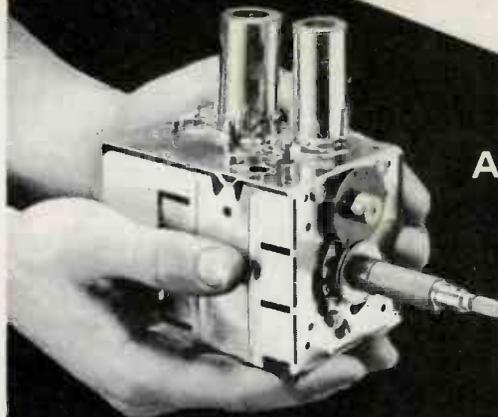

ALL MAKES —  
ONE PRICE

# 9.95

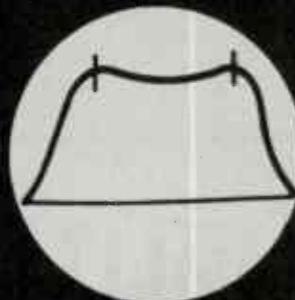


3.58

ALL LABOR  
AND PARTS  
(EXCEPT TUBES  
& TRANSISTORS)\*
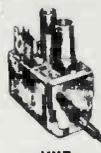
## COLOR TUNERS

GUARANTEED COLOR  
ALIGNMENT — NO  
ADDITIONAL CHARGE



VHF



UHF



COLOR



U-V



TRANSISTOR

Simply send us the defective tuner complete; include tubes, shield cover and any damaged parts with model number and complaint. Your tuner will be expertly overhauled and returned promptly, performance restored, aligned to original standards and warrantec for 90 days.

UV combination tuner must be single chassis type; dismantle tandem UHF and VHF tuners and send in the defective unit only.

Exact Replacements are available for tuners unfit for overhaul. As low as \$12.95 exchange. (Replacements are new or rebuilt.)

And remember—for over a decade Castle has been the leader in this specialized field . . . your assurance of the best in TV tuner overhauling.

Pioneers of TV




Tuner Overhauling

# CASTLE

TV TUNER SERVICE, INC.

MAIN PLANT: 5701 N. Western Ave., Chicago 45, Illinois  
EAST: 41-90 Vernon Blvd., Long Island City 1, N.Y.

Circle 7 on literature card

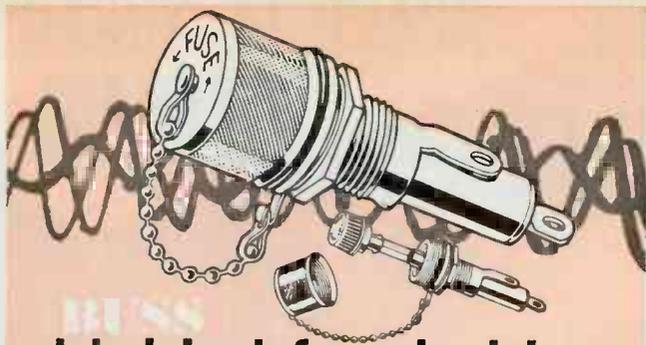

# shielded fuseholders

PREVENT RADIO  
FREQUENCY INTERFERENCE

For use where fuse and fuseholder could pick up radio frequency radiation which interferes with circuit containing fuseholder — or other nearby circuits.

Fuseholder accomplishes both shielding and grounding.

Available to take two sizes of fuses —  $\frac{1}{4}$  x  $1\frac{1}{4}$ " and  $\frac{1}{4}$  x 1" fuses.

Meets performance specifications of both MIL-I-6181D and MIL-F-19207B.



BUSSMANN MFG. DIVISION, McGraw-Edison Co., ST. LOUIS, MO. 63107

- 52,000 total techs and perform 75-80% of the service work.
5. 19,100 one-man operators perform 12%-16% of the service work.
6. Fringe operators, hobbyists, factory technicians, non-business perform 4-8.5% of the service work.
7. Approximately 25% of the dealers hire additional part time technicians sporadically.
8. Of 19,100 multiple-technician shops, approximately 80% also sell one or more brands of TV-Radio.
9. Of 19,100 one-man operators, approximately 20% also sell one brand of Radio-TV.

### \$20/Hr To Test New Meter

Amphenol Distributor Division wants to show TV service technicians how a new, solid state voltmeter can make them "keymen" in their areas for servicing transistorized equipment. And, the division is willing to pay the electronic technician for his time in testing the unit just to prove its worth.

Under a new Fall promotion employing the "keyman" theme, technicians purchasing an Amphenol Model 870 Millivolt Commander from their local distributor will receive a \$5 Keyman certificate redeemable at face value for any products carried by the distributor. Since the voltmeter can be checked out in about 15 minutes the \$5 figure represents compensation for the technician's quarter-hour of time.

## BUSS: The Complete Line of Fuses and . . . . .

program expenditure will be utilized on this important sector. Radio and television spots, news articles depicting the enormity of the problem of keeping over 500 million televisions, radios, phonographs and tape recorders and players in repair will be prepared and the good record of the industry in this area will be shown.

### National Manpower Survey

During July and August, the N.E.A. Apprenticeship and Training Committee conducted a survey of independent TV-Electronic Service Dealers to determine present manpower needs.

Response from 618 dealers, in 18 states contacted, who presently employ 1,664 technicians, showed a need for 503 new employees.

Extension of survey results brings the following conclusions:

1. Total manpower needs of present Independent Electronic Service Dealers is approximately 15,600 (figures do not include manufacturer service companies or electric set distributor service departments).
2. Total number (advertising, registered, licensed, etc.) full time dealers: 38,200.
3. Number of one-man operators included in total, approximately 50%: 19,100.
4. 19,100 shops with over one technician employ

Screw type slotted knob that is recessed in holder body and requires use of screwdriver to remove or insert it.

Screw type knob designed for easy gripping, even with gloves. Has a "break-away" test prod hole in knob.

# SPACE SAVER

## Panel Mounted Fuseholders

Fuseholder only  $1\frac{5}{8}$  inches long, extends just  $\frac{2}{32}$  inch behind front of panel. Takes  $\frac{1}{4}$  x  $1\frac{1}{4}$  inch fuses. Holder rated at 15 ampere for any voltage up to 250.

Write for BUSS Bulletin SFH-10

INSIST ON

BUSSMANN MFG. DIVISION, McGraw-Edison Co., ST. LOUIS, MO. 63107

# FUSETRON

## dual-element FUSES

*Slow Blowing*



"Slow blowing" fuses prevent needless outages by not opening on harmless overloads—yet provide safe, protection against short-circuits or dangerous overloads.

Write for BUSS Bulletin SFB

INSIST ON

# BUSS QUALITY

BUSSMANN MFG. DIVISION, McGraw Edison Co., St. Louis, Mo. 63107

The revised acquisition agreement is subject to approval by the directors of the two companies and of Ling-Temco-Vought and by the shareholders of LTV Ling Altec and Allied Radio, as well as to other legal requirements.

A new research and development center that will permit expansion of technical services to customers has been announced by **Belden**.

President Robert W. Hawkinson announced that Belden has purchased a 22,000-sq. ft. building near Geneva, Ill. "All research and development activities now being conducted at both our Chicago and Richmond, Ind., plants will be centralized in this modern new location," he said.

**Westinghouse** announced major expansions of its semiconductor production facilities on two continents. At the company's semiconductor division in Pennsylvania, a new building—the fifth expansion since 1956—has added 72,000 square feet of manufacturing capability to the existing plant.

And at Le Mans', France, site of the world-famous automobile race near Paris, a new manufacturing facility has been acquired by the division. The new organization is known as Compagnie des Dispositifs Semiconducteurs Westinghouse (CDSW). ▲

## Fuseholders of Unquestioned High Quality

### Holiday Gifts

General Electric's Tube Department has "fired up" its boilers to get the fall promotion for GE receiving tube distributors rolling. Termed the "GE Tube Holiday Gift Express", the campaign will offer valuable family gifts for tube purchases.

Premium coupons will be awarded to dealer customers for tube purchases, which will entitle the participants to select from an impressive array of valuable gifts. After accumulating the proper number of coupons, the customer will forward his order to the "Holiday Gift Express Depot" to receive his gifts. Gifts include items ranging from toys for the children to household and hobby items for mom and dad.

### Mergers and Expansions

Agreement in principle on revised terms for the acquisition of **Allied Radio** by **LTV Ling Altec** was announced by both companies.

Under terms of the revised agreement, LTV Ling Altec will buy all of the assets and business of Allied Radio in exchange for 992,830 shares of LTV Ling Altec common stock and the assumption of substantially all liabilities of Allied. Allied would then distribute to its shareholders approximately nine-tenths of a share of LTV Ling Altec common for each of the 1,103,145 shares of Allied Radio common stock outstanding.

# TRON SUB-MINIATURE

## PIGTAIL FUSES


BODY SIZE ONLY .145 x .300 INCHES

For use on miniaturized devices, or on gigantic space tight multi-circuit electronic devices.

Glass tube construction permits visual inspection of element.

Smallest fuses available with wide ampere range. Twenty-three ampere sizes from 1/100 thru 15 amps.

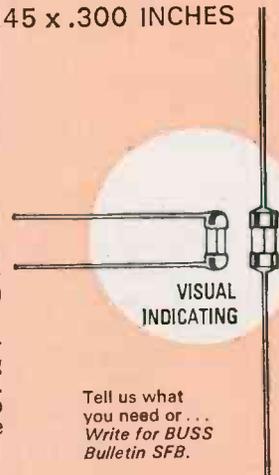Hermetically sealed for potting without danger of sealing material affecting operation. Extremely high resistance to shock or vibration. Operate without exterior venting.



Tell us what you need or...  
Write for BUSS  
Bulletin SFB.

INSIST ON

# BUSS QUALITY

BUSSMANN MFG. DIVISION, McGraw Edison Co., St. Louis, Mo. 63107

# KNOW YOUR 68 COLOR CIRCUITS

PART 2

by J. W. Phipps

## CRT Control Circuits

The CRT control circuits employed in Motorola's all-transistor chassis are shown in Fig. 13. Since the color and Y signals are combined and fed to the cathodes, there is no signal applied to the G1, or control, grids. Instead, they are tied together and furnished a common voltage. The G2 (screen) controls determine the cutoff of each gun

and are supplied approximately 600 volts DC from the focus voltage supply. Voltage for the green G2 control is supplied through a fixed 2.2-megohm resistor, while the voltage for the red and blue G2 controls is supplied through a potentiometer which serves as the tint control. Adjusting the tint control splits the supply voltage between the two controls so that the CRT screen

can be tinted according to individual preference. Note that the 5-kv focus voltage is obtained by dividing the second anode voltage through a bleeder network. This configuration provides a fixed ratio between the high voltage and focus voltage at any brightness setting.

An automatic brightness limiter circuit (ABL) is employed in conjunction with the CRT input circuitry and video drivers. The primary function of this circuit (Fig. 14) is to limit the maximum CRT beam current to a value that can be safely delivered by the horizontal output and high-voltage circuits. This is accomplished by monitoring the focus voltage which decreases with an increase in CRT beam current and using the resultant reference voltage to control the two common-emitter DC amplifiers. As the CRT beam current increases, the focus voltage drops, decreasing the reference voltage applied as forward bias to the ABL driver. The resultant decrease in the conduction of the ABL driver reduces its emitter voltage which, in turn, lowers the forward bias on the brightness control amplifier and reduces its conduction. With the output from the emitter of the brightness control applied as forward bias to the three video driver stages, the conduction of these sta-

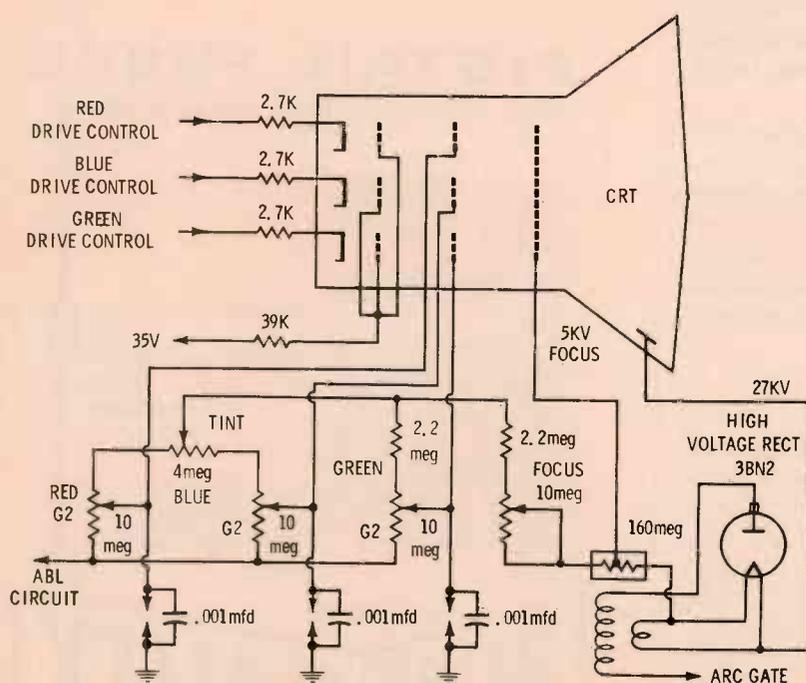


Fig. 13. CRT circuits employed in Motorola's all-transistor chassis.

# THE COLOR TV SERVICING BOOM IS ON!

BE IN ON THE PROFIT PICTURE *with the know-how you get in*  
**COMPLETE PHOTOFACT® COLOR TV COVERAGE**

283 Here are the PHOTOFACT sets with Color TV coverage from the beginning in 1954 through 1967:

1	31	61	91	121	151	181	211	241	271	301	331	361	391	421	451	481	511	541	571	601	631	661	691	721	751	781	811	841	871	901
2	32	62	92	122	152	182	212	242	272	302	332	362	392	422	452	482	512	542	572	602	632	662	692	722	752	782	812	842	872	902
3	33	63	93	123	153	183	213	243	273	303	333	363	393	423	453	483	513	543	573	603	633	663	693	723	753	783	813	843	873	903
4	34	64	94	124	154	184	214	244	274	304	334	364	394	424	454	484	514	544	574	604	634	664	694	724	754	784	814	844	874	904
5	35	65	95	125	155	185	215	245	275	305	335	365	395	425	455	485	515	545	575	605	635	665	695	725	755	785	815	845	875	905
6	36	66	96	126	156	186	216	246	276	306	336	366	396	426	456	486	516	546	576	606	636	666	696	726	756	786	816	846	876	906 Sept.
7	37	67	97	127	157	187	217	247	277	307	337	367	397	427	457	487	517	547	577	607	637	667	697	727	757	787	817	847	877	907 Sept.
8	38	68	98	128	158	188	218	248	278	308	338	368	398	428	458	488	518	548	578	608	638	668	698	728	758	788	818	848	878	908 Sept.
9	39	69	99	129	159	189	219	249	279	309	339	369	399	429	459	489	519	549	579	609	639	669	699	729	759	789	819	849	879	909 Sept.
10	40	70	100	130	160	190	220	250	280	310	340	370	400	430	460	490	520	550	580	610	640	670	700	730	760	790	820	850	880	910 Sept.
11	41	71	101	131	161	191	221	251	281	311	341	371	401	431	461	491	521	551	581	611	641	671	701	731	761	791	821	851	881	911 Sept.
12	42	72	102	132	162	192	222	252	282	312	342	372	402	432	462	492	522	552	582	612	642	672	702	732	762	792	822	852	882	912 Oct.
13	43	73	103	133	163	193	223	253	283	313	343	373	403	433	463	493	523	553	583	613	643	673	703	733	763	793	823	853	883	913 Oct.
14	44	74	104	134	164	194	224	254	284	314	344	374	404	434	464	494	524	554	584	614	644	674	704	734	764	794	824	854	884	914 Oct.
15	45	75	105	135	165	195	225	255	285	315	345	375	405	435	465	495	525	555	585	615	645	675	705	735	765	795	825	855	885	915 Oct.
16	46	76	106	136	166	196	226	256	286	316	346	376	406	436	466	496	526	556	586	616	646	676	706	736	766	796	826	856	886	916 Oct.
17	47	77	107	137	167	197	227	257	287	317	347	377	407	437	467	497	527	557	587	617	647	677	707	737	767	797	827	857	887	917 Oct.
18	48	78	108	138	168	198	228	258	288	318	348	378	408	438	468	498	528	558	588	618	648	678	708	738	768	798	828	858	888	918 Nov.
19	49	79	109	139	169	199	229	259	289	319	349	379	409	439	469	499	529	559	589	619	649	679	709	739	769	799	829	859	889	919 Nov.
20	50	80	110	140	170	200	230	260	290	320	350	380	410	440	470	500	530	560	590	620	650	680	710	740	770	800	830	860	890	920 Nov.
21	51	81	111	141	171	201	231	261	291	321	351	381	411	441	471	501	531	561	591	621	651	681	711	741	771	801	831	861	891	921 Nov.
22	52	82	112	142	172	202	232	262	292	322	352	382	412	442	472	502	532	562	592	622	652	682	712	742	772	802	832	862	892	922 Nov.
23	53	83	113	143	173	203	233	263	293	323	353	383	413	443	473	503	533	563	593	623	653	683	713	743	773	803	833	863	893	923 Nov.
24	54	84	114	144	174	204	234	264	294	324	354	384	414	444	474	504	534	564	594	624	654	684	714	744	774	804	834	864	894	924 Dec.
25	55	85	115	145	175	205	235	265	295	325	355	385	415	445	475	505	535	565	595	625	655	685	715	745	775	805	835	865	895	925 Dec.
26	56	86	116	146	176	206	236	266	296	326	356	386	416	446	476	506	536	566	596	626	656	686	716	746	776	806	836	866	896	926 Dec.
27	57	87	117	147	177	207	237	267	297	327	357	387	417	447	477	507	537	567	597	627	657	687	717	747	777	807	837	867	897	927 Dec.
28	58	88	118	148	178	208	238	268	298	328	358	388	418	448	478	508	538	568	598	628	658	688	718	748	778	808	838	868	898	928 Dec.
29	59	89	119	149	179	209	239	269	299	329	359	389	419	449	479	509	539	569	599	629	659	689	719	749	779	809	839	869	899	929 Dec.
30	60	90	120	150	180	210	240	270	300	330	360	390	420	450	480	510	540	570	600	630	660	690	720	750	780	810	840	870	900	930 Jan.

## Order Your PHOTOFACT COLOR TV LIBRARY Now!

### 3 SPECIAL OFFERS:

- ① 1954 up to 1964—full coverage in 60 PHOTOFACT Sets
- ② 1954 through 1966—full coverage in 180 PHOTOFACT Sets
- ③ 1954 through 1967—full coverage in 240 PHOTOFACT Sets

**FREE** 1-drawer file cabinet with 60 Set Offer; 4-drawer file cabinet with 180 Set Offer; 4-drawer cabinet plus 1-drawer cabinet with 240 Set Offer

### USE THE SPECIAL EASY-PAY PLAN


- No interest or carrying charges
- Only \$20 down
- From 12-30 months to pay
- Prepaid transportation
- Save 25¢ per Set—special \$2.25 Set price applies on Easy-Buy (instead of the regular \$2.50 price)

**ASK ABOUT THE PHOTOFACT "TRADE-IN" DEAL**  
*(offer available through June 30, 1968)*

SEE YOUR SAMS DISTRIBUTOR FOR FULL DETAILS OR MAIL COUPON BELOW TODAY

**GET GOING IN  
 COLOR TV!**
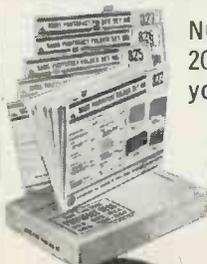
### JOIN THE PHOTOFACT-OF-THE-MONTH CLUB:



**JOIN  
 P.O.M.**

NOW! Only \$10 per month brings you 20% MORE Photofact coverage to keep you current—saves you over \$60 per year!

- Get 6 new Photofact Sets each month
- Covers at least 50 new chassis
- At least 6 Color TV Folders monthly

NEW BONUS: MINIMUM OF 10 "ADVANCE" TV SCHEMATICS (MOSTLY COLOR) WITH EACH MONTH'S ISSUE—PLUS GREAT FILE CABINET DEAL WITH TRIAL 6-MONTH SUBSCRIPTION TO P.O.M. (PHOTOFACT-OF-THE-MONTH CLUB).

HOWARD W. SAMS & CO., Dept. PFF-12  
 4300 W. 62nd St., Indianapolis, Indiana 46206

- Send full details on Library Offer and Easy-Buy Plan
- Send Photofact-of-the-Month Club details
- Send FREE 1968 PHOTOFACT Cumulative Index

My Distributor is \_\_\_\_\_


Shop Name \_\_\_\_\_

Attn.: \_\_\_\_\_

Address \_\_\_\_\_


City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_
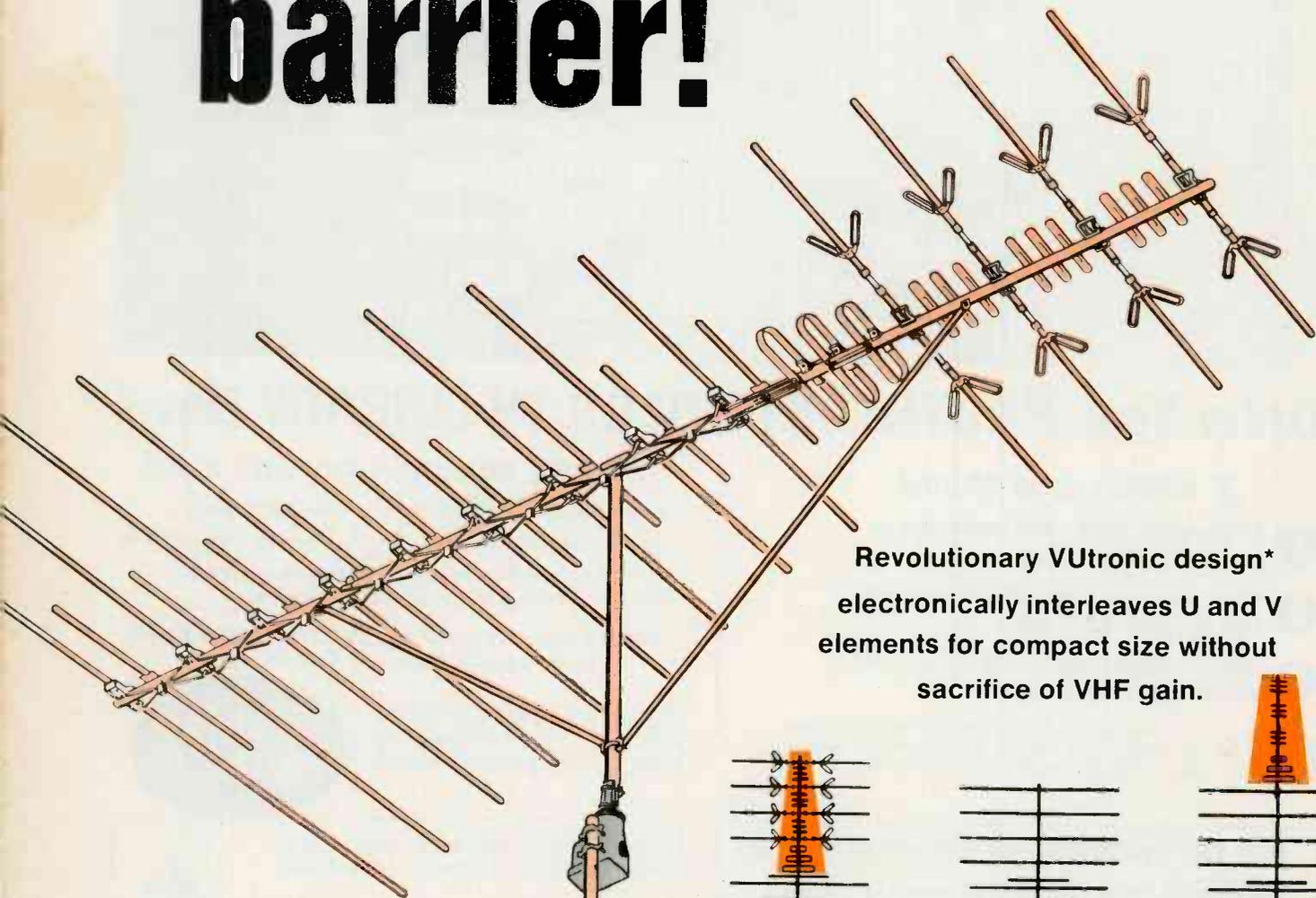
# Channel Master smashes the 82 Channel size barrier!




Revolutionary VUtronic design\*  
electronically interleaves U and V  
elements for compact size without  
sacrifice of VHF gain.

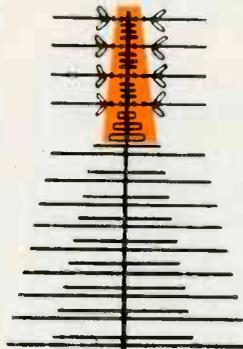
Deep Fringe  
Model 3661-G  
Same VHF gain as  
Color Crossfire  
Model 3610-G



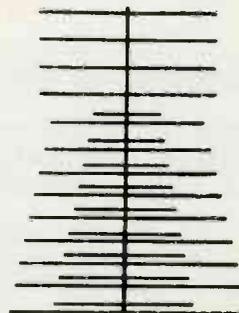Fringe area Model 3661G has all UHF elements contained within the over-all length of the VHF section



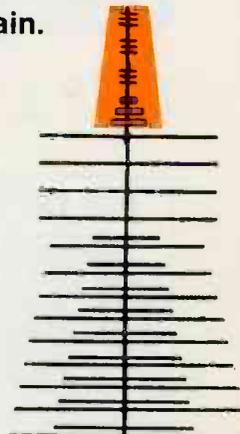A VHF only antenna with exactly the same VHF gain as the 82-channel Model 3661G is also practically the same size.



Usual design 82-channel antenna would have to be 34% longer to provide the same UHF and VHF gain as Model 3661G Color Crossfire 82.

\*Patent Applied For

# New Color Crossfire 82

## UHF/VHF Antennas plus FM/FM Stereo

Totally new concepts in UHF/VHF design are joined with Channel Master's proven Crossfire principle to produce the first 82-channel antennas that meet UHF reception needs yet also provide unsurpassed VHF gain...and with no appreciable increase in over-all size.

Here is another example of a major development from Channel Master Laboratories where, as always, leadership begins with research.

Until now, antenna manufacturers have created combination UHF/VHF antennas by coupling a UHF section to the front of a VHF antenna. To avoid costly, unwieldy, and unsightly construction, this has always meant sacrificing VHF gain. Now Channel Master fills the 82-channel gain gap with Color Crossfire 82 antennas designed for metropolitan to fringe areas where maximum VHF gain is as important as UHF reception power.


In addition to the famous Channel Master Crossfire VHF Proportional Energy Absorption Principle, these new antennas employ unique series-fed folded UHF dipoles with carefully engineered dimensions so that they literally "disappear" and operate as a perfect 300 ohm line at VHF frequencies...no "lossy" couplers required as is the case with the usual parallel-fed UHF elements.

And, of course, every Color Crossfire 82 antenna features Channel Master's famous E.P.C. golden coating and rugged preassembled construction.

### COLOROTORS... for the complete U/V installation


Color Crossfire-82 antennas and Channel Master Colorotors go hand-in-hand for best color on all U and V channels, crisp, clear FM, and FM Stereo reception.
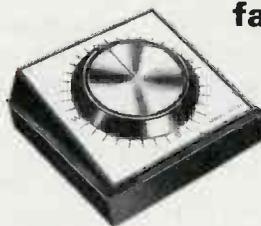
#### The Nation's largest, fastest-selling rotator line



Automatic Model 95 12.  
Also Deluxe Cabinet  
Automatic,  
Semi-Automatic,  
and Manual Models.

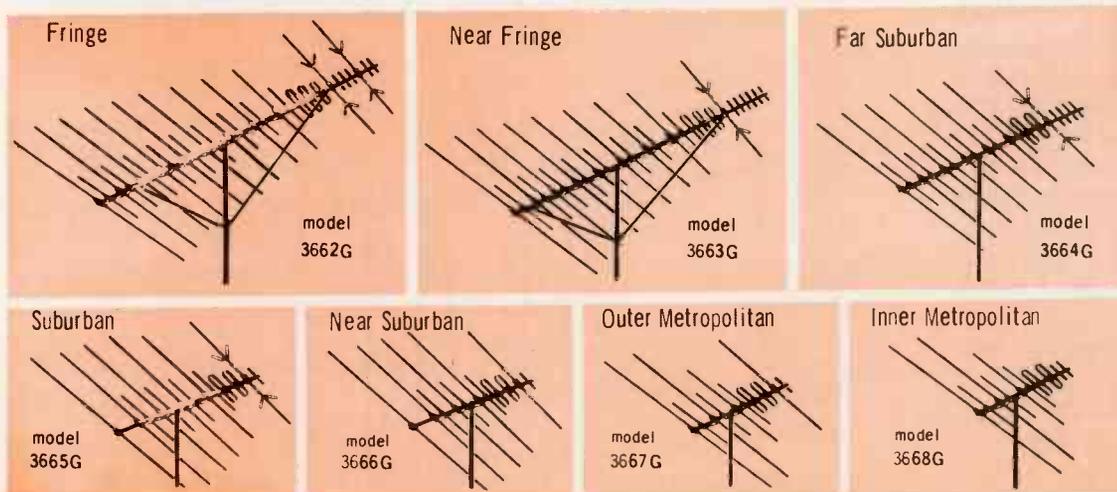Now the first and only complete line of full VHF Power 82-channel antennas.



More Channel Master Crossfire Series Antennas have been sold and are being sold...than any other antenna in the history of television.

**CHANNEL  
MASTER**  
Ellenville, N.Y.

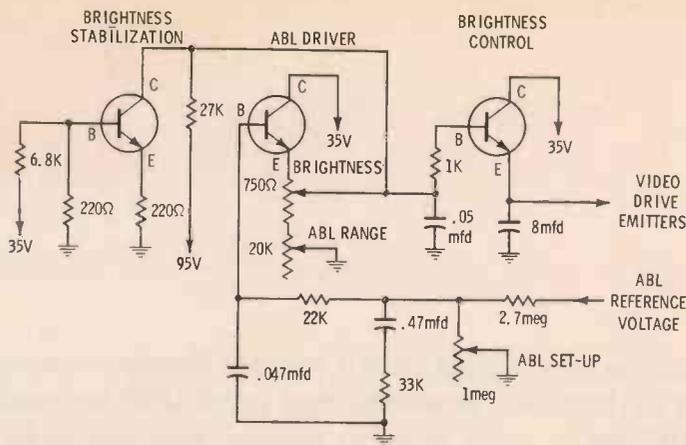


Fig. 14. Motorola's automatic brightness limiter circuit.

ges is reduced because of the decrease in the emitter voltage of the brightness control stage. Since the video drivers are DC coupled to the CRT cathodes via the video output stages, the decreased conduction of the video drivers reduces the drive to the CRT cathodes, thus decreasing the beam current. The brightness stabilization stage prevents variations in brightness resulting from changes in B+.

An additional advantage derived from the ABL circuit function is independent control of the contrast and brightness. This advantage is realized because the ABL circuit automatically adjusts the beam current in the direction needed to compensate for changes in brightness caused by adjustment of the contrast control.

CRT blanking in Motorola's TS-915 and TS-919 chassis is accomplished by the monostable multivibrator circuit shown in Fig. 15. The emitter of each video output transistor returns to ground through X2, which is normally saturated (maximum conduction). The application of either a vertical or horizontal positive pulse to X1 (normally cut-off) triggers it into conduction. Conduction of X1 decreases the positive potential at the base of X2, cutting it off and opening the emitter-to-ground path of all three video output stages. With no emitter return to ground, the video output stages are cut off and their collector voltages rise to the source voltage (255 volts). Since the video output stages are DC coupled to the CRT cathodes, the high positive source vol-

tage is also applied to the cathodes, biasing them off. No DC restoration circuitry is required in the Motorola all-transistor chassis because 100% DC coupling exists between the video detector and CRT cathodes.

The use of the new red phosphor in RCA's color CRT's has made it necessary to add a red drive control. In previous CRT designs, red was the least efficient of the three phosphors, and the green and blue drive signals were reduced to compensate for this. However, with the increased efficiency of the new red phosphor, it may be necessary to reduce both the red and green drive controls with respect to the blue. The red drive control is utilized in all five of RCA's new color chassis.

#### Luminance Circuits

Emerson Chassis Group C-77, used in various 18", 20" and 23"

models, employs a combination sync/AGC/chroma amplifier in the luminance channel. As shown in Fig. 16, the 1st video amplifier functions as a cathode follower with a separate output to both the combination amplifiers and the final video output stage. The sync, AGC, and chroma stages receive their respective input signals from the plate circuit of V1B. The chroma signal is fed to the burst amplifier and the chroma take-off coil in the grid circuit of the 1st bandpass amplifier. Voltage for the brightness control circuit is obtained from a separate half-wave rectifier.

Chassis group C-75A, used in the Dumont Custom Series and five 23" Emerson models, employs a new potentiometer-type video peaking coil in place of the slide switch found in earlier chassis. Chassis group C-75 continues to use the slide-type video peaking switch. Both types of controls are electrically located in the cathode circuit of the 3rd video amplifier.

The hybrid amplifier section introduced in General Electric's KC chassis is also found in the new KD chassis. NPN transistors are employed in the 1st and 2nd video amplifier stages, while the pentode half of a triode-pentode 6AG9 is used in the final video stage.

Philco's color line continues to use hybrid chassis with transistorized video IF, video driver, and AGC circuits. The only major change in this design involves the new 18QT86 chassis employed in two 23" models. The video driver

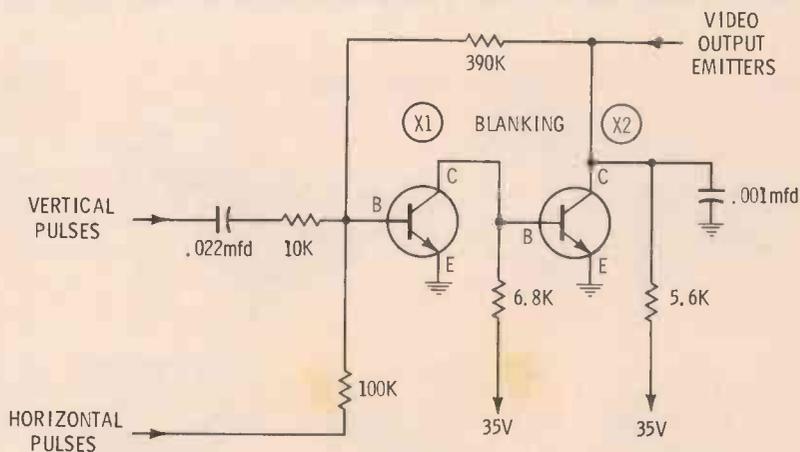


Fig. 15. Motorola's blanking system opens emitters of video output stages.

circuit in this chassis uses an integrated circuit in place of the NPN transistor found in the same stage in other Philco color chassis.

A new method of horizontal retrace blanking is utilized in RCA's CTC31 chassis. In previous chassis designs from this manufacturer, horizontal blanking was accomplished at the CRT control grids via the color difference amplifiers. However, a new chroma clamp diode is employed in the CRT grid circuit and precludes use of the grids for retrace blanking. Instead, both horizontal and vertical retrace blanking are now accomplished through the CRT cathodes via the video output stage. As shown in Fig. 17, both horizontal and vertical negative blanking pulses are applied to the grid of the output stage. During the normal scan time (no blanking pulse present), a positive voltage is applied to the anode of diode X1 through a 680K-ohm resistor. This causes X1 to conduct, passing the luminance information on to the grid of the output tube and through the tube to the CRT cathode. However, during horizontal retrace, the negative portions of the blanking waveforms bias off the blanking diode, video output stage and, consequently, the CRT cathodes. This action is accomplished regardless of

the contrast or brightness control settings.

Also found in the same chassis is a brightness limiter control (Fig. 17). The limiter control supplies one end of the normal brightness control with a variable amount of positive voltage. The other end of the normal brightness control is supplied with a negative voltage from the grid of the horizontal oscillator via the filter network comprised of two resistors and a .047-mfd capacitor. The normal brightness control adjusts the bias on the video output grid, thus establishing the brightness level. Adjusting the limiter control varies the positive potential supplied to the brightness control and, therefore, determines the range of positive voltage supplied to the video output grid. When the limiter control is properly adjusted, the normal brightness control can be advanced fully clockwise (maximum brightness) without excessive blooming.

All new RCA color chassis, with the exception of the CTC22, employ a push-pull type normal/service/raster switch mounted on top of the chroma circuit board. In addition, the normal/service/raster switch circuitry in the CTC31 chassis is designed to provide approximately 20 volts of AC-coupled

blanking to the CRT cathodes when the switch is in the service position. The 20-volt blanking signal is obtained from the plate of the video output stage and coupled to one side of the service switch through a 39K-ohm resistor and .01-mfd capacitor (R1 and C1). The service switch, in turn, applies the blanking signal to the CRT cathodes via the drive controls, as shown in Fig. 17. The necessity of this added blanking signal is a result of the previously described CTC31 blanking system, which cuts off the cathodes via the video output stage. If the service position of the normal/service/raster switch completely removed the video output from the CRT cathodes, as is done in other RCA chassis, no horizontal blanking signal would be applied to the cathodes during color temperature setup and the resultant visible retrace lines would interfere with the temperature adjustments.

Sylvania's new D10 series chassis, employed in various 23" models, features a hybrid design with the complete three-stage video IF and three-stage keyed AGC circuitry transistorized. In addition, the sync amplifier, noise gate, and first two video amplifiers are also transistorized. This manufacturer's DO6 and DO7 chassis (used in 20" and 18" models, respectively) employ tran-

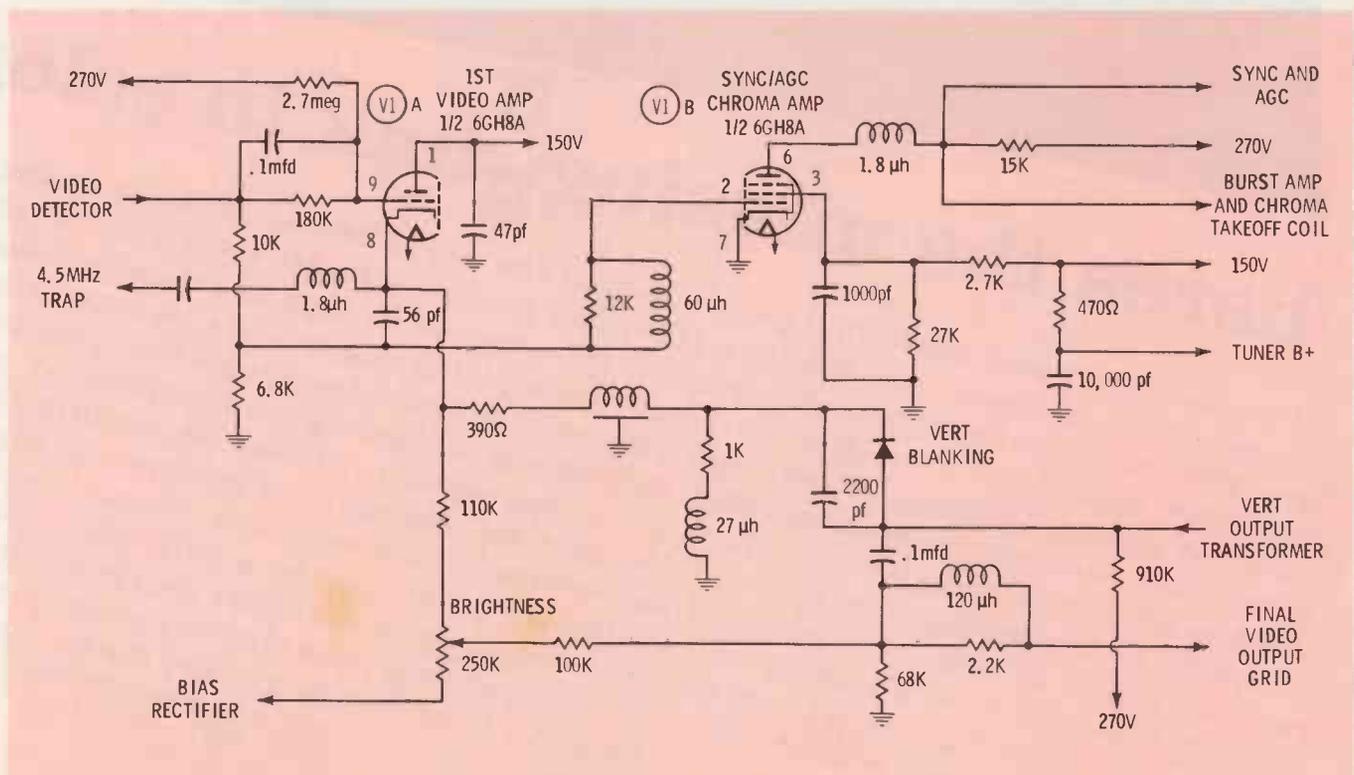


Fig. 16. Combination sync/AGC/chroma amplifier stage is employed in Emerson chassis.



# here's the missing link in color

Belden's Color Twins deliver full color power all the way to the set. Eliminate many causes of lead-in signal loss. Deliver a ghost-free picture. ■ Belden's COLOR TWINS are: 8290<sup>†</sup> Shielded Permohm with Beldfoil\* for congested or high interference areas; and 8285<sup>†</sup> Unshielded Permohm for rural, low-signal-strength areas. ■ 8290 with patented Beldfoil shielding prevents line pick up of interference signals that produce ghosts and electrical interference. 8285 Permohm's conductors are encapsulated in low-loss cellular polyethylene to maintain a strong signal in all weather conditions, especially in fringe reception areas. ■ 8290 Shielded Permohm is designed so that you can install it without expensive transformers, connectors, and "stand offs." You can even tape it to a mast or run it through a rain gutter. ■ With Permohm lead-ins, the set gets the full color power of the signal (full power for UHF or VHF, too.) Now owners can get the kind of picture they bought a color set for. You get the laurels.

**BELDEN CORPORATION**  
P.O. Box 5070-A • Chicago, Illinois 60680

reception!

8285<sup>†</sup>

Belden  
Unshielded Permohm  
for rural areas.

Call your Belden distributor about the  
Color Twins—



**BELDEN**

PERMOHM

8285



8290<sup>††</sup>

Belden  
Shielded Permohm  
with Beldfoil  
for congested areas.


ALL CHANNEL TV

don't forget  
to ask them  
what else needs  
fixing?

\*Belden Trademark Reg. U.S. Patent Office †Belden Patent No. 2,782,251 ††Belden Patent No. 2,782,251 and Pat. Pending

Circle 10 on literature card



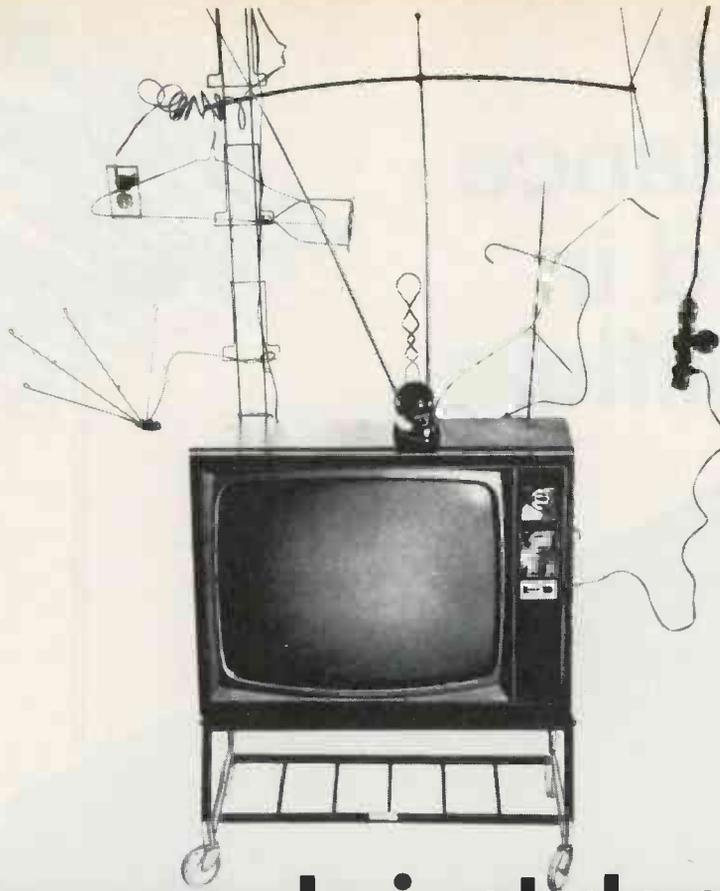

# Some people just don't like to admit they need a service man.

They know they're going to have to pay bills for something they don't really understand. They feel a little uneasy, a little helpless.



That's why millions of Philco owners automatically choose their local Philco Qualified Service Center when they need something fixed. They feel safer with the specialist.

There's a lot of new business waiting for you when you hang out the Philco sign.

Your service technicians can get all the training they need right there in your area. And when they're through, our Tech Data Service keeps them in the picture with all the new developments and service short cuts.

When your shop appears in our Yellow Pages listings you become the headquarters for Philco Service in your area. You can get new business you'd probably never have uncovered. And you get the fastest parts delivery in the industry.

That's briefly how it works — how it'll mean more business for you. Your local Philco-Ford Distributor will give you all the details. Call his Service Manager.

Philco-Ford Corporation  
Philadelphia, Pa. 19134



# The new performance standard in preamplifiers




**New Jerrold Lightning-Protected Powermate® Preamplifiers** now bring you a degree of reliability never before achieved in mast-mounted solid-state preamplifiers. Our extensive field tests in lightning storms prove it. Powermate models are available for every signal situation—VHF, UHF, and FM. And you can expect them to deliver snow-free, ghost-free, line-free TV in color or black and white for plenty of reasons:


- High gain
- Extremely low noise figures
- Unusually flat response

- Elimination of cross modulation and herringbone distortion
- Excellent overload capability

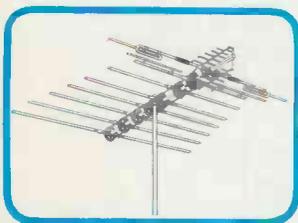Get more details on the preamplifier designed to be an antenna's best friend. The reliable, new Jerrold Lightning-Protected Powermate Preamplifier. The newest product in Jerrold's Spectrum '67. Ask your Jerrold Distributor. Or write for further information to: Jerrold Electronics Corporation, Distributor Sales Division, 401 Walnut St., Philadelphia, Pa. 19105.



Outdoor antennas

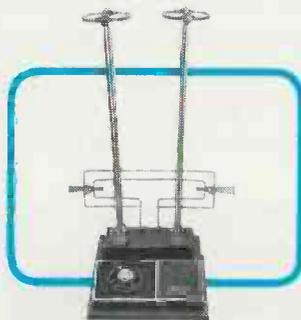

Indoor antennas



Distribution equipment



*Focusing on one thing...  
better reception*

Electrics' large-screen chassis has been changed; the previously used 3A3 high-voltage rectifier has been replaced by a 3CN3, and the shunt-type high-voltage regulator (formerly a 6EF4) now utilizes a 6LJ6.

Changes are also evident in the sweep circuitry of this chassis. Both horizontal and vertical centering are included in their respective circuits. Horizontal centering is provided by a potentiometer placed across the sweep supply windings of the horizontal output transformer (Fig. 19A.) The moveable arm of the pot is connected to the hot side of the horizontal yoke windings, thus controlling the potential supplied to them. The vertical centering provision consists of a jumper that can be placed at either end of a 3.3K-ohm resistor in the 400-volt line of the low-voltage supply (Fig. 19B).

The horizontal sweep system employed in RCA's new color chassis is changed somewhat from this manufacturer's previous designs. One change was made to increase the

amplitude of the horizontal grid drive wave-form and assure that the horizontal output tube remains cut-off during retrace time, thus preventing unnecessary plate power dissipation. Instead of furnishing the horizontal oscillator plate with only B+, both boost and B+ voltages are supplied to the plate of this stage in the new color chassis, providing an additional 20- to 30-volt increase in plate voltage. This increase in voltage produces a similar increase in the drive waveform at the grid of the output stage which, in turn, results in an increase in the negative portion of the waveform.

Another sweep system change incorporated in all '68 RCA chassis involves a new horizontal efficiency coil with a core designed to reduce the possibility of saturation. Also, a new 6CL3 damper is used in chassis CTC35, CTC30, and CTC28. The increased efficiency of the 6CL3, as compared to the older 6DW4, has made it possible to reduce the screen dissipation of the 6JE6 hori-

zontal output tube by increasing the screen resistor from 13 to 15K ohms.

### Sound Circuits

The all solid-state sound system shown in Fig. 20 is employed in three of Catalina's 23" consoles and one 23" combination model. An integrated circuit is used in the sound IF and sound detector stages of this system. Motorola and Sylvania also use integrated circuits in their sound systems. Motorola's IC sound system is found in their TS-915 and TS-919 all-transistor chassis, while Sylvania has selected their D10 chassis series for the IC application. Another example of the increasing use of solid-state components in TV sound systems is found in Delmonico/Nivico's 18" portable chassis. Fig. 21 shows the transistorized sound section employed in this chassis.

• Please turn to page 44


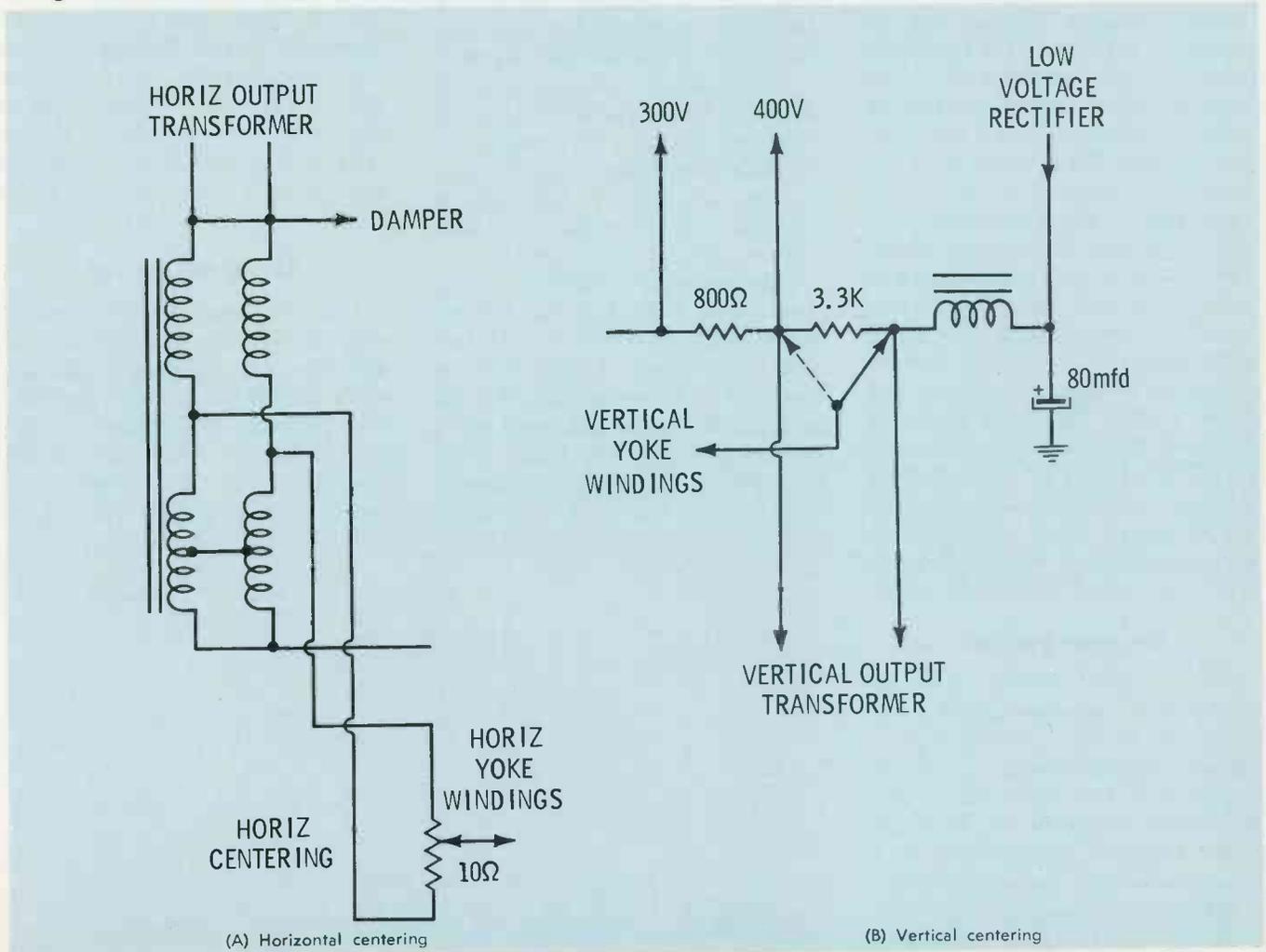


Fig. 19. Sweep centering provisions found in General Electric chassis.

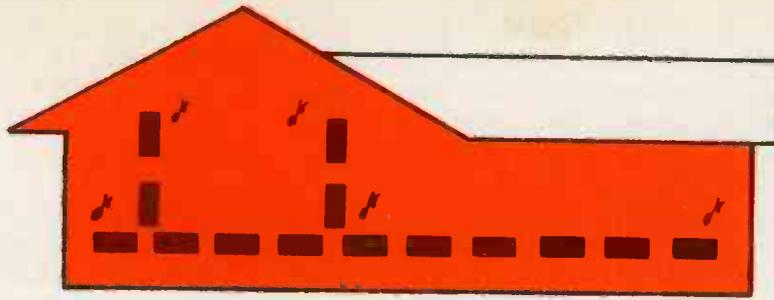

□ A little "boning-up" on system designs and applications, together with the electronic knowledge you already possess, will put you in a position to make money.

## installing intercom and music distribution systems

by Louis M. Dezettel

There is no reason why the radio and TV servicemen cannot get a share of this increasingly prosperous business. Anyone capable of servicing radio and TV sets is capable of installing intercoms and music distribution systems in homes, businesses, and schools. The electrical knowledge required is fundamental, and no special tools or test equipment are needed.

The one requisite which you may not have is an understanding of the various intercom systems that are currently available. This knowledge is absolutely necessary if you are to properly advise your customer on what he needs to fill his particular requirements. Such information can usually be obtained at your local radio and TV parts distributor. The distributor may have a representative system of the line he handles hooked up and operating. If so, look it over carefully, paying particular attention to the cable connection strip, or separate junction box if one is used. Then, pick up all the pertinent literature you can, and spend an evening or two studying it to get a thorough idea of what the system(s) offers. Following is a general description of both intercom and music distribution systems.

### Intercom Systems

An intercom system provides loudspeaker communication between two or more points without the use of microphones. A single amplifier is normally used. The loudspeaker is switched to the input of the amplifier and functions as a microphone when one station talks. A push-to-talk switch does the switching of speakers. While this eliminates duplex communication,

such as that provided by a telephone, and does require switching each time one desires to talk, it is more economical from the standpoint of the equipment required.

The station in which the amplifier is located is called the "master," and the other station, consisting of only a speaker and switch, is called the "substation," or sometimes the "slave." Masters can be connected to a number of substations as in Fig. 1, or all stations may be masters (Fig. 2), or a system may combine several masters and slaves.

In nonprivate configurations, the master station's push-to-talk switch functions for both the master and the substation. Thus, only the master can originate a call and, in addition, can listen in on a substation, such as the nursery.

The nonprivate hook-up is also used for the front door station when one is installed. When the door bell rings, the master station can be switched to that substation, and the lady of the house can carry on a conversation with the visitor without opening the door. (Obviously, such a safety feature is an effective

selling point.) There are other combinations of intercom systems, but the preceding ones are the most commonly found.

### Music Distribution Systems

A home music distribution system is basically an intercom system with a radio tuner (Fig. 3) and/or record player (Fig. 4) added, in addition to a few other equipment refinements. The added refinements include better quality speakers for improved music fidelity and a switching function at each substation to permit selection of a particular music channel. Deluxe systems even include a dual-speaker installation in each room for stereo reception of music (not voice).

### Sizing Up the Job

Once you have become familiar with the available music distribution and intercom equipment, you are ready to call on your first prospective customer. Determine his requirements and match these to the equipment you are prepared to install. After you have reached an

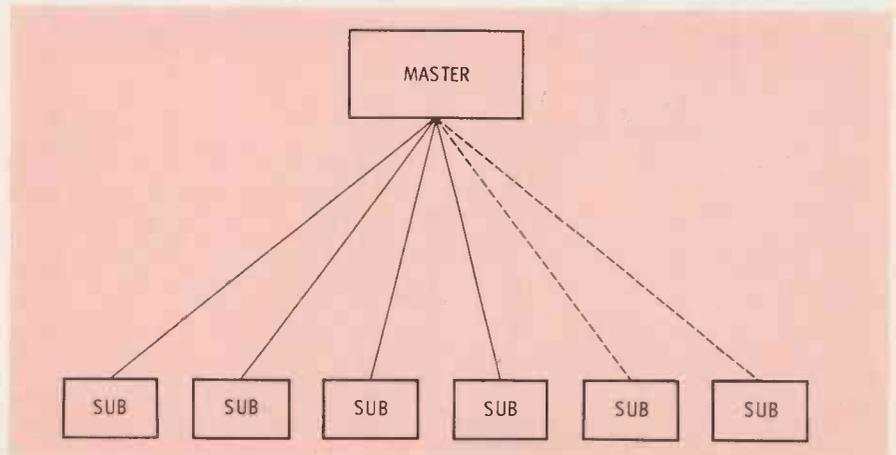


Fig. 1. System employing one master and any number of substations.

Industry Demanded - only Sencore delivered

# AN ALL NEW IMPROVED COLOR CRT TEST



**Simple - Fast - Accurate • Automatic Color Tracking!  
No Time-Wasting Logging and Computing!**


CRT manufacturers, set manufacturers, distributors, technicians — all demanded a better CRT tester than any available. This is it — the new Sencore CHAMPION — a winner on every count.

Separate G2 screen grid controls, just like the color circuit itself, enable you to set up each color gun, then automatically compare it with the others for tracking — exactly according to industry standards. This check is important when claiming credit for a defective color CRT. No time consuming logging of each color gun reading at every setting of the G2 control like competitive models. It's automatic with the CR143 Champion.


The CHAMPION also makes all the standard color and black and white CRT tests — shorts, emission, and life tests. Its Line Adjust control assures exceptional accuracy. Its exclusive three step Automatic Rejuvenation Circuit lets you save many a faulty black and white tube or equalize gun currents in color tubes.

The all-new CHAMPION is equipped with plug-in sockets for fast testing and easy updating. Rugged vinyl-clad steel case has spacious lead compartment.


For a sure thing, put your money on the champion — the Sencore CR143 CHAMPION.

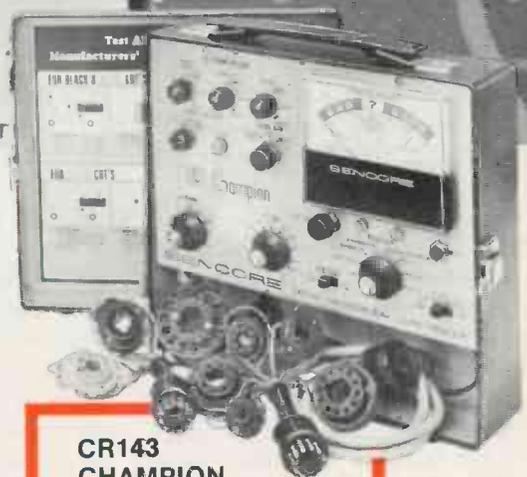

**CR143  
CHAMPION**

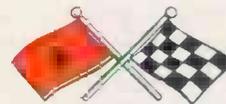

**\$99.50**

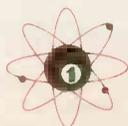

## SENCORE

NO. 1 MANUFACTURER OF ELECTRONIC MAINTENANCE EQUIPMENT  
426 SOUTH WESTGATE DRIVE, ADDISON, ILLINOIS 60101

Circle 13 on literature card

December, 1967 / PF REPORTER 25

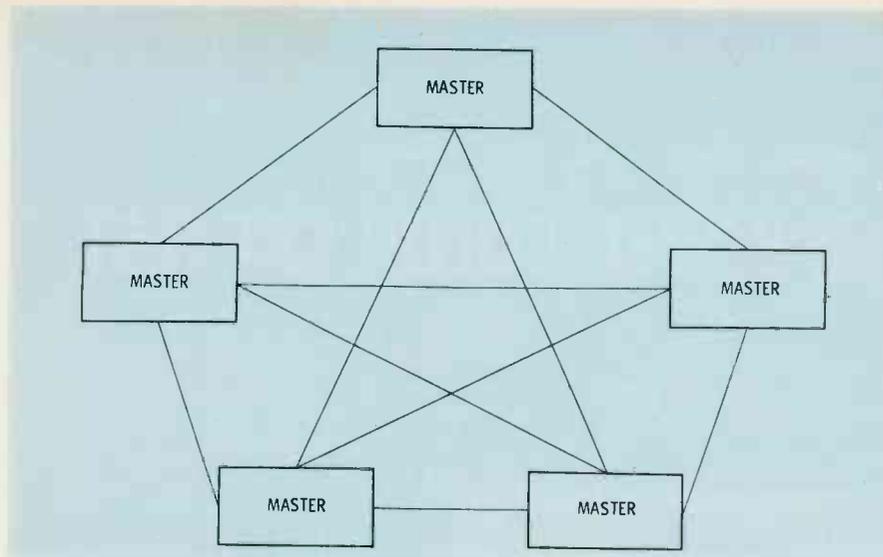


Fig. 2. Intercom system using master units at each station.

agreement on the type of system and number and location of stations, prepare a layout, such as the one in Fig. 5, to present to your customer for final approval before you make any definite statements concerning price.

There are a few pointers to keep in mind when you are selecting the location of the stations. The master station will need a source of AC, so locate it at or near an AC outlet (exception: some systems use a battery-operated transistor amplifier). Interconnecting cable should not be run near AC lines, even if the AC lines are in conduit. Reduce the risk of hum pickup by keeping the intercom cables and AC lines as far apart as practical.

There are a number of other factors to be considered in the layout of the system. Obviously, you must know something about the construction of the building or house in which the system is to be installed. A brick house has two courses of brick and only  $\frac{3}{4}$ " furring strips between the inner layer of brick and the plaster wall, offering very little room through which to draw cable. Only the inside walls, constructed of  $2" \times 4"$  studs, offer

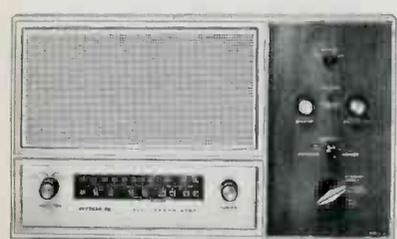


Fig. 3. Music distribution system.

room for cables. A brick veneer house has one course of brick, with  $2" \times 4"$  studs in the outer as well as the inner walls. Frame houses have  $2" \times 4"$  studs in all walls.

Connecting the system from room to room requires running the cables up the space between studs to the attic, across the attic, and then down between studs in another wall. An alternate method is to run the cable down into the basement or crawl space, across and up into the wall between the studs again. The bottom of the studs are usually nailed to horizontal  $2 \times 4$ 's (called the sole plate) which, in turn, are nailed to the flooring. Thus, you will have to drill through both the sole plate and the flooring to get into the space between studs. Similar construction is used at the top of the studs, so about the same amount of drilling will be required if you go up to the attic and over.

The toughest job is running the cable from floor to floor in a two-story house. This requires removal of the baseboard on the second floor and drilling down to the space between the studs in the floor below. Outlet holes to the stations should be drawn through the baseboard. (You will need an electrician's fish line to draw the cables through holes and spaces.)

Of course, installation is much easier in homes or buildings under construction. However, the job will probably be spread over a long period of time. In addition, the actual layout of the cable will probably have to be done by a union elec-

trician. Indicate to the electrician where the cables are to run and, if junction boxes are used, have him leave about 3" of cable hanging out. If the cable is to run directly to the stations, have him leave about 8" of cable. Roll up the excess cable close to where it comes out of the baseboard, and enclose it in a plastic bag to keep it clean during plastering and painting, as shown in Fig. 6. After the interior is completely finished, you can return and hook up the stations.

#### Intercom Systems

During the planning phase of the operation, it must be determined if the complete installation is to be in-wall or on-wall, or if only the master station is to be built-in and the substations on-wall. For built-in installations in new homes, you either will have to let the plasterer know where the wall outlets are to be located, or return to do the cutouts yourself after the plastering is completed and before the painting is started. Most in-wall stations hang from the plaster or wallboard, but some heavier units require wood framing for support. Also, some systems use metal boxes that can be put in by the plasterer.

If a front door station is to be part of the system installed in a brick house, it must be put in when the bricks are laid. The architect should include the box in his masonry specifications.

When a single in-wall master amplifier is centrally located and is not part of the master station, be sure the electrician provides an AC outlet where the amplifier is to be located. This should be a behind-



Fig. 4. Both radio and phonograph are included in this design.




## "I like the results . . .

. . . when I install the JFD Color Laser," comments Elmer Whitmore, Hill's Antenna Service, Saginaw, Michigan, who has made over 13,000 antenna installations in the 14 years he has been in business.

"That's a real good color picture!" is what I like to hear after I put up a new antenna because to me a pleased customer is like money in the bank. So I don't take chances—I install JFD Color Lasers for top color pictures.

"I like the way the Color Lasers work on all the VHF and UHF stations here. They rig up fast and give us better results in the form of precise color and ghost-free images."

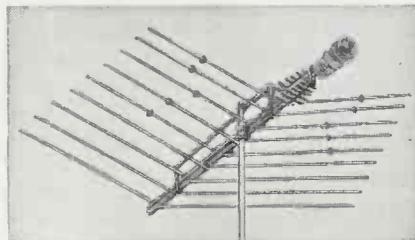Elmer Whitmore prefers JFD engineered-for-color Color Lasers, like many other professional antenna installers, for best possible performance.



**BRILLIANT COLOR** — flat (frequency independent) response across each channel, free from suck-outs or roll-offs. Keeps colors vivid and alive.

**PATENTED W-I-D-E BAND LOG PERIODIC DESIGN** — the most efficient ever developed — provides higher gain, better signal-to-noise ratios, needle-sharp directivity. Eleven patents cover its revolutionary space-age design.

**MORE DRIVEN ELEMENTS.** Harmonically resonant capacitor coupled design makes dual-function elements work on both VHF and UHF frequencies. *Entire* antenna (not just part of it as in other log periodic imitations) responds on every channel.

**LUSTROUS, ELECTRICALLY CONDUCTIVE GOLD ALODIZING** promotes signal transfer, protects against corrosion, enhances appearance.

### PROFESSIONAL ANTENNA INSTALLERS KNOW —

*The Best Antenna for Color TV is The Color Laser by*

**JFD**<sup>®</sup>  
Now at your JFD distributor!

### JFD ELECTRONICS CO.

15th Avenue at 62nd Street, Brooklyn, N.Y. 11219

JFD International, 64-14 Woodside Ave., Woodside, N.Y. 11377

JFD de Venezuela, S.A., Avenida Los Haticos 125-97, Maracaibo, Venezuela

LICENSED UNDER ONE OR MORE OF U.S. PATENTS 2,958,081; 2,985,879; 3,011,168; 3,108,280; 3,150,376; 3,210,767. RE. 25,740 AND ADDITIONAL PATENTS PENDING IN U.S.A. AND CANADA. PRODUCED BY JFD ELECTRONICS CO. UNDER EXCLUSIVE LICENSE FROM THE UNIVERSITY OF ILLINOIS FOUNDATION. LICENSED UNDER ONE OR MORE OF U.S. PATENTS 2,955,287 AND 3,015,821 AND ADDITIONAL PATENTS PENDING.

Circle 14 on literature card

December, 1967 / PF REPORTER 27

the-wall outlet for a permanent connection. The same stipulation also applies to in-wall master stations with a built-in amplifier.

Since the output voltages from intercom amplifiers are low, it is not necessary to run the cables in conduit—unprotected cable meets electrical codes. The basic cable employed between a master and a sub-station is three-conductor; one wire is common, one is used for incoming, and one is used for outgoing. For convenience, most intercom systems employ multiconductor cable serving a number of stations. Some systems are designed with balanced lines and use twisted pairs. Others use shielded wire for the incoming lead; however, most do not. It is usually best to use the cable specified by the manufacturer of the equipment, even if it costs more. In most cases, the manufacturer's specified cable will assure proper operation.

You will not be faced with the problem of matching speaker impedances to the amplifier, as in public address systems. Most intercom systems utilize 45-ohm voice coil speakers. Although the amplifiers are designed to feed into a lower impedance, a near match for optimum power output is achieved when a number of speakers are connected in parallel. Since relatively little power is required for any one speaker, any mismatch associated with the system will not seriously affect the overall operation.

#### Music Distribution Systems

This type of system is nearly always an in-wall installation, which means additional plaster cutouts, not only for the control amplifier/tuner/record player, but also for the speakers in each room. (The plaster

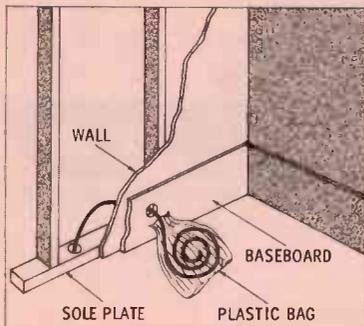


Fig. 6. Plastic bag protects cable.

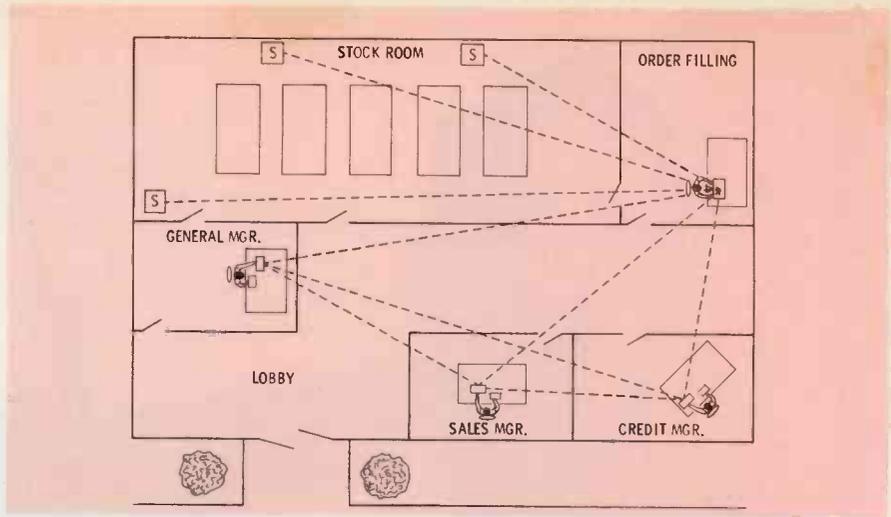


Fig. 5. Floor plan showing positions of stations and communication between each.

walls make excellent baffles for the speakers). Proper ventilation can be a problem with in-wall applications, so use transistorized amplifiers when possible—they run cooler. Also, don't forget the possibility of outdoor speakers. The cable can be run during the initial installation and the speakers added then, or if the patio has not been built or its location has not been determined, the speakers can be added later.

#### Industrial Installations

Installations in offices and plants are often easier than in homes. Frequently, the customer will permit you to tack the cables along the outsides of the walls. However, you will still have to go through the walls to get from one room or office to another. This will require a star drill and a lot of pounding or an easier method such as using an electric drill equipped with a carbide-tipped bit.

#### Schools

Most schools require that an "all-call" function be included in their intercom systems to permit the principal to make a general announcement to all classes at one time. Except for this added function and a few minor cable differences, installations in schools are no different electrically than a home or small office system. However, schools are frequently sensitive to even the most remote possibility of a fire hazard and may go beyond the requirements of local codes by demanding that the intercom cables be run in conduit.

#### Pricing

After you have sized up the job and determined what is going to be required in terms of equipment and labor, you are ready to sit down and figure out what you must charge to realize a reasonable profit.

Perhaps the most important point to remember about pricing is to quote the customer a "package" price; don't price the equipment and labor separately. The primary reason behind this rule is that in today's marketing arrangements it is probable that the customer will be able to obtain the equipment at a price that is competitive to your "wholesale" or "dealer net." Thus, in many instances, if you are able to realize a profit on the equipment and yet retain the customer's good will, you must include your profit in the "package" price. Remember, you are not just selling the customer equipment and labor, but also your experience and knowledge. One vote of caution here concerning "package" pricing: some states regard package pricing as a form of contracting, and in order to do so you must have a contractor's license.

#### Conclusion

Once you have familiarized yourself with the line(s) of equipment you plan to install, solicit the business and get the experience. You may quote too low a price for the first installation, but it's worth it to get the experience. After two or three installations you will be getting your share of this profitable field. ▲

# TRIPPLET

## EXTRA QUALITY IS HIDDEN\*

### MODEL 630 V-O-M PRICE † \$58<sup>00</sup>

### Standard Of The Industry

#### USES UNLIMITED:

- Field Engineers
- Application Engineers
- Electrical, Radio, TV, and Appliance Servicemen
- Electrical Contractors
- Factory Maintenance Men
- Industrial Electronic Maintenance Technicians
- Home Owners, Hobbyists



#### FACTS MAKE FEATURES:

- 1** Popular streamlined tester with long meter scales arranged for easy reading. Fuse protected.
- 2** Single control knob selects any of 32 ranges—less chance of incorrect settings and burnouts.
- 3** Four resistance ranges—from .1 ohm reads direct; 4½ ohm center scale; high 100 megohms.

Attention to detail makes the Triplet Model 630 V-O-M a lifetime investment. It has an outstanding ohm scale; four ranges—low readings .1 ohm, high 100 megs. Fuse affords extra protection to the resistors in the ohmmeter circuit, especially the X1 setting, should too high a voltage be applied. Accuracy 2% DC to 1200V. Heavy molded case.

#### RANGES

DC VOLTS	0-3-12-60-300-1,200-6,000 at 20,000 ohms per volt.
AC VOLTS	0-3-12-60-300-1,200-6000 at 5,000 ohms per volt.
OHMS	0-1,000-10,000.
MEG OHMS	0-1-100.
DC MICRO-AMPERES	0-60 at 250 millivolts.
DC MILLI-AMPERES	0-1-2-12-120 at 250 millivolts.
DC AMPERES	0-12.

DB: -20 to +77 (600 ohm line at 1 MW).

OUTPUT VOLTS: 0-3-12-60-300-1,200; jack with condenser in series with AC ranges.

†630A same as 630 plus 1½% accuracy and mirror scale only \$68<sup>00</sup>  
**TRIPPLET ELECTRICAL INSTRUMENT COMPANY, BLUFFTON, OHIO**



THE WORLD'S MOST COMPLETE LINE OF V-O-M'S. AVAILABLE FROM YOUR TRIPPLET DISTRIBUTOR'S STOCK.

Circle 15 for information  
[www.americanradiohistory.com](http://www.americanradiohistory.com)



**Table 1.**

Reading at Point A (Fig. 1)

1. AGC voltage is normal.
2. Abnormally high AGC voltage
3. Abnormally low AGC voltage.

2nd Step in Service Procedure

1. AGC can be considered as functioning normally.
  1. Usually caused by divider resistors in supply lines. Check all resistors in bleeder networks for value changes.
  2. Bias voltages (grid and cathode) incorrect. Check bypass capacitors for opens; check cathode resistor for change in value.
1. Check shape and amplitude of pulse derived from horizontal output transformer.
2. Check shape and amplitude of waveform from video output circuit.

simultaneously, the plate voltage rises to a much higher potential, the grid voltage overcomes the fixed bias, and an instantaneous pulse of plate current flows. This rise in plate voltage and change in grid bias (caused by simultaneous arrival of signal pulses) must occur at the same time. Either pulse arriving by itself will not cause the tube to conduct.

When the AGC tube conducts and plate current flows, capacitor C1 charges very rapidly, but is prevented from discharging rapidly by the combined resistance of R1, R2, R3, and R4. Because of this rapid charge and slow discharge of C1, an average current flow is developed which, in turn, produces the AGC voltage. Additional filtering of the AGC voltage is accomplished by C2, C3, C4, and C5.

When a station signal with extremely stable strength is received, charge and discharge of C1 is almost nonexistent, and a constant negative AGC voltage is developed. This voltage is applied to the RF and IF stage(s) in the receiver.

When a weak signal is received, a comparatively weaker sync pulse is applied to the control grid of the AGC keyer and the control grid voltage becomes less positive. Consequently, the AGC keyer conducts less and the plate current decreases. The ratio of charge and discharge of C1 through the bleeder network changes, causing a decrease in the average current flow and, consequently, a decrease in the negative

AGC voltage. The decrease in AGC voltage permits more amplification in the RF and IF stages.

Changing the channel selector to receive a station of comparatively strong signal strength results in the following actions: A much stronger sync pulse is applied to the control grid, driving it more positive. The AGC tube conducts more and the increased plate current charges the AGC capacitor. The charge-to-discharge ratio of C1 changes, and the negative AGC voltage is increased. When this increased AGC voltage is applied to the RF and IF stages, they conduct less and the amplification of the incoming signal is reduced.


### Noise-Canceling Effects

In the foregoing discussion, it was noted that the AGC keyer tube will

not conduct unless the proper signal pulses are applied simultaneously to its plate and grid. It was also noted that these pulses must be of the correct amplitude and polarity. The pulse applied to the plate is derived from a winding (separate or tap) on the horizontal output transformer. The pulse applied to the control grid is obtained from the video output circuit. Since both of these pulses occur during horizontal retrace and must arrive at the plate and grid at the same instant in order to cause conduction, any random, spurious pulses arriving at either the plate or grid cannot cause the tube to conduct. A spurious pulse arriving at the plate will not cause conduction because the grid bias keeps the tube cut off. A random noise pulse arriving at the grid of the AGC keyer will not produce conduction because of the extremely low value of voltage at the plate. Thus, any spurious noise pulses are prevented from reaching the RF and IF stages through the AGC line.

### Servicing Procedures

The servicing of AGC circuits has always been a source of irritation to most service technicians, mainly because of difficulty in localizing the trouble to the AGC circuits. Visual indications on the picture tube screen often leave doubt as to whether the trouble is in the IF's, sync, or AGC circuits. The first step in localizing a trouble of this nature is to measure the AGC voltage. There can be three indications when you read this voltage: (1) AGC voltage is normal, (2)

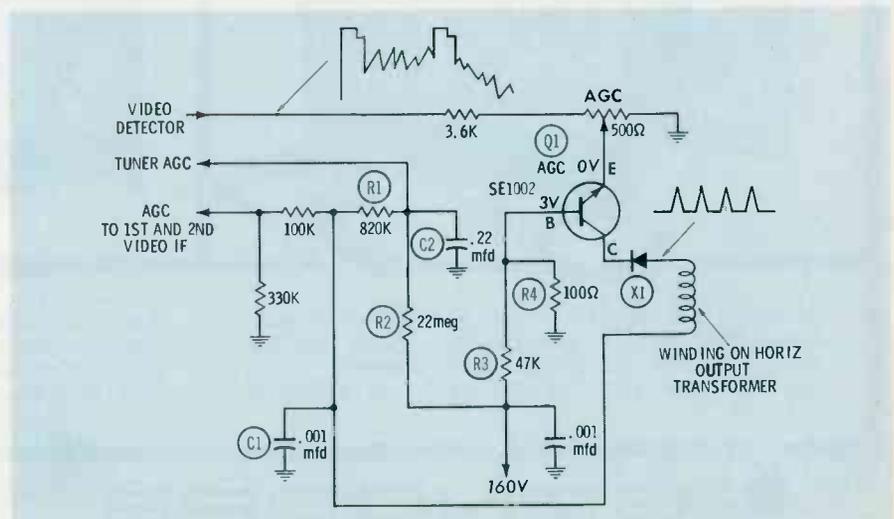

**Fig. 2. Transistor-equipped AGC system employed in hybrid chassis.**

# COLOR GENERATORS

# FOR EVERY NEED

4 reasons why Sencore is your best buy  
in professional test instruments

1

## LOBOY CG10

America's lowest priced professional quality standard color bar generator. All solid state. Battery powered for maximum portability.

\$89.95



2

## LOBOY CG12

AC operated version of the CG10. Also has 4.5 MHz crystal controlled signal for fine tuning adjustment.

\$109.95



3

## COLOR KING CG141

Absolute stability assured by exclusive "Temp Control" and new timer circuitry. All standard patterns, plus new movable single dot and single cross. Analyzing features too.

\$149.95



4

## COLOR ANALYZER CA122B

The complete analyzer for color and B&W—far more than just a color generator. Has variable RF and IF outputs, composite video, chroma, and horizontal and vertical sync pulses.

\$187.50



Whatever the need, Sencore has the color generator that is just right for you. Each has the built-in quality you expect from Sencore. Each has standard RCA licensed color bar patterns.

Each is triple tested for guaranteed accuracy. Each is steel encased with chrome panel. See your distributor for more reasons why Sencore is your best buy, always.



# SENCORE

NO. 1 MANUFACTURER OF ELECTRONIC MAINTENANCE EQUIPMENT  
426 SOUTH WESTGATE DRIVE ADDISON ILLINOIS 60101

AGC voltage is abnormally high, (3) AGC voltage is abnormally low. The next step in the servicing procedure is determined by which of these three indications you received. Table 1 lists the steps to be taken with each indication.

### Hybrid Designs

Hybrid television receivers usually use a transistor in the AGC circuit. Transistors used in this function can be connected in a common-emitter configuration because the output is applied to the high impedance offered by the grids of the electron tubes in the RF and IF circuits.

The basic operation of the hybrid TV AGC circuit in Fig. 2 is as follows: Video signals from the video detector are applied to the emitter. The base is fixed biased, while the collector is pulsed or keyed from a winding on the horizontal output transformer. When the video signal is impressed on the emitter, the forward bias of the transistor increases and, consequently, the collector current increases. As the collector current flows through the external collector circuit, the voltage drop across R2 becomes more negative and an increased negative voltage is applied to the IF and RF stages via their respective AGC lines. Filtering and smoothing of the keyed output is accomplished by C1, C2, and R1.

This circuit, like all AGC circuits, has one basic function: To

sample the video signal and produce a regulating voltage that is used to keep the gain of the RF and IF amplifier stages constant, thus providing a video output signal that is relatively independent of the strength of the received signal.

Waveform, DC voltage, and resistance measurements are all beneficial when servicing defects in this circuit. One inherent trouble symptom associated with this circuit is "negative picture." Some possible causes of "negative picture" are: shorted C1 or C2, open X1, defective AGC control, value changes of components, and faulty transistor (Q1). The main problem in troubleshooting this circuit, as with nearly all AGC problems, is in localizing the defect to the AGC circuit.

### Transistor AGC Circuits

AGC circuit action in television receivers employing transistors differs from that of tube-type receivers. In tube-type receivers, the characteristics of the tubes (remote cutoff types) allows the tube to be biased to a level that requires simultaneous application of pulses from the video and horizontal output circuits before conduction will occur. The amount of conduction is dependent on the strength of the incoming pulses; therefore, the average plate current flow fluctuates in accordance with the strength of incoming signals.

This type of action is somewhat more difficult to accomplish in transistor circuitry. Characteristics of

transistors are usually described as "sharp cutoff"; consequently, the design of a transistor circuit to regulate the stage gain of RF and IF amplifiers is a little more complicated.

As mentioned before, the purpose of any AGC system is to sustain constant voltage at the input of the final video amplifier stage, regardless of the signal strength at the antenna. Most transistor receivers accomplish this by controlling the gain of the RF amplifier and 1st video IF amplifier stages. This is done in the RCA KCS156 chassis (Fig. 3) in the following manner:

As the signal level increases at the antenna, the output of the video amplifier increases. Horizontal pulses from the horizontal output transformer arrive at the collector at the same time that pulses from the video amplifier arrive at the base, causing the AGC gate transistor to conduct. The long time constant of the AGC gate output circuit sustains the positive voltage during horizontal scan time. To prevent the collector-to-base junction of the AGC gate from becoming forward biased by the AGC voltage, a diode is connected in the AGC gate collector circuit. The AGC voltage is then applied to the RF AGC amplifier and, subsequently, to the RF amplifier stage.

The RF amplifier has two purposes: (1) to amplify the incoming RF signal and (2) to amplify and couple the AGC voltage variations to the IF AGC amplifier. The IF AGC amplifier then amplifies and couples the signal to the first video IF amplifier as reverse bias, reducing the gain of this stage in accordance with the strength of the AGC voltage. The stronger the AGC voltage, the more the gain of the first video IF is reduced. This circuit maintains a fairly constant signal level at the emitter of the 1st video amplifier transistor over a comparatively wide range of input signal levels.

The gain of a transistor amplifier circuit can be reduced by either forward or reverse bias. In the case of the RF amplifiers in Fig. 4, the gain is reduced by applying forward bias voltage; and in the video IF stage, the gain is reduced by applying reverse bias voltage. ▲

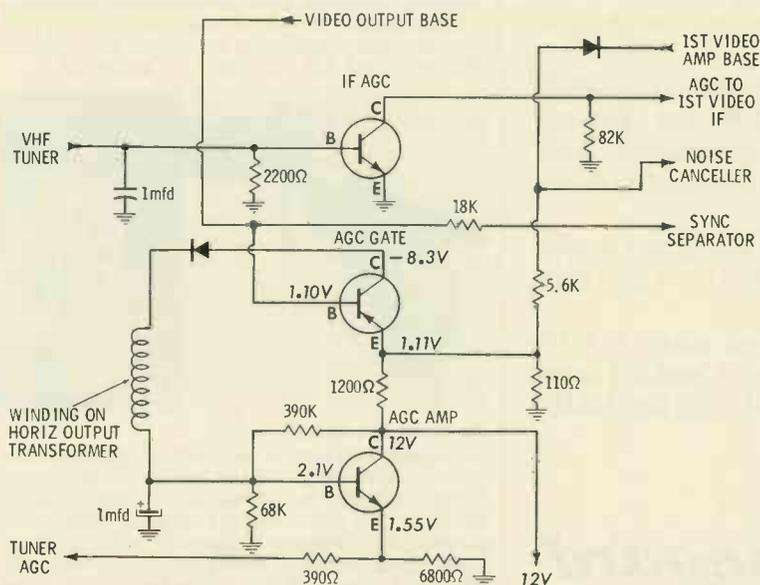


Fig. 3. Multistage AGC system required by transistor chassis.

# When it comes to 82-channel, ONLY EVERY to install any



Doesn't make any difference how big or how small the system, or where you plan to install it (apartment building, hotel, motel, school, home, etc.) Winegard has all the products you need from antenna to outlet.

And we're not just talking about quantity. Winegard MATV products, all of them, are the finest quality commercial equipment available. They feature printed circuitry utilizing the newest, best performing temperature stable hi-input transistors.


Winegard not only gives you more products to choose from, but more professional assistance, too. That's right! Our staff of MATV engineers is ready to give you all the system layout service you need. And, of course, the service costs you nothing.

Yes, Winegard gives you everything you need to guarantee the best possible reception on each and every set in the system—on all channels—and in color as well as black & white.

You get maximum reliability with minimum maintenance. You get easy installation using standard fittings. You get attractive design and complete customer satisfaction. And, just as important, you get that feeling of personal satisfaction that comes from a job well done.


What more could you ask for except the highest profits in the new and skyrocketing MATV industry. And that's exactly what you get from Winegard!

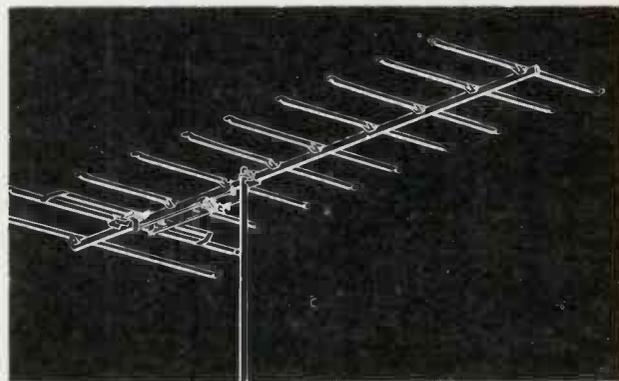(You can see here just a very few of our many MATV products.) Get all the facts today, and start making more money faster with Winegard. Send for MATV kit No. DMS.


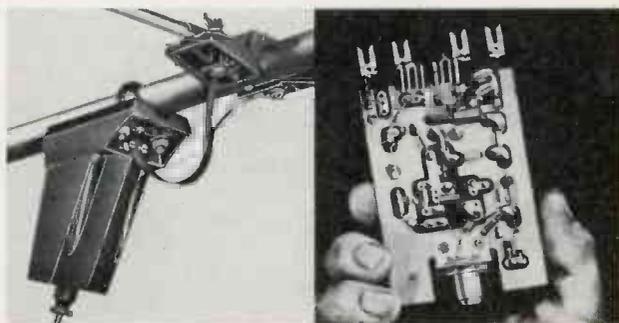
#### Transcoupler Yagis

Whether you're planning a master antenna system for a single set in a home, or several hundred sets in an apartment complex, it's essential that you provide the strongest, cleanest signal possible on all channels. And especially in color. It takes the best performing, longest lasting antenna available. And Winegard has them; 25 five and ten element Transcoupler yagis plus a full line of Super Colortron VHF-FM, VHF-UHF-FM, UHF and FM antennas.




#### Antenna Pre-Amplifiers

Winegard's exclusive solid-state, printed circuit cartridge pre-amplifiers slip into the built-in, weatherproof housing of Super Colortron antennas, or into the Model ACH-1 Universal Cartridge Housing that mounts easily on any antenna. Downlead connection is internal, with 100% protection from the weather. Eight different cartridge pre-amplifiers are available, enabling you to customize each antenna installation for perfect color and black & white reception on all channels. All models utilize the newest silicon overlay transistors with an unequalled input of 500,000 microvolts (1/2 volt). Totally eliminates overload problems regardless of location.



Winegard Company • 3000 Kirkwood Street • Burlington, Iowa 52601
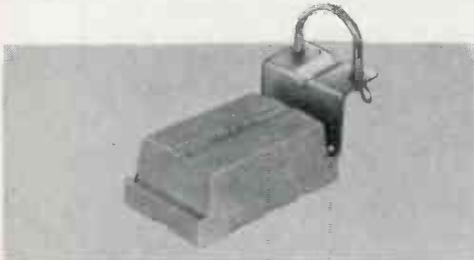
# solid state, color MATV systems, WINEGARD HAS THING YOU NEED size system easily and profitably!



### Channel Control Couplers

Allow you to couple any number of VHF-FM antennas, equalize the signals to a predetermined level and match the 300 ohm antennas to a 75 ohm coaxial download. Any coupled antenna can be attenuated from 0 to -20 db with special plug-in attenuator pads.

### Ultra-Plex Distribution System

Ultra-Plex is a unique, solid state, 82-channel modular plug-in MATV distribution system. Components of the Ultra-Plex system are designed to match and work perfectly with each other. Ultra-Plex equipment will never become obsolete—new VHF stations, UHF stations and FM bands may be added at any time with negligible expense to the owner. Ultra-Plex gives the installer an unprecedented flexibility and complete signal control, regardless of system size. It works equally well in small or large systems—in apartment buildings, motels, hotels, hospitals, schools, etc.



### Solid State Distribution Amplifiers

Winegard tv system amplifiers are designed to highest commercial standards with models and accessories available to provide optimum color and black & white reception to any number of sets. Each amplifier incorporates the most recent developments in solid state circuitry with the advantages of increased life expectancy, reliability and less power consumption. Higher gain, greater band-width, lower noise figures and improved VSWR are other advantages of Winegard's high performance amplifiers.

### 82-Channel Line Splitters



Line splitters divide the tv signals on a trunk line into equal parts and, when properly used, greatly increase the

number of taps in a tv distribution system. Winegard line splitters have very low insertion loss, low VSWR and high isolation between outputs to insure perfect transmission of color tv signals.

### TV Signal Equalizers

Broad band distribution amplifiers operate most efficiently when input signals are equal and total picture carrier signals are the specified level. Winegard makes equalizers that can couple and equalize up to four low band or FM single channel antennas—or couple and equalize up to four high band single channel antennas.


### Variable Isolation 82-Channel Line Drop Taps

Drop taps allow the system designer to layout trunk lines in a straight line and operate outlet devices in remote locations with feeder lines. Variable isolation control from .10 to 25 db, with fast, easy adjustment, makes it unnecessary to specify and order several fixed values of tap to best utilize signals at the end of each trunk line.


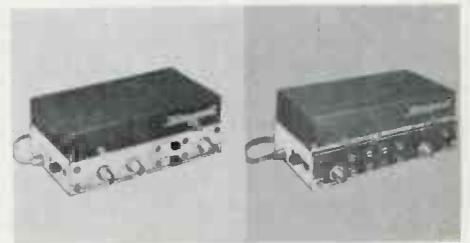
### Variable Isolation 82-Channel Line Tap Offs

All Winegard line taps have 82-channel capability, and can be used for VHF, UHF or FM or any combination of the three. The variable isolation feature enables the installer to independently vary the VHF and UHF isolation values from 10 to 25 db through simple adjustment of "wiper arms" located at front of tap. Use of 82-channel line taps insures that a system cannot become obsolete regardless of what channels are later added to the system. Flush and surface mounts.



### Solid State Booster-Couplers

Winegard offers several transistorized booster-couplers which will handle up to 4 TV/FM outlets or sets from a single antenna—up to 16 sets using 75 ohm outlets. Seven different models: some for channels 2-13 plus FM, some for channels 2-83 plus FM. Built to finest commercial quality standards. Available in both 300 and 75 ohm models. Extremely high (500,000 microvolt) input eliminates overload problems.

### 82-Channel + 25 db Amplifier

New "color system" amplifier is ideal for home and smaller systems. Solid state, printed circuitry with excellent stability. Can't become obsolete when new channels come on the air. By adding Winegard's unique line amplifiers, you can lay out and install most systems without calculations of any kind. Separate VHF and UHF inputs and power for VHF and UHF preamplifiers. Easy to customize each installation to exact signal conditions.

Plus... UHF single channel converters, antenna and back-of-set matching transformers, band separators, interference rejection filters, etc.

**"I was TROUBLE-SHOOTING  
in the DARK 'til Sencore's Scope  
Showed Me What Color Waveforms  
Really Look Like."**



**Technicians everywhere are talking about the PS127 5" Wide Band Oscilloscope. Try one and you, too, will send us comments like these—**

"So easy to use! With my Sencore scope I can read high or low frequency signals without band switching. As easy to use as a voltmeter."—R. L., Portland, Ore.

"I've only had my PS127 a couple of months, but it's more than paid for itself already with the extra jobs I've been able to handle."—S. O., New Orleans, La.

"With the direct peak-to-peak readout I can compare voltage readings to those on the schematic without wasting valuable time setting up my scope with comparison voltages."—J. M. F., Plymouth, Michigan.

"Those Sencore exclusives really sold me, like the extra 500KC Horizontal Sweep range and the free high voltage probe."—D. N., Brooklyn, N.Y.

You'd expect a wide band scope of this quality to cost at least double."—W. L., Chicago, Ill.

"With the PS127, I find I can trouble-shoot those tough ones twice as fast as before—especially color TV."—F. C., Burlingame, Calif.

"Once I compared the specs, I knew Sencore had the best buy in scopes. We now have three PS127's in our shop."—J. S., Ft. Lauderdale, Fla.

#### SPECIFICATIONS

Vert. Freq. Resp. 10 CPS to 4.5 MC  $\pm$  1 db, - 3 db @ 6.2 MC • Rise Time .055 Microseconds • Vert. Sens. .017 Volts RMS/inch • Horiz. Freq. Resp. 10 CPS to 650 KC • Horiz. Sens. .6 Volts RMS/inch • Horiz. Sweep Ranges (10% overlap) 5 to 50 CPS, 50 to 500 CPS, 500 CPS to 5 KC, 5 to 50 KC, 50 to 500 KC • Input Impedance 2.7 megohms shunted by 99 MMF, 27 megohms shunted by 9 MMF thru low-cap. jack • High Voltage Probe 5000 Volts Max. • Dimensions 12"x9"x15½", Wt. 25 lbs. • Price Complete \$199.50



NO. 1 MANUFACTURER OF ELECTRONIC MAINTENANCE EQUIPMENT

**SENCORE**

426 SOUTH WESTGATE DRIVE, ADDISON, ILLINOIS 60101

Circle 18 on literature card

## Book Review

**FET Circuits:** Rufus P. Turner; Howard W. Sams & Co., Inc., Indianapolis, 1967; 160 pages, 5½ x 8½", soft cover; \$3.25.

An interesting book for the technician who likes to build or modify his test equipment. It is equally valuable to the Ham, CB'er, Hi-Fi addict, and other electronic hobbyists.

Mr. Turner devotes the first chapter to the fundamentals of the FET. This section is 10 pages of field-effect theory, geometry, history, and ratings.

With the necessary theory out of the way, we move to amplifier circuits. There's 22 pages here, and 18 circuits are shown. All circuits include complete parts data, so the reader can duplicate them as projects. Included in the chapter on amplifiers are: a simple small-signal AF pre-amplifier, AF source follower, two-stage RC-coupled AF amplifiers, transformer coupled amplifiers, phase inverters, audio mixers, audio bandpass and band-reject amplifiers, video amplifiers, IF amplifiers, etc.

Chapter 3 deals with oscillator circuits. Twelve circuits are shown, ranging from AF oscillators to HF crystal oscillators. Analyzing these circuits, the reader immediately perceives that FET's can be substituted for tubes in nearly all triode applications.

Chapter 4 is titled "Receiver and Receiver - Accessory Circuits." The first circuit shown is a basic broadcast-band superhet receiver. There are several interesting innovations, including the use of ceramic filters instead of IF transformers. Other circuits in this chapter include crystal converters, BFO's, a Q-multiplier, and a squelch circuit.

Chapter 5 deals with transmitters and accessories. Several flea-powered transmitters are shown, as well as frequency multipliers, a balanced modulator, and two monitors.

Control circuits are explained in Chapter 6. Among the projects are every kind of controlled relay imaginable, from VOX to light-operated. Also shown is a modulated-light detector/amplifier.

The last chapter covers instruments. Circuits are shown for nineteen different test instruments, from voltmeters to light meters. Included is a circuit for a direct-reading audio-frequency meter. This instrument employs two FET's and eighteen resistors and capacitors, covering 0-100 kHz in four ranges.

Included in the appendixes are basing diagrams and source guides for all the FET's mentioned in the text. ▲

# EXTRA POWER

with

# FINCO

# AMPLIFIERS

*For perfect color TV and  
FM Stereo Reception*

**FINCO MODEL #65-4**  
Antenna Amplifier  
\$47.95 list VHF-TV  
Two-transistor Antenna  
Amplifier for 75 OHM  
Downlead, and power  
supply with built-in  
single or dual 300 ohm  
outputs. Provides 12  
dB gain in the low band  
and 14 dB gain in the  
high band.



**FINCO MODEL #65-1**  
Distribution Amplifier  
\$29.95 list 2-tube 4-  
output VHF-TV or FM  
Distribution Amplifier  
for 300 OHM Opera-  
tion, providing 8 dB  
gain at each 300 ohm  
output to feed home or  
commercial systems.



**FINCO MODEL #65-5**  
Distribution Amplifier  
\$44.95 list VHF-TV 75  
OHM Single Outlet Dis-  
tribution Amplified for  
deluxe home or com-  
mercial use to feed  
multiple sets through  
line tap offs or split-  
ters. Delivers 17 dB  
Low Band and 14 dB  
High Band.



**FINCO MODEL #65-2**  
Distribution Amplifier  
\$39.95 list 2-tube 4-  
output VHF-TV or FM  
Distribution Amplifier  
for 75 OHM CO-AX  
Operation, providing 6  
dB gain at each 75 ohm  
output to feed deluxe  
home or commercial  
systems.



**FINCO MODEL #65-6**  
Amplifiers \$79.95 list.  
VHF-TV Antenna Mount-  
ed two-transistor pre-  
amplifier with 75 OHM  
two-tube Single Output  
Distribution Post-am-  
plifier up to 30 dB gain  
for improved reception.  
Used in home or com-  
mercial installations to  
feed multiple sets.



**FINCO MODEL #65-3**  
Antenna Amplifier  
\$44.95 list New VHF-  
TV Antenna Amplifier  
and Power Supply with  
built in single or dual  
outputs to improve re-  
ception of weak signals  
in fringe areas. Pro-  
vides 12 dB gain in the  
low band and 14 dB  
gain in the high band.



**FINCO MODEL #65-7**  
FM Signal Amplifier  
\$24.95 list. One-trans-  
istor Indoor Behind-  
the-set FM amplifier  
with a passive filter in-  
put circuit to reject sig-  
nals outside the FM  
band which cause in-  
terference. Delivers 20  
dB Gain.



## Sets "COME ALIVE" with Brilliant Sound and Color

A Finco high-gain, low-noise amplifier  
will bring in the sharpest **COLOR** or  
B & W TV picture and the finest sound!

**All FINCO Products are Engineered  
For Color!**



Write for Color Brochure #20-411.

**THE FINNEY COMPANY**

34 W. Interstate Street • Dept. 310 • Bedford, Ohio 44146



ACE

TV-REPAIR

# Surprising what you can pick up in a good week's work.

Play along with us and we'll see that you get a little something extra to take home. Like a shiny new toaster or an electric percolator. Maybe a fishing reel or a Harris Tweed jacket.

For that matter, we'll get you a toboggan, if that's what you want most.

What we ask in return is that you use Sylvania tubes when you're repairing TV sets—both our own make and others.

As you know, we make color and black & white picture tubes and receiving tubes for virtually every make set on the market. In fact, 15 out of 21 color set manufacturers use some Sylvania picture tubes as original equipment.

So you shouldn't have much trouble moving a lot of our tubes, week in and week out.

When you use our tubes, you get our Sylvania Bright Guys award certificates as a bonus. They're not quite the same as money. But they will get you the kinds of things only money can buy.

Your distributor is the man to contact for details. He'll give you a Sylvania Bright Guys award kit (which includes a catalogue listing the good things we offer—about 1500 in all).

Naturally, the more tubes you buy from him, the more certificates he'll give to you.

It's a pretty fair way to work, wouldn't you say?



**SYLVANIA**  
A SUBSIDIARY OF  
GENERAL TELEPHONE & ELECTRONICS

# NOTES ON TEST EQUIPMENT

*analysis of test instruments  
...operation...applications*

by T. T. Jones

## CRT Cadet

The new CRT tester/rejuvenator shown in Fig. 1 is SENCORE's Model CR13. It's an update of the older model CR133. Several improvements have been incorporated, including the use of a more rugged heater transformer. It is no longer necessary to have a separate switch position for color tubes. The new heater transformer has only seven windings; some of the voltages formerly furnished have been considered to be unnecessary. The voltages actually furnished are given in the table.

Switch Position	Actual Voltage
2	2.3
4	4.2
5	4.7
6	6.3
8	8.4
12	12.6

Another new feature is the added sockets, one for the GE 11SP22,

and one for 7-pin portables. This latter we think has been long overdue. These small-size 7-pin CRT's have been around for several years, and it's surprising that only in the last few months have the equipment manufacturers begun to incorporate sockets for them in CRT testers.

The CR13 performs all essential tests on both color and B-W CRT's. For an analysis of the circuit, see

### SENCORE CR13 Specifications

#### CRT's tested:

All presently manufactured TV types, both color and B-W.

#### Tests performed:

Interelectrode shorts; emission; cutoff; life; color gun balance.

#### Corrective functions:

Rejuvenates cathode; removes cathode-to-grid shorts; welds open cathode.

#### Features:

Variable G1 and G2 voltages; line voltage compensation; replaceable plug-in socket cables; automatically controlled rejuvenation and weld.

#### Size (HWD):

10¼" × 10¾" × 4¼".

#### Weight:

8½ pounds.

#### Power Source:

105-125 VAC, 50-60 Hz,  
23 watts.

#### Price:

\$79.95.



Fig. 1. SENCORE's CRT Cadet.

"Notes on Test Equipment", Feb. and Sept., 1965.

The tester is housed in a black vinyl-covered steel case. It's quite rugged, yet weighs a pound-and-a-half less than its predecessor.

### Transistorized Voltohmmeter

The model designation on Triplet's new FET meter leads us to believe there's more to come. Fig. 2 shows this meter, the Model 600 Type 1. Remembering the Model 630, with all its variations, we wonder just how far the Triplet engineers intend to go with this one. In any event, the Type 1 is a first-rate meter and may well be the start of a new family.

The instrument (Fig. 2) is a completely new concept in design, and resembles nothing that Triplet has produced heretofore. The styling is eye-catching, with a modern high-impact plastic case. The leads are streamlined and compact, through the use of an RCA-type phono jack for the signal lead. The signal probe has a switch to select either



Fig. 2. Model 600 Type 1 FET meter.

# Why not sell the best

## ZENITH TUBES built to the quality standards of Zenith original parts

### "Royal Crest" Circuit Tubes

More than 875 tubes—a full line with the same quality as original Zenith equipment. Get Zenith tubes for greater dependability and finer performance.

Order all genuine Zenith replacement parts and accessories from your Zenith distributor.



### TV Picture Tubes

For color TV, B&W TV or special purposes. A complete Zenith line of more than 200 tubes built for greater reliability, longer life.

Zenith B&W replacement picture tubes are made only from new parts and materials except for the glass envelope in some tubes which, prior to reuse, is inspected and tested to the same high standard as a new envelope. Some color picture tubes contain used material which, prior to reuse, is carefully inspected to meet Zenith's high quality standards.

**ZENITH**<sup>®</sup>  
The quality goes in before the name goes on

Circle 21 on literature card

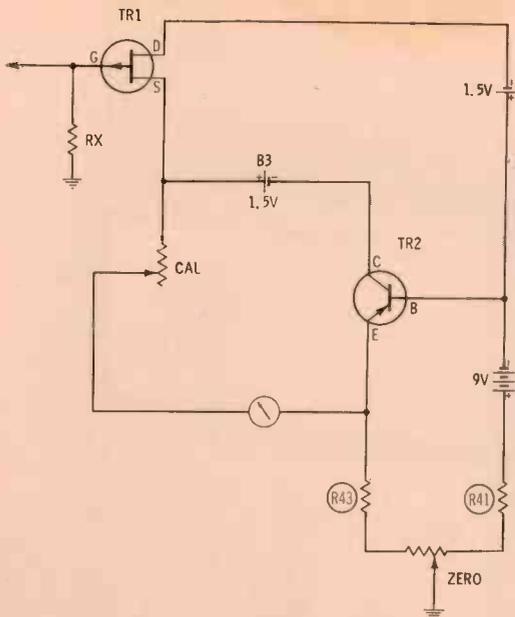


Fig. 3. Simplified schematic of the FET meter.

### Triplet Model 600 Type 1 Specifications

#### DC Voltmeter

##### Ranges:

0-.4, .8, 1.6, 4, 8, 16, 40, 160, 400, 1600V.

##### Input Resistance:

2.75M $\Omega$  at .4V, 5.5M $\Omega$  at .8V, 11M $\Omega$  remainder of scales.

Accuracy:  $\pm 3\%$ .

#### AC Voltmeter

##### Ranges:

0-4, 8, 16, 40, 160, 400, 800V.

##### Input Impedance:

.75M $\Omega$  minimum.

##### Accuracy:

$\pm 3\%$ .

#### Ohmmeter

##### Ranges:

0-1K, 10K, 100K, 1M, 10M, 100M $\Omega$  with 10 center.

##### Voltage:

1.06V on 100M $\Omega$ , 1.47V on 10M, 1.5V remainder of scales.

##### Accuracy:

Unspecified.

##### Size (HWD):

6 $\frac{1}{2}$ "  $\times$  5 $\frac{1}{2}$ "  $\times$  3 $\frac{1}{2}$ "

##### Weight:

2 $\frac{1}{2}$  pounds.

##### Power requirements:

One size D cell, two size AA cells, one 9-Volt #216 cell.

##### Price:

\$78.

DC or AC-ohms measurements, yet it is only 7/16" diameter.

The basic circuit is shown in Fig. 3. Rx is a lump representation of the multiplier resistors, all of which are 1% tolerance units. The input is fed to the gate of TR1, the FET. The drain of the FET is connected to the base of TR2, which in turn has its output connected to the source of TR1. The result is a stabilized circuit, relatively insensitive to changes in supply voltage and ambient temperature. The circuit arrangement also tends to raise the input impedance of the FET, which is already quite high.

The meter is actually reading two voltages; that produced by the source current of TR1, and also the collector-emitter voltage on TR2. R43 and R41 are hand-picked resistors, chosen to match the FET parameters so that the TR2 emitter-collector voltage is 1.5 volts under zero input conditions. B3 is inserted to buck out this voltage, so the meter reads zero.

Putting the Model 600 Type 1 through its paces in the lab, we quickly found that the meter leaves little to be desired. Inserting the batteries was a snap, and this is often not true of modern battery-operated equipment. There's one large thumbscrew in the rear which, when removed, gives access to the battery compartments. The instrument uses one size D cell, 2 penlight

cells, and one 9-volt #216 cell. These are all common-type cells, usually for sale at your front counter. We purposely left the meter on overnight with a mid-scale reading, to see how quickly the batteries ran down. After 18 hours, the needle had not perceptibly moved. Characteristics of the transistors indicate that the battery consumption under normal usage should be little more than shelf-life.

We ran some frequency response checks in the lab since the manual gave only a response range (15Hz to 2 MHz) rather than an accuracy figure. The meter proved acceptable for audio work. From 20 Hz to 20 kHz there was a gradual rise in readings, about  $\pm 1$  dB with 1.5 kHz reference. Above 20 kHz the meter seemed to flatten out, and climbed only about 1/10 dB in the next 500 kHz. (We did not measure above 500 kHz.)

DC measurements were simple. All the ranges were useful, but we would trade the .8V range for an 800V range. Many TV sets have voltages between 400 and 600 volts, and these voltages appear a bit cramped on the top scale.

The ohmmeter is setup on the most popular linearity configuration, with a 10 center. On the lowest range it is possible to read .2 ohm; the highest reading is 100 Megohms. In an interesting though not new variation, zero ohms is on the left end of the scale, the same as zero volts. Whether this is easier to use depends on the operator's preference, but we like it.

Also included in the Model 600 is a zero-center scale which is actually readable. Many of the meters presently on the market omit this scale; others include it as an after thought so that it's not really convenient to use. The usefulness of a center-zero scale becomes apparent when you attempt to align a discriminator stage.

The internal construction of the Model 600 Type 1 shows careful engineering and assembly. The circuit board is epoxy-fiberglass, a very rugged material. All components are laid out in neat rows, and each is mounted so the value may be easily read. The instrument should be very easy to service, should it become necessary. ▲

 CAPACITOR XC1-8	 CAPACITOR XC1-18	 CAPACITOR XC1-19	 CAPACITOR XC1-19.2
 CAPACITOR XC1-21	 CAPACITOR XC2-1.1	 CAPACITOR XC2-26	 CAPACITOR XC2-36.1
 CAPACITOR XC3-45	 CAPACITOR XC4-4.2	 CAPACITOR XC4-5.1	 CAPACITOR XC4-6.1
 CAPACITOR XC4-9.1	 CAPACITOR XC4-10.2	 CAPACITOR XC4-55.1	 CAPACITOR XC4-63.1
 CAPACITOR XC4-68.1	 CAPACITOR XC4-68.2	 CAPACITOR XC4-70.1	 CAPACITOR XC4-80

# 20 ways to break the exact replacement capacitor habit:

## Stock only 20 General Electric Service-Designed replacement capacitors and meet over 70% of your replacement needs.

Use General Electric extended-range replacement capacitors. Just 20 General Electric Service-Designed replacement units will meet over 70% of all TV can style needs!

"Extended-range" means that fewer General Electric types are needed to meet your requirements. Every GE aluminum capacitor meets not just one, but a range of capacitance and voltage requirements. And, to make selection easier, the application range of every General Electric capacitor is shown clearly on the unit, and on the carton.

You can quickly see, for example, that the GE capacitor rated 50-60 mfd up to 450 VDC will replace any unit between

50 and 60 mfd at any voltage up to 450 VDC. You save time and money in making replacements because General Electric capacitors are Service-Designed with you in mind!

Your local GE electronics distributor carries a complete line of replacement capacitors from General Electric, a leader in supplying capacitors to the radio and television industry. Call him today for full details.


430-31

# GENERAL ELECTRIC



Call your GE distributor now for a special offer on replacement capacitors for COLOR TV!

It's a Treasure Chest loaded with 12 of the most popular General Electric replacement capacitors for COLOR TV! Your distributor's offering it at a special low, low price. And to make it more appealing, you get an Xcelite® nut driver set with each Treasure Chest. Don't delay, call today! Offer is limited.

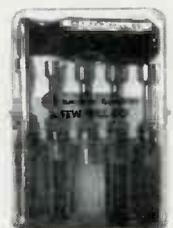

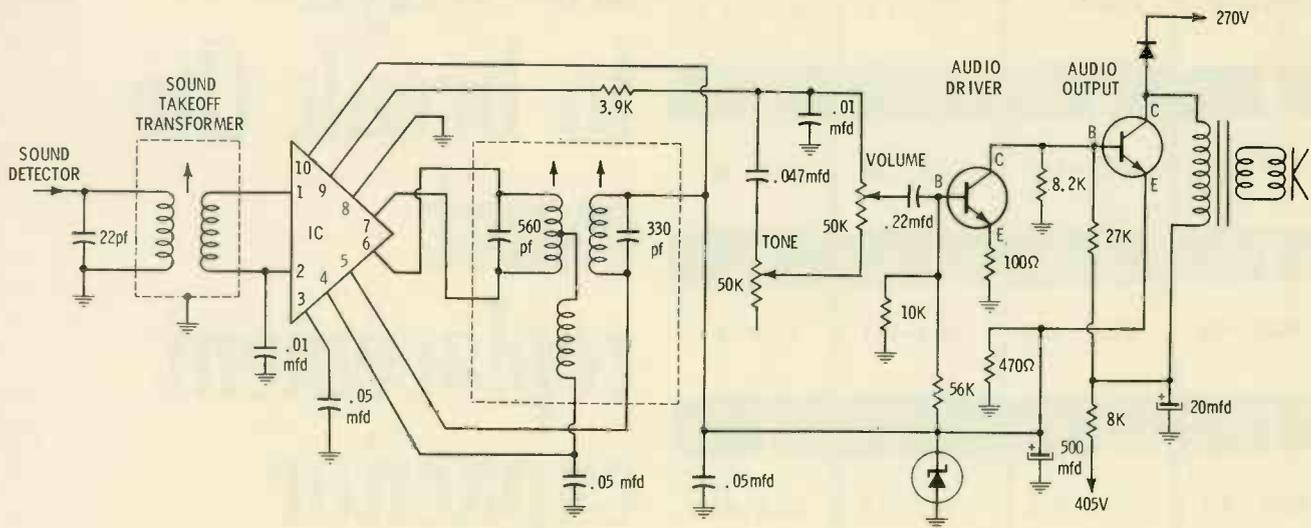


Fig. 20. Catalina's solid-state sound system utilizes IC in IF amplifier and detector stages.

**Tuning and Indicator Circuits**

Automatic frequency control of the VHF and UHF tuners employed in Admiral's 23" color models (Chassis 4H12) is accomplished by the new AFC circuit shown in Fig. 22. This system samples the video IF carrier (45.75 MHz) and develops a correction voltage that corresponds to any deviations from this frequency.

The video IF carrier is amplified by Q1, the AFC transistor, and is then coupled to the discriminator circuit via two paths. One route is through loosely coupled coils L1 and L2. The other path is from the

top of L1 through C1 and C2 to diodes X1 and X2. With the receiver correctly tuned (video IF carrier exactly 45.75 MHz), both discriminator diodes will conduct equally and, since their load resistors are connected so that their outputs add algebraically, no AFC correction voltage will be developed.

When the fine tuning is not properly adjusted, or if the local oscillator in the tuner drifts, the phase of the signal across L2 will shift, causing diodes X1 and X2 to conduct unequally, developing a correction voltage across their outputs. If the video IF carrier shifts down-

ward, diode X2 will conduct more and a negative correction voltage will be developed. An upward shift in the frequency of the video IF carrier causes diode X1 to conduct more, producing a positive correction voltage.

The correction voltage is applied to both tuners, as shown in Fig. 23. Although an NPN transistor is used in the AFC circuit of the VHF tuner, it is connected so that its base-to-collector junction functions as a diode. Changes in the AFC correction voltage produce corresponding changes in the capacitance of the base-to-collector junction. Since the

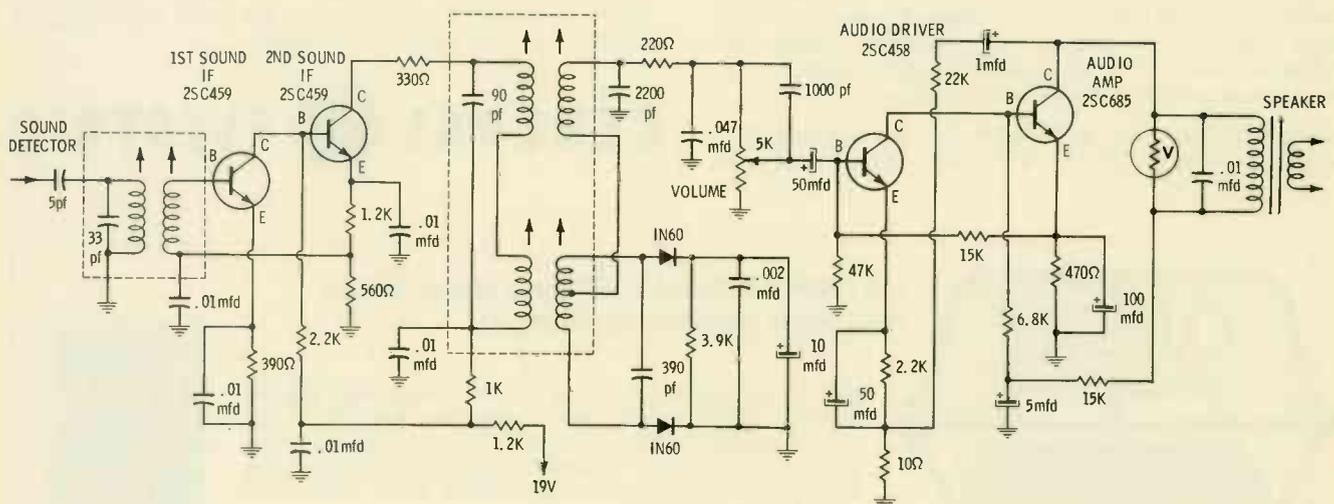


Fig. 21. Sound circuitry of Delmonico/Nivico's 18" chassis is also solid-state.





has  
everything  
in

# chemicals

From service cements to aerosol cleaners, from solvents to lubricants, only GC satisfies the critical chemical needs of the electronics field.

All GC chemicals are formulated to meet rigid requirements; packaged for convenience; and "proven in use" to make electronic jobs easier, faster, more profitable.

Remember too, with GC aerosols you get double value . . . highest product quality plus valuable GC "BONUS COUPONS".

Get more for your money . . . always insist on GC!


Write for your Giant FREE GC Catalog today . . . over 12,000 items including TV Hardware, Phono Drives, Chemicals, Alignment Tools, Audio, Hi-Fi, Stereo & Tape Recorder Accessories, Nuts & Bolts, Plugs & Jacks, Service Aids, and Resistive Devices.

*only GC gives you  
everything in electronics.  
..... for almost 40 years!*


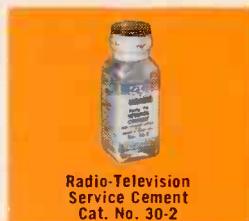
## GC ELECTRONICS COMPANY

400 South Wyman Street  
Rockford, Illinois 61101  
A DIVISION OF HYDROMETALS, INC.



Radio-Television  
Service Cement  
Cat. No. 30-2



SPRA-KLEEN  
Contact-Control Cleaner  
Cat. No. 8666



SPRA-LUBE  
Cleaner-Lubricant  
Cat. No. 8888




GC "JIF"  
Contact and Control  
Cleaner  
Cat. No. 8670



"Super Grip"  
Epoxy Glue  
Cat. No. 347



Super Freeze Mist  
Cat. No. 8668

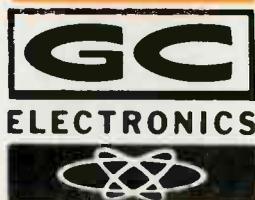

IF carrier signal and a pulse from the horizontal output system before the indicator light is illuminated. X1 rectifies the video IF carrier signal and forward biases Q1 into conduction. Q1, in turn, forward biases Q2, which conducts only when a horizontal sync pulse is applied to its collector circuit. The necessity of this "keying" action results from the fact that the video IF carrier level fluctuates with the modulated signal impressed on it and is at a constant level only during the horizontal sync pulse time. Thus, the use of a keyed circuit prevents the indicator light intensity from fluctuating because of modulation-produced video IF carrier level changes. R1, the indicator sensitivity control, is properly adjusted when maximum carrier level does not saturate Q2 and, therefore, the intensity of the indicator light.

Some Emerson models are equipped with an automatic fine tuning (AFT) circuit. This particular AFT system is designed around the now familiar discriminator circuit. Operation of the system is nearly identical to the previously described AFC system. Other manufacturers using the basic discrimination-type tuner AFC systems are Sylvania and Zenith.


Twelve General Electric models continue to use the "Meter-Guide" tuning system introduced in last year's color models. This system detects the video IF carrier, amplifies it with a transistor amplifier and feeds it to a meter.

Seven models in Hoffman's new line are equipped with the transistorized color indicator circuit (Colorcaster) that has been used in this manufacturer's color models for the past two years. During color reception, the gated DC transistor amplifier of this system is triggered by the bandpass amplifier and fires three neon bulbs that illuminate the color controls.

Motorola also employs a fine tuning indicator (FTI) in their all-transistor color chassis. A voltage doubler (X1 and X2 in Fig. 25) detects the 45.75-MHz video IF carrier, converting it to a positive DC voltage that forward biases a two-stage DC amplifier. A feedback path via R1 saturates both DC am-

Circle 24 on literature card
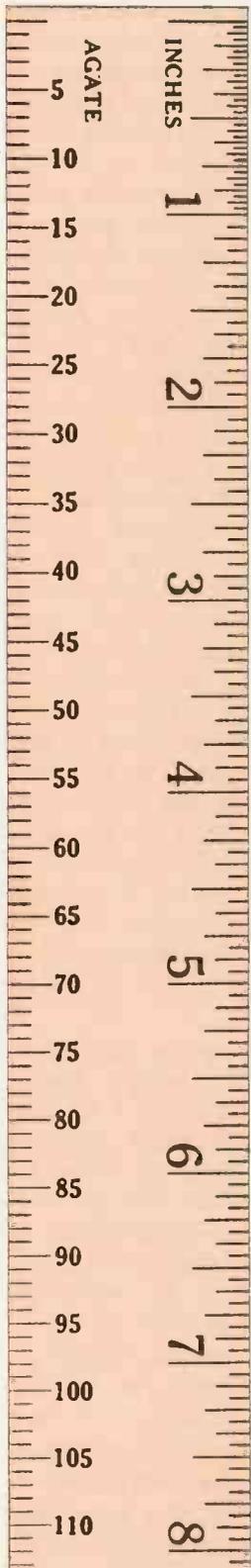
# NOW...a full-sized **VOM** in a palm sized "package"



160 Volt-Ohm-Milliammeter  
Complete with alligator clip  
leads and operator's manual.

..... \$50.00



Carrying Case—  
Cat. No. 2225..... \$ 9.50

Accessory Leads—  
Probe Tip Lead—  
Cat. No. 2055..... \$ 2.75

## Simpson 160 Handi-VOM®

Simpson Handi-VOM gives you the ranges, the time-saving conveniences and the sensitivity of a full-sized volt-ohm-milliammeter—yet it's only 3-5/16" wide, weighs a mere 12 ounces. Recessed range-selector switch never gets in the way . . . polarity-reversing switch saves fuss and fumble. Self-shielded taut band movement assures high repeatability and freedom from external magnetic fields. Diode overload protection prevents burn-out—permits safe operation by inexperienced employees and students. The demand is BIG, so get your order in to your electronic distributor, TODAY!

### RANGES

ACCURACY:  $\pm 3\%$  FS DC,  $\pm 4\%$  FS AC  
DC VOLTS: 0-0.25, 1.0, 2.5, 10, 50, 250, 500, 1000 @ 20,000  $\Omega/v$   
AC VOLTS: 0-2.5, 10, 50, 250, 500, 1000 @ 5000  $\Omega/v$   
DC MICROAMPERES: 0-50  
DC MILLIAMPERES: 0-1, 10, 100, 500  
DB: -20 to +10, -8 to +22, +6 to +36, +20 to +50  
"0" REFERENCE: 1 MW into 600 $\Omega$   
RESISTANCE: Rx1, Rx10, Rx100, Rx1000, Rx10K (30  $\Omega$  center)



DIVISION



**SIMPSON ELECTRIC COMPANY**

5200 W. Kinzie Street, Chicago, Illinois 60644 • Phone: (312) 379-1121  
Export Dept: 400 W. Madison Street, Chicago, Illinois 60606, Cable, Simelco

JN INDIA: Ruttonsha-Simpson Private Ltd., International House, Bombay-Agra Road, Vikhroli, Bombay

Representatives in Principal Cities  
... See Telephone Yellow Pages

WORLD'S LARGEST MANUFACTURER OF ELECTRONIC TEST EQUIPMENT

Circle 25 on literature card

December, 1967/PF REPORTER 47

plifiers which, in turn, triggers the output amplifier. Conduction of the output transistor completes the ground path for a panel light operated from a 55-volt DC source. When the receiver is properly tuned, all three DC amplifiers are saturated and the panel light remains on.

RCA has introduced a new integrated circuit (IC) automatic fine tuning (AFT) system in their top-of-the-line CTC30 color chassis. The new circuit, shown in Fig. 26, employs a single IC that performs

the functions of IF amplification, detection, and differential DC amplification. Operation of the circuit is similar to the transistor AFT system introduced in the CTC21 chassis in June '66. A portion of the video IF carrier is amplified and fed to a discriminator circuit. The discriminator output is delivered to a differential amplifier that produces two voltages, the difference of which is the correction voltage. When the video IF carrier is exactly on frequency (45.75 MHz),

there will be no difference in the two voltages and no correction voltage is developed. However, when the video carrier deviates from 45.75 MHz, one output will increase or decrease in relation to the other, depending on the direction of carrier deviation. A maximum differential voltage of  $\pm 9$  volts is possible with this system, providing nearly twice the pull-in range of the transistor system. A customer AFT defeat switch is located on the receiver front control panel, in addition to the normal defeat provided during channel switching and manual fine tuning (depressing the spring-loaded VHF fine tuning switch defeats the AFT). Some RCA models continue to use the transistor AFC system introduced in the '67 color model line.

The most unique tuning indicator introduced for the coming year is Westinghouse's "on-screen tuning bar" that uses the CRT itself as the visual indicator. Depressing a button labeled "tuning bar", located on the front control panel, produces two black vertical lines on the screen. One is a stationary reference line down the center of the screen and the other is displaced from it to indicate that the receiver is mis-tuned. Rotating the fine tuning control causes the two lines to converge when the set is properly tuned. A functional block diagram of the transistorized circuitry employed in this system is shown in Fig. 27.

The reference bar on the CRT is generated by the marker multivibrator which produces a 25-volt negative pulse of short duration each time it is keyed by the comparing multivibrator. The purpose of the comparing multivibrator is to delay the horizontal sync pulse exactly one-half of the horizontal scan interval to produce the reference bar and a variable amount to produce the indicating bar. It consists of two transistors in a free-running multivibrator circuit which is synchronized by the horizontal sync pulses. When it is generating the delay for the reference pulse, its output is symmetrical, that is, the two half-cycles are of equal duration. The end of the first half-cycle is used to key the marker multi-

## THE BEST PERFORMING UHF CONVERTER TODAY!



**RMS SOLID-STATE ALL TRANSISTOR UHF CONVERTER HAS BUILT-IN AMPLIFIER... INCREASES GAIN AN ADDITIONAL 10 db!**


Updates any VHF TV set to receive any of the 83 UHF/VHF Channels. Low noise, drift-free UHF performance. Amplifier increases gain an additional 10 db gain to bring in reception where all other converters fail! Simple hook-up for profitable installation. Easy operation. Attractive Charcoal Gray cabinet.

Model CR-550A with Amplifier..... List price \$49.95  
Model CR-500 without amplifier..... List price \$39.95
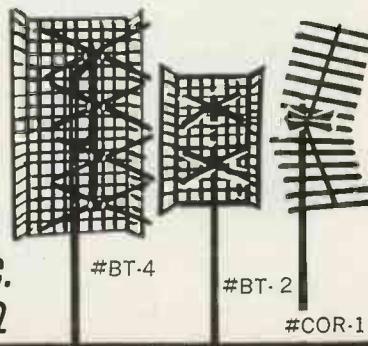
### UHF ANTENNAS

Make your next installation profitable with these dependable RMS Antennas. Write for FREE Informative Catalog! . . . Dept. PFC.

**RMS ELECTRONICS, INC.**  
50 Antin Place, Bronx, N. Y., 10462



Circle 26 on literature card

# Customers wear out the Yellow Pages getting to New Haven Appliance



**"We average ten to fifteen calls a day and the majority are from Yellow Pages,"** says Edward P. Jesanis, president, New Haven Appliance Servicenter, Hamden, Connecticut. "We get an awful lot of college people that move into town, and Yellow Pages is about the only place they could find us. On the other hand, if old customers have lost that slip with our name on it, then Yellow Pages is the next best place to look. We also get calls from manufacturers in the area—their purchasing agents find us in the Yellow Pages. It's also a good back-up to other advertising we might run. People who see the newspaper ad still can go to Yellow Pages for our number when something breaks down. We've come to the conclusion that Yellow Pages is our best bet to reach the greatest number of people, and to keep our name in front of them at all times."

Advertise for action...



**NEW HAVEN APPLIANCE**  
*Servicenter*

**FACTORY AUTHORIZED SERVICE ON MOST BRANDS**  
38 CONNOLLY PKWY., HAMDEN . . . . . 288-6229  
(Across from Hamden High School - Next to A & P)  
240 GEORGE ST., NEW HAVEN . . . . . 865-4116

ARVIM	GENERAL ELECTRIC	REGINA
AMERICAN BEAUTY	HAMILTON BEACH	REXINGTON
BERNS	HANDYMA	ROBESON-ROCHESTER
BISSELL	HOOVER	ROWSON
BLACK JAGUIS	IONA	ROYAL
BLUCK & DECKER	JETSpray	SCHLICK
B.V.I.	JOHNSON	SILEX
CASCO	KRAPP-HOHMICH	SHEFLAND
CHRYSLER	LEWITT	SHILL
CORY	MARLING-BORHAM	SPIERTZ SUN LAMPS
DAKES	MCGRAW-EDISON	SUNBEAM
DANLON	MECHANOMATIC	TENSOR
DORMEYER	MOTOROLA	THOR
ELECTROLUX	NORELCO	TOASTMASTER
EUREKA	OSTER	TRILOCATOR
FARBER	P.I.T.	ULICO
FASCO	PRESTO	UNIVERSAL
FRESH-DOMATIC	PROCTOR	WARING
GENERAL FLOORCRAFT	RAM	WEST BEND
	WESTINGHOUSE	

**REPAIRING**

AUTO RADIOS	ELECTRIC POWER MOTORS	MIXERS
BLANKET'S	FANS	PORTABLE TV'S
BLENDERS	FLOOR POLISHERS	POWER DRILLS
BROILERS	HAIR DRYERS	& SAWS
CLOTH REPAIRS	HEATERS	POLISHERS
COFFEE MAKERS	LAMPS	TAPE
DEEP FRYERS	THINGS (Steam Spray-Dry)	RECORDER'S
TOASTERS	VACUUM CLEANERS Etc.	

**TOASTMASTER**


MON. to FRI. 8:30 A.M. - 5:30 P.M. • SAT. 9 A.M. to 1:30 P.M.

Today's customers wear out the Yellow Pages instead of themselves. This ad\*, under ELECTRIC APPLIANCES—SMALL—REPAIRING, leads them to New Haven Appliance. Call your Yellow Pages man to plan your program. Find him in the Yellow Pages under ADVERTISING—DIRECTORY & GUIDE. \*shown reduced

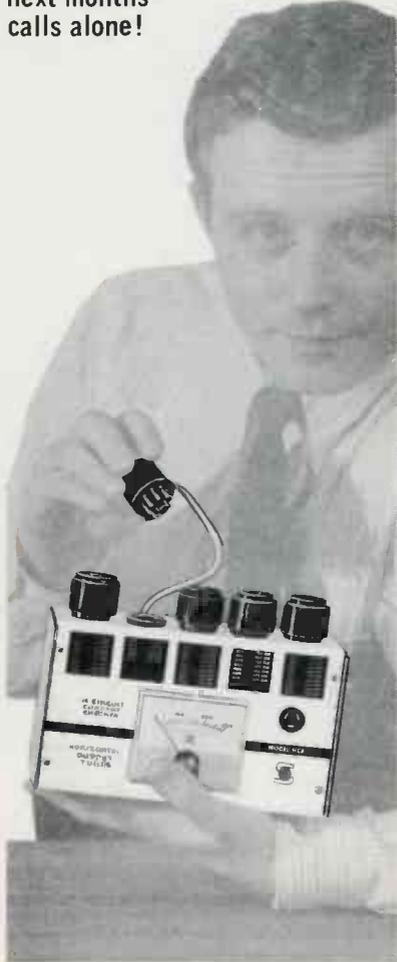**NEW!** from **SECO**

**"IN-CIRCUIT"  
CURRENT CHECKER**

Eliminates most common cause of "callbacks" (unstable focus, shrinking pictures, etc.)! Should pay for itself on next months' calls alone!



Nothing else like the HC-8 available! Tune horizontal drive and linearity for "dip"—and in seconds—you've got best possible focus, width and stability at minimum cathode current. Makes convergence adjustments faster, easier—longer lasting!

Especially useful on color TV where a slight misadjustment of horizontal linearity or efficiency coils drives cathode currents sky high! 5 pre-wired sockets for all popular horizontal output tubes lets you plug into circuit fast—no clipping or unsoldering of leads!

**\$34<sup>50</sup>**  
Net

**ASK YOUR DISTRIBUTOR**  
or write for full details.

**SECO**  
**ELECTRONICS CORP.**

1001 Second St. So. • Hopkins, Minn. 55343  
Circle 28 on literature card

50 PF REPORTER/December, 1967

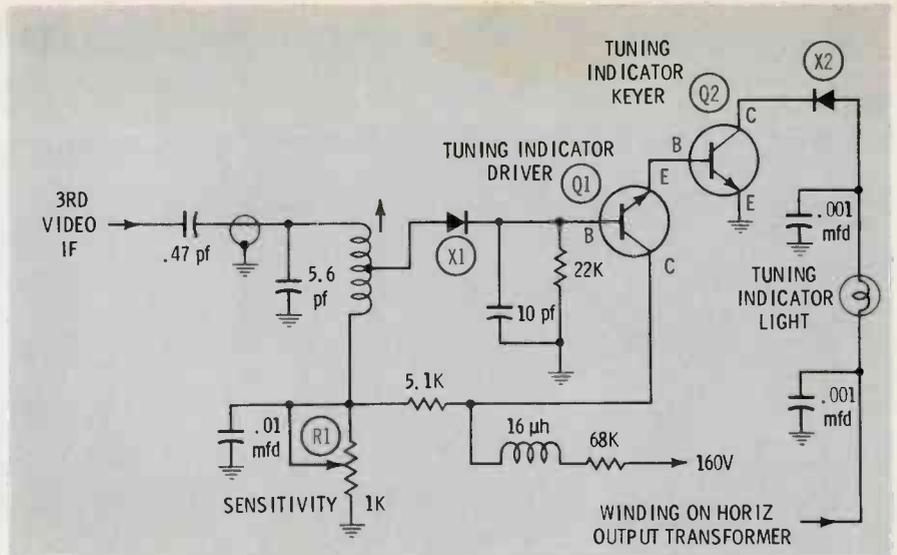


Fig. 24. Coronado's lamp-type fine tuning indicator circuit.

vibrator, and so the video pulse appears on the CRT at the center of the horizontal scan. A bias adjustment, labeled "pulse position adjustment", is used to center the reference bar.

Two other signals are applied alternately to the comparing multivibrator. During one vertical scan of the CRT, bias voltage from the "reference voltage adjust" potentiometer is fed through the gate circuit and operates in conjunction with the "pulse position" adjustment to control the delay of the comparing multivibrator, and the position of the reference bar. During the next vertical scan, the output of the peak detector (error signal) is applied to the comparing multivibrator through the gate circuit in lieu of the voltage from the "reference voltage adjust" potentiometer. If the receive-

er is correctly tuned, the voltage to the comparing multivibrator remains the same and the reference bar and the indicator bar are superimposed on each other.

The vertical gating multivibrator is a 2:1 counter synchronized by the vertical sync pulses. Thus, the gate circuit applies the reference signal and error signal to the comparing multivibrator on alternate vertical scans.

The error signal is generated in the top four blocks of Fig. 27. The slope detector is essentially a discriminator which develops a DC voltage proportional to the difference between the actual IF frequency and the correct IF frequency of (45.75 MHz). This voltage is added to the horizontal sync pulses (of constant amplitude), passed through the buffer, amplified by

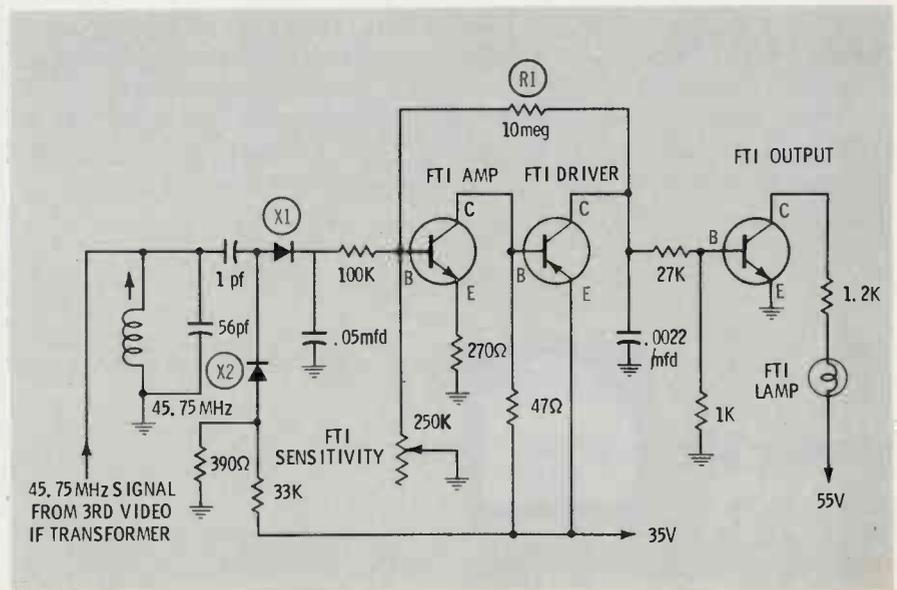


Fig. 25. Fine tuning indicator circuit employed in Motorola chassis.

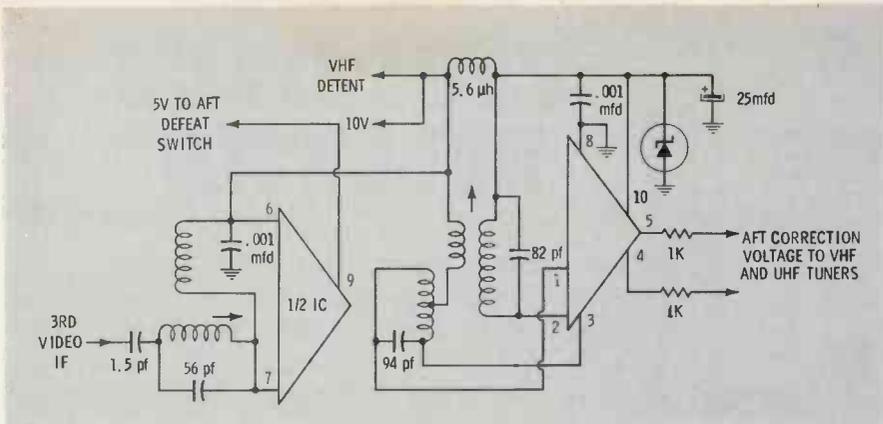


Fig. 26. Integrated circuit is used in RCA's new automatic fine tuning (AFT) system.

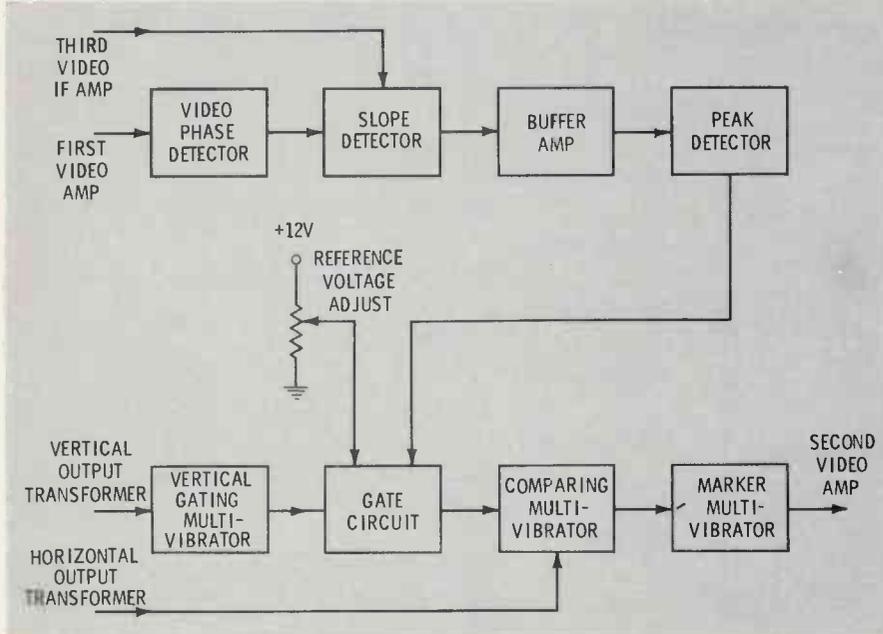


Fig. 27. Block diagram of Westinghouse's "on-screen tuning bar" system.

the peak detector and, finally, integrated to a DC level in the output of the peak detector.

Philco and Setchell Carlson are also on the list of manufacturer's who employ fine tuning indicator systems in their '68 color chassis.

Philco is using the eye-type system they introduced in their '67 models, while Setchell Carlson employs a lamp-type indicator. Olympic has included the familiar "Colorglide" color indicator circuit in their new chassis. ▲



"He's my best customer. When he says the picture is lousy, it's lousy!"

# BUY



**GE**  
**ALL WEATHER**  
 VINYL PLASTIC  
**ELECTRICAL**  
**TAPE**


the first  
 all weather tape  
 at standard  
 tape prices

**NOW** at your  
 local  
**GE Distributor**

Insulating Materials Dept.  
**GENERAL ELECTRIC**  
 846-02

# 4 ways to increase your income

RCA Institutes, Inc. offers these four comprehensive home study courses especially designed to help build your income immediately!

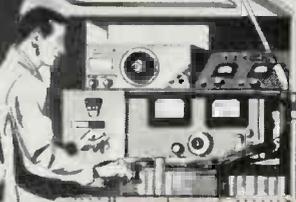 <p><b>COLOR TV</b> Add Color TV Servicing to your skills with this up-to-the-minute home training course and take advantage of the growing profit potential in this area! Train under the direction of RCA...experts in Color TV.</p>	 <p><b>TRANSISTORS</b> You get the necessary background for semiconductor technology including characteristics of tunnel diodes, rectifiers and other solid state devices. Transistor trainer also available.</p>
 <p><b>AUTOMATION ELECTRONICS</b> Trains you for the many applications of automation electronics in industry and government including Photoelectronics, Digital Computer Techniques, Synchros and Servomechanisms, Automatic Control Systems, and many more!</p>	 <p><b>MOBILE COMMUNICATIONS</b> Trains you to service and maintain 2-way radio communications on land, sea, and air! Gives you the technical foundation for space communications!</p>

Take advantage of RCA's Liberal Tuition Plan. You only pay for lessons you order; and have no long-term obligations. Licensed by New York State Education Department. Approved for Veterans.

## RCA INSTITUTES, INC.

A Service of Radio Corporation of America  
320 West 31st Street, New York, N.Y. 10001



The Most Trusted Name in Electronics

SEND THIS COUPON NOW FOR COMPLETE FREE INFORMATION

RCA INSTITUTES, INC. Home Study School, Dept. PF-D7

320 West 31st Street, New York, N.Y. 10001

Without obligation, rush me free information on the following RCA Home Training Course:  COLOR TV  TRANSISTORS  MOBILE COMMUNICATIONS

AUTOMATION ELECTRONICS

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

CANADIANS—Take advantage of these same RCA courses at no additional cost. No postage. No customs. No delay. Send coupon to: RCA Victor Company, Ltd., 5581 Royalmount Ave., Montreal 9, Quebec.

# PHOTOFACT™ BULLETIN

PHOTOFACT BULLETIN lists new PHOTOFACT coverage issued during the last month for new TV chassis. This is another way PF REPORTER bring you the very latest facts you need to keep fully informed between regular issues of PHOTOFACT Index Supplements issued in March, June, and September.

<b>Admiral</b>	Chassis H1055-1, 3H10NC57-1, 4H10NC57-2, 4H10NC57-3, 4H10NC97-1, 5H10NC64-1 .....	920-1
<b>Catalina</b>	122-745A, 122-747A .....	919-1
<b>Curtis Mathes</b>	Chassis CMC26/27/28/29 .....	921-1
<b>Magnavox</b>	Chassis T917-01-AA .....	922-1
<b>Olympic</b>	CT-910 .....	918-1
<b>Panasonic</b>	TR-210D .....	923-1
<b>Penncrest</b>	4621A-48, 4622A-46, 4623A-47 4631A-48, 4632A-46 .....	922-2
<b>Sears</b>	8103 (Ch. 562.10330) .....	918-2
	8167 (CH. 564.80030) .....	923-2
	Chassis 562.10370 .....	921-2
	Chassis 562.10410 .....	919-2
<b>Setchell-Carlson</b>	9CT84EA, 9CT84W (Ch. U804) .....	918-3
<b>Sylvania</b>	Chassis D06-1, D06-2 .....	922-3
<b>Westinghouse</b>	Chassis V-2655-1/-2/-3/-7/ -8/-9/-13/-14 .....	920-2
<b>Zenith</b>	Chassis 13X16, 13X16Z, 13Y16, 13Y16Z .....	920-3
<b>Production Change Bulletins</b>		
<b>Admiral</b>	Chassis H1-1A, H1-2A, 1G11, 2G11, 3G11 .....	922-4
<b>Electrohome</b>	Tasman .....	922-4
<b>Olympic</b>	Chassis NB, NBU .....	922-4
<b>Silvertone</b>	PC-2170, PC-2171, 2170, 2171 (Ch. 456/528.52452 thru 456/528.52459) .....	921-3
<b>Westinghouse</b>	Chassis V-2476-1/-2, V-2486-1/ -3/-6/-11/-12/-14, V-2515-19, V-2535-1 .....	921-3

# COLOR


## COUNTERMEASURES

SYMPTOMS AND TIPS FROM ACTUAL SHOP EXPERIENCE

**Chassis:** RCA CTC22

**Symptoms:** Intermittent horizontal and vertical sync; similar to AGC trouble. Brightness control acts like AGC control.

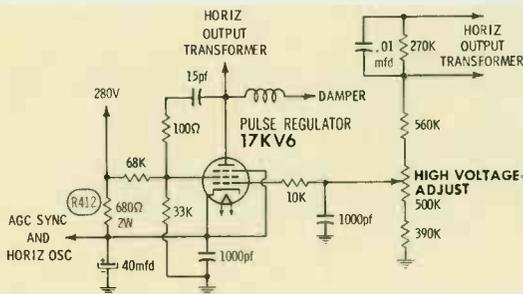
**Tip:** Trouble of this nature in several CTC22 chassis was caused by an open R412 (680 ohms, 2W) in the cathode of the pulse regulator stage. R412, in addition to serving as the cathode resistor, doubles as a B+ dropping resistor. Several other circuits—including sync and AGC—receive their operating voltage via R412.



**Chassis:** RCA CTC15

**Symptoms:** Insufficient width; picture tends to defocus during station breaks or camera changes.

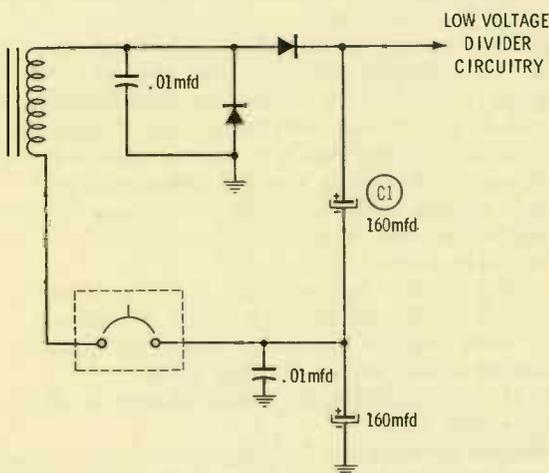**Tip:** Loss of width will be marginal—raster fills screen to within 1/4" to 1/2" on left side. Replacement of horizontal oscillator, horizontal output, and damper does not help condition. Possible trouble is defective C1 in the B+ voltage doubler circuit. Aging of C1 decreases efficiency, although B+ voltage may read within tolerance.




# LEADER

TEST INSTRUMENTS

*Much in little*

*New!*

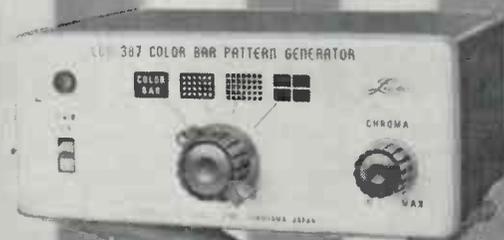

**\$13450**

LCG-387

## COLOR BAR PATTERN GENERATOR

Here it is—LEADER's new color bar pattern generator which includes the keyed rainbow, SQUARE crosshatch, dots, AND the single cross bar. In fact, this cross pattern will speed up adjustments on raster centering, purity at the center and dynamic convergence. Sharp and clear lines, both vertical and horizontal, produced by return trace blanking. Two switchable channels, 5 and 6, with 10mV output. Solid state, of course, with voltage regulated supply. Compact and sturdy construction for field use—supplied with carrying bag for convenience. Size only 2 3/4 H x 6 3/4 W x 4 3/4 D in., and weight 3.3 lbs approx.

**LEADER ELECTRONICS CORP.**

NEW YORK OFFICE

101-103 ROME ST., FARMINGDALE, L.I., N.Y. 11735

TEL (516) 694-1534 541-5373

Circle 30 on literature card



## “My shop’s been loaded... since I got my FCC License.”

“And I could kick myself for not getting it sooner. I’m pulling in all kinds of mobile, marine and CB business that I couldn’t touch before; have even had some calls to work on closed-circuit television. I’ve hired two new men to help out and even with them, I’m two weeks behind.”

And so it goes. Once you have that FCC ticket, you open the door to all kinds of new business. And that’s not all. The knowledge you need to pass the FCC exam gives you a fundamental understanding of *all* electronics. You’ll find you can do more work in less time...work on almost *any* kind of electronics gear.

What’s the best way to get a Commercial FCC License...and still keep up with your work? Thousands of men will tell you “Cleveland Institute of Electronics.” CIE has been preparing men for FCC License exams since 1934. What’s more, they back their Home Study Licensing Programs with this remarkable money-back offer:

**A CIE FCC License course will quickly prepare you for a Commercial FCC License. If you fail to pass the FCC examination...on the very first try...after completing your course, CIE will refund all your tuition. You get an FCC License...or your money back!**

And only CIE offers you new, up-to-the-minute lessons in all these subjects: Logical Troubleshooting, Laser Theory and Application, Micro-miniaturization, Single Sideband Technique, Pulse Theory and Application, Boolean Algebra, and many more.

Send coupon today for CIE’s FREE informative book “HOW TO GET A COMMERCIAL FCC LICENSE.” Cleveland Institute of Electronics, Dept. PF-42, 1776 East 17th Street, Cleveland, Ohio 44114.

**ENROLL UNDER NEW G. I. BILL.** All CIE courses are available under the new G. I. Bill. If you served on active duty since January 31, 1955, OR are in service now, check box in coupon for G. I. Bill information.

**MAIL COUPON TODAY FOR FREE BOOK**

**CIE** Cleveland Institute of Electronics  
1776 East 17th Street, Cleveland, Ohio 44114

Please send FREE book, “How To Get A Commercial FCC License.”

Name \_\_\_\_\_ (please print)


Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Occupation \_\_\_\_\_ Age \_\_\_\_\_

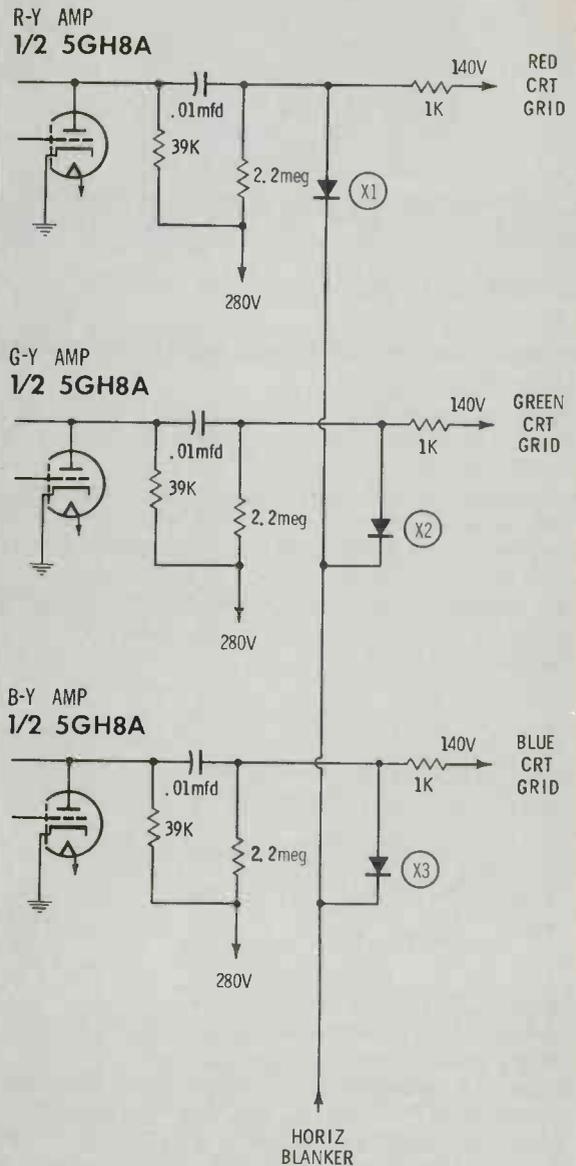**Check here for G.I. Bill information**

Accredited Member National Home Study Council  
A Leader in Electronics Training... Since 1934 PF-42



**Chassis:** RCA CTC22

**Symptoms:** Screen temperature slowly shifts to some predominate hue after warmup; hue *may* or *may* not be fully saturated.

**Tip:** This chassis uses DC clamp diode circuits at picture tube control grids. X1, X2, and X3 reset red, green, and blue CRT grids to approximately 140 volts at end of each horizontal scan. Voltage on all three grids should read the same. A change in diode characteristics during warmup unbalances grid voltages, causing either red, green, or blue gun to increase conduction. Defective diode is easily isolated using following method:

1. Select diode corresponding to predominate color on screen—X1 for red; X2, green; X3, blue.
2. With receiver operating, apply freeze-spray to selected diode while watching screen.
3. If diode is defective, instant change in shade of color will occur.

**Additional Information:** If fully saturated color appears, check corresponding diode for open or shorted condition—either defect will cause increased conduction of picture tube gun. ▲

# THE TROUBLE-SHOOTER

## Video and Audio Disappear

Please help with this tough dog. It's a Philco chassis 14N50 (Photofact folder 705-3).

When the contrast is turned down, both the video and audio disappear. The video output screen drops to 50 volts, and at the same time the plate of the AGC keying tube goes to 90 volts negative.

The plate and screen of the first IF tube are both 170 volts without signal; the screen drops to 150 volts with signal.

Bridging a 180-pf capacitor from plate to ground on V4 helps some, and shorting R74, the VDR, allows full range of contrast, but with slightly narrow and dim picture.

Please give me some helpful suggestions.

RICHARD K. SMITH  
Richmond, Michigan

Mr. Smith's letter is the kind we can sink our teeth into. He's done most of the work for us. In addition to the many symptoms and voltage readings, he also furnished a list of components he has tested. Let's analyze his tests in order:

First, the video tube. The contrast control affects conduction by varying the screen voltage. The screen voltage reading is not greatly significant since it varies both with contrast setting and



signal contact. The AGC grid signal is extracted from the video amp plate, so the contrast control is, in effect, an AGC control.

The reading of -90 volts on the AGC plate is an important clue. This indicates that the keying tube is not conducting properly. At this point, scoping the plate signal would reveal the error.

The high screen voltage on the first IF tube indicates the tube is operating near cutoff. Type 6EH7 is a semi-remote cutoff tube, and requires about -19 volts bias to cutoff. This is also significant, since it again indicates the AGC voltage must be greatly in error. (We are surprised that Mr. Smith did not include a grid reading here. He did indicate that both cathode and screen resistors are OK.)

Partial restoration of operation by bridging a 180-pf cap from plate to ground on V4 again indicates that the keying pulse is too strong; the bridge bypasses some of the excess signal. The final test, shorting the VDR again effectively is bypassing keying pulses, since it is loading the flyback through C50.

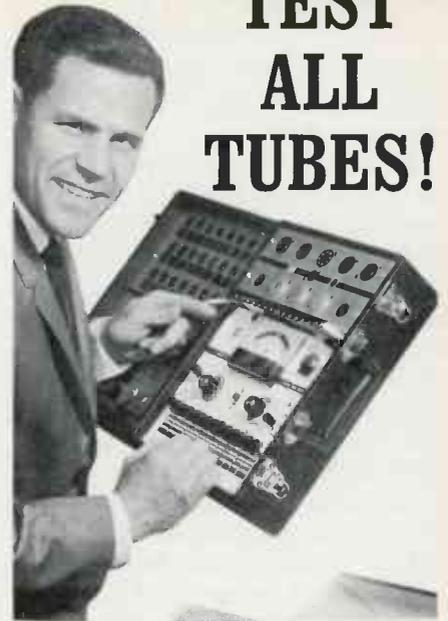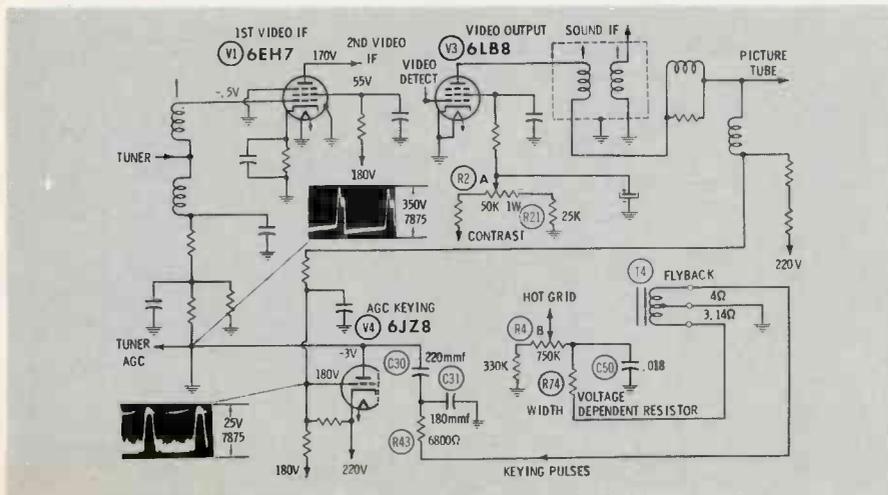Our conclusion then, is that the AGC keying pulses are much too strong. The likely suspect is an open C31, which is 1/2 of a capacitance voltage divider. If C30 increases in value, it would produce similar symptoms.



# TEST ALL TUBES!

## New Deluxe 107C Tester


Exclusive "eye" tube spots momentary shorts. Superior accuracy and stability from constant voltage transformer—no line adjust.

Now a portable tube tester unmatched in speed, sensitivity and reliability for all modern TV, radio, hi-fi, industrial and foreign tubes. Tests more than 1000 different tubes without setup, more than 3000 in total. Patented Grid Circuit Test; Dynamic Mutual Conductance and Cathode Emission Tests; many others.

**\$19850**  
NET

**MODEL 98.** For comprehensive analysis of all modern TV and radio tubes. Includes patented Grid Circuit, Cathode Emission, Tube Merit, Heater Current tests for more than 2500 types of receiving and picture tubes.

**\$10950**  
NET

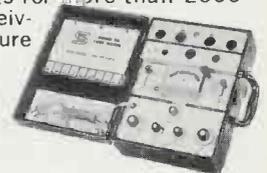

**MODEL 88.** Popular, low cost Grid Circuit and Tube Merit Tester. Complete coverage of all popular receiving tubes plus adaptor for more than 400 picture tubes. Includes speed indexed setup data.

**\$7450**  
NET



**ASK YOUR DISTRIBUTOR**  
or write for full details.

**SECO**  
**SECO ELECTRONICS CORP.**

1001 Second St. So. • Hopkins, Minn. 55343

Circle 32 on literature card

December, 1967 / PF REPORTER 55

## DC Voltage

(Continued from page 6)

voltage drop across the emitter resistor and increases the emitter voltage.

To make a control-action test of the transistor in Fig. 8, connect a voltmeter across the 10-k collector load resistor, and short-circuit the base to the emitter. With the base and emitter at the same potential, the collector current normally cuts off. Therefore the voltmeter reading drops practically to zero. A sensitive voltmeter will show a very slight deflection from zero because of the small saturation current. If the collector junction is leaky, the leakage current flows through the collector load resistor and appreciable voltage drop is indicated across the 10-k resistor.

### Common-Collector Circuits

The common-collector circuit (also called the emitter-follower circuit) is also found to some extent in electronic circuitry. Fig. 9 is typical. Note that the normal DC voltage values are the same as in the common-base circuits, because the DC circuit is the same in both instances. The distinction is that in the common-base circuit, the emitter is driven and the output is taken from the collector; in the common-collector circuit, the base is driven and the output is taken from the emitter. Note the collector-bypass capacitor in Fig. 9. This is not a part of the DC circuitry; its only effect is to keep the collector at AC ground potential when a signal is applied.

Since the DC circuitry is the same in both common-base and common-emitter circuits, the same DC distribution is found both in normal and abnormal operation. If there is collector-junction leakage in the transistor in Fig. 9, the base, emitter, and collector voltages increase. If we make a control-action test of the transistor by short-circuiting the base to the emitter, the voltage drop across the 10-k collector resistor normally goes to practically zero. On the other hand, if the collector junction is leaky, we will measure an appreciable voltage across the collector resistor when the base and emitter are connected together.

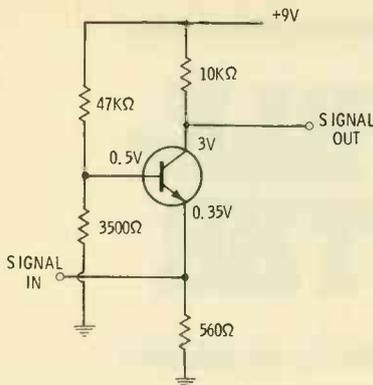


Fig. 8. Common-base circuit.

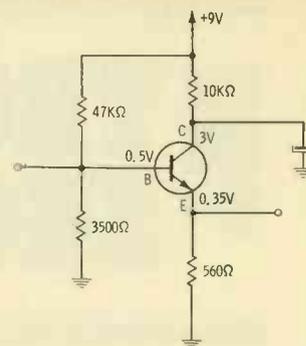


Fig. 9. Common-collector circuit.

### Bias Circuits

The most common DC bias circuits are shown in Fig. 10. These circuits are all comparable since transistor defects cause changes in the normal electrode voltages. A control-action test of the transistor can be made in the unstabilized bias circuit by short-circuiting the base to the emitter and observing the voltage drop across the collector load resistor. Normally, the voltage falls to practically zero in the test.

The series-stabilized bias circuit can be checked for transistor control action in the same manner. However, a short-circuit test cannot be made in the voltage-stabilized bias circuit, because the base and emitter resistors continue to draw current through the collector resistor when the base is short-circuited to the emitter. The stick bias circuit can be tested for transistor control action, however.

Please turn to page 61


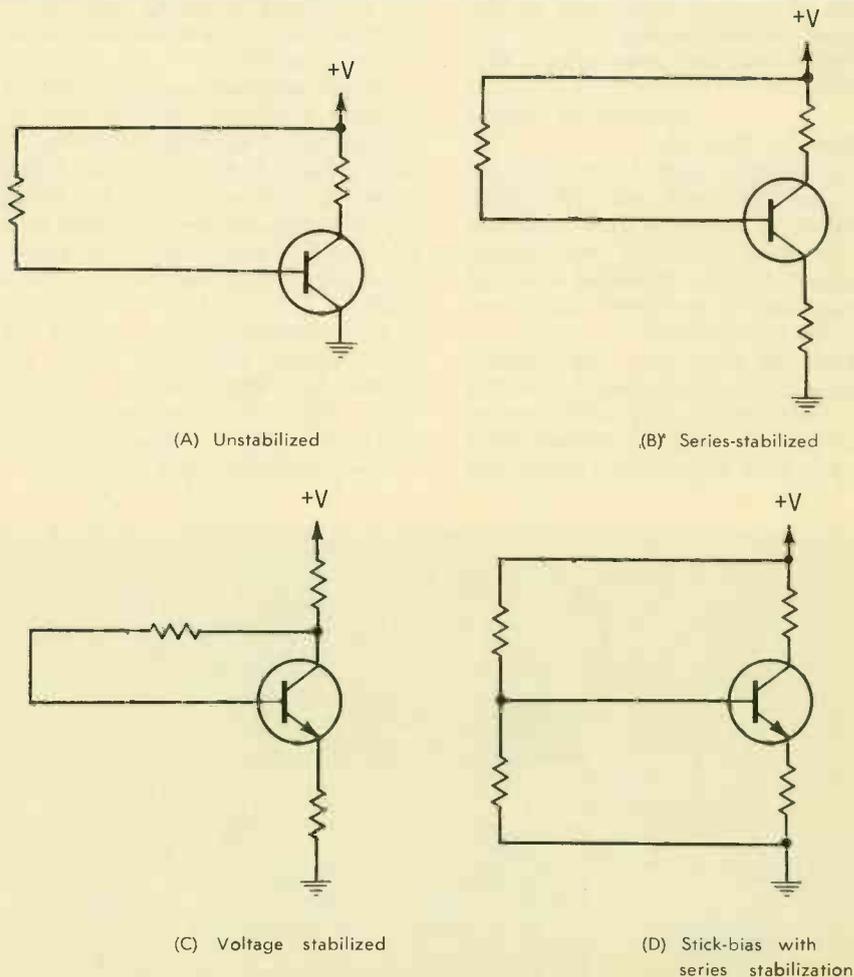


Fig. 10. Bias circuits.

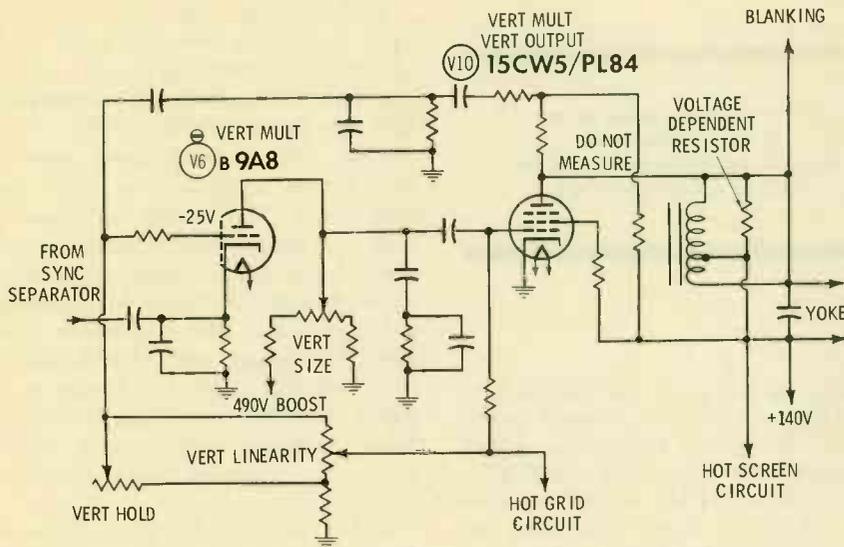

### Insufficient Height

I am having trouble with a Motorola TS-586/Y (PHOTO-FACT 688-3). When the set is first turned on it has insufficient height. By adjusting the linearity and height controls it has slight nonlinearity and bottom fold-over. I have replaced or checked the tubes, VDR, output transformer, yoke, resistors, capacitors, voltage and waveforms. Grid voltage on V6B is slightly high, and the V6B cathode waveform is slightly low.

IRVING RENZ

Missoula, Montana

*The problem can often be narrowed down by observation during warmup. If the height slowly comes up, the problem is often in the power supply. If the height never comes up, then the problem is usually in the vertical stages.*

*Measure the B+ at the 140-volt source at cold start, and again after the raster is full. If there is little or no change, the power supply is probably OK. The same measurement should be made at the boost source since this supplies the vertical multivibrator through the height control.*

*Also measure the heater voltage on V10 to make sure is not a "slow warm-up;" this trouble can often be traced to the heater series dropping resistor.*

*Other causes of slow warm-up in height could be specific capacitors and resistors in either of the vertical stages, but your letter indicates these have been checked.*

### Share Your Troubles

*Have you recently cured an unusual trouble symptom? If so, how about*

*sharing your experience with the other readers of PF REPORTER? Include the make, model and/or chassis number of the set; a detailed description of the symptom(s); your troubleshooting procedure; and the exact nature of the defect that caused the trouble. Material for submission can be either typed or handwritten. Mail to:*

The Troubleshooter  
PF REPORTER  
4300 W. 62nd St.  
Indianapolis, Indiana 46206

## tests all color tubes

the way tube manufacturers do!



ONE YEAR WARRANTY

## LECTROTECH CRT-100 picture tube analyzer

No other brand has all these features. Tests each color gun to a standard set of test conditions. With variable G-2 voltage, each grid is normalized to a reference cut-off voltage. Line voltage adjustment (to insure all tube voltages are correct regardless of line voltage). Tests all black and white and all color tubes for leakage, shorts and emissions. Rejuvenates and removes shorts on both color and black and white tubes for increased brightness. Continuously variable G-2 voltage for all tubes, present and future, including new 15 inch color tubes.

Made in U.S.A. Only **89<sup>50</sup>**




See your distributor or write PF-12  
**LECTROTECH, INC.**  
1221 W. Devon Ave., Chicago, Illinois 60626  
Circle 34 on literature card

# Speedy TUNER REPAIR

## FAST SERVICE

ONE YEAR WARRANTY

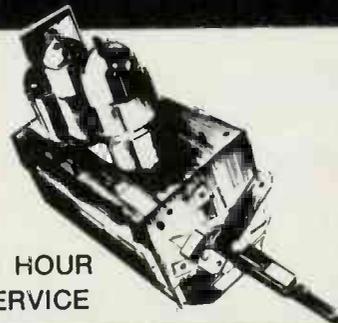

24 HOUR SERVICE

COLOR • UHF • VHF

**\$950** (\$14.50 COMBO) COMPLETE

Includes all parts (except Trans. & Tubes)

We are new in name only—Behind every tuner repair is 15 yrs. of experience. Our base price is compatible with other companies, but the extra service and high quality workmanship makes our service cheaper in the long run. Send the defective tuner with all parts, include tubes, make, model No. and complaint. Pack well and insure. All tuners returned C.O.D. unless accompanied by an open check. (Dist. write for price structure)



## SUPERIOR TUNER SERVICE

1377 N. CURRY PIKE

BOX 368


Bloomington, Indiana 47401

Circle 33 on literature card

December, 1967/PF REPORTER 57
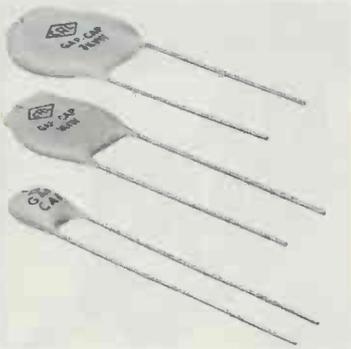
# PRODUCT REPORT

for further information on any of the following items, circle the associated number on the Catalog & Literature Card.



## New Capacitors (60)

The Centralab line of Gap-Cap spark gap capacitors is now available

through all Centralab distributors. The Gap-Cap is a low-cost, reliable safety device with many applications where transient overvoltage is a possibility.

Voltage appearing at the terminals of the Gap-Cap is prevented from exceeding a specified value, and any excess energy which could endanger sensitive components is harmlessly dissipated across the spark gap.

Units can be furnished with working voltages of 1 KV and 3 KV and arc start voltages of 1-2 KV, 2-3 KV and 4-6 KV. Available capacitances are .75 pf and .01 mf in the 1 KV unit and .004 mf in the 3 KV unit. Initial leakage resistance is 10,000 megohms minimum and dissipation factor is 2% maximum at 1 KC. Unit prices range from \$0.21 to \$0.66 net each.

## Multitester (61)

A fully illuminated dial, a probe light built into the test lead, and molded-in magnets on the rear cover are featured in **Components Specialties'** new Speco Model P-100-L Multitester. The magnetic cover permits the service technician to stick the unit on a TV chassis, refrigerator door, or other convenient iron-based metal surface, thus enabling the technician to use both hands for handling the test leads. The multitester provides DC ranges with 10,000 ohms/volt sensitivity and AC ranges with 5000 ohms/volt sensitivity. All functions, including current and resistance, are selected with a single switch.

Other features of the multitester include banana-type jacks, carrying strap, 1% precision resistors, printed-circuit board construction, and meter fuse protection. Price is \$21.95, including batteries, test leads, probe-light test lead, and instruction manual.

## Barrier Strip Terminal (62)

A new barrier strip terminal for use in music, sound, and low-voltage control systems has been announced by the **3M Company**. Called "Scotch-

## Swing-O-Lite ONE OF AMERICA'S LEADING SOURCES... THE RIGHT LIGHT AT THE RIGHT PRICE!

Who Says Top Quality Has to Cost More?

**INCANDESCENT**

**ALL-PURPOSE LAMP** Model BB-45

The basic work-tool of industry, proven in installations everywhere.

- Full 45" Arm Reach
- Completely Flexible, Yet "Freezes" in Any Position

**FLUORESCENT MAGNIFIER-LAMP** Model BBM-9

One of several popular types essential for inspection of work, schematics, blue-prints, miniature assemblies. Basic to production line and research laboratories.

- Full 45" arm reach
- 5" Diameter
- Magnifying Glass with Powerful 13" Focus

Colors: Grey, Desert Tan, Dark Brown.

**"ROBOT" FLUORESCENT LAMP** Model SF-2-15

Presto lighting where, when you need it. Automatic stops prevent slipping, wire twisting. Superb construction.

- Full 45" arm reach
- Low Power Usage with 2 Bulbs
- Adjustable Tension Control
- All Metal Construction — All Lamps Available with Optional Mounts.

Write for full descriptive literature to Dep't. P F - 127

We have lamps for every purpose, including hi-intensity.

**OPTIONAL EXTRA!**  
Exclusively Ours: Handy Electrical Outlet in Base  
All Lamps UL Approved

Swing-O-Lite 13, Moonachie Road INC. Hackensack, N.J. 07601



Circle 35 on literature card



flex" brand No. 515 Barrier Strip, the new connector comes with a foam adhesive backing. The vinyl foam backing is designed to provide greater gripping quality for installations on porous or sand-finished surfaces.

The new barrier strip works in

conjunction with this manufacturer's "Scotchflex" brand cable system No. 500, and also can be used independently as a terminal box for standard solid and stranded hookup wire. Four openings in the barrier strip's cover provide the necessary flexibility to handle various wiring arrangements. Connections are easily made to the four-post terminal either by using No. 571 Terminal Spades or by affixing connecting wires on the binding posts and tightening the screw. Terminal spades automatically grip the cable wire when screwed down to the terminal and no stripping of insulation is required. The barrier strips are individually priced at 93¢, or 74¢ each in lots of 10.

#### Solid-State Multimeter (63)

Full-scale sensitivities of the transistorized multimeter shown here are 500 mv to 5000 volts DC, 10 volts to 5000 volts AC, and 10 microamps to 1 amp DC. Resistance ranges cover  $R \times 1$  through  $R \times 10K$ . The design of the unit provides protection against damage to the transistorized circuits.

AUL Instrument's battery-operated Model TVOM 3 employs a taut band meter and measures  $3\frac{1}{16}$ " wide by  $2\frac{1}{16}$ " deep by  $5\frac{7}{8}$ " long. Price is \$44.00. An optional carrying case is available for \$4.50.

#### Color Test Unit (64)

Equipped with a 19" rectangular 90° bonded-shield color picture tube,



deflection yoke, convergence assembly, and blue lateral magnet assembly, the Sylvania Chek-a-Color unit allows service technicians to quickly check all 19", 21", 22", or 25" color TV receiver chassis without disturbing the neck components or picture tube.

**WORLD'S FINEST 5-CORE SOLDER**

**ERSIN MULTICORE**

**NEW EASY DISPENSER PAK ONLY 69¢**

BUY IT AT RADIO-TV PARTS STORES

Multicore Sales Corp. Westbury, N.Y. 11591

Circle 37 on literature card

for **PROFITABLE, TIME-SAVING SERVICING**

OF: Black & White TV Color TV

AM and FM, Tube or Transistor Home, Portable and Auto Radios

Communications equipment & Home Appliances

Hi-Fi Components

**B & K PROFESSIONAL TEST EQUIPMENT**


WITH SIGNAL INJECTION AND IN-AND-OUT OF CIRCUIT MEASURING TECHNIQUES

Send today for your free copy of Catalog AP22

**B&K**  
DIVISION OF DYNASCAN


DS-602  
1801 WEST BELLE PLAINE AVENUE, CHICAGO, ILL. 60613  
Telephone: (312) 327-7270 • Cable Address: BANDKCO

Circle 36 on literature card

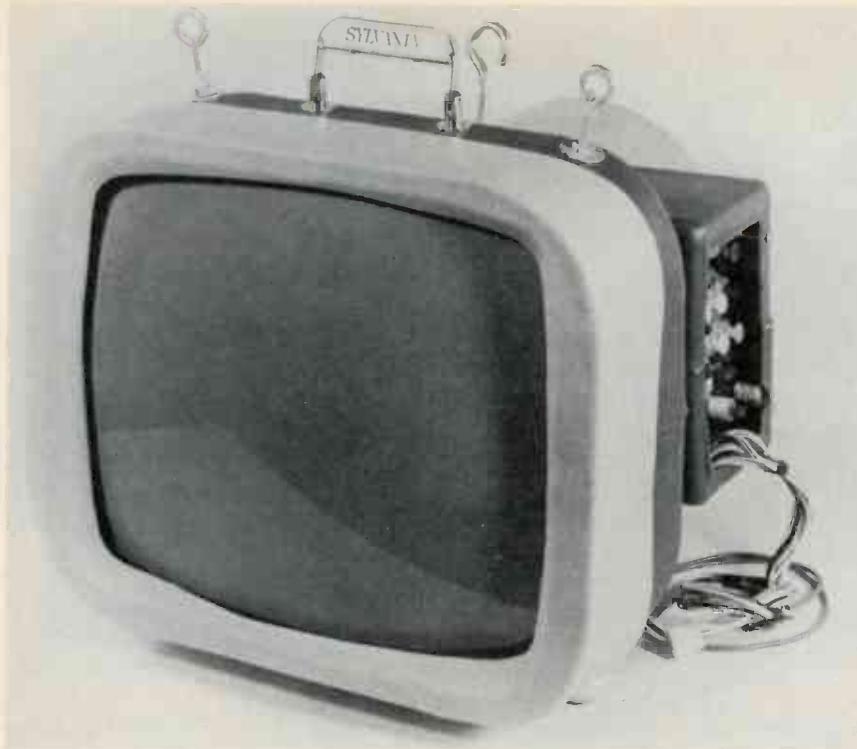

the problem is in the chassis/tuner group.

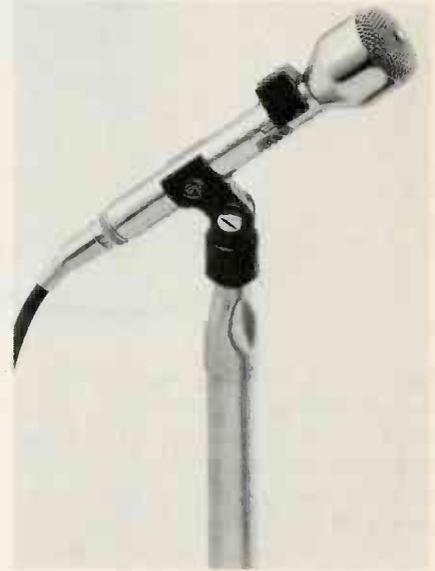In the repair shop, the unit can be used as a bench tool for trouble shooting and testing color chassis. The unit is contained in a high-impact plastic case and weighs less than 50 lb. Attachable feet and brackets permit use of Chek-a-Color as a standing or suspending bench unit. Price is \$225.00.



In addition to saving time and effort on service calls, Chek-a-Color provides conclusive support of the serviceman's recommendations for repair. For example, if the test unit delivers a good picture when con-

nected to the chassis of a malfunctioning set, it shows that the trouble lies within the picture tube or neck components. On the other hand, if the same problems appear on the Chek-a-Color screen, it shows that

### New Microphone

(65)

The new Electro-Voice "hand-and-stand" entertainer's microphone, model 631, evolved from design concepts developed for the E-V professional 635A omnidirectional, dynamic microphone. Sharing the same background, and designed and field-tested under actual use conditions by stage and recording artists, the 631 has features that performers demand; ruggedness, reliability, good looks, and ease of handling, plus additional features for live performance use.

One such feature is the E-V "Uni-seal" switch, a magnetically operated reed relay switch, sealed from dirt and corrosion. A magnet in the removeable actuator closes or opens the switch contacts when it is moved forward or back on the case; and, when the actuator is removed, the contacts remain in a fail-safe "on" position.

Inside the new microphone is a four-stage filter that traps dirt and magnetic particles before they can get to the element. This filter also provides blast and "pop" protection when performers work ultra-close. Frequency response is 100 to 13,000 Hz shaped for presence and control of feedback and rumble. The microphone's output is -55 dB. Available in satin chrome or matte satin nickel finish for \$60.00.

NEW FROM INJECTORALL



# HERE'S PROOF!

PROOF that "SUPER 100" tuner cleaner is BETTER!  
Tested by a leading independent laboratory against competitive products!

	SUPER 100	A	B	C
CLEANING	Excellent	Good	Fair	Fair
LUBRICATION	Good	Fair	Fair	Poor
PLASTIC ATTACK	None	None	None	None
FLAMMABILITY	None	None	None	None
CONDUCTIVITY	None	None	Slight	Slight
ANTI-STATIC PROTECTION	Excellent	Fair	Poor	Poor
DRIFT	None	Slight	Yes	Yes



SUPER 100 TUNER CLEANER... for COLOR and Black and White TV tuners  
6 oz. spray can with INJECTORALL steel needle  
CAT. NO. 100-6 net \$1.95

Buy it at your Electronic Parts Dealer.  
For free catalog on the complete line, write to:

**INJECTORALL ELECTRONICS CORP. • Great Neck, N. Y.**

Circle 38 on literature card

## DC Voltage

(Continued from page 56)

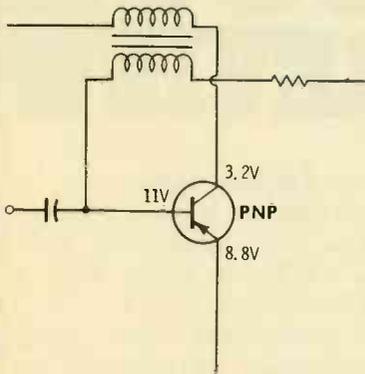


Fig. 11. Typical vertical oscillator.

### Measurement Conditions

The circuits previously discussed are basically Class-A amplifiers. In theory, a Class-A amplifier is entirely linear, and the DC operating voltages do not change when a normal input signal is applied. However, transistors are not perfectly linear devices, and the DC operating voltages do tend to change somewhat when a signal is applied. Therefore, normal DC voltages are commonly specified with no-signal input. Exceptions are local-oscillator, vertical-oscillator, and horizontal-oscillator circuits, which generate their own AC signal. Self-generated signals do not affect the accuracy of DC voltage measurements because the signal amplitude is constant.

Even though no signal is applied to a TV receiver, there still is an AC signal present, in the video-output stage, for example. Noise voltages are appreciable at this stage when the receiver is tuned to a vacant channel. However, this noise signal has a reasonably constant level in normal operation, and does not affect the practical accuracy of DC voltage measurements. If the video-driver stage is dead, the DC voltages in the video-output stage will be changed to some extent. In this abnormal operating condition, however, the DC voltage changes in the driver stage will be greatly off-value, and attention is thereby directed to the actual location of the trouble.

We find that transistors in oscillator circuits are often reverse-biased in normal operation. Fig. 11 for example, depicts a PNP transistor with the DC electrode voltages found in a normally-operating vertical-oscillator circuit. Note that the base is more positive than the emitter, or, the transistor is reverse-biased. The reason for this is that the self-generated signal drives the base into heavy peak-current flow; the resulting surges of base-emitter current leave an average positive charge on the right-hand side of the base capacitor. Therefore, although DC voltage measurements make it appear that the transistor is cut off, it actually conducts heavily in short pulses.

A sync-separator transistor operates with an average reverse bias when signal is present, because the incoming sync pulses drive the base into heavy current flow on pulse peaks; the coupling capacitor is charged to an average value that represents reverse bias in DC voltage measurements. On the other hand, if the stage preceding the sync separator is dead, the transistor in the sync-separator stage will measure a small forward bias (typically 0.6 volt). This can be a confusing symptom if it is not understood; the transistor seems to violate Ohm's law when the AC signal is ignored.

The normal DC voltages in a sync-separator stage are specified for no-signal input. This does not mean that there is actually no signal present, because noise voltages are normally applied to the transistor. Therefore, if the stage preceding the sync separator is dead, we measure seemingly abnormal DC voltages in the sync-separator stage. In summary, it is sometimes necessary to be on the alert for reflected trouble symptoms. A good understanding of transistor circuit action is the best insurance against wasted time looking for trouble in the wrong places.

### Conclusion

DC voltage measurements are the basic approach to trouble localization in transistor circuitry. The first step is to compare the measured values with those specified in the

## new Sams books

### Microminiature Electronics

by Israel Kalish. Microminiature electronics developed for the space and missile programs is now spreading into all phases of electronics, and will soon be commonplace in entertainment, commercial, and industrial electronic equipment design. This book clearly explains microminiature basics, and will not only help the reader prepare for packaging, operating, and servicing military microminiature equipment, but also orient him in the "think small" trend in civilian equipment. The text is of the programmed type, including questions and answers to review and accelerate learning. 304 pages; 5 1/2 x 8 1/2". Order 20582, only \$495

### AM-FM-TV Alignment

by Robert G. Middleton. This book tells you all you need to know about the proper alignment of a-m, f-m radios and tv sets. Each section of the receiver is analyzed step by step, and the fastest, easiest methods of alignment are shown. Separate chapters are devoted to alignment of the following: a-m receivers, f-m receivers, black-and-white tv, color-tv, f-m stereo multiplex adapters; special chapter on audio-amplifier frequency-response checks. 160 pages; 5 1/2 x 8 1/2". Order 20602, only \$350



### ABC's of Thermocouples

by John D. Lenk. This book provides much-needed information on the important but little known subject of thermocouples. Provides a basic understanding of how they work, how they are constructed, and the many ways in which they are applied. Standard types of thermocouples and their accessories are described; color coding is explained; includes full data on calibrating and methods of compensation control for use in laboratory, flight, data system, and other environments. Also covers thermocouple readouts, recorders, and controllers. 128 pages; 5 1/2 x 8 1/2". Order 20586, only \$225

### Symfact® Guide to TV Servicing

by Howard W. Sams Engineering Staff. Explains the normal operation of a given tv circuit, and then shows exactly the waveform display, voltage, symptoms, picture-tube display, etc., that occur when any component in that circuit is faulty. This invaluable book, in eight main sections, illustrates and describes the malfunctions that occur in specific circuits and shows how to identify and overcome them. Unbelievably practical for fast troubleshooting. 160 pages; 5 1/2 x 8 1/2". Order 20597, only \$295

### Practical Power Supply Circuits

by John Potter Shields. Provides a thorough understanding of the basic types of power supplies used in current electronic equipment. Explains the operation of various rectifier circuits—half-, full-wave, and bridge types—and describes the characteristics of gas and high vacuum tubes, as well as scr's used in these circuits. Explains the basics of filters and voltage regulators; describes solid-state voltage and current regulation. Includes semiconductor-type power supplies, converters, and inverters. Provides typical values and construction data. 112 pages; 5 1/2 x 8 1/2". Order 20571, only \$250

These and over 300 other SAMS Books are available from your local Electronics Parts Distributor . . .

HOWARD W. SAMS & CO., INC.  
4300 WEST 62nd ST. INDIANAPOLIS, INDIANA 46268

Circle 39 on literature card

December, 1967/PF REPORTER 61

# BUZIT TRANSISTORIZED SIGNAL TRACER

FOR ONLY **\$9.57** DEALER NET  
WITH BATTERIES

NO CLIPS  
NO WIRES



MADE IN  
U.S.A.

## USED FOR TROUBLE SHOOTING

- A.F. CIRCUITS • I.F. CIRCUITS
- R.F. CIRCUITS • CONTINUITY CHECKS • SPEAKERS, ETC.

EXCELLENT FOR TRANSISTOR  
RADIO'S BECAUSE BUZIT USES  
ONLY A 3 VOLT POWER SUPPLY

ASK YOUR ELECTRONIC  
PARTS DISTRIBUTOR FOR

**WEP** MODEL NO. **BZ-1**

MANUFACTURED BY

**WORKMAN**

SARASOTA FLORIDA

*Electronic*  
PRODUCTS INC

Circle 40 on literature card

## Save Time on PC Board Repairs!



MODEL 100A

Melted solder  
disappears up  
hollow tip  
into tube

## The ENDECO Desoldering Iron Removes Soldered Components in seconds... without damage!

Endeco melts solder, then removes it by vacuum • Leaves terminals and mounting holes clean • Resolders too • One-hand operation • Temperature controlled for continuous use • Ideal for use with shrinkable tubing • 4 tip sizes • Quickly pays for itself in time saved • Only \$18.75 net.

SMALLER SIZE AVAILABLE. SEE YOUR DISTRIBUTOR OR WRITE:



ENTERPRISE  
DEVELOPMENT  
CORPORATION

5151 E 65TH • INDIANAPOLIS, IND. 46220

Circle 41 on literature card

receiver service data. Specified test conditions, such as "no signal applied" must be observed to avoid confusion. The next step, particularly in case of doubt, is to check suspected transistors for normal control action, provided the DC bias system permits this check. Remember that a leaky coupling capacitor can produce the same symptoms as a transistor with collector-junction leakage. If we are checking the later stages in a receiver, we would keep in mind the fact that noise voltages are normally present, and may affect the DC voltage measurements. In other words, we must be on guard for reflected trouble.

Most transistor failures are associated with leaky collector junctions. However, if circuit trouble causes a transistor to "punch through", the collector junction will be either open-circuited or practically short-circuited. An ohmmeter test out-of-circuit will give either an infinite reading, or a resistance value less than 100 ohms. Emitter junctions become damaged less often than collector junctions. However, if the collector is short-circuited to the base for any reason, it is possible for the maximum emitter-base current to be exceeded. The emitter junction then becomes either open-circuited or short-circuited.

Technicians often test a suspected transistor for control action by bleeding some collector voltage into the base circuit. However, this test is not as conclusive as a control-action test, to check whether the transistor can be cut off. In case a cut-off test is impractical (as in Fig. 10C), the bleed test must be used. Therefore, to speed up service jobs we must learn how transistor circuits operate, recognize the basic configurations, know the most useful tests, and keep the tricks of the trade in mind. ▲

## MOVING?

Don't lose touch . . .  
RECEIVE PER AS USUAL  
(INCLUDE OLD AND NEW ADDRESS)

PF REPORTER  
CIRCULATION DEPT.

4300 W. 62nd St.  
Indianapolis, Ind. 46206

# BOOK REVIEW

## Audio Amplifier Design:

Farl J. Waters; Howard W. Sams & Co., Inc., Indianapolis, Indiana, 1967; 160 pages, 5½" x 8½", soft cover, \$4.25.

A combination book which can be used for study or reference, this book also includes a number of projects up to and including a 50-watt, solid-state, hi-fi amplifier.

Though this book is perfectly understandable to the educated hobbyist, is certainly should not be limited to just those readers. The author has managed to present an astonishing amount of information in what seems like a limited-size book. Design parameters are treated in depth, with considerable math, but all in simple algebraic form. For those readers who do not like algebra, nomographs are included for nearly every formula. For instance, nomographs are available for determining part values such as power supply filters, feedback capacitors, base biasing resistors, screen resistors, etc, etc.


Chapter titles include: Amplifier Theory, R-C Coupling of Transistors, Drivers, Controls, and others. Each stage of a typical amplifier is treated separately in its own chapter, and the final chapter illustrates how to join the stages to design a complete instrument.

"Audio Amplifier Design" answers such questions as "How much amplification is needed? How many stages will this require? What values of coupling and bypass capacitors are needed for a specified frequency response?" Building an audio amplifier should become a simple project with the help of the information in this book. ▲

*Plug in  
with a  
winner...*

**TV  
SERVICE  
CORDS** by

*Columbia*

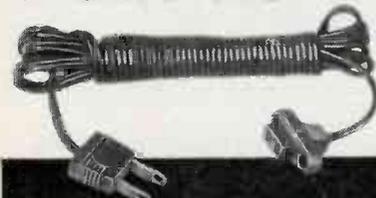

Match the requirements of most every TV set in use today from the broad selection of service cords Columbia produces and stocks to meet immediate needs.



Choose from a variety of non-polarized and polarized caps and connectors for safer operation, added customer protection against shock hazards. Available in standard 6 and 9-foot lengths, Columbia cords have durable vinyl or rubber insulation, are available in brown or white to meet color preferences.



All are quality built to give long, trouble-free service life, added customer satisfaction, and greater profits for you.

*Order from  
your  
distributor today!*

*Columbia*  
**WIRE PRODUCTS COMPANY**  
2850 Irving Park Road  
Chicago 60618

Circle 43 on literature card

## INDEX TO ADVERTISERS

December, 1967

American Telephone & Telegraph .....	49
B & K Mfg. Co., Div. of Dynascan Corp. ....	59
Belden Mfg Co. ....	18, 19
Bussmann Mfg. ....	10, 11
Castle TV Tuner Service, Inc. ....	9
Channel Master .....	14, 15
Chemtronics, Inc. ....	63
Cleveland Institute of Electronics .....	54
Columbia Wire Products Co. ....	63
Eico .....	1
Enterprise Development Corp. ....	62
The Finney Co. ....	37
G. C. Electronics .....	46
Gem City Tuner Repair Service .....	8
General Electric Co. ....	43, 51
Injectorall Electronics Corp. ....	60
Jerrold Electronics Corp. ....	22
JFD Electronics Co. ....	27
Leader Electronics Corp. ....	53
Lectrotech, Inc. ....	57
Littelfuse, Inc. ....	Cover 4
Mallory, P. R. & Co., Inc. ....	Cover 2
Miller Mfg. Co. ....	8
Multicore Sales Corp. ....	59
Philco-Ford Co. ....	21
RCA Components & Devices (Entertainment Tubes) .....	Cover 3
RCA Institutes, Inc. ....	52
RMS Electronics, Inc. ....	48
Sams Howard W. & Co., Inc. ....	13, 61
Sarkes Tarzian, Inc. ....	7
Seco Electronics Corp. ....	50, 55
SENCORE, Inc. ....	25, 32, 36
Simpson Electric Co. ....	47
Sprague Products Co. ....	3
Superior Tuner Service .....	57
Swing-O-Lite .....	58
Sylvania Electric Products Corp. ....	38, 39
Triplet Electrical Instrument Co. ....	29
Winegard Co. ....	34, 35
Workman Electronics Products, Inc. ....	62
Xcelite, Inc. ....	45
Zenith Sales Corp. ....	41



The NEW  
NO. 800

**TUN-O-LUBE  
TUNER CLEANER**

*Specially*

**FORMULATED  
FOR TV-TUNERS**

**USING NUVISTORS &  
TRANSISTORS**

**NO TUNER DRIFT**

Nuvistors and Transistors are highly sensitive to drift from ingredients in most ordinary TV tuner cleaners. Drift has been found to cause call backs and expensive tuner repairs. For over 18 months CHEMTRONICS has been formulating and testing this new cleaner in both the lab and field. Under the most critical test, there has been NO DRIFT on scope patterns. We invite you to try this test yourself.

NO. 800

\$1.98

DEALER

NET

**NEW IMPROVED  
FAST FLOWING**

**ACTIVATED  
ROSIN CORE**

**SOLDER**



CHEMTRONICS' high quality solder is non-corrosive and non-hygroscopic.

Exceeds requirements of Federal Specifications QQ-S-571d.

**CHEMTRONICS**

BROOKLYN

N. Y. 11236

Circle 42 on literature card

December, 1967 / PF REPORTER 63



# \$ FREES \$

## CATALOG AND LITERATURE SERVICES

\*CHECK "INDEX TO ADVERTISERS" FOR FURTHER INFORMATION FROM THESE COMPANIES

### ANTENNAS

65. **ALLIANCE** — Colorful 4-page brochure describing in detail all the features of Tenna-Rotors.
66. **ANTENNACRAFT** — New 6-page full color brochure describing vinyl-finished all channel antennas.
67. **BLONDER-TONGUE** — Colorful new flyer describes a complete line of UHF, VHF, & FM antennas. Describes various types to use depending on local reception problems.
68. **CORNELL-DUBILIER** — New 4-page brochure with instructions for installation of the AR10B skyline Series rotor.
69. **DELHI** — Twelve-page catalog introducing a complete new line of home TV towers, ham towers, citizen's band towers, masts and telescoping masts.
70. **FINNEY** — 4-color brochure with description and technical details on new Finco color spectrum frequency dependent antennas for UHF-VHF-FM, VHF-FM, and UHF. Form 20-413.\*
71. **JERROLD** — New 4-page full-color catalog describes the new Paralog Plus antennas.\*
72. **JFD** — Color Laser and LPV antenna brochures. New 1967 dealer catalog covering complete line of log-periodic outdoor antennas, rotators, and accessories.\*
73. **MOSLEY** — Catalogs on CB, Amateur radio, and TV/FM antennas.
74. **WINEGARD** — New 40-page MATV catalog features Ultra-Plex amplifier system and installation instructions.\*

### AUDIO

75. **ALTEC-LANSING** — Brochure AL-1315-3 describes speaker systems for theaters, night clubs, auditoriums, arenas, etc.
76. **ATLAS SOUND** — Specification sheets on new models AP-15, AP-15T, and APT-34T paging speakers.
77. **ELECTRO-VOICE** — Catalog 167 on microphones and PA equipment.
78. **OXFORD TRANSDUCER** — Bulletin A-109 features speaker installation in automobiles, hospitals, and recreation rooms.
79. **SWITCHCRAFT** — Bulletin 170 describes seven new audio accessories.

### COMMUNICATIONS

80. **AMPHENOL** — 2-color spec sheets on new Model 650 CB transceivers and Model C-75 hand-held transceiver.
81. **MOTOROLA** — New brochure tells how to reach people on-the-move through use of personal two-way radio.
82. **SQUIRES-SANDERS** — Brochure entitled "Skip is Legal".

### COMPONENTS

83. **BELDEN** — Catalog 867, a 56-page catalog of the complete Belden Line.\*
84. **BUSSMANN** — 12-page booklet listing the complete line of BUSS and FUSETRON small dimension fuses by size and type, also indicates proper fuseholder — also shows list prices. Ask for **BUSS Bulletin SFUS**.\*

85. **CENTRALAB** — 24-page replacement parts catalog No. 33GL.
86. **LITTELFUSE** — Pocket-sized TV circuit breaker cross-reference gives the following information at a glance. Manufacturer's part number, corresponding *Littlefuse* part number, price, color or b/w designation. A second glance gives trip ratings and acquaints you with a line of caddies. Ask for CBCRP.\*
87. **MALLORY** — Bulletin 4-82 describes radial and axial lead tantalum capacitors.\*
88. **MILLER** — Catalog 167, a 156-page general catalog with complete cross-reference guide to the J.W. Miller Line.\*
89. **NATIONAL TEL-TRONICS** — Flyer about a new flexible terminal block.
90. **QUAM-NICHOLS** — New catalog No. 67 has complete, detailed information on the entire Quam line.
91. **RELCOA**—Tech-Spec Series SR-1 about sensitive miniature relays.
92. **SPRAGUE** — C617, a complete catalog of the Sprague Line.\*
93. **TEXAS CRYSTALS** — 12-page catalog of crystals including engineering data, specifications and prices.

### SERVICE AIDS

94. **CASTLE TUNER** — How to get fast overhaul service on all makes and models of television tuners is described in leaflet. Shipping instructions, labels, and tags are also included.\*
95. **GC-FR-67**, the full-line catalog.\*
96. **INJECTORAL**—24-hour service on any make tuner is described in colorful brochure.
97. **MID-STATE TUNER** — Colorful brochure describes 24-hour service on any make tuner.
98. **PERMA-POWER** — New 4-page catalog of TV accessories.
99. **PRECISION TUNER** — Free mailing kit and replacement tuner list for same-day tuner service.
100. **T.V. TUNER SERVICE** — Brochure lists cost and mailing instructions for 24-hour service on any make tuner. Repair tags and shipping labels included.
101. **VECTOR** — Flyer sheet on current test tube socket adaptors.

### SPECIAL EQUIPMENT

102. **ANDREA** — Folders on the new line of color and B/W TV receivers.
103. **ATR** — Literature about DC-AC inverters up to 600 watts load.
104. **KEARNEY** — Folder describes new "Shock-Shield safety circuit breaker. Instantly senses danger of ground leakage.
105. **LUXO** — 4-page catalog A-421 about bench and desk lamps.
106. **WINDSOR ELECTRONICS** — Booklet entitled "The Open Door to TV Profits".

### TECHNICAL PUBLICATIONS

107. **CLEVELAND INSTITUTE OF ELECTRONICS** — Free illustrated brochure describing electronics slide rule and four lesson instruction course and grading service.\*
109. **RCA INSTITUTES** — New 1967 career book describes home study programs and course in television (monochrome and color), communications, transistors, industrial, and automation electronics.\*
110. **SAMS, HOWARD W.** — Literature describing popular and informative publications on radio and TV servicing, communication, audio, hi-fi, and industrial electronics, including special new 1967 catalog of technical books on every phase of electronics.\*

### TEST EQUIPMENT

111. **B & K** — New 1967 catalog featuring test equipment for color TV, auto radio, and transistor radio servicing, including tube testers designed for testing latest receiving tube types.\*
112. **EICO** — New spec sheet describes model 100A4 multimeter with DC sensitivity of 100K ohms per volt.\*
113. **HICKOK** — Quick reference catalog No. 67D gives brief descriptions and prices for complete test equipment line. Also specification data on Models CR-35 CRT tester, GC-660 color generator, and 860 Injecto-Tracer.
114. **JACKSON** — New full-line brochure includes the all-new in-circuit transistor checker with 8" meter.
115. **LECTROTECH** — Two-color catalog sheet on new Model V-6 color bar generator, the latest improved model of the V-6. Gives all specs and is fully illustrated.\*
116. **MERCURY** — All-new 16-page test instrument catalog.
117. **PRECISION APPARATUS** — 12-page illustrated catalog describes the application and features of a complete line of test equipment — scopes, sine-square wave generators, RF generators, sweep generators with marker adder, Low- and High-voltage power supplies, VOMS and VTVMs.
118. **SECO** — Operating manual for the HC8 in-circuit current checker for horizontal output tubes.\*
119. **SENCORE** — New 12-page catalog on all SENCORE products.\*
120. **SIMPSON** — Reprint: "A Guide to the Selection of Multitesters." Explains how to evaluate multitesters before you buy.\*
121. **TRIPLETT** — Catalog No. 51-T features the complete line of VOM's, VTVM's, tube and transistor analyzers and accessories.\*

### TOOLS

122. **ARROW** — Catalog sheet showing 3 staple gun tackers designed for fastening wires and cables up to 1/2" diameter.
123. **BERNS** — Brochure about three models of pin-crimpers.
124. **DIAMOND TOOL AND HORSESHOE** — 16-page booklet W-68 describing several lines of wrenches, pliers, snips, and electronic pliers.
125. **ENTERPRISE DEVELOPMENT** — Time-saving techniques in brochure from Endeco demonstrate improved desoldering and resoldering methods for speeding and simplifying operations on PC boards.\*
126. **UNGAR** — Catalog of 2 lines of soldering equipment.
127. **VACO** — Catalog SD-126 describing complete line of Pow-Rivets for blind riveting.
128. **XCELITE** — Bulletin N867 describes hollow-shaft nutdrivers which speed locknut/screw adjustments.

### TUBES AND TRANSISTORS

129. **MOTOROLA** — New semiconductor catalog HMA-27 lists device ratings and characteristics of the HEP line.
130. **RCA** — PIX 300, a 12-page product guide on RCA picture tubes covering both color and black-and-white. Includes characteristics chart, terminal diagrams, industry replacement, and interchangeability.\*

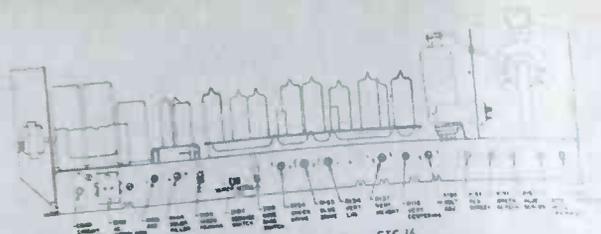


Fig. 7 - Rear Chassis View - CTC-16.


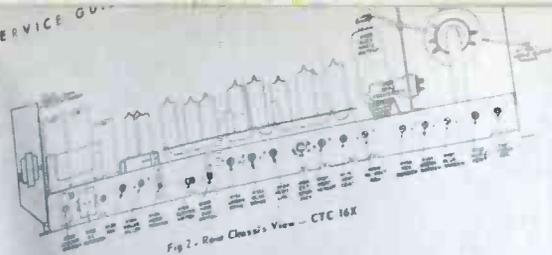


Fig. 2 - Rear Chassis View - CTC-16X

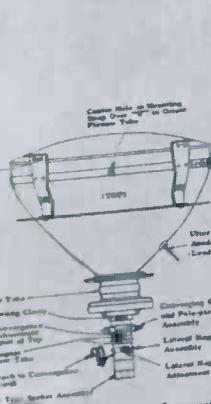

Tube Assembly and Components.

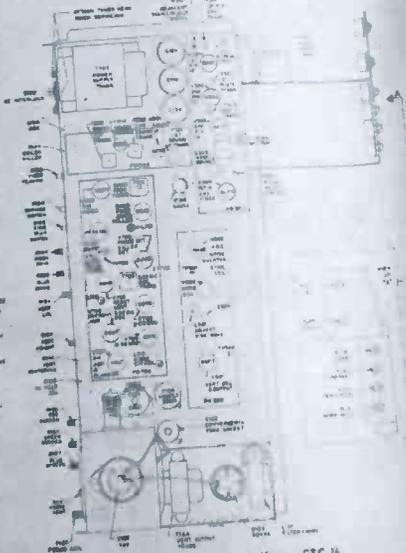


Fig. 6 - Top Chassis View - CTC-16.

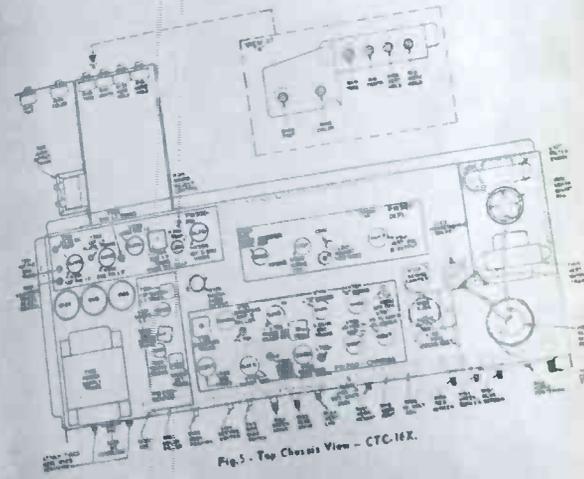


Fig. 5 - Top Chassis View - CTC-16X.

# You need this guide for RCA Color Home Service Calls!

RCA'S NEW FIELD SERVICE GUIDE, ERT-200 helps you make all adjustments on all RCA color sets from 1955 to 1966 that can be performed in the home... including step-by-step procedure for replacing a color picture tube.

Three part index lets you look up the set you are working on by model number, name or chassis number. You'll find the ERT-200 Field Service Guide indispensable. There's nothing like it on house calls for RCA color sets.

**WHAT THIS GUIDE CONTAINS:**


- Schematics on all RCA color sets from 1955 to 1966
- Field service adjustments (AGC, linearity, centering, etc.)
- Convergence, purity and black and white setup adjustments
- Parts lists
- Wave forms keyed to test points for majority of chassis
- Top and rear chassis views
- Photos of typical receivers
- Index of models from CTC2 through CTC20
- Separate section on tuner schematics
- Separate section on remote tuner schematics

See your RCA Tube Distributor today and arrange to get your copy.



**FIELD-SERVICE GUIDE**

**RCA COLOR-TV RECEIVERS**  
1955-1966

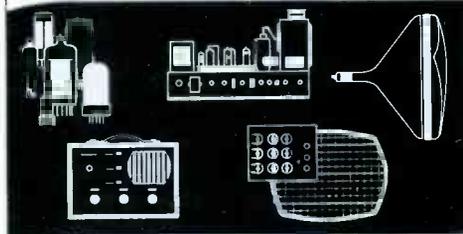

- FEATURES:**
- Field Service Adjustments - CTC-28 Through CTC-20A
  - Top and Rear Chassis Views
  - Schematic Diagrams
  - Voltage Waveforms Keyed to Test Points
  - Separate Section on Tuner Schematics
  - Parts Lists
  - Comprehensive Index of Model Number, Model Name, and Chassis Number

RCA Electronic Components and Devices, Harrison, N.J. 07029



The Most Trusted Name in Electronics

See the caddy



See the fuse box  
through the caddy



See the fuses  
through the  
fuse box  
through the caddy



See more profits through

**LITELFUSE**

DES PLAINES, ILLINOIS

Circle 44 on literature card