


▲ A HOWARD W. SAMS PUBLICATION

FEBRUARY, 1968/75¢

PF Reporter[®]

PHOTOFACT


the magazine of electronic servicing

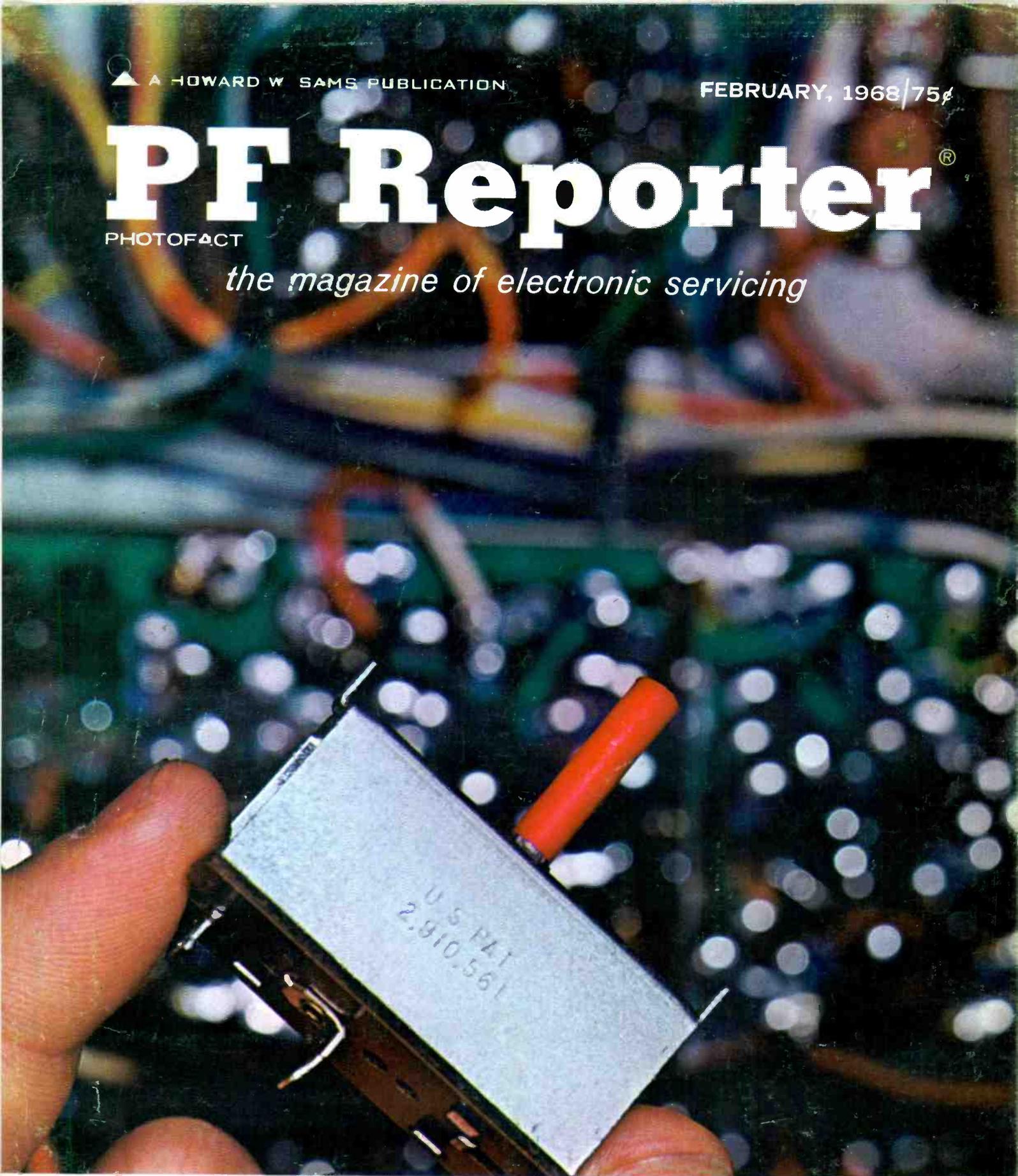

IA SL 4279 1268
WV. M. DAVIS
RADIO & TV SERVICE
118 RIVERSIDE AVE.
GAYON CITY, COLORADO 81632

- Notes on Test Equipment
- Tube Substitution Supplement
- The Electronic Scanner
- Color Countermeasures
- The Troubleshooter

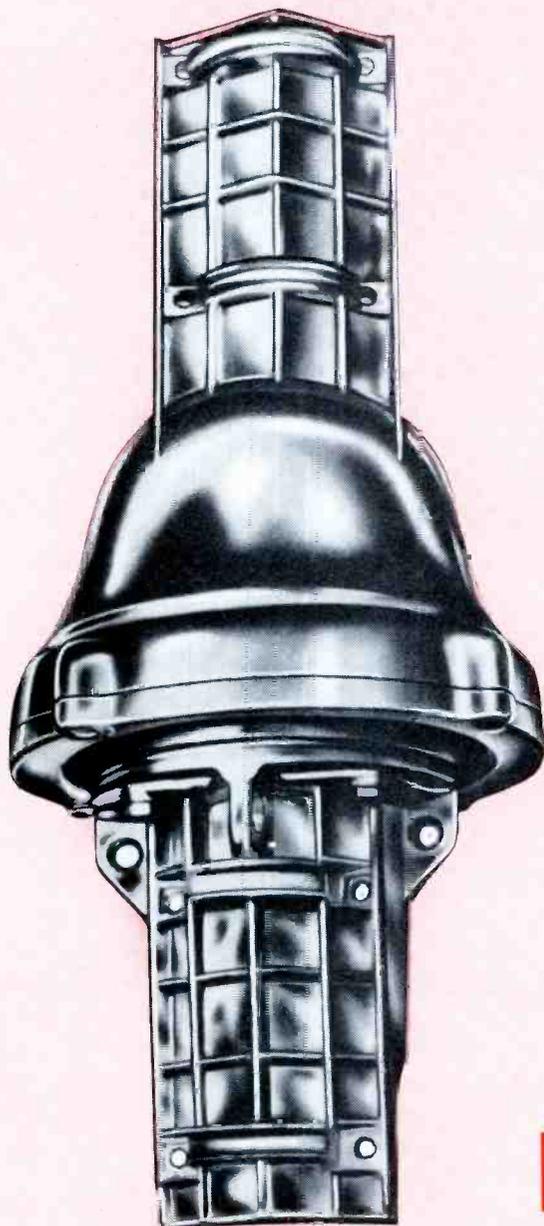Never ask a lightweight rotor to do a heavyweight's job.



Selling your customer a lightweight rotor when he has a large antenna array just doesn't make sense. Especially since you can offer him an alternative: the heavy-duty "Bell Series" rotor, from CDE.

Available in both automatic and manual forms, this rotor is designed specifically for large, heavy antenna arrays... designed specifically for unmatched fringe-area reception... designed to give your customers the finest color TV reception possible. In fact, this is the *only* heavy-duty rotor available.

We call it the Bell Series because of its completely weatherproof, die-cast aluminum housing. You'll call it rugged because it has 4 to 5 times the stalling and braking torque of any other rotor! This means *any* antenna will turn, even under the most adverse weather conditions... and that your customers will get terrific color or black and white reception despite high winds or heavy icing. Great FM reception too!

The Bell Series rotor: one-of-a-kind built for one-of-a-kind performance!

CDE CORNELL-
DUBILIER

Circle 1 on literature card

EICO Makes It Possible

You get 100% professional test equipment quality—and economy. EICO's uncompromising engineering-for-value makes it possible. Twenty-three years ago we started EICO to deliver "Laboratory Precision at Lowest Cost." Today, three million customers like us for it. Compare EICO products with anybody's at your local dealer. You'll see for yourself how you save up to 50% with EICO kits and wired equipment—and enjoy electronic excellence too!



- 1/2-volt Full-Scale DC Transistor Servicing Range. Accurate measurements down to 0.01 volts.
- Deluxe full-view 6" 200 microamp meter movement.
- Unique ease & speed by exclusive color coding of switches with meter scales.
- Dual purpose EICO exclusive AC/DC Uni-Probe.®
- Signal isolation floating ground.

NEW EICO 235 PROFESSIONAL VTVM

Feature-packed 6" professional VTVM brings you more in functional styling, convenience, and dependable performance for exacting measurements in solid state circuitry.

8 DC Ranges: 0-0.5-1.5-5-15-50-150-500-1500 (to 30,000 volts with optional high voltage probe). 7 AC Peak-to-Peak Ranges: 0-4-14-42-140-1400-4200. 7 AC RMS Ranges: 0-1.5-5-15-50-150-500-1500. 7 Resistance Ranges Covering: 0.2Ω to 1000MΩ. Frequency Response: 3 cps to 3Mc ±1db (up to 250Mc with optional PRF probe). Input Resistance: DC 11MΩ; AC 1M shunted by 60mmf. 1% precision multiplier resistors. 3% accuracy on AC and DC scales.

Kit \$49.95
Wired \$69.95

Terrific time-saver! Only 1 probe performs all functions — a half-turn of probe-tip selects DC or AC-OHMS!

TRUVOHM PROFESSIONAL PORTABLE MULTIMETERS by EICO.

The industry's greatest V-O-M values. Designed & manufactured to Eico's high standards of professionalism. Each complete with batteries & test leads. Backed 100% by famous EICO warranty.

100,000 Ohms/Volt Model 100A4, \$34.95 optional carrying case \$5.95
The best buy in a bench-size multimeter. With AC sensitivity 12,500Ω/V, combines minimal circuit loading with wide-ranging functional utility. Double-jewelled ±2% D'Arsonval meter movement; full-view 4-inch mirror-back two-color scale eliminates reading parallax; matched pair of silicon diodes prevents accidental overload of meter movement. High-impact, custom-molded case protects against shock



30,000 Ohms/Volts Model 30A4 \$19.95



30,000 Ohms/Volts Model 30A3 \$15.95



20,000 Ohms/Volts Model 20A3 \$12.95



4,000 Ohms/Volts Model 4A3, \$8.95



1,000 Ohms/Volts Model 1A1, \$5.95

ATTENTION EICO TUBE TESTER OWNERS: NEW TUBE DATA AND SUBSCRIPTION PLAN NOW AVAILABLE FOR ALL MODELS. Write To: EICO Tube Data Division, 1744 Rockaway Ave., Hewlett, N.Y. 11557



Model 232 Peak-to-Peak VTVM. A must for color or B&W TV and industrial use. 7 non-skip ranges on all 4 functions. With exclusive Uni-Probe.® \$29.95 kit, \$49.95 wired.



New Model 567 VOM Kit \$34.95 Wired \$44.95

- 20,000 ohms-per-volt sensitivity
- 0.25 volt full-scale range
- Silicon diode meter protection circuit


DCV: 0-0.25, 2.5, 10, 50, 250, 1000, 5000V. ACV: 0-2.5, 10, 50, 250, 1000, 5000V. DCI: 0-50 uA, 1 mA, 10 mA, 100 mA, 500 mA, 10 amps. —12 to +55 db in 5 ranges. RES: 0-2KΩ, 200KΩ, 2MΩ.



laboratory precision at lowest cost.



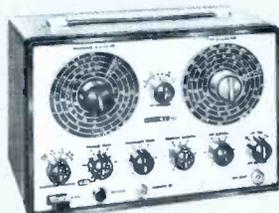Model 460 Wideband Direct-Coupled 5" Oscilloscope. DC-4.5mc for color and B&W TV service and lab use. Push-pull DC vertical amp., bal. or unbal. input. Automatic sync limiter and amp. \$109.95 kit, \$149.95 wired.



Model 369 Sweep and Post-Injection Marker Generator. For easiest, fastest visual alignment of color B & W TV and FM RF and IF circuits. Five sweep ranges from 3-220 Mc/S. Four marker ranges from 2-225 Mc/S. Crystal marker oscillator. Post injection of markers. Kit \$99.95. Wired \$149.95

FREE 1968 CATALOG PFR-2


EICO Electronic Instrument Co., Inc. 283 Malta Street, Bklyn., N.Y. 11207

Send me FREE catalog describing the full EICO line of 200 best buys, and name of nearest dealer.

Name _____
Address _____
City _____
State _____ Zip _____

Circle 2 on literature card

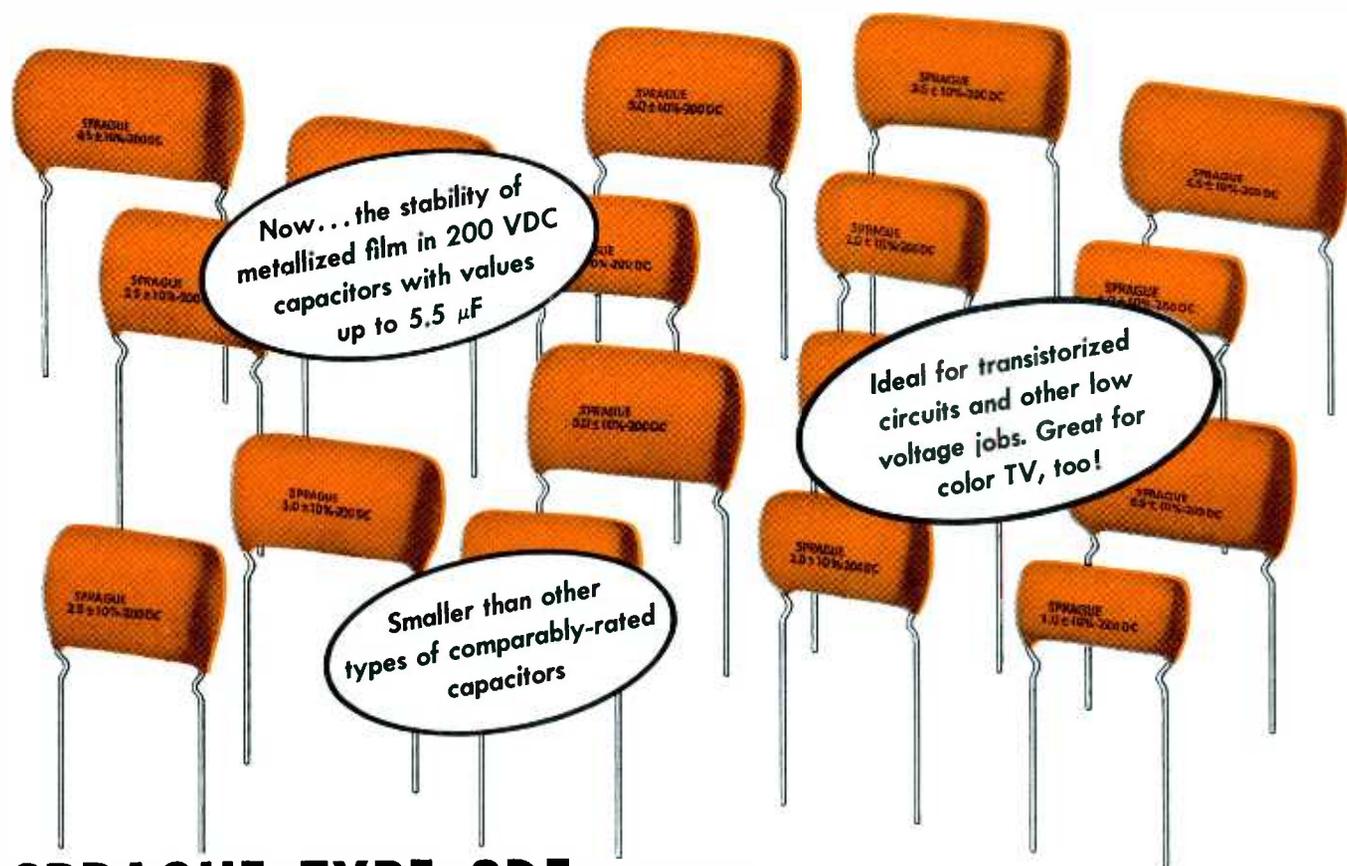BRAND NEW...TO KEEP YOU OUT OF CALL-BACK TROUBLE!



SPRAGUE TYPE 2DF METALLIZED FILM ORANGE DROP[®] CAPACITORS

For the first time, the capacitance stability of metallized film is provided in 200 VDC service-type capacitors with values that start at .15 μ F and include the higher 1 to 5.5 μ F range, generally available only in electrolytics.

These new Sprague Type 2DF Orange Drops offer you many other advantages, too!  They have an

extremely high insulation resistance to insure peak performance at temperatures up to +85 C (185 F).

 Double-dipped in orange epoxy resin, they're amply protected against heat and humidity.

 Radial leads are not only extra long for point-to-point wiring but also crimped for printed boards.


 They're easier to fit into tight spots.

For trouble-free service, start using Type 2DF capacitors now. They're available at your Sprague distributor. Or write for Bulletin M-877 to Sprague Products Co., 509 Marshall St., North Adams, Mass. 01247.


**DON'T FORGET TO ASK YOUR CUSTOMERS
"WHAT ELSE NEEDS FIXING?"**

Circle 3 on literature card




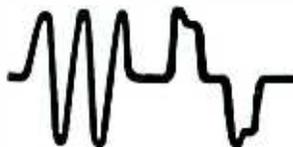

New circuit breakers for color TV

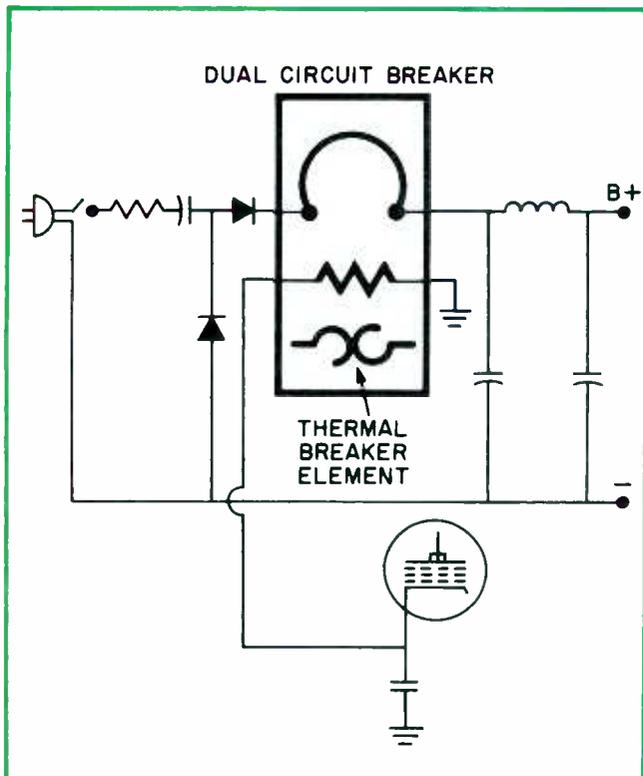

Typical hook-up for dual circuit breaker

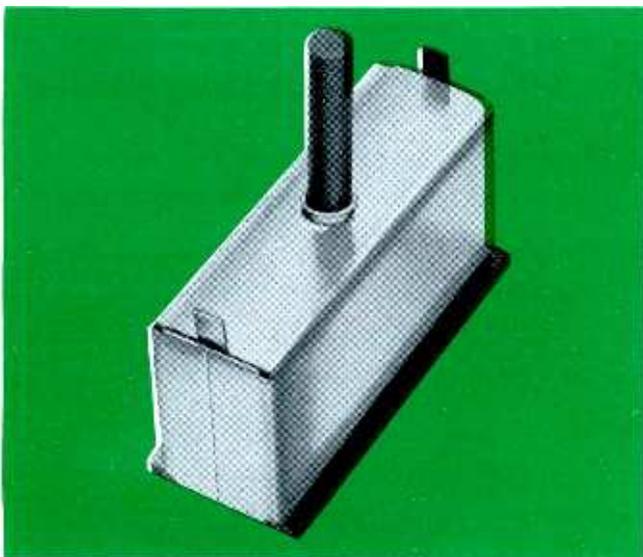

Dual circuit breaker

Practically all the new color TV sets have a new kind of dual circuit breaker in them which you may not have run into before. Here's the story.

Remember back when black-and-white television used two fuses—one in the power supply input, and one in the horizontal output circuit? Next, in the interest of economy, the fuse in the horizontal output was eliminated. Then the designers switched to re-settable breakers, in the B+ line.

Along came color. Overload protection became necessary, because the horizontal circuits are more complicated, and more expensive components including the flyback transformer could be knocked out by a defect in the horizontal circuit.

The answer: a dual breaker which pops out from excess current in *either* the B+ or the horizontal output . . . in a single breaker case. It has two electrically isolated but thermally connected circuits, either of which can cause the B+ contacts to open.

The diagram shows a basic hook-up for the breaker. The thermal breaker element goes directly in the B+ line. A resistor inside the breaker, usually about 1.3 ohms, is connected between the cathode of the horizontal output stage and ground. This resistor is located so it will heat up the thermal breaker element.

Along comes an overload in the B+. The thermal element pops the contacts open, in the usual manner. When there's excessive current in the horizontal output, the heating of the breaker's resistor has the same effect as a B+ overload, opening the contacts and removing voltage from the circuit.

Tip No. 1: breakers can fail because they get repeatedly reset into a fault. Check for gassy tubes and leaky capacitors before you replace the breaker, or you'll have the whole job to do over.

Tip No. 2: always replace with a Mallory breaker. We have three different dual breaker ratings in our line. They will replace the dual breakers in all existing color set applications. All are made to original equipment specifications. Your nearby Mallory distributor can supply you off the shelf. See him soon, or write to Mallory Distributor Products Company, a division of P. R. Mallory & Co. Inc., Indianapolis, Indiana 46206.

REMEMBER TO ASK—*“What else needs fixing?”*

Circle 4 on literature card



BY M. F. MELVIN, PRESIDENT MEL-RAIN CORPORATION

In the history of components, probably none has been as misunderstood and unfairly judged as the circuit breaker. Approximately 80% of the units returned to the manufacturer are *not* defective! The circuit breaker has gained increased popularity in the electronics industry during the past several years; in fact, there are over 50,000,000 in use, which speaks well of the circuit breaker's acceptance. Of particular interest is the fact that its failure rate has been so low that only recently, and now only because of the large number of protectors in the field, has it been reasonable to establish a replacement program.

The fact that such a large number of good circuit breakers are mistakenly labeled defective indicates that we all need a better understanding of the unit and what it is designed to do. A close look at the circuit breaker (Fig. 1) and its function will permit us to view it in a new light.

The circuit breaker is a far cry from the simple fuse and must be considered as a relatively complex device, incorporated in the set at an *additional* cost to the manufacturer. Since manufacturers are continually trying to lower costs, there must be a reason for their willingness to accept this additional expense.

Design

The circuit breaker for a particular chassis is selected by first deter-

mining the amount of current the set normally draws. In order to be safe, the design engineer will measure several sets that are operating satisfactorily. In addition, he will also measure them at various line voltages, realizing that the set will be operated in areas where the line voltage can be as low as 105 volts, or as high as 130 volts. Once the maximum current load (I_{set}) is determined, the engineer then adds a safety factor of approximately 10 percent and, thus, arrives at the "operating current" (I_0). This is the maximum current level (and below) at which the circuit breaker must stay closed.

Once the "operating current" has been established, the "break current" is calculated by multiplying the "operating current" by slightly more than 1.5. For example, if the "operating current" is 1.45 amperes, the "break current" would be about 2.2 amperes. "Break current" is defined as the current at which the circuit breaker will *definitely* open. With these two levels established by the set manufacturer, the manufacturer of the circuit breaker adjusts the new units to open their contacts at a current somewhere between "operate" and "break." In the above example, one circuit breaker might open at 1.5 amperes while another opens at 2.1 amperes. A third unit might have 1.95 amperes as its actuating level.

A graphical representation of the preceding information is given in

Fig. 2. In the previous example, 1.3 amperes (I_{set}) was the maximum line current drawn by the group of normally operating sets. Since a safety factor (10%) was desired to prevent unnecessary "nuisance" openings, the "operating current" (I_0) was established at 1.45 amperes. From this, the "break current" was calculated as being 2.2 amperes. Approximately 150 circuit breakers were adjusted for this range and then tested to find the actual current level at which they would open. The graph shows that most of them (23) opened at 1.9 amperes. Many more opened quite close to this level (20 at 1.95 amperes and 17 at 1.85 amperes). The opening level of the remaining circuit breakers tapered off so that all fell within the current range from "operate" to "break." It should be noted that the number diminished as the current approached the "break" current (2 opening at 2.2 amperes). Also note that none

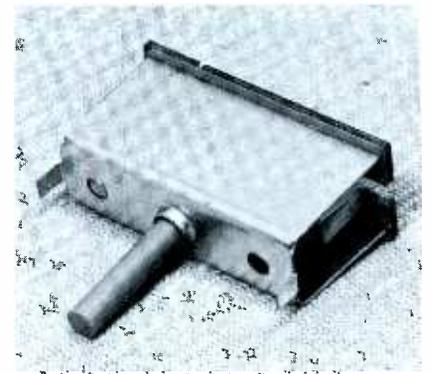


Fig. 1. Size does not reflect the circuit breaker's importance.

exceeded the specified "break" or "operate" levels.

Let's take a look at some of the problems that occur in TV sets returned for repair. One of the most common is that the protector keeps "popping out," or opening up, when there doesn't seem to be anything wrong with the set. The first analysis is that "the breaker is bad." This is possible, but this particular trouble symptom usually is caused by a change in circuit current attributed to the aging or changing of a component. This argument doesn't seem to stand up, however, if another circuit breaker of the same rating is substituted and the trouble symptom disappears. But wait—are all circuit breakers with the same rating actually the same? Not quite. Admittedly, they are quite close to being "peas in a pod"; however, remember Fig. 2.

Our analysis of 150 circuit breakers showed that some units opened near the "operating current," others opened at or near the "break current," while most opened somewhere in between. Let's say that the troublesome set we have been discussing has an electrolytic capacitor that is a bit leaky and the "normal" current changes from a figure at or below I_{set} to a level of 1.5 amperes. This

is within the range between "operating" and "break." From the illustration it was determined that one of the 150 units would open at 1.5 amperes. It is possible that the protector in the troublesome set was one of the "low-limit" units. When the 1.5-ampere current level was attained, this "more sensitive" unit opened.

To follow our example further, suppose the serviceman replaced the circuit breaker with an "exact replacement." This identical unit would still be between limits, (I_0 to I_B), but it might be one of those that would not open until the current reached 2.1 amperes. The "defective breaker" seemed to have been taken care of, because there were no longer any nuisance "popouts." However, the capacitor is still leaky, and the leak will increase with time. This probably will occur after the set has been returned to the customer, and he has just gotten over paying a repair bill for a "lousy breaker." The result: more trouble, and the set goes back to the shop—and probably not the same shop.

There have been many instances where the serviceman has understood only enough about circuit-breaker characteristics to cause him

to replace it with one having a much higher current rating. Although the original circuit breaker should open at a point somewhere between 1.45 and 2.2 amperes, this fellow's solution to the problem is to replace the unit with a circuit breaker that opens at about 4 amperes. This is the same character who puts a penny behind the fuse in his fuse box. He doesn't mind seeing the smoke roll. By using an incorrect replacement, he has sacrificed all of the sensitive advantages of the circuit breaker and, in so doing, has created an extremely dangerous condition—not to mention the expense incurred by added damage to the set.

What should have been done in the above case? The serviceman should have consulted the available service literature and determined what current was considered to be normal. Such information is now available in PHOTOFAC schematics. Since the line current drain of the set was at or above the normal figure, he should have suspected a defective component or other trouble that would cause this symptom. Replacing the guilty part would have brought the current well below the "operating current" of the breaker, and the set could have been returned to a satisfied owner who would call the same serviceman in the event of other trouble(s).

Fuses

In the preceding example, the repairman could have taken another approach and used a fuse. What kind of protection would this have provided the set? Let's examine the facts.

A fuse with a standard rating would have been used—probably 1.5 amperes. Fuse literature usually states that the fuse will carry 110% of rating without blowing. In this case, the 110% current would be 1.65 amperes — temporarily satisfactory; however, in time, some components could suffer.

Further interpretation of most fuse curves shows that the fuse has a "blow" rating of 135% within one hour. 135% of 1.5 is 2.025 amperes; a current which, if present for an extended time, could result in component deterioration.

For relatively quick action with a fuse, the overload must approach

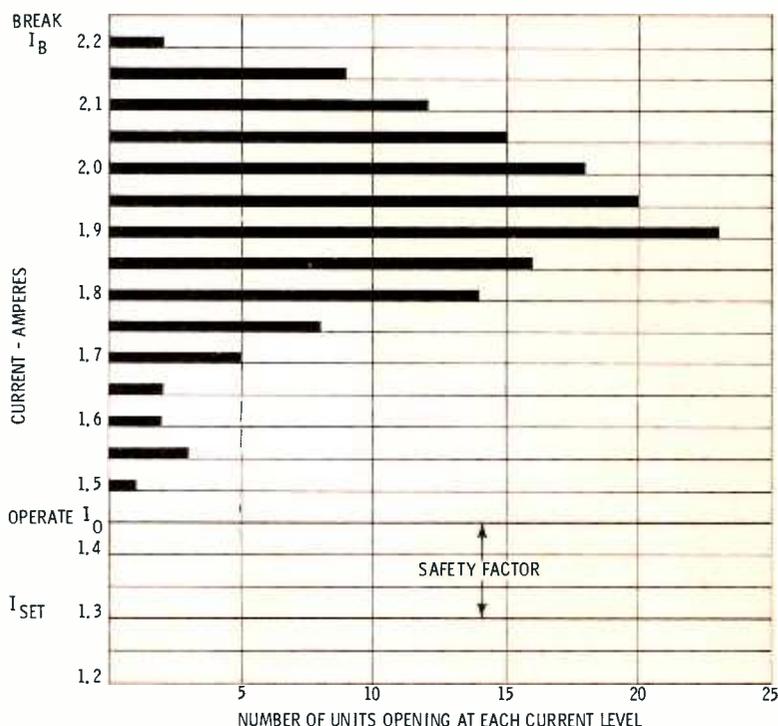


Fig. 2. An analysis of the actual operating range of a group of circuit breakers.



\$975

EFFECTIVE 8/1/67

GUARANTEED

Nine-seventy-five buys you a complete tuner overhaul—including parts (except tubes or transistors)—and absolutely no hidden charges. All makes, color or black and white. UV combos only \$15.

Guaranteed means a full 12-month warranty against defective workmanship and parts failure due to normal usage. That's 9 months to a year better than others. And it's backed up by the only tuner repair service authorized and supervised by the world's largest tuner manufacturer—Sarkes Tarzian, Inc.

Four conveniently located service centers assure speedy in-and-out service. All tuners thoroughly cleaned, inside and out . . . needed repairs made . . . all channels aligned to factory specs, then rushed back to you. They look—and perform—like new.

Prefer a replacement? Sarkes Tarzian universal replacements are only \$10.45, customized replacements \$18.25. Universal replacements shipped same day order received. On customized, we must have original tuner for comparison purposes, also TV make, chassis, and model number. Order universal replacement by part number. Send orders for universal and customized replacement tuners to Indianapolis.

Part #	Intermediate Frequency	AF Amp Tube	Osc. Mixer Tube	Heater
MFT-1	41.25 mc Sound 45.75 mc Video	6GK5	6LJ8	Parallel 6.3V
MFT-2	41.25 mc Sound 45.75 mc Video	3GK5	5LJ8	Series 450 MA
MFT-3	41.25 mc Sound 45.75 mc Video	2GK5	5CG8	Series 600 MA

Genuine Sarkes Tarzian universal replacement tuners with Memory Fine Tuning—UHF Plug in for 82-channel sets—Pre-set fine tuning—13-position detent—HI gain—Lo noise—Universal mounting

FOR FASTEST SERVICE, SEND FAULTY TUNER WITH TV MAKE, CHASSIS, AND MODEL NUMBER, TO TUNER SERVICE CENTER NEAREST YOU



TUNER SERVICE CORPORATION FACTORY-SUPERVISED TUNER SERVICE

MIDWEST.....817 N. PENNSYLVANIA ST., Indianapolis, IndianaTEL: 317-632-3493
(Home Office)

EAST.....547-49 TONNELE AVE., Jersey City, New JerseyTEL: 201-792-3730
(Under New Management)

SOUTH-EAST.....938 GORDON ST., S. W., Atlanta, GeorgiaTEL: 404-758-2232

WEST.....SARKES TARZIAN, Inc. TUNER SERVICE DIVISION
10654 MAGNOLIA BLVD., North Hollywood, CaliforniaTEL: 213-769-2720

Circle 5 on literature card

200%. For the preceding case, the current would have had to be at least 3 amperes and persist for several minutes. In comparison, 90% of the circuit breakers in the graph in Fig.2 would have opened at 2.1 amperes—not in an hour, but in less than a minute. (Most circuit breaker opening times are around 15 seconds. Higher percentage overloads open the unit in even less time.)

From the examples given, it can be seen that *sensitivity* to trouble is sacrificed when using a fuse. The quick action of the circuit breaker to even slight overloads prevents a component from being “cooked,” changing value, or being destroyed and, thus, necessitating expensive repairs.

Breaker Precautions

The circuit breaker, like most products, isn't 100% perfect—it does have a weak point or two. Understanding these limitations can be helpful and may lead to test procedures that will prevent unnecessary servicing problems.

The most important point to be remembered is that the circuit breaker will not successfully handle extremely high short-circuit currents. Remember, even the house circuit breaker has limitations!

The normal circuit breaker has a short-circuit current rating of 12 amperes or less. In some sets, this rating is not adequate, so special construction and a special contact are used to permit normal operation with

currents as high as 25 amperes without circuit breaker or added set damage. Most circuits have sufficient internal impedance to prevent the current from even approaching 12 amperes.

Don't be surprised to learn that a circuit breaker can fall victim to its own actuating medium—current. Recall, however, that the units are engineered to be employed in circuits where excessively high current can't happen because of current limitations imposed by design. Something must be wrong then, because a high percentage of factory returns come back literally burned in two because of excessively high current. This condition can only occur when a lead or a screwdriver is inadvertently shorted from the line to ground. Remember, some wall outlets, if near enough to the junction box or transformer, can deliver as much as 5000 amperes. A screwdriver that has the point melted is proof of the power that is available. No wonder the inside of the circuit breaker suddenly looks like a blown fuse.

It should be pointed out that, although the protector is a low-power device, many times it will accommodate much higher currents than the specified 12 or 25 amperes. However, don't ask it to do so, because the power overload can't help but affect its calibration—and calibrated performance is the device's greatest asset. Some manufacturers of circuit breakers may claim considerably higher short-circuit current

capabilities because of the use of a certain type of contact. Nevertheless, if the contacts must slide against each other, calibration suffers. The safe rule is to not poke that screwdriver into the innards of the set.

There are other points that should be kept in mind when servicing a receiver employing a circuit breaker. First, install a replacement very carefully. Don't allow solder to flow into the unit through a hole in the base; a short (or worse) can be the result. Also, be sure that the solder joint is satisfactory. A cold joint (high resistance) can generate considerable heat which will be conducted into the circuit breaker, thus causing the unit to open. Another point to remember is to not pull wires too tight, causing mechanical distortion of the circuit breaker. Such distortion can change the calibration and could result in a breakdown between the circuit breaker and its cover.

At this point it should be pointed out that it is practically impossible to readjust a circuit breaker without special equipment. Variation of the mechanism for only a few thousandths of an inch within the frame can change the current range considerably. Even an apparently satisfactory readjustment may not be proper after the set is warm, or at different control settings.

Possibly the most important point to remember when replacing a circuit breaker is to use a unit whose characteristics are comparable to those of the original unit. Fig. 3 shows pages from circuit breaker cross-reference charts that enable the user to select the proper unit if the set name and chassis or part number is known. The proper replacement is important; consider that much study and design effort has been spent in selecting the proper breaker range. The engineers involved have made an experienced decision—don't deviate from it.

Conclusion

The information presented in this article should make the service technician more aware of the circuit breaker, its design and function, and most important, how to interpret the evidence of trouble so dramatically represented by a “popped-out” unit. ▲

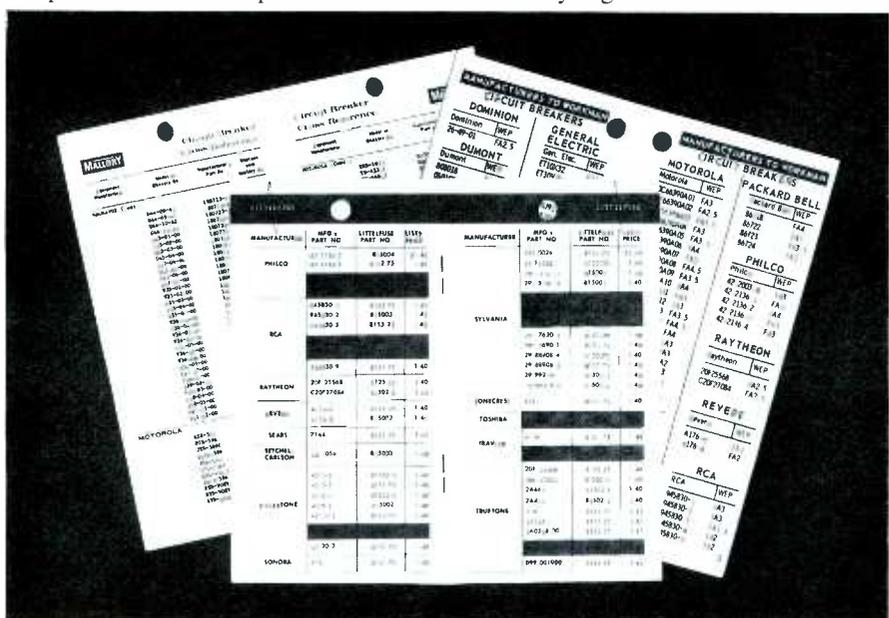


Fig. 3. A circuit breaker cross-reference chart aids replacement.

This little part plays a big role in radio.

This box gives you top revues.



The transistor is no bit player when it comes to radio performance. That's why Delco transistors are manufactured under controlled conditions that assure extremely high reliability.

And why they're thoroughly tested before being placed in the familiar blue and black box.

Delco Radio engineers are leaders in auto radio design and transistor technology. One reason why Delco radios are original equipment on over half of the cars on the road today.

That United Delco box is your guarantee of genuine OEM

quality replacement parts.

Doesn't it make good sense to stock the best for your customers?

Remember these facts when you re-order. And remember, too, that your United Delco supplier handles the most widely advertised, merchandised and recognized name in the parts business.

Next time you think little, think big. Think Delco.

DELCO RADIO, Div. of General Motors, Kokomo, Ind.



MARK OF EXCELLENCE



WHAT'S NEW in public-address systems

BY LOUIS M. DEZETTEL

Driver, horn, driver and horn combination, or column—they are all covered in this review of the speakers currently available for public address applications.

Most of the speakers which are available for public address systems fall into two general categories. One of these is the familiar driver and horn combination. Most of this year's offerings are in the 30-watt class and feature one-piece driver and horn construction, light weight materials, and ease of mounting. The other category is the increasingly popular column speakers. These are characterized by a small vertical angle of dispersion which provides the answer to many problems in acoustics. They are now available in higher power ratings than before.

New Horn Speakers

Since most of them use molded plastic horns, the new horn speakers are light in weight, between 5 lbs and 6½ lbs. They feature ease of installation by incorporating solderless connections and one-knob tightening of both the horizontal and vertical adjustments. All are available with provisions for a built-in, multitap transformer, and some have switches for selecting the taps.

The Atlas AP-30 series of horn speakers (Fig. 1) uses a lightweight, square horn measuring 10" x 9½" x 10½". While it is a metal horn, it has a melamine coating for reso-

nance damping. The dispersion angle is 100° both horizontally and vertically. A 30-watt driver is an integral part of the speaker. The basic AP-30 is available with either an 8-ohm voice coil for public address use, or a 45-ohm voice coil for intercom applications. The AP-30T has a built-in transformer with a tap-selecting switch for operation from a 70-volt line. The AP-30T-25 has a built-in transformer for 25-volt lines.

Similar to the AP-30, but differing in horn contour, is the Atlas APC-30 shown in Fig. 2. Its flattened shape gives it a dispersion angle of 120° horizontally and 60° vertically. A 15-watt version of the AP-30 is the AP-15, available with built-in 70-volt transformer. Another model, the APT-34T is a "twin" version of the AP-30T for bi-directional paging.

An example of Electro-Voice's PA30 series is shown in Fig. 3. With a 30-watt rating, it is also available with a built-in 70-volt transformer (PAT30AT). The rectangular horn is made of molded plastic material. The dispersion angle is 120° in one plane and 90° in the other.

The Jensen VH-100 series of horns (Fig. 4) has a 32-watt rating and a 120° x 90° dispersion angle.

The horn is a nonmetallic molded unit and has the driver built in. The VH-100 has an 8-ohm voice coil, the VH-100V a 45-ohm voice coil, and the VH-100T a built-in 70-volt transformer. The transformer taps are brought to a screwdriver-operated switch so adjustments are easy to make after the unit is installed. This speaker is designed for solderless installation and has the terminals in the base of the mounting foot.

Oxford's contribution to the lightweight, integrated type of horn speaker is their OP-8 shown in Fig. 5. The basic unit weighs 6 lbs. and includes an 8-ohm driver built into the "Implex" plastic horn. It has a 30-watt power rating. A transformer with 70- and 25-volt taps is built in, and a 45-ohm tap to adapt this speaker to intercom use is also available. The OP-6 is a 15-watt version of the same speaker.

With the addition of three sound-deflection vanes, the OP-8 speaker becomes the COP-8 series (Fig. 6). The vanes give it a 120° x 60° dispersion angle instead of the 100° x 100° angle of coverage of the OP-8. Otherwise, the electrical and mechanical specifications are the same as for the OP-8.

The availability of these speakers with a 45-ohm voice coil makes them convenient for use as paging speakers in an intercom system. Since intercom amplifiers usually have low power, the high efficiency of the horn speakers makes them ideal for paging service. The speakers can be used for talk-back when answering the page, if they are not located too high.

New Drivers

Although they are not in the two categories of speakers reported here, two new series of drivers by Electro-Voice are worth mentioning. The 1828 series (Fig. 7) has a 30-watt rating, and the 1829 series is rated at 60-watts. The manufacturer's literature describes them as having lower distortion and flatter frequency response than older units. The suffix "T" in the series stands for a built-in, 70-volt transformer. They have the standard throat with a 1⅜"-18 thread for use with all horns.

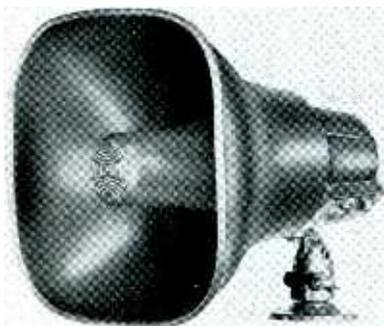


Fig. 1. The Atlas AP-30 is a reflex horn with an integral 30-watt driver and built-in line transformer.

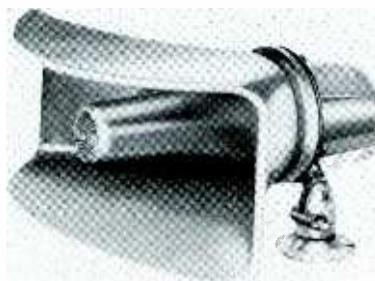


Fig. 2. The Atlas APC-30 has a different coverage pattern; otherwise, it is like the AP-30 series.



Fig. 3. The Electro-Voice PA-30 features a molded plastic horn and a 30-watt, integral driver.

Column Speakers

In the past ten years, a revolution in public address speakers has been taking place in the development of the column speaker. Now, nearly all manufacturers of speakers and enclosures have some column speakers in their line. The most outstanding advantage of the column speaker is its small vertical angle of radiation. When the column is properly installed and directed, this small radiation angle makes possible a fairly even blanket of sound over an entire audience, without blasting those in the front rows.

A stacked Yagi TV antenna has greater sensitivity than a single unit because the angle of the vertical lobe is decreased. In the same manner, by stacking a number of speakers, in phase, the vertical dispersion angle decreases, but the horizontal angle is the same as for a single speaker. This is ideal for covering

an audience situated in a horizontal plane, as in a theatre. So, a column speaker is a long, narrow box standing on end, with a large number of cone-type speakers installed in a vertical row and connected in phase.

To get the best coverage of an audience with column speakers, it is important to use the vertical sound pressure curves which manufacturers of this type speaker supply with their literature. Jensen makes available large, clear plastic charts of equal sound pressure contours for their speaker columns, which they call "Iso sonic" contour charts. By placing the appropriate chart over an elevation view of the auditorium, it is easy to predetermine the exact height and tilt of the speaker that will give the best coverage. Unlike the more familiar polar pattern which shows the relative sound levels at various vertical angles from the major axis, the "Iso sonic" curves locate the points at which the sound has a constant level.

Sound columns use several speakers with soft-cone suspension to produce a husky amount of total power with good frequency response. A single speaker column over the center of a stage, or two, one on each side of the stage, can cover an audience with a sound level that varies no more than ± 1.5 dB from front to back.

It is very important to an effective stage presentation to give the illusion that the sound is coming from the stage. If it doesn't seem to come from the stage, it isn't natural. This dictates the use of high-power speakers placed at or near the stage



Fig. 6. The Oxford COP-8 series has deflection vanes to alter the dispersion angle.

rather than placing small speakers around the perimeter of the audience area. This is another advantage of high-power column speakers—good audience coverage, yet the illusion that the voice and music are coming from the actual source is retained.

No less important are some of the other results of the small angle of vertical dispersion. Proportionately less sound from the speaker reaches the microphone on the stage and acoustic feedback is reduced. This means that higher amplifier levels may be used without spillover. There is also less reverberation from the ceiling, contributing to reduced microphone feedback, as well as more pleasant sound in the listening area. Column speakers are not confined to the reproduction of music. Their flat frequency response (no "peaks") and good low-frequency response improve speech articulation, making them excellent for speech paging.

Another advantage of column speakers is appearance. While they are rather tall, they are neither wide nor deep. When mounted against a



Fig. 4. Available with either an 8- or 45-ohm voice coil, the Jensen VH-100 series is rated at 32 watts.

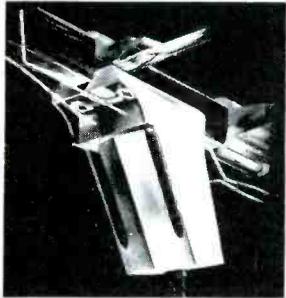
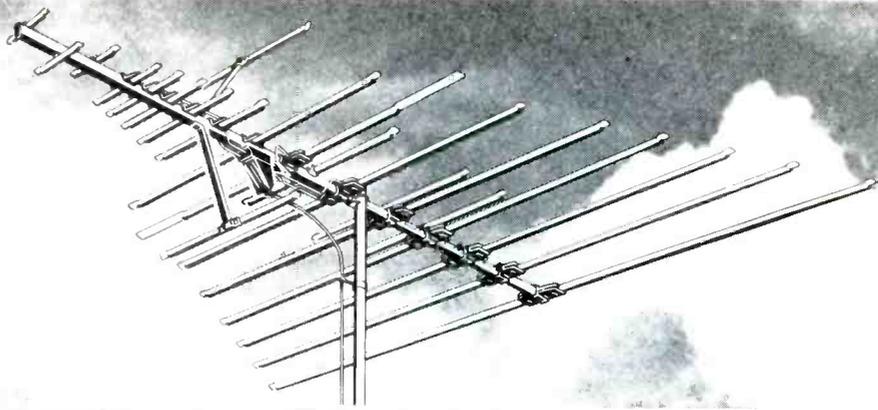


Fig. 5. The Oxford OP-8 has a 30-watt rating. 70-volt and 25-volt built-in transformers are available.

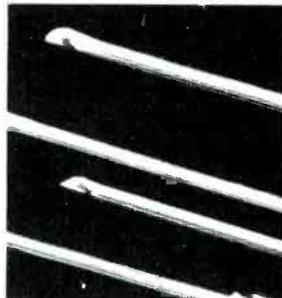


Fig. 7. The Electro-Voice 1828 is a new driver with a 30-watt rating and built-in transformer.

Winegard put these features in to bring the best color out




Download and Pre-Amplifier Housing—permanent housing is built-into the antenna; provides complete weather-proofing for download connector cartridge or pre-amp cartridge.




High Tensile Aluminum Elements; with Gold Anodizing—aluminum alloy has PSI rating of 38,000 compared to 27,000 PSI for alloys used in other antennas. More than 49% stronger and 29% more resistant to bend and wind distortion. Elements and boom are gold anodized for the only permanent protection against corrosion and fading.



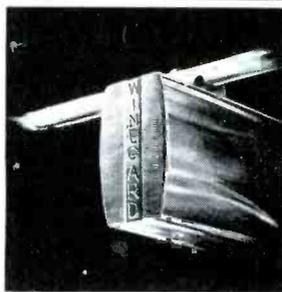Solid State Pre-Amplifiers—incorporate revolutionary new silicon overlay transistors, the best performing and most powerful transistors available for antenna use. Drop into pre-amplifier housing at point of signal interception.




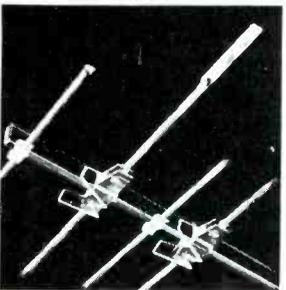Ellipsoidal Boom—the only aluminum shape engineered especially for antenna use; proved far stronger than any other boom design.




Electro-Lens* Director System—patented system absorbs entire signal and focuses it directly onto driven elements for pinpoint directivity.

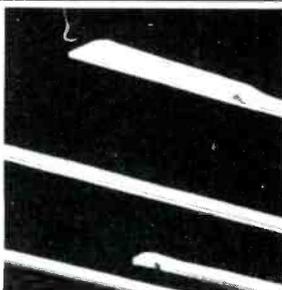
*U. S. Patent No. 2700105
Canada No. 511984



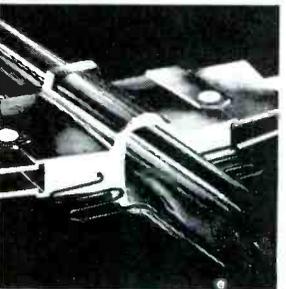
FM Control Element—provide exceptionally high gain on FM bands and provide for the attenuation of FM bands in areas where strong FM signals interfere with tv reception.



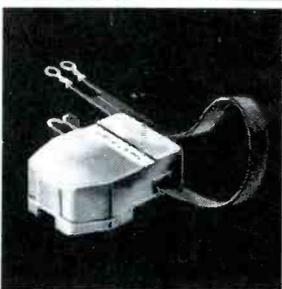Impedance Correlators—patented correlators automatically increase 75 ohm driven elements to 300 ohms to provide 100% signal transfer from antenna to set.



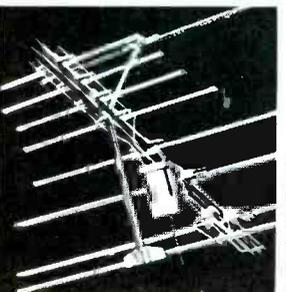CS-285 Band Separator (with printed circuit)—comes at no additional cost with all 82 channel Super Colortrons to separate UHF and VHF signals. Attaches easily to terminals on back of set.



Vertical Resonant Reflectors—UHF reflectors achieve highest realizable gain on channels 14 to 83 because of exceptionally large vertical capture area; more UHF gain than any other 82-channel design.

Antenna Model No.	Registration Number	00000
Installed By	Date	
 Winegard		
24 Month Antenna Replacement Warranty (2 YEAR)		
<small>See Reverse For Details.</small> SAVE FOR YOUR RECORDS		

2-Year Antenna Replacement Warranty—the only antenna in the industry that gives your customer a 2-year replacement privilege.

No wonder so many dealers are selling so many Winegard Super Colortrons so fast.

You're right, that's a lot of features. A lot more than any other antenna ever designed.

But what's really important is what happens when all those features are sandwiched into one super-performing, super-compact antenna.

And just in case you don't know yet, we'll tell you what happens.

First off, you get an antenna so powerful and with such pinpoint directivity (even without solid state pre-amps) that it eliminates ghosts and snow more effectively than anything you've ever seen before.

And when you drop-in an instant-loading pre-amplifier (there are eight to choose from not counting the color spectrum filter) you've got yourself an antenna that does just about anything you want it to do, just about anywhere—

especially when it comes to color tv.

The solid state pre-amplifiers enable you to instantly increase gain on all channels. They let you custom match the Super Colortron to any reception requirement in seconds, using either 75 ohm coax or 300 ohm downlead—and with all connections completely enclosed and protected against the weather.

You can take your choice. There are ultra high gain, low noise 82-channel UHF-VHF-FM pre-amplifiers... VHF-FM pre-amplifiers... UHF pre-amplifiers... and FM pre-amplifiers. And then there's that color spectrum filter. It shuts out electro-magnetic interference... lets only pure TV signals come through for the clearest color pictures ever.

So you see, there's really a lot to talk about when it comes to Super Colortron

antennas, all 14 models—with 7 patents and patents pending.

And that's why we're doing a lot of talking in Life and Newsweek and Sunset. 17 ads, between now and Christmas, telling more than 60,000,000 prospects exactly how remarkable the "transistorized" Super Colortron is.

No wonder so many dealers are selling so many Super Colortrons so fast.

So what are you waiting for?



—biggest, most powerful national advertising campaign in the industry.



WINEGARD COMPANY • 3000 KIRKWOOD STREET • BURLINGTON, IOWA 52601

©Copyright 1967, Winegard Company, Burlington, Iowa

wall, they can be quite inconspicuous in a theatre or auditorium, especially if they are painted to match the decor of the room. Most enclosures are vinyl covered and are easily painted.

The big move lately in column speakers has been to higher and higher power. Jensen has just announced three new ones, each with a rating of 100 watts. Their HFC-84, shown in Fig. 8, is a high-fidelity speaker for indoor use. It contains four 8" speakers of husky design. The cones have resilient-edge suspension, and a supplementary high-frequency radiator is attached to the apex of the cone. The overall frequency response is

50 to 15,000 Hz, and the speaker coverage angles are 100° horizontally, but only 30° in the vertical plane. The input impedance is 8 ohms, but a well in the top of the enclosure accommodates a matching transformer, if one is required. Screw terminals within the well permit installing the transformer without solder.

The Jensen TXC-56 and TXC-84 "total exposure" loudspeaker systems are designed to withstand the extremes of any climate or weather conditions. The TXC-56, the smaller of the two, is designed for outdoor paging purposes where wide-area paging from a single source is required. It contains six 5¼" speakers and has horizontal and vertical coverage angles of 120° and 50°, respectively. The TXC-84 is the size of the HFC-84 (52½" h., 13⅞" w., and 7¼" d.) and is ideal for outdoor concert areas. It has a 95° × 30° dispersion angle and good frequency response, from 50 to 10,000 Hz.

Also in the power race is the Argos "Thunder Column" (Fig. 9), designed specifically for electrically amplified musical instruments. It has a 150-watt rating and contains four Jensen 10" speakers, each with

a magnet weight of 1¼ lbs. This column speaker has a handle for portability.

Summary

The column speakers described here are only a few of the newer ones. Literally dozens of models are available with a wide variety of coverage angles, frequency response, power ratings, etc. You should definitely look into the use of speaker columns for many of your PA installations, and when you do, look over the entire literature of the lines available in your areas. Your local radio and TV parts distributors probably carry several makes.

A review of the latest lines of speakers indicates that there is a trend toward smaller and lighter, horn-and-driver type speakers in which ease of installation is an important feature. Horns with integral drivers are becoming more and more popular, and in column speakers, the trend is in the direction of higher power.

Of course, the requirements of each specific installation are the important considerations, and the regular lines of PA speakers should be considered at all times. It is still true that the reflex horn and driver is the most efficient type of speaker for industrial sound. The electrical-to-acoustical conversion efficiency of a horn is several times that of cone-type speakers and it is not unusual for a 30-watt reflex horn and driver to produce more acoustic energy than a 100-watt sound column using cone speakers. However, horn speakers have one drawback, the low-frequency-cutoff point is a function of the area of the horn mouth.

$$F = \frac{1140}{2\sqrt{3.14A_m}}$$

where,

F = low-frequency cutoff, and
A_m = Area of horn mouth

Air loading on the driver is poor below this frequency and unless a capacitor is connected in series to attenuate low-frequency voltage delivered to the driver, the voice coil may be damaged. Nevertheless, when confined to voice paging or oscillator alarm systems, reflex horns are often the best choice. ▲

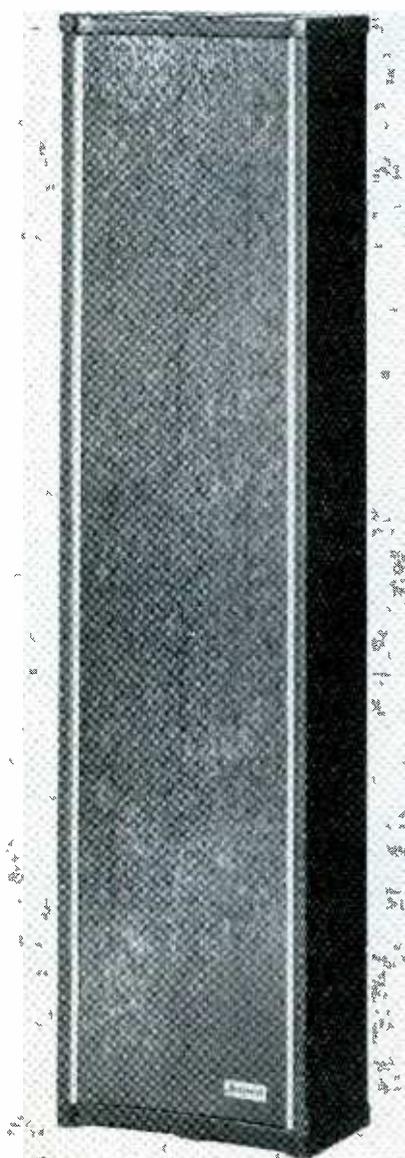


Fig. 8. The Jensen HFC-84 is a 100-watt column speaker with a 30° vertical angle of sound radiation.

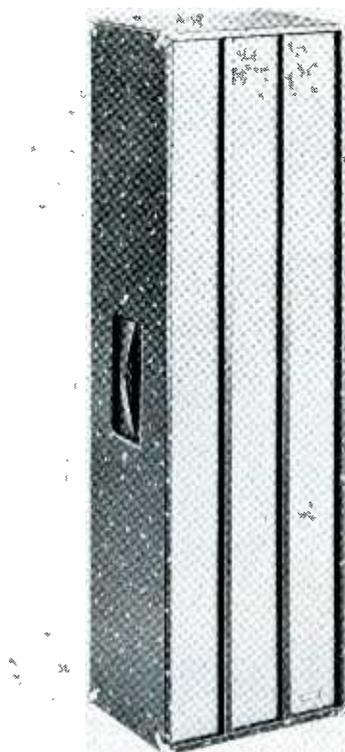


Fig. 9. The Argos "Thunder Column" has a 150-watt rating. It is designed principally for use with electronically-amplified musical instruments.

Customers wear out the Yellow Pages getting to K & B



"We usually ask callers how they located us and they tell us 'through the Yellow Pages,'" say Mr. and Mrs. Karl E. Betz, Sr., owners, K & B General Services, Toledo, Ohio. "We didn't get into Yellow Pages until we'd been in business four years, and right away we noticed the difference. We got a lot of phone calls. We still do, and Yellow Pages is the only advertising we do. We know our ad there is producing business because we keep card files on all repair business and note the source. Roughly, I'd say more than twenty-five percent of our business comes directly from the Yellow Pages."

Advertise for action...



K & B
GENERAL SERVICES

**IF IT CAN BE REPAIRED
WE CAN DO IT**

**WE SERVICE ALL BRANDS
& TYPES OF**

Small Electrical Appliances

- REASONABLE SERVICE CHARGES
- PARTS & SERVICE

**OPEN DAILY 8:30-6:00
SAT. 8:30-4:00**

Free Pick Up & Delivery


248-2822

3129 CHERRY

Customers wear out the Yellow Pages instead of themselves. This ad, under ELECTRIC APPLIANCES - SMALL - REPAIRING, leads them to K & B. Call your Yellow Pages man to plan your program. Find him in the Yellow Pages under ADVERTISING - DIRECTORY & GUIDE.

If you have a fuse problem **BUSS** can help you solve it

For Example . . .

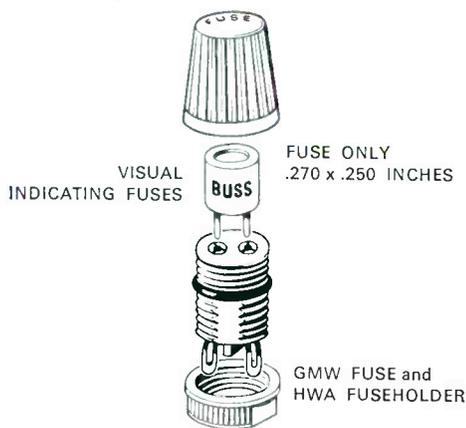

Sub-Miniature FUSEHOLDER COMBINATION


For space-tight applications. Fuse has window for inspection of element. Fuse may be used with or without holder.

Fuse held tight in holder by beryllium copper contacts assuring low resistance.

Holder can be used with or without knob. Knob makes holder water-proof from front of panel.

Military type fuse FM01 meets all requirements of MIL-F-23419. Military type holder FHN42W meets all military requirements of MIL-F-19207B.

For Example . . .

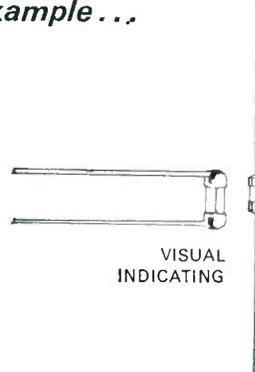

Tron SUB-MINIATURE Pigtail Fuses

BODY SIZE ONLY .145 x .300 INCHES

For use on miniaturized devices, or on gigantic space tight multi-circuit electronic devices.

Glass tube construction permits visual inspection of element.

Smallest fuses available with wide ampere range. Twenty-three ampere sizes from 1/100 thru 15 amps.

Hermetically sealed for potting without danger of sealing material affecting operation. Extremely high resistance to shock or vibration. Operate without exterior venting.

Tell us what you need or . . . Write for BUSS Bulletin SFB.

IN THE COMPLETE BUSS LINE

you'll find the type and size fuse to fit your every need . . . plus a companion line of clips, blocks and holders.



BUSSMANN MFG. DIVISION,
McGraw-Edison Co., St. Louis, Mo. 63107

BRIDGE CIRCUITS

A REVIEW/PART 1

A continuing need for exceptionally accurate measurement of such electrical quantities as resistance, capacitance and inductance has sustained the use of this relatively old circuit. This two-part article will refresh your knowledge of the various designs and applications of the bridge.

BY RUFUS P. TURNER

Material for the following article was adapted from a Howard W. Sams book titled "Bridges and Other Null Devices" by Rufus P. Turner.

The basic bridge circuit was invented by S. H. Christie, an Englishman, who described it in a paper in the February 28, 1833, issue of *Philosophical Transactions*. But the device attracted little attention until 1843, when it was publicized by Sir Charles Wheatstone, from whom it came to be called the Wheatstone bridge, despite Sir Charles's painstaking credit to Christie.

The bridge enables an unknown quantity to be checked directly against a standard which is permanently contained in the circuit. Bridges are used for accurate measurement of such properties as resistance, capacitance, inductance, impedance, and frequency.

The Basic DC Bridge

In the dual voltage-divider circuit shown in Fig. 1, voltage divider R1 supplies a selected fraction (E1) of voltage E_s , while R2 similarly supplies a selected fraction (E2) of voltage E_x . Both E1 and E2 are positive; therefore, the meter deflects downscale when E1 is more positive than E2, upscale when E1 is less positive than E2, and reads zero when $E1 = E2$.


A disadvantage of this design is that both E_s and E_x are constantly under load and therefore may not be able to put out their true open-circuit voltages.

The dual voltage-divider circuit shown in Fig. 1 can be used to compare resistances as well as voltages. Thus, in Fig. 2A, batteries E1 and E2, which are exactly equal in voltage, force currents I1 and I2, respectively, through voltage dividers R1 and R2. The resultant voltage drops E3 (= I1R3), E4 (= I1R4), E5 (= I2R5), and E6 (= I2R6) are proportional to resistances R3, R4, R5 and R6, respectively. At null, $E3/E4 = E5/E6$, so $R3/R4 = R5/R6$. From this relationship, any one of the resistances may be determined in terms of the other three: $R3 = (R4R5)/R6$, $R4 = (R3R6)/R5$, $R5 = (R3R6)/R4$, and $R6 = (R4R5)/R3$. In this way, one unknown resistance may be determined from the values of three accurately known resistances.

Resistance determinations may be made without the two separate batteries; the voltage dividers may be connected in parallel and operated from a single DC source, as shown in Fig. 2B. Here, the current, voltage, and resistance relations are the same as in the preceding example. With Fig. 2B, the basic configuration of the bridge emerges.

Usually, a bridge circuit is drawn in the diamond shape shown in Fig. 2C. Here, R1, R2, R3, and R4 are separate arms of the bridge and correspond to the selected resistances R3 and R4 of potentiometer R1, and to R5 and R6 of potentiometer R2 in Fig. 2A. One arm, such as R1, may be made continuously variable for balancing the circuit to null, and one (such as R2) may be the unknown. The two remaining arms, R3 and R4, then are accurate resistances whose ratio determines the ratio of the unknown (R2) to the standard (R1). Thus, at null the unknown $R2 = (R4/R3) R1$. In bridge terminol-

Fig. 1. The dual voltage-divider circuit measures resistance and voltage.

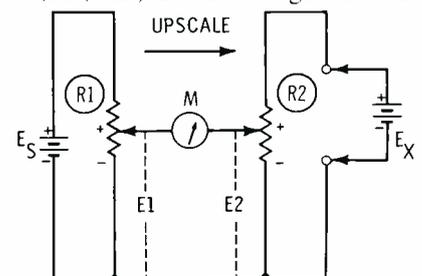

ogy, the power source (such as the battery in Fig. 2C) is termed the *generator*, and the null indicator (such as the center-zero galvanometer in Fig. 2C) is the *detector*.

Basic AC Bridge

As a test instrument, a DC bridge can be used only for the measurement of resistance. Capacitance, inductance, and impedance measurements, however, require that the bridge be powered by alternating current.

Fig. 3 shows the basic configuration of an AC bridge. Note that the circuit is essentially like the DC bridge, except that an AC generator (GEN) has replaced the battery, and an AC null detector (DET) has replaced the center-zero DC galvanometer. The AC detector may be a vacuum-tube (or transistorized) voltmeter, oscilloscope, magic-eye tube, or headphones (with or without an amplifier). Also, the resistance arms of the DC bridge have been replaced with corresponding impedance arms Z_1 , Z_2 , Z_3 , and Z_4 . Calculations of unknown impedance in terms of standard impedance and ratio arms

may be made in the same way described previously for resistance, simply by substituting Z 's for R 's in the formula.

At low (audio) frequencies, an AC bridge also may be used to measure resistance in the manner described for the DC bridge, with the same R formula being used.

Generator and Detector Requirements

For the most efficient bridge operation, the generator (whether AC or DC) must have good output-voltage regulation, and its maximum output voltage must be held low enough to prevent damage to the bridge arms. Moreover, if the generator is of the DC type, its output must be free from ripple. If the generator is of the AC type, its output should exhibit a constant frequency and low distortion.

The detector (whether AC or DC) should have provision for adjusting the response, so that its sensitivity may be increased as null is approached, thereby increasing the closeness to which the bridge may be set. Closeness of setting is enhanced also by a very high detector-input resistance (impedance) with respect

to that of the bridge arms. To sharpen the null response of the bridge, the detector must be sharply tuned to the fundamental frequency if the generator output has significant harmonic content.

In AC bridges, performance is improved by using an isolating transformer between the generator and bridge, and between the bridge and detector. For best performance, these transformers must be well shielded internally.


For a given combination of resistances or impedances in the arms, the sensitivity of a bridge may be increased by raising the generator voltage (bridge signal). However, there is a safe limit beyond which the bridge current becomes excessive and damages the arms. It is for this reason that moderate generator output often is preferred, and the detector sensitivity is increased proportionately, as through AC or DC amplification. But some amplifiers tend to become unstable and susceptible to stray pickup when operated at high sensitivity, so a compromise must be reached between generator voltage and detector sensitivity.

NEW COAX MATCHING TRANSFORMER for Color TV


One transformer for indoor or outdoor use. The Mosley MTR-37 provides a perfect match of 300/75, 75/300 ohm connections. Easily attached to antenna (close to the signal source) or directly to receiver terminals. Solderless. Easy to install.

Write Dept 160 for FREE detailed brochure.

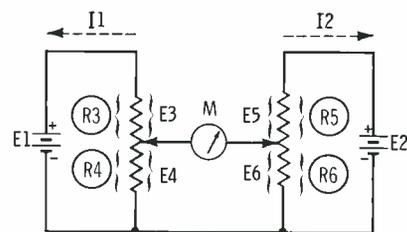
Mosley Electronics Inc. 4610 N. Lindbergh Blvd., Bridgeton Missouri 63042



(A) Two-battery circuit.

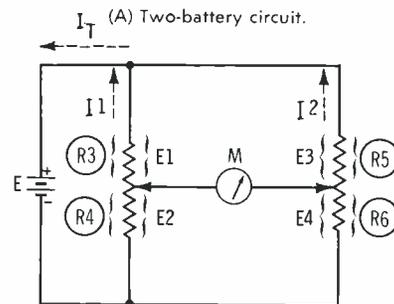

(B) Single-battery circuit.

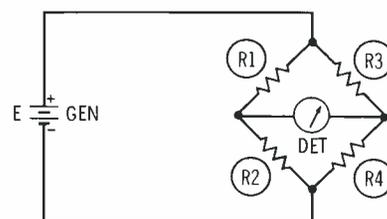

(C) Conventional representation.

Fig. 2. Evolution of the bridge from two-battery circuit to present design.

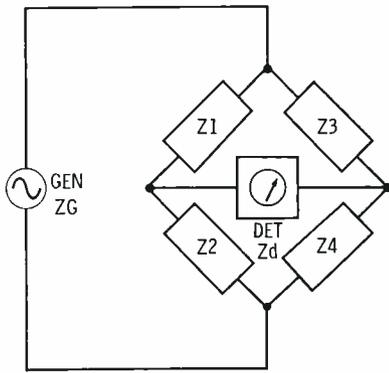


Fig. 3. The basic AC bridge employs AC generator and null detectors.

Maximum sensitivity with a given fixed-output generator and fixed-sensitivity detector is obtained when $R_1 = R_2 = R_3 = R_4 = R_G = R_D$, in the DC bridge, and when $Z_1 = Z_2 = Z_3 = Z_4 = Z_G = Z_D$, in the AC bridge. (The symbol R_G or Z_G is the generator output resistance or impedance; R_D or Z_D is the detector input resistance or impedance.)

Resistance Bridge

Although bridges are used today to measure many different quantities, such as resistance, capacitance, inductance, and frequency, the original bridge was strictly a resistance-measuring device. At present, resistance measurement remains a major function of the bridge. Modern resistance bridges as a group cover the range from 0.01 milliohm to 1000 teraohms—a spread of 10^{20} to 1; and, depending on make, model, and technique, their accuracy can be as close as 0.0001 percent of the indicated resistance value.

Described below are representative resistance bridges from the rudimentary slide-wire type to more complicated varieties.

Basic Slide-Wire Bridge

Fig. 4 shows the most rudimentary resistance bridge circuit. In this arrangement, the variable balancing resistor is a single strand of resistance wire (the slide wire) tautly stretched between points A and B (or wound around a form having a circular cross section) and provided with a sliding contact (the slider). The wire is of uniform cross section and purity, so its resistance is directly proportional to its length.

As the slider is moved along the wire, it divides the latter into two parts; D1, the length from point A to the slider, which has a resistance of R3; and D2, the length from point B to the slider, which has a resistance of R4. Thus, the resistance increases on one side of the moving slider and decreases on the other side.

The bridge is composed of unknown resistance R1 (connected to terminals X-X), standard resistance R2, and the two sections (R3 and R4) of the slide-wire variable resistor. Battery B is the generator, and the center-zero DC galvanometer, M, is the detector. The on-off switch,


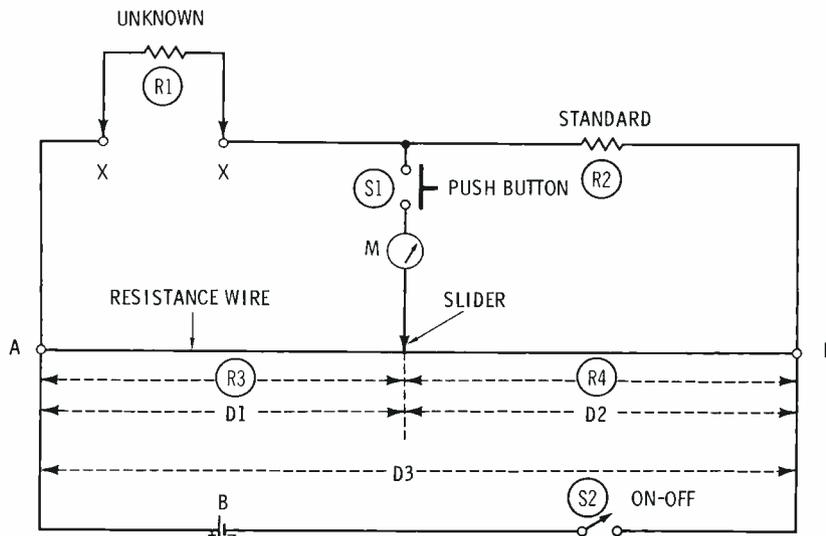


Fig. 4. Basic slide-wire bridge designed for resistance measurements.

look at the tips of these blades

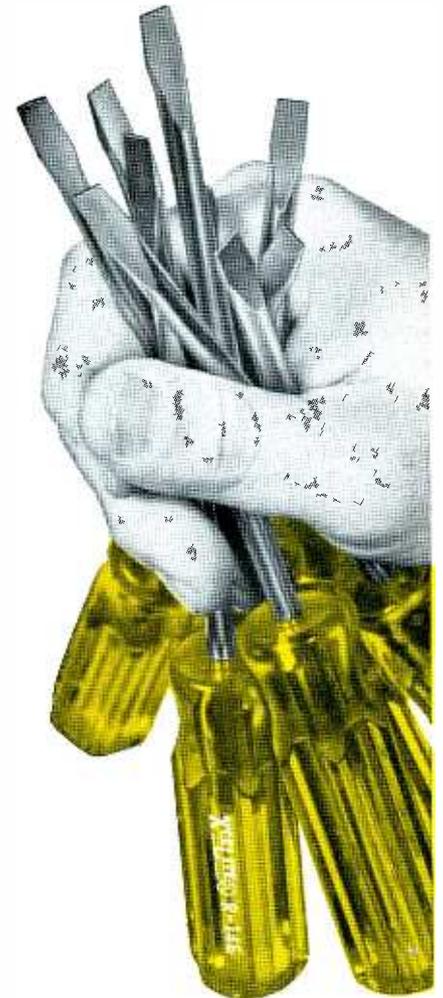

Here's uniformity that's readily apparent and undeniable. Here's precision . . . achieved only through modern production methods, skilled workmanship, close quality control.

All Xcelite screwdrivers are made this way . . . slotted, Phillips, Allen type, Frearson, Bristol, Scrulox . . . fixed handle or interchangeable blade types . . . to fit precisely, preventing damage to fastener or tool.

That's why they're first choice of manufacturers who seek zero defects on the assembly line, of technicians who take pride in their handiwork.

If you service or assemble precision products, look for screwdrivers, nutdrivers, and other precision tools you need in the extensive Xcelite line.

XCELITE®

XCELITE, INC., 18 Bank St., Orchard Park, N.Y. 14127
In Canada contact Charles W. Pointon, Ltd.

Circle 10 on literature card
February, 1968/PF REPORTER 19

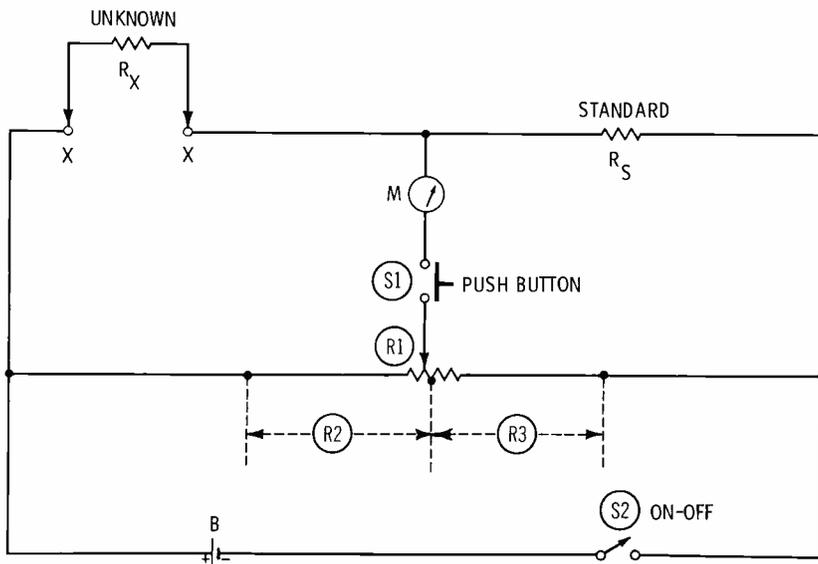


Fig. 5. Slide-wire resistance bridge employing a potentiometer.

S2 permits disconnection of the battery when the bridge is idle. The pushbutton switch, S1, allows the galvanometer to be cut into the circuit momentarily to check the state of balance, thus protecting the galvanometer from continuous exposure to excessive unbalance current.

With the unknown resistance (R_X) connected to terminal X-X, the bridge is balanced by moving the slider along the wire until zero deflection is shown on the galvanometer. At this null, $R_1/R_2 = R_3/R_4$, and from this relationship the unknown may be determined in terms

of the standard: $R_1 = R_2 (R_3/R_4)$. From this, it is clear that the slide wire provides the ratio arms of the circuit.

The total resistance of the slide wire is unimportant to the calculation. So also are the two resistance values on each side of the slider. Distances D_1 and D_2 may be measured in inches or centimeters and used in the calculation in place of the actual resistances R_3 and R_4 . Thus: $R_1 = R_2 (D_1/D_2)$. For this reason, the basic slide-wire bridge is convenient for emergency measurements of resistance, since it requires only a standard resistor and a length of bare resistance wire stretched along a meter stick or yardstick, in addition to a battery and DC meter.

Sometimes it is more convenient to read the position of the slider with respect to the total length (D_3) of the wire than to measure D_1 and D_2 separately. In such an instance: $R_1 = R_2 [D_1/(D_3 - D_1)]$.

It is apparent from the preceding equation that the unknown (R_1) is equal to the standard (R_2) when null occurs with the slider halfway between A and B (i.e., $D_1 = D_2$, and $D_1/D_2 = 1$). Also the slider must move to the right of center when R_1 is greater than ($>$) R_2 , and to the left of center when R_1 is less than ($<$) R_2 . In practice, a meter stick or similar linear scale is usually mounted under the wire for reading D_1 and D_2 from the position of the slider.

If the wire is long (say 1 meter), little difficulty is experienced in measuring resistance over the range $0.01R_2$ to $100R_2$, provided a sensitive galvanometer is used. Unless the wire has reasonably high resistance, however, the current may heat it and impair the accuracy of measurement.

Slide-Wire With Potentiometer

The modern slide-wire bridge substitutes a potentiometer for the single strand slide wire of the basic circuit. Otherwise the circuit is unchanged. In Fig. 5, for example, potentiometer R_1 is the "slide-wire" element, and its slider divides the total resistance R_1 into the bridge ratio arms R_2 and R_3 .

As before, at null the unknown (R_X) is determined in terms of the standard: $R_X = R_S (R_2/R_3)$.

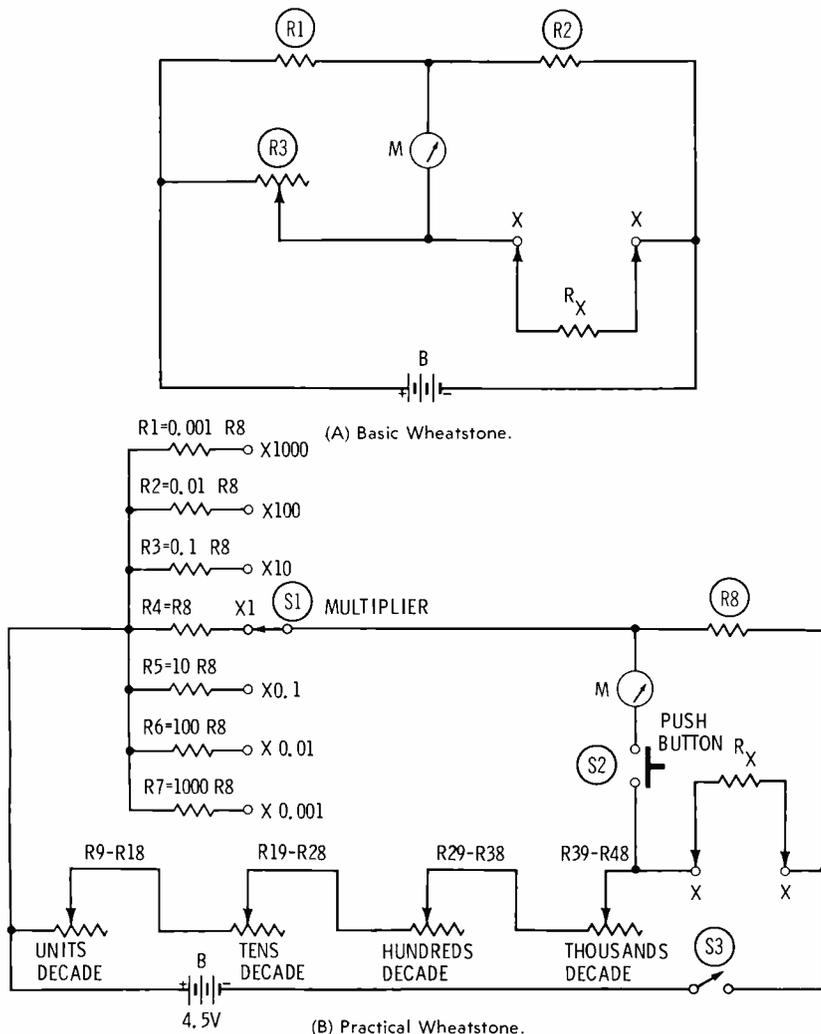


Fig. 6. The Wheatstone bridge is suitable for general purpose applications.

Compare Color Generators

look at the rest... and you'll buy the best, new B&K model 1245

The all solid-state B&K Model 1245 Color Generator duplicates the waveforms transmitted by a color TV station.


Adherence to these waveforms makes it easy to converge the color tube, check sync and make other raster adjustments... and the color generator with station quality signal will be able to sync next year's sets. Generators with compromise waveforms do not give you this obsolescence protection.

Here are oscilloscope photographs from the outputs of two typical competitive color generators, one transistorized and one tube type, and the B&K Model 1245. The detailed analysis with each photograph shows a few of the reasons why you'll save time and effort with B&K.


COLOR

CROSSHATCH

STANDARD STATION SIGNAL

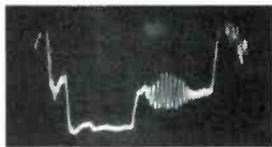


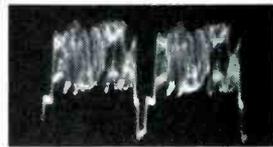One horizontal sync pulse with its color burst.




Two lines showing horizontal sync pulse with black and white tv signal.

TRANSISTORIZED B&K MODEL 1245

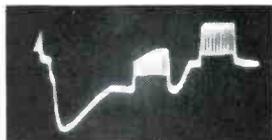


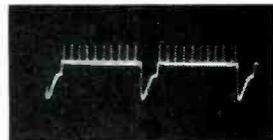Good duplication of station signal including back porch. If the set won't sync, the set is defective.




Well defined back porch on horizontal sync pulse permits accurately setting color killer and almost eliminates need to adjust brightness and contrast.

TRANSISTORIZED GENERATOR A

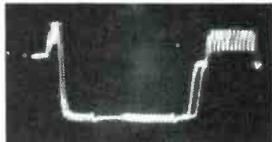


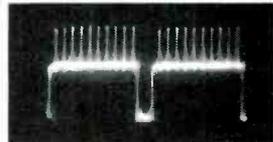No back porch causes unstable color sync. Burst amplitude compression may permit sync on wrong color bar.




Square wave horizontal sync pulse with no back porch and poor dc coupling forces adjustments of brightness, contrast & fine tuning to obtain usable pattern.

GENERATOR B

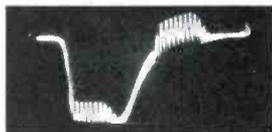


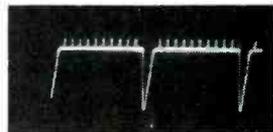No back porch; color information on top of sync-pulse makes sync difficult on some sets.



Complete absence of any back porch necessitates readjustment of brightness, contrast and fine tuning to obtain a usable pattern.

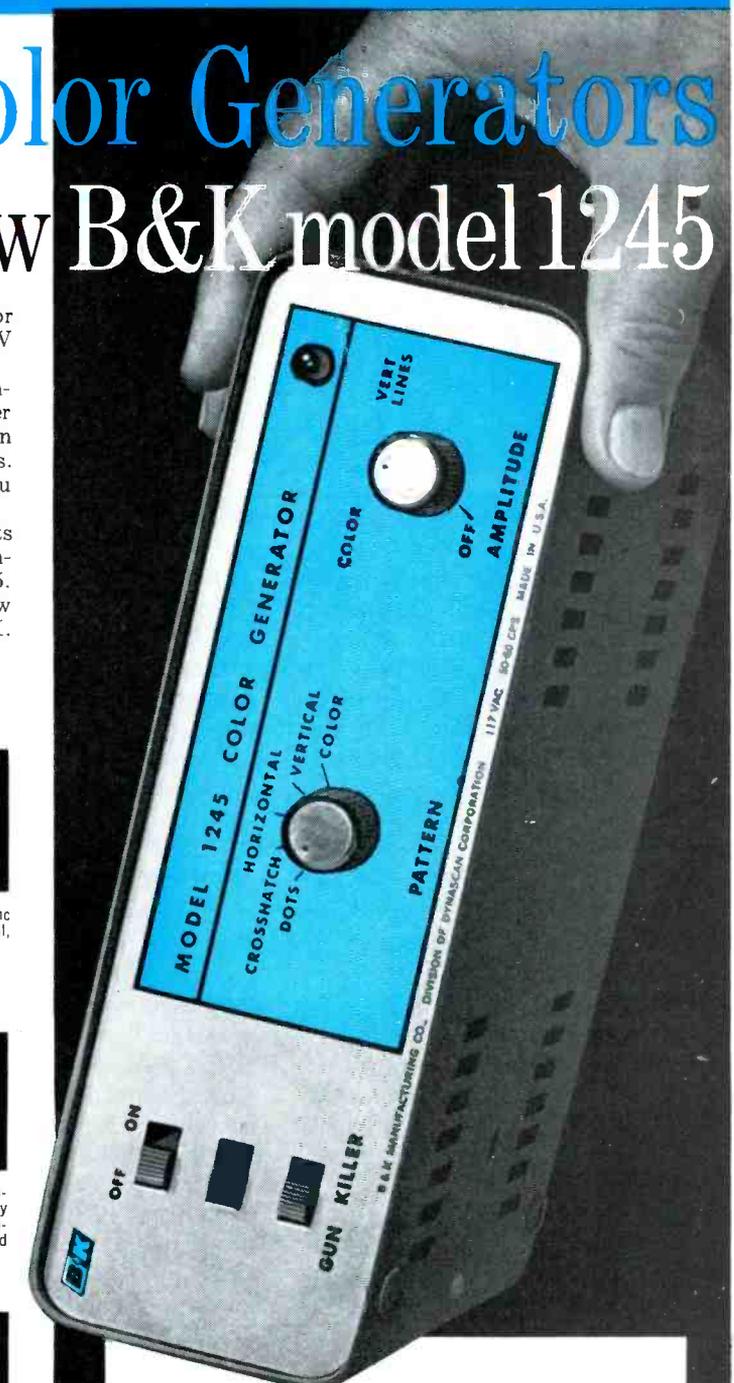See your B&K Distributor for a demonstration or write for Catalog AP22.



For the first time, with the no-compromise waveforms from the B&K Model 1245, it is possible to accurately set the color killer threshold control with a color generator.

The miniature size and convenience of the Model 1245 match its performance. It provides crystal-controlled keyed rainbow color bar display, and dot, crosshatch, horizontal line and vertical line patterns as well as gun killer controls that will work with any picture tube. Size only 2 7/8 x 8 1/2 x 8 7/8". Net \$134⁹⁵.

A DIVISION OF DYNASCAN CORPORATION

1801 W. Belle Plaine, Chicago, Illinois 60613

WHERE ELECTRONIC INNOVATION IS A WAY OF LIFE

Export: Empire Exporters, Inc., 123 Grand Street, New York, N.Y. 10013



Circle 11 on literature card

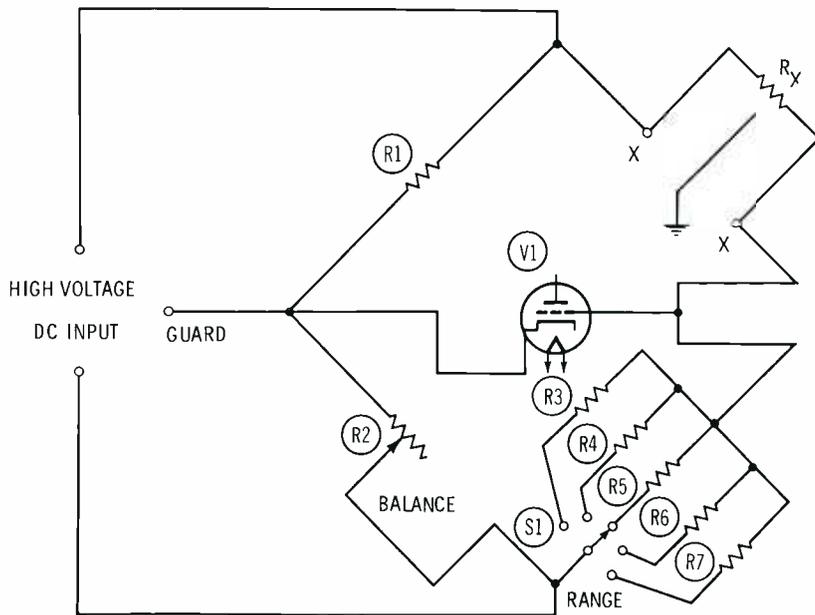


Fig. 7. Bridge design for measuring resistances in the megohm range.

A dial reading directly in ohms, based upon the preceding equation, usually is attached to the potentiometer and calibrated by means of a number of accurately known resistors connected successively to the circuit in place of R_X . When, instead, the dial reads the resistance setting (R_2) of the potentiometer (as is usual with modern 10-turn potentiometers), $R_3 = R_1 - R_2$, and the unknown resistance is determined from a modification of the equation: $R_X = [R_2 / (R_1 - R_2)] R_s$ where,

R_X is the unknown resistance,

R_s is the standard resistance,

R_1 is the total resistance of the potentiometer,

R_2 is the resistance setting of the potentiometer at null.

The slide-wire bridge has the advantage of simplicity, since it requires a minimum of parts. However, with a single-turn potentiometer of commercial grade, its resistance coverage with any given standard resistor (R_s) is restricted for accurate reading, to 100:1 (i.e., from $0.1R_s$ to $10R_s$ —thus, 0.1-10 ohms, 10-1000 ohms, 1K-100K, etc). Also, the divisions tend to become crowded in some parts of the dial.

The Wheatstone Bridge

Many of the disadvantages of the slide-wire bridge are resolved by the modern Wheatstone bridge. This is the classic bridge for general-purpose resistance measurement.

Fig. 6A shows the basic Wheatstone circuit. In this arrangement, a rheostat, R_3 , has been substituted for the potentiometer of the slide-wire bridge. A dial attached to R_3 reads directly the resistance setting of this rheostat. R_1 and R_2 are the ratio arms of the bridge. The unknown resistance, R_X , is connected

to terminals X-X. At null, $R_X / R_3 = R_2 / R_1$, from which: $R_X = R_3 (R_2 / R_1)$.

Thus, the setting of rheostat R_3 simply is multiplied by the bridge ratio (R_2 / R_1) to determine the value of R_X . In practice, various values of R_1 and R_2 are switched into the circuit to provide standard multipliers from X0.001 to X1000.

The total resistance of the rheostat usually is 10,000 ohms, but other values, such as 1000 or 5000 ohms, sometimes are used. A logarithmic taper for the rheostat winding provides a dial having uniform spacing throughout its range.

Fig. 6B shows a typical circuit of a practical Wheatstone bridge. Here, the rheostat has been replaced with a set of resistance decades (R_9 to R_{48}). This type of balance control allows closer settings and readings than are possible with a dial-calibrated rheostat; it covers the range from 1 ohm to 11111 ohms in 1-ohm steps.

The bridge ratio is established by resistor R_8 in combination with any resistor in the R_1 - R_7 group selected by means of switch S_1 . At null, the resistance setting of the decades is multiplied by this ratio to obtain the unknown resistance, R_X . The multipliers provided are 0.001, 0.01, 0.1, 1, 10, and 1000; and these multipliers applied to the full resistance range of the decades (1-11,111 ohms) gives the bridge a measurement range of 0.001 ohm to 11,111 megohms.

Various commercial bridges use other methods of ratio-arm switching than that shown in Fig. 6B. In some instruments, for example, the ratio resistors are switched in pairs, rather than against single resistors such as R_8 .

The Megohm Bridge

Very high resistances (several megohms to several teraohms) may be measured with special bridges. While the coverage of a standard bridge may be extended into the megohm range, the very high resistance standards required for each extension are usually less accurate than lower resistance ones, and the extreme division of voltage between at least two of the bridge arms demands


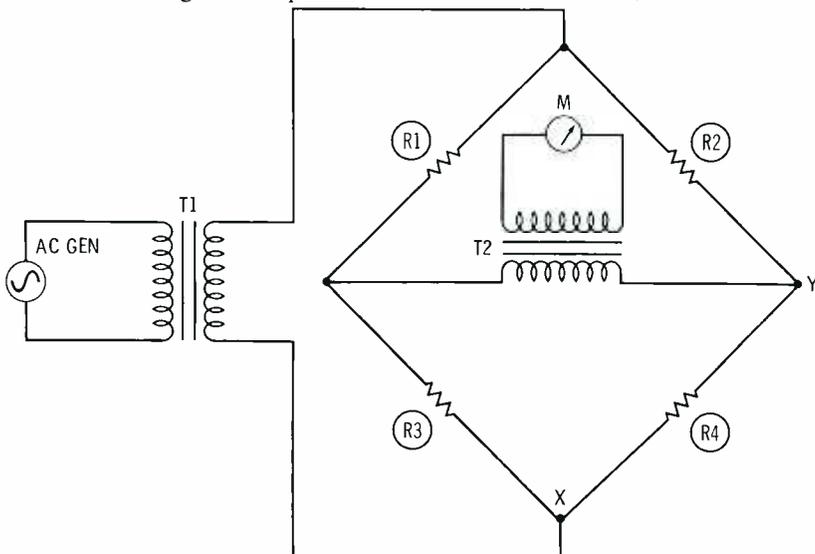



Fig. 8. The AC resistance bridge offers high sensitivity.

• Please turn to page 58

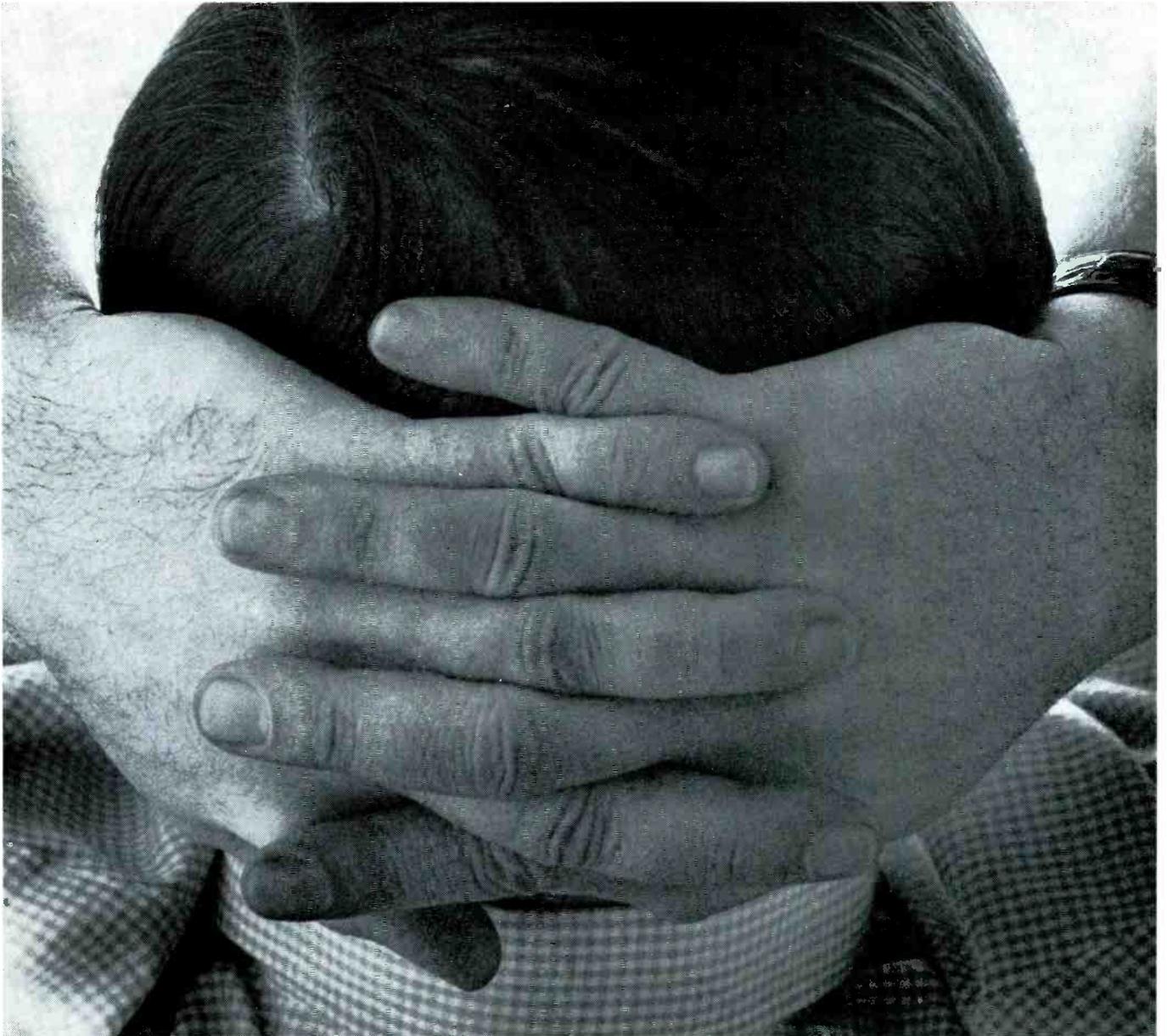

**The simplest and most effective demonstration
of color TV fine tuning there is.**

RCA Automatic Fine Tuning.

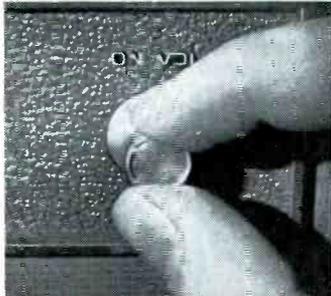

Color TV that fine-tunes itself
when you turn it on. All you do is
sit back and write the order.

RCA



get the service data you need in PHOTOFACT® COMPLETE COLOR TV COVERAGE

283 Here are the PHOTOFACT sets with Color TV coverage from the beginning in 1954 through 1967:

1	31	61	91	121	151	181	211	241	271	301	331	361	391	421	451	481	511	541	571	601	631	661	691	721	751	781	811	841	871	901
2	32	62	92	122	152	182	212	242	272	302	332	362	392	422	452	482	512	542	572	602	632	662	692	722	752	782	812	842	872	902
3	33	63	93	123	153	183	213	243	273	303	333	363	393	423	453	483	513	543	573	603	633	663	693	723	753	783	813	843	873	903
4	34	64	94	124	154	184	214	244	274	304	334	364	394	424	454	484	514	544	574	604	634	664	694	724	754	784	814	844	874	904
5	35	65	95	125	155	185	215	245	275	305	335	365	395	425	455	485	515	545	575	605	635	665	695	725	755	785	815	845	875	905
6	36	66	96	126	156	186	216	246	276	306	336	366	396	426	456	486	516	546	576	606	636	666	696	726	756	786	816	846	876	906 Sept.
7	37	67	97	127	157	187	217	247	277	307	337	367	397	427	457	487	517	547	577	607	637	667	697	727	757	787	817	847	877	907 Sept.
8	38	68	98	128	158	188	218	248	278	308	338	368	398	428	458	488	518	548	578	608	638	668	698	728	758	788	818	848	878	908 Sept.
9	39	69	99	129	159	189	219	249	279	309	339	369	399	429	459	489	519	549	579	609	639	669	699	729	759	789	819	849	879	909 Sept.
10	40	70	100	130	160	190	220	250	280	310	340	370	400	430	460	490	520	550	580	610	640	670	700	730	760	790	820	850	880	910 Sept.
11	41	71	101	131	161	191	221	251	281	311	341	371	401	431	461	491	521	551	581	611	641	671	701	731	761	791	821	851	881	911 Sept.
12	42	72	102	132	162	192	222	252	282	312	342	372	402	432	462	492	522	552	582	612	642	672	702	732	762	792	822	852	882	912 Oct.
13	43	73	103	133	163	193	223	253	283	313	343	373	403	433	463	493	523	553	583	613	643	673	703	733	763	793	823	853	883	913 Oct.
14	44	74	104	134	164	194	224	254	284	314	344	374	404	434	464	494	524	554	584	614	644	674	704	734	764	794	824	854	884	914 Oct.
15	45	75	105	135	165	195	225	255	285	315	345	375	405	435	465	495	525	555	585	615	645	675	705	735	765	795	825	855	885	915 Oct.
16	46	76	106	136	166	196	226	256	286	316	346	376	406	436	466	496	526	556	586	616	646	676	706	736	766	796	826	856	886	916 Oct.
17	47	77	107	137	167	197	227	257	287	317	347	377	407	437	467	497	527	557	587	617	647	677	707	737	767	797	827	857	887	917 Nov.
18	48	78	108	138	168	198	228	258	288	318	348	378	408	438	468	498	528	558	588	618	648	678	708	738	768	798	828	858	888	918 Nov.
19	49	79	109	139	169	199	229	259	289	319	349	379	409	439	469	499	529	559	589	619	649	679	709	739	769	799	829	859	889	919 Nov.
20	50	80	110	140	170	200	230	260	290	320	350	380	410	440	470	500	530	560	590	620	650	680	710	740	770	800	830	860	890	920 Nov.
21	51	81	111	141	171	201	231	261	291	321	351	381	411	441	471	501	531	561	591	621	651	681	711	741	771	801	831	861	891	921 Nov.
22	52	82	112	142	172	202	232	262	292	322	352	382	412	442	472	502	532	562	592	622	652	682	712	742	772	802	832	862	892	922 Nov.
23	53	83	113	143	173	203	233	263	293	323	353	383	413	443	473	503	533	563	593	623	653	683	713	743	773	803	833	863	893	923 Nov.
24	54	84	114	144	174	204	234	264	294	324	354	384	414	444	474	504	534	564	594	624	654	684	714	744	774	804	834	864	894	924 Dec.
25	55	85	115	145	175	205	235	265	295	325	355	385	415	445	475	505	535	565	595	625	655	685	715	745	775	805	835	865	895	925 Dec.
26	56	86	116	146	176	206	236	266	296	326	356	386	416	446	476	506	536	566	596	626	656	686	716	746	776	806	836	866	896	926 Dec.
27	57	87	117	147	177	207	237	267	297	327	357	387	417	447	477	507	537	567	597	627	657	687	717	747	777	807	837	867	897	927 Dec.
28	58	88	118	148	178	208	238	268	298	328	358	388	418	448	478	508	538	568	598	628	658	688	718	748	778	808	838	868	898	928 Dec.
29	59	89	119	149	179	209	239	269	299	329	359	389	419	449	479	509	539	569	599	629	659	689	719	749	779	809	839	869	899	929 Dec.
30	60	90	120	150	180	210	240	270	300	330	360	390	420	450	480	510	540	570	600	630	660	690	720	750	780	810	840	870	900	930 Jan.

STAY AHEAD IN COLOR TV SERVICING—

JOIN the P.O.M. (Photofact-of-the-Month) CLUB!

AND OWN THE COMPLETE PHOTOFACT COLOR TV LIBRARY

NOW! Only \$10 per month brings you 20% MORE PHOTOFACT coverage to keep you current—and you save more than \$60 per year!

- Get 6 new Photofact Sets each month
- 6 to 9 Color TV Folders monthly
- Covers at least 50 new chassis
- Includes b & w TV, FM-AM, AC-DC, Stereo Hi-Fi, Phonograph, and Record Changer models

GET GOING IN
COLOR TV!

GET THIS BIG "BONUS"! Now exclusively for P.O.M. Club members—a minimum of 10 "advance" TV schematics (mostly color) with each month's issue! Keeps you ahead on new model releases. Extra: Special File Cabinet deal with trial 6-month subscription to the P.O.M. Club.



JOIN
P.O.M.

SEE YOUR SAMS DISTRIBUTOR FOR FULL INFORMATION, OR MAIL THE COUPON TODAY...

HOWARD W. SAMS & CO., Dept. PFF-2
4300 W. 62nd St., Indianapolis, Indiana 46206

- Send Photofact-of-the-Month Club details
- Send full details on Library Offer and Easy-Buy Plan
- Send FREE 1968 PHOTOFACT Cumulative Index

My Distributor is _____

Shop Name _____


Attn.: _____

Address _____


City _____ State _____ Zip _____

Circle 12 on literature card

INTERMITTENTS ARE A CHALLENGE

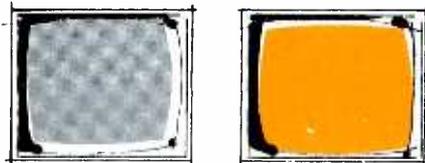

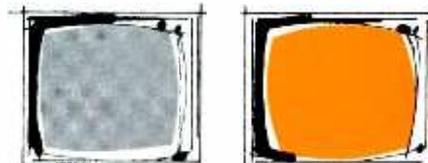Now you see them, now you don't. Although many intermittent troubles appear to be related to the supernatural, you do not have to be a magician to cure them—simply follow the servicing methods outlined here.



BY DAVID HELD AND J. W. PHIPPS

A lot of valuable service time can be consumed in locating the defect that is causing an intermittent trouble symptom. Much of this time can be saved by employing a few test procedures that have proven particularly successful for uncovering intermittent defects. In the following paragraphs, we'll discuss those procedures, along with test equipment requirements and case histories of intermittent trouble symptoms.

Most service shops already possess the test equipment necessary for coping with intermittents: A VTVM or VOM for voltage and resistance measurements, an oscilloscope for waveform checking and monitoring, a signal generator for signal substitution, and a variable-voltage isolation transformer.

In addition to the normal test equipment, there are other gadgets and devices that can aid in the solution of an unusually difficult intermittent trouble. These aids will be mentioned next as we analyze the general test procedures for uncovering intermittent defects.

General Test Procedures

Nearly all intermittent defects fall into one of two categories: either the symptom appears immediately or shortly after the receiver is turned on, or it does not appear until the receiver has operated for an hour or longer. In either case, the first step is to localize the defect to a specific section or circuit by carefully analyzing the trouble symptom and then performing such troubleshooting functions as voltage and waveform checks, signal substitution, etc.

Although the customer may have given a detailed account of the trouble symptom, it is usually advantageous to witness the symptom(s) yourself before doing any trouble-

shooting. Often, a single detail that has been overlooked or left out of the customer's description of the trouble symptoms can be the one that pinpoints the trouble. In any event, have a look yourself.

To save time and prevent unnecessary monitoring of intermittent defects that appear only after extended receiver operation, speed up the process by focusing a heat lamp on the chassis or suspected circuit area, or place a blanket over the cabinet while the receiver is operating. Either method will increase the ambient temperature of the circuitry and cause "premature" breakdown of a heat-sensitive component. Slow intermittent defects can also be speeded up or triggered by increasing the line voltage applied to the receiver—a function of the previously mentioned, variable-voltage isolation transformer. No matter which method you use, the primary purpose is to produce the defect so that you can analyze the symptom(s) and, thus, more accurately localize the cause of the trouble to a specific section or circuit. If necessary, supplement your analysis with signal tracing (scope is best) and/or signal substitution (signal generator).

Once you have tentatively localized the trouble to one particular section or circuit, you may wish to add weight to your conclusion by performing a few preliminary comparative voltage and/or waveform checks within the suspected section or stage before attempting to isolate the trouble to a specific component. Obviously, when dealing with intermittent defects that appear almost immediately after the receiver is turned on, you must perform measurements very quickly before the defect occurs. Once the trouble symptoms appear, perform the same voltage and/or waveform checks again; then compare the "before"

and "after" measurements, carefully noting the implications of any differences in the readings.

Concurrent with voltage and/or waveform checks, perform a quick but thorough visual examination of the suspected section or circuit looking for obvious indications of trouble such as burned resistors, loose wires, poor solder connections, leakage from electrolytics, etc. Also, be alert for the usual odors associated with the failure of such components as selenium rectifiers, thermistors, transformers, etc.

Assuming that you have accurately localized the intermittent defect to one particular circuit, you are now ready to isolate the trouble to the defective component. This can occasionally be accomplished by voltage and resistance measurements alone; however, such readings normally only confirm that the defect lies within a specific circuit, leaving more than one component as the possible suspect. Also, in many instances, the application of the VTVM or VOM probe to the circuit will temporarily "cure" the intermittent, thus hiding it. Although the scope will disturb the circuit conditions less than the VTVM or VOM in most situations, it too can only confirm that you are searching for the defect within the correct circuit. At this point you can replace all suspected components in the circuit, or further isolate the defective component by applying the techniques discussed in the following paragraphs.

Capacitors

Probably the most effective method for pinpointing a defective capacitor is to either heat or cool the capacitor within the circuit—the choice depending on whether or not the trouble symptom is present. If the trouble symptom is present, applying some form of cooling mist



Test your MATV profit potential.

The design and installation of 82-channel Master Antenna Television Systems can be one of the most lucrative opportunities open to the modern service dealer. Potential customers include everyone from

average homeowners to apartment complexes. However, your choice of equipment often dictates the difference between winning and losing a bid... the difference between trouble-free installations

and frustrating callbacks... and the difference between handsome returns and financial headaches. It is your business, but are you making the most profitable choice?

You have an obvious advantage in selling and pricing a system when the entire system, from antennas to amplifiers to cable to tapoffs, was designed and built to function as one integrated unit.

1. Who has the industry's only true 82-channel master antenna system?

In the age of color, the antenna is king. Customers aren't satisfied with anything less than the finest color reception available. Especially when it's available at no extra cost.

2. When you need the highest gain 82-channel color antenna you can get, where do you go?

On-channel amplification is the most economical means of providing both VHF and UHF in small and medium sized systems. When you're going for economy—why not go all the way?

3. Which solid-state color distribution amplifiers provide the most economical ON CHANNEL amplification?

Less loss requires less amplification and lower cost systems—doubly important in 82-channel systems where UHF cable losses can be staggering with ordinary coax.

4. What is the lowest loss RG/59 type coaxial cable designed for 82-channel master antenna systems?

Most 82-channel tapoffs have much higher losses on UHF—where you can least afford it. But wall taps with no additional UHF loss are like money in the bank.

5. Which 82-channel wall tapoffs give you the same low losses on UHF as VHF?


Why pay premium prices for 82-channel splitters, line taps, wall taps, matching transformers, etc.—when one line gives you all 82-channel distribution equipment at no extra cost?

6. Who has the most complete line of 82-channel master antenna distribution system equipment?

Score yourself.



1. Channel Master MATV

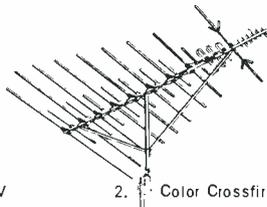

2. Color Crossfire 82



3. Color Amps



4. Color Duct 82



5. U-V Wall Tapoffs



6. U-V Distribution Equipment

You guessed it.
CHANNEL MASTER
Master Antenna Television Systems

You score extra MATV profits every time you choose Channel Master. If you aren't picking Channel Master—your profits

can be improved. See your Channel Master distributor or write to Channel Master, Ellenville, New York 12428.

to the suspected capacitor will cause the symptom to disappear if the capacitor is heat-sensitive and actually intermittently defective. If the trouble symptom is not present, applying the heat of a soldering iron near the suspected capacitor will produce the symptom if the capacitor is the culprit causing the trouble. Of course, care must be exercised so that excessive heat does not destroy capacitors that were *not* originally defective. Suspected electrolytic capacitors should be replaced with a known good capacitor and the receiver then operated under controlled, excessive ambient temperature for a short period of time. If you have selected the correct defective electrolytic, the trouble symptom will not reappear.

Resistors

Intermittently defective resistors can best be uncovered by measuring the voltage across them and then calculating the resistance using Ohm's law (provided the current is known). If the current in the circuit is not known, an alternate method is to turn the receiver off after the trouble symptom has appeared and quickly check the value of the resistor before it cools down. Open or increased values are the most common intermittent defects displayed by resistors.

Tubes and Transistors

Intermittent defects within tubes can be uncovered by checking the tube in a mutual conductance-type tube tester. This usually involves monitoring the testing for a period of time. Emission-type tube testers

are useful only for uncovering intermittent shorts. It is much quicker to substitute the suspected tube and then "cook" the receiver.

Perhaps the quickest check of a suspected intermittently defective transistor is to connect it to an in-circuit transistor tester while the trouble symptom is present (many times this will cause the symptom to disappear, thus quickly pinpointing the trouble). Switch the function switch to "AC Beta" and monitor the meter reading while applying cooling mist to the transistor. Either the meter reading will change drastically toward a high beta reading, or the trouble symptom will disappear. Both results indicate that the transistor is defective and should be replaced. An out-of-circuit transistor tester and cooling mist can be used in the same manner (Fig. 1) except, of course, you don't have the double (and more positive) check of the actual trouble symptom disappearing while the meter reading changes.

Often, while trying to localize the intermittent trouble to a section or stage, touching the generator lead to a transistor's base will cause the trouble symptom to disappear. In many instances this can indicate a bad transistor, while in others it merely confirms a bad component in the transistor base circuit. The same results are obtained when a scope probe is applied to the element of a transistor.

Transformers

Defects related to IF transformers can usually be isolated by careful probing and/or wiggling of the wir-

ing lugs and shield can while monitoring voltage and/or resistance readings. Of course, in some cases such careful manipulations can also cause the trouble symptom to disappear, thereby pinpointing the actual defect without the aid of voltage or resistance readings.

With other type transformers, troubleshooting for intermittents is usually limited to voltage and/or resistance checks and close visual inspections supplemented by careful probing of terminal connections, etc. Any suspected solder joints and connections should be resoldered, paying particular attention to those on printed-circuit boards.

Case Histories

The foregoing paragraphs have been devoted to a general discussion of intermittent defects. Now, let's direct our attention to more specific problems by reviewing a few case histories.

Intermittent Radio

Mr. Allen, a gray-haired retired railroader, set the clock radio down on the shop counter and bellowed "They just don't build these things the way they used to. I remember when you could buy one that . . ."

Not wishing to hear Mr. Allen's often-repeated tales of the "good ole bargain days," shop owner Ed Stagley interrupted him with "What's the trouble with your radio Mr. Allen?"

"If I knew what was wrong with the thing, I'd open up an establishment down the street and run you out of business," retorted Mr. Allen, with a twinkle in his gray eyes that betrayed his joy at poking barbs at Ed. "I was listening to the 6 o'clock news and the thing just went dead. I fiddled around with the knobs, banged on it a couple of times, and the silly thing came back on and then went off again. You know how these mass-produced things carry on. It's gettin' so . . ."

"You've probably been listening to too much of that 'rock' music" interjected Ed with a chuckle. "Did the pilot light go out when the sound quit?"

"Yes, I believe it blinked off and on. Say how much is this thing going to cost me? I didn't pay much for it to begin with and I'm not figgerin' on . . ."

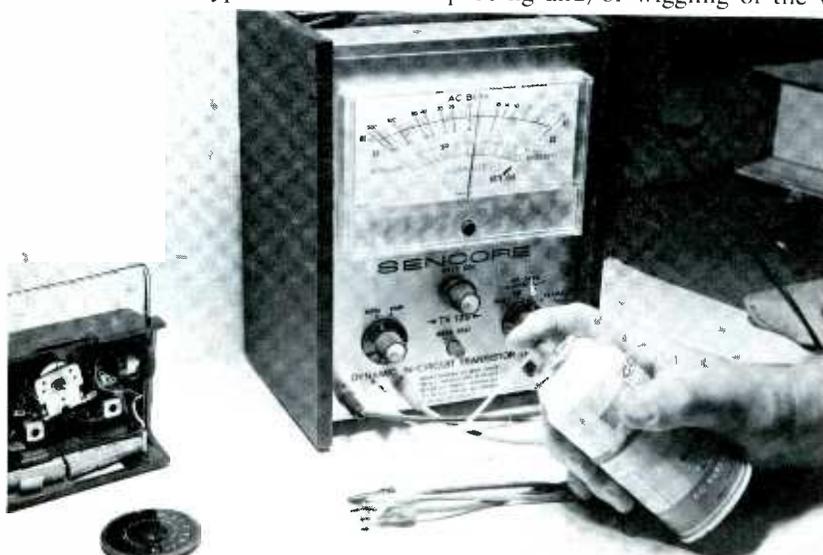


Fig. 1. Set up for checking intermittent transistor.

"I'll try to keep the damages below forty or fifty dollars," laughed Ed. "I know how you hate to let go of the moldy green stuff you got stashed away in those fruit jars."

Mr. Allen grunted something about wild rumors and asked if Ed thought he'd be able to muster up enough ambition to have the thing fixed by five o'clock.

Ed replied he'd try, and Mr. Allen left after stating he'd phone around four to make sure it was fixed.

Ed carefully laid the AC-DC radio down on a drop cloth and contemplated the problem while he removed the chassis from the cabinet. From his conversation with Mr. Allen, he had received two clues to the trouble: (1) The receiver went dead suddenly, and (2) the pilot light blinked off and on. Although several components could cause the same intermittent sound symptom, the blinking pilot light narrowed the possibilities down to the series heater string that also supplied voltage to the pilot light. One of the tubes had a filament that was opening and closing.

After removing the Admiral 5E3 chassis from the cabinet, Ed turned it over so he could get to the tube socket connections. Next, he connected power to the chassis and turned it on. Most thermal-heater intermittents open at once, or in only a very few minutes. Sure enough, all tube filaments and the pilot light went out in a short time. Using a VOM, Ed started at the tube having the highest filament voltage—in this case a 50C5—and measured across each filament (Fig. 2). When he placed the meter leads across the 12AV6 filament, the meter indicated the full AC line voltage—a sure indication of an open filament. After replacing the 12AV6, the receiver returned to normal operation.

The quick repair of Mr. Allen's radio contrasted with another intermittent situation Ed had recently had the misfortune of experiencing. The trouble had begun with a call from a customer who complained that the set (an Admiral 20X5B chassis) Ed had fixed with a damper tube replacement a couple of days ago had suddenly developed the same symptom: increasingly reduced width that finally resulted in a black raster.

So Ed had obligingly returned, checked the set out and decided to pull the chassis for a bench check at the shop. Back at the shop, the chassis had refused to display any trouble symptoms whatsoever. Three days went by and the thing just sat there and stubbornly acted normal. Meanwhile, the customer had developed a telephone dialing habit and constantly pressured Ed for information concerning the status of the set.

At this point, Ed decided to give the problem a little mental exercise. It wasn't long before Ed was tripping off to the customer's house to retrieve the cabinet. With the chassis reinstalled in the cabinet and a blanket thrown over the whole thing, the raster turned black within four hours.

Peeking under the blanket, Ed discovered that the 6AX4 damper tube was as dark as its immediate environment. A new damper tube was installed in place of the seemingly defective 6AX4, the blanket was removed, and within three minutes the receiver was operating normally once again.

However, Ed's mood of satisfaction began to dwindle when the supposedly defective 6AX4 checked normal in the tube tester—even with the filament supply increased to 8 volts. Obviously, the tube was good.

Ed replaced the blanket over the operating receiver and occupied himself with converging a recently repaired color set. Having completed the convergence procedure and repaired two b-w receivers, Ed returned to the blanket job. He wasn't too surprised to see a dark raster again. Nor was he surprised to see the new 6AX4 dark when he lifted off the blanket. However, Ed did

experience surprise when he wiggled the 6AX4 and witnessed a slight flickering of the filaments. After removing the tube from the chassis and the chassis from the cabinet, he inspected the heater pins on the socket. Both appeared normal, with good solder connections. That left only the tube socket itself. Sure enough, after the damper tube socket was replaced, the set cooked for two days without the old dark-raster symptom reappearing.

When an open tube filament appears to be the cause of an intermittent trouble, but the tube checks normal, don't overlook the tube filament pins—corrosion or arc scars can cause intermittent symptoms. It is also possible for solder to melt out of the tube pin holes. Replacing the tube may temporarily solve the problem. Also, don't overlook the socket pins themselves. Replace the socket if in doubt. It can save you a costly call back. Remember: low-voltage rectifiers, dampers, and horizontal output tubes usually provide the most tube-to-socket intermittent troubles.

Intermittent Sync

From the preceding paragraphs, it is obvious that Ed Stagglely has had his share of intermittent problems. Let's have a look at a few more and see how he handled them.

One involved an RCA CTC16XA color chassis that appeared to exhibit either intermittent sync or AGC trouble. First, the raster would pull horizontally, and then break into a vertical roll. Sometimes large black horizontal bars would roll vertically through the picture. Replacing the triode-pentode 6KA8 that served the AGC keying, noise inverter, and sync separator functions cured the

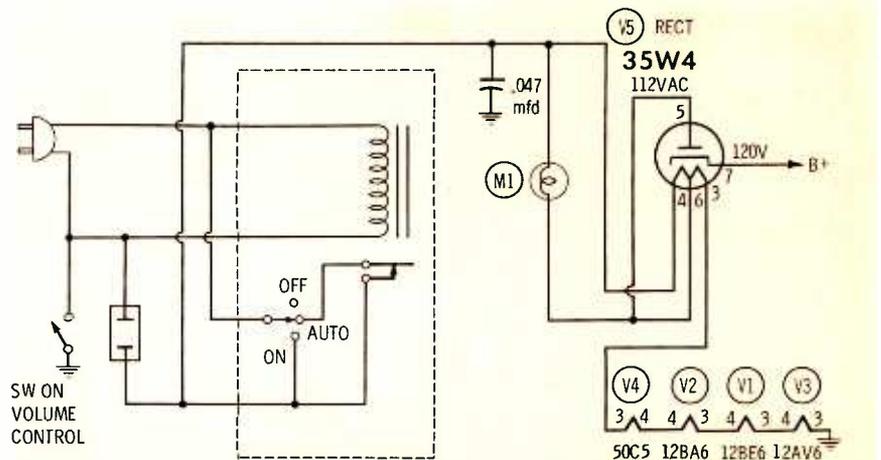


Fig. 2. Partial schematic of clock radio that suffered intermittent filament.

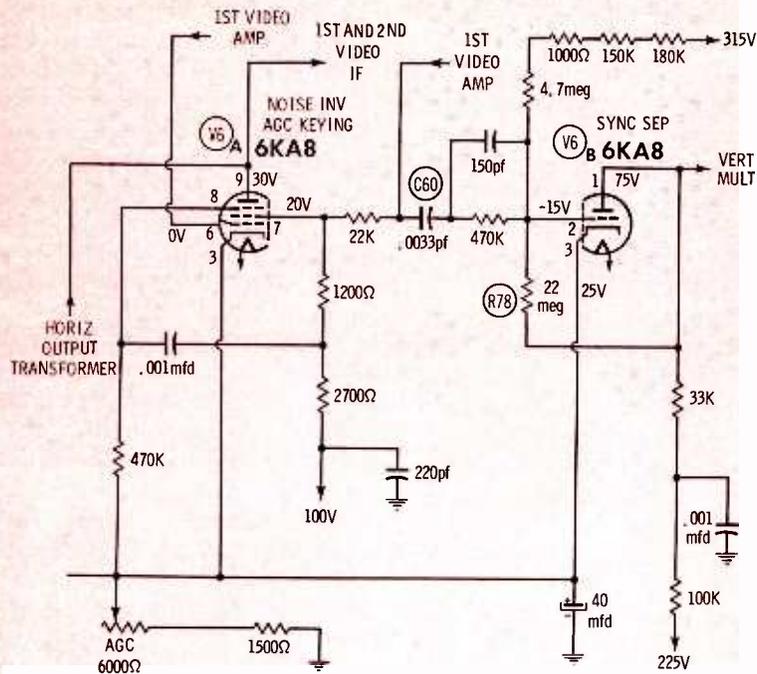


Fig. 3. Heat sensitive capacitor caused intermittent defect.

sync problem for a few minutes, then the same old symptoms returned for approximately three minutes. Ed decided to remove the chassis for a shop checkout.

Upon arriving back at the shop, Ed immediately checked the voltages on the 6KA8 (Fig. 3). However, all voltages were within normal tolerance of those indicated on the PHOTOFACT. Using the variable-voltage isolation transformer, Ed attempted to trigger the trouble symptom by increasing the line voltage; however, this failed to produce even a slight pull or roll. So Ed decided to let the thing cook until the symptom returned; meanwhile, he focused his attention on the small backlog of ailing sets whose owners were missing out on all the summer reruns.

Four days passed before the intermittent symptom popped up again. But Ed was ready with the VTVM and quickly took some voltage readings on V6A, the AGC section, were normal. However, the readings on V6B were significantly abnormal. The reading on the plate, pin 1, was 50 volts—down 15 volts from that listed in PHOTOFACT. Pin 2, the control grid, indicated a positive 22 volts instead of the normal -15 volts. The cathode voltage was the only element voltage of V6B that measured normal.

Checking over the schematic (Fig. 3) Ed reasoned that the most probable cause for the high positive voltage on pin 2 of V6B was either a

change in the value of R78 or a leaky C60. Ed unsoldered one end of R78 and checked the resistance; it was within tolerance—no help there. Next, Ed disconnected the sync separator side of C60 from the circuit and applied a VTVM between the open end and ground—no reading. Leaving the VTVM connected, Ed held a heated soldering iron near the capacitor—the meter reading gradually climbed to a high positive voltage, indicating that C60 was breaking down (leaking) under heat. As a double check, Ed resoldered C60 and R78 back into the circuit and then, once again, held the heated soldering iron near C60. Sure enough, the raster lost both horizontal and vertical sync. Ed replaced C60, and the receiver was returned to the customer—who was overjoyed at being able to once again view the reruns.

Intermittent Ford Radio

We'll continue Ed Staggley's experiences with intermittent problems by relating an encounter he had with a Ford Model 6TBF car radio.

The customer, a traveling salesman who lived near Ed's shop, came into the store one morning and stated that the radio in his car was behaving sort of funny (as he put it). "Every once in a while the thing just goes off and stays off for two or three hours," he explained. "Then, just as suddenly, the thing will come back on."

Ed asked if the radio was in a playing mood at the present time.

"No. It quit about an hour ago."

Ed went out to the car, slid across the seat and turned the receiver's on-off control to the on position; as he did so, a loud thump was heard in the speaker. When he rotated the volume control, the barely audible rushing noise in the speaker changed in intensity. Both checks—the thump and the changing noise—indicated that the receiver's audio section was operating properly.

Next, Ed performed a few preliminary checks of other suspected items, including the antenna lead-in connection. When nothing appeared wrong externally, Ed decided to pull the radio out for a bench check. The customer agreed to this course of action, and once Ed had the radio out, left to continue his business.

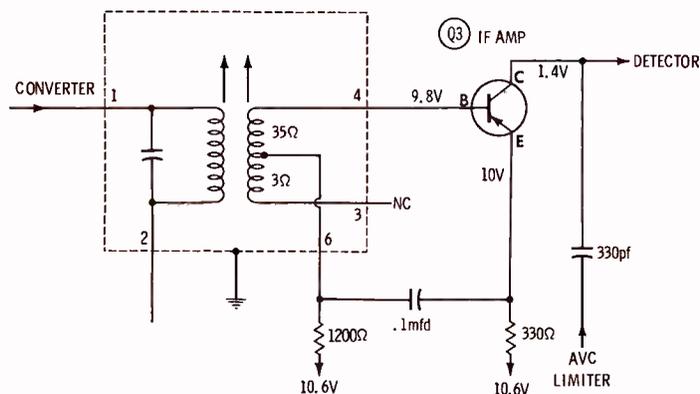


Fig. 4. Defective IF amplifier stage in Ford Model 6TBF car radio.

• please turn to page 50

Industry Demanded - only Sencore delivered

AN ALL NEW IMPROVED COLOR CRT TEST



**Simple - Fast - Accurate • Automatic Color Tracking!
No Time-Wasting Logging and Computing!**

CRT manufacturers, set manufacturers, distributors, technicians — all demanded a better CRT tester than any available. This is it — the new Sencore CHAMPION — a winner on every count.

Separate G2 screen grid controls, just like the color circuit itself, enable you to set up each color gun, then automatically compare it with the others for tracking — exactly according to industry standards. This check is important when claiming credit for a defective color CRT. No time consuming logging of each color gun reading at every setting of the G2 control like competitive models. It's automatic with the CR143 Champion.

The CHAMPION also makes all the standard color and black and white CRT tests — shorts, emission, and life tests. Its Line Adjust control assures exceptional accuracy. Its exclusive three step Automatic Rejuvenation Circuit lets you save many a faulty black and white tube or equalize gun currents in color tubes.


The all-new CHAMPION is equipped with plug-in sockets for fast testing and easy updating. Rugged vinyl-clad steel case has spacious lead compartment.

For a sure thing, put your money on the champion — the Sencore CR143 CHAMPION.



**CR143
CHAMPION**

\$9950

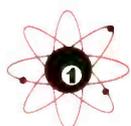

SENCORE

NO. 1 MANUFACTURER OF ELECTRONIC MAINTENANCE EQUIPMENT
426 SOUTH WESTGATE DRIVE, ADDISON, ILLINOIS 60101

Circle 14 on literature card

COLOR TV

PART
6

service training



CHROMA CIRCUITS

Burst Amplifier
Reference Oscillator
Difference Amplifier
Demodulators
Color Killer

Since the function of the chroma bandpass amplifier (or amplifiers) is simply one of increasing the level of the chrominance signal, there is very little to be said about it. The bandpass considerations were discussed in Part 4 of this series. The means by which it is gated by the color killer and controlled by the ACC circuit were covered in Parts 4 and 5.

Malfunction in the chroma bandpass amplifiers will normally result in insufficient color or no color at all. If the gain of the amplifier is reduced, color saturation will be decreased; if the amplifier fails completely, there will be a complete loss of color. Improper alignment of the amplifier will cause color smearing or "grainy" color, but alignment problems are more likely to be the result of tampering than drift. Realignment should be attempted only if the necessary test equipment is available. "Eyeball"

alignment will usually result in further degradation of picture quality.

Diode Chroma Demodulators

In essence, a chroma demodulator is simply a phase-sensitive detector —no more, no less. Although phase-sensitive detectors (PSD) have been used in the majority of b-w receivers built in the past 20 years, the use of a pair of phase detectors to extract the color-difference signals from the chroma sidebands seems to excite a great deal of interest. Thus, a thorough discussion of each of the four popular types of chroma demodulators is included here. Since the circuit which utilizes diodes is perhaps the most easily explained, we will begin this discussion with it.

Fig. 1 shows a simplified phase-sensitive detector and associated waveforms. The input from the reference transformer is constant, while the phase of the information input varies. Cases 1 and 2 show the information signal at two possible phase angles. In case 1, diode X1 cannot conduct since the instantaneous cathode and anode voltages are equal throughout the cycle. Consequently, the voltage at point A is a simple sine wave whose first excursion is positive.

During the first half of the cycle, X2 conducts because its cathode is

negative with respect to its anode, and the instantaneous voltage at point B is equal to the sum of the two applied voltages. These are equal in amplitude, but opposite in polarity; the potential at point B is 0 during the time that X2 is conducting. During the second half-cycle, X2 is cut off because the cathode is positive with respect to the anode. The voltage at point B is the positive excursion of a sine wave.

The voltage at point C, the output, is the sum of the instantaneous voltages at points A and B. During the first half of the reference sine wave, the voltage at point A completes a positive half-cycle while the voltage at point B is clamped to zero. Therefore, the voltage at point C is a positive half-cycle having an amplitude equal to one-half the amplitude of the half-cycle at point A. During the second half of the sine wave, the voltages at points A and B are equal in amplitude but of opposite polarity, and the voltage at point C is zero. Thus, if the input signals are in phase, the circuit func-

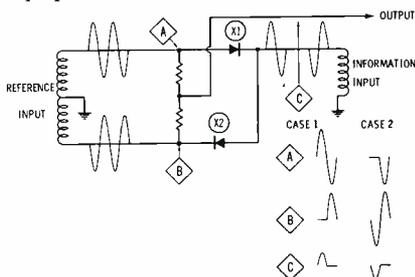


Fig. 1. Simplified phase-sensitive detector using diodes.


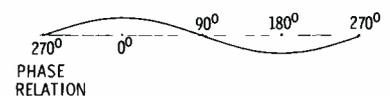


Fig. 2. Typical output curve for a phase-sensitive detector.

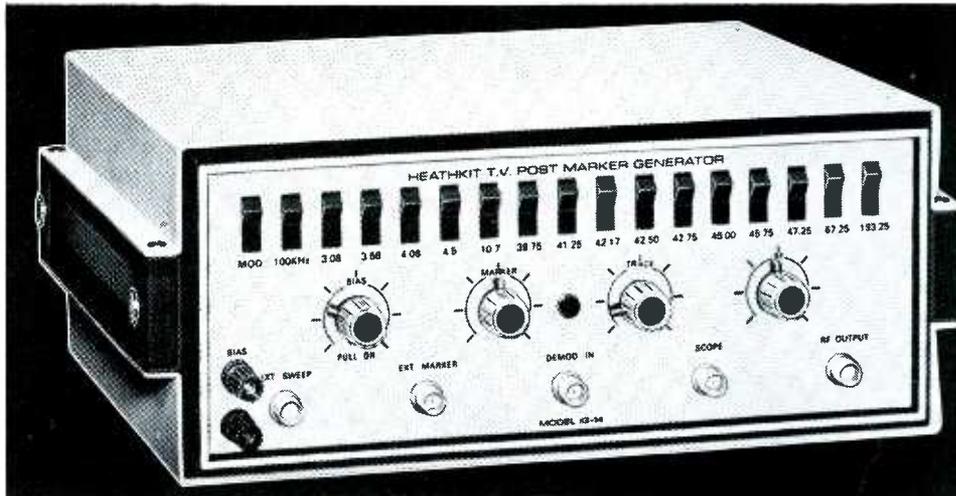

new
HEATHKIT®
solid-state
crystal-controlled
POST-MARKER
GENERATOR
only \$99.95

the most important instrument you can own for Color TV and FM alignment now costs a lot less...the Heathkit IG-14

• 15 crystal-controlled marker frequencies • Switch-select picture and sound IF frequencies, color bandpass and trap frequencies, 6 dB points, plus FM IF center frequency and 100 kHz points • Use up to six markers simultaneously for faster TV alignment • Birdie-type markers • Trace and Marker amplifiers and size controls • 400 Hz modulator • Variable bias supply • All solid-state, 22 transistors, 4 diodes • Circuit boards

Fast, Accurate Color Alignment. Speed and accuracy are important in today's service work . . . important to your customers, important to your profits. Speed and accuracy are what the new Heathkit IG-14 gives you . . . plus features usually costing five to ten times as much.

Just Push A Button. That's all it takes to set a frequency . . . no dial to twiddle, no searching, no resetting problems. Fifteen switch selected crystal-controlled markers. Nothing could be easier or more accurate. The IG-14 has input and output connections so that it can be used with any sweep generator and scope. Also an external marker input. BNC connectors are used throughout.

No Trace Distortion. One of the big values to using a post marker generator like the IG-14 is that markers are injected after the sweep signal passes through the set being tested, thereby eliminating the 'scope trace distortion usually found when injection or absorption type marker generators are used.

Crystal-Controlled Markers For Any TV Alignment Task. Four marker frequencies are provided for setting color bandpass, one marker for TV sound, eight at the IF frequencies between 39.75 and 47.25 MHz, and markers for channel 4 and channel 10 picture and sound carriers for checking tuner RF response. With the ability to use up to six markers at once, such as picture and color carriers at 6 dB points, corner marker and trap frequencies, alignment is fast and precise. Trap alignment is just a matter of selecting the appropriate trap frequency, applying the 400 Hz modulation, and tuning the trap for minimum audio on a scope or meter.

Easy FM IF and Discriminator Alignment. The IG-14 provides visible markers at the 10.7 MHz center frequency plus 100 kHz markers on each side . . . visible because they are applied to the trace after detection and so are not attenuated by the discriminator. Use of harmonics, fully explained in the manual, provide tracking markers as well.

Trace and Marker Amplitude Controls . . . on the front panel permit using a regular service type 'scope instead of a wide-band, ultra-sensitive model . . . and stage by stage alignment is easier.


Variable Bias Supply . . . 0 to 15 VDC @ 10 milliamps is isolated from chassis so you can use positive or negative bias.

New Look . . . Circuit Board Construction. Handsome low profile, "stackable" cabinets in the new look of Heath instruments . . . finished in beige and black. Easy-to-build layout with two circuit boards.


Save Hundreds of Dollars. Until now, an instrument with these features cost much more. Order the IG-14 now . . . it's the best investment in alignment facilities you can make.

Kit IG-14, 8 lbs., no money dn., \$10 mo. \$99.95

IG-14 SPECIFICATIONS—Crystal Marker Frequencies: 3.08, 3.58, 4.08, 4.5, and 10.7 MHz @ .01%; 39.750, 41.250, 42.170, 42.500, 42.750, 45.000, 45.750, 47.250, 67.250, and 193.250 MHz @ .005%. **FM Bandwidth Marker:** 100 kHz. **Modulation:** 400 Hz. **Input Impedance:** External sweep, 75 ohm; External marker, 75 ohm; Demodulation input, 220K ohm. **Output Impedance:** RF output, 75 ohm; Scope output, 22K ohm. **Bias Output Voltage:** Variable from 0 to 15 VDC @ 10 MA. Isolated from chassis for either negative or positive bias. **Type of Marker:** "Birdie." **Controls:** Bias voltage with AC on/off; Trace size; Marker amplitude; RF output; Modulation on/off; Markers, individual switches for each frequency. **Semiconductors:** Transistors: (16) 2N3692; (6) 2N3395; (3) Silicon diodes; (1) Zener diode, 13.6-V. **Power requirements:** 105-125 volts, 50/60 Hz AC @ 7.5 watts. **Net weight:** 8 lbs.

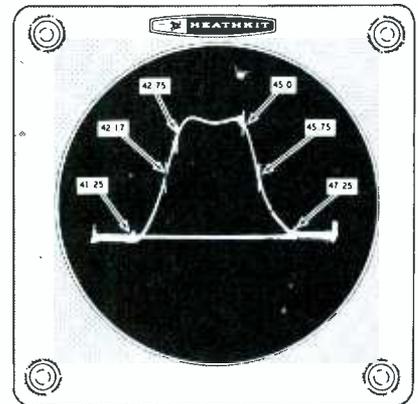

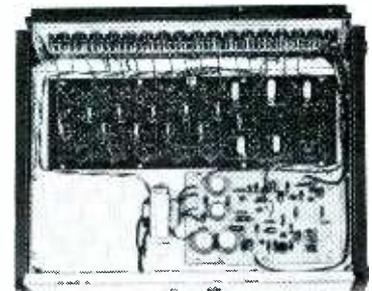SIX MARKERS SIMULTANEOUSLY. The scope trace above shows how six markers can appear at the same time. Note the trap markers, 6 dB points, and picture and sound carriers . . . all on one trace with the IG-14.



EASY TO BUILD. Note how everything except the front panel switches and controls mount on two circuit boards . . . even the crystals.



FREE 1968 CATALOG!

Now with more kits, more color. Fully describes these along with over 300 kits for stereo/hi-fi, color TV, electronic organs, electric guitar & amplifier, amateur radio, marine, educational, CB, home & hobby. Mail coupon or write Heath Company, Benton Harbor, Michigan 49022.

HEATH COMPANY, Dept. 25-2
 Benton Harbor, Michigan 49022

Enclosed is \$ _____ plus shipping costs.

Please send _____ Heathkit IG-14 Post Marker Generator(s).

Please send FREE Heathkit Catalog.

Name _____

Address _____

City _____ State _____ Zip _____

Prices & specifications subject to change without notice.

TE-174

SPRA-LUBE

non-drift tuner cleaner




specifically formulated by GC for color TV tuners

CATALOG No. 8888
Suggested Net \$1.95

Only SPRA-LUBE safely cleans away all oxidation, dust and dirt, dries quicker, will not harm plastics, and leaves a fine, light protective lubricating coating essential to keeping color tuners in peak operating condition. Often imitated, never duplicated... SPRA-LUBE is the one proven cleaner-lubricant for all color TV tuners, the only product in its field carrying the proud GC label, your assurance of quality in electronic chemicals.

Always insist on GC...
you'll get more for your money, everytime!

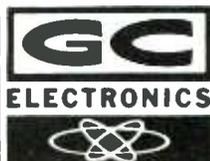GC ELECTRONICS
A DIVISION OF HYDROMETALS, INC.
MAIN PLANT: ROCKFORD, ILL. U.S.A.




Giant FREE Catalog...

Only GC gives you everything in electronics... has for almost 40 years. Match every part and service need from over 10,000 quality items. Write for your copy today!

Circle 16 on literature card



has everything in CHEMICALS

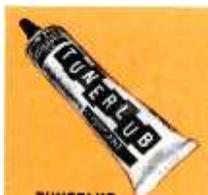

TUNERLUB
For quiet TV tuner operation.
Cat. No. 26-01-S
1 3/4 oz. Tube
Suggested Net .99¢



DC-29 Silicone
heat sink compound
Cat. No. 8109...
1-Oz. Tube
Suggested Net \$2.39



EPOXY GLUE
"Super Grip"... NASA Approved
Cat. No. 347... 2-Tube Kit
Suggested Net \$2.50



plifier is the R-Y signal which is fed to the red control grid of the CRT gun.

The B-Y demodulator is identical to the R-Y demodulator but the phase of the reference signal has been changed. In the B-Y demodulator, a "blue" (B-Y) chroma signal produces the maximum negative output. This is amplified and inverted in the B-Y color-difference amplifier and finally appears as a positive signal at the blue grid of the CRT, turning on the blue gun and causing a blue field.

It was stated previously that a specific amplitude and polarity of output from a demodulator may be the result of either of two phase relationships. For example, observe from Fig. 2 that phase relationships of 160° and 200° each produce a negative output which is 94% of the 180° output. However, since the reference signal applied to the B-Y demodulator is shifted 90° from the reference signal at the R-Y demodulator, the 160° signal at the R-Y demodulator becomes a 70° signal at the B-Y demodulator. Again referring to Fig. 2, this signal will produce an output from the B-Y demodulator which is positive with an amplitude that is 34% of maximum. By the same token, the 200° signal at the R-Y demodulator becomes a 110° signal at the B-Y demodulator, and a negative output with an amplitude which is 34% of maximum is produced.

From the above, it is apparent that even though two chroma signals having different phase angles can produce the same output from a single demodulator; when these same chroma signals are fed to the second demodulator, they cause radically different outputs. Therefore, any phase of chroma signal may be described in terms of the outputs it produces from the two demodulators. Stated another way, two demodulators are sufficient to extract all of the color information from the chroma signal.

In spite of this, three color difference signals are necessary to operate the color CRT because the colors from three phosphors are required to produce all the visible hues. There are two methods of producing control voltage for the

only during the negative half-cycles of the cathode signal. At the instant when the reference voltage is peak negative, the tube bias is reduced to 3.5 volts and the tube current is about 8.2 ma. The unfiltered plate waveform would consist of negative-going half-cycles. However, the pi filter (C145, L35, and C146) integrates the pulses, and the voltage at the output of the pi filter is at a DC level of 235 volts.

When a chroma signal is fed to the grid of V14A, the instantaneous current is determined by the instan-

taneous grid-cathode voltage. This voltage is the sum of three potentials: (1) the cathode bias, (2) the instantaneous reference-signal voltage, and (3) the instantaneous chroma-signal voltage. For example, if the chroma and reference signals are 180° out of phase, the control grid is nominally 1.25 volts positive at the same instant that the cathode potential is + 3.5 volts (bias less the peak reference signal of 4.5 volts.) Thus, the total grid-cathode voltage is -2.25 volts. From Fig. 5, the tube current is about 12.7

ma at this instant. This is an increase of about 4.5 ma from the peak current with no chroma signal applied. After a number of cycles of voltage, the plate voltage will stabilize at a new voltage which is less positive than it was when no chroma signal was applied.

In the example just cited, the instantaneous peak tube current reaches its maximum value. The minimum instantaneous peak current may be approximated by considering the effect on tube conduction of in-phase chroma and reference signals. In this case, the grid is maximum negative at the same instant that the cathode is maximum negative (minimum positive) and the instantaneous grid-cathode potential is -4.75 volts. Again referring to Fig. 5, the current is approximately 4.5 ma. A third condition which is easily described is the 90° or 270° phase relationship. In this case, the chroma signal is passing through zero when the reference signal is maximum negative, and the peak tube current is the same as if no chroma signal were applied, 8.2 ma.

From the above examples, we find that the maximum and minimum instantaneous peak tube currents are 12.7 and 4.5 ma, respectively. Since the plate load resistor is 3.9K ohms in the actual circuit of Fig. 4, the swing in plate voltage may be predicted to be 32 volts. Since the chroma reference-signal amplitude at the grid of V14A is 2.5 volts, p-p, during normal operation with a keyed-rainbow generator as a signal source, the predicted "gain" is 12.8. Actual observations showed this "gain" to be 10.

Bear in mind that the above examples are an oversimplification of the operation of the circuit since only the instantaneous peak currents were considered. In actual practice, the tube conducts throughout approximately 180° of the reference-signal sine wave, and the magnitude of the current may be represented by the positive half of a sine wave. Nevertheless, we can conclude that the tube conduction is proportional to the sum of the instantaneous amplitudes of the reference signal and chroma signal during the intervals when the tube is out of cutoff. In

New
Perma-Power
Solutions

to these
common
color TV

problems
problems
problems
problems

washed-out
unclear color pictures
from loss of
the black-and-white



color-brite
ISOLATION BRITENER
(NO BOOST)
CORRECTS FOR
CATHODE-TO-FILAMENT
SHORTS—RESTORES
BLACK & WHITE—
REVIVES COLOR QUALITY

MODEL C-502
for round tubes
\$7.25 net

MODEL C-512
for rectangular tubes
\$7.25 net

picture distortion
shrinking, flutter, flop-over,
dullness
from low line voltage



avr
400 WATT
AUTOMATIC
VOLTAGE REGULATOR

Automatically boosts voltage 10 volts
when line drops below 110 V—
automatically cuts out when line
is normal—
Maximizes
color TV set
performance

MODEL D-210
400 watt AVR
\$14.95 net

These units are now available from your Perma-Power distributor. Write for Catalog LCB-66 on the full line of Perma-Power products for color and black and white TV service.

Perma-Power
COMPANY

5740 North Tripp Avenue
Chicago, Illinois 60646
Phone (312) 539-7171

Circle 17 on literature card

the circuit of Fig. 4, these intervals correspond to the negative half-cycles of the reference signal. The operation of the X demodulator of Fig. 4 is similar to that of the Z demodulator just described.

Now, consider the operation of the two demodulators if the signal source is an unkeyed-rainbow generator. Using an unkeyed-rainbow signal, there is a constant rate of change of phase difference between the chroma signal and the reference signal. Since the chroma signal is fed to both demodulators at the same phase angle, the outputs of the two demodulators differ in phase by the same amount as the phase difference of the reference signals applied to the two demodulators. In a system using X and Z demodulation, the phase of the reference-oscillator signal applied to the two demodulators differs by 63.9° . Observations of the outputs of the two demodulators when an unkeyed-rainbow generator is used as a signal source confirm that the sinusoidal output of the Z demodulator passes through zero about 64° later than the output of the X demodulator passes through zero.

The operation of the color-difference amplifier shown in Fig. 4 is typical of most color-difference amplifiers used in conjunction with low-level, vacuum-tube demodulators. The difference signals from the demodulators are coupled through C147 and C151 to the B-Y and R-Y amplifiers, respectively. These signals are amplified and fed to the respective control grids of the CRT.

Notice that there are two apparent discrepancies in the foregoing discussion. First, since the signals at the red and blue control grids of the CRT are R-Y and B-Y respectively, the signals at the inputs to the difference amplifiers must bear the negative sign, $-(R-Y)$ and $-(B-Y)$. Hence, the demodulators are actually -X and -Z demodulators. However, it is common practice to ignore this reversal of polarity.

Also observe that while the demodulators operate on the X and Z axes, the difference amplifiers operate on the R-Y and B-Y axes. Although this seems unlikely, it is actually the case. Since the difference amplifiers have a com-

mon cathode circuit, a portion of the -Z signal which is fed to the B-Y amplifier appears at the cathode of the R-Y amplifier and vice versa. Thus, a small portion of the -Z signal is added vectorially to the -X signal, shifting the true axis of the difference amplifier to R-Y. Also, a portion of the -X signal is added vectorially to the -Z signal in the B-Y amplifier to establish its true axis.

The means of deriving the G-Y signal is similar to the method described in the explanation of the General Electric circuit. In the circuit of Fig. 4, an additional portion of the R-Y signal is fed from the plate of V15B to the grid of V13B where it is added to the $-(R-Y)$ signal being fed to the cathode of V13B. A sample of the $-(B-Y)$ signal is also fed to the cathode of V13B. The total of these three signals produces a voltage at the plate of V13B which is $-.51(R-Y) - .19(B-Y)$, equal to G-Y.

Low-Level Pentode Demodulators

The operation of a low-level pentode demodulator is quite similar to the triode demodulator just discussed. The demodulator circuit used in Packard-Bell Chassis 98C15 is shown in Fig. 6. The 6GY6 tubes used as demodulators belong to the family of tubes having two independent control grids. That is, both the suppressor grid and the control grid have considerable effect on the plate current.

The plate current of V18 and V19 are controlled by the instantaneous values of chroma and reference signals and detection takes place at the plate of the tube. The operation of the color-difference amplifiers is essentially the same as the ones discussed previously.

Sheet-Beam Demodulator

The sheet-beam demodulator used in Zenith receivers is actually

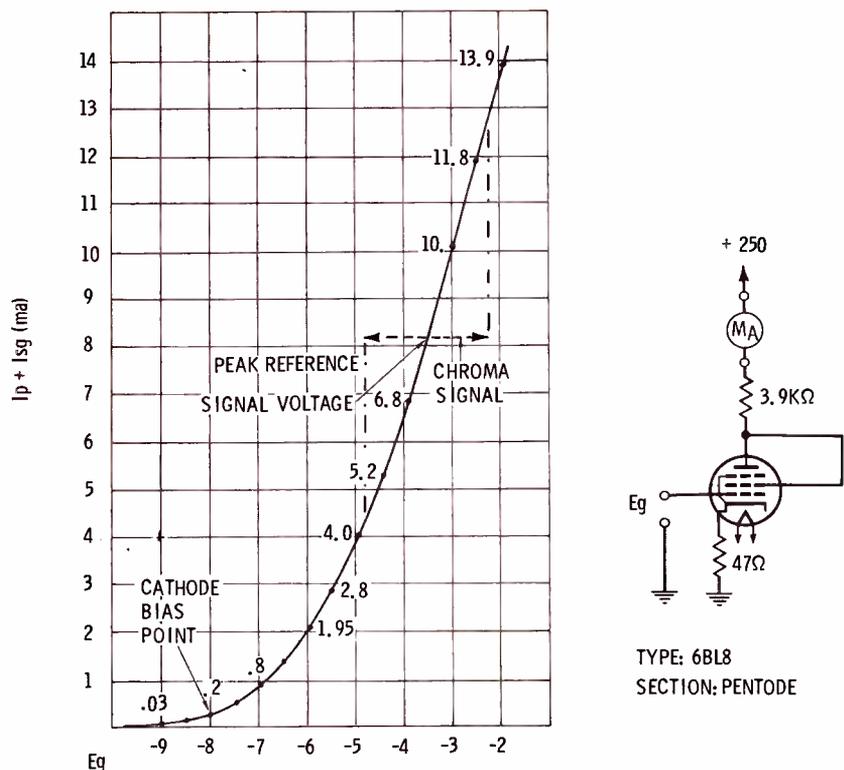


Fig. 5. Characteristics of the 6BL8.

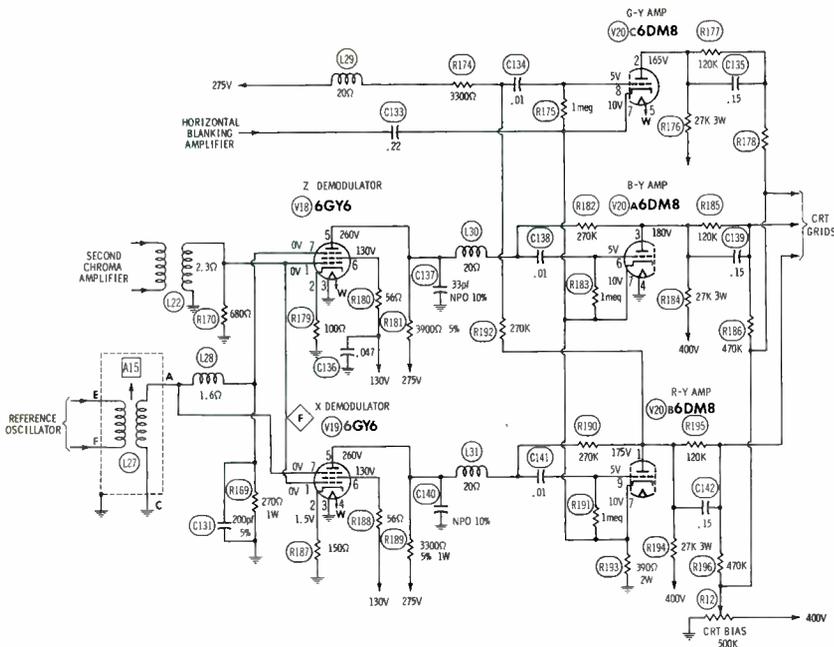


Fig. 6. Chroma demodulators and color-difference amplifiers of Packard-Bell Chassis 98C15.

a variation of the pentode demodulator. However, there are two significant departures from the conventional design. Since the amplitude of the output from sheet-beam demodulators is sufficient to drive the CRT directly, they are known as high-level demodulators. The more

important difference is the means by which detection of the chroma signal is accomplished. In the triode and pentode circuits just discussed, the amount of cathode current is controlled jointly by the chroma and reference signals. In the sheet-beam demodulator, cathode current

is controlled solely by the chroma signal, but the selection of which plate receives the current is controlled by the reference signal.

Fig. 7 shows the demodulators used in the Zenith 24MC32 and 42 chassis. Consider the B-Y demodulator under no-signal conditions. The reference signal is fed to the two deflection plates in opposite phases and so the cathode current is directed alternately to each of the plates. Since the amplitude of the reference signal is considerably greater than the minimum required to deflect all of the current to one plate, the current at each plate consists of a series of square-wave pulses of constant amplitude.

During color reception, the chroma signal is fed to the control grid and determines the amount of instantaneous current that is available to the plates. Assume, for example, that the left deflection plate, pin 1, is maximum positive at the same instant that the control grid is maximum positive. In this case, the current of the left plate is maximum and the plate voltage is minimum. Since the right deflection plate is positive one-half cycle later, the control-grid voltage is negative during the time that the right plate is gated on. Thus the current of the right plate is minimum and the voltage is maximum.

A 90° phase difference between reference and chroma signals causes one plate to be gated on while the chroma signal swings from peak positive to peak negative. The other plate is gated on while the chroma signal swings from peak negative to peak positive. Therefore, the average of all the values of instantaneous grid voltage present while one plate is gated on equals zero and the average value of plate current is equal to the amount of current under no-color conditions. For intermediate phase relations of the reference and chroma signals, the current of a specific plate varies in the same manner as in any of the other demodulators described. The curve shown in Fig. 2 applies to this circuit except that the phase relationship is shifted 180°.

The phase of the reference signal is established so that the left side of V21 demodulates on the R-Y

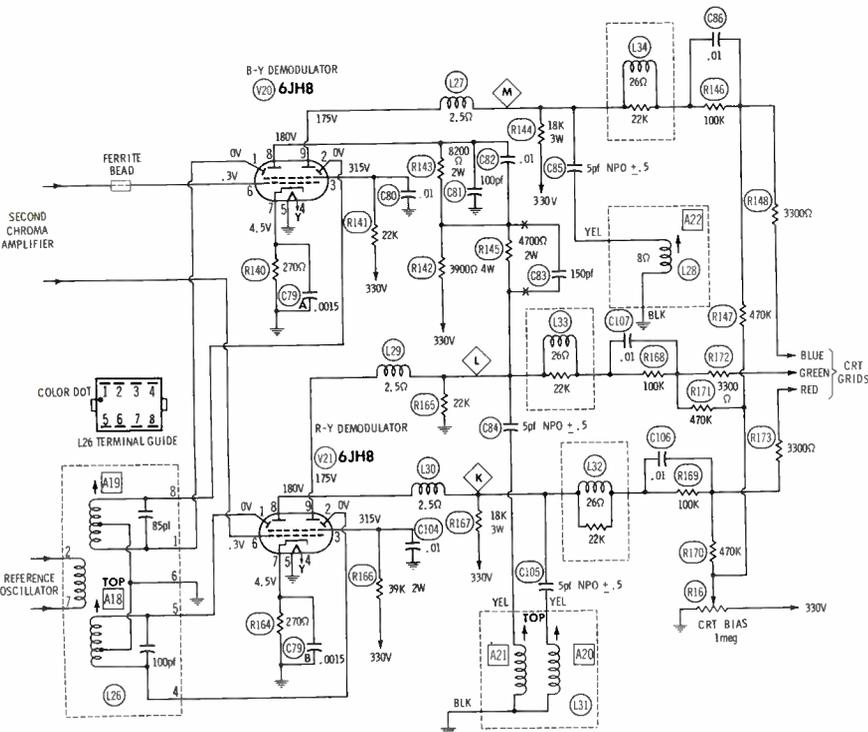


Fig. 7. Sheet-beam demodulator of Zenith Chassis 24MC32.

• Please turn to page 47

See PHOTOFACT Set 826, Folder 1

Mfr: General Electric

Chassis No: CA


Card No: GE CA-1

Section Affected: Color sync.

Symptom: Intermittent color sync; black-and-white pix normal.

Cause: Poorly soldered connections on burst phase detector transformer (especially terminal 3).

What To Do: Resolder connections to L29.

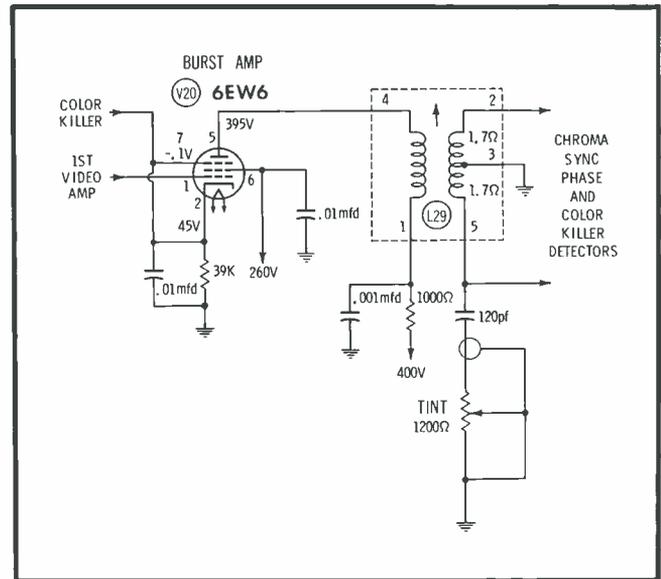

See PHOTOFACT Set 826, Folder 1

Mfr: General Electric

Chassis No: CA


Card No: GE CA-2

Section Affected: Pix.

Symptom: Vertical foldover and insufficient height.

Cause: Open vertical cathode bypass capacitor.

What To Do: Replace C5 (50 mfd, 150V).

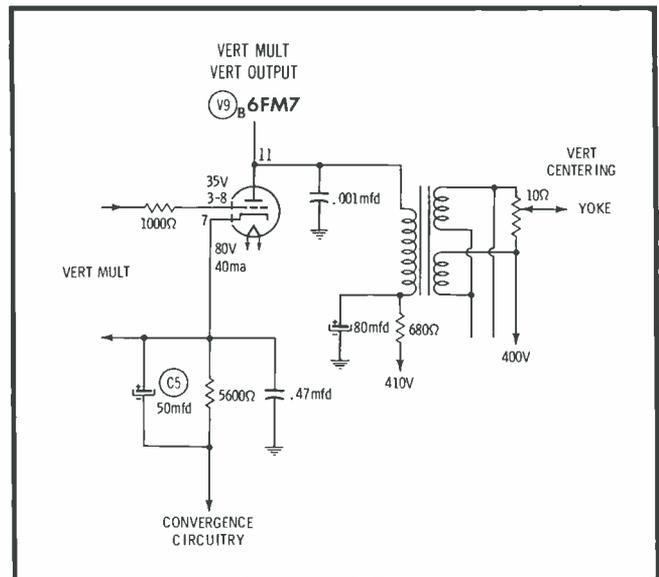

Mfr: General Electric

Chassis No: CA


Card No: GE CA-3

Section Affected: Color uix.


Symptom: No color pix; black-and-white pix normal.

Cause: Shorted bypass capacitor in grid circuit of color killer.

What To Do: Replace C157 (.01 mfd).

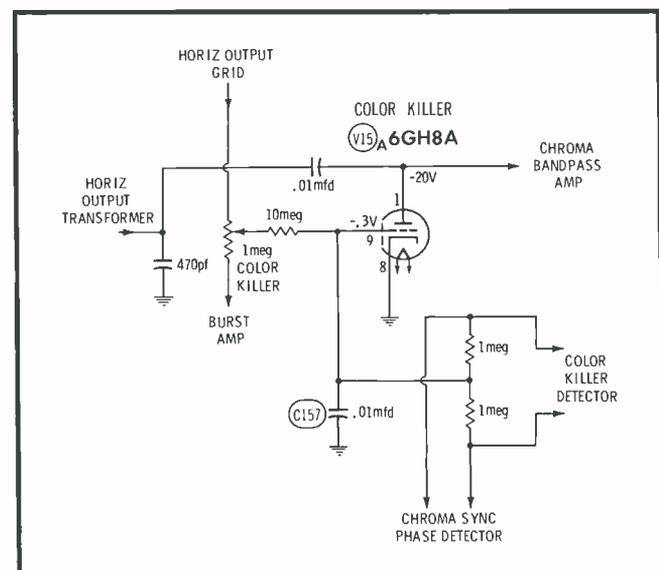

See PHOTOFACT Set 826, Folder 1

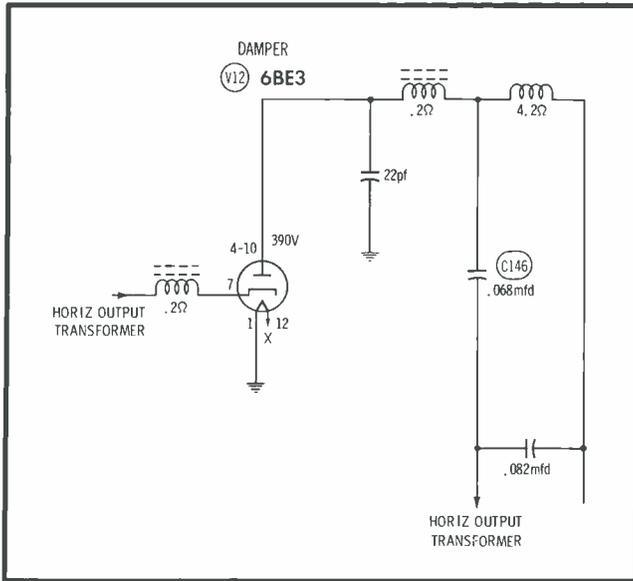

See PHOTOFACT Set 826, Folder 1

Mfr: General Electric

Chassis No: CA


Card No: GE CA-4

Section Affected: Raster.

Symptom: No raster; no high voltage.

Cause: Shorted bypass capacitor in damper plate circuit.

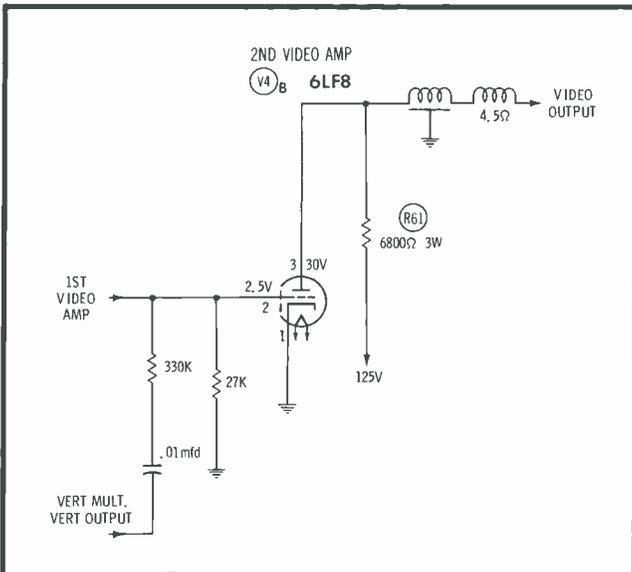What To Do: Replace C146 (.068 mfd, 600V)



Mfr: General Electric

Chassis No: CA


Card No: GE CA-5

Section Affected: Pix.

Symptom: Black-and-white and color pix smeared.

Cause: 2nd video amplifier plate load resistor reduced in value.

What To Do: Replace R61 (6800 ohms, 3W).

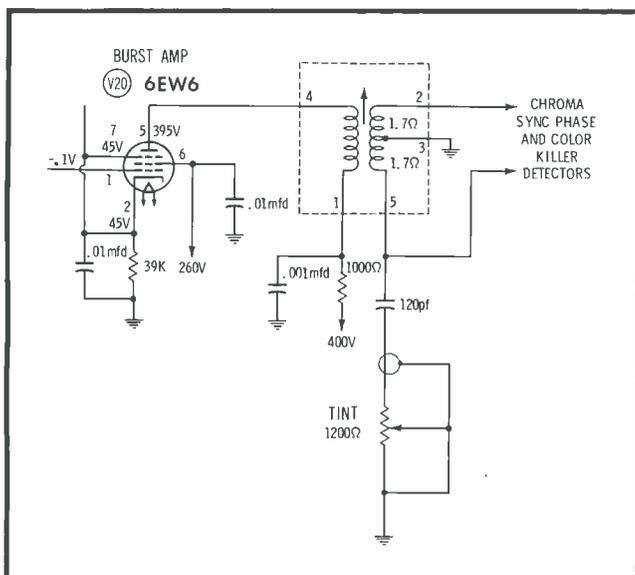

Mfr: General Electric

Chassis No: CA

Card No: GE CA-6

Section Affected: Color pix.

Symptom: Tint control has no effect on hue.

Cause: Shorted cable in tint control circuit.

What To Do: Replace tint control cable.

See PHOTOFACT Set 759, Folder 4

Mfr: Sylvania

Chassis No: 580-1, -2


Card No: SY 580-1-1

Section Affected: Color pix.

Symptom: No color pix; black-and-white pix normal.

Cause: Open coil in grid circuit of Z demodulator.

What To Do: Replace L27 (5.6 μ h).

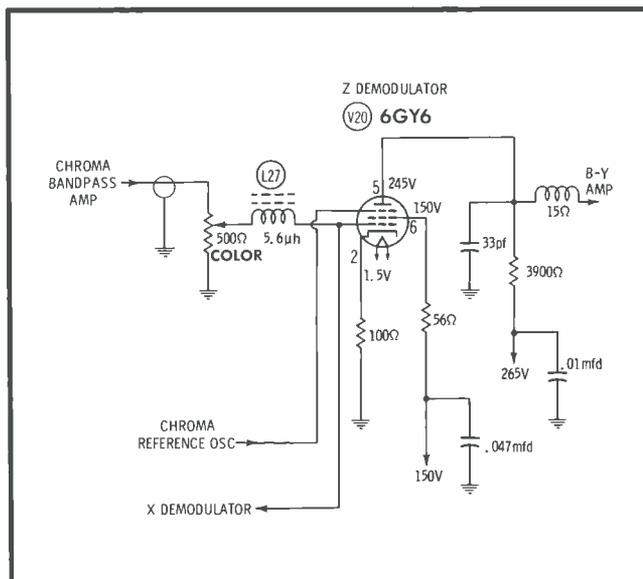

Mfr: Sylvania

Chassis No: 580-1, -2


Card No: SY 580-1-2

Section Affected: Raster.

Symptom: Raster shaded red; shading increases as operating period of receiver lengthens. Voltage on plate (pin 1) of R-Y amplifier increases.

Cause: Resistor in plate circuit of R-Y amplifier decreases in value.

What To Do: Replace R200 (27K, 2W).

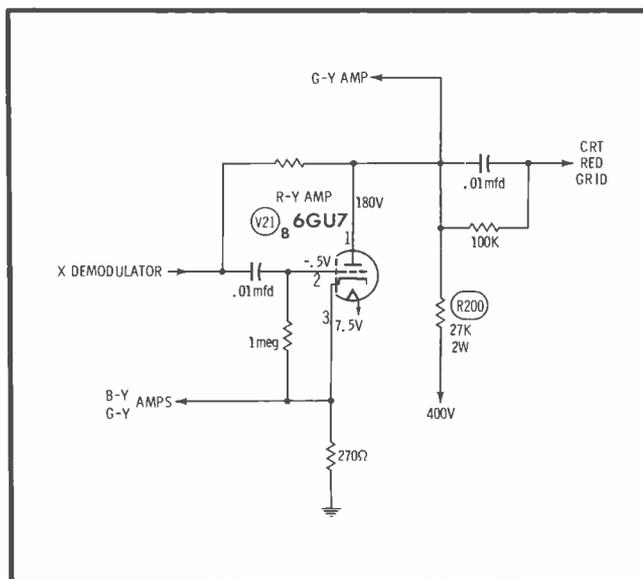

Mfr: Sylvania

Chassis No: 580-1, -2


Card No: SY 580-1-3

Section Affected: Color sync.


Symptom: Intermittent color sync; black-and-white pix normal.

Cause: Poorly soldered connection on chroma reference oscillator control coil.

What To Do: Resolder connections on L30.

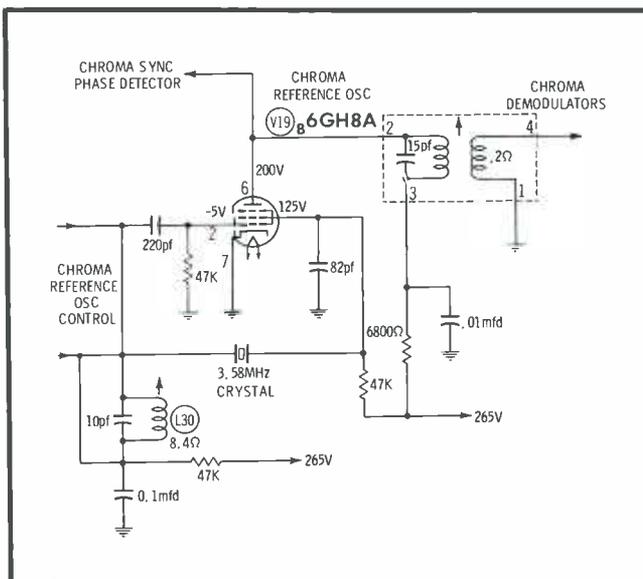

See PHOTOFACT Set 759, Folder 4

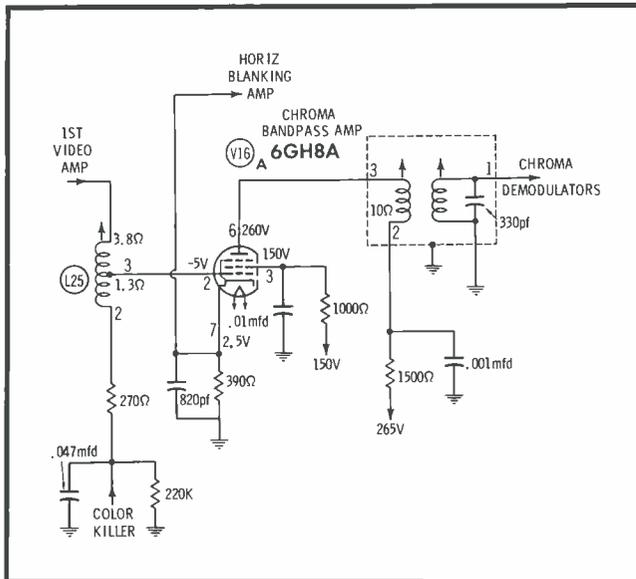

See PHOTOFACT Set 759, Folder 4

Mfr: Sylvania

Chassis No: 580-1, -2


Card No: SY 580-1-4

Section Affected: Color pix.

Symptom: No color pix; black-and-white pix normal.

Cause: Open chroma takeoff coil.

What To Do: Replace L25.

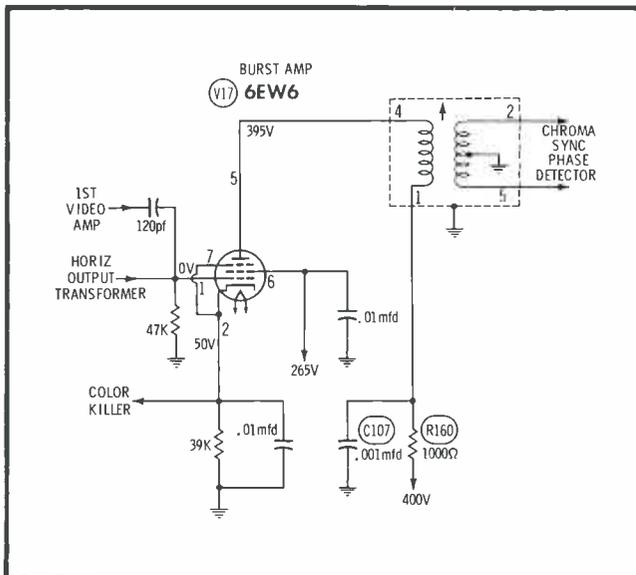

Mfr: Sylvania

Chassis No: 580-1, -2


Card No: SY 580-1-5

Section Affected: Color pix.

Symptom: No color pix; black-and-white pix normal. Voltage low on screen grid (pin 6) of burst amplifier.

Cause: Leaky screen-grid bypass capacitor causing overload of screen-grid resistor in burst amplifier.

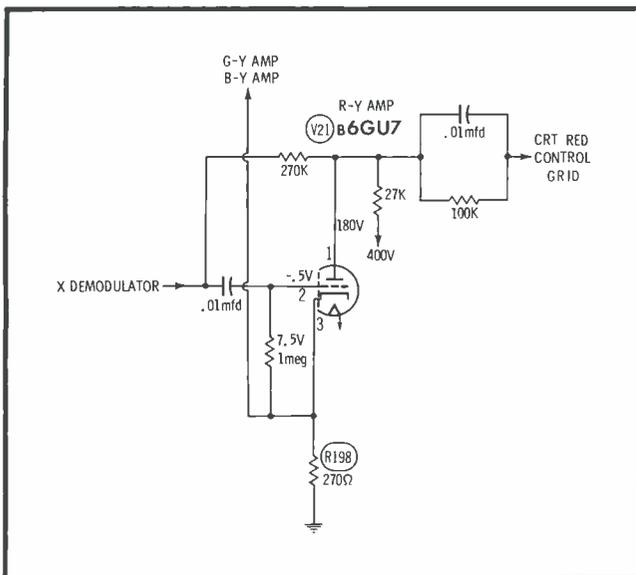What To Do: Replace C107 (.001 mfd) and R160 (1K).



Mfr: Sylvania

Chassis No: 580-1, -2

Card No: SY 580-1-6


Section Affected: Raster.

Symptom: Raster predominantly red. Voltage high at cathode (pin 3) of R-Y amplifier.

Cause: Open cathode resistor in R-Y amplifier.

What To Do: Replace R198 (270 ohms).

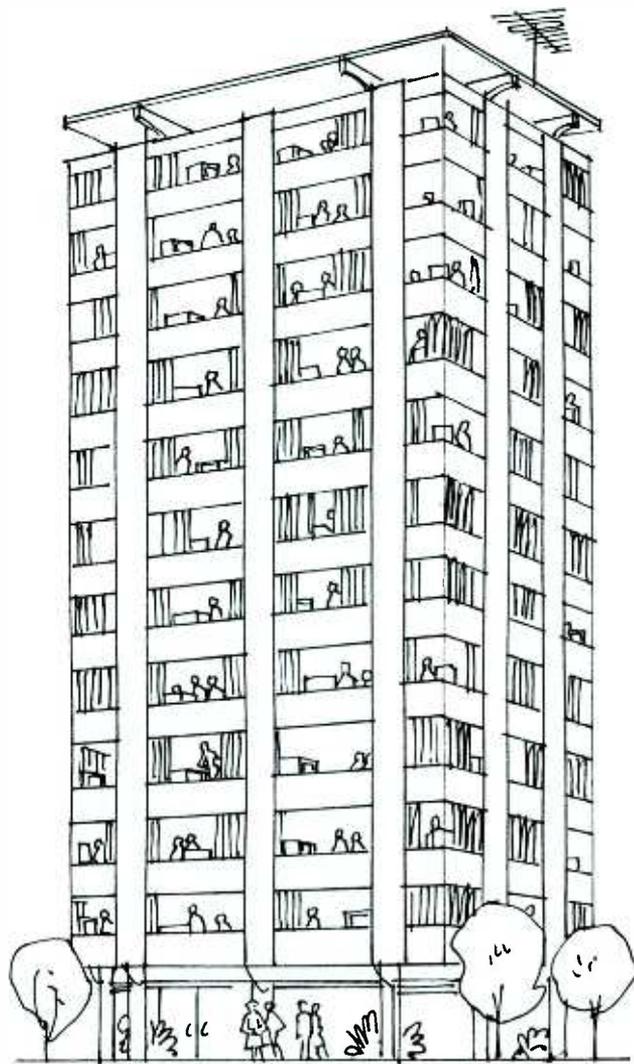Now! Cash in on the big boom in TV distribution systems



for two sets ... to two hundred

Right now, a golden opportunity to make big money is staring you right in the face. TV reception distribution systems. For homes. For motels. For hotels. For industry. And with Color TV, it's important to get the best. Jerrold's home and system amplifiers.

Jerrold pioneered TV distribution systems more than 15 years ago. We've harnessed our experience in space-age technology to solve down-to-earth reception distribution problems. The result is the most complete, up-to-date line in the business—and the know-how

to help you build your reputation in the TV distribution system business.

Free *Jerrold Handbook of TV Distribution Systems*. Features 100 typical systems layouts and all the information you'll need. Just fill out and mail the coupon.



Focusing on one thing
... better reception

Jerrold Electronics Corporation
Distributor Sales Division
401 Walnut Street
Philadelphia, Pa. 19105

Please send free Jerrold Handbook of TV Distribution Systems.

Name _____ Title _____


Company _____

Street _____

City _____ State _____ ZIP _____

Circle 8 on literature card

FUTURE PROFITS

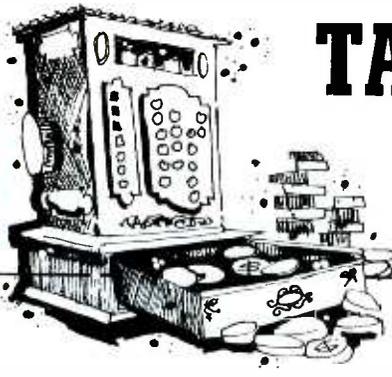

TAKE PLANNING TODAY

BY ERNEST W. FAIR

Whether or not you have a profitable electronic service business in future months and years can be determined, in part, by the day-to-day planning you make toward those profits now. Tomorrow does not take care of itself in any type of business. Future profits depend on what is being done in one's business today. Here are some of the steps which, taken now, can make those profits in distant tomorrows much more certain.

Keep today profitable. Doing so is always an assurance that business strength will be present in the future. Sacrificing profit today, with the hope that such a step will pay off in the future, usually results otherwise. Bankruptcy court records are overflowing with data on business firms whose management felt that shaving profit to the bone was the surest way to obtain customers from which real profits could be made in the future.

Worthwhile business does not come from the type of customer whose loyalty depends solely on the depth of profit-cut offered him in order to obtain his business. Just as the lure of drastically reduced prices dragged him away from some other shop to your business, so will the same inducement coming from another shop eliminate him as your customer tomorrow.

Find top-notch employees. Locating and holding onto such men and women so that they will be present in the future is a must for profitable operation, both today and tomorrow. The lack of such foresight could leave one's firm in a desperate condition should a skilled employee shortage develop—a possibility at any time in the future. This type of individual may cost a few more dollars per month than others, but the contribution he will make to the business is just one more assurance that it will be a profitable service shop in the future.

Guard the small customer. Take care of the smallest and least important customer today, for he may be the most important one in the area in just a few years. If this man is neglected at present in favor of the more affluent individual, the slight will quickly become apparent to him. Long experience in the field points out that every successful business has been built upon the care exercised in serving these small customers through the years.

Look for better lines and services. Every study of this phase of business operation has revealed that continuous profitable growth of any business depends on keeping this principle in sight. The shop which keeps searching for and adding better lines and services today, while at the same time it weeds out those that are unprofitable, creates a far more favorable competitive situation as each year goes by. Any service business that has the best of everything already working for it when tomorrow comes around will have an important advantage over its competition.

Guard financial resources. The service business that seeks continued growth toward a very profitable future must insure that its financial resources have not only held their own, but have shown a slight gain. The desired strong position of any firm in the distant future can only be assured when it has ample financial resources. When one depends on "providence," "good luck," or any other similar intangibles, the future is always questionable.

Look for management skills. A profitable future for any business is invariably dependent upon how successful its management has been in maintaining staff personnel with management talent and skill. Such people can seldom be found on a moment's (or a month's) notice. As the need arises for them, they will have to be there on the staff, or the

If you have a good crystal ball or your sister-in-law is a fortune teller, you don't need the information contained in this article. However, if you do not have either service, and you are a shop owner who would like to continue prospering in the future, the following information is for you.

opportunities which are presenting themselves may never be grasped. Scores and scores of surveys have shown that too many business concerns suffer because the management has neglected to provide a constantly available source of employees with management skill. They have completely overlooked the important fact that as any firm grows older, so does its present personnel. Depending on being able to "pick up" such individuals as they are needed can be the undoing of a service business operation.

Protect against hazards. It is always best to provide the maximum protection the budget will allow against every possible business hazard. Too often, such protection is scaled down or management "takes a chance" in the early days of the business. These are invariably the concerns which never build to leadership. All the gains of any business can be wiped out overnight when such protection is absent, and that is usually what happens to inadequately protected business firms. There is never a tomorrow, profitable or otherwise, for such firms.

Watch your own health. Failure to follow this rule has accounted for the demise of far more business firm's (or failure to grow and prosper from small beginnings) than is commonly imagined. The shop owner should make it one of his cardinal business principles to protect his own health as carefully as he protects that of his business. The chance for growth and success can pass him by—as it has many others—because it came at a time when his health was bad.

Finally, *it pays to keep the number of long-range fixed commitments of all kinds to a minimum.* Too many of these can tie a shop owner's business hands so tightly that he will be unable to grasp forthcoming opportunities as they appear.

Color Training

(Continued from page 40)

axis and the output is fed to the red grid of the CRT. The right side of L31 is a filter which attenuates the 3.58-MHz ripple. Since the right deflection plate of V21 is driven 180° out of phase with the left deflection plate, the right side of V21 is operating on the $-(R-Y)$ axis, another way of saying that its output polarity is reversed. In the same fashion, the right side of V20 operates on the $B-Y$ axis and drives the blue grid of the CRT while the left side produces the negative or $-(B-Y)$ output.

As we have pointed out previously, the $G-Y$ signal is composed of $-.51(R-Y)$ and $-.19(B-Y)$. The signals from the left side of V20 and the right side of V21 are combined in the proper proportions and the $G-Y$ signal which results is fed to the green grid of the CRT.

Twin-Pentode Demodulators

The twin-pentode demodulator used in Admiral and Motorola receivers is still another significant variation of the conventional pentode demodulator. The circuit shown in Fig. 8 is used in the Admiral 1G1155-1 chassis.

Insofar as demodulation of the $R-Y$ and $B-Y$ signals is concerned, the operation of this circuit is not greatly different from the operation of a circuit employing a pair of pentode demodulators. The reference signal is fed to the suppressor grids at the correct phase to cause the left and right halves of the tube to demodulate on the $B-Y$ and $R-Y$ axes, respectively. After the 3.58-MHz ripple has been filtered, these plate signals are used to drive the blue and red grids of the CRT.

Before attempting to explain the method used to develop the $G-Y$ signal, we must digress somewhat to consider the distribution of the cathode current between the screen grid and plate of a pentode. An oversimplified explanation may be developed by considering what happens if the plate voltage is removed from a pentode having a low-impedance screen supply. There is an immediate increase in screen current followed by a gradual decrease as the screen-grid structure melts and flows to the bottom of

the envelope. While this demonstration is, perhaps, more dramatic than useful, it does indicate that the screen current increases if the plate current decreases.

Actually, the screen current depends to a great degree on the velocity of the electrons passing between its conductors. If the electrons are travelling at very high velocities, the positive potential of the screen grid deflects them from their path only slightly. Thus, the only electrons which impinge on the screen grid are the ones which happen to be travelling directly towards the wires of the grid. However, if the velocity is decreased, the screen grid causes more deflection of the electrons. Since the screen grid is positive, the electrons are deflected toward its conductors and more of the electrons actually strike the wires. This, of course, causes an increase in screen current.

Now, consider the electron velocity with various suppressor grid potentials. If the voltage on the suppressor is driven negative, electrons in the region between the screen and the suppressor are decelerated to a lower velocity and the screen current increases. Conversely, if the suppressor is driven positive, elec-

trons are decelerated a lesser amount, and the screen current is reduced.

A positive suppressor voltage which decreases the screen current also increases the plate current, and, while the plate swings negative, the screen swings positive. Thus, a signal on the suppressor grid may be amplified in both the plate circuit and the screen circuit. The signal is inverted between suppressor and plate, but, since a decrease in plate current is attended by an increase in screen current, the signal at the screen is in phase with the suppressor grid and out of phase with the plate.

Returning to the circuit of Fig. 8, since the signals at the two plates of V16 are $B-Y$ and $R-Y$, the common screen grid has elements of the $-(B-Y)$ and $-(R-Y)$ signals on it. However, the suppressor-to-screen transconductance is comparatively low and the $G-Y$ signal at the screen grid is insufficient to drive the green grid of the CRT. To increase the $G-Y$ signal at the screen, portions of the $R-Y$ and $G-Y$ signal from the plates of V16 are coupled back to the control grid. This signal is amplified in the control-grid/screen-grid circuit and

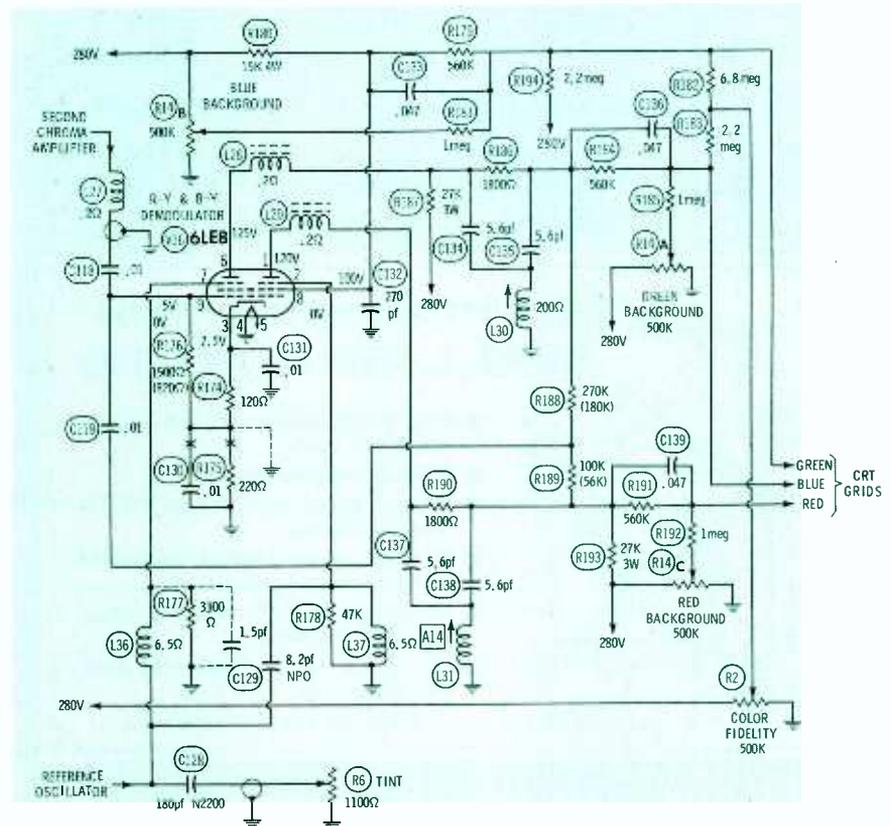


Fig. 8. Chroma demodulator of Admiral Chassis 1G1155-1.

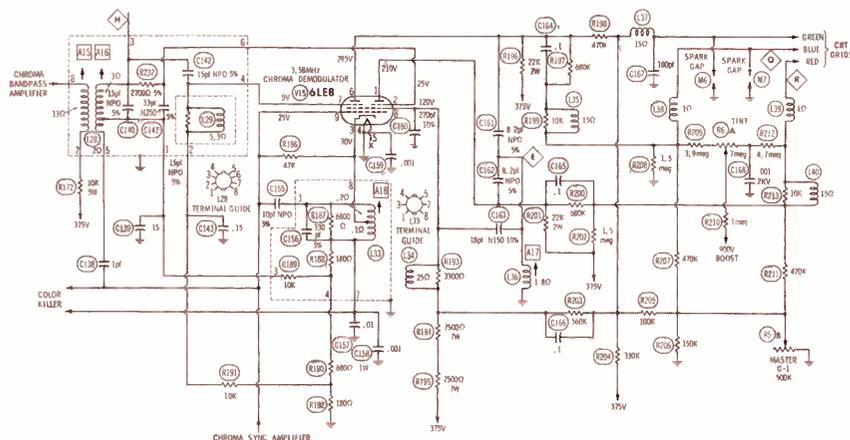


Fig. 9. Chroma demodulator of Motorola Chassis A22TS-918A.

the amplified signal adds to the G-Y signal already present at the screen. Since the (R-Y) + (B-Y) signal at the control grid is a video frequency and the chroma-signal frequency is much higher, the interaction between them is too small to be objectionable. The concept of amplifying two dissimilar signals in the same tube (reflex amplification) is by no means a new one. For example, a single tube is used as the second video IF amplifier and first sound

IF amplifier in the Muntz J chassis (PHOTOFACT Folder 444-2).

The demodulator used in Motorola chassis A22TS-918A (Fig. 9) uses the twin-pentode which serves as the reference oscillator to demodulate all three color axes. The explanation of the division of current between plate and screen grid which was given above also applies to this circuit.

In Part 5 of this series, it was pointed out that the cathode, control-grid, and screen-grid circuits of

V15 (Fig. 9) function as a reference oscillator in a Hartley configuration. In considering V15 as a demodulator, we need only remember that a high-level reference-oscillator signal is being fed to the control grid.

Since this control grid is common to both pentode sections, the reference signal cannot be split prior to demodulation. Consequently, the phase of the chroma signal is shifted between the two suppressor grids. Since the axis of a particular demodulator depends on the relative phases of the reference and chroma signals fed to it, it is not important where in the reference or chrominance circuits the phase-shifting network is located. In Fig. 9, the phases of the chroma signal are established by L28 and its associated components so that the left plate of V15, pin 6, demodulates on the B-Y axis and the right plate, pin 1, demodulates on the R-Y axis.

Because the division of current between plate and screen grid is determined by the instantaneous voltage of the suppressor grid, elements of the -(R-Y) and -(B-Y) signal are present on the screen grid of V15. A portion of the B-Y signal from the junction of R208 and R207 is added to the screen-grid signal, reducing the -(B-Y) content. The total of the three signals is the G-Y voltage fed to the green grid of the CRT. C161, C162, and C163 in conjunction with L36 are used to attenuate the 3.58-MHz ripple which is present on the plates and screen grid of V15.

THE BEST ANTENNA INSTALLATIONS START WITH . . .

South River QUALITY MOUNTING ACCESSORIES

THE MOST COMPLETE LINE IN THE INDUSTRY


South River "Y" TYPE 6"/9"/12"/15"/18"/24" WALL BRACKETS

- Quality-engineered with heavy gauge embossed steel.
- Riveted construction.
- Tubular tripod support legs for additional rigidity.
- Factory pre-assembled; complete with all mounting hardware.
- Choice of "U"-bolt type or snap-in type mast holders.
- Feet with snap-lock feature for easy wall mounting.

SEND FOR COMPLETE CATALOG

AT SOUTH RIVER QUALITY IS OUR MOST IMPORTANT PRODUCT
SOLD THROUGH DISTRIBUTORS
SOUTH RIVER METAL PRODUCTS CO., INC. / SOUTH RIVER, N. J. 08882

Fig. 10. CRT grid clampers of RCA Chassis CTC27.

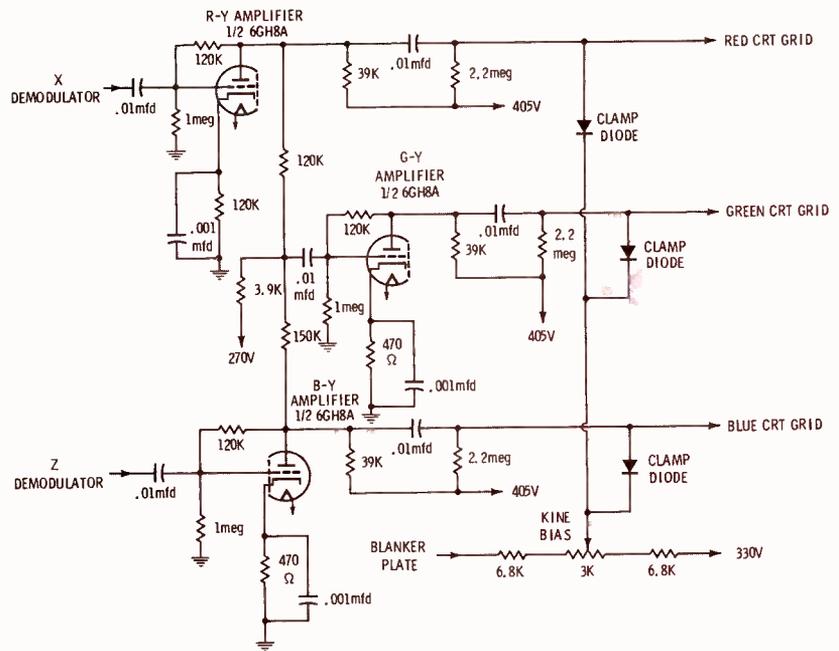

Miscellaneous Circuits

Three circuits which are being used more frequently are CRT grid clampers (DC restorers), color tracking circuits, and tint controls. Fig. 9 shows an example of the latter. R6A is connected between the red and blue grids of the CRT and allows the customer to adjust the relative conduction of these two guns.

Fig. 10 shows the CRT grid clampers used in the RCA CTC27 and CTC31 chassis. By inserting coupling capacitors between the plates of the difference amplifiers and the CRT grids, it is possible to operate these two elements at non-related DC potentials. This allows simplification of the circuits and


also precludes changes in color temperature caused by changes in the static conduction levels of the difference amplifiers. Thus, the CRT grids are not affected by aging of the difference-amplifier tubes and components.

Although the use of coupling capacitors is desirable for the reasons stated above, a means of maintaining the correct CRT grid voltages during b-w reception had to be devised. Otherwise, the right sides of the coupling capacitors would slowly charge through the 2.2-megohm resistors to 405 volts, saturating the CRT. To prevent this, a negative-going pulse with a negative peak of 180 volts positive above ground (refer to waveform in Fig. 10) is fed through the clamper

diodes to the CRT grids during horizontal-retrace time. Between pulses, the CRT grid voltages rise from 180 volts to about 181 volts, but this is insufficient to cause a noticeable change in brightness across the screen.

A method of increasing color saturation, as well as contrast, with a single control is illustrated in Fig. 11. As the contrast control is adjusted for greater contrast, the forward bias on Q1 is increased. The increased current through Q1 causes the collector voltage to decrease, reducing the positive cathode bias of the chroma bandpass amplifier and increasing its gain. Positive blanking pulses are also fed to the cathode of the chroma-bandpass amplifier. ▲


Fig. 11. Color-tracking circuit of Hoffman Chassis 913-187486.

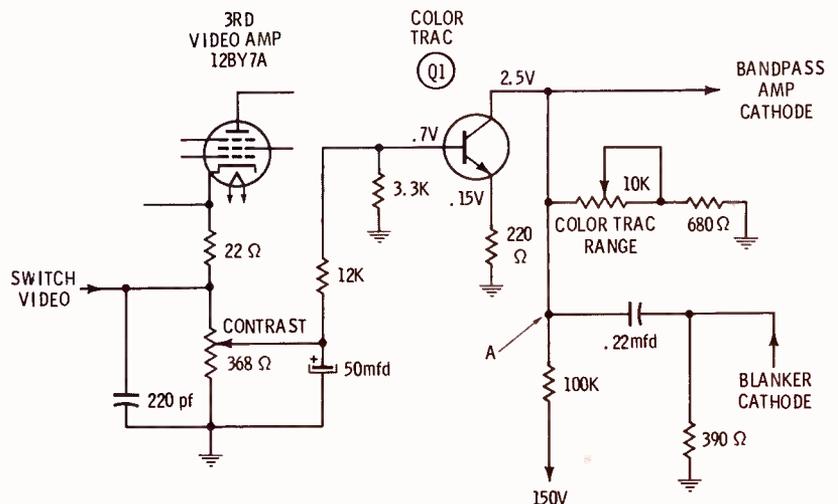

ARROW

Automatic STAPLE GUN TACKERS

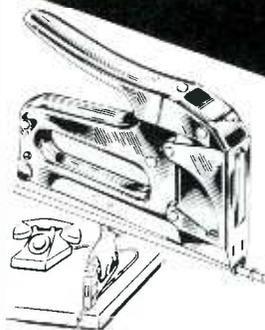Specially designed for
SAFE — FAST — SECURE
WIRE & CABLE FASTENING



No. T-18
For wires up to
3/16" in dia.
Uses round crown
staples in
3/8" leg only.


BELL, TELEPHONE, THERMOSTAT,
INTERCOM, BURGLAR
ALARM and other
low voltage
wiring.



No. T-25
For wires up to
1/4" in dia.
Uses round crown
staples in 9/32",
3/8", 7/16", and
9/16" leg.

Fastens same wires
as No. T-18

Also
used for
RADIANT
HEATING
CABLE

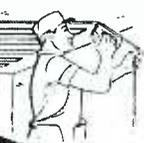

No. T-75
For wires and
cables up to
1/2" in dia.
Uses tack-pointed
staples in 9/16",
5/8" and 7/8" leg.

SHEATHED CABLE, RADIANT
HEATING CABLE WIRE
CONDUIT, COPPER
TUBING, DRIVE
RINGS, ETC.

- All-steel,
chrome finish.
- Jam-proof mechanism
for trouble-free operation

SAFE! Driving blade automatically
halts staple at right depth of penetration!
Can't cut or injure wires and cables.

FAST! Powerful single stroke action
shoots staples in 1/1000 of a second!
Saves 70% in time, effort and efficiency!

HOLDS! Staple points diverge to
imbed firmly in wood. Rosin-coated for
tremendous holding power!

Write for catalog and information.

ARROW FASTENER COMPANY INC

Saddle Brook, New Jersey 07863

"Pioneers and Pacesetters
For Almost A Half Century"

Circle 19 on literature card

Intermittents

(Continued from page 30)

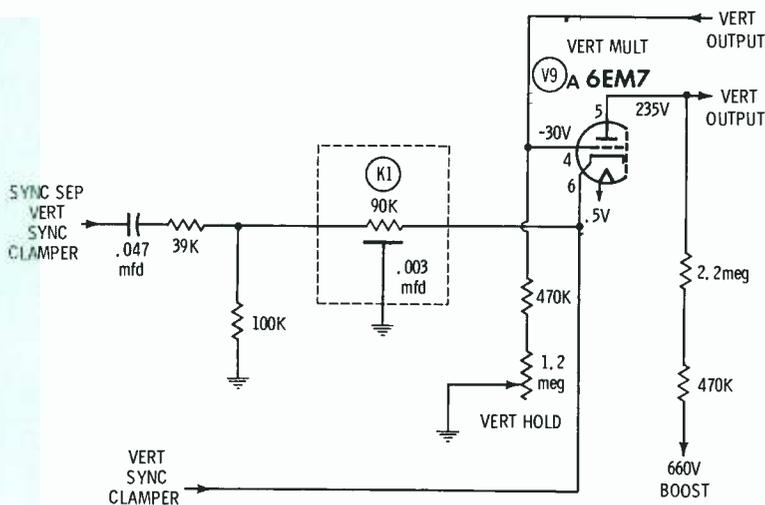


Fig. 5. Printed component caused intermittent defect in this circuit.

Back inside the shop, Ed warmed up the RF-audio signal generator, and starting at the receiver volume control, began a signal substitution procedure, working his way back toward the receiver's front end. When the generator probe was touched to the collector of Q3, the IF amplifier transistor (Fig. 4), the modulated signal was heard; however, when the probe was placed at the base of the same transistor, nothing happened. Obviously, Ed had found the defective stage.

Since the only transistor tester Ed had was an out-of-circuit checker, he removed the transistor from the circuit and clipped the tester leads to the proper transistor elements. Pressing the beta switch on the tester, Ed watched as the meter hand began to fluctuate wildly. After releasing the beta switch, Ed quickly sprayed the transistor with a cooling mist. When checked again, the transistor tester indicated a high beta reading—proof that the transistor was intermittently defective. Replacing Q3 cured the receiver's fickle playing habits.

Intermittent Vertical Roll

After a few year's experience and several intermittent trouble situations later, Ed has found that these come-and-go symptoms can be conquered in short order by proven techniques and just a little patience.

Our last account of Ed's experiences with intermittents deals with an intermittent rolling condition displayed by an RCA KCS136Y chassis. Tube substitution and control adjustments performed in the cus-

tom's home had no effect on the symptom, so Ed transported the chassis to the shop.

Because the rolling lasted for only a short period each time it occurred, Ed moved quickly. Using the scope, he traced the sync signal from the separator, through to the vertical oscillator. The sync signal at the cathode (pin 6) of V9A (Fig. 5) appeared to be reduced in amplitude. Just as Ed removed the scope probe from the cathode, the rolling stopped. Quickly, Ed checked the waveform at pin 6 of V9A again—it had returned to normal. Carefully probing around in the vertical multiplier input circuit, Ed pryed against printed component K1; the rolling suddenly started again. By moving and twisting K1, Ed could start and stop the vertical rolling.

Ed unsoldered K1 from the printed-circuit board and clipped ohmmeter leads across the resistance terminals. By twisting K1, Ed could make the meter fluctuate from 230K ohms to 90K ohms. According to the PHOTOFACT, the normal reading should be 90K ohms. Replacing K1 with a new printed component solved the intermittent rolling, and Ed could begin cooking the set within two hours of the original service call.

Conclusion

Intermittents can be tough to analyze and pin down—but they don't have to be. Logic and a few proven techniques can transform those intermittents from pains to challenges—well, almost. ▲



THE ELECTRONIC SCANNER

news of the servicing industry

Admiral Predicts 1968 Even Better

Prospects for the consumer electronics and appliance industry for 1968 are tied more closely than ever to general economic conditions, Ross D. Siragusa, chairman of the board, Admiral Corporation, said in his recent yearend statement.

"Despite such uncertainties as higher taxes next year, inflation, the prospects for escalation of the Viet Nam War, and the restlessness of labor, I am conservatively optimistic for the future," he said.


"Many of the economic perplexities of 1967 have been resolved and business generally is in a good position to move ahead, although the competitive pressures of higher labor and material costs will continue. Inventories have been reduced and brought into proper perspective.

"While this year's industry distributor sales of color television receivers will show an increase of 12% over 1966 volume, we expect 1968 movement to increase about 14% to 6,000,000 sets. While any industry would be gratified with an annual sales increase of 12% over the preceding year, the rate of increase in 1966 was so abnormal—about 70%—that it makes the color TV growth in 1967 seem pale by comparison.

"Color TV sales will surpass black-and-white business for the first time, since we are estimating sales of approximately 4,700,000 monochrome receivers in 1968 for a total of nearly 11,000,000 sets." The Admiral chairman said he believes that future expansion of color television sales will be at a more normal level and will enable the industry to grow in a less hectic manner with fewer problems.

Mr. Siragusa said that radio business continues at a high level and attributed this to the expansion of FM radio and increasing acceptance of multi-band models. Distributor sales of 13,500,000 American-branded ra-

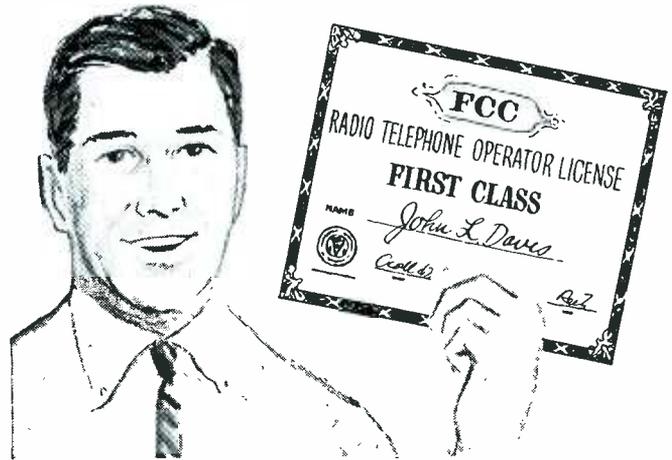For a top job in Radio-TV ... get a FIRST CLASS FCC LICENSE ...or your money back!



Your key to future success in electronics is a First-Class FCC License. It will permit you to operate and maintain transmitting equipment used in aviation, broadcasting, marine, microwave, mobile communications, or Citizens-Band. Cleveland Institute home study is the ideal way to get your FCC License. Here's why:

Our electronics course will *quickly* prepare you for a First-Class FCC License. Should you fail to pass the FCC examination after completing your course, you will get a *full refund* of all tuition payments. You get an FCC License ... or your money back!

And only CIE offers you new, up-to-the-minute lessons in all these subjects: Logical Troubleshooting, Microminiaturization, Single Sideband Technique, Pulse Theory and Application, Boolean Algebra, and many more.

You owe it to yourself, your family, your future to get the complete details on our "proven effective" Cleveland Institute home study. Just send the coupon below for FREE book or write to Cleveland Institute of Electronics, 1776 E. 17th St., Dept. PF-44 . Cleveland, Ohio 44114.

ENROLL UNDER NEW G. I. BILL

All CIE courses are available under the new G.I. Bill. If you served on active duty since January 31, 1955, OR are in service now, check box in coupon for G.I. Bill information.



MAIL COUPON TODAY FOR FREE BOOK

CIE Cleveland Institute of Electronics
1776 East 17th Street, Cleveland, Ohio 44114

Please send me your FREE book, "How To Get A Commercial FCC License."

Name _____ (please print)

Address _____

City _____ State _____ Zip _____

Occupation _____ Age _____

Veterans check here for GI Bill information

Accredited Member National Home Study Council
A Leader in Electronics Training . . . since 1934 **PF-44**


Circle 20 on literature card

February, 1968/PF REPORTER 51

LEADER TEST INSTRUMENTS

Much in little

New!

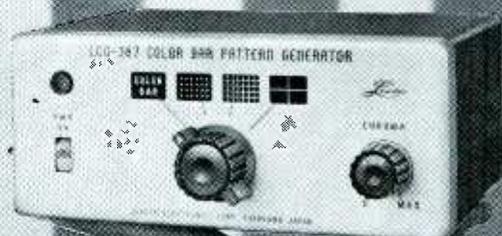

\$13450

LCG-387

COLOR BAR PATTERN GENERATOR

Here it is—LEADER's new color bar pattern generator which includes the keyed rainbow, SQUARE crosshatch, dots, AND the single cross bar. In fact, this cross pattern will speed up adjustments on raster centering, purity at the center and dynamic convergence. Sharp and clear lines, both vertical and horizontal, produced by return trace blanking. Two switchable channels, 5 and 6, with 10mV output. Solid state, of course, with voltage regulated supply. Compact and sturdy construction for field use—supplied with carrying bag for convenience. Size only 2 $\frac{3}{4}$ " H × 6 $\frac{3}{4}$ " W × 4 $\frac{3}{4}$ " D in., and weight 3.3 lbs approx.

LEADER ELECTRONICS CORP.

NEW YORK OFFICE

101-103 ROME ST., FARMINGDALE, L.I., N.Y. 11735

TEL (516) 694-1534 541-5373

Circle 21 on literature card

dios are anticipated next year, compared with an estimated 12,800,000 in 1967. This does not include imported brands which should add up to a total of approximately 20,000,000 radios.

Portable and console stereo phonograph sales are expected to increase 10% to a total volume of 5,800,000 units.

Mergers & Expansions

Belden and Complete-Reading Electric Co., of Chicago, announced an agreement in principle for Belden to acquire Complete-Reading and its subsidiaries. Terms of the negotiation provide for the issuance of approximately 65,000 shares of Belden stock. Complete-Reading is a diversified distributor with sales divisions in Chicago, Cleveland, Kansas City, Houston, Pittsburgh and Mexico City. Its sales for the fiscal year ended October 31, 1967 were \$9 million.

The Pink ribbon to **EICO's** new headquarters plant was officially cut at the recent ceremonies by Brooklyn Borough President Abe Stark, in the presence of members of the press and company officials.

The new air-conditioned EICO building is a one-level 100,000-square foot high-efficiency manufacturing structure. In addition to management offices, it houses enlarged facilities for engineering, quality control and consolidated production of both wired and kit equipment—and provides amply for future expansion.

General Telephone & Electronics International announced the formation in Venezuela of a new subsidiary, Sylvania Venezolana, C.A., and the start of construction on a plant which will manufacture black-and-white television picture tubes. The new company was formed to consolidate and expand Sylvania marketing efforts in Venezuela and to manufacture TV picture tubes and sets. Sylvania sets presently are assembled in Caracas.

Jensen Manufacturing Division, The Muter Company started to move into its new plant facilities in late December. The 174,000 sq. ft. plant more than doubles Jensen's previous facilities in Chicago. The corporate offices of the Muter Company will be housed in the new building as well as Jensen's offices, engineering staff and manufacturing operations.

Chamberlain Manufacturing Company and Perma-Power have signed an agreement providing for the acquisition by Chamberlain of substantially all the assets and business of Perma-Power in exchange for common stock of Chamberlain. The closing is scheduled for early in 1968. Perma-Power will continue its operations, under the same management, as a division or subsidiary of Chamberlain. Perma-Power's garage door openers make a natural combination with the garage doors manufactured by Chamberlain.

STDP Gets Exposure

The **Electric Industries Association's** Consumer Products Division began implementing the first phase of its Service Technician Development Program (STDP) by means of an intensive "win friends and influence people" effort at the recent American Vocational Association (AVA) annual convention at the Sheraton-Cleveland Hotel. The AVA represents some 45,000 vocational education teachers and counsellors and is considered a major factor in that field.

The STDP is the EIA Consumer Products Division's long-range effort aimed at increasing the number of qualified service technicians for consumer electronic products. Over half a million dollars has been earmarked for this manufacturer-sponsored effort over the next five years. One thrust of the program will seek to work closely with vocational educators and counsellors at the secondary school level.

The STDP eventually intends to influence and improve electronics teaching at the classroom level all over the country through teacher training seminars and institutes, curriculum upgrading programs and consultation services. In conjunction with a public relations and career guidance program, these activities are intended to gradually bring more and more well-trained and well-motivated young people into consumer electronics servicing as a career.

New Camera Tube

A new television camera tube developed at **Bell Telephone Laboratories** combines the best features of the vidicon with the highly developed silicon technology used in integrated circuits. This marriage of tube and semiconductor technologies removes certain shortcomings of present camera tubes and promises a more rugged and longer-lived, more sensitive camera tube. The new tube is being used in the Model II PICTUREPHONE® set.

The heart of the tube is a new type of target structure consisting of a self-supporting silicon wafer the size of a nickel, containing over half a million silicon photo-diodes in an area less than one-half inch square. The target, only 2 mils thick, is fabricated using techniques identical to those used in making silicon integrated circuits.

One advantage of the silicon target in the new camera tube is that its performance is not degraded or modified by exposure to bright light sources or by electron beam bombardment. In conventional camera tubes bright lights or long exposure to fixed scenes can cause optical burn-in, resulting in a lingering ghost pattern superimposed on the displayed images. Image defects caused by optical burn-in are so severe that the lifetime of standard television camera tubes is reduced. Conventional television camera tubes also exhibit a similar defect known as raster burn-in, which is produced by the scanning electric beam. Neither form of burn-in occurs in the silicon camera tube because the electrical and optical properties of crystalline silicon are not modified by exposure to intense light or by bombardment from a low energy electron beam. ▲

Weller®

...the soldering tools professionals depend on



The original Dual Heat Soldering Guns

Preferred by technicians for their fast heating copper tips, exclusive trigger-controlled dual heat, and high soldering efficiency. Available in 3 wattage sizes, each with spotlight.

100/140-watt Model 8200, 145/210-watt Model D-440, and 240/325-watt Model D-550. Also in complete kits:

- **Model 8200PK** includes 100/140 watt gun, extra tips, tip-changing wrench, flux brush, soldering aid and solder
- **Model D-550PK** heavy-duty 240/325 watt gun kit with soldering, cutting and smoothing tips, wrench and solder

Dependable MARKSMAN Irons in a size for every job



Ideal for deep chassis work and continuous-duty soldering, Marksman irons outperform others of comparable size and weight. All five feature long-reach stainless steel barrels and replaceable tips.

- 25-watt, 1¾-oz. Model SP-23 with 1/8" tip (In kit with extra tips, soldering aid, solder—Model SP-23K)
- 40-watt, 2-oz. Model SP-40 with 1/4" tip
- 80-watt, 4-oz. Model SP-80 with 3/8" tip
- 120-watt, 10-oz. Model SP-120 with 1/2" tip
- 175-watt, 16-oz. Model SP-175 with 5/8" tip

NOW a BATTERY OPERATED IRON for field servicing

Use this lightweight service tool for automotive wiring, model planes, or mobile communications. Works from any 12 volt battery or 12-14 volt AC/DC supply. Supplied complete with long-life patented "Temperature Sensing" tip, 12-ft. power cord and terminal clips. Model TCP-12—12 volt; Model TCP-24—24-28 volts.



Complete Weller Line includes replacement tips and solder at your Electronic Parts Distributor

WELLER ELECTRIC CORPORATION, Easton, Pa.

WORLD LEADER IN SOLDERING TOOLS

Circle 22 on literature card

February, 1968/PF REPORTER 53

FAST

COMPLETE OVERHAUL ON ALL MAKES OF TV TUNERS

Maximum Time In Shop 24 Hrs.

(WE SHIP C.O.D.)

\$9.50




Black &
White
or Color

VHF or
UHF

UV Combo's \$15.00

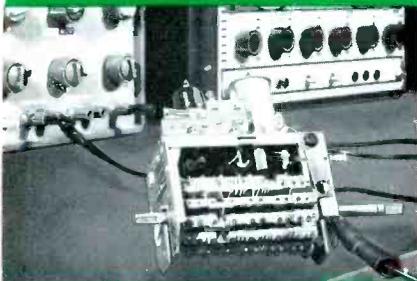Price includes all labor and parts except Tubes, Diodes & Transistors. If combo tuner needs only one unit repaired, disassemble and ship only defective unit. Otherwise there will be a charge for a combo tuner. Ship tuners to us complete with Tubes, Tube Shields, Tuner Cover and all parts (including) any broken parts. State chassis, model number and complaint.



All tuners are serviced by **FACTORY TRAINED TECHNICIANS** with years of experience in this specialized field. All tuners are **ALIGNED TO MANUFACTURERS SPECIFICATION** on crystal controlled equipment and air checked on monitor before shipping to assure that tuner is operating properly.

GEM CITY TUNER REPAIR SERVICE

Box 6C Dabel Station
2631 Mardon Drive
Dayton, Ohio 45420

Circle 23 on literature card

54 PF REPORTER/February, 1968

LETTERS TO the EDITOR

How to Use Signal Generators in Color TV Servicing: John D. Lenk; John F. Rider Publisher, Inc., New York, N.Y., 1967; 97 pages, 8 7/8" x 6", soft cover; \$3.25.


Although it is possible to operate a piece of test equipment without a thorough understanding of its basic circuitry, the lack of such knowledge can limit the versatility and, in some instances, the accuracy of the instrument. Also, when trouble develops within the instrument, the technician must rely on someone more familiar with the circuitry to repair it.

It is the obvious intent of this text to overcome such shortcomings, as they relate to color generators, by completely familiarizing the technician with the signal generators commonly employed in color TV servicing.

The text begins with a block diagram presentation of the operating principles associated with keyed and unkeyed rainbow generators, NTSC-type generators, and the flying spot scanner video generator. The operating controls and basic operating procedures of these instruments are outlined in Chapter 2. Chapter 3 discusses the testing and calibration of color generators, including percentage-of-modulation, output, chroma- and Y-signal, shading-bar, and burst-signal checks of NTSC-type generators.

Specific applications of color generators are described and analyzed in Chapters 4 through 7, including purity, convergence, and linearity adjustments; and testing of color sync, chroma demodulation, and matrix circuit characteristics. In addition, Chapter 8 discusses a variety of uncommon and miscellaneous generator applications such as picture-detector output, IF signal, and bandpass amplifier output checks; as well as various methods of localizing color troubles.

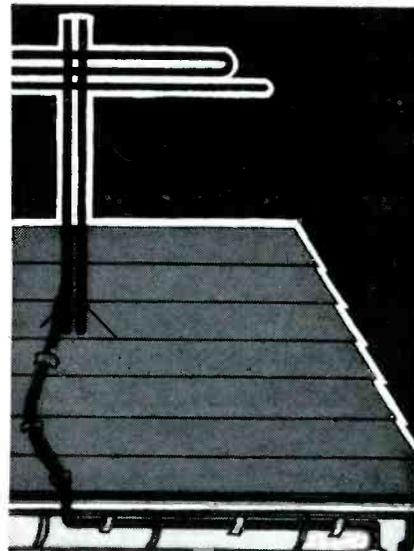An understanding of color TV theory is essential to the understanding of the content of this text. ▲



When the cable goes down the gutter... does the picture go down the drain?

Not with Columbia Wire's new ultra-low loss shielded Permafoam transmission cable! You can tape it to the antenna mast... run it down gutters... tape it to downspouts... lead it in by the quickest, easiest route... and there's **never any pickup interference!** And the antenna terminals are already installed for you... so you get the job done faster than you ever have before... easily terminated. Shielded Permafoam cable makes set hookup more profitable. Ask for a spec sheet at your distributor.



Available in 50', 75' and 100' coils — 500' spools and 1000' reels.

Columbia 
WIRE PRODUCTS COMPANY
2850 Irving Park Rd., Chicago, Ill. 60618

Circle 24 on literature card

NEW

GOOD BAD

Transistor Testing... in or out-of-circuit!

- No guesswork or confusion
- No numerical readings to interpret.



NEW LECTROTECH **TT-250** TRANSISTOR ANALYZER

One Year Warranty

IN-CIRCUIT TESTS. Positive Good/Bad in-circuit and out-of-circuit testing. No numerical readings to interpret. In-circuit testing is a measurement of dynamic AC gain. No transistor leads to unsolder or disconnect.

OUT-OF-CIRCUIT-TESTS (BETA OR GAIN). Measures transistor Beta or Gain on 2 scales: 0 to 250 and 0 to 500. Automatic biasing . . . no calibration required.

LEAKAGE. Measures transistor leakage. (I_{cbo}) directly in microamperes.

DIODES AND RECTIFIERS. Measures reverse leakage and forward conduction directly to determine front-to-back ratio.

POWER TRANSISTORS. Simple Good/Bad test instantly determines condition of power transistors. Power Transistor Socket on panel for ease of testing.

ELECTROLYTIC CAPACITORS. Measures leakage current of transistor electrolytics at a test voltage of 6 volts.

PNP OR NPN determined immediately . . . no set-up book needed for testing.

NON-DESTRUCTIVE TESTING. Regardless of misconnections, you cannot damage transistors or components tested.

SPECIFICATIONS

- Large easy to read 6" meter • 3 color-coded test leads with self-storing feature • Power and Milliwatt Sockets on panel for ease of out-of-circuit testing • Zener Diode Regulated Power Supply • All steel case • Size: 10½" x 7" x 4" • Wt. 5½ lbs. • 115 volts, 60 cycles.

NET **87⁵⁰**



See your distributor or write . . . DEPT. PF-2

LECTROTECH, INC.


1221 W. Devon Ave., Chicago, Illinois 60626

Circle 25 on literature card

COLOR

COUNTERMEASURES

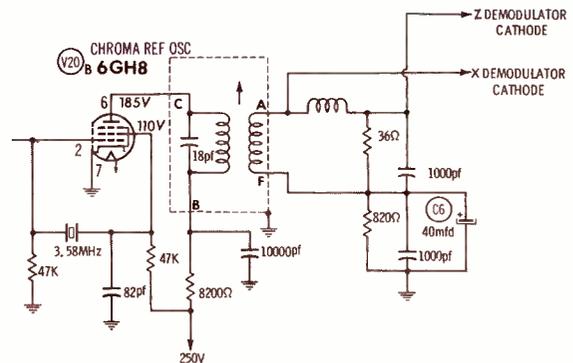
SYMPTOMS AND TIPS FROM ACTUAL SHOP EXPERIENCE



Chassis: RCA CTC10

Symptom: Spaces between color bars of keyed rainbow color pattern are predominantly green instead of neutral.

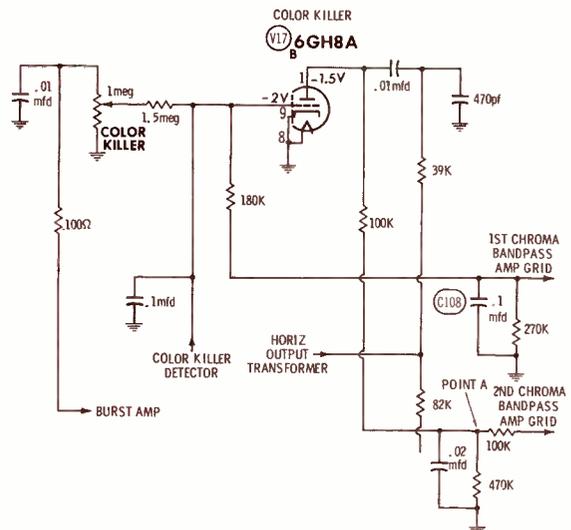
Tip: Possible cause of trouble is open C6 in common cathode circuit (phase shifting network for output of chroma reference oscillator) of chroma demodulators.



Chassis: Admiral G11 and G13

Symptoms: No color or intermittent color.

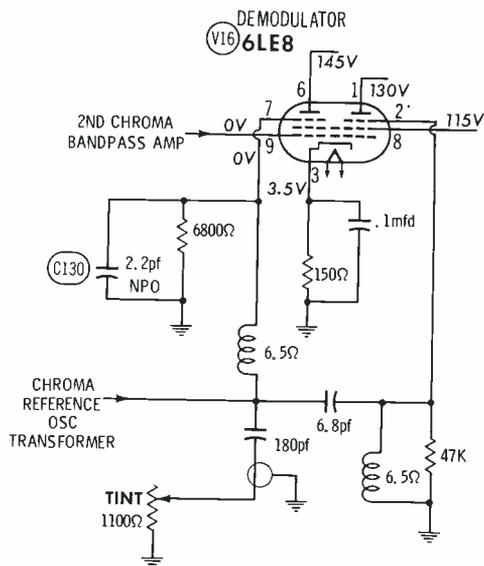
Tip: Possible cause of trouble is leaky C108. If this is trouble, grounding point A should restore color. Replace defective capacitor.



Chassis: Admiral G11

Symptoms: Poor reproduction of greens (not caused by a component defect).

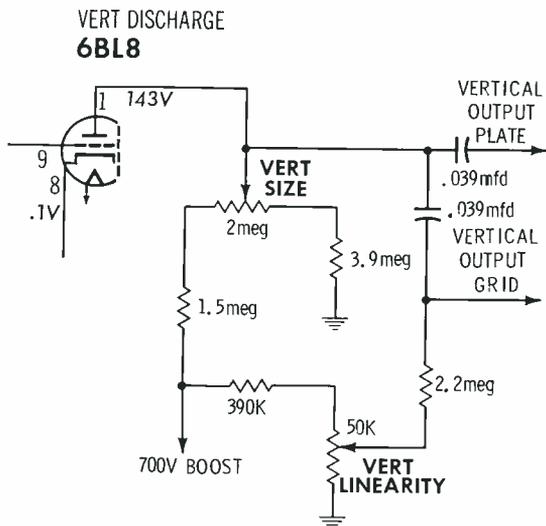Tip: Condition can be improved by removing C130 from circuit. (After removal of C130, it may be necessary to readjust the chroma reference oscillator plate transformer for correct tint control range).



Chassis: Motorola TS-914

Symptoms: Raster height reduced.

Tip: Before performing routine troubleshooting of vertical section, check horizontal output tube for gassy condition. Defective horizontal output tube reduces boost voltage that is supplied to plate of vertical discharge tube via vertical size control and to grid of vertical output tube via vertical linearity control. Vertical trouble symptom usually appears before horizontal trouble symptom is obvious.

Swing-O-Lite ONE OF AMERICA'S LEADING SOURCES...
THE RIGHT LIGHT AT THE RIGHT PRICE!

Who Says Top Quality Has to Cost More?

INCANDESCENT ALL-PURPOSE LAMP Model BB-45

The basic work-tool of industry, proven in installations everywhere.

- Full 45" Arm Reach
- Completely Flexible, Yet "Freezes" in Any Position

FLUORESCENT MAGNIFIER-LAMP Model BBM-9

One of several popular types essential for inspection of work, schematics, blueprints, miniature assemblies. Basic to production line and research laboratories.

- Full 45" arm reach
- 5" Diameter Magnifying Glass with Powerful 13" Focus

Colors: Grey, Desert Tan, Dark Brown.

"ROBOT" FLUORESCENT LAMP Model SF-2-15

Presto lighting where, when you need it. Automatic stops prevent slipping, wire twisting. Superb construction.

- Full 45" arm reach
- Low Power Usage with 2 Bulbs
- Adjustable Tension Control
- All Metal Construction - Outlet in Base

All Lamps Available with Optional Mounts.

Write for full descriptive literature to Dept. PF-28

Approved We have lamps for every purpose, including hi-intensity.

Swing-O-Lite 13 Moonachie Road INC. Hackensack, N.J. 07601

Circle 26 on literature card

Discriminate Between Desired Signal and Unwanted Noise

FREE SPACE STANDING WAVE MAGNETIC ANTENNA UHF-VHF-FM-COLOR

Investigate now!

S&A Electronics Inc.

Manufacturers of the TARGET ANTENNA

Phone 419-693-0528

206 West Florence Street Toledo, Ohio 43605

Circle 27 on literature card

a detector so sensitive as to be unstable and susceptible to noise. For these and other reasons, a special megohm bridge is advisable.

Fig. 7 shows the basic circuit of a megohm bridge typified by the General Radio Type 544-B. This arrangement is seen to be similar to the conventional Wheatstone bridge except for guard terminals and paths (to minimize the effects of surface resistance of the unknown and standard resistors and of leakage between the unknown terminals and from terminals to ground) and the

inclusion of a sensitive DC VTVM-type of null detector (triode V1) in the bridge.

The dial of balance-control rheostat R2 is direct reading in megohms, and standard resistors R3 through R7 are switched by means of S1 to change range (i.e., to multiply the reading of R2). In the General Radio bridge, these standard resistors extend from 10K ohms to 100 megohms; R1 is 100K ohms; and R2, 12K ohms.

The DC input voltage often is high (say, 500 volts) to permit test-

ing R_x under actual working conditions and to provide an off-balance output voltage high enough to ensure accurate null adjustment.

AC Bridge

Where desired, a resistance bridge may be used with an AC generator and an AC detector. One reason for choosing the AC procedure is the easily obtained high detector sensitivity in such high-input-impedance indicators as vacuum-tube millivoltmeters, amplifier-type meters, and oscilloscopes.

From Fig. 8, the bridge is seen to be conventional. While, for simplicity, a meter (M) is shown as the null detector in this circuit, the detector may be any one of the devices mentioned earlier. The generator usually is an oscillator (conventional test frequencies are 120, 400, 500, and 1000 Hz). For a sharp null, either the bridge signal must be harmonic-free or the detector must be sharply tuned to the fundamental frequency of the signal.

Problems of isolation and strays are more pronounced here than in DC bridge circuits, and are solved in various ways. For example, well

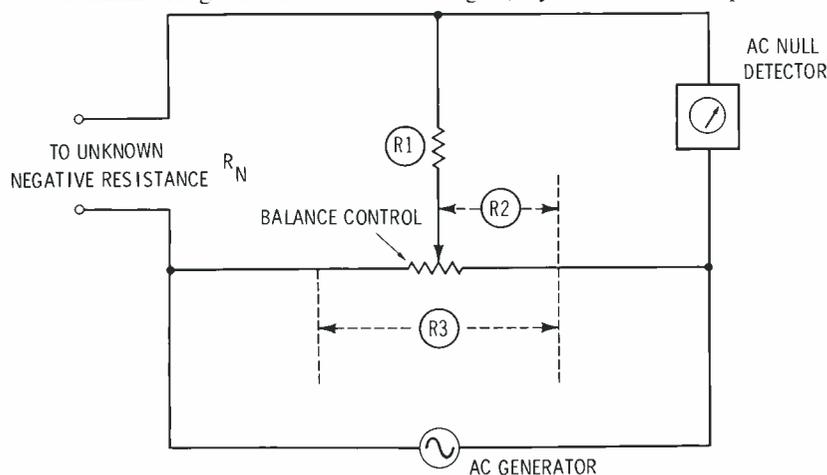


Fig. 9. Negative resistance bridge displays unconventional design.

Why not sell the best


Now...get
genuine Zenith parts
three ways faster—
with ZIP!

Your Zenith Distributor has a revolutionary new system to speed your replacement parts ordering. Called "ZIP" (Zenith Instant Parts), it gives you much improved service.

1. Looking up parts numbers is 100% quicker than before. Because parts lists and schematics for the past ten years are now microfilmed on compact, easily-handled filmcards.

2. "Out-of-stocks" are cut down. The new ZIP program helps your Zenith distributor keep tighter inventory controls and maintain a more complete stock.

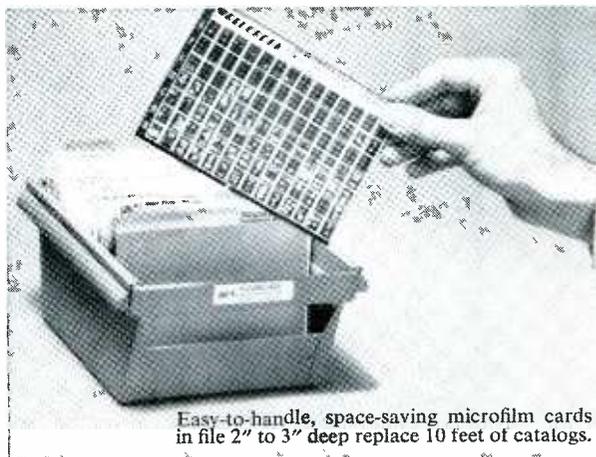3. Factory special orders are shipped faster. Under the new ZIP program, the Zenith factory is geared to ship orders without delay.



Easy-to-handle, space-saving microfilm cards in file 2" to 3" deep replace 10 feet of catalogs.

Order from your Zenith Distributor for "Zenith Instant Parts" service on all genuine Zenith replacement parts and accessories.

ZENITH®
The quality goes in before the name goes on

shielded isolating transformers (T1 and T2) are inserted between the generator, bridge, and detector. (In some instances, one of these transformers—often T-2—is omitted). In addition, either point X or point Y (but not both) may be grounded. The shortest practicable leads (preferably shielded) must be employed between generator, bridge, and detector. Additionally, efficient high-frequency operation (20 KHz and beyond) requires that each bridge arm be individually shielded. Reactive components in the bridge arms must be minimal; otherwise, the bridge will be balanced for complex impedance instead of simple resistance. (Standards, ratio arms, and balance control therefore are designed for extremely low inductance and capacitance). The harmful effects of stray reactance are most pronounced at high frequencies and high resistance values.

A standard Wheatstone bridge may be adapted for AC measurement of resistance by replacing its battery and galvanometer with an AC source (of suitable voltage output) and an AC detector. Isolating transformers enhance the accuracy of measurement and should be used unless they are already provided in the generator and detector.

Negative Resistance Measurement

Although the circuit shown in Fig. 9 is not a conventional bridge, it permits measurements of negative resistance by the null method which is common to bridge operation. An AC test signal (e.g., 1000 Hz) is supplied by the generator, and the null is indicated by a high-impedance detector such as a vacuum-tube millivoltmeter.

The unknown negative resistance, R_N , is connected to terminals X-X, and the balance-control potentiometer, R_3 , is adjusted for null. At null: $R_N = R_1 (R_3/R_2) + (R_3 - R_2)$.

To prevent swamping the negative resistance, the positive resistance (R_T) of the measuring circuit must be significantly higher than the negative resistance. For best results, $(R_3 - R_2) + 1/R_1 + [1/(R_2 + R_1)]$ must be much higher than $10R_N$.

Part 2 of this article will continue our review with a discussion of capacitance and inductance measuring bridges. ▲

BOOK REVIEW

Understanding and Using Your Oscilloscope: Edited by William A. Stocklin; Allied Radio Corp., Chicago, Illinois, 1967; 128 pages, 8½" × 5½", soft cover; 75c.


If you need to know how an oscilloscope works—and how to use it for everyday servicing—this book should fit your needs. Written for students and apprentice technicians, it also will be valuable to the many service technicians who have never really learned how to get the most out of their scopes.

Starting with a brief history of cathode-ray tubes, Chapter 1, the text proceeds logically to the circuit analysis of a simple oscilloscope in Chapter 2. Chapter 3, entitled "Interesting Applications for an Oscilloscope," shows how to use the scope to measure AC voltages and currents, and introduces signal-tracing techniques in radio and TV service. Chapter 4 presents a detailed analysis of the formation of Lissajous patterns, square waves, and peaked waves, followed by a discussion

of how these various waveforms are modified by distortion, phase shifts, and nonlinearity.

Chapter 5 should be of special interest to anyone who is contemplating the purchase of a scope. A number of circuit features, such as DC, wide-band, dual-trace, and differential-input vertical amplifiers, are explained. Several pages are devoted to explaining the advantages of using a triggered-sweep oscilloscope, particularly for servicing TV chroma circuits. The final pages of this chapter summarize the requirements for a scope to be used in each of several service applications: audio, AM radio, FM radio, TV, and industrial electronics.

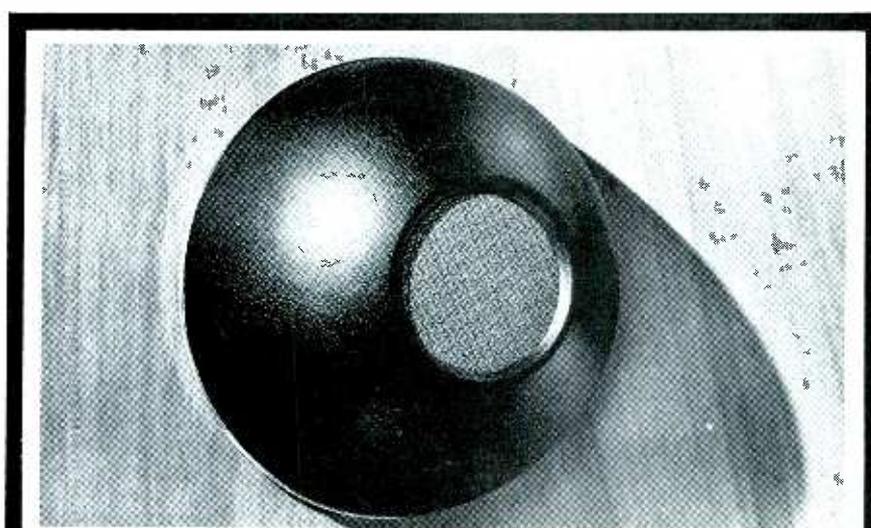Chapter 6, "Auxiliary Equipment" discusses the use of sweep generators, marker generators, pulse generators, color-bar generators, and probes, and should be of interest to anyone. Chapter 7 covers kits and will interest only those who are planning a construction project. ▲



THE FIRST NEW IDEA IN A SPEAKER ENCLOSURE COMBINATION IN 20 YEARS

REDUCES YOUR COST
REDUCES INSTALLATION TIME
INCREASES YOUR PROFIT

For complete information,
send for Brochure #673.

OAKTRON INDUSTRIES, INC.
Monroe, Wisconsin 53566



Circle 30 on literature card


PHOTOFACT TROUBLE-SHOOTER

Wrong Resistance?

I have an Admiral Model 14YP3C, covered in PHOTOFACT 350-1. The PHOTOFACT resistance table gives a value of 5.2 megohms from pin 2 V10 to ground. I read only 1.3 megohm. When I unsolder the grounded end of R66, I read 5.2 megohms from the unsoldered end to Pin 2 V10. I have substituted all parts on the line, and the results are the same. All other readings on the tube are normal, and the tube operates OK in another set. What am I doing wrong?

ROBERT HEMPHILL SR.

Cleveland, Ohio

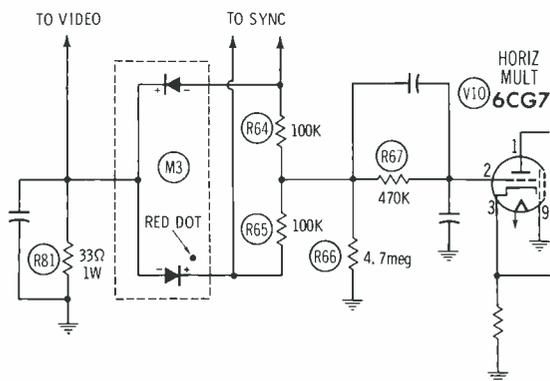

Unfortunately, there was an error in the PHOTOFACT. As can be seen the actual resistance will be 470K ohms plus the resistance made up of R66 in parallel with R64, R65, M3, and R81. Since the resistance of M3 can vary widely, depending on the ohmmeter used, the reading could be anything from about 600K ohms to several megohms. The 1.3 megohms you measure sounds reasonable.

We have entered a correction in the records, and future printings of PHOTOFACT 350-1 will contain this change. Thank you for drawing our attention to this error.

No Boost

I'm having trouble with HV, boost, and raster in a Westinghouse V2372-27 (PHOTOFACT 388-3). The hori-

zontal output transformer was open, and I replaced it with a Merit HV-168. Since the replacement, the set has had low HV and low boost. I can get a raster at about 1/2 rotation of the brightness control, but the raster rapidly fades out. The boost reading is 350V, and should be 660V. Is it possible the Merit HVO-168 is not an exact replacement for this set?

HENSEL LYONS

Baltimore, Md.

The Merit HVO-168 should serve fine in your set. Though the DC resistance and inductances are slightly different than the original flyback, the ratios between windings are the same. Like all PHOTOFACT Folder recommended replacements, the Merit flyback was actually tried in the chassis in question, and it functioned properly. We suggest you thoroughly recheck your wiring, especially the boost-forming capacitor. If this fails to turn up the trouble, look for defective components in the boost, damper, and yoke circuits.


Another Inch of Width

The PHOTOFACT alignment procedure for the RCA KCS109 (PHOTOFACT 392-3) seems rather difficult. To get to the overall alignment check point "B", it is necessary to remove and dismantle the tuner. Is there an alternative method?

On another KCS109, I just barely was able to fill the screen, after replacing the rectifiers and handpicking the horizontal output and damper tubes. Any suggestions?

C. R. WILLIAMS

Baltimore, Md.

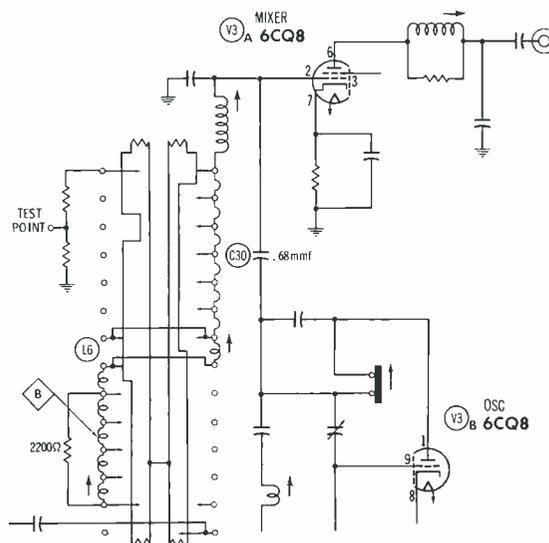

As an alternative to the injection point "B", you may clip pin 9 from the 6CQ8, and inject the signal at the test point (it's in a hole in the chassis), or through an ungrounded tube shield. Clipping pin 9 disables the oscillator. A slightly weak or used 6EA8 or 6U8 with pin 9 clipped will work equally well in this case, since the operating frequency and amplification are of slight importance. The main thing is to couple a signal to the plate.

Wayne Lemon's book "Servicing Horizontal Sweep Circuits" (Sams catalog No. 20225) has a section titled "How to get another inch of width."


Among the points he mentions are: Check the drive, check B+, check screen voltage on output tube, check for open screen bypass, etc. etc. He also gives some novel tips, including: Remove the width coil entirely, or add a 33 pf, 4KV capacitor from plate to cathode on the damper. A complete explanation on the whys and wherefores of these "unauthorized modifications" is included in the book. It's interesting reading!

Kind Words

I would like to take this opportunity to thank you for helping me solve an intermittent horizontal sync problem. I followed your advice, using a freezing spray on the parts you suggested. The 4700-pf capacitor shunting the ringing coil proved to be the culprit. Troubleshooting time—about 3 minutes. Many thanks for your kindness.

J. F. DALY

New York, N.Y.

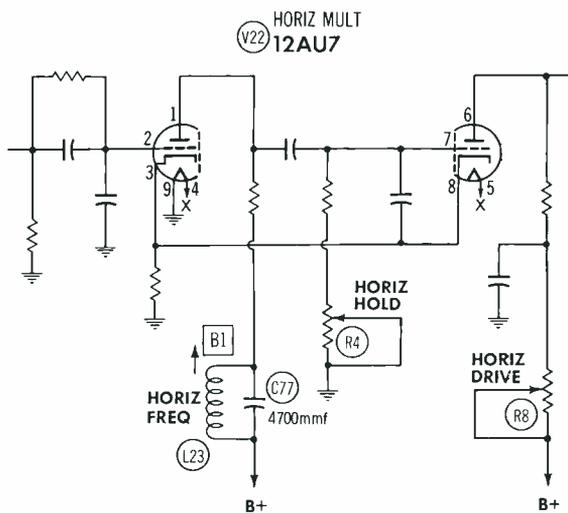


Thanks to you, too, Mr. Daly, for confirming our diagnosis. The original problem was an RC-101 TV receiver (PHOTOFACT 142-10) that would drop out of sync during warmup. Our advice: "The trouble is probably caused by a thermal drift of one of the frequency determining components in the horizontal oscillator."

"Several parts could cause this problem and it is usually easiest to locate these defects with one of the freeze sprays obtainable at your distributor. Just perform a quick horizontal alignment from a cold start, and when the set drops out of sync, spray the suspected components one-by-one until the set falls back into sync."

As can be seen, there are more troubleshooting tools than just meters and scopes. Problems of this nature can often be ferreted out with freeze spray in less time than it takes to hook up the scope. ▲

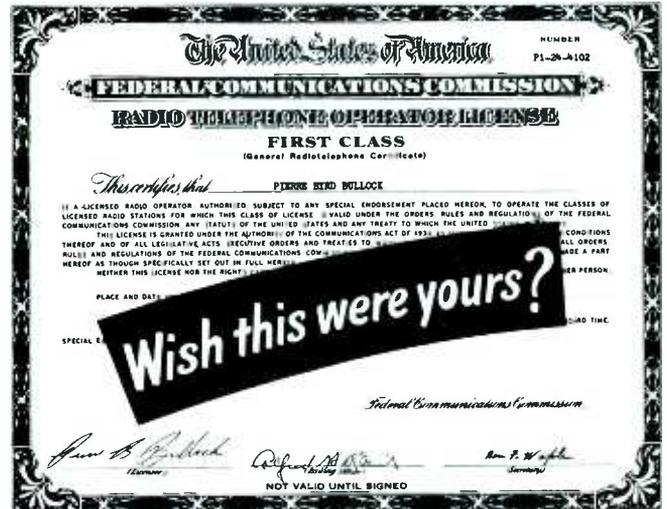YOU EARN YOUR FCC FIRST CLASS LICENSE or your money back!



5 NRI COMMUNICATIONS COURSES INCLUDE FCC LICENSE TRAINING

Earning an FCC License can be quick and easy the NRI way. You can concentrate on a short FCC License course—"specialize" by training in Mobile, Aviation, or Marine Communications—or go all-out with the job-simulated NRI course in Complete Communications. It is the **only** home-study training plan that includes professional lab equipment specifically designed to give you on-the-job, "hands on" experience as you train.

Whichever NRI Communications course you choose, with an FCC License you're ready to operate, service and install transmitting equipment used in broadcasting stations, aviation, on board ships, and in mobile and Citizens-Band radio. And you **MUST PASS** your FCC exams or **NRI refunds your tuition in full**. Can you do it? The NRI record of success is outstanding. 87% of NRI graduates pass their FCC exams.

Get full details today about five courses that include FCC License preparation, plus seven other training plans offered by NRI, the oldest and largest school of its kind. Mail coupon. No obligation. No salesman will call. **NATIONAL RADIO INSTITUTE, Electronics Div., Washington, D.C.**

APPROVED UNDER GI BILL. If you served since January 31, 1955, or are in service, check GI line in coupon.

MAIL NOW for FREE CATALOG



NATIONAL RADIO INSTITUTE 22-028
Electronics Division, Washington, D.C. 20016

Please send complete data about FCC License training, other NRI courses checked below. (No salesman will call.)

- | | |
|--|--|
| <input type="checkbox"/> FCC License | <input type="checkbox"/> TV-Radio Servicing (with color) |
| <input type="checkbox"/> Complete Communications | <input type="checkbox"/> Advanced Color TV |
| <input type="checkbox"/> Aviation Communications | <input type="checkbox"/> Industrial Electronics |
| <input type="checkbox"/> Marine Communications | <input type="checkbox"/> Basic Electronics |
| <input type="checkbox"/> Mobile Communications | <input type="checkbox"/> Electronics for Automation |
| <input type="checkbox"/> Math for Electronics | <input type="checkbox"/> Electrical Appliance Repair |

CHECK FOR FACTS ON NEW GI BILL

Name _____ Age _____

Address _____

City _____ State _____ Zip _____

ACCREDITED MEMBER NATIONAL HOME STUDY COUNCIL

Circle 31 on literature card

February, 1968/PF REPORTER 61

Speedy TUNER REPAIR

FAST SERVICE

ONE YEAR WARRANTY



24 HOUR
SERVICE

COLOR • UHF • VHF

\$950 (\$14.50 COMBO)
COMPLETE

Includes all parts
(except Trans. & Tubes)

We are new in name only—Behind every tuner repair is 15 yrs. of experience. Our base price is compatible with other companies, but the extra service and high quality workmanship makes our service cheaper in the long run. Send the defective tuner with all parts, include tubes, make, model No. and complaint. Pack well and insure. All tuners returned C.O.D. unless accompanied by an open check. (Dist. write for price structure)



**SUPERIOR
TUNER SERVICE**

1377 N. CURRY PIKE
BOX 368

Bloomington, Indiana 47401

Circle 32 on literature card

Precision Sound Alignment — The Easy Way

by Robert F. Heaton

Sometimes, not often mind you, experienced service technicians fail to pass along valuable tips to younger technicians. For example, few electronics schools teach "time-saving" troubleshooting procedures. Usually, actual servicing experience or "old pro" training is necessary after graduation—the information isn't available in schools for it would make the course of training prohibitively long.

Alignment of sound systems in television receivers could be a typical example. There are many acceptable procedures for sound align-

ment, used by various technicians. Many, I'm sure, use the method outlined herein—and have for years! However, let's see if your present method matches mine. We'll use a typical sound system as illustrated (simplified) in Fig. 1.

Assume, regardless of reason (circuit repair, transformer replacement, or normal aging) sound alignment is needed. Here's a method which is quick and easy, yet highly accurate. The method can be used on service calls in the home or in the shop. The only equipment needed is a bias box, alignment tools, and a station signal.

Preliminary Steps

Tune in on a local channel and set the volume control to normal. Connect a variable negative bias supply to the IF stages, set for $-8V$; another variable negative bias to the RF stage, set for $-6V$.

Step 1

If background noise or distorted sound is heard, decrease RF bias towards zero until sound is relatively noise-free. If zero RF bias is reached and sound is still distorted, reduce IF bias (from $-8V$) until sound clears. Now, carefully increase IF bias until sound just becomes noisy (buzz is heard on peaks).

Step 1 is performed to attenuate the incoming signal just to the point of sound distortion. Under these conditions, the passband of the tuned circuits in the sound stages are indirectly narrowed, demanding accurate tuning to produce clear sound. This will be evident when adjustments are made, for sound "breakout" (noise and/or distortion) will occur with only a fraction of a turn of any coil slug.

**WORLD'S
FINEST**

ERSIN
MULTICORE

ONLY **69¢**

BUY IT AT RADIO-TV PARTS STORES

Multicore Sales Corp. Westbury, N.Y. 11591

Circle 33 on literature card

NOTES ON TEST EQUIPMENT

*analysis of test instruments
...operation...applications*

by T. T. Jones

New Color Generator

The latest entry into the color generator market is Leader's Model LCG-387 pictured in Fig. 1. We were dubious when we ordered a sample, since the market really is somewhat saturated, and just about any feature you can imagine is already available in American-made generators, at competitive or better prices.

The advertisements from Leader didn't indicate too much, because every feature mentioned in the ads is available in one or another of the American generators. Why then, we wondered, would the Japanese attempt to penetrate this difficult market?

When we unpacked the sample,

the most interesting features readily apparent were that the instrument comes in a nice little leather case, and has a miniature screwdriver and a diddle-stick packed with it. Incidentally, it's a very good stick, with a reversible hex bit in a plastic handle that provides a firm grip. The smaller bit fits tuner slugs just right.

After a quick glance over the externals, we unscrewed the cover (2 screws) for a peek inside. It then became apparent why Leader challenged the U.S. market. This quick peek took several hours before we even plugged in the generator for a trial. Under the cover, the LCG-387 is one of the most fascinating instruments we've seen (Fig. 2). The most striking thing is the number of components they've managed to

cram into the case, which is about the size of the average VTVM. There's 50 transistors, 78 diodes, and more resistors and capacitors than we would care to count.

This high-density packaging is made possible by the use of plug-in, computer-style PC boards. Fig. 3 is typical of one of these boards. This particular board includes most of the synthesizing circuits, and the horizontal countdown stages. The vertical countdown are on the center board (Fig. 2), and the RF, color, and 189-kHz oscillators are on the rear board.

The color oscillator is the standard offset-carrier type, but the output goes through a buffer stage before passing on to the keying stages. Again there are buffers and shapers after the 10-bar keying, so the chroma signal passes through 6 transistors in all before reaching the video stages.

The RF oscillator is a modified Hartley, operating on channel 5 or 6. A slide switch at the rear of the instrument selects either of two trimmer capacitors in the tank circuit, to arrive at the proper operating channel. We tried readjusting the channel 5 trimmer to channel 4, but it did not have sufficient range. However, the basic oscillator circuit is quite simple, and it appears as though it could easily be padded down to reach channel 4, or even 3 with a possible reduction in output level. The RF carrier is matrixed with the video in a simple diode modulator, and then feeds directly



Fig. 1. New color generator has leather case.



Fig. 2. Top view with cover removed.

to the output terminals through an impedance matching network. The output impedance is 300Ω , so the output cable furnished is twinlead, rather than coax. The level is approximately 10 mV.

The output of the 189-kHz crystal oscillator is fed to multi-vibrator-buffer stage, which produces a 189-kHz squarewave. A portion of this signal feeds to the color circuits to key the rainbow. The rest of the signal feeds to the horizontal count-down circuits. The horizontal chain is made up of 4 identical bistable multivibrators such as Fig. 4, and a buffer stage. The overall block diagram is shown in Fig. 5.

As can be seen in Fig. 5, the hori-

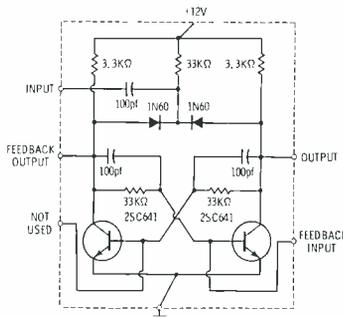


Fig. 4. Typical divider stage.

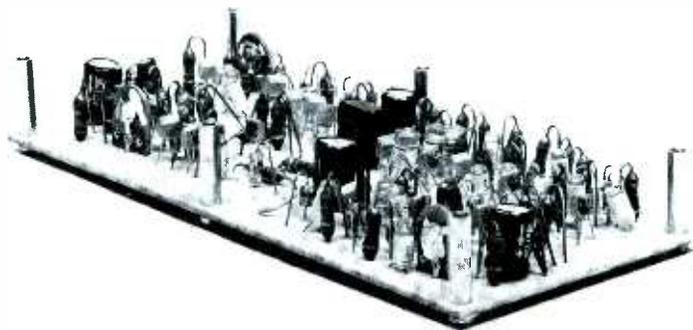


Fig. 3. Sync and horizontal board.

Listen!



Service Dealers ...Eliminate the "Time Killer"!

It's not that we have anything against catalogs or those who must refer to them umpteen times a day. It's just that we're in complete sympathy with the time-conscious dealer who'd rather turn a profit than a page.

That's one reason why Jensen has *every* loudspeaker in the book ... so you won't *need* a book. Simply tell your Jensen distributor the type speaker you need and he'll take it right off the shelf. Easy as that!

When you need a speaker—any speaker—call your local Jensen distributor.

... insist on Jensen.

jensen

Jensen Manufacturing Division, The Muter Company,
6601 South Laramie Avenue, Chicago, Illinois 60638.

Circle 36 on literature card

February, 1968/PF REPORTER 65

new Sams books

So You Want to Be a Ham. 4th Ed.

by Robert Hertzberg, W2DJJ. Completely revised and updated to include full information on changes introduced by the new incentive licensing. Here is everything you need to know to get into Amateur radio; chapters are devoted to the code, the receiver, the antenna, kits, getting the ticket, going on the air, going mobile, how to be a good operator, test equipment and safety measures, etc. Describes modern equipment, operating procedures; gives helpful guidance on passing the FCC exam. A "must" book for anyone out after the ham ticket. 192 pages; 5½ x 8½". \$3.95
Order 20607, only

FET Principles, Experiments & Projects

by Edward M. Noll. The field-effect transistor is coming into wide acceptance in industry, and is beginning to appear in electronic products for home use. Low-cost FET types are now available for the build-it-yourselfer. This book by a well-known authority clearly explains the unique FET principles of operation, provides data for circuit designs, and includes experiments demonstrating the operating characteristics of field-effect transistors. Practical projects using FET's are also included; simple circuits can be constructed on pegboards or inexpensive chassis. Has chapter on FET math. A fascinating book for audio, amateur, short-wave, CB and do-it-yourself fans. 256 pages; 5½ x 8½". Order 20594, only \$4.95

Outboard Motor Service Manual. 4th Ed. (In 2 Volumes)

Vol. 1. Complete service data for motors under 30 HP, covering models made by 37 leading manufacturers.

Vol. 2. Comprehensive maintenance and repair information for motors of 30 HP and over; covers models made by 21 manufacturers.

Each volume includes design fundamentals (engine types, fuel, ignition, and cooling systems); drive-unit fundamentals (propeller, gearcase, and lower housing); service fundamentals, troubleshooting, maintenance, and general repairs. Volumes are 8½ x 11½". \$4.95

Vol. 1. 240 pages. Order 20598, only \$4.95

Vol. 2. 208 pages. Order 20599, only \$4.95

Inertial-Guidance Systems

by Training & Retraining, Inc. Explains the importance of these unique systems which are completely self-contained, require no outside stimulus, and are isolated from all external influences of electromagnetic radiation. Inertial-guidance systems are used in all U.S. ballistic missiles and in such space projects as Gemini and Apollo; the same principles and equipment techniques are being increasingly utilized in major aircraft operations. The book explains basic theory, coordinate systems and earth effects, inertial sensors, the inertial-measurement unit, the guidance computer, and system operation. Includes review summaries and instructive self-test feature. 176 pages; 5½ x 8½". Order 20605, only \$4.95

RECENT BESTSELLERS

Modern Dictionary of Electronics

New 3rd edition. Now defines approximately 16,500 terms; includes pronunciation guide, most widely used symbols and abbreviations, new terms in latest specialized fields. The most complete and authoritative electronics dictionary available. 608 pages; 6 x 9"; hardbound. \$9.95
Order 20600, only

Stereo/FM

Bestselling book value for everyone interested in stereo, hi-fi, and FM. Highlights components, consoles, tape recorders, auto stereo, and tape recorder/player systems. Includes buyer's guide for all types of equipment. \$1.25
Order 50012, only

These and over 300 other SAMS Books are available from your local Electronics Parts Distributor . . .

HOWARD W. SAMS & CO., INC.
4300 WEST 82nd ST. • INDIANAPOLIS, INDIANA 46226

Circle 37 on literature card

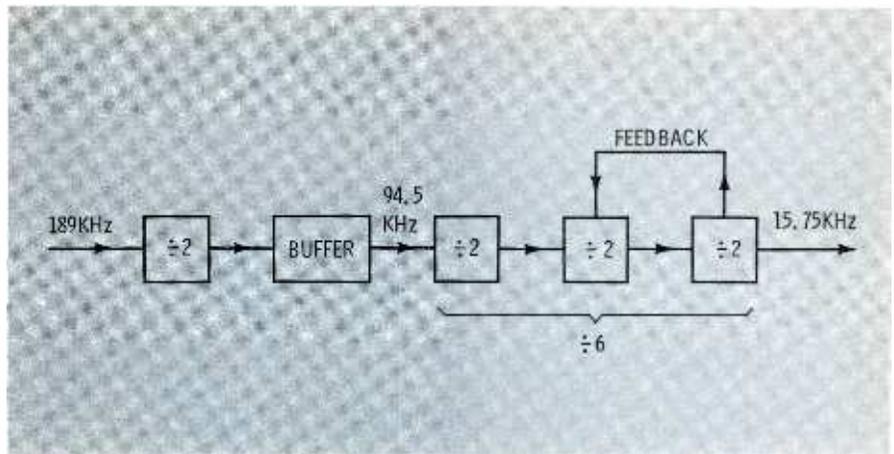


Fig. 5. The horizontal divider chain.

zontal chain achieves a division of 12 using 4 stages dividing by 2. Since the normal sequence would be $\div 2 - 4 - 8 - 16$, feedback is used to acquire the proper output.

The incoming 189-kHz square-wave signal is differentiated and results in positive and negative pulses. The dividers are multivibrators with two stable states and respond only to negative pulses; each successive negative pulse flips the multivibrator to the other of the two stable states. The output therefore is a squarewave of 94.5 kHz. The basic block then, of the divider chain, is a binary which divides by two.


The buffer isolates the first divider from the subsequent stages; these latter stages must be treated as a single block which divides by 6. Here's how it works: If we were to arrange a three-stage chain so that each time the output stage rose it would feed back a pulse to the input stage and cancel an incoming pulse, we would have a seven count. This is because 1 out of every 8 pulses is cancelled. If the feedback is applied to the second stage, as in Fig. 5, we have a six count.

The rule then is when feedback is taken from the Nth stage the count will be $2N - \frac{2M}{2}$ where N is the total number of stages and M is the stage into which the feedback is introduced.

The vertical countdown chain, again on a different board, divides the 15.750 kHz by 263 to arrive at the 59.89-Hz vertical sweep. Each of the 9 vertical stages also divides by 2, so again it is necessary to use an intricate feedback arrangement in the vertical chain to arrive at the proper countdown factor.

Because the dividers use silicon transistors and divide by 2, the whole countdown chain is extremely stable. The only adjustment in the chain is a trimmer for the 189-kHz crystal oscillator.

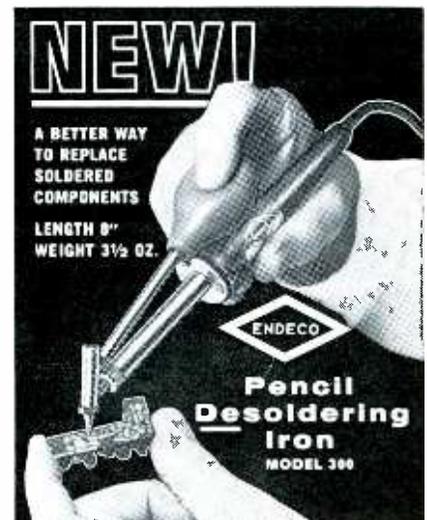The many diodes are necessary for pulse shaping circuits, and the end result is the squarest sync pulses we've seen outside a laboratory instrument. Fig. 6A is a photo of the generator signal in the crosshatch mode, with Fig. 6B showing a station signal for comparison. The pattern appears instantly when the



Now—remove miniature soldered components in seconds—without damage

Hollow tip fits over connection; vacuums all solder for easy removal of component. Leaves terminals and mounting holes clean. Then, with 360° contact, it resolders even faster and better than regular irons. Handles miniature and standard components in printed circuit boards and conventional wiring. Self-cleaning. All parts replaceable. 40 watts, 115-v. 5 tip sizes. Pays for itself in time saved. \$9.95 net East of the Rockies.

Larger model available. See your distributor or write:

ENTERPRISE DEVELOPMENT CORPORATION

5151 E. 65th St. • Indianapolis, Ind. 46220

Circle 38 on literature card

LCG-387 is turned on, and it is as stable as a station signal. There is absolutely no jitter nor crawl on the dot or line patterns. The color bar pattern shows a slight vertical crawl which is unavoidable in the standard 10-bar signal derived from an offset subcarrier.

Using the LCG-387 is a real pleasure, because of the stable pattern. Other conveniences include the single-cross pattern (also available on several American generators) and the small size and light weight. ▲

For further information circle 56 on literature card

Leader Model LCG-387 Specifications

RF Output

Frequency:

Channel 5 or 6 ± .5%, switch selectable.

Voltage:

10 mV on open circuit.

Impedance:

300 Ω balanced.

Patterns

Color:

Standard keyed rainbow.

Crosshatch:

11 H x 14V. Horizontal bars are one scan line wide, with blanking. Vertical bars are 0.2 μs wide with 4 μs spacing.

Dots:

At crosshatch intersections.

Single Crossbar:

Centered on raster.

Blanking

Horizontal:

Interval 0.16H, Front porch .02H, Back porch 0.6H.

Vertical:

Interval 15H. Back porch 12H. H = one scan line or 63.5 μs.

Power Supply:

Fullwave bridge, transistor regulated in both series and shunt modes, zener regulated output is 12V, adjustable.

Power requirements:

115 VAC, 2 watts.

Size (HWD):

2¾" x 6¾" x 4¾"

Weight:


3½ pounds with all accessories

Accessories:


300 Ω output cable, screwdriver, alignment tool, leather carrying case.

Price:

\$134.50.

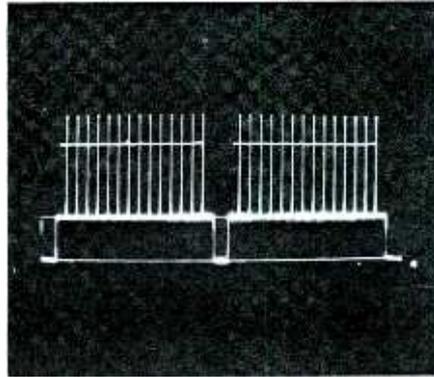

(A) LCG-387 crosshatch.

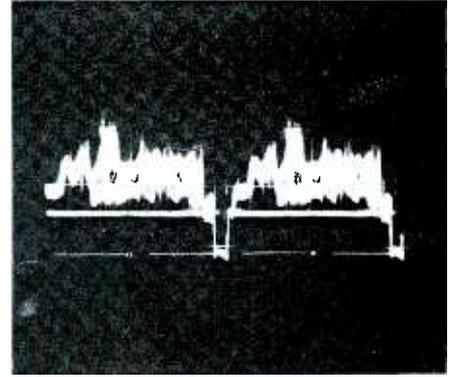

(B) Station signal.

Fig. 6. Waveforms at 7875 Hz.

THE BEST COLOR ANTENNAS!
RMS SUPER TRANS POWER'D

Incomparable performance on All Channels 2-13 plus FM! Exclusively features Reynolds Aluminum COLORWELD!

Model	Area Used	No. of Elements	Reception Range	List Price
STP-7	Metropolitan	7	Up to 50 miles	\$13.45
STP-11	Suburban	11	Up to 75 miles	19.95
STP-15	Semi-Fringe	15	Up to 100 miles	26.95
STP-19	Fringe	19	Up to 125 miles	39.95
STP-23	Extreme Fringe	23	Up to 150 miles	44.95
STP-28	Extreme Fringe	28	Up to 175 miles	53.95

RMS DYNERGY

Complete UHF/VHF and FM Coverage, Channels 2-83! Single down-lead for simple, economical installation! Features COLORWELD!

Model	Area Used	No. of Elements	VHF Range	UHF Range	List Price
DYN-33US	Metropolitan	6	to 35 miles	to 20 miles	\$19.95
DYN-54US	Suburban and Semi-Fringe	9	to 60 miles	to 30 miles	29.95
DYN-66US	Suburban and Semi-Fringe	12	to 75 miles	to 50 miles	34.95
DYN-88US	Semi-Fringe and Fringe	16	to 125 miles	to 75 miles	44.95
DYN-118US	Semi-Fringe and Fringe	19	to 125 miles	to 75 miles	44.95
DYN-158US	Fringe	23	to 150 miles	to 75 miles	49.95

Make your next installation profitable with these dependable RMS Antennas. Write for FREE Informative Catalog! . . . Dept. PFA

Dependable construction and performance for long-life installation!

RMS ELECTRONICS, INC.

50 ANTIN PLACE, BRONX, N. Y. 10462

Circle 39 on literature card

PRODUCT REPORT


for further information on any of the following items, circle the associated number on the Catalog & Literature Card.

Antennas For Mobile Use (60)

Two new antenna kits for use on travel trailers and mobile homes have been introduced by **The Finney Company**. The FINCO model TTR-1 (shown here) consists of an all-channel UHF-VHF-FM antenna mounted on a telescoping mast and rotator mechanism which allows the antenna to be rotated from inside the vehicle through a full 360°. When traveling, the antenna is folded down, closed up and locked in a safe travel position below the vehicle roof top. It is not necessary to disconnect the transmission line or do any disassembly.

Model TTW-1 consists of an all-channel UHF-VHF-FM antenna mounted to the vehicle on a wall mount. The antenna and top mast section are removed for travel, and the fully preassembled antenna elements are closed for storage.

Both models come complete with all transmission line, hardware and accessories needed to complete an installation using simple tools. Both models use a new FINCO model CS-A1 Color Spectrum frequency-dependent antenna designed to receive color or black-and-white signals from all channel frequencies—UHF-VHF, plus FM—on a single transmission line, and include a behind-the-set splitter to deliver the respective signals to the proper antenna terminals on the set. The antennas are gold corodized to provide corrosion protection from weather and road dirt. Model TTR-1 is priced at \$54.95 and Model TTW-1 at \$29.95.

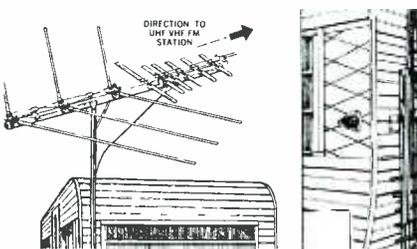

Transistorized VOM (61)

This solid-state, battery-operated voltmeter and ohmmeter requires no

warm-up time and eliminates the zero-shift that can occur in tube-operated units. The **RCA WV-500A VoltOhmyst** is completely portable, making it ideal for home and shop servicing or industrial and laboratory applications.


Seven overlapping resistance ranges are provided to allow measurements from 0.2 ohm to 1,000 megohms. Eight overlapping DC-voltage ranges measure from 0.02 volt to 1,500 volts (including a special 0.5-volt DC range), AC p-p voltages of complex waveforms from 0.5 volt to 4,200 volts, and AC rms voltages from 0.1 volt to 1,500 volts. The input impedance of all DC ranges is 11 megohms.

All measurements are made with a wired-in, single-unit probe (WG-410A) equipped with a fully-shielded input cable. The probe is quickly adapted to either DC measurement or AC and resistance measurement by means of the built-in switch near the tip of the probe. A new slip-on high-voltage probe (WG-411A) can be used with the WG-410A probe to make possible measurements up to 50,000 volts DC. Price is \$75.00.



Rigid Cable Cover (62)

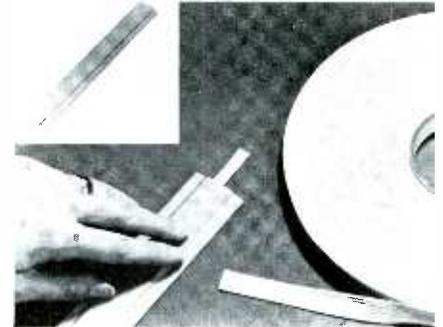A new rigid cable cover for telephone, intercom and other low-voltage wire installations has been announced by **3M Company**. Called "Scotchflex" brand No. 724 Cable Cover, it comes



in 4' lengths measuring 1/8" high by 1 1/2" wide. Narrow strips of foam adhesive are applied to the edges along the length of the duct. The foam adhesive adheres to nearly any clean, relatively smooth surface and eliminates the need for drilling holes or using mechanical fasteners.


Suggested commercial applications include wire protection for telephone extensions, intercom systems, remote control hookups and paging systems. The duct is useful for protecting wiring on the floor along well-traveled areas. Price is \$1.65 per unit.

Antenna Fittings (63)


A new series of solderless, coaxial-cable TV antenna fittings, designed for use with RG-59/U, 75-ohm cable, has been released by **GC Electronics**. The new fittings are available in two types, Type "C" and Type "F", to



TYPE "C"
33-36
MALE CONNECTOR

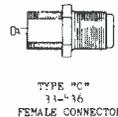

TYPE "C"
33-36
FEMALE CONNECTOR

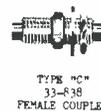

TYPE "C"
33-38
FEMALE COUPLER



TYPE "F"
33-8L0
MALE CONNECTOR




TYPE "F"
31-8L2
FEMALE CONNECTOR

facilitate all commonly encountered antenna hook-up problems. The Type "C" fittings include a male and female connector for cable and chassis mountings, and a female coupler for cable splicing or chassis feed-through applications. The Type "F" fittings, adaptable to the newer cable antenna systems, provide a male connector for crimp-on connection to the incoming cable, and a female connector, complete with hardware for chassis mountings. The Type "F" fittings will also accommodate all antenna couplers and splitters. While designed primarily for TV antenna cable systems, the new fittings can also be used in closed circuit television camera installations.

The new parts are supplied in standard packs of 10 fittings each, with discounts on quantities of 30 or more of each type.

TV Camera (64)

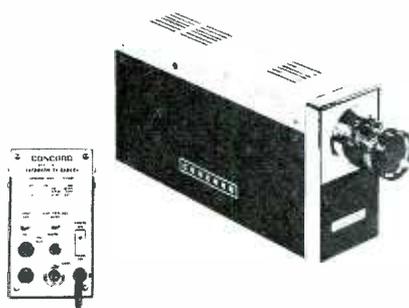A new, solid-state television camera designed for video tape recorder use and CCTV applications where fixed (2 to 1) interlace is desired has been introduced by **Concord Communications Systems**. The new MTC-18 camera provides its own sync and operates as a sync generator for other MTC-18 cameras, or will accept sync from an external sync generator.



The sync output feature allows video tape recorder users to design or expand their system, permitting switching from camera to camera and sharp scene changes without loss or distortion of picture image. The added feature of a light-control selector on the camera permits either totally automatic or manual compensation for varying light conditions. Video tapes with fades, titles, and superimposed images may be created economically with the addition of the Concord TCP-1 television control panel.

The new camera is completely solid-state with silicon transistors. The camera may be used with any standard monitor or Concord video tape recording system. The signal output

level permits longer distances between camera and video recorder without amplification.

The MTC-18 camera measures 5½" x 3" x 11" and weighs 7.5 lbs. Video resolution is 550 lines. The unit comes equipped with a 25-mm. f 1.9, adjustable iris lens, with other lenses available. Price is \$450.00.

Mini Tools (65)

Four "mini" tools for professional servicemen and home workshop buffs have been introduced by **Vaco Products Company**. One tool is the TK-500 Circuit Tester Screwdriver which is handy for testing 100- to 500-volt circuits simply by inserting the blade into the hot side of the socket and holding a finger on the metal cap of the trans-



BUZIT

TRANSISTORIZED SIGNAL TRACER

FOR ONLY \$9.57 DEALER NET
WITH BATTERIES

NO CLIPS
NO WIRES

MADE IN U.S.A.

USED FOR TROUBLE SHOOTING

- A.F. CIRCUITS • I.F. CIRCUITS
- R.F. CIRCUITS • CONTINUITY CHECKS • SPEAKERS, ETC.

EXCELLENT FOR TRANSISTOR RADIOS BECAUSE BUZIT USES ONLY A 3 VOLT POWER SUPPLY

ASK YOUR ELECTRONIC PARTS DISTRIBUTOR FOR


MODEL NO. BZ-1

MANUFACTURED BY

WORKMAN

SARASOTA FLORIDA

Circle 40 on literature card

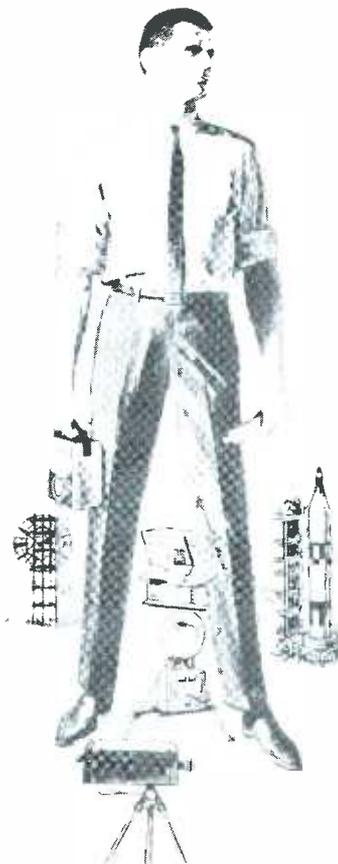

Portable "computer" for electronics men.

WANT FAST ANSWERS to math and electronics problems? Now, compute them in a flash with this new Electronics Slide Rule.

Calculate resonant frequencies, solve inductive or capacitive reactance problems, find reciprocals for resistance formulas, locate decimal points—all in just seconds, without pencil and paper.

Whiz through regular math problems, too: multiplication, division, square roots, logarithms, even trigonometric functions.

Sturdy 12-inch, all-metal slide rule comes complete with handsome leather carrying case—plus 4-lesson instruction course. Deliberately priced low as our way of making friends with electronics men. **FREE** booklet gives full details. Mail coupon below today.

Mail Coupon for FREE Booklet

CIE

Cleveland Institute of Electronics
1776 East 17th Street, Cleveland, Ohio 44114

Please send me, without charge or obligation, your booklet describing the Electronics Slide Rule and 4-lesson instruction course. Also free if I act at once—a handy, pocket-sized Electronics Data Guide.

Name _____ (Please Print)

Address _____

City _____ State _____ ZIP _____

Accredited Member National Home Study Council
A Leader in Electronics Training... Since 1934


PF-120

Circle 41 on literature card

NEW! from **SECO**

**"IN - CIRCUIT"
CURRENT CHECKER**

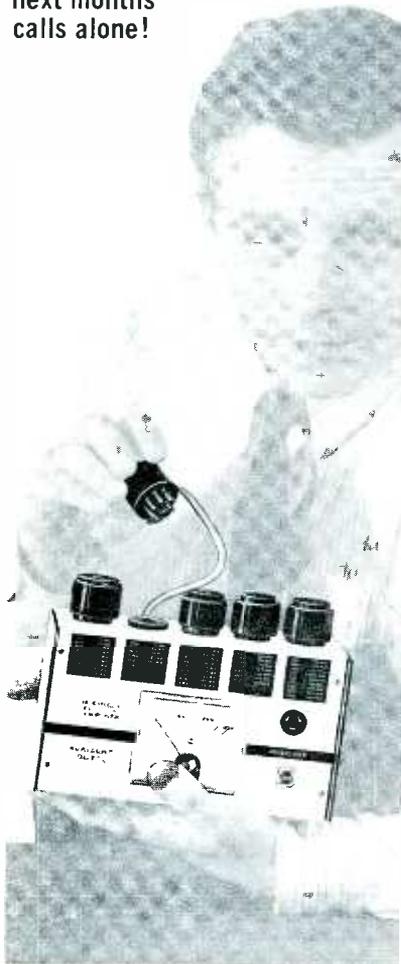Eliminates most common cause of "callbacks" (unstable focus, shrinking pictures, etc.)! Should pay for itself on next months' calls alone!



Nothing else like the HC-8 available! Tune horizontal drive and linearity for "dip"—and in seconds—you've got best possible focus, width and stability at minimum cathode current. Makes convergence adjustments faster, easier—longer lasting!

Especially useful on color TV where a slight misadjustment of horizontal linearity or efficiency coils drives cathode currents sky high! 5 pre-wired sockets for all popular horizontal output tubes lets you plug into circuit fast—no clipping or unsoldering of leads!

Model HC-8
\$34.50
Net

ASK YOUR DISTRIBUTOR
or write for full details.

SECO
SECO ELECTRONICS CORP.
1001 Second St. So. • Hopkins, Minn. 55343

Circle 42 on literature card

70 PF REPORTER, February, 1968

parent handle. If the circuit is alive, the handle will light up.

Another tool in the miniature group is the K-21 1/8" x 3" Screw Launcher. This too will hold, start and drive miniature screws. Because of these features, plus its small size, the Launcher is particularly suited for hard-to-reach places. The two-bladed bit grasps the screw when the user slides a gripping sleeve forward on the shaft.


The third tool is a miniature reversible screwdriver (No. DU-1) with a 1/8" square blade at one end of the shaft and a No. 1 Phillips blade at the other end. The fourth tool is the K-14, a Phillips screw launcher only 5" long. It is useful for starting or retrieving all cross-slot screws in awkward, hard-to-reach places.

Each of the four tools may be purchased separately—the TK-500 Circuit Tester Screwdriver at \$1.00; the K-21 Screw Launcher at \$1.50; the DU-1 reversible screwdriver at \$1.25 and the K-14 Phillips screw launcher at \$2.30.


Matching Transformer
(66)

This new transformer matches 72-ohm coax to 300-ohm TV sets and 300-ohm antennas.

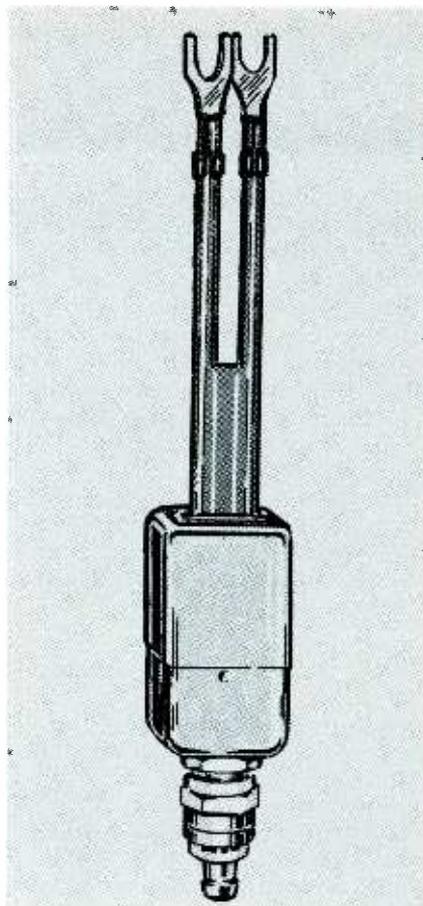The **Workman** unit features an all-aluminum case, with double crimp-



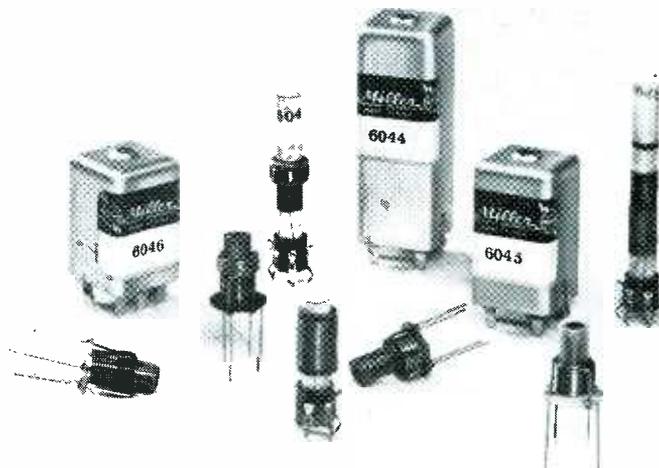in of both wire and insulation to the connectin lugs. Price is \$1.80. ▲



**Video and Chroma Coil Exact Replacements
for More than 25 Color TV Manufacturers**

Ten Color TV coils replace more than 550 video and chroma coils for sets made by manufacturers such as RCA • GE • MOTOROLA • PHILCO • MUNTZ. Installation instructions and diagrams are included.



Write today for latest Color TV Coil Cross Reference Guide

J.W. MILLER COMPANY

5917 South Main Street • Los Angeles, California 90003

SEE YOUR LOCAL DISTRIBUTOR FOR THE FULL LINE OF RF AND IF COILS, CHOKES, FILTERS AND TRANSFORMERS

Circle 43 on literature card



The NEW
NO. 800
**TUN-O-LUBE
TUNER CLEANER**

Specially
**FORMULATED
FOR TV-TUNERS**
USING **NUVISTORS &
TRANSISTORS**
NO TUNER DRIFT

NO. 800
\$1.98
DEALER
NET

Nuvistors and Transistors are highly sensitive to drift from ingredients in most ordinary TV tuner cleaners. Drift has been found to cause call backs and expensive tuner repairs. For over 18 months CHEMTRONICS has been formulating and testing this new cleaner in both the lab and field. Under the most critical test, there has been NO DRIFT on scope patterns. We invite you to try this test yourself.

**AMAZING
HIGH VOLTAGE
INSULATOR
NO-ARC**
20,000 VOLTS
DIELECTRIC STRENGTH
CHEMTRONICS' highly effective NO-ARC provides a tough and protective insulating coating for hi-voltage transformers, yokes, chassis and leads in high voltage sections.

No. 830



BROOKLYN


N. Y. 11236

Circle 44 on literature card


INDEX TO ADVERTISERS

American Telephone & Telegraph Co.	15	Multicore Sales Corp.	62
Arrow Fastener Co., Inc.	50	National Radio Institute	61, 63
B & K Mfg. Co., Div. of Dynascan Corp.	21	Oaktron Industries, Inc.	59
Bussmann Mfg.	16	Olson Electronics, Inc.	63
Channel Master	26, 27	Perma-Power Co.	38
Chemtronics, Inc.	71	Radio Corporation of America ...	Cover 3
Cleveland Institute of Electronics ...	51, 69	RCA Institutes, Inc.	55
Columbia Wire Products Co.	54	RCA Sales Corp.	23
Cornell-Dubilier	Cover 2	RMS Electronics, Inc.	67
Delco Radio Division	9	S & A Electronics, Inc.	57
Eico	1	Sams, Howard W. & Co., Inc.	24, 66
Enterprise Development Corp.	66	Sarkes Tarzian, Inc.	7
G. C. Electronics	36	Seco Electronics Corp.	70
Gem City Tuner Repair Service ...	54	SENCORE, Inc.	31
Heath Co.	35	South River	
Jensen Mfg. Div., The Muter Co.	65	Metal Products Co., Inc.	48
Jerrold Electronics Corp.	45	Sprague Products Co.	3
JFD Electronics Co.	71	Superior Tuner Service ...	62
Leader Electronics Corp.	52	Swing O-Lite, Inc.	57
Lectrotech Inc.	56	Weller Electric Corp.	53
Littelfuse, Inc.	Cover 4	Winegard Co.	12, 13
Mallory, P. R. & Co., Inc.	4	Workman Electronic Products, Inc.	69
Miller, J. W. Co.	70	Xcelite, Inc.	19
Moseley Electronics, Inc.	18	Zenith Sales Corp.	58

JFD® V/U/FM Couplers have muscle!

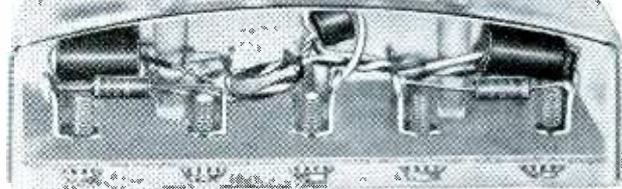

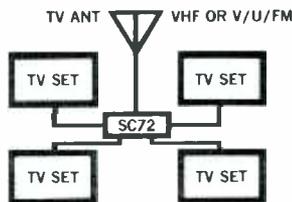**DESIGNED BETTER!
BUILT BETTER!**
FOR COLOR-PERFECT HOME
DISTRIBUTION SYSTEMS



Model **SC72** 4-Set V/U/FM COUPLER
Model **SC62** 3-Set V/U/FM COUPLER
Model **SC42** 2-Set V/U/FM COUPLER

world's largest manufacturer

JFD ELECTRONICS CO.


1462 - 62 Street Brooklyn, N.Y. 11219
of TV/FM antennas and accessories.

- COUPLES up to 4 sets to a single V/U/FM antenna with lowest possible loss—only 7.2 db maximum.**
- CONSTANT inter-set isolation—15 db minimum across all VHF, UHF and FM frequencies.**
- OPTIMUM VSWR of 1.2:1—both forward and backward—for noise-free color.**
- FLAT response ($\pm \frac{1}{4}$ db per 6 MHz channel) for perfect chroma registration.**
- MATCHED quality components, operating well below rated parameters, insure long-life reliability.
- NO-STRIP terminals make positive contact, eliminate 300 ohm twin lead stripping or splicing.
- COMPLETE with hardware and adhesive Insta-Mount for quick and convenient indoor installations.
- ATTRACTIVE non-breakable housing sheds rain and moisture.

**For model SC72 4-set coupler.

Solve all reception problems permanently and profitably with the couplers, splitters, combiners, antennas, transformers and amplifiers that have muscle. Now at your JFD distributor. Write for brochure 834.

Circle 45 on literature card

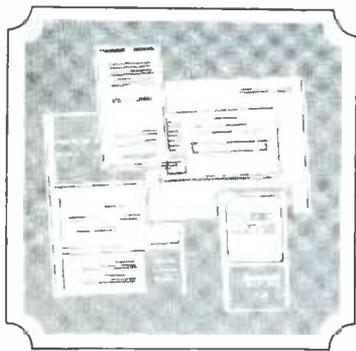

\$ FREES \$

CATALOG AND LITERATURE SERVICES

*CHECK "INDEX TO ADVERTISERS" FOR FURTHER INFORMATION FROM THESE COMPANIES

ANTENNAS

100. *ALLIANCE* — Colorful 4-page brochure describing in detail all the features of Tenna-Rotors.
101. *BLONDER-TONGUE* — Flyer sheet on new "Colortap" outlet plates and plugs for 300Ω leadin.
102. *DELHI* — Twelve-page catalog introducing a complete new line of home TV towers, ham towers, citizen's band towers, masts, and telescoping masts.
103. *FINNEY* — New point-of-sale changing-image full color sign to promote antenna sales with color TV sets. Form 20-431.
104. *JERROLD* — New 4-page full-color catalog describes the new Paralag Plus antennas.*
105. *JFD* — 24-page design booklet shows how to estimate costs, prepare bids, design, sell, and install MATV systems.*
106. *MOSLEY* — Catalogs on CB, Amateur radio, and TV/FM antennas.*
107. *WINEGARD* — Fact-finders on "Color-Line 82" coaxial cable pack, "Trans-coupler" cut-to-channel Yagi antennas, and "Red-Head 82" solid-state antenna preamplifier.*

AUDIO

108. *ATLAS SOUND* — Specification sheets on new models AP-15, AP-15T, and APT-34T paging speakers.
109. *ELECTRO-VOICE* — Pocket-size guide-books for EV microphones, Hi-Fi loudspeakers, and systems.
110. *JENSEN* — Form PH describes and illustrates a new professional series of horns columns, and leveler controls.*
111. *OXFORD TRANSDUCER* — Bulletin A-109 features speaker installation in automobiles, hospitals and recreation rooms.
112. *RACON* — Catalog C665T on horns, drivers, sound columns, and accessories.
113. *UNIVERSITY SOUND* — New 28-page 1968 commercial sound product catalog.

COMMUNICATIONS

114. *AMPHENOL* — 2-color spec sheets on new Model 650 CB transceivers and Model C-75 hand-held transceiver.
115. *COMCO* — Brochure about Model 900 series VHF and UHF-FM two-way radio.
116. *NUTONE* — Full-color booklet illustrating built-in stereo music, intercom, and radio systems.

COMPONENTS

117. *BELDEN* — Catalog 867, a 56-page catalog of the complete Belden line.

118. *BUSSMANN* — 24-page booklet giving detailed information on the complete line of BUSS and FUSETRON Small Dimension fuses and fuseholders—the ones most used for protecting electronic equipment. Ask for BUSS BULLETIN SSB.*
119. *CENTRALAB* — 24-page replacement parts catalog No. 33GL.
120. *CORNELL-DUBILIER* — New 4-page Color-lytic list.*
121. *LITTELFUSE* — Pocket-sized TV circuit breaker cross reference gives the following information at a glance. Manufacturer's part number, price, color or h/w designation. A second glance gives trip ratings and acquaints you with a line of caddies. Ask for CB'RP.*
122. *MALLORY* — Bulletin 4-82 describes radial and axial lead tantalum capacitors.
123. *MILLER* — Catalog 167, a 156-page general catalog with complete cross-reference guide to the J. W. Miller Line.*
124. *QUAM-NICHOLS* — New catalog N. 67 has complete detailed information on the entire Quam line.
125. *SPRAGUE* — C617, a complete catalog of the Sprague Line.*
126. *TEXAS CRYSTALS* — 12-page catalog of crystals including engineering data, specifications and prices.
127. *WORKMAN* — 46-page catalog #100 on resistors, fuses, circuit breakers, brighteners, adaptors, and test accessories. Cross-reference charts included.

SERVICE AIDS

128. *CASTLE TUNER* — How to get fast overhaul service on all makes and models of television tuners is described in leaflet. Shipping instructions, labels, and tags are also included.
129. *GC* — FR-67, the full-line catalog.*
130. *AM BUSINESS FORMS* — Brochures about and samples of two new professional service contract forms designed to earn extra money.
131. *PERMA-POWER* — New 4-page catalog of TV accessories.*
132. *PRECISION TUNER* — How to get fast tuner service described in leaflet. Free mailing kit and replacement tuner list included.

SPECIAL EQUIPMENT

133. *ATR* — Literature about DC-AC inverters up to 600 watts load.
134. *BAY PRODUCTS* — 40-page catalog of steel shelving, workbenches, tool cabinets, etc.

135. *3-M* — Flyer sheets and brochures about flat cable with adhesive backing for attractive sound and control installations.
136. *TERADO* — Flyers on portable electric power sources, and a device to prolong light bulb life.

TECHNICAL PUBLICATIONS

138. *CLEVELAND INSTITUTE OF ELECTRONICS* — Free illustrated brochure describing electronics slide rule and four lesson instruction course and grading service.*
139. *LAFAYETTE* — 124-page winter sale catalog.
140. *RCA INSTITUTES* — New 1968 career book describes home study programs and course in television (monochrome and color), communications, transistors, industrial, and automation electronics.*
141. *SAMS, HOWARD W.* — Literature describing popular and informative publications on radio and TV servicing, communications, audio, hi-fi, and industrial electronics, including special new 1968 catalog of technical books on every phase of electronics.*

TEST EQUIPMENT

142. *B & K* — New 1968 catalog featuring test equipment for color TV, auto radio, and transistor radio servicing, including tube testers designed for testing latest receiving tube types.*
143. *EICO* — New 1968 short-form catalog. Shows the complete EICO line.*
144. *HICKOK* — Specification literature on models CR-35 CRT tester, GC-660 color generator, 677 wide-band scope, 661 NTSC color generator, 860 "Injecto-Tracer" and 6000A tube tester.
145. *LECTROTECH* — Two-color catalog sheet on new Model V-6B color bar generator, the latest improved model of the V-6. Gives all specs and is fully illustrated.*
146. *MERCURY* — All-new 16-page test instrument catalog.
147. *SECO* — Operating manual for the IIC8 in-circuit current checker for horizontal output tubes.*
148. *SENCORE* — New 12-page catalog on all SENCORE products.*
149. *SIMPSON* — Reprint: "A Guide to the Selection of Multitesters." Explains how to evaluate multitesters before you buy.
150. *TRIPLETT* — New panel meter catalog D-68 with complete line of measuring instruments.

TOOLS

151. *ARROW* — Catalog sheet showing 3 staple gun tackers designed for fastening wires and cables up to 1/2" diameter.*
152. *ENTERPRISE DEVELOPMENT* — Time-saving techniques in brochure from Endeco demonstrate improved desoldering and resoldering methods for speeding and simplifying operations on PC boards.*
153. *SWING-O-LITE* — Catalog sheet on Models BBM-9 and BB45 low-priced bench lamps.*
154. *UNGAR* — Catalogs of the "Standard" and "Imperial" line of soldering and desoldering irons.
155. *IACO* — Catalog SD-125 describing expanded line of specialty hand tools for electronic servicing.
156. *XCELITE* — Bulletin N. 867 describes hollow-shaft nutdrivers which speed lock-nut/screw adjustments.*

TUBE AND TRANSISTORS

157. *RCA* — Pix-300, a 12-page product guide on RCA picture tubes covering both color and black-and-white. Includes characteristics chart, terminal diagrams industry replacement, and interchangeability.*

**At RCA our new
corporate symbol
is really a minor change
compared with
the innovations
it will signify
in decades to come.**

RCA

Give yourself a break you can depend on!



actual size
1 3/4" x 1 3/8" x 1 1/2"



#094077

CIRCUIT BREAKER CADDY

10 ratings, one each 2-1/4, 2-1/2, 2-3/4, 3, 3-1/4, 4, 4-1/2, 5, 6 and 7 amps.

SERVICE CADDY Breakers and Fuses

One service call is all —8 breakers—one rating each 2-1/4, 2-3/4, 3, 3-1/4, 4, 4-1/2, 5 and 7 amps and 30 fuses—five each type C3/10, C1/2, C3-1/2, N3/10, N7/10 and N1.



#094076

Designed for the protection of television receiver circuits, the Littelfuse Manual Reset Circuit Breaker is also ideally suited as a current overload protector for all types of electronic and electrical control wiring such as model railroads and power operated toy transformers, hair dryers, small household appliances, home workshop power tools, office machines and small fractional horsepower motors.

Available individually packaged one breaker per display card; or 5 breakers of same rating per unit pack or as complete, versatile assortments for shop use or replacements in the field.



Included with each assortment:

Pocket size cross reference on color and black/white TV circuit breaker applications.
Form No. CBCRP-1266H

LITTELFUSE

DES PLAINES, ILLINOIS

Circle 46 on literature card

www.americanradiohistory.com