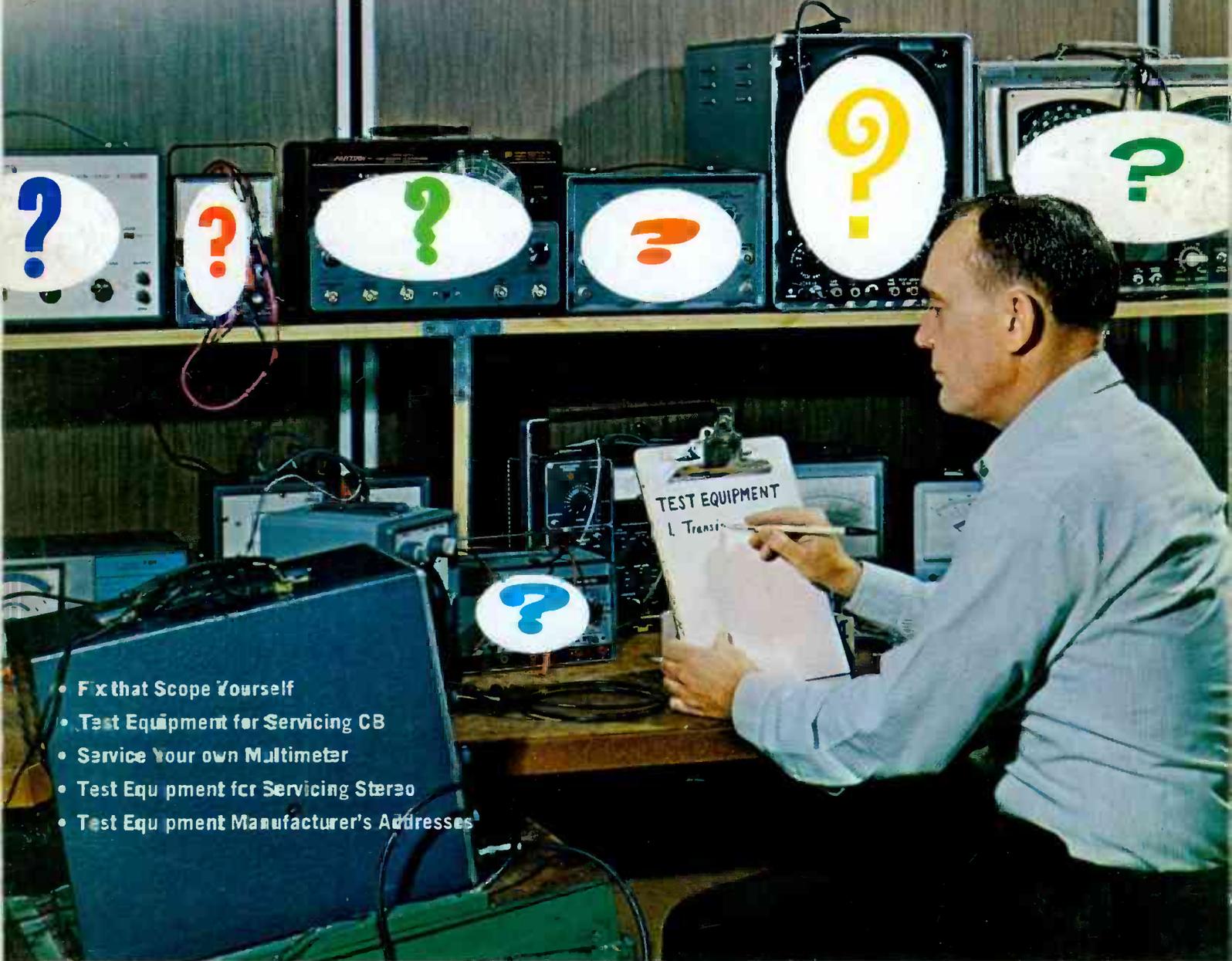


# PF Reporter

PHOTOFACT

*the magazine of electronic servicing*

## Is Your Test Equipment Up to '68 Standards?



- Fix that Scope Yourself
- Test Equipment for Servicing CB
- Service Your own Multimeter
- Test Equipment for Servicing Stereo
- Test Equipment Manufacturer's Addresses

PHILADELPHIA, PA. 19133  
 2244 NORTH 10TH ST.  
 SAMUEL SACHS  
 SA 5D 3879 568

REMEMBER TO ASK —


*“What else needs fixing?”*

**ELECTROLYTICS ARE DIFFERENT THE WAY A WET BATTERY DIFFERS FROM A DRY CELL.**




- A wet battery rated at 100 amp hours versus a dry cell rated at .01 to 1 amp hour.
- An electrolytic rated at 1 to 10,000 mfd versus a tubular or wrap or film at .000001 to 1 mfd.
- Wide tolerance (-10 to +150%) versus close tolerance (+2%).

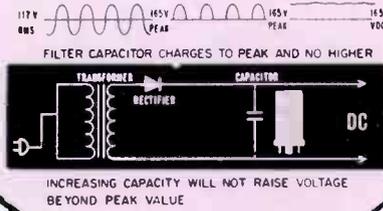**ELECTROLYTICS ARE USED AS FILTER CAPACITORS FOR POWER SUPPLIES — IN CIRCUITS WHERE CLOSE TOLERANCES ARE NOT NEEDED.**



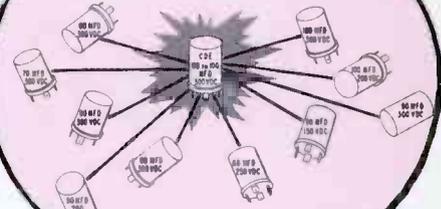**ONE CAN REPLACE MANY; NO NEED FOR EXACTITUDE.**




**EIA TOLERANCES PROVE THIS.**

3.4.5 The tolerance from nominal rated capacitance shall be:

Rated DC Voltage	Capacitance Tolerance
From 3 to 50 volts, inclusive	-10% to +100%
From 51 to 350 volts, inclusive	-10% to +100%
From 351 to 450 volts, inclusive	-10% to +50%

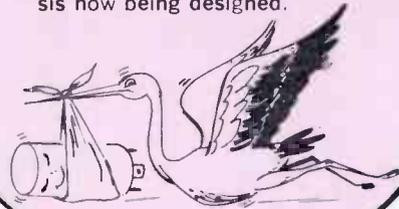**NEW RATINGS ARE USUALLY COVERED BY WIDE RANGE COLOR-LYTICS.®**

No waiting for new "exact" replacements; wide range lytics will replace many cans in chassis now being designed.



**MAKE MORE MONEY!**



- Faster turnover
- More dollars earned
- Less dollars invested
- Less obsolescence
- Better customer service
- Fewer lost sales
- Less back orders
- Quicker inventory
- Less shelf space
- Better and wider coverage

**Six straight shots from the Wide Ranger.**

For TV replacement electrolytics there are many advantages with Wide Range Color-Lytics.® Most important for you, it means more profit. The Wide Ranger represents CDE's wide range electrolytic program. His 200-plus replacement electrolytics do the job of over 2000 so-called "exact" replacements. Since each of CDE's units are suitable for a number of different ratings, you can serve your customers better and faster with reduced inventories at greater profit. CDE Wide Range Color-Lytics—they should make everyone in the business happy except the Exact Kid.



**CDE CORNELL-DUBILIER**


50 Paris Street, Newark, New Jersey 07101

Circle 1 on literature card

*You asked for it, waited for it and now here it is!*


# WINEGARD ULTRA-<sup>®</sup>PLEX

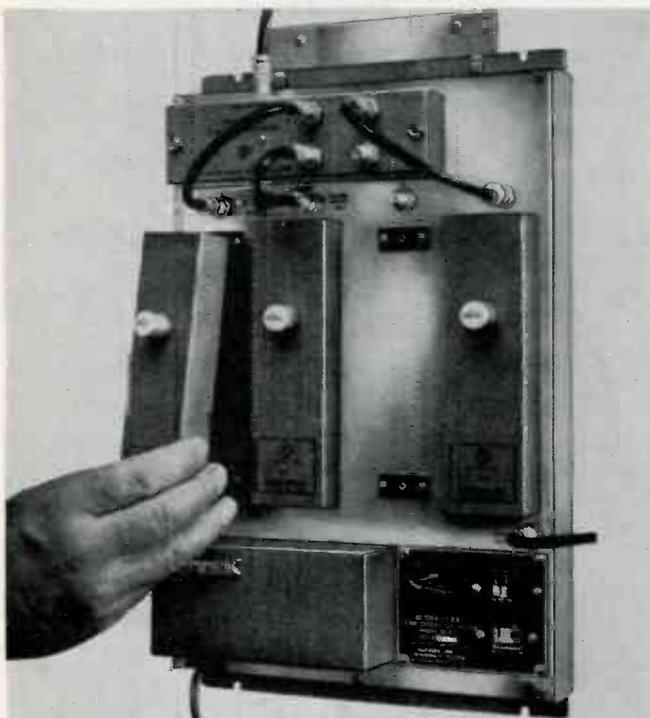**The first 82-channel, solid state MATV color distribution system!**



**82-Channel Ultra-Plex System**  
using lo band plug-in VHF amplifier  
... hi band plug-in VHF amplifier ...  
and broad band UHF amplifier.

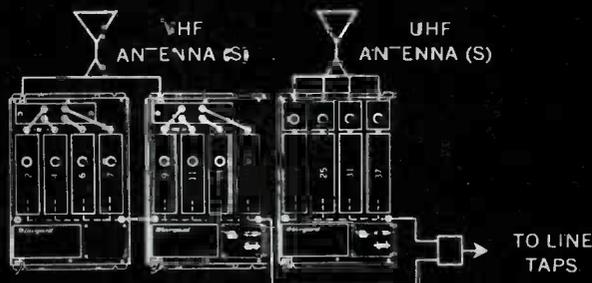**82-Channel Ultra-Plex System**  
using single channel plug-in amplifiers.



Winegard Ultra-Plex is a unique 82-channel, modular plug-in distribution system with all components matched to work together perfectly. The system never becomes obsolete, because you can add new LHF or VHF channels quickly, easily and inexpensively whenever needed.

Now you can have complete signal control of each channel!

- Amplifies! ■ Equalizes!
- and Feeds any number of channels to any number of tv sets —with a minimum of labor and equipment—and at a cost that's actually lower than most "VHF ONLY" systems!

For use in homes, as well as in the largest apartment buildings, hotels & motels, hospitals, etc.

Sensational Winegard **Ultra-Plex** is the best thing to ever happen to MATV system installers. Because **Ultra-Plex** gives the installer unprecedented flexibility regardless of system size. Because **Ultra-Plex** covers the full range of UHF, VHF and FM frequencies.

And because **Ultra-Plex** is super compact...installs easier than old fashioned equipment...costs less...and operates inexpensively with little or no maintenance.

Plenty of other reasons, too. **Ultra-Plex** incorporates your choice of either single channel or broad band solid state amplifiers that plug into the modular power panel. **Ultra-Plex** is totally designed with all the components needed to solve every conceivable distribution system problem. And **Ultra-Plex** equipment is manufactured to the highest commercial standards of quality—second to none.

If you are now installing MATV systems, you'll want to know more about profitable Winegard **Ultra-Plex**. Or if you've wanted to get into the booming MATV business, but thought it too complicated, let us show you exactly how easy and profitable it is. Write for Fact Finder #246 today. It gives you all the facts on MATV systems in general, and **Ultra-Plex** in particular.

 **Winegard**  
ANTENNA SYSTEMS

WINEGARD COMPANY • 3000 KIRKWOOD STREET  
BURLINGTON, IOWA 52601

© Copyright 1967, Winegard Company, Burlington, Iowa

# PF Reporter®

PHOTOFACT

*the magazine of electronic servicing*

VOLUME 18, NO. 3

MARCH, 1968

## CONTENTS

<b>Tube Substitution Supplement</b>		<b>a</b>
<b>The Electronic Scanner</b>		<b>4</b>
<b>Book Review</b>		<b>10</b>
<b>Is Your Test Equipment Up To '68 Standards</b>	T. T. Jones	<b>13</b>
<small>Out-moded servicing procedures are one result of out-dated test equipment.</small>		
<b>Fix That Scope Yourself</b>	Ellsworth Ladyman	<b>17</b>
<small>Don't let a circuit defect idle your scope and force you to change your servicing techniques.</small>		
<b>Test Equipment for Servicing Stereo</b>	Carl F. Moeller	<b>20</b>
<small>Equipment requirements and how to use what's available.</small>		
<b>Test Equipment for Servicing CB</b>	William E. Daupert	<b>26</b>
<small>A discussion of instruments currently on the market and the need for each.</small>		
<b>Service Your Own Multimeter</b>	Ellsworth Ladyman	<b>29</b>
<small>VOM's, VTVM's, FET Meters, and Transistorized Multimeters —troubleshooting tips on each.</small>		
<b>Volts Are Where They Find You</b>	A. J. Dilles	<b>43</b>
<small>A little negligence goes a long way . . . toward serious injury or even death.</small>		
<b>PHOTOFACT BULLETIN</b>		<b>44</b>
<b>Notes on Test Equipment</b>	T. T. Jones	<b>45</b>
<small>Lab reports on Jackson Model 810 Transistor Tester and Precision Apparatus Model V-95 VTVM.</small>		
<b>Video Speed Servicing</b>		<b>49</b>
<small>Service hints on Motorola Chassis STS-914YA, B, and Zenith Chassis 25NC37.</small>		
<b>Bridge Circuits—Part 2</b>		<b>53</b>
<small>Continuing our analysis of this most accurate electronic measuring circuit.</small>		
<b>Symfact: Balanced Diode Chroma Demodulator</b>		<b>59</b>
<b>The Troubleshooter</b>		<b>64</b>
<b>Test Equipment Manufacturers' Addresses</b>		<b>66</b>
<small>A list of those who produce service-type equipment.</small>		
<b>Product Report</b>		<b>67</b>
<b>Free Catalog and Literature Service</b>		<b>72</b>
<b>Monthly Index On Free Literature Card</b>		

PUBLISHER  
HOWARD W. SAMS

PUBLICATIONS  
DIRECTOR  
J. J. LIELAND

EDITOR  
WILLIAM E. BURKE

MANAGING EDITOR  
J. W. PHIPPS

ASSOCIATE EDITORS  
Thomas T. Jones  
Carl F. Moeller

CONSULTING EDITORS  
Noel C. Egler  
Joe A. Groves  
George B. Mann  
James M. Moore  
C. P. Oliphant

PRODUCTION MANAGER  
Susan M. Hayes

RESEARCH LIBRARIAN  
Mrs. Bonny Howland

CIRCULATION MANAGER  
Pat Osborne

ART DIRECTORS  
Louis J. Bos, Jr. & Robert W. Reed

PHOTOGRAPHY  
Paul Cornelius, Jr.

ADVERTISING SALES MANAGER  
ROY HENRY

Howard W. Sams & Co., Inc., 4300 W. 62nd St.  
Indianapolis, Ind. 46206 • 317-291-3100

ADVERTISING SALES OFFICES

*Eastern Regional Sales Manager*

ALFRED A. MENEGUS

Howard W. Sams & Co., Inc., 3 W. 57th St.  
New York, New York 10019 • 212-688-6350

*Midwestern Regional Sales Manager*

TOM MOWRY

Howard W. Sams & Co., Inc., 4300 W. 62nd St.  
Indianapolis, Ind. 46206 • 317-291-3100

*Southwestern Regional Sales Manager*

MARTIN TAYLOR

P. O. Box 22025, Houston, Texas 77027  
713-621-0000

*western/Los Angeles*

G. R. HOLTZ

The Maurice A. Kimball Co., Inc.  
2008 W. Carson St., Suites 203-204  
Torrance, Calif. 90501 • 213-320-2204

*western/San Francisco*

The Maurice A. Kimball Co., Inc.

580 Market St., Room 400  
San Francisco, Calif. 94104 • 415-392-3365  
Address all correspondence to PF REPORTER  
4300 W.62nd Street, Indianapolis, Indiana 46206



Copyright © 1968 by Howard W. Sams & Co., Inc. PF REPORTER is a trademark of Howard W. Sams & Co., Inc. No part of PF REPORTER may be reproduced without written permission. No patent liability is assumed with respect to use of information herein. Acceptance of advertising does not in any manner signify the products, policies and services so advertised have been approved, endorsed or recommended by this magazine.

Subscription Prices: 1 year—\$5.00, 2 years—\$8.00, 3 years—\$10.00, in the U. S. A., its possessions and Canada. All other foreign countries: 1 year—\$6.00, 2 years—\$10.00, 3 years—\$13.00. Single copy 75c; back copies \$1.

Indexed in Lectrodex. Printed by the Waldemar Press Div. of Howard W. Sams & Co., Inc.

## ABOUT THE COVER


The switch from tube to solid-state components in nearly all areas of electronic design has affected the service technician's test equipment requirements. Not only must the technician keep abreast of the latest development in circuit design, but he must also continually evaluate his test equipment to assure that its capability matches the servicing demands of new circuitry and components. Our cover this month illustrates this point and indicates the featured contents of this annual test equipment issue.



DEAR ANT GRACE.

OUR TV BROKE. UNKLE JOE  
TRIED TO FIX IT. THEY TOOK  
UNKLE JOE TO THE HOSPITAL  
AN THE TV WAS WORZER.  
DADDY CALLED THE TV MAN  
WHO FIXED IT. WE ARE  
GLADDER THE TV WORKZ  
SO GOOD AZ NEW. BUT  
NOT UNKLE JOE. HE WILL BE  
HOME ZOON BUT THE DR. SAYD  
KEEP HIZ HANDZ OUT OF  
THE TV.

LOVE BOBBY.

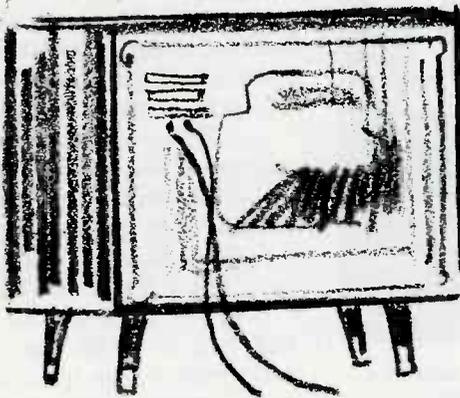

See your Sprague Distributor for window-size blow-ups of this message. Or, send 10¢ to Sprague Products Co., 105 Marshall St., North Adams, Mass. 01247 to cover handling and mailing costs. Please ask for poster RP-36.


**Call in your neighborhood TV technician when your set first starts acting up...you'll please the family ...and SAVE money in the long run!**

**THIS MESSAGE WAS PREPARED BY SPRAGUE PRODUCTS COMPANY,  
DISTRIBUTORS' SUPPLY SUBSIDIARY OF SPRAGUE ELECTRIC COMPANY, NORTH ADAMS, MASSACHUSETTS FOR...**

**YOUR INDEPENDENT TV-RADIO SERVICE DEALER**

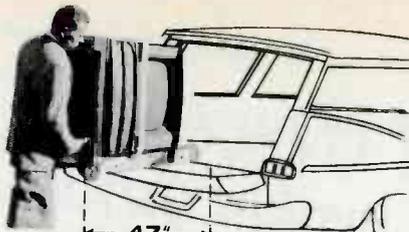**DON'T FORGET TO ASK YOUR CUSTOMERS "WHAT ELSE NEEDS FIXING?"**

**SAVES**  
your back...  
**SAVES**  
your time...



# YEATS SHORTY DOLLY


for RADIO and TV

just 47 inches high for STATION WAGONS  
and PANEL PICK-UPS



FOLDING PLATFORM  
15 1/4" x 24 1/2" top.  
Snaps on or off.  
(Platform only)  
\$11.95

Designed for TV, radio and appliance men who make deliveries by station wagon or panel truck... the short 47 inch length saves detaching the set for loading into the "wagon" or pick up. Tough, yet featherlight aluminum alloy frame has padded felt front, fast (30 second) web strap ratchet fastener and two endless rubber belt step glides. New folding platform attachment, at left, saves your back handling large TV chassis or table models. Call your YEATS dealer or write direct today!

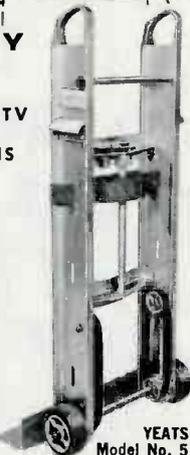

YEATS  
Model No. 5  
Height 47"  
Weight 32 lbs.



FURNITURE PAD

## "Everlast" COVER AND PADS

YEATS semi fitted covers are made of tough water repellent fabric with adjustable web straps and soft, scratchless white flannel liners. All shapes and sizes — Write



TV COVER


**YEATS**

APPLIANCE DOLLY SALES COMPANY

1307 W. Fond du Lac Ave. • Milwaukee, Wisconsin

Circle 4 on literature card

# EIGHT INSTRUMENTS IN ONE

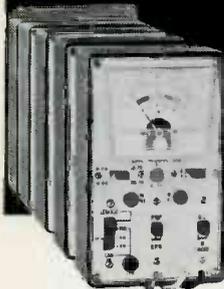

- Out-of-Circuit Transistor Analyzer
- Dynamic In-Circuit Transistor & Radio Tester
- Signal Generator
- Signal Tracer • Voltmeter
- Milliammeter
- Battery Tester
- Diode Checker

## Transistor Analyzer Model 212

Factory Wired & Tested — \$19.50  
Easy-to-Assemble Kit — \$13.50

**YOU DON'T NEED A BENCH FULL OF EQUIPMENT TO TEST TRANSISTOR RADIOS!** All the facilities you need to check the transistors themselves — and the radios or other circuits in which they are used — have been ingeniously engineered into the compact, 6-inch high case of the Model 212. It's the transistor radio troubleshooter with all the features found only in more expensive units. Find defective transistors and circuit troubles speedily with a single, streamlined instrument instead of an elaborate hook-up.

**Features:**

Checks all transistor types — high or low power. Checks DC current gain (beta) to 200 in 3 ranges. Checks leakage. Universal test socket accepts different base configurations. Identifies unknown transistors as NPN or PNP.

Dynamic test for all transistors as signal amplifiers (oscillator check), in or out of circuit. Develops test signal for AF, IF, or RF circuits. Signal traces all circuits. Checks condition of diodes. Measures battery or other transistor-circuit power-supply voltages on 12-volt scale. No external power source needed. Measures circuit drain or other DC currents to 80 milliamperes. Supplied with three external leads for in-circuit testing and a pair of test leads for measuring voltage and current. Comes complete with instruction manual and transistor listing.

EMC, 625 Broadway, New York 12, N.Y.

Send me **FREE** catalog of the complete value-packed EMC line, and name of local distributor. **PF-3**

NAME \_\_\_\_\_


ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ ZONE \_\_\_\_\_ STATE \_\_\_\_\_

**EMC**

ELECTRONIC MEASUREMENTS CORP.  
625 Broadway, New York 12, New York  
Export: Pan-Mar Corp., 1270 B'way, N.Y. 1

Circle 5 on literature card

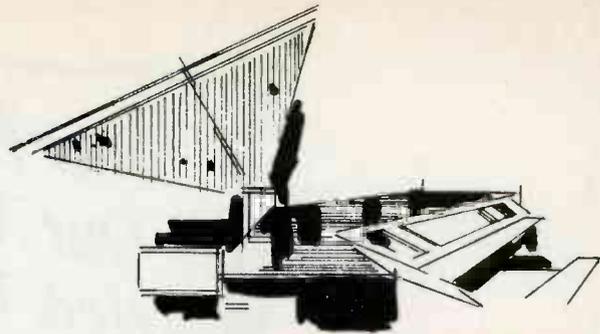

# THE SCANNER

## ELECTRONIC

RCA Sales Top \$3 Billion

RCA's sales in 1967 exceeded \$3 billion for the first time in the company's forty-eight year history and profits also registered a slight advance to a new record level for the sixth successive year, President Robert W. Sarnoff announced.

He told the company's 330,000 shareholders in a year-end statement that the sales and profit rises were achieved despite general economic uncertainties and a month-long strike at nine RCA plants which contributed to a 21% decline in second quarter earnings.

Among the highlights of RCA's performance in 1967 singled out by Mr. Sarnoff were the following:

—Color television manufacturing and broadcasting "continued to make the largest contribution to the company's overall progress." Dollar sales of RCA color sets were 20% ahead of 1966. RCA strengthened its traditional position of leadership in the color industry. Its share of the total set market was greater at year's end than at the beginning.

—NBC revenues exceeded the \$500 million mark for the second successive year, reaching a new sales peak.

—The Hertz Corporation, which became an RCA subsidiary in 1967, registered its highest sales, as did the RCA Service Company, RCA Communications, Inc., and sales of RCA products and services abroad.

—RCA continued its capital expenditures at the high rate of 1966. For the two years, approximately \$400 million was spent for domestic plant and equipment, "representing the greatest investment effort in the history of the company."


Looking to the future, Mr. Sarnoff said RCA will intensify its emphasis on the company's development as a broadly based and diversified communications, electronics, and service organization with an increasingly international orientation.

**Auto Sound Sales Exceed \$1 Billion**

Automotive sound equipment—radio and tape player systems—has passed the billion-dollar mark in world wide annual sales and already exceeds the growth rate of color television.

Oscar P. Kusisto, vice president and general manager of Motorola's automotive products division, reported that automotive sound sales—AM, FM, multiplex radio,
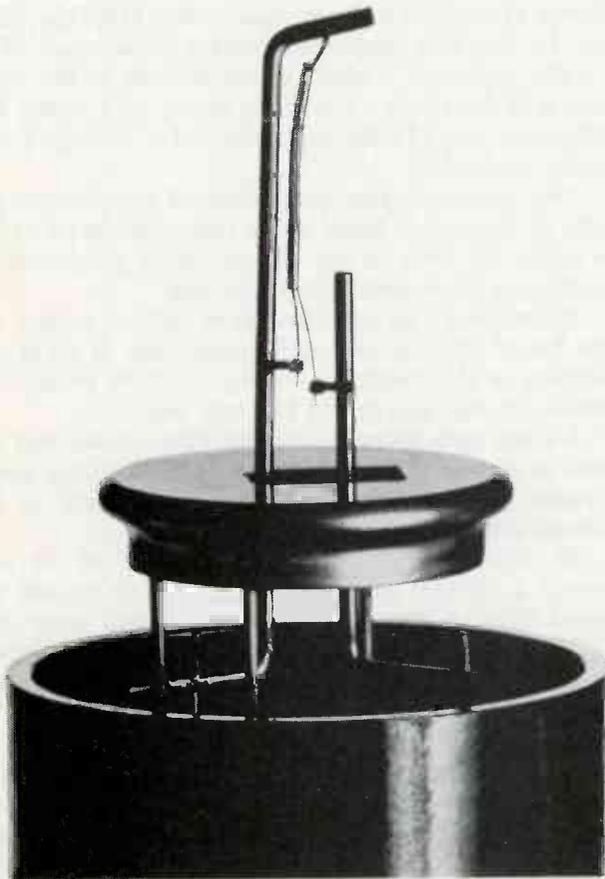
# We've rectified high-voltage rectifiers.



How it used to be.

Take a look at our new "Posted filament" design. There's no delicately suspended heater-cathode system. There's no need to heat up a metal sleeve and then an oxide coating.


It takes less than a second for the 3CU3 to start rectifying full swing.

In case of a break, there's no way for the 3CU3's filament to fall against the anode, creating a short and knocking out other components in the circuit.

The 3CU3's filament is always perfectly centered. It emits electrons uniformly in every direction. From a much larger surface than in the old design. There's no suspension post in the way to create an "electron shadow" that cuts down the plate current.

The uniform electric field around the rigid support reduces high voltage stresses. Arcing and its resulting troubles are eliminated.

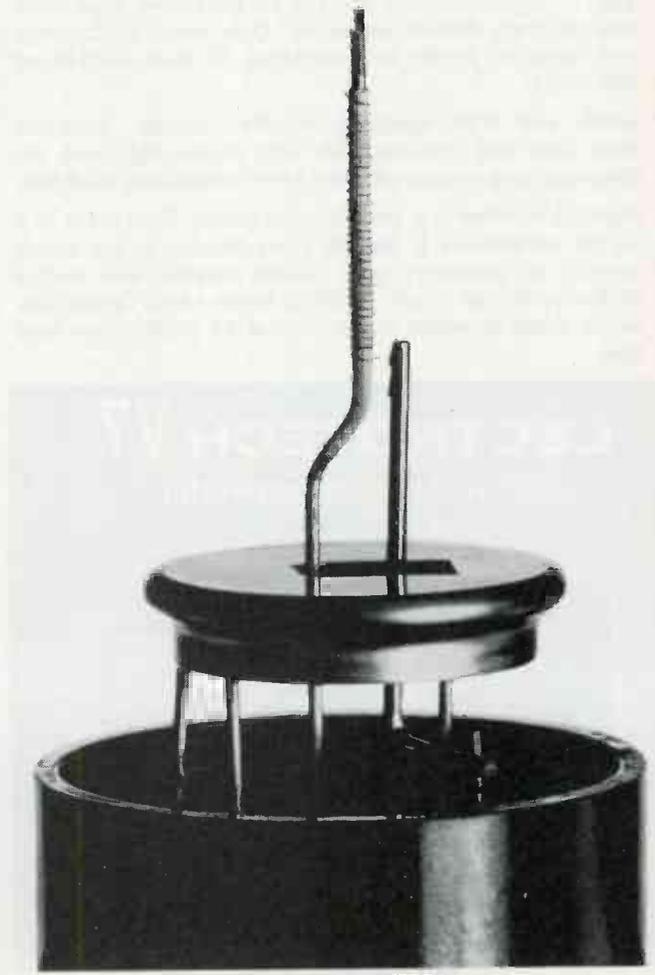The 3CU3 is interchangeable with 3A3 and 3A3A




Our new 3CU3

high voltage rectifiers. And it's made exclusively by Sylvania.

The 3CU3 is just one of a new "posted filament" family which includes the new 3BL2 and 3BM2. They're designed for use in new color TV sets. These tubes are especially good for transistorized TV where their fast warm-up fits in with the "instant on" feature of solid state circuitry.

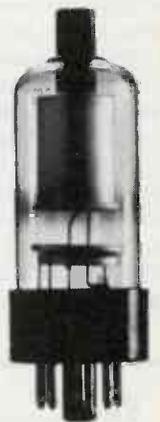The new construction has higher reliability and longer life and should give you fewer and less troublesome callbacks.



From the outside you can hardly tell it's changed.

**SYLVANIA**  
A DIVISION OF  
GENERAL TELEPHONE & ELECTRONICS

# Why is a Vectorscope essential for Color TV servicing?

- 1 Check and align demodulators to any angle . . . 90°, 105°, 115° . . . accurately and quickly. No guesswork. New color sets no longer demodulate at 90°. Only with a Vectorscope can these odd angles be determined for those hard-to-get skin tones.
- 2 Check and align bandpass-amplifier circuits. Eliminate weak color and smeared color with proper alignment. No other equipment required. Only a V7 Vectorscope does this.
- 3 Pinpoint troubles to a specific color circuit. Each stage in a TV set contributes a definite characteristic to the vector pattern. An improper vector pattern localizes the trouble to the particular circuit affecting either vector amplitude, vector angle or vector shape. Only a V7 Vectorscope does this.



## EXCLUSIVE FEATURES:

**Color Vectorscope:** Until now, available only in \$1500 testers designed for broadcast use. Accurately measures color demodulation to check R-Y and B-Y, for color phase and amplitude. A must for total color and those hard-to-get skin tones. **Self-Calibrating.** Adjust timing circuit without external test equipment. **Dial-A-Line.** Adjust horizontal line to any width from 1-4 lines. **Solid State Reliability** in timer and signal circuits. **Plus:** All Crosshatch, Dots, Vertical only, Horizontal only and Keyed Rainbow Patterns. RF at channels 3, 4 or 5. Video Output (Pos. and Neg. adjustable) for signal injection trouble-shooting. Red-Blue-Green Gun. Killer. All transistor and timer circuits are voltage-regulated to operate under wide line voltage ranges. Lightweight, compact—only 8¼x7½x12½". **NET 189<sup>50</sup>**

**ONE YEAR WARRANTY**

**V6-B** New, improved complete color bar generator with all the features of the V7 except the Vectorscope. Only **99.50**



For the full story, see your distributor or write for literature.

Dept. PF-3

**LECTROTECH, INC.**

1221 W. Devon Ave., Chicago, Ill. 60626

Circle 7 on literature card

and tape cartridge systems—have increased 25% in the past year and could exceed a third of color television's dollar volume by the end of 1968. Kusisto made his predictions at a press briefing during the annual Automobile Accessories Manufacturers of America (AAMA) show in Chicago. He based his comments on Motorola studies of the original equipment, distributor, and retail markets in the U.S. and abroad.

Kusisto said automotive sound equipment involves a total world market this year of 13 million units, at least three-fourths of which are sold in the United States. His figures exclude cassette and PlayTape players. He said this burgeoning market is the result of an "audio explosion," which is attributable to the interaction of three major marketing forces: (1) youth, (2) affluence, and (3) the availability of a variety of new audio equipment.

"An ever-increasing percentage of population—not only in the United States but in other nations as well—is under 25 years of age. These young people are an audio, verbal, mobile group," he said.

"Combined with this is our more affluent society and the broad range of new audio equipment. A great percentage of the market is 'trading up' from simple AM radio, for example, to FM and tape players."

Kusisto said Motorola studies have shown that the rate of growth of worldwide sales of automotive sound systems will continue to increase substantially for the foreseeable future.

In 1968, he pointed out, retail value of the estimated 2,750,000 automotive tape units to be sold will reach \$220 million. He predicted sales of more than 2,300,000 after-market car radios for \$160 million, and 8,000,000 radio and tape players will go into new cars at an estimated cost of \$600 million.

Further, Kusisto said, automotive tape player systems have fostered a new market for other units which use the same tape cartridges. The result, he said, is that from 1,000,000 to 1,500,000 four- and eight-track portable, battery-operated tape players and home tape players will add up to \$80 million to the market total.

Beyond that, he said, "will be sales of a wide range of related products—speaker, tuners, multiplex, reverb units, and other hardware—which easily will amount to another \$200 million.

## Littelfuse To Sell

The Board of Directors of **Littelfuse** has approved the definitive agreement for the sale of substantially all of its assets of **Tracor Inc.**, of Austin, Texas. The transaction had been approved in principle on November 30, 1967.

The Agreement will now be submitted for approval by the Board of Directors of Tracor. Under the terms of the agreement, Littelfuse shareholders will receive one share of Tracor convertible preferred stock for each two common shares of Littelfuse.

## FTC Renders Opinion

The Commission was recently requested to render an advisory opinion with respect to the legality of a trade



# \$975

EFFECTIVE 8/1/67

## GUARANTEED

*Nine-seventy-five* buys you a complete tuner overhaul—including parts (except tubes or transistors)—and absolutely no hidden charges. All makes, color or black and white, UV combos only \$15.

*Guaranteed* means a full 12-month warranty against defective workmanship and parts failure due to normal usage. That's 9 months to a year better than others. And it's backed up by the only tuner repair service authorized and supervised by the world's largest tuner manufacturer—Sarkes Tarzian, Inc.

Four conveniently located service centers assure speedy in-and-out service. All tuners thoroughly cleaned, inside and out . . . needed repairs made . . . all channels aligned to factory specs, then rushed back to you. They look—and perform—like new.

*Prefer a replacement? Sarkes Tarzian universal replacements are only \$10.45, customized replacements \$18.25. Universal replacements shipped same day order received. On customized, we must have original tuner for comparison purposes, also TV make, chassis, and model number. Order universal replacement by part number. Send orders for universal and customized replacement tuners to Indianapolis.*

Part #	Intermediate Frequency	AF Amp Tube	Osc. Mixer Tube	Heater
MFT-1	41.25 mc Sound 45.75 mc Video	6GK5	6LJ8	Parallel 6.3V
MFT-2	41.25 mc Sound 45.75 mc Video	3GK5	5LJ8	Series 450 MA
MFT-3	41.25 mc Sound 45.75 mc Video	2GK5	5CG8	Series 600 MA

*Genuine Sarkes Tarzian universal replacement tuners with Memory Fine Tuning—UHF Plug in for 82-channel sets—Pre-set fine tuning—13-position detent—Hi gain—Lo noise—Universal mounting*

**FOR FASTEST SERVICE, SEND FAULTY TUNER WITH TV MAKE, CHASSIS, AND MODEL NUMBER, TO TUNER SERVICE CENTER NEAREST YOU**



**TUNER SERVICE CORPORATION**    *FACTORY-SUPERVISED TUNER SERVICE*

MIDWEST.....817 N. PENNSYLVANIA ST., Indianapolis, Indiana .....TEL: 317-632-3493  
(Home Office)

EAST.....547-49 TONNELE AVE., Jersey City, New Jersey .....TEL: 201-792-3730  
(Under New Management)

SOUTH-EAST.....938 GORDON ST., S. W., Atlanta, Georgia .....TEL: 404-758-2232

WEST.....SARKES TARZIAN, Inc. *TUNER SERVICE DIVISION*  
10654 MAGNOLIA BLVD., North Hollywood, California .....TEL: 213-769-2720

Circle 8 on literature card

# LEADER TEST INSTRUMENTS

*Much in little*

*New!*



**\$13450**

LCG-387

## COLOR BAR PATTERN GENERATOR

Here it is—LEADER's new color bar pattern generator which includes the keyed rainbow, SQUARE crosshatch, dots, AND the single cross bar. In fact, this cross pattern will speed up adjustments on raster centering, purity at the center and dynamic convergence. Sharp and clear lines, both vertical and horizontal, produced by return trace blanking. Two switchable channels, 5 and 6, with 10mV output. Solid state, of course, with voltage regulated supply. Compact and sturdy construction for field use—supplied with carrying bag for convenience. Size only 2½ H × 6¾ W × 4¾ D in., and weight 3.3 lbs approx.

**LEADER ELECTRONICS CORP.**

NEW YORK OFFICE

101-103 ROME ST., FARMINGDALE, L.I., N.Y. 11735

TEL (516) 694-1534 541-5373


Circle 9 on literature card

association preparing and distributing a standard rate and service pricing manual for common use by electronics servicemen in dealing with the general public.

It was represented that a major problem in the industry is the lack of guides by which the public can determine whether prices charged for various repair services are fair and equitable. This lack has led to many customers complaints and to fraudulent operations by unethical repairmen. The association took the position that a standard rate schedule would protect the public and free ethical servicemen from unjust accusations.

The Commission advised that it could not give its approval to the proposed common use of a standard rate and service pricing manual by competing electronics servicemen. While the adoption and dissemination by the association of such a manual may be motivated by a purpose to remove evils affecting the industry, it appears to go further than is reasonably necessary to accomplish the desired result. Even though use of such manual be accompanied by disclaimers, there is implicit therein too grave a danger that it will serve as a device through which service rates and fees would become uniform and stable throughout the industry. While adoption of a means likely to create competitive uniformity in terms of service pricing may be a convenience to trade association members, this factor is far outweighed by the benefits to the public of the intense competition between competing servicemen, and it is this competition which the law protects. *Editor's note: The above is a copy of a recent news release from the Federal Trade Commission. In essence it says that the FTC holds the opinion that a trade association cannot legally issue a pricing guide.*

### Mighty Microscope

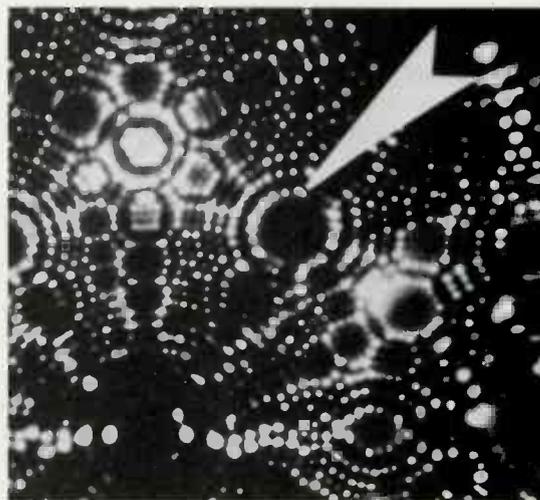

In the photo above, the arrow points to a single atom of tungsten. The new microscope, called the atom-probe, field-ion microscope, is currently being developed by Professor Erwin Mueller at the Pennsylvania State University.

This new microscope can not only focus on a single atom, but also separates it from thousands of surrounding atoms and then identifies it in a spectrometer. The above photo represents a magnification of approximately 2.1 million times. ▲

# The people puller



\*Optional with dealer

## RCA's Headliner: first and finest of the 14-inch portable color TVs.

First because it's pulled the most sales of any 14-inch diagonal color set made. Finest because it's got the big features. Like advanced circuitry that won't go haywire. Like true room-to-room portability. And a 102 sq. in. picture that's true to life—and true to the reputation of the pioneer name it bears. Sell the first and finest, the Headliner. It's one reason we say: When you're the first name in home entertainment there's got to be a reason.

# RCA

# FAST

## COMPLETE OVERHAUL ON ALL MAKES OF TV TUNERS

Maximum Time In Shop 24 Hrs.



(WE SHIP C.O.D.)


### \$9.50

Black &  
White  
or Color

VHF or  
UHF

UV Combo's \$15.00

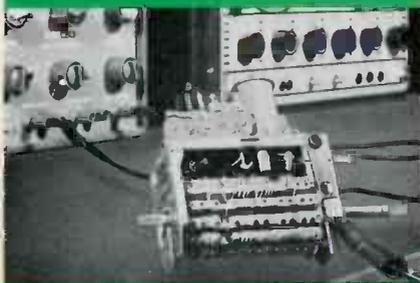Price includes all labor and parts except Tubes, Diodes & Transistors. If combo tuner needs only one unit repaired, disassemble and ship only defective unit. Otherwise there will be a charge for a combo tuner. Ship tuners to us complete with Tubes, Tube Shields, Tuner Cover and all parts (including) any broken parts. State chassis, model number and complaint.



All tuners are serviced by **FACTORY TRAINED TECHNICIANS** with years of experience in this specialized field. All tuners are **ALIGNED TO MANUFACTURERS SPECIFICATION** on crystal controlled equipment and air checked on monitor before shipping to assure that tuner is operating properly.

## GEM CITY TUNER REPAIR SERVICE

Box 6C Dabel Station  
2631 Mardon Drive  
Dayton, Ohio 45420

Circle 10 on literature card

## BOOK REVIEW

**Lasers and Masers:** Charles A. Pike; Howard W. Sams and Co., Inc., Indianapolis, Indiana, 1967; 176 pages, 8½" x 5½", soft cover; \$4.95.

Although an understanding of the laser (Light Amplification by Stimulated Emission of Radiation) and maser (Microwave, etc.) is hardly essential to the TV technician, many will enjoy having some knowledge of this subject. Physics is introduced only to the extent necessary for explaining the subject at hand, and the treatment of the material in this book is remarkably concise for so complex a subject. The author has employed the style of programmed instruction. That is, each subtopic is treated in a page or two, and a few pertinent questions are asked at the end of the page. The answers are at the top of the next page, allowing the reader to check himself before proceeding.

The text is divided into seven chapters as follows: Chapter 1 is introductory and covers atoms and molecules, the elements, chemical combinations and valence bonds, wave motion, and some of the basic principles of light. Chapter 2 is a short (10 pages) resume of early developments in atomic theory, and Chapter 3 proceeds to quantum theory, quantum numbers, and the dual nature of the electron.

The principles of masers and lasers are explored in Chapter 4. This chapter is divided into sections, such as population of energy levels, maser and laser action, and application of these principles to specific materials: gas, solid-state, and semiconductor. Chapters 5 and 6 explain the actual construction and operating characteristics of masers and lasers, respectively. The final Chapter discusses applications of both lasers and masers. ▲

## impedance mismatch problems?

When most voice coil impedances were either 3.2 ohms or 8 ohms, speaker replacement was relatively simple. Then came transistor sets, and equip-

ment without output transformers, and now voice coil impedances range all over the map.

It's important to remember that a mismatched impedance in a speaker replacement will almost surely create problems . . . from a loss of volume to a blown transistor.

## Quam... and only Quam... helps you avoid these problems these three ways:

**1. WIDE CHOICE**—As Photofacts/Counterfactors participants, we know in advance what voice coil impedance the new equipment will require, so we generally have the right speaker in our comprehensive line *when you need it*.

**2. VERSATILE SPEAKERS**—Quam *multi-tap speakers* offer a choice of impedances in a single unit. Available in all the sizes you need for automotive replacement, Quam multi-taps handle 10, 20, or 40 ohm applications.

**3. SPECIAL SERVICE**—Just in case you run across an oddball, we offer this convenient exclusive: *any Quam speaker can be supplied with any voice coil impedance, only \$1.00 extra, list price.*



### QUAM

THE QUALITY LINE  
FOR EVERY SPEAKER NEED

**QUAM-NICHOLS COMPANY**  
234 East Marquette Road • Chicago, Illinois 60637

Circle 11 on literature card

# Join "THE TROUBLESHOOTERS"

who get paid top salaries for keeping today's electronic world running

Suddenly the whole world is going electronic! And behind the microwave towers, push-button phones, computers, mobile radio, television equipment, guided missiles, etc., stand THE TROUBLESHOOTERS—the men urgently needed to inspect, install, and service these modern miracles. They enjoy their work, and get well paid for it. Here's how you can join their privileged ranks—without having to quit your job or go to college to get the necessary training.



**J**UST THINK how much in demand you would be if you could prevent a TV station from going off the air by repairing a transmitter... keep a whole assembly line moving by fixing automated production controls... prevent a bank, an airline, or your government from making serious mistakes by servicing a computer.

Today, whole industries depend on electronics. When breakdowns or emergencies occur, someone has got to move in, take over, and keep things running. That calls for one of a new breed of technicians—The Troubleshooters.

Because they prevent expensive mistakes or delays, they get top pay—and a title to match. At Xerox and Philco, they're called Technical Representatives. At IBM they're Customer Engineers. In radio or TV, they're the Broadcast Engineers.

What do you need to break into the ranks of The Troubleshooters? You might think you need a college degree, but you don't. What you need is know-how—the kind a good TV service technician has—only lots more.

### Think With Your Head, Not Your Hands

As one of The Troubleshooters, you'll have to be ready to tackle a wide variety of electronic problems. You may not be able to dismantle what you're working on—you must be able to take it apart "in your head." You'll have to know enough electronics to understand the engineering specs, read the wiring diagrams, and calculate how the circuits should test at any given point.

Learning all this can be much simpler than you think. In fact, you can master it without setting foot in a classroom . . . and without giving up your job!

For over 30 years, the Cleveland Institute of Electronics has specialized in teaching electronics at home. We've developed special techniques that make learning easy, even if you've had trouble studying before. Our AUTO-PROGRAMMED™ lessons build your knowledge as easily and solidly as you'd build a brick wall—one brick at a time. And our instruction is personal. Your teacher not only grades your work, he analyzes it to make sure you are thinking correctly. And

he returns it the same day received, while everything is fresh in your mind.

### Always Up-To-Date

To keep up with the latest developments, our courses are constantly being revised. This year CIE students are getting new lessons in Laser Theory and Application, Microminiaturization, Single Sideband Techniques, Pulse Theory and Application, and Boolean Algebra.

In addition, there is complete material on the latest troubleshooting techniques including Tandem System, Localizing through Bracketing, Equal Likelihood and Half-Split Division, and In-circuit Transistor Checking. There are special lessons on servicing two-way mobile radio equipment, a lucrative field in which many of our students have set up their own businesses.

### Your FCC License—or Your Money Back!

Two-way mobile work and many other types of troubleshooting call for a Government FCC License, and our training is designed to get it for you. But even if your work doesn't require a license, it's a good idea to get one. Your FCC License will be accepted anywhere as proof of good electronics training.

And no wonder. The licensing exam is so tough that two out of three non-CIE men who take it fail. But our training is so effective that 9 out of 10 CIE graduates pass. That's why we can offer this famous warranty with confidence: If you complete a license preparation course, you get your FCC License—or your money back.

### Mail Coupon for 2 Free Books

Want to know more? Send for our 40-page catalog describing our courses and the latest opportunities in electronics. We'll also send a special book on how to get a Government FCC License. Both are free—just mail coupon below.

### ENROLL UNDER NEW G.I. BILL

All CIE courses are available under the new G.I. Bill. If you served on active duty since January 31, 1955, or are in service now, check box in coupon for G.I. Bill information.

**CIE** Cleveland Institute of Electronics  
1776 E. 17th St., Dept. PF-45 Cleveland, Ohio 44114

Cleveland Institute of Electronics  
1776 E. 17th St., Cleveland, Ohio 44114

Please send me without cost or obligation:

1. Your 40-page book "How To Succeed In Electronics" describing the job opportunities in electronics today, and how your courses can prepare me for them.
2. Your book on "How To Get A Commercial FCC License."

Name \_\_\_\_\_  
(Please Print)

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

Occupation \_\_\_\_\_ Age \_\_\_\_\_

Check here for G.I. Bill information  
Accredited Member National Home Study Council  
PF-45

Circle 12 on literature card

Industry Demanded - only Sencore delivered

# AN ALL NEW IMPROVED COLOR CRT TEST



**Simple - Fast - Accurate • Automatic Color Tracking!  
No Time-Wasting Logging and Computing!**

CRT manufacturers, set manufacturers, distributors, technicians — all demanded a better CRT tester than any available. This is it — the new Sencore CHAMPION — a winner on every count.

Separate G2 screen grid controls, just like the color circuit itself, enable you to set up each color gun, then automatically compare it with the others for tracking — exactly according to industry standards. This check is important when claiming credit for a defective color CRT. No time consuming logging of each color gun reading at every setting of the G2 control like competitive models. It's automatic with the CR143 Champion.

The CHAMPION also makes all the standard color and black and white CRT tests — shorts, emission, and life tests. Its Line Adjust control assures exceptional accuracy. Its exclusive three step Automatic Rejuvenation Circuit lets you save many a faulty black and white tube or equalize gun currents in color tubes.

The all-new CHAMPION is equipped with plug-in sockets for fast testing and easy updating. Rugged vinyl-clad steel case has spacious lead compartment.


For a sure thing, put your money on the champion — the Sencore CR143 CHAMPION.



**CR143  
CHAMPION**




**\$9950**

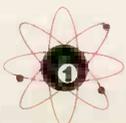

## SENCORE

NO. 1 MANUFACTURER OF ELECTRONIC MAINTENANCE EQUIPMENT  
#26 SOUTH WESTGATE DRIVE, ADDISON, ILLINOIS 60101

Circle 13 on literature card

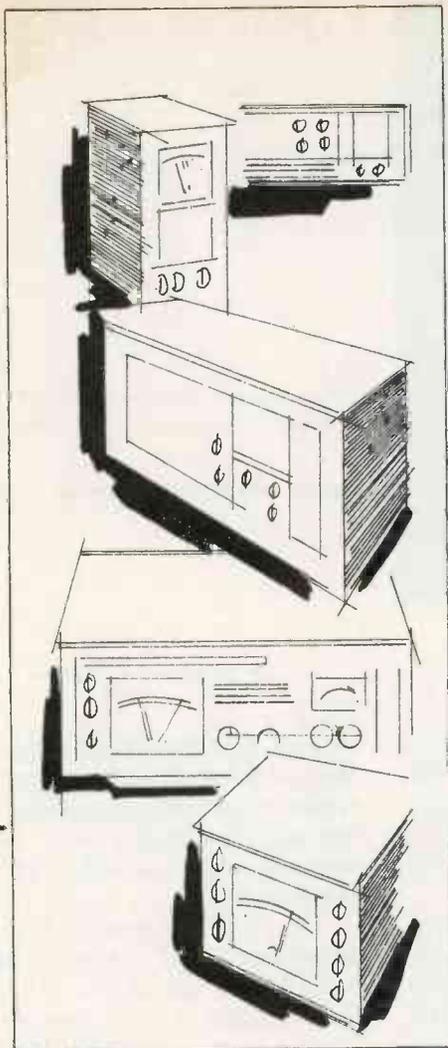

# IS YOUR TEST EQUIPMENT UP TO '68 STANDARDS?

by T. T. Jones

Nearly all test equipment has changed during the past few years; some have changed drastically, while others reflect only minor alterations. Also, a few types are gradually disappearing from the list of available equipment. The following paragraphs relate the most significant changes evident in service-type test instruments.

The 1968 service business is quite different from that of even two years ago, and customers are changing just as radically as the sets they bring in for service. Though there are still many customers who shop around for the cheapest service, more and more of your customers are discovering that the cheapest repair is not necessarily, and in fact is seldom, the best repair. So the 1968 customers are willing to pay realistic prices for your service. But they do demand value received for payment rendered—a fast repair, and most important, an accurate repair. Good test equipment can help you effect a quick, accurate repair.

There are some instruments on the market today which are considered essential to a well-equipped shop, yet had not even been invented a few years back. An FM Stereo generator is a good example. Other instruments on the market today are

not especially new in concept, but the features available today make it mandatory that you compare your present equipment with the new models. Perhaps some of the new features are valuable enough that you will wish to buy the new instrument, even though your old one is operating perfectly. Let's take a closer look at the features available in 1968 test equipment.

## Meters

An entirely new breed of meter has recently taken its place alongside the VTVM and VOM. We're talking of course, of the solid-state voltohmmeter. Nearly all of these use a field-effect transistor in the input stage, with a resulting input impedance quite similar to that of a VTVM. FET meters, therefore, can replace the VTVM in most applications, with the added advantage that

they're normally battery-operated.

For the most part, FET meters have been designed to cover the same ranges as the contemporary VTVM. Fig. 1 shows the ranges of an FET Voltohmmeter that is atypical, in that the designer has added two very low AC-DC voltage ranges and two extremely low AC ranges. This instrument, therefore, is much more sensitive to DC than the usual meters of a few years back, and its AC scales are as good as yesterday's AC VTVM—formerly a specialized instrument.

The AC input impedance of most FET VM's is as good as the DC impedance. Usually both are about 10 to 11 megohms, but some instruments have DC inputs as high as 15 megohms, while others have AC inputs as low as 1/2 megohm. In general, the FET meters are a decided improvement over VTVM's or VOM's in one area, while possibly

# COLOR GENERATORS

# FOR EVERY NEED

**4 reasons why Sencore is your best buy  
in professional test instruments**

**1**

## LOBOY CG10

America's lowest priced professional quality standard color bar generator. All solid state. Battery powered for maximum portability.

**\$89.95**



**2**

## LOBOY CG12

AC operated version of the CG10. Also has 4.5 MHz crystal controlled signal for fine tuning adjustment.

**\$109.95**



**3**

## COLOR KING CG141

Absolute stability assured by exclusive "Temp Control" and new timer circuitry. All standard patterns, plus new movable single dot and single cross. Analyzing features too.

**\$149.95**



**4**

## COLOR ANALYZER CA122B


The complete analyzer for color and B&W—far more than just a color generator. Has variable RF and IF outputs, composite video, chroma, and horizontal and vertical sync pulses.

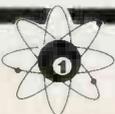**\$187.50**



Whatever the need, Sencore has the color generator that is just right for you. Each has the built-in quality you expect from Sencore. Each has standard RCA licensed color bar patterns.

Each is triple tested for guaranteed accuracy. Each is steel encased with chrome panel. See your distributor for more reasons why Sencore is your best buy, always.



# SENCORE

NO. 1 MANUFACTURER OF ELECTRONIC MAINTENANCE EQUIPMENT

426 SOUTH WESTGATE DRIVE ADDISON, ILLINOIS 60101



comparatively basic instrument composed of familiar electronic circuits. A comparison of basic block diagrams of a scope and a black-and-white receiver should remove all doubts you might have concerning your ability to effectively repair your own scope (Figs. 1 and 2).

A quick glance at the block diagrams should point up the fact that there are similarities in the design of the two instruments, and that the TV receiver is much more complex. Troubleshooting procedures are much the same for a scope as for other electronic devices. The first step is a careful analysis of the trouble symptom (to prevent the possibility of lost time checking properly functioning circuits) followed by a point-to-point check of the suspect

area. A brief description of oscilloscope theory, followed by typical scope circuit diagrams may help in relating this information to your particular scope. As is the case with radio and television manufacturers, test equipment manufacturers can find many different methods of doing the same job, and this fact precludes the use of specific scope circuits for illustration purposes.

#### What Is A Scope?

In a final analysis a scope is simply an electronic graph, which plots variations in voltage amplitude against time. This electronic graph indicates two (and sometimes more) separate and distinct values (amplitude and time) simultaneously, thus allowing the operator to view

changes in voltage amplitude at any given or specific instant. The importance of this tool is incalculable. Without a scope, it is virtually impossible to check the operation of a stage (such as an AGC amp) that depends on two simultaneous voltage pulses for proper operation.

#### Theory of Operation

Any functional scope found in an electronic repair shop will contain:

1. Input circuits.
2. Vertical amplifier and control circuits.
3. Horizontal amplifier and control circuits.
4. Horizontal sweep oscillator (to establish a time base).
5. Indicating circuits (CRT and associated circuitry to control brightness, focus, etc.).

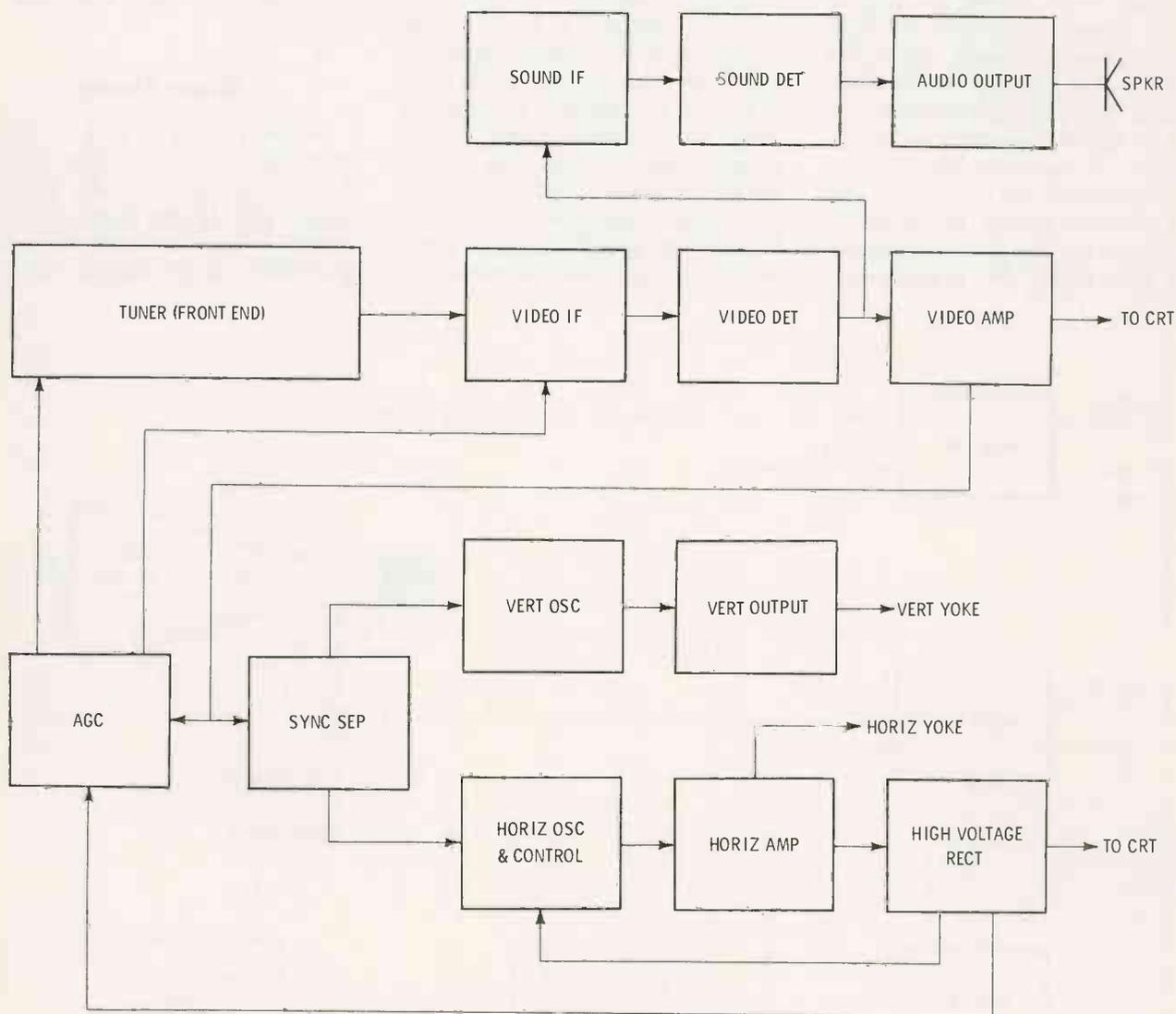


Fig. 2. Basic block diagram of a black-and-white receiver.

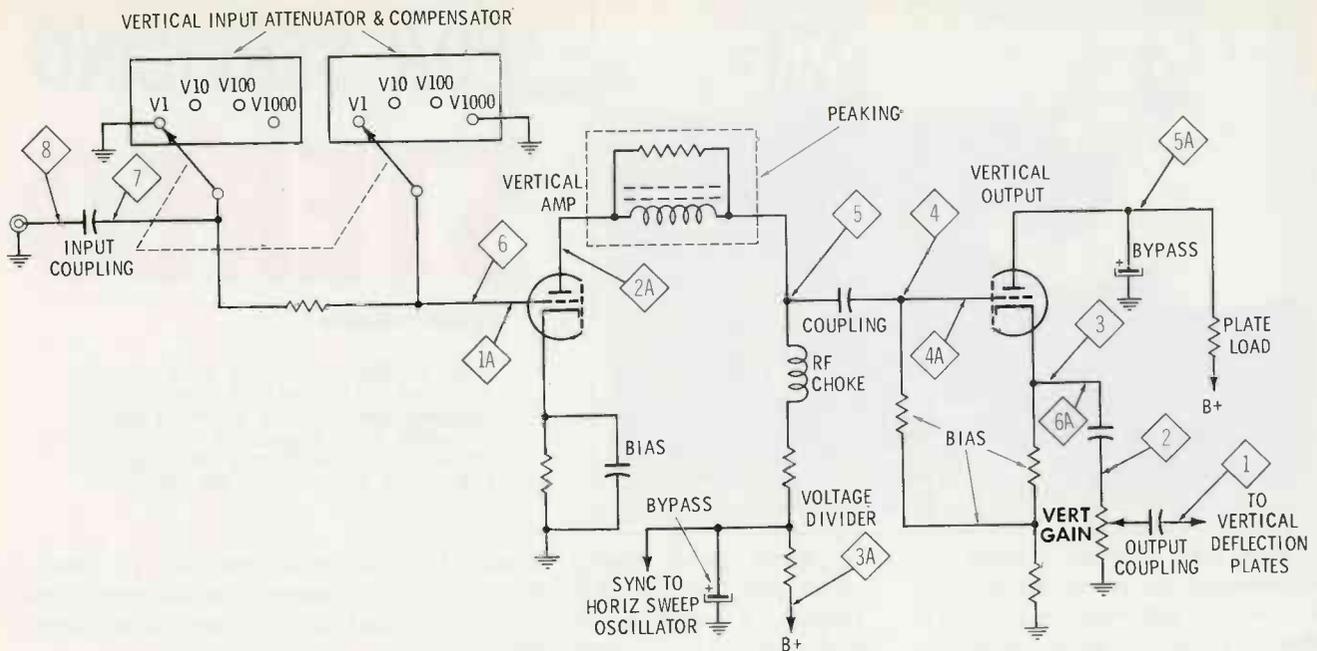


Fig. 3. Typical simplified vertical amplifier circuit.

6. Low-and high-voltage power supplies (many times combined in one section).

The vertical amplifier, or the output of the vertical section, is connected directly to the vertical deflection plates (Fig. 3). It makes very little difference, from a servicing standpoint, whether there is one or a half-dozen vertical amplifier stages before the CRT. In the initial analysis, if you do not have vertical gain, you do have trouble in the vertical circuit. The only reason for employing vertical amplifiers in the design of a scope is *increased sensitivity*. In fact, in most scopes you can apply the input directly to the vertical deflection plates of the CRT. If the signal is of sufficient magnitude, vertical amplification is not necessary. Most ignition analyzer scopes used by automobile mechanics do not have vertical amplifier stages, since the voltage spikes or pulses from the plugs and coils of modern high-compression engines are of sufficient magnitude to drive the vertical plates.

Vertical amplifier stages are usually operated Class A to insure the most faithful reproduction possible of the voltage signal under analysis. A careful check of the simplified, partial schematic of a typical vertical section will not introduce any new terms. The bias networks, decoupling capacitors, coupling capacitors, peaking coils, plate loads, voltage

dividers, and other circuits will all be found in the most simple of electronic devices.

The sawtooth voltage applied to the horizontal deflection plates of the CRT is usually derived from a horizontal sweep oscillator stage, such as shown in Fig. 4. This voltage provides a linear time base. The sweep oscillator is variable in fre-

quency so that you can adjust the sweep to display the desired number of cycles on the CRT screen. The terminology applied to these controls will vary from scope to scope. Names such as horizontal sensitivity, horizontal amp, horizontal frequency, microseconds-per-centimeter, etc. will be found. Regardless of the name, the function remains the

• Please turn to page 41


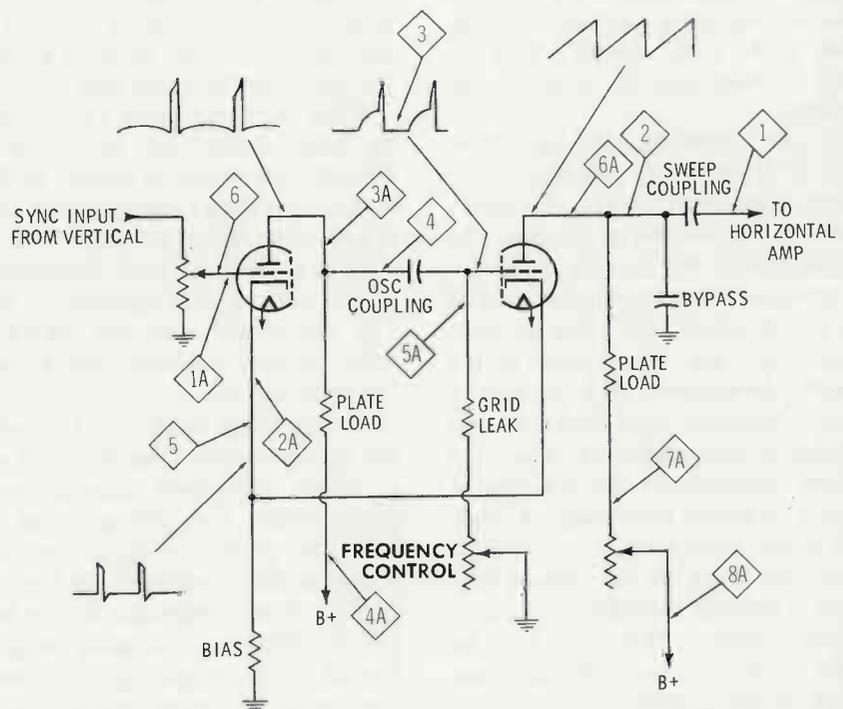


Fig. 4. Typical sweep oscillator circuit.

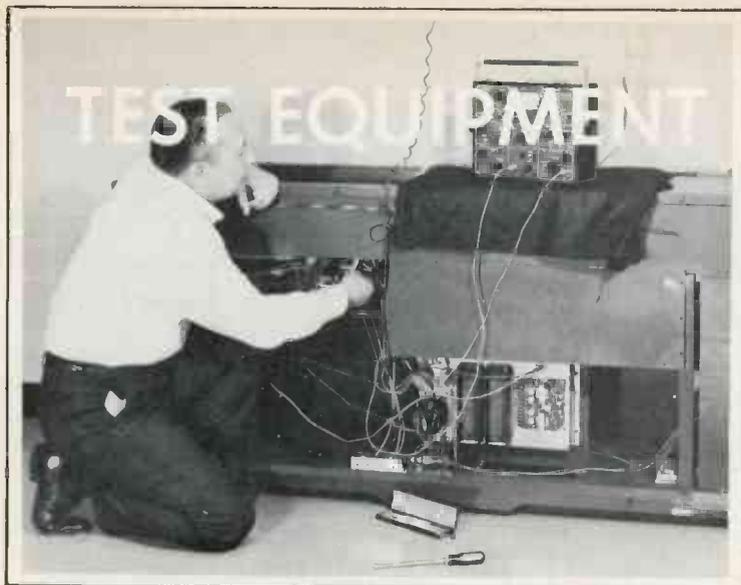

# FOR SERVICING STEREO

by Carl F. Moeller

While a VTVM, scope, and signal generator will permit you to solve most defects in stereo equipment, proper servicing demands a few test instruments designed specifically for audio and FM applications. The following article discusses both common and specialized test instruments.

Once upon a time, a farm boy unharnessed the team, greased the plow share, and went to town. He rented a room, bought a multimeter, seven vacuum tubes (one 12SA7, one 12SK7, one 12SQ7, and a pair of 50L6's and 35Z5's), a tube tester, and a board. On the board, he painted "Clyde's Radio Repair." Some months later, our hero added a 5Y3 and a pair of 6V6's to his inventory and repainted the board. "Clyde's Radio and Phonograph Service" was the most successful (and only) complete shop within a twenty-mile radius. During the "Big War," Clyde made a wad of money which he invested in Electric Canoe common, and, when TV hit the market, he hung up his soldering iron so he could devote all of his time to managing his finances and fishing.

Today, breaking into the stereo and hi-fi business requires a lot more effort than it did in Clyde's time. The evolution of the five-tube superhet into the modern color TV is perhaps more spectacular, but of no greater magnitude, than the evolution that has taken place in the sound reproduction field. To service stereo receivers, tape decks, record changers, and amplifiers, you need highly specialized test equipment plus a thorough knowledge of modern sound equipment.

At this point, we can almost hear what is running through many shop-owners' minds—"This guy must be some kind of a nut. People have been dragging their record players and FM radios into my shop for years and I fix them, no sweat. Now

he wants me to buy a bunch of exotic test gear that I'll never use. Besides, a customer squawks like mad over a \$12.00 repair bill; after all, his radio cost only \$39.95, brand new."

These low-priced radios and phonographs are always going to be a nuisance to the service industry, but there is a brighter side. During 1967, about 1,600,000 console phonographs were sold in this country. This is 200,000 less than in 1966, but the fact remains that in the past two years alone, almost 3.4 million phonographs, ranging in price from \$150 to \$2000, were delivered to their owners. In addition to these, a sizable number of stereo component systems were sold. All in all, there is a large, growing market for service in the stereo field.

Since the purchase of a high-quality radio/phonograph represents a considerable outlay of money by the owner, two things are apparent: (1) a legitimate repair bill (say, \$30 to \$50) is a relatively small percentage of the cost of the equipment, and (2) the owner who can afford a \$500 stereo is probably able to pay for good service.

On the other hand, a person who has invested several hundred dollars in stereo equipment expects good performance. Just getting sound to come out of the speakers does not complete the servicing procedure on quality stereo equipment. Before the job is completed, you must be certain that the original specifications concerning frequency response, sensitivity, distortion, hum, power output, wow and flutter, and separation

have been restored. To meet these requirements, some rather specialized test equipment is necessary.

## General Electronic Test Equipment

Before enumerating the instruments which have very specialized functions, let's review the ways in which you can service stereo with the equipment you already have—or should have. These are the scope, VTVM, VOM, transistor tester, capacitor tester, and tube tester.

Since the highest modulating frequency you will encounter in a stereo system is the SCA carrier at 67 kHz, there is no particular reason for the scope you use on the stereo bench to have a wide-band vertical amplifier. On the other hand, the vertical amplifier must have good low-frequency response, and a DC vertical input is very convenient. A high-impedance vertical input and a stable time base are also important. Since there are no sync pulses in a stereo, the scope has to "lock on" to sine waves, which is difficult.

Nearly all modern stereo equipment is transistorized. Therefore, you will require a VTVM with a low-voltage scale (no higher than 1 volt, full scale, and preferably lower). Since you will want to measure signal voltages, your VTVM must have flat frequency response up to 20 kHz. The same requirement applies to your VOM. It is also desirable that these meters have dB scales and built-in blocking capacitors to allow measurement of signals which are "riding" on a DC level. Since solid-state power ampli-

## First twist-prong electrolytic to identify itself.

Add up the time you've lost waiting for counter men to look up part numbers for twist-prong electrolytic capacitors.

That's how much time you'll save—when your Distributor stocks new RCA "P" type and "R" type twist-prong electrolytics. The reason: new RCA twist-prong capacitors have self-identifying stock numbers . . . the first in the industry. Your counter man can forget his catalogs and go right to the shelf . . . because RCA stock numbers enable him to stock his inventory in voltage rating and capacitance value sequence. His shelves are his RCA catalog.

These twist-prong electrolytics are the beginning of a complete capacitor line from RCA.

Other General Purpose Electronic Parts, with RCA quality assurance, will be available from your RCA Distributor in the near future. Insist on RCA parts. Your customers will appreciate it.

RCA PARTS AND ACCESSORIES, Deptford, N.J.

**Type: R = Regular Solder Terminals**

**P = Printed Circuit Board Terminals**

**Number of Sections in Can**

**W.V.D.C.**

**Capacitor Can Size**

**Capacitance Code for Shelf Location**



fiers often have resistors with values of one ohm or less, one of your meters should have a low ohms scale.

The transistor tester you are using now is probably adequate for servicing stereo. However, since the output transistors of power amplifiers are paired, replacement transistors should be checked for matching characteristics. This will minimize amplifier distortion, but a fairly accurate transistor tester is required.

A capacitor tester is more necessary for servicing audio amplifiers than it is for servicing RF and video amplifiers. While the latter rarely operate with a bandwidth of more than 5 octaves, a high-quality stereo amplifier must pass almost 9 octaves. For this reason, audio coupling circuits are critical in design, and a small loss in capacity of a coupling capacitor can seriously affect the frequency response of the amplifier. Leaky capacitors may be located by numerous methods, but it is quite difficult to locate a below-tolerance capacitor without a capacitor tester.

Vacuum-tube stereo equipment is becoming so passe that there is little need for a tube tester on the stereo bench. For the occasional tube-type sets that are still around, nearly any tube tester will suffice. However, it should have a sensitive grid-emission test.

### Turntables

Four pieces of test equipment are essential for servicing turntables. The one you should use most often is the simple strobe disc. Since many of the problems you encounter will involve speed variations or incorrect speed, every turntable that goes out of your shop should be checked with a strobe. Next comes the test record. This is a recording of pure tones at specified levels, making it useful for several purposes. Using it in conjunction with a scope (the third essential instrument) connected to the cartridge output, you can check the cartridge for frequency response, output level, and, roughly, for distortion. (A distortion meter connected to the cartridge via a linear amplifier gives a better check of distortion, of course.)

The last essential instrument is a stylus scale or pressure gauge. Today's cartridges perform best at their specified stylus tracking force.

More important, stylus and record wear is directly proportional to tracking force. If a cartridge and its stylus are designed for 1 gram of pressure against the record, 4 grams of pressure will quadruple the wear. Damage a couple of record albums for a customer, and you'll be convinced that you need this instrument.

A microscope is not essential, but it is an excellent tool for boosting your stylus sales. The profit margin on styli is very attractive, so it is just good business to invest a few dollars to help you sell them. A 30X to 60X microscope will let you show the customer that his present stylus is worn. When you explain how a worn stylus can ruin a record in a single playing, you are almost certain to make a sale. Sell a stylus a day, and your light bill is paid. Incidentally, even a diamond stylus finally wears out.

### Tape Transports

About the only test device you require specifically for tape decks is a test tape. This has standard recorded tones for head alignment and also may be used for checking the frequency response and distortion of a complete tape recorder. Strobe tapes are also available for checking tape speed. A strobe tape has alternate black-and-white transverse stripes and is used in the same manner as a strobe disc is used for turntables.

Although they are not items of test equipment, several other items are necessary for tape-deck maintenance. Tape-care kits are available from several manufacturers. These contain solvent, brushes, etc., and they may be sold as well as used in the shop. Another handy item is a lubricating tape. Running a lube tape through the tape deck lubricates the heads and guides. This is another item which you can also sell. Finally you will need a tape-head demagnetizer to degauss the tape heads before you return the deck to your customer.

### Audio Amplifiers

Getting a signal through a dead amplifier is not particularly difficult for a qualified technician. Assuming that the power supply is functioning, it is a simple matter to find the faulty stage by injecting a signal at the input of each stage, starting at the output. Simple, that is, if you have a signal generator. Any audio

generator may be used, but one of the pen-sized, transistorized harmonic generators is by far the most convenient. This little gadget is one of the greatest time-savers since sliced bread, so if you don't already have one, get one.


For checking frequency response and distortion, an audio signal generator is necessary. It should cover the entire audible frequency range (at least from 30 Hz to 15 kHz) and have a distortion content of no more than 1%. It is desirable that the generator have a built-in output meter, although this increases the cost. Naturally, any meter having a suitable range and flat frequency response may be used to monitor the generator output. Some audio generators are equipped with a calibrated output attenuator; others are not. Separate variable and step attenuators are available. For that matter, fixed attenuators are easily constructed from ordinary resistors.

A harmonic-distortion meter is essentially an audio output meter (VTVM) with a variable-frequency high-Q trap in its input circuit. To measure harmonic distortion, a pure sine wave is fed into the amplifier under test. The analyzer is connected to the output, and the trap is tuned to the frequency of the input signal. If there is no distortion, the trap completely rejects all of the signal and the meter reads zero. Naturally, if the amplifier under test generates any harmonics or spurious frequencies such as hum or noise, these pass through the trap to the meter.

Most harmonic-distortion meters also may be used as AC VTVM's. Depending on the particular make and model, the VTVM may have full-scale ranges from .01 volt to 300 volts. Thus, it may be used for noise and output measurements.

For reasons which are beyond the scope of this article, the intermodulation-distortion characteristics of an amplifier are of greater importance than the harmonic-distortion characteristics. However, equipment for measuring intermodulation (IM) distortion was not available at a moderate price until fairly recently. This equipment is now available separately or as part of a packaged stereo test set designed for the complete servicing of stereo receivers and amplifiers.

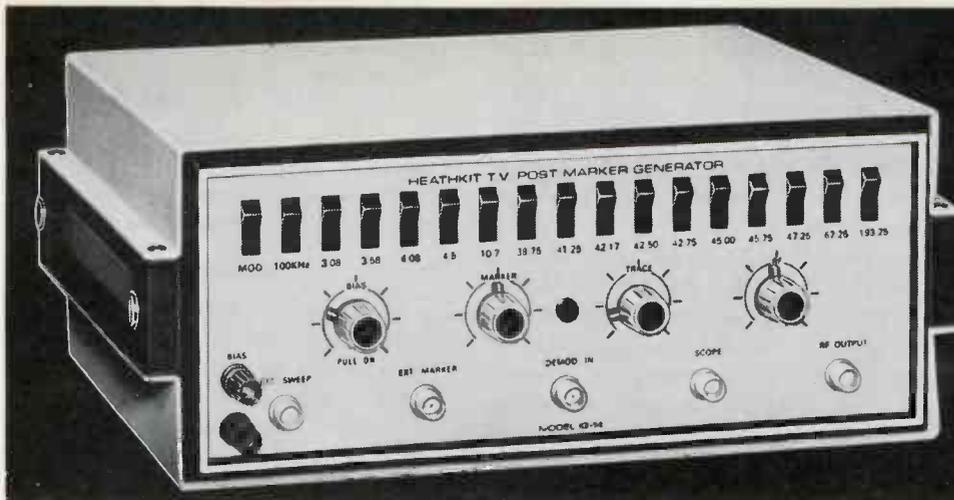The usual method of measuring IM distortion is to feed two signals of



**new**  
**HEATHKIT®**  
**solid-state**  
**crystal-controlled**  
**POST-MARKER**  
**GENERATOR**  
**only \$99.95**

**the most important instrument you can own for Color TV and FM alignment now costs a lot less...the Heathkit IG-14**

- 15 crystal-controlled marker frequencies • Switch-select picture and sound IF frequencies, color bandpass and trap frequencies, 6 dB points, plus FM IF center frequency and 100 kHz points • Use up to six markers simultaneously for faster TV alignment • Birdie-type markers • Trace and Marker amplifiers and size controls • 400 Hz modulator • Variable bias supply • All solid-state, 22 transistors, 4 diodes • Circuit boards

**Fast, Accurate Color Alignment.** Speed and accuracy are important in today's service work . . . important to your customers, important to your profits. Speed and accuracy are what the new Heathkit IG-14 gives you . . . plus features usually costing five to ten times as much.

**Just Push A Button.** That's all it takes to set a frequency . . . no dial to twiddle, no searching, no resetting problems. Fifteen switch selected crystal-controlled markers. Nothing could be easier or more accurate. The IG-14 has input and output connections so that it can be used with any sweep generator and scope. Also an external marker input. BNC connectors are used throughout.

**No Trace Distortion.** One of the big values to using a post marker generator like the IG-14 is that markers are injected after the sweep signal passes through the set being tested, thereby eliminating the 'scope trace distortion usually found when injection or absorption type marker generators are used.

**Crystal-Controlled Markers For Any TV Alignment Task.** Four marker frequencies are provided for setting color bandpass, one marker for TV sound, eight at the IF frequencies between 39.75 and 47.25 MHz, and markers for channel 4 and channel 10 picture and sound carriers for checking tuner RF response. With the ability to use up to six markers at once, such as picture and color carriers at 6 dB points, corner marker and trap frequencies, alignment is fast and precise. Trap alignment is just a matter of selecting the appropriate trap frequency, applying the 400 Hz modulation, and tuning the trap for minimum audio on a scope or meter.

**Easy FM IF and Discriminator Alignment.** The IG-14 provides *visible* markers at the 10.7 MHz center frequency plus 100 kHz markers on each side . . . visible because they are applied to the trace after detection and so are not attenuated by the discriminator. Use of harmonics, fully explained in the manual, provide tracking markers as well.

**Trace and Marker Amplitude Controls . . .** on the front panel permit using a regular service type 'scope instead of a wide-band, ultra-sensitive model . . . and stage by stage alignment is easier.


**Variable Bias Supply . . .** 0 to 15 VDC @ 10 milliamps is isolated from chassis so you can use positive or negative bias.

**New Look . . . Circuit Board Construction.** Handsome low profile, "stackable" cabinets in the new look of Heath instruments . . . finished in beige and black. Easy-to-build layout with two circuit boards.


**Save Hundreds of Dollars.** Until now, an instrument with these features cost much more. Order the IG-14 now . . . it's the best investment in alignment facilities you can make.

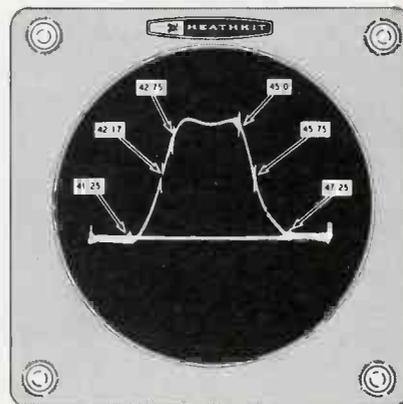**Kit IG-14, 8 lbs., no money dn., \$10 mo. . . . . \$99.95**

**IG-14 SPECIFICATIONS**—Crystal Marker Frequencies: 3.08, 3.58, 4.08, 4.5, and 10.7 MHz @ .01%; 39.750, 41.250, 42.170, 42.500, 42.750, 45.000, 45.750, 47.250, 67.250, and 193.250 MHz @ .005%. FM Bandwidth Marker: 100 kHz. Modulation: 400 Hz. Input Impedance: External sweep, 75 ohm; External marker, 75 ohm; Demodulation input, 220K ohm. Output Impedance: RF output, 75 ohm; Scope output, 22K ohm. Bias Output Voltage: Variable from 0 to 15 VDC @ 10 MA. Isolated from chassis for either negative or positive bias. Type of Marker: "Birdie." Controls: Bias voltage with AC on/off; Trace size; Marker amplitude; RF output; Modulation on/off; Markers, individual switches for each frequency. Semiconductors: Transistors: (16) 2N3692; (6) 2N3395; (3) Silicon diodes; (1) Zener diode, 13.6-V. Power requirements: 105-125 volts, 50/60 Hz AC @ 7.5 watts. Net weight: 8 lbs.



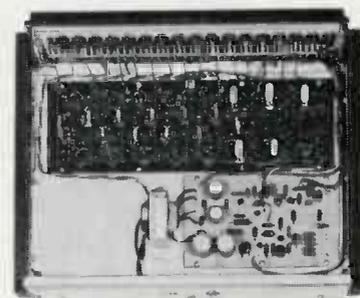**SIX MARKERS SIMULTANEOUSLY.** The scope trace above shows how six markers can appear at the same time. Note the trap markers, 6 dB points, and picture and sound carriers . . . all on one trace with the IG-14.



**EASY TO BUILD.** Note how everything except the front panel switches and controls mount on two circuit boards . . . even the crystals.



**FREE 1968 CATALOG!**  
 Now with more kits, more color. Fully describes these along with over 300 kits for stereo/hi-fi, color TV, electronic organs, electric guitar & amplifier, amateur radio, marine, educational, CB, home & hobby. Mail coupon or write Heath Company, Benton Harbor, Michigan 49022.

**HEATH COMPANY, Dept. 25-3**  
 Benton Harbor, Michigan 49022

Enclosed is \$ \_\_\_\_\_ plus shipping costs.  
 Please send \_\_\_\_\_ Heathkit IG-14 Post Marker Generator(s).  
 (quantity)

Please send FREE Heathkit Catalog.

Name \_\_\_\_\_  
 Address \_\_\_\_\_  
 City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Prices & specifications subject to change without notice. TE-174

different frequencies into the amplifier under test and then measure any intermodulation products which are developed in the amplifier. Using the SMPTE methods of measurement, a signal between 40 Hz and 100 Hz (F1) and a second signal between 1 kHz and 12 kHz (F2) with one-fourth (-12 dB) of the amplitude of the low-frequency signal are fed into the amplifier. The output of a perfect amplifier would consist of F1 and F2, and nothing else. Outputs having frequencies of (F2 - F1), (F2 + F1), (2F2 ± F1), (F2 ± 2F1), . . . . (F2 ± 5F1) are intermodulation products. The IM-distortion meter filters out the desired frequencies with a series of filters and measures only the intermodulation products which remain.

The lack of stereo separation is not usually a problem in stereo power amplifiers; however, separation may be measured by feeding a signal into one channel and comparing the outputs of the two channels. This requires a signal generator and an output meter, the same instruments required for measuring frequency response.

Many audio servicemen prefer to use a square-wave generator, rather than a sine-wave generator, for observing the performance of an audio amplifier. While quantitative measurements of distortion and response are difficult or impossible using a square-wave signal, an experienced observer can estimate the performance of an amplifier quite accurately by observing the appearance of its square-wave output. For example, if the output square wave has a sloping leading edge, the high-frequency response is poor. If the flat top of the waveform sags at the trailing end, the low-frequency response is poor. Overshoot and ringing are indications of peaks in the response curve, excessive distortion, or instability.

The square-wave generator and scope are also valuable in isolating faults to a particular stage. It is difficult to inject a signal into an amplifier at any point except the input while still maintaining a good impedance match, and a mismatch at the point of injection will, in itself, introduce distortion. Thus, signal-tracing techniques, rather than injection tracing, are required for finding sources of distortion and incorrect response. Unfortunately, output met-

ers and distortion meters usually require low-impedance, high-level inputs. However, a scope may be used at any point in the circuit, and, by using it in conjunction with a square-wave generator connected to the amplifier input, the faulty stage may be quickly isolated.

Several audio-signal generators on the market today will produce either square waves or sine waves at the flick of a switch. This is especially convenient since it makes both waveforms available without changing connections. A word of caution: If you are operating the amplifier "full bore" with a sine-wave input, switching to the square-wave input may seriously overload the output transistors if the peak-to-peak amplitude of the input signal remains the same or increases.

### Tuners and Decoders

Since most modern FM stereo tuners also contain the multiplex decoder, the test equipment required for each of these is included under one heading. For servicing the tuner, two signal generators are necessary. One generator must be tunable across the FM broadcast band (88 to 108 MHz) and is used to align the RF stages of the tuner. Since the RF bandpass of an FM receiver is not usually critical, servicing of the front end rarely requires the use of a sweep generator; however, the IF section of the tuner does require sweep alignment. This requires a sweep generator with a center frequency of 10.7 MHz and a 10.7-MHz marker, in addition to a scope.

Several stereo testers currently on the market generate the above-mentioned signals and also the composite stereo modulation. Generally, the RF carrier which they generate may be tuned only slightly above or below 100 MHz by a screw-driver adjustment. This carrier is frequency modulated by a choice of a monaural tone, a pilot subcarrier with tone modulation, unmodulated pilot subcarrier, 67-kHz or 72-kHz subcarriers for adjusting SCA traps, and external modulation. Some of these instruments generate separate left and right signals simultaneously, others generate "left only" or "right only" signals. Still other instruments have additional features such as a VTVM, impedance bridge, square wave-generator, IM-distortion tester, etc.

Again, depending on the complexity of the particular test set, all of the modulating signals may be available separately. At least one tester on the market performs all the functions of a miniature FM stereo transmitter, requiring only a stereo tape deck or turntable to modulate it.

### Summary

In the limited space available, we have attempted to enumerate the types of test equipment required for servicing stereo receivers, amplifiers, turntables, and tape decks. The selection of specific instruments can be made only by the shop owner. Personal preferences will affect each individual's choice, and, of course, the cost of the various instruments is an important consideration. For example, prices of audio signal generators range from less than \$100 to nearly \$1000.

Until the advent of stereo FM broadcasting and the rising popularity of high-quality stereo, there was little or no market for "middle-grade" audio test equipment. "Lab-quality" equipment was available—at a price—but equipment having reasonably good accuracy and stability at a moderate cost just was not available. (Of course, the all-in-one stereo test set has appeared only since the inauguration of FM stereocasting in June, 1961.)


Today, however, the situation is rapidly changing. A wide selection of audio signal generators, distortion analyzers, and all-in-one test instruments designed for service work is available at reasonable prices. In selecting your stereo test equipment, we suggest that you proceed along these lines:

1. Take inventory of your test equipment and determine which of the tests we have mentioned you can perform with the equipment you already have.

2. Estimate the amount of additional service you can sell by augmenting your present equipment.

3. Study the specifications, features, and prices of the various instruments that will satisfy your needs. Remember that your stereo service business will grow as you establish a reputation and promote this new service.

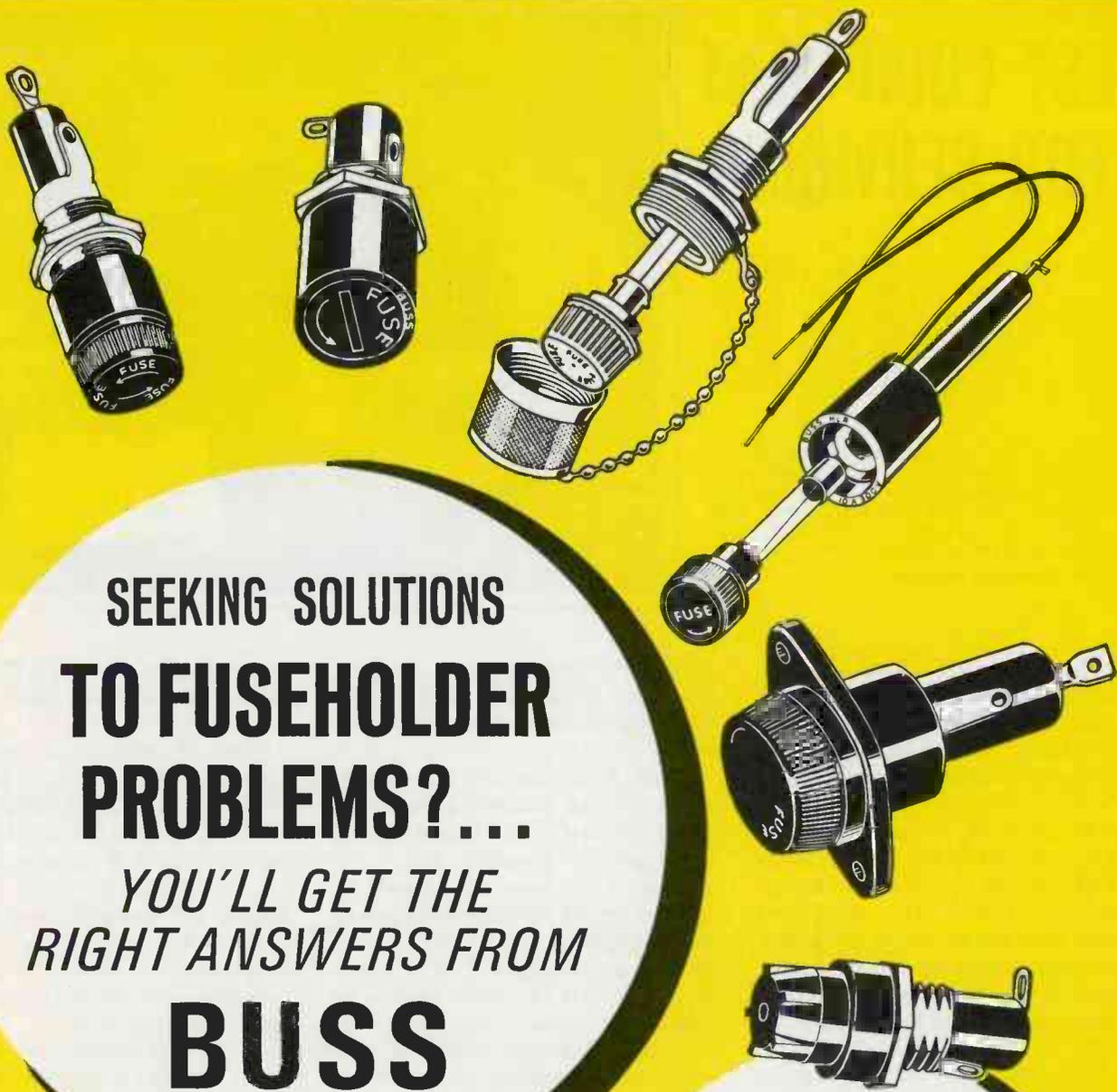4. Buy your new test equipment, repaint *your* board, and cash in on the growing market of stereo service. ▲



SEEKING SOLUTIONS  
**TO FUSEHOLDER  
 PROBLEMS?...**  
*YOU'LL GET THE  
 RIGHT ANSWERS FROM*  
**BUSS**


Panel mounted, in-the-line, lamp indicating, signal activating, visual indicating fuseholders—with solder terminals, quick-connect terminals or special terminals—for fuses from  $\frac{1}{4}$  x  $\frac{5}{8}$  inches and larger.

Fuseholders of various types to meet Commercial and Military specifications.

For full information on the many small dimension fuse mountings and companion fuses available from BUSS... write for BUSS Bulletin SFB.

BUSSMANN MFG. DIVISION, McGraw-Edison Co., St. Louis, Mo. 63107

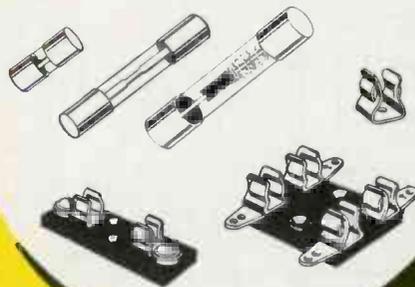**BUSS:** Makers of the complete line of fuses, blocks and holders of unquestioned high quality.



Supplied the Economical Way—  
 thru Distributors

**BUSS QUALITY**

# TEST EQUIPMENT FOR SERVICING

# CB

Although the test equipment requirements for servicing a particular type of electronic equipment usually overlap those for another type, most require a few items of specialized gear. Such special test equipment is needed for proper servicing of Citizens-Band equipment.

by William E. Daupert



When the old 11-meter amateur band was reassigned to the Citizens Radio Service, the American public immediately took advantage of it. The earliest equipment for this service was neither plentiful nor fancy, but now both the manufacturers and users have greatly increased in number and just about any kind of equipment is available. This equipment ranges from simple two- or three-tube superregenerative receivers to single-sideband, suppressed-carrier equipment, and at a price to fit any pocket book.

There are four classes of Citizens Band Stations. Class A stations are

licensed to operate on an assigned frequency in the 460 to 470-MHz band with an input power of 60 watts or less.

Class B stations are licensed to operate on an authorized frequency in the 460 to 470-MHz band with an input power of 5 watts or less.

Class C stations are licensed to operate on an authorized frequency in the 29.96 to 27.23-MHz band or on the frequency of 27.255 MHz, for the control of remote objects or devices by radio, or for the remote actuation of devices which are used solely as a means of attracting attention, or on an authorized fre-

quency in the 72 to 76-MHz band for the control of model aircraft only.

Class D stations are licensed to operate on an authorized frequency in the 26.96 to 27.23-MHz band or on the frequency 27.255 MHz with input power of 5 watts or less, and for radiotelephony only. Class D stations are authorized to use amplitude voice modulation including single sideband and/or reduced or suppressed carrier for radiotelephone communications only.

Power measurements must be made during maximum peaks of modulation, and with meters having

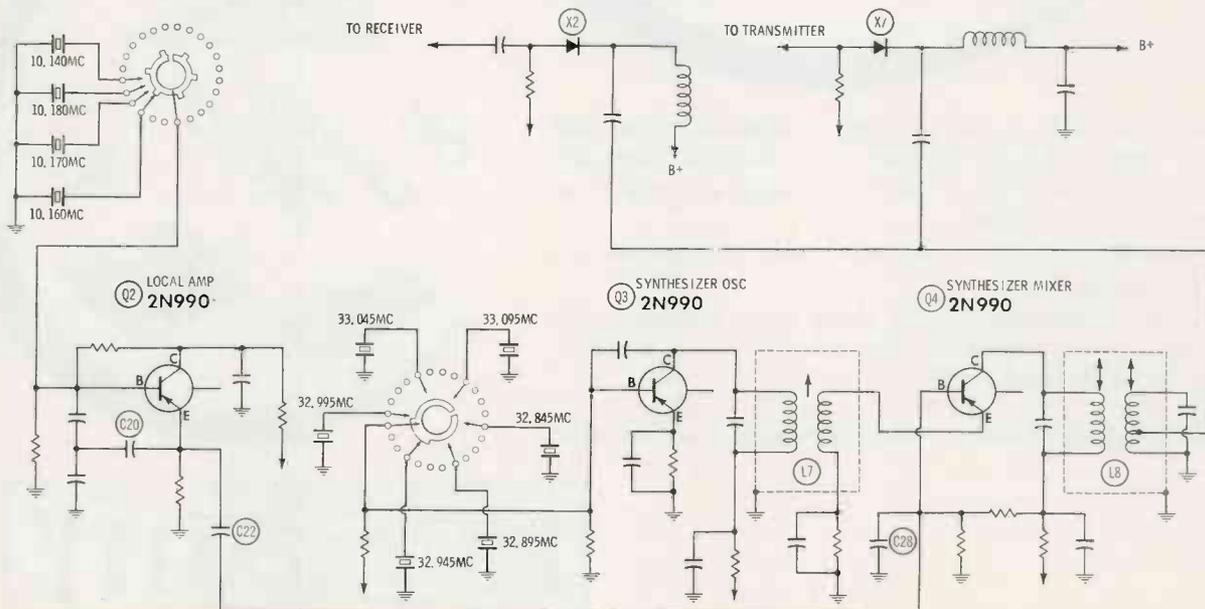


Fig. 1. Schematic of typical synthesizer stages.



Fig. 2. Lectrotech CB analyzer.

full scale accuracy of 2% or better. The frequency of the Class D transmitter must be maintained within  $\pm .005\%$ .

### Equipment Features

Among the latest auxiliary features of the Citizens Band equipment are built-in standing-wave-ratio bridges, output meters, and S-meters. Lately there have also been tremendous improvements in the main equipment; more receivers are using dual conversion, crystal filters, and mechanical filters, and transmitters are using compression amplifiers in the speech section. Ring modulators are popular in sideband equipment.

One of the latest additions to Citizens Band equipment is the frequency synthesizer circuit which maintains the transmitter and receiver on the same frequency at all times. Fig. 1 is a diagram of a typical frequency synthesizer circuit.

The synthesizer section consists of a low-frequency local oscillator (Q2) and its 4 crystals, the high-frequency oscillator (Q3) with its crystals, and the mixer (Q4). As shown in Fig. 1, the synthesizer is set for operation on Channel 11. Here's how it operates:

The 10.160-MHz crystal is connected directly into the base of Q2, a Colpitts oscillator. C22 and C28 form a capacitive voltage divider for the output. The high-frequency oscillator Q3 operates on third overtone crystals, in this case a 32.895-MHz crystal. The signal from Q3's collector is fed into L7 and thence to the emitter of the synthesizer mixer, Q4. At Q4, the low frequency signal, 10.160 MHz, is fed to the base and subtracted from the high frequency signal of 32.895 MHz. The resulting frequency is 22.735

MHz. The 22.735-MHz signal is coupled through L8 to switching diodes X1 and X2.

In receive position X1 is cut off and X2 couples the synthesizer mixer signal to the emitter of the receiver mixer transistor. The receiver IF amplifiers are tuned to 4.3 MHz (channel 11 minus 22.735 MHz). During transmit, X2 is cut off and X1 will conduct the signal from the synthesizer mixer to the transmitter mixer emitter. The transmitter oscillator, which always operates at 4.3 MHz, will add to the synthesizer mixer frequency and become the channel frequency.

### Available Test Equipment

For bench service of Citizens and Business Band radio equipment, different types of test instruments are needed depending upon the band class of the radio equipment. Since most modern Citizens Band equipment is completely transistorized, care should be taken in the selection of test equipment.

The DC power supply on the service bench does not need to be very heavy for most class D Citizens Band equipment, since most of these rigs draw from 100 ma to about 1 amp in the transmit position. However, for Business Band equipment you will need a considerably heavier power supply. These transmitters run up to 60 watts input and draw from 10 to 30 amps. The rip-

ple content should be less than 2% with good regulation.

The DC bench supply should be metered for voltage as well as current, as voltage is often a determining factor in locating a trouble quickly. The meter accuracy should be at least  $\pm 4\%$  or better. The supply voltage should be variable at least in two ranges. The smaller supplies, suitable for Citizens Band radios, run from 0 to 6 volts in one range and 0 to 20 volts in the second range. The larger DC supplies used in Business Band and other services usually run from 0 to 15 volts and 0 to 35 volts DC at about 30 amps.

In most cases it is beneficial to have a variable DC supply, since you can check the vibrator in vibrator power supplies to see whether it will start, and at what voltage. In the case of small DC supplies with poor regulation, try putting a small value resistor across the output terminals. A resistor of 20 to 30 ohms with 20 watts capacity will often help regulation problems.

There are several types of frequency meters available to meet FCC requirements. Available types range from comparatively inexpensive heterodyne meters to lab-type counters with digital display. Buy the most accurate you can afford.

Fig. 2 shows one of the newest instruments for CB servicing. This instrument is a combination frequency, power output, and modulation meter. Note that the frequency measurement is read by setting the

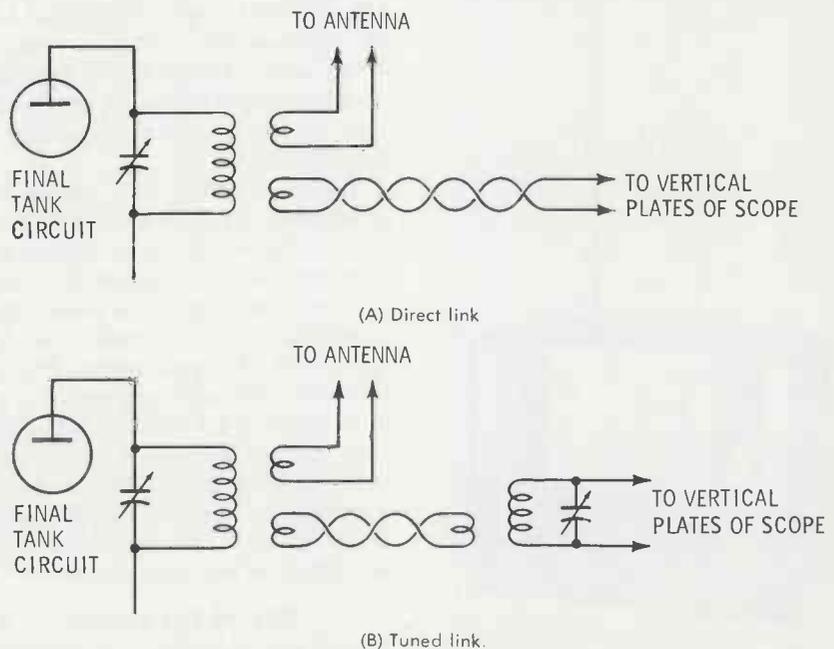


Fig. 3. Connecting scope for modulation envelope.

channel selector to the desired channel, and then reading the error in Hz on the meter. This instrument's frequency accuracy is .0015%, which is fine for CB work.

A good oscilloscope or output analyzer is helpful in checking modulation and/or percentage of modulation with A2 or A3 emission. Fig. 3 shows two methods of checking the modulation of a Citizens Band rig with an oscilloscope.

The circuit in Fig. 3A is a convenient way in which to couple the transmitter output to an oscilloscope. However, if you do not have enough deflection on the vertical plates of the scope, the circuit in Fig. 3B will increase deflection. The tuned circuit in Fig. 3B should be tuned to the output frequency of the transmitter, and the height of the scope pattern increased or decreased by adjusting the coupling of the line to the final tank coil.

A somewhat simpler way of checking approximate modulation percentage is with a transceiver tester such as that in Fig. 4. This instrument also checks a number of things including VSWR of the antenna. Most of these transceiver testers are limited to instruments of 5 watts output or less; but they are relatively inexpensive. Many features are available in these testers, so it is best to compare specifications before purchase.

The instrument in Fig. 5 is designed for VSWR and power mea-



Fig. 4. B&K Cobra transceiver tester.

surements alone. However, it can handle transmitters up to 1 kw output, which makes it useful for testing all classes of Citizens and Business Band operations.

A well-equipped service shop should not be without a good VTVM or FET meter. Low range volt and ohm scales are essential, as transistor circuitry is common. Meters are now available with scales as low as .01 volt and up to 1000 volts DC, and ohms scales which read from .1 ohm to 50 megohms. Some of these meters are battery operated, which is very handy in servicing of units in the car. An AC VTVM is a good addition to any service shop, for alignment of ordinary home radio equipment as well as Citizens and Business Band equipment. Most AC VTVMs have ranges from .001 volt to 300 volts AC and a dB scale from -72 dB to +50 dB—which is very helpful in measuring the stage gain of a receiver.

A good in-circuit transistor tester should be considered standard equipment in any modern communications shop. Most of these instruments are completely trustworthy; if the meter says "good," then the transistor can be eliminated as a possible trouble source. These instruments are also useful for checking power rectifiers and signal diodes.

Another must in servicing Citizens Business Band radios is a good signal generator for aligning RF and IF circuits. The generator should have a dial calibrated with an accuracy of 1% or better, and a modulated output continuously variable down to about .1  $\mu$ V. Quite a few of the latest transistor receivers can be overloaded with a strong signal, resulting in misalignment.

When selecting and using test equipment, attention should be given to such characteristics as impedance, insertion loss, attenuation etc. Also, it should be noted that these characteristics will vary with the frequency of the equipment. For instance, a wattmeter may read 5 watts at 27 MHz and 3 watts at 150 MHz, even though the power input is the same in both cases. The manufacturer usually furnishes specification charts to show the frequency characteristics of his equipment.

#### Use of Equipment

The first check for trouble in a unit should be visual. Look to see if



Fig. 5. Seco antenna tester.

there are any burned components, and check for cracked or blistered resistors. The circuit board should be carefully checked for cracks or breaks. Sometimes in a mobile installation there is a tendency for parts to vibrate out of their sockets.

The frequency meter is very useful in troubleshooting, especially when checking synthesizers and local oscillators. Care should be taken not to couple too much signal from an oscillator into the frequency meter. Never key the transmitter directly into the frequency meter as serious damage could result.

Power consumption checks should be made while the unit is on the bench, in both receive and transmit modes. Excessive input current could indicate leaky filters or transistors. The radio will operate more or less normally, but will soon cause trouble.

When any parts have been replaced that might affect the operating frequency of the equipment, such as any part that will affect the input of the transmitter or modulator, the frequency and the modulation percentage should be checked. Also, the input power to the final stage should be checked to see that it does not exceed legal limits.

#### Conclusion

The use of good test equipment will ease troubleshooting in most Business or Citizens Band radio equipment, and will do a more efficient job of putting the equipment back on the air. Time will be saved by the serviceman who is using the best equipment. Customers will be satisfied and the customer's equipment can be kept within the legal limits as set forth by the Federal Communications Commission. ▲



# SERVICE YOUR OWN MULTIMETER

Don't shove that defective VOM, VTVM, or transistorized multimeter into a corner to collect dust while you ponder whether it's worth the effort and expense involved in sending it away for repair. If the meter movement isn't damaged, you can repair any multimeter yourself.

by Ellsworth Ladyman

Effective and profitable repair of electronic devices can be accomplished only by using the proper test equipment. The successful service shop displays an imposing array of test instruments designed to perform specific tests to isolate defective components in electronic gear. This array of test equipment represents a considerable monetary investment, and as such, should be carefully maintained. Careful maintenance and repair of test equipment can add greatly to the efficiency of the average service organization. Rare is the shop that doesn't have a defective VOM, VTVM, scope, or generator lying around. Although it may not be completely defective, in many cases only the people well ac-

quainted with its peculiarities can operate it.


Test instruments that probably rank highest on the casualty list are meters, VOM's and VTVM's. This is primarily due to the rough handling they get on the bench and the many rides they get in the service truck. Also, it is not too uncommon for a technician who is absorbed in a particularly difficult servicing problem to unknowingly attempt to measure B boost with the function switch in "ohms" position. Regardless of what causes the failure, the instrument must be returned to service as soon as possible.

## Servicing VOM's


The first step in the repair of a

meter is to decide whether it is repairable in the shop or whether it must be returned to the factory. This usually is not a difficult decision; if the meter movement is damaged, it should be returned to the factory; if not, the instrument in all probability can be repaired in the shop. Referring to Fig. 1 (an illustration of two types of meter movements) will quickly point up the folly of attempting repair of the meter movement itself.

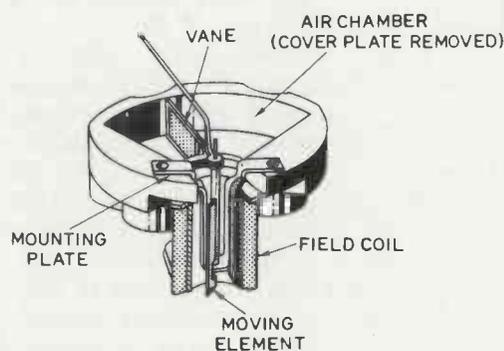After deciding to repair the instrument yourself, remove it from the case, being careful to prevent scarring or scratching the clear plastic or glass covering the meter face. The rear cover or back of the case is usually secured by four retaining




(A) Moving iron vane

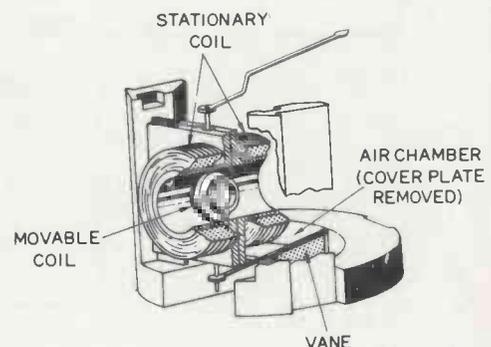

(B) Dynamometer

Fig. 1. Drawings of two basic types of meter movements illustrate intricate parts.

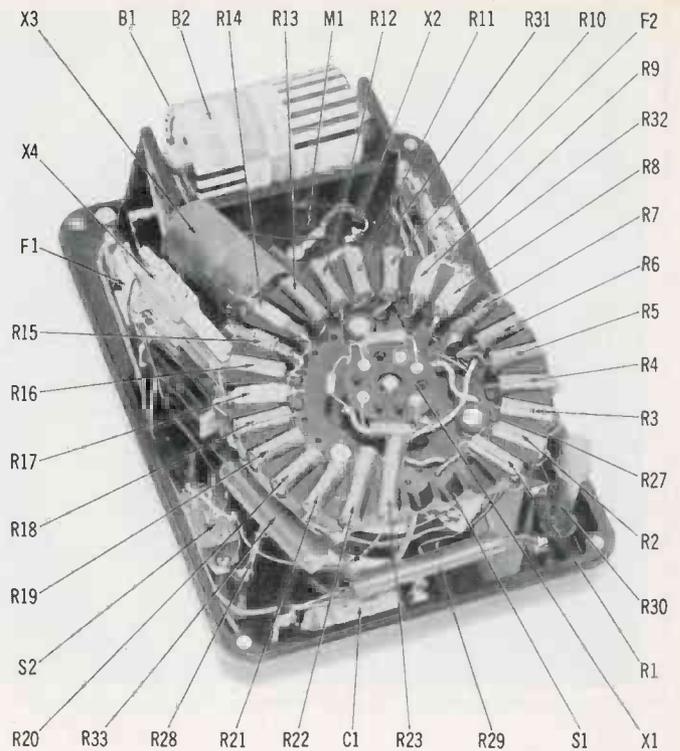

(A) Meter includes resistance, DC, AC, and dB scales.

(B) Component layout reflects compact size.

Fig 2. Front-cabinet and internal views of typical volt-ohm-milliammeter.

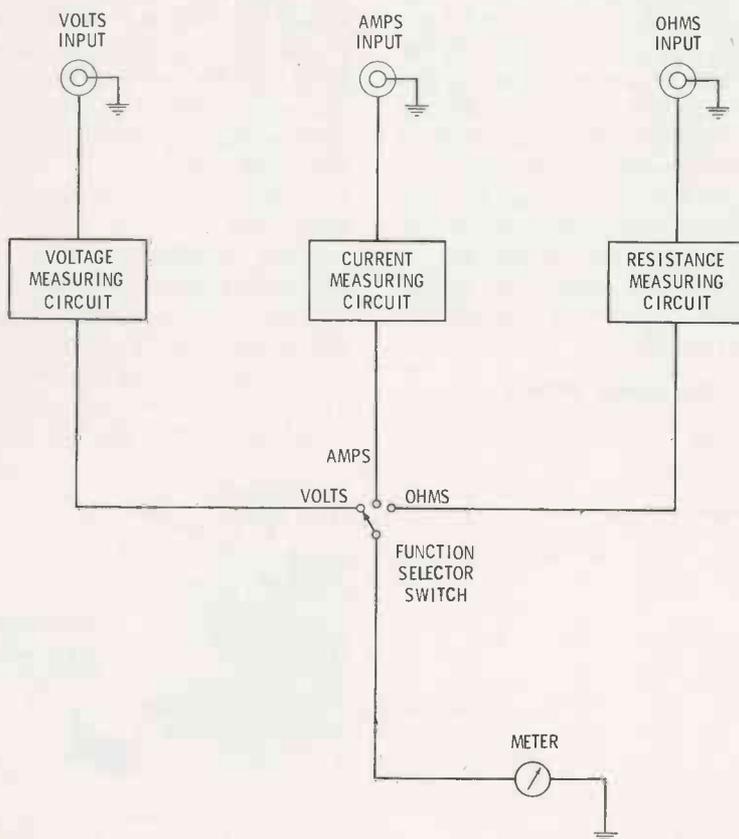


Fig. 3. Block diagram of VOM emphasizes isolation between functions.

screws. These screws are sometimes recessed and not visible until four rubber fet are removed.

When removal from the case is completed, make a careful visual inspection of all components; look specifically for evidence of overheated parts, defective contacts, etc. At first glance, the layout of the components will appear to be a complicated conglomeration of parts (Fig. 2), but an analysis of the trouble symptom(s) will, in most cases, automatically eliminate a major portion of the components from further consideration as the probable cause. The block diagram in Fig. 3 bears this out. If the meter readings are erratic during resistance measurements, the voltage and current measuring circuits can be eliminated as possible trouble suspects; conversely, if the voltage readings are inconsistent, the resistance and current measuring circuits can be eliminated. In the same manner, the resistance and voltage circuits are eliminated when erroneous readings prevail only during current measurements.

Further localization of the defect results when the erroneous readings are confined to a particular scale

(this is usually the case). At this point, reference to the manufacturer's schematic of the instrument under test should localize the defective component to a particular leg of the circuit; for instance, if erroneous readings are present only on the  $R \times 100K$  range, the defect has to be in that particular circuit—i.e., the switch contact(s) or resistors related to that particular setting of the function switch. This will hold true for any scale. An analysis of the schematic shown in Fig. 4 will illustrate this fact.

#### Meter Sensitivity

Most VOM's used for servicing electronic apparatus have a sensitivity of 20,000 ohms-per-volts. This is about the maximum sensitivity available in ruggedly constructed VOM's—and they have to be rugged to stand the pounding they get in the course of duty. Most 20,000 ohms-per-volt instruments utilize a 50-microampere meter with an internal resistance of 20,000 ohms. Of course, due to excessive circuit loading, even the best VOM's leave something to be desired when grid voltages are to be measured.

#### Meter Shunts

Occasionally, it may be necessary to compute the value of a shunt and/or multiplier resistor; the value of a resistor might be unreadable, making identification impossible, and the schematics for the VOM or VTVM under repair may not be available

#### Ammeter Shunt

The formula for determining the value of an ammeter shunt is:

$$R_S = \frac{I_M \times R_M}{I_S}$$

where,

$R_S$  is the resistance of the shunt resistor

$I_M$  is the full-scale current rating of the meter

$R_M$  is the meter resistance

$I_S$  is the current that will flow through the shunt at full scale.

The current flow through the shunt ( $I_S$ ) is the difference between the meter current (usually 50 microamperes) and the current to be measured; for example, to calculate the shunt resistance requirements for a 100-microampere scale using a 50-microampere meter:

# RATCHET-TYPE CHIMNEY MOUNT

## With Stainless Steel Strapping



Catalog No. 8008  
Suggested Net \$4.28  
(12' lengths)

Catalog No. 8008-L  
Suggested Net \$5.10  
(18' lengths)

New in design... tops in materials... first in service life. Here is the quality-constructed two-bracket chimney mount designed to give maximum service in high wind, seasonal storms, adverse weather conditions. Available with 12 or 18-foot lengths of stainless steel strapping to fit any chimney, a locking "U" bolt that accepts antenna masts up to 1½" in diameter. This mount installs in minutes, requires only a single wrench to secure to chimney. Buy with confidence from the world's largest basic manufacturer of television hardware... you'll make your job easier, faster, and more profitable... more satisfying to your customer.

Always insist on **GC**...  
you'll get more for your money, everytime!



### GC ELECTRONICS

A DIVISION OF HYDROMETALS, INC.  
MAIN PLANT: ROCKFORD, ILL. U.S.A.



#### Giant FREE Catalog...

Only GC gives you everything in electronics... has for almost 40 years. Match every part and service need from over 10,000 quality items. Write for your copy today!

Circle 17 on literature card

# GC

has  
everything  
in  
**TELEVISION  
HARDWARE**





list made up in Step 1, used in conjunction with the schematic, should help you pinpoint the trouble area.

3. Check out the suspected circuit leg using another VOM. Remember, most resistors used as shunts, multipliers, etc., have at least 1% tolerance, and sometimes less.

#### Calibration

Due to the variation in circuitry from manufacturer to manufacturer, a detailed calibration procedure that would apply to all instruments is impossible. In general, an instrument can be checked in several different ways:

1. Its performance can be checked against that of another instrument of its type. The meter being used as a standard must have a known performance rating.
2. The ohmmeter portion can be quickly checked by measuring resistors of known value; a decade box is useful for this purpose.
3. The voltage portion can be checked by measuring various outputs of a variable power supply, battery outputs, etc.
4. The ammeter portion can be evaluated in the same manner as the voltage portion except, of course, current is used in place of voltage.

Do not overlook the possibility of trouble external to the meter. Most meter failures occur when probes, test leads, adapters, etc., become worn. A loose test lead can give such a wide range of indications that it will be almost impossible to evaluate a meter's performance. Always suspect leads and probes first, then the meter itself.

#### Servicing VTVM's

The VTVM utilizes the same basic operating theory associated with the VOM; that is, current flowing through a meter movement produces deflection of the pointer. The major difference between the two instrument types is that at least one vacuum tube circuit is employed in the VTVM (Fig. 6). The use of the vacuum tube(s) gives the VTVM several advantages over the VOM, but as is true in nearly all phases of electronic design, "when you gain something, you lose something"; so, there are also disadvantages.

## The Transistor Testers that really work in circuit



TR139

NEW TR15A

Locate defective transistors in circuit in seconds with a true AC signal gain test (BETA) . . . without disconnecting a single lead . . . what a time saver. Also measure AC beta and  $I_{cbo}$  leakage out of circuit for complete analysis of the transistor. It's easy, fast and accurate. Also checks diodes and rectifiers in and out of circuit.

**TRUE BETA MEASUREMENTS:** the transistor's AC gain factor. Set the CAL knob, press the beta test button and read the actual AC gain on the meter. This is the ratio of AC signal on the base of the transistor to that obtained on the collector and is a standard of measurement in the industry.

**$I_{cbo}$  LEAKAGE MEASUREMENTS.** An important check since many transistors have good beta but don't work because the leakage current has become too high. Both instruments show the leakage current ( $I_{cbo}$ ) in microamps right on the meter.

**OUT-OF-CIRCUIT TESTS.** Test procedure is the same for in or out-of-circuit testing. Out of circuit, transistors may be sorted, selected and matched for specified values of beta and  $I_{cbo}$ .


**COMPLETE PROTECTION.** Special circuitry protects even the most delicate transistors and diodes, even if the leads are connected incorrectly. No possibility of damage to the transistor, circuit or instrument. Zener regulated power supply.

**NO SET-UP BOOK.** No need for a set-up book or manual. Just refer to the handy transistor checking guide on the back of the instrument. Even unknown transistors can be checked. PNP and NPN types can be determined at the flick of a switch.

**ALL STEEL CASE.** Vinyl covered, with brushed chrome panel. Beta range, 2 to infinity;  $I_{cbo}$ , 0 to 5000 microamps.

**DELUXE TR139.** "Howard W. Sams" transistor manual included for beta and  $I_{cbo}$  reference. 9" x 7½" x 6", with large 6" meter, 8 lbs. ----- **\$89<sup>50</sup>**

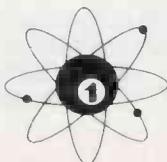**COMPACT TR15A.** Only 5" x 7-3/16" x 3-1/16"—just right for easy handling. Easy-to-read 4½" meter. 4½ lbs. ----- **\$64<sup>50</sup>**



# SENCORE

NO. 1 MANUFACTURER OF ELECTRONIC MAINTENANCE EQUIPMENT

426 SOUTH WESTGATE DRIVE, ADDISON, ILLINOIS 60101

Circle 18 on literature card

March, 1968 / PF REPORTER 33

#### VTVM Advantages

1. A much higher input impedance. This is due to the inherently high input impedance of the vacuum-tube grid circuit. This higher input impedance results in greatly reduced circuit loading, and increases the use of the meter.
2. Another inherent feature of the vacuum tube circuit is the low input capacitance. This allows measurement of AC voltages at much higher frequencies than the VOM.

3. The amplification of the input signal by the vacuum tube amplifier increases the sensitivity of the meter, allowing measurement of much smaller voltages and greatly extending the range of resistance measurement.

#### VTVM Disadvantages

1. More frequent calibration required (compared to VOM) due to aging of vacuum tube.
2. The very nature of a vacuum tube circuit is indicative of less stable operation.

3. An external power source (usually 110 VAC, 60 cycle) is required.
4. The VTVM must reach operating temperature and correct voltages before stable operation is possible.
5. The circuit is somewhat more trouble prone than the VOM because of the more complex circuitry.

#### VTVM Maintenance and Repair

Since specific circuits are used for specific measurements, the overall circuit can be broken down into sections to facilitate troubleshooting procedures:

1. DC voltage measurement circuit.
2. AC voltage measurement circuit.
3. Ohms or resistance measurement circuits.
4. Power supply.

A careful analysis of the trouble symptom(s) permits quicker isolation of the circuit defect to a particular stage. The circuits associated with one function are fairly well isolated from those of another; for instance:

1. Amplifier circuit—DC (negative and positive) voltage readings.
2. Rectifier stage—AC voltage measurements.
3. Battery and multiplier resistors—Resistance Measurements.
4. Power supply—Both AC and DC voltage measurements.
5. Probe—All measurements.
6. Function selector switch—All measurements.
7. Range selector switch—All measurements.

#### Tube Failure

As in any electronic apparatus, the amplifier or rectifier tubes can and do fail. This condition is immediately discernible and can be evidenced by any of the following indications:

1. No response whatever.
2. Response only on AC readings.
3. Response only on DC reading.
4. Erroneous or erratic readings on AC and DC measurements.
5. Readings lower than expected.
6. Will not balance, or inability to perform calibration procedures.

Following replacement of defective tubes in a VTVM, the instrument must be recalibrated. Calibration should be carried out in accordance with the manufacturer's instructions.

# Knuckle-Saver.



Putting a sleeve on a connection can be frustrating. (If your hand slips, it can also be rough on the knuckles.)

Why not use Krylon Crystal Clear Spray Coating instead?

Krylon forms a hard, waterproof coating that stops many of the causes of high-voltage section loss and picture

fading. It doesn't dry out or crack. It prevents rusting.

Try it. All you have to lose are a few skinned knuckles.

*Krylon Crystal Clear...standard equipment for all TV/Radio installation and repair work.*



Circle 19 on literature card

It will be necessary to "age" replacement tubes before installation. This is necessary due to changes in tube characteristics during their first 100 hours of operation. One method of "aging" is accomplished by installing the tubes in the VTVM, turning the VTVM on and applying operating voltage to the tubes for approximately 100 hours before calibrating.

#### Component Replacement

Tolerance is the main factor to be considered when replacing a component in a VTVM, or any meter

circuit. Replacement parts must be within the tolerance stated in the manufacturers information. Extreme care should be exercised during the replacement operation. Avoid overheating terminals, excessive solder on joints and unnecessary heating of adjacent components.

The battery employed in the ohm-meter circuit (B1, Fig. 6) should never be allowed to reach a badly discharged condition, nor should a discharged battery be allowed to remain in the case. To check the level of charge, proceed as follows:

1. Set the function selector to "ohms."
2. Turn the range selector to "RX1" position.
3. Rotate the ohms-adjust control to attain full-scale deflection.
4. Short the probe and ground leads together.
5. Remove the short between probe and ground leads.
6. The meter should read full-scale; if not, the batteries are probably weak.

#### External Troubles

When troubleshooting any device, the most logical trouble source is usually the part that is handled the most; consequently, the probes and ground leads of the VTVM require special attention. Frequent inspection of probes and leads can save time and prevent the frustration of erroneous meter indications.

#### Servicing Transistor VOM's

Electronic meters utilizing transistors rather than vacuum tubes are able to combine most of the advantages of the VOM and the VTVM. Such meters have an extremely high


## Important New SAMS BOOKS

THE BOOK YOU NEED
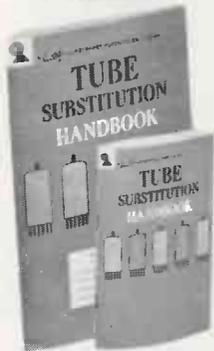
### NEW 11th Edition of the famous HOWARD W. SAMS Tube Substitution Handbook

TWIN PAK: 2 Books in 1 Package!

Regular size for your bench  
Pocket-size for your tube caddy



Completely revised, each book contains identical up-to-date listings of over 10,000 direct substitutes for all types of American and foreign receiving and picture tubes. The most complete and updated direct tube substitution guide available. Includes cross reference for all American receiving tubes, list of picture tubes and substitutions, cross reference for miniature tubes, industrial substitutions for receiving tubes, substitutions for communications and special-purpose tubes, cross reference for American and foreign tubes. Instructions tell you when and how to make proper substitutions. You get two books, each with exactly the same information—the full-sized book for your bench or reference library, the pocket-size for your tube caddy. \$2.25  
Order 20615, both books for only . . . . . \$2.25  
Shop edition only (5 1/2 x 8 1/2", 96 pages). Order 20614, only . . . . . \$1.75

#### ABC's of Ham Radio. 3rd Ed.

by Howard S. Pyle, W7OE. Newly revised to contain all the information you need to get your novice-class amateur license. Covers all the latest FCC regulations, including the new incentive licensing program. Explains how to apply for a license and what to expect in the FCC exam. Shows you how to learn the code, and how to set up your station and operate it; provides a world of helpful hints to get you into ham radio in the shortest time. \$2.50  
144 pages; 5 1/2 x 8 1/2". Order 20638, only . . . . . \$2.50

#### Understanding Electronic Test Equip.

by Joseph A. Risse. Explains the operating principles, functions, and applications of the test equipment most commonly used in electronic testing and troubleshooting. Clear, in-depth explanations help you to better understand and make more effective use of test instruments; also shows you how to repair and even calibrate them. Includes data on the latest solid-state instruments. Fully illustrated with schematics, drawings, and photographs. \$4.25  
192 pages; 5 1/2 x 8 1/2". Order 20613, only . . . . . \$4.25

#### 101 Easy Audio Projects

by Robert M. Brown and Tom Kneitel. Includes complete instructions for building 101 simple, low-cost audio projects using parts salvaged from discarded radio and television receivers. Projects include a-m and f-m tuners, reverb units, eavesdropping amplifiers, time-delay control boxes, hearing aids, and test equipment. Many can be completed in just one evening. Construction is enjoyable, and at the same time you will also learn the basics of electronics. \$3.25  
168 pages; 5 1/2 x 8 1/2". Order 20608, only . . . . . \$3.25

#### ABC's of Transformers and Coils. 2nd Ed.

by Edward J. Bukstein. Because transformers and coils are a part of almost all electronic equipment, you must know how they work in order to understand how circuits operate. This book explains the basic principles of inductance, transformer and coil construction, inductor applications, and how to test and measure inductance components. Includes computer developments (magnetic-core memory and logic circuits, and toroidal and ferrite-bead inductors). 96 pages; 5 1/2 x 8 1/2". Order 20612, only . . . . . \$2.25

These and over 300 other SAMS Books are available from your local Electronics Parts Distributor.

COMING NEXT MONTH

49 EASY TRANSISTOR PROJECTS  
SERVICING DIGITAL DEVICES  
101 QUESTIONS & ANSWERS ABOUT COLOR TV




HOWARD W. SAMS & CO., INC.

4300 W. 62nd St., Indianapolis, Ind. 46268

Circle 20 on literature card

## ELIMINATE CALL-BACKS

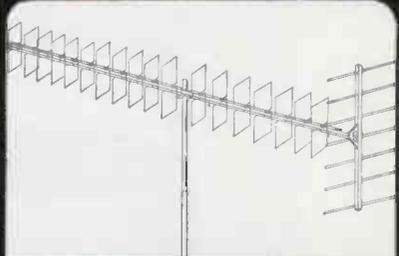

### Revolutionary MODEL UPW UHF PASSIVE WAVE ANTENNA

This system in which there are no electrical connections,  
**PROVIDES HIGH GAIN ACROSS THE ENTIRE UHF BAND**  
and eliminates noise caused by loose elements at high frequencies. High overall gain across the entire UHF band makes this antenna more desirable than any frequency conscious yagi types being marketed today. Excellent color reception assured. More gain than a Parabolic. Top quality construction.

*Write for literature and low retail prices. All inquiries given prompt attention.*

## S & A ELECTRONICS INC.

Manufacturers of the TARGET ANTENNA  
West Florence Street • Toledo, Ohio 43605  
Phone 419-693-0528

Circle 21 on literature card

March, 1968 / PF REPORTER 35

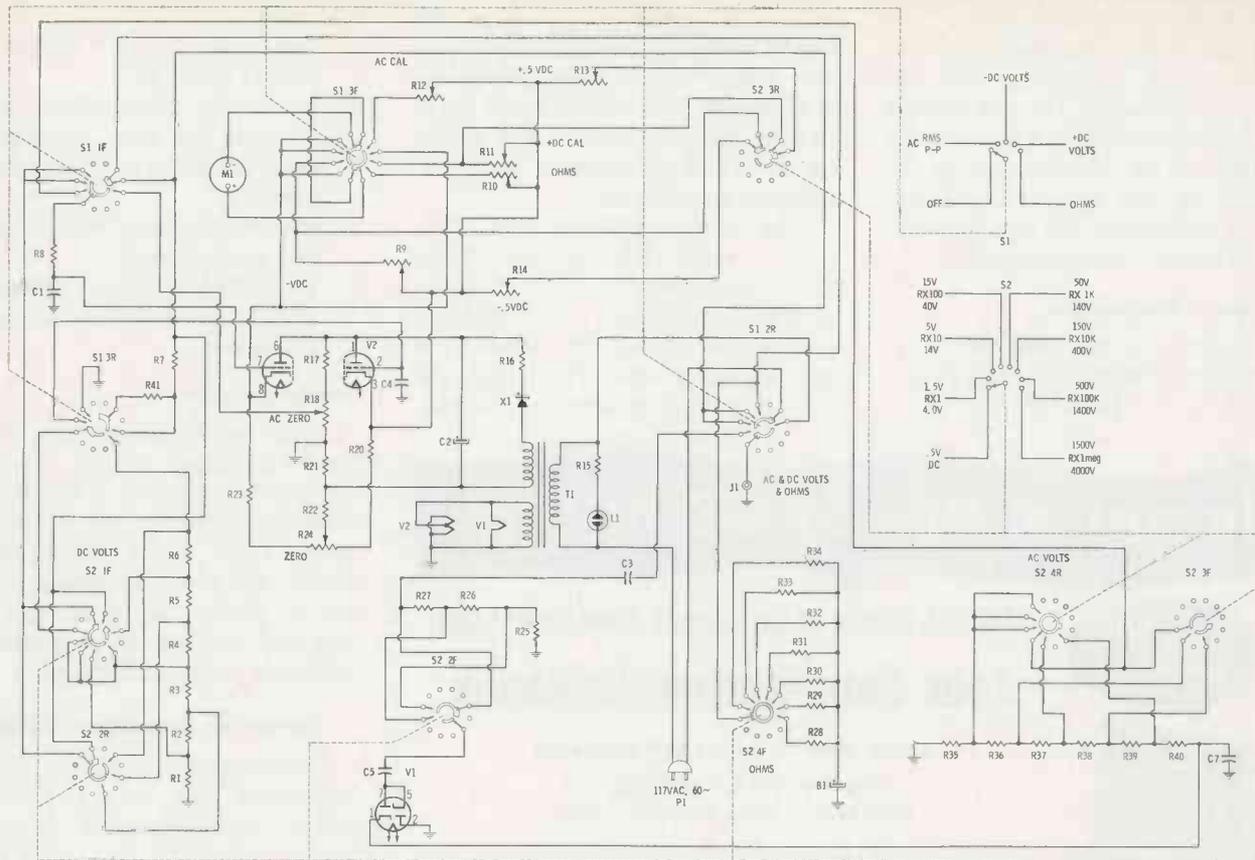


Fig. 6. Complete schematic diagram of vacuum-tube voltmeter.



Fig. 7. Multimeter employing field-effect transistors.

input resistance (10-22 Megohms), require no warm-up time, and are portable since no external power source is needed.

One such instrument (Fig. 7) employs field-effect transistors (FET) in the circuitry (Fig. 8). The operation of a field-effect transistor is very similar to that of a vacuum tube; one suitable (but over-simplified) description of it is: "a transistor that thinks it's a tube."

The FET and vacuum-tube circuits illustrated in Fig. 9 point up the similarities of the two configurations; terminology is about the only significant difference. Bias is obtained for the FET circuit in the same manner used in the vacuum tube (current flowing through the bias resistor develops a voltage across it). The operation of these two devices is so similar that like terms can be applied when describing their operation: The gate (grid) controls the current flow between the source (cathode) and the drain (plate) by regulating or governing the effect of the existing electrostatic field between the gate (grid) and the source (cathode). However, there are differences: The FET

doesn't have a "treated" cathode that becomes depleted of electrons, and the circuit is far more stable and resistant to operational changes than the vacuum tube circuit.

#### FET Meter Circuit Analysis

Transistors Q1 and Q2 (Fig. 8) make up the differential amplifier required for use in DC voltage and ohmmeter measurements. When there is no voltage applied to the input of Q1, the zero adjust control is adjusted so that the voltages developed across source resistors R14 and R22 are equal in amplitude; consequently, no current will flow through the meter. The DC balance control (R29) works the same as the zero adjust control; however, it is an internal adjustment and is used to compensate for internal component tolerances. When a DC voltage is applied to the input circuit of Q1, the balance existing between Q1 and Q2 is upset, current flows through the meter, and the pointer indicates the value of the applied voltage. Input divider resistors R1 through R8 permit a total of seven AC and DC ranges. Capacitors C2 through C8 compensate the divider resistors for the different AC ranges. The DC calibrate control functions as the name implies: It calibrates the meter for accuracy when a known value of DC voltage is applied. If a voltage higher than the limit indicated by the range selector switch is applied to the input of Q1, the neon bulb (NE2) will light (fire) and hold the voltage applied to Q1 at a safe level, protecting Q1 from damage.

Resistance measurements are accomplished by a voltage divider consisting of a known and unknown value of resistance; the value of the voltage developed across the unknown resistance is translated to resistance on a meter scale calibrated in ohms.

With the value of the unknown resistance at "zero" (leads shorted together), the ohms-adjust control (R23) is adjusted so that the pointer deflects full-scale when the full potential from B1 is applied to Q1; as increasing amounts of resistance are applied between the leads, the pointer deflects less due to smaller amounts of current applied to the meter.

With the function selector set for AC measurements, the AC voltage

is applied to a divider resistor (R2-R8), as was done for DC measurements. The output of transistor Q1 is then fed to a p-p detector made up of C10, C11, X1 and X2. This DC output is then applied to transistor Q2 through the divider network made up of R25, R26, R27, and CR6. The meter is located in the source circuit of transistor Q2. The DC voltage developed in the source circuit of Q2 (proportional to the p-p voltage applied to Q1) is fed to the meter. Diodes X5 and X6 are

for temperature compensation and make the meter independent of temperature changes occurring between 32° and 122°F.


DC current measurements utilize meter and shunt resistors R16 through R19. The transistors and their associated circuitry are not required during current measurements. The meter is rated at 100 microamperes; consequently, the meter is connected directly into the circuit when using the 100-microampere scale. To troubleshoot field-effect

# 50,000

users can't be wrong!

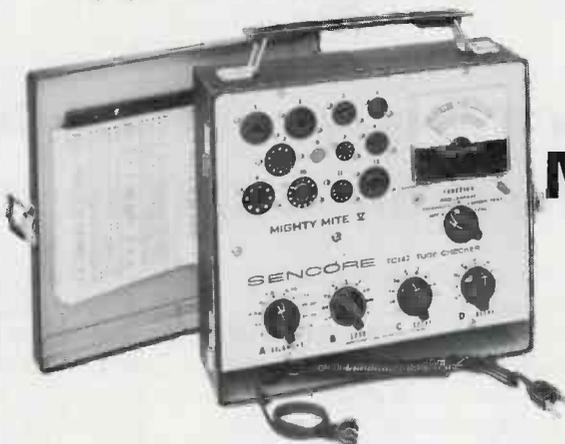**TECHNICIANS EVERYWHERE RELY ON FAMOUS SENCORE MIGHTY MITES. HERE'S WHY.**

- Grid Leakage Test with ultra-high sensitivity of 100 megohms
- Emission Test at full rated cathode current
- Shorts Test picks out interelement shorts of 180K ohms or less
- Mighty Mite accurately checks over 3,000 tubes, including foreign



**NEW  
MIGHTY  
MITE  
V  
TC142**

Now, Sencore's new Mighty Mite V gives you the same reliability and accuracy, plus new features that make the "V" the most up-to-date tester of all.

- NEW**—Magneval socket so you check many more tubes.
- NEW**—Horizontal in-line switch layout saves setup time.
- NEW**—Rugged vinyl-clad steel case stays new longer.
- NEW**—Brushed chrome panel; detachable cover.

The new TC142 is truly Sencore's mightiest  
Mighty Mite and it's only .....

**\$79.50**

**IN STOCK AT YOUR DISTRIBUTOR NOW.**



**SENCORE**

NO. 1 MANUFACTURER OF ELECTRONIC MAINTENANCE EQUIPMENT

426 SOUTH WESTGATE DRIVE, ADDISON, ILLINOIS 60101

Circle 22 on literature card

***Introducing the finest Color TV***

# New Zenith Super 50

***Designed better for easiest servicing!***  
***Handcrafted for unrivaled dependability!***

The new Zenith Super 50 Handcrafted chassis is in forty-three of Zenith's forty-six color TV models—including 20" and 23" (diag. picture) Zenith Color TV.

The new Super 50 chassis is designed for better performance and greater reliability. Installation in the home and adjustment of alignment is easier. And if the necessity for service ever arises, you'll find the Super 50 chassis has been specially planned in many ways for fast, easy and efficient servicing.

Circuitry is simplified, clutter has been eliminated. Heat critical components are isolated in the coolest area of the chassis, for longer life. Important servicing test points are clearly identified by chassis stampings or by "flags." All parts are more accessible. And all separated assemblies (tuner, convergence assembly, deflection yoke, speakers, etc.) have a "plug in" connection.

Now the best color TV chassis is made even better!


BEST YEAR YET



TO SELL THE BEST

**ZENITH**  
The quality goes in  
before the name goes on

# chassis ever!

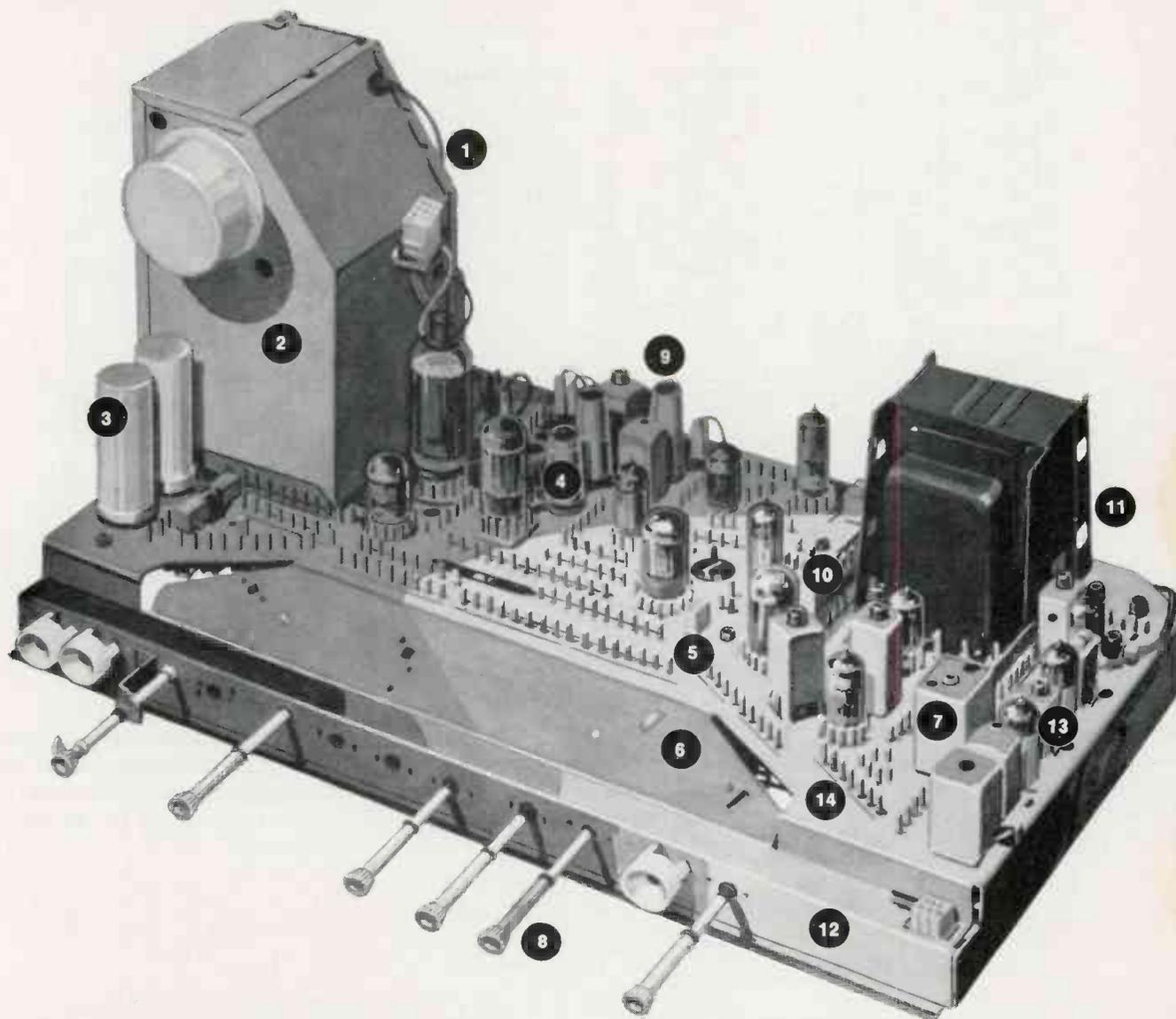

## 1. Exclusive Zenith High Voltage Regulator Circuitry

Zenith's regulator tube keeps a constant 25,000 volts of picture power while itself operating at 5,000 volts or less — one-fifth the operating voltage of a conventional shunt regulator tube when maintaining the same picture power.

## 2. High Voltage Sweep Transformer

Zenith's new sweep transformer is shielded within a metal cage. And it's sealed in polyester resin virtually impervious to moisture and protected against corona discharge.

## 3. Heat Critical Components Isolated

The electrolytics, relocated to the chassis's coolest corner, are isolated from heat producing components for longer life.

## 4. Automatic Color Level

Keeps colors constant—station to station, channel to channel. Helps compensate for variations in signal transmission.

## 5. Plug-In Assemblies

All assemblies not mounted on the rugged metal chassis have "plug-in" electrical connectors for easy removal without breaking soldered connections.

## 6. Automatic Degaussing Circuit

Automatically demagnetizes the color tube each time the set is turned on from a cold start.

## 7. Zenith AFC (Automatic Fine-tuning Control)

Electronically fine-tunes Zenith Color TV at the flick of a finger. Assures the sharpest color picture. Most of the 23" diagonal models are equipped with this feature.

## 8. Pull-Out Secondary Control Knobs

Now all secondary control knobs pull out one full inch for easier access and adjustment.

## 9. Advanced Color Demodulator Circuit

Zenith patented circuit extracts color from the incoming

signal and sends it to the picture-tube with peak precision for natural, life-like colors.

## 10. Solid-State Video Amplifier

This transistor amplifies the picture information and assures excellent highlight brightness and picture detail.

## 11. Fin-Cooled Power Transformer

With excellent heat-dissipating characteristics, it assures constant, full voltage.

## 12. Exclusive Horizontal Handcrafted Chassis

No printed circuits. No production shortcuts. Rugged 16-gauge steel base provides up to 200% greater heat conduction ability than phenolic material used in ordinary plastic printed boards.

## 13. 3 Stage I.F. Amplifier

All three stages—each with its own frame grid tube and interstage transformer—have been relocated to reduce possible interaction with other circuits for greater stability.

## 14. Metal Cone Check Points

Easy-to-read numbers and "flags" identify the metal cone check points, help to make diagnosis easy and accurate.

## NOT SHOWN ABOVE

### Easy Access Front Convergence

In most 20" and 23" (diag.) models simply remove the grille and speaker assembly for easy access to the entire convergence panel assembly, saving you time and trouble.

### Removable "Easy-Service" Plate

The bottom of the cabinet is cut out and covered with a perforated metal plate. Alignment tools may be inserted through slots in this plate. Or the plate can be removed for easy access to up to 90 per cent of the circuitry.

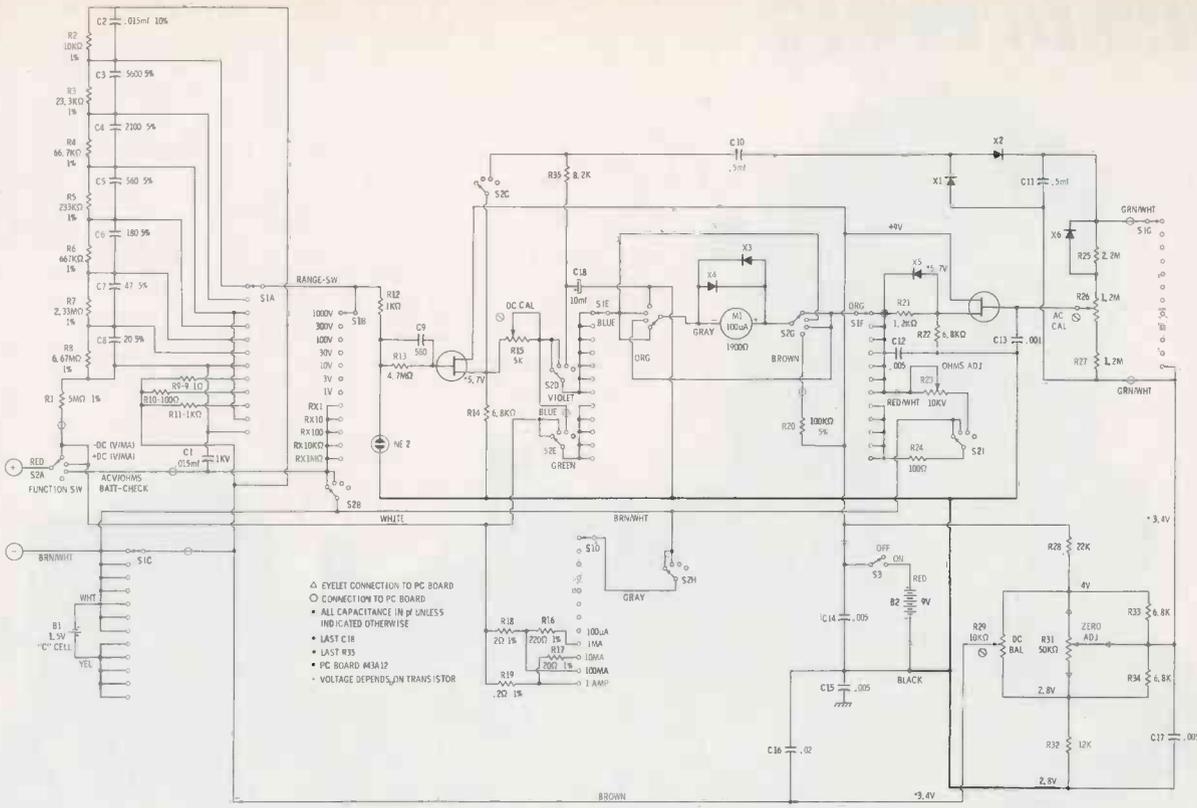


Fig. 8. Schematic diagram of multimeter employing FET's in place of vacuum tubes.

or conventional transistor volt-ohm-meters, use the same procedures that were outlined for VOM'S and VTVM's:

1. Carefully analyze the trouble

symptoms.

2. Be sure you are checking in the right circuit.
3. Make a careful visual inspection.

4. Check components carefully; make replacements only with components rated well within the tolerances stated by the manufacturer. ▲

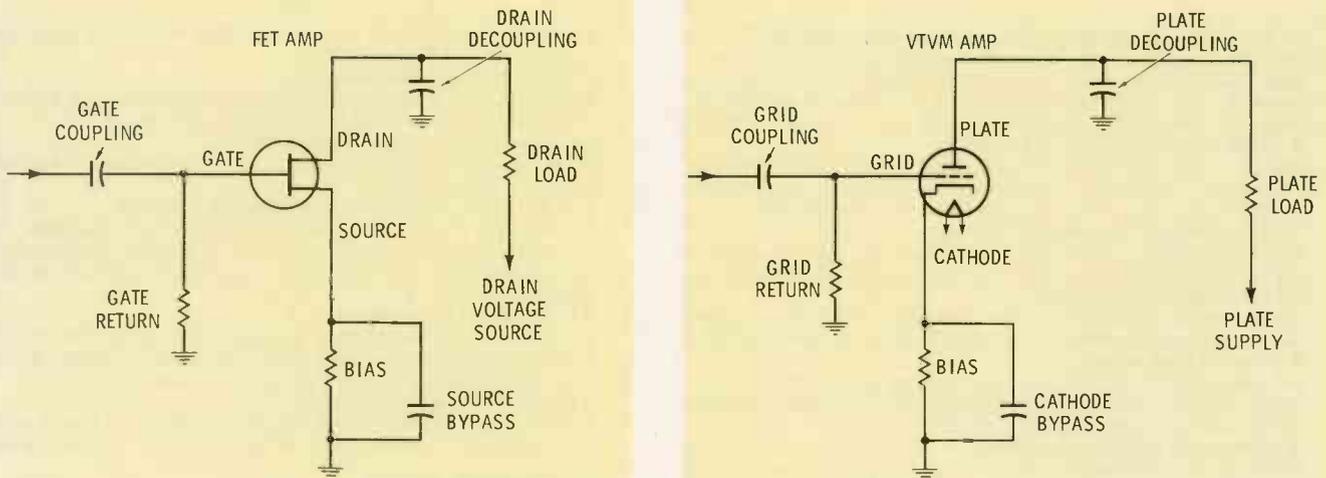


Fig. 9. Comparison of amplifiers employing field-effect transistor and vacuum tube.

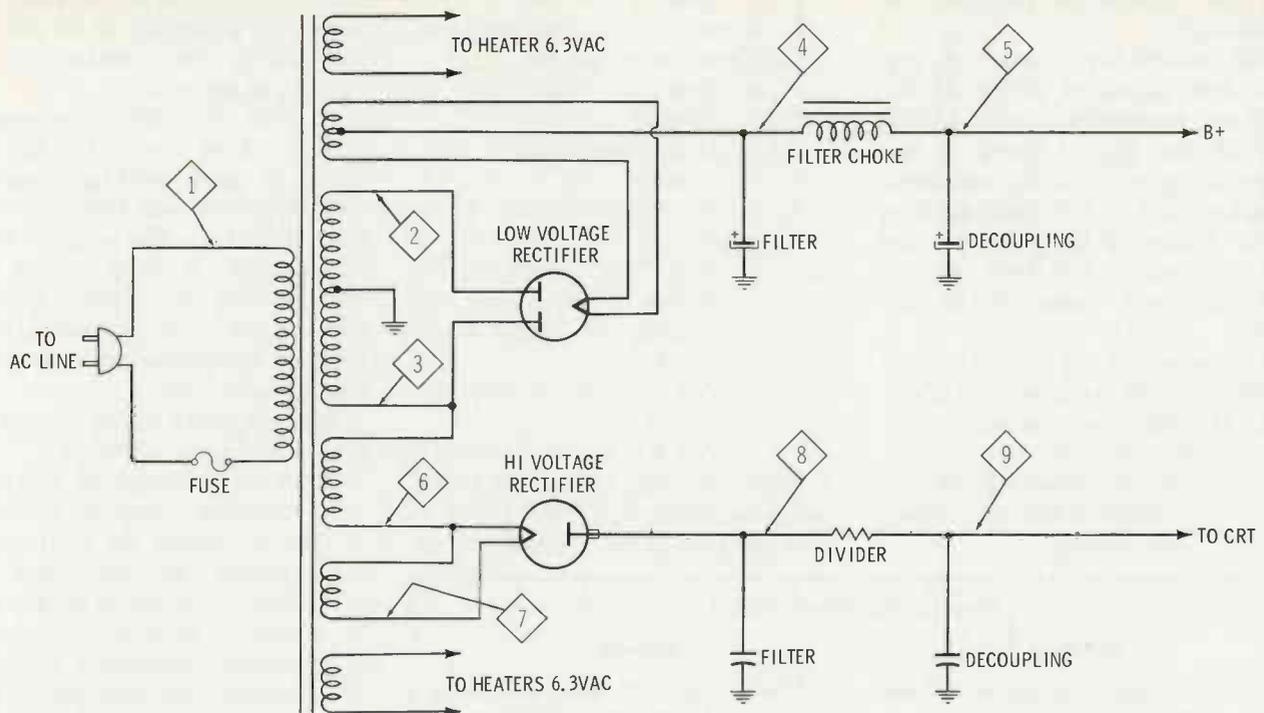


Fig. 5. Typical scope power supply.

## Fix That Scope

(Continued from page 19)

same. Two controls are normally provided for control of the horizontal sweep oscillator. One of these is usually a rotary switch and it will probably be termed "Coarse Frequency"; the other will be a potentiometer and in all probability will be named "Fine Frequency."

There must be some method of synchronizing the vertical input signal with the internal horizontal sweep oscillator. This is accomplished by picking off a portion of the vertical input and applying it to the horizontal sweep oscillator stage (Fig. 3). This signal (the portion picked off the vertical section) is used to trigger the horizontal sweep oscillator. When you adjust the horizontal controls to view the desired number of vertical pulses or cycles, you are locking the horizontal oscillator "ON" at a specific multiple or submultiple of the input vertical signal. Practically all scopes on the market today also provide facilities for application of an external horizontal sync signal.

Scope power supplies must be capable of providing both low voltages (in the order of 300 volts) and high voltages (ranging from 450 to 1200 volts). These power supplies can be incorporated into one

section, or they may be separated. Nothing goes wrong in a scope power supply that doesn't go wrong in a radio, television, amplifier, or any other power supply. Filters short or open up, bleeder and divider resistors change value, and transformers break down. These troubles are comparatively easy to isolate, and should cause you very little concern in troubleshooting. Fig. 5 shows a typical scope power supply.

The cathode ray tube (CRT) must be considered the heart of an oscilloscope. The size and type of the CRT to a large extent determines the power supply requirements. Operation of a CRT is as follows (Refer to Fig. 6):

1. The heater current is supplied by a winding of the power transformer.
2. As the heater warms up, the cathode is heated and starts emitting electrons.
3. Electrons emitted from the cathode are attracted by the nearest positive CRT element, which will be grid No. 2.
4. These electrons will pass through the aperture in grid No. 2 and continue through anodes No. 1 and No. 2.
5. Anodes No. 1 and No. 2 shape the electrons into a tight beam.

6. The deflection plates (vertical and horizontal) will then attract the electron beam, causing it to bend on its path to the phosphorous CRT coating in accordance with applied signal volts.
7. The electrons are then collected by the interior coating (internally connected to anode No. 2), and the circuit is completed.

## Servicing Procedure

As is the case in any servicing problem, the initial analysis of the trouble symptom is of utmost im-

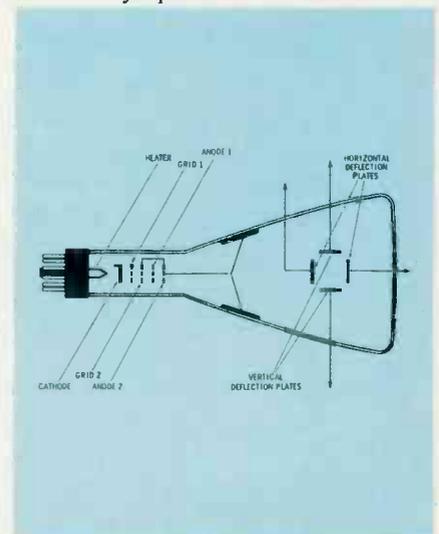


Fig. 6. Important elements of a CRT.

portance. The time spent learning how the instrument functions is never wasted.

The vertical input circuit, amplifiers, and deflection plates of the CRT are responsible for the amplitude of the signal. Sweep is the responsibility of the sweep oscillator, amplifier and horizontal-deflection plates. Failure of the power supply will, of course, affect both vertical and horizontal operation of the scope.

An analysis of the trouble should contain the following information:

1. If trouble is occurring in the vertical section:
  - a. Is it occurring on all ranges of the input selector switch?

- b. Is it intermittent or continuous in nature?
2. If the trouble affects the horizontal sweep circuits:
  - a. Does it occur on all ranges?
  - b. Is it intermittent or continuous?
3. If the trouble consists of no sweep:
  - a. Is a "dot" visible in the center of the screen, indicating no sweep whatever?
  - b. Are external connections okay?
  - c. Are B+ voltages normal?

Before actually attempting to repair your scope, it is a good idea to have answers to these questions. Be

sure you are not having trouble with external equipment. Probes and leads take a beating, so be sure you are making good connection to the equipment under test.

A little preventive maintenance can go a long way in keeping your scope in good working condition. One thing that will help immeasurably is to keep the controls of the scope clean. A dirty control (and if one is dirty, it is a pretty good bet they all are) can provide a multitude of symptoms such as erratic trace, bounce, etc.

A quick check of the controls can be accomplished as follows:

1. Turn the scope on, and adjust controls to provide horizontal trace across the CRT screen.
2. Adjust the horizontal gain control slowly in such a manner as to cause the trace to spread completely across the screen, then decrease the trace (adjust the control) to a minimum. The trace should move smoothly across the screen. Any jerky movement of the trace is indicative of a dirty horizontal control, or improperly operating horizontal section.
3. Apply a 60-Hz sine-wave signal to the vertical input terminal. Adjust the controls to provide a visual indication of the input voltage. Run the vertical input selector switch through its various positions, adjusting the vertical gain potentiometer to keep the trace (as much as possible) within the confines of the CRT screen; if it does not move smoothly, cleaning of both switch and control is in order.
4. Other controls (horizontal frequency, etc.) can be checked in the same manner by applying an appropriate, known signal to the inputs. Adjust controls for a normal visual indication. Any jerky or abnormal indication should be checked out.

NOTE: A properly operating piece of equipment should be left alone, but any deviation from normal operation should be checked out at once. A little cleaning here and there can prevent a lot of trouble and insure that the equipment is ready when you need it. ▲

### Troubleshooting Chart

#### Symptom

#### Remedy

- |   |   |
|---|---|
| <ol style="list-style-type: none"> <li>1. No trace, screen not illuminated, pilot light on.</li> </ol>  | <ol style="list-style-type: none"> <li>1. Check fuses. If fuse is blown, make all checks to eliminate possibility of direct short to ground. Never clip or jump across fuse terminals.</li> <li>2. Don't overlook the possibility of a bad tube.</li> <li>3. Make voltage and/or resistance checks from test points 1 through 9 to ground (Fig. 5).</li> </ol>  |
| <ol style="list-style-type: none"> <li>2. Trace moves from left to right across CRT screen, but no vertical sweep.</li> </ol>                 | <ol style="list-style-type: none"> <li>1. Check the probe.</li> <li>2. If another scope is available, monitor waveforms at test points 1 through 8 in Fig. 3. With a VTVM, check voltages at test points 1A through 6A.</li> <li>3. Be sure wafer contacts on vertical attenuator switch are clean and making good contact. Check compensation networks for value changes, although value changes in these circuits should show up as poor frequency response.</li> </ol>                               |
| <ol style="list-style-type: none"> <li>3. Vertical trace in center of screen, trace changes in amplitude, but no horizontal sweep.</li> </ol> | <ol style="list-style-type: none"> <li>1. Check waveforms at test points 1 thru 6, make voltage checks at test points 1A thru 8A (See Fig. 4).</li> <li>2. Check compensating networks at input circuit. Be sure input selector switch wafer contacts are clean and making good contact.</li> <li>3. If external horizontal sync is applied, check probe for good contact at circuit point under test and for good contact with scope connector. Probe ground straps are frequent offenders.</li> </ol> |

# VOLTS ARE WHERE THEY

# FIND YOU

He who understands electricity and its potential, usually respects it. However, familiarity does breed contempt, and most of us are guilty at one time or another.

by A. J. Dilles

You probably haven't done much service work if you haven't been "zapped" a few times. Maybe they were pretty mild or possibly they were the real teethgrating, body-quivering, quick-jerk-to-escape type—the kind that keep you honest for a long time. The sources are many and varied, ranging from 110 volts AC to B+ to Boost B+ to the snapping 25 kv in the color sets. Unpleasantly sometimes, volts are prone to turn up in some of the least expected places, which means that most of us, at one time or another, absently touch a wire or a component or a cabinet, and then—Zap!

Take one person I know, an experienced serviceman who really should have known better. He kept an AC/DC radio on the kitchen sink of his home, and the knob was missing from the tuning shaft. But Al was no fool. He simply moved the radio to the far end of the drainboard, nicely out of reach of the faucet, a perfect ground. We all know what a nuisance finding just the right knob can be and, after all, Al's was such an easy solution.

And so one night Al stood idly tuning the radio as his wife busily washed the dinner dishes. An affectionate mood came over him and, still holding the unprotected shaft, he stretched over toward his wife to kiss her. She in turn leaned responsively toward him, one hand resting on the faucet. Their lips met and—Zappo! Talk about kisses!

I recall a real jolt I once caught while repairing an antenna. Who would have stopped to consider the probability of a shorted capacitor in the receiver? I subsequently found out—the hard way—that the culprit was one of the two RF bypass tubulars that shunt each side of the AC input. The set played fine, but unfortunately for me, the chassis was now hot, and the AC, obeying

the laws of electricity, ran a devious, crazy path from the chassis through the balun, through the twin-lead, through the antenna and through me to the vent which I was touching. Needless to say, I now unplug the set before I climb on the roof.

This experience was, of course, with a transformer-equipped set. On series-string models, the manufacturer will generally isolate the antenna terminals from the tuner by inserting a small capacitor in series with each side. Whenever you have the back off such a set, it's a good idea not to bypass these capacitors by connecting the lead-in directly to the tuner. Remember that cable systems are almost always grounded, while a conventional antenna system may very well be. Thus, you could end up with a burned-out balun or—if you got between the lead-in and the chassis—a healthy jolt. If the tuner input lead must be removed, the problem can be solved very nicely by carrying in your tube caddy a short length of twin-lead with alligator clips at each end and an isolating capacitor in series with each side.


Along the same line, I once made a service call where the owner complained of having been shocked by the rabbit ears. Even after the set was unplugged, he refused to touch them. I noticed that a wall heater was mounted directly beside the set. A voltage check confirmed that 110 volts AC existed between it and the rabbit ears. Undoubtedly, the customer had touched them both simultaneously. A brief inspection and subsequent questioning disclosed that he had thriftily replaced a defective line cord himself, bypassing the interlock and soldering the ends directly under the chassis. He had allowed the sharp edge of the chassis to rest on the cord and, predictably, the metal had cut

through the insulation and made contact with one of the wires. It was the same story: A hot chassis with current flow through balun, lead-in, and antenna to the most convenient ground—in this case, the wall heater. The customer's person had acted as the switch that closed the circuit.

Other potential trouble spots are to be found in the metal cabinets that enclose the many transformerless portables and table models, including some color sets. Standard manufacturing procedures call for insulating the chassis from the cabinet by the use of nylon spacers. Here again the error factor sometimes occurs, and the two may contact each other. Thus, if the plug is not polarized, a potentially lethal situation exists. You can help avoid this possibility by not using screws that are too long and that might extend beyond the nylon and touch the chassis. Also, inspect for loose wires, misplaced ground braids or missing spacers. And finally, before you button it up, make an ohmmeter check between the cabinet and the chassis, flexing the cabinet as you do so.

Another, less serious, problem exists in residual voltages. Many a technician (not to mention customer) has felt a sharp jolt and rubbed a suddenly numb hand, suppressing what he would have said if the lady of the house had not been watching curiously. Capacitors will hold a charge—often a substantial one. Here the serviceman's best friend comes in handy—the common, ordinary, inexpensive clip lead. Before making any static checks, ground out the fuse holder and any exposed electrolytics. When changing high-voltage tubes, attach the clip to the high-voltage lead and leave it there till the tube has been substituted. Remember, even though the shock may only sting, it could cause you to tear open your hand as you jerk away.

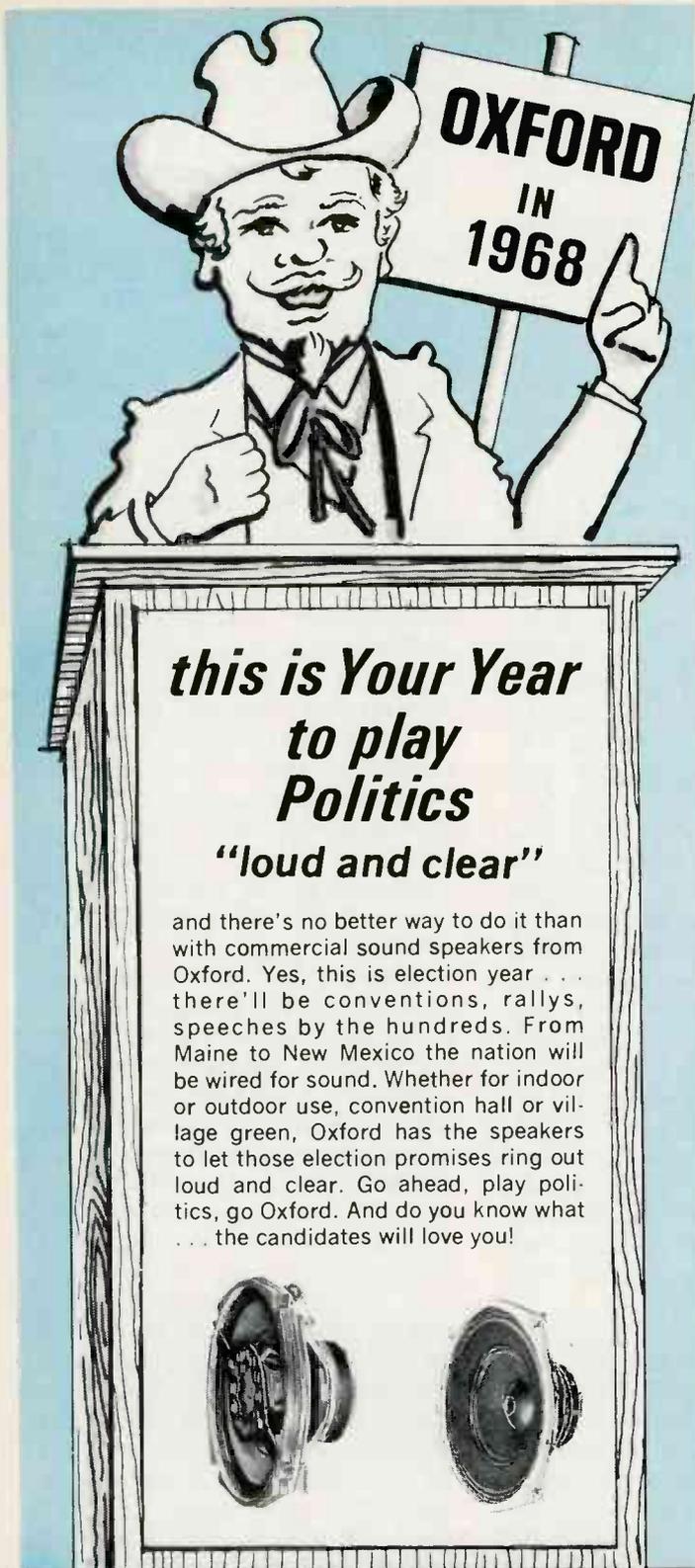
And so, the next time you troubleshoot a set, take that extra minute to be sure. If there's any question, use your meter to eliminate doubt. And be skeptical—don't take anything for granted. Don't just assume the set is unplugged. Think in terms of safety. Precautions pay off—especially when they become a habit. ▲




**this is Your Year  
to play  
Politics**

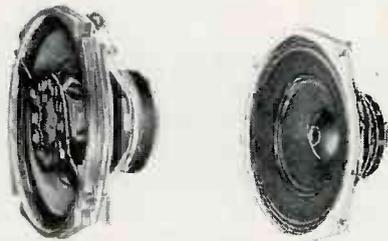**"loud and clear"**

and there's no better way to do it than with commercial sound speakers from Oxford. Yes, this is election year . . . there'll be conventions, rallies, speeches by the hundreds. From Maine to New Mexico the nation will be wired for sound. Whether for indoor or outdoor use, convention hall or village green, Oxford has the speakers to let those election promises ring out loud and clear. Go ahead, play politics, go Oxford. And do you know what . . . the candidates will love you!



**OXFORD TRANSDUCER COMPANY**

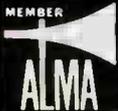

A Division of  
Oxford Electric Corporation  
3911 S. Michigan Avenue  
Chicago, Illinois 60653

Circle 24 on literature card

# PHOTOFACT<sup>TM</sup> BULLETIN

PHOTOFACT BULLETIN lists new PHOTOFACT coverage issued during the last month for new TV chassis. This is another way PF REPORTER brings you the very latest facts you need to keep fully informed between regular issues of PHOTOFACT Index Supplements issued in March, June, and September.

<b>Aiwa</b>	11T-05 .....	940-1
<b>Bradford</b>	CWGE-55301A, CWGE-59576A .....	938-1
<b>Coronado</b>	TV2-6611A, TV2-6612A, TV2-6810A .....	941-1
	TV2-6613A, TV2-6615A, TV2-6616A, TV2-6811A .....	939-1
	TV2-7112A .....	938-2
<b>Electrohome</b>	Chassis M4 .....	937-1
<b>Magnavox</b>	Chassis U/T916-01-AA .....	936-1
<b>Motorola</b>	Chassis 20TS-592, 22TS-592 .....	941-2
<b>Packard Bell</b>	CRQ-310, CRQ-312 .....	937-2
<b>Philco</b>	Chassis 18KT50, 18KT50B .....	940-2
<b>RCA Victor</b>	Chassis CTC28A, CTC28AA, CTC28B .....	936-2
<b>Sears Silvertone</b>	Chassis 528.70480/481/482 .....	939-2
<b>Shibaden</b>	TU12US .....	938-3
<b>Toshiba</b>	T2T, T2W (Ch. TAT-2002) .....	940-3
<b>Zenith</b>	Chassis 8Y4B36 .....	936-3
<b>Production Change Bulletins</b>		
<b>Admiral</b>	Chassis G308-3, G310-1/-2, G334-2, G344-1/-3, G346-1/-2/-3, G347-1/-3, G1255-4/-5, G1256-2, G1257-2, G1295-1 .....	941-3
	Chassis 20B6CB, 20B6TB, 20UB6CB, 20UB6TB, 25E6, 25F6, 25UE6 .....	937-3
<b>General Electric</b>	Chassis AA, AY, MW (19"), MW (23"), SA .....	937-3
	Chassis SY, TA .....	939-3
<b>Silvertone</b>	Chassis 456/528.61227/ 236/239 .....	939-3
<b>Zenith</b>	Chassis 29JC20, 29JC20Q .....	939-3

# NOTES ON TEST EQUIPMENT

*analysis of test instruments  
...operation...applications*

by T. T. Jones

## Transistor Tester

One of the most attractively styled instruments to be marketed in recent months is Jackson's Model 810 Dynamic Transistor Tester. It has a sloping edge on the front of the case, coupled with just the right touch of color present in the push-button switches. It's a real eye-catcher. Jackson is the first manufacturer we've noticed using the new Centralab switches, but the latter are so versatile that we expect to see more of them in the future.

Circuit-wise, the Model 810 uses an AC-beta test which is becoming somewhat of an industry standard. Fig. 2 is a simplified schematic of the beta test, with the tester set to read NPN transistors on the "HI" scale. The meter is reading collector

current. The internal resistance of the meter is 220 ohms, so the actual value of the collector load is about 22 ohms (R8 and the meter in parallel). Note that the base resistor is 220 ohms. The meter is set to fullscale by adjusting the power transformer primary voltage. The capacitors are in the circuit for bypassing and stability.

When the "Beta Test" switch is depressed, the meter and R7 are

transposed. The collector load remains the same since R7 and the meter have the same resistance. The base bias remains the same, for the same reasons, but now the meter is reading base current, and since the meter is no longer shunted, the sensitivity is 10 times greater. If the deflection of the meter is the same in both positions of the "Beta Test" switch, the transistor under test would have a beta of 10.

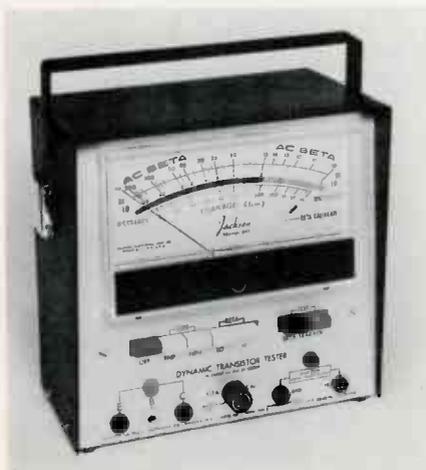


Fig. 1. Jackson Model 810 transistor analyst is eye-catcher.


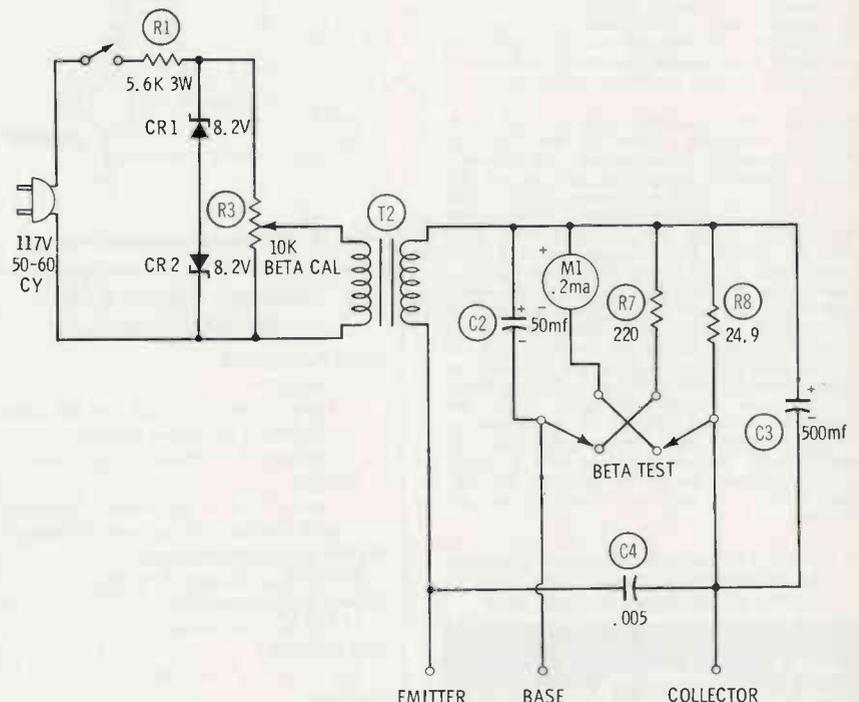


Fig. 2. Beta test NPN HI range.

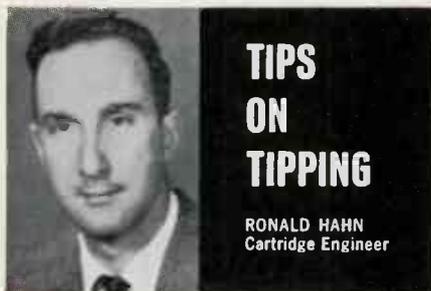One of a series of brief discussions  
by Electro-Voice engineers



There is no room in today's small, light, stereo ceramic cartridges for sloppy tolerances or poor assembly. And as the design trend continues toward even smaller models, the need for improved uniformity and tighter tolerances increases.

Of course, entirely new designs often will give the desired improvements in performance and uniformity. More often, however, the greatest progress can be seen in improvements of existing products by the application of new techniques and methods.

Such is the case with a popular 2-element plug-in stereo cartridge now being produced by Electro-Voice. Even with the highest standards of manufacture and assembly, it became clear that improvements were necessary to optimize performance and reduce rejects. A study revealed that the primary problem centered about the proper orientation of the two ceramic elements with respect to the needle cap and the cartridge shell.

The original design called for a plastic molded needle cap, to be cemented to the elements using conventional cartridge assembly techniques. Despite great care in assembly, however, the desired level of uniformity could not be satisfactorily maintained in production. Another approach was needed.

At this point, a new assembly technique was developed. The two ceramic elements are introduced directly into the cavity of the mold used to produce the plastic needle cap. Location of the elements is precise, and the additive effect of cumulative tolerances needed for cementing the separate parts is eliminated. An excellent bond between the elements and the needle cap is achieved using normal thermoplastic materials in standard plastics molding equipment.

The mold itself is unique only in that it includes a removable holder for the elements, precisely machined to locate two close-tolerance ceramic elements so that the tips of the elements extend a specific distance into the mold cavity, and at a specified angular relationship. The benefits of this new technique have been dramatic. Rejects have dropped to 1/3 their former level, and a larger percentage of completed cartridges fall close to the design center when tested for both mechanical and electrical specifications. Improvements have been noted in more uniform lateral tip location, reduced tip lean, and more uniform needle set-down on turnover models. The improved angular orientation and more uniform parallelism of the elements has increased isolation of stereo signals, lowered distortion, and lessened differences in channel level. The net result has been a significant improvement in performance for the consumer without an increase in the cost of production.

For reprints of the entire engineering discussions, write: ELECTRO-VOICE, INC., Dept. 383R, 632 Cecil St., Buchanan, Michigan 49107



Circle 25 on literature card

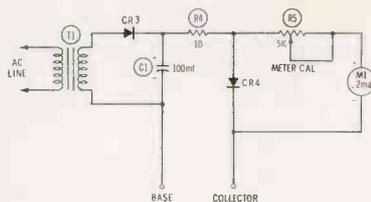


Fig. 3. Leakage test—NPN range.

The leakage test is shown in Fig. 3. This circuit is also quite simple since it is nothing more than a continuity test of the Base-Collector junction. Note though, in the photo (Fig. 1), that the leakage scale is linear to a midscale reading of 100 microamps, and then becomes semi-logarithmic in the second half, to a fullscale reading of 5 milliamps. This is accomplished by CR4 and R5. Remember that most diodes do not conduct until a certain amount of forward bias is applied—usually about 0.5 volt. They then conduct in a semi-logarithmic fashion. If CR4 is chosen so that it just begins to conduct when the meter is at midscale, it will take an increasing share of the current as the current is increased.

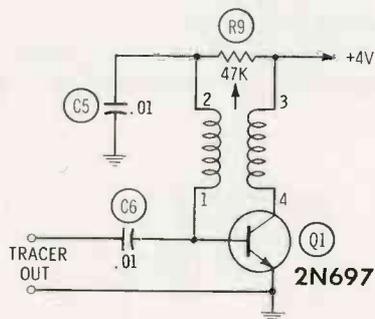


Fig. 4. The signal generator stage.

### Jackson Model 810 Specifications

#### Tests Performed

##### Transistors:

Beta 2-100, 10-500 in- or out-of-circuit, signal or power.

Leakage 0-5000  $\mu$ a ( $V_{CB} = 4V$ ).

##### Diodes:

Open or short in-circuit. Forward and reverse current out-of-circuit.

#### Signal generator output:

8.5 VPP semi-square wave.

#### Power Requirements:

117 VAC 2½ watts.

#### Size (HWD):

7½" × 7½" × 4½"

#### Weight:

4½ pounds.

#### Price:

\$89.95.

The Model 810 also has a built-in signal generator which can be used in a variety of troubleshooting applications. The output signal is a semisquare wave with a considerable amount of frequency modulation. Since the shape of the output is quite complex, it can be heard on the speaker even when injected into an AM RF stage. The manufacturer claims the fundamental frequency is about 3500 Hz, but we synced it on a scope at about 20 kHz. To further confuse matters, when we injected the output in an audio amplifier we got a zero beat at about 600 Hz, so we can't really say what the fundamental frequency is. Regardless, the generator does the job for which it was intended—it feeds through most any amplifier stage and you can hear a signal in the speaker if the stages are good.

### New VTVM

A recent addition to the Precision Apparatus test equipment line is the Model V-95 VTVM, shown in Fig. 5. This VTVM is the first of a new generation of instruments carrying the Precision Apparatus name, and it's quite different from their earlier equipment.

It's immediately apparent that the engineers were as much style-conscious as they were concerned with producing an instrument which is functional. The case is a very heavy gauge vinyl-clad steel, and the vinyl carries a walnut-grain pattern. It appears as though the whole instrument was designed around the meter movement, as about 2/3 of the front panel is occupied by the meter. The Model V-95 should make a very



Fig. 5. Precision Apparatus Model V-95 VTVM is first to carry name.





B&K MODEL 970 RADIO ANALYST

## SERVICE AM & FM AUTO AND TRANSISTOR RADIOS AT A PROFIT!

Jobs that used to be unprofitable now go so quickly that you can make good money handling them! There are millions of auto radios and transistor radios in the field—portables, auto and table models, plus hi-fi and communications equipment. Instead of turning them away, you can turn them into money-makers with the B&K Model 970 Radio Analyst.

The 970 is effective because it's *accurate* and *complete*. Using the famous B&K signal injection technique, this all-in-one instrument provides the required dc power, lets you test power and signal transistors in and out of circuit; generates RF and audio signals, and includes a rugged, accurate VOM. Four functions in one compact package—with solid state reliability, B&K professional quality.

### LOW INVESTMENT—QUICK RETURN

See your B&K Distributor or write for Catalog AP22-R

Net \$199<sup>95</sup>



**B & K MANUFACTURING CO.**  
DIVISION OF **DYNASCAN CORPORATION**  
1801 W. BELLE PLAINE AVE. • CHICAGO, ILL. 60613

Export: Empire Exporters, 123 Grand St., New York 13, U.S.A.

### FEATURES:

#### BUILT-IN POWER SUPPLY

**Auto Radios**—High current, low-ripple, for transistor, hybrid, and vibrator types.

**Transistor Portables**—1½ to 12 volts for battery substitution—plus separately variable voltage tap for bias.

#### QUICK AND ACCURATE TESTING OF POWER AND SIGNAL TRANSISTORS

**In-Circuit**—stage by stage DC signal injection and sensitive metering of power supply current.

**Out-of-Circuit**—Direct Beta and Leakage meter scale readings. Easy balancing or matching.

#### VERSATILE SIGNAL GENERATORS

**RF Generators**—provide broadcast and IF frequencies for both AM and FM bands.

**Audio Generator**—for AM or FM modulation of the RF signals, and for troubleshooting audio circuits.

#### RUGGED VOM

**Volt-OHM-Milliammeter**—with rugged, taut band meter—provides correct ranges for easy, fast servicing of all home and auto radios, as well as transistor portables.

SEE PHOTOFACT Set 798, Folder 2

Mfr: Motorola

Chassis No: STS-914YA, B


Card No: MO 914Y-1

Section Affected: Color pix.

**Symptoms:** No control of hue on color pix, hue remains unchanged. Black-and-white pix normal.

**Cause:** Shielded cable connected to hue control defective. Also, check 3.58-MHz crystal.

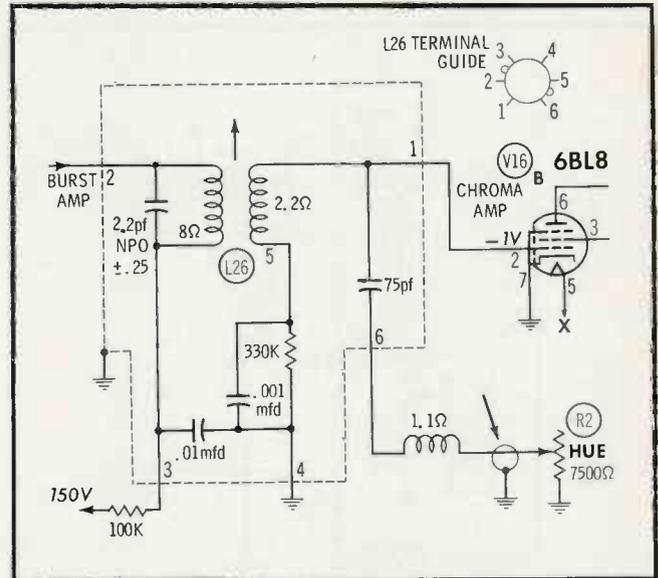**What To Do:** Replace shielded cable connected to R2.



Mfr: Motorola

Chassis No: STS-914YA, B


Card No: MO 914Y-2

Section Affected: Raster.

**Symptoms:** No high voltage. No 150-volt output from low-voltage supply.

**Cause:** Open resistor in 150-volt line of low-voltage supply.

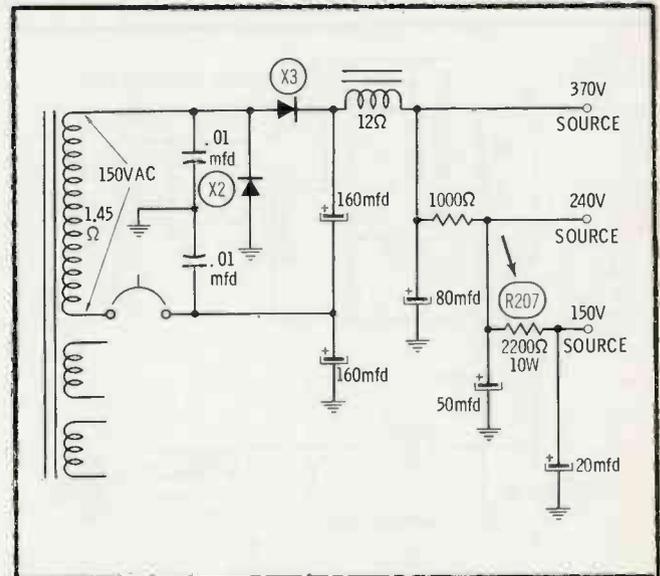**What To Do:** Replace R207 (2.2K ohm, 10 watt).



Mfr: Motorola

Chassis No: STS-914YA, B


Card No: MO 914Y-3

Section Affected: Sync.


**Symptoms:** Vertical sync drifts after set warms up.

**Cause:** Leaky feedback capacitor in grid circuit of vertical multivibrator.

**What To Do:** Replace C69 (.01 mfd).

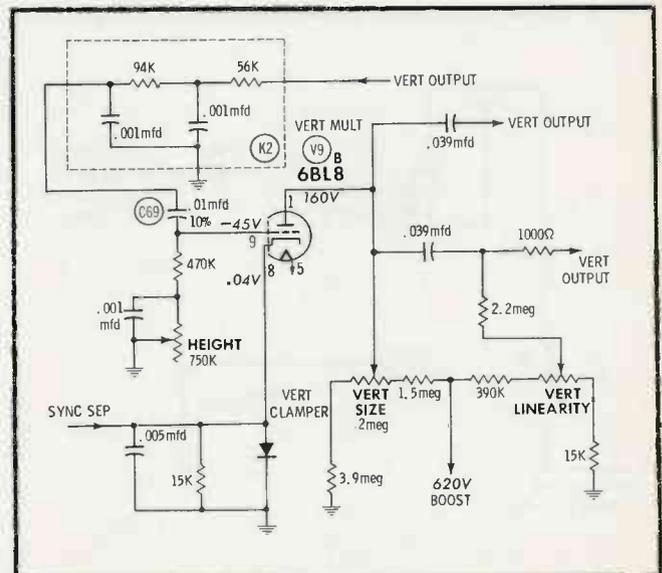

SEE PHOTOFAC Set 798, Folder 2

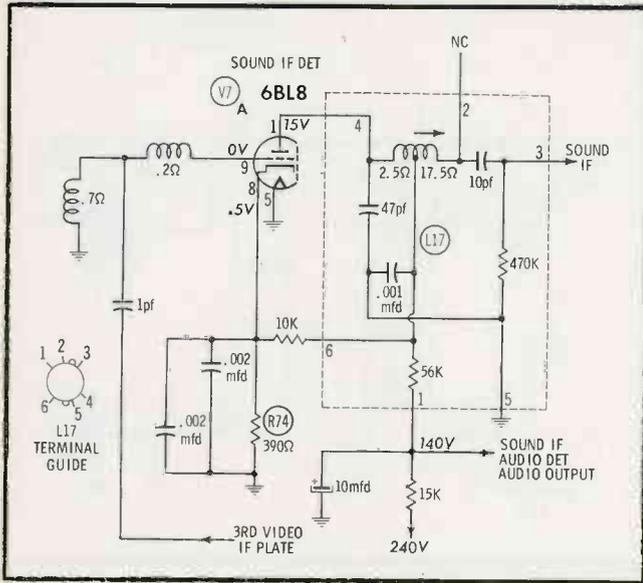

SEE PHOTOFAC Set 798, Folder 2

Mfr: Motorola

Chassis No: STS-914YA, B


Card No: MO 914Y-4

Section Affected: Sound.

**Symptoms:** Intermittent, crackling sound. Voltage fluctuates on cathode (pin 8) of sound IF detector.

**Cause:** Overheated resistor in cathode circuit of V7A, sound IF detector—may even burn open.

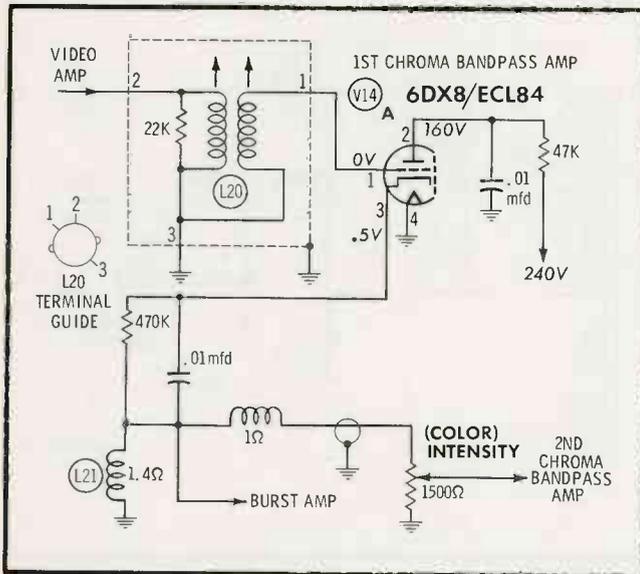**What To Do:** Replace R74 (390 ohms) and check V7 for shorts.



Mfr: Motorola

Chassis No: STS-914YA, B


Card No: MO 914Y-5

Section Affected: Color pix.

**Symptoms:** Color unstable in pix. Black-and-white pix normal. Voltage at cathode (pin 3) of 1st chroma bandpass amplifier normal.

**Cause:** Choke in cathode circuit of V14A opens intermittently.

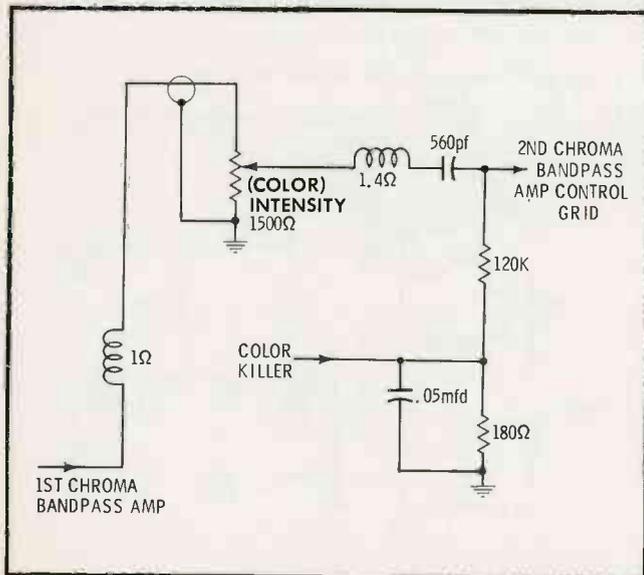**What To Do:** Resolder connections to L21, or replace coil if defective.



Mfr: Motorola

Chassis No. STS-914 YA, B

Card No: MO 914Y-6

Section Affected: Color pix.

**Symptoms:** No color pix. Black-and-white pix normal.

**Cause:** Defective shielded cable leading to intensity control.

**What To Do:** Replace shielded cable.

SEE PHOTOFACT Set 869, Folder 3

Mfr: Zenith

Chassis No: 25NC37


Card No: ZE 25NC37-7

Section Affected: Raster.

Symptoms: Bright screen; no control of brightness level.

Cause: Open video output plate load resistor.

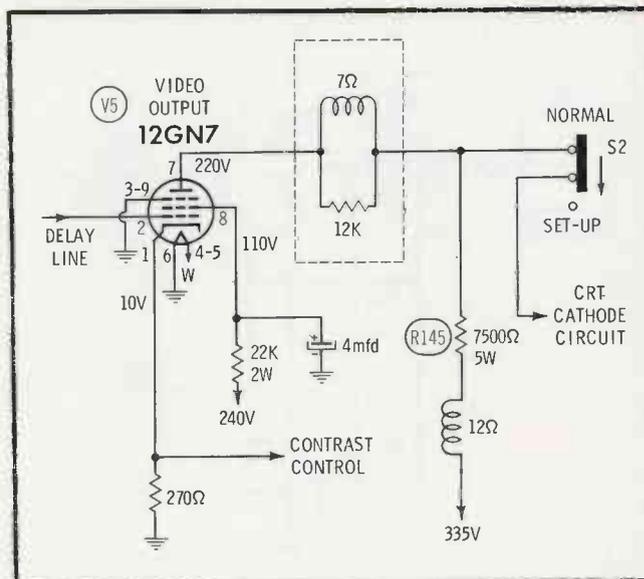What To Do: Replace R145, (7.5K ohms, 5W).



SEE PHOTOFACT Set 869, Folder 3

Mfr: Zenith

Chassis No: 25NC37


Card No: ZE 25NC37-8

Section Affected: Color.

Symptoms: Color far out of phase.

Cause: Defective capacitor in color killer phase detector.

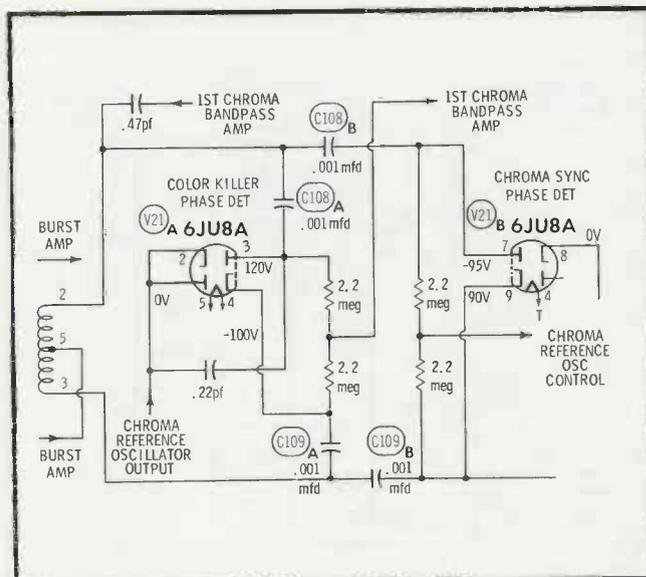What To Do: Replace C108 or C109 (dual section, .001 mfd).



Mfr: Zenith

Chassis No: 25NC37


Card No: ZE 25NC37-9

Section Affected: Sound.


Symptoms: Buzz in sound.

Cause: Open feedback coupling capacitor in sound detector circuit.

What To Do: Replace C42 (2.2pf, 5%).

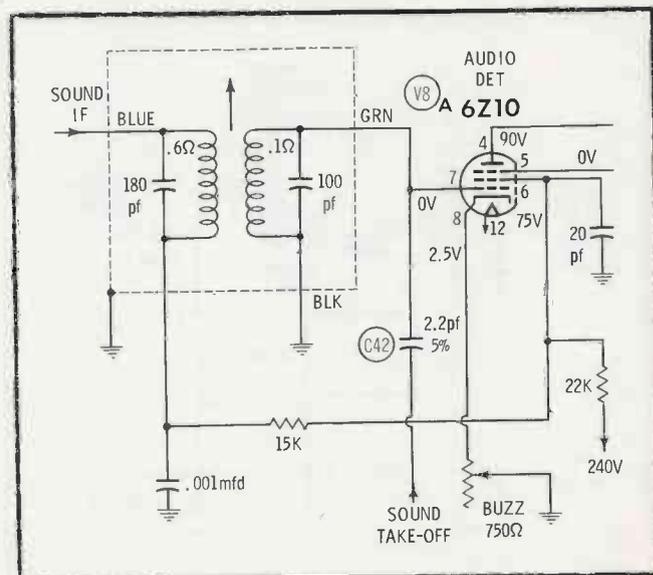

SEE PHOTOFACT Set 869, Folder 3

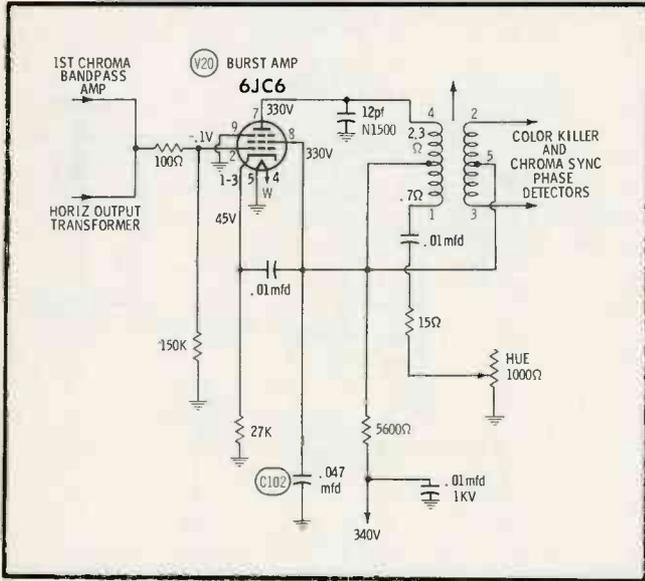

SEE PHOTOFACT Set 869, Folder 3

Mfr: Zenith

Chassis No: 25NC37


Card No: ZE 25NC37-10

Section Affected: Color.

Symptoms: Poor color sync; raster tinted green when receiver properly fine-tuned.

Cause: Open grid bypass capacitor in burst amplifier circuit.

What To Do: Replace C 102 (.047 mfd).

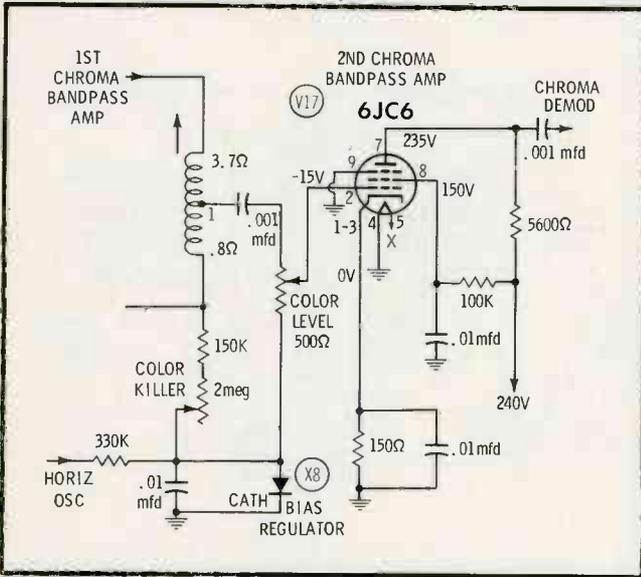

Mfr: Zenith

Chassis No: 25NC37


Card No: ZE 25NC37-11

Section Affected: Pix.

Symptoms: Color killer inoperative

Cause: Shorted bias regulator diode in grid circuit of 2nd chroma bandpass amplifier.

What To Do: Replace X8, bias regulator.

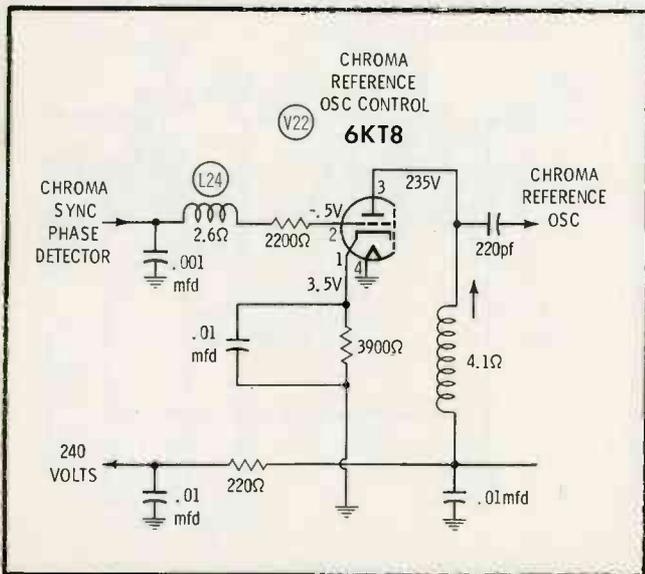

Mfr: Zenith

Chassis No: 25NC37

Card No: ZE 25NC37-12

Section Affected: Color.

Symptoms: No color, or intermittent color.

Cause: Open coil in grid circuit of chroma reference oscillator control.

What To Do: Replace L24.

# BRIDGE CIRCUITS

## A REVIEW/PART 2

A continuing need for exceptionally accurate measurement of such electrical quantities as resistance, capacitance and inductance has sustained the use of this relatively old circuit. This two-part article will refresh your knowledge of the various designs and applications of the bridge.

BY RUFUS P. TURNER

Part 1 of this article began with an analysis of the evolution and operation of the basic AC and DC bridges, then focused attention on the resistance measuring bridge. Part 2 continues our review of bridge circuits with a discussion of capacitance- and inductance-measuring bridges.

### Capacitance Bridges

The capacitance bridge is similar to the resistance bridge in configuration and operating principle, the chief difference being the presence of capacitors in two or more of the bridge arms. Unlike the resistance bridge, the capacitance bridge is always an AC device.

For a long time, the capacitance bridge was the only means of measuring capacitance accurately and quickly without calculations. As a group, capacitance bridges cover a range extending from a few tenths of a picofarad to several thousand microfarads.

The descriptions in this article progress from the simple slide-wire type of bridge through the more complex types which are in common use. Similarities between these bridges and their resistance-measuring counterparts will be apparent.

#### Basic Slide-Wire

Fig. 10 shows the most rudimentary type of capacitance bridge, the basic slide-wire type. This circuit is seen to be similar to the basic slide-wire resistance bridge described in Part 1 of this article. Here,  $C_x$  is the unknown capacitance,  $C_s$  the standard capacitance; the balancing device is the slide-wire — a single strand of resistance wire of uniform cross section, stretched taut between

terminals A and B or wound around a form having a circular cross section, and provided with a sliding contact. An AC generator (e.g., an audio oscillator) and an AC detector (e.g., VTVM or oscilloscope) are connected to the GEN and DET terminals, respectively. Transformer coupling is advisable.

The circuit is balanced by moving the slider between A and B to locate the null. At null:  $C_x = C_s (R_2/R_1)$ . Thus, the unknown capacitance is found by multiplying the standard capacitance by the resistance ratio established by the position of the slider along the wire. Note that the resistance fraction in the equation is inverted with respect to its counterpart in the slide-wire resistance-bridge equation given in Part 1. This results from the fact that in reality the reactance, not the capacitance, of  $C_x$  is balanced against the reactance of  $C_s$  (i.e.,  $X_{Cx}/X_{Cs} = R_1/R_2$ ). It also accounts for the fact that null points for the higher capacitances occur near point A, and those for the lower capacitances near point B (the reverse of the situation in the resistance bridge).

Neither the total resistance ( $R_1 + R_2$ ) of the slide wire nor the individual values  $R_1$  and  $R_2$  need be known in order to make a  $C_x$  measurement. The calculation may be made in terms of distances  $D_1$  and  $D_2$  measured along the slide wire in centimeters, inches, or arbitrary linear units. Thus:  $C_x = C_s (D_2/D_1)$ . From the balance equations, it is seen that null occurs halfway between A and B when the unknown capacitance equals the standard capacitance, to the left of this center when  $C_x$  is greater than  $C_s$ , and to the right of center when  $C_x$  is less than  $C_s$ . To change the capaci-

tance range, one needs only to change the value of the standard capacitance  $C_s$ .

Like the slide-wire resistance bridge, this type of capacitance bridge has the advantages of simplicity and relative economy. It requires few components and needs no capacitance or resistance calibration if the aforementioned equation is used. And it is convenient for emergency measurements, as it requires only a standard capacitor, a length of resistance wire (stretched over a meter stick, yardstick, or other linear scale), and a generator and detector—all usually available in the laboratory or shop. A disadvantage is the failure of the circuit to give a complete null (absolute zero balance) unless the losses in the unknown capacitor equal those in the standard capacitor.

#### Slide-Wire with potentiometer

A more compact version of the slide-wire capacitance bridge, like the similar version of the resistance bridge, substitutes a wirewound potentiometer for the slide wire. Fig. 11 shows this arrangement.

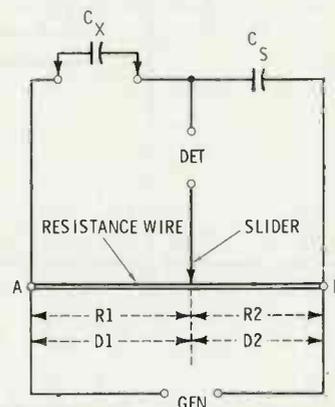


Fig. 10. Basic slide-wire bridge used for measuring capacitance.

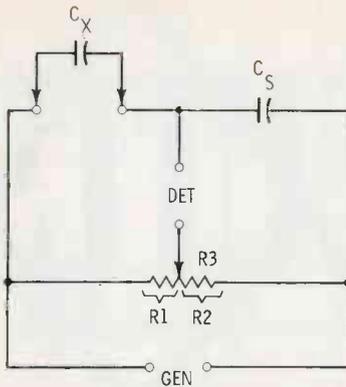


Fig. 11. Slide-wire capacitance bridge employing wirewound potentiometer.

In this circuit, the balancing potentiometer has a total resistance  $R_3$ . At any setting,  $R_3 = R_1 + R_2$ , the resistance between the contact blade and the low end, and the contact blade and the high end, respectively, of the resistance element. Resistances  $R_1$  and  $R_2$  determine the bridge ratio.

At null, the unknown capacitance ( $C_X$ ) is determined from the standard capacitance ( $C_S$ ) and the resistance ratio:  $C_X = C_S(R_2/R_1)$ . The potentiometer dial may be calibrated to read directly in picofarads or microfarads by locating the null points for a number of known capacitances connected successively at  $C_X$ . It may also be calibrated with the aid of the equation, in terms of measured  $R_1$  and  $R_2$  values. If the potentiometer dial reads directly in resistance setting (as the dial of a multiturn potentiometer often does), the unknown capacitance may be calculated with reference to that setting by using the formula  $C_X = C_S$

$$[(R_3 - R_1)/R_1]$$

where,

$R_1$  is the resistance setting indicated by the dial,

$R_3$  is the total resistance of the potentiometer.

Like the basic slide-wire bridge, the potentiometer-type circuit is simple and economical. However, it has three disadvantages: (1) because of stray capacitances in the circuit,  $C_X$  values lower than 100 pf cannot be measured accurately; (2) unless the potentiometer has a special taper, such as logarithmic, the graduations will crowd at the ends of the dial, seriously impairing accuracy, and for that reason the capacitance range with any one standard capacitor  $C_S$  should not exceed 0.1 to 10 times  $C_S$ , even though the potentiometer can afford a wider range; and (3) a complete null occurs only if losses in the unknown capacitor equal those in the standard capacitor.

The degrading effect of stray capacitances in the useful ranges of the bridge may be reduced somewhat by keeping the potentiometer resistance,  $R_3$ , reasonably low — say 5000 ohms. Also, the wasted ends of the potentiometer in the simple circuit may be resolved by means of extension arms (such as  $R_1$  and  $R_3$  in Fig. 12) which allows the useful 100:1 capacitance range to be spread over the entire resistance range of the potentiometer.

#### Practical Slide-Wire Bridge

Fig. 12 shows the circuit of a practical bridge using a 5000-ohm wirewound potentiometer ( $R_2$ ) as the

balance control. This bridge covers the range 100 pf to 100 mfd in three steps: 100 pf-0.01 mfd, 0.01-1 mfd, and 1-100 mfd. The capacitance ranges are selected by switching in standard capacitors ( $C_1$ ,  $C_2$ ,  $C_3$ ). The 100-ohm noninductive resistors  $R_1$  and  $R_3$  provide the extension arms explained in the analysis of the basic potentiometer-type slide-wire bridge.


Any convenient test frequency may be employed, up to about 5kHz. Best stability is obtained when the generator is coupled to the bridge through a shielded transformer. It is advisable also to insert a transformer between the bridge and the detector; however, this second transformer may be omitted if the first one is used, especially if the lower DET terminal is grounded.

This bridge may be calibrated by balancing it with a number of accurately known capacitors connected successively to terminals X-X, and inscribing the potentiometer dial accordingly. Only one range need be calibrated in this manner; the others will track if accurate values are used at  $C_1$ ,  $C_2$ , and  $C_3$ . Thus, the lowest range (0.0001-0.01 mfd) may be calibrated, and the A, B, and C settings of switch  $S_1$  used to multiply this basic range by 1, 100, and 10,000, respectively.

The null balance is sharp if losses in the capacitor under test equal those in the standard capacitor ( $C_1$ ,  $C_2$ ,  $C_3$ ). Since high-quality capacitors customarily are used as standards, this usually means that a sharp null is obtained with low-loss test of significant losses in the capacitor under test.
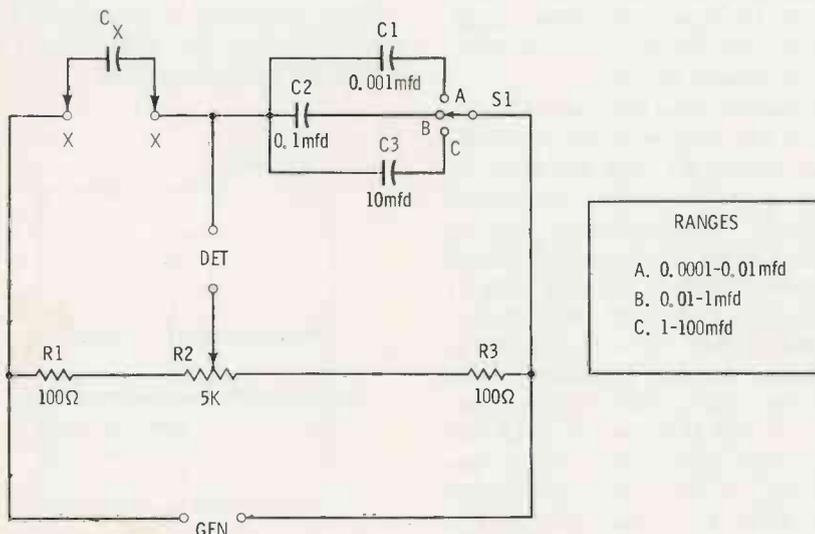
#### Power-Factor Balance

The preceding sections explained that a complete null is impossible with a simple slide-wire bridge unless the losses in the unknown and standard capacitors are equal. The reason for this is the complex nature of the capacitor as an impedance network (resistance and capacitance in combination, the resistance component representing the losses). When the unknown and standard capacitors are of the same kind and magnitude, and when their equivalent impedances are the same in all respects, then a complete null may be obtained. Separate balances are required for the resistive and reactive components.



RANGES	
A.	0.0001-0.01mfd
B.	0.01-1mfd
C.	1-100mfd

Fig. 12. Practical slide-wire bridge for measuring capacitance.

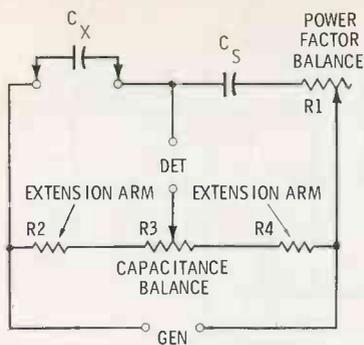


Fig. 13. R1 in series with C<sub>s</sub> balances power factor of capacitors.

It is convenient to express the relation between losses (resistive component) and capacitance (reactive component) as the power factor of the capacitor. Numerically, power factor  $pf = R/Z = \cosine$  of the phase angle of the equivalent RC network. The highest value which power factor can reach is 1 (also expressed as 100%). A low-loss capacitor therefore has a very low power factor. Capacitor quality may be expressed also as the quality factor  $Q = X_C/R = \text{tangent}$  of the phase angle, or as the dissipation factor  $D = R/X_C = \text{cotangent}$  of the phase angle. A low-loss capacitor has a high Q and low D.

In somewhat more specific terms, the original statement may be expressed in the following way: A complete null is obtained only when the power factor, Q, or D of the unknown capacitor equals that of the standard capacitor. When these factors are unequal, as they almost always are in practice, enough resistance can be added in series (or sometimes in parallel) with the low-loss capacitor and thus make it equivalent to the higher-loss capacitor (usually the standard) to increase its power factor (reduce its Q) and thus make it equivalent to the higher-loss capacitor. Fig. 13 shows this arrangement. Here, rheostat R1 is adjusted to improve the null. Additional adjustments of R1 and R3, alternately, will give complete null (dip to zero). The resistance of R1 does not enter into the calculation of unknown capacitance. Nor does the resistance of R3 enter into the calculation of power factor.

For complete null, the resistance of R1 must be adjustable to the equivalent series resistance of the unknown capacitance, C<sub>x</sub>. A dial attached to this rheostat may be calibrated to read directly the power factor (shown either as a decimal or as a percentage;) however, this dial

will read correctly only at the calibration frequency. All complete capacitance bridges are equipped with such a power, Q, or D balance.

Under some circumstances, resistive balance may be obtained also by means of a rheostat in parallel with the standard capacitor. This method works best when the dissipation factors of the unknown capacitor is higher than 1, particularly when the unknown capacitor has a significant equivalent parallel resistance (as in electrolytic capacitors). It tends sometimes to broaden the capacitance null.

Fig. 14 shows how a power-factor balance rheostat is included in a universal bridge so that it may be switched in series with either the unknown or standard capacitor, whichever has the lower power factor—i.e., the lesser resistance as related to capacity. (A universal bridge is a skeleton-type instrument to which unknown and standard resistors, capacitors, or inductors may be connected.) Such a bridge is convenient for checking an unknown (C<sub>x</sub>) against any available capacitor (C<sub>s</sub>) whose capacitance is known, but not necessarily its power factor. When switch S1 is in position A, the power-factor rheostat (R3) is in a series with standard capacitor C<sub>s</sub>; when S1 is in position B, rheostat R3 is in series with unknown capacitor C<sub>x</sub>.

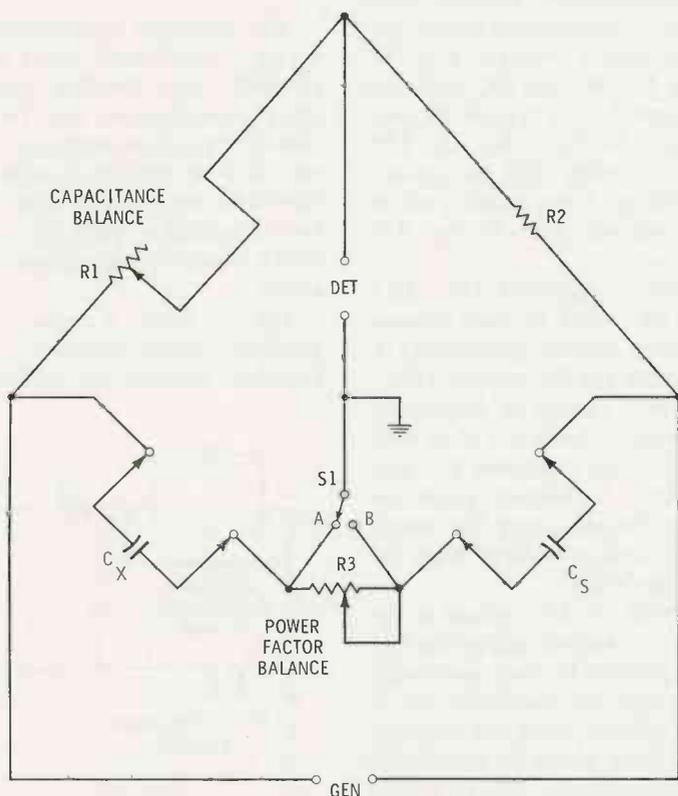


Fig. 14. Universal bridge employing power factor balance control.

#### Capacitance Comparison Bridge

The simplest and perhaps most common capacitance bridge merely substitutes capacitance arms for two of the resistance arms in the Wheatstone bridge, retains the other two resistance arms to complete the basic circuit, and adds a power-factor balance. Because of the similarity of the two bridges, the capacitance type is sometimes familiarly called a

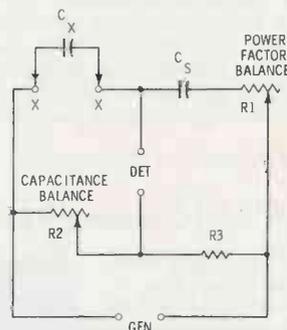


Fig. 15. Capacitance comparison bridge is similar to Wheatstone design.

“Wheatstone capacitance bridge,” but the term “capacitance comparison bridge” appears most often in technical literature.

The comparison bridge overcomes many of the shortcomings of the slide-wire bridge, principally the dial crowding and lower-capacitance limit of the latter instrument. Fig. 15 shows the basic circuit of the comparison bridge. Here the bridge ratio ( $R3/R2$ ) is established by fixed resistor  $R3$  and the capacitance-balance rheostat,  $R2$ . A second rheo-

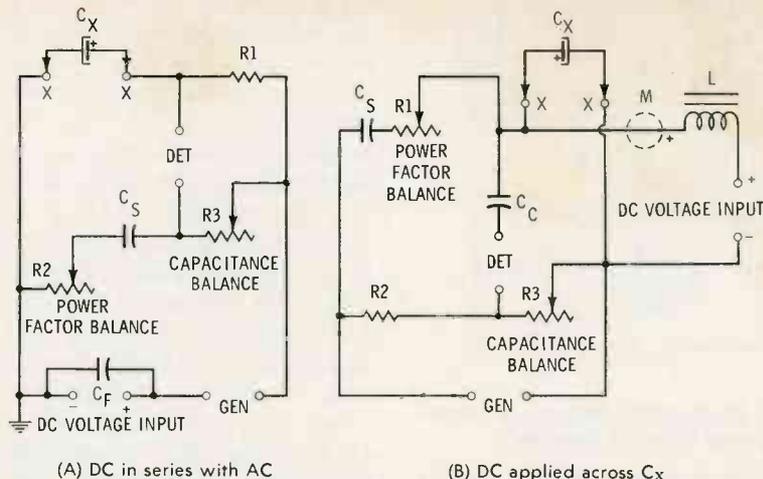


Fig. 16. Both AC and DC voltages must be used when measuring some capacitors.

stat,  $R1$ , provides the power-factor balance. At null:  $C_x = C_s(R3/R2)$ .

#### DC Polarizing Voltage

The capacitance of an electrolytic capacitor is not the same with and without a DC polarizing voltage. The direct application of an AC signal to an unpolarized electrolytic capacitor, besides giving false readings, is also damaging because of polarity reversal. Moreover, the capacitance varies with the magnitude of the DC voltage. The same is true of a capacitor having a nonlinear ceramic dielectric.

Such capacitors must be measured with their normal DC working voltage applied simultaneously with the AC bridge signal voltage. Fig. 16 shows how the AC and DC voltages may be applied to a typical capacitance bridge. In Fig. 16A, the DC voltage is in series with the generator AC voltage. Capacitor  $C_F$  offers a low-impedance path to the AC signal.

Note that a capacitor ( $C_x, C_s$ ) sets up a DC block in each branch of the bridge circuit, preventing a short circuit of the DC supply. However, the DC voltage is impressed upon standard capacitor  $C_s$ , as well as upon unknown capacitor  $C_x$ , and the standard capacitors must be rated to withstand safely the maximum DC voltage which may be applied to the bridge.

In Fig. 16B, the DC voltage is applied across unknown capacitor  $C_x$ . This arrangement is often used with bridges having no provision for a polarizing voltage, since an external DC supply may easily be connected to the X-X terminals. Choke coil  $L$  (30 henrys or higher) prevents the DC supply from short-circuiting the

AC bridge signal. A DC milliammeter,  $M$ , may be inserted to indicate leakage current of the unknown capacitor. Capacitor  $C_C$  provides DC blocking to protect the null detector. In this arrangement, the output capacitance of the DC power supply must be negligible with respect to the capacitance being measured; otherwise, it must be subtracted from each measured  $C_x$  value. The DC voltage must be free from ripple, or the ripple frequency will interfere with the AC signal and obscure the bridge balance.

#### Substitution Method

The difficulty of accurately measuring capacitances lower than 100 pf with some bridges, because of stray capacitances, has been mentioned in previous sections. Low values may be measured satisfactorily, however, with any bridge by using the substitution method, a process which automatically compensates for strays.

Fig. 17 shows a conventional capacitance bridge adapted to the substitution method by addition of a

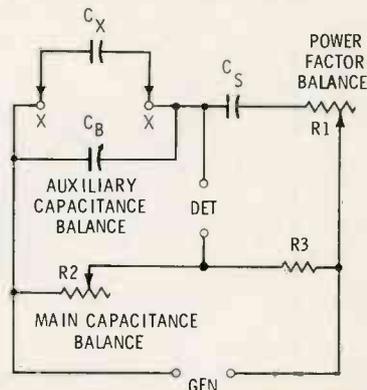


Fig. 17. Substitution method permits measurement of low values.

## FIRST WITH

- Digital Integrated Circuits
- 4 Crystal-Controlled Oscillators
- Battery & AC Operation Standard



The New Pace-Setting  
CONAR Model 680

# COLOR GENERATOR

KIT \$83.50 WIRED \$114.50

Until now, no commercially available color generator has offered so many quality features in a single instrument at such a low price. Only the CONAR COLOR GENERATOR has all these features at any price: exclusive digital integrated circuits; exclusive 4 crystal-controlled oscillators; exclusive AC or battery operation standard; completely solid state; color amplitude control; color phase adjustment; regulated power supply; stability control; TV station sync and blanking pulses; nine patterns; red, blue and green gun killers; compact; lightweight; portable.

For details write Dept. C08C

## CONAR instruments

DIVISION OF NATIONAL  
RADIO INSTITUTE  
3939 Wisconsin Ave.,  
Washington, D.C. 20016

WRITE FOR  
FREE CONAR CATALOG



Circle 28 on literature card

calibrated variable capacitor,  $C_B$ , connected to the unknown terminals, X-X. This capacitor is usually a 100- or 1100-pf air type having a dial reading directly in picofarads. In all other respects, this bridge is identical to the one shown in Fig. 15.

A four-step procedure is employed:

1. With no unknown capacitor ( $C_X$ ) connected to terminals X-X, variable capacitor  $C_B$  is set to its maximum capacitance ( $C_M$ ), and the bridge then balanced in the regular manner by adjustment of R2 and R1. Hence, R2 is not disturbed.

2. The unknown capacitor next is connected to terminals X-X by the shortest possible leads. This adds capacitance and accordingly unbalances the bridge.

3. The bridge is rebalanced by setting variable capacitor  $C_B$  to a lower capacitance ( $C_L$ ) and readjusting power-factor balance R1.

Finally, the unknown capacitance is calculated from the two settings of the variable capacitor:  $C_X = C_M - C_L$ . In this way, capacitances of less than 0.1 pf are measured with good accuracy. If long connecting leads are unavoidable, the bridge may be initially balanced in Step 1 with the leads connected to X-X and in the same position they will have when connected to the capacitor  $C_X$ . Then the capacitor is connected for the remaining steps.

A practical advantage of the substitution method is the ease with which it may be used with any capacitance bridge. Thus, a dial-calibrated variable air capacitor may be connected externally to the unknown terminals of any bridge, provided that short rigid leads are used and that the four-step procedure described previously is employed.

In commercial substitution bridges, the variable capacitor dial sometimes is graduated with zero at the maximum-capacitance setting of this capacitor, and with maximum capacitance at the zero-capacitance setting. The initial balance with R2 (see Step 1 above) then becomes a zero adjustment, and after rebalance (Step 3) the dial reads  $C_X$  directly in pf, no calculation being required.

### Inductance Bridges

Inductance bridges may be regarded as forming the second large class of AC bridges. In general con-

figuration, the inductance bridge resembles the capacitance bridge and the resistance bridge. It differs from the capacitance bridge, however, in the presence of inductors in one or more of its arms and also in the respect that it can, in some versions, compare unlike impedances, i.e., inductance with capacitance.

As a class, inductance bridges cover the range from 0.1 nanohenry to 10,000 henrys with accuracies reaching  $\pm 0.1\%$  or better. Like the resistance bridge and capacitance bridge, the inductance bridge may

be either simple or complex to suit individual demands.

### Basic Slide-Wire

Fig. 18 shows the most basic inductance bridge. In this arrangement, the variable balancing resistor (the slide wire) tautly stretched between points A and B (or wound around a form having a circular cross section) and provided with a sliding contact (the slider). The wire has a uniform cross section and is of constant composition, so its

**NO MORE GUESSWORK!**



**AMERICA'S MOST RELIABLE TUBE ANALYZER**


## CONTINENTAL

You don't need three guesses to tell if a tube is bad — or why. With the new Sencore MU140 Continental, you **know**. Right now. And you simply can't go wrong. Because it's a complete tube analyzer for 4-way testing — true mutual conductance (using exclusive 5000 hertz square wave), full cathode emission, 100 megohm grid leakage, and internal shorts. Tests all tubes, including foreign — over 3000 in all. Obsolete-proof, too — with "new socket" panel, and controls so standard the switch numbers correspond to the pin numbers in any tube manual.

**If it's reliability you want — for years to come — you need the Continental. It's the best way to be sure —**

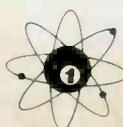**for only \$179<sup>50</sup>**

See America's most complete line of professional test instruments — at your Distributor now.



**SENCORE**  
NO. 1 MANUFACTURER OF ELECTRONIC MAINTENANCE EQUIPMENT  
426 SOUTH WESTGATE DRIVE, ADDISON, ILLINOIS 60101

Circle 29 on literature card

resistance is directly proportional to its length.

As the slider is moved along the wire, it divides the latter into two parts: D1, the length from point A to the slider, which has a resistance of R1, and R2, the length from point B to the slider, which has a resistance of R2. Thus, the resistance increases on one side of the moving slider and decreases on the other side.

The bridge is composed of unknown inductor  $L_x$  (connected to

terminals X-X), standard inductor  $L_s$ , and the two sections (R1 and R2) of the slide-wire variable resistor, which provide the ratio arms.

The bridge is balanced by moving the slider along the wire until the detector response is minimum. At this null point,  $L_x/L_s = R1/R2$ , and from this relationship the unknown inductance may be determined in terms of the standard:  $L_x = L_s (R1/R2)$ .

The total resistance of the slide wire is unimportant to the calcula-

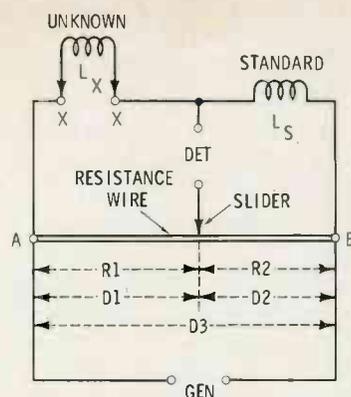


Fig. 18. Basic inductance bridge.

tion. So also are the actual resistance values on each side of the slider. In fact, distances D1 and D2 may be measured in inches, centimeters, or arbitrary linear units and used in the preceding calculation in place of resistances R1 and R2; thus,  $L_x = L_s (D1/D2)$ . For this reason, the basic slide-wire bridge is convenient for emergency measurements of inductance, since it requires only a standard inductor and a length of bare resistance wire stretched along a meter stick or yardstick, in addition to a generator (e.g., an audio oscillator) and a detector (e.g., AC VTVM, oscilloscope, or high-resistance headphones)


Sometimes it is more convenient to read the position of the slider with respect to the total length (D3) of the wire than to measure D1 and D2 separately. In such an instance:  $L_x = L_s [D1/(D3 - D1)]$ .

It is apparent from either of the latter two equations that the unknown ( $L_x$ ) is equal to the standard ( $L_s$ ) when null occurs with the slider halfway between A and B (i.e., when  $D1 = D2$ , making  $D1/D2 = 1$ .) Also, the slider must move to the right of center when  $L_x$  is greater than  $L_s$ , and to the left of center when  $L_x$  is less than  $L_s$ .

If the wire is long (say, 1 meter or more), little difficulty is experienced in measuring inductances over the range  $0.01L_s$  to  $100L_s$ , provided a sensitive detector is used. Unless the wire has reasonably high resistance (large ratio of length to thickness), however, the current may heat it enough to impair the accuracy of measurement.

Part 3 of this article will continue our analysis of inductance-measuring bridges and will conclude this series.
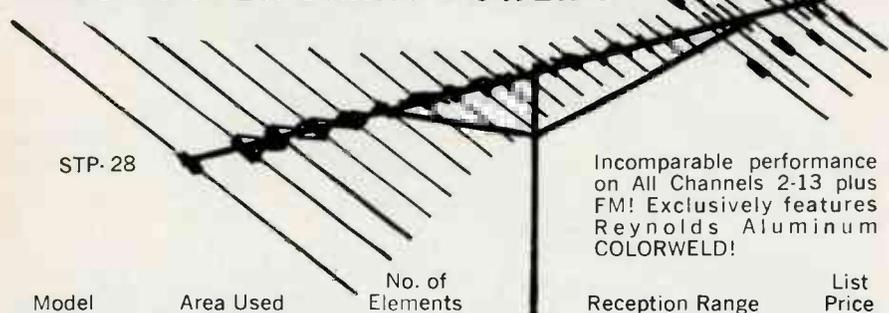
## THE BEST COLOR ANTENNAS! RMS SUPER TRANS POWER'D




STP-28

Incomparable performance on All Channels 2-13 plus FM! Exclusively features Reynolds Aluminum COLORWELD!

Model	Area Used	No. of Elements	Reception Range	List Price
STP-7	Metropolitan	7	Up to 50 miles	\$13.45
STP-11	Suburban	11	Up to 75 miles	19.95
STP-15	Semi-Fringe	15	Up to 100 miles	26.95
STP-19	Fringe	19	Up to 125 miles	39.95
STP-23	Extreme Fringe	23	Up to 150 miles	44.95
STP-28	Extreme Fringe	28	Up to 175 miles	53.95

## RMS DYNERGY

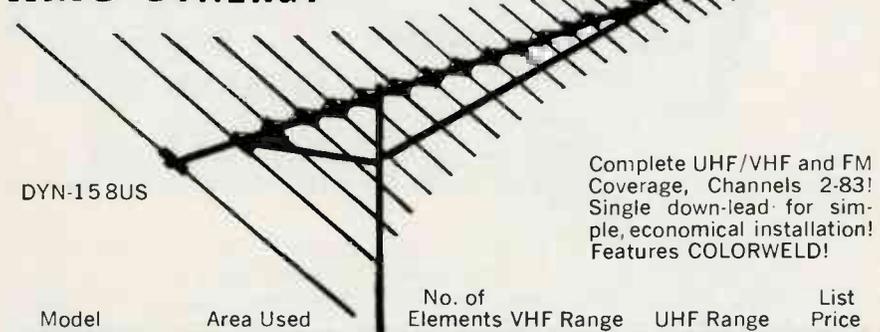

DYN-158US

Complete UHF/VHF and FM Coverage, Channels 2-83! Single down-lead for simple, economical installation! Features COLORWELD!

Model	Area Used	No. of Elements	VHF Range	UHF Range	List Price
DYN-33US	Metropolitan	6	to 35 miles	to 20 miles	\$19.95
DYN-54US	Suburban and Semi-Fringe	9	to 60 miles	to 30 miles	29.95
DYN-66US	Suburban and Semi-Fringe	12	to 75 miles	to 50 miles	34.95
DYN-88US	Semi-Fringe and Fringe	16	to 125 miles	to 75 miles	44.95
DYN-118US	Semi-Fringe and Fringe	19	to 125 miles	to 75 miles	44.95
DYN-158US	Fringe	23	to 150 miles	to 75 miles	49.95

Make your next installation profitable with these dependable RMS Antennas. Write for FREE Informative Catalog! Dept. PFA

Dependable construction and performance for long-life installation!


# RMS ELECTRONICS, INC.

50 ANTIN PLACE, BRONX, N. Y. 10462

Circle 30 on literature card



## Balanced Diode

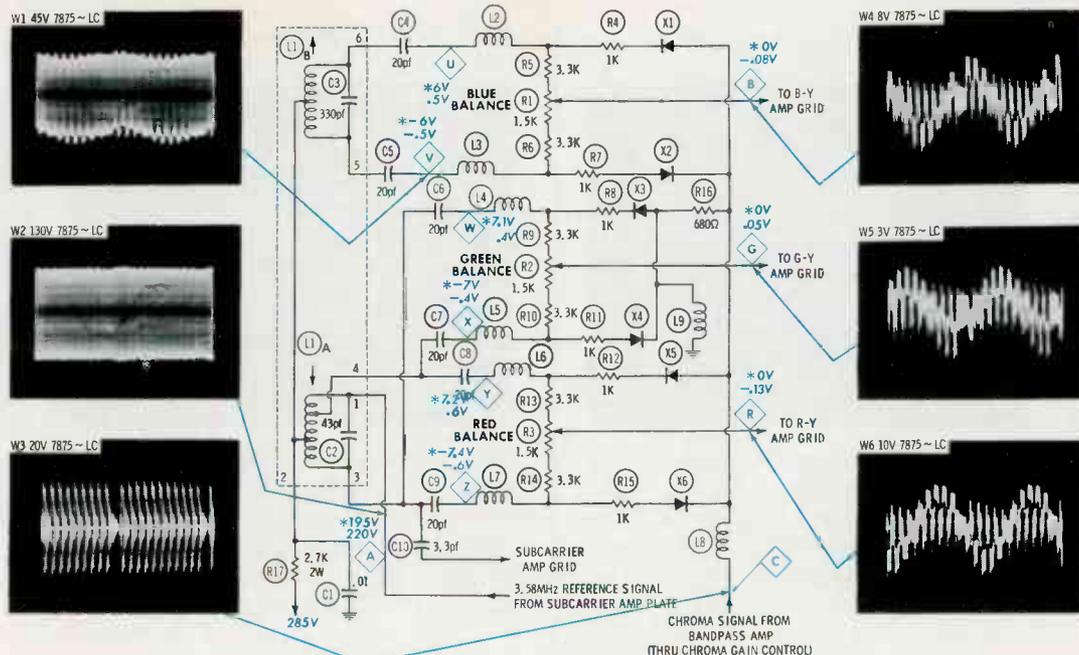

DC VOLTAGES taken with VTVM—color bar generator not operating. \*Indicates voltage taken with generator operating—see "Operating Variations."

WAVEFORMS taken with wide-band scope TV controls set to produce normal color-bar pattern on screen. LC (low-cap) probe used to obtain all waveforms.

### Normal Operation

Circuit shown is balanced-diode color demodulator used in General Electric chassis. Balancing out 3.58-MHz reference signal at detectors maintains zero potential at difference amplifier grids, even if amplitude of reference signal varies—thus preventing color shading. L1 between terminals 1 and 2 is plate boost for subcarrier amplifier. Reference signal of proper phase for red modulation is tapped off at terminals 3 and 4. 3.58-MHz signal is also coupled to L1B where correct phase for blue demodulation is tapped off at terminals 5 and 6. Green demodulator uses same phase of 3.58-MHz signal as red, but composite chroma signal is delayed by R16 and L9 so that green is detected at proper phase. Configuration of L1 may vary between different chassis but basic operation is same. Since each demodulator functions similarly (component values are same) only blue (B-Y) demodulator will be analyzed. 3.58-MHz signal is coupled to diodes X1 and X2 thru C4 and C5. Diodes function as peak detectors after initial full charge of C4 and C5. Composite chroma signal is connected to anode and cathode of X1 and X2, respectively. When diodes are conducting, chroma signal is detected by each diode. X1 develops positive voltage which is proportional to sum of chroma and in-phase reference signal. X2 develops negative voltage proportional to sum of chroma and the 180° out-of-phase reference signal. Equal but opposite reference signals produce zero DC output, but detected chroma information adds across R5, R1, and R6. Chroma output at point B is negative-going signal with amplitude equal to half the total across resistors R5, R1, and R6.

### Operating Variations

- A** With color signal present, burst excites reference oscillator into conduction; plate voltage drops from no-signal potential of 220 volts to 195 volts.
- U thru Z** Dc voltages are direct result of rectified reference signal (near zero with no signal) and vary somewhat according to amplitude of burst signal. Voltages indicated are typical with good signal input from keyed rainbow generator. Voltages at two test points in each demodulator section should be equal in amplitude but of opposite polarity.
- C, B, G, R** These test points remain at zero volts with or without color signal.
- Waveforms** W2 amplitude varies according to level of burst—measures about 50 volts p-p on fringe station, 110 volts p-p on local station. Tint control varies W2 p-p reading from 50 volts to 150 volts. W1 changes in direct proportion with W2 since it is same signal, only coupled through L1 for proper phase—tint control varies amplitude of reference signal portion, chroma gain control changes content (jagged peaks). W3 varies from zero (no color) to about 40 volts p-p (severe color "bleeding") according to chroma gain control (good color if about 10 volts p-p). W4, W5, and W6 vary with signal strength and setting of chroma level control (0 to 150% of values shown). Color bar pattern good with 75% of values shown.


## Weak or No Color

Color Bars Correct


### R17 Increased In Value

(Voltage Divider—2.7K, 2W)


#### SYMPTOM 1

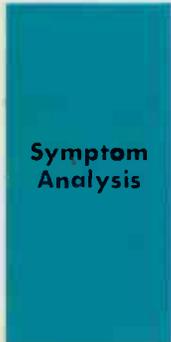

Symptom Analysis

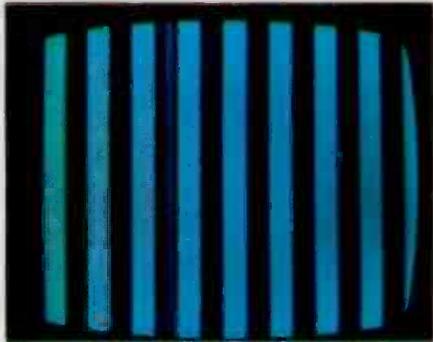

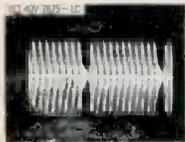
Almost normal color with chroma gain at maximum on local station; little or no color on fringe station. Generator signal color bars in correct order but weak. Tint control operates when color present. B-W picture normal. Symptom indicates chroma signal loss.



#### Waveform Analysis

W3 eliminates chroma circuitry trouble since amplitude is at least 200% of required level and content is good. Although not shown, W4, W5, and W6 isolate defect to demodulator circuitry—all are 25 to 30% of normal amplitude. W1 is good clue—amplitude reduced (normally about 45 volts p-p) and content lacks 3.58-MHz signal. W2 amplitude localizes trouble to L1—only about 10 volts p-p (normally about 130 volts p-p).

#### Voltage and Component Analysis

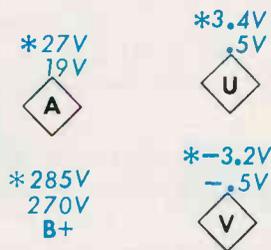

Voltages at points U thru Z are about 50% of normal but are balanced—readings of each section are equal but opposite—confirms demodulators are operating but at reduced level. 27-volt reading at point A isolates trouble to R17, C1, or L1A since B+ checks near normal. Increased resistance of R17 (voltage divider supplying subcarrier amplifier) results in loss of 3.58-MHz signal supplied to demodulators. R17 completely open or open between terminals 1 and 2 of L1, or shorted C1, would cause complete loss of color.

Best Bet: Scope then VTVM.


## No Blue

B-W Picture Normal

### Open X2

(Blue Demodulator Diode)

#### SYMPTOM 2


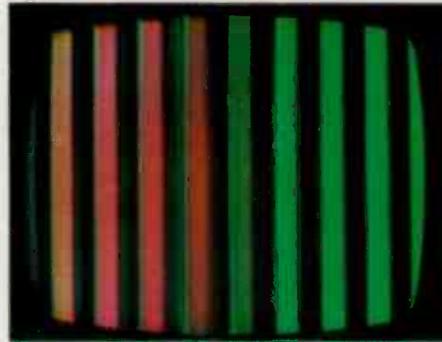


Symptom Analysis


Loss of blue evident on station color programs—whites have yellow tint, other colors using blue are wrong. Tint and chroma gain controls operate. Bar pattern shows only green and red—blue missing and background yellow with chroma gain at minimum. B-W normal.
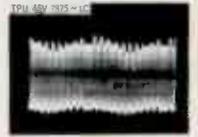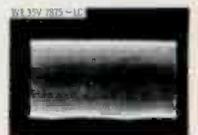
#### Waveform Analysis

Amplitude of W4 explains loss of blue—normally about 8 volts p-p, now only 1.5 volts p-p. Content shows excess 3.58-MHz signal. Although not shown, W5 and W6 are normal. W2 (3.58-MHz input to B-Y demodulator) shows sufficient reference signal but content lacks rectified chroma signal riding on subcarrier. Thick waveform at point U is near normal in content and amplitude. Comparison of waveforms at U and V gives clue to trouble.



#### Voltage and Component Analysis

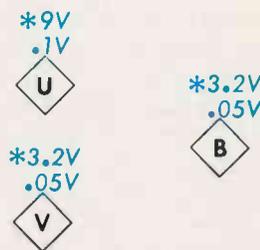

Voltage at U and V 3.2 and 9 volts, respectively (normally near equal but opposite). This unbalance is reflected at points B; reading is 3.2 volts, should be zero. DC voltage at these points is result of diodes rectifying reference signal, thus no-signal readings (b-w) are near normal (zero). CRT B-Y grid is cut off as result of demodulator unbalance (positive voltage at B-Y amplifier grid)—blue is lost, whites are tinted yellow, and other colors using blue are incorrect. Good b-w picture helps isolate trouble.

Best Bet: VTVM for voltage and resistance measurements.

## Red Predominant


B-W Picture Normal

### Leaky X5

(Red Demodulator Diode)

#### SYMPTOM 3

Symptom Analysis

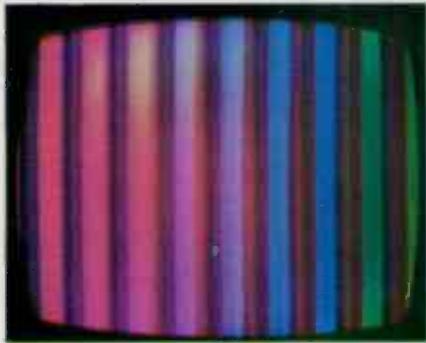

Color programs show excessive red—also, areas that should be white are red. Near normal color picture obtained by misadjusting tint and color controls. Screen is tinted red with color signal; but with chroma gain control at minimum b-w picture has proper gray scale.

#### Waveform Analysis

W6 (shown), as well as W4 and W5 (not shown), have sufficient amplitude and proper content to produce good color bars. Second and third waveforms shown here, from points Y and Z (3.58-MHz reference signal input to red demodulator), although slightly higher in amplitude, are similar to W1. W1 is representative of waveforms at points U thru Z—all similar in amplitude; content is 3.58-MHz signal with detected chroma signal riding on carrier.

\* 3.5V  
0V

Y

\* -2.2V  
-.04V

R

\* -9.2V  
0V

Z

#### Voltage and Component Analysis

Defective X5 measures approximately 3K either direction; causes unbalance in red demodulator section—voltage at point Y is 3.5 volts, point Z is -9.2 volts—produces negative voltage (-2.2V) at point R. This results in continuous R-Y amplifier conduction which causes red shading with color signal input. B-W picture normal since unbalance caused by rectified 3.58-MHz signal. Leaky X6 would cause loss of reds. Any component value change in balanced demodulator causes too much color or loss of color.

Best Bet: VTVM and circuit analysis.

## Green Screen


On Color Only

### Open C1

(Bypass Capacitor—.01 mfd.)

#### SYMPTOM 4

Symptom Analysis

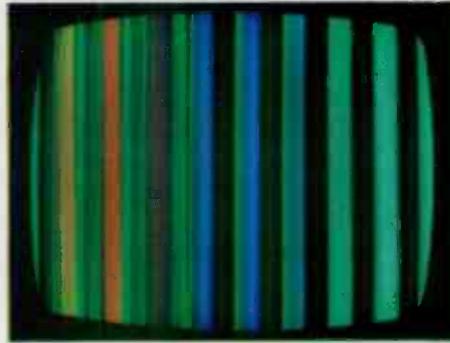

Station program with chroma gain at normal setting is predominately green—flesh tones green and tint control inoperative—white areas are green—other colors weak. Other colors wrong with chroma gain at maximum. Color bar pattern mostly green. B-W normal.

#### Waveform Analysis

Amplitude of W5 is satisfactory but content shows reason for excessive green: negative portion which causes G-Y amplifier conduction is relatively straight—conducts constantly. W4 and W6 content mostly 3.58-MHz reference signal. Although not shown, W5 with chroma gain at minimum contains 4-volt p-p 3.58-MHz signal—normally less than .5 volts p-p. W1 amplitude low but acceptable. R17-C1 indicates trouble, normally only DC here.

\* 7.1V  
0V

B

\*.5V  
0V

R

\* -.3V  
0V

G

#### Voltage and Component Analysis

Comparative DC voltages at inputs of each demodulator section (L1 thru Z) all show unbalance which causes abnormal readings at points B, G, and R. B-Y and R-Y amplifier conduction is limited by positive potential, while G-Y is allowed to conduct heavily. Open C1 allows burst frequency to be coupled to chroma bandpass circuitry, then to point C. L1 is also detuned—3.58-MHz reference signal to demodulators is reduced and phase relationship upset. G-Y amplifier conducts constantly and heavily at burst phase.

Best Bet Careful scope and VTVM work will solve.


## Reds Missing

Blues and Greens Near Normal


### Symptom 5

#### R3 Wiper Arm Open



(Red Balance Control—1.5K)

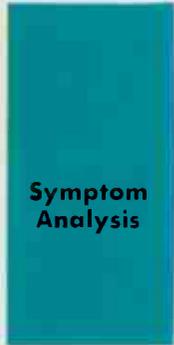

Symptom Analysis

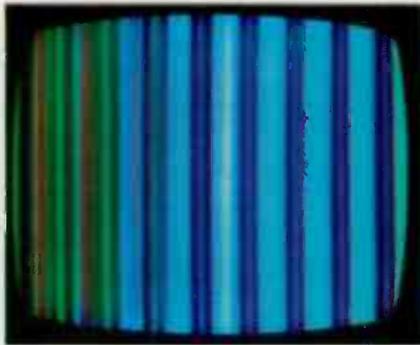

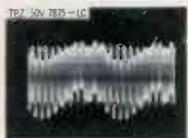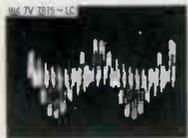Impossible to get proper flesh tones on station color signal—tint control varies hue from purple to green but no normal flesh tones between. Red reduced in picture—color bar pattern shows little red even at maximum chroma gain setting. B-W normal.



#### Waveform Analysis

W4 (shown) and W5 not (shown), blue and green demodulator outputs, have normal amplitude and content. W6 (input to R—Y amplifier) is very poor—amplitude only 2.5 volts p-p compared to normal 10 volts p-p, and content is all wrong—third negative-going pulse should be at maximum—instead, all pulses nearly equal. Waveform at point Z (shown) and Y (not shown) have normal amplitude and content— isolates trouble to red demodulator.

\*0V  
-.08V



\*0V  
0V



\*0V  
.05V



#### Voltage and Component Analysis

Proper DC potentials (0V) at points B, G, and R, along with sufficient 3.58-MHz input signal at points U thru Z, eliminates demodulator unbalance. To adjust DC balance: Connect color bar generator, set chroma gain control to minimum, adjust R1, R2, and R3 for zero volts at points B, G, and R, respectively. Controls normally vary DC potential about 1 volt above and below zero. With open wiper arm, R3 has intermittent or no effect on voltage at point R. Open control itself would unbalance demodulator—R3 voltage not zero.

Best Bet: Scope first; then VTVM.


## Reds Lost

Greens Incorrect

### Symptom 6

#### Transformer Winding Open

(L1—3.58-MHz Phase Transformer)


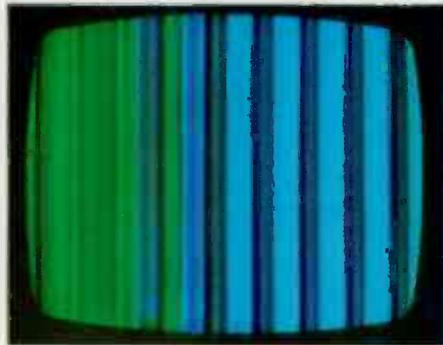


Symptom Analysis

Flesh tones are greenish, as is most everything except for some blue information. Chroma gain control operates, but tint control has no effect. Color bar pattern shows blues in approximately correct position. Most other bars green or shaded blue. B-W normal.
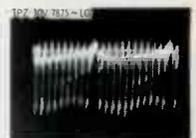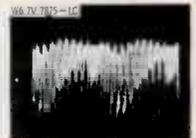
#### Waveform Analysis

Waveforms at test points R (W6, shown) and G (W5, not shown) are similar; amplitude of about 7 volts p-p is sufficient, but content is very poor—normal sine-wave effect of pulses is missing. Waveform at Z is weak—normally about 50 volts p-p, now 10 volts p-p—content all wrong—appears to be negative-going spikes of chroma signal. Waveform at point W similar but positive going. W2 (3.58-MHz input) is about 50% of normal.



\*-.1V  
0V



\*.9V  
0V



\*-.6V  
0V



#### Voltage and Component Analysis

DC voltages at points U and V are low but nearly balanced—voltages at points W, X, and Y, Z are unbalanced. This results in nearly correct potential (0V) at point B but negative voltage at point G and positive at point R. Open winding between terminals 2 and 3 of L1 causes loss of reference signal input to one side of red and green demodulators, resulting in unbalance, as well as detuning subcarrier amplifier plate circuit. Blue demodulator is affected to lesser extent by reduced and incorrect phase of reference signal.

Best Bet: Scope; then VTVM for voltage and resistance.



# get the service data you need in PHOTOFACT® COMPLETE COLOR TV COVERAGE

283 Here are the PHOTOFACT sets with Color TV coverage from the beginning in 1954 through 1967:

1	31	61	91	121	151	181	211	241	271	301	331	361	391	421	451	481	511	541	571	601	631	661	691	721	751	781	811	841	871	901
2	32	62	92	122	152	182	212	242	272	302	332	362	392	422	452	482	512	542	572	602	632	662	692	722	752	782	812	842	872	902
3	33	63	93	123	153	183	213	243	273	303	333	363	393	423	453	483	513	543	573	603	633	663	693	723	753	783	813	843	873	903
4	34	64	94	124	154	184	214	244	274	304	334	364	394	424	454	484	514	544	574	604	634	664	694	724	754	784	814	844	874	904
5	35	65	95	125	155	185	215	245	275	305	335	365	395	425	455	485	515	545	575	605	635	665	695	725	755	785	815	845	875	905
6	36	66	96	126	156	186	216	246	276	306	336	366	396	426	456	486	516	546	576	606	636	666	696	726	756	786	816	846	876	906
7	37	67	97	127	157	187	217	247	277	307	337	367	397	427	457	487	517	547	577	607	637	667	697	727	757	787	817	847	877	907
8	38	68	98	128	158	188	218	248	278	308	338	368	398	428	458	488	518	548	578	608	638	668	698	728	758	788	818	848	878	908
9	39	69	99	129	159	189	219	249	279	309	339	369	399	429	459	489	519	549	579	609	639	669	699	729	759	789	819	849	879	909
10	40	70	100	130	160	190	220	250	280	310	340	370	400	430	460	490	520	550	580	610	640	670	700	730	760	790	820	850	880	910
11	41	71	101	131	161	191	221	251	281	311	341	371	401	431	461	491	521	551	581	611	641	671	701	731	761	791	821	851	881	911
12	42	72	102	132	162	192	222	252	282	312	342	372	402	432	462	492	522	552	582	612	642	672	702	732	762	792	822	852	882	912
13	43	73	103	133	163	193	223	253	283	313	343	373	403	433	463	493	523	553	583	613	643	673	703	733	763	793	823	853	883	913
14	44	74	104	134	164	194	224	254	284	314	344	374	404	434	464	494	524	554	584	614	644	674	704	734	764	794	824	854	884	914
15	45	75	105	135	165	195	225	255	285	315	345	375	405	435	465	495	525	555	585	615	645	675	705	735	765	795	825	855	885	915
16	46	76	106	136	166	196	226	256	286	316	346	376	406	436	466	496	526	556	586	616	646	676	706	736	766	796	826	856	886	916
17	47	77	107	137	167	197	227	257	287	317	347	377	407	437	467	497	527	557	587	617	647	677	707	737	767	797	827	857	887	917
18	48	78	108	138	168	198	228	258	288	318	348	378	408	438	468	498	528	558	588	618	648	678	708	738	768	798	828	858	888	918
19	49	79	109	139	169	199	229	259	289	319	349	379	409	439	469	499	529	559	589	619	649	679	709	739	769	799	829	859	889	919
20	50	80	110	140	170	200	230	260	290	320	350	380	410	440	470	500	530	560	590	620	650	680	710	740	770	800	830	860	890	920
21	51	81	111	141	171	201	231	261	291	321	351	381	411	441	471	501	531	561	591	621	651	681	711	741	771	801	831	861	891	921
22	52	82	112	142	172	202	232	262	292	322	352	382	412	442	472	502	532	562	592	622	652	682	712	742	772	802	832	862	892	922
23	53	83	113	143	173	203	233	263	293	323	353	383	413	443	473	503	533	563	593	623	653	683	713	743	773	803	833	863	893	923
24	54	84	114	144	174	204	234	264	294	324	354	384	414	444	474	504	534	564	594	624	654	684	714	744	774	804	834	864	894	924
25	55	85	115	145	175	205	235	265	295	325	355	385	415	445	475	505	535	565	595	625	655	685	715	745	775	805	835	865	895	925
26	56	86	116	146	176	206	236	266	296	326	356	386	416	446	476	506	536	566	596	626	656	686	716	746	776	806	836	866	896	926
27	57	87	117	147	177	207	237	267	297	327	357	387	417	447	477	507	537	567	597	627	657	687	717	747	777	807	837	867	897	927
28	58	88	118	148	178	208	238	268	298	328	358	388	418	448	478	508	538	568	598	628	658	688	718	748	778	808	838	868	898	928
29	59	89	119	149	179	209	239	269	299	329	359	389	419	449	479	509	539	569	599	629	659	689	719	749	779	809	839	869	899	929
30	60	90	120	150	180	210	240	270	300	330	360	390	420	450	480	510	540	570	600	630	660	690	720	750	780	810	840	870	900	930

STAY AHEAD IN COLOR TV SERVICING—

## JOIN the P.O.M. (Photofact-of-the-Month) CLUB!


AND OWN THE COMPLETE PHOTOFACT COLOR TV LIBRARY

NOW! Only \$10 per month brings you 20% MORE PHOTOFACT coverage to keep you current—and you save more than \$60 per year!

- Get 6 new Photofact Sets each month
- 6 to 9 Color TV Folders monthly
- Covers at least 50 new chassis
- Includes b & w TV, FM-AM, AC-DC, Stereo Hi-Fi, Phonograph, and Record Changer models

GET GOING IN  
COLOR TV!

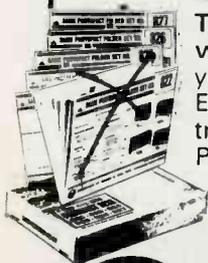GET THIS BIG "BONUS"! Now exclusively for P.O.M. Club members—a minimum of 10 "advance" TV schematics (mostly color) with each month's issue! Keeps you ahead on new model releases. Extra: Special File Cabinet deal with trial 6-month subscription to the P.O.M. Club.



JOIN  
P.O.M.

SEE YOUR SAMS DISTRIBUTOR FOR FULL INFORMATION, OR MAIL THE COUPON TODAY...

HOWARD W. SAMS & CO., Dept. PFF-3  
4300 W. 62nd St., Indianapolis, Indiana 46206

- Send Photofact-of-the-Month Club details
- Send full details on Library Offer and Easy-Buy Plan
- Send FREE 1968 PHOTOFACT Cumulative Index

My Distributor Is \_\_\_\_\_

Shop Name \_\_\_\_\_

Attn.: \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

# THE TROUBLESHOOTER

## Picture and Sound Missing


A Dumont Model RA-168 (PHOTOFACT Folder 216-2) that I am servicing will produce a beautiful picture for hours, then suddenly both the picture and sound disappear, leaving a blank but normal raster. Following are the only voltage clues I have obtained:

Tube and Element	Normal operation, no signal input	Picture and sound missing
RF amplifier grid	-1	-50
1st video IF grid	-3	-20
2nd video IF grid	0	-20
3rd video IF grid	0	-20
AGC clamber plates, pin 5	+3	-60
pin 6	-7	-60
AGC keyer plate	+1	-130

OTTO HAIM

Allentown, Pa.

The foregoing symptoms indicate that you are confronted with an "excessive AGC" problem. The grid cutoff voltage for a 6CB6 with 125 volts applied to the plate (the type of tube employed in the video IF's of this particular Dumont chassis) is approximately -6.5 volts—you now measure -20 volts. The cutoff voltage for the 6BK7A employed in the RF amplifier is about -7 or -8 volts with a plate voltage of 105 volts—you measure -50 volts.

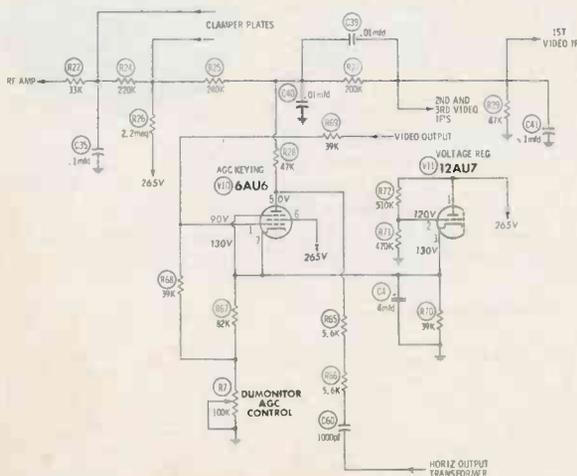

Recently we have received a number of letters requesting assistance with AGC problems; therefore, instead of merely indicating the most probable circuit defects, let's cover the operation of this particular keyed AGC system along with associated troubleshooting techniques.

The AGC keying stage (V10) is a coincidence amplifier; that is, it requires two input signals for conduction. One input signal is a horizontal pulse that is applied to the plate (pin 5) of V10 via R65, R66, and C60. The other input signal is a positive-going video signal applied to the grid (pin 1) of V10 from the plate circuit of the video output stage (via R69). The video signal contains positive-going horizontal sync pulses whose amplitude reflect the level of the received signal—i.e., the larger the received signal, the higher the amplitude of the horizontal sync pulses.

When both input signals arrive simultaneously at their respective tube elements (grid and plate), the tube conducts, with the amount of conduction depending on the level of the horizontal sync pulse at the grid and the setting of the R7, the AGC control. Both factors affect the bias of the keying tube. Note that the cathode of the keying tube is maintained at 130 volts by triode voltage regulator V11A. Adjusting R7 so that its wiper arm moves toward ground causes the DC bias at the grid of V10 to become more positive, increasing the conduction of the keying tube and, thus, developing more AGC voltage. Moving the wiper arm of R7 toward the top (as viewed on the schematic) produces an opposite effect.

When V10 conducts, a negative voltage is developed at its plate. The reason the voltage is negative instead of positive is because no positive DC potential is supplied to the plate; instead, the normal requirement of a positive plate for conduction (with respect to the cathode) is fulfilled by the highly positive horizontal pulse, which exists for only a relatively short period of time. The plate DC current path is from plate to ground via the voltage divider network of R28, R27, and R29. The AGC voltage supplied to the first three video IF stages is the negative DC potential present at the junction of R27 and R29, while the DC voltage that exists at the junction of R28, R27 and R25 is supplied to the tuner AGC line.

The function of the dual diode clamper in the tuner AGC line is to delay the application of AGC voltage to the tuner until a relatively strong input signal is received, thus preventing attenuation of weaker input signals in the tuner. Note that the tuner AGC line and clammers are tied to the 65-volt source through R26 and R24. When a relatively weak input signal is being received, the AGC voltage (negative) present at the junction of R28 and R25 is small compared to the positive potential that exists at the top of R26; consequently, with a positive potential at its plates, the clamper conducts and the tuner AGC line is maintained, or clamped, at a potential somewhere between .5 and 1 volt. However, when a relatively larger input signal is received, the negative voltage at the junction of R26 and R24 increases sufficiently to overcome the positive potential at the top of R26. With the positive potential removed from its plates, the clamper ceases to conduct, and the tuner RF amplifier grid is supplied with a negative voltage to reduce its gain.

When the input signal and bias requirements of V10 are satisfied and it conducts, coupling capacitor C60 is charged so that the side connected to V10 is negative. Capacitors C40, C39, and C41 are also charged at the same time. When conduction ceases, the negative charge on C60 bleeds off to ground through R66, R65, R28, R27 and R29. The charge on the other capacitors connected to the AGC line also bleeds off through their respective resistors, filtering and smoothing the AGC voltage. This concludes our brief discussion concerning the operation of

the keyed AGC system. Now let's do a bit of troubleshooting.

As stated before, the probable trouble causing the symptoms you describe is excessive AGC. The high level of negative voltage at the plate of the keyer tube (V10) and at the tuner amplifier and video IF grids is the basis for this conclusion. You could begin your troubleshooting by disabling the keyer (05-mfd, 1-kv capacitor from plate to ground will remove the horizontal pulse) and applying a clamping voltage from a negative voltage, or bias, source (variable, 0 to 45V). The picture and sound should return with the AGC (clamping) voltage at the proper level. However, the tube element voltage levels already mentioned preclude such action because they clearly localize the source of trouble. What remains is to consider the possible troubles that could upset the bias of the keyer, causing it to increase conduction and, thus, develop excessive AGC voltage. The most probable causes fall into two categories: (1) increased level of input signal at grid of V10 and (2) a defect within the keyer circuit itself that decreases the bias on the keyer tube.

Since the amount of AGC voltage developed by a normally operating AGC keyer stage is dependent on the level of the horizontal sync pulse present in the composite video signal applied to its grid, any overamplification of the video signal will cause an increase in the level of the horizontal sync pulse and, consequently, an increase in the AGC voltage. Normally, such overamplification is caused by a gassy video output tube (the keyer grid pulse is obtained from the plate circuit of the video output stage) or increased conduction of a video IF stage not controlled by AGC voltage—such as the 4th video IF in this chassis. (The increased conduction of such a stage could be caused by a circuit defect that reduces the bias of the stage or a defect that causes regenerative feedback and, consequently, oscillation). You can prove the existence of any one of the foregoing possibilities by checking the output of the video detector, or the amplitude of the waveform at the grid of the keyer—excessive signal amplitude will be found at either or both points. Further voltage checks within the suspected circuit or stage will isolate the specific cause.

Next, let's consider possibility No. 2—a defect within the keyer circuit itself that decreases the bias and, thus, causes increased conduction. If C4 is leaky or shorted, the voltage at the top of R70 will be reduced (to ground potential if C4 is shorted), causing the cathode of V10 to become more negative with relation to the grid, thereby reducing the bias of V10 and causing it to conduct more. A substantial decrease in the value of R71 will increase the bias on V11, reducing its conduction and the potential at the top of R70 and, in turn, will decrease the bias on the keyer tube. Other possible defects include a gassy keyer tube and an increase in the value of R68.


It is highly unlikely that a defective component on the AGC line itself is causing the trouble. Normally, a defect on the AGC line will dissipate the AGC voltage instead of increasing it; exceptions include a substantial increase in the value of R27 or R29. Also, an increase in the value (or complete opening) of R26 will kill the AGC delay or clamping action to the tuner, placing excessive AGC on the tuner RF amplifier and, thus, reducing the receiver sensitivity. Such a defect is characterized by a weak picture or washed out picture with excessive snow.

It is doubtful that a defective R7, R29 or R26 is the trouble in this particular case, because a defect in any one of these components would increase the AGC voltage of only the video IF's or the tuner—not both, as has happened in the situation under consideration.

From the preceding, it can be seen that an understanding of the basic operation of a circuit is essential to successful trouble analysis—anything less is simply guessing. ▲
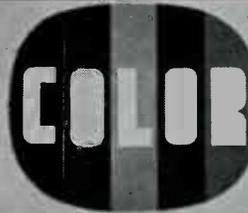
# 4 ways to increase your income

RCA Institutes, Inc. offers these four comprehensive home study courses especially designed to help build your income immediately!




**COLOR TV** Add profitable color TV to your skills with this home training course, newly revised to include information on the latest techniques, receiver circuitry and equipment. Train under the direction of RCA Institutes...experts in Color TV home study training.



**TRANSISTORS** You get the necessary background for semiconductor technology including characteristics of tunnel diodes, rectifiers and other solid state devices. Transistor trainer also available.



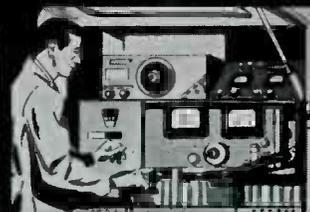**AUTOMATION ELECTRONICS** Trains you for the many applications of automation electronics in industry and government including Photoelectronics, Digital Computer Techniques, Synchros and Servomechanisms, Automatic Control Systems, and many more!



**MOBILE COMMUNICATIONS** Trains you to service and maintain 2-way radio communications on land, sea, and air! Gives you the technical foundation for space communications!

Take advantage of RCA's Liberal Tuition Plan. You only pay for lessons you order; and have no long-term obligations. Licensed by New York State Education Department. Approved for Veterans.



■ ■ ■ SEND THIS COUPON NOW FOR COMPLETE FREE INFORMATION ■ ■ ■

RCA INSTITUTES, INC. Home Study School, Dept. PF-38  
320 West 31st Street, New York, N.Y. 10001  
Without obligation, rush me free information on the following RCA Home Training Course: COLOR TV \_\_\_\_\_ TRANSISTORS \_\_\_\_\_ MOBILE COMMUNICATIONS \_\_\_\_\_  
AUTOMATION ELECTRONICS \_\_\_\_\_

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_



# TEST EQUIPMENT

## MANUFACTURERS' *addresses*

The following is a list of manufacturers who are active in the service equipment industry. We have purposely left out the names of those manufacturers who deal exclusively with the laboratory and production markets. In compiling this list, every effort has been made to insure completeness and accuracy. Nevertheless, because of changes of address, corporate names, etc., this listing is not as complete as we would like it to be. PF REPORTER will welcome any corrections to this list.

**Amphenol Distributor Division**  
2875 South 25th Avenue  
Broadview, Illinois 60153  
B & K division of


**Dynascan Corporation**  
1801 W. Belle Plaine Ave.  
Chicago, Illinois 60613  
**Blonder-Tongue Laboratories, Inc.**  
9 Alling Street  
Newark, New Jersey 07102  
**Channel Master Corporation**  
Ellenville, New York 12428  
**Components Specialties, Inc.**  
101 Buffalo Avenue  
Freeport, L. I., N. Y. 11520  
**Eico Electronic Instrument Co., Inc.**  
Malta Street & Wortman Ave.  
Brooklyn, New York 11207  
**Electronic Measurements Corp.**  
625 Broadway  
New York, New York 10012  
**Hallmark Instruments**  
6612 Denton Dr.  
Dallas, Texas 75235

**Heath Company**  
Benton Harbor, Mich. 49022  
**The Hickok Electrical Instrument Co.**  
10514 DuPont Avenue  
Cleveland, Ohio 44108  
**Jackson Electrical Instrument Co.**  
35 Windsor Avenue  
Mineola, New York 11501  
**Jerrold Electronics Corporation**  
401 Walnut Street  
Philadelphia, Pennsylvania 19105  
**Karg Laboratories, Inc.**  
162 Ely Avenue  
South Norwalk, Conn. 06854  
**Lampkin Laboratories, Inc.**  
Bradenton, Florida 33505  
**Leader Electronics Corp.**  
101-103 Rome Street  
Farmingdale, L. I., N. Y. 11735  
**Lectrotech, Inc.**  
1221 W. Devon Ave.  
Chicago, Ill. 60626  
**Mercury Electronics Corp.**  
315 Roslyn Road  
Mineola, New York 11501  
**Pace Communications Corp.**  
24049 Frampton Ave.  
Harbor City, California 90701  
**Precise Electronics division of Designatronics Inc.**  
Mineola, L. I., N. Y. 11501  
**Precision Apparatus division of Dynascan Corporation**  
1801 W. Belle Plaine Ave.  
Chicago, Ill. 60613  
**Precision Electronics, Inc.**  
9101 King Street  
Franklin Park, Illinois 60131  
**Radio Corporation of America Electronic Components and Devices**  
Harrison, New Jersey 07029  
**Seco Mfg. Co.**  
1001 S. 2nd St.  
Hopkins, Minn. 44343  
**Sencore, Inc.**  
426 South Westgate Drive  
Addison, Illinois 60101  
**Simpson Electric Company**  
5200 West Kinzie Street  
Chicago, Illinois 60644  
**Sprague Products Company**  
North Adams, Massachusetts 01247  
**The Triplett Electrical Instrument Co.**  
Bluffton, Ohio 45817  
**Waterman Instrument Corporation**  
400 South Warminster Road  
Hatboro, Pa. 19040  
**Workman Electronic Products, Inc.**  
Box 3828  
Sarasota, Fla. 33578

THE BEST ANTENNA INSTALLATIONS START WITH . . .

## *South River* QUALITY MOUNTING ACCESSORIES

THE MOST COMPLETE LINE IN THE INDUSTRY

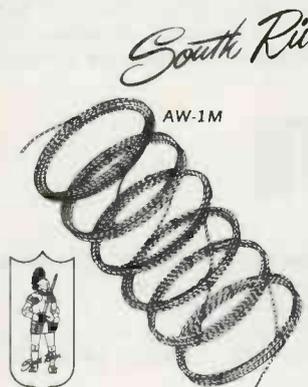

SEND FOR COMPLETE CATALOG

- ALCLAD ALUMINUM GUY WIRE**
- High quality, 7 strand, 17 gauge, high strength, tight twist, tempered and normalized for maximum flexibility.
  - Breaking strength: Over 500 lbs.
  - Tight twist keeps wind effect to a minimum.
  - Special Alclad process provides protection against corrosion, weathering, chemical fumes and salt air.
  - Pre-set curvature on each loop prevents snarling and keeps wire under control during installation.

AT SOUTH RIVER QUALITY IS OUR MOST IMPORTANT PRODUCT

SOLD THROUGH DISTRIBUTORS

SOUTH RIVER METAL PRODUCTS CO., INC. / SOUTH RIVER, N. J. 08882

Circle 32 on literature card

**GENERAL ELECTRIC'S  
NEW  
HEADACHE  
SOLVER**

**509**

**Passivated  
Rectifier**

- Up to 1000 volts PIV
- Transient Voltage Protection
- Passive Junction
- All Diffused Structure
- High Surge Current Capacity
- Hermetic Sealed
- Dual Heat Sink Design
- Low Thermal Impedance

**TYPICAL APPLICATIONS**

- Freewheeling Rectifier
- TV & Radio Power Supplies
- Time Delay Circuits
- Communications Equipment
- Power Logic Circuits
- SCR Trigger Circuits
- ARC Suppression
- Small Portable Appliances
- Battery Chargers
- General Purpose Power Supplies
- TV Damper Diodes
- Low Level Limiters

See Your Authorized GE Distributor For  
All Your Semiconductor Requirements

**GENERAL ELECTRIC**

**INDEX TO  
ADVERTISERS**

March, 1968

B & K Mfg. Co. Div. of Dynasean Corp.....48

Borden Chemical Co., Krylon Div. ....34

Bussmann Mfg. Div., McGraw-Edison Co. ...25

Chemtronics, Inc. ....71

Cleveland Institute of Electronics .....11

Cornell-Dubilier ..... Cover 2

Electronic Measurements Corp. .... 4

Electro-Voice, Inc. ....46

GC Electronics, Div. of  
Hydrometals, Inc. ....31, 68

Gem City Tuner Repair Service .....10

General Electric Co. ....47, 71

Heath Co. ....23

Jensen Mfg. Div., The Muter Co. ....69

Leader Electronics Corp. .... 8

Lectrotech, Inc. .... 6

Littelfuse, Inc. .... Cover 4

National Radio Institute .....56

Olson Electronics, Inc. ....71

Oxford Transducer Co. ....44

Quam Nichols Co. ....10

Quietrole Co. ....69

RCA Institutes, Inc. ....65

RCA Parts & Accessories .....21

RCA Receiving Tubes ..... Cover 3

RCA Sales Corp. .... 9

RMS Electronics, Inc. ....58

S & A Electronics, Inc. ....35

Howard W. Sams & Co., Inc. ....35, 63

SENCORE, Inc. ....12, 16, 33, 37, 67

South River Metal Products Co., Inc.....66

Sprague Products Co. .... 3

Superior Tuner Service .....70

Sylvania Electric Products, Inc. .... 5

Texas Crystals .....70

Tuner Service Corp. .... 7

Winegard Co. .... 1

Yeats Appliance Dolly Sales Co. .... 4

Zenith Sales Corp. ....38, 39, 67

**THERE'S ONLY ONE  
COLOR LUBE®**

That's  
**CHEMTRONICS**  
INSIST ON IT!  
ACCEPT NO IMITATIONS



**NON-DRIFT  
COLOR TV  
TUNER CLEANER**

TEST AFTER TEST HAS PROVEN  
**COLOR LUBE**

- To clean better
- To be safe on plastics used in TV sets
- Non-flammable
- To cause no drifting

**\$2.39**  
Net



*Another First*  
**SUPER  
FROST AID**

Cools Faster • Leaves No Liquid Residue  
SUPER FROST AID is a faster circuit freezer designed to locate intermittent components without leaving a liquid residue. 2.79 Net

No. 1550



BROOKLYN

N. Y. 11236

Circle 40 on literature card

March, 1968/PF REPORTER 71

**Olson**



**FREE**

Fill in coupon for a FREE One Year Subscription to OLSON ELECTRONICS' Fantastic Value Packed Catalog—Unheard of LOW, LOW PRICES on Brand Name Speakers, Changers, Tubes, Tools, Stereo Amps, Tuners, CB, Hi-Fi's, and thousands of other Electronic Values. Credit plan available.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_


GIVE ZIP CODE \_\_\_\_\_

If you have a friend interested in electronics send his name and address for a FREE subscription also.

**OLSON ELECTRONICS, INC.**

831 S. Forge Street Akron, Ohio 44308

Circle 39 on literature card

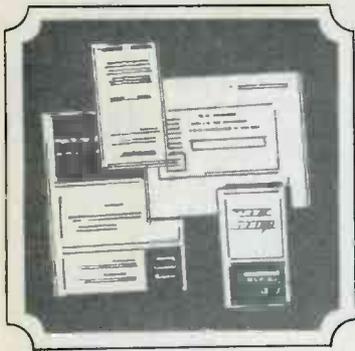

# \$ FREES \$

## CATALOG AND LITERATURE SERVICES

\*CHECK "INDEX TO ADVERTISERS" FOR FURTHER INFORMATION FROM THESE COMPANIES

### ANTENNAS

100. **ALLIANCE**—Colorful 4-page brochure describing in detail all the features of Tenna-Rotors.
101. **BLONDER-TONGUE**—Flyer sheet on new Colortap outlet plates and plugs for 300-ohm lead-in.
102. **DELHI**—Twelve-page catalog introducing a complete new line of home TV towers, ham towers, citizens-band towers, masts, and telescoping masts.
103. **FINNEY**—4-color brochure with description and technical details on new Finco Color Spectrum, frequency-dependent antennas for UHF-VHF-FM, VHF-FM, and UHF. Form 20-413.
104. **JERROLD**—New 4-page, full-color catalog describes the new Paralog Plus antennas.
105. **JFD**—Color Laser and LPV antenna brochures. New, 1968 dealer catalog covering complete line of log-periodic, outdoor antennas, rotators, and accessories.
107. **WINEGARD**—Data sheet on Color-Tracker UHF antenna; folders on complete antenna line and MATV products.\*
108. **G. F. WRIGHT STEEL AND WIRE CO.** Flyer gives specifications and packaging data for steel and aluminum guy wire.

### AUDIO

109. **ACTION SYSTEMS CO.**—Brochure 715A, "SOUND BUSINESS," tells how to enter paging and intercom business.
110. **ATLAS SOUND**—Form #PP-2537 describes the Banshee voice speaker for music groups.
111. **BELL P/A**—Complete specifications, operating instructions, and schematics on the new Carillon series amplifiers.
112. **ELECTRO-VOICE**—Pocket-size guide-books for microphones, hi-fi loudspeakers, and hi-fi systems.\*
113. **NUTONE**—24-page booklet describes built-in stereo, intercom, and radio systems.
114. **OAKTRON**—Brochure #673 describes the PVS-800 acoustic-lens speaker.
115. **OXFORD TRANSDUCER**—Bulletin A-109 features speaker installation in automobiles, hospitals, and recreation rooms.\*
116. **RACON**—Catalog C665T on horns, drivers, sound columns, and accessories.
117. **RECOTON**—42-page catalog and reference guide gives information on phonograph needles, tape and accessories, and record accessories.
118. **UTC**—Brochure describes Maximus line of hi-fi speakers.

### COMMUNICATIONS

119. **AMPHENOL**—2-color spec sheets on new Model 650 CB transceivers and Model C-75 hand-held transceiver.
120. **COMCO**—Brochure on marine radiotelephone models 626 and 802.

121. **CUSH CRAFT**—Full-line catalog, CB-68, of CB base-station antennas and accessories.
122. **DOBBS/STANFORD**—1968 catalog of microphones, headphones, and wireless headphones.
123. **MOSLEY**—Catalogs on antennas for TV/FM, CB, and ham use.

### COMPONENTS

124. **BELDEN**—Catalog 867, a 56-page catalog of the complete Belden line.
125. **BUSSMAN**—12-page bulletin, SFUS, listing the complete line of BUSS and FUSE-TRON small-dimension fuses by size and type also indicates proper fuseholder and shows list prices.\*
126. **CENTRALAB**—24-page replacement parts catalog 33G1.
127. **CORNELL-DUBILIER**—New 4-page Color-lytic list.\*
128. **MALLORY**—Bulletin 4-82 describes radial- and axial-lead tantalum capacitors.
129. **MILLER**—Catalog 167, a 156-page general catalog with complete cross-reference guide.
130. **LITTELFUSE**—Pocket-sized TV circuit-breaker cross reference, CBCRP, gives the following information at a glance: manufacturer's part number, price, color or b-w designation, and trip ratings.\*
131. **QUAM-NICHOLS**—Catalog No. 67 has information on the entire line.\*
132. **SPRAGUE**—C618, the 1968 general-line catalog, is offered.\*
133. **TEXAS CRYSTALS**—12-page catalog of crystals including engineering data, specifications, and prices.\*
134. **WORKMAN**—46-page catalog #100 of resistors, fuses, circuit breakers, brighteners, adaptors, and test accessories. Cross-reference charts are included.

### SERVICE AIDS

135. **CASTLE TUNER**—Fast overhaul service on all makes and models of television tuners. Shipping instructions, labels, and tags are also included.
136. **GC**—FR-67, the full-line catalog.\*
137. **MID-STATE TUNER SERVICE**—Flyer describes 24-hour tuner service.
138. **PERMA-POWER**—Technical Bulletin LCC-502 describes brighteners for color CRT's.
139. **T.V. TUNER SERVICE**—Brochure lists cost and mailing instructions for 24-hour service on any make tuner. Repair tags and shipping labels included.

### SPECIAL EQUIPMENT

140. **ATR**—Literature about DC-AC inverters up to 600 watts load.
141. **COMPONENTS SPECIALTIES**—Flyer on SPECO Fire Guard is offered.
142. **SONIC INDUSTRIES**—Flyer describes wireless converters for intercepting police and fire calls.
143. **SOUNDOLIER**—Specifications of 2-amp and ½-amp DC power supplies.

144. **STANDARD KOLLSMAN**—Flyers describe replacement TV tuners, built-in UHF converters, external UHF-to-VHF and VHF-to-VHF converters, and contact-cleaner kits.
145. **TERADO**—Flyer describes voltage booster for portable electric tools.

### TECHNICAL PUBLICATIONS

147. **CLEVELAND INSTITUTE OF ELECTRONICS**—Free illustrated brochure describing electronics slide rule, four-lesson instruction course, and grading service.\*
148. **RCA INSTITUTES**—New 1968 career book describes home study programs and course in television (monochrome and color), communications, transistors, and industrial and automation electronics.\*
149. **SAMS, HOWARD W.**—Literature describing popular and informative publications on radio and TV servicing, communications, audio, hi-fi, and industrial electronics, including special new 1968 catalog of technical books on every phase of electronics.\*

### TEST EQUIPMENT

150. **B & K**—Bulletin ST-32B describes test-equipment line.\*
151. **COLETRONICS**—Flyers give specifications and prices of tube-socket adapters.
152. **EICO**—New spec sheet describes model 100A4 multimeter with DC sensitivity of 100K ohms per volt.
153. **HICKOK**—Quick-reference catalog No. 67D gives brief descriptions and prices for complete test-equipment line.
154. **LECTROTECH**—Two-color catalog sheet on new Model V6-B color bar generator gives all specs and is fully illustrated.\*
155. **MERCURY**—All-new 16-page test-instrument catalog.
156. **PRECISION**—Bulletin PST-35 describes test-equipment line.
157. **SECO**—Operating manual for the HC8 in-circuit current checker for horizontal-output tubes.
159. **SENCORE**—New 12-page catalog on all SENCORE products.\*
160. **SIMPSON**—Reprint, "A Guide to the Selection of Multimeters," explains how to evaluate multimeters before you buy.
161. **TRIPLETT**—New catalog 52-T describes complete line of VOM's, test equipment, and accessories. The Model 600, transistorized volt-ohmmeter is featured.

### TOOLS

162. **ARROW**—Catalog sheet showing 3 staple-gun tackers designed for fastening wires and cables up to ½" diameter.
163. **ENTERPRISE DEVELOPMENT**—Brochure from Endeco demonstrates improved desoldering and resoldering methods for speeding and simplifying operations on PC boards.
164. **SWING-O-LITE**—Catalog sheet on Models BBM-9 and BB45 bench lamps.
165. **UNGER**—Information sheets and technical data for various soldering irons and equipment.
166. **VACO**—Catalog SD-119 describes Snap Driver kit featuring 30 blades that fit one handle.
167. **XCELITE**—Bulletin N867 describes hollow-shaft nutdrivers which speed lock-nut/screw adjustments.

### TUBES AND TRANSISTORS

168. **GENERAL ELECTRIC**—Entertainment semiconductor almanac, ETR-4311C, and picture-tube replacement guide, ETR-702K, are offered.\*
169. **INTERNATIONAL RECTIFIER**—New MRO (maintenance, repair, and operation service) catalog has 12 pages of semiconductor listings and a 4-page glossary.
170. **MOTOROLA**—HEP cross-reference guide lists approximately 12,000 semiconductor types.
171. **RCA**—PIX-300, a 12-page product guide for RCA picture tubes covering both color and black-and-white.\*
172. **SEMITRONICS**—A zener-diode replacement chart is available.

# USE THE HANDY CARD BELOW TO OBTAIN FREE CATALOGS & LITERATURE

As a service to its readers, PF REPORTER makes this postpaid card available for your convenience in obtaining current manufacturers' literature.

To use the card simply:

- a. Circle the numbers corresponding to the numbers of the items appearing either in the "Catalog & Literature" department or in the "Product Report" department.
- b. Print your name and address and check your occupation.
- c. Include ZIP code—requests may not be filled without it.
- d. Tear out lower half of this insert and place in mailbox.

Note the deadline date — Requests received after this cannot be handled.

Subject Index on Reverse Side

MARCH, 1968  
OFFER EXPIRES JUNE 1, 1968

1 2 3 4 5 6 7 8 9 10 11  
23 24 25 26 27 28 29 30 31 32 33  
45 46 47 48 49 50 51 52 53 54 55  
67 68 69 70 71 72 73 74 75 76 77 7  
89 90 91 92 93 94 95 96 97 98 99 10  
111 112 113 114 115 116 117 118 119 120 121 122  
133 134 135 136 137 138 139 140 141 142 143 144  
155 156 157 158 159 160 161 162 163 164 165 166

Print plainly or type below

Name \_\_\_\_\_

Firm \_\_\_\_\_

Firm Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Did you receive this issue through  
 Distributor  Subscription

## Subscription Offer

Enter my subscription to PF REPORTER

3 Years \$10.00  2 Years \$8.00  1 Year \$5.00

Bill Me  Remittance Enclosed

Extend Present Subscription

**BOOK REVIEW**

Lasers and Masers .....10

**GUIDES**

Test Equipment Manufacturers .....66

**PHOTOFACT BULLETIN**

—936 through 941 .....44

Tube Substitution Supplement ..... a

**SAFETY**

Avoiding electric shock .....43

**SERVICING**

Theory of keyed AGC .....TS 64

**SYMFACT**

Balanced diode chroma demodulator .....59

**TEST EQUIPMENT**

Bridge Circuits

—capacitance bridge .....53

—inductance bridge .....57

Features of available equipment

—audio test equipment .....22

—color generators .....14

—communications test equipment .....27

—meters .....13

—signal generators .....15, 23

Jackson Model 810 Transistor

Tester .....NTE 45

Precision Apparatus

Model V-95 VTVM .....NTE 46

Servicing Test Equipment

—meters .....29

—oscilloscopes .....17

**VIDEO SPEED SERVICING**

Motorola STS-914YA, B .....49

Zenith 25NC37 .....51

(Note: Code letters NTE and TS indicate Notes on Test Equipment and The Troubleshooter, respectively.)

FIRST CLASS

PERMIT NO. 217

Clinton, Iowa

**PLY MAIL**

ed in the United States

**PAID BY—**

**RTER**


**A 52732**
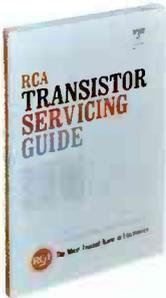
# Put yourself in the profit picture

All the items shown are available from your local participating RCA Tube Distributor with your purchases of RCA receiving tubes and picture tubes.




**FABULOUS ELECTRIC RAZORS FROM SCHICK (1A1694M) (1A1694L)**—For men, the Schick "Traveler". For ladies, the "Lady Petite".



**RCA TRANSISTOR SERVICING GUIDE (1A1673)**—This very important Guide will be indispensable to you in your understanding of transistor theory, amplifier principles and considerations and servicing!

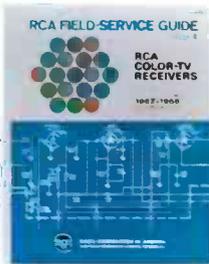A complete Subscription to RCA Service Notes for 1968 (1A1687)



**THE RCA FIELD SERVICE GUIDE FOR RCA COLOR RECEIVERS FOR 1967 AND 1968 (ERT-201)**—This Guide helps you perform all adjustments on 1967 and 1968 RCA Color TV Receivers that can be performed in the home.



**RCA HOT CHECK LAMP (1A1677)**—Adjust the horizontal output tube current of a color TV set quickly and easily, to prevent premature tube failure and the resulting call back.



SAFETY GOGGLES (1A1691)



MODERN CLOCK DISPLAY (1A1683)



**IMPERIAL NON-STICK TEFLON\* COATED CUTLERY (1A1697) (1A1696) (1A1698)**—A 6" French Chef's knife, a 7½" slicing and carving knife, and a spreader-trimmer blade.

\*TEFLON is a DuPont approved finish



SATIN COLOR TV SERVICE BANNER (1A1686)



INDOOR THERMOMETER (1A1689)



**PORTA-FILES FROM HAMILTON SKOTCH (1A1699) (1A1700)**—The Porta-File

is a great way to organize your important records and valuable papers. Porta-File and Kabinette combination is even better.



**REFLECTIVE SAFETY BUMPER STRIP (1D1335)**—Offers day and night visibility for a service message on back of truck. 3" x 12".



VINYL COUNTER CHANGE MAT (1A1684)

**WINDOW DISPLAY ON RCA RECEIVING TUBES AND PICTURE TUBES (1A1685)**—33½" high; 19¼" wide; 6" deep.

Available through your local participating RCA Tube Distributor with your purchases of RCA Receiving Tubes and Picture Tubes. See him today!  
RCA Electronic Components, Harrison, N.J.

# RCA

# Introducing a Complete Line of Littelfuse Quality Circuit Breakers



Actual Size  
1 3/4" x 1 3/16" x 1/2"

## Exact replacement from factory to you

Designed for the protection of television receiver circuits, the Littelfuse Manual Reset Circuit Breaker is also ideally suited as a current overload protector for model railroads and power operated toy transformers, hair dryers, small household appliances, home workshop power tools, office machines, small fractional horsepower motors and all types of electronic or electrical control wiring.

# LITTELFUSE

DES PLAINES, ILLINOIS

Circle 41 on literature card