




Electronic Servicing

Formerly PF Reporter


TUBE CIRCUIT OPERATION...

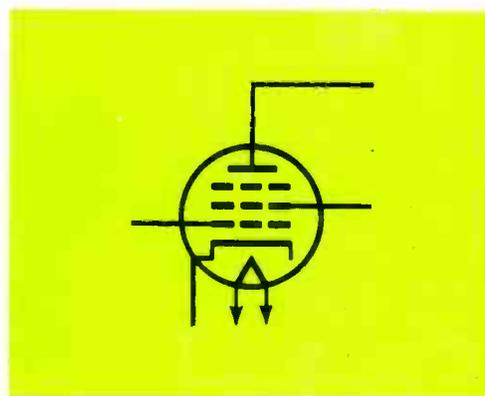How defects upset voltages and parameters page 34




AGC SYSTEMS...

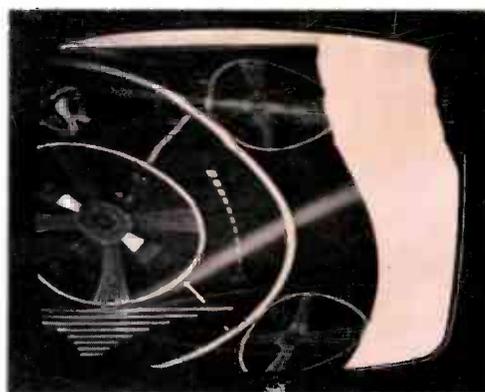Servicing tube, hybrid and solid-state types page 42



HOME ANTENNA SYSTEMS...

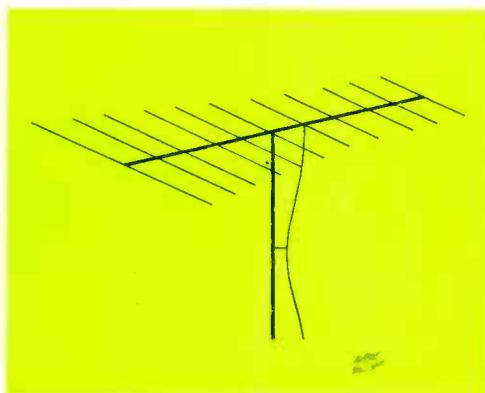Basic facts about characteristics and installation page 50



Index of 1969 Content page 62

The first and only solid-state test equipment guaranteed for 5 years.

Now EICO, because of its emphasis on reliability in engineering and manufacture, offers the industry this breakthrough.

EICO's new line of solid-state test equipment comes with an unprecedented 5-year guarantee of performance and workmanship. (Send

for full details of this EICO 5-year GUARANTEE on factory-assembled instruments.)

Additional advanced features include: new functional design, new color-coordinated esthetics, new PC construction, new easier-to-build kit designs.

New EICO Solid-State Test Equipment



EICO 240 Solid-State FET-VOM \$59.95 kit, \$79.95 wired.

One all-purpose DC/AC OHMS Uniprobe®. Reads 0.01V to 1 KV (to 30 KV with optional HVP probe). 7 non-skip ranges, in 10 dB steps. AC or battery operated. RMS & DCV: 0-1, 3, 10, 30, 100, 300, 1000V P-P ACV: 0-2.8, 8.5, 28, 85, 280, 850, 2800V. Input Z: DC, 11 M Ω ; AC, 1 M Ω . Response 25 Hz to 2 MHz (to 250 MHz with optional RF probe). Ohmmeter reads 0.2 to 1 M Ω in 7 ranges. 4 1/2" 200 μ A movement. HWD: 8 1/2", 5 3/4", 5", 6 lbs.

EICO 242 Solid-State FET-TVOM \$69.95 kit, \$94.50 wired.

All the versatility of the EICO 240 plus: AC/DC Milliammeter, 1 ma to 1000 ma in 7 non-skip ranges; single all-purpose DC/AC-Ohms — MA Uniprobe®; and large 6 1/2" 200 μ A meter movement.

EICO 150 Solid-State Signal Tracer \$49.95 kit, \$69.95 wired.

Multi-purpose troubleshooter for TV/FM/AM & Audio Equipment. Independent RF Audio inputs. Speaker and meter output indicators. 400 mW continuous power output. Substitution amplifier, output transformer, speaker. Input for rated output: 1 mV RF, 63 mV audio.

Hum 60 dB below 400 mW, 105-132 VAC, 50/60 Hz, 5VA. HWD: 7 1/2", 8 1/2", 5", 6 lbs.

EICO 330 Solid-State RF Signal Generator. \$59.95 kit, \$84.50 wired.

5 fundamental bands 100 kHz to 54 MHz. Vernier control 0-100%. Output 300,000 μ V into 50-Ohm load. External signal modulation or internal 400 Hz, 0 to 100%. 105-132 VAC, 50/60 Hz, 1.7 VA. HWD: 7 1/2", 8 1/2", 5", 5 lbs.

EICO 379 Solid-State Sine/Square Wave Generator. \$69.95 kit, \$94.50 wired.

5 sine wave and 4 square wave bands. Low distortion Sultzer feedback FET circuit. Sine: 20 Hz to 2 MHz; 0-7.5V rms into hi-Z, 0-6.5V into 600 ohms Max. distortion 0.25%. Square: 20 Hz to 200 kHz; 0-10V p-p into hi-Z, pos. direction, zero ground. Rise time at 20 kHz less than 0.1 μ sec. 105-132 VAC, 50/60 Hz, 10VA. HWD: 7 1/2", 8 1/2", 8 1/2", 9 lbs.

New EICO High Performance Instruments



- EICO 385 — Solid-State Portable Color Generator \$79.95 Kit, \$109.95 Wired.
- EICO 465 — Wideband Vectorscope/Oscilloscope \$179.95 Kit, \$249.95 Wired.
- EICO 1025 — Solid-State Power Supply \$79.95 Kit, \$119.95 Wired.
- EICO 443 — Semiconductor Curve Tracer \$69.95 Kit, \$99.95 Wired.
- EICO 633 — CRT Tester & Rejuvenator \$69.95 Kit, \$99.95 Wired.
- EICO 635 — Portable Tube Tester \$44.95 Kit, \$69.95 Wired.

New EICO Probes for the Pros

Hi-Voltage Probe HVP-5, Wired \$19.95.

Convenient built-in voltmeter. Barrier sections isolate HV tip from handle and meter. Measures up to 30 KV. Lightweight, compact.

Solid-State Signal Injector Probe PSI-1, Kit \$5.95, Wired \$9.95.

Pen-size, 1-ounce, self-powered signal generator. Frequency range from 1kHz to 30MHz, with harmonics. Clip it to your pocket — ideal for signal tracing in the field.

Solid-State Signal Tracer Probe PST-2, Kit \$19.95, Wired \$29.95.

Flashlight-size, 2.2oz, self-powered. Hi-gain amplifier, 50Hz to 200MHz with demod tip. Input Z: 3500 Ω , 35K Ω , 350K Ω ; Output: 0.3 p-p volts. Noise —45dB. Distortion <5%. Complete with earphone, all probe tips, AA battery, pocket clip.



SEND FREE 1970 CATALOG

Name _____
Address _____
City _____ State _____ Zip _____



EICO Electronic Instrument Co., Inc.
283 Malta Street, Brooklyn, N.Y. 11207
EICO Canada Ltd.
20 Millwick Drive, Weston, Ontario

Circle 1 on literature card

The absolute end of an old fear.

The new B&K Sweep/Marker Generator does for TV sets what no other instrument or instruments can do. It makes alignment of color, as well as black & white TV, simpler and easier than ever.

Remember all your old fears about TV alignment (especially color)? Well, now you can forget them!

In the past, a marker generator and a separate sweep generator were used with a marker adder and a bias supply. All four of these now are combined in one easy-to-use instrument.

(We've made benchwork so much simpler by doing away with the need for hooking together a lot of cables and costly instruments.)

The Sweep/Marker Generator is both an instrument and a guide. As a guide, the bandpass

and chroma bandpass curves are visually reproduced and the individual markers are clearly indicated by lights—right on the front panel—for quick, easy reference.

As an instrument, the Sweep/Marker Generator not only generates the marker frequencies (all crystal controlled), but also sweeps the chroma bandpass, TV-IF, and FM-IF frequencies.

See it soon at your B&K distributor or write us for advance information on the product that makes TV alignment procedures of old a fearless operation: simple, fast, accurate. The new Sweep/Marker Generator, Model 415, Net: \$399.95



PRODUCT of DYNASCAN CORPORATION
1801 W. Belle Plaine - Chicago, Illinois 60613
Where electronic innovation is a way of life.



New B&K Sweep/Marker Generator.

Circle 4 on literature card

Electronic Servicing

Formerly PF Reporter

in this issue...

18 Dale's Service Bench: How to Make Adjustments in FM Multiplex Systems. Allan Dale explains the step-by-step procedure for adjusting the multiplex section of a stereo FM receiver, and briefly reviews the basic operation of such units.

24 Test Equipment Input Impedance and Its Effects. How resistive and reactive components in the input circuits of test instruments affect measurements. **by Robert G. Middleton.**

34 How Defects Affect the Operating Voltages and Parameters of Tube Circuits. An analysis of abnormal voltages on tube elements—their common causes and how they affect the operation of the circuit. **by Bruce Anderson.**

39 Tube Substitution Supplement. Characteristics, basing diagrams and recommended substitutes of recently introduced tubes.

42 Servicing AGC—Tube, Hybrid and Solid State. A detailed description of the operation of the three common designs of automatic gain control circuits employed in today's TV receivers, along with proven troubleshooting methods. **by Carl Babcoke.**

50 Facts About Basic Home TV Antenna System Components. A review of the fundamental characteristics of basic designs of TV antennas and lead-in, plus tips on installation. **by Bruce Anderson.**

62 Index of 1969 Content.

DEPARTMENTS

Letters to the Editor	4	Antenna Systems Report . . .	32
Electronic Scanner	9	Troubleshooter	48
Test Equipment Report . . .	12	Product Report	56
Syncure	22	Catalog and Literature . . .	60
PHOTOFACT BULLETIN	31	Advertisers' Index	61

Second class postage paid at Kansas City, Mo. and additional mailing offices. Published monthly by INTERTEC PUBLISHING CORP., 1014 Wyandotte St., Kansas City, Mo. 64105. Vol. 20, No. 1. Subscription rates \$5 per year in U.S., its possessions and Canada; other countries \$6 per year.

Copyright, 1970, Howard W. Sams & Co., Inc. All rights Reserved. Material may not be reproduced or photocopied in any form without written permission of publisher.

EDITORIAL

GEO. H. SEFEROVICH, Director
J. W. PHIPPS, Managing Editor
CARL BABCOKE, Technical Editor
WENDALL BURNS, Business Operations Editor
CAROLYN TICE, Editorial Production
MARY M. SYMON, Editorial Assistant
DUDLEY ROSE, Art Director

CONTRIBUTING AUTHORS

Bruce Anderson
Allan Dale
Wayne Lemons
Robert G. Middleton

TECHNICAL CONSULTANT

JOE A. GROVES

EDITORIAL ADVISORY BOARD

LES NELSON, Chairman
Howard W. Sams & Co., Indianapolis

CIRCULATION

R. VINCENT WARD, Director
EVELYN RODGERS, Manager

ADVERTISING SALES

Kansas City, Missouri 64105
Tele: 913/888-4664
E. P. LANGAN, Director
R. JACK HANCOCK, Manager
S. F. WILSON, Production

REGIONAL ADVERTISING SALES OFFICES

Indianapolis, Indiana 46280

ROY HENRY
2469 E. 98th St.
Tele: 317/846-7026

New York, New York 10019

CHARLES C. HORNER
3 W. 57th St.
Tele: 212/688-6350

Mission, Kansas 66208

JAKE STOCKWELL
C. H. Stockwell Co.
4916 W. 64th St.
Tele: 913/722-4417

Los Angeles, California 90005

JOHN D. GILLIES
3600 Wilshire Blvd., Suite 1510
Tele: 213/383-1552

London W. C. 2, England

JOHN ASHCRAFT & CO.
12 Bear Street
Leicester Square
Tele: 930-0525

Amsterdam C. Holland

JOHN ASHCRAFT & CO.
W.J.M. Sanders, Mgr.
for Benelux & Germany
Herengracht 365
Tele: 020-240908

Paris 5, France

JOHN ASHCRAFT & CO.
9 Rue Lagrange
Tele: 033-2087

Tokyo, Japan

INTERNATIONAL MEDIA
REPRESENTATIVES LTD.
1, Shiba-Kotohiracho, Minatoku
Tele: 502-0656



ELECTRONIC SERVICING (with which is combined PF Reporter) is published monthly by Intertec Publishing Corp., 1014 Wyandotte Street, Kansas City, Missouri 64105.


Subscription Prices: 1 year—\$5.00, 2 years—\$8.00, 3 years—\$10.00, in the U. S. A., its possessions and Canada.

All other foreign countries: 1 year—\$6.00, 2 years—\$10.00, 3 years—\$13.00. Single copy 75¢; back copies \$1.



Robert E. Hertel, Publisher
Intertec Publishing Corp.
Subsidiary of Howard W. Sams & Co., Inc.

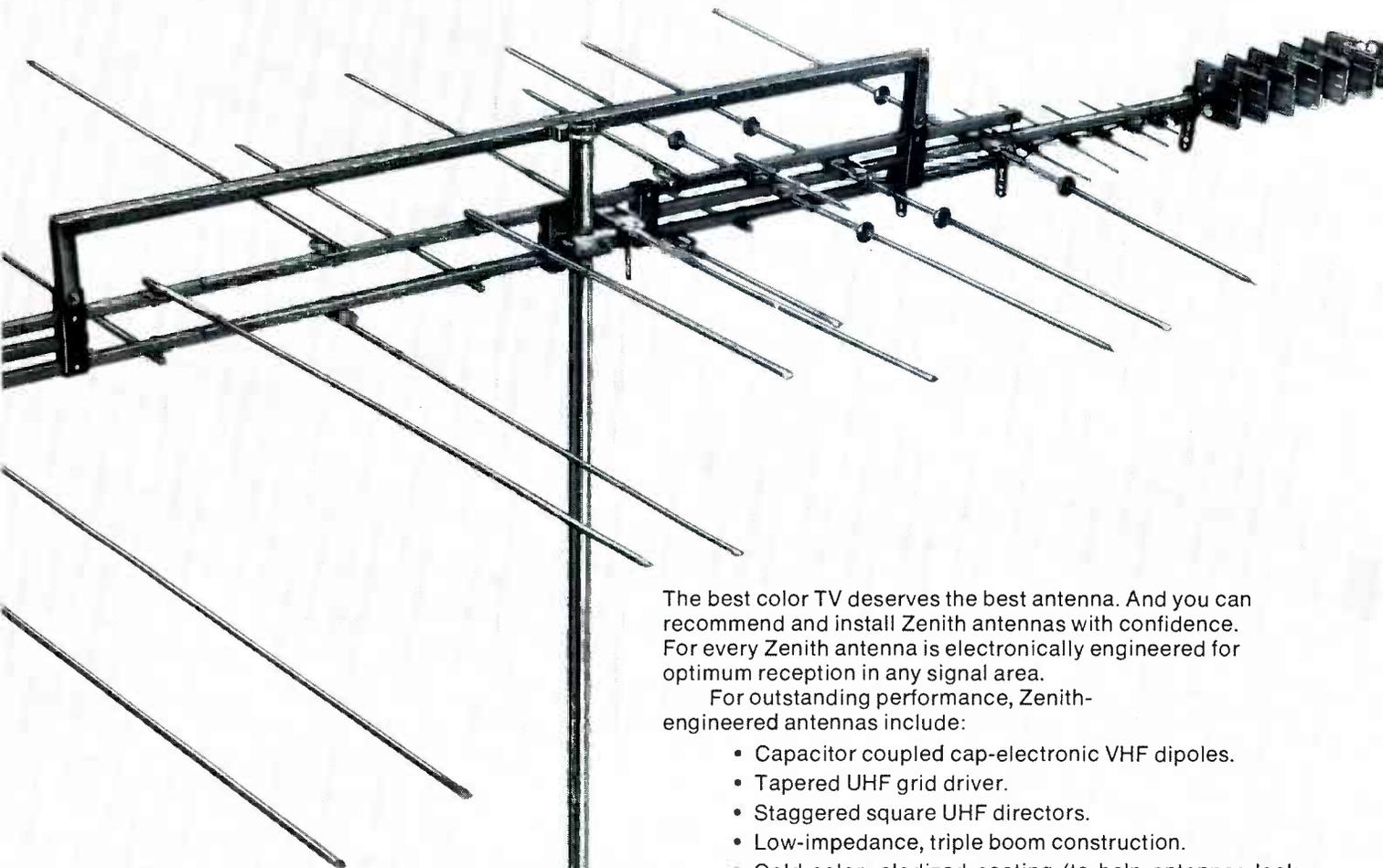Engineered for outstanding reception— Zenith outdoor antennas for Color TV!



The best color TV deserves the best antenna. And you can recommend and install Zenith antennas with confidence. For every Zenith antenna is electronically engineered for optimum reception in any signal area.

For outstanding performance, Zenith-engineered antennas include:

- Capacitor coupled cap-electronic VHF dipoles.
- Tapered UHF grid driver.
- Staggered square UHF directors.
- Low-impedance, triple boom construction.
- Gold-color alodized coating (to help antennas look better and last longer, with greater corrosion resistance and electrical conductivity).

Your Zenith Distributor has the complete line of Zenith quality-engineered TV antennas and antenna accessories. His staff has the technical experience and knowledge of your area to recommend the best antenna for any installation.

EXCITING SURPRISES FOR YOU—and Your Family!
Get the details at your Zenith *Distributor's Parts Department.*

Why not sell the best

ZENITH®

*The quality goes in
before the name goes on
Circle 5 on literature card*

AT LAST solid state triggered sweep, wide-band at a price you can afford!



Made in U.S.A.

5" oscilloscope / vectorscope

Triggered Sweep: Easy to use. Positive sync results in absolute stability of patterns.

Solid State: For reliability and performance.

Wide Band: 10 MHz—for increased use in all servicing, industrial and educational applications.

D.C. Amplifiers: Eliminates pattern bounce. Permits viewing A.C. signals and D.C. level simultaneously. Use as a sensitive D.C. voltmeter.

plus . . . Calibrated vertical attenuator. • Calibrated horizontal time base. • Automatic sync mode. • TV sync selector. • Vectorscope input for color TV servicing. • External horizontal amplifier. • 60 cycle horizontal sweep (sine wave) with phasing control. Compatible with all sweep generators. • Edge lit calibrated scale. • All solid state (tube protected input).

ONE YEAR WARRANTY

TO-50—oscilloscope / vectorscope Net 329⁵⁰

See your distributor or write Dept. ES-1



LECTROTECH, INC.

4529 North Kedzie Avenue • Chicago, Illinois 60625

Circle 6 on literature card

4 ELECTRONIC SERVICING/January, 1970

letters to the editor

Questions About Antenna System Components

(The following letter was directed to one of our contributing authors, Bruce Anderson. I think Mr. Anderson's reply will be of interest to all readers—the Editor)

I have some questions regarding the article titled "TV Antenna System or Receiver Defect?" which appeared in the June 1969 issue of ELECTRONIC SERVICING.

First, what is a UHF standoff (what does it look like)? Second, what type of VHF antenna is needed for deep fringe areas of 100 miles? And, what type of UHF antenna is needed for deep fringe areas of 50 miles?

I have done antenna work for 18 years and still found some things in the article which were new to me.

Charles E. Hunter
West Middlesex, Pa.

A UHF standoff has a pliable plastic tab which extends outward from the metal screw so that the lead-in is not encircled by the wire of which standoffs are made.

Your second question is a tough one. I am sure that I don't know the answer in its entirety, although I can perhaps shed some light on the subject. For single-channel reception, I would suggest a stacked pair of 10-element Yagi's as the best buy in microvolts per dollar. I once installed four of these in an array (two stacked pairs harnessed with 300-ohm line, trimmed for maximum signal using a signal-strength meter) and received a constant 125 microvolts from a station 145 miles away and behind a mountain.

If you are in the clear, a hundred-mile pull should be possible with most any good fringe-area antenna. The built-in preamplifier type antennas as well as the log-periodic types give good results.

In my experience, the parabolic UHF antenna works best in deep fringe. A 16-element Yagi with corner reflector also works well. It doesn't have quite as much sensitivity, but it is much easier to install. I have worked on a 20-watt translator satisfactorily at 20 miles with the Yagi and out to 40 miles with the parabolic antenna by using a mast-head booster.—Bruce Anderson.

Back Issues

Is there any demand for PF REPORTER magazines in A-1 condition? I have all the issues from August 1957 to February 1968. I am retired now, and it seems a shame to throw away all this valuable information.

Mr. Virgil V. Bowlin
Route #1
Hermitage, Mo.

Help Needed

I would like to obtain an operator's handbook on the Meissner Analyst, Model 9-1040. I have written letters to Meissner CR Co., New York, and to Meissner



\$975

TUNER SERVICE CORPORATION

PROVIDES YOU WITH A COMPLETE SERVICE FOR ALL YOUR TELEVISION TUNER REQUIREMENTS AT ONE PRICE.

TUNER REPAIR

VHF Or UHF Any Type \$9.75.

In this price all parts are included. Tubes are charged at cost.

24 hour service at our conveniently located service centers.

1 year guarantee backed up by the largest tuner manufacturer in the U.S.—SARKES TARZIAN INC.

All tuners are cleaned inside and out, repaired, realigned and air tested.

TUNER REPLACEMENT

Replacement Tuner \$9.75.

This price buys you a complete new tuner built specifically by SARKES TARZIAN INC. for this purpose.

The price is the same for every type of universal replacement tuner.

Specify heater type

- Parallel 6.3V
- Series 450 mA
- Series 600 mA

All shafts have the same length of 12".

Characteristics are:

- Memory Fine Tuning
- UHF Plug In
- Universal Mounting
- Hi-Gain Lo-Noise

If you prefer we'll customize this tuner for you. The price will be \$18.25. Send in original tuner for comparison purposes to our office in INDIANAPOLIS, INDIANA.



TUNER SERVICE CORPORATION

FACTORY-SUPERVISED TUNER SERVICE

- MIDWEST** 817 N. PENNSYLVANIA ST., Indianapolis, Indiana TEL: 317-632-3493
(Home Office)
- EAST** 547-49 TONNELE AVE., Jersey City, New Jersey TEL: 201-792-3730
- SOUTH-EAST** 938 GORDON ST., S. W., Atlanta, Georgia TEL: 404-758-2232
- WEST** SARKES TARZIAN, Inc. TUNER SERVICE DIVISION
10654 MAGNOLIA BLVD., North Hollywood, California TEL: 213-769-2720

Circle 7 on literature card

Only Admiral gives you the color picture tube with built-in customer satisfaction.



The exclusive Admiral 3-year warranty.

Now Admiral offers all new Super-Brite color picture tubes with the exclusive Admiral 3-year warranty. This industry exclusive provides your customers with maximum satisfaction.

Every Admiral Super-Brite color picture tube has Admiral-engineered thermal compensation for unexcelled color purity and the newest phosphors that give your customers clear, bright, sharp color pictures.

Here's another Admiral exclusive: In model 25SP22 (25AP22), our engineers have developed a vacuum deposited thin-metallic film on the inside of the envelope to assure trouble-free operation and longer life.

Admiral Super-Brite service color picture tubes aren't rebuilt. They're 100% brand new. From Admiral, producers of more rectangular color picture tube sizes than anybody in the world—the only one with the 3-year protection you asked for.

Admiral®

 Mark of Quality

Admiral Corporation warrants this picture tube to be free from defects in material or workmanship for 3 years after date of sale to the consumer.

Admiral's obligation is limited to supplying a suitable replacement picture tube. This warranty is effective if the picture tube is registered with Admiral within 10 days after date of sale to the consumer.

Circle 8 on literature card

& Landaver, Inc., Westfield, Mass., but received no answer. Could you or any of your readers help me find a manual? Any help would be greatly appreciated.

John L. Delaney
7527 Brous Avenue
Philadelphia, Pa. 19152

I am interested in obtaining resistor cord like the type used in the 1930's and 1940's on AC and DC radios. These cords were used to reduce filament voltage.

I would like to obtain a large quantity—at least a few hundred feet. Any information will be greatly appreciated.

Nilo A. Michelin
P. O. Box 6743
Los Angeles, Calif. 90022

I would like to buy an established one-man TV servicing business that has growth potential. The preferred area is in southeastern Florida, but I will consider the Gulf Coast. I would appreciate a snapshot with the first letter.

D. Mihychuk
755 Giasson St.
Seven Islands, Quebec, Canada

I need a schematic for a Model M345 VTVM made by Radio City Products Co. They seem to be out of business. I will be glad to pay any expenses for the schematic.

P. S. Raju
493 Wickham
St. Lambert, Quebec, Canada

I have a Philco Universal Color Bar and Dot Generator Model 7100 which I purchased used and which is giving me some trouble. I have been unable to find any circuit diagrams or technical information which tells what it is supposed to put out or exactly how it is hooked up. I have written to Philco and to Philco-Ford but to no avail.

I would appreciate it if one of your readers could help me find this information.

Donald W. Graf
2949 S.E. Boyd St.
Milwaukie, Ore. 97202


Dial-Stringing

I would like information on stringing the dial on an 8-transistor radio. It is a Sirasuna-Den Model 8TS-290. I don't know what the "Den" is, as the rest is gone. I have been unable to find a schematic on this radio. I would appreciate any help you or your readers could give me.

I am a subscriber to ELECTRONIC SERVICING and like it very much. I get a world of knowledge from it.

William B. Leake
2830 Redwood St.
San Diego, Calif. 92104

(Continued on page 8)

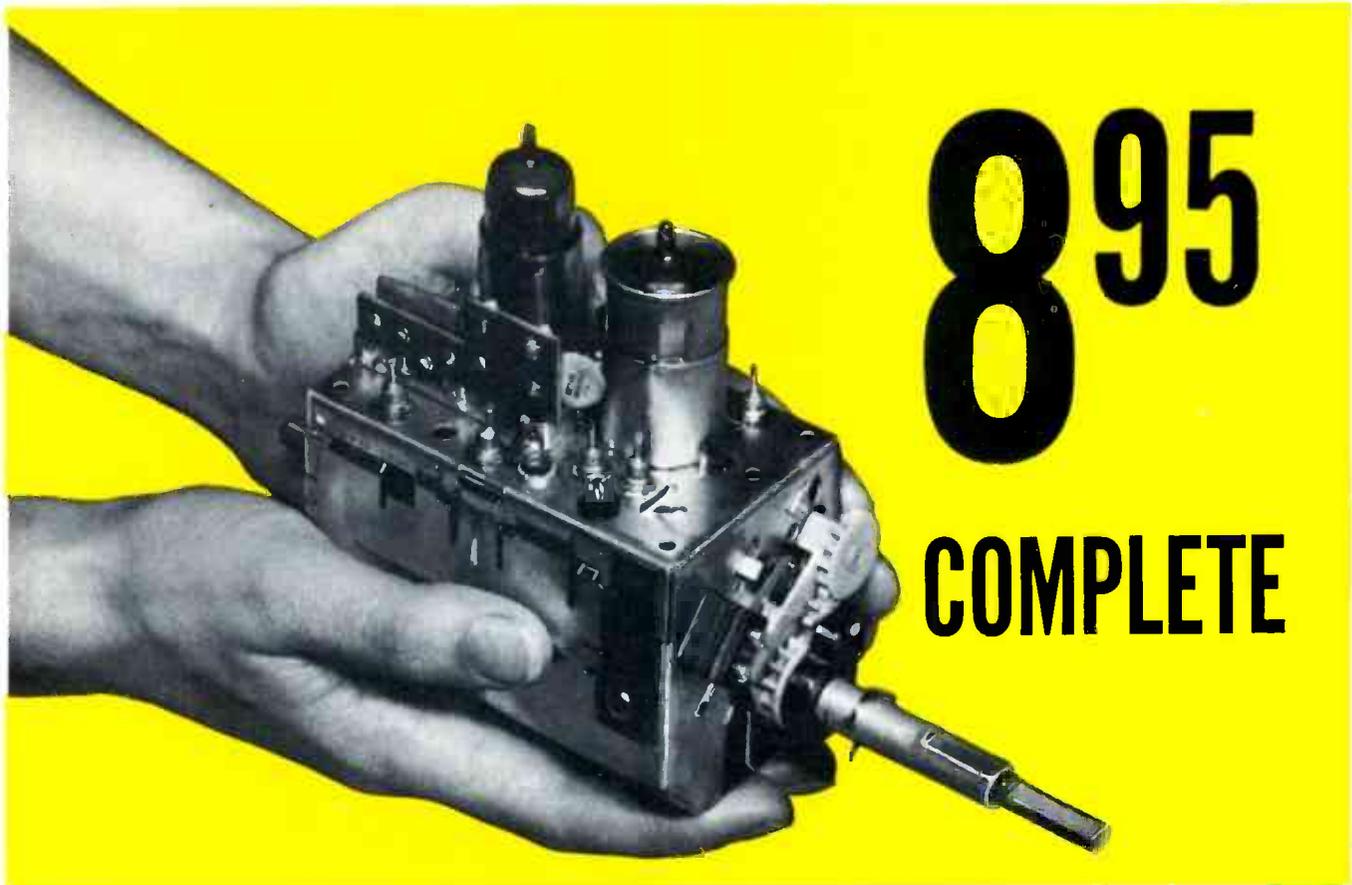

895 COMPLETE

Castle, the pioneer of television tuner overhauling, offers the following services to solve ALL your television tuner problems.

● **OVERHAUL SERVICE** — All makes and models.

- VHF or UHF tuner \$9.95
- UHF-VHF combination (one piece chassis) \$9.95
- TRANSISTOR tuner \$9.95
- COLOR tuner \$9.95
(Guaranteed color alignment . . . no additional charge)

Overhaul includes parts, except tubes and transistors.

Simply send us the defective tuner complete; include tubes, shield cover and any damaged parts with model number and complaint. Your tuner will be expertly overhauled and returned promptly, performance restored, aligned to original standards and warranted for 90 days.

UV combination tuner must be single chassis type; dismantle tandem UHF and VHF tuners and send in the defective unit only.

And remember—for over a decade Castle has been the leader in this specialized field . . . your assurance of the best in TV tuner overhauling.

● **CUSTOM REPLACEMENTS**

Exact replacements are available for tuners that our inspection reveals are unfit for overhaul. As low as \$12.95 exchange. (Replacements are new or rebuilt.)

● **UNIVERSAL REPLACEMENTS**

Prefer to do it yourself?

Castle universal replacement tuners are available with the following specifications.

STOCK No.	HEATERS	SHAFT		I.F. OUTPUT		PRICE
		Min.*	Max.*	Snd.	Pic.	
CR6P	Parallel 6.3v	1¾"	3"	41.25	45.75	8.95
CR7S	Series 600mA	1¾"	3"	41.25	45.75	9.50
CR9S	Series 450mA	1¾"	3"	41.25	45.75	9.50
CR6XL	Parallel 6.3v	2½"	12"	41.25	45.75	10.45
CR7XL	Series 600mA	2½"	12"	41.25	45.75	11.00
CR9XL	Series 450mA	2½"	12"	41.25	45.75	11.00

*Selector shaft length measured from tuner front apron to extreme tip of shaft.

These Castle replacement tuners are all equipped with memory fine tuning, UHF position with plug input for UHF tuner, rear shaft extension and switch for remote control motor drive . . . they come complete with hardware and component kit to adapt for use in thousands of popular TV receivers.

Order universal replacements out of Main Plant (Chicago) only.



CASTLE TV TUNER SERVICE, INC.

MAIN PLANT: 5701 N. Western Ave., Chicago, Illinois 60645

EAST: 41-90 Vernon Blvd., Long Island City, N.Y. 11101

Circle 9 on literature card

A Reader Speaks Out Against Licensing

The article titled "Consumer Electronic Servicing—Licensing, A Special Report" in the July issue of *ELECTRONIC SERVICING* impels this reply.

I would suggest that our business environment is in the grip of a disease, fondly referred to as "Consumerism," which has made its impact these past few years, fostered by the press, radio and television. It got its start with Mrs. Peterson as a consumer-affairs overseer, followed by that female huckster, Betty Furness, and since fostered by bleeding hearts, hand wringers, band-wagon followers and coat tail riders, with a few conscientious, concerned people who are caught up in the hot winds of demagogery. This ailment has become a bonanza vote-getter for politicians at all levels who find it is the gravy train into public office.

If we were to probe deep into the motivation of the consumer-oriented politician, we would find lurking in the recesses of that astute mind a concern more for himself and his public image than for any good which might attach to the recipients of his tender regard.

All business has its buccaneers—looters of the public purse, pursuers of the fast buck. The dealers and the service people of electronic home devices are no exception. Through the years, organized society evolved laws to seek out and punish willful characters guilty of fraud and deceptive practices of one kind or another. For some obscure reason, radio and television service people have been singled out for special vigilance and stringent punitive legislation not asked for nor sought against other lines of business, service or whatever the type.

What better way to endear oneself to the public—to inflame the public mind: Besmirch the character of the serviceman and, with the help of newspaper and magazine hack writers and radio and television commentators, distort and spread misinformation to the set-owning public, creating resentment and illwill against servicemen out of all proportion to actual fact and honesty, thereby creating a clamor from the "there-oughta-be-a-law"

claque which political demogogs are quick to act on.

Serenely overlooked by these biased and hypocritical mudslingers are the sickening, unethical activities of lawyers, doctors, judges and run-of-the-mill public officials, whose chicanery and misdeeds in public office and professionally makes the chiseling of television servicemen look like peanuts in comparison.

When highly-placed professional and political people are found out, separating them from their income sources is a job defying imagination. Unashamed judges, unethical lawyers, doctors and other licensed professional and political people continue on for years, engaging in highly questionable and unprofessional conduct for big money, challenging their removal. BUT, let some little TV shop operator be accused and charged with some minor fraud practice under stringent license laws now in effect or proposed and he will be lucky if he can stay out of jail, prevent the revoking or cancellation of his license to make a living and keep from having his little business shut down overnight and his earnings cut off.

This is the evil of evils with respect to license laws seeking to control and regiment radio and television servicemen, which are now in effect or sought in other states. These laws could, would and are manipulated to the detriment of the small shop owner—the "Mom and Pop" operation—by disgruntled and resentful customers, jealous competitors and, in extreme cases, by the eventual political appointees to a license board, who would want to look "good" for the record. No amount of denials and protestations on the part of license proponents can wave away this ever-present danger. There are other important reasons too numerous to mention here, but the little man would be absolutely defenseless against the multiplied attrition of numerous phony complaints that could be brought to bear against him and which would, in time, put him out of business with no one the wiser.

Much can be said about the license laws mentioned in your article. I will make but one reference—the Berder regulation of Cali-

fornia. As stated, it has been in effect 5½ years; in that time, 12,000 complaints have been made, 12,000 investigations followed, 143 criminal actions brought and, finally, 52 licenses revoked—in 5½ years! With all that elaborate legal machinery, uncounted wads of taxpayers' money, unnumbered political payrollers, investigating, unknown informers and entrapment methods—what a record?

I have spent 16 years opposing licensing in Illinois—the more I have seen and read of it, the less that can be said for it.

Howard Wolfson
Tape Recorder Sales Co.
Chicago, Ill.

Help Needed

I need a schematic and service literature for a Mety Model 1506/7/8 AM/FM S. Wand phono combination. I have been unable to locate any information on it.

Edward J. Weimer
75-23 67th Rd.
Middle Village,
L.I., N.Y. 11379

I have a battery-operated Airline radio designated Models 62-169 and 62-172. I need the size and/or voltages on the tubes and batteries. I would appreciate it if anyone could help.

Lewis J. Clark
Box 14
Colton, N.Y. 13625

Perhaps *ELECTRONIC SERVICING's* readers could help me locate Volumes AR-1, AR-9, AR-10, AR-12, AR-13 and AR-15 of Sams' auto radio series. I would pay premium prices for these issues. I am also interested in buying complete libraries of car radio technical publications.

Clifford M. Gazaway
P.O. Box 46156
Seattle, Wash. 98146 ▲

Got A Troubleshooting Tip?

If you've recently run across an unusual trouble symptom, send a thorough description of it and the solution to:

Troubleshooting Tip,
Electronic Servicing
1014 Wyandotte St.
Kansas City, Mo. 64105

RCA to Market Home Video Tape Player in '72

The laboratory model of a cartridge video tape player system for use with home color and b-w TV sets has been demonstrated by RCA.

Called SelectaVision, the unit reportedly will be priced at less than \$400. Production will begin in 1972, and the unit will be available to the public shortly thereafter, according to a company spokesman.

Basics of the SelectaVision system, which is attached to the antenna terminals of the TV set, include a 2-mW laser whose beam passes through clear plastic tape on which appear video and color information in the form of holographic reliefs. The images and color coding illuminated by the laser are picked up by a low-cost TV camera.

The 30-minute, pre-recorded SelectaVision tapes reportedly will be scratch-proof, dust-proof and virtually indestructible under normal use. Cost of the pre-recorded tapes will be about \$10.00, according to an RCA spokesman. Speed of the 1/2-inch tape will be 7 1/2 ips; reel diameter will be 6 inches.

FCC Says CATV Can Use Microwave To Carry Own Programming

Programming originated by community antenna television systems (CATV) can be transmitted over CATV microwave relay facilities.

This recent ruling by the Federal Communications Commission (FCC) removes one major obstacle that, in the opinion of many observers, had prevented the emergence of a CATV network.

The new rule, which permits use of frequencies between 12,700 and 12,950 MHz for CATV systems, also makes available such microwave relay facilities for remote pickups.


Japanese Home Cassette VTR Systems Will Be Available in Early '70's

Sony, Matsushita and Victor, Japanese manufacturers of home entertainment products, have announced the availability in the early '70's of low-cost home video cassette systems, according to recent reports in **Home Furnishings Daily**.

A Victor video cartridge recorder for use with color and monochrome TV sets reportedly will be available early this year. Victor's video cartridge is 5.5 x 5.5 inches and is 1 inch thick. The Victor tape recorder is 17.5 x 16.6 x 7.8 inches and weighs 33 pounds. The cartridge runs for 30 minutes with 1/2-inch tape at a speed of 7.5 ips. Price of the cartridge is \$25.00, according to the report, while the entire Victor recorder package will sell for about \$500.

The Sony system, to be available late this year, is designed primarily for playback, but, according to the company, a simple adapter will enable the home user to record either color or monochrome on a video cassette. Price of the playback unit reportedly is about

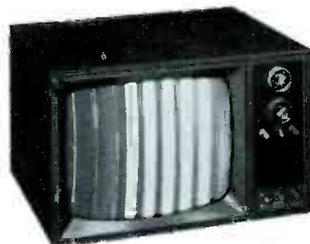You're making money in electronics now.
RCA Offers 4 Ways to Make More.
Study at home...set your own pace.
RCA Institutes has an easy approach
to bring you bigger earnings.



COLOR TV:

During this course you'll perform over 50 experiments—and receive all parts and instructions to build your own color TV.

The cost of the Color TV Kit is included in the tuition—in both the beginner's program and the advanced course in color TV servicing. (Picture tube optional)
Course is based on the latest receiver circuitry and equipment.

SOLID STATE TECHNOLOGY

New courses include the latest findings and techniques in this field. Information you must have if you are to service the multitude of solid state instruments and devices used in TV, Digital, and Communications equipment.



FCC LICENSE TRAINING:

Choose the course for the FCC License you want: third, second or first phone. If you need basic training first, apply for the complete License Training Program. Get your License—or your money back.

CATV TRAINING:

You'll receive two comprehensive lessons, covering the practical phases of CATV systems in either the Television Servicing or Communications courses.

Licensed by New York State Education Department. Approved for Veterans. Accredited Member National Home Study Council.

RCA

MAIL THE COUPON NOW FOR COMPLETE INFORMATION.

RCA INSTITUTES, Inc., Dept. 661-001-0
320 West 31st Street, N.Y., N.Y. 10001

Please rush me FREE illustrated catalog. I understand that I am under no obligation, and that no salesman will call.

Name _____ Age _____
(please print)

Address _____

City _____

State _____ ZIP _____

Circle 10 on literature card

The Complete Line of Signal-Indicating Alarm-Activating Fuses

For use on computers, microwave units, communication equipment, all electronic circuitry.



BUSS GLD- $\frac{1}{4}$ x $1\frac{1}{4}$ in. Visual-Indicating, Alarm-Activating.

BUSS GBA- $\frac{1}{4}$ x $1\frac{1}{4}$ in. Visual-Indicating.



BUSS MIC- $\frac{13}{32}$ x $1\frac{1}{2}$ in. Visual-Indicating, Alarm-Activating.

BUSS MIN- $\frac{13}{32}$ x $1\frac{1}{2}$ in. Visual-Indicating.



FNA FUSETRON Fuse $\frac{13}{32}$ x $1\frac{1}{2}$ in. slow-blowing, Visual-Indicating, Alarm-Activating. (Also useful for small motors, solenoids, transformers in machine tool industry.)



BUSS Grasshopper Fuse, Visual-Indicating, Alarm-Activating.



BUSS ACH Aircraft Limiter, Visual-Indicating.



BUSS GMT and HLT holder, Visual-Indicating, Alarm-Activating.

Write for BUSS Form SFB



BUSSMANN MFG. DIVISION, McGraw-Edison Co. St. Louis, Mo. 63107

BUSS: The Complete Line of Fuses and

\$350; the recording adapter will cost an additional \$100.

The Sony color video player utilizes a magnetic video tape cassette, can be used with any standard color TV set without modification and is fully compatible with any b-w set, according to the report. The unit measures 8 x 5 x $1\frac{1}{4}$ inches and weighs 1 pound. Tape width is $\frac{3}{4}$ inch and speed is 8 cm/sec.

Matsushita reportedly will have a home video cassette player available in 1972. The Japanese company, which markets products in the country under the Panasonic brand name, will have an open-reel color VTR home unit ready this year.

Precision Tuner Adds Florida Branch

Precision Tuner Service, Bloomington, Indiana based servicer of TV tuners, has announced the opening of a new facility in Miami, Florida. The address of the new tuner servicing center is Box 91, Miami, Florida 33156.

Earlier this year Precision Tuner opened other new facilities in Turlock, California and Longview, Texas.

Reversible Auto Cassette Player Developed By TEAC

A cassette player for automobiles incorporating automatic reverse has been developed by TEAC Corporation of Japan.

The cassette player has a fixed drive mechanism,

which allows the user to install the system in a space-saving vertical position. Easy insertion of cassettes is permitted through the use of a spring-supported guide structure.

Two-way tape drive and stable performance under rough road conditions reportedly are made possible by two independent flywheels. "Soft-touch" push buttons are provided for stop and reverse operations, and the player can be operated by remote control.

Admiral Film Available To Interested Groups

Admiral Corporation has completed and is making available free of charge to interested groups and organizations a new 25-minute color film, titled "Admiral Creative Excellence," which portrays the production of color TV tubes and the manufacture of color sets.

The film covers the production of color picture tubes in the company's plant in Chicago; the manufacture of tuners and yokes at McHenry, Illinois; the crafting of wood cabinets for color television sets at the Shelbyville, Indiana, division; and the assembly of color receivers at the giant Harvard, Illinois, consumer electronics facility.

Morse Name Added to List of TV Marketers

Morse Electric Products, marketers of stereo consoles under the name "Morse" and compact stereos under the name of "Electroponic," reportedly will market, either late this year or early next, a large-screen

SUB-MINIATURE FUSES

Ideal for space tight applications, light weight, vibration and shock resistant. For use as part of miniaturized integrated circuit, large multi-circuit electronic systems, computers, printed circuit boards, all electronic circuitry.



TRON Sub-miniature Pigtail

Fuses — Body size only $.145 \times .300$ inches. Glass tube construction permits visual inspection of element. Hermetically sealed. Twenty-three ampere sizes from 1/100 thru 15.



BUSS Sub-miniature GMW Fuse and HWA Fuseholder

Fuse size only $.270 \times .250$ inches. Fuse has window for visual inspection of element. Fuse may be used with or without holder. 1/200 to 5 amp. Fuses and holders meet Military Specifications.

Write for BUSS Form SFB




BUSSMANN MFG. DIVISION, McGraw-Edison Co. St. Louis, Mo. 63107

Circle 11 on literature card

The Complete Line of Fuses For The Protection of Semi-Conductor Rectifiers

TRON Rectifier Fuses

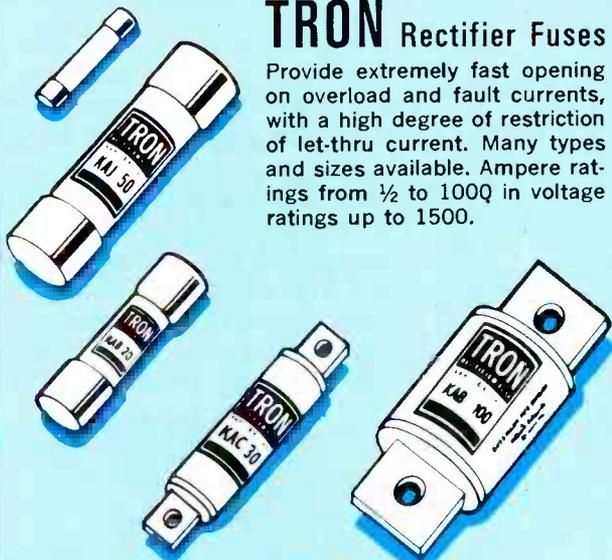Provide extremely fast opening on overload and fault currents, with a high degree of restriction of let-thru current. Many types and sizes available. Ampere ratings from 1/2 to 100Q in voltage ratings up to 1500.



Write for BUSS Form SFB



BUSSMANN MFG. DIVISION, McGraw-Edison Co. St. Louis, Mo. 63107

The present allowable level of 500 μ V/m at 100 feet was established by the Commission in December, 1955 and went into effect February, 1956. However, requests by TV manufacturers for delays in implementation of these limits have been granted by the Commission and, as a result, a limit of 1000 μ V/m at 100 feet has been allowed up to the present time.

Customer Can Choose Own Servicer Under New Midland Warranty Program

The in-warranty servicing of Midland International Corporation's TV receivers can be performed by any reputable service facility the customer chooses.

Midland International Corporation, Kansas City based importer of home entertainment products, has adopted a new television warranty policy that gives the customer the privilege of choosing the servicer who will perform the in-warranty servicing of his Midland TV.

Under the terms of the new program, which Midland calls "Customer's Choice Television Service Policy," Midland will supply the necessary replacement parts and will re-imburse the service center for labor. The warranty covers TV sets for 90 days. B-W picture tubes are warranted for one year and color picture tubes are warranted for two years. ▲

Fuseholders of Unquestioned High Quality

color TV home entertainment center and one smaller-screen color and one personal-size b-w TV.

Solid-State Device Reportedly Eliminates Color TV X-radiation

Scientific Components Inc. has developed a solid-state device which is reported to virtually eliminate the alleged harmful X-radiation in color television sets. The device is being shipped to a major TV manufacturer, whose name is being withheld.

The device, called a triplet, reportedly replaces the high-voltage rectifier, the focus diode and associated components.

FCC Proposes Reduction of Allowable TV Receiver Radiation


A rule to reduce the allowable amount of electromagnetic energy (radiation) emitted by TV receivers has been proposed by the Federal Communications Commission.

The rule would reduce the field-strength limit of electromagnetic energy from the present allowable level of 500 μ V/m at 100 feet in the 470-1000 MHz band to 350 μ V/m at 100 feet in the same frequency band.

Ten field-strength measurements taken on ten specified frequencies—520, 550, 600, 650, 700, 750, 800 and 931 MHz—also would be required by the rule.

THE COMPLETE LINE OF Small Dimension FUSES

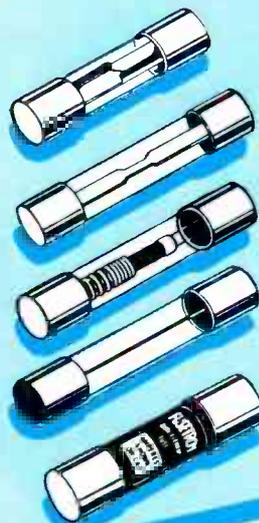For The Protection of All Types of Electronic and Electrical Circuits and Devices . . .



. . . includes dual-element "slow-blowing", single-element "quick-acting" and signal or visual indicating types . . . in sizes from 1/500 amp. up.

For special fuses, clips, blocks or holders, our staff of fuse engineers is at your service to help in selecting or designing the fuse or fuse mounting best suited to your requirements.

Write for BUSS Form SFB



BUSSMANN MFG. DIVISION, McGraw-Edison Co. St. Louis, Mo. 63107

Circle 12 on literature card

WE WON'T GIVE A 6 MONTHS GUARANTEE THAT BLUE STUFF WON'T CAUSE A CALLBACK!

We've had over 4½ years of service experience with BLUE STUFF and we don't have to limit OUR guarantee to 6 months. Our guarantee is the same as it's always been.



We guarantee that BLUE STUFF will not cause callbacks when used according to instructions no matter HOW long it is in a tuner, or we'll refund your money.



for tuners from

TECH SPRAY

BOX 949, AMARILLO, TEXAS 79105
Canada: Wm. Cohen, Montreal, Quebec

Circle 13 on literature card

test equipment

notes on analysis of test instruments, their operation and applications

Color-Bar Generator

Sencore announces the availability of an updated version of their "Color King" color-bar generator. The new generator, Model CG153, will supersede the company's earlier Color King Model CG141.

New features include increased circuit stability through doubling of the timing ranges, decreased current



drainage and an all-new panel and case, according to the manufacturer. The new two-toned case uses vinyl-clad steel against a brushed steel divider.

Two additional patterns, not present on the company's lower-priced models, are a moveable cross and a moveable dot. Sencore states that both can be set at center for centering the color TV raster. The CG-153 Color King features "temp control", which preheats all of the circuits so that a service technician does not have to wait for the generator to warm up and stabilize on very cold days. It is also reported that all circuits now have been voltage-regulated.


The price of the Model CG153 color-bar generator is \$169.95.

Circle 55 on literature card

Standard FM Deviation Meter

Measurements announces the availability of their new Model 140A standard deviation meter and standard test receiver.

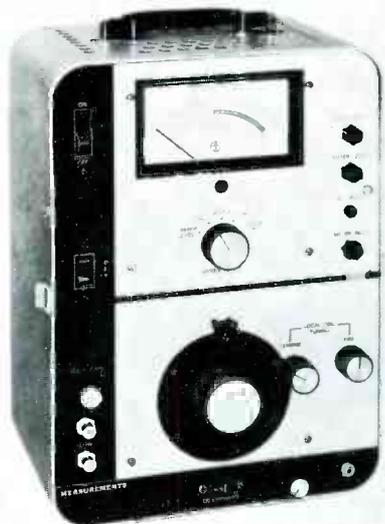The new instrument, completely portable and designed to measure accurately the peak frequency deviation of FM communications transmitters, is specially suited for lab use and mobile radio servicing,



according to the manufacturer. The deviation meter contains accurate, linear, counter-type discriminator and degenerative voltmeter. A stable conversion oscillator reportedly permits measurements to 1000 MHz with 3% deviation accuracy. The unit is said to be easily standardized without an accurate FM source or requirement for Bessel-null techniques.

The output system includes a 750 micro-second de-emphasis network to permit use as a standard test receiver meeting EIA Standard RS-152-A, enabling simple measurements of noise, distortion and audio frequency response of transmitters. The network may be switched out of the circuit when not required. It has a front panel phone jack for monitoring. The meter has direct reading ranges of 0-5 KHz and 0-20 KHz.

The price of Model 140A is \$550.00.

Circle 56 on literature card

In- or Out-of-Circuit Transistor Tester

Commander Electronics has developed a low-cost tester for all semiconductors, including the new FET's, it is reported.

Designated the Model 830, the



Confused by Fancy Names and Gimmicks?

Never Trust A Stranger.



Choose G.C. Electronics Chemicals Leaders since the 1930's.

G.C. is committed to quality and value, not fancy names and gimmicks. We are manufacturers and fillers, not just selling agencies.

G.C. is the only company that supplies all your chemical needs. Tubes - bottles - cans - drums — a size and formula for every need.

Put Brand X, Y and Z together, and G.C. Chemicals outsells them all.

The reason: Quality — service — selection — fair value — national advertising — free catalogs.

Free — Brochure available on G.C. Chemicals. Write...

GC ELECTRONICS

400 SO. WYMAN ST., ROCKFORD, ILLINOIS 61101

A DIVISION OF HYDROMETALS, INC.



Circle 14 on literature card

Show and Sell!



Now Electro-Voice makes it even easier than ever to profit from phono needle replacement sales. This new counter top needle merchandiser is the answer to dealer requests from coast to coast.

Inside are 109 E-V needles selected from our "hot 50" list of fast-moving types. With extra room for special types that sell best in your area.

Underneath is space for your up-to-date copy of the complete E-V needle/cartridge replacement guide (up-to-date because we compile it with the aid of our computer).



And the E-V needle merchandiser design puts your entire basic stock on display, yet discourages pilferage with its four-drawer glass covered construction.

Don't overlook the profits you can make with phono needle service. Straighten up your stock with an E-V merchandiser, and we can assure you of a neat profit. Your Electro-Voice distributor is ready to help today.

ELECTRO-VOICE, INC., Dept. 107
632 Cecil St., Buchanan, Michigan 49107

Electro-Voice[®]

A SUBSIDIARY OF GULTON INDUSTRIES, INC.

unit reportedly is efficient and versatile, checking transistors, FET's, etc., for all critical parameters, in or out of circuit, giving calibrated readings for G_m , AC and DC Beta and leakage.

The tester utilizes a large, sensitive (200 μ a) taut band meter and full-size control knobs for easy setting of function or bias levels, according to the manufacturer. A big, easy-to-read meter is color-coded to match switch positions and there is also an integral voltmeter with expanded scale. A luggage-type carrying case with handle is standard equipment.


Commander is offering a free modification kit to all owners of earlier 830 models to update their equipment for testing FET's. The cost of the new Model 830 is under \$80.

Circle 57 on literature card

Dual dB Meters

Cyclotronics Corp. has made available a line of dual dB meters for monitoring stereo recorders or speaker output levels.

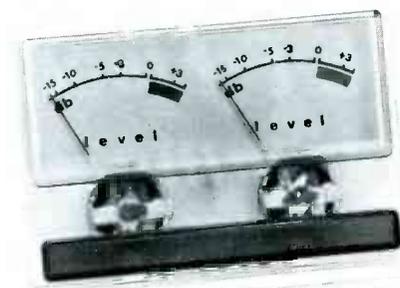It is reported that the meters indicate any simultaneously occurring functions which can be reduced to electrical characteristics. The units



primarily are used in balancing signal levels in stereo record or playback systems. They also can be used in monaural multi-channel monitors.

The price of Model UF-3D ranges from \$6.96 each for quantities of less than 50 to \$2.91 each for quantities of 20,000 to 49,999.

Circle 58 on literature card

Digital Frequency Meter

Lampkin Laboratories, Inc., has introduced the Lampkin Type 107 Digital Frequency Meter (DFM) for mobile-radio servicing.

It is both a solid-state, heterodyne-type frequency meter and a signal

generator, according to the manufacturer. A power supply of either a 12-volt battery or a 117-volt, 50- to 400-Hz AC source, 8-watts nominal, is needed. A three-wire AC



plug and cord and a plug and cord to fit an automobile cigarette lighter are furnished with the instrument.

Characteristics

- Frequency range: 10 KHz to 500 MHz, for both measurement and generation.
- Accuracy: 0.0001%. Internal crystal secondary standard with proportional oven temperature control—3.0 MHz nominal. Aging rate—3 in 10° per day; stability—1 in 10°.
- Variable-frequency Crystal Oscillator: 1 MHz, proportional oven temperature-controlled; calibrated dial ± 0.005 .
- Output: 1.0 volt rms, 10 KHz to 10 MHz, controlled by a step attenuator, 0 to -60 dB in 10-dB steps and by a variable panel control -8 to +2 dB. Attenuator accuracy— ± 2 dB; output impedance—less than 20 ohms.
- Modulation: AM—approximately 1000 Hz. No FM modulation.
- Temperature range: 32°F to 122°F.

The DFM weighs 22.3 lbs. and measures 7 $\frac{3}{8}$ " x 17 $\frac{3}{8}$ " x 11". Without the handles, the height is 6 15/16", compact enough to mount in a standard relay-rack.

The price is \$2,390.00.


Circle 59 on literature card ▲

Moving?

Send your new address to:
ELECTRONIC SERVICING

Circulation

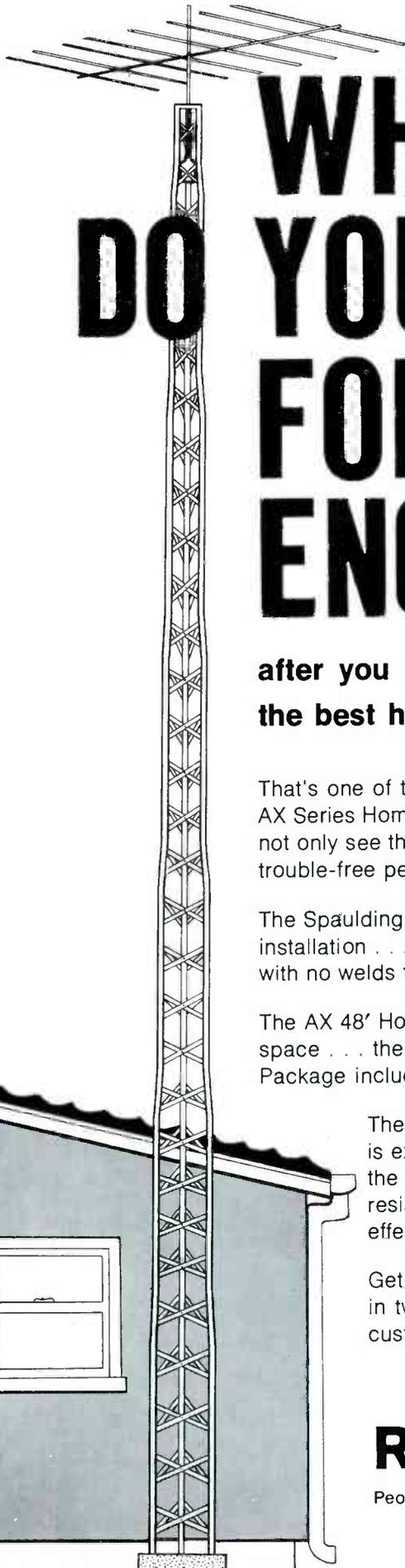1014 Wyandotte St.
Kansas City, Missouri 64105



DO YOU DO FOR AN ENCORE...?

**after you have sold your customers
the best home TV towers.**

That's one of the big advantages when you stock and sell Spaulding AX Series Home TV Towers. You're offering a tower in which they'll not only see the quality, which is apparent, but they'll also see the trouble-free performance they are looking for.

The Spaulding AX Home TV Tower is designed for quick economical installation . . . and is all-steel, galvanized and all riveted construction with no welds to rust.

The AX 48' Home TV Tower package only requires 2 sq. ft. of floor space . . . the AX series packages are available in heights up to 64'. Package includes base stubs, hardware, mast and mast kit.

The Spaulding AX Series Tower is a self-supporting tower and is extremely rigid under most erection situations. The higher the tower goes, the greater the strength at the base. The wind resistance at the top decreases with height. The "tapering" effect adds to the attractiveness of the tower.

Get specifications on this complete tower package, and profit in two ways—bigger sales and greater goodwill from your customers.

ROHN-SPAULDING, INC.

Peoria, Illinois • Birmingham, Alabama • Frankfort, Indiana

Circle 15 on literature card

**This is 30,000
solid state replacement parts.**



So is this.



It used to be if you wanted to satisfy everyone, you had to stock over 30,000 different solid state replacement parts.

Well, everyone realized that was ridiculous. So some enterprising people came up with a bunch of universal replacements.

Then you only had to stock about eleven or twelve hundred.

That was a lot better, but we still thought it was a little ridiculous.

So two years ago (when we went into this business), we figured out how to replace all 30,000 with only 60.

Now all you have to do is stock 60 of our diodes, transistors, integrated circuits, etc., and you can replace any of the 30,000 parts now in use. Including

all JEDEC types, manufacturers' part numbers, and foreign designs.

That means you invest less money.

You don't tie up valuable space.

You do away with complicated inventory control.

And you operate more efficiently.

To make life even easier, we've got a new book that gives you all the cross references you need to figure out which part replaces which.

It's available from your Sylvania distributor.

If the whole thing sounds rather incredible, you're right. But why not give your distributor a call and let him narrow the incredibility gap.

SYLVANIA
GENERAL TELEPHONE & ELECTRONICS

Circle 16 on literature card

by Allan Dale

How to make adjustments in FM multiplex systems

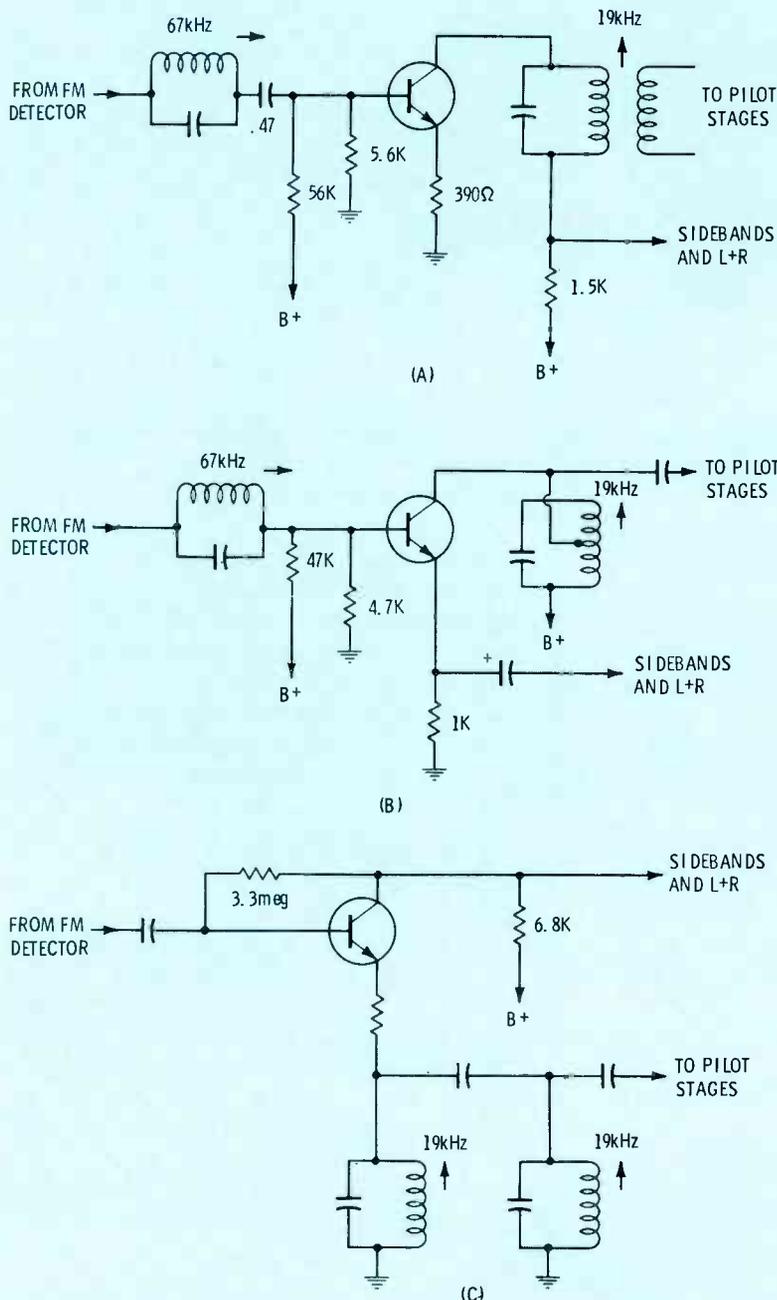


Fig. 1 Preamplifiers in many multiplex receivers have the 67-KHz SCA traps preceding them, as in A and B. In others such as C, they are further along, in the branch of the section that handles the L - R sidebands and the L + R signal.

Not long ago I described how to simplify sweep alignment (August 1969, page 12). From what I hear, a natural followup is a story about easy alignment for FM-stereo multiplex receivers.

Stereo FM sets still baffle a good many technicians. Mostly, I think it's because no one has explained to them just what goes on inside the multiplex section and what it takes to decode a stereo broadcast. So that's where I'll start.

The signal from a stereo FM station has three components. They are: 1) the pilot carrier, a steady 19-KHz tone that is used for synchronizing the stereo; 2) the L + R signal, which is a combination of the audio signals from the left and right microphones; and 3) a complex signal made by subtracting the right microphone signal from the left, amplitude-modulating the result on a 38-KHz carrier and then eliminating the carrier, leaving a pair of L - R sidebands. All of these are put together and frequency-modulated on the station carrier.

At the receiver, the FM carrier, with its modulation, is converted to an IF signal and amplified in regular 10.7-MHz tuned amplifiers. Bandwidth is designed into the IF amplifiers; for alignment you need only peak them at 10.7 MHz.

The FM detector that follows the IF strip recovers the composite stereo signal just described, with its three components. The multiplex section, then, has the task of handling these three components. The object is to recover the left and right audio channels.

Separating Sync from Sidebands

The first stage of a multiplex section is almost always a preamplifier. It's not always for amplifying. More often, it's a coupling device and a splitter. As a coupler, it

matches detector-to-multiplex impedances. As a splitter, it separates the 19-KHz pilot signal from the L - R sidebands and the L + R signal. Sometimes, it amplifies one or the other.

Some popular preamplifiers are shown in Fig. 1. The first one, in Fig. 1A, is common in home stereo receivers. The composite stereo signal comes through a trap that's tuned to 67 KHz (I'll explain that later) and a coupling capacitor.

This stage does amplify. The L - R sidebands and L + R signals find very little impedance in the 19-KHz tuned circuit. The 1.5K-ohm resistor is the load for them.

The 19-KHz pilot signal is developed across the tuned circuit. This load does two jobs: Its impedance to 19 KHz, in series with the collector load resistor, effectively blocks 19 KHz from the sideband/L + R portion of the multiplex section. Its main job is to

couple the 19-KHz pilot signal to stages that prepare it for synchronizing the stereo detector.

About that 67-KHz tuned circuit. Some FM stations broadcast a special store music channel. Sound for it is amplitude-modulated on a 67-KHz subcarrier. It's often called an SCA (Subsidiary Communications Authorization) subcarrier. The modulated 67-KHz subcarrier becomes a fourth signal multiplexed on the FM carrier. If broadcast simultaneously with regular stereo, the SCA subcarrier might cause interference noises in a receiver. A 67-KHz trap blocks the SCA signal out of the sideband/L + R stages.

During alignment, you feed a plain 67-KHz signal into the multiplex section and tune the trap for minimum response to it. The tuning dip will be sharp if the coil is okay.

The stages in Figs. 1B and 1C are common to FM stereo receivers in automobiles. However, they may

show up anywhere. In Fig. 1B, the preamplifier stage amplifies the 19-KHz pilot. It feeds out the sidebands and L + R signals from the emitter, without gain. The stage in Fig. 1C is just the opposite. The tuned 19-KHz load is in the emitter circuit; the sidebands and L + R are taken from the collector load.

Adjusting Pilot Stages

The stages in the pilot-handling portion of a multiplex section have two things to accomplish: 1) They must amplify the 19-KHz signal, and 2) one of them must convert the 19-KHz signal to a precisely phase-accurate 38-KHz signal. These steps are necessary for converting the L - R sidebands back into an accurate reproduction of the original L - R signal. Fig. 2 shows in semi-block form how this is done in various receivers.

The most popular way to produce a 38-KHz signal for subcar-

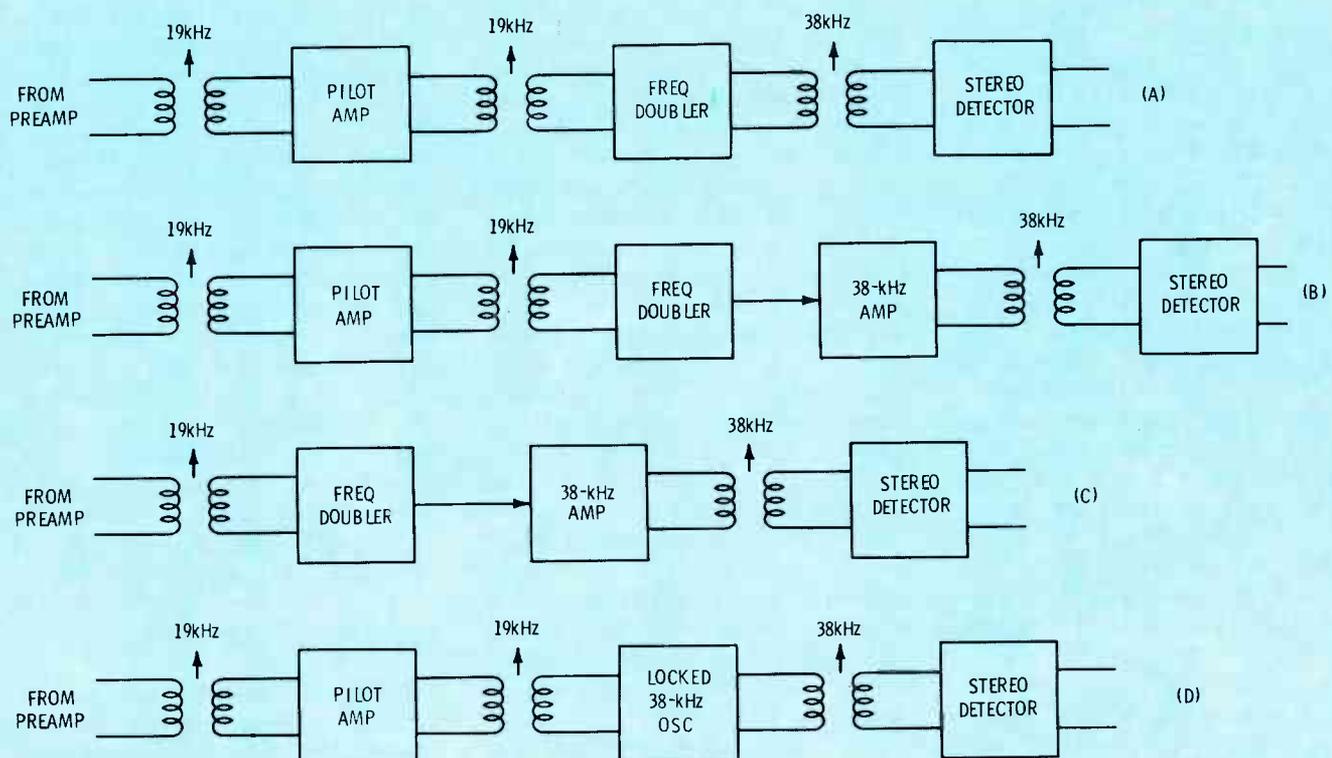


Fig. 2 Typical arrangements for handling the 19-KHz pilot carrier and generating the 38-KHz reinserter carrier. This is also called the "stereo sync" section by some hi-fi technicians.

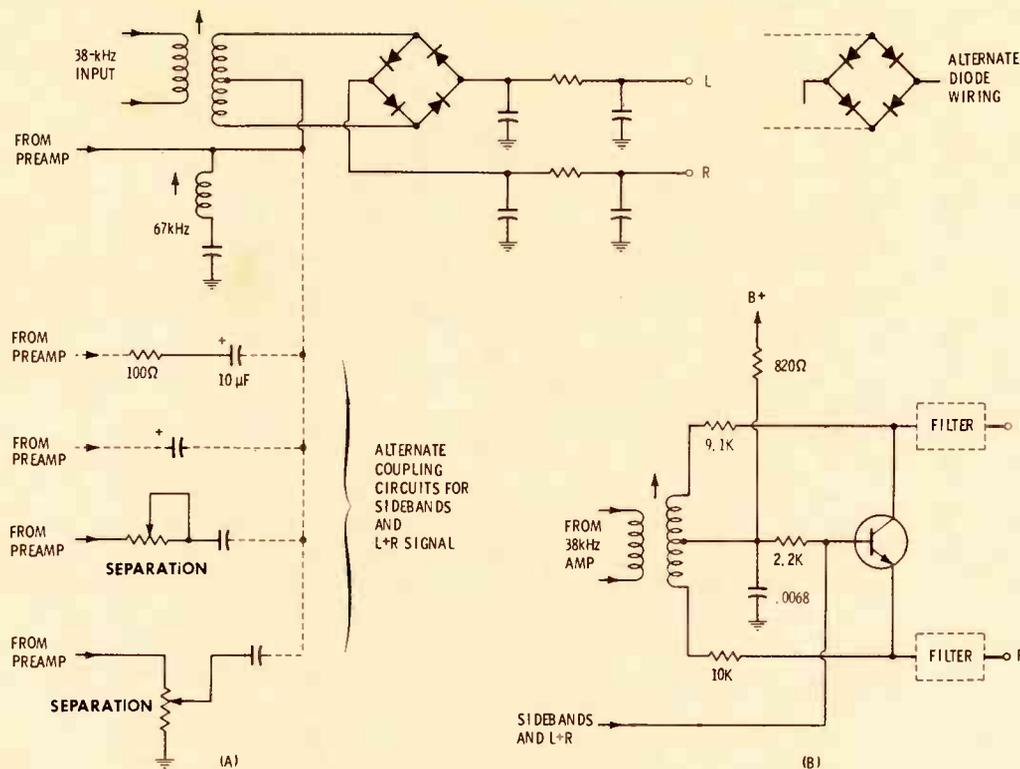


Fig. 3 Stereo detectors, shown with some of the feed paths that bring the sidebands and the L + R signals to the detector from the preamplifier. A) The alternate set of diodes is a regular bridge, which is used more often than the "ring" connection shown in the main diagram. B) This detector is used in certain Zenith chassis.

rier reinsertion at the stereo detector is by frequency-doubling the 19-KHz pilot itself. That certainly takes care of phase-locking. The primary differences among the systems illustrated in Fig. 2 are where and how much amplification occurs. There are two 19-KHz and one 38-KHz adjustments in Figs. 2A and 2B. There's only one of each in Fig. 2C.

The unit in Fig. 2D has an oscillator to produce the 38-KHz signal. However, it is phase-locked by the pilot carrier. Otherwise the stereo signals recaptured by the stereo detector would not be faithful reproductions of the originals.

Some of the frequency doublers are class-C transistor stages. Most often, though, a full-wave twin-diode setup is used, fed by the center-tapped secondary winding of a 19-KHz transformer. However, alignment is the same no matter what kind of stage is used for doubling.

The best thing about all these pilot sync systems is how simple they are to adjust. You just peak all the transformers. The main requirement is that the test signal you feed to the stages be extremely accurate. Either use a stable stereo

generator or the signal from an FM station that's broadcasting stereo.

The Sidebands and L + R Signal

The branch of the multiplex section that connects the preamplifier to the detector is the simplest (Fig. 3A). In many receivers it is nothing but a capacitor that couples the L - R sidebands and the L + R signals from the preamplifier to the stereo detector. In some, a resistor and a capacitor are wired in series, for frequency compensation. Only in a few models is an active stage used, and then it's an emitter follower, which is used to match a high-impedance circuit to a low-impedance one, but which doesn't add gain.

When the multiplex section has a **Separation** control, it is usually in this branch. Proper operation of the stereo detector depends on how much L - R sideband and L + R signal it mixes with the 38-KHz reinsertion subcarrier. So, a control that affects this ratio makes a good separation adjustment.

The stereo detector in Fig. 3A is drawn with some typical sideband/L + R paths, and a couple of separation controls are included. As you can see, they merely determine

how much sideband and L + R signal is fed to the detector.

You adjust a **Separation** control with only one channel of stereo modulation, usually the left. For an indicator, you connect an audio VTVM to the output of the right channel. Your regular VTVM, set for AC, is okay. Feed into the receiver a stereo signal that contains only left-channel audio information; be sure there is no right-channel audio present in the input signal. Adjust the separation for **minimum** left signal in the right-hand channel.

An unusual stereo detector, which uses a transistor, is shown in Fig. 3B. Its base is the input coupling device for the sideband/L + R signals. This is a balanced mixer. The sideband and L + R signals are applied in parallel with the two "branches" (emitter and collector circuits), and the 38-KHz signal is fed to them in push-pull.

Stereo Indicator Lamps

Some of these may need adjustments. The idea is to make sure they light during stereo programs and go out during mono programs. The adjustment is a sensitivity control.

You first make sure the lamp is out when the receiver is not tuned to any station. If it stays on, there's a defect that must be corrected before adjustment.

Then, tune in a strong station with a stereo program. Turn the adjustment, usually a potentiometer shaft, slowly until the lamp comes on. Then tune in a strong station with a monophonic program. If the lamp doesn't go out, reduce sensitivity slightly.

This is an easy adjustment, and you'll have no trouble getting it set.

Making It Quick and Easy

Aligning a stereo FM multiplex section can be reduced to a group of simple steps. The only problem then is to find the right coils.

The number of each coil often is marked beside it on the printed board. That and the schematic should be enough to keep you from turning the wrong cores.

Here, to help you take care of any multiplex alignment, is a procedure you can use for any of them:

- (1) Connect your DC VTVM to any point in the stereo detector that produces an increase in the meter reading as you increase the level of signal fed into the preamplifier. (Try it first with a 10-KHz audio tone.)
- (2) Feed an unmodulated 67-KHz (or other trap frequency) signal into the multiplex section input. A handy injection point, usually, is at the output of the FM detector of the receiver.
- (3) Adjust each trap for minimum reading on the VTVM. Be sure to feed in enough signal at each trap frequency to make a noticeable reading on the VTVM.
- (4) Feed in a precise 19-KHz pilot signal. An FM station with a stereo program in progress is the most accurate source you're likely to find.
- (5) Adjust all the 19- and 38-KHz transformers for maximum reading on the VTVM. Use as weak an input signal as you can while still getting a healthy VTVM reading.
- (6) Feed in a stereo signal that has only the **left** channel modu-

lated. You'll need a stereo generator for this, or a station that makes regular announcements on left channel only.

- (7) Connect an AC VTVM to the output of the **right** channel.
- (8) Adjust the separation control for minimum meter reading.
- (9) With a stereo program tuned in, back the stereo-lamp sensitivity control off till the lamp goes out. Then turn the control up just enough to light it again.

Coming Next Month

I have received many requests for help with solid-state troubleshooting. One circuit that seems to demand a lot of explanation is forward AGC, the type used most often in transistor IF stages. You find it in tiny transistor radios and in transistor TV sets.

In my next column I'll explain more carefully what forward AGC is, how it is developed and how it is applied. More important, I'll tell you how to find and eliminate the troubles that sometimes crop up in these circuits. ▲

TeleMatic

**SPEEDS
SERVICING**

ADMIRAL,
MAGNAVOX,
RCA AND ZENITH.

WITH
THE NEW


**MOLEX
EXTENSIONS**

ALL POPULAR
SOCKET - PLUG
ARRANGEMENTS

TeleMatic

Telematic Div. U. X. L. CORP.
BROOKLYN, N. Y. 11207. U. S. A.

Circle 17 on literature card

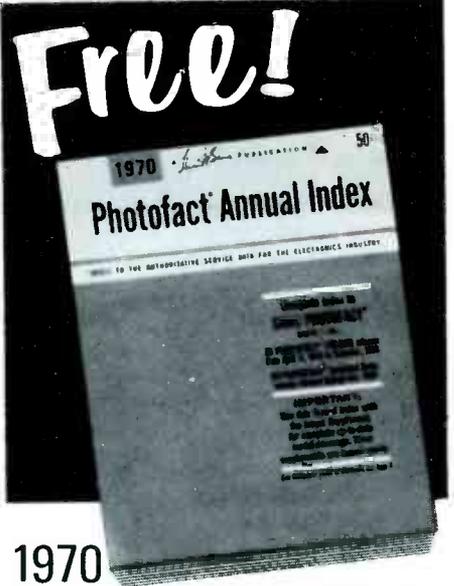

1970 Photofact® Annual Index

your instant guide to the world's finest troubleshooting data . . .

COVERS OVER 81,000 DIFFERENT MODELS:

- TV Receivers
 - Home & Auto Radios
 - Phonos & Hi-Fi
 - CB Radios
 - Tape Recorders
 - Record Changers
- Special Color TV Index*

Send today for this valuable 136-page index to PHOTOFACt troubleshooting data for virtually every model of electronic home-entertainment equipment produced since 1946!

PHOTOFACt provides *everything* you need in complete, uniform style for quick, effective repairs: Famous Standard Notation Schematics packed with the trouble-shooting details you need; Full Photo Coverage of all chassis views; Complete Replacement Parts Lists; Tube Placement Diagrams; Troubleshooting Charts; Alignment Instructions; CircuiTrace[®] for printed boards; Disassembly Instructions; Dial Cord Diagrams; Changer and Recorder "Exploded Views"—plus dozens of other great features.

Get your **FREE** copy of the latest PHOTOFACt Index to the service data you need!

Available from
your Sams Distributor,
or send coupon today

**FREE
INDEX**

Howard W. Sams & Co., Inc.
Dept. ESF-1
4100 W. 62nd St.,
Indianapolis, Ind. 46268


Send **FREE** 1970 Photofact Annual Index

Send full details on money-saving Photofact-of-the-Month Club subscription plan

Name _____
Address _____
City _____
State _____ Zip _____


Circle 18 on literature card

Chassis—Admiral H12
PHOTOFACT—876-1

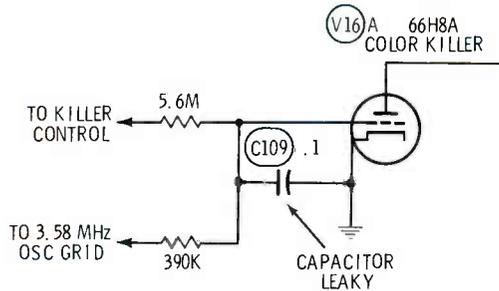


Symptom—No color
Cure—Check and replace leaky capacitor C109

Chassis—Magnavox T940
PHOTOFACT—none

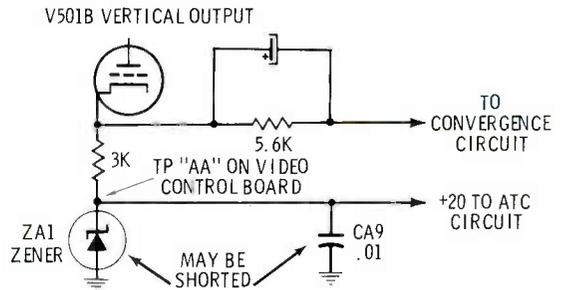


Symptom—No color
Cure—Check for +20 volts at TPAA on video control board; zener ZA1 or capacitor CA9 may be shorted if voltage is missing.

Chassis—Admiral 6H10
PHOTOFACT—949-1

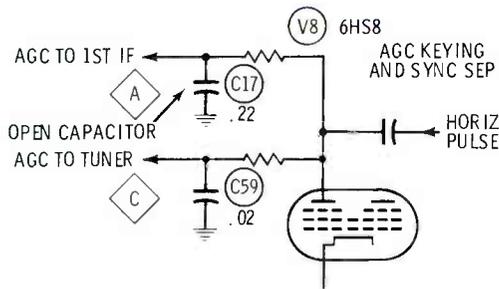


Symptom—Bad horizontal locking, picture dark on left side
Cure—Resolder or replace open capacitor C17

Chassis—RCA CTC40
PHOTOFACT—1030-2

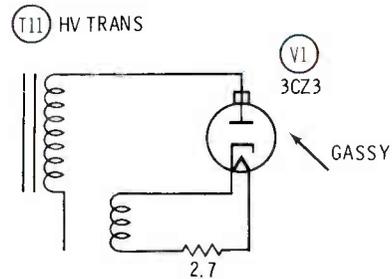


Symptom—Circuit breaker opens each time it is reset
Cure—Replace 3CZ3 high-voltage rectifier tube

Chassis—Admiral 4H12
PHOTOFACT—1049-1

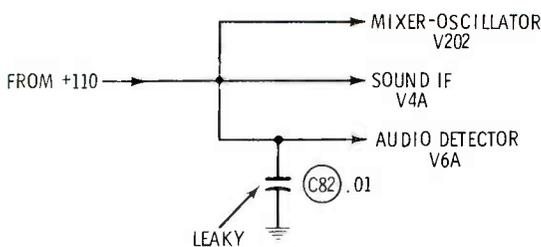


Symptom—All high-band channels dead
Cure—Check and replace leaky capacitor C82

Chassis—Magnavox T927
PHOTOFACT—963-1

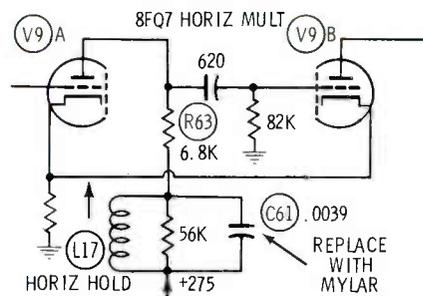


Symptom—Horizontal frequency drift
Cure—Replace C61 with a Mylar-dielectric type

Chassis—RCA CTC36
PHOTOFACT—1012-2

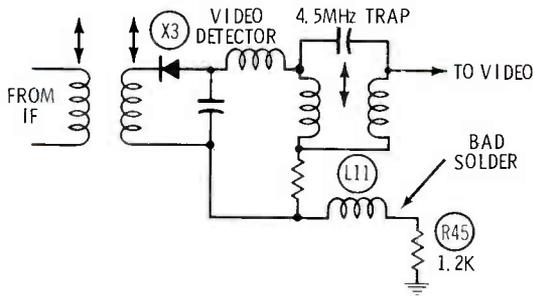


Symptom—Low sensitivity and overload on strong signals
Cure—Check and resolder connection on peaking coil L11

Chassis—Sylvania D12
PHOTOFACT—1045-2

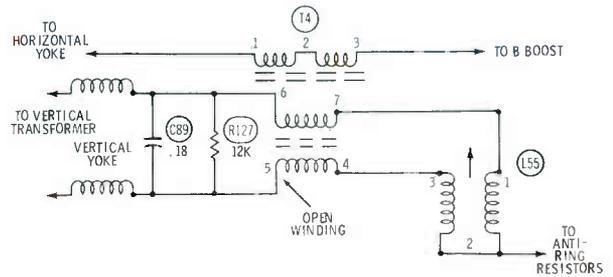


Symptom—Very little vertical deflection
Cure—Check the windings of T4 and L55 for open circuits

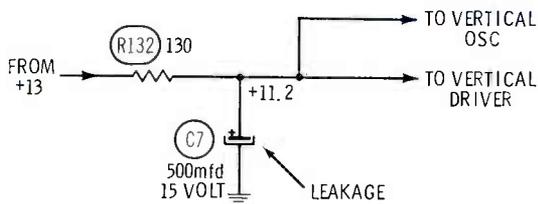Chassis—Sony TV710U and 720U
PHOTOFACT—1019-2




Symptom—Lack of height when first turned on
Cure—Replace leaky capacitor C7

Chassis—Sylvania D12
PHOTOFACT—1045-2

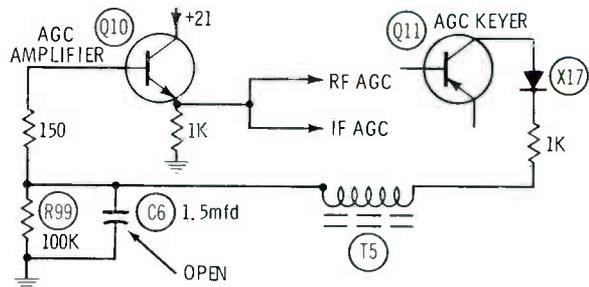


Symptom—Right half of picture black, left half washed out; sync missing
Cure—Check and replace open electrolytic capacitor C6

Chassis—Sylvania D12
PHOTOFACT—1045-2

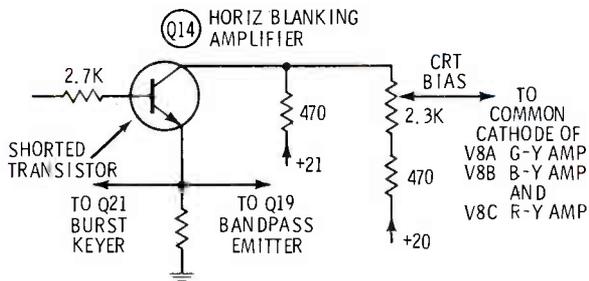

Symptom—Dark vertical bars; dark picture
Cure—Check and replace shorted blanker transistor Q14

Chassis—Zenith 16Z7C17
PHOTOFACT—1014-3

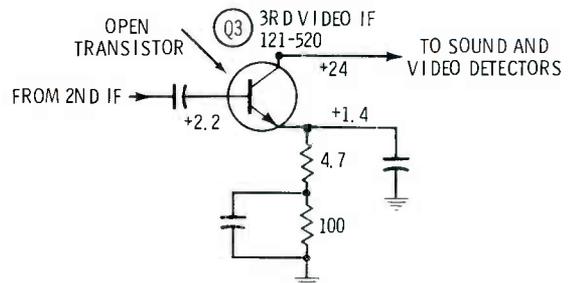

Symptom—Very low sensitivity and no snow off channel
Cure—If the emitter voltage is zero, replace 3rd IF transistor Q3

Test Equipment Input Impedance and Its Effects

The effects of resistive and reactive components combine vectorially to produce impedance, which varies with frequency. This article explains what impedance is, how much of it typical test instruments have, what its effects are, and how these effects can be reduced or eliminated.

by Robert G. Middleton

The effects of test-equipment input impedance must be taken into account if you are to avoid incorrect measurements and resultant false conclusions. Apprentice technicians are particularly apt to be misled, because the beginner does not always have a clear understanding of impedance.

From a very general point of view, impedance is merely an opposition to current flow. On the other hand, when the characteristics of impedance are detailed, we find that an impedance is considerably more complex than pure resistance. In the first place, resistance is a measure of opposition to DC current flow. The effects of test-equipment input resistance in DC voltage and current measurements will be discussed first.

Resistance-Loading Errors

More volt-ohm-milliammeters (VOM's) are used to measure DC voltage and current than any other type of electronic instrument. Accordingly, we will begin with an analysis of resistance-loading errors in DC voltage measurements with a VOM.

Various types of VOM's differ greatly in sensitivity; however, the 20,000 ohms-per-volt type is most common. As we know, the input resistance of a 20K ohm/volt meter is equal to the full-scale indication multiplied by 20,000 ohms. For example, if we are operating on the 2.5-volt range, its input resistance will be 50,000 ohms; if we are operating on the 10-volt range, its input resistance will be 200,000 ohms.

When a voltmeter is connected across a circuit, it diverts current from the circuit. If the voltmeter has a low resistance, it will draw an appreciable amount of current. This current produces an abnormal voltage drop across the internal resistance of the circuit, which subtracts from the normal voltage value across the test points. Consequently, the voltage reading is lowered. For example, some AGC circuits have a high internal resistance; in turn, a 20K ohm/volt VOM gives subnormal voltage readings, and these readings are different on each range, as shown in Table 1.

The equivalent circuit for testing an AGC circuit having an internal resistance of 180K ohms is shown in Fig. 1. Because the internal resistance of a series-parallel circuit

is different between various pairs of test points in a circuit that has high internal resistance, the voltmeter reading will change when the various test points are checked. For example, in Fig. 2 a higher value of voltage will be measured between test point X and ground, compared with the value measured between test point Y and ground.

If we use a VOM that has comparatively higher sensitivity, such as 100,000 ohms-per-volt, the circuit disturbance due to instrument loading is much less, and the voltage readings will be more accurate. Older technicians will remember how the sensitivity of DC voltmeters has been increased over the years. Table 2 shows the input resistance values on the 150-volt range and the full-scale current demand for typical voltmeters used in the past 50 years. The large increase in voltmeter sensitivity after 1924 was due to the advent of electron tubes. For obvious reasons, the vacuum-tube voltmeter (VTVM) gained increased acceptance in the 1930's.

Measurement of Input Resistance

If the input resistance of a DC voltmeter is not known, a simple test can be made to measure it. Connect the voltmeter across a battery or a power supply and note the scale reading. Then connect sufficient resistance in series with the voltmeter to reduce the scale reading to one-half of the former value. The input resistance of the voltmeter is equal to the value of series resistance that was inserted. This is called the "half-scale method" for measuring the internal resistance of a meter; the internal resistance of an instrument, as "seen" from its input terminals, is called the input resistance.

TABLE 1
 Typical AGC Voltage Indications with a 20,000
 Ohms-Per-Volt VOM
 (True AGC voltage is -7.8 volts)

Range (Volts)	Indication (Volts)	Actual Error (%)
2.5	-1.7	78
10	-4.1	47
50	-6.6	15

Next, let us consider the effects of the input resistance of a VOM when it is operated on its current ranges. A typical 20,000 ohms-per-volt instrument has the following input resistances on its various current ranges:

- 50 μ a 2,000 ohms
- 10 ma 25 ohms
- 100 ma 2.5 ohms
- 500 ma 0.5 ohm.

Observe that the input resistance is substantial on the first current range. If the circuit under test has an internal resistance of about 2,000 ohms or more, the indicated value of current will be less than the actual value. For example, the load resistor in Fig. 3A normally draws 66 μ a. However, if we insert the VOM in the circuit as shown in Fig. 3B the indicated value of current will be 38 μ a. Therefore, a direct measurement of current is impractical in this example. It is better practice to check the value of the load resistance with an ohmmeter; then, the voltage drop can be measured across the load resistor and the actual current flow calculated using Ohm's law ($I=E/R$).

In most cases, the input resistance of a VOM on its various current ranges is unknown. However, it is easy to measure input-resistance values with the aid of a small battery and a pair of precision ($\pm 1\%$) resistors. Connect one of the resistors into the test circuit as shown in Fig. 4, and note the current reading. Then, connect the second resistor in place of the first, and again note the current reading. (Resistance values should be chosen so that both readings can be taken on the same current range. For example, the first reading might be about $\frac{1}{3}$ of full scale, and the second reading might be $\frac{2}{3}$ or $\frac{3}{4}$ of full scale.) Calculate the input re-

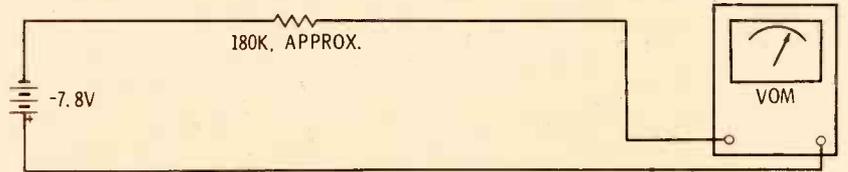


Fig. 1 Equivalent circuit of AGC circuit and values listed in Table 1.

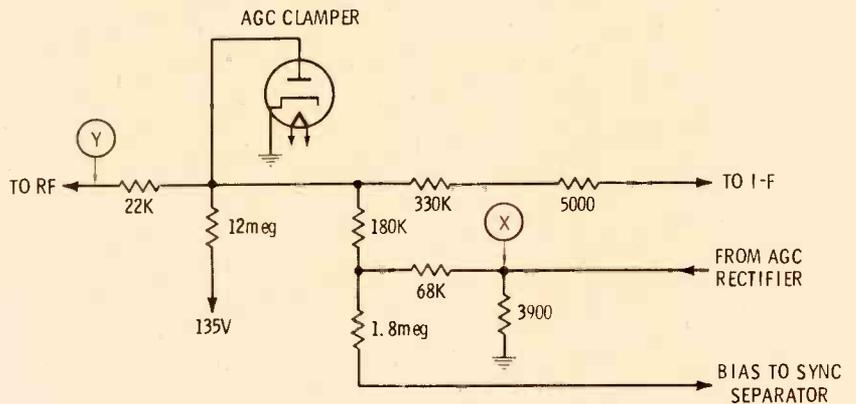


Fig. 2 A typical simple AGC circuit.

TABLE 2
 Increase in sensitivity of voltmeters

Time of manufacture	Sensitivity	Resistance	Current to deflect full scale
Before 1924	10 ohms per volt	1.5 k-ohms	100 ma
After 1924	100 ohms per volt	15 k-ohms	10 ma
Today	1,000 ohms per volt	150 k-ohms	1 ma
	20,000 ohms per volt	3 megohms	50 μ a
	200,000 ohms per volt	30 megohms	5 μ a

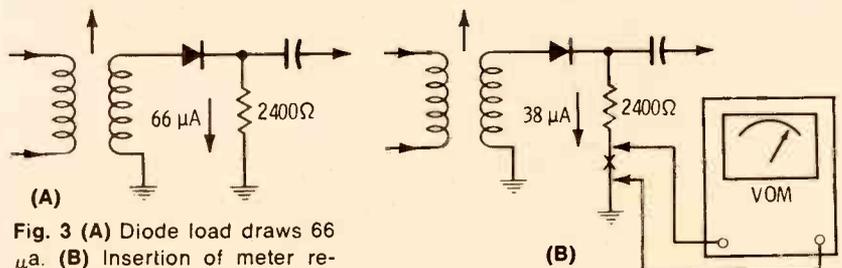


Fig. 3 (A) Diode load draws 66 μ a. (B) Insertion of meter reduces current to 38 μ a.

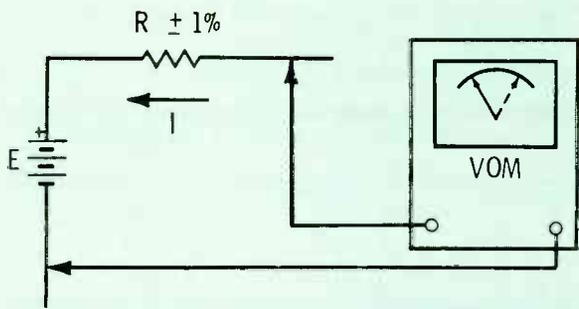


Fig. 4
Test setup.

sistance on the given current range as follows:

$$R_{in} = \frac{I_2 R_2 - I_1 R_1}{I_1 - I_2}$$

$$I_1 - I_2$$

where R_{in} is the input resistance, I_1 is the current measured with R_1 in the test circuit, and I_2 is the current measured with R_2 in the test circuit.

Impedance Characteristics

Impedance is measured in ohms; however, as stated earlier, impedance is more complex than pure resistance, because an impedance is a combination of resistance and reactance. A capacitor develops capacitive reactance, and an inductor develops inductive reactance. Reactance values are measured in ohms, although "reactive" ohms cannot be measured with an ohmmeter. Similarly, the number of ohms in an impedance cannot be measured with an ohmmeter. Fig. 5 shows some basic impedance configurations. Insofar as test-equipment input impedance is concerned, the arrangement in Fig. 5A is the most common.

The value of a reactance, whether it be capacitive or inductive, depends on two factors. As shown in Fig. 6A, the amount of capacitive reactance (X_C) varies **inversely** with frequency and/or capacitance; as frequency and/or capacitance increase, capacitive reactance decreases. The amount of inductive reactance (X_L) varies **proportionally** with frequency and inductance; as frequency and/or inductance increase, inductive reactance increases (Fig. 6B).

Since the value of a reactance changes with frequency, impedance also varies with frequency. For example, a 250-pf capacitor has a reactance of 636 ohms at 1 MHz, and a reactance of only 6.36 ohms at 100 MHz. Or, consider the parallel arrangement in Fig. 7; at a frequency of 1 MHz, the input impedance of the configuration is 450 ohms, approximately; however, at a frequency of 100 MHz the input impedance will be about 6.36 ohms.

Because impedance is a function of frequency, we must state either the chosen frequency or the resistance and capacitance values when specifying the input impedance of a test instrument. It is common prac-

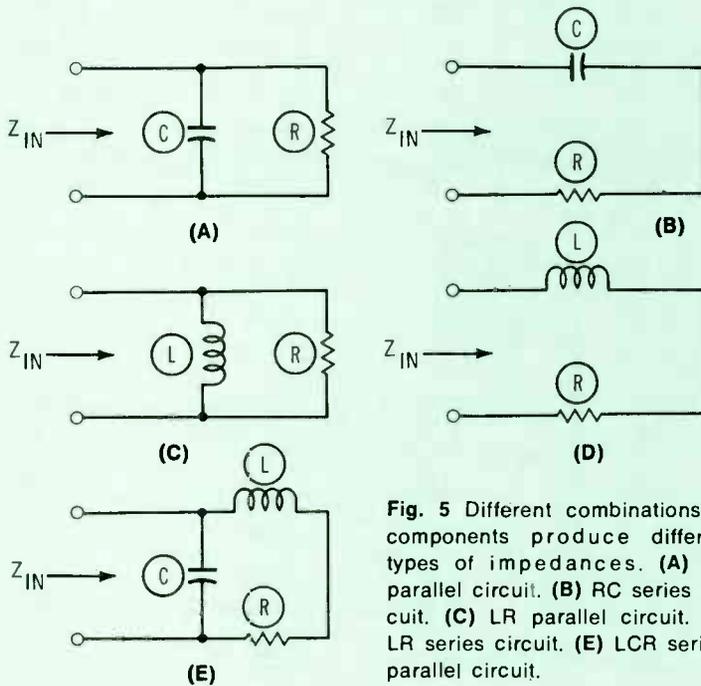


Fig. 5 Different combinations of components produce different types of impedances. (A) RC parallel circuit. (B) RC series circuit. (C) LR parallel circuit. (D) LR series circuit. (E) LCR series-parallel circuit.

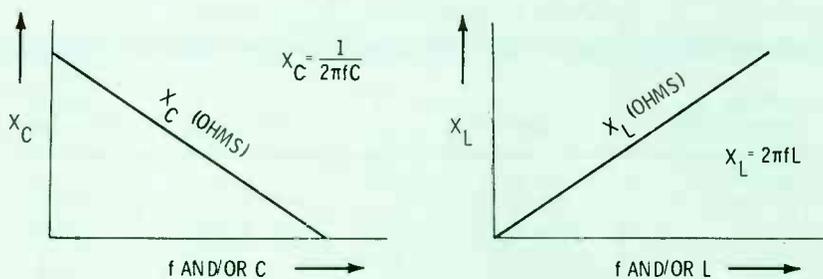


Fig. 6 Capacitive reactance varies inversely to frequency, while inductive reactance varies directly. (A) Capacitive reactance. (B) Inductive reactance.

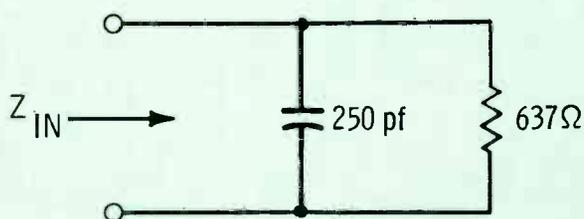


Fig. 7 637-ohm resistor in parallel with a 250-pf capacitor.

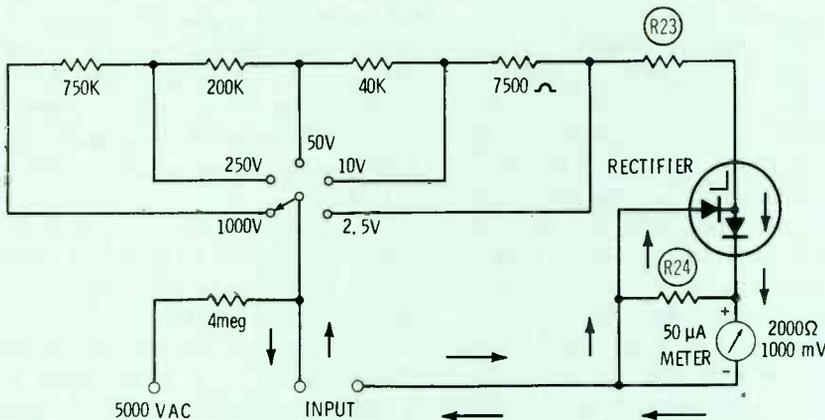


Fig. 8 Configuration of a typical AC voltmeter. (Courtesy, Simpson Electric Co.)

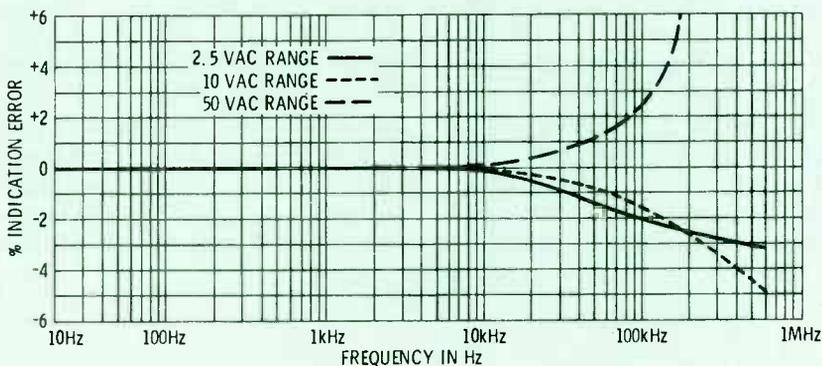


Fig. 9 Percentage of error versus frequency. (Courtesy, Simpson Electric Co.)

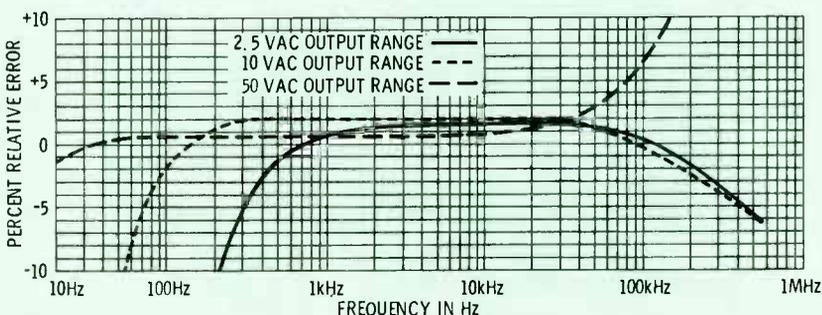


Fig. 10 Accuracy for output measurements with a typical VOM. (Courtesy, Simpson Electric Co.)

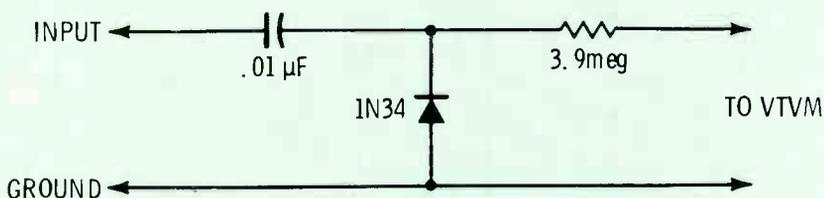


Fig. 11 Typical accessory RF probe for a VTVM.

tice to state the resistance and capacitance values. For example, the input impedance of a test instrument may be listed in a manufacturer's manual as 3 megohms shunted by 90 pf.

The input impedance of a test instrument can determine the useful frequency range of the instrument. For example, consider the AC voltmeter circuit shown in Fig. 8. It is evident that the configuration has input resistance. Although the diagram does not show it, input capacitance is also present in the form of stray capacitance between the test leads and between the various components and their connecting wires, and there is distributed capacitance in the moving coil of the meter movement. Also, although the diagram does not show it, there is inductance in the moving coil. The input impedance of the AC voltmeter can be represented by the LCR series-parallel circuit depicted in Fig. 5E. (Note, however, that the equivalent circuit changes on each position of the range switch.)

Any LCR circuit has a resonant frequency, at which the impedance value of the circuit is maximum. In a parallel LC circuit, there is an increase of current in the coil and in the capacitor at resonance; this is usually referred to as the "current magnification of a parallel-resonant circuit," and it is equal to Z (impedance) multiplied by the input current of the circuit. It causes an error in the reading at frequencies higher than the rated range of the VOM, as shown in Fig. 9. Note that the amount of error and the sign of the error depend on the meter range that is used. The change in sign occurs because the AC voltmeter circuit is actually a highly complex network when all of the stray capacitances are taken into account.

When a VOM is operated on its "output" function, a series capacitor is employed in the input lead to the AC voltmeter circuit. This is a blocking capacitor that has a value in the range of 0.1 or 0.25 mfd. With this series capacitance present in the input circuit of the instrument, the input impedance is changed, and the frequency characteristic of the VOM is shown in Fig. 10. As would be expected, the

input impedance increases rapidly at low frequencies, with the result that the meter reads low at frequencies below 30 Hz.

Input Impedance of VTVM

A VTVM has higher input resistance than a VOM on the lower DC voltage ranges. For example, a typical VTVM has an input resistance of 11 megohms on all DC voltage ranges, whereas a 20,000 ohms-per-volt VOM has an input resistance of 50,000 ohms on its 2.5-volt range, and an input resistance of 10 megohms on its 500-volt range. However, the VOM has higher input resistance on the higher DC voltage ranges than does the VTVM. Thus, the VOM has an input resistance of 30 megohms on its 1500-volt range. In other words, the chief advantage of a VTVM is its comparatively high value of input resistance on its lower DC voltage ranges.

The capacitive component of the input impedance of a VTVM also must be considered. The capacitance between a pair of test leads used

with a VOM is typically 25 pf. This is an objectionable amount of capacitance when measuring the DC voltage at the plate of a local oscillator, for example. That is, the input capacitance of the VOM detunes the oscillator considerably, and may "kill" the oscillator. In turn, an incorrect value of DC voltage is measured, because the circuit is not operating normally. On the other hand, a VTVM has a 1-megohm isolating resistor in its DC probe, which reduces the input capacitance to 1 or 2 pf. This is sufficiently low enough to permit accurate measurement of DC voltages in high-frequency circuits.

The input impedance of the AC voltage ranges of a VTVM often must be taken into account in routine service tests. A typical VTVM has an input resistance of 830K ohms and an input capacitance of 70 pf. The input resistance is sufficiently high so that it usually can be ignored. On the other hand, the shunt capacitance (70 pf) of a VTVM has a greater detuning effect than that imposed by a VOM.

In general, applications of the AC voltage function of a service-type VTVM should be restricted to vertical and horizontal-frequency waveform amplitude tests. However, there is one exception: The AGC keying pulse is so narrow that it cannot be measured with reasonable accuracy in most receivers by a VTVM.

For measurement of voltages in the range from 20 KHz to 100 MHz with a VTVM, it is advantageous to use an accessory RF probe. The circuitry for a typical probe is shown in Fig. 11. Its advantage is a high input impedance, which minimizes circuit loading and detuning. This type of probe has an input capacitance of 2.5 pf, which is about the same as the input capacitance of a DC probe for a VTVM. The probe shown in Fig. 11 rectifies an applied RF voltage; the VTVM is operated on its DC voltage function. The chief limitation of a probe that employs a semiconductor diode is its maximum input voltage rating, which usually is approximately 20 volts peak. Note that

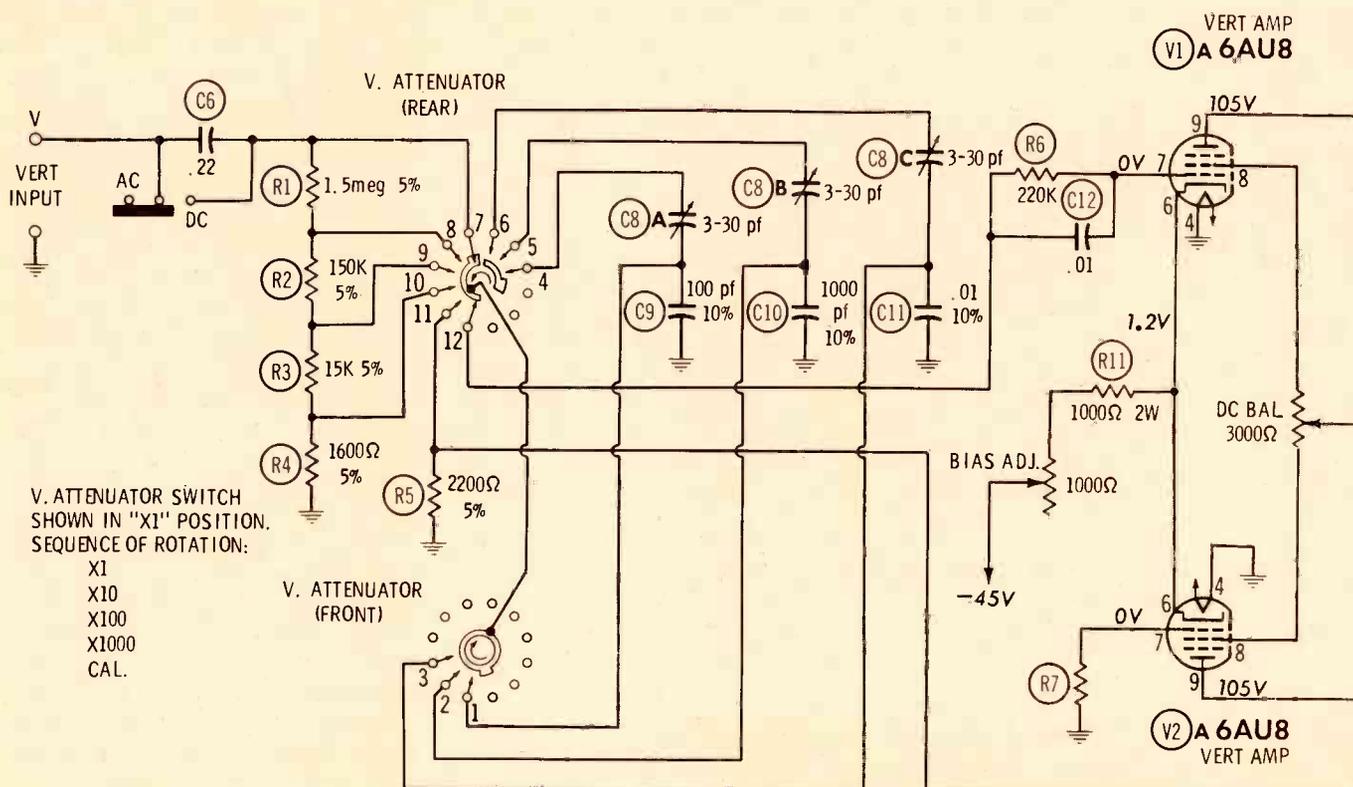


Fig. 12 Step-attenuator circuitry of vertical input of typical service-type scope.



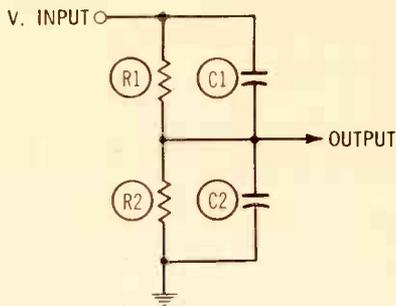


Fig. 13 Time constants R_1C_1 and R_2C_2 are equalized to provide constant value of input impedance at all settings of step attenuator.

Fig. 14 (A) Fast-rise waveform in a video amplifier. (B) Distorted waveform caused by input capacitance of scope.

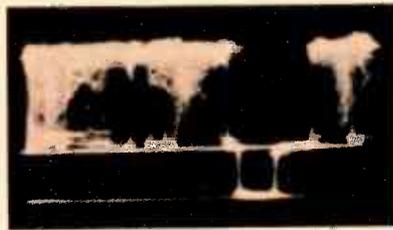

(A)

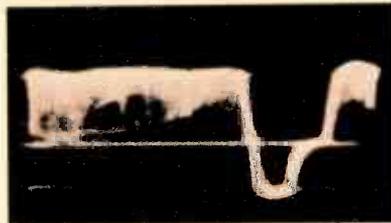

(B)

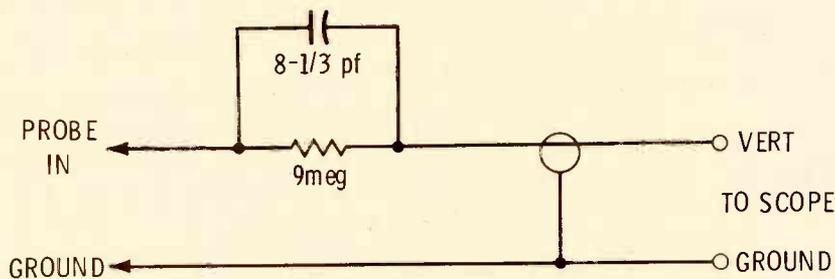


Fig. 15 Compensated low-capacitance probe.

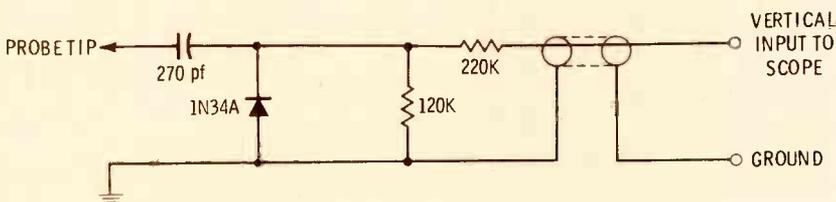


Fig. 16 Typical demodulator probe and specifications.

FREQUENCY RESPONSE CHARACTERISTICS:

RF CARRIER RANGE	500 kHz to 250 MHz
MODULATED-SIGNAL RANGE	30 to 5000 Hz
INPUT CAPACITANCE (APPROX.)	2.25 pf
EQUIVALENT INPUT RESISTANCE (APPROX.):	
AT 500 kHz	25,000 OHMS
1 MHz	23,000 OHMS
5 MHz	21,000 OHMS
10 MHz	18,000 OHMS
50 MHz	10,000 OHMS
100 MHz	5000 OHMS
150 MHz	4500 OHMS
200 MHz	2500 OHMS

MAXIMUM INPUT:

AC VOLTAGE	20 RMS VOLTS
	28 PEAK VOLTS

this type of probe cannot be used at frequencies below 20 KHz because of the increasing reactance of the 0.01-mfd. input capacitor at lower frequencies.

Oscilloscope Input Impedance

All wide-band scopes have compensated step attenuators in the vertical channel, as shown in Fig. 12. Individual attenuator sections are arranged as shown in Fig. 13 to provide decimal voltage division, and with equal time constants: $R_1C_1 = R_2C_2$. The sum of R_1 and R_2 is made equal on each step; hence, the scope has the same value of input resistance and capacitance on each step. For example, a typical service-type scope has an input resistance of 1 megohm and an input capacitance of 40 pf on each step. In practical applications a shielded input cable must be utilized, which adds another 35 pf to the value of input capacitance. In other words, when the scope is used with a shielded direct cable, it has an input impedance consisting of 1 megohm of resistance and 75 pf of capacitance.

A shunt capacitance of 75 pf can detune peaking coils and seriously disturb a high-impedance video-amplifier circuit. For example, the fast-rise sync pulse illustrated in Fig. 14A is seriously distorted when checked with a scope that employs a direct vertical-input cable (Fig. 14B). Observe that high-frequency components also are removed from the camera signal. In such a situation, the distortion caused by the value of scope input impedance might falsely be charged to the video amplifier. To avoid this type of circuit disturbance, technicians generally use a low-capacitance (L-C) probe. This is a form of accessory probe that makes a useful trade-off by exchanging signal voltage for a step-up in input impedance.

Fig. 15 shows a low-capacitance probe designed for use with a scope and input cable that presents an input impedance of 1 megohm shunted by 75 pf. Circuit analysis will show that the probe attenuates an applied signal to 0.1 of its original amplitude, while presenting an input impedance of 10 megohms and 8 pf, approximately. In other words, we lose 0.9 of the signal voltage through the probe, but obtain in return a

SOLVE YOUR TV REPAIR PROBLEMS WITH TV TECH AID

A monthly TV publication of actual repairs, and troubles encountered in OUR business. The information will be gathered from technicians, field reps, and all the leading manufacturers.

TV TECH AID will present up to 40 DIFFERENT TROUBLE SHOOTING CASES EACH MONTH. Each manufacturer will have its own page.

Each symptom will have a clearly marked schematic of the particular faulty stage. The faulty components, and corrections will be listed to aid in repair. No guess work.

It will contain current models, older models, circuit changes and modifications on various models as they occur.

The days of "Trial and Substitution" are over.

Time means money. Don't forget those valuable profits.

ONE repair is worth more than four times the investment.

Each monthly issue will contain a series of timely sheets and the cost to you is only \$7.95 for a full years subscription.

TV TECH AID

P.O. BOX 603
KINGS PARK, L. I.
NEW YORK 11754

ENCLOSED IS A CHECK OR M.O. FOR \$7.95 PLEASE SEND 12 ISSUE OF TV TECH AID

TO:

NAME

ADDRESS

CITY

STATE ZIP

Circle 19 on literature card

10-times step-up of input impedance. This increased input impedance permits most of the circuitry in both black-and-white and color TV receivers to be checked without noticeable circuit loading. Most low-capacitance probes are rated for a maximum applied peak potential of 600 volts.

Demodulator Probe Impedance


A demodulator probe, such as the one shown in Fig. 16, is a familiar item in TV service shops. It primarily is used for signal-tracing in IF amplifiers, and sometimes in inter-carrier-sound circuits. Demodulator probes also are used in certain color-TV visual-alignment procedures. As seen in the tabulation of Fig. 16, a demodulator probe has a rather low input capacitance—2.25 pf in this example. This input capacitance remains practically constant regardless of frequency; on the other hand, the input resistance of the probe decreases from 25,000 ohms at 500 KHz to 2,500 ohms at 200 MHz. This is a reasonably high input impedance, although it is not

sufficiently high to avoid the possibility of problems when testing 40-MHz IF amplifiers. In a 40-MHz IF amplifier, a capacitance of 2 or 3 pf can detune appreciably the plate-load circuit. If the circuit is detuned away from the frequency of the associated grid circuit, the only practical effect is a weakening of the IF signal. On the other hand, if the circuit happens to be detuned toward the frequency of the associated grid circuit, the IF stage will become regenerative, or may break into oscillation. Regeneration results in serious waveform distortion; oscillation causes the stage to block and, therefore, to kill the IF signal. Consequently, any trouble symptom indicated when a demodulator probe is employed should be confirmed by supplementary tests.

A demodulator probe badly distorts horizontal-frequency waveforms because of limited envelope response. Therefore, it is advisable to operate the scope on 30-Hz horizontal deflection when signal-tracing in IF amplifiers. This deflection rate provides display of the vertical sync pulse in the video signal. Since the vertical sync pulse is much wider than the horizontal sync pulse, the resulting pattern is reproduced with greater fidelity. Because of the detuning and loading effects produced by the input impedance of a demodulator probe, its usefulness is largely restricted to determining whether a signal is present or absent in the IF channel.

The input impedance of a demodulator probe is of less concern when it is used in many transistor IF circuits, because the collector-circuit capacitance is comparatively higher. A transistor also has a low input resistance, whereas a vacuum tube has an extremely high input resistance. The practical result is that a transistor IF stage is less likely to be thrown into oscillation by the input impedance of a demodulator probe. Moreover, the comparative waveform amplitudes at the input and output of a transistor IF stage will usually give at least a rough indication of stage gain. ▲

MODEL 3000

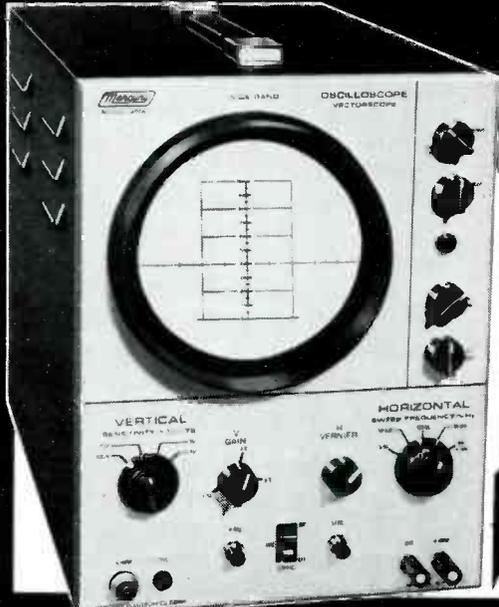

Mercury

NEW VECTORSCOPE
5" OSCILLOSCOPE

5 MHz HIGH SENSITIVITY
WIDE BAND 'SCOPE PLUS
Input-Compensated VECTORSCOPE

- Direct reading Graticule, instantly removable (2 supplied) plus special V input circuit
- Peak-to-Peak readings as easy as reading VOM or VTVM
- Vertical amplifier, 4.6 Mv RMS/Cm usable to 10 MHz for truly high sensitivity . . . 10 Hz to 5 MHz ± 3Db . . . 0.08 Microsecond rise time
- Horizontal amplifier, 5 Hz to 500 KHz
- Internal, external and line synch.

JUST 109⁹⁵ KIT
179.95
WIRED, probes optional.

Power req. 115V 50/60 Hz 85W.
11 x 9 x 16, 22 lbs.

All Mercury Test Equipment Guaranteed For One Full Year!

The Model 3000 is perfect for general purpose waveform observation applications, meeting all the requirements of technical schools, industry, electronic experimenters and development engineers.

Write for complete catalog of Mercury Test and Repair Equipment, and name of your nearest dealer.

MERCURY ELECTRONICS CORPORATION
315 Roslyn Road • Mineola, N.Y. 11501 • (516) 742-5400
CANADA: William Cohen Corp. • 8900 Park Ave. • Montreal-11

Circle 20 on literature card

This BOOK is a 'must'!
"Servicing Color TV With The Vectorscope" \$2.95



ELECTRONIC SERVICING. . .
the country's only magazine
devoted 100% to the
ELECTRONIC SERVICING
industry . . .

photofactTMbulletin

PHOTOFACT BULLETIN lists new PHOTOFACT coverage issued during the last month for new TV chassis. This is another way ELECTRONIC SERVICING brings you the very latest facts you need to keep fully informed between regular issues of PHOTOFACT Index Supplements issued in March, June, and September. PHOTOFACT folders are available through local parts distributors.

ADMIRAL

Chassis T2H3-1A, T3/
T11/T12/T13/T16H4-1A,
TH3/TH4-1A1068-1
Chassis 4K10-1A1071-1

CURTIS MATHES

53M023/033/043/053/063
(Ch. CMC-33)1070-1
10M1001074-1

OLYMPIC

9P90, 9P91 (Ch. 30720) ..1072-1

PANASONIC

AN-189D (Ch. N-919B) ..1074-2
AN-169, AN-179 (Ch.
N-919A)1076-1

PENNCREST

28831073-1

RCA

Chassis KCS176A,
KCS176B1075-1

SEARS SILVERTONE

Chassis 528/529.72840 thru
528/529.72849, 529/529.72860
thru 528/529.728681073-2

SHARP

CN-52T1076-2

SYLVANIA

Chassis D06-3, D06-41072-2

TRUETONE

EIS1015A-96,
EIS1017A-961071-2

WARDS AIRLINE

GEN-11160A (63-11160),
GEN-11260A (63-11260) ..1072-3
GHJ-15829A, GHJ-15849A,
GHJ-15859A1075-2
AM-FM Radio used in Models
GHJ-15829A/49A/59A1075-2-A

ZENITH

Chassis 16Z8C501074-3
Chassis 13A16, 13A16M,
13A16S1076-3

PRODUCTION CHANGE BULLETIN

ADMIRAL

4021P, 4027P
(Ch. K10-2A)1072-4

EMERSON

Chassis 120933S, 120933T .1075-3

SEARS

4110 (Ch. 564.80091)1072-4

SYLVANIA

Chassis B10-1, B10-2
(Codes 01, 02)1075-3

PLAY IT SAFE: Start now to save their hearts



Help your children form good health habits now to reduce risk of heart attack later:

- Maintain normal weight; obesity in youth may persist throughout life
- Encourage regular physical activity
- Serve them foods low in saturated fats;
- Teach them that cigarette smoking is hazardous
- Make medical check-ups a family routine

Do as a good parent should. Set a good example. Follow the rules yourself, and guard your heart, too.

**GIVE ... SO MORE
WILL LIVE**




HEART FUND

SKINNY,
YES.

undernourished?

HARDLY!

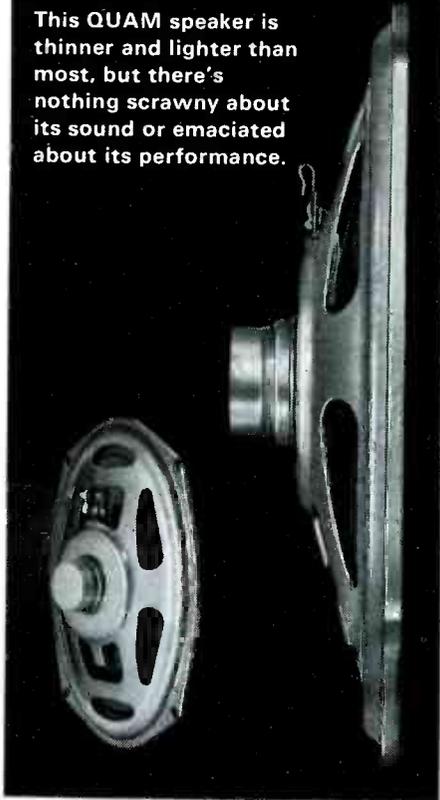This QUAM speaker is thinner and lighter than most, but there's nothing scrawny about its sound or emaciated about its performance.



It's one of 25 models in the Quam line that's being fed a special diet . . . an exclusive new high energy magnet material we call Q/8.

Q/8 provides more gap energy for less weight, so a .65 ounce magnet gives you the same performance as a full ounce of Alnico V. Ideally suited to Quam's high density cup-pot structure, Q/8 slims the speaker down in contour as well as weight—while delivering full, robust sound.

Q/8 magnets are exclusively available today on Quam speakers—part of our ongoing program of nourishing our customers first with the finest.

QUAM—always the Quality Line, for every speaker need.

QUAM-NICHOLS COMPANY
234 East Marquette Road
Chicago, Illinois 60637

Circle 22 on literature card


antenna systems report

Omni-Directional Antenna

Antenna Specialists' sector-phased electronic beam CB antenna, "The Scanner", has incorporated new control circuitry which permits omni-directional, instantaneous 360° scanning.

The effect is achieved through an additional switch position on the control box, located at the transceiver. In this position, the antenna works omni-directionally with a 2.5-dB gain in all directions. The operator may search and identify desired mobile or base stations and then switch electronically to the appropriate directional sector, in which the "Scanner" operates as an electronic beam.

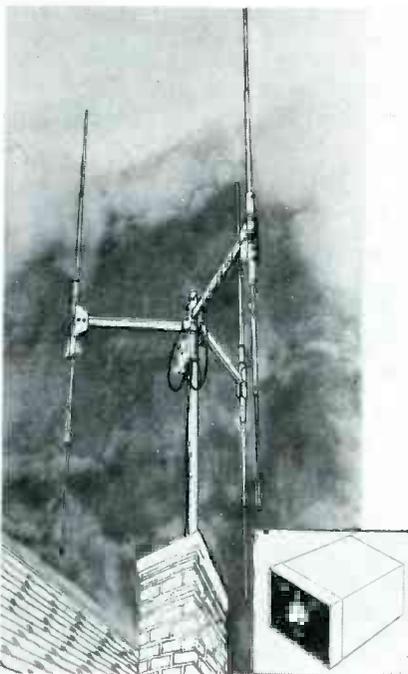In the beam mode, the antenna, identified as Model MR119 "Super Scanner," delivers 7.75 dB forward



gain with a front-to-back ratio of 23 dB, thus substantially eliminating interference and extraneous signals from the back side and greatly increasing directional range, according to the manufacturer. The beam effect is achieved electronically and, therefore, no mechanical rotor is needed.


Model MR119 weighs 17 lbs. and is designed to withstand wind forces of up to 100 miles per hour. The suggested price is \$79.95.

Circle 60 on literature card

Window TV Antenna

A new 82-channel, swiveling window antenna for VHF, UHF and FM has been introduced by JFD Electronics, Consumer Division.

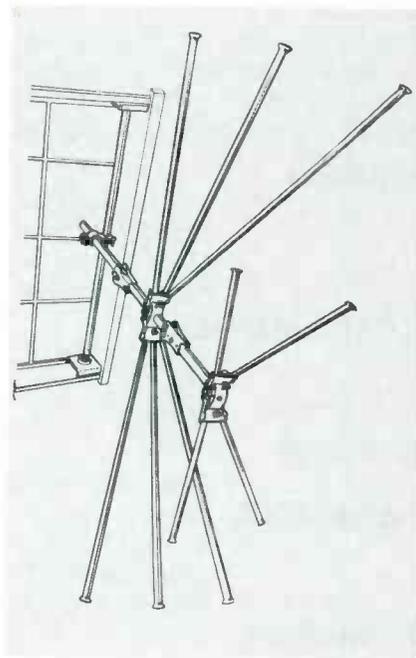The new antenna features separate swivels for UHF and VHF antenna elements. This reportedly



permits orientation for best reception, even if UHF and VHF channels are not located in the same direction. The Model C119-82 window antenna is designed for apartment buildings, hotels, institutions and wherever it is impractical to install a rooftop antenna.

JFD states that the antenna can be mounted in less than a minute through the use of a spring-loaded bracket that expands to fit any window frame up to 42 in. wide, and is locked into place by means of a single bolt. Extension bars are available to accommodate windows up to either a 5-ft. or 6-ft. width. To further simplify installation, UHF and VHF signals are carried into the room over a single twinlead, it is reported.

The C119-82 antenna is constructed of a golden-colored, heavy-duty aluminum alloy. All elements are held securely in place with snap-out spring contacts, assuring excellent electrical and mechanical contact, according to the manufacturer. This feature reportedly enables the new antenna to deliver steady, top-quality pictures, even when vibrated by high winds. High gain is provided by six VHF elements and four UHF elements.

The C119-82 window antenna lists for \$14.95. A VFH-only version, Model C119, lists for \$12.35.


Circle 61 on literature card

Omni-Directional Base Station Antenna

A new series of rugged professional base station antennas for the 25- to 50-MHz frequency range has been announced by the Antenna Specialists Company.

Designed to meet or exceed all EIA Standards for base station antennas (RS-329), the ASP-600 series reportedly will handle 500 watts of input power with reserve. A true 3 dB omni-directional gain provides more reliable total system operation.

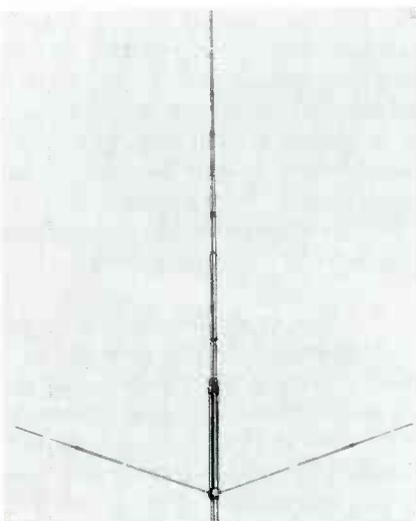For rugged wind-loading capabilities, a new high-strength aluminum alloy is used in the radial and support tubes. This new material, combined with the fiberglass reinforced coil jacket, which shares the flexural load of the wind, provides a 100-MPH load rating with a 1.65 safety factor, Antenna Specialists states. A molded neoprene suspension gasket separates the base tube



of the radiator and the transformer to seal out moisture. The braided transformer jacket design also provides ultraviolet stabilization characteristics.

Antenna Specialists reports that the ASP-600 series antennas are DC grounded to minimize precipitation static and reduce receiver noise interference, and that tuneable radials provide for maximum decoupling of RF. Three models in the series cover 25-28, 30-40 and 40-50 MHz. The list price of each is \$149.00.

Circle 62 on literature card ▲

Important **New** SAMS Books

Electronic Organs—Vol. 2

by NORMAN CROWHURST. Explains the fundamental principles of electronic organs, including theory, development, features and operation. In block diagram and schematic illustrations, the book shows what is inside an organ. Order 20754, only.....\$5.50

Space-Flight Simulation Technology

by LEX PARRISH. Presented as a primer covering the contributions, capabilities, and future potentialities of a very rapidly expanding industry. Deals in detail with simulation and the simulator—a training innovation without which manned space flight would be impossible. 144 pages. Order 20756, only.....\$4.95

How to Use Integrated Circuit Logic Elements

by JACK STREATER. Written for the engineer or technician who has not previously used or designed digital logic circuits. Also, electrical hobbyists will find this book interesting and understandable and will appreciate the fascinating logic circuits dealt with in the material. 136 pages. Order 20755, only.....\$3.95

'This Is Electronics' SERIES

A remarkable introduction to electronics, written under the direction of the Training Department of ITT Educational Services, Inc. These books impart to any reader a clear and sound understanding of the basics of electronics. All topics treated are short and easy to master; each includes a simple self-test.

Vol. 1. Basic D-C Principles. Covers: Wonderful World of Electronics; Components & Symbols; Matter and Electricity; Current, Voltage, & Resistance; Series & Parallel Circuits; Conductors, Semiconductors, & Insulators; Resistors; and Sources of D-C Power. Order 20657, only.....\$5.95

Vol. 2. Basic A-C Principles. Covers: Alternating Voltage & Current; Capacitors & Capacitive Reactance; Magnetism & Electromagnetism; Magnetic Induction; Measuring Instruments; Inductors & Inductive Reactance; Transformers & Inductive Circuits; A-C Circuits I; A-C Circuits II; Resonance; and Filters. Order 20727, only.....\$6.95

RECENT AND TIMELY BESTSELLERS

Computers and Artificial Intelligence

This book deals with basic computer principles, both analog and digital with emphasis on the latter. Describes in detail what computers can and cannot do, and is concerned with the binary number system and its adaptability to electronic circuitry. Fully discusses information theory and cybernetics, inductive and deductive logic, number systems, and the case for artificial intelligence. Order 20757, only.....\$3.95

ABC's of Radio-Frequency Heating

Explains the basic principles of heating by means of radio-frequency energy, covering both induction heating and dielectric heating. Describes the power supply sources; discusses the microwave range; fully covers the servicing of heating equipment. Final chapters are devoted to special applications of heating. Includes experimental projects. Order 20747, only.....\$2.95

1-2-3-4 Servicing Automobile Stereo

The "1-2-3-4 Method" is a simple, logical step-by-step process which helps do the servicing job in the easy way and the right way. This book first applies the Method to both mechanical and electrical equipment, and then proceeds to cover the electronic and mechanical principles of automobile stereo, fm multiplex, and tape cartridge systems. Finally, the book shows how to apply the "1-2-3-4 Method" to auto stereo systems. Includes a wealth of schematics, charts, and illustrations. Order 20737, only.....\$3.95

Record Changer Servicing Guide

This book provides a complete understanding of record changers, how they operate, and the various systems employed. Provides detailed instructions on how to track down troubles encountered in record changers and how to repair them in the fastest and most effective way. Order 20730, only.....\$3.95

NEW 2nd EDITION OF THE FAMOUS Audio Cyclopedia

by Dr. Howard M. Tremaine. This completely revised edition is the most comprehensive work on every phase of audio—virtually a complete reference library in a single volume. Includes the latest developments, right down to the newest solid-state and integrated circuits. Contains authoritative, concise explanations of thousands of topics in the fields of acoustics, recording, and reproduction. Over 1700 pages; 1600 illustrations. Truly the definitive reference work covering the entire audio art. Order 20675, only.....\$29.95

FM From Antenna to Audio

A complete picture of fm reception and receiving equipment, from the basic principles of fm to the latest developments in afc and tuning aids. Thoroughly explains the fm signal and describes the receiving system, beginning with the fm antenna, and progressing step-by-step through each section of the fm receiver. Covers receiver measurements and alignment procedures. Order 20723, only.....\$3.95

Auto Radio Servicing Made Easy, 2nd Ed.

Explains the circuitry of both new and old auto radios, covering each of the tube and transistor stages. Provides step-by-step troubleshooting and repair details; explains how to eliminate noise and interference, how to set the bias on output transistor stage without breaking circuit, how to determine correct bias on transistor stages, what to do about AVC trouble in transistor radios, etc. Order 20719, only.....\$3.95

More Bestselling Sams Titles

- AM-FM-TV Alignment Order 20602, only.....\$3.95
- Color-TV Servicing Guide Order 20358, only..... 4.25
- Transistor Color-TV Servicing Guide Order 20693, only..... 4.50
- Symfact® Guide to Color-TV Servicing Order 20710, only..... 3.95
- Antennas and Transmission Lines Order 20716, only.....\$7.95
- Closed-Circuit Television Handbook, 2nd Ed. Order 20726, only.....\$5.95
- Using Scopes in Color-TV Order 20718, only..... 3.95

HOWARD W. SAMS & CO., INC.

Order from any Electronic Parts Distributor, or mail to Howard W. Sams & Co., Inc., Dept. ES-1 4300 W. 62nd St., Indianapolis, Ind. 46268

Send books checked at right. \$_____enclosed.
 Send FREE 1970 Sams Book Catalog

Name _____
PLEASE PRINT

Address _____

City _____ State _____ Zip _____

- 20754
- 20756
- 20755
- 20657
- 20727
- 20757
- 20675
- 20723
- 20719
- 20747
- 20737
- 20730
- 20602
- 20358
- 20693
- 20710
- 20716
- 20726
- 20718

Circle 23 on literature card

How Defects Affect the Operating Voltages and Parameters of Tube Circuits

by Bruce Anderson

Many of the servicing procedures we find in servicing literature direct the technician to the general area of the problem and end by suggesting that he measure a few voltages to isolate the trouble to a specific component. In this article, we shall examine just how the voltages on tube elements can become abnormal, and also the effects on circuit performance which may result from off-tolerance components.

The Filament Circuit

When TV receivers with series filaments first appeared on the market, a lot of discussion centered around improper filament voltage. When these receivers first were designed, tube technology simply had not advanced to the point where 13 to 18 tube filaments could be connected in series and each drop its exact specified voltage. True, at the time of manufacture the hot-filament resistance of the tubes could be expected to be within fairly close tolerance limits, but after a few months of use, a horizontal-output tube, for instance, might drop more or less than the specified 25 volts when the filament current was 300 milliamperes.

If its filament resistance increased by, perhaps, 25%, the tube would drop in the neighborhood of 31 volts, thereby reducing the filament voltage available for the remaining filaments in the string.

Whichever of the other tubes happened to be in the most critical circuit then would no longer perform properly and often were replaced, while the real culprit remained precisely where it was, to cause a callback in a month or so.

Of course, better design of tube filaments makes this type of trouble relatively rare nowadays, but other failures which result in reduced filament voltage still do happen.

Referring to Fig. 1, suppose that the bypass capacitor becomes leaky. The result is that the resistance of the complete filament circuit is reduced, increasing the current through the filaments of V1 through V9. (For simplicity, V3 through V8 are omitted.) Accordingly, the voltage drop across each of these filaments will be increased, shortening their lives, but possibly not leading to any immediate reception problems. However, the voltage drops across the filaments of V10 and V11 will be decreased, reducing their temperatures and ultimately reducing the cathode emission. This, of course, has about the same result as if the tube were weak and, unfortunately, installing a new tube normally will remove the symptoms—for a month or so.

How, then, should this type of problem be avoided? Since the object of being in the TV servicing business is to make money, it is impractical to make exhaustive tests every time a tube is replaced. Even testing those tubes which are replaced is not particularly satisfactory, because a tube tester often will indicate that a tube is good when it

is not, thereby starting you on a wild-goose chase. Because of this, callbacks for this type of problem must be expected; however, when replacing a specific tube for the second time, it is worth the effort to do a bit of investigating. After all, the second callback is going to cost just as much money as the first one—plus, it probably will drive away the customer.

If a set of tube socket extenders and some sort of inexpensive voltmeter are kept in the service truck, it will take but a few minutes to check the filament voltage of the tube in question. If it is less than 95% of the rated value, assuming the line voltage is correct, a filament-voltage problem should be suspected. Since meters which regularly ride about in the service truck are likely to have inaccuracies greater than $\pm 5\%$, several filament voltages in the string will have to be checked to obtain any useful information. Referring again to Fig. 1, if the filament voltage of V10 (the tube which is causing the trouble in this example) is low, also check the filament voltage of V11 and a couple of the other tubes. If the filament voltage of V11 is low and all of the others are slightly high, it is almost certain that there truly is a filament-voltage problem. Most meters, even though inaccurate, will read consistently in the same direction on one particular range.

The Cathode Circuit

Abnormal cathode voltage on a tube can be either the cause or the result of abnormal tube operation. Referring to Fig. 2, all of the bias supplied to the tube is cathode bias, since the control grid is at DC ground potential by virtue of the low resistance of the input transformer. Therefore, if the cathode voltage is out of tolerance, it is reasonable to assume that the fault is located in the cathode circuit. Since the design cathode voltage is 1.5 volt and the cathode resistance is 150 ohms, a simple calculation

$$(I = \frac{E}{R})$$

indicates that the normal cathode current is 10 ma.

If the cathode voltage is greater than 1.5 volt, either there is additional cathode current or the value of the cathode resistor has in-

creased. A large increase in screen voltage would increase the cathode voltage slightly, but the most likely fault is an above-tolerance cathode resistor.

In the same fashion, a decrease in cathode voltage also is likely to be caused by a change in cathode resistance; but in this case, the resistance would be decreased. (A less likely cause is an increase in the value of the screen resistor, causing a net decrease in cathode current.) A failure which causes the same effect as a decreased cathode resistor is a leaky cathode-bypass capacitor. By disconnecting the capacitor from the resistor and checking the resistance of each, it is possible to determine which is at fault.

The Control-Grid Circuit

The bias voltage present on the control grid of a vacuum tube can be developed in one of two fashions, or by a combination of them. If it is derived from some source external to the tube, this source should be suspected if the bias is abnormal. On the other hand, grid bias may be developed by the grid current of the tube itself; in which case improper drive may be the result of a change in this resistance, or from the introduction of an unwanted voltage.

The circuit shown in Fig. 3 is typical of the horizontal-output circuit used in many color receivers. An analysis of how the grid bias is developed and the types of failures that can change this bias will help you understand the bias systems of nearly all the circuits in a television receiver.

Grid-leak is the principal method of obtaining bias for the horizontal-output stage. So, for the moment, assume that the small amount of fixed bias obtained from the 140-volt supply through R1 is not present, and the high end of R1 is returned to ground, rather than to B+. Each time the grid is driven positive by the signal, it draws some grid current, which charges C1 to a negative potential. Since the time constant of R1 and C1 is long compared to the pulse rate, a constant level of DC bias is developed. If the amplitude of the driving pulses is decreased, less grid current flows and the bias decreases. This is desirable up to a point. But if the

drive is reduced radically, the bias will decrease to a point where the cathode current of the tube will exceed the maximum rating for the tube, and the tube will be damaged. In an extreme case, such as oscillator failure and complete loss of drive, the bias will fall to zero and the tube will be damaged in a matter of seconds, unless overload protection is provided.

Although loss of drive is the most frequent cause of loss of bias in grid-leak-biased circuits, leakage of the coupling capacitor (C1 in Fig. 3) is another possibility. In effect, this connects the plate supply of the preceding stage to the control grid via the leakage resistance of the capacitor. If this leakage resistance is quite high, the bias may shift only slightly, causing excessive current and shortened tube life, and also can cause distortion of the signal. Of course, a leaking coupling capacitor will cause a bias shift in any grid circuit that has fairly high DC resistance to ground.

Excessive bias in a grid circuit employing grid-leak bias is not apt to be caused by excessive drive, because few malfunctions can occur which will allow excessive drive.

The most likely cause of excessive bias is an increase in the value of the grid resistor. When the grid resistance becomes excessive, a condition known as grid blocking results, which causes the tube to become biased near cutoff. If a meter is connected from grid to ground, the shunting effect of the meter often will be sufficient to restore nearly normal operation—a handy point to remember. Naturally, grid blocking can occur in circuits that are not grid-leak biased.

R1 in Fig. 3 is connected to the 140-volt supply, instead of ground, to slightly reduce the grid bias and increase the output power from the tube. This, in turn, increases the scanning width and the high-voltage power. Since R1 is quite large, nearly all the supply voltage is dropped across it, and the actual grid voltage is only a little less negative than it would be if R1 were grounded. However, the circuit is there for a purpose, and if R1 changes value, the bias will be upset and width will be affected.

In various color receivers, a negative supply voltage is required for some circuits, such as the ACC or chroma-blanking circuit. Rather

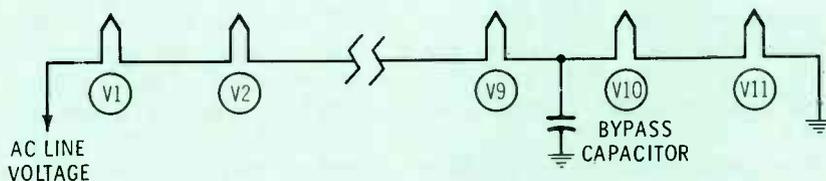


Fig. 1 Typical series filament string.

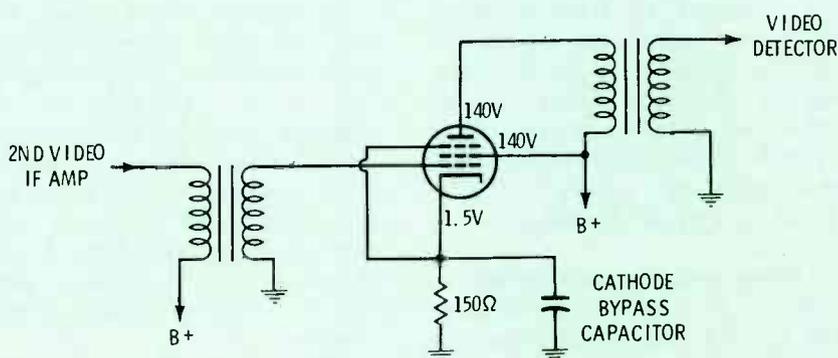


Fig. 2 A transformer-coupled amplifier.

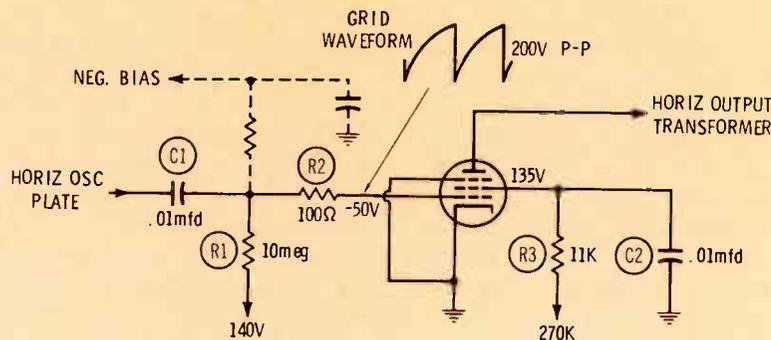


Fig. 3 Typical horizontal-output amplifier.

than construct a negative power supply, it is customary for some of the manufacturers to obtain this negative voltage from the horizontal-output grid circuit. By "tapping" the grid circuit, as shown by the dotted-line connections in Fig. 3, an unloaded negative supply of about 50 volts may be obtained for these purposes. This is a frequently overlooked source of problems, because the circuit which uses this negative voltage may be more critical than the horizontal deflection system. In this case, insufficient drive to the horizontal output stage might produce trouble symptoms in the ACC circuit rather than in the deflection system.

The horizontal-output circuit has been discussed in detail because it demonstrates both methods of obtaining grid bias, and because it is subject to nearly all the bias failures that can occur in any of the other circuits in a TV receiver. Other stages which use some form of grid-leak bias are the various oscillators—horizontal, local, color reference and vertical—and the sync separator. The RF amplifier of the tuner, usually two of the IF amplifiers, the chroma amplifier and the color-killer circuit normally obtain bias from sources external to themselves, but dependent on signal level. Most other stages are fixed-biased, or cathode-biased.

Plate and Screen Circuits

If the control-grid-to-cathode voltage of a tube is abnormal, the cathode current will be abnormal, and the plate and screen voltages will be incorrect. Because of this, it is unwise to assume that the cause of a trouble symptom is in either

of these latter circuits until it has been determined that the bias is within specifications. If the bias is correct, reduced plate or screen voltage may be caused by an increase in the value of a plate-load resistor or a screen-dropping resistor. Conversely, an increase in voltage on one of these elements indicates a decrease in the value of the associated resistor. It is assumed, of course, that the power-supply outputs are normal.

It should be remembered that in some types of tubes if either the plate or screen voltage is very far off value it will affect the voltage on the other element. For example, a plate-load resistor greatly increased in value will cause the plate voltage to be reduced. This, in turn, will result in decreased plate current, although not in proportion to the reduction in plate voltage. The cathode current of a pentode tube is relatively independent of plate voltage, and some of the normal plate current now will flow to the screen grid, reducing the screen voltage.

On the other hand, a decrease in the value of a screen-dropping resistor will tend to increase the cathode current, probably increasing both the plate and screen currents. The increased plate current will cause the plate voltage to be lower than normal, but the screen voltage may be only slightly high, since the increased current partially offsets the effect of the reduced dropping resistor.

Dynamic Considerations

Thus far, the static conditions of a stage which is operating with off-tolerance circuit components have

been discussed, since these are the symptoms most likely to be discovered in routine troubleshooting with a meter. Nevertheless, it is useful to have some knowledge of how these component failures will affect the ability of the stage to perform its normal function.

We already have considered the effect of a shorted or leaking capacitor on a circuit. It also is possible that a capacitor may lose some of its capacitance or become completely open. If it is a coupling capacitor, the result is attenuation of the signal, particularly the low-frequency components; this will affect the bias if grid-leak bias is employed (as in a horizontal-output stage).

If a cathode-bypass capacitor loses its capacitance, the voltage measured at the cathode may not change noticeably. With proper bypassing, the cathode voltage is essentially DC; in the absence of the capacitor, the voltage is the sum of the DC voltage dropped across the resistor and the AC signal developed across this same resistor. But since a meter will average the signal voltage to zero, this "ripple" may go undetected. However, the stage will not amplify as it should because of the severe degeneration of the unbypassed cathode. If the cathode is only partially bypassed (some capacitance lost), low-frequency response will deteriorate noticeably.

One method of detecting improper bypassing is to use a DC scope for all voltage measurements, since it will indicate signal voltage (AC) if any is present. If such a scope is not available, a large-value blocking capacitor in series with the leads of an AC meter will allow signal to be measured. A properly bypassed cathode seldom will have a ripple voltage (signal voltage) in excess of 10% of the specified DC voltage. It is assumed, of course, that signal is present when the measurements are being made.

Insufficient or no bypassing of a screen grid also can result in reduced gain, although the reasons are less obvious. Referring to Fig. 3 once more, if C2 were removed from the circuit, the voltages measured on the tube elements would not be greatly affected, but reduced high voltage and insufficient width

might be observed. As the control grid is driven positive, the screen current normally increases; but, without the bypass capacitor, this causes the screen voltage to decrease, tending to decrease the cathode current and also the plate current. Accordingly, there is less energy in the output circuit. Conversely, on the negative-going excursion of the input signal, the decrease in cathode current causes the

screen voltage to increase if it is unbypassed, and this has the tendency of increasing the cathode current. Therefore, the effect of an unbypassed screen grid is always to oppose the signal at the control grid and, hence, to reduce the effective gain of the stage.

Another effect of an unbypassed screen results from the fact that considerable signal is present across the screen-dropping resistor (which

now is actually a **screen-load** resistor). This signal may be radiated around the chassis, producing various types of interference, and sometimes causing the stage to break into oscillation.

The dynamic effects of a change in bias may be slight or rather drastic, depending on the amount of shift, the characteristics of the tube and the particular circuit involved. If the tube is of the sharp-cutoff variety, the amount which it amplifies remains fairly constant between the points of cutoff and saturation, and gain is not seriously affected so long as operation remains within these limits. However, if the bias is shifted so that the tube is cut off or saturated during part of the input cycle, serious distortion will follow.

Suppose that a certain tube cuts off with 10 volts of bias. If it is operated at a bias level of 5 volts, a 4-volt peak-to-peak signal will cause the instantaneous grid voltage to vary from -7 volts to -3 volts (Fig. 4A). Amplification remains fairly constant throughout this range of grid voltages and the signal will be amplified with little or no distortion. If the bias, or operating point, were shifted to either -7 volts or -3 volts, the operation would not be seriously affected, although the voltage measured at the plate would change.

If the bias, or operating point, were shifted to zero volts, as shown in Fig. 4B, the instantaneous grid voltage would vary from -2 volts to +2 volts, and the tube would be in saturation during the positive half-cycle. This would cause the negative half-cycle of the output to be amplified very little, causing lowered gain and severe distortion. Obviously, a shift in bias to -9 volts would clip the positive half-cycles of the output.

If the tube just discussed had been a remote-cutoff tube, distortion would result in the same manner as cutoff and saturation were reached. Even if these extremes are not reached, the amplification of the stage would depend on the bias. For example, in an AGC-controlled IF amplifier, insufficient bias will increase the gain, causing the picture to have excessive contrast. If the bias is reduced to the point where the tube saturates on peak-

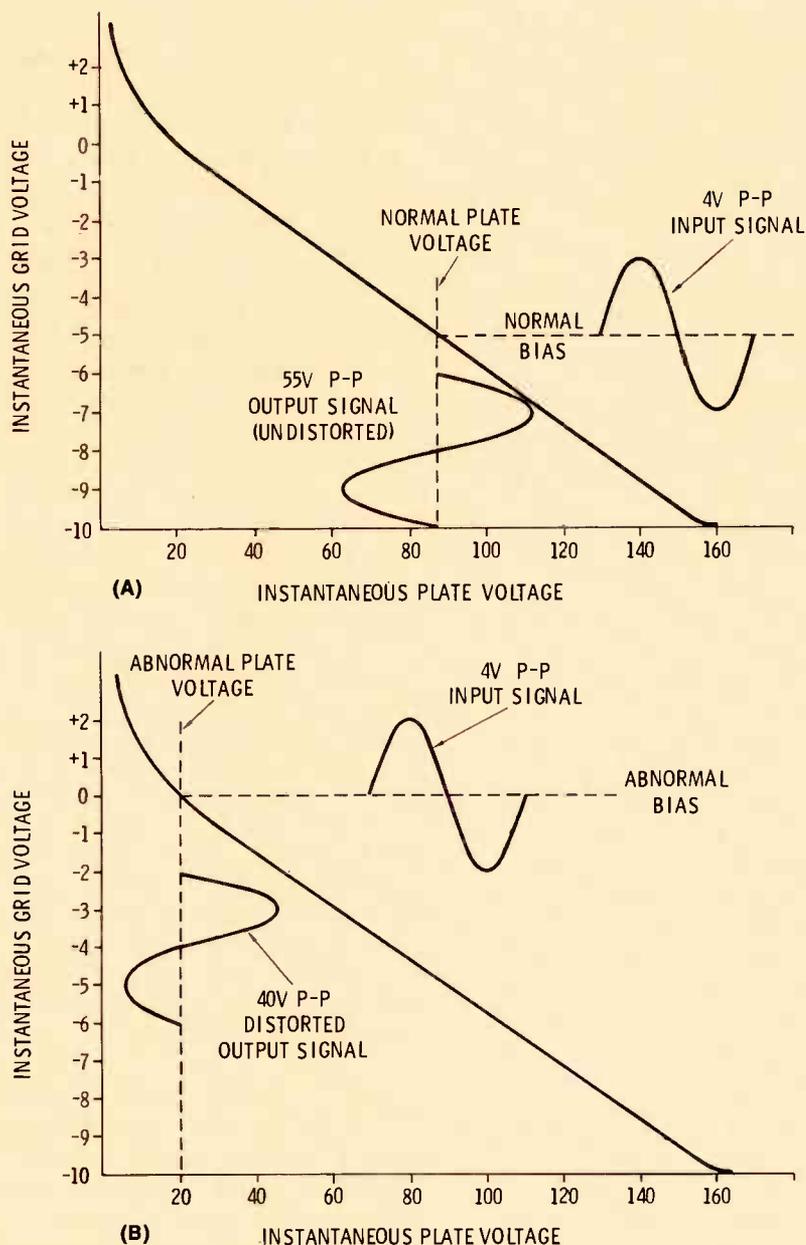


Fig. 4 The effects of bias on gain and distortion. **(A)** Operating point at -5 volts. **(B)** Operating point at 0 volts.

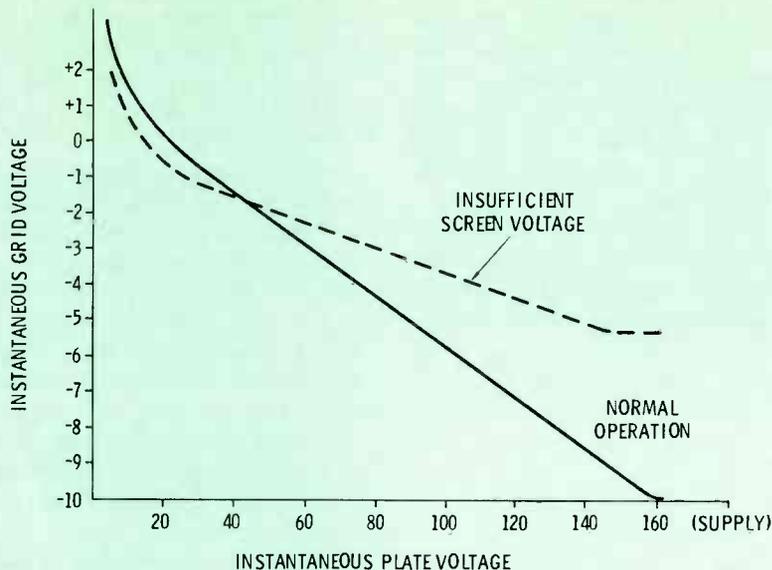


Fig. 5 The effect of insufficient screen voltage on amplification in a pentode.

amplitude signals, the sync pulses will be amplified less than the lower-amplitude video signals, and sync compression will result.

Increasing the value of the screen-dropping resistor of a pentode will reduce the screen voltage, thereby decreasing the dynamic operating range of the tube; it will cut off with less bias and saturate more quickly, as shown in Fig. 5. The effect of an excessively large plate-load resistor in a triode circuit is much the same, with one additional complication: As the plate load resistance is increased, the effect of the stray shunt capacitance becomes more pronounced and high-frequency response is reduced.

If the plate-load resistance of a pentode is increased, gain will tend to increase to a point, but the voltage at the plate will be reduced because of the additional drop across the resistor. Obviously, if the quiescent plate voltage is reduced from, say, 75 volts to 25 volts, the possible maximum amplitude of the negative half-cycles of signal is reduced from slightly less than 75 volts to slightly less than 25 volts; the plate cannot swing negative with respect to the cathode if a resistive load is used. In certain RF power-amplifier applications, it is possible for the plate to actually swing negative with respect to the cathode, but this is beyond the scope of this article.

Summary

Some of the effects of changes in value of the components associated with tube circuits have been discussed in this article. These component changes will affect both the voltage present at the various tube elements and the amplifying ability of the circuit.

The changes in tube-element voltages are probably of greater concern and of more practical interest to the servicing technician, since these are more readily utilized in actually troubleshooting the instrument.

It should be remembered that the effects described here are general in nature; how much circuit voltages deviate from normal depends on such factors as the degree of failure of a component; how much the value of the component changes, and in which direction; the normal operating potentials; the presence or absence of feedback loops; the purpose of the circuit; etc. For example, a 5-megohm grid resistor is normal for a sync separator, because this high resistance causes a large amount of self-bias to be developed; but this much resistance in the grid circuit of a video amplifier would be highly abnormal, and the bias developed would cause severe distortion.

In spite of the vast differences in the ways tubes may be used, there are some patterns of behavior which

are consistent. If the grid voltage, or bias, of a particular tube is incorrect, it is reasonable to assume that the trouble lies before the circuit of the tube itself. It may be because of improper bias supply, as in the case of AGC bias supplied to an IF amplifier, or it may be the result of insufficient drive, as in the case of a horizontal-output tube. In any circuit using a coupling capacitor, this component should be checked for leakage if the bias is more positive than specified. It is unlikely that faulty components in the plate, screen or cathode circuits of a tube will affect the grid voltage, but the opposite is not true. In fact, if the control-grid voltage is wrong, it is probable that all the other element voltages also will be affected.

Since the voltage applied to the plate of a pentode has but slight effect on the cathode current, a failure in the plate circuit may not change the cathode voltage very much. The cathode current of a pentode is affected by the screen voltage in much the same manner as the cathode current of a triode is affected by the plate voltage, and it may affect the cathode voltage. Radical changes in cathode voltage are likely to be the result of a change in the cathode resistance.


Changes in plate and screen voltages often affect the division of the cathode current between these two elements, so that the voltages on both may be affected. Also, it should be remembered that decoupling circuits often are common to both the plate and screen supplies. If the resistance of a decoupling resistor should change, or the capacitor become leaky, it will change the voltage on both elements. The power supply voltage should be checked before attempting to check voltages in the various amplifying stages of the instrument.

Coming Up


The effects of component changes in solid-state circuits will be considered in a following article. These often are complicated by the effects of forward biasing, constant emitter-base potentials, the low-impedance characteristics of many transistor circuits, direct coupling between stages and the use of numerous feedback loops. ▲

Compaction
Double Triode Pentode
Used in color TV Video
Filament—10.7V @ .6A


	Triode	Triode	Pentode
E_p	200	200	200
E_{g2}	---	---	120
E_g	-5.5	-6.3	-5.0
I_p	7.1	7.6	27.5
I_{sg}	---	---	4.9
G_m	5500	6300	21200

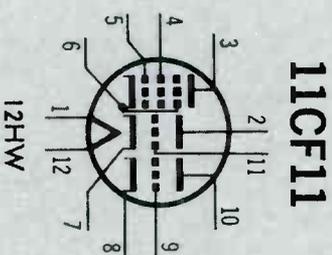

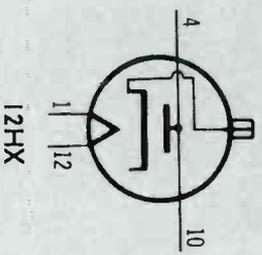Compaction diode (Damper)
Filament—19V @ 0.6A—11 sec warmup
PIV—5000V @ 350mA



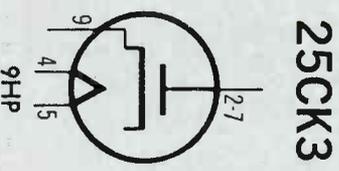Filament—25.2V @ .3A—11 sec
PIV—5200V @ 250mA



Electronic Servicing Tube Substitution Supplement

This Supplement has been designed to provide you with the latest up-to-date information on new tubes. The format allows maximum use during a house call or at the bench.



REMOVE THIS
SUPPLEMENT FROM

Electronic Servicing
and put it in
the back of your

**TUBE
SUBSTITUTION
HANDBOOK**

direct substitutes

Included are the older tubes that will substitute directly for the new tubes. This information supplements the sections in the Tube Substitution Handbook for American Receiving Tubes and Picture Tubes.

basing diagrams

The basing diagram for each new tube will help you in the servicing of new receivers when service literature is not available.

typical characteristics

The typical, or average, characteristics of each new tube can be of great help when troubleshooting new circuits.

easy reference



The direct substitution list will be cumulative each month. Thus, only the latest edition need be carried in the Tube Substitution Handbook.

Direct Substitutions

To Replace	Use	To Replace	Use
2AS2A	•	16DCP4	•
3BN2A	•	16LU8	•
4LU6	•	16LU8A	•
5MQ8	•	17FCP4	•
6AG9	•	18AJ10	•
6AK10	•	19DE3	•
6AL9	•	20AHP4	•
6AG9	•	22AHP22	•
•	•	25CK3	•
•	•	25GP22A	•
•	•	31AL10	•
•	•	32HQ7	•
•	•	33HE7	•
•	•	12DEP4	•
•	•	12DHP4	•
•	•	19GEP4	•
•	•	19HNP22	•
•	•	22TP4	•
•	•	22ZP4	•
•	•	25ALP22	•


*No substitution at present time.
 Twelfth edition of Tube Substitution Handbook now available at your distributor.

General Specifications
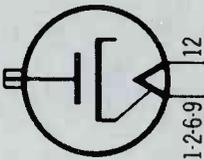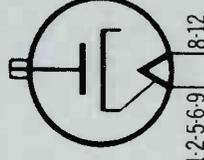
<p>Diode—H.V. Rect. Filament—2.5V @ 0.33A PIV—30KV @ 1.7mA</p>	<p>2AS2A</p>  <p>1-2-6-9 12 12EW</p>
<p>Diode—H.V. Rect. Filament—3.15V @ 0.30A PIV—30KV @ 1.7mA</p>	<p>3BN2A</p>  <p>1-2-5-6-9 8-12 12FV</p>

b


4LU6

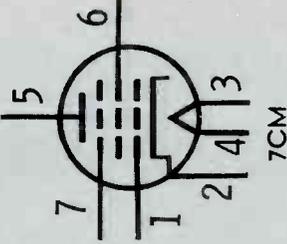

Filament—4.2V @ 0.6A
 EP = 200V
 E_{SG} = 125V
 E_G = -8.6
 I_P = 20mA
 I_{SG} = 4.4mA
 G_m = 8000

7CM


6BW3

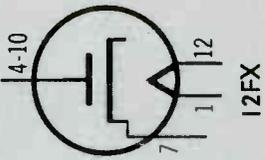

Damper Diode
 Filament—6.3 Volts @ 1.6A
 PIV—5KV @ 175mA

12FX

6KV6A


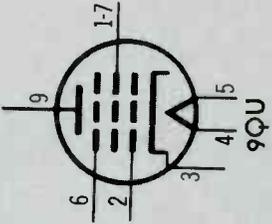


Filament—6.3V @ 1.6A
 EP = 140
 E_{SG} = 140
 E_G = -24.5
 I_P = 40
 I_{SG} = 2.4
 G_m = 6000

9QU

c

ICTJ

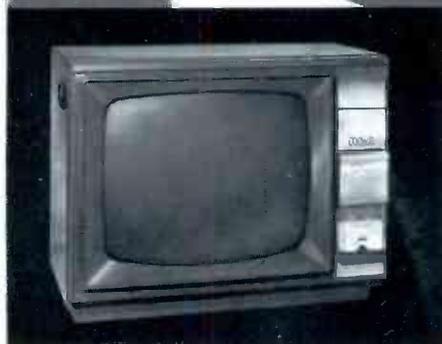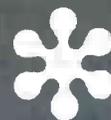

RCA CALLS IT ICTJ. YOU'LL CALL IT THE GREATEST SERVICE AID EVER TO COME ALONG.

ICTJ* is more than a test jig. It's a complete system designed by RCA to help you service Color Television faster and more precisely.

With the updated ICTJ system you'll be able to service more than 90% of *all* Color TV consoles on the market—that's over 1,500 different models from more than 17 different manufacturers.

Here's what it includes: First, the test jig itself, in bench or portable models.

Second, an assortment of adapters engineered to match almost any Color console chassis to the test jig.

*Industry Compatible Test Jig

Third, a complete reference book to take the guesswork out of which adapter to use with each chassis—and RCA keeps it up to date through a subscription service.

And there's also a new optional high voltage meter kit to give you safe, accurate and continuous monitoring.

ICTJ lets you pull a chassis with the complete assurance that the picture in your shop will be the same as the customer sees in his home.

See your RCA Parts and Accessories Distributor today; chances are you'll find a less important use for that old jury rig.

Deptford, New Jersey

RCA Parts and
Accessories

Circle 24 on literature card

January, 1970/ELECTRONIC SERVICING 41

Servicing AGC—Tube, Hybrid and

Analysis of the circuit operation and troubleshooting of old and new system designs, plus lists of common trouble symptoms and their probable causes.

By Carl Babcoke

Keyed AGC is a closed-loop system in which the control signal is taken from amplifier stages that are being controlled. One of the inherent characteristics is that a defect will usually change the voltages in all parts of the closed-loop. An analysis of the DC voltages is recommended as the fastest and most accurate method of finding the malfunctioning stage.

Three types of AGC circuits are discussed here: Those with tubes only, hybrids with tubes and transistors intermixed, and all-transistor designs.

A typical AGC system employed in the older and simpler tube-powered television receivers, such as the RCA KCS92 chassis, is shown in the partial schematic of Fig. 1. Operation of this system is as follows: DC and video voltages from the detector (testpoint C) are applied to the grid of the first video amplifier tube, V6A. The detector polarity is negative-going, so an increase in signal strength makes the grid more negative, which in turn makes the plate more positive. Part of this plate voltage is connected to the grid of the AGC keyer tube, V7B, where it is compared to a fixed voltage on the cathode of that tube.

The keyer tube is a grid-controlled rectifier that converts the horizontal pulses applied to the plate to negative DC voltage. The less negative the grid is during the time the horizontal sync pulse is applied to it, compared to the cathode, the more rectification takes place and the larger the DC voltage at the plate.

To minimize snow, AGC is not applied to the tuner RF stage until the input signal is quite strong. This is done by applying B+ through R51 to the tuner AGC line. A

diode (part of the 6AV6 audio tube) prevents the AGC voltage from going positive when weak signals are being received.

The large amount of negative voltage necessary to make the tuner AGC operate correctly is too high for the IF's, so a simple voltage divider, consisting of R22 and R24, reduces it. It may surprise you that the second IF tube, V4, also has some AGC indirectly applied to it. Referring to Fig. 1, the first and second IF tubes are DC coupled (some of the filtering components have been omitted for better clarity). When a negative AGC voltage is applied to the grid of V3, its plate voltage rises. Since the cathode of V4 is DC coupled to this plate circuit, the cathode of V4 also becomes more positive. This increases the bias on V4 because the grid is clamped, by the voltage divider R29 and R30, to a fixed positive voltage.

Troubleshooting All-tube AGC Circuits

Three voltages should be checked in each tube set that has, or is suspected of having, AGC trouble. These three voltages are: Tuner AGC voltage, IF AGC voltage and the DC video detector voltage. When these have been checked in a number of sets, and the results analyzed, several conclusions can be made:

1. If the set has normal gain, as evidenced by normal snow off channel, loss of **both** RF and IF AGC voltages will cause excessively high detector voltage, a blank raster on b-w sets or a black raster on a color receiver.
2. If a set has normal gain, **low** RF and IF AGC voltages will cause high detector voltage, overload or locking instability, and a darker picture on color sets.
3. A weak tuner or IF stage makes all three readings low.
4. Too much RF and IF AGC voltage (on or off channel) causes a blank raster on all channels.
5. Low IF AGC and high RF

AGC voltages cause snow in the picture. This is true whether the defect is in the IF or RF AGC.

6. High IF AGC and low RF AGC voltages can cause mixer overload with "windshield wiper" or sync instability on strong signals.

In all keyed AGC circuits, the AGC voltage is divided, with part of the gain-reduction voltage going to the RF stage and part to the IF's. If a defect reduces one of these two voltages, the AGC will attempt correction by increasing the remaining one. This may not give perfect reception, but it does make the voltage analysis easier.

Several visual symptoms from the picture, the three measured AGC voltages, a description of the conditions under which the receiver was operated and a few suggestions about what components could cause each symptom are listed in Table 1. The most important thing about these voltages is not their exact value (because they will vary according to signal strength and AGC control adjustment) but their relative value compared to normal AGC voltages for that model and location. The symbols indicate whether the readings are higher or lower than normal.

Case Histories—Tube Circuits

Case #1: An RCA KCS92 chassis had snow off channel, but a clear white raster on any strong channel. The AGC voltages were:

RF	+1 (normal: -2)
IF	+5 (normal: -6)
detector	-14 (normal: -1.5).

The video amplifier was biased to cutoff, thus no picture. High detector voltage and low AGC voltages indicated a defect in the AGC circuit at a point before the RF and IF voltages separate. The positive AGC voltage to the IF's indicated a defect other than a mere loss of AGC voltages. The symptoms were similar to those listed in item #6 in Table 1, except for a positive IF voltage.

Referring to Fig. 1, the voltage at the plate of the AGC keyer was

Solid State

+115 instead of the normal negative voltage. Capacitor C82 was suspected of being leaky; however, before clipping it loose for a voltage-leakage test, a voltage reading at the junction of R48, R50 and C54 made that step unnecessary—the +290 volts measured at that point indicated that C54 was shorted. With a new capacitor soldered in place and the AGC control properly adjusted, two more voltages were added to the three already penciled on the PHOTO-FACT schematic: -38 at the plate (pin 1) of V7B, the AGC keyer, and -23 at the junction of R48, R50 and C54, with normal signal.

Here is a helpful, fast test: Short the grid of the AGC keyer tube to the cathode, and measure the negative voltage at the plate. In this set it was -215 volts. This test will help you determine that the keying pulse is present at the plate, the cathode circuit has continuity (ever have an open socket pin?) and all conditions are good except for the grid or cathode voltages.

Case 2: Very snowy picture. At first, the tuner was suspected, but voltage analysis, similar to item 5 in Table 1, eliminated the tuner as the source of trouble. The trouble was found to be a gassy first IF tube that was reducing the IF AGC; replacement cured the snow.

Circuit Changes In Later Designs

The first basic circuit variation that might seem to defeat the usefulness of Table 1 is shown in Fig. 2, the schematic of the AGC circuit in the Zenith 23XC36 chassis. The function of R46, the 1.2K resistor in the cathode return of the first IF amplifier, is to provide smoother AGC action. The voltage drop across R46 is so high that the grid-to-ground voltage will measure positive until the station signal reaches extremely high amplitudes. If the true IF bias is measured from cathode to testpoint A in the grid return circuit, the analysis in Table 1 is still valid.

In the absence of any signal, the plate of the AGC keyer tube, V6A, is slightly positive because of R40.

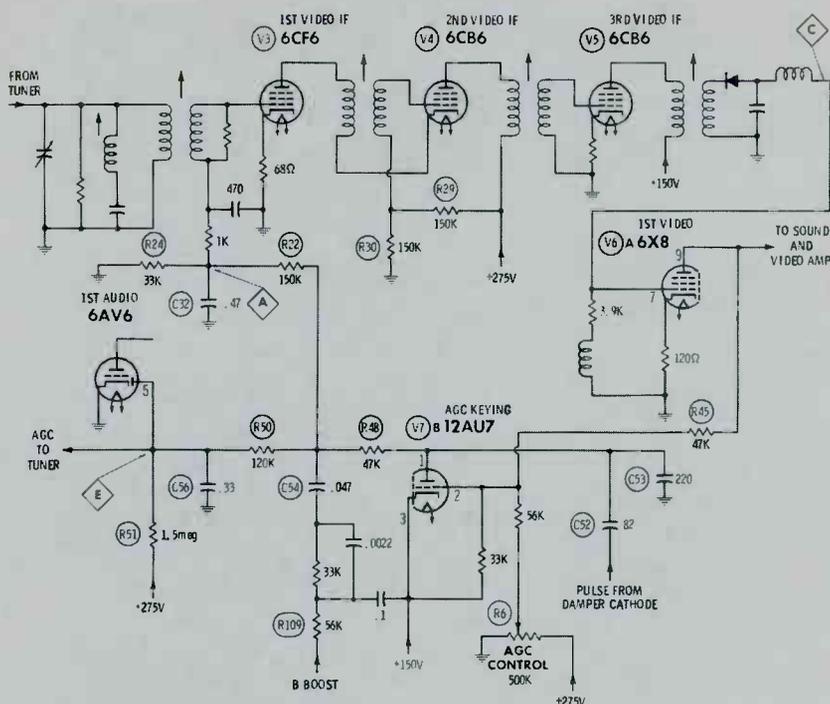


Fig. 1 RCA KCS92 chassis AGC schematic.

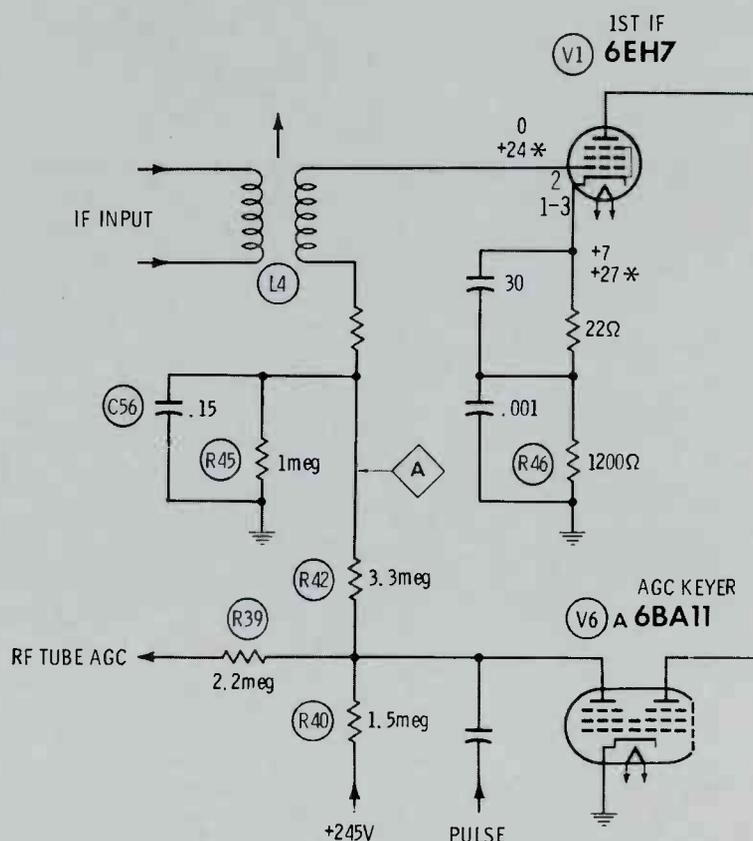


Fig. 2 High-value cathode resistor used in the Zenith 23XC36 chassis makes most of the AGC voltages at TP1 (A) measure positive.

TABLE 1

AGC Voltages for Analysis of Trouble in RCA KCS92 Chassis

Visual Symptoms	Detector Voltage	IF AGC	Tuner AGC	Receiver Condition or Probable Sources of Trouble
1. Stable picture, normal contrast and snow	-1.5	-6	-2	Normal for moderate signal
2. Stable picture, slight snow	-1.4	-5	0	Normal for weak signal
3. Grainy picture with "windshield wiper"	-1.7	-7	-8	Normal for very strong signal
4. Overload, little sync	-2†	-9‡	0†	Tuner AGC too low, C56 leaky, R50 raised, RF tube gassy.
5. Snow on medium strength signal, normal on weak signal	-1.5	-2†	-10‡	Tuner AGC too high, R51 open, IF AGC too low, C32 leaky, 1st IF gassy, R22 too high
6. Blank raster on channel, normal snow off channel	-12‡	-3†	0†	AGC keyer stage dead, C52 open, C53 shorted, R48 open, V7 dead
7. Blank raster	0†	-12‡	-20‡	V7 conducting too much, tube shorted, open R6, low 150 volts, video tube open
8. Low contrast, no snow	-1†	-3†	0†	Weak IF stage
9. Low contrast, some snow	-1†	-3†	0†	Weak mixer stage
10. Normal contrast, heavy snow	-1.3†	-4†	0†	RF stage dead
11. Low contrast, poor locking	-.4†	-3†	0†	Defective detector diode
12. Overload, no sync	+2	-3†	0†	Detector diode reversed

†Voltage is low ‡Voltage is high

TABLE 2

AGC Voltages for Analysis of Trouble in Zenith 14A9C51 Chassis

Visual Symptoms	Detector Voltage	IF AGC	Tuner AGC	Receiver Condition or Probable Sources of Trouble
1. Raster with normal snow	+6	+4.9	+1	Normal for no signal
2. Normal, stable picture	+3	+7.4	-5	Normal for strong station
3. Dark, snowy, overloaded picture	+8‡	+4.9†	-15‡	Loss of IF AGC, C to E short in Q202, defective Q202
4. No snow off channel, no weak signal received	+1†	+7.4‡	0	Q202 not conducting on weak signals, R1 open, Q202 open, R3 open, C218 shorted.
5. Overload on strong channel	+5‡	+7.4	0†	Loss of AGC to RF stage, R4 open, C1 shorted, gassy RF tube, shorted feedthru capacitor on tuner
6. Dark, overloaded picture	+8‡	+4.9†	+1†	Loss of negative voltage at 6BA11 plate, bad tube, shorted or open C5, no video at pin 5, open AGC control
7. Normal picture of very low contrast	+1†	+7.4	-5	Might be misadjusted AGC level control, or CR102 may be defective (control of AGC comes from sound detector—not picture detector)
8. Snowy, low contrast picture—no weak stations	+2†	+7.4	-35‡	Excessive conduction in 6BA11, shorted tube, open R5, shorted C228, shorted C6

†Voltage is low ‡Voltage is high

This is necessary to make the grid of V1 nearly as positive as its cathode, and to delay application of the AGC voltage to the RF tube. Yet, the voltage at the AGC terminal on the tuner is only a few tenths of a volt, because the value of R39 is so high (2.2 megohms) that the current drawn by the positive grid reduces the voltage to a low value that will not cause damage to the tube. When using Table 1, consider any positive tuner AGC voltage as being zero.

Hybrid AGC Circuits

A partial schematic of the Zenith 14A9C51 hybrid chassis is shown in Fig. 3. Note that the video detector is positive-going. The output from the plate of V201A, the first video amplifier, supplies a negative-going signal to the common control grid (pin 4) of the 6BA11 sync/AGC tube for the purpose of noise inversion. Another signal from the negative-going sound detector at testpoint C2 is fed to the grid (pin 7) of V203A, the 6KT8 sound/sync/AGC amplifier. The positive-going output at the plate (pin 9) of V203A supplies the sound IF and sync separator circuits and also the suppressor grid (pin 5) of V204A, the 6BA11 sync/AGC tube. This is the signal that controls the amount of rectified negative voltage developed at the plate of V204A.

AGC voltage for the RF tube in the tuner is developed and delayed in exactly the same way as was described for the all-tube circuit in Fig. 2.

Most transistor IF stages require a transistor AGC amplifier to supply the power required by the base circuit of the stage that is being controlled. In this case, phase inversion is also needed, since the AGC plate becomes less positive with increases in signal level, and even reaches a few volts negative on very strong signals. Two resistive networks limit the action of the IF AGC amplifier, Q202. If the base voltage becomes near zero, or slightly negative, the base will be biased insufficiently or reversed biased, respectively, and will be cut off. With such bias conditions, maximum collector voltage is limited by the 470-ohm resistor and the 400-ohm AGC delay control to about +7.5. The function of the AGC delay control is to set the maximum

amount of AGC that ever can be applied to Q101, and this indirectly sets the bias on the RF tube to produce the minimum amount of snow. With no signal being received, Q202 transistor is heavily forward biased so that the emitter and collector effectively are nearly shorted together. The 820-ohm emitter resistor prevents the AGC from being reduced too much (minimum bias for weak signals). A non-polarized capacitor (needed because the voltage varies between +5 and -1) bypasses the base to ground for AC signals.

The 1K emitter resistor stabilizes Q101 against drift caused by thermal changes. Because of the emitter-follower action to DC, a change of 2.5 volts (measured to ground) is required to produce a true change of forward bias of only .04 volt

(measured from base to emitter). Saturation biasing is used in this chassis; the forward bias on the 1st IF amplifier is +.78 volt with no signal applied and +.82 volt with a strong local signal.

If transistor Q101 is not excessively leaky and the 1K emitter resistor is not out of tolerance, the AGC voltage at testpoint E is usually the only IF voltage measured in analyzing overload or AGC problems. It is not necessary to actually measure directly the base-emitter voltage.

Table 2 gives some clues for analyzing the visual symptoms and AGC voltages in the Zenith hybrid chassis. A "†" after a voltage reading indicates the voltage is too low and a "‡" indicates that it is too high.

The AGC delay control actually

delays application of the AGC voltage to the RF stage by limiting the maximum amount of gain-reduction voltage applied to the 1st IF stage. Variations in positive voltage at the plate of the AGC keyer change the IF but not the RF AGC voltage. When the voltage at the keyer plate goes negative because a very strong signal is being received, the IF AGC transistor is reverse biased and cut off (the AGC delay control sets the minimum amount of IF gain), but the negative voltage applied to the RF tube continues to increase as the received signal becomes stronger, and gradually reduces the gain of the RF stage.

Case Histories—Hybrid Circuits

Case #1: Slight pressure on the IF compartment caused the picture to become very weak and the follow-

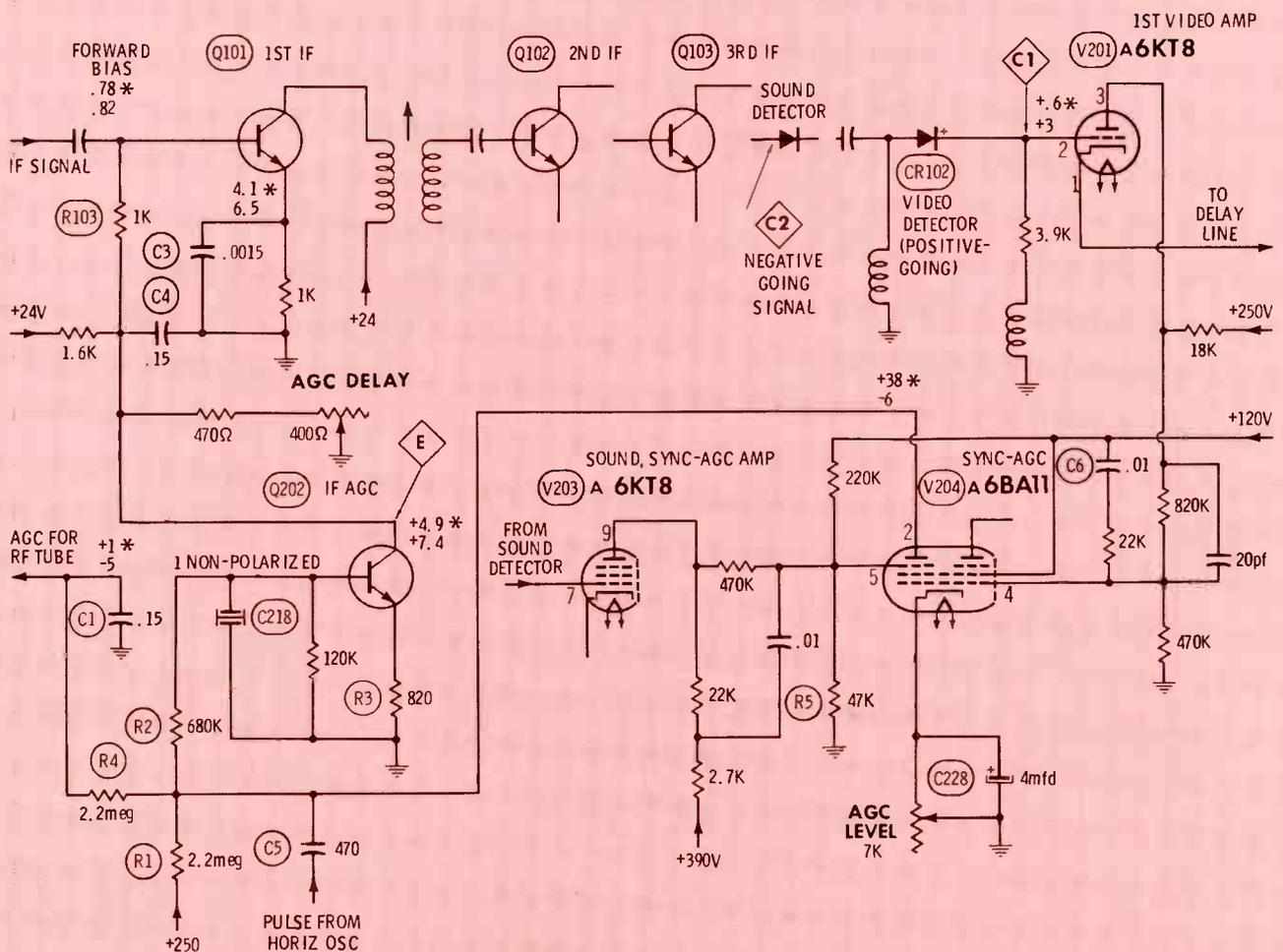


Fig. 3 Zenith 14A9C51 chassis has an AGC circuit with a positive-going video detector, sound/sync/AGC amplifier, keyed AGC and an IF AGC transistor. (*Indicates voltage with no signal applied.)

ing voltages to read:

RF	+1
IF	+3.1
detector	+1.0.

Analysis of these voltages indicated a loss of tuner or IF gain, plus an abnormally low IF AGC voltage. This latter clue pointed to the IF's.

After the IF top shield was removed, the emitter voltage of Q101 was monitored as the defect was cycled on and off. When the gain was low, the emitter voltage was zero.

Repositioning the emitter lead so

that it could not touch a grounded point solved the problem. With the emitter voltage grounded, the base was highly forward biased even though the AGC supply voltage decreased because of the added load, and the gain of that stage went to zero and the collector current increased greatly. Only the B+ decoupling resistors prevented the transistor from being destroyed.

Case #2: The receiver operated normally for about 15 minutes, then lost contrast and sensitivity. Analysis of the AGC voltages indicated a loss of signal in an IF stage (see

item 1 in Table 2). After the set had heated enough to lose sensitivity, each IF transistor was sprayed with circuit cooler. The 3rd IF transistor was found to be heat sensitive, and was replaced.

All-Solid-State AGC Circuits

Fig. 4 is the simplified schematic of the AGC system in the RCA CTC40 chassis. The video detector is similar to that used in many older RCA chassis designs, except it produces a positive-going signal, and +2.3 volts is applied to its cathode, which normally is

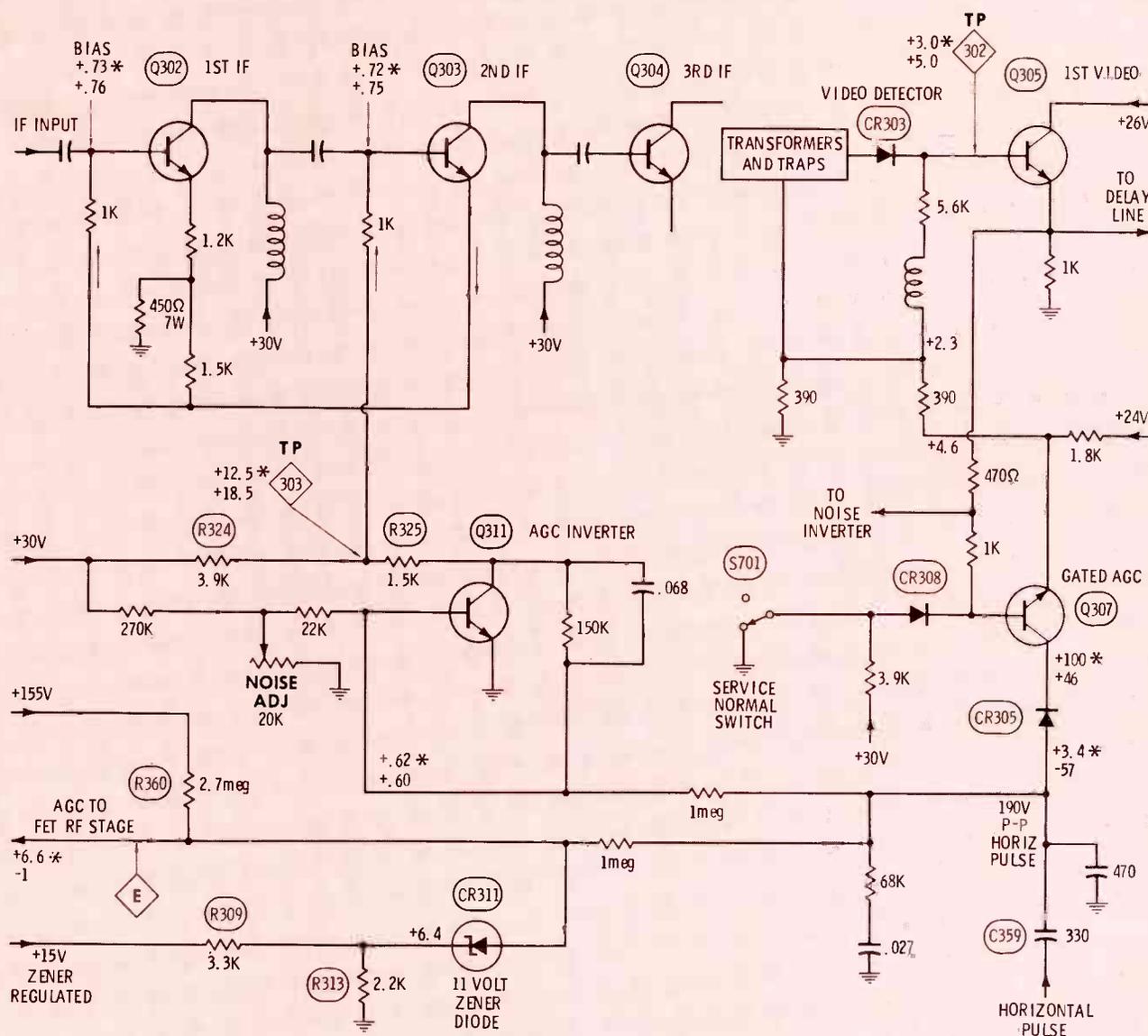


Fig. 4 RCA CTC40 chassis is all-transistor, limits the AGC voltage applied to the RF FET and has no AGC level control. (*Indicates voltage with no signal applied.)

grounded. The purpose of this voltage is to forward bias the first video amplifier, Q305.

DC and AC signals from the emitter of Q305 are applied to the base of Q307, the AGC keyer, where they are compared to a fixed voltage at the emitter. The more forward bias applied to the base of Q307, the more it conducts, which increases the negative DC voltage at the anode of CR305. Without CR305, the horizontal pulses would be rectified by the collector of Q307, and the negative voltage thus produced would find the collector-emitter path a virtual short circuit. Much of this negative voltage would leak off between horizontal cycles. CR305 effectively is a short circuit when the horizontal pulse is present on its anode, but is an open until the next pulse arrives. This is important information for servicing, because either an open or shorted diode or open keying transistor will cause AGC overload.

RF amplification in the tuner is accomplished by a field-effect-transistor (FET), which reportedly is protected from damage from external voltages by zeners at each gate input. As added protection, the variation of AGC voltage to this stage is limited by a circuit consisting mainly of R309, R313 and zener diode CR311. If the voltage at testpoint E (RF AGC) starts to become more positive than +6.6, zener diode CR311 operates in the normal diode mode, and since its

anode is positive compared to the +6.4 at the cathode, it conducts and clamps the AGC to the fixed +6.4-volt supply (plus the drop across the diode). If the voltage at testpoint E attempts to become more than -5 volts negative, the 11-volt rating of the zener is exceeded, zener action takes place, and the AGC is clamped to a level that is 11 volts more negative than the +6.4 volts on its cathode, or slightly less than -5 volts.

AGC control of the IF transistor requires a power gain and a polarity inversion that is accomplished by Q311. The noise control varies the bias on the AGC inverter to change the amount of AGC action applied to the IF stages. This indirectly changes the AGC applied to the RF stage, and has the most effect on the visible snow in the picture. Experience has shown that RF AGC voltages in excess of -1 will noticeably increase the snow. Adjust the noise control for minimum snow on a medium-strength station. There is no AGC level control on this model.

The AGC inverter actually controls the voltage supplied to the base of the 2nd IF stage (forward bias is increased to decrease gain). Because of the large emitter resistor in the 2nd IF stage, the emitter voltage changes almost as much as the base voltage; part of this emitter voltage is applied to the base of the 1st IF amplifier to function as AGC voltage.

Case Histories—Solid-State Circuits

Case #1: Visual symptoms were typical of those caused by insufficient AGC. The voltage at the three AGC testpoints read:

RF	+6.6
IF	+9
detector	+6.

The voltage readings in item 4 of Table 3 are the most similar to these readings, but the IF AGC voltage reading is lower, and probably significant.

Further voltage tests revealed about +60 volts on the anode of CR305, with less on the other ends of the 1-megohm resistors connected there. C359 was disconnected and found to be leaking. Replacing this capacitor eliminated the trouble symptoms.

Case #2: On channel, the picture was blacked out; off channel, the snow was normal. The three AGC voltages on channel were:

RF	+6.6
IF	+12.5
detector	+9.0.

Total loss of AGC and a very high detector voltage were indicated. A normal horizontal pulse was measured on the collector of Q307, and the base was very forward biased, but there was no rectification. Replacing transistor Q307 cured the AGC problem.

Conclusion

Almost all new circuitry is more complex than it has been in the past, particularly when it uses solid-state components. Also, transistors often are soldered into circuit boards, and the boards can be damaged if components are removed and reinstalled too often. For all of these reasons, it is becoming even more imperative that most of our servicing be done with a minimum of component removal.

Good test equipment helps, of course. Every test used or recommended in this article can be accomplished with a scope and a VTVM (or FET meter). We need to **measure more** and **analyze more**.

One last word on AGC servicing: Remember that the desired end-product is an undistorted, constant-amplitude signal at the video detector. Make certain this consideration is included in your analysis because all parts of the circuit are merely means to this end. ▲

TABLE 3

AGC Voltages for Analysis of Trouble in RCA CTC40 Chassis

Visual Symptoms	Detector Voltage	IF AGC	Tuner AGC	Receiver Condition or Probable Sources of Trouble
1. Raster with normal heavy snow	+3.0	+12.5	+6.6	Normal for no signal
2. Normal, stable picture	+5.0	+18.5	-1	Normal for a strong station
3. Bright, snow-free raster	+2.3†	+20‡	-5‡	Overactive AGC, S701 open, Q307 shorted
4. Unstable, overloaded picture	+7‡	+14†	+6.6†	Very low negative voltage at CR305, Q307 open or shorted, open Q305, C359 open
5. Very snowy picture	+4.4†	+17†	-5‡	Too much AGC at RF FET, R363 raised in value, noise control misadjusted, Q311 leaky, AGC to IF too low
6. No picture	+2.3†	+24‡	+6.6†	Q311 not conducting, R325 open, no forward bias, Q311 open

†Voltage is low

‡Voltage is high

Weller® simplifies soldering



New TEMPMATIC® Temperature Controlled Soldering Tool

Combines all the advantages of a pencil iron, a fast heating soldering gun, and tip temperature control. Exclusive removable Powerhead contains Weller's temperature control system. Protects components even in the most delicate work situations. Tool weighs 7 oz. Use it for light or heavy duty soldering. Model GT-7A has 700°F. $\frac{3}{16}$ " chisel point Powerhead. Model GT-6B has 600°F. $\frac{1}{8}$ " conical point Powerhead.



The original Dual Heat Guns

Fast heating. Long-life tips. Exclusive trigger-controlled dual heat. High soldering efficiency. Spotlight. 3 models from 100/140 watts to 240/325 watts.



Dependable MARKSMAN Irons

They outperform other irons of their size and weight. Long-reach stainless steel barrels. Replaceable tips. 5 models from 25 watts to 175 watts.



Weller 25-watt Iron for intricate work

Industrial rated. Weighs $1\frac{1}{4}$ oz. Delivers tip temperatures to 860°F. Cool, impact-resistant handle. Model W-PS with $\frac{1}{16}$ " tip.

Weller®

WELLER ELECTRIC CORP., Easton, Pa.
WORLD LEADER IN SOLDERING TOOLS

Circle 37 on literature card

troubleshooter


I am working on a Sears Model 6165 color TV that is covered by PHOTOFACT folder 861-2. Here are the symptoms: When it first is turned on, sound is heard in about 20 seconds, stays on about 10 seconds and then disappears as the high voltage comes on. There is a raster without sound or picture.

The trouble seems to be in the AGC. According to the schematic, the plate of the 6AU6 AGC keyer should be +15 volts, but it measures -150 volts. Other readings are: 88 volts on the 6AU6 grid (pin 1), 88 volts on the cathode (pins 2 and 7) and 160 volts on the screen (pin 6). When I clip out C69, the sound returns and the picture is overloaded. With the antenna removed, the picture is weak and snowy.

What other checks do you suggest?

David B. Kaufman
Inglewood, Calif.

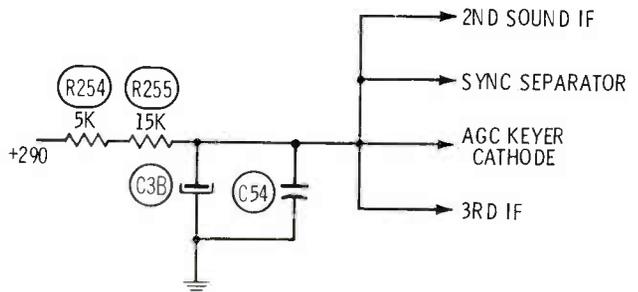Yes, this is an AGC problem concerned with the bias on the AGC keyer tube. Both grid and cathode are the same voltage so the bias is zero. Under that condition, the plate should be *very* negative. The wrong voltage is the cathode voltage. PHOTOFACT




specifies +130 volts while it measures about +90 volts. Refer to the schematic. R254 or R255 may have increased in value, C3B or C54 may be leaky, or one of the stages may be drawing too much current. Find the source of the low supply voltage, repair it, and the AGC problem should be cured. You might want to refer to the AGC article in this issue for more information.

Horizontal Oscillator Off Frequency

Can you please give me some help with regard to a Zenith chassis 14M29 (PHOTOFACT 743-4)? There is a high-pitched whine from the horizontal circuit, no light on the screen and the horizontal frequency is too high. The horizontal output transformer has been replaced because it was shorted, and the oscillator coil was replaced because it was open. All voltages in the horizontal circuit are good except the 650-volt boost voltage, which is only 325 volts. Sometimes I get a dim light on the screen, but it is only about one inch high. Why?

Harold Braden
Riverdale, Illinois

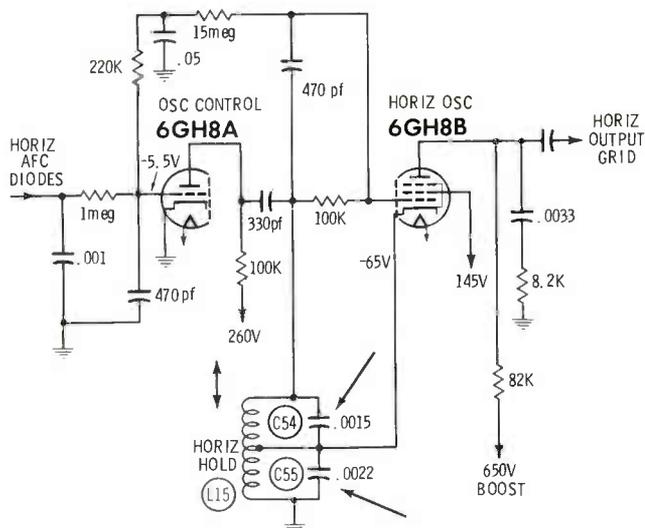Harold, the number one priority is to get the oscillator back on 15,750 Hz. The boost voltage indicates it is



running 30 to 40 KHz. This horizontal oscillator is a sine-wave type with a coil and capacitor tuned circuit. A blocked oscillator or a multivibrator might deviate that far off frequency from a large change in positive feedback or from a RC time-constant change, but a sine-wave oscillator must have a defect in the oscillator coil or one of the tuning capacitors (L15, .0015 and .0022) for the frequency to have changed that much. Is the oscillator coil an exact duplicate? Are C54 and C55 on the right coil lugs, and are the solder joints all good?

Biasing of RCA CTC17X Vertical Blanking Transistor

The September '69 issue of *ELECTRONIC SERVICING* shows the last item of Symcure on page 25 to be an NPN transistor with .9 volt on the emitter and .6 volt on the base. The transistor is not forward biased. Is this correct?

B. J. Brown
Trion, Ga.

The bias indicated on the vertical blanking transistor in the CTC17X RCA chassis is incorrect. This diagram was reproduced from the PHOTOFACT for that model, so we did not cross-check for wrong values and voltages as we normally do.

The correct voltages, according to my own tests on dozens of these circuits, are:

- base—+.6
- emitter—0
- collector—between +.2 and +.9.

The emitter returns to ground through a winding on the vertical output transformer, and there is not enough DC resistance to cause a measureable emitter voltage. Between vertical pulses, the transistor is heavily forward biased, and the pulse reverse biases it for a short period of time during each cycle. This accounts for an output of about 10 or 11 volts p-p from a collector on which there is less than a volt of DC.

The voltage measured across the base-emitter junction of class "C" stages (oscillators, sync separators, etc.) usually indicates a reversed-bias condition; this is because of base rectification. The pulse input to such circuits is usually of the polarity that will forward bias the base at the maximum level of the input pulse. ▲

flameless 1000° heat

Instant, precise heat for 1001 uses — shrink tubing, soldering-desoldering, forming, bonding, deburring, drying, setting adhesives. World's most complete line. Models from 200-1,000 F. Send for new free Catalog #01.



MASTER HEAT GUNS

1745 FLETT AVE., RACINE, WI 53403

Circle 25 on literature card

FREE CATALOG



CRT COLOR CHAMPION

TV PICTURE TUBE REBUILDING EQUIPMENT

C.R.T. Equipment Company, Inc.
2740 Old Lebanon Road
Nashville, Tennessee 37214

Telephone (615) 883-0215

Mail Coupon Today

(Please Print)

Name _____

Firm Name _____


Address _____

City _____ State _____ Zip _____

Clip Me Out

Circle 26 on literature card

January, 1970/ELECTRONIC SERVICING 49

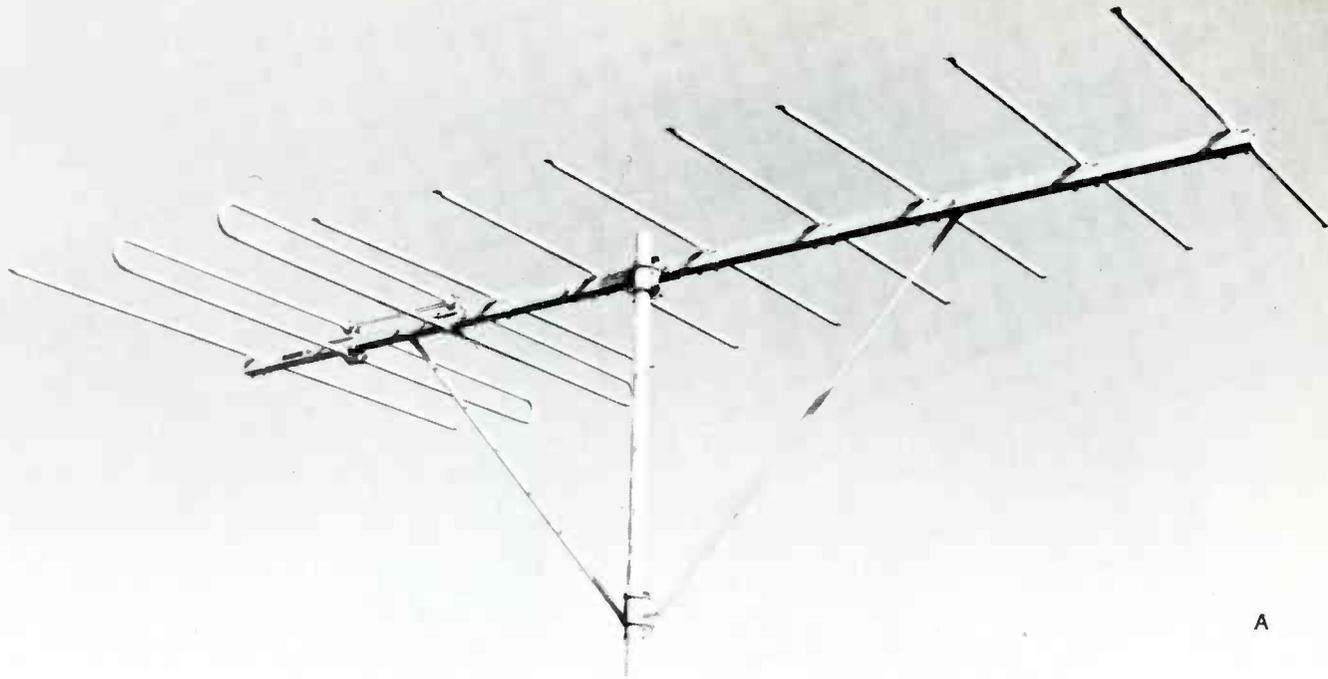

A

Facts about basic home TV antenna system components

Understanding the fundamental characteristics of basic designs of antenna and lead-in will help you select the correct combination of components for each installation. Knowing how to properly install the system is also important. This article discusses both aspects.

by Bruce Anderson

Characteristics of Basic Antenna Types

The Yagi

One of the earliest types of antennas used for TV reception was the familiar Yagi. Fig. 1 shows an example of this type antenna along with a sketch of its directivity pattern. Probably, if the only consideration was microvolts per dollar of antenna cost, this type would still be the most popular; however, a couple of other considerations enter into the problem. First of all, the Yagi is essentially a one-channel antenna. This means that it is a sharply tuned device which "reflects" the signals from all channels except the one for which it is tuned. This, in itself, could be desirable because it tends to reduce interference from other channels, but, because of the narrow passband, the response

to the higher-order sidebands within the channel for which it is tuned may be rejected to a degree which is undesirable. Yagi antennas manufactured after the advent of color TV usually have been designed to provide adequate bandpass for color.

The other disadvantage is more obvious. Since the Yagi will receive only one channel, an array of several antennas, one for each channel, would be required in most areas. This can be done, of course, and the several antennas may be connected to a single lead-in by use of a passive mixing device (multicoupler), but the installation is cumbersome, overly expensive in some cases, and the mixing losses may exceed the advantage in sensitivity of the antennas themselves.

The Conical

One of the early antennas which was designed to receive all the VHF channels more or less equally well was the conical (or "flying V") an-

tenna shown in Fig. 2. Two of these antennas often were stacked and connected together with matching bars to provide additional signal. While this type of antenna served well for monochrome reception, it, too, has some disadvantages. One of the problems with the "connie" is that it has fairly high sensitivity to signals which arrive at its sides. This makes it particularly susceptible to ghosts, as shown in Fig. 3. Also, because the "connie" has an output impedance which varies from channel to channel, it usually is mismatched to the lead-in, and standing waves result. This causes picture smearing, which is particularly troublesome in color reception.

Log Periodics

Ideally, an antenna should combine the good features of both the foregoing antennas while avoiding their disadvantages. The log-periodic types of antenna are broadly tuned to receive all VHF channels,

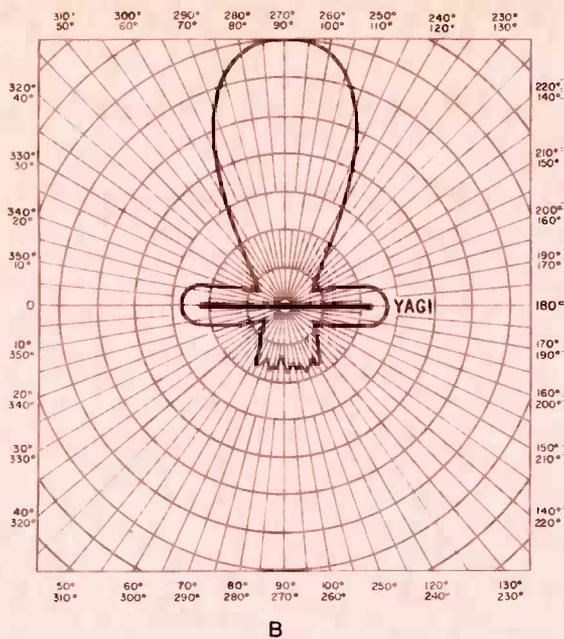


Fig. 1 A) A single-channel, heavy-duty Yagi antenna. B) The directivity pattern of a simple yagi.

VHF channel. Fig. 6 shows that this type of antenna has some of the rearmost elements "V-ee'd" towards the station, similar to the V-type log-periodic; notice also that, unlike the Yagi, a number of the elements are connected to the lead-in. The remaining elements are passive (not driven) as are all but one element in the conventional Yagi.

In the foregoing discussion of all these antennas, it was assumed that maximum sensitivity to the signal was a desirable quality; however, this is not always the case. In many metropolitan areas, signal strengths are so high that the reception problem is one of not overloading the AGC circuits of the receiver, rather than the conventional problem of obtaining enough signal to bring the picture out of snow. For reception in this type of high-signal-level area, the ideal antenna is one having little or no gain, or perhaps some loss, but also having very little sensitivity to signals coming from the sides and the rear. An antenna such as this is shown in Fig. 7.

UHF antennas

Several types of UHF antennas

maintain fairly constant impedance throughout the band and suppress the side lobes. To do this, of course, there is some sacrifice of sensitivity (microvolts per dollar), and the antenna is somewhat more complex than the conical type.

As the name implies, the log-periodic antenna has elements which are spaced logarithmically and also graduated in length, as shown in Fig. 4. By proper selection of lengths, at least one element (and usually two or three of them) is tuned to each channel. This may seem impossible at first glance, but remember that an element which is one-half wavelength at some frequency, and therefore tuned to that frequency, will act as a good receptor for a higher frequency, for which the element becomes electrically $1\frac{1}{2}$ wavelengths long.

Unfortunately, the elements which are tuned to the $3/2$ mode and those which are not tuned at all to the particular channel being received cause the antenna to have rather serious side lobes. Several "cures" for this problem have been devised; the two most popular ones are to incline the outer ends of the elements towards the transmitter (thus forming the V-type log-periodic antenna shown in Fig. 5), or to carefully design the element lengths and add loading devices where necessary to minimize the side lobes (resulting in the design shown in Fig. 4).

V-Yagi

The type of antenna known as a "V-Yagi" attempts to recover some of the gain lost by the log-periodic type while still maintaining flat response across the frequencies of the



Fig. 2 Typical conical antenna.

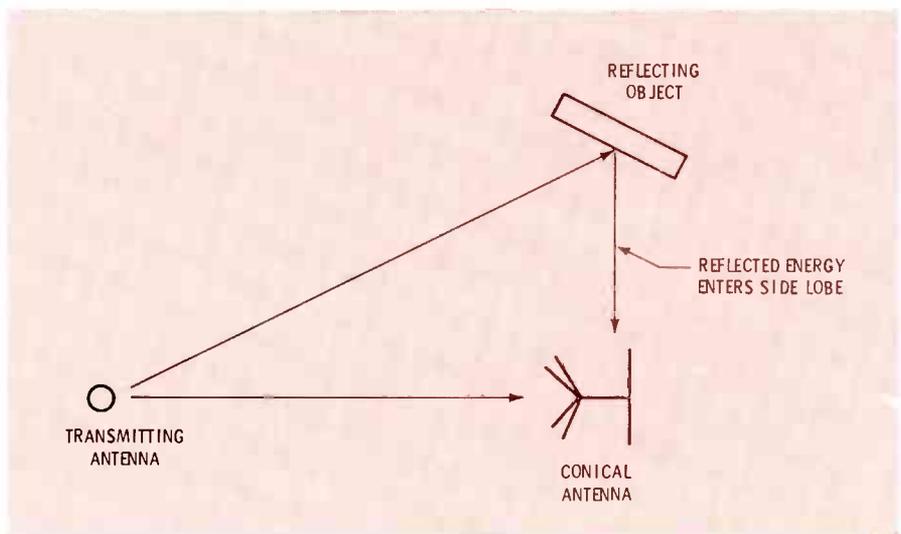


Fig. 3 How side lobes aggravate the reception of ghosts.

Fig. 4 Straight-element log-periodic antenna.

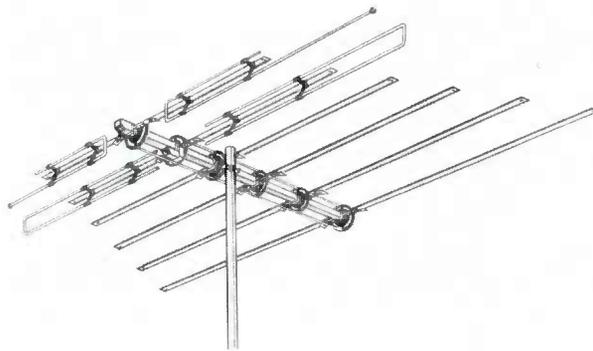


Fig. 5 V-element log-periodic antenna.

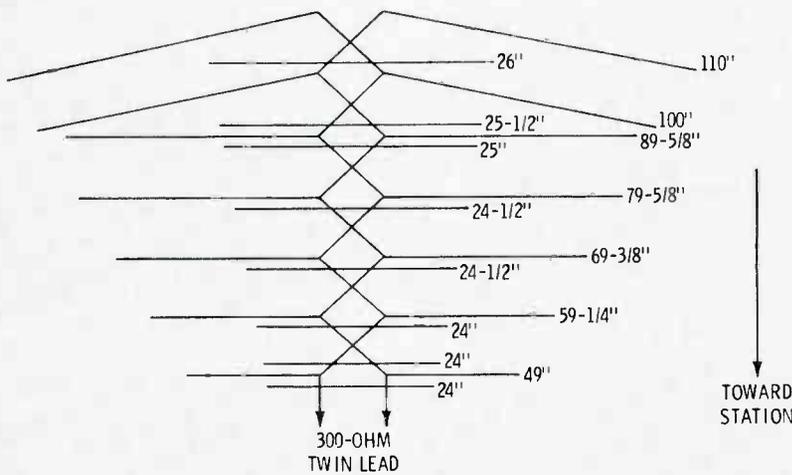
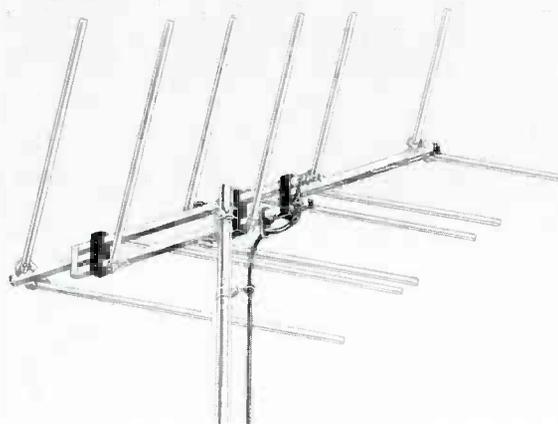


Fig. 6 Typical V-Yagi antenna.

also are available. Since the wavelengths of the UHF channels are much shorter, most of these antennas are characterized by their small size and relatively high gain.

Fig. 8 shows the always-popular bow-tie-and-corner-reflector type. (The bow-tie antenna placed in front of a flat reflector also is popular.) Such antennas can be expected to work reasonably well over a frequency range of perhaps 25 channels. Some manufacturers design this type of antenna with a variety of sizes of the bow tie (driven element); the largest element is for the lowest channels. If a new, higher-channel station should happen to go on the air, improved performance may be obtained by trimming off the edges of an existing antenna. Of course, this may result in poorer reception on a lower UHF channel.

While the Yagi antenna may be tuned too sharply for VHF reception, this is not the case with UHF. (A bandwidth of $\pm 5\%$ of center frequency on channel 2 is only about 5.5 MHz, but on channel 40 it is more than 60 MHz, the spectrum of 10 consecutive channels. Naturally, the response to all the sideband frequencies of a single channel is essentially constant.) UHF Yagi's have good sensitivity and they are highly directional, making them very desirable in fringe areas, or where ghosts are a problem. In many designs, the Yagi configuration is modified slightly by placing a corner reflector behind the antenna to reduce back-lobe response.

Increasing Gain

The concept of 'aperture' in antennas may perhaps be most easily understood by considering the sketch in Fig. 9. Obviously, the light **intensity** observed at each aperture will be the same, but if all the light passing through hole "A" were concentrated into a beam equal in diameter to the beam passing through hole "B" (by use of a lens), this concentrated beam would be the brighter. Therefore, it is apparent that more light **energy** can be obtained from the larger aperture. In much the same manner, an antenna having the ability to intercept the energy from a larger cross-section of a TV wave front will provide more signal strength.

To increase the aperture of a

Fig. 7 Low-gain, highly directional "metropolitan" antenna.



Fig. 8 UHF "bow-tie" antenna with corner reflector.

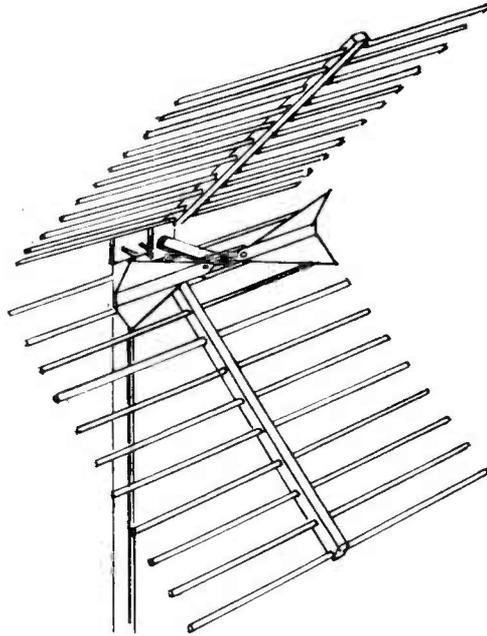


Fig. 9 Relation of aperture to energy obtained.


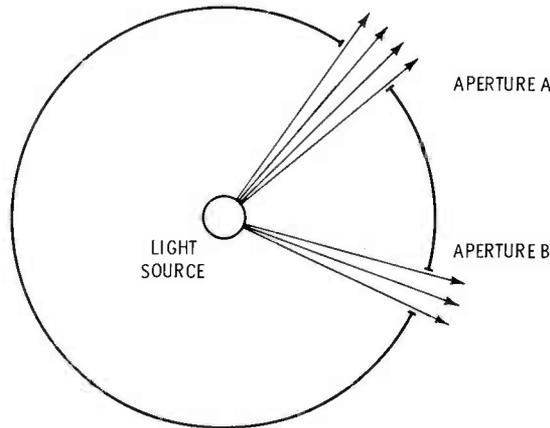


Fig. 10 A large aperture UHF antenna, the parabolic.

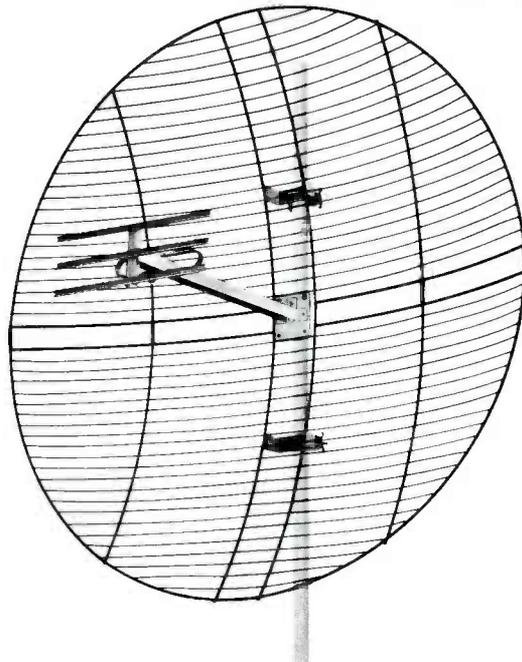

VHF antenna, it is common practice to stack antennas—the stacked conical or Yagi, for example. Large-aperture UHF antennas are available as a single unit. Two examples are the "cat-whisker" and the parabolic-reflector types (see Fig. 10). Of the two, the parabolic reflector is the more efficient, but its cost is proportionately greater. Also to be remembered is the fact that a large-aperture antenna intercepts additional wind energy (added wind-loading) as well as additional RF energy.

Combination Types

Today, most manufacturers sell combination UHF/VHF antennas, and also UHF/VHF/FM antennas. These are usually variations of the types described here, with all antennas mounted on one boom. A passive matching device is normally provided to allow the use of a single lead-in. In installing these, or any UHF antenna, use a good grade of UHF lead-in, such as foam-filled twin-lead.

Lead-in

The subject of lead-in has been covered at length in previous issues (see PF REPORTER, May 1968—"Facts About Antenna Lead-In"), but, for convenience, a short summary of the subject is included here.

Flat twin lead

For VHF applications, the conventional type "ribbon lead" (Fig. 11A) is still popular. It has the advantage of being cheap, but this is about all that can be said in its favor. It tends to "check" after prolonged exposure to the weather, thereby increasing its losses; it is affected most by deposits of foreign material on its surface; and its standing-wave ratio is increased by the proximity of metallic objects.

Foam-filled twin lead

Lead-in of the foam-filled variety (Fig. 11B) is much less affected by all of the conditions described above. This is of some importance in color reception, of great importance in UHF reception, and of particular importance in UHF color reception. Because of this, a good quality, foam-filled lead-in is perhaps the minimum type that should be considered for use in a modern installation.

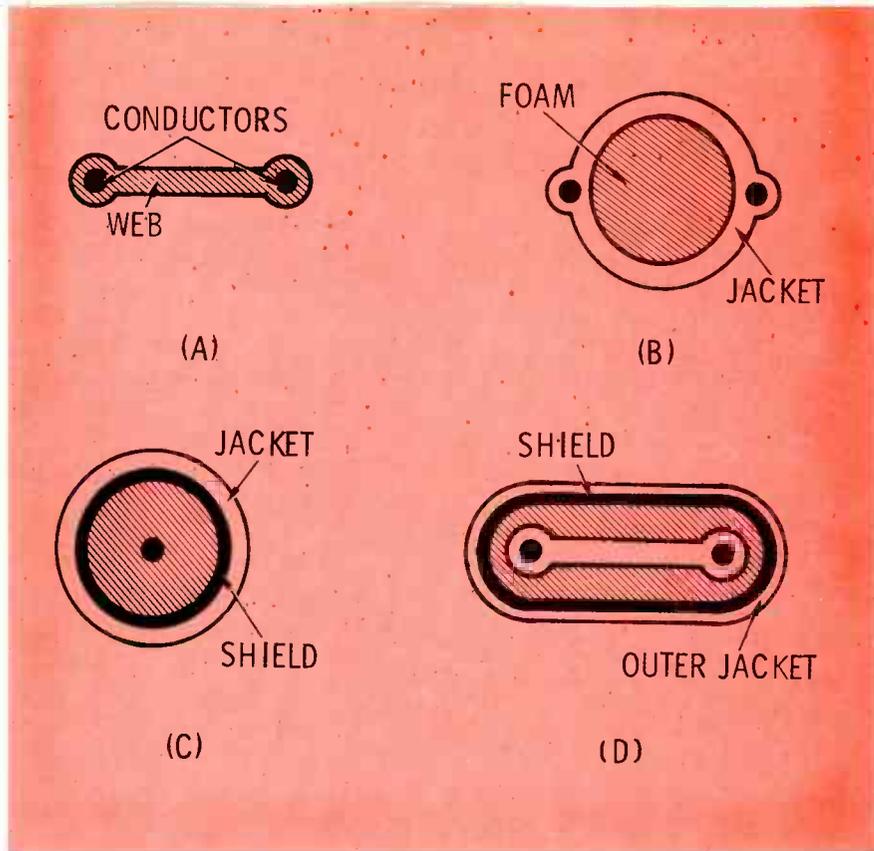


Fig. 11 Popular types of lead-in. A) 300-ohm flat or "ribbon" line. B) 300-ohm foam-filled line. C) 75-ohm coaxial cable. D) 300-ohm shielded line.

In the paragraphs above, we were careful to stipulate that the UHF lead-in under discussion was the foam-filled variety. When UHF television first appeared on the scene, it was recognized that the cross section of the lead-in should be circular so that more of the field surrounding the conductor would be in a controlled environment. The attempt to do this by means of a hollow, circular line was a rather dismal failure. Even with careful attention to sealing the ends of the line and providing drip loops with holes cut in the tubing to allow water to escape, it seemed that water always managed to fill at least a portion of the line after a short time (usually during the first rain). This, of course, resulted in very high attenuation of the signal, as well as a gross mismatch of impedance. For this reason, hollow, tubular lead-in should be used **only** if its entire length is installed inside a building where there is no possibility of moisture entering it. Even under these conditions, moisture may condense inside the line after a few years, rendering it useless.

Coaxial cable

The use of coaxial cable (Fig.

11C) for lead-in has never been very popular because it has much higher attenuation than 300-ohm lead-in, particularly at UHF frequencies, and because nearly all antennas are designed for 300-ohm operation. As an example of the increased signal loss incurred by the use of coaxial cable, 100 feet of typical 300-ohm lead-in will have a loss of about 1 dB, and coaxial cable (RG-59) will have a loss of about 2.5 dB on channel 2. On channel 13, these losses increase to 2 dB and 5 dB, respectively; but on channel 14, the losses are about 3 dB and 8 dB, again, in the same order. Assuming a 1000-microvolt input to the line, 1 dB of loss results in about 900 microvolts output, 3 dB loss results in 700 microvolts output, and for losses of 6 and 9 dB, the outputs are about 500 and 350 microvolts, respectively.

Recently, some manufacturers have made available antennas designed for direct connection to 75-ohm coaxial cable, such as RG-59. Also, some TV tuners are constructed so that they may be directly connected to 75-ohm cable. Of course, matching transformers having only moderate losses are available.

The major advantages of coaxial lead-in are that it is unaffected by the proximity of metallic objects, and dirt or water on its surface does not affect its operation. Also, since all the signal energy is contained inside the shield, it is completely immune to RF interference from automobiles, welders, medical electronics equipment, etc. When the amount of signal strength is sufficient so that the increase losses of coaxial lead-in can be tolerated, its use normally is satisfactory; however, this seldom will be the case for UHF reception.

Shielded 300 ohm lead-in

Gaining considerable popularity during the past few years is the shielded type of 300-ohm lead-in seen in Fig. 11D. This type seems to combine the best features of both foam-filled line and coaxial cable. It is unaffected by its surroundings, like "coax," and its losses are only slightly greater than conventional lead-in. At the frequencies of channels 2, 13, 14, and 83, its attenuation will be roughly .75, 2, 3, and 4 dB greater than the best foam-filled, 300-ohm lead-in. Since no standoffs are required and the shielded lead-in need not be routed away from metallic objects, the modest additional cost of the lead-in is normally offset by the savings in installation time and hardware. For these reasons, the average installation should use shielded lead-in.

Installation

After having installed antennas for more years than I care to admit, I feel confident that the best way by far to do the job is to build from the ground up. A mast or tower firmly "planted" in the ground and fastened to the edge of the roof is simple to install, sturdy, requires a minimum of lead-in, simplifies electrical grounding, and is less apt to involve you in a law suit for damages to a roof or chimney, either during installation or subsequent to a storm.

If the mast must be mounted on a chimney, be certain that it is mounted well above it and on the predominate up-wind side. Otherwise, the antenna and lead-in soon will become corroded or covered with soot, reducing their effectiveness.

A second rule to follow is to carefully inspect the chimney to determine if it is strong enough to support the antenna under all conditions. I recall installing an antenna without taking this precaution (because the building was only two or three years old and the cement-block chimney looked strong enough), only to have the chimney break off at the roof-line after the first wind storm. Then I discovered that the builder had not installed a liner in the chimney. Of course, this was a violation of the building ordinances, but I still had to re-install the antenna to avoid losing a good customer.

If an antenna is to be mounted on a roof vent, be sure that the vent pipe is cast iron or steel. Nowadays, many plumbers use copper vent pipe, which is not strong enough to support large antennas. Always be sure that the roof jack (the inverted cone through which the vent passes) is secure and well sealed against moisture. If the vibrations of the TV mast are likely to loosen the joint between the roof jack and the roof so that water can enter, some other means of mounting the antenna should be found.

Mounting a mast directly on a roof is relatively simple and completely satisfactory if a few precautions are observed. Never walk on a composition roof in cold weather, and never walk on a dry shingle or "shake" roof. Always wear "sneakers" or some other type of soft-soled shoes when working on a roof. Use liberal amounts of roofing tar at any point where you puncture the roof, and finally, use a safety rope—or buy more insurance!

All antenna installations should be securely grounded to prevent lightning damage to the television receiver and to the building. If the mast or tower extends to the ground, it may be connected to a ground rod at least six feet long by means of #6 (or larger) copper wire. Nearly all antennas are constructed so that all elements are DC connected to the boom, and thence to the mast, so that this method of grounding is satisfactory. Even if the mast does not come near the ground, this type of lightning protection is recommended, although a lightning arrestor properly attached to the lead-in normally will prevent any lightning damage, except possibly to the receiver itself. Cast-iron vent pipes may make a good ground

connection, but it is possible that the joints will form reasonably good insulators—don't depend on them for lightning protection.

Summary

Some of the fundamental characteristics of various basic types of antennas have been mentioned in this article along with some observations (based on my own experiences) about the choice of lead-in and installation methods.

There are so many variables involved in antenna installation that no single antenna type or installation method can possibly be correct for all cases, even in the same locality.

Because of this, the technician should be familiar with the advantages and disadvantages of the basic types of antenna and lead-in so that he can weigh them against the requirements of each installation and recommend the best possible system design to the customer, who, in turn, must make the final decision based on economic considerations.

Once the design is agreed on, the technician must be capable of properly installing the system components so that all the advantages of the design are realized. ▲


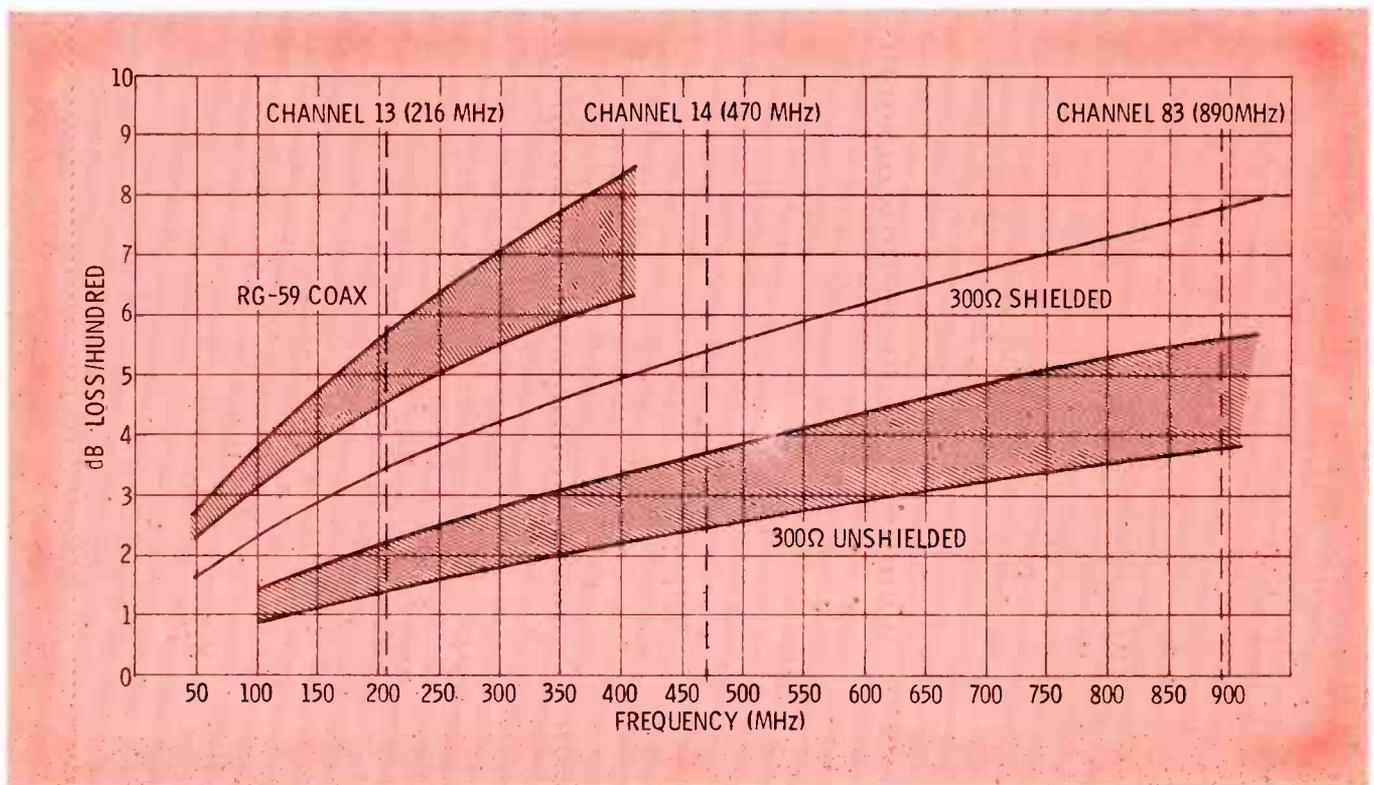


Fig. 12 Typical lead-in attenuation curves show losses of basic types of lead-in.

**A NEW AND IMPORTANT
DEVELOPMENT FOR
TV SERVICING**

12 MODELS

SANS-A-FUSE®

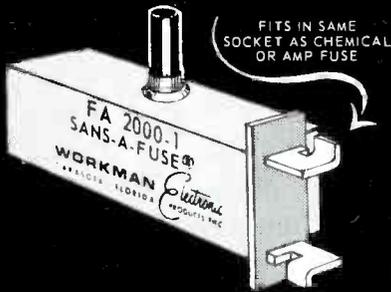

FITS IN SAME
SOCKET AS CHEMICAL
OR AMP FUSE

**COLOR CODED CIRCUIT
BREAKER REPLACEMENT
FOR CHEMICAL OR
AMP FUSE**


**SAVES TIME AND FUSES
WHEN LOCATING SHORTS
IN TELEVISION CIRCUITS**

DEVELOPED AND
MANUFACTURED BY

WORK-MAN *Electronic*
PRODUCTS, INC.
BOX 3828 SARASOTA, FLA. 33578
TELEPHONE: Area Code 813 955-4242

Circle 27 on literature card

**REBUILD
YOUR OWN
PICTURE TUBES?**

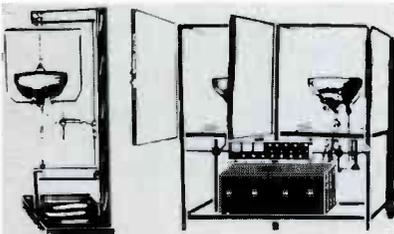

With Lakeside Industries precision equipment, you can rebuild any picture tube!

EASY TO OPERATE!

Requires only 4x8 ft. of space.
Your cost to rebuild black and white—
\$1.50

Your cost to rebuild Color—\$5.80

For complete details, mail coupon.

Lakeside Industries

5234 N. Clark St.
Chicago, Ill. 60640
Phone: 312-271-3399

- Free demonstration appointment
- Send me more information

Name

Address

City State

Circle 28 on literature card


productreport

for further information on any of the following items, circle the associated number on the reader service card.

**Low-voltage
Power Supply Transformer**

The Stancor TP-5 Rectifier Transformer, for use in low-voltage power supplies, is available from Essex International, Inc.

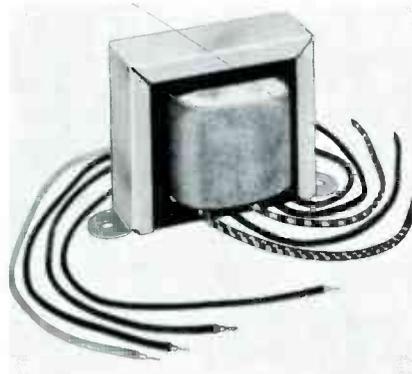The Stancor TP Series (TP-2 thru TP-5) is designed for 117-volt, 60-hz input. It has multiple primary



and secondary taps for output voltages ranging from 6.5 to 42 volts (center tapped). Each unit differs in the secondary current rating.

The TP-5 cost range is from \$6.77 to \$11.27 each in quantities of one to nine.

Circle 70 on literature card

TV Pole Stand


The Slip Seal Co. has introduced a new adjustable pole stand for use with either color or black-and-white television.

According to the manufacturer, the stand can be moved from location to location, without dismantling, in a matter of several minutes. It adjusts to either a high, medium or low height without taking the unit apart. It swivels easily and takes little floor space.

The Slip Seal Co. states that the stand requires no tools for assembly and is designed for standard ceilings, ranging from 7 ft. 10 in. to 8 ft. 2 in. in height. Extensions of 6 in. and 12 in. are available for higher ceilings.

Two models of the TV pole stand are available. Model C-20 holds color televisions up to and including 20-in. screens and b-w televisions up to and including 23-in. screens. Model BW-69 holds color sets up

NEED CRYSTALS?

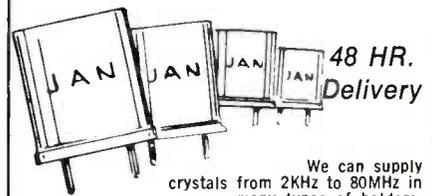

SPECIALS

Color TV crystal (3579, 545KHz) wire leads \$1.60; 4 for \$5.00
100KHz freq. std. crystal (HC13/U) \$4.50 (HC13/U)
1000KHz freq. std. crystal (HC6/U) \$3.50
Any CB crystal, transmit or receive \$2.25
Any amateur band crystal (except 80 meters) \$1.50 or in FT-243 holders 4 for \$5.00
Any marine frequency (HC6/U) \$2.85
80 meter—FT243 holders \$2.50

We have in stock over six million crystals which include types CR1A/AR, FT243, FT241, MC7, FT249, HC6/U, HC13/U, HC25/U, HC18/U, etc. Send 10¢ for our 1970 catalog with oscillator circuits, listing thousands of frequencies in stock for immediate delivery. (Add 10¢ per crystal to above prices for shipment 1st class mail, 15¢ each for air mail).



Special Quantity Prices to Jobbers and Dealers
ORDER DIRECT with check or money order to:

2400 Crystal Drive
Fort Myers, Florida 33901

Circle 29 on literature card


*Who needs a tuner wash?
Save your money and use
QUIETROLE*

The product that cleans while it lubricates. Zero effect on capacity and resistance. Harmless to plastics and metals. Keeps color and black and white on the beam. Non-flammable.



manufactured by
QUIETROLE CO.
Spartanburg, South Carolina

Circle 30 on literature card

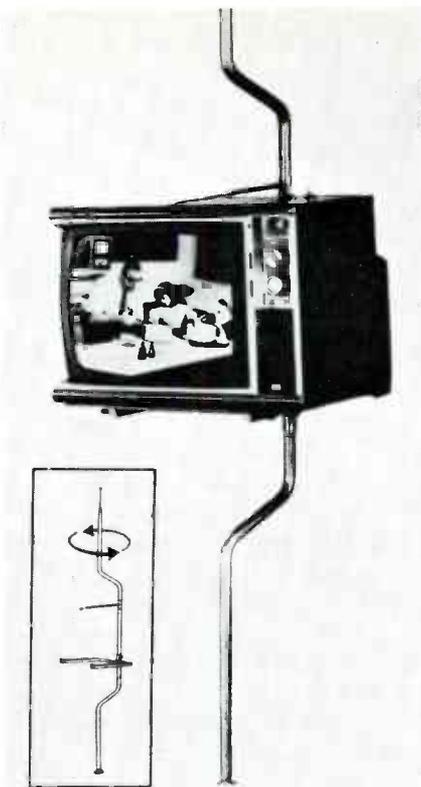

to and including 18-in. screens, providing the depth does not exceed 15 in. It will hold b-w television sets up to and including 21-in. screens.

The stands are manufactured from 1 1/4-in. steel tubing and are guaranteed by the manufacturer against all defects in material and workmanship. Model C-20, finished in gold, sells for \$24.95. Bronze-finished Model BW-69 sells for \$22.95.

Circle 71 on literature card

Miniature Welding Torch



Tescom Corp. has announced the development of the "Little Torch," designed for precision welding.

The torch is said to weld metal smaller than .002-in. wire and up to 16-gauge steel. It is applicable for heat bonding, welding and soldering. Tescom states that "Little

Torch" uses oxygen and a fuel gas (acetylene, hydrogen, LP-gas or natural gas) to produce flame temperature to 6300° F. It operates at pressures of 2 to 4 psi and uses gas at the rate of .023 to 2.54 cfh.

The "Little Torch" is equipped with five different tips which swivel 360° for ease of handling. The two smallest tips (#1 and #2) have sapphire jeweled orifices for extra durability and precision performance, it is reported.

The torch is available in a variety of different kits, ranging in

price from \$74.65 to \$294.45, depending on the accessories needed.

Circle 72 on literature card

Hand Stripper for Metal Braid Shielding

Availability of a hand stripping tool for metal braid shielding has been announced by the Henry Mann Co.


The tool reportedly removes shielding from metal braid 500% faster in production line applications and is fully portable, requiring no power connections. It is stated

Introducing the world's only \$339 triggered scope.

Before you say you don't need a triggered scope, look what's happening to TV servicing: tubes are out, transistors and IC's are in.

With tubes you could play hit-or-miss, knowing the tube would take the overload. Try the same thing now, and good-bye transistors.

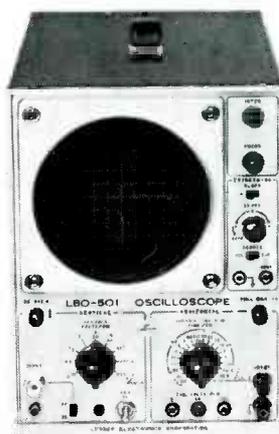For new-era circuitry, Leader introduces a new-era troubleshooter. A triggered scope, just like the ones the TV designers use.



Now the wave shape is locked in and continuously displayed. Now you can look at a waveform containing high and low frequency components. Now you can determine voltage directly and instantly.

Before you say \$339 is a lot of bread, look what it buys: Leader's LBO-501 5-inch triggered scope, with a bandwidth of DC to 10MHz and a solid state package.

Going like hotcakes at your Leader distributor.


Seeing is believing.

LEADER INSTRUMENTS

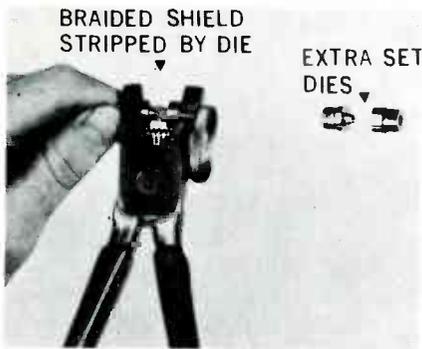37-27 27th Street, Long Island City, N.Y. 11101, (212) 729-7411

Circle 31 on literature card

that inner plastic insulations cannot be damaged because no heat or razor blades are employed.



Wire is inserted into the "Shield-Stripp" tool, the plier-like handles are pressed and, as the jaws close, the braided shielding bulges out and is sheared off as the punch enters the die. The manufacturer states that the shielding on the wire is cut cleanly and left slightly flared to receive the ferrule and ground connector.

The tool is available in three different models. Dies numbered 1 through 13, covering OD of shielding from sizes .055 to .248 are in-

terchangeable on Model 8. Model 10 is designed for use with dies numbered 43 through 56, which range in sizes from .077 to .307. Model 10X is designed for stripping metal shielding in sizes of 5/16 in. to 1/2 in. OD.

Model 8 is priced at \$31.50, Model 10 sells for \$34.50 and Model 10X is listed at \$59.50.

Circle 73 on literature card

VOM Teaching Aid and Demonstrator

A special jumbo-size training aid and VOM instrument demonstrator designed for classroom and industry use is being offered by the Triplett Electrical Instrument Co.

The demonstrator is a large-scale replica of Triplett's 630-APLK overload-protected VOM instrument. It can be used for demonstration purposes for the entire Triplett Series 630 product line. The 630-APLK training aid simulates DC measurements in current, voltage and ohms, and AC measurements in voltage only.


The demonstrator comes equipped with a knife-edge pointer that the instructor or student can operate manually. The overload button is triggered by full-scale deflection of the pointer, causing it to pop out, simulating an overload condition.

An ohms adjust knob is operable for simulated zeroing operation.




TOP PERFORMING UHF/VHF ANTENNAS FOR ALL AREAS!...

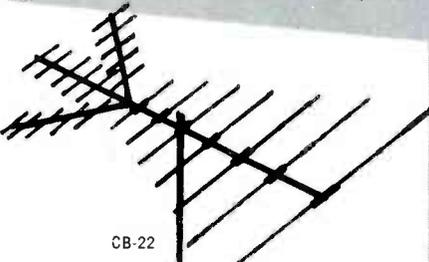Color engineered for best reception on UHF/VHF Channels 2 to 83!
Exclusively features Reynolds Aluminum durable Colorweld Gold finish!
Single down-lead for economical, simple installation!
Durable all-aluminum weather proof construction for long installation life!




COLOR-BOOSTER SERIES

Model	Number of elements			Range of Reception		
	VHF	UHF	Total	VHF up to	UHF up to	
CB-22	7	5	10	22	50 miles	35 miles
CB-28	11	7	10	28	125 miles	60 miles
CB-34	15	9	10	34	150 miles	80 miles

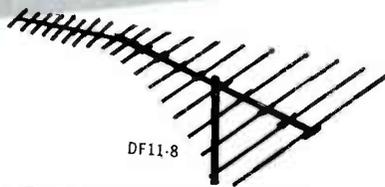


DIRECTION-FINDER SERIES

Model	Number of elements			Range of Reception	
	VHF	UHF	Total	VHF up to	UHF up to
DF3-3	3	3	6	30 miles	20 miles
DF5-4	5	4	9	45 miles	40 miles
DF7-8	7	8	15	50 miles	75 miles
DF7-11	7	11	18	50 miles	100 miles
DF11-8	11	8	19	75 miles	75 miles
DF11-11	11	11	22	75 miles	100 miles
DF15-8	15	8	23	100 miles	75 miles
DF15-11	15	11	26	100 miles	100 miles
DF19-8	19	8	27	125 miles	75 miles
DF19-11	19	11	30	125 miles	100 miles

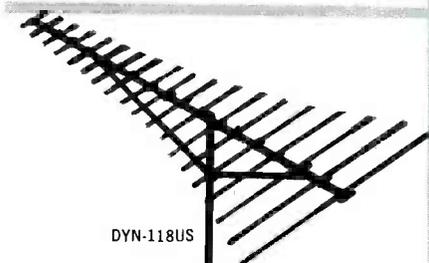

DYNERGY SERIES

Model	Number of elements			Range of Reception	
	VHF	UHF	Total	VHF up to	UHF up to
DYN-33US	3	3	6	35 miles	20 miles
DYN-54US	5	4	9	60 miles	30 miles
DYN-66US	6	6	12	65 miles	50 miles
DYN-88US	8	8	16	125 miles	75 miles
DYN-118US	11	8	19	125 miles	75 miles
DYN-158US	15	8	23	150 miles	75 miles

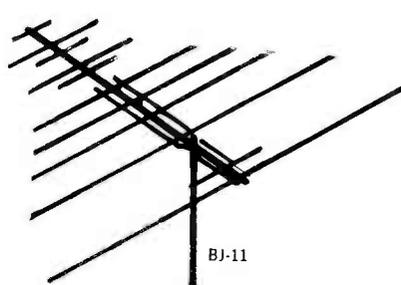

BIG SHOT JR. SERIES

Model	Number of elements	Area Used
BJ-8	8	Metropolitan and Suburban
BJ-11	11	Metropolitan and Suburban
BJ-12	12	Semi-Fringe

For complete specs and Profit picture—Write:

RMS ELECTRONICS, INC.

50 Antin Place, Bronx, N.Y. 10462 • Tel. (212) 892-6700

Circle 32 on literature card

The large polarity-reversal switch may be rotated enabling the instructor to demonstrate range selection and dial association. The use of the mirrored scale incorporated in the unit may also be utilized to teach the student or trainee the value of anti-parallax. A set of test leads is also supplied which can be plugged into the demonstrator to familiarize the student with the operation and set-up of the VOM.

The Triplet demonstrator, complete with a set of instructions and a schematic diagram of a typical basic circuit that can be used for making simulated measurements, is user net priced at \$30.00. ▲

Circle 74 on literature card

Jerrold Offers Free 3-Day MATV Course

A three-day Master Antenna Television (MATV) course covering design and installation techniques will be conducted January 20-22 by Jerrold Electronics at their General Office facilities, 401 Walnut Street, Philadelphia, Pa.

The course is offered without charge, except for travel and living expenses, which are to be paid by each person attending, or their sponsor. All classroom and laboratory materials, refreshments at morning and afternoon breaks, and lunches will be provided without cost by Jerrold.

Decibels, antennas, transmission lines, amplifiers, splitters, taps, MATV system layout techniques, problems and demonstrations will be presented during the first two days. An "advanced system school" on the third day will cover strip amplifier head-ends including PMA, HPM and Modlin systems, plus all-channel J-Jacks equipment and layouts.

The starting time each day will be 9:00 a.m. Russell Gimellaro, Technical Director of Jerrold MATV Products, will conduct the course. Dealers, technicians and sales personnel are invited to attend the course.

Course reservations can be made by calling Janis Lerman at Jerrold's offices in Philadelphia (phone WA5-9870). Motel accommodations can be made at Holiday Inn, 1311 Walnut Street, Philadelphia. ▲



When you charge your customer \$137.00* for a replacement color picture tube, you'll want to be certain it was his tube that was defective... not your tester!

You can be sure, if you use RCA's really reliable, all solid-state WT-509A to test for emission quality, interelectrode leakage, shorted elements... (WT-509A even includes an "activate" function to boost the performance of some low-emission tubes.)

Along with the WT-509A, you get five test sockets, one of them a "universal" test adaptor — unique from RCA — that can be used with any type of tube or socket arrangement.

Useful extra's: big, readable meter and a sturdy luggage-type carrying case with a handy storage compartment.

Add this fact: the suggested retail price is only \$118.00**

See WT-509A at your Authorized RCA Test Equipment Distributor, or write RCA Commercial Engineering, Department 25X/A-93,415 South Fifth Street, Harrison, New Jersey 07029.

RCA

*Optional List Price for RCA H-25XP22
**Optional Distributor Resale Price

Circle 33 on literature card

Magnavox PARTS & TUBES

... help keep Magnavox products working like new. Buy them from our nearest factory parts branch.



PACIFIC COAST/
NORTH BRANCH:
Magna-Par Company
1366 San Mateo Ave.
South San Francisco
California 94080
Telephone: 415 871-5080
Teletype: 910-371-7237

NORTHEAST BRANCH:
Magna-Par Company
159 E. Union Avenue
E. Rutherford, N.J. 07073
Telephones:
201 935-1212
(NYC) 212 279-3973
Teletype: 710-898-0105

PACIFIC COAST/
SOUTH BRANCH:
Magna-Par Company
2825 Maricopa Street
Torrance, Calif. 90503
Telephones:
213 328-0770
(L.A.) 775-3572
Teletype: 910-349-6957

SOUTHERN BRANCH:
Magna-Par Company
144 Enterprise Blvd., SW
Atlanta, Georgia 30331
Telephone: 404 349-1313
Teletype: 810-751-8637

SOUTHWEST BRANCH:
Magna-Par Company
8809 W. Carpenter
Freeway
Dallas, Texas 75247
Telephone: 214 637-1710
Teletype: 910-861-4543

MIDWEST BRANCH:
Magna-Par Company
7500 Frontage Road
Skokie, Illinois 60076
Telephones:
312 679-8700
(CHI) 312 282-8088

THE **Magnavox** COMPANY

FORT WAYNE, INDIANA 46803
Circle 34 on literature card

catalogs literature

ANTENNAS

100. *New-Tronics Corp.* — announces the publication of a 3-color, 20-page 1970 Hustler CB Catalog, which covers over 80 models of their CB antennas.

AUDIO

101. *Nortronics Co., Inc.* — has released a short form Tape Head Replacement and Conversion Guide, covering 218 manufacturers and over 2,100 tape recorder models.

SPECIAL EQUIPMENT

102. *Dazor Manufacturing Corp.* —has issued 4 new bulletins: Catalog No. 6300, covering their complete line of "floating" lights; Supplement A to Catalog No. 6300; Form 850, which illustrates the Dazor float-

ing magnifier; and Form 821, which also covers their floating magnifier.

103. *Lucasey Manufacturing Co., Inc.*—has released a 4-color, 4-page catalog covering their line of television brackets.

TECHNICAL PUBLICATIONS

104. *Howard W. Sams*—Literature describes popular and informative publications on radio and TV servicing, communication, audio, hi-fi and industrial electronics, including 1969 catalog of technical books on every phase of electronics.*

TEST EQUIPMENT

105. *Lectrotech* — Catalog describing the complete Lectrotech line of vectorscopes, color-bar generators, oscilloscopes, picture tube analyzer, transistor TV sweep circuit analyzer, CB analyzer and frequency meter, power supplies, Lectrocell, and Metergard.*

*Check "Index to Advertisers" for additional information.

MODEL **880** *Mercury* **NEW PICTURE TUBE TESTER/REJUVENATOR and COLOR TRACKING ANALYZER**

Be SURE if your tube is good or bad

gives you the correct answer — always!

JUST **79⁹⁵** ALL MERCURY TEST EQUIPMENT GUARANTEED ONE FULL YEAR!
WIRED

- Tests ALL color tubes
- Tests beam current (or emission) of each gun
- Analyzes color track of the 3 guns and gray scale
- Rejuvenates low brightness picture tubes
- Easy tracking between the 3 guns and positive
- Rewelds most intermittent elements
- "Life" test predicts remaining cathode emission test
- Lifetime anodized aluminum panel and damage — resistant carrying case
- Complete — Color and B/W sockets, Data Book and instruction manual.

Write for complete catalog of Mercury Test and Repair Equipment, and name of your nearest dealer.

MERCURY ELECTRONICS CORPORATION
315 Roslyn Road • Mineola, N.Y. 11501 • (516) 742-5400
CANADA: William Cohen Corp. • 8900 Park Avenue • Montreal-11

Circle 35 on literature card

Admiral Corp.	6
B & K Mfg. Co., Div. of Dynascan Corp.	1
Bussmann Mfg. Div. Div. of McGraw-Edison Co.	10-11
C.R.T. Equipment Co., Inc.	49
Castle TV Tuner Service Inc.	7
EICO Electronic Instrument Co. Inc.	Cover 2
Electro-Voice, Inc.	14
G-C Electronics	13, 61
Jan Crystals	56
Lakeside Industries	56
Leader Instruments Corp.	57
Lectrotech, Inc.	4
Littelfuse, Inc.	Cover 4
Magna-Par Co., Parts Div. of Magnavox Co.	60
Master Appliance Corp.	49
Mercury Electronics Corp.	30, 60
Quam-Nichols Co.	32
Quietrole Co.	56
RCA Electronic Components Picture Tubes	Cover 3
RCA Electronic Components Test Equipment	59
RCA Institutes Inc.	9
RCA Parts & Accessories	41
RMS Electronics, Inc.	58
Rohn Mfg. Co.	15
Howard W. Sams Co., Inc.	21, 33
Sylvania Electric Products, Inc.	16-17
TV Tech Aid	30
Tech Spray	12
Tektronix, Inc.	63
Telematic Div., U.X.L. Corp.	21
Tuner Service Corp.	5
Weller Electric Corp.	48
Workman Electronic Products, Inc.	56
Zenith Sales Co.	3

All New from GC-Walsco!



A Complete line of Phono Drives, Belts & Accessories

New — Expanded Listing — includes replacement parts for Cassettes, foreign models, and many new domestic recorders and changers.

All Walsco numbers cross referenced in new, helpful 24-page cross-reference guide.
See your distributor today.



GC ELECTRONICS

Division of Hydrometals, Inc.
Los Angeles, Calif. Hicksville, L.I., N.Y.
Main Plant: Rockford, Illinois



Circle 36 on literature card

Index of 1969 content

The following code system is used to indicate department coverage of a subject: ASR, Antenna Systems Report; CCM, Color Countermeasures; ES, The Electronic Scanner; LE, Letters to the Editor; NTE, Notes on Test Equipment; PR, Product Report; SYM, Symcure; TER, Test Equipment Report; and TS, The Troubleshooter.

AGC

- Color TV setup May 16
- Oscilloscope, troubleshooting
with Oct. 24
- Solid-state, troubleshooting
 - Circuit, analysis of typical .. Apr 25
 - DC voltage distribution Apr 25
 - Trouble symptoms, common Apr 26

ANTENNA SYSTEMS

- AGC modules, JFD ASR Dec 32
- Attenuators, 75-ohm, JFD Models
SL-6801; SL-6803; SL-6806;
SL-6812; SL-6820 ASR Aug 46
- CB beam, three-element, Mosley
Model PA-311 ASR Nov 34
- Coax, MATV, UHF and VHF,
Belden PR Feb 58
- Flashing Jun 22
- Ghosts Jun 20
- Indoor, Mercury Electronics PR Feb 60
- Installation Jun 22
- Lead adapter, coax to clip, Pomona
Model 2885 and Model
2886 ASR Aug 46
- MATV distribution amplifier
kits, Mosley Models AMP-
25/2; AMP-25/62; AMP-
25/T2; AMP-25/BL2 . ASR Jul 37
- MATV line extenders, JFD Models
SL-6300; SL-6301; SL-6310;
SL-6311 ASR Jul 38
- MATV mobile display unit ES May 4
- MATV tester, JFD Model
SL-6900 TER Aug 45
- Matching transformer, JFD Model
MT60 (indoor) and Model
MT61 (outdoor) ASR Oct 48
- Mobile co-phasing harness,
Avanti ASR Oct 50
- Mobile snap mount, Avanti ASR Sep 38
- Mount, South River Metal Products
Model #TRM PR May 56
- Parameters, TV Jun 16
- Preamplifier, boom-mounted TV,
Finney Models M-20; M-11;
M-12 ASR Aug 46
- Replacement elements, Audiotex-
Home Electronics ASR Nov 34
- Ring and edge-effect Jun 20
- Rotator, multi-set, Alliance
Model T-45 ASR Jul 37
- Satellite-to-home, Sylvania . ES Aug 4
- Signal splitter, UHF/VHF/FM,
JFD ASR Dec 32
- Single channel pre-amplifier,
Finney PR May 54
- Snow Jun 20
- TV, dome-type, Omni Mark
II ASR Jun 62
- TV, all-channel, Jerrold . ASR Dec 32
- Use AFT to diagnose TV antenna

systems

- AFT action, sources of trouble
that affect Sep 32
- Procedure Sep 34
- Simplified theory of AFT .. Sep 35
- VHF-TV/FM amplifier, Finney
Model M-101 ASR Jun 62
- Wall plate, feed-through, Mosley
Model M-1 ASR Jun 62

ASSOCIATIONS, SERVICE

- EIA committee gets NATESA
viewpoint about problem
areas Dec 50
- EIA consumer electronics
show ES Jan 6
- EIA provides color TV servicing
booklet ES Nov 6
- EIA says TV sets are safe .. ES Dec 4
- Eastern service conference,
May 9-May 11 ES May 4
- Home electronic service days,
Chicago, Aug. 15-Aug. 17
(NATESA Convention) . ES Aug 6
- NAB wants comparable VHF and
UHF tuning ES Aug 4
- NARDA convention Mar 8
- NATESA friend of service award
award goes to Zenith .. ES Oct 6
- NATESA friends of service man-
agement award ES May 6
- NATESA policies
 - Accomplishments May 43
 - Certification program May 46
 - Conventions May 46
 - Licensing May 46
 - Objectives May 43
 - Organization May 42
 - Other activities May 44
- NATESA revises code-of-ethics
certificate; assumes arbitrator
role ES Mar 4
- NEA annual convention,
July 23-27 ES May 7
- NEA board of directors meeting,
May 9, 10 ES May 7
- NEA convention speakers ES Jul 6
- NEA electronic hall of fame;
John Graham selected .. ES Mar 4
- NEA hall of fame elects
Finneburgh ES Oct 4
- NEA insurance program ES Jan 6
- NEA gets new director of apprentice-
ship and training ES Jun 6
- NEA outlines serviceability
project ES Nov 4
- NEA Policies
 - Conventions May 46
 - Insurance May 46
 - Objectives May 43
 - Organization May 42
- NEA's certified electronic technician

certificate now inter-

- national ES Jun 4
- Nat'l Assoc. of FM Broadcasters
call for AM and FM on all
radios ES Sep 6
- Nebraska Assoc. re-elects president
for '69 ES Mar 6
- TEA licensing survey ES May 6

AUDIO GENERATORS

- Microphone adapter, Midland-
Ross PR Dec 69
- Solid-state, Century General
Model 4110 TER Aug 44
- Sound system packages, Bell
P/A PR Dec 69

AUDIO SYSTEMS

- Crosstalk amplifiers LE Apr 4
- Loudspeaker, commercial, Jensen
Model FX-52 PR Sep 59
- Output transistor, repeated failure
of, Ranger Model RR29PBTS Sep 56
- Reduced sound, RCA KCS
157A TS Aug 55

AUTO RADIO

- Audio output transistor, repeated
failure of, Ranger Model
RR29PB TS Sep 56
- Capacitor failure, Chevrolet
Model 986545 TS Jul 48
- Direct-coupled audio circuits,
troubleshooting Nov 27
- Single- and double-ended audio
 - Complementary push-pull .. Oct 64
 - Direct-coupled circuits Oct 63
 - Push-pull audio Oct 64
- Stereo FM
 - Bendix system Dec 44
 - Bias pots, trouble in Dec 48
 - Bypass capacitors, trouble in Dec 48
 - Delco system Dec 44
 - Motorola system Dec 44
 - Multiplex PCB's, cracked .. Dec 49
 - Operation, basic Dec 44
 - Output transistors, trouble in Dec 48
 - Stereo-indicator lamp circuits Dec 45
 - Transformer wires loose .. Dec 48
 - Troubleshooting, general .. Dec 46
 - Tuners, trouble in sealed ... Dec 49
- Stereo FM Multiplex
 - Block diagram functional
analysis Nov 18
 - Circuit analysis of individual
states Nov 21
 - Multiplex signal, the Nov 16
 - Stereo-indicator sections Nov 24

BOOK REVIEWS


- Advanced Techniques for
Troubleshooting with the



DUAL TRACE
TYPE D54 — \$550

NEW OSCILLOSCOPES FROM TELEQUIPMENT

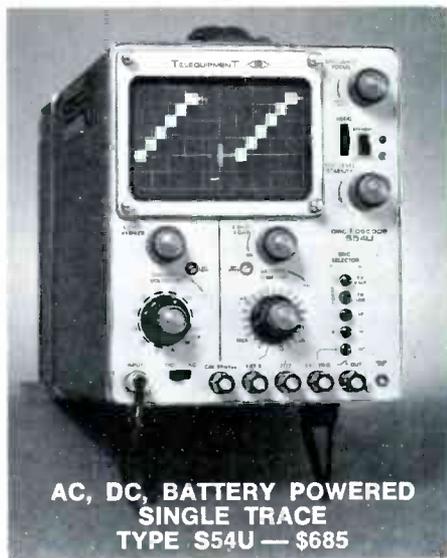- FULLY SOLID STATE
- 10 mV/cm DEFLECTION FACTOR
- 10 MHz BANDWIDTH
- TRIGGERED SWEEP



AC, DC, BATTERY POWERED
SINGLE TRACE
TYPE S54U — \$685



SINGLE TRACE
TYPE S54A — \$435

The 54 Series represents a new standard of performance for low priced oscilloscopes. The use of field effect transistors in the input stages means that the trace is stable . . . even at a deflection factor of 10 mV/cm. The ability to trigger at TV field or line rate, coupled with magnified sweep speeds to 40 nano-seconds per centimeter, permits high resolution analysis of video signals. Want to look at the 3.58 MHz color subcarrier? You can do it with any of the 54 Series.

The Dual-Trace Type D54 lets you look at two signals *simultaneously*, a real help in aligning FM Stereo equipment.

You can take the battery powered Type S54U anywhere. It offers you the convenience of being able to service equipment, like 2-Way radios, right in their own environment.

For *even greater economy* and comparable performance, select the Type S54A.

Telequipment products are backed by a one year warranty, parts support and 26 service centers; marketed through 55 Tektronix Field Offices.

For more information call your local Tektronix Field Engineer or write Tektronix, Inc., P. O. Box 500, Beaverton, Oregon 97005.

U.S. Sales Prices FOB Beaverton, Oregon



..... a subsidiary of **Tektronix, Inc.**

Circle 39 on literature card

Oscilloscope May 58
 Closed-Circuit TV for Engineers
 and Technicians May 58
 FM From Antenna to Audio Aug 43
 How to Fix Transistor Radios
 & Printed Circuits Dec 72
 How to Select and Install
 Antennas Apr 33
 How to Use Grid-Dip
 Oscillators Jun 63
 Know Your Tube and
 Transistor Testers Apr 33
 1-2-3-4 Servicing Automobile
 Stereo Oct 68
 Practical CB Radio Servicing Mar 43
 Servicing the Solid-State Chassis Sep 57
 TV Servicing Guidebook,
 Problems and Solutions Jan 60
 Using Scopes in Color TV Aug 43
 Using Scopes in Transistor
 Circuits Mar 43
 Waveform Measurements Aug 29
 Working with Semiconductors .. Aug 29

B-W TELEVISION

Alignment
 —Markers Aug 14
 —Tips, timesaver Aug 14
 —Traps and coils together Aug 13
 —Tuned circuit, nature of Aug 12
 Bandpass, improper Jun 18
 Control, strip, IRC PR Apr 55
 Converter developed ES Aug 6
 EIA says TV sets are safe ES Dec 4
 Flashing Jun 22
 Fuse burns out repeatedly,
 RCA KCS68E TS Jan 57
 Gain
 —Excessive Jun 18
 —Insufficient Jun 18
 High-voltage failure, Sears Silvertone
 Model M2737U TS Nov 53
 Horizontal and vertical sync
 intermittent, RCA
 KCS104H TS May 50
 Horizontal oscillator intermittently
 does not start, GE "S" and
 "V" series SYM Nov 47
 Horizontal pulling caused by oxi-
 dation, Magnavox
 U47-005 TS Apr 53
 Horizontal white lines at top of
 raster, RCA KCS130F .. TS Jan 57
 Imported TV on upswing ES May 6
 Miniature TV picture tube ES Jul 4
 Noise, excessive Jun 18
 Picture smear and pulling,
 Olympic NDP SYM Nov 47
 Picture weak Jun 18
 Picture weak, sound and sync
 normal Jun 20
 Picture weak, sync weak, sound
 garbled, Magnavox
 U44-01-31 TS Jun 54
 RF transistor shorted, Sony
 TV710U and 720U .. SYM Nov 47
 Raster missing, sound good,
 Zenith 14M20Z TS Oct 67
 Raster missing, no high voltage,
 squeal in flyback, Admiral
 portable TS Jan 57
 Reduced sound, RCA
 KCS157A TS Aug 55
 Ringing and edge-effect Jun 20
 TV Tube Brightener, Perma-
 Power Model C-414 PR Jun 66
 Thinner CRT using deflection
 technique, Philco-Ford .. ES Aug 44
 Vertical foldover, RCA
 KCS140A TS Jan 57

Vertical sweep insufficient, com-
 pression at top, Magnavox
 T908 TS Apr 53
 Vertical sweep insufficient, Sears
 Silvertone 528.51800 TS Jan 58
 Vertical sync intermittent,
 Emerson 120758A TS May 50
 Zenith 1Y21B55, loading, horizontal
 output circuit TS Feb 57

BUSINESS

Chances of armed robbery
 —Popularity of service shops
 among robbers Aug 22
 —Lessen the chances, how to Aug 23
 —Reaction to robbery Aug 23
 Consumer electronic sales,
 1968 ES Mar 4
 Manufacturer owned and operated
 service centers
 —General Electric service
 facilities Apr 48
 —RCA Service Company Apr 47
 Perspective, 1969 Dec 24
 Pricing
 —Lower limits Dec 13
 —Upper limits Dec 10
 Service contracts sustain high-
 volume business
 —Customer relations and
 scheduling of service calls .. Nov 14
 —Parts availability Nov 12
 —Training and incentives Nov 12
 Sperry TV
 —Building setup Jan 13
 —Job control center Jan 13
 —Manpower management Jan 16
 —Parts inventory Jan 13
 —Profile of policies and
 operation Jan 10
 —Rates Jan 18
 —Specialization Jan 12
 —Technician training Jan 20
 —Work area Jan 13
 Tele-Quick
 —Concept of franchising Mar 14
 —Method of servicing Mar 12
 —Methods of developing the
 operation Mar 10

CITIZENS BAND

TVI filter, Gold Line
 Connector PR Jan 61

COLOR GENERATORS

Eico Model 385 NTE May 48
 Heathkit Model IG-28 TER Aug 45
 Leader Model LCG-388 TER Nov 30
 Leader Model LCG-389 PR Mar 70
 Leader Model LCG-390 TER Oct 46
 RCA Model WR-502A NTE Jan 54
 Sylvania TER Dec 30

COLOR TV

Admiral introduces 12-inch picture
 tube ES Mar 6
 Admiral K10
 —Amplifier, color difference .. Apr 38
 —Chroma oscillator Apr 37
 —Circuit description Apr 34
 —Color killer system Apr 39
 —Demodulation Apr 37
 —Horizontal blanker Apr 38
 —Power supply Apr 34
 —Sound circuits Apr 35
 —Sync and sweep Apr 36
 —3.58-MHz reference feedback
 system Apr 39
 —Video IF Strip Apr 34
 Alignment

—Diagnosis, sweep curves
 aid in Jul 51
 —Equipment connections, IF
 and VSM sweep Jul 54
 —Equipment specifications, sweep
 alignment Jul 52
 —Markers Aug 14
 —Misalignment, reasons for .. Jul 51
 —Misalignment, symptoms caused
 by Jul 50
 —Tips, general Jul 53
 —Tips, timesaver Aug 14
 —Traps and coils together Aug 13
 —Tuned circuit, nature of Aug 12
 Alignment, RCA CTC38 and CTC40
 —Approach Sep 44
 —Chroma Sep 51
 —Complete procedure for
 CTC38 Sep 48
 —Difficulties in alignment,
 solutions to Sep 53
 —Equipment considerations .. Sep 44
 —Generator checkout Sep 46
 —Non-critical settings, use of .. Sep 48
 —Specifications Sep 44
 —Video sweep modulation
 (VSM) alignment Sep 52
 Alignment, Zenith 14A9C51 Nov 58
 All-IC portable, Japan
 develops ES Jun 4
 Automatic Tint Control, Magnavox
 —Automatic Color Gain
 Control Oct 32
 —Operation Oct 26
 —Problems, common Oct 26
 —Troubleshooting the circuit .. Oct 33
 Bandpass, improper Jun 18
 Baumritter to manufacture TV ES Aug 6
 Blue lateral and purity assembly,
 J. W. Miller Model 7604 PR Jun 65
 Brightness excessive, weak color,
 Olympic CT910 SYM Nov 46
 Color weak, color sync missing,
 General Electric CA TS Aug 56
 Color intermittent, RCA
 CTC25X TS May 52
 Control, strip, IRC PR Apr 55
 Converter developed ES Aug 6
 Flashing Jun 22
 Flashing and blurred picture,
 intermittent, RCA
 CTC7A SYM Nov 46
 Focus poor, Admiral
 G11G1-3 CCM Feb 52
 Gain
 —Excessive Jun 18
 —Insufficient Jun 18
 Ghosts (not antenna, delay line or
 tunable), RCA CTC21 SYM Nov 47
 Green and red missing,
 RCA CTC17X TS Apr 53
 Horizontal "lock-out" and critical
 locking, Magnavox
 T924 SYM Nov 47
 Horizontal sync, method for
 checking, Zenith sets TS Dec 52
 Horizontal white line, Sylvania
 DO3 CCM Feb 53
 Hum bar in picture, GE
 KE SYM Nov 46
 Imported TV on upswing ES May 6
 Intermittent arcing,
 GE KE SYM Nov 46
 Intermittent color,
 RCA CTC25A TS Dec 52
 Intermittent color sync,
 Motorola TSA914 TS Apr 54
 Irregular line in upper left screen;
 difference in contrast,
 Zenith 15Y6C15 TS Aug 55

- Laser TV ES Jul 4
Laser TV display system ES Jan 4
Line-voltage regulator,
 Terado PR Dec 71
Low voltage decreased,
 Admiral 25B6 TS Feb 56
Mitsubishi begins marketing
 of TV in U.S. ES Nov 6
Motorola memory-module
 remote control Feb 16
New for 1970
 —Admiral Dec 54
 —Andrea Dec 55
 —General Electric Dec 55
 —Magnavox Dec 56
 —Motorola Dec 57
 —Packard Bell Dec 58
 —Philco Dec 59
 —RCA Dec 60
 —Sony Dec 63
 —Sylvania Dec 64
 —Zenith Dec 65
Noise, excessive Jun 18
110-degree CRT developed by
 Japanese ES Dec 6
Overload, smeared picture,
 RCA CTC24 SYM Nov 47
Picture and sound missing,
 RCA CTC35A CCM Feb 52
Picture and sound missing,
 Zenith 20Z1C37 TS Aug 56
Picture flickers,
 RCA CTC30 CCM Feb 53
Picture missing, high voltage and
 boost low, RCA CTC31A TS Apr 54
Picture tube troubles
 —Dog ear in lower left corner,
 RCA TS May 52
 —Purity misadjusted,
 Zenith TS May 53
Picture weak Jun 18
Picture weak, sound and sync
 normal Jun 20
Ringing and edge-effect Jun 20
RCA CTC16
 —Color circuitry, trouble in .. Aug 53
 —Focus problems, poor Aug 53
 —Horizontal and high-voltage
 circuit trouble Aug 52
 —Intermittent contact, RF, IF
 and video circuit troubles .. Aug 50
 —Picture, sound missing, RF,
 IF and video circuit troubles Aug 50
 —Picture, sound, raster missing,
 low-voltage circuit troubles Aug 48
 —Sound problems Aug 50
 —Vertical circuits, trouble in Aug 51
RCA CTC40
 —AFT operation Jan 37
 —Automatic Fine Tuning Jan 37
 —Automatic frequency and
 phase control detector Feb 33
 —Bandpass amplifier Feb 32
 —Burst amplifier Feb 32
 —Chroma amplifiers,
 1st and 2nd Feb 32
 —Chroma demodulators Feb 34
 —Circuit analysis Jan 36
 —Clamp circuitry Feb 37
 —Color driver and output
 circuitry Feb 34
 —Color-killer circuits Feb 34
 —Horizontal AFC and oscillator,
 theory of operation Mar 38
 —Horizontal deflection Mar 39
 —Horizontal oscillator
 B+ source Mar 39
 —Phase splitter Feb 32
 —Pincushion correction Jan 42
 —Power supply Jan 43
 —Sound section Jan 36
 —Temperature induced frequency
 change, control of Mar 39
 —3.58-MHz reference
 oscillator Feb 33
 —Tracking Feb 37
 —Vertical sweep Jan 38
RCA twice-as-bright
 picture tube ES Jul 6
Raster missing, sound normal,
 RCA CTC31A TS Jul 48
Raster narrow, RCA CTC20A TS Jun 54
Raster weak, RCA CTC31A TS Jul 48
Safety of TV, EIA
 statement concerning ES Dec 4
Servicing booklet available
 from EIA ES Nov 6
Setup
 —AGC May 16
 —B-W tracking Jun 30
 —Brightness range May 17
 —Color-killer adjustment May 17
 —Convergence Jun 38
 —Degaussing May 14
 —Focusing May 17
 —High voltage May 15
 —Horizontal size May 16
 —Major setup adjustments .. May 14
 —Pincushioning May 16
 —Purity, adjustments of Jun 30
 —Set-up switch, procedure
 for sets with Jun 31
 —Set-up switch, procedure
 for sets without Jun 32
 —Tilt May 16
 —Vertical size and linearity .. May 16
Sony Corp. Single-Gun tube .. ES Mar 4
Sound diminishing, RCA
 CTC16 TS Mar 62
Sylvania D12 and D13, operation of
 —Blanker circuit Feb 28
 —Brightness control Feb 30
 —Burst amplifier Feb 28
 —Chroma IF amplifiers Feb 24
 —DC restoration Feb 30
 —High-voltage circuits,
 protection for Feb 30
 —X and Z demodulators Feb 29
Sylvania HO1 Scanner
 —Adjustments and set-up Jan 29
 —Amplification, signal Jan 28
 —Automatic brightness control Jan 28
 —Automatic slide changing
 and "beep" insertion Jan 29
 —Flying-spot tube circuitry .. Jan 24
 —Gamma correction circuit .. Jan 25
 —Matrixing, signal Jan 28
 —Matrixing, X and Z Jan 28
 —Photomultiplier tube theory Jan 24
 —Restoration, DC Jan 25
 —Scanner operation Jan 22
Sylvania schedules three new CRT's
 for '70 ES May 4
TV tube brightener, Perma-
 Power Model C-414 PR Jun 66
Troubleshooting in home
 —B-W video, loss of May 22
 —Brightness and screen
 problems May 22
 —Color, missing or weak May 21
 —Contrast dim, picture
 blurred May 22
 —How much work should be
 done in the home? May 20
 —Hum May 22
 —Overpeaking May 22
 —Tools and equipment needed May 18
 —Vertical retrace lines May 22
Tuner intermittent,
 Olympic CT919 SYM Nov 46
Vertical sync missing, RCA CTC-
 11A, 11, 10, 9, 7 LE Jan 9
Video amplifiers, troubleshooting
 —Brightness, incorrect May 30
 —Isolating faults May 26
 —Response poor May 30
 —Theory May 24
 —Weak or missing May 28
Video and sound missing,
 RCA CTC28 TS Mar 62
Video missing, raster missing,
 GE KE SYM Nov 46
Visual-aid system for adjusting
 tint ES Jul 6
Voltage adjustor, Terado
 Model 50-172 PR-Jul 58
X-radiation testing ES Aug 6
COMMUNICATIONS
CATV can carry paid ads and
 originate own programs, FCC
 has ruled ES Dec 6
Converter, Herbert Salch & Co.
 Pro Tunaverter PR Jul 58
Crystals, transmit and receive,
 Shepherd PR Sep 62
Marine SSB
 —Linear power amplification .Oct 54
 —Modulator, balanced Oct 53
 —Receiving single-sideband ... Oct 52
 —Signal, the Oct 51
 —Transmitter, the Oct 52
Pay-TV standards set ES Dec 6
TV cable duct, 3M Model
 No. 807 ASR Oct 48
CONNECTORS AND ACCESSORIES
Banana plug adapters, miniature,
 Pomona Electronics PR Jan 61
Banana plug patch cord,
 Pomona Electronics PR Mar 68
Clip, cable or tubing,
 Richco Plastic PR Dec 70
Coax cable assemblies,
 Amphenol PR Apr 55
Harnessing system,
 Electrovert PR Apr 55
Indoor TV coupler, Craftsman
 Model 761 ASR Sep 38
Patch cords, Methode Mfg. .. PR Feb 60
Solderless connector, Gold Line
 Model PL 259 PR Oct 70
DIODES
Curve tracer, Measurement Control
 Devices Model CT-501 .PR Mar 69
High-voltage ES Jul 4
Tester, Texscan Model
 DT-100 NTE Jun 42
FET METERS
In- or out-of-circuit,
 Sencore Model TF17 .. TER Oct 46
Sencore Model TF151 NTE Mar 66
FM RADIO
Stereo Multiplex in Auto
 —Block diagram functional
 analysis Nov 18
 —Circuit analysis of individual
 stages Nov 21
 —Multiplex signal, the Nov 16
 —Stereo-indicator sections ... Nov 24
GUIDES
Source guide to imported consumer
 electronic products Nov 38
Test equipment availability Mar 44
Test equipment manufacturers,
 list of Mar 61

Tube substitution supplement Jan a
 Feb a
 Mar 63
 Apr 41
 Nov 51

HIGH VOLTAGE

Admiral portable TV, in TS Jan 57
 Arc from rear of high-voltage
 rectifier TS Feb 55
 Circuits, Sylvania D12 and D13 Feb 30
 Color TV setup May 15
 Failure, Sears Silvertone
 Model M2737U TS Nov 53
 Low, boost low, picture missing,
 RCA CTC31A TS Apr 54
 Missing, causes of
 —Horizontal oscillator or control
 circuits, failure in Aug 20
 —Loads, excessive Aug 19
 —Pinning down the trouble Aug 17
 —Using the senses Aug 16
 Regulator problems, solving
 —Adjustment without meters Jun 58
 —Emergency regulator systems Jun 61
 —Pulse regulators Jun 58
 —Series vs shunt regulators Jun 56
 —Shunt regulators,
 troubleshooting Jun 57
 —Shunt regulator circuits,
 practical Jun 56
 —Sweep power regulators Jun 59
 Selenium rectifiers, Rectifier
 Components PR Oct 72

HORIZONTAL SWEEP

Barkhausen lines Apr 22
 Color TV setup, adjusting during May 16
 Foldover at right edge of screen Apr 22
 Oscillator defective TS Aug 55
 Pulling due to oxidation,
 Magnavox U47-47-005 TS Apr 53
 Streaking across entire raster Apr 23
 Width and height excessive Apr 22
 Width and height reduced Apr 22
 White lines at top of raster,
 RCA KCS130F TS Jan 57
 White line, Sylvania DO3 CCM Feb 53

HORIZONTAL SYNC

Method for checking, Zenith
 color sets TS Dec 52
 Simplified explanation of
 —AFC detector, the Oct 58
 —AFC tube, the Oct 60
 —Direct oscillator frequency
 control Oct 60
 —Separating horizontal sync
 from vertical sync Oct 57
 —Separator Oct 56

INTERFERENCE

Hum, sources of Jan 45
 Splotches at right side of screen Apr 23
 Vertical line at extreme left of
 screen Apr 23

INTERMITTENT TROUBLES

Color, RCA CTC25X TS May 52
 Color sync, Motorola
 TSA914 TS Apr 54
 Vertical sync, Emerson
 120758A TS May 50

LICENSING

Consumer electronic service
 licensing, special report on Jul 10
 —Formulating your own ideas
 about licensing Jul 13
 —Laws in operation Jul 10
 —Legislation, initiation of Jul 10

—Objectives Jul 10
 —Opposition Jul 10
 —Trade associations' attitudes Jul 12
 NATESA's approach to May 46
 New York state again
 tries TV licensing ES Mar 4
 TEA survey ES May 6

LOW-VOLTAGE POWER SUPPLY

Admiral L71N52,
 chassis 25B6 TS Feb 56
 DC bench, Lafayette Radio Model
 No. 99-5077 TER Sep 36
 DC regulated, Electro Products
 Models PSR-12-25,
 PSR-12-50 TER Oct 47
 Voltage doubler,
 open capacitor TS Feb 55

MARKER GENERATORS

Sweep/marker, B & K Model
 415 TER Nov 54
 Sweep/marker, Sencore Model
 SM152 TER Sep 37

MISCELLANEOUS

Battery, rechargeable,
 Yardney PR May 54
 Garage door opener system,
 Alliance Model Genie
 AC-24 PR May 54
 Lamps, high-intensity, Swing-O-
 Lite Models No. 800 and No.
 900 PR Aug 58
 Magnifier, Ocvi Instrument
 Div./Ednalite PR Nov 66
 Panel lamp, low-voltage,
 Mura PR Nov 69
 Switching system, wireless,
 Workman Model SW-24 PR Sep 58
 3-D TV ES Jul 4
 Typewriter, voice-operated ES Jun 6

OSCILLOSCOPES

Diagnostic, B & K
 Model 1450 NTE Feb 49
 Dual-beam, Tektronix TER Dec 30
 Leader Model LBO-52B PR Apr 56
 Mercury Electronics Model
 3000 PR Mar 70
 Poly-Trace, Grand Industries PR Feb 61
 Probes, use of TS Oct 65
 Recurrent or Triggered
 —Bandwidth Dec 38
 —TV alignment, use for Dec 41
 —Triggered, dial labels and
 markings Dec 36
 —Usage Dec 40
 Solid-state plug-in, Tektronix
 Type 3A9 PR Apr 55
 Triggered scopes
 —Placing Sep 19
 —Time base Sep 21
 —Trace, stable Sep 18
 Troubleshooting TV
 —AGC troubleshooting Oct 24
 —IF amplifiers Oct 14
 —RF tuners Oct 10
 —Sync waveforms and tests Oct 22
 —Video amplifier tests Oct 21
 —Video detectors Oct 14
 X-Y with 7-inch CRT, Data
 Instruments Model 572 TER Jul 35

PICTURE TUBES

Admiral introduces
 12-inch color tube ES Mar 6
 Miniature color TV tube ES Jul 4
 RCA twice-as-bright tube ES Jul 6
 Servicing kit, mini-base, UXL PR Oct 69

Sony Corp. single-gun color
 tube ES Mar 4
 Sylvania schedules three new
 color CRT's for '70 ES May 4
 Tester, Seco Model 88A TER Jul 35

PROTECTION DEVICES

Alarm system, wireless,
 Selectron PR Aug 58
 CCTV Surveillance system,
 Packard Bell GTS-1 PR Aug 59
 Choke, smoothing, Essex
 Wire PR May 54
 Circuit breaker/fuse,
 Workman Electronics .. PR Nov 68
 Isolation transformer,
 Essex Wire PR May 55
 TV and FM Receiver protector,
 Telecommunications
 Model 300 ASR Sep 39

RADIO

AM receiver in a single IC.
 Amperex ES Sep 4
 Improper neutralization,
 Panasonic Model
 RE746/756 TS Mar 62

REMOTE UNITS, TV

Motorola memory-module
 —Audio and chroma controls Feb 16
 —Power supplies Feb 16
 —Receiver operation Feb 14
 —Transmitter Feb 14

SERVICE AIDS

Air filter cleaner,
 NYCO Product PR Nov 64
 Bench assembly station,
 Henry Mann PR Jun 66
 Connector potting and junction-
 molding compound, EPD
 TC-447 PR Jul 57
 Dolly, mechanically-powered,
 Yeats Appliance PR Dec 70
 Electrical contact lubricant,
 Trans Atlantic PR Nov 64
 Electronic equipment cleaner,
 M. P. Odell PR Dec 71
 Equipment cart, Technibilt .. PR Nov 68
 Inventory system, APSCO
 Fill n' File PR Aug 58
 Record cleaning and maintenance
 kit, Elpa Marketing
 Industries PR Mar 68
 Screw checker, Ruelle Bros. .. PR Feb 59
 Shrinkable tubing reducer,
 Hi-Shear PR Jan 62
 Solder, 5-core, Multicore PR Sep 60
 Soldering Flux, liquid,
 Multicore PR Jan 61
 Solders, solid bar, Multicore .. PR Jan 61
 Spray cleaner and degreaser,
 Injectorall PR Nov 66
 Storage unit, "Rollaway",
 Bay Products PR Dec 69
 Tape head cleaner,
 GC Electronics PR Mar 68
 Tape head cleaner, Chemtronics
 Model THC-6 PR Aug 57
 Wire tie, Richlok Twist-Lok PR-Oct 70

SERVICE CONTRACTS

RCA reduces color service
 contracts ES Mar 4
 Sustain high-volume business
 —Customer relations and
 scheduling service calls Nov 14
 —Parts availability Nov 12
 —Training and incentives Nov 12

SIGNAL GENERATORS

- B & K Model 415 sweep/marker Nov 54
- Knight-Kit Model KG-644, solid-state TER Aug 44
- Radio Research Model 61 PR Mar 71

SOLID-STATE CIRCUITS AND COMPONENTS

- All-IC color portable TV, Japan develops ES Jun 4
- AM receiver in a single IC, Amperex ES Sep 4
- Diodes, testing TS Feb 56
- FET's
 - Classification of Dec 22
 - Operation of Dec 20
 - Types of Dec 21
- IC VHF tuner, Oak Electronics ES May 7
- IC's marketing speeded up by Motorola ES Apr 8
- IC's, new method may lead to cheaper ES Oct 6

- Interpreting voltages in solid-state circuits
 - Base circuit, short in Apr 18
 - Base-to-emitter bias, loss of Apr 13
 - Base voltage, wrong Apr 12
 - Capacitors, open Apr 20
 - Capacitors, shorted Apr 21
 - Emitter-to-collector voltage, loss of Apr 14
 - IF coils, defective Apr 20
 - Lead open inside transistor Apr 14
 - Open circuits, review of Apr 16
 - Transistor, leaky Apr 18

- Printed circuit-board kit, Injectorall PR Feb 58
- Test probe, Dynascan PR Jan 61
- Transformers, power, Essex Controls Div., Stancor PR Feb 58
- Transformers for use with, Essex Stancor Pico Series PR Sep 62

STEREO

- FM multiplex in auto radio
 - Bendix system Dec 44
 - Bias pots, trouble in Dec 48
 - Bypass capacitors, trouble in Dec 48
 - Circuit analysis of stages Nov 21
 - Delco system Dec 44
 - Functional analysis, block diagram Nov 18
 - Motorola system Dec 44
 - Multiplex PCB's, cracked Nov 16
 - Multiplex signal, the Dec 49
 - Operation, basic Dec 44
 - Output transistors, trouble in Dec 48
 - Stereo-indicator lamp circuits Nov 24
 - Transformer wires loose Dec 48
 - Troubleshooting Dec 46
 - Tuners, trouble in "sealed" Dec 49

- FM stereo servicing
 - Alignment Feb 46
 - Balance check Jan 48
 - Cartridge output voltage, checking of Mar 30
 - Crosstalk Jan 50
 - Distortion, harmonic Jan 50
 - Distortion, intermodulation Jan 53
 - Distortion measurements Feb 38
 - Distortion, system intermodulation Feb 44
 - Frequency response, measurement of Jan 46
 - Frequency response, test of Mar 31
 - Hum interference, sources of Jan 45
 - Hum tests Mar 31

- Localization of trouble Feb 41
- Needle pressure, measurement of Mar 30
- Push-pull stages, AC balance in Jan 46
- Push-pull stages, DC balance in Jan 44
- Stylus angle, verification of Mar 33
- Stylus tip, observation of Mar 34
- Tracking distortion, measurement of Mar 32
- Turntable speed, measurement of Mar 34

TAPE RECORDERS

- Cassette-tape splicing kit, Robins PR Dec 69
- Operation, measurements and troubleshooting Jul 39
- Brake troubleshooting Jul 46
- Belt-drive troubleshooting Jul 43
- Design Jul 39
- Flywheel drive Jul 43
- Head defects and symptoms Jul 42
- Lubrication Jul 47
- Speed measurements Jul 41
- Torque measurements Jul 40
- Portable VTR uses 1/4-inch tape, Roberts ES Sep 6

TEST EQUIPMENT (General)

- Availability guide
 - Color-bar generators Mar 44
 - CRT testers Mar 46
 - FET meters Mar 48
 - Field-strength meters Mar 50
 - Marker generators Mar 52
 - Oscilloscopes Mar 52
 - RF signal generators Mar 54
 - Semiconductor testers Mar 56
 - Solid-state equipment analysts Mar 58
 - Television analyst Mar 59
 - Vectorscopes Mar 59
 - VTVM's Mar 59
- Decade amplifier, Syntex Model SDA-100 TER Aug 44
- Digital measuring system, Hickok Model DMS 3200 NTE Jun 40
- Diode curve tracer, Measurement Control Devices Model CT-501 PR Mar 69
- Manufacturers, list of Mar 61
- Power supplies, regulated solid-state, RCA Models WP-700A and WP-702A TER Jul 36
- Resistance substitution unit, Phipps & Bird Model 236 TER Jul 35
- Torque-measuring spring scale LE Dec 8

THEORY (General)

- Current flow LE Apr 7
- Current-electron flow LE Jun 10
- Polarity LE Aug 8
- TV waveforms
 - Exponential characteristics Aug 36
 - Pulse or square wave, rise time Aug 38
 - Sine-wave characteristics Aug 30
 - Square-wave and pulse characteristics Aug 34
 - Vectorgram analysis Aug 40

TOOLS

- Alignment tool set, JW Electronics Kit PA68 PR Jun 65
- Clamps, test, Trico Fuse PR Jan 62
- Desoldering/soldering iron, Thermal Industrial Products PR Jan 61

- Desoldering tool, American Beauty No. 495 PR May 56
- Kits, Vaco PR Jan 62
- Nut and stud kit, captive, Precision Metal Pressert Design Kit PR Sep 58
- Parallel-wire splitter, P. K. Neuses Model N-2500 PR Oct 71
- Ratchet kit, midget, Chapman No. 4320 PR Oct 72
- Screw drivers, cushion-grip Vaco PR Aug 58
- Screw extractor, Vaco Kit No. 70007 PR Jul 57
- Solder gun, solid-state, Ungar Model No. 6760 PR Oct 69
- Soldering iron, Wall Manufacturing Model IDL PR Sep 61

TRAINING

- RCA pilot electronic course for hard-core unemployed ES Sep 4
- Seasonal farm workers to be trained as TV technicians ES Nov 6

TRANSISTOR TV, SERVICING

- AC pulse voltages, comparison of May 35
- Class B or C, circuits operating Jul 32
- Collector junctions, open or shorted May 38
- Control-action test May 39
- DC current values, of comparison May 34
- DC voltage distribution May 37
- DC voltage measurements May 36
- DC current values, comparison of May 34
- Feedback loops, circuits with Jul 31
- Resistance measurement difficulties May 36
- Scope tests Jul 32
- Short-circuits, accidental May 40
- Substitution, notes on Jul 32
- Test-equipment requirements May 40
- Vacuum and transistor similarities Jul 30
- Vacuum tube and transistor differences Jul 30

TRANSISTOR TESTERS

- Electronic Measurements (EMC) Model 215 NTE Jun 42
- In-circuit
 - Application, examples of Mar 26
 - Defects, checking for Mar 24
 - Leads, connecting Mar 22
 - Leakage Mar 24
 - Operation Mar 22
 - Other tips Mar 28
 - Parameters Mar 22
- In-circuit, Leader Model LTC-901 TER Nov 30
- In- or out-of-circuit, Sencore Model TF17 TER Oct 46
- Model DT-100, Texscan NTE Jun 42
- Portable, Holland Model TT285 TER Aug 44
- Sencore Model TF 151 NTE Mar 66
- Test probe, Dynascan PR Jan 61

TUBES

- RCA 6LQ6/6JE6 interchangeability TS Sep 56
- RCA 6LQ6/6JE6C replacement LE Feb 8
- Replacement, 1619 tube LE May 8
- Substitution supplement Jan a

..... Mar 63
 Apr 41
 Nov 51

TUBE TESTERS

Electronic Measurements
 (EMC) Model 215 NTE Jun 42
 Seco Model 88A TER Jul 35
 Solid-state, Sylvania TER Dec 30

TUNERS, TV

IC VHF, Oak Electronics .. ES May 7
 Dirty TS May 51
 FCC calls for comparable UHF
 and VHF tuning ES Apr 8
 VHF and UHF tuning, NAB
 wants comparable ES Aug 4

TURNTABLE

Brushless DC Motor,
 Panasonic ES Aug 6

VECTORSOPES

Application and interpretation of
 patterns
 —Information in display Jul 19
 —Starburst Jul 18
 —Variations Jul 20
 —Various types Jul 19
 Mercury Electronics Model
 3000 PR Mar 70

VERTICAL SWEEP

Color TV setup May 16
 Foldover, RCA KCS140A TS Jan 57
 Height and width excessive Apr 22
 Height and width reduced Apr 22
 Height excessive Apr 22
 Insufficient, compression at top,
 Magnavox T908 TS Apr 53
 Insufficient, Sears Silvertone
 528.51800 TS Jan 58
 Linearity, poor
 —Bypass capacitors, defective Jul 27
 —Coupling capacitors, defective Jul 28
 —Height and linearity controls,
 interaction of Jul 25
 —Overloading, distortion due to Jul 24
 —Peaking pulse Jul 26
 —Resistor defects Jul 28
 —Transformer characteristics,
 waveshaping by Jul 27
 —Waveform distortion and
 correction Jul 22
 —Waveshaping circuit action Jul 23
 RCA CTC40 chassis in Jan 38

VERTICAL SYNC

Intermittent, Emerson
 120758A TS May 50
 Missing, RCA CTC11A, 11,
 10, 9, 7 LE Jan 9
 Simplified explanation of
 —Improper input to the
 separator Sep 12
 —Oscillator-caused problems Sep 16
 —Separation Sep 11
 —Separator output Sep 14
 —Signal, the Sep 10
 Weak, isolating indirect causes of
 —Common causes Nov 37
 —Technique Nov 36

VOM'S

FET VOM, miniature,
 Triplett TER Dec 30
 Portable Guardohm, Hirst
 Associates PR Mar 70
 RCA Model WV-500A Volt-
 Ohmyst NTE Apr 43

WARRANTIES

Changes in programs
 —Admiral ES Dec 4
 —Hitachi ES Dec 4
 —Philco-Ford ES Dec 4
 —Radio Shack ES Dec 4
 Hitachi provides 5-year warranty
 of solid-state components ES Nov 4
 Question and answer form,
 Sylvania ES Aug 6
 Report, special
 —Evaluation of service
 agencies, manufacturers' Sep 30
 —Length of, TV Sep 26
 —Radio Sep 27
 —Reaction to programs Sep 28
 —Replacement parts supplied
 by Sep 28
 —Service performed by Sep 28
 Symphonix increases labor
 rates ES Apr 8

INDEX OF TITLES

A Look at RCA's Solid-State
 Color, Part 2 Jan 36
 A Look at RCA's Solid-State
 Color, Part 3 Feb 32
 A Look at RCA's Solid-State
 Color, Part 4 Mar 38
 A Look at Today's Stereo FM
 Auto Radio Dec 44
 Admiral's K10 Hybrid Color
 Chassis Apr 34
 Automatic Tint Control Comes to
 Color TV Oct 26
 Color TV Setup—The Professional
 Way, Part 1 May 14
 Color TV Setup—The Professional
 Way, Part 2 Jun 30
 Consumer Electronic Service
 Licensing . . . A Special
 Report Jul 10
 Consumer Electronic Servicing,
 1969—A Perspective Dec 24
 Dale's Service Bench—Auto Stereo
 Tape Units Jun 12
 Dale's Service Bench—Marine
 SSB Made Simple Oct 51
 Dale's Service Bench—Really
 Understanding TV
 Alignment Aug 12
 Dale's Service Bench—Triggered
 Scopes Simplified Sep 18
 Dale's Service Bench: Which Type
 of Scope—Recurrent or
 Triggered? Dec 36
 Dale's Service Bench—Why Vec-
 torscopes Are Popular Jul 18
 EIA Committee Gets NATESA
 Viewpoint About Problem
 Areas Dec 50
 FCC Bureau Chief Discusses TV
 Interference Aug 28
 Facts About Servicing Solid-State
 TV Jul 30
 Franchise Service System—Another
 Approach to Servicing Mar 10
 Horizontal Sync Simplified Oct 56
 Interference . . . A Neighborhood
 Project Aug 47
 Interpreting Voltages in
 Transistor Circuits Apr 12
 Isolating Indirect Causes of Weak
 Vertical Sync Nov 36
 Is Your Shop Ripe for Armed
 Robbery? Aug 22
 Manufacturer Owned and Operated
 Service Centers Apr 46
 Motorola's Memory Module
 Remote Control Feb 12

NARDA Convention Mar 8
 NATESA Convention Report Oct 42
 NEA Convention Report Sep 40
 New in Color TV for 1970 Dec 54
 National Associations of the
 Electronic Servicing
 Industry May 42
 New From Sylvania for '69 Feb 24
 New in Color for 1970 Dec 54
 Picture Symptom Quiz Apr 22
 Plain Talk About FET's, Part 1 Dec 20
 Poor Vertical Linearity Jul 22
 Practical Stereo FM Servicing,
 Part 3, Jan 44
 Practical Stereo FM Servicing,
 Part 4 Feb 38
 Practical Stereo FM Servicing,
 Part 5 Mar 30
 Profile of the Electronic Servicing
 Business Jun 44
 Reader Survey Questionnaire Jan 32
 Same Trouble . . . Another
 Chassis Aug 48
 Separating Management from the
 Bench—The First Step to
 Growth Jan 10
 Service Contracts Sustain High-
 Volume Business Nov 10
 Servicing Solid-State TV is
 Different May 34
 Single- and Double-Ended Audio in
 Auto Radio Oct 62
 Solving High-Voltage Regulator
 Problems Jun 56
 Source Guide to Imported Sets,
 1969 Feb 20
 Source Guide to Imports Nov 38
 Stereo FM Multiplex in Auto Radio
 —Theory of Operation Nov 16
 Survey of 1968 Cost of Doing
 Business Jun 50
 Sylvania's Color TV Slide
 Projection System Jan 22
 TV Antenna System or Receiver
 Defect? Jun 16
 Test Equipment Applications
 and Techniques Nov 54
 Test Equipment Available for TV
 Servicing Mar 44
 The In-Circuit Transistor Tester—
 A Time Saver Mar 22
 The Pricing Dilemma: Reaching for
 a Solution Dec 10
 Tips and Shortcuts for More
 Accurate Color TV Alignment,
 Part 1 Jul 50
 Tips and Shortcuts for More
 Accurate Color TV Alignment
 Part 2 Sep 44
 Toward A Better Understanding
 of TV Waveforms Aug 30
 Troubleshooting Color In The
 Home May 18
 Troubleshooting Color Video
 Amplifiers May 24
 Troubleshooting Direct-Coupled
 Audio in Auto Radio Nov 27
 Troubleshooting Solid-State AGC Apr 24
 Troubleshooting the Mechanics
 of Tape Recorders Jul 39
 Troubleshooting TV With the
 Scope Oct 10
 Tube Types Most Used in 1968 Aug 58
 Use AFT to Diagnose TV Antenna
 Systems Sep 32
 Vertical Sync Simplified Sep 10
 Warranties . . . A Special Report Sep 26
 Zeroing in on the Causes of
 "No High Voltage" Aug 16

How do you “install” confidence when you install an RCA color picture tube?



The surest way to compliment a customer is to agree with his opinion. This is pretty easy to do when it comes to deciding which brand of replacement color picture tube to install in his set.

Here both set owner and service technician agree—and by a wide margin—on RCA! And for one very good reason: RCA's reputation...for experience, quality, and proven performance...over the years. More years than anyone else in the business.

Place your confidence in the company that perfected the color TV system in use today. Introduced more technical innovations than any other company. Stays on top of the state-of-the-art not just in technology, but in tube sizes as well.

Whether it's an all-new RCA HI-LITE or the popular priced quality rebuilt RCA Colorama—when you recommend RCA—you'll not only flatter your customer, you'll also be protecting your own hard-earned service reputation. That's because RCA picture tubes are designed to protect the biggest reputation in the COLOR TV industry.

RCA Electronic Components, Harrison, N.J.

RCA

Circle 2 on literature card

THE SAFEST SETS YOU'LL EVER SERVICE HAVE LITTELFUSE CIRCUIT BREAKERS.



Standard Catalog Part No.	Hold Rating (Amps.)	Standard Catalog Part No.	Hold Rating (Amps.)
815.650	.490	8152.75	1.92
815.800	.600	815003	2.1
815001	.650	8153.25	2.2
8151.25	.930	815004	2.5
81501.5	1	81504.5	3
8151.75	1.2	815005	3.25
815002	1.4	815006	3.9
8152.25	1.5	815007	4.14
81502.5	1.65		

Littelfuse TV set circuit breakers are the safe, reliable, money saving short-circuit-problem-solvers . . . 17 available models—exact replacements—cover the entire range of domestic television sets.

Littelfuse circuit breakers are available from your distributor—singly or in bulk.

Super-simple in operation—the sensitive breaker flips open under current overloads protecting the circuitry. Reset by merely pressing the red reset plunger. A built-in "trip free" feature of Littelfuse breakers prevents forced closing when dangerous overload currents are present.

Nothing's more reliable than a Littelfuse circuit breaker. Thermal-responsive Littelfuse breakers are dual operated bi-metallic devices providing temperature compensation over a wide range of ambient temperature variation. Molded phenolic construction eliminates warping and distortion of the base, maintaining exact factory set calibrations. The unit is completely enclosed to protect critical moving parts from dirt and other foreign matter.

Any TV set you're likely to service will take Littelfuse circuit breakers.

They'll flip for safety.

You'll flip for satisfaction.

LITTELFUSE

DES PLAINES, ILLINOIS 60016

SUBSIDIARY OF TRACOR, INC.

Circle 3 on literature card

IL 80 1849 1270
WM. M. DAVIS
RADIO & TV SERVICE
118 RIVERSIDE AVE.
CANYON CITY, COLO. 81212