

PHILADELPHIA PA 19111
809 BERGEN ST
SAMUEL SACHS
ESS-2074 R 1A 577 4

November, 1976 □ 75 cents

Electronic Servicing®




MURIEL

REPAIRING "WIRELESS" CB RADIOS

GE And Philco Circuits

Upgrading MATV

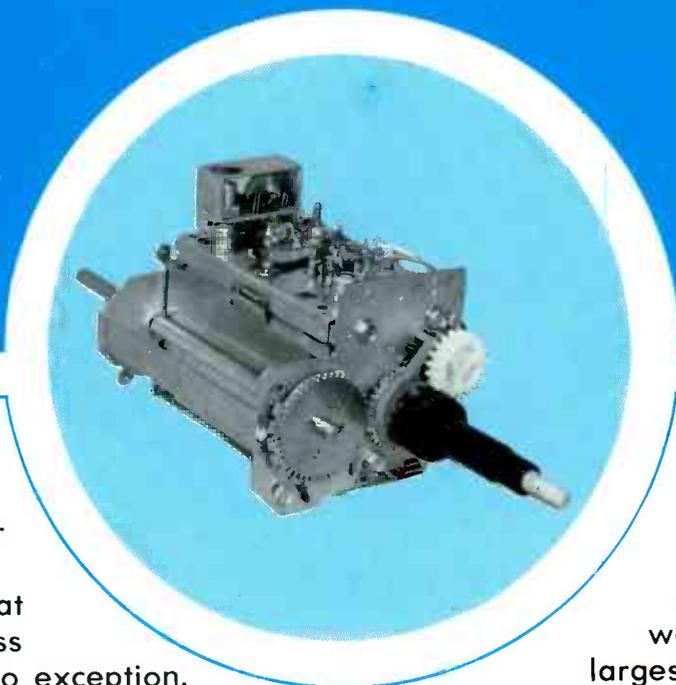THE BEST OF EVERYTHING HAS ITS PRICE ...EVEN TUNER SERVICE!



From the beginning, our goal has been to provide the best tuner service—never the cheapest. You get what you pay for in business and tuner service is no exception. The extra dollar you might pay at PTS is peanuts when you consider the added

reliability and the standards of excellence we apply to every job. Thousands of PTS customers must agree or we wouldn't be the world's largest tuner service company. When you are comparing tuner service companies, price alone doesn't tell the story.

SAME DAY SERVICE • ORIGINAL PARTS • ONE YEAR WARRANTY

WE REPAIR THEM ALL . . . COLOR, BLACK & WHITE, TUBE, TRANSISTOR OR VARACTOR . . . ANY MAKE OR MODEL.

VHF or UHF. . . \$10.95 UV-Comb. . . \$17.95

(MAJOR PARTS AND SHIPPING EXTRA — DEALER NET)



PTS ELECTRONICS, INC.

PRECISION TUNER SERVICE

General Headquarters: P.O. Box 272, Bloomington, IN 47401

Consult the white pages of your telephone directory for the address and number of your nearest PTS Service Center.

MIDWEST
Bloomington, IN
Indianapolis
Cleveland
Cincinnati
Columbus
Kansas City, KS
St. Louis
Davenport
Omaha

NORTHERN
Detroit
Grand Rapids
Milwaukee
Minneapolis

SOUTHWEST
Longview
Oklahoma City
Houston

MOUNTAIN
Denver
Salt Lake City
Phoenix

SOUTH
Jacksonville
Washington, DC
Charlotte
Birmingham
Memphis
Norfolk
New Orleans
Tampa
Nashville

NORTHEAST
Springfield, MA
Philadelphia
Pittsburgh
E. Paterson
Buffalo
Boston
Syracuse

PACIFIC
Sacramento
San Diego
Los Angeles
Portland
Seattle

CANADA
Montreal

For More Details Circle (1) on Reply Card

www.americanradiohistory.com

Electronic Servicing®

in this issue...

- 20 "Wireless" Radio Repairs—Servicing procedures for Royce modular CB radios, and the basics of Phase-Locked Loops (PLL) are explained—*Marvin J. Beasley, CET.*
- 30 Philco E21 Chassis...Circuits And Servicing, Part 2—Operation of the horizontal-sweep circuits are discussed, plus several case histories—*John Simrell.*
- 40 Servicing Electronic Organs, Part 6—If you repair old organs, you'll need to know how to tune them. Here are two methods of tuning by musical "fifths", starting from Middle "A"—*Norman H. Crowhurst.*
- 45 Upgrading MATV Systems—Many MATV systems badly need repairs and upgrading. Suggestions are given for direct-mail letters, signal-level tests, and typical repairs—*Bert Wolf.*
- 52 Servicing GE Modular Color TV, Part 4—Several stages of the 19YC-2 vertical-sweep circuit are direct coupled. Theory, waveforms, and voltages are included—*Gill Grieshaber, CET.*

ABOUT THE COVER

Don Clayton was too busy to pose for the photographer, as he worked in Westcon's, a well-equipped CB service facility in Kansas City. Picture is by Marvin Beasley.

DEPARTMENTS

Electronic Scanner 4	Product Report 64
Symcure 8	Book Review 65
Troubleshooting Tips 11	Photofact 67
Reader's Exchange 12	Advertiser's Index 68

Second class postage paid at Shawnee Mission, Kansas and additional mailing offices. Published monthly at 9221 Quivira Road, Overland Park, Kansas 66212 by Intertec Publishing Corp., 9221 Quivira Road, Overland Park, Kansas 66212. Send Form 3579 to 9221 Quivira Road, P.O. Box 12901, Overland Park, Kansas 66212.

© Copyright, 1976, Howard W. Sams & Co., Inc. All rights reserved. Material may not be reproduced or photocopied in any form without written permission of publisher.

**MORE
DEALERS
THAN EVER
BEFORE
HAVE US
WHERE THEY
WANT US!**

THE NEWEST PTS SERVICE CENTERS

CHICAGO, IL 60630

4477 1/2 N. Elston
312-725-2314

Les Bertolini, Manager

OMAHA, NB 68132

5008 Dodge Street
402-558-1800

Donald Rausch, Manager

GRAND RAPIDS, MI 49501

1134 Walker Northwest
P.O. 1435

616-454-2754

Dale Johnson, Manager

NASHVILLE, TN 37214

2426 A Lebanon Rd.
615-885-0688

Steve Lewis, Manager

SYRACUSE, NY 13204

418 Solar St.
315-475-2330

Melvin E. Burns, Manager

DAVENPORT, IA 52805

2024 E. River Dr., P.O. 187
319-323-3975

Keith Pyatt, Manager

Now More Than 40 Locations
Offer Complete Tuner Service

VHF or UHF...\$10.95

UV Comb...\$17.95



PTS ELECTRONICS, INC.

PRECISION TUNER SERVICE

For More Details Circle (30) on Reply Card

MEET OUR family of GRABBERS



MODEL 4233 MICRO GRABBER
Tests high density packaging



MODEL 3925 MINI GRABBER
Tests conventional packaging



MODEL 4011 THREADED GRABBER
Accepts 6-32 threaded leads



MODELS 3780 - 3789 GRABBER LEADS
10 choices of connectors other end

Our Grabber family is five years old now, and we're adding new members to keep pace with the complexities of state-of-the-art electronic packaging. Grabber is our name for a series of test clips designed to simplify testing of electronic packages from conventional components to maximum density DIP's. They're rugged, dependable, versatile, and very easy to use. Write for our catalog and get the complete story on the whole family of Grabbers. Find out why they are your best solution to your electronic testing problems.

**AVAILABLE THROUGH YOUR
FAVORITE ELECTRONIC
PARTS DISTRIBUTOR**

MODEL 4225 MAXI GRABBER
Tests high rise packaging

All Grabbers shown actual size

ITT POMONA ELECTRONICS

1500 East Ninth St., Pomona, Calif. 91766
Telephone (714) 623-3463, TWX: 910-581-3822



For More Details Circle (31) on Reply Card

Electronic Servicing

Editorial, advertising and circulation correspondence should be addressed to: 9221 Quivira Road, P.O. Box 12901, Overland Park, Kansas 66212 (a suburb of Kansas City, Missouri). (913) 888-4664

EDITORIAL

RONALD N. MERRELL, Director

CARL H. BABCOKE, Editor

SHARON ELWOOD, Editorial Assistant

DUDLEY ROSE, Graphic Designer

EDITORIAL ADVISORY BOARD

LES NELSON, Chairman
Howard W. Sams & Co., Indianapolis

JOE A. GROVES, Technical Consultant
Howard W. Sams & Co., Indianapolis

CIRCULATION

GREG GARRISON, Director

EVELYN ROGERS, Manager

ADVERTISING SALES

Overland Park, Kansas 66212
(a suburb of Kansas City, Missouri)
Tele: (913) 888-4664

MIKE KREITER, Director

GLORIA PARMENTER, Production

REGIONAL ADVERTISING SALES OFFICES

Indianapolis, Indiana 46280

ROY HENRY
2469 E. 98th St.
Tele: (317) 846-7026

Greenlawn, New York 11740

CHUCK HORNER
P.O. Box 175
Tele: (516) 757-7863

Mountain View, California 94043

DENNIS TRIOLA
2680 Bayshore Frontage Road, Room 102
Tele: (415) 961-0378

London W.C. 2, England

JOHN ASHCRAFT & CO.
12 Bear Street
Leicester Square
Tele: 930-0525

Badhoevedorp, Holland

John Ashcraft & Co.,
John J. Lucassen, Mgr.
Sloterweg 303
Tele: 2968-6226

Tokyo, Japan

INTERNATIONAL MEDIA
REPRESENTATIVES LTD.
1, Shiba-Kotohiracho, Minatoku
Tele: 502-0656



Member, American Business Press
Member, Audit Bureau of Circulations

ELECTRONIC SERVICING (with which is combined PF Reporter) is published monthly by Intertec Publishing Corp., 9221 Quivira Road, Overland Park, KS 66212.

ELECTRONIC SERVICING is edited for technicians who repair home-entertainment electronic equipment (such as TV, radio, tape, stereo, and record player), and for industrial technicians who repair defective production-line merchandise, test equipment, or industrial controls in factories.

Subscription Prices: 1 year—\$6.00, 2 years—\$10.00, 3 years—\$13.00, in the U.S.A. and its possessions. All other foreign countries: 1 year—\$7.00, 2 years—\$12.00, 3 years—\$16.00. Single copy 75 cents; back copies \$1. Adjustment necessitated by subscription termination to single copy rate. Allow 4-6 weeks delivery for change of address. Allow 2-3 weeks for new subscriptions.



Robert E. Hertel, Publisher

INTERTEC PUBLISHING CORP.
Subsidiary of HOWARD W. SAMS & CO., INC.



EPC
Electronic
Parts

EPC129
500P
50VDC
capacitor
SUGG. PRICE \$1.19

switch

Mallobin[®]
Merchandise Cabinets

Rechargeable
Batteries

Duracell[®] Batteries

Resistors

Capacitors

Controls and Switches

Duraface[®]
and Fliptape[®] Cassettes

Sonalert[™] Audible Signals

PTC Semiconductors

Mallory-Richco Fastening Devices

**With a line like this, no wonder
your Mallory distributor is a yes man.**

He almost never has to say no. Which adds up to a lot of single-source buying convenience for you. Give your Mallory distributor a call. You'll like what you hear. You'll like what he delivers.



MALLORY DISTRIBUTOR PRODUCTS COMPANY

a division of P. R. MALLORY & CO. INC.
Box 1284, Indianapolis, Indiana 46206; Telephone: 317-856-3731

© Registered trademark of P. R. Mallory & Co. Inc.

electronic scanner

news of the industry

About 50% of the 40-channel CB radios have failed the FCC tests for chassis radiation. A specially-designed test system measures the frequency error and power output of all 40 channels, with results recorded by a printer. Next, a test for over-modulation is made, then the chassis-radiation testing is done outdoors, followed by visual inspections to make sure the sample is not a "lab queen" which has been doctored to pass the strict specifications.

Frank Moch, Executive Director of NATESA, writes that our summary of his beliefs about state-versus-city licensing of TV shops was not quite correct (see page 6 of September ELECTRONIC SERVICING). Frank does not think either kind of licensing is needed, but state licensing would be preferable to Chicago licensing. He writes, "The days of incompetent tube jockeys...are gone. They can't cope with solid state, modules, and unitized chassis." "Our study reveals that 80% of all (Chicago) complaints are against about six well-known sharpshooters. The answer is for law-enforcement agencies to eradicate these offenders." "Continuous maligning of ethical and professional servicers is doing nothing to assure availability of service tomorrow. It will increase service costs, as in the medical profession faced with many get-rich-quick malpractice suits, because abuse has to have a price."

Sanyo has purchased for a reported \$10 million the 57% of Warwick Electronics owned by Whirlpool. Sears retains a 25% interest. TV manufacturing will be continued by Sanyo Manufacturing Corporation, a subsidiary of Warwick.

If you think electronic magazines are too expensive, consider the "AMR Reporter" (an anti-union publication) which has a subscription rate of \$95 for 12 monthly issues!

Technicians in the Chicago area are mourning the death of George (Gus) Cook, one of the pioneers in electronic servicing. Also, **John B. (Mac) McCulloch** died in July. He was active in NATESA-Detroit for 20 years.

RCA Sales Corporation has sold three branches of the RCA Distributing Corporation, and is attempting to sell the remaining six. Facilities in Lenexa, Kansas; San Antonio, Texas; and Chicago, Illinois now operate under new management. Most of the former RCA employees and executives are being retained. Although the sales reduce the cash tied up in the branches, RCA says the main reason for the change is that independent distributors can do a better job in those areas.

A sales ban and a recall of all smoke detectors of the ionization type has been requested from the U.S. Nuclear Regulatory Commission by the Health Research Group, according to **Retailing Home Furnishings.** A small amount of the radioactive element americium is used in such detectors. Dr. Sidney Wolf, of HRG, maintains that the amount of radioactivity from the detectors has been found to cause cancer in animals, and that HRG believes the alternate photoelectric type of detector will be more reliable in the long run. In rebuttal, Richard Cunningham, an assistant director of the National Regulatory Commission, says the radiation

(Continued on page 6)

How to fit 119,000 parts in your desk drawer.



Our 1976 ECG™ Semiconductor Replacement Guide is the compact way to keep the parts you need right at your fingertips.

It's the most comprehensive book in the industry.

There are cross-references for over 119,000 part numbers including domestic and foreign entertainment, commercial and industrial types. Plus a brand new section on CB radio replacements.

An expanded technical data section gives you detailed specs on new transistors, ICs, rectifiers and high-voltage dividers in the ECG line.

You can get your copy where you get your parts—at your Sylvania distributor. It's almost as good as having your own key to his stockroom.

We're helping you make it.

GTE SYLVANIA

(Continued from page 4)

from such a smoke detector is less than from a color TV, and so the danger is negligible.


Oldsmobile Toronados for 1977 have an electronic spark-timing microprocessor. The "Microprocessor Sensing and Automatic Regulation" (MISAR) system is built around a Rockwell 10-bit custom microprocessor by the Delco-Remy division, reports **Electronic News**. Engine speed, crankshaft position, manifold vacuum, and engine coolant temperature are monitored, and MISAR determines the precise time the high voltage is applied to each spark plug. An improvement of fuel economy, and a reduction of emission are expected to result. Ford Motor Company plans for 1978 models a microprocessor control of engine and exhaust gas recirculation. Within two years, Chrysler Corporation expects to have microprocessor control of the new lean-burn engine, and eventually might have a total of three or four microprocessors in each car. General Motors is the only auto manufacturer making IC's, at this time.

A portable heart-defibrillator weighing only 8 pounds recently was demonstrated at a medical convention. The machines operate from internal batteries. It was estimated that as many as 200 heart-attack victims per day could be saved, if the defib machine became as readily available as a fire extinguisher.

Have you ever heard of the "Shakespeare College of Electronic Knowledge"? Well, perhaps it's not in a class with Harvard and Yale, but "Shakey U" operated for two days in September at Hilton Head Island, South Carolina. Fifty sales representatives of the Shakespeare Electronics and Fiberglass Division (CB and radio manufacturer) earned their "Bachelor of Antenna Arts" degree. As you have guessed, the theme was borrowed from colleges and universities, and the courses covered electronic theory, product engineering and sales management.



Tuner Service Corporation

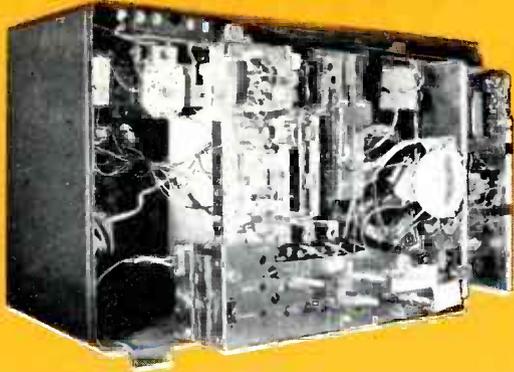

STILL ONLY
\$995
 U.S.A. ONLY

Major Parts and Shipping Charged at Cost

One Year Guarantee

MODULE REPAIRS


TSC has been repairing private brand TV modules for over 2 years.

Expanded facilities now include modules for

- RCA
- GE
- ZENITH
- W. T. GRANT
- J. C. PENNEY
- WESTERN AUTO
- GAMBLES

as well as Zenith IF subchassis.

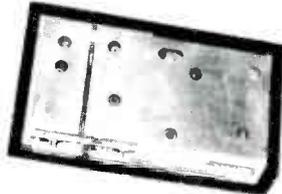For free Price List and complete information write or phone; TSC HEADQUARTERS, BLOOMINGTON, IND. or any of the TSC locations listed below.



PROVIDES YOU WITH A COMPLETE SERVICE FOR ALL YOUR TELEVISION TUNER REQUIREMENTS.

REPAIR

VHF OR UHF ANY TYPE (U.S.A. ONLY) \$ 9.95
 UHF/VHF COMBINATION (U.S.A. ONLY) \$15.00

MAJOR PARTS AND SHIPPING CHARGED AT COST.

- Fast, efficient service at our conveniently located Service Centers.
- All tuners are ultrasonically cleaned, repaired, realigned, and air tested.

REPLACE

- UNIVERSAL REPLACEMENT TUNER \$12.95 (U.S.A. ONLY)
- This price buys you a complete new tuner built specifically by Sarkes Tarzian Inc. for this purpose.
- All shafts have a maximum length of 10½" which can be cut to 1½".
- Specify heater type parallel and series 450 mA. or 600 mA.

CUSTOMIZE

- Customized tuners are available at a cost of only \$15.95. With trade-in \$13.95. (U.S.A. ONLY)
- Send in your original tuner for comparison purposes to any of the Centers listed below.

SAME DAY SERVICE — ONLY ORIGINAL FACTORY PARTS USED




HEADQUARTERS	BLOOMINGTON, INDIANA 47401	537 South Walnut Street	Tel. 812-334-0411
ARIZONA	TUCSON, ARIZONA 85713	1528 S. 6th Ave.	Tel. 602-791-9243
CALIFORNIA	NORTH HOLLYWOOD, CALIF. 91601	10654 Magnolia Boulevard	Tel. 213-769-2720
	SAN MATEO, CALIF. 94402	600 S. Amphlett Blvd.	Tel. 415-348-3292
	MODESTO, CALIF. 95351	123 Phoenix Avenue	Tel. 209-521-8051
FLORIDA	TAMPA, FLORIDA 33606	1505 Cypress Street	Tel. 813-253-0324
	FT. LAUDERDALE, FLORIDA 33315	104 S.W. 23rd St., Bay 16	Tel. 305-524-0914
GEORGIA	ATLANTA, GA. 30310	646 Evans St. S.W.	Tel. 404-758-2232
ILLINOIS	URBANA, ILLINOIS 61801	908 E. Main Street	Tel. 217-384-2052
	DOLTON, ILL. 60419	1507-09 E. 142nd St	Tel. 312-841-4444
	SKOKIE, ILLINOIS 60076	5110 West Brown Street	Tel. 312-675-0230
INDIANA	INDIANAPOLIS, INDIANA 46204	112 West St. Clair Street	Tel. 317-632-3493
KENTUCKY	LOUISVILLE, KENTUCKY 40205	2244 Taylorsville Road	Tel. 502-452-1191
LOUISIANA	SHREVEPORT, LOUISIANA 71104	3025 Highland Avenue	Tel. 504-393-0999
MARYLAND	BALTIMORE, MARYLAND 21215	5505 Reisterstown Rd., Box 2624	Tel. 301-358-1186
MASSACHUSETTS	SPRINGFIELD, MASS. 01108	405 Dickinson St.	Tel. 413-788-8206
MISSOURI	ST. LOUIS, MISSOURI 63132	9577 Page Avenue	Tel. 314-429-0633
NEVADA	LAS VEGAS, NEVADA 89102	1412 Western Avenue	Tel. 702-384-4235
NEW JERSEY	TRENTON, NEW JERSEY 08638	1139 Pennsylvania Ave	Tel. 809-393-0999
	JERSEY CITY, NEW JERSEY 07307	547-49 Tonnesse Ave. Hwy. 1 & 9	Tel. 201-792-3730
NEW YORK	ROCHESTER, NEW YORK 14615	37 Pullman Ave.	Tel. 716-647-9180
N. CAROLINA	GREENSBORO, N.C. 27405	2914 E. Market Street	Tel. 919-273-6276
OHIO	CINCINNATI, OHIO 45216	7450 Vine Street	Tel. 513-821-5080
	CLEVELAND, OHIO 44109	4525 Pearl Road	Tel. 216-741-2314
OREGON	PORTLAND, OREGON 97210	1732 N.W. 25th Ave. P.O. Box 10141	Tel. 503-222-9059
PENNSYLVANIA	PITTSBURGH, PA. 15209	515 Grant Avenue	Tel. 412-821-4004
TENNESSEE	MEMPHIS, TENNESSEE 38111	3158 Barron Avenue	Tel. 901-458-2355
TEXAS	DALLAS, TEXAS 75218	11540 Garland Road	Tel. 214-327-8413
VIRGINIA	NORFOLK, VIRGINIA 23513	3295 Santos Street	Tel. 804-855-2518
CANADA	ST. LAURENT, QUEBEC H4N-2L7	305 Decarie Boulevard	Tel. 514-748-8803
	CALGARY, ALBERTA T2H-1Y3	P.O. Box 5823, Stn. "A"	Tel. 403-243-0971

WATCH US GROW


For More Details Circle (33) on Reply Card

Chassis—Zenith 25FC45
PHOTOFACT—1466-3

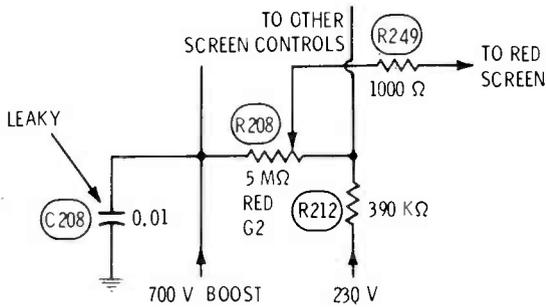


Symptom—Low brightness (sometimes color smear on b-w)
Cure—Check C208, and replace it if leaky

Chassis—Zenith 25FC45
PHOTOFACT—1466-3

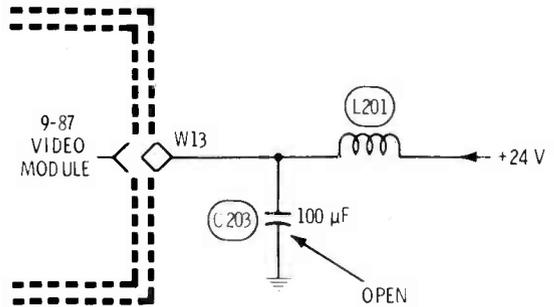


Symptom—Loss of horizontal sync
Cure—Check filter C203, and replace it if open

Chassis—Zenith 13GC10
PHOTOFACT—1540-2

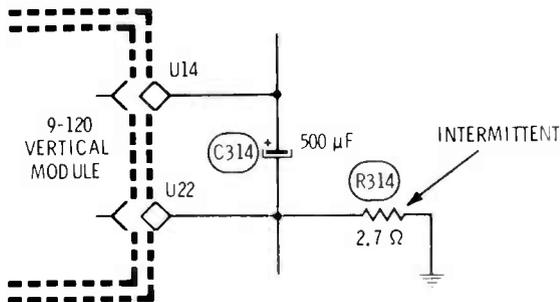


Symptom—Height varies at top and bottom
Cure—Check R314, and replace it if intermittent

Chassis—Zenith 19GC45
PHOTOFACT—1546-2

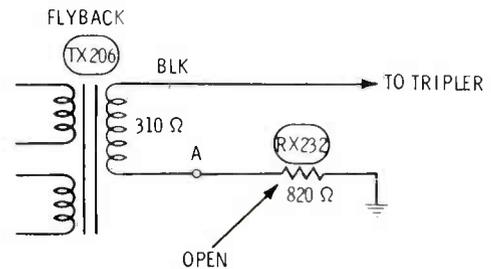


Symptom—Low HV (perhaps 12 KV)
Cure—Check RX232, and replace it if open or increased

Chassis—Zenith 23GC45
PHOTOFACT—1558-2

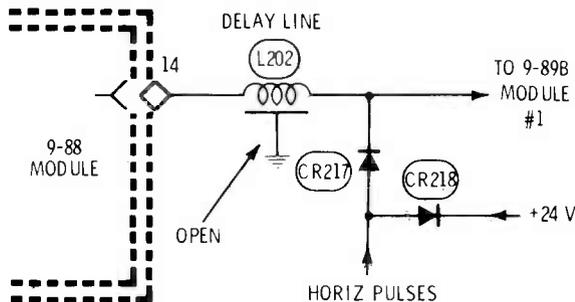

Symptom—No control of brightness; retrace lines; foldover on left
Cure—Check the delay line, L202, and replace it if open

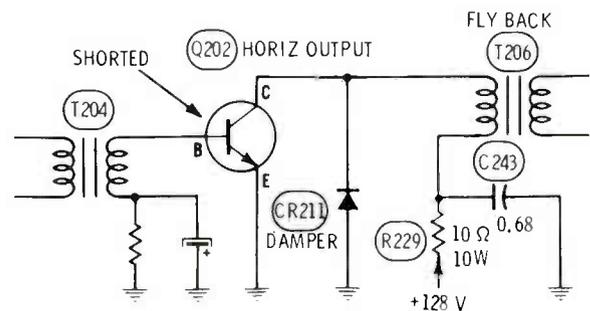Chassis—Zenith 25FC45 (others, also)
PHOTOFACT—1453-3



Symptom—Loud hum, no HV
Cure—Check horizontal-output transistor, and replace it if shorted

Electronic Servicing... ON-TARGET cards

YOUR DIRECT "HOTLINE" TO MANUFACTURERS/SUPPLIERS

•FILL IN THE CARD •PRINT CLEARLY •DROP IT IN THE MAIL

Don't Miss
This
Special Offer!



PTS ELECTRONICS, INC.

MODULE REBUILDING

PTS invites you to save **\$1** on your first module repair or exchange order. (Our prices already are lowest in the industry.) Send this card with your order.



FREE INFORMATION

Please send me information about PTS module rebuilding costs including list of all modules you can rebuild.

Name _____
Firm _____
Address _____
City _____ State _____ Zip _____

- 1 Year Warranty
- Same Day Service
- Quality Parts & Workmanship
- Tested, Temperature Cycled, Retested and Air Tested
- We rebuild, buy and exchange Dud Modules

Subscription Offer

Enter my subscription to **ELECTRONIC SERVICING**

- 3 years \$13.00 2 Years \$10.00 1 Year \$6.00
 Bill Me Remittance Enclosed Extend Present Subscription

IMPORTANT! Please check your business classification.

Type of Business

Check One

- | | |
|---|--|
| A. <input type="checkbox"/> Independent Electronic Service Organization | F. <input type="checkbox"/> Wholesale, Jobber, Distributor |
| B. <input type="checkbox"/> Retailer with Electronic Service Department | G. <input type="checkbox"/> Other (Specify) _____ |
| C. <input type="checkbox"/> Independent or Self-Employed Service Technician | Position |
| D. <input type="checkbox"/> Electronics, Radio, TV Manufacturer | H. <input type="checkbox"/> Owner, Manager |
| E. <input type="checkbox"/> Industrial Electronic Service | I. <input type="checkbox"/> Ser. Manager |
| | J. <input type="checkbox"/> Technician |
| | K. <input type="checkbox"/> Other |

Be sure you have checked one box in each column above!

Print plainly or write below:

Name _____
Firm _____
Firm Address _____
City _____ State _____ Zip _____

Did you receive this issue through Distributor Subscription

Electronic Servicing
SUBSCRIPTION
OFFER...

Use this handy card to subscribe or renew your subscription.

New Catalog!

Hot Off
The Press...
from PTS!

ORDER NOW!

Get Your Copy Now!



PTS ELECTRONICS, INC.

VHF-UHF-FM
1976-1977

Tuner Replacement Guide
and Parts Catalog No. 6

- 134 pages of vital information.
- Blow-ups of all tuners for easy part identification.
- Largest tuner replacement guide available anywhere.

Name _____ Title _____
Firm _____
Address _____
City _____ State _____ Zip _____



Please send me the New Tuner Parts Catalog. I understand the cost is \$2.

BUSINESS REPLY MAIL

No postage necessary if mailed in the United States

Postage Will Be Paid By

PTS Electronics, Inc.
Bloomington Module Center
P.O. Box 272
Bloomington, IN 47401

First Class
Permit No. 323
Bloomington, IN



**Don't Miss
This
Special Offer!**



PTS ELECTRONICS, INC.

PLACE
FIRST CLASS
POSTAGE
HERE

Electronic Servicing.

P.O. Box 12901
Overland Park, KS 66212

BUSINESS REPLY MAIL

No postage necessary if mailed in the United States

Postage Will Be Paid By

PTS Electronics, Inc.
P.O. Box 272
Bloomington, IN 47401

First Class
Permit No. 323
Bloomington, IN



New Catalog!

**Hot Off
The Press...
from PTS!**


ORDER NOW!

troubleshootingtips


Send in your helpful tips—we pay!

Blue picture; vertical-retrace lines, General Electric 16JA (Photofact 1335-2)

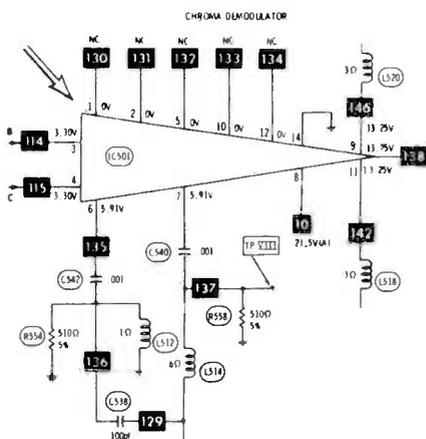The raster was a bright blue, with blue retrace lines. I checked the collector DC voltages of the three chroma/video output transistors (Q606, Q600, and Q604). The



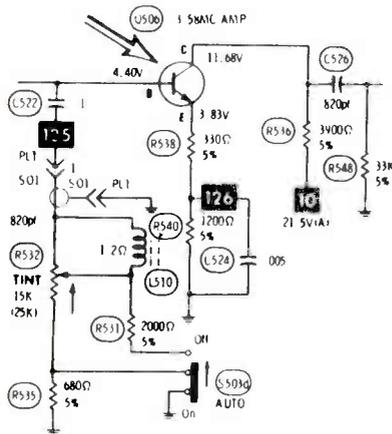blue output had near-normal voltage, but Q606 and Q604 measured the same as the supply voltage. This proved the two transistors were cutoff (that is, had insufficient forward bias).



Q606 and Q604 did not have enough positive voltage at their bases. So, because the bases were supplied by IC501, I replaced the IC. This restored normal voltages to the two transistors, allowing adjustment of good gray-scale tracking without retrace lines.

However, the color bars did not have enough red saturation. Some extensive testing uncovered these voltages at the 3.58-MHz amplifier, Q506:

collector was +21 volts
base was +5 volts
emitter was +2 volts

A forward bias of 3 volts, but without collector current, indicates an open transistor. I replaced Q506, adjusted the AFC, touched up the gray-scale screen color, and returned the set to the customer.

Ed Pena
Oaks, Pennsylvania

No horizontal locking Zenith 17EC45 (and others using 9-57 and 9-70 horizontal modules—Photofact 1377-3)

Visual examination of the horizontal module located a burned R808, which brings in horizontal pulses that are integrated into sawteeth for the horizontal phase detector. After removal, the 330-ohm R808 measured above 50K ohms. Installation of a new one gave good locking.

Since that first repair, I have found four more open or burned R808's. Evidently, a half-watt size is not enough; late production 9-90 modules have 1-watt resistors.

(Continued on page 17)

NEW 40 Channel CB Receiver Test Set

Reduces test time up to 40%

Improves accuracy, too. Has fully synthesized channels. Internally leveled. Self-calibrating. Single rotary knob for a full 40 channels. Continuous rotary attenuator calibrated in absolute microvolts and dBm. Full transmitted power absorption. Write or call today for complete details.

23 channel LogiMetrics models will be upgraded free of charge.



LogiMetrics

121-03 Dupont Street, Plainview, New York, 11803
(516) 681-4700/TWX 510-221-1833
RF Signal Generators, Frequency Synthesizers,
Traveling Wave Tube Amplifiers

For More Details Circle (20) on Reply Card

FAST

COMPLETE SERVICE ON ALL MAKES OF TV TUNERS

Maximum Time In Shop 24 Hrs.

(WE SHIP C.O.D.)
YOU PAY SHIPPING
\$9.95

(Warranty: One Full Year)



Black & White or Color

VHF or UHF

UV Combo's \$16.50

Price includes all labor and parts except Tubes, Diodes & Transistors. If combo tuner needs only one unit repaired, disassemble and ship only defective unit. Otherwise there will be a charge for a combo tuner. When sending tuners for repair, remove mounting brackets, knobs, indicator dials, remote fine tuning arrangements and remote control drive units.

WE UNCONDITIONALLY GUARANTEE All Tuners FOR ONE FULL YEAR




All tuners are serviced by EXPERTLY TRAINED TECHNICIANS with years of experience in this specialized field. All tuners are ALIGNED TO MANUFACTURER'S SPECIFICATION on crystal controlled equipment and air checked on monitor before shipping to assure that tuner is operating properly.

GEM CITY TUNER SERVICE

Box 6G Dabel Station
1621 Mardon Drive
Dayton, Ohio 45420

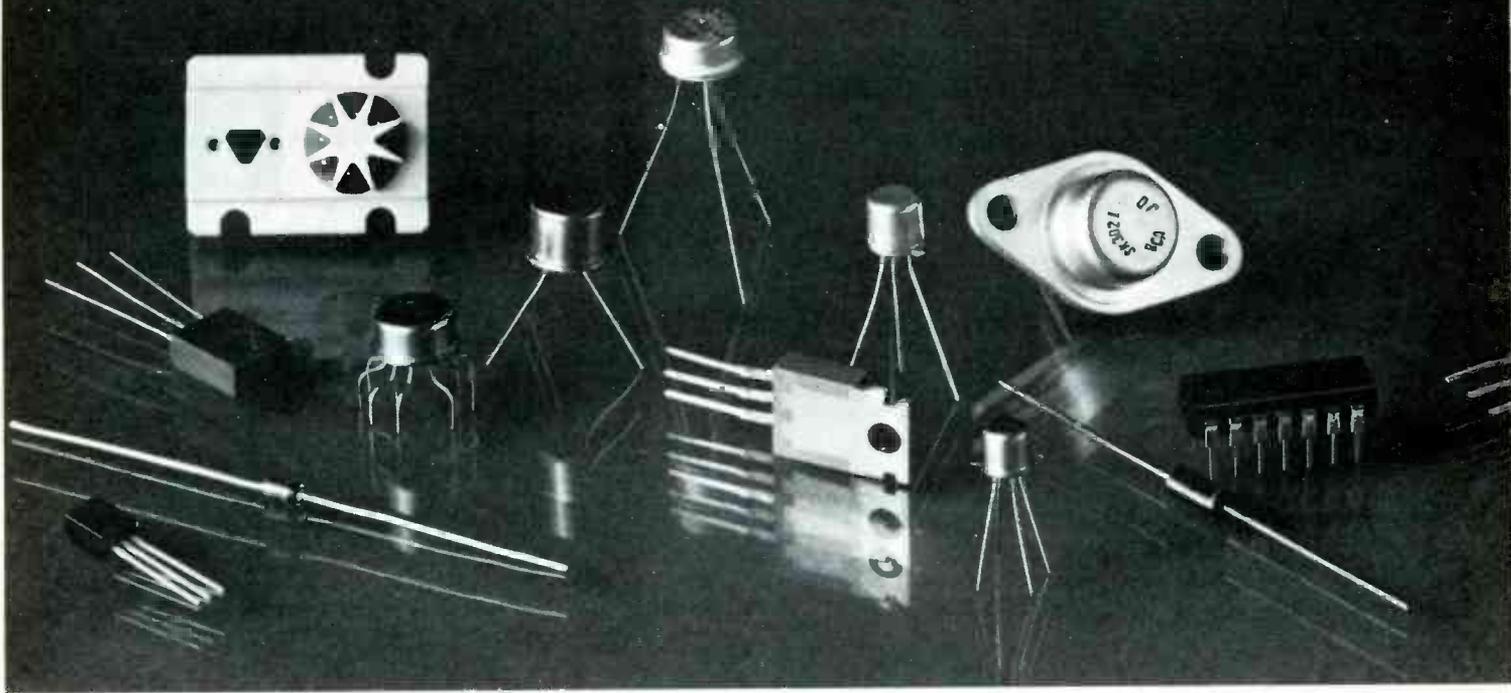Now you can stock only 300 semiconductors instead of 112,000.



reader's exchange

There is no charge for listing in *Reader's Exchange*, but we reserve the right to edit all copy. If you can help with a request, write direct to the reader, not to *Electronic Servicing*.

Needed: Operating/servicing literature, schematics, and tube charts for B&K Model 650 Dyna-Quick tube and transistor checker, 610 and TC-615 adapter panels. Will buy, or copy and return.

Tom's TV & Electronics
R. R. #1, Box 218A
Hortonville, Wisconsin 54944

For Sale: Bell and Howell color TV course, complete, sell all or parts; make offer.

Roman Watashi
2412 13th Ave. So.
Minneapolis, Minnesota 55404

Needed: 2EP4 picture tube for Philco TV, Model H2010.

Larry Auman TV
Route 1, Box 368
Dover, Ohio 44622

For Sale: Heath Model 10-18 oscilloscope with probes, perfect, \$75. Also, Leader Model LSG-11 RF signal generator, like new, \$35.

C. J. Porcari
630 N. 65th Way
Hollywood, Florida 33024

Needed: Schematic, parts list, and other service information for an old Crosley radio, Type 1121. Will buy, or copy and return.

Raymond Friend
236 W. Pearl St.
Butler, Pennsylvania 16001

Needed: 19-KHz transformer for Knight Model KG-765A stereo tuner. Original part #142-135L3, 273F6652. Will pay reasonable price for new or good used transformer.

Allan Siirila
P.O. Box 561
Belvidere, Illinois 61008

Needed: Schematic and/or service manual for Martel Model 40W AM-FM stereo receiver (made in Canada), or address of company. Also, need manual for Tektronix Model 316 scope.

Stony Point TV
Route 9W, Liberty Drive
Stony Point, New York 10980



With RCA's SK Series you need stock fewer different semiconductors than you'd have to with any other major brand. Because our 300 devices can replace 112,000. And they're all immediately available.

OEM Quality. You don't have to be concerned about quality with RCA SK's. They measure up to strict AQL Standards to protect you from time-wasting callbacks. Lets you make more calls. And more profits.

See your RCA Distributor for a copy of the new RCA SK Replacement Guide. Or send \$1.00 to RCA Distributor and Special Products Division, P.O. Box 85, Runnemede, N.J. 08078.

RCA SK Replacement Semiconductors

For More Details Circle (27) on Reply Card

Wanted: Schematic and service data for a Grunow Teledial cabinet type radio, chassis 10D. Manufactured in 1930's by General Household Utilities. Will buy, or copy and return.

Larry Frank
13701 Force Street
Houston, Texas 77015

Needed: Vertical-output transformer, #TO-0061, for a Muntz b-w TV combination, Model 3521W, chassis A5001. Part can be new or used, but good.

E. J. McCain
Town & Country TV Service
600 Cate Avenue
Jonesboro, Arkansas 72401

Needed: Source of 1 RPM, 60 Hz, 120-volt motors for various Japanese-made digital clock radios. One is marked "OMRON 1 RPM 60 Hz Japan". Motor capsule is similar to Telechron type, but much smaller.

Bernard Serota
2502 South Phillip St.
Philadelphia, 19148

For Sale: Sprague/Jud Williams Model A transistor curve tracer, good condition, \$75.

Casco/Maitland
2241 Gillis Court
Maitland, Florida 32751

Needed: Complete series of "programmed instruction" publications (1964-1966) by Tektronix, titled "Semi-conductors, Diodes, and Transistors". I have Volumes 1 & 2. Will pay shipping. Send price and titles of other volumes, or I will copy and return. Also, would like information on source of any "Programmed Instruction" course, manuals, or books on digital concepts, electronics, etc.

S. O. Sellers
1504 51st Street West
Birmingham, Alabama 35208

Needed: Hammond organ service manual and schematic for Model B, C, or D, circa 1940. 2A3 and 56 tubes used in power amp. (Will buy complete Hammond power amplifier, any condition.) Also, need Sams "Electronic Organs, Volume 1", #20188.

ATS Instrument Co.
P.O. Box 86
Farmington, Connecticut 06032

Needed: Schematic for Euphonics intrusion alarm, Model #SA-3A, manufactured by Euphonics Corporation, Guaynabo, Puerto Rico 00657. Will buy, or copy and return.

Gordon H. Williams
859 N.E. 121st St.
N. Miami, Florida 33161

(Continued on page 14)

Low cost tool for design and trouble-shooting

**Pocket Size
Slide-Switch
Resistance
Substitution Unit
still only \$58**

- Over 11 million step range
- 1% accuracy resistors
- Unique in convenient size
- Rugged construction



Small enough to take anywhere in your pocket, this aluminum-housed unit delivers a very broad range of resistance steps. Excellent for both development and repair work.

Half-watt 1% tolerance resistors give an accurate range from 1 to 11,111,110 ohms, in one-ohm steps. Has three binding posts, one to ground case.

Available now from stock. Catalog No. 7092-236. Cash savings available, see coupon. Write, or call (804) 264-2858. Phipps & Bird, Inc.

- Please send _____ Units @ \$58 each. (Check enclosed less 5% cash discount)
- Send _____ Units @ \$58 each C.O.D. (Phipps & Bird will pay C.O.D. charges)

Name _____
Firm _____
Address _____
City, State _____ Zip _____

Ask your dealer, or contact:



PHIPPS & BIRD, INC.

Manufacturers of Scientific Instruments

P.O. Box 27324 • Richmond, Virginia 23261 • Phone: 804/264-2858
For More Details Circle (21) on Reply Card

(Continued from page 13)

Needed: Pages one through six of the tube-chart book for Model 157 Accurate Instrument Company tube tester. Will pay postage, copy and return.

D. L. Konicki
4443 N. Greenview Avenue
Chicago, Illinois 60640

Wanted: Howard W. Sams book #24014 "Single Sideband: Theory & Practice." Quote price and condition.

Barnes TV & Radio Service
118 West Main Street
Camden, Tennessee 38320

Needed: Instruction book or service manual for Model 30-B Fleet Courier receivers. Will pay for copying, or will copy and return.

John Havery
Specialist, Electronics
Oregon Department of Education
942 Lancaster Drive, N.E.
Salem, Oregon 97310

Needed: Schematic or service manual for Bradford TV, Model 1004B30, W.T.G. #30-55988. Will buy, or copy and return.

William S. Reid
18506 Indiana
Detroit, Michigan 48221

(Continued on page 18)



Fix it Quick...

with an

Ungar® Cordless Quick-Charge Soldering Iron

- Cordless portability
- Quick 4-hour charge
- Holder automatically charges high performance NI-CD battery
- Rigid coaxial tip rotates to desired working position
- Easy-touch switch, tunnel light
- Quick heat-up

SPECIAL OFFER

Free Micro-Spade Element Tip

Present this coupon to your local participating Ungar electronic distributor and receive a FREE #195 Micro-Spade Element Tip worth \$1.99 with your purchase of a #200 QUICK-CHARGE CORDLESS SOLDERING STATION.

HURRY! Offer EXPIRES December 1, 1976.



Division of Eldon Ind., Inc. • Compton, CA 90220




For More Details Circle (22) on Reply Card

(Continued from page 11)

These defects remind us that **both** the sync pulses and a sawtooth sample from the horizontal-sweep circuit are necessary for proper operation of this type of phase detector.

George Persico
Thiells, New York

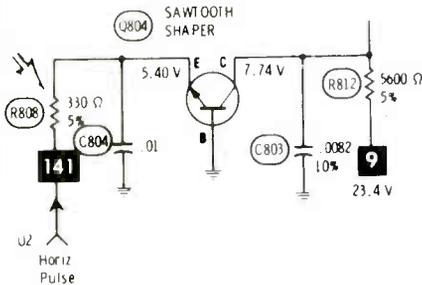

Editor's Note: This typical defect has been reported and published several times, but we are telling it again for any technicians who might have missed it before. Refer to page 30 of the August issue of **ELECTRONIC SERVICING** for another case history.

**Insensitive remote
Zenith Chassis 23DC14**
(Photofact 1306-3)

The complaint against the remote-control operation was that the hand unit had to be very near the TV, else it would not change channels. I pulled the remote amplifier, transducer, and hand unit for the shop.

While checking the DC voltages at the amplifier transistors, I found a high collector voltage for Q1, the first amplifier. Much additional testing proved nothing, until I disconnected the transducer. That reduced Q1's collector voltage to normal.

After I obtained a new transducer and connected it, the abnormal voltage was gone and the sensitivity of the remote was good.

The defective transducer measured about 20K ohms, and it should have checked open. Strangely enough, the bad one worked okay in a tube-equipped remote!

In my 43 years of servicing, I have replaced only one other transducer.

D. W. Alleeson
Los Angeles, California □

Money Generator

PAT. PEND.

\$299.95




**ATC-10
GENERAL TELEVISION
SERVICER**

- Extra wide range RF/IF attenuator for testing receiver sensitivity.
- **HATCHDOTS** - versatile composite pattern for dynamic & static convergence plus other checks.
- **COLOR BARS** pattern with 6th bar marked to make your job easier.
- **3.58 MONITOR** pattern for oscillator frequency checks with no need to short the AFPC test point.
- **RED RASTER** pattern for checking and adjusting purity at the flip of a switch.
- High level, 75 ohm output provided.
- ◆ 2 year factory warranty.
- ◆ 30 day money back guarantee.
- ◆ 2 volume owner's manual available separately - \$1.00.

Unique

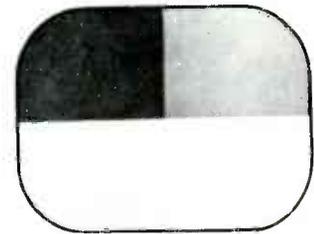One of the most useful, **UNIQUE** patterns of the ATC-10 is the **GRAY QUAD** pattern below. Use it for checking and adjusting gray scale tracking or for checking effects of video level upon horizontal sync. Use it to check for reversed yoke connections - vertical, horizontal or both. Use it to check low frequency video response. *It can save you time, trouble and money!* Write us.



American Technology Corporation

225 Main Street, Dept. 11A, Canon City, Colo. 81212

Credit card & COD phone orders accepted. Same day shipment. (303) 275-8991, ext. 1.

For More Details Circle (3) on Reply Card

DIGITAL MULTIMETERS

NLS proves NLS' DMMs have more capability at lower prices.

THE VOLKSMETER FAMILY LM SERIES

Features Include:

- Super Rugged - Ideal for field service use.
- Battery powered with batteries and charger unit included.
- Exclusive NLS fuseless protection in kΩ mode - up to 500 vdc or rms ac may be applied without damage.
- Overload indication.
- Automatic zeroing and polarity.
- Operating temperature - 0° to 45°C.
- Large 0.3" LED display.
- Small size: 1.9" H x 2.7" W x 4.0" D.
- Six optional shunts for current measurement - LM-3.5 includes three shunts in values of 10 mA, 100 mA and 1A.



MODEL	RANGES	DC ACCURACY	RESOLUTION	DIGITS	PRICE
LM-3	VDC & VAC	±1% Rdg	1 mV	3	\$125
LM-3.5	1V, 10V, 100V & 1000V	±0.5% Rdg	1 mV	3-1/2	\$147
LM-40	OHMS	±0.1% Rdg	1 μV	4	\$190
LM-4	1 kΩ, 10 kΩ, 100 kΩ, 1 MΩ & 10 MΩ	±0.03% Rdg	1 μV	4	\$227



Non-Linear Systems, Inc.



Originator of the digital voltmeter.

Box N, Del Mar, California 92014 Telephone (714) 755-1134

See your local distributor!
Distributor inquiries invited.

For More Details Circle (4) on Reply Card

**Tear
'n
Share**TM

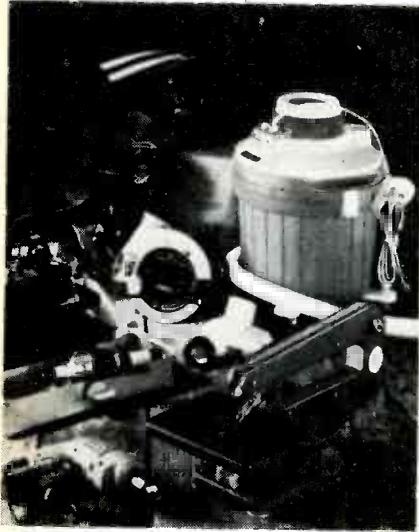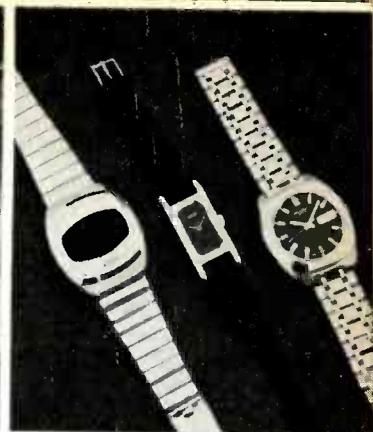

(Continued from page 14)

For Sale: B&K television analyser, Model 1075, and Dyna-Sweep circuit analyzer A107; best offers.

Max Stern
2011 Picton St.
Ocean, New Jersey 07712

Needed: One 4GZ5 tube.

Sam Yuppa
16191 Melody Lane
Huntington Beach, California 92649

Needed: Schematic or technical manual for Bell Boy personal pager, Bogen Model TR-54B.

Derek Watson
R.R. 3
Bridgewater,
Nova Scotia, Canada

Needed: A Satchel Carlson Model U800 color chassis, or any plug-ins for it.

Malcolm McCarty
4401 Wildwood Road
Dallas, Texas 75209

Needed: Service information on Mercury vacuum tube voltmeters, Model 1700C in particular.

R. S. Hamilton
4509 Richardson
Fort Worth, Texas 76119

Needed: Schematics and operating manuals for Century VTVM, Model VT-10; also probe, or schematic of probe. Also, need schematics and/or wiring diagrams for Eico VTVM, Model 232; and Supreme Instruments Model 542 multimeter.

Allen C. Fryou
3735 Fairmont Drive
New Orleans, Louisiana 70122

Needed: Operating and servicing literature or schematics for Solar capacitor analyzer Model CB-1-60. Will buy, or copy and return.

Tom Garz
R. R. #1, Box 218A
Hortonville, Wisconsin 54944

Needed: Service manual for a B&K Model 1450 scope. Will buy, or copy and return.

Dan L. McGrath
616 Paris Ct.
Columbia, Missouri 65201

For Sale: One Sencore CR143 picture-tube tester/rejuvenator, just overhauled and calibrated, with all manuals and test sockets, for \$30 or best offer.

Al Hawkes
U.S. Route 302
Westbrook, Maine 04092

Just Tear and Get your Share.


RCA's Super Prize Program is Back by Popular Demand! As before, just save your RCA entertainment receiving tube carton ends and color picture tube warranty serial number stickers* — to earn valuable awards:

- Lots of great merchandise premiums. Choose from a wide selection for yourself, your family, or your home.



- Money-saving discount certificates, good toward purchases of more RCA receiving and color picture tubes.

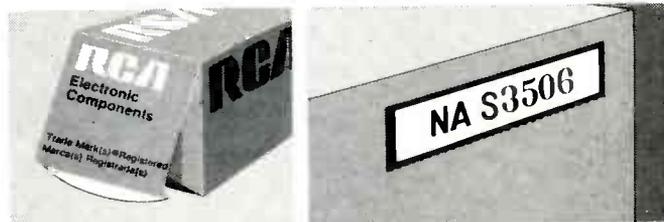Pick up your copy of the RCA "Tear and Share '76" Prize Book, saver envelope and gift order form at your participating RCA distributor. You have until November 30, 1976 to tear 'n share in RCA's bonanza of great gifts. RCA Distributor and Special Products Division, Cherry Hill, N.J. 08101.



*Save the receiving tube carton end that is *not* marked with the tube type number, and the warranty serial number sticker that appears above the warranty envelope on the upper right hand corner of the color picture tube carton. One warranty serial number sticker is equal in value to 20 receiving tube carton ends.

RCA

Needed: Schematic and/or service manual for I.T.T. Industrial Products Division medical monitor solid-state oscilloscope, Type KM402, Serial 7284. (12" screen). Any information would be helpful. Will buy, or copy and return.

Joe Amenta
534 W. Addison St.
Suite One South
Chicago, Illinois 60613

For Trade: Will trade radio and TV tubes for test equipment and Rider's radio manuals.

Troch's TV
290 Main St.
Spotswood, New Jersey 08884

Needed: Schematic for Zenith transoceanic portable radio, Model 8G00STZ1. Will buy, or copy and return.

Walter J. Theurer
Fulton-Montgomery Community College
Johnstown, New York 12095

For Sale: B&K 1460 scope, B&K color bar generator, Sencore 7-in-1 bias supply, like new; all for \$300.

John Durkin
4231 Ely Ave.
Bronx, New York 10466

Needed: Service data for a Model 2085 8-track tape recorder/player by Mayfair Sound Products. Also, need service data for a stereo receiver Model STA-2100 manufactured by Monarch Electronics International.

John Nicoll
18812 Cypress
Tinley Park, Illinois 60477

Needed: Power transformer for Jackson oscilloscope Model CRO-2 (part #14-59); and a power transformer for Mercury tube checker Model 301. (part #10066410 or 10-1-6).

St. George Electronics
P.O. Box 7, Water Street
St. George, Bermuda

Needed: One power transformer 54-26 for Heathkit Model 0-12 oscilloscope.

Joseph J. Babis
66 Pumpkin Ground Road
Stratford, Connecticut 06497

Needed: Schematic and/or assembly manual for Lafayette Genometer Kit 38-1001, Model 156, manufactured by Accurate Instrument.

Bill's TV Service
William E. Schaefer
1136 Limekiln Pike
Ambler, Pennsylvania 19002

"Wireless" Radio Repairs

Servicing the "wireless", modular CB transceivers by Royce is different from repairs of conventional radios having circuit boards and many connecting wires. The basics of Phase-Locked Loops (PLL) also are explained.

The outside appearance of the Royce Model 655 CB radio transceiver gives no hint of the unusual construction inside.



By Marvin J. Beasley, CET
Technical Associates, Inc.

Wires Versus Modules

We technicians have no reasons for judging the merits of various kinds of wiring or mechanical layout, except as they affect either the performance, or the difficulty of making repairs. And we tend to ignore most claims made by manufacturers about the products. In fact, most technicians might be described as being blasé.

Even so, my first glance inside a Royce "wireless" type of CB radio transceiver startled me. Much of the works seemed to be missing (Figure 1), as though the radio might be a sample or a mockup.

But a closer look revealed a "mother" circuit board (Figure 2), into which the terminals of four modules and a shielded synthesizer were inserted and soldered. The

mother board had all of the copper-foil type of connecting wires on it, and this eliminated the usual clutter of wires that tend to hide the components and give an untidy appearance to radios of conventional construction.

The modules are spaced rather close together. In fact, there's not enough room for any extensive testing on the modules. A solution is shown in Figure 2; unsolder the terminal pins, remove the module, place it in the same position below the circuit board, solder the pins, and you have unlimited space on both sides of the module for "live" tests.

Figure 3 pictures three of the modules, removed from the radio. And Figure 4 shows the conventional 23-channel Royce synthesizer, which uses 14 crystals and 4 transistors. Not shown is the Phase-Locked Loop (PLL) module and switch; in appearance it is merely a

shielded box.

Good accessibility to most circuits and components is shown by the two pictures in Figure 5. Both metal sides have cutouts.

Servicing Procedures

Efficient servicing requires you to match the trouble symptoms with the functions of the basic circuits. Now then, if you can do that (without problems) from the full schematic alone, you need nothing else. But, when the maze of symbols interfere with your logical analysis, you should have a block diagram (Figure 6).

Incidentally, the service literature from Royce is excellent. It includes specifications, troubleshooting charts (Figure 7), voltage charts, and alignment instructions.

If you are tired of squinting over the usual 3-inch schematic, the Americanized 11-by-17-inch schematic (that's supplied with each

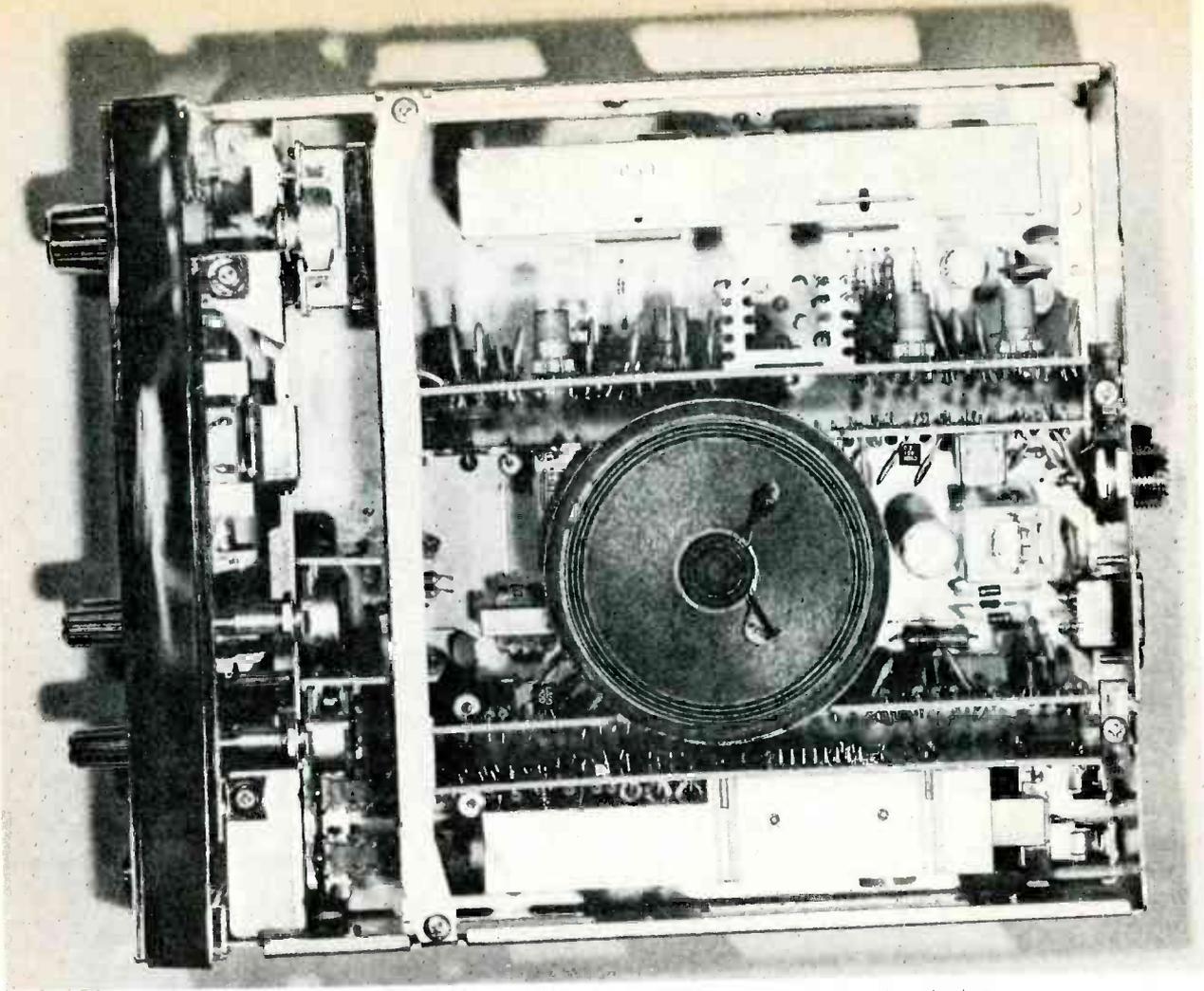


Fig. 1 The Model 655 seems to be unfinished; the usual maze of connecting wires is missing.

radio) will be a relief.

Warranty

Although the terminals of the Royce modules are soldered to the mother board (as a precaution against intermittent connections in rough mobile service), any module can be unsoldered and removed in less than 5 minutes. Therefore, the Royce warranty provides for the no-charge exchange of a new module for the defective one, and for labor to replace (**not** repair) the module.

Royce appoints warranty stations, but independent shops can buy service manuals, modules, and components from the factory for out-of-warranty repairs.

Of course, if the radio is out of warranty, you either can replace individual components on the modules, or obtain and replace complete modules; it's your choice.

The exchange price of modules is

about 25% of the list price of new modules.

Phase-Locked Loops

It seems likely that all of the new 40-channel CB radios to be sold after January 1 of 1977 will employ frequency synthesizers of the Phase-Locked Loop (PLL) type, rather than ones using quartz crystals.

The reason for this prediction is the high cost and scarcity of crystals. A crystal synthesizer for 40 channels might require 21 crystals, while a PPL synthesizer could use 3 crystals and 10 IC's.

Very little information has been released about the Royce PLL system; however, we can give some general data and history that should help you understand basic phase-locked loops.

History of PLL

In 1932, British engineers described a system of synchronous

reception of radio signals by locked-phase signals. This method was developed in the search for a circuit to compete with the superheterodyne. However, both the cost and complexity were excessive, and PLL circuits never became popular for AM reception.

Even so, other simple applications of Phase-Locked Loops have been used over the years. For example, all of the frequency-locking circuits for horizontal oscillators in TV receivers are PLL's.

FM Automatic-Frequency Control (AFC) operation, which sampled the positive-zero-negative "S"-curve output voltage from the FM detector and used it to fine-tune the oscillator frequency, also was (and is) a type of PLL action. And what of color-oscillator locking circuits? Think of the ones that had two diodes to compare the phase of burst and 3.58-MHz oscillator signals. From the diodes came a DC

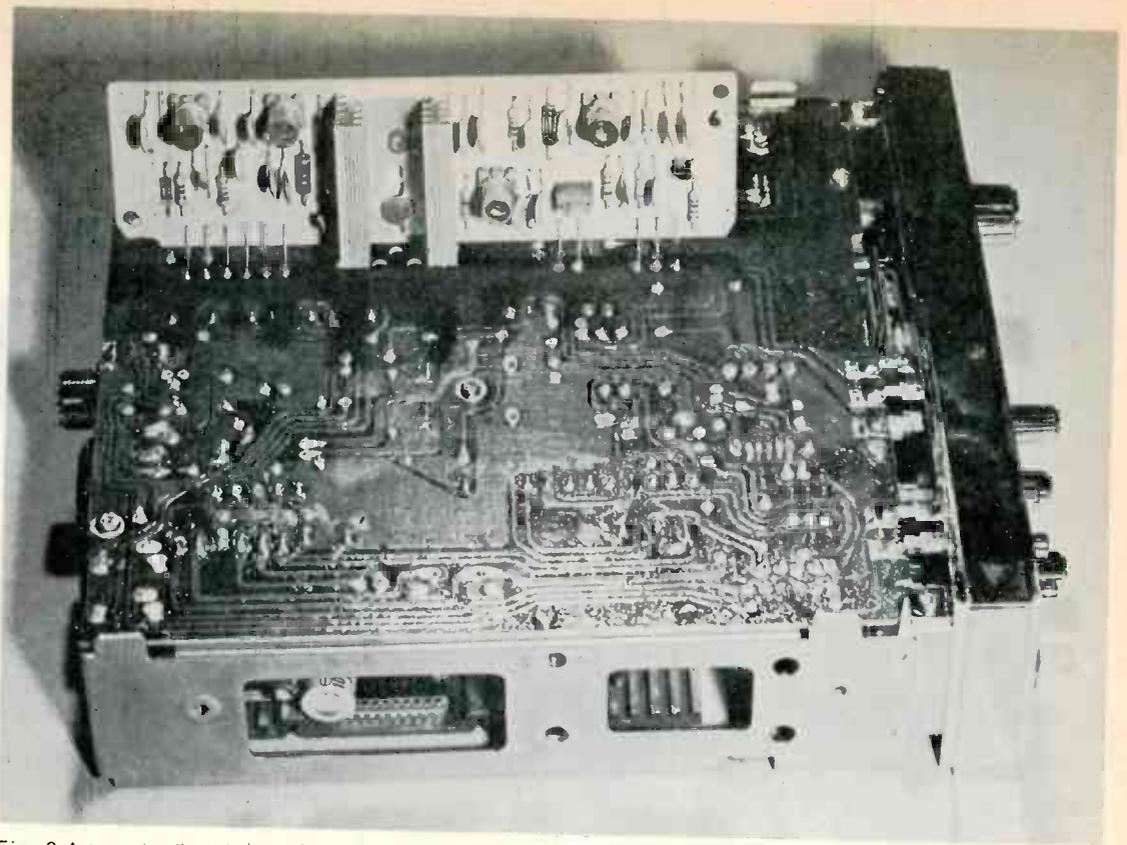


Fig. 2 A "mother" circuit board supplies the copper-bonded connecting wires, and the module pins are soldered to this board. To obtain more room for power-on servicing, the modules can be removed and soldered on the bottom of the board, as shown.

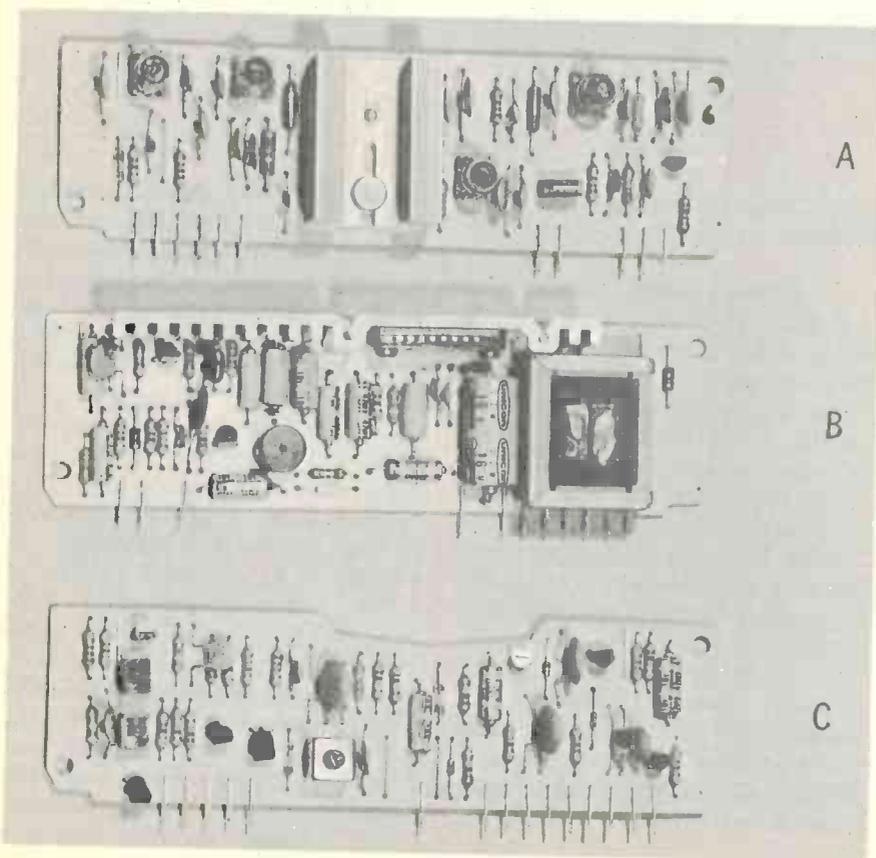


Fig. 3 These are three Royce modules. (A) The U4 module has the transmitter pre-driver and output stages; (B) the audio/modulator stages and the modulation transformer are on the U3 module; (C) U2 module contains the IF stages.

voltage used to vary the capacitance of a reactance stage. In turn, the reactance circuit determined the final frequency and phase of the 3.58-MHz oscillator. Those circuits, too, were simple examples of PLL, although we didn't call them by that term.

Notice that all of these circuits forced the frequency of an unstable oscillator to keep in step with the frequency of some standard.

Of course, having a PLL and a crystal oscillator which both produce the **same** frequency in a CB radio would not be desirable. But a PLL would have great value if it could generate a phase-locked signal at **many** different **ratios** (either higher or lower) of frequency relative to the standard stable oscillator. Even then, it's true that the **two signals supplied to the phase comparator ALWAYS have identical frequencies and a 90-degree phase**. Proper operation of any PLL depends on these primary conditions.

When the standard and the variable oscillators are locked together (even though the locking is between octaves, sub-octaves, or

Announcing an . . .

Exclusive New Broadband MATV Amplifier

with Automatic Overload Control



Model 3662

Just set it.. and forget it.

- Automatic control for input variations of up to 20 dB
- Eliminates nuisance service calls
- 45 dB Gain, VHF High Band
- +52 dBmV Output Capability
- Separate Lo and Hi VHF band controls
- Operates at full output rating
- Switch selectable AOC or MAN operation
- Lightning protected
- Universal rack or surface mounting bracket
- UL listed

Jerrold Model 3662 is the only broadband MATV amplifier with output signal levels automatically controlled. This exclusive feature permits use of the full output capability of a broadband amplifier without fear of overload due to input signal fluctuations. AOC operates to:

1. Prevent overloading the amplifier when input levels increase.
2. Increase amplifier gain to compensate for signal fades.
3. Prevent system cross-modulation even if only one channel level increases or fades.

TRY THE 3662 FOR YOUR NEXT MATV INSTALLATION

JERROLD ELECTRONICS
GENERAL INSTRUMENT CORPORATION



For More Details Circle (5) on Reply Card

other ratios), the output-signal frequency will have the **same** drift as the standard signal. If a CB radio has 40 channels from a PLL, all 40 will have the **same** drift and percentage of accuracy. This is an important advantage, because it's much easier to stabilize one oscillator than several.

Basic PLL

Figure 8 gives the block diagram

of a simple basic PLL circuit. Except for a couple of details, it could be the diagram of horizontal locking, color locking, or AFC correction. Error-correction amplifiers aren't always used in locking circuits; and for AFC, the phase of a tuned circuit is the standard, rather than a separate master signal. Any loop system needs amplification somewhere, for high gain is essential for precise correction and

operation over wide pull-in and lock-in ranges.

PLL differences

In TV circuits, the DC error-correcting voltage from the phase comparator (detector) often is zero when the oscillator needs no correction, and it swings negative or positive as required to maintain the locking and phase.

Other kinds of PLL circuits might operate with a correction voltage of a designated positive value, with the actual voltage swinging up or down from that point to hold the locking.

PLL phase-comparator circuits usually do not have two diodes as rectifiers. Instead, a flip-flop multivibrator might be used, one which varies the width of the output pulses according to the phase difference between the input signals. After processing and filtering, the output pulses become a DC voltage whose value depends on the width of the pulses.

Also, the voltage-controlled oscillator probably would be tuned by a varicap diode, whose capacitance is determined by the DC control voltage from the phase comparator. In that case, the comparator is arranged so the control voltage is highest when the phase difference between the inputs to the comparator is the greatest. The error-correction voltage pulls the voltage-controlled oscillator in the direction of the standard input-signal frequency until locking occurs.

Adding dividers

A PLL system can be fooled into believing the voltage-controlled oscillator has the same frequency as the input standard by adding a digital frequency divider to the sample of oscillator signal that is fed to the comparator (see Figure 9).

Suppose the frequency divider gave a reduction of 10 times. When the error-correcting DC voltage brought the two signals at the phase comparator into lock (same frequency and phase), the output signal from the Voltage-Controlled Oscillator (VCO) would have 10 times the frequency of the standard signal input to the comparator. This frequency-multiplied signal would have the same stability of frequency as the standard signal.

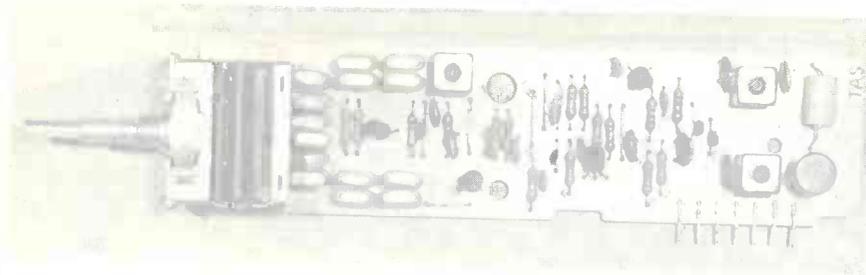


Fig. 4 The U6 Royce module contains a conventional synthesizer with 14 crystals and four transistors.


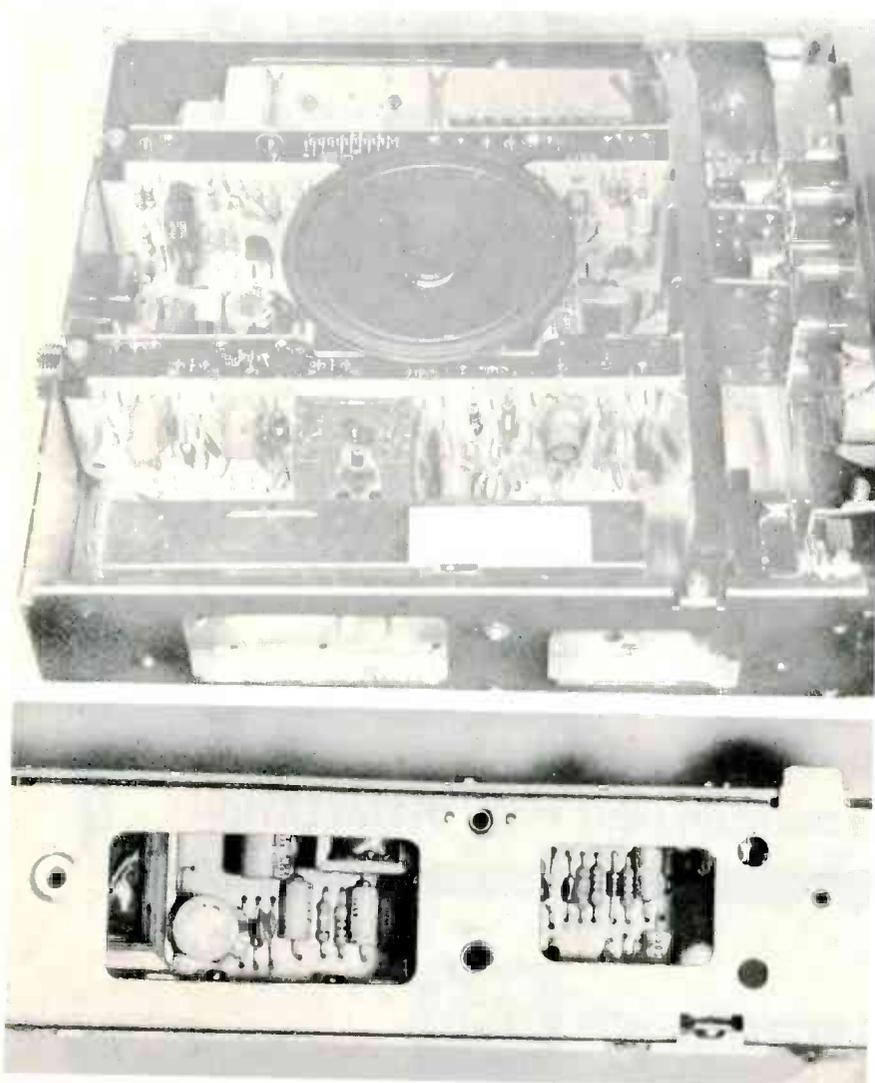


Fig. 5 These two pictures illustrate the good accessibility to most components. Both side panels have cut-outs.

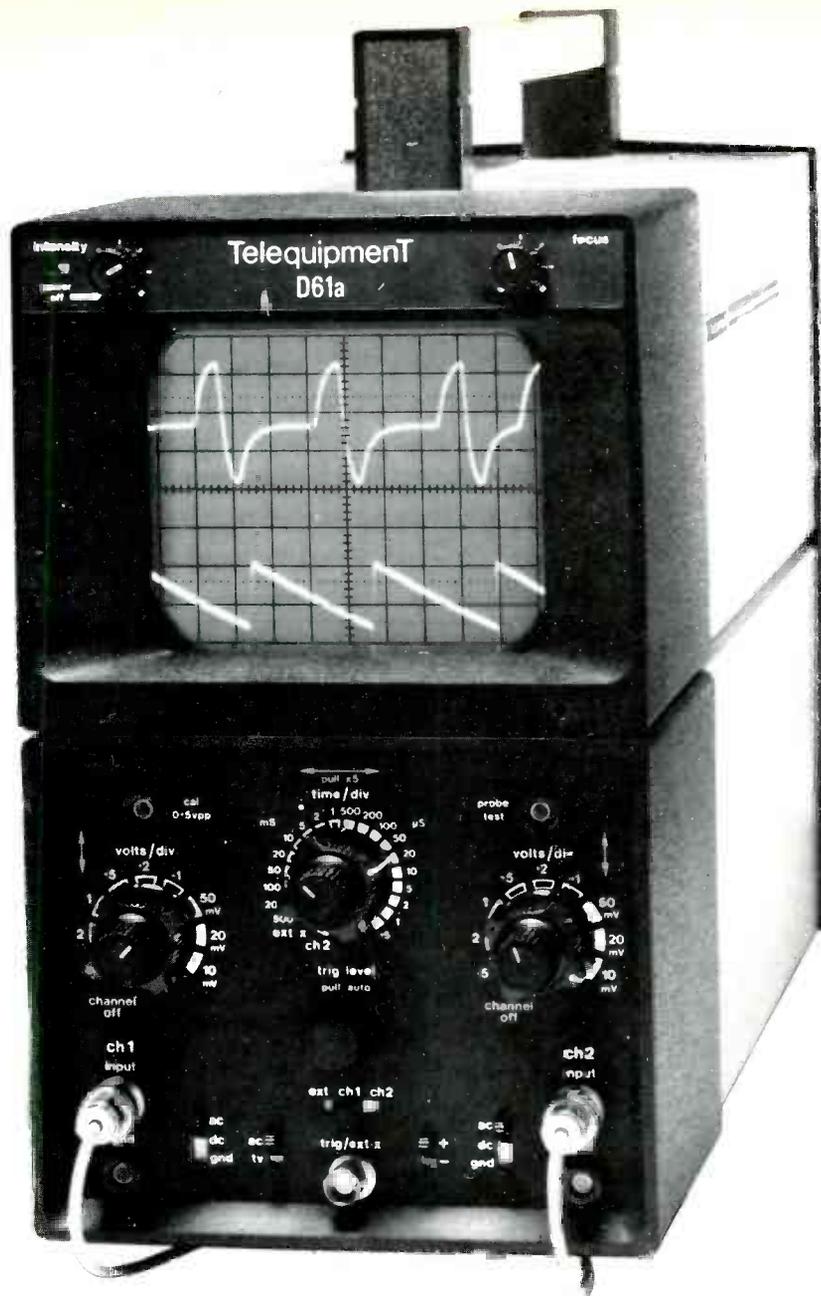

A NEW LOW-COST, DUAL-TRACE SERVICE OSCILLOSCOPE FULLY BACKED BY TEKTRONIX

Now for only \$595 you can get a portable, 10 MHz dual-trace service oscilloscope. The 18 lb TELE-EQUIPMENT D61a has front-panel controls that are easy to understand, easy to use. Full-sensitivity X-Y gives you vector displays that are in true phase relationship—displays that you can rely on. And automatic selection of alternate or chopped mode and automatic selection of tv line or frame triggering

make this oscilloscope ideal for classroom use as well as the service shop.

D61a features a bright 8 x 10 cm display, and 10 mV sensitivity in dual-trace and X-Y operation. It is fully backed by a standard Tektronix one-year warranty and may be serviced at any of 50 Tektronix Service Centers nationwide. Call your nearest Tektronix Field Engineer or circle the reader interest

number below for specifications and ordering information on the new D61a and other low cost TELE-EQUIPMENT Oscilloscopes.

U.S. Sales Prices FOB Beaverton, Oregon



P.O. Box 500
Beaverton, OR 97077

For Technical Data Circle (6) on Reply Card
For Demonstration Only Circle (7) on Reply Card

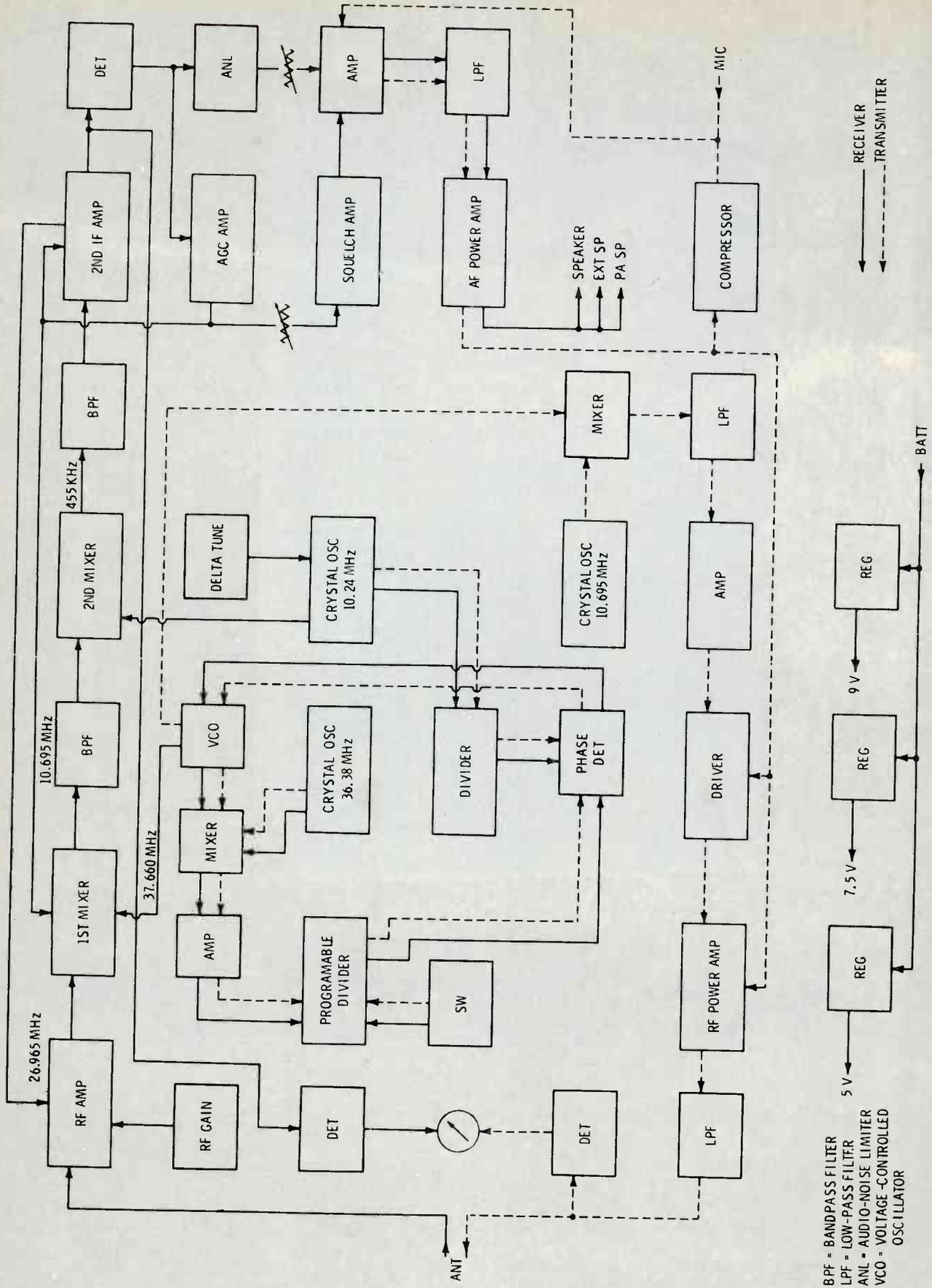


Fig. 6 This block diagram of the Royce Model 655 CB radio shows the major stages, components, and signal-flow paths.

So far, the performance has not been spectacular; after all, a series of doublers could have given 4, 8, 16, or more amounts of frequency change. But, there is more.

The fixed divider can be replaced by one giving a **series** of different divisions, the number controlled by a switch. Such a circuit is called a "programmable" or "variable" divider (even though it is not continuously variable, but has definite steps).

Also, a divider (either fixed or variable) can be added between the standard signal and the phase comparator. When variable dividers

are used with both signals applied to the phase comparator, the VCO can be forced into operating at any one of a large number of stable frequencies. Also, additional crystal oscillators can be switched in, when needed, to provide even more frequencies.

Notice that the output signal from a PLL can be much more pure than it is from other synthesizers which **mix** two frequencies in a non-linear circuit, because there are no sum-and-difference frequency products in the output (only the normal oscillator harmonics).

One of the fascinations about

PLL circuits in general is the many (almost endless) array of functions that can be done with variations of the basic PLL circuit.

For example, SCA demodulation of background music on FM stations can be done with one IC, six capacitors, and ten resistors. AM or FM demodulation is nearly that simple. The voltage-controlled oscillator can be made to lock to a weak signal that's buried under noise, thus giving the effect of amplification and tuning, but requiring fewer components. Or, a PLL can be locked to the harmonic of a signal, for another kind of


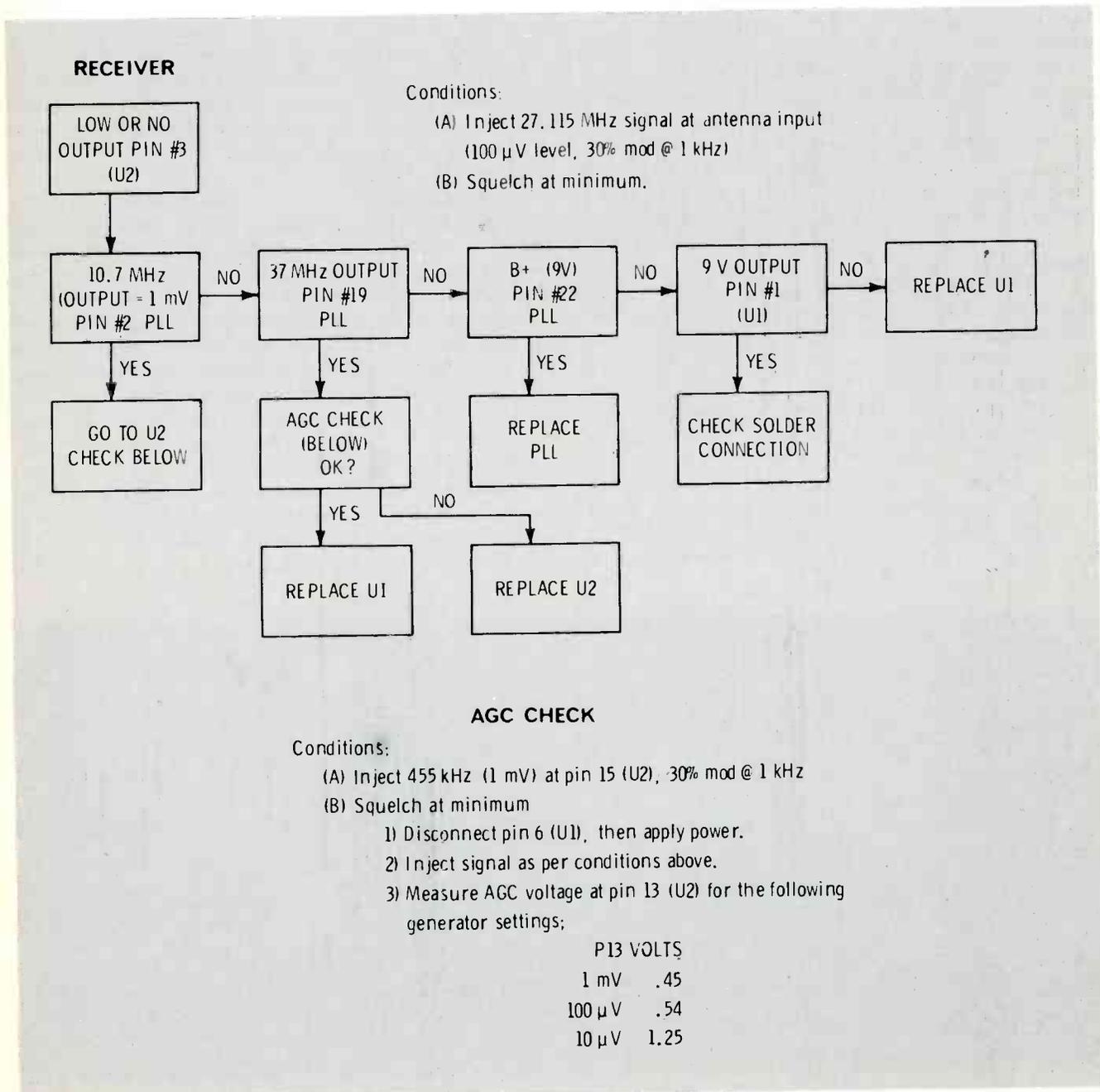


Fig. 7 Typical of the Royce service aids is this troubleshooting chart.

Fig. 8 The basic block diagram of a Phase-Locked Loop (PLL) is the same as many circuits used in TV receivers. When the frequency of the VCO is wrong, the phase comparator produces an error-correction DC voltage which varies the frequency until it is in lock.

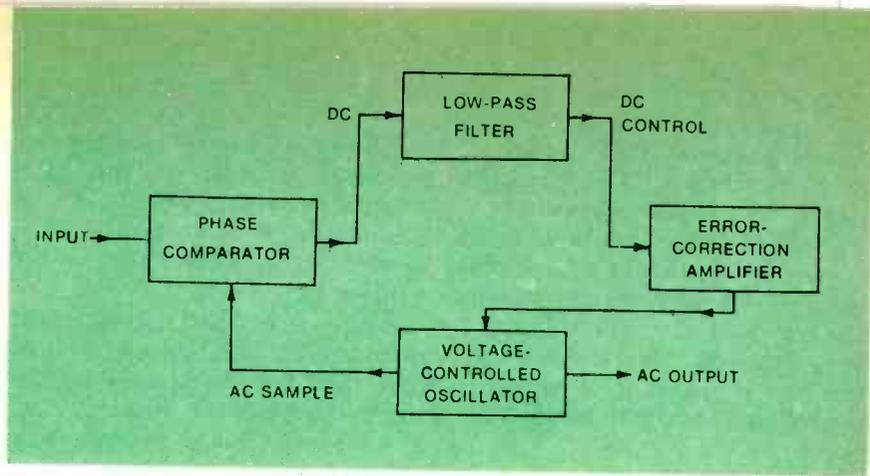

frequency multiplication.

Unwanted sidebands (even those too close to be filtered out) can be removed by locking a PLL to the fundamental.

Laboratory frequency standards have been built at low cost by using a PLL that is locked to WWV, the National Bureau Of Standards station.

These are just a few of the possible applications for PLL's.

Royce PLL

At this time, Royce does not recommend field repairs of the Gyro-Lock PLL modules. For that reason, the following circuit explanation is not detailed.

Even so, we can learn part of the operation from Figure 6. Of the three crystal oscillators, two are used together at a time. One variation from the basic PLL circuit is that the variable-frequency signal is not obtained solely from a VCO,

but by heterodyning the 36.38-MHz and VCO signals in a mixer, then the resultant is amplified and divided by a programmed divider before it reaches the phase comparator.

To obtain the transmitting frequency (26.965 MHz for Channel 1), the 10.695-MHz signal is mixed with the output of the VCO. For receiving, the VCO output supplies the first mixer, producing a first IF of 10.695 MHz, which is heterodyned down to 455 KHz by a signal from the 10.24-MHz oscillator.

Frequency and frequency drift during transmitting depends on both the 36.38-MHz and 10.695-MHz oscillators. All channels will have the same percentage of frequency error.

Frequency and frequency drift during receiving are functions of both the 10.24-MHz oscillator and the 36.38-MHz oscillator, plus the variation of the 10.24-MHz fre-

quency by the "Delta" control. This control can vary the oscillator frequency during receiving by as much as 1.5 KHz, to allow proper tuning of any out-of-tolerance stations.

Length and position of the connections to the channel switch are not critical because only DC voltages go there.

Comments

Modular design of CB transmitter radios, and the consequent elimination of most connecting discrete wires can be important by permitting faster (more profitable) repairs. Of course, the modules must be readily available through an exchange program, and the service data should be of good quality. All of these desirable things are true about Royce "Wireless" models, and we can hope that other manufacturers will follow a similar plan, which would help the CB repair business. □

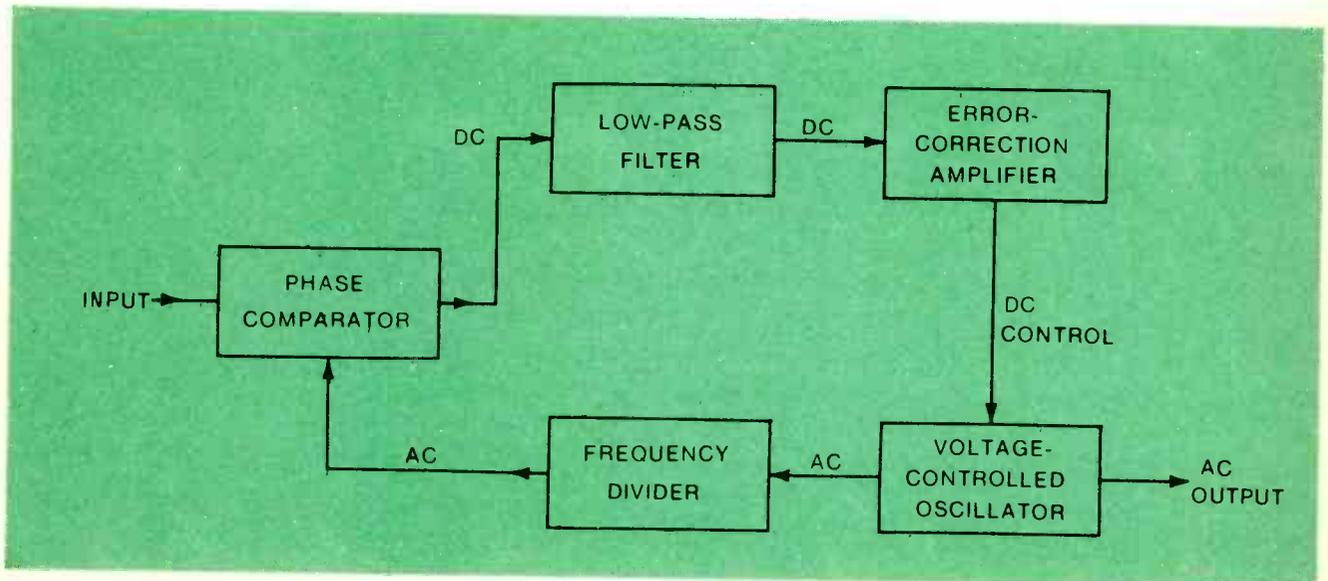


Fig. 9 For use in frequency synthesizers, a frequency divider is added so the VCO can be locked to frequencies other than the standard.

THE CB SERVICE MONITOR BY MEASUREMENTS



MODEL CB 27E
\$495.00*

Low-cost, rugged, portable instrument for accurately checking, trouble shooting and aligning Citizens Band Transceivers operating in any of 40 Channels presently assigned.

- Phase-locked loop circuitry referenced to "AT" cut crystal.
- Monitor and transmitter are both protected against overloading if transmitter is accidentally keyed.
- Provision for adding future channels.
- Built-in transmitter power meter.
- Built-in speaker monitors transmitter frequencies down to zero-beat and provides on-the-air voice evaluation.

Write or call for additional information.

*F.O.B. Manchester, N.H.




McGRAW-EDISON COMPANY
Edison Electronics Division

Grenier Field Municipal Airport, Manchester, N.H. 03103
(603) 669-0940 • TWX 710-220-1747

Philco E21 Chassis... Circuits and Servicing

Part 2/By John Simrell

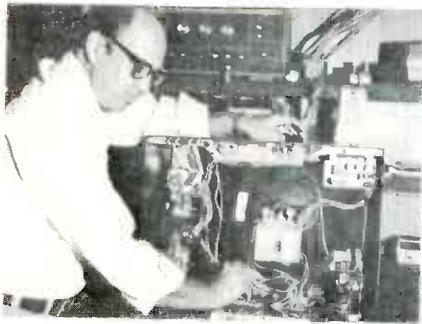

Power supplies of the Philco E21 chassis were covered last month, including the safety shut-down circuit that kills the horizontal drive. This month, the horizontal-sweep circuits and several case histories are examined.

Functions Of IC400

Four functions are accomplished inside one integrated circuit, IC400 (Figure 1). These four are: noise-inversion; sync separation; phase comparison and oscillator control; and horizontal oscillation.

Noise inversion


Instability from impulse noise is minimized by separating the pulses from the video signal, inverting the phase, and feeding these clipped and inverted noise pulses into the video where they cancel the noise pulses of the original phase. Most of this occurs inside the IC, where

you can't trace it. But the inverted noise comes out of the IC at pin 2.


Sync separation

Although the transistors are inside the IC, the network that's always supplied at the input of the sync separator is external. Positive-going video emerges at pin 4, goes through the network, and goes back into the IC at pin 5.

Testpoint "SS", at pin 5, allows you to observe with a scope the video after it has passed through those filtering components. But the testpoint also has another useful function. When you ground that point, all sync (both vertical and horizontal) is eliminated, thus allowing you to accurately adjust the frequency of the horizontal oscillator. Otherwise, if you don't use the testpoint, the oscillator hold-in range is so tight that it's difficult to know where to adjust the core of the oscillator coil. No hold control is provided for the customer, so it's up to you to adjust the frequency accurately.

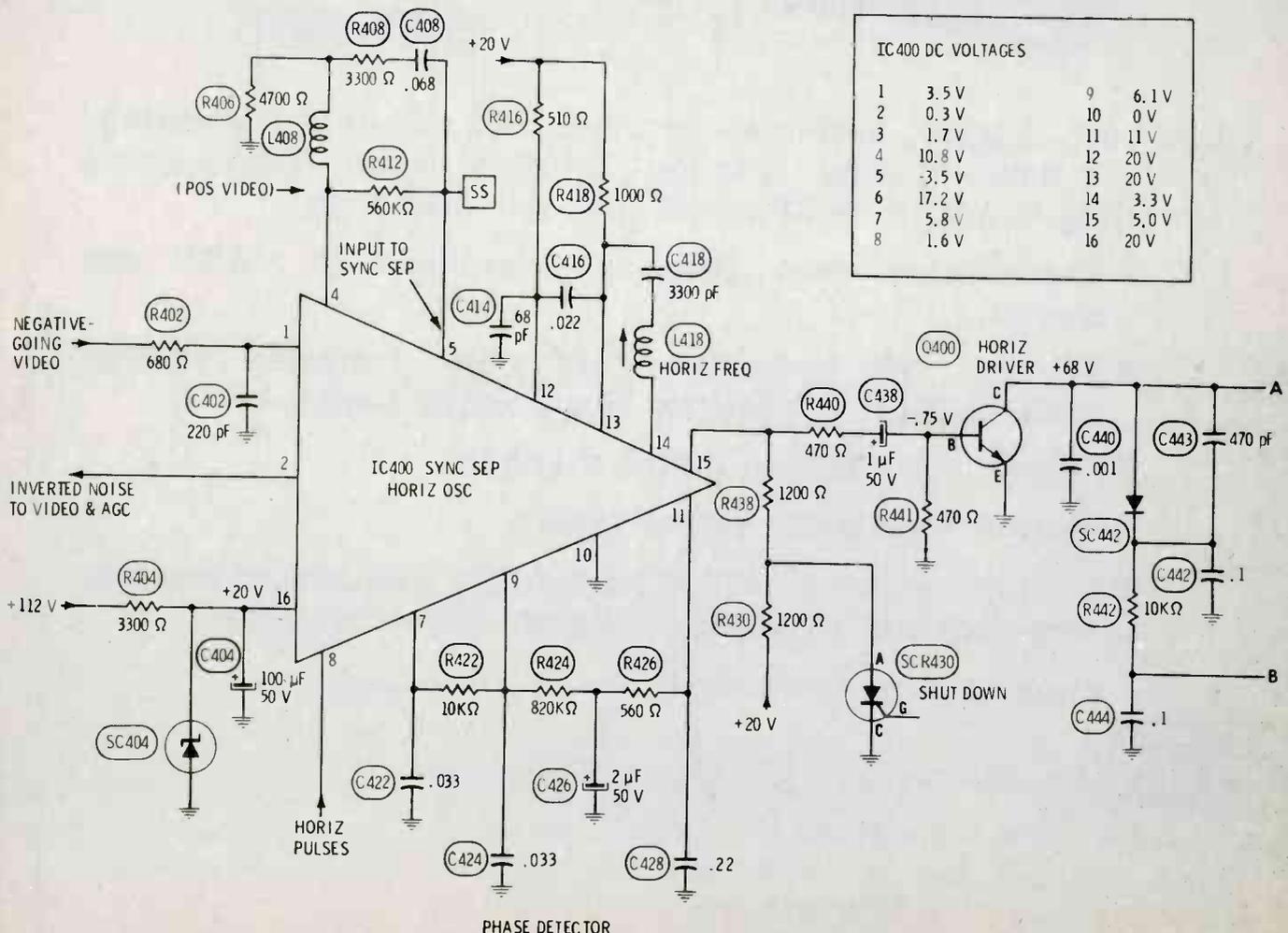

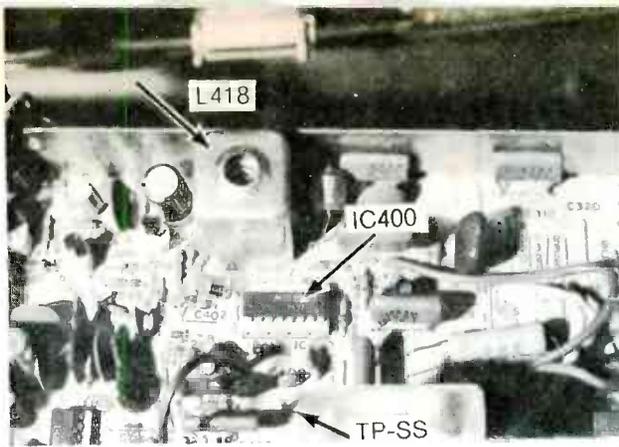After separation of the sync tips from the composite video, the signal is divided, with the vertical sync emerging from the IC at pin 6, and the horizontal-sync pulses going internally to the phase detector. Some components of the phase detector are mounted outside the IC (those tied to pins 7, 9, and 11), and these points can be used to observe the waveforms.



These are the main components of the horizontal-oscillator circuit in the Philco E21-4 chassis (the Sylvania E21 is the same).

Phase detection and oscillator control

Horizontal pulses, which are filtered into a sawtooth waveform for the phase detector, come from the horizontal-blanker stage, and they enter the IC at pin 8. Of course, both sync pulses and a sawtooth from the horizontal-sweep circuit are necessary for correct phase detection and horizontal locking. The horizontal sawtooth can be viewed at pin 7.

Horizontal oscillation

The last function of IC400 is to furnish most of the components for

the horizontal oscillator. Again, some components are external to the IC, and they include B+ and oscillator coil parts that are connected to pins 12, 13, and 14. Notice that no customer horizontal-hold control is provided.

A scope waveform taken at pin 14 will prove whether or not the oscillator is operating.

Typical DC voltages for IC400 are given in a block on the schematic. Keep them handy for reference during troubleshooting.

Square waves from the oscillator emerge from pin 15. Last month, we described how the shut-down circuit (which was triggered by excessive voltage of the +112-volt supply, or the excessive current of the +29-volt supply) forced SCR430 to short out most of the amplitude of square waves coming from pin 15. This reduction of drive signal turned off the driver and output transistors so they drew no current.

Of course, loss of the drive signal eliminates the high voltage and the

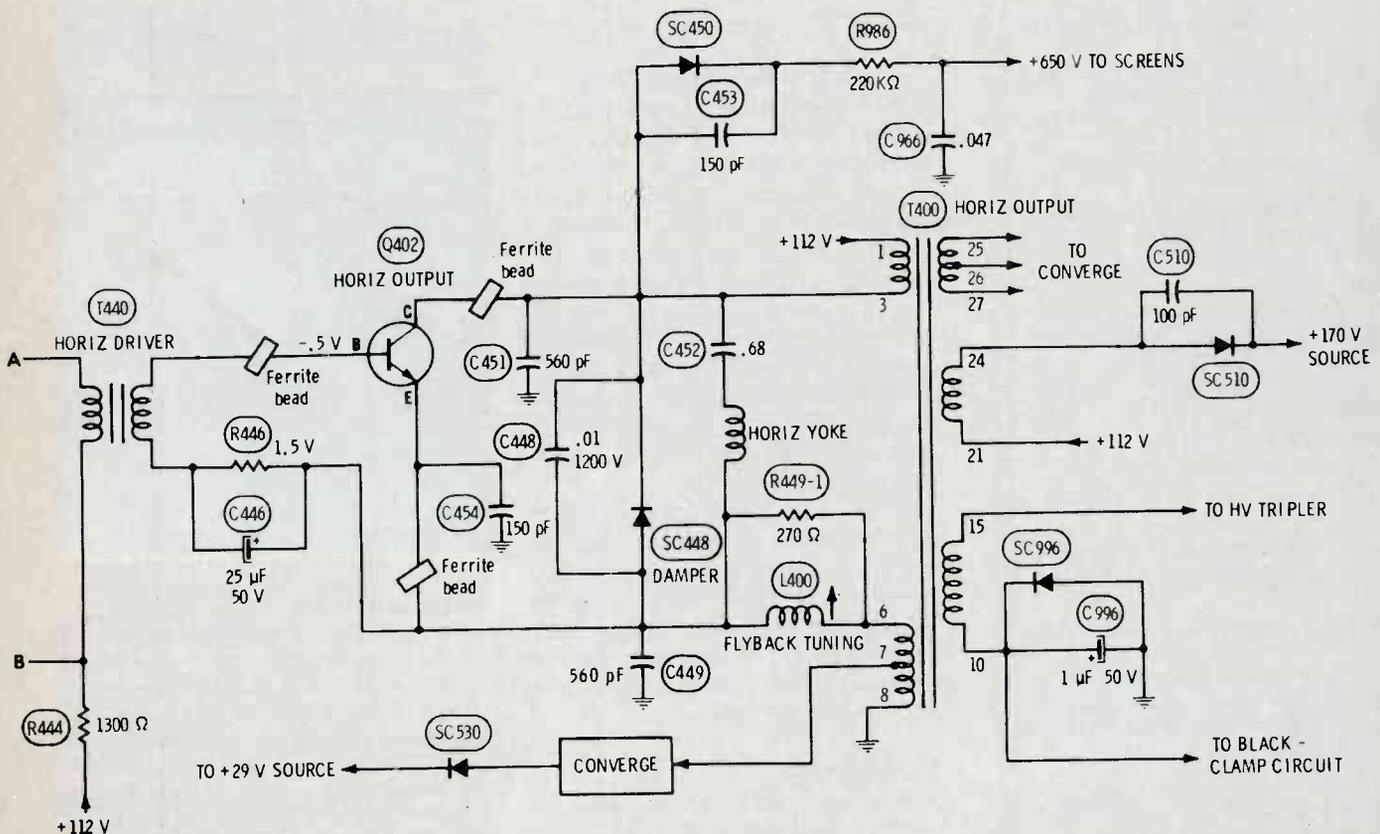


Fig. 1 Many of the components for the noise-inversion, sync-separation, and horizontal-oscillator functions are inside IC400; however, the vital waveforms can be viewed at the pins. The shut-down circuit was described in the September issue of *ELECTRONIC SERVICING*. Notice that the emitter of Q402 is not grounded, but drives one winding of the flyback transformer.

New
B&K-PRECISION
10MHz
Dual-Trace
Scope
Triggers to
20MHz



B&K-PRECISION
 MODEL 1471B \$495

Typical response is less than 6dB down at 15MHz and usable response is much greater.

- 5" CRT with bright P31 blue phosphor
- Mode automatically shifts between CHOP and ALTERNATE as you change sweep time for fast set-up.
- Fully regulated high- and low-voltage supplies, for accuracy over 105-130VAC range.
- 18 calibrated sweeps— $1\mu\text{S}/\text{cm}$ to $.5\text{S}/\text{cm}$
- 10 mV/cm sensitivity
- TV sync separators
- Front panel X-Y vectorscope operation
- Plug-in PC board construction
- TTL compatible Z-axis

Available from your distributor.

B&K PRECISION
 PRODUCTS OF DYNASCAN

6460 West Cortland Avenue
 Chicago, Illinois 60635 • 312/889-9087
 In Canada: Atlas Electronics, Toronto

raster, so one of your first tests when you encounter those symptoms is to measure the frequency and amplitude of the square waves at pin 15.

Horizontal Driver

From pin 15 of IC400, the square waves go through R440 and C438 to the base of Q400, the horizontal-driver transistor. No DC bias is provided for the base; therefore, loss of the square waves there merely cuts off all the collector current of Q400.

In normal operation, each positive peak of the square waves acts as a temporary forward bias of Q400, causing it to draw heavy current during those peaks, and no current between the peaks.

Q400 is an intermediate-power type of silicon transistor, operating with a collector voltage of about +70 volts, and it does run warm. R442, C442, and diode SC442, in the collector circuit, are necessary to shape the waveform which is sent to the base of the horizontal-output transistor.

When you are checking this driver stage, your best tests will involve the DC voltages and waveforms at the base and the collector.

Horizontal-Output Stage

It is interesting to note that the collector of Q400 is the last point where the drive can be viewed (if the set is working properly). That's because the output transistor, Q402, is floated high above ground. Both the collector and the emitter feed separate windings of the flyback; therefore, a scope connected to the base or the emitter has the same 420-volt PP signal of negative-going pulses, while the collector has positive-going pulses of the same amplitude.

Both the damper diode (SC448) and the yoke with its capacitor, C452, are paralleled across the C/E terminals of Q402, in the conventional way. C448 has a major effect on the amount of high voltage, and you should not substitute any other size for the .01 value.

Flyback tuning



In many solid-state television receivers, the horizontal-output stage (yoke and flyback) is tuned to the third harmonic of the sweep fre-

quency. This is done for two reasons. It gives better high-voltage regulation, and the amplitude of the flyback pulse is reduced, thus minimizing the possibility of damage to the output transistor. (The waveform at the emitter of Q402, the output transistor, changes slightly as the "flyback tuning" coil is adjusted. But the change is not sufficient to use as a symptom.)

With Philco E20 and E21 chassis, the tuning is adjustable by means of L400 coil, which is labeled "flyback tuning". The method of adjusting is simple: turn down the brightness until the raster goes black, then adjust L400 for **minimum** high voltage. That's all.

Black-clamp

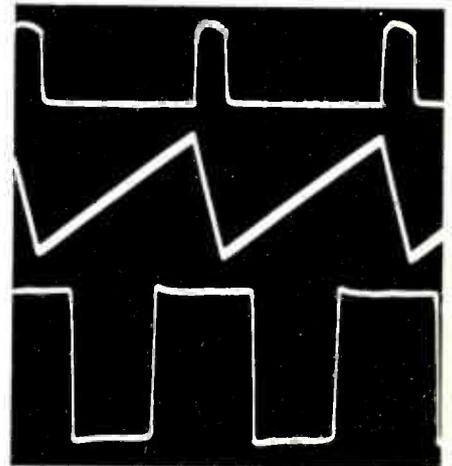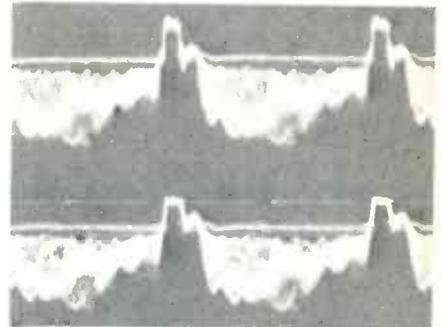The black-clamping circuit (called Automatic-Brightness Limit-



Here are typical waveforms from the IC400 and Q400 stages. The dual-trace 10-volt PP video waveforms are (at the top) pin 4 of IC400, and pin 5 (at bottom). Top trace of the three shows the 3.9-volt PP positive-going pulses at IC400 pin 7. These are inverted and integrated into 1.7-volt PP sawteeth (center trace) for the phase detector (the sync pulses do not leave the IC). The square waves at the bottom are the oscillator-output signal at pin 15 (10-volts PP).

**BE ONE OF THE FIRST IN YOUR AREA WITH THIS
GREAT NEW "TV REPAIR ITEM"**

NU-COLOR Restorers retail for \$24.95 — they are only available through Oneida distributors who in turn make them available to authorized TV service outlets. We've an extensive national consumer ad program in the making that will spread the word about this revolutionary item.

Get in on the PROFITS... write for complete details today!

**Now...Put *NEW LIFE* in your
old color picture tube...**

**Restores ALL the needed
colors to old, washed out,
even colorless pictures...
just plug in and adjust!**

NU-COLOR
**PICTURE TUBE
RESTORER**

U.S. PATENT NO. 3,967,314

from

Oneida

Here is another FIRST from Oneida . . . and it's ours exclusively. Patents have been issued on this revolutionary NEW "TV item." The all-new ONEIDA NU-COLOR PICTURE TUBE RESTORER will, for the first time ever, prolong the original color quality and performance of costly color TV picture tubes. This new electronic item is being manufactured by Oneida and is only available through an Oneida distributor.

NEW NEW NEW NEW NEW

Colorful New Beauty is Good or even better than Original Quality...

ONEIDA'S NU-COLOR **Picture Tube Restorer** provides precise color control to do what the name implies . . . restores color to original quality. It's versatile; a simple adjustment at time of installation provides the proper new color or colors to correct the weak tube. One restorer is all it takes . . . it brings back any degree of any or all of the colors . . . and it does it without damaging the basic tube or shorting any of the elements.

No More need for replacing a costly color tube because of poor, weak or missing colors...

ONEIDA'S NU-COLOR **Restorer** is available, at the present time, for use on all major makes of 70° and 90° picture tubes . . . two models accommodate most all 12" thru 25" color picture tubes. Installation is quick and simple. No wires to connect . . . Simply plug unit in. (Complete instructions are packed with each unit.) Original color strength is restored through boosted and individual biasing networks that increase emission and maintain constant color levels.

Oneida's NU-COLOR Restorer will add new life at a fraction of the cost of a picture tube replacement.

No more need to put up with poor color because of cost of a new picture tube . . . the Oneida NU-COLOR Restorer will bring color back to "as good or better than new" and keep it that way. This restorer should not, in anyway, be confused with brighteners that can shorten tube life and possibly cause tube damage. The Oneida NU-COLOR Restorer is warranted against any defect and complete satisfaction is guaranteed.

Illustrations are simulated, not actual pi



NO RED



NO BLUE

NEW NEW NEW NEW NEW

AN INDUSTRY
FIRST

**EXCLUSIVE
WITH ONEIDA!**



Photos of TV screens.



NO GREEN



WEAK COLOR



Here's how it works

It Enhances the Circuitry to Operate at its Maximum Capability!

The Oneida NU-COLOR Picture Tube Restorer is a completely new concept of TV Circuitry. In essence it is a color amplifier . . . it adds a whole new power circuit to your tube so that, working with the tube, it amplifies and gives new depth, color and dimension to new as well as old weak tubes.

It does not increase the filament voltage as do some types of picture brighteners, and it will not restore color to tubes with burned out filaments, where phosphorous is gone or when the circuitry of the tube has been completely destroyed. So long as the tube has a good filament and phosphorous the NU-COLOR Restorer is capable of producing good new color results.

Ideal for NEW as well as OLD sets . . .

The modest investment of a NU-COLOR Restorer can provide untold hours of colorful new TV picture viewing. Even brand new sets can have picture quality improved . . . and old sets life can be prolonged indefinitely saving the cost of \$100 to \$250 new picture tubes.

Installation is quick and simple . . .

The NU-COLOR Restorer is installed as a bridge between the sets harness and the picture tube.

No need to haul your set away for this major improvement . . . NU-COLOR Restorer can be installed in just a few minutes by any qualified TV serviceman. And you can "try before you buy" for exacting color adjustments are made at time of installation . . . you can see color improvements being made and have your serviceman give you the degree of color most pleasing to you.


NOTE: The NU-COLOR Picture Tube Restorer is not a "cure-all." Its function relates only to the color correction of the TV Picture Tube. If faulty color, etc. is due to other components in the set the NU-COLOR Restorer will not solve the problem.

© 1976, Oneida Electronic Mfg., Inc., Meadville, Pa. U.S.A. Printed in U.S.A.

Oneida
ELECTRONIC MANUFACTURING COMPANY, INC.

P. O. BOX 678 MEADVILLE, PENNSYLVANIA 16335 TELEPHONE 814 336-2125

www.americanradiohistory.com

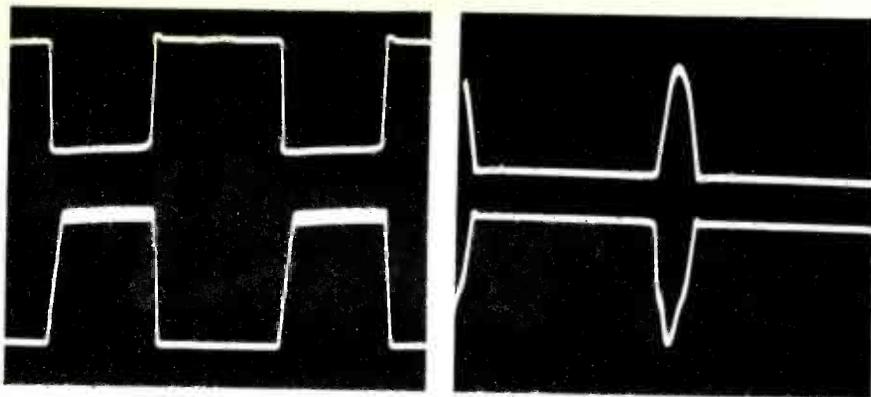

Top trace of the square waves is the 4-volt PP base waveform of Q400, the driver transistor. The 130-volt PP collector waveform is shown by the trace at the bottom. Referring to the pulses, the top ones are the 400-volt PP pulses at the collector of Q402, the horizontal-output transistor, while the bottom trace shows the 400-volt PP negative-going pulses at the emitter (and base), measured relative to ground. Be careful when you test around this area: all three terminals of Q402 have strong horizontal pulses.

er or ABL in other brands) monitors the HV current that passes through the flyback winding to the HVT401 tripler rectifier (see Figure 2).

Before you can understand the operation, you must remember the rule-of-thumb about rectifier circuits: **Any DC voltage coming from rectification will be positive if it is taken from the cathode of the diode, or negative if it comes from the anode of the diode.** Look at the tripler diagram in Figure 2; the last diode feeds the picture tube from its cathode. Therefore, the voltage is positive. At the other end of the tripler, the input AC goes to the anode of the first diode.

Now, if you could measure the DC voltage there (that's virtually impossible because of the high-amplitude pulses), you would find a negative voltage whenever the picture tube draws HV current. Similarly, if you added a resistor from the low end of the HV winding of the flyback (terminal 10, in this case) to ground, you could easily measure a negative voltage from the cold end of the winding to ground (across the resistor).

Well, that's essentially how the circuit operates, except the voltage is positive (because R996 goes to B+, not ground), and it becomes less positive (negative-going) when the HV current increases. This control voltage from terminal 10, C996, and SC996 acts to reduce the positive voltages at the bases of Q900 and Q902. Indirectly, the

brightness control also changes the base voltages, so the action of the black-clamp circuit is to reduce the **brightness** of the picture when it tends to become excessively bright, regardless of the reason for the extra brightness. These changes of base voltages go down through the video stages, changing the operating points of each stage until the cathodes of the picture tube are reached. And there the black-clamp action raises the positive voltage at the CRT cathodes to decrease the brightness, and avoid overloading the sweep system and the picture tube.

Case Histories

Here are some actual repairs that illustrate service procedures for the horizontal sweep of the Philco E20 and E21 chassis.

Case #1

The original symptoms are no-raster and no-sound. Removing the shut-down SCR might bring back the operation. But usually output of the horizontal oscillator is lost some time later.

Voltage checks of IC400 show +17 volts at pin 14 (instead of the usual +3.3 volts). A new IC does not help. After many tests, we find C416 has excessive leakage.

This problem started happening quite often, before the factory made some corrections to prevent it. Later-production sets have the capacitor mounted off of the printed board to prevent heat damage

Can another portable DMM measure up to our popular 280?



B & K-PRECISION
MODEL 280
\$99.95

You be the judge!

?? 280

- Completely portable—uses ordinary C cells or re-chargeables.
- Measures AC/DC voltage, AC/DC current and resistance.
- High accuracy. DC accuracy is $\pm 0.5\%$ on all but the highest range ($\pm 1\%$). Ohms accuracy is 1% on most ranges.
- Full measurement capability, including current measurement to 1 amp.
- 1mV, 1 μ A, 0.1 Ω resolution.
- High/Low-power ohms measurements.
- Large, bright LED display.
- Auto-polarity and decimal point.
- 10-megohm input impedance.
- 0° to +50° C operating range.
- Measures only 6.4 x 4.4 x 2". Under 2 lbs. with batteries.
- Full line of accessories including AC adapter/battery charger, tilt stand and carrying case.

Compare our features, accuracy and price and you'll see why thousands of buyers have selected the B & K-PRECISION 280.

Now in stock at your local distributor.

BK PRECISION
PRODUCTS OF DYNASCAN

6460 West Cortland Avenue
Chicago, Illinois 60635 • 312/889-9087
In Canada: Atlas Electronics, Toronto


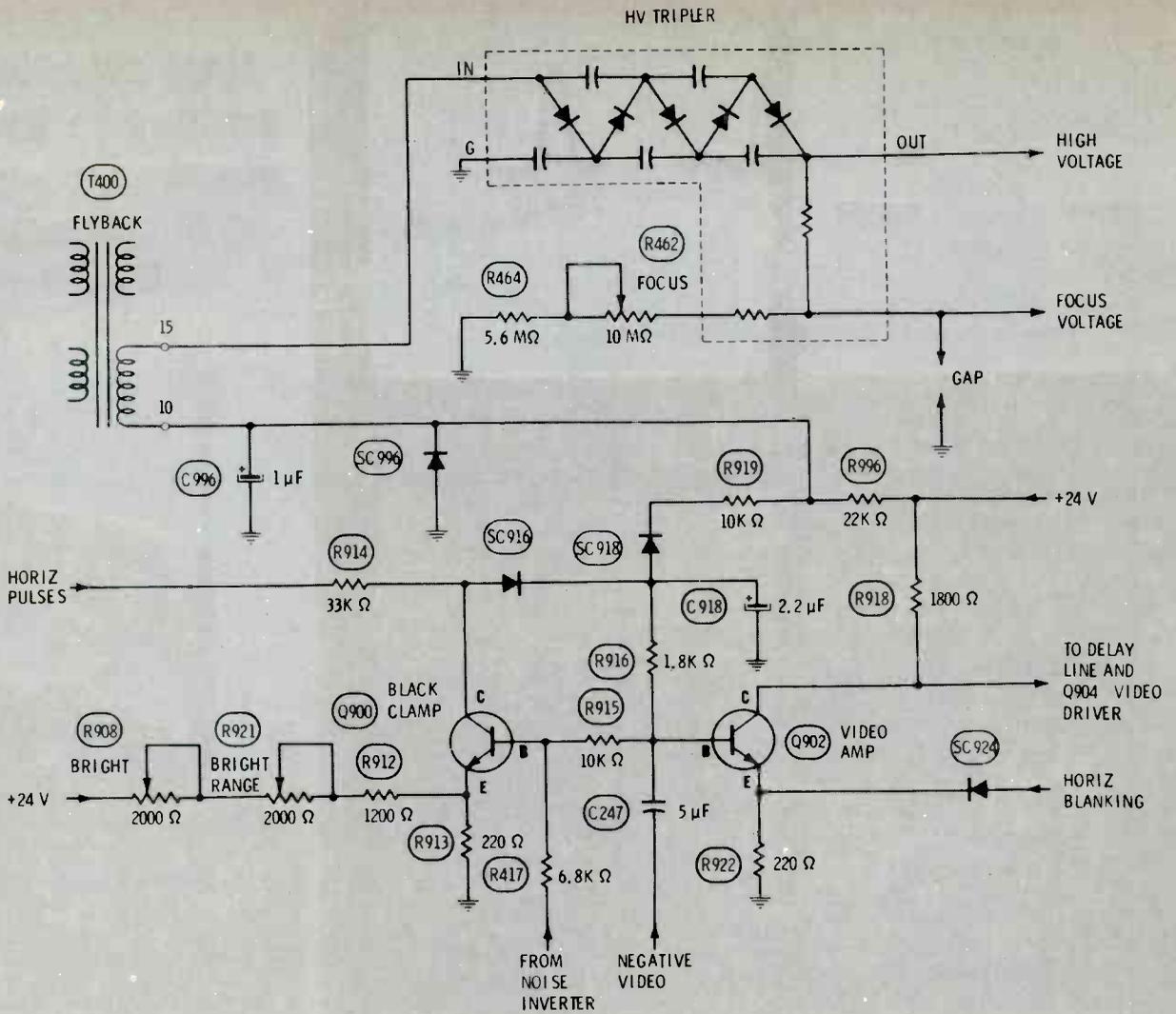


Fig. 2 Details of the automatic-brightness limiter and the black-clamp circuits are shown here. High-voltage current through the tripler to the picture tube produces negative DC voltage at terminal 10 of T400, the flyback (increased current gives higher voltage). This negative voltage cancels part of the positive voltage at the base of Q902. The circuit opposes any increase of brightness, above the design point. Also, changes of video amplitude vary the collector voltage of Q900, the black-clamp transistor, and the voltage goes through SC916 and R916 to the base of Q902, where it maintains the correct black level (brightness versus contrast).

during the time the board is in the solder flow bath.

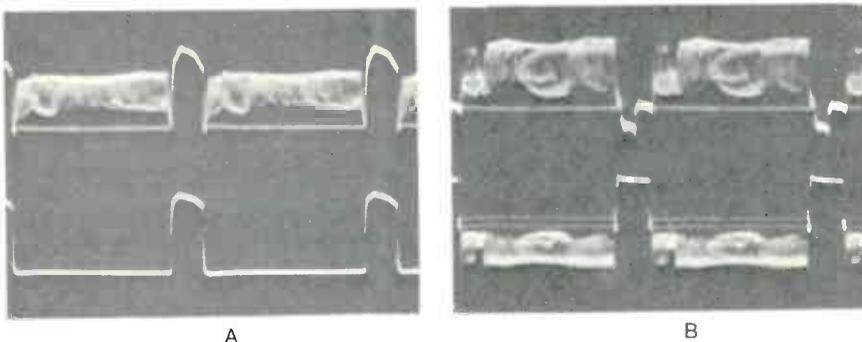Use only an exact replacement capacitor. If you substitute a standard .0033 capacitor, the chances are good the irate customer will be on the phone the first thing next morning after he gets the set back. Since there is no customer hold control, the customer can't chase the wandering horizontal frequency as the capacitor drifts.



Some Q902 waveforms are different because of the horizontal blanking that's added there. (A) Top trace shows the emitter waveform with video and horizontal blanking pulses; the pulses at the anode of SC924 are shown by the bottom trace. (B) Top waveform is the conventional composite video signal at the base of Q902; while the bottom trace shows the broadened blanking area of the collector waveform.

Case #2

This E21-04 chassis set came in with a complaint of "no horizontal locking". Replacement of IC400 made no change, and normal video was found at pin 5 of the IC.

When testpoint "SS" was grounded, the oscillator could be adjusted for a floating picture of the correct frequency, but removing the ground caused the picture to go farther out of lock.

Obviously, the defect was in the

phase detector. Pulses from the blanker at pin 8 were 3.6 VPP, which is about 10% low, but not alarming. DC voltages at the video input (pin 5) and the phase-detector reference (pin 8) were slightly high. Pin 8 was 2.4 volts instead of the normal 1.6. These voltage discrepancies were not enough to upset a technician who still thinks in "tube" language.

Perhaps the defect was in the string of capacitors and resistors around pins 7, 9, and 11. But testing them involves a lot of unsoldering. So, back to the scope again. At pin 8 the waveform was wrong. The base had a lot of "grass". In fact, half of the pulse was video!

How could video get into horizontal pulses? However, the pulses do not come from the flyback, but from the blanker transistor. Checking the schematic, I found a diode, SC924, between the emitter of the blanker and the emitter of video amplifier, Q902. When I disconnected one end of the diode, the locking improved. A new diode cured the problem.

(Continued on page 66)

The "New Generation" Flat-Rate Pricing...

is proving itself in thousands of shops from coast to coast—it prices your work profitably while creating customer good-will.

Fast tab indexing to 19 major repair categories prices all bench, home and over-the-counter repairs with authority.

tv & radio tech's guide to pricing

Plus, Computerized Pocket-Size Parts Catalog.

Customized to your desired parts profit. Lists over 3500 most-used parts, continually up-dated. Can easily recover initial investment in less than 30 days... \$75.00 plus \$10.00 per catalog.

P.O. Box 5234
Lincoln, NE 68505

sperry tech inc.

___ copies, Hardbound. ___ copies, Satellite
___ copies, Parts Catalog. More information
___ Amount enclosed, check or money order.
(NE res. add sales tax)

NAME _____
CO. _____
ADDRESS _____
CITY _____
STATE _____ ZIP _____

Professional
6 × 9 hard cover,
steel ring-bound
edition....
\$19.95 ea. post pd.

Satellite Edition...
the same system described
above, only reduced to
shirt-pocket size for
outside service...
\$16.95 ea. post pd.
Quantity prices available.

For More Details Circle (15) on Reply Card

we've got you covered!

Handle 90% or more of all TV antenna rod replacements with a minimum of stock! Antenna Replacement Rod Program No. 49-458 features 10 different rods with exclusive adaptor to fit 7mm and 8mm diameter rods, and precision cutting tool. Also included is a pocket-sized TV Antenna Rod Replacement Guide and Cross Reference.

TV ANTENNA ROD REPLACEMENT GUIDE & CROSS REFERENCE

Quick cross reference and replacement method guide for all popular TV antenna rods. 3-5/8" x 8" - fits in your pocket!

PRECISION CUTTING TOOL

Cuts broken antenna fast and easily.

Cat. No. 1620

UNIVERSAL TV ANTENNA REPLACEMENT RODS



PROG. NO. 49-458
(27" W x 19 3/4" H x 6 1/2" D)

COUNTER-TOP DISPLAY CONTAINS:

- 14 ANTENNA REPLACEMENT RODS - 10 DIFFERENT MODELS
- 2 ROD ADAPTORS
- 5 REPLACEMENT GUIDES
- 1 PRECISION CUTTING TOOL



GC ELECTRONICS

DIVISION OF HYDROMETALS, INC.
ROCKFORD, ILLINOIS 61101 U.S.A.



CONTACT YOUR GC DISTRIBUTOR TODAY!

For More Details Circle (10) on Reply Card

www.americanradiohistory.com

SERVICING ELECTRONIC ORGANS



Part 6/By Norman H. Crowhurst

Most modern organs have very little frequency drift, and do not require tuning at regular intervals. But, if you repair old ones as well as new models, you will need to know how to tune all types of organs. And, of course, certain component replacements make a retuning necessary for the one note that is affected. Two methods of tuning by "fifths" from the audible beats are explained thoroughly.

Tuning Electronic Organs

Many of the new organs do not require tuning in the traditional way. So, as the older organs become obsolete and disappear, the need for tuning methods or tuning machines will be gone, also.

However, with the mix of brands and models at present, the tuning of organs is a necessary part of servicing them.

There are several methods of setting the "temperament" of the notes near the center of the keyboard, without any equipment other than a tuning fork for one note, plus a timing device (stop watch, etc). Two such methods will be described.

I advise you to try these methods until you become proficient with them. When you first start tuning, probably you will take so much time that each tuning will show a loss instead of a profit. Of course, you should gain speed with practice until tuning jobs become profitable.

However, I must say that both methods require close attention and careful listening. In other words, they are tiring and time-consuming. Therefore, when your number of tunings per year increases, you will save both money and strain by buying some kind of a strobe tuning device. One such machine, the Conn Strobotuner, was described in the May, 1976 issue of

ELECTRONIC SERVICING, starting on page 12.

The exact method of tuning an organ depends on the basic design and how many tuning adjustments are provided. Some have one tuning adjustment, many have 12, and some have several dozens (even several hundred, in a complex model).

Single Master Oscillator

New "space-age" models have one master oscillator, which operates in the megahertz range. Some oscillators are crystal controlled (thus are not tunable), and others have one frequency adjustment. From this one oscillator, the count-down circuits produce the 12 tempered semi-tones. Next, from the 12 semi-tones, the lower octaves are obtained by some kind of frequency dividers.

If the master oscillator can be adjusted, you can tune the whole organ to any reasonable pitch (concert pitch, or any other that's desired) merely by turning one adjustment. An organ that is not defective moves **all** notes up or down in perfect step with the variations of the master oscillator frequency. Therefore, **you can zero-beat any note against a standard to tune the entire organ.** Obviously, the elaborate and traditional tuning procedure is not needed here!

Following the tuning (or a check of the tuning), try all the notes of the keyboards. If **any** note (or notes) is out of tune with the others, the problem is not tuning, but a defect in the count-down or divider circuits, which must be repaired.

Twelve Master Oscillators

Organs that have 12 identical circuit boards, each with one tuning adjustment, undoubtedly are of the master-oscillator/divider type. Those 12 adjustments tune the entire organ. One tunes all the "C's", the next all the "B's", and so forth.

A few models have more than one set of generators; for example, a second set tuned slightly sharp or flat to give a "celeste" effect from the beats produced relative to the main generator. In such cases, each additional generator will have 12 tuning adjustments.

When all the dividers are operating correctly, you can tune **any** 12 consecutive notes (all sharps and naturals) and the entire organ will be in tune. Of course, tuning is useless when one or more notes are silent, play an octave high, or have a gurgle. **Make certain all notes are playing correctly before you tune an organ.**

All Notes Tuned

An organ with rows and rows of tuning adjustments probably is

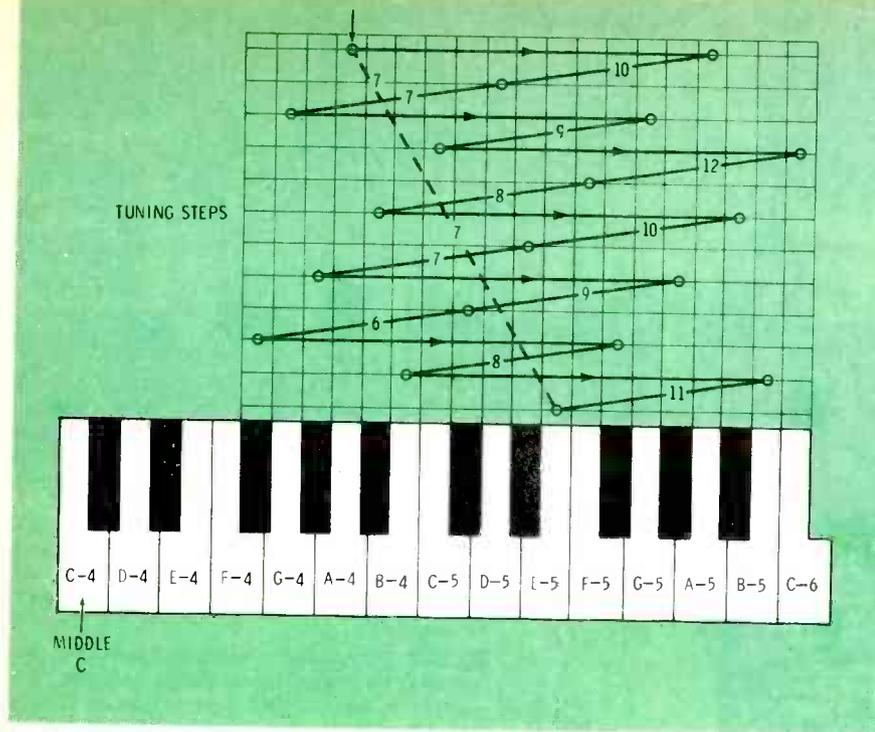


Fig. 1 Both the start and finish of this tuning method are at "A" above middle "C" (that's A-4 in universal notation). The straight lines going to the right represent tuning the higher octave to zero beat. Some of the lines that slant down to the left show two separate tuning steps. For example, the one near the top with "A-5/D-5" instructs you to play those two notes while you adjust the lower one (D-5) to obtain 10 beats (on the high side of zero beat) during 5 seconds. Then, continuing on the same line, you play "D-5" and "G-4" while adjusting "G-4" for 7 beats on the high side during 5 seconds. And so on through the chart, until you reach "E-5", which is played with the original "A-4" to see if 7 beats are obtained. If not, the sequence must be done over.

a "all-master-oscillators" type. In other words, each note can be tuned independently of all others. That sounds like a lot of hard work, but actually it's not quite that bad. After the temperament has been set near the center of the keyboard, you can tune both up and down from there by octaves. Tuning by octaves is easy.

Setting The Temperament

If the natural tuning scale were in use, you could start with one note tuned to a standard pitch, then sound the musical "fifth" above it, and tune for a zero beat. Actually, the zero beat is not between the two fundamentals, but is between the third harmonic of the first note and the second harmonic of the fifth. But in practice, the "equally-tempered" scale is used instead of the natural, and with the tempered scale, the fifth must be tuned slightly flat. This is done by counting the audible "beats".

Beats

The word "beats" is short for beat-frequency, and it is exactly the same thing in music as it is with electronics: two frequencies together in a non-linear circuit produce sum-and-difference frequencies.

In music, the non-linear element is your human ears. And the sum frequency is too high to be noticed

by most ears. But audio tones are low frequency; therefore, the difference beat between them is very low frequency.

What's more, the beat between the harmonics can be even lower in frequency; as low as one beat in several seconds.

You must train your ear to listen for these beats. First, tune the second note and listen for the beat to go faster or slower. This change of speed will help you notice the beat. A fast beat is a continuous audio tone.

As the two frequencies are moved apart, the frequency of the beat increases (higher pitch); and that is true regardless of which one moves. Conversely, the nearer you adjust the second frequency to the fixed one, the slower the beat, until at "zero beat" there is no beat at all.

A slow beat might sound like: "a-wah, a-wah". After you have heard these beats, you will not forget the sound.

Temperament is the same

Regardless of whether the organ has 12 tuning adjustments or 176, the method of setting the tuning (temperament) is the same. It's done near the center of the keyboard.

I will explain two different methods of setting the temperament. The first one counts the

number of beats in five seconds, and the second one requires you to time the number of seconds for 10 beats.

Counting Beats

Usually, an organ should be tuned to "concert" pitch, which is 440 Hz for middle "A". A tuning fork is the most inexpensive true standard, and you should invest in an "A-440" fork.

Prepare the organ by running it for several minutes, turning off the vibrato, and selecting one 8' stop, perhaps a flute or diapason. It's difficult to manage a tuning fork and play a note, so block the note down. Wedge the plastic blade of a screwdriver or an alignment tool between middle "A" and the next note, then push down on the "A" as you pull up on the other note until "A" is the only note sounding, and it stays down without any attention from you.

Next, strike one tine of the tuning fork on a piece of wood (these forks are strong, but don't overdo it), and quickly touch the fork handle to a flat surface. Without this contact, which makes the surface act as a sounding board, the fork tone will be too weak to be heard.

Slowly, tune the "A-440" organ note and listen for the beat note. Strike the fork as often as necessary

YOU CAN BE SURE

MORE TIMES IN MORE CIRCUITS WITH SENCORE DIGITAL MULTIMETERS

SENCORE

A NEW BREED OF DVM'S BACKED BY 25 YEARS OF ALL AMERICAN CRAFTSMANSHIP, WITH SIX EXCLUSIVE FEATURES, SO YOU CAN BE MORE SURE, MORE OFTEN AND ALL WITH HI & LO POWER OHMS FOR MEASURING ACCURATELY IN SOLID STATE CIRCUITS.



DVM35 \$124
3 digit LED display,
1% DCV accuracy,
battery or AC operated



15 ONE THIRD LESS CIRCUIT LOADING to make you sure that you are affecting the circuit being tested as little as possible for more accurate measurements. Sencore digitals are 15 megohm, others are 10 megohm.



2000 DCV range to make you sure that you can measure TV boost volts, scope voltages, medical equipment, etc. Other digitals stop at 1000 volts. High voltage probe extends measuring capabilities to 50 KV.



PROTECTED INSIDE AND OUT so you can be sure that your meter is working and not in the repair shop. Drop it from 10 feet, apply 1000 volts overload and even apply volts on ohms accidentally and Sencore digitals keep right on working.

to keep the tone loud. Turn the tuning in the direction to make the beat sound slower, until finally there is no beat (that's zero-beat).

Tuning fifths

As shown in Figure 1, we now jump back and forth across the middle octave, tuning for a flatted fifth. Actually, we are tuning the root note, rather than the fifth, so the root note must be tuned **sharp**. That's why the sequence calls for a certain number of beats on the **high** side.

Remember, we will be counting the number of beats in five seconds, on the high side of zero beat. I'll explain what that means. The beats become faster on either side of zero beat, but for this method the phrase "high side of zero beat" means the note you are tuning should be on the sharp (higher frequency) side of zero beat. You can hear the note as it goes sharp.

Here is the sequence:

- Starting with middle "A" (that's A-4 according to universal notation) tuned to the standard, tune the

"A" one octave above (A-5) for zero beat;

- Using this "A" as the new standard, play it and the "D" next below (D-5). While listening for the beat, tune the "D" to zero beat, then sharp for 10 beats in 5 seconds;

- Next, using the "D" as a standard, play it and the "G" below (G-4), adjusting the "G" for 7 beats per 5 seconds;

- Zero beat "G-4" with the "G" one octave higher (G-5), then play "G-5" with the next lower "C" (C-5), adjusting "C" for 9 beats on the high side;

- Using this "C" as a standard, tune the "C" two octaves above middle "C" (C-6) for perfect zero beat;

- Play this new "C" with the next "F" below (F-5), and adjust the "F" for 12 beats;

- Play the same "F" with the next lower "A#" (A#-4), and adjust the "A#" for 8 beats;

- Adjust the "A#" one octave above (A#-5) for perfect zero beat;

- Play "A#-5" with the "D#" lower

(D#-5), adjusting the "D#" for 10 beats;

- Play this "D#" with the next lower "G#" (G#-4), and adjust the "G#" for 7 beats;

- Use the "G#-4" to tune "G#-5", an octave higher, to zero beat;

- Play "G#-5" with the next lower "C" (C#-5), tuning the "C#" for 9 beats;

- Play the "C#" with the "F#" next below (F#-4) for 6 beats;

- Using the "F#" for a standard, tune the next higher "F#" (F#-5) for zero beat;

- Play the "F#-5" with the next lower "B", tuning for 8 beats;

- Tune the previous "B-4" for zero beat with "B-5", one octave above;

- Play "B-5" with the next lower "E", tuning the "E-5" for 11 beats;

- Play "E-5" with the next lower "A", and count the number of beats for 5 seconds. If every tuning step has been done perfectly, there should be 7 beats.

This "A-4" is the one used to start the tuning sequence, so it should **NOT** be adjusted to make 7 beats. However, it might have



DVM36 \$148
3½ digit LED display,
.5% DCV accuracy,
battery or AC operated



DVM32 \$198
3½ digit LED display,
.5% DCV accuracy,
battery or AC operated
with automatic battery saver



DVM38 \$348
3½ digit LED display,
.1% DCV accuracy,
AC operated, auto-ranging,
auto-zero, king size pushbuttons

ISO DCV x 2 PUSH ON

4 BATTERY SAVING FEATURES WHEN INSTRUMENT IS NOT IN USE so you can be sure that your meter will be ready the next time you need it. Push the button on the probe on the DVM35 and DVM36 and only then do you start drawing current from your battery. An automatic patented circuit does the same job for you automatically when you apply voltage to the DVM32. The DVM38 is AC operated.

TEN DAY FREE TRIAL

5 10 DAY FREE TRIAL to be sure that Sencore digitals are all that we say they are. Simply march into your Sencore distributor and ask for a free trial or pay cash with a promise of a 10 day money back guarantee, if not 100% satisfied. Or, write Sencore, and we will see that our distributor contacts you.



5 100% MADE RIGHT LIFETIME GUARANTEE so you can be sure your meter was made right. If at any time you discover that a Sencore DVM was not made right, Sencore will make it right, parts and labor free of charge, for the lifetime of the product.

Plus other "make sure" features such as - direct reading with no parallax error - no effect from magnetic fields such as motors & RF fields - lab accuracy with high resolution - auto-polarity auto-zeroing and auto-ranging on the DVM38 . . . and you can see why you can be sure more times, in more circuits, than with any other multimeter on the market today - and for less money than old fashioned analog meters.

SENCORE 3200 SENCORE DRIVE
SIOUX FALLS, S.D. 57107

For More Details Circle (11) on Reply Card

drifted during the time you were tuning; therefore, you should check it again with the original standard.

If the last test with the "E" and lower "A" gave more than 8 beats or less than 6 beats, you should repeat the entire sequence for better accuracy.

Fine-tuning the 5 seconds

In the event your tuning sequence consistently gives the wrong number of beats at the end, perhaps the 5-second counting time is slightly wrong.

The original "A" should not be changed, so you can sound the final

"A" and "E", then carefully tune the "E", noticing which way (flat or sharp) it must be tuned to achieve the required 7 beats in 5 seconds, **on the low side of zero beat.** Notice that this count is on the opposite side of zero beat, according to the way it was done previously. That's because we are tuning the **other** note of the two. This is the true fifth tuning, in which the fifth must be flatted slightly.

Now, if the beat rate is on the low side, but is too fast (say 11 beats), it proves the other beats were not quite fast enough. **Shorten the 5-second interval used for timing the beats.**

On the other hand, if the beats are on the wrong side of zero (or are on the right side, but not fast enough), it proves the beats were all slightly fast. In that case, **lengthen the 5-second reference.**

Home-Made Timer

Figure 2 shows the schematic of a simple timer you can build. The transistors can be almost any kind

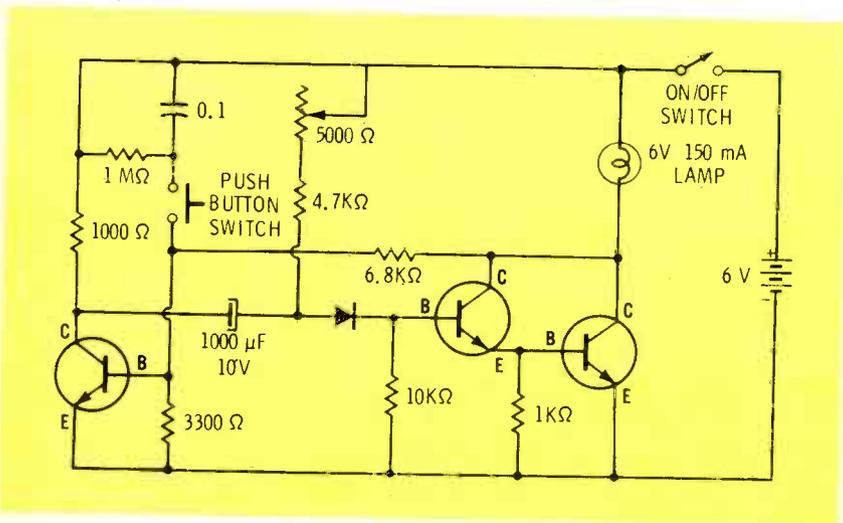


Fig. 2 This 5-second timer can be built easily, then you can fine-tune it for the precise time necessary for perfect tuning by the beats.

Upgrading MATV Systems

By Bert Wolf, Vice President of Sales, Jerrold Electronics



Many if not most of the MATV installations are in dire need of repairs and updating. Before you can bid on such work, you must know where the system is, and who to contact. Examples of direct-mail letters are given, plus many suggestions for tests and repairs of ailing MATV systems.

Just before one of the space flights, an astronaut was asked what one thing worried him most. He replied, "The fact that everything in this capsule was supplied by the lowest bidder."

Master Antenna TV (MATV) systems, too, usually are installed by the lowest bidder. If the specifications were not tight, or the inspection not made carefully, an MATV system might not have operated correctly when it was first installed. In addition, defects can occur, and the system can be tampered with. All of these causes add up to poor MATV performance, as any traveler can testify about most hotel and motel systems. Experience has shown that MATV performances in apartment houses, trailer-parks, and condominiums often fall far short of the best.

So, the need is there and you are competent (or can become so with our help) to make repairs or revisions. But how do you obtain the names on the dotted lines of the contracts? First, there must be an interest on the part of the owner or manager for better reception. Next, you need permission to make a survey. From that data, you submit a bid. Lastly, if you sell the contract, the work must be accomplished correctly.

Steps For Selling

Direct-mail messages are your best marketing tools for obtaining MATV upgrading business. If you restrict the mailing to hotels, motels, apartment houses, trailer parks, and condominiums, the list is short enough that you can cover every one in your area, without excessive cost.

Mailing lists

A complete mailing list is necessary before you have any sales

letters printed. If you have the money to hire the whole project, check with your local Chamber of Commerce or the telephone Yellow Pages for a responsible firm which specializes in direct mailings. Give such a company a sample letter, and it will handle the whole thing, for a fee.

On the other hand, if you have more time than money, make up your own list from an apartment guide (ask your Chamber of Commerce for a source); copy from the Yellow Pages; or obtain a specialized list from Standard Rate and Data Service (SRDS).

Sample letter

As long as a system operates at all, most managers will procrastinate. An added inducement is needed to get action **now**. Perhaps the most powerful pitch is to offer a "free" survey of the MATV system.

Any answer to this offer allows you to analyze the performance and layout of the system, which is the first technical step.

Figure 1 shows one suggestion for a simple sales letter. Remember the rules of good advertising; start with an eye-catching headline, then add just enough material to induce the reader to call or write you. **After** the prospect contacts you is the time to go into details. Excessive and complicated writing is likely to make the reader toss the paper in the wastebasket.

Printing

The prospect's first impression of you comes from the sales letter. So, don't risk a drab letter from your office typewriter, with the center of the "E's" and "O's" filled with ink.

Most areas have modern "instant" printing facilities for short runs at reasonable prices. Many such firms will set the message for you. This is recommended, for it

makes possible the use of different sizes of type and various styles of lettering. All of these things are important in making a good impression and maintaining the reader's interest so he **finishes** your message.

The Survey

Because you are doing the technical survey of the system performance at no-charge, you must limit the amount of time spent to perhaps 20 or 30 minutes (plus transportation). However, this time must be used efficiently; and that means planning and preparedness before the call.

A chart form, as shown in Figure 2, is essential for recording data about signal strength and picture quality of each individual channel.

Of course, an accurate, portable Signal-Strength Meter (Figure 3) is required for testing the levels, and a small battery-operated TV receiver enables you to see the picture quality.

Check the headend

Start with the signal at the output of the headend amplifiers. Check and record on the chart the signal levels of both picture and sound carriers of each active channel. And then, through a suitable attenuator needed to prevent overloading the TV used for testing, check the picture quality of all channels, using the portable TV.

Next, check the outputs of any splitters at the headend. It isn't necessary to record the sound and picture levels of all channels. Just measure the picture carriers of the highest channel and lowest channel carried by the system.

Quality at a TV

If at all possible, you should check the visual quality of all channels at a typical receiver, and record your comments on a form.

Better TV equals *Happier Tenants!*

Sharp, steady TV pictures can help your tenants or guests to be happy with life, and satisfied with your facilities. On the other hand, ghostly, jumping, and blurred pictures contribute to their dissatisfaction.

That's why the Master TV antenna system for your building is so important to *your* long-range profits.

If the picture quality from your antenna system is imperfect, contact me for a no-charge, no-obligation checkout of your installation. After my inspection (using precision test equipment), I will submit quotations for any needed repairs, and for additional equipment to improve on the original performance.

Also, we can install security cameras, or time-weather-music channels, and provide yearly maintenance contracts to free your mind of any possible repair expenses.

Call me today, or return the enclosed reply card for prompt action.

Cordially,

(your name and title)
(address, city, and zip)
(phone number)

(Note: the word "tenants" can be changed to "guests" when the letter is sent to hotels and motels.)

A

B

Fig. 1 Here is a suggestion (A) for sales letters to owners/managers of hotels, motels, apartments, trailer parks, and condominiums. If you change the wording, remember to keep it interesting and brief. Make this first contact a "soft sell". (B) shows a suggestion for a reply card.

Dear Mr. (your name):

Yes, I would like to have more information about the master TV antenna services you offer.

Please call to discuss our antenna needs.

Please make a no-charge, no-obligation survey of the antenna system

at _____
(address, city, state, ZIP)

Signed _____

Title _____ Phone _____

Company Name _____

Address _____

City _____ State _____ ZIP _____

It's very possible for the signal to be fine at the head end, but be unacceptable at the end of a cable run.

Problems

If you spot a trouble with the signal, you should take a few minutes to localize the source. A final, precise diagnosis is not necessary at this time, but it is helpful to know which branch or amplifier has the problem.

Estimates

After the survey is complete, it should be easy to make an estimate. Actually, you should make **two** estimates: one for the cost of **restoring** the system to the **original** performance; and the second for making the system work right, that is, **better than it was originally**.

For example, suppose the survey showed that one trunk line was dead because of a defective splitter. The first estimate should include the cost of a new splitter and labor.

However, the second estimate might recommend replacing the old headend amplifier with a new-type solid-state unit, adding a pre-amplifier to boost a weak channel ahead of the main amplifier, adding a UHF channel, wiring in filters or traps to minimize interference, or adding a closed-circuit TV and background music channel.

Make your proposals in writing, attaching a copy of the survey results as proof. **But do NOT mail these papers!** Deliver them in person, direct to the owner or manager. That way, you can sense the attitudes, and know when to add technical data or present the practical benefits of the technical suggestions.

Frequent MATV Troubles

In most cases, you must assume that the MATV system worked fairly well when it was first installed. Otherwise, the contractor would have had trouble collecting for it. (Of course, there are exceptions, where the installer was more glib than skillful. This possibility must be kept in mind.)

Therefore, you look primarily for troubles that develop with the passing of time. A knowledge of typical defects helps to identify the problems. Here are some possibilities:

- **AC Hum.** Hum appears on the TV screen as one or two horizontal dark bars, which usually move slowly upward. One hum bar indicates 60-Hz hum from a leaky tube or a defective half-wave power supply; two bars indicate 120-Hz hum, which can originate only from a full-wave power supply. If the hum shows on all TV sets connected to the system, it's certain the defect is in the MATV. Hum on one TV only indicates a fault in that TV.

- **Rolling Picture.** If the rolling is with only one channel, the cause usually is sync compression in a single-channel amplifier. Aging of the components might have decreased the AGC action, thus increasing the gain. Use the manufacturer's procedure for resetting the AGC. Of course, if the amplifier is tube-powered or without AGC, you might suggest a new solid-state replacement.

- **Cross Modulation.** Grainy pictures, perhaps with "windshield wiper", indicate excessive gain in a broadband amplifier. A maintenance man or tenant might have reset the gain, or the amplifier could have aged. Reset the levels, and add filters or traps as required.

- **Ghosts.** It's not unusual for a tenant to compensate for a bad tuner in his TV receiver by shorting out the isolation in the tap-off. This might help his picture, but it would add ghosts to other sets on the same trunkline. Another common problem is caused when a landlord or supervisor has added cable to the line. If this is done without the proper termination (75-ohm non-

inductive resistor), standing waves (which resemble ghosts on the screen) are created.

- **Snow.** If snow can be seen throughout the entire system, suspect the amplifier first. Replace the tubes, or substitute a higher-gain modern solid-state amplifier. A broken downlead between the antenna and amplifier, water in a splitter or tap-off, or a new building which shields the signal path all can cause snow.

Old Problems

After you have repaired all the defects that were not present when the system was new, the picture quality still might be poor on some channels. The following are some common deficiencies.

Ghosts and smear

True ghosts are caused by multipath. That is, part of the station signal goes direct to the receiving antenna, while another part goes in another direction, is reflected by some object, and finally reaches the antenna, but at a later time. Because the CRT beam is traveling to the right, this signal that arrived later appears to the right of the main one.

Misunderstandings arise, sometimes, about the distances involved with ghosts. A mountain 5 miles to the side makes a ghost that's displaced about 8 inches to the right of the main picture on the screen of a 21-inch receiver. A ghost reflected from a watertower 400 feet behind the antenna would be seen only 1/4-inch to the right. Such a "close" ghost would appear

MATV Survey			
Channel Number	Picture Carrier Level	Sound Carrier Level	Picture Quality
_____	_____	_____	_____
_____	_____	_____	_____
_____	_____	_____	_____
(etc.)			

Fig. 2 Make up a survey sheet, such as this, for the level data.

Five big reasons to buy the RCA test jig.

1. When you buy the RCA 10J106, you get a color TV test jig complete with a 19-inch picture tube for servicing almost all TV consoles.

2. RCA's up-to-date line of optional accessories permits you to service sets of 45 different makes: tube, hybrid, solid-state, or PIL types.

3. With its high-quality construction, built-in, high-voltage meter, safe operating capability to 33kV without the use of costly voltage limiters, and a set-up data subscription service, the RCA 10J106 is designed to give you years of dependable service.

4. Unique with the 10J106 system are two front-panel switches for quick changing of yoke impedances for almost any type of tube or solid-state set. These switches eliminate the need to plug in external transformers and impedance-matching devices.

5. A built-in, high-voltage meter, calibrated to 35kV, together with adequate shielding and picture-tube design, permit measurements to 33kV without danger from x-ray radiation. Allows you to service all of the bigger chassis that normally operate in excess of 30kV.



These are only a few features of the high-quality RCA 10J106 Color TV Test Jig. For details and price information, see your RCA Distributor. Or contact RCA Distributor and Special Products Division, Deptford, N.J. 08096, attn: Sales Promotion Services.

as ringing, or perhaps as a smear.

Certain kinds of multiple, closely-spaced ghosts are seen as a smear, not as ghosts. They are difficult to analyze sometimes, because they are similar to the smear produced by a misaligned single-channel amplifier.

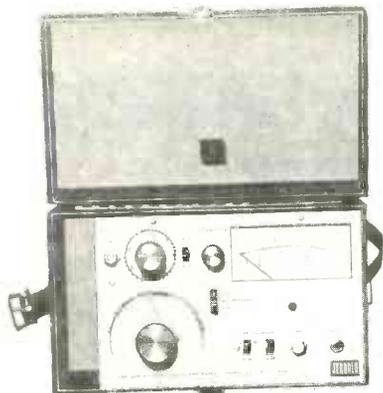


Fig. 3 A professional signal-strength meter which can measure the amplitude of both picture and sound carriers of all VHF and UHF stations is a necessity for upgrading MATV systems

A mismatched coaxial cable (perhaps from a crushed cable, or a missing termination resistance) produces ghosts from standing waves, where the signal bounces from one end of the cable to the other, and with each bounce adding a ghost. Incidentally, this is the same effect as a defective delay line (or wrong delay-line load) in a color receiver.

MATV systems slow down the passage of the signals; therefore, any pickup of signal that does not travel through the system shows as a ghost to the left. If the cable path is less than about 200 feet, the ghosts from the direct signal will be seen as a smear.

The solution to the problem of ghosts coming through the antenna is to obtain antennas with a narrow forward lobe and weak side and rear lobes. Then, find the best position, height, and directional orientation for them. Sometimes, it helps to stack two identical antennas horizontally (side-by-side); this cancels the signal at certain angles. The cancellation depends on the distance between the antennas,

so you must experiment to find a distance that cancels the ghost. Aim both antennas directly at the transmitting tower. Watch the picture on a TV set while you move the two antennas closer or farther apart. The spacing is right when the ghost is minimized.

Multiple ghosts in one leg of a system could be caused by a partial short that changed the loading. A short caused by a single strand of loose cable shielding at a connector will do it. Also, a loose connector, a nicked or broken center conductor, or an open circuit has the same effect. One way of finding the section with the short or open is to insert a 6-dB loss pad into one line at a time. The attenuator improves the match of one line and isolates any short from the others. So, when the attenuator pad improves the picture quality, it's likely a defect is in that section of the cable.

Some MATV systems have 300-ohm outputs inside the wall tap-offs. This eliminates a matching transformer at the TV, but it leaves a length of unshielded twin-lead

... And, here are 50 more!

\$50

\$50

\$50

worth of 10J106 Test Jig Accessories FREE

When you buy the RCA 10J106 Test Jig now through December 31, 1976, you can select, free, up to \$50 worth of adapters and extensions from the full line of available accessories.

All you do is send the following to RCA D&SP, P.O. Box 100, Deptford, N.J. 08096, attn: Customer Service/Order Processing:

Original proof of purchase (receipt, invoice or statement) which includes date of purchase, stock number of

Test Jig, and name of RCA Distributor. Filled out Purchase Registration Card. Order for your choice of free accessories (not to exceed \$50 at suggested resale prices), which will be sent direct to you by RCA.

To select your free accessories, check the list included in the "Set-Up Index" booklet which comes with the Test Jig when you buy it, or consult with your RCA Distributor on selection and prices.

This offer expires December 31, 1976. So don't delay. Buy a 10J106 Test Jig soon!



\$50

RCA Color TV Test Jig

\$50

between the wall and the TV receiver. The twin-lead can pick up a signal (in strong-signal areas), causing a leading ghost. Other than changing to a coaxial cable system with a matching transformer at the TV, the only solution is to increase the signal strength at each tap-off, perhaps by a more powerful head-end amplifier.

Radio interference

Radio carriers of lower than 50 MHz can enter a MATV system in two general ways. First, any harmonics of the radio transmitter are received the same as any other signal of that frequency, mixing

with the TV carriers and producing various kinds of beats. Usually, the radio carrier must be very strong (high power or very near) for this to occur.

Or, radio signals of very high intensity can overload a MATV amplifier. The overload causes non-linearity, and the radio signal modulates the TV signals.

Sometimes, you can identify the offending signal by tuning the signal-strength meter for maximum on the interfering signal, and then listening with earphones to hear what modulation is on the carrier.

A sub-channel/TV splitter added between the antenna lead and the

first amplifier might help by reducing all frequencies below 54 MHz.

In some cases, filters or traps are required. **Remember, any traps or filters must be inserted before the first amplifier stage.**

FM interference

FM interference most often appears as a herringbone pattern that moves with the modulation.

Minimize FM interference by inserting either a single-frequency trap or an FM band-rejection filter before the first amplifier. The trap provides much more attenuation, but it must be adjusted for each station, and it tends to drift. Band-rejection filters give less attenuation, but do not drift. Therefore, use a band-rejection filter, if it reduces the interference enough.

Electrical interference

Arcs from power lines or inside defective equipment cause electrical interference which covers all frequencies, but is stronger at the low frequencies. UHF reception seldom



Fig. 4 New solid-state UHF broadband amplifiers, such as this Jerrold Model UA-421, allow adding UHF channels to older MATV systems.

is bothered by such interference.

Although the appearance on a TV screen often is different, depending on the source, generally the interference appears as many tiny black dots or dashes. Sometimes these black specks are random, but others are found together in horizontal bars, which move up or down slowly.

Noise pulses from vacuum cleaners, mixer, or other brush-type motors usually are random, and the source can be identified by turning

them on and off as a test (the motor is very near, perhaps in your own home).

Interfering noise that occurs in regular cycles might be from some machine controlled by a thermostat. Furnaces, air conditioners, and refrigerators are possibilities, although those motors don't make noise unless there's a defect.

Arcs in the power lines or transformers are hard to identify. The power-company men don't know how to find the defect unless it

burns up something or affects the flow of power. Direction-finding with portable radios is frustrating because the noise follows the power wires and radiates from every wire and pole.

Ignition noise

Ignition noise from trucks and autos looks very much the same as some kinds of random power-line noises. Sometimes the solution for both ignition and power noises is to increase the signal in the MATV

Fig. 5 Another way of adding UHF to MATV systems which are inefficient on UHF frequencies is to convert each UHF channel to a VHF channel, before it's fed into the system.


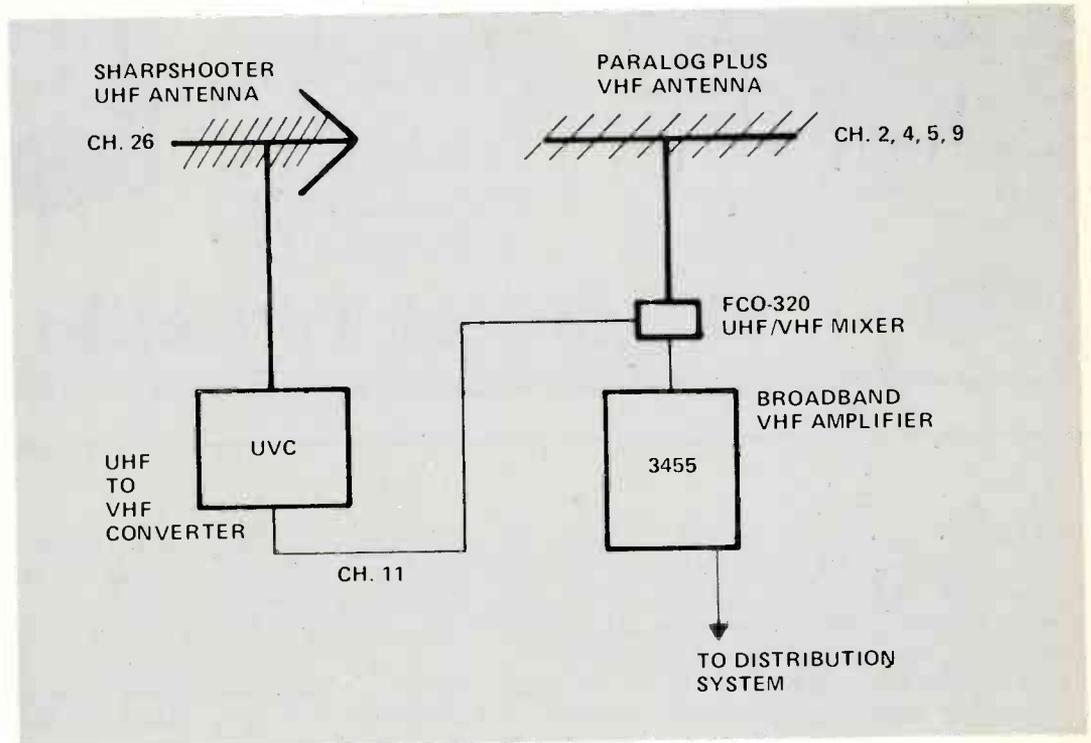


Fig. 6 Closed-circuit TV cameras can be included by having each one modulate a "Uni-Mod". The output is a VHF channel which is added to the other VHF signals at the head-end amplifier. Each camera then is tuned-in the same as a conventional TV station.

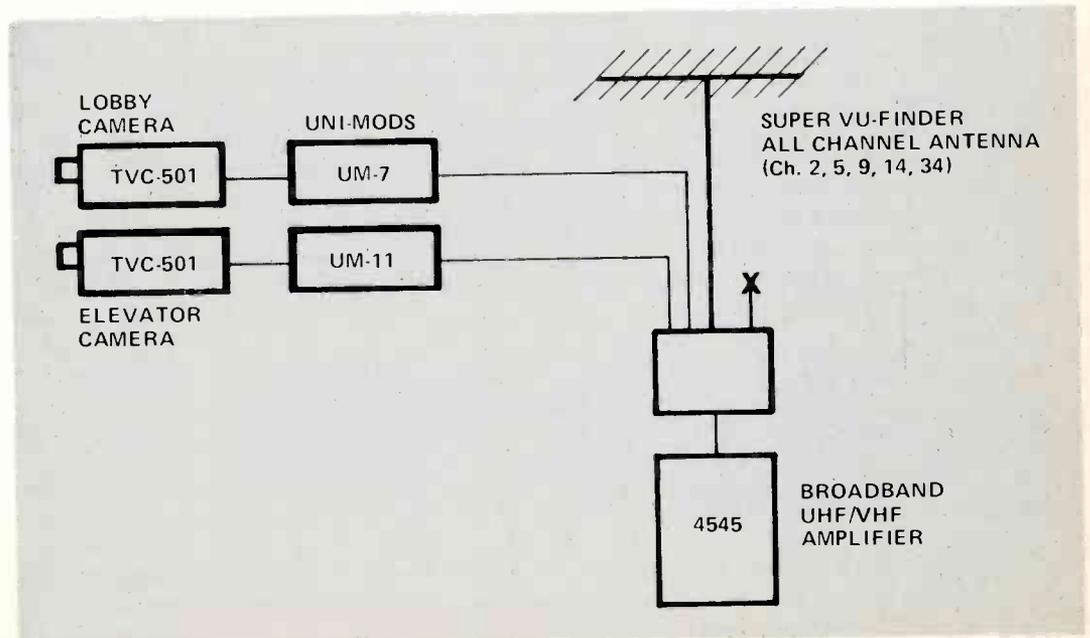

system so it overrides the noise.

Better antennas, perhaps with vertical stacking, and higher-gain amplifiers often help cover the noise. 300-ohm twin lead between the tap-off and the TV should be replaced by a shielded 75-ohm cable with matching transformer. Of course, this solution is not practical for an entire system, but it's suggested where the noise affects only a few TV's.

Converter interference

In many MATV systems, the UHF channels are converted to the frequencies of unused VHF channels. Signal losses in the coaxial cable are reduced at VHF frequencies, so lower-gain VHF-only amplifiers can be used. This can be a substantial saving on a large system.

The tradeoff is the possible interference to other channels caused by radiation from the local oscillator in the UHF converter. Although the best converters are crystal-controlled, either kind can cause problems. With crystal control, the interference is stable; and with other oscillators, the interference pattern changes with the drift.

It's very difficult to calculate all of the possible beats from converters, but the test for interference is easy: just unplug the power cable to the converter (or each converter in turn) and notice if the beat pattern is missing.

A radiating converter can be isolated by placing it in a separate shielded housing. Sometimes, rebalancing the levels will eliminate the interference; it's worth a try.

Modulators can cause beats in the same way, and the cures are the same.

Overload

Too much signal creates as many problems as produced by too little, because of overload. Of course, overload bothers only active components, such as preamplifiers, amplifiers, and TV receivers.

Overload of single-channel amplifiers weakens the sync by compressing it. Often the largest symptom is critical vertical locking on that one channel. Eliminate the overload by adjusting the AGC, reducing the gain setting, or adding a loss pad at the input signal.

Broadband amplifiers produce cross-modulation distortion when overloaded. Strong channels modulate weaker ones, although the symptoms vary according to the severity of the overload. A slight overload causes a small constantly-changing beat pattern, or a kind of grainy look. Strong overload shows a "windshield wiper" pattern: the modulating-station picture can be seen behind the desired picture. Less severe overload might appear as a tiny beat pattern and a dark vertical bar that moves slowly to one side.

It's more difficult to eliminate overload in broad-band amplifiers. The most important remedy is to balance carefully the levels of all the channels, making sure one is not dominant. Single-channel filters or frequency splitters might be added before the amplifier. Or separate yagi antennas with individual pads might be used in extreme cases.

Adding UHF or CCTV

UHF channels can be added to a VHF MATV system by either of two ways. If the splitters and tap-offs can pass UHF, an all-channel antenna and a UHF broadband amplifier is the best bet (Figure 4).

But if the system is so old that the cable, splitters, and tap-offs give excessive UHF loss, it's better to add a UHF antenna and converter, as shown in Figure 5.

Modern apartment buildings are concerned about security of the tenants, and a Closed-Circuit TV (CCTV) camera placed in the lobby and elevator can be installed without great expense. Add a Jerrold UNI-MOD for each camera, and feed the signals into the MATV system (Figure 6).

Comments

Modern MATV equipment and techniques now permit good-quality TV signals in most locations. Many systems are working poorly, and the owners and managers only need some reminders to have their systems upgraded. That's where you can make money and do them a favor, too.


Make up your sales letters, distribute them, and start making your share of the MATV profits. Now!

ARROW AUTOMATIC STAPLE GUNS

CUT WIRE & CABLE INSTALLATION COSTS

... without cutting into insulation!

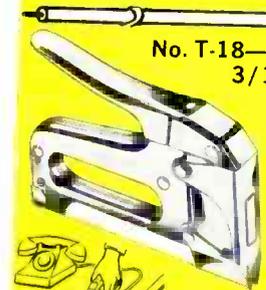SAFE! Grooved Guide positions wire for proper staple envelopment! Grooved Driving Blade stops staple at right depth of penetration to prevent cutting into wire or cable insulation!



No. T-18—Fits wires up to 3/16" in diameter.

BELL, TELEPHONE, THERMOSTAT, INTERCOM, BURGLAR ALARM and other low voltage wiring.

Uses T-18 staples with 3/16" round crown in 3/8" and 7/16" leg lengths.



No. T-25—Fits wires up to 1/4" in diameter.

Same basic construction and fastens same wires as No. T-18.

Also used for RADIANT HEAT WIRE

Uses T-25 staples with 1/4" round crown in 9/32", 3/8", 7/16" and 9/16" leg lengths.




NEW! Intermediate No. T-37—Fits wires and cables up to 5/16" in diameter.

Same basic construction as Nos. T-18 & T-25.

Also used for CATV and DRIVE RINGS in stringing wires.

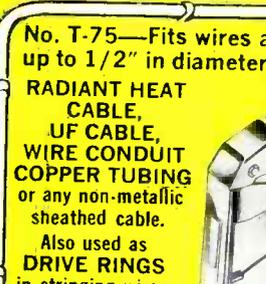Uses T-37 staples with 5/16" round crown in 3/8", 1/2" and 9/16" leg lengths.



No. T-75—Fits wires and cables up to 1/2" in diameter.

RADIANT HEAT CABLE, UF CABLE, WIRE CONDUIT COPPER TUBING or any non-metallic sheathed cable.


Also used as DRIVE RINGS in stringing wires.

Uses T-75 staples with 1/2" flat crown in 9/16", 5/8" and 7/8" leg lengths.

ARROW FASTENER COMPANY, INC.
271 Mayhill Street, Saddle Brook, N. J. 07663

For More Details Circle (12) on Reply Card

Fig. 1 In the GE 19YC2 chassis, the vertical oscillator transistor is reverse biased when power first is applied. The base voltage arrives at once, but the emitter voltage is delayed by the large time-constant R/C circuit. When the emitter positive voltage finally exceeds the base positive voltage, Q610 has forward bias, causing the collector to conduct through resistor RB (actually the next stage) and discharging C616 (shown by SW1). Two other signals at the base reduce the positive voltage (increasing the forward bias). The sync signal fires the oscillator ahead of time, for locking; and the regenerative signal causes a stronger collector current for a short period of time before C616 is discharged and conduction stops until the next cycle.

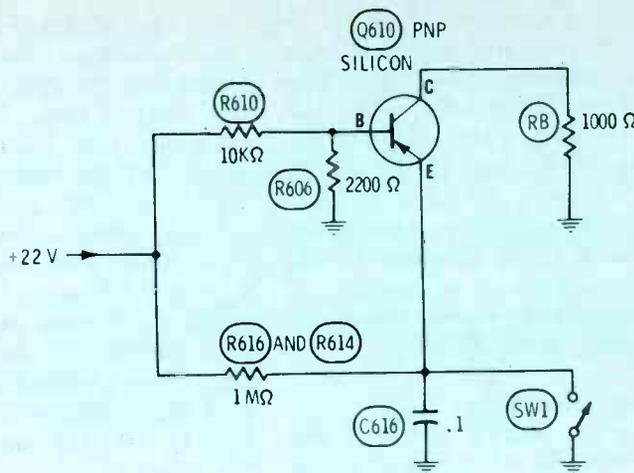

Servicing GE Modular Color TV

Part 4/By Gill Grieshaber, CET

Power supplies of two polarities for the vertical sweep come from rectification of horizontal signals. Also analyzed are other unique features and circuits of the vertical sweep in the 19YC2 General Electric solid-state, portable color-TV.

Vertical Sweep Of GE 19YC2

Although the vertical-sweep circuit of the GE 19YC2 has some superficial similarities to both the Zenith and RCA circuits previously examined in this series of articles, there are some unique differences.

The YC2 has an oscillator circuit using a PNP and an NPN transistor, without any feedback from a later stage, and so does the 19EC45 Zenith circuit. Feedback from the output stage is necessary in the RCA CTC58 to make the single

switch-transistor oscillate.

Both the RCA and the Zenith employ complementary-symmetry output stages with one PNP and one NPN power transistor. However, the RCA has a single power source and an output-coupling capacitor to the yoke. The Zenith uses two power supplies to create a zero DC output voltage, and it doesn't require a capacitor to couple to the yoke. Refer to the April, 1975 issue of ELECTRONIC SERVICING for an explanation of the RCA vertical circuit, and to the December, 1975 issue of ELECTRONIC SERVICING for an explanation of the RCA vertical circuit. A comparison of the three circuits is both interesting and informative.

This GE vertical output stage has two NPN-polarity power transistors, thus an extra phase inverter-driver is required. Two power supplies are furnished, one positive and one negative, and the output signal has practically no DC component, making a yoke-coupling capacitor unnecessary.

Vertical Oscillator

The vertical oscillator circuit is very uncomplicated, operating with one PNP and one NPN silicon transistor. One result of this selection is that both transistors draw current at the same time, in

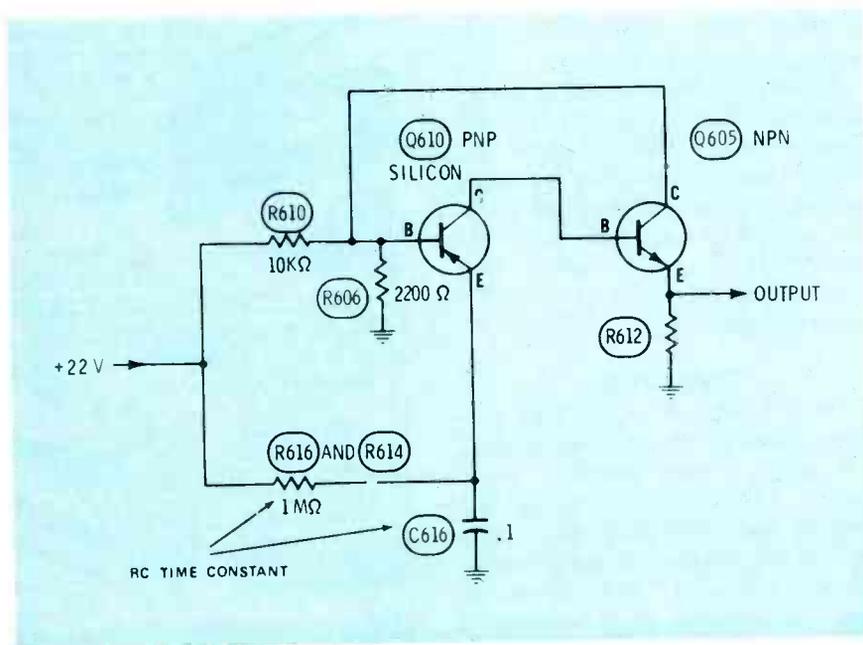


Fig. 2 Q605 acts as a switch to reduce the Q610 base voltage when Q610 collector current flows, thus increasing the Q610 current and depleting the charge in C616 more rapidly and completely. The circuit is a variation of a multivibrator, but the two transistors conduct at the same time in narrow pulses of current, and not alternately as is conventional.

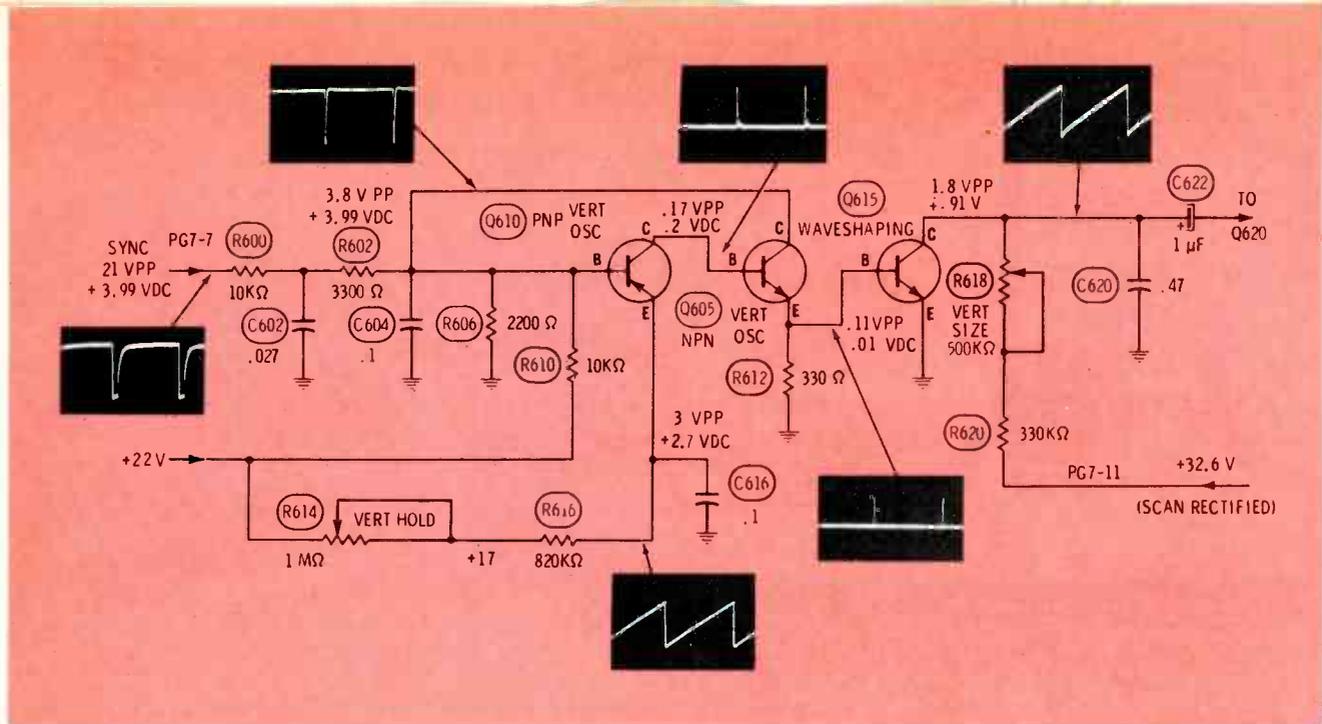


Fig. 3 Voltages and waveforms have been added to the schematic of the oscillator and sawtooth-shaping stages. All three transistors are direct coupled. The vertical-hold control changes the time constant in the emitter circuit of Q610. By the way, the "vertical size" control changes the amplitude of the sawteeth because of the variation of time constant, and not because of any change of DC voltage at the collector of Q615.

contrast to a multivibrator which has the transistors conducting alternately. Also, these two transistors oscillate by themselves: they do not require any feedback from a subsequent stage. Even though the circuit is simple, it is easier to understand when analyzed in two steps.

Bias by time constant

Figure 1 shows only the main wiring of Q610, the PNP oscillator transistor.

When DC power first is applied to Q610, the transistor is cutoff by a strong reverse bias. (Remember that transistor bias is base-to-emitter, and not base-to-ground.) A voltage divider having a very short time constant applies about +4 volts to the base. At first, the emitter has zero voltage, because the voltage must travel through R614/R616 and charge C616 before the emitter voltage can rise. And until the emitter voltage becomes more positive than the base positive voltage, the B/E junction is reverse biased (the base must be less positive than the emitter for the bias to be forward).

Finally, after a time determined by the time constant of R614/R616 (about 1 megohm) and C616 (0.1 microfarad) versus the amount of

supply voltage, the emitter positive voltage finally rises above the base positive voltage. The transistor now has forward bias, and the emitter/collector current flows to ground through the collector load.

If there were no more to the circuit, the emitter voltage would stabilize. But with the next stage added, a "snap" action (type of regeneration) suddenly increases the forward bias, and the stronger emitter/collector current discharges C616.

SW1 is not in the circuit, but was shown to simulate the way Q610 E/C current discharges C616; and the resistance RB actually is the B/E resistance of the next transistor.

Regeneration

Adding a few more components (Figure 2) increases the Q610 current, and shortens the time the current flows. It does this by decreasing the positive base voltage (more forward bias), the extra emitter current bleeds C616, and the low emitter voltage is reversed bias, which turns off the C/E current of Q610.

Q605 is used as a switch, which reduces the base voltage of Q610 when it conducts. Also, Q605 acts as an emitter follower to couple the

pulse signal to the next stage.

Here is the sequence, after Q605 has been added:

- At turn-on the base voltage of Q610 rises immediately to about +4 volts, but the emitter voltage increases more slowly, because of the RC circuit;
- Therefore, at first there is no Q610 conduction, but eventually the emitter voltage rises above the base voltage (forward bias), and Q610 begins to draw C/E current;
- The collector current of Q610 flows to ground through the B/E junction of Q605;
- This B/E current causes Q605 to conduct C/E current, and the collector obtains the required positive voltage from the base of Q610;
- In turn, the Q605 collector current reduces the positive base voltage of Q610. This is a large increase of forward bias (for a PNP), and Q610 conducts much more;
- The large Q610 current comes from the charge stored in C616, and the charge rapidly is drained until (when about one-third remains) the emitter drops below the base voltage, removing the forward bias and stopping the conduction. Therefore, the Q610 current has the waveshape of a very narrow pulse;
- Discharge of C616 is through the

There is only
one
2-WAY
RADIO
HOME
STUDY
COURSE
exclusively devoted
to professional FM radio equipment

We don't know how many
TV repairman or
other people there are
in electronics
who would like to move up to
professional FM two-way radio.

Nor do we know how many
servicemen and installers
there are
already in the field
who want to expand
and upgrade their knowledge.

But we do know how many
home study schools
cater exclusively
to both these groups

ONE!

Please send me more information.

Name _____

Address _____

Code _____

- I am a former MTI student.
 I am presently in the military.
 I am a veteran. Y8



Formerly

MOTOROLA
TRAINING INSTITUTE

Summerdale, PA 17093

(717) 732-3636

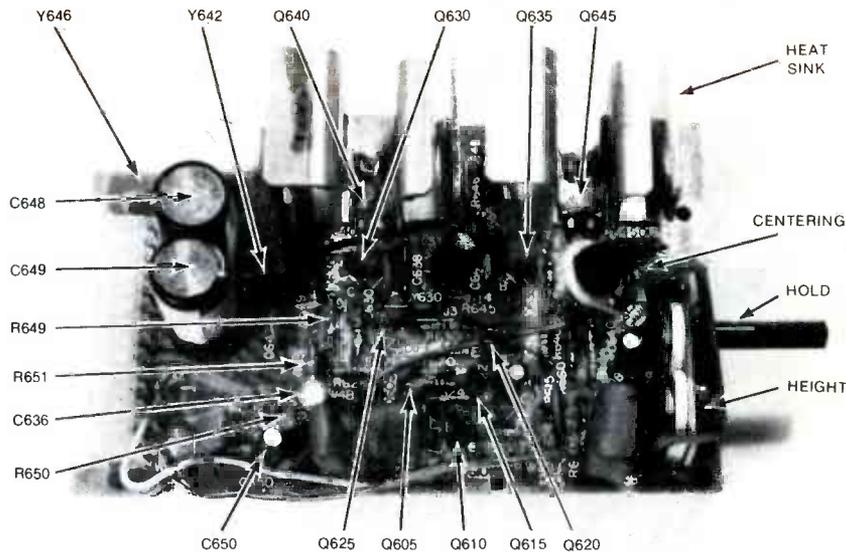


Fig. 4 Many components on the EP93X103 GE vertical module are identified.

C/E path of Q610, base-to-emitter of Q605, and R612 (the emitter resistor of Q605), which is another reason that C616 does not discharge to zero voltage; and

- Vertical sync also is applied to the base of Q610. It is negative-going, and triggers conduction just before the oscillation otherwise would occur.

Therefore, this two-transistor oscillator circuit operates at 60 Hz (determined by the sync and the time constant of the components in the emitter circuit of Q610, which includes a variable vertical-hold control). The output waveform is a series of narrow, positive-going pulses.

Sawtooth shaper

The complete vertical-oscillator schematic is shown in Figure 3, plus the waveshaping stage using Q615, along with the important waveforms.

Positive-going vertical pulses (with the baseline at zero) are the sole forward bias of Q615, an NPN-polarity silicon transistor.

Of course, normally the collector signal would be amplified negative-going pulses, because of phase inversion in Q615. But these pulses are integrated into sawteeth by R618/R620 and C620. Then, C622 couples the sawteeth to the next stage.

A better way of describing the

integration is to say that Q615 acts as a switch. Conduction of Q615 discharges C620 (notice the zero line in the waveform, at the bottom tip), then C620 starts the textbook charging curve, which is interrupted (before it reaches the rounded non-linear portion) by the next conduction of Q615, bringing the voltage to zero again.

It is interesting to note that, although the waveshape is a good basic sawtooth, the current of Q615 remains a pulse shape.

Many of the components on the vertical module are pointed out in Figure 4.

Vertical Drivers And Outputs

The remainder of the vertical-sweep schematic (Figure 5) strongly resembles that of many conventional audio power amplifiers.

There is one major difference: feedback from the yoke **current** improves the linearity automatically, so no linearity control is necessary (Figure 6). Low end of the yoke goes to ground through R642 on the module. Voltage developed across the resistor goes through C636 and R636 to the base of Q625, the differential amplifier.

Operation of the two "differential" amplifiers seems rather mysterious, even with the waveforms, and needs some explanations.

Differential amplifiers

Although Q620 and Q625 are

drawn to resemble a classic differential stage, the circuit is not exactly a differential stage. Output is taken from **one** collector only.

Perhaps we should view Q620 as having two input signals, one to the base (it appears amplified and inverted at the collector), and another to the emitter (this one appears amplified at the collector, but not inverted). Also, Q625 is an emitter follower, with input at the base, and the non-inverted output taken from the emitter. This signal is connected to the emitter of Q620, where it is the second input signal.

In summary, the signal at the base of Q620 appears phase inverted at the collector of Q620, while the signal at the base of Q625 appears at the collector of Q620 not phase inverted. **The two signals subtract from each other!** If they were identical, the output would be zero.

But they are not identical. The major difference is in the rise time, and there are some differences of amplitude and linearity, also. Therefore, the signal at Q620's collector has been **pre-distorted** to cancel subsequent opposite distortion occurring later. That's why the waveform is so different from the sawteeth we would expect.

Figure 7 shows the actual Q620 input waveforms and the result of subtracting in a scope by inverting the base waveform and adding them. The resulting waveform consisted of positive-going pulses, and that's the waveform found at the collector of Q620, except for the tiny sawteeth between each pair of pulses.

Output-drive waveforms

From the preceding, you probably conclude logically that the output of Q630 driver should be negative-going pulses (Q630 inverts the polarity). Not so. You see, Q630 is a PNP, so the positive-going base pulses are in the cutoff direction. Therefore, most of the pulse amplitude is clipped, leaving amplified sawteeth. However, the B/E conduction of the output transistors leaks some of the yoke flyback pulses and the "butterfly wings" from the pinchion circuit. In fact, the base signal of Q640, the NPN output transistor, is virtually identical in waveform to that of the sweep-output signal as its emitter.

Statement of Ownership, Management and Circulation, Act of August 12, 1970; Section 3685, Title 39, United States Code.

1. Title of Publication: Electronic Servicing
2. Date of Filing: September 30, 1976
3. Frequency of issue: Monthly
- 3A. Annual subscription price: \$6.00
4. Location of known office of publication (Street, city, county, state, zip code): 9221 Quivira Road, Overland Park, Johnson County, Kansas 66215.
5. Location of the headquarters or general business offices of the publishers (not printers): 1014 Wyandotte St., Kansas City, Jackson County, Missouri 64105.
6. Names and addresses of publisher, editor, and managing editor: Publisher, Robert E. Hertel, 1014 Wyandotte St., Kansas City, Missouri 64105; Editor, Carl Babecke, 1014 Wyandotte St., Kansas City, Missouri 64105.
7. Owner (if owned by a corporation, its name and address must be stated and also immediately thereunder the names and addresses of stockholders owning or holding 1 percent or more of total amount of stock. If not owned by a corporation, the names and addresses of the individual owners must be given. If owned by a partnership or other unincorporated firm, its name and address, as well as that of each individual must be given.) Howard W. Sams & Co., Inc.—a wholly owned subsidiary of International Telephone and Telegraph Corporation, 320 Park Ave., New York, New York 10022.
8. Known bondholders, mortgages, and other security holders owning or holding 1 percent or more of total amount of bonds, mortgages or other securities (If there are none, so state): None.
9. Paragraphs 7 and 8 include, in cases where the stockholders or security holder appears upon the books of the company as trustee or in any other fiduciary relation, the name of the person or corporation for whom such trustee is acting, also the statements in the two paragraphs show the affiant's full knowledge and belief as to the circumstances and conditions under which stockholders and security holders who do not appear upon the books of the company as trustees, hold stock and securities in a capacity other than that of a bona fide owner. Names and addresses of individuals who are stockholders of a corporation which itself is a stockholder or holder of bonds, mortgages or other securities of the publishing corporation have been included in paragraphs 7 and 8 when the interests of such individuals are equivalent to 1 percent or more of the total amount of the stock or securities of the publishing corporation.
10. This item must be completed for all publications except those which do not carry advertising other than the publisher's own and which are named in sections 132.231, 132.232, and 132.233, postal manual (Sections 4355a, 4355b, and 4356 of Title 39, United States Code.)

	Average No. Copies Each Issue During Preceding 12 Months	Single Issue Nearest To Filing Date
A. Total No. Copies Printed (Net Press Run)	70,812	73,000
B. Paid Circulation		
1. Sales through dealers and carriers, street vendors and counter sales	3,485	3,541
2. Mail Subscriptions	63,931	63,420
C. Total Paid Circulation	67,416	66,961
D. Free Distribution (in- cluding samples) by Mail, Carrier or Other Means	1,102	609
E. Total Distribution (sum of C and D)	68,518	67,570
F. Office Use, Left-Over, Unaccounted, Spoiled after Printing	2,294	5,430
G. Total (sum of E and F— should equal net press run shown in A)	70,812	73,000

I certify that the statements made by me above are correct. (Signature of editor, publisher, business manager, or owner).

ROBERT E. HERTEL



CASTLE Timesavers
... for the Professional

SUBBER® signal circuit analyzing
Instruments

* Made in USA

Mark V



Mark IV-CUV



Mark IV-C



Ask your electronic distributor for them
... or write for more details.

CASTLE ELECTRONICS, INC.

5701 N. Western Ave., Chicago, Ill. 60645

• Ph. (312) 728-1800

In Canada: Len Finkler Ltd., Ontario

For More Details Circle (24) on Reply Card

APPLIANCE REPAIR BOOKS

Written in easy-to-understand language by experts with illustrations & diagrams. Acclaimed by instructors & professionals. How to diagnose & repair air conditioners, refrigerators, vacuum cleaners, ranges, washers, dryers, steam irons, portable kitchen appliances, water heaters; plus how to set up a shop, using test instruments and more. Only \$2.95 to \$4.90 each!

SEND FOR FREE DESCRIPTIVE PRICE LIST

C & N, DEPT. ES, 5841 MONTROSE, CHICAGO 60634

For More Details Circle (25) on Reply Card

FREE CATALOG

HARD-TO-FIND PRECISION TOOLS

Lists more than 2800 items: pliers, tweezers, wire strippers, vacuum systems, relay tools, optical equipment, tool kits and cases. Also includes ten pages of useful "Tool Tips" to aid in tool selection.

JENSEN TOOLS AND ALLOYS
4117 N. 44th Street, Phoenix, Ariz. 85018



For More Details Circle (26) on Reply Card

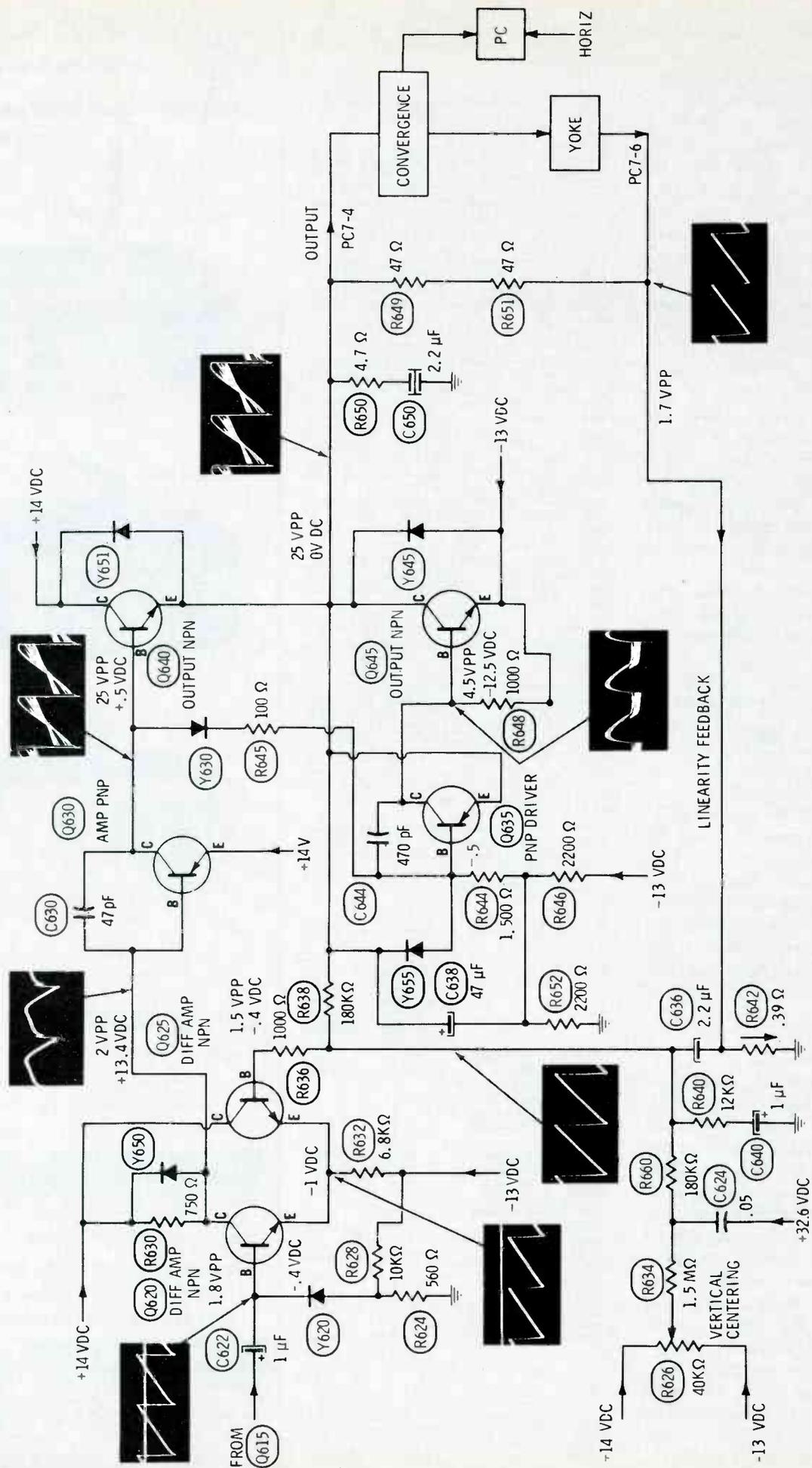


Fig. 5 Here are the waveforms and voltages of the "differential" amplifiers, drivers, and outputs. Feedback from the yoke current comes back to the base of Q625, along with a variable DC voltage for vertical centering. Notice the absence of a vertical linearity control. None is needed with this kind of circuit.

Electronic Servicing... ON-TARGET cards

YOUR DIRECT "HOTLINE" TO MANUFACTURERS/SUPPLIERS

•FILL IN THE CARD •PRINT CLEARLY •DROP IT IN THE MAIL

BOOST your TV service PROFITS with the new Heath CRT TESTER/REJUVENATOR!



Checks, cleans, rejuvenates black-and-white and color TV tubes, including new IN-LINE-GUN color tubes without add-ons or adapters.

ONLY **89⁹⁵** KIT
140⁰⁰ ASSEMBLED

Heath Company, Dept. 555-231, Benton Harbor, MI 49022

Send for our NEW FREE HEATH CATALOGS

KIT: Nearly 400 practical, fun-to-build electronic products in money-saving kit form.

ASSEMBLED: High-performance, low cost instruments for all your TV or audio servicing needs—factory assembled and calibrated at direct-to-you savings.



Dept. 555-231

- Please send me the new Heathkit Catalog.
- Please send the latest Assembled Instruments Catalog.

NAME _____

TITLE _____

COMPANY/INSTITUTION _____

ADDRESS _____

CITY _____

STATE _____ ZIP CA-112A

Send this postpaid card today!

Electronic Servicing
SUBSCRIPTION OFFER...
 Use this handy card to subscribe or renew your subscription.

Subscription Offer

Enter my subscription to **ELECTRONIC SERVICING**

- 3 years \$13.00 2 Years \$10.00 1 Year \$6.00
- Bill Me Remittance Enclosed Extend Present Subscription

IMPORTANT! Please check your business classification.

Type of Business

Check One

- | | |
|---|--|
| <ul style="list-style-type: none"> A. <input type="checkbox"/> Independent Electronic Service Organization B. <input type="checkbox"/> Retailer with Electronic Service Department C. <input type="checkbox"/> Independent or Self-Employed Service Technician D. <input type="checkbox"/> Electronics, Radio, TV Manufacturer E. <input type="checkbox"/> Industrial Electronic Service | <ul style="list-style-type: none"> F. <input type="checkbox"/> Wholesale, Jobber, Distributor G. <input type="checkbox"/> Other (Specify)..... |
|---|--|

- Position**
- H. Owner, Manager
 - I. Ser. Manager
 - J. Technician
 - K. Other

Be sure you have checked one box in each column above!

Print plainly or write below:

Name _____

Firm _____

Firm Address _____

City _____ State _____ Zip _____

Did you receive this issue through Distributor Subscription

How much better off would you be...if you had your 1st Class FCC License?



A 1st Class FCC "ticket" is a legal requirement for some jobs. But even where it's not required, it is Government certification of certain electronics skills and knowledge. CIE has several professional career courses specifically aimed at preparing you to pass the government-administered FCC License exam. And, based on continuing surveys, close to 4 out of 5 CIE graduates who took the exam got their licenses!

For details, get a copy of CIE's FREE school catalog — plus a complete package of independent home study information. School rep contact in some areas. All career courses are approved for educational benefits under the G.I. Bill.

FREE CATALOG —
Mail card today.

Print Name _____

Home Address _____ Apt. _____

City _____ State _____ Zip _____

CIE Cleveland Institute of Electronics, Inc.
 1775 East 17th Street, Cleveland, Ohio 44114
Accredited Member National Home Study Council

Phone (Area Code) / _____

Check here for G.I. Bill information: Veteran Active Duty

BUSINESS REPLY MAIL

No Postage Stamp Necessary If Mailed In United States

Postage will be paid by

HEATH COMPANY

Dept. 555-231

Benton Harbor, Michigan 49022

FIRST CLASS PERMIT

No. 395

Benton Harbor,
Michigan 49022



**A POCKET
FULL OF
PROFITS**

with the new
Heath
Shirt Pocket
Color Alignment
Generator

ONLY
\$64⁹⁵
KIT

\$85⁰⁰
ASSEMBLED

Crystal controlled carrier oscilator, sixteen test and alignment patterns, automatic turn-off feature, and it fits in the palm of your hand.

Heath Company, Dept. 546-211, Benton Harbor, MI 49022

PLACE
FIRST CLASS
POSTAGE
HERE

Electronic Servicing.


P.O. Box 12901

Overland Park, KS 66212

BUSINESS REPLY CARD

No Postage Stamp Necessary if Mailed in the United States

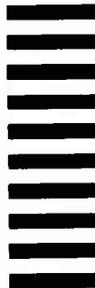FIRST CLASS
PERMIT NO. 8685
CLEVELAND, OHIO



POSTAGE WILL BE PAID BY:

CLEVELAND INSTITUTE OF ELECTRONICS, INC.
1776 East 17th Street
Cleveland, Ohio 44114

Non-symmetrical output

As I mentioned before, the two output transistors are alike, both of NPN polarity, and not a PNP balanced against a NPN as is done in many models.

This means that the two bases cannot be tied together by a diode, as is true with the complementary-symmetry circuits. Instead, a phase inverter (Q635) must be provided. The collector of Q635 is directly connected to the base of Q645, the NPN output, and the collector of Q645, along with the emitter of Q640, drives the yoke.

Notice that both Q635 and Q645 are connected for highest gain (common-emitter type circuit; signal in at the base and out at the collector), and yet together produce a gain of approximately 1 (unity). I will not attempt to explain this phenomena; probably it's because each transistor feeds an extremely low impedance, and that always reduces gain.

Centering

Normally, the two output transistors conduct the same, and because they are fed from two separate power supplies of opposite polarity, the output signal to the yoke has virtually no DC voltage or current. Any unbalance between the two transistors causes current to flow through the yoke, thus changing the vertical centering. Going back a step, any shift of DC voltages in the differential or driver stages upsets the balance of output transistor currents.

This balance (and the vertical centering) can change because of defective components, or it can occur because of the "vertical centering" circuit which deliberately varies the balance. The base voltage of Q625 is adjustable through R626, R634, and R660. The picture can be moved about 1 inch up and down (Figure 8).

Horizontal-Sweep Rectification

One DC supply voltage from outside the module feeds the vertical-size control. In addition, the vertical module contains two other power supplies that rectify different polarities of horizontal pulses (Figure 9). Because the vertical power comes from the horizontal, the height does not increase when



The arrow points to the vertical-centering control, at the side and in front of the vertical-hold control. The height control is to the left of the hold control.

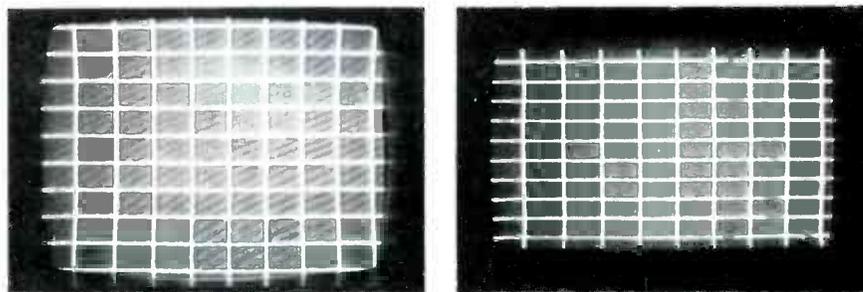


Fig. 6 When the height is reduced by the vertical size control, the linearity continues to be excellent.

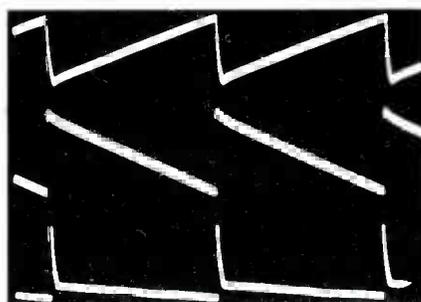


Fig. 7 When the yoke-current waveform at the base of Q625 (top trace) is subtracted from the drive sawteeth at Q615 (inverted to simulate the polarity change in Q620, shown by center trace), the result in the scope is positive-going pulses and small sawteeth (bottom trace). That's nearly the waveform obtained at the collector of Q620, produced by the action of the "differential" transistors.

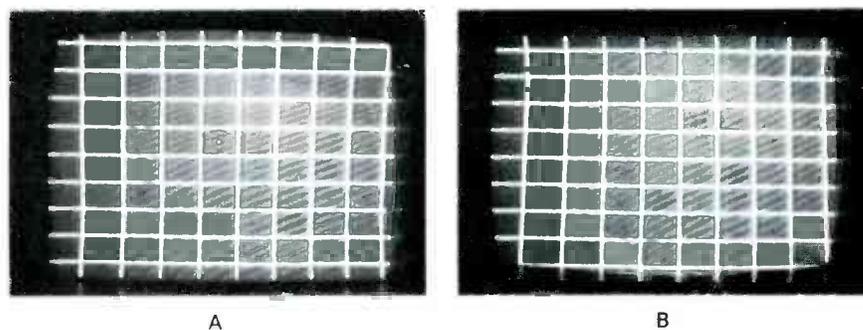




Fig. 8 With the vertical-centering control turned to one end, the picture was about 1/2-inch too high (notice the center dot in photo A), and -1.25 volts was measured at the yoke. At the other extreme of the centering control, the yoke had +1.5 volts, and the picture was about 3/4-inch too low on the screen (photo B).

excessive brightness causes blooming.


One surprise from the waveforms was the large 60 Hz (actually 59.45

Hz) ripple present at the output of both DC supplies. At first thought, it seems impossible, because the diodes are fed horizontal pulses,


Fig. 9 Here are the circuits and waveforms of the two power supplies for the output transistors. The input waveforms were photographed at horizontal rate; the output ripples at vertical rate, as explained in the text.

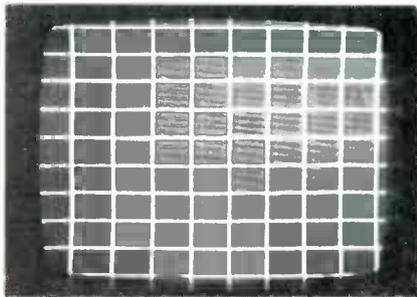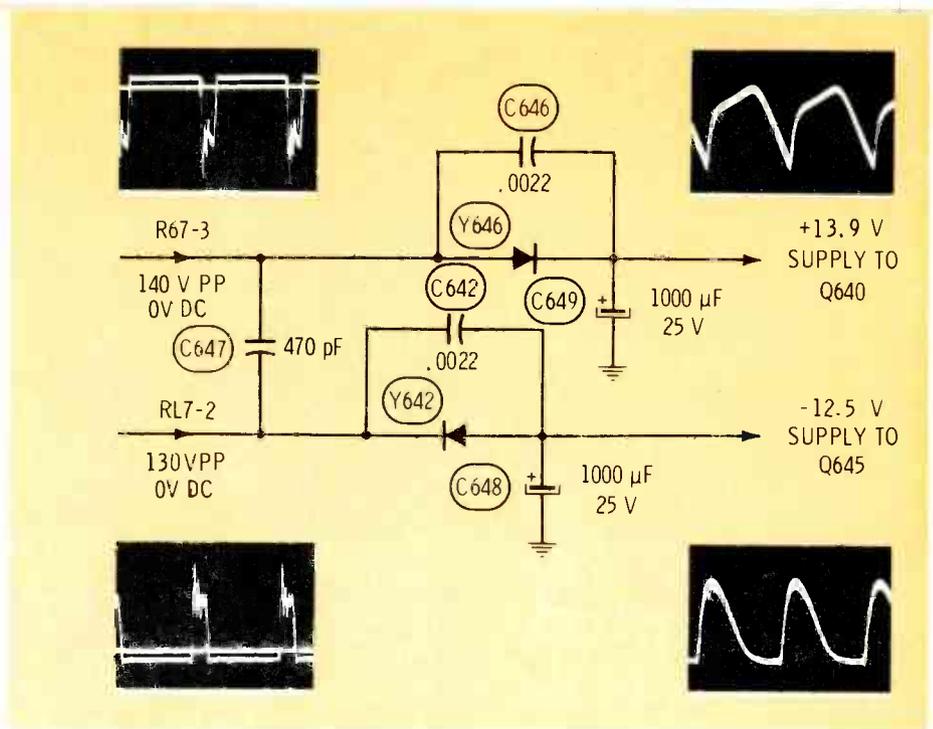


A

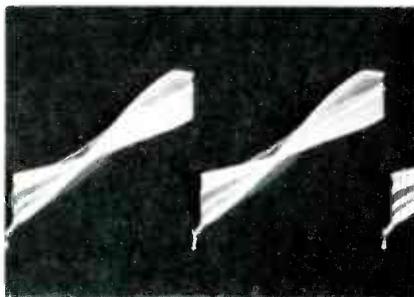


A

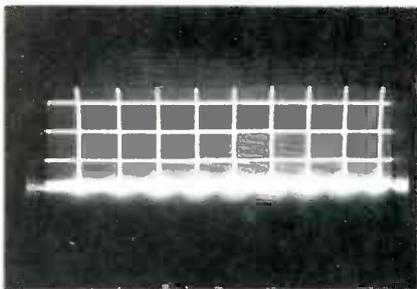


B

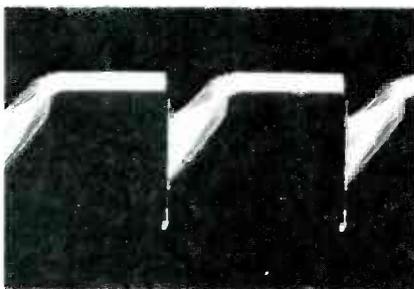

B

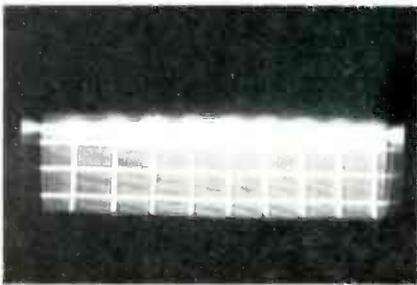

C

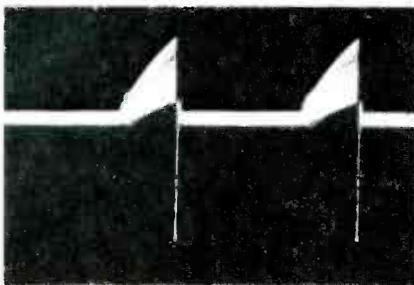

C

Fig. 10. These three pairs of pictures show what happens when either output transistor opens. (A) gives the normal crosshatch on the screen and the normal scope waveform at the output of the module. An open Q640 produced the crosshatch and waveform of (B), and -1 volt at the output. Evidently Q640 deflects the bottom of the raster. When Q645 was open, the crosshatch and waveform of (C) were found; the yoke had +1 volt. Q645 deflects the top half of the raster.

and this should eliminate all 60-Hz ripple, regardless of the size of the filter capacitors. The hum waveforms are created by the large currents of the vertical-output transistors which are not bypassed completely by the 1,000 microfarad filters (C649 and C648). In other words, the "hum" is from the vertical, not the AC line.

Open Output Transistors

In order to show the symptoms of an open Q640 or Q645 output transistor, I removed one at a time, and photographed the scope waveform and the crosshatch pattern from the picture tube. The results are shown in Figure 10. In addition to the distinctive patterns, the DC voltages were changed significantly. When Q640, the transistor for "bottom" deflection, was open, the positive supply voltage was high, and also the DC voltage at the yoke was about -1 volt.

When the transistor for top deflection (Q645) was removed, the negative voltage supply was high, and the yoke measured about +1 volt DC.

Even with such a huge amount of distortion, the small amount of visible height had good linearity; a tribute to the circuit design.

Incidentally, the output transistors and resistors on the module were unusually difficult to remove from the board. Even with all solder removed, and the leads

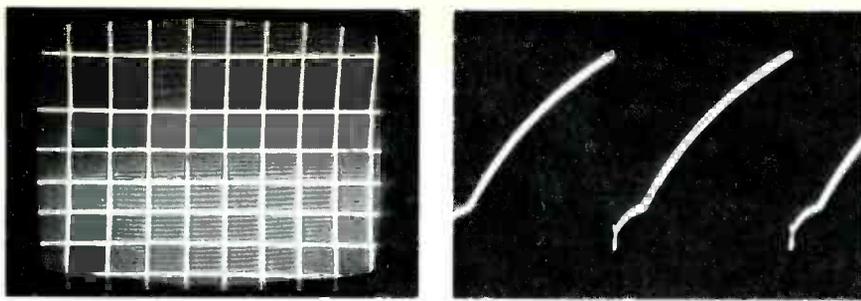


Fig. 11 An open C636 gave these symptoms on raster and scope. This is one of the few defects that can stretch the linearity. It removes the negative feedback.

wobbling like a loose tooth, the wires could hardly be removed without breaking them. Bends of the leads at the board seems to be the reason. Perhaps you can straighten out the leads of any you remove, and do it easier than I did.

Defects Causing Poor Linearity

Circuits such as these having feedback from the yoke current are **almost** immune to poor linearity because of defective components. But I did discover two interesting symptoms involving the linearity.

No feedback

Excessive height and stretched linearity at the top (see Figure 11) were caused by an open C636, the capacitor that couples the feedback from the yoke to the differential stage. Strangely enough, the "butterfly wings" from the pincushion correction were missing from the yoke waveform.

Probably the height could have been reduced by lowering the setting of the vertical size control, but the linearity would have remained poor.

Open loads

Strange crosshatch and scope patterns, like none I have ever seen before, were produced by open circuits in some of the components wired in parallel with the yoke coils.

When R649 or R651 was removed, the raster scanning lines were bent in curves near the center of the screen, leaving two oval areas without lines (Figure 12). Also, R650 burned to a crisp.

After R650 was removed to remove the heating, the open ovals were reduced to just one located slightly to the left of center. However, when R650 or C650 were opened while R649 and R651 were in the circuit, no visible defect could be seen on the crosshatch pattern.

Two scope waveforms are shown; one was at the horizontal rate, and the other at vertical. Both show unwanted movements, coming from the pincushion action. The waveform taken at horizontal rate should have shown nothing, but it revealed strong horizontal-sweep patterns, which were a cross between pulses and square waves, and

they moved. These evidently obscured the usual sweep waveform, so that the picture of the pattern at vertical rate showed no resemblance to the correct waveform.

Comments

As I remember the problems we had (and still do sometimes) with the old tube-powered vertical circuits, I appreciate the new solid-state vertical systems. The tube circuits commonly changed height or linearity as they heated, they might roll or flip unexpectedly for no good reason, and often it was nearly impossible to obtain both full height and good linearity.

By comparison, the GE vertical circuit was totally stable, never rolled (except during a channel change), and had perfect height and linearity.

And yet I shudder a bit when thinking of the weird and difficult-to-analyze voltages and symptoms that can happen when something upsets the DC voltages in the differential, driver, or output stages (all direct coupled).

As a test, I shorted base-to-emitter of Q620. Of course, there was no vertical sweep, but the horizontal line was about 2 inches from the **top** of the screen, and the yoke measured -5 volts. Evidently Q640 was biased to cutoff, and Q645 was saturated. I chickened out, and quickly shut off the power to prevent ruining any transistors. Perhaps later, I can strengthen my courage enough to analyze some of these massive failures.

Next Month

Chroma and video circuits will be spotlighted next month.


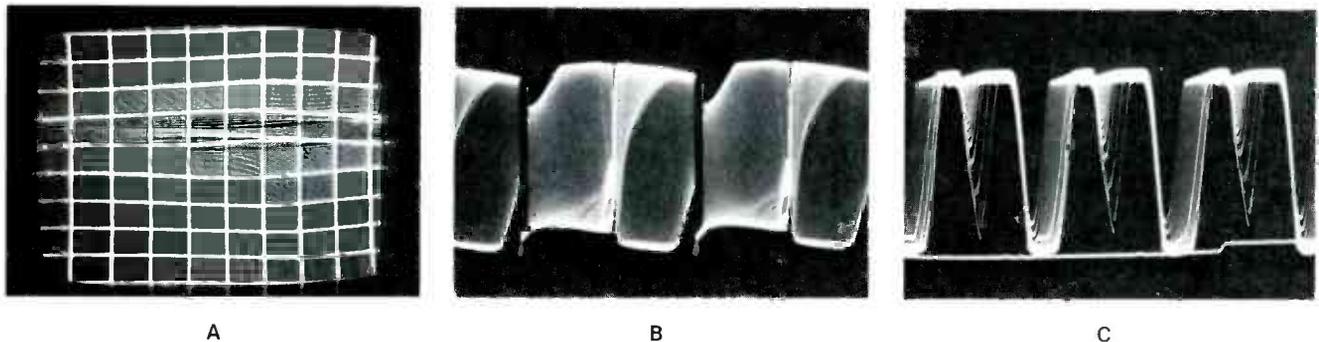


Fig. 12 An open R649 or R651 anti-ringing resistor produced these strange results. Unstable bending of the scanning lines near the center (A) were slightly different with and without R650 in the circuit. Output to the yoke had this waveform (B) when the scope was set for vertical rate; and the foreign areas of (B) proved to be horizontal signal when the scope was set for horizontal rate (C).

Are you,
of all people,
still opening
your garage

the
hard
way?

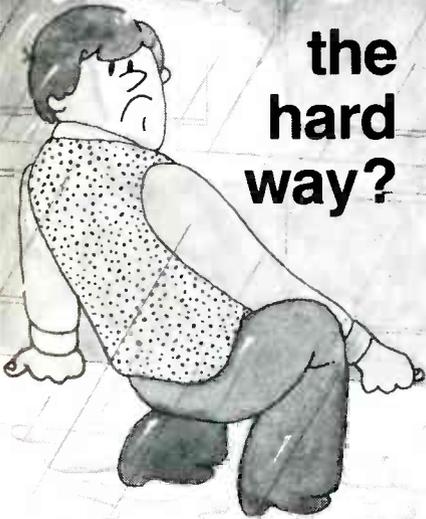

Anybody who's into electronics

certainly should be getting the everyday convenience and family security of automatic garage door operation... especially now, with Perma Power's great Electro Lift opener... made to fit in the trunk of your car, designed for easy handling and simple do-it-yourself installation. Available now at a surprisingly low price from your distributor.



P.S. Show off your opener to your friends and neighbors. You'll probably be able to pay for yours with what you make installing openers for them.

**Perma Power
Electro Lift®**

PRODUCTS OF **Chamberlain**
Chamberlain Manufacturing Corporation
Perma Power Division
845 Larch Avenue, Elmhurst, Illinois 60126
Telephone (312) 279-3600

64 For More Details Circle (34) on Reply Card

productreport

These features supplied by the manufacturers are listed at no-charge to them as a service to our readers. If you want factory bulletins, circle the corresponding number on the Reply Card and mail it to us.

Picture-Tube Restorer

A different method of increasing the gun current of weak color picture tubes is incorporated into the NU-COLOR Picture-Tube Restorer offered by **Oneida**. This unit does not change the heater voltage, although the physical appearance is similar to those that do. Instead, three linear controls adjust the amount of current applied to some elements of the picture tube. The color of the levers identifies the correction of red, blue, and green gun current.

The NU-COLOR Restorer is installed by plugging it in between the base of the picture tube and the CRT socket. Then, with the color control turned down, the three sliding controls are adjusted for the best balance giving a good black-and-white picture. Afterwards, the color control can be turned up for a pleasing picture. Some picture tubes, according to the manufacturer, require operation with



Two versions are available; Model 70A with large plug and socket is for the older round color tubes, and Model 90A is for the rectangular tubes. Retail price of each is \$24.95.

For More Details Circle (45) on Reply Card

Purchasing Guide

Allied Electronics' 1977 Engineering Manual and Purchasing Guide now is ready. The 212-page guide is filled with a wide selection of industrial-type electronic parts, components, supplies, and equipment. Some items featured are: test equipment, trimmers and potentiometers, transformers, tools, capacitors, new solar-energy products, CB test equipment, and even a microcomputer. Also, new in this year's guide is the introduction of metric measurements on many electronic parts and components.

A copy of the guide can be obtained by sending \$1.00 to cover postage and handling to: Allied Electronics, Dept. 77, 401 East 8th Street, Fort Worth, Texas 76102.

For More Details Circle (46) on Reply Card

FM Converter

Audiovox Corporation has expanded its line of mini, under-dash units with the introduction of a tiny FM converter.


The gold-finished, micro-sized Model FMC-4C converter measures 4" X 3-3/4" X 1". It has a black-out dial with an LED station indicator, all-solid-state circuitry, and a push on/off switch. It features a built-in "Tune



Tone" which simplifies tuning to the proper frequency. A tone is emitted indicating the correct frequency for FM tuning of AM radios.

(Continued on page 66,

ELECTRONIC SERVICING

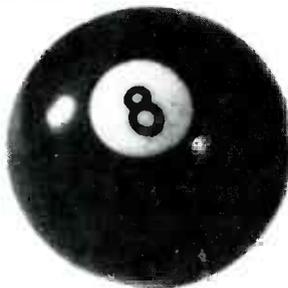

8-TRACK REPAIRS?

Want to get out from behind the 8-Ball? Then pocket your 8-Track repair problems with an FRM Kit from Projector-Recorder Belt Corporation. A revolutionary repair concept! Each kit contains 25 endless flat rubber belts, sizes 6.1" to 16.8" I.C. These precision belts fit virtually all 8-Track players. Each kit contains our handy Belt Sizer. You select the belt you need without cross reference or catalogs. For a limited time, the FRM Kits have been reduced to \$34.18, a 10-percent saving to you. Order your FRM Kit today; it's a repairman's must.

Dealer Inquiries Invited

PROJECTOR-RECORDER BELT CORPORATION

301 Whitewater St., Whitewater, WI 53190
(414) 473-2151

24-Hour Answering Service

For More Details Circle (35) on Reply Card

bookreview

CB Rules and Regulations

Author: Compiled By The Howard W. Sams Editorial Staff

Publisher: Howard W. Sams & Co., Inc., 4300 West 62nd Street, Indianapolis, Indiana 46268

Size: 44 pages, book number 21341

Price: \$1.00 paperback (Canadian Price slightly higher)

The complete text of Part 95 of the FCC Rules and Regulations is included, revised to reflect the latest changes. It also contains copies of two important FCC Forms: Form 505, Application for Class C or D Station License in the Citizens Radio Service; and Form 555-B, the Temporary Permit. Complete instructions for completing these forms are given in the book. In addition, "10" signals and "Q" signals, the verbal shorthand used by CBers, and a section on CB slang are included in this guide.

Handbook Of Solid-State Troubleshooting

Author: Hershhal Gardner

Publisher: Reston Publishing Company, Inc., P.O. Box 547, Reston, Virginia 22090

Size: 318 pages


Price: \$15.95 hardbound

State-of-the-art semiconductor troubleshooting is emphasized, also the practical aspects of semiconductor devices, circuits, and systems, with theory held to a minimum. Test and measurement techniques are explained and illustrated for each individual subdivision of semiconductors. The broad spectrum of topics includes device testing, instruments, tools, component replacement, solid-state amplifier servicing, power-supply troubleshooting, control-circuit servicing, and test-equipment maintenance.

Contents: Solid-state Principles and Testing Procedures; Normal and Abnormal Voltages and Waveforms; Troubleshooting Basic Solid-state Amplifiers; Troubleshooting Solid-state Power Supplies; Troubleshooting Solid-state Control Circuits; Troubleshooting Solid-state Test Equipment; Troubleshooting Solid-state Radio Receivers; Troubleshooting Solid-state FM Mono and Stereo Receivers; Troubleshooting Solid-state Quadriphonic Equipment; Troubleshooting Solid-state Industrial Electronic Equipment; Troubleshooting Solid-state Television Receivers; Troubleshooting Solid-state Digital Equipment; Answers to Review Questions; Index.

the bright one

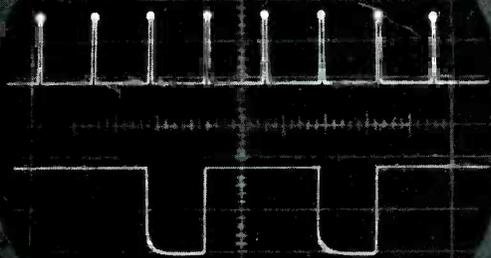new phosphor picture tube
with twice the brightness



TO-60 automatic dual-trace triggered-sweep oscilloscope

P-31 phosphor CRT has double the brightness for bright displays even in high speed dual-trace modes. Bandwidth: DC to 15 mhz. Unique features for the industry's greatest value are: • Automatic Triggering • Automatic Astigmatism • Automatic Horizontal Sweep • Automatic Horiz/Vert. TV Triggering provides positive display on composite video signals. Vertical sensitivity: .01 volts/cm to 20 volts/cm in 1-2-5 step sequence. Horizontal Sweep Speeds: .2 sec/cm to .5 μ sec/cm in 1-2-5 step sequence. Has 5X magnifier at all sweep speeds. External Horiz. Amp. Bandwidth: DC to .5 mhz; Sensitivity: .5 volts/cm. Calibrated Test Signal: 1 volt P-P square wave. Power: 105-125 volts, 60 cycles, 65 watts

Model TO-60 Less Probes. Net \$489.50

TO-55 automatic single-trace triggered sweep oscilloscope. Features same as TO-60 except Vert. Bandwidth is DC to 10 mhz.

Model TO-55 Less Probes. Net \$379.50

For the "bright one," see your distributor, or write:



LECTROTECH, INC.

5810 N. Western Avenue, Chicago, Illinois 60659

Area (312) 769-6262

For More Details Circle (36) on Reply Card

INTRODUCING THE FAST WORKING COUNTERS FROM HICKOK.



**Four affordable, deluxe
counters — one for every need.**

MODEL 380.
1 Hz to 80 MHz, 10 ppm **\$269**

MODEL 380X.
1 Hz to 80 MHz, 1ppm **\$395**

MODEL 385.
1 Hz to 512 MHz, 10ppm **\$499**

MODEL 385X.
1 Hz to 512 MHz, 1ppm **\$625**

Perfect for CB,
communications servicing,
audio and digital work, and
laboratory applications.

Full 7-digit display with
automatic decimal, full
autoranging. SPEED READ
mode updates display 5 times
each second to aid tuning
and adjustments.

Resolution is 1 Hz to 10
MHz, and 10 Hz to 80 MHz.
Models 385, 385X feature a
built-in prescaler to take you
all the way to 512 MHz.
Models 380X, 385X incorporate
temperature compensated
crystal oscillators with 1 ppm
accuracy, auxiliary 1 MHz
timebase output. External
timebase inputs on Models
380, 385.

See these exciting new
counters at your distributor
now!

HICKOK

the value innovator

INSTRUMENTATION & CONTROLS DIVISION
THE HICKOK ELECTRICAL INSTRUMENT CO.
10514 Dupont Avenue • Cleveland, Ohio 44108
(216) 541-8060 • TWX: 810-421-8286

For More Details Circle (37) on Reply Card

(Continued from page 64)

The compact converter installs easily with grip-tight mounting strips, and uses a regular AM antenna. It weighs 11 ounces, and has a tuning range of 88-108 MHz.

Suggested list price of the Model FMC-4C is \$39.95.

For More Details Circle (47) on Reply Card

Removable Mount For CB Antenna

"Hide-It", from RMS Electronics, is a quick-disconnect trunk mount for CB antennas. The trunk-lip half of the mount is installed permanently in place on the car. The other half of the mount attaches to the antenna, so it can be placed on the truck bracket for radio operation, or removed by loosening one screw when the antenna/mount assembly is to be hidden inside the trunk as a protection against theft or damage.

The mounting bracket fits most cars and accepts most CB antennas; also, it secures the coaxial cable in place and grounds it.


"Hide-It" Model CBTM-20 removable antenna mount is supplied with a self-adhering rubber strip to protect the finish of the car, and installation instructions. List price is \$11.95. □

For More Details Circle (48) on Reply Card

The quick charge iron with 16 different quick change tips.

ISO-TIP®
QUICK CHARGE
Cordless
Soldering Iron
completely
recharges in
3½-4 hours.
Low voltage,
battery powered,
ground free
isolated tip
design.

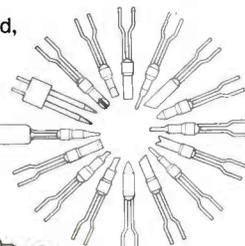16 snap-in tips
to fit any job
plus a PC
Drill.



WAHL CLIPPER CORPORATION
ORIGINATORS OF PRACTICAL CORDLESS SOLDERING
• Sterling, Illinois 61081 • (815) 625-6525
"Manufacturing Excellence Since 1919"

For More Details Circle (38) on Reply Card

www.americanradiohistory.com

Philco E21 Chassis

(Continued from page 39)

Case #3

The symptoms of this E21 pointed to power-supply problems, because the picture was shrunken on all four sides. In the past, the defect always was the filter C520, which reduced the 140 volts to about 100. Oops! The voltage was 140 volts; so it couldn't be C520. Also, the +112-volt supply was okay.

Now, this is one of the worst corners a technician can paint himself into. Your preconceived idea is proved all wrong, and you are left with no other solution. The solution is to go back to basics, and stop the short-cuts. First, what about other symptoms?

At loud volume, the vertical would pull-up even more and the width would change in step. The supply voltages were normal, except the 29-volt line which was down about 4 volts. Perhaps the vertical was drawing too much current, and loading-down the horizontal. That was wrong, because the drop across R532 (see last month) was only 0.3 volt.

Finally, I got around to measuring the high voltage, and I was astounded to find 42 KV. WOW!

Waveforms around the output transistor emitter showed a couple of foreign curves that didn't belong. And, finally, an ohmmeter test from emitter to ground showed 4,000 ohms. (The emitter should go to ground through a flyback winding of less than 1 ohm.) Yes, the winding was open.

The symptoms finally began to make sense. Lacking a return to ground through the flyback winding, the emitter of Q402 sought the next path through SC530 and the transistors supplied by that power supply.

I assumed the increase of high voltage was due to a change of the turns ratio of the flyback. Undoubtedly, the pulses were increased at the collector, and the primary has one less winding, so the voltage would be stepped-up more at the secondary.

Next Month

Vertical and chroma circuits, and some typical problems there, are the subjects for the next article. □

ELECTRONIC SERVICING

CORONADO TV2-20163A, TV2-20460A	1618-1
GENERAL ELECTRIC Chassis 19YA	1617-1
JC PENNEY 685-2041/-2046, 855-0139/-0147, 2041, 2046	1614-1
MGA CS-1330, CS-1530	1617-2
MIDLAND 15-032	1615-1
PANASONIC CT-925/C	1612-1
PHILCO Chassis E22-2	1618-2
RCA Chassis CTC76AA/AB	1616-1
SEARS 562.40230500, 562.40250500, 562.40291500	1612-2
SHARP C-1955	1616-2
SYLVANIA Chassis E11-5/-6/-7/-8/-13	1613-2
RC17	1613-2-A
TOSHIBA Chassis TAC520/530/535/545	1597-2
TRUETONE ADM1719A-77 (2DC1719)	1608-2
ZENITH Chassis 9GB1X, 9GB2X, 9HB1X	1611-2

FREE ALARM CATALOG

Huge selection of burglar & fire systems, supplies. Motion detectors, infrared beams, controls, door switches, bells, sirens. 300 items, 64 pp. packed with technical details, notes.

Phone (602) 263-8831



mountain west alarm
4215 n. 16th st., phoenix, az. 85016

For More Details Circle (41) on Reply Card

IT'S NO PUZZLE

TO ORDER

OELRICH SERVICE FORMS

FOR TV-RADIO & 2 WAY RADIO SERVICE LEGAL FORMS FOR CALIF. FLA. UTAH NOW AT YOUR PARTS JOBBER OR WRITE FOR CATALOG B64

OELRICH PUBLICATIONS

4040 N. NASHVILLE AVE. CHICAGO, ILLINOIS 60634

For More Details Circle (42) on Reply Card



GO DIGITAL, GO DANAMETER®

(The New VOM For Today's Needs.)

- 0.25% Accuracy
- Full Overload Protection
- Really Drop-Proof
- Full One Year Battery Life

DANA

Dana Laboratories, Inc.

2401 Campus Dr, Irvine, Ca 92715, (714) 833-1234

For More Details Circle (39) on Reply Card

The 5 SECOND TUNER RESTORER



**CLEANS!
LUBRICATES!
POLISHES!**

Spray TUN-O-POWER on tuner contacts, rotate the tuner and *within 5 seconds* you get beautiful color pictures on all channels. It's a minor miracle!

TUN-O-POWER is the most powerful polisher and lubricant ever developed. It works so well, you use a lot less. You can spray twice as many tuners with TUN-O-POWER as you can with an ordinary cleaner/lubricant.

What's more, TUN-O-POWER lubricant lasts for months longer than ordinary sprays. Detent action stays smooth as silk so you never have to worry about callbacks.

**CHEMTRONICS
INCORPORATED**

45 HOFFMAN AVE. HAUPPAUGE, N.Y. 11767 • (516) 582-3322

Our business is improving yours!



For More Details Circle (40) on Reply Card

The MARKETPLACE

Advertising rates in the Classified Section are 35 cents per word, each insertion, and must be accompanied by cash to insure publication.

Each initial or abbreviation counts a full word.

Minimum classified charge \$3.00.

For ads on which replies are sent to us for forwarding (blind ads), there is an additional charge of \$3.00 per insertion to cover department number, processing of replies, and mailing costs.

Classified columns are not open to advertising of any products regularly produced by manufacturers unless used and no longer owned by the manufacturer or a distributor.

HELP WANTED

\$19,000.00 PLUS per year for excellent outside-man. Qualifications: Totally honest, industrious, non-drinker, non-smoker. Prefer 15 years or more experience. If lazy do not apply. Send resume to American Television Service, 1032 South State, Orem, Utah 84057. 10-76-21

BUSINESS OPPORTUNITY

TV SALES & SERVICE in same location 15 years. Nets over \$25,000. Retiring. Including truck, equipment & inventory \$25,000. A. Bofin, 6361 Balsam Lake, San Diego, Ca. 92119. 6-76-tf

TIRED OF CUSTOMER ABUSE? Expand into lucrative patented MATV. Preliminaries \$3.00. Box 809, Boynton Beach, FL 33435. 10-76-61

TV SALES & SERVICE—Established 15 yrs. 2 houses, shop on corner lot. Servicing over 500 motel sets, mostly color, very good volume, drive-in service, good reputation. Inquire 305-267-9570, Titusville, Florida. Will show figures to interested buyers only. 509 Park Ave., Titusville, Florida 32780. 11-76 1t

BUILD ELECTRONIC DEVICES in your home. Get started in your spare time. Big profits. Experience not necessary. Ask for free literature telling how. Electronic Development Lab, Box 1535, Pinellas Park, Fla. 33565. 11-76 1t

TELEVISION SALES AND SERVICE BUSINESS—Central East Coast of Florida where its warm. Zenith sales and service plus RCA and Sylvania service work. Good established business. For details call, George Lewis, Realtor, 305-784-1290, 3500 N. Atlantic Ave., Cocoa Beach, Fla. 32931. 11-76- 1t

FOR SALE—TV SALES & SERVICE BUSINESS. Zenith dealership, stocked TV's & parts. In the beautiful Bitterroot Valley, clean air, mild winters, recreation, fishing, hunting, skiing, in Gods Country. Priced to sell. Retiring. PH. 406-777-5111, John Mednansky, Stevensville, Mt. 11-76- 1t

FOR SALE TV SALES & SERVICE—Business Chicago sub area. Zenith distributorship—established 1937. For info Mr. Luberda, 646 Burnham Ave., Calumet City, Ill. 60409, 312-862-7274. 11-76 1t

EDUCATION-INSTRUCTION

REPAIR TV TUNERS—High Earnings; Complete Course Details. 12 Repair Tricks, Many Plans, Two Lessons, all for \$2. Refundable. Frank Bocek, Box 3236 Enterprise, Redding, Calif. 96001. 8-76-tf

TV PROBLEMS? Send symptoms with a COPY of schematic and self-addressed-stamped envelope and \$3.00 cash or M.O. (NO checks) to Hart, Box 2041, Downey, CA 90242. Results Guaranteed. 10-76-tf

TV HINTS—Repair your TV. Send make & model, \$2.00 + stamp. Charles TV, 2033 McGraw Ave., Bronx, N.Y. 10462. 11-76-1t

HOW TO INCREASE YOUR SERVICE volume without expensive advertising. Work pulling secrets in new manual, \$5 ppd. E. P. S., Box 8736, Denver, CO 80201. 11-76-1t

FOR SALE

TV & RADIO TUBES 36c EA!! Free color catalog. Cornell, 4221 University, San Diego, California 92105. 8-76-tf

UNUSUAL SURPLUS AND PARTS Catalog \$1. ETCO Electronics, Dept. E.S., Box 741, Montreal "A" H3C 2V2. 7-76-10t

INCREASE SERVICE PROFITS & Collect In Advance. Service Contract Manual, Practical Home Electronics Service Business Manual. Each Manual \$12.50, both \$22.00. NATESA, 5906 S. Troy St., Chicago, Ill. 60629. 11-76-3t

POTTER BRUMFIELD RELAYS: fc 11d-24, SL-7005-28, 8 on Board. Unused—\$20.00. CKT. Board, Loaded, \$1.00, 6/\$5.00. 11-76 1t

SAMS—8 to 466 (156 folders)—\$125. Paul Ellis, 419 Bellevue St., Santa Cruz, Calif. 95060. 11-76-1t

FREE—Giant bargain electronic catalog, listing thousands of components, tubes, transistors, IC's, kits, test equipment. Edie's, 2700-EC, Hempstead Tpke., Levittown, N.Y. 11756. 8-76-3t

SAMS PHOTOFACTS—approx. 485 sets, starts at 2. Solid 1044 to 1231. \$485.00 for the lot. Sencore SM152 sweep & marker with book and cables \$100.00. Sencore CR143 CRT tester with book and cables \$50.00. Royce's Electronics, P.O. Box 1267, Moab, Ut. 84532, Ph: 801/259-6630. 11-76 1t

HEATH KIT Postmarker Sweepgenerator. Mini condition with cables and attenuator. \$195.00. David Tully, 586 Buttonwoods, Warwick, R.I. 02886. 11-76 1t

PICTURE TUBE MACHINE—We buy and sell NEW and USED CRT rebuilding machinery. COMPLETE TRAINING. Buy with CONFIDENCE from the ORIGINAL MFRG. For complete details, send name, address and zip code to: LAKESIDE INDUSTRIES, 3520 W. Fullerton Ave., Chicago, Ill. 60647, Phone: 312-342-3399. 11-76 1t

WANTED

NEEDED: 2EP4 Picture Tube for Philco TV, Model H2010. Larry Auman TV, Rt. 1, Box 368, Dover, Ohio 44622. 11-76-1t

**Let's keep
Scouting
going
stronger
than ever.**

advertisers' index



American Technology Corp.	17
Arrow Fastener Company, Inc.	51
B & K Precision—	
Dynascan Corp.	32, 37
Bussmann Mfg. Division	Cover 3
Castle Electronics, Inc.	57
Charous & Niebergall	57
Chemtronics Incorporated ...	67
Cleveland Institute	59
Dana Laboratories	67
Edison Electronics—Div. McGraw Edison	29
John Fluke Mfg. Co.	Cover 4
GC Electronics	39
Gem City Tuner	11
Heath Company	59
Hickok Electrical Instrument Co.	66
Jensen Tools and Alloys ...	57
Jerrold Electronics, General Instrument Corp.	23
Lectrotech, Inc.	65
LogiMetrics, Inc.	11
MTI	56
Mallory Distributor Products	3
Mountain West Alarm Supply Co.	67
Non-Linear Systems	17
Oelrich Publications	67
Oneida Electronic Mfg. Co.	33, 34, 35, 36
Perma Power Company	64
Phipps & Bird, Inc.	14
Pomona Electronics	2
Precision Tuner Service	Cover 2, 1, 9
Projector Recorder Belt Co.	64
RCA Distributor & Special Products ...	12, 13, 18, 19, 48, 49
Sencore Inc.	42, 43
Sperry Tech, Inc.	39
GTE Sylvania-ECG Consumer Renewal	5
Tektronix, Inc.	25
Tuner Service Corp.	7
Ungar Div. of Eldon Industries, Inc.	14
Wahl Clipper Corporation ...	66

Buss® Fuses Specialize Too!

in the protection of

CB


EQUIPMENT

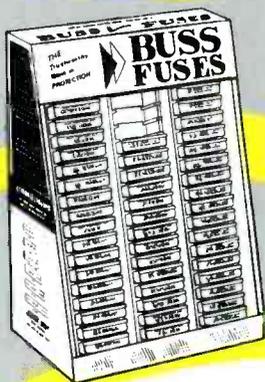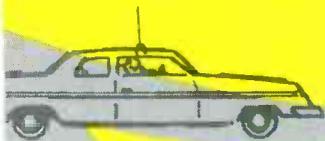

No. 240CB-3
Metal Display Stand



No. 80CB-1
Metal Display Stand

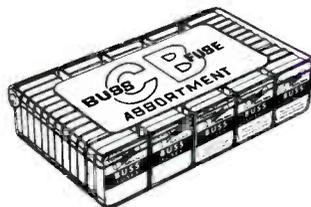

No. 240CB-4
Plastic Display Box



No. 80CB-2
Plastic Display Box

Now . . . four new BUSS fuse assortments exclusively designed with replacement fuses to service most Citizen-Band Radios — offering a whole new area of opportunities for increased profits.

Two assortments contain 48 — 5 in metal boxes (240 fuses). BUSS No. 240CB-3 fuse assortment comes in a handy metal display stand. BUSS No. 240CB-4 fuse assortment is packed in a compact plastic display box.

In addition, there are two fuse-assortments containing 16 — 5 in metal boxes (80 fuses). BUSS No. 80CB-1 fuse assortment packed in a metal display stand and BUSS No. 80CB-2 fuse assortment in a plastic display box.

Both BUSS fuse assortments contain a careful selection of the most popular fuses used in CB radios.

CB dealers can now have the fuses they need in a neat complete package to service all their customers fuse needs.

For full fuse assortment details, write for BUSS Bulletin CBA.



BUSSMANN MANUFACTURING
a McGraw-Edison Company Division
St. Louis, Missouri 63107



FLUKE PROVES AN INEXPENSIVE, HANDHELD DMM CAN BE BUILT WITHOUT LEAVING EVERYTHING OUT.

Let's face it.

Before now, if you bought an inexpensive, handheld digital multimeter you didn't get much—they just left most everything out.

We knew that was no answer.

So we built the 8030A 3½-digit DMM. It's a small, portable, inexpensive, handheld DMM, but it performs like our benchtop units.

With one basic difference. The 8030A was designed, built and tested to a size and shape proven best for field service and laboratory technicians. There's a built-in hood that can be slipped forward to shade the readout in sunshine. It has rms capability. The best overload protection. Diode test. It weighs 2.2 pounds, and will take a beating without failing. Finally, we guarantee accuracy specifications for one year.

And it only costs \$235*.


True rms.	Fluke
1-year accuracy specs.	Fluke
High voltage protection.	Fluke
Diode test.	Fluke

A full line of accessories offering rf voltage, high current ac, high voltage dc, and temperature measurement probes. Fluke

There's only one place to go for all the performance you need in a handheld DMM.

There are measurement functions in five selectable ranges for dc volts, ac volts (true rms), dc current, ac current (true rms), and resistance. DC voltage measurement is from 100 μ V to 1100V with basic accuracy of $\pm 0.1\%$, ac measurement is from 100 μ V to 750V rms with basic accuracy of $\pm 0.5\%$. DC and ac current is from 100 nanoamps to 1.999 amps with basic dc accuracy of $\pm 0.35\%$ and basic ac accuracy of $\pm 1\%$. Resistance measurement is from 100 milliohms to 2 megohms with a basic accuracy of $\pm 0.4\%$.

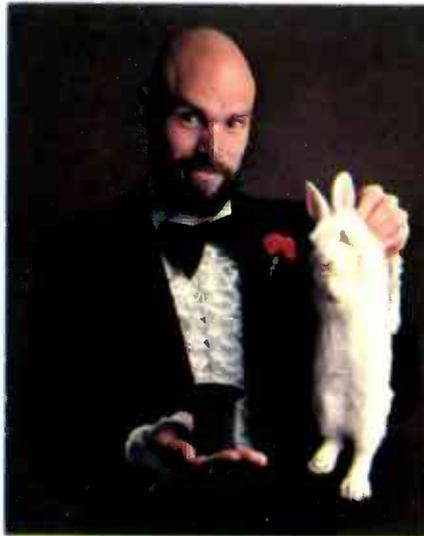We added true rms response for ac measurements. Specified accuracy is still attainable when the measured waveform is distorted.



"Fluke does the impossible again."

There is extensive overload protection. It has been tested with transients up to 6000V peak across the input terminals.

Options include two battery operations: a rechargeable NiCad for 8 hours operation and throw-away alkaline cells. Accessories include probes for measure-

ment of rf voltages, high current ac, high voltage dc and temperature.

80T-150 Temperature Probe	
Sensitivity:	1 mV/°C or 1 mV/°F
Accuracy:	
+15°C to +35°C ambient:	$\pm 2^\circ\text{C}$ (3.6°F) - 25°C to $+125^\circ\text{C}$ $\pm 3^\circ\text{C}$ (5.8°F)
	-50°C to -25°C and +125°C to +150°C
0°C to 15°C, 35°C to 50°C ambient:	Add 1°C (1.8°F) to above

You can also get temperature measuring capabilities with the 8030A.

And because the 8030A gives you so much in performance, let us remind you once more of the price.

Only \$235*.

For the first handheld DMM that's small in size, small in price, but huge in performance.

For data out today, dial our toll-free hotline, 800-426-0361.

John Fluke Mfg. Co., Inc., P.O. Box 43210, Mountlake Terrace, WA 98043

Fluke (Nederland) B.V., P.O. Box 5053, Tilburg, The Netherlands.

Phone: (013) 673-973 Telex: 52237

*U.S. price only.



A NEW ADVANCE. 8030A DMM. 

For More Details Circle (2) on Reply Card