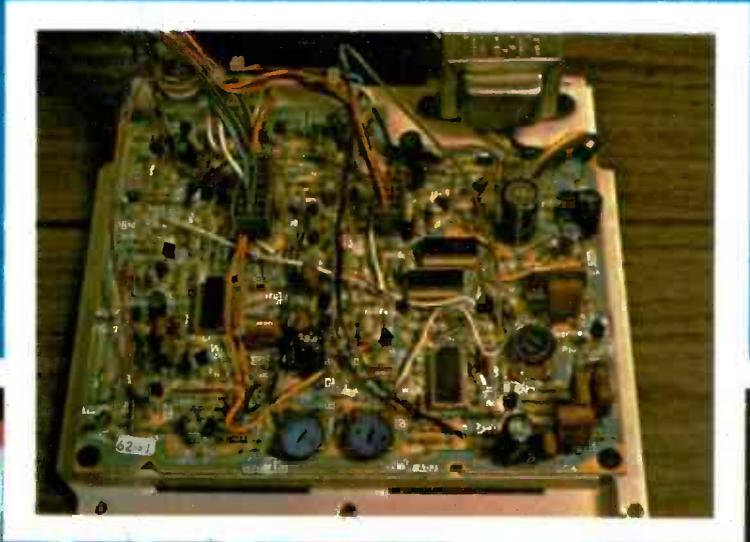


Electronic Servicing




A HOWARD W. SAMS PUBLICATION

VIR-CONTROLLED COLOR




5

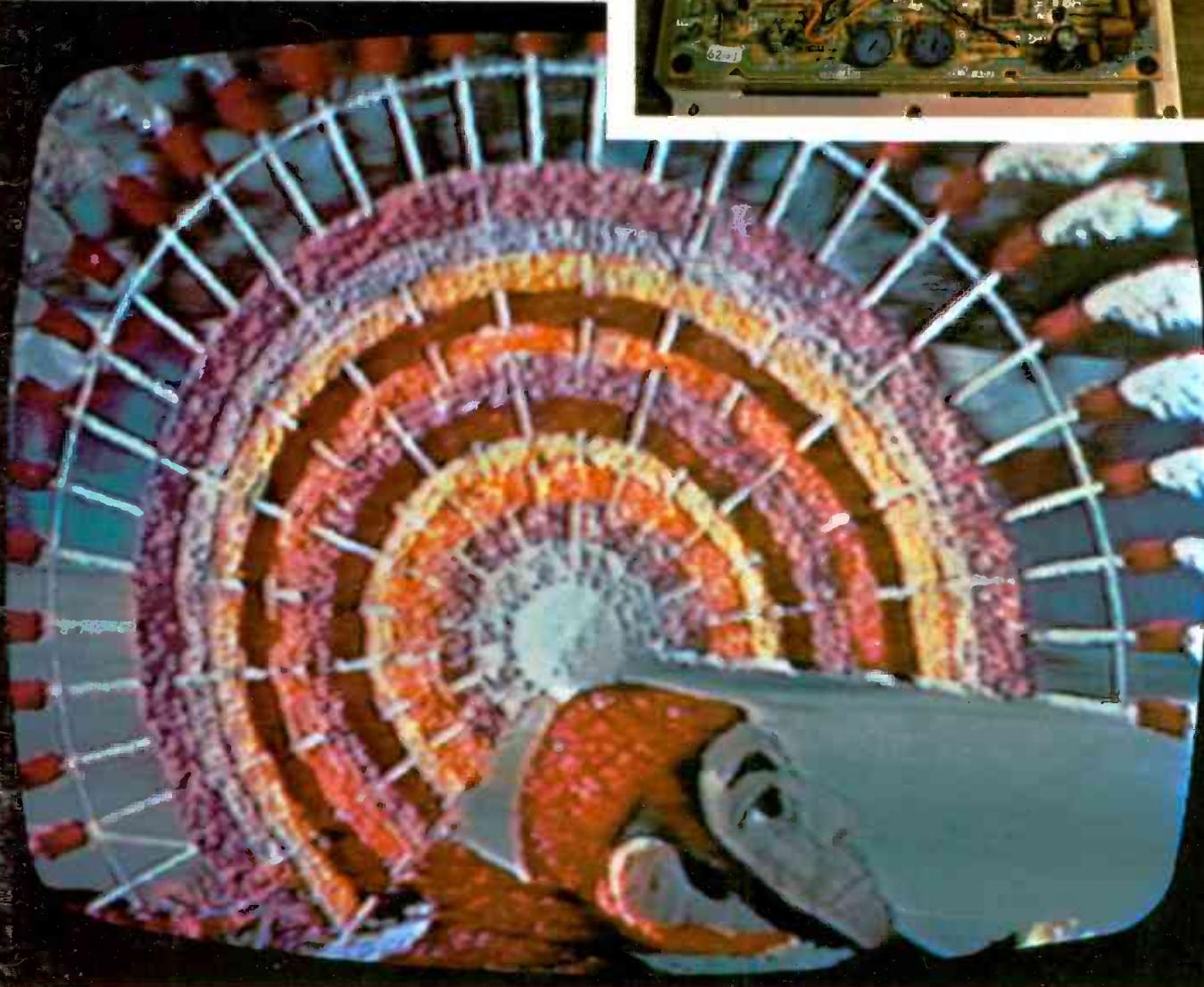

ESS-2074 R IA 577 4
SAMUEL SACHS
809 BERGEN ST
PHILADELPHIA PA 19111

PLL—New Brain for CB Convergence Facts and Tips

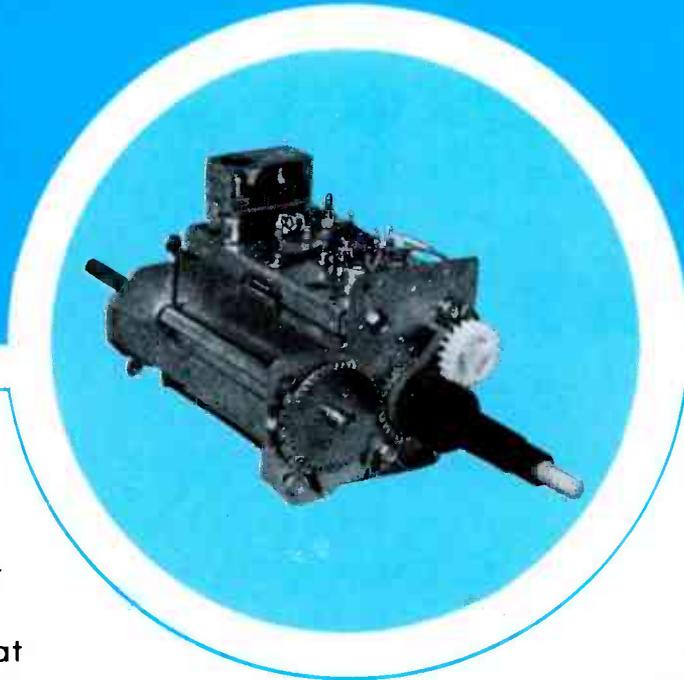THE BEST OF EVERYTHING HAS ITS PRICE ...EVEN TUNER SERVICE!



From the beginning, our goal has been to provide the best tuner service—never the cheapest. You get what you pay for in business and tuner service is no exception. The extra dollar you might pay at PTS is peanuts when you consider the added

reliability and the standards of excellence we apply to every job. Thousands of PTS customers must agree or we wouldn't be the world's largest tuner service company. When you are comparing tuner service companies, price alone doesn't tell the story.

SAME DAY SERVICE • ORIGINAL PARTS • ONE YEAR WARRANTY

**WE REPAIR THEM ALL . . . COLOR, BLACK & WHITE, TUBE,
TRANSISTOR OR ELECTRONIC/VARACTOR . . . ANY MAKE OR MODEL.**

VHF or UHF. . . \$11.95 UV-Comb. . . \$18.95

(MAJOR PARTS AND SHIPPING EXTRA — DEALER NET)



PTS ELECTRONICS, INC.

PRECISION TUNER SERVICE

General Headquarters: P.O. Box 272, Bloomington, IN 47401

THE COMPLETE LIST OF ALL PTS SERVICE CENTERS APPEARS ON THE NEXT PAGE.

For More Details Circle (1) on Reply Card

Electronic Servicing®

in this issue...

- 18 Servicing GE Modular Color TV, Part 7 (VIR-Controlled Color)**—Both color level and tint are adjusted automatically by this unique digital system, during those TV programs that include the VIR signal. Many scope waveforms are included—*Gill Grieshaber, CET.*
- 29 Convergence Trouble Symptoms And Repairs**—Here is a refresher course in convergence principles, the new circuits for solid-state color TV's, and suggestions for finding defects in convergence circuitry—*Robert L. Goodman, CET.*
- 41 TV Tube Stock**—According to one independent service dealer, who repairs all brands, these were the fast-moving tubes for 1976—*Gill Grieshaber.*
- 42 PLL...A New Brain For CB Radios**—Phase-Locked Loop (PLL) technology makes possible a transmit/receive oscillator for all 40 CB channels with only three crystals—*Marvin J. Beasley, CET.*
- 53 Reports From The Test Lab**—This month, the WD-750A Digital VoltOhmyst and the WA-504B/44D Audio Generator from VIZ are examined—*Carl Babecke, CET.*

ABOUT THE COVER

This picture, photographed from the screen of a color-TV receiver, illustrates the operation of the General Electric module (see inset picture) which automatically corrects the color and tint according to the condition of the VIR signal.

DEPARTMENTS

| | | | |
|----------------------------|----|-------------------------------|----|
| Electronic Scanner | 4 | Test Equipment | 57 |
| Troubleshooting Tips | 8 | Product Report | 58 |
| Symcure | 12 | Audio Systems | 59 |
| Readers' Exchange | 15 | Catalogs and Literature | 59 |
| Book Review | 56 | Advertisers' Index | 60 |
| Photofact | 56 | | |

Second class postage paid at Shawnee Mission, Kansas and additional mailing offices. Published monthly at 9221 Quivira Road, Overland Park, Kansas 66212 by Intertec Publishing Corp., 9221 Quivira Road, Overland Park, Kansas 66212. Send Form 3579 to 9221 Quivira Road, P.O. Box 12901, Overland Park, Kansas 66212.

© Copyright, 1977. Howard W. Sams & Co., Inc. All rights reserved. Material may not be reproduced or photocopied in any form without written permission of publisher.

**YOU'VE GOT US
WHERE YOU
WANT US!**

**THE WORLD'S
LARGEST
TUNER SERVICE
IS CLOSE TO YOU!**

MIDWEST

Home Office
BLOOMINGTON, IN 47401
 5233 S. Hwy. 37, P.O. 272
 812-824-9331
CLEVELAND, OH 44134
 5682 State Road
 216-845-4480
KANSAS CITY, KS 66106
 3116 Merriam Lane, P.O. 6149
 913-831-1222
MINNEAPOLIS, MN 55408
 815-W. Loke St., P.O. 8458
 612-824-2333
ST. LOUIS, MO 63130
 8456 Page Blvd., P.O. 24256
 314-428-1299
DETROIT, MI 48235
 13707 W. 8-Mile Rd.
 313-862-1783
GRAND RAPIDS, MI 49501
 1134 Walker Northwest
 P.O. 1435
 616-454-2754
CINCINNATI, OH 45216
 8172 Vine St., P.O. 15491
 513-821-2298
MILWAUKEE, WI 53218
 7211 Fond du Lac
 414-464-0789
COLUMBUS, OH 43227
 4005A E. Livingston
 614-237-3820
INDIANAPOLIS, IN 46202
 28 E. 14th St.
 317-631-1551
DAVENPORT, IA 52805
 2024 E. River Dr., P.O. 187
 319-323-3975
OMAHA, NE 68132
 5008 Dodge Street
 402-558-1800
CHICAGO
 Berkeley, IL 60163
 1756 S. Taft Street
 312-449-2082

NORTHEAST

SPRINGFIELD, MA 01103
 191 Chestnut, P.O. 3189
 413-734-2737
PHILADELPHIA
 Upper Darby, PA 19082
 1742-44 State Road
 215-352-6609
PITTSBURGH, PA 15202
 257 Riverview Ave., P.O. 4130
 412-761-7648
E. PATERSON, NJ 07407
 158 Market St., P.O. 357
 201-791-6380
BUFFALO, NY 14212
 993 Sycamore St., P.O. 1241
 716-891-4935
BOSTON
 Somerville, MA 02144
 52 Holland St., Davis Sq., P.O. 187
 617-666-4770
SYRACUSE, NY 13204
 418 Solar St., P.O. 207, Salina Sta.
 315-475-2330
BALTIMORE, MD 21215
 5505 Reisterstown Rd.
 301-358-1186

PACIFIC

SACRAMENTO, CA 95841
 4611 Auburn Blvd., P.O. 41354
 916-482-6220
SAN DIEGO, CA 92105
 5111 University Ave., P.O. 5794
 714-280-7070
LOS ANGELES, CA 90023
 4184 Pacific Way
 213-266-3728
PORTLAND, OR 97213
 5220 N.E. Sandy Blvd.
 P.O. 13096
 503-282-9636
SEATTLE, WA 98109
 432 Yale Ave. N., P.O. 9225
 206-623-2320

SOUTH

JACKSONVILLE, FL 32210
 1918 Blanding Blvd., P.O. 7923
 904-389-9952
WASHINGTON, DC
 Silver Spring, MD 20910
 8880 Brookville Rd.
 301-565-0025
CHARLOTTE, NC 28225
 724 Seigle Ave., P.O. 5512
 704-332-8007
BIRMINGHAM, AL 35222
 524-32nd St. So., P.O. 31004
 205-323-2657
MEMPHIS, TN 38118
 3614 Lamar Ave., P.O. 18053
 901-365-1918
NORFOLK, VA 23504
 3118 E. Princess Anne Rd.
 804-625-2030
NEW ORLEANS
 Metairie, LA 70004
 3920A Airline Hwy., P.O. 303
 504-837-7569
TAMPA, FL 33690
 2703 S. Macdill, P.O. 14301
 813-839-5521
NASHVILLE, TN 37214
 2426 A Lebanon Rd.
 615-885-0688

MOUNTAIN

DENVER
 Arvada, CO 80001
 4958 Allison St., P.O. 672
 303-423-7080
SALT LAKE CITY, UT 84106
 1233 Wilmington Ave.
 P.O. 6218
 801-484-1451
PHOENIX, AZ 85061
 2412 W. Indian School Rd.
 P.O. 27248
 602-266-0582

SOUTHWEST

LONGVIEW, TX 75601
 Mopac Rd., P.O. 7332
 214-753-4334
OKLAHOMA CITY, OK 73106
 3007 N. May, P.O. 60566
 405-947-2013
HOUSTON, TX 77207
 4326 Telephone Rd., P.O. 26616
 713-644-6793

CANADA

MONTREAL, QUEBEC H2 P2 M4
 8400 St. Laurence Blvd., Room 205
 514-381-5838




PTS ELECTRONICS, INC.
 PRECISION TUNER SERVICE

For More Details Circle (3) on Reply Card

SUBBER®

MARK IV-CUVB

A TIMESAIVING
INSTRUMENT
BY CASTLE

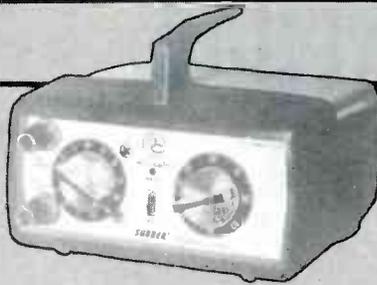

UHF-VHF TV tuner and i-f signal analyst
Incorporates these important features:

- Tunes all UHF & VHF Channels
- Electronic Fine Tuning
- Dual 40 MHZ IF Output Jacks
- Battery Condition Indicator

MARK IV-CUVB
(BATTERY POWER ONLY)

Net \$64.95



CASTLE ELECTRONICS

5233 Clc South Highway 37 Bloomington, Indiana 47401

For More Details and Specifications Contact Your Nearest Distributor
In Canada: Len Finkler Ltd; Ontario

For More Details Circle (4) on Reply Card

SpaceSaver: New RCA Flameproof Film Resistor Kit



Introducing RCA's convenient, preloaded and prelabeled Flameproof Resistor Kit containing a wide range of the most-needed, standard value resistors in 1/2, 1 and 2 watt ratings. Two of each rating for a total of 330 resistors; all ±2% tolerance. Packed in a sturdy metal-frame cabinet for easy availability.

Service Technicians prefer RCA Flameproof Film Resistors because of their inherent safety characteristics. Design Engineers prefer them because they won't flame or short even under severe conditions. Look to RCA — your best single source for a complete line of flameproof film resistors.

Contact your authorized RCA Parts Distributor for all the details, or write to RCA Distributor and Special Products Division, 2000 Clements Bridge Road, Deptford, NJ 08096.

RCA Flameproof Film Resistors

For More Details Circle (5) on Reply Card

Electronic Servicing

Editorial, advertising and circulation correspondence should be addressed to: 9221 Quivira Road, P.O. Box 12901, Overland Park, Kansas 66212 (a suburb of Kansas City, Missouri). (913) 888-4664.

EDITORIAL

RONALD N. MERRELL, Director
CARL H. BABCOKE, Editor
DEBORAH POWELL, Editorial Assistant
DUDLEY ROSE, Graphic Designer

EDITORIAL ADVISORY BOARD

LES NELSON, Chairman
Howard W. Sams & Co., Indianapolis
JOE A. GROVES, Technical Consultant
Howard W. Sams & Co., Indianapolis

CIRCULATION

GREG GARRISON, Director
EVELYN ROGERS, Manager



Member, American Business Press
Member, Audit Bureau of Circulations

ADMINISTRATION

GEORGE H. SEFEROVICH, President
MIKE KREITER, Publisher

ADVERTISING SALES

Overland Park, Kansas 66212
(a suburb of Kansas City, Missouri)
Phone: (913) 888-4664

GLORIA PARMENTER, Production
Regional and Advertising Sales Offices
with Advertising Index

ELECTRONIC SERVICING (with which is combined PF Reporter) is published monthly by Intertec Publishing Corp., 9221 Quivira Road, Overland Park, KS 66212.

ELECTRONIC SERVICING is edited for technicians who repair home-entertainment electronic equipment (such as TV, radio, tape, stereo, and record player), and for industrial technicians who repair defective production-line merchandise, test equipment, or industrial controls in factories.

Subscription Prices: 1 year—\$6.00, 2 years—\$10.00, 3 years—\$13.00, in the U.S.A. and its possessions. All other foreign countries: 1 year—\$7.00, 2 years—\$12.00, 3 years—\$16.00. Single copy 75 cents; back copies \$1. Adjustment necessitated by subscription termination to single copy rate. Allow 4-6 weeks delivery for change of address. Allow 2-3 weeks for new subscriptions.



INTERTEC PUBLISHING CORP.
Subsidiary of HOWARD W. SAMS & CO., INC.

ELECTRONIC SERVICING

BE COMPETITIVE . . .

45 CHANNEL CAPABILITY
with exclusive
Percent Off Channel
direct readout
(Patent Pending)



\$975

All cables included

With Everything You Need for Fast CB Service in One Lower Priced, Compact Instrument . . .

AVOID TIME-WASTING MULTIPLE INSTRUMENTS AND CONFUSING CABLE SYSTEMS. GET AT THE PROBLEM IN A JIFFY WITH THE

SENCORE CB42 AUTOMATIC CB ANALYZER

It's a CB Profit Center All in One Handsome Instrument

The CB service market is growing and more "on the ball" technicians are getting into the act every day. Competition for the CB business is getting tougher and you'll want to be sure you can compete. Knowledge alone won't be enough. You'll want to get ahead by simplifying your work to get the most jobs out with the least effort. You'll want to concentrate on your troubleshooting and not fiddle with 15 cable connections and 28 knobs on different instruments. So you will want to get an instrument that takes you from antenna input to speaker, and from mike to antenna load in one neat package.

To top that off, the complete CB42 is hundreds of dollars below the nearest competition, and thousands below most. We've got our competition beat, and you'll beat your competition, too, by saving these six ways with this CB42 Profit Center.

\$AVE ON REPAIR TIME:

One simplified tester in a single case saves time on every test on any CB that comes in your door, including Single Sideband sets; you won't even need a scope.

\$AVE ON BENCH SPACE:

The CB42 takes less than one-third the bench space of other equipment. You can even take it to the field with you, for on-the-spot mobile checks, since it is also 12 Volt battery powered.

\$AVE ON ANNOYING HOWL:

Why get a screwdriver in the back from the guy next to you, when you can substitute for that annoying speaker howl? Just plug the built-in speaker sub cable into the transceiver and quietly monitor the audio output on the meter.

\$AVE ON READOUT TIME:

One direct-reading digital readout saves interpretation time and reading errors. You'll know the CB's frequency, generator frequency, Percent Off-Channel, positive/negative modulation and distortion, RF output, and audio output with a simple flick of a switch. Only the CB42 is this simple and complete.

\$AVE ON TIME CONSUMING CONNECTIONS:

Three cables, provided with your CB42, do the entire job; audio cable, transmitter cable, and receiver cable.

\$AVE ON CHANNEL CHECKING:

Simply rotate the CB42 and CB selectors through all 40 channels and read "percent off center frequency" on the direct-reading digital meter (.005% FCC maximum deviation) in less than two minutes for all 40 channels.



SENCORE

3200 Sencore Drive, Sioux Falls, South Dakota 57107
Phone (605)339-0100

**VALUE LEADERS IN RADIO-TV,
2 WAY AND MRO INSTRUMENTS**

For More Details Circle (6) on Reply Card

electronicsscanner

news of the industry

The first legal sale of a 40-channel CB radio in the United States was credited to Chick Whitfield, owner of the Radio Shack dealership in Tamuning, Guam. On January 1, 1977 at 12:01 A.M. (13 hours before midnight in the continental United States) Whitfield sold the first Realistic 40-channel model CB to Fritz Heiss. The event took place at a New Year's Eve party.

GTE Sylvania has received a contract from the US Army to explore applications for fiber-optics technology in future electronic communications equipment. A team of specialists is studying how hair-thin strands of glass called optical fibers can replace conventional cable and copper wire in tactical defense communications systems. Optical fibers are particularly well suited for defense communications, because of their immunity to electromagnetic interference.

The RCA Service Company recently began a new consumer program to increase customer satisfaction with television set repairs, by making certain that service is provided on the day promised. "When we make a date to visit a customer's home, we'll keep that date. If we fail to keep it, the customer will pay no labor charge," says Sigmund Schotz, Vice President of Consumer Affairs.

Many television manufacturers are "looking at, but keeping away from" video games, according to Retailing Home Furnishings. It is feared that building simpler nonprogrammable games into sets will result in immediate obsolescence because of the rapid production of new video games.

Increased federal regulation must be used to prevent self-destruction of the consumer-electronics industry, according to statements of Raymond Spence, Jr. (chief engineer of the FCC), which were quoted in Retailing Home Furnishings. Many new products radiate signals. Examples are radio-controlled toys, light bulbs of higher efficiency, and video games. Also, the radiation specs of TV receivers and CB radios might require tightening to minimize the RF pollution. Here at ELECTRONIC SERVICING, we are receiving more reports of CB stations being heard on stereo systems and electronic organs, so these concerns about RF interference seem to be justified.

Television sets with permanent VHF antennas must also have permanent UHF antennas as of January 1, 1978. According to the Wall Street Journal, the FCC acted on this ruling in answer to complaints from UHF broadcasters who claim they are placed at a disadvantage. Manufacturers usually ship loose UHF antennas with the set, but if the buyer fails to attach it, UHF channels will not be received.

continued on page 6

Sylvania introduces the first 5-year warranty* on picture tubes.

How can we give you a limited warranty this good?

Because we have complete confidence that our Color Bright 85° picture tubes will outlast this 5-year warranty and keep on giving your customers beautiful pictures.

We produce these tubes on the same equipment as our All-New line which is sold as original equipment to TV set manufacturers.

It's terrific to be able to offer your customers a high-quality tube with a warranty like this at no risk to you. There's good profit in it, too. So get in touch with your local distributor today, and get cracking on your first five years.

***Limited Warranty, naturally.
It doesn't cover labor for replacing a tube.**

GTE SYLVANIA

GTE Sylvania, Electronic Components Group, 100 First Ave., Waltham, MA. 02154

continued from page 4

Johnson Educational Training Packages (JET PACS) are available for in-home or in-shop training on E. F. Johnson CB and two-way communication radios. The JET PACS, costing about \$25 each, come in a variety of audio-visual formats, including film strips with tape cassettes, 3M soundpage 35-MM slides with synchronized audio, and video tape with sound. The subject matter includes circuit analysis, alignment procedures, product familiarization, and digital synthesis. For more information, contact Daryl J. Thompson, E. F. Johnson Technical Education Center, Waseca, Minnesota 56093.

Forest Belt illustrates a point at his first CB Training Workshop in Indianapolis, where he introduced the new Easi-Way™ Servicing Method. A dozen more Workshops are scheduled around the country during 1977, ending with a two-week combination vacation and seminar in Hawaii! For details, write to Forest at Box 68120, Indianapolis, Indiana 46268.




Sony Corporation of America has announced a new schedule of National Video Production Workshops. Seven workshops are scheduled for video users in business, industry, education, government, and medicine. Additional information on the availability and costs of the services can be obtained from Jeff Glasser at Sony, 700 West Artesia Boulevard, Compton, California 90220.

Raytheon has completed the acquisition of Switchcraft, whose 1976 sales totalled \$27 million. Switchcraft manufactures switches, jacks and plugs, audio connectors, and related equipment. The company will be operated as a wholly-owned subsidiary of Raytheon.

A tiny Micro Switch solid-state sensor now used in 1977 Oldsmobile Toronados improves both gas mileage and performance. The Delco Remy Division of General Motors developed the sensor for Honeywell. At the heart of the pressure transducer is a sensor chip of 0.110-inch size. Pressure changes inside the intake manifold of the engine flex the thin membrane of the sensor chip, causing the embedded resistors to change value. Other circuitry changes the resistance variation into a varying voltage, which through the microprocessor adjusts the firing of the spark plugs. It's said that the sensor operation increases the gas mileage by about 1.3 mpg and gives cleaner combustion for less pollution.

Tuner Service Corporation

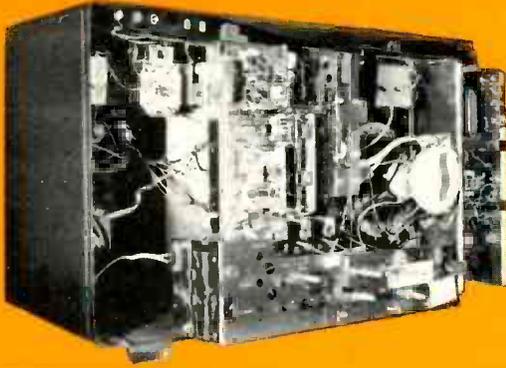

\$10⁹⁵

U.S.A. ONLY

One Year Guarantee

MODULE REPAIRS


TSC has been repairing private brand TV modules for over 2 years.

Expanded facilities now include modules for

- RCA
- GE
- ZENITH
- W. T. GRANT
- J. C. PENNEY
- WESTERN AUTO
- GAMBLES

as well as Zenith IF subchassis.

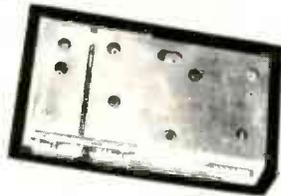For free Price List and complete information write or phone;
TSC HEADQUARTERS, BLOOMINGTON, IND.
or any of the TSC locations listed below.



PROVIDES YOU WITH A COMPLETE SERVICE FOR ALL YOUR TELEVISION TUNER REQUIREMENTS.

REPAIR

VHF OR UHF ANY TYPE (U.S.A. ONLY) \$10.95
UHF/VHF COMBINATION (U.S.A. ONLY) \$17.95

MAJOR PARTS AND SHIPPING CHARGED AT COST.

- Fast, efficient service at our conveniently located Service Centers.
- All tuners are ultrasonically cleaned, repaired, realigned, and air tested.

REPLACE

UNIVERSAL REPLACEMENT TUNER \$13.95 (U.S.A. ONLY)

- This price buys you a complete new tuner built specifically by Sarkes Tarzian Inc. for this purpose.
- All shafts have a maximum length of 10 1/2" which can be cut to 1 1/2".
- Specify heater type parallel and series 450 mA. or 600 mA.

CUSTOMIZE

- Customized tuners are available at a cost of \$14.95 and up. (U.S.A. ONLY)
- Send in your original tuner for comparison purposes to any of the Centers listed below.

SAME DAY SERVICE — ONLY ORIGINAL FACTORY PARTS USED



| | | | |
|---------------|-------------------------------|-------------------------------------|-------------------|
| HEADQUARTERS | BLOOMINGTON, INDIANA 47401 | 537 South Walnut Street | Tel. 812-334-0411 |
| ALABAMA | BIRMINGHAM, ALABAMA 35212 | 5623 1st Avenue North | Tel. 205-592-9150 |
| CALIFORNIA | NORTH HOLLYWOOD, CALIF. 91601 | 10654 Magnolia Boulevard | Tel. 213-769-2720 |
| | SAN MATEO, CALIF. 94402 | 600 S. Amphlett Blvd. | Tel. 415-348-3292 |
| | MODESTO, CALIF. 95351 | 123 Phoenix Avenue | Tel. 209-521-8051 |
| FLORIDA | TAMPA, FLORIDA 33606 | 1505 Cypress Street | Tel. 813-253-0324 |
| | FT. LAUDERDALE, FLORIDA 33309 | 3516 N.W. 10th Ave. | Tel. 305-566-4882 |
| GEORGIA | ATLANTA, GA. 30310 | 646 Evans St. S.W. | Tel. 404-758-2232 |
| ILLINOIS | URBANA, ILLINOIS 61801 | 908 E. Main Street | Tel. 217-384-2052 |
| | SKOKIE, ILLINOIS 60076 | 5110 West Brown Street | Tel. 312-675-0230 |
| INDIANA | INDIANAPOLIS, INDIANA 46204 | 112 West St. Clair Street | Tel. 317-632-3493 |
| KENTUCKY | LOUISVILLE, KENTUCKY 40205 | 2244 Taylorsville Road | Tel. 502-452-1191 |
| LOUISIANA | SHREVEPORT, LOUISIANA 71104 | 2423 Southern Avenue | Tel. 318-221-3027 |
| MASSACHUSETTS | SPRINGFIELD, MASS. 01108 | 405 Dickinson St. | Tel. 413-788-8206 |
| MISSOURI | ST. LOUIS, MISSOURI 63132 | 9577 Page Avenue | Tel. 314-429-0633 |
| NEVADA | LAS VEGAS, NEVADA 89102 | 1412 Western Avenue | Tel. 702-384-4235 |
| NEW JERSEY | TRENTON, NEW JERSEY 08638 | 1139 Pennsylvania Ave. | Tel. 609-393-0999 |
| | GERSEY CITY, NEW JERSEY 07307 | 454 Central Ave. | Tel. 201-792-3730 |
| NEW YORK | ROCHESTER, NEW YORK 14615 | 37 Pullman Ave. | Tel. 716-647-9180 |
| N. CAROLINA | GREENSBORO, N.C. 27405 | 2914 E. Market Street | Tel. 919-273-6276 |
| OHIO | CLEVELAND, OHIO 44109 | 4525 Pearl Road | Tel. 216-741-2314 |
| OREGON | PORTLAND, OREGON 97210 | 1732 N.W. 25th Ave., P.O. Box 10141 | Tel. 503-222-9059 |
| PENNSYLVANIA | PITTSBURGH, PA. 15209 | 515 Grant Avenue | Tel. 412-821-4004 |
| TENNESSEE | MEMPHIS, TENNESSEE 38111 | 3158 Barron Avenue | Tel. 901-458-2355 |
| TEXAS | DALLAS, TEXAS 75218 | 11540 Garland Road | Tel. 214-327-8413 |
| CANADA | ST. LAURENT, QUEBEC H4N-2L7 | 305 Decade Boulevard | Tel. 514-748-8803 |
| | CALGARY, ALBERTA T2H-1Y3 | P.O. Box 5823, Stn. "A" | Tel. 403-243-0971 |

WATCH US GROW

For More Details Circle (7) on Reply Card


FAST

COMPLETE SERVICE ON ALL MAKES OF TV TUNERS

Maximum Time In Shop 24 Hrs.

(Warranty: One Full Year)

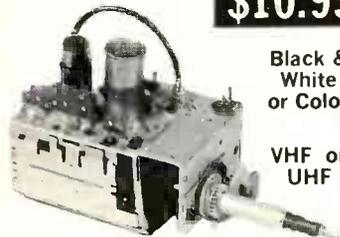(WE SHIP C.O.D.)
YOU PAY SHIPPING
\$10.95



Black & White or Color

VHF or UHF

UV Combo's \$17.95

Price includes all labor and parts except Tubes, Diodes & Transistors. If combo tuner needs only one unit repaired, disassemble and ship only defective unit. Otherwise there will be a charge for a combo tuner. When sending tuners for repair, remove mounting brackets, knobs, indicator dials, remote fine tuning arrangements and remote control drive units.

WE UNCONDITIONALLY GUARANTEE All Tuners FOR ONE FULL YEAR



All tuners are serviced by EXPERTLY TRAINED TECHNICIANS with years of experience in this specialized field. All tuners are ALIGNED TO MANUFACTURER'S SPECIFICATION on crystal controlled equipment and air checked on monitor before shipping to assure that tuner is operating properly.

GEM CITY TUNER SERVICE

Box 6G Dabel Station
1621 Mardon Drive
Dayton, Ohio 45420


troubleshooting tips

Send in your helpful tips—we pay!

No Raster, no HV
Zenith Chassis 12A12C52
(Photofact 1120-3)

For the first test, I used my B&K Model 1077B Analyst to supply plate drive to the flyback, and found the raster and HV were restored. Next, the DC voltage at the control grid of the horizontal-output tube was measured and found to be within tolerance. From this, I assumed the horizontal oscillator was working okay.

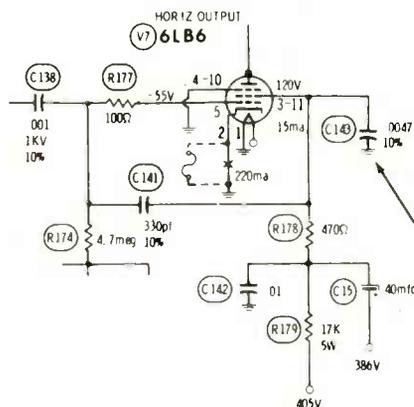My conclusion was that the trouble must be in the wiring or components of the horizontal-output tube, since the circuit appeared to be normal on both sides.



Finally, I checked the DC voltage at the screen grid (should be 120 volts), but found only about 25 volts. I tried three separate output tubes, but with no change of symptoms. However, an ohmmeter test showed only about 1,000 ohms from the screen (pins 3 and 11) to ground. Of course, that's much too low. I removed the output tube from its socket, and short was gone.

Although I didn't really understand the full implications of that last test, I tried to find the short by disconnecting all of the components from the screen grid pins, while monitoring the voltage at the screen. The voltage did not rise properly until I disconnected C297. Yes, the capacitor checked very leaky.

The thing that fooled me was that C141 and R178 were soldered to pin 3, while C297 connects to pin 11. I was checking the DC voltage

at pin 3, so the internal jumper of the tube showed a short with the tube in socket, but no short with the tube removed.

The moral is to watch out for internal jumpers in the tubes.

Richard Sanderford, CET
Raleigh, North Carolina

Don't cut yourself out of a career as a two-way radio technician...

MTI offers the only training for professional FM two-way radio available. Qualified technicians are employed in government, industry, and public service. But training is your key.

You could cut out a career as a two-way radio technician by cutting out this coupon. We'll send you information on how you can learn more about this specialized field, at home.

Name _____
Address _____
City/State/Zip _____
 I am a veteran or serviceman on active duty. CCB



formerly

MOTOROLA TRAINING INSTITUTE

College Hill, Summerdale, Pennsylvania 17093

For More Details Circle (19) on Reply Card

IT'S NO PUZZLE TO ORDER

OELRICH SERVICE FORMS

FOR TV-RADIO & 2 WAY RADIO SERVICE LEGAL FORMS FOR CALIF. FLA. UTAH NOW AT YOUR PARTS JOBBER OR WRITE FOR CATALOG B64

OELRICH PUBLICATIONS

4040 N. NASHVILLE AVE. CHICAGO, ILLINOIS 60634

For More Details Circle (32) on Reply Card

FREE ALARM CATALOG

Huge selection of burglar & fire systems, supplies. Motion detectors, infrared beams, controls, door switches, bells, sirens. 900 items, 64 pp. packed with technical details, notes.

Phone (602) 263-8831

mountain west alarm

4215 n. 16th st., phoenix, az. 85016

For More Details Circle (31) on Reply Card

ELECTRONIC SERVICING

GE designed its new VIR system to make you a living room hero.



Simply join bypass plugs to keep the set working.

General Electric's new VIR Broadcast Controlled Color system is a true breakthrough for the consumer. But we also designed it to make your business easier.


All the sophisticated VIR control circuits are on one plug-in module which you can bypass and remove in minutes. The set keeps working with manual color controls while you exchange or repair the module. Simple service instructions are packed with each set.

At last, an advanced color control system designed to make your servicing easier. It helps you get the set back in action in less time than your customer expects. And that's the stuff heroes are made of. It's our business to make your business easier.

 **performance**
TELEVISION

SIMULATED TV PICTURE AND WOOD CABINET.

GENERAL  ELECTRIC

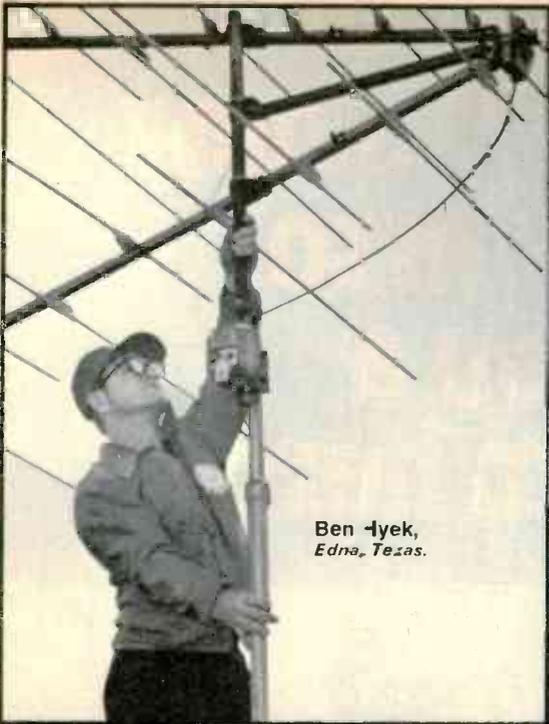


Ben Hyek,
Edna, Texas.



Dean Johnson and Pete Childers,
Joliet, Ill.




John Buckner,
Lyndon, Ky.

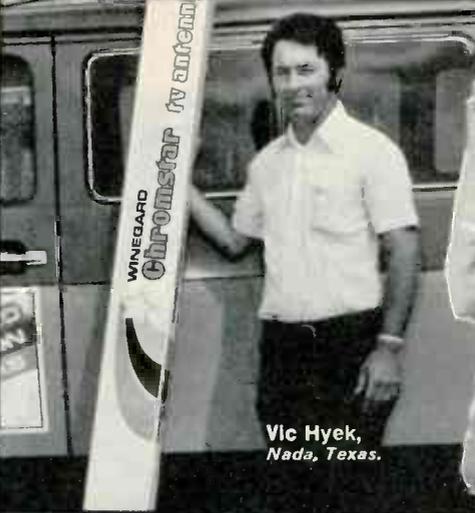

Vic Hyek,
Nada, Texas.



Bill Hughes,
Norville, Florida.

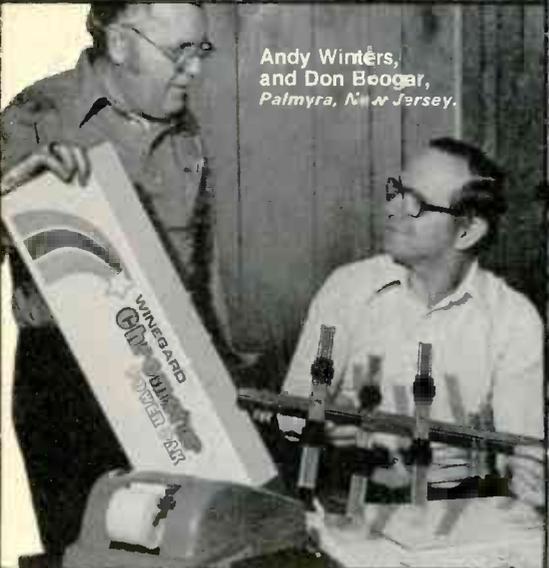

**Andy Winters,
and Don Boogar,**
Palmyra, New Jersey.



WINEGARD WORKS...For Me!

Here are 10 of the reasons why WINEGARD WORKS...For ME!

- 1. Winegard PRODUCTS work for me.** Variety as well as quality in the complete line of TV reception products is important to me. I can take care of my customers, with confidence. Winegard engineering research innovates new products to solve problems, or improve TV reception, as I found with the new low noise UHF preamp-antenna combination.
- 2. The Winegard NAME works for me.** It gives me the top national brand name in my business, to sell, install, and recommend. When you are in your own business, you have to have a manufacturer back of you that you can depend on.
- 3. The Winegard REPUTATION works for me.** Most all my customers and prospects know the Winegard name, and know their products are excellent. This consumer acceptance makes my selling job easier than it would be with an unknown or lesser known brand.
- 4. Winegard's MARKETING works for me.** Their advertising, publicity and promotions reach customer prospects and create sales opportunities for me. Winegard helps build my business.
- 5. Winegard INFORMATION works for me.** Winegard communicates with me, through distributor meetings, trade advertisements, product announcements, technical articles by their engineers, and with their Dealer Newsletter.
- 6. Winegard DISTRIBUTION works for me.** My local distributor carries Winegard products in stock so I can always get what I need, fast.
- 7. Winegard PROFITABILITY works for me.** Winegard has stayed in business for over 20 years because they make the finest products, and because they make a profit. They expect me to make a profit, too. With the right products, and my experience, I do make a good profit.
- 8. Winegard SALES HELPS work for me.** Literature, sales tools, ad materials and displays are available to me, to promote and secure new business. My store, truck, and uniform also identify me as a Winegard antenna dealer. This all helps me cash in on Winegard advertising.
- 9. Winegard RELIABILITY works for me.** Winegard's manufacturing facilities, research capabilities, product testing, quality control, and delivery via their own truck fleet are aimed at getting to me the kind of reception products I need to satisfy my customers. They count on me. I count on Winegard.
- 10. Winegard INSTALLATIONS work for me, too.** Whenever I install Winegard products, I can count on the customer being satisfied. I also expect to get additional business from that customer's neighbors and friends. And that's the best part . . . when your customers recommend you.


Winegard works . . . for professional installers all over the country. Just call your Winegard distributor, or write to us. Let us work for you.



WINEGARD


The Winegard Company • 3000 Kirkwood • Burlington, Iowa 52601

Chassis—Sylvania E08
PHOTOFACT—1481-2

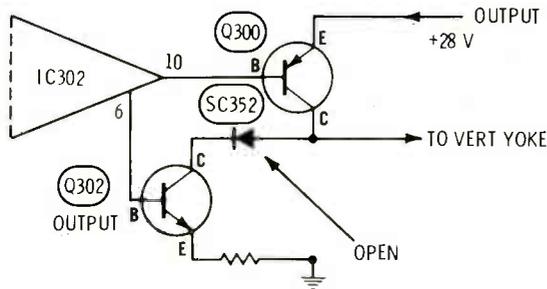


Symptom—Drive to IC302 okay, but no vertical sweep
Cure—Check diode SC352, and replace it if open

Chassis—Sylvania E10
PHOTOFACT—1477-3

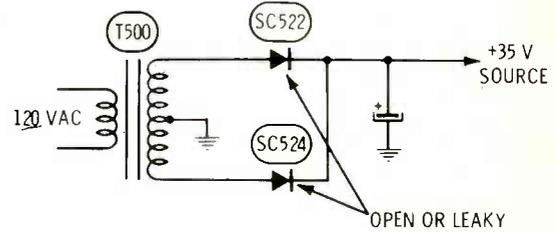


Symptom—Single hum bar in picture
Cure—Check SC522 and SC524, and replace them if leaky or open

Chassis—Sylvania E02
PHOTOFACT—1324-3

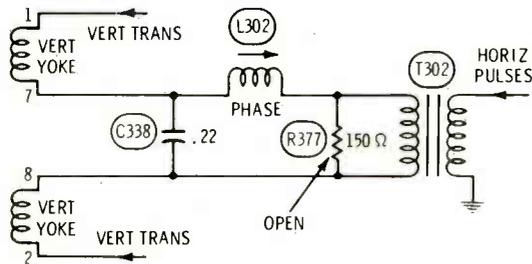


Symptom—Excessive height near center of picture
Cure—Check R377, and replace it if open or increased

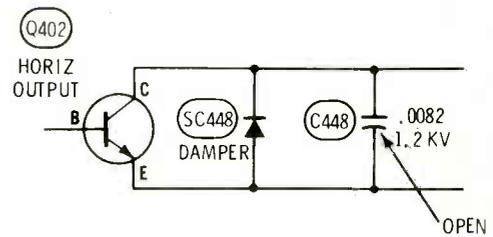Chassis—Sylvania E06, etc.
PHOTOFACT—1432-3




Symptom—HV arcing, or excessive HV
Cure—Check C448, and replace it if open (part #45-33037-13)

Chassis—Sylvania D05
PHOTOFACT—905-3

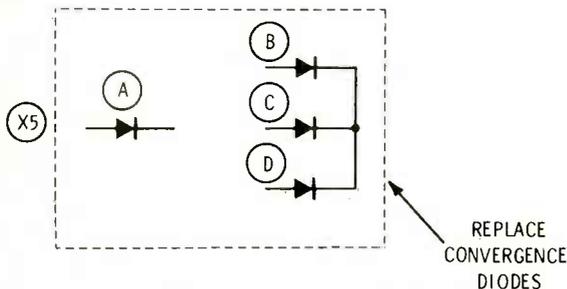

Symptom—Erratic height, or bottom foldover
Cure—Replace assembly of diodes on the convergence board

Chassis—Sylvania D06
PHOTOFACT—1072-2

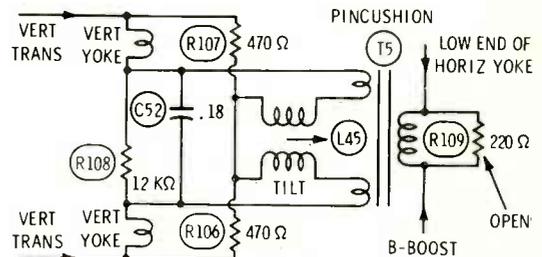

Symptom—Rounded vertical bars at left edge of picture
Cure—Check R109, and replace it if open or increased

reader's exchange

There is no charge for listing in *Reader's Exchange*, but we reserve the right to edit all copy. If you can help with a request, write direct to the reader, *not to Electronic Servicing*.

Needed: Service manuals for electronic organs, all makes and models. Quote price, and conditions of sale.

Bill Cushing
630 NW 11th Avenue
Boca Raton, Florida 33432

Needed: Schematic and/or service manual for Sencore CG10 color bar generator. Will buy, or copy and return.

Lloyd Stoops
RT 3 Box 127-B
Foxworth, Mississippi 39483

Needed: Schematic or owner's manual for RCA six-band radio, Model RLM-77A, Serial #80550012.

John Brouzakis
RD 2 Box 602B
Charleroi, Pennsylvania 15022

Needed: For my antique-radio library: old text books: old Rider, Gernsback, Supreme, and factory man-

uals; magazines from the '20's and '30's. Please describe what you have and price wanted.

Lawrence Beitman
1760 Balsam Road
Highland Park, Illinois 60035

Needed: Two 6N6G tubes; also Sentinel radio Model 344, part number 35E34-pointer.

K. W. Hamilton
Route #1 Box 66-3
Friendly, West Virginia 26146

Needed: "Electronic Organs, Volume 2" written by Norman Crowhurst. Sams book number 20754, now out of print.

M. W. Scheldorf
835 First Avenue, Box 84
Marseilles, Illinois 61341

For Sale: Back issues of *Electronic Servicing* from 1970 to present, 20 cents per copy, or 10 cents per copy for all.

Louis J. Kozelsky
115 Iroquois Lane
Liverpool, New York 13088

Needed: E. H. Scott radios, parts and literature. Would like correspondence with owners.

Robert Fabris
3626 Morrie Drive
San Jose, California 95127

continued on page 16

Built to last

Our new 3½-digit LED autopolarity digital VoltOhmyst® is quality-constructed for long, hard service.



WD-750A
\$267.00

- Fast and accurate measurement of ac and dc volts, current, and resistance.
- Built-in analog panel meter for peaking and nulling.
- Hi- or Lo-power ohms selector.
- 120V/240V ac or battery operation with built-in charger.
- RF shielded, with rugged vinyl-clad case.

**VIZ Test
Instruments Group**

of VIZ Mfg. Co.

335 E. Price St.
Phila. PA 19144

6645

Formerly
RCA
Instruments

Be a SuperTech... Get RCA's new Module Kit for the 1977 "XtendedLife" chassis series.



Readers' Exchange continued from page 15

Needed: A good, used 440MB4 B&W CRT. Also, a source for other used CRT's.

M. B. Danish
Mike's Repair Service
P.O. Box 217
Aberdeen Proving Ground,
Maryland 21005

Needed: Schematic for Dumont stereo Model 511, Series B.

E. W. Dennis
3830 Bernard Place
Columbus, Ohio 43224

Needed: 189-KHz crystal, plug-in type for a Precision color-bar generator, Model E-450.

E. W. Dennis
3830 Bernard Place
Columbus, Ohio 43224

Needed: Schematic for Shield VOM, TE-97. Will buy, or copy and return.

William B. David
209 Fir Avenue
Montgomery, Minnesota 56069

Needed: Horizontal-output transformer for a Waltham portable color TV, Model CP15W. Part can be new or used, but good.

Maurice M. Bolin
2315 El Toro Circle
Hemet, California 92343

For Sale: Most issues of *Electronic Servicing* and *Radio-Electronics* for the past 25 years. Any reasonable offer.

Paul Smith
44 West Drive
New York Mills, New York 13417

Needed: A schematic of Stromberg-Carlson AU-29 amplifier. Will buy, or copy and return.

Martin H. Cecil
5305 Sheffield Drive
Owensboro, Kentucky 42301

For Sale: Two B&K 1076 analyzers, \$150 each; RCA audio signal generator WA44B, \$25; RCA RF signal generator WR49B, \$25; Eico 460 scope, \$75; Eico 324 VTVM (new probe), \$50; and B&K 360 VOM, \$25. Most equipment with cables and manuals.

Duane M. Gage
Box 202
No. Truro, Massachusetts 02652



Be prepared to make service calls faster than a speeding bullet. The new RCA 199045 Module Kit, available for a limited time at a special introductory price, contains 8 modules for quick and easy servicing of the new 1977 color TV sets. This new kit, plus your ColorTrak and XL-100 Module Kits, lets you fix most RCA sets right in the customer's home. You'll save time, make more service calls per day, and earn more profit.

Be an RCA SuperTech — carry these 3 RCA Module Kits and meet almost all RCA color-module needs. All 3 kits contain RCA replacement modules which include the

latest design improvements. And don't forget the RCA Module Caddy — makes it easy to carry all three kits on home service calls.

See your authorized RCA Parts Distributor, or contact RCA Distributor and Special Products Division, 2000 Clements Bridge Road, Deptford, NJ 08096, for additional information.

RCA Distributor and Special Products Division

For More Details Circle (10) on Reply Card

Trade: One manual for S-54 and S-54/AR tele-equipment scopes to trade for an S-52 manual. Or, send price for S-52 manual.

R. P. Frohwerk
TV Industries
4330 SE Woodward Street
Portland, Oregon 97206

Needed: A complete set of original manufacturer's test leads in new condition for an RCA Model WV-97A.

Paul Capito
637 West 21 Street
Erie, Pennsylvania 16502

Trade: B&K Model 415 solid state sweep/marker generator for B&K Model 1077B television analyst.

Ronald Olcott
7616-4 Sewells Pt. Rd.
Norfolk, Virginia 23513

Needed: Schematic for a Curtis Mathis B&W TV Model 55M 2733.

Peter J. Golumbus
64 Coolidge Street
Irvington, New Jersey 07111

For Sale: RCA Model WO535A DC-10 MHz scope, \$185. Lectrotech Model TO 50-MHz triggered sweep scope, \$195.

Ronald Olcott
7616-4 Sewells Pt. Rd.
Norfolk, Virginia 23513

For Sale or Trade: PF Reporter and Electronic Servicing 1963 to 1977 for Sencore sweep-marker generator, Model SM-152.

Steve Topley
145 Quarry Street
Mt. Pleasant, Pennsylvania 15666

Needed: Schematic and alignment information for Knight Kit, Model #83Y102000 radio receiver. Will pay reasonable price.

Herbert Naugle
1792 Finch Court
Hayward, California 94545

Needed: Manual (or copy) for MITS sweep marker MG-1K.

M. W. Scheldorf
835 First Avenue Box 84
Marseilles, Illinois 61341

Servicing GE Modular Color TV

Part 7/By Gill Grieshaber, CET



VIR-Controlled Color

The editor strongly suggests you carefully study these articles about the new General Electric system of automatic color that's controlled by the condition of the VIR signal from the station. Not only is it a unique circuit that all technicians need to understand for purposes of servicing, but also it is the forerunner of many other digital circuits. We need to understand practical digital circuits, and how to troubleshoot them. This first article covers the counter for identification of Line 19, where the VIR signal occurs, and the so-called "slicers" that produce the keying pulses of the correct width and phase.

Stampede For The Vertical-Retrace Space

Of the 525 horizontal-scanning lines, just 504 have video, and the remaining 21 lines originally had nothing by vertical-sync pulses in this barren area set aside for vertical blanking and retrace. But only 9 lines are needed for the vertical sync of each field, leaving 12 empty lines. Lately, the trend is toward filling these lines.

A few years ago, an observant TV technician might have noticed some strange dots and lines just above the top of the picture (see Figure 1). On the face of a picture tube, these shapes are without meaning, for they are intended for viewing on special oscilloscopes. Figure 2 shows three different kinds of Vertical-Interval Test Signals (VITS), which at first were on lines 18 and 19 of each field. The patterns were selected to show any video defects (such as poor frequency response, ringing or poor transient response, and variations of amplitude linearity) occurring in the network lines. Similar patterns still are used today, but they have moved to lines 17 and 18. TV stations operating by remote control must use VITS to check the operation of the Studio-Transmitter Link (STL). Other uses are optional.

Another VITS blinks one time per second; I don't know its purpose. Also, serious proposals have been made to reserve other lines for

subcaptions for deaf TV watchers. Yes, the retrace time is getting to be very busy. But the most important of these to the viewer is the Vertical-Interval Reference signal (VIR signal).

This VIR signal is very simple (see Figure 3), but it is intended to evaluate color quality only, and does not duplicate or replace the VITS.

In practice, the VIR signal is added to the program video immediately following the point in the originating equipment where the color parameters have been established. Then, the VIR remains with the program, through network lines, video-tape recorders, studio, and TV transmitter. It is never blanked out, as the VITS frequently is. At many stages of the system, the VIR can be observed on special scopes, and corrections made as necessary. In fact, equipment is now available that makes several corrections automatically at the TV transmitter, and shows by meter readout the extent of those corrections!

Perfection?

According to these facts, few or no color level or tint adjustments should be made at each individual TV receiver. Unfortunately, the VIR signal is not mandatory yet. Some programs have it; others do not.

continued on page 20

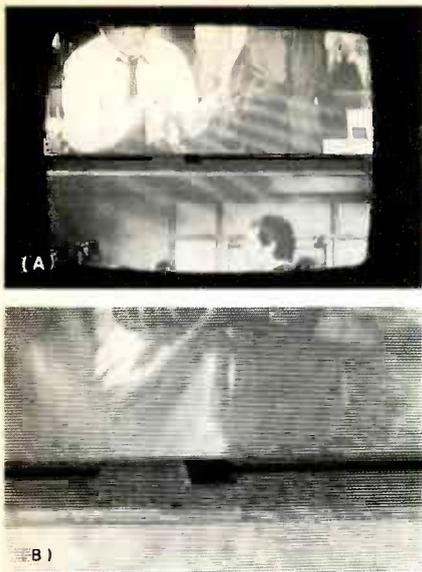


Fig. 1 Although the VITS and VIR signals can be seen at the top of a picture when you reduce the height, the only way to see the entire vertical-retrace area is to slowly roll the picture downward, with the brightness high and the contrast low. **(A)** The broad horizontal bar across the center is the 21 lines of the retrace period, including the black "hammer" (vertical equalizing and sync pulses), and the narrow white lines of the VITS and VIR signals down near the start of the picture. **(B)** This is a closeup of the hammer area. The hammer is useful for analyzing compression or poor vertical sync, but the VITS and VIR signals can't be analyzed profitably from the picture tube; they are intended for scope viewing.


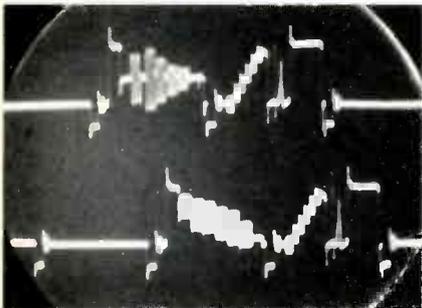


Fig. 2 Here is one of the best pictures I have made of the ABC network VITS waveforms, before the start of the VIR test signal. When a service-type triggered scope is used, the brightness is so low (only 6 lines out of 525 are shown on the screen) that analysis is difficult. (Broadcasting stations have specialized scopes which are better for this job.) Also, the roll-off of the receiver IF curve automatically reduces the high-frequency bursts of signal, as well as reducing the burst amplitude to 50% of what it is at the broadcasting station. These limitations prevent a scope analysis of receiver VITS and VIR signals from being very helpful.

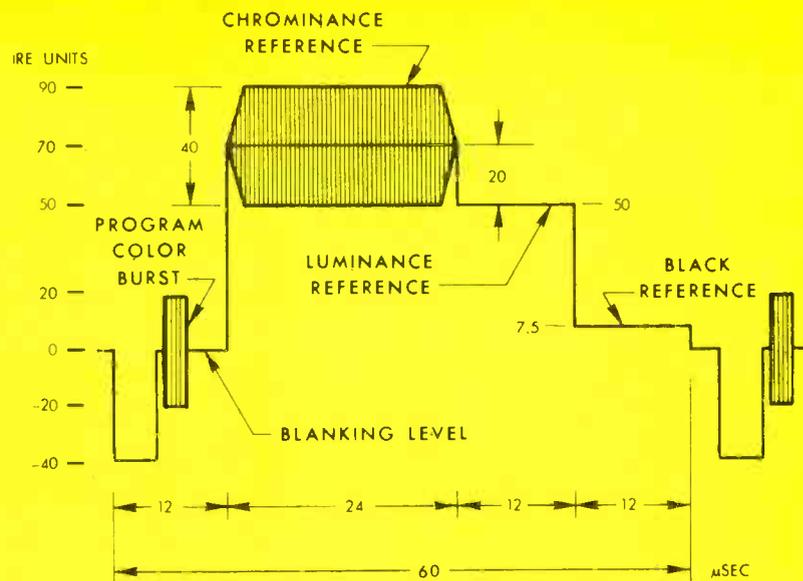

NOTE: THE CHROMINANCE REFERENCE AND THE PROGRAM COLOR BURST HAVE THE SAME PHASE.

Fig. 3 The Vertical-Interval Reference (VIR) signal was designed to evaluate color TV parameters, only. Both the burst and the chrominance portions have the same frequency and phase. That's why the left half of the VIR line in the TV picture is greenish-yellow in color.



Fig. 4 Outwardly, a General Electric color portable appears similar to other new-generation modular TV receivers. The picture quality of our sample was excellent.

VIR

continued from page 18

Fig. 5 Both VHF and UHF tuners share the digital channel readout. When the door over the seldom-used controls is closed, only the VIR LED light, a "custom picture" (combination color and contrast) knob, and the on/off knob can be seen (A). An open door (B) reveals an on/off sliding switch for the VIR function, a brightness knob, plus manual color and tint knobs.



And this brings us to the need for a unit in TV receivers that can correct color and tint by analyzing the VIR signal (which was intended for station use).

Just now, only General Electric has such a unit. The feature is called "VIR Broadcast-Controlled Color" and it is available in certain GE receivers using the YM and YC-2 color chassis. Although GE has an excellent training manual covering the VIR circuitry, we will present a slightly different viewpoint, based in part on my own measurements and scope patterns.

Digital circuitry is used extensively; however, you should not find it too difficult to understand. Even if you don't intend to service sets that have the VIR circuitry, the circuit analysis can serve as good practice for the digital circuits (such as digital video, etc.) to come.

General Electric With VIR Circuits

The picture of a GE 19-inch color TV receiver in Figure 4 does not seem to be very unusual. But if you look more closely, you find a VIR LED light, and an on/off switch for VIR (Figure 5).

When a color broadcast lights the LED a brilliant red, and the VIR switch is moved to "on", the color and tint controls under the door have no effect on the picture, when you turn them. Instead, the VIR signal on video Line 19 controls the color level and tint, subject to a minor amount of variation possible if you adjust the "color preference" controls that are located on the cabinet back, near the top. When the program has no VIR signal, the LED is dark, and the front-panel color and tint controls operate conventionally. Of course, you can slide the VIR switch to "off", leaving the VIR light glowing, and the color can be controlled manually by the front-panel knobs.

The first time you operate one of these models, you probably will switch back and forth often, trying the response of the controls, and watching curiously to see if the VIR system actually works effectively. I must confess that I certainly did!

continued on page 22

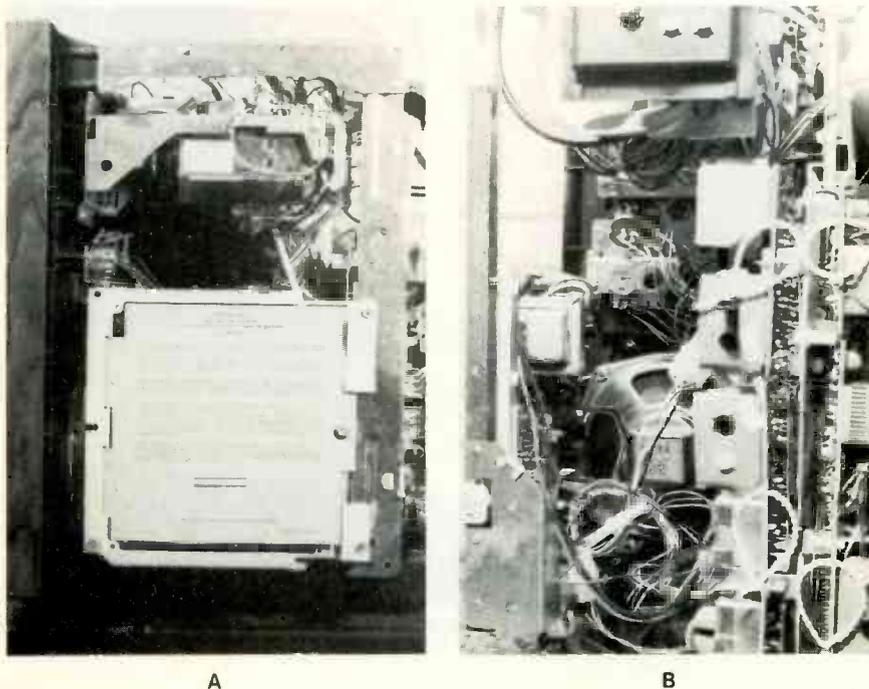


Fig. 6 A cardboard with instructions for using the VIR feature covers the VIR module (A) that's mounted below the tuners. Console models have the VIR module mounted horizontally, under the picture tube. You can see part of the VIR module (B) by looking to the left of the IF module.

CB servicing is PROFITABLE with the B&K-PRECISION 40-channel CB Test Bench



MODEL 1040
\$260

The B&K-PRECISION CB service-master is designed for rapid programmed testing and trouble shooting of any CB transceiver—even 40-channel models!

When used with a scope and signal generator, you can:

- Measure signal-to-noise ratio of CB receiver
- Measure audio output power
- Measure audio distortion percentage
- Measure receiver sensitivity
- Check AGC
- Measure effectiveness of CB noise limiter or blanker (when used with an impulse noise generator)
- Measure squelch threshold
- Measure adjacent channel rejection on any channel
- Measure transmitter AM power output—even mobile!
- Measure SSB power output with TRUE peak-reading RF Wattmeter
- Check AM modulation
- Check SSB modulation with a two-tone test—the only accurate way!
- Measure antenna SWR—even mobile!
- Check the transceiver in the car to determine if the problem is in the antenna system or the transceiver

You can save \$500—\$1,500 in equipment costs because the CB Servicemaster eliminates many of the test instruments you would otherwise need for CB servicing. These instruments, or their functions, are built into the unit:

- Audio wattmeter • Audio generator • Distortion meter • RF wattmeter/dummy load • DB meter • SWR bridge

These instruments—which you should have, if you don't own them already, are all you need to get the maximum use from your CB Servicemaster. And the B&K-PRECISION CB Servicemaster is compatible with most oscilloscopes, frequency counters, signal generators and power supplies on the market today.



MODEL 1403A—3", 5 MHz
Recurrent Sweep Oscilloscope

Checks CB modulation and provides viewing of 27MHz CB envelope when used with the Model 1040. Small, compact and inexpensive, it frees other scopes for more effective use. **\$219**




MODEL 1640—Regulated Power Supply

Designed especially for CB and other mobile equipment, the 1640 eliminates changes in supply voltage due to load variations. A stable power supply is essential to precise testing of the transceivers. Less than 0.8% variation from zero to full load, 3 amps continuous, 5 amps surge. Adjustable to any output from 11 to 15 VDC. Suppressed zero scale for greater accuracy. Overload protected. **\$100**



MODEL 1801—
Digital Frequency Counter

To quickly determine the exact frequency of a CB channel, the 1801 automatically displays it for you in large, easy-to-read digits. You can tune oscillators precisely, conduct audio frequency analysis tests. Six digit display is updated five times per second. Accuracy guaranteed to 40MHz; 60MHz typical. **\$240**

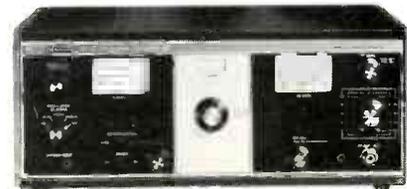

MODEL 2040—40-Channel CB Signal Generator

Covers all 40 channels, AM and SSB with built-in capability. Ultra-stable crystal-controlled, phase-locked-loop frequency generation. Has 5 ppm accuracy. Output attenuator and vernier provide calibrated outputs from 100,000 μ V to 0.1 μ V for receiver sensitivity measurements. Includes EIA standard noise test signal generator to check receiver noise suppression. Internal 400, 1000 and 2500 Hz modulating frequencies—can also be externally modulated. Internal protection against 5W RF input. **\$475**

B&K PRECISION DYNASCAN CORPORATION
Makers of Cobra CB Equipment

6460 W. Cortland Avenue, Chicago, Illinois 60635 • 312/889-9087
In Canada: Atlas Electronics, Ontario

For additional information, contact your B&K-PRECISION distributor for our comprehensive brochure describing the operation of the Model 1040 CB Servicemaster and the CB Service Center—or write us for your free copy.

For More Details Circle (11) on Reply Card

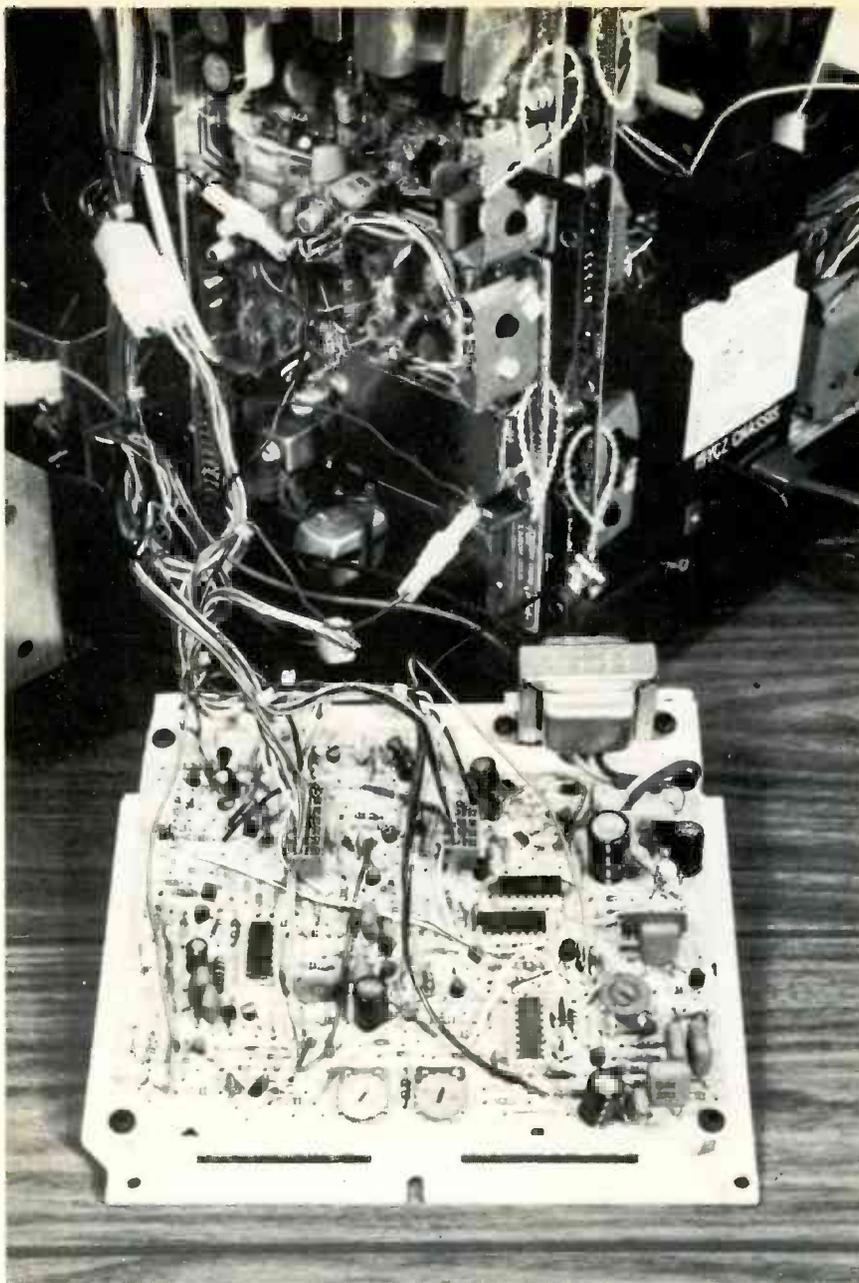


Fig. 7 Wires to the many plugs and connectors are long, allowing the module to be positioned behind the main chassis, when examination or testing is needed.

VIR

continued from page 20

After the back of the receiver is removed, you might not notice immediately any striking differences from a GE YC-2 chassis without VIR. However, on the side under the tuners is a piece of cardboard (Figure 6A) which says in part: "Read before servicing. Do NOT remove this label." The notice continues by giving a short course about how to operate the VIR controls.

If you peek between the IF module and the cardboard, you can

get a partial view of some kind of circuit board (Figure 6B). Remove four screws, and the module can be removed for your inspection (Figure 7).

VIR Module

The General Electric EP93X101 module for controlling color and tint from the Line-19 VIR signal has 30 transistors and 5 IC's on a circuit board that's approximately 7-inches square.

Length of the connecting wires is sufficient to permit the module to be positioned behind the chassis, where you can examine it or make

tests without being cramped for space. Speaking of the wires, it's possible to operate the receiver without the VIR module. Disconnect all of the cables to the module, then connect two certain chassis plugs together. Of course, there is no automatic color action, but the manual controls operate normally. This could prevent any interruption of the customer's TV entertainment while you repair the module or obtain a replacement.

Background theory

From mathematical formulas, the GE design engineers have determined these two facts:

- When the chrominance reference and the black-level reference of the VIR signal (see Figure 3) have identical amplitudes in the R-Y signal of a color receiver, **the tint matches that of the program at the time of origination;** and
- When the amplitudes of the VIR chrominance reference and the black-level reference are equal in the blue drive signal (for example, B-Y plus Y), **the color level (saturation) conforms to the original.**

Therefore, the VIR module operates to compare those important amplitudes. When they are **not** equal, an error-correcting DC voltage is produced to change automatically the color gain or tint phase until the amplitudes are matched. Also, other circuits switch from manual to VIR control when the program contains a VIR signal.

These basic objectives seem simple, until you remember that Line 19 occurs only twice in each frame of two fields! That means the circuit has only 60 chances in every second for making any needed corrections.

Basic circuits

Circuits of the VIR module divide naturally into five basic categories:

- The first circuit starts with the vertical sync pulse of each field and counts digitally up to Line 19. That "identifies" Line 19, then slicers produce the required pulses of partial line width;
- Next, the "VIR sensor" circuit checks to determine if Line 19 has a VIR waveform or not. If yes, DC voltages switch in the color and tint comparators and turn off the

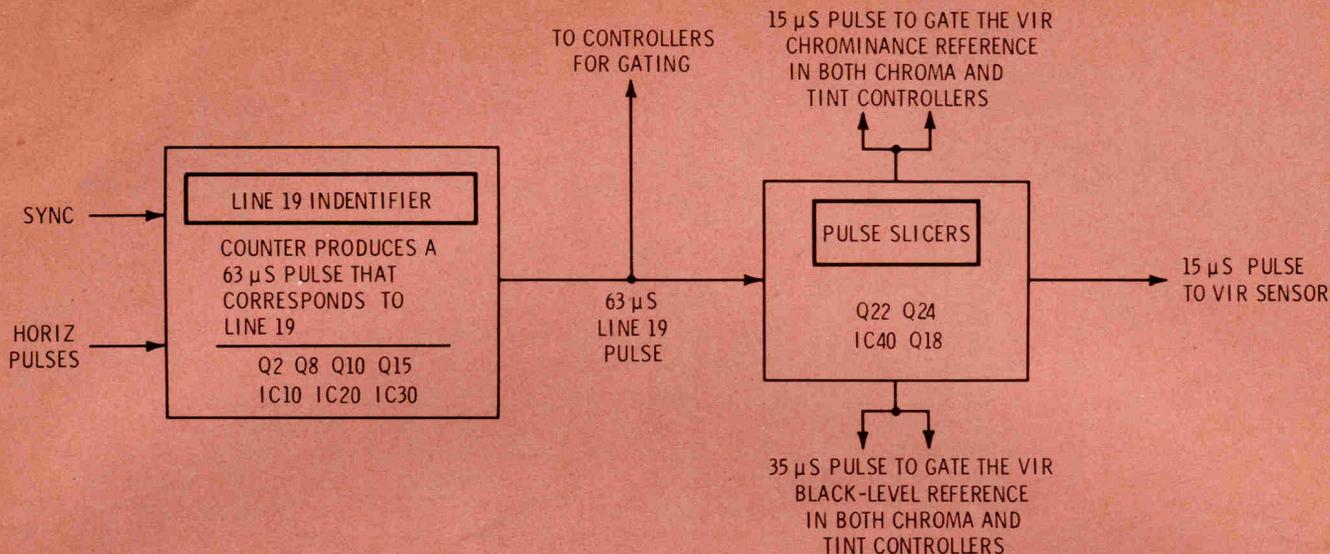


Fig. 8 The block diagram shows the stages we will examine this month. A combination of transistors and IC's, as well as both linear and digital techniques, are used throughout the VIR stages.

manual controls. If no, the DC voltages are reversed to switch on the manual controls and switch off the automatic color and tint controllers;

- In the "tint controller" section, the sliced pulses allow segments of the VIR waveform to enter a comparator at the proper time. From the amplitude comparison comes a DC voltage which determines the VIR automatic tint adjustment;

- Operation of the "color controller" is similar, but the input signal is different, and the output DC voltage determines the color level; and
- Some DC power-supply voltages come from the main chassis; others are developed by the power transformer and rectifier/filter/regulator system on the VIR module.

Of course, only the most important functions are listed here. The complete explanations show many refinements and details.

Identifier Of Line 19

Figure 8 shows a block diagram of the "Line 19 Identifier" and "Pulse Slicer" sections. Notice particularly the inputs and outputs. The identifier stages not only locate Line 19, but also they produce a 63-microsecond pulse that corresponds to the location of Line 19. (Remember that one horizontal line

for color has a duration of 63.56 microseconds.)

From this pulse that has the width and location of Line 19, the slicer circuits produce 15-microsecond and 35-microsecond pulses to be used for keying-on the comparators.

Counting to line 19

Numbering of the lines of each vertical field begins with the 6 equalizing pulses that occupy lines 1, 2, and 3 just before the 6 serrations of the vertical sync pulse. This serrated vertical sync pulse (lines 4, 5, and 6) of each field is the start of the counting to Line 19. As we go through the following explanation, notice the similarity to the sync for vertical-deflection oscillators.

A complete schematic of the "Line 19 Identifier" and "Pulse Slicer" stages is in Figure 9.

Sync from the regular separator enters at R1, and goes to Q2, which is wired as an emitter follower, giving isolation and impedance matching. The incoming clipped sync has a DC component that provides the base bias of Q2. Following Q2 is a two-section integrating network (R3, C3, R4, C4) that forms a kind of triangular wavelike shape from the vertical sync, and this signal is passed along to Q8.

Q8 has a heavy forward bias so it

operates completely saturated before the signal from the integrator reaches the base. The negative-going vertical-sync waveform cuts off Q8's C/E current, forming a large positive-going pulse at the collector. The pulse is filtered a bit before it reaches the base of Q10. Q10 has no base bias except as provided by the Q8 collector voltage. So, Q10 is cut off, except during the sync pulse.

Both Q8 and Q10 are pulse generators, and they work together as a team to produce (at the collector of Q10) a negative-going 520 microsecond pulse (about 8 lines) that starts between lines 4 and 5.

Now, it is absolutely essential for the proper timing of Line 19 that the Q10 collector pulse start precisely at the end of line 4. Therefore, the bias of Q8 is adjustable by means of R7, which is called "delay". This is a factory adjustment, and should not be changed unless vital components are replaced in these stages.

(Because it is easier to describe as a single event, rather than many repetitions, we refer to the Q10 signal as a "pulse", as though there were only one. Actually, a 520 microsecond pulse is generated for every vertical field, or 59.96 pulses

continued on page 24

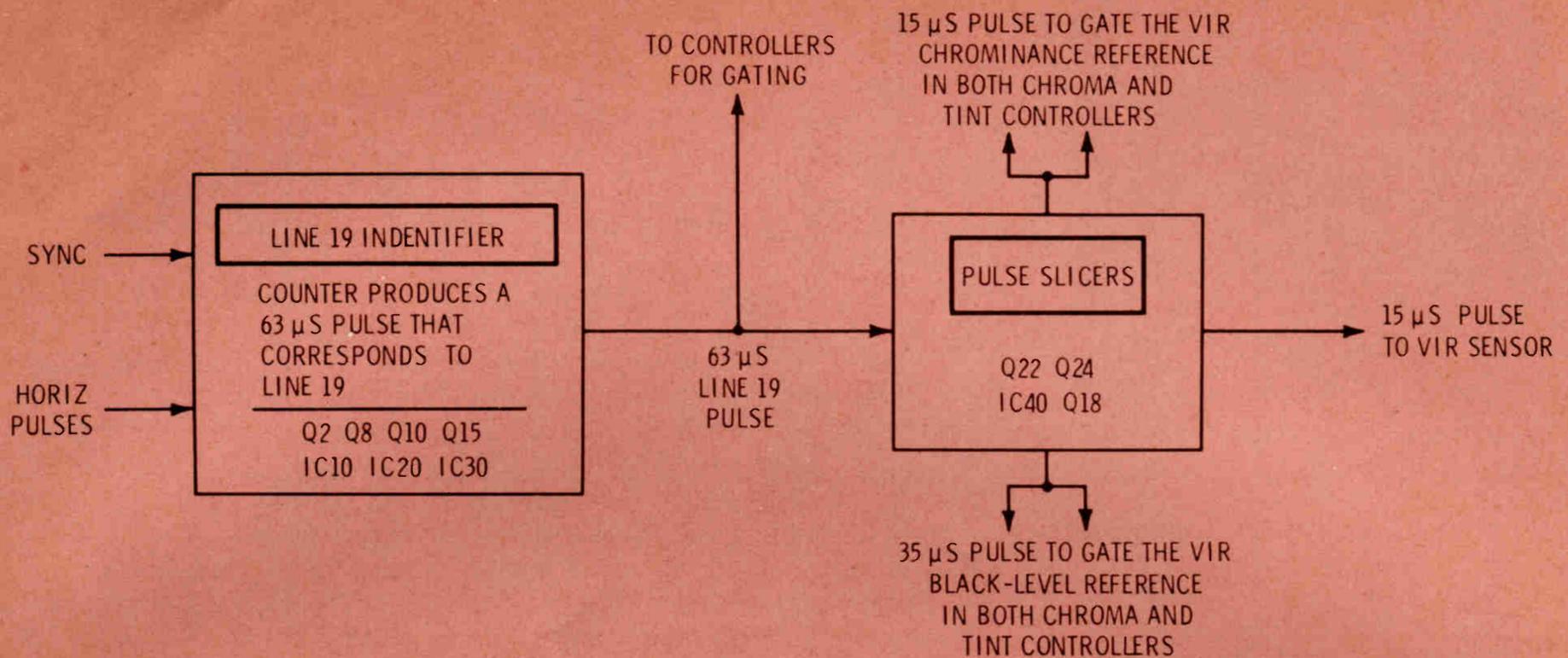


Fig. 8 The block diagram shows the stages we will examine this month. A combination of transistors and IC's, as well as both linear and digital techniques, are used throughout the VIR stages.

manual controls. If no, the DC voltages are reversed to switch on the manual controls and switch off the automatic color and tint controllers;

- In the "tint controller" section, the sliced pulses allow segments of the VIR waveform to enter a comparator at the proper time. From the amplitude comparison comes a DC voltage which determines the VIR automatic tint adjustment:

- Operation of the "color controller" is similar, but the input signal is different, and the output DC voltage determines the color level; and

- Some DC power-supply voltages come from the main chassis; others are developed by the power transformer and rectifier/filter/regulator system on the VIR module.

Of course, only the most important functions are listed here. The complete explanations show many refinements and details.

Identifier Of Line 19

Figure 8 shows a block diagram of the "Line 19 Identifier" and "Pulse Slicer" sections. Notice particularly the inputs and outputs. The identifier stages not only locate Line 19, but also they produce a 63-microsecond pulse that corresponds to the location of Line 19. (Remember that one horizontal line

for color has a duration of 63.56 microseconds.)

From this pulse that has the width and location of Line 19, the slicer circuits produce 15-microsecond and 35-microsecond pulses to be used for keying-on the comparators.

Counting to line 19

Numbering of the lines of each vertical field begins with the 6 equalizing pulses that occupy lines 1, 2, and 3 just before the 6 serrations of the vertical sync pulse. This serrated vertical sync pulse (lines 4, 5, and 6) of each field is the start of the counting to Line 19. As we go through the following explanation, notice the similarity to the sync for vertical-deflection oscillators.

A complete schematic of the "Line 19 Identifier" and "Pulse Slicer" stages is in Figure 9.

Sync from the regular separator enters at R1, and goes to Q2, which is wired as an emitter follower, giving isolation and impedance matching. The incoming clipped sync has a DC component that provides the base bias of Q2. Following Q2 is a two-section integrating network (R3, C3, R4, C4) that forms a kind of triangular wave-shape from the vertical sync, and this signal is passed along to Q8.

Q8 has a heavy forward bias so it

operates completely saturated before the signal from the integrator reaches the base. The negative-going vertical-sync waveform cuts off Q8's C/E current, forming a large positive-going pulse at the collector. The pulse is filtered a bit before it reaches the base of Q10. Q10 has no base bias except as provided by the Q8 collector voltage. So, Q10 is cut off, except during the sync pulse.

Both Q8 and Q10 are pulse generators, and they work together as a team to produce (at the collector of Q10) a negative-going 520 microsecond pulse (about 8 lines) that starts between lines 4 and 5.

Now, it is absolutely essential for the proper timing of Line 19 that the Q10 collector pulse start precisely at the end of line 4. Therefore, the bias of Q8 is adjustable by means of R7, which is called "delay". This is a factory adjustment, and should not be changed unless vital components are replaced in these stages.

(Because it is easier to describe as a single event, rather than many repetitions, we refer to the Q10 signal as a "pulse", as though there were only one. Actually, a 520 microsecond pulse is generated for every vertical field, or 59.96 pulses

continued on page 24

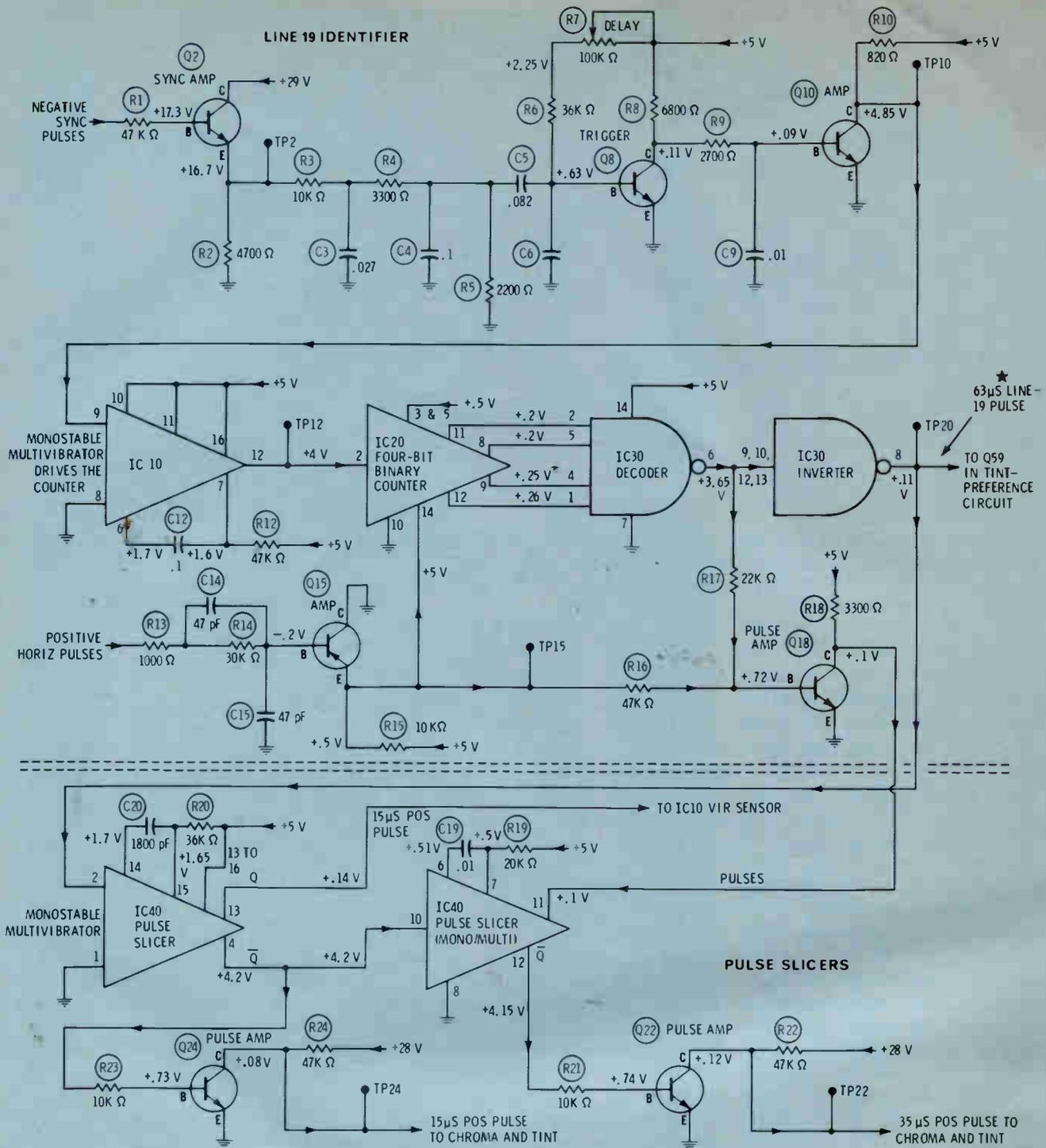


Fig. 9 The use of IC's, whose internal components are not shown on a schematic, makes this full diagram of the Line-19 Identifier and Slicer stages seem less formidable. Therefore, the circuit operation is not difficult to understand.

VIR

continued from page 23

per second. Each pulse is triggered by the vertical sync.)

Figure 10 shows the composite video, sync pulses, integrated vertical sync pulse, and the 520

microsecond pulse at TP10.

One more condition must be established before the digital counting can begin: a negative-going pulse (wide enough to include all of the lines for the counter) must be produced. This wide pulse is generated by half of IC10, which is wired as a monostable multivibrator, and

is triggered by the falling edge of the negative-going pulse at TP10. The width of the output pulse at pin 12 is determined by the values of the network C12 and R12 (they are a time-constant filter).

Although the width of the pulse at the output of IC10 is not critical, it must be slightly wider than 20

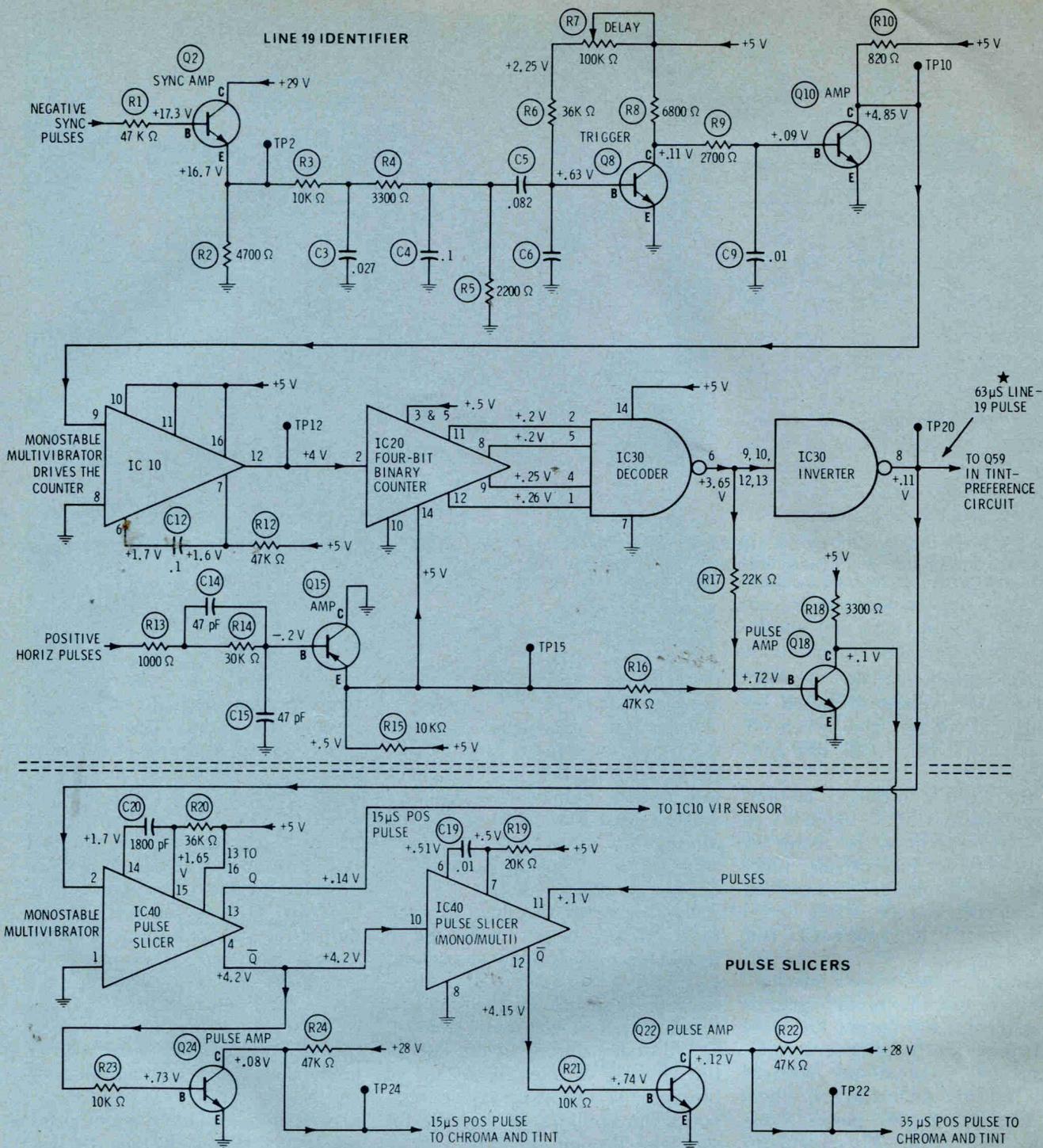


Fig. 9 The use of IC's, whose internal components are not shown on a schematic, makes this full diagram of the Line-19 Identifier and Slicer stages seem less formidable. Therefore, the circuit operation is not difficult to understand.

VIR
continued from page 23

per second. Each pulse is triggered by the vertical sync.)

Figure 10 shows the composite video, sync pulses, integrated vertical sync pulse, and the 520

microsecond pulse at TP10.

One more condition must be established before the digital counting can begin: a negative-going pulse (wide enough to include all of the lines for the counter) must be produced. This wide pulse is generated by half of IC10, which is wired as a monostable multivibrator, and

is triggered by the falling edge of the negative-going pulse at TP10. The width of the output pulse at pin 12 is determined by the values of the network C12 and R12 (they are a time-constant filter).

Although the width of the pulse at the output of IC10 is not critical, it must be slightly wider than 20

horizontal lines (about 1300 microseconds), so the width usually is specified as 1400 microseconds.

The output pulse of this monostable multivibrator triggers (or enables) the digital counter which follows. Therefore, it is called a "counter enabler".

For the benefit of those of you who are not familiar with digital terminology, I will try to identify the stages and actions by both digital and more-conventional labels. For example, the space between the negative-going pulses is +5 volts DC (a "high" digital signal), and the tip of the pulses nearly reaches zero volts (or a digital "low").

Binary counter

IC20 is a 4-bit binary counter. When enabled, it counts up to 15, resets and counts up to 15 again, and repeats. At least, the counter would repeat endlessly if enabled all of the time. But the 1400-microsecond pulse both starts and stops the counting.

The IC20 counter has two inputs. Pin 2 has the enabling pulse, and pin 14 has a series of horizontal-sweep pulses.

When the 1400-microsecond enabling pulse at pin 2 of IC20 goes low, the binary counter begins counting the horizontal-rate pulses at pin 14. The count began at line 4 and the counter continues for its maximum of 15 counts, when the four output pins all are in a high state. (That corresponds to the start of video Line 19, as we shall see later.) However, the counter is still enabled, so it does not stop, but resets and begins counting up toward 15 again. Before it reaches maximum (actually just four more counts), the enabling pulse goes high (at about line 24), and the counter stops, with all outputs low.

The enabling pulse and the counting pulses at the four outputs are shown with the correct phase in Figure 11.

Those four outputs of the counter connect to four inputs of IC30, a decoder. The decoder is a four-input NAND gate, which has a low output **only** when all of the four inputs are high. Therefore, at the count of 15 horizontal pulses, the

decoder has a low (negative-going pulse) that's exactly as wide as one video line.

Next, this low pulse goes through the IC30 inverter, which inverts the phase by 180 degrees. At the output pin 8, therefore, is a positive-going (high) pulse of the width of one horizontal line of video, and having the same phase as Line 19 of the composite video (see Figure 12 for the 520 microsecond pulse, the enabling pulse, and this Line 19 pulse).

Line 19 has been identified, since it corresponds with this pulse.

The drawing of Figure 13 shows all of the operation up to this point, plus the 15-microsecond and 35-microsecond pulses that will be made by "slicing" the 63-microsecond pulse that identifies Line 19.

Now, the question is: does Line 19 of the composite video from the station have the VIR waveform or not? But first, one more pulse must be produced.

Pulses Made By Slicing

Two other pulses, of narrower width and different phase, are made by "slicing" the "Line-19" 63-microsecond pulse previously described.

Slicer #1

To be honest about it, those slicers don't actually "slice" anything. But, that's just a simple way of saying what **seems** to happen. Slicer #1 is another monostable multivibrator. It's set to trigger on the **rising edge** of the pulse at pin 2, and this pulse is the 63-microsecond **positive-going** Line-19 waveform. So, **the pulse from slicer #1 begins with the start of Line 19.**

The time constant filter, C20 and R20, determines how long the slicer functions. Thus, the RC values give the desired pulse width of 15 microseconds. This is not a critical specification; normal parts tolerances are sufficient.

Actually, there are **two** 15-microsecond output pulses. The positive-going one at pin 13 (marked Q) feeds the VIR sensor circuit; and the negative-going one at pin 4 (Q) drives the next pulse slicer and Q24.

continued on page 26

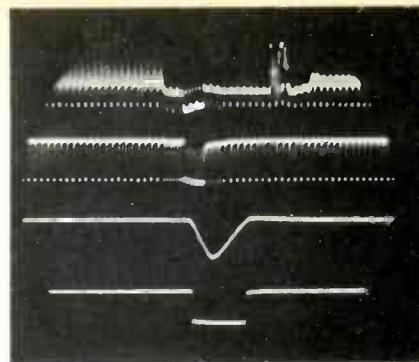


Fig. 10 These waveforms (top to bottom) are: composite video; sync pulses (negative-going) at TP2; the negative-going pulse at C4 after the serrated vertical pulse is integrated; and the 520-microsecond pulse at TP10. The falling edge at the left triggers the IC10 counter at the end of video line 4. Labeling a pulse with a microsecond rating refers to the horizontal width. All of these waveforms repeat 60 times per second (that is, once for each field of video).

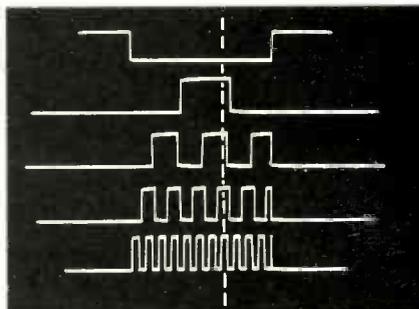


Fig. 11 Here are the waveforms at input and the four outputs of IC20, the four-bit binary counter. From top to bottom they are: the 1400 microsecond "enabling" pulse that keeps the counter running; pin 11; pin 8; pin 9; and pin 12. Compare these waveforms to the digital truth table in Figure 13. Notice that when "highs" occur in sequence, they form wider pulses, and do not show as separate pulses. Since the counter continues operating past the Line-19 pulse that's wanted, Line 19 is about one-third from the right, as shown by the dotted line. Vertical lines have been drawn in for clarity.

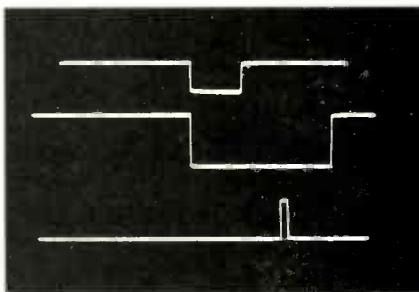


Fig. 12 From top to bottom are: the 520 microsecond pulse at TP10; the 1400 microsecond pulse at TP12; and the 63 microsecond Line-19 pulse.

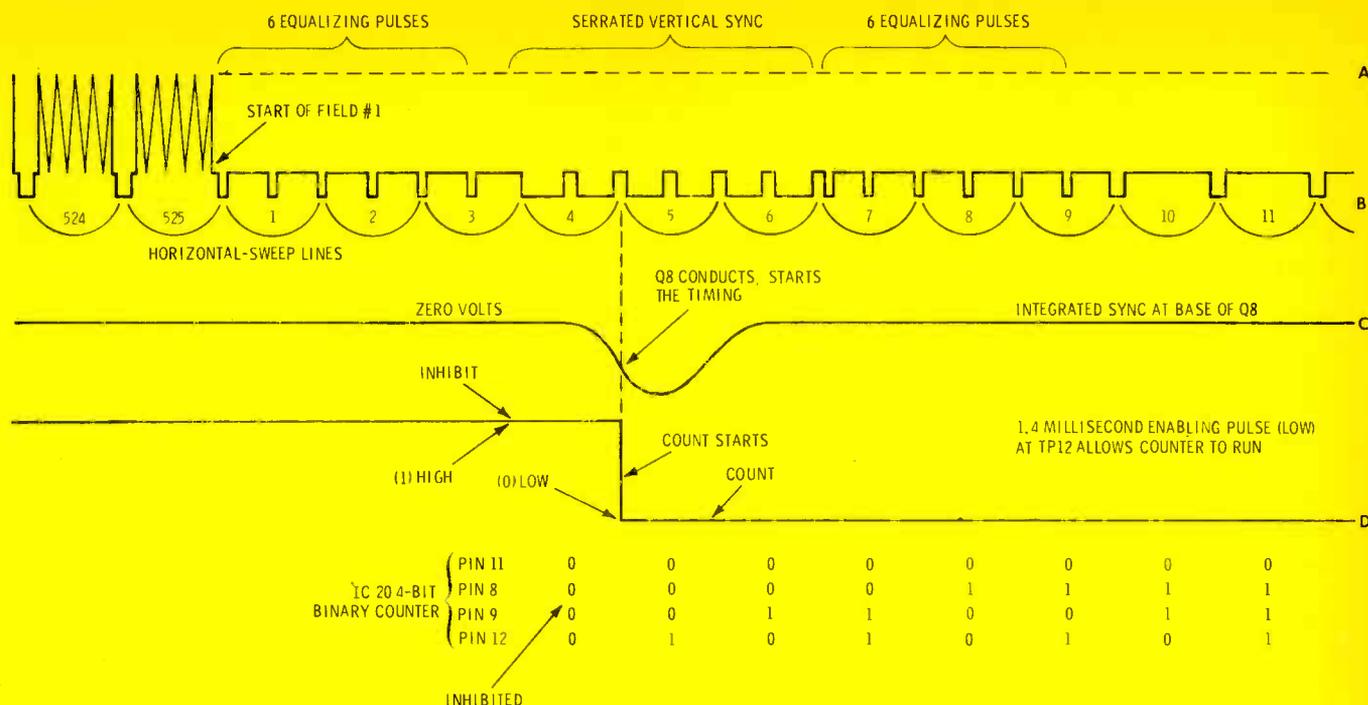


Fig. 13 Many useful facts can be learned from this drawing. Lines "A" and "B" represent the video of Field #1; "C" is the base voltage of Q8, including the negative pulse formed by integration of the vertical sync; "D" is the 1400 microsecond "enabling" pulse at TP12 (the counter runs only when this pulse is "low"); below line "D" are the columns of the counter

truth table (also see Figure 11 for the actual waveform); "E" shows the 63-microsecond Line-19 pulse; "F" is the 15-microsecond pulse from slicer #1 at TP24; "G" is the 35-microsecond pulse from slicer #2 at TP22; while "H" and "I" show the DC switching voltages that change the operation from manual to VIR-controlled.

VIR

continued from page 25

Slicer #2

Pulse slicer #2 is similar to #1, except for a wider output pulse, and an additional important input waveform. More about that later.

Slicer #2 also is triggered by a **rising** pulse edge. But notice carefully that the input waveform at pin 10 is a 15-microsecond **negative-going** pulse, whose beginning (fall-


ing) edge marks the **start** of Line 19. So, the **first** rising pulse edge is the **end** of the 15 microsecond pulse. In other words, **the output pulse from slicer #2 starts 15 microseconds from the beginning of Line 19.**

This tells us why the output pulse can't be allowed to exceed 35 microseconds: it would extend into line 20, if so. Both pulses (plus the skew time to reach full amplitude) use up the whole 63 microseconds of Line 19. The tolerances of C19

and R19 can't provide such accuracy.

Therefore, C19 and R19 are selected to give **more** than 35 microseconds, then the second waveform at pin 11 terminates (clears) the pulse with high accuracy at the end of Line 19. That's the job for Q18 and other components.

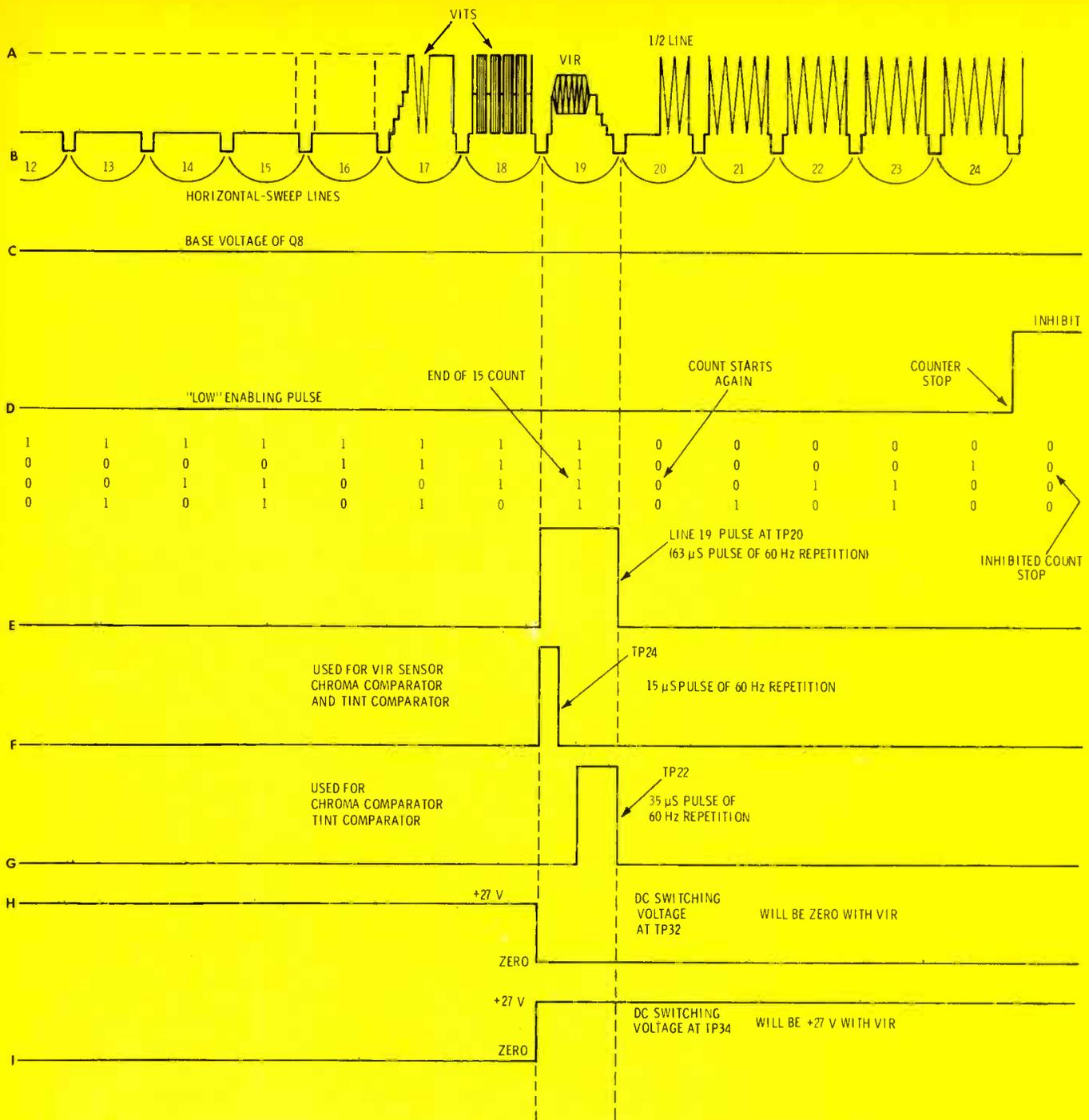Now, Q18 appears to be merely a simple amplifier of horizontal pulses, but a second source of input signal comes from the negative-going Line-19 pulse from the de-



coder output at pin 6.

The General Electric explanation says Q18 functions similarly to a 2-input NOR gate. Q18's output can be high (transistor cut off) **only** when both signal inputs are low (zero—no input bias). That's understandable, even without digital theory. Anyway, the "clear" input at pin 11 **must** go "low" (zero) to "reset" (terminate) the pulse at the output, pin 12.

Unfortunately, the GE explanation implies that the two input


signals at the base of Q18 both are strong pulses. Yet, scope waveforms (see Figure 14) prove the narrow horizontal pulses have an amplitude of only 0.02 volts PP, while the broad Line-19 pulse measures 0.65 volts PP. So, when it's stated, "The R16 input from Q15 couples a positive-going horizontal retrace pulse (HIGH state) to the base of Q18 just prior to the end of Line 19. This pulse saturates Q18, pulling the collector back to 0 volts (LOW state) and resetting Pulse

Slicer number 2", **I must disagree.** There is **no** way a pulse of 0.02 VPP can saturate the base of a transistor that also has more than 0.6 VPP of opposite-polarity pulse! At the most, the tiny positive-going base pulse speeds up the rising side of the negative Line-19 pulse, making more rapid and precise the resetting of slicer #2.

Waveforms

Figure 15 shows the Line-19, the *continued on page 28*

A "bestseller" you'll never put down.

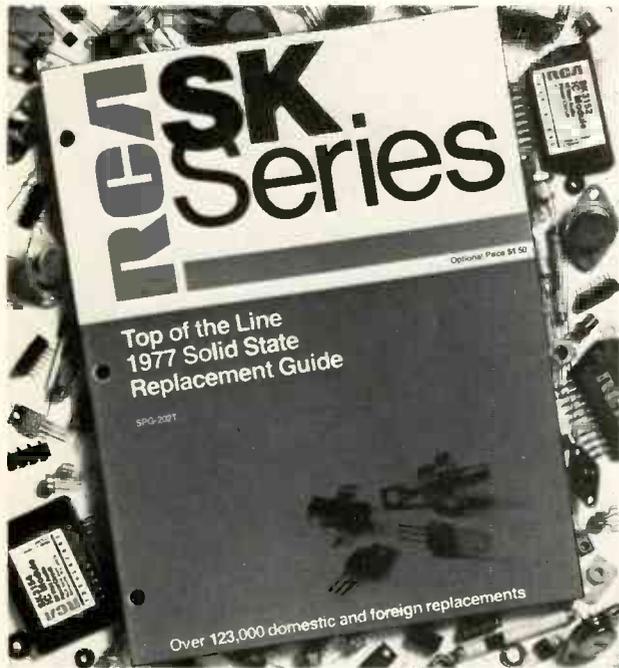

It's RCA's all new 1977 "Top of the Line" SK Series Replacement Guide. The most comprehensive list to date of transistors, rectifiers, thyristors and integrated circuits — 381 RCA types, including 68 brand new, that will replace 123,000 domestic or foreign semiconductors in entertainment and industrial equipment. The 68 new types have enabled us to increase our replacement capability by over 11,000 additional industry devices. **You can't afford to be without it.** The 1977 Replacement Guide is a complete, accurate information source for your Solid State replacement needs. The book represents thousands of hours of engineering know-how. Keep in mind, too, that RCA SK replacement semiconductors measure up to strict AQL standards. **Get yours now.** RCA's SK Replacement Guide. Contact your RCA Distributor. Or send \$1.50 (check or money order) to RCA Distributor and Special Products Division, PO Box 85, Runnemede, NJ 08078.

RCA SK Replacement Semiconductors

For More Details Circle (12) on Reply Card

VIR

continued from page 27

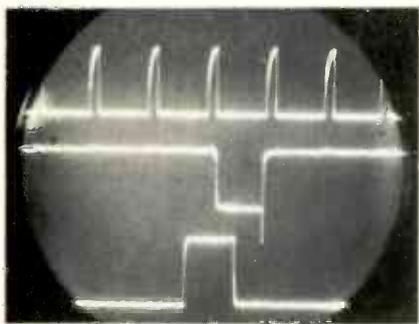


Fig. 14 The two upper waveforms have correct phase; the bottom one should be to the right, under the other broad pulse. From top to bottom, the waveforms are: horizontal sweep pulses at the emitter of Q15; the base waveform of Q18 (the broad pulse has an amplitude of 0.65 VPP); and the 4.8 VPP positive pulse at the collector of Q18. No trace of the horizontal pulses can be seen in this latter waveform. No touchup of the waveforms was done.

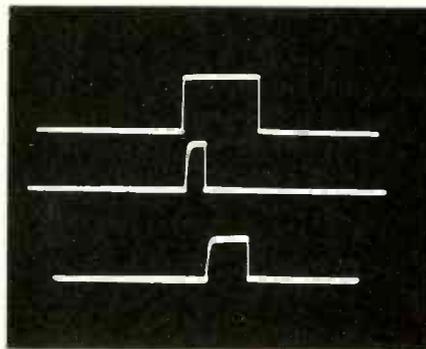


Fig. 15 These are the actual waveforms, in the correct phase, but with the vertical lines drawn in. From top to bottom, the pulses are: The Line-19 pulse at TP20; the 15-microsecond pulse at TP24; and the 35-microsecond pulse at TP22. Notice that the two lower pulses add to equal the Line-19 pulse (except for the slight gap required for the 35-microsecond slicer to begin). Although the two narrower pulses were produced individually by monostable multi-vibrators, the fact that they seem to be parts of the Line-19 pulse probably is the reason the pulse generators are called "slicers".

15-microsecond, and the 35-microsecond pulses, all in the correct phase.

Q22 and Q24 invert the polarity and amplify the 35-microsecond and 15-microsecond pulses, respectively, before they go to the controllers.

Next Month

Composite video is examined for the falling side of the Line-19 blanking during the life of the 15-microsecond pulse. A falling blanking side indicates that Line-19 has the VIR waveform. If the falling side is not there, that's proof of no VIR signal. Reception of the VIR signal reverses the switching voltages, allowing the automatic circuitry to control color and tint. Watch for these interesting explanations.

Also, instructions will be given telling how you can use your own triggered scope to look at the VIR waveform in the composite video. □

Convergence Trouble Symptoms And Repairs

By Robert L. Goodman,
CET and Carl Babcoke, CET

Defects in convergence components are rare, so it's possible for us to become rusty in this kind of troubleshooting. Here is a refresher course in the fundamentals and methods of servicing both old and new convergence systems.

Convergence repairs admittedly are not interesting to most technicians. You won't hear this topic of conversation when the men gather after a service seminar, or relax in a bar. But, there was a time when convergence **adjustments**, and how well they could be done, were a worry to many color-TV technicians. Of course, the receiver circuits were not so effective as they are now, and more work was required to attain a "good" job of set-up. Finally, we developed methods that worked

very well, and the subject faded away.

Before we give troubleshooting methods, and illustrate some of the new solid-state variations of circuitry, let's recap a few of the reasons why convergence is necessary, and how it's accomplished.

What Is Convergence?

Convergence (sometimes called merging) refers to anything done to bring the three colored pictures into register with one another. When

continued on page 30

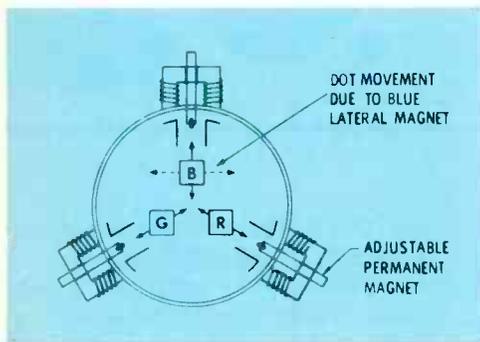


Fig. 1 The center-convergence permanent magnets of delta-gun picture tubes are mounted with the dynamic convergence coils. Rotating or sliding a magnet in its holder varies the magnetic field, which moves the entire picture of that color. Red and green can only intersect at one point near the center; then blue is moved up or down and sideways to converge.

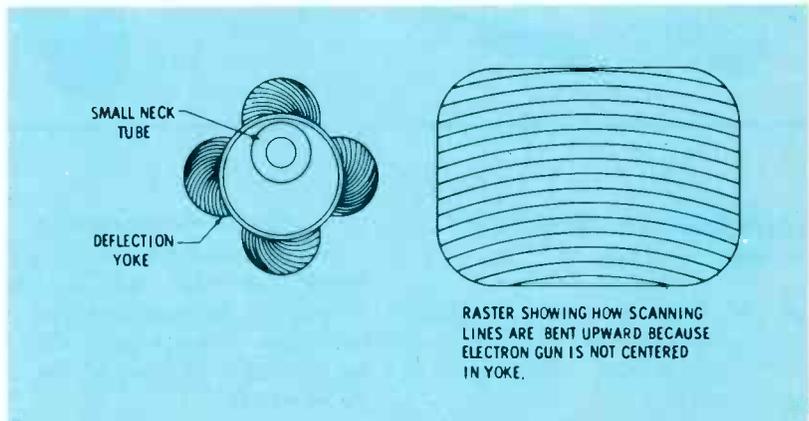


Fig. 2 An experiment made with a deflection yoke that's too large for the picture-tube neck will prove that the crosshatch lines bend according to the position of the electron gun in the yoke. Only in the center will straight lines be produced. Although the flat face plate of a color tube causes somewhat the same bending effect, it is a much smaller distortion.

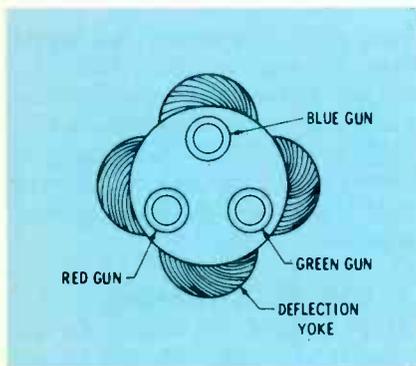


Fig. 3 Each gun of the delta tube is off-center in the yoke. Therefore, the crosshatch lines will be curved.

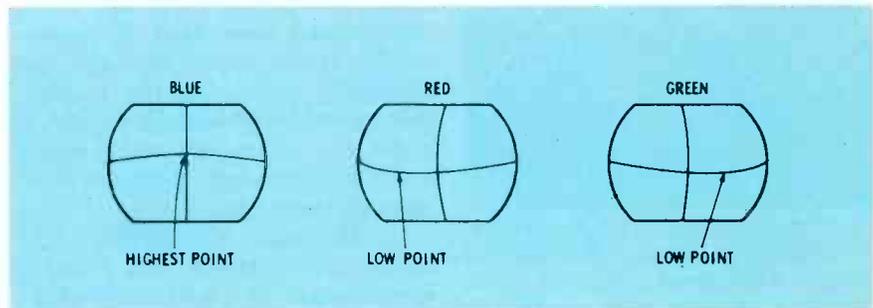


Fig. 4 Viewed on the screen, all of the crosshatch lines are curved, except for the blue-vertical lines. They are not bent, because the blue gun is midway between the vertical yoke coils (which are at the right and left sides).

The drawings of Figures 1 through 4 are from "Color TV Servicing Made Easy, Volume 1" (book 20135) by Howard W. Sams.

RCA's FREE & EASY '77 Dealer Awards



Convergence Trouble

continued from page 29

this is done properly, a B&W picture will not have red, blue, or green lines around the objects in the scene.

Actually, there are two basic types of convergence. (These first descriptions apply to the original "delta" arrangement of the guns.)

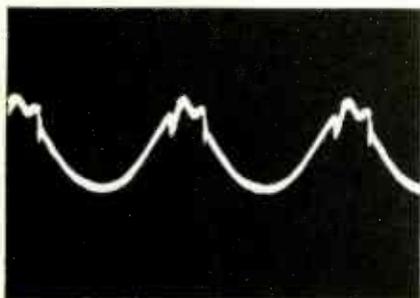


Fig. 5 Theoretically, a perfect parabola of current is necessary through the dynamic-convergence coils for total correction of the bent lines. In practice, the horizontal-correction current waveforms range from near-sine-waves to distorted parabolas. This waveform from a GE is better than most.

Center Convergence

Center convergence often is called "static" or "DC", and it means a moving of the complete red, blue, and green pictures until they overlap perfectly, at least in the center of the raster.

Originally, the moving of the three rasters was done by running an adjustable DC current through a coil of wire located "over" each gun. (In this case, "over" refers to the location relative to the gun and the center of the picture-tube neck, and does not mean up.) Later models used some kind of permanent magnet, whose strength was adjustable by moving the magnet. One system is shown in Figure 1, where the permanent magnets are mounted on each dynamic-convergence assembly.

In all cases, a magnetic field moves each complete red, blue, or green picture as a unit, without affecting the straightness of the lines, or changing the linearity of the sweep.

Viewed on the face of the picture tube, the blue picture moves up

and down; the red picture moves diagonally along the south-west to north-east line; and the green picture moves diagonally along the north-west to south-east line.

With only these three movements, it would be possible for the pictures to not converge exactly at the center. So, an extra magnet is given to the blue gun, allowing adjustment horizontally (laterally).

With four adjustments, the three pictures always can be made to overlap perfectly, near the center of the screen. Without these adjustments, which compensate for minor errors of electron gun locations, very few picture tubes would have satisfactory center convergence.

Also, without the next type of convergence, the B&W picture would still not be converged around the edges.

Dynamic Convergence

If you were to eliminate all dynamic convergence, almost all lines of a crosshatch pattern would be curved. Only the blue vertical lines are straight when there is no



When you think of receiving tubes, think RCA! When you think of dealer awards, think RCA "Free and Easy '77." Then get both from your local participating RCA tube distributor. Quality tubes and quality awards go hand in hand from RCA.

Free with your purchase of RCA Entertainment Receiving Tubes

Check out these 17 values; select the award you want; then visit your participating RCA distributor and find out how easily you can take home that award when you place your tube order.

- SPALDING "DRIBBLER" BASKET-BALL — FE-4102 — Value: \$12.00 (Not Illustrated)
- SPALDING TENNIS CARRY-ALL — FE-4103 — Value: \$15.40 (Not Illustrated)
- WILSON PRO STAFF GOLF BALLS — FE-4118 — Value: \$15.75
- SPALDING REBEL FOOTBALL — FE-4104 — Value: \$17.00
- WATER PIK SHOWER MASSAGE — FE-4105 — Value: \$24.95
- SPALDING PANTO GONZALES SIGNATURE RACKET — FE-4106 — Value: \$22.60
- PRESTO BURGER/2 — FE-4107 — Value: \$35.90
- GARCIA MITCHELL SPINNING COMBO - FE-4108 - Value - \$39.95
- SCHICK PRO JET-1200 STYLING DRYER - FE-4109 - Value: \$39.00
- SKIL DOUBLE INSULATED 2-SPEED JIG SAW — FE-4110 — Value: \$40.95 (Not Illustrated)
- TAYLOR AMERICAN EAGLE BINOCULARS — FE-4111 — Value: \$56.95
- SHEPHERD BALL-B-Q FAMILY SIZE GRILL — FE-4112 — Value: \$54.95
- HAZEL SAXONY 21" DUFFEL BAG — FE-4113 — Value: \$50.00
- ROCKWELL 16" HEDGE AND SHRUB TRIMMER — FE-4114 — Value: \$34.95
- SKIL MULTI-PURPOSE X-TRA TOOL — FE-4115 — Value: \$67.95
- OLIVETTI UNDERWOOD PORTABLE TYPEWRITER — FE-4116 — Value: \$79.50
- OLIVETTI "DIVISUMMA 32" ELECTRONIC PRINTING CALCULATOR — FE-4117 — Value: \$109.00

RCA Distributor & Special Products Division, Deptford, N.J. 08096

RCA Receiving Tubes

correction.

Most textbooks and color courses say the lines are curved because the faceplate of the picture tube is not a section of a ball, but is too flat. Well, the flat screen causes some problems with purity and edge focus, but it's **not** the cause of the bent lines.

You can prove the cause for yourself by placing the yoke of an old B&W TV over the smaller neck of a newer B&W picture tube, and then operating the receiver. Look at a horizontal-lines or crosshatch pattern. If you hold the yoke so the neck is centered, the horizontal lines are straight. When you allow the yoke to rest on the neck, the scanning lines and crosshatch horizontal lines are bowed up in the center (see Figure 2). The deflection power is unbalanced because the electron beam does not pass through the center of the yoke.

In Figure 3, notice that **all** guns of a delta picture tube are off-center in the yoke. Accordingly, you would expect **all** crosshatch lines to

be curved. That's almost right, but there's one exception. The vertical-deflection coils are located at the right and left sides of the picture-tube neck. Therefore, vertical lines of the blue gun are straight, be-

cause the blue gun is midway between the coils. The bending of the lines in Figure 4 have been verified by operating a color tube without convergence coils.

continued on page 32

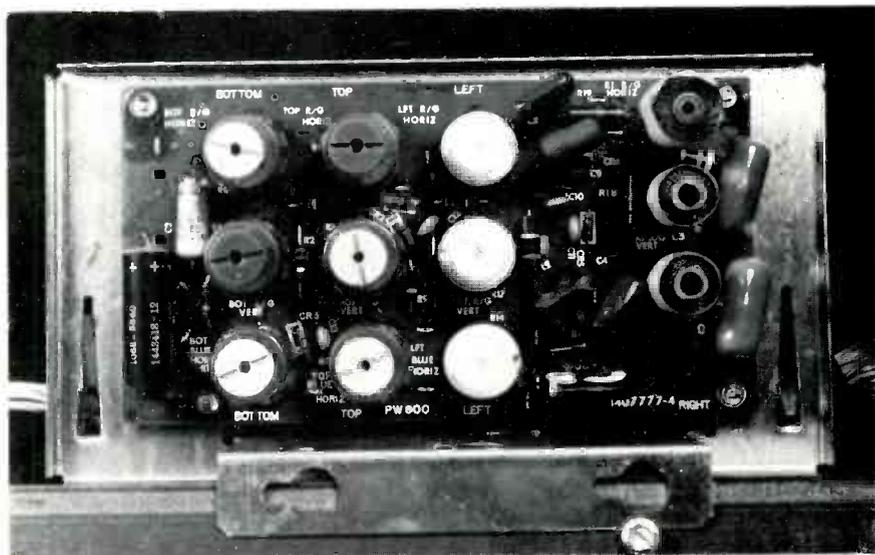


Fig. 6 This is the convergence circuit board of a 25" color tube. The six controls on the left are for vertical convergence. The three controls and three coils on the right are for horizontal adjustments.

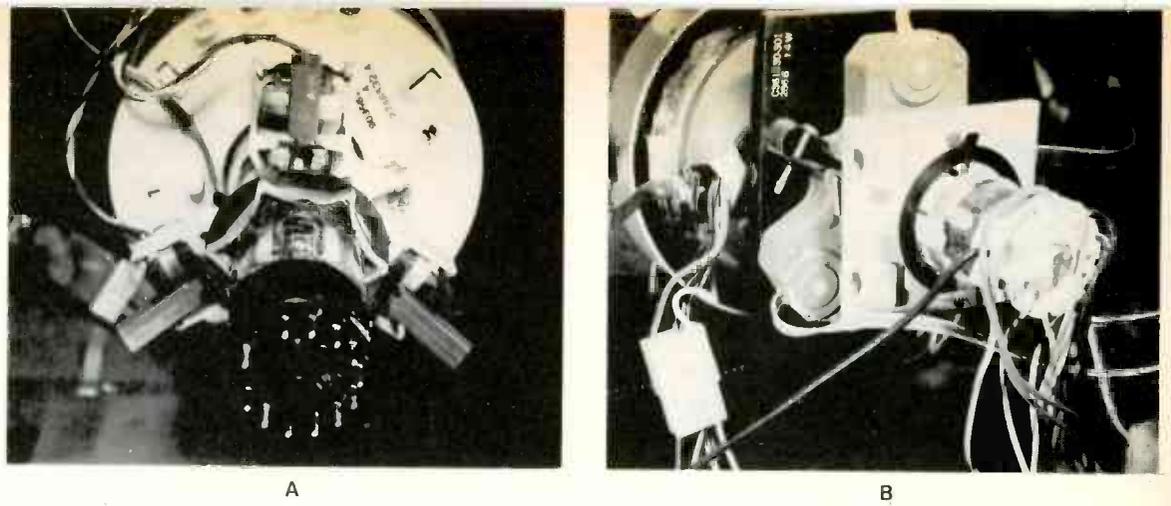


Fig. 7 On 21" round color tubes, the convergence coils and sliding magnets were part of a separate assembly mounted on the picture-tube neck behind the yoke (A). Rotary magnets and enclosed coils were used in the convergence assembly of this old 23" tube (B).

Convergence Trouble

continued from page 31

Dynamic Convergence— In General

Straightening of the curved lines must be done with AC signals. So, it's called "dynamic" convergence, to prevent any confusion with center convergence, which operates from steady magnetic fields without AC signals.

Studies of crosshatch patterns, without correction for the bent lines, indicate that a parabolic

correction is required. And because the correction signal is applied to electromagnetic coils, it follows that **the convergence CURRENT should have a parabolic waveform** (see Figure 5).

In all models of color receivers, samples of vertical and horizontal sweep signals first are filtered or mixed, and then are adjusted for amplitude, usually by controls and coils on a convergence board or panel, as shown in Figure 6.

Next, these red, blue, and green horizontal, and red, blue, and green

vertical signals are sent to coils (with powdered-iron cores) mounted "over" the three guns (Figure 7). The coils act like individual non-linear deflection yokes, operating on the electron beams before the conventional deflection yoke. In a way, the action is similar to a stage that pre-distorts a signal to compensate for an opposite distortion that happens later.

Many years ago, before the circuits were improved, a control that regulated the amount of parabolic current was called "amplitude". And others that increased the current at the beginning and decreased the current at the end of each parabola (or the opposite) were called "tilt". Usually, one amplitude and one tilt control for horizontal, plus one amplitude and one tilt control for vertical were supplied for each of the three colors.

Later, after the adoption of some controls that affected two colors simultaneously, the controls were labelled to show where the main correction was located on the crosshatch. One knob might be marked, "TOP R&G VERT LINES", or "BOT BLUE HORIZ LINES".

Problems Travel Both Directions

One reason for telling these basics is to illustrate the interconnections between sweep and convergence.

For example, a defect in the convergence circuit might cause a change of linearity or vertical height. Or, other defects might

continued on page 34

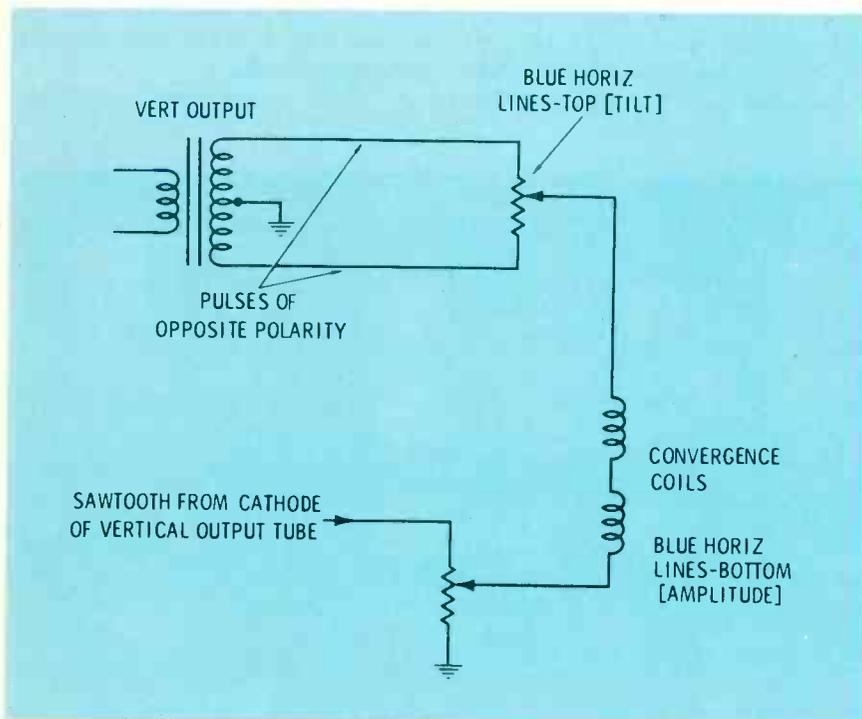


Fig. 8 Tube-powered chassis often used a vertical tilt and amplitude circuit, with the pulses for the tilt obtained from separate windings of the vertical-output transformer.



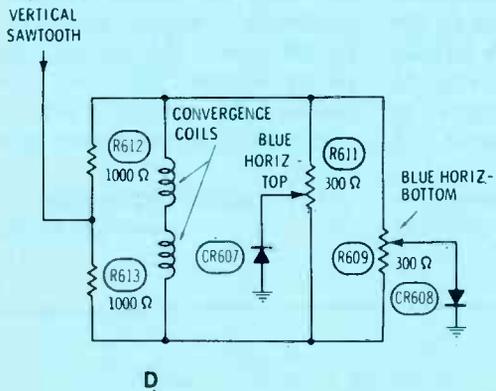


Fig. 9 Solid-state vertical-sweep circuits without output transformers demand convergence circuits with only one input from the deflection. Operation of the Zenith 19EC45 blue-verical convergence is illustrated in several steps for clarity. (A) When a variable control (shown here by two separate resistors) is adjusted to the exact center of its resistance, the positive peak of the sawtooth forces the diode CR608 to draw current. However, the same positive voltage appears at both ends of the coil assembly; therefore, the coil has no current. During the negative peak, CR607 conducts in the same way, and both ends of the coil are negative, so again no coil current flows. (B) When control R609 is rotated to place CR608 at the R612 end of the coil, the positive peak causes CR608 to conduct, grounding that end of the coil. The positive input voltage appears at the R613 end of the coil, causing electron current to flow, as shown by the arrow. (C) When control R611 is rotated to place diode CR607 at the R613 end of the coil, the negative peak forces CR607 to conduct, grounding the R613 end of the coil. The negative input voltage at R612 causes electron current to flow in the coil, as shown by the arrow. Did you notice that the current flowed in the same direction in both (B) and (C)? (D) Here is the complete blue convergence circuit. One control acts as an amplitude control at the top of the picture; the other acts as an amplitude control for the bottom lines of the picture. When one is advanced more than the other, the effect is the same as tilt.

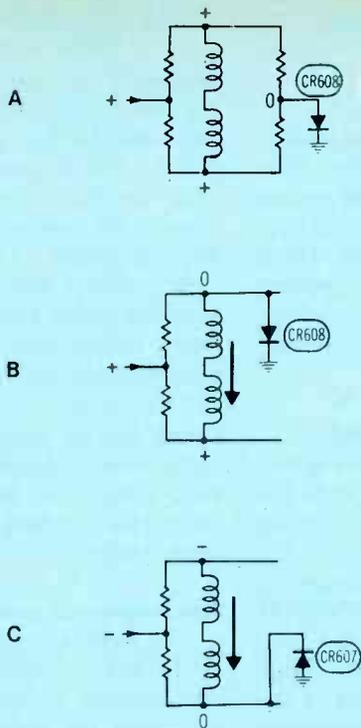

GE Introduces Spike Protection

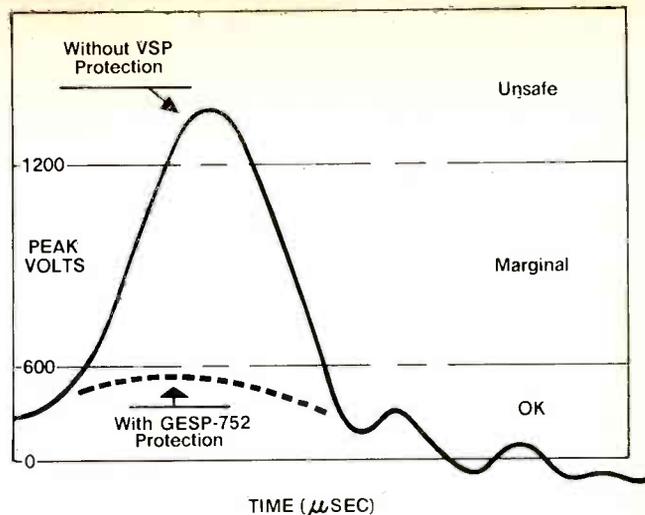Protects TV's, Stereos and other sensitive electronics from brief high voltage surges from lightning strikes near power lines or switching Off and On of major appliances.



Insurance research has shown that TV sets are more susceptible to lightning caused voltage spike damage than other kinds of electronic equipment. Tube-type sets are less susceptible than solid-state circuitry. Some manufacturers offer built-in spike-protection circuits; others don't. Why take a chance? Especially when spike protection is made so easy.

Just plug the GE Voltage Spike Protector into any 15 amp, 125 volt wall outlet, then plug in the TV set.

Every service technician should carry several GE Voltage Spike Protectors in his service kit. Every service call means a sales opportunity. See your GE Authorized Tube Products Distributor; ask for Part No. GESP-752.

Tube Products Department
General Electric Company
Owensboro, Kentucky 42301

GENERAL  ELECTRIC

ARROW AUTOMATIC STAPLE GUNS

CUT WIRE & CABLE INSTALLATION COSTS

... without cutting into insulation!

SAFE! Grooved Guide positions wire for proper staple envelopment! Grooved Driving Blade stops staple at right depth of penetration to prevent cutting into wire or cable insulation!

No. T-18—Fits wires up to 3/16" in diameter.

BELL, TELEPHONE, THERMOSTAT, INTERCOM, BURGLAR ALARM and other low voltage wiring.



Uses T-18 staples with 3/16" round crown in 3/8" and 7/16" leg lengths.

No. T-25—Fits wires up to 1/4" in diameter.

Same basic construction and fastens same wires as No. T-18.

Also used for RADIANT HEAT WIRE



Uses T-25 staples with 1/4" round crown in 9/32", 3/8", 7/16" and 9/16" leg lengths

NEW! Intermediate No. T-37—Fits wires and cables up to 5/16" in diameter.

Same basic construction as Nos. T-18 & T-25.

Also used for CATV and DRIVE RINGS in stringing wires.



Uses T-37 staples with 5/16" round crown in 3/8", 1/2" and 9/16" leg lengths.

No. T-75—Fits wires and cables up to 1/2" in diameter.

RADIANT HEAT CABLE, UF CABLE, WIRE CONDUIT COPPER TUBING or any non-metallic sheathed cable.

Also used as DRIVE RINGS in stringing wires.



Uses T-75 staples with 1/2" flat crown in 9/16", 5/8" and 7/8" leg lengths.

ARROW FASTENER COMPANY INC.
271 Mayhill Street, Saddle Brook, N. J. 07663

Convergence Trouble

continued from page 32

affect the horizontal sweep.

And, of course, the dynamic convergence signals are taken from the sweep circuits, so many sweep defects temporarily can upset the convergence. That's a strong reason to obtain the best size and linearity of the sweep circuits before making any dynamic convergence adjustments.

Vertical Convergence

Figure 8 gives the convergence circuit for vertical correction of the blue gun in an old color receiver with tubes.

To obtain a parabolic current it's necessary to apply a sawtooth of voltage to the inductance of a coil. A sawtooth waveform is developed across an unbypassed section of the cathode resistor of the vertical-output tube. The sawtooth goes to the "amplitude" control, which adjusts the voltage fed to the convergence coil, and the circuit returns to ground through the tilt control and transformer windings.

If an amplitude adjustment is lopsided, a sawtooth of current

should be added to the parabola. And a pulse voltage generates a sawtooth of current. A center-tapped winding of the vertical-output transformer provides vertical pulses of both polarities. When the "tilt" control is set to the electrical center, the pulses cancel, giving no tilt correction. Then turning the "tilt" control one way or the other provides either positive- or negative-going pulses, and also changes the amplitude of the pulses.

This circuit works fine, when the circuit has an output transformer to supply the opposite-polarity pulses. But, what can be done for the solid-state circuits that have no transformer?

Transformerless vertical

The vertical convergence circuit of the Zenith 17EC45 operates very well without an output transformer to supply the pulses. Instead, two amplitude controls are used, one for the top of the picture, and one for the bottom. The effect of tilt is obtained by operating one of the amplitude controls higher than the other.

The vertical-convergence circuit
continued on page 36

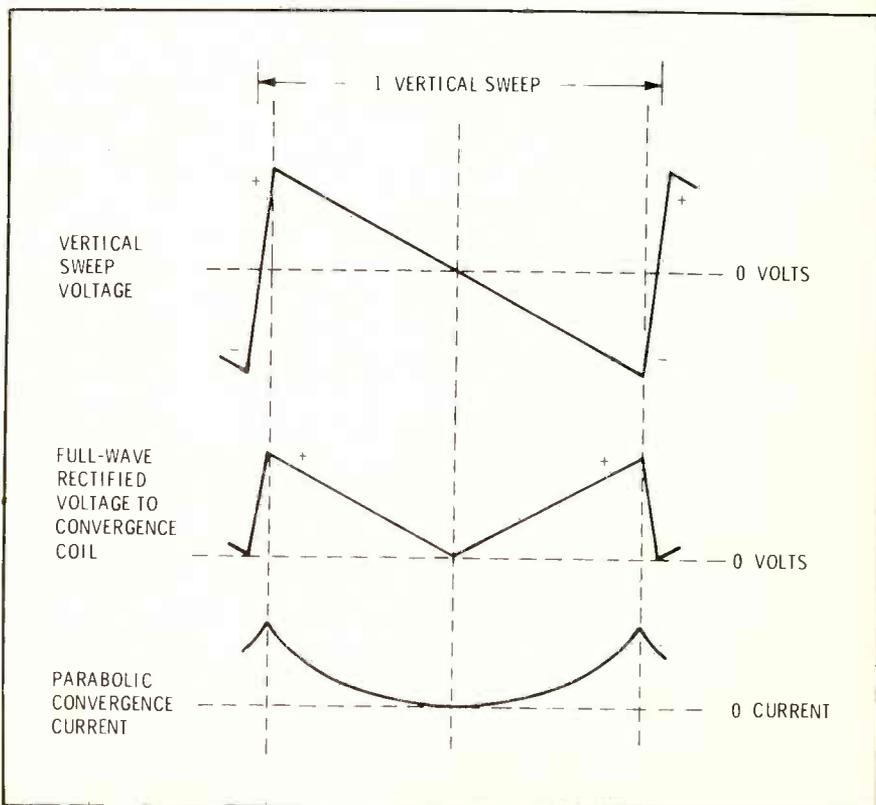


Fig. 10 These drawings show the operation of the circuit of Figure 9, explaining how one positive and one negative peak combine to make two positive peaks. In turn, those peaks produce a near-parabolic current.

Performance features at a price you can afford— and fully backed by Tektronix

Only Telequipment offers you:

TEKTRONIX GUARANTEE

The Telequipment family of oscilloscopes is fully guaranteed by Tektronix, the world's leading oscilloscope manufacturer. This guarantee means that during your first year of ownership, if there are any defects in Telequipment parts or workmanship, you can bring your oscilloscope to any of 35 Tektronix Service Centers across the United States for fast repair by experts—free of charge.

PERFORMANCE FEATURES YOU NEED AT A PRICE YOU CAN AFFORD

Model D61a Designed for portability and easy operation, the D61a is a dual trace 10 MHz 'scope for only \$595. For easy, accurate viewing, the D61a features automatic triggering and bright, stable waveforms on an 8 x 10 cm display.

Model S61 NEW from Telequipment, the S61 is a 5 MHz single trace oscilloscope featuring automatic triggering and 8 x 10 cm display for \$375. This lightweight (14 lb.) instrument has a straightforward, easy to read front control panel—well suited for education applications.



Model D32 When you demand an extremely portable 'scope, the D32 is ideal. Battery or ac line operated, this 10 MHz dual trace 'scope weighs only 10 lbs. An optional shoulder strap or attaché carrying case can be used to take your 'scope into the field. The \$750 price includes batteries and probes.

IDEAL FOR MANY APPLICATIONS

If you're servicing pocket calculators, TV, radio, microwave ovens, alarm systems or dozens of other consumer products, Telequipment 'scopes can do the job for you. Easy viewing and operating make Telequipment ideal for classroom use too.

TELEQUIPMENT... THE CHOICE FOR YOU

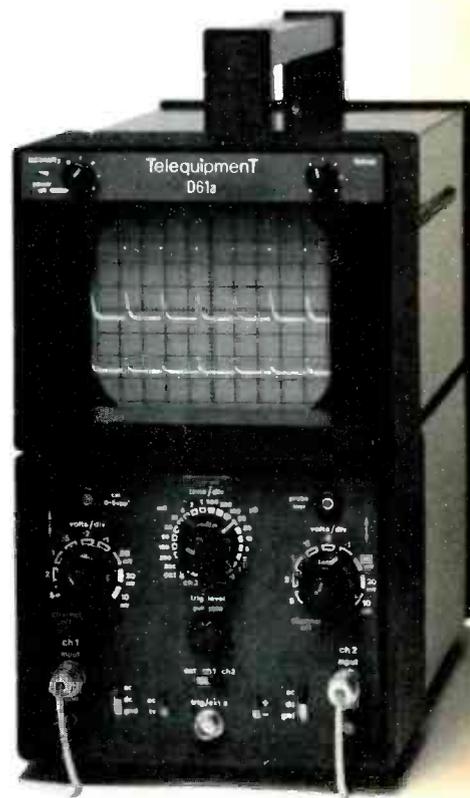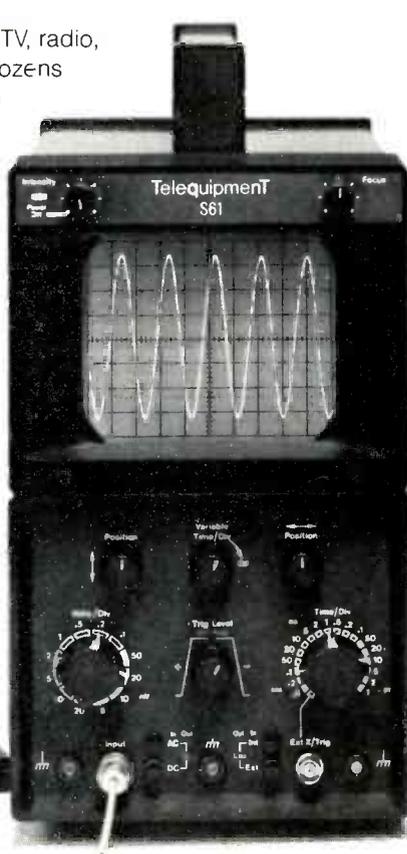Performance features at a price you can afford, plus full backing by Tektronix make Telequipment a wise choice when you're looking for low-cost oscilloscopes.



For more information about Telequipment oscilloscopes, contact your nearest Tektronix Field Sales Office, or write Tektronix, Inc., P.O. Box 500, Beaverton, Oregon 97077. For immediate information, call Bill Glaze at Tektronix: (503) 644-0161, extension 7163.



Telequipment is a division of Tektronix U. K. Ltd., a wholly owned subsidiary of Tektronix, Inc. U. S. Sales Price F.O.B. Beaverton, Oregon.

THE GENERAL TELEVISION SERVICER



Patents Pending
covering 13 unique features.

YOUR PORTABLE, COST EFFECTIVE SOURCE OF A CONVENTIONAL COLOR BAR PATTERN GENERATOR, A SUBSTITUTE TUNER AND MOST USED FUNCTIONS OF AN ANALYST, PLUS:

- Extra wide range RF/IF attenuator for testing receiver sensitivity.
- **GRAY QUAD** pattern for gray scale tracking checks/adjustments.
- **COLOR BARS** pattern for oscillator frequency checks with no need to short the AFPC test point.
- **RED RASTER** pattern for checking and adjusting purity at the flip of a switch.
- **HATCHDOTS** - versatile composite pattern for dynamic & static convergence plus other checks.
- High level, 75 ohm video output.

ALL THIS FOR ONLY \$299.95!

Write for more information on the ATC-10 General Television Servicer, or try it at our risk.
— 30 DAY SHOP TRIAL —
(If not 100% satisfied in every way, return for instant refund in full.)

American Technology Corporation

225 Main Street, Dept. 3A,
Canon City, CO 81212

For your convenience, we accept Master Charge, BankAmericard and COD phone orders.
Same day shipment!
(303) 275-8991

For More Details Circle (50) on Reply Card

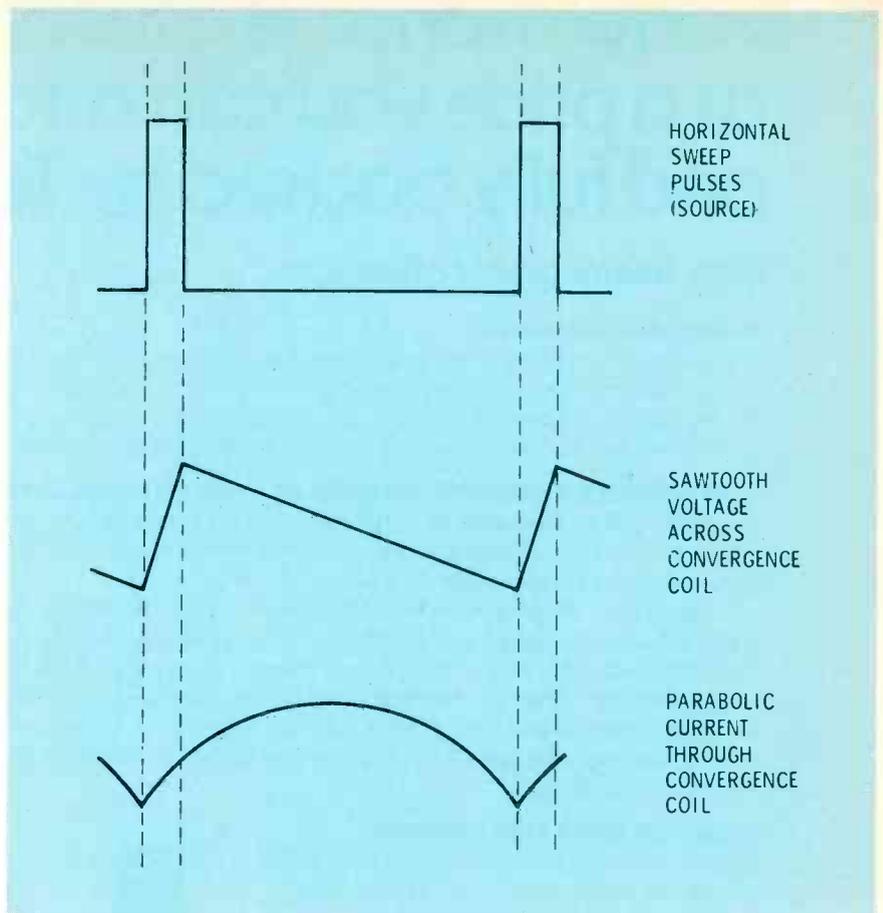


Fig. 11 Parabolic-shaped currents for horizontal convergence are produced by filtering (integration). Horizontal-sweep pulses (top waveform) are integrated by the inductance of a coil on the convergence board, forming a sawtooth of voltage (center). When the sawtooth of voltage is integrated by applying it to the inductance of the convergence-yoke winding, the yoke current has a parabolic waveform (bottom).

Convergence Trouble

continued from page 34

receives the full output power of the vertical-deflection module, as shown in Figure 9D. This circuit is not grounded, except through the two diodes, which act as voltage-controlled switches to conduct current at the proper times. Although the sweep waveform has some pulse amplitude, most of the amplitude is sawtooth. Therefore, we refer to it as sawtooth.

Several partial schematics in Figure 9 help explain the diode-conduction and convergence-coil currents, followed by the complete diagram of the blue vertical-convergence circuit.

The waveform drawings of Figure 10 show how switching by the diodes can change one positive peak and one negative peak into two positive voltage peaks that add

together forming an approximate parabolic waveform of convergence current.

Horizontal Convergence

Parabolic current waveforms for horizontal convergence are formed by a different method. Figure 11 shows the progression from horizontal voltage pulses, integration by a coil into a sawtooth of voltage, and the parabola of current produced by the sawtooth of voltage. These parabolas are not classic waveforms—remember the actual waveform of horizontal-convergence current shown before.

The simplified schematic of a 1965 horizontal-convergence circuit (Figure 12) and another manufactured in 1974 show several similarities.

Pulses and waveforms

What should you check first, when the crosshatch pattern looks

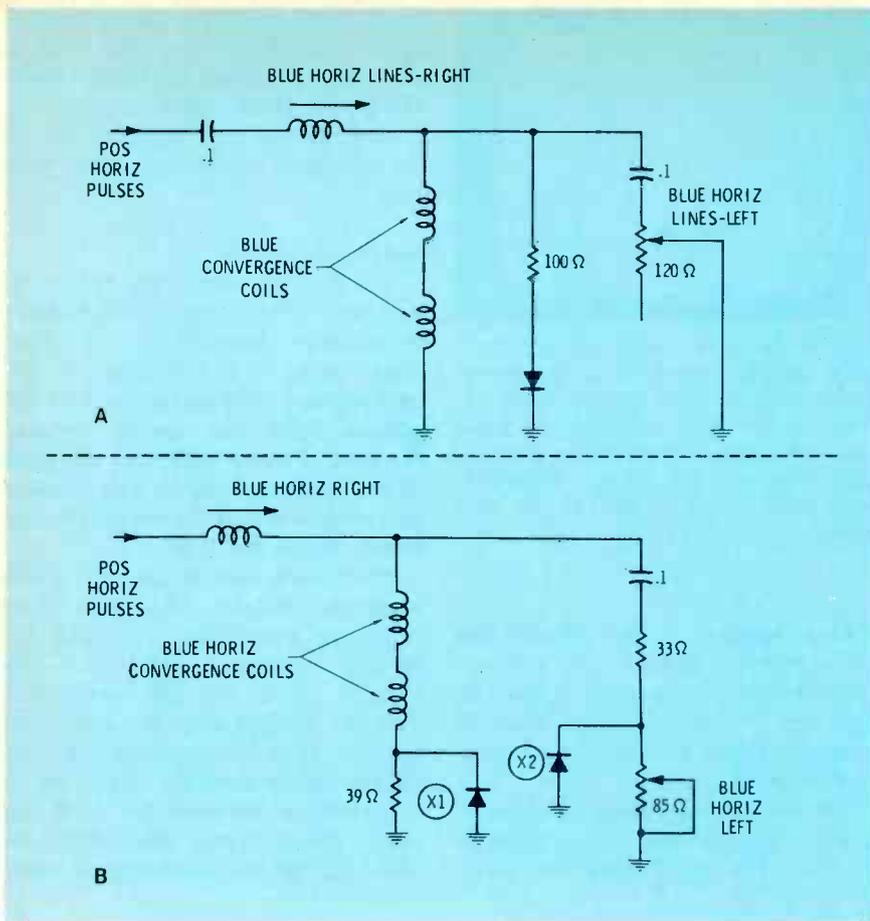


Fig. 12 The schematic of (A) comes from a CTC16 RCA TV. The adjustable coil and the .1 capacitor form a tuned circuit, while the control changes the tuning slightly. The diode is said to provide a small DC voltage to minimize changes of center convergence with adjustments, and also helps shape the waveform. The blue-horizontal convergence circuit of a newer model, the Zenith 17EC45, is shown in (B). There are improvements over the other circuit, but the similarities are obvious.

like the one in Figure 13? This appears to show a total loss of all convergence functions. Is that possible? Both horizontal sweep and vertical sweep samples (usually more than one kind) are brought to the convergence board, and the chances are slim of a defect eliminating all of them at the same time. But, an open in a ground wire common to both vertical and horizontal signals might do it. A loose or unplugged convergence connector is more likely.

However, when some functions work, but others don't, it's time to

continued on page 38



CET — MD

Just a few letters
Spell the difference
That is professionalism

If you are a service technician,
Servicing:

- * TV
- * CB
- * Video
- * Antenna systems
- * Industrial electronics
- * Medical electronics

Don't be
"Just another repairman"
Be a CERTIFIED
ELECTRONICS TECHNICIAN

Write to ISCET for details
On how and where
To take the exam

ISCET - 1715 Expo Lane
Indianapolis, IN 46224
317-241-8172

DIGITAL MULTIMETERS

NLS proves NLS' DMMs have more capability
at lower prices.

NLS' Silver Jubilee Year

THE VOLKSMETER FAMILY

LM SERIES

Features Include:

- Super Rugged - Ideal for field service use.
- Battery powered with batteries and charger unit included.
- Exclusive NLS fuseless protection in kΩ mode - up to 500 vdc or rms ac may be applied without damage.
- Overload indication.
- Automatic zeroing and polarity.
- Operating temperature - 0° to 45°C.
- Large 0.3" LED display.
- Small size: 1.9" H x 2.7" W x 4.0" D.
- Six optional shunts for current measurement - LM-3.5 includes three shunts in values of 10 mA, 100 mA and 1A.



| MODEL | RANGES | DC ACCURACY | RESOLUTION | DIGITS | PRICE |
|--------|-----------------------------------|-------------|------------|--------|-------|
| LM-3 | VDC & VAC | ±1% Rdg | 1 mV | 3 | \$125 |
| LM-3.5 | 1V, 10V, 100V & 1000V | ±0.5% Rdg | 1 mV | 3-1/2 | \$147 |
| LM-40 | OHMS | ±0.1% Rdg | 100 μV | 4 | \$190 |
| LM-4 | 1 kΩ, 10 kΩ, 100 kΩ, 1 MΩ & 10 MΩ | ±0.03% Rdg | 100 μV | 4 | \$227 |



Non-Linear Systems, Inc.

Originator of the digital voltmeter.

Box N, Del Mar, California 92014 Telephone (714) 755-1134

See your local distributor!

Distributor inquiries invited.

For LM-3 Circle (54) on Reply Card
For LM-3.5 Circle (55) on Reply Card

For LM-40 Circle (56) on Reply Card
For LM-4 Circle (57) on Reply Card

Convergence Trouble

continued from page 37

enlist your scope to see if all of the sweep signals are there. Figure 14 gives the amplitudes and waveforms of the four input signals of the Zenith 19EC45 chassis.

Try all adjustments

When the convergence is wrong in just one area, the best quickie test is to tune in a crosshatch pattern and attempt to do a complete convergence job. Then, notice which controls do not respond in the usual way. The problem often will be in the coil or control that does nothing, or operates incorrectly. Or, at least, the defect probably is in the immediate circuitry.

Think of the convergence board as the command post, telling the convergence yoke on the neck of the picture tube what to do. Now, are the proper signals leaving the convergence board? If so, perhaps the convergence coils are at fault.

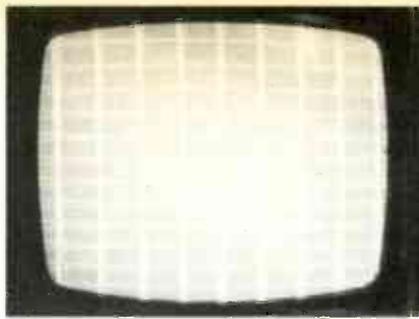


Fig. 13 When all convergence corrections are eliminated, all of the crosshatch lines (except blue-vertical), exhibit the parabolic bending. In addition, the vertical lines at the extreme right and left are moved sideways, with blue in the center of red and green.

One method is to attach the scope probe **across** the coil or control that you suspect. Adjust it, and see if the waveform changes enough. Some examples are given in Figure 15.

Of course, waveform analysis is not an exact science in convergence circuits. The amplitudes and wave-

forms both change with the adjustments. And that's just the point of this test. You should expect **something** to happen, when you turn the knobs. If nothing happens this is an excellent place to start your search.

Picture tube paths

These last steps of the convergence system have fooled more technicians than all of the other stages have. I'm referring to: **the convergence coils on the neck of the picture tube; the spaces between the core of these coils and the glass of the tube; and the spaces between the neck and the convergence electrodes inside the tube.**

First, we'll look at the coils. Each assembly (Figure 16A) has four separate windings. Two are for vertical correction, and two (the smaller ones) are for horizontal. The two vertical coils are connected together by a twisting and soldering of the wires (usually the joint is then hidden between the coils and under the covering). Also, there are two lugs, or two connections where

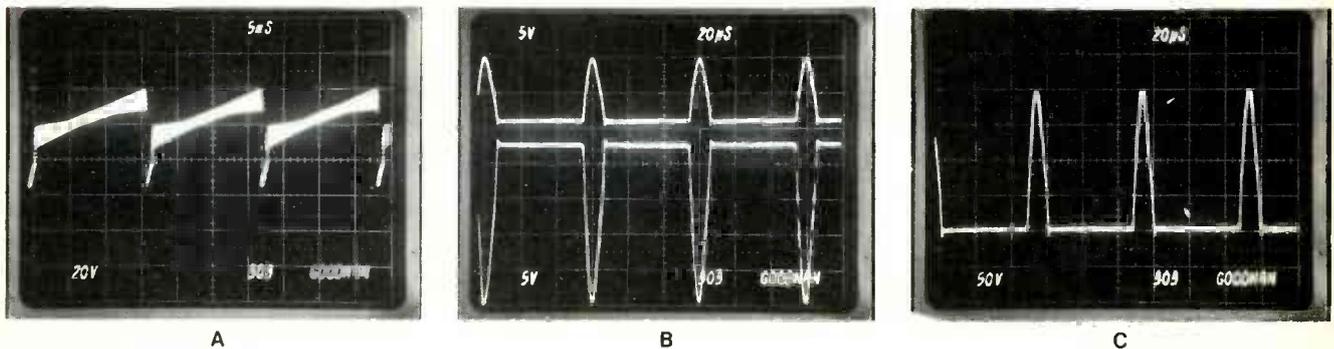


Fig. 14 These are the four input waveforms to the convergence board of a Zenith 19EC45 chassis. (A) Vertical-sweep sawteeth (with butterfly wings from the pincushioning) of about 55 VPP enter at pin 6. (B) The waveform at top is the 8.8 VPP horizontal pulses at pin 7, while below are shown the 27 VPP negative-going pulses at pin 2. (C) More positive-going pulses of 200 VPP are found at pin 4 of the convergence plug.

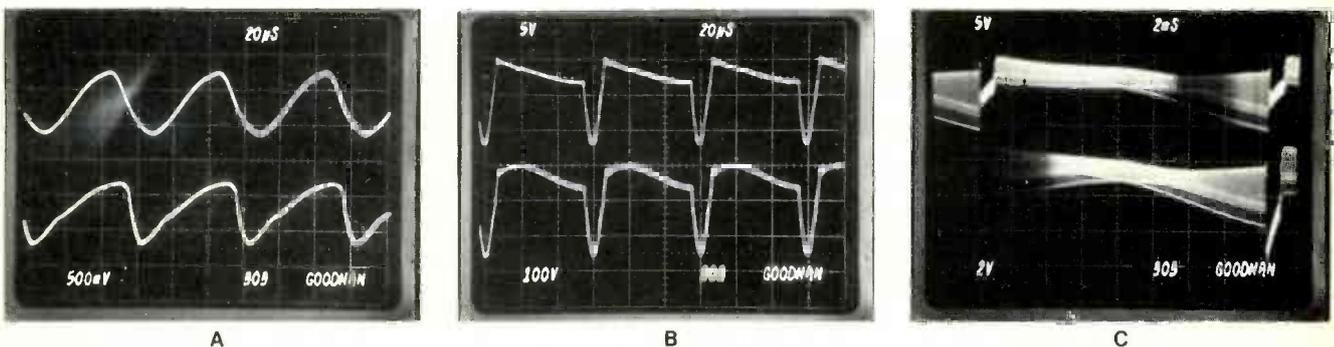


Fig. 15 One test of a convergence control or coil is to attach the scope probes across the terminals and adjust it. The waveforms of (A) were found across T601 when R601 was turned from one end to the other. (B) shows the waveform of L601 at the two extremes of adjustment. The waveforms of (C) were taken at the end adjustment of R618, when the scope was across T601.

You get **MORE** from the **RCA 10J106 Test Jig**

MORE ease in changing yoke impedances. Tapped horizontal and vertical transformers with front-panel switches eliminate plug-in impedance adapters.

MORE sets can be serviced . . . almost all makes — standard focus tube, hybrid or solid state, including PIL types.

MORE screen area. Bigger, shielded 19" picture tube gives large raster area.

MORE high-voltage capability. No expensive "extras" needed to service 33kV sets.

MORE ease in troubleshooting with Set-Up Index, extension cables, and a range of optional adapters.

MORE savings in time and labor. Quick to hook up, easy to use.

MORE dollar savings because the need for external impedance-matching devices is minimized.

MORE convenience. Simple adapters and no transformers mean less clutter in your shop.

MORE safety. Designed to handle chassis up to 33kV without danger from X-ray radiation.

MORE years of dependable service thanks to RCA high-quality design and construction.

Contact your RCA Test Jig Distributor or write RCA Distributor & Special Products Division, P.O. Box 100, Deptford, N.J. 08096, Attn: Sales Promotion Services.



RCA Color TV Test Jig


For More Details Circle (24) on Reply Card

the wires to the convergence board are attached. The horizontal coils are connected in the same manner.


That makes a total of six connections with a possibility of opens or intermittents for each

assembly (there's one assembly for each gun).

continued on page 40

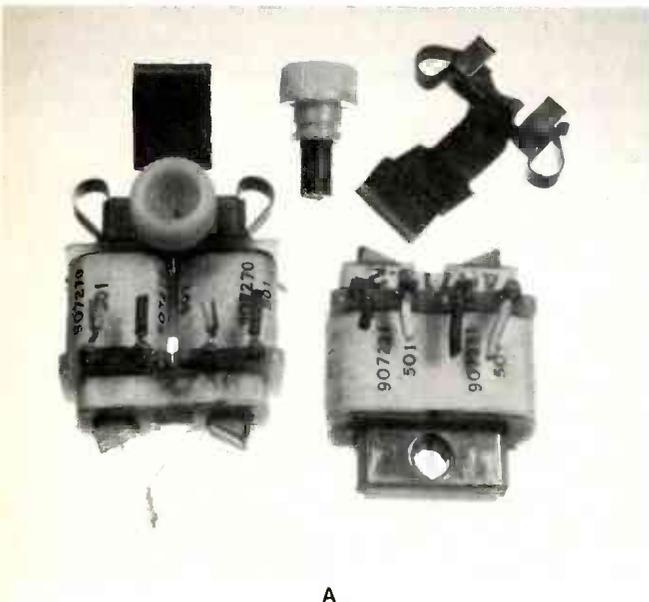

A

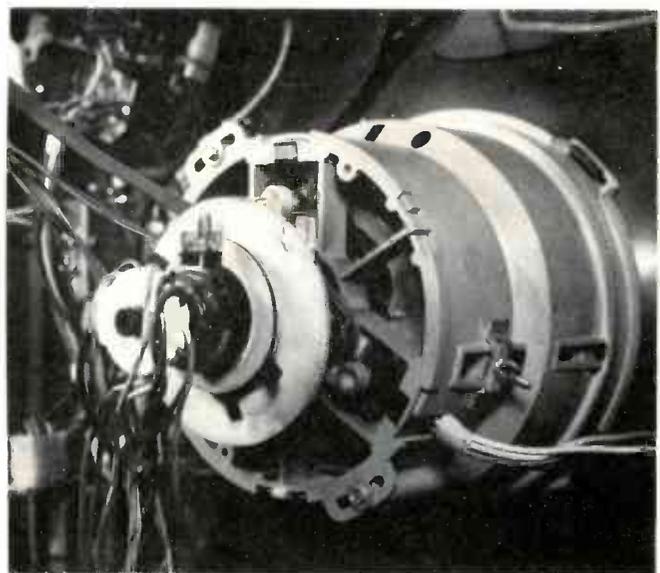

B


Fig. 16 Two convergence winding/magnet assemblies are shown in (A); one is complete. Notice the beveled tips that should fit tightly against the glass neck of the picture tube, and the spliced wires between the horizontal coils at the bottom. The disassembled unit shows the rotary magnet that should be clamped between the two core halves, by the complex spring. If the spring is weak, the magnet can move randomly, causing mysterious changes of center convergence. These convergence assemblies are mounted in the deflection-yoke housing (B) in many of the early rectangular models. Make sure the convergence cores are seated firmly against the neck of the picture tube.

Convergence Trouble


continued from page 39

Even worse, the ends of the powdered-iron cores don't always fit snugly against the glass neck. Convergence systems usually have barely enough power for proper corrections; there is no reserve. So, a small gap between core and glass can reduce the correction for one gun.

Coil assemblies that fit tightly

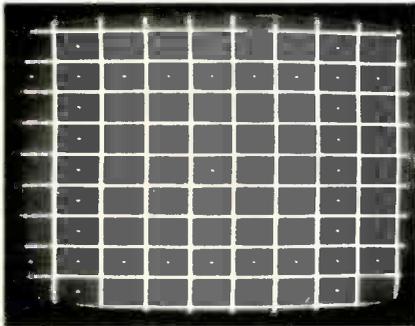

A

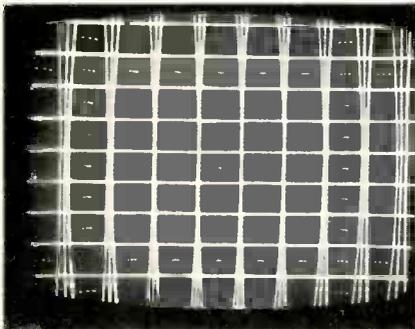

B

Fig. 17 Picture (A) is a normal crosshatch pattern on a new General Electric receiver that uses an in-line-guns picture tube. When the convergence coil was shorted out, the horizontal lines of the crosshatch (B) were not affected.

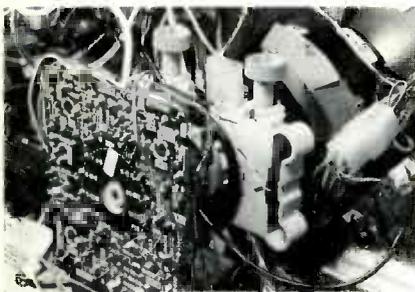


Fig. 18 Picture tubes with in-line guns typically have simplified convergence adjustments and components. This GE convergence assembly has four rotary magnets for center converging the red and blue with the green. Most of the dynamic convergence comes from a special winding inside the deflection yoke.

inside deflection-yoke covers, as pictured in Figure 16B, have been known to bind against the plastic, thus they were prevented from touching the glass neck.

But the worst problems of all can happen with those convergence-coil assemblies that are mounted separately on the neck of the picture tube. If the assembly becomes twisted in a circle (even a small amount), or is moved forwards or backwards a bit, the convergence coils no longer are "over" the metal pieces that conduct the magnetic fields to the gun. When these lengthened gaps appear in the magnetic paths, the field strengths are weakened, and the convergence adjustments are not sufficient to accomplish the usual correction.

Tubes With In-Line Guns

Many of the new color TV's have picture tubes with all three electron guns in a horizontal line, rather than in a triangle. The convergence boards are less complex, and fewer adjustments are required.

Figure 17 shows a "hatchdots" pattern (from an ATC-10 American Technology generator) when the convergence was correct, and another pattern when the convergence coil was shorted out. Notice that the horizontal lines did not change. With this Chassis 19YC-2 General Electric, the "vertical" adjustments changed the spreading of the vertical lines **only** at the extreme top and bottom of the picture. The "horizontal" adjustments affected the **sideward** position of the vertical lines **only** at the extreme right and left edges of the screen. The green gun is the center one of the three guns, and it does not need any convergence adjustments.

Only two vertical and two horizontal center convergence magnets are on the convergence assembly (Figure 18), plus terminals for adding or removing a set of coils from the circuit. The small convergence board has only about six adjustments. One unique difference, compared to the delta circuits, is that **most of the convergence correction is applied to an extra winding** (or windings, it's difficult to see inside) **of the deflection yoke.**

Recommended Servicing Methods

These are the servicing methods

we have found to be most effective for identifying convergence problems:

- Tune in a stable crosshatch pattern, which allows you to see all vertical and horizontal lines;
- Lock the TV vertical and horizontal to the crosshatch pattern, then check and correct (if necessary) any problems of improper width, height, and linearity;
- Check the purity of all three colors, and readjust it if necessary;
- Try all adjustment controls to determine if an average amount of line movement can be obtained (controls that do not respond, or the components connecting to them, should be suspected);
- Visually examine the board area around any coils or controls that do not control the lines correctly;
- If the core of a coil is stuck, or if turning the core doesn't produce the desired action, check the core for cracks in the powdered iron. Remove each suspected core and substitute one for another coil, as a test;
- Operate the receiver for a time (perhaps 10 to 15 minutes), turn off the power, and feel the coils, controls, and resistors for any excessive heat. **Coils having shorted turns often operate too hot;**
- Check in-circuit the forward and reverse resistances of the diodes. Remove any suspected ones for external resistance tests;
- Remember that multiple-diode assemblies have been known to cause hard-to-find intermittents. Replace the entire assembly, if there is any question;
- If all vertical (or all horizontal) adjustments of one color have little or no effect, check the resistance of the proper convergence coil on the neck of the picture tube. Some opens or intermittents have been found where the two halves of the winding are connected;
- Waveform analysis in convergence circuits is not very accurate, but a definite change of waveform or amplitude should be seen on a scope when it's connected across a coil or control, and the adjustment is changed; and
- When none of the adjustments are strong enough, suspect wrong positions of the convergence yoke. Remember that circular or front-to-back errors of more than 1/4 inch can be important. □

TV TUBE STOCK

By Gill Grieshaber, CET

These were the fast-moving TV tubes during 1976 in my shop. We service all brands, but do few warranty repairs.

Local conditions, such as the number of carry-in portables, or any unusually-high sales of one brand in your area, can change these figures. Therefore, you should adjust your buying, just as soon as a trend becomes apparent. Larger shops should expect to stock multiples of these quantities.

An arrow pointing upward beside a quantity indicates the sales have increased recently, and a downward arrow shows decreased sales of the tube.

| TUBE Type | Quantity | TUBE Type | Quantity | TUBE Type | Quantity | TUBE Type | Quantity |
|--------------------|----------|-------------------------|----------|-----------|----------|-------------|----------|
| 1G3/1B3 | 1 ↓ | 6BS3 | 1 | 6HA5 | 2 | 6LQ6/6JE6 | 10 ↓ |
| 1V2 | 1 ↓ | 6BW3/6DQ3 | 2 | 6HB7 | 1 | 6LR6 | 2 |
| 2AV2 | 1 ↓ | 6BZ6 | 1 ↓ | 6HF5 | 1 ↓ | 6LT8 | 1 |
| 2BV2 | 1 ↓ | 6CB6 | 1 ↓ | 6HQ5 | 2 | 6LU8 | 2 |
| 3A3 | 10 ↓ | 6CG3/6CD3/ 6CE3/6DT3 | 4 | 6HS5 | 2 ↓ | 6LY8 | 2 |
| 3AT2 | 2 ↓ | 6CG8 | 1 | 6HS8 | 1 | 6MD8 | 1 ↓ |
| 3AW2 | 1 | 6CJ3 | 2 | 6HV5 | 4 | 6T10 | 1 |
| 3BS2/3BT2/ 3BW2 | 1 | 6CL3 | 3 ↓ | 6HZ6 | 3 | 6U10 | 1 |
| 3CN3 | 1 | 6CM3 | 1 | 6J10/6Z10 | 2 | 6X9 | 1 ↓ |
| 3DB3 | 1 | 6CS6 | 1 ↓ | 6JA5 | 1 ↑ | 8FQ7 | 1 |
| 3DF3 | 1 | 6DS4 | 1 | 6JB5 | 2 | 8LT8 | 1 ↓ |
| 3DG4 | 1 | 6DQ5 | 1 | 6JB6 | 1 ↓ | 10GK6 | 1 ↓ |
| 3DJ3 | 3 ↑ | 6DW4 | 10 | 6JC6 | 2 ↓ | 12AU7 | 1 |
| 4BZ6 | 1 | 6DX4 | 1 ↓ | 6JD6 | 1 | 12AX7 | 1 ↓ |
| 4DT6 | 1 ↓ | 6EA7/6EM7 | 1 ↓ | 6JF6 | 1 | 12BY7 | 2 |
| 4EH7 | 1 ↓ | 6EA8 | 1 ↓ | 6JH6 | 1 ↓ | 12CL3 | 1 |
| 4EJ7 | 1 | 6EC4 | 1 ↓ | 6JK5 | 1 ↑ | 12GW6/12DQ6 | 1 ↓ |
| 5GH8 | 2 | 6EH7 | 1 | 6JS6 | 4 | 12HG7/12GN7 | 2 ↓ |
| 5U4 | 1 | 6EJ7 | 2 | 6JT8 | 1 | 12HL7 | 2 ↑ |
| 6AD10 | 1 ↓ | 6EN4 | 1 | 6JU8 | 2 | 17BS3 | 1 |
| 6AF9 | 1 | 6EW6 | 2 | 6JW8 | 1 | 17CT3 | 1 ↑ |
| 6AG9 | 1 ↓ | 6FM7 | 1 ↓ | 6JZ8 | 1 | 17JZ8 | 1 |
| 6AL5 | 1 ↓ | 6FQ7 | 5 | 6KA8 | 2 | 17KV6 | 1 |
| 6AQ5 | 1 ↓ | 6GE5 | 1 | 6KD6 | 3 | 19CG3 | 1 |
| 6AS5 | 1 ↓ | 6GF7 | 3 | 6KE8 | 2 | 21GY5 | 1 ↓ |
| 6AU4 | 1 | 6GH8 | 10 ↓ | 6KM6 | 1 ↑ | 21LR8 | 1 ↓ |
| 6AU6 | 1 | 6GJ7 | 1 ↑ | 6KN6 | 1 | 23Z9 | 1 |
| 6AW8 | 1 ↓ | 6GM6 | 2 ↓ | 6KT8 | 2 | 24LQ6 | 1 |
| 6AX4 | 1 | 6GN8 | 1 ↓ | 6KZ8 | 2 ↓ | 26HU5 | 1 ↓ |
| 6BA11 | 1 | 6GU7 | 6 | 6LB6 | 4 | 31JS6 | 1 ↓ |
| 6BE3 | 1 ↓ | 6GW6/6DQ6 | 1 | 6LE8 | 1 | 33GY7 | 1 ↓ |
| 6BK4 | 10 ↓ | 6GX6 | use 6HZ6 | 6LF6 | 1 | 34CE3 | 1 |
| 6BL8 | 2 | 6GY6 | use 6HZ6 | 6LF8 | 1 | 35LR6 | 1 |
| 6BQ5 | 1 | 6GX7 | 1 | 6LH6/6LJ6 | 2 | 36MC6 | 1 |
| | | | | 6LJ8 | 1 ↑ | 40KD6/36KD6 | 2 |

Note: ↑ indicates sales are increasing
↓ indicates sales are decreasing

PLL... A New Brain For CB Radios

By Marvin J. Beasley, CET

All of the new 40-channel CB radios have Phase-Locked Loops (PLL's) to generate the receive and transmit frequencies, using just a few crystals. These PLL's include both digital and analog circuits, and you need to understand the operation of this important development.

Will the diagnosis and repair of a defect in the circuit shown in Figure 1 be a "nightmare" or a "piece-of-cake"? You can keep it from being a nightmare, if you thoroughly understand the circuit operation.

This circuit is a Phase-Locked Loop, which is usually shortened to PLL. A quick look at a typical schematic will convince you that the circuit is complicated. Why, then, should the CB-radio manufacturers decide to use it in preference to other systems, such as the frequency synthesizer? The reasons can be condensed into these three words: cost, scarcity, and performance.

Even when the 23-channel radios required 14 crystals, a shortage of crystals had begun. Therefore, building millions of new CB radios for 40 channels, with each radio having perhaps 25 crystals, certainly is not practical, considering the cost and scarcity of good quartz crystals.

In contrast, a PLL circuit might have only one, two, or three crystals (depending on model and design) to generate the 80 frequencies (40 for transmitting and 40 for receiving) needed for the new allocation of 40 CB channels. The cost factor is obvious; we'll discuss the improved performance later.

Analog Plus Digital

One mental roadblock on our way to complete understanding of PLL's is the combination of analog and digital principles. Most analog

stages amplify the signal, making good linearity desirable. The signal usually varies both in amplitude and waveform.

Digital circuits seldom amplify; unity gain is the norm. Waveforms of the signal usually are pulses or square waves, which are important only for the peaks, for these determine the "states". One peak is at supply voltage ("high") and the other is near zero ("low").

However, the digital circuits in PLL's either have DC switching voltages, or dividers which are self-contained inside IC's, so they are analyzed as "black boxes". Therefore, troubleshooting these circuits probably is easier than other types of digital devices.

Before analyzing the operation of PLL's, we'll take a short look at conventional heterodyne synthesizers.

Crystal-Controlled Heterodyne Synthesizers

A total of 46 crystals would be necessary for the original CB circuits which had one transmit crystal and one receive crystal for each channel. Figure 2 shows that a careful selection of crystal frequencies in a heterodyne-type of frequency synthesizer can reduce the crystal count to 14. If synthesizers were used in the new 40-channel CB radios, it's likely 25 crystals would be required. Of course, such a large number cannot be considered. This leaves PLL's as the only practical solution to the crystal problem.

PLL's Are Not New

Phase-Locked Loop circuits are not new, but many additional uses have been found for them lately. One example of an old PLL circuit is found in the horizontal locking of TV receivers (see Figure 3). Both the television and digital names for the stages are given on the block diagram, so you can become accustomed to the unfamiliar ones. The AFT action in TV receivers is very similar; however, the phase detector has only **one** input signal. When the frequency changes, a DC voltage is developed because of the changing **phase** of the signal.

Well-designed circuits such as these can be depended on to keep the output signal locked to the desired phase and frequency of the standard signal (horizontal sync, in one example). At least, they can over a narrow range of frequency. Broader pull-in and locking ranges require a DC amplifier between the low-pass filter and the oscillator. DC amplifiers in CB PLL's permit solid locking over a wide range of frequencies.

There's one serious limitation, if we want to adapt the circuit to other applications: the standard signal (sync) and the output signal (drive for the horizontal-output stage) have the **same** frequency.

For other applications it is desirable for the standard and output frequencies to be different. Sounds difficult, but it isn't.

Even with analog circuits, it's possible to fool the simple PLL of Figure 3 into locking at specific

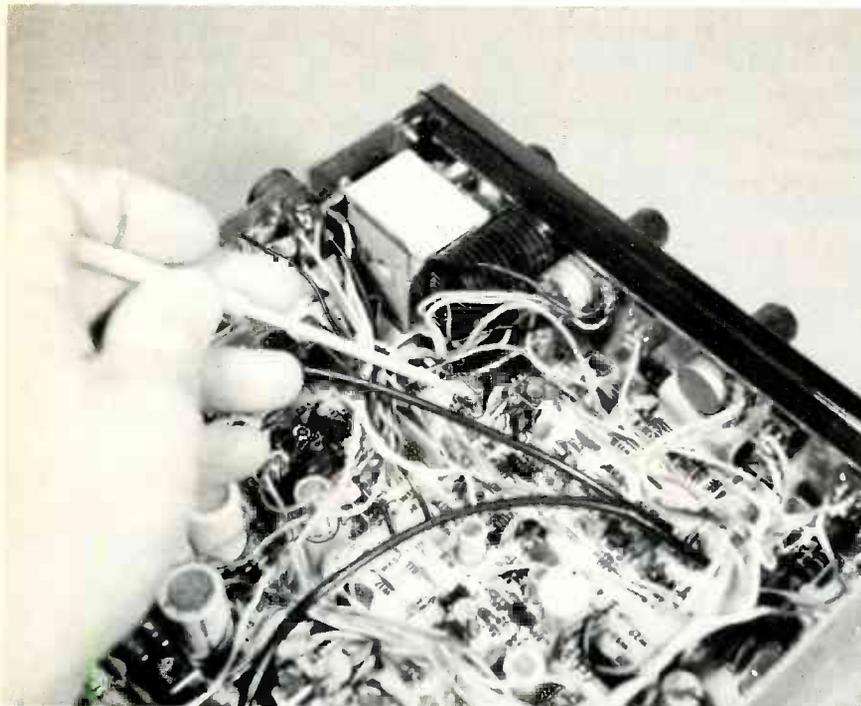


Fig. 1 The reference-frequency crystal of this Johnson PLL is pointed out by the alignment tool. Just to the right is the large IC, and beyond is the combination channel switch and digital readout.

multiples of frequency. A resonant circuit, tuned to the **third** harmonic of the standard signal and inserted at point "X" between the standard signal and the phase detector will cause locking at the third harmonic of the standard signal. **This is frequency multiplication;** the frequency of the output signal is three times that of the standard.

Alternately, adding a resonant circuit tuned to the **third** harmonic of the **desired** output frequency and inserting it at point "Y" will produce phase-lock with an output frequency that's one-third of the standard. **This is frequency division.**

Notice, in both cases, that when locking occurred, both signal inputs to the phase detector had identical frequency. So, **the secret of obtaining either higher or lower output frequencies** (relative to the standard) **is to add a frequency-changing device in series with one or both of the input signals to the phase detector, making the sample conform to the standard.**

Locking to harmonics doesn't give much choice of output frequencies, but by making some minor changes, it's possible to increase the number of phase-lock output frequencies. This is where digital circuits are far better than analog.

Include A Divider

Several changes are required to improve the simple PLL so it will operate over a larger range of output frequencies (Figure 4). First, the phase detector with the double diodes is replaced with a phase comparator, which might be a flip-flop multivibrator arranged so the widths of the output pulses vary with the differences of frequency and phase between the two signals coming into the comparator. After filtering, the output pulses become a DC voltage of a value determined by the width of the pulses. Incidentally, the filtering prevents locking at the **sum** frequencies. A tiny trace of the desired frequency fed into an oscillator along with the DC error-correcting voltage helps the locking. Without filtering, both the

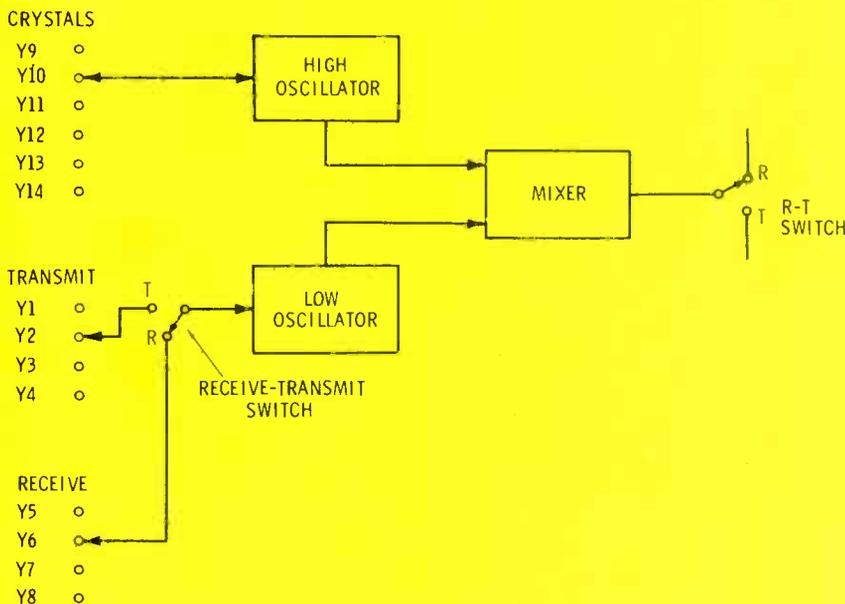


Fig. 2 Heterodyne frequency synthesizers were developed to reduce the number of crystals (46) that previously were necessary for 23 CB channels. By combining in a mixer stage the RF outputs of two crystal oscillators, extra sum-and-difference frequencies are produced. A proper selection of 14 crystals can supply the 46 frequencies necessary for receive and transmit of 23 channels.

difference and sum frequencies would be present in the DC control voltage. This might tend to pull the oscillator to the wrong frequency.

An amplifier stage increases the amplitude of the error-correcting DC voltage. Higher gain in the loop increases the accuracy of the locking.

Controlling the bias of an oscillator transistor or tube (often the case with horizontal oscillators) cannot change the frequency as much as is desired in most PLL's. So, a varicap diode is used to provide a wide choice of frequencies

when controlled by the error DC voltage.

Finally, a digital frequency divider is placed between the oscillator and the phase comparator. Closed-loop locking varies the frequency of the AC-sample signal at the phase comparator until it matches that of the standard signal (usually a crystal-controlled oscillator). That forces the frequency of the VCO (and the output signal) to be higher than the standard frequency by the same multiple as the division of the divider.

In other words, if the divider has

a ratio of 15, the output frequency must be 15 times that of the standard. The number of possible output frequencies is limited only by the divider ratio. However, these are the limitations: the output frequency always is higher than the standard frequency; and the frequencies are in steps which are equal to the standard frequency. For example, if the standard frequency is 1 MHz, the output frequency might be 2 MHz, 3 MHz, 4 MHz, and so on, in 1 MHz steps, depending on the divider ratio.

CB channels are spaced every 10

Fig. 3 These are the stages necessary for frequency control by the Phase-Locked Loop (PLL) principle. Many AFC stages for horizontal oscillators in TV's are PLL's. The TV stages are listed in parentheses. The limitation of this circuit, when adapted to other applications, is that the standard and output signals have the same frequency.

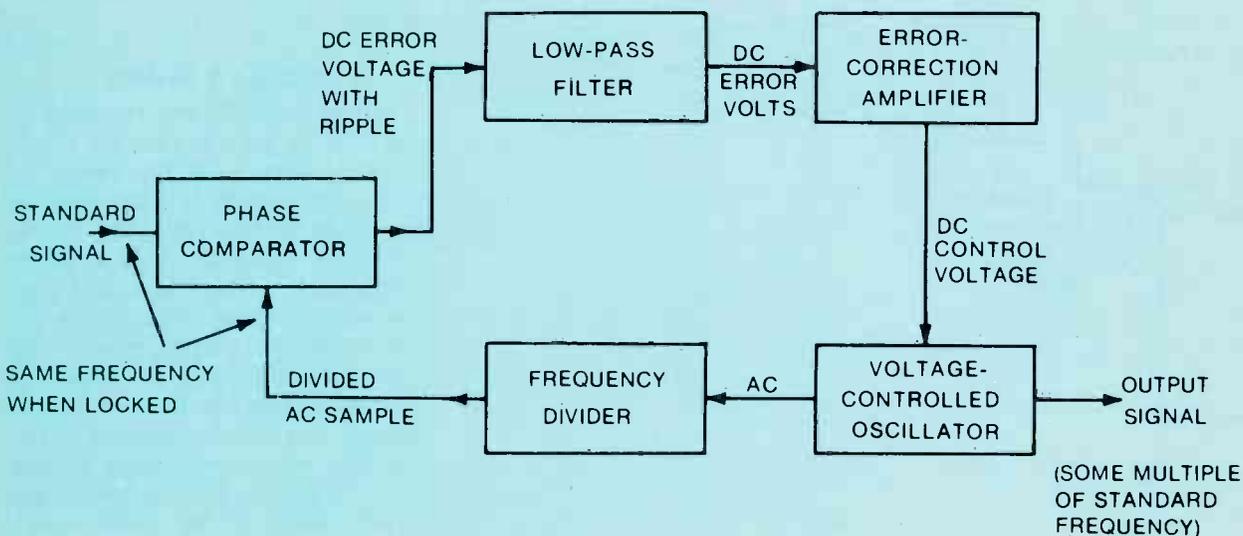
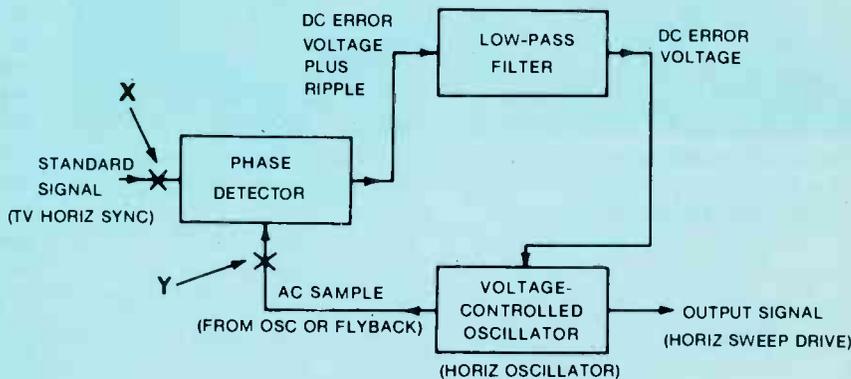


Fig. 4 Addition of a frequency divider to the sample signal before it reaches the phase comparator tricks the voltage-controlled oscillator (VCO) into producing multiples of the standard frequency. Notice that the two inputs to the phase comparator continue to have the same frequency

when locked. The output frequency depends on the standard and the ratio of the divider; it equals the standard frequency times the "divide-by" of the divider. The limitation is that a fixed-ratio divider allows only one output frequency.

KHz, so the circuit of Figure 4 can work properly only when the standard signal measures 10 KHz. However, it's a long jump up to 27 MHz, and there are other problems. More circuit refinements are necessary.

At Last, 27 MHz

Figure 5 shows the block diagram of a practical PLL for CB transmitter use. Crystal oscillators for 10 KHz are difficult to build. Instead, a higher-frequency standard is chosen, with a following fixed divider to provide 10 KHz to the phase comparator.

Next, the fixed divider for the AC-sample voltage is replaced by a programmable-frequency divider. These dividers change ratio according to the switching of several control voltages in Binary-Coded Decimal (BCD) logic. Because the reference is 10 KHz, the VCO frequency changes by 10 KHz each time the divider changes one step.

For example, dividing by 928 makes the VCO frequency 9.28 MHz; or dividing by 929 gives 9.29 MHz.

However, it isn't possible to divide even more and obtain the transmit frequency directly. Dividing by 2725 provides 27.250 MHz, and a division by 2726 gives 27.260 MHz, but Channel 23 is 27.255 MHz. The CB channel frequencies are **not** divisible by 10. The reference frequency could be 5 KHz, but this would require a division by 5451 for Channel 23.

Therefore, some models include another crystal oscillator, which, along with the VCO, feeds the mixer. Sum-or-difference frequencies from the heterodyne mixing can provide the correct channel frequencies.

The other reason for the additional oscillator is to provide the receive frequency, which always is above or below the transmit frequency by the frequency of the first

IF in the receiver. Changing the PLL from receive to transmit could consist of switching-in the proper crystal.

Notice that the same two crystals are used for all transmit frequencies, so all channels will have exactly the same accuracy (or error). Likewise, all of the receive frequencies have the same accuracy.

We are ready now to examine the circuit actions of one PLL. There are many other variations, and our explanation does not necessarily apply to them. We will cover the other types at a later date.

Johnson PLL

The block diagram of an E. F. Johnson 23-channel Phase-Locked Loop digital synthesizer (originally developed for the Messenger Model 191) is given in Figure 6.

This PLL is nearly the same as the example in Figure 5, although it doesn't appear that way at first.

Heat it Cool it

Hot 750°F Air or a cooling breeze at the flick of a switch lets you . . .

- Shrink most heat shrink tubing
- Cure Epoxies
- Reflow Solder
- Shrink packaging films
- Heat and cool components
- Expand frozen fasteners
- Reflow hot melt adhesive
- Repair vinyl
- Soften conformal coatings

Precisely control the air flow of this compact Ungar Heat Gun. The tool *weighs only 13 oz.* and is equipped with a 3-way, Hot-Off-Cold switch, a reducing baffle for pin-point heating, and three reflectors for shrink tubing.

See the UNGAR HEAT GUN at your local Authorized Ungar Distributor or call or write us for more information.

Ungar.

DIVISION OF ELDON INDUSTRIES, INC.
P.O. Box 6005, Compton, Ca. 90220 • (213) 774-5950



For More Details Circle (53) on Reply Card

The drawing is turned around from the example, because several of the basic circuits of the Johnson PLL are inside one IC (U101).

The oscillator for the standard frequency (crystal Y101 and part of U101) does double duty, supplying the comparator, and also furnishing a signal to the offset mixer. The oscillator labeled "high oscillator" is the one we mentioned as being necessary to solve the problem of the channel frequencies not being divisible by 10. In addition, the high oscillator has one crystal for transmit and another for receive.

Output from the VCO does not go directly to the programmable divider, but first goes through the "synthesizer mixer" and the Q106 amplifier before reaching the divider (which is inside of U101).

Now that you are oriented to the locations of the various stages, we'll start the circuit analysis.

Transmit Operation

When any circuit has a closed loop, it's difficult to know where it all starts. Where is the beginning, and where is the ending of a circle? Although the Voltage-Controlled Oscillator (VCO) can be considered as the heart of a PLL circuit, any explanation starting there gets very confusing. Actually, you need to know everything at once, so keep in mind the purpose of each stage, as we start with the channel switch

and the frequency standard.

Crystal-controlled frequency standard

Crystal Y101 and part of IC U101 comprise the oscillator of the 5.120-MHz frequency standard, that's used as a reference for the VCO signal. Because a frequency of 10 KHz is needed at the phase comparator, the signal goes through a "divide-by-512" non-adjustable divider, and the 10-KHz output is sent to the phase comparator (the divider and the comparator both are inside U101). These conditions and frequencies do not change, regardless of the channel selected or the receive/transmit mode.

When the loop is locked, the other comparator input (from the programmable divider) also **must** have a 10-KHz signal. In fact, **the PLL will vary the frequency of the VCO until the 10-KHz frequency is obtained.**

Channel switching

The main duty of the channel-switch contacts, the switching-logic IC's (U102 and U103), and the programmable divider is to select the proper divider ratio so that the number on the channel dial and the transmit output frequency both are correct for the channel desired.

Up to Channel 23, the programmable divider operates from a hexadecimal code (six numbers). One section of the channel switch

activates U102 and U103, which are connected as NAND gates. In turn, they determine the DC voltages at 4 divider pins of U101. Voltages at two other divider pins are controlled directly by the channel switch. (Above Channel 23, the 40-channel models also control two more divider pins, making a total of eight pins. More about that later.)


On Channel 1, the divider ratio is 81, for Channel 10 it's 92, and for Channel 23 the ratio is 110. All "divide-by" ratios are determined by the "high" or "low" state of the six inputs to the programmable divider.

Comparator and VCO

Inside U101 is the phase comparator. It is not a duo-diode type, but uses a type of pulse-width modulation. From the comparator, comes a DC voltage; a zero voltage when the two input frequencies are identical (phase locked), and a negative or positive voltage when the two frequencies are not the same. The polarity is such that it changes the VCO frequency in the direction necessary for phase-lock at the comparator. Major errors of frequency produce large voltages, and the voltage becomes smaller as the error is reduced.

However, the varicap diode (CR101), which determines the VCO frequency, requires a reverse

Fig. 5 The previous schematic plus changes and additions becomes a practical PLL for a CB radio. In order to produce 10-KHz steps, the phase comparator requires 10 KHz at both inputs. A fixed divider changes the standard frequency to 10 KHz. A programmable frequency divider replaces the one-ratio divider shown previously. It is controlled by switching circuits. Output of the VCO is in 10-KHz steps, but the channel frequencies are not divisible by 10 KHz, so another crystal oscillator is necessary to permit the channel frequencies to end in 5 KHz. Another requirement, not shown, is for a frequency change during receive.

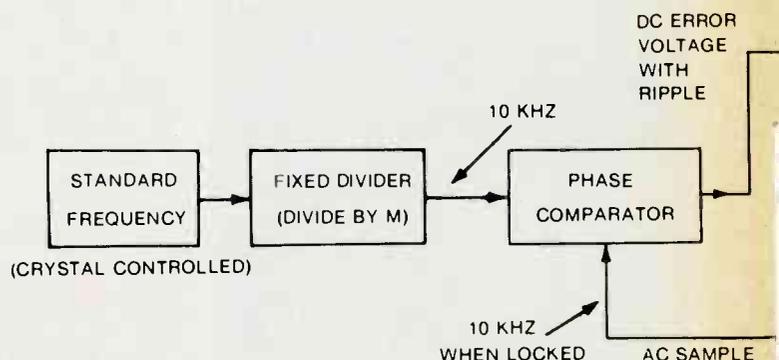

voltage (positive to the cathode). Consequently, a fixed positive bias is added to the variable-polarity voltage from the comparator. Following filtering of the error-correcting DC voltage, the voltage at the varicap diode might swing from near zero to about 6 or 7 volts, according to the amount of frequency error, with phase-lock occurring at about +3.5 volts.

Of course, it is true that the varicap voltage **must** be different for each channel. When the operation is normal, the varicap control voltage (at TP1) should change slightly with each channel selected. If the circuit can't achieve phase-lock, the voltage will be too high or too low, and probably not change with each channel. This voltage can provide important clues during troubleshooting.

High oscillator and mixer

Output frequency from the VCO is not the final or desired frequency, either for the receive/transmit functions, or for the sample signal for the programmable divider.

So, the Q104 "high oscillator", Q105 "synthesizer mixer", and the Q106 "amplifier" stages have these **three** functions:


- They act as a strange kind of divider, giving a frequency reduction of slightly more than 34 for Channel 10, and more than 29 for

Channel 23. The purpose is to obtain a lower frequency that can be handled by the CMOS programmable divider. The difference frequency between the VCO and the high oscillator ranges from 810 KHz at Channel 1 to 1.1 MHz at Channel 23. That is the sample signal at the output of the amplifier, Q106.

- The high oscillator supplies the extra carrier (having a frequency ending in 5 KHz, such as 31.275 MHz for Y103) that must be mixed with the output of any VCO which is controlled by this kind of divider (produces only frequencies that are divisible by 10). The problem was explained before.

- It's easy to obtain the necessary 455 KHz decrease of PLL frequency during the receive function by switching in quartz crystal Y103 for transmit and Y102 for receive. This switching is done with diodes. CR105 is forward biased into conduction by the transmit B+, thus grounding the low side of Y103 for transmit. Then for receiving, CR104 is made conductive by the receive B+ and Y102 is properly grounded. The diode switching eliminates any need for additional talk/listen contacts, for the two B+ supplies already are selected by the talk/listen switch.

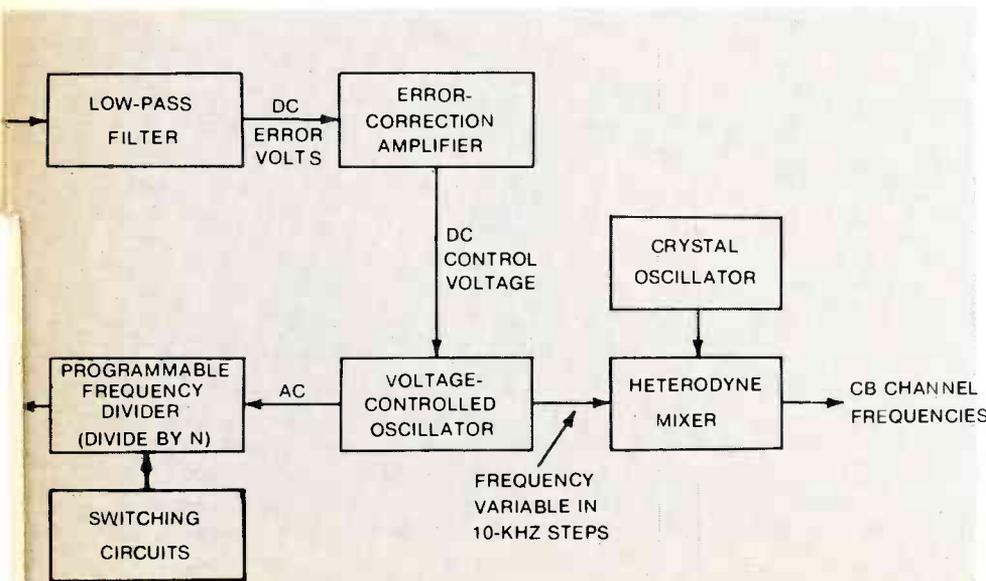Those are the stages and their functions in the Johnson PLL,



MORE FUNCTION GENERATOR FOR YOUR MONEY.



The Hickok Model 270 Function Generator gives you a lot more waveform generating capability than you'd expect for its price.

- Puts stable, calibrated, high quality sine, square and triangle waveforms from 1 Hz to 500 kHz at your fingertips.
- With external connections you can produce logic pulses, sweeps and ramps, AM and FM outputs, phase and frequency shift keying signals, tone bursts and more.
- Its an audio generator and much more.

Before you buy another function generator, check out the Hickok Model 270. Ask your Hickok distributor for full details or write us for our 4-page technical brochure.

\$225⁰⁰

HICKOK

the value innovator

INSTRUMENTATION & CONTROLS DIVISION
THE HICKOK ELECTRICAL INSTRUMENT CO.
10514 Dupont Avenue • Cleveland, Ohio 44108
(216) 541-8060 • TWX: 810-421-8286

For More Details Circle (25) on Reply Card

except for the "offset mixer" and the output switching.

Offset mixer and diode switching

At first, I could not understand why a sample of the 5.120-MHz carrier and a sample of the VCO output were fed to the "offset mixer". Of course, the VCO output frequency was not correct for any CB channel, but the divider **could** have been re-programmed to supply it. A Johnson design engineer gave me the answer: when the VCO operates on the same frequency as the RF 4-watt power output stage, there is a possibility of a few radios suffering a feedback between those two circuits. This would appear as a small amount of FM, and the

transmitting carrier would be wider than usual. To prevent any chance of such a problem, the VCO is operated at another frequency, then the 5.120-MHz carrier heterodynes it to the correct channel frequency.

CR102 and CR103 are operated as voltage-controlled switches, routing the transmitter signal to the transmitter predriver, and the receiver signal to the receiver mixer. They are keyed by the two B+ supplies.

PLL for receive

Functions of the PLL are the same during receiving as for transmitting, except for the two circuits that are switched by diodes. However, many of the frequencies are

different, so we have included a block diagram of the receive mode (Figure 7). The frequencies are for Channel 10, and the stars indicate the frequencies that are different for each channel.

Overall Operation

To make sure we have not gotten buried under a multitude of facts, let's briefly go through the basic operation, in slow motion.

Suppose the receiver is tuned to a channel, and all circuits are working correctly. Then, we turn to another channel, temporarily interrupting the phase-lock. For a split second, the VCO remains on the frequency of the previous channel. However, the programmable divider

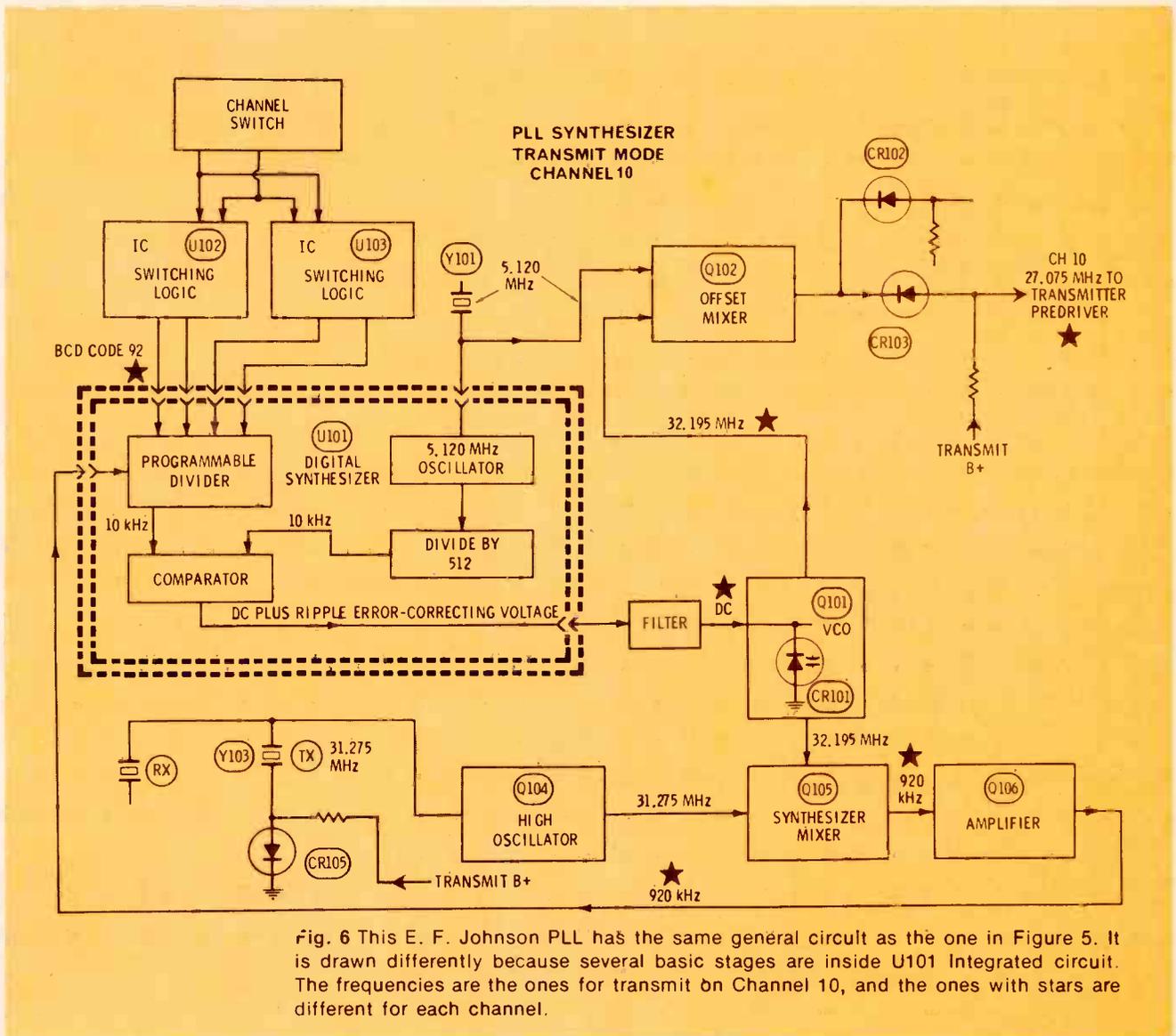


Fig. 6 This E. F. Johnson PLL has the same general circuit as the one in Figure 5. It is drawn differently because several basic stages are inside U101 Integrated circuit. The frequencies are the ones for transmit on Channel 10, and the ones with stars are different for each channel.

Chart 1

Johnson Phase-Locked Loop

| Channel | Divide-By Number | U101 Pin State | | | | | Transmit Frequency |
|---------|------------------|----------------|----|----|----|---|--------------------|
| | | 12 | 13 | 14 | 15 | 2 | |
| 1 | 81 | 1 | 0 | 0 | 0 | 0 | 26.965 MHz |
| 5 | 86 | 1 | 0 | 0 | 0 | 1 | 27.015 MHz |
| 10 | 92 | 1 | 0 | 0 | 1 | 0 | 27.075 MHz |
| 23 | 110 | 1 | 0 | 1 | 1 | 0 | 27.255 MHz |
| 30 | 115 | 1 | 0 | 1 | 1 | 0 | 27.305 MHz |
| 40 | 125 | 1 | 1 | 0 | 0 | 1 | 27.405 MHz |

Note: The first number of two-digit "divide-by" numbers (or the first two numbers of 3-digit "divide-by" numbers) determines the binary code for U101 pins 12, 13, 14 and 15. The second number of the two-digit "divide-by" numbers (or the third number of the 3-digit "divide-by" numbers) determines the binary code for U101 pins 2, 3, 4 and 5.

Decimal-To-Binary Conversion

| Decimal | Binary |
|---------|--------|
| 0 | 0000 |
| 1 | 0001 |
| 2 | 0010 |
| 3 | 0011 |
| 4 | 0100 |
| 5 | 0101 |
| 6 | 0110 |
| 7 | 0111 |
| 8 | 1000 |
| 9 | 1001 |
| 10 | 1010 |
| 11 | 1011 |
| 12 | 1100 |

Chart 1 The "divide-by" number of the programmable divider applies to the Johnson PLL (other brands probably have different numbers), while the "pin state" uses conventional binary "high" and "low" states. Enough examples of decimal-to-binary conversion are given for you

to check the programming. For example, the state for pins 12, 13, 14 and 15 are for the first divide-by number, and the second number gives the states for U101 pins 2, 3, 4 and 5. Channel 10 has divide-by 92. From the conversion, 9 is 1001, and 2 is 0010, for a total code of 1001/0010 for U101.

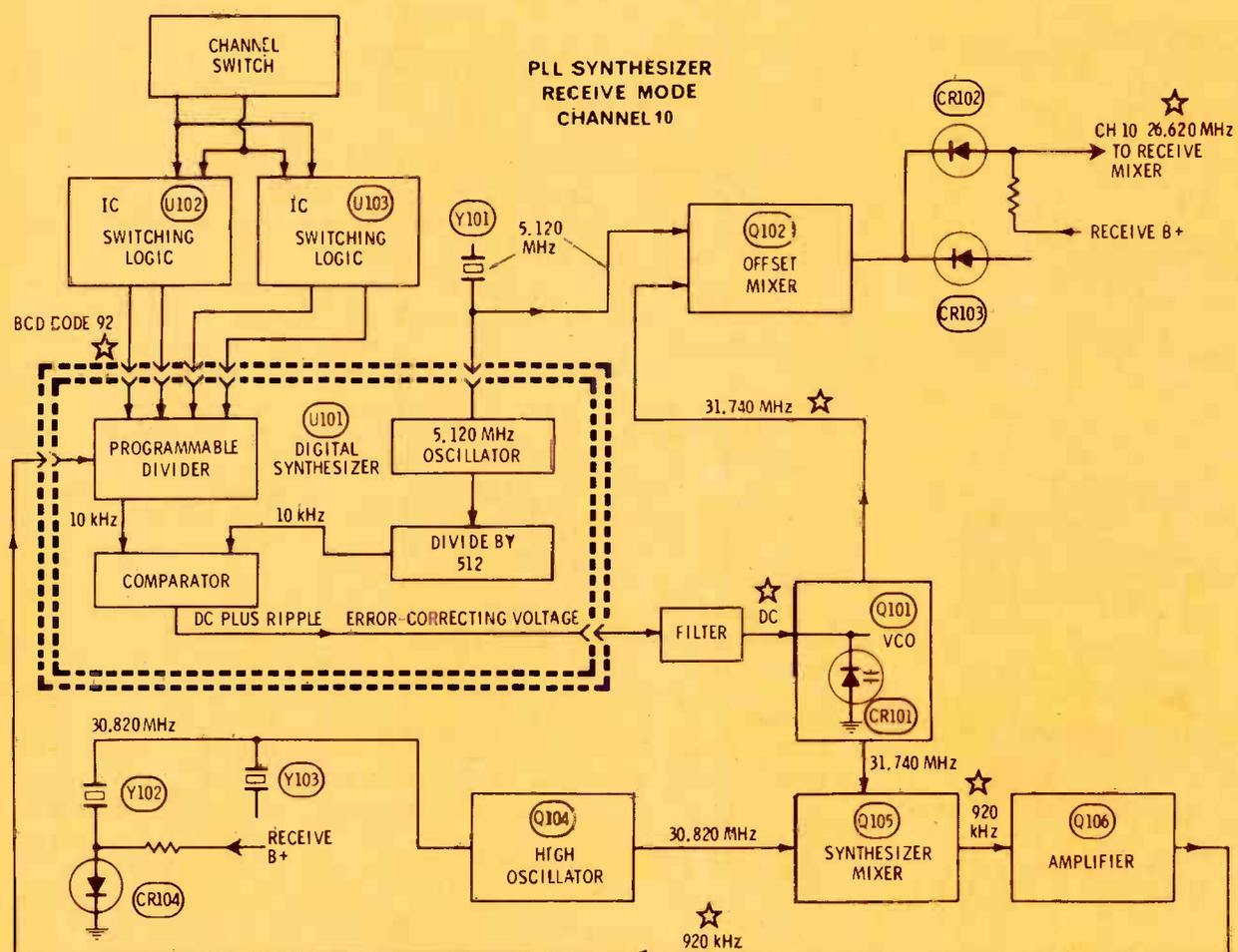


Fig. 7 The receive-function block diagram is the same except for the Channel 10 receive frequencies, and the diode keying of the high-oscillator crystal and the output from the offset mixer.

And In
This Corner...
The P.A. Champ!

New Champion

PC Series Public Address Line

Compact to fit more places, from offices to auditoriums. Versatile, to meet up to 90% of all P.A. needs. Solid state, for better performance and longer life. The finest, low cost, line on the market!



Model PC-10
10 WATT AMPLIFIER WITH SINGLE
MICROPHONE, CAN ALSO BE USED
AS A REMOTE LINE AMPLIFIER.



Model PC-20-1
20 WATT AMPLIFIER WITH SINGLE
MICROPHONE.



Model PC-20-2, PC-35, PC-60, PC-100
20, 35, 60 AND 100—RMS WATTS WITH
TWO MICROPHONES.



Model PC-112
Special high performance FM-AM monaural
tuners can be used with any amplifier, since
volume control is located on front panel.



Model PC-4
ADDS FOUR MICROPHONES TO ANY
AMPLIFIER.

To Order, Call Toll Free,
800-323-0228
or, write for complete information today.

Precision Electronics, Inc.
9101 King Street • Franklin Park, Illinois 60131
In Canada, Superior Electronics
In Caribbean, E. D. Magnus, Chicago, Ill.
Foreign, Morhan Exports, New York, N.Y.

has changed to another code, so the signal sent to the phase comparator is **not** 10 KHz.

Because the two input signals at the comparator do not have the same frequency and phase, an error voltage is generated and sent toward the varactor diode in the VCO. However, the AC filter slows down the travel time of the DC voltage, thus making the correction a gradual operation.

The change of varactor voltage swings the VCO frequency slightly, forcing the slave frequencies (output of the synthesizer mixer, and output of the programmable divider) to follow in turn. This brings the PLL nearer to phase-lock, which reduces the amount of DC correction voltage. It is a gradual process, somewhat like a car braking to a stop at a certain point. When the phase-lock is accomplished, the correction voltage virtually is zero.

Main job of PLL

The PLL has just one automatic and single-minded purpose, to vary the VCO frequency until the two input signals to the phase comparator have the same frequency and phase. That's all! Then it's up to the other stages to take the phase-lock condition and produce the correct channel frequency.

Reverse look at PLL

Now, the VCO signal travels through the synthesizer mixer (which acts as a kind of divider) and the programmable divider to the comparator. Also, it's certain the signal can't retrace the same path back to the VCO. Yet, it helps us understand the PLL operation better, if we start with the 10-KHz sample signal at the comparator, and mentally trace the signal backwards through the divider, the synthesizer mixer, and to the VCO. Visualize these dividers as frequency multipliers, as you do this.

Refer to the frequencies in Figure 7. The sample signal at the comparator is 10 KHz (we're assuming phase-lock), and the divider is programmed for code 92. Multiply the 10 KHz by 92. The answer is 920 KHz. Mix this with the high-oscillator receive frequency of 30.820 MHz, taking the sum product. The frequency now is 31.740

MHz. That's exactly the value needed for Channel 10 receive VCO.

Go one more step by mixing the 5.120 MHz signal in the offset mixer, and taking the difference product. Now, the frequency is 26.620 MHz, the correct Channel 10 receive frequency, and just 455 KHz less than the transmit frequency multipliers as you do this.

Doesn't this reverse view of the PLL help clarify your overall concept?

Divider Programming

In the discussion of channel switching, we mentioned that the divider is programmed by selecting the proper "high" state (+10 volts) of the "low" state (near zero) for six pins of the internal divider.

However, the divider is capable of many more ratios, but two more pins of the IC must be switched. (In the 23-channel version, these two were connected to B+ and ground.) That makes eight logic control points.

Also, the switching logic IC's (U102 and U103) have been eliminated. The channel switch has been changed to include the extra switch contacts.

Most of the CB radio manufacturers include in the service manuals the programming tables for the PLL's, so you don't have to become a mathematician, when you need the information during troubleshooting.

Chart 1 lists just a few representative figures for the 40-channel Johnson PLL.

Another advantage of the digital programming is that it is compatible with digital readout circuits. LED channel numbers can be added at only moderate extra cost. This is a valuable feature; a dial with 40 numbers on it would hardly be readable; while the digital numbers can be read at a glance.

Comments

In future articles, we'll present some detailed troubleshooting procedures for PLL's. For now, here is this one tip: determine by tests and symptoms whether wrong frequencies are caused by a programming defect, or from a malfunction in one or the other of the oscillators. □

Reports from the test lab

By Carl Babcoke

Each report about an item of electronic test equipment is based on examination and operation of the device in the ELECTRONIC SERVICING laboratory. Personal observations about the performance, and details of new and useful features are spotlighted, along with tips about using the equipment for best results.

VIZ products probably seem familiar to you, although the name might not be. For many years, VIZ designed and manufactured test equipment that was marketed by RCA. Last December, VIZ also obtained the distribution rights for the entire line. Other items have been added since then. These are the reasons why the instruction books (and even a few of the instruments) have the name "RCA" on them.

VIZ Model WD-750A Digital VoltOhmyst

This new digital multimeter (Figure 1) seems to be a worthy successor to the famous VoltOhmyst VTVM.

Here are some of the basic specs and features:

- automatic polarity indication for DC volts and current;
- automatic zeroing for all functions;
- 3½ digits with bright 0.45-inch red LED's;
- the automatic overrange causes the digits to flash rapidly in a random reading;
- an analog meter, with an uncalibrated sensitivity control, gives conventional swings of the pointer for peaking and nulling readings;
- all ranges and functions are selected by push-buttons;
- one pushbutton selects either low-voltage or high-voltage for resistance readings;
- each range button positions the decimal;
- the AC and DC volts, AC and DC current, and resistance functions have five ranges. In addition, a separate 20-megohm button is provided; and
- provisions are made for internal Ni-Cad batteries, if desired.

The readout conforms to that of most 3½-digit meters. The highest reading is 1999. Above this figure, overrange occurs. For example, the 2-volt range reads up to 1.999 volts, but any increase of voltage does not produce 2.000 volts; overrange is triggered instead. It might be explained as a 1000 readout with a 100% overrange (less one count).

DC volts

Five DC-voltage ranges are provided: 0.2 volt (200



Fig. 1 The VIZ Model WD-750A Digital VoltOhmyst has the features most needed for TV and electronic servicing, including high accuracy of readings, auxiliary analog meter, low-power ohms, plus extra voltage and resistance ranges.

millivolts) and 2, 20, 200, and 1200 volts. The positive or negative polarity sign is displayed automatically. It's not necessary to reverse the test probes. Tests showed that the readings changed by no more than one digit, when the probes were reversed, thus forcing a change to the other polarity. That's good performance; not all analog meters can pass this test.

Accuracy of the DC voltage ranges is 0.1% of reading ± 1 digit, and the input resistance is 10 megohms. Several test readings were almost identical to those of another brand of meter having similar accuracy ratings.

AC volts

Ranges of RMS AC voltage are the same as those for DC, and the input resistance also is 10 megohms. Typically, the accuracy of any meter is less for AC than for DC. The specs show $\pm 0.75\% \pm 2$ digits between 45 Hz and 4 KHz, and $\pm 2.5\% \pm 2$ digits between 4 KHz and 10 KHz. I believe the Model WD-750A exceeds that frequency accuracy.

These ratings bring up one characteristic of many digital meters that usually is buried inside many figures: frequency response. The desirable 10-megohm input resistance often costs two trade-offs. One is the loss of peak-to-peak readings (I don't know of any digital meter that offers such a calibration), and the other is the possibility of narrow-band frequency response. (One meter of another brand rolled off drastically above 4 KHz.)

I am happy to report that the WD-750A meter has excellent frequency response; as good as any similar meter I have checked. The variation in the usual hi-fi audio range between 20 Hz and 20,000 Hz was less than 1%; and, even at 100 KHz, the reading was only about -8%.

Think about that for practical audio measurements. One dB is about 11%, and few specs for hi-fi equipment demand any higher accuracy than about 0.2 dB. That's about 2%. Now, look at the previous paragraph again. For all except the most precise audio frequency-response or voltage measurements,

continued on page 54



Fig. 2 This photo shows the unretouched 0.45-inch LED display, and the pushbutton operated switches, including those for the separate 20-megohm resistance range, the "LP" ohmmeter voltage, and the low-range millivolt, microampere, and 200-ohm functions. (This instrument has the RCA name.)



Fig. 3 The small "analog ref. set" knob should be adjusted to give a useful reading on the "analog reference" meter, for those times when you want a pointer swing, of no particular value except to show maximum and minimum, for peaking and nulling operations.



Fig. 4 The VIZ Model WA-504B/44D Audio Generator has a Weinbridge solid-state oscillator to supply the low-distortion sine waves, and a Schmitt trigger which reshapes the sine waves into square waves.


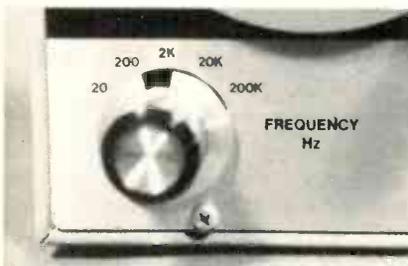


Fig. 5 Limits of each range are indicated by a slit in the knob which shows a black bar between the low and high frequencies.

Fig. 6 Waveforms of the WA-504B/44D are very good. The top waveform of (A) shows 20-Hz square waves; and below it are the 200-KHz square waves, which have slightly rounded corners and slower rise and fall times. Over the audio range, the square waves are perfect. In picture (B), the top waveform shows 20-Hz sine waves, and the bottom trace has 200-KHz sine waves. At 1,000 Hz, the sine waves had only 0.22% total harmonic distortion.

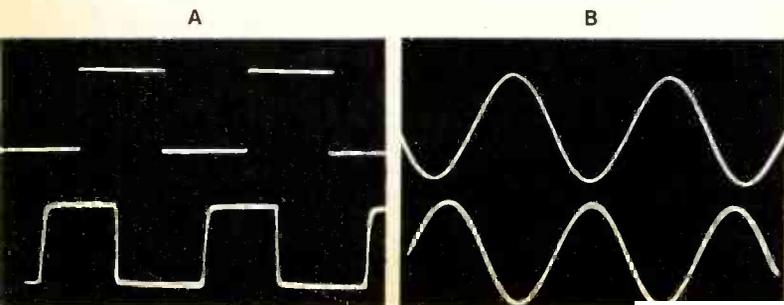

Test Lab *continued from page 53*

the readout can be taken as accurate, without any correction factor!

DC current

The DC current ranges are the same as those for DC volts, except they are expressed in amperes, instead of volts. Accuracy is rated at 0.3% of reading ± 1 digit, voltage drop across the meter is 200 millivolts, and a 2-ampere fuse gives overload protection.

AC current

Ratings for AC current readings are similar to those for DC, except the basic accuracy is $\pm 1\%$ ± 2 digits, plus some derating for high frequencies.

Resistance readings

Four of the resistance ranges are direct-reading in thousands of ohms. In addition, the 200-ohms range reads in ohms up to 199.9 ohms, and a separate pushbutton allows readings up to 20 megohms (actually 19.99 megohms).

Another excellent feature is the "LP" button which allows a choice of "high-power" or "low-power" operation (see Figure 2). When you **want** to read the resistances of diodes or transistors, select the high-power mode. At the high end of each range, about 2 volts is applied to the test leads. Near the low end, about 0.1 volt is applied. This is slightly more than that from VTVM's. With infinite resistance across the test leads, the voltage measured about 11 volts.

When you are measuring circuit resistances, and **don't want** the transistor conduction to give erroneous readings, select the low-power mode. Although the open-circuit voltage also is about 11 volts, the highest resistance not causing overrange produces about 0.1 volt across the test leads, and 0.006 volts near the low end of each range.

Only about 1 digit difference of reading was noticed when changing from low-power to high-power. The "hot" test lead is the positive one.

Analog meter

To the left of the digital display is the "analog reference" meter, which gives a conventional reading on the edge-wise scale that has lines for reference, but is marked only "min" and "max", without any calibration numbers. Adjustment of a small knob (without markings except "analog ref. set", as shown in Figure 3) determines how high or low the meter pointer moves.

The analog meter is very handy when you only



Fig. 7 An audio generator usually is thought of in connection with frequency response curves and distortion measurements. But, there are many more uses, such as the one shown here, where an adjustable tone is fed to an amplifier and speaker system to check for buzzes and rattles.



Fig. 8 Another good test, that's probably not done often enough, is to identify an unknown frequency by displaying a Lissajous figure on a scope. Connect the unknown signal to the scope's vertical amplifier, and the output of the audio generator to the external horizontal input. Adjust the gain controls to give approximately equal height and width. Then, adjust the generator frequency until some variation of a circle spins slower, and finally stops. (When the frequency is high, it's difficult to stop the rotation completely. In those cases, slow it enough that you can be certain it is a circle.) **The frequency of the unknown is the same as the generator frequency.** The waveform was made by a signal from a solid-state vertical sweep and a sine wave from the VIZ generator.

want to know minimum or maximum voltage points during certain adjustments, and don't need precise readings. This eliminates the minor irritation of a digital display that flashes when a reading varies.

VIZ Model WA-504B/44D Audio Generator

Four decades ranges supply low-distortion sine waves or fast-rise-time square waves from 20 Hz to 200 KHz. The compact generator (Figure 4) has a large metal tuning dial with clear calibrations. For fast adjustments of frequency, the center knob can be turned, giving direct drive. Or, the smaller knob can function as a vernier, when accurate or critical adjustments are needed.

An unusual way of showing the tuning limits of each range is supplied by the frequency selector knob (Figure 5). A cut-out in the rim of the knob exposes part of a black area on the panel, showing a black rectangle between the low and high frequencies of the range in use. In the picture, the second range (from 200 Hz to 2 KHz) is in use. This range with other machines might be marked "X10", or 10 times the dial calibration.

Figure 6 shows waveforms of the lowest and highest sine and square waves produced by the generator. Total-harmonic distortion of sinewaves measured 0.22% at 1,000 Hz. Only the most expensive generators have lower distortion.

Two knobs determine the output level. The top one is a variable control, which should be turned to maximum, when exact calibration of the other is desired. The lower attenuator is a four-position switch giving 0.01, 0.1, 1, or 10 volts peak-to-peak.

The circuit provides a constant 600-ohms impedance at all attenuator settings. This unit checked slightly above 11 volts PP, without any external load (the waveforms do not change with or without a load).

No DC appears at the output banana jacks (it does with some square-wave sources), because a coupling capacitor is placed before the attenuator.


Do not connect the generator to a circuit that has DC voltage, unless you first add an external capacitor at the output of the jack. This is to avoid damage to the attenuator.

The operating manual shows and illustrates many uses for the audio generator in traditional audio applications (such as the one of Figure 7, where the generator is helping to find rattles in a guitar

continued on page 56

VIBRA-JET®

URNS TUN-O-WASH INTO A

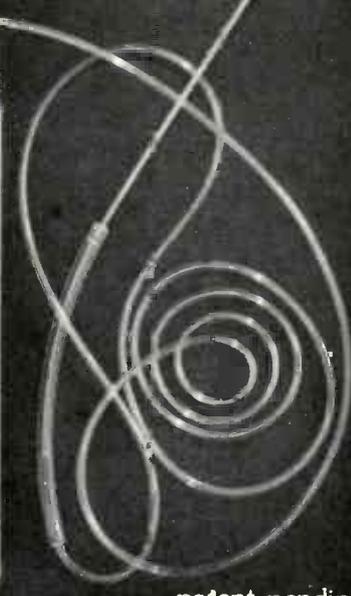

patent pending

PULSATING... VIBRATING... "CLEANING MACHINE"

You have never seen anything like Vibra-Jet, our new patent pending aerosol pulsating device. Just plug it into a can of Tun-O-Wash and you get strong vibrational solvent impacts that instantly penetrate heavy grease, gunk and baked-on contaminants. Vibra-Jet action even washes away dirt on horizontal surfaces . . . makes Tun-O-Wash more effective, leaving tuner parts and controls "vibrantly clean."

Vibra-Jet is made of strong durable polyurethane construction. Works in all positions and comes complete with 26 in. hose and 12 in. probe for hard-to-reach parts.

FREE! FREE! FREE!

FOR A LIMITED TIME ONLY, Vibra-Jet will be offered free with the purchase of 2 cans of Tun-O-Wash or Super Tun-O-Wash. Pick up our "Cleaning Machine" . . . it will be the best time saving investment you've ever made.

Available at participating Chemtronics distributors.



CHEMTRONICS INCORPORATED
95 HOFFMAN AVE., HAUPPAUGE, N.Y. 11787 • (516) 582-3322

Our business is improving yours!

For More Details Circle (27) on Reply Card

Test Lab

continued from page 55

amplifier/speaker). However, the generator also is useful in television servicing for finding and measuring the approximate frequency of vertical and horizontal sweep by the display of Lissajous figures (Figure 8).

Comments

The VIZ WD-750A Digital VoltOhmyst performed all of the usual digital functions very well. In addition, I especially liked the analog meter, the choice of ohms voltages, and the added very-low and very-high ohms ranges.

However, another thing that "sold" me on the equipment was the excellent way it passed a little test I made up for digital DC voltmeters. You see, some digital meters give high accuracy when the DC voltage under test is steady and pure DC. But, when used with DC having high ripple or pulses, the reading can be all wrong (one model had a 40% error). So, I try them using two kinds of DC voltage. One source is half-wave unfiltered DC from a rectifier. The other is taken from a vertical-output transistor. The VIZ meter gave very accurate readings from both of these difficult sources.

The operating manuals for the digital meter and for the audio generator contained a wealth of information about the instruments, and how to use them properly in service work.



GO DIGITAL, GO DANAMETER®

(The New VOM For Today's Needs.)

- 0.25% Accuracy
- Full Overload Protection
- Really Drop-Proof
- Full One Year Battery Life

DANA®

Dana Laboratories, Inc.

2401 Campus Dr, Irvine, Ca 92715, (714) 833-1234

For More Details Circle (28) on Reply Card

photofactbulletin

| | |
|--|--------|
| JCPenney 689-4907/-4919, 4907, 4919 | 1634-1 |
| PANASONIC Chassis NMX-G8A | 1636-1 |
| QUASAR Chassis 16TS-/19TS-485 | 1636-2 |
| RCA Chassis CTC81C/D/E/F/H/J/P/R/T/U/W/AA, CRK24A/C,CTP23A | 1615-2 |
| SANYO PC-52N00 | 1638-1 |
| SEARS 564.50140600, 564.50750600 | 1635-2 |
| SONY Chassis SCC-63D-E | 1625-2 |
| TRUETONE SCJ4709A-77 | 1640-1 |
| ZENITH Chassis 23HC45 | 1637-2 |

bookreview

Solid State Electronics

Authors: Frank P. Tedeschi and Margaret R. Taber

Publisher: Van Nostrand Reinhold (A Division of Litton Educational Publishing, Inc.), 450 West 33rd Street, New York, New York 10001

Size: 202 pages plus index

Price: \$8.95

The authors have compiled fundamental semiconductor and electronic principles into this introductory book to reflect the current state of the art in electronics technology. All information adheres to the IEEE Standard No. 260, Symbols for Units. The book sets out to provide a more comprehensive working knowledge of actual electronic components in practical circuits. Eleven self-contained sections concentrate on specific semiconductor components. Numerous example problems, laboratory experiments, and illustrative aids such as graphs, formulas and actual wiring circuits help bridge the gap between theory and practice.

ACA

**Chroma
POWER**
TV and FM ANTENNAS
AND ELECTRONICS

**ANTENNAS
FIELD-ENGINEERED
and TESTED
in your area
FOR YOUR AREA**

CALL or WRITE:

ACA, P. O. Box 865,
Burlington, IA 52601
Phone: 319-753-1625

For More Details Circle (51) on Reply Card

**SERIOUS ABOUT
YOUR FUTURE IN HOME
ELECTRONIC SERVICE?**



The Sign of
Professional
Service

...a not for profit association championing independents' right to compete, and delivering valuable benefits continuously since 1950.

NATESA offers low cost group insurance, discounts on everything from eyeglasses to motor vehicles, individual consultation on particular problems, representation to government and industry at all levels and a place to unite to protect each individual member with the strength of all.

Send this ad with your card or letterhead to:

NATESA, Dept. ES
5908 S. Troy St.
Chicago, Il. 60629

- Membership check \$60.00 enclosed, please send
- a free Practical Business Manual. OR
- a free Service Contract Cookbook.

test equipment report

These features supplied by the manufacturers are listed at no-charge to them as a service to our readers. If you want factory bulletins, circle the corresponding number on the Reply Card and mail it to us.

RF Generator

Hickok has introduced a general-purpose RF signal generator, having special features for CB radios. Model 256 has four bands for variable tuning of any frequencies from 100 KHz to 16 MHz. These cover the IF needs for AM, FM, and CB radios, plus other applications.

The fifth band is calibrated in CB channels, and gives expanded tuning from Channel 1 to Channel 40.

An internal 1 KHz oscillator provides modulation which is variable



from 0% to 100%, with calibration at 30%. Or, modulation can be produced from an external source.

The RF attenuator has 20-dB steps plus a 20-dB variable control.

Perhaps the most important feature for precision CB work is the extra signal-output jack for feeding a frequency counter. The level is not affected by the attenuator setting, so the accuracy can be as good as the counter that's used.

Model 256 sells for \$199 to technicians or repair shops.

For More Details Circle (38) on Reply Card

Dry Dummy Load

Coaxial's Model 4260 dry, coaxial RF load contains no oil, so it can be operated at full rating in any position without any messy leaks. Rated at 50-ohms impedance and a maximum average power of 200 watts, the Model 4260 is a suitable dummy load during transmitter testing without RF radiation at frequencies from DC to 512 MHz.

For More Details Circle (39) on Reply Card

ONE RIG DOES IT ALL!



\$229.95

PJS-298
C.R.T. Included

33KV

TUBE AND SOLID STATE

33KV Leaded Glass CRT • 40KV Meter
Built-In Speaker • Obsolete-Proof

The PJS-298 Universal Test Rig for tube and Solid State TVs designed for servicing high voltage chassis. Built-in speaker for convenient audio checking, 40KV-50Ua sensitivity meter for convenient audio checking, 40KV-50Ua sensitivity meter constant monitoring of the anode voltage. Up-dating is accomplished by means of plug-in modules. (Extension cables included).

TeleMatic

2849 Fulton St.,
Brooklyn, N.Y. 11207

Please send me more information.

NAME _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

SOLD THROUGH DISTRIBUTORS ONLY

For More Details Circle (29) on Reply Card

PUT YOUR FINGER ON THE TRUTH

It's the one and only flat-rate increment system that gives you the great feeling of pricing every job right. A system that treats both customer and shop owner fairly. Fast finger-tabs in both editions: **6x9 Hard Cover**, steel ring-bound - \$19.95 ea. post pd.

Or The Satellite Edition for pocket sized convenience - \$16.95 ea. post pd.

New
**Computerized
Parts Pricing**
manual lists
over 3,500
most-used
parts - \$75
initial set-up
plus \$10
per copy.



tv & radio
**tech's guide
to pricing**

P.O. Box 5234
Lincoln, NE 68505

Nebr. residents
add sales tax

sperry tech inc. (No. editions)

My check enclosed _____

BankAmericard _____ Exp. _____

Master Charge _____ Exp. _____

Name _____

Co. _____

Address _____

City _____

State _____ Zip _____

For More Details Circle (30) on Reply Card 57


CARTOON CORNER



"Next time you need car-radio service, please call my competitor."



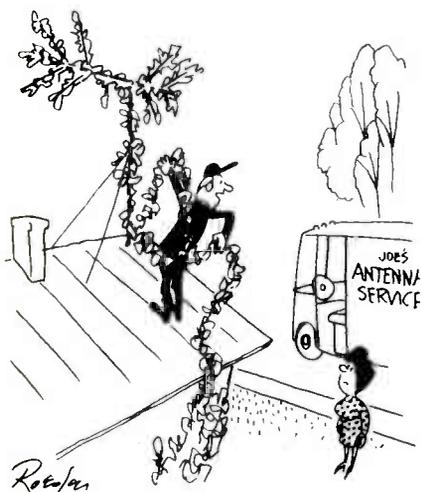"Your TV has conked out, Mr. Smith? Great! I'll be right there."



"Better keep that green thumb of yours under control!"

productreport

These features supplied by the manufacturers are listed at no-charge to them as a service to our readers. If you want factory bulletins, circle the corresponding number on the Reply Card and mail it to us.

Spray-Thru Caps

A new convenience for TV technicians is available in the "spray-thru" caps on **Chemtronics** aerosols. It has been said this is the first time non-removable caps of this type have been used in the electronics industry. Misplaced caps and accidental sprays are eliminated with spray-thru caps. Also, the extension tube can be left



permanently in place, reducing any risk of loss.

For More Details Circle (40) on Reply Card

CB Converter

Sparkomatic has introduced Model CB-11 CB converter that is connected between a standard auto antenna and any AM or AM/FM radio for listening to any of the 40 CB channels. Some of the features include: an illuminated channel-selector knob; a switch to select either radio or CB reception; a noise silencer; a fine-tuning control, and a red LED that shows when the CB converter is on.


The converter retails for approximately \$39.95.



For More Details Circle (41) on Reply Card

Tool Kit

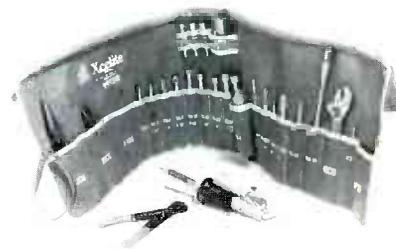The 99SMW service kit by **Weller-Xcelite** features the addition of a wire stripper/cutter and a 25-watt soldering iron. The tools fit into a roll-up, plastic-coated canvas case. The kit also includes long-nose and diagonal-cutting pliers, adjustable wrench, an assortment of regular and stubby screwdrivers and nut drivers, plus both regular and stubby handles, extension blade, and reamer.



For More Details Circle (42) on Reply Card

Shielded Power Wiring

Gold Line is offering a "Noise-Filtering Hookup Harness" Number 1106 which is said to reduce the noise picked up by the power wiring of CB or communications radios. Heavy-duty shielded coaxial cable with connectors, and an inductive filter are supplied to replace the unshielded power wires commonly used. An in-line fuse offers additional protection against shorts or overloads.

For More Details Circle (43) on Reply Card

DC Adapter Charger

Dynamic Instrument's "Auto-Vert" DC-to-DC adapter/chargers plug into a cigarette lighter, and reduce the 12 volts DC to other DC voltages as low as 3 volts, as required for lower-voltage devices. It also can be used to charge rechargeable-type batteries, such as lead acid or Ni-Cad.

Four interchangeable plug tips, called "Quadraplug", allows matching to various polarities and receptacles.

For More Details Circle (44) on Reply Card

audio systems report

These features supplied by the manufacturers are listed at no-charge to them as a service to our readers. If you want factory bulletins, circle the corresponding number on the Reply Card and mail it to us.

CB/Public Address Speaker

A CB/public address speaker that mounts in most places is available from **Audiovox**. Model CBS-20 is a



weatherproof horn speaker, having a horn length of 4½ inches, and a bell diameter of 3½ inches X 3 inches.

The speaker has a frequency range of 800 Hz to 6000 Hz, and a nominal input power rating of 5 watts.

A 12-foot cord with a 1/8-inch plug is furnished with the speaker, which lists for \$11.95.

For More Details Circle (47) on Reply Card

Auto Speaker

Model KK-6069 "Kriket" auto speaker by **Acoustic Fiber Sound** is



designed for high-volume operation without damage. The 8-ohm speaker handles up to 30 watts, with an extended frequency response said to be from 35 Hz to 20 KHz from a dual-cone speaker with air-suspension and front-loading designs. Suggested retail price is \$44.95 each.

For More Details Circle (48) on Reply Card

need belts?



Standard and special belts and tires ready for immediate shipment — fit over 3,000 new and obsolete makes of tape recorders, projectors, dictating machines, video recorders, and turntables. Simplified cross reference system makes ordering easy with **one day service** on most items. Drive tires, wheels, phono idlers also listed. Call or write for **free catalog**. DEALER INQUIRIES INVITED.

PROJECTOR-RECORDER BELT CORP.

319 Whitewater St., Whitewater, WI 53190 — (414) 473-2151

For More Details Circle (34) on Reply Card

catalogs literature

Circle appropriate number on Reader Service Card.

87. Mountain West—offers a 64-page catalog featuring over 900 intrusion and fire-alarm products, ranging from simple kits to the latest ultrasonic, radar, and infrared intrusion detectors. Product categories include burglar systems, fire systems, fire and burglar detectors, control instruments, telephone dialers, and lock specialties, among others. Products are described in detail regarding application, principle of operation and specifications, with connection diagrams and pictures.

93. Fordham—has released a discount mail-order catalog catering to radio and TV servicemen, electronic technicians, CB users, and hobbyists. 148 pages list test equipment, CB equipment, tools, tubes, antennas, speakers and microphones, phonograph cartridges and needles,

and other items. Particular emphasis is devoted to test equipment.

94. Hewlett-Packard—has a 32-page publication which provides background on such subjects as thermal printing, testing, servicing, C-MOS, P-MOS, and N-MOS circuits and RPN language. A catalog section provides background on each of the hand-held and printing calculators, including an explanation of functions, physical specifications and accessories. The publication also includes a question and answer section and a collection of unusual case histories.

96. Lansdale Transistor and Electronics—offers 16 pages about their line of germanium power transistors with single and quantity prices. A selector guide is included for reference and selection of power alloy transistors with 3A to 60A ratings, diffused-base power transistors with 10A to 60A ratings, and low-current transistors for audio amplifier and switching applications. A cross reference guide also is provided.

NATIONAL ELECTRONIC

NESDA

SERVICE DEALERS ASSOCIATION INC

1715 EXPO LANE
INDIANAPOLIS, INDIANA 46224
PHONE (317) 241-8160

WE'RE GROWING!
To better represent
YOU

The successful service
business operator.

- * Over 2000 firms belong
- * 35 State Affiliates
- * 162 Local Associations

YOU CAN JOIN

And learn how to make
money and work less
hours.

Write today for a
membership application
and more information.

The MARKETPLACE

Advertising rates in the Classified Section are 35 cents per word, each insertion, and must be accompanied by cash to insure publication.

Each initial or abbreviation counts a full word.

Minimum classified charge \$3.00.

For ads on which replies are sent to us for forwarding (blind ads), there is an additional charge of \$3.00 per insertion to cover department number, processing of replies, and mailing costs.

Classified columns are not open to advertising of any products regularly produced by manufacturers unless used and no longer owned by the manufacturer or a distributor.

BUSINESS OPPORTUNITY

TIRED OF CUSTOMER ABUSE? Expand into lucrative patented MATV Preliminaries \$3.00. Box 809, Boynton Beach, FL 33435 10-76-61

T.V. SHOP for sale. RCA authorized Service Center. Repairs on all brands. New and used T.V. sales and rentals. Sixteen years in same location. Owner retiring. Arnold's T.V., 3533 Adams, San Diego, Ca. 92116. 3-77-1f

FOR SALE

TV & RADIO TUBES 36c EA!! Free color catalog. Cornell, 4221 University, San Diego, California 92105. 8-76-1f

BUILD ELECTRONIC DEVICES in your home. Get started in your spare time. Big profits. Experience not necessary. Ask for free literature telling how. Electronic Development Lab, Box 1535, Pinellas Park, Fla. 33565. 3-77-1f

RIDER'S MANUALS 15 unabridged. 7 through 9, 11 through 20, 22 and 23. Will take best offer. Central Electric Service, 712 Cherry Hill Drive, Staunton, Virginia 24401. 3-77-1f

SELLING SUPREME PUBLICATIONS' manuals to 50% discount. Beitman, 1760 Balsam, Highland Park, IL. 60035. 3-77-1f

RADAR DETECTORS are Big Business! Dealers can buy the LONG RANGER RADAR RECEIVER with light & buzzer & cigarette lighter connector for \$62.50 each. Retail for \$89.95 to \$99.95. Distributed by Ronkel, Inc., P.O. Box 13151, Arlington, Texas 76013. 3-77-1f

FULLY DEPRECIATED T.V. & C.B. test instruments we no longer need. Write or call for list and prices. Frazier Electronics, 105 Church St., Fredericktown, Missouri 63645. 314-783-5732. 3-77-2f

PICTURE TUBE REBUILDING EQUIPMENT COMPLETE. Duds and accessories included. Easy to operate. Two stage oven for fast production of color or B&W tubes. Cost over \$12,000—will take \$6,000. Hurry, don't let this opportunity pass you by. Pete Karan, 2604 Adams, San Diego, Calif. (714) 298-5501 or (714) 263-1538. 3-77-1f

FOR SALE (CONT.)

REPLACEMENT COLOR YOKES-DEALERS ONLY Zenith 95-2501-2532-2638-2667-S-89633 etc. 14.95. Magnavox 361380-1 18.95. Sylvania, GE etc. 14.95 to 19.95. Request for price list on your Letterhead. David Sims Enterprises, Inc. 665 Jericho Turnpike, Huntington Station, N.Y. 11746 12-76-1f

UNUSUAL SURPLUS AND PARTS Catalog \$1. ETCO Electronics, Dept. E.S., Box 741, Montreal "A" H3C 2V2 7-76-10f

SAMS PHOTOFACTS 1 to 1626. Complete and excellent. Six filing cabinets. Best reasonable offer. C. W. Riley, CET, 715 Angela Dr., Normal, Ill. 61761. 309-452-4593. 3-77-1f

TV REPAIR HINTS. Send make and model. \$3.00. Charles TV, 2033 McGraw Ave., N.Y. 10462. 3-77-2f

HELP WANTED

OUTSIDE SERVICE TECHNICIAN. Paying top wages for best qualified men. Qualifications for position: Total honesty, industrious, ten or more years direct television experience, non-drinker, non-smoker, must be able to work without supervision. Present employees grossing over \$20,000.00. Send resume to American Television Service, 1032 So. State, Orem, Utah 84057. 3-77-4f

EDUCATION-INSTRUCTION

REPAIR TV TUNERS—High Earnings. Complete Course Details, 12 Repair Tricks, Many Plans, Two Lessons, all for \$2. Refundable. Frank Bocek, Box 3236 Enterprise, Redding, Calif. 96001. 8-76-1f



EARN YOUR PROFESSIONAL BACHELOR DEGREE

with 4 or more years of Electronic Business Management, Sales, or Servicing Experience. For FREE Information Write:

EBERT PROFESSIONALS INSTITUTE
Box 1651 Dept. R
Columbia, Missouri 65201

REGIONAL ADVERTISING SALES OFFICES

Indianapolis, Indiana 46280

ROY HENRY

2469 E. 98th St.

Phone: (317) 846-7026

Greenlawn, New York 11740

CHUCK HORNER

P.O. Box 175

Phone: (516) 757-7863

Mountain View, California 94043

DENNIS TRIOLA

2680 Bayshore Frontage Road, Room 102

Phone: (415) 961-0378

London, W.C. 2, England

JOHN ASHCRAFT & CO.

12 Bear Street

Leicester Square

Phone: 930-0525

Badhoevedorp, Holland

JOHN ASHCRAFT & CO.

JOHN J. LUCASSEN, Mgr.

Slooterweg 303

Phone: 2968-6226

Tokyo 1, Japan

INTERNATIONAL MEDIA


REPRESENTATIVES LTD.

Shiba-Kotohiracho, Minatoku

Phone: 502-0656

advertisers' index

| | |
|--|---------------------------|
| American Technology Corp. | 36 |
| Antenna Corporation of America ... | 57 |
| Arrow Fastener Co., Inc. | 34 |
| B & K Div., Dynascan Corp. | 21 |
| Bussmann Mfg. Div., McGraw-Edison. | Cover 4 |
| Castle Electronics | 2 |
| Chemtronics Incorporated | 55 |
| Dana Laboratories, Inc. | 56 |
| Gem City Tuner | 8 |
| General Electric Company, Television Business Division | 9 |
| General Electric Company, Tube Products Div. | 33 |
| Hickok Electrical Instrument Co. ... | 49 |
| ISCET | 37 |
| MTI | 8 |
| Mountain West Alarm Supply Co. | 8 |
| NATESA | 57 |
| NESDA | 59 |
| NonLinear Systems, Inc. | 37 |
| Oelrich Publications | 8 |
| Precision Electronics | 52 |
| Precision Tuner Service | Cover 2, 1 |
| Projector Recorder Belt Co. | 59 |
| RCA Distributor and Special Products ... | 2, 16, 17, 28, 30, 31, 39 |
| Sencore | 3 |
| Sperry Tech, Inc. | 57 |
| Sprague Products Co. | Cover 3 |
| GTE Sylvania-ECG Consumer Renewal | 5 |
| Tektronix, Inc. | 35 |
| TeleMatic | 57 |
| Tuner Service Corp. | 7 |
| Ungar, Division of Eldon Industries | 45 |
| VIZ Manufacturing Co. | 15 |
| Winegard Company | 10, 11 |

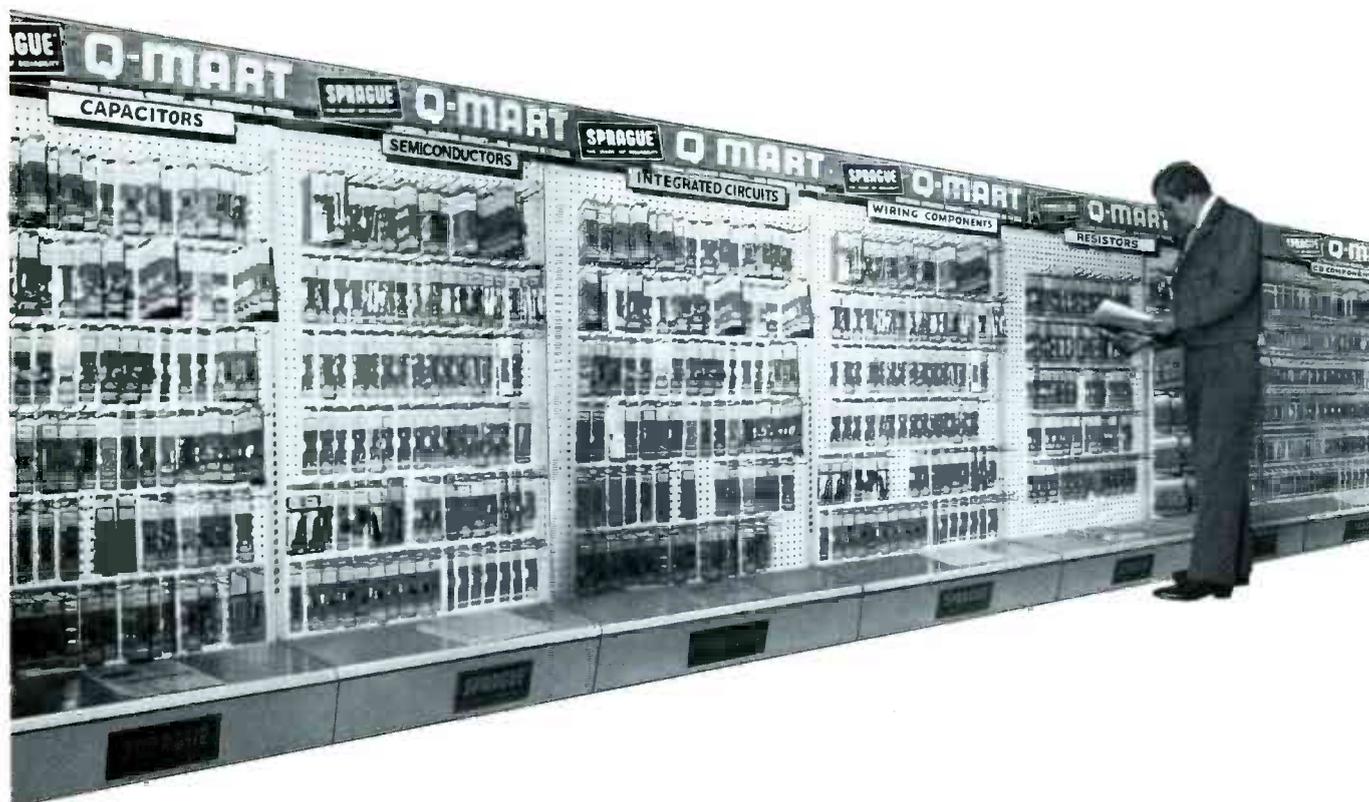

Picture of an astute service technician

Whether you're servicing TV, AM/FM radio, CB transceivers, Hi-Fi equipment, garage-door openers, or other electronic gear, it pays you to go to your nearest Sprague Q-MART distributor for replacement parts.

Sprague Q-Line components are the best, easiest-to-use, quickest-to-locate parts available to the service trade. Hundreds of Sprague Q-MARTS are located throughout the country. They're out there to keep you and your customers happy by letting you spend more time at the bench and less time in those frustrating searches for needed replacements.

On Q-MART displays you'll find the hottest, most-needed capacitors, resistors, filters, transistors, diodes, rectifiers, ICs, quartz

crystals, solid state tubes, semiconductor hardware, LED devices, alpha-numeric displays, switches, lamps, and wiring components such as solderless terminals, specialty connectors, terminal blocks, cable clamps, etc. They're all neatly packaged and marked for easy, time-saving selection.

But the best news is that the Sprague name on every package assures you of high-quality call-back-free components that help build your reputation for dependable service.

Get to know the Sprague Q-MART distributor in your area. If you're not sure who he is, write to us for the location of the Q-MART nearest you. Sprague Products Company, 509 Marshall St., North Adams, Mass. 01247.

71 Marshall St., North Adams, Mass. 01247.

MEMBER



AMERICA'S LARGEST MANUFACTURER OF ELECTRONIC COMPONENTS

SPRAGUE®


THE MARK OF RELIABILITY

BUSS® Fuses

FOR QUALITY-RELIABILITY


For anything you need in protecting electronic circuits and devices —

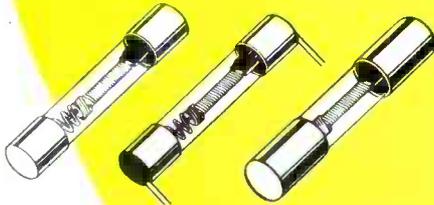FUSETRON®
dual-element — time-delay fuses




Avoid nuisance opening, yet get full short-circuit protection. Available from 1/100 amp. to 40. Size ¼ x 1¼ in. and 9/32 x 1¼ in.

TRON® rectifier fuses

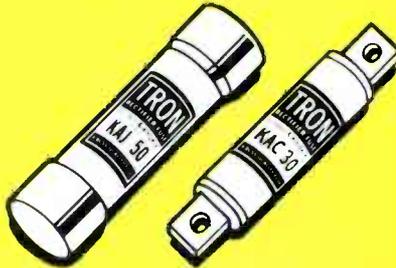

Provide extremely fast opening and high degree of restriction of let-thru current to protect Solid State Devices. Ampere rating ½ to 1000 in voltages up to 1500.

BUSS GLASS TUBE FUSES
"quick-acting"

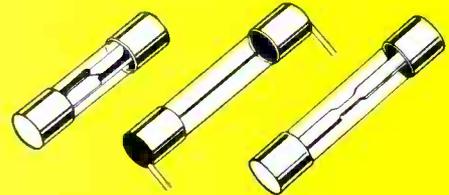


Provide high speed action to protect delicate instruments and apparatus. Available from 1/500 to 30 amp. Size ¼ x 1 in. and ¼ x 1¼ in.

BUSS
Signal-Indicating
Alarm-Activating
FUSES




Available with time-delay or quick-acting characteristics. Available from 1/10 to 30 amp. Size ¼ x 1¼ in. and 13/32 x 1½ in.


BUSS Fuses
for
TELEPHONE
COMMUNICATIONS
Similar equipment

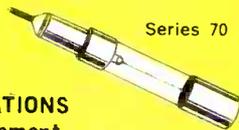

Series 70

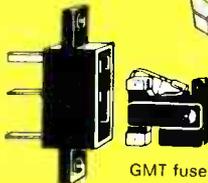

GMT fuse

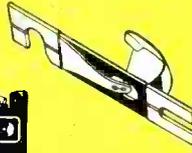

Grasshopper



TRON® Sub-Miniature Pigtail Fuses

Size only .145 x .300 in. Glass tube permits visual inspection. Hermetically sealed. Available from 1/200 to 15 amp.

BUSS
Sub-Miniature
GMW fuse



and HWA fuseholder.

Full size .270 x .250 in. with window to check fuse element. Available 1/200 to 5 amp.

BUSS SNAP-LOCK
FUSEHOLDER

Rear panel mount fuseholder for ¼ x 1¼ in. fuses. Snaps into place. Specify HTA-00 for space saver type. HLD-00 to take visual indicating fuses. HKP-00 for standard fuseholder. HJM-00 to take ¼ x 1 in. fuses.

HLT holder



HKP
panel
mounted
fuseholder
for ¼ x 1¼ in.
fuses.



HKA
lamp
indicating,
signal-activating
fuseholder.

BUSS FUSES and
FUSEHOLDERS
to meet military
specifications.

BLOCKS FOR
BUSS FUSES

All types available for every application. Single pole, multiple pole, small base, laminated base, porcelain base for fuses from ¼ x ¾ in. up. Also signal fuse blocks and special blocks of all types.

FOR THE
PROTECTION OF ALL
ELECTRONIC
CIRCUITS

Write for Bulletin SFB
— See for yourself —



BUSSMANN MANUFACTURING
a McGraw-Edison Company Division
St. Louis, Missouri 63107



For More Details Circle (2) on Reply Card