

Electronic Servicing

A HOWARD W. SAMS PUBLICATION

7-SEGMENT

[YELLOW] PROGRAM ON-OFF SWITCH

[RED] CHANNEL NUMBER SWITCH

[BLUE] TUNING SWITCH

910 kHz CLOCK

910 kHz OSC

3.6 OSC

IC101 CONTROL PROCESSOR

Magnavox Touch-Tune Digital Circuits

20-LOCATION CHANNEL NUMBER AND BAND MEMORY



ON-OFF BUTTON

60 Hz [2 PHASE]

REMOTE TRANSMITTER




TONE CONTROL

TO TV

SHARPNESS CONTROL

TO TV

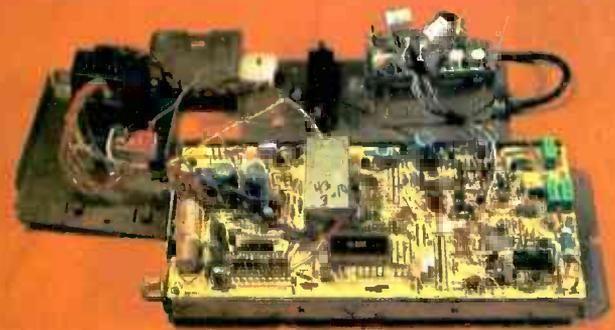

POTOMER; BRIGHTNESS; CONTRAST; COLOR; INT.

PRESET; BRIGHTNESS; CONTRAST

580 05 1877 PA 19111

SACSO129052PE01A
SANUEL SACHS
809 BERGEN ST
PHILADELPHIA

Wrong CRT Voltages Inductive Transducers Five Easy Steps

DO MORE BUSINESS... MAKE SERVICING MORE PROFITABLE



with Sprague Replacement Component Assortments

Whatever you're servicing . . . CB radios, TV sets, AM/FM radios, Hi-Fi equipment, or other electronic gear . . . you've won half the battle when you've got ready access to the right replacement components. Sprague assortments can save you a lot of aggravation.

Sprague component assortments include only the most-popular, most-frequently-used parts you use in everyday service work . . . and they come pre-filled in durable 6-drawer or 9-drawer cabinets at no extra cost to you!

With 43 different assortments to choose from, there's one sized and priced just right for you. Select from assortments of capacitors, trimmers, resistors, transistors, diodes, rectifiers, ICs, LEDs, and switches.

For complete information, get descriptive brochure M-946A (if you service CB radios ask for M-994A as well) from your nearest Sprague distributor. Or, write to Sprague Products Co., 71 Marshall St., North Adams, Mass. 01247.

MEMBER



AMERICA'S LARGEST MANUFACTURER OF ELECTRONIC COMPONENTS

For More Details Circle (2) on Reply Card

SPRAGUE

THE MARK OF RELIABILITY

6S-7117


Electronic Servicing®

CONTENTS

- 18 **Servicing Magnavox Modular Color TV, Part 6**—This is the beginning of "Touch-Tune" coverage, including explanations of the sophisticated digital circuits that control the varactor tuners in the T995 chassis. Learn why two batteries are needed in the memory circuit—*Gill Grieshaber, CET.*
- 25 **All Around Ohm!**—Test your knowledge of electronic terminology with this just-across-word puzzle—*Edmund A. Braun.*
- 26 **Five Easy Steps To Successful TV Repair**—In a spirit of fun, the author presents "suggestions" for improving your business—*Terry L. Turner.*
- 28 **Picture-Tube Voltages...the cause of many problems**—Many basic signals and DC voltages are applied to color picture tubes. So defects here can cause a variety of symptoms, some of them very confusing—*Paul Shih.*
- 36 **The Basics Of Industrial Electronics, Part 5**—The unique principles of inductance transducers are analyzed. Digital basics begin next month—*J. A. "Sam" Wilson, CET.*
- 46 **Reports From The Test Lab**—A model TRC-82 TV pushbutton remote control system by Jerrold received typical in-home operation, and it performed very well—*Carl Babcoke, CET.*



page 18

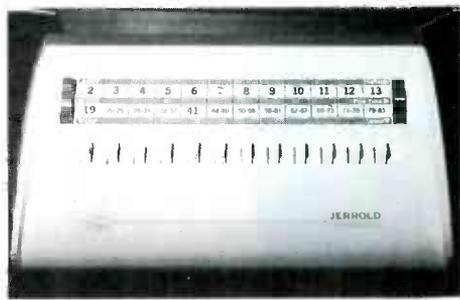

page 46

About the cover—Many details of the Magnavox "Touch-Tune" system are shown in these pictures. No solid-state components are in the pushbutton panel assembly. Memory circuits in the control chassis "remember" the digital codes for 20 VHF and UHF TV channels.

DEPARTMENTS

- | | |
|-------------------------|-----------------------|
| 6 Electronic Scanner | 48 Test Equipment |
| 11 Symcure | 49 Antenna Systems |
| 12 Troubleshooting Tips | 50 New Products |
| 15 Reader's Exchange | 51 The Marketplace |
| 45 Photofact Bulletin | 52 Advertisers' Index |
| 45 Book Review | |

Second class postage paid at Shawnee Mission, Kansas and additional mailing offices. Published monthly at 9221 Quivira Road, Overland Park, Kansas 66212 by Intertec Publishing Corp., 9221 Quivira Road, Overland Park, Kansas 66212. Send Form 3579 to 9221 Quivira Road, P.O. Box 12901, Overland Park, Kansas 66212.

©Copyright, 1977, Howard W. Sams & Co., Inc. All rights reserved. Material may not be reproduced or photocopied in any form without written permission of publisher.

New B&K-PRECISION 3½ digit portable DMM



Model 2800

**Industrial Quality
at \$99.95!**

- 3½ digit bright LED display
- Completely portable—use it anywhere!
- Auto-zeroing on all 22 ranges
- Fully overload protected on all ranges
- Typical DC accuracy is ±1%
- 100% overrange reading
- High-/Low-power ohms for in-circuit resistance measurements or semiconductor checks
- 1mV, 1µA, 0.1 ohm resolution
- Full range of optional accessories available

Compare features, performance and price...you'll choose the new 2800 from the "cost-effective" instrument specialists at B&K-PRECISION.

Available for immediate delivery at your nearest B&K-PRECISION distributor.



DYNASCAN CORPORATION

6460 West Cortland Avenue
Chicago, Illinois 60635 • 312/889-9087

In Canada: Atlas Electronics, Ontario
Int'l. Sls: Empire Exp., 270 Newtown Rd,
Plainville, LI, NY 11803

For More Details Circle (4) on Reply Card


MEET OUR family of dip clips



Model 3916
14/16 Pin

Model 4124
24 Pin

Model 4140
40 Pin

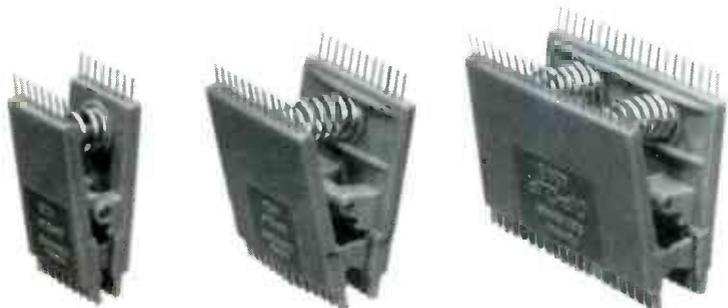

Model 4236
14/16 Pin
For Ultra Dense
Packaging

Model 4324
24 Pin
For Ultra Dense
Packaging

Model 4340
40 Pin
For Ultra Dense
Packaging

Count on Pomona Electronics to keep pace with the industry's trend toward higher density Dual In-Line packaging. We introduced the first Model 3916 in 1972. Now there are six improved models, including three designed for ultra dense packaging.

DIP CLIPS are designed for hands-free testing of integrated circuit packages. Lower contacts are .050 wide for improved surface contact with I.C. packages. Test contacts are .025 square, and are serrated for improved connection of test clips. Molded barrier between contacts minimizes accidental shorting. Can also be used as insertion and removal tool for DIPs.

Available Through Your Favorite Electronic Parts Distributor

ITT POMONA ELECTRONICS

1500 East Ninth St., Pomona, Calif. 91766
Telephone (714) 623-3463. TWX: 910-581-3822



For More Details Circle (5) on Reply Card

Electronic Servicing

Editorial, advertising and circulation correspondence should be addressed to: 9221 Quivira Road, P.O. Box 12901, Overland Park, Kansas 66212 (a suburb of Kansas City, Missouri), (913) 888-4664.

EDITORIAL

RONALD N. MERRELL, Director
CARL H. BABCOKE, Editor
MICHAEL SCHEIBACH, Associate Editor
DUDLEY ROSE, Art Director
CINDY NELSON, Editorial Assistant
MARY CHRISTOPH, Graphic Designer

EDITORIAL ADVISORY BOARD

LES NELSON, Chairman
Howard W. Sams & Co., Indianapolis
JOE A. GROVES, Technical Consultant
Howard W. Sams & Co., Indianapolis

CIRCULATION

GREG GARRISON, Director
EVELYN ROGERS, Manager



Member, American Business Press
Member, Audit Bureau of Circulations

ADMINISTRATION

GEORGE H. SEFEROVICH, President
MIKE KREITER, Publisher

ADVERTISING SALES

Overland Park, Kansas 66212
(a suburb of Kansas City, Missouri)
Phone: (913) 888-4664

PAT FOX, Production
Regional and Advertising Sales Offices
with Advertising Index

ELECTRONIC SERVICING (with which is combined PF Reporter) is published monthly by Intertec Publishing Corp., 9221 Quivira Road, Overland Park, KS 66212.

ELECTRONIC SERVICING is edited for technicians who repair home-entertainment electronic equipment (such as TV, radio, tape, stereo, and record player), and for industrial technicians who repair defective production-line merchandise, test equipment, or industrial controls in factories.

Subscription Prices: 1 year—\$6.00, 2 years—\$10.00, 3 years—\$13.00, in the U.S.A. and its possessions. All other foreign countries, 1 year—\$7.00, 2 years—\$12.00, 3 years—\$16.00. Single copy 75 cents; back copies \$1. Adjustment necessitated by subscription termination to single copy rate. Allow 6-8 weeks delivery for change of address. Allow 6-8 weeks for new subscriptions.



INTERTEC PUBLISHING CORP.
Subsidiary of HOWARD W. SAMS & CO., INC.

ELECTRONIC SERVICING



We've got the longest running feature on TV.

Our Color Bright 85[®] picture tube warranty is the longest in the industry. We can offer it because we're confident that a Color Bright 85 picture tube will probably last longer than five years.

The warranty is a great selling tool that builds customer confidence in your quality work. Plus, it lets you form a long-term customer relationship with each picture tube you replace.

*Limited warranty, naturally. It does not cover labor for replacing a tube.


The Color Bright 85 picture tube offers economy with the high quality standards you expect from Sylvania. Couple that with the new 5-year warranty* and you'll find the Color Bright 85 is an easy sale. And it can be better for you in the long run.

GTE SYLVANIA

Zenith tuners and sub-assemblies repaired with the latest advancements built-in!

Tuner Replacement

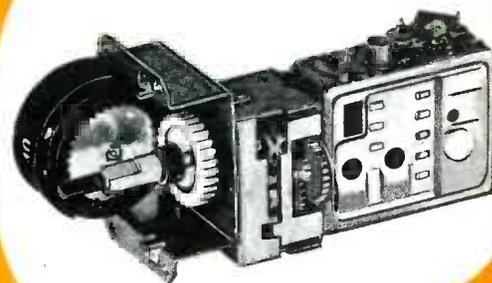Only Zenith
quality replace-
ment compon-
ents used
throughout.
Each tuner
packaged in
shrink-type
film to keep it
factory-fresh
and clean
for use.



No waiting. No turn-around time.

Just bring to your Zenith distributor the Zenith tuner or sub-assembly that needs repair.

You'll walk out with a Zenith factory repaired and reconditioned replacement serviced by the same people who made the original.


Not only will component failure be repaired, but the replacement part will be reconditioned to incorporate the latest factory technical advancements.

Don't risk your reputation when you get all this backed by a limited one-year warranty.


See your Zenith distributor now for Zenith repaired and reconditioned tuners and sub-assemblies!



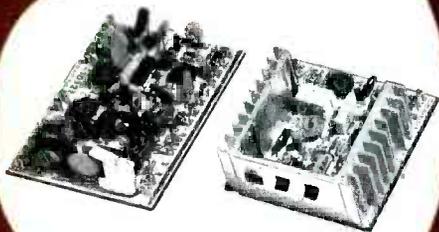I.F. Chassis
Alignments to the factory specifications assure accuracy in replacement.



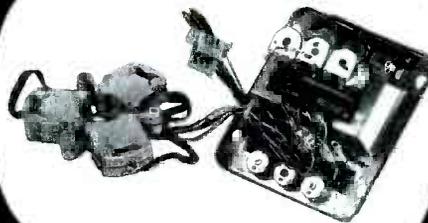Dura Modules®
Repaired not only for component failure but up-dated to any changes which aid in performance.



Convergence Assemblies
Carefully inspected and reconditioned with the exact value components.

ZENITH
®

The quality goes in before the name goes on.®

Zenith Radio Corporation/Service, Parts & Accessories Division/11000 Seymour Avenue/Franklin Park, Illinois 60131

For More Details Circle (6) on Reply Card

electronicscanner

news of the industry

The International Society of Certified Electronics Technicians, the technical arm of NESDA, has moved to 310½ Main Street, Ames, Iowa 50010; (515) 232-4720. The move was necessary because Dick Glass, CET, and most of the Indianapolis staff that administered the CET and other technical programs resigned. Ron Crow will continue as executive director.

The long-term outlook for personal two-way radio equipment is excellent. However, this rapid growth probably will not occur until after a two-year slump in sales of CB radios, which might eliminate more than 25% of the present CB manufacturers. That is the conclusion of a 210-page report entitled, "CB Radio and the Future Portable Telephone," issued by International Resource Development (IRD). The report predicts a merger between the portable telephone market and the declining CB market, resulting in hand-held, vehicle-mounted or wristwatch-type two-way radios for telephone calls or CB use. IRD also projects additional UHF or VHF CB channels and cordless home telephones by 1985.

A pressing need to reduce labor and overhead costs has forced Zenith to transfer much of the module and chassis assembly operations to Mexican and Taiwan plants. This move eventually will cut about 5,600 American workers from the Zenith payroll. Stereo machines will be obtained from foreign suppliers, but the final-assembly of color receivers will be continued in Chicago, Illinois and Springfield, Missouri. The Lansdale, Pennsylvania picture-tube plant (closed since 1974) will be written off the books.

Total sales to U.S. television and radio dealers increased in August and continued to out-pace 1976 on a year-to-date basis. According to the marketing services department of the Electronic Industries Association, radio sales are up 40% and television sales are up 9.6% over last August.

Dealers are worried about the profitability and supplies of RCA's \$1,000 videocassette recorder, according to *Retailing Home Furnishings*. Reports suggest that only 40,000 units will be available this year, and the dealer's markup will range from 20% to 25%.

The California State Electronics Association has asked manufacturers and distributors to stop limiting the number of service shops authorized to provide warranty work. The association says manufacturers are using the current system as economic leverage to obtain warranty work at below cost.

Two direct-to-home satellite receivers using dish antennas of less than a 2-foot diameter were displayed for the first time at the IEEE conference, *Video News* reports. The receivers, developed by Sony and Sumitoma Electric, were said to have excellent performance, including signal-to-noise ratios of about 43 dB. One engineer predicted that such systems might some day be operated in homes, with the dish located in the attic, and the amplifier-converter unit placed near a conventional TV receiver.

continued on page 8

BUSS ELECTRONIC FUSES.

Nearly every type of fuse and fuse holder you need to protect electronic circuits and devices you can get from us, easy. For example, Buss® Semiconductor Fuses; 700 volts, with extremely low I^2t and I_p let-thru values. TRON® Rectifier Fuses, ½ to 1,000 amps, up to 600 volts. Fusetron® dual-element time-delay fuses. Buss quick-acting glass tube fuses. Buss signal-indicating, alarm-activating fuses. TRON sub-miniature pigtail fuses. Buss sub-miniature GMW fuses. Buss telecommunications fuses. Buss military fuses. And Buss fuse holders and fuse blocks. Get your hands on exactly what you want. Write us now. Ask for Buss Bulletin SFB.

SUPPLIED THE ECONOMICAL WAY
THRU DISTRIBUTORS
BUSS® FUSES
THE QUALITY LINE

BUSSMANN MANUFACTURING
a McGraw-Edison Company Division
Earth City, Missouri 63045



**WE MAKE IT EASY
TO GET YOUR HANDS
ON WHAT YOU WANT.**

continued from page 6

A common UHF-VHF antenna will be accepted under two conditions to meet FCC requirements that manufacturers attach a UHF antenna to every receiver marketed with a VHF antenna. The request to install the antenna must be supported by measurement data showing either that the common antenna is comparable to the loop antenna, or, that a built-in splitter circuit is effectively used.

Ninety-four percent of the nation's state police organizations have CB radios for direct communication between citizens and police in emergency situations. The Electronic Industries Association reports that CB radios are installed in 48% of the police vehicles in 34 states. Six states have CB installations in 100% of their state patrol vehicles, while five states are proposing 100% installation in the near future.

In an effort to improve its communications with thousands of boaters in small crafts, the U.S. Coast Guard will begin installing CB radio equipment at its Search and Rescue (SAR) stations. The Coast Guard intends to have CB service available in time for the 1978 recreational boating season.

A "Citation of Outstanding Achievement in Engineering Development" for improving the efficiency of UHF klystron tubes was presented to Varian Associates at the third annual Emmy Award luncheon. The ABC-TV network received an engineering citation for installing and checking circularly polarized antenna systems.

Sony is offering the first pulse-code-modulation (PCM) audio unit for home use. The unit converts a Betamax or U-Matic videotape recorder into a hi-fi audiotape recorder. According to *Retailing Home Furnishings*, Matsushita will offer a similar unit soon, as well as a 1/4-inch PCM tape recorder for professional use.


U.S. Marshals accompanied by FCC agents seized more than \$25,000 worth of illegal CB and amateur radio equipment in Tennessee. The raids uncovered illegal CB linear amplifiers and illegally modified equipment.

Blind persons seeking careers in computer sciences now can be helped by MOUTH, a computer which uses verbal responses rather than computer printouts. MOUTH (Modular Output Unit for Talking to Humans) was developed by James Kutsch, a professor at West Virginia University, and is just one example of new electronic devices designed to assist disabled persons. The *Kansas City Star* reports that among these new devices are: a wheelchair that can stop, move, or change speed by verbal command; a sight switch activated by eye movement; a typewriter keyboard triggered by a tongue switch; and, an all-purpose system that can dial a telephone, change television channels, or turn on the radio by blowing into an air tube or flicking the tongue.

The Federal Communications Commission has been asked to extend the cutoff date for the sale of 23-channel CB radios to March 1, 1978, according to *Electronic News*. The request was made by Jules Steinberg, executive vice president of the National Appliance and Radio-Electronics Dealers Association (NARDA). The current deadline is January 1, 1978.


Fuji-Svea Enterprise now has two toll-free phone numbers for customer service and to expedite shipping. Ohio customers should call (800) 582-1630; all others call (800) 543-1607. The firm specializes in original Japanese semiconductors, FETs, ICs and diodes.

Chassis—RCA CTC81
PHOTOFACT—1615-2

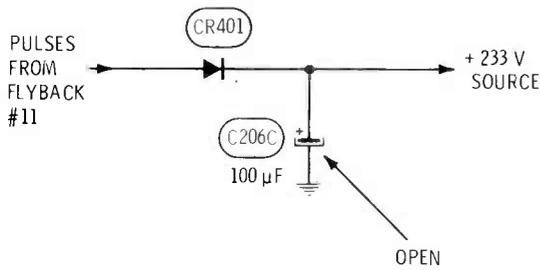


Symptom—No video, and excessive brightness with retrace lines
Cure—Check C206C, and replace it if open or low in value

Chassis—RCA CTC81
PHOTOFACT—1615-2

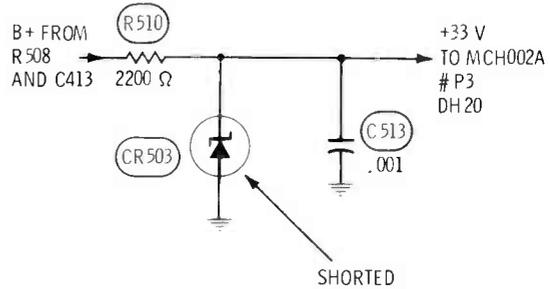


Symptom—No vertical sweep
Cure—Check CR503, and replace it if leaky or shorted

Chassis—RCA CTC81
PHOTOFACT—1615-2

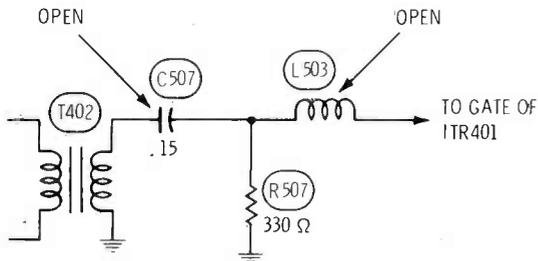


Symptom—Not locked horizontally, has squeal, and perhaps foldover with low HV
Cure—Check C507 and L503, and replace either if open

Chassis—RCA CTC58
PHOTOFACT—1365-1

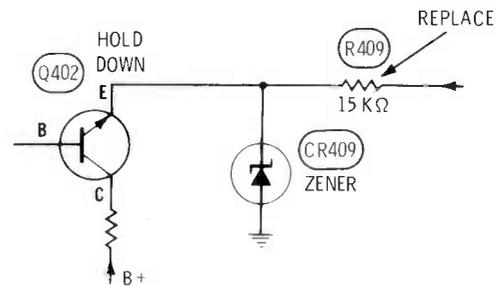


Symptom—Vertical lines at the edges are crooked
Cure—Check R409, and replace it if out of tolerance

Chassis—RCA CTC74
PHOTOFACT—1588-1

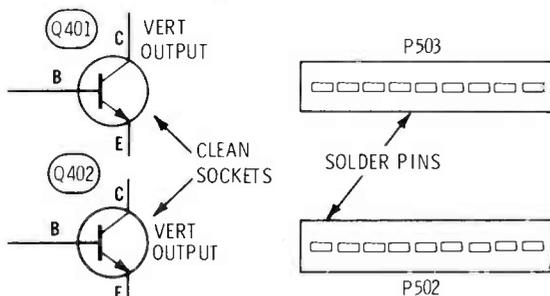

Symptom—Intermittent height, intermittent roll, or intermittent loss of vertical sweep
Cure—Clean socket contacts of Q401 and Q402; also, solder pins to spring contacts in P502 and P503 on PW500.


Chassis—RCA CTC68
PHOTOFACT—1437-2

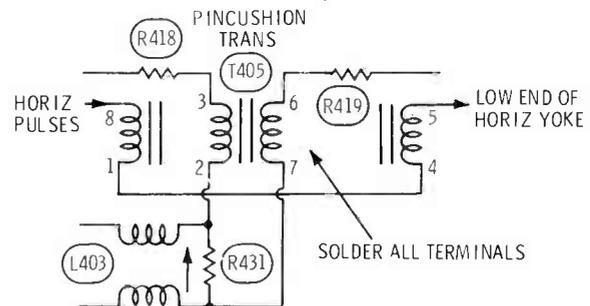

Symptom—Vertical at right side is compressed, similar to a distorted trapezoid
Cure—Check and resolder all joints at terminals of T405

GTS-10

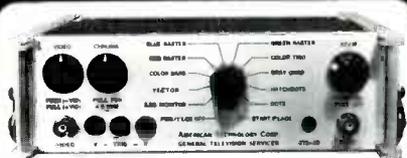our new model of
General Television Servicer



The original General Television Servicer, model ATC-10, set new standards of performance and versatility that far surpassed ordinary color bar pattern generators.

Our new model, the GTS-10, now introduces still more time and money saving features like 4.5 MHz Sound Carrier . . . Blue Raster . . . Green Raster . . . Color Trio. The model GTS-10, with in-home portability, replaces an ordinary color bar pattern generator and includes most of the capabilities of a substitute tuner and an analyst. It also provides capabilities that none of these other instruments can match.

Advanced yet sensibly priced at \$349.00 the GTS-10 is the ultimate instrument on the TV service equipment market.

Write for comprehensive 6 page full color brochure that describes these and many more features.

Telephone orders on VISA and MASTER CHARGE accepted for same day shipment.

2 year factory warranty against all failures in normal use.
30 day money back guarantee.

ATC AMERICAN TECHNOLOGY CORPORATION

225 Main Street, Dept. 11A, Canon City, CO 81212
Phone (303) 275-8991

For More Details Circle (7) on Reply Card

PUT YOUR FINGER ON THE TRUTH

It's the one and only flat-rate increment system that gives you the great feeling of pricing every job right. A system that treats both customer and shop owner fairly. Fast finger-tabs in both editions: **6x9 Hard Cover**, steel ring-bound - \$19.95 ea. post pd.

Or **The Satellite Edition** for pocket sized convenience - \$16.95 ea. post pd.

New **Computerized Parts Pricing** manual lists over 3,500 most-used parts - \$75 initial set-up plus \$10 per copy.



tv & radio
tech's guide
to pricing

P.O. Box 5234
Lincoln, NE 68505

Nebr. residents
add sales tax

sperry tech inc. (No. editions)

My check enclosed _____
 BankAmericard _____ Exp. _____
 Master Charge _____ Exp. _____
 Name _____
 Co. _____
 Address _____
 City _____
 State _____ Zip _____

For More Details Circle (8) on Reply Card

troubleshooting tips

No picture Motorola 23TS921 (Photofact 1096-3)


Only channel 10 showed a picture, and it had multiple images. At first, I suspected misadjustments, since the owner admitted moving some screws. However, better fine tuning of channel 10 cleared most of the ghosts, and my suspicions changed to the tuner.

Then I noticed that the other stations came in with snow, **when the antenna was disconnected**. But with an antenna, the screen would black out. Also, the AGC control had no effect on these symptoms.


When I checked components of the AGC circuit, I found that R95 (connected from one end of the AGC control to ground) had become open.

A new R95 and tuner cleaning gave good reception on all channels

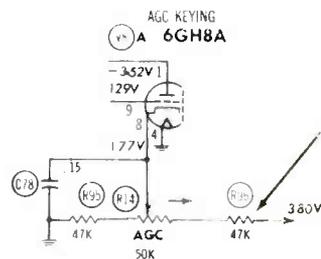except channel 10. After the set warmed up, the sound became garbled. A new audio-output tube cured the distortion.



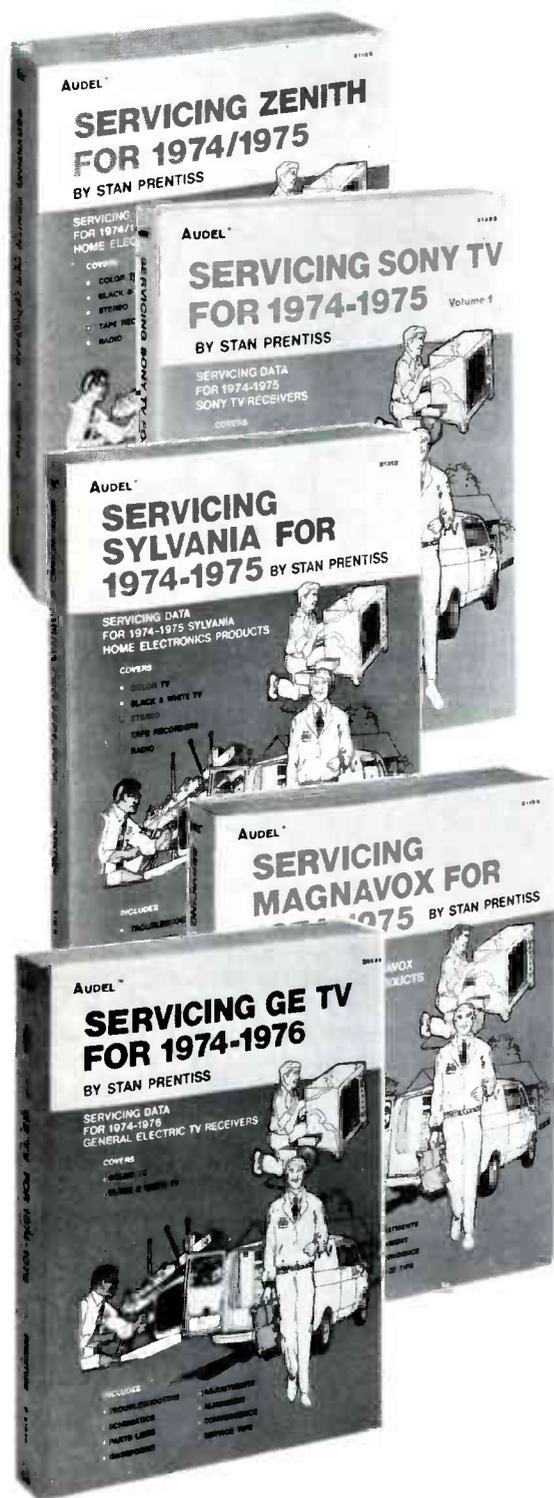Now at big savings complete factory information plus valuable service tips



This is your opportunity to buy Sams popular Audel® TV Servicing Books at substantial savings. Each clearly written volume contains complete factory information. All the factory data such as schematics, parts lists, waveforms, adjustments, alignment and convergence. In addition, these books are packed with valuable service tips, trouble shooting information and detailed theory of operation. The kind of reference material that every shop needs for TV servicing. Why pay for only factory information when Sams Audel Servicing Books offer you so much more?

Right now take advantage of the big savings on Sams Audel Servicing Books. Any of the titles listed below with their original prices can be yours for only \$8.95 each. You save up to \$4.00 a copy. Order today from your Sams distributor or use the coupon below.

Send the books checked below at the special price of \$8.95 each (plus sales tax where applicable). Amount enclosed \$ _____

- | | |
|--|--|
| <input type="checkbox"/> Servicing Admiral TV for 1975/76
NO. 21358 \$12.95 | <input type="checkbox"/> Servicing Panasonic TV for 1974/75
NO. 21220 \$12.95 |
| <input type="checkbox"/> Servicing Magnavox TV for 1976
NO. 21342 \$9.95 | <input type="checkbox"/> Servicing Quasar for 1973/75
NO. 21211 \$12.95 |
| <input type="checkbox"/> Servicing Philco TV for 1973
NO. 21347 \$12.95 | <input type="checkbox"/> Servicing RCA for 1975
NO. 21155 \$12.95 |
| <input type="checkbox"/> Servicing Philco TV for 1974/75
NO. 21384 \$12.95 | <input type="checkbox"/> Servicing Sony TV for 1974/75
NO. 21223 (Volume 1) \$12.95 |
| <input type="checkbox"/> Servicing Sony Color TV for 1969/72
NO. 21422 \$9.95 | <input type="checkbox"/> NO. 21224 (Volume 2) \$12.95 |
| <input type="checkbox"/> Servicing GE TV for 1974/76
NO. 21328 \$12.95 | <input type="checkbox"/> Servicing Sylvania for 1974/75
NO. 21212 \$12.95 |
| <input type="checkbox"/> Servicing Magnavox for 1974/75
NO. 21199 \$12.95 | <input type="checkbox"/> Servicing Zenith for 1974/75
NO. 21165 \$12.95 |
| | <input type="checkbox"/> Servicing Zenith TV for 1976
NO. 21331 \$10.95 |

NAME _____

BUSINESS NAME _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

My Sams Distributor is: _____

CITY _____ STATE _____

SEND TO: Howard W. Sams & Co., Inc./4300 W. 62nd St.
Indianapolis, IN 46206

TCB35

 **Howard W. Sams & Co., Inc.**

4300 West 62nd Street/Indianapolis, Indiana 46206

OPTIMA VALUE SALE

G. E., Sylvania, Zenith, RCA, Etc.
75% Off! List New Jobber—Boxed Tubes

□ 3A3	5 for \$7.44	□ 6JE6	5 for \$15.50
□ 5GH8	5 for \$8.75	□ 6JS6	5 for \$13.75
□ 6BK4	5 for \$13.81	□ 6LB6	5 for \$14.94
□ 6FQ7	5 for \$5.63	□ 8FQ7	5 for \$5.63
□ 6GH8	5 for \$5.88	□ 12GN7	5 for \$10.38
□ 6GJ7	5 for \$5.69	□ 17J28	5 for \$7.69
□ 6DW4	5 for \$6.94	□ 23Z9	5 for \$9.44
□ 6HA5	5 for \$7.13	□ 38HE7	5 for \$13.63

*All tubes not advertised write in at 75% off list.

Sleeves only. Singles at 72% off list.

Special: 100—6GH8's G. E. \$99.00.

Transistors Equivalent Up to 90% Off List

35 each—Minimum 20 per number

SK	ECG	SK	ECG
□ 3018	108	□ 3114	159
□ 3024	128	□ 3122	123A
□ 3025	129	□ 3124	123A

Minimum 5 of a Number

SK	ECG	SK	ECG	ea.	SK	ECG	ea.
□ 3027	130	ea.	90c		□ 3115	165	ea. \$2.75
□ 3054	184	ea.	70c		□ 3248	186A	ea. \$ 7.00
□ 3103	157	ea.	60c		□ 1155	—	ea. \$2.50
□ 3041	152	ea.	70c		□ 1058	—	ea. \$2.50
□ 3079	162	ea.	\$1.50		□ 3197	235	ea. \$2.00

RCA Original Transistors

□ SK 3040	ea. \$2.90	□ 3501	ea. \$3.45
□ SK 3115	ea. \$6.75	□ 3504	ea. \$5.00

IC's Equivalent to ECG

\$1.00 each Minimum 5 of a Number

□ 708	□ 709	□ 710	□ 712	□ 713	□ 714
□ 718	□ 719	□ 722	□ 723	□ 725	□ 731
□ 740	□ 743	□ 748	□ 780	□ 783	□ 788
□ 790	□ 791	□ 793	□ 912	□ 923D	

YOKES

□ Y88	□ Y130	□ Y94	□ Y105	ea.	\$5.75
□ 95-2779				ea.	\$8.95
□ Y153	□ DY92C	□ DY99AC			

Diodes, Rectifiers, Equivalent

□ 6500 PIN Color Focus Rect.	10 for \$4.95
□ 2.5a 1000 PIN IR 170	100 for \$9.00
□ B+ Boost Rect.	20 for \$6.00
□ Syl. Zen. Tripler 212-139	ea. \$6.50
□ Admiral Tripler	ea. \$4.95

Audio—Cartridges—Needles Equiv.

□ Astatic 133	ea. \$1.95	□ 142	ea. \$1.45		
□ BSR SC7M2	□ SC8H2	□ SC12H	ea. \$1.90		
□ CV 26	ea. \$1.50	□ EV 5015	ea. \$2.15		
□ GE LC2	ea. \$.85	□ GECC650	□ 660	ea. \$2.95	
□ Panasonic EPC 42	ea. \$2.00	□ EPC70LTS	ea. \$1.00		
□ Tetrad All Numbers SN-1 to 6	ea. \$1.95				
□ Varco CN75	□ TN48	ea. \$1.40	□ ST4X	ea. \$1.15	
□ Zenith 142-166	□ 167	□ 168	ea. \$2.75		
□ N44	□ 77	□ 75	□ 91	□ V15	ea. \$1.95
□ BSR ST170					10 for \$6.90

CB Hardware and Wire

□ PL 259	10 for \$3.10	□ PL 258	10 for \$3.90
□ 3 ft. RG58 2PL259	ea. \$1.25	□ 20 ft.	\$2.00
□ 20 ft. RG58 1PL259-1 Spade Lug			\$1.70
□ CB Lightning Arrestor			\$.99
□ 50 ft. 59U Incl. F Conn.	ea. \$1.89	□ 100 ft.	\$3.69
□ 500 ft. 59U Coax Mill Ends	3c ft.		\$15.00
□ 50 ft. RG 8U	ea. \$7.55	□ 100 ft.	\$12.95
□ 400 ft. 300 ohm wire 40' hanks White			\$5.00

General

□ 60 Min. Irish Cassette Tapes	24 for \$8.00
□ \$300 Surprise Package	\$10.00
□ 100 Asst. Caps	\$4.00
□ 20 Asst. Belts	\$7.00
□ 300 ohm signal splitters. (TV)	10 for \$7.90
□ TV Lightning Arrestors	10 for \$5.00
□ 75-300 ohm Matching Transformers	10 for \$5.90
□ Deluxe Lock Mounts w/PL259	\$3.95
□ 18" earplug. (Min. 50)	ea. \$.15
□ Speco 2 station Intercom	\$7.95
□ 19" & 25" Color Boosters	3 for \$10.00
□ C Cell Batteries	24 for \$2.40
□ Piggy Back Antennas	5 for \$10.00
□ 25 ft. Headphone Extensions	2 for \$2.98
□ Stereo "Y" Adaptors 1/4"	10 for \$6.90
□ 8 Track Head Cleaner	10 for \$5.90
□ Clothes Pins	100 for \$10.00
□ Pillow Speakers	10 for \$7.90
□ Universal Tone Arm incl. Cartridge and Needle	10 for \$7.90

Speakers

□ 4"	4 for \$4.00	□ 8"	ea. \$2.95
□ 3x5	4 for \$5.00	□ 4x6	4 for \$6.00
□ 4x10			ea. \$3.95
□ 5x7 speaker kit incl. grill			ea. \$1.95
□ 6x9 kit incl. grill and swick			ea. \$3.95
□ 6"x9" OP-69—Min. 10			ea. \$.55
□ 1 Pr. 20" Speaker Baffles. Incl. Speakers			\$19.95
□ 1 Pr. 12" Speaker Baffles. Incl. Speakers			\$9.95

WANTED: Electronic Merchandise.

WILL PAY CASH

- LETTERS OF CREDIT AND ALL CHECKS PLACED ON DEPOSIT WITH MANUFACTURERS HANOVER TRUST BANK, N. Y. C.
- MASTER CHARGE—MIN. \$100—C. O. D.'s 50% DEP.
- BANK AMERICARD—VISA—MIN. \$100—C. O. D.'s 50% DEP.
- MINIMUM ORDER \$75 FOB BROOKLYN, N. Y.
- CATALOGUE \$3, REFUNDABLE UPON ORDER

SEND CHECK OR MONEY ORDER TO:

OPTIMA ELECTRONICS

Box 372 Ryder Street Station
Brooklyn, New York 11234
Phone (212) 439-7434

For More Details Circle (9) on Reply Card

troubleshootingtips

continued from page 12

checked okay; the belt was in good shape, and the capstan had not been worn smooth. Everything appeared okay, except the motor.

Connecting the motor to my regulated power supply and monitoring the current, I identified the trouble right away. The current was very erratic, jumping between 20 and 50 milliamperes, even with the belt off.

Apparently, when the motor hesitated, it allowed the slack in the tape to unwind and catch around the capstan, jamming the tape. Since replacing the motor, I've heard no complaints from this customer.

Gary Steenwyk
Hudsonville, Michigan

Intermittent sound and video Philco 22QT79

(Photofact 1239-3)


We had two different models in the shop with the same problem: intermittent sound and video.

Checking out one set, we found the raster to be okay, but there was no control of brightness when the set lost sound and video.

The transistors also tested all right, so we decided to monitor the 20-volt B+ line, which went to the tuner and was easier to get at for checking. This voltage was intermittent. After spraying canned coolant, we located the problem.

The Q200 active-filter transistor was intermittent. The same trouble was found in the other set, plus a


carbonized VR200 active-filter control.

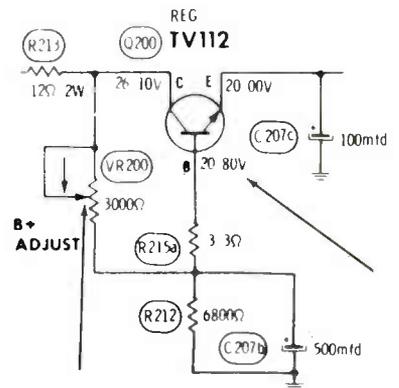

Mac Kellman
Brooklyn, New York

Loss of AGC after warmup Sharp C-6010

(Photofact 1189-2)

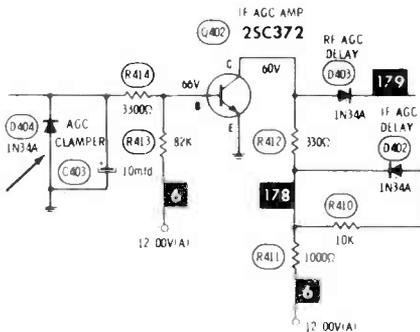

reader's exchange

For Sale: Regency model EC-175 frequency counter (6-digit LED readout), measures to 175 MHz, has crystal oven, FCC type approved, \$300; and Sencore model TF40 transistor tester, \$60. Both in mint condition. Bob Goodman, P.O. Box 452, Alexandria, Louisiana 71301.

Needed: Cabinet for Standardyne model B-6. Also, power transformer for Clarion Jr. model AC-60. William Fox, Jr., 624 Jefferson Court, San Jose, California 95133.

Needed: Schematic and instructions for a RTTA signal generator model K-7, or the name of the manufacturer. Will buy, or copy and return. Walt Studer, 418 Walton Drive, Buffalo, New York 14225.

Needed: Schematic and alignment data for Milovac model RA-1120 AM/FM radio/phono/8-track. Will copy, pay for use and return. David W. Dane, P.O. Box 44, Plaistow, New Hampshire 03865.

Needed: Service and operations manual with schematic for a Century Mark IV Multiband AM/FM/SW1/SW2/AIR/PB portable radio model CF1888, chassis numbers 001029-352. Will buy, or copy and return. Major Norman H. Ball, USAF [RET], Box 565, 32531 Merion Drive, 1000 Palms, California 92276.

For Sale: RCA television calibrator model 39C, mint condition, with manual and cable. Make offer. Matt Rusk, 211 SW Madison Circle North, St. Petersburg, Florida 33703.

For Sale: A B&K model 415 sweep/marker generator used five times, all literature and probes, \$250. One Precision model EV-10 VTVM in excellent condition, \$50, or best offer. One Sencore portable CG-10 color-bar/dot/crosshatch generator, \$50 or best offer. Also, a Sencore transistor tester model TR-139B used little, make an offer. Mert Albert, Clintonville Electric Service, 44 S. Main Street, Clintonville, Wisconsin 54929.

Needed: Tube chart for model 116 tube tester by Precise Development Corp. Also, schematics for Milovac stereo tape recorder model SC-240; Aiwa stereo 5-inch reel recorder TP-1013; GE 2V wet-cell portable radio model 250; and KX Imp II wireless transmitter by Kinematix. Will buy, or copy and return. Bob's TV Service, 8296 Portulaca Way, Buena Park, California 90620.

For Sale: B&K model 280 3-digit DMM with manual and test leads, \$55. Jerry McKouen, 534 Pacific Avenue, Lansing, Michigan 48910.

continued on page 16

Your new RCA QT Parts Inventory Program with annual drop-ship updating.



Here it is! Your new RCA QT (Quick Turnover) Parts Program that assures you an up-to-date inventory of the most used RCA exact replacement TV parts.

Simply contact your RCA Distributor and register as a QT Dealer. You will receive your package of 150 of the most-needed, fastest-moving parts.

Automatically, once a year, QT parts will be evaluated, and the program will be updated to include only the 150 fastest-moving parts. You return the parts that are dropped from the fastest-movers list to your RCA Distributor, and get *full credit*. At the same time, the new parts added to the QT list will be *shipped directly to you from RCA*. A quick, automated inventory control system designed for your convenience.

And, to keep your parts organized for fast servicing, ask your RCA Distributor about the QT Parts Rack. It's sturdy, but light enough to hang on a wall. Saves you time and space.

Call your RCA QT Parts Distributor for all the details, or write to RCA Distributor and Special Products Division, Deptford, N.J. 08096.

RCA QT Parts

reader's exchange

continued from page 15

Needed: Will pay \$30 for a Coronado color flyback, model TV22-1611A, part #15-097079 (VZ12032A) in new condition. This 1971 flyback is unavailable from the factory. *J. Bennett, Economy TV, 617 E. Thirteenth Avenue, Denver, Colorado 80203.*

Needed: Schematic and service information for Philco radio, model 39-116. Will buy, or copy and return. *John T. Rowland, 3646 Pillsbury Avenue, Minneapolis, Minnesota 55409.*

Needed: A C6407 picture tube for Symphonic model AC-30 IPS-5050. Or an address where one can be bought. *R. L. Hallett, 65 Somerset Avenue, Pittsfield, Maine 04967.*

For Sale: Two B&K-Precision model 1076 Analysts. One in good condition for \$100, and another in excellent condition, \$125. Also, an Eico 460 scope, good condition, \$75; one B&K-Precision 700 tube tester, good electrically but rough appearance, \$35; and one Knight tube tester for \$15. *R. L. Hallett, 65 Somerset Avenue, Pittsfield, Maine 04967.*

For Sale: 490 assorted receiving tubes (send for a list, or state requirements); also one B&K-Precision HV probe model HV-32. Best offer. *B. A. Harpool, Harpool's Radio & TV, P.O. Box 267, New Middletown, Indiana 47160.*

For Sale: B&K model 1077B TV Analyst with instruction book and cables; Sencore TC162/TC28 tube-transistor checker; B&K model 467 picture tube restorer/analyzer with new chart; Polaris model 651 HV probe (40KV); and degaussing ring. All equipment in excellent condition. *REO Electronics, 1175 Cling Circle, Hanford, California 93230.*


Needed: Schematics and technical data for the Everett "Orgatron" manufactured by the Everett Piano Company, South Haven, Michigan. (Wurlitzer may have bought company.) Appreciate any information, leads or suggestions. Will copy and return manuals or schematics. *L. R. Broun, Electronic Service, P.O. Box 62, Coolin, Idaho 83821.*

Needed: Back issues of *Electronic Servicing*, Rider's radio 23, any Rider's TV, or other manuals and magazines. Will buy or trade. *Donald Erickson, 6059 Essex Street, Riverside, California.*

Needed: One Precision sine and square wave generator model E-310 by Precision Apparatus. Generator does not need to be in working order. *Jim Shoemaker, 600 First Street, Leechburg, Pennsylvania 15656.*

Needed: A schematic for a Schaub Lorenz Touring T20 transistor portable radio with AM, FM and SW. *W. M. Dennehy, 14-77 160th Street, Beechhurst, New York, New York 11357.*

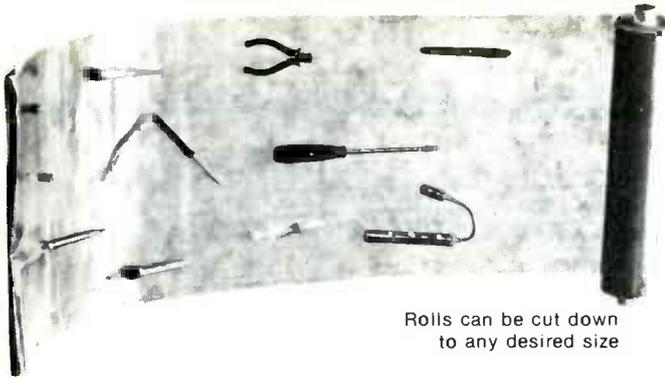Needed: 16BXP4 picture tube. *Raymond W. Shirk, Radio and TV Repair, 440 Poplar Street, Lebanon, Pennsylvania 14042.*



Rolls can be cut down to any desired size

KAGER PRODUCTS - Innovations for Production, Laboratory and Workshop ANTI-SLIDE

Stops everything from slipping and sliding around—indispensable in assembly work. Tools and components are playful little devils. They love to dance or play hide and seek on and around the work surface. ANTI-SLIDE puts an end to this time consuming and wasteful mischief. This unique fully washable and reusable plastic material holds objects placed on it as if they were glued. Components do not move even if they are pushed. In addition, ANTI-SLIDE acts as a noise and vibration dampener. No other even remotely similar product exists. Available in five attractive colors. Send Inquires to:

KAGER INTERNATIONAL

SUITE 710 • 1180 SOUTH BEVERLY DRIVE • LOS ANGELES, CALIFORNIA 90035
Telephone: (213) 879-1575, TWX 910-490-2121

For More Details Circle (11) on Reply Card

NEW & DAZZLING!!!

MS-15 Miniscope—the Ultra
Oscilloscope for \$289.00 from NLS



Features Include:

- Bandwidth: 15 MHz.
- External & internal trigger.
- Automatic & line sync modes.
- Input sensitivity: vertical -10 mV; horizontal -1V.
- Vertical gain: .01 to 50V/div - 12 settings.
- Time base: .1 μSec to .5 Sec/div - 21 settings.
- 3% accuracy on all functions.
- Power consumption: <15 W.
- Battery or line operation with batteries and charger unit included.
- Weighs only 3 lbs & dimensions are 2.7" H x 6.4" W x 7.5" D.
- Options include a 10 to 1, 10 megohm probe and leather carrying case.



Non-Linear Systems, Inc.

Originator of the digital voltmeter.

Box N, Del Mar, California 92014 Telephone (714) 755-1134


For More Details Circle (12) on Reply Card

SHERLOCK OHMS & DR. WATTS

IN THE CASE OF THE EXPIRED ENGINEER

OR DMM DE DMM DMM

by DUMONT

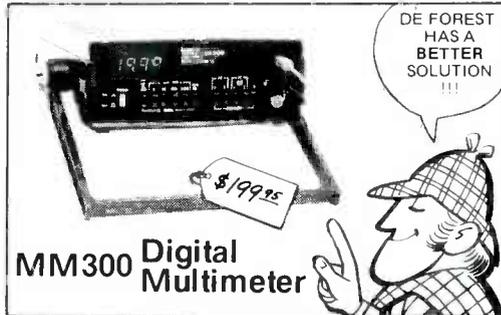

QUALITY AND PERFORMANCE YOU EXPECT... AT A PRICE YOU CAN LIVE WITH!

- TRUE RMS
- A4 TO 1 CREST FACTOR
- OPEN CIRCUIT OHMMETER VOLTAGE LIMITED TO 2 VOLTS
- BATTERY \$18.00

JUST CALL US TOLL FREE (800) 631-1043. WITH YOUR CHARGECARD NUMBER FOR IMMEDIATE DELIVERY

DE FOREST

A Subsidiary of
DUMONT OSCILLOSCOPE
LABORATORIES, INC.
40 FAIRFIELD PLACE
WEST CALDWELL, N.J. 07066

For More Details Circle (13) on Reply Card

Needed: Schematic and service manual for Philco color-bar and dot-bar generator, model 7100. Will buy, pay for copy, or copy and return. Roland Strauss, 11 Chieftain Drive, Creve Coeur, Missouri 63141.

For Sale: Heath scope model IO-102, factory wired and calibrated, good condition, with low-capacity probe, \$95. Also, Telematic VHF/UHF sub tuner, AC/battery operation, never used, \$55. Willis Ormes, 1420 Melrose Avenue, Fort Wayne, Indiana 46808.

Needed: Schematic for model 98 VTVM Tektronix 512 scope. Will buy, or copy and return. Donald C. Maeyer, 12696 Greenhall Drive, Woodbridge, Virginia 22191.

For Sale: Heathkit video game model GD-1380. Play three games plus practice; also, two different size target practice. Target gun not included, but can be obtained from Heath. Assembled and in excellent condition; \$40. Robert C. Knapp, Box 145, Lyndhurst, Virginia 22952.

For Sale: Two Sorensen model 1000S, 1000-watt line-voltage regulators, adjustable output voltage. Good condition, best offer. Sam Eassa, 407 Huntclub Road, Nashville, Tennessee 37221.

Needed: Schematic for model 240 Callmaster telephone-answering device made for Phonemaster by Altec Lansing. Will buy, or copy and return (pay for postage and handling). Bob Williams, 1613 Lorraine Drive, Plano, Texas 75074.

Needed: Schematic (or photocopy) and instructions on conversion of UTI-COM FM commercial receiver to 2-meter ham band. Also, need Dow-Key coaxial antenna relay 12 VDC for TX-62; state price. Anthony Bodo (WA9YOZ), 4380 Hayes St., Gary, Indiana 46408.

For Trade: Sencore senior field-effect meter, model FE-149, like new. Need He-Ne Laser, 0.5 milliwatt, BRH Class II. Dwight Miller, 901 Daggett Drive, Napoleon, Ohio 43545.

For Sale: Hickok research and development square-wave generator model 1715A, 1 Hz to 1 MHz, 75-ohm and 600-ohm variable output levels, like new, \$50. James Ryder, 101 Clayman Road, Sandston, Virginia 23150.

Needed: Schematic and service manual for AKAI M-10 or M-9 stereo recorder (especially interested in alignment specs). Will buy, or copy and return. Michael Craig, 421 Fairmount NE, Warren, Ohio 44483.

For Sale: Sencore PS148 oscilloscope/vectorscope, five-inch, wideband, high-sensitivity, never used, \$200. J. A. Robinson, P.O. Box 181, Bluffton, South Carolina 29910.

Needed: Symphonic TV model AC-20 7PS5050. Will buy, working or not. W. Cullen, 3701 W. First, Suite 201, Los Angeles, California 90004.

Needed: Power transformer (part 32-10006-3) for Philco AM-FM stereo radio, model M-1666WA, new or used. State price. John Iannelli, 1501 Saunders Cres., Ann Arbor, Michigan 48103.

For Sale or Trade: EICO 369 TV-FM sweep and marker generator; factory wired, A1-shape, with manual. Or trade even for EICO 379 solid-state sine and square audio generator, in A1 condition. William O'Lekas, 33650 Baldwin Road, Solon, Ohio 44139.

Needed: Rauland RS-10A intercom units, or other Rauland items. Need not be operating; wanted for parts. Ed Howell, Folly Beach, South Carolina 29439.

Needed: Schematic and service information for a Detectron model DG-2, serial number E2551901-CE) geiger counter. K & W Electronics, P.O. Box 692, South 215 Washington, Newport, Washington 99156.

For Sale: Riders radio manuals 6-17 inclusive, without indexes, \$15 each. Tubes 01A, 112, 199, etc. Want good dual-trace 15 MHz scope with probes and manual. J. A. Call, 1876 E. 2990 So., Salt Lake City, Utah 84106. □

Servicing Magnavox Modular Color TV, Part 6



By Gill Grieshaber, CET

*No moving parts or switches are in the UHF and VHF tuners of the Magnavox Videomatic Touch-Tune system. These tuners operate with varactor and switching diodes. Such designs are not new; however, the sophisticated **digital** circuits that control the tuners are as modern as tomorrow. Because these circuits will be used more often in the future, we strongly suggest that you study the explanations carefully.*

The most interesting and complicated circuits of the Magnavox T995 chassis are found in any model with Videomatic Touch-Tune (Figure 1), which *digitally* controls both tuners, the volume, and power on/off.

A remote-control kit can be installed in the field, without requir-

ing modifications. Undoubtedly, this compatibility was responsible for some of the principles of the Touch-Tune designs. No motors or other moving parts are used with either the Touch-Tune station selection, or the remote-control functions.


Before starting detailed explana-

tions of these intricate circuits, we'll tell you the general operations and purposes.

STAR Versus Touch-Tune

Magnavox has two distinct types of digital-controlled tuner systems. The STAR electronic tuning uses random-access digital logic to lo-

Figure 1 These are the normal in-cabinet locations of the control panel and control chassis of the Magnavox Touch-Tune system. The chassis is at the bottom.

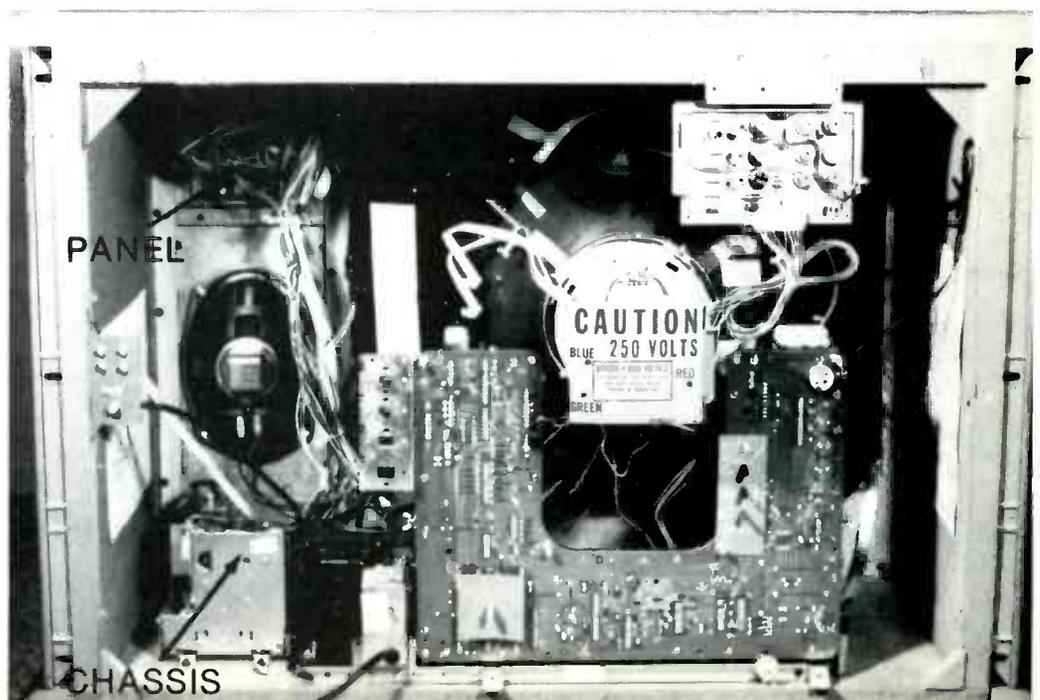



Cables to the selector panel are long enough to permit removal of the assembly from the cabinet. The left picture shows the panel with the door closed. The same panel after the door was opened is shown at the right. Operating and programming controls are behind the door.

cate the desired channels; no programming is required. **An opposite approach is used with the Touch-Tune system, for it operates from memory circuits, and each active channel must be programmed separately.**

Other Features

The Touch-Tune front panel has no knobs or variable controls (although variable operating controls are behind the door that's over the panel). Stations are selected by pushing in two of the calculator-type buttons, in sequence. For example, channel 5 is tuned by pushing zero and 5. Channel 41 requires 4 and 1. To the left of the buttons is the two-digit display for the channel numbers. When the first button is pressed, the channel digits disappear; however, the previous channel still operates. After the second button is pressed, the LEDs light up with the new channel number, and the picture and sound come on a split second later. The action is virtually instantaneous.

Twenty VHF and UHF channels can be programmed into the memory banks. VHF channels 2 through 13 are programmed at the factory, and they should not require any additional adjustment. That leaves eight channels for UHF. All desired UHF channels must be manually programmed.

The Magnavox manual does not say so, but I believe any inactive VHF channels could be reprogrammed for UHF, if more than eight were desired.

Two volume buttons are provided. One has an arrow pointing down (for lower volume), and the

other has the arrow pointing up, for louder sound. The volume gradually becomes softer or louder, taking several seconds to make large changes. Therefore, you must hold the button down until the desired level is reached. In normal operation, the circuit has a good "memory." But if the receiver is unplugged for a time, the sound level is soft when power is restored and switched back on.

A similar action occurs with the power on/off operation. The power switching is done by electronic latching circuits that activate a relay. If the receiver is off (but has power to it), one push of the on/off button switches on the power. A second push of the *same* button

turns off the power. However, if the receiver is on when the power cable is unplugged, the power will be off when it is plugged into an outlet the next time. Another push of the button is necessary for turn-on.

Programming The Channels

Although the entire method of programming TV channels into the Touch-Tune system seems extremely complicated at first, it actually can be done accurately and rapidly the *second* time. A knowledge of the operation can be very helpful.

Before the UHF channels are programmed, the buttons for any channel can be pressed, lighting the LED channel number. However, only snow can be seen on the

continued on page 20



A large two-digit seven-segment red LED display shows the channel number. Above the display are the Videomatic button (gives a choice of preset or customer-operated controls) and the button for electronic on/off of the TV power. The 12 buttons are for selection of the channels, plus volume up and volume down.

Figure 2 This closeup of the manual color controls and the programming controls show: the tuning meter that's calibrated in the channels of three bands; the band-indicating LEDs beside the meter (almost invisible in the picture); and the four programming controls. The small knob at the far right is the "yellow" knob that enables programming, the left one of the three levers is the "green" location lever, the "red" channel-number lever is in the center, and at the right is the "blue" tuning-voltage lever. Readjustment of the preset color controls can be done by inserting a small screwdriver through the center holes of the manual knobs.



Magnavox

continued from page 19

screen, and the LED readout flashes to indicate that the channel has not yet been programmed.

That's because the eight spaces have been factory adjusted for a varactor tuning voltage of zero, and for a channel readout of zero (the readout can show any number from 0 to 99). Incidentally, during remote-control operation, any channels programmed to "zero" will be skipped during the up or down search. Merely pull out the yellow knob and use the red lever to run the channel number back to zero. It's not necessary to zero the tuning voltage.

Four programming steps

Programming a zero channel to receive a UHF station is done in

four steps. **Separate adjustments are provided for: the programming switch; the channel location; the digital channel readout, and the tuning voltage** required for the varactor diodes in the tuners to reach the desired channel.

The programming controls are behind the door that's just above the channel pushbuttons. As shown in Figure 2, the tuning meter is at the left. This meter reads the varactor tuning voltage, and is calibrated in the channel numbers of three bands (2 through 6, low VHF; 7 through 13, high VHF; and 13 through 83, for UHF). Three LEDs at the right of the meter show which band is in use.




The **green lever** operates the "location" switch, which is the equivalent of the detents of a conventional tuner. Channel number of the desired station is selected

by the **red lever**, and the **blue lever** adjusts the tuning voltage to receive the correct station.

At the far right are two knobs with many functions. The gray knob near the panel operates the peaking (or sharpness) control. In front of it is a smaller yellow knob that has *three* functions. When turned fully counterclockwise, the master power switch opens (this switch must be on for remote operation, or to allow power turn-on from the panel on-off button. Clockwise rotation operates the tone control, while pulling out on the yellow knob allows (enables) the other programming controls to be operated (otherwise, the programming switches don't work).

Sequence of programming

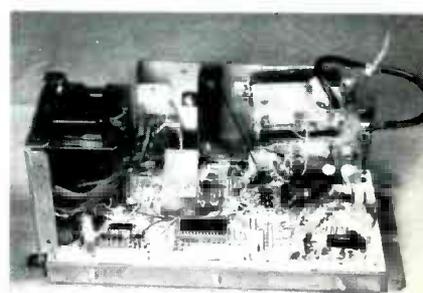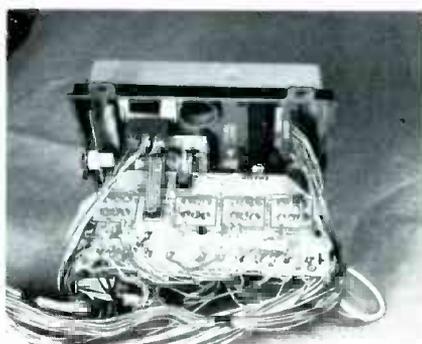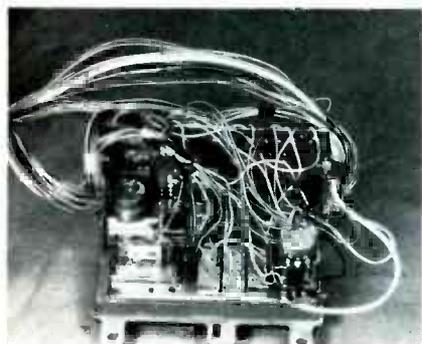Although the Magnavox programming instructions are detailed,



The left picture shows the programming and other controls when the panel is inverted with the top nearest the camera, while the center picture shows the bottom of the circuit board and the back of the display and keyboard. All cables of the tuner-control chassis can be unplugged, and the

chassis removed for testing or replacement. Six ICs and twenty transistors are used to control the two tuners. A remote-control kit can be mounted in the corner near the power transformer for a simple field installation.

there are a few peculiarities omitted. Therefore, I'll give the method, along with comments of my own.

Here are the programming steps:

- Pull out the small **yellow knob** (Figure 2) of the programming switch (this disables the AFT automatically). Note: the station, tuned in before the knob is pulled out, remains on the screen, and the channel digits do not change, but the three programming levers now can operate.

- Each flip up or down of the **green** (memory location) lever jogs the system to a new location, including the programmed channels. For example, suppose you have channel 9 tuned in. After you pull out the yellow knob, nothing apparently changes. But when you flip up the green lever, channel 10 digits are displayed, and the picture or snow (if your area does not have a channel 10 station) is on the screen. Flip it up again for channel 11, and so on. (Of course, you can flip the green lever down to jog to the next lower channel.) The next channel above 13 reads zero (remember only 2 through 13 are factory programmed). This is the first position for UHF, and it must be assigned a channel number (red lever) and a tuning voltage (blue lever).

- Push up on the **red** (digits) lever, and hold it there. The digits slowly and automatically advance from zero to 2, 3, etc. In the same way, a continued pressure downward on the red lever causes the channel digits to count down. Stop at the channel number you want programmed. (If you pause at the

channel number of an active VHF station, **no picture appears**. This adjustment moves the digits only, not the location or tuning.) Both the *location* and the digital *channel number* now have been programmed into the memory.

- The **blue** lever adjusts the varactor-tuning DC voltage for the station. This tuning voltage is measured by the panel meter, which is calibrated in channels (Figure 2). Also, one of the three meter LEDs lights to indicate which of the three ranges is in use. The system varies the tuning voltage between zero and +30 volts. The voltage gradually increases when the blue lever is held in the upper position, and it slowly decreases while the blue lever is held down. If the meter is not reading the range that you want, scan to the top, where the meter suddenly returns to zero at the left, and changes to the next higher range. For example, at channel 13 the meter has been near the maximum deflection for the high-VHF range. After you use the green lever to find the first UHF location above that, the meter changes to the UHF scale with a reading of zero volts. Therefore, press up on the blue lever, holding it there for several seconds as the pointer slowly moves to the right toward the desired channel number. After you pass through the station, press down or up alternately on the blue lever, as needed to give best picture, color, and sound (just as you adjust a fine-tuning control). That completes the programming of the first UHF channel. For the next UHF channel, push up once on the

continued on page 22

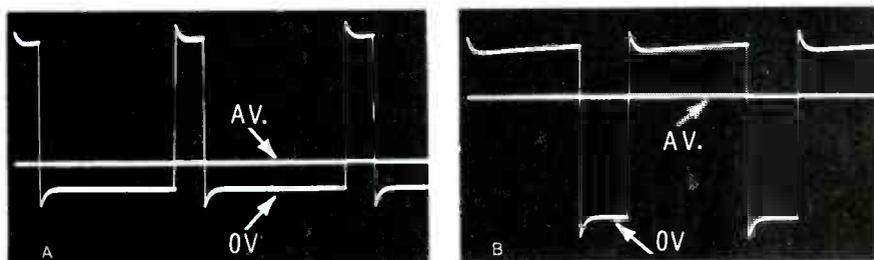


Figure 3 The bottoms of these waveforms are at zero DC volts. Therefore, each horizontal line represents the average DC voltage. The waveforms vary in pulse width (duty cycle), and thus produce different DC voltages after passing through three RC low-pass filters. The waveform on the left (A) was generated by channel 2, and the tuning voltage was +4.42; the wider pulses of the right waveform (B), channel 6, gave a tuning voltage of +21.2.

ARROW

AUTOMATIC

STAPLE GUNS

CUT WIRE & CABLE
INSTALLATION COSTS

... without cutting into insulation!

SAFE! Grooved Guide positions wire for proper staple envelopment! Grooved Driving Blade stops staple at right depth of penetration to prevent cutting into wire or cable insulation!

No. T-18—Fits wires up to 3/16" in diameter.

BELL, TELEPHONE, THERMOSTAT, INTERCOM, BURGLAR ALARM and other low voltage wiring.

Uses T-18 staples with 3/16" round crown in 3/8" and 7/16" leg lengths.



No. T-25—Fits wires up to 1/4" in diameter.

Same basic construction and fastens same wires as No. T-18.

Also used for **RADIANT HEAT WIRE**

Uses T-25 staples with 1/4" round crown in 9/32", 3/8", 7/16" and 9/16" leg lengths.



NEW! Intermediate

No. T-37—Fits wires and cables up to 5/16" in diameter.

Same basic construction as Nos. T-18 & T-25.

Also used for **CATV and DRIVE RINGS** in stringing wires.

Uses T-37 staples with 5/16" round crown in 3/8", 1/2" and 9/16" leg lengths.




No. T-75—Fits wires and cables up to 1/2" in diameter.

RADIANT HEAT CABLE, UF CABLE, WIRE CONDUIT COPPER TUBING or any non-metallic sheathed cable.

Also used as **DRIVE RINGS** in stringing wires.

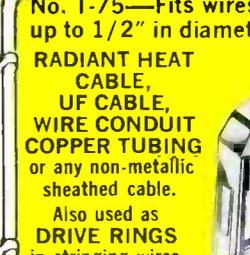Uses T-75 staples with 1/2" flat crown in 9/16", 5/8" and 7/8" leg lengths.



ARROW FASTENER COMPANY, INC.

271 Mayhill Street, Saddle Brook, N. J. 07663

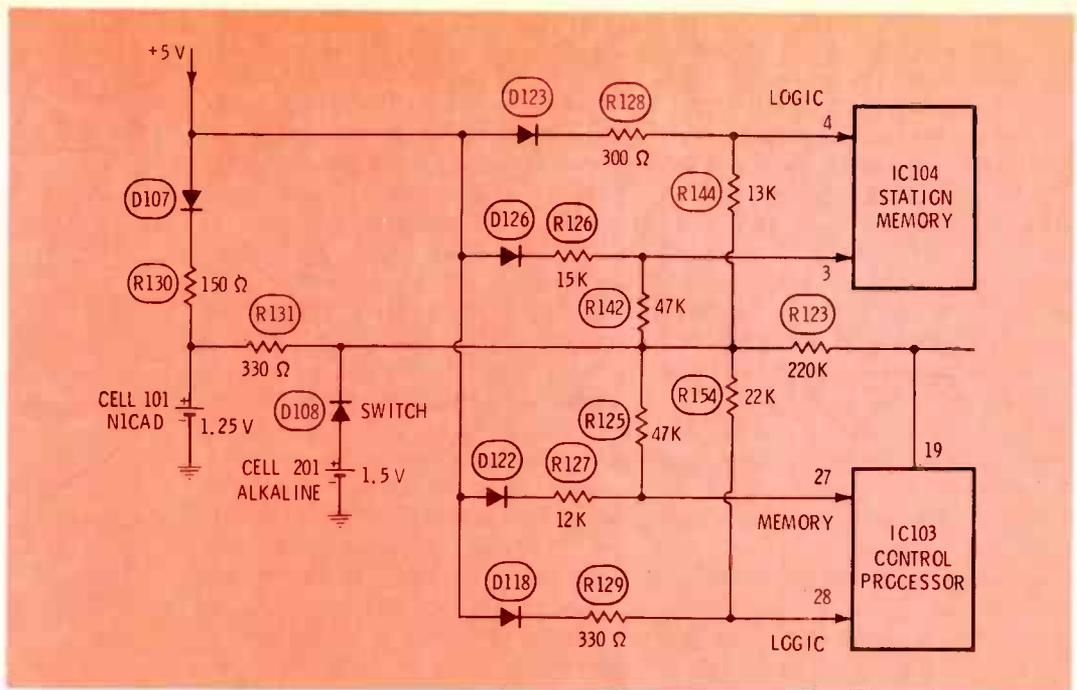


Figure 4 "Keep-alive" voltage for the memories in IC103 and IC104 is supplied by two batteries. For about 18 months after manufacture, the alkaline cell 201 supplies this voltage through D108. When the set is not plugged into the power, diode D107 prevents cell 201 and cell 101 from discharging into the +5-volt supply. With power, diode D107 brings in the normal operating voltage, and D108 opens to disconnect the alkaline cell. During this time, the NiCad cell 101 is being charged through R130 from the +5-volt supply. After it is charged, the NiCad cell will hold a sufficient minimum voltage for about four months to prevent loss of memory. The other diodes act as switches to prevent the ICs from being supplied by both the batteries and the normal supply. It's not likely that a loss of battery voltage ever will occur. However, in that event, all channels will require reprogramming.

Magnavox

continued from page 21

green lever to reach the next blank position. Then program it with the red and blue levers. Repeat the procedure for any other UHF channels. After all of the channels are programmed, you can operate the green lever as a channel selector to check all of the active channels. In my location, I programmed UHF channels 19, 27, and 41, which left five blank locations. In other words, when starting at channel 12 and going up, the next channel is 13, then 19, 27, 41, zero, zero, zero, zero, and zero, before starting with channels 2, 3, 4, etc.

- Push in the **yellow knob** (which activates the AFT and disconnects the programming controls), and use the regular Touch-Tune buttons to select each programmed channel, especially the UHF stations. If any one channel seems to have a borderline frequency, pull out the yellow knob, and jog the blue lever for correct fine tuning. Push in the yellow knob, then recheck all of the programmed channels. This con-

cludes the programming adjustments.

Cable channels

CATV systems often convert UHF stations to an unused VHF channel. Also, some systems change the frequency of each station by a megahertz or so. The Touch-Tune adjustments can overcome both of these problems.

Suppose a channel 25 station is distributed on the channel 6 frequency. Merely program the channel digits for 25 (rather than 6), but use the low-VHF range and the blue lever to tune in the station on channel 6.

Cable channels with only a slight frequency shift can be accommodated easily. Push the buttons for the nominal channel frequency, pull out the yellow knob, and jog the blue lever as needed for best fine tuning. Push the yellow knob back in. That's all.

Developing The Tuning Voltage


One of the most interesting circuits of the Touch-Tune system

is the method of obtaining the DC tuning voltage for the varactor diodes in the tuners.

Generally speaking, digital circuits do *NOT* operate with or produce a variable DC voltage. Digital operation works with pulses or square waves.

However, it's possible to obtain a DC voltage from pulses, when the conditions are right. First, the pulses or square waves cannot be fed through a coupling capacitor. Instead, either the top or bottom of the waveform must be at a DC voltage (such as ground or B+).

Secondly, the pulses or square

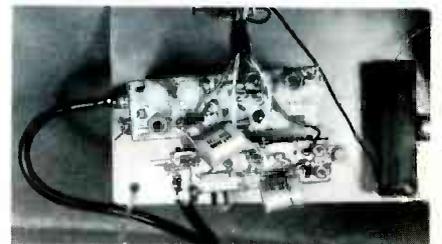

Both small tuners are mounted on a side panel of the control chassis. The alkaline cell is inside the housing to the left of the tuners.

waves are filtered in a low-pass circuit to remove the waveform, but leave the *average* DC component, which is developed by the filtering.

Given those conditions for obtaining a DC voltage from pulses or square waves, it's a small step to **obtaining a variable DC voltage by filtering pulses that vary in width (duty cycle).**

Look at the principle this way: assume an electronically driven relay that passes a B+ voltage for half of the time. **To a DC meter, this will measure the same as a steady DC voltage of one-half of the supply.** Or, change the duty cycle so the relay applies power for only 10% of the time. The DC meter will *average* the voltage and give a reading of 1/10 of the supply voltage.

Now, pulses and square waves (that are clamped to ground or B+) follow this same action. The average DC as read by a DC meter equals the DC steady voltage after the AC waveform is removed by a low-pass filter.

Therefore, **the Touch-Tune tuning voltage is developed by filtering pulses whose width is determined by the memory of the conditions that were programmed into IC104.** Refer to Figure 3, for the actual waveform and measurements from the Magnavox circuit.

Maintaining The Memory

IC103 and IC104 each contains a Random Access Memory (RAM) of 20 "locations." The data necessary for pushbutton selection of the channels is programmed into these two ICs. (Incidentally, three of the ICs use the new logic technology called Integrated Injection Logic (or I squared L). I²L provides many components on a chip, fast operation, and low current requirements.)

Unfortunately, the RAMs can be deprogrammed by any total removal of the DC voltage from certain inputs. To prevent this problem, *two* battery cells are provided, as shown in Figure 4. Why two batteries? That takes a bit of explaining.

The control unit is operating at all times (except when the "vacation" switch is off, or when the power cable is unplugged). So, it appears that a NiCad single cell

continued on page 24

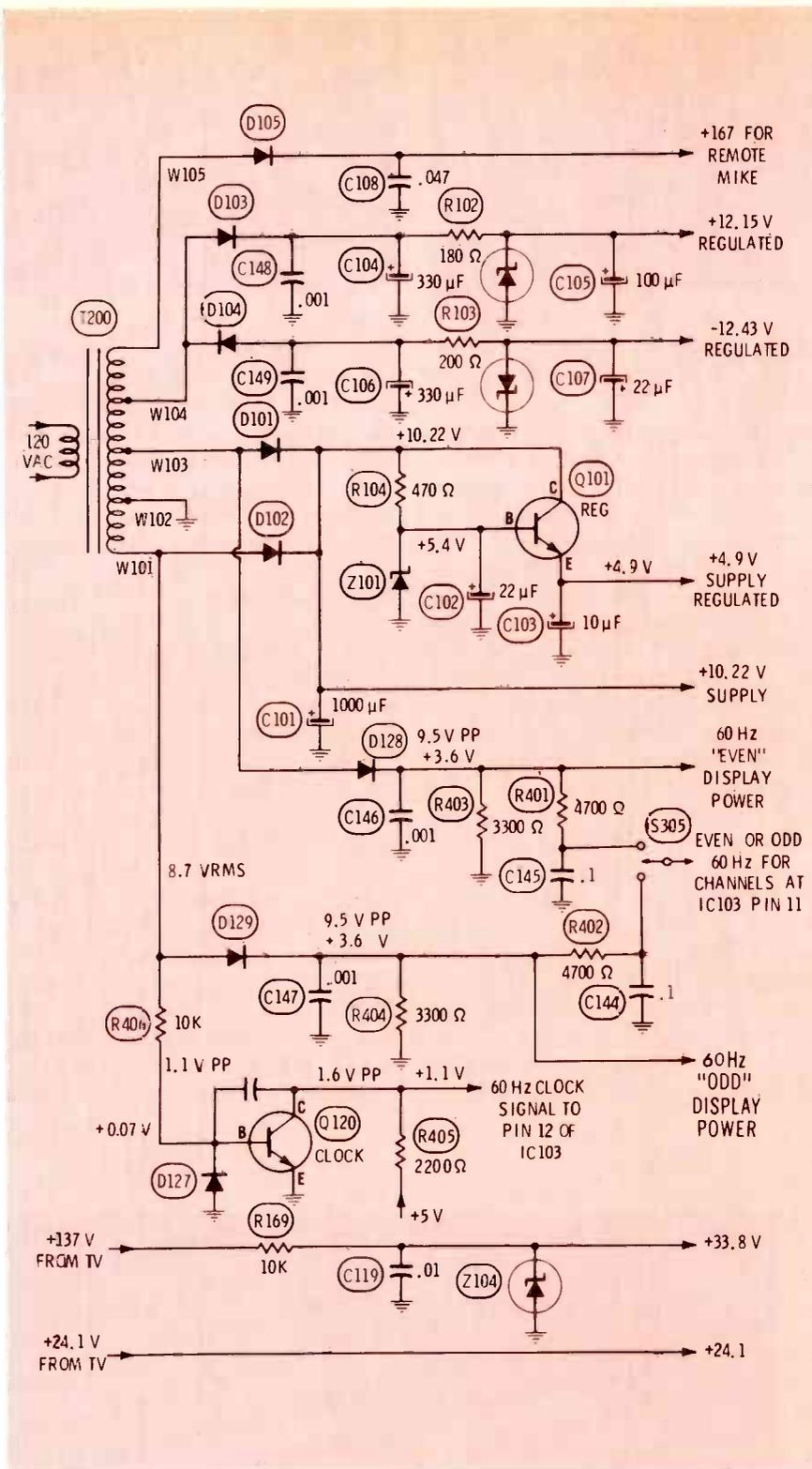


Figure 5 This complete power-supply schematic shows the sources of all tuner-control DC voltages. Notice that two come from the TV chassis. The others are present at all times when the set is plugged in and the master switch is on, even after the TV is turned off. Regulation of the 5-volt supply is accomplished by a conventional series-pass transistor, whose base bias is clamped by zener Z101. Out-of-phase clipped 60-Hz signals are needed, and they are produced by D128 and D129 (the waveforms are shown in Figure 6). The signals through R401 and R402 to S305 are delayed in phase a bit, but otherwise have the same waveshape as those at D128 and D129. Q120 has no forward bias except from the 60-Hz voltage coming through R406. Also, diode D127 clips the negative peak. Therefore, the output of Q120 at the collector consists of clean square waves (see Figure 6). This is the 60-Hz clock signal required by one of the ICs.

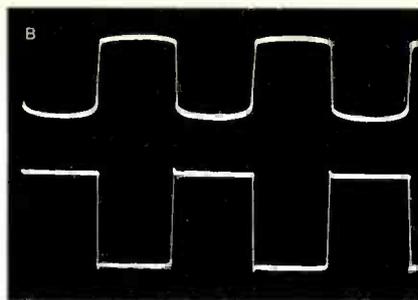
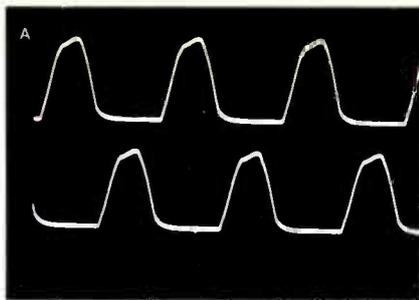


Figure 6 The top trace of photo A is the clipped output from D128, and the bottom trace is the output waveform from D129. Photo B shows the base waveform (top trace) and the collector waveform (bottom trace) of Q120, which acts as a 60-Hz clock.

Magnavox

continued from page 23

(under charge from the power supply) would be a perfect standby voltage source. But, there is a problem. NiCads discharge slowly between charges, and they are completely discharged after about four months. Even if the factory installed a charged NiCad, the charge might be gone before the TV was sold and plugged into the power. In that case, all of the programming would be eliminated, and all channels would require new programming.

The answer is to include the NiCad with a charging circuit, but also to add an alkaline battery that has a shelf life of about 18 months.

Both of the batteries and the tuner-control power supply are decoupled by diodes. The NiCad is charged when the power is on; but when the power is off, D107 prevents the NiCad from feeding the power supply. In addition,

diode D108 opens when the alkaline cell voltage drops below that of the NiCad. Thus, the alkaline cell is effectively disconnected from the supply voltage, and does not require removal after it fails.

The other diodes decouple the battery voltage and the supply voltage so that only one source feeds the ICs at a time.

Power Supply


Figure 5 shows the complete power-supply schematic of the Touch-Tune system. Seven DC voltages are required. Also generated are a 60-Hz square-wave that functions as a clock signal, and two phases of clipped 60-Hz sine waves for the digital display. Voltages on the schematic are those measured in the chassis, while several typical waveforms are shown in Figure 6.

Two of the voltages come from the TV chassis. These become zero when the power is turned off by the on/off button. All of the other voltages are there at all times

(except when the power cable is unplugged).

There are no dial lamps or tubes to glow and remind you that the circuit is operating, so it's easy to forget. You could burn up an ohmmeter by trying to check a supply voltage for shorts.

Although I knew better, I made a mistake that wasted much time. The AFT was not operating while I practiced programming, and without reading the entire Magnavox explanation, I thought that a defect had killed the AFT. (Actually, pulling out the yellow knob defeats the AFT.) Sure enough, the collector of Q107 checked about 8 ohms to ground. That's the point grounded by the Videomatic and AFT switches when in the off position. Only after I had removed C122 and Q107, plus checking everywhere for the short, did I find that *conduction* of Q107 was producing the short. The control power was on (I had forgotten that), and the yellow switch was out, so the circuit called for saturation of Q107. Well, after kicking myself for such stupidity, I studied the circuit more thoroughly. Remember my mistake, and avoid a similar one.

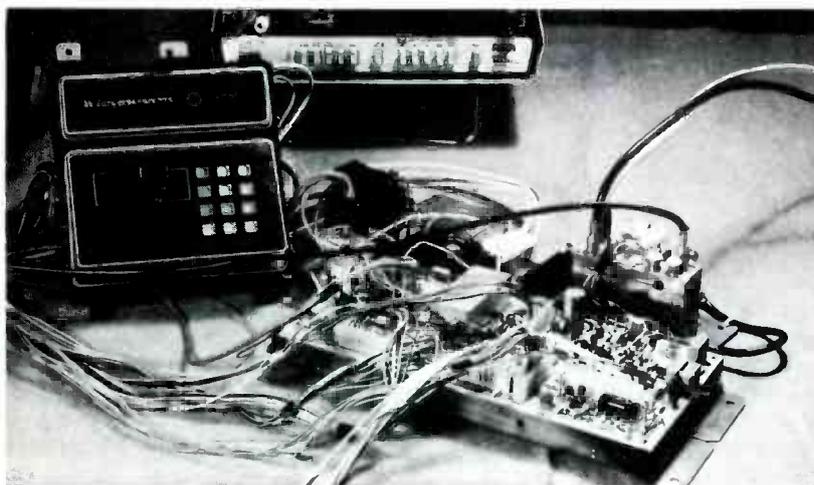

Most of the cables to the panel unit and the control chassis are long enough (after the cable ties are removed) to permit locating the panel and chassis on a table or bench near the TV. Only two extender cables are required, and they can be obtained from Magnavox. All components of the Touch-Tune system are easily accessible, and all functions can be operated, when the two units are removed from the cabinet.

Next Month

In this first article about the Magnavox Touch-Tune digital tuner control system, we have shown you pictures of the system, and provided a general idea of the way the circuits operate.

Next month, we will continue with detailed circuit analysis of the various control functions. □

Correction


In last month's article (Part 5), the caption for Figure 5 should have read, "Major components of the M110 color-oscillator module are identified on the photograph."

ALL AROUND OHM!

by Edmund A. Braun

Hi there!
Here's a Pinwheel
Puzzle guaranteed
to have you going a-
round in circles no mat-
ter how well versed you
are with Electronics! The
last letter of each word
is the first letter of the
next word. Each correct
answer is worth 3
points; a perfect score
is 108. A high rating
should be fairly easy
except perhaps for some-
one who thinks "gram"
is a cracker, or that
"loudspeaker" is an an-
gry housewife! One good
turn deserves another,
so GO!

- 1 Sections of a switchboard.
- 2 Unites two or more wires to make electrical connection.
- 3 Device for controlling current.
- 4 Sinusoidal wave with frequency that's a multiple of fundamental wave.
- 5 Clay-like substance which, after processing, is used as insulation.
- 6 Receiver cabinet that stands on the floor.
- 7 Type of insulation that's baked on.
- 8 Greek letter to designate wave-length measurements.
- 9 To adjust components of a system to proper interrelationship.
- 10 The usual condition, degree, quantity, or the like.
- 11 An interconnection.
- 12 A protuberance.
- 13 Method of winding a non-inductive resistor.
- 14 Variety of electronic systems for locating, direction-finding, etc.
- 15 Type of variable resistor.
- 16 High slender structure.
- 17 To enlarge a hole or to bevel out.
- 18 Something serving as a base, backing, support, etc.
- 19 Connection, accidental or intentional, between earth or chassis, etc.
- 20 Arrangement of parts in a device to facilitate servicing or improve efficiency.
- 21 A hard, silver-white metallic element much used in various alloys.
- 22 Connection wire for testing, etc.
- 23 Decreasing the amplitude of oscillations, waves, etc.
- 24 Mineral used as detector in early radio sets of simple design.
- 25 The sound portion of a telecast.
- 26 Hard alloy of the platinum group.
- 27 Trade name of du Pont for a highly durable plastic film of outstanding strength.
- 28 Type of crystal-controlled vacuum tube oscillator named for its inventor.
- 29 Representing nothing at all.
- 30 Instrument for direct reading of resistance to flow of current.
- 31 A headed, malleable metal pin used to fasten pieces together.
- 32 Messages handled by communications or amateur stations.
- 33 A waterproof, insulated bundle of wires.
- 34 To give out; radiate; send forth.
- 35 Hand implement such as a screwdriver, wrench, pliers, etc.

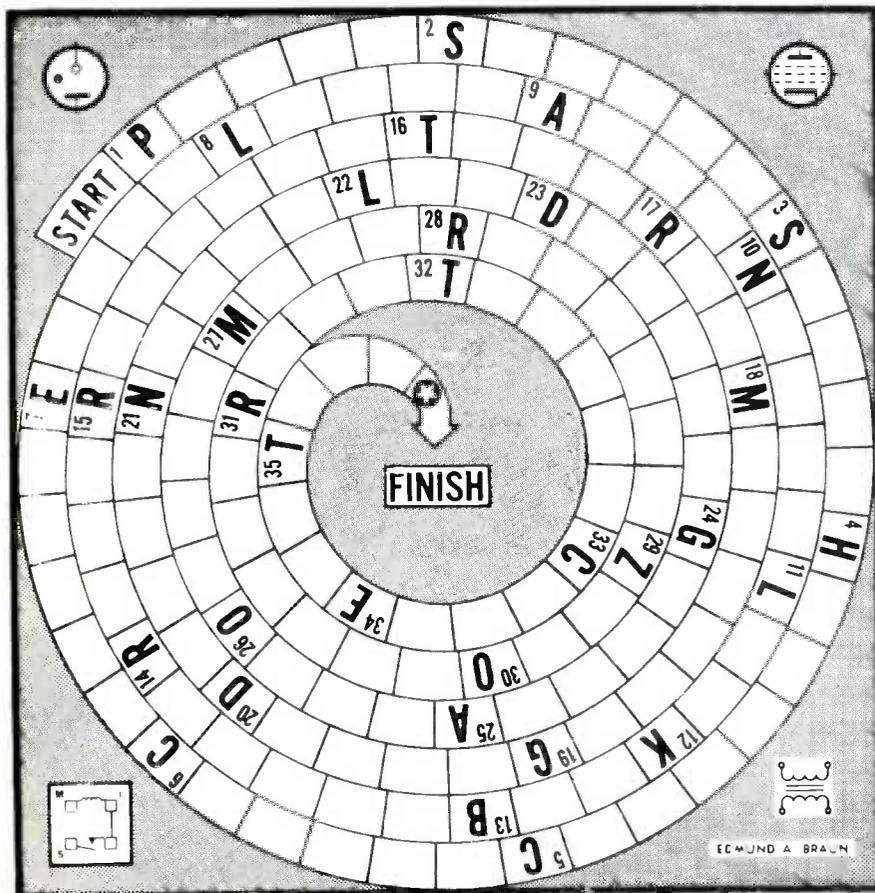

Now turn your attention to the solution on page 48.

5 Easy Steps to Successful TV Repairs

By Terry L. Turner

After servicing TVs for many frustrating years, I've come to the conclusion that a *definite system is essential* for making rapid and successful repairs. Luckily for you, those years of hard work and inspired ideas have shown me the following foolproof system of systems.

Now, you must follow the instructions precisely, and in the proper order. It also might help to keep your tongue firmly in your cheek as you do so. Here is the amazing system:

1. Approach the ailing TV with confidence. Swagger up to it with the attitude that you already know all possible defects, and you're slightly bored because you've done the same thing time after time.

2. Determine the nature of the problem. This can best be accomplished by: (A) asking the customer; (B) consulting your horoscope; (C) consulting the customer's horoscope (B and C are known to us experts as "scoping the set"); (D) or, as a last resort, turning on the power and examining the chassis.

3. Find the solution. After you've determined the nature of the problem, you must think of a solution. Remove the back of the TV and look to see if all those little glass bulbs are glowing. Of course, if the set is one of those newfangled models with solid-state, then proceed to step 3A.

3A. Use double talk. Tell the customer that his framus is shot, and probably he needs a new clavicle. This, of course, means nothing, but it sure impresses the heck out of people, who are awed by this massive display of knowledge. Your purpose for the diversion is to obtain permission to cart the set back to the shop. Who knows, maybe your wife again will point a finger toward a resistor, saying, "Those blue and purple stripes on that firecracker sure clash!" Naturally, that component will be the one giving all the trouble. Right?






4. **Make the repair.** If the repair is to be completed in the home, perform it with the flair of an artist. Pick up a screwdriver by the blade, flip it once or twice in the air, and catch it by the handle. (Note: don't reverse those instructions.) This provides a good show for the kiddies of the home, and makes for good customer relations. Of course, avoid throwing the screwdriver too hard so it sticks in the ceiling or one of the kiddies. Sometimes this curdles the customer relations.

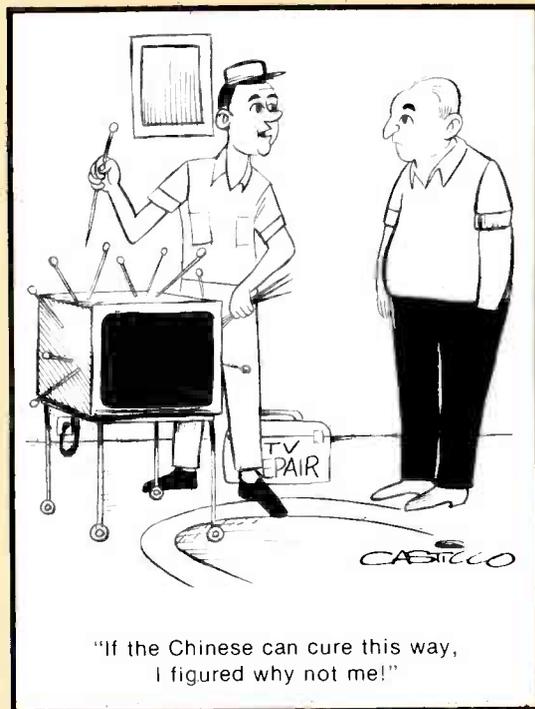5. **Present the bill.** You've now reached the most crucial and dangerous stage of the repair: collecting for the work. This is the time when many technicians cringe behind their color-bar generators. Fear not, TV tech, you are protected by "the system." (Note: if you are more than seven feet tall, and your hobby is ripping telephone books in half, then skip over to the actual presentation.) For the rest of us ordinary mortals, the procedure is simple. Use diplomacy. Look the customer straight in the eye and clearly quote the total price. Watch for a reaction, for your next move depends on the reaction. If he stares at you with glassy eyes and with his mouth hanging open, call for medical aid immediately; he's gone into shock. But, if the veins in his neck stand out, his face turns red, and small wisps of smoke drift up from his collar, prepare to defend yourself. *He's going to kill you!* On the other hand, if he nods slightly, and reaches for his wallet or checkbook, congratulate yourself. You have just completed the five steps and gotten paid for your knowledge and labor.

These five steps are all you need to know about TV repair. If, after studying these simple steps, you believe they will help you in your own business, I'd like to talk to you about some nice land in Florida, overlooking a beautiful swamp, that I've been trying to give away....er, sell. □



The picture tube is the "end of the line" for many signals and voltages, such as video, -Y chroma signals, screen voltages, focus voltage, and high voltage. Therefore, it's not surprising to learn of the many varied symptoms produced by defects in those circuits. Also, such chassis defects can mimic some picture-tube defects.

Picture-Tube Voltages...

the cause of many problems

by Paul Shih

Picture-Tube Problems

All of the principal voltages and signals of color-TV receivers are designed to reach the picture tube. Therefore, this area is noted for the wide variety of problems and malfunctions that can occur there. If we were forced to check each of these with instruments, every repair would require an excessive amount of time. Luckily, it's usually possible to analyze the appearance of the TV screen, thereby learning enough about the problem that we can limit the number of stages needing detailed testing.

The sweep circuits and high voltage will not be discussed here; those are subjects needing a different approach. Instead, the voltages and signals that are applied to the base sockets of picture tubes will be studied.

Symptoms

Typical symptoms of problems caused by wrong voltages and signals that are applied to the base of the picture tube include: wrong

or intermittent gray-scale tracking; wrong color hues or missing colors; and, excessive or dim brightness.

It might surprise you to learn that many other symptoms can begin here, including: low contrast and color saturation; loss of high voltage; elimination of the raster; color without video; and, excessive blooming. The conditions tend to be highly intermittent, and this complicates the analysis and testing.

Chassis Or Picture Tube?

Most of these visible symptoms result from defects in the chassis circuits, although a few can appear to be caused by a bad picture tube. Now, it's embarrassing, as well as damaging to your technical reputation, to have the same problem symptoms remain even after you have changed to a new picture tube. Therefore, we need definite tests to prove whether the chassis or the tube is at fault.

Although we will attempt to provide examples of most basic

problems, your best source of information and inspiration is your own knowledge of how these circuits operate. We might term this as "theory in action."

Matrixing Inside The Picture Tube

Figure 1 shows the partial schematic of a typical tube-equipped color receiver. A control provides DC voltages ranging from B+ to B-boost for each of the three screen grids. Each control grid is fed by the amplified -Y chroma signal from a demodulator. In addition, a positive DC voltage is applied to each grid, often by a resistor and coupling capacitor in parallel, from the plate of the -Y amplifier. The correct -Y signal is necessary for normal colors; while the correct and *unvarying* DC voltage is essential for maintaining the desired B&W screen color.

Video signals (with pots to allow variation of amplitude) are applied to the three picture-tube cathodes. Now, the circuit would operate if

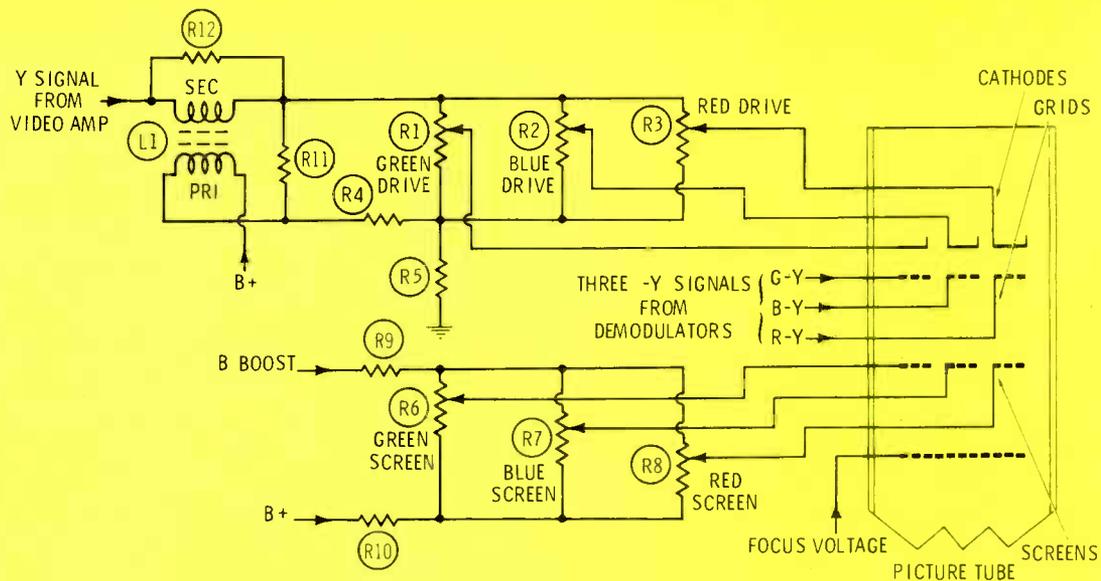


Figure 1 Almost all tube-equipped color receivers matrixed the video (Y) and chroma (-Y) signals inside the picture tube, as shown. The precise DC voltages at the control grids, screen grids, and cathodes affect the brightness or gray-scale screen color and tracking. An open in the

primary winding of L1 causes excessive gun currents which kill the high voltage instantly. When the secondary of L1 opens, the contrast is reduced, white parts of the picture are compressed, and the brightness changes too easily, causing blooming.

the three cathodes were fed the same amplitude. But better tracking can be obtained when they are independently adjusted. However, the same waveform of video goes to all three cathodes.

Matrixing of the color and B&W video signals occurs inside the picture tube. Remember that **any picture tube is only a specialized type of tube**. In grounded grid (or grounded base) amplifiers, the input signal goes to the cathode (or emitter, with transistors). Although the impedance is lower and the output phase is reversed, amplification still occurs. (In color TVs, the phase reversal is cancelled by a previous phase reversal in the video circuit.) So it is with picture tubes; both the grid (chroma) signal and the video cathode signal affect the total electron current, and matrixing therefore occurs in the electron stream.

Take special note of this principle: a specific change of grid voltage affects the electron current exactly the same (although in

reverse fashion) as the same change of cathode voltage. In other words, a 10-volt increase of grid voltage increases the tube current exactly the same as a 10-volt decrease of cathode voltage does.

Effects Of Bias Changes

True bias of a picture tube is the *instantaneous difference* in the voltages at each grid and its corresponding cathode; this includes both DC and AC voltages. Usually we measure the grid and cathode voltages *to ground*, and this requires subtraction of the positive grid voltage from the positive cathode voltage to give the negative grid bias. A more direct method is to measure between grid and cathode.

A DC bias change to just one gun (and no change of the other two biases) **shifts the gray-scale tracking**, and gives a red, blue, or green tint to a B&W picture.

An identical bias change to all three guns shifts the brightness, but maintains the balance of color and

B&W signals. Of course, almost all TVs vary the brightness deliberately by changing the video DC level, and this change goes through the video stages to the cathodes of the picture tube.

Sometimes we forget that changes of CRT grid voltage can vary *either* the screen color or the overall brightness.

Brightness is affected also by the exact screen voltage of each gun. Increasing the positive voltage at one screen does increase the gun current and brightness of that gun (although the brightness difference per volt of change is less than for grids or cathodes). Erratic screen controls have been known to cause mysterious changes of screen color.

Next, we'll give some examples of troubles in circuits similar to Figure 1.

Low Color Saturation

Away back about 1963, one model of color receiver often seemed to have an insufficient or barely-sufficient amount of color.

continued on page 30

Picture Tube

continued from page 29

In many cases, the solution was simple: just decrease the screen voltages and retrack the B&W screen color.

You see, **brightness alone is not enough.** The beams must be modulated from full intensity to complete cutoff. This is one aspect of **contrast.**

Perhaps the idea of *visible contrast* on the screen of a picture tube being affected by the various DC voltages has not occurred to you before. But, it's true.

Think of the picture tube as if it were a small pentode audio tube. **When the grid bias is highly negative** and almost has the plate current cut off, we find that **the screen-grid voltage affects the current more** than a proportionate change of bias. (This corresponds to **low brightness with a picture tube.**)

On the other hand, **when the negative grid bias is low** and the plate current is high, the precise screen voltage is not critical, and **the bias affects the plate current more.** (This corresponds to **high brightness with a picture tube.**)

After we digest these facts, we

can sum up the conclusion by saying: less swing of the bias is required to vary the plate current when the screen-grid voltage is low. When applied to picture tubes, the conclusion is: **a low screen-grid voltage increases the contrast.**

Of course, decreases of screen voltage can be carried too far. Picture tubes have better beam focus, and thus a sharper picture at high brightness, when the screen voltages are high.

Blank Raster

When the brightness was turned down, the action was normal until the picture became moderately bright. But, when the control was turned for *less* brightness, the B&W picture gradually disappeared, leaving just a **blank dim raster with bright vertical-retrace lines.** (Circuits similar to Figure 1 will show color when it's turned up. Pre-CRT matrixing circuits, as in Figure 2, lose both color and video.)

The cause of this symptom usually is excessive screen voltages. Here's how it happens: higher screen voltages require that the

cathode voltages become more positive than usual to cut off the guns and give a black raster. Unfortunately, this higher picture-tube cathode voltage can be obtained only by applying more negative grid bias to the video-output tube, in turn increasing the plate voltage, which is coupled to the CRT cathodes. However, as the bias approaches cutoff, the tube amplification decreases, finally reaching a point of no output. Even then, the CRT cathode voltages are not positive enough for a black raster, so the screen shows a blank dim raster with vertical retrace lines (because the blanking of the video has been lost).

The solution is easy; merely **retrack the gray-scale, after reducing all three screen controls.** Incidentally, this problem often occurs after a technician has attempted to adjust the raster color without doing the whole procedure for gray-scale tracking. Or, perhaps he had adjusted the screens to the top in an effort to brighten a raster that was too dim because of a parts defect, then he forgot to reset the

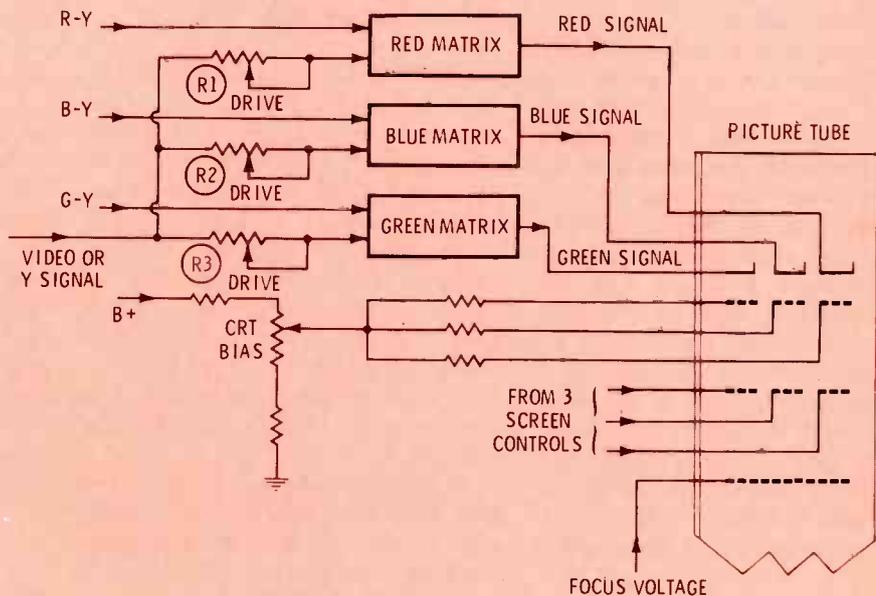


Figure 2 Many solid-state color sets matrix the video and chroma signals in power-amplifier stages that drive the CRT cathodes.

screens following the repair.

The only component in Figure 1 that can cause the same symptoms is an open in R10, which gives the same effect as misadjusted screen controls.

A B&W Picture Has Areas In Color

When some areas of a B&W picture (or a colorcast with the color turned down) show weak and wrong colors, check the drive controls for opens, and test for heater-to-cathode shorts in the picture tube.

Examine Figure 1, and imagine an open at the high end of R1, the green drive control. The green gun would have minimum video, while the blue and red usually have settings near maximum. DC bias of the green gun is not affected much (R4 and R5 are supposed to apply about the same DC voltage to the bottom of the drive controls as is applied to the top by the video circuit). Therefore, the bright highlights of the picture would have full current from the blue and red guns, but only partial current from the green gun. This makes the highlights magenta, and the lowlights are cyan.

Now, imagine a short between heater and the red cathode, when the red drive control is operated at maximum. The heater of the picture tube has a positive voltage applied to it (to minimize such H-K shorts), and it is bypassed to ground. Therefore, the red cathode now is bypassed to ground with a 0.1 microfarad capacitor, which removes all of the video from the red cathode. But that's not all. Since the red drive is at maximum, the video is removed from all three cathodes. The picture has only the chroma signals, which appear almost normal, except the picture is very blurred.

Not all H-K shorts remove all of the video. Imagine a short between heater and the blue cathode, when the blue drive control is adjusted about in the center. All of the blue video is eliminated, but the DC remains about the same. The video to the red and green cathodes is blurred slightly, but neither the sharpness nor the amplitude is

noticeably different. However, the picture has yellowish highlights (red plus green) and blue lowlights with a B&W picture.

Although these shorts and opens also affect the color reproduction, the color degradation is more subtle. Therefore, I strongly recommend turning down the color at the beginning of your diagnosis, any

time there is any suspicion of similar defects.


No High Voltage

Excessive high-voltage current through the picture tube can load down the sweep circuit and kill the high voltage. A common occurrence in some models is an open (often

continued on page 32

NEW FROM LEADER

The 20MHz Dual Trace Scope.

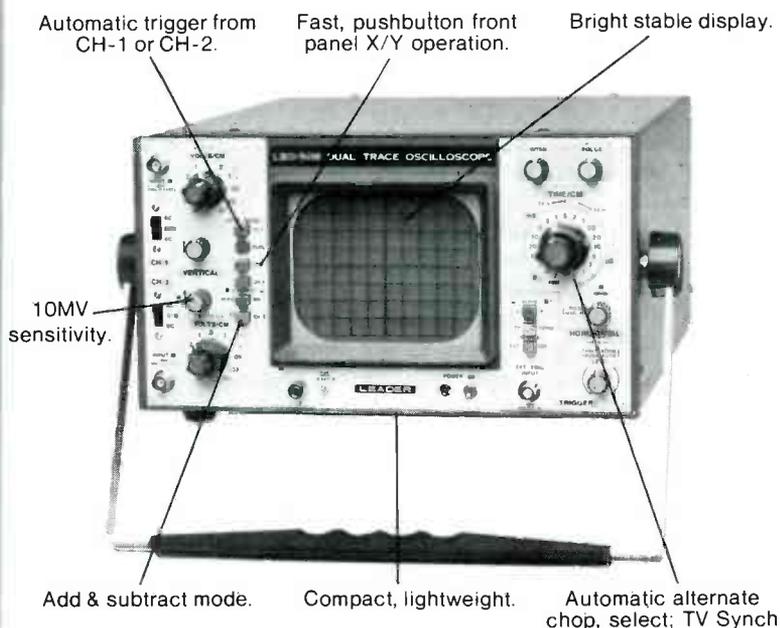

Faster. Brighter. More Versatile. Economical.

Model LBO-508. . . . \$689.95 with accessories
See your distributor or write direct for details.


151 Dupont Street, Plainview, N.Y. 11803
(516) 822-9300
In Canada: Omnitronix Ltd. Montreal Quebec

When Quality Counts . . .

LEADER
Instruments Corp.

For More Details Circle (15) on Reply Card

Figure 3 The Sony Trinitron has only one gun, one grid, and one screen (or G2), but there are three cathodes.

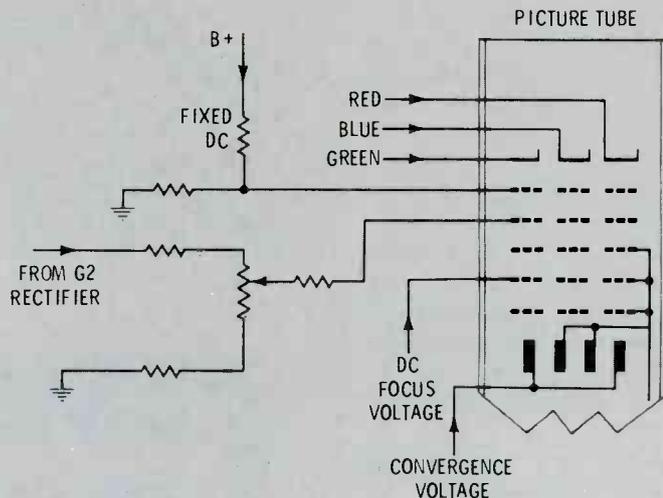

Picture Tube

continued from page 31

intermittent) in the primary winding of peaking coil L1 in Figure 1.

Notice that all of the DC voltage for the video plate comes through the coil, including the balancing DC voltage at the bottom of the drives. Therefore, **an open L1 reduces all three cathode voltages almost to zero**. At the same time the three grids might have between +120 to +170 volts. In other words, the picture-tube bias is *positive* by more than 100 volts! Of course, the guns draw a huge current for a split second before the overload kills the HV.

In intermittent cases, the HV leaves so rapidly that the screen gives absolutely no clue. Either the picture is there, or the raster is black; there is no sign of any blooming in between those two conditions.

Your best bet to find such an open coil winding is to check the DC voltages, starting with the picture-tube cathodes and working back to the resistors and the peaking coil. Ohmmeter tests are not very reliable when the open is intermittent.

Focus Voltage

Color picture tubes that require between 4 KV and 6 KV of focus voltage will not show a raster if the focus voltage is missing. In con-

trast, the low-voltage-focus tubes (requiring between zero to several hundred volts) show a bright raster and picture even with zero focus voltage (of course, the raster lines might be blurred). Check the schematic voltages to determine which type is used.

So, add **"missing focus voltage" to your list of things causing loss of raster**.

Incidentally, I have encountered several cases of out-of-focus pictures where all components of the focus system were normal. All of these circuits used a separate focus rectifier (either a tube or a diode). One case is vivid in my mind. I used a HV probe to monitor the focus voltage, and found the voltage to be **too high**. What's more, **adjustment of the focus transformer did not change the focus voltage at all**. After some time, I assumed the extra voltage was coming from inside the picture tube, probably from the mask or other internal parts that connect to the high voltage. This was proved by disconnecting the focus wire and finding the same voltage there. While the wire was not connected, I grounded it a couple of times until no spark could be seen. When the circuit was restored, the focus-transformer adjustment worked correctly, and good focus was obtained.

Apparently, the leakage voltage was higher than the voltage from the focus rectifier; therefore, the diode was reverse biased and could not conduct. That's why the focus transformer could not change the focus voltage.

Comments

Before we leave Figure 1, we need these facts:

- A malfunction that changes the DC voltage at the output of *one* of the -Y amplifiers, shifts the gray-scale B&W screen color. Such defects are more common than are bad parts in the drive-control circuitry. Therefore, a good tip for cases of wrong B&W raster color is **to check the components and voltages of the -Y amplifier stages**. In rare instances, an open or erratic CRT screen control can upset the balance of colors in the raster.
- Insufficient or excessive brightness can be caused either in the -Y amplifier stages (perhaps a blanker defect, or a supply voltage failure) or in the video-amplifier stages. The latter is more likely. Therefore, **first check the video stages and DC voltages for the cause of wrong brightness**.

Some exceptions have been given already, but these tips emphasize the most-likely causes of the problems.

Pre-CRT Matrixing

Many of the newer solid-state television receivers matrix the video and -Y chroma signals, and amplify them before the pure red, blue, and green signals reach the picture tube (usually to the three cathodes, as shown in Figure 2). Some models have an adjustable voltage fed to all three control grids in parallel; others apply a fixed voltage to all three.

All variations have video-drive controls and individual screen controls. The drive controls do two things. Lower resistance of a drive control applies increased video to the matrixing transistor. Also, most circuits feed the chroma -Y signals to the base of a power transistor, while the video is supplied to the emitter of the same transistor. So, decreasing the drive resistance reduces the emitter-to-ground voltage (which is an increase of forward bias). The increased bias lowers the collector voltage (connected to the corresponding CRT cathode), and increases the brightness of that one color. **Both the brightness and contrast are increased.**

In systems of this kind, the drive controls are used for best tracking of highlights (brightest parts of the picture), and the screen controls of the picture tube are adjusted for best balance and tracking of the dark parts of the picture (lowlights). Usually the screens are adjusted while the vertical sweep is eliminated. This represents gun currents that are much less than those giving near-black areas, and provides extreme accuracy and speed.

Comments

Most of the troubles previously discussed also apply to the pre-CRT matrixing circuits. However, the three paralleled grids stop any possibility of a single grid-voltage shift changing the raster color. Video defects are the most likely source of brightness problems.

Trinitron

Figure 3 shows the base wiring of Trinitron single-gun picture tubes. Although the theory, construction, and operation of these tubes are very different from the others, the CRT base wiring is similar. Of course, the single-gun type requires only one control-grid voltage, and

one screen-grid voltage.

Therefore, both the control grid and the screen grid voltages can affect the brightness, but not the B&W screen color.

Case History #1

Two examples showing how circuit problems can be mistaken for a bad picture tube are presented next.

Symptoms

The picture on the TV that had an RCA CTC36M chassis was badly out of focus, and the colors were pale. "Bad picture tube" was the snap diagnosis. But I spoke too soon, for tube-tester checks showed the emissions of the guns to be acceptable.

During additional tests, I noticed that the high voltage and focus

continued on page 34



**TECH-WICK®
TOOL FOR FAST
PINPOINT DESOLDERING**

No burned fingers. No electrical shock.

AT LONG LAST . . . a hand-held desoldering tool that's safer, more accurate AND has superior absorption capacity. The unique patented design of the heat-resistant plastic dispenser makes TECH-WICK® TOOL a true tool—allowing steady pin-point positioning of the wick on the connection to be desoldered—without the hazard of burned fingers or electrical shock. TECH-WICK® is constructed of fine strands of pure copper treated with non-conductive, non-corrosive rosin flux. The stranded wick contains more voids to absorb the molten solder faster. Send for data sheet and name of your nearest distributor.

**MOHAWK
WHOLESALE & EQUIPMENT CO.**
Marketing Agent
P.O. BOX 4490, YUMA, AZ 85364
PHONE (602) 782-4313

No. S-16
Ten feet of #16 Ga.
wick O.D. .064
Ideal for larger
connections
\$2.75 ea.

No. R-20
Twenty feet of #20
Ga. wick O.D. .040
Ideal for small and
mini connections
\$3.75 ea.

Stranded
pure copper
wick

For More Details Circle (16) on Reply Card

Picture Tube

continued from page 33

voltage became erratic at normal-to-high brightness, but were okay at low brightness. Also, each grid of the picture tube measured about 20 volts DC too high. The reduced CRT bias voltages allowed the guns to draw excessive current, and the high current was loading down the high voltage, causing poor focusing and a small amount of blooming.

Repairs

After I gave up the idea of a picture-tube defect, I located the cause of the problem within a reasonable time. **The blanker tube (V19B in Figure 4) was weak and gassy.**

Circuit operation

Many techs are mixed up about the operation of the blanker stage in the CTC36. One false belief is that the diode (X18 in Figure 4) passes the negative-going pulses from the plate of V15A to the picture-tube grid. That seems logical, since the tube is usually called a "horizontal-blanking" tube, and negative pulses to the grid of a

picture tube *would* produce blanking. Unfortunately, it just isn't so. Of course, the sharing of a common cathode resistor (R159) with the chroma-bandpass amplifier tube *does* blank out the burst from the chroma signal. But no pulses reach the CRT grids.

Here's the correct operation:

- Resistor R186 tries to charge coupling capacitor C119 (and the grid of the picture tube) to the full +280 volts coming from the power supply;
- Opposing this climb to the supply voltage are the negative-going pulses from the plate of V15A. During the time of each pulse, the cathode of X18 becomes more negative than the anode. When that happens, the diode conducts, clamping the CRT grid voltage (and the charge in C119) to the instantaneous voltage at the tip of the pulse. Let's assume a 180-volt-peak pulse, which would set the tip at +100 volts. Therefore, the CRT-grid end of C119 would be charged to +100 volts;
- Between pulses, X18 opens, and

the voltage through R186 adds to the charge in C119. (Without pulses, it would increase to supply voltage, +280 volts.) But, the time constant is long, and the charge increases only a volt or two before the next negative pulse arrives at X18, causing clamping again to the tip voltage;

- Therefore, the CRT grid voltage varies only a couple of volts.


Scope waveforms at the picture-tube grids show merely a few volts of ripple, produced by the short conduction times of the diodes. Perhaps it would help if you thought of X18 as a rectifier of the pulses, with C119 acting as the peak-reading capacitor. As you know, series rectifier circuits have a very low amplitude of ripple.

Using diode gating to reset each CRT grid voltage is necessary to prevent a shift of DC voltage because of the non-symmetrical signal waveforms there.

Comments

Failure of the bias diodes is common. But note this: **either an**

Figure 4 A malfunctioning horizontal-blanker stage in an RCA CTC36 gave symptoms of excessive brightness and poor focussing. Study the explanation for the pulses and the operation of X18, X17, and X16, as given in the text.

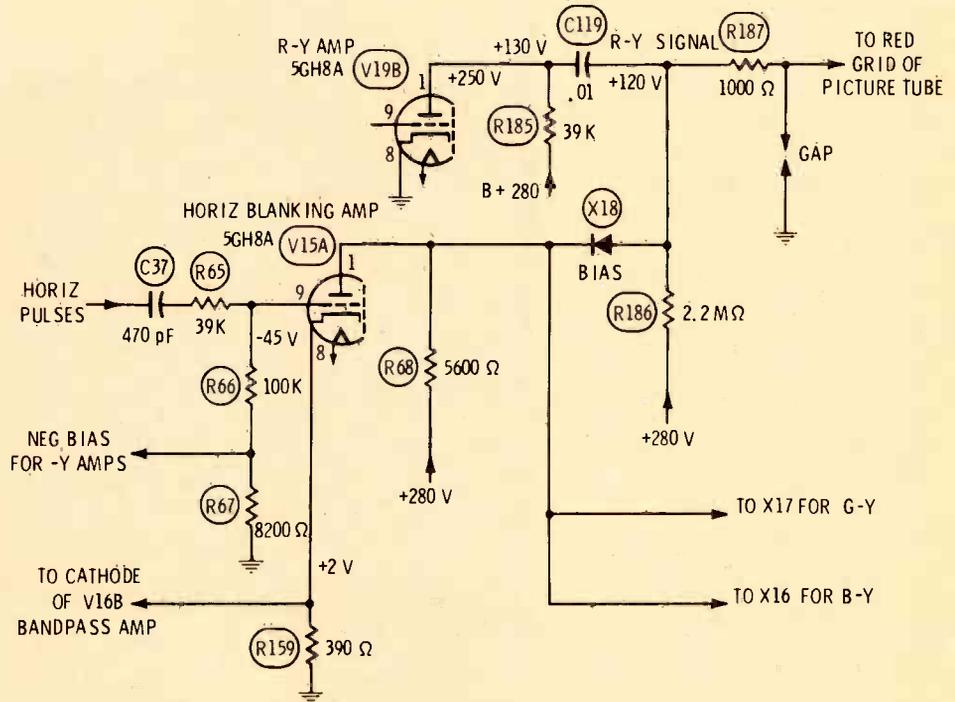

open diode or a leaky one drastically raises the DC voltage of the associated CRT grid. Therefore, the best test is to disconnect one end of any suspected diode and measure forward and reverse resistances by using an ohmmeter.

Case #2

No raster could be obtained on the Zenith that had a 16Z8C50 chassis, for the high voltage measured almost zero. However, the HV would return if the CRT socket was removed from the base, or if the HV lead was disconnected from the picture tube.

Another technician had diagnosed the problem as being caused by a bad picture tube. However, the HV returning when the base socket was removed pointed to wrong bias of the picture tube. Check all the DC voltages at the picture tube to verify such a suspicion.

In this case, none of the CRT cathodes had any appreciable DC voltage, but all of the grids were positive. This proved that the loss of HV was caused by positive grid

bias of the CRT guns.

By a series of voltage and resistance measurements, I found **R76 was burned enough to reduce the resistance, and the 12HL7 tube had a plate-to-suppressor short** (see Figure 5). Replacement of the tube and resistor brought back the high voltage.

Comments

This case history underlines the importance of voltage measurements for proving whether a chassis defect or a bad picture tube is causing the trouble.

Also, many of the CRT base sockets now have several spark gaps internally, to prevent damage to the chassis solid-state components. These spark gaps can become leaky or shorted and simulate a bad picture tube or a defective circuit in the chassis. One quick test is to disconnect the chassis end of the socket metal ground strap, and measure the voltage between the strap and ground, with the receiver in operation. The voltage should be nearly zero. Any reading above zero

is reason to suspect leakage of the spark gaps in the socket.

Suggestions

If the symptoms hint at a possible CRT problem, use a picture-tube tester to check the emission of all guns, and for possible shorts or leakage.

Emission tests should be made before the TV is operated, if possible. Weak guns sometimes drift to increased emission over a period of 15 to 30 minutes, and operation of the TV often obscures these varying emission conditions.

Another indirect test of picture tubes is to operate the TV chassis on a test-jig setup. If your test tube has good brightness and focus, and does not display the malfunction that was present with the chassis operating with its own tube, this is proof the old tube is bad.

Your DC voltmeter and scope (and particularly the DC meter) are the best test equipment to use when the symptoms point toward a wrong signal or DC voltage at the color picture tube. □

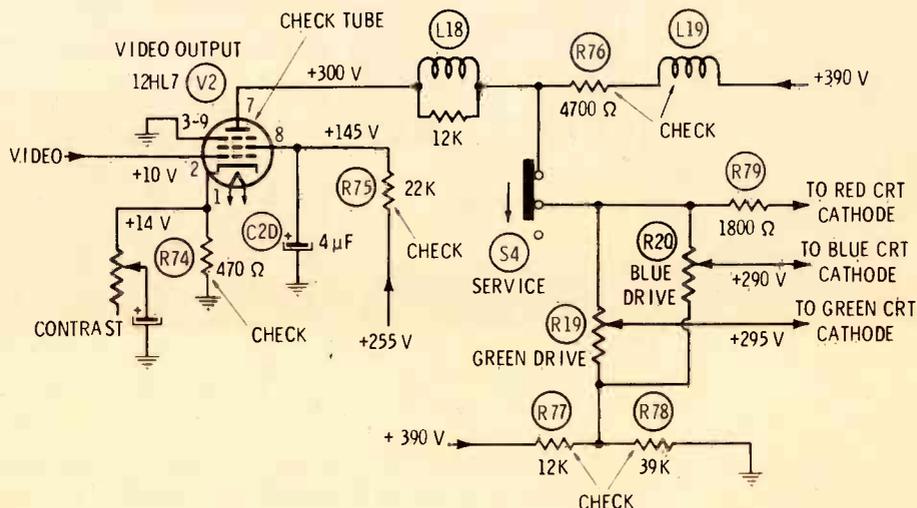


Figure 5 In a Zenith 16Z8C50, excessive gun currents had killed the high voltage. Use DC-voltage analysis to find similar problems.

The Basics of Industrial Electronics, Part 5

By J. A. "Sam" Wilson, CET

Inductance-type passive transducers are analyzed in this concluding coverage of transducers.



Resistive and capacitive types of transducers have been examined in preceding articles. In this part, the subject is transducers which change inductance according to the conditions being monitored.

Properties Of Inductance

Here are two definitions of inductance:

- Inductance of a coil causes it to

oppose any change of current through it. It is the characteristic that forces an inductor to oppose or impede the flow of alternating current.

- Inductance of a coil enables it to store energy in the form of a magnetic field.

An inductor or coil operates by the magnetic field that surrounds the conductor of a current, so any

change of field strength affects the operation of the inductor.

Inductive reactance

The opposition of a coil to the flow of alternating current is called **inductive reactance** (X_L), and it is expressed in ohms.

Mathematically, $X_L = 2 \pi FL$. Therefore, the inductive reactance increases from an increase of fre-

quency (F) and/or the increase of inductance (L).

With inductive transducers, the varying reactance of the inductor determines the amount of circuit current, according to the condition of the material being sensed. In other words, a change of the condition that's being monitored produces a corresponding change of the reactance, and it in turn modifies the amount of current in the control circuit.

Effect Of Cores

An iron core inserted into a coil (see Figure 1) produces an increase of inductance and inductive reactance. In practice, the core must be laminated or made of powdered iron to minimize the core losses at high frequencies, but this does not alter the basic principle. (In Figure 1, the term "soft iron" refers to iron that cannot permanently hold magnetism.)

Position indicator

One practical application of the core principle is shown in Figure 2. When the core is completely inside the coil, the inductance and reactance are maximum. Therefore, the current is low, and is not strong enough to energize the relay. The contact points are in the open position to illuminate the correct-position light.

When the material being monitored is too far to the left, the core is withdrawn from the coil, reducing the inductance and the reactance, which allows increased current. The stronger current energizes the relay, pulling down the contact and illuminating the wrong-position light.

Of course, the change of inductance and reactance is gradual, when the core is moved gradually, but the relay has a snap action so it either is on or off. For other applications, the gradual change of inductance can provide an analog-meter readout of the position or dimension of a work item.

Using a tuning wand

A copper core in a coil decreases the inductance, while a powdered-iron core increases the inductance.

These two actions can be combined in a helpful tool for determining whether an inductance is too small or too large for the best operation of a circuit. The tool is a "tuning wand," illustrated in Figure 3A. As we go through the explanation, remember that the current through

a series-tuned circuit is maximum at the resonant frequency.

In Figure 3B, the resonance of the tuned circuit is below the input frequency; therefore, the alternating current is not maximum, but has an intermediate value. When the copper end of a tuning wand is

continued on page 38

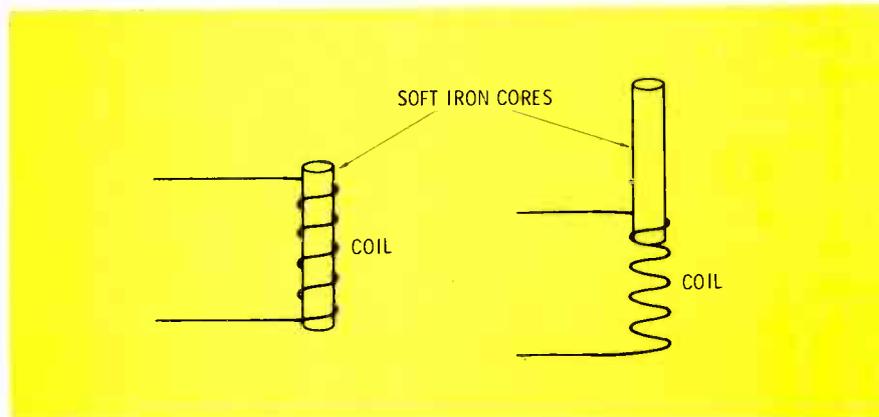


Figure 1 The inductance of a coil is increased by the addition of an iron core. For high-frequency operation, the core should be made of powdered-iron particles held in place by insulating material.


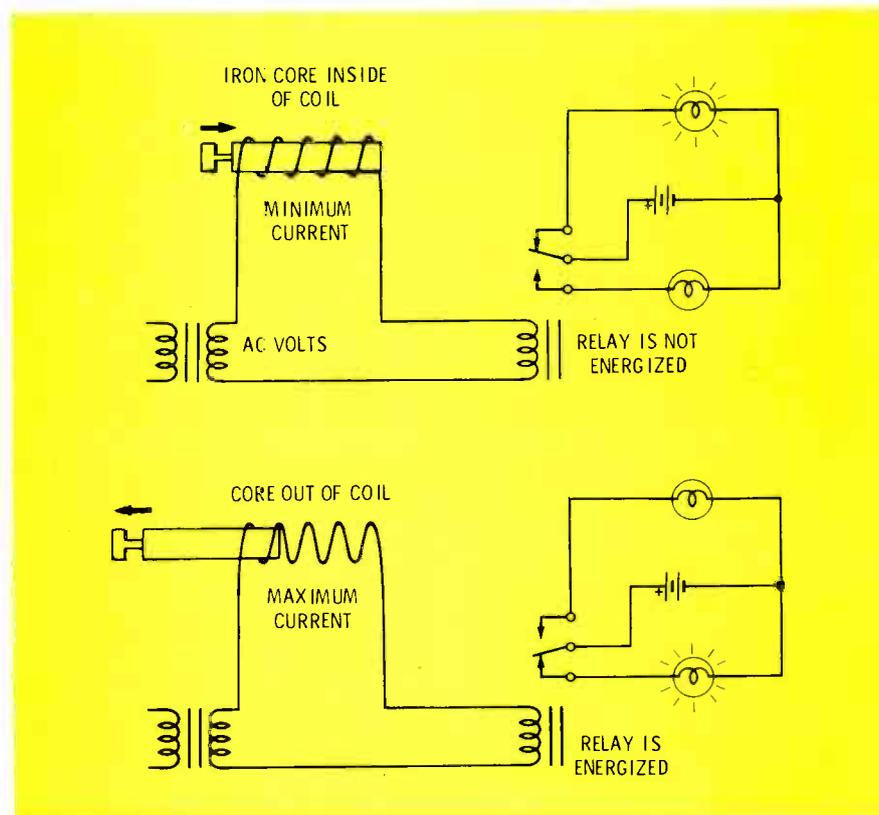


Figure 2 Position of an object can be sensed by connecting it to the core of a coil. (A) When the core is inside the coil, the coil inductance and inductive reactance are high, giving low current which does not trip the relay. (B) Withdrawing the core reduces the inductance, allowing increased current that trips the relay.

Figure 3 A "tuning wand" (A) has one tip of copper and one of iron. (B) Current is less than normal, because the LC circuit resonates below the input frequency. (C) Inserting the copper tip of the wand reduces the coil inductance, raising the resonant point to 100 KHz, and producing maximum current. (D) When the wand iron tip is inserted in the coil, the inductance is increased, lowering the resonant point to 96 KHz, which reduces the current below the original amount.

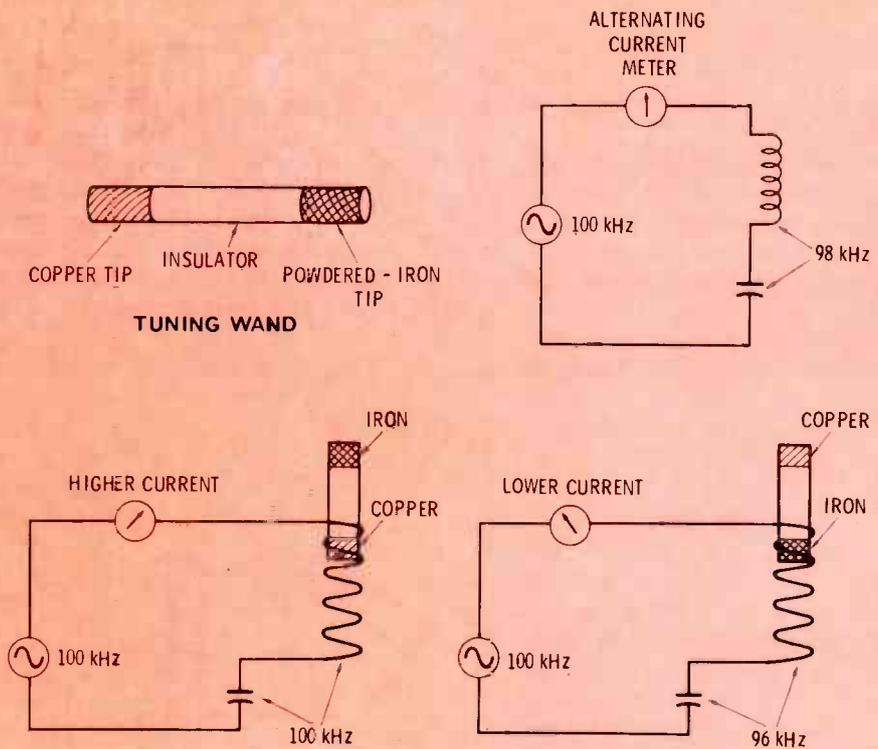

Industrial

continued from page 37

inserted into the coil (Figure 3C) the coil inductance is decreased, raising the resonant point to 100 kHz, and providing maximum current.

Inserting the powdered-iron tip of the wand into the coil (Figure 3D) increases the inductance and lowers the resonance to 96 kHz. This additional mistuning results in a small current.

With parallel-tuned circuits, the signal voltage is monitored as the two tips are inserted in turn. If both tips reduce the signal equally, the tuned circuit is adjusted to the correct frequency. If the copper tip increases the signal level, the frequency of the tuned circuit is too low. Conversely, a signal increase with the iron tip proves the frequency is too high. Of course, the amount of correction by the wand is limited, so no change probably indicates an error that's too large to be helped.

The Effects Of Turns

Additional turns of wire on a coil increase the inductance. In practical devices, it is difficult to vary the

number of turns except by means of a shorting bar (Figure 4). Shorting across three turns of the coil is the same as removing three turns (except for a loading effect when the various turns have tight coupling; a lower load reduces the "Q").

Also, the dimensions and shape of the coil winding affects the inductance. All of the coils of Figure 5 have the same number of

turns, but each has a different inductance. The coil of Figure 5A is used as a standard. When the diameter of the coil form is increased (Figure 5B), but the number of turns and the spacing remains the same, the inductance is increased.

But, if the diameter and number of turns are the same, a wider spacing of the turns on a longer coil form decreases the inductance.

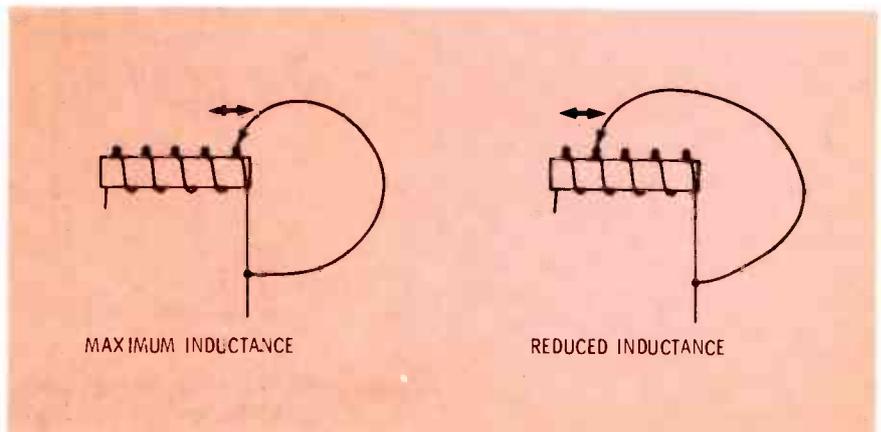


Figure 4 A shorting bar or shorting jumper gives the effect of removing turns from a coil, thus decreasing the inductance.

(Equations for inductance can be simplified by relating the inductance to the core area, rather than to the core diameter. Therefore, it is not necessary to specify the cross-sectional shape of the core.)

Magnetostriction Effect

Magnetostriction refers to the dimension change of magnetic material when it is affected by a magnetic field. The **Joule Effect** is the name given to the change in length of a magnetic material when the magnetic flux through it is varied. Also, there is a reverse effect (called the **Villari Effect**), where a change of dimension of a magnetized material in turn changes the amount of magnetization.

Magnetostriction transducer

Figure 6 shows one practical application of the magnetostrictive effect: a transducer that converts an AC signal into high-energy, high-frequency sound waves. These supersonic sound waves clean dirty components that are immersed in a fluid. They literally shake the dirt loose and into suspension.

Other kinds of supersonic equipment are useful for testing and inspecting specific materials.

Variable-Reluctance Transducers

In diagrams, magnetic field strength usually is represented by flux lines. Stronger fields require more flux lines through a given cross-sectional area.


It is easier to establish flux lines in some materials—such as iron or steel—than it is in many other materials (such as air). **Reluctance** is the name given to the opposition that a material offers to the forming of flux lines.

The elements of magnetic circuits versus electric circuits sometimes are compared as shown in Table 1.

Incidentally, the term "electromotive force" would fit better in the table as a "cause." But the term no longer is in favor. In the new concept, a volt is a unit of **work**, and not a force. As used in science, work is equal to force multiplied by distance. A volt, then, is the amount of work done by

continued on page 40

Save design, troubleshooting and evaluation time with the Fluke Temperature Probe.

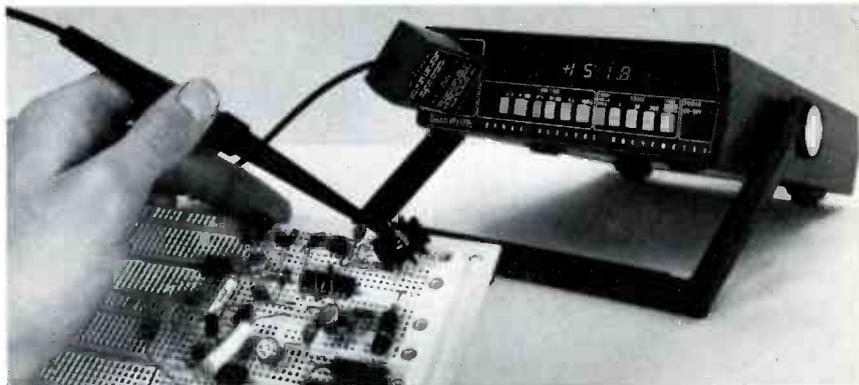

The 80T-150 Temperature Probe can be used with any voltmeter to quickly locate malfunctioning and overstressed components, or to confirm difficult thermal calculations.

The Fluke 80T-150 Temperature Probe easily converts any DVM to a direct reading thermometer (1mV/degree). Range is -50°C to $+150^{\circ}\text{C}$ (or -58°F to $+302^{\circ}\text{F}$), and the probe can be used in surface, air or liquid

applications. Additionally, a 350V standoff allows measurement of live circuits. It is fast responding and battery powered. \$125.*

Call today—800-426-0361 toll-free—and ask for Application Bulletin

AB-28 for information on other ways to make thermal measurements with the 80T-150. Or, write: John Fluke Manufacturing Co., Inc., P.O. Box 43210, Mountlake Terrace, WA 98043.

*U.S. Price Only



1806-7014

For Literature Only Circle (1) On Reply Card

A Heart-Warming Gift for Her...

A bright way for you to save on a four-pack of Perma Power Color-Brites

Save money now on a four-pack of the popular Perma Power C-511 Color-Brite ... while you warm the heart of someone special with the beautiful gold-plated 15" floating heart necklace. Necklaces like this sell in fine stores for \$4.95, but it's yours free with your purchase. Designed by Elsa Pareté, it's a gift that's sure to brighten her day. You'll brighten your day too, as you save more than \$1.00 per Britener, on the Britener you use most often. And your customers will give you heartfelt thanks, because Model C-511 Color-Brite immediately restores sharpness, detail and contrast to faded color picture tubes... defers the need to buy a new picture tube.



PERMA POWER
Electronics Inc.

5615 West Howard Avenue · Chicago, Illinois 60648 · Telephone (312) 647-9414

Offer valid only while supply lasts.
Hurry to your distributor today!

For More Details Circle (17) on Reply Card

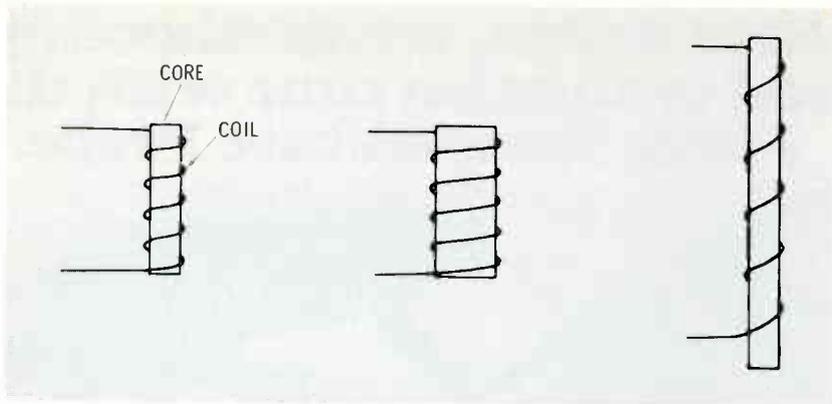


Figure 5 Changing the diameter of the coil winding and changing the spacing between the turns produces a different inductance of a coil.

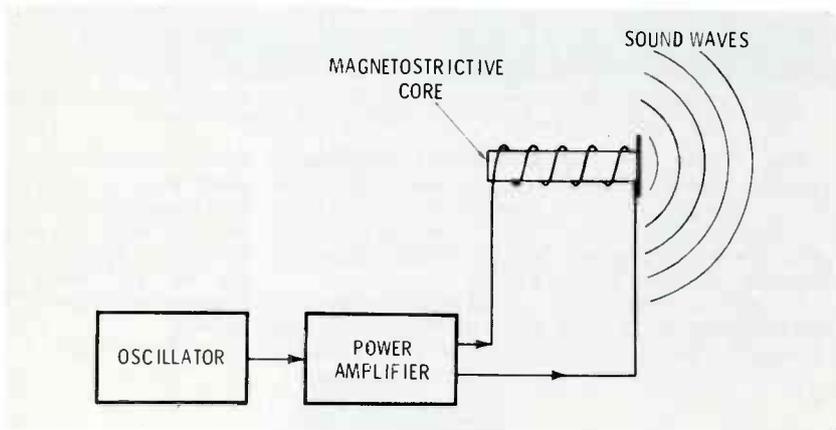


Figure 6 The magnetostrictive effect causes the length of a magnet to vary in step with the AC signal from an amplifier.

Industrial

continued from page 39

moving a unit charge around a defined circuit. Also, to be technically accurate, we must say that magnetomotive force is measured in units of work.

From Table 1, you can conclude correctly that varying the reluctance of a magnetic circuit also varies the flux.


Faraday's Law

Before studying variable-reluctance transducers, we should review the concept of Faraday's Law. It states that relative motion between a conductor and a magnetic field produces a voltage.

Transformers operate under this principle. Changes of primary current produce changes of flux around the secondary winding, which induces a voltage in the winding.

The variable-reluctance transducer of Figure 7 is designed to sense vibration. A DC current in one winding establishes a flux in the soft-iron circuit. When the

Figure 7 This variable-reluctance circuit senses vibration by the movement of a vane in the magnetic path. Position of the vane giving a large gap (A) allows only a small flux to travel around the core. When the vane bridges the gap (B), the flux is increased. Rapid movements of the probe and vane cause fast changes of reluctance and flux, producing an AC signal at the output winding.

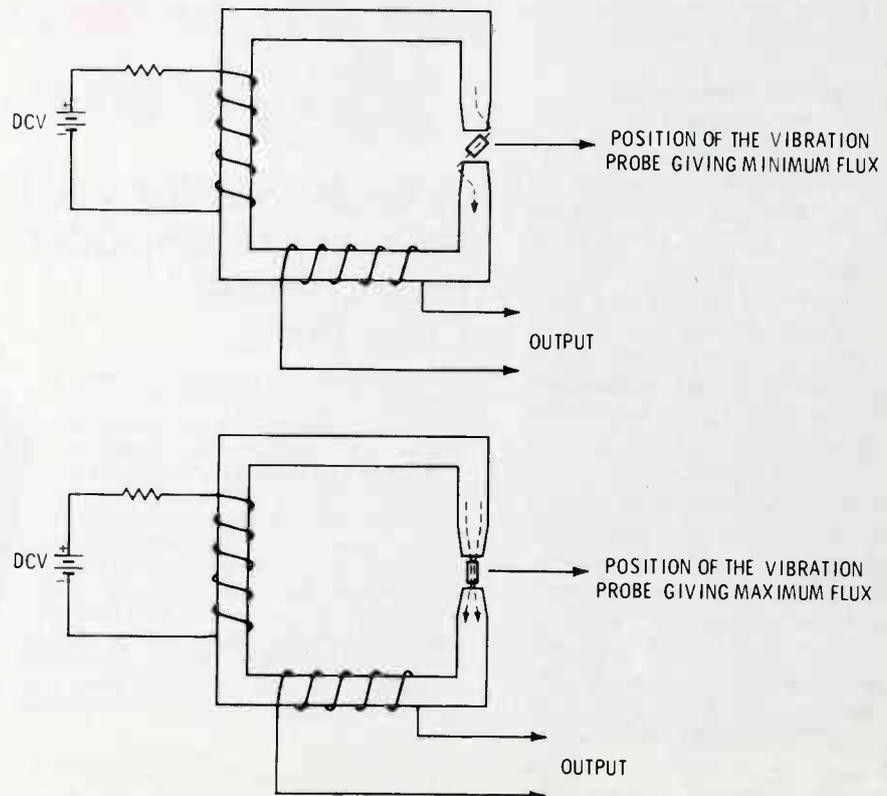

sensor vane is at an angle to the gap (Figure 7A), the flux is at minimum because of the large air space.

Figure 7B shows the vane in line with the gap, allowing maximum flux through the low-resistance path across the small gap. Movements of the vane cause a varying flux, which produces an AC voltage at the output terminals.

Although this is an active transducer—because it emits an output voltage—it is presented because of the variable-reluctance operation.

Also, the principle, with minor modifications, applies to saturable reactors, which are passive components.

Magnetometer

Magnetic fields can be sensed by the magnetometer of Figure 8. Complex versions are used to measure the strengths of magnetic fields accurately.

Here's how it operates: When there is no external magnetic field,

the core of the coil saturates equally on the positive peak and on the negative peak of the signal source. An external magnetic field adds to the coil flux during one half-cycle and subtracts from it on the following half-cycle, producing a change of waveform. Changes of waveform have been exaggerated to demonstrate the point.

Comments

When we elaborate about actual devices used in industrial sensors, one of the important types to be discussed will be the instruments that determine shaft rotation. For example, a magnet can be fastened on a rotating shaft. Each time it passes a coil of wire, a voltage pulse is produced. The repetition rate can be counted directly or it can be read-out on an analog meter. Another variation has the coil wound over a magnet, and the pulse from the coil occurs each time an iron or steel vane passes the coil. □

TABLE 1 Comparison Of Electric And Magnetic Circuits

	Electric Circuit	Magnetic Circuit
Cause	voltage	magnetomotive force
Effect	current	flux
Opposition	resistance	reluctance

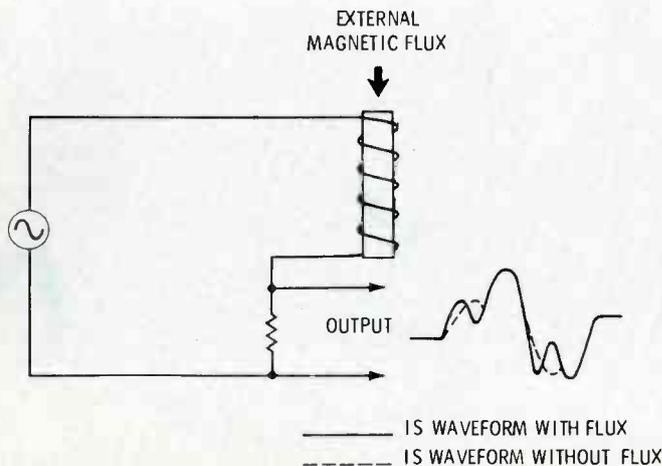


Figure 8 External magnetic fields can be detected by phase and linearity changes of the output signal. The external flux aids one peak of the input AC, but it subtracts from the opposite peak.

Want to cut out a career as a two-way radio technician?

MTI offers the only training for professional FM two-way radio available. Qualified technicians are employed in government, industry, and public service. But training is your key.

You could cut out a career as a two-way radio technician by cutting out this coupon. We'll send you information on how you can learn more about this specialized field, at home.

Name _____
 Address _____
 City _____
 State/Zip _____



formerly

MOTOROLA TRAINING INSTITUTE

Summerdale, Pennsylvania 17093

LL8

For More Details Circle (18) on Reply Card



WE'RE GROWING!

to better represent

YOU

the successful service business operator.

- *Over 2500 firms belong
- *39 State Affiliates
- *167 Local Associations


YOU CAN JOIN!

and learn how to make money and work less hours.

Write today for a membership application and more information.

1715 Expo Lane
 Indianapolis, Indiana 46224
 Phone (317) 241-8172

CARTOON CORNER

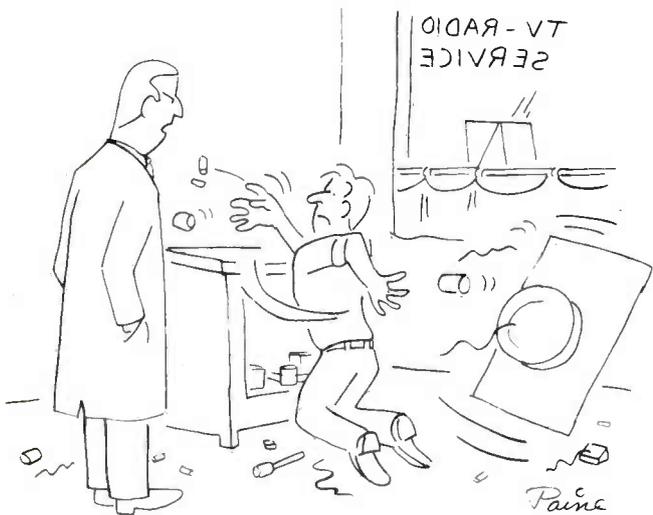

"I can't say that I approve of your troubleshooting methods, Cranby."



"Surely you can find a better way to build a one-second delay into the circuit than to use 186,000 miles of wire."



"I found their trouble. The entire family is color-blind."



"The hard part of this job is trying to keep up with all the advances in the field."

bookreview

Security Electronics

Author: John E. Cunningham
Publisher: Howard W. Sams & Co., Inc., 4300 W. 62nd Street, Indianapolis, Indiana 46268
Size: 192 pages
Price: \$5.95 paperback

This second edition describes the operating principles of electronic security devices and systems, including the technical advances made since the first edition appeared in 1970. Chapters cover: a general description of electronic intrusion alarms; principles of various intrusion detection devices; object detectors; alarm and signalling devices; accessories common to all systems; practical installations; bugging and debugging; and speech-scrambling systems. Completely-new chapters cover: automobile protection; personnel-identification and statement-verification systems; and computers as integral parts of security systems. The text covers the subject in sufficient detail to enable the electronics man to apply his knowledge and experience to the security field.

Electronic Meters: Techniques and Troubleshooting

Author: Miles Ritter-Sanders, Jr.
Publisher: Reston Publishing Company, Inc., Reston, Virginia 22090
Size: 299 pages
Price: \$16.95 hardbound

Purpose of the troubleshooting guide is to bridge the gap between classroom instruction and field or shop hands-on training. The material is suitable for home study, or for junior-college and trade-school classes, and the author assumes that the reader has completed basic training in electronic theory. After a preliminary analysis of typical trouble symptoms, he gives examples of various troubleshooting techniques. The chapters progress from a brief overview of basic meter movements to color television analysis, with an additional chapter about troubleshooting scopes, CCTVs, and fuel-vapor detectors. Quantitative considerations are illustrated, and the use of mathematics has been minimized. This text is a practical guide for testing a variety of modern electronic equipment.

photofactTMbulletin

TRUETONE

Models WEG2769B-87/91C-87/97C-87/99B-871675-2

SHARP

19A73, 19A751691-1

SYLVANIA

Chassis A16-71691-2

CURTIS MATHES

Chassis CMC-571692-1

ZENITH

Chassis 19GB1Z1692-2

CORONADO

TV2-2057A1693-1

QUASAR

Chassis DTS-/ETS-951 (Codes B-00 thru B-03)1693-2

ADMIRAL

Chassis 9M50ET2M (Codes 11 thru 19)1694-1

TRUETONE

SCJ3712A-771694-2

HITACHI

I-601695-1

RCA

Chassis CTC74AD/AF/AM/AN/AT1695-2

Chassis CRK24C, CTP23A/B1695-2-A

MAGNAVOX

Chassis T985-05/-06/-07/-08, T986-061696-1

TEKNIKA

CI-31131696-2

K MART

SKC-1310, SKC-15101697-1

SYLVANIA

Chassis E20-61697-2


MIDLAND

15-023/-0341698-1

RCA

Chassis CTC85A/B/D1698-2

Figure 1. Twelve pushbuttons on the selector panel of the Jerrold TRC-82 TV remote control system can tune in a total of 24 TV channels, when used with the off-VHF-UHF lever switch (at the left). A variable fine-tuning control is provided for those sets that do not have AFT. The UHF channels must be adjusted at the time of installation; a simple process. Only DC-tuning and relay voltages go through the small-diameter 25' cable that connects the pushbutton and converter units.

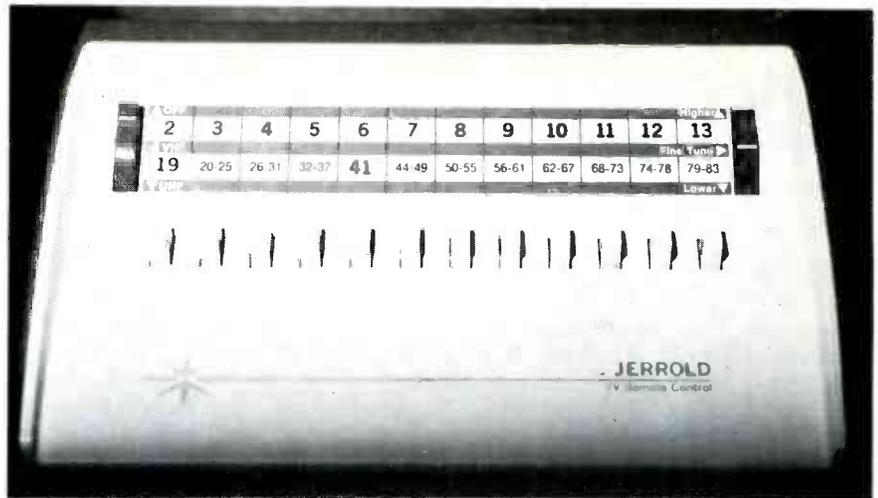

Reports from the test lab

By Carl Baboike, CET

Most of our test-lab reports discuss various items of test equipment. But, this report is about the model TRC-82 all-channel universal remote control system manufactured by Jerrold.

Most remote control systems are designed to be factory-installed in just a few models of each manufacturer's line of television receivers. Older versions were mechanical monsters, requiring several motors and relays, because the tuner and other controls were rotated by the remote mechanism. Modern remote

controls have been improved greatly, and have few or no moving parts. However, even these only work with certain sets. One reason is that the tuning and control functions are accomplished by DC voltages from the remote circuits. Therefore, the remotes and TVs must be designed to work together as complementary units.

Only one brand of remote can be operated with any make or model of color or B&W TV: the Jerrold model TRC-82. Of course, there are a few limitations (such as no control over sound, color, or tint), but the advantages outweigh them.

The Jerrold Remote Control

Model TRC-82 (Figure 1) is the second generation of Jerrold uni-

versal remote control units. The first was model TRC-12, which tuned the 12 VHF channels only, and had 75-ohm input and output impedances. (This model was described starting on page 25 of the January, 1975 issue of **Electronic Servicing**.)


Although the remote control is a converter unit, it operates as an external voltage-tuned varactor tuner, which in effect replaces the original TV tuner. However, the TV tuner is NOT removed or modified. Instead, it is adjusted permanently to channel 3 or channel 4 (Jerrold offers a choice, depending on the channel that is not used in your area), and it becomes the equivalent of the second mixer-oscillator of a double-conversion superheterodyne circuit.

Pushbuttons provide faster and easier station selection, and the button stays down to indicate the channel that's in use. Together, the converter principle plus the pushbuttons give convenience and good performance for remote-control operation with any television receiver.

Other features

Two separate units make up the Jerrold remote-control system. The one with the pushbuttons (Figure 1)

Figure 2. The converter unit usually is placed near the TV receiver. For example, on top of the cabinet, on the floor behind the TV, or fastened to the back of the TV. Power for the TV comes through the converter, and separate VHF and UHF 300-ohm inputs are provided, in addition to provision for 75 ohms.

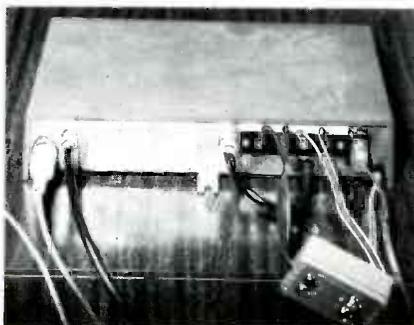

has at the left edge of the panel a combination power on and VHF/UHF selector switch. A relay in the other unit does the actual power switching, so the TV power switch must be left on at all times.

A pointer on the lever knob shows whether VHF or UHF channels will be received. The buttons do double duty. For example, when the lever knob is down in the UHF position, the same button that selects channel 5 on VHF will tune in the assigned UHF station.

All VHF channels have been pre-tuned at the factory, and none in the sample needed a touchup. (Inside the unit are 24 pots for tuning in the 24 possible channels. Any or all can be adjusted, if desired.) Although the buttons are marked for several UHF channels, each should be adjusted for just one active channel. For my tests, the 14-19 button was set for an educational station on channel 19, and the 38-43 button was adjusted for channel 41. A sheet of UHF channel numbers is supplied for installation on the buttons.

At the right edge is a variable fine-tuning knob and control. A white line on the knob shows the nominal position. After the permanent antenna and remote wiring has been installed, you might want to touch up the pots so each channel will be correctly tuned when the white mark of the fine-tuning knob is in line with the arrow. Of course, TV-receiver AFT makes such accuracy unnecessary. If the receiver has AFT, but the users accidentally turn the fine-tuning knob out of the AFT hold-in range too often, you can tape the knob.

The converter-and-power unit (Figure 2) connects to the push-button box by a single small 25-foot cable. No signal voltages, AC voltages, or high DC voltages go through the cable. This new version has a plug and socket on the panel of the converter unit, and extender cables are available.

At the extreme right are the converter power cable, and an AC socket for the TV power cable. The remote power must be on at all times, and the drain is 10 watts.

Output of the converter to the

TV is from an "F" coax socket near the left edge. If the TV tuner can accommodate a 75-ohm connector, the coax can be plugged in directly. Otherwise, a 75/300-ohm matching transformer must be added at the end of the coax cable, for attachment to the receiver 300-ohm-antenna terminals.

A choice of converter input impedances is provided. The "F" connector near the center should be used when a 75-ohm coax cable brings in the input signals. For 300-ohm operation, separate VHF and UHF 300-ohm inputs are furnished (in the picture, an external frequency splitter divides the VHF and UHF frequencies to the proper terminals). Then, the stub of coax that protrudes out of the panel is connected to the input "F" connector.

Comments

In the ES laboratory, we don't have the specialized equipment necessary to check all of the technical specifications of items such as this remote control. There-

fore, the sample unit was installed in a home, operated in typical fashion for several weeks, and the performance and convenience results noted.

The in-home-use tests were done by a family whose color receiver did not have a UHF tuner. No problems were encountered, and the reports were favorable.

In fact, the quality of the color picture was improved by the remote control. Jerrold data indicates a gain of between 4 dB and 11 dB for the entire converter unit, and the extra signal strength can be beneficial to the older receivers.

Only a slight frequency drift was noted on channel 41, and none on VHF. This represents excellent performance.

The "testers" of the Jerrold remote-control system liked the convenience of operation, and appreciated the UHF reception (Figure 3). In fact, although they now have a modern solid-state TV which has both AFT and UHF, they would like to have the remote again. □



Figure 3. Mrs. J. H. Babcoke (my mother) is shown selecting a TV station, with the Jerrold model TRC-82 remote control.



CET — MD

Just a few letters
Spell the difference
That is professionalism

If you are a service technician,
Servicing:

- * TV
- * CB
- * Video
- * Antenna systems
- * Industrial electronics
- * Medical electronics

Don't be
"Just another repairman"
Be a CERTIFIED
ELECTRONICS TECHNICIAN

Write to IS CET for details
On how and where
To take the exam

IS CET - 1715 Expo Lane
Indianapolis, IN 46224
317-241-8172

Solution to

ALL AROUND OHM!

- | | |
|-------------|-------------|
| 1 Panels | 19 Ground |
| 2 Splices | 20 Design |
| 3 Switch | 21 Nickel |
| 4 Harmonic | 22 Lead |
| 5 Ceramic | 23 Damping |
| 6 Console | 24 Galena |
| 7 Enamel | 25 Audio |
| 8 Lambda | 26 Osmium |
| 9 Align | 27 Mylar |
| 10 Normal | 28 Reinartz |
| 11 Link | 29 Zero |
| 12 Knob | 30 Ohmmeter |
| 13 Bifilar | 31 Rivet |
| 14 Radar | 32 Traffic |
| 15 Rheostat | 33 Cable |
| 16 Tower | 34 Emit |
| 17 Ream | 35 Tool |
| 18 Mounting | |

Start with 108 points and deduct
3 points for any part you may
not have answered correctly.

- 66 or less. Ugh.
69-78 Better.
81-93 Good.
96-105 Very good.
108 PERFECT! You can't
do better than that!

test equipment report

Digital Multimeter

A 3½-digit portable digital multimeter has been announced by **B&K-Precision**. The new model 2800 DMM is a full-feature instrument providing a wide range of voltage, current, and resistance measurements.

The 2800 has 22 ranges that measure as high as 1000 volts (AC of DC), or up to 40,000 VDC with optional PR-28 probe. Resolution is 1 millivolt, 1 microampere, or 0.1 ohm. Typical DC accuracy is 1%, and the input impedance is 10 megohm. All ranges are protected against overloads.


The 2800 also features auto-zeroing and 100% overrange reading on all ranges. Overage reading capability allows the user to read to 1999 on a scale normally limited to a maximum reading of 1000, thus reducing frequent range changes.

The new DMM comes complete with test leads, detailed operating manual, and spare fuse. A full range of optional accessories also are available. Suggested retail price is \$99.95.

For More Details Circle (30) on Reply Card

Multicounters

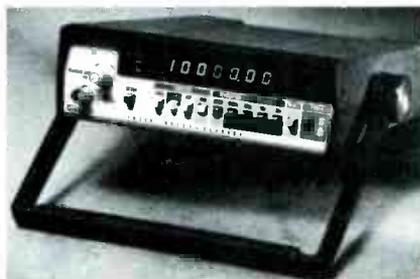John Fluke Company has added two new models to its counter line: the 1910A and 1911A Automatic-Counters.



The 1910A provides a frequency range of 5 Hz to 124 MHz, while the 1911A offers 5 Hz to 250 MHz. Both counters have period, period average, and totalize capability as well as frequency measurement. A trigger-level control and attenuator provide the signal conditioning needed to make accurate measurements in the presence of noise. In addition, the 1911A offers a 50-ohm input impedance from 50 MHz to 250 MHz to allow proper matching for 50-ohm RF applications. The 1910A and 1911A feature 15-mV

sensitivity across the major portion of the input range. Both units use a 7-digit LED display with overflow capability and full units annunciation.

For More Details Circle (31) on Reply Card

Triggered Oscilloscope

VIZ has introduced a high-caliber triggered scope for industrial, educational, research and laboratory applications, as well as for general-purpose service testing.



WO-527A features a special TV line-selector, which permits line-by-line display of video frames. This is an aid in broadcast-transmission monitoring, CATV testing, and servicing television, video-games, and videotape-recording.

The 5-inch scope has a vertical-amplifier frequency response to 15 MHz; the bandwidth of the horizontal amplifier is from DC to 1 MHz. A trigger-level adjustment system uses LEDs to indicate trigger polarity.

For More Details Circle (32) on Reply Card

Directional Wattmeter

Model 4431 from **Bird Electronic** is a "Thru-line" RF directional wattmeter for measuring forward and reflected CW power. It also can supply an adjustable RF sample signal for scope, spectrum analyzer, or frequency counter. This sample signal is adjustable between 15 dB and 70 dB below the main signal.

Power can be measured from 100 milliwatts to 5000 watts between 2 MHz and 30 MHz, or up to 1000 watts between 30 MHz and 1000 MHz, with an accuracy of $\pm 5\%$.

For More Details Circle (33) on Reply Card

These features supplied by the manufacturers are listed at no-charge to them as a service to our readers. If you want factory bulletins, circle the corresponding number on the Reply Card and mail it to us.

antenna systems report

Mobile TV Antenna

RCA's new Mini-State TV antenna system can operate from either a 12-volt DC battery or 120-volt AC house current. The model was designed to provide sharp TV signals for recreational vehicles, vans, and boats.

Other models of the antenna system operate from house current only.



The unidirectional antenna of the Mini-State system can be rotated by a hand-held remote control unit. The UHF-VHF antenna rotates inside a weather-protected polyethylene radome, which also houses a solid-state amplifier, interference filter, and a motor-driven rotator.

The 5MS550 comes with a 30-foot coaxial cable with attached connectors combined with three-wire rotator cable; DC power cord, UHF-VHF antenna matching transformer; a stainless-steel bracket and hardware for outdoor mast mounting; tripod-type legs for indoor use; and an instruction manual. Optional retail price is \$99.95.

For More Details Circle (34) on Reply Card

CB Base-station Antennas

The "Wavemaster" series, six compact ground-plane base-station antennas from Winegard, are engineered for 40-channel operation.

These antennas come in four basic parts, and can be assembled without tools. The units feature twist-lock sockets which hold the radiator and radial elements in place. Gain of the models ranges from 3.5 dB to 5.0 dB.

There are three aluminum models: GA-445, GA-845, and GA-885. The stainless-steel models are: BF-440, BF-840, and BF-880.

For More Details Circle (35) on Reply Card

TVI Filter

Communications Power now has a television interference filter for CB radios that absorbs harmonic emissions rather than reflecting them

where they might cause other interference problems.

The FL-1 filter is said to attenuate all harmonics of 27-MHz carriers by 90 dB, or more, and dissipate up to 10 watts while passing a power of up to 650 watts.


In addition, the TVI filter also serves as an antenna-transceiver matchbox. Input and output tuning controls in the FL-1 filter will match a 3:1 antenna SWR down to 1:1 at 50 ohms. Insertion loss is reduced to only 0.3 dB.

For More Details Circle (36) on Reply Card

Resistor-terminated Plug

A type-N resistor-terminated plug, model 4240, has been developed by ITT Pomona Electronics.

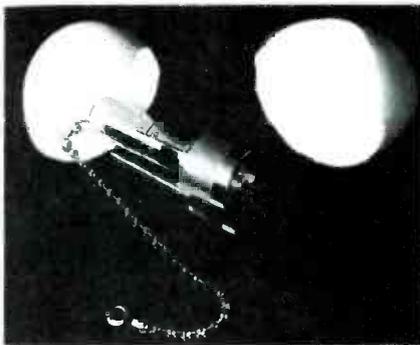The unit, designed for terminating coaxial lines, is available in resistances of 50, 75, 93, 100, and 600 ohms.



It has a 1% 1-watt, deposited-carbon resistor, Teflon insulation, non-tarnish finish, and a gold-plated male contact. The VSWR is 1.15 maximum from DC to 100 MHz.

For More Details Circle (37) on Reply Card

CB Antenna

Wawasee Electronics' "Black Cat" factory-tuned antenna (model JB 100) has a top-loaded coil wound on a fiberglass core, and is covered with a black dielectric sheath to reduce precipitation static.

Model JB 100 is 4-feet long, constructed of resilient fiberglass. Its 3/8 by 24 ferrule is chrome-plated brass.

For More Details Circle (38) on Reply Card

These features supplied by the manufacturers are listed at no-charge to them as a service to our readers. If you want factory bulletins, circle the corresponding number on the Reply Card and mail it to us.

Statement of Ownership, Management and Circulation, Act of August 12, 1970; Section 3685, Title 39, United States Code.

1. Title of publication: Electronic Servicing.
2. Date of Filing: October 13, 1977.
3. Frequency of Issue: Monthly.
4. Location of known office of publication: 9221 Quivira Road, Overland Park, Johnson County, Kansas 66215.
5. Location of the headquarters or general business offices of the publishers: 9221 Quivira Road, Overland Park, Johnson County, Kansas 66215.
6. Names and addresses of publisher and editor: Publisher, Michael D. Kreiter, 9221 Quivira Road, Overland Park, Kansas 66215; Editor, Carl H. Babcoke, 9221 Quivira Road, Overland Park, Kansas 66215.
7. Owner: Howard W. Sams & Co., Inc., 4300 W. 62nd Street, Indianapolis, Indiana—a wholly owned subsidiary of International Telephone and Telegraph Corporation, 320 Park Ave., New York, NY 10022.

8. Known bondholders, mortgagees, and other security holders owning or holding 1 percent or more of total amount of bonds, mortgages or other securities: None.

9. Paragraphs 7 and 8 include, in cases where the stockholders or security holder appears upon the books of the company as trustee or in any other fiduciary relation, the name of the person or corporation for whom such trustee is acting, also the statements in the two paragraphs show the affiant's full knowledge and belief as to the circumstances and conditions under which stockholders and security holders who do not appear upon the books of the company as trustees, hold stock and securities in a capacity other than that of a bona fide owner. Names and addresses of individuals who are stockholders of a corporation which itself is a stockholder or holder of bonds, mortgages or other securities of the publishing corporation have been included in paragraphs 7 and 8 when the interests of such individuals are equivalent to 1 percent or more of the total amount of the stock or securities of the publishing corporation.

10. This item must be completed for all publications except those which do not carry advertising other than the publisher's own and which are named in sections 132.231, 132.232 and 132.233 postal manual (Sections 4355a, 4355b and 4356 of Title 39, United States Code).

	Average No. Copies Each Issue During Preceding 12 Months	Single Issue Nearest To Filing Date
A. Total No. Copies Printed (Net Press Run)	71,578	64,651
B. Paid Circulation		
1. Sales through dealers and carriers, street vendors and counter sales	3,223	1,859
2. Mail subscriptions	64,035	61,387
C. Total Paid Circulation	67,258	63,246
D. Free Distribution (including samples) by Mail, Carrier or Other Means	1,371	623
E. Total Distribution (sum of C and D)	68,629	63,869
F. Office Use, Left-Over, Unaccounted, Spoiled after Printing	2,949	782
G. Total (sum of E and F—should equal net press run shown in A)	71,578	64,651

I certify that the statements made by me above are correct.

MICHAEL D. KREITER
Publisher

Digital CB Transceiver

A digital-logic 40-channel SSB/AM CB transceiver now is available from **Communications Power**.



The CP-400 includes a high-power JFET mixer that minimizes overloading and intermodulation problems; a built-in logarithmic speech compressor for the power microphone; and an eight-pole crystal filter that provides adjacent channel rejection of -80 dB for both SSB and AM.

For More Details Circle (39) on Reply Card

Electronic Tools

A new "troubleshooters" tool kit for field engineers and electronic technicians is available from **Jensen Tools and Alloys**.

The kit (JTK-81) contains more than 25 tools, including pliers, cutters, screwdrivers, nutdrivers, wire strippers, hex and spline keys, soldering equipment, and hammer. The tools come in a multi-pocketed 12"x21" vinyl-covered roll pouch. A Triplett 310 VOM meter is offered as an optional accessory.



The kit without meter is priced at \$75. With meter, the price is \$127. Quantity prices are lower.

For More Details Circle (40) on Reply Card

TV Theft Alarm

The H1 TV Theft Alarm from **Mountain West** is designed for motels, hotels, hospitals, colleges and other owners of many TV sets that are vulnerable to theft. Home owners who need protection can use the same model.

The alarm is installed inside the TV cabinet. When the set is both

unplugged and moved, a penetrating wail audible up to a quarter mile is set off; only an electronic key will shut it off. All solid-state alarm uses AA rechargeable NiCad batteries and a trickle charger.

For More Details Circle (41) on Reply Card

Soldering Gun

The new ISO-TIP Cordless Soldering Gun by **Wahl Clipper** provides a soldering "uni-tool" with the power to solder everything from #12 electrical connections to micro circuitry.

The gun contains a built-in refillable .062 solder spool and self-feeding mechanism that operates when the trigger is completely depressed. Solder feeds through a tube at the tip, for one-hand soldering. (A standard model soldering gun is available without the automatic feed.)



A plug-in battery charger comes as standard equipment, and it will fully recharge the nickel-cadmium batteries overnight. The tip comes up to full soldering heat within 5 to 10 seconds, and performance is said to equal a conventional soldering iron. A "lock-off" switch prevents accidental heating of the tip while the iron is in storage or during transportation.

For More Details Circle (42) on Reply Card

Midget Driver Sets

Xcelite's line of midget screwdriver and nutdriver sets and combinations come in eight assortments, each with a stand-up plastic case for bench or tool kit.

The series covers slotted, Phillips, Allen, Scrufox, hex screws, and hex nuts. Metrics are available for nutdrivers and hex socket screws.

Each set includes the "piggyback" torque-amplifier handle, which slips over the handle of the 3½-inch color-coded midget tools.

For More Details Circle (43) on Reply Card

Compact Electric Drill

Wahl Clipper has introduced a 5-inch electric drill that accommodates drills and burrs with a shank size up to .123 (1/8"). The ISO-TIP Electronic Technician Drill is designed for solder removal; lead hole cleaning; and a variety of other jobs.



The drill's compact size allows use in confined areas and within cabinetry. High impact plastic housing makes it lightweight and an extra-long 10-ft. cord provides a wide working radius. On/off switch provides both "intermittent-on" and "locked-on" positions.

For More Details Circle (44) on Reply Card

These features supplied by the manufacturers are listed at no-charge to them as a service to our readers. If you want factory bulletins, circle the corresponding number on the Reply Card and mail it to us.

IT'S NO PUZZLE 

TO ORDER

OELRICH SERVICE FORMS

FOR TV-RADIO & 2 WAY RADIO SERVICE LEGAL FORMS FOR CALIF. FLA. UTAH NOW AT YOUR PARTS JOBBER OR WRITE FOR CATALOG B64

OELRICH PUBLICATIONS

4040 N. NASHVILLE AVE. CHICAGO, ILLINOIS 60634

For More Details Circle (20) on Reply Card

FREE CATALOG

HARD-TO-FIND PRECISION TOOLS

Lists more than 3000 items: pliers, tweezers, wire strippers, vacuum systems, relay tools, optical equipment, tool kits and cases. Also includes ten pages of useful "Tool Tips" to aid in tool selection.



JENSEN TOOLS & ALLOYS

130 SOUTH PREST DRIVE TEMPE, AZ 85281

For More Details Circle (21) on Reply Card

Advertising rates in the Classified Section are 35 cents per word, each insertion, and must be accompanied by cash to insure publication.

Each initial or abbreviation counts a full word.

Minimum classified charge \$3.00.

For ads on which replies are sent to us for forwarding (blind ads), there is an additional charge of \$3.00 per insertion to cover department number, processing of replies, and mailing costs.

Classified columns are not open to advertising of any products regularly produced by manufacturers unless used and no longer owned by the manufacturer or a distributor.

FOR SALE

TUNERS-DEALERS ONLY—Sylvania SS 54-35054 -1, 54-29331-3, 54-29332-2, Zenith—175-1122 (3HA5-6EA8) \$4.95 ea. Magnavox SS - 340226-2, 340184-3, 340187-1, Quasar - 77G10249A30-A31-A36-A37-A38-A41, Varactor-77G10728A01 \$7.95 ea. UPS-COD, David Sims Enterprises, Inc. 665 E. Jerico Tpke., Huntington Sta., N.Y. 11746. 10-77 21

YOU CAN GET DIRECTLY: from Japan any electronic part, even if only one piece. Write me your inquiry, I'll do my best to help you. My main lines are semiconductors, capacitors, resistors, switches, lamps or so. K. SOEDA, No. 5-9-503, Toshima 5-Chome, Kita-Ku, Tokyo 114, JAPAN. 10-77 3t

BUILD ELECTRONIC DEVICES in your home. Get started in your spare time. Big profits. Experience not necessary. Ask for free literature telling how. Electronic Development Lab, Box 1535, Pinellas Park, Fla. 33565. 4-77 15

TV & RADIO TUBES 36c EA!! Free color catalog. Cornell, 4221 University, San Diego, California 92105. 8-76-1f

REPLACEMENT COLOR YOKES-DEALERS ONLY. Zenith 95-2501-2532-2638-2667-S-89633 etc. 16.95, Magnavox 361380-1 18.95, Sylvania, GE etc. 14.95 to 19.95. Request for price list on your letterhead. David Sims Enterprises, Inc., 665 Jericho Turnpike, Huntington Station, N.Y. 11746. 12-76-1f

TUNER SUB ONLY \$19.95, wired, tested, complete with batteries and ready to use on tube or transistor sets. This unit is without knobs or cabinet but very compact with no wires or controls dangling. Easy to use, simply hook set's coax to sub and view picture (instructions provided). Only \$19.95, we pay the shipping. This is not a gimmick. If not completely satisfied, return within 10 days for full refund. **TEXAS TUNER SERVICE**, 4210 N.E. 28th Street, Fort Worth, Texas 76117. Phone (817) 834-8201. 9-77 3t

SHOP OWNERS/SERVICE MANAGERS: No "off season" layoffs for your personnel. Lock in your customers "year-round" with a service and maintenance agreement. Details - \$5 and copy of your letterhead to: Peck's Plan, Box 64, Hillsdale, New York 12529. 10-77 3t



Seeking Original Japanese Replacement Parts for CB and Stereo Repair Use?

SEE US AT THE 1978 WINTER CONSUMER ELECTRONICS SHOW IN LAS VEGAS JANUARY 5-8

CB REPAIR PACKAGE
\$63.00 value for only \$39.95
Contains 2 each. Repair almost all CB Sets

2SB 405 2SC 1014 2SC 1307
2SC 710 2SC 1173 2SC 1678
2SC 756 2SC 1226 2SD 235
2SC 828 2SC 1239 TA 7205P
2SC 945 2SC 1306 BA 511

SPECIAL PACKAGE OF MOST COMMON DRIVERS & FINALS

This kit contains 6 each of:
2SC 1678 2SC 756
2SC 1018 2SC 799
2SC 1226 2SC 1239
2SC 1306 2SC 1307
\$145.00 value for Just \$99.95

Original Japanese Transistors FET, IC, Diodes CHECK OUR LOW PRICES!

TRANSISTORS		FET	
2SA 49	.59	2SA 818	1.40
2SA 70	1.10	2SA 839	2.15
2SA 101	.59	2SA 841	.59
2SA 102	.59	2SA 847	.59
2SA 204	.59	2SA 850	.70
2SA 342	.90	2SA 872A	.90
2SA 353	.70	2SA 908	11.00
2SA 377	2.00	2SB 54	.59
2SA 440	.90	2SB 55	1.10
2SA 483	3.00	2SB 75	.59
2SA 484	2.50	2SB 77	.59
2SA 485	2.00	2SB 186	.59
2SA 489	1.60	2SB 187	.59
2SA 495	.70	2SB 202	1.60
2SA 496	1.10	2SB 220	.70
2SA 497	1.60	2SB 303	.59
2SA 509	.70	2SB 324	.70
2SA 525	2.50	2SB 337	1.60
2SA 537	2.25	2SB 367	1.50
2SA 539	.70	2SB 368B	2.15
2SA 561	.59	2SB 379	1.10
2SA 562	.59	2SB 400	.59
2SA 564A	.59	2SB 405	.70
2SA 565	1.10	2SB 407	1.40
2SA 566	3.40	2SB 415	.70
2SA 606	1.90	2SB 434	1.20
2SA 624	1.10	2SB 463	1.50
2SA 627	3.60	2SB 471	1.60
2SA 628	.59	2SB 472A	2.80
2SA 634	.59	2SB 474	1.20
2SA 640	.59	2SB 492	1.00
2SA 643	.70	2SB 507	1.60
2SA 659	.59	2SB 509	1.90
2SA 663	4.90	2SB 514	1.90
2SA 666	.70	2SB 525C	1.30
2SA 672	.70	2SB 527	1.90
2SA 673	.70	2SB 528D	1.60
2SA 678	.70	2SB 531	3.40
2SA 683	.70	2SB 536	1.60
2SA 684	.70	2SB 537	1.60
2SA 695	.70	2SB 538	4.90
2SA 697	.70	2SB 541	4.40
2SA 706	1.60	2SB 554	10.00
2SA 715	1.40	2SB 557	3.40
2SA 719	.70	2SB 561B	.70
2SA 720	.70	2SB 564	1.90
2SA 721	.70	2SB 595	1.90
2SA 725	.59	2SB 600A	7.00
2SA 726	.59	2SC 183	.59
2SA 733	.59	2SC 184	.59
2SA 740	2.65	2SC 186	.59
2SA 744	3.70	2SC 284	1.40
2SA 745R	4.40	2SC 287	.90
2SA 747	5.80	2SC 369	.70
2SA 750	.59	2SC 371	.59
2SA 756	3.40	2SC 373	.59
2SA 758	5.80	2SC 374	.59
2SA 774	.59	2SC 380	.59
2SA 777	1.10	2SC 381	.59
2SA 798	.70	2SC 382	.59
2SA 814	1.90	2SC 387	.59
2SA 816	.70	2SC 394	.59
2SC 403	.59	2SC 430	1.10
2SC 454	.59	2SC 454	.59
2SC 458	.59	2SC 458	.59
2SC 460	.59	2SC 460	.59
2SC 461	.59	2SC 461	.59
2SC 481	1.60	2SC 481	1.60
2SC 482	1.50	2SC 482	1.50
2SC 485	1.60	2SC 485	1.60
2SC 486	1.60	2SC 486	1.60
2SC 493	.90	2SC 493	.90
2SC 495	1.00	2SC 495	1.00
2SC 497	1.60	2SC 497	1.60
2SC 509	.90	2SC 509	.90
2SC 517	3.95	2SC 517	3.95
2SC 535	.70	2SC 535	.70
2SC 536	.59	2SC 536	.59
2SC 537	.59	2SC 537	.59
2SC 538A	.70	2SC 538A	.70
2SC 562	2.15	2SC 562	2.15
2SC 563	1.10	2SC 563	1.10
2SC 620	.59	2SC 620	.59
2SC 627	1.60	2SC 627	1.60
2SC 632A	.70	2SC 632A	.70
2SC 644	.59	2SC 644	.59
2SC 645	.70	2SC 645	.70
2SC 650	1.30	2SC 650	1.30
2SC 680	2.80	2SC 680	2.80
2SC 684	1.40	2SC 684	1.40
2SC 693B	.59	2SC 693B	.59
2SC 696	1.95	2SC 696	1.95
2SC 708A	1.90	2SC 708A	1.90
2SC 710	.59	2SC 710	.59
2SC 711	.59	2SC 711	.59
2SC 712	.59	2SC 712	.59
2SC 717	.59	2SC 717	.59
2SC 730	4.40	2SC 730	4.40
2SC 732	.59	2SC 732	.59
2SC 733	.59	2SC 733	.59
2SC 734	.59	2SC 734	.59
2SC 735	.59	2SC 735	.59
2SC 738	.59	2SC 738	.59
2SC 756	2.80	2SC 756	2.80
2SC 763	.59	2SC 763	.59
2SC 773	.70	2SC 773	.70
2SC 774	1.60	2SC 774	1.60
2SC 775	1.95	2SC 775	1.95
2SC 776	2.65	2SC 776	2.65
2SC 777	3.50	2SC 777	3.50
2SC 778	3.60	2SC 778	3.60
2SC 781	2.65	2SC 781	2.65
2SC 783A	3.60	2SC 783A	3.60
2SC 784	.59	2SC 784	.59
2SC 785	.70	2SC 785	.70
2SC 789	1.00	2SC 789	1.00
2SC 793	2.80	2SC 793	2.80
2SC 799	3.60	2SC 799	3.60
2SC 815	.59	2SC 815	.59
2SC 828	.59	2SC 828	.59
2SC 829	.59	2SC 829	.59
2SC 838	.59	2SC 838	.59
2SC 839	.59	2SC 839	.59
2SC 870	.59	2SC 870	.59
2SC 871	.59	2SC 871	.59
2SC 897	2.65	2SC 897	2.65
2SC 898	4.40	2SC 898	4.40
2SC 900	.59	2SC 900	.59
2SC 929	.59	2SC 929	.59
2SC 930	.59	2SC 930	.59
2SC 943	1.20	2SC 943	1.20
2SC 945	.59	2SC 945	.59
2SC 959	1.50	2SC 959	1.50
2SC 971	1.00	2SC 971	1.00
2SC 983	1.00	2SC 983	1.00
2SC 984	1.00	2SC 984	1.00
2SC 1000BL	.59	2SC 1000BL	.59
2SC 1014	1.20	2SC 1014	1.20
2SC 1017	1.40	2SC 1017	1.40
2SC 1018	1.20	2SC 1018	1.20
2SC 1030C	2.80	2SC 1030C	2.80
2SC 1047	.70	2SC 1047	.70
2SC 1060	2.25	2SC 1060	2.25
2SC 1061	1.40	2SC 1061	1.40
2SC 1080	4.40	2SC 1080	4.40
2SC 1096	1.00	2SC 1096	1.00
2SC 1111	3.40	2SC 1111	3.40
2SC 1115	3.40	2SC 1115	3.40
2SC 1116	4.40	2SC 1116	4.40
2SC 1116A	4.90	2SC 1116A	4.90
2SC 1124	1.30	2SC 1124	1.30
2SC 1162	1.10	2SC 1162	1.10
2SC 1166	.59	2SC 1166	.59
2SC 1173	.90	2SC 1173	.90
2SC 1175	.90	2SC 1175	.90
2SC 1177	14.00	2SC 1177	14.00
2SC 1189	1.40	2SC 1189	1.40
2SC 1211D	1.40	2SC 1211D	1.40
2SC 1213	.70	2SC 1213	.70
2SC 1222	.45	2SC 1222	.45
2SC 1226	1.00	2SC 1226	1.00
2SC 1237	4.25	2SC 1237	4.25
2SC 1239	3.50	2SC 1239	3.50
2SC 1279	.70	2SC 1279	.70
2SC 1306	4.40	2SC 1306	4.40
2SC 1307	4.90	2SC 1307	4.90
2SC 1312	.59	2SC 1312	.59
2SC 1313G	.59	2SC 1313G	.59
2SC 1317	.59	2SC 1317	.59
2SC 1318	1.40	2SC 1318	1.40
2SC 1327	.59	2SC 1327	.59
2SC 1330	1.50	2SC 1330	1.50
2SC 1342	.59	2SC 1342	.59
2SC 1344	.59	2SC 1344	.59
2SC 1345D	.59	2SC 1345D	.59
2SC 1359	1.40	2SC 1359	1.40
2SC 1360	1.00	2SC 1360	1.00
2SC 1362	.59	2SC 1362	.59
2SC 1364	1.40	2SC 1364	1.40
2SC 1377	4.90	2SC 1377	4.90
2SC 1383	.59	2SC 1383	.59
2SC 1400	.59	2SC 1400	.59
2SC 1402	3.70	2SC 1402	3.70
2SC 1403	3.70	2SC 1403	3.70
2SC 1419	1.10	2SC 1419	1.10
2SC 1444	2.80	2SC 1444	2.80
2SC 1448	1.10	2SC 1448	1.10
2SC 1449	1.00	2SC 1449	1.00
2SC 1451	1.60	2SC 1451	1.60
2SC 1475	1.40	2SC 1475	1.40
2SC 1478S	.70	2SC 1478S	.70
2SC 1509	1.10	2SC 1509	1.10
2SC 1584	8.50	2SC 1584	8.50
2SC 1586	6.60	2SC 1586	6.60
2SC 1624	1.30	2SC 1624	1.30
2SC 1626	1.10	2SC 1626	1.10
2SC 1628	1.30	2SC 1628	1.30
2SC 1647	.59	2SC 1647	.59
2SC 1659	1.60	2SC 1659	1.60
2SC 1674	.59	2SC 1674	.59
2SC 1675	.59	2SC 1675	.59
2SC 1678	2.25	2SC 1678	2.25
2SC 1682	.45	2SC 1682	.45
2SC 1684	.59	2SC 1684	.59
2SC 1708	.59	2SC 1708	.59
2SC 1728	2.00	2SC 1728	2.00
2SC 1760	2.00	2SC 1760	2.00
2SC 1775	.45	2SC 1775	.45
2SC 1816	.65	2SC 1816	.65
2SC 1885	.70	2SC 1885	.70
2SC 1908	.45	2SC 1908	.45
2SC 1909	4.40	2SC 1909	4.40
2SC 1951	1.10	2SC 1951	1.10
2SC 1957	1.20	2SC 1957	1.20
2SC 1969	4.90	2SC 1969	4.90
2SC 1983	1.10	2SC 1983	1.10
2SC 1975	4.40	2SC 1975	4.40
2SC 2028	.90	2SC 2028	.90
2SC 2029	3.90	2SC 2029	3.90
2SC 2091	3.60	2SC 2091	3.60
2SC 2092	3.90	2SC 2092	3.90
2SC 2098	3.90	2SC 2098	3.90
2SD 28	2.00	2SD 28	2.00
2SD 55	1.30	2SD 55	1.30
2SD 68	1.30	2SD 68	1.30
2SD 72	2.55	2SD 72	2.55
2SD 75	2.25	2SD 75	2.25
2SD 85	2.25	2SD 85	2.25
2SD 90	2.25	2SD 90	2.25
2SD 95	2.50	2SD 95	2.50
2SD 100	2.00	2SD 100	2.00
2SD 101	3.40	2SD 101	3.40

FOR SALE (CONT.)

OWNERS OF HEATH CRT Checker rejuvenators # IT-5230. Sockets for most B&W and color CRT's wired & tested for \$7.00 P.P. CONUS. Money Orders or Certified Check only to Anthony E. Bodo, 4380 Hayes, Gary, Ind., 46408. 11-77-2t

FOR SALE: CRT model 5UP1-500 pcs. available; also AT-4041 Philips pincushion device made for Zenith-5000 pcs. Ask for free tube and semiconductor catalog. Temtron Electronics Ltd., 138-69 Francis Lewis Blvd., Rosedale, N.Y. 11422. (212) 978-5896. 11-77-1t

MANUFACTURER CLEARANCE: 9 792A Pulse Generators* \$200 each; 17 7092 Plugin carriers for 766 Series \$10 each; 35 4292 4" 100:1 probes \$20 each; 140 Scope covers for 1050 Series \$20 each; *Thirty-day Warranty. Cash sales only. Shipping charges extra. Dumont Oscilloscope Laboratories, Inc. 40 Fairfield Place, West Cladwell, New Jersey 07006. (201) 575-8666. 11-77-1t

COLLECTOR'S ITEMS FOR SALE: Electronics books. Sams Photofacts Service 1-150 plus index. Make offer. Ed Zaharatos, EZ Electronics, Box 817, Medford, N.Y. 11763. 11-77-1t

SPECTRUM ANALYZER singer SB12B. Panoramic head singer RF7A. 2-tone generator singer TTG2. Lab-stand on rollers \$600.00 complete. Bird PEP watt meter MDL-4314 DC/AC \$400.00. Bird Elements \$35.00 each. B&K Color generator MDT 1246 \$90.00 Tawas 2-Way Radio, 1165 South US 23, Tawas City, Michigan 48763. Call (517) 362-3428, 24 hours daily. 11-77-1t

WANTED

WANTED: CB radio repair contract work. A&R Service, North Haven, Conn., 203-239-0155 (evenings). 9-77 3t

WANTED: to buy used Sams Photofax volumes for automobile radio repair, 1970 to present. Must be reasonable and in good condition. Bill Walters, P.O. Box 78, Nevada, Missouri 64772. State price and volume's numbers in first letter. 11-77-1t

WANTED TO BUY: A well established TV sales and service shop and/or sewing machine & vacuums. Send shop photo, asking price & last three years gross and general information, location, etc. W. R. Collins, USALOGC (SST), Fort Lee, Va. 23801. 11-77-1t

NEEDED: complete picture tube rebuilding equip. for B&W and color tubes (second hand). Write to: Julio Romero Fonseca, Fabrica de Brassieres El ChoCho, Calle Monserrat, Col. Sta. Ursula No. 1221, Tel. 21-7239, San Salvador, El-Salvador, Central America. 11-77-1t

BUSINESS OPPORTUNITY

MATV INSTALLERS. Want more profits with less headaches? Information \$5.00 (free with MATV letterhead). Box 809, Boynton Beach, Fla. 33435. 11-77-eom-tf

TV SALES & SERVICE BUSINESS in small Ozark town. 32 years in same location. City approved for \$2 million dollar grant for industrial park. Will sell inventory & test equipment & lease building & fixtures or buy inventory & lease test equipment & building. Only full-time shop in town-good volume-large trade area—Reason for selling—Retiring. Ellsworth Carroll, P.O. Box 22, Cabool, Mo. 65689 (417) 962-3446. 11-77-1t

TV REPAIR SHOP in Bakersfield, California. Well established, low overhead, plenty of customer goodwill, excellent stock of tubes, parts, etc. Well equipped van. Lots of test equipment. Sams coverage from 1946 to current. \$29,000. Technician willing to help train. (805) 871-3580. 11-77-1t

START ELECTRONIC FACTORY IN YOUR HOME. GET STARTED IN YOUR SPARE TIME. ONE MAN OPERATION. EXPECT BIG PROFITS. EXPERIENCE NOT NECESSARY. PRACTICALLY NO INVESTMENT. WRITE FOR FREE LITERATURE TELLING HOW. ELECTRONIC DEVELOPMENT LAB, DEPT. A, BOX 1535, PINELLAS PARK, FL 33565. 8-77-tf

SMITTY'S TV SALES & SERVICE. Must retire. Two houses and shop. Low overhead. Established 18 years. Good reputation. \$50,000 yearly net income. \$25,000 inventory. Servicing most major motels in town, approximately 600 color sets. Will show figures to interested parties only. Call 1 (305) 267-9570 or write 509 Park Avenue, Titusville, Florida 32780. 10-77 3t

EDUCATION-INSTRUCTION

REPAIR TV TUNERS—High Earnings: Complete Course Details. 12 Repair Tricks, Many Plans, Two Lessons, all for \$2 Refundable. Frank Bocek, Box 3236 Enterprise, Redding, Calif. 96001. 8-76-tf

USED COURSES. We buy-sell electronics, other subjects. TVT Courses, Box 396, Griffith, Indiana 46319. 10-77 2t

SERVICES

ELECTRONIC MANUFACTURERS: electronic and printed circuits requiring hand finish assembly or modification work wanted. Via drop ship method. Gilbert Whitley, R.R.2, Metamora, Ill. 61548. 11-77-3t

advertisers' index

American Technology Corp.	12
Arrow Fastener Co., Inc.	21
B&K Precision, Dynascan Corp.	1
Busman Mfg. Div. McGraw-Edison Co.	7
Castle Electronics	Cover 4
Cleveland Institute of Electronics, Inc.	9
DeForest Elec. Subsidiary of Dumont Oscilloscope Labs, Inc.	17
Dictaphone Corp.	9
Dumont Oscilloscope Labs, Inc.	17
John Fluke Mfg. Co., Inc.	39
Fuji-Svea Enterprise	51
General Electric Co.-TV Dealer.	Cover 3
Heath Company	9
ISCET	48
ITT Pomona Electronics	2
Jensen Tools and Alloys	50
Kager International	16
Leader Instruments Corp.	31
MTI Inc.	41
Mohawk Wholesale & Equipment	33
NESDA	41
Non-Linear Systems, Inc.	16
Oelrich Publications	50
Oneida Electronics Mfg. Inc.	43
Optima Electronics	14
Perma Power Electronics Inc.	39
Pomona Electronics, Div. of ITT.	2
RCA Distributor & Special Products Div.	15
Howard W. Sams & Co., Inc.	13
Sperry Tech, Inc.	12
Sprague Products Co.	Cover 2
GTE Sylvania ECG/Consumer Renewal	3
Zenith Radio Corp.	4-5

REGIONAL ADVERTISING SALES OFFICES

Indianapolis, Indiana 46280
ROY HENRY
2469 E. 98th St.
Phone: (317) 846-7026

Greenlawn, New York 11740
CHUCK HORNER
P.O. Box 175
Phone: (516) 757-7863

Mountain View, California 94043
DENNIS TRIOLA
2680 Bayshore Frontage Road, Room 102
Phone: (415) 961-0378

London, W.C. 2, England
JOHN ASHCRAFT & CO.
12 Bear Street
Leicester Square
Phone: 930-0525

Badhoevedorp, Holland
JOHN ASHCRAFT & CO.
JOHN J. LUCASSEN, Mgr.
Sloterweg 303
Phone: 2968-6226

Tokyo 105, Japan
INTERNATIONAL MEDIA REPRESENTATIVES LTD.
2-29, Toranomon 1-chome, Minato-ku
Phone: 502-0656

Help!

Anytime you have a question about your subscription to Electronic Servicing, please include a mailing label to insure prompt service on your inquiry.

Change of Address

If you're about to move, please let us know approximately four weeks before the move comes about. Simply affix your present label here, and carefully print the updated information below.

Please Help Us
to Serve You Better

Electronic Servicing
P.O. Box 12901
Overland Park, Kansas 66212

Name _____
(Please Print)

Employer _____

Address _____

City _____ State _____ Zip _____

AFFIX LABEL HERE

Here Today, Gone Tomorrow.



At General Electric we're treating every TV parts order like a rush order. Here's how it's paying off: Over 99% of the General Electric TV replacement parts ordered this year were in stock in our national computer-linked parts distribution system. And on the average better than 90% were ready for immediate shipment from the Regional Replacement Parts Centers.

This is why most parts are now shipped the same day an order's received or by the close of business the following day.

But ordering parts from us is more than fast. It's easier than ever before. In almost all areas, our toll-free ordering numbers connect you directly with GE Parts Centers. And you can charge your order to Master Charge, VISA (BankAmericard) or your approved GE Open Credit Account.

What's more, when you order several parts and one isn't immediately available, we don't leave you hanging. Instead we ship what's in stock and include the expected shipping date for what isn't.

How did General Electric's parts distribution come so far so fast? One factor was the enlargement of stocks at many



GE Parts Centers. But the deciding factor was our determination to build a streamlined, efficient system that simplified the parts ordering process for both of us.

Now comes the easiest part of all. Clipping out and sending in the coupon below. When you do, we'll send you a list of our toll-free numbers and all the information you need to take the easy way out next time you order TV replacement parts from us. It's our business to make your business easier.

"I've got your number."

"DUTCH" MEYER/GENERAL ELECTRIC COMPANY
TELEVISION BUSINESS DEPARTMENT
COLLEGE BOULEVARD/PORTSMOUTH, VA. 23705

Dear "Dutch":

Please send me the items checked below:

- Brochure covering GE toll-free ordering numbers
- Listing of Parts Distributors.
- Master Charge and VISA (BankAmericard) information.
- GE Open Credit Account information.

Name _____

Service Company _____

Address _____

City _____ State _____ Zip _____

THIS IS GE PERFORMANCE TELEVISION

GENERAL  ELECTRIC

THE AGE OF CASTLE HAS ARRIVED!

TO A PROFESSIONAL TV SERVICE TECHNICIAN, A MAJOR KEY TO INCREASING PROFITS IS SAVING TIME. CASTLE'S ADVANCED TECHNOLOGY WILL HELP YOU!

MEZZER™ TV FIELD STRENGTH METERS Put an End to Guessing About the Signal Level

VHF Field Strength Meter Model FSM-V
Range: 20 microvolts-100 millivolts
Attenuator: x1, x10, x100
Inputs: 75 ohms & 300 ohms
AC-DC (Batteries not included) net \$137.95



SUBBER® TV SIGNAL CIRCUIT ANALYSTS Analyze the Entire Signal Circuit of any TV Receiver

Master Subber® Model Mark V
Outputs at video IF, sound IF, video & audio
Built-in Monopole Antenna
Built-in Loudspeaker
Complete with 120 vac/wall plug-in transformer
and matched test cables.
Video Carrier Level Meter
Battery Indicator Meter
net \$169.95



CASTLE ELECTRONICS

5233 OLD HIGHWAY 37 S.
(812) 824-9791

BLOOMINGTON, IN. 47401

For More Details and Specifications Contact
Your Nearest Castle Products Distributor
In Canada: Len Finkler Ltd, Ontario



For More Details Circle (3) on Reply Card