

# ELECTRONIC


*Servicing & Technology*


FEBRUARY, 1982  
\$2.25

More light on optical-fiber systems

Servicing excessive high voltage

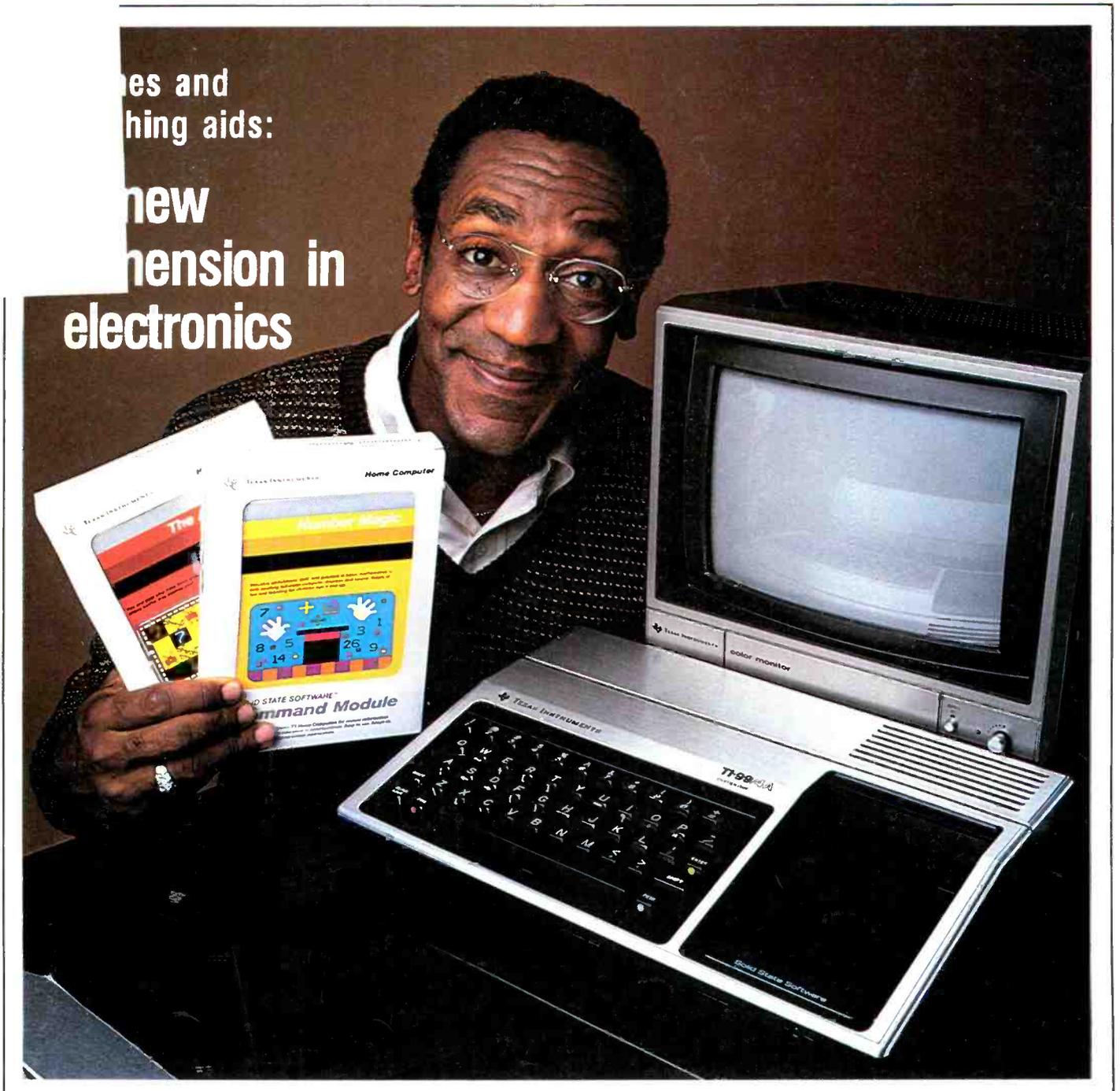es and  
hing aids:  
new  
ension in  
electronics



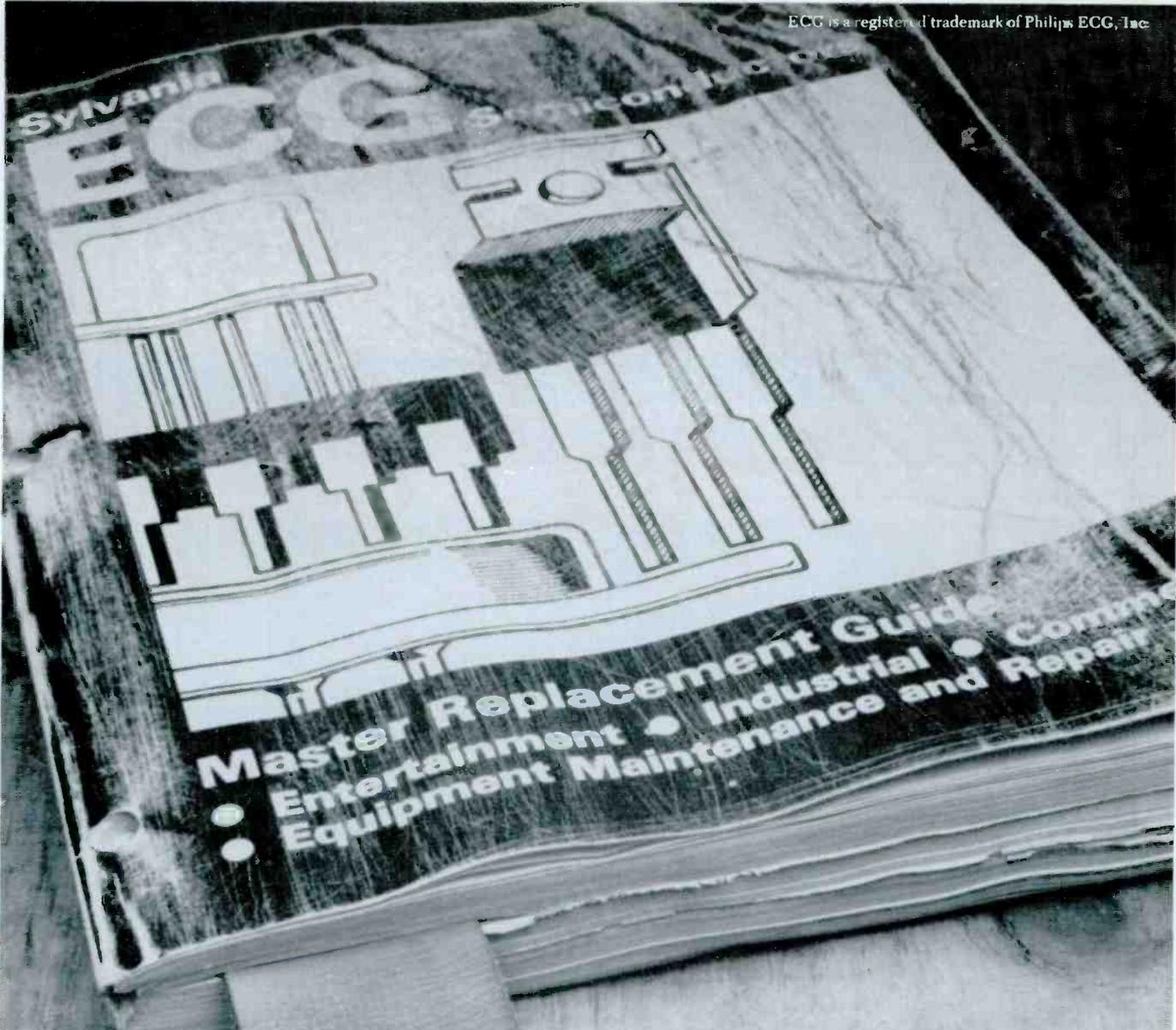

**It's not the bible,  
but a lot of service technicians  
swear by it.**

Behold! The Sylvania ECG® Master Replacement Guide, the most comprehensive publication of its kind used by the industry.

Inside you will find more than 170,000 industry part numbers cross referenced to over 2,500 ECG numbers, including most of the hard-to-find foreign parts that are plaguing more and more repairmen every day.

If the part number is illegible, there are also easy to use comprehensive selection tables to help you identify and replace

transistors and linear IC's by application. You will find clear, concise descriptions and illustrations on each type from diodes to IC's with specifications, applications and package dimensions.

What's more, you also have Philips ECG technical resources ready to help you with any questions you might have regarding particular situations or applications; and as always, all ECG parts you will receive come with the knowledge that they've met specifications which are equal to

and usually exceed those of the original parts and that they've been tested using stringent procedures established by the U. S. Military.

To find out more, seek your nearest authorized Philips ECG distributor.

If you are not already a believer, one look at our catalog should convert you.

**Philips ECG**

*A North American Philips Company*

Circle (1) on Reply Card

# ELECTRONIC

Servicing & Technology

Editorial, advertising and circulation correspondence should be addressed to: P.O. Box 12901, Overland Park, KS 66212-9981 (a suburb of Kansas City, MO); (913) 888-4664.

## EDITORIAL

Bill Rhodes, *Editorial Director*  
Carl Babcoke, *Consumer Servicing Consultant*  
Rhonda Wickham, *Managing Editor*  
Tina Thorpe, *Associate Editor*

## ART

Dudley Rose, *Art Director*

## CIRCULATION

John C. Arnst, *Director*  
Evelyn Rogers, *Manager*  
Dee Manies, *Reader Correspondent*

## ADMINISTRATION

R. J. Hancock, *President*  
Cameron Bishop, *Publisher*

## ADVERTISING

Greg Garrison, *National Sales Manager*  
Jeanette Staley, *Production Manager*  
Mark Raduziner, *Marketing Coordinator*

Regional advertising sales offices listed near Advertisers' Index.



Member, Audit Bureau  
of Circulation



Member, American  
Business Press

**ELECTRONIC SERVICING & TECHNOLOGY** (USPS 462-050) (with which is combined PF Reporter) is published monthly by Intertec Publishing Corp., P.O. Box 12901, 9221 Quivira Road, Overland Park, KS 66212-9981. Second Class Postage paid at Shawnee Mission, KS 66201. Send Form 3579 to P.O. Box 12901, Overland Park, KS 66212-9981.

**ELECTRONIC SERVICING & TECHNOLOGY** is the "how-to" magazine of electronics. It is edited for electronic enthusiasts who are interested in buying, building, installing and repairing home-entertainment electronic equipment (audio, video, microcomputers, electronic games, etc.).


Subscription prices to qualified subscribers: one \$15, two years \$26, three years \$34 in the USA and its possessions. Foreign countries: one year \$20, two years \$30, three years \$40. Single copy price \$2.25; back copies \$3.00. Adjustment necessitated by subscription termination to single copy rate. Allow 6 to 8 weeks delivery for change of address. Allow 6 to 8 weeks for new subscriptions.

**PHOTOCOPIY RIGHTS:** Permission to photocopy for internal or personal use is granted by Intertec Publishing Corp. for libraries and other registered with Copyright Clearance Center (CCC), provided the base fee of \$2 per copy of article is paid directly to CCC, 21 Congress St., Salem, MA 01970. Special requests should be addressed to Cameron Bishop, publisher.  
ISSN 0013-497X/81 \$2



INTERTEC PUBLISHING CORP.

©1981 All rights reserved.

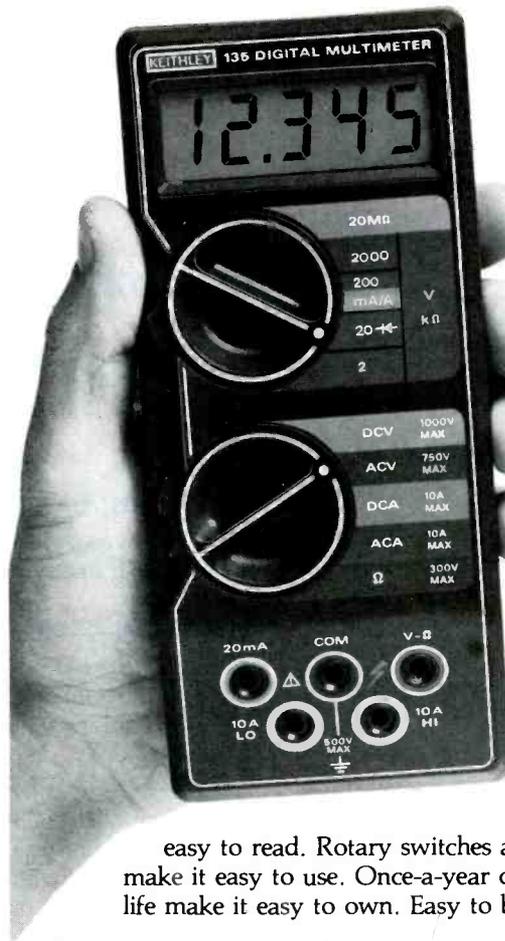

## Easily the best.

In terms of resolution and accuracy, the Model 135 is easily the best handheld DMM available at any price. It's the only handheld offering 4½ digits. That gives it 10 times better resolution than the best 3½-digit DMM and provides 3 to 4 times more useable accuracy. Resolution isn't all you get. You get an easy-to-use instrument that's rugged and reliable enough to live in the read world. You get Keithley packaging.

Its large, crisp LCD makes it

easy to read. Rotary switches and a color-coded faceplate make it easy to use. Once-a-year calibration and long battery life make it easy to own. Easy to buy at \$235.

## Best in price, best in performance.

There is a DMM designed specifically for your application in the Keithley line. Your Keithley distributor has instruments in stock for your convenience. Call today for complete information and a demonstration.


## Sound Choice.

New Model 128 Beeper DMM. Audible/visual indication on all 5 functions of this 3½-digit DMM lets you test faster, and the user adjustable threshold and special diode test function make it a sound choice. Unique features, \$139.


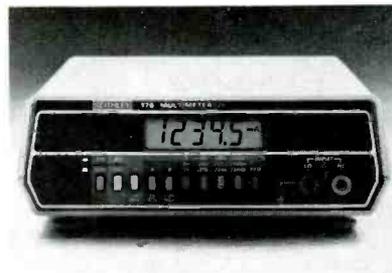
## Bench Bargain.

Model 176, Portable Bench DMM. Full 5-function LCD 4½-digit bench DMM offers 0.05% basic DCV accuracy. Keithley ease of use features include range and function annunciators, 1000 hour battery life and optional line operation. A bargain at \$269.



# KEITHLEY

Keithley Instruments, Inc.

28775 Aurora Road/Cleveland, Ohio 44139/(216) 248-0400

Circle (2) on Reply Card


February 1982 *Electronic Servicing & Technology* 1

The how-to magazine of electronics...

# ELECTRONIC


**Servicing & Technology**

February 1982  
Volume 2, No. 2

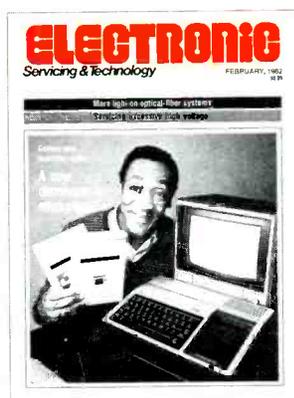

In the past few years, video games and teaching aids have exploded into a billion-dollar industry. Featured on the cover is Bill Cosby, a spokesperson for Texas Instruments. See story on page 26. (Photo courtesy of Texas Instruments Inc.)

- 12** **Stumbling blocks on the CET exam**  
Check out your electronics knowledge with this sampling of typical CET exam questions.
- 14** **Servicing excessive high voltage, Part 1**  
*By Homer L. Davidson and Carl Babcoke*  
High voltage must be suspected when a picture tube, flyback, tripler or horizontal-output transistor fails.
- 20** **Programming games for business or pleasure**  
*By Walter Dean, Computer Concepts Corporation*  
Data processing equipment can be used to pursue bandits across the screen, as well as organize your finances.
- 25** **Consumer guide to portable audio**  
These tips on quality, price, sound, portability, comfort, fit, adaptability and company reputation will help you choose a portable stereophone.
- 26** **Games people play**  
A menu of 60 video games and learning aids, from five different manufacturers, shows the variety of cartridges offered on the market today.
- 37** **More light on optical-fiber systems**  
Optical-fiber transmission systems have many advantages over wire cable systems.
- 46** **How to repair electronic garage-door openers**  
*By Carl Babcoke, CET*  
This case history describes the first attempt of a color TV technician to troubleshoot a garage-door opener.
- 52** **Test Lab**  
*By Carl Babcoke, CET*  
B&K-Precision 3020 sweep/function generator is featured.
- 56** **Elmo Manufacturing—entering a race of giants**  
*By Joel A. Samberg*  
A 57-year-old photographic equipment company has come out with its own version of a videodisc player.

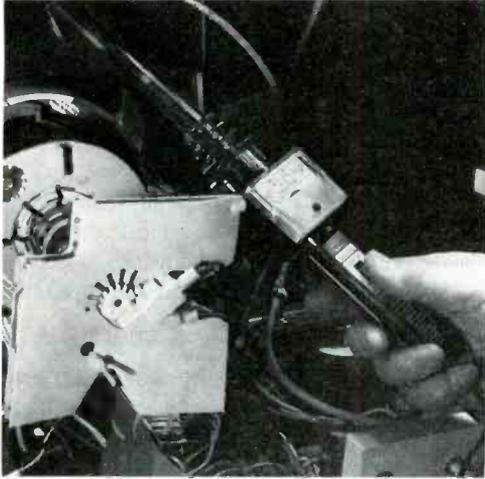

Page 14



Page 25



Page 26

## DEPARTMENTS

- 4 Electronic Scanner
- 6 Association News
- 8 Symcure
- 11 Reader's Exchange
- 13 Calendar of Events
- 58 New Products
- 66 New Literature



## ELECTRONIC SCANNER

### Westinghouse defense experts call engineer shortage critical

National efforts to boost industrial productivity and maintain technological superiority in industry and defense could be hampered by a critical shortage of engineers.

The problem is particularly acute in the high technology defense sector of American industry. Some experts in the field have labeled the technical manpower shortage "the Achilles heel of our national defense."

"The current shortage of engineers is evolving into a national crisis," says Marvin E. Jones, director of human resources for Westinghouse Electric Corporation's Defense and Electronic Systems Center in Baltimore. Westinghouse is a billion-dollar defense contractor specializing in advanced electronics such as radar and electronic countermeasures systems.

"There simply are not enough people entering the engineering field today to meet industry's demands," Jones noted. "The microelectronics revolution, the increasing threat of foreign competition, and the development of other new technologies have brought about fundamental changes in society. But, our educational system has been unable to keep up with these sweeping changes. As a result, our universities are graduating only about 60,000 engineers with bachelor's degrees each year. That's well short of the technical manpower demands of industry."

### Hilton suites sell out at drawing for space

The Electronic Industry Show Corporation has announced that space at the Electronic Distribution Show and Conference is rapidly running out. EDS will be held

April 29–May 1, at the New Orleans Hilton hotel.

For the first time in the EDS history, the full allotment of suites in the main headquarters hotel was assigned at the drawing for space. Conference rooms are also sold out, according to David L. Fisher, EDS executive vice president. Additional suites remain at the New Orleans Marriott and International hotels, and these, too, are expected to be claimed quickly. A dwindling supply 8' x 10' and 10' x 10' exhibit booths is still available in the Hilton's two halls to accommodate most, if not all, late applicants for EDS.

### Computer network design featured in course from ICS

A comprehensive, state-of-the-art foundation in computer communication network concepts, technology and implementation, is provided in a course offered this spring and summer by Integrated Computer Systems (ICS).

The 4-day course, entitled "Computer Network Design and Protocols," emphasizes the practical aspects of network design, interfacing, protocols and packet switching.

Priced at \$845, the course will be held in Boston, April 13-16; Minneapolis, May 4-7; Los Angeles, May 18-21; Washington, D.C., June 15-18; San Francisco, July 13-16; and Boston, July 20-23.

For further information, contact Ruth Dordick, Integrated Computer Systems, 3304 Pico Blvd., P.O. Box 5339, Santa Monica, CA 90405; 213-450-2060.

### Sony serviceability scores 94.09%

Changes in chassis design, quick access to components, and many snap-in parts all contributed to Sony's rating of excellent on a recent serviceability inspection of Sony model KV-1946R 19" color television, using the SCC342A chassis. The inspection was conducted for the International Society of Certified Electronics Technicians by a team headed by Dean Mock, CET, chairman.

The 94.09% total is the highest

rating, to this date, of any previously evaluated chassis from any manufacturer. Sony scored 1100.8 points out of a possible 1170.

The inspection was conducted at the Sony Corporation in Long Island City, NY.

Sony was commended for using common snap-in fuses and snap-on shields and for a clean and uncluttered circuit board with excellent roadmapping and grouping. The mounting position of the chassis for easy access also received positive comments.

The chassis incorporated a number of changes that were recommended in a 1980 inspection conducted on another Sony model. Serviceability is an industry effort to make electronic servicing easier and more efficient.

Serviceability Inspections were held during 1981 by RCA, General Electric and Sony. Other manufacturers interested in conducting inspections should contact ISCET, 2708 West Berry, Fort Worth, TX 76109, 1-817-921-9101.

### Pace Inc. announces new training program


Pace Inc. has announced the introduction of a complete 8-part training program in "Rework and Repair for Electronics."

According to Bill Siegel, president of Pace Inc., this is one of the most comprehensive training programs ever undertaken and can result in saving companies hundreds of thousands of dollars in costly repair, plus reduce critical downtime.

"We believe that everyone involved in electronics manufacture and maintenance should be trained in high reliability rework and repair," Siegel said.

"Few people are trained in repair for electronics and it's a lot more sophisticated than most people imagine. An unskilled person can cause more damage in trying to repair a PCB than was already there."

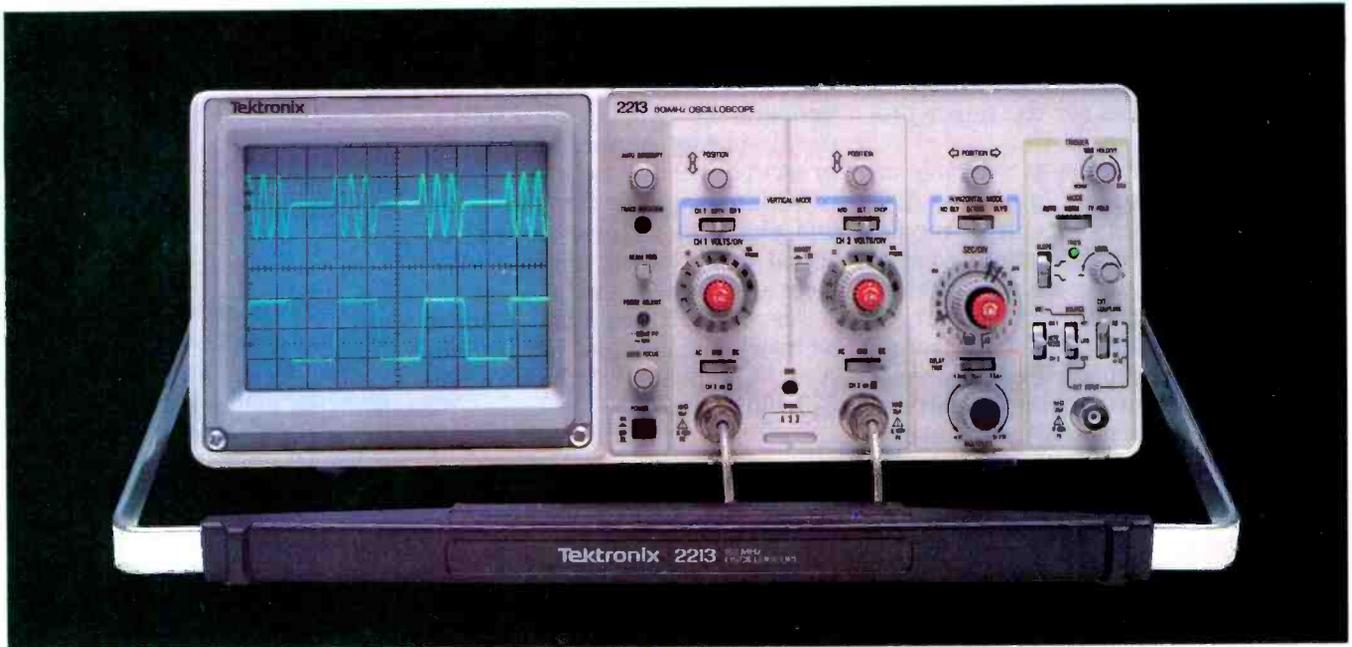It is practically impossible to see how someone repairs a PCB because of the tiny point of action, so Pace has used the dynamics of



## The \$1100 scope. Only Tektronix could make so much performance so affordable!

The 60 MHz Tek 2213 and 2215 introduce a scope design so radically different, it delivers full-range performance at prices well below what was ever possible before.

Not surprisingly, it is from Tektronix, the world's largest and most respected scope manufacturer, and a legend for instrument reliability and value.

Design for the 2213 (\$1100) and dual time base 2215 (just \$1400) includes some 65% fewer mechanical parts. Fewer circuit boards. Fewer electrical connectors and cabling. Result: a lower purchase price for you plus far greater reliability.

**Performance is pure Tektronix:** there's the

bandwidth for digital and high-speed analog circuits. The sensitivity for low signal measurements. The sweep speeds for fast logic families. A complete trigger system for digital, analog or video waveforms. And, with the 2215, you get fully calibrated delayed sweep for fast accurate timing measurements. New high-performance 10X Tektronix probes are included!

### 2213/2215 PERFORMANCE DATA

**Bandwidth:** Two channels, dc—60 MHz from 10 V/div to 20 mV/div. (50 MHz from 2 mV/div to 10 mV/div).

**Sweep speeds:** Sweeps from 0.5 s to 50 ns (to 5 ns/div with X10 mag).

**Sensitivity:** Scale factors from 100 V/div (10X probe)

to 2 mV/div (1X probe). Accurate to  $\pm 3\%$ . Ac or dc coupling.

**Delayed sweep measurements:** 2213: standard sweep, intensified after delay, and delayed. 2215: A only, B only, or A and B alternately with A intensified by B.

**Complete trigger system:** Modes include TV field, normal, vertical mode, and automatic; internal, external, and line sources; variable holdoff; separate B sweep trigger on 2215.

**Probes:** High performance, positive attachment, 10-14 pF and 60 MHz at the probe tip.

**The price: Just \$1100 for the 2213 and \$1400 for the dual time base 2215\*.** Order direct from the

**Tektronix National Marketing Center, your hotline for the 2200 Series and all Tektronix accessories.**

Phones are staffed by sales engineers who can answer your technical questions.

Your direct order includes a 15-day return policy and full Tektronix warranty. Call today. You can't buy a more advanced scope for less.

**ORDER TOLL FREE  
800-547-1845**

**Ask for Department 905** (In Oregon, Alaska and Hawaii: 1-503-627-4502 collect.) Lines are open from 8 am EST to 5 pm PST.

\*Prices F.O.B. Beaverton, OR

**Tektronix**  
COMMITTED TO EXCELLENCE

motion pictures that feature animation, cutaways and bigger-than life graphics to give students a hands-on feel for the repair process.

The 8-part series is available on 16mm, Super 8, or video. The series includes concepts of repair, elements of construction, component removal, solder extraction, removing conformal coatings, repair of damaged PCBs, refurbishing and replating edge connectors and preventing electrical damage to sensitive components. It also includes student handbooks and an instructor's guide with information on how to customize the presentation if desired.

Preview copies of *Rework and Repair for Electronics* are available to people with training responsibilities. Contact: Pace Training, 9893 Brewers Court, Laurel, MD 20707, 1-301-490-9860.

### **ERA and NSCA to host seminars for sound and electronic installers**

The New York chapter of the Electronic Representatives Association (ERA) and the National Sound Contractors Association (NSCA) will host a series of technical and marketing seminars on emerging markets for sound and electronic installers on March 30-31, 1982, at the Marriott La Guardia, Flushing, NY.

Sponsored by both organizations, the seminar will deal with how the installer can get involved profitably in major emerging markets. Technical updates, industry trends and marketing techniques will be covered by experts drawn from various segments of the industry.

For further information, contact Joel Schwartz, L-C-A Sales Company, 76 Main Street, Tuckahoe, NY 10707; 914-961-4700 or 212-585-1645.

### **Sensors & Systems '82 conferences presented**

A series of 3-day conferences and exhibitions will be held in the western and central regions of the

United States in May/June 1982. The events will cover all aspects of sensor technology from temperature sensors to displacement, velocity, acceleration, force, pressure, temperature, light, radiation, magnetic field, moisture and chemical vapors, as well as signal conditioning, digital interfaces and system interfaces.

For more information, contact Network Exhibitions, 785 Harriet Ave., Campbell, CA 95008; 408-370-1661.

### **NATESA urges action on copyright bill**

The National Association of Television & Electronic Servicers of America (NATESA), through an appeal by Sony Corporation, is attempting to overturn bill S.1758. The order, which bans all recording of copyrighted video material, runs contrary to current recognition on personal recording of copyrighted audio material, according to NATESA.

The organization is urging concerned persons to write to Senators Dennis DiConcini of Arizona and Alphonse D'Amato of New York, sponsors of the bill, and senators from their own states.

### **Club and magazine launched for Odyssey<sup>2</sup> players**

Behind-the-scenes information, tips from the experts, new product previews and the opportunity to officially register high scores for free prizes can all be found in *Odyssey<sup>2</sup> Adventure*, a new quarterly magazine for Odyssey<sup>2</sup> video gamers.

"As the official publication of the Odyssey<sup>2</sup> Adventure Club," said Gerald A. Michaelson, vice president sales, special markets, "it will keep Odyssey<sup>2</sup> owners abreast of the latest developments involving their computer home video game."

The Odyssey<sup>2</sup> Adventure Club membership certificate and the club membership card will be enclosed with the March 1982 issue of *Odyssey<sup>2</sup> Adventure*.

**ES&T**



### **NEDA presents symposium at EOS '82**

The first annual Test and Measurement Distribution Conference will be a highlight of the National Electronic Distributors Association (NEDA) Management Conference, April 28, 1982, the day before the Electronic Distribution Show opens at the New Orleans Hilton Hotel.

At the keynote luncheon, Thomas Kurlak, vice president-technology, Merrill Lynch Pierce Fenner and Smith, will discuss "Electronic distribution—the view from Wall Street".


A second concurrent afternoon Symposium will begin after the keynote luncheon on "Opportunities in semiconductor distribution". Paul Carroll, president, Semiconductor Specialists Inc., will serve as chairman of this meeting.

In addition to the two symposiums on April 28th, NEDA also has scheduled a variety of EDS '82 educational programs to be held each morning of the show. Two seminars will be repeated April 30 during show hours.

The NEDA Management Conference brochure may be obtained by writing the National Electronic Distributors Association, 1480 Renaissance Drive, Suite 214, Park Ridge, IL 60068, or phoning 1-312-298-9747.
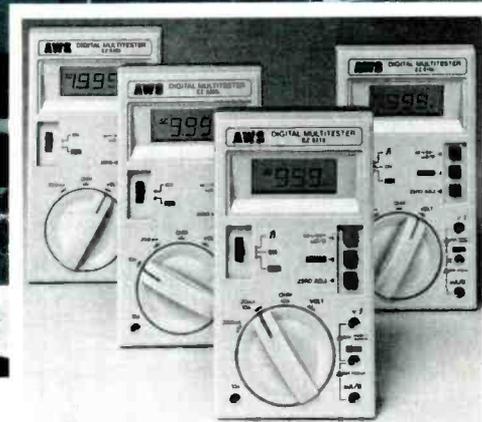
### **National Sound and Electronic Systems Conference program announced**

Plans for the third National Sound and Electronic Systems Conference, the sound contracting industry's forum for the exchange of ideas and information, has been announced by Robert F. Ancha, president of the National Sound and Communications Association. The NSCA-sponsored conference will be held April 29–May 1, at the



# “Fast and accurate readings. That’s why we use the AWS EZ-Meter™ DMMs.”

Bob Murray, ITS Equipment & Leasing Corp.

“At ITS, we maintain and service hundreds of pieces of computer equipment used by over 200 airline companies throughout the world. If even one piece of equipment goes down, serious back-up problems can occur. So our job is not only to make the proper repairs, but to make them fast. That’s why we use the AWS EZ-Meter series of Digital Multi-Meters. With their Autoranging feature (volts & ohms) we can count on quick, accurate readings hundreds of times a day – both on the bench and in the field. And with their Five-Year warranty, we think they’re the best hand-held DMMs you can buy.”

### Other outstanding features include:

- Autoranging and full manual mode (Models EZ-6100 & 6110)
- Audible continuity tone with 5 settings (Models EZ-6100 & 6110)
- Nominal DC volt accuracy 0.5% of reading (Models EZ-6100 & 6110)
- Zero adjust feather-touch button
- Low and normal power Ohm ranges
- 300 hours minimum continuous operation with two 1.5V “AA” batteries
- 3½ digit LCD indicates the function, reading and feature simultaneously
- Exclusive FIVE-YEAR Warranty!

For more information on the EZ-Meter series or any of the other fine AWS instruments call your local distributor or contact A.W. Sperry Instruments Inc., 245 Marcus Blvd., Hauppauge, N.Y. 11788 • 800-645-5398 Toll-Free (N.Y., Hawaii, Alaska call collect 516-231-7050).

## A.W. SPERRY INSTRUMENTS INC.

The Measurable Advantage.

Circle (3) on Reply Card

New Orleans Marriott hotel. It combines management and technical sessions with an intensive program covering new markets for the sound and electronic systems contractor.

In addition, the conference again offers the benefit of being concurrent with the Electronic Distribution Show and Conference, where a healthy percentage of the exhibits are of direct interest to sound and electronics systems contractors.

Information about the National Sound and Electronic Systems Conference is available from the National Sound and Communications Association, 5105 Tollview Drive, Rolling Meadows, IL 60008, 1-312-577-8360.

### NATESA study offers solutions to service problems

The National Association of Television & Electronic Servicers of America’s (NATESA) study of problems that afflict all servicers

and add to the cost and frustrations of set owners, servicers and set producer/marketers, has revealed several simple solutions.

(1) Costly multiplicity of forms required by warrantors to authenticate compensation claims could be better served if each company authorized use of the NATESA Service Order form.

(2) Parts procurement policies and procedures by various companies often cause serious delays in completing service and add to costs and time delays to servicers and set owners. The study indicates that installing toll-free phone numbers can eliminate misunderstandings.

(3) Service problem, back-up toll-free numbers can reduce cost of service to purchasers of your brand and servicers, resulting in better acceptance for your products.



Coming in the March

## ELECTRONIC

Servicing & Technology


**Microprocessor...revolutionizing electronics.** A look at some of the most elementary concepts in microprocessor operations explains this development in electronics.

**How to choose the right interactive video equipment.** With the movement of computers out of the expensive, elitist category, interactive video has become a popular way to present material.

**Servicing excessive high voltage, part 2.** Operation and servicing of high-voltage regulators in solid-state color TV receivers are explained.

**Chassis — Zenith 19FC45**  
**PHOTOFACT — 1466-3**


1

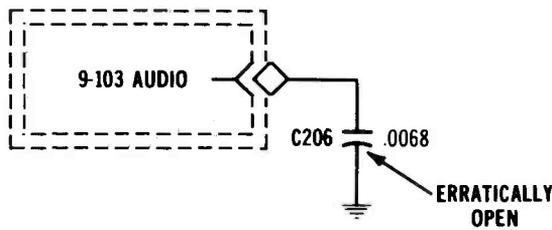

**Symptom** — Intermittent noise in sound, heard at all volume levels  
**Cure** — Check capacitor C206, and replace it if open

**Chassis — Zenith 20CC50z**  
**PHOTOFACT — 1238-3**


2

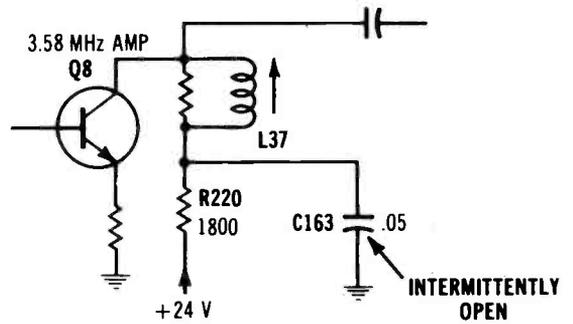

**Symptom** — Vertical color stripes appear erratically  
**Cure** — Check capacitor C163, and replace it if intermittently open

**Chassis — Zenith 19BG1z (monochrome)**  
**PHOTOFACT — 1692-2**


3

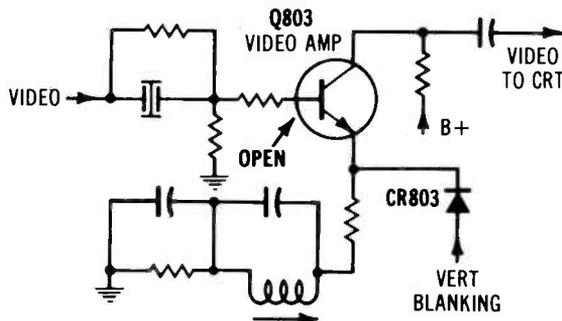

**Symptom** — Retrace lines in a low-contrast picture  
**Cure** — Check video-output transistor Q803, and replace it if open

**Chassis — Zenith 20CC50z**  
**PHOTOFACT — 1238-3**


4

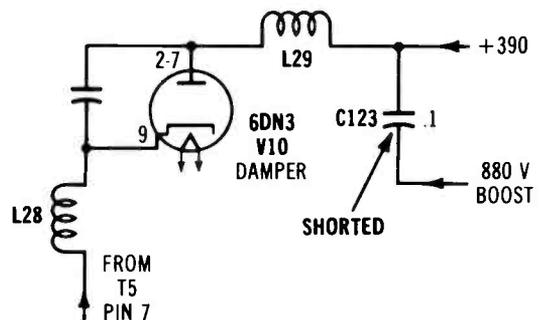

**Symptom** — Loss of HV; horizontal-output plate glows red  
**Cure** — Check capacitor C123, and replace it if shorted

**Chassis — Zenith Space Command with Zoom**  
**PHOTOFACT — many**


5

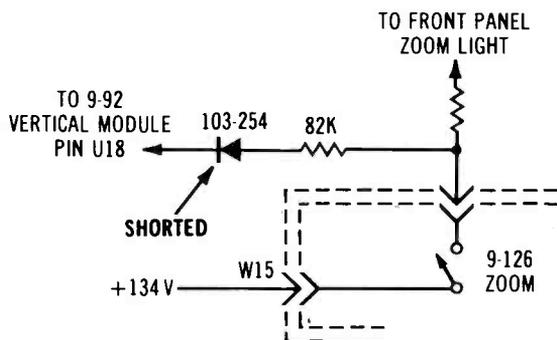


**Symptom** — Insufficient vertical height in non-Zoom operation  
**Cure** — Check diode shown here, and replace it if shorted

**Chassis — Zenith 25DC57**  
**PHOTOFACT — 1315-3**

6

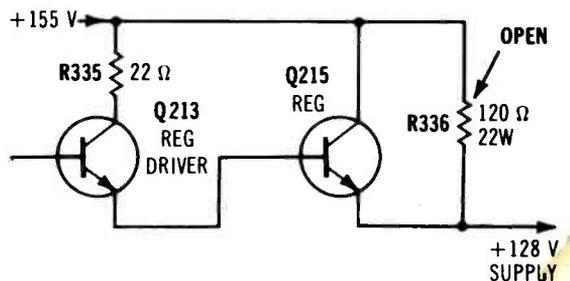

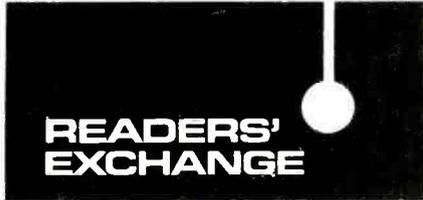**Symptom** — Loss of raster; regulator transistor overheats  
**Cure** — Check 22W dropping resistor R336, and replace it if open



**READERS'  
EXCHANGE**

**Needed:** Sencore Mighty Mite VII tube tester, model TC162. State condition and price. Call 1-512-968-3913 or write *Max Emerson, Rt. 2, Box 345, Weslaco, TX 78596.*

**Needed:** Instruction manual for Electronics Measurement Corporation model #215 tube and transistor tester. *R. L. Brown, Enterprises Unlimited, P.O. Box 1244, Carson City, NV 89701.*

**Needed:** Service schematic for Magnavox model 10S150D b&w solid state TV set, serial #86249, chassis #U91507. Will buy, pay for copy or copy and return. *Mrs. Magdalene Tyler Ramos, P.O. Box 214 Hub Sta., Bronx, NY 10455-0214.*

**Needed:** BEAM-A-SCOPE SW band loop antenna (external plug in) for GE radio, model 260. *J. F. Perry, Box 488, Lewisporte, Nfld., Canada A0G 3A0.*

**Needed:** Sam's Photofact folders 1536 through 1927, all or part, in sequence. Also sales and service literature and test equipment items from the early days of radio for a museum display. *Bill Springer, 923 Nelda, Houston, TX 77088.*

**Needed:** A 50 $\mu$ A meter with a 4 $\frac{1}{2}$ -inch square case to replace a bad one in an old Ideal Instrument VOM that came with an RCA Radio Course. *Donald Coleman, 231 Kershaw Court, Joppa, MD 21085.*

**Needed:** Schematic for a PRB custom hi-fi receiver, model 8TPR-888P. *Robert Alvarez, 424 Denver, San Antonio, TX 78210.*

**Needed:** Three #51 and two #45 tubes. Will pay a reasonable price. *Gus A. Green, 12692 Green St., Boron, CA 93516.*

**Needed:** Manual and schematic for a Paco model G-30 RF signal generator. Will buy or copy and return. *Krist Pirovsky, 211 Rose Ellen Drive, Crown Point, IN 46307.*

**Needed:** Any leaflets, brochures, handouts, etc. that would help me learn more about radio, audio and video technology. *Ebby K. Joseph, "Ramalyan", Pedder Rd., Cumballa Hill P.O., Bombay 400 026, India.*

**For Sale:** Sencore TC 162 tube tester, \$100; Sencore handy "75" substituter, \$40; Mark IVCUV tuner subber, \$45. *Robert Garrett, 1259 Carl St., Alton, IL 62002, 1-618-465-8950.*


**For Sale:** B&K model 1460 oscilloscope in excellent working condition, \$375. *Tim Allen, Douglas Television Service, 2540 Trenainsville Rd., Toledo, OH 43613, 1-419-475-9322.*

**For Sale:** Sencore VA48, like new, best offer over \$600. Also a TF46 Super Cricket, best offer over \$100. *Mike Shepherd, 394 E. Hwy. 20, Republic WA 99166, 1-509-775-3035.*

**For Sale:** Radio Shack-TRS-80 microcomputer, model 1, level II, 16K, including 32K expansion interface and RS 232C board. Shipping prepaid, \$1460.00. Also a Macrotronics-TM-800 ham interface for TRS-80 microcomputer. Includes M-80 (version 2), M-800 module, FSD-1 and AFSK. Factory assembled and tested in original packing, \$350.00. Also RCA master voltomist type 510A, \$150.00, shipping prepaid. *William Shevtchuk, Clifton, NJ. Please call: 201-471-3798.*

**For Sale:** B&K 415 generator; B&K CR143 CRT tester, B&K 1076 analyst. Best offer. *Reiney's TV, 4733 Lewis Drive, Port Arthur, TX 77640.*

**ES&T**

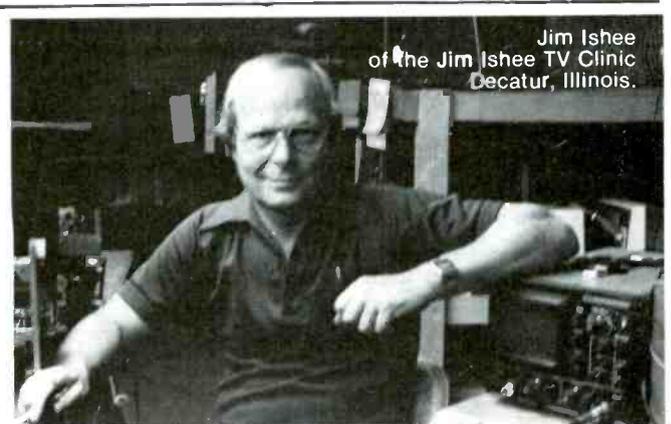

Jim Ishee  
of the Jim Ishee TV Clinic  
Decatur, Illinois.

**For 14 years Jim Ishee  
has relied on one  
electronics remanufacturer.**

Like so many professional TV service dealers, Jim Ishee knows the importance of fast, quality service. That's why, year after year, he's turned to PTS for quality remanufactured tuners and modules. Because PTS puts quality service first, customers

like Jim Ishee keep coming back. There's one electronics remanufacturer you can depend on, year after year, for quality tuners and modules.

**Only One.**



**PTS CORPORATION**

For the name of the PTS Distributor or Servicenter nearest you write PTS Corporation, P.O. Box 272, Bloomington, IN 47402

Circle (4) on Reply Card

February 1982 *Electronic Servicing & Technology*

# Stumbling blocks on the CET exam

Most of us think that we will have difficulty on the certification exams in areas in which we have not had much experience—such as PIOs and PIAs in microcomputers, disk drive interfaces, or earth station frequency converters. You may have trouble there, but that isn't where most of us get into trouble on the exams. Instead it is usually on basics—the things you once learned and felt comfortable with, but may not have had the opportunity to use very much since then.

Here is a sampling of the types of questions that keep many techs from becoming certified. See how you do. If they are “duck soup” for you, you should have little problem with the exam. If you find them tough, bone up a little and when you do take the exam, you will be ready.

1. This is the formula for capacitive reactance:

$$X_c = \frac{1}{2\pi fC}$$

If the size of the capacitor decreases, what happens to the reactance?

- it increases
- it decreases


2. What is the formula for finding the time constant in an RC circuit?

- $T = RC$
- $e = MC^2$

3. Now that you know the formula, how long will it take a resistor/capacitor combination to charge to 67% of the supply

voltage if the resistor is 2700  $\Omega$  and the capacitor is 20,000 microfarads?

- forever
- 540 seconds or 9 minutes.

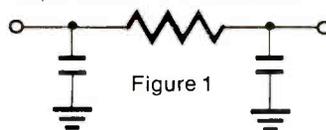

4. What kind of a filter is shown in Figure 1?


- low pass
- hi pass

5. Because higher frequencies are passed to ground through the caps, it is called a hi-pass filter.

- false
- true

6. If the resistor was 100  $\Omega$  and the caps were .001 picofarads, what effect would the filter have on 60Hz ripple in a power supply?

- practically none
- lots

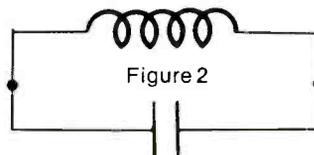

7. Figure 2 is a parallel-tuned circuit. The total combined impedance at resonance is:

- high
- low

8. Frequencies below the resonant frequency pass through the \_\_\_\_\_ easiest.

- cap
- coil



Figure 3

9. Figure 3 is a series-tuned circuit. At resonance, which element has the higher impedance?

- coil
- cap
- both the same

10. Below the resonant frequency, which element will have the higher impedance?

- coil
- cap

11. In Figure 3, could it be that the impedance of C is 1000  $\Omega$  and the impedance of L is 5000  $\Omega$ , yet the total impedance is only 4000  $\Omega$ ?

- yes
- no

12. If, in Figure 2, the coil is 1000  $\Omega$  and the cap is 5000  $\Omega$ , what is the total impedance?

- 125  $\Omega$
- 1250  $\Omega$
- 12,500  $\Omega$

13. Which is correct for normal 110V house current?

- RMS = 110V; P-P = 145V; Avg. = 290V
- Peak = 145V; Avg. = 0V; RMS = 110V

14. If the formula for wavelength is:

$$f = \frac{984,000}{\lambda}$$

then what size antenna would be needed for a  $\frac{1}{4}$ -wave mast at 27MHz?

- 36.44 feet
- 9.11 feet

15. What voltage will a lead-acid battery have if fully charged?

- 1.4V
- 2.1V

16. An LED will light up when forward-biased.

- ( ) true
- ( ) false

## ANSWERS

- |      |       |
|------|-------|
| 1. a | 9. c  |
| 2. a | 10. b |
| 3. b | 11. a |
| 4. a | 12. b |
| 5. a | 13. b |
| 6. a | 14. b |
| 7. a | 15. b |
| 8. b | 16. a |

This information was submitted courtesy of Electronics Technicians Association (ETA). For more information regarding the Associate Level Certification Test, contact Dick Glass, CET, Route 3, Box 564, Greencastle, IN 46135.

**ETA**

## CALENDAR OF EVENTS

### February

2-4

Southcon '82, Orlando, FL, at the Sheraton/Hyatt. For more information call (800) 421-6816.

23-25

NEPCON WEST, Anaheim Convention Center, Anaheim, CA. For more information, contact Cahners Exposition Group, 222 W. Adams St., Chicago, IL 60606, (312) 263-4866.

### March

19-21

Computer Fair, Civic Auditorium, Brooks Hall, San Francisco, CA. For more information call (415) 851-7075.

23-25

Southcon/82 Show and Convention, Sheraton Twin Towers Hotel, Orlando Hyatt Hotel and Holiday Inn International Drive, Orlando, FL. Call (800) 421-6816 for more information.

29-May 1

1982 Electronic Distribution Show and Conference, New Orleans Hilton, New Orleans, LA. Contact David L. Fisher, Electronic Industry Show Corp., 222 S. Riverside Plaza, Suite 1606, Chicago, IL 60606, (312) 648-1140.

### April

14-18

Electronic Home Entertainment Show, Arlington Park Race Track Exposition Hall, Chicago. Contact Expo Management Inc., Suite

S2-132 Arcade, The Apparel Center, Chicago, IL 60654, 1-312-329-1191.

23-25

Hamvention '82, Dayton Hara Arena, Dayton, OH. For more information call (513) 277-5314.

29-May 1

Electronic Distribution Show, New Orleans Hilton, New Orleans, LA. For more information call (312) 648-1140.

### May

10-12

The 32nd Electronic Components Conference, Sheraton Harbor Island Hotel, San Diego, CA. Contact program chairperson D. J. Bendz, IBM Corp., Dept 649/014-4, 1701 North St., Endicott, NY 13760.

11-15

National Association of Television & Electronic Servicers of America (NATESA) 31st Annual Convention, Indian Lakes Resort, Bloomingdale, IL. Contact Frank J. Moch, 5930 S. Pulaski Rd., Chicago, IL 60629, 1-312-582-6350.

18-20

Northcon/82 Show and Convention, Seattle Center Coliseum, Seattle, WA. Call (800) 421-6816 for more information.

25-27

Electro '82, Hynes Auditorium, Boston, MA. For more information, call (800) 421-6816.

### June

6-9

Summer CES '82, McCormick Place, Chicago, IL. Contact Consumer Electronics Shows, Two Illinois Center, Suite 1607, 233 North Michigan Avenue, Chicago, IL 60601, (312) 861-1040.

ES&T

# NOW, a mini-scope with the features most wanted by field engineers!



B&K-PRECISION MODEL 1420 \$825

This new 15MHz dual-trace mini-scope was designed by B&K-PRECISION engineers to respond to the special needs of field engineers... a *mini-scope* with *lab-scope* features.

It easily fits into a standard *attache* case with plenty of storage room for a DMM, tools and accessories. The 1420 can be powered from the AC line, 10-16VDC or an optional *internal* battery pack.

The rugged 1420 features dual-trace operation and an honest 15MHz response, with useful response beyond 20MHz. An efficient rectangular CRT displays waveforms with good readability under all field service conditions.

There is no sacrifice of features or performance for compact size. The 1420 has 18 sweep ranges from 1  $\mu$ S/div. to 0.5S/div. in a 1-2-5 sequence; variable between ranges. Sweep magnification is X10, extending the maximum sweep rate to 100nS/div. For use with computer terminals or video circuits, a video sync separator is built in. Automatic selection of chop and alternate sweep modes is provided, as is front-panel X-Y operation.

The Model 1420 measures only 4.5 X 8.5 X 12", weighs 7.75 lbs., with batteries and comes with two 10:1 probes.

FOR IMMEDIATE DELIVERY contact your local distributor or call TOLL-FREE, 800/621-4627 for a 16-page catalog brochure on the complete B&K-PRECISION oscilloscope line.

**BK PRECISION**


**DYNASCAN  
CORPORATION**

6460 West Cortland Street  
Chicago, Illinois 60635 • 312/889-9087  
Intl. Sls. 6460 W. Cortland St., Chicago, IL 60635  
Canadian Sales: Atlas Electronics, Ontario.

Circle (9) on Reply Card



**Figure 1** (left). High voltage in the RCA CTC35 chassis is regulated by providing a constant current on the high voltage. When the picture tube draws increased current, the 6BK4 regulator-tube current is reduced, and vice versa. Control of the 6BK4 comes from the +650V boost supply.

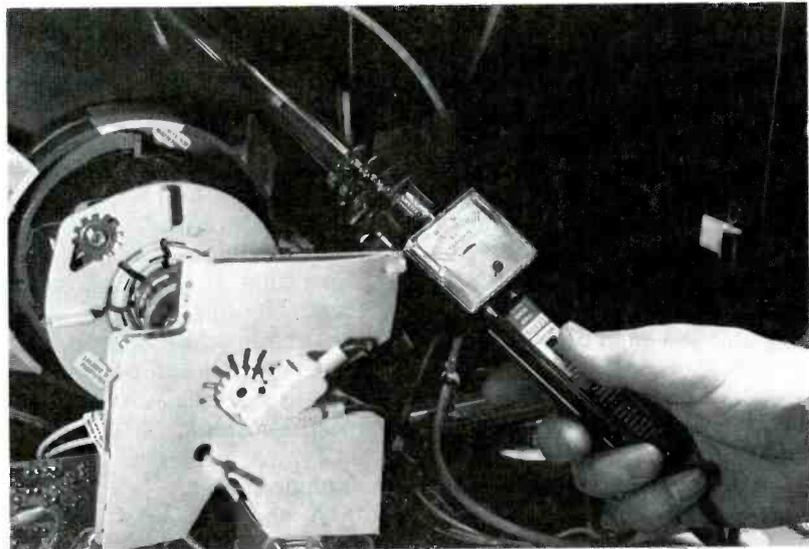

**Figure 2** (right). High voltage should be measured at the picture-tube anode button using a high-voltage probe with internal (as shown) or external meter. Be certain the cold wire of the probe is connected to the picture-tube shield ground.

rent that increases the HV also increases the B-boost voltage, which raises the 6BK4 grid voltage, causing it to conduct more current and reduce the HV almost down to the original value. Of course, increased CRT current and reduced HV reverses the action with decreased regulator current.

The Figure 1 regulation is improved by dc voltage brought from the drive controls (at the CRT cathodes) through R180 to the 6BK4 grid. The drive-control dc voltage varies with brightness levels. A higher brightness reduces the positive voltage; a reduced brightness raises the positive voltage. Therefore, this voltage sample adds to the boost-voltage change coming through R176. Without R180, the regulation might be  $\pm 500V$ , but it can approach  $\pm 100V$  with the R180 voltage.

Two other factors make this excellent regulation possible. A 6BK4 (or similar tube) has a very high gain. Current cutoff is produced by only about -13V (relative to its cathode), while plate current of about 1.5mA requires about -2V to -3V. That is a range of only 10V from zero to maximum. Obviously, the precise values and temperature drift of resistors R176 and R177 are very critical, and no gas in the 6BK4 or leakage in C84 can be tolerated.

Also, the 6BK4 cathode is clamped by connection to the +400V supply, allowing a larger percentage of the +650V B-boost voltage to reach the grid.

Therefore, the 6BK4 grid voltage varies only from approximately +387V with maximum picture brightness to +397V when the picture is black. (These figures are modified slightly by the  $1000\Omega$  cathode resistor, which accounts for about 1.5V of the bias at minimum brightness, but the point is valid). This illustrates the futility of measuring the grid-to-ground voltage. A meter with  $10M\Omega$  input resistance will cut off all regulator current when connected from grid-to-ground. The 6BK4 bias should be checked *only* from grid to cathode.

The only accurate test of regulator operation involves measurement of the 6BK4 current. In the CTC35 circuit, the testing is made easier by the  $1000\Omega$  cathode resistor. By Ohm's Law, 1mA of current produces a voltage drop of 1Vdc. Therefore, connect any sensitive dc voltmeter across the  $1000\Omega$  resistor, after it has been checked for resistance previously when power was off. A power-on voltage reading of 0.5V indicates a current of 0.5mA. A reading of 1.5V translates to 1.5mA (which usually is the maximum current that is safe for the tube).

Some books and many technicians maintain that these regulators should be adjusted by monitoring the CRT high voltage while the HV *adjust* control is rotated to obtain the rated value of high voltage. Unfortunately, that method produces approximate results of questionable accuracy,

while permitting possible overcurrent of the regulator to ruin the tube later.

#### Unavailable wiring and components

The following method is recommended whenever the chassis wiring is not available for voltage tests (perhaps during service calls):

(1) Check the voltage vs. performance by monitoring the HV at the picture-tube anode (Figure 2) while the television brightness is varied from a black picture to full brightness. Watch for any change of picture size, blurring of the focus, rustle of varying HV, or the sound of arcing. Notice the range of the high voltage. If none of these symptoms are seen, and the high voltage is approximately normal without excessive drop at high brightness, the regulation probably is adequate and nothing further is needed. But if some symptoms are noted and the high voltage changes excessively, the regulator needs repairs or adjustments.

(2) Decrease the receiver's brightness to obtain a dim picture. Monitor the HV with HV probe and meter as the R11 HV control is varied between about 22kV and 30kV. If this wide range is obtained, the sweep and the regulator probably are normal, and R11 should be left adjusted at 25kV. Repeat Step 1 for identification of any symptoms. If no adverse symptoms are noted, the adjustment is finished.

## High voltage

(3) If the high voltage was not varied by the R11 rotation in Step 2, the 6BK4 tube is bad, the 1000  $\Omega$  cathode resistor is open or one of the resistors is out of tolerance. Replace the 6BK4 and repeat the test. If no HV variation is found, the chassis needs repairs. If the HV changes normally, set it properly and test as in Step 1.

### Accessible wiring and components

When the chassis wiring and components are accessible (on the bench), the testing procedure is longer and more accurate:

(1) Connect a VOM, VTVM or digital multimeter across R181 (the 1000  $\Omega$  cathode resistor), remembering that the cathode end is positive. Select a range that can measure 1.5V with accuracy, and apply power to the receiver, obtaining a good picture.

(2) Turn down the brightness and contrast until no picture or raster can be seen, then adjust R11 HV control for a meter reading of +1.5V or +1.6V.

(3) Turn up the brightness slowly while watching the meter reading drop smoothly in step with the brightness increase until the meter barely indicates zero voltage with the CRT screen showing normal high brightness.

(4) Locate the 6LQ6 screen grid (pins 1 and 7) on the tube socket and measure the screen-to-ground voltage (Figure 3) while adjusting the horizontal-efficiency (or linearity) coil core for minimum meter voltage reading.

(5) Repeat Steps 2, 3 and 4 until no improvement of results can be obtained.

(6) The high voltage obtained will be totally correct for the line voltage applied to the receiver and its component values. Next, measure the HV at the picture tube. If it is lower than the 24kV to 25kV that is average for the model, the output tube or damper tube is weak or the main supply voltage is too low. If it is high, the screen voltage and the capacitors across the yoke socket should be tested. Open yoke capacitors increase the HV.

Remember that any major deviation

from the expected results of these tests and adjustments can indicate a component defect in horizontal-sweep or regulator circuits.


Symptoms of blurred focus, dim picture (when the regulator current cannot be reduced to zero by brightness adjustments) and slow warmup might point to a weak picture tube. However, a narrow picture, blooming at high brightness or erratic white flashes in the picture suggest component problems in horizontal-sweep or HV-rectifier areas.

Typical problems in this circuit include these:

- A shorted 6BK4 will burn up R181. If the tube (but not the resistor) is replaced, the regulation remains completely inoperative. The HV rises to about 32kV when the picture tube is black, and the picture size varies with brightness. R181 should be replaced anytime its value is out of tolerance.
- Welds sometimes break inside the large 6BK4 insulated plate cap (Figure 4) causing loss of regulation, arc lines in the picture and possibly excessive heat from cap arcs.
- Many 6BK4 tubes become black internally after considerable operating time. This often indicates a weak tube or an imminent failure.
- Resistance changes in R180, R178, R176 and/or R177 can cause total loss of HV if the 6BK4 grid voltage is increased by the change. Or, loss of regulation occurs when resistance changes reduce the grid voltage.
- The slightest leakage in C84 causes a pulling in on the left edge of the picture. Increased leakage can kill the HV completely. Operate the receiver briefly with the 6BK4 cap removed to prove regulator current is the cause. A normal picture without HV regulation proves the regulator operation is faulty.
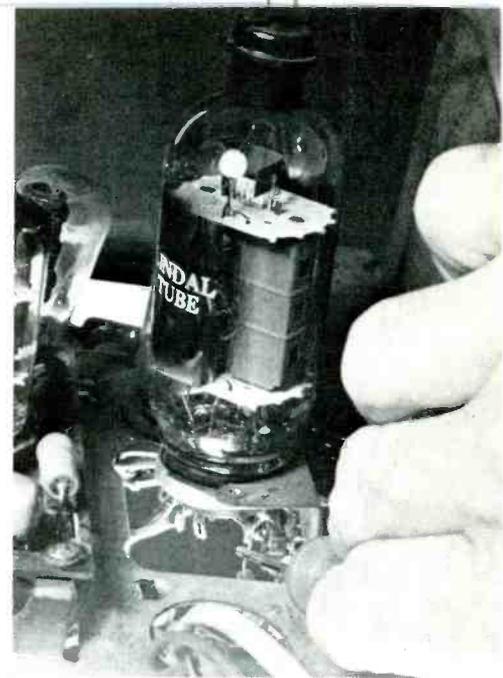
### Pulse-load regulation

HV regulator tubes of the 6BK4 variety were costly and could emit X-rays if the applied voltage was excessive. Therefore, the television designers next introduced



*pulse regulation.* One version used extensively in Zenith models is shown in Figure 5.

The purpose of pulse-amplitude regulation was to stabilize the ac load on the horizontal-sweep system by adding a tube to simulate a variable resistor that changed the sweep load inversely to the load of the high voltage. Again, the idea was to increase the regulator's ac load on the sweep when the HV current was low and decrease it when the HV current was high.


Although the basic premise is simple, there is a severe technical problem: a pure resistive linear load across the deflection signal produces several unacceptable symptoms, including poor linearity and reduced width.

A solution was worked-out by the design engineers. The ac-load regulator tube was biased and keyed so its conduction occurred *only* during the tip of each deflection pulse. This conduction was forced to occur at the same time as the HV-rectifier conduction. Therefore, the total load of HV-rectifier and ac-regulator current determined the amount of high voltage, and no undesirable changes were produced when the ratio of the two currents changed with variations of picture-tube brightness and the accompanying regulation action.

Bias for the 6JH5 regulator tube of Figure 5 (Zenith 20CC50 in Photofact 1238-3) is the difference between the pin-1 cathode dc voltage and the pin-5 grid ac+dc

**Figure 3 (left).** Several older RCA chassis have the horizontal output-tube socket on a small shelf that allows measurement of control-grid and screen-grid voltages.

**Figure 4 (right).** The large insulated plate caps on 6BK4 (or similar) regulator tubes can cause several problems. Heat can remove all temper from the spring cap, or the weld can break, causing arcing or loss of regulation. The plastic insulation shown here has crumbled from heat and age. Arcs probably will occur later.

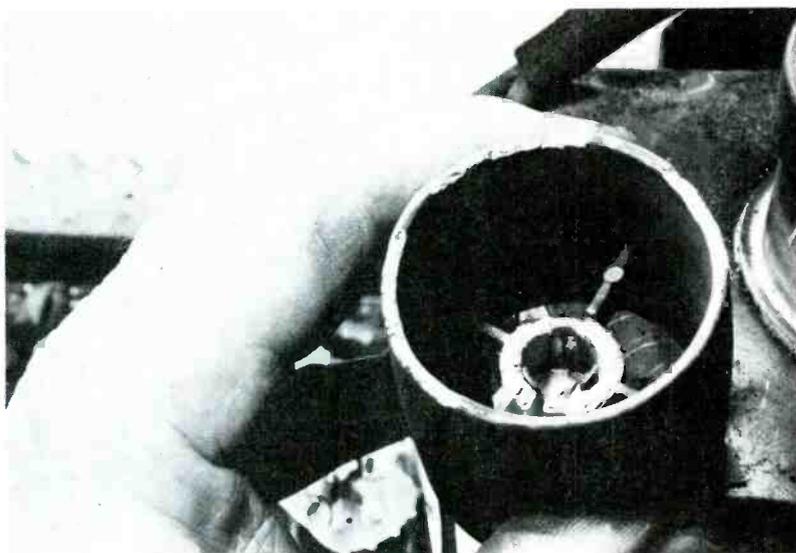

combined voltage. The cathode is clamped to the +390V supply by diodes X26 and X28 (part of a fail-safe circuit to be described later). Grid voltage is a composite of differentiated positive-going pulses (from the horizontal oscillator through C121 to the grid) plus a steady dc voltage from the HV-adjust control.

Boost of +880V is reduced by varistor R178 and resistor R261 before reaching the top of R21 HV-adjust control. The low end of R21 returns to ground through R262 and R172. Output of this voltage divider comes from the center lug of R21, passing through R174 (part of a filter) and R175 (parasitic suppressor) to the 6JH5 grid. Incidentally, varistor action of R178 increases the percentage of boost-voltage *change* that reaches the regulator grid. Any increase of boost voltage decreases the varistor resistance, passing an even higher increase to the regulator.

When the receiver is normal in all ways except incorrect regulation, use the following sequence:

- Turn up the brightness to just below the blooming point, and measure the HV at the picture tube.
- Turn down the brightness until no raster can be seen, then rotate R21 until the high voltage is the same as when measured at full brightness in the previous step.
- Repeat the previous two steps to remove any original error. Finally, monitor the HV while the

brightness is adjusted through all levels. If the HV does not vary more than about 2kV, the regulator is adjusted correctly.

If no variation of HV is noticed when R21 is rotated, or the HV is consistently above or below the rated value, the horizontal-sweep or regulator circuit must be tested and repaired before the next adjustment is attempted.

#### Fail-safe operation


The 6JH5 and its normal operation are part of a fail-safe circuit to prevent production of X-rays if the 6JH5 regulator should become inactive.

Notice the polarity of diodes X26 and X28 in Figure 5. Each anode is toward the 6JH5 cathode, and there is no source of positive voltage except 6JH5. Therefore, when the 6JH5 draws plate/cathode current, the diodes are forward biased, conducting the cathode current to the +390V supply (this has no effect on the +390V supply because the regulator current is very low). A sample of the 6JH5 cathode positive voltage (about +391V) is sent through R192 to the grid of 6LB6, the horizontal-output tube. This does not upset the normal negative bias there because an equal negative voltage comes from "rectification" of horizontal pulses by varistor R193 (through R159 to the same grid). Therefore, normal operation of the 6LB6 horizontal-output tube is not degraded or changed.

The balance of negative and

positive voltages is altered drastically if regulator 6JH5 is dead or draws no current. Diodes X26 and X28 have no 6JH5 cathode current. They become open circuits, disconnecting the 6JH5 cathode and the input of resistor R192 from the +390 supply, and reducing the voltage there to nearly zero. The balancing positive voltage through R192 is now missing, but the negative voltage from VDR R193 continues to function. Therefore, the dc voltage at the 6LB6 control grid changes to -90V or more. This reduces the maximum plate current of the 6LB6 and weakens the horizontal-deflection operation, producing a narrow and dim picture whose width varies with the brightness. A byproduct of the weak horizontal operation is a reduction of the maximum high voltage. The reduced high voltage prevents generation of X-rays; and the narrow, slightly blurred picture inspires the viewer to call for repairs.

In Zenith model 20CC50 (and others using the same circuit), symptoms of a narrow picture (especially on the left edge of the picture), poor focus, and picture size that changes noticeably (from brightness variations) indicate a loss of HV regulation. Proof of fail-safe operation can be obtained easily by shorting across X26 and X28. When loss of 6JH5 regulation has caused the symptoms, the symptoms will disappear, but the HV then will be excessive, perhaps causing arcing.

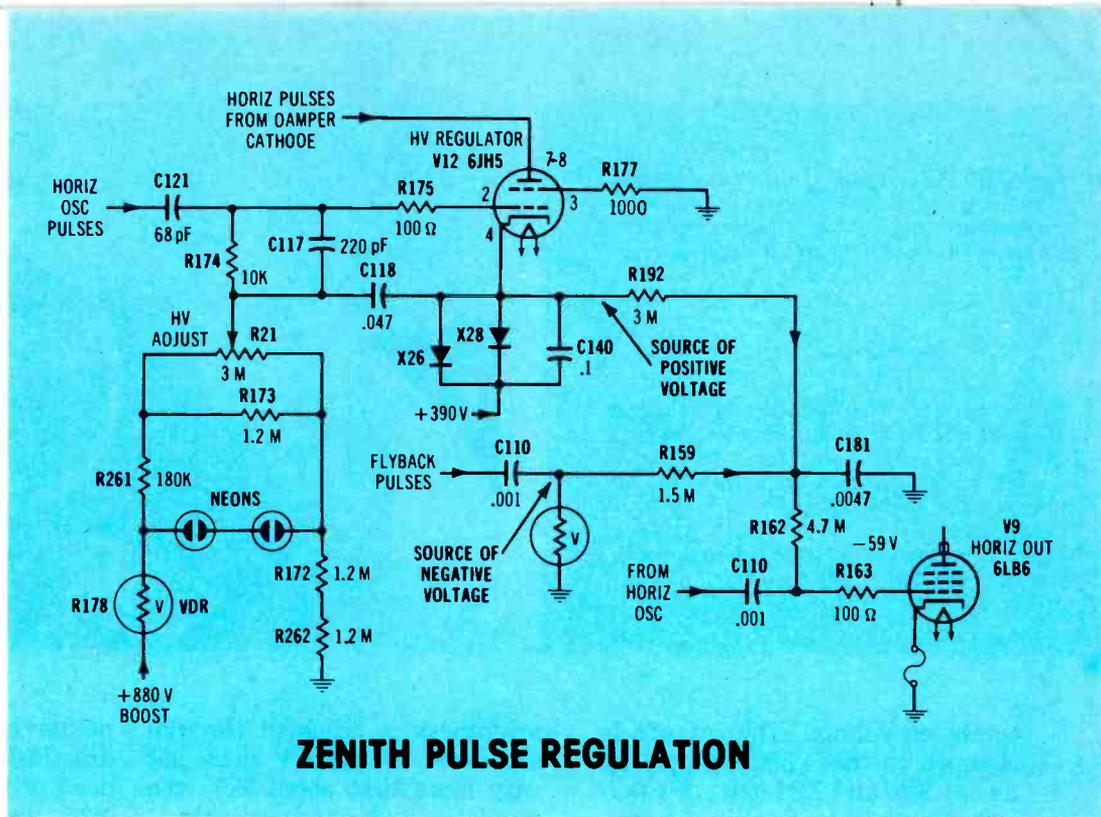

## High voltage

The only weak spot in the X-ray protection is that a very small 6JH5 current forces X26 and X28 to conduct, thereby preventing operation of the fail-safe circuit. Also, a short in X26 or X28 prevents activation of the fail-safe circuit, regardless of the 6JH5 cathode current.

Typical failures in this (and similar Zenith circuits) include the 6JH5 tube, resistor R177 (perhaps the tube shorts first), and resistance drift in other resistors.

After tube replacement or circuit repairs, the regulation should be adjusted, as described before.

### Regulation by output bias

One additional basic type of sweep/HV regulation has been incorporated in tube-equipped color receivers. Although the regulator operation in Sylvania 3M20 (Figure 6 from Photofact 1434-1) increases the grid bias of the 6LW6 horizontal-output tube to reduce the high voltage, and control does not come from any variation of tube gain. Instead, the increased negative voltage at the control grid limits the maximum current that can flow at the tip of the sawtooth drive signal. In other words, the varying grid bias changes the *power* that is applied to the yoke and flyback system.

During normal operation at maximum brightness, negative

voltage (from pulse rectification by varistors R110 and R111) through R109 is applied to R108, which is connected to the 6LW6 grid. However, adjustment of HV-adjust control R113 provides an equal positive voltage at R108, also. The two voltages cancel, and therefore do not interfere with the output-tube bias or the maximum sweep power that is in operation then.

When the brightness is turned down, or the program fades to black for a time, the picture-tube current is reduced, causing the high voltage to increase. However, increased HV also is accompanied by increased negative voltage at the varistors. Because the positive voltage from the HV-adjust control now is fixed (it varies only during its adjustments), the negative and positive voltages are not equal. The negative is dominant, thus forcing the 6LW6 control-grid bias up to about -100V (high brightness bias is about -60V). With the higher negative bias, the 6LW6 average plate current is decreased, which in turn decreases the sweep power and the HV. The higher negative bias decreases the HV nearly to the original value.

Regulation with this bias/power regulator is not as effective as that of the shunt systems described previously. Variations of  $\pm 2kV$  are to be expected.


There are no critical components in the Figure 5 circuit except R110 and R111 varistors. Do not install any varistors except ones with characteristics precisely equal to the originals. Substitution of unlike varistors will make the regulation completely ineffective.

When new varistors are installed, they should be checked by monitoring the control grid voltage of 6LW6 output tube at low and high brightness. Turn down the brightness to eliminate the raster and measure the grid voltage. If it is less negative than about -90V, either the varistors are not matched to the circuit or R113 is badly adjusted. Reset the regulation by the method given before, and then recheck the black-screen grid voltage. The repair is not finished unless the grid voltage is between -90V and -110V when the raster is blacked-out.

### Varistor rectification

Several years ago when varistors first were employed to replace diodes in small-current voltage sources, several technicians denied that varistors were capable of rectification. Certainly, a varistor by its nature must draw the same current on positive peaks as on negative peaks of *sinewaves* (when no dc voltage is present). However, all applications (such as in Figure 5) that produce dc

**Figure 5 (left).** High voltage in Zenith 20CC50 is regulated by providing a constant ac load on the horizontal-sweep system. A lighter load from decreased CRT current is offset by a heavier load from the regulator tube, and vice versa. Complete loss of 6JH5 cathode current activates the fail-safe circuit that overbiases the horizontal-output tube to reduce width and high voltage, as explained in the text.

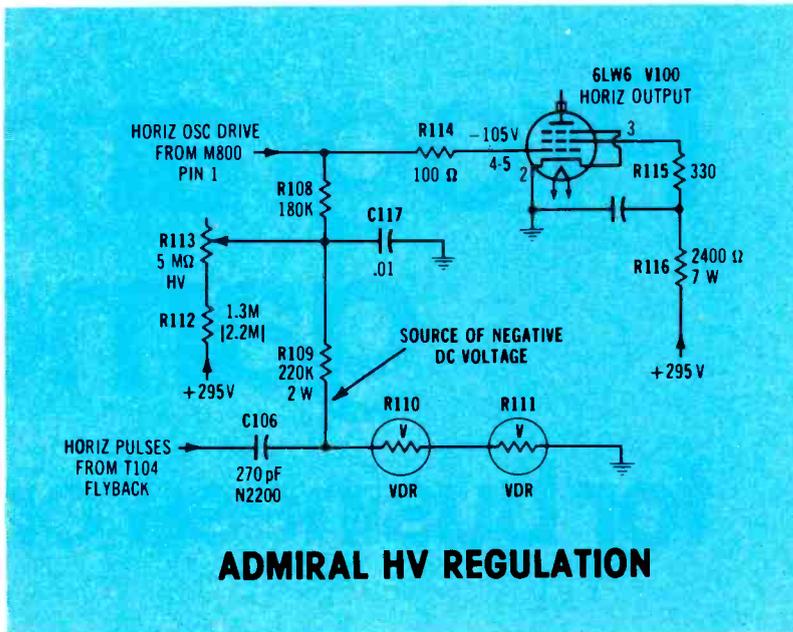

**Figure 6 (right).** Admiral 3M20 (Photofact 1434-1) regulates the high voltage by controlling the maximum current in 6LW6, the horizontal-output tube. Higher pulse amplitude from reduced CRT current is offset by increased negative voltage from the VDRs, while the balancing positive voltage from R113 is fixed. A more-negative output grid limits the maximum plate/cathode current, thus controlling the power and pulse amplitude coming from the flyback.

voltage from varistors apply *pulses* to the varistors, not sinewaves.

A pulse fed through a coupling capacitor has its zero-voltage point near the base line and far removed from the tip (the precise position depends on the duty cycle of these pulses). Therefore, the voltage level in the positive peak of a positive-going pulse is much greater than the voltage level of the negative peak. The stronger positive-peak *current* overpowers the weaker negative-peak *current*, so the effect is to produce a small negative voltage as through a diode is connected with its anode at the coupling capacitor and its cathode grounded.

There are several important points to remember. Polarity of the dc voltage obtained by varistor rectification of pulses cannot be reversed by reversing the varistor; instead, *the pulse polarity must be inverted*. Positive-going pulses produce negative dcV, while negative-going pulses produce positive dcV.

Also, a varistor is an inefficient rectifier of pulses (and cannot rectify sinewaves or triangles). The ratio of positive versus negative conduction is much lower than for diodes. If diodes of the proper polarity were to be substituted for R110 and R111 in Figure 5, the negative dc voltage produced probably would be three or four times

higher. In addition, diodes are more susceptible to damage from arcs or overloads. For these reasons, *do not replace varistors with diodes*.

### Summary

Tube-equipped TV receivers have very few potential defects that can increase the HV significantly. Open retrace-tuning capacitors (usually connected across the horizontal-yoke coils) can increase the high voltage by no more than 2kV. Loss of dc-shunt or ac-shunt regulation can raise the HV above 30kV when the fail-safe backup circuit continues to operate. Loss of both regulation and fail-safe circuit operation at the same time might increase the HV to nearly 50kV, but this is very unlikely. Shorted turns in the flyback primary winding merely kills all high voltage.

Unfortunately, old myths continue to confuse many situations. Years ago, a technician wanted to know how to increase the rid drive to a horizontal-output tube so the high voltage would increase enough to permit bright operation of a much larger picture tube. In reality, grid drive has little to do with the amount of high voltage. If the grid drive is below the design value, the high voltage *will* be reduced. However, increasing the drive above normal level only

distorts the sweep linearity, sometimes causing drive lines.

It is possible for unauthorized rewiring of circuit values by a misguided technician to produce excessive high voltage. I remember a classic case with an RCA in which the customer complained of horizontal-tube replacements every two to three weeks. A quick check of the line voltage proved it was not responsible (although other similar cases had shown line voltages of up to 136Vac), and operation of the receiver appeared to be normal, with good HV regulation. However, visual and VTVM tests of the horizontal-output stage showed high screen voltage and several resistor changes. The previous technician, evidently trying to increase the picture brightness, had decreased the value of the screen resistor from the specified 16K to about 3K. This increased the boost voltage and the high voltage, so to restore regulator operation, he changed resistor values in the grid circuit of the 6BK4 regulator tube. Output and regulator tubes were overloaded by these changes, accounting for the repeated failures. Restoration of original values and an accurate regulator adjustment eliminated the problem.

**ES&T**

# Programming games for business or pleasure

By Walter Dean, production manager,  
Computer Concepts Corporation, Shawnee Mission, KS

Everybody knows that computers are expensive and should be treated with respect and decorum. But, behind the serious Dr. Jekyll facade of any business computer lurks a Mr. Hyde wanting to show everybody a good time.

You will likely find the data processing equipment in any facility used to pursue bandits across galaxies or to establish the resident chess champion. Take, for example, a small laboratory in central Texas that conducts research on secret Navy projects. The elaborate apparatus normally used to process marine data also presents a fairly good game of Space War. The computer will accommodate several players, each with his own joystick control and CRT. Like most space war games, the object is to french fry your fellow players while simultaneously staying in orbit around a star located in the center of the screen. The joysticks used in this game are surplus from actual fighter planes.

A company in the Midwest that manufactures radio navigation equipment for airplanes provides an even more subtle example. They make a color radar that uses several tiny computers—each one

only 3 inches long. It seems that the programming necessary to generate, analyze and display radar information on the color CRT does not entirely fill the allowable memory for these computers. Thus, the remaining room has been used to create a game similar to Space Invaders. The word is that this game is not available as an option once the unit is installed in the airplane.

Managers are reluctant to admit to what extent this “didactic programming” has displaced the intended purpose of their computers. In extreme cases, I’ve seen managers attempt to catch players by making subtle changes to the more popular game programs so a permanent record was made of the date, time and name of the person playing.

#### Widespread appeal

Although playing a computer game rarely accomplishes anything except to waste time and money, fun programs do have their place.

Computer Concepts Corporation is now realizing the appeal that a simple game of blackjack can add to a multi-thousand-dollar com-

puter package. I have actually seen a 9 kilobyte game sell a multi-terminal system and 5 man-years of software. This is something similar to a lighted vanity mirror selling a fleet of Cadillacs.

As a marketing strategy, Computer Concepts uses their favored games during idle hours at a convention. Salesmen who would otherwise be standing around in shoes they’ve worn three hours too long are suddenly interested in those cute things the programmers have cooked up. It was during one of these intermissions that they discovered how a computer can even beckon prospects from the booths of competitors. Then the salesmen turn the controls over to the newcomer and move smoothly into a sales pitch.

Practical use of games (let’s call it “applied gaming”) has also spread to installers and service men. When a new computer is delivered to the proud customer, the installing technician will bring up a game with lots of display magic and sounds. The idea here is to help convince the staff that the computer is not the enemy out to get their job, but a friend instead. The video display terminal (VDT)

has a lot of buttons, but a computer game can demonstrate that they are no more mysterious than those on a typewriter or an adding machine.

The service people at Computer Concepts use games as diagnostics. Sometimes, running a complex game that fills all available memory is a better sleuth than running a special diagnostic program for several hours.

It should come as no surprise that games have increased in sophistication over the years just as impressively as has the hardware itself (remember TV Pong?).

#### Static vs. dynamic

In creating a game program, it is sometimes useful to consider the possible categories now making the rounds. I have identified the following:

- Games of Chance—blackjack and roulette
- Board Games—chess or Othello
- Adventure—Cave or Wumpus
- Space—Star Trek or Space Invaders

Any of these games can be formatted to be either static or dynamic in nature. A static game is one that does nothing until the human enters data. After processing, the computer then generates a response and waits for more information. A dynamic game continues to evolve even in the absence of human stimulus. The gremlins of Space Invaders, for example, will march relentlessly toward your missile launcher, bombing their way through any obstacle, regardless of the player's attention to the game. In most forms of chess or Star Trek, however, the player could take a two-week vacation between moves with no detriment to the game. Dynamic games were not very practical before the days of CRT terminals.

In a dynamic game, a display moves and changes according to the current conditions. In static games, the player is usually asked to pretend that pieces moved in a natural manner and accept their current status based on a series of coordinates.

Star Trek is the classic—the Monopoly of computer games. There is no telling how many peo-

ple became programmers because of their exposure to those early versions of this game.

Based loosely on the TV show, Star Trek usually involves “flying” the Starship Enterprise around the galaxy, phasing down Klingons and other undesirable. The computer-generated Enterprise is appointed with an array of gadgetry that must be kept serviceable in order to “go where no man has gone before.” The game is further complicated by the natural hostility of Klingons and the recurring need to replenish the Enterprise.

These early forms of Star Trek had a simple, nondynamic nature. The captain of the Enterprise would enter a number representing a command and wait for the computer to tell him what had happened. You saw nothing move because in the early days everybody had teletype machines. A lot of time was spent waiting for the updated map of the galaxy to be printed out at 110 BAUD. As with traditional board games, play progresses only as long as you enter commands (in more advanced versions, though, a clock was kept running to terminate the game when the Enterprise had not been sufficiently zealous).

I have found that no matter how limited, any computer can be endowed with a challenging pro-

*The idea is to convince the staff that the computer is not their enemy.*

gram. Programmers must be respected for overcoming the fact that their computer was designed for business or science, and therefore cannot easily be made to go

“zap,” “pow,” or show explosions in Technicolor.

If you are interested in designing your own games, whether for business or pleasure, here are some random comments culled from my own experience.

Designing a game requires planning in at least three areas:

1. Display—How is the game to be presented to the player(s)? The considerations for displaying a game on a printer device vs. a VDT usually differ radically.
2. Algorithm—How does the game progress? In games where the computer represents one of the opponents (in the case of Star Trek, the computer is playing for the Klingons), how are intelligent moves selected for the computer?
3. Modeling—How is the game to be represented internally to the computer? No matter how you might fantasize the interior of a castle or the shape of a pawn, the computer must be told the essentials of your vision only in numbers.

#### Display

I have often been asked by novice programmers how objects are made to move smoothly across the screen of a VDT. The truth is, a computer simulates motion in the exact way as does a movie projector. That is, the object is displayed in constantly changing locations several times a second to give the object a smooth, natural movement. As you can see, this kind of effect would be impossible on a printing terminal, no matter how fast it might operate.

Here's a simple algorithm to illustrate this principle.

1. Select a starting place to print moving character
2. Print character
3. After a brief delay (long enough for the eye to see the character), erase the character.
4. Select a new place to print the character. (If relocated too far away, the character will appear to jump).
5. Return to Step 2.

## Programming games

If you are programming in BASIC, the algorithm above might be implemented as follows:

```
10 REM INITIALIZE VARIABLES:
  R = 10: C = 40: T = 9
20 REM PRINT CHARACTER:
  PRINT AT (R,C); "X";
30 REM KILL A LITTLE TIME:
  FOR I = 1 TO 1000: NEXT I
40 REM ERASE CHARACTER:
  PRINT AT (R,C); " "
50 REM COMPUTE NEW LOCATION:
  R = R + SIN(T):
  C = C + 2 * COS(T): T = T + 9
60 REM REPEAT: GOTO 20
```

*When designing, show off the game with some romance and use graphics when possible.*

When executed, the letter X will effortlessly glide around in a circle. Naturally, the letter X could be replaced with any character or combination of characters. The delay loop on line 30 will need to be adjusted for the particular computer the code is executed on to compensate for varying clock speeds.

BASIC is adequate for most moving displays (especially on a WANG). However, the busier the game, the more strongly I recommend a compiled or an assembled language.

More tips on displays:

1. Show off the game with some unnecessary romance. Don't just print an X or O in the appropriate location in tic tac toe, make them flash on and off a few times first, or grow in size until they fill up the entire square. Make the hanged man swing in the

breeze in hangman.

2. Use graphics when possible. Playing chess is much easier with properly shaped pieces rather than with pieces represented with letters K, Q, N and so on. When graphics are not available, use equals signs for laser beams, pound symbols for explosions, letters surrounded by "less than" and "greater than" symbols for targets and asterisks for stars.
3. Write your code so that the entire display can be reprinted with a single keystroke. This will help you recover from accidents such as power failures to your VDT or failures in your program that you have to fix on the spot. With this feature, you can mend your code as necessary and merely press a button to resume play.
4. Be efficient and use every position on a VDT to advantage. It helps to have all the necessary information on the screen at the same time in a game such as Star Trek.

### Algorithms

An algorithm can be thought of as a set of instructions by which a desired goal may be met. Below is an algorithm for calling your mother on Mother's Day:

1. Obtain phone number.
2. Locate phone.
3. Dial number (this involves a separate algorithm).
4. If it rings, go to Step 5. Otherwise, some error might have occurred. If you want to keep trying the same number, go to Step 3. Otherwise, return to Step 1.
5. If someone answers go to Step 6. If no answer, wait a while and return to Step 1.
6. Say "Hi," tell her you miss her and ask her to send down some of those oatmeal cookies she used to make when you were in college.

The task of identifying each step of any process is quite tricky. In my experience, a programmer almost never successfully thinks of them all before he starts writing code. The art of representing these

steps on paper is called "flow charting." Each programmer seems to have his favorite techniques.

Once you've learned how to program a computer, the algorithm is all important. An assumption is made that if the steps to achieve a process can be fully identified, a computer can be programmed accordingly.

In writing games, the kinds of algorithms you will likely encounter include:

1. Calculating the distance from one point in a plane to another.
2. Calculating the trajectory of a particle as it is accelerated in the presence of gravity.
3. In chess, knowing when the king is in check.
4. In Othello, knowing when a given player has no possible moves.
5. In tic tac toe, knowing when the game is won.

We have all played our share of tic tac toe, but have you ever tried to list all of the steps your mind processes to determine your next move? Here is an algorithm that very easily translates into code (written from the viewpoint of the person playing the "Xs"):

1. Play the first applicable step from those that follow:

*Have you ever tried to list the steps your mind processes in a tic tac toe game?*

2. Look for two Xs in a row. If found, make three Xs in a row. The game is won at this point.
3. Search for two Os in a row. If found, place an X to block

your opponent.

4. Search for two rows that contain only Xs and no Os that intersect with an empty square. If found, place an X at the intersection.
5. Search for two rows that contain only Os and no Xs that intersect with an empty square. If found, place an X at the intersection to block O from making the same move.
6. Search for a vacant corner square. If found, place an X there.
7. Search for a vacant square. If found, place an X on the vacancy.

*Theoretically, a perfect game of chess could be played by a computer.*

The case of tic tac toe is somewhat unique among other board games because there are only nine squares and two types of "pieces" that can occupy each square. The complexity of the algorithm increases geometrically when the types of pieces increase (such as the six colors of a Rubik's Cube) or when the number of squares is larger (such as Go or Othello—games played with only two types of pieces, but with a minimum of 64 squares) or both (such as chess).

In board games, there are many ways to determine the next, best move. Theoretically, a perfect game of chess could be played by a computer if a tree search technique were used (a useful technique but beyond the scope of this article). Unfortunately, even the world's fastest computer would take years to compute a move using such a tree.

My favorite way to implement a board game is to use prioritization. This builds the programmer's experience into the program and tremendously reduces the amount of computation.

Take, for example, a version of the game Othello that I wrote in BASIC for the WANG 2200 series computer. For those of you not familiar with Othello, the game is played on a standard 8x8 matrix (like a chess board), using black and white button-like pieces. The object is to place more of your pieces on the board than your opponent. In a given turn, a player is allowed to place only one of his pieces on the board. In addition, the piece must be placed on an unoccupied square in such a way that it would outflank at least one of his opponent's pieces. An outflank is defined as one or more pieces of the opponent's color on a row that has a piece of the player's color on each end. When an outflank occurs, the enemy pieces all convert to the other color. Thus, by placing only one piece, a player may gain several.

In the manual version of this game, the pieces are white on one side and black on the other. Converting a piece is simply a matter of turning it over. However, when the board becomes crowded, this process becomes tedious, and the players must count their own pieces to determine the winner. Thus, this game is a prime candidate for computerization.

I used two modules in my program to select the next move by the computer. The first module examines the current status of the board and assigns priorities to the remaining squares accordingly. The second module then comes along and picks its move according to the following algorithm:

1. Examine each square on the board under the following rules until all 64 squares have been examined. If no legal moves are found, forfeit turn.
2. Search squares in order until one is found that is not occupied.
3. Examine the priority of this square. If this square is more

important than the previous favorite, discard the previous favored move (if it exists yet) and make this one the new favorite. If this square is of equal importance to the previous favorite, count the number of pieces that would be converted by making this move. If the number of pieces would be fewer, discard the previous favorite and make this the new favorite. If the number of pieces converted is equal by either move, randomly discard or keep the previous favorite. If the number of pieces converted by this new move is more, retain the previous favorite and return to Step 2.

*These rules will probably beat any player who has played Othello less than 10 times.*

You may be wondering why this algorithm would discard a move that converts more pieces to its own side when, after all, the object of the game is to have more of your own pieces on the board. I will leave the explanation of this mystery to the reader with the assurance that this little twist can make a much better player out of you and your computer.

I use the following prioritization to begin my computer version of Othello. Because of the learning curve associated with this game, these priorities will probably beat any player you know who has played less than 10 games. In fact, these priorities are sufficient to play a fair game without constant reappraisal as in my version. Note

## Programming games

that I used a descending priority scale; that is, the more important the square, the lower its assigned number. Thus corners are regarded above all other squares (with a priority of 1) because once captured, they cannot be outflanked. Therefore, the person that captures a corner keeps it. Likewise, the squares surrounding the corner squares are given a bad priori-

*A 1-dimensional array is often easier to process, even with a 2-dimensional game.*

ty because placing a piece here can provide a bridge for the opponent to use to capture the corner square (naturally, once the corner is occupied, the priority of the surrounding squares can be upgraded).

According to the rules of Othello, the game begins with two pieces from each player placed in the center of the board. Thus the center four squares are assigned a null priority (0) because they will already be occupied.

		COLUMN							
		1	2	3	4	5	6	7	8
ROW	1	1	8	2	4	4	2	8	1
	2	8	9	7	6	6	7	9	8
	3	2	7	3	5	5	3	7	2
	4	4	6	5	0	0	5	6	4
	5	4	6	5	0	0	5	6	4
	6	2	7	3	5	5	3	7	2
	7	8	9	7	5	5	6	9	8
	8	1	8	2	4	4	2	8	1

In accordance with good display practices, my version flashes each piece with increasing rapidity a few times as it is placed on the board—just for fun.

## Coding

Here are a couple of hints that make game writing somewhat easier for me. Again, it can be shown that the most obvious approach is often not the best.

When your game involves a 2-dimensional model, such as a chess board or an 8x8 representation of the galaxy, do not succumb to the obvious. Using a 2-dimensional array to store variables seems the natural thing to do, but it usually leads to grief. Often, a long 1-dimension array is easier to process.

It is easier for a human to think in terms of coordinates (that is, Row 2, Column 5), but it is easier for a computer to think linearly. Therefore, use both conventions. Let the human think the game is played on a 2-dimensional board, but program the computer with a single subscripted array. In the case of an 8x8 chess board, don't use an 8x8 array, but rather a 1x64 linear array instead (if you're programming in assembly language, you don't have a choice).

Use these conversion formulas:

$$\begin{aligned} R &= \text{INT}((I-1)/W)+1 \\ C &= W-(R*W-I) \\ I &= (R-1)*W+C \end{aligned}$$

where R = Row coordinate, C = Column coordinate, I = element number of linear array, and W = width of array.

For example, when a chess player enters the row/column coordinates of 5/3, he is referring to the element number of 35 (4\*8 + 3). Likewise, to inform the chess player of the status of array element 21, the computer display should print the row/column coordinates of 3/5. Naturally, these conversion calculations would be done by subroutine.

The advantage of using linear arrays is in calculating radials. Take the problem of determining whether a king located on any square is in check by either a queen, pawn, bishop or rock. The programmer must examine the contents of each square located on any radial from the square occupied by the king. With the 1-dimensional array, this is possible through these simple formulas:

$$\begin{aligned} \text{Directly North} &= I + (-W)*N \\ \text{Directly Northwest} &= I + (-W+1)*N \\ \text{Directly West} &= I + (-1)*N \\ \text{Directly Southwest} &= I + (W-1)*N \\ \text{Directly South} &= I + W*N \\ \text{Directly Southeast} &= I + (W+1)*N \\ \text{Directly East} &= I + 1*N \\ \text{Directly Northeast} &= I + (W-1)*N \end{aligned}$$

where I = element occupied by the King, W = Width of 2-dimensional array, and N = Number of squares away from hub to check.

Whenever I is computed to be less than one or greater than the number of elements in the array, you know instantly that you have exceeded the boundary of the playing board—you can't go any further.

To check for boundary overrun with the coordinate approach requires that you make two comparisons on each coordinate—a

*Don't be too lazy to write code that is only useful during the development stage.*

total of four comparisons.

A final tip on coding—don't be too lazy to write code that is only useful during the development stage (we call them utilities). For example, during the development of my Othello game, I wrote several lines to create a display entirely different from the one normally used while playing the game. This extra display showed the current priority of each square and the thinking process of the program. It was with this utility that I was able to debug Othello quickly.

**ES&T**

# Consumer guide to portable audio

The portable lightweight stereophone has become the star of the audio industry, serving as the most important component of the shirt-pocket AM/FM stereo receivers popular around the world.

There are so many different portable audio products on the market that some consumers may be having difficulty choosing a unit to suit their purposes. These few, easy tips will help the buyer make the final decision.

## Quality

The portable unit should reproduce music as well as most larger home stereos. These portables should be compared with home receivers in retail outlets for sound quality and detail.

## Company reputation

Receiver technology is widely available, but few audio companies have significant experience with the stereophone. The portables are the first product designed to reproduce music exclusively with stereophones, so it is all the more important that the stereophone manufacturer have the engineering background and record of success with the product.

## Price

The market has developed into two tiers: low priced and quality. It is suggested that at least \$29 be spent on the stereophone alone; below that range, there is a notable drop-off in performance.


## Sound

The buyer should listen to the unit before leaving the store. The buyer should look for how well the full range of the musical spectrum is reproduced, with bass notes especially important. Because a portable unit is small, treble notes

are easier to obtain. But only more technically sophisticated units provide the bottom tones to give music an ear-pleasing dimension.
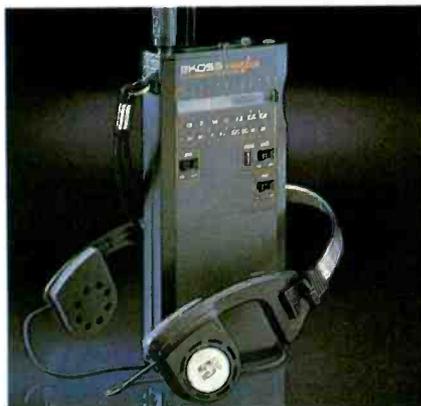
## Portability

If the stereophone will not always be in use and has to be concealed or transported, the consumer should check its portability. Some units must be folded up. Some come in only one position and have to be worn around the neck or left hanging out of a pocket when not in use.



## Comfort

A lightweight stereophone should be comfortable for wear during long periods of time.

## Firm fit

A snug fit is important so that the unit does not fall off with physical activity. The potential user should make sure the unit will stay on tight without discomfort.

## Foam density

The foam should not be too light, nor too dense; it should admit sounds, such as auto horns, but it should also not become too wet

when in use during vigorous activity. It should also enhance the unit's level of comfort.

## Usage

Lightweight stereophones are ideal for personal, portable listening pleasure when used properly. Because listeners often enjoy substantial volume levels, it is not recommended that they be used in cars, on foot or other transportation modes while on public ways. Traffic safety hazards caused by impaired external hearing capabilities affect not only the user, but others around him.

## Adaptability

The portable stereophone can also be used in other applications, such as with televisions, home stereos and other radios and cassette players. Some units come with extra adapter plugs for this purpose.

## Cord lengths

While in use with a music box-type shirt-pocket receiver, the cord need not be too long to reach from the pocket to the ear. But when in use with televisions or other stereos, some distance may be required—at least 10 feet for optimum multiple use.

Features to look for in portable receivers include: stereo indicator lights, tone and distance/local switches, presence of AM band for news, weather and sports and reception distant from big cities. Also, with stereophone jacks, personal listening can be shared.

This report was provided by the Koss Corporation. The company manufactures stereophones and loudspeakers, a digital delay system and an AM/FM receiver.

**BSA**



The programmable video game and home computer markets promise to be one of the fastest growing consumer markets of the 1980s. There are approximately 5 million game systems currently in use, and new system sales are increasing by about 50%. Cartridge sales are more than doubling annually. As more new systems are sold, more interesting new cartridge ideas are released, and game marketers devote more advertising and merchandising support to cartridges. The market for video game cartridges alone is expected to exceed \$1 billion at retail by 1985. ES&T has collected some of these exciting cartridges from major games manufacturers. For more information from these manufacturers, simply circle the Reader Service numbers given at the end of this section.




#### **Skiing**

Challenge yourself to a wide variety of high speed downhill or slalom runs. Trees and moguls rush by as you race through the course.


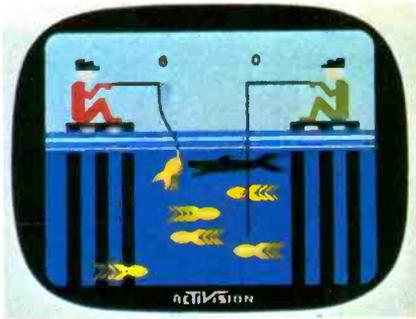
### Fishing Derby

A relaxing afternoon at the old fishing hole? Not quite. The bay is full of beautiful sunfish, and all you have to do is land them faster than your opponent. However, watch out for the shark. His voracious appetite makes fishing a constant challenge.



### Ice Hockey

Face off. Fight for the puck. Skate down the ice past the defender for a slap-shot. Then, hurry back on defense as your opponent makes a remarkable save and a long pass to his forward.



### Kaboom

You have three buckets of water. The mad bomber at the top of the screen tosses bombs and you catch them in your buckets. But before you know it, the bombs are falling at a rate of 13 per second.



### Laser Blast

As commander of a fleet of intergalactic spacecraft, you come upon some unfriendly alien types. Get them before they get you and you are awarded points.


### Dragster

Watch the countdown, shift gears, pop the clutch and burn rubber. You can rev your engine but be careful not to blow it. Sound effects and grueling competition bring all the action of the dragstrip right into your livingroom.


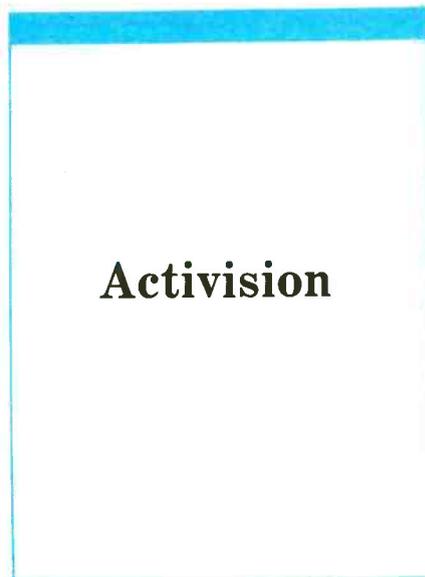
### Bridge

This cartridge deals hundreds of millions of hands at random and provides a computer partner who bids by the rules. After you have established a contract, the computer plays as your opponents.




### Tennis


Never wait for a court again. Charging players can rush the net, lay back and play the baseline or roam the court.
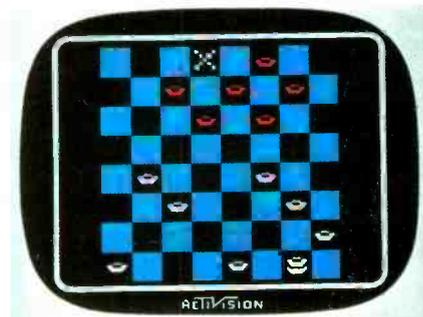
### Checkers

There are three different skill levels to choose from. Warm up with novice, and then tackle the tougher levels. Your computer opponent plots the results of each of his available moves and then picks the one that is toughest on you.




## Games people play

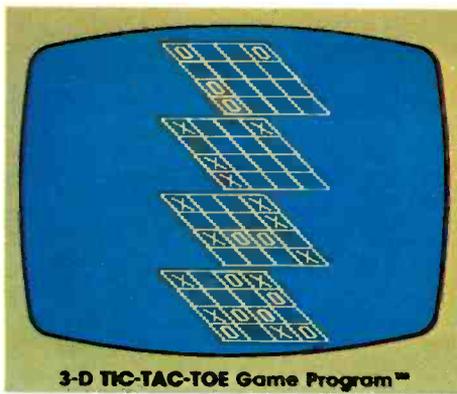

3-D TIC-TAC-TOE Game Program™

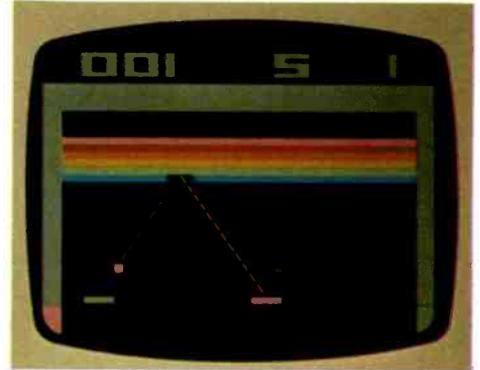
### 3-D Tic-Tac-Toe

Place four Xs or four Os in one horizontal, vertical or diagonal row, or through all the planes. Play against an opponent or against the computer in trying to complete your row first.


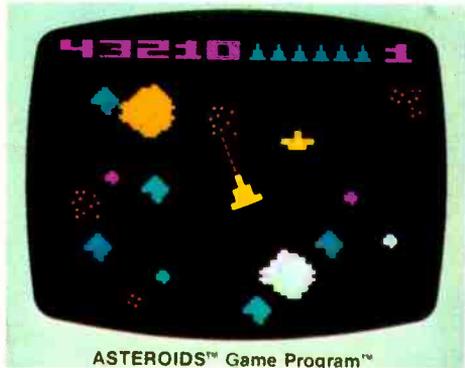
### Breakout


Smash your way out of a thick wall of bricks with a tricky ball. The first few bricks are easy, but as you come closer to breaking out, it gets tougher. The program also includes Breakthru, where you knock a hole in the wall in one shot.




ASTEROIDS™ Game Program™
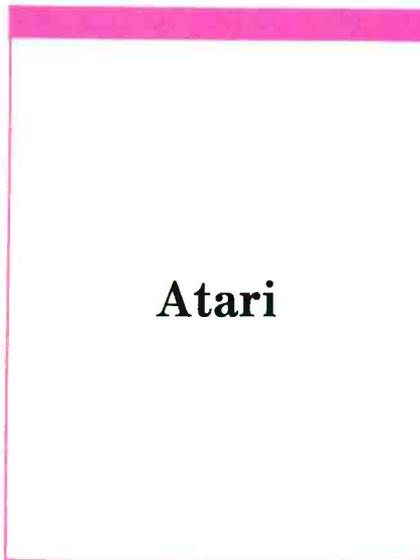
### Asteroids

Your spaceship is trapped in a deadly asteroid belt and you must score points by destroying the boulders before they, or the enemy spacecraft, destroy you. Hyper-space in all directions and fire your missiles to protect your spaceship.



Atari

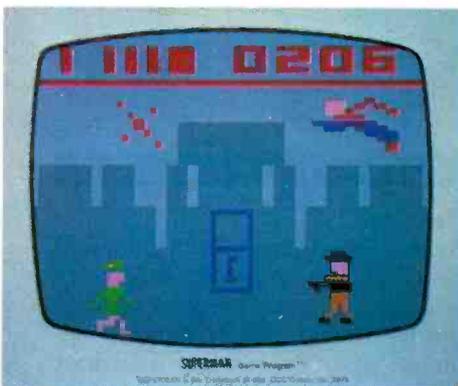

SUPERMAN Game Program™

### Superman

Flying faster than a speeding bullet, you use your X-ray vision to find the hideout of your enemy, Lex Luthor, and put the gang behind bars. But you must watch out for the deadly Kryptonite satellites, or you will lose your super powers.


### Backgammon

Use all the strategies you know and play against the computer or another player. The program includes the popular version of Acey-Deucey, in which throwing a one and a two is the name of the game.


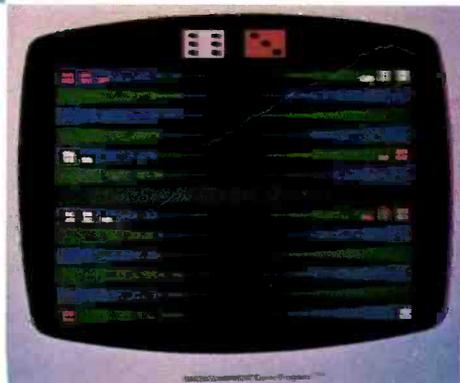
### Casino


Games include blackjack (with up to four players trying to beat the house), stud poker and poker solitaire (where you can play up to 12 hands by yourself).



CASINO Game Program™

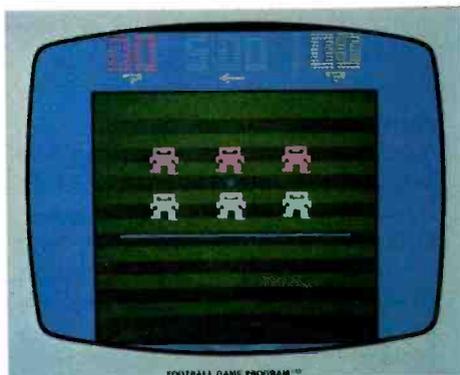
### Football

You're the quarterback calling all the offensive plays, and on the defense, you're in total control. Kick, pass, run or punt for a touchdown.


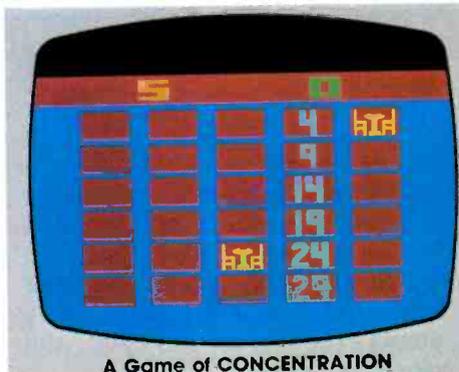
### A Game of Concentration

Thirty numbers flash on the screen and a familiar object or wild card is hidden behind each. Match wits with your opponent or the computer in matching pairs of objects. Millions of different combinations in eight game variations keep players on their toes.




### Video Chess

It's you against the computer in this version of the classical game. You plan your strategy to break down the computer's defenses and reach checkmate.



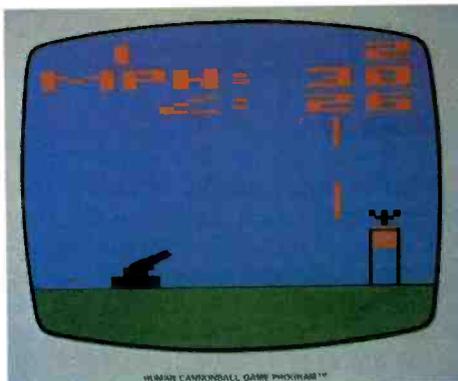
### Human Cannonball

Position the cannon, set the angle and pick your speed; the calculations will appear on the screen. You fly through the air toward a water tower in this daredevil stunt.



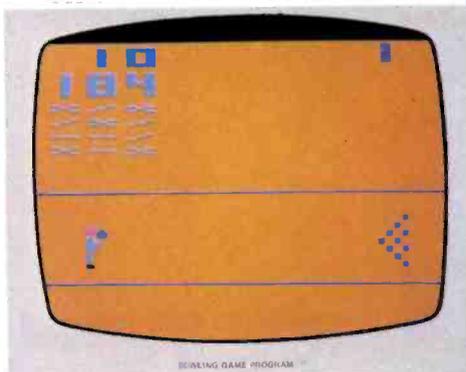
### Bowling

Choose your alley and roll the ball. It may be a straight, curve or even a gutter ball. The score is kept automatically on the screen, frame by frame. The cartridge includes six variations of the game.


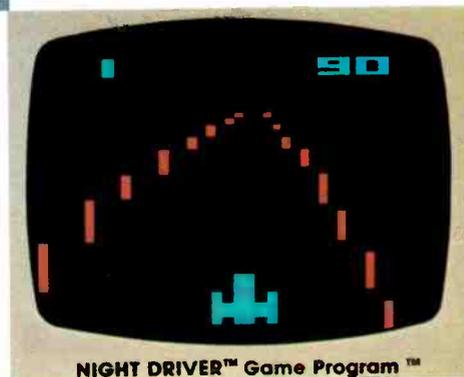
### Night Driver


The road ahead is dark and winding as you keep your eyes peeled for oncoming cars. The longer you stay on the road, the higher your score, but you never know what will jump out on the road at night.



## Games people play

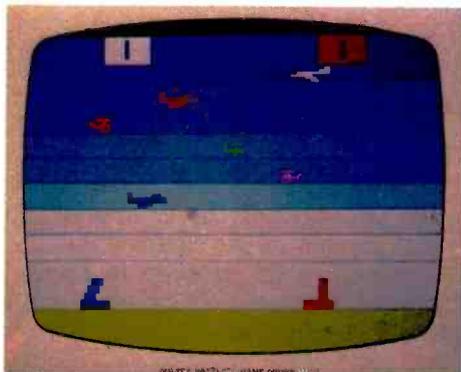
### Air-Sea Battle

Be an artillery commander, submarine captain or aircraft bombardier in six variations of one program. Targets come from different directions at different speeds in games such as Anti-Aircraft, Torpedo, Shooting Gallery, Polaris, Bomber and Polaris vs. Bomber.



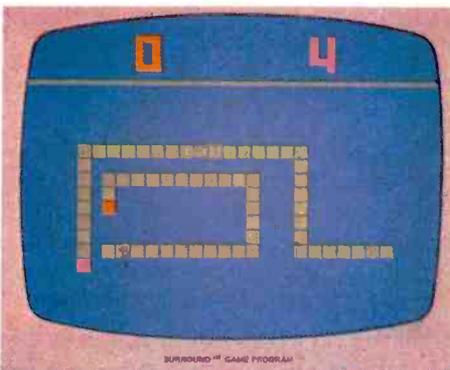
### Surround

You control a moving wall as you try to trap your opponent before he traps you. It's a game of speed, wits and skill as you move and erase sections of wall. A variation in this program is Video Grafitti, in which you draw with video blocks.



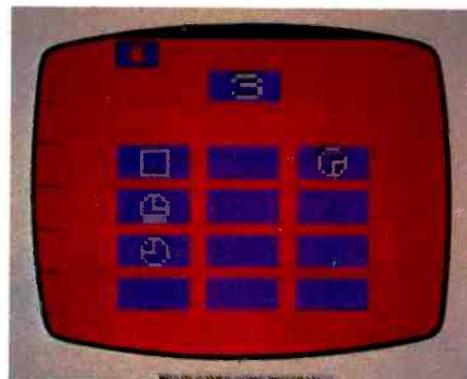
### Brain Games

Race against time and distractions in the six variations of this program. Focus on a series of symbols, numbers or musical notes, then repeat them in order; add columns of numbers in the allotted time; or watch four objects appear on the screen and eliminate the one that doesn't belong.



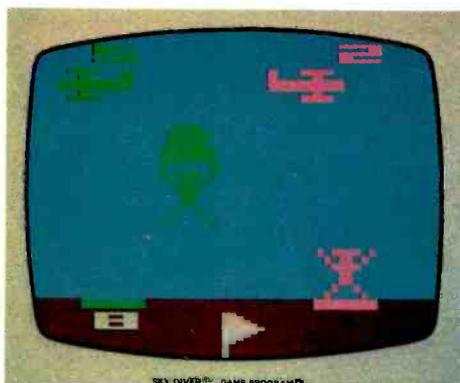
### Sky Diver

The longer you wait to open your chute after your jump, the more points you score. After it opens, steer against varying wind velocities toward the bull's eye.


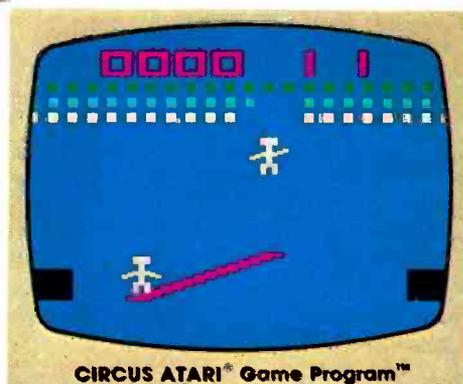
### Circus Atari

As the clown bounces around in different directions, try to catch him on the teeter-totter. Send him up to pop red, white and blue balloons worth different points—the harder the pop, the more you score.




### Black Jack

You and up to two other card sharks are seated around the television, each armed with 200 chips. Bet up to 25 chips each hand as the computer deals the cards on the screen. (An additional set of paddle controllers is needed for the 3-player version.)


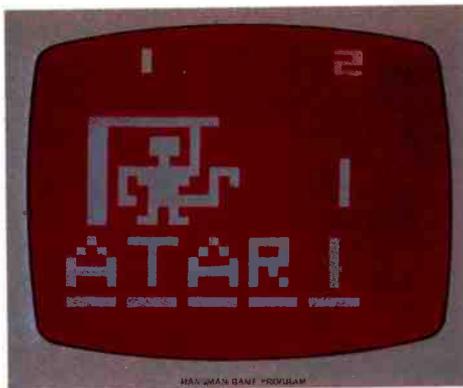
### Hangman

Play alone or with an accomplice against the computer as you guess the missing letters to complete the mystery word. Variations include vocabularies for grades three, six, nine and high school. In the Lexicontest variation, you and your opponent choose words for each other.




### Adventure

Once upon a time an evil magician stole an enchanted goblet and hid it in the kingdom. Now you must find it. Three deadly dragons and a black bat try to stop you but you use the magic sword for protection.



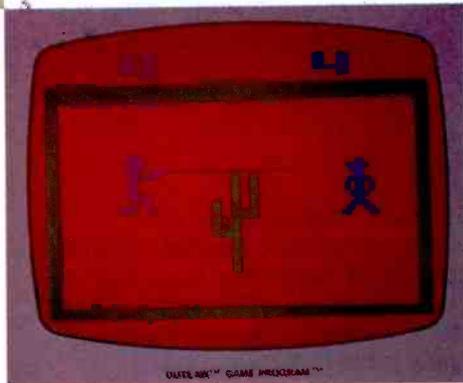
### Outlaw

Your gunfighter draws, kneels and aims at your opponent. Blow away walls, stagecoaches and cacti as you nail the enemy with a clever ricochet. In the Target Shooting variation, shoot at a moving target while racing against time and obstacles.



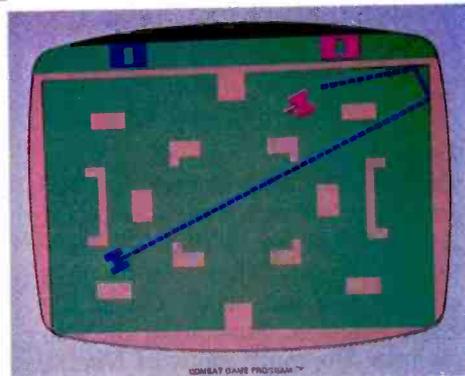
### Combat

Use your missiles, rapid-fire machine guns and single shots to arm yourself against the enemy. Blast your opponent as many times as possible for the highest score.



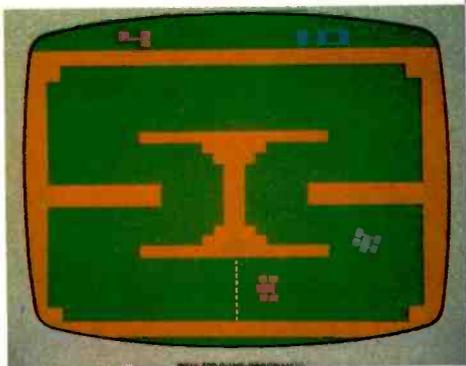
### Indy 500

Race around one of many tracks in 14 1- and 2-player variations, such as Race Cars, Crash 'N Score, Tag and Ice Race. Steering controllers come with each Indy 500 game program.


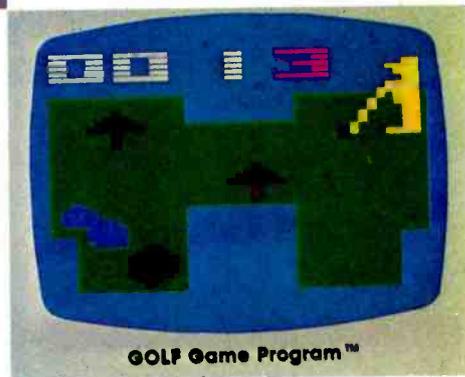
### Golf

One to four players move around the nine holes of Atari's course. You control the direction and power of your shot and get a close-up of the green for your putt. Your score is automatically recorded.



## Games people play


### Video Pinball

Hit bumpers, spinners, targets and rollovers to rack up points. You get three balls, but if you hit the rollover four times, you get an extra ball. You can even nudge, but if you tilt, you're out of the action.


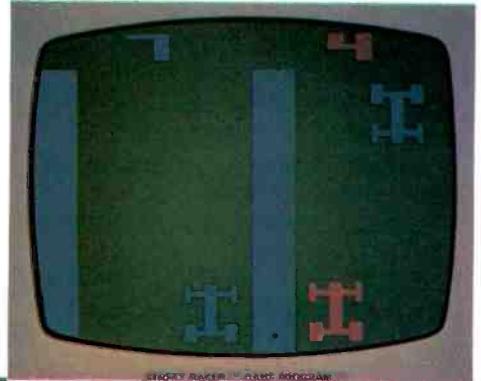
### Street Racer

Steer your way through six games in Street Racer, Slalom, Dodge 'Em, Jet Shooter, Number Cruncher and Scoop Ball. Race a clock or a friend, and with extra paddle controllers, up to four can play.




### Home Run

As the pitcher, you mix up your pitches to send fast, slow or curve balls and, as the batter, you take a swing at the computer's pitches. Experience balls, strikes, double plays, triple plays, force outs, tag outs and sacrifice flies. The difficulty switch allows for eight variations, from bush league to major league.



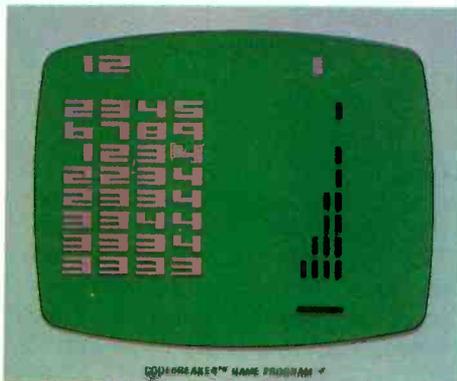
### Codebreaker

Deduce the secret code in the fewest turns with variations for novice and super sleuths. The computer tells you when you guess a code cipher and when it's in the right position. This program also includes the math game of Nim.



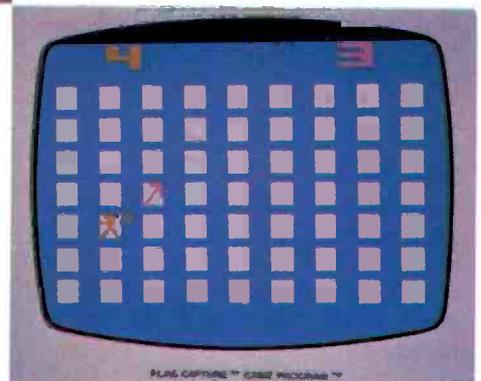
### Flag Capture

The flag is hidden on the map and the first to find it wins. Send out scouts to gather clues—if they find numbers or arrows you'll know where to look, but if they dig up bombs they'll be blown off the map. Race the clock or an opponent.



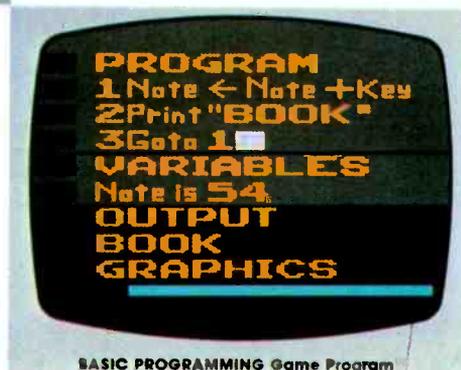
### Basic Programming

This cartridge teaches you the basics of computer language and programming. You can program your computer to print messages, play games or play a tune.



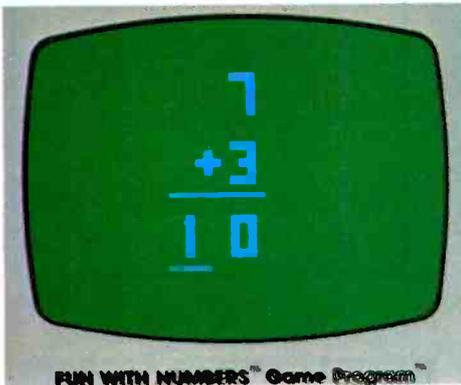
### Fun With Numbers

Solve problems of addition, subtraction, multiplication and division on your TV set. The computer tells you if you're right and flashes the correct answer if you're wrong.



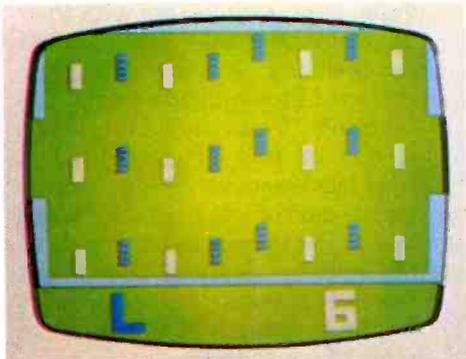
### Video Olympics

Compete in eight events against the computer or up to three competitors (additional paddles required for 4-player games). Match skills in Pong, Soccer, Foozpong, Hockey, Quadrapong, Handball, Volleyball and Basketball.



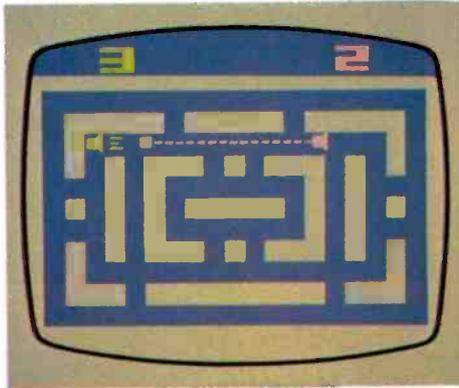
### Slot Racers

You and your enemy are pursuing each other at breakneck speed through big city streets, blowing each other away with the bazookas on your hoods. The first to blast his opponent 25 times wins.



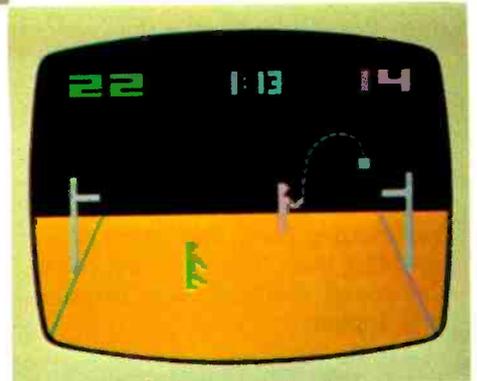
### Basketball

You control when to jump, dribble, steal or shoot your way past human or computerized opponents. Use the difficulty switches to arrange great matches between pros and double dribblers.


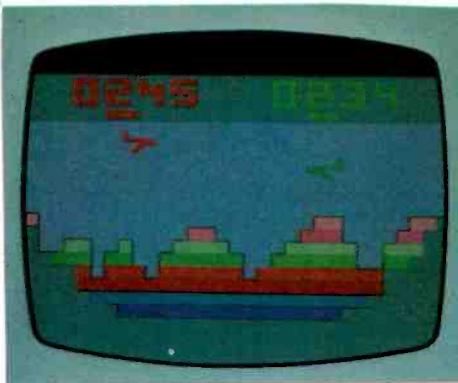
### Canyon Bomber

Blast away boulders with the tons of bombs you are in control of as you play against the computer or another player. Or play Sea Bomber and bomb the carriers, tankers and ships below you.



### Warlords


The other kings are out to destroy your castle and kill your king but you keep him safe behind the castle walls and use your shield to deflect the deadly, fast fireball. To destroy the other kings you must break through their castle walls and hit them with the fireball.



## Games people play


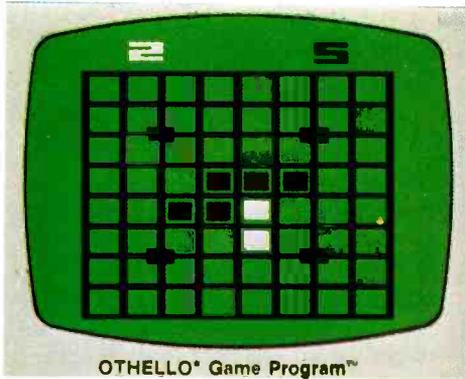
### Othello

Each player takes turns trying to capture as many squares as possible. You'll need a solid strategy and real cunning to be successful at this game, but don't try any illegal moves or the computer will "razz" you. You can play against the computer at three different skill levels or against another player.


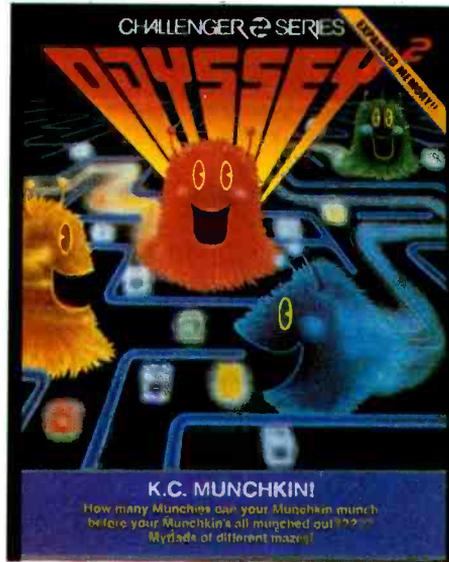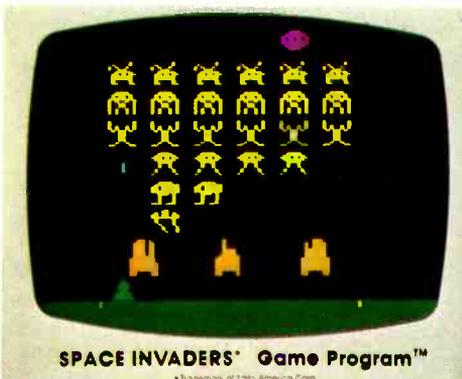
### Space Invaders

Your mission is to destroy the aliens with your laser cannon before they reach the Earth, while avoiding their bombs. When you've destroyed them all, new invaders will appear.



### K. C. Munchkin!

How many Munchies can your Munchkin munch before your Munchkin's all munched out? The object is to skillfully negotiate a maze while trying to gobble the edible Munchies and avoid being munched by the Munchers. It's a game of video survival—munch or be munched.

N.A.P.  
Consumer  
Products


## Intellivision



The Electric Company Word Fun Monkeys swing through the jungle, capturing letters with their tails to make words. Three games are included in this program, developed in conjunction with The Children's Television Workshop for one or two players. Find A Word has learners weaving words in and out of each other, Word Hunt sends them into the jungle to find missing letters and Word Rocket has them blasting vowels into the sky to make words out of clouds of consonants.

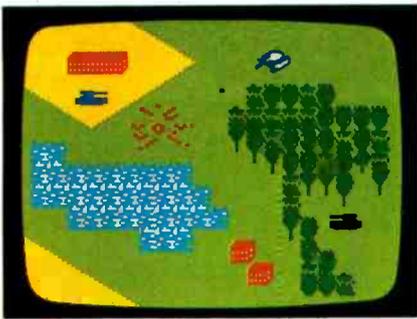
### Armor Battle

Two players move across the battlefield, scanning the horizon for tanks and hoping to fire a split second sooner than the enemy. When you have beaten your opponent, move to one of hundreds of new battlefields.


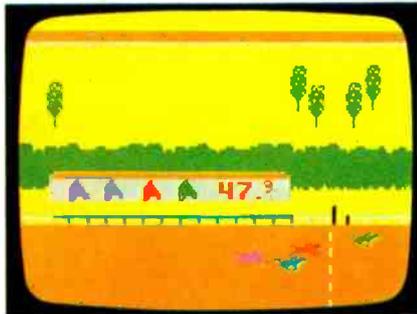
### Horse Racing

Up to six players look over the tout sheet, pick their horses, handicap them and bet. Watch as the horses move around the track and hit 15 to 1 exactas.



### Las Vegas Roulette

One or two players place their bets and watch as the roulette wheel turns toward the lucky number. A payoff table and odds listing are included in the program.




### Las Vegas Poker and Blackjack

One or two players can play 5-card stud, 5-card draw or 7-card stud poker against a dealer who raises, drops and even bluffs. Blackjack is also included in this cartridge.


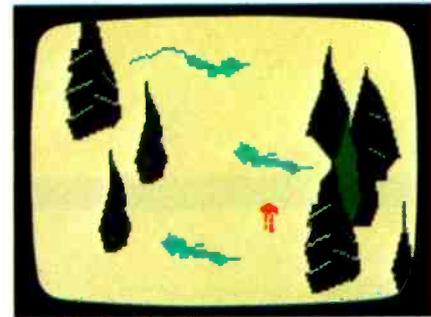
### U.S. Ski Team Skiing

Don't cut corners too closely as you wind down these downhill or slalom courses, or you'll go tumbling! Up to six players jump moguls, edge through turns and race downhill against the clock in this U.S. Ski Team licensed game.




### The Electric Company Math Fun

This game, developed in conjunction with the Children's Television Workshop, makes solving addition, subtraction, multiplication and division problems fun. One or two players race their gorillas along the river bank, ducking past obstructing animals. The cartridge accommodates a wide range of learning levels.



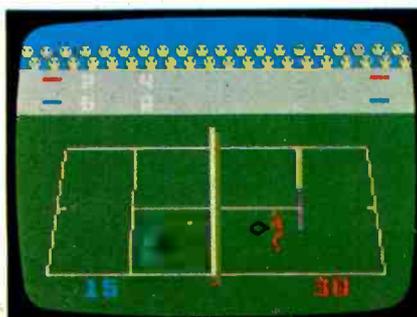
### Tennis

Play an entire 3-set match, and each game will be different and exciting. You control ball placement, velocity and strategy to make it a game of wits as well as dexterity. Even the crowd turns their heads to follow the ball and cheer at the right time.


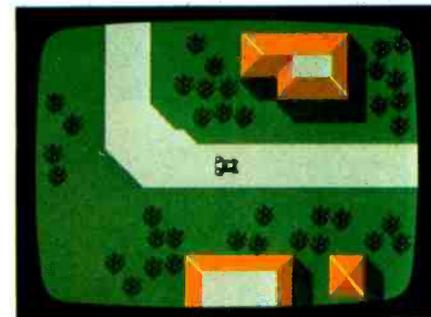
### Auto Racing

Players race each other or the clock as they guide their Formula 1 through the course. Five different race cars and five different courses provide variety, along with skidding cars and unexpected hairpin turns.



### NHL Hockey

The National Hockey League has licensed this game, in which two players move their teams across the ice. The program includes face offs, trapping, interception and a penalty box.



### Games people play

#### Sea Battle

Lay invisible minefields where you think the enemy ships will travel, then man your battle stations and fire shells and torpedoes. Two players compete, using long-range and closeup views from their ships.




### NBA Basketball

Each 3-man team can dribble, pass in any direction, rebound, jump, block, steal and take set shots. Two players race a 24-second clock in four quarters in this game, licensed by the National Basketball Association.


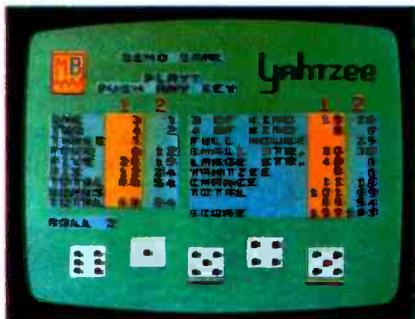
### Yahtzee


This dice game combines strategy and chance as players accumulate points by rolling certain number combinations. Developed by Milton Bradley Company.



## Texas Instruments
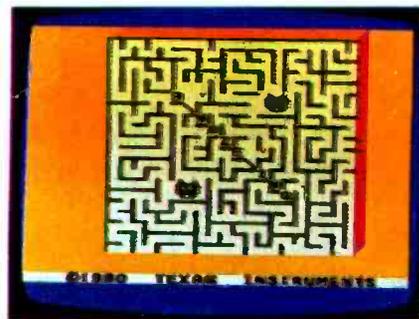
### A-Maze-Ing

The 13 options on this program offer a total of 5200 different variations, from simple mazes to a cat-and-mouse chase situation.



Activision .....	65
Atari .....	66
Intellivision .....	67
N.A.P. Consumer Products .....	68
Texas Instruments .....	69

# More light on optical-fiber systems

Courtesy of GTE

Like most communications systems, fiber-optics systems require a transmitter, a transmission medium and a receiver. Fiber-optics systems use a light transmitter and receiver, and a glass or plastic fiber is the transmission medium.

## Transmitter

A light transmitter consists of two parts, a light source and a modulator. The modulator imposes the information on the source. Most modulators accomplish this by turning the light source on and off or by varying the intensity of the light.

Two kinds of light sources are suitable for fiber-optic communications: the LED (light-emitting diode) and the laser (light amplification by stimulated emission of radiation).

There are several types of lasers but the one most commonly used for fiber-optic communications is the semiconductor laser, which is

also known as an injection or junction diode laser. The LED is also a semiconductor junction diode device, so some knowledge of junction diodes is helpful in understanding the two light sources.

As shown in Figure 1, junction diodes are made from two kinds of semiconductor material: a positive (P) type that has a deficiency of electrons in its atoms and a negative (N) type that has an excess of electrons in its atoms. If a positive voltage is connected to the P-type material and a negative voltage is connected to the N-type, forward bias is applied to the diode and current will flow through it. The amount of current is determined by the amplitude of the applied voltage.

Reversing the polarity of the voltage so that negative is applied to P and positive is applied to N cuts off the current flow. This is known as reverse bias. The diode can be switched on and off millions of times per second by reversing

the polarity of the applied voltage.

When forward bias is applied to the LED, the electrons in the relatively unstable N-type atoms receive energy from the battery. This extra energy allows them to cross the junction and current flows.

After crossing the junction, the electrons lose energy and enter the atoms of the P material. Some of the energy the electrons lose is emitted as light from the LED. The intensity of the light emission varies with the amount of current flowing through the junction.

Light generated by atomic action of this kind is known as luminescent, as opposed to incandescent light, which is generated by heating an element. Ordinary light bulbs are incandescent and are not suitable for high speed communications.

Referring to Figure 2, the semiconductor injection laser is a junction diode with both ends polished to reflect light. One end is more highly polished than the other.

Forward bias causes the N-material electrons to raise to a high energy level and move into the junction. As a high-energy electron falls to a lower energy level, it emits a small burst of light. The light may strike another electron and raise it to a high energy level. When this electron falls to a lower energy level, it also emits a burst of light. These bursts of light are reflected when they hit the polished ends of the junction. A stream of light is created that moves back and forth between the ends of the junction. When these light waves reach a high enough intensity, some of the light will emerge from the least polished end of the junction in the form of a beam of light.

The frequency of the light generated by the laser is a function of the diode material and temperature. The intensity of the light increases with the current flow.

The light wave spectrum is generally expressed in wavelength rather than frequency. The shorter the wavelength, the higher the frequency. Typical wavelengths for both LED's and lasers are in the

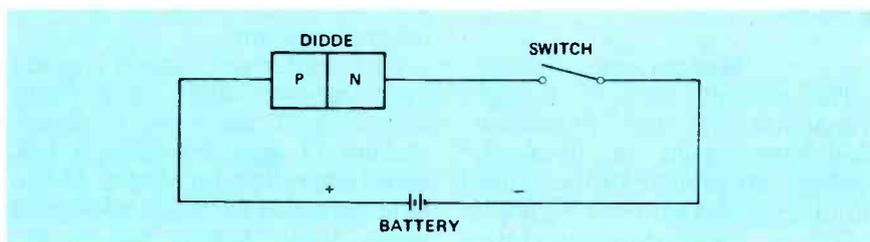


Figure 1. Junction diodes are made from positive (P) and negative (N) semiconductor material.

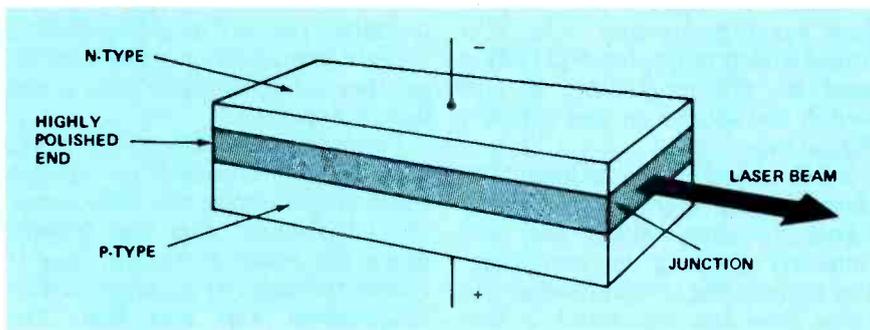


Figure 2. The semiconductor injection laser is a junction diode with both ends polished to reflect light.

## Optical-fiber

800 to 850nm range. A nanometer is one billionth of a meter.

### LED and laser comparison

The emission from an LED is lambertian, which means the light rays emanate over an entire hemisphere. Another term used to describe the way light emanates from an LED is isotropic, which means the light rays are emitted at all angles. This makes it difficult to efficiently couple an LED to a fiber.

The LED output is nearly directly proportional to the current through the junction. The change in lightpower output is essentially linear over a large range of input current, so LEDs can be amplitude modulated.

Some LEDs can be switched at rates up to 200 million a second, although 50 million a second is about the fastest rate used in actual practice. Switching rates are usually stated in megabits per second (Mbps). A megabit is one million bits or pulses.

The modulation method that switches the source on and off is called pulse code modulation (PCM). This is the modulation method commonly used in digital systems.

The laser is a threshold device. It "turns on" and provides a large amount of light power when the drive current reaches a threshold value. The light power output versus current input is linear over a very limited range, so lasers are not suitable for amplitude modulation (AM).

The spectral width of laser light is much narrower than that of LEDs. Therefore, lasers can be switched at much faster rates than LEDs because material dispersion is not a problem. Material dispersion is explained later, in the discussion of optical fibers. Lasers can be switched at gigabit (Gb/s) rates, so lasers are very suitable for PCM or other forms of pulse modulation. A gigabit is one billion bits.

Laser beams are directional, so coupling to the fiber is more efficient than for LEDs. Lasers also have a higher power output than LEDs.

Terms used to describe laser light are coherent and collimated.

Coherent means that the rays are in phase and reinforce each other. The light from a coherent light source has only one wavelength. Collimated means that all the rays travel on parallel paths. Coherence and collimation are ideal properties for a light source to be used in optical fiber communications. Lasers approach this ideal.

Other requirements for a light source to be used in mass communications are low cost and high reliability. In the telephone network, for example, sources must be able to provide many years of continuous stable operations at ordinary room temperatures. They should also be capable of being efficiently coupled to the fiber.

Another factor that must be considered is the distance bandwidth product. This is a "figure of merit" for a system. The product is largely determined by the light source.

Lasers have a better coupling efficiency and distance-bandwidth product than LEDs. On the other hand, LEDs are lower in cost and because of simpler construction, generally more reliable than lasers. Specially constructed LEDs with greatly improved coupling efficiencies are available but they cost more and have a shorter life than the standard type.

Generally speaking, LEDs are used for relatively short, limited-bandwidth systems. Lasers are required for long-haul broadband systems.

### Modulators

The second part of a light transmitter is the modulator. Modulators used in fiber-optic systems are similar to those used for microwave radio (see Figure 3).

If a frequency-division multiplexer (FDM) is used as the modulator, it will amplitude modulate the light source to produce varying intensity light. If a time-division multiplexer (TDM) is used as the modulator, it will switch the source on and off at a digital rate.

FDM combines information channels represented by analog signal voltages, which are continuously varying in amplitude. The signals are transmitted at the same time but separated in frequency.

A TDM combines information

channels represented by the presence and absence of signal voltage pulses of constant amplitude. The time position of a pulse, relative to other pulses, determines the voltage quantity it represents. The signals are transmitted at the same frequency but separated in time.

FDM signals and their components parts are referred to as analog; TDM signals and their component parts are referred to as digital. Digital signals are more commonly used for fiber optic communications systems because it is easier to detect on-off states than it is to detect variations in light intensity.

### Transmission path

The glass fibers used in fiber-optical cable are very small, with typical diameters from 50 to 200 $\mu$ m. The fiber shown in Figure 4 has a cylindrical core with a uniform index of refraction. The core is encased in a concentric layer called the cladding. The cladding index of refraction is lower than that of the core.

A light ray entering the core at one end of this fiber will travel down its length and exit at the other end. This action conforms to the reflection principle of physical optics, which says: When a light ray passes from one optical transmission medium to a boundary of another medium with a lower index of refraction, the ray will be reflected back into the original medium.

This reflective action occurs over and over again as the light travels down the core. A minute amount of light intensity is lost each time reflection occurs. As the light traverses the fiber, additional losses occur, largely due to impurities in the fiber. These two factors, reflection loss and fiber loss, are the main components of attenuation per unit length of fiber.

Light transmission is affected by another cable characteristic, input light acceptance.

Figure 5 shows three light rays, a, b and c, entering an optical fiber. Ray a enters the fiber along the longitudinal axis and travels down the cable as shown. Ray b enters the cable at an angle to the longitudinal axis less than the angle  $\theta$  and is reflected down the cable as shown. Ray c enters the

cable at an angle greater than  $\theta$  and escapes through the side as shown. Light rays entering the cable at angles within the cone defined by the dotted lines will propagate along the cable. Rays entering the cable at larger angles will be absorbed by the opaque jacket that surrounds the fiber.

The angle  $\theta$  is known as the maximum propagation angle. It is mathematically related to the difference between the reflective indices of the fiber and the cladding. So, the light gathering capacity of a cable can be expressed as a number, called the numerical aperture, abbreviated NA.

NA is equal to the square root of the difference between the square of the peak value of the reflective indices of the core and the cladding, which is also equal to the sine of  $\theta$ . The NA for most fibers falls between 0.1 and 0.3 which approximately corresponds to the sines of angles between 5.7 and 17.4 degrees. As shown in Figure 5, these are  $\frac{1}{2}$  angles. Two things to remember about light acceptance are (1) only the light entering the fiber at a small angle to its longitudinal axis will travel down the fiber and (2) the greater the difference between the reflective indices of the core and cladding, the larger this angle will be.

The maximum propagation angle is also known as the critical acceptance angle. The reflective property of an optical fiber is also described in terms of the critical angle, which is the maximum angle to the cladding at which a light ray will be reflected. Rays striking the cladding at a larger angle will escape through the cladding.

Optical fibers that have an abrupt change of reflective index between the core and cladding are called step-index fibers. Step-index fibers are further divided into single-mode and multimode. The number of modes that can propagate along a fiber is determined by the core diameter, the numerical aperture and the wavelength. For a given wavelength, the number of modes can be decreased by reducing the diameter of the core.

When the diameter equals the wavelength, only a single mode will propagate. A single-mode, step-index cable eliminates modal dispersion, which is a limiting factor on the bandwidth of fiber-optical systems.

The cause of modal dispersion is shown in Figure 6, which shows the path of two rays, A and B, through a fiber.

As shown in the figure, ray A travels a shorter path because it is not reflected as often as ray B. Therefore, ray A will exit the cable sooner than ray B. Light pulses, formed of rays that enter the cable at the same time will be stretched or broadened in time as they travel down the cable.

This effect is known as modal dispersion. Severe dispersion causes an overlap between pulses,

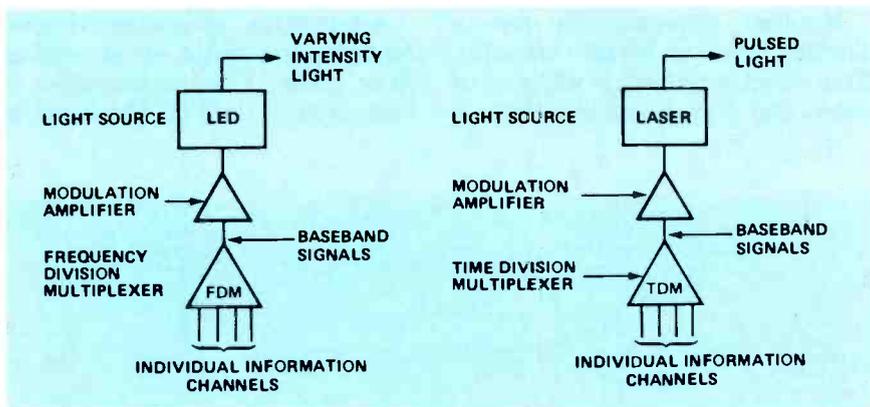


Figure 3. Modulators used in fiber-optic systems are similar to those used for microwave radio.

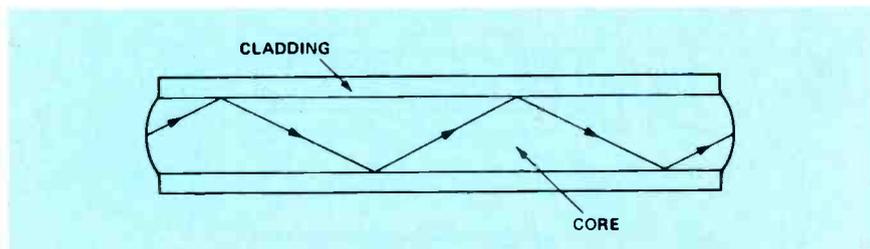


Figure 4. This optical fiber has a cylindrical core and uniform index of refraction.

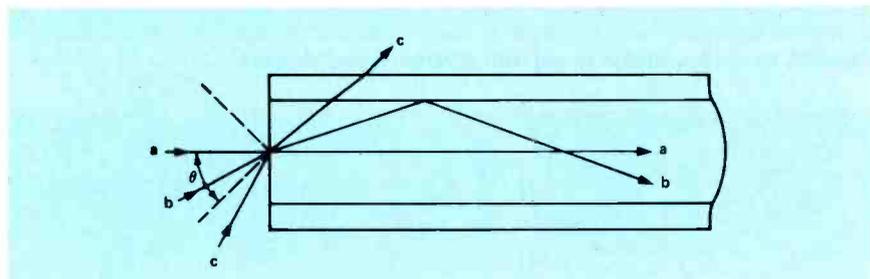


Figure 5. The critical angle,  $\theta_c$ , is also known as the maximum propagation angle.

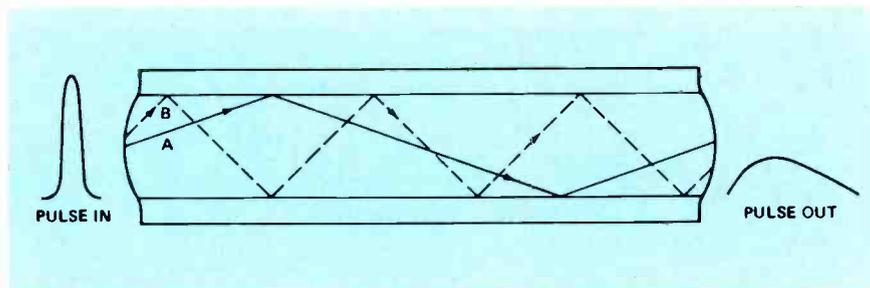


Figure 6. The cause of modal dispersion is shown by the path of rays A and B through the fiber.

## Optical-fiber

which makes it difficult to distinguish between them. Also, overlap may make it appear that a pulse is present where one is not. It is apparent that allowing more space between pulses, i.e., sending fewer pulses per unit time, could alleviate overlap. However, the information capacity (bandwidth) of the system would be reduced.

As previously stated, single-mode fiber eliminates modal dispersion. However, its core diameter is so small that it is difficult to achieve and maintain efficient coupling between a light source and a single-mode cable under other than laboratory conditions. A step-index, multimode cable has a much larger core diameter so efficient coupling can be achieved, but it has the disadvantage of dispersion effects.

A compromise between the step-index, single-mode and multimode fibers is the graded index fiber. This fiber provides a good coupling efficiency and reduces modal dispersion. This is accomplished by using a graded index of refraction across the fiber core instead of the uniform index of refraction used for step-index core.

The graded-index, multimode fiber has an index of refraction that is maximum at the center of the core and decreases with radial distance from the center. Because the speed of light is inversely proportional to the index of refraction of the material through which it propagates, rays traveling along the centerline will travel lower than those traveling off the centerline. The centerline rays travel a shorter distance at a slower speed. The off-center rays travel a longer distance at a faster speed, so the rays exit the cable at more nearly the same time than is the case with the step-index, multimode fiber. The pulse spreading is substantially less for graded index multimode fiber than it is for step index multimode fiber. For systems of appreciable length, pulse spreading must be minimized because it is a limiting factor on the bit rate capacity (bandwidth). Graded index or single-mode is the fiber of choice for these systems. Figure 7 shows the modal dispersion of the three basic fiber types.

## Material dispersion

Another dispersion effect is called material dispersion. It is a result of the fact that different wavelengths of light travel at different velocities through a given medium.

Practical light sources emit light at different wavelengths. An LED may have a wavelength spread of 50nm. A laser is much better in this respect; its spread is on the order of 4 nm.

Material dispersion is also a limiting factor on bit rate capacity. This effect is present in all types of cable. One way it could be reduced

is by a truly monochromatic light source (one which radiates light at only one wavelength). Another way material dispersion can be reduced is by using long wavelength transmission. Material dispersion approaches zero at a wavelength around  $1.3\mu\text{m}$ . Material dispersion is also referred to as wavelength dispersion.

## Attenuation

Attenuation is another important characteristic of an optical fiber cable. Fiber attenuation is measured in decibels the same as

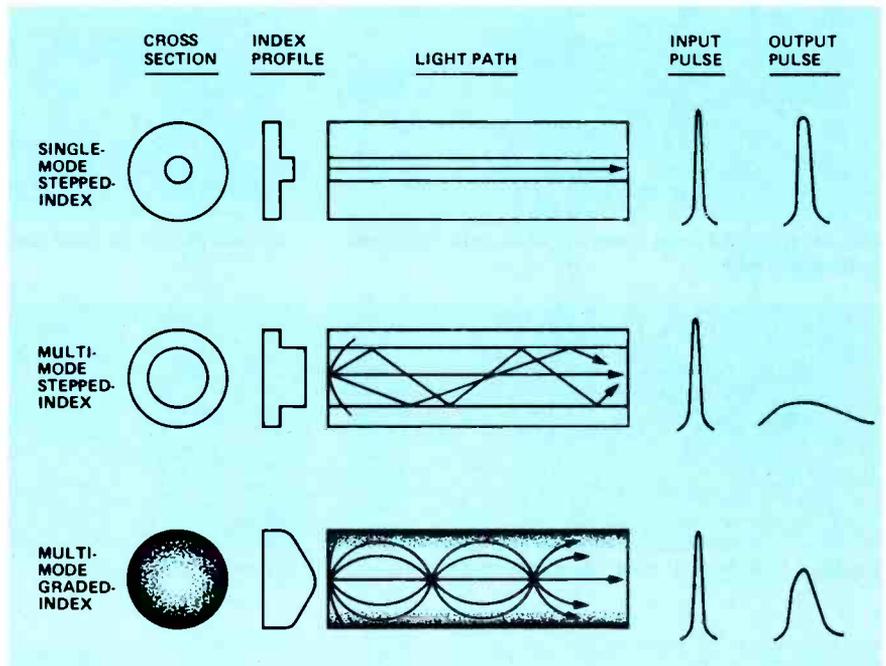


Figure 7. Modal dispersion varies with different types of fibers.

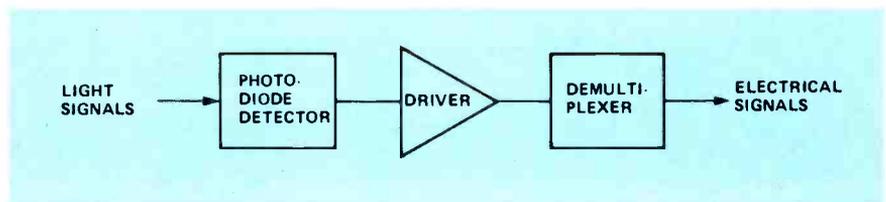


Figure 8. An optical receiver consists of a photodiode detector, a driver amplifier and a demultiplexer.

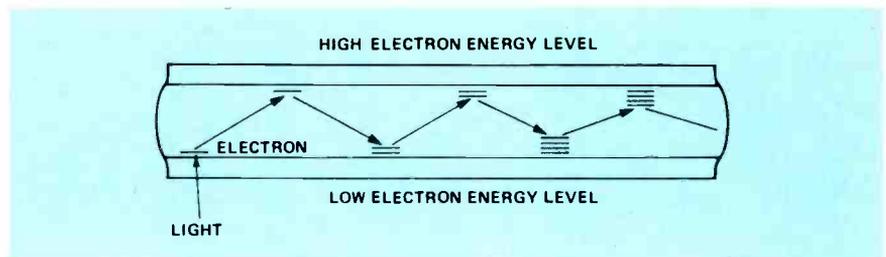


Figure 9. Light striking an electron will raise it to a higher energy level, creating the avalanche effect.

wire attenuation. A decibel is 10 times the logarithm of the ratio of two power levels. For example, if the ratio of the power input to the power output of a 1-kilometer fiber is 10, the fiber has an attenuation of 10dB per kilometer; if the ratio is 100 the attenuation is 20dB per kilometer.

In a wire cable system, a principal cause of attenuation is electrical resistance. The optical equivalent of electrical resistance is called absorption, which, in this particular case, means the conversion of light into heat.

One cause of absorption is impurities in the core material. Impurities can be reduced by carefully controlling the core material.

Another cause of absorption loss is scattering effect. Scattering loss results from fluctuations in the glass density and imperfections at the core/cladding boundary. Again, careful construction and quality control can reduce these losses.

Scattering loss is also inversely proportional to the fourth power of the light wavelength, so scattering losses are lower at longer wavelengths. However, efficient, cost-effective, reliable light sources and detectors are currently limited to wavelengths from about 0.8 to 1.0 $\mu$ m. Intensive research and development efforts are under way to perfect sources and detectors that provide satisfactory operation at longer wavelengths.

Radiation losses are also present in fiber optical systems. Radiation losses result from minute bends in the fiber and from dirt or abrasions on the fiber's outer surface. Microbends often occur during cable manufacture. These can be minimized by avoiding contact between the fibers and other substances—as can dirt and abrasions. Again, careful fabrication and quality control are important.

Total cable losses vary greatly between types of cable and for different wavelengths, but usually range between 2 and 20dB per kilometer. If the attenuation specifications are being used to judge the relative transparency between two or more cables, it is important to be sure the comparison is made for identical lengths of cable and at the same wavelength of light.

Another source of losses in a system are connectors and splices. These losses result from misalignment and reflective discontinuity at the junction. Splices have a lower loss than connectors because splices are carefully aligned and fusion welded or the joint is permanently bonded with index-matching, splicing epoxies that reduce reflection discontinuities. Connectors are detachable, so their alignment is less precise. Splice losses range from about 0.1 to 0.6dB; Connector losses are in the order of 1.0 to 2.0dB.

### Optical receiver

As shown in Figure 8, an optical receiver consists of a photodiode detector, a driver amplifier and a demultiplexer. The following paragraphs discuss each of these parts in turn.

At the receiving end of the optical communications system, the first step in recovering the intelligence used to modulate the transmitting light source is to convert the incoming light back to electrical signals. The device used to accomplish this conversion is called a detector or demodulator. Two types of photodiodes are most useful for this purpose. One of these diodes consists of a PN junction with an intrinsic layer between the P and N regions. It is known as a PIN diode. The other diode is the avalanching photodiode (APD).

In each of these diodes, light striking at or near the junction will raise the energy level of electrons in the junction. In effect, the resistance of the junction is lowered, which allows current to flow (or the flow of current to increase) through the junction and therefore through the external circuit across the diode.

The avalanche photodiode is more efficient than the PIN. As shown in Figure 9, light striking an electron will raise it to a higher energy level. This electron strikes two other electrons and increases their energy level although the original electron loses energy in the process. The two high energy electrons strike additional electrons, boosting them to the high energy level. This avalanche process continues with an increasing number of electrons achieving higher energy levels.

Because higher energy electrons in the junction represent current flow, the avalanche effect causes a gain in signal power through the diode. Because they have gain, APDs have better sensitivity than PIN diodes.

The sensitivity of an optical detector is defined in terms of the minimum light input required to provide a given performance level. The performance level is stated in terms of signal to noise ratio for analog systems and in terms of bit error rate for digital systems.

The APD is more suitable than the PIN for systems with large bandwidth requirements. However, APDs have the disadvantages of high bias voltage requirements and temperature sensitivity. These factors make it necessary to provide a regulated bias supply with voltages in the order of 100 to 400V. Operating at higher bias voltages may also require additional circuitry to compensate for temperature-gain variations.

The electrical output signals from the photodetector are connected to the input of a driver amplifier. The signals at this point may be either analog or digital. The amplifier design is essentially the same in either case. It is important that this amplifier be of a low noise, broadband design and that it does not load-down the photodiode.

The output of the amplifier is an exact replica of the baseband signals used to modulate the light transmitter of the distant end. These signals are passed through the demultiplexer to separate and recover the original information channels.

### Optical fiber vs. wire cable

Fiber optical cable has several advantages in comparison to wire cable. One of these is fiber's immunity to electromagnetic interference. Glass is an insulator so current cannot be induced in it from surrounding sources. Fiber cable may be run parallel and adjacent to power lines without picking up any interference. Similarly, light signals on fiber cable do not cause electromagnetic radiation, so signals on the cable are inherently secure against eavesdropping. This is particularly important for military applications and

## Optical-fiber

voids the necessity for the complex encryption devices used for wire and radio communications.

A multipair fiber cable is much smaller than a multipair copper cable capable of carrying the same amount of traffic. This is an important advantage when installing cable in crowded ducts under city streets. Also, fiber cable is more flexible and lighter weight, which makes it easier to "snake" through duct. Fiber cable is more resistant to heat and moisture than copper cable, which is an advantage where ducts are shared with steam and water pipes.

Signals are attenuated as they pass through any transmission medium. "Repeater" amplifiers are inserted at intervals along the path to overcome the signal loss due to attenuation. The distance between repeaters is determined by the path attenuation. The greater the attenuation per unit length, the more repeaters required for a given path.

High quality optical fiber cable has substantially less attenuation than twisted-pair or coaxial cable, so a fiber system requires fewer repeaters than either of these wire systems. This is an economical advantage, but the fiber-optical system repeater is more complex than the wire system repeater, as shown in the following discussion of Figure 10.

Referring to the figure, analog signals enter the terminal and are converted to PCM signals (encoded) by the PCM channel bank (MUX). The digital signals are amplified and used to modulate the LED.

The light output pulses of the LED are carried over an optical fiber cable to the repeater input. The photodiode at the repeater input converts the light pulses to electrical pulses.

The electrical pulses are detected, amplified, retimed and regenerated by the PCM repeater. The PCM repeater output pulses are converted back to light pulses by another LED. These pulses are transmitted over optical fiber to the distant terminal.

At the terminal the light signals are again converted to electrical pulses. These pulses are processed and decoded, just as any PCM

received signals, to return them to their original analog form. Signals to be transmitted in the opposite direction go through the same process.

A conventional wire cable system operates in a similar manner but does not require any of the optical components.

In a typical system several repeaters are required between terminals. Because an optical system requires fewer repeaters, the total cost of repeaters for an optical system of appreciable length will be less than the repeater costs for a wire system of the same length. The repeater cost comparison is even more favorable when optical systems are compared to coaxial cable systems but is not so favorable when the comparison is made to microwave radio systems.

Currently, the greatest use of optical fiber transmission is in digital trunks between telephone offices. This application has won wide acceptance by telephone companies. A substantial portion of the future requirements for high-density trunks will be filled by fiber optics rather than paired copper cable, coaxial cable or microwave radio.

Optical fiber has a greater bandwidth than wire-cable. The advantages of a wide bandwidth are that a greater volume and variety of signals can be transmitted over a wideband system. The types of signals that are transmitted over telecommunications systems, in order of bandwidth requirements are:

- Voice;
- Special services;
- Data—low, medium and high speed;
- Television, including high fidelity music.

Special services include health-care systems such as medalert, security systems, viewdata, energy management, facsimile, teletype and telex. Figure 11 charts the ability of various transmission systems to carry the types of signals listed above.

Coaxial cable systems have the greatest broadband capability. There are coaxial cable television systems in service that carry more than 50 TV channels. Eight video channels per fiber is the maximum achieved by fiber-optics to date,

although a 9-channel experimental system is planned.

Component linearity problems are the limiting factors on the fiber system. When these problems are solved, the TV channel capacity of optical fiber systems may equal or surpass that of coaxial systems. As previously stated, the optical/electrical conversion step adds to the cost of fiber systems, but they have the advantage of greater repeater spacing. Repeater amplifiers are known as trunk amplifiers in cable television systems.

There are several techniques for transmitting video over optical fibers. The simplest method is illustrated in Figure 12. The video-baseband, electronic signals are used to intensity modulate an LED.

The maximum path length is established by the light source output power, the cable loss, the photodetector sensitivity and the required signal-to-noise ratio of the video output signal at the receiving end. Considering all these factors, the path loss of the optical fiber is limited to around 10 to 15dB, which equates to a fiber length between 3 and 6km. In its most straight-forward form, this system requires an individual fiber for each video signal.

Wavelength division multiplexing (WDM) is a technique for transmitting two or more optical signals over a single fiber. Light sources operating at different wavelengths are used in systems of this type. At the transmitting end, the sources' outputs are coupled to a single fiber and their outputs are separated at the receiving end. If each source is modulated with a different signal, several signals can be sent over a single fiber, as shown in Figure 13.

Another method for transmitting video is shown in Figure 14. The light source is intensity modulated with a frequency-modulated radio frequency carrier. Video signals are used to modulate the rf carrier, which might be in the 30 to 300MHz range; corresponding to the entire TV VHF band.

These frequency-modulated, intensity-modulated (FM-IM) systems can use a laser instead of an LED to achieve a higher signal-to-noise ratio than the previously described systems. The permissi-

ble path loss is around 30dB, so substantially longer paths are possible.

Several frequency-modulated rf carriers at different frequencies

can be combined to form a frequency division multiplexed (FDM) signal. This signal is used to intensity modulate the light source. This FM-FDM-IM process allows

several video channels to be transmitted over a single fiber, as shown in Figure 15.

The number of channels can be increased by using a combination of FM-FDM and wavelength division multiplexing methods, as shown in Figure 16. However, the per channel receive signal-to-noise ratio is reduced each time a channel is added, so the number of channels is limited. This is true for both the FM-FDM-IM and combined FDM-wavelength division systems.

Video channels can be encoded to form PCM signals, which are used to modulate a laser. This method provides the best signal-to-noise ratio. Fiber span with losses in the order of 40dB are possible. Also, repeaters can be used without appreciably degrading the signal so long-haul systems are feasible. The drawback is the large bandwidth requirements for PCM video. This limits the number of channels that can be transmitted over a fiber.

### Video applications

Remote monitoring and surveillance systems probably are the video applications with the greatest potential for fiber-optics use. This is particularly true for systems where it is important to provide any of the following characteristics:

- Immunity to electromagnetic interference;
- Immunity to electrical potential; and
- Immunity to lightning strikes.

Optical fiber systems are superior to wire systems in all three of these areas.

Surveillance systems usually provide black and white transmission of television signals from remotely located cameras to a control monitoring point. Transmission is generally one way, although two-way transmission is sometimes required to provide camera control signals.

System lengths range from less than 5 up to 20km. For the shorter systems, video signals from the camera are used directly to intensity modulate an LED. Longer systems use an FM-IM modulated laser. Long systems, with a number of surveillance points, might be most economically served by using wavelength or frequency

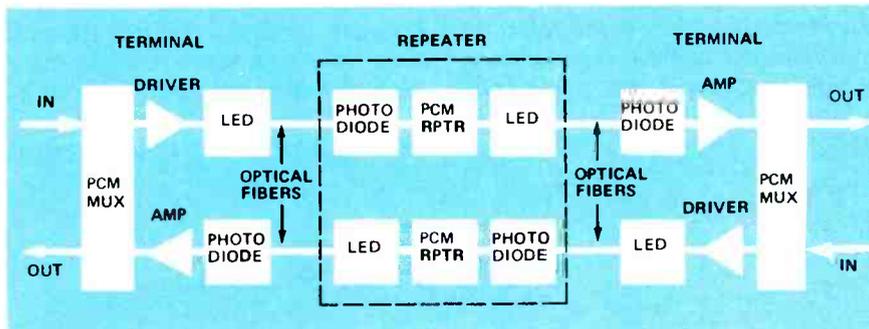


Figure 10. An optical PCM system requires fewer repeaters than a wire system but is more complex.



Figure 11. Optical fiber has a greater bandwidth than wire cable or microwave.

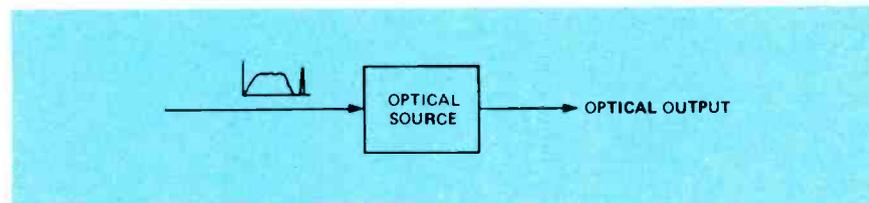


Figure 12. Intensity modulation is the simplest method for transmitting video over optical fibers.

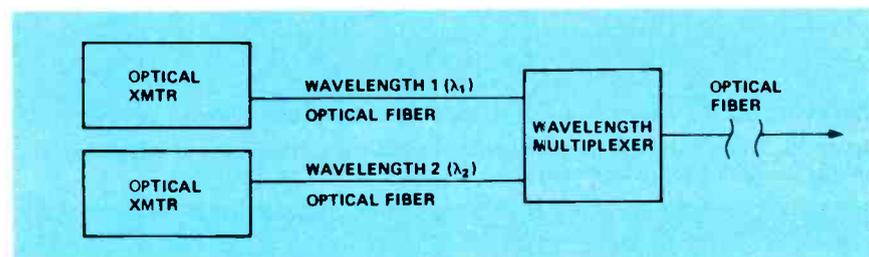


Figure 13. If each source is modulated with a different signal, several signals can be sent over a single fiber with wavelength multiplexing.

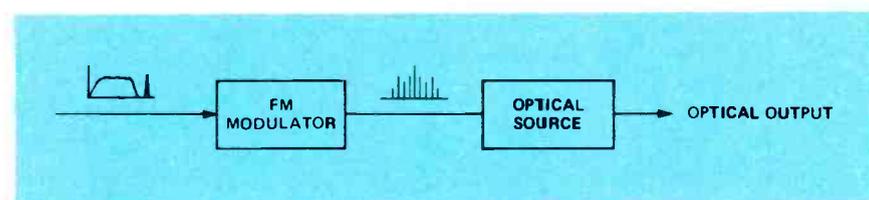


Figure 14. Frequency-modulated, intensity-modulated systems can be used for transmitting video.

## Optical-fiber

division multiplexing to reduce the number of fibers required.

### Broadcast TV

Practically all of the optical fiber video transmission methods have been used for TV broadcast applications. The systems must transmit a color video signal with a 5MHz bandwidth plus an audio signal with a 15kHz bandwidth. The audio uses a subcarrier above the video baseband.

Fiber optics are used for short links; studio to transmitter; auditorium, stadium or theater to studio; or as end links in the broadcast network. Industry standards specify a minimum signal-to-noise ratio of 58dB, end-to-end for a long-haul broadcast link. Since the noise contributions of the end links are only a part of the total system noise, their performance must be better than that of the total system. Consequently, the end link signal-to-noise ratio specification is 67dB minimum.

The first fiber end link to a TV broadcast network was installed between a telephone company central office in downtown Tampa, FL and Tampa Stadium. The link is 8km long and has a repeater located 6.6km from the central office. The light source is a laser diode. The modulation method is FM-IM.

During the 1980 Winter Olympics, two optical fiber video links were used to transmit signals a distance of 3.3km, from the games to the Lake Placid central office. Diode lasers and FM-IM were also used for this path. The upcoming 1984 Olympics will use optical fiber systems to transmit video signals from several locations to a Los Angeles central office. Digital transmission will be used with a line rate of 90 megabits per second.

### Voice frequency transmission

Telephone companies define a voice channel bandwidth as 300 to 3000Hz. Voice channels are used to carry electrical signals analogous to conversations or data signals that have been converted to analog form.

Several methods are used to multiplex vf channels for carrier

transmission over twisted pair, coax or microwave radio.

Low density analog systems use double sideband modulation with carriers in the 8 to 140kHz range to frequency division multiplex up to 6 vf channels. High density systems use single-sideband, suppressed-carrier modulation to multiplex up to 600 vf channels.

Digital systems use pulse code

modulation to time division multiplex 24 vf channels into the 1.544 megabits per second T1 carrier or 48 channels into the 3.12 megabits per second TIC carrier. Digital systems require a greater bandwidth than an analog system with the same number of channels because a signal in the general form of a sine wave must be sampled at least twice per cycle to be

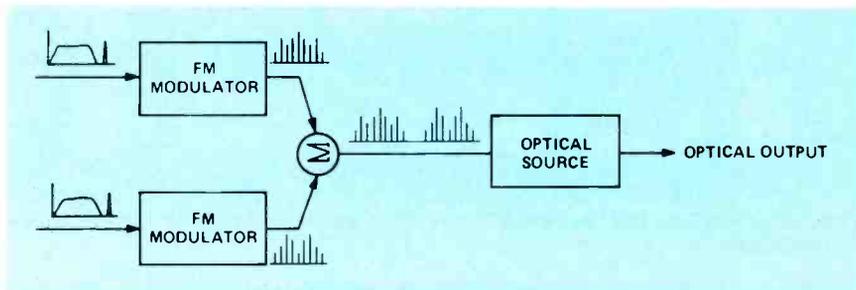


Figure 15. With FM-frequency division multiplexing-IM, several video channels can be transmitted over a single fiber.

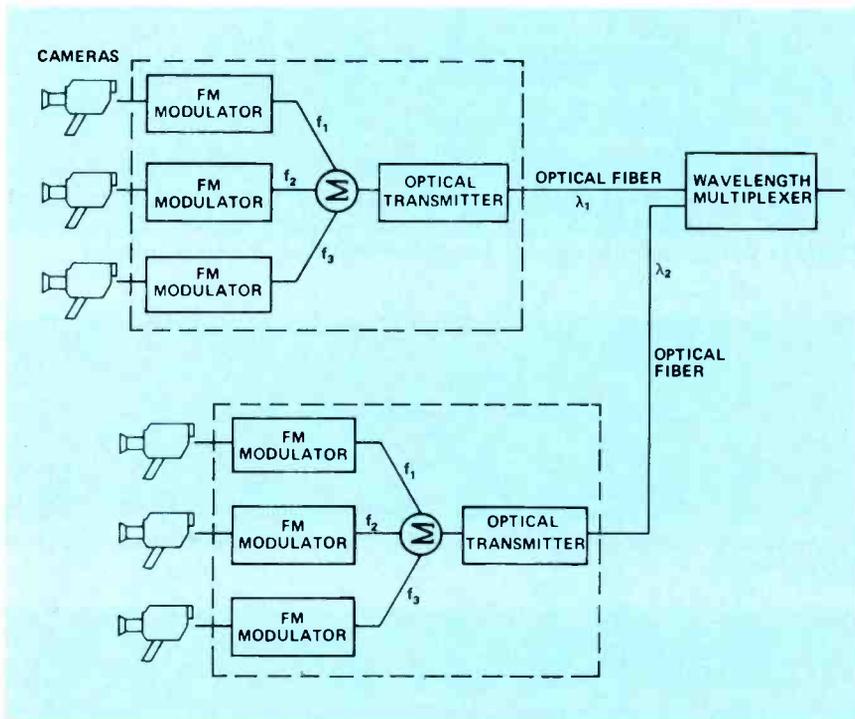


Figure 16. When FDM-FM is combined with wavelength division multiplexing, the number of channels can be increased.

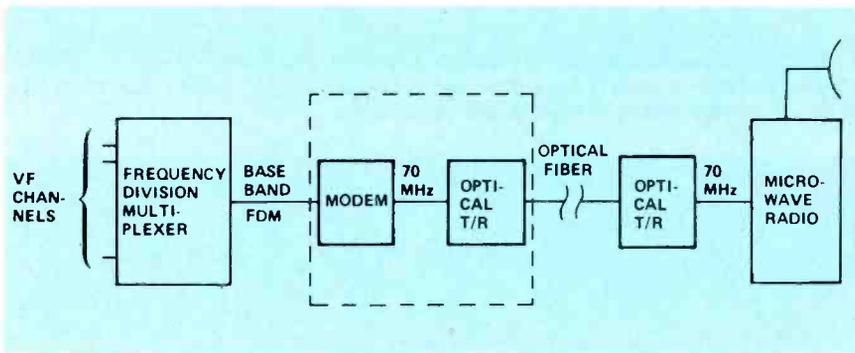


Figure 17. Systems with a fiber-optics link to microwave radio are being developed.

accurately represented digitally. For example, a signal with a 4000Hz bandwidth must be sampled at a rate of 8,000 times per second, minimum.

The outputs of any of the above multiplex systems can be converted to light signals for transmission over optical fibers. The low-density analog carrier can be used to intensity modulate an LED in a short range FDM-IM optical system.

There is a demand for this kind of low-density system to serve as an entrance link to power generating stations. The insulating qualities of the fiber protect personnel and equipment from voltages that might accidentally be placed on the communications systems by line-to-ground faults. Fiber systems provide more positive isolation from these faults and are more economical than wire systems, which rely on transformer or capacitor isolation devices.

These optical systems are seldom more than one or two kilometers long. The quality of the voice channels is very good. They can be used for data transmissions as well as voice.

The analog output signal from the higher-density FDM system can be used to frequency modulate an RF carrier. The modulated carrier is used in turn to intensity modulate an LED or laser. The result is a high channel capacity, FDM-FM-IM optical fiber system.

There is a demand for short to medium length (up to 12km) systems of this kind to serve as links between microwave radio stations and communications centers in congested areas. The first reason for this demand is the limited microwave frequency spectrum. Generally, it is difficult to obtain a frequency assignment in these areas because most of the frequencies have already been licensed. The second reason is the increasing number of objections, by environmentalists and municipal authorities, to microwave antenna installations. A possible arrangement for an optical system for this purpose is shown in Figure 17.

The digital output signals of a PCM system can be used to modulate an LED or laser. As previously stated, PCM optical trunks between telephone offices

are the largest application of fiber-optics to date. However, the use of digital microwave systems is increasing and PCM optical systems could serve as entrance links for these systems. Digital microwave systems are becoming more popular, despite the higher bandwidth-per-channel requirements, because they cost less than FM systems when the cost of the associated multiplex and switching equipment is taken into consideration.

#### Data and computer systems

Several properties of fiber-optic transmission systems make them particularly suitable for computers and data network applications. One such application may be considered as internal to a computer. The transmission distances are very short. For example, between computer components inside a cabinet, or between cabinets or racks in the same room. Because the distances are so small, a directly modulated LED can be used for the transmitter and a PIN diode can be used for the receiver.

High transmission speeds and small error rates are required. Speeds around 200 megabits per second with error rates as low as 1 part in a thousand billion ( $10^{-12}$ ) are typical. The smaller space requirement of fiber in comparison to coaxial cable and the elimination of errors due to potential differences and ground loops are the principal advantages gained by using fiber in this application.

Another application for fiber optics is in inter-system communications. These systems interconnect between computers and peripheral devices within the same buildings or cities. Transmission distances range from less than 100m to up to 12km.

The interconnections may be point-to-point, a looped network, a common-bus parallel arrangement or a star network. A lack of suitable coupling devices (taps) makes it difficult to establish some network arrangements. However, this problem will be solved when new taps are developed.

Data rates up to 64kb/s are used for computer to peripheral connections. Depending upon the accuracy requirements of the specific application, bit error rate specifications vary from  $10^{-6}$  to  $10^{-9}$ .

The stringent space and weight limitations of aircraft, ships and submarines and their increasing use of computers and electronic devices combine to make optical fiber systems an excellent choice for these applications. The systems can be used to interconnect between component parts of computerized systems used for navigation and control and to connect these systems to remote display devices. In many ways aircraft systems are small-scale versions of the data systems previously described, but aircraft systems may have greater accuracy requirements. Also they must operate in adverse environments of altitude, temperature and vibration.

An emerging opportunity for fiber-optic systems lies in the area of business communications. There is a growing demand by business for an integrated communications system capable of handling all types of traffic: voice, data and video.

Such a system is technically and economically feasible. The nature of the traffic and the technology make a digital system most suitable for this application.

Since the greatest current demands for this type of system is by business, there is a requirement for a system to operate on the user side rather than the telephone company side of a private branch exchange (PBX).

The operating specifications for this system are the same as those previously described, insofar as voice and data traffic are concerned. The per-channel bandwidth requirements for video signals are generally somewhat less than those for broadcast or cable TV systems.

Optical fiber systems are quite suitable for small-to medium-sized systems of this kind. Several of these systems could be tied together by microwave radio or land lines. This kind of cluster arrangement appeals to businesses with branches in several different geographic locations.

*This story is provided courtesy of GTE Lenkurt, Inc.; copyright, 1981 GET Lenkurt Demodulator.*



# How to repair electronic garage-door openers

By Carl Babcoke, CET

**Few experienced TV/radio technicians repair home-type garage-door openers, although the circuitry is far less complicated. This case history describes the first attempt of an expert color TV technician to troubleshoot and repair erratic operation in a Genie door opener.**

Modern garage-door openers perform these general functions:

- Raising or lowering the garage door is initiated by pushing a button either on the radio-control unit or inside the garage.
- The garage door is locked in the position it is in when the mechanism stops.
- A safety circuit stops the motor at any time when easy movement of the door is hindered. Therefore, downward motion of the door onto a person or a car is not likely to cause injury or damage.
- Many models include a light that is turned on each time the motor runs and remains lighted for a minute or two afterward.

Of course, the methods of obtaining these functions vary with the brand and model.

The repair described here was performed by the writer on his own garage door. However, the lessons learned from it can be applied to other garage doors.

## Genie model 450

Genie model 450 (from Alliance Manufacturing) meets all these

basic general specifications in an all-solid-state machine. Figure 1 shows one of the two identical door openers in the writer's home garage. An internal view of the radio remote control is shown in Figure 2. The remote control has a 9V battery mounted internally, so no connections are needed to other power.

Locations of several important components are described and pointed out in Figure 1. A rigid track connects the mechanism to the bracket fastened on the door's top edge. The chain dangling in Figure 1B is used to disconnect the door opener from the door when the electric power has failed or when manual operation of the door is desired. Inside the track is a threaded rod that rotates when the motor runs. The follower mechanism is moved by the grooves in the rod and it in turn moves the door.

Each limit switch is a leaf type with a lever to close it and they are wired in parallel electrically. Closing either switch changes the electronic control to the *stop* mode. A switch closure of only short duration is sufficient. Because of the


gear-reduction drive, the door coasts very little after the motor power is removed. Rotation direction of the motor is changed electrically (rather than mechanically) by relay switching of the motor windings (Figure 3).

## Erratic operation


The twin Genies performed well for almost two years, except for two service calls during the 1-year warranty period, before serious trouble developed. One afternoon, we came home and found one garage door open. However, the door obediently went down and stayed down the next time the remote control was used.

False operation of these door openers is rare because the radio control system requires a specific carrier frequency plus a specific audio modulation before activation can occur. A violent thunderstorm with lightning had moved through the area the previous night, but storms never had caused any false operation before.

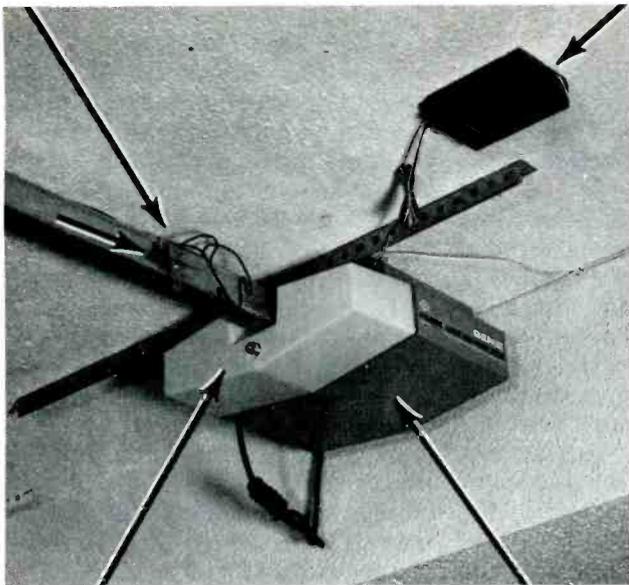Unfortunately, the door opening was the first of many unpredictable openings. That was an intolerable situation, so the offend-



A

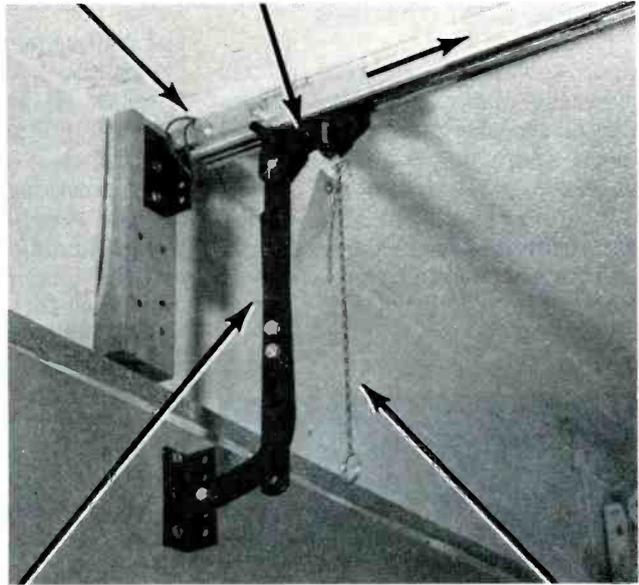

B

**Figure 1** Two views of model 450 Genie garage-door opener show locations of major components. (A) At the motor-drive end, the top-left arrow points to the door-up limit switch, the arrow on the drive rail beside it shows direction of the door when it is being raised, the top-right arrow shows the radio remote-control receiver, the lower-right arrow points to the white plastic cover over two light bulbs that stay lit for about two minutes after the door is moved. (B) The upper-left arrow points to the door-down limit switch, the upper-center arrow indicates the follower assembly that moves down the threaded rod, the arrow to the right on the rail shows direction of the follower during door-up movement, lower-left arrow points to the arm connecting follower and door, and the lower-right arrow identifies the chain used to disconnect the door opener from the door when manual operation is desired (for example, when there is no ac power).

ing door was locked, and the ac plug for that opener was pulled.

### Preliminary troubleshooting

A call to the installation and service man for the installing door-opener company revealed that they did no troubleshooting, but usually installed the entire *sequencer* circuit board, which cost about \$35 plus labor.

After considering all alternatives, I decided to make some simple preliminary tests to determine if a short in the manually operated switch or an intermittent in the radio control was responsible.

The white plastic cover over the light bulbs was removed, allowing access to the three terminal screws. Two terminals had two sets of wires that went to the wall switch and the radio receiver. However, with all these wires disconnected, the motor continued to raise the door intermittently. There could be no doubt, *something in the sequencer circuit was defective.*

Having gone so far, I decided to continue the investigation, which unfortunately required removal of the metal housing of the motor/sequencer mechanism. Even worse, the metal housing could not be

removed until that end of the opener was unbolted from the ceiling. This was beginning to present some serious physical problems. How does one man take down both ends simultaneously? Incidentally, the motor/sequencer unit is heavy and difficult to manage when it is mounted at ceiling height. I was beginning to regret the decision to test the unit.

Finally, noticing that the front end of the rail was fastened by only one bolt that could be loosened enough to allow the motor/sequencer end of the rail to be dropped down, I decided to unbolt the motor/sequencer and rest it on top of a stepladder, with the rail still fastened at the door (Figure 4). Although that location was more convenient than the original one at the ceiling, it was necessary for me to stand on a step while balancing multimeter, tools and clip leads for the tests.

No servicing information was available, so it was necessary to develop my own. Figure 5 shows left and right rear views of the motor/sequencer, with the sequencer circuit board at the left side and motor capacitor and B+ power transformer at the right of the motor. The reduction gears are enclosed and not visible from the

outside.

Three screws held the circuit board to the cast-metal frame. No disconnect plugs were furnished, but when the board-mounting screws were removed, the board could be moved around and turned over because the connecting wires had sufficient slack (Figure 6).

Wiring on the board was traced visually, as far as possible, then other connecting continuities were verified using the low-resistance range of a DMM. Resistors were color-coded types, and each resistance was measured. Finally the schematic of Figure 7 was developed and used to test the performances.

### Electronic circuit tests


One integrated circuit, three transistors, five diodes and three enclosed relays comprised the major components. The diodes and various transistor junctions were tested by the voltage-drop method (some digital multimeters have an excellent diode test that applies a constant current and measures the resulting voltage drop). However, none was judged defective.

Voltages at most circuit junctions were measured during normal operation and again when the circuit was attempting to move the

## Garage-door openers

door upward. Of course, by this time the motor had been disconnected and the garage door locked down manually because complete operation was not wanted.

The only voltages that varied significantly between normal and abnormal operation were those at base and collector of Q1, the up-

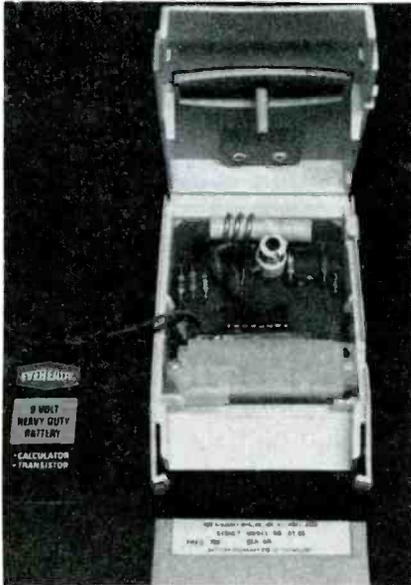

**Figure 2** The radio remote-control transmitter (normally operated from a car) opens easily to permit installation of a replacement 9V battery. Several thousand combinations of carrier frequency and audio-modulation frequency minimize the chances of false operation.

relay driver. At unpredictable times, a saturation bias of about +0.7V appeared at the base of Q1. Of course, during those times the collector voltage was almost zero and relay X1 was activated. To check the possibility that internal leakage in Q1 was producing its own excessive bias at incorrect times, the base was unsoldered and voltage test made again. However, pin 1 of the sequencer IC produced more than +0.7V while the Q1 base measured about zero. This proved the voltage was coming from the IC and Q1 was not defective.

Next, while the various important voltages were monitored with meters, I attempted to step the sequencer through the various stages of control. Normally, starting with the door down and the

motor not running, these should be the various modes:

(1) In the *off* mode, no voltages from the IC reach the base of Q1 or Q2, the motor is not energized, and the door is motionless in the down position.

(2) The *door-up* mode is initiated by grounding the manual/radio-control terminal. This applies a logic low to IC pin 7, producing +0.7V of bias at the base of Q1, activating up-relay X1, which rotates the motor in the proper direction to raise the garage door.

(3) When the door reaches the top, that limit switch applies a logic low to the IC pin 12, removing the saturation bias from Q1, deactivating X1, and stopping door and motor in a second *off* mode.

(4) The *door-down* mode is initiated by grounding the manual/radio-control terminal (producing a low at IC pin 7), which causes the IC to deliver +0.7V from pin 2 to Q2 base, activating door-down relay X2 to rotate the motor (opposite the previous door-up direction) and move the door down.

(5) The third *off* mode begins when the door reaches the floor and a limit switch is tripped, thus applying a logic low to IC pin 12 again. The IC then removes the saturation bias from the Q2 base, deactivating relay X2 and stopping door and motor.

That completes one cycle of sequencing from the *off* mode with door down to *off* mode with the door down. Notice that *it is impossible to go from one door movement to the other without first having the door (and motor) stopped between the two modes*. This has several important advantages. Only one *off* function is necessary, and it operates from both limit switches (alternately) which are connected in parallel.


A more important reason for the *off* mode is *safety*. For example, assume that the door is coming down, and a dog is caught between the door's bottom edge and the floor. After moderate pressure has been applied to the dog, the overload mechanism (at rear of motor in Figure 5) operates. This too changes the IC to the *off* mode, stopping the door movement. It is necessary only to activate the mechanism again (by remote radio or garage manual switch) to energize the motor, which moves

the door upward and off the dog.

Now, back to tests of the sequencing actions. With the motor disconnected, it was necessary only to monitor the dc voltages at IC pins 1 (for door up), 2 (for door down) and 3 (for light on), as the sequencing is activated by a clip lead grounding the manual/radio-control terminal.

In this case, the sequencing was incorrect because a dc voltage of +0.7V would appear erratically at pin 1, regardless of which step of sequencing was selected.

Because these last voltage measurements were performed while the Q1 base was disconnected from the IC, there could be no doubt: *the IC was defective*.

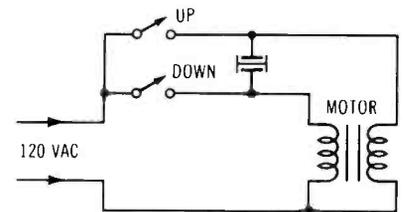

**Figure 3** Reversing the opener motor is performed differently than with larger general-purpose motors. Both motor windings are identical. Direction of rotation is determined by which winding receives direct power and which winding receives phase-shifted power through the non-polarized capacitor. This same simplified switching has been used in older television remote controls that have motors.

### Locating an IC

An IC could not be located in the city but complete circuit boards were in stock. One dealer provided a phone number of the factory parts department, and a long-distance call had only partial success. The woman in the parts department verified that complete boards were available for \$32, but it was very unlikely that an IC could be found. Evidently the Alliance company believes that supplying complete boards is sufficient. Finally, I asked them to send the IC, if one could be located there, and to notify me by mail if an IC was not available.

About 10 days to two weeks later (without any further word from the factory), a COD package arrived. Total cost was slightly more than \$10 for the IC and instructions for changing the value of one resistor to accommodate this particular brand of IC.

The factory address and phone

number (for anyone else needing Genie parts) is:

The Alliance  
Manufacturing Company  
22790 Lake Park  
Alliance, Ohio 44601  
Phone: 1-216-821-1221

### Installation of IC

Removal of the defective IC was easy. Excess solder was removed

by manual operation of a vacuum device. Installation of the replacement IC was equally simple, but with some concern about the proper pin-1 end identification. Several precautions were taken by grounding soldering iron and the technician's body during handling of the IC to prevent possible damage by static electricity (this IC was believed to be a FET or MOSFET

type). R12 was changed from the original  $4.7K\Omega$  to the suggested  $1.8K\Omega$ .

Finally, the circuit board was screwed to the cast framework, and the sequencer unit was ready for testing (the motor/sequencer unit remained on top of the ladder).

*Tests of the sequencing modes were successful* (without the motor). Of course, it was not practical to test with power applied to the motor while the unit was on the ladder.

The rear cover was fastened in place and the motor/sequencer unit bolted loosely to the ceiling, wires from the wall switch and the radio control were connected, the door was unlocked and the line cable was plugged into ac power. The door opener was ready for the test with full power.

When the hand-held radio transmitter was activated, the door raised to the top and stopped. With mounting relief, I stepped the opener through several complete sequences. There were no malfunctions.


For a final wrap-up, the unit was bolted tightly to the ceiling, and the plastic cover placed over the light bulbs. Again, the door opener was stepped through all functions and all was well.

### Lessons learned


Although the details are different for other brands and models of garage-door openers, the same general functions are performed. And that is the *first* requirement for any repair: *You must understand what the unit was designed to do.*

In this case, I thoroughly understood what the garage-door opener was supposed to do. Not only from operating it as a normal customer, but also because my cousin and I designed a door opener in 1944 for manufacture after the war. Unfortunately, the company went bankrupt (building juke boxes) before they could begin production of the Babcoke/Babcoke door opener.


You might be interested in a general description of that crude unit. The mechanism had worm gears to rotate a grooved drum, which held and moved several turns of steel cable. The cable was held in place by pulleys as it moved

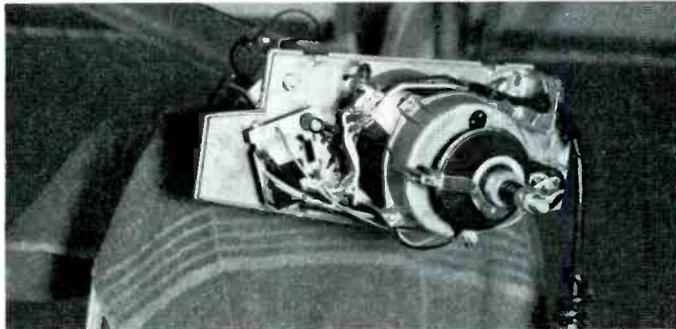

**Figure 4** Unbolting only the motor/sequencer end of the door opener allowed that end to be placed on a stepladder, thus avoiding the time-consuming work of dismantling the entire opener. Measurements and adjustments can be made while the opener is on the ladder, but the motor should not be allowed to run.

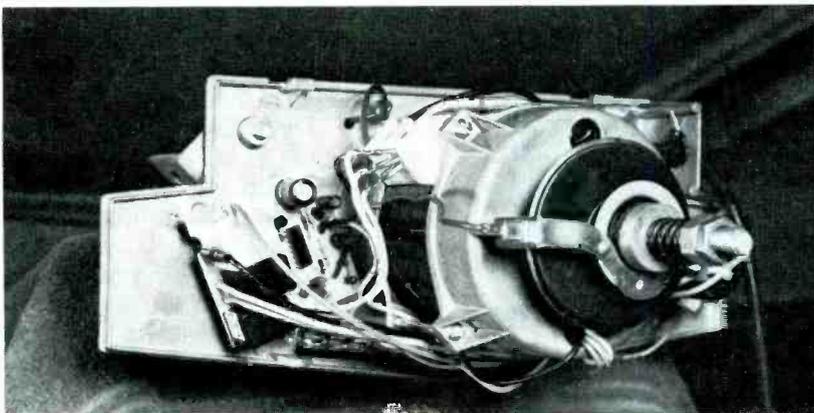


A

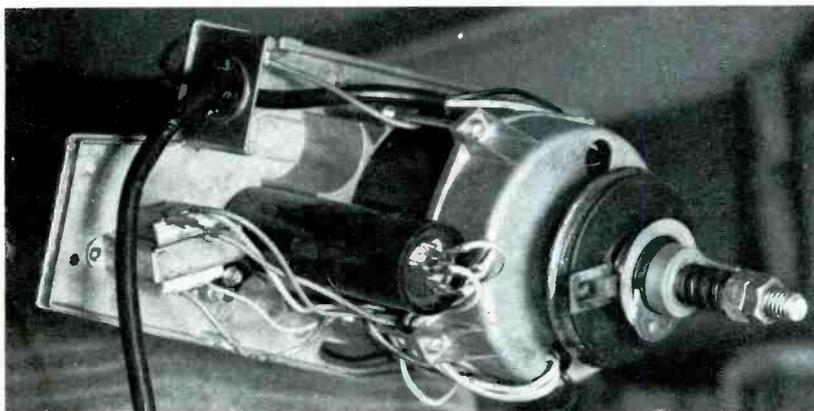


B

**Figure 5** Two views of the motor/sequencer unit show locations of important components. (A) The left view shows the sequencer circuit board mounted on the front wall of the metal frame. (B) On the right is the motor-starting phase-shifting capacitor, and at the far right is the isolation-type power transformer. On the rear of the motor shaft is the overload switch that stops the door movement if the door jams, is locked, or strikes an object.

## Garage-door openers

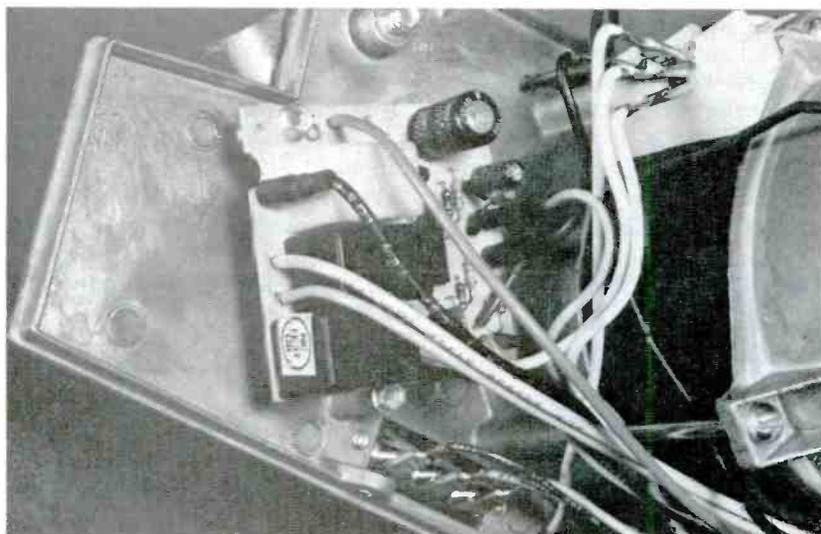

A

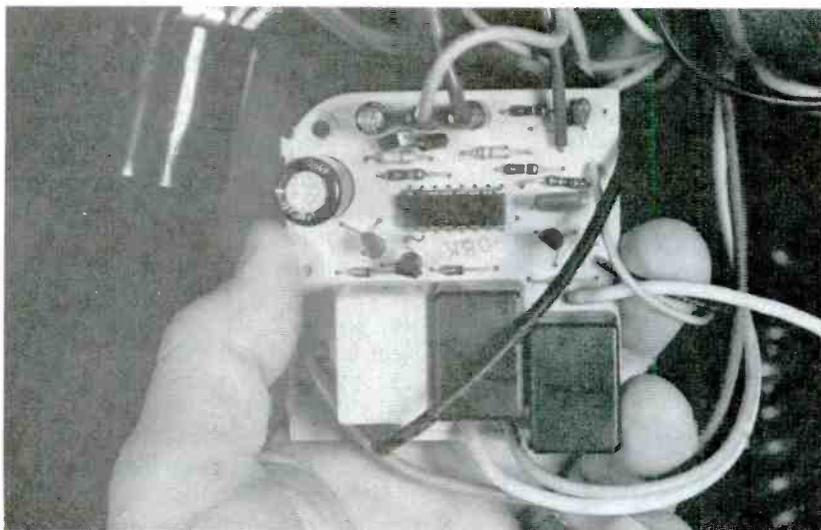

B



C


**Figure 6** The sequencer circuit board can be unfastened from the frame during measurements. (A) Three screws hold the board in place. At lower-right of the board are seen the three terminals for manual switch and radio receiver. (B) This is a closeup view of the board's top after removal. (C) Wiring side of the board shows etched wiring similar to that in most TV receivers.

the garage door. A bracket mounted near the bottom of the door activated limit switches at door-open and door-closed positions.

The upper limit switch had extra contacts that activated the motor-reversing relay when the motor was started at the door-up position. As soon as the door moved away from the limit switch, the reversing relay returned to normal, but the motor by that time was operating on the running winding, and the starting winding had no power because the internal centrifugal switch was open. Therefore, anytime the door's descent was stopped (by an object under the door or by the limit switch), the motor would be automatically in the non-reversed mode to raise the door.

This ancient unit had a radio remote-control system long before transistors were invented. The transmitter used two tubes (type 49, I believe) as a push-pull oscillator that operated on raw ac pulses from an auto-type vibrator and step-up transformer. The RF output signal was sent to a rectangular loop mounted underneath the car. Operating frequency was either 175kHz or 262kHz. At the radio receiver (which was on the same chassis as the motor control and reversing relays), the signal was received by a larger tuned loop, and amplified by one pentode tube followed by an IF-type transformer that fed a diode detector. A sensitivity control was provided to give a measure of noise immunity.

The dc voltage from the diode detector drove the grid of a 2050 grid-controlled gaseous rectifier (thyratron). These tubes were the forerunner of our modern SCRs, and have several SCR characteristics. After a thyratron was activated into conduction, removal of the grid signal would not stop the conduction. It was necessary to remove the plate voltage long enough for the ionization to disappear before plate conduction would cease. This was the basis for the safety overload operation. The motor mounting was made to swivel slightly with increasing mechanical load. Therefore, if the door struck something before it reached the floor, the swiveling of the motor mounting tripped an

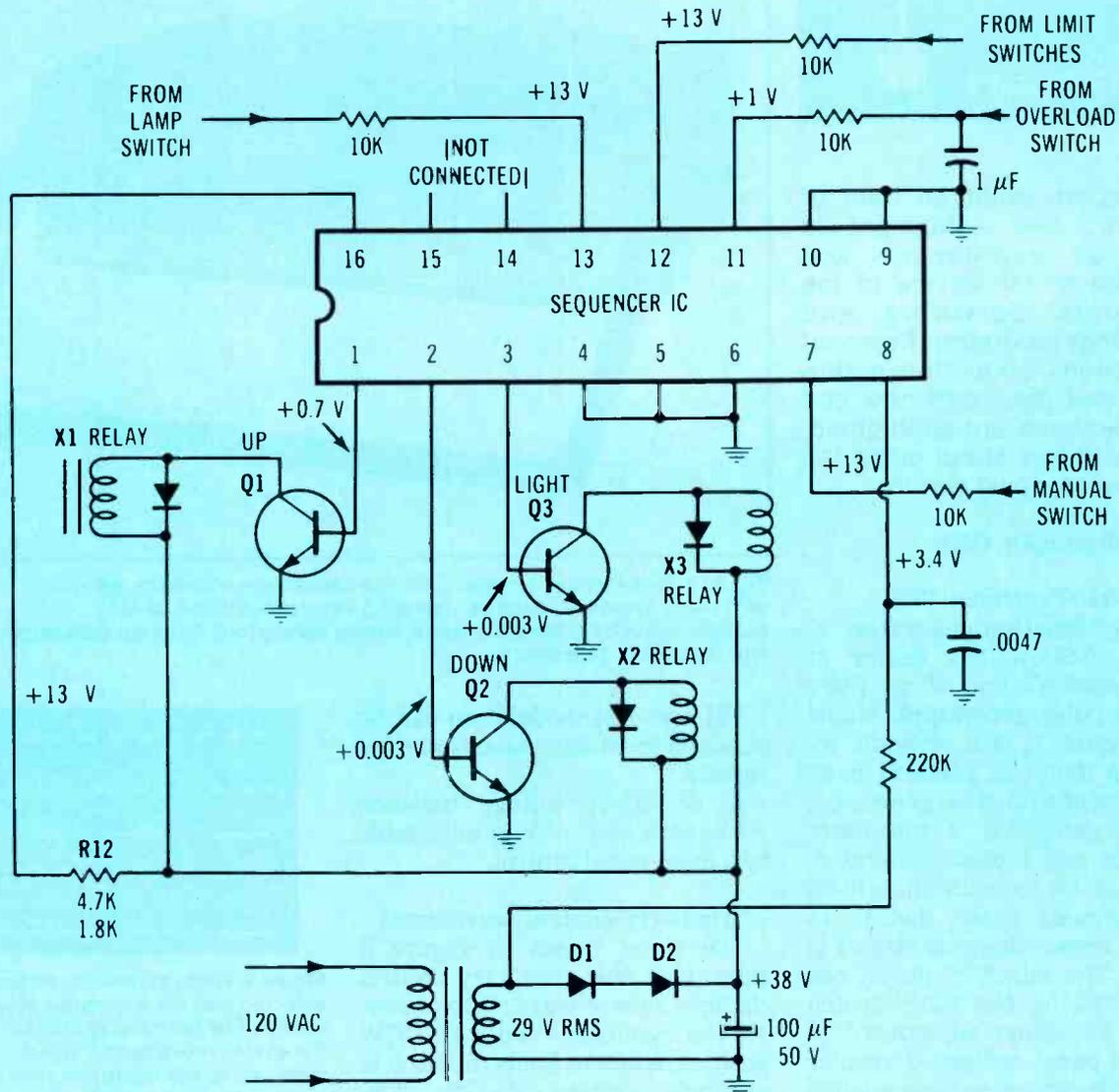

**Figure 7** This schematic was developed by visual examination and meter measurements of the Genie model 450 sequencer unit. It is not a factory schematic. All voltages are assumed to be normal, except the +0.7V saturation bias at the Q1 base, which appeared erratically because the IC was defective.

overload switch, which temporarily removed the positive dc voltage from the plate. In the absence of a remote-control signal, the grid had cut-off bias, so the tube was de-ionized and it allowed the motor-on relay to open, stopping the motor.

Strangely enough, the old design performed identical functions and gave almost the same protection as provided by the much newer solid-state Genie.

The *second* requirement for successfully repairing any unfamiliar electronic device is: You must know how to test the functions. The *third* requirement is related to the second: You must have proper

equipment and tools to make all needed tests accurately.

### Comments

Details of this troubleshooting-and-repair case history are presented for two reasons. First, they give technicians some familiarity with the functions and circuits of electronically controlled garage-door openers, so they will not be reluctant to attempt similar repairs. Second, they show how a good general knowledge of electronics can be used to troubleshoot almost any kind of machine.

One more comment: During almost seven months of constant

operation after the described repair, the Genie garage-door opener has performed perfectly.

If you have had a similar experience troubleshooting electronic household appliances, send a description to **Electronic Servicing & Technology**. Payment will be made upon publication.

**ES&T**

Each report about an item of electronic test equipment is based on examination and operation of the device in the Electronic Servicing and Technology laboratory. Personal observations about the performance and details of new and useful features are spotlighted, along with tips about using the equipment for best results.

By Carl Babcoke, CET

**B&K-Precision 3020 sweep/function generator**

Model 3020 is the center of B&K-Precision's line of six function and pulse generators. Model 3020 (Figure 1) is a versatile instrument that can perform most operations of a function generator, a sweep generator, a tone-burst generator and a pulse generator. Frequency (or repetition) rate of output signals spans 0.02Hz to 2MHz in seven ranges arranged in decades. The output frequency can be adjusted by the range-switch position vs. either adjustment of the front-panel calibrated vernier dial or a dc control voltage applied to the proper phono input connector on the back panel. This control voltage can be a non-varying dc voltage, or it can be a dc waveform. The voltage-controlled oscillator (VCO) allows many AM and FM functions.

A choice of three conventional output waveshapes (sine, square or triangle in Figure 2) is provided by push-buttons. These standard waveshapes can be modified by the symmetry variable control in normal or inverted modes. For example, square waves become pulses, triangles become ramps (sawteeth) and sines are stretched and distorted.

The sweep mode enables rapid assessment of frequency response in amplifiers, tone controls, equalizers and tape recorders.

Tone-burst mode is useful for TIM tests, tone-burst decoder alignment and other audio measurements.



Figure 1 B&K-Precision model 3020 is a 2MHz sweep/function generator with many excellent features, including several functions usually accomplished by pulse generators, sweep generators, function generators and tone-burst generators.

FM and AM modulation can be obtained from internal or external signals.

A dc offset voltage between +5V, zero and -5V is adjustable by a front-panel control.

**Symmetry-control waveforms**

The three traces in Figure 3 show how the symmetry control changes square waves into pulses. At the symmetry control's CCW position, a detent holds the knob in calibrate position. As the symmetry control is slowly rotated

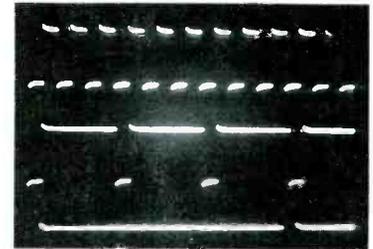


Figure 3 When squarewaves are selected and the symmetry control is rotated CW from the calibration point, the cycles move farther apart (decreasing the repetition rate) to form pulses. The pulse width does not change from symmetry adjustments.

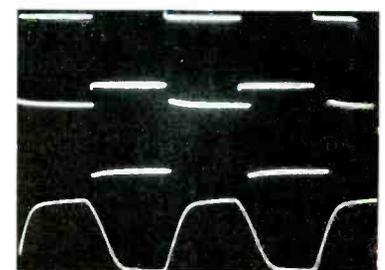
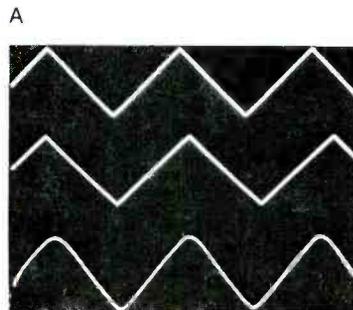
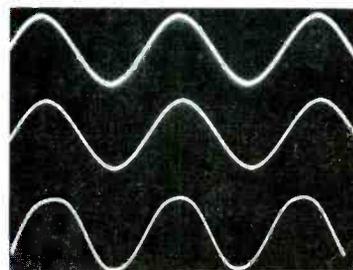


Figure 2 These are the three basic waveforms from model 3020. The top trace shows the waveform at 20Hz; the center trace at 1000Hz and the bottom trace at 2MHz. (A) Sine waves were good, except for a tiny pip at each peak of the low-frequency signals, and a slight rounding of the tips when the frequency was near 2MHz. (B) Some edge overshoot is evident in the low-frequency square waves, and slow rising and falling edges at 2MHz. (C) All triangular waveforms had excellent linearity, although the 2MHz triangles had some rounding of the peaks.

clockwise, the square waves on the right begin to move to the right (as viewed on a scope) and become farther apart. Notice that the pulse width is not changed.

This action can be continued until the ratio of space to pulse width is about 40-to-1. With this ratio, the pulses are so narrow that they are difficult to see on a scope screen. Ramps appear to have perfectly vertical rising edges. (*Important:* If the symmetry control is rotated completely clockwise, no output signal is obtained. Therefore, always begin adjustments with the symmetry

control in its calibrate position.)

All increases of space between pulses of fixed width are decreases of the repetition rate. Therefore, any use of the symmetry control changes all calibrations of the frequency dial.


Remember that *both* pulse width and repetition rate are changed by adjustments of the range switch *and* the frequency dial, when the symmetry control is not at its calibrate position. However, rotation of the symmetry control varies the repetition rate but *not* the pulse width. Therefore, if a specific duty cycle or repetition

rate is needed, both the frequency and symmetry controls must be adjusted alternately until the desired conditions are shown on a scope.


Figures 4 (sine waveshape), 5 (pulse waveshape) and 6 (triangle waveshape) show a few of the many possible waveforms resulting from normal and inverted symmetry adjustments. These are compared with the TTL pulses coming from a phono jack on the rear panel.

### Frequency-sweep mode


Almost any section of the 2MHz

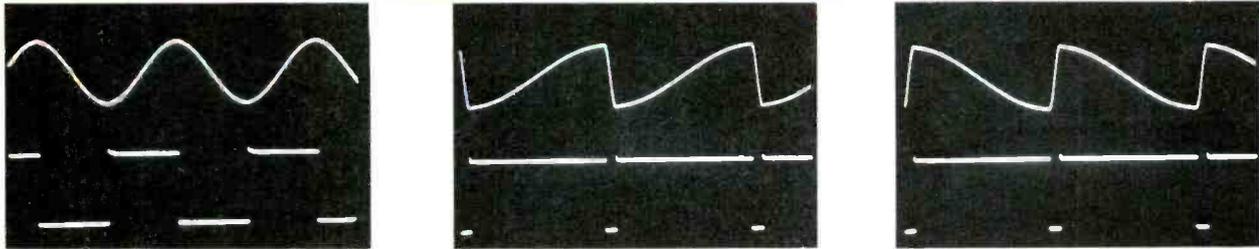

**Figure 4** Top trace in each waveform photograph is the sinewave appearance under stated conditions, while each bottom trace shows the corresponding TTL waveform (that is available from a phono jack on the rear panel). (A) These are normal traces when the symmetry control is in the calibrate position. (B) CW rotation of the symmetry control produces a distorted ramp waveform. With this normal symmetry mode, the ramp rises to the right. (C) These are the same conditions as in B, but the symmetry has been inverted by the normal/inversion pushbutton. The ramp falls to the right. Notice that the TTL pulses did not invert with the signal waveform.

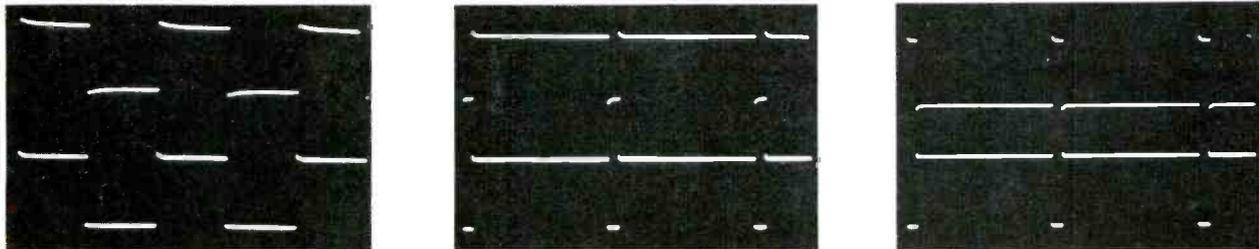

**Figure 5** Top trace of each photograph is the modified squarewave appearance under stated conditions, while each bottom trace shows the corresponding TTL waveform. (A) The unmodified squarewave and the TTL pulses resemble each other. (B) CW rotation decreases the repetition rate. The TTL pulses (lower trace) change in step. (C) Changing the symmetry normal/invert switch to invert position inverted the pulses, making them positive-going (top trace), while the TTL pulses (bottom trace) were unchanged.

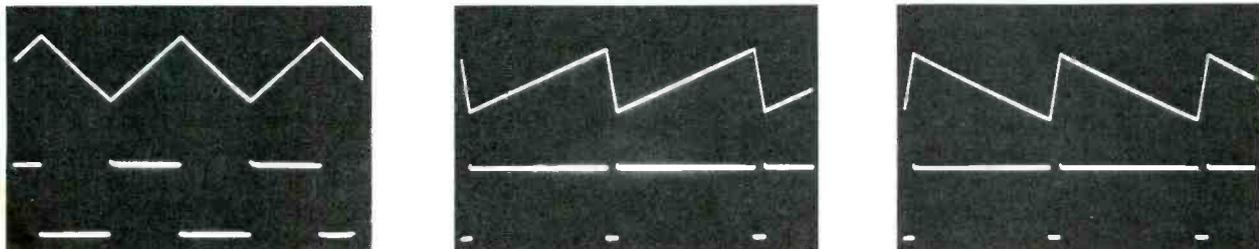

**Figure 6** Top trace of each photograph is the appearance of triangular waveshapes under the stated conditions, and the bottom trace shows the corresponding TTL signal. (A) These are the normal triangular waveshapes with the symmetry control in calibrate position. The TTL signal shows square waves. (B) CW rotation of the symmetry control changes the triangles to ramps. Continued CW rotation lengthened the up side and made the falling side more vertical. The TTL signal consists of pulses that are identical to those from pulses or sinewaves. (C) Changing the normal/invert switch to invert position inverted the ramps, but the TTL pulses were unchanged.

## Test lab

range of output frequencies can be swept, provided the ratio of end frequencies does not exceed 1000-to-1. A popular test is to measure frequency response of an audio amplifier between 20Hz and 20kHz (the maximum allowable 1000-to-1 ratio).

Figure 7 shows an audio-sweep pattern with amplitude increases at 500Hz (at left) and 16kHz (at right). These level boosts were obtained by feeding the 3020 generator signal through a 10-frequency audio equalizer. One of the difficulties is determining where the various frequencies are located on the waveform.

The same audio-sweep signal can be used for measuring equalization or adjusting bias levels in tape recorders.


### Tone-burst tests

Two examples of tone-burst applications are shown in Figure 8. Both are 1000Hz sinewave carriers keyed into bursts. The first example shows a burst of about 4mS and a space between bursts of about 14.4mS. Notice that only whole cycles are generated. Corresponding TTL pulses are shown by the bottom dual trace.

A much longer burst is pictured in Figure 8B. Approximately 84 sinewaves are produced. Therefore, the burst required 84mS. The top trace shows the output signal of a compressor when the compression was disabled, giving maximum gain. When compression was switched on, the gain was reduced in an exponential curve (bottom trace). A gain reduction of about 6dB required 16mS (16 cycles), which is typical of many audio compressors. A long burst was chosen to allow stabilization of the output level at the maximum gain reduction (minimum output amplitude), and a longer space between bursts was needed to allow a return to maximum of the output amplitude (zero gain reduction).

### AM and FM modulation

Model 3020 can produce several types of modulation, including amplitude modulation (Figure 9A), suppressed-carrier modulation (Figure 9B), and frequency modulation (Figure 9C).

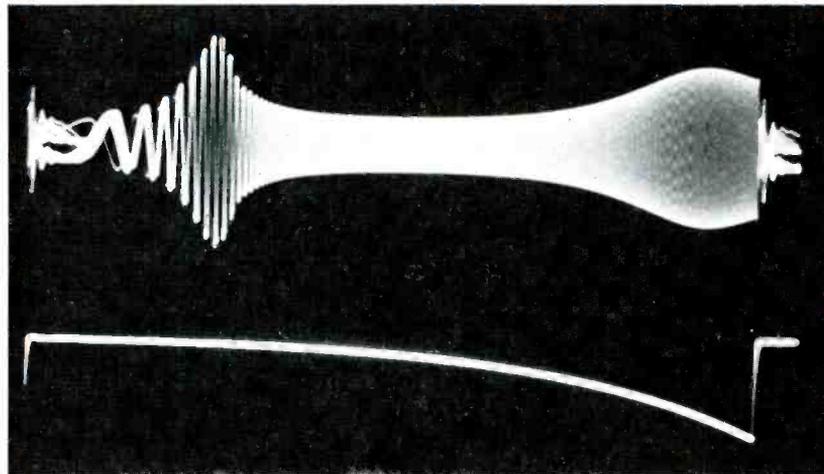

**Figure 7** This 20Hz to 20kHz audio-sweep pattern has increased amplitude at 500Hz and 16kHz, showing the action of a graphic equalizer with 8dB boost at 500Hz and 16kHz. A graphic equalizer can be used to calibrate audio sweeps. Log sweep was employed here to spread the low frequencies. These controls required adjustment to obtain audio sweep: sinewave pushbutton; frequency-range switch; frequency vernier dial; sweep-width control; sweep-rate control; burst-gate control; and lin/log switch. The lower-trace ramp is the sweeping voltage scoped at the GCV output.


### dc offset voltage

A dc voltage can be mixed with the output signal by adjustment of the *dc offset control*. At minimum setting of the variable amplitude control, the offset control can produce any voltage from about +6V to -6V when the output is loaded with a 50Ω load. Higher voltages can be obtained when the output has no external load resistor. With the amplitude control at maximum, the range is between about +4.5V and -4.5V. These readings were obtained when the output *attenuator* switches were adjusted


for 0dB attenuation. When the attenuator switches are pushed, the reduction of output dc voltage is the same as the signal attenuation. In other words, a 10dB attenuation reduces the dc to about one third.

This feature is valuable for biasing a transistor while the generator also supplies the signal. The signal level and waveshape should be checked by a scope. The dc component can be tested by the scope, but a digital multimeter will give much higher accuracy.


Figure 10 shows how the dc and

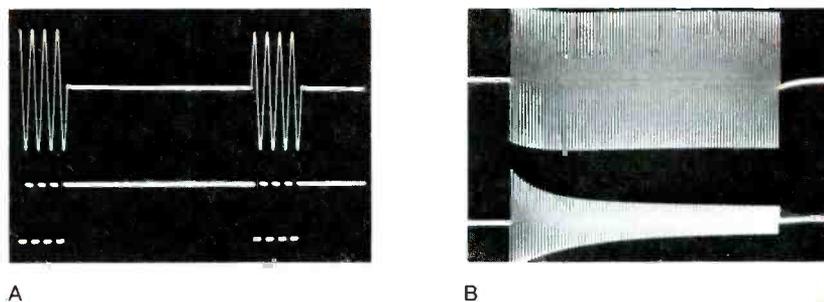

**Figure 8** Two types of gated tone bursts are shown here. (A) A 1000Hz sinewave carrier is gated according to adjustments of the burst-gate and sweep-rate controls (top trace). The TTL output has a pulse for each sinewave cycle (bottom trace). (B) Gating the 1000Hz carrier at a much slower rate (tone is present for only about 84mS) produces a signal that is ideal for showing the action of an audio compressor. Top trace is the signal without compression. Normal compression is shown by the bottom trace.

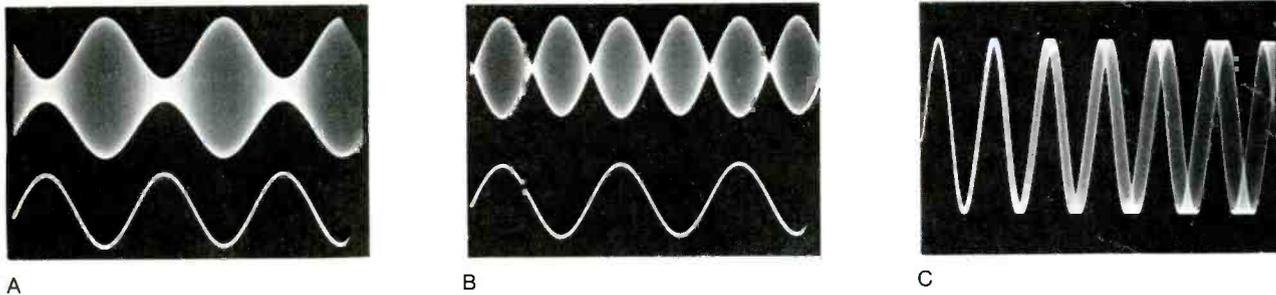

**Figure 9** AM, suppressed-carrier AM, and FM modulation are possible with model 3020. (A) Internal high-frequency sinewaves are amplitude-modulated (AM) by a low-frequency sinewave from another generator. Percentage of modulation is adjustable. (B) By balancing out the carrier before the modulation is applied, the carrier is suppressed and only the positive-peak and negative-peak envelopes of carrier are present in the output signal. (C) Frequency modulation is shown by this waveform. The scope locks to one cycle, and the following cycles are moving sideways (varying frequency).

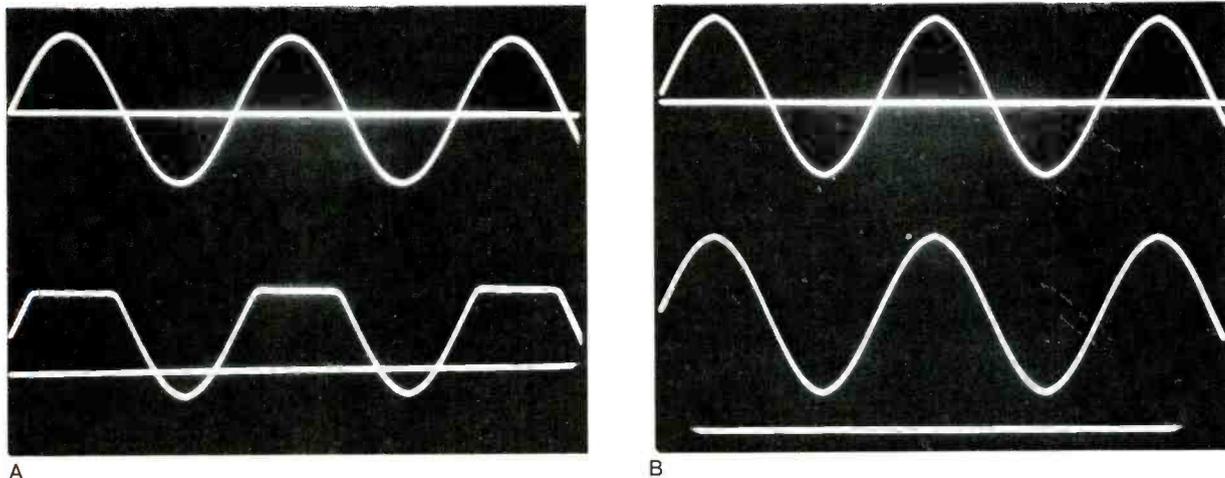

**Figure 10** A steady dc voltage of either polarity can be added to the output signal by rotation of the *dc-offset* control. When this feature is not needed, the control must be adjusted to center of rotation where a voltmeter measures zero voltage at the signal output. There is one possible complication if the variable *amplitude* control is rotated for maximum output level. (A) Top trace shows sinewave output with its zero-voltage line in the exact center. Notice that neither peak is clipped or rounded. When the *dc-offset* control is rotated to produce about +3V at the output, the top of the waveform is clipped (bottom trace). This is a safety feature preventing damage to the generator, but it might give a false waveform and test results if the operator did not notice the clipped waveform. The *dc-offset* control can be adjusted without a meter by scoping the output sine or triangle waveshape and rotating the *dc-offset* to where *neither* peak is clipped when the amplitude control is at maximum (full CW). (B) Clipping does not occur so easily when the level is reduced with the amplitude control. Top trace again shows zero *dc* voltage in the output signal, while the lower trace shows an unclipped sinewave *above* the zero line when the *dc-offset* control is adding about +3V to the reduced signal.

ac components are combined. There is one precaution: When full amplitude is required from the generator (amplitude control fully CW and attenuator switches without attenuation), adjustment of the *dc-offset* control must be checked. If it is producing anything other than 0Vdc, one peak of the signal will be clipped. This is particularly noticeable with sines and triangles.

#### Comments

B&K-Precision model 3020 performed all functions without any problems. Slight corner overshoot was noticed with squarewaves of some repetition rates. The rise and

fall times of squarewaves near the maximum 2MHz limit was somewhat slow. However, it must be noted that the scope is rated at 35MHz, and 35MHz is only about the 17th harmonic of 2MHz—not enough to create good squarewaves.

An excellent feature is the symmetry control that changes squarewaves to pulses and triangles to ramps. Another excellent feature is the audio-sweep mode that gives either log (for better view of low frequencies) or linear sweep. The setup for obtaining audio sweep could be more convenient. The range and fre-

quency adjustments must be made to predetermined points, but then three variable controls must be painstakingly adjusted and readjusted to obtain the desired display.

TTL pulses for some functions and the AM or FM modulation modes are valuable features for specific types of testing.

Model 3020 sweep/function generator from B&K-Precision is an extremely versatile piece of test equipment that would be an asset for any audio or general electronics shop.

**B&K**

# Elmo Manufacturing — entering a race of giants

By Joel A. Samberg

In the United States, there is no particular center of consumer electronics marketing and manufacturing. Although a middle-sized, partially suburban community in New York's Nassau County seems an unlikely place for a strong surge of consumer electronics there is one company that may put New Hyde Park firmly on that map. Elmo Manufacturing Corporation, a 57-year-old photographic equipment company, has come out with its own version of the long-anticipated videodisc player developed by RCA and has recently released it to the market.

Elmo, with an employee roster at the Long Island facility of less than 100 (small compared to most other electronics manufacturers) is entering a videodisc race already heated with the presence of giants such as Zenith, Hitachi, Toshiba, Sanyo and, of course, RCA.

The company has a scheme, however, that may put *its* player ahead of the competition in one particular retail market. Elmo will sell its player almost exclusively through the camera stores and photographic equipment dealers that are already familiar and successful with the Elmo brand name, thereby instantly winning the support of thousands of salespeople, managers and store owners across the country. Also, as one RCA ex-

ecutive points out, photographic salespeople are among the most professional and technically oriented retailers around and can do an extraordinary job of marketing the Elmo player.

Most electronics professionals not in the photographic retail business say, "Elmo who?" Elmo, which is an acronym taken from electricity, light, motion and organization, the basic ingredients of engineering, was founded by Hienobu Sakaki, a Japanese engineer. The company began manufacturing and marketing a slide projector that used a propeller-cooling mechanism designed by Sakaki. A line of still cameras came next, followed by motion picture projectors. After World War II, Sakaki established Elmo as a worldwide distributor of consumer and professional photographic equipment.

Among Elmo's current product lines are \$35,000 theater projectors, 16mm portable projectors and top-of-the-line overhead projectors. "We sell in excess of 15,000 to 20,000 overhead projectors to schools and institutions in the United States alone each year," said Vice President Vincent G. Marotti. An Elmo facility in Woodland Hills, CA, helps keep the supply in pace with the demand.

In 1980, Elmo had its team of

engineers examine a videodisc player to see how they could improve upon it.

"It was mostly done in conjunction with Toshiba," Marotti explained. "A great many of the components were manufactured by Toshiba, and our unit is very similar to theirs in appearance and performance."

RCA developed the Capacitance Electronic Disc format (CED), which Toshiba and Elmo are now using. Elmo executives selected the CED format because they feel it is the one most likely to dominate the videodisc market. One factor in support of that theory is that the CED format has more movie titles available than the laser format videodisc players manufactured by Magnavox and Pioneer.

RCA, which underwent a huge market introduction last spring, has such disc titles as *Urban Cowboy*, *Ordinary People*, *Airplane*, *The Muppet Movie* and several James Bond films. Some reports indicate, however, that it had not been entirely successful, apparently because RCA rushed into its introduction before the company had completed an effective test marketing campaign (though more recent reports indicate a steady gain in popularity).

What makes the Elmo player different from the RCA is the addition of a built-in stereo adapter jack and optional remote control. RCA expects to add stereo capability to its player within the next few years.

"I had several meetings with RCA when we first conceived the idea," says Marotti. "We basically discussed program distribution but they are fully aware that we're in the market with a compatible and competitive system. Their comments were very favorable. I think it just expanded their own disc horizons."

Arnold Valencia, president of RCA Sales Corporation, agreed. "It's an endorsement of the CED system," he said.

Though Valencia is not familiar with Elmo, he welcomes their participation. Both he and Marotti acknowledge that the photographic and camera stores that have ventured into video have been surprisingly successful.

Personnel at two camera stores






IV cartridge, in a high-performance, miniature cartridge that is integrated with an SME carrier arm. The integrated design results in significantly reduced effective mass, virtually eliminates headshell resonances, and provides easy-to-mount convenience.

Circle (31) on Reply Card

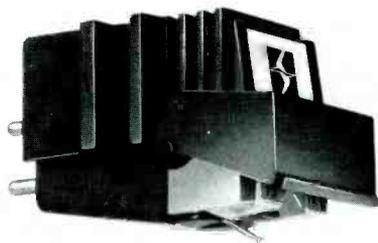**Phono cartridge**

Shure Brothers Inc. has announced a low-mass phono cartridge, designed for SME 3009 Series III and IIIS tone arms.

Called the MV30HE, the unit offers SME owners the performance of Shure's top-of-the-line V15 Type



**Temperature probe**

Accurate electronic thermometry is affordable for anyone owning a digital multimeter with Alpha Magnum's Tempa Tool.

A DMM plugs into the module's standard prod tip jacks for a measurement of 1mV per degree.

The sensor lead plugs into the module as well, permitting extension of the 48-inch, 2-wire sensor lead to 2 miles with no error in reading. This miniature phone plug also doubles as a power switch, preventing accidental power activation during storage, preserving the 300-hour life of the

Tempa Tool's 9V transistor battery.

The unit measures temperatures over a range of -55°C to +150°C and is factory calibrated to ±0.3°C. A 15-turn externally accessible trimmer permits user calibration of the Tempa Tool or correction of DMM error to 0.1° accuracy.

Circle (32) on Reply Card

**B&W TV sets**

The 1982 line of Philco black and white televisions by N.A.P. Consumer Electronics Corp. includes new 5-inch and 9-inch ac-dc models.

The 5-inch portable includes a built-in AM/FM radio, continuous VHF/UHF tuning, a 5-inch round speaker, sunscreen and an automobile power cord. The unit can operate from four power sources: car cord, nine "D" cells, optional battery pack and current.

A 2¾-inch round speaker,

**COMPLETE TEST EQUIPMENT SERVICE.**

**We pick it up.  
We fix it fast.  
We deliver it back  
or  
We service on-site.**

We handle calibration, repair, maintenance, and modification. We've been providing this service for 20 years—at fair rates. Today we service more than 7,500 pieces of equipment annually.

Padded van, no shipping container required...  
Emergency 24-48 hour service... Certificate of calibration (NBS traceable)... Automatic recall notification... Scheduled preventive maintenance and calibration... Mil-Spec compliance...  
Estimates before servicing.

Equipment acting up? Call (201) 757-3730.



Instrumentation Measurements Laboratory  
1501 U.S. Highway 22 C.S. #1, Plainfield, New Jersey 07061

Circle (11) on Reply Card

**Want MORE Information on Advertised Products?**

Just refer to the Bingo # beneath each ad.

Circle the appropriate number on the Reader Service Card in the back of this issue.

**Complete the remaining information and mail!**

sunscreen and 70-position click-stop UHF tuning are featured in the new walnut-grain plastic 9-inch portable, which can operate via the included automobile power cord or an optional battery pack.

Circle (30) on Reply Card

### TV projection system and cabinet

*Edmund Scientific* is offering a complete TV projection lens system and a cabinet to house it. The cabinet is constructed from flakeboard material with laminated walnut wood-grained finish. The unit is 14" x 21".



Designed for use with all 12-inch to 15-inch TV sets, it's the kind of do-it-yourself project that can be completed during a weekend.

In addition to the partially assembled cabinet, the TV projection system includes a f/2.4 glass lens, a 45-inch TV projection screen, lens focusing mount, wall brackets and an instruction manual.

Circle (15) on Reply Card

### Satellite positioner

*Basic Systems* has developed a new control system for positioning TV satellite receiver dishes. The system consists of a telescoping actuator, a totally enclosed gear motor, a limit switch assembly and a control panel that contains all of the indicators and controls for positioning receiver dishes up to 12 feet in diameter.

Designed for use on polar-type antenna mounts, the actuator, gear motor and limit switch are located at the antenna site, and the control panel is wired into where the TV set is located. The control

box has a 3-digit LED display that continuously shows relative antenna position plus a red and a green indicator light to show when the actuator is at its upper and lower limits.

A memory reset push-button and yellow indicator light are also supplied to reset the display in the event of a power failure. Antenna position is controlled by a center-off-type rocker switch on the front panel.

Circle (16) on Reply Card

### Microwave sweep generator

*Wavetek Indiana* has announced a new line of digital display generators and has incorporated a number of innovations into a compact unit.

The model 1084 has three operating modes: CW,  $\Delta F$  and full sweep. Frequency in the CW mode is set by a 10-turn potentiometer and displayed with a resolution of 1MHz on a 3 $\frac{1}{2}$ -digit display. In the  $\Delta F$  mode, center frequency is selected by the 10-turn potentiometer; the sweep width range of 500kHz to 1000MHz is controlled by a 100MHz/step selector and a 100MHz vernier. The model 1084 features 1% display linearity.



In the full sweep mode, the start frequency is 3.5GHz and the stop frequency is 4.5GHz. The 10-turn potentiometer and 3 $\frac{1}{2}$ -digit frequency display operate as a variable marker. The marker produces a bright spot on the display by momentarily delaying the sweep ramp for approximately 2 $\mu$ s. Accuracy is  $\pm$  10MHz. External marker input is standard.

Circle (17) on Reply Card

### Keyless door lock

*Mountain West Alarm* has announced a weatherproof push-

## ESR METER

checks electrolytics  
IN-CIRCUIT and is TV shop  
FIELD-TESTED:

The most fantastic instrument I've ever bought—Billings, Mt. Used it 3 months; it only missed once—Marinette, Wis. (Typical). Squeal & no sync: 3 bad caps in B+ & AGC; Many Thanks—Taos, N.M. Please ship another; very satisfied—Glen Rock, Pa. It's fantastic—St. Joseph, Mo. Please rush; heard good reports—Hicksville, N.Y. One tremendous meter—Alexandria, Minn. Send your Super meter; heard about it—N. Olmstead, Ohio. Love that ESR Meter—Acton, Mass. Used it intensively for 30 days; it's been 100% effective—Pittsburgh, Pa.

Ideal for preventive maintenance: measures electrolyte dryness & shows up intermittent opens.

60-day Satisfaction Guarantee.

Send check or M.O. or call  
(313) 435-8916 for COD


Or write for free brochure to:

*Creative Electronics*

ESR Brochure \$ 99.00  
1417 N. Selfridge postpaid  
Clawson, Mich. 48017 USA & CAN.

Circle (5) on Reply Card

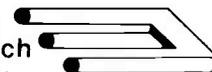It's no puzzle  
to order Oelrich  
Service Forms



For TV-radio and two-way radio service—  
legal forms for Calif., Florida and Utah.  
Now at parts jobbers or write for cat. B64.

**OELRICH PUBLICATIONS**

4040 N. Nashville Ave., Chicago, IL 60634  
Now call toll-free! 800-621-0105

Circle (6) on Reply Card

Your  
ad gets  
quick  
results.  
Advertise  
in  
classifieds.

button door lock. The lock eliminates the need for keys and locksmiths. Easy-to-install kit is practically pickproof and the combination is easily changed.

A weatherproof solid-state keyboard resists vandals and has no moving parts to wear out or jam. System can also be programmed on the keyboard with a secondary combination to allow temporary access to neighbors and friends, similar to loaning key, without revealing master code. A tamper



alarm feature activates an electronic tone and locks out the keyboard for 25 seconds after 16 random numbers are pressed.

Circle (18) on Reply Card

### Video still camera

Sony Corporation has announced the development of a revolutionary video still camera, which uses the full advantages of advanced electronic technology in magnetic recording, CCD and IC semiconductors.

Called the MAVICA system, the new magnetic video still camera uses no photographic film and therefore does not require developing and printing processes, which are essential to conventional chemical photography.

Sony's MAVICA system replaces chemical processes with an electromagnetic system. The MAVICA is no larger than a conventional 35mm single-lens reflex camera. An image produced through the lens is converted into electronic signals by a solid-state imager called CCD (Charge Coupled Device), which was previously

developed by Sony. The signals are recorded on a very small magnetic disk that Sony has developed for the new camera system.

Circle (19) on Reply Card

### Static-conductive soldering iron

The Ungar Division of Eldon Industries Inc., has introduced a



modular soldering iron that is electrically grounded from tip to plug connection to prevent static electricity damage to microcircuits.

Three wattages and temperature ranges are available: Ungar 1270, 27W, 650-750°F; Ungar 1350, 35W, 750-850°F; and Ungar 1450, 45W, 900-1000°F.

All models have thermoplastic "soft-touch grips" and handles are balanced to reduce worker fatigue and resistant to fluxes and acids.

Circle (20) on Reply Card

### VCR accessory rack

Channel Master's counter-top, revolving VCR accessory rack displays up to 150 items, and is free with model 0700 VCR Accessory Display Package. The 32-inch-tall rack features a compact turning radius of 24 inches and is now available from Channel Master distributors.

VCR equipment and accessory



items included in the package are: 75Ω and 300Ω matching transformers, band separators, VCR band separators, 2- and 4-set U/V/FM couplers, 2-way and 4-way line splitters, single channel joiners, baluns and 75Ω cable and connector kits and switches.

Circle (21) on Reply Card

### Display and minicomputer

New electronics from the John Fluke Manufacturing Company Inc. allow people to interact with machinery, information systems, filing systems, instruments, inventory, process control, orders, cash machines and numerical control systems just by touching a display screen. The 1780A Infotouch Display is a special display screen with a touch sensitive overlay. Messages, numbers, graphics, menus, switches and special characters can be displayed through computer programming to guide an operator's response




step by step. Almost any desktop computer, home computer, minicomputer or large computer system can use the 1780A as a man-machine interface.

The 1720A is a minicomputer with many diverse applications from controlling automated manufacturing to monitoring medical instruments.

Circle (22) on Reply Card
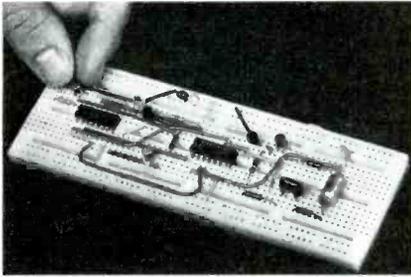
### Erasable circuit building

A P Products Inc. Super-Strips allow you to build a circuit almost as fast as you can dream one up. They combine a power/signal distribution system with a matrix of 128 terminals, each with five tie points. The distribution system has eight different buses, with each individual bus comprised of a line of 25 tie points. All tie points are the solderless plug-in type that have been pioneered by A P Products.



Super-Strips will accommodate up to nine 14-pin DIPs and are compatible with all DIPs and discretes with lead diameters to 0.032 inches. The distribution system features a universal 0.1" x 0.1" matrix and requires no special patch cords. Any solid wire up to no. 20 A.W.G. can be used for interconnections.

Circle (23) on Reply Card

### Electronics soldering course

The *PACE Inc.* Basic Soldering Course in Electronics is now available in 11 languages.

The course is a widely used training program to instruct beginners and upgrade the skills of experienced personnel in performing high reliability soldering.

The films are available in French, German, Italian, Spanish, Mandarin Chinese, New People's Republic Chinese, Norwegian, Swedish, Dutch, Hebrew and Portuguese.

The course is a comprehensive, in-depth training program intend-



ed primarily for classroom use by an instructor. The films in multilanguage forms can be easily integrated into training programs nearly anywhere in the world.

Circle (24) on Reply Card

### Video switching consoles

*Marshall Electronics Inc.* has announced a new series of video

switching control consoles designed for home video systems. All of the units feature high isolation and low loss.

The series includes three RF (VHF/UHF) switching consoles and one direct audio/video switcher.

The MCC-500 is a 5-way high isolation RF switch that can pass signals in any direction. The MCC-500 can provide control of five program sources to a television or video recorder or can send one signal to five selectable loca-



tions. Unique vertical mounting of the switches prevents cable and cabinet movement during program selection.


Circle (25) on Reply Card

### Video selector

*Winegard Company*, manufacturer of TV system equipment, has introduced a second generation video selector, model VS-4002.

The Winegard VS-4002 features simple slide switches that allow the viewer to watch, record, edit and monitor programming without connecting or disconnecting cables.

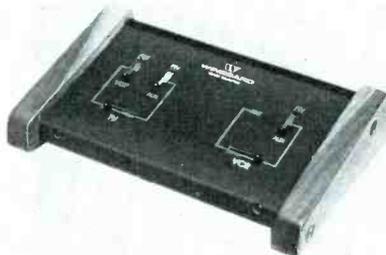Four 75  $\Omega$  inputs will accept any combination of the following: cable television, outdoor antenna, over-the-air pay television (STV, MDS), VCR, video disc, video games,



Now, more than ever  
... Men who KNOW say ...



IS THE ANSWER

HELP NATESA HELP YOU  
BY DOING YOUR PART

Are YOU the operator of an ethical, professional caliber tv-radio-home electronics service business?

Write for details on how you can gain great benefits and participate in the destinies of this great industry.

**NATESA**  
5930 S. Pulaski Road  
Chicago, Illinois 60629

### FREE CATALOG



Burglar/Fire Alarms  
Controls • Wireless Components  
• Ultrasonic • Microwave • Infrared • Sirens • Bells • CCTV  
• Locks • Safes • Fire Systems  
Mountain West Dept. ES-2

4215 N. 16th St. Phoenix, Ariz. 85016 800-528-6169

Circle (7) on Reply Card

**Want  
MORE Information  
on Advertis-  
ed Products?  
Just refer to the  
Bingo #  
beneath each  
ad. Circle the  
appropriate  
number on the  
Reader Service  
Card in the  
back of this  
issue. Complete  
the remaining  
information and  
mail!**

earth station, computer terminals. Dow Jones wire service and more.


Circle (26) on Reply Card

### Outlet strips

Five new industrial models of Sockets Plus multiple outlet strips for assembly line and test stations and similar applications have been

introduced by *Perma Power Electronics Inc.*

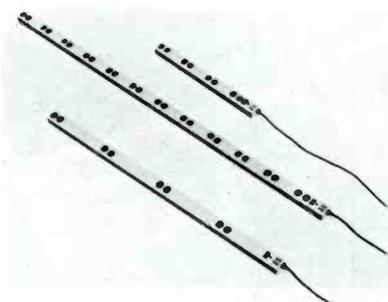The new industrial strips are 2-, 4-, and 6-foot long, and provide up to 24 outlets for plugging in tools, test instruments and appliances. Each is protected by a circuit breaker and is available with either a 6- or 12-foot, double-insulated, 14-gauge power cord.



All units are UL listed, and all have a master switch and indicator light.

Circle (27) on Reply Card

### Waveform analyzer

*Sencore* has introduced the model SC61 waveform analyzer. The SC61 fully integrates a digital readout with the waveform analyzing capability of a high performance oscilloscope.

Unlike "piggyback" scope/DVM combination units, the SC61 makes all measurements through one probe, including digital readout of dc volts, peak-to-peak volts (patent applied for), frequency (patent applied for) and time. The single probe not only



eliminates the loading experienced when you hook up more than one probe to a test point, but speeds every measurement as it eliminates the need to connect and disconnect other instruments.

Circle (28) on Reply Card

### Service kit

*Vaco Products Company's* no. 4900-63 solderless terminal service kit contains 20 of the most popular insulated terminal styles with more than 400 terminals in all, plus the no. 1963 wiring and crimping tool, which crimps ter-

**You could be making extra cash...**

**...and have the personal satisfaction and prestige of having your work published in a national magazine.**

Electronic Servicing & Technology, the new magazine for the electronics of today and the future is in need of technical servicing articles on audio and video consumer electronic products.

As a professional electronics technician, you could be making extra cash by submitting articles for publication to ES&T. You may think, "I know my stuff, but I'm no writer."

**No problem.**

Our expert staff will polish your original material and graphics into a finished product with your byline.

This is your opportunity to earn extra money, and also benefit your fellow technicians with your own expertise.

For more details, write or call:

**DO IT NOW!**

Bill Rhodes  
Editorial Director  
Electronic Servicing & Technology  
P.O. Box 12901  
Overland Park, KS 66212  
(913) 888-4664

minals, cut and strips wire, and slices bolts.

The various terminal styles are packed separately in individual bags, then placed in their own compartments keeping the assortment neatly organized. And an identification chart on the side cover illustrates and describes each terminal style, making it easy for the user to identify and select the proper terminal needed for the job.

Circle (29) on Reply Card

### Insulation resistance tester

Universal Enterprise's IRT1000 is a versatile, three-range ( $2M\Omega$  ranges: 0-100M $\Omega$  and 0-1000M $\Omega$ ; 1 $\Omega$  range: 0-100 $\Omega$ , 4 $\Omega$  mid scale) insulation resistance



tester for shop and field use. The IRT1000 can be used for testing electrical machinery, hermetic compressors, transformers, switch blocks, electronic components and cables.

Features of the IRT1000 include battery operation for complete portability, solid-state circuitry, automatic zero adjust, internal electronic voltage regulator (no-drift reading), color-coded meter face, battery check feature, automatic circuit discharge, and fuse protection on all ranges. The IRT1000 comes with tilt-stand carrying case, batteries, data cards, test leads, instructions and a one-year warranty.

Circle (39) on Reply Card

### Desoldering pump

A desoldering pump that can be

operated with one hand and without external power has been introduced by the *Ungar Division of Eldon Industries.*



A spring-loaded piston creates a vacuum that instantly removes molten solder. Double O-ring piston seals achieve maximum vacuum in a piston stroke of less than 2 inches. The piston is set with the thumb and released by push-button for maximum spring force. The worker's other hand is left free to hold the soldering iron that melts the solder.

The Ungar 7874 vacuum desoldering pump is made of anodized aluminum and includes a self-cleaning, no-clog Teflon tip that is replaceable (part no. 7875).

Circle (40) on Reply Card

### Protective cover

PPS of Santa Fe Springs, CA, has announced the introduction of their G-line of protective vinyl covers for home electronic games.

The G-line protective covers are light, easy to store and protect the unit from scratching and fading while enhancing the beauty of the unit.

All G-line models feature a unique cable cut-out that makes them compatible with the Atari, Mattel, Magnavox and Sears electronic games.

Circle (42) on Reply Card

**ES&T**  
magazine

# SAVE TIME

For fast, accurate service, please remove the Peel-Off Label (which is used to address your magazine) and affix it to the Reader Service Card, the Address Change Card, or to any correspondence you send us regarding your subscription.

NATIONAL ELECTRONIC  
**NESDA**  
SERVICE DEALERS ASSOCIATION, INC.

Your **KEY**  
to **SUCCESS**

NESDA OFFERS

- A National Certification Program
- National Recognition
- Government Representation
- Business Contacts
- Purchase Discounts
- Low Bankcard Rates
- Educational Materials
- Industry and Business Information

PLUS

- A Subscription to "ServiceShop" Magazine and Yearbook

Please send more information about:

NESDA, 2708 West Berry St.  
Ft. Worth, TX 76129

name \_\_\_\_\_

address \_\_\_\_\_

city \_\_\_\_\_ state \_\_\_\_\_ zip \_\_\_\_\_

business \_\_\_\_\_

## ATTENTION TECHNICIANS

- ★ JOB OPENINGS
- ★ MONTHLY TECHNICAL TRAINING PROGRAM
- ★ BUSINESS MANAGEMENT TRAINING
- ★ LOW COST INSURANCE
- ★ CERTIFICATION
- ★ TECHNICAL SEMINARS

All of this in a nonprofit international association for technicians

FIND OUT MORE:



R.R. 3 Box 564  
Greencastle, IN 46135

## ES&T

### classified

### ads

### are well-read.

### Use them at a

### low-cost

### insertion.




A 12-page, 4-color brochure explaining the services offered to dealers, distributors, manufacturers and the consumer by the **Satellite Services Bureau** is offered free by the organization. The text explains the purchasing consortium concept where dealers may purchase products at attractive discounts as well as a list of six other services including lead generation, promotional assistance, information updates, management training programs, business counsel and a code of professional practice. Also included is the bureau staff and a membership application form.

Circle (45) on Reply Card

are 10 new products with unique capabilities. A vectorscope with CRT-generated vector targets, an X-Y display module that can be precisely customized to OEM user needs and requirements, and a CRT display designed for use in microwave swept frequency measurements are included.

Circle (46) on Reply Card

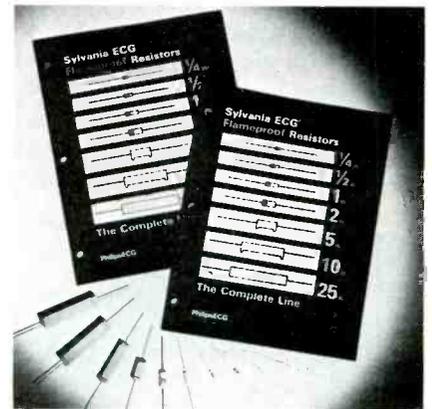
Publication of a detailed, 16-page catalog on Sylvania brand ECG flameproof resistors has been



**Leader Instruments Corporation** has announced the availability of their 1982 catalog. The 48-page, comprehensive catalog includes detailed descriptions, specifications, photographs and pertinent charts and illustrations of more than 70 products, including oscilloscopes, frequency counters, digital multimeters, function generators and video and audio test instruments.

Announced in the new catalog

**LEADER**  
Instruments Corporation

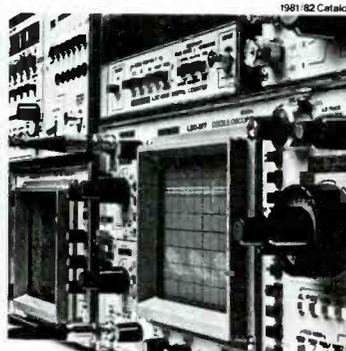

announced by the Distributor & Special Markets Division of **Philips ECG Inc.**

Entitled *The Complete Line*, this catalog lists the characteristics of more than 1000 individual ECG types, ranging in power handling capability from  $\frac{1}{4}W$  to 25W, with resistance values from  $0.1\Omega$  to  $100M\Omega$ .

Sylvania brand ECG flameproof resistors can be used to replace carbon composition, carbon film, metal film, cermet film, wire-wound and fuse resistors.


Circle (47) on Reply Card

**TRW Power Semiconductors** has published a comprehensive cross-reference list of industry and TRW part numbers.

The new 8-page, 2-color publication contains more than 1,900 entries, showing EIA numbers in conventional order and the corresponding TRW number.

Circle (56) on Reply Card

**ES&T**

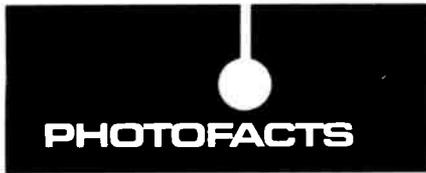

**BROADMOOR**  
3619, 8019 .....2040-1

**BOHSEI**  
Chassis M9C3-5B1, B3 .....2042-1

**JCPenney**  
685-1020F, -00 (855-2879) .....2040-2  
685-1037E, -00, .....  
6875-1037F, -10 .....2041-1  
685-1034F, -10 .....2042-2  
685-2008F, -00, .....  
685-2053F, -00 .....2043-1

**MGA**  
BB-1242/270 .....2044-1

**PANASONIC**  
TR-1214T/15T .....2041-2  
TR-5040P/41P .....2042-3  
Chassis NMX-K7A .....2043-2  
CT-9000/010/020/030 .....2046-1

**QUASAR**  
Chassis ALDTS/LDTS/YALDTS-989 .....2045-1

**RCA**  
Chassis KCS205CA .....2046-2

**SHARP**  
FF19661, 19F86 .....2046-3  
FF13601, 13F22 .....2045-2

**SONY**  
Chassis SCC-352A-A .....2040-3  
Chassis SCC-350A-A .....2041-3  
Chassis SCC-341A-A .....2044-2

**WARDS**  
GEN-11950A .....2044-3  
GEN11120A .....2045-3



## GET COMPLETE DETAILS

about the products  
advertised or described  
in this issue.

Use Free Inquiry Card.

# CUSTOMER ENGINEERS

## Discover The Career Challenge And Prestige Which Only Cray Can Offer!

Working with one of the world's fastest supercomputers offers challenge and prestige unmatched anywhere. It's what you can experience as a customer engineer with Cray Research, developer of the Cray-1, an advanced super-computer, capable of producing up to 240 million floating point operations per second.

Customer engineering positions now exist with Cray in the Great Lakes, Southeastern and Southwestern sections of the U.S. offering individuals unique opportunities for hands-on work with state-of-the-art, high-technology computers.


Servicing the Cray computer at on-site customer locations requires individuals with 1-3 years on-site experience in dealing with large-scale or digital computers. An associate technical degree is helpful, and a thorough, in-house training program will be provided to qualified candidates.

If you feel it's time your experience earned you more than a job, consider a career backed with the challenge and prestige which only Cray can offer. To find out more, including information on our excellent company benefits and competitive salaries, please send your resume in confidence to:

**CRAY**  
RESEARCH, INC.

John F. Borchers  
Department 201  
**CRAY RESEARCH INC.**  
1440 Northland Drive  
St. Paul, MN 55120

Equal Opportunity Employer M/F/H/V

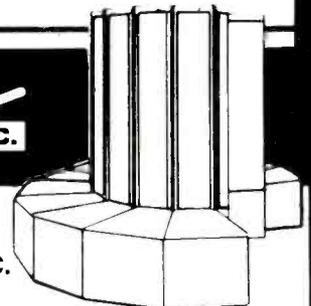

Circle (10) on Reply Card

# THE MARKETPLACE

Advertising rates in the Classified Section are 50 cents per word, each insertion, and must be accompanied by cash to insure publication.

Each initial or abbreviation counts a full word.

Minimum classified charge \$10.00.

For ads on which replies are sent to us for forwarding (blind ads), there is an additional charge of \$3.00 per insertion to cover department number, processing of replies, and mailing costs.

Classified columns are not open to advertising of any products regularly produced by manufacturers unless used and no longer owned by the manufacturer or distributor.

## For Sale

**FREE**

**THE GREAT ELECTRONIC THINGS & IDEAS BOOK!**

HUNDREDS OF UNUSUAL PARTS, GADGETS & IDEA ITEMS, UNAVAILABLE IN STORES OR CATALOGS ANYWHERE! Bargain prices on everything! New items in every issue! Rush postcard for your copy!

ELECTRONICS  
Dept. 311  
Plattsburgh, N.Y. 12901

Circle (8) on Reply Card

**AUTOMOBILE RADIO** and tape replacement parts: Delco, Chrysler, Philco-Ford, Motorola, Panasonic and many others. Large inventory. Laran Electronics, Inc., 3768 Boston Road, Bronx, NY 10469. (212) 881-9600, out of New York State (808) 223-8314. 5-79-tf

**TV & RADIO TUBES**, 36 cents EA!! Free color catalog. Cornell, 4221 University, San Diego, California 92104. 8-76-tf

**ELECTRONIC SURPLUS: CLOSEOUTS, LIQUIDATIONS!** Parts, equipment stereo, industrial, educational. Amazing values! Fascinating items unavailable in stores or catalogs anywhere. Unusual FREE catalog ETCO-011, Box 762, Plattsburgh, N.Y. 12901. 6-78-tf

**SCRAMBLED TELEVISION**, encoding/decoding. New book. Theory/circuits. \$9.95 plus \$1 shipping. Workshop, Box 393ES, Dept. E, Bethpage, N.Y. 11714. 7-80-tf

**PRINTED CIRCUIT** boards from your sketch or artwork. Affordable prices. Also fun kit projects. Free details. DANOCINTHS INC. Dept. ES, Box 261, Westland, MI 48185. 5-81-tfn

**TUBES FOR TV AND RADIO** - 35¢ ea. Washington TV Service, 1330 E. Florence Ave., Los Angeles, CA 90001. 10-81-5t

**PICTURE TUBE REBUILDING EQUIPMENT** capable of producing four high quality tubes per day (WILL TRAIN TO OPERATE). Call or Write Atoll Television, 6425 Irving Park, Chicago, Illinois 60634, ph. 312-545-6667. 10-81-6t

**RADIO-TV TUBES INCLUDING ANTIQUES!** Many tubes thought to be obsolete are still being manufactured. Write for free discount price sheet of over 1,800 types. Electronic Parts Co., 1015 S. Escondido Blvd., Escondido, CAL 92025, (714) 741-2300. 1-82-6t

## FOR SALE (Cont.)

**FOR SALE: SAMS PHOTOFACTS FOLDERS** 100 to 910 plus, \$1.00 each, plus shipping. Bordan's, 1781 Aurora Rd., Melbourne, Florida (305) 259-2146. 2-82-1t

**FOR SALE - MINISCOPE NLS M5215** with Probes. Excellent Condition \$250.00. Al Rose, 650 Daphne St., Broomfield, CO 80020. 2-82-1t

**FOR SALE: SENCORE VA48**, nearly new, best offer over \$600. Frank Knight, RFD 1, Box 675, New Gloucester, Maine 04260, (207) 926-3323. 2-82-1t

## Business Opportunity

**TV TECHNICIAN!** Increase your income up to \$60,000 yearly. Rent-lease-sell TVs new-used, even from comfort of your home. Basic Preliminaries \$4.00. Perrys TV Systems, 1467 Hwy. 90 West, Milton, FL 32570, 904-994-0068 12-81-tf

**COMPUTERIZE YOUR ENTIRE TV OPERATION.** GL-AP-AR-INV. Tubes - Parts - Customer - Vendor & TV rental files-programs. Start small & add to later. For Apple TRS80-NEC-Heath-Zenith. Free details. Perrys Computer Systems, 1467 Hwy 90 West, Milton, FL 32570. 904-994-0068. 11-81-tf

**FLORIDA'S WEST COAST:** Small T.V. Service Business attached to home; plus separate rental house. Have CERTIFIED APPRAISAL. Ph. 1-813-541-2039 or write: Owner, 7744 - 46 Ave. North, St. Petersburg, Fla. 33709. 1-82-tfn

**SOUTH FLORIDA TV SERVICE** business for sale. Established same location over 20 years. Buy inventory and phone number and move right in. P.O. Box 159, Boynton Beach, Fl. 33435. (305) 734-6121. 2-82-2t

## Help Wanted

**TV and 2-way Technicians** wanted. \$15K to \$22K per year. Benefits include employee stock purchase plan, in the largest Retail Service Center in Northwest Kansas. Friendly community, good schools, short drive to the Rockies. Equal Opportunity Employer. Miller's Electronics Inc., Goodland, KS 67735. 913-899-2386. 10-81-tfn

**HIGHEST EARNINGS AVAILABLE** to top-notch TV technicians. Must be totally honest, non-smoker, non-drinker. Low crime area. Excellent for families. Superior camping, hunting, boating, fishing and skiing area. Send resume and recent snapshot to American Television Service, 1032 South State St., Orem, UT 84057 (801-226-1776). 2-82-1t

Support the  
**March of Dimes**  
BIRTH DEFECTS FOUNDATION



THIS SPACE CONTRIBUTED BY THE PUBLISHER

# ADVERTISERS' INDEX

Reader Service Number	Page Number
9 B&K Precision .....	13
10 Cray Research .....	67
5 Creative Electronics .....	61
ETA .....	66
8 ETCO .....	68
2 Keithley Instruments Div. ....	1
7 Mountain West Alarm Supply .....	63
1 NAP/Philips ECG .....	IFC
NATESA .....	63
NESDA .....	65
6 Oelrich Publications .....	61
4 PTS Corp. ....	11
Sencore, Inc. ....	BC
3 A. W. Sperry Instruments Inc. ....	7
Tektronix, Inc. ....	5

# ELECTRONIC

*Servicing & Technology*

### Advertising Sales offices

#### NATIONAL SALES MANAGER

*Greg Garrison*  
P.O. Box 12901  
Overland Park, KS 66212  
Phone: (913) 888-4664

#### LONDON, ENGLAND

*John Ashcraft & Co.,  
John Ashcraft*  
12 Bear Street, Leicester Square  
London WC2H 7AS, England  
Phone: 930-0525 Telex: 895-2387

#### AMSTERDAM, Holland

*John Ashcraft & Co.  
John J. Lucassen*  
Akerdijk 150A  
1171 PV-Badhoevedorp, Holland  
Phone: 0-2968-6226 Telex: 18406 HARKE NL

#### TOKYO, JAPAN

*International Media  
Representatives, Ltd.*  
*Sumio Oka*  
2-29, Toranomon 1-chome  
Minato-ku, Tokyo 105, Japan  
Phone: 502-0656

#### NORWOOD, AUSTRALIA

*Williamson & Associates Pty. Ltd.*  
P.O. Box 419  
Norwood S.A. 5067, Australia  
Phone: 42-7074

#### TAIPEI, TAIWAN. R.O.C.

*Antony Liu*  
*Long Life Advertisement Agency Co.*  
P.O. Box 17-134  
Taipei, Taiwan. R.O.C.  
Telephone: (02) 561-6629  
Cable: Photop Taipei



For the man that would rather fix it himself—  
**Technical Publications has  
 service manuals designed for you!**

SES-13 Small (Air Cooled) Engines Service Manual. \$9.95 (336 pages). You can service your own engines on lawnmowers, tractor sprayers and other power equipment. Special section on fundamentals, troubleshooting, preventive maintenance. Step-by-step instructions.

WLMS-1 Walking Lawnmower Service Manual \$7.95 (128 pages). The **complete** guide to the care and repair of your walk-behind, push-type lawnmower. Exploded views and diagrams.

CSS-6 Chain Saw Service Manual. \$8.95 (over 300 pages). Here's everything you need to know to tear down, repair, reassemble and adjust most popular chain saws. A truly **complete** chain saw manual.

GSM-1 Small AC Generator Service Manual \$7.95. A brand new manual that contains maintenance, service and troubleshooting procedures, as well as wiring schematics for most generator models. Covers electrical powerplants under 8kW that generate alternating current and are driven by air cooled engines.

OS1-8 Outboard Motor Service Manual Volume 1 \$8.95 (236 pages). Covers motors below 30 hp.

OS2-8 Outboard Motor Service Manual Volume 2 \$8.95 (232 pages). Covers motors with 30 hp and above. Both Volumes 1 and 2 provide detailed fundamentals on periodic servicing.

**Put these books to work on your own equipment... (Or service outside equipment for profit!)**

- Small (Air Cooled) Engines Service Manual
- Walking Lawnmower Service Manual
- Chain Saw Service Manual
- Small AC Generator Service Manual
- Outboard Motor Service Manual (Vol. 1)
- Outboard Motor Service Manual (Vol. 2)

Remittance must accompany orders of less than \$25.00. **Postage paid when payment accompanies order. Allow four weeks for delivery.**

*How to send money: The best way to send money is your own personal check, post office money order, express money order or by bank draft or check. DO NOT SEND CURRENCY OR STAMPS.*

- Check Money Order Enclosed
- Ship C.O.D. (No C.O.D.s outside of U.S.)

Missouri and Kansas Residents add 4% sales tax.  
 Tennessee Residents add 6% sales tax.

Write for a free catalog covering our entire line of service manuals and wheel-type tractor service manuals.

VISA     MASTERCARGE  
 Credit Card Number \_\_\_\_\_  
 Expiration Date \_\_\_\_\_

Please Print:

Name \_\_\_\_\_

Street \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_


Signature \_\_\_\_\_



Division  
 Intertec Publishing Corp.  
 P.O. Box 12901, Dept. ES  
 Overland Park, KS 66212  
 (913) 888-4664

# CUT YOUR TV-VCR SERVICE TIME IN HALF WITH SENCORE'S VA48 VIDEO ANALYZER

*double*  
**PATENTED**  
\$1,395

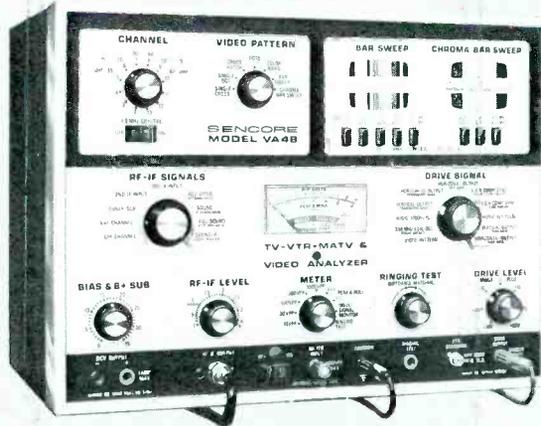

Used by 22,000 techs  
The patented Bar Sweep patterns now appear on all Sams TV and VCR Photofact schematics

**Cut your service time in half**  
You can cut your service time in half. It's a fact. We surveyed 1,500 VA48 owners. The results showed that the average tech cut his service time by 54% using the VA48 and the signal substitution method of troubleshooting.

**What is signal substitution?**  
In a nutshell, signal substitution lets you inject known good signals from the VA48 into any stage of the TV or VCR. (Normally you start somewhere in the middle,

like the detector of a TV. That's why we call this "divide and conquer".) If you get a good picture on the screen, you know everything is working from that point forward. You then back up stage by stage, until the problem develops on the screen (or speaker). Once the problem reappears, you know you are injecting into the defective stage.

It's that simple and only the VA48 provides all the signals necessary to inject from antenna to CRT so you can

cut your service time in half (or double your output for the same time on the job.) This increased productivity is why the VA48 has become the industry servicing standard for TVs and VCRs.

**The VA48 is the industry standard**  
Over 22,000 techs nationwide now use the VA48. The patented Bar Sweep pattern even appears on Sams Photofact schematics. Isn't it time you cut your service time in half?

Here's our offer . . .

- YES**, I'd like to cut my service time in half. Please mail me complete info, and put me on your mail list.
- YES**, I'd like more information. Please have a phone sales engineer call me.
- YES**, I'm ready to order. Contact me immediately.

Name \_\_\_\_\_  
Company \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_  
Zip \_\_\_\_\_ Phone ( ) \_\_\_\_\_

Best time to call:  AM  PM  Evening

Mail to:

## SENCORE

3200 Sencore Drive, Sioux Falls, SD 57107 (605) 339-0100  
TWX: 910-660-0300

**30-DAY MONEY-BACK GUARANTEE**  
Use the VA48 for 30 days. If you find that at the end of 30 days you have not cut your service time in half, you can return your VA48 to Sencore for a full refund.



For Information Circle (12) on Reply Card  
For Demonstration Circle (13) on Reply Card