

# ELECTRONIC<sup>TM</sup>


*Servicing & Technology*

SEPTEMBER 1983/\$2.25

What's behind the computer keyboard?


Servicing the RCA CTC 108 unitized chassis

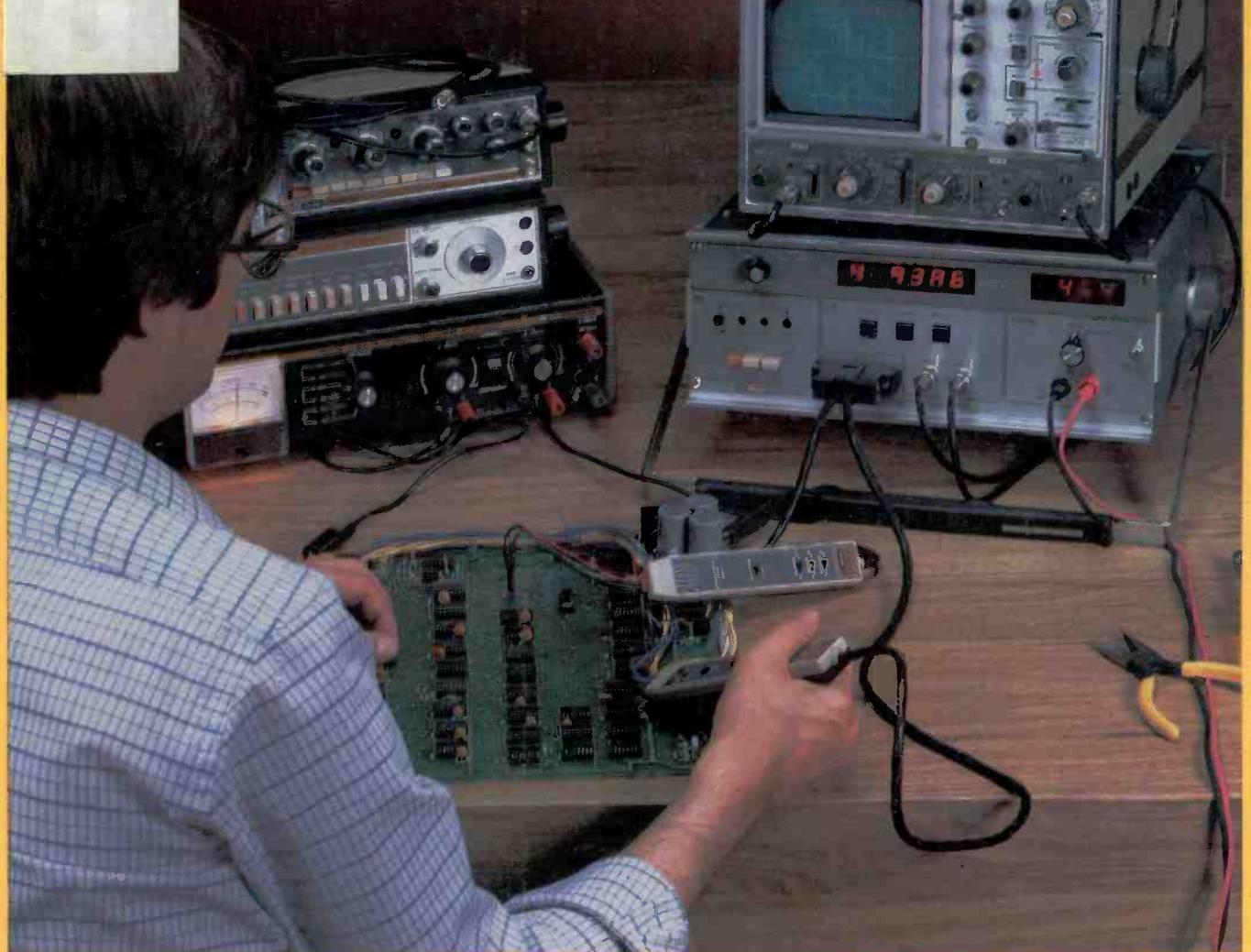**Logic testers  
for digital  
measurements**



**PTS CORPORATION**  
No. 10 in a series  
General Electric EP93X168


# Module Update

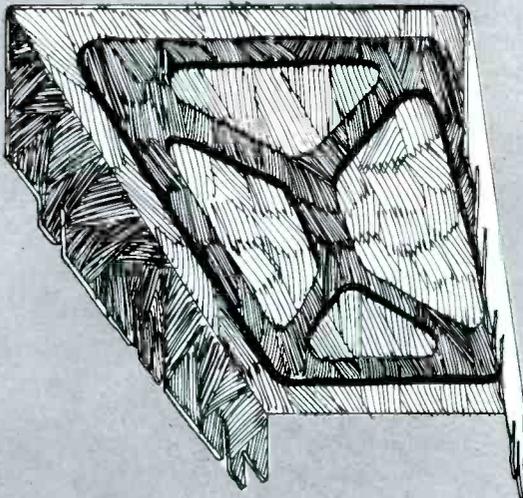

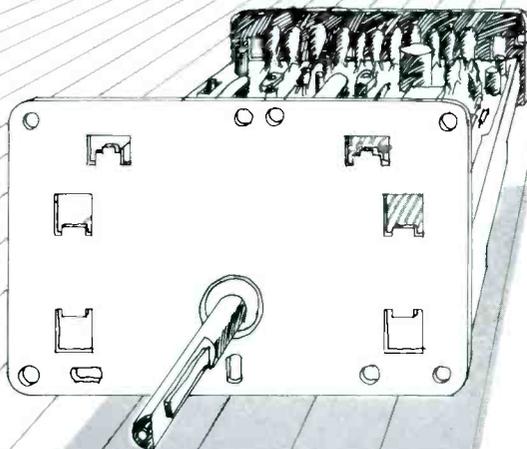***Intermittent voltage drop was traced to a griplet in this tuner control and by-passed with a PTS automatic update.***

The griplet was unreliable. It was designed to connect foil on both sides of the module board. And when the griplet failed, voltage dropped out in the 7.5 volt supply. Video was lost.

**PTS** computerized repair logs pointed a finger at this excessive failure. Now PTS automatically updates every EP93X168 with a jumper wire for a solid connection. Automatic updates are only one reason thousands of service technicians specify quality PTS rebuilt tuners and modules. You can also depend on complete overhaul, stringent testing in live chassis, fast service and nationwide availability. So in addition to complete repair, you actually get a better module with PTS automatic updates.




You'll find PTS quality rebuilt modules with automatic updates at over 1,500 locations nationwide. For the name of the location nearest you and your free copy of the PTS Price and Technical Information Guide, use the reader response card or write: PTS Corporation, P.O. Box 272, Bloomington, IN 47402.



**PTS CORPORATION**

Circle (1) on Reply Card

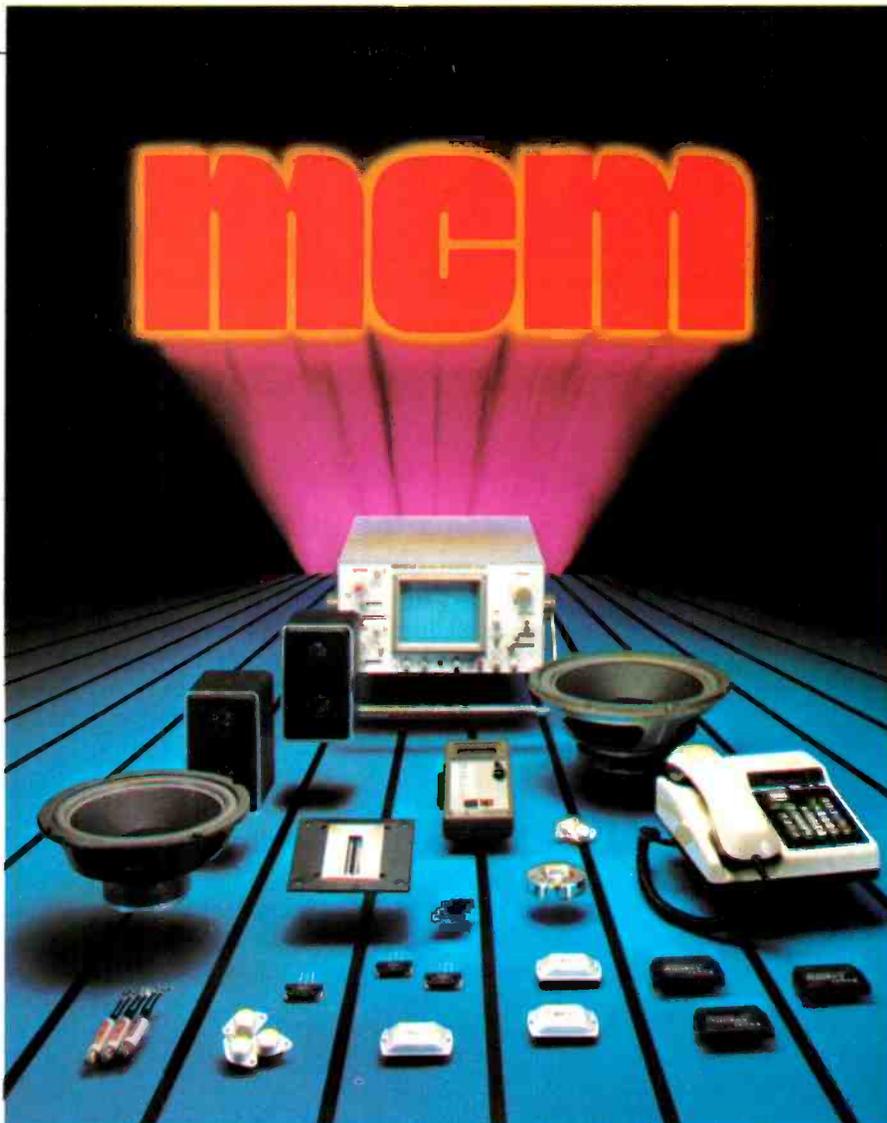

## THE ONLY ELECTRONIC PARTS COMPANY YOU'LL EVER NEED.

You can hunt everywhere for hard-to-find parts and the most up-to-date radio, tv and computer components. Or you can call MCM.

MCM's wide selection of electronic replacement parts and original semiconductors are all high quality name brands such as Toshiba, NEC, Sanyo, Hitachi, Sony and Matsushita. **And they're in stock!**

MCM offers more than just the right parts. When we take your order, we make sure it's carefully packaged and shipped direct within 24 hours. We not only guarantee our parts, but our prompt, personal service as well.

Good service and quality electronic parts doesn't mean we're expensive. Check around. You'll find you can count on incredible savings with MCM.

Don't settle for second best . . . demand MCM electronic parts!

**CALL TODAY** for Your **FREE** copy of our **NEW** 96-page Summer Catalog.

**CALL TOLL FREE** 1-800-543-4330  
(In Ohio 1-800-762-4315.)

  
**MCM**  
**ELECTRONICS**

RIGHT PARTS. RIGHT PRICE,  
SHIPPED RIGHT AWAY.

858 E. CONGRESS PARK DR. CENTERVILLE, OHIO 45459

Circle (4) on Reply Card

September 1983 *Electronic Servicing & Technology* 1

The how-to magazine of electronics...

# ELECTRONIC

Servicing & Technology

September 1983

Volume 3, No. 9



A few of the instruments that can be used for checking out digital circuitry are a wide-band oscilloscope and a logic system analyzer, which includes a signature analyzer, a logic analyzer and a DVOM. The article on page 16 explains one way digital circuitry is used in electronics. (Photo courtesy of B&K Precision.)

## 6 Servicing the RCA CTC108 unitized chassis

By Stan Vittetoe, CET

Servicing unitized chassis, as opposed to modular chassis, requires a high degree of skill. Fortunately, there are many similarities between manufacturers, so these tips on the RCA CTC108 apply to many different chassis.

## 16 What's behind the computer keyboard?

By Joe Carr

The keyboard is the computer operator's means of "talking" to the computer, so understanding the workings of the keyboard is an important step in troubleshooting microcomputers.

## 54 Test your electronic knowledge

By Sam Wilson, ISCET test director

See how you would do on the Certified Electronic Technician test. This month's questions cover resistors.



Page 16

# Departments

4 Editorial

24 Readers' Exchange

29 Profax

42 Photofact


50 Troubleshooting Tips

53 Books

56 Literature

57 Sycmure

58 Products

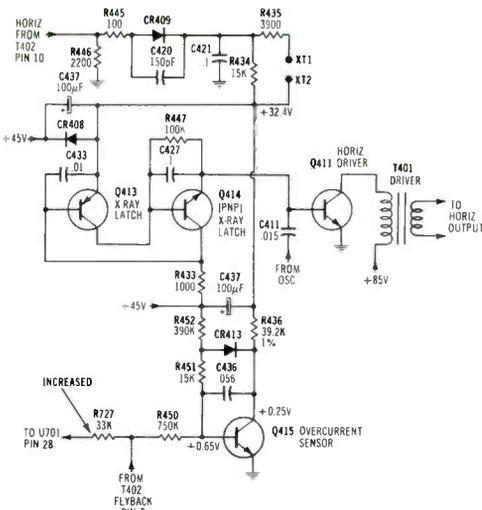

Page 6

## Next month...

Advances in flat-plan LCD technology have enabled BBC-Metrawatt/Goerz to introduce a new digital scope that measures only 10" x 7" x 3.5" when folded and weighs only 4.3 pounds. The October Technology department describes this instrument, which combines the capabilities of a digital scope, multimeter and transient recorder.



# Hey good buddy

In 1975 the FCC made a few changes relaxing the rules governing CB radio operations. Within a year, the FCC was receiving more than 500,000 applications per month for CB licenses.

During this period, everywhere you looked CB antennas sprouted from cars, and drivers were seen speeding down the road with one hand on the wheel and the other holding a microphone to their mouths. The airwaves crackled with CB jargon. Anyone listening ("on the side") to Channel 19 might hear conversations such as, "Hey good buddy, better back off the hammer. There's a smokey with an X-ray machine up ahead." If you knew the jargon, you knew that the speaker was telling another driver to slow down because of a policeman ahead with a radar unit.

Frequently it was possible to travel in unfamiliar territory without a map. CBers who knew the area would help guide a driver to his destination. Someone whose car broke down could call for help via his CB radio, and people had a great time just chatting with each other via the CB.

An entire subculture grew up around the CB. CBers from Boston to Los Angeles began talking in the southern drawl characteristic of CB speech. Terms such as "twenty" (location), "smokey" (policeman), and "convoy" (group of travelers driving together) entered the language. Everyone had a "handle" (code name for a CBer). Even the wife of the president was "First Momma."

Then several country/western style songs came out with CB as their subject. The whole country, it seemed, was communicating via CB and talking about it.

Then it stopped. Abruptly. Presumably, truckers

and a handful of other people who spend a lot of time on the road still use their CBs to communicate. But it's a disused item for the most part, these days.

CB radios are now being sold mostly as emergency units. You buy it and put it in the trunk next to the spare tire to use should your car break down.

The CB craze lasted just a few years, then died. What happened? I haven't seen any studies or discussion on the subject, but my guess is that the craze got started when people found that it was an inexpensive, simple way to communicate over distances (something that seems to have fascinated humanity since the days of signal fires, smoke signals and "talking" drums) and died when they found that they really had nothing to say to each other.

With electronic devices of all kinds being cranked out and tried out, it seems likely that the CB experience will be repeated. Will video games last or are they just a fad? How about personal computers? Where will compact digital audiodiscs, videodiscs, videotapes and all the other new electronic equipment be in 10 years?

I don't know the answers, and I don't know anyone who does. But it's a subject that bears careful consideration by anyone who purchases, sells or services electronic equipment.

10-7 Good Buddy. We gone!

*Nils Conrad Persson*

## **ELECTRONIC** Servicing & Technology

Editorial, advertising and circulation correspondence should be addressed to: P.O. Box 12901, Overland Park, KS 66212-9981 (a suburb of Kansas City, MO); (913) 888-4664.

### EDITORIAL

Bill Rhodes, *Editorial Director*  
Nils Conrad Persson, *Editor*  
Carl Babcoke, *Consumer Servicing Consultant*  
Rhonda Wickham, *Managing Editor*  
Tina Thorpe, *Associate Editor*

### ART

Kevin Callahan, *Art Director*  
Kim Nettie, *Graphic Designer*

### CIRCULATION

John C. Arnst, *Director*  
Evelyn Rogers, *Manager*  
Dee Manies, *Reader Correspondent*

### ADMINISTRATION

R. J. Hancock, *President*  
Cameron Bishop, *Publisher*  
Eric Jacobson, *Associate Publisher*

### ADVERTISING

Greg Garrison, *National Sales Manager*  
Liz Turner, *Production Manager*  
Robyn Kahn, *Marketing Coordinator*



Member, Audit Bureau  
of Circulation



Member, American  
Business Press

ELECTRONIC SERVICING & TECHNOLOGY (USPS 462-050) (with which is combined Electronic Technician/Dealer) is published monthly by Intertec Publishing Corp., 9221 Quivira Road, P.O. Box 12901, Overland Park, KS 66212-9981. Second Class Postage paid at Shawnee Mission, KS 66201. Send Form 3579 to P.O. Box 12952, Overland Park, KS 66212-9981.

ELECTRONIC SERVICING & TECHNOLOGY is the "how-to" magazine of electronics. It is edited for electronic professionals and enthusiasts who are interested in buying, building, installing and repairing home-entertainment electronic equipment (audio, video, microcomputers, electronic games, etc.).

**SUBSCRIPTION PRICES:** one year \$15, two years \$26, three years \$34 in the USA and its possessions. Foreign countries: one year \$20, two years \$30, three years \$40. Single copy price \$2.25; back copies \$3.00. Adjustment necessitated by subscription termination to single copy rate. Allow 6 to 8 weeks delivery for change of address. Allow 6 to 8 weeks for new subscriptions.

**PHOTOCOPY RIGHTS:** Permission to photocopy for internal or personal use is granted by Intertec Publishing Corp. for libraries and others registered with Copyright Clearance Center (CCC), provided the base fee of \$2 per copy of article is paid directly to CCC, 21 Congress St., Salem, MA 01970. Special requests should be addressed to Cameron Bishop, publisher. ISSN 0278-9922



INTERTEC PUBLISHING CORP.

©1983 All rights reserved.


# MCM ELECTRONICS

THE ONLY ELECTRONIC PARTS COMPANY YOU'LL EVER NEED\*

QUALITY PARTS AT EVERYDAY LOW PRICES
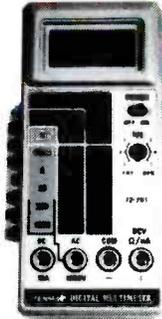
### 3 1/2 DIGIT L.C.D. MULTIMETER

.5" display 10 mEG input imp Auto polarity .1 ohm resolution overload protected. DC current 200u, 2 m, 20 m, 200 m, 10 A. Ohm 2K, 20K, 200K. 2M—1 yr. Warr.



#72-050  
(Formerly DVM-1)

**\$49<sup>95</sup>**

### DIGITAL CAPACITANCE METER

1 pF to 1999 uF accuracy .5%, 3 1/2 digit .5" 8 ranges full scale 200 pF to 2000 uF .1 pF resolution .5 sec. sampling time crystal OSC time base 1 yr. warranty.



#72-040 **\$69<sup>95</sup>**  
(Formerly DCM-1)

### AC VARIABLE TRANSFORMER

Has a built-in AMP Meter which shows excessive current draw to check for shorts before they can cause costly component failure 0-140 volts 10 AMPS.



#72-110 **\$89<sup>95</sup>**  
(Formerly AT-3)

### MCM NOW CARRIES

**THORDARSON**

FLYBACKS & YOKES  
**50% OFF LIST**  
on in-stock items

Ask for your **FREE** Replacement Guide with order.

### SANYO FOCUS BLOCK

Sanyo Part #ESPA-98-F1 #Z0064



#33-748 **\$23<sup>95</sup>** **\$19<sup>95</sup>**  
(1-9) (10-up)

### UNIVERSAL BEHIND THE SET

5 section, dual VHF antenna



#30-070 **\$3<sup>30</sup>** **\$2<sup>90</sup>** **\$2<sup>45</sup>**  
(Formerly U-38) (1-9) (10-49) (50-up)

### NEW! TOUCH TONE\* TELEPHONE

Attractive modern design ■ High quality durable ABS plastic ■ Bell type ringer ■ Wall or desk phone ■ Last number redial ■ FCC approved ■ Available in Ivory or Brown ■ Tone-dial, access computers and MCI type long distance carriers ■ **Available mid-August.**



\*TOUCH TONE is a registered trademark of AT&T  
#36-240 **\$23<sup>95</sup>** **\$19<sup>95</sup>**  
(1-2) (3-up)

### SHARP FLYBACK TRANSFORMERS

Sharp #RTRNF2037TAZZ

Sharp #RTRNF1106CEZZ



#33-655 **\$22<sup>50</sup>** **\$19<sup>95</sup>**  
(1-9) (10-up)

#33-750 **\$28<sup>95</sup>** **\$25<sup>95</sup>**  
(1-9) (10-up)

### 25C1308K — ORIGINAL SANYO!

Most reliable horizontal output sold today, replaces ECG® 238, 165 and most other outputs.



1500v **\$1<sup>99</sup>** **\$1<sup>85</sup>**  
7a (10-99) (100-up)  
50w

### T-WIK SPECIAL


■ Tenma brand braided solder remover ■ 5 ft.

#21-327

**74¢**  
(Min. 10 pcs.)

### 8 VOLT FUSE TYPE LAMPS

8 volt 250 MA  
1 1/4" x 1/4"

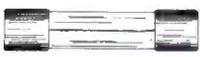

#25-090 **29¢**  
(min. 100)

### AGC FUSES



Buy any AGC Fuse for

**4¢ ea.**

(min. 100, no mixing)

### F-59 ALM



#33-410 (min. 10)  
**24¢** **21¢** **18¢**  
(10-99) (100-499) (500-up)

### F-81 FEMALE SPLICE



#33-460 (min. 10)  
**26¢** **24¢** **19¢**  
(10-99) (100-499) (500-up)

### CONNECTORS

#### GROUNDING BLOCK



#33-470  
**50¢** **40¢** **35¢**  
(1-9) (10-99) (100-up)


#### MATCHING TRANSFORMER



75-300 Ohm  
#33-050 (min. 100) **34¢**
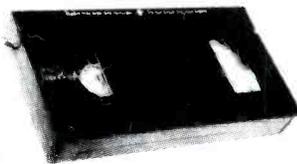
### 2-4-6 HOUR VHS VIDEO TAPE

■ Top quality video tape. ■ Made in USA  
■ VHS T-120. ■ Attractive packaging for display. Comes with heavy cardboard case.



#38-090

**\$7<sup>95</sup>**  
(1-9)

**\$6<sup>95</sup>**  
(10-49)

**\$5<sup>95</sup>**  
(50-up)

### COTTON SWABS


■ Great for tape machine maintenance  
■ 6" wooden stick for getting into tight places ■ 100 per bag

#21-060

**85¢**  
(1-49 bags)

**70¢**  
(50-99 bags)

**65¢**  
(100 bags-up)

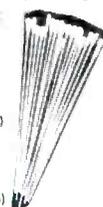

### VCR FOAM SWABS

■ Absorbent foam material. Perfect for delicate cleaning jobs. Will not separate or leave fibers on the VCR head ■ 50 per bag

#21-050

**\$1<sup>60</sup>**  
(1-49 bags)

**\$1<sup>50</sup>**  
(50-99 bags)

**\$1<sup>35</sup>**  
(100 bags-up)



### HIGH GAIN DELUXE VHF TO UHF 40 CHANNEL CABLE CONVERTER

+ 5 to + 8 db GAIN!

■ Amplifies low level CATV lines [ ]. Includes mid and superband channels.

FULL FEATURES

■ Uses your UHF tuner to access cable TV channels


■ Channel conversion chart included ■ Front fine tuning adjustment ■ +5 to 8 dB UHF gain ■ Wide input range ■ Flat frequency response ■ Easy installation

■ High reliability ■ Compatible with built-in remote tuning systems ■ Accessible master oscillator control for entire band adjustment for multiple STV applications

#32-100

**\$23<sup>95</sup>** **\$19<sup>95</sup>**

(1-9) (10-up)

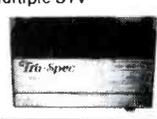

**mcm**  
ELECTRONICS  
RIGHT PARTS, RIGHT PRICE,  
SHIPPED RIGHT AWAY

\*Call Today for Your **FREE** 96-pg. Summer Catalog #6 and see our complete line of over 4,000 parts.

CALL TOLL FREE **1-800-543-4330** (In Ohio 1-800-762-4315)

858 E. CONGRESS PARK DR. CENTERVILLE, OH 45459

Circle (5) on Reply Card

# Part 1 Servicing the RCA CTC 108 unitized chassis

By Stan Vittetoe, CET

Newer TV receivers can be classified either as unitized or modular (with plug-in panels). Unitized receivers often have all the components (except tuner systems) mounted on one large circuit board, so troubleshooting requires a high degree of skill. Fortunately, many similarities are retained by the manufacturers over several models, and a technician can become familiar with the circuits and the typical failures.

This article is specifically for the RCA CTC108 chassis (Photofact 2030-2), but many explanations and tips apply equally to CTC107, CTC109 and CTC110, although the component identification number on schematics might be different.

All these receivers are the "hot chassis" type, which have dangerous ac voltages between chassis ground and earth ground. To prevent damage to test equipment and shocks to technicians, the receiver *must* be plugged into an isolation transformer. Also, many troubleshooting procedures call for variable line voltages, so a *combination* isolation transformer and variable-voltage transformer is strongly recommended.

## Power supplies and start-up

In the past, troubleshooting color TV receivers usually began with the technician making tests in the circuits that were most likely to cause the observed symptoms. Sometimes, these measurements eventually included all the supply voltages for the suspected stages, but the importance of testing supply voltages has a higher priority with late-model receivers. This is

because of the many voltage sources that rectification and filtering of horizontal-sweep power from the flyback produce. Remember that no dc voltages can come from these power sources when the horizontal-sweep circuit is dead.

Figure 1 shows a partial schematic of several important CTC108 power supplies, assuming there are no defects or incorrect adjustments. Only the +33.5V zener-regulated voltage source and the SCR-regulated +121V source are derived directly from the +167V main power source. Several other start-up and continuous operation supplies are taken from the +121V regulated source. However, the +121V source cannot operate with more than partial voltage until start-up occurs and two sources of horizontal pulses are supplied to the SCR and its control circuitry.

Various start-and-run (continuous operation) and separate start sources and run sources are marked on the schematic. A knowledge of these voltages and how they perform start-up is essential for efficient troubleshooting.

Part defects can stall the start-up sequence at some intermediate stage. In some cases, for example, R437 (which supplies start-up B+ to the driver transistor) has been found open, causing a dead set each time by preventing start-up. Even worse, the resistance sometimes has increased to about 10k $\Omega$ , producing erratic start-up.

Also, the shut-down circuitry (which protects by eliminating the driver-transistor gain) is activated

by excessive amplitude of some flyback pulses, or by excessive high voltage or high-voltage current. Therefore, correct start-up can be followed instantly by shut-down, perhaps seeming to be start-up failure. Either condition gives the symptoms of loss of all sound, high voltage and raster.

## Troubleshooting startup problems

The failure of the CTC108 to achieve proper start-up produces a receiver with no sound, no raster and no high voltage. These outward symptoms can be caused either by an inoperative horizontal-sweep system or by a missing start-up power-supply voltage. Use this checklist to locate the defect:

- Measure the dc voltage at input filter-capacitor C105; it should be +165V or higher. If it is zero, the F101 fuse or RF101 probably is open, perhaps from a shorted bridge rectifier or C105 filter capacitor. A voltage between +100V and +120V might indicate an open C105. When C105 is normal, a low +167V-supply reading hints at excessive load on the bridge-rectifier supply.
- If the C105 dc voltage is normal, measure the +20.5V supply (CR111 cathode), the +182V supply (CR112 cathode) and the collector voltage of Q412 output transistor. If all have typical start-up dc voltages, a defect in one of the three horizontal stages is eliminating the horizontal sweep or the circuit is in shut-down.

Meet the New  
Low-Cost

# Simpson 470™!

The Made-in-USA, Full-Function 3½ Digit Hand-Held DMM

Professional-Grade Design and Construction  
Full Measurement Capability—100  $\mu$ V to 1000 V DC, 100  $\mu$ V to 750 V AC, 0.1  $\Omega$  to 19.99 M $\Omega$ , up to 10 A AC/DC current  
0.15% DC V Accuracy  
0.5" High-Contrast LCD Display—with auto low-battery indication

Wide Temperature/Humidity Operating Range—up to +55°C at 70% humidity, up to 90% humidity at +35°C  
Audible Tone—for quick continuity checks  
Diode Test—for "good-bad" semiconductor tests

Transient Protection—All V and  $\Omega$  ranges protected to 6 kV up to 100 microseconds  
Double Fusing System—for both low and high energy overload protection  
Built-in-Tilt Stand—for convenient bench or hanging-upright viewing

Anti-Skid Pads—keep the instrument firmly in place when making measurements  
Thumbwheel Knobs—for easy range and function selection

Single 9-Volt Battery—approximately one-year life with average use  
UL-Recognized Test Leads—complete with screw-on, insulated alligator clips

Full Line of Optional Accessories—including high-voltage, temperature and RF probes, two "universal" test lead systems, and UL-recognized Amp-Clamp adapter  
Choice of Two Optional Carrying Cases—deluxe Ever-Redy neck strap case that provides 2-way hands-free/bench-top use, or soft vinyl-padded pouch with belt strap

**High-Impact Molded Case**  
—Choice of two-tone Brown or two-tone Gray

SHOWN  
ACTUAL  
SIZE

MANUFACTURED  
\$139  
IN U.S.A.

Complete with battery,  
test leads and manual

THE NEW SIMPSON 470™ WILL SOON JOIN THE FAMILY OF  
29 OTHER UL-LISTED SIMPSON INSTRUMENTS... AVAILABLE AT  
LEADING ELECTRICAL/ELECTRONICS DISTRIBUTORS WORLDWIDE

**Simpson**  
INSTRUMENTS THAT STAY ACCURATE

**SIMPSON ELECTRIC COMPANY**  
A Katy Industries, Inc. Subsidiary

853 Dundee Avenue, Elgin, Illinois 60120  
(312) 697-2260 • Telex 72-2416 • Cable SIMELCO

IN CANADA: Bach-Simpson Ltd., London, Ontario  
IN ENGLAND: Bach-Simpson (U.K.) Ltd., Wadebridge, Cornwall

Circle (6) on Reply Card

- If only one of the three start-up dc voltages is much lower than the typical voltages shown in Figure 1, the defect involves the source of the incorrect voltage. Check all components in and around the source.
- If the three horizontal stages have typical start-up dc voltages and the entire horizontal-sweep system *appears* to be normal, check the overvoltage shut-down safety circuit to de-

termine whether the receiver is in shut down. Refer to the shut-down circuit analysis later in this article.

- If the C105 voltage is approximately +167V, but the +121V regulated voltage is zero, the problem is in the SCR101 regulator circuit. (See Figure 2).

### Regulation by SCR

The regulation of the high voltage and picture width in the

CTC108 is accomplished by regulating the +121V supply. In turn, the 121V-supply voltage is regulated (in part) by adjustment of the percentage of time a filter capacitor is charged from a source of higher dc voltage. This is integration of dc voltage, a principle used in many other makes of color receivers.

Figure 2 shows a partial schematic of a 121V regulator that has four small transistors and a

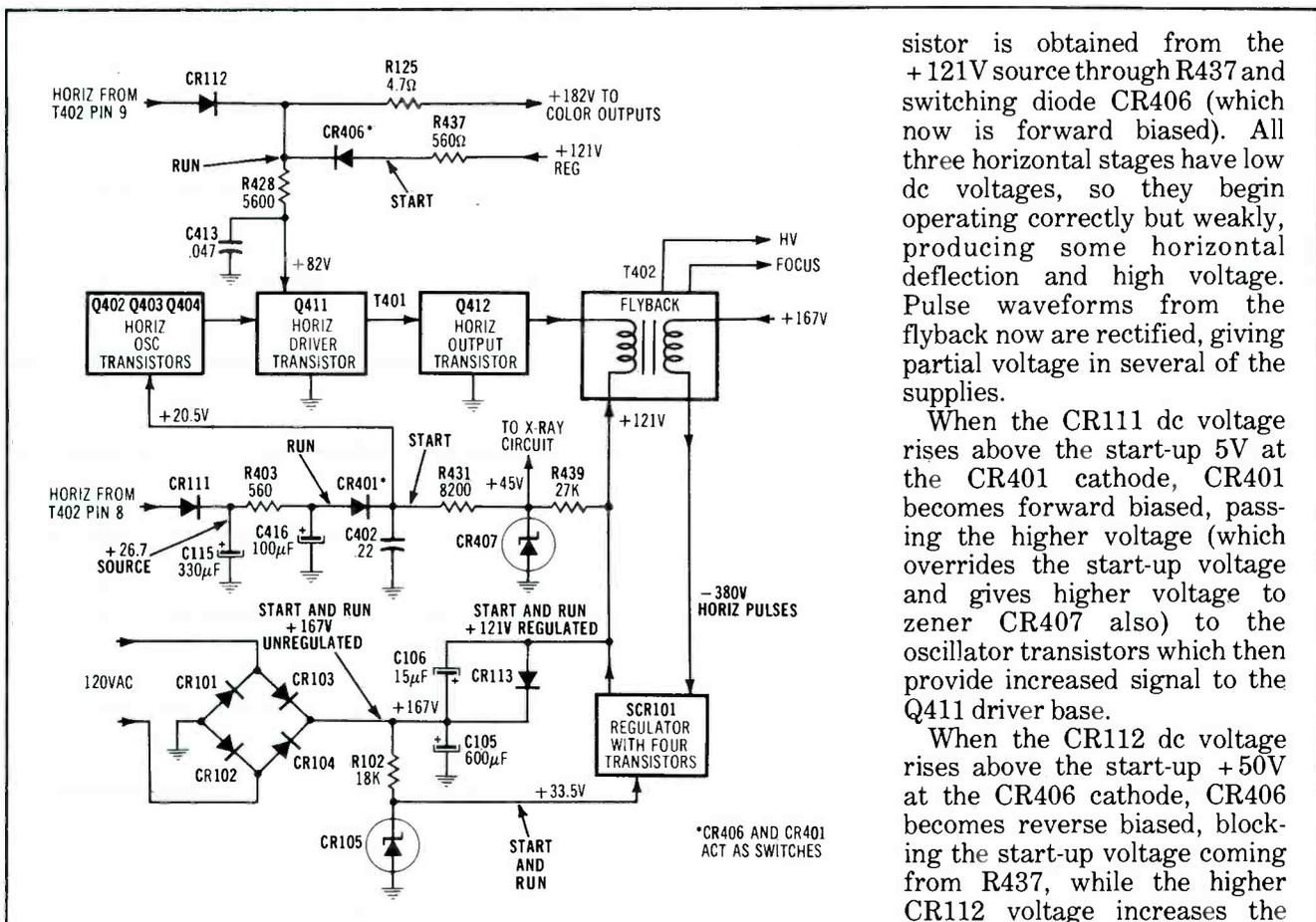


Figure 1. This partial schematic shows several important power supplies.

At turn-on, before the horizontal-sweep system begins to operate, the only CTC108 active power sources are the +167V line-rectified principal source and two others derived from it. All three operate continuously when the power is on. Power from the +167V source passes through R102, where it is regulated by zener diode CR105 to +33.5V, and then applied to the four regulator transistors. The +121V source is regulated by SCR101 and sent to the collector of the horizontal-output transistor Q412.


During start-up, however, Q412 draws no current because it has no base drive, and the +121V supply has only partial voltage. Some voltage from the +121V supply goes through R439 to the overvoltage shut-down circuit, but that is not essential to start-up. About 5V comes from the +121V supply through R439 and R431 to the oscillator circuit (switching diode CR401 is reverse biased from CR111), providing weak oscillation. Similarly, about +50V for start-up of the Q411 driver tran-

sistor is obtained from the +121V source through R437 and switching diode CR406 (which now is forward biased). All three horizontal stages have low dc voltages, so they begin operating correctly but weakly, producing some horizontal deflection and high voltage. Pulse waveforms from the flyback now are rectified, giving partial voltage in several of the supplies.

When the CR111 dc voltage rises above the start-up 5V at the CR401 cathode, CR401 becomes forward biased, passing the higher voltage (which overrides the start-up voltage and gives higher voltage to zener CR407 also) to the oscillator transistors which then provide increased signal to the Q411 driver base.

When the CR112 dc voltage rises above the start-up +50V at the CR406 cathode, CR406 becomes reverse biased, blocking the start-up voltage coming from R437, while the higher CR112 voltage increases the output signal from Q411 that drives Q412. Therefore, the higher dc-supply voltages force the horizontal-sweep system to operate more strongly. In turn, the higher amplitude of horizontal-sweep operation produces higher dc voltages from all the horizontal-rectified voltage supplies. This is a regenerative condition that rapidly reaches maximum and then stabilizes with the dc voltages shown on the schematic, including correct operation of the +121V regulated supply that now has proper pulses for synchronization and SCR turn-off.

# CASH REBATES

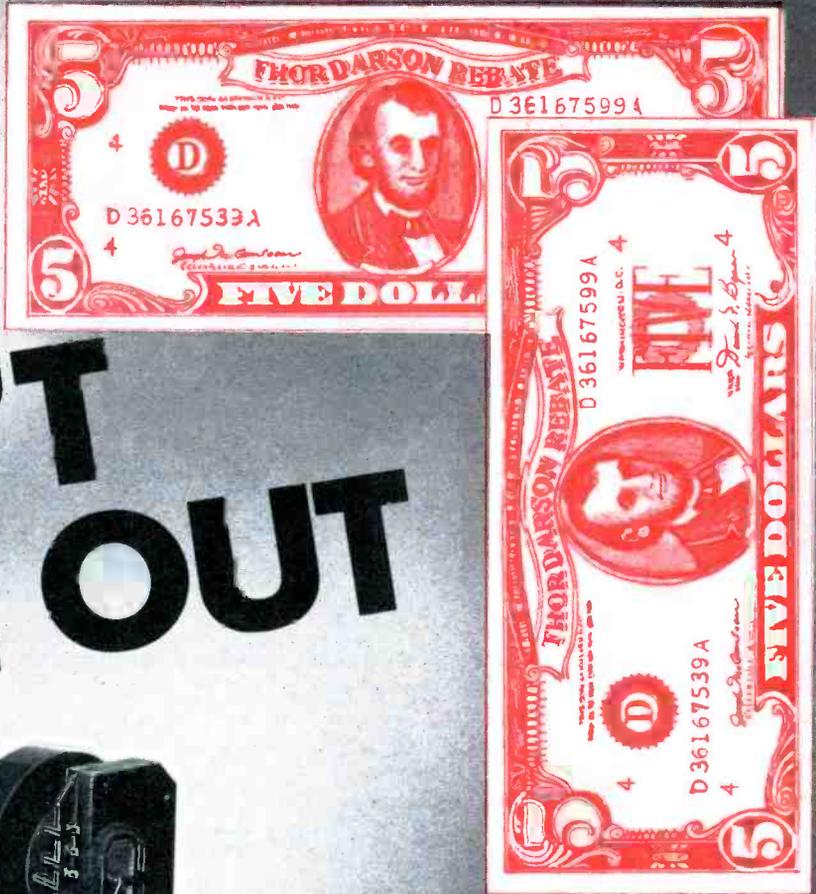

# DON'T LOSE OUT



Replacement for

RCA 1439849-501 (145722)  
**BUY OUR FLY 691,  
Receive \$5.00 Rebate!**

Replacement for

RCA 1439242-501 (143732)  
**BUY OUR FLY 692, Receive \$5.00 Rebate!**

**IT'S SIMPLE!** Purchase Thordarson's exact replacements for these two popular RCA products. Remove the box label and return to:

**THORDARSON MEISSNER, INC.  
DEPT. LL, ELECTRONIC CENTER  
MT. CARMEL, IL, 62863**

**We will promptly send you a check; \$5.00 for every FLY 691 and/or FLY 692.**


**NO LIMIT! OFFER EXPIRES NOVEMBER 15, 1983!**

**Take advantage of Thordarson's Rebate Offer and we will send you a complimentary copy of the New RCA Flyback Cross Reference.**

## THORDARSON MEISSNER, INC.


ELECTRONIC CENTER 628 BELMONT STREET MT. CARMEL, IL 62863 PHONE (618) 262-5121

Circle (7) on Reply Card

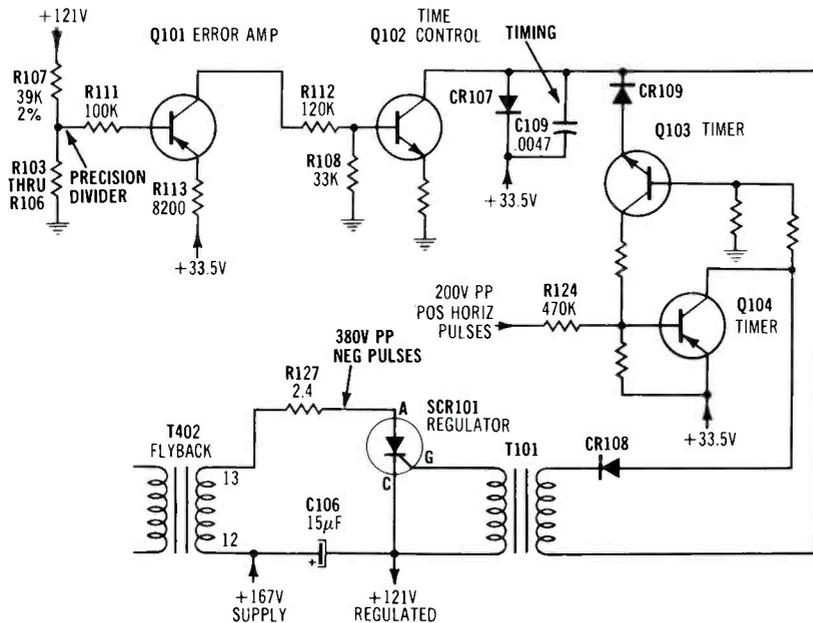

**Figure 2a.** This CTC108 regulator schematic has been simplified to show the general operation more clearly.

**Figure 2b.** A discharged capacitor usually is considered to have 0V at both ends. However, in the CTC108, +33V is at both ends of C109 when it is discharged following each Q104 conduction. Zero at one end and +33V at the other represents a full charge.

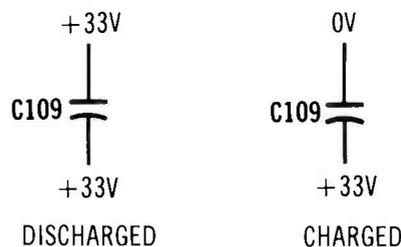

The four transistors gate-on the SCR101 conduction at the proper time during each horizontal cycle. C106 integrates these dc pulses of SCR current, and the duty cycle of the current pulses is varied as needed to maintain a regulated +121V for the horizontal-output transistor. Pulses from Q103 and Q104 gate-on the SCR101, and the current continues until the next negative-going pulse at the SCR101 anode.

The operation of transistors Q103 and Q104 has been described as a multivibrator action. The circuit is *not* a multivibrator oscillator, but there are some similarities. Notice that the Q104 collector is directly connected by a resistor to the Q103 base, and the Q103 collector is connected through a resistor to the Q104 base. A coupling capacitor at the base of either Q103 or Q104 would have produced a multivibrator, but

there is no coupling capacitor. Instead, the circuit is a one-shot regenerative switch that is activated when the Q103 emitter voltage decreases to a point that provides forward bias for the base of NPN-polarity Q103. A rapid regenerative action follows (because the collector/base phases are correct for oscillation). This action ends with the saturation of Q104, forcing voltage from the +33.5V supply through the Q104 emitter/collector, the forward-biased CR108 diode, the primary winding of T101 triggering transformer and on to capacitor C109. Notice that this temporarily connects one end of C109 to the +33.5V at Q104's emitter while the other end is permanently connected to the +33.5V supply. In other words, C109 has just been discharged by having the same voltage at both ends.

Figure 2B shows why this is true. The short-duration pulse

of Q104 saturation current passes through the T101 primary, generating a similar pulse in the secondary winding that gates-on SCR101 conduction, raising the +121V-supply voltage. Resistor R127 limits the maximum current flow into C106 and also prevents an ac short across the flyback winding when SCR101 conducts. Next, a circuit action must initiate the Q104 maximum-current pulses (that discharge C109) at proper times.



Actually, C109 must be discharged twice during each horizontal cycle. One discharge is produced during horizontal retrace by a positive flyback pulse through R124 to the Q104 base. This applies a pulse to the SCR101 gate (which is ignored because the SCR is being turned-off by an anode pulse at that time) and also discharges C109, thus preparing C109 to accept a precision-timed charge that triggers the next Q103/Q104 single-shot pulse.

The timing circuit includes Q101 and Q102, which control the slow charging of C109. Emitter voltage for Q101 is stabilized by zener CR105 (see Figure 1), while the Q101 base voltage comes from a precision voltage divider connected between the +21V regulated supply and ground. When the regulated voltage rises, for example, Q101 has a decreased forward bias that reduces the collector positive voltage, which goes through R112 to the Q102 base. This produces decreased Q102 collector current that charges C109 more slowly (the C109 charging current is the Q102 collector current), so a longer time is required for the Q103 emitter (connected to C109) to reach the critical triggering voltage. Therefore, SCR101 current is gated-on later in the cycle, reducing the +121V-supply voltage to normal. Of course, a decrease of +121V-supply voltage because of increased CRT current will reverse the action previously described, increasing the voltage to normal.


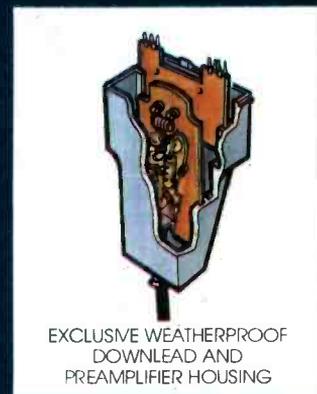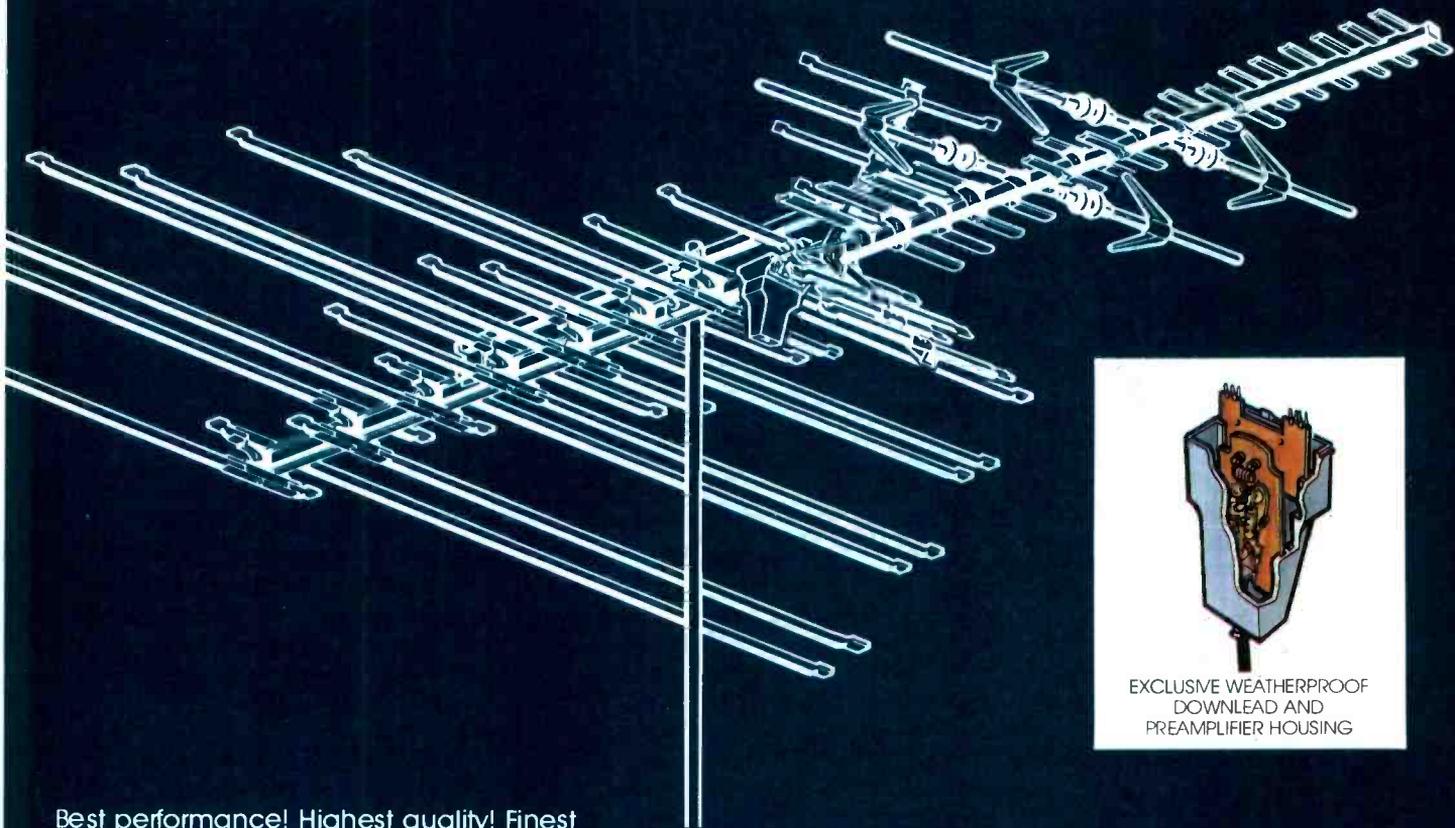
# ALL THE BEST CHROMSTAR II

WINEGARD'S NEW EVOLUTIONARY LINE OF  
OUTDOOR ANTENNAS AND PREAMPLIFIERS



EXCLUSIVE WEATHERPROOF  
DOWNLEAD AND  
PREAMPLIFIER HOUSING

Best performance! Highest quality! Finest construction! Competitively priced! Antennas engineered in the Winegard tradition of quality and craftsmanship.

Chromstar II antennas feature the sharpest directivity, highest gain and more benefits than any competitive series. Models to satisfy every reception requirement.

Chromstar II antennas are rugged. High tensile aluminum alloy tubing provides rigidity and stability. Every antenna boasts famous Winegard anodizing—the only positive, permanent protection yet against corrosion and fading.

Chromstar II antennas are engineered for extra strength at all points of stress: scissor-type struts on wedge models; double boom on longer flatline models, high-impact girder design support insulators molded of super-tough G-E Noryl® plastic; preassembled snap-out corner reflectors on all 82-channel and UHF models; and truss-type phasing bars.

## WINEGARD CHROMSTAR II PREAMPLIFIERS

The Chromstar II preamplifiers are Winegard's finest ever and at 13-35% lower cost! Designed for the ultimate fringe and deep fringe reception, these solid-state preamplifiers slip into the new, improved weatherproof cartridge housing at the point of the signal interception. There are a wide choice of models for VHF-UHF-FM, VHF-FM and UHF only.

The housing built into every Chromstar II antenna (or available separately for use on any antenna) is molded of clear G-E Lexan® to prevent breakage and provide protection against ultra-violet rays and chemical deposits.

Compare Winegard Chromstar II antennas and preamplifiers with competitive models. Compare construction. . . Compare performance. . . Compare price. . . You'll agree, Chromstar II antennas and preamplifiers set the quality and value standards for the industry.



**WINEGARD®**  
TELEVISION SYSTEMS

WINEGARD COMPANY • 3000 KIRKWOOD STREET • BURLINGTON, IOWA 52601 • (319) 753-0121

Circle (8) on Reply Card

[www.americanradiohistory.com](http://www.americanradiohistory.com)

**Now 27 choices! Free, free, free...**



Hurry, hurry, step right up! It's RCA's Carnival of Awards. And what a lineup of acts. First, the headliners: RCA receiving tubes, very popular with TV technicians for their top performance and dependability.

Plus, a stupendous carnival of valuable awards. Shown here are just a few of the 27 great gifts waiting for you. To earn them, just purchase RCA receiving tubes in required quantities from your participating RCA distributor. Each purchase helps qualify you for the award of your choice. See your participating RCA distributor for details. And come one, come all to RCA's Carnival of Awards!

power SCR. Simply stated, the four transistors gate the SCR into conduction at the proper point during each horizontal-sweep cycle, so the dc voltage from the +167V supply can travel through a flyback winding, a resistor and the SCR anode/cathode conduction and replenish any C106 power needed to maintain +121V at C106 and the SCR101 cathode. Negative-going horizontal-sweep pulses from T402 flyback pin 13 turn off SCR101 conduction of dc current by making the anode more negative than the +121V at the SCR cathode.

When the line voltage is low or the picture tube draws increased high-voltage current, the +121V supply voltage drops. The regulator circuit restores the original voltage by gating-on the SCR101 conduction earlier in each horizontal cycle. A longer time of charging C106 (up to 50% of each cycle) from the +167V supply raises the C106 voltage until the desired +121V is obtained. At the other extreme, higher line voltage or decreased CRT current forces

the +121V supply to a higher voltage, which is reduced by gating-on the SCR101 conduction later, giving perhaps only 25% conduction time.

The 4-transistor circuit monitors the +121V-supply voltage, and from the instantaneous dc voltage there, it adjusts the time between the previous horizontal pulse and the beginning of SCR101 conduction. Once gated-on, any SCR current continues until the anode/cathode current is interrupted (becomes zero). Gating off the SCR in this circuit is accomplished by the next negative-going horizontal pulse that reaches the anode. Therefore, regulation correction occurs during each horizontal cycle, with the SCR conduction just prior to each horizontal pulse.

#### **Enhanced regulation**

CTC108 regulation operates as described in Figure 2 except for one effect that is seldom explained. Measurements published in the January 1980 issue of **Electronic Servicing** showed only 0.7V

C410 is the principal frequency-determining component, although some resistors and dc voltages also determine and vary the frequency. Notice that Q401, Q402 and Q404 emitters are connected together, sharing a single R418 resistor. For the purpose of analysis, imagine that these three transistors are one transistor with three bases. Q402 and Q403 are connected almost as an unbalanced multivibrator. That is, the Q402 collector is connected directly to the Q403 base, and the Q403 collector is connected through two resistors to the Q402 base. Only a coupling capacitor at the Q402 base is needed to form a multivibrator, but this much of the circuit cannot oscillate.

R423 and C410 form an integrator for the Q403 collector square waves, forming a triangular waveform at the

# with your purchase of RCA Receiving Tubes!



CG7170  
RAY-O-VAC "Magnum"  
5-Function Light  
Value: \$27.45



CG7178  
Waring  
Ice Cream Parlor  
Value: \$44.99



CG7163  
Cobra Cordless  
Extension Phone  
Value: \$189.95



CG7164  
Wittnauer "Saturn"  
Man's Quartz Watch  
Value: \$175.00



CG7169  
Skil Cordless  
Screwdriver  
Value: \$39.99



CG7180  
London Fog  
Man's Raincoat  
Value: \$150.00



CG7162  
Canon Palm-sized  
Printing Calculator  
Value: \$64.95



CG7168  
Skil Double Insulated  
7 1/4" Power Saw  
Value: \$65.99

CG7167  
American Tourister  
5 Inch Attache Case  
Value: \$56.00



## RCA Receiving Tubes

RCA Distributor and Special Products Division, Deptford, NJ 08096

Q404 base. Because the three emitters are connected together, the Q404 base signal affects the Q402 bias in reverse.

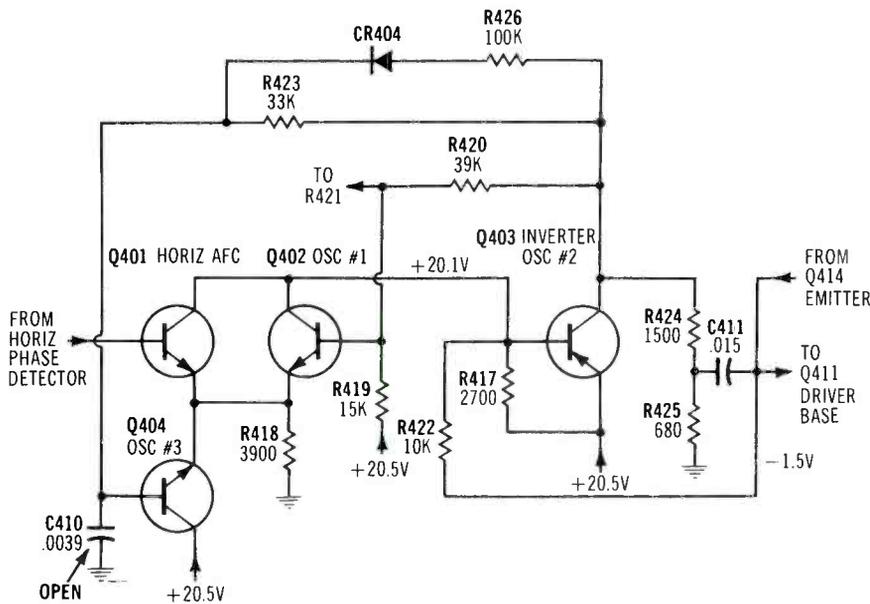


Figure 3. The oscillator circuit of CTC108 can be seen clearly in this schematic.

For example, the triangle positive peak at Q404 base increases the common emitter positive voltage, which is equal to a decrease of the Q402 base voltage. Therefore, Q402 is cut off. When the Q404 base negative peak arrives, Q402 is biased to saturation. In this way, the three transistors become an oscillator (but without a frequency control). Q401 base receives the varying dc voltage produced by the horizontal phase-detector action of CR402/CR403. Also, the Q401 base receives an adjustable dc positive voltage from the R416 horizontal-frequency control. The Q401 emitter is connected to the Q404 and Q402 emitters, so a change of Q401 emitter current affects their bias and varies the oscillator frequency.

variation of the +23V regulated voltage in a CTC99 when the line voltage was varied from 125Vac to 100Vac. That was excellent regulation, but readings made at line voltages lower than 100Vac showed regulated voltages that were *higher* than the source-supply voltage. Of course this is impossible, because no derived voltage can exceed its source.


There is another reverse proof that SCR conduction of dc power cannot be the sole source of the regulated voltage. Waveforms of the CTC99 showed the maximum

conduction time of the SCR was only about 50%, even at a 60Vac line voltage. C106 integration of these CTC108 50% duty-cycle dc pulses from the SCR produces only 50% of the supply voltage, and 50% of +167V is +83.5V, which is far below the +121V actually obtained. Obviously, another circuit action is increasing the regulated-voltage level.

Research conducted on the CTC99 previously showed the higher regulated dc voltage was produced by rectification of the SCR-anode pulses that turn off the

SCR conduction. Rectification of these pulses appears to be very unlikely, because they are negative-going and ordinarily could produce little rectified dc voltage. However, the +167V introduced at flyback pin 12 shifts the zero-voltage point down on the waveform by the equivalent of 167V peak-to-peak. Therefore, most of the pulse height is positive and can be rectified by the SCR diode action until the pulses become negative and turn off all SCR conduction.

*(To be continued next month.)*

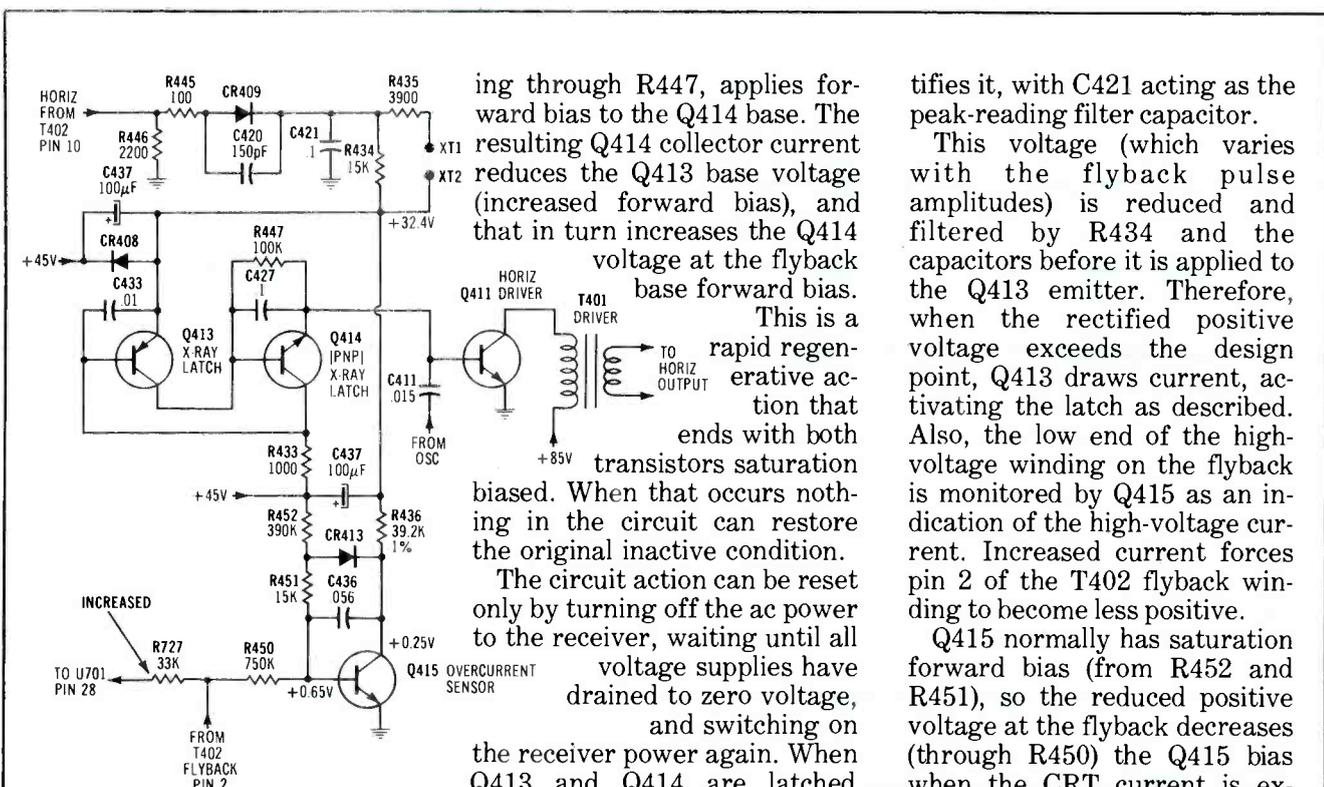

**Figure 4.** The Q413 and Q414 collectors are shown here.

Q413 and Q414 form a locking switch. The collector of Q413 is connected directly to the Q414 base, and the Q414 collector is connected directly to the Q413 base. At rest, neither transistor has C/E current. Q413 is reverse biased, and Q414 has zero forward bias.

If the Q413 cathode dc voltage becomes +0.6V or more above the Q413 base voltage, this is forward bias that produces Q413 C/E current, which pass-

ing through R447, applies forward bias to the Q414 base. The resulting Q414 collector current reduces the Q413 base voltage (increased forward bias), and that in turn increases the Q414 base forward bias.

This is a rapid regenerative action that ends with both transistors saturation biased. When that occurs nothing in the circuit can restore the original inactive condition.

The circuit action can be reset only by turning off the ac power to the receiver, waiting until all voltage supplies have drained to zero voltage, and switching on the receiver power again. When Q413 and Q414 are latched (with saturation forward bias) a positive dc voltage from the Q414 emitter is applied to the base of Q411. This excessive forward bias eliminates all Q411 gain, so the horizontal-sweep operation stops.

As noted before, nothing can unlatch the shutdown action except turning off the power. Two different conditions can activate this safety shutdown latch: one is excessive high-voltage current; the other is excessive pulse amplitude from the flyback. Diode CR409 receives horizontal power from pin 10 of the flyback and rec-

tifies it, with C421 acting as the peak-reading filter capacitor.

This voltage (which varies with the flyback pulse amplitudes) is reduced and filtered by R434 and the capacitors before it is applied to the Q413 emitter. Therefore, when the rectified positive voltage exceeds the design point, Q413 draws current, activating the latch as described. Also, the low end of the high-voltage winding on the flyback is monitored by Q415 as an indication of the high-voltage current. Increased current forces pin 2 of the T402 flyback winding to become less positive.


Q415 normally has saturation forward bias (from R452 and R451), so the reduced positive voltage at the flyback decreases (through R450) the Q415 collector voltage applies (through R452, CR413 and R436) a higher positive voltage to the Q413 emitter, activating the shutdown operation that kills the horizontal sweep.

The operation of the shutdown circuit can be tested by shorting together testpoints XT1 and XT2. If the shutdown operation is normal, the sound and picture should disappear. This circuit protects the receiver against two basic overloads.




# SIMPLY AMAZING.

## B&K-PRECISION's under \$170 100 MHz frequency counter.

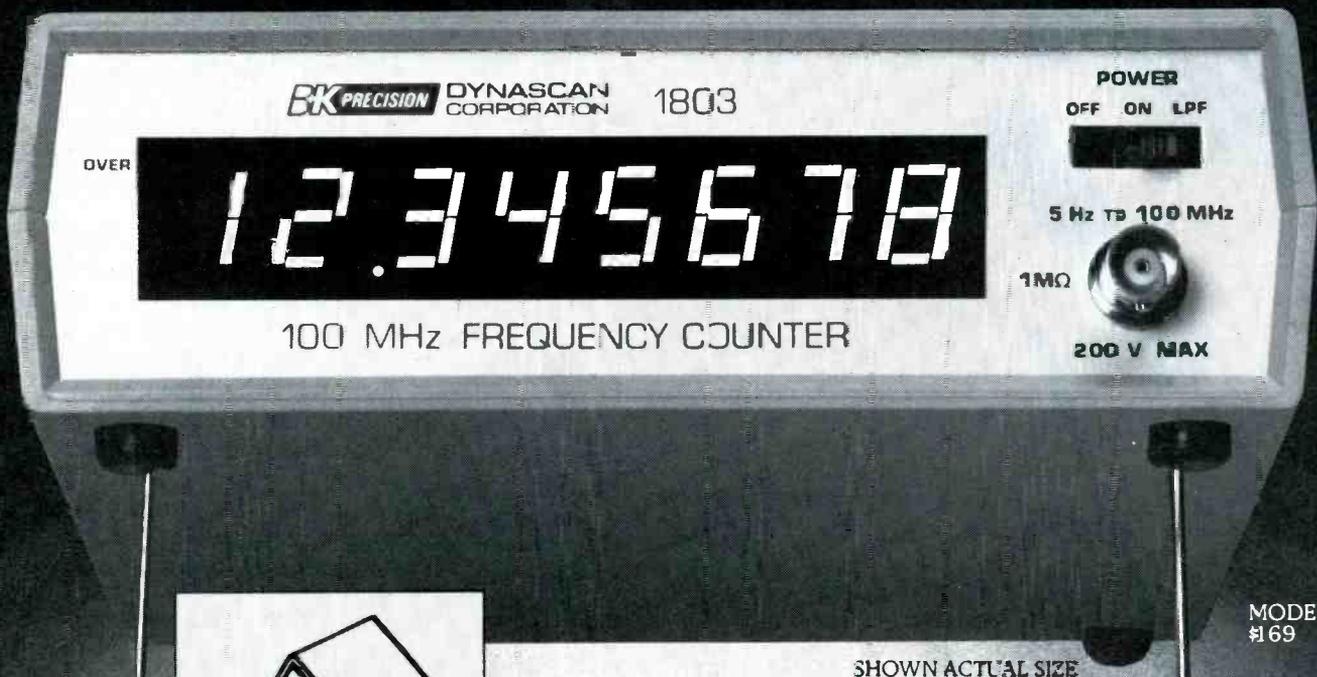


MODEL 1803  
\$169


SHOWN ACTUAL SIZE

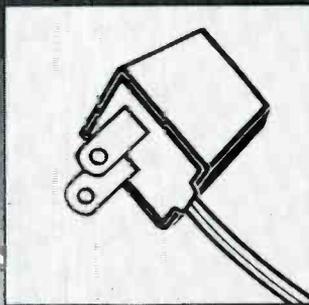

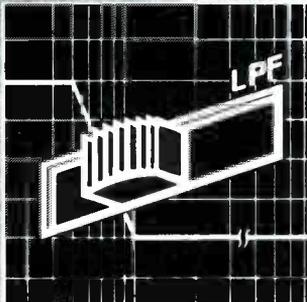SIMPLE TO POWER.  
BATTERY OR AC LINE  
OPERATION  
(ADAPTER INCLUDED)



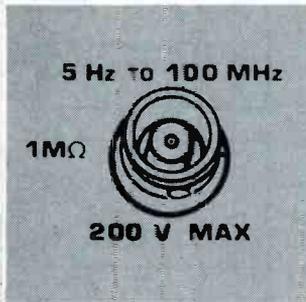SELECTABLE LOW-PASS  
FILTER FOR ACCURATE  
LOW-FREQUENCY  
MEASUREMENTS.



BNC INPUT CONNECTOR  
SIMPLIFIES HOOK-UPS  
—ELIMINATES NEED FOR  
ADAPTERS.



EASY-TO-READ,  
8-DIGIT DISPLAY  
PROVIDES 1 Hz RESOLUTION

For more details on the amazing 1803 and the full line  
of new B&K-PRECISION frequency counters, see your local  
distributor or call 1-312-889-9087.

**B&K PRECISION** DYNASCAN  
CORPORATION

6460 W. Cortland Street • Chicago, IL 60635 • 312/889-9087

International Sales, 6460 W. Cortland St., Chicago, IL 60635

Canadian Sales, Atlas Electronics, Ontario

South and Central American Sales, Empire Exporters, Plainville, NY 11803

Circle (10) on Reply Card

# HUNTER HAS HEX APPEAL.



Hunter is your single source for the widest range of hex tools available, including the original "Smitty" and other hex tool innovations. All tools made of selected grade of steel, heat treated and tempered to exacting specifications. For more information, contact your Hunter Sales Representative or write: Easco Hand Tools, Inc., 6721 Baymeadow Drive, Glen Burnie, Maryland 21061.

## Easco®

Circle (11) on Reply Card

tains four independent, non-inverting buffers, each of which has an active-low control line. By connecting all four CE lines together on the two devices shown in Fig. 4B, the input port is turned on with the  $\overline{IN}$  signal generated by the computer. (An  $\overline{IN}$  signal is generated when the port address and control signals combine to select a

particular port.)

The pair of 74125 devices forms a single 8-bit input port. The input terminals on the chips are treated the same as in Figure 3A. The 74125 is an example of a suitable input chip. The 74126 is similar except that it uses active-high chip enable lines. The Intel 8216 and 8226 are 4-bit, bidirectional, non-inverting and inverting, respectively, buffers used for I/O port service. The 8212 Intel device is an 8-bit bidirectional I/O port chip. There are also 8-bit input-only devices such as the 74LS244. Special-purpose I/O chips are made for specific microprocessor chips such as the 6522 for the 6502 and the Z80-PIO for the Z80.

### Debouncing keyboards

Mechanical switches don't close cleanly but bounce several times before making solid contact. This phenomenon is rarely a problem in analog circuits, but in digital circuits the noise spikes produced by contact bounce may be interpreted as valid signals. Most keyboards, therefore, require some form of debouncing scheme.

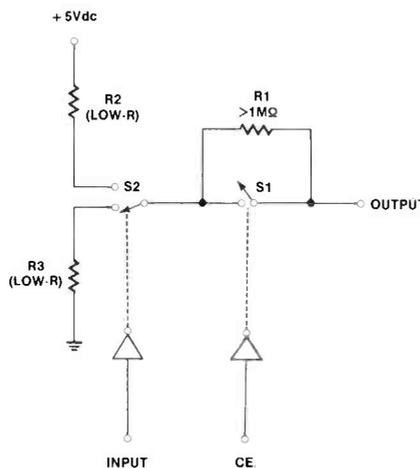


Figure 4a. If no output port is available, one must be provided. In a tri-state output, the third state is a high-impedance in series with the output terminal.

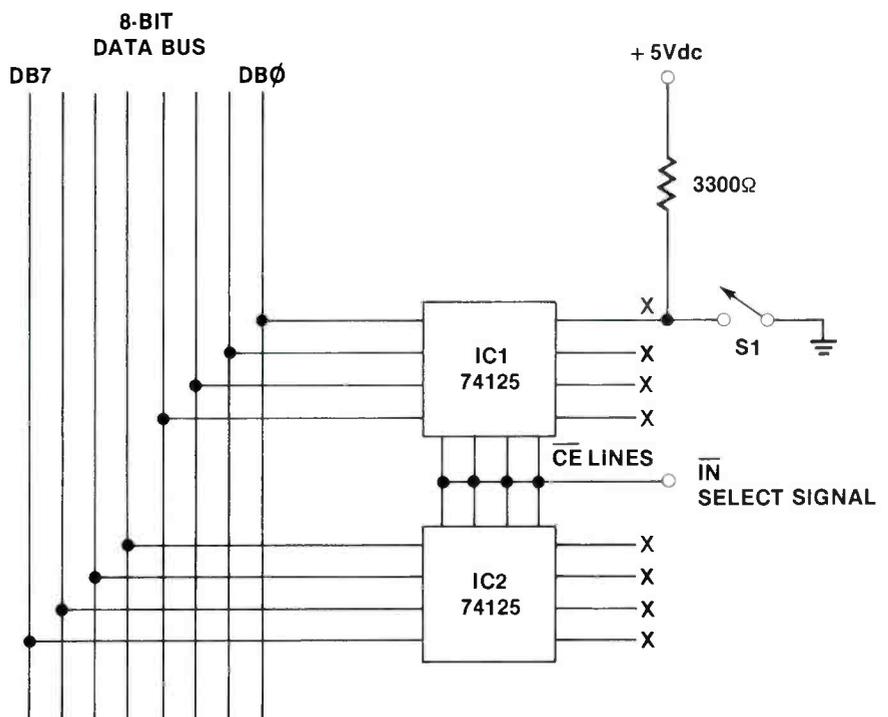


Figure 4b. Here, two 4-bit chips are used to fabricate an 8-bit output port.

# OMNITRON:

# SEPTEMBER SPECIALS

NOTE: Must Use "ETD" Part #'s For Special Prices

Silicon  
H.V. Triplers  
**HIGH VOLTAGE  
MULTIPLIERS**



Original ECG **SYLVANIA Triplers**

**ECG-500A**    **ECG-523**    **ECG-526A**

212-139	212-141	212-141-02
212-139-01	212-141-01	212-141-03
212-139-02	#ETD-21	212-141-04
#ETD-20		#ETD-22

\$10.99 ea.    \$10.99 ea.    \$10.99 ea.

**SANYO**    **TOSHIBA**




2SC1308K    2SC1172B  
#ETD-5B    #ETD-5C

**\$1.49** /50 up  
\$1.69    10-49

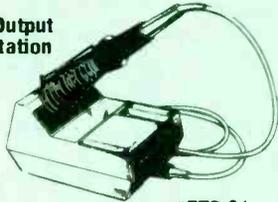**Weller**

**Controlled Output  
Soldering Station**



**\$64<sup>95</sup>**

Model WTCPN

#ETD-34


**ADJUSTABLE-TEMPERATURE  
SOLDERING STATION**

- Temperature 0°C to 750°C
- LED indicators
- 50-B182-Replacement Tips \$3.<sup>99</sup> each

Model 50B-180

**\$49<sup>95</sup>**

#ETD-18

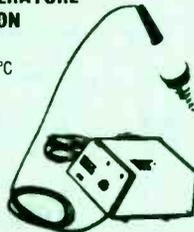

**30 WATT ECONOMY SOLDERING IRON**


Model FS-30    #ETD-36    **\$1<sup>99</sup>**



**25 WATT INDUSTRIAL GRADE SOLDERING IRON** Model KSI-25

KST-252 Replacement    #ETD-36    **\$7<sup>99</sup>**

Tips... \$2.<sup>99</sup> each

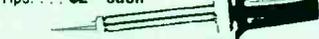

**SOLDER** (60/40 Rosin Core)  
1 lb. - .062 dia. (regular size)

**\$7<sup>99</sup>**

#ETD-2



1/2 lb. (thinner size)

**\$3<sup>99</sup>**

#ETD-3

**Weller All-Purpose Dual Heat Soldering Gun** #ETD-23

8200

**\$17<sup>99</sup>**

Snap-Vacuum Solder Remover  
KST-412 - Replacement Tips - \$2.<sup>99</sup> each    #ETD-24  
KSR-410    **\$4<sup>99</sup>**



**4 1/2" DIAGONAL CUTTING PLIER**

#ETD-25

#1934

**\$3<sup>99</sup>**



#1930

**\$3<sup>99</sup>**



#1930

**\$3<sup>99</sup>**

**3AG FUSE ASSORTMENT**

#ETD-27

Model 3AG-300FK

**300 pieces for**

**\$15<sup>00</sup>**

Assortment of 100 each, any value 3AG fuse, or 1-5A Recommended Selection: 100 each of 2A, 3A & 5A fuses



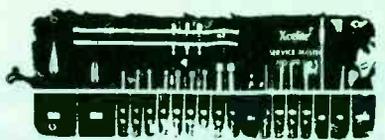
#ETD-4 **SOLDER WICK** (Solder Removal) 1/8" (Thick Type)

**99¢** SW-5



**Xcelite** #ETD-28    **\$54<sup>00</sup>**  
**99 SM SERVICE MASTER TOOL KIT**



**ECONO-LAMP**

#ETD-29



Model XL-334A

Our Price

**\$14<sup>75</sup>**

**MAGNIFIER LAMP**

Model LUX-2A

Our Price

**\$29<sup>95</sup>**



#ETD-30

**WABER GROUNDED OUTLET STRIPS**

- #207 BC - 6 outlets • circuit breaker
- on/off switch
- pilot light

**\$24<sup>95</sup> each**

#ETD-31

#101AC - 4 outlet version of 207BC



#ETD-32

**\$14<sup>95</sup>**

**LCD 3 1/2 DIGIT DMM**

Model 30B-140

**\$39<sup>95</sup>**

#ETD-33

- 0.5" LCD display
- DC input impedance 13MΩ
- DC 100 V, 100 mA, 0.1 ohm resolution
- DCA up to 10A
- Auto polarity




**6.5 MHz LABORATORY OSCILLOSCOPE**

1 year warranty — Very popular

**\$174<sup>95</sup>**

#ETD-12

Mode 31B-430

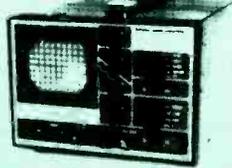

**JERROLD 60 CHANNEL CORDLESS TV CONVERTER**

MODEL DRX-3-105

#ETD-10

Call For Quantity Prices

**\$110<sup>00</sup> ea.**



**BK PRECISION DYNASCAN CORPORATION** Model 1476

**10 MHz**

dual trace  
10mV/div  
sensitivity  
video sync  
separators  
includes  
probes



#ETD-17

**\$435<sup>00</sup>**

Reg. \$545<sup>00</sup>

**EICO 20 MHz DUAL TRACE SCOPE** Model 482

Reg. \$799<sup>95</sup>


Our Price

**\$450.00 each**
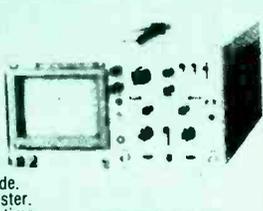
#ETD-19

Features:

- Dual Trace
- 5 mV/cm
- 5 mV/cm sensitivity.
- Automatic triggering.
- Add and subtract mode.
- Built in component tester.
- 1.5 nanosecond rise time.
- Includes 10:1/direct probes.
- Automatic selection of alternate or chop mode.



**SPECIAL!**

**BK PRECISION DYNASCAN CORPORATION** Model 1479B

**30 MHz**

#ETD-16

dual trace  
5mV/div  
sensitivity  
10:1/reference/  
direct probes  
included



**\$635<sup>00</sup>**

REG. \$795<sup>00</sup>

# OMNITRON

**ELECTRONICS**  
770 Amsterdam Ave., New York, NY 10025

Write for FREE 112 page Catalog

Send Purchase Order, Check, Money Order or C.O.D.

## SHIPPING CHARGES

For Orders	ADD
\$25-100	\$6.50
\$100 - \$500	\$8.50
\$500 - \$750	\$10.50
\$750 - and up	\$15.00

PARCEL POST...\$20.00


**or Call Toll Free 800-223-0826**

in NY STATE (212) 865-5580

MASTER CARD • VISA


Circle (12) on Reply Card

There are several strategies for overcoming contact bounce. If a keyboard encoder IC is used, a capacitor will fill the function (see

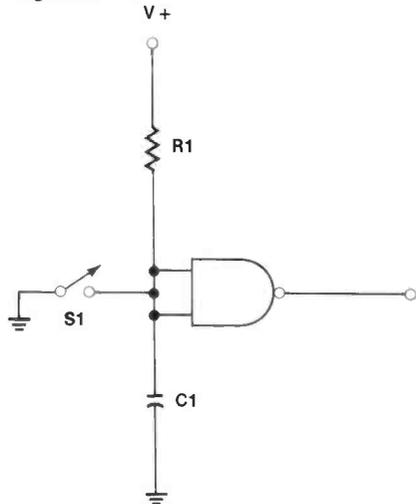


**Figure 5a.** One method of "debouncing" keyboard inputs is to use a Schmitt trigger or CMOS inverter and an RC network.

Figure 1). In other cases, such as Figure 3, the switch interfaces directly to a port, so the computer program must do the debouncing. In those machines, the keyboard input or scanning program will contain a time delay loop that

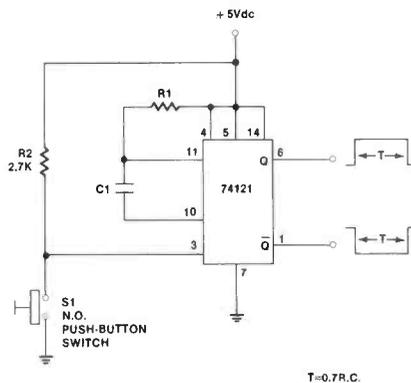

**Figure 5b.** The 74121 IC monostable multivibrator produces a single pulse of period  $T = 0.7RC$  when a negative-going pulse is applied to pin 3.

reads the port data 5 to 10ms after the port is turned on. The delay gives the contact bounce enough time to die out. Another technique uses circuits such as those in Fig-

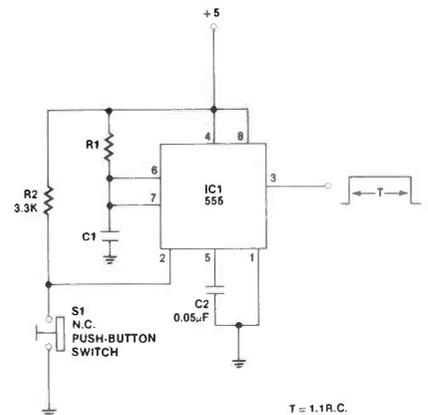

**Figure 5c.** A 555 Timer IC is another way to provide a stable output pulse even if the input "bounces."  
*(continued on page 44)*



**Service more than 95 RCA and other brand models with these VCR Parts Kits:**

199094 and 199095 Belt Kits, 199096 Lamp Kit, 199097 Fuse Kit, 199300 IC Kit

# One source for thousands of VCR parts.

RCA VCR parts are available from more than 600 authorized RCA parts distributors. See your local RCA distributor for RCA's new VCR parts kits — they're easy to use and reuse. Each package has a handy slide top — and features detailed cross-references to other manufacturers' model numbers and stock numbers.

One more thing. Kit prices are lower than the total cost of the individual parts. So see your RCA distributor today. Also ask for a copy of the VCR Parts Cross Reference of more than 8000 VCR parts (Form 1F6627) and VCR Tool Catalog (Form 1F6857). Or write: RCA Distributor and Special Products Division, 2000 Clements Bridge Road, Deptford, NJ 08096.

# RCA VCR Parts


For more proficient color TV servicing,  
in-home and on the bench . . .


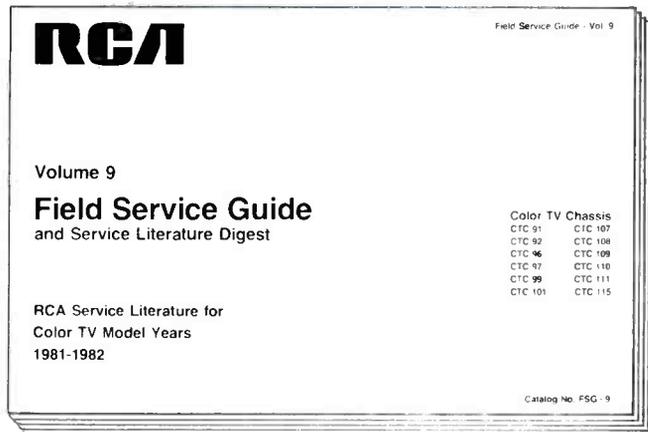
## Field Service Guide and Service Literature Digest

Up-to-date service information compiled from regular RCA color TV service literature . . . in convenient, easy-to-use 17" x 11" volumes that each cover two years of RCA color TV models . . . designed especially for in-home servicing but equally useful as handy bench references . . . featuring:

- Complete chassis and tuning system schematics
- Chassis circuit board illustrations
- Disassembly/reassembly instructions
- Comprehensive parts lists
- Tables of common trouble symptoms and typical causes
- *Quick-Find Indexes* and cross references



### VOLUME 9 NOW AVAILABLE!

This latest addition to RCA's popular series of service literature digests covers model years 1981-1982 and RCA color TV chassis CTC91, 92, 96, 97, 99, 101, 107, 108, 109, 110, 111, 115 . . . 520 pages, 17" x 11", saddlestitched . . . **ONLY \$14.95**

### VOLUME 8 STILL AVAILABLE

Covers model years 1979-1980 and RCA color TV chassis CTC 85, 86, 87, 88, 89, 90, 91, 92, 93, 96, 97, 99, 101 . . . 424 pages, 17" x 11", saddlestitched . . . **ONLY \$12.95**

### SPECIAL LIMITED-TIME TWO-VOLUME OFFER!

Save \$5.40 . . . Volume 8 and 9 together cover four years of RCA color TV models . . . Order now and receive both volumes for only \$22.50.

#### RCA Field Service Guide Order Form

Check appropriate boxes, indicate quantities & prices, enclose check payable to "RCA Consumer Electronics"

MAIL TO: RCA TECHNICAL PUBLICATIONS 1-450  
P.O. Box 1976  
Indianapolis, IN 46206



#### FIELD SERVICE GUIDES

- VOLUME 9  
 VOLUME 8  
 TWO-VOLUME SPECIAL OFFER (VOLS. 8 & 9)

#### PRICE

\$14.95 ea.  
 \$12.95 ea.  
 \$22.50 ea.

#### QUANTITY

\_\_\_\_\_  
 \_\_\_\_\_  
 \_\_\_\_\_

#### PRICE TOTAL

\_\_\_\_\_  
 \_\_\_\_\_  
 \_\_\_\_\_

(PLEASE PRINT)

NAME \_\_\_\_\_ TOTAL (AMOUNT OF YOUR CHECK) \_\_\_\_\_

STREET ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

EST 983

# SOLTEC® OSCILLOSCOPES


Model No.	Description	Price
5100	100 MHz, Quad Trace, Portable	\$1,995.00
560	60 MHz, Triple-Trace, Portable	1,695.00
540P	40 MHz, Triple-Trace, Portable	1,295.00
540D	40 MHz, Triple-Trace, Desk Top	1,295.00
540M	40 MHz, Triple-Trace with Built-in DMM, Portable	1,995.00
540C	40 MHz, Triple-Trace with Built-in Counter/Timer, Portable	1,995.00
530	30 MHz, Dual-Trace, Portable	895.00
520	20 MHz, Dual-Trace, Portable	695.00
515-2	15 MHz, Dual-Trace, Portable	595.00
515-1	15 MHz, Single-Trace, Portable	495.00
512-2	12 MHz, Dual-Trace, Portable	545.00
512-1	12 MHz, Single-Trace, Portable	445.00

## CALL NOW

for the name of the distributor in your area and a color catalog with full details TOLL FREE

**800 - 423-2344**

MODEL 5100

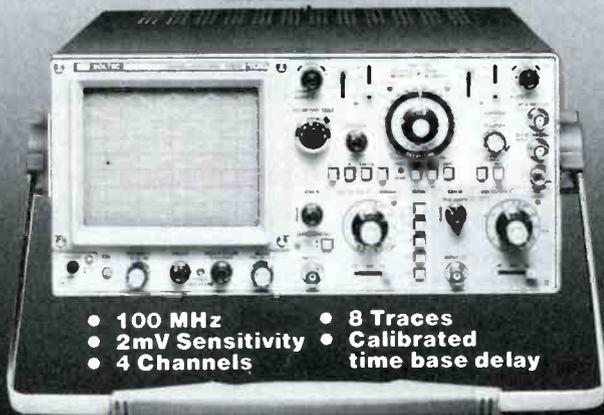

- 100 MHz
- 2mV Sensitivity
- 4 Channels
- 8 Traces
- Calibrated time base delay

No other manufacturer offers comparable quality, design features and proven performance in a 100 MHz Scope at this price. Let us prove it to you!

Two Probes Included

**NOW 100 MHz**  
**\$1,995.00!**

- 1500 hrs. MTBF
- Glass epoxy circuit boards
- 2 year warranty on all parts and labor

**SOLTEC®**  
**CORPORATION**

11684 Pendleton Street  
Sun Valley, California 91352  
213 - 767-0044

Circle (13) on Reply Card

## Readers' Exchange

**Needed:** Schematic, manual or operating instructions for Fairchild frequency meter (counter) model 8220 or same product made by Systron Donner. Will pay expenses or reasonable cost. *Phillip Clay, 5533 Roanoke, Kalamazoo, MI 49002.*

**Needed:** Sencore LC-53 Z-meter. Please contact with condition and price. *Robert Query, 6346 King Louis Drive, Alexandria, VA 22312; 1-703-354-3721 after 4:30 p.m.*

**Needed:** Schematic for a TV set from Canada, Fleetwood chassis no. CTS 1965. *Joseph J. Eberhardt, D7 Hans Brinker Street, Box 354, Windmill Village, North Ft. Myers, FL 33903.*

**Needed:** Pilot TV picture tube #3KP4 (circa 1949 3-inch CRT). *John Miller, 3704 Bold Bidder Drive, Lexington, KY 40502.*

**Needed:** Schematic with transistor part numbers for Woodson model W190-8 PA system. *B&L TV, 7331 Highway 90 W., San Antonio, TX 78227.*

**Needed:** Sony color CRT 470KXB22, Escutcheon (front panel) for Sony color KV-1743R, Escutcheon for b/w Panasonic TR-579. Send price by post card. Need SAMS 1225, 1273, 1335, 1371, 1382, 1392, 1497, 1505, 1509, 1522, 1681, 1723, 1742, 1881 and 1902. Will pay \$3.50 each. *Frederick Jones, 407 Morningbird Court, Niceville, FL 32578.*

**Needed:** Back issues of **Electronic Servicing & Technology** from January 1979 through December 1982. Will pay reasonable price. *John Ruiz, 624 Hester Ave., River Ridge, LA 70123; 1-504-737-8374.*

**Needed:** Sams Photofact TR682 and Tekfax Vol. 101-105. *C.T. Huth, 146 Schonhardt St., Tiffin, OH 44883.*

**Needed:** Sencore VA48 TV analyzer or B&K model 1250 NTSC color bar generator. *Kenneth Selby, KDS Sales, 4124 E. Stanley Road, Mt. Morris, MI 48458.*

**Needed:** Schematic for Sears television, model 562, 40090301. *Barney Lonzo, P.O. Box 112-C15716, Joliet, IL 60434.*

**Needed:** Original owner's manual and service manual for a Halicrafters model SX-62 radio receiver. *Paul Capito, 637 W. 21st St., Erie, PA 16502.*

**Needed:** Power transformer for Sansui model 800 stereo receiver. *Fleming's TV, Box 647, Rome, NY 13440; 1-315-337-3340.*

**Needed:** Schematic and parts list for Philharmonic stereo grand electronic accordion. Willing to pay cost and shipping. Picture tube #25AP22A Hi Lite in good condition. Call or write stating price and condition. *John Iannelli, 1501 Saunders Crescent, Ann Arbor, MI 48103; 1-313-662-9623.*

**Needed:** Wiring diagram and schematic for Fisher Radio model E-48 AM/FM radio and record player. *John A. Kappral, 101 Newberry Circle, Oak Ridge, TN 37830; 1-615-432-1487.*

**Needed:** Service or operator's manuals and schematics for Heathkit model TS-4A sweep generator, Data Tech model 30R DMM, and Imperial (German) Carri model stereo, chassis 609. *Leon Thornton, 38 Sheridan St., Ft. Rucker, AL 36862.*

**Needed:** Circuit print of a Blaupunkt model Typ 40323 radio, Ser. B250C150. *John Buchanan, 2065 Virginia, Detroit, MI 48206.*

**Needed:** Deflection yoke Triad-Utrad 80-85-4C or its substitute Thordarson 4-109, Triad 4C-312-2 or Stancor DY-95AC. *Edward Harrigan, 5165 S. Magellan Drive, New Berlin, WI 53151.*

**Needed:** Extra accessories/attachments for Don Bosco stethotracer test instrument. Also need a good electrolytic-capacitor checker. *Murray's Repair Service, 8842 Grange Hill Road, Sauquoit, NY 13456; 1-315-737-7192.*

**Needed:** Zenith #95-3312 Power transformer. *WSEP, 318 S.K. St., Sparta, WI 54656; 1-608-269-2392.*

**For sale:** Computer Measurements Corp. model 616A frequency counter and 1400MHz 630 heterodyne converter, \$300 or will consider Collins 51J-3,4 in trade. *Walter Schwartz, Lakewood Drive, Rt. 1, Box 109C, Jefferson City, TN 37760; 1-615-475-8220.*

**For sale:** Early radio and TV tubes; send SASE for list. Also radio and TV prints for sets manufactured since 1946, \$4.95 postpaid. *Don Maurer, 29 S. 4th St., Lebanon, PA 17042.*

**For sale:** Approximately 200 Sams from 590-1000 (most numbers past 750); \$1 each plus shipping. *Ezra's Electronic Service, Route 2, Box 725, Eureka Springs, AR 72632.*

**For sale:** Nikoltronix CB analyzer, model GN-1375; 23 channels with added channel 22A and B; can be updated to 40 channels. All probes, cables, NiCd batteries and instruction manual included. *Fred's Electronic Serv., 1203 Corties Ave., Neptune, NJ 07753; 1-201-988-8841.*

**For sale: Electronic Servicing, 1968-1980, \$75 plus shipping; Sencore TF-151 \$150; Mercury model 801 CRT tester reactivator, \$50. Paul S. Funk, 607 E. Cherry Lane, Souderton, PA 18964; 1-215-725-2855.**

**For sale:** Sencore SG 165 AM/FM stereo analyzer. Also most of Sams Photofacts from 374-713 and Philco model 48-2500 projection TV screen. Will accept reasonable offer. *E & J Radio & TV, 211 River Ave., Holland, MI 49423; 1-616-392-2291.*

**For sale:** Sencore SG 165 stereo analyzer, \$475; Leader LCG-396 NTSC generator, \$550; Hewlett-Packard 209A sine/square oscillator, \$475. All in mint condition with leads and manuals. *Great Northern Video, 133 Loudon Road, Concord, NJ 03301; 1-608-228-0412.*

**For sale:** Hewlett-Packard model 1703A portable lab storage oscilloscope. Dual-trace sensitivities of 10MV/div to 5V, main and delayed sweep, \$2300. *Hinton TV & Video, 5130 E. Charleston Blvd., Las Vegas, NV 89122; 1-702-459-2108 (call collect).*

**For sale:** Sencore PS163 dual-trace triggered scope; excellent condition with two probes and manual; \$575. *Frank J. Wojcik, 33 Hughes St., Maplewood, NJ 07040.*

**For sale:** Sencore CB servicing system (CB41 and CB42 with manual), \$750. *Andy Chan, 9 Corylus Court, Rexdale, Ontario, Canada; 1-416-675-7985.*

**For sale:** Dencron model MLA-2500 linear amplifier, \$600; RCA model WV-38A VOM, including high-voltage probe, \$45; Leader Electronics model LTC-905 transistor curve tracer, \$100. *William Sheutchuk, 1 Lois Ave., Clifton, NJ 07014; 1-201-471-3798.*

**For sale:** Large inventory of car radio parts dated back to Packard and Kaiser Fraizer; new and rebuilt car radio back to 1949. Catalog available. *Gorski TV-Radio, RD No. 7, Box 655, Flemington, NJ 08822.*

**For sale:** Complete electronics shop of Sencore test equipment, with accessories, manuals, parts modules and schematics. Send for list. *N.E. Downer, 1710 Santa Fe Terrace, Atchison, KS 66002.*

**For sale:** Leader LCO SO8A 20MHz, dual-trace, triggered oscilloscope, \$299; RCA (or VIZ) WV-98C senior volt/ohmmeter, \$99; Zenith 852-241 50MHz frequency counter, digital readout, \$125. *Terrick TV, 809 Amity St., Homestead, PA 15120; 1-412-462-8720.*

**For sale:** Sams Photofacts, 22 through 976; 799 complete folders in all (some duplicates). Will sell to highest bidder; shipping to be paid by buyer. *Ron Brault, RR #6, 5703 Poplar Road, Fond Du Lac, WI 54935; 1-414-922-2351.*

**For sale:** Sencore Super Mack CRT checker (CR31) with 15 sockets. \$250; Lafayette HA-600A 5-band shortwave RCUR, \$40. *David Marley, 134 Diller Road, New Cumberland, PA 17070.*

**For sale:** Sams auto-radio manuals AR-18 to AR-255. *Myers TV, 109 S.E. 2 St., Delray Beach, FL 33444; 1-305-276-5782.*

**For sale:** Sams Photofacts in intermittent sequence from 1 through 791 (total of 191 folders); \$150 plus postage. Send SASE for complete listing. *Theodore S. Kruppa, 210 Weeks Drive, Camden, WY 19934.*


**For sale:** Eico model 342 FM stereo multiplex generator with manual and schematic, \$60; Heathkit model 1M22 audio analyzer with manual and schematic, \$50; Sencore FP201=10kV focus probe and 39G89=50kV extender probe used on YF33 ringer, \$25. *Long's TV Service, 720 Goshen St., Salt Lake City, UT 84104; 1-801-539-8093.*

**For sale:** B&K TV analyst, model 1077B, \$325; good condition with manual. *Hoyt Smith, 6802 Star Drive, Austin, TX 78745; 1-512-441-8355.*

**For Sale:** Sencore SG-165 AM/FM stereo analyzer; like new with all manuals, \$450. *Paul Omlor, POES, 1801 Brooks, Missoula, MT 59801; 1-406-728-3022.*

**For sale:** Sencore FC-51 1GHz frequency counter, \$600; B&K 1477P dual-trace scope, \$500; B&K model 970 transistor analyzer and auto power supply, \$225. *George Lazoryszak, George's TV, 4432 N. Chadwick St., Philadelphia, PA 19140.*

**ES&T**

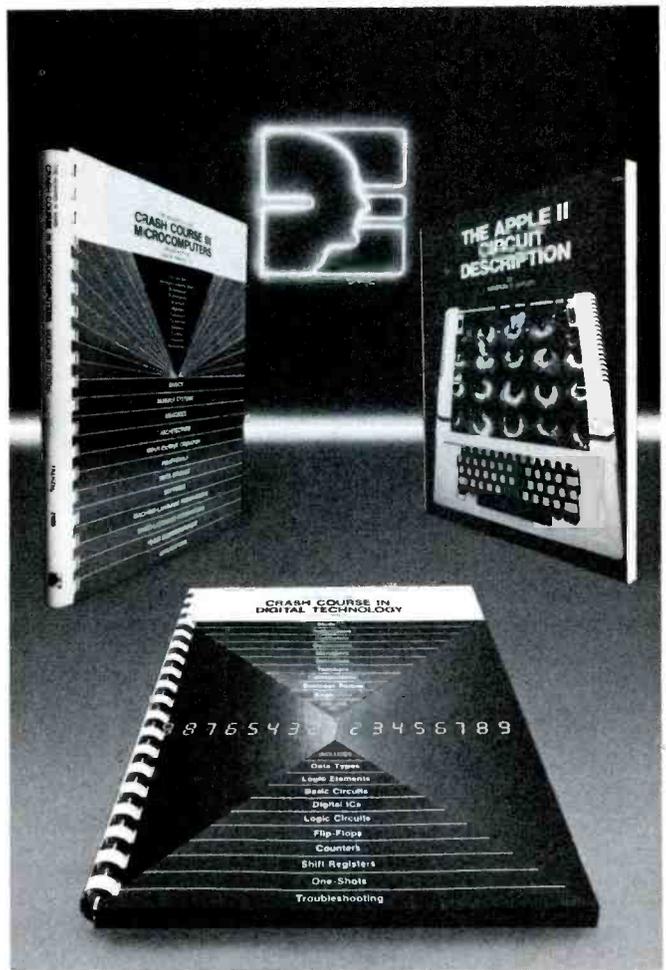

## SAMS COMPUTER UPDATE.

Here's news for computer technicians. Sams library of computer books can help you keep up-to-date on the latest in computer servicing and technology. Some recent examples are:

THE APPLE II® CIRCUIT DESCRIPTION which provides a detailed circuit description of all Apple II motherboards. No. 21959, \$22.95.

CRASH COURSE IN DIGITAL TECHNOLOGY is the fastest way to learn about digitals on the market today. It covers all the necessary fundamentals, components, ICs, and techniques of digital technology. No. 21845, \$19.95.

CRASH COURSE IN MICROCOMPUTERS (2nd Edition) is an outstanding book for anyone who needs to learn fast about microcomputers and programming. This new edition of one of Sams best-sellers has new chapters on 16-bit microcomputing, BASIC programming, photos, an expanded applications chapter on software, and more. No. 21985, \$21.95.

**To order these Sams Books, contact your local electronics distributor. Or call 800-428-3696 or 317-298-5566 and ask for Operator 420.**

### SAMS BOOKS AND SOFTWARE

HOWARD W. SAMS & CO., INC.  
4300 West 62nd Street • P.O. Box 7092  
Indianapolis, IN 46206


Offer good in USA only and expires 1/31/84. Prices subject to change without notice. In Canada, contact Lenbrook Electronics, Markham, Ontario L3R 1H2.

Apple and Apple II are registered trademarks of Apple Computer, Inc.

AD420

Circle (14) on Reply Card

# INTRODUCING

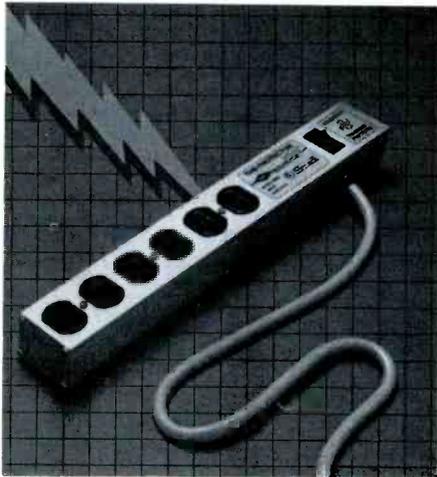

## THE PROTECTOR 6000™

### TOTAL PROTECTION FOR YOUR SENSITIVE ELECTRONIC EQUIPMENT.

Something that you can't even see may be slowly but surely killing your expensive electronic equipment. It's transient voltage, and it can be fatal to computers, medical equipment, electronic games, videotape recorders, electronic test equipment, electronic cash registers — almost any of today's sophisticated solid state equipment.

### THE TRANSIENT VOLTAGE PROBLEM.

Most of this modern electronic equipment uses LSI and MOS semiconductor devices which are extremely sensitive to voltage transient surges or "glitches." In fact, a large percentage of equipment failures can be directly linked to the damaging effects of over-voltage line transients to unprotected, highly fragile components.

### THE PROTECTOR 6000™ SOLUTION.

Not to be confused with other transient voltage protection units available today, THE PROTECTOR 6000 uses state-of-the-art solid state components and exclusive circuitry to provide you with complete and total protection from transient voltage surges of up to 6,000 volts. THE PROTECTOR 6000 uses silicon PN junction devices — proven to provide the fastest response to surges! They have a statistical life expectancy of over 20 years. THE PROTECTOR 6000 has a maximum clamping voltage of only 335 volts, well below the voltage rating of other transient protection devices which commonly use much less effective MOV's or gas discharge tubes. It also provides full protection from electro-magnetic and radio frequency interference. The unit operates in both common and differential modes, and is outfitted with a circuit breaker to guard against severe current overloads over 15 amps.

Why take chances with your expensive electronic equipment? For full details contact your local NTE distributor or write:



**NEW-TONE ELECTRONICS, INC.**  
44 Farrand St., Bloomfield, NJ 07003  
**THE PEOPLE WHO BRING YOU THE TCG LINE OF SEMICONDUCTORS.**

© 1983 New-Tone Electronics, Inc.

# Photofact

## HITACHI

CT1929 ..... 2185-1  
CT2526/28 ..... 2186-1

## JC PENNEY

685-1036,A,-00,-10 ..... 2180-1

## JVC

7690US, 7790US, 7890US, 7990US ..... 2186-2

## PHILCO

Chassis UWA ..... 2184-1  
B451PWA ..... 2185-2

## RCA

Chassis CTC118A ..... 2184-2

## SANYO

61T64,A ..... 2182-1

## SEARS

564.49950250/52 ..... 2182-2  
564.43200250/3200251/3300250/3300251/  
3400250/3400251/3500250/3500251 ..... 2185-3

## OPTIMA ELECTRONICS

TO ORDER CALL TOLL FREE 1-800-327-0224

G.E., SYLVANIA, ZENITH, RCA, 75% OFF LIST NEW-BOXED

- |                               |               |                               |               |
|-------------------------------|---------------|-------------------------------|---------------|
| <input type="checkbox"/> 3A3  | 5 FOR \$15.75 | <input type="checkbox"/> 6LF6 | 5 FOR \$34.44 |
| <input type="checkbox"/> 6MJ6 | 5 FOR \$34.88 | <input type="checkbox"/> 6LB6 | 5 FOR \$31.50 |
| <input type="checkbox"/> 6JE6 | 5 FOR \$32.75 | <input type="checkbox"/> 6CJ3 | 5 FOR \$14.69 |
| <input type="checkbox"/> 3DJ3 | 5 FOR \$17.44 | <input type="checkbox"/> 6JS6 | 5 FOR \$29.00 |
| <input type="checkbox"/> 6GH8 | 5 FOR \$12.44 | <input type="checkbox"/> 6BL8 | 5 FOR \$12.25 |

All Tubes Not Advertised, Write in at 75% Off List.

Sleeves Only: Singles 72% Off List

### HORIZONTAL OUTPUT TRANSISTORS

- |                                    |  |  |
|------------------------------------|--|--|
| \$1.95 ea. Min. 10, 2 yr. Warranty | <input type="checkbox"/> 500A .. \$11.95 | <input type="checkbox"/> 526A .. \$14.95 |
| <input type="checkbox"/> RKS1172B  | <input type="checkbox"/> RKS238          | <input type="checkbox"/> 522 .. \$11.95  |
| <input type="checkbox"/> RKS1308K  | <input type="checkbox"/> RKS165          | <input type="checkbox"/> 523 .. \$13.95  |
|                                    |  | <input type="checkbox"/> 539 .. \$15.75  |

### TRANSISTORS & I.C.'s...MIN. 10, CAN MIX

- | T.V. #'s                                   | Pop. I.C. #'s                          | STEREO #'s                                   |
|--|--|--|
| <input type="checkbox"/> 2SC1114 .. \$3.75 | <input type="checkbox"/> 712 .. \$1.40 | <input type="checkbox"/> DM133 .. \$5.95     |
| <input type="checkbox"/> MN8303 .. \$3.95  | <input type="checkbox"/> 713 .. \$1.40 | <input type="checkbox"/> DA101 .. \$5.75     |
| <input type="checkbox"/> 2SC1034 .. \$5.95 | <input type="checkbox"/> 714 .. \$1.50 | <input type="checkbox"/> HA1377A .. \$3.25   |
| <input type="checkbox"/> 2SC867A .. \$3.50 | <input type="checkbox"/> 731 .. \$1.50 | <input type="checkbox"/> HA1388 .. \$5.25    |
| <input type="checkbox"/> 2SD870 .. \$4.75  | <input type="checkbox"/> 790 .. \$1.50 | <input type="checkbox"/> HA1396 .. \$5.50    |
| <input type="checkbox"/> 2SD871 .. \$5.50  | <input type="checkbox"/> 791 .. \$1.95 | <input type="checkbox"/> HA1398 .. \$4.95    |
| <input type="checkbox"/> AN5210 .. \$6.50  | <input type="checkbox"/> 792 .. \$2.00 | <input type="checkbox"/> UPC1181 .. \$1.25   |
| <input type="checkbox"/> AN5310 .. \$3.95  | <input type="checkbox"/> 793 .. \$2.00 | <input type="checkbox"/> UPC1182 .. \$1.25   |
| <input type="checkbox"/> AN5320 .. \$3.25  | <input type="checkbox"/> 819 .. \$1.50 | <input type="checkbox"/> UPC1185H .. \$2.95  |
| <input type="checkbox"/> AN5435 .. \$2.95  | <input type="checkbox"/> 820 .. \$2.00 | <input type="checkbox"/> UPC1367 .. \$3.25   |
| <input type="checkbox"/> LM1818 .. \$3.25  | <input type="checkbox"/> 821 .. \$2.25 | <input type="checkbox"/> UPC1368H2 .. \$3.95 |

### GENERAL

- |  |                |
|--|----------------|
| <input type="checkbox"/> Exact Rep. for SG613                  | 5 for \$30.00  |
| <input type="checkbox"/> Pop. HI DIV-3...focus block divider   | 10 for \$35.00 |
| <input type="checkbox"/> 6 ft. Cheater Cords SPT2              | 10 for \$ 7.95 |
| (Heavy Duty - UL App. 7 Amp. 125V. P & NP)                     |                |
| <input type="checkbox"/> Matching Transformers 75-300 ohm      | 30 for \$10.50 |
| <input type="checkbox"/> BSR Changers                          | 33.95          |
| <input type="checkbox"/> Replacement Tone Arms (mono & stereo) | 5 for \$6.00   |
| <b>ATARI GAME CHIPS:</b>                                       |                |
| <input type="checkbox"/> Voltage Regulator                     | \$ .95         |
| <input type="checkbox"/> CPU                                   | \$ 4.95        |
| <input type="checkbox"/> RAM/I/O                               | \$ 6.50        |

### Quantity Prices Available

Letters of credit and all checks placed on deposit with Bank of Hallendale, FL. VISA & Master Charge accepted. Min. order \$75. FOB Dania, FL. Catalog \$3, refundable upon order.

## SEND CHECK OR MONEY ORDER TO: OPTIMA ELECTRONICS

2022 Tigertail Blvd., Dania, FL 33004

Phone (305) 920-3550 TOLL FREE: 1-800-327-0224

Circle (33) on Reply Card

# We've got some great names up our sleeve.



CONSUMER  
ELECTRONICS  
CORP.

## PRODUCT SERVICES ORGANIZATION



**MAGNAVOX**  
**ODYSSEY**  
**PHILCO**  
**SYLVANIA**  
AUDIO • VIDEO

A North American Philips Company

### **SUCCESSFUL SERVICE SELLERS**

The Product Service Organization—always ready to support the brands with factory authorized parts, training seminars, technical materials and everything in-between.

**N.A.P. Service Parts** supports servicers thru a nationwide network of regional parts depots and local parts distributors.

**N.A.P. Field Services** supports servicers with specialized training, consumer affairs, and field engineers.

**N.A.P. Technical Services** provides technical training programs, service manuals, schematics and technical service tips.

**N.A.P. Product Services**  
P.O. Box 555, Dept. 741  
Jefferson City, TN 37760

1-615-475-3801, Ext. 7348  
Circle (16) on Reply Card

(Continued from page 22)

ure 5 to clean up the problem. All three techniques are monostable multivibrators.

The circuit in Figure 5A uses a Schmitt trigger or a CMOS inverter (or inverter-wired gate) and an RC network. In the normal condition (*low* output), switch S1 is open so that capacitor C1 will be charged to V+ (usually +5Vdc). Closing S1 causes C1 to become discharged. In this discharged state, the input sees a *low*, so the output will be *high*. The output remains *high* for a period, T, which is the time required for C1 to charge to what the IC sees as *high*.

Two other monostable multivibrators are shown in Figures 5B and 5C. Both are IC versions. The circuit in Figure 5B is the TTL 74121 device. This device produces a single pulse of period  $T = 0.7RC_1$  every time a negative-going trigger pulse is received on pin 3. This trigger input normally is held *high* by resistor R2 and is dropped *low* when switch S1 is closed.

The circuit in Figure 5C uses the 555 IC timer chip for the same purpose. A 555 is TTL compatible if the V+ voltage applied to pins 4 and 8 is +5Vdc. If some CMOS device is being addressed by the pulse and uses a V+ greater than +5Vdc, then this circuit still can be used. The 555 operates to +18Vdc.

### Testing a keyboard

From a troubleshooting perspective, it is necessary to know whether a keyboard is producing the correct code and whether the strobe, if used, is present. The key to troubleshooting without using a logic analyzer is to use a device or instrument that will indicate whether a point is *high* or *low*. A bench oscilloscope that is decoupled can do this. Vary the position and vertical sensitivity/deflection controls so that the trace is near the bottom of the screen for *low* conditions and near the top for *high* conditions. The strobe signal used on many keyboards

may have a fast rise time and short duration. This combination makes the strobe hard to see on some oscilloscopes. Many logic probes, however, have a "pulse catcher" circuit that will latch and turn on a light when the strobe pulse occurs.

A *high/low* indicator can be built using an open-collector TTL inverter, an LED and a resistor (see Figure 6). When the level applied to the input probe is *low*, then the inverter output is *high* so the LED is off. If the input is *high*, the output is *low*, turning the LED on.

One can build an 8-bit state monitor using this circuit. Inverters come in groups of six, so two hex inverter packages will make an 8-bit monitor with four inverter sections left over.

If a keyboard has only switches across an input port, then the criteria in troubleshooting is de-

termining whether each bit is appropriately *high* or *low*. If the keyboard is ASCII-encoded, the *high/low* status of all seven lines must be examined to determine whether the correct ASCII code is present.

### Displays

For a terminal or keyboard to interact with a user, there must be some form of display device. The display may be a CRT video terminal, 7-segment numerical display device or an LED indicator lamp that turns on when certain conditions occur.

Figure 7 shows how an LED indicator is interfaced to a computer I/O port. The LED will draw 10 to 20mA, so it cannot be directly driven by the output port bit. Instead, a higher current TTL inverter-with-open-collector-output is used. If the state of output bit

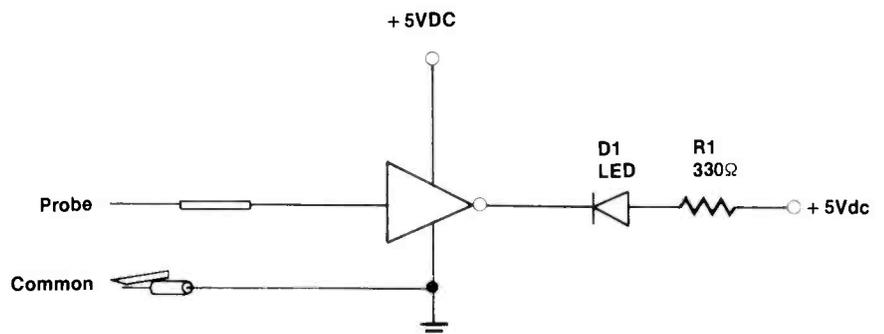


Figure 6. The LED on the *high/low* indicator remains off when a low state is sensed, and turns on when a high state is sensed.

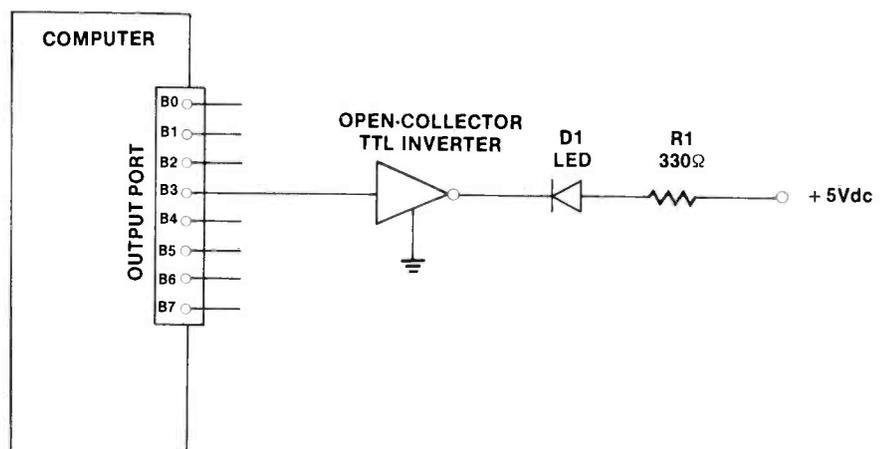


Figure 7. The LED indicator is interfaced to the I/O port through the TTL inverter.

# New LM-4. The 40-Channel Logic Monitor you hold in your hand.

Now, there's a unique new way to speed and simplify your work with complex digital circuits. By simultaneously monitoring up to 40 points in a logic system with a compact, easy-to-use instrument that's faster than a scope and safer than a voltmeter. Our new multi-family LM-4. At \$199.00,\* it's one of the best buys in logic today!

Simply slip its 40-pin IC test clip over your CMOS or TTL ROM, RAM, microprocessor or MSI/LSI chip and instantly see the logic state of each pin on a big, easy-to-read liquid crystal display.

But that's only the beginning. You can wire the LM-4 into a computer bus; fit it with two 16-pin test clips or sockets for comparing known good and questionable ICs; use it as a clip-on display for micros, minis and other computers during design, setup, testing, troubleshooting... there's no limit to the ways LM-4 can save you time and money!

Measuring just 5.9 x 3.2 x 1.2", the pocket-sized LM-4 comes with a 24" 40-conductor ribbon cable terminated in a 40-pin IC test clip, plus instructions/applications manual and high-impact carrying case. (An optional Universal Cable Kit is also available for special interfacing requirements, priced at \$75.00.\*)



So whatever the job—in design, production or service—simplify your testing with the power of 40-channel monitoring: Order your LM-4 today.

Call toll-free for details  
**1-800-243-6077**  
During business hours

## GLOBAL SPECIALTIES CORPORATION

70 Fulton Terr., New Haven, CT 06509 (203) 624-3103, TWX 710-465-1227.  
OTHER OFFICES: San Francisco (415) 648-0611, TWX 910-372-7992,  
Europe: Phone Saffron-Walden 0799-21682, TLX 817477,  
Canada: Len Finkler Ltd., Downsview, Ontario.

\* U.S. Resale only; price, specifications subject to change without notice.  
© Copyright 1981 Global Specialties Corporation.

Circle (17) on Reply Card



**TOLL FREE ORDERS • 1-800-826-5432**

(IN CALIFORNIA: 1-800-258-6666)

AK, HI OR INFORMATION • (213) 380-8000

**5 KEY ASSEMBLY**  
  
 \$1.00 EACH  
 CONTAINS 5 SINGLE-POLE NORMALLY OPEN SWITCHES. MEASURES 3 3/4" LONG.

**6 KEY ASSEMBLY**  
  
 \$1.25 EACH  
 CONTAINS 6 SINGLE-POLE NORMALLY OPEN SWITCHES. MEASURES 4 1/4" LONG.

**120V INDICATOR**  
  
 NEON INDICATOR RATED 120 V 1/3 W MOUNTS IN 5-16" HOLE. RED LENS.  
 75¢ EACH  
 10 FOR \$7.00  
 100 FOR \$65.00

**MINIATURE 6 VDC RELAY**  
  
 SUPER SMALL SPDT RELAY. GOLD COBALT CONTACTS.  
 RATED 1 AMP AT 30 VDC. HIGHLY SENSITIVE. TTL DIRECT DRIVE POSSIBLE. OPERATES FROM 4.3 TO 6 V. COIL RES. 220 OHM.  
 3.16" x 1.32" x 7/16"  
 AROMAT # RSD-6V  
 \$1.50 EACH  
 10 FOR \$13.50

**13 VDC RELAY**  
  
 CONTACT S.P.N.C. 10 AMP @ 120 VAC. ENERGIZE COIL TO OPEN CONTACT.  
 COIL 13 VDC 650 OHMS.  
 SPECIAL PRICE \$1.00 EACH

FREE SEND FOR NEW LARGER 48 PAGE CATALOG

**MINIATURE TOGGLE SWITCHES**  
 ALL ARE RATED 5 AMPS @ 125 VAC

<b>S.P.D.T. (on-on)</b>  P.C. STYLE NON-THREADED BUSHING 75¢ EACH 10 FOR \$7.00	<b>S.P.D.T. (on-on)</b>  SOLDER LUG TERMINALS \$1.00 EACH 10 FOR \$9.00 100 FOR \$80.00	<b>S.P.D.T. (on-off-on)</b>  SOLDER LUG TERMINALS \$1.00 EACH 10 FOR \$9.00 100 FOR \$80.00
<b>S.P.D.T. (on-off-on)</b>  NON-THREADED BUSHING P.C. STYLE 75¢ EACH 10 FOR \$7.00	<b>S.P.D.T. (on-on)</b>  P.C. LUGS THREADED BUSHING \$1.00 EACH 10 FOR \$9.00 100 FOR \$80.00	<b>D.P.D.T. (on-on)</b>  SOLDER LUG TERMINALS \$2.00 EACH 10 FOR \$19.00 100 FOR \$180.00

**ALL ELECTRONICS CORP.**  
 905 S. VERMONT • P.O. BOX 20406 • LOS ANGELES, CA 90006

- QUANTITIES LIMITED
- MINIMUM ORDER \$10.00
- USA \$2.50 SHIPPING NO C.O.D.
- FOREIGN ORDERS INCLUDE SUFFICIENT SHIPPING
- CALIF. RES. ADD 6 1/2%

Circle (18) on Reply Card

**TeleMatic**  
 PROFESSIONAL COLOR TV SERVICE EQUIPMENT  
 NOW AVAILABLE...



**SONY**  
 TEST JIG ADAPTERS  
 Yoke and Picture Tube for Popular Sets



**UPDATE KIT**  
 Modernizes any test jig  
 Model 10J107

WRITE FOR FREE CATALOG  
 Sold through distributors only  
**TeleMatic Div. of U.X.L. Corp.**  
 108-02 Otis Ave., Corona, NY 11368

Circle (19) on Reply Card

B3 is low, then the inverter output is high. Under this condition, both ends of the LED are at the same potential so no current flows—the LED is off. But when bit B3 is high, the LED will turn on. Under this condition, the output of the inverter is low, so the LED cathode is grounded and its anode is at +5Vdc. The resistor in series with the LED is used to limit the current to a safe value. Some CMOS inverters and buffers will drive one LED without the need for a

resistor. If the LED goes from the inverter to ground, it will light when the output is high. If the LED is connected between the inverter and V+, it will light when the output is low.

Figure 8 shows interfacing between a latched computer output port and a 7-segment numerical display. Each segment is an LED, so the display can be treated like an ordinary LED. An inverter and resistor are provided for each segment.

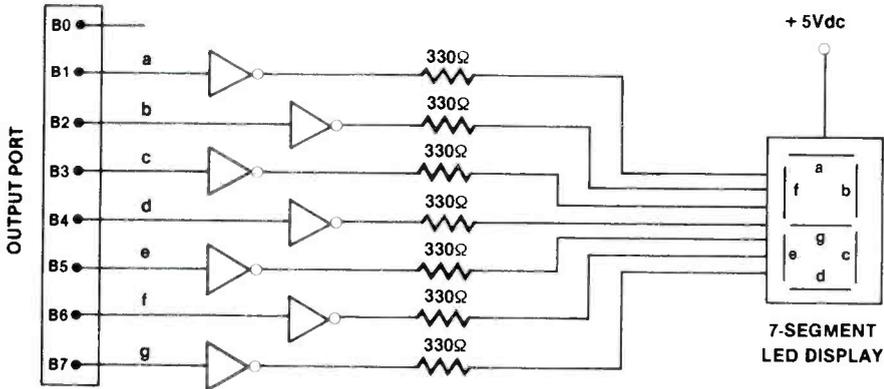


Figure 8. In the case of this latched computer output port, each output line is connected to the appropriate LED segment in the 7-segment display.


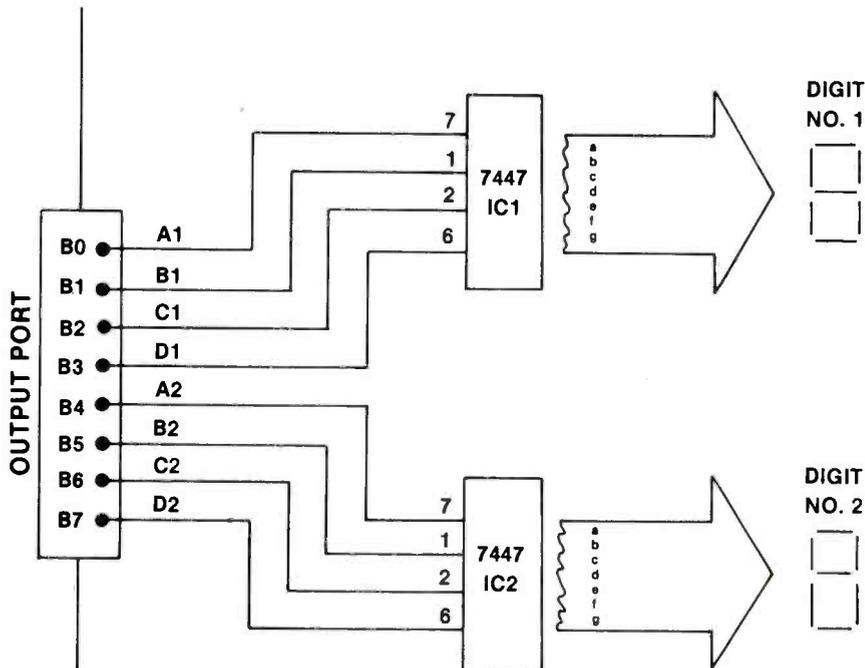


Figure 9. The BCD to 7-segment decoder converts 4-bit binary-coded-decimal number into signals to light the appropriate segments of 7-segment display.

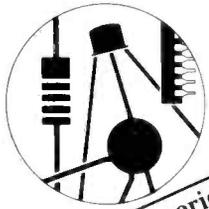

# The **ELECTRONICS BOOK CLUB**


18 years experience

Hundreds of time- and money-saving ideas for hobbyists, experimenters and technicians!

Select 6 fact-filled volumes for only **\$2<sup>95</sup>** (total value up to \$120.75)



1531  
List \$17.95

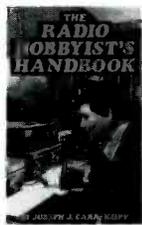

1346  
List \$19.95



1465  
List \$15.95



1497  
List \$15.95



1183  
List \$14.95




1393  
List \$19.95




1490  
List \$19.95




1406  
List \$19.95

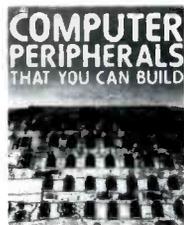


1449  
List \$19.95

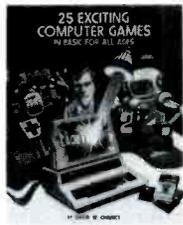

1427  
List \$21.95

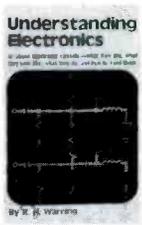

1113  
List \$11.95

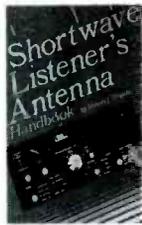

1487  
List \$15.95



1473  
List \$18.95



1271  
List \$18.95



1431  
List \$17.95



1225  
List \$16.95




1409  
List \$15.95



1305  
List \$15.95



1486  
List \$17.95

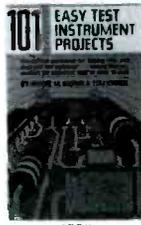

1339  
List \$13.95



1390  
List \$14.95



1050  
List \$13.95



1296  
List \$18.95




1218  
List \$17.95



1529  
List \$21.95



1451  
List \$18.95

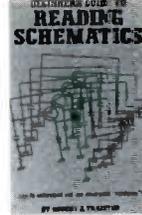


1536  
List \$13.95



1277  
List \$19.95



1128  
List \$12.95

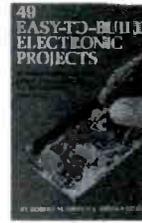

1337  
List \$9.95

## 7 very good reasons to try Electronics Book Club

Blue Ridge Summit, PA 17214

- **Reduced Member Prices.** Save 20% to 75% on books sure to increase your know-how
- **Satisfaction Guaranteed.** All books returnable within 10 days without obligation
- **Club News Bulletins.** All about current selections—mains, alternates, extras—plus bonus offers. Comes 13 times a year with dozens of up-to-the-minute titles you can pick from
- **"Automatic Order."** Do nothing, and the Main selection will be shipped automatically! But... if you want an Alternate selection—or no books at all—we'll follow the instructions you give on the reply form provided with every News Bulletin
- **Continuing Benefits.** Get a Dividend Certificate with every book purchased after fulfilling membership obligation, and qualify for discounts on many other volumes
- **Bonus Specials.** Take advantage of sales, special events, and added-value promotions
- **Exceptional Quality.** All books are first-rate publisher's editions, filled with useful, up-to-the-minute information



## ELECTRONICS BOOK CLUB

Blue Ridge Summit, PA 17214

Please accept my membership in Electronics Book Club and send the 6 volumes circled below, billing me \$2.95 plus shipping and handling charges. If not satisfied, I may return the book within ten days without obligation and have my membership cancelled. I agree to purchase 4 or more books at reduced Club prices (plus shipping/handling) during the next 12 months, and may resign any time thereafter.

1050 1113 1128 1183 1218 1225 1271  
1277 1296 1305 1306 1337 1339 1346 1390  
1393 1409 1427 1431 1449 1451 1465  
1473 1486 1487 1490 1497 1529 1531 1536

Name \_\_\_\_\_ Phone \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

Valid for new members only. (Orders outside U.S. or Canada must be prepaid in International Money Orders in U.S. dollars. Canada must remit in U.S. dollars.) This order subject to acceptance by The Electronics Book Club. EST-983

Circle (20) on Reply Card

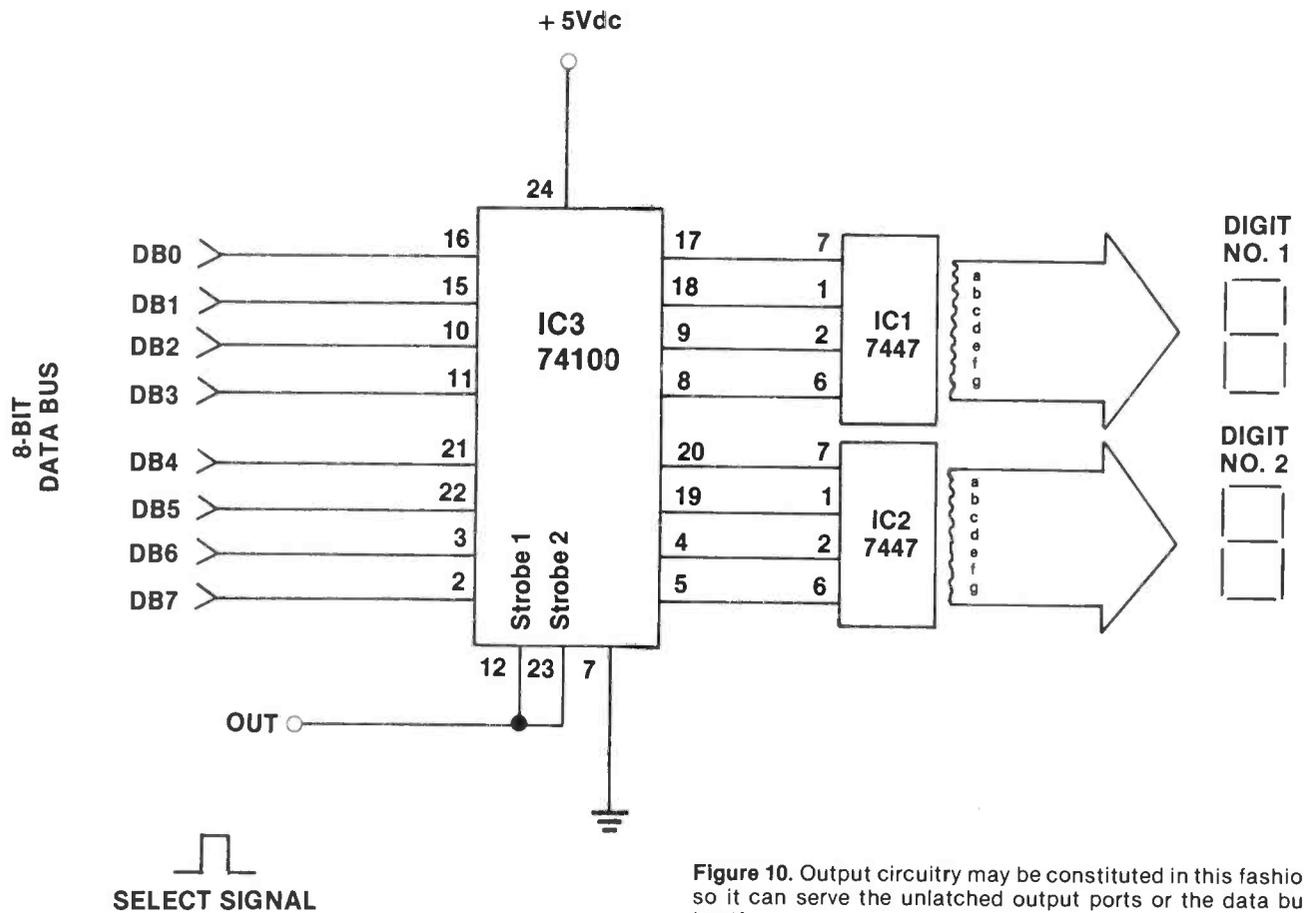


Figure 10. Output circuitry may be constituted in this fashion so it can serve the unlatched output ports or the data bus itself.

**PROFESSIONAL  
TECHNICIANS & SERVICEMEN**

WE CAN SUPPLY ALL THE COMPONENTS FOR YOUR  
MAINTENANCE, REPAIR & DESIGN WORK

REPLACEMENT FOR ECG® TYPES (Min. 5 pcs. each type)

TYPE NO.	YOUR PRICE	TYPE NO.	YOUR PRICE	TYPE NO.	YOUR PRICE
85	.30	152	.40	375	.99
123A	.25	153	.40	500A	8.95
124	.95	154	.65	523	10.20
128	.45	165	2.25	526A	10.75
129	.45	238	2.25	712	1.25
130	.85	291	.99	852	4.95

**SUPER SPECIAL** (Min. 5 pc. each)

TYPE NO.	YOUR PRICE
276	6.95

EXACT REPLACEMENT FOR SG613H  
2SC1172B 100 PCS. FOR 1.60 EACH

**SPECIAL JAPANESE TYPES** (Min. 5 pcs. each)

TYPE NO.	YOUR PRICE	TYPE NO.	YOUR PRICE	TYPE NO.	YOUR PRICE
2SC867A	2.75	AN214Q	1.45	UPC1181H	1.25
2SC1172B	1.95	M51515BL	2.95	UPC1182	1.25
2SC1308K	1.95	TA7205AP	1.25	STK435	3.95

FOR A COMPLETE 1983 COMPONENT CATALOG CALL OR WRITE

**CALL TOLL FREE 800-526-4928**  
IN NEW JERSEY (201) 379-9016  
COD ORDERS WELCOME (\$25 Min. Order)

***DIGITRON ELECTRONIC***  
110 Hillside Avenue, Springfield, N.J. 07081

\*ECG IS A TRADE MARK OF PHILIPS ECG.  
DIGITRON ELECTRONIC IS NOT ASSOCIATED IN ANY WAY WITH PHILIPS ECG.

Circle (21) on Reply Card

**COMPACT  
ECONOMICAL  
DESOLDERING**

**It's so Dependable, there's a Two-Year Warranty on the Pump.** The EX-525 may be A.P.E.'s lowest-cost portable solder extractor, but it's full of features: • easily desolders components from multi-layer PC boards • pump is vibration-isolated for quiet operation • Model 550 for use with shop air • EX-1000 handpiece is non-clogging and temperature-regulated by panel controls.

You need the A.P.E. EX-525 in your shop. Call or write today for all the details. **Automated Production Equipment Corp.**, 142 Peconic Ave., Medford, N.Y. 11763 • 516-654-1197. TWX: 510-228-2120

**DEPEND ON A.P.E.**

Circle (22) on Reply Card

Figures 9 and 10 show methods of interfacing LED 7-segment readouts with a data bus or unlatched output port. In Figure 9, a pair of LED readouts is connected to a latched output port via 7447 decoder chips. Each chip is a 4-bit, BCD-to-7-segment decoder that examines the binary coded decimal (BCD) input word and generates the active-low 7-segment code that corresponds to the decimal digit. Since BCD codes use four bits to represent the decimal digits 0 through 9, two BCD digits can be packed into one 8-bit word. Most microprocessor chips have instructions that change an 8-bit binary word stored in the accumulator into a pair of equivalent BCD words.

Figure 10 shows the circuit of Figure 9 expanded so that it can serve unlatched output ports or the data bus itself. IC3 is a 74100 dual-quad data latch. Each latch is

a 4-bit circuit and consists of four type-D flip-flops. Each 4-bit data latch section of the 74100 has a strobe line that is made by tying all four internal FF clock lines together. If both external strobe lines are connected, then the 74100 acts like a single 8-bit data latch.

The strobe lines are active-high, so they will cause data to be transferred from the inputs to the outputs when the strobe is high. When the strobe lines go low again, the data transferred will remain latched on the output lines. The common strobe line is connected to an out select signal in the microcomputer. This signal has several names but almost always is available. It comes active when an output operation to the designated peripheral, such as the LED displays, is designated to receive data. From the outputs of the


74100, the Figure 10 circuit is identical to the Figure 9 circuit.

Custom keyboards are used frequently in special purpose microprocessor-based devices. Basically, troubleshooting boils down to determining the high/low status of keyboard lines while a button is actuated and then deciding whether the correct code is present. In addition, if a strobe signal is used, its presence and timing must be correct.

When interfacing a new keyboard to an existing system, be sure that the high and low voltage levels are compatible and the strobe signal is time-compatible and has the right direction. Also, be sure that the strobe is the right type—continuous level or pulse. Some computer software is sensitive if the keyboard output data is latched or unlatched.

ES&T
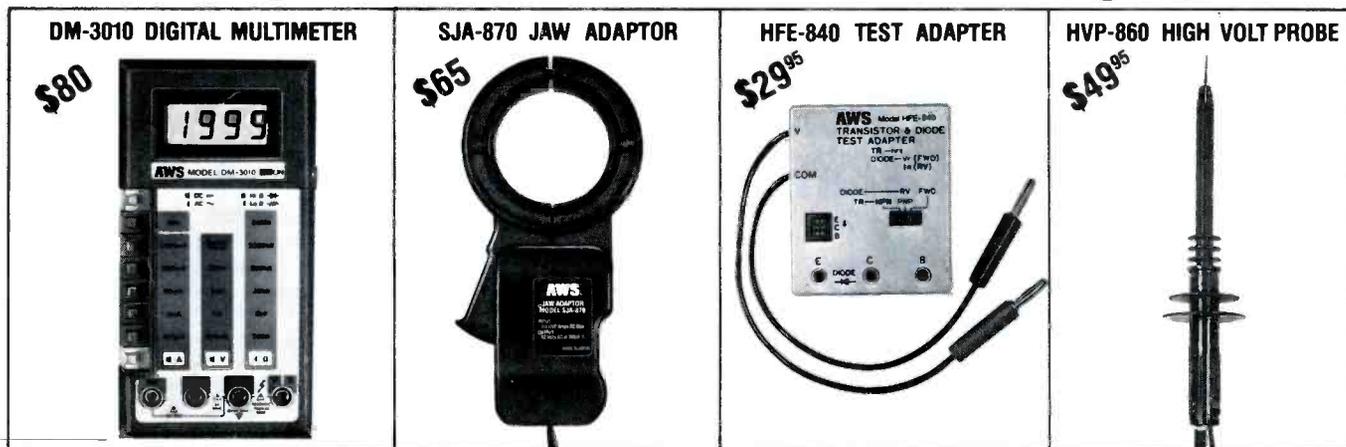
## The new AWS DM-3010. It's not just another DMM. It's a complete electrical/electronic testing system.



Today's electrical and electronic testing requirements call for equipment that can handle a wide range of applications. That's why now more than ever you need the new AWS DM-3010 Testing System.

To start off with, the **DM-3010 Digital Multimeter** has an unbelievable \$80 price tag. It offers 34 ranges with push-button control plus features usually found in much more expensive models such as: 10 Amp AC/DC range; UL1244 type test leads; overload protection on all ranges; Hi and Low power ohms in all resistance ranges and more.

Complete the system by simply adding the following accessories as you need them...

**SJA-870 Snap-Around Jaw Adaptor.** Reads 0-1200 Amps AC. Its large jaws fit easily around any conductor up to 2-15/16" in diameter.

**HFE-840 Test Adaptor.** If your work requires transistor and diode testing, this pocket-size adaptor is a must.

**HVP-860 High Voltage Probe.** Provides safe, easy and reliable readings of 0-50KVDC on low power high impedance circuits.

So compare the DM-3010 Testing System for yourself. You'll find that no other company offers a comparable system at these low prices.

For more information on the AWS DM-3010 Testing System, see your local distributor today or contact A.W. Sperry Instruments Inc., P.O. Box 9300, Smithtown, N.Y. 11787. Call Toll-Free 800-645-5398 (N.Y., Hawaii, Alaska call collect 516-231-7050).

**A.W. SPERRY  
INSTRUMENTS INC.**

Circle (23) on Reply Card

# Troubleshooting Tips


## No sound or picture Zenith monochrome model 19GB1 (Photofact 1692-2)

No sound, raster or picture was produced by the 19GB1-chassis Zenith b/w TV receiver. Although the picture-tube anode had almost zero high voltage, the power-supply voltages were normal. The only clue was an overheating resistor RX520 that filtered the +133V supply to the horizontal-output transistor. The 68Ω, 5W resistor (some models have 100Ω, 7W values) had about 50V across it, indicating excessive current drawn by the output transistor.

I removed the QX505 horizontal-output transistor and tested it carefully, but it was not defective. Scope waveforms of the horizontal-oscillator and driver stages appeared to be within tolerance. To test for excessive picture-tube current or a shorted picture tube, I pulled the high-voltage lead out of the CRT-anode and moved it near the chassis, producing a long arc. This proved high voltage (at least unrectified high voltage) was being produced *when the picture tube was not connected to the flyback*. Dur-

ing this time while the lead was disconnected from the CRT, resistor RX520 did not overheat and the voltage drop was minimal. I thought the CRT might have an internal short, so I connected the high-voltage wire and tested the CRT base voltages. All voltages were in tolerance, and gentle tapping of the CRT base and neck did not indicate an intermittent short or leakage.

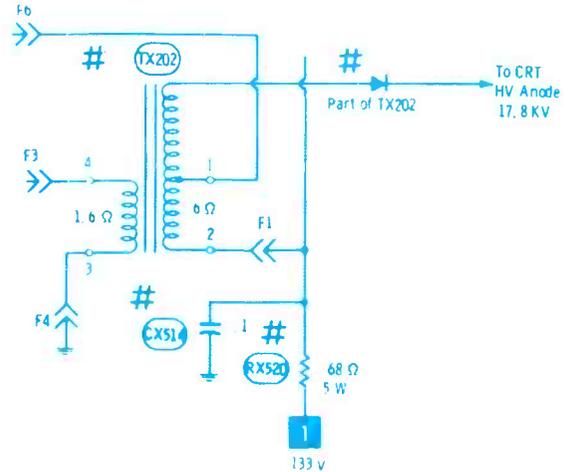After the power was turned off, I felt the flyback transformer and found it was abnormally warm. This condition made me suspect that the high-voltage diode inside the flyback was shorted. (A shorted diode applies ac pulses to the CRT capacitance, adding a huge load to the flyback.) As a



a temperature-adjustable soldering iron for less than

**\$40**

A 50-watt iron that can be adjusted with ±2% accuracy anywhere between 400°F and 750°F using the allen wrench provided. 3-wire burn resistant cord, stainless steel shaft and on/off light with 10 different long-life replacement tips available. **No. 7200**

Add an ISO-TIP safety stand with tip-wiping sponge for a complete soldering station. **No. 7295**

Write for the name of your nearest distributor and a free catalog.



**WAHL CLIPPER CORPORATION**  
Sterling, Illinois 61081 • (815) 625-6525

Circle (24) on Reply Card

## FINALLY. COMPUTERS AS A NEW TOOL FOR T.V. REPAIR.



Primefax puts computer-assisted repair capability in your shop today.

Primefax drastically reduces the number of sets requiring extensive trouble-shooting procedures.

Through the use of today's technology, Primefax maintains—in a central computer—a database of problem-solving solutions for television set malfunctions.

Primefax is a compilation of the most current, applicable technical information acquired from hundreds of valuable sources . . . and updated daily.

With a Primefax Computer Terminal installed in your shop, you can do your job more quickly and more

accurately. You have more satisfied customers, and your profits are increased substantially.

Reduced call backs • faster turn-around • reduced chance of repeated failure • more thorough service and complete repair at reasonable cost.

The more Primefax is used, the more profit you realize.

CALL US OR WRITE. No matter how you compute it, Primefax means profit for you. It's worth looking into.

In Texas, call (512) 344-5999 • Out of Texas, call 800-531-5953


**Primefax**

4825 Fredericksburg Road • San Antonio, Texas 78229

Circle (25) on Reply Card


# THINKING TVRO?

## Take A Look At Winegard!

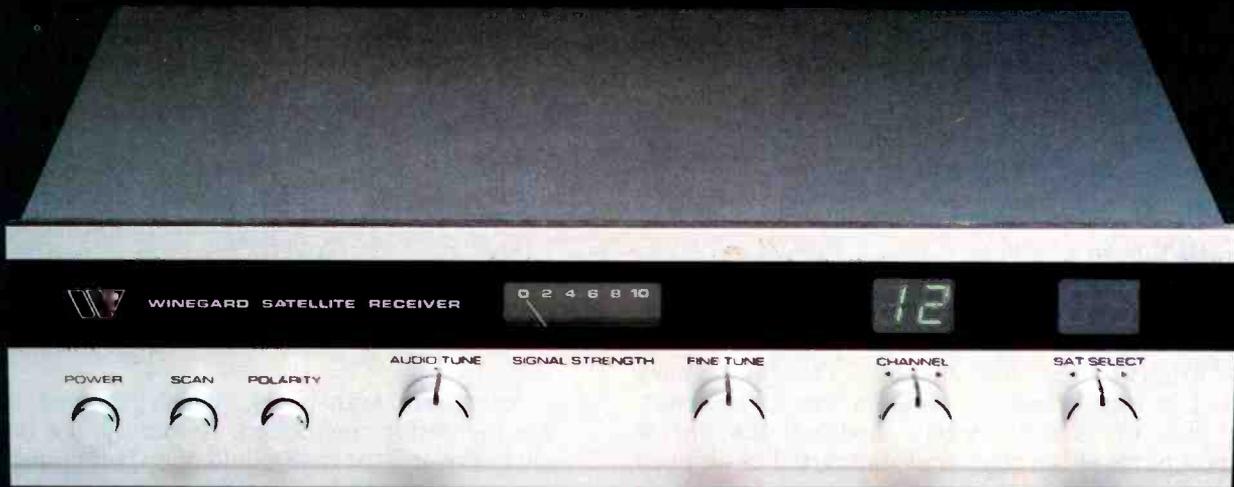

Excellent picture quality and low cost. That's what you get with Winegard's SC-5000S home satellite television system.

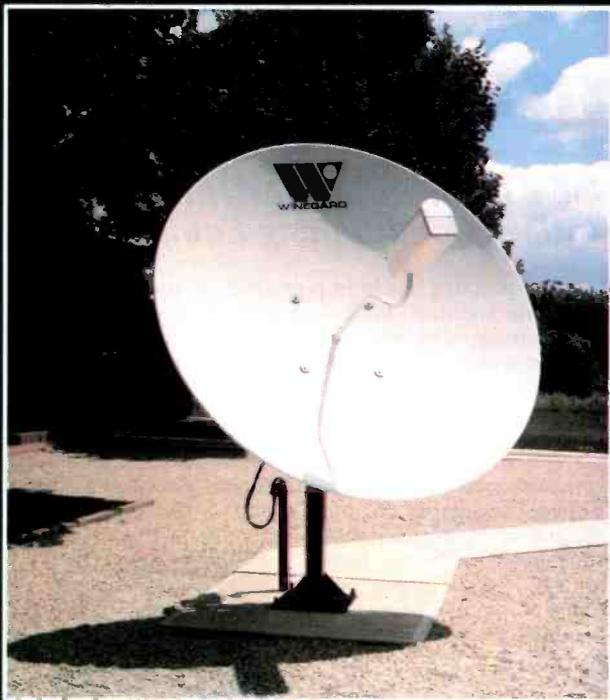You'll discover that Winegard's 8-foot package incorporates all the latest in TVRO solid-state design and engineering for a dramatic difference in satellite TV reception. All the features that your customers want are there!



### Why Buy Winegard Home Satellite TV Reception Products?

All Your Satellite Product Needs From One Source • Competitive Pricing • Easy to Handle, Ship and Inventory • All Satellite Products Backed By A Full-Year Warranty • Easy-To-Install • Complete And Professional Factory Support And Service • Rigid Quality Control Standards For Satellite TV Products

#### SC-7032S RECEIVER FEATURES:

- Rapid Scan Control
- Fine Tune
- Polarity Switch
- Channel Select Control
- Audio Tune
- Satellite Select
- Signal Strength Meter
- Remote Control Optional

#### SC-8009 ANTENNA FEATURES:

- 8-ft. Durable Spun Aluminum Reflector with Weather Resistant White Epoxy Finish
- Easy Handling and Shipping
- Complete Arc Coverage
- Choice of Rugged Pedestal or Post Polar Mounts
- Prime Focus Feed with Automatic Electronic Polarity Switching
- 90mph Wind Survival

Write for information about SASA, the professional satellite TV installers network.



WINEGARD COMPANY • 3000 KIRKWOOD STREET • BURLINGTON, IOWA 52601 • (319) 753-0121

Circle (26) on Reply Card

test, I temporarily connected a high-voltage rectifier externally between the flyback and the CRT anode. Normal operation was restored when the television was turned on again.

To save the customer the flyback's price when only the high-voltage diode was bad, I cut the high-voltage lead wire and installed the diode permanently, using a surplus of insulation to prevent arcs.

In addition to the lower price charged, there was another benefit. I learned an excellent troubleshooting method for use with other TV receivers in the future.

Tommy Small  
Gallion, AL

### Erratic height

#### Zenith monochrome 19GB1


(Photofact 1692-2)

According to the customer, the picture collapsed to a bright line at random times. Our preliminary tests confirmed that the problem was an intermittent loss of vertical sweep. Moderate flexing of several parts of the chassis often started or stopped the loss of height, so the b/w receiver was brought to the shop.

Eight transistors (including one vertical-sync injector) are in the vertical-sweep system, and tests located no defects in any of them. The problem seemed to originate with a bad connection, perhaps

a solder joint or a hairline crack of the circuit board, but a careful visual examination of the board revealed no such defects.

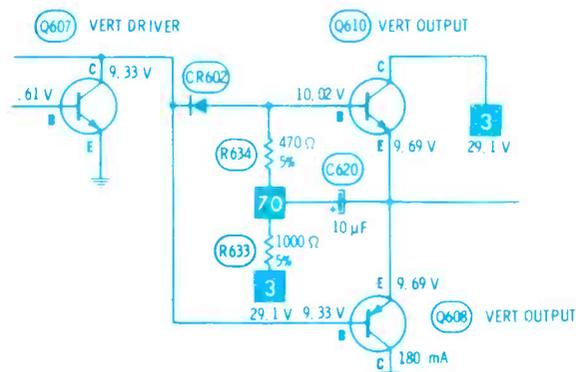Next, I decided to check the transistors again by using a high-power ohmmeter that forced the transistor junctions to conduct. Each transistor was tapped while the junction resistance was measured. All transistors were normal except Q608 (the PNP



power-output transistor), which showed erratic base-to-emitter conduction. Evidently, the bond inside the transistor case would open from mechanical movement or strain. The problem was an erratic open circuit, but *it was inside a transistor*.

Of course, replacement of Q608 allowed stable and dependable vertical deflection.

Peter J. Reno  
High Bridge, NJ

# Power line problems? No problem.

## Analyze them with STABILINE® AC Voltage Monitors . . .

Truly portable multi-site disturbance analyzers — the *only* systems with detachable, microprocessor based Detector Modules which can be left at each site. Depending on whether 1- or 3-phase models are selected, Printer/Controllers can provide categorized formats of

high/low voltages, surges, sags, impulses, common-mode noise, dropouts, power outages, d-c voltage, voltage and angle unbalances. Summaries include date, time, magnitude and duration of each category's 10 worst events and a list of the last 10 chronological events that qualify by threshold. Detector Modules can communicate with Printer/Controllers directly or over conventional telephone lines with suitable interfacing. Models available for 120, 240 or 480 VAC.

## Solve them with STABILINE® Voltage Conditioning Equipment . . .

Once the problem has been pinpointed, condition aberrations that create malfunctions and erratic behavior: **Transient Voltage Suppressors** reduce the magnitude of (attenuate) voltage spikes or transients; **Automatic Voltage Regulators** deliver constant output voltage regardless of input line variations; **Computer Regulators** maintain properly conditioned voltage and attenuate common-mode noise and impulses; **Power Conditioners** regulate voltage, provide isolation for common-mode noise and reduce transverse-mode noise; **Transient Suppressors /Voltage Regulators** combine voltage correction and impulse attenuation; **Isolation Transformers** isolate equipment from common-mode noise generated by power consuming devices.

Write or call for  
STABILINE  
literature.



## The Superior Electric Company

383 Middle Street / Bristol, Connecticut 06010 / (203) 582-9561 / Telex: 962-446

IN EUROPE: Superior Electric Nederland B.V.  
The Hague, Netherlands / (070) 679590 / Telex: 31436 Supe nl

IN CANADA: The American Superior Electric Company, Ltd.  
Toronto, Ontario / (416) 255-2318 / Telex: 06-967806

Circle (27) on Reply Card

## Books

**Editor's note:** Periodically *Electronic Servicing & Technology* features books dealing with subjects of interest to our readers. Please direct inquiries and orders to the publisher at the address given for each book, rather than to us.

**Servicing Home Video Cassette Recorders, by Marvin Hobbs; Hayden Book Company; 237 pages; \$11.95.**

This 10-chapter book is a guide to the basic operations and servicing of video tape recorders. It includes a glossary of videocassette terms and two appendices explaining the automatic assembly recording system with special consideration for cable television.

Some chapters cover video signal circuitry, servo circuit operation and system control operation of the VHS system, and the differences between VHS and Beta. A comparison of the mechanical aspects of these formats also is made.

Other chapters explain the tools and test equipment used for VTR servicing, mechanical adjustments and replacements, and electrical alignment and adjustment. The last chapter covers personal video camera theory and servicing.

Published by Hayden Book Company, 50 Essex St., Rochelle Park, NJ 07662.

**Know Your Oscilloscope, by Bob Middleton; Howard W. Sams & Co.; 192 pages; \$9.95.**

This fourth edition covers oscilloscope basics, cathode-ray tubes, input impedance and sensitivity, the general requirements of power supplies, voltage regulation, power-supply systems, sweep systems, synchronization, vertical amplifiers, the different types of oscilloscope probes and scope tests using different types of generators.

Ways to adjust and service oscilloscopes, methods of taking fre-

quency and phase measurements, methods of amplifier testing and types of digital equipment are discussed in the last four chapters.

Published by Howard W. Sams & Co., 4300 W. 62nd St., Indianapolis, IN 46206.

**Handbook of Advanced Troubleshooting, by John Lenk; Prentice-Hall; 352 pages.**

This guide maps a 4-step procedure for troubleshooting communications, television, VCR and microprocessor-based system equipment. It has 174 technical schematics, charts and diagrams.

The handbook gives shortcuts designed to help pinpoint malfunctions in specific circuits and parts, and suggests ways to troubleshoot microprocessor-based systems. The guide also offers alternative procedures to use if microprocessors do not respond to routine approaches.

Published by Prentice-Hall, Englewood Cliffs, NJ 07632.

**The VOM-VTVM Handbook, by Joseph A. Risse; Tab Books; 176 pages; \$14.95 hardbound, \$8.95 paperback.**

This book gives information for understanding and using volt-ohm-milliammeters (VOMs), vacuum-tube voltmeters (VTVMs), solid-state electronic voltmeters (SSEVs) and digital VOMs. The principles, uses, advantages, disadvantages, care, maintenance and repair of these test instruments are covered.

The book also examines the internal and external features of typical VOMs, VTVMs, EVMs (electronic voltmeters) and solid-state meters. It shows the functions and characteristics of the important components and provides data on accessories such as high current shunts, test leads, probes and adaptors.

Information on testing, troubleshooting, repair and maintenance procedures is provided. Test sequences are given for capacitance and capacitor-leakage measurement, forward and reverse rectifier tests, fuse testing, open-filament checks, battery testing and sensitive circuit measurements. Plus, readers can learn how to replace instrument batteries,

test meter movement, replace rectifiers and calibrate instruments.

The book features review questions after each chapter and answers at the back of the book.

Published by Tab Books, Blue Ridge Summit, PA 17214.

**Crash Course in Digital Technology, by Louis E. Frenzel; Howard W. Sams & Co.; 198 pages; \$19.95.**

This text-style programmed course offers a solid foundation in digital fundamentals to hobbyists, students, industrial training programs and those with even a minimal understanding of electronics. It is written in a programmed learning format using brief informational frames and frequent self-tests. It is a learning tool, rather than a reference, and is illustrated with photography, diagrams and examples.

The author covers what digital means, how it represents real-world phenomena, the devices used in handling digital data, how these devices perform logical operations, how these are combined and more. The instruments used to troubleshoot digital circuits are also discussed.

Published by Howard W. Sams & Co., 4300 W. 62nd St., Indianapolis, IN 46206.

**Build a Personal Earth Station for Worldwide Satellite TV Reception, by Robert J. Traister; Tab Books; 304 pages; \$15.95 hardbound, \$9.95 paperback.**

This comprehensive, do-it-yourself guide tells how to pick the best location for an earth station antenna, and how to assemble the equipment, hook it up, tune it in, and pipe the signals to the television.

The manual reviews standard TV reception fundamentals, then explains how communications satellites work and what happens to TV signals from the time they leave the transmitting earth station until they are received by a "dish." It also provides a refresher course on microwave signals, reception techniques, and antenna and feedline operating characteristics.

Published by Tab Books, Blue Ridge Summit, PA 17214.

**ES&T**

## ANTENNA & VIDEO ACCESSORIES

### CHECK OUR PRICES:

- 2-WAY SPLITTER UV2J 75 OHM UHF/VHF \$0.95
- A-B SWITCH HI ISOLATION 60 DB TERMINATED COMPACT 2"x3" CS1 \$4.50
- UHF/VHF SEPARATOR 75 OHM IN 75 OHM VHF UHF 300 OHM SHIELDED UVS 75 300 \$1.35
- MINI UV SEPARATOR 75 OHM IN 300 OHM OUT 1/2"x2 1/2" MT6UVJ \$1.05
- HI Q CHANNEL TRAPS & BP FILTERS 6 STAGES \$40.00

CHECK READER SERVICE CARD FOR CATALOG OF OVER 300 ITEMS OR CALL COLLECT: 213-355-2510

## ANTSCO CORP.

P.O. BOX 188  
SIERRA MADRE,  
CA 91024

Circle (28) on Reply Card



SINCE 1950

- LEADING SPOKESMAN
- TRADE INFORMATION DISPENSER
- WATCHDOG
- NATESA SCOPE
- STANDARDS YARDSTICK
- CONSUMER RELATIONS
- PROBLEM SOLVER
- CONCISE PRACTICAL BUSINESS OPERATIONS MANUAL
- SERVICE CONTRACT MANUAL
- CUSTOMER PLEASING PROFIT PRODUCING ORDER FORMS
- PARTS PROCUREMENT EXPEDITOR
- SERVICE BUSINESS
- DIVERSIFICATION PLANS
- TECHNICIAN DEVELOPER

5930 So. Pulaski Rd. • Chicago, Illinois 60629

# Test your electronic knowledge

By Sam Wilson, IS CET test director

The subject this month is resistors. Questions of this type are distributed throughout the CET tests.

- \_\_\_C. the color for the power rating.
- \_\_\_D. the color for the reliability rating.
- \_\_\_E. None of these choices is correct.

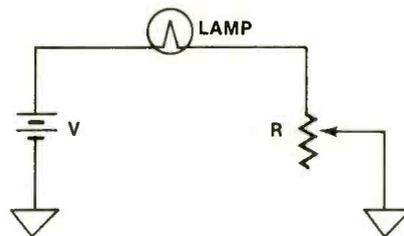


Figure 1

1. In the circuit of Figure 1, variable resistor R is connected as a
  - \_\_\_A. rheostat.
  - \_\_\_B. potentiometer.



Figure 2

2. For the color-coded carbon resistor of Figure 2, the arrow points to
  - \_\_\_A. the color for the first digit.
  - \_\_\_B. the color for the tolerance rating.

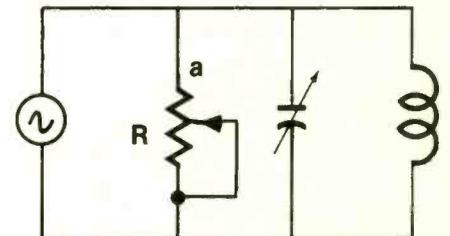


Figure 3

3. The resistor in Figure 3 is called a
  - \_\_\_A. swamping resistor.
  - \_\_\_B. surge limiter.
  - \_\_\_C. parasitic suppressor.
  - \_\_\_D. foldback limiter.
  - \_\_\_E. step down resistor.

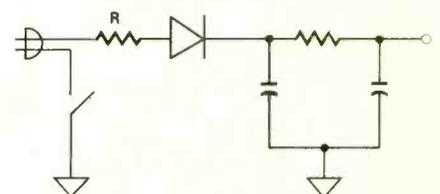


Figure 4

4. For the circuit of Figure 3,

moving the arm of R toward point *a* will

- \_\_\_ A. reduce parasitics.
- \_\_\_ B. decrease the surge.
- \_\_\_ C. broaden the tuned bandwidth.
- \_\_\_ D. increase the power absorbed by the circuit.
- \_\_\_ E. increase parasitics.

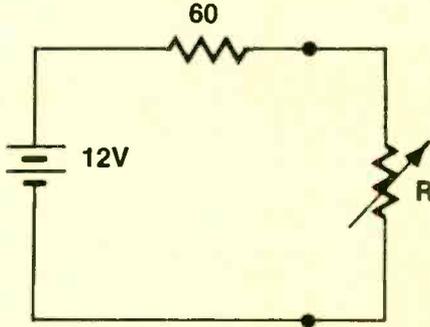


Figure 5

5. In the circuit of Figure 3, adjustment of R
- \_\_\_ A. will affect the resonant frequency of the circuit.
  - \_\_\_ B. will not affect the resonant frequency of the circuit.

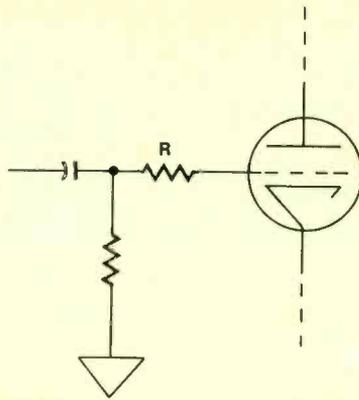


Figure 6

6. The resistance of a voltage-variable resistor (varistor)
- \_\_\_ A. increases with an increase in voltage across it.
  - \_\_\_ B. decreases with an increase in voltage across it.
7. A certain resistor is color coded *yellow purple silver*. The resistance value of the resistor is
- \_\_\_ A.  $47\Omega \pm 10\%$ .
  - \_\_\_ B.  $47\Omega \pm 5\%$ .
  - \_\_\_ C.  $47\Omega \pm 20\%$ .
  - \_\_\_ D.  $4.7\Omega$ .
  - \_\_\_ E.  $0.47\Omega$ .

8. Resistor R in Figure 4 is
- \_\_\_ A. a filter resistor.
  - \_\_\_ B. a surge limiting resistor.
  - \_\_\_ C. a parasitic suppressor.
  - \_\_\_ D. a swamping resistor.
  - \_\_\_ E. never used as shown.
9. What is the maximum amount of power that can be dissipated by resistor R in Figure 5?
- \_\_\_ A. 0.06W
  - \_\_\_ B. 0.6W
  - \_\_\_ C. 6W
  - \_\_\_ D. 0.036W
  - \_\_\_ E. None of these choices is correct.
10. Figure 6 shows a partial schematic of a high-frequency amplifier. The purpose of R is to
- \_\_\_ A. prevent thermal runaway.
  - \_\_\_ B. prevent parasitic oscillations.
  - \_\_\_ C. prevent grid emission.
  - \_\_\_ D. provide a bootstrap input circuit.
  - \_\_\_ E. provide class A bias.

Answers on page 60.

## ATTENTION TECHNICIANS

- ★ JOB OPENINGS
- ★ MONTHLY TECHNICAL TRAINING PROGRAM
- ★ BUSINESS MANAGEMENT TRAINING
- ★ LOW COST INSURANCE
- ★ CERTIFICATION
- ★ TECHNICAL SEMINARS

All of this in a nonprofit international association for technicians

FIND OUT MORE:



R.R. 3 Box 564  
Greencastle, IN 46135

EPS 276A  
equivalent to Sony  
SG 613 \$9.50 ea.  
10 for \$85.00



We guaranteed it works in the Sony circuit or your money back.

### ICs SPECIAL

HA1398	Min 5 pcs	\$3.50
HA1377A		2.50
TA7222		1.50
TA7227		3.50
UPC1185		2.50

2SC1308K  
10 for \$19.50  
100 for \$185.00




Replace most horizontal output transistors like ECG\* 238, ECG\* 165, 2SC1172B, and others.



CV-1



CV-94A

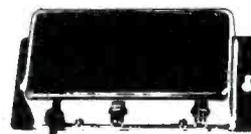

CV-25



CV-27

20B-830

UV 75-300 Ohms matching transformer	10 for \$4.50
46 Channel Cable converter with fine tuning	\$19.95
24 db distribution amplifier U/V/FM with FM Trap	\$18.00
0-900 MHz Xinc die-cast 2-way splitter	10 for \$10.00
Universal adaptors for Atari Computer	\$4.00

MIN. 5 pcs.

AN214Q	\$1.50
AN239	5.43
AN245	2.57
AN247	2.99
AN313	2.79
AN315	2.00
AN331	3.59
AN7145	2.46
AN7146	3.70
AN7150	2.33
BA511	1.44
BA421	1.23
BA532	1.62
BA1310	1.56
HA1339A	1.84
HA1342A	1.84
HA1366W	1.89
HA1377	2.93

HA1388	\$4.82
HA1398	4.22
LA4440	4.00
LA4461	3.75
MB3705	1.56
MB3710	2.80
MB3730	3.18
MB3756	1.99
MB8719	4.78
PL102A	6.34
STK013	7.70
STK430	5.50
STK433	4.00
STK435	5.34
STK437	6.50
STK439	6.80
STK463	9.65
STK0029	3.88
STK0039	4.63

STK0040	\$ 5.82
STK0050	5.87
TA7204P	1.35
TA7205AP	1.20
TA7217AP	1.81
TA7222AP	1.87
TA7608	10.45
TA7609	4.10
UPC1001H2	2.89
UPC1156H	1.69
UPC1181H	1.28
UPC1182H	1.28
UPC1185H	3.11
UPC2002	1.43
2SA771	2.08
2SA1105	3.21
2SB555	3.09
2SB595	1.24

2SB618	\$2.05
2SB697	3.23
2SC789	1.20
2SC945	0.11
2SC1061	0.56
2SC1114	3.45
2SC1116A	4.06
2SC1124	0.99
2SC1306	0.92
2SC1307	1.72
2SC1986	1.42
2SC2580	2.64
2SD425	3.03
2SD525	0.90
2SD613	0.60
2SD733	2.50

Equivalent to ECG\*

min. 10 pc	no
85	\$0.45
123A	0.35
128	0.50
129	0.50
152	0.55
153	0.60
165	2.25
175	0.95
186A	0.60
187A	0.65
196	0.65
238	2.25
291	1.00
292	1.06
375	0.95

TRIPLES min.	500A	\$11.50
	520	17.00
	521	14.00
	522	13.90
	523	13.50
	526A	15.50
	528	17.60
	529	17.90
	531	17.90
	534	15.90
	535	17.00
	538	15.90
	539	17.60

ECG is the trade mark of Philips ECG  
PARTIAL LIST FOR COMPLETE CATALOG CALL 415-532-2711

### NO MINIMUM SHIPPING:

\$4.50 under \$5.00, \$3.50 over \$15.00, COD \$1.75, UPS Blue Label extra.  
M/O, VISA, M/C, COD, Company Check.  
CA residents add appropriate sales tax

### EPS

P.O. BOX 5356, BERKELEY, CA 94705  
TOLL FREE: 800-227-0104  
In CA, AK, HI: 415-532-2711  
THIS SPECIAL EXPIRES SEPT. 30, 1983

Circle (29) on Reply Card

# PREVENT HI-TECH HEADACHES

Our Isolators eliminate equipment interaction,



clean up interference, curb damaging power line spikes and lightning bursts.

## ISO-1 Isolator

3 isolated sockets; quality spike suppression; basic protection. . . \$76.95

## ISO-3 Super-Isolator

3 dual isolated sockets; suppressor; commercial protection. . . . . 115.95

## ISO-17 Magnum Isolator

4 quad isolated sockets; suppressor; laboratory grade protection. . . 200.95

**ESP** Electronic Specialists, Inc.  
171 S. Main St., Box 389, Natick, MA 01760  
Toll Free Order Desk 1-800-225-4876  
MasterCard, VISA, American Express

Circle (30) on Reply Card

It's no puzzle to order Oelrich Service Forms



For TV-radio and two-way radio service - legal forms for Calif., Florida and Utah. Now at parts jobbers or write for cat. B64.

## OELRICH PUBLICATIONS

4040 N. Nashville Ave., Chicago, IL 60634  
Now call toll-free! 800-621-0105

Circle (31) on Reply Card

Your ad gets quick results. Advertise in classifieds.

# Literature

Vaco Products' line of professional wire strippers can be found in the *Wire Stripper Catalog*. This 4-page, color catalog contains complete descriptions and illustrations of the easy-to-use wire stripper, multipurpose wire stripper and precision wire stripper. Each of these tools can strip wire, cut wire and bolts, and loop, bend and pull wire.

Also featured are Vaco's other wire strippers, including the self-adjusting wire stripper, automatic wire stripper and wire stripping tool.

Circle (101) on Reply Card

The 1983-84 catalog and buyer's guide of electronic test and measurement instrumentation is available from **Keithley Instruments**. The 100-page catalog includes two new product sections: system components and thermometers. Other product sections are digital multimeters, electrometers/picoammeters, nanovoltmeters and sources. Each product section is preceded by a selector guide. In addition, four product sections are prefaced with technical data, theory of operation, and design considerations.

A new accessory section has photos and descriptions of avail-

able accessories. Accessory selector guides are located at the end of appropriate product sections.

Circle (106) on Reply Card

RCA distributor and special products division has published a chart of the *Fastest Moving VHS VCR Parts*. This chart cross-references identification/stock numbers of Magnavox, NAP, Panasonic and Sylvania to RCA stock numbers in order to expedite parts selection for 100 of the industry's fastest-moving mechanical and electrical replacement parts for portable and table-model VHS instruments.

Circle (103) on Reply Card


**ETCO Electronics** has released a 112-page catalog featuring items from the electronics, communications, telephone, cable TV and video fields. It also has a complete parts selection for the hobbyist or repair shop owner.

A 16-page section of the catalog has been devoted to telephone and related equipment for small systems applications and home use. An addition to this catalog is the classified section.

Circle (104) on Reply Card

A free data sheet describing long strip industrial multiple outlet strips is available from **Perma Power Electronics**. The data sheet describes 10 Sockets Plus outlet strip models, which provide up to 24 outlets.

Circle (105) on Reply Card

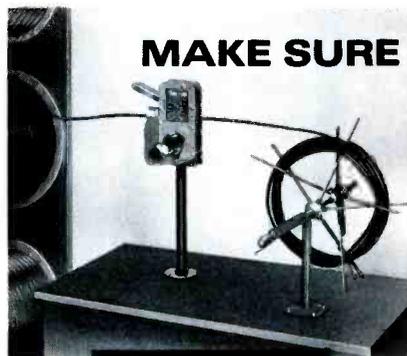

**MAKE SURE** you get paid for every inch of wire sold

**EXACT MEASURING** is a must when you retail coaxial cables, audio cables, and electronic/electrical wires. You can work confidently and quickly . . . yet keep close control . . . with **HYKON WIRE METERS** and **REELS** set up on a counter or as a portable combo. Wire up to 1" diameter pulls from stock through the meter onto take-up reel for neater delivery. Write for details or call us at AREA 216 821-2320

**Hykon**

**MANUFACTURING CO.**


Post Office Box 3800-ET

Alliance, OH 44601

Circle (32) on Reply Card

Chassis — Admiral 4M10 chassis  
PHOTOFACT — 1522-1


1

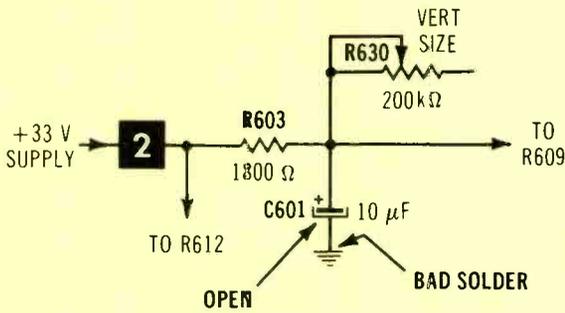

**Symptom** — Vertical lines near center of picture  
**Cure** — Check capacitor C601, and replace it if open

Chassis — Admiral 4M10  
PHOTOFACT — 1522-1


2

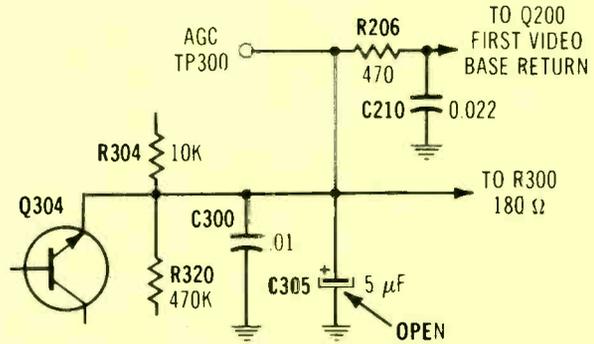

**Symptom** — Poor AGC, picture pulls and rolls  
**Cure** — Check capacitor C305, and replace it if open

Chassis — Samsung CT501  
PHOTOFACT — 2055-2


3

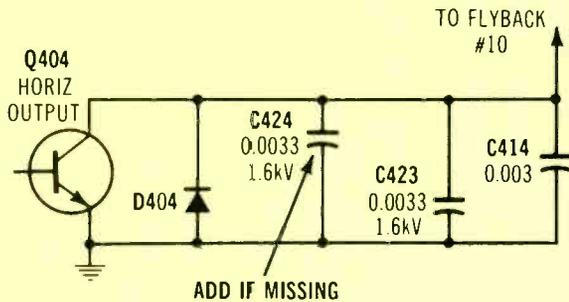

**SYMPTOM** — Narrow picture and excessive 32kV HV  
**Cure** — Install C424 if it was omitted. Also, change C971 to 180K from 120K

Chassis — RCA CTC90  
PHOTOFACT — 1710-2


4

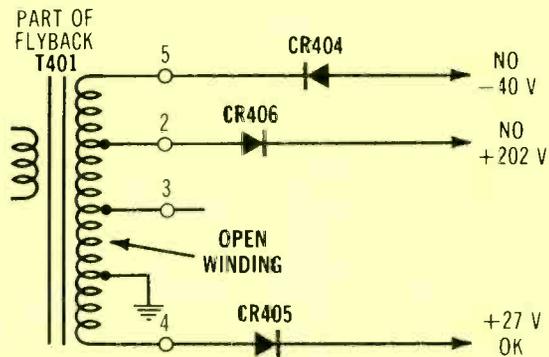

**Symptom** — No sound and no raster  
**Cure** — Check flyback pin 3 to ground, if open replace the flyback T401

Chassis — RCA CTC81  
PHOTOFACT — 1572-2


5

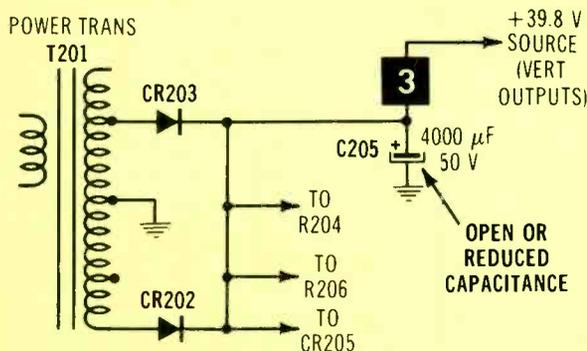

**Symptom** — Height decreases every 8s regularly  
**Cure** — Check the ripple at C205, and replace it if ripple is excessive (high ripple varies the supply voltage to the vertical-output transistors)

Chassis — RCA CTC90  
PHOTOFACT — 1710-2

6

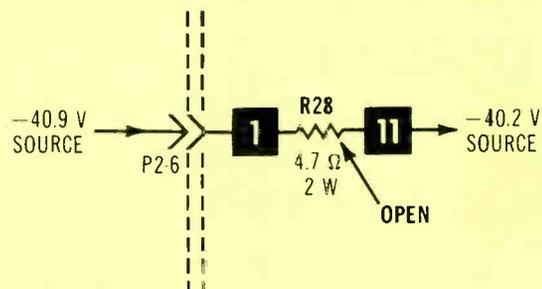

**Symptom** — No height  
**Cure** — Check R28, and replace it if open

# Marketplace

## Put Professional Knowledge and a COLLEGE DEGREE in your Electronics Career through HOME STUDY

### Earn Your DEGREE

No commuting to class. Study at your own pace, while continuing your present job. Learn from easy-to-understand lessons, with help from your home-study instructors whenever you need it.

In the Grantham electronics program, you first earn your A.S.E.T. degree, and then your B.S.E.T. These degrees are accredited by the Accrediting Commission of the National Home Study Council.

Our free bulletin gives full details of the home-study program, the degrees awarded, and the requirements for each degree. Write for *Bulletin in T-83*.

**Grantham College of Engineering**  
2500 So. LaCienega Blvd.  
Los Angeles, California 90034

**ATTENTION ELECTRONIC TECHNICIANS**



Highly Effective Home Study BSEE Degree Program for Experienced Electronic Technicians  
Our New Advanced Placement Program grants Credit for previous Schooling & Professional Experience. Advance Rapidly! Our 36th Year!  
FREE DESCRIPTIVE LITERATURE!  
Cook's Institute of Electronics Engineering  
DESK 15 . P.O. BOX 20345, JACKSON, MS 39209

Circle (34) on Reply Card

**FREE KIT Catalog**

Test Equipment-Kit or Assembled  
FUNCTION GENERATOR Kit \$59.95  
Auto-Ranging Cap-meter kit \$79.95

contains TEST & EXPERIMENTER'S EQUIP.

Phone 209-772-2076  
Circle number or phone for catalog.

**DAGE SCIENTIFIC INSTRUMENTS**  
BOX 144 VALLEY SPRINGS CA 95252

Circle (35) on Reply Card

**FREE CATALOG**  
HARD-TO-FIND PRECISION TOOLS

Lists more than 2000 items: pliers, tweezers, wire strippers, vacuum systems, relay tools, optical equipment, tool kits and cases. Send for your free copy today!

**JENSEN TOOLS INC.**  
7815 S 46TH STREET PHOENIX AZ 85040

Circle (36) on Reply Card

# Products

## Digital multimeter

*Philmetric* has expanded its multimeter product group with the 10A-range, 3½-digit LCD readout, side-positioned push-button model MD 210.

The entry has a projected 2000-hour battery life and 0.25% dc accuracy. It provides a selection of 34 ranges and carries a 200µA scale for ac/dc readings.

Equipped with a 9V battery and safety guard test leads to deter shock hazard, the MD 210 features ac and dc current range from 0 to 10A in six steps—0-10A, 0-2000mA, 0-200mA, 0-20mA,




0-2mA and 0-200µA. Resistance range is 0 to 200Ω with a maximum of 200kΩ. Resolution ranges from 100nA to 100µA and to 10mA. Input impedance is 10MΩ for voltage ranges.

Circle (76) on Reply Card
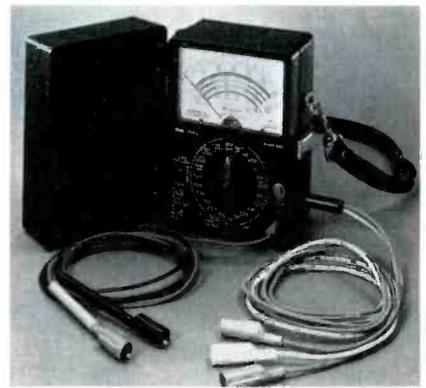
## Telephone loop tester

The model 3 loop tester introduced by *Triplet* is a multifunc-



tion tester that includes a transmission line test set, 10-tone generator and a volt-ohmmeter. The model 3 is designed for installation or repair service measurement of power influence, circuit noise, circuit loss or line milliamp checks on telephone company or privately installed cable systems.

The 10-tone, sine-wave generator set permits loop-around test capability where no tone is available. Measurements are achieved by simultaneous sending and receiving with the model 3 "talking to itself." Frequency ranges include 304, 404, 504, 750, 1004, 1750, 2804, 3004, 3204 and 4804Hz at -0 to +5% accuracy.

Circle (77) on Reply Card

## Soldering aids

The model 699 master soldering aid kit is available from *Desco Industries*. This 42-piece kit contains one of each soldering aid tool from Desco. Tools included are 24 double-ended soldering aids, six stainless steel scriber probes, two double-ended scriber probes and 10 hardwood or nylon probes and soldering aids.

Circle (78) on Reply Card

## Video vector display

*Leader Instruments* has introduced the LBO-51M-V vector display. The LBO-51M-V is driven by R-Y and B-Y video signals from a precision chroma decoder or Tek-

**FREE!!**

Send for our FREE 1983 Catalog of Computer Peripherals, Software, Electronics Kits, IC's, Components and Unique Products.

**CHANEY**  
electronics inc.

P.O. BOX 27038  
DENVER, COLORADO 80227  
303-781-5750

Circle (37) on Reply Card

**SATELLITE TV VIEWERS**  
Get the most complete weekly listings.  
Send \$1 for sample copy.

**Satellite TV Week**

P.O. Box 308, Fortuna, California 95540  
800-358-9997 (U.S.) • 800-556-8787 (Callif.)  
707-725-2476 (all others)

Circle (38) on Reply Card

# WE HAVE A LOT TO BRAG ABOUT AT ORA ELECTRONICS

## ONE HOUR SHIPPING



Other companies brag about 24-hour shipping, but we at ORA Electronics have the best shipping time in the industry. ONE HOUR — that means that you can have that important part in your hands as early as the next day.

## HIGH IN-STOCK RATIO

**95%  
IN  
STOCK**

ORA Electronics has the highest "in stock" ratio in the industry (95%). The average stocking ratio in the business is 75%. That means *less* back orders or "out of stock" items when you order from us!

## BETTER SERVICE




Nobody offers better service than ORA Electronics — that includes packing, order handling, customer service and quality control. Our employees are highly trained and experienced to better serve you.

## LOWER PRICES



Other companies lower the price on some items and advertise them heavily. We at ORA Electronics have a lower overall price—and yes, you'll like OUR total better!

## FREE SHIPPING

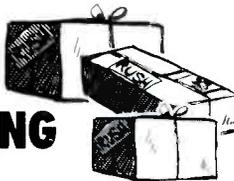

Only ORA Electronics offers free shipping for prepaid orders (in the continental U.S.A.). For COD, charge and open account orders, we charge only actual shipping costs, no handling charges whatsoever!

## TWO YEAR WARRANTY



All ORA Electronics' semiconductors and many other products are guaranteed for two full years. ORA Electronics has the longest warranty in the industry because we know what we sell: prime grade parts, and they are tested for quality.

## ORIGINAL PARTS



ORA Electronics offers you only original semiconductors, no "replacements" or "substitutes" or "almost the same" parts. Some other companies re-label their parts. When you order from us, you can be sure that every semiconductor you buy is a prime grade, ORIGINAL, tested part.

## POPULAR CATALOG



ORA Electronics' catalog is the most copied catalog in the industry. It's the easiest to follow, the prices are not confusing, and a comprehensive index is included. Send for your free copy today!

Call toll free: (800) 423-5336.  
Calif. toll free: (800) 382-3663.  
Non-order info: (213) 701-5850.  
Local: (213) 701-5848.

**ORA**  
ELECTRONICS  
A DIVISION OF ALLIANCE RESEARCH CORPORATION

"OUR SERVICE MAKES THE DIFFERENCE"  
18215 PARTHENIA ST., NORTHRIDGE, CA 91325

Circle (39) on Reply Card

tronix 650HR series picture monitor equipped with R-Y and B-Y outputs.

Its 7.6 x 9.5cm display area has a removable external vectorscope graticule that may be imprinted with user graphics. The 3MHz bandwidth on the X and Y axis and 4MHz on the Z axis permits use of the LBO-51M-V in a variety of vector, waveform, response curve and alphanumeric display presentations.

Circle (80) on Reply Card

### Logic analyzer

Tektronix has added the Sony/Tektronix 318 and 338 logic analyzers to its 300 series. The 318 provides 16 parallel channels of data acquisition at up to 50MHz.



The 338 delivers 32 channels at up to 20MHz. Both models provide glitch capture and three levels of triggering. The models weigh 11 pounds each.

Many of the Sony-Tektronix 318/338 functions were implemented in three LSI gate arrays. One chip uses 828 gates to implement counting, multiplexing and latching operations. A second chip employs 797 gates to implement clocking, timing and decoding functions. A third chip implements display controller functions.

Circle (81) on Reply Card

### Chip Clip

The Chip Clip from OK Industries attaches with a snap-action locking ring that ensures reliable contact with virtually no stress to the tested device. The clamshell design is spring loaded outwardly rather than inwardly. Spacing is regulated to ensure contact and attachment without undue strain on the component. The body is made of high-dielectric nylon, and contacts are hard gold plated. Molded

separators eliminate shorts between legs.

Circle (82) on Reply Card

### Digital multimeter

Sperry Instruments has introduced its 34-range, 3½-digit, push-button digital multimeter, model DM-3010.

Designed for field and laboratory work, the DM-3010 features a 10Aac/dc range; UL1244-type test leads; 500Vac/dc protection on resistance ranges; overload protection on ranges; ½-inch, 3½-digit LCD display and 200-hour battery life.

Ranges on the DM-3010 are 200mV/2/20/200/1000Vdc; 20mV/2/20/200/750Vac; 200A/2mA/20mA/200mA/2000mA/10A ac and dc current; and 200/2K/20K/200K/2M/20M high and low power ohms.

Circle (75) on Reply Card

## Answers to quiz

From page 55.

1. A Rheostats control current; potentiometers control voltage.
2. D Older resistors do not have this band.
3. A It lowers the Q of the tuned circuit and therefore increases its bandwidth.
4. C If the arm is moved all the way to point a, the circuit is shorted. It has the frequency characteristics of a piece of wire (which is a very broad bandwidth).
5. A
6. B
7. E On the CET test you may find the color that represents seven described as purple or violet.
8. B The resistor protects the diode against high current during the initial charge of the filter capacitors.
9. B Maximum power will occur when  $R = 60\Omega$ .
10. B There are still a few questions on tubes in the CET test.

## Maybe We're To Discrete About Our Discrete Products

### Diode Specials

In Lots of 100

1N4148	\$3.60/100	1N4004	\$3.60/100
1N4001	3.00/100	1N4005	4.00/100
1N4002	3.25/100	1N4006	4.50/100
1N4003	3.40/100	1N4007	5.50/100

### Transistor Specials

PN2222A	\$8.00/100	2N3906	\$12.00/100
PN2907A	8.00/100	2N3055	.65 ea.
2N3904	12.00/100		

### Carbon Film Resistors

¼ Watt 5% Tolerance

Now Only \$1.50/100

All 5% Values Available

### Specializing in:

**Resistors**  
**Transistors**  
**Diodes**  
**SCRs**  
**Full Wave Bridges**

STOCKED  
IN  
DEPTH

**And the Old and Exotic!**

Call Liz and ask about her parts today!

We also purchase excess inventories. Call Martha about your parts today!

"Have You Kissed Your Computer Lately?"

**Components Express, Inc.**



1380 E. Edinger • Santa Ana, Calif. 92705 • 714/558-3972

TWX 910-595-1565 • ADVACON SNA • International Orders Welcome

Terms of Sale: Cash, Checks, Credit Cards, M.O., C.O.D. FOB Santa Ana.

Calif. residents add 6% sales tax.


Circle (40) on Reply Card

# “The Deluxe II”

Is The Ultimate In UHF Sine Wave Converter Technology

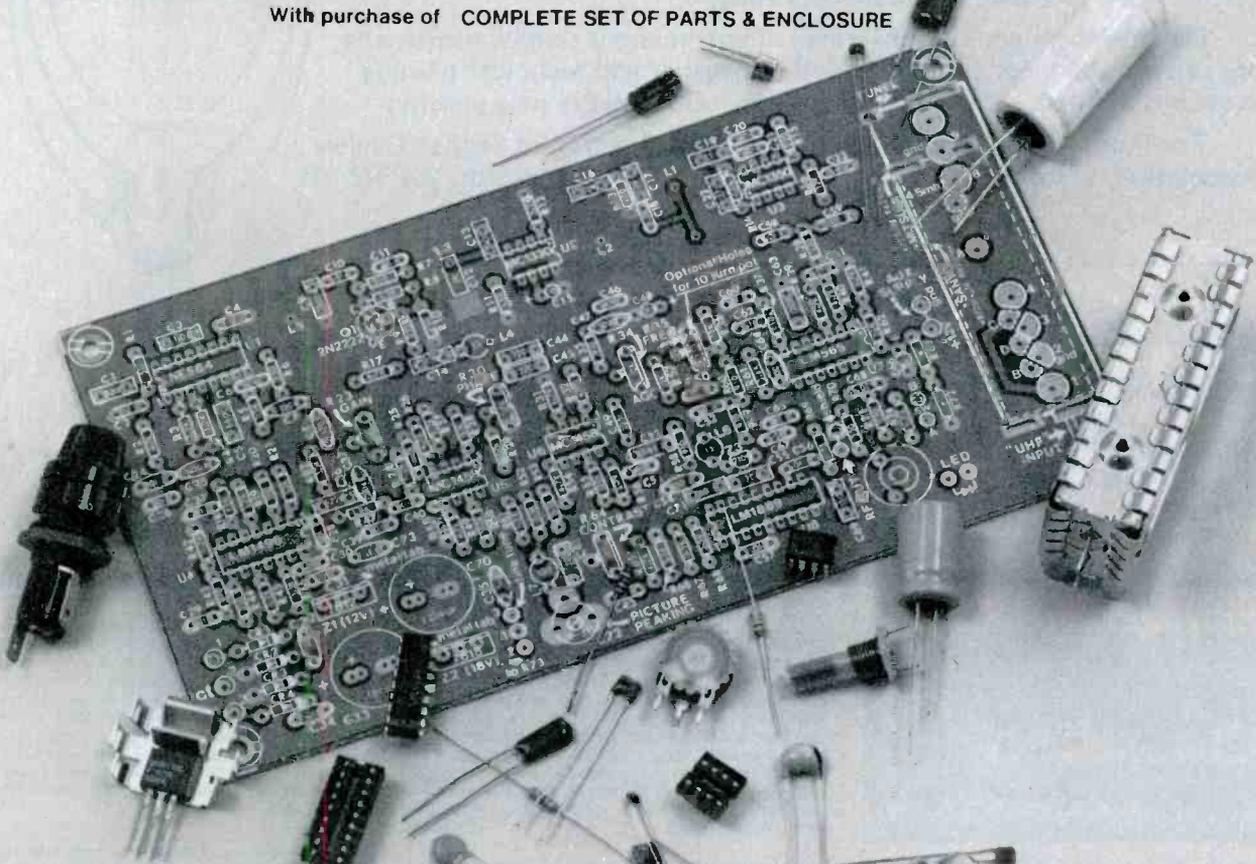**PC BOARD & PLANS \$20.00**

With purchase of COMPLETE SET OF PARTS & ENCLOSURE



The latest state of the art electronics combined with the excellence in printed circuit manufacturing creates this high performance UHF Sine Wave Converter kit that outperforms the imitations by a long shot. Engineered for reliable stability and outstanding reception clarity, uninterrupted modulated audio and fully illustrated instructions with the amateur in mind.

BETA ELECTRONICS, 1700 E. DESERT INN ROAD, SUITE 222, LAS VEGAS, NEVADA, 89109

TOLL FREE  
**1-800-782-2701**

QTY	DESCRIPTION OF ITEM	COST EACH	SHIPPING EACH	TOTAL
	PC BOARD, PLANS, PARTS & ENCLOSURE	\$152.99	\$4.95	
	PARTS & ENCLOSURE ONLY	\$132.99	\$4.95	
	PC BOARD & PLANS ONLY	\$30.00	\$1.50	
		<b>GRAND TOTAL</b>	<b>\$</b>	

PLEASE  
PRINT CLEARLY

SEND THIS  
ORDER FORM

NAME \_\_\_\_\_

GRAND  
TOTAL

\$

ADDRESS \_\_\_\_\_

QUANTITY DISCOUNTS AVAILABLE

CITY/STATE/ZIP \_\_\_\_\_

ORDER DATE \_\_\_\_\_

MO. DAY YR.

VISA  MST. CARD

CARD NO. \_\_\_\_\_

EXP. DATE \_\_\_\_\_

FOR IMMEDIATE DELIVERY MONEY ORDERS OR CERTIFIED CHECKS PREFERRED


PERSONAL CHECKS ALLOW 4 WEEKS FOR DELIVERY

# Opportunity knocks.

The professional world of the Electronics Service Dealer is rough. That's why we're working so hard to make it easier for you to operate a cost effective business. NESDA offers substantial savings on bank-card and insurance rates, business contacts, technical and management certification, and that's just the beginning.

Our members are kept informed about industry developments, and are offered the most comprehensive managerial and technical training programs available. Opportunity knocks. Don't let it pass you by.

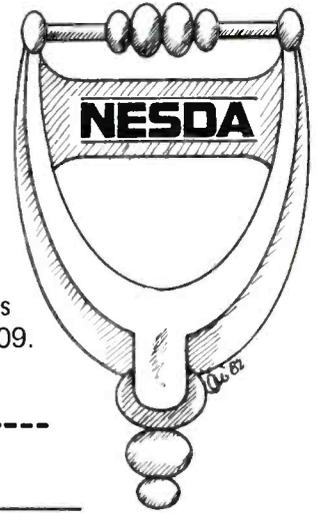For more information about the National Electronics Service Dealers Association, write to: NESDA, 2708 W. Berry St., Ft. Worth, TX 76109.



-----

NAME \_\_\_\_\_

FIRM NAME \_\_\_\_\_

FIRM ADDRESS \_\_\_\_\_ Member of State  Local  Assn.

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_ PHONE \_\_\_\_\_

## Classified

Advertising rates in the Classified Section are 50 cents per word, each insertion, and must be accompanied by payment to insure publication.

Each initial or abbreviation counts a full word.

Minimum classified charge \$10.00.

For ads on which replies are sent to us for forwarding (blind ads), there is an additional charge of \$3.00 per insertion to cover department number, processing of replies, and mailing costs.

Classified columns are not open to advertising of any products regularly produced by manufacturers unless used and no longer owned by the manufacturer or distributor.

### FOR SALE

**SCRAMBLED TELEVISION**, encoding/decoding. New book. Theory/circuits, \$9.95 plus \$1 shipping. Workshop, Box 393ES, Dept. E, Bethpage, NY 11714. 7-80-tfn

**TUBES FOR TV AND RADIO** — 35¢ ea. Washington TV Service, 1330 E. Florence Ave., Los Angeles, CA 90001. 1-83-12t

Use ES&T  
classified ads

**COMPLETE JERROLD WIRELESS REMOTE/DE-SCRAMBLER** — full warranty, \$159.00. Complete Oak descramblers, full warranty, \$169. Trap/filters in line type, \$49, 2 min. installation, SG613 transistors, only \$6.99. Original Toshiba 2SC1172B, only \$1.99 with hardware. 100/450, 80/480, 200/300, 40/450, 25 1st only \$1 each mixed or single lot. Super special while they last 800-860 41 each safety caps Zenith type, 10 lot only \$2.50. Bulk 2SC1172B only 50 lot, \$1.69. Redcoat Electronics, 104-20 — 68th Drive, Forest Hills, NY 11374, (212) 459-5088. 5-83-tfn

**CABLE CONVERTERS, DECODERS.** Free catalog! APS, POB 263, Newport, RI 02840. 6-83-12t

**SUBSCRIPTION TV MANUAL**, covers all three major scrambling systems, only \$12.95. Includes theory, circuits, waveforms and trouble shooting hints. Save your VIDEO GAME CARTRIDGES on EPROM with our EPROM duplicator. Plans \$9.95. Catalogue \$2.00, refundable. RANDOM ACCESS, Box 41770A, Phoenix, AZ 85080. 8-83-tfn

**2SC1172B's, 50 LOTS — \$1.69;** 2SC1308K's, original Sanyos, 50 lots — \$1.99; Cheater cords, 25 lots — 35¢; pol- and non-polarized, 1,000 ft. reels of RG 59 U. Coax Cable — \$39/roll. Minimum order \$75. Redcoat Electronics, 104-20 68th Drive, Forest Hills, NY 11375, 212-459-5088. 10-82-tfn

**ELECTRONIC SURPLUS: CLOSEOUTS, LIQUIDATIONS!** Parts, equipment stereo, industrial educational. Amazing values! Fascinating items unavailable in stores or catalogs anywhere. Unusual FREE catalog ETCO-011, Box 762, Plattsburgh, NY 12901. 6-78-tfn

**SPRING SPECIALS** on Popular Electrolytics — 40/450V — 75¢; 80/450V — 85¢; 100/450V — 95¢ 200/300V — \$1.05. Quantity 20 lot only. Minimum order of \$50. SUPER SPECIALS. Bulk Zenith safety capacitors 800-860, 12 lot only \$2.50 each. REDCOAT ELECTRONICS, 104-20 68th Drive, Forest Hills, NY 11375, 212-459-5088. 10-82-tfn

**REPLACEMENT COLOR YOKES-DEALERS ONLY.** Zenith 95-2501-2532-2887 etc. \$22.95. Magnavox 361380-1 etc. \$24.95. Sylvania \$24.95. American-made fuses in bulk-example 3AG 2 regular price .23 each our price .12 each. Factory packaged GE transistors at discounts. Example GE-20 regular price \$1.10 our price .65. Request circular on your letterhead. David Sims Enterprises, Inc., 665 East Jericho Tpke., Huntington Sta., NY 11746, 800-645-5030, NY State (516) 549-3925-1592. 10-82-tfn

**TUBES** — Receiving, Industrial and Semi-conductors, factory boxed. Free price list. Low; low prices. **TRANSLETERONIC INC.**, 1365-39th Street, Brooklyn, NY 11218E, 800-221-5802, 212-633-2800. 5-82-tfn

**TV TROUBLE ANALYSIS TIPS.** Over 300 symptoms/ remedies by circuit area; tough ones over the years. Save time and money. Send \$12.50 to CHAN TV, 8151 Grandview Rd., Chanhassen, MN 55317, 5-82-tfn

**PRINTED CIRCUIT** boards from your sketch or artwork. Affordable prices. Also fun kit projects. Free details. **DANOCINTHS INC.** Dept. ES, Box 261, Westland, MI 48185. 5-81-tfn

**SONY-PANASONIC-RCA-ZENITH-EXACT REPLACEMENT PARTS-LARGE INVENTORIES-SEND PART OR MODEL NUMBERS-WILL UPS OR COD-GREEN TELE-RADIO DISTRIBUTORS, 172 SUNRISE HIGHWAY, ROCKVILLE CENTRE, NY 11570. 5-82-tfn**

**AUTOMOBILE RADIO** and tape replacement parts: Delco, Chrysler, Philco-Ford, Motorola, Panasonic and many others. Large inventory. Laran Electronics, Inc., 3768 Boston Road, Bronx, NY 10469. (212) 881-9600, out of New York State (800) 223-8314. 5-79-tf

**COLOR PICTURE TUBES** direct from manufacturer. Prices from \$55 to \$75 exchange. One year warranty. Send your old tube ups to ATOLL Color Tubes, 6425 West Irving Park, Chicago, Illinois 60634. Phone: 312-545-6667. We also sell equipment for rebuilding CRT's. 9-83-3t

## FOR SALE (CONT.)

**ATTENTION TECH/SHOP OWNERS**—Profits getting smaller with increasing cost of parts? Take advantage of our buying power and huge inventory on well known electronic products and replacement parts. Prices below dealer cost. Write for information. United Services Assoc., Old Grand Union Shopping Ctr., Rt. 9W, Stony Point, N.Y. 10980, 914-942-2173. 7-83-tfn

**CB RADIO BOOKS**, kits, modifications. Catalog \$1.00 refundable. APS, POB 263, Newport, RI 02840. 6-83-121

**TV/FM SWEEP/MARKER GENERATORS:** Sencore SM-152, cost \$450, sell \$195. Leader LSW-333, cost \$775, sell \$495. Spectrum Analyzer, Polarad SA-84W, 10MHz to 40GHz, \$295. Barlowe, Box 293, Bethpage, NY 11714. 9-83-11t

**SOUTHERN CALIFORNIA SALES AND SERVICE OPERATION** available; Over .2 million gross 1982; Thirteen years in area with excellent growth and high visibility. Audio/Video Sales and Servicenter, 26837 Bouquet Canyon Road, Saugus, California 91350, 805-255-5562. 9-83-31t

**TELEVISION SALES & SERVICE**, Established 1941, owner retiring, \$20,000 and will lease building. Phone 919-835-2302. Elkin, North Carolina, Nites only. 9-83-21t

**PICTURE TUBE REBUILDING EQUIPMENT:** Small or Medium Plant Operation. Production Capability—12 to 28 High Quality Tubes Daily. Call or write: TELECO, 2610 E. Busch Blvd., Tampa, FL 33612, 813-935-4002. 9-83-21t

**NEW RADIO**—Television tubes, some old and scarce types. Also radio—TV schematics for sets since 1946. Send a large S.A.S.E. to Maurer TV, 29 South 4th Street, Lebanon, PA 17042. 9-83-11t

**ANTIQUE RADIO CATALOG:** 16 pages of tubes, parts, literature and more. Send \$1.00 to Antique Electronic Supply, 1725 W. University, Suite #2, Tempe, AZ 85281. 9-83-11t

**ADVENT VIDEO PARTS** and service available from professional electronics. Call 504-467-1717 for further information. 9-83-31t

**TV SHOP CLOSE-OUT:** all equipment two years old. Sencore VA48 Video Analyzer, CR31 Super Mack, Powerite Isolation, CA55 Cap Analyzer, MU150 Tube Checker, B&K 1820 Frequency Counter, 10J106 RCA Color Test Jig—Many adapters. Best offer, 206-473-1161. 9-83-11t

## HELP WANTED

**TV, VCR & STEREO TECHNICIANS NEEDED.** Live and work in sunny Orlando Florida near Disney World. Modern well equipped shop with latest test equipment. Full benefits. Non-smokers preferred. Opportunity of a lifetime! Call CHRISTIAN TV & STEREO SERVICE, 305-293-7288 TODAY! 9-83-11t

**TUNER TECHNICIAN** must have minimum of 5 years experience on tuner bench. Must know varactor and conventional tuners. Located in Dallas Texas area. Pay is \$5.00 per tuner. (817) 834-8201. 9-83-21t

## BUSINESS OPPORTUNITIES

**NORWALK, CALIFORNIA ESTABLISHED TV AND STEREO SERVICE AND SALES** very busy money maker, excellent location, low rent, very good lease, 2300 square feet, 10 minutes to beaches and Los Angeles. \$40,000 includes inventory, large enough for living quarters, owner retiring, phone 213-863-1919. 11-82-tfn

**TV TUNER REBUILDING BUSINESS, LOS ANGELES, CALIFORNIA** 23 years same location, other interests, requires sale very reasonable, (213) 342-4745. 7-83-tfn

**VIDEO CONVERSIONS**—earn extra profit converting older arcade games into the newer money-making models, complete info \$5.00 (refunded on first order) autonetec electronics, 3832 ellis, corona ca 91720. 9-83-11t

**SPEAKER RECONING:** Most makes, sizes, models. For prompt service send to Mercury Speaker Reconing, 2018 W. Division St., Chicago, Illinois, 60622; (312) 278-2211. 9-83-tfn

## Bus. Opportunity (Cont.)

"TELEVISION PLUS authorized service center 8-Manufactures, EVE 516 599-4374." 9-83-21t

**HIGH PROFITS—LOW INVESTMENT:** with our CRT rebuilding equipment. Complete training and technical assistance. Guaranteed result. Atoll Television, 6425 W. Irving Park, Chicago, Illinois 60634; PH 312-545-6667. 8-83-31t

**RAMPART SECURITY SYSTEMS DEALERS'** sales are booming. The Rampart Franchise Program offers ENORMOUS PROFIT POTENTIAL PLUS EXCITING RESIDUAL INCOME. Our success and reputation are a result of a total business format approach for the EXPLODING alarm market. Product, marketing and management training with complete backup has made success a reality for over 70 dealers. No experience necessary just a strong desire to succeed. Investment only \$15,000 backed by inventory. Call Bob Pollack (800) 523-8002 or write RAMPART INDUSTRIES, INC., 1 Oxford Valley, Suite 317, Langhorne, PA 19047. 8-83-tfn

**LEARN TO REPAIR HOME VIDEO GAMES IN YOUR OWN SHOP!** Did you know that more than 9 million HOME VIDEO games have been sold? Now you can learn to repair! Atari, Coleco, Intellivision, or Atari 400/800 computers in your own shop. Our courses are taught on VIDEO TAPE (Beta or VHS) and come with a manual containing all the necessary technical information you will need to do repairs. For more information or to order, call: Electronic Institute (800) 221-0834 (outside N.Y.) or (212) 377-0369 (in N.Y.) Customized live in shop training courses are also available, call for more information and price schedules. 7-83-tfn

**CENTRAL FLORIDA, RCA, Zenith Sales and Service.** High growth area, \$170,000.00 Gross. Will sell or lease shop building with separate three bedroom home. Write—435 Catamaran Dr. #58, Merritt Island, FL 32952. 9-83-11t

**FOR SALE: TV ELECTRONIC SERVICE BUSINESS,** located in East Tenn. on busy highway between two cities. Husband-wife team grossed over \$50,000 in 82. Easily expanded to sales, etc. In good building, reasonable rent, includes stock of parts—new and used. Approx. 1500 Sams, equipment to operate, no trucks. Owners Canadians, need to return this year, \$12,000. Cash only. Phone 615-477-8628. 9-83-11t

## WANTED

**WANTED FOR CASH:** 50, 53, 6AF6, 6HU8, 304TL, 4CX1000A, 4-1000A, all transmitting, special purpose tubes of Eimac/Varian. DCO, Inc., 10 Schuyler Avenue, North Arlington, New Jersey 07032. Toll Free (800) 526-1270. 5-82-tfn

# Advertisers' Index


Reader Service Number	Page Number
19	All Electronics Corp. .... 46
28	Antsco Corp. .... 54
22	Automated Production Equipment ..... 48
10	B&K Precision ..... 19
	Beta Electronics ..... 61
37	Chaney Electronics ..... 58
	Chemtronics, Inc. .... 27-28
	Cleveland Institute of Electronics ..... 27-28
40	Components Express ..... 60
41	Consolidated Electronics ..... 37-38, 64
34	Cook's Institute of Electronics Engineering ... 58
9	The Cooper Group ..... 15
	D.A.T.A. Books ..... 25-26
35	Dage Scientific Instruments ..... 58
21	Digitron Electronics Corp. .... 48
29	EPS ..... 55
	ETA ..... 55
11	Esco Hand Tools, Inc. .... 20
30	Electronic Specialists, Inc. ... 56
20	Electronics Book Club ..... 47
17	Global Specialties Corp. 37-38, 45
	Grantham College of Engineering ..... 58
32	Hykon Mfg. Co. .... 56
36	Jensen Tools Inc. .... 58
	Leader Instruments Corp. . 27-28
4,5	MCM Electronics ..... 1,5
	NRI Schools—
	Electronics Division ... 25-26
	NATESA ..... 54
	NESDA ..... 62
	Nippon Shokuhin Sangyo Co. .... 39-40
16	North American Philips ..... 43
31	Oelrich Publications ..... 56
12	Omintron Electronics ..... 21
33	Optima Electronics ..... 42
39	Ora Electronics ..... 59
1	PTS Corp. .... IFC
	Pace ..... 37-38
	Philips ECG ..... 17
25	Primefax ..... 39-40, 50
	RCA Distributor & Special Products ... 12-13, 22
	RCA Technical Publications . 23
	RNJ Electronics ..... 39-40
14	Howard W. Sams & Co. .... 41
38	Satellite TV Week ..... 58
2,3	Sencore ..... 25-26, BC
6	Simpson Electric Co. .... 7
13	Soltec ..... 24
23	A.W. Sperry Instruments Inc. .... 49
27	The Superior Electric Co. ... 52
	TCG/New-Tone Electronics ... 42
18	TeleMatic Div. of U.X.L. Corp. .... 46
7	Thordarson Meissner Inc. .... 9
24	Wahl Clipper Corp. .... 50
29,22	Winegard Co. .... 11,51
	Zenith Radio Corp. .... IBC

## To get more information...

on items advertised or described in this publication, use the Reader Service Card. As a free service for our readers, we forward your inquiry to the product's manufacturer. Reader Service Card is pre-addressed.

# CEI Consolidated Electronics, Inc.

## LCD 3 1/2 DIGIT DMM

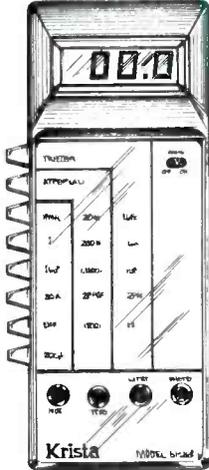

- 0.5" LCD display
- DC input impedance 10M ohm
- DC 100uV, 100mA, 0.1 ohm resolution
- DCA up to 10A
- Auto polarity
- Diode & hFE transistor tests
- Low battery indicator
- Overload protection

**SPECIFICATIONS:** Ranges: DCV: 200mV, 2, 20, 200, 1000V. ACV: 200, 1000V. DC CURRENT: 200u, 2m, 20m, 200m, 10A. RESISTANCE: 2K, 20K, 200K, 2M ohm. **Accuracy:** DCV: ±0.5%(200mV), ±0.8%(2V up) of full scale. ACV & DC CURRENT: ±1.2% of full scale. RESISTANCE: ±1%.

Size: 7" x 3 1/4" x 1 1/2"  
Weight: 16 oz.



PART NO.

**CE-537**

ONLY

**\$39.95**

## FREE T-SHIRT

W/ \$75.00 ORDER  
REG. \$7.95 ea.

**E.T.**  
ELECTRONIC TECHNICIAN



PLEASE SPECIFY SIZE  
WHEN ORDERING.  
MEN'S S,M,L,XL

## YOUR COMPLETE ELECTRONIC PARTS SOURCE!

### 2SC1172B

HORIZONTAL OUTPUT  
TRANSISTOR  
SIMILAR TO ECG® 238



#### ALSO REPLACES:

ECG 165	C1875	D350
C1172B	C1893	D368
C1174	C1922	D627
C1295	C1942	D649
C1413A	C1894	D380
C1309	D200	D663
C1358	D201	D869
C1454	D348	D870

ECG is a registered trademark

**\$1.79**    **\$1.95**  
100-up            10-99

REPLACEMENT STYLUS FOR

### SHURE M44-7

PART NO.  
**N-44**

**\$3.75**  
(1-9)

**\$3.50**  
(10 or more)



REPLACEMENT STYLUS FOR

### PICKERING V15-AT2

PART NO.  
**V-15**

**\$3.90**  
(1-9)

**\$3.50**  
(10 or more)



REPLACEMENT FOR

### ADC QLM 30 MK 111

PART NO.  
**CE-487**

- 3-5 gm. tracking
- 50-18K frequency response

**\$5.95**  
(1-9)

**\$4.95**  
(10 or more)



## SEMI SPECIALS

PART NO.	MIN. 10
<b>D613</b>	<b>50¢</b>
<b>C1306</b>	<b>95¢</b>
<b>C1307</b>	<b>\$1.75</b>
<b>C1226</b>	<b>40¢</b>
<b>AN214</b>	<b>\$1.25</b>

## CONTIPHONE™

- FCC Approved
- Bell Type Ringer
- European Style
- Automatic Redial
- Almond Colored

PART NO.

**7EI-100**

**\$27.95**  
1-4

**\$24.95**  
5-up



SEE MORE TELEPHONE ACCESSORIES IN OUR NEW CATALOG

MINIMUM \$10 ORDER  
NO MIXED QUANTITIES



**CONSOLIDATED  
ELECTRONICS  
INCORPORATED**

**1-800-543-3568**

NAT. WATS LINE

705 WATERLIET AVE., DAYTON OHIO 45420

**1-800-762-3412**


OHIO WATS LINE

IN DAYTON OHIO CALL 252-5662

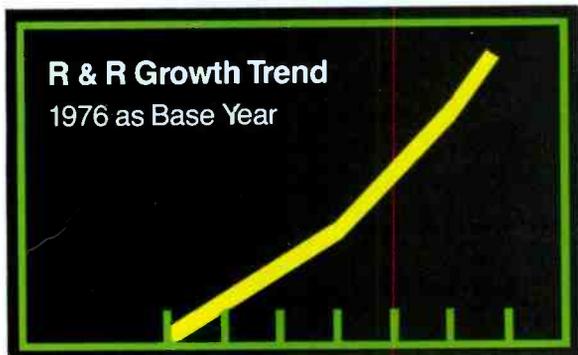**CALL TOLL FREE TODAY!**

Circle (41) on Reply Card

**We got bigger because  
we're better.**



**Now we're better  
because we're bigger.**

Year in and year out, Zenith's remanufacturing business gets bigger and bigger. And 1983 appears to be no exception.

That is why we are forecasting our remanufacturing business this year to be bigger than last year. Our remanufacturing business next year to be bigger than this year. And our remanufacturing business in the foreseeable future to be bigger and better each succeeding year.


But it's one thing to forecast and quite another to increase production year after year. That's why we at Zenith are thinking in terms of larger facilities and newer techniques in remanufacturing to meet the demand of the marketplace.

You should be as ready, willing and eager to look into the future as we have and, having seen the kind of growth we anticipate, position yourself as we have to meet and capitalize on it.

Right now you should be in the habit of purchasing a Zenith repaired and reconditioned replacement at your participating Zenith distributor's — with an exchange allowance in most instances — for every tired and worn-out module, tuner, channel selector and sub-assembly you remove from a Zenith TV.

Exchanging with your Zenith distributor is the one sure way to receive a genuine Zenith replacement part repaired, reconditioned and serviced for reliability by people as knowledgeable as those who made the original. And also a replacement updated to incorporate the latest factory technical improvements.

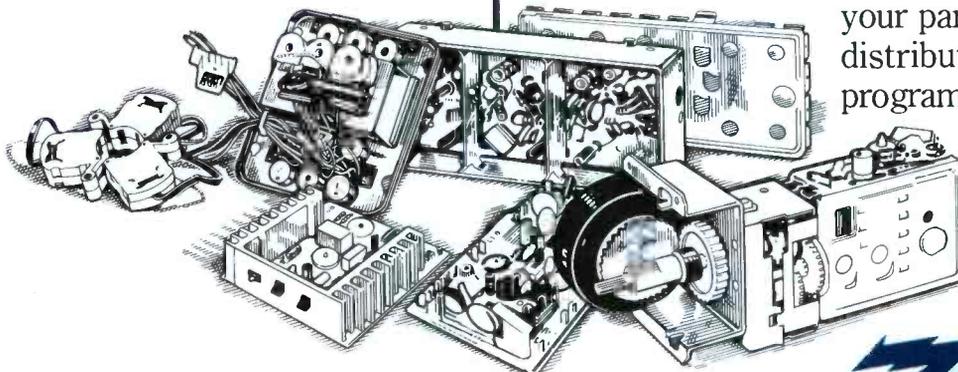Make sure you are taking advantage of your participating Zenith distributor's exchange program. Call now and tell the Zenith Parts Manager we sent you!



Zenith Radio Corporation/Service, Parts & Accessories Division  
11000 Seymour Avenue/Franklin Park, Illinois 60131

**ZENITH**  
The quality goes in before the name goes on.®

# Double Your Troubleshooting and Testing Productivity . . . Or Your Money Back!

**Six-digit readout:** Automatically tracks every CRT test. We call it digital autotracking. It's patent pending.

**Bright dual-trace CRT:** 60 MHz (-3 dB); 100 MHz (-12 dB).

**Delta PPV, Time, Freq:** Measure any part of a waveform for PPV, time or frequency using Delta measurements. Just dial in the waveform section you want to measure and push.

**Simplify Freq ratio tests:** Automatically compare input/output ratio of multiply/divide stages from 1:1 to 1:999,999 with the push of a button.



**Autotracking DCV, PPV, Freq:** Measure DCV to .5%; PPV to 2%; freq. to .001%. Just push a button for either Channel A or B.

**One probe input:** One probe input per channel for all measurements - digital and scope - with 5 mV to 2000 V measuring range. (2 lo-cap probes provided.)

**Super sync:** ECL provides rock-solid sync trigger circuits with only 4 controls; includes TV sync separators for video work.

U.S. Patent Pending  
Financing Available

**The first scope with push button digital readout.** If you use general purpose oscilloscopes for troubleshooting or testing, we can double your present productivity with the SC61 Waveform Analyzer, the first instrument to turn every conventional scope measurement into an automatic digital readout.

**No more graticule counting.** Connect only one probe to view any waveform to 100 MHz. Then, just push a button to read DCV, PPV, frequency and time — automatically!

There are no graticules to count or calculations to make, which speeds every measurement.

The digital readout is from 10 to 100,000 times more accurate as well.

Plus you have everything you want to know about a test point, at the push of a button, which speeds troubleshooting tremendously.

A special Delta function even lets you intensify parts of a waveform and digitally measure the PPV, time or frequency for just that waveform section.

And it's neat. No more tangled leads, piles of probes or dangling cords. The SC61 is an entire test station in one unit.

**The one and only.** There are other scopes with digital readout, but none of them completely automate every conventional scope measurement so you can automatically analyze any waveform without counting one single graticule. Totally automatic waveform analyzing at the push of a button. It will make all the difference in your productivity.

**Double your productivity.** When we say the SC61 will double your productivity, we're being conservative. We've seen cases of

three, four, even ten time increases in productivity with this first-of-its-kind, automated oscilloscope. Every situation is different, however, so try the SC61 and judge for yourself. Here's our offer.

**Money back guarantee.** If the SC61 does not at least double your productivity during the first thirty days, you may return it for a full refund, including freight both ways.

**Call today.** Get the entire SC61 Waveform Analyzer story. Call toll-free today, and ask for our eight page color brochure. It could be the most productive call you make this year!

**Phone Toll-Free  
1-800-843-3338**

Alaska, Hawaii, Canada and South Dakota call collect (605) 339-0100

**SENCORE**  
3200 Sencore Drive, Sioux Falls, SD 57107

For Information Circle (2) on Reply Card  
For Demonstration Circle (1) on Reply Card