

POPULAR ELECTRONICS

NOVEMBER
1956

35
CENTS

8 New Construction Projects
Intercom... Novice Beam... Signal Chaser... Crystal Set
Transistorized Timer... R/C Triplex... Receiver... Phono Player



Here it is!

the
All-New



HAMMARLUND HQ-100

COMMUNICATIONS RECEIVER

Keep up with the world—listen to radio programs from all countries—listen to the amateurs, ships, and many other interesting conversations. The whole wide world can be received like domestic stations on the brand-new Hammarlund HQ-100.

Variable selectivity permits you clear reception of even the most remote stations. Electrical bandspread tuning provides extra-accurate tuning in those crowded spots on the dial.

Many new and exciting features have been built into the new HQ-100. An amazing Auto-Response circuit automatically sets the audio characteristics for the very best performance on either communications or high-fidelity music.

This is not a reworked broadcast receiver, but a thoroughbred communications instrument made by the leading manufacturer of such receivers. See it and try it at your Hammarlund dealer.

**Complete technical information and
name of nearest dealer on request.**

Ask for bulletin P-11

only
\$169⁰⁰

*Teletimer automatic clock-timer switch for warm-up operation, \$10. extra

(Without Speaker)



Established 1910

HAMMARLUND

MANUFACTURING COMPANY, INC.,
460 West 34th Street, New York 1, N. Y.

BUILD THIS NEW FABULOUS MODULAR RADIO



Typical MODU-E
Supplied with Kit



Modular Construction eliminates use of individual resistors, capacitors and wiring.

Assemble this sensitive AC-DC Table Model Super Heterodyne Radio Receiver in less than 1/2 hour

ONLY \$17.50

Complete Kit with Tubes, Loudspeaker and Ivory Molded Cabinet



**NO WIRING
NO SPECIAL TOOLS
ONLY A SOLDERING
IRON REQUIRED**

In years to come, every radio, TV receiver, test instrument — in fact, every electronic device — will be modular constructed.

Be among the first to assemble a modular radio-broadcast receiver!

Supplied with easy-to-follow step-by-step instructions.

You have read about the Navy's 'Project Tinkertoy.' You have heard about 'Module' construction in military electronic applications.

This remarkable new pre-fab technique is now available to you — for the first time — in the first civilian product to feature both: PRINTED CIRCUITRY and MODULAR COMPONENTS.

Here is an exciting opportunity to work with one of the latest developments in modern electronics and learn about the new, fabulous module technique.

ACT NOW!

Send your check or money order... today!
10% required on C.O.D.

Use this convenient order form

R & D Electronic Laboratories Inc. Dept. PE-11
21-28 45th Road, L.I.C. 1, N.Y.

Send.....MODULAR RADIO KIT(S) at \$17.50.

I enclose check; money order in the sum of \$.....

In full payment — postage prepaid.

As 10% deposit for C.O.D. — I pay all charges.

NAME.....

ADDRESS.....

CITY.....ZONE.....STATE.....

All Parts Unconditionally Guaranteed

POPULAR ELECTRONICS

CONTENTS

FEATURE Articles and Electronic Developments

Electronic Election Bet.....	Herbert Reid	39
See Who's on the Phone.....		41
Tricked-up Cathode Rays Are "On the Beam".....	H. H. Fantele	43
Drive-In Church Attracts Motorist Congregation.....		51
Electronics on the Fishways.....	Margaret Magna	60
Radar Tames the Wild Blue Yonder.....	Shane Smith	74
Electronics Comes to Drive-In.....	Stanley Clark	92

ELECTRONIC Build-It-Yourself Projects

The "Tirade Terminator".....	Harvey Pollack	47
Capacitor Duo-Decades for the Experimenter.....	Frank H. Tooker	56
Transtopic Experiment No. 12—Electronic Timer	Louis E. Garner, Jr.	59
The "Economy" Signal Chaser.....	Richard Graham	63
Storing Small Components in the Workshop.....	Robert B. Kuehn	65
Handy Connections for Ferrite-Rod Loop Antennas.....	Art Trauffer	65
Long-Wave DX'er—a Single-Tube Receiver.....	Frank H. Tooker	66
Progressive Crystal Receiver.....	Carl Dunant	73
A Beam and Tower for the 15-Meter Novice.....	William I. Orr	78
R/C Triplex—Three Controls on One Channel	Claude McCullough	86
Novel Probe Adds Range to Your VOM.....	Robert G. Middleton	88
A First Project—Putting Together a Clock Radio.....	Allen C. Trainer	89
The Third Hand You Have Often Wanted.....	Clyde D. Adams	90

AUDIO and Hi-Fi Features

The Hi-Fi Boost.....	Leon Fields	53
What's New in Hi-Fi.....		70
Amplifierless Record Player.....	Art Trauffer	80
Mixing It Up.....	Richard H. Dubbe	84

Miscellaneous Electronic News

Simplified Radar to Use "Wamoscope".....		40
Electronic Alarm Guards Pools.....		42
Live TV to S.A.?.....		42
TV Turned Traffic Cop.....		42
Unique Video Generator.....		42
Chart Dials TV Troubles.....		46
Fast/Slow TV Scanner.....		46
Computer Speeds Supplies.....		46
Video Rig Checks Freight.....		46
Bell Shakes Them Up.....		52
Gas with a Kick.....		52
Good-Bye Barnacles.....		52
TV Peeks from Sky.....		52
Auto Antenna Replacement.....		72
Capacitors Use No Leads.....		72
Pocket Size Tester.....		72
Robot Helicopter.....		72
Metal Monitor.....		92

(Also see page 6 for DEPARTMENTS)

© 1956 by Ziff-Davis Publishing Company. All rights reserved.

Average Net Paid Circulation 240,151

NOVEMBER 1956

VOL. 5—NUMBER 5

Publisher
OLIVER READ, W1ETI

Managing Editor
OLIVER P. FERRELL

Technical Editor
CHARLES S. YEPFER

Feature Editor
NORMAN EISENBERG

Associate Editors
HANS H. FANTEL
MARGARET MAGNA

Contributing Editors
H. BENNETT **L. E. GARNER, JR.**
H. S. BRIER **H. POLLACK**
J. T. FRYE **R. P. TURNER**

Art Editor
ALFONS J. REICH

Art and Drafting Dept.
FRANK SAYLES
J. A. GOLANEK **M. WHELPLEY**
W. K. VAHLISING **J. A. ROTH**

Advertising Director
L. L. OSTEN

Advertising Manager
WILLIAM G. MCROY

Midwest Adv. Manager
JIM WEAKLEY

Western Adv. Manager
JOHN E. PAYNE



Member
Audit Bureau of
Circulations



ZIFF-DAVIS PUBLISHING COMPANY
W. B. ZIFF (1898-1953) FOUNDER

Also Publishers of
RADIO & TELEVISION NEWS
Editorial and Executive Offices
366 Madison Ave., New York 17, N. Y.
MU 7-8080

President
B. G. DAVIS

Vice-President
H. J. MORGANROTH

Vice-President
M. FROELICH

Vice-Pres. & Circ. Dir.
M. MICHAELSON

Secretary-Treasurer
G. E. CARNEY

Art Director
AL GRUEN

BRANCH OFFICES
CHICAGO (1)
64 E. Lake St., AN 3-5200
LOS ANGELES (14)
215 W. 7th St. (Room 412)
Trinity 8043

SUBSCRIPTION SERVICE:
All communications concerning subscriptions should be addressed to Circulation Dept., 64 E. Lake St., Chicago 1, Ill. Include your old address as well as new—enclosing if possible an address label from a recent issue of this magazine. Allow at least 4 weeks for change of address.

CONTRIBUTORS:
Contributors are advised to retain a copy of their manuscripts and illustrations. Contributions should be mailed to the New York Editorial Office and must be accompanied by return postage. Contributions will be handled with reasonable care, but this magazine assumes no responsibility for their safety. Any copy accepted is subject to whatever adaptations and revisions are necessary to meet the requirements of this publication. Payment covers all author's, contributor's and contestant's rights, title, and interest in and to the material accepted and will be made at our current rates upon acceptance. All photos and drawings will be considered as part of material purchased.

POPULAR ELECTRONICS



Train in Great Shops of COYNE for better jobs in ELECTRICITY - TELEVISION ELECTRONICS RADIO - COLOR TV



TWO TOP OPPORTUNITY FIELDS

Whether 17 or up to 45 years of age, train the Coyne way for a better job and a real future in **ELECTRICITY-ELECTRONICS** or **TELEVISION-RADIO**, fields that offer a world of opportunities. Train on real, full-size equipment at COYNE where thousands of successful men have trained for nearly 60 years—largest, oldest, best equipped school of its kind—established 1889. No advanced education or previous experience needed. Employment service to graduates. **START NOW—PAY LATER**—Liberal Finance Plans and Easy Payment Plans. Also part-time employment help for students. Training in Refrigeration and Electric Appliances can be included.

B. W. COOKE Jr., President

COYNE
ELECTRICAL SCHOOL

FOUNDED 1889

A Technical Trade Institute Operated Not For Profit
500 S. Paulina Street, Chicago, Dept. 86-71H

ELECTRICITY • RADIO • TELEVISION • REFRIGERATION • ELECTRONICS

MAIL COUPON FOR FREE BOOK

Send coupon for 48-page illustrated book "Guide to Careers in Electricity-Electronics and Television-Radio." No cost; no obligation; no salesman will call. Vets and Non-Vets get vital facts now!



B. W. COOKE Jr., President
COYNE ELECTRICAL SCHOOL
500 S. Paulina St., Chicago 12, Ill., Dept. 86-71H

Send **BIG FREE** book and details of your training offer. This does not obligate me and no salesman will call. I am interested in:

() Electricity-Electronics () Television-Radio

Name _____

Address _____

City _____ State _____

COYNE QUALITY TELEVISION RADIO - COLOR TV Home Training at Unbelievably Low Cost

The future is **YOURS** in **TELEVISION!**
A fabulous field—good pay—fascinating work—a prosperous future in a good job, or independence in your own business!

Coyne brings you **MODERN-QUALITY** Television Home Training; training designed to meet Coyne standards at truly lowest cost—you pay for training only—no costly "put together kits." Not an old Radio Course with Television "tacked on." Here is **MODERN TELEVISION TRAINING** including **Radio, UHF and Color TV**. No Radio background or previous experience needed. Personal guidance by Coyne Staff. **Practical Job Guides** to show you how to do actual servicing jobs—**make money early in course**. Free Lifetime Employment Service to Graduates.

B. W. COOKE, Jr.,
President




Coyne—the Institution behind this training... the largest, oldest, best equipped residential technical institute kind. Founded 1889.

COYNE
ELECTRICAL SCHOOL

A TECHNICAL TRADE INSTITUTE OPERATED
NOT FOR PROFIT


500 S. Paulina Street, Chicago 12, Dept. 86-HT7

November, 1956

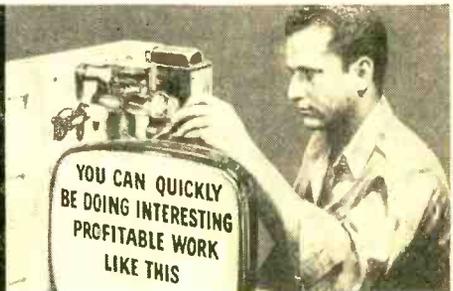

Send Coupon for Free Book

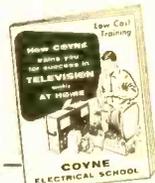and full details, including easy Payment Plan. No obligation, no salesman will call.



COYNE Television Home Training Division

500 S. Paulina St., Chicago 12, Ill.
Dept. 86-HT7

Send Free Book and details on how I can get Coyne Quality Television Home Training at low cost and easy terms.


Name _____

Address _____

City _____ State _____

DEPARTMENTS

Carl & Jerry.....	John T. Frye	10
Letters from Our Readers.....		26
POP'tronics Bookshelf.....		34
Transistor Topics.....	Lou Garner	57
Sound Impressions.....		71
After Class.....		76
The Transmitting Tower.....	Herb S. Brier	81
Tuning the Short-Wave Bands.....	Hank Bennett	91
Tips and Techniques.....		98
Tools and Gadgets.....		102

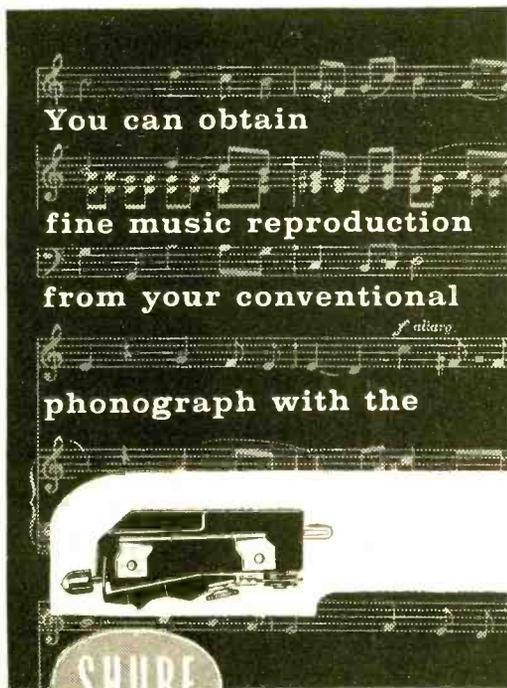

"Twin Lever" Ceramic Phono Cartridge

The WC10 "Twin-Lever" Improvement Cartridge will dramatically improve the tone quality of your conventional home phonograph—will actually make it better than new! The low price of the "Twin-Lever" permits anyone to enjoy the luxury of faithful reproduction of recorded music.

This remarkable cartridge replaces practically all three-speed, plastic-cased cartridges, crystal or ceramic, turnover or single needle.

It is easily installed in any tone arm with standard 1/2" mounting centers. Needle replacement can be accomplished in seconds—without tools—with the cartridge in the arm.

MODEL WC10

List Price..... \$9.50
with two sapphire needles

MODEL WC10D

List Price..... \$34.00
with a 1-mil diamond and
a 3-mil sapphire needle




The Mark of Quality
"IN ELECTRONICS SINCE 1925"

SHURE BROTHERS, INC.

Microphones—Electronic Components

214 HARTREY AVENUE • EVANSTON, ILLINOIS

COMING NEXT MONTH (DECEMBER)

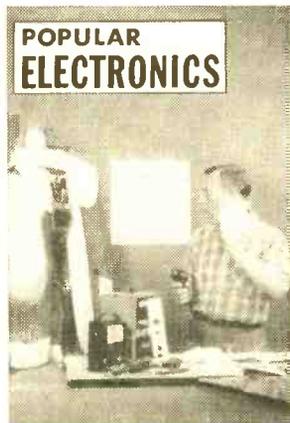

(ON SALE NOVEMBER 20)

In accordance with our annual Christmas custom, there will be several projects for both adults and children: "A Child's Radio," "Electronic Tiddly-Winks," "Electronic Roulette," and "Electronic Harmonica." Also look for construction details on the "Economy" audio signal generator and a simple converter for long-wave DX'ing.

Other assorted subjects include: how the effect of an atomic bomb on huge population centers is "tested" with an elaborate computing system; the electronic "composer" and the two-ton monster that plays every imaginable musical instrument; how to listen to police calls; the purpose of a loudness control in hi-fi amplifiers.

IN THIS MONTH'S RADIO & TELEVISION NEWS

(NOVEMBER)

The "Distributed Port" Loudspeaker Enclosure

All-Transistor Hi-Fi Amplifier

An Air Raid Alarm for Home Receivers

How to Choose a Tape

The "Electro-Tach"—An Electronic Tachometer

LOOKING FOR JOB SECURITY AND SUCCESS?

LET MY STUDENTS AND GRADUATES TELL YOU

ABOUT MY TRAINING—

\$60 A WEEK IN SPARE TIME



I have the skill and know-how to do the work I love best and to enjoy better things in life, thanks to RTTA. I am working at TV servicing and making \$60 a week sparetime.

Harold Gimlen, Flint, Mich.

AIRCRAFT INSPECTOR



With RTTA training and through repairing radios and televisions for the right people at the right price, I was able to make the right contacts. I am now an Inspector for Douglas Aircraft at about \$125 a week.

Hugh Maddox, Los Angeles, Calif.

ELECTRICAL TESTER



RTTA training has helped me understand TV and many variations of simple circuits. The course covers all subjects very clearly. I am now an Electrical Tester for Western Electric Co. at \$83.42 a week.

Raymond Lapan, Burlington, N. C.

HAS OWN BUSINESS



I have a shop at home and have been working on radio and TV after working hours of my regular job. I average \$50 a week for this part time work. RTTA training helped me in making extra money and giving me experience in the electronic field.

Richard Hennis, Little Rock, Ark.

SERVICE MANAGER



I manage two radio and television shops, one here and one in Pompano Beach. RTTA training increased my knowledge of TV circuits and showed me new, quicker methods of repairing. Lessons as presented are very concise and clear.

William Phillips, Fort Lauderdale, Fla.


REPAIRED EVERY SET



RTTA training helped me to understand TV more thoroughly. I have repaired every set that I was called on to repair.


Andrew Busi, Jr., Iselin, Pa.

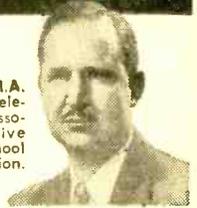L. C. Lane, B.S., M.A.
President, Radio-Television Training Association.
Executive Director, Pierce School of Radio & Television.



— ABOUT MY EQUIPMENT

YOU GET ALL THIS EQUIPMENT

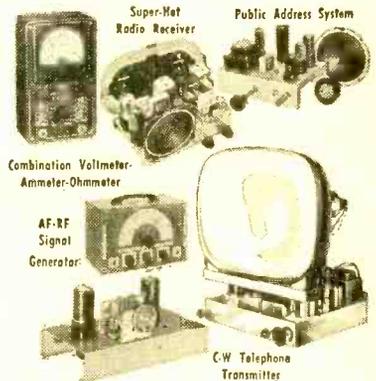

"... a money making little gem."
I have completed kit #6 and was amazed at how it works. I showed it to a friend of mine and he asked me to set it up for one of the picnics his social club was having. That sure is a money making little gem.
John Fernandez, Fresno, Calif.

"We get excellent pictures..."
I would like to compliment you on an excellent and complete course. We get excellent pictures on my TV set from WSYR (Syracuse, N.Y.), approximately 110 air miles away. The set is working good and I have had to replace only three tubes since I assembled it two years ago.
Larry M. Stafford, Kingston, Ont., Canada

"... very good reception..."
I have really enjoyed the course and have come a long way in TV servicing. I am getting very good reception on my TV station considering that the nearest VHF station is 120 miles.
J. W. Hanlon, Jr., Henderson, Texas

YOU, TOO, CAN GET A BETTER-PAYING JOB IN THE EVER-EXPANDING RADIO-TELEVISION-ELECTRONICS FIELD

Why limit yourself and your earnings because of your lack of training. Learn **AT HOME** in your **SPARE TIME** to be an electronic technician, television repairman, or studio technician. You don't need any experience whatsoever.

After you finish my Radio-FM Television Course or FM-Television Course you can have, if you want it, two weeks of laboratory training at my associate resident school in New York City—**AT NO EXTRA COST.**

If you have had previous radio and television experience you can take my practical TV Studio Technician Course to qualify for a good-paying job in a TV studio.

Write to me today and let me show you how you can begin now to put yourself on the road to a better future.

VETERANS!

My school fully approved to train veterans under new Korean G.I. Bill. Don't lose your school benefits by waiting too long. Write discharge date on coupon.


Radio-Television Training Association

52 EAST 19th STREET • NEW YORK 3, N. Y.

Licensed by the State of New York • Approved for Veteran Training

November, 1956

YOU GET THESE FREE

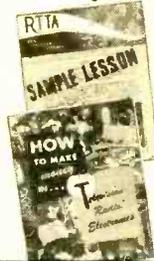

MAIL THIS COUPON TODAY!

Mr. Leonard C. Lane, President
RADIO-TELEVISION TRAINING ASSOCIATION
Dept. PE-11C, 52 East 19th Street, New York 3, N. Y.

Dear Mr. Lane: Send me your NEW FREE BOOK, FREE SAMPLE LESSON, and FREE aids that will show me how I can make TOP MONEY IN TELEVISION. I understand I am under no obligation.

(PLEASE PRINT PLAINLY)

Name _____ Age _____

Address _____

City _____ Zone _____ State _____

- I AM INTERESTED IN:
- Radio-FM-TV Technician Course
 - FM-TV Technician Course
 - TV Studio Technician Course


VETERANS!

Write discharge date

**BUILD THE
BEST
AND SAVE!**

**you get the most for your money when you build
ALLIED'S own knight-kits**

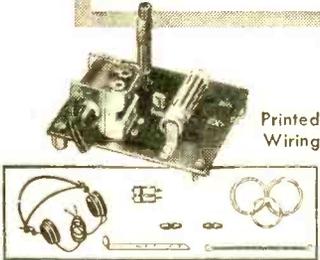- ★ You get maximum value for your kit dollar
 - ★ You get advanced design and top performance
 - ★ You get easiest-to-follow instructions for assured success in the finished equipment
 - ★ You get premium quality parts
 - ★ You get exclusive new features
- BUY WITH CONFIDENCE FROM THE PIONEERS IN ELECTRONIC KITS**



Printed Wiring


**Fascinating knight-kit
TRANSISTOR RADIO KIT**

Model S-765 Experiment with the marvel of transistors! Printed circuit mounting board simplifies assembling. Just mount components, solder a few connections and enjoy excellent AM broadcast reception. Compact; fits in palm of your hand; operates from single penlight cell that lasts for months. Complete with all parts, transistor and penlight cell. Easy to assemble. Shpg. wt., 2 lbs.

only \$4.35

Model S-765. Net only **\$4.35**

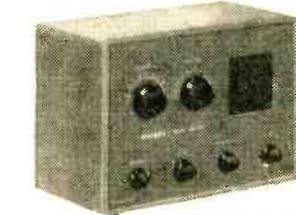S-266. Accessory kit; 4000 ohm double headphones and all parts for outdoor antenna. Net. **\$3.15**




**knight-kit "SPACE-SPANNER"
BANDSWITCHING RECEIVER KIT**

Model S-243 All-new 2-band receiver, easy to build—a great value. Band-switch selects thrilling short wave, including amateur, aircraft, police and marine radio (6 to 18 mc), and standard broadcast. Highly sensitive regenerative circuit. Has 4" PM speaker and beam-power output for strong volume. Kit includes calibrated panel, punched chassis, all parts and tubes (less cabinet). Easy to build. 7 x 10 1/2 x 6"; for 110-120 v. 50-60 cycle AC or DC. Shpg. wt., 4 1/2 lbs.

only \$15.95

Model S-243. Net only **\$15.95**

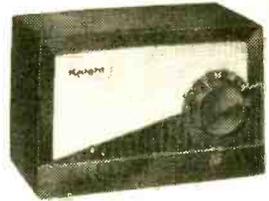S-247. Matching cabinet for above **\$2.90**



**knight-kit "RANGER II"
AC-DC SUPERHET RADIO KIT**

Model S-735 Build this top quality table model radio at low cost! Tunes full AM broadcast, 540 to 1680 kc (includes police calls). Features Alnico PM dynamic speaker; automatic volume control; sensitive Superhet circuit; handsome plastic cabinet. Easy, step-by-step assembly. Complete with punched chassis, all parts and tubes, speaker and smartly styled bakelite cabinet (6 x 9 x 5"). For AC or DC. Shpg. wt., 8 lbs.

only \$17.25

Model S-735. Net only **\$17.25**




**knight-kit TWO-WAY
INTERCOM SYSTEM KIT**

Model S-295 Easy to build—ideal for home or office. Consists of Master and Remote unit, each with press-to-talk switch. Remote can be left "open" for distant answering or baby-sitting. In "closed" position, Remote remains private, but can be called and can originate calls. High-gain 2-stage amplifier and 4" PM speakers. With tubes and 50-ft. cable. (Up to 200-ft. may be added.) Each unit 4 3/4 x 6 1/2 x 4 3/8"; antique white finish. For AC or DC. Easy to assemble. 7 lbs.

only \$14.75

S-295. Net only **\$14.75**

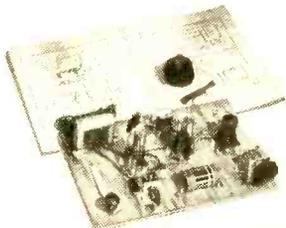

knight-kit 10-IN-1 LAB KIT

Model S-265 Instructive, fascinating! Enables you to build any one of 10 circuits: Broadcast receiver for headphone reception; Phono Oscillator to play records through any radio; Phono Amplifier; Code Practice Oscillator; Signal Tracer; Electronic Timer; Relay, etc. Includes tubes, all parts, instructions (less photo-tube and socket, and headphone). Ready to build. For 110-120 v., 50-60 cy. AC. 10 lbs.

only \$12.65

Model S-265. Net only **\$12.65**

J-112. Headphone for above. **\$1.05**

C-100. Antenna Kit for above. **\$1.05**



IDEAL KIT FOR THE HAM

Model S-255 only **\$43.75**

**knight-kit 50-WATT
CW TRANSMITTER KIT**

Compact, value-packed, low-power rig. 50 watts input to 807; 6AG7 oscillator takes crystal or VFO; bandswitching covers 80, 40, 20, 15, 11-10 meters; pi matching network eliminates separate antenna tuner; clean cathode keying of oscillator and final; excellent TVI suppression; meter reads plate or grid of final. With all parts, tubes, wire, solder and instructions (less key and crystal). 8 1/4 x 11 1/4 x 8 3/4". 18 lbs.

Model S-255. Net only. **\$43.75**

order from **ALLIED RADIO** 100 N. WESTERN AVE., CHICAGO 80, ILL.

YOU BUILD THE BEST AND SAVE MORE WITH knight-kits



**knight-kit
VTVM KIT**
with printed
circuit board

Model F-125
only **\$24⁹⁵**

Easy to build. Reads peak-to-peak. 1% resistors. Balanced-bridge push-pull circuit; 4 1/2" meter, 200 microamp. Ranges: AC peak-to-peak volts, 0-4-14-40-140-400-1400-4000; AC rms v. and DC v., 0-1.5-5-15-50-150-500-1500; ohms, 0-1000-10K-100K, 1-10-100-1000 meg; db scale, -10 to +5. Zero-center scale; direct-reading db scale; polarity reversing switch. Ready to build. 7 1/4 x 5 1/4 x 4 3/8". 6 lbs.

Model F-125. Net only.....**\$24.95**

F-125. High Voltage Probe.....**\$4.75**

F-127. High Frequency Probe...**\$3.45**



**knight-kit
20,000 OHM/VOLT
VOM KIT**

Model F-140
only **\$29⁵⁰**

Low cost 32-range VOM. Features 4 1/2" 50-microampere meter; 1% precision multipliers; 2% accuracy full-scale deflection. Ranges: AC, DC and output volts, 0-2.5-10-50-250-1000-5000; Resistance, 0-2000-200,000 ohms and 0-20 meg; DC ma, 0.1-10-100; DC amps, 0-1-10; Decibels, -30 to +63 (6 ranges). Black bakelite case, 6 3/4 x 5 1/4 x 3 3/4". Ready to build. 5 lbs.

Model F-140. Net only.....**\$29.50**



**knight-kit
'IN CIRCUIT'
CAPACITY
CHECKER KIT**

Model F-119 only **\$12⁵⁰**

Remarkable unit checks capacitors while they're still wired in the circuit! All you do is press a button—and the "magic eye" shows opens and shorts. Tests opens and shorts on capacitors of 20 mmf or greater, even if in parallel with a resistance as low as 50 ohms. Complete; ready to build. 5 lbs.

Model F-119. Net only.....**\$12.50**




**FREE 356-PAGE
1957 CATALOG**

It's your money-saving guide to everything in Electronics, featuring more than 25 other KNIGHT-KITS, including Test Instruments, Hobbyist Kits and Amateur Kits. Send for it!

ORDER NOW →

November, 1956

BUILD YOUR OWN QUALITY HI-FI AND SAVE!

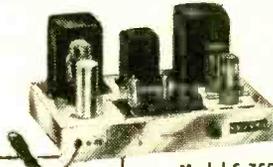

**knight-kit LINEAR-DELUXE
BASIC 25-WATT HI-FI
AMPLIFIER KIT**

Custom quality at very low cost. For use with any tuner or preamp with full set of controls. Deluxe features: Chrome-plated chassis; potted transformers and chokes; printed circuit wiring board; balance and damping controls. *Output:* 25 watts. *Response:* +0.5 db. 10 to 120,000 cps at 20 watts.

Model S-755
only **\$44⁵⁰**

Distortion: 0.15% at 25 watts. *Speaker Outputs:* 4, 8 and 16 ohms. 6 1/4 x 14 x 9". With all parts, tubes, instructions; ready to build. Shpg. wt., 27 lbs.

Model S-755. Net only.....**\$44.50**

S-759. Metal enclosure for above; black finish....**\$4.25**



**knight-kit 10-WATT
ECONOMY HI-FI AMPLIFIER KIT**

True Hi-Fi at lowest cost. Only 0.5 volt drives amplifier to full 10 watts output! *Response:* +1 db, 30 to 20,000 cps at 10 watts. *Distortion:* less than 0.5% at 10 watts. Chrome-plated chassis is punched for preamp kit listed below. Matches 8-ohm speakers. With tubes, all parts, easy instructions. 7 x 13 x 6" Shpg. wt., 14 lbs.

Model S-753
only **\$23⁵⁰**

Model S-753. Net only.....**\$23.50**

S-235. Preamp kit (for magnetic cartridges).....**\$3.10**

S-757. Metal enclosure for above; black finish....**\$3.95**




**knight-kit 20-WATT
LOW COST HI-FI AMPLIFIER KIT**

Delivers deluxe Hi-Fi sound. Includes built-in preamp; inputs for magnetic cartridges, etc.; record compensator; bass and treble controls, etc. *Response:* +1 db, 20-20,000 cps at 20 watts. *Speaker Outputs:* 4, 8, 16 and 500 ohms. Chrome-plated chassis, 7 1/2 x 13 x 8 1/4". With all parts, tubes and easy instructions. 23 lbs.

Model S-750
only **\$35⁷⁵**

Model S-750. Net only.....**\$35.75**

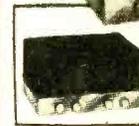S-758. Metal enclosure for above; black finish....**\$4.15**



ALL PRICES NET F. O. B. CHICAGO • EASY TERMS AVAILABLE

ALLIED RADIO

ALLIED RADIO CORP., Dept. 079-L-6
100 N. Western Ave., Chicago 80, Ill.

OUR
36th
YEAR

Ship me the following KNIGHT-KITS:

Quantity	Description	Model	Price


\$ _____ enclosed. For parcel post, include postage (express is shipped collect).

Send me your FREE 1957 ALLIED 356-Page Catalog.

Name _____

Address _____

City _____ Zone _____ State _____

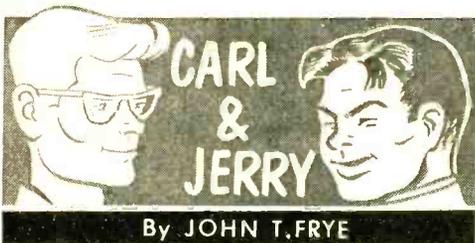

Eeeeelectricity!

CARL WAS JUST ARRIVING home after spending a short week-end vacation with an aunt and uncle in Chicago. He burst in the front door; yelled "Hi, Dad!"; planted an awkward kiss on the bridge of his mother's nose; and sailed right on out the back door, across the yards, and into the basement laboratory of his neighbor and best friend, Jerry Bishop.

Jerry was there all right, and he was just as glad to see his pal as Carl was to see him; but it was against the Code of Boyhood to show their feelings. Jerry hardly looked up as he grunted a greeting. To tell the truth, though, he was pretty busy trying to strap a squirming, wriggling *something* into the concave side of a short section of gutter trough. It kept slithering through the rubber gloves he was wearing.

"Holy cow, Jer, what is that thing?" Carl demanded. "Is it a snake?"

"Of course not, stupid. It's an eel that my uncle in the Navy sent me from South America. I want to make some tests on it. Put on that other pair of rubber gloves and help me fasten it in this trough."

"Not on your life!" Carl said emphatically as he backed toward the door. "I wouldn't touch that snaky-looking thing with a ten-foot pole, let alone my hands. Why on earth would your uncle send you something like that? Has he sprung his hatch?"

"Certainly not. This is not just an ordinary eel. In fact, it's not really an eel at all. Strictly speaking, it's an electric fish. My uncle says if I'm going to be an electronics engineer I should know about all forms of electricity; and electric fishes have been stirring electrons for thousands of years. Pictures of them appear in Egyptian tombs and they are mentioned in Aristotle's *Historia Animalium*. In addition to this so-called electric eel, there are five other fishes with shocking power: the torpedo or electric ray, the electric catfish, the star-gazer, the numb-fish, and the elephant-snout fish."

"NEVER MIND the lecture, Professor," Carl said impatiently. "Just tell me

The newest hobby under the sun!

BUILD THIS SOLAR POWERED RADIO!

and many other sun-powered electronic, electrical and photometric devices featuring International Rectifier Corporation SUN BATTERIES!

Everyone—from the beginner with a basic understanding of electrical work to the experienced professional engineer—can build this pocket-size portable radio—powered by the sun! No batteries—not even an On-Off switch. All you need is sunshine! The basis for this radio is the International B2M Sun Battery. This unit is a scientific, accurate, precision-made photovoltaic instrument that directly converts light into electrical energy. This radio is just one of many devices you can build powered by solar energy. You have read about this new field of science. Be among the first in this newest hobby. Put the sun to work for you!

THIS NEW BOOK TELLS YOU ALL ABOUT SUN BATTERIES—PHOTOCELLS—AND HOW TO USE THEM. Packed with information and applications, this illustrated book shows wiring, diagrams and plans—every detail necessary to build many interesting devices.

\$1.50

THIS IS THE FAMOUS B2M SUN BATTERY YOU'VE READ ABOUT. Widely used in experiments, this unit in bright sunlight (10,000 ft. candles) will deliver 2 milliamperes at 250 millivolts under optimum conditions, will last indefinitely with proper care. A \$2.50 value for only.....\$1.50



FREE

Complete plans for building this radio. At your electronic parts distributor.

GET THE B2M SUN BATTERY AND ALL OTHER COMPONENTS REQUIRED AT LEADING ELECTRONIC PARTS DISTRIBUTORS EVERYWHERE. If your favorite distributor doesn't feature the B2M Sun Battery send check or money order to

International Rectifier Corporation
El Segundo, California

SPECIAL OFFER, The book and the B2M Sun Battery for only \$2.85 at your distributor

NOW in YOUR OWN HOME!



ELECTRO-LAB

LEARN AUTOMATION ELECTRONICS

TELEVISION

RADIO • ELECTRONICS

FASTER and EASIER with the aid of

DTI EXCLUSIVE TRAINING FEATURES

EXCLUSIVE! Only DTI Provides Visual Aid Motion Pictures AT HOME

One of the most helpful . . . most modern aids to learning, is motion pictures AT HOME. They are an important part of your DeVry home training. Through the magic of films, you see electricity in action, you see electrons "inside" of a circuit . . . and other important principles of electricity and electronics. DeVry loans you a special movie projector and a series of highly instructive movie films that enable you to see these principles quickly . . . easily . . . and in a much shorter time than by reading alone.



OPPORTUNITIES ARE GROWING

The vast Electronics field is growing fast! It is calling for skilled technicians to step into good jobs paying real money. These are interesting positions—in plants . . . TV studios . . . laboratories . . . offices . . . radio stations . . . plus equally wonderful opportunities for starting a profitable full time or part time sales and service business of your own.

Electronics offers a real future! With over 400 TV stations on the air, with more than 30 million TV sets in use, with so many opportunities opening up in Radio Broadcasting, Communications, Instrumentation, Military Electronics and the newer field of Automation Electronics, the need for skilled personnel is increasing.

But to make progress in this fast-moving field you need real KNOW-HOW—the kind you get from an industrial training program—the kind you get from DEVRY TECHNICAL INSTITUTE.

Yes, you get the benefit of a program geared to the needs of industry, and backed by our 25 years of experience in helping men prepare for good jobs or their own business.

EXCLUSIVE! The Unique ELECTRO-LAB[®] (obscure) Provides Needed Practical Experience

To make real progress, you need practical experience. That's the reason you get and KEEP the recently-developed DeVry Electro-Lab. Using its transparent base, you see each circuit top and bottom; you follow special diagrams—quickly attached and detached. You use quick-opening spring clip connectors that cut time-consuming soldering to a minimum. You build circuits faster . . . learn more thoroughly.

Altogether you get 16 shipments of fine quality parts. You perform over 300 practical projects, including the building of the versatile 5-inch Oscilloscope and the sensitive, multi-range Vacuum Tube Voltmeter both shown at right. No need to buy this valuable test equipment elsewhere. You build it . . . use it . . . KEEP it, as part of your training.
*Trademark



EMPLOYMENT SERVICE


DTI's efficient Employment Service is ready to help you make your start in the field when you complete the training. Over the past 25 years, we have built up hundreds of contacts with employers of Electronic specialists. You even get valuable advice on starting and operating your own business!

MILITARY SERVICE

If you are subject to military service, we have important information for you.

GET PRACTICAL TRAINING IN CHICAGO

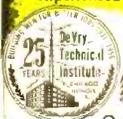If you desire, you can get all of your preparation in our large, well-equipped Chicago training center . . . under expert supervision of experienced instructors. Ask for details!



Member of
National Home
Study Council

One of America's Foremost Electronics Training Centers

DEVRY TECHNICAL INSTITUTE
CHICAGO 41, ILLINOIS
FORMERLY
DEFOREST'S TRAINING, INC.

MAIL COUPON FOR DETAILS!



DEVRY TECHNICAL INSTITUTE
4141 Belmont Ave., Chicago 41, Ill. Dept. PE-11-M

Please give me a copy of "89 Ways to Earn Money in Television-Radio-Electronics," together with facts about the opportunity fields I have checked below.

- TELEVISION COMMUNICATIONS RADIO
- NUCLEAR INSTRUMENTATION AUTOMATION ELECTRONICS

Name _____ Age _____
(PLEASE PRINT)

Street _____ Apt. _____

City _____ Zone _____ State _____

1021A DTI's training is available in Canada.

Perfect Pair...



CK722 and CK768

TRANSISTORS

You won't find a better performing, easier to use, less expensive combination than these two, top-quality Raytheon Transistors.

The CK768 is specially designed for RF application with the Raytheon CK722 for audio circuits. They pair up perfectly. Yet the CK722 costs but 99¢, the CK768 only \$1.50 — \$2.49 for the best transistor combination that money can buy. Available from stock through your Raytheon Tube Supplier.

Get the Raytheon
TRANSISTOR APPLICATIONS BOOK
116 pages — over 50 practical circuits — using low cost Raytheon Transistors. For your copy send 50¢ to Raytheon, Dept. P7.



Excellence in Electronics

RAYTHEON MFG. CO.

Receiving and Cathode Ray Tube Operations
Newton 58, Massachusetts

Carl & Jerry (Continued from page 10)

what you are trying to do with old Squirmy there."

"I want to strap him in this rubber-lined trough so I can find out something about the electric charge he emits. The rubber lining will prevent his being short-circuited by the metal trough. When I get him fastened down, I'll slide these little tin-foil strips underneath his body at different points to pick off the charge he emits. Then, by using the 'scope and the VTVM, I'll know if he has a.c. or d.c. wiring and how much voltage he puts out."

"You mean you don't have any idea what to expect? And are you wearing those rubber gloves because you don't want to touch the slimy thing or because you're afraid of being shocked?"

"To answer the last first, I'm wearing them cause I don't want to be shocked. A full-grown electric eel can put out a jolting five-hundred volts that can stun a horse or paralyze a man. Since eight feet is about as long as they get, and since this one is nearly five feet long, I'd guess he was full grown. He acts fully charged, too. An adult eel that puts out only three hundred volts is either sick or simply not letting himself go. Even a baby eel can deliver around 120 volts—as much voltage as there is in the a.c. house line."

"How do you know all this? You been boning up at the library?"

"Yes, and I got a lot more information



... Jerry was trying to strap a squirming, wriggling something into the short section of gutter trough, but it kept slithering through his rubber gloves ...

Always say you saw it in—POPULAR ELECTRONICS

HERE'S HOW YOU CAN MAKE BIG MONEY IN ENGINEERING!

Because of the critical engineering shortage you don't have to be a graduate engineer to win lifetime success

Pick up a newspaper. Turn to Help Wanted. Look as far as "E." The paper's black with big ads offering big pay for engineers. It's the country's most critical shortage — and one that isn't going to be overcome for many long years.

You're not an engineer, you say. You don't even have a college degree.

O.K.

If you've got brains, if you've got ambition, if you've got the sheer determination to work and *be* somebody — you can win a secure place in engineering.

Each year, I. C. S. prepares thousands of men just like you for a lifetime career in engineering. In just a few short months, many begin

a fast move upward with positions as engineering aides, and with healthy boosts in pay.

How about *you*? Tired of the treadmill you're on? Take the first big step to success by sending in that I. C. S. coupon now. In your spare time, working at your own pace, you can ready yourself for a really big job — in a lot less time than you may think!

Send Coupon Now . . . Get Three Books Free!

These books free if you act now!

1. "How to Succeed"—a gold mine of career tips
2. Big catalog outlining opportunities in the field of your choice
3. Sample lesson text (math) showing clear, step-by-step I. C. S. method

For Real Job Security—Get an I. C. S. Diploma!

I. C. S., Scranton 9, Penna. Member, National Home Study Council

INTERNATIONAL CORRESPONDENCE SCHOOLS

65TH YEAR

BOX 15622K, SCRANTON 9, PENNA.

(Partial list of 256 courses)

Without cost or obligation, send me "HOW TO SUCCEED" and the opportunity booklet about the field BEFORE which I have marked X (plus sample lesson):

<p>ARCHITECTURE and BUILDING CONSTRUCTION</p> <input type="checkbox"/> Air Conditioning--Refrig. <input type="checkbox"/> Architecture <input type="checkbox"/> Architectural Interiors <input type="checkbox"/> Building Contractor <input type="checkbox"/> Building Estimator <input type="checkbox"/> Building Maintenance <input type="checkbox"/> Carpentry and Mill Work <input type="checkbox"/> Heating <input type="checkbox"/> Painting Contractor <input type="checkbox"/> Plumbing <input type="checkbox"/> Reading Arch. Blueprints <p>ART</p> <input type="checkbox"/> Cartooning <input type="checkbox"/> Commercial Art <input type="checkbox"/> Fashion Illustrating <input type="checkbox"/> Magazine Illustrating <input type="checkbox"/> Show Card and Sign Lettering <input type="checkbox"/> Sketching and Painting <p>AUTOMOTIVE</p> <input type="checkbox"/> Auto Body Rebuilding <input type="checkbox"/> Auto Elec. Technician <input type="checkbox"/> Auto-Engine Tune Up <input type="checkbox"/> Automobile Mechanic	<p>AVIATION</p> <input type="checkbox"/> Aeronautical Engineering Jr. <input type="checkbox"/> Aircraft & Engine Mechanic <p>BUSINESS</p> <input type="checkbox"/> Advertising <input type="checkbox"/> Bookkeeping and Accounting <input type="checkbox"/> Business Administration <input type="checkbox"/> Business Correspondence <input type="checkbox"/> Public Accounting <input type="checkbox"/> Creative Salesmanship <input type="checkbox"/> Federal Tax <input type="checkbox"/> Letter-writing Improvement <input type="checkbox"/> Office Management <input type="checkbox"/> Professional Secretary <input type="checkbox"/> Retail Business Management <input type="checkbox"/> Sales Management <input type="checkbox"/> Stenographic-Secretarial <input type="checkbox"/> Traffic Management <p>CHEMISTRY</p> <input type="checkbox"/> Analytical Chemistry <input type="checkbox"/> Chemical Engineering <input type="checkbox"/> Chem. Lab. Technician <input type="checkbox"/> General Chemistry <input type="checkbox"/> Natural Gas Prod. & Trans. <input type="checkbox"/> Petroleum Engineering <input type="checkbox"/> Plastics <input type="checkbox"/> Pulp and Paper Making	<p>CIVIL, STRUCTURAL ENGINEERING</p> <input type="checkbox"/> Civil Engineering <input type="checkbox"/> Construction Engineering <input type="checkbox"/> Highway Engineering <input type="checkbox"/> Reading Struct. Blueprints <input type="checkbox"/> Sanitary Engineering <input type="checkbox"/> Structural Engineering <input type="checkbox"/> Surveying and Mapping <p>DRAFTING</p> <input type="checkbox"/> Aircraft Drafting <input type="checkbox"/> Architectural Drafting <input type="checkbox"/> Electrical Drafting <input type="checkbox"/> Mechanical Drafting <input type="checkbox"/> Mine Surveying and Mapping <input type="checkbox"/> Plumbing Drawing and Estimating <input type="checkbox"/> Structural Drafting <p>ELECTRICAL</p> <input type="checkbox"/> Electrical Engineering <input type="checkbox"/> Electrical Maintenance <input type="checkbox"/> Electrician <input type="checkbox"/> Contracting <input type="checkbox"/> Lineman <p>HIGH SCHOOL</p> <input type="checkbox"/> Commercial <input type="checkbox"/> Good English <input type="checkbox"/> High School Subjects <input type="checkbox"/> Mathematics	<p>LEADERSHIP</p> <input type="checkbox"/> Foremanship <input type="checkbox"/> Industrial Supervision <input type="checkbox"/> Leadership and Organization <input type="checkbox"/> Personnel-Labor Relations <p>MECHANICAL AND SHOP</p> <input type="checkbox"/> Gas—Electric Welding <input type="checkbox"/> Heat Treatment <input type="checkbox"/> Metallurgy <input type="checkbox"/> Industrial Engineering <input type="checkbox"/> Industrial Instrumentation <input type="checkbox"/> Industrial Supervision <input type="checkbox"/> Internal Combustion Engines <input type="checkbox"/> Machine Design-Drafting <input type="checkbox"/> Machine Shop Inspection <input type="checkbox"/> Machine Shop Practice <input type="checkbox"/> Mechanical Engineering <input type="checkbox"/> Quality Control <input type="checkbox"/> Reading Shop Blueprints <input type="checkbox"/> Refrigeration <input type="checkbox"/> Sheet Metal Worker <input type="checkbox"/> Tool Design <input type="checkbox"/> Toolmaking <p>RADIO, TELEVISION</p> <input type="checkbox"/> Industrial Electronics <input type="checkbox"/> Practical Radio TV Eng'ing <input type="checkbox"/> Radio and TV Servicing <input type="checkbox"/> Radio Operating	<input type="checkbox"/> Television Technician <p>RAILROAD</p> <input type="checkbox"/> Air Brake Equipment <input type="checkbox"/> Car Inspector <input type="checkbox"/> Diesel Engineer & Fireman <input type="checkbox"/> Section Foreman <p>STEAM AND DIESEL POWER</p> <input type="checkbox"/> Combustion Engineering <input type="checkbox"/> Diesel—Elec. <input type="checkbox"/> Diesel Eng's <input type="checkbox"/> Electric Light and Power <input type="checkbox"/> Stationary Fireman <input type="checkbox"/> Stationary Steam Engineering <p>TEXTILE</p> <input type="checkbox"/> Carding and Spinning <input type="checkbox"/> Cotton, Rayon, Woolen Mfg. <input type="checkbox"/> Finishing and Dyeing <input type="checkbox"/> Loom Fixing <input type="checkbox"/> Textile Dressing <input type="checkbox"/> Textile Eng'g <input type="checkbox"/> Throwing <input type="checkbox"/> Warping and Weaving <p>MISCELLANEOUS</p> <input type="checkbox"/> Domestic Refrigeration <input type="checkbox"/> Marine Engineering <input type="checkbox"/> Ocean Navigation <input type="checkbox"/> Professional Engineering <input type="checkbox"/> Short Story Writing <input type="checkbox"/> Telephony
---	---	--	--	--

Name _____ Age _____ Home Address _____

City _____ Zone _____ State _____ Working Hours _____ A.M. to P.M. _____

Occupation _____

Canadian residents send coupon to International Correspondence Schools, Canadian, Ltd., Montreal, Canada. . . . Special tuition rates to members of the U. S. Armed Forces.

What's new in magnetic recording

"Scotch" Brand Magnetic Tape has been played thousands of times with perfect results. However, for maximum performance throughout the years, these simple suggestions on tape storage will prove of benefit:

1. Avoid storing unboxed reels of tape. Original box provides protection from dust and damage.
2. Reels of tape should be loosely wound and stored on edge or laying flat on individual shelves. Stacking many reels one on top of the other should be avoided.
3. If tape is subject to extreme temperatures, allow the tape to return to room temperature before running on machine.
4. Tape should be stored in a room with relative humidity maintained between 40 and 60%. If the relative humidity is subject to large variations, magnetic tape can be safely stored in a sealed metal can. Occasional use of the tape improves storage characteristics by releasing strains.

Do you record symphony concerts, operas, news events? Then, for true economy, "Scotch" Brand Extra-Play Magnetic Tape 190 is the tape for you. With 50% more tape wound on a standard size reel, amazing Extra-Play Tape lets you record even longer radio programs and home celebrations with pauses for reel changeover reduced to a minimum.

JUST ONE of the many advantages of "Scotch" Brand Magnetic Tape . . . it's "dry" lubricated to prolong recording head life. The only magnetic tape on the market with patented silicone lubrication, "Scotch" Brand glides smoothly over the head to end high frequency flutter caused by sticking and squealing. No wonder it's the favorite brand of recording engineers.

NEW PLASTIC LEADER AND TIMING TAPES! 50% stronger than paper leader . . . takes both ball point and pencil writing . . . has special anti-static coating . . . carries new convenient timing markers. Ask your dealer for it.

The term "Scotch" and the plaid design are registered trademarks for Magnetic Tape made in U.S.A. by MINNESOTA MINING AND MFG. CO., St. Paul 6, Minn. Export Sales Office: 99 Park Avenue, New York 16, N. Y. © 3M Co. 1956

Carl & Jerry (Continued from page 12)

from a story that appeared in the June-July, 1956, edition of a storage battery house organ called *Exide Topics* that my uncle sent me. What I want to do right now is to double-check on some of the statements in that story."

"Looks like you've got Old Squirmy pretty well trussed up; so let's start double-checking," Carl suggested.

"Okay," Jerry agreed. "First let's see if this eel is a.c. or d.c. According to the eel experts, the electrical discharge he puts out is a series of rapid direct-current discharges in the form of short-duration pulses sent out at a rate of about four hundred per second. But these pulses are of such short duration, about two-thousandths of a second, that the actual wattage output of an adult electric eel is only about forty watts."

THEN SUPPOSE we hook Buster here to a forty-watt bulb," Carl suggested.

"He's no good for lighting bulbs," Jerry explained. "Those pulses are too short to overcome the thermal lag of an incandescent bulb filament. Voltage has to be applied to such a filament for about one-fiftieth of a second before it begins to glow, and one of these pulses only lasts about one-tenth that long. But he could light a neon bulb, and I'm sure he'll make some interesting traces on our 'scope. I've got an idea about how to check his polarity, too. We'll simply run his output into this 0.5-microfarad capacitor and let him charge it up with his pulsating voltage. Then our VTVM connected across it will show his peak voltage and polarity."

As he talked, Jerry slipped one tin-foil electrode beneath the tail of the eel and another beneath the center of his body. Leads from the electrodes went to the capacitor, and the VTVM was connected to read the voltage charging this capacitor.

"Three-hundred-and-fifty volts!" Carl announced; "and the way the pointer swings proves that Old Squirmy's tail is the negative pole of his battery and the front part of him is the positive pole."

"Watch the meter while I slide this front electrode back and forth," Jerry suggested. "I want to find where the front end of his generator actually is."

This method soon showed that the maximum voltage, four hundred and eighty volts, was obtained when the negative electrode was at the eel's tail and the positive electrode was at a point about a foot back from his head.

"That squares with what the books say,"

(Continued on page 18)




CARL E. SMITH, E. E.
President



Accredited by National
Home Study Council

How to Pass

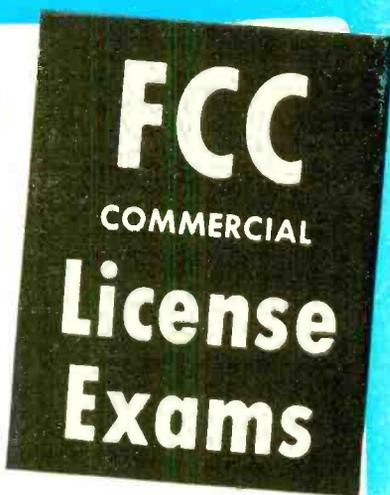

Get your FCC License
Quickly!

We Guarantee to train you **Your FCC License**
until you receive

Get all 3 FREE

CLEVELAND INSTITUTE Training results in
success with commercial FCC examinations—
easily—and quickly. Here's Proof:

Name and Address	License	Time
Walter Eggers, Pacific Grove	1st	12 weeks
Paul Reichert, West Salem, Ohio	2nd	10 weeks
Harold Phipps, LaPorte, Indiana	1st	28 weeks
John H. Johnson, Boise City, Okla.	2nd	12 weeks
James Faint, Johnstown, Pa.	1st	26 weeks

(Names and addresses of trainees in your area sent on request)

**Cleveland Institute training results in
job offers like these:**

Radio Operators & Technicians

American Airlines has openings for radio operators and radio mechanics. Operators start at \$334.53 per month. Radio mechanic's salary up to \$1.99 per hour. Periodic increases with opportunity for advancement. Many company benefits.

Electronic Technicians

Convair Electronics Department: Radio and Radar Mechanics, Electronics Technicians, and Junior Engineers are wanted for a special program on fire control development and installation. Beginning rate: \$365 and up.

And our trainees get good jobs

Electronics Technician

"I am now employed by the Collins Radio Company as a Lab Technician. (This job was listed in your bulletin.) I have used the information gathered from your course in so many ways and I know that my training with Cleveland Institute helped me a great deal to obtain the job."

Charles D. Sindelar, Cedar Rapids, Iowa

CLEVELAND INSTITUTE OF RADIO ELECTRONICS

4900 Euclid Bldg. Desk PE-18 Cleveland 3, Ohio

November, 1956



MAIL COUPON TODAY

Cleveland Institute of Radio Electronics

Desk PE-18, 4900 Euclid Ave., Cleveland 3, O.

Please send Free Booklets prepared to help me get ahead in Electronics. I have had training or experience in Electronics as indicated below:

- | | |
|---|---|
| <input type="checkbox"/> Military | <input type="checkbox"/> Broadcasting |
| <input type="checkbox"/> Radio-TV Servicing | <input type="checkbox"/> Home Experimenting |
| <input type="checkbox"/> Manufacturing | <input type="checkbox"/> Telephone Company |
| <input type="checkbox"/> Amateur Radio | <input type="checkbox"/> Other _____ |

In what kind of work are you now engaged?

In what branch of Electronics are you interested?



Name _____ Age _____

Address _____

City _____ Zone _____ State _____

Special Tuition Rates to Members of Armed Forces

New! A MACHINE THAT COMPOSES MUSIC

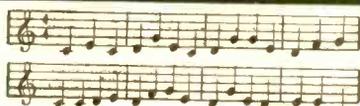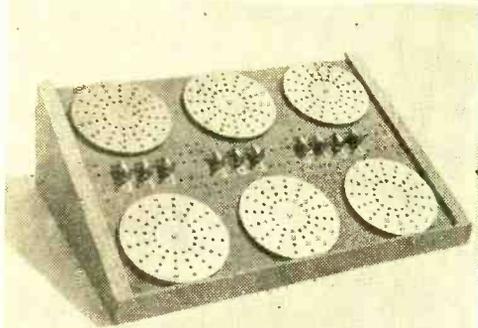

Actual tune composed on GENIAC

**COMPUTES, "REASONS"
PLAYS GAMES**

**GENIAC
ELECTRIC BRAIN**

BUILD IT YOURSELF in a few hours!

Yes, you build any one of 33 exciting electric brain machines in just a few hours by following the clear-cut, step-by-step directions given in a thrilling booklet! No soldering required . . . no wiring beyond your skill! GENIAC is a genuine brain machine—not a toy. The **only** logic machine kit that not only adds, subtracts, etc., but presents the basic ideas of cybernetics, Boolean algebra, symbolic logic, automation, etc. So simple to construct that even a twelve-year-old can make a machine that will fascinate people with advanced scientific training! With the special circuitry of GENIAC, the Electric Brain Construction kit, you can compose tunes automatically. These new circuits were never available before!

OVER 400 COMPONENTS AND PARTS. Circuits operate on one flashlight battery, and the use of ingeniously designed parts makes building circuits one of the most fascinating things you've ever done! You set up problems in a variety of fields—and get your answers almost quicker than you can set them up! Play games with the machine—nim, tic-tac-toe, etc.—and pit your brain against its logic! Solve puzzles in a few seconds that would take you hours without the aid of the machine. You actually see how computing and problem-solving is analyzed with algebraic solutions transferred directly into circuit diagrams.

YOUR COST FOR GENIAC KIT: only \$19.95 postpaid. The 1956 Model GENIAC KIT contains: (1) a complete 200-page text, "Minds and Machines"—a basic introduction to computers. (2) "How to Construct Electrical Brains At Home"—a fully illustrated text book on basic computer design theory and circuits with specific instructions for building circuits. (3) Wiring Diagram Manual. A special booklet with full scale diagrams that you can tear out and place on your work bench for easy assembly. (4) Beginners' Manual. Starting from scratch, the manual adds fifteen extra experiments, thoroughly tested using GENIAC components to teach the basic symbols of electric circuits. (5) Over 400 components and parts.

So—mail the coupon for your GENIAC today! Your money back if not delighted!

Some Firms and Institutions that have ordered GENIAC:

Allis-Chalmers
Remington-Rand
International
Business
Machines
Wheeldex Mfg. Co.
Manuel Missionary
College


Walter V. Clarke
Associates
Barnard College
Westinghouse
Electric
Phillips
Laboratories

General Insurance
Co. of America
Lafayette Radio
Rohr Aircraft Co.
Albert Einstein
Medical College
Naval Research
Laboratories

Los Angeles
Public Schools
Kansas State
University
Duke University
Coral Gables
Bell Telephone
Laboratories

K1—Only
\$19⁹⁵
Postpaid


New! CIRCLE-O-PHONIC SOUND SYSTEM

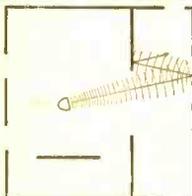

CONVENTIONAL LOUDSPEAKER

Sound travels only in set direction, resulting in an uneven spread of sound intensity.

A revolutionary new sound system which can increase the effectiveness of conventional amplifying and loudspeaking units over several hundred percent has been developed by our engineers. This patented speaker hookup rotates the loudspeaker at fixed speeds distributing the sound in a complete circle without distortion, echo or microphone feedback. In actual demonstrations, one 25 Watt speaker covered the entire Ebbetts Field Grandstands and in acoustically dead nightclubs, one CIRCLE-O-PHONIC speaker took the place of 21 individual loudspeakers mounted around the room. If you need special stereophonic effects with CIRCLE-O-PHONIC sound, you will want to read "EXPERIMENTS WITH CIRCLE-O-PHONIC SOUND." Postpaid L.P1-\$2.00 Or buy our CIRCLE-O-PHONIC kits. 10 Watt kit with motor, baffle, full frequency range speaker and cabinet. F.O.B. N.Y. L1-\$4995 25 Watt kit with motor, baffle and cabinet, F.O.B. N.Y. L2-\$135.00

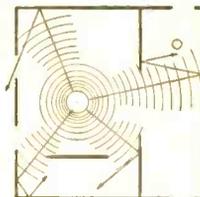

CIRCLE-O-PHONIC LOUDSPEAKER

Sound spreads at an even intensity throughout the entire enclosure.




OLIVER GARFIELD COMPANY
126 Lexington Avenue, New York 16, New York

LEARN HOW TO BUILD COMPUTERS!

ELECTRONIC MEMORY COURSE


An essential part of every computer is the memory—a storage device for retaining bits (binary digits) of information. The ELECTRONIC MEMORY course contains instructions for building relay memories, magnetic core "Matrix" memories and "SEAC" tube storage memories, with detailed descriptions of over 15 different methods of storing information and automatically giving instructions to electronic devices now in use. The booklets, texts and manuals are a complete course in this fascinating subject. Suitable for all levels—particularly designed for people who have some knowledge of electronics but want to know specific details of electronic computers for professional reasons. Complete question answering service. The memory "Matrix" can be expanded to any desired degree and can be used in conjunction with the digital computer kit as an outside memory store. Price of course with all instructions and training C1- **\$22.00** manuals, texts, etc., postpaid.

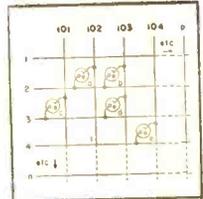

SECTION OF MATRIX Diagram of a Neon Tube Digital Storage Unit.

DIGITAL COMPUTER COURSE


Have you ever wanted to build a small digital computing device? One that reproduces in miniature what computers like ENIAC, SEAC, BIZMAC, etc., do on a large scale? Our DIGITAL COMPUTER course shows how to set up and build computers and experiment with pulses, storage, gates, flip flops, adding, subtracting, multiplying and applications of Boolean Algebra to circuit design. You get an introduction to programming. More important, you learn how and where to buy computer parts to build your own computers. Manuals, wiring diagrams and texts provide a complete introduction to theory and practice of DIGITAL COMPUTERS clearly explained. We have a complete question answering service. This is the finest and only DIGITAL COMPUTER course on the market, postpaid. C2- **\$28.00**

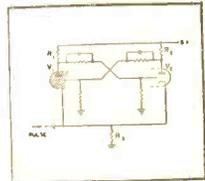

A modulo 2 counter. More commonly a flip-flop arrangement of 2 triodes. This is the main elementary component from which counters and accumulators are assembled.

ANALOG COMPUTER COURSE

ANALOG COMPUTERS are widely used in engineering and scientific research to duplicate actual physical conditions and to integrate and differentiate directly. Our ANALOG COMPUTERS course lists sources of materials, parts, theory and practical instructions, plus wiring diagrams and schematics for adding, multiplying, integrating and differentiating specific experiments, give practice in calculating scale factors, choice of time scales, machine equation and block diagrams, phase inverting amplifiers, use of parallel inputs, solution of simple differential equation. We show you how you can build computers at home. Texts discuss theory and design of computer elements, network and operational amplifiers, multiplication and function generation. This is your best and only comprehensive introduction to ANALOG COMPUTERS. Each course is a complete introduction to the subject with all necessary instructional material and parts. Course, Manuals, postpaid. C3- **\$28.00**

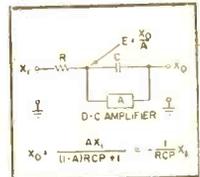

Block diagram for a simple integrating circuit.

New! WRIST RADIO weighs 2.5 oz.



All-transistor wrist radio receiver

A broadcast band all-transistor wrist radio has been designed with r-f reflex circuit to provide good selectivity and sensitivity. Three transistors are used which require 4.5 ma total battery current and five button-size mercury cells last up to 100 hours. The receiver features a 2-stage transformer-coupled audio amplifier and a no-whistle regenerative circuit. A high quality hearing aid receiver allows for private listening. Printed circuitry is used throughout. Band coverage is 550 to 1600 kc. Its small size (2 3/4 in. long, 1 3/4 in. wide and 3/4 in. thick) and weight (2.5 oz. with batteries) make it well suited for wearing on the wrist or in a shirt pocket. Completely assembled with all batteries. Postpaid. R1- **\$29.95**

Order Now!

Oliver Garfield Co., Dept. PE-116
126 Lexington Avenue
New York 16, New York

Please send me:


- K1 —\$ 19.95 Postpaid
\$ 20.95 West of Mississippi
\$ 21.95 Outside U. S.
- PL1—\$ 2.00 Postpaid
- L1 —\$ 49.95 F.O.B. N. Y.
- L2 —\$135.00 F.O.B. N. Y.
- C1 —\$ 22.00 Postpaid
- C2 —\$ 28.00 Postpaid
- C3 —\$ 28.00 Postpaid
- R1 —\$ 29.95 Postpaid

Check, Cash or Money Order is enclosed. My name and address are attached.
DEALER INQUIRIES INVITED



OLIVER GARFIELD COMPANY
126 Lexington Avenue, New York 16, New York

GREATEST VERSATILITY!

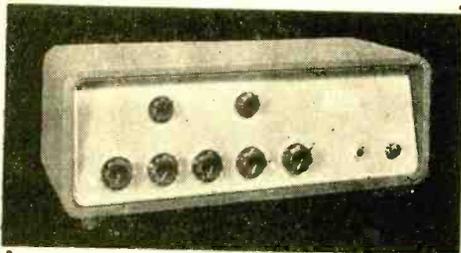

NEW Altec 342A AMPLIFIER with the "input-matcher" feature

Typical specification

Gain:	110 db
Input Sensitivity:	.0042 volts rms for rated output
Power Output:	20 watts at less than 2.0% thd, 40—20,000 cps
Frequency Response:	±1 db, 20—20,000 cps
Input Impedance:	Nominal 100,000 ohms
Source Impedance:	30/50, 250/300, 500/600 with 4665 plug-in transformer
Load Impedance:	4, 8, 16 ohms and 70 v line
Output Impedance:	Less than 20% of nominal load impedance
Noise Level:	Equivalent input noise—123 db, output noise—13 dbm
Controls:	4 mixer controls, 1 master volume control, 1 each bass, treble equalizer control; all cont. variable composition
Power Supply:	117 volts, 60 cps, 110 watts
External Power Available:	117 volt AC receptacle at rear of chassis
Tubes:	3—12AX7, 1—6CG7, 2—6L6GB, 1—5U4GB
Dimensions:	7" H, 19 3/4" W, 8 1/4" D overall
Color:	Green
Weight:	22 lbs.
Accessories:	4665 Plug-in Transformer 12227 Assembly—plug-in phono equalizer 12210 Assembly—rack mounting assembly Canon XL-3-12 straight cord plug.

The new Altec 20 watt public address amplifier is truly outstanding in its flexibility of function. Pick any combination of four inputs, plug in the convenient "input-matcher" for each source and the Altec 342A amplifier is matched to your exact circuit needs. In minutes the 342A can be input-matched to any high or low impedance microphone, crystal or magnetic phono pickup, tuner or tape recorder—merely plug in the proper "input-matcher."

The 342A has individual volume controls for each of four inputs, a master volume control and separate bass and treble tone controls. DC operation of the heaters of the input tubes insures hum-free performance and eliminates the need for tube selection. The quality, reliability and amazing flexibility of the new Altec 342A amplifier make it ideal for every public address use either permanent or portable.



ALTEC FIDELITY IS
HIGHEST FIDELITY

Dept. 11-P
9356 Santa Monica Blvd., Beverly Hills, Calif.
161 Sixth Avenue, New York 13, New York

Carl & Jerry (Continued from page 14)

Jerry reported, "According to them, all of the critter's vital organs are in the front fifth of his body, and the rest is made up of 'electric tissue.'"

"Whatever that is."

"It's a flabby whitish jelly composed of 92% water. This stuff is organized into three pairs of electric organs. The eel can use one pair for a major discharge, one pair for a medium-size whammy, and the third pair for a small shock. Each organ is made up of smaller units separated by another kind of tissue that acts like the insulating separators in a storage battery. The electricity is actually produced in these smaller units. Each one produces about one-tenth of a volt. Somehow, in some way, the creature is able to connect these units in series to produce the high voltage discharges. But how he can throw thousands of 'switches' on and off several hundred times a second in perfect unison is still a mystery."


JERRY CONNECTED the leads from the electrodes to the horizontal input terminals of his 'scope and adjusted the linear sweep until he had two of the voltage spikes visible on the screen. Since the frequency of the eel's output was irregular, this pattern was not easy to hold, but a sweep frequency of around 200 cycles per second displayed two complete pulses. Once again this proved the books were right when they said that the eel put out about 400 discharges per second.

"For the rest of our experimenting," Jerry mused, "we should have the eel swimming freely about. Wonder where we can manage that? He's too big for a wash-tub."

Jerry and Carl looked deep into each other's eyes and saw the same thought. "Okay," Jerry said, "but you'll have to go ahead and make sure the coast is clear. Mom is deathly afraid of this thing, and if she saw us sneaking it into the bathroom, she would never set foot in there again."

Jerry gathered Old Squirmy, still strapped to the length of gutter trough, under his arm and cautiously followed Carl up the basement stairs. Jerry's mother, fortunately, was busy talking on the telephone and never noticed the boys tiptoeing past the door on their way to the second floor. Safely inside the bathroom, Carl started quietly filling the tub with water while Jerry made another trip to the laboratory for other equipment he wanted. When the tub was two-thirds full, the eel was released inside it. He seemed to enjoy his freedom and went slithering around on

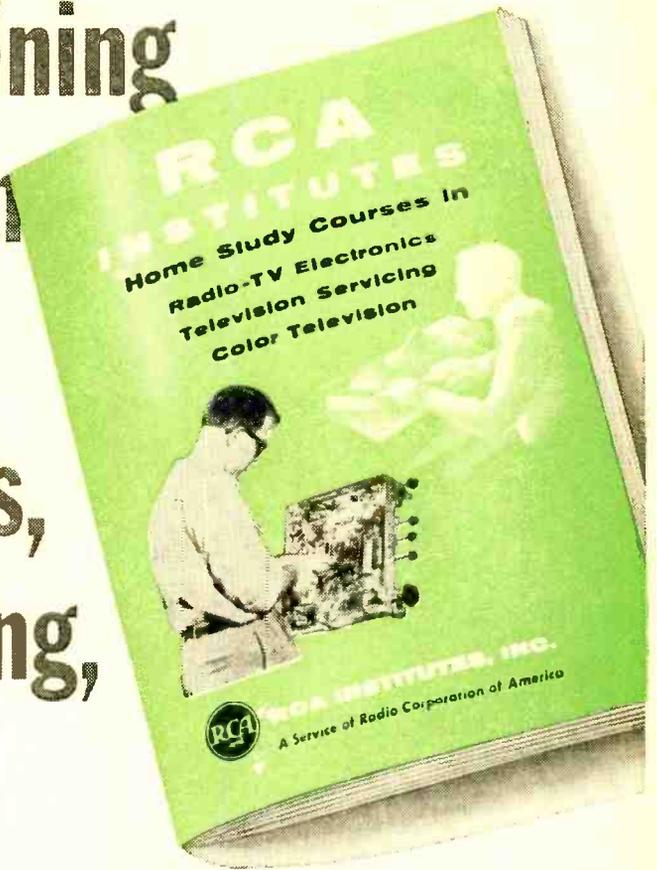RCA offers you the
 finest training
 at home in
 Radio-TV
 electronics,
 TV servicing,
 Color TV



**SEND FOR THIS FREE
 BOOK NOW!**

The instruction you receive and equipment you get (and keep) will start you on your way. Pay-as-you-learn. You pay for only one study group at a time. This 52 page book contains complete information on Home Study Courses for the beginner and the advanced student.



RCA INSTITUTES, INC.
 A SERVICE OF RADIO CORPORATION OF AMERICA
 350 WEST FOURTH STREET, NEW YORK 14, N.Y.

RCA Institutes, Inc., Home Study PE-116
 350 West Fourth Street New York 14, N. Y.
 Without obligation, send me FREE CATALOG
 on Home Study Courses in Radio, Television
 and Color TV. No salesman will call.

Name
 Please Print
 Address
 City Zone ... State

**VETERANS
 KOREAN G.I.
 P.L. 550
 CHECK HERE**

IN HI-FI SPEAKERS

Linthrop SETS
THE PACE AT
AMAZINGLY LOW PRICES!



6.8 OZ. ALNICO V
MAGNETS, 6.4 OHM
ALL MODELS

Yes, Linthrop leads the way with finer, heavier construction, superb acoustical engineering and tone quality that cannot be matched in any speakers at comparable price. When you order Linthrop you enjoy the savings of direct factory dealing, the superior tone you've wanted for your hi-fi, and you'll own a speaker that gives years and years of uninterrupted service . . . a speaker made by one of the biggest suppliers to the Radio-TV trade.

ORDER DIRECT


6"\$ 8.95

8"\$10.85

12"\$13.95

POSTPAID and
TAX PAID

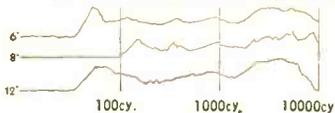
MINIMUM DISTORTION
FOR MAXIMUM LISTENING PLEASURE



AND NOW . . . THE LOW COST

Linthrop

TWIN EXTENSION SPEAKER

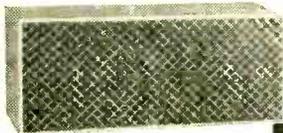

Here it is . . . a compact twin-speaker unit that connects in seconds to any hi-fi, phonograph, TV or radio, and brings the full tone of your set to any remote part of the house. Or use it in the same room for rich, all 'round sound. Made by one of America's outstanding hi-fi speaker manufacturers. Beautiful light or dark wood cabinet containing an 8" woofer and 3½" tweeter, frequency range 40-15000. 4 ohm impedance. Measures 20½" wide x 10" deep x 8¼" high. Faced with attractive grille cloth.

ORDER DIRECT TODAY . . . send just \$23.95 for complete unit postpaid and tax paid, with money back guarantee. Specify light or dark finish. Send check or money order to:

Linthrop MFG. CO.
433 FULTON, N.W.
GRAND RAPIDS, MICH.

BRING GLORIOUS SOUND TO YOUR

- KITCHEN
- BEDROOM
- BASEMENT
- DINING ROOM
- PATIO
- REC. ROOM

MUSIC, SPORTS,
DRAMATIC SHOWS
ANYWHERE IN
YOUR HOME OR
COTTAGE AT
LOW, LOW COST!

ONLY
\$23⁹⁵
COMPLETE!

Carl & Jerry (Continued from page 18)

the bottom of the tub in graceful coils. Jerry separated the earpieces of a pair of headphones and handed one to Carl.

"Listen!" he said, as he dipped the metal-tipped ends of the headphone cord in the water. Clearly heard in the phones was a static-like noise. When the eel was quiet, this noise subsided; but as soon as it started to move, the noise returned.

"Any time he is moving," Jerry explained, "the electric eel gives off a series of weak discharges. These serve two purposes: first, they warn enemies to keep their distance; and secondly, they form a kind of radar that enables the eel—which is virtually blind when it is adult—to seek out its prey."

"**WAIT A MINUTE!**" Carl interrupted. "I'm not so dumb that I don't know a radar system consists of a receiver as well as a transmitter. I'll admit Old Squirmy has a dan-dan-dandy low-frequency transmitter; but where's his receiver?"

"He's got one all right, according to the books," Jerry replied. When one eel in a tank discharges, all the other eels come to the spot, apparently to horn in on the result. Obviously they know when one of their fellows is trying to stun something and can judge very nicely where the current is coming from. But now let's see if we can prove this with the eel-caller I've built up. It's a blocking oscillator that produces sharp spikes of voltage over a frequency range which is adjustable from about 500 to 2000 cycles per second. The output of the oscillator drives an output tube so as to produce pulses of very respectable amplitude across these two electrodes. Let's place the electrodes in the water at this end of the tub and see if we can sweet-talk him into coming over."

Carl did as he was told, and Jerry began varying the frequency of the blocking oscillator. As a certain frequency was reached, the eel on the bottom of the tub began to stir and swim directly to the electrodes. When they were transferred to the opposite end of the tub, he immediately moved toward them.

"Old Squirmy's receiving frequency seems to be around 800 cycles per second," Jerry announced.

"Say! That thing really puts the comethier on him," Carl said enthusiastically. "We ought to patent it."

"We're a little too late," Jerry told him. "Eel hunters in South America are already using earphones to locate electric fish and then are employing eel-callers something like this one to lure them into

BUILD 16 RADIO

CIRCUITS AT HOME only \$19.95

with the New Improved
PROGRESSIVE RADIO "EDU-KIT"

A Practical Home Radio Course

Now Includes
TESTER, SOLDERING IRON, HIGH
FIDELITY SIGNAL TRACER, CODE
OSCILLATOR, PRINTED CIRCUIT
SIGNAL INJECTOR

- No Knowledge of Radio Necessary
- No Additional Parts or Tools Needed
- Excellent Background for TV

NOW! FREE TOOLS WITH "EDU-KIT"

WHAT THE "EDU-KIT" OFFERS YOU

The "Edu-Kit" offers you an outstanding PRACTICAL HOME RADIO COURSE at a rock-bottom price. Our Kit is designed to train Radio & Electronics Technicians, making use of the most modern methods of home training. You will learn radio theory, construction practice and servicing.

You will learn how to build radios, using regular schematics; how to wire and solder in a professional manner; how to service and trouble-shoot radios. You will work with the standard type of punched metal chassis as well as the latest development of Printed Circuit chassis.

You will learn the basic principles of radio. You will construct, study and work with RF and AF amplifiers and oscillators, detectors, rectifiers, test equipment. You will learn and practice using the Progressive Code Oscillator. You will learn and practice trouble-shooting, using the Progressive Signal Tracer, the Progressive Signal Injector, the Progressive Dynamic Radio & Electronics Tester and the accompanying instructional material.

You will receive training for the Novice, Technician and General Classes of F.C.C. Radio Amateur Licenses. You will build 16 Receiver, Transmitter, Code Oscillator, Signal Tracer and Signal injector circuits, and learn how to operate them. You will receive an excellent background for Television.

Absolutely no previous knowledge of radio or science is required. The "Edu-Kit" is the product of many years of teaching and engineering experience. The "Edu-Kit" will provide you with a basic education in Electronics and Radio, worth many times the complete price of \$19.95. The Signal Tracer alone is worth more than the price of the entire Kit.

THE KIT FOR EVERYONE

You do not need the slightest background in radio or science. Whether you are interested in Radio & Electronics because you want an interesting hobby, a well paying business or a job with a future, you will find the "Edu-Kit" a worth-while investment.

Here is an excerpt from a letter that we received from Loren DePriest, 1496 4th St., Mansfield, Ohio: "I have spent many pleasant hours in constructing the radios from the schematics in your book, and have learned a great deal from them. Being as I am interested in Radio, I consider the money spent for your course as a wise investment. I have learned more from your course by actually doing than I did from an expensive course."

Many thousands of individuals of all ages and backgrounds have successfully used the "Edu-Kit" in more than 79 countries of the world. The "Edu-Kit" has been carefully designed, step by step, so that

you cannot make a mistake. The "Edu-Kit" allows you to teach yourself at your own rate. No instructor is necessary.

The "Edu-Kit" is also used for courses of study, extra-curricular activities, industrial personnel training and rehabilitation. The "Edu-Kit" is used by Jr. High Schools, High Schools, Technical Schools, Jr. Colleges, Colleges, Universities, Industrial firms, Rehabilitation Hospitals, Boards of Education, U. S. Govt. agencies, United Nations Educational, Scientific and Cultural Organizations (UNESCO), Veterans Administration, and numerous adult, radio and young peoples' groups and clubs. The "Edu-Kit" is also popular with servicemen throughout this country and abroad.

Designed for universal use, the "Edu-Kit" operates on any voltage from 105 to 125 volts, AC and DC. For use in countries employing higher line voltages, a 210-250 Volt AC/DC model is available.

PROGRESSIVE TEACHING METHOD

The Progressive Radio "Edu-Kit" is the foremost educational radio kit in the world, and is universally accepted as the standard in the field of electronics training. The "Edu-Kit" uses the modern educational principle of "Learn by Doing." Therefore you construct, learn schematics, study theory, practice trouble-shooting—all in a closely integrated program designed to provide an easily-learned, thorough and interesting background in radio.

You begin by examining the various radio parts of the "Edu-Kit." You then learn the function, theory and use of these parts. Then you build a simple radio. With this first set you will enjoy listening to regular broadcast stations, learn theory, practice testing and trouble-shooting. Then you build a more advanced radio, learn more advanced theory and techniques. Gradually, in a progressive manner, and at your own rate, you will find yourself constructing more advanced multi-tube radio circuits, and doing work like a professional Radio Technician.

THE "EDU-KIT" IS COMPLETE

You will receive all parts and instructions necessary to build 16 different radio and electronics circuits, each guaranteed to operate. Our Kits contain tubes, tube sockets, variable electrolytic and paper dielectric condensers, resistors, wire strips, coils, hardware, tubing, punched metal chassis, Instruction Manuals, etc.

In addition, you receive Printed Circuit materials, including Printed Circuit chassis, special tube sockets, hardware and instructions. You also receive a useful set of

tools, a professional electric soldering iron, and a self-powered Dynamic Radio & Electronics Tester. The "Edu-Kit" also includes Code Instructions and the Progressive Code Oscillator, in addition to F.C.C. type Questions and answers for Radio Amateur License training. You will also receive lessons for servicing with the Progressive Signal Tracer and the Progressive Signal Injector, a High Fidelity Guide and a Quiz Book. You receive all parts, tools, instructions, etc. Everything is yours to keep.



Reg. U.S. Pat. Off.

FREE Hi-Fi, Radio & TV Servicing Manuals on request

(see coupon below)

SERVICING LESSONS

You will learn trouble-shooting and servicing in a progressive manner. You will practice repairs on the sets that you construct. You will learn symptoms and causes of troubles in home, portable and car radios. You will learn how to use the professional Signal Tracer, the unique Signal Injector and the dynamic Radio & Electronics Tester. While you are learning in this practical way, you will be able to do many a repair job for your friends and neighbors, and charge fees which will far exceed the price of the "Edu-Kit." Our Consultation Service will help you with any technical problems you may have.

J. Sakatis, of 25 Poplar Pl., Waterbury, Conn., writes: "I have repaired several sets for my friends, and made money. The "Edu-Kit" paid for itself. I was ready to spend \$240 for a Course, but I found your ad and sent for your Kit."

FROM OUR MAIL BAG

Ben Valerio, P. O. Box 21, Magna, Utah: "The Edu-Kits are wonderful. Here I am sending you the question and also the answers for them. I have been in Radio for the last seven years, but like to work with Radio Kits and like to build Radio Testing Equipment, I enjoyed every minute I worked with the different kits; the Signal Tracer works fine. Also like to let you know that I feel proud of becoming a member of your Radio-TV Club."

Rob L. Shuff, 1534 Monroe Ave., Huntington, W. Va.: "Thought I would drop you a few lines to say that I received my Edu-Kit, and was really amazed that such a bargain can be had at such a low price. I have already started repairing radios and phonographs. My friends were really surprised to see me get into the swing of it so quickly. The Troubleshooting Tester that comes with the Kit is really sweet and finds the trouble if there is any to be found."

PRINTED CIRCUITY

At no increase in price the "Edu-Kit" now includes Printed Circuitry. You build a Printed Circuit Signal Injector, a unique servicing instrument that can be used on many Radio and TV troubles. This revolutionary new technique of radio construction is now becoming popular in commercial radio and TV sets.

A Printed Circuit is a special insulated chassis on which has been deposited a conducting material, which takes the place of wiring. The various parts are merely plugged in and soldered to terminals.

UNCONDITIONAL MONEY-BACK GUARANTEE

ORDER DIRECT FROM AD RECEIVE FREE BONUS RESISTOR KIT WORTH \$5

- Send "Edu-Kit" Postpaid. I enclose full payment of \$19.95.
 - Send "Edu-Kit" C.O.D. I will pay \$19.95 plus postage.
 - Send me FREE additional information describing "Edu-Kit." Include FREE valuable Hi-Fi, Radio and TV Servicing Literature.
- (Outside U.S.A.—No C.O.D.'s. Send check on U.S. bank or Intern'l M.O. "Edu-Kit" for 105-125 V. AC/DC \$20.95; 210-250 V. AC/DC \$23.45.)

Name
Address

PROGRESSIVE "EDU-KITS" INC.

497 Union Ave., Room 525D, Brooklyn 11, N. Y.

FREE EXTRAS

- SET OF TOOLS • RADIO & ELECTRONICS TESTER • ELECTRIC SOLDERING IRON • TESTER INSTRUCTION MANUAL • HIGH FIDELITY GUIDE • QUIZZES • TELEVISION BOOK • MEMBERSHIP IN RADIO-TV CLUB • CONSULTATION SERVICE

FULL FIDELITY MUSIC ENJOYMENT

TWIN-CONES IN A SINGLE

F.R.S. **SPEAKER**

COVER THE AUDIBLE RANGE



In a single speaker, Norelco has created an unusually efficient sound radiator. These twin-cone speakers incorporate a small cone for reproducing high frequencies and a large cone for lower frequencies. Both cones operate in conjunction from a single voice coil—producing balanced sensitivity and uniform sound for all ranges. Arrangement of both cones reflect and diffuse the sound while moving in phase to provide even sound distribution.

A deep air gap within a homogeneous magnetic field provides unusually large movement of the voice coil resulting in distortion-free reproduction over the entire frequency range. Impedance does not diminish with higher frequencies and volume is practically constant throughout the whole audible range.

Send today for your catalog on Norelco *FRS Twin-Cone Speakers. It contains specification data, sound distribution curves, frequency characteristics on these speakers as well as the new Norelco Speaker Enclosures.

Send to Dept. N11 for more details

North American Philips Co., Inc.
100 E. 42nd Street
New York 17, N. Y.



Carl & Jerry (Continued from page 20)

their traps. But to get back to his built-in radar, by means of it the electric eel can move straight toward his prey and can detect a variation of just a few inches. What's more, he can tell instantly if his prey is moving and can make allowances for that movement."

"YOU KNOW," Carl mused, "that's all pretty wonderful when you stop to think about it. Here we think of electricity itself as being quite modern, but that ugly creature resting there on the bottom of the tub and his ancestors have been using electricity for thousands of years. What's more, they've been using it in ways that we think of as being ultra-modern. Since electric eels talk to each other by means of their electric discharges, we must admit that they are equipped with wireless telephones. Those same discharges are employed as a compact, efficient, and highly effective weapon to secure food and to combat enemies. Finally, the lowly eel has been quietly using radar—which we did not discover until the last war—for countless centuries. It kind of makes you wonder if man—in spite of all his scientific development and progress—is so doggone smart as he thinks he is, doesn't it?"

"It certainly does," Jerry agreed, "and I think my uncle had something like that in mind when he sent me the eel and told me to study it. When we work with electricity that is man-produced by batteries and generators and so on, we sort of take it for granted and forget how magic it really is, but when you see electricity being generated within the living tissue of a live creature such as this, all the wonder and mystery of it sweeps over you, and you are glad that you intend to make a lifetime study of it."

—30—



NATIONAL SCHOOLS

proudly presents

FOR MEN WHO WANT TO EARN MORE MONEY

TELERAMA • ALL 8 BRANCHES OF TELEVISION • ELECTRONICS • RADIO IN ONE DYNAMIC, MODERN SHOP METHOD, HOME TRAINING COURSE

*Registration applied for

Another great advance in **HOME STUDY TRAINING**. Let National Schools, of Los Angeles, a practical Technical Resident Trade School for over 50 years, train you at home by Shop-Method, for today's unlimited opportunities in **ALL 8 BRANCHES** of the Television, Electronics, Radio Industry.

Check all you receive in *One Master Course* at One Low Tuition

1. Television — Including Color TV
2. Radio — FM and AM
3. Industrial Electronics
4. Sound Recording and Hi-Fidelity
5. Preparation for FCC License
6. Automation
7. Radar and Sonar
8. Communications

YOU DO MANY PRACTICAL JOBS.

You do servicing, circuit analysis and many other down-to-earth experiments. You build a modern TV set from the ground up... with equipment kits we give you, including a new large screen picture tube and professional Multitester, at no additional charge.

EARN AS YOU LEARN! Many of our students earn their entire tuition and more in Spare Time jobs we show them how to do while learning. **YOU GET GRADUATE ADVISORY SERVICE, TOO**

- ALL OF THIS MODERN, NEWEST, PRACTICAL EQUIPMENT IS YOURS TO KEEP!
- Parts to Build a modern TV set, including large screen Picture Tube.
 - Parts to build a powerful Superhet Receiver, standard broadcast and short wave.
 - Parts to conduct many experiments and build Continuity Checker, RF Oscillator, TV Circuits, Audio Oscillator, TRF Receiver, Signal Generator.
 - Professional Multitester
 - These are a MUST for all technicians.

ALL YOURS TO KEEP



L. J. ROSENKRANZ
President of NATIONAL SCHOOLS



This Master-Shop-Method course is completely up-to-date. Here in Los Angeles, the TV and Electronics center of the world, we are able to keep in constant touch with the industries' latest developments. As a student, you will quickly master all phases at home... in your spare time. Your earning power will grow with every lesson. Just as thousands of National Schools graduates do every day, you can handle servicing, manufacturing, repairing, hundreds of other jobs, or make good money in your own business. **SECURE YOUR FUTURE—NOW. SEND COUPON BELOW.**



IN THESE MODERN TV STUDIOS, SHOPS AND LABORATORIES, your Shop Method Home Study Course was developed by experienced instructors and engineers. What an advantage that is to you at home — each lesson is tested, proved, easy to understand. You can master the most up-to-date projects, such as color TV set repair, printed circuits — even prepare for F.C.C. License and industrial electronics without taking a special course. **TAKE YOUR FIRST STEP NOW TO A TOP-PAY JOB IN TV, ELECTRONICS, RADIO. SEND COUPON BELOW TODAY.**



APPROVED FOR VETERANS AND NON-VETERANS

NATIONAL SCHOOLS

4000 S. FIGUEROA ST., LOS ANGELES 37, CALIF
187 N. LA SALLE ST., CHICAGO 1, ILL

IN CANADA: 811 W. Hastings St., Vancouver, B. C.



FREE!

Fully illustrated "CAREER" BOOK in TV, Radio, Electronics. AND actual Sample Lesson—yours at no cost, no obligation **SEND COUPON NOW—TODAY!**



NATIONAL SCHOOLS


TECHNICAL TRADE TRAINING SINCE 1905
Los Angeles, California

GET FAST SERVICE—MAIL NOW TO OFFICE NEAREST YOU!

NATIONAL SCHOOLS, DEPT. R22-113
4000 S. FIGUEROA ST. OR 187 N. LA SALLE ST.
LOS ANGELES 37, CALIF. CHICAGO 1, ILL.
Rush free TV-Radio "Opportunity" Book and sample lesson. No salesman will call.

NAME _____ BIRTHDAY _____ 19 _____
ADDRESS _____
CITY _____ ZONE _____ STATE _____

VETERANS: Give Date of Discharge

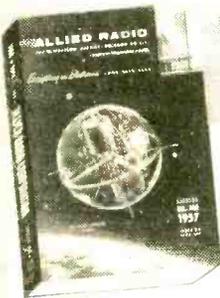

Save on
hi-fi

SEND FOR THE 1957
ALLIED CATALOG

Features the world's largest selection of systems and components. Shows you how to choose a custom Hi-Fi music system for your home at no more than the cost of an ordinary phonograph. Tells you what to look for and how to save money. Offers dozens of complete systems and hundreds of individual units, including the famous money-saving Hi-Fi Knight-Kits. For everything in Hi-Fi and Electronics, get the FREE 1957 Allied Catalog.

free

ALLIED RADIO
America's Hi-Fi Center

ALLIED RADIO CORP., Dept. JJ-116
100 N. Western Ave., Chicago 80, Ill.

Send FREE 1957 ALLIED Catalog.

Name _____

Address _____

City _____ Zone _____ State _____



ATTENTION!

ENGINEERS

SERVICEMEN

AMATEURS

STUDENTS

Almo RADIO CO.
OFFERS THE BEST MULTIMETER
VALUES ON THE MARKET TODAY...
World Famous "FUJI"
ELECTRONIC TEST EQUIPMENT




MODEL LP-3 POCKET TESTER

An attractive Black Bakelite cabinet.
Response: 170 μ A
AC Volt: 10v 50v 250v 500v 1000v
(500 μ A V/2000 Ω)
DC Volt: 10v 50v 250v 1000v
(250 μ A V/4000 Ω)
DC Current: 250 μ A 10mA 250mA
Resistance: 0~1M Ω 0~10K Ω
Decibels: -20db~+22db
(at AC 10v Range)
+20db~+36db
(at AC 50v Range)
(0db-0.775v-800 Ω)

Almo RADIO CO.
509 ARCH ST., PHILA., PA.

CAMD., N.J. ATL. CITY, N.J. TRENT., N.J. NORRIST'N. PA. WILM. DEL. SALIS'B'Y, MD.

* simple installation

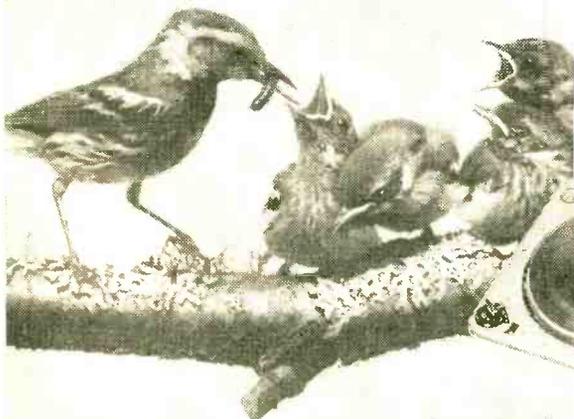

Another reason why today's
fastest selling high fidelity
record changer is

Collaro

* Simple Installation —

the pre-wired audio cable and the
power cord with standard plugs elimi-
nate need for making solder connections.
Pre-cut mounting board available.



For other features and new popular price, see your
hi-fi dealer or write Dept. PL-18

ROCKBAR CORPORATION 650 Halstead Avenue, Mamaroneck, N. Y.

Thousands of Central-Trained Engineering Technicians Now in Permanent HIGH-PAY ELECTRONICS CAREERS!



C. L. Foster, President, Central Technical Institute. Mr. Foster is one of the nation's best known technical institute educators.

Central's "Progressive Plan"

Trains You in Shortest Possible Time!

3 Proven Training Plans

1. **HOME STUDY COURSE** (with 9 kits of equipment)—Qualifies you for diploma, FCC license exam, and a variety of electronics jobs (or transfer into advanced resident training).
2. **HOME STUDY — RESIDENT COURSE** (with 9 kits of equipment) — Home study, followed by short period of resident training. Qualifies you for diploma, FCC license exam, and a wide variety of positions (or continue with advanced resident training). An ECPD-accredited engineering technician program.
3. **FULL RESIDENT COURSE** — Qualifies you for Associate of Science (A. S.) degree and top-pay employment opportunities as Electronics Engineering Technician. An ECPD-accredited engineering technician program. Part-time employment opportunities available for students while training.

VETERANS! Central offers courses approved under the G. I. Bill.

**Mail Coupon for
FREE BOOK**

**YOUR FUTURE
IN
ELECTRONICS**

YOU, TOO, can enjoy the financial security and rewarding opportunities now open in

ELECTRONICS TELEVISION - RADIO

- AM-FM-TV Technician
- Automation Technician
- Electronics Inspector
- Field Service Engineer
- Broadcast Engineer
- Electronics Technician
- Calibration Engineer
- Customer Service Engineer
- Research and Development Assistant
- Technical Writer (or Illustrator)

The jobs listed above as well as scores of others . . . are available right now in the fascinating field of Electronics. Naturally, the pick of these jobs go to the best-trained men. The quality of your training and, the caliber of the school where you receive it are two of the most important items considered by employees of electronics specialists. Proof of the excellence of Central's training is demonstrated almost daily by requests for job interviews from some of the country's foremost industrial giants . . . from leading radio and TV stations . . . and from the nation's major airlines. All want *fully qualified* engineering technicians . . . and they know Central can provide them!

P. h. Foster

You reach your goal *fast* with Central's streamlined program of *complete* training! There's no lost motion! If you've had previous electronics experience or training, civilian or military, Central starts you at whatever training level best fits your qualifications. And, *most important*, through Central's "Progressive Plan" of study, as you complete each phase of training, your earning capacity goes higher. Every week you train adds to your value as an electronics specialist. A few short weeks of training prepares you for certain basic jobs. Then, as you progress through Central's accredited training, you qualify yourself for more advanced types of positions.

You can settle for any of a wide variety of well-paid, worthwhile jobs along the way — or you can use Central's complete training to advance right up to the top-level, top-pay positions.

DON'T LIMIT YOURSELF! How far you go in the electronics field as an engineering technician depends upon (1) the thoroughness of your training; (2) the prestige of the school that trains you. Central has a national reputation for excellence in both. Get the facts on Central's outstanding training today — they'll speak for themselves! Send coupon now for full information without obligation.

CENTRAL TECHNICAL INSTITUTE

Dept. 116, 1644 Wyandotte
Kansas City 8, Mo.

Please give me the facts that will get me into a high-pay electronics career.

Name Age

Address Phone

City, State County

If Korean veteran, give approximate discharge date.....

TRAINED MEN NEEDED!

BIG PAY!—GOOD FUTURE!

- DIESEL ELECTRONICS
 AUTO AUTOMATION

NEVER BEFORE has the opportunity been so good for the properly trained mechanic and technician to step into **BIG PAY POSITIONS** with rapid advancement and future security virtually assured.

YOUR SUCCESS depends on the quality of training you receive... and the reputation of the school you attend.

YOUR GUARANTEE we are giving the best in mechanical and technical training is proved by the fact... we have a waiting list of good pay positions for our graduates, with leading companies throughout the United States.

RESIDENT SHOP TRAINING is easier and costs less than you may think! We provide you with housing and part-time jobs while in school, plus free nation-wide placement service for graduates.

Check subject above in which you are interested and mail for

FREE BOOKLET

BAILEY
Technical Schools
 Veteran Approved
 1626 S. Grand, St. Louis 4, Mo.

Name _____ Age _____
 Street _____
 Town _____ Zone _____ State _____

LETTERS FROM OUR READERS

Wanted: Parabolic Dishes

■ I am looking for a parabolic dish or horn to be used with a speaker or microphone similar to those used on sound trucks. I used to be able to get them for about \$10, but now have no luck. Have any of your readers seen some in other cities?

FRANCIS FOSSA
 Nashua, N. H.

The editors of POPtronics are also scouting around for one of those war surplus dishes. Carl and Jerry located one for their May 1956 story installment, but they're not telling anyone where they found it. How about it, guys, have you seen or heard of any parabolic dishes lately?

Must Meet FCC Standards


■ I would like to obtain a diagram to build a transceiver such as the Vocaline (June and August issues) Citizens band Model JRC-400.

(name withheld)

We cannot stress too strongly that all radio transmitters used for two-way voice communications must meet FCC standards. In the case of radio amateurs, we are sure you are aware that they must pass strict examinations. Citizens band equipment must be approved by the FCC laboratories—constructing your own is impractical.

Twinkling Xmas Tree

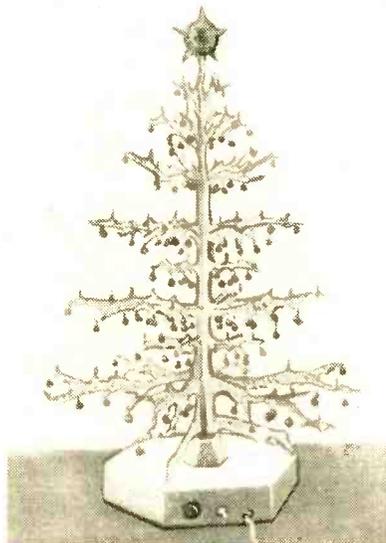■ In your December 1954 issue, you featured a twinkling tree which interested me greatly. I constructed one from plastic in six sections. It is 30"



high. The neon bulbs are cemented in notches filed in the upper edges of the limbs. All wires are carried to the base of the tree where war-surplus

COLOR TELEVISION

Home Study for
 Technicians

NOW AVAILABLE THE MOST COMPLETE, COMPREHENSIVE COLOR TV HOME STUDY COURSE ILLUSTRATED WITH NEW BLOCK-A-MATICS

This new seven-lesson HOME STUDY COURSE in COLOR TELEVISION was compiled by Albert C. W. Saunders, internationally noted author-lecturer on Radio and TV Servicing, and is the best course available today. It is just off the press with the latest technical information. Lessons are fully illustrated with simplified diagrams including BLOCK-A-MATICS—*The New Look in Schematics*. Also Color Illustrations.

COST OF COMPLETE COURSE ONLY \$25.00

\$5.00 Enrolls You Immediately Under Our Budget Plan

For Particulars Write


**SAUNDERS ELECTRONICS
 CORRESPONDENCE SCHOOL**

137 FEDERAL STREET
 BOSTON 10, MASSACHUSETTS

8 reasons why the world's most respected name in communications is **hallicrafters**

model S-38D \$49.95

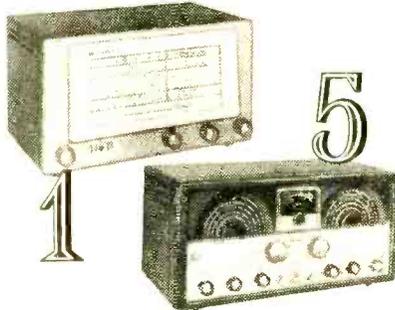Wonderful starting point for the new amateur or short-wave listener. Same meticulous engineering found in all Hallicrafters equipment—at down to earth prices. Coverage: standard broadcast from 540-1650 kc. plus 3 short wave bands from 1650 kc. to 32 Mc.




model SX-99 \$149.95

The best at its price with all features demanded by DX enthusiast. Has "S" meter, separate bandspread tuning condenser, crystal filter and antenna trimmer. Easy-read dial has over 1000° calibrated bandspread through 10, 11, 15, 20, 40, and 80 meter amateur bands. Coverage: standard broadcast 540-1680 kc. plus three Short-Wave bands 1680 kc-34 Mc.

model S-53A \$89.95

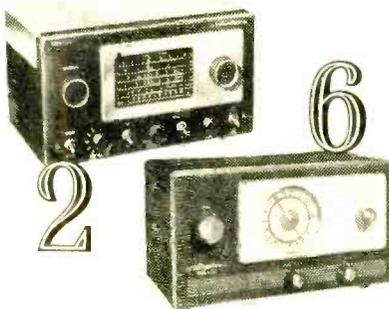Has easy-read overseas dial with international stations indicated. Electrical bandspread and logging scale. Complete with 5 in. speaker, head-phone jacks plus phono-jack. Two stages of i.f. Coverage: standard broadcast from 540-1630 kc. plus four SW bands over 2.5—31 and 48—54.5 Mc.




model S-102, S-106 \$59.95

The only inexpensive complete receivers for 2 and 6 meter bands. New models with all of Hallicrafters famous engineering. Have 7 tubes with rectifiers, built-in 5" PM speaker, low frequency drift, compact bandspread design, phone jacks. Coverage: S-102—143 to 149 Mc. in 2 meter band; S-106—49 to 55 Mc. in 6 meter band.

model S-85, S-86 \$119.95

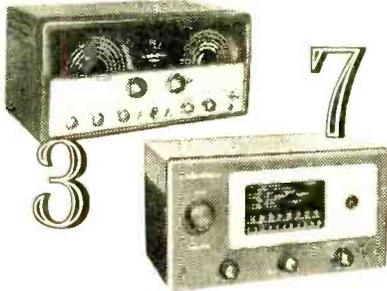A superb receiver that pulls them in on 10, 11, 15, 20, 40 and 80 meter amateur bands. Over 1000° calibrated bandspread gives better selectivity on large easy-to-read dial. Features separate tuning condenser and built-in PM 5" speaker. Coverage: Broadcast band 540-1680 kc. plus three S/W bands 1680 kc—34 Mc. S-85 AC, S-86 AC-DC.




model SX-104, SX-105 \$89.95

Two new high frequency crystal controlled/tunable receivers at low cost. First time available on single band receiver. Ideal for monitoring government marine, fire, police and other emergency frequencies. Coverage: SX-104—30 to 50 Mc.; SX-105—152 to 173 Mc.

model S-94, S-95 \$59.95

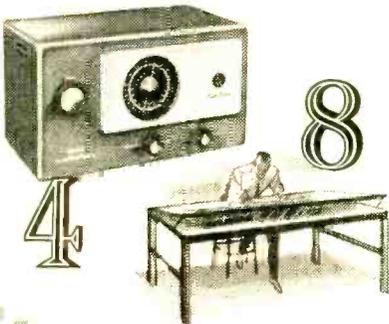Advanced models that bring in emergency radio, police and fire calls. Newly engineered FM chassis provides low frequency drift and low noise figure. Modern styling with simplified control gives easy operating. Coverage: S-94—30 to 50 Mc.; S-95—152 to 173 Mc.



**THE NEW ONE
THAT'S ON THE
DRAWING BOARD
TODAY!**

hallicrafters where the best ideas in communications are born!

CHICAGO 24, ILLINOIS

Export Sales: Philips Export Co.
100 E. 42nd St., New York 17, N.Y.


9
**NEW
 SPEAKER
 MODELS
 WITH A
 FREQUENCY
 RESPONSE
 FOR EVERY
 APPLICATION**

**MID RANGE
 EXTENDED
 TWEETER
 WOOFER
 COAXIAL**

FABULOUS IS THE ONLY WORD FOR THEM



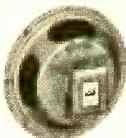High Frequency
 Model GT5F
 List Price \$8.75



Mid Range
 Model GM8J
 List Price \$13.80



Woofers
 Model G15P
 List Price \$42.65



Coaxial
 Model G12J3
 List Price \$39.75

Utah

**FABULOUS "G" SERIES
 SOUND REPRODUCERS**

Are ideal for single or multiple installations, additions in Hi Fi systems or for bi-naural applications. Their fabulous features of superb range, response and overall perfection of performance—and unbelievable low price—makes Utah's new "G" series your best buy in Hi Fi. The incomparable, precision combination of molded, seamless cones permanently welded with indestructible adhesive to rugged, 8 oz. voice coils powered by oriented grain Alnico V magnets, assures you of full power handling capacities.

Write for complete Fabulous "G" Catalog and technical folder.

See the FABULOUS "G" at your dealers today.

UTAH RADIO PRODUCTS CORP.

HUNTINGTON, INDIANA

Export Dept. Rocke International, N. Y. C.

Letters (Continued from page 26)

0.5- μ fd. capacitors are employed to control the twinkling frequency.

R. J. NORTON
 Everett, Wash.

Many thanks for remembering to send in the photo of your Xmas tree. Other readers interested in duplicating this tree can obtain the plans from our back issue department. Each back issue costs only 30 cents.

Comments on August/September

■ Thanks for the story in your August issue on tape correspondence. This QSL card is my own



idea. How do you like it? I am using a DeJur model TK820, dual speed, and a Shure 51 microphone.

ART RUBIN
 355 Summit Ave.
 Cedarhurst, N. Y.

■ Your August issue was one of the best yet. I particularly liked the article on memory devices.
 O. RELLING
 Oceanside, N. Y.

Many thanks, Otto, for your note. Readers that missed the August issue will soon see the memory device article reprinted in SCIENCE DIGEST.

■ Just finished the series by Lou Garner on printed circuits. It was excellent! Please continue the series with more on methods using silk screens and photographic techniques.

JOHN YORK
 Fishkill, N. Y.

■ Congratulations on McIntyre's dual control system in your September issue (page 63). It was just the thing I was looking for. I appreciated the well-written description.

LEE AURICK, W1RDV
 Hartford, Conn.

■ Specifically liked the issue devoted to electrets (August, page 85).

DOUG MOSHER
 Portland, Ore.

More Help for Mr. Grenier

■ To make faded tube numbers reappear (see request by Gerard Grenier, August issue, page 28), I would suggest melting some black carbon with candle wax, then pouring it over the spot on the
 (Continued on page 32)

Send for FREE booklet and get the

BIG PAYOFF

in **RADIO-TV-ELECTRONICS**

What would a \$10 or \$20 a week raise mean to you?

Just one \$10-a-week raise will repay your investment in CREI training, and leave you a profit of \$200 or more the very first year! All further raises are pure profit, and you'll be prepared for many more promotions and raises in the future!

Today thousands of electronics hobbyists have an opportunity to turn their hobbies into profits. It's the "Age of Electronics"! Trained men are in crucial demand! You may be "outside" the electronics industries now, working on a job you enjoy far less than experimenting, building, transmitting, receiving; working for less money than is being paid to electronics engineering technicians. But your "true love" is electronics. Why not awaken to your opportunities—now.

ELECTRONICS IS SCREAMING FOR MEN LIKE YOU!

Here are just two of the high-level opportunities available from coast to coast:

"Just about four months have passed since I made my first recruiting trip to CREI. As a result of that visit Messrs. Kohs, Plante and Wenger are now members of the Laboratories and Mr. Kresge soon will be . . . we have some openings now and will have others . . ."—Bell Telephone Laboratories, Murray Hill, N. J.


"Two openings in our Field Service . . . aircraft electronics . . . starting salary is \$380 and up . . ."—North American Aviation, Inc., Columbus, Ohio.

COUNTLESS POSITIONS MUST BE FILLED

And only trained men can fill them. You can get your share, if you take time now to gain that indispensable knowledge.

ALL YOU NEED IS ADVANCED TECHNICAL TRAINING

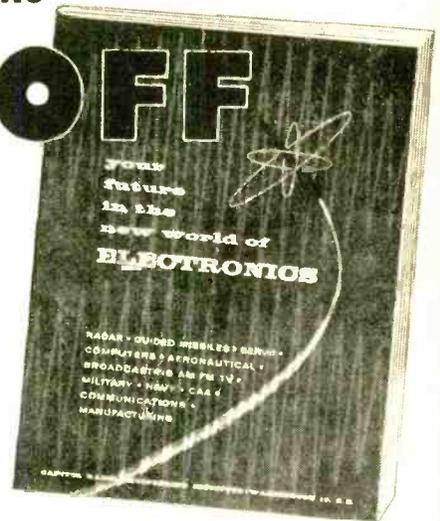Sure you have some experience. But the fellows with only partial technical knowledge move slowly, or stand still, while you—the man with advanced technical training—plunge ahead in the golden world of electronics opportunities.



ACQUIRE NECESSARY TRAINING AT HOME

Use spare-time hobby hours for CREI Home Study as thousands of successful technicians have since 1927. Get concentrated training in minimum time, then step into a good job and enjoy good pay in the mushrooming electronics industry.

SEND FOR FREE BOOKLET. IT TELLS YOU HOW

How to gain career success in the tremendous electronics industries. It pinpoints opportunities which exist. By 1960, the electronics industries will do no less than \$15 billion worth of business per year, not counting military orders. Take TV for example: There are about 34,000,000 TV sets and over 425 TV stations on the air. Color TV is pushing ahead furiously. There is but one field of maximum opportunity in this electronic age.

CREI TRAINS YOU IN MINIMUM TIME AT HOME

Thousands of men before you have benefited quickly from CREI Home Study training. Thousands of CREI graduates are now employed in industry here and abroad. Here is what they say:

"In this time of less than two years, I have almost doubled my salary and have gone from wireman, to engineering assistant and now to junior engineer. I have CREI to thank."—Frank A. Eckert, 22 Clover Lane, Levittown, Pa.

VETERAN?

If discharged after June 27, 1950, let new GI Bill of Rights help you get resident instruction. Check coupon for full data.

LIKE TO STUDY IN WASHINGTON?

CREI also offers resident instruction at same high level day or night. Classes start often. Check coupon for Residence School catalog. Qualified residence graduates earn degree: "Associate in Applied Science."

FAMOUS FOR 29 YEARS

CREI is known and respected throughout the Electronic world. Since 1927 we have trained thousands in the military, industry and government. "ASK ANY ENGINEER."

MAIL THIS COUPON . . . TODAY!

CAPITOL RADIO ENGINEERING INSTITUTE

Accredited Technical Institute Curricula—Founded in 1927
3224 16th St., N.W., Dept. 1211-C, Washington 10, D. C.

Send booklet "Your Future in the New World of Electronics" and course outline.

- CHECK FIELD OF GREATEST INTEREST
- Practical Radio Electronics Engineering
 - Broadcast Radio Engineering (AM, FM, TV)
 - Practical Television Engineering
 - Practical Aeronautical Electronics Engineering

Name Age

Street

City Zone State

Check: Home Study Residence School Korean Veteran



To help us answer your request intelligently, please give the following information:

EMPLOYED BY

TYPE OF PRESENT WORK

SCHOOL BACKGROUND


ELECTRONICS EXPERIENCE

IN WHAT BRANCH OF ELECTRONICS ARE YOU MOST INTERESTED

Lafayettes

4 AND 6 TRANSISTOR SUPERHET KITS POCKET AND HOME RADIOS FOR SPEAKER AND EARPHONE OPERATION

FIRST
BUILD
THIS

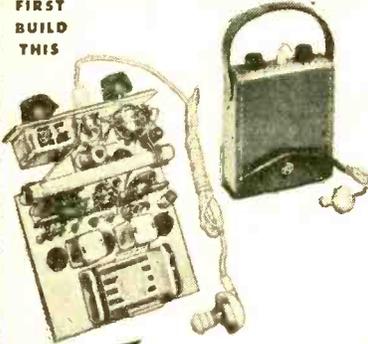

POCKET SIZE: 4" L x 3-5/16" W x 1" D BUILT-IN ANTENNA! REQUIRES NO EXTERNAL ANTENNA OR GROUND!

Lafayette engineers have designed this fascinating 4-transistor superhet receiver kit in a unique and interesting form. It is, by itself, a completely self-contained, pocket sized personal portable set which operates a miniature earpiece so only you can hear; by plugging into the KT-96 kit listed below, it is instantly converted to a full 6-transistor home radio, complete with speaker for the entire family to enjoy. The set is completely subminiaturized and utilizes the new, radically different Argonne "Poly-Vari-Con" ultra miniature 2-gang variable condenser. You will be delighted with the truly subminiature parts, from the variable which measures only 1-1/16" square x 3/8" deep, to the tiny I.F.'s and electrolytics. The chassis measures only 4" L x 3-5/16" W x 1" D. You'll be amazed at its performance. Circuit features use of 4 transistors (2 high frequency and 2 audio type) plus a germanium diode, 2 I.F. stages and built-in high gain ferrite core and antenna. The result is a sensitive, stable and selective set covering the entire broadcast band. Requires no outside antenna or ground connection. The kit is furnished complete with transistors and all parts, including battery and chassis already drilled and punched. The earpiece and carrying case are accessory items, not supplied. All necessary pictorial and circuit diagrams are furnished with simple, easy-to-follow instructions. Shpg. wt., 2 lbs.

KT-94 Kit Net 19.95

MS-311 LEATHER CARRYING CASE Net 1.95

MS-260 Super power dynamic earpiece Net 3.95

MS-278 Economy earpiece Net 1.95

THEN
BUILD
THIS

19.95

2-TRANSISTOR CLASS B PUSH PULL OUTPUT STAGE KIT WITH SPEAKER SELF-CONTAINED IN BEAUTIFUL PLASTIC CASE.

• CONVERTS 4-TRANSISTOR KIT INTO A 6-TRANSISTOR HOME RADIO WITH SPEAKER



11.50

Add a completely transistorized push-pull audio stage to your 4 transistor receiver. Complete stage including speaker and case measures only 3" H x 2 3/4" W x 1 3/8" D. Plugs right into 4 transistor kit above. Converts your 4 transistor set to a 6 transistor plus diodes superhet receiver. Performance equal or superior to commercially wired sets selling at more than twice the price. Kit includes 2 transistors, 2 transformers, 2 1/2" PM speaker, pre-punched chassis, speaker case to hold entire stage, battery, hardware, instructions and diagrams. Shpg. wt., 1 lb.

KT-96 Net 11.50

FM-AM TUNER KIT

Basic FM-AM Tuner having outstanding specifications and delivering astonishing performance — all at a budget price in easily assembled kit form.

34.95

- AFC DEFEAT CIRCUIT WITH FRONT PANEL CONTROL
- FOSTER-SEELEY DISCRIMINATOR CIRCUIT
- GROUNDED GRID TUBE AMPLIFIER
- 20-20,000 CPS RESPONSE

Choose this 7 tube compact high-fidelity FM-AM tuner whose characteristic features are found in units costing many times as much, and whose performance is unheard of at this low price. There are two front panel controls, a function control for AM, FM, PHONO, TV and a tuning/AFC defeat control. Features Armstrong FM circuit with limiter and Foster-Seeley discriminator. Simplified tuning with slide-rule dial and flywheel counter-weighted mechanism, high impedance phono input and high impedance audio output.

SPECIFICATIONS


FREQUENCY RANGE: FM 88-108MC, AM, 530-1650 KC. ANTENNA INPUT: FM, 300 ohms, AM Ferrite loopstick and high impedance external antenna. DISTORTION: Less than 1% at rated output. FREQUENCY RESPONSE: FM, + 5 db 20 to 20,000 cps, AM ± 3 db 20 to 5000 cps. SENSITIVITY: FM, 5 UV for 30 db quieting, AM, Loop sensitivity 80 UV/meter. SELECTIVITY: FM, 200 KC bandwidth, 6 db down; 375 KC FM discriminator peak to peak separation, AM, 8 KC bandwidth, 6 db down. IMAGE REJECTION: 30 db minimum. HUM LEVEL: 60 db below 100% modulation. TUBE COMPLIMENT: 2-12AT7, 1-6BE6, 1-6A8, 2-6AU6, 1-6AL5 plus selenium rectifier. SIZE: 6 1/4" high x 9 3/4" wide x 9 1/2" deep (excluding knobs). CONSUMPTION: 30 watts. For 110-120V 60 cycles AC. Attractive etched copper-plated and lacquered finish. Less metal case. Shpg. wt., 9 lbs.

KT-100 NET 34.95

ML-100.....Metal cage for above, Shpg. wt., 3 lbs. 5.00

LAFAYETTE SIGNAL GENERATOR

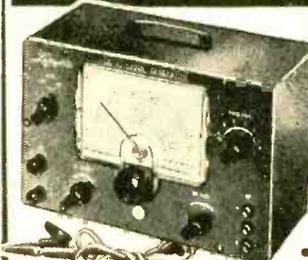COMPLETELY
WIRED
AND TESTED!
ACCURACY AND
QUALITY
GUARANTEED!



22.50

• FREQUENCY 120KC to 260MC!

- 120KC to 120MC ON FUNDAMENTALS!
- 30 DAY TRIAL PERIOD! FULL REFUND IF YOU ARE NOT SATISFIED FOR ANY REASON

Completely wired and tested instrument. Do not confuse with kits sold in the same price range. Has the quality and accuracy of instruments selling for 3 to 4 times as much. Six overlapping ranges — 120KC to 320KC, 320KC to 1000KC, 1MC to 3.2MC, 3.2MC to 11MC, 11MC to 38MC, 37MC to 130MC — all on fundamentals — calibrated harmonics from 120MC to 260MC. Switch between internal modulation at 400 cps or any external source at other frequencies. 400 cps signal can be used separately. Outputs are unmodulated RF, modulated RF and 400 cps audio. RF output is in excess of 100,000 micro volts. Jacks are provided for high or low RF output.

Highly stable special circuit design. Fine adjust RF control. AF output 2-3 volts, input 4 volts, across 1 megohm. 5 inch etched dial plate — protected by clear plastic bezel. Common AF terminals for EXT-MOD input and INT-AF output eliminates need for special connectors. Gray metal case — carrying handle — complete with leads, line cord and plug. For 105-125V, 60-60 cycle A.C. Shpg. wt., 8 lbs.

LSG-10 — Signal Generator 22.50

Lafayette Radio

165-08 Liberty Ave.
JAMAICA 33, N. Y.

100 SIXTH AVE. NEW YORK, N. Y.
PLAINFIELD, N. J., 542 E. Fordham Rd. NEWARK 2, N. J., 24 Central Ave.
BROMY 69, N. Y., 542 E. Fordham Rd. NEWARK 2, N. J., 24 Central Ave.
include postage with order.

FREE! LAFAYETTE CATALOG



ELECTRONIC CATALOG PACKED WITH MONEY SAVERS


Packed with the largest selection of Electronic, Radio and TV Parts, and equipment, PA, Hi-Fi systems, tubes, antennas, Transistor Kits, parts and components, Test Equipment, new build your own kits, tools, books, Microscope, drafting equipment, Binoculars, Telescopes, All Radio, TV and Ham supplies — ALL AT GREAT SAVINGS — For the economy minded serviceman, dealer, engineer and technician. **CHUCK FULL OF BUYS! SEND FOR YOUR FREE COPY TO-DAY.**



3 TRANSISTOR HI-FI PREAMPLIFIER KIT

New Lafayette HI-FI Pream Kit using new GE 2N190 quality audio transistors. Separate Volume, Bass and Treble controls. Frequency response 20-20,000 cps. Three phono and microphone. Provides low-noise, stable preamplification without hum and microphonics. Complete with all parts transistors, pre-punched chassis, battery and detailed step-by-step instructions. Size 4 1/2" x 3 3/4" x 1 1/2". Shpg. wt., 2 lbs.

KT-117—Complete Kit.....Net 18.45

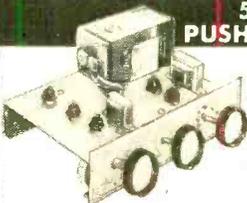

5 TRANSISTOR PUSH PULL AMPLIFIER KIT

- 1/2 WATT, CLASS B, PUSH-PULL OUTPUT
- CRYSTAL AND MAGNETIC INPUT
- SEPARATE BASS AND TREBLE CONTROLS


New 5 transistor audio amplifier for phono—microphones—tuners—etc. Excellent for the experimenter—student—or any one desiring a good transistorized amplifier.

Uses new G.E. 2N169 and 2N186A transistor. Inverse feedback for reduction of distortion. Transformer coupled driver and output stages. Complete with punched chassis, knobs, transistors, all parts and detailed instructions and diagrams.

KT-104—3.2 ohm output.....Net 22.95

KT-105—8 ohm output.....Net 22.95

TRANSISTOR CODE PRACTICE OSCILLATOR KIT

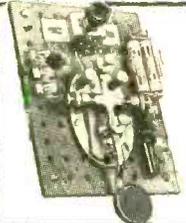

For those interested in mastering the International code, an audio tone oscillator is essential. The circuit of this transistorized feedback oscillator has the simplicity of the neon glow, the signal strength of the vacuum tube, and requires only two penlite cells for weeks of service. It may be used for solo practice, or two may send and receive with the same unit. Kit comes complete with Transistor, Telegraph Key, Resistors, Condensers, Masonite Board, etc. and Schematic Diagram.

KT-72.....Net 2.99
Cannon ECI—Single Headset.....Net 1.13

2 TRANSISTOR POCKET RADIO KIT



Packed into a 2 1/2" x 3 1/2" x 1 1/4" plastic case. This Two Transistor plus crystal diode radio kit offers many surprises, utilizing a regenerative detector circuit with transformer coupled audio stage, gives you high gain and excellent selectivity. Puls in distant stations with ease with more than ample earphone volume. Kit comes complete with two transistors, crystal diode, loopstick, Argonne transistor audio transformer, resistors, condensers, plastic case, etc. Including schematic and instructions.

KT-68A.....Complete Kit less earphones. 10.95

MS-260 New Super Power Dynamic Earphone, Ideal for Transistor Circuit Imp. 8000 ohm, D.C. 2000 ohm.....3.95

NEW POCKET AC-DC VOM MULTITESTER 2,000 ohm per Volt on AC & DC

- Completely wired — Not a kit

Accurate VOM with a sensitivity of 2000 ohms per volt on both AC and DC. Single selector switch. 3" 160 amp. meter. Scales: DC Volts: 0-10-50-500-1000; AC Volts: 0-10-50-500-1000; Ohms: 0-10K, 0-1 Mez; DC Current: 500 ua and 500 ma; Decibel: -20 to +22, +20 to 36; Capacity: 250 mmf to .2 mfd and .005 to 1 mfd. Heavy plastic panel, metal bottom. 4 1/2" x 3 1/2" x 1 3/4". With batteries and test leads. Shpg. wt. 4 lbs. RW-27A.....8.95



NEW! Mail Order Center ----->

3 TRANSISTOR SUPERHET POCKET RADIO KIT

- A TRUE POCKET SUPERHET RECEIVER—NO EXTERNAL ANTENNA!
- NO EXTERNAL GROUND!



A remarkable sensitive, super-selective pocket superhet receiver with astonishing performance over the complete broadcast band. Uses 2 high-frequency and one audio transistor plus efficient diode detector and features 2 specially matched IF transformers for maximum power transfer. The components are housed in a professional looking beige plastic case.

The receiver's appearance enhanced by attractive maroon and silver station dial. Sensitive built-in ferrite antenna eliminates need for external antenna. A designer's dream in a true pocket superhet receiver! Complete with all parts, transistors battery, case, dial and easy to follow step-by-step instructions. 4 1/2" x 2 1/2" x 1-1/16". Shpg. wt., 1 lb.

KT-116—Complete Kit, less earphone.....Net 16.95

MS-260—Super Power Dynamic Earphone.....Net 3.95

1 AND 2 TRANSISTOR POCKET RADIO KITS

ONE TRANSISTOR POCKET RADIO KIT—KT-97

- IDEAL FOR STUDENTS, HOBBYISTS AND EXPERIMENTERS

- PRE-PUNCHED CHASSIS FOR ADVANCEMENT TO 2 TRANSISTOR KIT



Ideal, low-cost transistor pocket radio kit. Super-selective ferrite loop antenna permits good reception up to 50 mile radius with approx. 50 ft. antenna and good ground. Provisions for advancement to 2 transistor receiver. Complete Kit with simple detailed instructions. 3 3/4" x 2 3/4" x 1". Shpg. wt., 1 lb.

KT-97—Complete, less earphones.....Net 4.50

TWO TRANSISTOR POCKET RADIO KIT—KT-98

Contains all KT-97 components plus additional R-C coupled transistor stage for increased sensitivity and output. Complete with instructions. Shpg. wt., 1 lb.

KT-98—Complete 2 Transistor Kit, less earphone.....Net 5.95

MS-111—Crystal earphone for KT-97 and KT-98.....Net 1.49

MS-260—Super power dynamic earphone.....Net 3.95

20,000 OHM PER VOLT MULTITESTER SEMI KIT



A new kind of kit—the difficult work is already done—you wire in only a few multipliers and mount the battery holder to complete the unit. A fine high sensitivity (20,000 ohms per volt DC — 5000 ohms per volt AC) instrument employing a 3" 40 microamp movement. Has 4 DC voltage, 4 AC voltage, 2 DC current, 3 resistance and 2 db ranges. Complete with test leads and detailed instructions. Size 3 3/4" x 4 3/4" x 1 1/4". Shpg. wt., 3 lbs.

KT-20—Kit.....Net 11.95

**Lafayette
Radio**
DEPT IK

165-08 Liberty Ave.
JAMAICA 33; N. Y.

SEND FREE
CATALOG!

NAME -----

ADDRESS -----

CITY -----

ZONE ----- STATE -----

**CUT OUT
AND MAIL
TODAY!**



KITS! KITS!

HERSHEL'S KITS ACCLAIMED BEST!

ALL KITS CONTAIN THE FINEST ASSORTMENTS. OVER 10,000 SOLD!

YOUR CHOICE ANY KIT LISTED IN THIS AD 97c

- 30 TUBE SOCKETS
- 2 1/2-lbs of HARDWARE
- 15 ROTARY SWITCHES
- 10 Electrolytic Condensers
- 40 Radio & TV KNOBS
- 40 BY-PASS Condensers
- 60 CARBON RESISTORS
- 60 MICA CONDENSERS
- 100 SET SCREWS
- 8 1N22 XTAL DIODES
- 50 Ceramic Condensers
- 15 Variable Condensers (Air and Mica)
- 50 RF CHOKES
- 20 POWER RESISTORS
- 1 Phono Motor 115 Vac.
- 50 TERMINAL STRIPS
- 200 ft. HOOK-UP WIRE
- 1 TRANS. 6.3V-110 Vac.
- 5 Meissner Plug-In COILS
- 5 PILOT PANEL LITES
- 50 FUSES 3AG UP
- 1 Meter Rectifier O-1MA.
- 1 IGN. COIL 3V-15,000 VSEC.
- 25-Ft. Phono-Mike Cable
- 3 SELENIUM RECTIFIERS (65 MA. 110V.)
- 1 PHOTO Electric CELL

- 10 STRAIN INSULATORS
- 1 TELEGRAPH KEY
- 5 MICRO SWITCHES
- 75-Ft. 300 OHM TV LEAD-IN
- 25 TV STAND OFFS
- 24 SHOCK MOUNTS
- 1 PHONO XTAL with NEEDLE
- 1 PIX TUBE BRIGHTENER
- 3 CONDENSERS (500 MMFD 20,000 Volt)
- 100 Ft. of SPAGHETTI
- 1 RCA Flyback Trans.
- 10 BATHTUB CONDENSERS
- 10 GRAIN WHEAT LAMPS
- 5 RADIO-PHONO CHASSIS
- 4 LOOP ANTENNAS (RADIO)
- 1 PHANTOM ANTENNA A-62
- 100 SPRINGS (RADIO-PHONO)
- 5 RADIO NOISE FILTERS
- 25-Ft. RG-58/U COAXIAL CABLE with PLUGS
- 2 Powerful ALNICO 5 Magnets

All New MYSTERY PACKAGE of ELECTRONIC PARTS



Worth \$40.00

Our Price **\$3.95**

Ship Wt. 20 lbs.

It's the surprise of your life! 20 pounds of BRAND NEW usable GOVT. surplus. The ideal gift for hams, etc.

OIL CONDENSER

\$1.65



2 MFD. 3000 VDC. Pyranol Oil W/ Mounting Brackets. 1-1 Mid. 3000 VDC. removed from equip. 4 3/4" x 4 1/4" x 2 1/2"

ARC-5 COMMAND TRANSMITTER

\$8.95



Hottest Buy in the Country

TERMS: Cash with order or 25% DOWN—BALANCE C.O.D. ALL PRICES NET F.O.B. DETROIT MINIMUM ORDER \$2.00

TYler 8-9400

HERSHEL RADIO CO.

5249 GRAND RIVER Detroit 8, Michigan

Letters (Continued from page 28)

tube where you think the numbers were originally positioned. Let the black wax cool, and after a short time heat the tube to melt the wax. Once the lump of wax is removed, rub the tube briskly—the numbers should suddenly reappear. Do this a few times, as the numbers will soon fade out again.

PHILIP HOFF
McKees, Pa.


■ Best method is to apply full strength household ammonia to the tube. This will generally bring the numbers up.

F. R. COLEMAN
Victory, W. Va.

Once again, many thanks to all readers suggesting ideas on how to bring up invisible tube numbers. Other methods were printed on page 30 of the October issue.

Building P.E. Projects

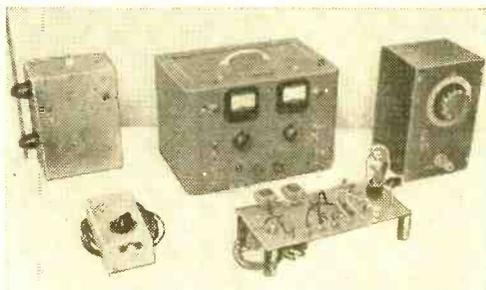■ This photo shows most of the construction projects that I have built from the pages of P.E. I had a real "ball" building them. There are eight in all, counting the extra metal locator, field strength meter, and R/C battery rejuvenator that



are not shown. In the photo (from left to right) are the Lorenz transmitter, headphone adapter, battery eliminator, thyratron experiments and metal locator.

DON BOGGS
Manhattan Beach, Calif.

Medium-Wave DX

■ I have been reading the letters about long-wave DX and thought some readers might be interested in medium-wave (broadcast-band) DX. Some of my best loggings include: LRA, PAR, CB138, BED2, CMBZ, WNEW, WWVA, WINS, WCAU, CMQ, PRES, and WMGM.

I use an Eddystone 740 receiver and a 33' antenna. I would like to hear from other readers about their DX.

EDDIE W. BURY
81 Pyenot Hall Lane
Cleckheaton, Yorkshire
England

Thank you, Eddie, for your interesting letter. Although POP'tronics does not publish a column on medium-wave DX, we do recommend that you contact the Newark News Radio Club, 215 Market St., Newark 1, N. J., about its bulletins on broadcast-band (as we call it in the states) DX. —30—

QUALITY INSTRUMENTS BY EMC

Save More . . . Service Better



A COMPLETE "ECONOMY-LINE" WITH HIGH-PRICED FEATURES.

Advanced production techniques and extensive quality controls assure you of a high quality, reliable instrument at the lowest possible price . . . compare and you'll agree — it's smart to buy EMC.



VOLOMETER — EMC Model 102

Durable molded bakelite case, pocket size. Features 800 micro amperes D'Arsonval-type meter, 3 1/2 inch plastic meter, accurate to within 2%. Three AC current ranges — and the same zero adjustment for both resistance ranges.

\$14.90 wired & tested \$12.50 kit form

VOLOMETER — EMC Model 104

This precision-engineered instrument features a 4 1/2 inch, 50 microampere meter, with alnico magnet . . . with 3 AC current ranges to 3 amps and three resistance ranges to 20 megohms.


\$26.95 wired & tested \$19.25 kit form



MUTUAL CONDUCTANCE TUBE TESTER — EMC Model 206 P

One of the finest pieces of tube testing equipment at a price comparing favorably with emission-type testers. This completely flexible model using lever-type switches offers extremely accurate results with ease of operation.

\$83.50 (hand rubbed carrying case)

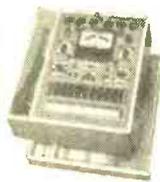

TUBE TESTER and REJUVENATOR — EMC Model 209

Miniaturized instrument gives fast, absolutely accurate checks for tube quality, shorts, leakages, continuity, and opens on all modern and future tubes . . . uses standard emission test for quick readings on modern, 3 1/2" plastic meter. \$38.50 in hand rubbed carrying case.

\$35.90 (hammertone metal case)
\$25.90 kit form



VACUUM TUBE VOLTMETER — EMC Model 106

Specially designed for field alignment of TV and radio sets. Uses 1% precision resistors for voltage multipliers. 5 db ranges. Full scale deflection of 1 1/2 volts for both AC-DC volts. Housed in compact portable bakelite case. Size 4 1/4" x 5 1/4" x 2 7/8". Net weight 3 lbs.

\$35.00 wired and tested \$23.90 kit form

VOLT-OHM-CAPACITY METER — EMC Model 107

Directly measures capacity, resistance and complex waveforms peak to peak. Some of the high quality features at no extra cost are: expanded scale cannot burn out . . . measures 50 mmd to 5000 mfd . . . inductance from 1.4 henries to 140,000 henries in 4 ranges . . . 1% multipliers for voltage capacity and resistance measurements.

\$48.90 wired & tested \$34.50 kit form




WIDE BAND OSCILLOSCOPE FOR COLOR AND MONOCHROME TV EMC Model 601

EMC Model 601 oscilloscope gives you the highest quality features ever found in this price field. Exclusive features: full 5 mc bandwidth for color TV servicing — push-pull vertical amplifier, .02 volt per inch sensitivity — 5 UP1-5" scope tube — 60 cycle phasing control — DC positioning controls eliminates overshooting and bounce — built-in peak-to-peak calibration reference — 2-step compensated attenuator input — multivibrator sweep, from 15 cycles to over 75 kilocycles.

\$117.90 wired and tested — \$70.90 kit form

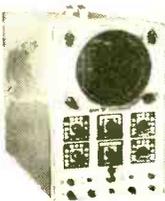Write today for FREE illustrated catalog and technical information on the EMC economy line.



RF—AF CRYSTAL MAKER TV Bar-Generator — EMC Model 700

The popular 700 has three extra features — bar generator for TV adjustment with a variable number of bars available for horizontal or vertical alignment. Complete coverage from 18 cycles to 108 megacycles on fundamentals.

\$55.90 wired and tested



Yes, send me a complete catalog of all EMC Instruments plus full information about the EMC "Profit" Plan for jobbers. P1-9

NAME _____
OCCUPATION _____
COMPANY _____
STREET _____
CITY _____ STATE _____

EMC

ELECTRONIC MEASUREMENTS CORP.
280 Lafayette Street • New York 12, N. Y.
EXPORT DEPT. — 370 BROADWAY, N. Y. 13, N. Y.

Save at Esse

Parts Kits: Buy in Kit Form and Save \$\$\$

Many of these kits may be purchased for less than any single item alone. Convenience of having parts at hand saves you time and money. All new useful parts. No dogs. All popular brand mdse. Your word-of-mouth advertising makes our business. Satisfaction Guaranteed or money refunded. Illustrated are kits like those you receive.

A. KIT Power Resistors



\$2.99

Navy power resistor kit. 50 of various values from 10-160,000 ohm 25 to 200 watts. Check what the 160,000 ohm 200 watt bleeder would cost separately. Ship. wt. 11 lbs.


B. KIT Variable Condensers



\$2.99

10 new popular replacement variables from one to five gang. Ship. wt. 9 lbs.


C. KIT Midget Variables

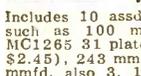

\$2.99

Includes 10 ass'd. variables such as 100 mmfd. BUD NC1285 31 plate (reg. net \$2.45), 243 mmfd. dual 33 mmfd, also 3, 15, 35, 50 and 100 mmfd. All midline types. Ship. wt. 3 lbs.


D. KIT Paper Tubular Condensers

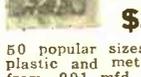

\$2.99

50 popular sizes including plastic and metal encased from .001 mfd. to 1 mfd. 600 V. and cathode by pass types. Popular brands, no freak types or sizes. Ship. wt. 3 lbs.

E. KIT Tube Sockets

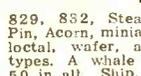

\$2.99

829, 832, Steatite, XU-4 Pin, Acorn, miniature, octal, loctal, wafer, and molded types. A whale of a buy. 50 in all. Ship. wt. 3 lbs.


F. KIT Radio Knobs



\$2.99

100 various knobs for radio & television. Push on, set screw, pointer, audio, red, brown, black and white. All for reg. 1/4" shaft. Ship. wt. 3 lbs.


G. KIT Wafer Switches

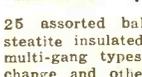

\$2.99

25 assorted bakelite and steatite insulated single & multi-gang types for band change and other circuits. Ship. wt. 4 lbs.


H. KIT Rheostats & Potentiometers

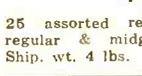

\$2.99

25 assorted replacement, regular & midget types. Ship. wt. 4 lbs.


I. KIT Mounting Hardware

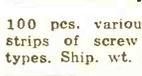

\$2.99

100 pcs. various terminal strips of screw & solder types. Ship. wt. 3 lbs.

J. KIT Coil Kit

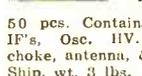

\$2.99

50 pcs. Contains RCA TV IF's, Osc. HV. osc. RF choke, antenna, & RF coils. Ship. wt. 3 lbs.

K. KIT Insulators



\$2.99

50 pcs. Includes aircraft strain, antenna, feed thru, stand off, and mounting types. All low loss. Ship. wt. 6 lbs.


L. KIT—RF IF



\$2.99

Contains 25 ass'd. IF, RF, OSC, antenna, and a \$5.75 Meissner wave trapper. Ship. wt. 4 lbs.


M. KIT Lamp Bulb Replacement

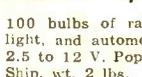

\$2.99

100 bulbs of radio, flashlight, and automobile types 2.5 to 12 V. Popular types. Ship. wt. 2 lbs.


N. KIT Fuses

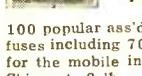

\$2.99

100 popular ass'd. cartridge fuses including 70 amp. type for the mobile installations. Ship. wt. 3 lbs.

O. KIT Television Yokes

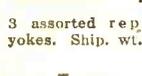

\$2.99

3 assorted replacement yokes. Ship. wt. 4 lbs.


P. KIT Hook Up Wire



\$2.99

Over 7 lbs. or 1000' of various cut lengths hook up wire all ready stripped at each end and tinned for easy soldering. A real time saver. Multi colors to give the professional look. Ship. wt. 9 lbs.


Q. KIT Electrolytic Caps

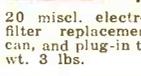

\$2.99

20 misc. electrolytics for filter replacement. Paper, can, and plug-in types. Ship. wt. 3 lbs.


R. KIT Oil Bathtub Cond.

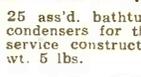

\$2.99

25 ass'd. bathtub by pass condensers for that rugged service construction. Ship. wt. 5 lbs.


S. KIT Box of 50 Crystals

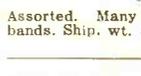

\$2.99

Assorted. Many for ham bands. Ship. wt. 3 lbs.

T. KIT Carbon Brushes

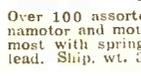

\$2.99

Over 100 assorted new dynamotor and motor brushes, most with spring & bronze lead. Ship. wt. 3 lbs.

Christmas Special!! ALL 20 KITS \$49⁹⁵

Save money and give the gift that will keep any radio man busy for hours going thru this treasure house of parts that will be the envy of his fellows. Over a \$1,000 inventory. Remember, this is all picked, useful, new merchandise. All sold to satisfy or money refunded.

ESSE BARGAIN BOX

Include these items in orders of \$5.00 or more or remit 50c addn. for cost of handling. All new mdse.


Butterfly — 8 stator 7 rotor for 300-1000 Mc. Ship. wt. 3 lbs. Price. **\$3.95**



Co-axial relay — 12 V. or 24 V. operated & can be connected for 6 V. operation with mtg. plate. Size 4 3/4 x 5 3/4 x 2 1/2". Ship. wt. 2 lbs. Price **\$1.25 ea.**



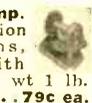Miniature pump. Ideal for aeration of aquariums, labs, etc. with strainer. Ship. wt 1 lb. Price. **79c ea.**



J-47 Key. Ship. wt. 1 lb. Price **\$1.00 ea.**



Remote tuning head for CRV Receiver or other equip. 2:1 gear ratio. Ship. wt. 2 lbs. Price . . . **79c ea.**



Field Telephone Case. Ideal for portable equipment or replacement. New canvas or leather, choice. Ship. wt. 3 lbs. Price. **79c ea.**



Wood varnished instrument case for precision instruments. Size 20" x 9" x 4 1/4". Ship. wt. 7 lbs. Price. . . **\$1.75 ea.**



1 RPM Haydon Timer Motor. Ship. wt. 1 lb. 24 V. AC. **79c** 110 V. AC. **\$1.49**



4 MFD — 600 V. Capacitor. Oil type. Ship. wt. 1 lb. Price. **79c ea.**



Push button control C30/ARC-5. Ship. wt. 2 lbs. Price. **79c ea.**



Shock mounts. Lord **1179A/U.** Ship. wt. 3 lbs. Set of four. Price. **.79c**



Thermometer — 40° to 110° F. Mount element thru wall for outside temp. Ship. wt. 4 lbs. Price. **\$3.50 ea.**



Cam operated switch. Six individual SP switches with roller type push buttons. Ship. wt. 2 lbs. Price **79c ea.**



AS 27/ARN-5 110-335 Mc. Antenna. Ship. wt. 54 lbs. boxed. Price **\$1.25**

AN-148A Antenna 150-180 Mc. Ship. wt. 8 lbs. Price **\$2.79 ea.**



Dual .1 mfd. 4500 V. Cap. GE Pyranol type. Ship. wt. 2 lbs. Price. **\$1.79 ea.**



RBM 6 V. 35 Amp. Contact Relay. Ship. wt. 1 lb. Price . . **79c ea.**



.2 mfd. 5000 V. Oil Capacitor. Ship. wt. 2 lbs. Price **\$1.79 ea.**



.12 mfd. 15,000 GE Pyranol Capacitor. Ship. wt. 9 lbs. Price **\$3.75 ea.**



GOLF CAR MOTOR \$4.50

New 1 3/4 HP. battery operated motor for building up your golf car or other use. Operates from 12 to 24 V. with speed to 6000 RPM. Measures 1 1/4" dia. x 9" long, 5/8" shaft. Wt. 1 1/2 lbs. Ship. wt. 13 lbs.



ANNUNCIATOR PANEL \$2.95



Contains four sensitive coils which drop announcing plate on energizing. Contains also 8 phone jacks for use on switchboard, door systems, etc. Panel size 7 1/4" x 2 1/2". Ship. wt. 3 lbs. New.

1 KW PLATE TRANSFORMER \$17.50



Arma HV. Plate transformer for the construction of that 1 KW. Rig. Two CT 400 V. windings may be series connected for 800 V. Size 9 1/2" x 9" x 8". Ship. wt. 100 lbs. New Navy surplus. Price. **\$17.50 ea.**


OAV-1 TEST SIGNAL GENERATOR \$19.95

This signal generator was used to provide a test signal of constant frequency for operation and alignment of IP amplifier stages in the CG-46ACQ type receivers. The generator covers the range between 150-250 megacycles. Amplitude modulated square wave output is obtained at frequencies of 1, 10, and 100 Kc. depending on the position of the Freq. mod. Pulse switch. A 15 Mc. signal is also provided by a second osc. stage. Power is supplied by internal 115 V., 60 cycle AC supply connected to source by cord provided. Wt. of unit 62 lbs. Brand new with instruction book. Price. **\$19.95**



POWER SUPPLY KIT \$2.99

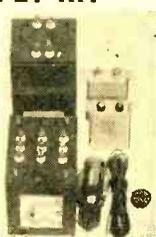Components include power transformer, dual 12 henry choke, two 4 mfd. 600 V. oil condensers, rectifier tube & socket, and hook up wire. Use usual power supply circuits for full wave 250 V. 150 Ma. DC or half wave 500 V. 150 Ma. DC supplies. Ship. wt. 30 lbs. All for **\$2.99**




TEST SET EE-1 NEW—\$19.50

A test set for aircraft containing AC & DC volt, ohms, meter, tachometer, pressure gauge & test gauge cords & tools. In aluminum suitcase type case that opens forming sloping 2 sec. panel. Ideal for your test bench applications. Cost hundreds of dollars but yours in original evacuated shipping container for only **\$19.50**. Ship. wt. 270 lbs.



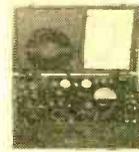Tube Checker... Dynamic Mutual Cond. \$22.50 ea.



Here is a real buy on a portable dynamic mutual conductance tube checker built for the Signal Corp. by leading mfgs. Checks most of latest tubes including TV types. Some defect is in all but can be easily repaired by the radio man, sometimes only a tube needs replacement. Ship. wt. 18 lbs.

ESSE RADIO CO. -42 WEST SOUTH ST., INDIANAPOLIS 25, INDIANA

REMIT SHIPPING CHARGE AND INSTRUCTIONS WITH ALL ORDERS. OTHERWISE ORDER WILL BE SHIPPED EXPRESS COLLECT. ALL ITEMS GUARANTEED TO YOUR SATISFACTION OR MONEY REFUNDED IF RETURNED PREPAID WITHIN 10 DAYS OF RECEIPT.

FREE

1956 EICO® CATALOG

SAVES YOU 50% on your TEST INSTRUMENT & HI-FI COSTS 50 KITS & WIRED MODELS to choose from!

EICO® 84 Withers St., Bklyn., N. Y.

Show me HOW TO SAVE 50% on Laboratory Precision test instruments & Hi-Fi. Send FREE catalog & name of neighborhood EICO Distributor. **PE-11**

Name

Address

City Zone State

Occupation

Prices 5% higher on West Coast



Home, car, TV, appliance repairs:
#540 NEW!
REDI-TESTER
KIT \$12.95
WIRED \$15.95



VACUUM TUBE
VOLT METER
#221
KIT \$25.95
WIRED \$39.95




NEW! PEAK-TO-PEAK
VTVM
#232 & UNI-PROBE
(pat. pend.)
KIT \$29.95
WIRED \$49.95



1000 Ohms/Volt
MULTIMETER
#536
KIT \$12.90
WIRED \$14.90

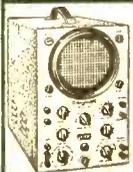PERFORMANCE-PROVED by TV manufacturers, electronic schools and over 100,000 Servicemen. OVER 1 MILLION in use today!



5" PUSH-PULL
SCOPE #425
KIT \$44.95
WIRED \$79.95
Lowest-priced
professional Scope



NEW! COLOR &
BLACK-&WHITE
5-MC TV
SCOPE #460
KIT \$79.95
WIRED \$129.50



TUBE TESTER #625
KIT \$34.95 WIRED \$49.95



#666
NEW! DYNAMIC
CONDUCTANCE
TUBE &
TRANSISTOR TESTER
KIT \$69.95 WIRED \$109.95

YOU BUILD EICO KITS in ONE evening, but — they LAST a LIFETIME!



NEW! 20-WATT
Ultra-Linear
HIGH
FIDELITY
AMPLIFIER
#HF20
KIT \$49.95 WIRED \$79.95



NEW! HIGH
FIDELITY
PREAMPLIFIER #HF61
KIT \$24.95 WIRED \$37.95
with Power Supply:
KIT \$29.95 WIRED \$44.95



Sine &
Square Wave
AUDIO
GENERATOR #377
KIT \$31.95 WIRED \$49.95



RF-AF SIGNAL
GENERATOR
#320
KIT \$19.95 WIRED \$29.95

LATEST engineering • FINEST components • EASY instructions

NEW!
RF-AF SIGNAL
GENERATOR #324
(150 kc to 435 mc!)
KIT \$26.95 WIRED \$39.95



TV-FM SWEEP
GENERATOR
#360
KIT \$34.95 WIRED \$49.95



MULTI-SIGNAL TRACER #145
KIT \$19.95 WIRED \$28.95



1000 Ohms/Volt
MULTIMETER
#556
(4 1/2" METER)
KIT \$16.90
WIRED \$23.50

EXCLUSIVE 5-WAY GUARANTEE on components, instructions, performance — and LIFETIME service and calibration!



6V & 12V
BATTERY
ELIMINATOR &
CHARGER
KIT \$29.95 WIRED \$38.95



R-C BRIDGE & R-C-L
COMPARATOR #950B
KIT \$19.95 WIRED \$29.95



Test radio, hearing aid,
flashlight, photo-flash,
electronic equipment
batteries:
BATTERY TESTER
#584
KIT \$9.95 WIRED \$12.95



RETMA Res. Sub.
Box #1100
KIT \$5.95 WIRED \$9.95



RETMA Cap. Sub.
Box #1120
KIT \$5.95 WIRED \$9.95



Politics and pure reason mix in computer guesswork on national elections



Lewell Thomas (above) and Charles Collingswood (left) take tips from Univac in following the progress of the election.

By HERBERT REID

Electronic Election Bet


DWIGHT EISENHOWER and Adlai Stevenson won't be the stars of the show when TV covers the election. At the moment of decision, CBS cameras turn their backs on personalities, parties, and passions. Instead, Univac, Remington Rand's giant electronic computer, swings into focus. With its blinking lights and shining dials, this computer out-sparkles even the flashiest politico. But, unlike the candidates and their drum-beaters, Univac never raises its voice. The even-tempered humming of its circuits and the logical nature of its innards bespeak the very opposite of politics: pure reason.

For all its rationality, Univac won't throw a wet blanket of cool mathematics over the excitement of election night. On the contrary, with the whole nation figur-

ing the odds of the race, Univac gets into the act as champion guesser of them all.

Hindsight for the Future. If you are planning to wager some last-minute election bets, better take a tip from Univac, no matter what your own "expert" notions may be. CBS learned this the hard way on election day in 1952. At 8:30 P.M., November 4, less than two hours after the first poll closed, the computer had predicted an Eisenhower landslide. At that time, only three million returns were in from scattered Eastern states. No returns at all had been received from 21 states. Univac had to rely solely on historical information in those cases. But the machine wrote: "100:1 in favor of Eisenhower."

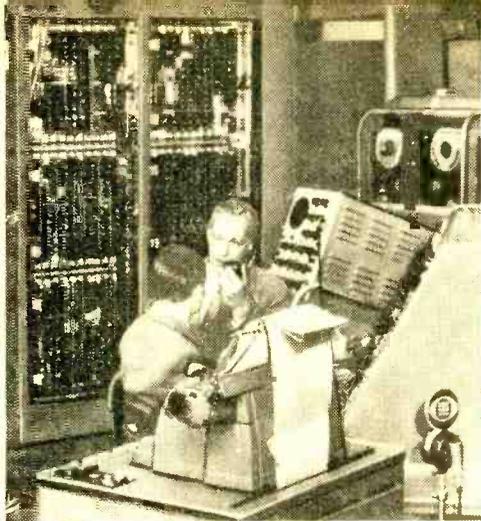Everybody had been expecting a close race. The scientists masterminding the



Latest election forecast rolls out of automatic typewriter. Rack in rear does the reckoning.

computer were doubtful of their own robot. They threw out the prediction, not daring to put it on the air. They thought something was wrong with the setting of the machine. There was a mad scramble, after which they proceeded to feed Univac a series of cautious "correction factors" to lessen the assumed chances of Eisenhower carrying Southern states. Despite this, Univac still stuck to Eisenhower, but reduced the odds to 6 to 5.

By midnight, evidence had piled up showing that Univac's first prediction had been amazingly accurate. And the final tally of electoral votes brought complete vindication. Univac had said, on the basis of a

relative handful of returns, that Eisenhower would get 438 electoral votes and Stevenson would get 93. The actual result was 442 to 89.

Had Univac been human, it probably would have spelled out as a final message: "I told you so!" Univac wasn't psychic. But primed with past election results, the machine had at its electronic fingertips more political data than any human brain could scan and digest. Thanks to this storehouse of facts and the fast sifting of information, the machine's agile hindsight out-smarted the foresight of the prognosticators.

History and Math. This trick of "looking backward" into the future is not at all unique. In fact, it is the basis of all science, which always assumes that the future will shape up as a logical outgrowth of the past. Thus, past experience becomes the raw material for future theory, and hindsight forms the basis of prediction.

Yet history and experience in themselves are not enough. The trick lies in knowing how to interpret the historical information. This is something no computer can do for itself. Like all so-called electronic brains, it hasn't really got an ounce of intelligence. It is merely an oversize gadget—blind, dumb, senseless and inert. What makes it work is the mind of its human masters, who have fed it in advance mathematical instructions as to how to deal with the numbers from the polls, and who,


(Continued on page 113)

Simplified Radar to Use "Wamoscope"

RADIO ENGINEERS attending the Western Electronic Show in Los Angeles recently were amazed to hear of a single-tube radar set. Developed by Sylvania Electric Products, Inc., for the U.S. Navy, the radar has been dubbed the "wamoscope." Literally interpreted, "wamoscope" means "wave-modulated oscilloscope." Mi-

crowave radar signals can be fed directly into the tube where—in a single glass envelope—they are amplified, detected, and finally displayed on a fluorescent screen.

Secret of the "wamoscope's" unusual ability is the traveling-wave focusing principle. (The focusing solenoid is shown in the photo as the metal cylinder.) The "wamoscope" can be designed for any u.h.f. band and with any size cathode-ray screen. Although the first one is reserved for the military, radio engineers are planning on possible applications in miniaturized commercial and industrial closed-circuit TV systems.

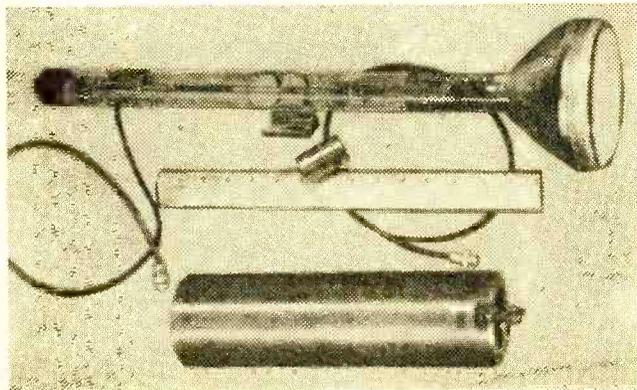

First "wamoscope" measures just under two feet, but contains complete radar reception system for direct signal display on cathode-ray screen on end of tube.

POPULAR ELECTRONICS

SEE WHO'S ON THE PHONE

SOON YOU WILL SEE as well as hear your partner in a telephone conversation. Practical two-way transmission of pictures along with the voice over ordinary telephone lines from coast to coast was recently demonstrated by Bell Telephone Laboratories. Head and shoulders of the callers appeared clear and recognizable on small TV attachments to ordinary telephone sets.


Unlike conventional video transmission channels, the new "picture-phone" uses a narrow frequency band, making it possible to send pictures over regular telephone wires rather than expensive coaxial cable. Because of such limitations, only two "frames" per second are transmitted. This suffices, however, since only the portrait of the caller is shown and there is no need for fast action on the screen.

Furthermore, the raster of the small tube requires only 40 lines for good picture definition. By such means, the video bandwidth was reduced to 600 cps (as compared to 4 megacycles on regular TV). This 600-cycle band travels over the telephone wires exactly like a voice signal, needing no special video lines or amplifiers. It is because of the drastic reduction in bandwidth that the picture-phone appears practical for general use in the not-too-distant future. Both local and long-distance service is planned.

Though transmission of spoken words remains the prime rational aspect of tele-



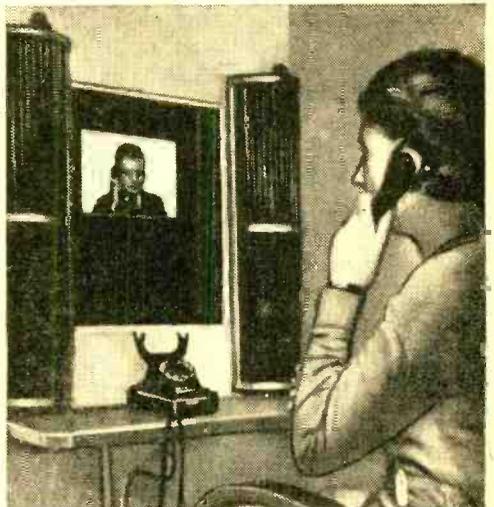
New "picture-phone" (above) displays caller on screen of small TV tube. The camera behind the phone completes the two-way setup. Shown below is the first practical picture-phone which operated in Germany twenty years ago. However, Hitler's military needs halted this promising development.



Picture tube, camera and controls are combined in this experimental model. Camera lens is visible above tube screen.


phony, millions of people rely emotionally on the telephone for its power of making physically distant people seem close. The addition of sight to sound will vastly enhance this psychological by-product of direct message transmission.

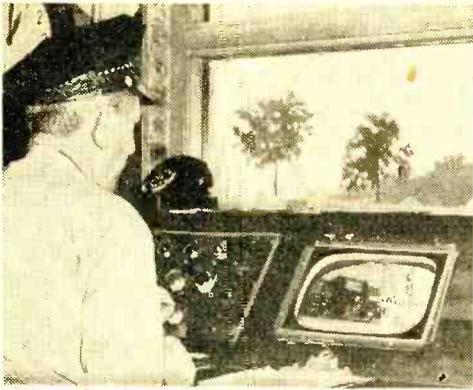Even the occasional need for privacy was foreseen by Bell engineers. If you have to answer the phone after running out of the shower, you can just switch off the video so that you can see your caller but he can't see you.



Unique Video Generator

ANY VISUAL PATTERN, picture, or printed message can be reproduced on a television set using the "Dyna-Scan" video generator. This flying spot scanner produces a fully modulated r.f. carrier containing synchronizing pulses and complete video information to drive a standard TV receiver. It can be used with a single set or any number of sets, or fed into a master antenna system. By inserting a slide transparency in the device, test patterns, messages, etc., printed on the slide will be shown on the TV set to which the unit is connected. Net price of Dyna-Scan is about \$200. For further information, contact the manufacturer, B & K Mfg. Co., 3731 N. Southport Ave., Chicago 13, Ill.

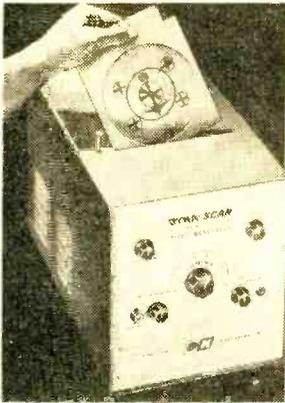

TV Turned Traffic Cop

REGULATING THE FLOW of truck traffic in and out of Zenith Radio Corp.'s main plant in Chicago is a company-installed closed-circuit TV system. Photo at left shows a plant guard coordinating truck movements with the aid of the traffic picture displayed on his TV screen. The TV camera which picks up the action is located at a strategic spot along the two-lane ramp leading to the plant.

Before the use of TV, a steady procession of trucks throughout the day presented problems of delay and stack-ups. With the new system, one man stationed at a single control point can regulate traffic safely and easily. Waiting time is reduced, all trucks move faster, and the guard need never leave his seat. The TV screen he uses is housed in a master panel along with controls for electrically operated ramp doors and gates. A two-way voice communications system permits the guard and the driver of a truck to exchange traffic and check-out information. The driver's microphone is mounted in the plant wall near the waiting truck.

Live TV to S.A.?

LIVE TELEVISION broadcasting from the United States as far south as Venezuela is entirely possible, according to Dr. Allen B. Du Mont, chairman of the Du Mont Laboratories, Inc., Clifton, N. J. On a recent trip to the Caribbean area and South America, Dr. Du Mont noted that local reception was as good as reception in the United States, and that there appears to be an eager audience for U. S. telecasts. Such programs could reach Venezuela by use of "forward scatter" facilities between Florida and Cuba. Dr. Du Mont suggests the installation of a receiving station and beam transmitter atop a 9000-foot mountain in Haiti to relay signals directly into the South American area.



Electronic Alarm Guards Pool


GUARDING against accidents as well as trespassers in this swimming pool is an electronic alarm system known as "Pool Guard." The system, activated by a body entering the water, sounds a loud warning bell. It requires no outside electrical connections, being operated on two low-voltage batteries.

A sensing device in the water responds to the displacement of water when an unwanted body enters the pool. The control unit, containing an "ON-OFF" switch, may be located at the pool or remotely. With the switch "OFF," the alarm system is deactivated, and the pool may be used normally. Pool Guard is made by Supertron Corp., Los Angeles 65, Calif.

The oscilloscope, the most versatile of all measuring devices, enables man to perceive facts of nature to which his own senses are blind. It is today's foremost instrument of basic research and applied technology.

By H. H. FANTEL
Associate Editor

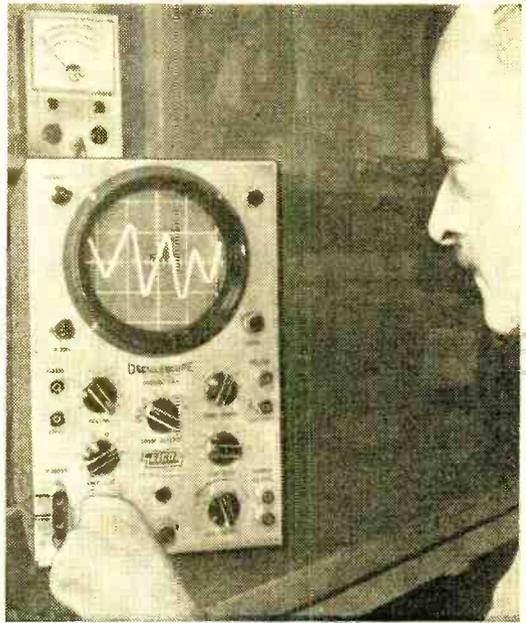**Past and present blend
in a single moment in
new cathode-ray display**



Tricked-up Cathode Rays Are "On the Beam"

AS AN "OLD DOG" that has been the pet of physicists ever since the early days of electronics, the cathode ray is lately learning an amazing number of new tricks. Instead of just dancing about on an oscilloscope or putting on TV shows in your home, the cathode ray has taken some memory training and also learned to write. But before showing off these latest frills, let's look at the basic function of the cathode-ray tube.


In its most familiar form, the cathode-ray tube acts as the "picture tube" in television sets. Electrons shoot out in a narrow beam from the "electron gun" in the neck of the tube. They hit a phosphor screen, which lights up under their impact. On the way between the electron gun and the tube screen, the beam is bent—or "deflected"—by electromagnetic fields set up by coils around the tube neck. Another way of deflecting the beam is to employ capacitor plates within the tube, which bend the beam by setting up electrostatic fields along its path. These deflections guide the beam across the tube face so that the "picture" appearing on the tube face represents the electric signal fed to the tube.

In oscilloscopes, the cathode-ray tube acts as a measuring device. It indicates anything that can be expressed as an electric voltage. Factors and forces like pressure, tension, temperature, distance, speed,


and weight, can be converted into electrical terms and gaged accurately by the beam pattern on the face of the cathode-ray tube. The measuring range is virtually unlimited, since the scale of representation can be varied from zero to a very high value by switching resistors of different sizes into the circuit. A half-inch line on the tube face might mean a little or a lot. Assuming you are measuring weight, that half-inch line might represent a ton or a grain, depending on the scale selected. This extreme variability of range makes the oscilloscope the most versatile of all measuring instruments.

The Instant Image. Speed is another asset of the cathode ray. No need waiting for a swinging pointer to come to rest; no chance for the pointer to lag behind the signal. For the "pointer" in a cathode-ray tube is a beam of free electrons, capable of moving at almost the speed of light. Since there is nothing faster, the beam can theoretically keep up with even the most rapid events. In actual practice, the time constants in the deflection circuit dictate a speed limit somewhat below the beam's unbeatable record. But for most practical purposes, the beam keeps a comfortable speed margin on almost anything it has to tackle.

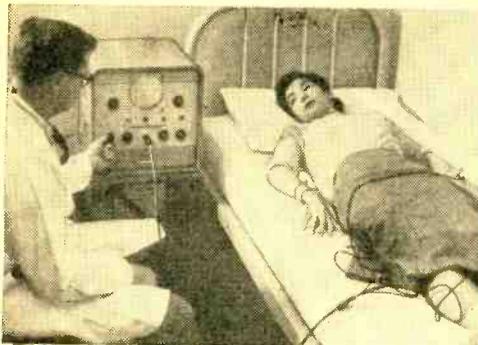But speed is only half the story. Weight, or rather the lack of it, makes up the rest,



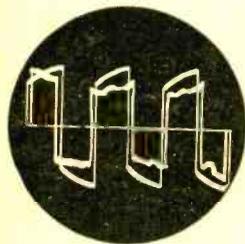In medical instruments, the memory-endowed cathode-ray tube retains traces of past heartbeats to compare successive heart contractions. The functioning of other organs can be similarly checked.



Two traces occurring one after the other are presented simultaneously for comparison on Memotron.

since electrons are virtually weightless. The beam has practically no inertia. It can shuttle back and forth through intricate patterns at breakneck speed without "going off" at the curve. This fast and accurate shuttling enables the beam to trace high-speed oscillations in their rapid rise and fall, showing them as the familiar waveform patterns.

With all these advantages, it is no wonder that the cathode ray became the universal measuring tool of nearly every science. Yet in all its countless jobs, the cathode ray suffered from one major disability. It could display information about any occurrence only during the instant that the event actually happened. It presented data from moment to moment without being able to compare the things happening "now" with the things that had happened "before." It took no account of the past. In other words, it had no memory. The past was always lost.

The Past Regained. Now the cathode ray—which as Man's lightest and speediest tool has helped him master mass and space—also enters the dimension of time. The Memotron, developed by Hughes Products, is a new cathode-ray tube with the ability to "store" information of past events so that they can be compared with later data. Both past and present show simultaneously on the screen of the tube.

The image on the tube face lasts until it is intentionally "erased." This is particularly convenient for the study of transients,

i.e., unique occurrences which happen very quickly and only once. A timing pulse in radar, a critical moment in music (e.g., the beat of a kettledrum), the current surge in starting a motor . . . all these are typical transients. The Memotron "holds" them permanently for thorough study. Tracings of events occurring at different times can be "stacked" on the tube for comparison at a single glance.



Hughes engineers went even a step further. Instead of simply "remembering" light curves against a dark background, as does the Memotron, their new Tonotron tube "remembers" whole pictures in all their various shades of grey. What's more, the amount of contrast is variable so that the halftones can be adjusted for best picture quality.

The length of time for which the picture is retained on the screen after being flashed on by the scanning ray is called the "persistence" of the image. The Tonotron features variable persistence, adjustable on the control panel. This, in addition to an accurately shaded presentation of the grey scale, assures "high fidelity" in picture reproduction.

Frozen Action. One Tonotron application is in the form of a TV tube capable of "freezing" the picture. Earlier this year, such a tube was demonstrated by the Institute of Radio Engineers in New York. Mounted side-by-side with a conventional TV receiver and tuned to the same channel, the Tonotron TV tube allowed viewers to push a button and "stop the action" while the program on the regular tube went ahead.

Yet the greatest need for the Tonotron and the new tube's immediate chance to

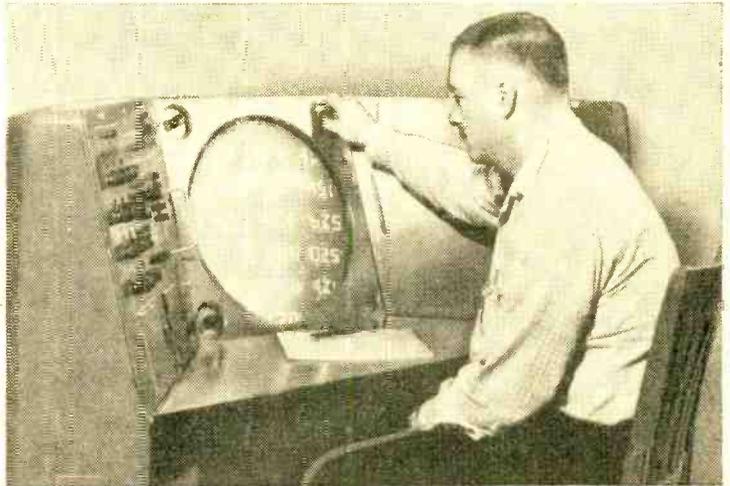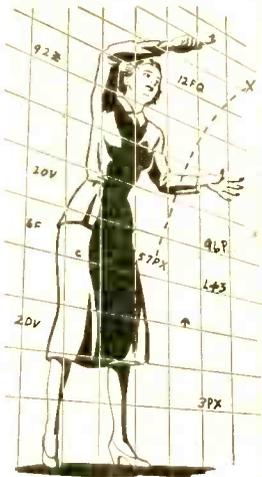The Tonotron, newest cathode-ray tube, retains complete images with halftone shading for variable time periods. It "freezes" action on TV picture at right while show continues on regular tube.



Air traffic patterns are marked in conventional way on transparent board by girl above. But to keep up with today's faster planes and denser traffic, human reactions proved too slow and human error too much of a risk. The "writing tube" (above, right) now takes over the job, marking the planes' positions as fast as radar can track them. This device, a recent development of the Boston Electronics Division of American Machine & Foundry Co., will contribute to greater air safety.

prove its usefulness lie in airborne radar. "With this tube, a pilot need not take his eyes from the control and peer into a hood to see a radar presentation," says Dr. A. V. Haefl of Hughes Aircraft Co. "The picture is so bright that he can see it at a glance, night and day, and he gets a continuous picture rather than fleeting blips. He controls the time it takes the picture to fade, holding it brilliant for as long as needed, or erasing it at will. Radar gives the pilot an electronic 'map' of the air around him, showing any storms or obstacles ahead. He will clearly see mountains and the ground below him even through blinding weather. With its ability to hold the picture and to
(Continued on page 116)

HOW IT WORKS

The "memory" of a cathode-ray tube is based on the well-known fact that a capacitor is capable of storing electric charges. Just behind the viewing screen on the tube is a fine wire mesh coated with a dielectric, which acts as a negatively charged capacitor. This capacitor-type storage mesh is usually flooded with a gentle stream of slow electrons sprayed on by a special "flood gun." But because of its negative charge, the storage mesh bars the path of these electrons. They never reach the screen and the tube stays dark.

Yet when a signal is to be recorded, the high-velocity, sharply focused beam from the regular electron gun smashes through the barrier of the storage mesh and disrupts its negative charge. This makes an electronically transparent "cutout" for the slow electron stream from the flood gun. Now the electrons can travel through the mesh and the tube screen lights up in the patterns "cut out" by the writing beam. The steady electron flow from the flood gun then keeps these areas lit. And the pattern is thus "remembered."

To erase, a positive voltage is pulsed over the whole storage mesh, equalizing all the charges and obliterating the stored pattern.


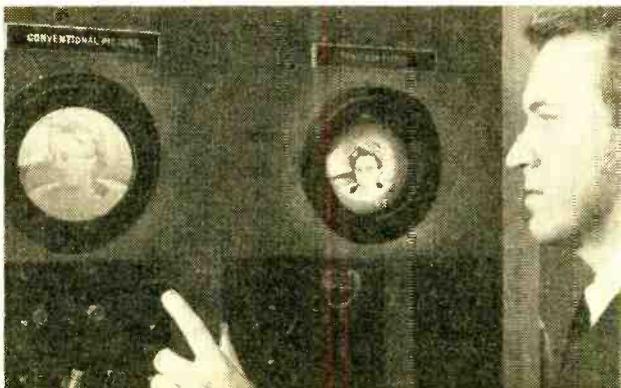


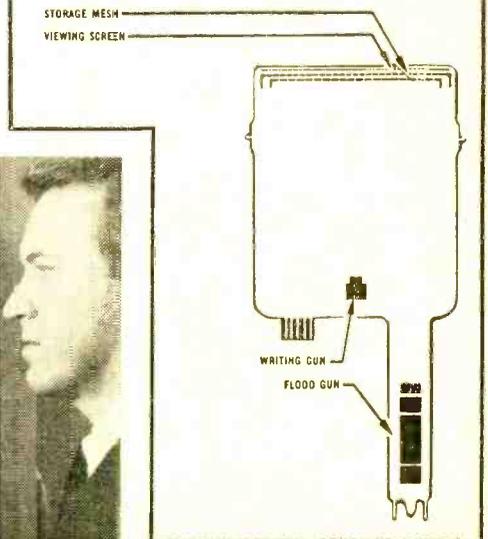

Chart Dials TV Troubles

DEFECTS in television reception that are caused by faulty tubes or adjustments are described and illustrated on a large circular chart, a portion of which is shown at right. When the chart's dial is turned to the difficulty encountered, a slide-rule index pin-points the adjustments to be made and the tube or tubes that may need replacing. Known as the "TV Tube Trouble Shooter," the chart is available for \$1.00 from Maple Enterprise, Box 42, Dept. 100, Hillside, N. J.



Video Rig Checks Freight

FREIGHT CARS entering Southern Railway's Citico yard, Chattanooga, Tenn., have their pictures taken by RCA closed-circuit TV system to speed sorting of cars for classification and switching to trains. Cameras, installed at yard entrances, enable clerk in office (photo below) two miles away to "see" and record action. Intercom system adds to rig's versatility.



Fast/Slow TV Scanner

A COMPATIBLE system for combining fast-scan and slow-scan television economically has been announced by General Electric Co., Syracuse, N. Y. The system changes fast TV (30 pictures per second) to slow TV (one picture every 4 or 5 seconds) by means of an electronic converter.

Fast TV is the kind used by broadcasting stations and is what you see on your home receiver. The slower scan, while not providing fine detail and unsuitable for action scenes, is considered adequate for many industrial applications, particularly when there is no motion involved. What's more, slow TV can be sent over modified telephone lines and is therefore a much cheaper method than fast TV which requires coaxial cables.

The new G.E. converter, still in its laboratory developmental stage, will permit industrial television users to take advantage of the good features of both scanning methods within one closed circuit system.

Computer Speeds Supplies

A GIANT computer (IBM 705) has been installed as the electronic brain for the Army Signal Corps computer-communications system for signal supply management



at the Army Signal Supply Agency in Philadelphia. Designed by International Business Machines Corp., it is a key element of the data processing network that provides high-speed control of global logistical operations of signal supplies.

Operating with the speed of light, the computer can make 30,000 decisions per second, 8400 additions or 1200 multiplications per second. It can process 8000 tabulating machine cards a minute—thousands of times faster than this can be done by manual operation. The IBM 705 is expected to effect a major saving in the cost of supply control and management.



The "Tirade Terminator"

an Instant Heating Intercom

By HARVEY POLLACK

UNLESS YOU LIVE in a very unusual household, you must have had more than one exasperating session with an irate wife or mother on the subject of time wasted in the workshop building useless gadgets. Here's a warranted method of putting an end to those dispiriting gripe sessions. Build something for *her* exclusive use and convenience!

As a protective device and step-saver, an instant-heating (no warm-up time) intercom between the kitchen and the front door will permit her to find out who is ringing the bell without approaching the door itself; undesirable callers can be sent on their way through the medium of a two-way conversation right from the kitchen sink!


Ordinary office intercoms are not satisfactory for home use. Generally, they use


tubes that have a 15 to 30 second warm-up time. To avoid this waiting period, such units are usually left running all day long—an unnecessary extravagance for the average apartment-dweller or home-owner. The intercom described in this article eliminates the need for a warm-up interval by using battery-type tubes arranged for 117-volt a.c. operation.

Construction. The plastic cabinet is supplied without holes for the controls in the front panel so that it may be used as either the master unit or the remote speaker housing. Three $\frac{3}{8}$ " holes should be drilled in the desired locations before doing anything else; they can be used as templates for locating the control openings in the front apron of the little chassis.

Mount the major parts on the top of the chassis (see the photo on page 50). Se-

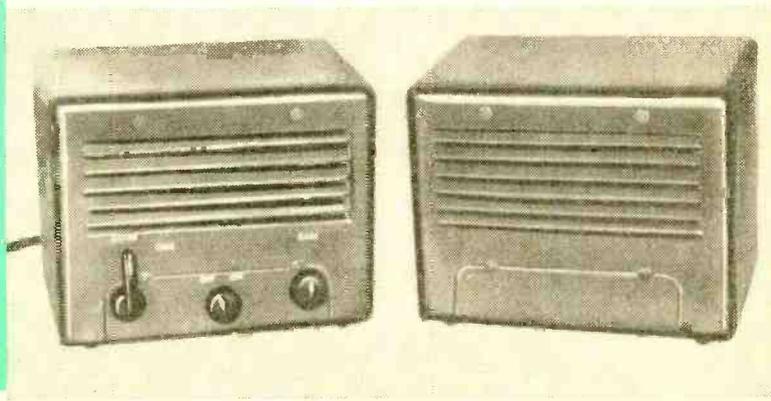Plastic cabinet comes without holes for controls drilled in front panel; it can serve either as master unit or remote speaker housing. Trimming the cabinet with decals will make intercom look like expensive commercial unit. Waterproof housing may be used for remote out-of-doors unit (see above).



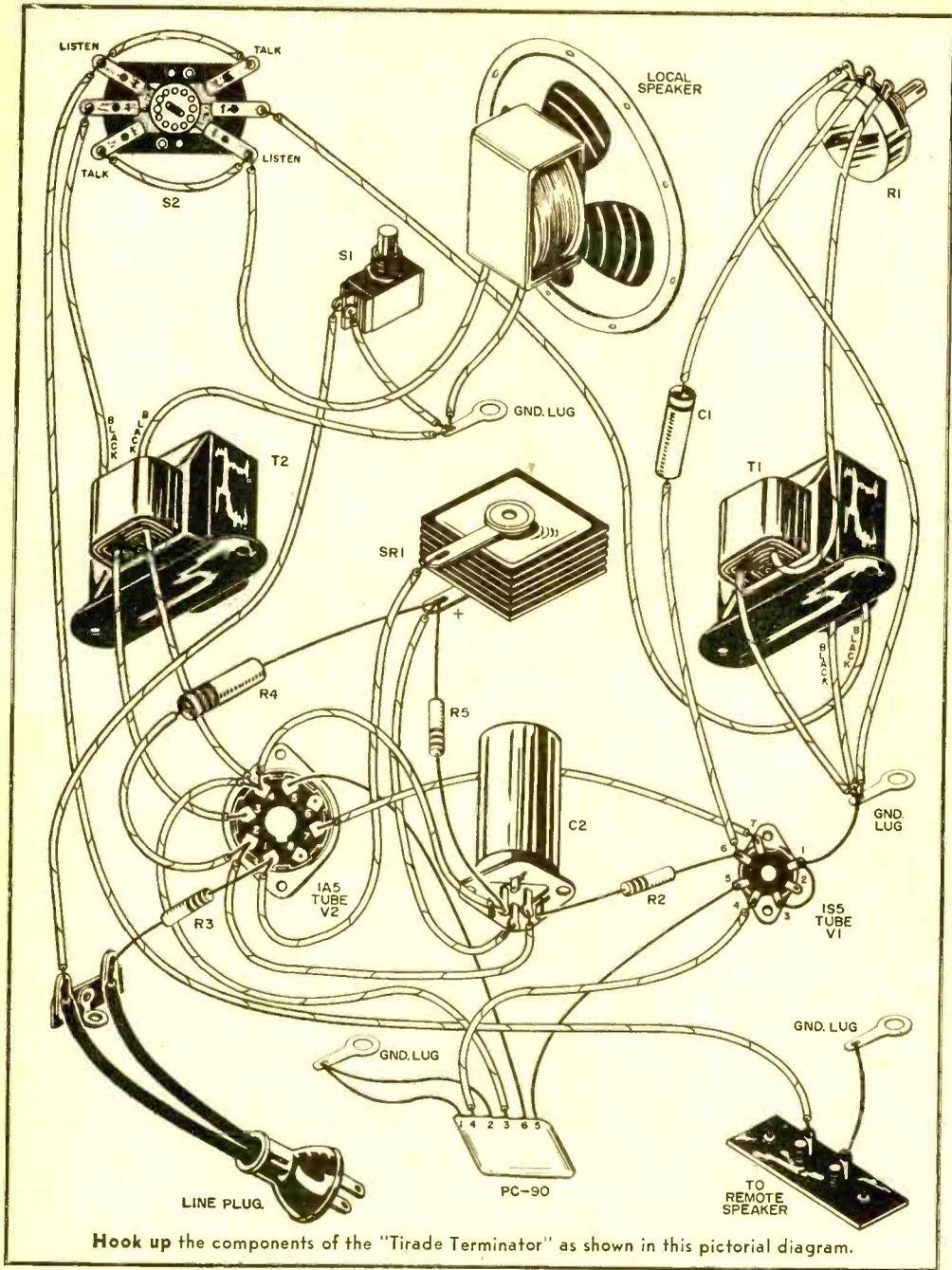


Hook up the components of the "Tirade Terminator" as shown in this pictorial diagram.

cure the gain control (*R1*), the canopy-type switch (*S1*), and the *TALK-LISTEN* selector switch (*S2*) to the front apron. Do not cut the shafts short as yet; this can be reserved for last once you are quite sure that everything fits properly.

Plan your layout so that input transformer *T1* is physically close to *R1* and pentode amplifier *V1*. Since connections

between these parts are high impedance paths, they are quite subject to hum pick-up and feedback unless made as short and direct as possible. Except for this grid circuit, the remainder of the wiring is not particularly critical. However, delicate filaments combined with high-gain amplifiers are subject to 60-cycle hum unless carefully handled. If the hum is excessive, it

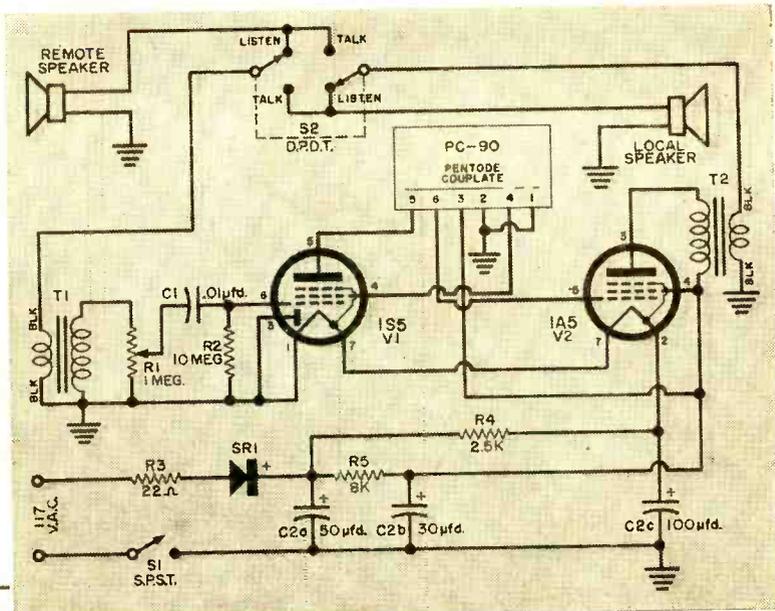Wiring diagram for instant-heating intercom. The "Trade Terminator" eliminates need for a warm-up interval by using battery-type tubes arranged for 117-volt a.c. operation—making it particularly suitable for home use. Only the wiring for the grid circuit is critical. The pentode Couplate (PC-90) should be installed after all other wiring is completed.



PARTS LIST

C1—0.01- μ d., 400-volt paper tubular capacitor
 C2a/C2b/C2c—Filter block capacitor, 50-30-100 μ d., 150-150-25 volt, Twist-lok type in can (Sprague TVL-3427)
 R1—1.0-meg. volume control potentiometer, audio taper (Mallory U-53, Midgetrol)
 R2—10-megohm, $\frac{1}{2}$ -watt resistor
 R3—22-ohm, $\frac{1}{2}$ -watt resistor
 R4—2500-ohm, 10-watt resistor (Sprague Kool-ohm Type 10KT)
 R5—8000-ohm, 1-watt resistor
 S1—S.p.s.t. switch, rotary canopy type with long shaft
 S2—D.p.d.t. TALK-LISTEN switch, spring return (Centralab Type 1464)
 SR1—65-ma. selenium rectifier (Sarkes-Tarzian Model 65)
 T1—Intercom input transformer, primary 4 ohms to secondary 25,000 ohms (Stancor Type A-4744)
 T2—Output transformer, 25,000-ohm load to 4-ohm voice coil (Stancor Type A-3327)

V1—1S5 tube
 V2—1A5 tube
 PC-90—Pentode-type Couplate (Centralab)
 SPEAKERS—4"-diameter, 4-ohm voice coil PM speakers (Lafayette SK-25)
 1—Miniature 7-pin socket, top mounting with shield saddle
 1—Octal socket, 1" mounting hole, bottom mounting
 1—Shield for 1S5 tube
 1—3" x 6 $\frac{1}{8}$ " x 1 $\frac{1}{4}$ " chassis (ICA 29080)
 1—Intercom cabinet, brown plastic (Available from Lafayette Radio, 100 Sixth Ave., New York, N. Y.)
 1—Cabinet for remote speaker (outdoor use—ICA 3988; indoor use—Lafayette unit above)
 1—Insulated terminal board, two terminals, for remote speaker leads
 1—Line cord and plug for 117-volt a.c. line, Elmenco fuse plug, with two 1-amp. fuses
 Misc. rubber grommets, solder lugs, hardware, hookup wire, line cord for remote speaker

usually means one of three things: poor grounds, defective filament filtering capacitor (C2c), or excessively long grid leads in the 1A5 circuit.

All wiring should be completed before the pentode Couplate (PC-90) is installed. This is a printed electronic circuit which replaces three capacitors and three resistors. It is a terrific space-saver and is quite inexpensive. Wire it in last, covering those leads which might touch each other with short lengths of "spaghetti" tubing.



Testing and Installation. Preliminary tests are always performed with the a.c. plug disconnected from the power line. These tests do not guarantee that the circuit wiring is correct in all details; they are intended merely as protective measures to avoid damaging tubes or other compo-

HOW IT WORKS

A permanent magnet dynamic speaker may be used as either a microphone or an audio reproducer. On the TALK position of the switch, the local speaker is connected to the input transformer (T1) and serves as a microphone. Varying acoustic pressure applied to the speaker cone by sound waves induces a tiny audio voltage in the voice coil. This voltage is stepped up by the high secondary-to-primary turns ratio of T1, further amplified by pentode V1, and the signal fed to the grid of the output tube where it is converted to audio power. The remote speaker is activated by the output tube via the selector switch. In the LISTEN position, the speaker functions are reversed, the local speaker now doing the reproducing and the remote speaker acting as a microphone.

Use of battery-type tubes is made possible by rectifying the a.c. from the 117-volt power lines and then by filtering it in C2a, C2b, and R5. R4 is the filament dropping resistor which insures that a maximum of only 0.05 ampere will flow through the series filaments. The remainder of the circuit is straightforward. To save considerable space, a printed circuit Couplate is used between V1 and V2.

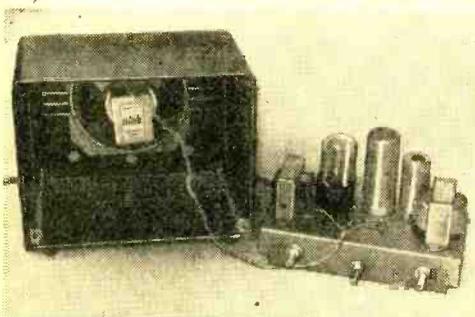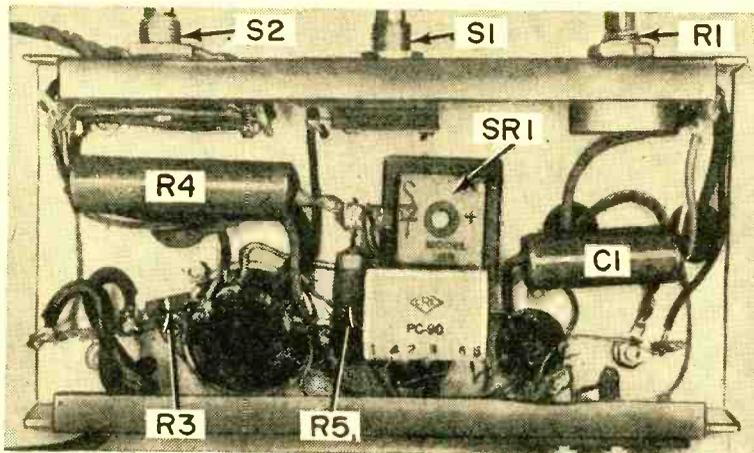Parts are mounted as shown in photos at right (under-chassis view) and below. If you fit a small piece of plywood tightly into slots near bottom of cabinet, the chassis can rest on this base. A small plywood lip glued to the back of the wood will prevent chassis from sliding, thus holding it securely in place without use of metal screws anywhere.





nents when power is first applied. (See chart below).

When the requirements of the tests have been satisfied, power may be applied with both speakers connected. *It must be remembered that the chassis is at the potential of one of the legs of the a.c. line.* The following precautions must be observed to avoid possible electrical shock and blown fuses.

Connect a 117-volt incandescent lamp (any wattage will do) from the chassis to a ground pipe or other ground point; often the screw which holds the wall outlet plate to the wall box is grounded and will serve the purpose. Turn the intercom on and then insert its line cord plug into the wall receptacle.

If the lamp lights, the a.c. plug is in the wrong way and must be reversed; reversal should cause the lamp to go out, indicating that the chassis is now at house-ground potential. If the lamp does not light, reverse the plug to make sure it does light when the plug is in the wrong way. This is the only means of establishing that the ground point you are using is *really* at house-ground potential.

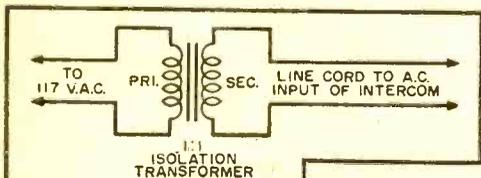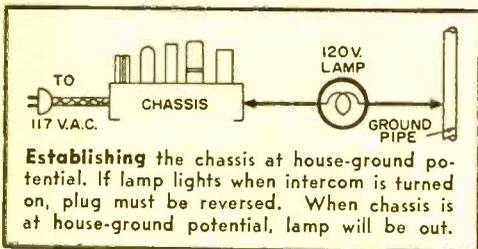Once this is ascertained, the plug should be reversed so that the lamp is extinguished. (Continued on page 131)




To eliminate any chance of shock, an isolating transformer having a 1:1 turns ratio could be connected as shown between the line and the a.c. input to the intercom—making precautions in text unnecessary.


Chart at right lists preliminary circuit tests that must be made before using intercom.

SECTION TESTED	OHMMETER CONNECTIONS		APPROX. READING SHOULD BE:
	From	To	
Filament circuit	Plus end of selenium rectifier SR1	Chassis	2500 ohms
Plate and screen circuits	Pin #4 of V2	Chassis	3300 ohms
TALK-LISTEN switch circuit. (Switch first on LISTEN, then on TALK)	Ungrounded remote speaker terminal screw on output terminal board	Ungrounded voice coil lug on local speaker	10 ohms for either switch position
A.c. input circuit (S1 off)	One prong of a.c. plug	Other prong of a.c. plug	Infinite

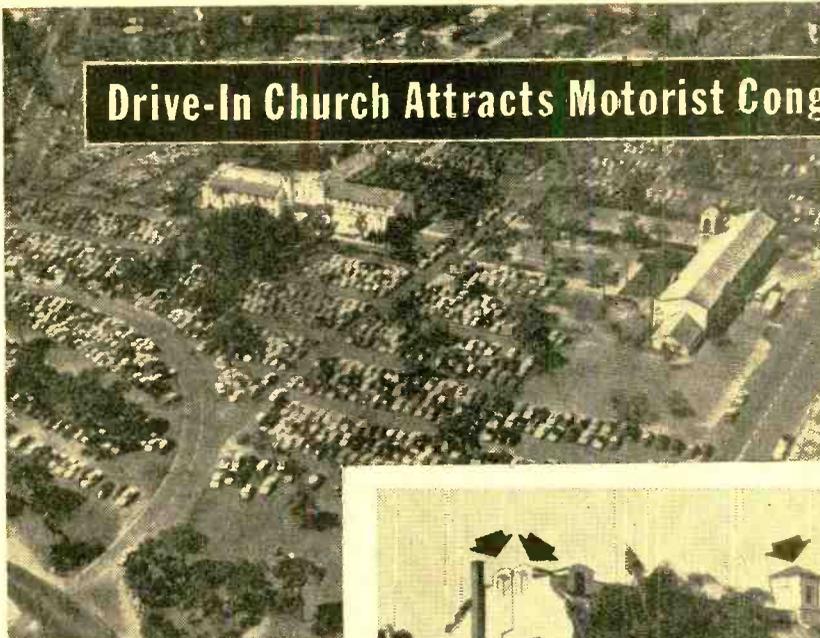Drive-In Church Attracts Motorist Congregation



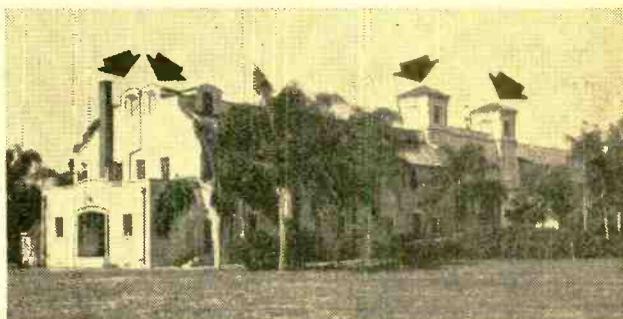
Aerial view (left) of drive-in church shows worshippers in parked cars during Palm Sunday services. Below, arrows indicate where four speakers are installed on main building.



PULPIT eloquence, aided by a unique public address system, has turned an acknowledged "white elephant" into a highly successful religious edifice that boasts congregations of as many as 10,000 people and a fame which is spreading over the world. Known as the Pasadena Community Drive-In Church, it consists of an aggregation of buildings and lush green ground located seven miles outside of St. Petersburg, Florida, and has built its present attendance from little more than a handful of worshippers.

Motivating force behind the drive-in church is dynamic, sparse-framed Pastor J. Wallace Hamilton, D.D. The p.a. system was installed by Altec Service Company whose problem—in addition to the indoor setups—was to cover 18 acres of outdoor area. A room high above the chancel was fitted with a control console, tape recorders, patch panel, amplifiers, and monitor speakers. Microphones and reproducing speakers are located at strategic spots within the church and about the grounds. The patch panel handles 24 circuits. Eight Altec "Voice of the Theatre" speaker systems serve to distribute the sound. Electrically operated windows and curtains, acoustical treatment of rooms, Hammond organ, concert grand piano, and a team of 60 ushers—in addition to Dr. Hamilton's personal staff of seven—complete the picture of this unique drive-in church.


-50-

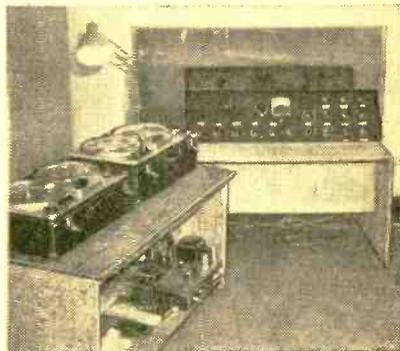

Control room (above), placed behind window affording view of parking area, shows professional sound setup used.



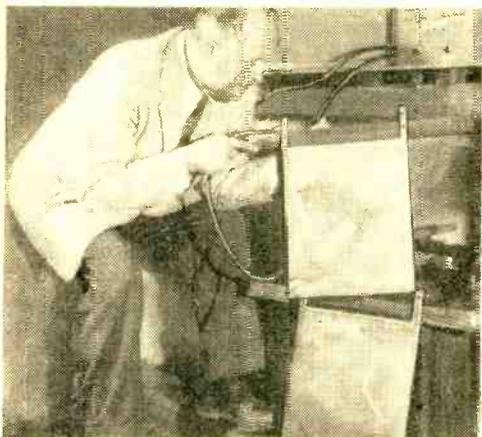Rev. J. Wallace Hamilton, D.D., in his study at left, has successfully applied electronics to religion in this famed drive-in church.




Good-Bye Barnacles

AN INVENTOR has developed an "electronic coating" for ship hulls with which he expects to eliminate the costly twin foes of the shipping industry—corrosion and barnacles. By electronic means, the ship's plates are polarized, causing a thin, flint-hard protective coating of minerals from the sea to form on the hull. This makes the ship very uninviting to plant and animal life and also keeps away rust and corrosion. Inventor Henry Burkey claims that the coating will save millions of dollars yearly by eliminating the need for scraping and painting hulls. At left, Burkey inspects test plates after submersion in raw sea water.


Gas with a Kick

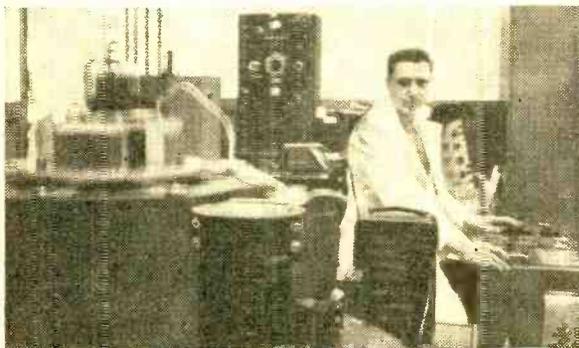A NEW TYPE of long-life dry battery is now under development at the Union Carbide and Carbon Co. Unlike conventional batteries, which use metals as their active chemical agent, these new cells (right) are energized by gases acting on a caustic paste. They will furnish uninterrupted power as long as oxygen or hydrogen are fed into them. Their first job may be as a power source for submarines.



Bell Shakes Them Up

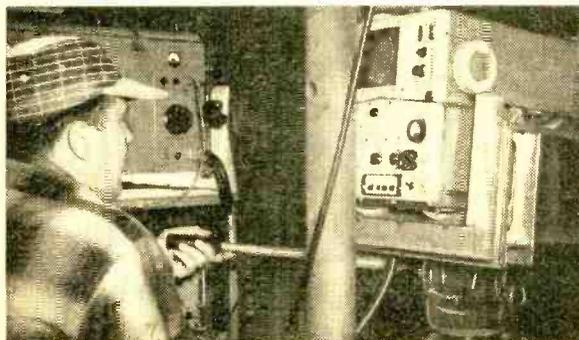VIBRATION TESTS for electronic components of ballistic missiles are made at Bell Telephone Laboratories. In the photo at left is equipment being subjected to severe test "punishment"—shock, vibration, and extreme temperatures. Electronic components intended for use in the intercontinental missiles Atlas and Titan must be inured to such rigors to endure rocket flight.



TV Peeks from Sky

WITHIN THE CABIN of a helicopter, an engineer pans the camera of a new airborne TV system developed by Philco Corp. for the U. S. Navy. From aloft, the TV transmitter scans amphibian landings and other ship-to-shore movement, relaying the information to remote command posts. Excellent pictures were obtained more than 50 miles away even before sunrise.



The Hi-Fi Boost

TREBLE BASS

By LEON FIELDS

ANYONE WHO HAS ever read a set of specifications describing a hi-fi amplifier has, at one time or another, done a double-take when confronted with the following typical statements: (1) the amplifier is flat from 20 cps to 30,000 cps ± 0.1 db, and (2) separate bass and treble controls provide as much as 20 db of boost or attenuation at low and high frequencies respectively.

"Why," inquires the hi-fi'er, "does the manufacturer go to such lengths to achieve uniform amplifier response, only to allow the 'uneducated' customer to upset it by the use of tone controls? Aren't we defeating the whole concept of high fidelity by incorporating these 'continuously variable amplitude-distorting' knobs?"

The question is a legitimate one and must be answered. After all, high fidelity does mean "faithfulness of reproduction," and it is highly doubtful that the first bassoon player of the Philharmonic Symphony has a "bass-boost" knob on his instrument. Your amplifier does have one,

Tone controls permit matching the output of your hi-fi rig to room acoustics as well as to your own listening tastes

and a treble control as well. And they're designed for your use. More than mere gadgets, they can serve you well in increasing your hi-fi enjoyment.

"Mellow Like a Cello." The history and development of tone controls parallels the changing public taste for reproduced music. It also follows the fidelity and flexibility of music that is broadcast and recorded. Early "tone controls" in the better

Separate treble and bass tone controls are standard items on hi-fi equipment and are indispensable to maximum enjoyment of hi-fi listening. They may be found on any of three types of components, representative examples of which are shown here. At upper left is the Harman-Kardon "Recital II," a combined tuner-preamp-amplifier; all controls are found on one chassis in this type of unit. At lower left is the McIntosh "Professional Audio Compensator;" this "front end" unit contains preamplifier and equalizer circuits as well as the most versatile control facilities for operating them—it must be used with a separate power amplifier. At lower right is the Rauland Model 1512 "Golden Chief" 12-watt amplifier; an "all-in-one" or "single-chassis" type amplifier, it combines power amplifier with built-in preamp.





... Given a pair of such controls, the listener becomes a virtual conductor of his own orchestra ...

console radios consisted generally of a simple treble-cut adjustment, shown in the first of the four schematic diagrams on page 55.

Turning the control knob of such a circuit may give the illusion of scaling from the depths of bass to the heights of treble, but to the ear trained to appreciate live music or initiated in the wide range afforded by hi-fi reproduction, such a "tone control" is practically worthless. At its best, it provides a limited kind of treble attenuation—and absolutely no bass boost. Used originally in radio receivers that were decidedly "un-hi-fi," its action was inherently limited to the relatively thin audio produced by such sets. Cutting the highs is not a real way of getting better bass.

Nevertheless, such a control could often be used to bring into balance the over-all audio spectrum. This balance, often disregarded in the broadcast studio and completely unstandardized in the record industry until recent years, had to be achieved somehow in the home listening situation. Then, too, up to the advent of hi-fi, a great many people preferred so-called "mellow music."

Muted trombones and alto saxophones seemed to have had the most say in pre-war popular music. And in "classical" music, cellos whose overtones were clipped off and tympani with an anonymous thud but no "bite" filled the air in the homes of serious music lovers. An entire generation was weaned on this kind of listening, whose "hangover" effect is still evident in

the opinion expressed now and then by newcomers to hi-fi that "it sounds too shrill." As a matter of fact, discounting those who had the opportunity to attend live concerts, relatively few "music lovers"—even those with extensive record collections—ever really knew what a live violin sounded like before the advent of hi-fi.

In such a reproducing and listening context, the simple treble-cut control had a justifiable, if not spectacular, role. There is still valid reason for its use in low-priced AM receivers and in applications where voice communication is the main thing. Despite recent advances in AM broadcasting, this type of transmission is still subject to static interference, especially in remote areas and during electrical storms. Most of the static heard is contained in the high-frequency portion of the audible spectrum. Since AM broadcasting is generally limited to a tonal range well below 10,000 cycles, it would seem pointless to run a sound system "wide-open" only to allow annoying noise and static to get through with no particular improvement in program content.

A second justification for treble cut lies in the fact that tastes in living room decor differ considerably. A relatively bare-walled, hard-floored "live" room seems to have more treble bouncing around than does a thickly carpeted, heavily draped room. In the former, the treble tones may sound too exaggerated despite the fact that the electronic system itself has perfectly flat response. In such a situation, cutting the treble by means of a convenient control would certainly be apropos. Circuit (A) shown on the next page might do the trick very nicely.

Why Bass Boost? FM broadcasting and LP records and the better equipment to go along with these recent program sources have brought the highs into the living room—sometimes with a vengeance. Usually, a hi-fi enthusiast passes through two initial stages upon being exposed to the new medium. First, he may be impressed by the presence of high frequencies in the reproduced sound. Violins, flutes, piccolos and brass choirs take on a new crispness and clarity of tone. Certain notes, like those struck on the triangle, may be heard for the first time. Everything is articulated more clearly and distinctly. The highs have been discovered!

Some time later, the listener reaches a more advanced state of aural sophistication in which he realizes that something is wrong—the bass tones aren't all there! After checking all the components of the system and re-reading their specifications, the listener concludes that either the components manufacturers are making overly

extravagant claims or that he, the listener, isn't hearing right.


In this case, the latter conclusion happens to be true. He *isn't* hearing right! It's a fact that human hearing does not respond uniformly to all tones at all levels. To put it another way: if you listen to a live concert, your ears respond in a certain manner to all the sound heard. If you play a recording of that concert in your living room at reduced volume, the low tones will seem to be reduced *more* than the middle and high frequency tones.

To restore the music to its relative tonal balance, some form of compensation must be used. A very simple type of "bass boost" control for this purpose is shown in the schematic (B) at the right. At high settings of the volume control (where we are closer to the original "loudness level" of the live sound), the circuit provides no bass boost action. As the volume control is lowered, the circuit may be used to increase the level of bass tones.


Knobs and More Knobs. Often, in listening situations, tone control may be required which has the opposite effect of that just discussed. We might need a means of reducing bass and boosting treble. Bass attenuation may be desirable, for example, in a multiple speaker system in which the woofer is more efficient than the other elements of the system. Treble boost, on the other hand, might be needed to some degree because at the extreme high end of the audible spectrum human hearing undergoes somewhat the same deterioration that is experienced with low frequencies at subdued listening levels (though to a lesser degree as a rule). Treble boost might also be required to add highs for tonal balance in a relatively "dead" room. This, of course, is largely a

(Continued on page 126)


Schematics of the basic types of tone control circuits in use today are shown at right. Many feel that types (A) and (B) are not versatile enough to be labeled as "hi-fi." Types (C) and (D), however, provide the required range and flexibility of adjustment expected in good audio equipment. Type (C) has been used very widely in modern equipment, although it is gradually being superseded by the Baxandall circuit shown in (D). A study of the wiring schematic of a particular preamplifier (or tuner, if it contains a built-in preamp) will help you identify the type of tone control circuit used in that component. Such identification can tell you just what you have in your present preamp and also serve as a guide to future purchases. Explanations of how these circuits operate are included in the text; for a comparison of the ranges of control available in types (C) and (D), see graphs on page 126.

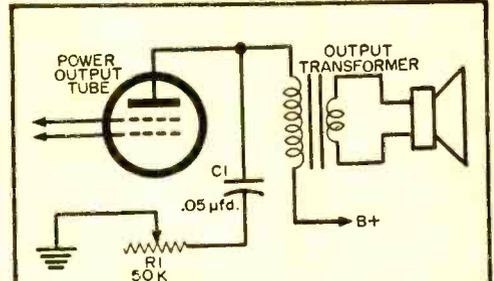


(A) Simple treble attenuation circuit.

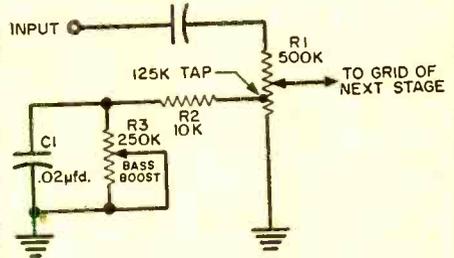

(B) Simple type of bass boost circuit.

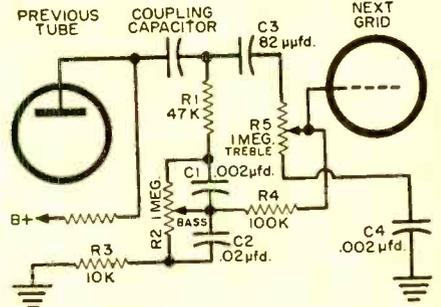

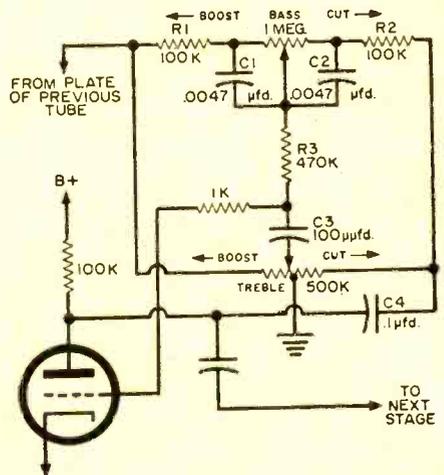(C) Popular type of treble and bass controls.



(D) Feedback tone controls (Baxandall system).

Capacitor Duo-Decades for the Experimenter


THE DIGITS "1," "2," "4," "5," and "8" can be added in various combinations to obtain all sums from 1 to 20 inclusive. For instance, the sum of 8, 5, 4, 2 and 1 is 20, and the sum of 8, 2 and 1 is 11. The author has adapted this interesting fact to the making of miniature capacitor duo-decades. (See table at right for a set of such digit combinations.)

A single duo-decade requires only five fixed capacitors and five s.p.s.t. toggle switches. The unit shown in the photos contains one each of 0.001-, 0.002-, 0.004-, 0.005- and 0.008- μ fd. (actually 0.0082- μ fd.) 5% tolerance, silver-mica capacitors. It covers the range from the 0.001 μ fd. to 0.02 μ fd. in 20 steps of 0.001 μ fd.


Other duo-decades may be made starting at 0.0001 μ fd. and 0.01 μ fd. Three such miniature units would use only 15 capacitors altogether, yet they would cover the entire range from 100 μ fd. to 200,000 μ fd. (0.0001 μ fd. to 0.2 μ fd.) and provide some 2000 different values of capacitance!

Accuracy of each duo-decade depends upon the accuracy of the capacitors used in it. Since only five capacitors are required per unit, a high order of accuracy can be obtained at reasonable cost. Most experimenters will find that an accuracy of 5% is sufficient for a large majority of applications.

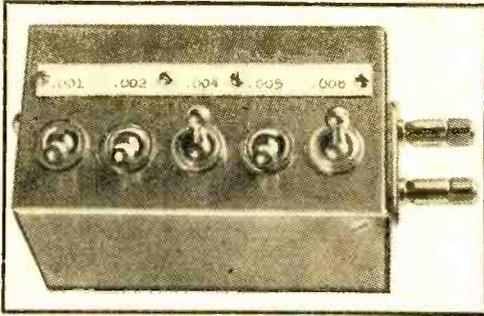Construction. The duo-decade is built in an LMB Type EL422 flangelock chassis box measuring 2 1/4" x 2 1/4" x 4". All switches, capacitors, and the terminal posts



Number:	Sum of:	Number:	Sum of:
1	1	11	8,2,1
2	2	12	8,4
3	2,1	13	8,5
4	4	14	8,5,1
5	5	15	8,5,2
6	4,2	16	8,5,2,1
7	5,2	17	8,5,4
8	8	18	8,5,4,1
9	5,4	19	8,5,4,2
10	8,2	20	8,5,4,2,1

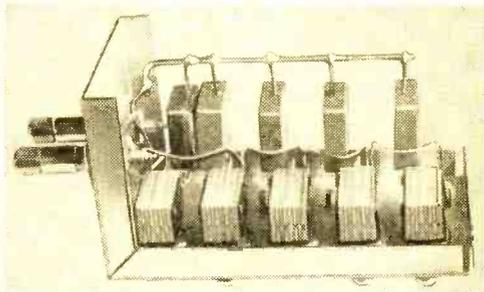


are mounted on the L-section of the box. The mating section merely serves as a protective cover and shield.

Make a label for the switches, bearing the values of the five capacitors contained in the box, out of a strip of thin, white card stock, using hand-lettering or a typewriter. This label is attached to the top of the box with four 4-40 screws.

Solder a length of No. 20 bare, tinned, copper wire to one lug of each of the five switches and then to the solder lug under one of the two terminal posts. Then solder a short length of heavy busbar wire to the lug under the other terminal post. This heavy wire runs almost to the end of the box. One wire lead of each of the capacitors is looped once around and soldered to the busbar, and the other lead of each capacitor is soldered to the second terminal on its own respective toggle switch.

—Frank H. Tooker

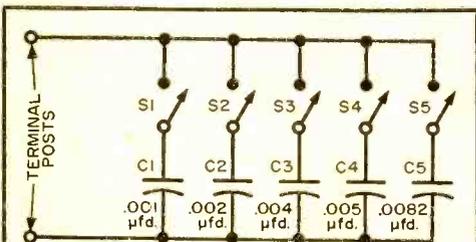

- C1—0.001- μ fd. silver mica capacitor
- C2—0.002- μ fd. silver mica capacitor
- C3—0.004- μ fd. silver mica capacitor
- C4—0.005- μ fd. silver mica capacitor
- C5—0.0082- μ fd. silver mica capacitor
- S1, S2, S3, S4, S5—S.p.s.t. toggle switches
- 1—2 1/4" x 2 1/4" x 4" aluminum box (LMB No. EL422 or equal)

1—Binding post terminal strip (National FWH or equal)

1—Length of No. 20 bare, tinned, copper wire

1—Short length of heavy busbar wire

Note: C1, C2, C3, C4, C5 may have other values in companion duo-decades. See text for details.

Diagram and parts list for a single duo-decade.

Transistor Topics

By LOU GARNER

NOVEMBER should be an exciting month, what with a presidential election and the Thanksgiving and Christmas holidays not too far away. Exciting things are happening in the electronics field, too . . . most of the mail order parts distributors have released their new catalogs, color TV is booming, and, in our "pet" field, there are new types of transistors, transistor components, and transistorized equipment. If you haven't visited your new car dealers yet, don't forget to "give a listen" to the recently developed *hybrid* (tube and transistor) auto receivers.

I don't honestly know whether the average reader of this column is an old-timer or a youngster as far as transistors are concerned . . . but I rather feel that many of you are "new-comers." As an old-timer myself, I'd like to reminisce a little . . . back to about the beginning of 1953. There was great news then . . . Raytheon had just introduced a new *low-cost* transistor, a *p-n-p* junction triode selling for the "give-away" price of merely \$7.50 . . . Type number CK722! And it was a real bargain at that price, for, prior to the release of the CK722, the *cheapest* transistor sold for about \$18.00, with many types selling for \$50.00 to \$100.00.

There were relatively few miniature components available in those days, and it was not unusual for an enthusiastic experimenter to assemble a two-transistor "pocket" radio which could barely be squeezed into an overcoat pocket. Few construction projects required more than


two transistors . . . the vast majority used only one!

But, as the expression goes, "time marches on" . . . and things change. Today, relatively few transistors sell for more than \$5.00, and two popular experimenter types sell for less than one buck! Raytheon's famous CK722 and G.E.'s popular 2N107 both *net* for only 99 cents. And there are a couple of r.f. transistors available for less than \$2.00 . . . Raytheon's CK768, a *p-n-p* unit selling for \$1.50, and G.E.'s *n-p-n* 2N170 which nets for \$1.45. At these prices, most experimenters don't hesitate to tackle four to six transistor projects at a time.

Looking to the future, your columnist fully expects to see the day when transistors sell for appreciably less than that other amplifying device . . . *you know what!*

Reader's Circuit. The old mail box informs us that radio receiver projects are by far the most popular with home builders and experimenters. Because of this, we have featured simple receiver circuits for the past few months. But we know there are many transistor experimenters who are interested in other applications . . . audio circuits, ham work, test gear, etc. So this month we are departing from usual custom and including a circuit for a "transistorized keying monitor"—a gadget every ham and c.w. operator should find interesting.

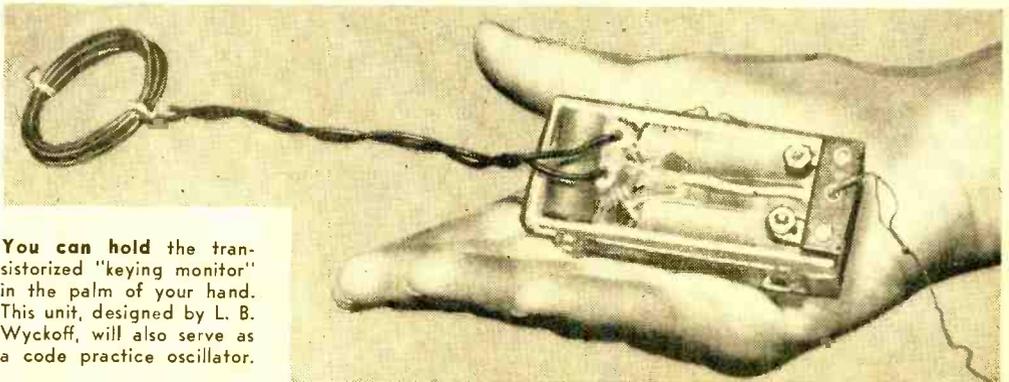Basically, a keying monitor is intended to permit a radiotelegraph operator to hear




You can hold the transistorized "keying monitor" in the palm of your hand. This unit, designed by L. B. Wyckoff, will also serve as a code practice oscillator.

himself "on the air." Hearing his own transmissions enables the operator to send cleaner, better code, and this, in turn, helps the fellow at the other end who has to copy the signals. L. B. Wyckoff submitted the circuit shown, and assembled the model illustrated.

Referring to the schematic diagram, a single CK722 *p-n-p* transistor is connected in a modified "Colpitts-type" audio oscillator. Frequency of operation is established by a tuned circuit made up of the earphone's inductance and capacitors *C1* and *C2*, in series. The ratio of these two capacitors determines the amount of feedback supplied to initiate and sustain oscillation. Operating power is supplied partially by a small penlite cell and partially by rectified r.f. energy, picked up by loop *L1*, rectified by the crystal diode, and filtered by *C3*. According to Wyckoff, the battery's current drain is so small that its useful operating life approximates its normal shelf life; hence no "on-off" switch is needed.

Construction is simple and straightforward, with neither layout nor lead dress critical. Wyckoff assembled the model pictured in a plastic box measuring 2½" x 1" x ¾". Capacitors *C1*, *C2* and *C3* may be either paper or ceramic units; *R1* is a half-watt carbon resistor; almost any crystal diode may be used . . . the CK705 or 1N34A will probably be the choice of most builders. The pickup coil, *L1*, consists of approximately five turns of hookup wire, wound in a 2"-diameter loop and secured with string or lacing twine . . . you can use Scotch tape for this job if you wish. A high-impedance (5000-ohm) *dynamic* ear-

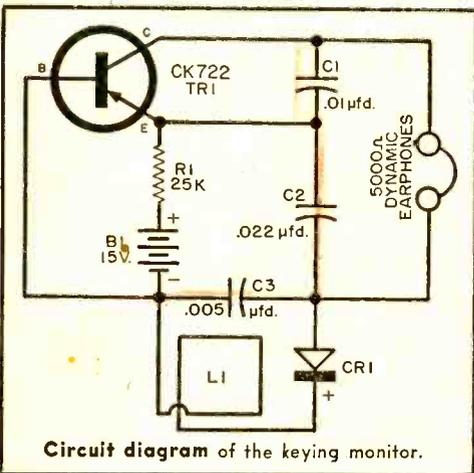

phone should be used . . . crystal earphones will *not* work in this circuit.

The completed gadget may be used as either a *code practice oscillator* or a *key-*

ing monitor. To use it as an oscillator, replace *L1* with another penlite cell, connected in series with your hand key, and with the negative terminal on the "diode" side. To use it as a monitor, place the pickup coil, *L1*, near the tank coil of your transmitter. Exact placement is not too critical, but will vary with the size of your rig. With low- and medium-powered rigs, the pickup coil may have to be within a few inches of the "tank" . . . with higher power rigs, it may be placed several inches—or even a foot or more—away.

Tickler File. Again, we "tickle" your memories about items mentioned in previous columns

. . . items we feel to be of special interest to you:

(1) *Sylvania's* new transistor kit (six transistors and a crystal diode) can be obtained from your regular distributor.

(2) *Lafayette's* new transistor checker kit . . . write to Lafayette Radio, 100 Sixth Ave., New

Lafayette's new transistor checker available in kit form.

York 13, N. Y., for price data and specifications.

(3) *G.E.'s* new *tetrode* transistor . . . there is no price data yet, but units will be available for operation up to 120 megacycles!

Hot News! We always devote space to tips about new products, but this month we have some news which we feel deserves special mention . . . *CBS-Hytron* has announced two new *power* transistors, designed and priced especially for experimenters. These two units, capable of outputs in the watts, should be available from your local distributor before too long. Type numbers are 2N256 and 2N257, for the 15-volt and 30-volt units, respectively. Selling price will be around \$2.50 to \$3.50, according to present plans. At these prices, the 2N256 and 2N257 will sell for *less than half* as much as other "high power" transistors, representing a major price break.

Product News. In addition to the "red hot" news tip mentioned above, we have quite a few items from other manufacturers and suppliers.

(Continued on page 118)



Transtopic

Experiment No.

12

Electronic Timer

THIS is another experiment in the series that started in the March, 1956 issue. The last experiment, No. 11, appeared on page 63 of the October issue.

Wiring hints and parts lists were included in the March issue. Further information on the components and chassis may also be found in that issue. This is Project No. 12 and concerns the construction of a simple electronic timer.

When the timer is assembled according to the circuit shown in the wiring schematic, it may be used for a variety of applications. If you're a photographic fan, you can control your enlarger or printing box with it. In chemistry, it might be used to control a small heater or an electric stirrer. The only precautions you need observe in assembling the unit are to double-check the polarities of the battery and electrolytic capacitor, *C7*, and to make sure a good-quality electrolytic capacitor is employed.

With the wiring completed, the relay should pull in and should hold in for a short period of time, finally dropping out. Afterwards, closing the "RESET" switch (hand key) and releasing it should cause the relay to pull in again, and to hold in for a period of time determined by the setting of *R1*, again finally dropping out. The relay's "OUTPUT TERMINALS" are used as a simple switch to control the circuit being timed.



Timing range depends on the adjustment of the relay, the setting of *R1*, and on the size of capacitor *C7*. A 25- μ f. capacitor provides a range of from approximately 1 to 3 seconds to a maximum of from 5 to 12 seconds. If this capacitor is a 100- μ f. unit, the minimum will be 5-8 seconds, the maximum 25-45 seconds.

When the power switch *S1* is first closed, there is a rush of current through the *R1-R4* parallel combination, through *R3* and through the base-emitter circuit of *TR1*, charging *C7*. This flow of base-emitter current closes *RL1*. The relay then holds closed as long as sufficient collector current flows.


As *C7* is charged, the current flow in this circuit gradually drops. Since collector current also drops, *RL1* drops out. The time required to charge *C7* depends on the *RC* time constant of the circuit. Closing the "RESET" switch discharges the capacitor, permitting the timing cycle to be repeated.

For a given transistor, and assuming *C7* to be fixed, the minimum timing period is determined by *R3*, whose value is chosen to keep the base-emitter current within a safe value as *C7* is shorted by the "RESET" switch. The maximum timing period is determined by the total resistance in the circuit.

—Louis E. Garner, Jr.

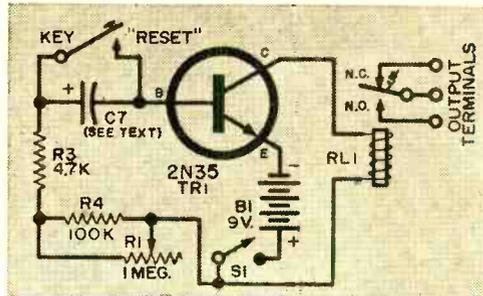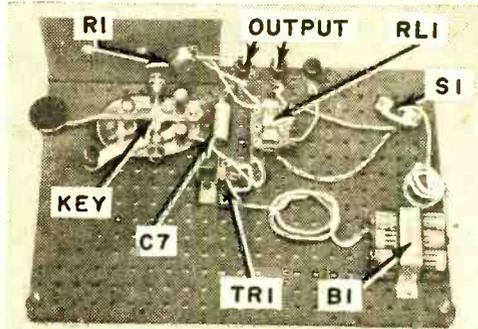

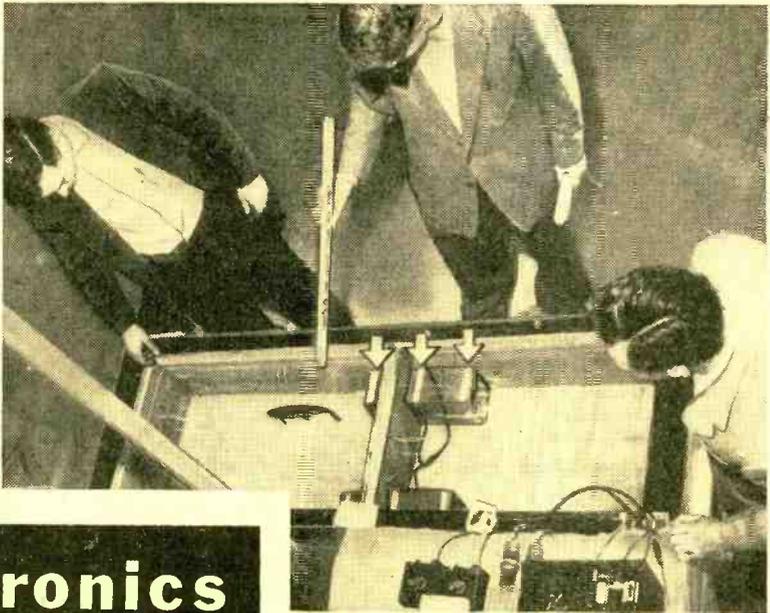Number of fish, size, and direction of travel are determined by electronic counter. In display model (right), trout in tank has just passed through tunnel, has been detected. The detector circuit can operate a camera which will photograph fish so as to identify species. Below, right, a technician tests the firing mechanism of the counter.



Above photo, "The Gregonian," by Rollie Dobson
All others, Fish and Wildlife Service


Electronics on the Fishways

By MARGARET MAGNA

ELECTRIC FENCES protect spawning salmon from Kodiak bears! Fish take their own pictures by means of electronic counters! Sonic trackers chart reactions to various types of fishways! Electrical weirs jolt life out of sea lampreys! And underwater telemeters indicate net depths for "mid-water" trawling!

All of these devices—and many others—are being utilized by the Fish and Wildlife Service, U. S. Department of the Interior, in fishery research and management. Electrical screens protect fish at power-plant intakes. Shockers temporarily "knock them out" to determine population figures. Fish are spotted for harvesting with special finders developed by electronic specialists. With the help of underwater TV, biologists determine methods of saving small fish from destruction. In other words, electronics is playing an increasingly active role on the fishways—the watery roads on which fish travel.

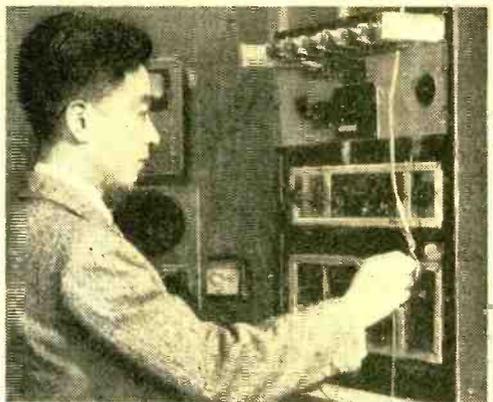Fish Count Themselves. Created by the Fish and Wildlife Service, the electronic counter is fully automatic. It counts



the fish and indicates their size and direction of travel. Through the medium of an underwater camera, it can also identify the species; in effect, enabling the fish to photograph themselves.

The basic element of the counter is a detector which, utilizing the difference in conductivity between fish and water, passes a signal when a fish is between its electrodes. This signal may be used to trip an electric tally, flash a light, ring a bell, etc. Arrangement of the electrodes in tunnels determines the minimum size of fish that can be counted.

Signals from two detectors can be used to actuate a logic device, which indicates the number of completed upstream and downstream passages on separate dials. It rejects all passages that are incomplete. The output of the logic device will also


operate automatic devices when a predetermined number of fish has passed, such as gates at hatchery holding ponds, thus preventing overcrowding.

Tunnels can be made of transparent, opaque or pigmented materials. Or detectors may be used with troughs, weirs, posts in stream beds, etc., if tunnels are not desirable. The system will work at any depth and in murky water, where visual observation is impossible.

At present, the chief value of the electronic fish counter is in testing effectiveness of the fishways and registering the number of salmon heading for spawning grounds. Continuance of a salmon fishery depends to a great extent upon whether or not a sufficient number of adult fish reach the spawning areas. A fish counting laboratory is now in operation at Ballard



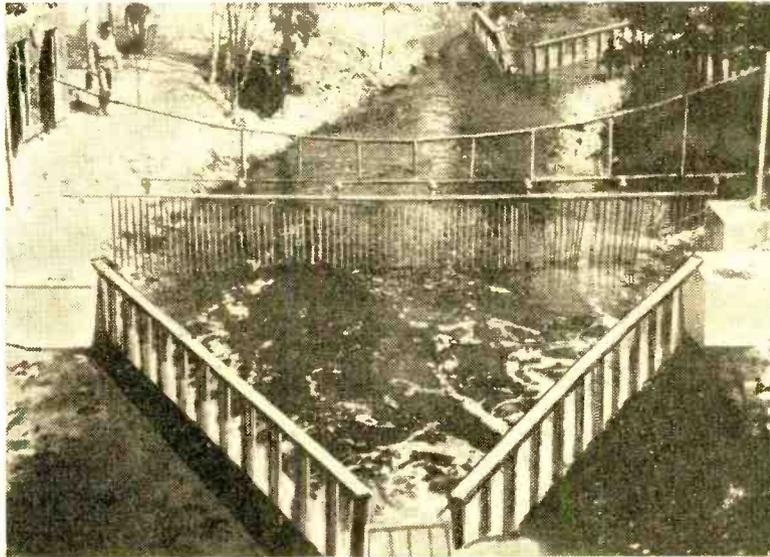Underwater TV housing being mounted on sled (above) prior to use at Coral Gables, Fla. The camera within the housing scrutinizes fishing gear while it is in operation.



Electrical weir at Carp Creek, Mich. (left) is located between two mechanical weirs used in checking the effectiveness of this barrier. Lampreys, which prey on smaller fish, are killed by its charged electrodes as they attempt to pass through on their way to spawning grounds.

Locks, near Seattle, Wash., and indications are that this device, when fully developed, will be used in many parts of the country where fish runs are important.

Sonic Tracker. A capsule about two-and-a-half inches long and less than one inch in diameter, the sonic tracker is fastened to the back of a salmon just to the rear of the dorsal fin. It contains a 15-volt battery and small transmitting apparatus capable of sending signals for 10 to 100 hours. This "tattle-tale" electronic device will flash every twist and turn of the fish to a recording instrument on land or in a boat.

Under ideal conditions, the signals from the tracker may be detected as far away as 2000 feet. A fish carrying the capsule can be tracked and its position pinpointed for about 800 feet in clear, still water, and for about 100 feet in rough, turbulent

streams. Movements of as many as ten fish can be traced simultaneously using transmitters with different frequencies.

Initial studies of the sonic tracker—one of the newest of the electronic devices—are being made at Bonneville Dam on the Columbia River. By investigating the passage of salmon through several types of fishways, technicians hope to be able to determine the most effective fish ladder design. Although the tracker is being applied particularly to salmon studies, it can be used on other species as well.

Telemetry and TV. The underwater telemeter will indicate the exact distance of a trawl or net below the surface of the water. As a means of discovering the fishery values of the mid-water ocean area, it is expected to increase the efficiency of commercial fishing considerably. Compar-



Fish are shocked into temporary unconsciousness by biologists in West Gallatin River, Montana. The men at left and right hold insulated handles to probes that pass shocking current through stream.

atively little mid-water fishing has been done by American fishermen, who have heretofore concentrated on surface and bottom fishing.

Underwater television tells the Fish and Wildlife Service more about fish in their regular habitat and more about what can be done to make fishing gear efficient and effective. The Service has two such units: one at the Gear Research Laboratory at Coral Gables, Florida, where a camera scrutinizes gear while it is actually in operation; the other at the Fishery Laboratory at Woods Hole, Mass.


At Woods Hole, biologists are more concerned with the effect of fishing gear on fish which are too small for market, rather than with efficiency of commercial gear. Looking for methods of saving such fish from destruction, they are studying the sizes of fish which can escape through the trawl meshes, and the manner of escape, as well as behavior within the net. These biologists are also making various studies

of the ocean bottom and the small marine animals which inhabit the bottom and serve as fish food.

Electrical Weirs. Since the power turbine and some of the big irrigation diversions offer a major threat to young fish, considerable research is being done on mechanical and electrical methods of meeting this problem. Numerous screening techniques have been tried. In small experimental streams, such devices have been about 95% successful in guiding the fish into the desired places. Testing is now being done on large streams. Two methods have been used, one based on the fact that fish are attracted to the positive pole, the other based on the principle of repulsion by an electrical field.

The sea lamprey weir is an electrical barrier placed across a stream used by the lamprey for spawning. Its charged electrodes kill any sea lampreys attempting to pass through. Such weirs are installed in tributary streams of the Great Lakes. The sea lamprey, which entered the upper Great Lakes about 20 years ago, destroyed the lake trout fishery of Lake Michigan and Lake Huron, and has now appeared in Lake Superior. Its control is a major objective of the Fish and Wildlife Service at the present time.

For about three years, the electric fence has successfully kept the big Kodiak bears away from critical sections of salmon streams. The electric shocker, which has also been utilized for some time in making fish population studies, is now effective in soft water, thereby extending the range of its usefulness. By and large, it might be said that the role of electronics on the fishways is to protect fish from harm until such time as they become useful to man, at which point it abdicates in favor of the electric stove.

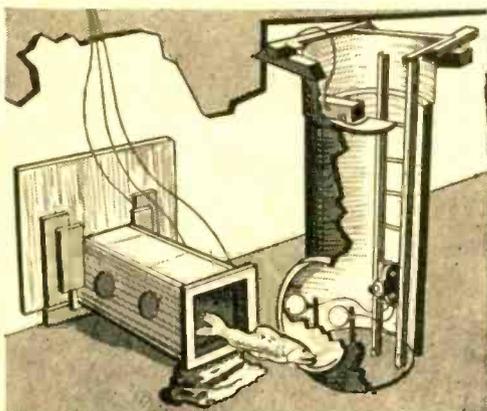

Pictorial drawing shows the photographic fish counting setup at Ballard Locks, Seattle, Wash.

The "Economy" Signal Chaser

By RICHARD GRAHAM



**Track down
trouble in your
receiver or amplifier
with this inexpensive device**

Touching probe to grid or plate will send out signal from 60 cycles to 10 mc. Housed in aluminum box, actual chassis is a bracket made of scrap aluminum. Major components are identified in open-chassis view shown below.


HOW TO DIAGNOSE a receiver failure is a problem that is practically as old as radio itself. Yet to the novice in the radio game, the problem is as acute as ever, for it often means many hours of head-scratching and experimenting before the trouble is found. For some, this state of affairs is due to the lack of proper test equipment to help point the way.


Somehow, the term "test equipment" conjures up visions of an elaborate test-bench loaded with scopes, meters, signal generators, etc. All of these items are valuable aids to successful servicing although basically they can do no more than the simple device described in this article to help you find what happened to the signal.

The device is called a "Signal Chaser" because it sends out a modulated signal over the entire audio and radio spectrum from 60 cycles to over 10 megacycles. It can be used for tracking down component and stage failures in audio amplifiers, pre-amplifiers, and speakers, as well as in any r.f. or i.f. stage of a radio receiver.

Simple to construct, the Signal Chaser uses only one tube, requires no d.c. power supply, and does not need alignment or adjustment to be put into operation. It is housed in a 2" x 4" x 1½" aluminum box.

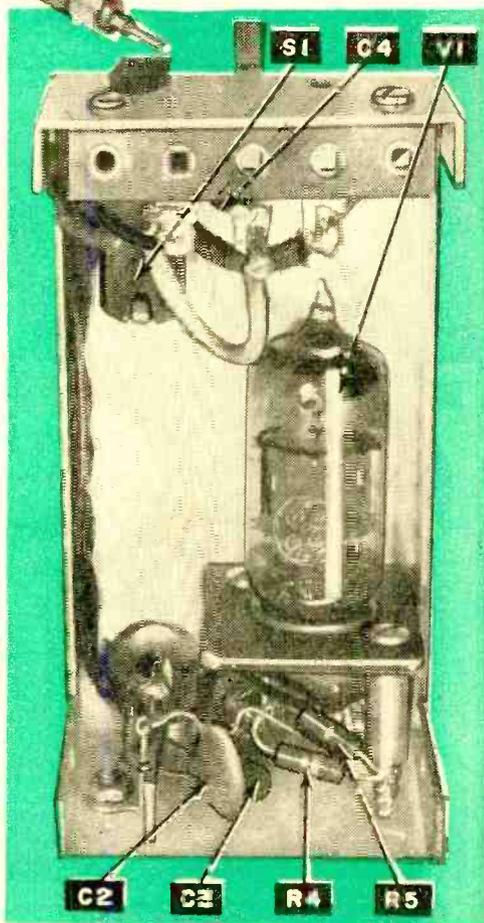
The actual chassis is a bracket formed from a 2" x 1¼" piece of scrap aluminum. A ½-inch lip is bent up on the two-inch



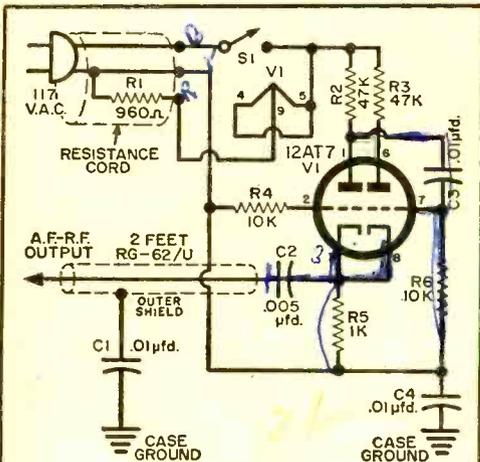

- C1, C3, C4—0.01- μ d., 600-volt disc ceramic capacitor
 C2—0.005- μ d., 600-volt disc ceramic capacitor
 R1—960-ohm resistance line cord
 R2, R3—47,000-ohm, $\frac{1}{2}$ -watt resistor
 R4, R6—10,000-ohm, $\frac{1}{2}$ -watt resistor
 R5—1000-ohm, $\frac{1}{2}$ -watt resistor
 S1—S.p.s.t. toggle switch
 V1—12AT7 tube

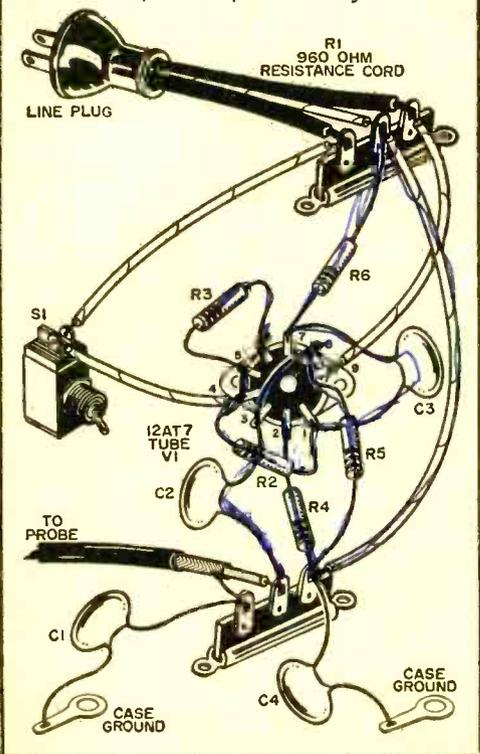
Diagrams and parts list for the "Economy" Signal Chaser. It is important that the output leads of the resistance line cord, which provides the filament voltage, be connected as shown in the schematic diagram above so that the filament will light and the tube will not burn out. You can see how the various parts are hooked up in the pictorial diagram below.



HOW IT WORKS

This circuit is basically a free-running cathode-coupled multivibrator with 60-cycle a.c. voltage applied to the plates. The multivibrator will operate only when the plate supply is positive with respect to the cathode. Frequency of the multivibrator is approximately 1000 cycles; however, it can be varied by the amplitude of the applied a.c. plate voltage (reduce or increase values of R2 and R3).

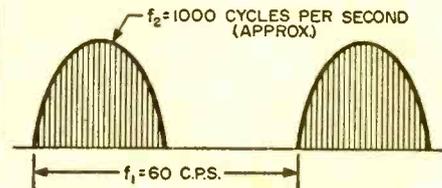Multivibrator output is interrupted at the power line frequency of 60 times per second. The resultant waveform has fundamental frequencies of 60 and 1000 cycles, both of which are extremely rich in harmonics. The 60-cycle modulation of the 1000-



cycle fundamental results in a signal every 60 cycles from 60 cycles to over 10 megacycles.

The output is taken from the common cathodes of the twin triode. Coupling and/or a.c. isolation are provided by capacitors C1, C3, and C4. A good grade of coaxial cable is necessary since the capacity of the cable will determine the output at the higher radio frequencies.

dimension. The 9-pin socket and two small stand-off insulators are mounted on this chassis, which can be assembled and wired before it is mounted permanently in the aluminum box.

Output from the Signal Chaser is fed through a capacitor (C2) and a 2' length of RG-62/U coaxial cable. If RG-62/U cable is not available, the second-best choice is RG-59/U. The cable ends in a standard meter test probe. Only the inner conductor of the coaxial cable is connected to the probe test point. The outer braid shield should extend down the probe handle to within approximately one-half inch of the tip. Details of the probe construction are clearly illustrated at the top of the following page.


In the interest of simplicity, the Signal Chaser is operated directly from the 117-volt a.c. power line. Therefore, it is necessary to isolate the output coaxial cable lead and the aluminum case of the Signal Chaser from the power line. This precaution must be taken to eliminate a dangerous shock hazard, particularly if the Signal Chaser is to be used to service a.c./d.c. sets where the chassis is commonly connected to one side of the power line. For this reason, the coaxial shield is connected to the case through 0.01- μ d. capacitor C3, and one side of the line is connected to the case through capacitor C4.

A resistance line cord is used to provide the filament voltage for the 12AT7. This type of line cord has three output leads on

the end. Make sure that the wires are connected as shown in the diagram. Otherwise, either the filament won't light or the tube will be burned out. An ohmmeter will help sort these wires if they are not coded clearly.

The basic procedure when using the Signal Chaser is to follow the signal path through the receiver in reverse. For example, in the typical receiver, the Signal Chaser probe can be placed on the grid of the audio output stage. If all is functioning correctly, a loud buzzing sound will be heard from the speaker. The probe can be placed on the plate and then the grid of the first audio stage in the receiver. If the loud buzzing sound is heard, all is well, and the probe can be placed on the grids, plates, and diode of the preceding detector, i.f., and r.f. stages.

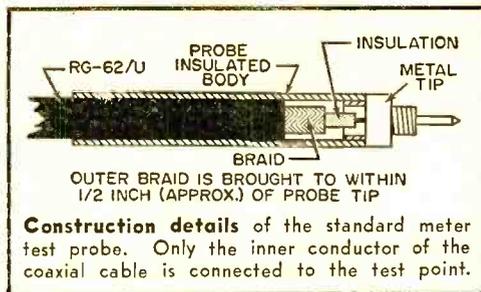Continue this procedure until the point is found where the loud buzzing sound cannot be heard. This, then, is the point




at which the signal path is broken. A closer visual inspection and perhaps a few measurements with a voltmeter will most likely enable you to locate the specific difficulty.

This method of servicing radio and audio equipment is known as the signal substitution method and is described in detail in many books on radio-TV servicing techniques.

-50-

Storing Small Components in the Workshop

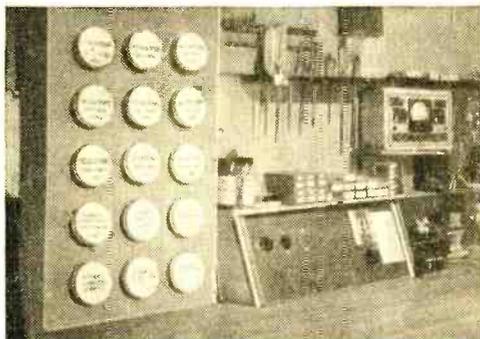STORING of parts and accessories is a major problem in the home workshop. Most electronic parts are small and delicate, requiring separation and protection



from breakage. Small glass jars are readily available, and are ideal for storage purposes—but how and where should you store them? Illustrated here is one of the most satisfactory methods yet developed.

Construction is self-explanatory, and the dimensions are tailored to suit the number and size of jars to be used. The holes can be cut with a carpenter's expansion bit and should be just large enough to let the jar slope slightly backwards when inserted. The jars are supported at the back of the board by strips cut to size from $\frac{1}{2}$ " x 1" molding, available in all lumber yards for a few cents a foot.

An additional bonus afforded by this system is that the contents of each jar can be printed directly on the cover for easy identification.

—Robert B. Kuehn

Handy Connections for Ferrite-Rod Loop Antennas


WHEN EXPERIMENTING with ferrite-rod transistor loop antennas, such as the Miller #2000 shown in the photo, it isn't very hard to break off the pigtail leads. Experimenters can avoid this danger by mounting three small Fahnestock clips on the insulating strip base, and soldering the pigtail leads directly to the small lugs on the clips.

Drill three $\frac{1}{16}$ "-diameter holes in the strip at the approximate positions shown in the photo, and mount three #15 Fahnestock clips using $\frac{1}{16}$ "-diameter round-head machine screws $\frac{1}{4}$ " long with hexagon nuts to fit. After mounting the clips, snip off the excess ends on the screws so they won't interfere with the levers on the clips. Do

not snip off the excess wire on the pigtail leads, but coil them up and then solder the tinned ends into the eyes of the small lugs on the clips.

Now you can experiment to your heart's content without danger of breaking off the wire leads.


—Art Trauffer

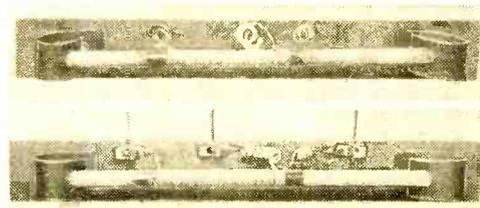

AN OFTEN UNTAPPED source of radio signals for code practice lies in what is known as the long-wave region above the broadcast band. This is a sort of "never-never land" where few experimenters ever tune. Perhaps it is because this area has no voice signals but instead is populated only with c.w. and m.c.w. signals that it has so little interest for the average person—but it's a gold mine for anyone who wants to learn the code.*

Receivers for use in this part of the radio spectrum are not too easy to find. Most, if not all, of those available in surplus are quite big, heavy contraptions with power requirements other than 117-volt, 60-cycle, a.c. If you're interested in tuning here, you are better off building your own converter or receiver. Elaborate, expensive equipment isn't at all essential, especially for code-practice purposes. Many long-wave stations use very high power, so even a simple, one-tube receiver—such as the "Long-Wave DX'er"—can do a good job.

Construction. Looking at the front-view photo of the receiver, the knob to the left of the tuning dial is the regeneration control. The one on the right varies R_4 , the volume control potentiometer. To the right of the volume control is the phone jack, $J1$, and to the right again, the power "on-off" switch $S1$. The tuning dial is of the vernier type for easy tuning. It is mounted on a small strip of sheet aluminum.

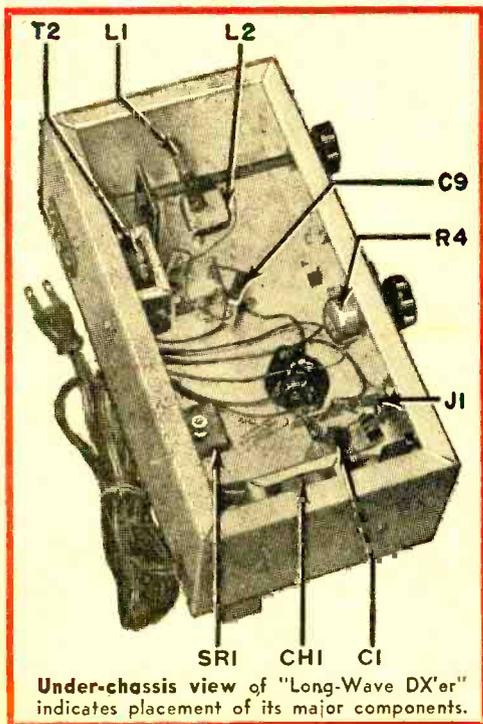

Under-chassis view of "Long-Wave DX'er" indicates placement of its major components.

Long-Wave DX'er a Single-Tube Receiver

The heart of any receiver is its "front end." In this particular receiver, it narrows down to the tuning capacitor gang, C_4/C_5 , and its coil, $L1$. A large maximum capacitance is necessary and is obtained by paralleling the two sections of a dual 420- μfd . variable capacitor.

Several different coils were tried at $L1$, but none were as sensitive as the Miller X-121-A specified in the parts list. Although this particular coil requires a fair amount of modification (as described below) before it can be used in the circuit, such modification is not difficult. The coil, as purchased, is enclosed in a $\frac{3}{4}$ " x $\frac{3}{4}$ " x 2" shield can. Since the can will not be used, it should be removed.

First, lift up the two little metal tabs on the underside of the shield. Straighten them up until they are flush with the sides of the can. Then, using a tiny screwdriver, pry out the little Bakelite terminal board and the coil. Do this carefully. Lift a little on one side, then another—working around the four sides of the Bakelite piece until it is free of the shield. The powdered iron core will remain in the can. Directions for removing it will be given shortly.

Study the lead arrangement on the coil. The lead nearest the terminal board is the ground point; slightly above it is a double lead that is the antenna tap. The lead furthest from the terminal board is the grid end of the coil. When you can recognize where these leads are to be connected just by looking at the coil, carefully unsolder the three leads from their solder lugs, drill out the eyelet in the center of the terminal

* A feature article on long-wave DX stations appeared in the October issue on page 51. This article described the stations that can be heard, the frequencies in use, and how DX stations may be verified.

By FRANK H. TOOKER

Want to learn c.w.? The long-wave region above the broadcast band is ideal for code practice, and the sensitive little receiver described in this article is simple to put together.


Co-er photo by Maynard Frank Wolfe

board, and remove the terminal board and the remains of the eyelet from the coil form. Remove 225 turns from the *grid end* of the coil, and snip off the wire about four inches from the coil form. Solder a 3" length of insulated wire to the antenna tap lead; then solder a 2" length of the same wire to the ground lead. Insulate these soldered connections and anchor them to the coil with small pieces of plastic insulating tape.

The powdered iron core is secured to the top of the shield can with an eyelet and a small nut. Remove the nut and file away the eyelet. Be careful not to damage the threads on the small projecting brass rod in the center, for these will be used with the nut to secure the core and the coil to the side of the chassis in your receiver. When the eyelet is filed away, a light tap on the end of the threaded rod will drop the core out of the can.

The tickler is a $\frac{3}{4}$ "-square coil. It consists of 25 turns of No. 28 enameled wire, and is made by scramble-winding the wire on the Miller shield can. Wind the coil over as narrow an area as possible. Slip it off the can and wrap the coil snugly with plastic insulating tape.

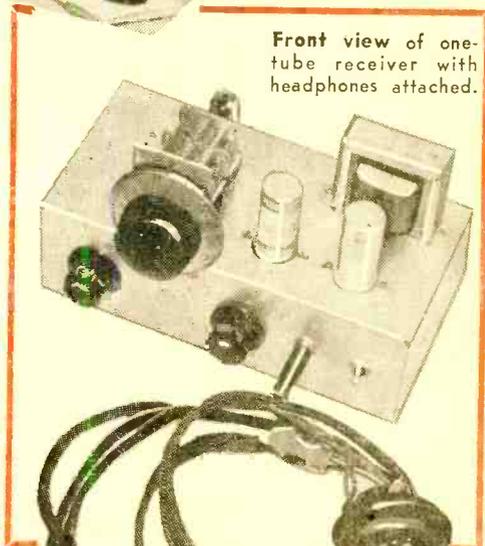
To make the tickler adjustable in the receiver, it is mounted against the side of a short length of $\frac{1}{4}$ "-diameter fiber rod. Prepare a place for the coil on the rod by filing a small flat on one side of the rod. Note that the tickler is located over the tuning coil. Spacing between the two coils is such that the tuning coil will be cen-



tered in the tickler when the latter is swung down over the tuning coil. You don't have to be especially precise about the coupling between the two coils.

Normal adjustment of the tickler has little, if any, effect on the tuning of the receiver. Mount the tickler coil on the rod by spreading a generous dab of polystyrene

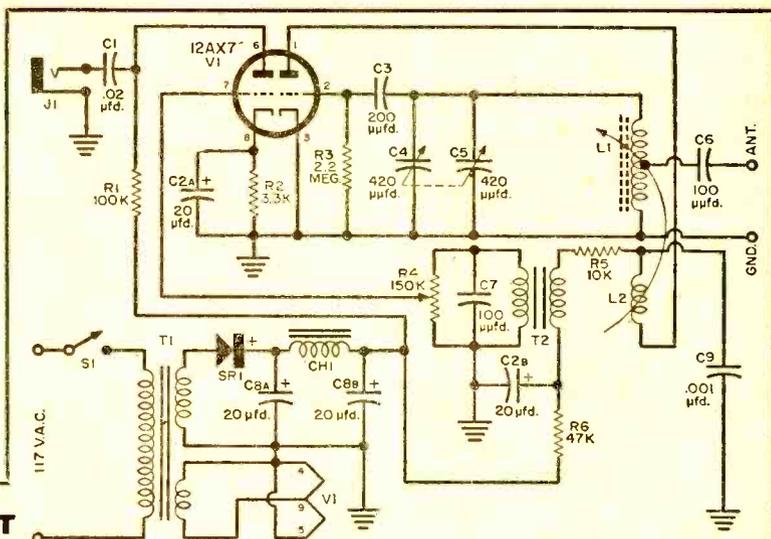Wire the "Long-Wave DX'er" as shown in schematic diagram at right. Complete details for modification of coil L1 are given in text. Components should be hooked up as illustrated in pictorial diagram at left.



PARTS LIST

- C1—0.02- μ fd. ceramic capacitor
 C2a/C2b—20/20 μ fd., 150-volt, can-type, dual electrolytic capacitor
 C3—200- μ fd. mica capacitor
 C4, C5—420/420 μ fd. dual variable capacitor
 C6, C7—100- μ fd. mica capacitor
 C8a/C8b—20/20 μ fd., 250-volt, can-type, dual electrolytic capacitor
 C9—0.001- μ fd. mica capacitor
 CH1—8.5-henry, 50-ma. filter choke
 J1—Open-circuit phone jack
 L1—Tuning coil (Miller Type X-121-A modified)—see text
 L2— $3\frac{1}{4}$ "-square tickler coil, 25 turns of No. 28 enameled wire (see text)
 R1—100,000-ohm, $\frac{1}{2}$ -watt composition resistor
 R2—3300-ohm, $\frac{1}{2}$ -watt composition resistor
 R3—2.2-megohm, $\frac{1}{2}$ -watt composition resistor
 R4—150,000-ohm volume control potentiometer
 R5—10,000-ohm, $\frac{1}{2}$ -watt composition resistor
 R6—47,000-ohm, 2-watt composition resistor
 S1—S.p.s.t. toggle switch
 SR1—65-ma., 130-volt selenium rectifier
 T1—Power transformer; 125 volts, $\frac{1}{2}$ -wave, at 50 ma.; 6.3 volts at 2 amperes (Stancor PA8421)—a smaller unit may be used here if desired
 T2—Single-plate to single-grid audio transformer, 3:1 step-up ratio
 V1—Type 12AX7 tube
 1—10" x 5" x 3" aluminum chassis

cement or plastic household cement along the flat. Then, hold one side of the coil against the flat and wrap a layer or two of plastic insulating tape snugly around this side of the coil and the rod.

The end of the tickler rod that is inside the chassis is supported by a strip of $\frac{1}{8}$ "-thick Bakelite. A $\frac{1}{4}$ "-diameter hole is drilled through one end of the strip at the appropriate height to accommodate the rod. The other end of the strip is secured to the underside of the chassis deck by means of a small L-bracket. Sufficient friction to make the rod (and the tickler coil) stay put in any position to which it is adjusted is obtained by passing the knob end of the rod through a $\frac{1}{4}$ "-i.d. rubber grommet.

Make a little spring in each of the two tickler leads by winding a couple of turns around the fiber rod on each side of the coil—and, when the leads are soldered into the circuit, leave enough slack so that the tickler can be rotated through 180°. In normal use of the receiver, the tickler adjustment will not be likely to require more than about 20° of rotation, so there is little danger of the leads fouling or break-

ing if the aforementioned procedure is followed. Mount the powdered iron core on the inside of the left panel of the chassis and slip the tuning coil, L1, over it *with the grid end of the coil toward the left panel of the chassis on which the core is mounted*. The tickler should be nearest the ground end of the tuning coil where it will have the least adverse capacitance coupling effect.

Mount the power transformer, T1, in the rear corner and the filter choke, CH1, below deck. Filter capacitor C8 is just in front of the power transformer, while rectifier SR1 is mounted on a long screw which also holds one end of the transformer.

Orient the tube socket so that the twisted heater leads will not have to cross or come near the detector grid lead. All ground leads in the power supply section go to the can solder lugs on filter capacitor C8; this capacitor is mounted on a metal plate. Audio transformer T2 is located below the tube socket on the rear panel of the chassis; mount this after the socket wiring is completed. A two-terminal strip

(Continued on page 112)

GARRARD SALES CORP.
80 Shore Rd.
Port Washington, N. Y.



Record changer, Model RC-88, is improved version of Garrard RC-80. Unit plays at three speeds automatically or manually, as desired. Motor is 4-pole, shaded induction type. Weighted turntable, 1" high, turns on ball bearings, and is covered with rubber mat. Wow and rumble are said to be negligible. Tone arm, made of aluminum, uses plug-in shell which accepts most pickups. Stylus pressure and pickup height adjustments are provided. Unit is supplied with two spindles; mounting base is extra.


LINTHROP MFG. CO.
433 West Fulton
Grand Rapids, Mich.



Two-way speaker system (8" woofer and 3 1/2" tweeter) is housed in compact attractive enclosure. The "Linthrop" speaker may be used as a reproducer in a modest hi-fi system, as an extension speaker for another room, or as an auxiliary speaker for stereophonic setups or to improve TV sound. Two leads connect unit to any amplifier. Net price, \$23.95.


what's new in hi-fi

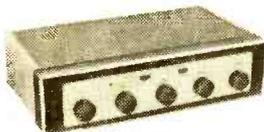HARMAN-KARDON, INC.
520 Main St.
Westbury, Long Island,
N. Y.



Forty-watt amplifier includes built-in preamp and full audio controls for hi-fi systems. Controls provide for program selection, equalization of tape and records, loudness, treble, bass, rumble filter, speaker damping, and speaker selection. The "Trend II" (Model A-1040) uses four 12AB5 tubes in a high-efficiency, low-power drain circuit. Net price, \$125.00.

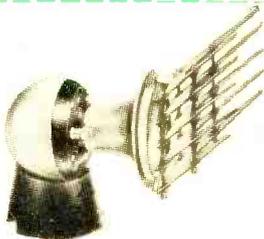LAFAYETTE RADIO
100 Sixth Ave.
New York 13, N. Y.




Tweeter (Lafayette "HW-7") features louvered "acoustic lens" for uniform dispersion of highs. Lens is detachable for panel mounting, and a separate base for mounting the tweeter externally is also available. The aluminum voice coil has an impedance of 16 ohms. Power rating is 25 watts. This tweeter is designed to take over at 2000 cycles. Net price, \$14.95.

HEATH COMPANY
Benton Harbor 5, Mich.



AM tuner (Heathkit Model BC-1) may be built from kit containing all parts and instructions. Designed for use in hi-fi systems, it provides broad bandwidth with good sensitivity and selectivity. Set features built-in power supply and cathode-follower output, uses five tubes. Net price of \$24.50 includes cabinet.

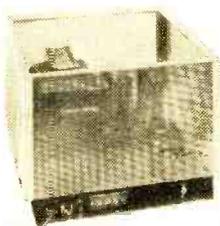REGENCY DIVISION,
I.D.E.A., INC.
7900 Pendelton Pike
Indianapolis 26, Ind.



Fifty-watt power amplifier, built from Regency HF-50K kit, provides enough reserve power to drive low efficiency, wide-range speaker systems. Response at 50 watts has less than 1% harmonic distortion from 20 to 20,000 cps. Multiple negative feedback circuits assure high damping. Step-by-step instructions are said to permit complete assembly in four hours. Amplifier must be used with audio "front end," or tuner having audio controls. Net, \$74.50.

Sound



Impressions

IN OUR platter-spinning this month, we came across several new ones that point up the natural affinity of woodwinds for the phonograph. Flute, oboe, clarinet and bassoon emerge from the loudspeaker with such lifelike tinge that the hi-fi listener finds it easy to forget all about his equipment and simply enjoy the music.

The husky, reedy sound of woodwinds is particularly easy on the foibles of electronic equipment. They sound good on medium-fi as well as on hi-fi because their overtone pattern does not get too badly twisted by a few jags in the frequency response or other minor distortions in amplifier and speaker. Besides, woodwinds don't produce sharp transients (bangs like in piano or percussion) that throw slightly ramshackle rigs into a jangling frenzy on every beat. Even on a less-than-perfect system, stylus, speaker and transformers can comfortably follow the waveforms of woodwind sound without getting rattled. Blended with orchestra, they add tangy spice or smooth sauce to the musical serving.

Unlike many other instruments, woodwinds sound fine even at low volume, which puts less strain on both your output tubes and your neighbors. Despite the absence of sheer decibel power, woodwinds create an amazing palette of tonal colors from acerbic snarls to silk sonorities.

Music in the Winds. The freshest wind to blow out of these woods is stirred up by Alec Wilder on Columbia CL-884. Wilder, one of America's most gifted young composers, reportedly was kicked out of the

Eastman School of Music at Rochester for what appears to be an extreme case of irrepressible high spirits, which compelled him to perpetrate all sorts of antics and spoofs. His good-natured practical jokes were always done with grand aplomb and a sense of style. The same mood of sparkling and imaginative fun pervades these woodwind compositions, variously entitled *Her Old Man Was Suspicious*, *The Neurotic Goldfish*, etc. The humor is pointed, never broad. The style combines an easy sense of aptness with arch mockery matched to musical craftsmanship. Maybe that's why top-notch musicians like Mitch Miller (oboe) and Julius Baker (flute) especially got together for this recording and gave it all they had—which is plenty. Their own evident pleasure in playing these pieces speaks from every groove. Behind the music there seems to be an inaudible chuckle. That's what makes this record something rather special.

Unusual things also happen on the other side. Here stands none other than Frank Sinatra, but this time he isn't singing. He's conducting an orchestra in more Wilder music, and doing a fine job of it. Frank accidentally came across these pieces when the composer and the music were quite unknown. He was so taken by a group of flowing, lyrical numbers for solo woodwinds and strings that he talked Columbia Records into letting him conduct them. The result is a deft blend of impressionism and pops: music to relax you

(Continued on page 105)

Frank Sinatra now makes his debut as a "classical" conductor in music by Wilder for solo woodwinds and string orchestra. He interprets this distinctively American music with conviction and finesse.





Robot Helicopter


FLOWN ALOFT by a technician operating a radio-control setup from the ground is the "robot" helicopter above. The ground controller is not a pilot himself; ease of control makes the robot capable of being "flown" by anyone. Inside the helicopter, in addition to the R/C equipment, are facilities for taking still pictures as well as TV pictures and transmitting them to ground observers.

In addition, the robot can fly communications lines, fly a "memory" course fed into a ground control station, and respond to commands transmitted from an airborne control station in a second helicopter. Developed by The Kaman Aircraft Corp., Bloomfield, Conn., the robot is shown in the above photo being demonstrated to U. S. Department of Defense officials at Fort Belvoir, Va.

Auto Antenna Replacement


MOTORISTS facing the problem of mischievous people breaking off or pilfering auto radio antenna staffs when a car is not under guard can now solve it in about 60 seconds. The answer is a glistening chrome-plated 3-section replacement auto antenna staff (Model RE-8) which will fit virtually every make of antenna.

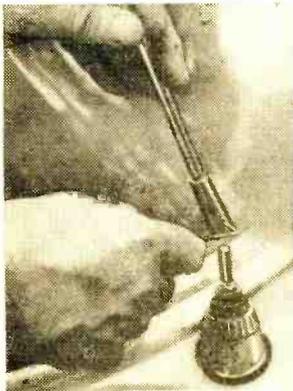The bell-shaped base of the replacement antenna staff merely fits over the old antenna base. A few turns of a special spline wrench, which comes with it, and the new staff is firmly fixed. Model RE-8 is 22" high when it is collapsed; with the three sections extended, the staff stands 56" above the bottom of the base. The unit is made by Snyder Manufacturing Co., Philadelphia, Pa.



Capacitors Use No Leads

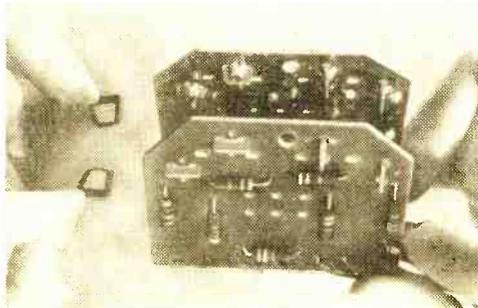A LINE of flat, tapered capacitors, designed specifically for use without leads in printed-circuit boards, has been announced by General Electric's Specialty Electronic Components Department, West Genessee St., Auburn, N. Y. Known as "Wejcaps," the units fit into




slots in the board and are bonded by dip-soldering. They will be used in TV receiver circuits.

Pocket-Size Tester

U NKNOWN voltages may be measured and circuit continuity checked with the pocket-size test instrument developed by Tele-Matic Industries, Inc., 16 Howard Ave., Brooklyn 21, N. Y. Known as the "Mini-Test," it uses a neon bulb rather than a meter movement for indications. Its range is from 65 to 800 volts.


As shown in the diagram below, its action depends on the amount of voltage impressed across the probe terminals. As the knob, controlling the potentiometer, is rotated from "Start" position, more resistance is shunted across the neon bulb until it is impressed with enough (65) volts to glow. The voltage being contacted by the probes may then be read from the knob setting on the outer cover of the "Mini-Test."

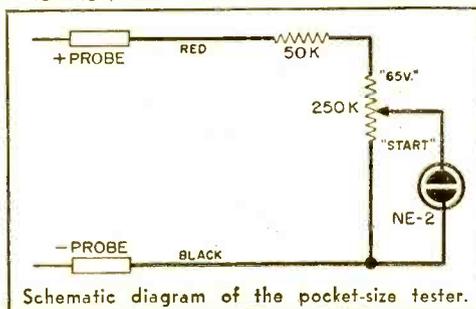To check circuit continuity, an auxiliary lead must be used which—together with one of the probes—is connected to an external voltage source. Measuring $1\frac{1}{8}$ " x $1\frac{1}{8}$ " x $\frac{5}{8}$ ", the "Mini-Test" lists for \$2.49.



Schematic diagram of the pocket-size tester.

Progressive Crystal Receiver

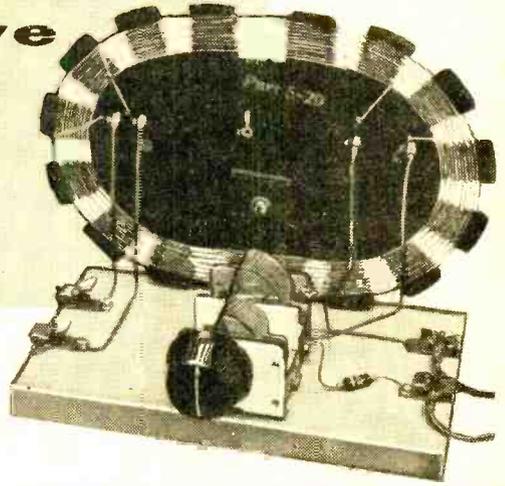

BEGINNING radio constructors who want to start with a simple crystal receiver would be wise to purchase parts which can be used later on for that inevitable three- or four-tube superhet. For example, if you buy a two-section superhet variable capacitor, you can use the large section for a crystal set and both sections later on for a superhet. Likewise, if you purchase a loop antenna to match the superhet capacitor, you can use the loop as a tuning coil in a crystal set and then use it later on as an antenna for a superhet. You could even use the crystal as a second detector in your superhet.

Almost every radio parts dealer, or radio mail order house, has two-section superhet variable capacitors with matching loop antennas. It would be well to buy a matching oscillator coil at the same time and put it on the shelf for that eventual superhet.

Mount the variable capacitor, loop, and four Fahnestock clips on a wood base $7\frac{1}{2}$ " long, 4" wide, and $\frac{3}{4}$ " thick. The loop can be bolted to a 2" x 5" wood upright screw-


fastened to the back edge of the wood base. A pair of Fahnestock clips about $1\frac{1}{2}$ " apart on the right-hand end of the base are used for the earphones, and another pair on the left end of the base for the antenna and ground connections.


The right-hand rear clip is connected directly to the capacitor frame (*rotor*) and from there to the lug on the loop which connects to the inside wire of the large loop winding. One lead of the germanium diode (*crystal detector*) connects to the right-hand front clip, and the other diode lead connects to the stator lug of the large section on the variable capacitor. Now connect the same capacitor lug to the lug on the loop which connects to the outside end of the large loop winding. The two remaining lugs on the loop are for the one-turn external antenna winding; connect these lugs to the remaining two clips on the left-hand end of the base.

If your loop has no external antenna winding, simply wind one turn of hookup wire around the outside of the loop, and fasten wire with cement or coil dope.

With regard to the antenna and ground connections for the crystal set, experiment for best results in your location. In some locations a good antenna is sufficient; in other cases a cold water pipe ground connection will give louder signals. Connecting the antenna directly to the stator lug on the variable capacitor will give strong signals, but poor separation between stations. As shown in the schematic diagram (dotted line), you can connect the antenna to the capacitor stator through a small value of fixed capacitor to improve selectivity. Try several different capacitor values until you find the one that is best for the job.

—Carl Dunant

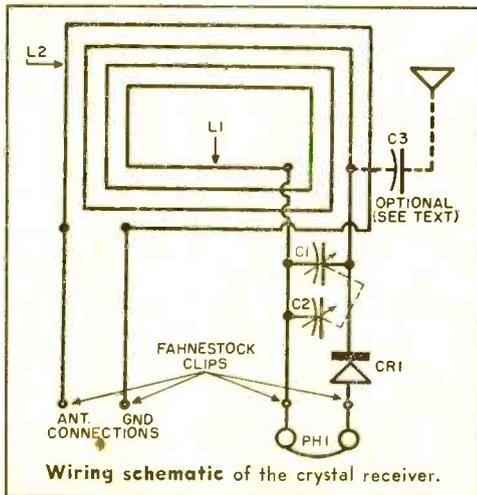

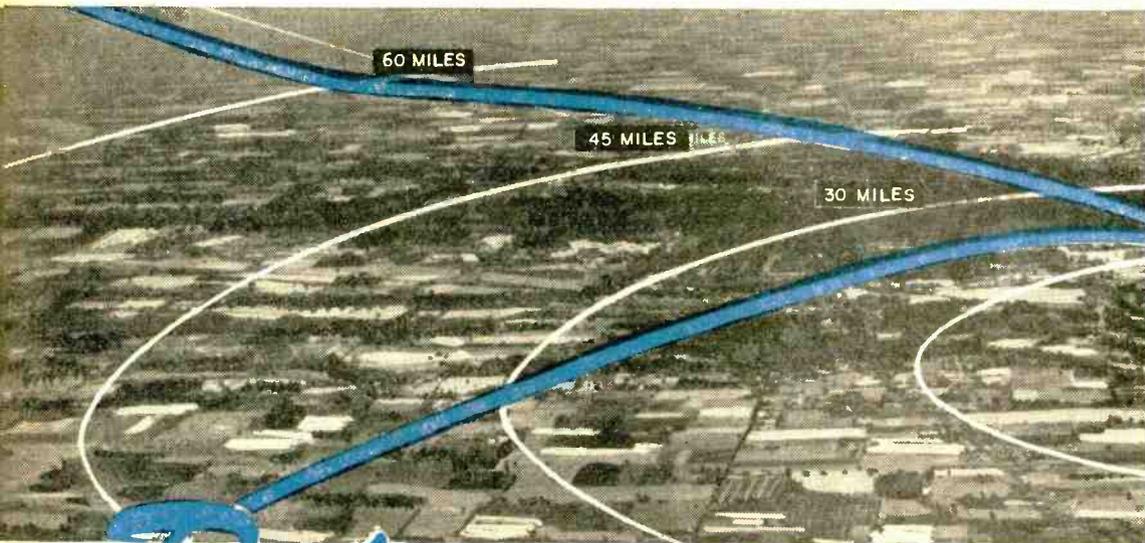

Radar

Tames the Wild Blue Yonder

By SHANE SMITH

THE SKY, once empty and beyond reach, is now a busy thoroughfare. Aviation has shrunk space aloft as well as on the ground. With the planes themselves made safe by today's superb engineering, congestion of the air has become the chief risk of flying.

As the wild, blue yonder grows wilder and more dangerous with fast planes crowding each other for space, the future of flying now depends on electronic aids to air safety.

Volscan, developed jointly by the Cambridge Research Center of the Air Force and the Crosley Corporation, is the latest answer to the urgent problem of air traffic control in the vicinity of busy airports. Combining ordinary radar data, Volscan converts a cloud of randomly arriving aircraft into an orderly, safe procession.

A supersonic jet plane may require as much as 50 miles for its landing approach, with some elbow room at either side. Therefore, an air traffic control system must assign each incoming aircraft a long "block of space" reserved exclusively for its use. Volscan automatically marks this space and follows the aircraft on its assigned path until the Instrument Landing System (ILS) takes over and sets it down on the runway.


Since pilots can't just step on the brake and slow down, the problem is complicated by faster planes overtaking the slower ones. A fast plane coming in later might wind up right on top of a slower plane that

had already started its landing approach. Hence, not only the sequence of the incoming aircraft but also their speeds must be taken into account. This adds to the space demand of fast planes and to the score of factors that every minute may tip the balance of life and death at a busy airport.

Volscan keeps all these factors "in mind" at any moment, and automatically parcels out to each plane precisely the air space it needs to keep that fateful balance firmly held down on the safe side. As the airport radar sweeps the sky, each plane in the area appears as a "blip" on the radar screen. The operator marks each newly appearing blip with a light gun, which triggers Volscan's electronic brain into action. The computer then "follows" the plane as the blip moves on the radar screen.

Acting as an electronic traffic manager, the computer has stored within itself the correct answers to every possible landing approach situation that may arise. Since the computer has the answer before the problem actually comes up, it needs only a fraction of a second to pick the correct approach instruction—in effect, to assign a block of space. These instructions are then given to the pilot by radio, or fed directly into the airplane's automatic controls by data-link transmission.

Always on guard against error, Volscan

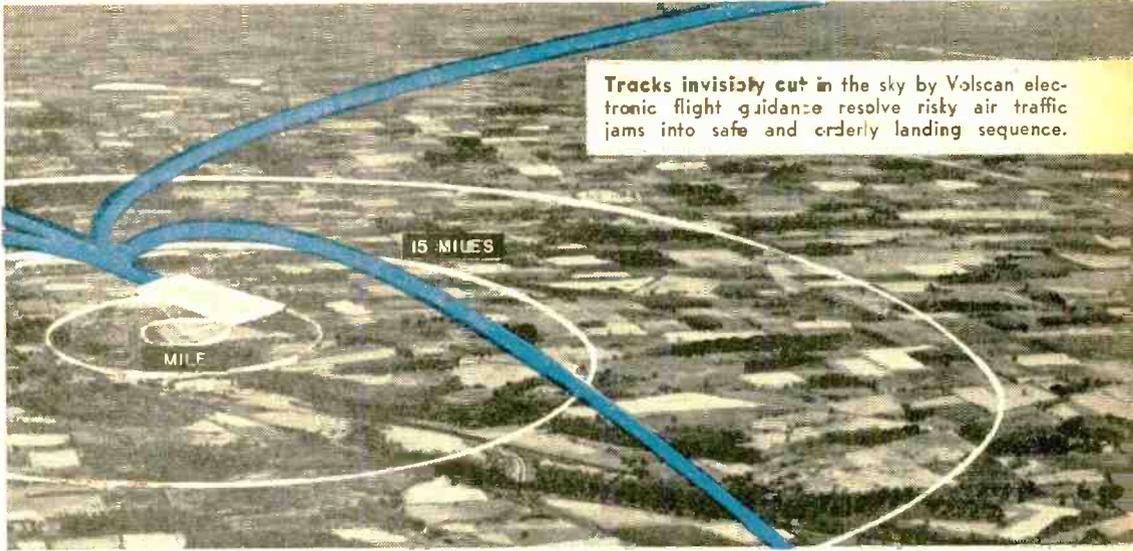

Tracks invisibly cut in the sky by Volscan electronic flight guidance resolve risky air traffic jams into safe and orderly landing sequence.


keeps its unblinking eye on up to 14 planes which it guides simultaneously. If either the human or the automatic pilot takes any plane off the assigned course, the computer immediately compensates for the mistake and issues new instructions for getting the plane back on its track and arrival schedule. It must "touch down" at just the right moment, for the 13 other planes are strung by the computer in a tight but safe landing sequence. The result is maximum use of the available runway facilities, increasing the safe traffic capacity of any airport almost three times.

In this manner, Volscan can handle one landing every 30 seconds, thus reducing the dangerous practice of "stacking" airplanes waiting around an airport for an

opportunity to land. Such stacking is discomforting in present-day planes, but for the jets of the not-distant future, it would be disastrous. For jets use almost three times as much fuel at approach altitude as they do at cruising altitude. While awaiting their landing clearance, they might exhaust their fuel reserve.

Volscan and the whole problem of air traffic control point up those ironic twists by which history bedevils human effort. Fifty years ago, when Man first transformed himself into a creature of flight, the main idea was to get him off the ground. Now, in the headlong progress of the air age, he seems to have trouble in getting down again. But electronics offers him a safe ladder for his descent. —50—

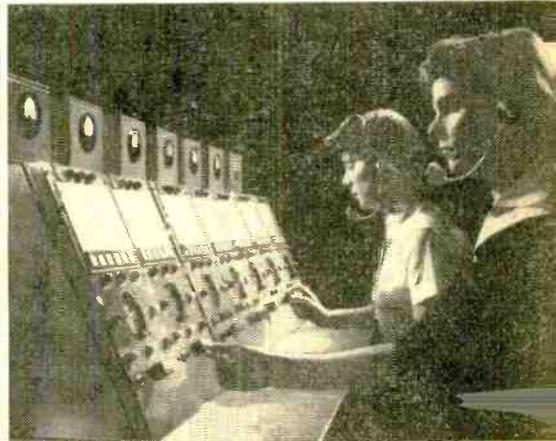Giant overhead radar scope (left) displays total air traffic situation. As newly arriving plane enters the monitored air space, an electronic computer co-ordinates its position and progress with every other plane in the area. Operators at right relay instructions to incoming aircraft in terms of azimuth and elevation.



AFTER CLASS



Special Information on Radio, TV,

Radar and Nucleonics

WORKING WITH THERMISTORS

WITH TRANSISTORS enjoying the spotlight in current experimental work, we tend to forget that there is another kind of semiconductor material—the thermistor—which is finding wide acceptance in all kinds of electrical jobs.

Just what is a thermistor?

All electrical conductors show a tendency to change electrical resistance as their temperature varies. Some materials such as the alloy "Invar" do this so slightly that they are said to have virtually zero *temperature coefficient of resistance*; metallic oxides used in today's commercial thermistors change resistance abruptly with relatively small temperature variations.

Modern thermistors have large *negative* temperature coefficients. This means that their electrical resistance *drops* sharply

when the temperature *rises*. The extent of the change can be predicted quite closely from the thermistor ratings—as you will see.

Forms of Fabrication. The most common physical shapes in which modern thermistors are fabricated are rods, beads, discs, and washers. Each unit starts life as a pasty black mix of several metallic oxides. Rods, discs, and washers are made


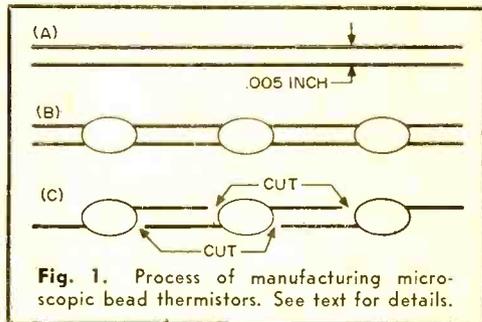


Fig. 1. Process of manufacturing microscopic bead thermistors. See text for details.

by first shaping the mix paste as desired and then firing the forms in temperature-controlled ovens. The "cold" resistance of an individual thermistor is governed by the composition of the original mix and by the time-temperature constants in the sintering process. This control permits a range of 5 to 100,000 ohms at 25° C by means of only two different mixes.

Manufacture of microscopic bead thermistors is a fascinating process to watch. (See Fig. 1.) Two extremely fine platinum wires (A) are held taut and parallel to each other, the distance between wires being less than .005". Tiny blobs of the mix are then daubed on the wires (B) so that they are bridged by the bead; after drying and shrinking, the strand of beads is sintered and glass-coated. Later, the wires are cut to precise lengths (C) and the units are mounted on holders. Bead thermistors are available in

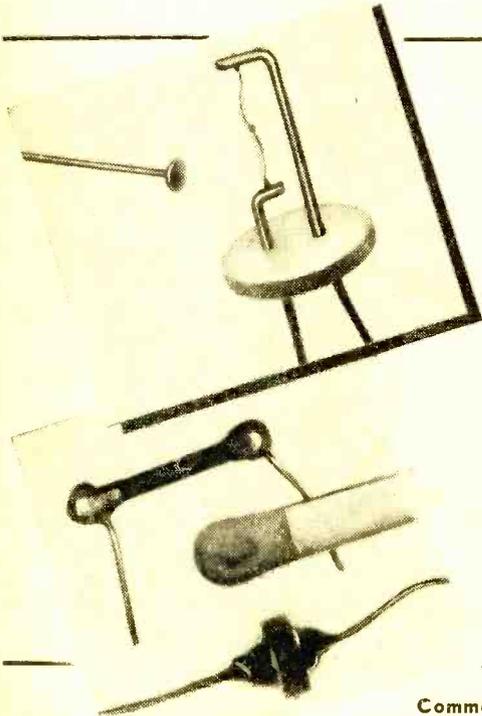

Common shapes in which thermistors are made. The head of a pin (top) is gigantic compared to tiny bead thermistor (A33 VECO) in center of fine wire. In the bottom square, a 51R2 VECO rod thermistor and a small disc thermistor are contrasted with ordinary paper match-head.

an assortment of values from about 500 ohms to 12 megohms at 25° C.

Varying Temperature. To take advantage of a thermistor's characteristics, its temperature must be made to vary and the resulting change of resistance put to use operating a meter, relay, etc. There are three distinct means by which this is done.

(1) *Ambient temperature changes.* A thermistor will follow the changes in ambient temperature by varying its resistance accordingly. This is the basis of thermometers, fire alarms, and thermostats.

(2) *Self-heating action.* If the current through a thermistor is made large enough, the thermistor temperature will rise, causing the resistance to drop, which in turn allows more current to flow and more heat to be generated. The build-up process continues until the temperature of the thermistor stabilizes at the point where the surrounding medium can carry heat away as fast as it is generated. This action is used in flowmeters, anemometers, liquid level gauges and controllers, and thermal conductivity measurement. The type of medium or its motion causes more or less rapid cooling of the self-heated thermistor, thus setting up the current-change conditions needed for measurement or control.

(3) *Independent heater.* Some special thermistor assemblies are provided with a heating element near the temperature-sensitive bead to permit heating control independently of the main circuit current or ambient temperature. This arrangement is used only in highly specialized industrial applications.

Thermistor Ratings. A sensible approach to thermistor experimentation requires understanding of thermistor ratings and the circuits for which they are best
(Continued on page 109)

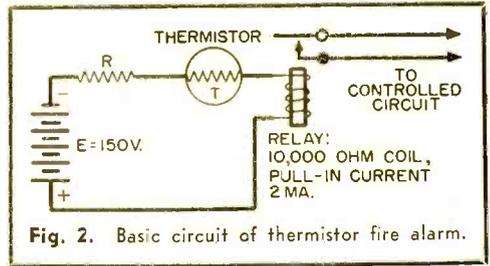


Fig. 2. Basic circuit of thermistor fire alarm.

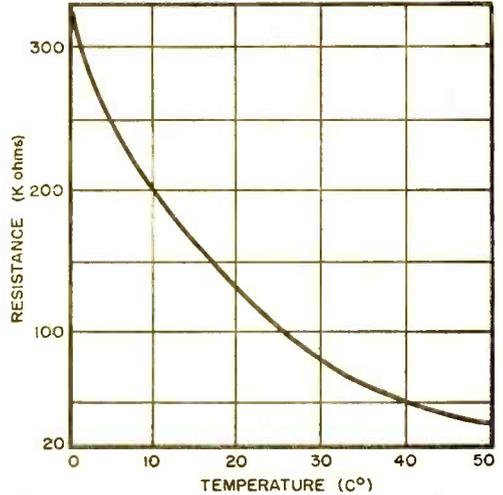


Fig. 3. Resistance-temperature curve for a 51R2.



Victory Engineering Corp.

Probe attachment on thermis- or thermom- eter at left is being used to measure soil temperature for agricultural control. In- accessible places are easily reached by a long probe like the one utilized above in measuring air-conditioner vent temperature.

A Beam and Tower for the 15-Meter Novice

By
WILLIAM I. ORR, W6SAI

paper," I ordered. "I remember a tower and beam antenna design that was used by W6VAT and some of the other DX-chasers. It worked fine, and was very inexpensive to build. It's just the ticket for a 21-mc. Novice antenna. Look here, I'll draw you a sketch of it. . . ."

A simple and inexpensive 32' tower can be built from two 20' "two-by-six" pieces of #1 lumber, as shown in Fig. 1. Each piece of material is cut lengthwise (the lumber yard will do it) to form two "two-by-three" pieces. A 4' section is cut off the end of each two-by-three, leaving four 16' pieces to form the legs of the tower. The tower should be flat, built much in the manner of a ladder. Make up each leg with two pieces of lumber, spliced together with a 4' section. A rigid joint is formed when the legs are drilled and four $\frac{3}{8}$ " steel bolts are passed through the holes in the leg sections and the splice.


The crosspieces of the tower are made of "one-by-four" lumber. These braces should be spaced about two feet apart, starting about four feet above the ground, and held in place with "sixteen penny" cement-coated nails.

"Why do you start the crosspieces four feet above the ground?" asked Jimmy. "That's to keep the little brats like your younger brother from climbing the tower," I replied, with a laugh.

The tower is three and one-half feet wide at the base, tapering to sixteen inches at the top. Splice each side joint and lay the two legs out in the driveway, in correct position. Then, temporarily nail a top and bottom crosspiece in place to steady the legs. After that, nail on the intermediate cross braces. Drive two cement-coated nails through each end of each cross brace.

These cross braces may be cut slightly

POPULAR ELECTRONICS

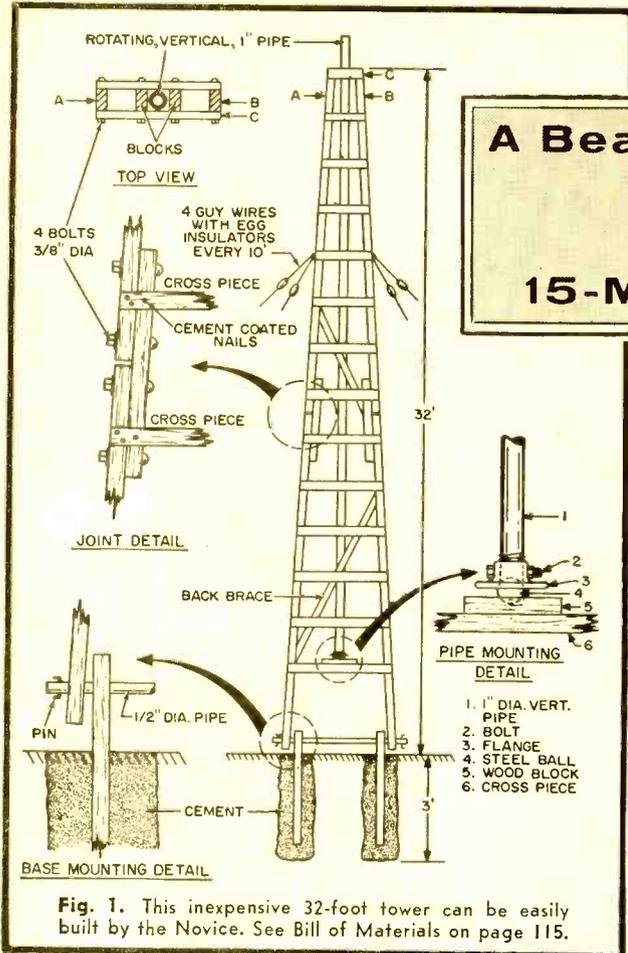

"WHAT do you think of this DX QSL card?" asked Jimmy, waving a gaudy red and blue Australian card.

"Looks real fine," I replied. "Is it in answer to a SWL card that you sent out?"

"NO!" snorted the young Novice. "This is my first DX card for 15-meter operation! I worked him! I'm in the big league now!"

"Well, not exactly, Jimmy! Not with a dipole antenna. You've just been lucky so far. The Novice QRM is getting pretty heavy on 21 megs. You had better start thinking about a beam antenna if you want to be a DX-man."

"That's why I'm here!" said Jimmy, collapsing into the easy chair next to the operating desk. "Let's design a good beam antenna and tower that I can put up for about thirty bucks. That's all the money I can scrape up. . . . Golly, a good rotator for the beam will cost that much, I bet." An unhappy look clouded Jimmy's face as he voiced this pessimistic thought.

"All right, pass me a piece of talking

longer than necessary, then trimmed up after they are all in place. Use two cross braces at the top and bottom of the tower, one on each side. Check each step carefully, and the tower will remain square and true. Avoid any wood that is split or warped. Finally, turn the tower over and nail the two diagonal braces in place, as shown in Fig. 1, to take the sway out of the tower.

The foundation for the tower is made of two pieces of "four-by-four" creosoted lumber (or redwood) that are sunk vertically in three feet of cement. Foundation holes should be about a foot and a half square. The base hinge is made from a 4' length of $\frac{1}{2}$ " water pipe. Drill the legs of the tower and the two mounting posts to pass the pipe, as shown in the drawings.

"How about the rotator?" demanded Jimmy. "Easy, Junior," I said. "You young squirts are getting soft! You can't afford a rotator. I had a beam antenna for ten years before I had a rotator. I used the Armstrong method of turning it. So can you. After all, you'll find that you only turn the beam occasionally. You won't spin it around too much. There's no reason why you can't rotate the beam by hand."

Obtain enough 1" (i.d.) water pipe to make a continuous section about 30 feet long. Threaded couplings may be used to make splices, but each coupling should be pinned with a bolt to prevent the couplings from coming undone in a heavy wind.

This pipe is passed down the center of the tower. Starting at the top, and at every fourth cross brace, place wood blocks on each side of the pipe to keep it in position. The blocks form a rough bearing, bracing the pipe but allowing it to turn. Wherever the blocks are used, that cross brace should be bolted to the tower legs with $\frac{3}{8}$ " steel bolts, as the nails might just loosen in a strong wind. Also bolt the wooden blocks in position.

At the bottom of the tower, the pipe rests on a wooden block attached to the top of the double cross braces. Thread a pipe flange on the base of the pipe, and pin it. Several holes should be drilled in the block, matching the holes in the flange. Finally, boost up the whole pipe an inch or two, and slip an old $1\frac{1}{2}$ " ball bearing under it to provide a smooth surface for rotating the pipe. A long bolt is passed through the flange into one of the holes in the block, locking the beam in the chosen direction.

"How do I turn the beam?" asked Jimmy. "Silly boy! You pull out the bolt, grab the flange, and turn! It's easy!" I replied.

Brace the tower at the 30' level by two sets of guy wires, running forwards and backwards from the tower, at an angle. The tower can be hinged at the base, and "walked up" into vertical position by three or four fellow hams. When the tower is erect, attach the guy wires to nearby points, and tighten them. A second set of guys could be attached at

the 20' level to make the tower even more rigid. When completed, the top of the supporting pipe should project about two feet above the top of the tower to take the beam antenna. As a final step, give the tower a coat or two of gray house paint for protection against the weather.

"The antenna! What kind of an antenna can a poverty-stricken Novice like myself build for a few dollars that will really bore a hole in the band?" demanded Jimmy. "Well, here it is," I replied, reaching for a second sheet of paper.

A two-element, 15-meter parasitic beam will provide about 5 db gain—enough to make the Novice 75-watt transmitter sound like a
(Continued on page 114)

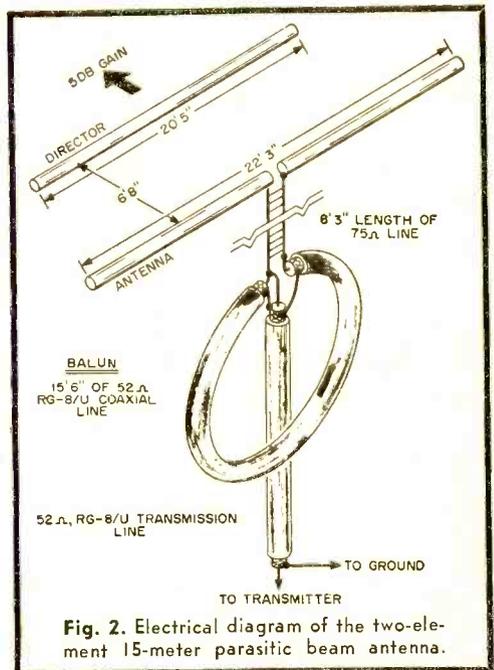


Fig. 2. Electrical diagram of the two-element 15-meter parasitic beam antenna.


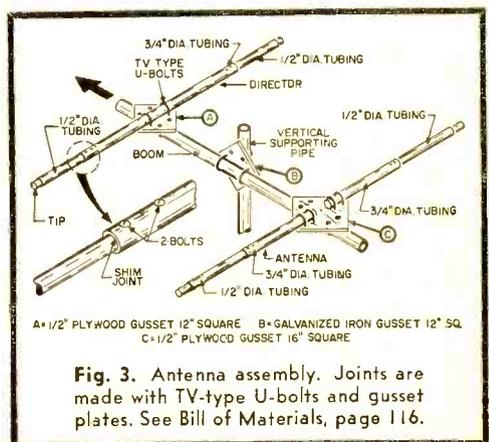


Fig. 3. Antenna assembly. Joints are made with TV-type U-bolts and gusset plates. See Bill of Materials, page 116.

Amplifierless Record Player

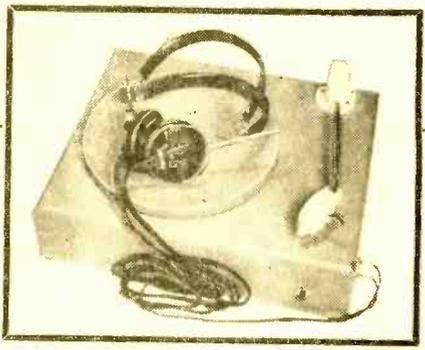

WHILE EXPERIMENTING with an old crystal phono cartridge, the author connected a pair of high-impedance magnetic earphones across the terminal lugs on the cartridge, and was pleased to find that the recorded material could be heard with surprising volume and clarity.

There are a number of instances where it might be desirable to dispense with an audio amplifier and speaker. Many public libraries, for instance, are equipped with record players using amplifiers for record-auditioning in their record-loaning departments. Every librarian would welcome a simple record player having improved fidelity, no hum, no tubes to wear out, and consisting of only a turntable with pickup, and a pair of phones. In record shops, the usual row of poorly ventilated booths, with their expensive amplifiers and noisy speakers, could be replaced with a row of turntables with pickups, and earphones.


Measuring 10" x 12" x 3", the author's record-player cabinet was constructed of wood and covered over with Contact adhesive plastic-coated material. You can build a cabinet, buy a ready-made one, or use


any suitable record-player cabinet you have on hand. The model utilizes a 33½-rpm phono motor that happened to be on hand, but you may want to use a modern 3-speed motor.

The crystal phono pickup is a Ronette FF2 low-resonance 12" arm containing a Ronette 284-P high-fidelity crystal cartridge. Although the voltage output of the 284-P is relatively low (between .15 and .38 volt) as compared with many crystal cartridges, the earphone volume seems to be entirely satisfactory. Those with below normal hearing, however, will need to use a crystal or ceramic cartridge having a high voltage output. Other high-fidelity crystal or ceramic phono cartridges which may be used are the Sonotone "3" series, the Electro-Voice "80" series, the Shure "Music Lovers Cartridge," etc. Magnetic and dynamic phono cartridges are not suitable for amplifierless earphone listening due to their very low outputs.

Use high-impedance earphones to match the high impedance of the crystal or ceramic cartridge. A crystal headset is the logical choice. The author uses a pair of Brush BA-206 crystal phones. Those who do not wish to invest in a pair of top-quality crystal earphones will find that the little crystal earpiece available from Lafayette Radio, 100 Sixth Ave., New York, N. Y. (Catalog No. MS-111, \$1.49 net), is as sensitive as a pair of phones. The frequency response is not nearly as smooth, though, and you'll have to push the earpiece firmly into your ear to get good bass response—which may result in discomfort over long periods of listening. Nevertheless, this little earpiece does a fine job for the money.

—Art Trauffer

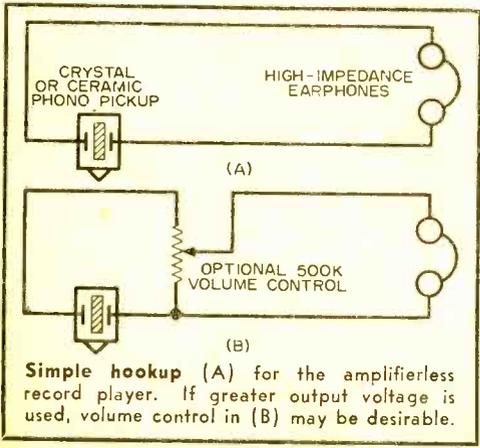

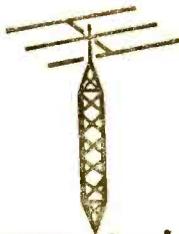

THE TRANSMITTING TOWER

Herb S. Brier, W9EGQ

USUALLY when a short-wave communications receiver is mentioned, one immediately thinks of an elaborate, multi-tube superheterodyne. The reason for this is that the basic superheterodyne circuit is flexible enough to accommodate the many tubes and special circuits required to give the best possible results under unfavorable conditions. It is the basis of the often repeated advice to get the best receiver you can afford for your radio shack. It does not mean, however, that you must have an elaborate superheterodyne receiver to hear short-wave signals. The much simpler regenerative receiver will also bring them in.

In the hands of a skilled operator, the performance of a two- or three-tube regenerative receiver will approach that of a superheterodyne costing several times as much. In addition, its simplicity makes constructing a regenerative receiver (either from "scratch" or from a kit) and learning how to operate it an ideal project for anyone just getting started in radio. Doing so is fun and will quickly develop the skill and knowledge required to tackle a more elaborate project successfully.

What Is Regeneration? The Knight "Space Spanner" short-wave and broadcast band receiver, available in kit form from Allied Radio Corporation, 100 N.


Western Ave., Chicago 80, Ill., is an example of a modern regenerative receiver. Before discussing it specifically, let's learn a bit about how a regenerative receiver works—with the aid of Fig. 1 on page 83.

To begin, all signals picked up by the receiving antenna are fed into the tuned circuit, consisting of a coil *L1* and a variable capacitor *C2*, via the antenna coupling capacitor *C1*. *L1* and *C2* select the signal and deliver it to the grid of the detector tube, *V1*, via the grid capacitor *C3* and grid resistor *R1*.

In the tube, the desired signal is amplified, and through the influence of *C3* and *R1*, the audio-frequency intelligence it carries is removed from the signal and is delivered to a pair of headphones or to an audio amplifier for further amplification.

Note that the signal from the plate of the detector tube does not go directly to the phones or audio amplifier. Instead, it first flows through the "tickler" coil *L2*, which is wound on the same form as *L1*. In this manner, part of the detector output signal is coupled back into *L1*, from whence it goes through the tube to be amplified again and again. This is *regeneration*.

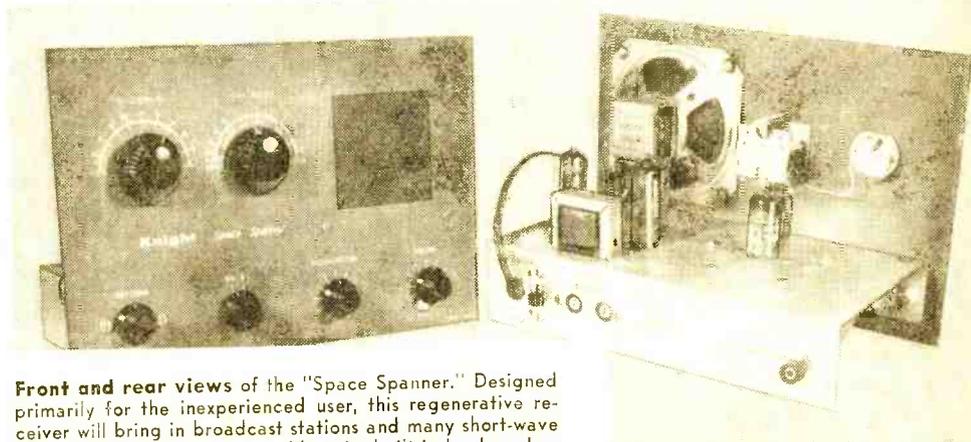Each time the signal makes the round trip through the circuit, it naturally becomes stronger. At the same time, the



Front and rear views of the "Space Spanner." Designed primarily for the inexperienced user, this regenerative receiver will bring in broadcast stations and many short-wave stations from all over the world on its built-in loudspeaker.

HELP US OBTAIN OUR HAM LICENSES

In this section of the Transmitting Tower, the names of prospective amateurs requesting help and encouragement in obtaining their licenses are listed. To have your name listed, write to Herb S. Brier, W9EGQ, % POPULAR ELECTRONICS, 366 Madison Ave., New York 17, N. Y. Please print your name and address clearly. Names are grouped geographically by amateur call areas.

K1/W1 CALL AREA

Bruce A. Childs, P.O. Box 226, Centerville, Cape Cod, Mass. (Code)
Edward Tanzer, 216 Vine St., Everett, Mass. (Code)
Joel L. Richmond, 2 Hiawatha Road, Mattapan 26, Mass. (Code)

K2/W2 CALL AREA

Joseph Essington (15), Pedricktown Rd., Penns Grove, N. J.
Jose Garcia, 1396 Stebbins Ave., 5-E, Bronx 59, N. Y.
George Stovall, 112-24 Northern Blvd., Corona 68, New York, N. Y.
Joseph Green, 60 Felice Crescent, Hicksville, N. Y.
Stuart Ring, Box 7, Adams, N. Y.
Martin Gucker, 65 E. Tremont Ave., Bronx 53, N. Y. (Code)
Stuart Mount, P.O. Box 62, Clintondale, N. Y. (Code)
Robert Batchelor, 20 McKinley Place, Glen Cove, N. Y.
Ronald Wilensky, 920 E. 17th St., Brooklyn 30, N. Y. (Code)
Bob Freeman (13), 88 Magnolia St., Westbury, N. Y. (Code)
Pete Tedesco (13), 26 Brookside Circle, Bronxville, N. Y. (Code)

K3/W3 CALL AREA

Robert Bair, 169 Craig Drive, Greensburg, Pa.
Robert Himler, 11 W. Madison St., Latrobe, Pa.
Michael W. Vore, 359 Whitfield Road, Catonsville 28, Md.

K4/W4 CALL AREA

Tad Buckland (14), 317 Blowing Rk. Rd., Boone, N. C. (Theory)
Jimmy Cheek (18), 107 Hampton St., Westminster, S. C.
Richard L. Warren (13), 2780 Skyline Drive, Memphis 8, Tenn.
Kip Coffeen, 126 Pinewood Ct., Lynnwood Subdivision, Woodbridge, Va.
Frank Piekarski, 27 Morgantown St., Fairchance, Va.
Don Blanton, 2523 Hale Ave., Louisville, Ky.
Kimp Talley (17), Route 2, Box 48, Henderson, N. C.
Jackie Blackwell, Box 367, Kernersville, N. C.
Mike Fletcher, SWL-42, (18), 300 W. Redbud Dr., Knoxville, Tenn. (Theory)
George Brookhyser (16), Box 157, Sylva, N. C. (Code and theory)

K5/W5 CALL AREA

Jimmy Day, Box 22, Lone Grove, Okla.
Jim Willcox (15), 309 Pinewood, Hot Springs, Ark.
Bobby Larse, VA Hospital, McKinny, Texas.
Ronald E. Alford (14½), 1802 Sullivan St., Pasadena, Texas.
John Kusianovich, P.O. Box 6, Fort Stanton, New Mexico.
Bill Blankenship, Box 306, Cooper, Texas.

K6/W6 CALL AREA

Don Petric, 1710 Malcolm Ave., Los Angeles 24, Calif.
Gary Young, P.O. Box 115, Lockeford, Calif.
Thomas Whiteley (14), 4637 18 St., San Francisco, Calif.
Leslie Stanford Cammer (12), 624 San Pascual, Santa Barbara, Calif.
Fred Capshaw, 1928 Chance Ave., Fresno, Calif.
Fred Reher, 12971 7th St., Chino, Calif.

Don Ziegler, 1855 Sonoma Ave., Santa Rosa, Calif.

Philip Saxe (11), 4624 18 St., San Francisco, Calif.

Robert A. Graeber, 456 Milford St., Glendale 3, Calif.

Jim Richman, 737 N. Mamfield, Hollywood 38, Calif.

Thomas Scott (14), 545 Redwood Ave., San Bruno, Calif.

Joe Sharmer (15), 902 Walnut Ave., Santa Cruz, Calif.

Jon Clark (14), 704 Gilroy Drive, Capitola, Calif.

Joseph W. Granville, 1864 Belmont Ave., San Carlos, Calif.

Earl Neoman, P.O. Box 1506, Shafter, Calif. (Code and theory)

Dug Stokes, 636 W. Cypress Ave., Covina, Calif.

Gary Grant, 9588 Upland St., Spring Valley, Calif. (Code)

Floyd L. Herbert, 2399 Ash Ave., Merced, Calif. (Code)

K8/W8 CALL AREA

Don Rees (13½), 706 Gill St., Huntington, W. Va.

Jim Toreson, 38207 Barth, Romulus, Mich.

Lewis Traxler, 535 Kaler Ave., Bucyrus, Ohio.

Bill Newbrough, 351 W. Washington St., Grafton, W. Va. (Theory)

Martin Webb, 717 Maryland Ave., Fairmont, W. Va. (Code)

Jerry Barker, 595 Hagadorn, S. Lyon, Mich. Phone: GE 8-8054. (Code and theory)

Len Behr, 5926 Cbplin Ave., Detroit 13, Mich. (Code and theory)

Jeff Bohl (14), 1717 W. Pasadena, Flint 4, Mich. (Code and theory)

Ricky Karash (10), 330 Walworth Dr., Euclid 32, Ohio.

Nicky Swan, P.O. Box 204, Ludington, Mich.

Gary Townsend, 838 Continental, Detroit 15, Mich.

Dennis Beshara, 5555 Stuber Dr., Canton 8, Ohio. (Theory)

K9/W9 CALL AREA

Nick Frato, 6903 So. Anthony, Ft. Wayne, Ind.

Ronald Isaacs (13), 819 N. 6th St., Mt. Vernon, Ill.

William L. Harris, 824 N. 10th St., Lafayette, Ind.

Fred Leadlove (15), 1615 Ohio Ave., E. St. Louis, Ill.

Charles Smith, 302 Sixth Ave., Sterling, Ind.

KO/WO CALL AREA

Roger E. Clark, 246 North 9th Ave., Broken Bow, Nebr.

I. J. Rusand, 702 W. 1 St., Pittsburg, Kansas.

Bob Ball, 1519 Main St., Lexington, Mo.

Dick Anderson, 4234 Raleigh Ave., St. Louis Park, Minn.

Tom Reiter, 1625 Prescott St., Dubuque, Iowa.

Mac Floyd, 117 No. Chautaugua, Wichita, Kansas. (Code)

Dale Kerwood (14), 4560 Wolff St., Denver 12, Colo.

David Bergan, Florence, So. Dakota. (Code, theory and regulations)

VE AND OTHERS

Carl O. Baptiste, Jacamel, Haiti, West Indies.

J. G. Bateau, P.O. Box 378, Station "A," Kitimat, B.C., Canada.

Nicky LeMoine, 608 Argyle Ave., Westmount, Montreal, Que., Canada.

Boris Auguste (VP2LB), I.C.T.A., St. Augustine, Trinidad, B.W.I. (Pen pals)

To help prospective amateurs obtain their Novice licenses, the Radio-Electronics-Television Manufacturers Association offers a set of code records (recorded at a speed of 33½ rpm) and a Novice Theory Course for \$10.00, postpaid. The complete course or more information on it is available from RETMA, Suite 800, Wyatt Bldg., 777 Fourteenth St., N. W., Washington 5, D. C.

process increases the ability of the receiver to select the desired signal from among other signals. This is because regeneration increases the strength of the desired on-tune signal much more than that of the off-tune signals.

In this circuit, regeneration is controlled by varying the detector plate voltage. However, if the regeneration control is advanced beyond a critical point, so much energy is fed back from the plate of the tube to its grid circuit that the tube breaks into sustained oscillations.

As a result, each time a signal is tuned in, it beats with the signal generated in the tube to produce an audible beat-note (also called a heterodyne, squeal, or whistle) in the phones or loudspeaker. The detector is operated in this manner to receive c.w. code signals. To receive signals carrying voice or music, the regeneration control is normally adjusted to just below the oscillation point.

Knight "Space Spanner." Returning now to the Knight "Space Spanner," this receiver uses a 12AT7 dual-triode tube as a regenerative detector and first audio stage. The 12AT7, in turn, drives a 50C5 output amplifier, which drives a built-in loudspeaker or a pair of phones.

Voltages to operate the receiver are obtained from a self-contained power supply. It utilizes a 35W4 rectifier tube to convert the power line current to the well-filtered direct current required for quiet, hum-free operation of the receiver.

The "Space Spanner" covers the standard broadcast band—545 kc. to 1605 kc.—in one position of its band selector switch and the short-wave range of 6.5 mc. to 17 mc. in the other.* Other panel controls include the main tuning dial, which adjusts the main tuning capacitor, and the "band-spread" dial which controls a small variable capacitor connected in parallel with the main tuning capacitor. This small capacitor permits any small segment of the frequency range covered by the main dial to be spread across the entire bandsread dial scale.

Assembling the kit is made easy by the exceptionally easy-to-follow instruction book included with it. All parts, except hookup wire and solder required to as-

* Its 6.5-mc. to 17-mc. short-wave coverage is a compromise. But it covers most of the international, short-wave broadcast bands and the 7- and 14-mc. amateur bands; therefore, it can be used as a 7-mc. Novice receiver. Strictly as a Novice receiver, it would be better if the coverage was from approximately 3 mc. to 8 mc., so that it would include the 3.5-mc. amateur band. But then most of the international short-wave broadcast bands would be omitted; consequently, the present coverage probably best meets the needs of the greatest number of potential users. Other bands could have been added to the receiver, but this would have increased its complexity and cost more than the intended purpose would warrant.

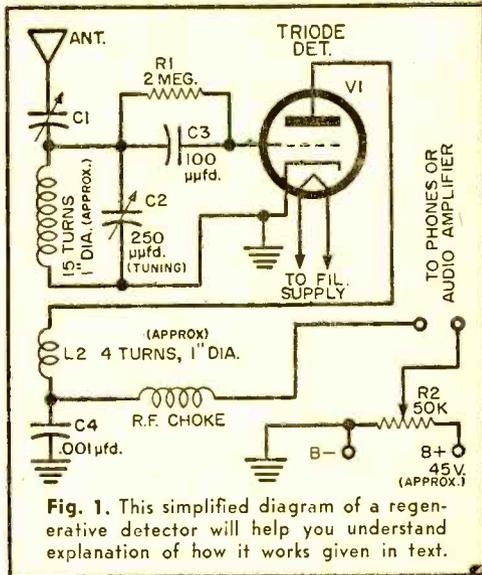


Fig. 1. This simplified diagram of a regenerative detector will help you understand explanation of how it works given in text.

semble the "Space Spanner" are included in the kit.

Results and Conclusions. Reception on the broadcast band with the Knight receiver compares favorably with that of the average table model receiver. A 15' antenna strung across the room will bring in all stations within the normal "service area" with good loudspeaker volume.

On the short-wave band, an antenna 50' to 75' long erected as high and clear of buildings and trees as convenient will give loudspeaker volume from the more powerful stations both from the United States and overseas. To receive the weaker ones, however, it is necessary to use headphones. This may be a blessing in disguise. Under unfavorable conditions, signals are always more readable through phones than through a loudspeaker, anyway.

On the basis of its simplicity, perform-
(Continued on page 119)



Dave Reddick, KØBIL, Naturita, Colo., has been a ham for a little over a year. He operates his DX-100 transmitter and SX-99 receiver on the 75-meter phone band but will be happy to work anyone who wants a Colorado contact on phone or code.

Singer's voice is blended with orchestral background from record by means of mixer. Result is recorded on tape.



Equipment Courtesy Fisher Radio Corp.



By Richard H. Dubbe

You can combine voice and music "professionally" on one tape

DO YOU WANT your tape recordings to have that final "finish" that makes them sound like professional programs? Use a "mixer"—it will open a new world of fun for you and program flexibility for your tape machine.

Suppose, for instance, you have taped some music by a favorite band. You want to combine this with voice announcements, coming in occasionally over or under the music, to describe who the musicians are, what they're playing, etc.

Or suppose you're creating on tape a drama in sound, consisting of a play with musical background and sound effects. The music must swell up, die down, and relate itself dramatically to the voice parts. Similarly, the loudness of the spoken parts must be separately controlled so that they can be faded in and out.

These are only two situations out of many in which a mixer could prove invaluable. The separate signal sources it accepts, blends, and feeds to the recorder may be from microphones, phono players, TV sound, radio tuners, other tape recorders, or any combination of such sources.

Mixing in the "Pot." To be really useful, a mixer should also be a "fader"—so that it will not only blend independent sound sources but will also permit you to control their relative levels.

The simplest kind of mixer-fader consists of two potentiometer volume controls wired to accept signals from two input jacks and to feed a common signal out of a third jack. A simple circuit for such a

device is shown in Fig. 1. It is easy and cheap to build, but it runs the risk of noise and improper impedance matching.

Electronic mixers provide smooth mixing and fading with little insertion loss and with maximum transfer of signal voltage. What's more, using tubes, you can build a very versatile mixer which will accept both high- and low-level signals simultaneously. In other words, the tube provides gain for the weaker signals available from low-level mikes or weak tuners, etc.

Single Triode Mixer. The simplest form of electronic mixer, with a single triode stage, is shown in Fig. 2. Sometimes termed a "parallel mixer," this circuit is useful only for mixing two signals of fairly high voltage level, such as the output from a phono preamp, high-level mike, radio tuner, etc. The series resistors (R_2 and R_4) prevent the fading controls (R_1 and R_3) from short-circuiting each other, but at the same time they reduce the voltage level of the incoming signals.

Dual Triode Mixer. An improved version of the single triode mixer is one which uses both halves of the dual triode tube (Fig. 3). Each input channel, with its own level control, feeds the grid of one triode. Any combination of signals—selected by adjusting R_1 and R_2 —is passed through C_2 to the next stage, which should be the low-gain, high-impedance input jack of a tape recorder.

Resistors R_6 and R_7 are needed for isolating the two plates, but they will reduce the output signal voltage. The amount of

reduction depends on the value of the grid resistor used in the following stage. The higher this resistor, the lower the signal loss. Thus, it is essential that the mixed signal be fed to a high-impedance input.

The incoming signals to be mixed should be high-level signals, such as are available from a phono preamp, radio tuner, high-level microphone, TV sound, etc.

Pentode Mixer. If the mixing stage must provide more gain than the triode circuit above can manage, a mixer with pentodes may be used. The circuit in Fig. 4 has been designed to accept a low-level signal in channel 1, and either a low- or high-level signal in channel 2. With the values shown for the components in this circuit, the mixer will have considerable gain. Either channel 1 or channel 2 (with the switch on "LOW") may be used—not only for mixing, but also as a preamp to boost low level signals. Suitable signal sources would be a low-level microphone, a magnetic phono pickup that has not been fed through its own preamp, the signal from a crystal detector tuner, etc.

With the switch in channel 2 on "HIGH," an additional large resistor is thrown into the grid circuit of the bottom 6AU6. This resistive network reduces the strength of an incoming signal to the point where it will not overload the 6AU6. Therefore, it enables you to feed a high-level signal into channel 2. Needless to say, you may feed a low-level signal into channel 1 at the same time. Such an arrangement provides maximum versatility of operation.

R1 and *R2* serve as the level and fading controls for their respective channels. *R8* serves as a "master level control" which

(Continued on page 131)

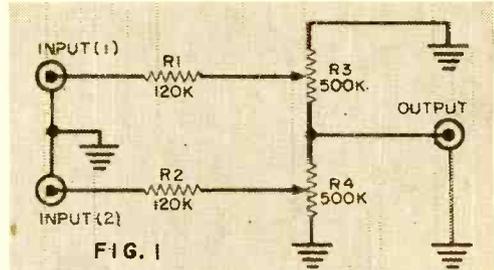


FIG. 1

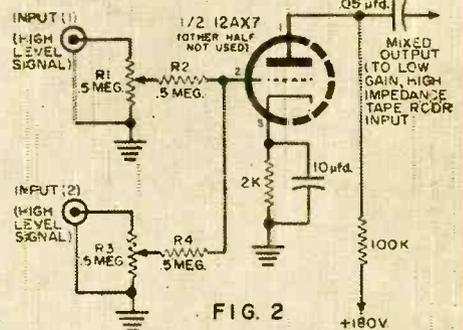


FIG. 2

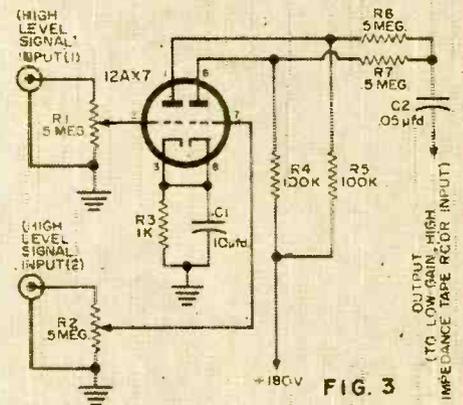


FIG. 3

Figs. 1, 2, 3, and 4 (top to bottom) are schematic diagrams for the four types of mixers discussed. Circuit details are given in text. Construction data for circuit in Fig. 1 appeared in an earlier article in POPULAR ELECTRONICS (July, 1955, page 81).

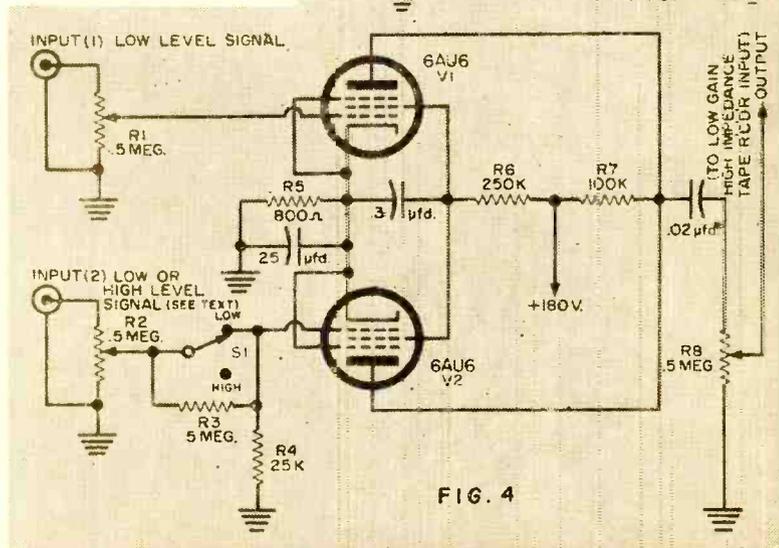


FIG. 4



R/C Triplex

Three Controls on One Channel

TO THE R/C FAN who has been flying single-channel models, the challenge of multiple controls is an enticing one. The "Triplex" circuit shown here was developed over a period of years and flown in a number of the author's models. "Triplex" provides three controls using any ordinary single-channel R/C receiver. Most "rudder-only" models may be easily modified to carry it.

The basic principle of this method is the use of a pulse system of proportional control. Addition of extra control features is accomplished in an uncomplicated manner. They are simple to maintain and also achieve a degree of "fail-safe" operation.

The R/C transmitter is keyed in the usual pulse method by a mechanical or electronic pulser, in which control stick movements vary the pulse length from no signal at one end of the range to a steady signal at the other. For the author's purposes, the movement of the stick is limited, so it doesn't quite reach the extreme positions. Two push-button switches have been added as shown in Fig. 1. One is a normally closed switch which gives "full off" when depressed; the other is a normally open switch which gives "full on" when depressed.

When the pulsed signal is received by receiver relay *RL1* in Fig. 2, the twin-coil


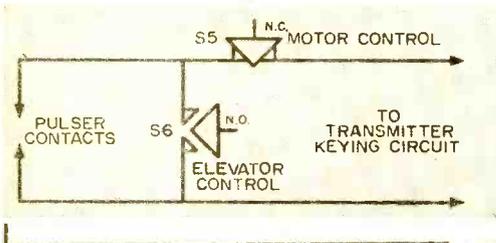


Fig. 1. Control switch hookup for proportional pulser. S5 and S6 (shown on top of unit at right, which was built by the author) are normally closed for motor control and normally open for elevator control.

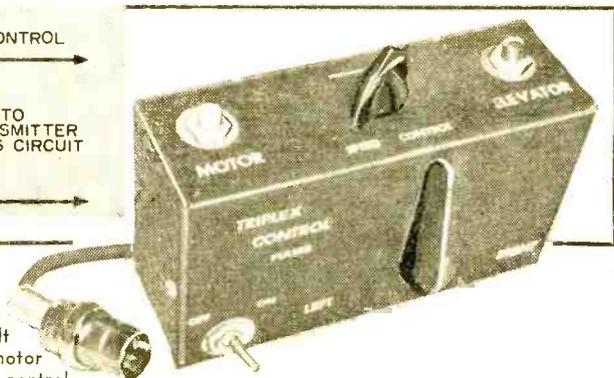


actuator displaces the rudder in proportion to the pulse rate. At the same time, *RL2* is keyed, which in turn keys *RL3* and *RL4*. Relays *RL3* and *RL4* are delayed for about one-half second by the 50- μ fd. capacitors *C1* and *C2*. A pulse rate above 150 pulses per minute will cause relays *RL3* and *RL4* to remain closed.

If a full-off signal of about $\frac{3}{4}$ -second duration is sent via *S5* (Fig. 1). *RL3* opens after a $\frac{1}{2}$ -second delay period and keys the motor control escapement. If the motor control is an escapement-operated air-bleed valve, then holding the full-off signal for several seconds will cut the motor. And since the continuity of the actuator is broken, the rudder will be left in neutral position. This prevents the model from a failure in flight due to the interruption of the radio signal in some manner (such as transmitter failure or flying out of range).

Similar action occurs in *RL4* when "full-on" is sent via *S6* in Fig. 1 to operate the elevator escapement. A four-position escapement is used in this case to give half positions. The rudder control will give maneuverability while the elevator is in any position.

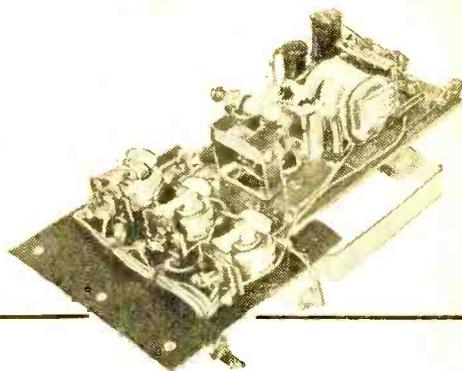When a full-on signal is sent, the rudder again falls to a neutral position after the first $\frac{1}{2}$ -second. If you have interfering ra-



The receiving unit is mounted as an extension of the chassis of the McNabb 465-mc. receiver.

PARTS LIST

- B1*—15-volt hearing-aid battery (Eveready #411 or one-ounce equivalent)—see text for other battery voltages
- C1, C2*—50- μ fd., 25-d.c.w.v. electrolytic capacitor (Aerovox Bantam SRE)
- RL1*—Receiver relay (part of receiver)
- RL2*—Neomatic or similar subminiature relay, about 300 ohms
- RL3, RL4*—Neomatic or similar subminiature relay, 5000 to 10,000 ohms
- S1, S2, S3, S4*—Miniature slide switches
- S5*—Push-button switch, normally closed
- S6*—Push-button switch, normally open

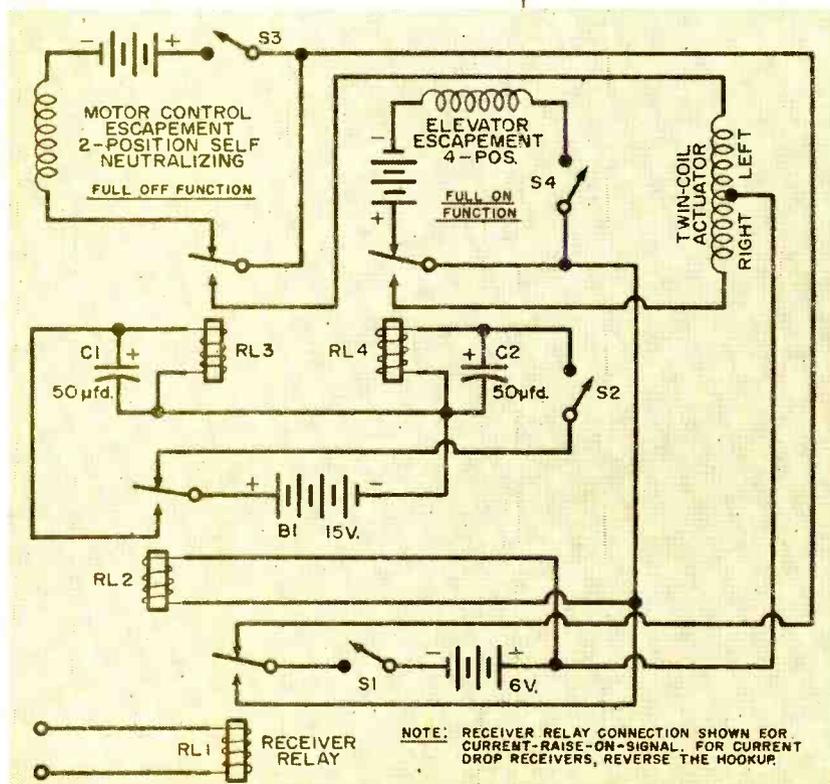


Fig. 2. Schematic diagram of "Triplex" control system. Component values are given in parts list above. See text for details of motor control and elevator escapements, actuator and pulser. Note that all switches are shown open in this diagram; they would be closed for normal operation.

dio signals present, simply switching off the elevator with S_4 will allow you to fly with only rudder and motor control. The single effect of an interfering signal will then be to return the rudder to neutral.

Since the "Triplex" is to be added to your present equipment, the method of mounting and installation is up to you. The photo shows a McNabb Citizenship 465-mc. receiver, with the extra components mounted on a Micarta extension to the chassis.

Any sensitive relay with coils of 5000-10,000 ohms can be used for RL_3 and RL_4 with the delay circuits shown; I used the Neomatic 7250-ohm subminiature type in this original unit. It may be necessary to adjust the value of capacitors C_1 and C_2 and the spring tension of the relays to give the required delay. The keying relay in this

circuit is a Neomatic with a 300-ohm coil, employed in conjunction with an actuator using 6 volts through 20-ohm coils. Be certain that the keying relay will close at the lowest voltage used to operate the actuator.

The escapements will determine battery voltage for the elevator and motor controls. Do not employ the same battery for both escapements or tap into the actuator battery. Use a 15-volt Eveready #411 battery or a one-ounce equivalent to power the delay relays. I recommend a twin-coil activator and a fully variable pulser. Since an elevator is a much larger load than a rudder, use a heavy-weight escapement and try balancing the elevator.

All of the components may be purchased from firms which specialize in R/C equipment.


-30-

Novel Probe Adds Range to Your VOM

MOST ELECTRONIC experimenters have used the temporary hookup illustrated in Fig. 1 to measure very high resistance values. With an auxiliary B battery and multiplier resistor, the top indication on the ohm scale of a VOM is multiplied ten times. Thus, resistance values up to 200 megohms can be measured provided that values up to 20 megohms could be measured without the external hookup.

While it is very useful to be able to measure high values of resistance, an ex-

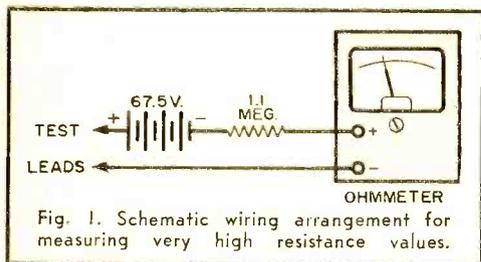ternal hookup is awkward and inconvenient. The obvious need for a compact and convenient ohmmeter multiplier can be met with miniature transistor batteries. Such a probe can be made completely self-contained and as convenient to use as the conventional test lead.



ternal hookup is awkward and inconvenient. The obvious need for a compact and convenient ohmmeter multiplier can be met with miniature transistor batteries. Such a probe can be made completely self-contained and as convenient to use as the conventional test lead.


The Futuramic Co. has announced the availability of a high-ohm probe utilizing the arrangement shown in Fig. 1. It can be used with most popular types of VOM's which have a 12-ohm center-scale indication and an $R \times 10,000$ ohm range with an internal $7\frac{1}{2}$ -volt ohmmeter battery.

The battery complement of the probe comprises three Mallory Y-15 transistor packs. Because the current drain is very small, battery life is long. However, after extended service, it will be necessary to

replace the batteries eventually. This point is reached when it is no longer possible to zero the pointer on the ohmmeter scale by adjustment of the "zero ohms" control of the VOM.

In effect, the high-ohm probe provides an additional range on the ohmmeter. The probe converts the $R \times 10,000$ range to an $R \times 100,000$ range. With the probe plugged into the VOM in place of the conventional test lead, a reading of "10" on the ohmmeter scale indicates a resistance value of 1,000,000 ohms; a reading of "1000" indicates a resistance value of 100 megohms.

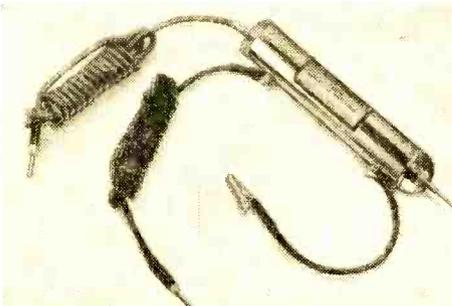The high-ohm probe finds valuable application in radio and television servicing, and in the electrical and industrial-electronic fields. A refrigeration service engineer is often required to test hermetic compressor-motor assemblies for leakage ("grounds"). Although a VTVM can be used directly to measure resistance values





up to 100 megohms (a commonly accepted limit), most technicians prefer a VOM because it requires no source of external power and is simpler to operate. By the use of a high-ohm probe, a valid test of the compressor-motor assembly can be made with a VOM.—Robert G. Middleton

A "First" Project—

Putting Together a Clock Radio

By ALLEN C. TRAINER

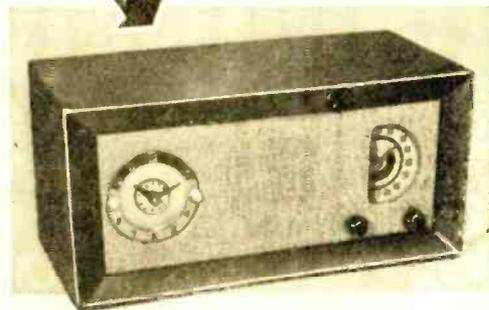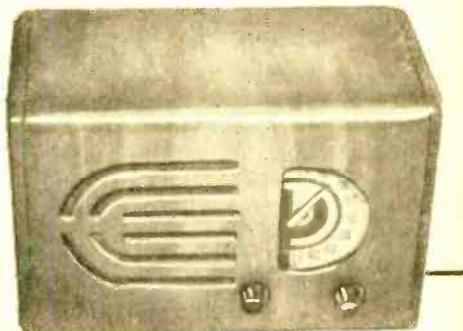Combine an old AM receiver with a clock timer as a start in radio



IF YOU FEEL that you don't know enough about electronics to tackle a resistor-and-capacitor project, try this ordinary conversion job. The project just consists of building a box to house an electric clock and AM radio, and of wiring the radio line cord to the clock. Any old table-model radio will do, and a clock timer can be purchased from a number of radio supply mail order houses for approximately four dollars.

Dimensions are not given for the new cabinet, because each dimension depends upon the size of the radio chassis. The easiest way to figure the size is to measure


the old cabinet and add sufficient length to one end to include the clock. Then cut the cabinet pieces to size. Be sure to figure the thickness of the top and bottom pieces when determining the over-all height.


Cut all the pieces to size and make a trial assembly of the parts without fasteners. Now place the radio chassis on the bottom piece and hold the front panel in position, then scribe the outline of the dial assembly and the control shafts. Next, hold the clock in position on the front panel, centering it between the top and bottom, and scribe the outlines of the clock face.

Remove the front panel and cut out the openings with a coping saw. Again place the panel in position and make sure that the dial and shafts, and the clock face, will fit through the openings.

Fasten a grille cloth to the front panel by tacking the cloth near the edges of panel face. In this position, the tacks will be covered by the molding strip. Puncture the cloth in the center of the dial and clock face openings, and make several cuts from the center to the edge. Fold the resulting wedge-shaped pieces into the open-

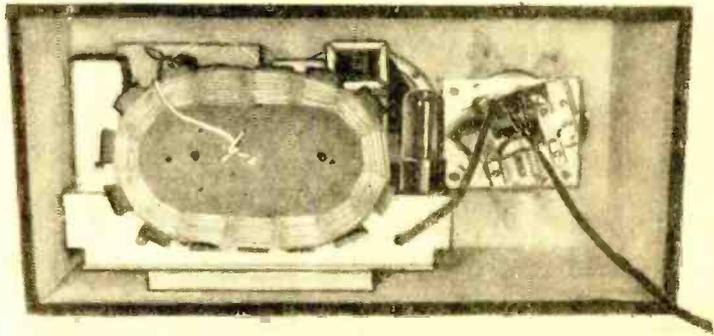Clock mounting position and wiring are shown in rear view of completed clock radio at the right. Above, left, is a front view of the new cabinet containing both the electric clock and the original AM radio (above, right).



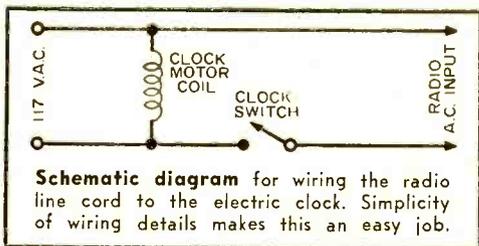

ings and tack the material to the back of the panel. This procedure will provide a cloth covering over the edges of the opening. Punch holes for the radio setting control shafts; the knobs will cover the openings.

Assemble the cabinet, using nails, or screws and glue. Always make sure that the radio chassis and clock are properly aligned.

Use finishing nails to fasten the molding strips to the front of the cabinet, and countersink the nails. Fill the nail holes and any cracks in the cabinet with wood putty and sand the whole cabinet. To finish the cabinet, use two coats of clear

shellac or some other filler, and a final coat of enamel or paint—choose a color to fit in with the furnishings of the room. It is a good idea to attach rubber feet, or glue felt, to the bottom of the cabinet to prevent scratching or marring other furniture. Suitable rubber feet are available at radio supply houses or hardware stores.

Place the radio chassis and the clock in their mounting positions and check the length of the radio a.c. line cord from the radio chassis to the clock switch contacts and motor coil. Cut the radio line cord and solder one radio lead to one clock switch contact and the other lead to one of the motor coil terminals. Solder a jumper from the remaining switch contact to the remaining motor coil terminal, and solder the line cord wires to the motor coil terminals. Secure the line cord to the inside of the case to relieve the strain on the soldered joints.

Now, plug the line cord into an outlet and see that the clock runs. Turn on the radio, and turn the clock setting knob until the switch contacts close. The radio should operate normally.

-30-

The Third Hand You Have Often Wanted

AN UNUSUAL—but indispensable—tool for the electronics worker can be a pair of "pliers" commonly used by a surgeon for clamping off arteries to prevent bleeding. The "forcep hemostat" has been found, by those who have tried it, to be the third hand that you may have often wished you had.

Such hemostats are made of fine surgical stainless steel and are practically indestructible. They are resistant to solder and soldering acids and fluxes. The beautiful feature which makes them shine is the locking device on the handles. Snap these little wonders on a piece of material and they hold it all by themselves. No help wanted!


There are many different sizes and shapes. My experience has proven, however, that the 6¼" straight model is the best size because of its holding power and capacity. The smaller models are a little too delicate and the larger models just a little husky. Model WW-150, shown in upper right-hand corner of photograph with a nut in its jaw, is available from Murray and Baumgartner Surgical Instrument Co., 5 West Chase St., Baltimore, Md., for \$4.00, f.o.b. Baltimore.

In use, hold the hemostat in your hand, lay it off the edge of

the workbench, or clamp the handles in a bench or drill vise. For the man who employs a soldering gun, it is the answer to that awkward feeling you get when working on small or subminiature parts. Such a portable "vise" is tops for holding two or more wires together when you are soldering in tight spots.

Keep a close watch on visitors when they start fondling your hemostat and you see that faraway gleam in their eyes. They are probably thinking: "Boy, could I use these when I . . ."

—Clyde D. Adams

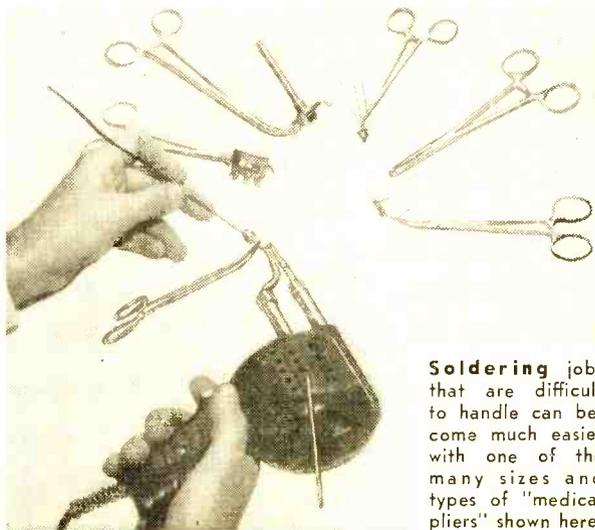

Soldering jobs that are difficult to handle can become much easier with one of the many sizes and types of "medical pliers" shown here.

Tuning the Short-Wave Bands

=with Hank Bennett

THIS month we are going to forego our usual visit into the listening post of one of our P.E. reporters and, instead, make a short trip to the Island of Haiti and the control room of *Radio Commerce* there. Our guide through the station is engineer Jan-Claude Bance. Mr. Bance, in addition to helping put the signals of *Radio Commerce* onto the air waves, can also be



Jan-Claude Bance is seated at the controls in one of the studios of Radio Commerce, Haiti.

heard operating his own amateur radio station, HH2JC.

Radio Commerce operates on three frequencies: 1080 kc. in the broadcast band; 6091 kc. in the 49-meter s.w. band; and 9485 kc. in the 31-meter s.w. band. For the medium-wave outlet, the power is 1000 watts; for the short-wave xmtrs, the power is 7500 watts. The call letters for the various outlets are 4VA (1080 kc.), 4VB (6091 kc.), and 4VC (9485 kc.). Mr. Bance tells us that all equipment has been manufactured by RCA and that the wiring of the station was done by engineer Edouard Gentil, a native of Haiti.

The antenna for m.w. station 4VA is a vertical, 200' high, with a transmission line of 230 ohms. This xmtr can be heard, with a good signal, without interference, for 200 miles. Your Editor is willing to bet that some of our readers in the southern states could hear 4VA without much trouble, on the nights when the Cubans and other

West Indian stations are coming through. The antennas for 4VB and 4VC are both horizontal Delta arrays, 80' high for 31 meters and 60' high for the 49-meter outlet.

Radio Commerce can be heard daily as follows: at 0630-2230 on 1080 kc.; at 0630-0930 on 9485 kc.; and at 1700-2230 on 6091 kc. In addition, a program in English is heard Sundays at 1700-1900. Two widely reported and well-heard programs in the English xmsn are "Glimpses of Haiti" at 1800-1830 and "Paris Star Time" at 1830-1900.

Our thanks go to Mr. Bance for the pleasant trip around the station, and to Herb Brier, of the *Transmitting Tower*, for his assistance in preparing this story.

Random Notes. Congratulations are in order for the Universal Radio DX Club for the "New Look" in their club Bulletin. By the same token, Roger Legge and Stewart West, of the Newark News Radio Club, are to be commended for the excellent "Band Survey" that they are writing monthly for the NNRC Bulletin.

Joel Richmond and Port Baughman wrote in to tell us that *Radio Netherlands*, Hilversum, is offering a pictorial map folder of the Netherlands and a folder entitled "Improving Shortwave Reception" (the latest edition, with more antenna information) to anyone requesting them.

For those who would like to experiment

(Continued on page 121)



Joseph Montoya, San Dimas, Calif., listens with a Hammarlund HQ-140X receiver. His antenna is a vertical steel rod, 70 feet off the ground.

Electronics

Comes to


Drive-In

WHILE a great many of the country's drive-in eateries still follow the conventional pattern of serving their hungry customers by way of attractive "car-hops," in view of the shortage of these girls some restaurant owners have enlisted the aid of electronics.

In the photo at right is a gadget that will accept and relay the order of a customer who is comfortably seated in his or her car on the drive-in lot. All the customer need do is read an illuminated menu, press a button, and place his food order via a two-way speaker system.

The dulcet tone at the other end of the system accepts the order and relays it to the kitchen. When the food is ready, the "glamor-gal" car-hop delivers it.

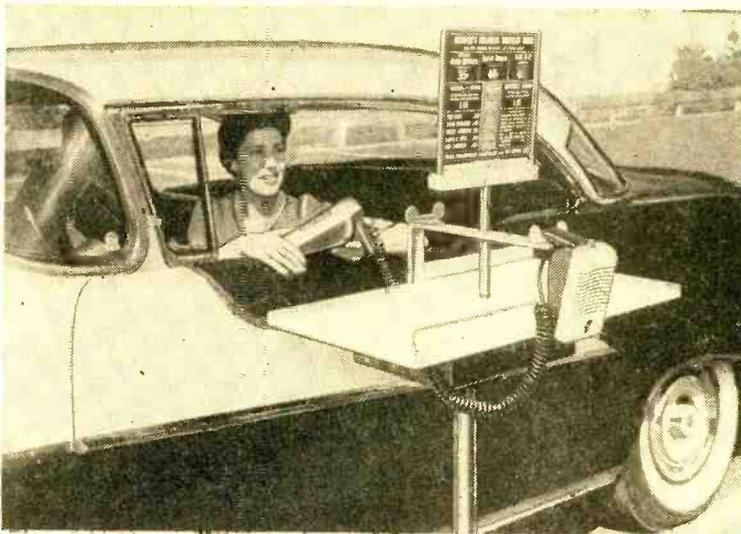This electronic gadget does away with the need for an estimated 50% of the fast-



When the customer places an order for "hamburger with," this robot "car-hop" accepts the order, relays it to the kitchen, and delivers the food.


stepping females. And when the device isn't in use for placing food requests, it dispenses a steady stream of music from a record player loaded to the gills with the waxings popularly demanded by teen-agers.

True, the intercom hasn't the glamor of a slender figure or a well-turned ankle or a welcoming smile. Nor does it beseech in twinkling soprano: "What'll you have?" But the robot-like efficiency of this electronic car-hop makes up for its lack of more personal attractions. —Stanley Clark

Metal Monitor

THE "Metal Monitor" checks metals without laboratory analysis. It can identify ferrous and non-ferrous metals by comparative testing with known samples, and it sorts mixed metals of unknown character into homogenous groups for further testing. Manufactured by Brush Electronics Company, division of Clevite Corporation, Cleveland, Ohio, it will check stock, parts in process or finished products for many characteristics—hardness, heat treatment, metallurgical structure, uniformity, plating thickness and plating adhesion.

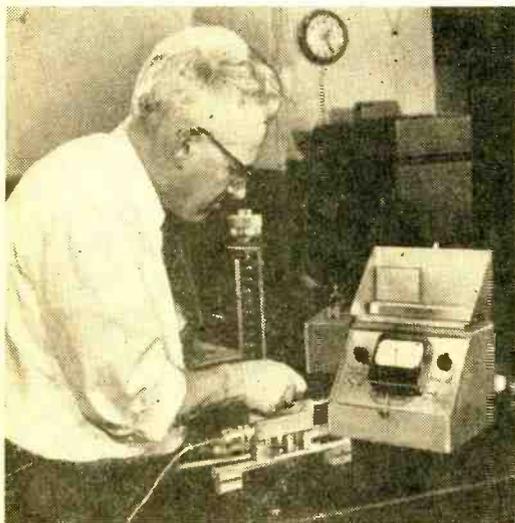In operation, an electrode (with a self-heating element) is placed in contact with the metal to be tested. Voltage generated by this contact is amplified and transmitted to a meter on the Metal Monitor. The reading is then compared to readings obtained from samples whose compositions and metallurgical characteristics are known. As many as 3000 pieces can be checked in an hour.



Checking metal parts for proper heat treatment is one of the many duties of the "Metal Monitor." Easy to operate, and requiring no special or technical skill, it is portable and can be moved to the job.


*You're invited
to a
Launching!*



**SPECIAL OFFER TO
READERS OF POPULAR ELECTRONICS**

8 months of POPULAR BOATING only \$2.00

(a \$3.45 single copy value!)

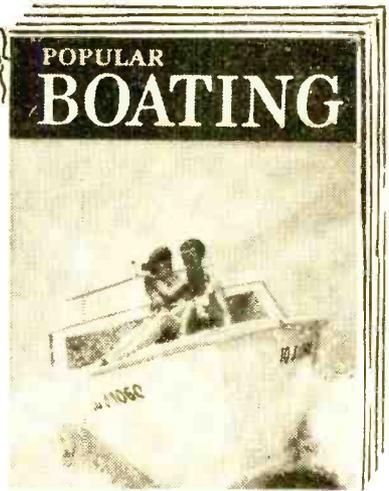

This is your special invitation to "sign on" as a Charter Subscriber to POPULAR BOATING—the new Ziff-Davis monthly for *everyone* who enjoys life on the water.


Beginners and "old salts" . . . inboard, outboard and sailing enthusiasts and their families—all are finding POPULAR BOATING the most enjoyable magazine in the boating world. Copies of the first big issue, on sale only a few days, have become hard to find because of their tremendous demand.

POPULAR BOATING, the first new major boating magazine in more than a generation—brings a completely fresh approach to the entire world of boats—from dinghy to power cruiser.

Published by the same company that has made POPULAR ELECTRONICS tops in its field, POPULAR BOATING features money-saving how-to articles that point the way to more fun, greater safety afloat . . . new construction ideas . . . information on repairing, improving, fitting out your boat . . . monthly classes on seamanship and boat handling by expert boatmen . . . exciting boating yarns that will transport you to every corner of the world where there's fun and adventure on the water . . . regular features on new products, junior activities, maintenance, fishing, free aids to better boating, and much more!

Here are just a few of the exciting articles in POPULAR BOATING's first issue:

- **BREAKING THROUGH THE "WATER BARRIER"**—America's best-known racing writer, Hank Bowman, describes the perils of high speeds afloat.
- **SHOULD YOUR FIRST BOAT BE POWER OR SAIL?**—Two top boating writers defend their favorite craft in a hot debate.
- **OUTBOARDS UNLIMITED**—There's no limit to the fun outboarding offers. Here's how to enjoy it more fully!
- **GUY LOMBARDO'S GREATEST BOATING MOMENTS**—In this exclusive article, the famed musician and boatman recalls the most thrilling moments in his racing career.
- **ANN DAVISON'S NEXT BOATING VENTURE**—An exclusive first-hand report by the only woman ever to sail the Atlantic alone!

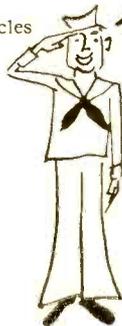

This first issue is already a complete sellout at many newsstands. For POPULAR BOATING offers readers far more than any other publication in the field . . . yet costs *less*. At regular rates, POPULAR BOATING sells for 35c on newsstands (Special Show Numbers: \$1.00) and \$4.00 a year by subscription.

SPECIAL \$2.00 OFFER

However, as a regular POPULAR ELECTRONICS reader, you can climb aboard POPULAR BOATING for a trial cruise at a not-to-be-repeated introductory rate—8 months for only \$2.00. You get the big \$1.00 January Boat Show Issue at no extra cost, too! All told, by taking advantage of this offer you save a whopping 42% over established rates.

And if you act now, your name will be entered on our list of Charter Subscribers. You'll be sent a special Charter Subscription Certificate. But most important—you'll be 100% sure of getting your copy of the very first issue of POPULAR BOATING. Volume 1, Number 1, sold out at many newsstands, is a "collector's item" in many homes.

But we have put aside a small supply for Charter Subscribers—and will start your subscription with the first copy as long as our supply lasts.

So use the coupon below to subscribe now. If you want us to begin your subscription with the very first issue—already on sale—check the special box. See how much boating enjoyment \$2.00 buy you in new exciting POPULAR BOATING!

**Welcome aboard as a
Charter Subscriber!
Fill out and
mail this coupon TODAY!**

POPULAR BOATING 366 Madison Avenue
New York 17, N. Y.

CHARTER SUBSCRIPTION ORDER FORM

Yes, please enter my Charter Subscription to POPULAR BOATING—at the special rate of eight months for only \$2.00. Also send me my Charter Subscription Certificate. My payment is enclosed.

Name.....
Address.....
City..... Zone..... State.....
PE-12-5

Please start my subscription with Volume 1, Number 1, if possible.

I've bought the first issue at a newsstand. Begin my subscription with the second (November) issue.


A NEW MAGAZINE BY THE PUBLISHERS OF POPULAR ELECTRONICS

November, 1956

93

build your own

HEATHKIT

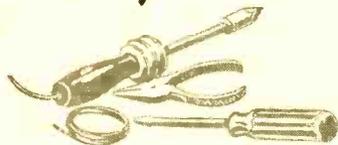


... and have fun doing it!

Circuit boards cut assembly time in half

1% resistors insure instrument accuracy.

High impedance and high sensitivity.

Attractive styling—functional design.

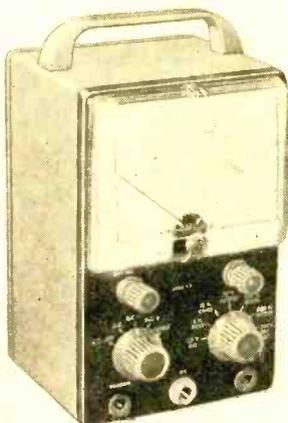

MODEL V-7A

\$24⁵⁰

SHIPPING WT. 7 LBS.

controls. Employs a 200 microampere meter for indication. Input impedance is 11 megohms.

Etched metal, pre-wired circuit boards insure fast, easy assembly and result in reliable operation. Circuit board is 50% thicker for more rugged physical construction. 1% precision resistors used for utmost accuracy.

etched circuit vacuum tube **voltmeter kit**

In addition to measuring AC (rms), DC, and resistance, the modern-design V-7A incorporates facilities for peak-to-peak measurements. These are essential in FM and television servicing.

AC (rms) and DC voltage ranges are 1.5, 5, 15, 50, 150, 500, and 1500. Peak-to-peak AC voltage ranges are 4, 14, 40, 140, 400, 1400, at 4,000. Ohmmeter ranges are X1, X10, X100, X1000, X10K, X100K, and X 1 megohm. A db scale is also provided. Polarity reversing switch provided for DC measurements, and zero center operation is within range of the front panel

Heathkit

HANDITESTER KIT

The Model M-1 measures AC or DC voltage at 0-10, 30, 300, 1000, and 5000 volts. Measures direct current at 0-10 ma and 0-100 ma. Provides ohmmeter ranges of 0-3000 (30 ohm center scale) and 0-300,000 ohms (3000 ohms center scale). Features a 400 microampere meter for sensitivity of 1000 ohms per volt. Handy and portable. Will fit in your coat pocket, tool box, glove compartment, or desk drawer.



MODEL M-1
\$14⁵⁰

Shpg. Wt. 3 lbs.

Heathkit VOM KIT

20,000 ohms/v. DC and 5,000 ohms/v. AC sensitivity. Ranges (AC and DC) are 0-1.5, 5, 50, 150, 500, 1500, and 5000 v. Direct current ranges are 0-150 ua, 15 ma, 150 ma, 500 ma, and 15 a. Resistance ranges provide center-scale readings of 15, 1500 and 150,000 ohms. DB ranges cover -10 db to ± 65 db.

Features 4 1/2" 50 ua meter and 1% precision resistors.



MODEL MM-1

\$29⁵⁰ Shpg. Wt. 6 lbs.

HEATH COMPANY A Subsidiary of Daystrom, Inc.
BENTON HARBOR 5, MICHIGAN

Heathkit 3" oscilloscope kit

ETCHED CIRCUIT



MODEL
OL-1

\$29.50 Shpg. Wt.
14 Lbs.

Push-pull vertical and horizontal amplifiers.

Light weight and small size for portability.

Good sensitivity and broad frequency response.

Etched metal circuit boards for simplified assembly.

Attractive panel and case styling.

This compact little oscilloscope is just the ticket for use in the ham shack or home workshop. Measures only 9½" H. x 6½" W. x 11¾" D. Weighs only 11 pounds.

Employing etched metal circuit boards, the Model OL-1 features vertical response with in ± 3 db from 2 cps to 200 kc. Vertical sensitivity is 0.25 volts rms per inch, peak-to-peak, and sweep generator operates from 20 cps to 100,000 cps. Provision for direct RF connection to deflection plates. Incorporates many features not expected at this price level. The 8-tube circuit features a type 3GP1 cathode ray tube.



Cathode-follower output for isolation.

No oscillator calibration required.

Covers 160 kc to 220 mc (including harmonics).



Heathkit signal generator kit

This signal generator covers 160 kc to 110 mc on fundamentals in 5 bands. Calibrated harmonics extend its usefulness up to 220 mc. The output signal is modulated at 400 cps, and the RF output is in excess of 100,000 microvolts. Output controlled by both a continuously variable and a fixed step attenuator. Audio output may be obtained for amplifier testing.

MODEL
SG-8

\$19.50

Shpg. Wt.
8 Lbs.

Audio output may be obtained for amplifier testing.

This is one of the biggest signal generator bargains available today. The tried and proven Model SG-8 offers all of the outstanding features required for a basic service instrument or for use in experimenting in the home workshop. High quality components and outstanding performance. Easy to build, and no calibration required for ordinary use.

Heathkit grid dip meter kit

This extremely valuable instrument is a convenient signal source for determining the frequency of other signals by the comparison method. Range is from 2 mc to 250 mc. Uses 500 ua meter for indication, and is provided with a sensitivity control and headphone jack. Includes prewound coils and rack. For hams, experimenters, and servicemen.



MODEL GD-1B

\$19.50

Shpg. Wt. 4 Lbs.

Heathkit ANTENNA impedance meter kit


Used in conjunction with a signal source, the Model AM-1 will enable you to measure RF impedance. Valuable in line matching, adjustment of beam and mobile antennas, etc. Will double as a phone monitor or relative field strength indicator. A 100 micro-ampere meter is employed. Covers the impedance range from 0 to 600 ohms. An instrument of many uses for the amateur. Easily pays for itself through the jobs it will perform.



MODEL
AM-1

\$14.50 Shpg. Wt.
2 Lbs.

HEATH COMPANY A SUBSIDIARY OF
DAYSTROM, INC.
BENTON HARBOR 5, MICHIGAN

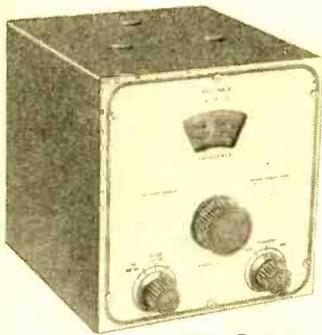

MODEL VF-1 **\$19.50**
Shpg. Wt. 7 Lbs.

a socket on the Heathkit Model AT-1 transmitter, or supplied with power from most transmitters.

Features illuminated and pre-calibrated dial scale. Cable and plug provided to fit crystal socket of any modern transmitter.


Heathkit

vfo

KIT

- ☆ 6AU6 electron-coupled oscillator.
- ☆ 0A2 voltage regulator tube for stability.
- ☆ Smooth-acting illuminated dial.
- ☆ Easy to build and attractively styled.

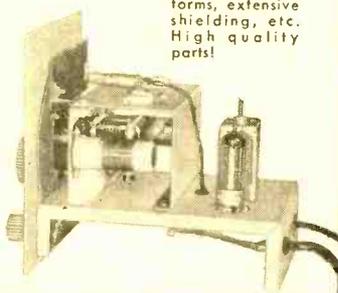Extra features include copper-plated chassis, ceramic coil forms, extensive shielding, etc. High quality parts!



SPECIFICATIONS:

RF Amplifier Power Input... 25-30 watts
Output Connection... 52 ohms
Band Coverage... 80, 40, 20, 15, 11, 10 Meters
Tube Complement:
5U4G... Rectifier
6AG7... Oscillator-Multiplier
6L6... Amplifier-Doubler

Heathkit CW amateur transmitter kit

This CW transmitter is complete with its own power supply and covers 80, 40, 20, 15, 11, and 10 meters. Incorporates such outstanding features as key-click filter, line filter, copper plated chassis, pre-wound coils, and high quality components. Employs a 6AG7 oscillator, 6L6 final amplifier. Operates up to 30 watts plate power input.


MODEL AT-1

\$29.50

Shpg. Wt. 15 Lbs.

Single-knob band-switching for 80, 40, 20, 15, 11 and 10 meters.
Plate power input 25-30 watts.

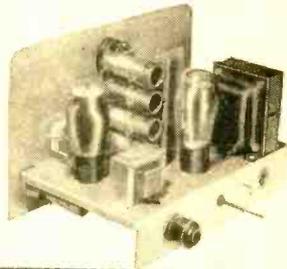
Panel meter monitors final grid or plate current.
Best dollar-per-watt buy on the market.



Slide-rule dial-electrical band-spread-ham bands marked.

Slug-tuned coils and efficient IF transformers for good sensitivity and selectivity.

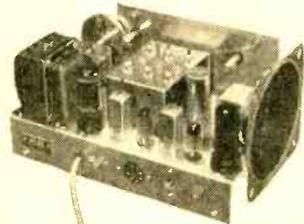Transformer-operated power supply for safety and high efficiency.



Heathkit

COMMUNICATIONS TYPE

all band receiver kit



\$27.95

MODEL AR-3
Shpg. Wt. 12 Lbs.

CABINET: Fabric-covered cabinet available. Includes aluminum panel, speaker grille, and protective rubber feet. Measures 12-1/4" W. x 8-3/4" H. x 7-3/4" D. No. 91-15. Shpg. Wt. 5 Lbs. \$4.50.

The Model AR-3 covers from 550 kc to 30 mc on 4 bands. Covers foreign broadcast, radio hams, and other interesting short wave signals.

Features good sensitivity and selectivity. Separate RF and AF gain controls—noise limiter—AGC—VFO, headphone jack—5 1/2" PM speaker and illuminated tuning dial.

SPECIFICATIONS:


Frequency Range... 550 kc to 30 mc on four bands
Tube Complement... 1—12BE6 oscillator and mixer
1—12BA6 IF amplifier
1—12AV6 second detector, AVC, first audio amplifier and reflex BFO
1—12A6 beam power output
1—5Y3 full wave rectifier

HEATH COMPANY A SUBSIDIARY OF DAYSTROM, INC.
BENTON HARBOR 5, MICHIGAN

TIPS and TECHNIQUES

HUM IN PHONO PICKUP

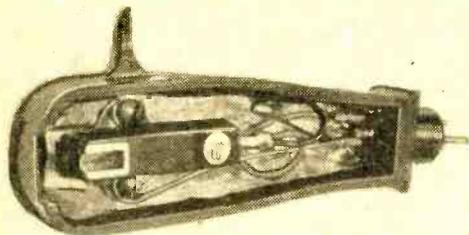Electrostatic hum develops sometimes in a phono system which uses a plastic tone arm and partially unshielded signal lead. Much, if not all, of this hum can be elim-




inated by lining the interior surface of the pickup end of the tone arm with heavy household aluminum foil, and then grounding the foil and the metal case or mounting of the cartridge to the braided shield of the pickup lead. —F.H.T.

NEW USE FOR OLD CONSOLE

Television sets and hi-fi equipment have relegated many an old console radio to the attic or junk-heap. With a little work, the cabinets of such sets can be re-done to provide a loud-speaker enclosure with a planter and lamp on top.

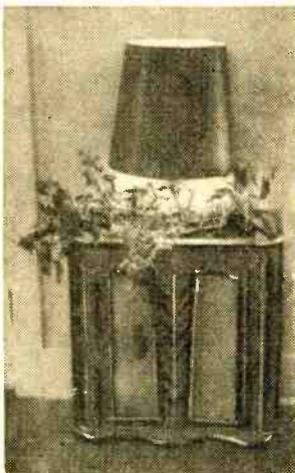To make the planter, cut carefully just below the holes that formerly accommodated the control shafts of the old set. Form a pan of galvanized iron and trim its top edges with copper or brass strips so that it fits snugly into the opened top of the cabinet. In this pan you may install your plants and even the base of a home-designed



lamp. And, if the rest of the unused area inside the cabinet is large enough, you can use it for mounting a hi-fi speaker. —O.W.


PORTABLE RADIO CHECKS DOORBELL

A portable radio set will pick up the pulses of radio frequency radiated by doorbell wires at the push button. If "hash" is heard in the portable when tuned to a weak station, you'll know that the bell or buzzer is working.

The idea is useful in repair of doorbells. There is no need to have someone upstairs inform the repairman if the bell or buzzer is functioning. The portable radio does the job, making the test for a working bell, buzzer, or door-opener a one-man proposition. —J.A.McR.

VERSATILE POWER TUBE SOCKETS

Different types of power tubes may be interchanged without revision in the filament voltage lines if the correct wiring is made at the tube socket. As many as 11 different types may be used on a 5-volt line. Wire together pins 5 and 6 to form one of the plate connections. Wire pins 3 and 4 for the other plate connection. Pin 8 serves as one side of the filament; pins 2 and 7—wired together—serve as the other side. The B-plus

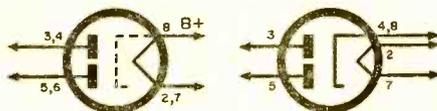

5-VOLT TYPE

6-VOLT TYPE

lead to the filter system must always come off pin 8. A socket wired in this manner will accommodate the following tube types: 5AX4GT, 5AZ4, 5R4GY, 5T4, 5U4G, 5V4G, 5W4, 5X4G, 5Y3G, 5Y4G, and 5Z4.

For 6-volt rectifiers, pin 3 serves as one plate and pin 5 as the other. Pin 2 is one side of the filament and pin 7 the other. Wire pins 4 and 8 together to form the cathode take-off. Such a socket will accommodate tube types: 6AX5GT, 6AX6GT, 6W5G, and 6X5.

In either case, just remember that the rating of the tube used must not be exceeded. —B.E.

DO NOT COIL TV LEAD-IN

When installing the flat twin-lead which serves as the lead-in from your TV antenna, there is a great temptation to leave considerable slack at the set to permit moving the TV for service access or changing its location in the room. If such slack is rolled up into a coil, there is apt to be a pronounced reduction in picture brightness—due to the loss of signal strength resulting from coupling effects between the coil turns. A good rule is to leave only enough

You Can Train at Home for Good Pay Jobs in RADIO-TELEVISION

Fast Growing Industry Offers Good Pay, Security, Bright Future

LESSON AND CATALOG FREE MAIL CARD



Training PLUS OPPORTUNITY is the ideal combination for success. Today's OPPORTUNITY field is Radio-Television. Over 125 million home Radios plus 30 million sets in cars and 40,000,000 Television sets mean big money, opportunity for trained Radio-Television Technicians. More than 4,000 Radio and TV Broadcasting stations offer interesting and important positions for technicians, operators. Color Television, portable TV sets, Hi-Fi, other developments assure future growth.




**J. E. SMITH
Founder**

Since 1914—for more than 40 years—N.R.I. has been training ambitious men at home in spare time for Radio-TV. Thousands of successful graduates say N.R.I.'s 50-50 training method is a fast, easy, effective way to higher earnings, desirable jobs. Planned experiments and practice bring basic principles, techniques to life right in your own home. Find out what dependable training can do for you.

You Learn by Doing—Get Practical Experience with Kits N.R.I. Sends

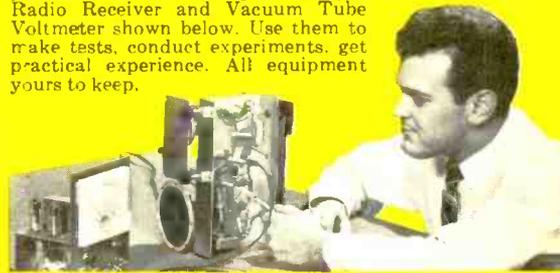Nothing takes the place of practical experience. As part of N.R.I. Servicing Course you build AC-DC Radio Receiver and Vacuum Tube Voltmeter shown below. Use them to make tests, conduct experiments, get practical experience. All equipment yours to keep.



Add to Your Income Starting Soon

Make \$10-\$15 a Week Extra Fixing Sets in Your Spare Time

Soon after enrolling, many N.R.I. students start earning extra money fixing neighbors' radio sets. Many earn enough extra to pay entire cost of course and provide capital to start their own full time Radio-TV business after getting N.R.I. Diploma. Mail Postage Free postcard for Sample Lesson. See how practical it is to learn at home. Get 64-Page Catalog, too. See equipment you get, opportunities in this growing field. Prices of N.R.I. Courses are low, terms easy.



Find Out What Oldest and Largest Home Study Radio-Television School Offers You

See Other Side
CUT OUT AND MAIL CARD NOW

N.R.I. TRAINED THESE MEN



Thanks N.R.I. for Good Start
—"Right now I am doing spare-time repairs on Radios and Television. Intend to go into full time servicing." **C. HIGGINS**, Waltham, Mass.



Engineer with Station WHPE
—"I operated a successful Radio repair shop. Then I got a job with WPAQ and now I am an engineer for WHPE." **VAN W. WORKMAN**, High Point, N. C.



Quit Job to Start own Business
—"I decided to quit my job and do TV work full time. I love my work and am doing all right financially." **W. F. KLINE**, Cincinnati, Ohio.



N.R.I. Course Started His Way up
—"I was a cab driver earning \$35 a week. Then I enrolled with N.R.I. Now I am a tester with TV maker." **J. H. SHEPHERD**, Bloomington, Indiana.

SAMPLE LESSON AND CATALOG BOTH FREE

**NO STAMP NEEDED!
WE PAY POSTAGE**

This card entitles you to Actual Lesson on Servicing, shows how you learn Radio-Television at home. You'll also receive 64-Page Catalog.

**NATIONAL RADIO INSTITUTE, Dept. D4
Washington 9, D. C.**


Please mail me the FREE sample lesson and 64-Page Catalog. (No Salesman will call.)

Name _____ Age _____

Address _____

City _____ Zone _____ State _____

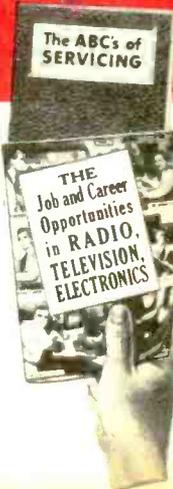Approved Member, National Home Study Council



Practice Servicing-Communications with Kits of Parts N.R.I. Sends



YOU BUILD AC-DC

Superhet Receiver

N.R.I. Servicing Course includes all needed parts. Get actual servicing experience practicing with this modern receiver.




YOU BUILD Signal Generator

You build this Signal Generator. Learn how to compensate high frequency amplifiers, practice aligning typical I. F. amplifiers in receiver circuits.

YOU BUILD


Broadcasting Transmitter

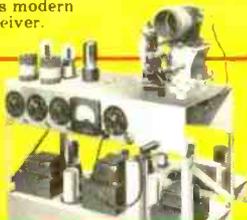As part of N.R.I. Communications Course you build this low power Transmitter, learn commercial broadcasting operators' methods, procedures.



YOU BUILD Vacuum Tube Voltmeter

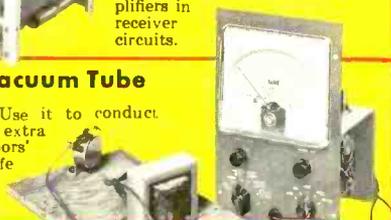Use it to conduct experiments; earn extra cash fixing neighbors' sets; bring to life theory you learn from N.R.I.'s easy-to-understand texts.



Radio-Television Can Give You a Good Job with a Future

N.R.I. Graduates do Important Work — Get Important Pay



Chief Engineer with Station

"I am Chief Engineer of Station KGCU. I have my own spare time business servicing two-way communications systems." R. BARNETT, Bismarck, N. D.



Paid for Instruments

"I am doing very well in spare time TV and Radio. Sometimes have three TV jobs waiting. Paid for instruments out of earnings." G. F. SEAMAN, New York, N. Y.



Has Own Radio-TV Business

"We have an appliance store with our Radio and TV servicing. During my Army service, N.R.I. training helped me." W. M. WEIDNER, Fairfax, S. D.

Here is a line of work that people respect—a vocation where you can advance, win a place for yourself, earn good pay and gain much personal satisfaction. And you can learn at home in your spare time. Smart fellows everywhere are using their spare time to develop new knowledge, new skills. They know it is the trained man who gets ahead, gets the better job, drives the better car, is respected for what he knows and can do.

Be a Skilled Technician

The technical man is looked up to. He should be. He does important work, gets good pay for it. Radio-Television offers that kind of work. There are more than 40 million Televisions, 150 million home and auto Radios. Millions more are sold each year. There are splendid opportunities for the man well trained in Radio-Television Servicing or Broadcasting. Micro-Wave Relay, Aviation and Police Radio, Two-Way Communications for buses, taxis, trucks, etc. are expanding—making more jobs, greater opportunity.

Tested Way To Better Pay

N.R.I. Training is practical, thorough. You get the benefit of N.R.I.'s 40 years experience training men for success in Radio-Television. N.R.I. training is backed by the record and reputation of the OLDEST and LARGEST home study Radio-TV school. Most successful N.R.I. men start without any knowledge of Radio, many without a high school education. Find out what Radio-Television training can mean to you. Make a decisive move today toward becoming one of that select group—a Radio-TV Technician. Send for Actual Lesson and 64-Page Catalog, both FREE. NATIONAL RADIO INSTITUTE, Dept. D4, Washington, D. C.



See Other Side



FIRST CLASS

Permit No. 20-R
(Sec. 34.9, P. L. & R.)
Washington, D. C.

BUSINESS REPLY CARD

No Postage Stamp Necessary If Mailed In The United States

POSTAGE WILL BE PAID BY

NATIONAL RADIO INSTITUTE

16th and U Sts., N. W.

Washington 9, D. C.


**SAMPLE LESSON
and CATALOG
Both FREE**

**Cut out and mail
Postage Free Card**

slack to permit moving the set a short distance, allowing the slack to hang uncoiled. If the set is to be relocated elsewhere in the room, it is no problem to splice on enough additional twin-lead as required. —E.F.C.


INCREASING B-BATTERY LIFE

A portable, dry-battery radio receiver may oscillate or howl as its batteries age. This condition is often due to the B battery's internal resistance, which increases quite rapidly as the battery nears the end of its useful life. The increased battery resistance permits positive feedback to occur across one or more of the receiver circuits. Frequently, in such cases, you can obtain a few more "howl-less" hours of operation from your receiver by connecting a .02- μ f.d. mica or ceramic capacitor across the B battery terminals. The same capacitor may work as well if a similar condition develops in a transistor receiver. —F.H.T.

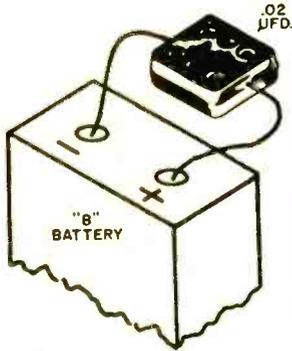

DOUBLE-CHECK FILAMENTS

When checking filament circuits with an ohmmeter, don't let the low resistance of the power transformer filament winding mislead you into thinking the winding is shorted. This winding carries the relatively heavy filament or heater current, which may be a couple of amperes, and is therefore made with heavy wire. Also, the step-down ratio from the house 117-volt a.c. line to the low heater voltage requires only a few turns on this winding as compared

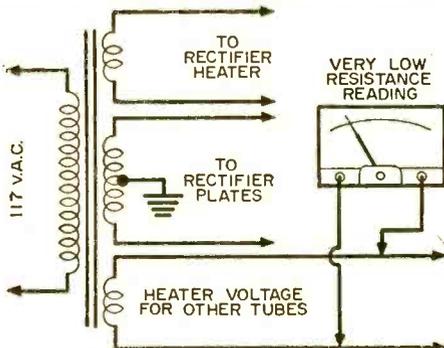

to the 117-volt winding. The small number of turns of heavy wire account for the very low resistance—which is often less than 1 ohm. —E.F.C.



Cat. No. PC-200
\$9.00
 without tubes
 (suggested net price)

Here's where the fun begins!

Centralab Ampec® 3-stage P. E. C.* Audio Amplifiers

You can use them to build all sorts of exciting, miniature projects — pocket radios, mike preamplifiers, signal tracers, portable megaphones, phonograph pick-ups, hearing aids, model controls—even stethoscopes

Yes, sir, you can really have a "picnic" with Ampec. It's the highest form of Printed Electronic Circuit and provides complete electrical service from input to output. Wiring, capacitors, resistor, and tube sockets are bonded to a single, master plate.

Even with tubes, Model 2 Ampec is smaller than a book of matches. Model 3 is smaller than a postage stamp—and it has a tone circuit, besides!

Ask your Centralab distributor to tell you more about Ampec. And send coupon for Booklet 42-142 with specifications and applications.

Centralab

*Trademark
 Y-1655B

A Division of Globe-Union Inc.
 994K E. Keefe Avenue, Milwaukee 1, Wisconsin

Send me free Booklet 42-142.

Name.....
 Address.....
 City..... Zone..... State.....

Give your
friends
**POPULAR
ELECTRONICS**
this Christmas



What more thoughtful gift to friends than a subscription to **POPULAR ELECTRONICS** this Christmas!

You'll be giving 12 full months of pleasure—all the enjoyment and fun that the wonderful world of electronics offers.

SPECIAL GIFT RATES

First 1-year gift subscription	\$3.00
Second 1-year gift subscription	\$2.00
Each additional 1-year gift	\$1.50

As you have no doubt noticed, **POPULAR ELECTRONICS** has raised its price to 35¢ per copy—because of increased paper and printing costs—effective with this issue.

Because **POPULAR ELECTRONICS** subscription rates will now be raised to \$4.00 per year, this very favorable Christmas offer can be kept open for a limited time only. We urge you to send in your order at once.

Each gift subscription will be announced by an attractive card naming you as donor.

Fill in and return the prepaid, self-addressed envelope facing this page for your own and gift subscriptions. List additional gift orders on an extra sheet of paper.

(Your own new or renewal subscription may be included.)

POPULAR ELECTRONICS

366 Madison Ave. New York 17, N. Y.

TOOLS
and
GADGETS



HOLE-SAW WITH SLUG-EJECTOR

Up to seven sizes of circular holes can be cut with the "Arco Hole-Saw," which features an automatic "slug-ejector." Powered by any electric drill, drill press, lathe or motor, it is said to cut perfect holes in wood, wallboard, plastics, sheet metal, etc. The exclusive automatic slug-ejector pops



out discs immediately, considerably decreasing working time.

No. 650, which retails at \$6.50, cuts 1", 1 1/4", 1 1/2", 1 3/4", 2", 2 1/4" and 2 1/2" holes through any 3/4" stock. The seven circular saw blades slip into grooves of tool head and are easily exchanged; a safety lock screw prevents blades from "jumping out." No. 600 (\$4.95) cuts 1", 1 1/2", 2" and 2 1/2" holes. (Arrow Metal Products Co., 140 West Broadway, New York 13, N. Y.)


TV BIAS SUPPLY

Providing any voltage from 0 to 18, either positive or negative, the "Align-o-Pak" Model BE3 TV bias supply is an im-



proved version of the Model BE2—which provided only 10 volts. The BE3 was designed to include high voltages recommended by some TV manufacturers on

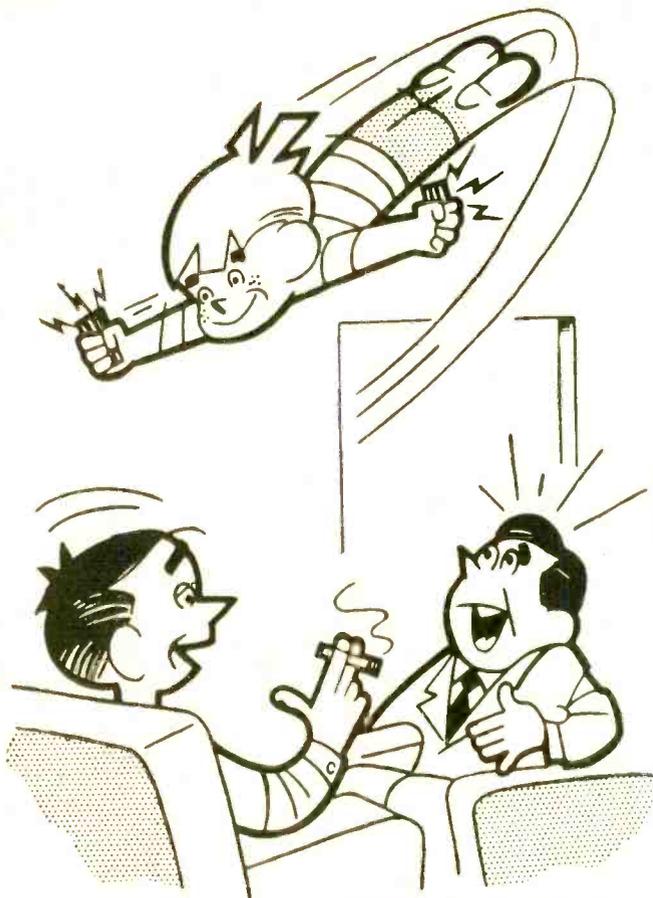Always say you saw it in—**POPULAR ELECTRONICS**



" I DUNNO... SAYS HE DOES IT WITH BURGESS BATTERIES "

LASTING POWER

UNIFORM DEPENDABILITY

STEEL CLAD GUARANTEE



Powerful, fresh Burgess batteries are out standing for dependable long life and uniform high quality They're guaranteed! Ask for them!



MAKERS OF THE FAMOUS RADAR-LITE

WONDERFUL NEW CHRISTMAS GIFT

PERSONAL POCKET RADIO

This is no ordinary pocket radio—it is equivalent in sensitivity to most household radios—tuggedly built (not a toy)—beautiful case. Look at the 3 tube superhet construction—1K5 Disc. and mixer, 174 IP Amp., 1U5 Det., AVC, 1st Audio. Built-in, supersensitive, high Q, ferrite antenna. Tunes broadcast with Comelrad frequencies plainly designed for extra earphone.

cast band (530 to 1650 marked) Case 1 1/4" x 3 1/2" x 5 5/8". Equipped with B battery and earphone. You'll use this radio every day—take it with you everywhere you go—perfect for sports, camping, Civil Defense emergencies—while walking, at work, at play, etc. Give it as a much appreciated gift.

send only \$5.00 (ck. or M.O.): pay postman \$14.95 plus small charge for COD and postage, or send \$19.95 for postpaid delivery. If not completely satisfied, return radio with- in 10 days for full refund. This imported radio carries a full 90 day guarantee on tubes and parts.

MINI-TRONICS CO. 5030 LINDEN LINCOLN, NEBR.

LEARN

RADAR MICROWAVES TRANSMITTERS

CODE TV RADIO

Phila. Wireless Technical Institute
1533 Pine St. Philadelphia 2, Penna.

A Non-Profit Corp. Founded in 1908
Write for free catalog "P"

BUILD your MULTIMETER!

Now in KIT form, the famous
MODEL M-1

"POCKETESTER"

The famous V-O-MA unit we
built by the thousands for the Army!

- Easy, step-by-step instructions
- Complete with cable harnesses, test leads
 - Military Accuracy
 - Precision parts for fast assembly
 - Dual color meter scale
- Rugged handsome vinyl carrying case
 - 14 broad ranges, for EVERY job!
 - BUILD IN 20 MINUTES!



ONLY
\$17.50
NET

MAIL
THIS
COUPON
TODAY!

Measure:
VOLTAGE: 0.2-5000 volts AC-DC
RESISTANCE: 1-500,000 ohms
CURRENT: 0.2-100 Milliamps

**ATOMIC
ENGINEERING
CORPORATION**

Manufacturers of
quality electronic
equipment.

Box 1701, Station P
Grand Junction, Colo.


Rush my M-1 "POCKETESTER" kits to me NOW! I
want _____ kits.
 Check enclosed. Money order enclosed.
 Send C.O.D.

NAME _____
ADDRESS _____
CITY _____ ZONE _____ STATE _____

current TV sets and also for some color receivers. (Service Instruments Co., 171 Official Rd., Addison, Ill.)

POCKET-SIZE VOM

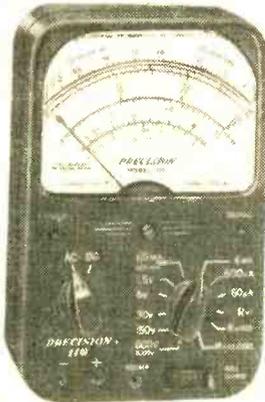Compact enough to fit into a technician's pocket or tube-caddy, the Model 110 VOM combines full-range instrument performance with small-size instrument convenience. This handy 20,000 ohms-per-volt multimeter—which measures only $1\frac{1}{16}'' \times 3\frac{1}{2}'' \times 5\frac{3}{8}''$ —provides six d.c. and a.c. voltage ranges, five d.c. current and three resistance and six db ranges.



Very flexible voltage measurements are possible due to extra low (1.5 volts, full scale) and extra high (3000 volts, full scale) voltage ranges. Current ranges up to 600 ma. and decibel ranges from -20 to +70 are also available. \$32.50, net. (Precision Apparatus Company, Inc., 70-31 84th St., Glendale 27, L. I., N. Y.)

TV AND RADIO TUBE TESTER

Most radio and TV set failures are due to burned-out tubes. The new Teleclear tube tester will automatically check all TV and radio tubes. Operating on 110 volts a.c. or d.c., it is safe, quick and easy to use. Just plug the tube into one of the sockets provided and the neon lamp will indicate its condition instantly.

In addition, this tester performs over 1000 electrical tests. It checks appliances, fuses, light or flash bulbs, wires, motors, resistors, etc. It can also be used to check line or other voltages, as a voltage indicator. Retailing for \$2.95, the Teleclear tube tester comes in a shockproof metal case. (Teleclear Company, 25 Willett St., New York 2, N. Y.)



-30-

Sound Impressions

(Continued from page 71)

but at the same time perk up your ears and wake your mind.

Classical Pipings. Columbia's record of *The Philadelphia Woodwind Quintet* (ML-5093) features flute, oboe, clarinet, bassoon and French horn in pieces specifically written for this combination.

One side contains works by composers of the past (Haydn and Beethoven); the other side is devoted to moderns like Hindemith and Ibert having a resounding romp among the tootling reeds. This lets the listener trace the evolution of woodwind writing from Haydn's simple band style to Ibert's sophisticated tricks and sensuous harmonies and Hindemith's urbane, yet warm and fun-filled modernism. In a sense, this is chamber music—the clever interplay of just a few instruments. But the woodwinds lend it pungency and bounce, far different from the sound of the usual strings.

The playing makes it quite clear why many listeners consider the woodwind section of the Philadelphia orchestra the finest in the world. The fidelity of this record matches the excellence of the performance. Each instrument stands out clearly, yet they all blend as a group. The "presence" is amazing.

Winds also blow at the hi-fi mikes in the jazzy regions of music. *Shifting Winds* by Bob Cooper and Jimmy Giuffre waft over both sonorous sides of Capitol T-6531. Here the reeds stir in a brisk breeze of jazz improvisation but seem at their best in the becalmed interlude on Band 3 of Side 1, called *'Round Midnight*. The recording is as lively and smooth as the music.

An American in Blue. George Gershwin's *Rhapsody in Blue*, and *An American*

RECORDS REVIEWED

Music of Alec Wilder

Columbia CL-884

Philadelphia Woodwind Quintet

Columbia ML-5093

Shifting Winds

Capitol T-6531

Gershwin: An American in Paris Rhapsody in Blue

Capitol P-8343

Soundproof

Westminster 6014

Folk Songs of the Old World

Capitol PBR-8345

Delibes: Coppelia Sylvia

Victor LM-1913

Westminster XWN-18241


Music for Barefoot Ballerinas

Decca DL-8034

1957 ALLIED ELECTRONIC SUPPLY CATALOG

free!

356
value-packed
PAGES

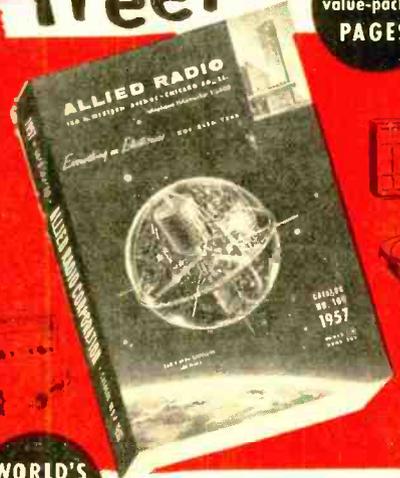

WORLD'S
LARGEST
STOCKS

SAVE ON EVERYTHING
IN ELECTRONICS

Everything for Experimenters, Builders,
Amateurs, Servicemen, Engineers
and Hi-Fi Hobbyists

Save on *everything* in Electronics:
Hi-Fi systems and components;
latest builders' kits (see the famous KNIGHT-KIT line); recorders
and phono equipment; TV tubes,
antennas, accessories; Amateur
station equipment; P.A. systems;
test instruments; industrial elec-
tronic supplies—plus *everything*
in parts, tubes, transistors, tools
and books. Get more for your
money—send today for your
FREE 1957 ALLIED Catalog!

Everything in Electronics
From One Reliable Source

Send
for FREE
Catalog

ALLIED RADIO

ALLIED RADIO CORP., Dept. 79-L-6
100 N. Western Ave., Chicago 80, Ill.

Rush FREE 1957 ALLIED 356-Page Catalog

Name _____

Address _____

City _____ Zone _____ State _____


NEW

HICKOK

VTVM

★ **KIT** ★

**King Size and Top Quality
in an easy-to-assemble Kit.**

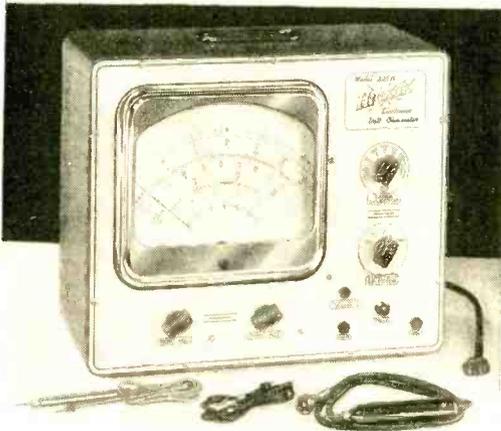

MODEL 225K

- Quality 9-Inch Meter with Extra-Long Scales
- Unusually High Input Impedance
- Dual-Purpose Single Unit AC-DC Probe
- DC Zero-Center Scale
- Plus and Minus DC Voltages
- Accurate Peak-to-Peak Scales
- Fast Continuity-Test Feature
- 60 Page Easy to Follow Instruction and Theory Book Included

More than 45 years of experience in the engineering design and production of electrical-electronic test equipment backs this Model 225K Quali-KIT. This experience and engineering accomplishment has gained the unchallenged leadership and universal recognition for HICKOK Equipment as "Choice of the Experts". All component parts of the 225K are of the highest practical quality to insure long life and trouble-free service. Numerous field studies have been made to prove the ease of assembly of this instrument. Only basic tools are necessary, and the task is both educational and pleasant.

\$59⁵⁰
Net
Complete

Portable, 13-1/4" H., 16-1/4" W. 7" D. (Factory wired... \$104.50)

Write today for additional technical information

THE HICKOK ELECTRICAL INSTRUMENT COMPANY

10500 Dupont Avenue • Cleveland 8, Ohio

in Paris have been recorded so often, and have so much in common, that the listener is apt to blend the two titles into one lazy phrase, such as the heading of this paragraph. Actually, the two compositions are two sides of the same record (Capitol P-8343) and very nearly two sides of the same coin. The "Rhapsody" was the first important American work which used jazz in a full-blown "classical" form.

An American in Paris continued this development. In both works, the composer throws together a rich assortment of melodies, rhythms, and harmonies. Ingenious blends of solo instrument passages with full orchestral choirs produce constantly changing musical patterns—rich in color and irresistible in their rhythm and sweep. From a strictly personal standpoint, the "Rhapsody" represents Gershwin voicing the restless energy—touched with the blues—that was so typical a part of American life in the hip-flask and beaver-coat era. The American then goes abroad and races about Paris—only to wind up with the same restless sadness—or is it nostalgia for the familiar places of his own land? However, even his homesick blues have plenty of bounce, coming from Gershwin's snappy pen.

The performance by Felix Slatkin—conducting the Hollywood Bowl Symphony Orchestra with Leonard Pennario as piano soloist—is truly great. Both sides are breathtaking examples of modern hi-fi recording, with excellent presence and realism. If you like the feeling of the orchestra "coming at you," play this record with your system wide open. Then step back to the far end of the room and hang on!

Searching for Sound. That's exactly what the two gentlemen below are doing. Expert pianists Ferrante and Teicher have discovered new ways of doctoring up instruments to give out bongs, clonks, pings and quivers like nothing on earth—a fact intimated by the flying saucer on the record cover. Old favorites like "Green-



Always say you saw it in—POPULAR ELECTRONICS

ALL TUBES UNCONDITIONALLY GUARANTEED FOR 1 YEAR

take your pick
any assortment

100 receiving tubes \$38

On orders of less than
100 tubes — 41¢ each

BRAND NEW TV PICTURE TUBES

RCA and DUMONT
Licenced

Partial Listing
No dud required

Type	T.M. Price
10BP4	\$10.95
12LP4	12.95
12QP4	10.00
14CP4	15.25
15DP4	16.95
16DP4	18.50
16QP4	19.25
16KP4	17.00
16RP4	17.00
17BP4	19.00
17GP4	21.00
17LP4	18.00
19AP4	23.00
20CP4	24.00
21ALP4A	24.00
21EP4	24.00

Picture tubes

F.O.B. PASSAIC, N. J.
via Railway Express

PRETESTED TUBES—INDIVIDUALLY BOXED

0Z4	6AU6	6SH7	12BA6
1B3GT	6AU5GT	6J7GT	12BE6
1H5GT	6AV5	6SK7GT	12A27
11C5	6AV6	6SL7GT	12BH7
11N5	6AX4GT	6SN7GT	12BR7
1N5GT	6AT6	6S7	35A7
1Q5GT	6AN4GT	6SR7	12S67
1R5	6BA6	6T8	12SJ7GT
1S4	6BC6	6T8	12SK7
1S5	6BE6	6V3	12SL7GT
1T4	6BGG6	6V6GT	12SN7GT
1T5GT	6B16	6W4GT	12SQ7
1U4	6BK6	6WG7	12SR7
1U5	6BK7	6X4	19T8
1X2	6BL7GT	6X5GT	19BG6G
3Q4	6B06GT	6Y6	25B06GT
3S4	6B07	7C5	25L6GT
3V4	6BY5G	7C6	25Z5
5U4G	6BZ7	7E7	25Z6GT
5V4G	6C4	7F7	35B5
5Y3	6CB6	7F8	35C5
6AB8	6C06G	7N7	35L6GT
6AC7	6F6	12A15	35W4
6AG5	6HG7	12A17	35Y4
6AG7	6J5GT	12A16	35Z5GT
6AF4	6J6	12A17	50A5
6AK5	6K6GT	12AV6	50B5
6AL5	6L6	12AV7	50C5
6AQ5	6S4	12AX7	50L6GT
6AS5	6S6GT	12AX4GT	117Z3
6AT6	6S47	12BY7	

Free Postage on all prepaid continental
U.S.A. orders. 25¢ handling charge on all
orders under \$5.00. 25% deposit on all
C.O.D. Subject to prior sale.

TUBE MART

DISCOUNT HOUSE

PRescott 3-0330

The Lakpet Bldg.

Passaic, N. J.

GIGANTIC
SAVE-TO-70%

MAIL SALE

WAR SURPLUS
EXCESS INVENTORY
BANKRUPT STOCK

ARMY GEIGER TUBE

• Finest beta-gamma precision radiation detection tube. Makes ultra sensitive uranium prospector. Geiger Counter unit worth \$100.00. Full instructions for constructing efficient counter-detector using tube plus few inexpensive components. Cost \$8.50 SALE, \$13.39 Ppd.

ULTRA-VIOLET (Black light) TUBE

• Conduct fascinating fluor-scent glow experiments with this tube in your home laboratory. Operate on 110-v thru resistor. Full instructions. Rocks and minerals glow brilliantly under black light. Locate valuable mineral deposits. Cost \$2.50 SALE, 49¢ Ppd.

LARGE AC SELSYNS

• Finest large 110-v 60-c powerful Selsyns. Marvelous for experimental use. Make wonderful wind direction weather units. Transmit mechanical motion electrically. Run on small AC generators, etc. Many uses. Size 4"x6" Wt. 8 lbs. each. Rins directly off 110-v 60-c. Govt. cost \$79.50 each. SALE, \$15.41 per pair Ppd. or \$8.00 each

BOAT & TRUCK ELECTRIC WINCH

Operates from 6 or 12-v battery over 1000-lb. capacity

• Powerful expensive fully reversible Govt. ball bearing motor with built-in 100-to-1 ratio precision reduction gear. Gives smooth powerful pull on winch cable.

• Hundreds of applications. Mount on boat trailers, boat docks, raising anchors, etc.

• Ideal for trucks, farm equipment trailers, industrial uses. Cuts haul loading costs 90%. Wt. 54 lbs. Size 17"x12"x8". Drum holds 40' 1/4" or 75' 3/16" cable. Orig. Govt. Cost over \$200. F.O.B. Lincoln... \$46.71

SURPLUS CENTER BUYS (Prepaid)

- Gear Reduction Unit 85 to 1 (\$86) \$ 8.91
- Govt. Weather Unit (\$125) 18.71
- 6-Volt Electric Winch (\$250) 48.71
- Power Plays (110-v 60-c 1000-w) 149.50
- Weston 0-100 Amp DC Meter 4.50
- G.E. 0-300 Amp DC Meter 6.89
- Triplet 0-15 Amp DC Meter 3.91
- Triplet 0-50 Volt DC Meter 3.91
- Simpson 0-120 M.A. RF Meter 6.91
- Westinghouse 0-35 M.A. DC Meter 3.91
- G.R. = 100-Q KVA Variac (F.O.B.) 39.20
- Handset Holders Screw on desk 2.37
- Edwards AC-DC Bell (\$3.75) .97
- Laboratory Sensitive Relay (\$11.50) .79
- Relay Spring Adjusters (\$2.50) 2.91
- Relay Gram Gauge (\$7.50) 2.91
- Machinists Calipers, polished, stainless 2.34
- Telephone Line Test Phone Unit (\$250) 24.95
- 110-v to 20-c Teleting (\$70) 9.91
- Federal Dual Amplifier-Repeater (\$150) 19.76
- Wire Chiefs Test Board (\$175) 30.72
- A.E. Step-by-Step Switch (\$105) 15.89

PERSONNEL CARRIER MOTOR

- Amazing buy! Use for golf carts, factory personnel carriers, boys auto, and 1100 other uses.
- Powerful expensive ball-bearing gear reduction motor runs on any 6-v or 12-v storage battery. Powerful high torque. Shaft speed 150-300 rpm. Full instr. Easily reversible. Wt. 34 lbs. Govt cost over \$200. SALE, \$19.46 F.O.B.

GEAR-HEAD MOTOR

- Brand new. Will operate air dampers, valves, remote boat steering, window and door locks, garage doors. Remote tuning, rotate antenna arrays, etc.
- 9000 rpm all ball-bearing motor driving a worm gear, rotary double shaft. Very powerful due to high (1000 to 1) reduction ratio. Output speed is 6-10 rpm. Will operate on 6 to 24 volts DC or 8 to 12 volts AC. Fully reversible.
- Limit switches to control travel limit. Splined dble. shaft 5/8" dia. Overall dimensions 9"x3"x4". Marvelous equipment buy. Govt cost over \$100. SALE \$8.72 Ppd.

SPECIAL OF THE MONTH POWER RECTIFIER

• New G.E. 115-v 60-c selenium rectifier unit. Will supply DC voltage for lab'y work, signaling, power supply systems, experiments, radio and TV test benches, etc.

• Furnishes pure, well filtered direct current adjustable from 25 to 210-v. Also AC voltage adj. from 50 to 230-v. Attractive cabinet. Rough and fine adjustments. Govt. Cost over \$200 SALE, \$15.61 F.O.B.

WESTON INDUSTRIAL TUBE TESTER

• Elaborate expensive laboratory type tube tester. Model 002. Test hundreds of types including industrial, home receiver, TV, etc.

• Attractive oak case 8"x12"x24". Three precision meters, rectifiers, etc. Works on 110-v 60-c. Full instructions. Slightly used—perfect. Wt. 35 lbs. Govt cost over \$100. SALE, \$14.90 F.O.B. Lincoln

G.E. AMPLIFIER-RECTIFIER

• New 110-v 60-c electronic unit. Push-pull amplifier-rectifier. Useful in lab'y, control circuits. In A-C control application, voltage applied to input will produce a DC voltage for motor or relay operation at output. Ideal for study of Servo-Selsyn circuits, etc. 10 1/4" x 9 1/2" x 5 1/4". Govt. Cost over \$150 SALE, \$6.96 Ppd.

DIAL TELEPHONE

• Genuine Kellogg standard dial telephone. Will work on any modern system either as main phone or as remote extension phone.

• Completely self-contained transmission circuit, signal bells. Easy to connect. Complete with cord. List \$30.50 SALE, \$13.91 Ppd.

ORDER FROM AD or write for big new 1000s of items
WINTER CATALOG Motors, sport hand-electric tools, watches, etc. We pay freight except where stated. "F.O.B."

"Nationally known—World famous!"

FREE CATALOG **SURPLUS CENTER**
842 "O" St., LINCOLN, NEBRASKA

sleeves" take on more spectacular hues and a tonal picture of "Man from Mars" shows the sonic climate of that planet most conducive to hi-fi. Brilliantly played, these tonal phantasies are resoundingly engraved from seventeen microphone channels on "Soundproof," Westminster Record 6014.

Folk Songs á la Carte. A new album of folk songs, recorded by the Roger Wagner Chorale (*Folk Songs of the Old World*, Capitol PBR-8345) samples songs from England, Ireland, Spain, Italy, France, Germany and the Scandinavian countries. Most of the selections are fairly familiar; a few are rarely heard but are certainly worthy of being recorded.

As a selection of representative folk songs "of the old world," the album raises a serious question: why the omission of any selections from the rich and tuneful storehouse of music from the Slavic and Central-European countries? Then too, the slick arrangements, the unnecessary and obtrusive drums and trumpets, the gaudy slides and swoops in the singing, the over-theatrical tricks with tempo . . . all add up to a very un-folksy way of doing folk songs.

As far as simple, down-to-earth folk-singing is concerned, this album definitely missed the boat. Instead, it provides an-

other vehicle—a sort of parade float, prettied up and bedecked with artificial flowers. It will probably take many listeners for a very enjoyable ride, providing they like slick arrangements.

As for the recording itself, it is a brilliant hi-fi job. The ensemble effect of the singing group is amazing. All parts are clearly discernible and yet blend very neatly. The words are understandable, even on first hearing. From a purely vocal standpoint, the effect is gratifying; much range and rich sonic effects are achieved by Roger Wagner as he makes of the folk songs showpieces for demonstrating the mettle of his group and the marvels of hi-fi.

Dancing—Public and Private. Thanks to the spate of musical comedies lately from Broadway and Hollywood, ballet dancing has become a popular art. Unlike other indoor sports, ballet demands physical prowess superior to that involved in most outdoor activities. For most of us, ballet therefore remains a spectator game. Hi-fi fans, who would just as soon listen as look, can now get both of Leon Delibes' top-notch ballets, *Sylvia* and *Coppelia*, served on a single platter. Here is a flood of easy melody to tingle your ears and tickle your toes. For all its charm and delicacy, this is old-fashioned music of solid

Abraham Marcus, co-author of famous best-seller "Elements of Radio" makes amazing offer!



TRY MY TV and RADIO REPAIR COURSE FREE FOR 1 MONTH

"If you haven't earned at least \$100 in spare time during that period you pay not a cent."

Here it is! The most amazing guarantee ever offered on any radio-TV course anywhere! We'll send you Abraham Marcus' course to use FREE for one full month! If in that time you haven't actually made \$100 fixing radios and TV sets, just return the books to us and pay not a penny!

Why do we make this sensational offer? First, because these books are so easy to use. They are written in the same clear, easy-to-understand language that made the author's "Elements of Radio" a 1,000,000-copy best-seller. Second, because these books get right to the point—tell you what to do in 1-2-3 fashion. For example, once you master the first few chapters of the TV book you are ready for business—ready to do service jobs in the field—jobs that account for over 80% of all service calls.

DON'T WAIT! You risk nothing when you send the coupon at right. You don't have to keep the books and pay for them unless you actually make extra money fixing radios and TV sets. Even when you decide to keep them, you pay on easy terms. Mail the coupon now.

WHAT YOU GET IN THESE 3 GIANT VOLUMES

ELEMENTS OF TELEVISION SERVICING. Analyzes and illustrates more TV defects than any other book, and provides complete, step-by-step procedure for correcting each. You can actually SEE what to do by looking at the pictures. Reveals for the first time all details, theory and servicing procedures for the RCA 28-tube color television receiver, the CBS-Columbia Model 205 color set, and the Motorola 19-inch color receiver.

RADIO PROJECTS. Build your own receivers! Gives you 10 easy-to-follow projects, including crystal detector receiver—diode detector receiver—regenerative receiver—audio-frequency amplifier—tuned-radio-frequency tuner—AC-DC super-heterodyne receiver—etc.

RADIO SERVICING Theory and Practice. Here is everything you need to know about radio repair: replacement and readjustment. Easy-to-understand, step-by-step self-training handbook shows you how to locate and remedy defects quickly. Covers TRF receivers, superheterodyne receivers, short-wave, portable, automobile receivers, etc. Explains how to use testing instruments such as meter, vacuum-tube voltmeters, tube checkers, etc., etc.



MAIL THIS COUPON

Prentice-Hall, Inc., Dept. 5702-P1
Englewood Cliffs, New Jersey

Please send me Abraham Marcus' TV & RADIO REPAIR COURSE (3 volumes) for 10 days FREE examination. Within 10 days I will either return it and owe nothing, or send my first payment of \$5.00. Then, after I have used the course for a FULL MONTH, if I am not satisfied I may return it and you will refund my first payment. If I will keep the course and send you two more payments of \$5.00 a month for two months.

Name

Address

City Zone State

Always say you saw it in—POPULAR ELECTRONICS



WANTED

Willing to pay cash for Early Phonographs with outside horns

WANT Coronet (Illustrated), Double Bell Wonder, Victor Types A, D, and O, Monarch Special, and Improved Monarch. Also Edison Idelia, Excelsior, and Treadle Phonographs. Want early Bell-Tainter, American Gramophones, Multiphone, Multinola, Scott Magazine Phonograph, Peerless, Sovereign, Wizard Phonograph, Regina Hexaphone, and Graphophones. Also catalogues or old literature on phonos made prior to 1906. Want unusual machines and coin-in-slot cylinder phonographs.

A few duplicate Edisons and graphophones are now available for sale or trade.

Send clear snapshot and full information to

Box 50


POPULAR ELECTRONICS

366 Madison Ave., New York 17, N. Y.

Real Time Savers...

Solderless Terminal Kits

by **VACO**

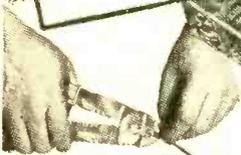

For Bench Work or Service Calls!

You get positive, trouble-free connections every time you close your hand... with VACO Solderless Terminals. No. 2195 kit contains supply of 10 different types of terminals and crimping tool in plastic storage box. No. 395 kit comes with assorted Pak and Crimping Tool in carrying case.

Get Them From Your Jobber or Write
VACO PRODUCTS COMPANY
317 E. Ontario Street, Chicago 11, Illinois
In Canada: Atlas Radio Corp., Toronto 10

No. 395... \$3.95

No. 2195
\$8.90

reference value at "room temperature."

Dissipation constant. This refers to self-heating action. To raise the temperature of a 51R2 thermistor from, say, 50° to 51° C, the current flowing in it would have to be increased. The increment would have to be such as to cause 2.5 more milliwatts to be dissipated at the new temperature. Dissipation constants are very dependent upon the type of mounting and the surrounding medium.

Consider a thermistor for which the dissipation constant is specified as 2.5 mw./° C when the thermistor is suspended by its leads in still air. If it is to be used as a thermometer which must have a maximum error of ½° C, then the maximum power in the thermistor must be limited to 1.25 mw. ($2.5 \times \frac{1}{2} = 1.25$). This limitation is required since the thermistor will self-heat by ½° C when subjected to still air environment while the self-heating in moving air or liquid may be negligible.

Time constant. There is a lag between the time that a current increase occurs and the time that the thermistor reaches the final temperature for the new current. The heating and cooling curves are so similar to those which apply to the charging of a capacitor through a resistor that we can use one as an analogy for the other. The *RC* time constant tells us how long it takes a given capacitor to charge to 63% of the full voltage through a specific resistor. Similarly, the thermistor time constant specifies the number of seconds required for the thermistor to attain 63% of the rise in temperature it will undergo as a result of the new current. In the case of the 51R2, the time constant is 20 seconds.

Assume that a 51R2 is self-heated to 30° C and a current increase is initiated which will cause the thermistor temperature to go to 40° C, given sufficient time. It will take the thermistor 20 seconds to cover 6.3° C, i.e., 63% of the 10° C increase. Therefore, at the end of the time constant period of 20 seconds, the 51R2 will have reached a temperature of 30° + 6.3° or 36.3° C.

Essentially, both the dissipation constant and the time constant depend upon how rapidly the thermistor can absorb heat from and liberate heat to its surroundings. Altering the mass of the thermistor affects both; i.e., if the mass is increased, the dissipation constant is increased and a larger time constant results.

Temperature-resistance ratio ($R_0 @ 0^\circ C / R_0 @ 50^\circ C$). This ratio provides information related to the resistance variation which may be expected for a given thermistor as its temperature changes. For the 51R2, the resistance at 0° C is 9.1 times

KITS • TOOLS
HI-FI
 Subminiature
OPTICS
PHOTO EQPT.
 for
Hams, Hobbyists,
Repairmen &
Industrial Firms

FREE! Our **Biggest Flyer EVER!**
 HUNDREDS OF BARGAINS,
 BONUS AND GIFT ITEMS!
 WRITE FOR YOUR COPY TODAY!
 FREE! ANY \$1 ITEM
 WITH EVERY \$10 ORDER!
 Free Gift with Every Order!

A LEKTRON EXCLUSIVE!
2-TRANSISTOR
POCKET RADIO
KIT only \$7.88



LATEST CIRCUIT DESIGN! Keeping up with new design trends, set uses direct coupling; including an impedance coupled amplifier for better gain and fidelity. New loopstick tuner for sharper selectivity. TWO hi-gain transistors. "Energy capsule" mercury cell as power source outlasts regular batteries 5 times! New miniature variable condenser. Compact, sturdy, pre-drilled styrene cabinet. All parts mounted; minutes to complete! Step-by-step instructions. INCLUDES: case, 2 hi-gain transistors, loopstick tuner, miniature variable condenser, impedance coupler, cell, jacks, posts, hardware, instructions. Wt. only 4 oz. Shipping wt. 1 lb.

HIGH IMPEDANCE HEADSET.....only \$1.99

EARN BONUS CREDITS TOWARD FREE DOLLAR-KITS!
 ANY PURCHASE ENROLLS YOU IN LEKTRON'S
 "CREDIT-BONUS PLAN"!

FAMOUS KIT KING DOLLAR BUYS!
ONLY ONE DOLLAR EACH!

- 60 XFMRs & COILS. 1P, 1P, slug-tuned coils, chokes. 25 types. Wt. 3 lbs. Reg. \$15.
- DIDIE RADIO KIT. Complete w/ pre-drilled cabinet, germanium diode, loopstick tuner, instructions. All parts mounted. Wt. 1 1/2 lb. Reg. \$3.
- PHOTO-ELECTRIC CELL. Famous Western Electric photo cell makes excellent sun battery; w/ greater output than named. 3/2" x 1 1/4" dia. Reg. \$5.
- 10 "POLY" BOXES. Ass'd. sizes clear plastic boxes; hinged w/ snap lock. Hundreds of uses. Reg. \$2.50.
- 125 RESISTORS. Insulated & un-insulated. 30 values: 22 ohms to 1 meg. 1/2 to 2 w; 5% too. Wt. 1 lb. Reg. \$1.19.
- 40 SUBMINIATURE RESISTORS. Exclusive! 20 popular values, 100 ohms to 1 meg. Only 1/4" long. 1/8 x 1/8 w. In poly box. Reg. \$8.
- 8-PC. NUTDRIVER KIT. Plastic handle; 3/16, 7/32, 1/4, 5/16, 11/32, 3/8, 7/16" steel socket wrenches in plastic case. Wt. 1 lb. \$3.
- 3 lbs. HARDWARE. 2,000 pcs. Ass'd. screws, springs, washers, etc. Hundreds of items! Reg. \$8.
- G-E PRE-AMP KIT; for magnetic cartridges. Complete w/ chassis, parts diagram, lens GSC7 (88¢ extra). Wt. 1 lb. Reg. \$4.50.
- 30 TUBE SOCKETS. 4, 5, 6, 7, 8, 9. 1-prong miniature, octals, 6-pin, 4-pin, 5-pin, molded. Tube shields, too. Wt. 2 lbs. Reg. \$7.
- 70 STANDARD KNOBS. Radio, TV, auto, distance, lab types. Ass'd. colors, bakelite & plastic. Wt. 2 lbs. Reg. \$1.50.
- 30 PRECISION RESISTORS. WW & carbon film. 30 values; 50 ohms to 1 meg. 1/2, 1 & 2 w, 1% tol. Some \$5. Wt. 1 1/2 lb. Reg. \$21.
- 20 AC, DC LINE CORDS. For clocks, motors, etc. Molded plugs, 2 cond. Wt. 1 lb. Reg. \$3.
- 70 MICA CONDENSERS. Famous makes. 30 values: 0.001 to .01 mf. to 1000V. Silver, 5% included. Wt. 1 lb. Reg. \$5.
- 175-FT. HOOKUP WIRE. 25-ft. rolls; ass'd. colors; stranding; insulation, #18 to 24. Wt. 2 lbs. Reg. \$13.75.
- 75 CERAMIC CONDENSERS. Scopul! 35 ass'd. values, tubulars & discs. 5 mmf to .01 mf up to 3 KV. Wt. 1/2 lb. Reg. \$11.
- 65 RESISTORS. Insulated IRC, Allen-Bradley, etc. 5 ohms to 10 megs. 1/2, 1 & 2 w; 1% & 5%. Wt. 1/2 lb. Reg. \$10.50.
- 10 ELECTROLYTICS. PP & 2-wire tubular, rect. Ass'd. sizes, multiples, too! 8 to 500 mf to 450V. Wt. 3 lbs. Reg. \$19.
- 4 SILICON DIODES. Sylvaria IN21, IN22, IN23, IN105. Reg. \$8.50.
- 15 ROTARY SWITCHES. Wide ass't. ceramic & bakelite units; including multiple gangs. Wt. 3 lbs. Reg. \$13.4.
- 3 GERMANIUM DIODES. Most popular types: IN34, IN51. Reg. \$4.
- 60 TUBULAR CONDENSERS. Popular makes, 30 types. .0005 to 0.5 mf to 1500 V. Wt. 2 lbs. Reg. \$12.
- 15 VOLUME CONTROLS. 10 types, values to 0.5 meg. Reg. \$9.
- 40 MOLDED CONDENSERS. Brown, black ceramic cased; .0001 to 0.1 mf up to 1000V. Wt. 1 lb. Reg. \$8.

88¢ PICK-A-TOOL SALE 88¢

HIGH-GRADE TOOLS • SIMPLY CIRCLE TOOLS WANTED
 6" SIDE-CUTTERS. 6" LONG-NOSE. 7-PC. MAGNETIC SCREWDRIVER SET. 5-in-1 SCOUT KNIFE. 10-in-1 HEX-NUT WRENCH. BENCH VISE, 1 1/2" jaws, clamp type.

FAMOUS MAKE 12" SPEAKER



10 watt. Response: 50-10,000 cps. Reg. \$10.00
 Heavy Alnico V magnet; 3-4 ohm voice coil **\$3.99**

3-SPEED PORTABLE RECORD-PLAYER

Ideal gift! True-fidelity sound; 33, 45, 78 rpm. Lightweight arm w/ long life needle; plays all records 7" thru 12". Alnico V speaker. Handsome 2-tone portable case. Wt. 10 lbs. Reg. \$28.00 **\$15.95**

250V POWER SUPPLY KIT

Complete w/ chassis; xfmr. (115 vac in; 500VCT @ 70 ma., 6.3 @ 3A); cord, tube, sockets, resistors, switch. ONLY **\$3.50**

SALE! FAIRCHILD ELECTRIC DRILL

Trigger type, w/ cast aluminum body, hand chuck, heavy-duty rubber cord. 115VAC. Reg. \$19 **\$9.98**

Same, with JACOBS CHUCK & KEY..... \$13.88

FAMOUS MAKE CRYSTAL MIKE!

Top American make, moisture proof crystal mike for hand or desk use. Resp. 100 to 8,000 cps. Ideal for recorders, P.A. systems, 5-rit. shielded cable. In original boxes..... Reg. \$8.00 **\$2.98**

★ SEE OUR "BARGAIN BASEMENT" AD! ★
LEKTRON
 28 GARDINER STREET CHELSEA 50, MASS.

HOW TO ORDER

Check items wanted. Return entire ad with check or M.O. Include sufficient postage, excess returned. C.O.D. orders, 25% down. Rated, net 30 days. Print name, address, amount money enclosed, in margin. PE-11
 Visit our salesroom, 131 Everett Ave., Chelsea

GET INTO ELECTRONICS

You can enter this unexplored, interesting field. Defense expansion, new developments demand trained specialists. Study all phases of radio & electronics theory and practice. TV; FM; broadcasting; servicing, aviation, marine, police radio. Prepare for good pay, 18-month course. Graduates in demand by major companies. If S. or equivalent required. Begin January, March, June, September. Campus fire. Write for Catalog.

VALPARAISO TECHNICAL INSTITUTE
 Dept. PE Valparaiso, Indiana

GARAGE DOOR OPENER Actuator Mechanism **\$24.50**
 EASY TO INSTALL, SAFE, RELIABLE
 WRITE for interesting free information... TODAY
P. E. HAWKINS CO.
 631 PROSPECT KANSAS CITY 24, MO.

Car Owners:
LOCATE MOTOR TROUBLE AT START
SAVE ON BATTERY & MOTOR WEAR

\$300 with NEW, AMAZING **Electronic** Auto-Ignition Indicator
 Mounted On Dash Board Any Car—In 2 Minutes, No Tools Required



When your car fails to start, this remarkable invention indicates immediately whether trouble is in fuel or ignition systems. While car is in operation, increased or decreased intensity of light tells whether you are getting optimum mileage from your gasoline. Indicator light works. Electrostaticity by Radio Frequency! Does not draw power from the battery! Bulb tests independently. ORDER TODAY! GUARANTEED.

KAR-AIDS, Inc.
 25 - 11B 49th St.
 Long Island City 3, N. Y., N. Y.

ASSEMBLE YOUR OWN
WALKIE-TALKIE
RADIOPHONE



for as little as
\$6.50
plus accessories

Specifications: 1 to 5 mile range with 18-inch antenna and much more with directional beam antenna. Tunes from 144 to 148 mcs. High level amplitude modulation. Silver plated tank circuit and many other exclusive features assure maximum efficiency and long battery life. Fully portable—no external connections ever needed. Meets FCC requirements for general class amateur license. No minimum age requirement.

The following components are all you need to assemble a complete walkie-talkie as illustrated. Factory wired and tested transceiver chassis complete with special dual tube \$6.50
High output carbon mike \$1.49
Miniature mike transformer \$1.98
Powerful alnico magnet headphone \$1.25
Strong 16 gauge aluminum case (8"x5"x2") with battery compartment, battery switch plus all hardware and fittings including 18 inch antenna \$3.98

Uses standard batteries available at your local radio store.

All components except tubes guaranteed for one year.

Please include 5% for postage. COD's require \$1.00 deposit.

Thousands sold throughout the world. Foreign currency of equivalent exchange value plus sufficient amount for postage accepted.

All orders immediately acknowledged.

SPRINGFIELD ENTERPRISES

Box 54-E

Springfield Gardens 13, N. Y.

NEW! PRINTED CIRCUIT
Transistor Radio

Pocket size—works anywhere

- Features P-N-P Junction Transistor
- Permeability tuning, Diode detection
- Printed circuit eliminates extra wires
- Batteries last for months
- Expensive hearing aid headset included
- Furnished complete, nothing else to buy



\$9.95
Only Postpaid
in kit form

Here is a powerful, completely portable radio, employing the latest type of transistor audio amplification and printed circuitry. Tiny size, only 2½"x3½"x¾" fits in pocket or purse. Uses so little current, batteries last for months. Kit can be assembled by anyone with just a soldering iron. Guaranteed to work. Comes complete with plastic case, batteries, headset, all parts. Nothing else to buy. See your distributor. If he doesn't stock, write direct.

Send no money. Just pay postman \$9.95 plus C.O.D. charges, or send check or money order for \$9.95 and we pay postage.

TRADYNE, INC., 11 W. MONUMENT AVE., DAYTON 2, OHIO Dept. E-7

WANT A BETTER JOB: BECOME AN
ELECTRONIC ENGINEER

ONLY 32 MONTHS TO EARN A BACHELOR OF
SCIENCE DEGREE IN ELECTRONICS ENGINEERING

Class enrollment limited to allow for individual instruction. Chartered by state of California. Nonprofit-nonsectarian, co-educational—established 28 years.

APPROVED FOR VETS—ENROLL NOW!

SEND FOR FREE CATALOG

PACIFIC STATES UNIVERSITY

1516 S. WESTERN AVE., Dept. M., LOS ANGELES, CALIF.

greater than the resistance at 50° C. This constant is an indication of the sensitivity of the thermistor to ambient temperature variations.

Determining Resistance. Although there are mathematical tools available which enable engineers to determine the resistance of a thermistor at any temperature, the formulas are too complicated to be given here. From a data table supplied by the manufacturer, however, any thermistor may be calibrated by means of a curve such as that of Fig. 3. With it, we can find the resistance of the 51R2 at any temperature between 0° C and 50° C (32° F to 122° F), a very useful range indeed.

As a check, note that the curve shows the resistance of the thermistor to be 100,000 ohms at 25° C, which agrees with the nominal rating R_0 given previously. Note also that the resistance at 0° C is 327,000 ohms and that at 50° C it is approximately 36,000 ohms. This verifies the temperature-resistance ratio of 9.1 ($36,000 \times 9.1 = 327,000$ ohms).

A number of practical thermistor circuits and designs will be presented in *After Class* in a forthcoming issue. Devices using thermistors were described in "Safeguard Your Home with a Thermistor Fire Alarm" (March, 1956, issue of POPtronics) and "Make Your Own Electronic Thermometer" (April, 1956). Look for an article on a "Thermistor Anemometer" scheduled to appear in the near future.

-30-

Long-Wave DX'er


(Continued from page 69)

on the back of the chassis accommodates the antenna and ground connections.

Adjustment and Operation. Plug the power cord into a 117-volt a.c. outlet, and plug a set of headphones into the headphone jack. Turn on the power switch. Set the volume control at maximum. A slight hum will be heard for a second or two, and will fade out and become inaudible as the tube comes up to operating temperature.

As soon as the slight hum has disappeared, you may check the regeneration control by rotating it back and forth. A soft "plop" should be heard in the headphones at a setting of the control where the receiver goes into or comes out of oscillation. If the "plop" is not heard at any setting of the regeneration control, turn off the power and reverse the two tickler lead connections.

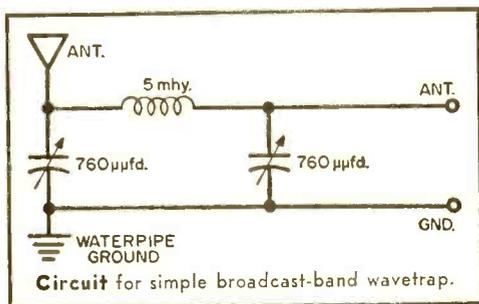With the detector oscillating weakly, and the antenna connected, rotate the tuning dial. As soon as you hit upon a station, rotate the tickler coil slightly away from the tuning coil. If you have tuned in a



c.w. station, backing off the regeneration control should cause the audio tone to disappear—indicating that the receiver has stopped oscillating. Advancing the control slightly will bring the audio tone back again. Some stations will come in more clearly when the detector is not oscillating—these are modulated c.w. stations. Try to keep the detector barely oscillating when you are tuning for weak stations, for this is its most sensitive condition.

One of the problems you may run into while using this or any other simple receiver on the long waves is picking up a strong nearby broadcast station. Such a station cannot be actually tuned in on the receiver. In fact, it may occupy half the tuning range. The best way to get rid of it is to insert a broadcast-band wavetrapp in your antenna lead, a circuit for which is shown in the diagram on this page. Adjust the tuning capacitors in the trap until the broadcast station comes in at the lowest level or not at all.

—50—

Electronic Election Bet

(Continued from page 40)

unlike the machine, can transmute numbers into meaning.

Political scientists and mathematicians have long known that elections in the United States usually follow certain definite patterns, and that these patterns can be expressed mathematically. But the arithmetic involved is so vast and complex that no human being could work out the equations fast enough to get ahead of the actual vote count. Fast figuring, rather than any political understanding, gives computers a margin over man.

The Fast Shuffle. Within its vast electronic memory (see POPULAR ELECTRONICS, August 1956), Univac stores a complete analysis of voting behavior all the way back to 1928. On election night, these vast stores of historical data are mixed in the Univac with red-hot news pouring in on the press wires and juggled together in the strict order of statistical method. The machine compares the early returns, precinct

November, 1956

LEARN basic electricity electronics

THE EASY "PICTURE BOOK" WAY!



Just Released: The fabulous
ILLUSTRATED Training Course
now used by the U. S. Navy!

You Learn by Pictures

Over 25,000 Navy trainees have already learned Basic Electricity and Basic Electronics this easy, "Picture Book" way! Now, for the first time, YOU can master the basics of Electricity and Electronics with this same "Learn-by-Pictures" training course! Over 1,700 simple, easy-to-understand drawings explain every section—these "teaching" pictures actually make up more than half the entire course! No other Basic Electricity or Basic Electronics course in America uses this revolutionary illustrative technique! You learn faster and easier than you'd dream possible!

A Complete Idea on Every Page

Here's how this easy, illustrated course works: every page covers one complete idea! There's at least one big illustration on that same page to explain it! What's more, an imaginary instructor stands figuratively at your elbow, doing "demonstrations" that make it even easier for you to understand. Then, at the end of every section, you'll find review pages that highlight the important topics you've just covered. You build a thorough, step-by-step knowledge at your own pace—as fast as you yourself want to go!

Everyday English—A Course Anyone Can Understand!

Sponsored by the Navy to turn out trained technicians in record time, this modern course presents Basic Electricity and Basic Electronics in a simple way that everyone can grasp—regardless of previous education! Every phase is made instantly clear—explained in plain, down to earth English—with hundreds of easy-to-understand illustrations to help you!

10 Complete Volumes

Volumes 1 and 2 of "Basic Electricity" cover DC components and circuits; Volumes 3 and 4 cover AC components and circuits; Volume 5 covers AC and DC motors and machinery. Volume 1 of "Basic Electronics" covers Diodes and Power Supplies; Vols. 2 and 3 cover Amplifiers and Oscillators; Vols. 4 and 5 cover Transmitters and Receivers.

Home Study Without Correspondence

This course is so different, so complete—there's no need for the usual letter writing, question and answer correspondence! Learn at home—at your own pace!

10 Day Examination—Money Back Guarantee

Send today for these exciting new training courses—you risk nothing! When you receive the volumes, examine them in your own home for 10 full days. If, at the end of that time, you're not completely satisfied, simply return the books to us and we'll gladly refund your full purchase price! Total cost for either 5-volume course is only \$9.00! In Canada, prices approximately 5% higher.

ORDER TODAY!

These books are sold by electronics parts jobbers and book stores. If YOUR dealer doesn't have these books, mail this coupon to us!

JOHN F. RIDER PUBLISHER, INC.
480 Canal Street, N. Y. C.

I have enclosed \$..... Please send me
 5-vol. Basic Electricity set @ \$9 set
 5-vol. Basic Electronics set @ \$9 set
 Both sets. I understand I may return the books in 10 days, and receive a complete refund of the full purchase price if I am not satisfied.
 Add state or city sales tax where applicable.

Name.....
 Address.....
 City & State..... P-10A

by precinct, with the patterns of the past. It weighs in variables, such as splinter trends, Dixiecrats and Independents, constantly checking them against the 15 million items of information stored in its magnetic memory.

In this fast shuffle, the computer completes about 2000 calculations per second. Every time it spots a lead of one party in any given precinct, it goes on to figure out whether the difference is small enough to fall within the limits of chance, or big enough to foretell a significant trend. In other words, it works out the odds by which the candidate with the early lead would go on to win the state.

From the state odds, Univac then switches to compute the presidential odds on the basis of the 531 electoral votes. Mathematically this is done by means of a "531-degree polynomial." By ordinary methods, this calculation takes at least two weeks to complete. Univac clacks out the answer in just six minutes. First it reports the number of states for each candidate, then the electoral and popular votes, and finally the odds in favor of the candidate expected to win. Then it goes on to cover the Congressional contest in the same way, state by state.

Univac's forecast is the best and fastest

guess possible within the margin of that proud unpredictability which is part of human nature. Fortunately, our democratic freedom always leaves a loophole through which sheer human mugwumpery may randomly assert itself to the consternation of all machines, political or electronic. —30—

A Beam and Tower

(Continued from page 79)

quarter-kilowatt. A simple two-element beam that may be fed with a 52-ohm coaxial transmission line is shown in Fig. 2. The antenna is pretuned for the Novice band, but will operate properly over the entire 21-mc. band. It should be used for reception as well as transmission, since there is a reduction of QRM from the back of the beam.

The antenna element is split in the middle, and fed with a quarter-wave section of 75-ohm balanced transmission line. Connect the bottom of this line to a balancing transformer (balun), and also to the 52-ohm coaxial line going to the transmitter. The purpose of the quarter-wave section and the balun is to match the unbalanced 52-ohm line impedance to the load of 20 ohms presented by the parasitic beam antenna.

Figure 3 shows the antenna assembly. The elements are made of 10' sections of electrician's aluminum conduit, known as "EMT

40¢ FOR ANY TUBE

WE WILL NOT BE UNDERSOLD

We Have OVER 1000 USED TV SETS

At All Times in Our Huge Warehouse, Buy one or more of these WORKING TV's to sell or use as your own second set! All sets in GOOD WORKING condition! Your Choice—Console or Table Model.

10".....	\$23.00	19".....	\$58.00
12".....	\$28.00	20".....	\$64.00
14".....	\$33.00	21".....	\$72.00
16".....	\$40.00	24".....	\$99.00
17".....	\$46.00		

When ordering TV's, state whether table model or console is desired. Also preference as to make of set. All TV's sent railway express P.O.B. Newark. On any quantity WRITE or CALL today!

SAME DAY SHIPMENT OF ALL ORDERS!

FREE BONUS ANTENNA GIVEN WITH ANY TV SET ORDER!

SEND for our FREE complete TUBE & PARTS LIST and order blank.

FREE POSTAGE in U.S.A. and Territories on orders over \$5.00. 25¢ handling charge on orders under \$5.00. 25¢ deposit required on C.O.D.'s. Please send approximate postage or freight on Canadian and foreign orders. Subject to prior sale.

DON'T PAY MORE FOR SET TESTED LONG LIFE DEPENDABLE RADIO & TV TUBES • BUY VIDEO • INDIVIDUALLY BOXED—ALL GUARANTEED FOR ONE YEAR OR YOUR MONEY BACK WITHIN 5 DAYS—37.00 Per Hundred

Some Standard Brand—Others With Famous VIDEO Brand

0A2	2X2	6AC7	6BK5	6SG7	7F8	12V6GT
0A3	3A4	6AG5	6BK7	6SH7	7N7	12X4
0A4	3A5	6AF4	6BN6	6SJ7GT	7Q7	14A7
0B2	3AL5	6AH4GT	6BL7GT	6SK7GT	7Y4	14B6
0C3	3AU6	6AK5	6BQ6GT	6SL7GT	7Z4	14Q7
0Z4	3BC5	6AL5	6BQ7	6SN7GT	12A6	19B6GG
1A7GT	3CB6	6AM8	6BVS6	6S07	12AH7GT	19T8
1B3GT	3Q4	6AN4	6E27	6S57	12AT6	24A
1C7G	3Q5GT	6N8	6C4	6S7	12AT7	25AV5GT
1J6GT	3S4	6AQ5	6C86	6T8	12AV6	25BQ6GT
1L4	3V4	6AQ7GT	6CD6G	6U4GT	12AU	25C6G
1M4	4B27	6AS5	6CF6	6U7G	12AV6	25C6G
1M5GT	4B97	6AS7G	6CS6	6U8	12AV7	25L6GT
1L4	5AM8	6AT6	6CU6GT	6V3	12AX4GT	25V4GT
1L6	5AN8	6AU4GT	6E5	6V6GT	12AX7	25Z6GT
1LA6	5AQ5	6AUSGT	6HG6GT	6W4GT	12AZ7	35L6GT
1LC5	5AT8	6AU6	6J4	6W6GT	12B4	35W4
1LM4	5AW4	6BV5GT	6JS6T	6K4	12BA6	35Y4
1LN5	5AZ4	6AV6	6J6	6K5GT	12BE6	35Z3
1N5GT	5J6	6AX4GT	6KG6T	6K8	12BH7	35Z5GT
1S4	5T4	6BA6	6L6	6Y6G	12Y7	50A5
1S5	5T8	6AX5GT	6N7GT	7A5	12C6	50B5
1T4	5U4G	6BE5	6S4	7A7	12SA7	50C5
1U4	5UB	6BC7	6S7G	7B5	12C7	50L6GT
1U5	5V4G	6BE6	6S7	7B7	12SH7	80
1V2	5V6GT	6BF5	6S87Y	7C5	12SJ7GT	117N7GT
1X2	5Y3	6BG6	6S67	7C6	12SK7	117P7GT
1Y4	5Y4G	6BM6	6SF5	7C7	12SN7GT	11Z3
2D21	6AB4	6BJ6	6SF7	7F7	12SQ7	

FREE RCA "CHEATER" CORD GIVEN WITH ANY TUBE ORDER OF \$7.00 OR MORE!

VIDEO ELECTRIC COMPANY

79 CLINTON PL. NEWARK, N. J. Phone Humboldt 4-9848

conduit." This material may be obtained at any electrical supply house. Each element is made of a 10' piece of $\frac{3}{4}$ " conduit, and has 5' tips of $\frac{1}{2}$ " aluminum conduit in each end. An overlap of about six inches at each joint is required. Place a short length of scrap $\frac{3}{4}$ " aluminum tubing in each tip to bring the elements to the required length. Each joint should be shimmed with small pieces of aluminum until a tight fit is obtained, then a hole drilled through the joint and a bolt passed through the hole to draw the joint tight. When the antenna element is finished, it is cut in two at the center. Finally, give each element a coat of aluminum paint to prevent rust and corrosion.

Make the supporting boom of the antenna from a 7' section of steel TV mast, obtainable at any large TV or radio supply house. The director element and antenna are supported on the boom by means of gusset plates cut from $\frac{1}{2}$ "-thick plywood. The director plate measures about a foot on a side, and the antenna plate is sixteen inches on a side. Give the plywood plates a good coat of house paint to prevent moisture from creeping in between the surfaces of the wood. Attach the director to the mounting plate by means of two TV-type "U-bolts." Then attach the plate to the boom with the same type of bolts. No electrical connection should be made between the director and the metal boom.

Four U-bolts are required to attach the antenna to its mounting plates. Use two bolts for each half of the element, allowing a 1" gap between the centers of the two halves. No electrical connection should be made between the halves of the antenna and the supporting boom.

Attach the quarter-wave 75-ohm section to the centers of the antenna by means of bolts passed through holes drilled in the elements. Solder the balun terminals to the bottom of the 75-ohm line, coil up the balun and tape it to the supporting boom of the antenna. The quarter-wave section is allowed to droop beneath the antenna. Make sure that no antenna connections touch the boom of the antenna or the vertical supporting pipe.

As a last step, attach the 52-ohm transmission line, as shown in Fig. 2. The antenna may now be carried up the tower, and attached to the vertical supporting pipe by means of a third gusset plate, made of heavy galvanized iron. This material can be obtained

Bill of Materials for Tower

- 2—20' pieces of 2" x 6" clear, knot-free #1 Douglas Fir or equivalent lumber—cut each piece lengthwise to form two 2" x 3" pieces
- 7—12' pieces of 1" x 4" clear #1 Douglas Fir or equivalent lumber for cross braces
- 1—6' piece of 4" x 4" redwood, or "creosoted" lumber for foundation—cut into two 3' pieces
- 2—Pounds of "sixteen penny" cement-coated nails
- 1—1" i.d. water pipe (enough to make up 30' of pipe) with couplings and pipe flange
- 1—4' length of $\frac{1}{2}$ " water pipe
- 1— $1\frac{1}{2}$ "-diameter ball (approx.) from old ball bearing
- 16— $\frac{3}{8}$ " iron bolts, $5\frac{1}{2}$ " long, with washers and nuts
- Misc. guy wire, egg insulators, paint

Free! THIS AMAZING NEW

ON THIS OFFER
TV "DETECT-O-SCOPE"

SPOTS
BAD
TV
TUBES
Instantly!



Most TV failures are due to faulty tubes. "Detect-O-Scope" tells at a glance how to spot bad ones. Gives numbers of tubes; shows how to locate, check, and replace them safely. 16 x 21 inches. Sells regularly for \$1.00—but it's

YOURS FREE WITH FAMOUS
MANUAL SHOWN BELOW

FIX TV AND RADIO SETS RIGHT AWAY

—even if you never fixed a lamp or doorbell before!

McGraw-Hill's Amazing New Low-Cost Instruction Manual Skips Hard-to-Understand "Theories" and Formulas—Tells HOW-TO-DO-IT in PLAIN ENGLISH

A T LANT—a well-known expert tells you how to fix TV or radio sets! Start from first chapters you start doing simple repairs. Soon you can actually start fixing your own and friends' sets... even start your own profitable business!

Why It's So EASY

The author made this manual easy-to-follow—even for the most "unhandy" beginner. A-B-C directions, 700 clear illustrations show exactly WHAT and HOW to fix, step-by-step. Where and how to buy parts; where to get circuit diagrams; how to test WITHOUT a tube tester; how to use 58 TV controls; simple "cures" for common troubles; how to fix speakers, phono pick-ups, in-

stall and check antennas—and much more.

SEND NO MONEY

Mail coupon NOW! If book doesn't pay for itself in 10 days, don't keep it! McGraw-Hill Book Co., Dept. PEL-11, 327 W. 41 St., New York 36, N. Y.



10-DAY FREE TRIAL OFFER

McGraw Hill Book Co., Dept. PEL-11
327 West 41st St., New York 36, N. Y.

Please send the TV "Detect-O-Scope" FREE with Markus' Television and Radio Repairing for 10 days' trial. If not delighted, I may return book, pay nothing. Otherwise, I will send only \$1.95 plus few cents shipping; then 3 monthly payments of \$2. ("Detect-O-Scope" is FREE in any case.)

Name _____ PEL-11

Address _____

City _____ Zone _____ State _____

SAVE MONEY. Check here if enclosing \$7.95 as payment in full WITH coupon. Then WE pay shipping costs. Same 10-day return privilege. (Offer good in U.S.A. only.)

JOBS IN ELECTRONICS

We can train you and place you in an electronics technician job in the short time of only 12 weeks!

F.C.C. License—the Key to Better Jobs

An FCC commercial (not amateur) license is your ticket to higher pay and more interesting employment. This license is Federal Government evidence of your qualifications in electronics. Employers are eager to hire licensed technicians.

Grantham Training is Best

Grantham School of Electronics specializes in preparing students to pass FCC examinations. We train you quickly and well. All courses begin with basic fundamentals—NO previous training required. Beginners get 2nd class license in 8 weeks. 1st class in 4 additional weeks.

Learn by Mail or in Residence

You can train either by correspondence or in residence at either division of Grantham School of Electronics—Hollywood, Calif., or Washington, D.C. Our free booklet, "Opportunities in Electronics," gives details of both types of courses. Send for your free copy today.

MAIL NOW TO OFFICE NEAREST YOU

(mail in envelope or paste on postal card)

Grantham School, Desk 3-C

1505 N. Western Ave. OR 821—19th Street N. W.
Hollywood 27, Calif. Washington 6, D. C.


Please send me your free booklet, telling how I can get my commercial FCC license quickly. I understand there is no obligation and no salesman will call.

NAME
ADDRESS
CITY..... STATE.....

LMB BOX CHASSIS OFFERS FREE Inside LMB boxes

10 tested kit diagram projectors for the builder. Each one of these kit diagrams built by a recognized expert. Kit projects are complete in every detail. Circuit diagram, photo of project both front and rear photo. Rear photo shows wiring and parts. Detailed instructions for building, complete parts list and approximate cost. Complete to build except parts and your distributor can supply the parts. Ask your distributor for the list of LMB kit Diagram Projects. If he does not have them, write to

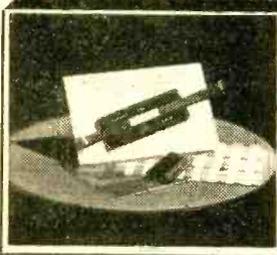LMB 1011 Venice Blvd.
Los Angeles 15, Calif.



Magnetic Tape Splicer
Satisfaction Guarantee
Complete with new pre-cut Mylar tape tabs.
ONLY \$1.50 Postpaid
If your dealer can't supply you—
Order direct from Cousins, Inc., 2107 Ashland Ave., Toledo 2, Ohio
Dealer and Distributor inquiries invited.

CABINET MAKING



LOW COST HOME TRAINING COURSE FOR BEGINNERS & ADVANCED CRAFTSMEN

Make money. Learn skills and secrets of fine woodworking and tool use. Professionally prepared shop method training tells and shows how. Covers everything. Easy to master.

Write for Free Booklet **INTERSTATE TRAINING SERVICE**
DEPT F-95 PORTLAND 13, OREGON

Bill of Materials for Antenna

- 2—10' lengths of 3/4" electrician's EMT aluminum tubing
- 2—10' lengths of 1/2" electrician's EMT aluminum tubing
- 1—10' length of 3/8"-diameter aluminum tubing
—cut into four pieces for element tips
- 1—7" section of 1 1/2"-diameter steel TV mast
- 3—Gusset plates (see A, B, and C in Fig. 3)
- 14—TV-type U-bolts
- 1—9' section of 75-ohm heavy-duty twin lead—cut to 8'6" and trim each end 1 1/2" clear (Amphenol 14-023 or equivalent)
- 1—16' section of 52-ohm coaxial line—cut to 15'10", and trim each end 2" clear (RG-8/U line or equal)
- 1—52-ohm coaxial line to transmitter (any length)

at any sheet metal shop. Use four U-bolts at this joint, two on the boom, and two on the supporting pipe, making a good electrical connection between the boom and the vertical pipe.

"Heck!" said Jimmy, "that sounds easy enough. Am I going to have any trouble getting it loaded?"

"Not particularly," I replied, "although you should keep in mind that sometimes cutting off a foot or so of the coaxial cable may help if things get rough. If you have any problems, give me a call. And by the way, after you've tested out the beam, let's kick around the idea of a better transmitter for you."

—30—

Tricked-up Cathode Rays

(Continued from page 45)

bring out the subtler details, the Tonotron gives the pilot enough time for careful study of what he sees on the screen."


Pictures by Phone. The most revolutionary aspect of the new Tonotron is its ability to receive TV-type pictures over ordinary telephone lines instead of complex and costly broadband channels. It is one of the basic facts of electronics that a fast sequence of signals spreads out over a greater bandwidth than a slow sequence of signals. This is the reason why, in radio, a wide r.f. frequency band is required to transmit the fast vibrations of high notes. It also explains why television, where the scanning beam follows very rapid pulses, needs a very broad frequency band of 4 megacycles per channel for clear transmission of these pulses.

Now the Tonotron, with its ability to "hold" the picture, makes it unnecessary for the scanning beam to retrace the picture pattern quite so rapidly. This means that the control pulses don't have to follow one another so closely. Consequently, one can get by with much narrower transmission bandwidth.

Of course, rapid motion is blurred on pictures that are "held" on the tube for relatively long time spans. Despite this limitation, however, the possibility of narrow-band TV transmission over ordinary telephone or radio channels has many potential uses. Navigation charts, weather maps or graphs can be flashed from shore to ship or ground to aircraft by means of already existing voice-radio transmitters and receivers. Most important, early warning radars at distant outposts can transmit a picture of their sky sector over ordinary telephone lines to centrally located defense headquarters. The whole sky area surrounding the North American continent can thus be "drawn together" for observation from a single point.

Writing Rays. Once the cathode ray knew how to remember, it became possible to teach it the alphabet. Realizing that electronic brains are now getting so smart that they might insist on having things put in writing, Stromberg Carlson taught their new cathode-ray tubes how to spell. The result is the Charactron, which writes on its own screen just like human beings write on a blackboard.

The Charactron owes its literacy to a small disc intercepting the electrons as they stream out of the electron gun mounted in the long, slender neck of this huge tube. The center of the disc is perforated with tiny letters, numerals, and other symbols to be written on the tube screen. No letter is larger than 12/1000th of an inch. As the electron beam passes through these perforations, it is shaped into the form of a letter, which is then projected on the screen. The beam is guided by the control signals to pick out the proper letters, one at a time. But since the tube is able to "remember" what letters have come before, it holds the image of the letter sequence until the entire message is spelled out on the screen. When the information is no longer needed, another sweep of electrons, like a sponge on a blackboard, erases the

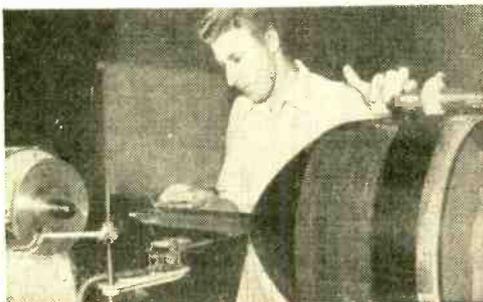

"Letter disc" is inserted into the neck of the Stromberg-Carlson Charactron. Tiny perforations in disc project alphabet letters on the tube screen.

November, 1956

950,000

NAME BRAND TUBES

FREE! 6 PC. SET SCREW WRENCH

SET WITH EVERY ORDER

regardless of size!

Your order will include one or more of these famous brands UNCONDITIONALLY GUARANTEED FOR ONE YEAR

Individually boxed—RETMA SPECS

WRITE FOR NEW FREE TUBE and PARTS LIST!

02C	.43	6AV6	.39	7B4	.44
1A2GT	.43	6AX4	.67	7B5	.41
1A2	.79	6AX5GT	.57	7B6	.42
1B2V6	.68	6BAG	.47	7B7	.43
1B4P	.35	6BA7	.49	7B8	.47
1C5GT	.41	6BC5	.50	7C4	.39
1D5GT	.43	6BD5GT	.53	7C5	.42
1E7GT	.41	6BEG	.46	7C6	.43
1G6GT	.41	6BF5	.40	7C7	.45
1H5GT	.47	6BGG	1.18	7E6	.30
1L44	.57	6BG6	.57	7E6	.30
1L4G	.47	6BJ6	.47	7E7	.49
1L84	.59	6BK5	.68	7F7	.59
1L85	.89	6BK7A	.76	7F8	.70
1L86	.47	6BL7GT	.75	7G7	.75
1N3GT	.50	6BNG	.58	7M7	.50
1R4	.66	6BQ6GT	.80	7T7	.75
1R5	.69	6BQ7A	.80	7K7	.75
1S4	.59	6BY5G	.58	7L7	.58
1S5	.51	6BZ7	.38	7N7	.50
1T4	.51	6C4	.37	7N7	.59
1T5GT	.58	6C5GT	.35	7Y4	.40
1U4	.47	6CF6	.80	7Z4	.40
1U5	.50	6C5	.47	12AT6	.41
1U5	.53	6C86	.51	12AT7	.66
1X2A	.68	6CL6	.71	12AU6	.43
2A3	.51	6CDE6	1.18	12AU7	.59
3A4	.51	6C6	.51	12AV6	.42
3A4L5	.57	6D6	.48	12AV7	.67
3AU6	.57	6E5	.44	12AX7	.45
3AV6	.57	6F6GT	.37	12AY7	.90
3BA6	.60	6HG6T	.38	12BA6	.46
3BE6	.60	6J5	.39	12BA7	.60
3C5GT	.57	6J5	.40	12B4	.68
3S4	.47	6J7	.43	12BE6	.46
3V4	.58	6J7GT	.45	12BH7	.60
5A0S	.60	6J8G	.80	12BY7	.64
5A7B	.60	6K5GT	.47	12J5GT	.40
5J5	.60	6GG6T	.39	12K8	.49
5T4	.69	6K7	.39	12K8A7	.48
5U5	.49	6K7GT	.69	12S47GT	.48
5U4G	.49	6K8G	.35	12S7	.55
5V4G	.68	6K8GT	.65	12SH7	.47
5V4G	.68	6L6G	.68	12SJ7GT	.45
5Y3G	.39	6S4	.40	12SK7	.48
5Y3GT	.39	6SA7	.48	12SK7GT	.50
5Y4G	.43	6SCT	.48	12L7GT	.50
5Y4G	.45	6SD7GT	.57	12SN7GT	.57
5Z4	.54	6SG7	.47	12SQ7GT	.40
6A7	.57	6SH7GT	.43	14A7	.40
6B4	.45	6SJT	.43	19BG6G	1.18
6B7	.80	6SK7	.50	10T8	.70
6C5GT	.59	6SL7GT	.57	25B6GT	.47
6AC7	.61	6SN7GT	.57	25L6GT	.47
6AF4	.79	6SQ7	.41	25Z6GT	.37
6AC5	.50	6SR7	.42	35R5	.46
6AC7	.61	6S57	.41	35R5	.48
6AH4	.80	6T7G	.63	35C5	.48
6AH6	.70	6T8	.68	35L6GT	.47
6AK5	.54	6U8	.80	35W4	.39
6AL5	.42	6V6GT	.46	35Y4	.40
6AL7GT	.70	6W4GT	.40	35Z3	.43
6AQ5	.46	6W6GT	.53	35Z5GT	.39
6AQ6	.42	6X4	.39	45T5GT	.40
6AQ7GT	.70	6X5GT	.39	50A5	.48
6AMB	.80	6X8	.75	50B5	.48
6AN8	.80	6Y6G	.60	50C5	.48
6A55	.48	7A4-XXL	.47	50L6GT	.45
6AT6	.39	7A5	.53	70L6GT	.45
6AU4	.65	7A6	.45	70L7GT	.60
6AUSGT	.60	7A7	.45	11Z3	.37
6AUG	.43	7A8	.45	11Z6GT	.62

Brand New DUMONT AND RCA Inc.

TV PICTURE TUBES

One year Guarantee—in factory sealed carton—

10 inch	No. 95	17 inch	\$17.95
12 inch	\$12.95	19 inch	\$20.95
14 inch	\$14.95	20 inch	\$20.95
16 inch	\$16.95	21 inch	\$22.95

Add \$4.00 to above prices for aluminumized tubes
TERMS: FREE POSTAGE on all prepaid continental U.S.A. orders on receiving tubes only. 50¢ handling charge on all orders under \$5. 25% deposit on all C.O.D.'s. Picture tubes F.O.B. Passaic, N. J. via Railway Express.

STANLEY 935 MAIN AVE.
PASSAIC, N. J.
ELECTRONICS CORP. Gregory 1-2498

Philco • Motorola • RCA • Raytheon • Westinghouse • Admiral • Hallcrafters • Tung-Sol • Sylvania • Zenith • National Union • SE

IT'S THE BIGGEST AND BEST EVER

FREE THE GIANT ALL NEW 1957 BA CATALOG



172
KING-SIZED
PAGES

EVERYTHING
IN RADIO
TV AND
ELECTRONICS

100'S OF
NEW ITEMS
LISTED HERE
FOR 1st TIME

21 PAGES
OF BARGAINS
NOT IN ANY
OTHER CATALOG

BURSTEIN-APPLEBEE CO.

Dept. PE, 1012 McGee St., Kansas City 6, Mo.
 Send Free BA Catalog No. 571

Name.....
 Address.....
 City..... State.....

SEND
FOR IT
TODAY

TRAIN FOR CAREER IN ENGINEERING OR COMMERCE

BACH. SC. DEGREE IN 27 MONTHS in Mech., Civil, Elect., Chem., Aero., Radio (TV-Electronics) Engineering. IN 36 MONTHS in Bus. Adm. (Gen. Bus., Acctg., Motor Transport Mgt.)... capable students faster. Visit campus, see well-equipped labs. Heavy demand for graduates. Placement service. Prep courses. Approved for Vets. Enter Jan., March, June, Sept. Low cost. Write Jean McCarthy, Dir. Adm., for "Your Career in Eng. & Com."

at TRI-STATE COLLEGE 36116 College Ave. Angola, Indiana

R.F. CURRENT INDICATOR

A "MUST" for every amateur. Quickly tune your transmitter by indicating relative field strength. Also useful as an audio monitor or output meter. Operates on any frequency, is portable and does not require batteries. At your distributor or order direct.

Amateur Net \$9.85 Postpaid
ALCO ELECTRONICS MFG. CO.
 3 Wolcott Ave., Lawrence, Mass.



Experimenters - Amateurs - Hobbyists

We are reducing a large inventory of brand new vacuum tubes and this get-acquainted offer is limited to the stock on hand. 13 different electron tubes, including 5" CRT—\$50 value for only \$2.95 postpaid in the U.S.A.; two assortments for \$4.95. Order early and we will include "giant acorn" (orbital beam pentode) and famous "lighthouse" tubes. Sample deal of half a dozen vacuum tubes including 3" CRT \$1.85 postpaid.

Write for free government surplus bargain bulletin.
JOE PALMER
 1440 LAS SALINAS WAY, SACRAMENTO, CALIF.

EASY TO LEARN CODE

Learn or Increase speed with an Instructograph—the Radio-Telegraph Code Teacher that takes the place of an operator-instructor and enables anyone to master code without further assistance. Available tapes from beginners alphabet to typical messages on all subjects. Speed range 5 to 40 WPM. Always ready—no QRM. Thousands have "acquired the code" with the Instructograph System. Write today for convenient rental and purchase plans.

INSTRUCTOGRAPH COMPANY
 4713-F Sheridan Road, Chicago 40, Illinois



writing and clears the tube face for the next message.

In fact, the tube was originally designed to replace a sort of "blackboard"; namely, the transparent plotting board on which Air Defense officers mark the location and movement of aircraft. Prior to the invention of the new writing tube, the defense coordinator received information by radar or telephone and then marked the board with grease pencil. But this manual plotting method proved too slow for keeping track of jet planes capable of outrunning their own noise. Besides, the plotting officer had to assimilate information from several sources at once, thus increasing the chance of a fatal human error. The Charactron writing tube replaces the slow and fallible human link in the chain between the source of information and its display.

The cathode ray, nimble servant of a thousand tasks, has extended the range of the human senses and hence of human knowledge further than any other instrument in the history of science. Not even the microscope in the three centuries of its use has contributed so much to so many fields of inquiry. In our time, the cathode ray is perhaps the chief exploratory tool of science. Its probing beacon casts the first light into the waiting darkness beyond the present frontier of knowledge. Now, with memory and the skill of writing added to its traditional accomplishments, the cathode ray is really "on the beam."

-30-

Transistor Topics

(Continued from page 58)

From Lafayette Radio (100 Sixth Ave., New York 13, N. Y.) comes news of the "world's smallest" shielded i.f. transformers. These units measure only 3/8" square by 9/16" high. Catalog numbers are MS-340 for the first and second i.f. units, MS-341 for the third i.f. transformer. An oscillator coil, to match Argonne's famous "Poly-Vari-Con" subminiature variable capacitor, is available as item No. MS-342.

Also from Lafayette comes news of a new four-transistor superhet receiver kit designed for earphone operation—their Catalog No. KT-94. Available as accessories are a leather carrying case (MS-311) and a Class B push-pull audio amplifier and speaker kit (KT-96). The KT-94 and KT-96, together, form a six-transistor loudspeaker-operated receiver.

From J. W. Miller Company, 5917 South Main St., Los Angeles 3, Calif., there has been an announcement of a whole line of transistor coils and i.f. transformers, including six different antenna coils, four i.f. transformers, three oscillator coils, and

two miniature variable capacitors. For details, write and ask for Catalog Sheet No. 2000 5M Fed. 7-56 . . . or check with your regular distributor.

Do you have trouble finding small resistors to match your other subminiature components? You can get a whole "kit" of around ninety (90) subminiature resistors at no more than you'd pay for a couple of transistors from Wholesale Radio Parts Co., Inc., 311 W. Baltimore St., Baltimore 1, Md. These resistors are but a fraction of the size of regular 1/2-watt units. For full specs, price info, etc., write directly to them and mention this column.

A new technique for the mass production of u.h.f. transistors has been announced by the Philco Corporation. Two new types of transistors, a *micro-alloy transistor* (MAT) and a *surface barrier diffused transistor* (SBDT) are now in engineering development. The MAT transistor is reported to be at least ten times faster than the fastest vacuum tube in electronic computers. The SBDT transistor operates in the 500-mc. range, but will probably find its widest use in the 20 to 200 mc. range.

That's it for now, fellows . . . see you next month.

Lou

The Transmitting Tower

(Continued from page 83)

ance, and cost (\$13.95), the Knight "Space Spanner" kit is an excellent doorway for anyone who wishes to get started in short-wave radio in easy steps.

As a broadcast receiver, the "Space Spanner" leaves little to be desired; therefore, when it is replaced by a more versatile short-wave receiver, it will still give many hours of service on the broadcast band.

News and Views

Since getting a new DX-35 transmitter and adding a Q-Multiplier to his receiver, **George, K2MBU**, (N.Y.), has brought his states-worked total up to 29 from his home location and up to 20 from his vacation site. . . . **Gary, KN9BNJ**, (Ind.), who for the first six months of his license term had a DX record of seven miles, is now able to work the east coast. . . . **Dave, KN2RSM**, (N.Y.), sticks to 40 meters, where his AT-1 feeds a 100' "long wire" through an AC-1 antenna coupler for a record of 24 states worked, with 16 confirmed. . . . **Gerry** (13), **KN0GPX**, (Minn.), uses a Johnson Adventurer transmitter to feed a 20' folded dipole antenna. His receiver is an SX-71, and he has made 36 contacts in eight states.

Ernie, VE3EGG, (16), (Ontario, Canada), has made 50 contacts in 17 states on 40 meters in the six weeks he has had his license. Ernie

WHICH TRANSMITTER KIT TO BUY?

I JUST GOT MY NOVICE TICKET, BUT WHICH KIT SHOULD I BUY?

THAT'S EASY! CHOOSE THE KIT THAT GIVES YOU THE MOST FOR YOUR MONEY!

LATER EVERYTHING IS SUPPLIED. ALL YOU NEED IS YOUR OWN KEY AND CRYSTAL.

JOHNSON MAKES A COMPLETE LINE OF TELEGRAPH KEYS, TOO. WRITE FOR FULL INFORMATION.


SAY, THIS VIKING "ADVENTURER" LOOKS LIKE THE ONE FOR ME!

YOU MEAN YOUR RIG WAS MADE FROM A KIT?

SURE, IT'S TVI SUPPRESSED--WORKS ALL BANDS--80 THRU 10--LOADS ALMOST ANY ANTENNA--AND IT'S PUNCHED AND DRILLED FOR YOU, TOO!

NOW YOU'RE TALKING!! I'VE GOT ONE AND IT'S GOT 'EM ALL BEAT!

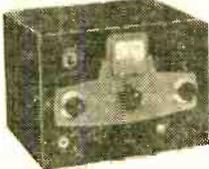SAY! STEP BY STEP INSTRUCTIONS! I'LL BE FINISHED TONIGHT!



VIKING "ADVENTURER" CW KIT
Compact, completely self-contained 50 watt transmitter kit. Single knob bandswitching—effectively TVI suppressed. Easy assembly by novice or experienced amateur. 80, 40, 20, 15, and 11-10 meters. Cat. No. 240-181-1 complete with tubes. **\$54.95**

MAIL TODAY

E. F. JOHNSON COMPANY
3002 Second Ave., S.W., Waseca, Minnesota


Please send me a copy of Bulletin 727, which describes the Viking "Adventurer" in detail.

NAME _____

ADDRESS _____

CITY _____ STATE _____

**ALL NEW
BIGGER THAN EVER!**

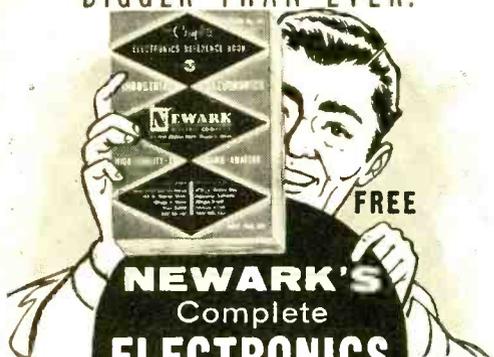

FREE

NEWARK'S
Complete
ELECTRONICS
Catalog No. 65

Here's everything in Industrial
Electronics, High Fidelity,
Radio, TV and Amateur
Equipment

Write
today

NEWARK
ELECTRIC COMPANY

Mail Order Division . . . Dept. P-11
223 W. Madison St., Chicago 6, Illinois
4736 W. Century Blvd., Inglewood, Calif.

uses a home-built 25-watt transmitter, a 1/2-wave antenna, and an S-38C receiver. One thing that amazes him is how American Novices can make so many contacts in the crowded Novice bands. . . . **Phil, K5BTW**, (Texas), has graduated from the ten-watter with which he started his ham career to a DX-100, an NC-98 receiver, and a choice of three antennas—a 33' vertical, a "long wire," and a 3-el, 10-meter beam. His record adds up to 43 states worked, three Canadian provinces, Colombia, and Puerto Rico. . . . **Dick, K4DDB**, after being on 40-meter c.w. exclusively, built a modulator for his AT-1 transmitter and tried 10- and 40-meter phone for a while, but he is back on c.w. again—20 meters this time, where he has recently worked Mexico and several Canadian stations.

In three months of operation, the Knight 50-watt transmitter and the ARC-5 receiver of **Rex, KN4JBJ**, have worked 30 states in all call areas. He is now gunning for Canada and Hawaii. . . . **Bert, WN1IHN**, (Maine), runs 12 watts to a single 6L6 feeding a 60' length of wire thrown out of the radio shack window. Best DX worked is Georgia and Michigan on 40 meters.


Bernie, KN8BVB, pushes his Globe Scout transmitter to 65 watts input to excite his "Windom" antenna. It took him five days to figure out the proper way to connect his balun coils between the transmitter and the antenna feed line, but then VE3DKQ answered his first CQ. . . . **Lou, KN2SZR**, (N.Y.), called for a month after getting on the air without making a single contact because of a poor antenna and insufficient knowledge of how to operate his equipment. In the six months since then, his AT-1 transmitter, AC-1 antenna coupler, and 135' antenna, plus an old EC-1 receiver (somewhat similar to the present-day S-38 series), have accounted for 15 states.

Helen, W9MXI, one of the first to submit news to the *Transmitting Tower*, is the new president of Chicago YLRL, Inc., and the compiler of an excellently prepared brochure for the information of Chicago YLRL members.

Bugs in his equipment prevented **Bill, KN2SLL**, from making many contacts with his Novice license, but he has them ironed out now. Bill sports a 10-wpm code certificate and is waiting for the 15-wpm one to arrive. He is just about ready for his General exam.

Foreign Notes. **Ben Gombo** (19), Philippine Islands, says reading the *Transmitting Tower* helped him pass the Philippine Commercial Radio Operator examination. He plans to build his own amateur equipment, starting with a one-tube receiver, and has been haunting the Manila radio stores, looking for 80- and 40-meter crystals—without success. . . . In Montevideo, Uruguay, **Jose A. Blanco** has finished building a 14-tube ham receiver and is now working on his 40-watt transmitter. The cost of higher power is prohibitive. He reports that Q-Multipliers are very popular among South American amateurs. . . . **T/Sgt. Wm. Cooper** first heard of amateur radio in the Philippines when he was "phone-patched" to his father in Illinois. Now stationed in Spain, the bug has really bitten, and he is going all out to get his own station.

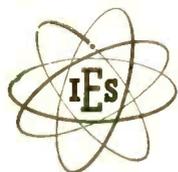Boris, VP2LB, started his amateur career using a "guess-timated" power of 15 watts to a



**ELECTRONIC TECHNICIANS
ARE IN DEMAND
TRAINED MEN ARE NEEDED NOW!**

In just 18 months you can complete Electronic Technicians training to enter this ever-growing industry. Day or evening classes.

Opportunity for employment in local industry. Approved for Korean Veterans.

Terms beginning January, April, July, September
Write for Catalog 224 TODAY

INDIANAPOLIS ELECTRONIC SCHOOL

312 E. Washington St. Indianapolis 4, Indiana

PEE WEE BATTERYLESS "LIFETIME" RADIO
TUBELESS



REALLY WORKS—FOR LIFE!
WORKS WITHOUT TUBES, BATTERIES OR ELECTRICAL PLUGS. Will never run down or burn out! World's smallest. SMALLER THAN A PACK OF CIGARETTES! GUARANTEED TO RECEIVE LOCAL RADIO STATIONS ANYTIME—ANYWHERE YOU GO! Sensational new Ferrite Selective Tuner — Permalloy Crystal diode. Super SPEAKER—PIPHONE, durable black and gold plastic case.

SEND ONLY \$2.00 (bill, ck, mo) and pay postman \$4.99 COD (postage on arrival or send \$6.99 for postpaid delivery). SENT COMPLETE READY TO LISTEN WITH LIFETIME GUARANTEE. Nothing extra to buy—ever. Available only from: MIDWAY COMPANY Dept. WPL-11 KEARNEY, NEBRASKA

QUAL-KITS ARE EASIEST!



Hi-Fi Amplifier Kit \$28.95
and they have the finest features and specs. Fully illustrated step-by-step 28-page manual makes assembly a snap! WRITE FOR FREE CATALOG! Add 10% for new Federal Tax.

Hi-Fi AM-FM Tuner Kit \$28.95

QUALITY ELECTRONICS
Dept. P-11 New York 13, N. Y.

2E26 modulated with a 6N7. When the plate of the 2E26 got red, he reduced the voltage. His modulation transformer was a small power transformer. The antenna was 18' high and the receiver was a Phillips, which worked okay on 40 meters, but always brought in several stations at once. In two months, this lash-up accounted for Puerto Rico, Virgin Islands, Montserrat, Antigua, Barbados, Grenada, Trinidad, Venezuela, British Guiana, and Curacao. Now in Trinidad, Boris is operating at VP4LT until he can get his own station going.

Low-Power Work. Using the "Sandwich Box" transmitter (10 watts) described in P.E. for March, 1956, **Jim, WN3GQT**, has worked 28 states in four weeks on the air using 40 meters. . . . **Dub, W4IHA**, uses the same type of transmitter, which he powers from the "accessory" socket on his AR-3 receiver. In ten weeks, he has worked 50 stations in 18 states, getting many 589/599 reports.

BFO Substitute. **Art Fregau**, (Conn.), reports that by placing an ordinary broadcast receiver on top of the old Sparton "all-band" receiver he uses to SWL, he can receive code signals by carefully tuning the broadcast receiver dial until a harmonic of its oscillator beats with the incoming code signals, to produce audible dots and dashes instead of just "thumps" from the loudspeaker.

Help Offered. **Gerry Parker** (13), **KNØGPX**, Barnesville, Minn., **M. F. "Skip" Nelson**, **W2ESQ**, 21 Knollwood Ave., Madison, N.J., and **Nathan J. Schulman** (19), 78 Atkins Ave., Brooklyn 8, N.Y., offer to help prospective amateurs qualify for their licenses.

Addresses of "News and Views" Contributors: **K2MBU**, Saw Mill R. Rd., Yonkers, N.Y.; **VE3EGG**, 64 Barrie St., Galt, Ontario, Canada; **K5BTW**, 3134 Harlandale Ave., Dallas 16, Texas; **K4DDB**, 1664 Spring Hill Ave., Mobile, Ala.; **KN4JBJ**, 403 East College St., Griffin, Ga.; **KN8VB**, 351 Willaman St., North Canton, Ohio; **KN2SZR**, 11 Ford Hill, Deposit, N.Y.; **WN1IHN**, Park St., Lisbon, Me.; **KN2SLL**, Rt. 2, Box 216, Farmingdale, N.J.; **Ben Gamboa**, Calapan, Or. Mindoro, Philippines; **Jose A. Blanco**, C/O U.S. Rubber International Corp., Cerro Largo #766-68, Montevideo, Uruguay, S.A.; **VP2LB**, I.C.T.A., St. Augustine, Trinidad, B.W.I.; **WN3GQT**, Box 399, Aliquippa, Pa.

Until next month, 73,

Herb, W9EGQ

▲▲▲▲▲ Tuning the Short-Wave Bands

(Continued from page 91)

on the ultra-high frequencies, the space satellites to be sent aloft next year to travel around the earth will be equipped with transmitters of about 10-milliwatt power operating on 108,000 mc. Our thanks to Stewart West for this information.

Current Reports

Here is a resume of the latest reports received by your Editor. Our apologies to all who do not find their reports printed. Please understand that our mail is very heavy and the column just a certain length. Please continue sending reports in, and sooner or later

November, 1956

DON'T THROW OLD RADIOS AWAY!



This giant book shows exactly how to fix them . . . without a lot of previous experience!

Just look up the how-to-do-it data on that old radio you want to fix! Four times out of 5, this giant, 3½-pound, 744-page Ghirardi RADIO TROUBLESHOOTER'S HANDBOOK gives exactly the information you need. Tells what is likely to be causing the trouble . . . shows how to fix it. Covers practically every radio receiver model made by 202 manufacturers between 1925 and 1942. Using it, even beginners can easily fix old sets which might otherwise be thrown away because service information is lacking. With a few simple repairs, most of these old sets can be made to operate perfectly for years to come.

Included are common trouble symptoms and their remedies for over 4,800 models of old home, auto radios and record changers: Airline, Apex, Arvin, Atwater Kent, Belmont, Bosch, Brunswick, Clarion, Crosley, Emerson, Fada, G.E., Kolster, Majestic, Motorola, Philco, Pilot, RCA, Silvertone, Sparton, Stromberg and dozens more. Includes hundreds of pages of invaluable tube and component data, service short cuts, etc. Price \$6.50—10-day free trial.


HERE'S HOW TO GET YOUR START

IN RADIO-ELECTRONICS

Here's basic training you can really understand . . . training that can help fit you for a good paying radio-television-electronic career! No matter what part of the work you want to do, this is the kind of training you need **FIRST!**

Ghirardi's RADIO PHYSICS COURSE is the oldest book of its kind . . . and still a best seller BECAUSE IT IS SO AMAZINGLY CLEAR AND COMPLETE. Thousands now in electronics got their start from this great book—AND THEY'LL RECOMMEND IT TO YOU TODAY!

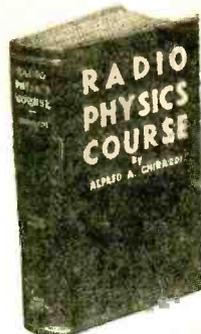Starts with Basic Electricity (over 300 pages) then takes you step by step through the entire radio-electronics field. Covers principles, theories and practices that are basic to even the most modern equipment. 972 pages; 508 pictures; 856 helpful self-review test questions. Price only \$6.50.



More experts got their basic training from this big book than any other of its type! 36 courses in one!

10 DAYS FREE TRIAL

Dept. PE-116, RINEHART & CO., INC.,
232 Madison Ave., New York 16, N. Y.

Send book(s) checked for free examination. In 10 days, I will either send price shown (plus postage) or return books postpaid and owe nothing.

Ghirardi's RADIO TROUBLE-SHOOTER'S HANDBOOK, \$6.50. Ghirardi's RADIO PHYSICS COURSE, \$6.50.

Name

Address


City, Zone, State

(OUTSIDE U.S.A.—\$7.25 each, cash only. Money back if books are returned in 10 days.)

Have you ever wondered how a Hi-Fidelity Loudspeaker produces sound?

Send for this FREE book revealing the inner secrets of the loudspeaker—told in a fascinating easy-to-understand manner. Illustrated with delightful cartoons and diagrams—a wonderful guide!

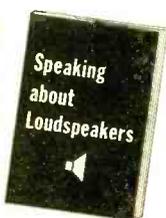This authoritative book is FREE—just send a dime to cover cost of mailing.



UNIVERSITY LOUDSPEAKERS, INC.



University Loudspeakers, Inc.
80 So. Kenisco Ave., White Plains, N.Y.

Gentlemen: Please send me a copy of "Speaking about Loudspeakers." Enclosed is 10c to cover the cost of mailing.

Desk, A-22

Name _____

Address _____

City _____ Zone _____ State _____

TALK · LISTEN · AROUND THE WORLD!



WITH THIS RADIO AMATEUR TRANSMITTER-RECEIVER!

SENDS AND RECEIVES THOUSANDS OF MILES on Amateur 80 and 40 meter bands—also, Aircraft and foreign bands (3 to 8 mc). PORTABLE, SELF-CONTAINED, BATTERY POWERED! NO AC PLUG-INS. NO DANGEROUS HI-VOLTAGES. Low cost battery lasts for MONTHS. Crystal controlled transmitter—Power input up to 5 watts—ENOUGH TO TALK 1 MILE OR 1000. REGENERATIVE RECEIVER pulls in weakest stations. Front Panel Send-receive switch—SIMPLIFIED—PHANTOM—SAFE for radio beginners (NOVICE). Easy to get license. Full information included.

No troublesome relays or complicated hookups. Uses any standard antenna. Size only 6" x 4" x 3". Wt. 3 lbs. TESTED—PROVEN—SIMPLIFIED—PHANTOM—SAFE for radio beginners (NOVICE). Easy to get license. Full information included. SEND ONLY \$5.00 (bill, check, mo) and pay postman \$9.95 C.O.D. postage on arrival or send \$14.95 and we will send postpaid. Complete kit includes all parts, tube, full instruction, lens batteries and crystal—or (COMPLETELY WIRED) AND TESTED FOR \$19.95! Steel Cabinet \$2.00 extra. Rush order today—NOW! WESTERN RADIO DEPT. BNE-11 KEARNEY, NEBRASKA

RADIO COURSES

FCC LICENSE PREPARATION

- COMMERCIAL
- AMATEUR
- CODE BRUSH-UP
- THEORY

TELEVISION AND RADIO SERVICING

Residence Courses Only

Personal Counseling Approved for Veterans

YMCA TRADE & TECHNICAL SCHOOL OF N. Y.

15 West 63 St. New York 23, N. Y.

EN. 2-6117

Catalog P.-E.



MOVING?

BE SURE POPULAR ELECTRONICS FOLLOWS YOU. PLEASE SEND YOUR CHANGE OF ADDRESS TO

POPULAR ELECTRONICS

CIRCULATION DEPARTMENT

64 E. Lake St.

Chicago 1, Ill.

yours will appear. All times listed are Eastern Standard, using the 24-hour system.

Australia—One of the lesser-heard stations is VLW9, a regional domestic station in Perth. This one can be heard on 9610 kc. with Eng. at 0845-1030 s/off. Music, popular and classical, and variety programs are featured. (BV)

Belgian Congo—*Radio Congo Belge*, Leopoldville, 9380 kc., usually has a good signal with popular and variety music at 0020-0100. News in French follows the ID at 0100. (BV)

Bolivia—CP5, *Radio Illimani*, La Paz, is now heard on 9555 kc. from 0600 s/on until 0700 fade-out. It is also on at 1900-2200 but heavy QRM usually mars reception. (RL, DX)

Brazil—*Radio Ministerio da Educacao* is again active on 17,875 kc. and can be heard after Cologne goes off at 0800. It apparently does not operate during the evening. *Radio Nove de Julho*, Sao Paulo, is a new station on 11,855 kc. and is noted at 1900-2100 with programs in Portuguese. (RL)

Two other new stations are *Radio Capacabana*, 4960A kc., with a program in German at 1700-1730, and *Radio Alanguara* on 5035 kc. No other details on either as yet. (DX)

Canada—Readers will recall that the Canadian heard a few months ago on 7920 kc. turned out to be the sixth harmonic of the m.w. station on 1320 kc. Another sixth harmonic is currently noted on 7320 kc. The engineer of CKCW, 1220 kc., is asking for reports in hopes of eliminating this harmonic. Reports should go to CKCW, Moncton Broadcasting Ltd., Knights of Pythias Building, Moncton, New Brunswick, Canada. (PM and others)

Canary Islands—*Radio Atlantico*, Las Palmas, 9490V kc., has popular and dance music at 1700-1900. Announcements are in English and Spanish; reports are welcomed. (PB)

Ceylon—Colombo is operating on two new outlets in the VOA Service, on 17,800 kc. at 1230-1600 to Africa, replacing 17,845 kc., and on 11,835 kc. at 1400-1600 with "Music USA," replacing 11,875 kc. (RL)

Costa Rica—T1FC, *The Lighthouse of the Caribbean*, San Jose, is often readable from 0700 to 0000, but peak signal is around 2300-0000 when they present religious programs in English. They operate on 9645 and 6037 kc. (TZ, CH, RS)

Denmark—OZF, *The Voice of Denmark*, 9520 kc., Copenhagen, has English to N.A. at 2100-2130, repeated at 2230-2300. The half-hour preceding each xmsn is in Danish to Danish listeners in N.A. The DX program can be heard Tuesdays at 2115 and 2245. This program is prepared by the *World Radio Handbook*. (SD, AF, NS)

Ecuador—HCJB, Quito, operates on 11,915, 11,115, and 9745 kc. Monday is a silent day. Station slogans are *Call of the Andes* and *Heralding Christ Jesus Blessings*. They carry English programs, mostly of religious nature, from 2100 to 0000. In this, their 25th anniversary, they are using their new 50-kw. xmtrs. The station sends a nice picture of the entire staff. (CM, MG, TW, LW, MA)

New s.w. stations in Ecuador include: HC-3RM, *Radio Cultura Machella*, Machella, 4845 kc., 250 watts, and HCSJC, *La Voz de San Seda* (?), 3380 kc., 220 watts. Stations that

have returned to the air are HC2ET, *Radio El Telegrapho*, 4825 kc., 250 watts, and HC2DC, *Radio Senit*, 6150 kc., 250 watts. (DX)

England—The Overseas Service of the BBC, London (NOT the General Overseas Service), is heard in a daily broadcast of recorded music announced in English at 2215-2245 on 3975A kc. Other channels in dual are 17,715, 15,447, 11,700, and 9625 kc. The 3975-kc. channel is well heard despite QRM from the 75-meter amateur phone stations. The BBC is on 17,700 kc., replacing both 15,310 kc. for the N.A. Service between 1000-1600, and 17,810 kc. for the General Overseas Service to N.A. at 1600-1930. (SW)

French Camerouns—*Radio Douala*, a new outlet on 9900 kc., can be tuned at 1300-1400,

SHORT-WAVE ABBREVIATIONS

A—Approximate frequency
 BBC—British Broadcasting Corp.
 Eng.—English language transmission
 ID—Identify, identification
 IS—Interval signal between transmissions
 kc.—Kilocycle
 L.A.—Latin America (n)
 mc.—Megacycle
 m.w.—Medium wave
 N.A.—North America (n)
 QRM—Interference from other stations
 s.w.—Short-wave
 s/off—Sign-off of station
 s/on—Sign-on of station
 xmsn—Transmission from station
 xmitr—Transmitter used by station
 V—Frequency varies
 VOA—Voice of America

with news at 1300-1310. Reports go to *Radio-diffusion du Camerouns*, Yaounde. (DX)

French Equatorial Africa—*Radio Brazzaville*, 11,970 kc., has an English period to North and South America at 1835-1900, parallel with 9625 kc. A "Mail Bag" and listener's request program can also be noted at 0650, but this is not beamed to N.A. (DC, TW, KM, JM)

Goa—English programs are broadcast by *Radio Goa* at 0130-0800 and 1000-1130 on 4890, 7071, and 9610 kc., according to a letter received from the station. The power for 4890 kc. is 5000 watts. (WRH)

Gold Coast—ZOY, Accra, can be heard nightly at 0055 s/on with a woman giving the schedule. They relay BBC news at 0100. (DX)

Guatemala—*Radio Universal*, 6208A kc., is heard at 0000-0035 with a musical program and ID of *Radio Universal en Guatemala*. This one verified with a letter but didn't list the frequency. The call is TGHC and it relays m.w. station TGHB. (PM)

New stations in Guatemala include: *Radio Programas de Guatemala*, TGZB, 3355 kc., 90 watts; TGZA, 6160 kc., 250 watts; *Radio Victoria*, TGLA, 5970 kc., 100 watts; and TGLAB, 4900 kc., 200 watts. (DX)

Hong Kong—*Radio Hong Kong*, 3940 kc., is heard at 0830-0900 with fair-to-good signals in Chinese. At times they may have cricket matches in Chinese. (GN)

Indonesia—*The Voice of Indonesia*, Djakarta, is heard on YDF6, 9710 kc., with a xmsn in English at 0930-1030. The program is made up of news, topical talks, and good music. They identify often throughout the English session. (BV)

Jamaica—*Radio Jamaica*, Kingston, can be noted on 4950 kc. mornings around 0600-s/on

EZ2 Build

Introducing the Brand New, Low-Cost, Top-Performing

90 Watt Globe Chief Kit (75 WATTS FOR NOVICE USE)



Just \$5.00 Down
 Cash: \$49.95

Only
\$500
 per mo.

Wired Form:
 \$64.95

All the power a Novice can use plus 20% safety factor in case of local line voltage drop.

Complete Instruction manual; all parts; chassis pre-punched; wires pre-cut and pre-tinned. No experience necessary.

- ✓ Completely bandswitching, 160-10M Built-in power supply!
- ✓ Pi-Net matches antennas, 52-600 ohms
- ✓ Sturdy, compact; handsomely styled
- ✓ Modified Grid-Block keying for maximum safety
- ✓ Provisions for Speech Modulator* and VFO input
- ✓ 100% trade-in value on Globe King or new Champion, within 1 year

* The new WRL Plug-In Screen Modulator Kit (complete) has been designed for use with the Globe Chief; may also be used with the Johnson Adventurer, Heath Kit AT-1, or similar CW Xmittrs. . . . \$13.95
 SEND FOR DETAILED BROCHURE TODAY!

FREE 1957 CATALOG!

WORLD RADIO LABORATORIES
 3415 West Broadway
 Council Bluffs, Iowa

Please rush to me:
 Free 1957 Catalog
 Globe Chief Brochure



NAME: _____

ADDRESS: _____

CITY & STATE: _____

36" FLEXIBLE SHAFT

For Precision Working
... Hard-To-Get-At-Places!

Reg. \$9.95...
Now **\$5.95**

plus 35c p. p. and hdlg.

This handy flexible shaft with complete handle increases the utility of your electric drill, electric motor, grinder or drill press where $\frac{1}{2}$ " shaft can be attached. Easily attached to do grinding, carving, buffing, sanding, polishing, drilling, slotting, engraving, buffing, etc., on wood, metal, glass and plastics. The Flexible Shaft is tamper proof, sealed and designed for lifetime service. Can be operated at speeds up to 6000 RPM.

12 Pc. Needle & Warding FILE SET




ONLY **\$2.49** (plus 25c hdlg. & pstg.)

Made from the best quality tool steel, to fit the exacting requirements of mechanics, watch and jewelry craftsmen, hobbyists. Attractive kit contains the following: 12" long needle and warding files with high test cutting qualities: round, flat, knife, square, triangular. In all textures: fine, medium fine, medium, medium coarse, coarse. Comes with polished wood handle and new type steel grip chuck.

Send Check or M.O. C.O.D. fee extra.

75c ea. for Finest Imported PRECISION PLIERS

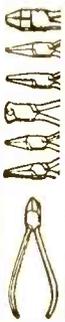- Flat Nose
- Combination
- Diagonal Cutter
- End Cutting Nippers
- Round Nose
- One Side Flat—One Side Round
- Snipe



FOR JEWELERS, OPTICAL WORKERS, HOBBYISTS, CRAFTSMEN OF ALL KINDS! These superb German instruments are of deep forged, heat-treated high quality tool steel, fabricated to most exacting specifications. All over ground and polished to smooth hard surfaces. Smooth working joints with just the right tension. Jaws meet perfectly to safely and securely hold even the most delicate objects in the hard-to-reach corners and angles. Each plier is 4" long and a veritable gem of precision and strength.

75c ea. ... all 7 for **\$5.00** p.p.d.

SET OF 6 SWISS PRECISION SCREWDRIVERS

NEW LOW PRICE **\$1.25** p.p.d.

Perfect for jewelers, watchmakers, hobbyists, etc. SIX DIFFERENT SIZES:

No. 3	No. 6
No. 4	No. 8
No. 5	No. 10

Knurled body grip assures easy handling. Finest steel and craftsmanship. A hard-to-beat value from Switzerland.

Send Check or M.O. C.O.D. fee extra. MONEY BACK GUARANTEE

SCOTT-MITCHELL HOUSE, INC. DEPT. M-265, 611 BROADWAY NEW YORK 12, N. Y.

YOUR F. C. C. LICENSE

GUARANTEED PREPARATION

Get Your License by the Easy Emig Method—Paced at Your Speed—Study Time at Your Convenience. Write Now For Free Information

EMIG SCHOOL OF ELECTRONICS

4902 SUNSET BLVD. HOLLYWOOD 27, CALIF.

Please Be Sure to Mention
POPULAR ELECTRONICS
When Answering Advertisements



Be a "key" man. Learn how to send and receive messages in code by telegraph and radio. Commerce needs thousands of men for jobs. Good pay, adventure, interesting work. Learn at home quickly through famous Candler System. Qualify for Amateur or Commercial License. Write for FREE BOOK, CANDLE SYSTEM, C.O.D.
Dept. 5-M, Box 928, Denver 1, Colo., U.S.A.

BIG MONEY FOR YOU THROUGH V.S.I. ELECTRONICS & TV SCHOOL

AGE—NO BARRIER—FUTURE UNLIMITED—EQUIPMENT—ALL THE LATEST—TECHNIQUES—THE BEST APPROVED FOR VEIS—CORRESPONDENCE OR RESIDENCE

WRITE FOR YOUR CATALOG—NOW

V.S.I. TELEVISION SCHOOL

4570 Firestone Blvd. Dept. P.E. South Gate, Calif.

to 0700 and evenings at 1730-2215. All xmsns are in English; news is heard at 2200-2205. (MP, NS)

Kashmir—Radio Kashmir is presently operating from Srinagar at 2100-2300 and 0230-0330 on 7270 kc., and at 0730-1230 on 6110 kc. This is a good catch for anyone. (WRH)

Lebanon—The Lebanese Army Signal Corps operates a station on 6500 kc. with 350 watts. It is scheduled at 0930-1100 on Tuesday and Saturday only and relays other programs of Army station. Further details requested. (DX)

Luxembourg—Radio Luxembourg, Junglinster, is currently constructing new short-wave facilities to be heard all over world. (CM)

Malaya—All stations of the British Far Eastern Broadcasting Service are now identifying as Singapore BBC Far Eastern Station. (DX)

Mexico—XEXE, Leon, formerly at Mexico City, is again in use on 11,900 kc. It operates at 0645-0100 in parallel with XEXG, 6065 kc., relaying m.w. XEX. (RL)

XEOI, Radio Mil, 6010 kc., Mexico City, transmits programs evenings for Southwest

SHORT-WAVE CONTRIBUTORS

Maurice Ashley (MA), Wichita, Kansas
Robert Barnes (RB), Long Beach, Calif.
Port Baughman (PB), Rockport, Texas
John Beaver (BV), Pueblo, Colo.
Bob Buckner (BB), Victoria, Texas
Donald Chester (DC), Woodlawn, Tenn.
Jim Cumbie (JC), Dallas, Texas
Gerry Dexter (DX), Waterloo, Iowa
Jimmy Duncan (JD), Horse Cave, Ky.
Silas Dunn (SD), Little Rock, Ark.
Arthur Fregeau (AF), Bristol, Conn.
I. J. Gatenby (JG), Vancouver, B.C.
Manuel Greco (MG), Atlantic Highlands, N. J.
Harley Grimmer (HG), Chamcook, N. B.
Clifton Hunn (CH), Lawton, Okla.
Ronald Jones (RJ), Indianapolis, Ind.
Roger Legge (RL), McLean, Va.
John Mann (JM), Montreal, P.Q.
Paul Mathieu (PM), Southbridge, Mass.
Chuck Maxant (CM), Baldwin, N. Y.
Kurt Metzger, Jr. (KM), Ortonville, Mich.
Jimmy Monahan (MO), East Haven, Conn.
Gordon Nelson (GN), Longwood, Calif.
Martin Potter (MP), London, Ont.
Joel Richmond (JR), Mattapan, Mass.
Dale Smith (DS), Milan, Pa.
Rick Stearns (RS), Osage, Iowa
Norman Syver (NS), Elverson, Pa.
Bill Waltz (BW), Seattle, Wash.
Tom Watkins (TW), Mansfield, Ohio
Stewart West (SW), Union, N. J.
L. Richard Woodyatt (LW), Scranton, Pa.
Ted Zagrodnick (TZ), Johnstown, Pa.
World Radio Handbook (WRH)

USA, Central and South America. They feature United States pop records with Spanish commentary. Their address is Fomento de Radio S.A., Ayuntamiento 101, Mexico City. XEHH, La Voz Potisina, Mexico City, is a good one for L-A music during most of the day on 11,880 kc., evenings on 11,880 kc., as is companion station. XERH, 1500 kc. (JC)

Mozambique—Radio Clube de Mozambique is being widely reported. It can be tuned on 15,085 kc. around 1500-1515 in a test xmsn of news and music with a gong before each ID. This xmsn is reported parallel with 17,795 kc. to Europe. Reports go to Box 594, Lourenco Marques. (SW)

CR7BE is noted on 11,984 kc. at 0030-0100 s/off with Portuguese language and popular

music. ID is *Aqui Radio Clube de Mozambique*. (BV)

The outlet on 4920 kc. can be heard in English around 2310-2320 but this might be difficult due to QRM. (JD)

Netherlands—*Radio Nederland*, Hilversum, presents a program called "Mail Bag" on Sundays at 2245-2300 on 9590 kc. They invite reception reports, comments, and record requests. Reports go to Mr. Edward Startz, P.O. Box 136, Hilversum. (RJ, TW)

New Zealand—*Radio New Zealand* has moved from 15,220 kc. to 15,110 kc. for its Australian beam at 2300-0115 s/off, dual to 15,280 kc., to the Pacific Isles. The DX program gave the schedule at 1905-0115 on 15,110 kc. and at 1500-1900 on 15,220 kc. (SW, BV)

Other outlets on 6080 and 9540 kc. can be noted 0100-0445 s/off with news, music, and talks. (RB)

Pakistan—*Radio Pakistan* can be heard on 21,580 kc. at 1330-1400 in English, with recorded music, to Turkey, and on 15,400 kc. at 1940-2000 with native music. (DS, MG)

Peru—OAX4T, *Radio Nacional del Peru*, 9562 kc., Lima, is often heard evenings around 2130 with excellent musical programs and announcements in Spanish. (BW)

New stations operating are: OAX1D, *Radio Chiclayo*, Chiclayo, 3380 kc.; OBX4Z, *Radio Luz*, Lima, 6115 kc.; and OAX8E, *Radio Loreto*, Iquitos, 6250 kc. (RL)

Portugal—Lisbon has resumed use of 21,495 kc. and is heard at 0600-0800 in dual with 17,895 and 21,700 kc. A new channel is 15,100

kc., heard at 1700-2030. The 15,380-kc. channel has apparently been dropped. The 17,895-kc. outlet can also be tuned in English at 1200-1245, in Portuguese after 1745. (RL, BV)

Spain—*Radio Mediterraneo*, Valencia, 6995 kc., has been heard again at fair level at 1800-1830 s/off with programs of Spanish music. Identity is *Transmite Radio Mediterraneo de la Sociedad Espanola de Radiodifusion*. Closes with *Viva Franco, Arriba Espana* and the Spanish National Anthem. (PM)

Switzerland—HER4, Berne, 9590 kc., is often heard, dual with HER3, 6165 kc., and HER5, 11,865 kc., in English at 2320-0000 with discussions, news, and musical programs. This is in N.A. Service. (BB and many others)

Tahiti—*Radio Tahiti*, Papeete, 6135 kc., can be heard in French and native languages at 2350-0030. English segment was changed from 0245-0300 to 0230-0245. (BW, JG)

Tangier—*Radio Tangier International*, not to be confused with WTAN, is testing at various times during the day with English and Danish announcements. It can be noted at 1730-1740 and 1800-1810. Test xmsns usually last about ten minutes. An announcement stated that a service in Danish probably would be started soon. Reports go to 33 Goya Street, Tangier, North Africa. (SW, PM, HG)

Union of South Africa—Johannesburg, 25,880 kc., is operating at 0730-0845 Monday to Friday in English and Afrikaans. It has also been noted at 1230-1345. The 3290-kc. outlet carries English at 1300-1600, Afrikaans at the same time on 3380 kc. (DX, MO)

-30-

Get This Valuable Book

FREE

150 Radio Picture Patterns and Diagrams Explained

Just For Examining COYNE'S New Set

"Applied Practical Radio-Television"

on 7 DAY FREE TRIAL!

NOW! 7 BIG BOOKS IN ONE GREAT SET!

Yes, you get this big, brand new book, "150 Radio-Television Picture Patterns and Diagrams Explained," absolutely FREE! Just off the press. Gives complete 11 x 22" Schematic Diagrams on leading models Radio and TV Sets. Easy-to-read, large 8 1/2 x 11" pages, with full instructions on how to use the diagrams. A "must" in every repair kit. You get this book as a FREE Gift for asking to see Coyne's new 7-book set, "Applied Practical Radio-Television!"

AT LAST! MONEY-MAKING "KNOW-HOW" ON TRANSISTORS, COLOR TV AND SERVICING

Coyne's great 7-volume set gives you all the answers to servicing problems—quickly! For basic "know-how" that's easy to understand, you'll find everything you want in Volumes 1 to 5 on over 5000 practical facts and data. Every step from fundamentals to installing, servicing and troubleshooting all types of radio and TV sets. So up-to-date it covers COLOR TV, UHF and the latest on TRANSISTORS. All this plus Volume 6—NEW Coyne TECHNICAL DICTIONARY with over 4000 definitions of the latest terms, symbols and abbreviations in radio-TV, electronics and electricity.

EXTRA! 900-PAGE TELEVISION CYCLOPEDIA INCLUDED

And then, for speedy on-the-job use, you get volume 7—the famous Coyne TELEVISION CYCLOPEDIA. It answers today's television problems on servicing, alignment, installation, etc. In easy-to-find ABC order, cross-indexed. Use this 7-volume TV-RADIO LIBRARY FREE for 7 days; get the valuable Servicing Book ABSOLUTELY FREE!

SEND NO MONEY! Just mail coupon for 7-volume set on 7 days free trial. We'll include book of 150 TV-Radio Patterns and Diagrams. If you keep the set, pay \$2 in 7 days and \$2 per month until \$24.50 plus postage is paid. (Cash price, only \$22.95.) Or you can return the library at our expense in 7 days and owe nothing. YOU BE THE JUDGE. Either way, the book of TV-Radio Patterns is yours FREE to keep! Offer is limited. Act NOW!

FREE BOOK—FREE TRIAL COUPON!

Educational Book Publishing Division
COYNE ELECTRICAL SCHOOL, Dept. B6-PE
500 S. Paulina St., Chicago 12, Ill.

YES! Send 7-Volume "Applied Practical Radio-Television" for 7 days FREE TRIAL per your offer. Include TV-Radio Patterns & Diagram Book FREE.

Name Age

Address

City Zone State

Where Employed

Check here if you want library sent C.O.D. You pay postman \$22.95 plus C.O.D. postage on delivery. 7-day money-back guarantee.

Educational Book Publishing Division

COYNE ELECTRICAL SCHOOL

500 S. Paulina St., Dept. B6-PE Chicago 12, Ill.



**ELECTRONIC
HOBBYISTS...
TAPE FANS...
HAM OPERATORS!**

Want to swap messages with friends in other states and countries? There are thousands of hobbyists all over the world who'd like to hear from you.

You'll find their names and addresses in the new **PEN PALS** magazine! Be sure to buy your copy of **PEN PALS**... now on sale at your favorite newsstand.

Shrinks Hemorrhoids New Way Without Surgery

Science Finds Healing Substance That Relieves Pain—Shrinks Hemorrhoids

For the first time science has found a new healing substance with the astonishing ability to shrink hemorrhoids and to relieve pain—without surgery.

In case after case, while gently relieving pain, actual reduction (shrinkage) took place.

Most amazing of all—results were so thorough that sufferers made astonishing statements like "Piles have ceased to be a problem!"

The secret is a new healing substance (Bio-Dyne*)—discovery of a world-famous research institute.

This substance is now available in *suppository* or *ointment* form under the name *Preparation H**. Ask for it at all drug counters—money back guarantee.

*Reg. U.S. Pat. Off.

INVENTORS

Send for
PATENT INFORMATION
Book and
INVENTOR'S RECORD
without obligation
GUSTAVE MILLER
116-PE WARNER BUILDING
WASHINGTON 4, D. C.

REGISTERED PATENT ATTORNEY
ASSOCIATE EXAMINER
U.S. PAT. OFF. 1922-1929
Patent Attorney & Advisor
U. S. NAVY DEPT. 1930-1947
PATENT LAWYER

**ENGINEERING
DEGREE IN
27 MONTHS**
INDIANA TECHNICAL COLLEGE

B.S. Degree, Aeronautical, Chemical, Civil, Electrical, Mechanical, & Electronic Eng. (inc. Radio & TV), B.S. degree in 36 mo. in Math., Chem., Physics, Prep. courses. Low rates. Earn board. Large industrial center. Students from 48 states, 21 countries. Demand for grads. G.I. appr. Enter Dec., Mar., June, Sept. Catalog. 2311 E. Washington Boulevard Fort Wayne 2, Indiana



The Hi-Fi Boost

(Continued from page 55)

matter of personal preference, the kind of thing that could require different control settings to suit different moods as well as room acoustics.

Then, too, components other than the amplifier may not have perfectly flat responses. It is by no means an insult to a phono pickup to say that it is "down 3 db at 15,000 cps." Neither can a speaker be deemed inferior because its response curve "drops several db below 50 cycles." A small amount of treble and bass boost respectively can restore the entire system to virtually flat response.

Offhand, it would seem that two more knobs would be required, winding up with a total of four tone controls: bass boost, bass cut, treble boost, and treble cut. Thanks to the ingenuity of hi-fi designers, the number of controls has been held to two—which provide all the tonal adjustment required. "Continuously variable" controls—one for bass cut and boost, the other for treble cut and boost—are now the rule in hi-fi amplifiers. Because of the wide range these controls cover, as well as the many intermediate settings and combinations of settings they provide, they are

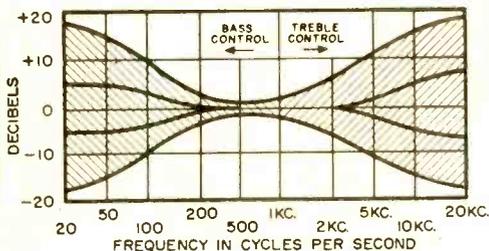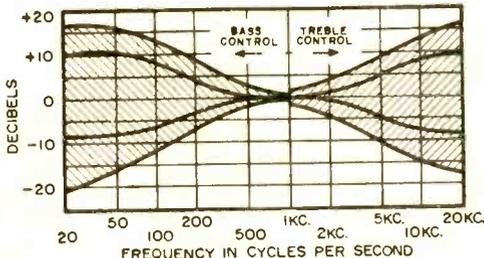

Ranges of control available with the circuits shown in (C) and (D) on page 55 are shown respectively in the two graphs above. Shaded areas indicate total range. Any combination of values between outer lines is possible. Note that the bottom graph shows that the point in the frequency spectrum, where tonal boost or cut begins, can be varied as well as the actual amount of boost or cut. For this reason, the circuit—the Baxandall system—is generally rated as best for hi-fi.

generally called "universal" tone controls.

One very widely used type is shown in the schematic (C) on page 55. The first graph on page 126 is the range of control available with this circuit. Given a pair of such controls, the listener becomes a virtual conductor of his own orchestra, and can add such coloration and emphasis (or de-emphasis) as he deems necessary for over-all tonal balance. As is true of less notable conductors, however, some audiophiles insist on overdoing it.

Generally accepted procedure for correct use of tone controls is to start by leaving them in the "flat" or uniform response position. This is usually the center position on the knob. As the listener becomes more perceptive, and more sensitive to the peculiar aspects of his own listening area, he may find that moderate amounts of boost or cut may be used until the system sounds "just right." Cranking up both treble and bass controls as far as they will go proves nothing about the fidelity of the system and generally results in jarred nerves.

Baxandall Tone Controls. While great flexibility and range of control is afforded by the system just described, it has what many consider a slight drawback. The point in the frequency spectrum at which boost or attenuation begins is always approximately the same, about 800 cps. Thus, if 6 to 8 db of boost is really needed at 50 cycles to bring a particular speaker system into line, it can only be achieved by including about 3 db of boost at 300 cps. But no boost at all is really desired at 300 cps—it would lend a boomy quality to the sound, particularly to male voices.

This difficulty is overcome by a recent type of universal tone control system which uses feedback. The basic schematic for this system is shown in diagram (D) on page 55; its range of control is shown in the second graph on page 126. Both boost and attenuation, as well as the point at which these effects begin, are made completely variable, depending on the control setting. For this reason, it is known as a "variable crossover" tone control, as well as by the name of its designer, P. J. Baxandall. This type of control system is considered by many to provide more pleasing results and flexibility. As a result, it has gained favor with many manufacturers in recent years.

The diagrams on page 55 and the two graphs (left) should help in identifying tone control circuits in amplifiers. To assess fully the merits of each system, the prospective buyer should try the action and listen to the results of the various systems. Don't ignore tone controls and the importance of using them correctly. They can pay off in years of pleasurable listening.

POPULAR SAMS BOOKS FOR THE EXPERIMENTER • AMATEUR • TECHNICIAN



USE THIS HANDY ORDER FORM

- Attenuators, Equalizers and Filters.** Describes the design, application and theory of operation of every type of Attenuator, Equalizer and Wave-Filter used in audio, recording and reproducing systems, both professional and home-type. 176 pages; 5½ x 8½". \$2.75
Library-bound deluxe edition \$4.00
- Transistors.** The first complete, practical book on Transistors and their application in TV-Radio-Electronics. Explains theory, circuitry, installation, testing techniques and servicing. 100 pages; 5½ x 8½"; illustrated \$1.50
- So You Want to Be a Ham.** Shows you how to get your license and acquire equipment. Covers: Conquering the Code, Getting Your Ticket, Going on the Air, etc. 196 pages; 5½ x 8½"; illustrated \$2.50
- Basic Radio Manual.** Complete course covers theory, definitions, components. Includes section on actual projects that translate theory into practice. 248 pages; 8½ x 11"; illustrated \$5.00
- Basic TV Manual.** Covers all phases of TV set operation and design from picture tube to antenna. Includes project section demonstrating theory in action. 312 pages; 8½ x 11"; illustrated \$5.00
- Atomic Radiation, Detection and Measurement.** Helps you understand nuclear science and its applications. Covers circuitry and operation of all types of detection devices. 200 pages; 5½ x 8½" \$3.00
- Recording & Reproduction of Sound.** Oliver Read's best-seller on all phases of Audio. Full analysis of recorders and recording techniques. Complete data on amplifiers, speakers, mikes, phono equipment, P.A., etc. 810 pages; 6"x9"; profusely illustrated \$7.95
- Radio Receiver Servicing.** Covers all basic receiver types—gives time-saving hints for solving common troubles, such as dead set, weak set, noisy set, etc. 192 pages; 5½ x 8½"; illustrated \$2.50
- Tape Recorders.** Explains recorder theory, tape characteristics, how recorders work; covers motorboard mechanism, drive motors, volume indicators, bias oscillators, amplifiers, magnetic heads, equalization circuits. 176 pages; 5½ x 8½"; illustrated \$2.75

HOWARD W. SAMS & CO., INC.

Order from any Radio & TV Supplier-Wholesaler, or mail to Howard W. Sams & Co., Inc., Dept. 14-1, 2201 E. 46th St., Indianapolis 5, Ind.

Send books checked above. My (check) (money order) for \$..... is enclosed.

Name


Address

City Zone State

(outside U.S.A. priced slightly higher)

Bargain Basement

STYLUS PRESSURE GAUGE

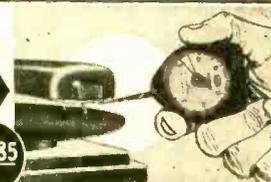

Precision stylus pressure gauges available in 2 models calibrated from 2 to 15 grams or 3 to 30 grams each way from center position.

The extra indicator "hand" will remain at the maximum reading of the device until reset by a knob on the dial face.

Send for Folder Code GIOJU

985

CORRECT STYLUS PRESSURE NOT ONLY GUARANTEES MINIMUM STYLUS AND RECORD WEAR, BUT ASSURES SOUND PICK-UP AT MINIMUM DISTORTION.

200-CS Lafayette St.
New York 12, N. Y.

GEO. SCHERR CO., INC.

TELEPHONES




Desk Stand Style
Slightly used but in excellent condition
Many Valuable Uses

Inter-House Phones House to Barn, etc.
Loud Suckers Microphones
Educational Purposes Toys, etc.

Come complete, ready to use **\$2.75** Postpaid
with wiring diagrams included. in U.S.A.
Two complete for only \$5.00.

TELEPHONE LAMP KIT—with illustrated instructions for making Desk Telephone Lamp including all parts (lamp, nipples, push switch, cord, plug, etc.) \$6.50 Ppd. (Shade is not included).

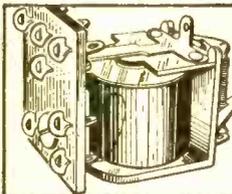MICROPHONE, Dept. X-607, 1760 W. Lunt Ave., Chicago 26, Ill.



LITTLE "JEWEL" R/C RELAY

The Mighty Mite of the R/C field. Weighs less than 1/2 oz. l Only 3/4" H x 17/32" W x 1-1/16" L. Highly sensitive—extremely rugged. Pulls at 1.4 Ma—drops out 1.2 Ma D.C. S.P.D.T. 5000 ohm coil.

F-260.....Net 2.75

Lafayette Radio 100 SIXTH AVE. BOSTON 10, MASS. 110 Federal St
NEWARK 2, N. J. 24 Central Ave
NEW YORK, N. Y. PLAINFIELD, N. J., 139 W. Second St
BROOKLYN 50, N. Y., 542 E. Fordham Rd
DEPT PE2 Include postage with order

SIMPLEX—DUPLIX—TRIPLEX

RADIO CONTROL OF MODELS—ALL SYSTEMS AVAILABLE FROM

ESSCO RC PRODUCTS—

WORLD'S LEADING RC MATERIAL SUPPLIER

Build the new multicontrol R/C system described in this issue.

Complete deluxe parts kit to build your own w/relays... \$16.95

Complete factory wired-tested, ready for use... 21.95

A Twin Tube Receiver At Price Of Single Tube

Super special Essco-Lorenz receiver for beginners and old-timers

too. Factory wired. Includes sensitive reliable Sigma relay and

Special Essco Control Panel... 14.95

Complete deluxe parts kit to build your own... 9.95

Essco as always brings you your best buy in XMTRES. Housed in

handsome black wrinkle case with sturdy whip antenna, remote

click type keyer. Diode antenna tuning network enables easy

tuning for maximum output. Complete factory wired ready for

use (except batteries). 5 watt MAC II or 3 watt Lorenz MOPA.

Both models at same low price, with Free FCC form... 21.95

Essco Products Available Also From Your Hobby Shop Dealer

ESSCO RC PRODUCTS 58 WALKER ST.
N.Y.C. 13, N. Y.

RAD-TEL SPECIAL DEAL!

ASSORTMENT OF Pkg. of 100

100 RADIO & TV TUBES

All Packaged!
All Popular Types!

RAD-TEL TUBE CO. Dept. B 115 Colt St.
Irvington, N. J.

\$11.89

HI-FI Custom-Kit

YOU can have superb Hi-Fi in your car with this amazing Rear Deck Speaker Kit. Response 50/15,000 cps. with Big 6"x9" woofer and extended range tweeter. Easy to install. Includes leads, attractive 3-pos. switch, handsome chrome grill, hi-fi speaker, complete instructions.

Money Back Guarantee

ONLY **\$795**

(Regular list \$15.95)

ORDER TODAY! Give car make and year. Include payment with order for prepaid shipment. (If C.O.D. fees and postage extra.)

NATIONAL ELECTRONICS

6612 Euclid
Cleveland 3, Ohio

EXCLUSIVE WITH LEKTRON!



3 IN 1 TRANSISTOR RADIO KIT

Sun-Powered, Mercury Cell-Powered or Dual-Powered pocket radio. Sensitive, selective, with ample power. Sun Battery for daylight operation (operates from 100 W lamp, too); mercury cell for night—outlasts regular batteries 5 times! ALL PARTS MOUNTED—only MINUTES to assemble! Pre-drilled styrene cabinet, hi-gain transistor, loop-stick, mini. variable condenser, phone jacks, switch, knob, wire, hardware and step-by-step instructions. Ship. wt., 1 lb.

\$7.88

LEKTRON SPECIALTIES

28 GARDINER STREET

CHELSEA 50, MASS.

USED TV CONSOLES

Guaranteed in working condition

RCA 12"\$24.95
MOTOROLA 16"\$38.95
MAGNAVOX 17"\$42.95
OTHERS 19"\$54.95

ZENITH
TELEKING
ADMIRAL

Order preferred make. We'll try to accommodate.

Free indoor antenna within each set

Send Check or Money Order. No C.O.D.'s.

All sets shipped F.O.B. Newark, N. J.

TV SUPER MART, INC.

1 White Terrace
Newark 8, N. J.

Telephone: Essex 5-2152



R-1/Arr-1 RECEIVER

Brand New

\$1.95

The ever popular 220 mc. one with conversion data. Times 238-256 mc. Brand new demilitarized (input coil base broken).

Ship. wt. 6 lbs. Ea. \$1.95


Brand new. Not demilitarized. Ship. wt. 6 lbs. Ea. \$2.95

INCLUDE POSTAGE. MONEY BACK IF

RETURNED PREPAID WITHIN 10 DAYS

ESSE RADIO CO. 42 WEST SOUTH ST.
INDIANAPOLIS 25, INDIANA

TWO TRANSISTOR RADIO KIT

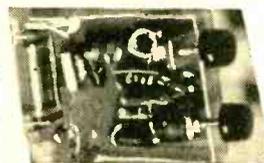

Tran-Kit Electronics Ad-
vertiser. Kit—Complete
with Battery and Plastic
Case. Step by Step In-
structions—Pictorial Dia-
grams—Schematic—Parts
List. Regenerative Cir-
cuit. Receives all Local
Stations. Shipping Weight,
8 oz. TK 101—Net \$11.80
Plus 10% F.E.T. Less
Postage. Phone for Above
\$3.98. Include Postage
with Order.

BRIDGEPORT ELECTRONICS

325 State St., Bridgeport, Conn., Dept. P.E.

**POPULAR
ELECTRONICS**

BARGAIN BASEMENT

SAVE ON THESE SPECIAL BUYS OF THE MONTH

7.95

LAFAYETTE SPECIAL R/C RECEIVER



Completely wired and assembled, with tube, ready to operate on exam free 27.25 Mc remote control band. Size: 1 3/8" x 1-15/16" x 3". Weight 3.3 oz. Uses one 1.5 volt and one 45 volt battery. Less batteries. Shpg. wt., 6 oz.

F-208Net **7.95**

Lafayette Radio 100 SIXTH AVE. BOSTON 10, MASS. 110 Federal St.
NEWARK 2, N. J. 24 Central Ave.
PLAINFIELD, N. J. 139 W. Second St.
BROOK 58, N. Y. 540 E. Fordham Rd.
Dept PE2 Include postage with order

SORRY, NO RETAIL

Resistors (in lots of 100 each, no mixed values), half-watt 10%, \$1.75; one-watt 10%, \$2.50; two-watts 10%, \$4.00/C. Tubular capacitors, 1 mf 400 V., \$3.00/C; 1 mf 600 V., \$5.00/C; .01-400 V., \$2.75/C; .01-600 V., \$3.85/C; .001-600 V., \$2.75/C; all wax impreg'd & axial leads. RCA #054 acorn tubes, \$3.00/C. Hookup wire, plastic, solid or stranded, color choice, \$3.50 #24-1000 ft. reels; \$4.25 #22-1000 ft. reels. DM-36 (used) but guaranteed \$95.00 for one hundred. Write for low-west prices on sockets; spaghetti; wirewound resistors; jacks; knobs; switches; molded mica, silver-mica, disc ceramic capacitors; adel clamps; grommets; screws; nuts; angle-brackets; terminal strips, etc. Please furnish credit ref. w/initial order. Sorry, no retail. 2/10, n/30.

GOULD GREEN, 252 Greenwich St., N. Y. C. 7

RADIO CONTROL Headquarters

For model airplanes, boats, cars, etc. FREE CATALOG "P." No operator's license required. FREE-SEND FOR FCC FORM 505 Garage Door Radio Control Transmitters & Receivers. Kits Available.

R/C TRANSMITTER & RECEIVER KIT

27 1/4 Mc. 5 Watt 2-Tube Simple Transmitter & Supersens. 2-Tube Simple Receiver—Parts incl. Drilled Bases Wound Coil, Res., Cond., SIGMA Relay, Instruc. Only **\$9.95**

SIGMA 4F RELAY: 8,000 ohm. \$3.85; 6 Reed Relay \$14.95

2-6V Battery Charger Kit \$4.95; wired 6.95

R/C BOOKS: Model Control \$1; Radio Control \$1; Handbook 2.25

CRYSTALS: 27.25 Mc. Petersen Z9A \$3.95; HOLDER 1.5

2 METERS, 150 MicroA. \$3.95; 500 MicroA 3.95

RELAY CONTROL UNIT Relay (1 1/2 Ma) Thermal Bimetal Strip, Heating Element, Hi Z Audio Choke, Mini Ailnico V Magnet, Neon Lamp, Resistors, Capacitors only .99

TUBES: XFG1, RK61, 3A4, 3AS, 1AG4, 6K4—TRANSISTORS99

Storage BATTERIES: Mini. 6V, NT6, \$2.45; 2 Volts 27A/Hour 2.75

Diethl PH WIDGET MOTOR, 27 VDC 10,000 RPM, 2" x 1" 1.95

Sigma RELAYS, 10K ohm 2 Ma DC or 110V AC SPDT 95c; SPST85

GYRO ELECTRONICS 325-P CANAL ST., N. Y. 13, N. Y.

ELECTRONIC KITS

COMPLETE KITS FOR ARTICLES

DESCRIBED IN THIS AND OTHER MAGAZINES—WRITE FOR PRICES

EACH MONTH

ALGERADIO ELECTRONICS CO.

236 N. Franklin St. Phone IV 9-0808 Hempstead, N. Y.

Classified

RATE: 50¢ per word. Minimum 10 words prepaid. January issue closes November 3rd. Send order and remittance to: POPULAR ELECTRONICS, 366 Madison Avenue, N. Y. C. 17.

When you order by mail . . .

please print your name and address clearly, be specific in your order, enclose proper amount, allow ample time for delivery.

FOR SALE

TUBES—Parts—80% off—Free List. Federal 986, 18th Ave., Newark, N. J.

COMPLETE Television sets \$11.95. Jones TV, 1115 Rambler Avenue, Pottstown, Pa.

TUBES-TV, Radio, Transmitting And Industrial Types At Sensibly Low Prices. New. Guaranteed 1st Quality Top Name Brands Only. Write For Free Catalog or Call Walker 5-7000. Barry Electronics Corp., 512 Broadway, New York 12N, N. Y.

DIAGRAMS for repairing radios \$1.00, Television \$2.00. Give make, model. Diagram Service, Box 672-PE, Hartford 1, Conn.

DIAGRAMS! Repair Information! Radios—Amplifiers—Recorders \$1.00. Televisions \$1.50. Give Make, Model, Chassis. Norelco-Philips and Ampex tubes in stock! TV Militie, Box 101-PE, Hicksville, New York.

"AUTOMATIC Garage Door Control" book; standard parts: radio or post control. Complete instructions, exploded view, photos; \$1.50. R-L Books, 13339-C Deby, Van Nuys, California. Guaranteed!

WALKIE-TALKIE. Build wireless portable radiophone for less than \$10.00. Plans for variable frequency and crystal control types, only 50¢ for both. Springfield Enterprises, Box 54-E11, Springfield Gardens 13, N. Y.

TRANSISTOR devices, walkie-talkies, VHF AM-FM portable radios, wireless mikes, etc. at wholesale prices direct from our factory. Free literature. Springfield Enterprises, Box 54-E11, Springfield Gardens 13, N. Y.

BUY Surplus radios, receivers, electronic, radar equipment. Direct from Government. List \$1.00. Box 1842BT Hartford 1, Connecticut.

DIODES, GE1N70, for crystal sets etc. Brand new. Two for \$1.00 postpaid. Miniradio, Box 468 Gainesville, Georgia.

NEW! Transistor code oscillators, professional Key and code sheet, \$6.00 postpaid. Stout, 2241-A E. Broadway, Muskegon, Michigan.

TAPE Recorded Code Course. None other comparable. Novice \$11, Details on request, Tapedcode, Box 31, Langhorne, Pa.

TRANSISTORIZED Allwave Radio, 12,000 Mile Range Kit \$7.95, transistorized F-M radio kit less transistor \$9.95. (Send Stamp For Information About The World's Smallest Thimble Radio) Ekeradio, 646 North Fair Oaks, Pasadena, California.

ELECTRIC Pencil: Engraves all Metals, \$2.00. Beyer Mfg., 10511-P Springfield, Chicago 43.

SOLAR Batteries—miniature selenium cell. Complete with experiments \$1.00 to Lab L, Box 3096, University Station, Columbus 10, Ohio.

"15 TESTED One-tube Circuits" and Experimenter's catalog—25¢. Laboratories, 328-L Fuller, Redwood City, California.

TELEPHONE Extension In Your Car. Answer your home telephone by radio from your car. Complete diagrams and instructions. \$1.25. C. Carrier Co., 734 15th Street, N.W., Washington 5, D. C.

PUSH Button Telephone Dialing, Effortless dialing of your home or business phone. Complete diagrams and instructions. \$1.25. C. Carrier Co., 734 15th St., N.W., Washington 5, D. C.

ULTRA High-Fidelity, by means of R.F. Absolutely flat power amplifier. Complete diagrams and instructions. \$1.25. C. Carrier Co., 734 15th St., N.W., Washington 5, D. C.

CAPACITORS Galore .0005 @ 600V .006 @ 200V 5¢ Ea., 100—\$4.00 P.P.D. Zoron Electronics, 1740 Wright St., Sacramento 21, Calif.

BUILD 3"-Sq. 4-Transistor Radio! Speaker! No Outside Antenna! Plans \$3.00. Details: D. W. Bush, 2345-P So-101, San Clemente, Calif.

SENSATIONAL album of 10 illustrated transistor pocket radio plans. Basic through speaker superhet circuits. \$2.00. Cook, 4003-E Roosevelt, Midland, Texas.

PLASTIC repair kit will repair most broken or cracked radio cases, dials, knobs etc. \$3.00 prepaid. Free information. Rayther Co., Box 264A, Station B, Toledo, Ohio.

ELECTRONIC Brains. Complete Kits. Home-Study Courses. Electric Slide Rule \$14.50. Computer Plans: Miniature—\$1.—, Analog—\$3.—, Digital \$3.— 50 Assorted Diagrams For Experimenters, \$2.—. EBE, 1015 Atkin Ave., Salt Lake City 6, Utah.

TRANSISTOR Kits. Amazing Portable one tube FM & TV receiver. Free data. Altronics P. O. Box 32, Normandy Branch, St. Louis 21, Mo.

PANEL Meters, Transformers, Tubes, Crystals. Free List. Rjor Products Co., Box 81, Rego Park, N. Y.

WALKIE-TALKIE chassis only \$6.50. Illustrated in this issue. See index on last page. Springfield Enterprises, Box 54-E 11, Springfield Gardens 13, N. Y.

TWO Transistor Pocket Radio Kit \$11.95. Free Literature. Highland Electric, Box 553E, Pasadena, Calif.

TELEPHONE Transmitter. Hand set type. Suitable for inter-house phones, speakers or any communication purpose. Delivered two for \$1.00. No C.O.D.'s. Telephones, Dept. C-529, 1760 Lunt, Chicago 26.

SALE—100 ass't resistors, 10 ohms-4.7 meg., 1/2-1 watt \$1.00. 100 ass't capacitors .5-1000mmf \$1.00. L & W Products, P. O. Box 266, Taunton, Mass.

WALKIE-TALKIE plans, constructional details. Inexpensive, simple, compact. 50¢ Fabco Electronics, 7400 Jackson Pk., Birmingham, Mich.

WANTED

CYLINDER and old disc phonographs. Edison, Conqueror, Idella, and Oratorio models. Berliner Gramophones and Zono-o-phones, Columbia cylinder Graphophones, and Coin-operated cylinder Phonos. Want old catalogues and literature on early phonos prior to 1919. Will pay cash or trade late hi-fi components. **POPULAR ELECTRONICS**, Box 50.

TUBES and equipment bought, sold and exchanged. For action and a fair deal write B. F. Gensler, W2LNI, 56 Crosby St., N. Y., 12N, N. Y.

SELL Your Way To Wealth! Wanted—Surplus Military And Commercial Aircraft Electronics: BC-788, I-152, ARN-7, ARC-1, ARC-3, transmitters, receivers, test equipment, etc.! Wanted—Electronic Tubes: Broadcast, transmitting, receiving, Magnetrans, Klystrons, miniature, sub-miniature, ruggedized, etc.! Top Prices Paid! For Fattest Checks—Sell to Rex! Write or phone description for immediate action. P. E. Sanett, W6REX, 1524 S. Edris Drive, Los Angeles 35, Calif. Phones: REpublic 5-0215, CRestview 1-3856.

EMPLOYMENT INFORMATION

JOBS—High Pay. South America, the Islands, USA, foreign countries. All trades. Clerical, labor, engineers, drivers, others. Women also. Fare paid. Application forms. For information. Write Section 92B, National Employment Information, 1020 Broad, Newark, N. J.

INVENTIONS WANTED

INVENTIONS wanted. Patented; unpatented. Global Marketing Service, 2420 77th, Oakland 5, Calif.

TAPE RECORDERS

RECORDERS, Tape, Hi-Fi. Wholesale Prices. Catalogue. Kerstin, 215 E. 88 St., N. Y. C. 28.

PRE-RECORDED Tapes, Low price recording tape. Accessories, Catalog, Efsco Sales, 270-A Concord Avenue, West Hempstead, N. Y.

TAPE Recorders. Tape. Unusual Values. Free Catalog. Dressner, 69-02F, 174 St., Flushing 65, N. Y.

TAPE Recorders, surplus, \$244.50 Webcor, brand new, scarred, for \$146.50; Electrosonic for \$64.50; Wilcox-Gay cost \$165.00, used, like new for \$75.00; Used Eicor good shape for \$59.50; Several P. A. System bargains. Geo. F. Bischof, Fort Worth 4, Texas.

WHOLESALE! Recorders. Tapes. Phonographs. Radios. Catalogue 10¢. Towers — 155, Philadelphia 5.

BUSINESS OPPORTUNITIES

TO \$100.00 Weekly. Sparetime, Home Operated Mail-order Business, Successful "Beginner's" Plan. Everything Supplied. Lynn, 10420-E National, Los Angeles 34.

VENDING Machines—No Selling. Operate a route of coin machines and earn amazing profits. 32-page catalog free. Parkway Machine Corporation, Dept. 12, 715 Ensor St., Baltimore 2, Md.

PLATE Baby Shoes, jewelry, gifts, bronze and colored pearl. Free booklet. Thompson, 11029 South Vermont, Los Angeles 44, Calif.

BUY Wholesale! Resell at big profits. Brand name merchandise. Appliances. cookware, housewares, watches, jewelry, dry goods, clothing, sporting goods, toys gifts, etc. Free 1957 color catalog listing over 1001 items with confidential cost sheet. Merit Home Products, Dept. PE 11, 107 Manhattan Ave., Brooklyn 6, N. Y.

\$150 WEEK—easy! Start home Venetian Blind Laundry. Revealing book free. E. O. Co., 101 So. 44th, Philadelphia 4, Penna.

FREE Booklet "Money-Making Facts" tells mechanically-inclined men how to start sparetime business at home. Lee Foley Company, Columbia Heights, Minnesota.

HUGE Monster Mail, 25¢ — William Greener, Box 306-L, Burley, Idaho.

SELL Rubber Stamps—Printing. Catalogs free. Jos. Abernathy, Barnesville, Ga.

INSTRUCTION

ENGINEERING Degrees earned by home study. Residential Courses also available. American College of Engineering, Box 27724-D, Hollywood 27, California.

BECOME Tax Consultant. Graduates earn \$3,000 every tax season preparing returns evenings. State approved. Union Institute, 68 Hudson, Hoboken 3P, N. J.

RECORDS

PHONOGRAPH Records Cheap. Catalogue. Paramount, TD—313 East Market, Wilkes-Barre, Penna.

MISCELLANEOUS

SONGPOEMS and Lyrics Wanted! Mail to: Tin Pan Alley, Inc., 1650 Broadway, New York 19, N. Y.

BECOME a Radio Amateur. Free Information on how to pass Code and Theory FCC examinations. American Electronics, 1203E Bryant Ave., New York 59.

GUARANTEED 100 Double Edge Blades. Finest Quality—\$1.00. United. Box 7, Corona 68, N. Y.

COMPLETE Pocket Printer, Pad, Handy Carrying Case. Three Lines \$1.00—500 Distinctive Useful Gummed Name & Address Labels \$1.00—United, Box 7, Corona 68, N. Y.

Always say you saw it in—**POPULAR ELECTRONICS**

The "Tirade Terminator"

(Continued from page 50)

guished and left that way throughout tests and installation. In the final installation, mark the plug and the receptacle with paint or crayon to insure that the plug, if inadvertently removed, will be replaced properly.

When the foregoing instructions for establishing the chassis at house-ground potential are followed to the letter, there is absolutely no danger of a.c. shock from the lines. For those who do not wish to perform these checks, it is suggested that an isolation transformer be inserted between the a.c. input to the intercom and the line. It should be remembered, however, that the use of a transformer carrying a.c. introduces the possibility of hum pickup in the high-gain stage of the intercom, so provision should be made for mounting it at a distance from the 1A5, preferably at the far end of the a.c. cable.

Any 117-volt lamp cord may be used between the master unit and the remote speaker. Use a weatherproof housing outdoors and the plastic cabinet indoors, as shown in the photographs, for the remote speaker.

-30-

Mixing It Up

(Continued from page 85)

may be used to set the over-all level of the mixed signal as it emerges from the mixer and enters the tape recorder.

Commercially Available Mixers. For those who want to have—but not build—their own mixers, there are several fine units on the market. They range from Switchcraft's modest little "Mini-Mix" to the elaborate, studio-type facilities found on such recorders as the Ampex 601. A neat two-channel mixer-fader, which may also be used as a preamp on one channel, is made by Fisher; a four-channel mixer is produced by Pentron. Some of the newer, high-quality preamp-control units for hi-fi systems have mixing facilities built in. For specific information regarding such units, contact the manufacturers or your local parts or hi-fi dealer.

The mixer you choose to build or buy should be the one that meets your needs as regards the type of signals to be fed into it, the number of different channels required, the degree of gain needed, and the audio quality expected from it in terms of the tapes you're recording. Whatever your choice, the mixer will bring a touch of the professional studio into your home and help you produce better recordings.

-30-

November, 1956

SHOOT TV TROUBLE FAST

With H. G. Cisin's Copyright RAPID "TV TROUBLE SHOOTING METHOD"

Without experience or knowledge, this guaranteed new method of servicing TV sets enables you to DIAGNOSE TV troubles as rapidly as an expert. **NO THEORY—NO MATH**—you can locate all faults in record-breaking time regardless of make or model. "TV TROUBLE SHOOTING METHOD" is the most valuable aid to TV servicing ever written. Be a TV Trouble Diagnostician. Increase your present earnings. Open your own Profitable Business or get a high-paying skilled job.

It's all in this book . . .

Nothing more to Pay—Nothing else to Buy

83 picture troubles, over 58 raster and 17 sound troubles. By this unique copyrighted method you know EXACTLY WHERE the trouble is; plus step-by-step instructions, including 69 RAPID CHECKS, enabling you to find the faulty part.

13 IMPORTANT PRELIMINARY CHECKS NEED NO INSTRUMENTS! Of the 69 Rapid Checks, **OVER 65 ALSO REQUIRE NO INSTRUMENTS!** Rapid checks include emergency checks for distorted pictures, defective tubes including PIX tube, plus 57 others. **ALL EXPLAINED IN SIMPLE LANGUAGE. PERFORMED WITHOUT INSTRUMENTS. MANY CHECKS USE THE PICTURE TUBE AS A GUIDE.**

H. G. Cisin, the author, is the inventor of the AC/DC midjet radio. He licenses RCA, AT&T etc. He has also trained thousands of technicians now owning their own prosperous TV service organizations or holding highly paid TV positions. His years of experience are embodied in this remarkable new book.

Guaranteed Money Back in 5 Days If Not Satisfied!

ABSOLUTELY FREE with each order: H. G. Cisin's new book "TV & RADIO TUBE SUBSTITUTION GUIDE." Gives direct replacements of set and picture tubes. Most valuable servicing aid. **ACT NOW—get both books postpaid at cost of only one!**

\$1 Post Paid

RUSH COUPON NOW!

H. G. CISIN, CONSULTING ENGINEER,
Amagansett, N. Y.

Dept. P-20

Enclosed find \$1. Rush both books.

Name

Address

City Zone State

1957 PHOTOGRAPHY ANNUAL

A collection of the world's greatest photographs by the editors of Popular Photography

PHOTOGRAPHY ANNUAL

1947 EDITION

From \$5.00
\$2.95 to Clubs
and subscribers



**NOW
ON SALE
EVERYWHERE!**



WRITE FOR NEW BONUS CATALOG

1000's of Un-Advertised Specials



INFRARED SNOOPERSCOPE

See in Dark Tube

SELECTED, GTD & TESTED for resolution. 1st class image converter viewing tube. High sensitivity simplified design 2" dia. Willgemite screen—Hi Resolution, Tube & Data.

"TAB" SPECIAL @ \$4.75; 2 for \$9
New Snooperscope High Voltage Power Supply Housed in caged AMPLIFIER Chassis... \$31.95
MODEL P5200Z, KIT same as above, all components and pre-drilled AMP Chassis... \$21.95
MODEL P5200S, Snooperscope Doubler Power Supply, Less Chassis... \$13.95

PORTABLE "TABLITE" ELECTRONIC FLASH KITS

AC & Battery Operation Inbuilt
All in One Camera Case

MODEL 400B, 80 Watt Sec'd; color 75+; B&W 225+, Recycles 2 Sec'd... \$29.95
MODEL 600B, 120 Watt Sec'd; color 100+; B&W 300+, Recycles 5 Sec'd... \$44.95
Two (2) 210 VOLT BATTERIES... @ \$4
KITS ASSEMBLED, Additional... \$10



Write for Complete Details and Specifications

TUBES "TAB" TESTED Guaranteed

OUR 12th YEAR IN BUSINESS

0A2 .70	6AQ5 .45	6S4 .45	12AX4 .70
0Z4 .42	6AS5 .75	6SA7 .45	12AX7 .55
1B3 .60	6AT6 .35	6SH7 .40	12BH7 .65
1L4 .44	6AU4 .75	6SJ7 .45	
1R5 .49	6AU6 .40	6SK7 .45	CK1028 3.25
1S4 .64	6AX4 .60	6SL7 .55	
1S5 .40	6BA6 .45	6SN7 .55	12BY7 .70
1T4 .49	6BC5 .45	6SQ7 .39	12SA7 .65
1U4 .45	6BE6 .45	6T4 1.00	12SK7 .43
1U5 .40	6BF5 .50		12SN7 .55
1X2A .60	6C12 .12	1N21 .25	12SQ7 .45
2V3 .75	6BK5 .75		14A7 .55
3A4 .48	6BL7 .80	6T8 .75	19B05 1.25
3A5 .75	6B6 .65	6U8 .75	25B06 .90
3Q4 .45	6B06 .90	6V6 .45	25Z6 .45
3V4 .55	6BQ7 .85	6W6 .55	35C5 .50
5U4G .60	6C4 .35	6X4 .30	35L6 .45
5Y3 .40		7A8 .50	35WA .50
6B4 .40	2D21 .75	7C5 .55	35Z5 .45
6AC7 .64		7F7 .55	50A5 .45
6AQ5 .45	6CB6 .48	7F8 .68	50B5 .55
6AH4 .75	6CD6 1.12	7N7 .55	50C5 .45
	6H6 .65	7Q7 .75	50L6 .40
	6J5 .38	12AT6 .40	75 .45
	6K6 .39	12AT7 .55	77 .40
6AK5 .52	6K7 .35	12AU7 .50	
6AL5 .38	6L6 .65	12AV6 .35	117L7/N7
		12AV7 .75	1.75

New "TABTRON" VARIABLE 0 to 6 & 12 VOLT/12 AMP DC Power Supply



Battery Eliminator, Charger, Model RR. Plater Aircraft, Marine or any DC requirement. Extra H.V. duty Selenium Rectifier, 2 meters V & A. Designed for cont. service & up to 20 amps intermittent overload.
MODEL T612V12AC... \$33.00

KITS! KITS!

Each "TAB" Kit Contains the Finest Selection of Top Quality Components in the Most Popular Values & Sizes

EXTRA: Free Kit with Each \$10 Kit Order

- | | |
|--|--|
| <ul style="list-style-type: none"> 25 Precision Resistors 10 Switches 25 Knobs 75 Carbon Resistors* 36 Panel Lamps 10 Electrolytic Cond's 15 Volume Controls 25 Tube Sockets 50 Tubular Condensers 500 Lugs & Eyelets* 10 Bathing Oil Cond's 5 lbs. Surprise Package 10 Transmit Mica Cond's 40 Insulators | <ul style="list-style-type: none"> 25 Power Resistors 65 Mica Condensers 5 Crystal Diodes 250 ft. Hook Up Wire, Ass't'd 100 Fuses 35 Ceramic Condensers 10 Rotary Switches 6 Crystals 60 Inductors & Coils 5 Microswitches 10 Wheat Lamps * In Plastic Box |
|--|--|

EACH KIT ONLY... 99c

1,000's OF SATISFIED CUSTOMERS

Every Kit Sold on "TAB" Money Back Guarantee

"TAB" FINEST HI-FI RECORDING TAPE

7" Reel—1200 Ft. Per Reel **\$1.45** Lots of 12

Sold on Money Back Guarantee... Highest quality Hi-Fi Precision Coated & SHI. FERRO-SHEEN processed, quality controlled, constant output. Noise FREE, Splice FREE Plastic Tape. Freq. 7 1/2 IPS. 40-15KC Oxide Wind In. "TAB" @ \$1.59 ea.; 3/\$1.50 ea.
Guaranteed Replacement Needles—All Cartridges Single Diamond \$9.95; Dual Dia \$19.95; Dia-Sapphire \$11.95 Please Send Cartridge Name & Number

"TAB"

TERMS: Money Back Gtd (cost of mfg. only), \$5 min. order. F.O.B. N.Y.C. Add ship. charges or for C.O.D. 25% Dep. Tubes Gtd. via R-Exp. only. Prices shown are subject to change.

Dept. 11PE6, 111 Liberty St., N. Y. 6, N. Y., Rector 2-6245

ADVERTISER'S INDEX

ADVERTISER	PAGE NO.
Aleo Electronics Mfg. Co.	118
Algeradio Electronics Co.	129
Allied Radio Corp.	8, 9, 24, 103
Almo Radio Co.	24
Altec Lansing Corp.	18
Atomic Engineering Corp.	104
Bailey Technical Schools	26
Bridgeport Electronics	124
Burgess Battery Company	103
Burstein-Appelbe Co.	118
Candler System Co.	124
Capitol Radio Engineering Institute	29
Central Technical Institute	101
Centralab	101
Cisin, H. G.	131
Cleveland Institute of Radio Electronics	15
Cousino, Inc.	116
Coyne Electrical School	5, 125
DeVry Technical Institute	11
Edlie Electronics	129
Electronic Instrument Co., Inc. (EICO)	38
Electronic Measurements Corp.	33
Electronic Specialty Supply	128
Electro-Voice	34
Emig School of Electronics	124
Esse Radio Co.	36, 37, 128
Garneld Company, Oliver	16, 17
Grantham School of Electronics	116
Green, Gould	129
Gyro Electronics	129
Hallcrafters	27
Hammarlund Mfg. Co.	2nd Cover
Hawkins Co., P. E.	111
Heath Company	94, 95, 96, 97
Hershel Radio Co.	32
Hickok Electric Co.	106
Indiana Technical College	126
Indianapolis Electronic School	120
Instructograph Co.	118
International Correspondence Schools	13
International Rectifier Corp.	10
Interstate Training Service	116
Johnson Co., E. F.	119
Kar-Aids	111
Lafayette Radio Corp.	30, 31, 128, 129
Lektron Specialties	111, 128
Linthrop Pkg. Co.	20
LMB	116
McGraw-Hill Book Co., Inc.	115
Major Brand Tube Co.	35
Microphone	128
Midway Company	120
Miller, Gustave	126
Milwaukee School of Engineering	109
Minnesota Mining & Mfg. Co.	104
Mini-Tronics Co.	13
Moss Electronics Distributing Co., Inc.	3rd & 4th Covers
National Electronics	128
National Radio Institute	99, 100
National Schools	23
Newark Electric Co.	120
North American Phillips	22
Pacific States University	112
Palmer, Joe	118
Pen Pals	126
Philadelphia Wireless Technical Institute	103
Photography Annual	131
Popular Boating	93
Prentice Hall	108
Progressive "Edu-Kits," Inc.	21
Quality Electronics	120
Rad-Tel Tube Co.	128
Radio TV Training Association	7
Raytheon Manufacturing Co.	12
RCA Institutes	19
R Electronics	3
Rider Publishing Co., Inc. John F.	113
Rinehart Books	121
Rockbar Corporation	24
Sams, Howard W.	127
Saunders Electronics Correspondence School	26
Scherr Company, George	128
Scott-Mitchell House, Inc.	124
Shure Brothers	6
Springfield Enterprises	112
Stanley Electronics	117
Surplus Center	107
"TAB"	128, 132
TraDyne, Inc.	112
Tri-State College	118
Tube Mart, The	107
TV Super Mart	128
University Loudspeakers	122
Utah Radio Products	28
V.S.I. Television School	124
Vaco Products	110
Valparaiso Technical College	111
Video Electronics Co.	114
Western Radio	122
Whitehall Pharmaceutical Co.	126
World Radio Labs	123
YMCA Trade Schools	122

Superior's New Model 770-A

The FIRST Pocket-Sized VOLT-OHM MILLIAMMETER

USING THE NEW "FULL-VIEW" METER

71% MORE SCALE AREA!!

Yes, although our new FULL-VIEW D'Arsonval type meter occupies exactly the same space used by the older standard 2 1/2" Meters, it provides 71% more scale area. As a result, all calibrations are printed in large easy-to-read type and for the first time it is now possible to obtain measurements instead of approximations on a popular priced pocket-sized V.O.M.

FEATURES


- ★ Compact—measures 3 1/8" x 5 7/8" x 2 1/4"
- ★ Uses Full View 2% accurate, 850 Microampere D'Arsonval type meter
- ★ Housed in round-cornered, molded case
- ★ Beautiful black etched panel. Depressed letters filled with permanent white, insures long-life even with constant use.

Specifications

- 6 A.C. VOLTAGE RANGES: 0-15/30/150/300/1500/3000 volts.
- 6 D.C. VOLTAGE RANGES: 0-7.5/15/75/150/750/1500 volts
- 2 RESISTANCE RANGES: 0-10,000 Ohms, 0-1 Megohm.
- 3 D.C. CURRENT RANGES: 0-15/150/1500 Ma., 0-1.5 Amps
- 3 DECIBEL RANGES: -6 db to +18 db, +14 db to +38 db, +34 db to +58 db.

The Model 770-A comes complete with self-contained batteries, test leads and all operating instructions.

\$15⁸⁵

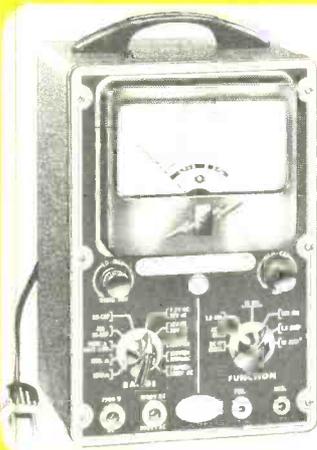

Superior's New Model 670-A

SUPER-METER

A COMBINATION VOLT-OHM MILLIAMMETER PLUS CAPACITY REACTANCE INDUCTANCE AND DECIBEL MEASUREMENTS

SPECIFICATIONS:

- D.C. VOLTS: 0 to 7.5/15/75/150/750/1,500/7,500 Volts
- A.C. VOLTS: 0 to 15/30/150/300/1,500/3,000 Volts
- OUTPUT VOLTS: 0 to 15/30/150/300/1,500/3,000 Volts
- D.C. CURRENT: 0 to 1.5/15/150 Ma. 0 to 1.5/15 Amperes

- RESISTANCE: 0 to 1,000/100,000 Ohms 0 to 10 Megohms
- CAPACITY: .001 to 1Mfd. 1 to 50 Mfd. (Quality test for electrolytics)
- REACTANCE: 50 to 2,500 Ohms 2,500 Ohms to 2.5 Megohms
- INDUCTANCE: .15 to 7 Henries 7 to 7,000 Henries
- DECIBELS: -6 to +18 +14 to +38 +34 to +58

ADDED FEATURE:

Built-in ISOLATION TRANSFORMER reduces possibility of burning out meter through misuse.

The Model 670-A comes housed in a rugged crackle-finished steel cabinet complete with test leads and operating instructions.

\$28⁴⁰

SHIPPED ON APPROVAL NO MONEY WITH ORDER — NO C. O. D.

We invite you to try before you buy any of the models described on this and the following page. If after a 10 day trial you are completely satisfied and decide to keep the Tester, you need send us only the down payment and agree to pay the balance due at the monthly indicated rate.

NO INTEREST OR FINANCE CHARGES ADDED!

If not completely satisfied, you are privileged to return the Tester to us, cancelling any further obligation.

MOSS ELECTRONIC DISTRIBUTING CO., INC.
Dept. D-287, 3849 Tenth Avenue, New York 34, N.Y.

Please send me the units checked. I agree to pay down payment within 10 days and to pay the monthly balance as shown. It is understood there will be no finance or interest charges added. It is further understood that should I fail to make payments when due, the full unpaid balance shall become immediately due and payable.

- Model TV-11... Total Price \$47.50
\$11.50 within 10 days. Balance \$6.00 monthly for 6 months.
- Model 670-A... Total Price \$28.40
\$7.40 within 10 days. Balance \$3.50 monthly for 6 months
- Model TC-55... Total Price \$26.95
\$6.95 within 10 days. Balance \$5.00 monthly for 4 months.
- Model 770-A... Total Price \$15.85.
\$3.85 within 10 days. Balance \$4.00 monthly for 3 months

Name _____

Address _____

City _____ Zone _____ State _____

SEE OTHER SIDE

CUT OUT AND MAIL TODAY! ▶

All prices net, F.O.B., N.Y.C.

Superior's New Model TC-55

Streamlined

TUBE TESTER

FOR

The Experimenter or Part-time Serviceman, who has delayed purchasing a higher priced Tube Tester. The Professional Serviceman, who needs an extra Tube Tester for outside calls. The busy TV Service Organization, which needs extra Tube Testers for its field men.

Speedy, yet efficient operation is accomplished by: Elimination of old style sockets used for testing obsolete tubes (26, 27, 57, 59, etc.) and providing sockets and circuits for efficiently testing the new Noval and Sub-Minor types.

Model TC-55 comes complete with operating instructions and charts and streamlined carrying case.

\$26⁹⁵

- You can't insert a tube in wrong socket. Separate sockets are used, one for each type of tube base.
- "Free-point" element switching system. Any pin may be used as a filament pin and the voltage applied between that pin and any other pin, or even the "top-cap".
- Checks for shorts and leakages between all elements. Provides a super sensitive method of checking for shorts and leakages up to 5 Megohms between any and all of the terminals. Continuity between various sections is individually indicated.
- Elemental switches are numbered in strict accordance with R.M.A. specification. The 4 position fast-action snap switches are all numbered in exact accordance with the standard R.M.A. numbering system.



Superior's new Model TV-11

Standard Professional

TUBE TESTER

- ★ Tests all tubes including 4, 5, 6, 7, Octal, Lock-in, Peanut, Bontam, Hearing Aid, Thyatron Miniatures, Sub-miniatures, Novals, Sub-minors, Proximity fuse types, etc.
- ★ Uses the new self-cleaning Lever Action Switches for individual element testing. Because all elements are numbered according to pin-number in the PMA base numbering system, the user can instantly identify which element is under test. Tubes having tapped filaments and tubes with filaments terminating in more than one pin are truly tested with the Model TV-11 as any of the pins may be placed in the neutral position when necessary.
- ★ The Model TV-11 does not use any combination type sockets. Instead individual sockets are used for each type of tube. Thus it is impossible to damage a tube by inserting it in the wrong socket.

- ★ Free-moving built-in roll chart provides complete data for all tubes.
- ★ Newly designed Line Voltage Control compensates for variation of any Line Voltage between 105 Volts and 130 Volts.
- ★ NOISE TEST: Phono-jack on front panel for plugging in either phones or external amplifier will detect microphonic tubes or noise due to faulty elements and loose internal connections.

The model TV-11 operates on 105-130 Volt 60 Cycles A.C. Comes housed in a beautiful hand-rubbed oak cabinet complete with portable cover.

\$47⁵⁰

EXTRA SERVICE — The Model TV-11 may be used as an extremely sensitive Condenser Leakage Checker. A relaxa-

tion type oscillator incorporated in this model will detect leakages even when the frequency is one per minute.

**SHIPPED ON APPROVAL
NO MONEY WITH ORDER — NO C. O. D.**

FIRST CLASS

Permit No. 61430

New York, N. Y.

BUSINESS REPLY CARD

No Postage Stamp Necessary if Mailed in the U. S.

POSTAGE WILL BE PAID BY —

MOSS ELECTRONIC DIST. CO., INC.

3849 TENTH AVENUE

NEW YORK 34, N. Y.

We invite you to try before you buy any of the models described on this and the preceding page. If after a 10 day trial you are completely satisfied and decide to keep the Tester, you need send us only the down payment and agree to pay the balance due at the monthly indicated rate. (See other side for time-payment schedule details.)

**NO INTEREST
OR FINANCE
CHARGES ADDED!**

If not completely satisfied, you are privileged to return the Tester to us, cancelling any further obligation.

**SEE OTHER
SIDE**

CUT OUT AND MAIL TODAY!