

SPECIAL-RADAR WAVES CAN BE DEADLY


POPULAR ELECTRONICS

MARCH
1961

35
CENTS

HI-FI • HAM & CITIZENS RADIOS • SWL

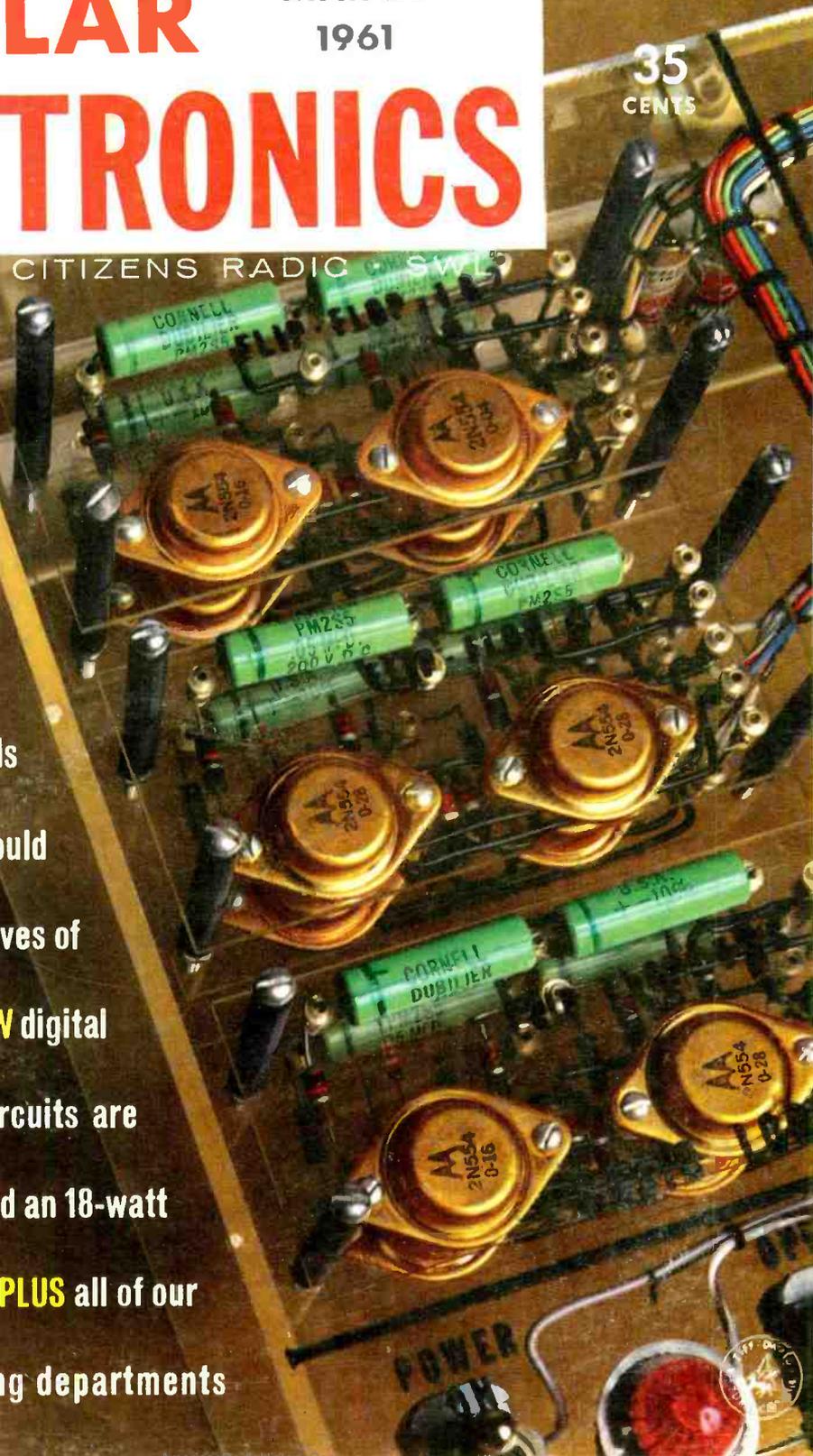In this issue
you will find **HOW**
Castro's propaganda
short-wave will work:
HOW a Q-multiplier aids
the CB'er: **HOW** you should
judge performance curves of
stereo amplifiers: **HOW** digital
computer flip-flop circuits are
designed: **HOW** to build an 18-watt
hi-fi power amplifier: **PLUS** all of our
valuable and exciting departments



NOW IN KIT FORM!

The RCA Senior VoltOhmyst®

WV-98B (K)

ONLY \$62.50*

With probe, cable, clips and instruction booklet.

Featuring Pre-Assembled Etched-Circuit Board and Pre-Assembled DC/AC-OHMS Probe (WG-299D)

- Easy-to-read meter—6½" wide
- 200-microampere meter movement with less than 1% tracking error
- Precision multiplier resistors accurate to ± 1%
- Meter electronically protected against burnout
- Separate color-coded peak-to-peak and rms-voltage scales
- Die-cast aluminum case with leather carrying handle

MEASURES:

DC voltages, 0 to 1500 volts.
AC voltages, 0 to 1500 volt rms or 0 to 4200 volts peak-to-peak.
Resistances from 0.2 ohm to 1,000 megohms.

RCA WV-98B available factory-wired and calibrated: \$79.50*

Real dollar-savings!

Assembly time is cut to the bone!

This extra-heavy etched-circuit board comes with all components completely mounted and soldered. The input probe and cable, likewise, comes to you already assembled and wired.

OTHER OUTSTANDING RCA KIT VALUES...



RCA VOLTOHMYST® KIT
WV-77E(K) Only \$29.95*

Famous VoltOhmyst® quality and performance at a low price! Special test features include: separate 1.5-volt rms and 4-volt peak-to-peak scales for accurate low AC measurements. Measures AC and DC voltages to 1500 volts, resistances from 0.2 ohm to 1,000 megohms. Complete with ultra-slim probes, long flexible leads, special holder on handle to store leads.

RCA WV-77E available factory-wired and calibrated: \$43.95*



RCA WV-38A(K)
VOLT-OHM-MILLIAMMETER KIT
Only \$29.95*

The V-O-M with the extras! • 0.25-volt and 1.0-volt DC ranges • Big easy-to-read 5¼" meter • Non-breakable sealed plastic case—no glass to crack or shatter • Jacks located below switches to keep leads out of the way • Spring clips on handle to hold leads • Attractive, scuff resistant, rugged carrying case, only \$4.95* extra.

RCA WV-38A available factory-wired and calibrated: \$43.95*



RCA SUPER-PORTABLE
OSCILLOSCOPE
KIT WO-33A(K) Only \$79.95*

Now in kit form. A 'scope you can carry anywhere! Rugged and compact, yet weighs only 14 pounds. Just right for in-the-home and shop troubleshooting and servicing of black-and-white and color TV, radio, hi-fi components, tape recorders, etc. Ample gain and bandwidth for the toughest jobs. Scaled graph screen and internal calibrating voltage source for direct reading of peak-to-peak voltage.

RCA WO-33A available factory-wired and calibrated: \$129.95*

See them all at
your Authorized RCA
Test Equipment Distributor



The Most Trusted Name in Electronics
RADIO CORPORATION OF AMERICA

*User Price Optional

new!




outstanding value

Electro-Voice®

ULTRA-COMPACT SPEAKER SYSTEMS

in kit form

Now Electro-Voice takes the mystery out of ultra-compact speaker systems. No longer are the components a "sealed" secret. You see what you get, know what you get, and enjoy the fun and economy of building your own speaker system. All the materials and instructions you need are included in the package. These new kits are exactly the same as the carefully-designed, assembled systems currently sold by Electro-Voice. Systems that produce a clarity of sound that enable you to feel the deepest bass, marvel at the effortless clarity in the midrange, and delight in the brilliant definition of the upper harmonics.

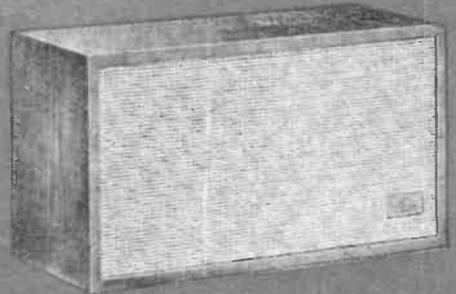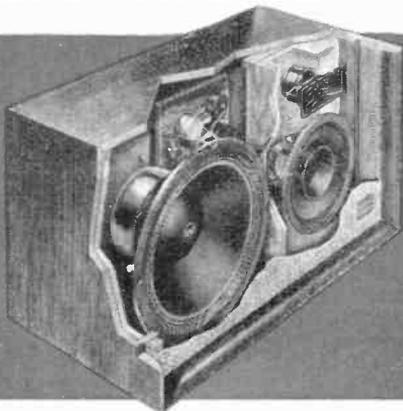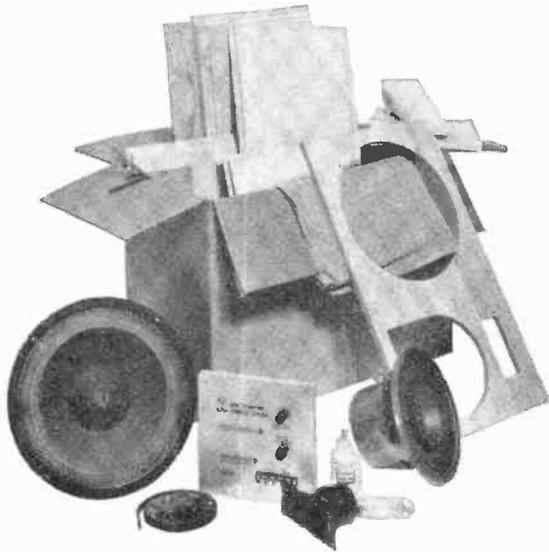

Performance Depends on Component Quality

Within each Electro-Voice system, every component is engineered to complement perfectly the others with which it is used. Some of the outstanding features you'll be receiving are illustrated in the cutaway view of the Esquire 200 featured above: (1) Substantial magnetic circuits for maximum sensitivity, power handling capacity, and uniformity of response. (2) High compliance viscous damped cloth suspension for smooth response and low resonant frequency. (3) Edgewise-wound voice coil for most effective use of available magnetic energy. (4) Die-cast frames for greatest reliability of performance. (5) True electrical cross-over, at exceptionally low frequency of 200 cycles, to minimize all forms of distortion associated with the use of woofers covering the midrange. (6) Midrange speaker in a totally isolated cavity for outstandingly uniform response throughout the range over which it is employed. (7) Sonophase® throat structure and integral diffraction horn to give virtually unequalled high frequency response range, with excellent coverage of the whole listening area. (8) Two level controls which permit exact adjustment of response characteristics to personal taste and individual acoustic environments.

A Variety of Prices and Performance

The Esquire 200—Now the value packed Esquire is available in three different forms... the handsome Esquire 200, the economical unfinished Esquire 200 Utility and the new Esquire 200 Kit. Each is a full three-way system with a 12" woofer, 8" cone-type mid-range speaker and E-V Super Sonax very-high-frequency driver. Esquire 200—14" high x 25" wide x 13½" deep. Hand-rubbed Walnut, Mahogany or Lined Oak.... \$133.00. Esquire 200 Unfinished Fir Utility—14" high x 23½" wide x 12" deep.... \$107.50. Esquire 200 in easy-to-assemble Kit form—14" high x 23½" wide x 12" deep.... \$93.00.

The Regal 300—A premium-quality, three-way system utilizing the finest quality components to assure the best sound possible in a small-sized system. Deluxe 12" woofer, a Deluxe 8" cone-type midrange speaker, and a compression-type, diffraction horn-loaded very-high-frequency driver. 14" high x 25" wide x 13½" deep. Walnut, mahogany, or lined oak.... \$179.00. Unfinished fir.... \$149.00. In Easy-to-assemble Kit Form.... \$125.00.

Consumer Products Division

Electro-Voice

Dept. 314P Electro-Voice, Inc., Buchanan, Michigan

POPULAR ELECTRONICS is published monthly by Ziff-Davis Publishing Company, William B. Ziff, Chairman of the Board (1948-1953) at 434 S. Wabash Ave., Chicago 5, Ill. Second-class postage paid at Chicago, Illinois. Authorized by Post Office Department, Ottawa, Canada, as second-class matter. **SUBSCRIPTION RATES:** One year U.S. and possessions, and Canada \$4.00; Pan-American Union Countries \$4.50. all other foreign countries, \$5.00.

AmericanRadioHistory.Com

POPULAR ELECTRONICS

VOLUME 14

NUMBER 3

MARCH

1961



Special Feature

The Danger of Radar Waves.....Ken Gilmore 41

Electronic Construction Projects

Two-Tube Screen Modulator.....Herb S. Brier, W9EGQ 68
Car Burglar Alarm System.....William C. Lewis 70
Citizens Band Q-Multiplier.....Donald L. Stoner, 11W1507 76
Radio-Control 11-Meter Receiver.....Perry Winter 81

Audio and High Fidelity

Hi-Fi Showcase 22
Direct-Coupled Hi-Fi Amplifier.....Herbert I. Keroes 46
Ping-Pong Stereo.....Bert Whyte 56
Curves (Amplifier Performance Curves).....G. H. Harrison 63

Amateur, CB, and SWL

FCC ReportRobert E. Tall 10
Castro's Radio Voice.....C. M. Stanbury, II 52
Radio Swan.....Tom Kneitel, WPE2AB 52
Across the Ham Bands: Trouble-Shooting Ham Equipment..Herb S. Brier, W9EGQ 67
On the Citizens Band.....Tom Kneitel, 2W1965 79
Short-Wave Report.....Hank Bennett, W2PNA 88
Short-Wave Monitor Registration..... 109

Electronic Features and New Developments

Notes from the Editor.....Oliver P. Ferrell 6
POP'tronics News Scope..... 8
Flip-Flop Circuits.....Julian M. Sienkiewicz 59
Electron Chemistry.....Fred E. Ebel, W9PXA 72
Transistor Topics.....Lou Garner 85
Carl and Jerry: A Low Blow.....John T. Frye, W9EGV 89

Departments

Letters from Our Readers..... 14
POP'tronics Bookshelf 18
Tips and Techniques..... 26
New Products 32

Copyright © 1961 by ZIFF-DAVIS PUBLISHING COMPANY. All rights reserved.

SAVE OVER \$3 ON THIS BRAND-NEW EDITION

Every Essential Term in Physics and Electronics—15,000 of Them

—NOW IN ONE GIANT DICTIONARY!

BRAND-NEW 2nd EDITION — Bigger, More Useful than Ever! Famous ONE-SOURCE reference book expanded to 1,400 pages — covers major new fields; presents latest ideas, discoveries in 17 basic areas! New multi-lingual indexes.

NOW completely revised and expanded, *The International Dictionary of Physics and Electronics* is the only book available that defines and explains every important term in 16 basic and many new fields of modern physics and electronics.

More than 15,000 laws, relationships, equations, basic principles, instruments, and techniques are described in over half a million words. It takes the place of a whole library of reference books on: Electronics • Meteorology • Mechanics • Gases • Liquids • Solids • Acoustics • Optics • Units and Dimensions • General Principles • Heat and Thermodynamics • Atomic and Nuclear Physics • Mathematical Physics • Quantum Mechanics • Electricity • Relativity.


Coverage of all of these fields has been brought completely up-to-date. In addition, there is NEW MATERIAL on new developments in thermonuclear research and magnetohydrodynamics . . . space physics . . . astrophysics. IRE definitions in networks, computers, etc. New review of physics: great developments from Newton to non-conservation of parity and strange particles.

Arranged to Give You Any Information in Seconds

No more hunting from book to book — no more guesswork, wasted time or effort. Here's everything you need in one 1,400-page easy-to-use reference volume. Articles are arranged progressively — begin with concise definition and add details in later paragraphs. Unique cross-reference system lets you find any fact fast: bold-face "word signals" refer you to related articles. And newly-added 4-language index — Russian, German, French, Spanish — lists all terms with English equivalents.

Special Money-Saving Offer

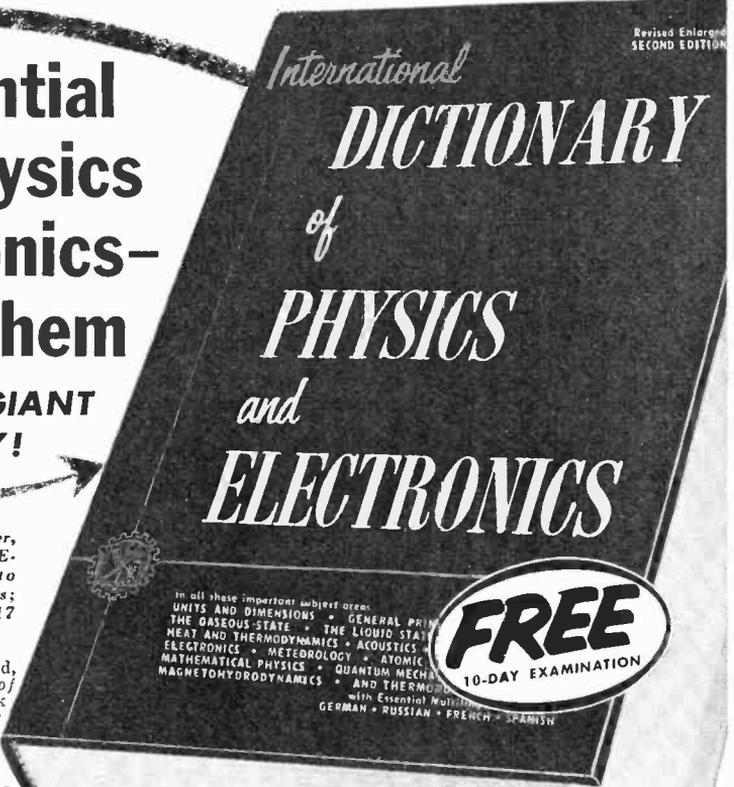This authoritative book is a monumental publishing achievement — 1,400 pages, 15,000 terms; bound and manufactured for a lifetime of use. After May 30 it will be priced at \$27.85.



FREE
10-DAY EXAMINATION

Acclaimed by Major Journals In Every Field of Science

- "Unique. Useful. Presents a wide variety of terms."
—SCIENTIFIC AMERICAN
- "Remarkably complete. Highly useful. Provides definite and concise answers to a myriad of questions."
—PHYSICS TODAY
- "Will undoubtedly make a well-deserved place for itself."
—SCIENCE
- "There has been a real need for such a work."
—ELECTRONICS
- "Recommended for all that do any reference work in physics."
—LIBRARY JOURNAL
- "Unique in its field and exceptionally clear in its typography. It should prove a most useful reference."
—NUCLEONICS
- "The best book of definitions available on the market today. Highly recommended."
—TELE-TECH

Until that time, however, the publishers are making a direct-to-reader offer of only \$24.75 (payable in installments) a saving of \$3.10. To take advantage of this \$3.10 saving you need send no money now — only certificate below. Book will be sent to you for FREE 10-DAY EXAMINATION.

Use this enormous Dictionary to recheck work, clarify data, catch up with new ideas, developments. See how it can repay its cost many times over in just one avoided error. If not convinced that it will be one of your most valuable books return it and pay nothing. (Cost of book is tax deductible if used in your work.) Mail no-risk certificate now to: **D. Van Nostrand Company, Inc., Dept. 17, 120 Alexander St., Princeton, N.J. (Estab. 1848.)**

SEND NOW — SAVE OVER \$3

**D. Van Nostrand Company, Inc.
Dept. 17, 120 Alexander St.,
Princeton, N.J.**

Name.....
(please print)

Address.....

City..... Zone..... State.....

Check Here and SAVE! Enclose full payment (\$24.75) with this certificate and all shipping costs will be prepaid. Money-back guarantee. (In Canada: 25 Holtzner Rd., Toronto 16. Price slightly higher.) Foreign and A.P.O. — please enclose \$24.75 with certificate.

Please send me the brand-new 2nd Edition of *The International Dictionary of Physics and Electronics*. If not delighted, I'll return it within 10 days and owe nothing. Otherwise, I'll remit \$9.75 plus small shipping cost then and \$5 a month for 3 months.

POPULAR ELECTRONICS

World's Largest-Selling Electronics Magazine

Average Net Paid Circulation Over 340,000

This month's cover photo by Al Gruen
Equipment: Aironics, Inc.
Digital Computer Demonstrator

Publisher

PHILLIP T. HEFFERNAN

Editor

OLIVER P. FERRELL, 2W1665

Managing Editor

**JULIAN M. SIENKIEWICZ
WA2CQL**

Art Director

ALFONS J. REICH

Associate Editors

**RICHARD A. FLANAGAN
MARGARET MAGNA
PERRY WINTER, K2VLR**

Editorial Assistant

MARIA SCHIFF

Editorial Consultant

OLIVER READ, W1ETI

Contributing Editors

**H. BENNETT, W2PNA
H. S. BRIER, W9EGQ
J. T. FRYE, W9EGV
L. E. GARNER, JR.
T. KNEITEL, 2W1965**

Art Associate

JAMES A. ROTH

Draftsman

ANDRE DUZANT

Advertising Director

JOHN A. RONAN, Jr., 1W6544

Advertising Manager

WILLIAM G. McROY, 2W4144

ZIFF-DAVIS PUBLISHING COMPANY,
One Park Ave., New York 16, N. Y.
William B. Ziff, Chairman of the Board
(1946-1953); William Ziff, President;
W. Bradford Briggs, Executive Vice
President; Michael Michaelson, Vice
President and Circulation Director;
Hershel B. Sarbin, Vice President;
Charles Housman, Financial Vice Pres-
ident; Richard Kislik, Treasurer.




BRANCH OFFICES: Midwestern Office,
434 S. Wabash Ave., Chicago 5, Ill.,
Jim Weakley, Advertising Manager;
Western Office, 9025 Wilshire Blvd.,
Beverly Hills, Calif., William J. Ryan,
Western Manager.

Foreign Advertising Representatives:
D. A. Goodall Ltd., London; Albert Mil-
hado & Co., Antwerp and Dusseldorf.

SUBSCRIPTION SERVICE: Forms 3579 and all subscription correspondence should be addressed to Popular Electronics, Circulation Department, 434 South Wabash Avenue, Chicago 5, Illinois. Please allow at least four weeks for change of address. Include your old address as well as new—enclosing if possible an address label from a recent issue.

CONTRIBUTORS: Contributors are advised to retain a copy of their manuscripts and illustrations. Contributions should be mailed to the New York Editorial Office and must be accompanied by return postage. Contributions will be handled with reasonable care, but this magazine assumes no responsibility for their safety. Any copy accepted is subject to whatever adaptations and revisions are necessary to meet the requirements of this publication. Payment covers all author's, contributor's and contestant's rights, titles, and interest in and to the material accepted and will be made at our current rates upon acceptance. All photos and drawings will be considered as part of material purchased.

COMING NEXT MONTH

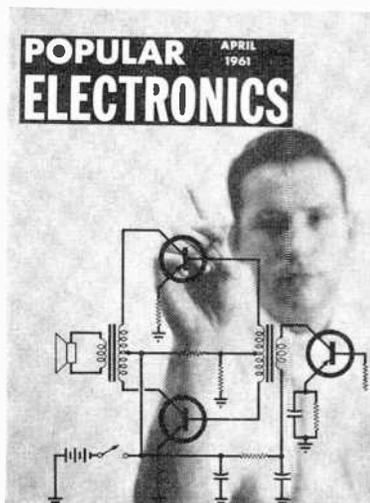

(ON SALE MARCH 28)

● DIGITAL COUNTING

After reading this month's informative discussion on flip-flops (page 59), you'll want to see the concluding installment in the April issue. Learn how flip-flops can be teamed up to perform counting operations—the article will cover both theory and construction plans.

● CUSTOM-MADE DIALS

Home-built projects can look professional if you just add some attractive, easy-to-make, anodized aluminum dials. Step-by-step instructions tell you how it's done.

● DARKROOM METER

You can make your own darkroom meter—and obtain professional enlargements the first time you try. A cinch to build and operate, this meter will indicate paper type and lens settings for any exposure time.

In Spare Time at Home—Prepare for a Better Job—or
Your Own Business in One of the Many Branches of

ELECTRONICS

You build and keep this valuable Vacuum Tube VOLT METER

You build and keep this 5-inch COLOR OSCILLOSCOPE—almost a "must" for TV servicing.



HOME MOVIES . . .
... make important points crystal clear. Speeds your learning. It's almost like having an instructor at your side!

MILITARY SERVICE

If you are subject to military service, the information we have should prove very helpful. Mail coupon today.

RADIO - TELEVISION - RADAR

If you are seeking a better job or a business of your own, the appealing field of Television-Radio-Electronics offers **REAL PROMISE!**

In this fast-growing field, trained Electronic technicians find many good-paying, interesting jobs in manufacturing, installing, operating, servicing. Equally important is the fact that these are **GOOD JOBS**—offering the kind of a future that an untrained man often dreams about.

No previous technical experience or advanced education needed. Prepare for this profitable field in your spare time at home, or in our modern Chicago or Toronto Laboratories. Nothing else like it! Send for **FREE** details.



21 INCH
Build and keep this BIG DeVry Engineered TV set—easily converted to U.H.F. (DeVry offers another home training, but without the TV set.)

EARN WHILE YOU LEARN

After you get part of DeVry Tech's training with equipment at home, you may then in your spare time, begin to earn real money servicing Radio and Television sets.

COLOR TV

DeVry Tech's program also includes training in Color Television

Your GUIDE

to Profitable Job Opportunities

- TV-Radio Broadcast Technician
- Color Television Specialist
- Radar Operator • Laboratory Technician
- Airline Radio Man • Computer Specialist
- Quality Control Manager
- Your Own Sales & Service Shop
- . . . PLUS MANY OTHERS**

YOU GET THE SAME EMPLOYMENT SERVICE

that has helped thousands of our graduates toward fine careers in Electronics.



Send for FREE BOOKLET TODAY!

Accredited Member of National Home Study Council

"One of North America's Foremost Electronics Training Centers"



DeVRY TECHNICAL INSTITUTE

CHICAGO 41, ILLINOIS



You work over **300** Learn-By-Doing projects

Build over 300 practical projects from many shipments of Radio-Electronic parts. You build and operate TV-Radio circuits . . . wireless microphone . . . and many other major projects—all designed to provide outstanding practical experience at home.

ACT NOW! Get information-packed publication **FREE!** Mail coupon today.

DeVRY TECHNICAL INSTITUTE

4141 Belmont Ave., Chicago 41, Ill., Dept. PE-3-R


Please give me your **FREE** booklet, "Electronics in Space Travel," and tell me how I may prepare to enter one or more branches of Electronics.

Name _____ Age _____

Street _____ PLEASE PRINT Apt. _____

City _____ Zone _____ State _____

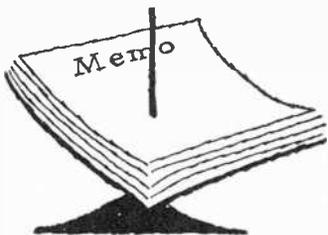2044 Canadian residents address: DeVry Tech of Canada, Ltd. 970 Lawrence Avenue West, Toronto, Ontario



Notes from the Editor

THE SHORT-WAVE CRISIS. I have been reading a rather disconcerting report on the future of long-distance (DX) communications. In talking about the influence of sunspots on short-wave reception, the writer of this report correctly points out that many hams and short-wave listeners are unaware that the superb short-wave receiving conditions experienced throughout the last four years may soon be a thing of the past. In fact, he predicts that most of the short-wave broadcasting bands will be almost totally useless by early 1963!

The effect of sunspots on short-wave reception has been well established. As the number of sunspots increase, so does the maximum usable short-wave broadcasting frequency. During the peak sunspot activity in late 1958, there were instances of transcontinental reception at frequencies above 50 mc. Throughout this same period, reception was astonishingly good on all of the major short-wave broadcasting bands from 9 mc. to 26 mc. As the number of sunspots decline, however, we can expect to hear fewer and fewer broadcasts on the 15-, 17-, 21-, and 26-mc. bands from overseas stations--regardless of power. In addition, the number of hours the 9- and 11-mc. bands will be usable may be reduced by up to 50%.

The rapidly approaching scramble for short-wave broadcasting frequencies below 12 mc. is not going unnoticed. Greater emphasis is being placed on v.h.f. scatter communications networks unaffected by sunspots. Extensive use of new underseas telephone cables is also visualized. POPULAR ELECTRONICS is in the midst of preparing a story on the "crisis in short-wave communications." But before that appears in print--a word to hams and SWL's. There is little doubt that the fall and winter of 1961-62 will be the last good seasons for DX above 15 mc.


REMEMBER YOUR FAVORITE AUTHOR. We would like to remind our readers of the "Double Rate Bonus" that is in effect for feature articles published in POPULAR ELECTRONICS from January through June of this year. Complete details were given in the December 1960 "Notes from the Editor." To review briefly, one bonus will be given for the best article on a hi-fi subject, a second one for a topnotch construction project, and a third will go to the writer of a major news feature in the field of electronics. The editors' decision as to the articles meriting consideration for the double rate will be based primarily upon reader reaction; so if you see a story that you particularly like, please let us know immediately. Since our feature articles normally pay between \$150 and \$300, the double rate will be good news for three deserving authors.

Oliver P. Fenell

AT LAST!

RADIO-TV and ELECTRONICS TRAINING

.... AT A PRICE YOU CAN AFFORD!

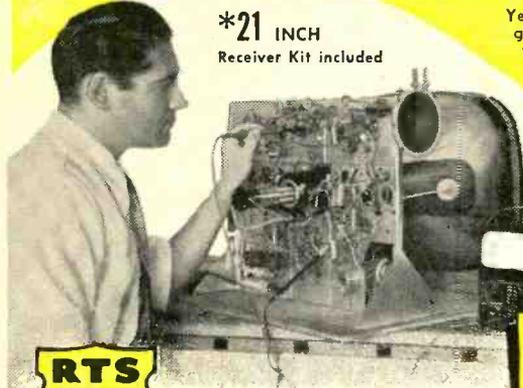

***21 INCH**
Receiver Kit included

Yes, this great course costs far less than any training of its kind given by other major schools! Radio-Television Training School will train you for a good job in Television or Industrial Electronics — **AT HOME IN YOUR SPARE TIME.**

Think of it—a complete training program including over 120 lessons, Fourteen Big Radio-Television Kits, Complete Color-TV Instruction, Unlimited Consultation Service . . . **ALL at a really big saving to you.** How can we do this? Write to us today . . . and find out!

And what's more — you can (if you wish)

OPEN YOUR OWN RTS-APPROVED AND FINANCED RADIO-TV SERVICE SHOP

We Want Many More Shops This Year

This 38 year old training organization — called RTS, that's Radio-Television Training School — wants to establish a string of Radio-TV Repair Shops in principal cities throughout the U. S. So far, a great many such shops are **NOW IN BUSINESS AND PROSPERING.** We are helping and training ambitious men to become future owners and operators of these shops in all areas.

FOR UNSKILLED INEXPERIENCED MEN ONLY — WE TRAIN YOU OUR WAY!

We must insist that the men we sign up to be trained in Radio-TV Repair, Merchandising and Sales by our training methods—because **WE KNOW** the requirements of the industry. Therefore, we will **TRAIN YOU . . .** we will show you how to earn **EXTRA CASH**, during the first month or two of your training period. **YOU KEEP YOUR PRESENT JOB. TRAINING TAKES PLACE IN YOUR OWN HOME, IN YOUR SPARE TIME!**

COMPLETE COLOR TV INSTRUCTION INCLUDED

you build these and other units




MULTIMETER KIT INCLUDED!

*tubes excluded

RADIO-TELEVISION TRAINING SCHOOL

815 EAST ROSECRANS AVENUE
LOS ANGELES 59 CALIFORNIA

Est. 1922

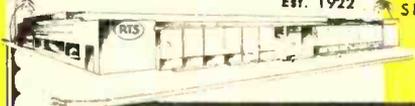

ACT NOW!

Get your free book on the **FAMOUS RTS BUSINESS PLAN** find out how you can open **A REPAIR SHOP OF YOUR OWN**

We supply and finance your equipment

When you are ready and qualified to operate one of our RTS-Approved TV Repair Shops **WE WILL SUPPLY AND FINANCE EVERY BIT OF EQUIPMENT YOU NEED TO GET STARTED** plus an inventory of parts and supplies. In other words we will stake you . . . **AN OFFER NEVER MADE BEFORE BY ANY TRAINING ORGANIZATION.** Under the RTS Business Plan you receive:

1. An electric sign for the shop front.
2. Complete laboratory of test equipment.
3. Letterheads, calling cards, repair tickets, etc.
4. Basic inventory of tubes, parts, supplies.
5. Complete advertising and promotional material.
6. Plans for shop arrangement.
7. Instructions on how to go into business.
8. Continuous consultation and help.
9. The right to use RTS Seal of Approval, and the RTS Credo.
10. The right to use the Famous Trade Mark.

CUT OUT AND MAIL — TODAY!

RADIO-TELEVISION TRAINING SCHOOL
815 EAST ROSECRANS AVE Dept. PE-31
LOS ANGELES 59 CALIFORNIA

SEND ME FREE — all of these big opportunity books — "Good Jobs in TV-Electronics," "A Repair Shop of Your Own" and "Sample Lesson." I am interested in:

- Radio-Television Industrial Electronics (Automation)

Name _____ Age _____

Address _____

City & State _____

30

Mail This Coupon Now — No Salesman Will Call.



ALL THESE FREE!



RTS' Membership in The Association of Home Study Schools is your assurance of Reliability, Integrity, and Quality of Training.




POP'tronics

NEWS SCOPE

◀ **HOLLYWOOD LOST OUT** when the Atomic Energy Commission signed up the Hughes mobile "Mobot Mark II." A "monster" on wheels, the Mark II is an improved version of its older brother. With three joints in each arm, it is strong enough to lift a lead brick, yet delicate enough to replace a light bulb. Two TV eyes mounted on snail-like tentacles focus on the work the hands are performing, keeping the operator—more than 100 "safe" feet away—informed of what is going on. Hughes engineers say this trainable "monster" can perform complicated jobs after only one lesson. Tapes, filed away for future use, act as its memory.



◀ **MOTOROLA BREAKS WITH TRADITION**—the inexpensive conventional a.c.-d.c. table radio, tagged the "All-American 5" by servicemen, is giving ground to a jazzed-up job which sports a push-pull audio output stage and a tone-compensated loudness control. Motorola admits that its new sets aren't hi-fi in the "purest" sense of the word, but they claim that the improved circuitry reproduces virtually everything being broadcast by AM stations. Maybe this is the greatest thing to happen to radio since Kate Smith.

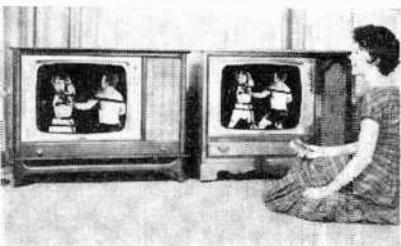

◀ **TV CLOSE-UPS** or enlargements of the broadcast picture can be had by remote control in the 1961 Hoffman Electronics' home television receivers. Depressing the "Close-Up" button on the remote unit beams a high-frequency, transistor-powered signal to the TV receiver, instantly increasing the center of the image on the viewing screen by 25%. This close-up feature is ideal for watching sporting events such as boxing matches, horse races, bowling, and baseball games—spitball pitchers better be careful this coming season! In addition, the remote control lets the user select any TV channel, adjust volume to desired level, kill commercials with a mute button, and turn the set on or off.




◀ **NEW SLANT ON SPACE**—Resembling a tilted outdoor movie screen, the skyward side of this white-faced structure contains nearly 9000 tiny radar antennas. The result: this electronic Cyclops—known as ESAR—can "look" at a wide expanse of space without turning its "head" and thus track hundreds of space targets at one time. Built by Bendix for the U.S.A.F. Rome Air Development Center and the Advanced Research Projects Agency, ESAR (Electronically Steerable Array Radar) is already in operation at Towson, Md. Bendix engineers report that systems of this type may some day be used to communicate with space ships millions of miles from Earth.


POPULAR ELECTRONICS



◀ **TOMORROW'S** U.S. Army riflemen will be able to spot the enemy better in the dark than World War II infantrymen—thanks to Raytheon's new lightweight "sniperscope" infrared gunsight. The target image on the new gunsight is twice as big, allowing more positive identification and making it easier to detect camouflage attempts. Also, the enemy can no longer detect the sniper—a remote infrared searchlight covers a large target area, and the sniper, using only the infrared detector on his "scope," simply hunts for suitable targets. When necessary, the rifleman can generate his own infrared beam at the flip of a switch.

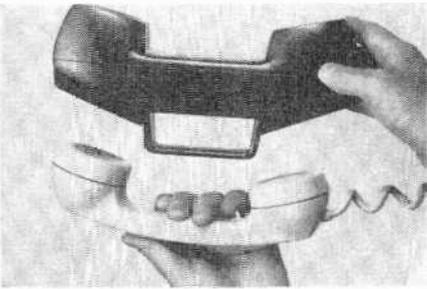

◀ **TELEPHONE "SCRAMBLERS"**—electronic devices to prevent "high-level eavesdropping"—were first popularized early in World War II by the late President Roosevelt and by Prime Minister Churchill. Now, a portable security "scrambler" device developed by Delcon Corp., Palo Alto, Calif., permits secret telephone communication in business, industry, and law enforcement. The transistorized device is produced in matched pairs—only two alike—weighing only 27 ounces. Fitted against any standard telephone handset—without any wire connections, the first scrambler converts ordinary speech into incoherent gibberish, then transmits it over the telephone line to the second scrambler which translates the gibberish back into normal speech. This may be new to the electronics field, but women have been doing it for years.

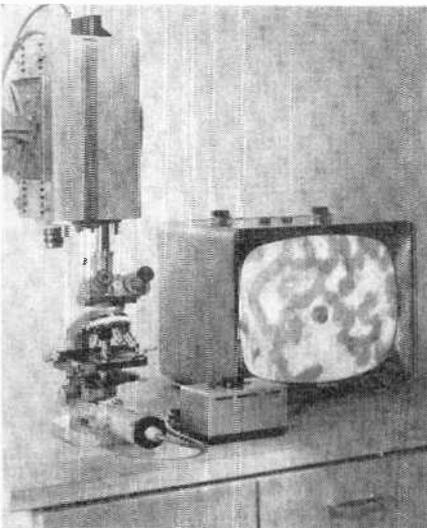

◀ **SNOOPING ON MICROBES** during classroom lectures is now possible with a closed-circuit TV-microscope system. Developed through the combined efforts of the Elgeet Optical Company (of Rochester, N. Y.), Allen B. DuMont Labs., and Sylvania, the TV microscope closes the gap between the maximum 2000X magnification capabilities of optical microscopes and the minimum 5000X magnification of electron microscopes. Accomplished by means of a special arrangement of objective lenses, the microscope's magnification potential is further increased by the 17-inch screen of the TV monitor. The TV microscope's comparatively low cost—under \$1500 for a 300-line resolution system and under \$2200 for 600-line resolution—places the new device within range of both schools and researchers.



**WITH VOCALINE
4-CHANNEL COMMAIRE
ED-27M CITIZENS BAND RADIO**

**Ranked first for
dependability • distance • clarity**

The difference between Vocaline Commaire ED-27M and ordinary Citizens band radios can be as substantial as the difference between the two photos above. For distance, reliability, flexibility and uniform clarity on the entire 22 channel citizens band . . . you have only to hear the Commaire to convince yourself that this is the one unit that is unmatched by any other in its class. Specifications and features: Finished to pass U.S. Navy 500 hour salt spray test! "Silent-Aire" squelch with exclusive noise suppression. Double conversion superheterodyne single crystal receiver — accepted as the finest. Transistorized power supply. 5 watts input — 3 watts output. 6 and 12 VDC — 115 VAC. Only 5¼" x 9¼" x 8¼".

\$189.50 each, list.

Also available in single channel model—Commaire ED-27M—proven as the world's finest performing class D Citizens Band Radio! Only \$179.50 each, list.



VOCALINE

COMPANY OF AMERICA

410 Coultter Street Old Saybrook, Conn.

Send complete literature to:

Name _____

Address _____

City _____ Zone _____ State _____

**FCC
Report**

By **ROBERT E. TALL**
Washington Correspondent

THE Class D Citizens Radio Service is destined to reach at least 300,000 licenses before its momentum starts to taper off (almost double the number of CB'ers as of December, 1959), and it will overtake and pass the Amateur Radio Service in number of licensees this year. These are the views of Ivan H. Loucks, who heads the FCC division responsible for the CB service.

The greatest utility of the CB service, the FCC official said, has been in introducing vehicular radio to the general population at bargain prices, and in serving as a steppingstone for more people to use radio communications of all kinds.

A flat "no" has been given to the Connelly Sales Co. of La Mirada, Calif., on its petition for CB rule changes to (1) increase the input power from 5 to 25 watts, and (2) require the use of the same frequency by two stations talking to each other. (See *FCC Report*, October, 1960.)


After the petition was publicized last year, the FCC received many letters from the CB fraternity, mostly concerned with the power question, and all but a few opposing any increase. Many of the CB'ers writing to the agency felt that complaints of too little communications range stemmed from the use of inefficient units and poorly designed antennas, and the FCC said it feels the same way.

According to the Commission, good engineering practice would require that an increase in power be accompanied by higher technical standards, such as those in effect for all other land mobile radio units operating with more than five watts; and this would increase the cost of the CB equipment and curb its appeal for many users. Also, the agency pointed out, the high-powered stations would not

Always say you saw it in—POPULAR ELECTRONICS

These men are getting practical training in...

ELECTRICITY ELECTRONICS

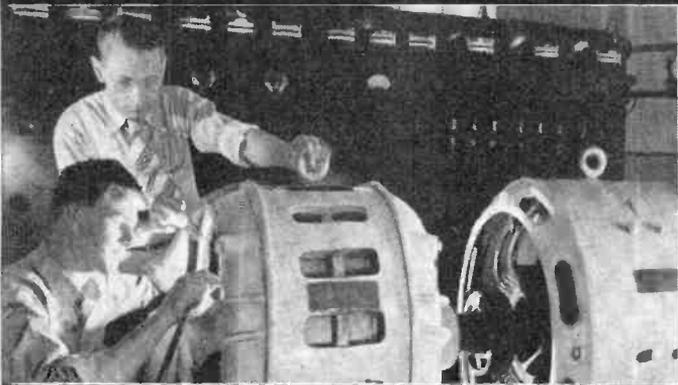

On Real:

**A. C. and D. C. Motors
Generators
Switchboards
Controllers
Modern Appliances
Automatic Electronic
Control Units**


(Shown at left—Instructor explaining operation and testing of a large Motor Generator in our A. C. Department.)

TELEVISION RADIO ELECTRONICS

On Real:

**Television Receivers
Black & White and Color
AM-FM and Auto Radios
Transistors—Printed
Circuits—Test Equipment**

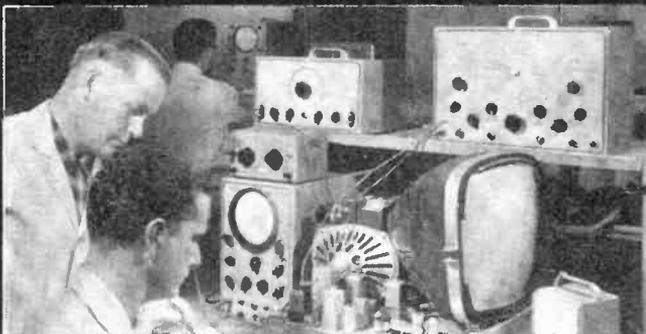(Right — Instructor helping students check the wiring and trace circuits of television receivers.)



Train in the NEW SHOP-LABS of COYNE

Largest, Oldest, Best Equipped School of its Kind in the U.S.

Prepare for your future now in today's top opportunity field. Don't be satisfied with a "No Future" job. Train the Coyne way for a better job in a field that offers a world of opportunities in the years ahead.

You train in Chicago—the Electrical and Electronic Center of the World—on real equipment. Professional and experienced instructors show you how, then you do practical jobs yourself. No previous experience or advanced education is needed.

FINANCE PLAN: Enroll now, pay most of tuition after graduation. Part-time employment help for students.

Mail coupon or write to address below for free book—"Guide to Careers". Whether you prefer Electricity, Television-Radio or Combined Electronics Training, which includes both fields, this book describes all training and gives facts to Vets and Non-Vets.



B. W. Cook, Jr., Pres. **COYNE** Founded 1899
ELECTRICAL SCHOOL

CHARTERED AS AN EDUCATIONAL INSTITUTION NOT FOR PROFIT
1501 W. CONGRESS PARKWAY, CHICAGO 7 Dept. 31-2C
ELECTRICITY ★ RADIO ★ TELEVISION ★ REFRIGERATION ★ ELECTRONICS

Mail Coupon or Write for FREE Book

Book comes by mail. No obligation and no salesman will call.

Mail coupon below in an Envelope or paste on a Postal Card or write Address given and Free book, "Guide to Careers", with information will be sent to you by return mail.

COYNE ELECTRICAL SCHOOL
Dept. 31-2C, New Coyne Building
1501 W. Congress Pkwy., Chicago 7, Illinois

Send BIG FREE book and details of all the training you offer. However, I am especially interested in:

Electricity Television Both Fields

Name _____

Address _____

City _____ State _____

(I understand no Salesman will call)

**TIME TO CLEAN UP
YOUR SYSTEM...**


Norelco[®]

T-7 LOUDSPEAKERS
with voice coil magnets of
Ticonal-7 steel (30% more
efficient* than Alnico V)

*... 30% more efficient
response to the full signal range
of your amplifier... **WHETHER
ITS RATED OUTPUT is
10 WATTS or a HUNDRED...**
at any listening level from a
whisper to a shout!

**GUILD-CRAFTED BY PHILIPS OF
THE NETHERLANDS TO GIVE YOU**

THE CLEANEST SOUND AROUND

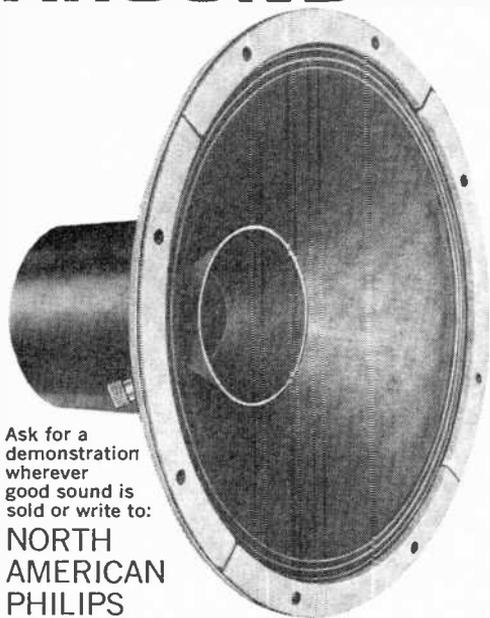

Ask for a
demonstration
wherever
good sound is
sold or write to:

**NORTH
AMERICAN
PHILIPS
CO., INC.**

High Fidelity Products Division,
230 Duffy Avenue,
Hicksville, L. I., N. Y.

be compatible in the same area with existing five-watt equipment, and hundreds of thousands of existing CB units could be obsoleted.

On the question of requiring use of the same frequency by two stations talking to each other, the agency said that such a practice would be a good idea whenever possible; but if single-frequency communications were required, it would restrict the fullest use of the service. The Commission added, however, that if CB licensees abuse the privilege of cross-channel operation to further any type of hobby activities, it's going to reconsider its position.

Additional types of emission for the Citizens Radio Service were also requested by Connelly, and the West Coast outfit came off a little better on this one. The Commission said that either single or double sideband, with or without carrier, or with reduced carrier, "is included" in its current definition of permissible CB communications. Here again, however, a close watch over any such uses is going to be made, particularly in connection with power input; and if there are a large number of violations on this score, or if too much interference is being caused to conventional CB units, a cutback will be in order.

The application form changes for amateurs that we told you about last October have now been put into effect on an optional basis, and will become mandatory the beginning of July. After that time, you can't use the present Form 405-A (renewal without modification) or Form 602 (for a station at a military post).


Amateur Form 610—now employed for operator and/or station licenses and for clubs and additional station licenses—can be used after June 30 only for an operator license, a combined operator and station license, or a station license where the licensee already has an operator's license. And there's a new Form 610-A—which replaces the 602—to be used for an additional station, a club station, and a station "for recreation under military auspices," where more detailed information about the station is required.

Also, the time for filing renewal applications for amateur licenses has been changed from "within 120 days" of expiration of the old license to "within 60 days" of the expiration date. -30-

BREAK THROUGH TO HIGHER PAY

in ELECTRONICS

TV-RADIO

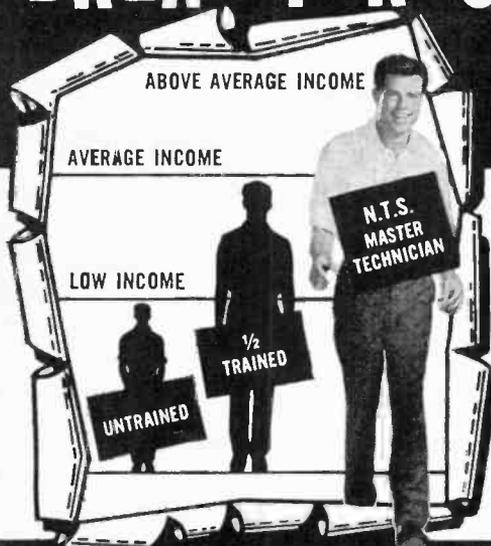

START NOW! Break through the Earning Barrier that stops half-trained men. N.T.S. "All-Phase" training prepares you — at home in spare time — for a high-paying CAREER in Electronics — TV — Radio as a MASTER TECHNICIAN. One Master Course at One Low Tuition trains you for unlimited opportunities in All Phases: *Servicing, Communications, Preparation F.C.C. License, Broadcasting, Manufacturing, Automation, Radar and Micro-Waves, Missile and Rocket Projects.*

A more rewarding job... a secure future... a richer, fuller life can be yours! As an N. T. S. MASTER TECHNICIAN you can go straight to the top in industry... or in your own profitable business.


You work on actual job projects



SUCCEED IN MANY HIGH-PAYING JOBS LIKE THESE...

- TV-Radio Sales, Service and Repair
- Profitable Business of Your Own
- Communications Technician — F.C.C. License
- Hi-Fi, Stereo & Sound Recording Specialist
- TV-Radio Broadcasting Operator
- Technician in Computers & Missiles
- Electronics Field Engineer
- Specialist in Microwaves & Servomechanisms
- Expert Trouble Shooter
- All-Phase Master Technician

19 BIG KITS YOURS TO KEEP

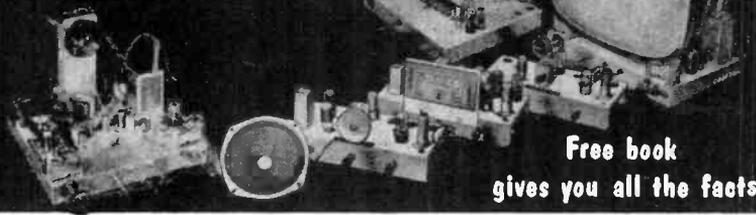

Free book gives you all the facts

NATIONAL TECHNICAL SCHOOLS

WORLD-WIDE TRAINING SINCE 1905
4000 SO. FIGUEROA ST., LOS ANGELES 37, CALIF., U. S. A.

Write Dept. R2G-31



N.T.S. Shop-Tested HOME TRAINING is **Better, More Complete, Lower Cost**... and it is your key to the most fascinating, opportunity-filled industry today!

ditional cost. You also get a Professional Multimeter for your practical job projects.

YOU LEARN QUICKLY AND EASILY THE N.T.S. SHOP-TESTED WAY

You get lessons, manuals, job projects, unlimited consultation, graduate advisory service. You build a Short Wave-Long Wave Superhet Receiver, plus a large-screen TV set from the ground up, with parts we send you at no addi-

EARN AS YOU LEARN... WE SHOW YOU HOW!

Many students pay for entire tuition — and earn much more — with spare time work they perform while training. You can do the same... we show you how.

SEND FOR INFORMATION NOW... TODAY! IT COSTS YOU NOTHING TO INVESTIGATE.

RESIDENT TRAINING AT LOS ANGELES
If you wish to take your training in our Resident School at Los Angeles, start NOW in our big, modern Shops and Labs. Work with the latest Auto and Diesel engines — all types — fuel injection, automatic transmissions, all power equipment — most complete facilities offered by any school. Expert, friendly instructors. Graduate Employment Service. Help in finding home near school — and part time job while you learn.
WRITE FOR SPECIAL RESIDENT SCHOOL CATALOG AND INFORMATION



ACCREDITED MEMBER... the only nationally recognized accrediting agency for private home study schools.

N.T.S. HOME TRAINING is

- Classroom Developed
- Lab-Studio Planned
- Shop-Tested
- Industry-Approved
- Specifically Designed for Home Study



MAIL COUPON NOW for FREE BOOK and ACTUAL LESSON

NATIONAL TECHNICAL SCHOOLS

WORLD-WIDE TRAINING SINCE 1905

Mail Now To
National Technical Schools, Dept. R2G-31
4000 S. Figueroa St., Los Angeles 37, Calif.

Please rush FREE Electronics-TV-Radio "Opportunity" Book and Actual Lesson. No Salesman will call.

Name _____ Age _____
Address _____
City _____ Zone _____ State _____
 Check here if interested ONLY in Resident Training at Los Angeles.
VETERANS: Give date of discharge _____

NO OBLIGATION! NO SALESMAN WILL CALL

fastest, easiest way
to learn math
BASIC MATHEMATICS

(A PICTURED-TEXT COURSE)
by Norman H. Crowhurst

New approach and pictorial technique makes it easier than ever before possible to learn all the math you need to get ahead.

This remarkable 4-volume course takes you in easy stages from counting through algebra, geometry, trigonometry to calculus so that you will understand easily, quickly, all the math you will need to get ahead—regardless of your previous education! It employs an exciting new technique wherein basic mathematics is presented as one continuous development of mathematics. The individual branches of mathematics are not divided into separate and unrelated subjects. Algebra, geometry, trigonometry, calculus are interwoven at progressively rising levels in the different volumes. Each volume reinforces your understanding as you penetrate more deeply into the subjects. Selected illustrations create clear images of mathematical ideas formerly difficult to understand or imagine through words alone.

NOW AVAILABLE VOLUME I—FIRST STEP TOWARD MASTERY OF MATHEMATICS—In Volume I you gain the self-confidence you need to master mathematics! You build a solid foundation in mathematics without realizing that you are being introduced to subjects usually considered dry and difficult-to-master. You learn addition, subtraction, multiplication, division, taking of roots, decimals, areas, angles, distance/time, rate of growth, ratios, percentages, etc. All subjects follow one another so easily that learning is 'painless'.


Imagine a dedicated teacher sitting next to you and very patiently and painstakingly explaining step by step the processes of mathematics in each subject area... This is Basic Mathematics.

WHY A KNOWLEDGE OF MATH SPEEDS YOUR PROGRESS IN ELECTRONICS—No matter what your plans are in electronics—mathematics plays a vital role. The more math you know, the easier it is to learn electronics. And, if you've set your sights on being an advanced technician or an engineer, you must have a firm foundation in mathematics to achieve your goal. This course will speed you towards your goal.

4 VOLUMES TAKE YOU FROM COUNTING TO CALCULUS—VOL. I—Arithmetic as An Outgrowth of Learning to Count—(now available) #268-1, \$3.90. VOL. II—Introducing Algebra, Geometry, Trigonometry, Calculus as Ways of Thinking in Mathematics. (available May). VOL. III—Developing Algebra, Geometry, Trigonometry, Calculus as Working Methods in Mathematics. (available in late 1961). VOL. IV—Developing Algebra, Geometry, Trigonometry, Calculus as Analytical Methods in Mathematics. (available in late 1961).

At book stores, parts distributors, or direct.

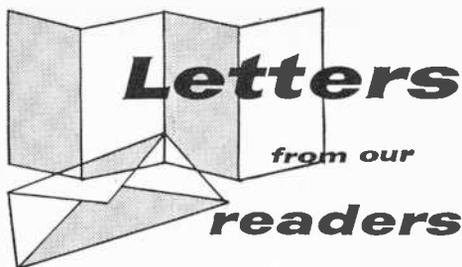No matter where you buy these books, we guarantee satisfaction or your money back within 30 days. PE-3



"Tiny Mite" P.A.

■ Glancing through some back copies of POPULAR ELECTRONICS, I came across the "Tiny Mite" amplifier in your June 1960 issue. I have been deliberating whether to construct this project, since I would like to connect the "Tiny Mite" to a public address system located some distance away. Could I get good results with this kind of a setup?

ALAN KOUDELKA
Long Island City, N.Y.

With the addition of suitable coupling components, the output from the "Tiny Mite" can be fed into any amplifier for greater gain or speaker listening. Since you state that the "Tiny Mite" would be located some distance from your amplifier, you would probably have to insert a cathode follower or other impedance-coupling device at the output of the "Tiny Mite."

One-Tube Tuner Recommended

■ I constructed several "one-tube wonders" similar to the FM tuner described in your August 1960 issue, and was completely dissatisfied every time. However, your model is an excellent performer and I should like to recommend it to others who want to listen to FM or who like to build experimental circuits. The parts values are not at all



critical—I substituted almost every part and wound my own coils from junk-box odds and ends. The resultant tuner is adequate in every respect.

DUANE R. DUNGAN
Manhattan Beach, Calif.

"Sweet Sixteen"

■ I plan to build two of your "Sweet Sixteen" speaker systems (January 1961 issue), but I wonder if you can tell me how I can extend the range from 10,000 to 20,000 cycles?

R. G. KING
Costa Mesa, Calif.

A small (3" or 5") tweeter can be easily added to cover the range you mention—simply wire the

Always say you saw it in—POPULAR ELECTRONICS

JOHN F. RIDER PUBLISHER INC.
116 West 14th Street, New York 11, N. Y.
Canada: Chas. W. Pointon, Ltd., 66 Racine Rd., Rexdale, Ont.
Export: Acme Code Company, Inc., 630 9th Ave., N. Y.

only for those who really need them...

CADRE



Only a short time ago, the FCC opened 22 channels for Citizens Band operation. Licensing was radically simplified. Where formerly two-way radio licenses were granted only to public safety agencies and certain other special groups, **SUDDENLY, EVERYBODY COULD HAVE 2-WAY RADIO!**

... providing, of course, he could afford the bulk and cost of the equipment that was then available.

Yet in spite of the bulk and the cost, nearly two million Citizens Band transceivers have been purchased to date! A tremendous demand has developed!

You can imagine what will happen now that compact, professional-quality instruments like the CADRE '500' and the CADRE '100' are available!


These CADRE units are built to the highest standards of the electronics industry, by a company that has been long established as a prime manufacturer of precision electronic research equipment and computer assemblies. CADRE transceivers are 100% transistorized—compact, lightweight... engineered for unparalleled performance and reliability.

The CADRE 5-Watt Transceiver, at \$199.95, for example, for offices, homes, cars, trucks, boats, aircraft, etc., measures a mere 11 x 5 x 3", weighs less than 6 pounds! Nevertheless, it offers 5 crystal-controlled transmit/receive channels (may be used on all 22), and a range of 10 miles on land, 20 over water!

The CADRE 100-MW Transceiver, \$124.95, fits into a shirt pocket! Weighs 20 ounces, yet receives and transmits on any of the 22 channels... efficiently, clearly... without annoying noise. A perfect "pocket telephone"!

For the time being, it is unlikely that there will be enough CADRE transceivers to meet *all* the demand. Obviously, our dealers cannot restrict their sale to the fields of medicine, agriculture, transportation, municipal services, etc. However, since these CADRE units were engineered for professional and serious commercial applications—and cost more than ordinary CB transceivers—we believe that as "water finds its own level," CADRE transceivers will, for the most part, find their way into the hands of those who really need them.

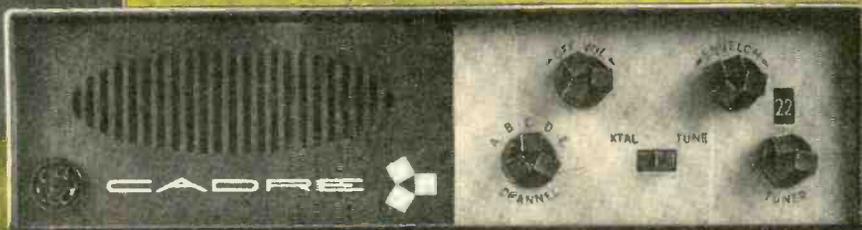Write for complete information and detailed specifications.



CADRE INDUSTRIES CORP., Endicott, N. Y.

Prices appearing in this advertisement are suggested retail prices.



**The
Beautiful
Schober
CONSOLETTA**

—only small organ with two full 61-note key-boards and 22 stops. Requires only 2'x3'2" floor space! Commercial value approximately \$1800 or more.

BUILD THIS SUPERB Schober ORGAN FROM SIMPLE KITS and save over 50%!

Give Your Family A Lifetime of Musical Joy With A Magnificent Schober Electronic Organ!

Now you can build the brilliant, full-range Schober CONSOLETTA or the larger CONCERT MODEL with simple hand tools! No skills are needed; no woodworking necessary. Just assemble, clearly marked electronic parts guided by step-by-step instructions. You build from kits, as fast or as slowly as you please... at home, in your spare time — with a small table serving as your entire work shop.

Pay As You Build!

Start building your organ at once, investing just \$18.94! The superb instru-

ment you assemble is as fine, and technically perfect, as a commercial organ... yet you save over 50% on quality electronic parts, high-priced labor, usual store mark-up!

THE GREAT CONCERT MODEL meets specifications of American Guild of Organists

Free Booklet

Send for 16-page booklet in full color describing Schober organs you may build for home, church or school, plus articles on how easy it is to build your own organ and how pleasant it is to learn to play. Also available is 10" LP demonstration record (price \$2.00 — refundable on first order). Send for literature. No obligation and no salesman will call.

Mail This Coupon For FREE Schober Literature And Hi-Fi Demonstration Record TODAY!



The Schober Organ Corp., Dept. PE-4
43 West 61st St., New York 23, N. Y.

- Please send me FREE full-color booklet and other literature on the Schober organs.
- Please send me the 10" hi-fi Schober demonstration record. I enclose \$2.00 (refundable on receipt of my first kit order).

Name.....
Address.....
City..... Zone... State.....

Letters

(Continued from page 14)

tweeter in series with a 1- or 2-uf. paper or oil-filled capacitor and hook it across the two leads from the amplifier. If you don't have such a capacitor on hand, you can reach the required value by wiring a number of smaller units in parallel—the smaller the capacitance, the higher the frequency at which the speaker will become effective.

"Down With the FCC"

■ You have said that you believe the caliber of the Citizens Band operator will improve as the novelty wears off (*Letters from Our Readers*, Oct., 1960). I think you are mistaken.

The Citizens Band has been "squelched" by the FCC in its usually efficient manner. They called it a "Civilian Band," then made rules that buttoned it up to form a "Business Band."

It is my opinion that we need a little more democracy in this country—in other words, all



Commissioners should be re-elected every two years so that we can vote them out when we want to do so.

MYRON R. FOX
Brookville, Ohio

It is our opinion that what you want is a loosening of the rules to permit rag-chewing on the Citizens Band. This would turn a band that is useful for both business and personal communications into a QRM-riddled mess. Why not consider amateur radio? There you can talk to your heart's content—if you can prove that you are technically competent to handle a transmitter.

Carl and Jerry Fan

■ I enjoy your Carl and Jerry series very much and think it is a strong point of the magazine. But the author always tells us about the interesting things that Carl and Jerry build and never gives any construction details. There have been about a dozen projects that I wanted to build but didn't have enough information.

H. K. MONROE
Berea, Ohio

Carl and Jerry are fictional characters and, as such, are intended to entertain—not instruct. About the only "construction" we think you're likely to get out of a Carl and Jerry episode is an idea for a project. From there on, it's up to you to dig into the available literature and come up with a project, much as they do. You'll have to work just that much harder, but you'll also experience the added satisfaction that comes from building "from the ground up."

-50-

FREE

Completion of the Master Course (both Sections) will prepare you for a First Class Commercial Radio Telephone License with a Radar Endorsement. Should you fail to pass the FCC examination for this license after successfully completing the Master Course, you will receive a full refund of all tuition payments. This guarantee is valid for the entire period of your enrollment agreement.



How to get a
Commercial
FCC License

tells how

Your FCC Commercial License —or your money back

**"License and \$25 raise due to
Cleveland Institute training"**

"I sat for and passed the FCC exam for my second class license. This meant a promotion to Senior Radio Technician with the Wyoming Highway Department, a \$25 a month raise and a District of my own for all maintenance on the State's two-way communication system. I wish to sincerely thank you and the school for the wonderful radio knowledge you have passed on to me. I highly recommend the school to all acquaintances who might possibly be interested in radio. I am truly convinced I could never have passed the FCC exam without your wonderful help and consideration for anyone wishing to help themselves."

CHARLES C. ROBERSON, Cheyenne, Wyoming

GIE HELPS
TRAINEES GET BETTER JOBS

a successful plan for . . .
Electronics Training

How to get a
Commercial
FCC License

Opportunities in
Electronics for You

Cleveland Institute Announces

A New And Dynamic

Technician Training Program
in Computers, Servo Mechanisms,
Magnetic Amplifiers, and Others

Other advanced fields covered include Basic Math, A. C. Circuit Analysis, Pulse Circuitry, Color TV, Radar, Advanced Measuring Techniques, Industrial Electronics, Instrumentation, Automation, Radio Telemetry. Send for information today.

GET THIS HANDY POCKET
ELECTRONICS DATA GUIDE

FREE...

Puts all the commonly used conversion factors, formulas, tables, and color codes at your fingertips. Yours absolutely free if you mail the coupon today. No further obligation!
TO GET THIS FREE GIFT, MAIL COUPON TODAY!



Cleveland Institute of Electronics

Desk PE-75, 1776 E. 17th St., Cleveland 14, Ohio
Accredited by National Home Study Council.

Please send Free Career Information Material prepared to help me get ahead in Electronics. I have had training or experience in Electronics as indicated below.

- | | |
|---|---|
| <input type="checkbox"/> Military | <input type="checkbox"/> Amateur Radio |
| <input type="checkbox"/> Radio-TV Servicing | <input type="checkbox"/> Broadcasting |
| <input type="checkbox"/> Manufacturing | <input type="checkbox"/> Home Experimenting |
| <input type="checkbox"/> Telephone Company | <input type="checkbox"/> Other |

In what kind of work are you now engaged?

In what branch of Electronics are you interested?

Name Age

Address

City Zone State

PE-75

Cleveland Institute of Electronics

Desk PE-75

1776 E. 17th St.

Cleveland 14, Ohio


March, 1961

17

POP'tronics Bookshelf

"ELECTRICITY: HOW IT WORKS," by Percy Dunsheath. Published by Thomas Y. Crowell Co., 432 Park Ave. S., New York 16, N. Y. 248 pages. Hard cover. \$3.95.

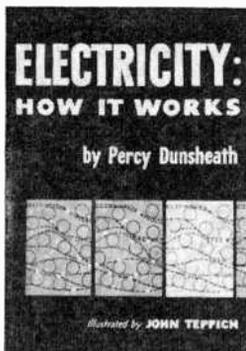This book takes you on a tour through the history of electricity, explaining new puzzles and mysteries as they appear. Sprinkled with descriptions of experiments illustrating many of the basic principles, the book also makes liberal use of figures and graphs. It concludes with a chapter on the free electron, thus bringing up the




theory of electronics. Recommended for the beginner who wants to know more about this fascinating subject.



"SERVICING TV TUNERS," by Jess E. Dines. Published by Howard W. Sams & Co., Inc., 1720 East 38th St., Indianapolis 6, Ind. Soft cover. 272 pages. \$4.95.

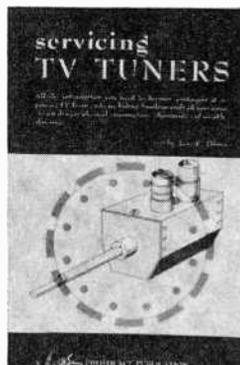The compact structure and rather complex circuitry of TV tuners do not make for easy servicing. But the author believes that a serviceman should have little difficulty in handling any tuner trouble—if he has the full understanding of this important component that this book is intended to provide. One of a series on TV servicing by Mr. Dines, the book not only



NEW DESIGN FEATURES

*
\$189.50



Attractively styled Silver Jet vinyl fabric covered aluminum enclosure with white molded vinyl front.

Citi-fone®

CITIZEN'S BAND RADIO TELEPHONE

- New "noise immune" squelch circuit.
- New "Pi" plate and output tuned circuit assuring maximum transfer of power to antenna.
- Gated audio response for greater talk-power.
- Front panel mounted modulation and R.F. indicator.
- Heavy duty power supply capable of more than twice normal operating requirements.
- Heavy duty, high efficiency coaxial antenna connector.
- External speaker connections.
- Hermetically sealed relay guarantees virtually trouble-free operation.
- High level, full power AM modulation.

TWO STYLES: CD6/6—6 Volt D.C. and 115 Volt A.C.; CD6/12—12 Volt D.C. and 115 Volt A.C.

*Suggested retail price \$189.50 complete with crystals for 1 channel, 2 power cords, mounting bracket, and ceramic microphone with coiled cord and hanger.

MULTI-PRODUCTS COMPANY • 21470 COOLIDGE HIGHWAY • OAK PARK 37, MICHIGAN

Do you WISH you were EMPLOYED in ELECTRONICS?

F.C.C. LICENSE—THE KEY TO BETTER JOBS

An F.C.C. *commercial* (not amateur) license is your ticket to higher pay and more interesting employment. This license is Federal Government evidence of your qualifications in electronics. Employers are eager to hire *licensed* technicians.

WHICH LICENSE FOR WHICH JOB?

The **THIRD CLASS** radiotelephone license is of value primarily in that it qualifies you to take the second class examination. The scope of authority covered by a third class license is extremely limited.

The **SECOND CLASS** radiotelephone license qualifies you to install, maintain and operate most all radiotelephone equipment except commercial broadcast station equipment.

The **FIRST CLASS** radio telephone license qualifies you to install, maintain and operate every type of radiotelephone equipment (except amateur) including all radio and television stations in the United States, its territories and possessions. This is the highest class of radiotelephone license available.

GRANTHAM TRAINING PREPARES YOU

The Grantham course covers the required subject matter completely. Even though it is planned primarily to lead directly to a first class FCC license, it does this by **TEACHING** you electronics. Some of the subjects covered in detail are: Basic Electricity for Beginners, Basic Mathematics, Ohm's and Kirchhoff's Laws, Alternating Current, Frequency and Wavelength, Inductance, Capacitance, Impedance, Resonance, Vacuum Tubes, Transistors, Basic Principles of Amplification, Classes of Amplifiers, Oscillators, Power Supplies, AM Transmitters and Receivers, FM Transmitters and Receivers, Antennas and Transmission Lines, Measuring Instruments, FCC Rules and Regulations, and extensive theory and mathematical calculations associated with all the above subjects explained simply and in detail.

OUR GUARANTEE

If you should fail the F. C. C. exam after finishing our course, we guarantee to give additional training at **NO ADDITIONAL COST**. Read details in our free booklet.


GET your first class commercial F.C.C. LICENSE QUICKLY!

Learn by Correspondence or in Resident Classes

Grantham training is offered by correspondence or in resident classes. Either way, we train you quickly and thoroughly---teach you a great deal of electronics and prepare you to pass the F.C.C. examination for a first class license. Get details now. Mail coupon below.

This booklet **FREE!**

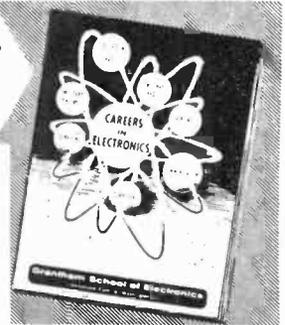This free booklet gives details of our training and explains what an F.C.C. license can do for your future. Send for your copy today.



Upgrade Your Income

To get ahead in electronics—first, you need the proper training; then, you need "proof" of your knowledge. Your first class commercial F.C.C. license is a "diploma" in communications electronics, awarded by the U.S. Government when you pass certain examinations. This diploma is recognized by employers. Grantham School of Electronics specializes in preparing you to **earn** this diploma.

Grantham training is offered in resident classes or by correspondence. Our free booklet gives complete details. If you are interested in preparing for your F.C.C. license, mail the coupon below to the School's home office at 1505 N. Western Ave., Hollywood 27, California—the address given in the coupon—and our free booklet will be mailed to you promptly. No charge—no obligation.

Grantham School of Electronics

HOLLYWOOD CALIF.

SEATTLE WASH.

KANSAS CITY MO.

WASHINGTON D. C.

RESIDENT CLASSES HELD IN FOUR CITIES

If you are interested in attending day or evening classes mail the coupon for free information to our home office in Hollywood, Calif.



(Mail in envelope or paste on postal card)

To: **GRANTHAM SCHOOL OF ELECTRONICS**
1505 N. Western Ave., Hollywood, Calif.

Gentlemen:

Please send me your free booklet telling how I can get my commercial F.C.C. license quickly. I understand there is no obligation and no salesman will call.

Name _____ Age _____

Address _____

City _____ State _____

I am interested in: Home Study, Seattle classes

Hollywood classes, Kansas City classes, Washington classes

MAIL COUPON NOW—NO SALESMAN WILL CALL →


March, 1961

130

**At last!
a speaker cabinet kit
with a choice of styling!**



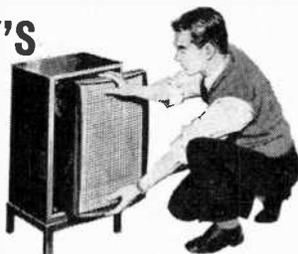**UNIVERSITY'S
MEDALLION
KIT features 5
'Select-a-Style'
snap-on grilles**



NOW, the exciting new styling concept of the Medallion XII speaker system is available in cabinet kit form too! For the first time, you can take pride in assembling a high fidelity speaker cabinet that's styled to your taste . . . and hers too! The secret's in the interchangeable snap-on grilles, available in Swedish Modern, Colonial, Italian Provincial, French Provincial and Contemporary. Practical? If you ever change your decor, just change the grille.

Each grille frame is authentically interpreted, expertly crafted and pre-assembled for you, with only the grille cloth and hardware to be mounted. The cabinet itself is easy to assemble, with every piece precision machined to the closest tolerances . . . selected $\frac{3}{4}$ " hardwoods assuring resonant-free performance. And smooth-grained veneers make it easy to achieve a professional finish.

The Medallion's exceptional versatility extends to its speaker mounting board as well . . . letting you plan virtually any type of multi-speaker system using either a high compliance or high efficiency 12" woofer, 8" cone speaker or driver/horn for mid-range, and wide-angle horn or University's fabulous Sphericon for treble. If you desire a single integrated wide-range speaker, University's new Series 200 high compliance speakers will easily outperform most multi-speaker systems.

And it fits anywhere! On floor or bench . . . even built-in. With or without its matching base, as highboy or lowboy. Only 17"x24"x12 $\frac{1}{2}$ " deep, it's ideal as a stereo pair.

See the Medallion at your University dealer now. You'll surely agree that as a kit, assembled cabinet, or complete Medallion XII speaker system, it's the most intriguing and sensible idea yet in high fidelity!

NET PRICES: Cabinet kit — \$49.95.
Grille kits—Contemporary, \$7.95.
others, \$12.95 each. Base kit—\$12.95.

Write for University's new 'Informal Guide to Component High Fidelity.' Desk A-3, University Loudspeakers, Inc., White Plains, N.Y.



A Division of Ling-Temco Electronics, Inc.

Bookshelf

(Continued from page 18)

describes the mechanical and electrical characteristics of practically every type of TV tuner ever built, but also contains hundreds of schematic diagrams and photos which clarify the detailed circuit discussions. Recommended for anyone who needs a one-source reference volume on all phases of TV tuners.

New Literature

A colorful 64-page catalog, FR-61-G, on TV and radio chemicals, alignment tools, service aids, and hardware is available from GC Electronics Co., 400 S. Wyman St., Rockford, Ill.

The newest (36th) edition of the Harrison Electronic Material Buyer's Guide contains nearly 300 pages and lists a wide range of parts and equipment produced by some 165 different manufacturers. Write to Harrison Radio Corp., 225 Greenwich St., New York 7, N. Y., for your copy.

A complete line of crystals as well as a variety of printed-circuit subassemblies and other items are described in the 32-page 1961 catalog of the International Crystal Mfg. Co., 18 North Lee, Oklahoma City, Okla. New this year are all-transistor subassemblies which, when interwired, form a complete transistorized transceiver for CB or ham use.

Two educational handbooks for secondary-school science classes, "Laboratory Experiments with Radioisotopes for High School Science Demonstrations" and "Teaching with Radioisotopes," are highly recommended to the science teacher and to the "science-fair"-minded student. Copies can be purchased from the Superintendent of Documents, U. S. Government Printing Office, Washington 25, D. C., for 35 and 40 cents respectively.

"Some Plain Talk About Fuel Cells" is a 12-page booklet that discusses recent work in fuel-cell experimentation and development. Write to General Electric Co., Schenectady 5, N. Y., for Booklet GED-4111.


—30—

Always say you saw it in—POPULAR ELECTRONICS

ALLIED value-packed 1961

444-PAGE ELECTRONICS CATALOG

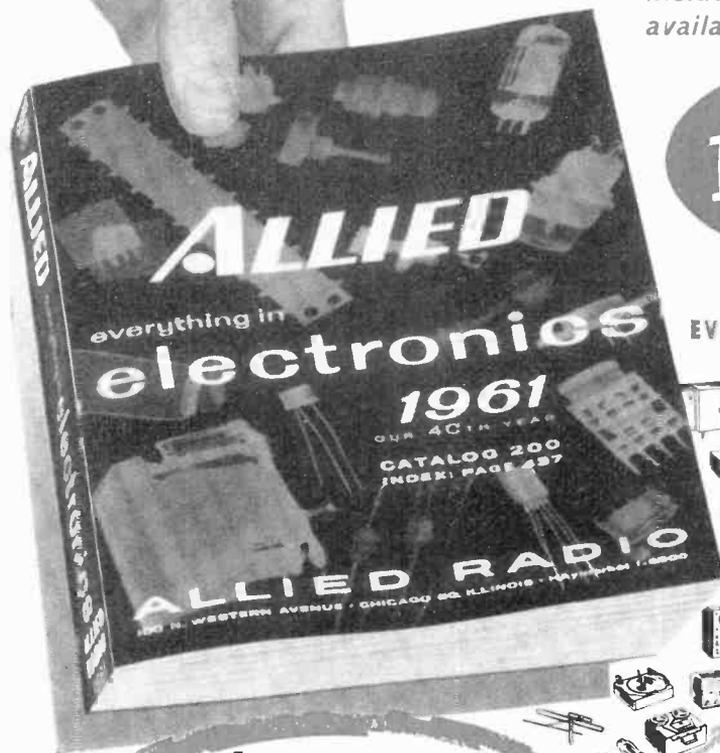including special products available only from Allied



free

SAVE MOST ON EVERYTHING IN ELECTRONICS

- New Stereo Hi-Fi Systems—Everything in Hi-Fi Components
- Money-Saving, Build-Your-Own KNIGHT-KITS® for Every Need
- Best Buys in Recorders & Supplies
- Newest Public Address Systems, Paging and Intercom Equipment
- Amateur Receivers, Transmitters and Station Gear
- Citizen's Band 2-Way Radio
- Test and Laboratory Instruments
- TV Tubes, Antennas, Accessories
- Huge Listings of Parts, Tubes, Transistors, Tools, Books

BUY ON EASIEST TERMS
 only \$2 down on orders up to \$50;
 only \$5 down on orders up to \$200;
 only \$10 down over \$200.
 Up to 24 months to pay.

ALLIED exclusives:

MONEY-SAVING KNIGHT-KITS®—truly the very best in build-your-own electronic equipment—lowest in cost, easiest to assemble, best for performance. Select from a complete line of Stereo hi-fi kits, Hobbyist kits, Test Instrument and Amateur kits. KNIGHT-KITS are an exclusive ALLIED product.

KNIGHT® STEREO HI-FI—Comparable to the best in quality, styling and performance, yet priced far lower. Select super-value KNIGHT components or complete systems and save most. Also see the largest selections of famous-name hi-fi components and money-saving ALLIED-recommended complete high-fidelity music systems.

Exclusive Allied products save you more

You get every buying advantage at ALLIED: Lowest, money-saving prices, fastest shipment, expert personal help, easiest-pay terms, satisfaction guaranteed or your money back.

send coupon today for 444-page catalog

free

ALLIED RADIO

Satisfaction Guaranteed or Your Money Back

World's Largest Electronic Supply House



ALLIED RADIO, Dept. 109-C1
 100 N. Western Ave., Chicago 80, Ill.

Send FREE 1961 Allied Catalog No. 200

Name _____
PLEASE PRINT

Address _____


City _____ Zone _____ State _____

IF

If you're in a weak signal area where all channels are not sharp and clear, or in a big city where buildings interfere with reception ■ If your TV set is growing old and doesn't perform the way it used to ■ If you're operating 2, 3 or more TV sets from a single antenna, and reception is not quite up to par ■ If your FM radio is not bringing in all stations in your area

ADD

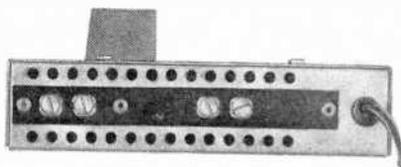NEW BLONDER-TONGUE TV/FM
POWER BOOSTER — MODEL BTA
\$18.95



TV PICTURES WILL SPARKLE
and FM will come through
crisp and static-free

■ offers more gain than ever before possible, at such a low price ■ improves TV and FM reception by boosting signal strength. (7 to 9 db, channels 2-13; 4-8 db, FM) ■ installs in seconds with only a screwdriver.

engineered and manufactured by

BLONDER-TONGUE, 9 Alling Street, Newark 2, N. J.

Canadian Div.: Benco Television Assoc. Ltd., Toronto, Ont.
Export: Morhan Export Corp., New York 13, N.Y.

Hi-Fi




Showcase

A WIDE RANGE of new hi-fi equipment—from complex and powerful stereo amplifiers to simple tape-head demagnetizers—continues to roll off production lines. Space prohibits us from covering every item, but some of the more noteworthy are discussed below. For additional information on any of the products mentioned, simply write to the appropriate manufacturers at the addresses given on page 24.

Quality is so high and price so low on Heath's AA-10 monophonic hi-fi amplifier that the old "two for stereo" argument need hardly be presented. The AA-10 boasts a power response within ± 1 db, 30 to 15,000 cycles, at 35 watts, yet sells for only \$49.95 in ready-to-build kit form. Among the AA-10's many outstanding features: EL-34/6CA7 output tubes for low distortion and long life; Heath's special "bass-bal" circuit for perfect balance between output tubes; two a.c. accessory sockets for powering associated preamps, tuners, and the like. . . . For the more conventional stereo setup, Allied Radio offers two Knight stereo amplifiers, one in kit form and one factory-wired. Selling at \$119.95, the kit incorporates a number of printed-circuit switches, boards, and resistor-capacitor assemblies, thus substantially reducing assembly time and minimizing any chance of error. This amplifier, 83YU934, delivers 35 watts per channel and incorporates several features that should appeal to tape fans. Among them: output recording jacks independent of volume and tone-control settings, a tape monitor switch permitting instant comparison between sound source and tape recording, separate and switchable equalization for $3\frac{3}{4}$ " and $7\frac{1}{2}$ " tapes. The fully wired stereo amplifier carries a conservative rating of 37.5 watts per channel from tubes and components operating well below their maximum ratings. Priced at \$169.50, the KN-775 includes provisions for headphones with a special front-panel jack that automatically silences speakers

Always say you saw it in—POPULAR ELECTRONICS


A MIRACLE IN SOUND

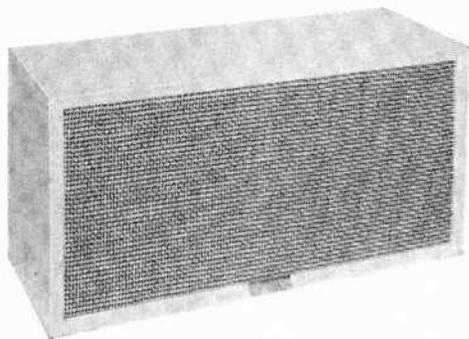

THE A.E.S. Gigolo

After two years of research and development a speaker system we can unconditionally guarantee to be the finest bookshelf unit ever built for home use that you have heard, REGARDLESS OF PRICE, or your money back.

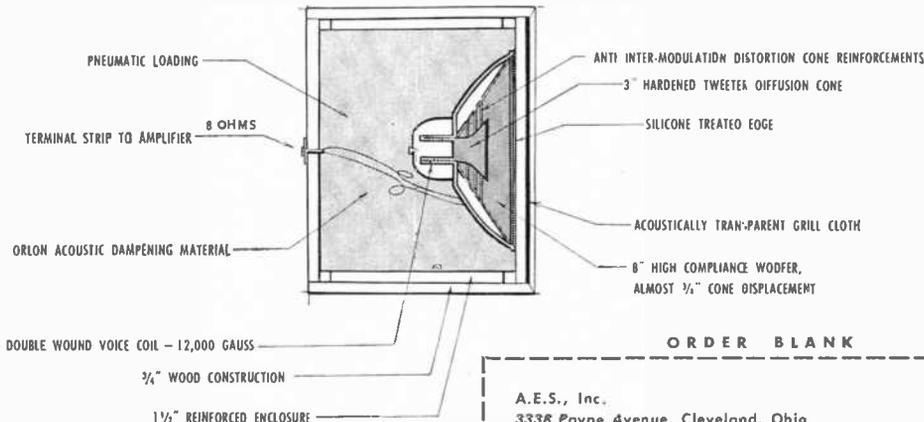Thousands of these gigolos are now in use all over the country. The acceptance has been unbelievable. Never before a sound so realistic to so many people in so many different homes! These are the facts that enable A.E.S. to make this bold offer.



SIZE: 24" wide, 12" high, 9 1/2" deep.
Response: 19-21,000 CPS

This unit will operate at maximum efficiency with amplifiers from 8 to 75 watts.

In limited quantity, and for a limited time only, \$15.00 complete, plus shipping.

Product Research & Development Company CONSUMER PRODUCT REPORT

A new product recently introduced is the subject of much controversy. It has been this controversy that prompted the Product Research & Development Company to make the following tests and report.

REPORT SUBJECT: A. E. S. GIGOLO

Description: Bookshelf type speaker system. Size, 21" wide, 12" high, and 9 1/2" deep. Which places the Gigolo among the few true bookshelf speakers. Cabinet construction is unusually heavy and well reinforced. Its weight is 25 lbs. Visual inspection showed care in assembly, with tightly sealed front and back. Cabinet was expertly sanded and ready for finishing. The grill material is of the plastic, acoustically transparent type, neutral in color and acceptable in style. Our first impression was that the manufacturer's efforts were directed to sound reproduction only, with little regard for furniture finish or style. But, some of the do-it-yourself finishing kits on the market will help rectify this situation. The wood product used throughout the cabinet is of a new type and differs from the usual plywood construction. The completely sealed enclosure is filled with spun orlon, which in our opinion will not only do a better job of dampening than fiberglass but also will eliminate the possibility of glass particles finding their way to the speaker voice coil. A real first—Good thinking A.E.S.—The reproducing unit is an eight inch high compliance silicon treated woofer, with an exceptionally long-throw double wound voice coil. This speaker is also equipped with a hardened high frequency reproducing cone.

Listening Test: This was the most enlightening part of our test. To exploit the manufacturer's claim of efficiency and power handling capacity, we went to the extreme of using a six transistor radio as a sound source. We found it had sufficient power to drive the A.E.S. Gigolo to a good listening level. What makes this simple experiment so remarkable is that the balance of this test was completed by using a Scott model 272-88 watt stereo amplifier.

The manufacturer's claim of frequency response from 19 cps. to 21 KC cannot be disputed from the standpoint of response only. But the test indicated that this was not a flat reproduction. However, we would like to point out that in group listening tests the Gigolo was repeatedly picked out from other bookshelf speakers ranging from \$49.00 to over \$200.00, to have the liveliest and a most realistic performance. These unusual reactions (considering price) may be somewhat explained by the fact that the Gigolo seemed to be the more efficient and to have the most mid-range presence of the units tested.

Summary: Without a doubt there are available speaker systems with specifications better than the A.E.S. Gigolo. But, at a selling price of fifteen dollars (\$15.00) this unit offered by A.E.S. Inc., 3338 Payne Avenue, Cleveland 14, Ohio, is, in our opinion, the best value ever offered to the audio market.

In conclusion it is the opinion of our marketing analyst that the manufacturer's cost of the Gigolo exceeds the present selling price of fifteen dollars (\$15.00). Look for a price increase in the very near future. PRD.

Reprinted with the permission of Product Research & Development Company, A.E.S., Inc., 3338 Payne Ave., Cleveland 14, Ohio.

ORDER BLANK

A.E.S., Inc.
3338 Payne Avenue, Cleveland, Ohio

Gentlemen please ship.....GIGOLOs.

I understand these units are guaranteed and if I am not satisfied I may return for a full refund of sales price, \$15.00 each.

Name.....

Address.....

City and State.....

Enclosed find check.....money order.....

QUICKLY CUT HOLES

in metal, plastics,
hard rubber...




GREENLEE CHASSIS PUNCHES

Make smooth, accurate openings in
1½ minutes or less . . . for sockets,
plugs, controls, meters, panel
lights, etc. Easy to use . . .
simply turn with wrench.

Many sizes and models.

Write for literature.

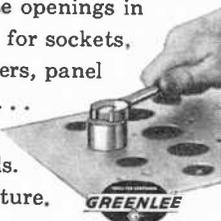

GREENLEE TOOL CO., 1915 Columbia Ave., Rockford Illinois

The Finest Amplifiers Use
ACROSOUND
ULTRA-LINEAR TRANSFORMERS
... the only output transformers
perfectly balanced for

- Lowest Leakage Inductance!
- Broadest Frequency Response!
- Full Rated Power from 20 CPS to 30 KC Double this from 30 CPS to 20 KC!

Now available at leading dealers:

T0-370 25 watt output transformer\$16.50
TP-535 Power transformer 11.75
Printed Circuit for medium power amplifier 7.50

ACRO Electronic Products Co.
410 SHURS LANE, PHILA. 28, PA.

Showcase

(Continued from page 22)

whenever headphones are plugged in.

If you're in the market for a "broadcast quality" four-speed transcription turntable and manual tone arm at a rock-bottom price, take a long look at *Lafayette Radio's* PK-449. A free-floating, shock-mounted induction motor drives a 3-lb, rim-weighted 12" aluminum turntable with wow and flutter held to a low, low 0.2%. A speed control permits a $\pm 7\%$ adjustment of each speed, and ball-bearing suspensions on the 12" tone arm result in extremely high vertical and lateral compliance. Price? Only \$49.50.

Completely assembled and wired, *Radio Shack's* Realistic 40/A stereo amplifier/preamplifier provides the heart of a stereo setup at a budget price. Priced at \$79.50, the 40/A delivers 20 watts per channel from any one of four different stereo inputs: magnetic phono, tuner, tape head, or auxiliary high level. . . . If you own a tape recorder, a tape-head demagnetizer is a "must." *Robins Industries'* HD-3, listing at \$5.95, is an American-made unit with a special plastic sleeve at the tip of the probe to prevent accidental scratches on tape heads. Although the HD-3 is a low-cost "little brother" to the company's HD-6, its specially shaped probe fits into just about any tape head, either mono or stereo, for ready demagnetization. . . . With a power output of 100 watts (monophonic), harmonic distortion of 0.5% and first-order intermodulation distortion of 0.1% (both at full power), *H. H. Scott's* new 100-watt stereo power amplifier approaches the last word in amplifiers. Output circuits on the 290 are meter-monitored, which means that output tube bias can be readily adjusted at any time to maintain perfect balance between channels. Functionally attractive, the 290 is designed for use with the company's 122, 130, or other high-quality stereo pre-amplifiers. Price: \$240.00.

Heath Co., Benton Harbor, Mich.
Allied Radio Corp. (Knight), 100 N. Western Ave., Chicago 80, Ill.
Lafayette Radio Corp., 165-08 Liberty Ave., Jamaica 33, N. Y.
Radio Shack Corp., 730 Commonwealth Ave., Boston 17, Mass.
Robins Industries Corp., Flushing 54, N. Y.
H. H. Scott, Inc., Dept. P, 111 Powdermill Road, Maynard, Mass.

Always say you saw it in—POPULAR ELECTRONICS



TD-124
Turntable \$99.75 net.
(Base only \$9.00)

A pleasure to buy...

Thorens has thought of many ways to make *buying* a Thorens TD-124 a distinct pleasure. A Thorens franchised dealer is a man of broad knowledge and ability, can command your immediate respect, That's why there aren't too many of them. The service *after* you buy is just as important as the initial sale. You get an almost unheard of full one year guarantee. All this in addition to "music as it's meant to be heard." See your Thorens dealer tomorrow... you're in for a real treat.

THORENS

FAMOUS SWISS HI-FI COMPONENTS • MUSIC BOXES
SPRING-POWERED SHAVERS • LIGHTERS

A Division of ELPA Marketing Industries, Inc. • New Hyde Park, New York

Guaranteed for one full year. Sold only through carefully selected franchised dealers.

March, 1961

a continuing pleasure to own!

No other turntable combines all these features. The Thorens TD-124 gives you...

- 4 speeds—plays any record you have or can buy.
- Easy-to-use illuminated strobe lets you set exact record speed for best musical reproduction while record is playing.

Extra heavy table (11½ lbs.) for extra smooth running... includes light-weight aluminum cueing table.


- Built-in level with easy-to-get-at fingertip control.
- Easy arm installation or change.
- Motor operates on 50/60 cps, any voltage from 100 to 250.



Tips and Techniques

XTAL PHONES ON TRANSISTOR SETS

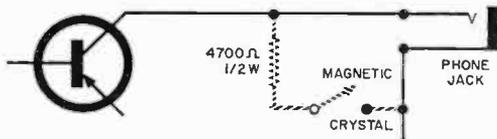Simple transistor radios and amplifiers for earphone use can be hooked up to operate with crystal as well as magnetic phones. Simply add a 4700-ohm, 1/2-watt resistor and a s.p.s.t. switch across the phone jack as shown in the schematic,



and either type of phone can be selected by flipping the switch. Open the switch when using magnetic phones, and close the switch when using crystal phones. The purpose of the resistor is to pass d.c. to the collector of the transistor

output stage when crystal phones are used. If crystal phones are accidentally plugged in with the switch in the magnetic phone position, no damage to the phones will result with most sets having low supply voltages.

—Art Trauffer

HANDY PARTS CONTAINERS

Empty fuse tins or pill boxes make fine containers for washers, nuts, lugs, and other small parts. Label each tin as to its contents—if you need a part in a hurry, you'll be able to find it quicker. Half a dozen of these tins will take up little space in your tool box and will keep the box ship-shape.

—Clyde C. Cook

REPLACING SOLDERING TIPS

Screw-type soldering iron tips that have become rusty can be easily removed for replacement. First, place a few drops of household ammonia around the threaded part of the tip after the iron is cool. Let the ammonia soak in a few moments and the tip will unscrew with little difficulty. Before installing the new tip, coat the

NOW YOU CAN SECURE A HIGH SALARIED • TOP PRESTIGE CAREER IN ELECTRONICS IN ONLY ONE YEAR!

ELECTRONICS is the fastest growing industry in America today, creating unlimited opportunities for high salaries, with rapid advancement in **INDUSTRY AND THE ARMED FORCES** for Bailey Trained electronic engineering technicians.

LARGE CORPORATIONS from coast to coast, and **BRANCHES OF THE ARMED FORCES** send recruiters to visit each graduating class at Bailey Tech, offering unusually high starting salaries.

BAILEY GRADUATES ARE BEING HIRED for such fascinating and interesting work as technical salesmen, research and development of guided missiles, electronic business machines and automatically controlled manufacturing plants, etc., also good **RATINGS IN THE ARMED FORCES**.

UP TO SEVEN TECHNICIANS are needed for every engineer... this, plus superior training is why Bailey Graduates are being paid more to start, and are advancing more rapidly than many men who have spent four years in training.

Resident training is easier and costs less than you may think! We provide housing and part-time jobs while in school, plus free nationwide employment service for graduates. If you want to quickly enter America's fastest growing and most exciting industry, write for free booklet... no obligation.

VETERAN APPROVED
BAILEY TECHNICAL SCHOOLS
1625 S. Grand • St. Louis 4, Mo.



This Minneapolis-Honeywell system controls hundreds of automatic manufacturing operations. Experience on live equipment is emphasized at Bailey and is another reason for the tremendous backlog of high pay positions waiting **BAILEY GRADUATES**.

MAIL TODAY

Please mail immediately this free booklet without obligation

Name _____

Address _____

City _____ State _____





PUZZLED

...no need to be

look to this sign of assurance!

The Distributor displaying this sign will solve your tuner problems at a profit to you.

He has available the New Standard Tuner Replacement Guide, including replacement parts listings. This is the only Guide of its kind in the world. Covers all Standard tuners produced through 1959. Includes replacements for many tuners not produced by Standard.

He handles our 48-hour Factory Guaranteed Repair Service and Trade-In Allowance on unrepairable Standard tuners.

See This Authorized Distributor Today




standard kollsman

INDUSTRIES INC. Formerly Standard Coil Products Co., Inc.
2085 N. HAWTHORNE AVENUE, MELROSE PARK, ILLINOIS

It's what you know about **Tips**

using instruments
that counts!

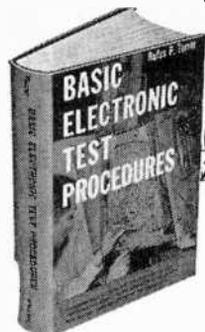

A complete, easy guide to **MODERN TEST PROCEDURES**

Almost anyone can repair TV's, radios and other electronic equipment AFTER the trouble has been found. The trick is to know how to locate troubles in the first place—and that means knowing how to use instruments fast and accurately. Actually, it's amazing what you can do with only a few instruments—providing you know how to use different kinds for the same job; how to select the right ones; where to use them; how to connect them into circuits; how to set controls; how to read them; and how to follow professional test procedures every step of the way. And that's exactly what this new 316-page **BASIC ELECTRONIC TEST PROCEDURES** manual with its more than 190 how-to-do-it pictures, operational procedure sketches and pattern designs teaches you.

HELPS YOU TROUBLESHOOT TV and RADIO SETS in lots less time!

BASIC ELECTRONIC TEST PROCEDURES by Rufus Turner helps you learn to troubleshoot any circuit, equipment or component fast and accurately. Covers different methods for doing specific jobs. For instance, you learn to check distortion by the 'scope, reflection filter, harmonic-distortion meter, wave analyzer or audio oscillator methods. You learn to make resistance measurements with a current-meter, a volt-ammeter, a volt-meter, an ohmmeter, or via the bridge method . . . and so on.

Subjects include current checks; power, capacitance, resistance, AF, RF, phase, distortion, and modulation measurements; tube and semiconductor testing; audio amplifier tests; sensitivity, RF gain, fidelity, AVC voltage, operating voltage checks, etc.; visual alignment techniques—even transmitter and industrial electronic test procedures.

Put your oscilloscope to work!

Simplified explanations of modern oscilloscope techniques show how to use your 'scope as a volt-meter, current meter, variable frequency oscillator, etc., or for making RF, phase or AM measurements; for distortion and deflection checking; square wave testing; visual AM and FM alignment, and for many other jobs. Every detail is explained—from making connections, to adjusting controls and analyzing patterns.

STILL ANOTHER BIG FEATURE is the book's usefulness in acquainting you with industrial electronic test techniques—including testing non-electronic phenomena such as strain, pressure, etc. Price \$8.00.

PRACTICE 10 DAYS . . . FREE!

Dept. PE-31, Technical Division
HOLT, RINEHART and WINSTON, INC.
383 Madison Ave., New York 17, New York

Send **BASIC ELECTRONIC TEST PROCEDURES** for 10-day FREE EXAMINATION. If I decide to keep book, I will then send you \$8.00 plus postage in full payment. If not, I will return book postpaid and owe you nothing. (SAVE! Send \$8.00 with your order and we pay the postage. Same 10-day guarantee with your money promptly refunded if you're not more than satisfied with book.)

NAME

ADDRESS

CITY, ZONE, STATE

OUTSIDE U. S. A.—Cash with order only. Price \$8.50. Money back if book is returned in 10 days.


(Continued from page 26)

threaded parts with a small quantity of powdered graphite or lead pencil "dust." The carbon dust will prevent the tip from oxidizing, thus making for easy replacement the next time.

—Edward Daniels

POWER TOOL SAFETY INTERLOCK

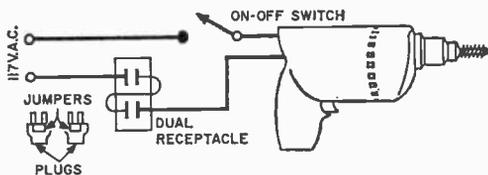You can prevent children from turning on your power tools with this simple safety interlock. Wire the interlock by connecting the power cord from the tool




to a dual a.c. receptacle as shown in the schematic. To operate the interlock, make a couple of jumpers by connecting a wire across the terminals of two long-handled male plugs; when both plugs are inserted in the receptacle, the power tool is turned on. Hide the plugs when the tool is not in use for safety's sake. The on-off switch shown here can be left out of the circuit if your power tool already has a built-in switch.

—Jamie Ellett

CROCHETING NEEDLE "TOOL"

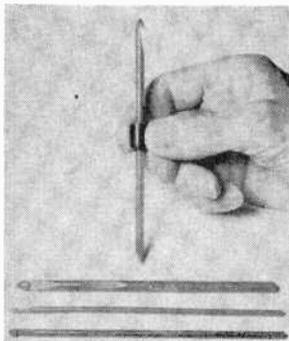Plastic crocheting needles make convenient dial cord stringing aids and alignment tools.



Use the hooked end of a needle to manipulate dial cords in tight corners; file the other end to fit tuning slugs and screws on i.f. transformers. A small "knob" can be formed in

the center of the "tool" by winding a few turns of plastic tape on it; the knob will provide more leverage when you're turn-

Always say you saw it in—POPULAR ELECTRONICS

FREE!

LAFAYETTE'S 1961 CATALOG 324 GIANT SIZED PAGES

The Complete Catalog Featuring
"The Best Buys In The Business"

- Stereophonic HI-FI Equipment
- Public Address Systems
- Tape Recorders
- Radio and TV Tubes and Parts
- Citizen Band Equipment
- Amateur Equipment
- Industrial Supplies

Send for Lafayette's FREE Catalog—the most complete, up-to-the-minute electronic supply catalog crammed full of everything in electronics at our customary down-to-earth money-saving prices.

CONTAINS HUNDREDS OF EXCLUSIVE LAFAYETTE ITEMS NOT AVAILABLE IN ANY OTHER CATALOG OR FROM ANY OTHER SOURCE — SEND FOR YOUR COPY NOW!

A "must" for the economy-minded hi-fi enthusiast, experimenter, hobbyist, engineer, technician, student, serviceman and dealer.



Our 40th Year:

EASY PAY PLAN—the simplest, and quickest way to get what you want when you want it. As little as \$2 down . . . up to 24 months to pay.

<p>NEW!</p> <p>29.95</p> <p>2.00 Down</p>  <p>RK-125 Transistorized Portable Tape Recorder with Built-In Speaker</p>	<p>19.95</p>  <p>TE-15 Tube Checker</p>	<p>93.50</p> <p>5.00 Down</p>  <p>HE-20 Deluxe Citizens Band Transceiver</p>
<p>13.50</p>  <p>RW-60 20,000 Ohms Per Volt Multitester</p>	<p>KT-200, KIT</p> <p>64.50</p> <p>5.00 Down</p>  <p>KT-200, KIT</p> <p>64.50</p> <p>5.00 Down</p> <p>Communications Receiver</p>	<p>HE-10, Wired</p> <p>79.95</p> <p>5.00 Down</p>  <p>HE-10, Wired</p> <p>79.95</p> <p>5.00 Down</p> <p>NEW!</p> <p>HE-23</p> <p>Two for 36.50</p> <p>5.00 Down</p> <p>'Walkie-Talkie'</p> <p>9-Transistor Portable Citizens Band</p>

Mail the coupon today for your FREE copy of Lafayette Radio's 1961 Catalog. 

LAFAYETTE RADIO

165-08 LIBERTY AVENUE, JAMAICA 33, N. Y.

OTHER LOCATIONS

NEW YORK 13, N.Y.	BRONX 58, N.Y.	NEWARK 2, N.J.
PLAINFIELD, N.J.	PARAMUS, N.J.	BOSTON 10, MASS

FREE!

Lafayette Radio
Dept. IC-1, P.O. Box 190
Jamaica 31, N. Y.

Send me the FREE Lafayette 324 page 1961 catalog 610

Name _____

Address _____

City _____ Zone _____ State _____



THE VERY FINEST CITIZENS' RADIO...



Farming,
delivery or
fleet operation



Car-to-office
or home
communication



Boat-to-boat or
ship-to-shore
communication

FREE
Color Brochure
WRITE TODAY

Messenger from

- Anyone can operate—license issued by FCC on request!
- 23 channel Class "D" Band coverage—choose 1 of 5 channels by flip of switch!

Designed for 10 watts—limited to 5 for Citizens' Radio. Excellent receiver sensitivity and selectivity. Built-in Squelch, Automatic Volume Control, and Automatic Noise Limiter. With tubes, microphone, and crystals for 1 channel.

Available from authorized Johnson Distributors—installation and service at all General Electric Communications Service Stations.



E. F. JOHNSON CO

126 Second Ave. S.W. • Waseca, Minn.



• Please rush me your full color brochure describing the Viking "Messenger" Citizens' Transceiver.

NAME _____
ADDRESS _____
CITY _____ STATE _____

KUHN

"LEADERS IN SPECIALIZED
RECEIVING EQUIPMENT"

MOBILE FIXED CONVERTERS

- POLICE
- FIRE
- COMMERCIAL
- CITIZEN'S BAND

331B Crystal controlled. Requires no high voltage supply. For transistor car radios. Can be connected in moments for emergency use. 2-54 MC.

Complete \$24.95
Other models for 108-162 MC available.



315A A practical converter for emergency use with home or auto sets. Easily installed. Tunable over 12 MC in 26-54 MC or 30 MC in 108-174 MC band.

COMPLETE \$13.95

315AC Crystal controlled up to 54 MC. COMPLETE \$18.95
Crystal controlled up to 165 MC. COMPLETE \$22.95

315AD Crystal controlled. For use with transistor car radios. 2-54 MC. COMPLETE \$17.95
316A VARIABLE CONVERTER. Front panel tuning permits rapid change between separated signals over 10 MC range in 26-54 MC or 108-174 MC band. COMPLETE \$19.95

CONVERTERS
ALL EQUIPPED
WITH SELF
CONTAINED
SWITCHING
AND LEADS
FOR RAPID
CHANGE-OVER

ORDER TODAY or
SEND FOR FREE
CATALOG... con-
taining complete
information on a
full line of
CONVERTERS AND
RECEIVERS FOR
EVERY APPLICATION



326B SUPER CON-
VERTER. Crystal con-
trolled. For transistor
car radios. Ultra high
gain. Self contained
ANL. 2-54 MC.

Complete \$44.95

20 GLENWOOD
CINCINNATI 17,
OHIO



Tips


(Continued from page 28)

ing tight adjustment screws. Since crocheting needles come in several hook sizes and diameters, it's a good idea to buy a few different ones—they cost only a few cents each at variety stores.

—Art Trauffer

SOLDERING IRON CLEANER

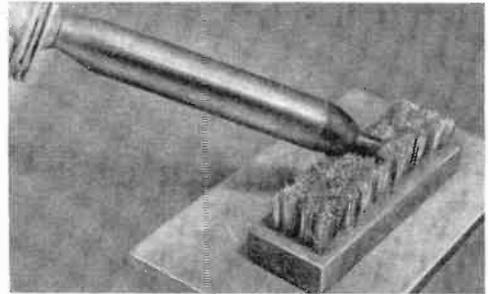A metal-bristled suede brush makes a handy soldering iron cleaner. Fasten the brush, bristles up, to your workbench or




to a piece of plywood which can be screwed or nailed to an adjacent wall. To use the brush, simply wipe the iron's tip on the bristles; sludge and dirt will come off, and the tip will do a better soldering job.

—Glen F. Stillwell

HEAVY-DUTY POWER CORD

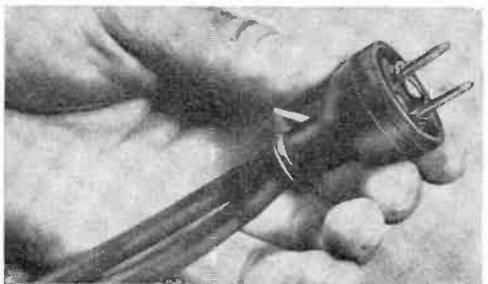When the power cord on a high-drain appliance wears out, you can use a length of ordinary two-wire rubber "zip-cord," with both wires in parallel, to replace each leg of the appliance's cord. The re-



sulting doubled-up power cord will safely carry up to 1200 watts. However, be sure not to overload your power outlets.

—Robert Micals

Always say you saw it in—POPULAR ELECTRONICS

For serious-minded men desiring higher income and status-

CREI has developed a program of home study that is comparable in technological content to advanced residence courses in electronics. The program was developed hand-in-hand with leading companies and Government agencies contributing to the Nation's efforts in electronics, communications, missiles, and space exploration.

This CREI program in Electronics Engineering Technology may be completed in 2 to 4 years, depending on how much of your spare time you can devote to study. The courses are presented in easy-to-understand form. Our instructors will give you personal attention and assist you when you need help.

To qualify CREI graduates for advancement to key technical positions, CREI offers a complete program in electronics, including—

Automation • Instrumentation • Industrial Electronics
Aeronautical Electronics • Guided Missiles • Radar
Servo-mechanisms • Computers • Astronautics • Telemetering • Communications • Electronics Manufacturing • Field Engineering

A COLLEGE-LEVEL EXTENSION PROGRAM IN ELECTRONICS

There is a drastic need in the electronics industry for well-educated engineers and technical personnel. Although the great majority of students find ample opportunity for advancement with their present companies, CREI maintains a Placement Bureau to assist graduates and advanced students in finding more desirable positions. For many years, the demand for CREI graduates and advanced students has far exceeded the supply.

A few of the private companies and government agencies whose officials approve CREI for their own personnel:

U. S. Navy (5,240 enrolled in extension program)	Florida Power & Light
Army, Air Force, Marine Corps, Coast Guard	Pan American Airways
Columbia Broadcasting System	United Airlines
National Broadcasting Company	The Martin Company
Federal Electric Corporation	All America Cable & Radio
	Voice of America
	... and many others

CREI's Extension Division offers you a college-level home study program in electronics comparable in technological content to advanced residence courses.

QUALIFICATIONS FOR CREI. You qualify if you have a high school diploma or equivalent, and if you have had basic electronic training and practical experience in electronics. Available to Veterans.

Mail this coupon . . . today!

CAPITOL RADIO ENGINEERING INSTITUTE

ECPD Accredited Technical Institute Curricula • Founded 1927
Dept. 1203-H, 3224 16th St., N.W., Washington 10, D.C.

Please send me your course outline and FREE 44-Page Book "Insurance for Your Future in the New World of Electronics" . . . describing opportunities and CREI home study courses in Advanced Electronic Engineering Technology.

- Check field of greatest interest Radar, Servo and Computer Engineering Technology
 Electronic Engineering Technology
 Communications Engineering Technology
 Television Engineering Technology
 Aeronautical Electronic Engineering Technology
 Automation and Industrial Electronics Engineering Technology

Name _____ Age _____

Street _____

City _____ Zone _____ State _____

Check: Home Study Residence School Korean Veteran



To obtain fast, immediate service and to avoid delay, it is necessary that the following information be filled in:

Employed by _____

Type of Present Work _____

Education: _____

Years of High School _____


Other _____

Electronics Experience _____

NEW products

SOLDERING IRON

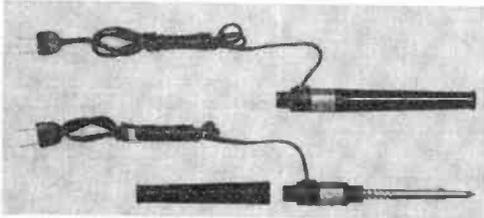A new 30-watt soldering iron available from L. I. Electro-Labs, Inc., subsidiary of Progressive "Edu-Kits" Inc. (1186



Broadway, Hewlett, N. Y.), has a removable handle that covers the tip when it's not in use. After a soldering job, you can switch the handle around and place the iron right in your tool box (or even

your shirt pocket) without waiting for the tip to cool. The Model A1000 comes complete with carrying case for \$2.75.

UNITIZED SPEAKER



The MISCO unitized speaker is designed for public address, test, or intercom use—indoors or out. A heavy steel case with a perforated and louvered front panel plus a plastic-impregnated speaker cone insures maximum reliability under adverse conditions. Installation is simple—the keyhole slot on the rear of the case will fit on a nail or hook on a wall. Available in 3.2-, 8-, and 44-ohm impedances, the speaker uses an Alnico V magnet and an aluminum voice coil. (Minneapolis Speaker Co., 3806 Grand Ave., Minneapolis 9, Minn.) (Continued on page 36)

your shirt pocket) without waiting for the tip to cool. The Model A1000 comes complete with carrying case for \$2.75.

35 C

TRU-VAC 1-YEAR GUARANTEED RADIO and TV TUBES

Factory Used or Factory Second Tubes! TRU-VAC will replace FREE any tube that becomes defective in use within 1 year from date of purchase! All tubes individually boxed, code dated & branded "TRU-VAC." Partial Listing Only—Thousands More Tubes in Stock!

SPECIALI		6SN7GT 30¢		6V4GT 30¢	
024	4858	6AH6	6BC5	6CDE6	6J7
1A7GT	4B27	6AK5	6BC8	6CF6	6K6GT
1B3GT	4CB6	6AL5	6BD6	6CG7	6K7
1H5GT	5AH8	6AM8	6BE6	6CG8	6N7
1R5	5AN8	6AN8	6BF5	6CH8	6Q7
1S5	5AT8	6AQ5	6BG6G	6CL6	6S4
1T4	5AV8	6AQ6	6BH6	6CM6	6S8GT
1U4	5AZ4	6AQ7	6BJ6	6CW7	6SA7
1U5	5CG8	6AR5	6BK5	6CN7	6SD7GT
1V2	5R4	6AS5	6BK7	6CQ8	6SF5
1X2	5T8	6AT6	6BL7GT	6CR6	6SG7
2AF4	5U4	6AU4GT	6BN6	6CS7	6SH7
2BN4	5U8	6AU5GT	6BQ6GT	6CU5	6SJ7
2CY5	5V4G	6AU6	6BQ7	6CU6	6SK7
3AL5	5V6GT	6AUB	6BR8	6D6	6SL7
3BC5	5X8	6AV5GT	6B58	6DE6	6SQ7
3BN6	5Y3	6AV6	6BY5G	6DGE6T	6SR7
3BZ6	6AB4	6AW8	6BZ6	6DQ6	6T4
3CB6	6AC7	6AX4GT	6BZ7	6F6	6T8
3S4	6AF4	6AX5GT	6C4	6H6	6U5
3V4	6AG5	6BB	6CAB	6J5	6U8
4BQ7A	6AH4GT	6BA6	6CB6	6J6	6V6GT

LOOK! 1000 USED TV'S
Costly, famous make console models with little or no tube replacement! Require only minor adjustments. Perfect for resale, or as your own second set! 16", 17" and 19" screens... none smaller! Sets shipped FOB, Harrison, N. J.

\$1695
(As Is)

BRAND NEW 1-YEAR GUARANTEED TV PICTURE TUBES
Below Listed prices do not include dtd. Add Additional \$3.00 Deposit immediately when dtd is returned prepaid. Aluminized tubes—\$4.00 extra. Picture tubes shipped only to continental USA and Canada—All tubes F.O.B. Harrison, N. J.

10B4	7.99	17CP4	16.99	21AMP4	17.99	21KP4	18.39
16CP4	16.09	17TP4	16.99	21AVP4	18.79	21YP4	18.39
16RP4	11.99	20CP4	15.89	21AWP4	17.49	21WP4	17.49
17AP4	15.49	20HP4	17.39	21BP4	17.29	21YP4	18.39
17BP4	13.49	21ALP4	18.79	21FP4	18.39	21CP4	27.79

ATTENTION QUANTITY USERS! Big Discounts Are Yours... Call or Write For Our 1000 Tube "Private Label" Special!
Money cheerfully refunded within five (5) days, if not satisfied!

SHIPPING INSTRUCTIONS: TRU-VAC PAYS YOUR POSTAGE on orders of \$5 or more in USA and Territories. Send approximate postage on Canadian and foreign orders. Any order less than \$5 requires 2% handling charge. Send 25¢ on C.O.D.'s.

ANY TUBE NOT LISTED ALSO AVAILABLE AT 35¢ EACH!

TRU-VAC

Harrison Avenue • Box 107 • Harrison, N. J. HUMBOLDT 4-977D

Sensational Offer!
"Self Service"
TUBE CHECKERS
\$37.95 FOB Our Warehouse

Let your customers test their own tubes! These reliable, reconditoned 22-socket tube checkers will return your investment in one week or less with little or no effort on your part! Hand some, field-tested console models, field-PLATED WITH KEV FOR LIGHTED HEAD!

Learn RADIO, TELEVISION AND ELECTRONICS

by Practicing at Home in Your Spare Time

At No Extra Cost you get specially developed Electronic Training Kits for practical experience. Shop and laboratory practice at home make learning easier, interesting, faster. You do not need a high school diploma or previous experience.

Increasing Demand for Trained Men

This is the Electronics age. Men with Electronic know-how are in demand. They enjoy high pay and growing opportunities for advancement. Satellites, Radar, Automation in Industry, Missiles, Rockets, Planes, Stereo, TV, Radio, Two Way Communications for transportation are a few of the fantastic developments in the fast growing Electronics industry. If you are not completely satisfied with your work; if you are doubtful about your future, investigate Electronics.



High Pay, Prestige, Bright Future

What branch of Electronics interests you? Thousands of successful NRI graduates prove that NRI's learn-by-practice method is the way to success. You start in your chosen career way ahead of the man who only learns from books. You do not need to give up your job. You do not need to go away to school. You learn at home, get practical knowledge from training kits NRI provides.

Train With the Leader



NRI is the world's oldest and largest home study Electronics school. You benefit from the experience NRI has gained from training men for 45 years. NRI offers you proven courses of home study in Electronics; Principles, Practices and Maintenance—Radio Television Communications—Radio Television Servicing.

Start Soon, Earn More

Soon after enrolling NRI shows you how to apply your knowledge to earn extra money doing Electronic repairs or servicing Radio and Television sets for friends and neighbors. Take the first step toward success now. Find out what NRI offers you. Mail the postage-free card. No obligation. Cost of NRI training is low.



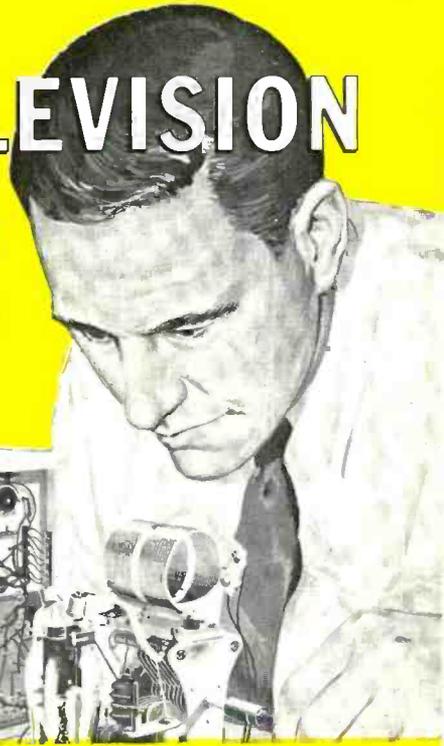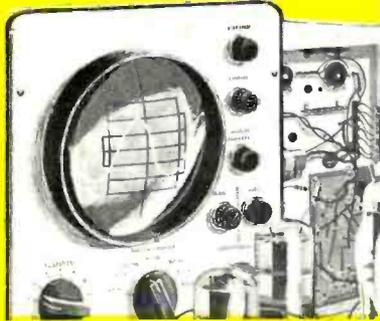Monthly payment plan available. NATIONAL RADIO INSTITUTE, Washington 16, D.C.



NRI Has Trained Thousands for Success



"I get over twice the salary I made before enrolling. NRI training gave me a thorough understanding." H. ATKINSON, Austin, Tex.

"Now in charge of sound effects for CBC. NRI opened doors to greater opportunity for me." F. TUDOR, Toronto, Ontario.

"Averaged \$150 a month spare time before I graduated. Now have my own full time business." F. W. COX, Hollywood, Cal.

NEW COURSE IN ELECTRONICS **TURN PAGE**

Cut Out and Mail—No Stamp Needed

64-PAGE CATALOG FREE

No Salesman will call. (Please PRINT) Dept. 100-4

Name _____ Age _____

Address _____

City _____ Zone _____ State _____

OLDEST & LARGEST HOME STUDY RADIO-TV SCHOOL
National Radio Institute
WASHINGTON 16, D. C.

ACCREDITED MEMBER NATIONAL HOME STUDY COUNCIL

The amazing field of electronics

How to train at home for its

National Radio Institute
WASHINGTON, D.C.



JOB COUNSELORS ADVISE LEARN ELECTRONICS



NEW Home Study Course in **ELECTRONICS** Principles-Practices-Maintenance **NOW READY**

This is the Electronic Age. Electronic equipment is already being used to count and control flow of liquids, solids, gases. Electronics is employed to search for oil, make surveys, control traffic, machine complex parts and in atomic installations. Military uses of Electronics are great and expanding rapidly. In business, Automation with Electronics plays an important part, prepares payrolls, calculates engineering formulas.

Learn More to Earn More

Now, to meet the growing demand for trained Electronic Technicians NRI has developed a comprehensive, complete course in Electronics Principles, Practices, Maintenance. This training stresses fundamentals. It is a course specially prepared for beginners and for Technicians. You get both theory and practical experience in an interesting, exciting way.

Ten Special Training Kits Give Practical Experience

You get practical experience with Thyatron Tube circuits, Multivibrators, build a D'Arsonval type Vacuum Tube Voltmeter (Kit 2); work and experiment with pentode tubes, selenium resistors, oscillators, transistors, magnetic amplifiers; and get practical experience in telemetry circuits as used in earth satellites, digital and analog computers (Kit 9).

SPECIAL TRAINING KITS NO EXTRA COST

NRI Oldest, Largest School

SEE OTHER SIDE

Wishing for success won't bring success. You must act. Get FREE 64-page Catalog from America's oldest and largest home study Electronic-Radio-Television school. It gives facts, opportunities in Industrial and Military Electronics careers, also shows what you learn, tells about NRI's other courses in Radio Television Servicing and Radio Television Communications. Monthly payments plan. Mail Postage Free Card for 64-page Catalog. NATIONAL RADIO INSTITUTE, Washington 16, D.C.

FIRST CLASS

Permit No. 20-R

(Sec. 34.9, P. L. & R.)

Washington, D.C.

BUSINESS REPLY CARD

No Postage Stamp Necessary if Mailed in the United States

POSTAGE WILL BE PAID BY

National Radio Institute

3939 Wisconsin Avenue

Washington 16, D.C.



POSTAGE FREE CARD
MAIL NOW

A DO-IT-YOURSELF GOLDMINE!

40 ALL-NEW PROJECTS! 20 DATA CHARTS & TABLES!

ALL IN THE 1961 ELECTRONIC EXPERIMENTER'S HANDBOOK

If you're an electronics hobbyist, you'll welcome the 1961 ELECTRONIC EXPERIMENTER'S HANDBOOK. It's packed with over 40 all-new projects you can build yourself, plus more than 20 information-packed charts and tables on circuits, resistors, transformers, capacitors, ham and citizens band radio, sound levels, and much more!



THESE ARE JUST A FEW OF THE EXCITING PROJECTS YOU CAN BUILD FROM THE COMPLETE DIAGRAMS AND EASY-TO-FOLLOW DRAWINGS:

PROJECTS FOR YOUR HI-FI & AUDIO SYSTEMS

- Speaker Cabinet Designs
- Unusual Amplifier
- Power Megaphone
- Intercom
- One-Tube FM Tuner
- Speaker Crossover

PROJECTS FOR THE HAM AND SWL

- Acoustic Phone Patch
- One Transistor Ham Transmitter
- Beam Antenna
- Mobile Short Wave Converter
- Practice Oscillator

PROJECTS FOR YOUR SHOP

- Direct Reading Frequency Meter
- Grid-Dip Meter
- Dual-Meter Transistor Tester
- Citizens Radio Tune-up Probe
- Field Strength Meter
- R.F. Power Meter

PROJECTS FOR FUN

- Electronic Music Box
- Transistorized Driver Alarm
- Auto Safety Flasher
- Transistorized Pocket Fence Controller
- Transistorized Pocket Radio

**1961 ELECTRONIC
EXPERIMENTER'S
HANDBOOK**



The new 1961 ELECTRONIC EXPERIMENTER'S HANDBOOK is now on sale at your favorite newsstand or electronic parts store. Pick up your copy today—or order now by handy coupon. Only \$1.00.

Ziff-Davis Publishing Company
1 Park Avenue
New York 16, N. Y.

Please send me a copy of the 1961 ELECTRONIC EXPERIMENTER'S HANDBOOK. I enclose \$1.00 plus 10¢ to cover mailing and handling charges. (Canada and Foreign \$1.25 plus 10¢ postage.)

NAME _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____

EF-2101

2017

FREE **GIANT 1961 204 PAGE CATALOG**

B-A 1961
ANNUAL CATALOG #17

SAVE UP TO 50% ON B-A SELECTED KITS

HI-FI AND STEREO SYSTEMS & COMPONENTS

TOP VALUES IN POWER AND HAND TOOLS

30 PAGES OF BARGAINS NOT IN ANY OTHER CATALOG

RADIO TV ELECTRONICS

BURSTEIN-APPLEBEE CO.

Dept. PE, 1012 McGee St., Kansas City 6, Mo.

Send Free 1961 B-A Catalog No. 611

Name _____

Address _____

City _____ State _____

SEND FOR IT TODAY

TV PICTURE TUBES AT LOWEST PRICES

NEW TUBES 14RP4-\$16.95 14W/ZP4-\$16.95 17BJP4-\$19.95
17BZP4-\$19.95 21CEP4-\$22.95 21DEP4-\$22.95
ALL ALUMINIZED: 24AEP4-\$26.95 24AHP4-\$26.95

10BP4 \$ 7.95	16WP4 \$12.00	17TP4 \$17.00	21EP4 \$13.50
12LP4 8.50	16PT4 9.95	19AP4 16.00	21FP4 14.50
14B/CP4 9.95	17AVP4 12.50	20CP4 13.50	21WP4 14.00
16DP4 12.00	17BP4 9.95	20HP4 14.50	21YP4 14.50
16EP4 12.75	17CP4 17.00	21AP4 22.10	21ZP4 13.50
16GP4 14.50	17GP4 17.60	21ALP4 15.75	24CP4 23.50
16KP4 9.95	17HP4 12.50	21AMP4 15.75	24DP4 24.50
16LP4 10.95	17LP4 11.50	21ATP4 15.75	27EP4 39.95
16RP4 9.95	17QP4 9.95	21AUP4 15.75	27RP4 39.95

1 YEAR WARRANTY

Aluminized tubes \$3.00 for 21"; \$5.00 for 24" and 27" additional. Prices include the return of an acceptable similar tube under vacuum. These tubes are manufactured from reprocessed used glass bulbs. All materials including the electron gun are brand new.

ALL PRICES FOB CHICAGO, ILLINOIS. Deposit required. When old tube is not returned, refundable at time of return. 25¢ deposit required on COD shipments. Old tubes must be returned prepaid. Tubes shipped Rail Express. We ship to the Continental U. S. and Canada, only.

WRITE FOR COMPLETE LIST


—PICTURE TUBE OUTLET—
2922 MILWAUKEE AVE., CHICAGO 18, ILLINOIS
Dickens 2-2048

products

(Continued from page 32)


ALL-WAVE RECEIVER

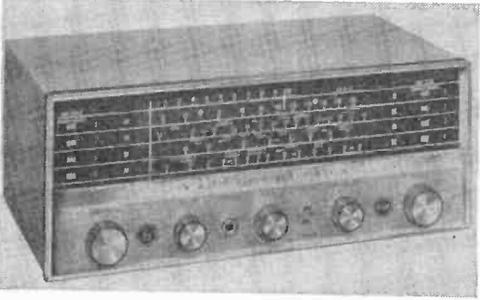A new Hallicrafters receiver covering the range from 550 kc. to 30 mc. offers compact, slim-line styling; an adjustable,



front-panel-controlled BFO; and provisions for up to three antennas. Essentially an improved version of the older S-38E, the S-120 comes with a built-in loopstick antenna for the standard broadcast band and a collapsible whip antenna for short-wave reception. Employing a sensitive, four-tube superhet circuit with a selenium rectifier, the S-120 also has its own built-in speaker. Price, \$69.95. (Hallicrafters, 4401 W. Fifth Ave., Chicago 24, Ill.)

RECTIFIER CHECKER

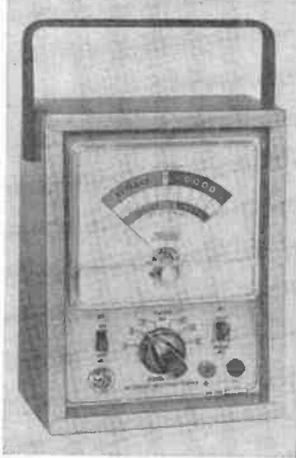

The Mercury Model 600 in-circuit tester will check any power rectifier, whether selenium, germanium, silicon, or copper oxide. You simply clip the instrument's leads across the rectifier (either in or out of the circuit), press the test

switch, and get an instant indication of the rectifier's condition. Having a large (4½") meter equipped with easy-to-read, three-color scales, the 600 will check any rectifier for quality, shorts, fading, opens,

Always say you saw it in—POPULAR ELECTRONICS



the giggles

Put one little girl together with something that tickles her funny bone—and out comes the purest, merriest of sounds.

We don't propose there's anything quite as nice. But we can tell you about another kind of purity of sound that's worth discovering. Make your next tape recording on Audiotape. Then listen. Audiotape . . . it's wonderful!

Audiotape has less distortion, less background noise, more clarity, more range than other tapes, because it's made to professional standards. Let it be your silent (but knowing) partner in capturing fresh, clear, memorable sounds. (Like Sissy's giggles, for instance.)

Remember: if it's worth recording, it's worth Audiotape. There are eight types . . . one exactly suited to the next recording you make.



audiotape
TRADE MARK

"it speaks for itself"

AUDIO DEVICES INC., 444 Madison Ave., N.Y. 22, N.Y.
Hollywood: 840 N. Fairfax Ave. Chicago: 5428 N. Milwaukee Ave.


products

(Continued from page 36)

arcng, and life expectancy. Price: \$27.50. (Mercury Electronics Corp., 77 Searing Ave., Mineola, N. Y.)

AUXILIARY VISE JAWS

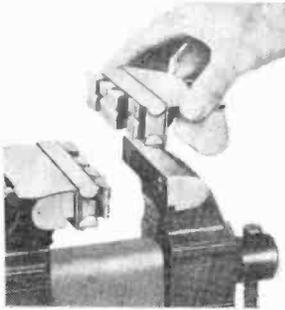Machine vises can be converted instantly to universal vises by "hooking on" a set



of adjustable jaws available from Mid-American Import Co., Inc., 1919 Champa St., Denver 2, Colo. Steel fingers in each jaw adjust to hold any shaped object firmly. The "Uni-Grips,"

as they are called, will hold a steel ball, a triangular wedge, pipe, or just about anything else you can think of.

HAM TRANSMITTER KIT

A successor to the Heathkit DX-40, the new DX-60 amateur transmitter kit makes an excellent rig for the Novice as



well as the General Class amateur. Power input is 90 watts peak, carrier-controlled phone or c.w., on amateur bands from 80 through 10 meters, but the unit can be run at reduced power for Novice operation. Other features include a built-in low-pass filter for harmonic suppression, a neutralized final for high stability, and grid-block keying. Price: \$82.95. (Heath Co., Benton Harbor, Mich.)

-30-

Study Programs in...

APPLIED SCIENCE AND ENGINEERING

Associate in Applied Science degrees — 2 years

- Electronics Communications Technology
- Electrical Power Technology
- Computer Technology
- Air Conditioning Technology
- Industrial Technology
- Metallurgical Technology

Bachelor of Science degrees — 4 years

- Electrical Engineering
 - Communications option
 - Electrical power option
- Mechanical Engineering

At MSOE, new classes begin quarterly. Pre-technology program, scholarships, financial aid, and placement service available.



New! FREE "Your Career" booklet. Send coupon today.

MILWAUKEE SCHOOL OF ENGINEERING
1025 N. MILWAUKEE STREET • MILWAUKEE 1, WIS.



MILWAUKEE SCHOOL OF ENGINEERING
Dept. PE-361, 1025 N. Milwaukee St., Milwaukee 1, Wis.


Name..... Age.....

Address.....

City..... State.....

Course Interest.....

(Please Print!)

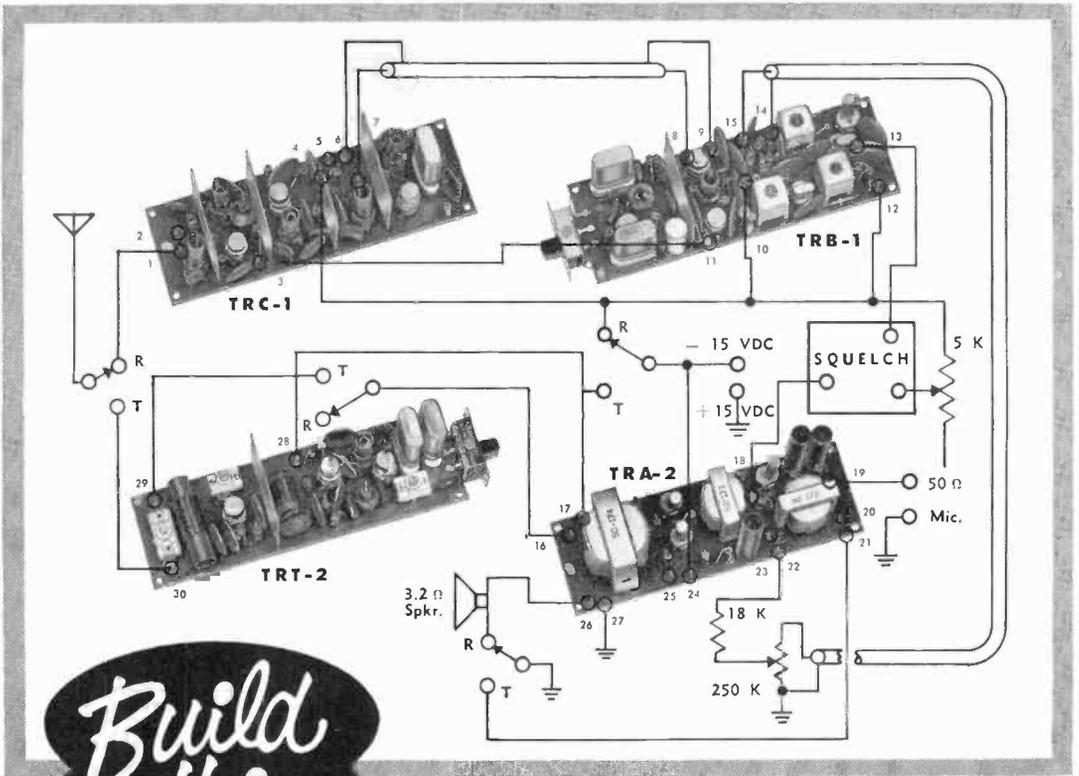

Build this

ALL TRANSISTOR TRANSCEIVER

Now you can build your own All Transistor, Crystal Controlled, Portable Transceiver for Citizens band or Amateur communications. International sub-assemblies, prewired and tested are "quickly" interwired and ready for operation. Fifteen transistors for transmitting and receiving. Dual conversion superheterodyne receiver. Noise limiter and squelch. International precision crystals and highest quality components throughout. Power requirements: 15 volts dc @ 60 ma average. Positive ground.

TRC-1 CONVERTER

Crystal controlled, 3 transistors for 10 meters or Citizens band. RF amplifier, mixer/oscillator. Double tuned front end. IF output 6 mc. Others on special order. Power: 15 volts dc @ 5 ma. Wired, tested with Crystal. Cat. No. 300-132 \$17.95
Special IF (Cat. No. 300-140) \$22.50

TRB-1 MIXER IF UNIT

Six transistors, 2 diodes. 6 mc RF amplifier/mixer. Crystal controlled

local oscillator. 455 kc IF. Noise limiter/squelch. Input 6 mc. Specify frequency. Wired, tested with crystals. Cat. No. 300-131..... \$32.50

TRA-2 AUDIO UNIT

Three transistors. Input 100,000 ohms and 50 ohms. Speech amplifier for dynamic microphone. Push-pull power amplifier class B. Output 300 mw. Wired and tested. Cat. No. 400-104 \$21.50

TRT-2 TRANSMITTER

Crystal controlled. Three transistors. Output 100 milliwatts minimum with #1 transistors. Power stage uses special HF transistors. Wired and tested less crystals and transistors. Cat. No. 200-116 \$10.00
#1 Transistor Kit (100 mw output). Cat. No. 150-128 \$17.50
#2 Transistor Kit (50 mw output). Cat. No. 150-129 \$ 8.00
Crystals FCB for Citizens band (.0025%) \$ 4.75
Crystals FA-5 for Amateur (.01%) \$ 4.00



ASSEMBLY PARTS KIT makes it easy to interwire subassemblies.

Kit includes base plate, squelch control, volume control, transmit-receive switch and antenna connector. Cat. No. 150-136 \$9.95

ORDER DIRECT FROM INTERNATIONAL CRYSTAL MFG. CO.

**INTERNATIONAL
CRYSTAL MFG. CO., INC.**

18 NORTH LEE • OKLAHOMA CITY, OKLAHOMA

**FREE
1961 CATALOG**

SEND FREE 1961 INTERNATIONAL CATALOG
NAME _____
ADDRESS _____
CITY _____ STATE _____

BEST BUYS IN STEREO AND MONO HI-FI

New Stereo/
Mono
4-Track
Tape
Deck
RP100
Semikit (electronics in kit
form) \$289.95 Wired \$395.00



New FM-AM Stereo Tuner ST96
Kit \$89.95 Wired \$129.95
Incl. FET

New 70-Watt Integrated
Stereo Amplifier ST70
Kit \$94.95 Wired \$144.95



New 40-Watt Integrated
Stereo Amplifier ST40
Kit \$79.95 Wired \$124.95



28W Integrated
Stereo Amplifier HF81
Kit \$69.95 Wired \$109.95

FM Tuner HFT90
Kit \$39.95 Wired \$65.95
Incl. FET Metal Cover \$3.95



AM Tuner HFT94 Incl. FET
Kit \$39.95 Wired \$65.95



Stereo Preamplifier HF85
Kit \$39.95 Wired \$64.95

Stereo
Power
Amplifiers



Kit Wired
100W HF89: \$99.50 \$139.50
70W HF87: \$74.95 \$114.95
28W HF86: \$43.95 \$ 74.95



Stereo/Mono Changer/Player
1007 with stereo cartridge
and dual sapphire styli \$49.75



Bookshelf Speaker System
HFS1 Kit \$39.95 Wired \$47.95

BEST BUYS IN CITIZENS TRANSCEIVERS, HAM GEAR, RADIOS

Citizens Band Transceivers
from
Kit
\$59.95
Wired
\$89.95



New 60W CW Transmitter #723
Kit \$49.95 Wired \$79.95



Transistor Portable Radio RA6
Kit \$29.95 Wired \$49.95
Incl. FET

BEST BUYS IN TEST EQUIPMENT

New Metered
Variable AC
Bench Supplies
Model 1073
(3 amps)
Kit \$35.95 Wired \$47.95
Model 1078 (7½ amps)
Kit \$42.95 Wired \$54.95



Peak-To-Peak
VTVM #232
& Uni-Probe®
Pat. #2,790,051
Kit \$29.95
Wired \$49.95



VTVM #221
Kit \$25.95 Wired \$39.95

DC-5 MC
5" Scope =460
Kit \$79.95
Wired \$129.50



5" Push-Pull Scope =425
Kit \$44.95 Wired \$79.95

Tube
Tester
#625
Kit \$34.95 Wired \$49.95



RF Signal
Generator
#324
Kit \$26.95
Wired \$39.95



1000
Ohms/
Volt
V-O-M #536
Kit \$12.90
Wired \$14.90



6- & 12V
Battery
Eliminator
& Charger
#1050
Kit \$29.95
Wired \$38.95




Extra-filtered for
transistor equip. #1060
Kit \$38.95 Wired \$47.95

R-C Bridge
& R-C-L
Comparator
#950B
Kit \$19.95 Wired \$29.95



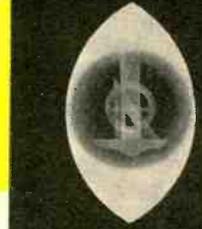Multi-
Signal
Tracer
#145A
Kit \$19.95
Wired \$28.95



EICO®

EXCELLENCE IN CREATIVE ELECTRONICS


Over 2 MILLION
EICO instruments in
use throughout the
world. Compare, take
them home — right
"off the shelf" —
from 1500
neighborhood
dealers, most of
whom offer
budget terms.



EICO, 3300 N. Blvd., L.I.C. 1, N.Y. PE-3
 Send free Catalog describing over
 80 top-quality products, free Stereo
 Hi-Fi Guide, free Short Course for
 Novice License, name of nearest
 EICO dealer. Send new 36-page
 GUIDEBOOK TO HI-FI for which I
 enclose 25¢ for postage & handling.

Name.....
 Address.....
 City..... Zone ... State.....
 Add 5% in the West

WHAT IS THIS MAN WEARING?

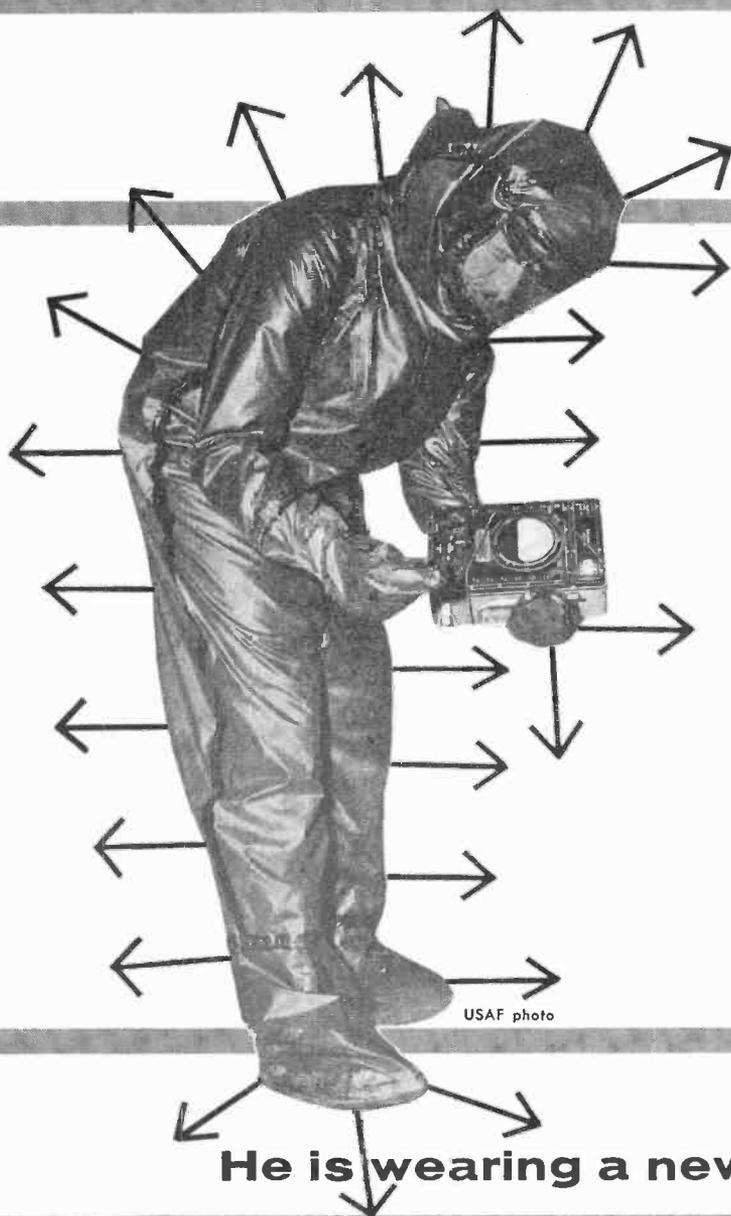

This four-layer suit consists of a neoprene-coated nylon coverall with attached mittens, boots, and headpiece to prevent arcing; two inner layers of silverized cloth to reflect radiation; and a cotton liner to protect the silverized cloth. It is designed to be worn by radar technicians at BMEWS radar stations.

**He is wearing a newly designed
radar-resistant suit**

To see why—turn the page

The Truth About THE DANGER OF RADAR WAVES

**EXCLUSIVE
REPORT**

**By
KEN GILMORE**


To make this Thule, Greenland, radar installation safe for the men who operate it, special passageways (visible at the lower right) were constructed. The peak r.f. power radiated exceeds 10,000,000 watts.


SHORTLY AFTER radar was introduced during World War II, rumors about its dangerous side effects swept through the armed services. Men working around radar, the story went, would never have children.

The rumors were officially denied and discredited, and eventually the furor died down. Everyone became so complacent, in fact, that until a few years ago it was common practice for men working around radar in cold climates to stand directly in the beam to warm themselves.

Recently we've been hearing again that radar waves are dangerous. The armed services and industries which manufacture, test, or operate radar and other powerful microwave equipment are going to a lot of trouble to keep workers away from the business end of high-powered microwave transmitters.

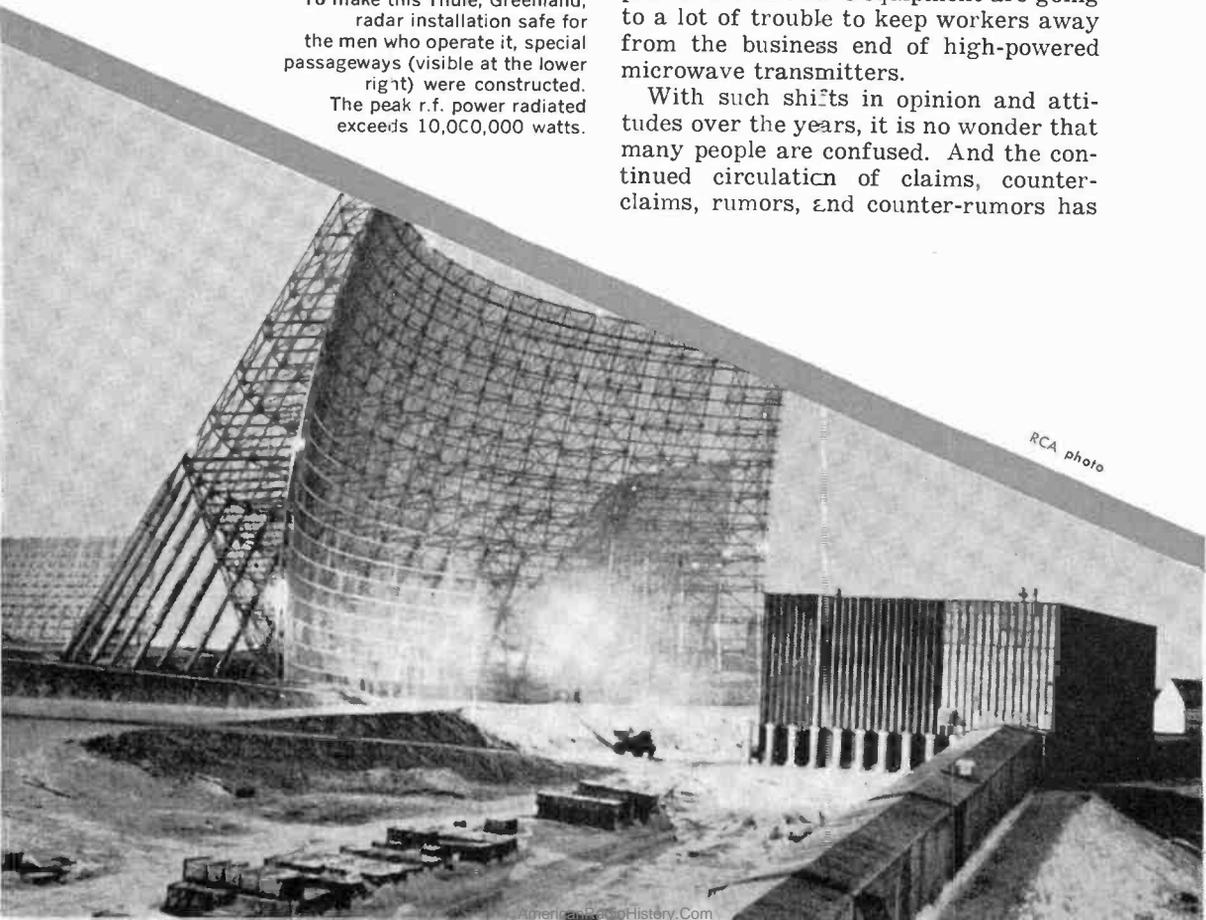With such shifts in opinion and attitudes over the years, it is no wonder that many people are confused. And the continued circulation of claims, counter-claims, rumors, and counter-rumors has



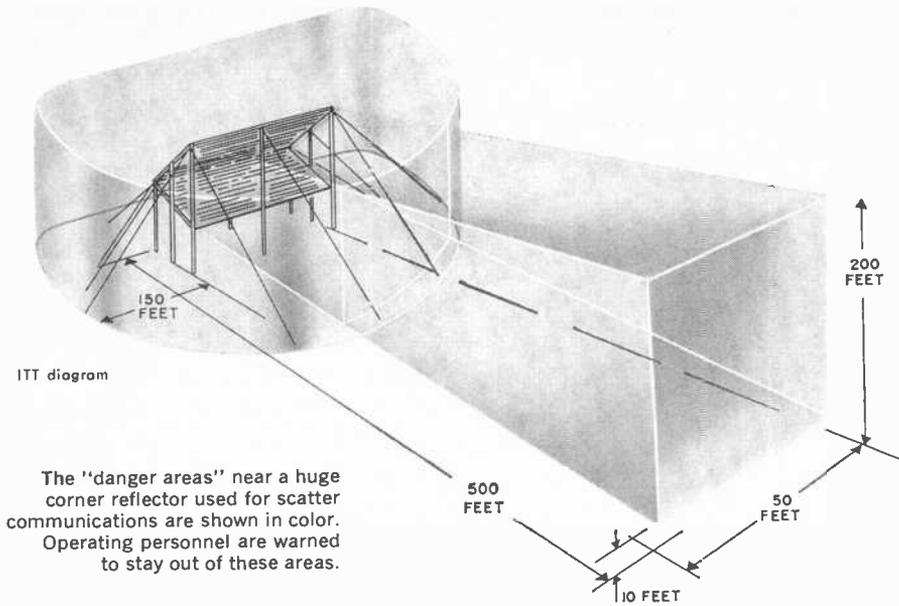

not helped. Less than two years ago, for example, a popular national news magazine reported that a radar technician had been killed by radar. True or false? To this day, not even the experts agree.

When it was announced that a powerful radar station would be installed in northern England as part of our *Ballistic Missile Early Warning System*, a storm of protest broke loose. British newspapers, citizens groups, and individuals claimed that the mammoth transmitter would do everything from killing people in the area to frying bees and thus ruining agriculture by preventing pollination of crops.

Adding to the general misunderstanding, *microwave* radiation has become widely confused in the public mind with *ionizing* radiation. The fact is, the two are completely unrelated. Microwave radiation—the kind we are talking about—is energy generated by radar and other electronic equipment operating roughly between 200 and 30,000 megacycles. Ionizing radiation, on the other hand, is produced by radioactive materials and X-ray machines—it is the radiation we think of in connection with atom bombs, fallout, and the Van Allen radiation belt.

But what of microwave radiation? Is

it dangerous, too? Should experimenters, hams, and others working with high-frequency electronic equipment be very careful?

Although much remains to be learned, intensive research over the past few years has pretty well answered these questions. Summarized briefly, here is what we now know about microwave radiation and the way it can affect us:

- Microwave radiation definitely can affect human tissue and cause damage.

- Only high-powered equipment, usually found either in military or industrial service, generates radiation sufficiently intense to be harmful to anyone.

- Even this high-powered equipment, if its hazards are understood and proper precautions taken, can be used in complete safety and confidence.

- And, most surprising, recent research indicates that microwaves, under certain conditions, can have beneficial effects that may some day be used in the treatment of disease.

Heat Causes the Trouble. Microwaves can cause damage by generating heat in human tissue. Diathermy machines used

by doctors apply this heat-generation principle in a controlled way. It also accounts for the fact that technicians can stand in radar beams and get warm. But this is a mighty dangerous way to chase a chill. Recent experiments show why.

Not long ago, scientists at the National Institute of Neurological Diseases put monkeys directly in the output beam of a 200-watt u.h.f. transmitter operating at various frequencies between 225 and 400 mc. In each case the animals were dead within five minutes. The diagnosis: death by "hyperthermia"—excessive internal temperature. In further experiments, rats, mice, and other animals have proved that microwaves can kill.

Man, of course, can take more. His heat-regulating system is far more effective than those of the lower animals. So he can absorb far more microwave radiation and get rid of the heat. But there is a limit.

Have microwaves actually killed anyone? Scientists do not agree.


About four years ago, a 42-year-old radar technician in Glendale, California, was working about ten feet in front of a radar antenna. He felt a sensation of warmth in his abdomen, and moved quickly away. Nevertheless, he was taken ill a few minutes later. Doctors rushed him to a hospital and found he had a ruptured appendix. He was operated on, but shortly afterwards went into shock and died a few days later. The doctor in charge diagnosed the case as death from exposure to microwave radiation.

But many questions remained. One frankly skeptical Air Force doctor, also an expert in the field of microwave radiation, asked: "Why have thousands of men worked with the same or more powerful radars without even minor injury or discomfort, let alone fatal consequences?"

Many authorities feel that the man died from the results of his ruptured appendix, the operation, shock, or a combination of the three. The case remains unsettled.

Microwaves and the Eyes. Although the danger is clearly present, cases of actual injury from radiation are hard to find. One doctor in Albuquerque, New Mexico, reported that a patient of his developed cataracts from exposure to microwave energy. The technician was in the habit of shoving his hand into a microwave horn to see if the transmitter was operating. If his hand got warm, the power was on.

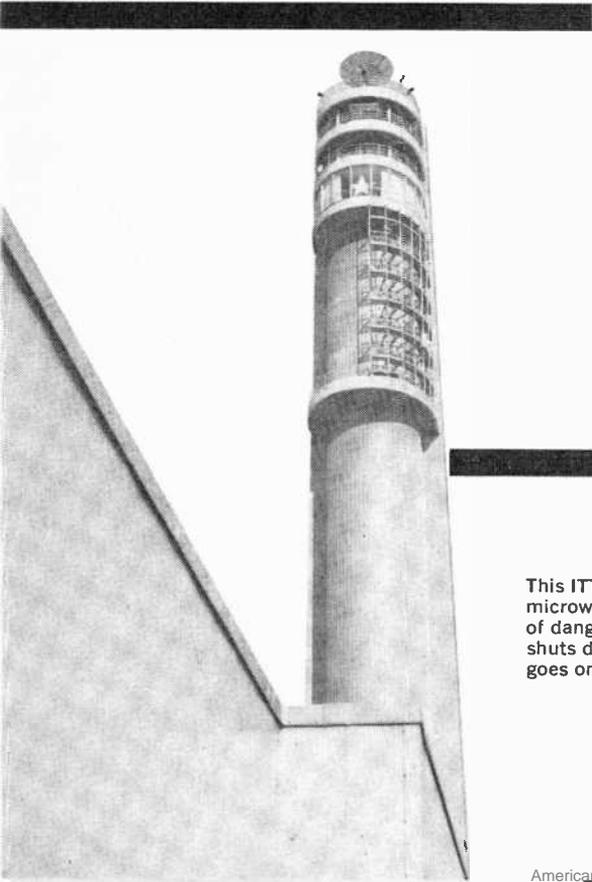
In making this check, he had to look into the horn, and thus also put his eyes directly in the beam. One day, after spending a longer than normal time at work, he found that he could not see



This ITT tower in Nutley, N. J., is used for microwave experiments. To prevent the possibility of dangerous radiation, a trapdoor interlock shuts down the transmitters whenever a technician goes on the roof to service the antennas.



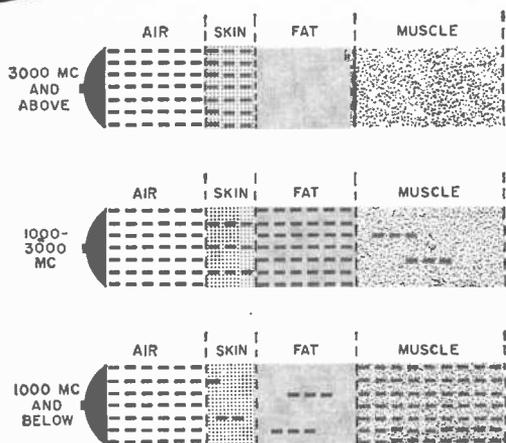A dosimeter developed by Dr. A. W. Richardson of Saint Louis University is used to measure r.f. radiation. Worn by a maintenance technician, it sounds an audible tone when r.f. intensity becomes dangerous.



Frequency determines whether r.f. will be absorbed or reflected by outer layers of skin.

As shown here, r.f. from about 200 to 1000 mc. is most dangerous—it penetrates the muscles and internal organs.

clearly. His doctor diagnosed the difficulty as several small cataracts resulting from r.f. radiation.

Can r.f. really cause cataracts? Tests with animals show conclusively that it can. Rabbits, whose eyes are very much like human eyes, have developed cataracts after exposure to intense radiation.

Tests have shown, as a matter of fact, that the eyes are the body's most radiation-sensitive organs, since they have the poorest heat dissipation system in the

body. Elsewhere, blood circulation and perspiration can quickly get rid of excess heat. But our eyes tend to retain it and get hotter and hotter until damage is done.

Other Strange Effects. Next to the eyes, the most radiation-sensitive organs are the testes. Excessive exposure to microwave radiation, can, as the old rumors had it, make a man sterile. But the situation is not as bad as it seems: the effect is only temporary. Sperm cells are extremely sensitive to heat. Thus, those already manufactured by the body may be killed by a temperature rise of only a few degrees. But radiation *does not* interfere with the body's ability to make more sperm cells. One researcher in the field estimates that a dose of radiation strong enough to permanently sterilize a man would also probably kill him.

All radiation damage to experimental animals so far noted is attributable to the effects of heating. But scientists have recently noted other strange effects that seem to have nothing to do with heat. Researchers at the University of Miami, for example, exposed chickens to a radar beam too weak to kill them. At certain frequencies the chickens began to stagger, lose control of their muscles, and sometimes collapse. When the beam was

(Continued on page 106)

DIRECT-COUPLED

**Complete construction details for a superior-quality
18-watt power amplifier with excellent
frequency response and low transient distortion**

By **HERBERT I. KEROES**

YEARS AGO, before the hi-fi era, an audio power amplifier was built that sounded better than any other then in existence. This unit was called the Loftin-White amplifier, after its designers, and had many ingenious features. It used direct coupling and a method of bias stabilization that was probably the first application of inverse feedback in an audio amplifier. Overall, it had distinctly better sound—noticeably reduced distortion and better bass response.


The modern theory of feedback amplifiers provides a ready explanation for

the improvement brought about by the Loftin-White circuit. Direct coupling reduced the low-frequency attenuation and phase shift, and improved the stability of the amplifier so far as low-frequency transients were concerned. Today we know that an amplifier lacking low-frequency stability sounds weak and puny compared to one that is more stable but less powerful.

Here is a modern version of the Loftin-White amplifier that is free from distortion, is exceptionally stable, and has excellent frequency response. (See power



HI-FI AMPLIFIER

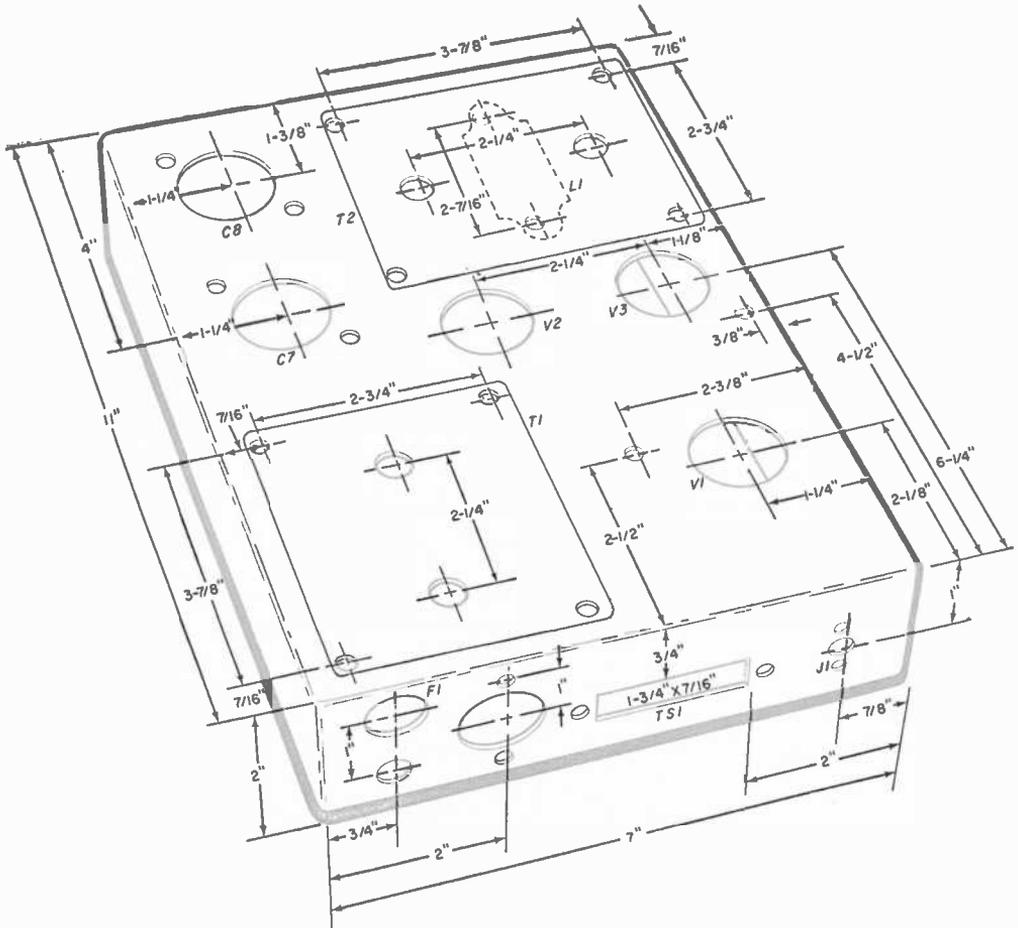


Drill and punch the amplifier's chassis before mounting any components. Filter choke L1 (dashed line) mounts under chassis below transformer T2.

output and frequency response curves on page 50.) With a push-pull ultralinear output stage and a voltage feedback of 20 db, the resulting amplifier is nominally rated at 18 watts but will actually outperform many amplifiers of considerably higher power.

Printed Circuit Optional. Building the amplifier is exceedingly simple if you follow the pictorial and schematic diagrams. If desired, you can purchase a pre-wired and pre-tested printed-circuit board which contains all of the circuit

wiring and components with the exception of the power supply, tubes, and output transformer. The circuit board, the Acrosound Model 20, can be ordered through Allied Radio, 100 N. Western Ave., Chicago 80, Ill.; Lafayette Radio, 165-08 Liberty Ave., Jamaica 33, N. Y.; or Radio Shack Corp., 730 Commonwealth Ave., Boston 17, Mass.

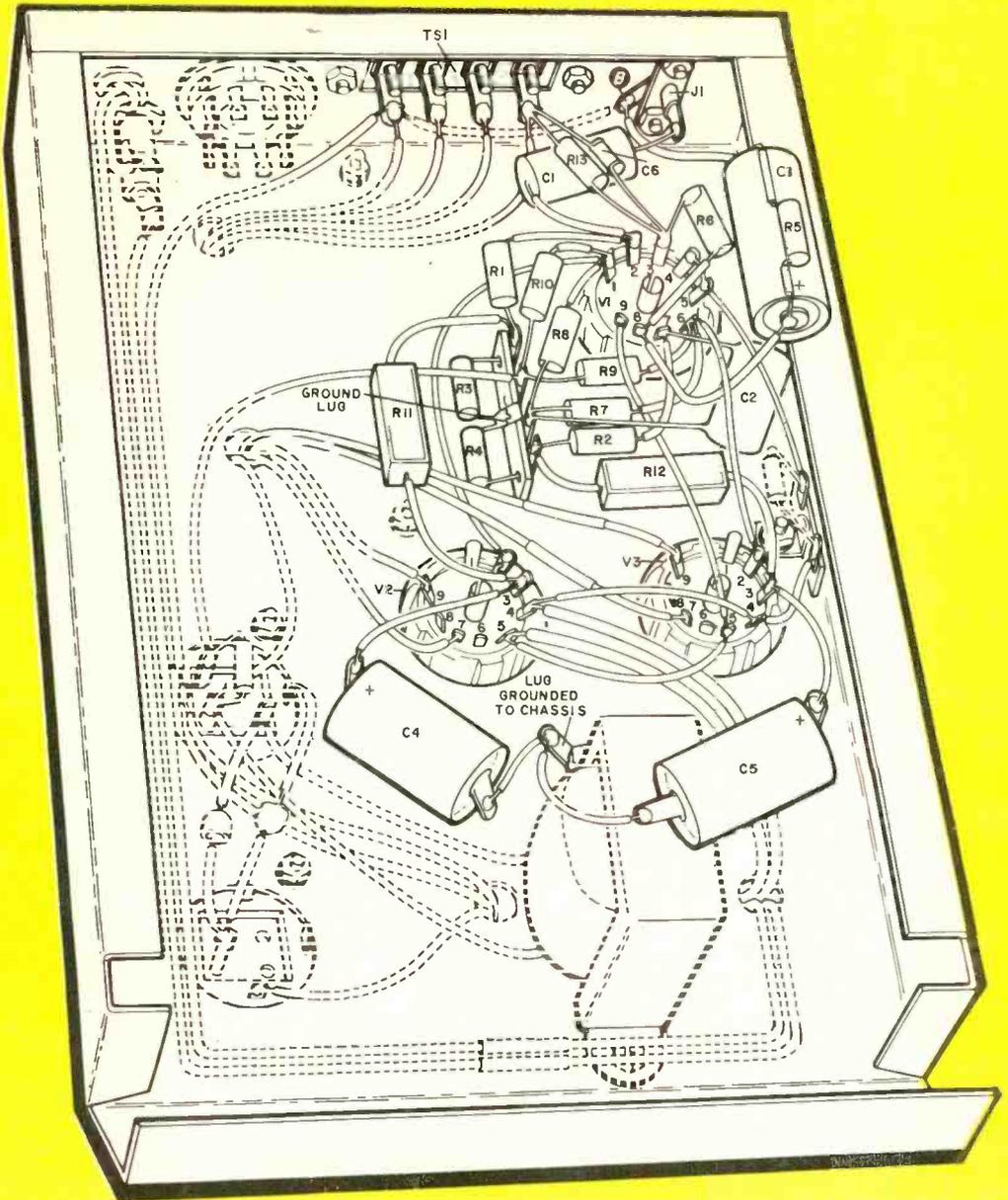Both the audio output and power transformer used in the amplifier can also be obtained from the above-mentioned suppliers. When ordering ask for the Acro-




Audio stages of amplifier are wired last; power supply wiring is indicated by broken lines. Note that circuit is grounded to chassis at only three points.

former, being careful to follow the wiring shown. Note that the power supply is grounded at point *B* only and that filter capacitors *C7* and *C8* are both mounted on the chassis with insulated mounting flanges. It is also important to use an insulated fiber sleeve on capacitor *C8*'s can, since both terminals of

C8 are "hot" with respect to ground. And be sure to polarize silicon diodes *D1* and *D2* correctly.

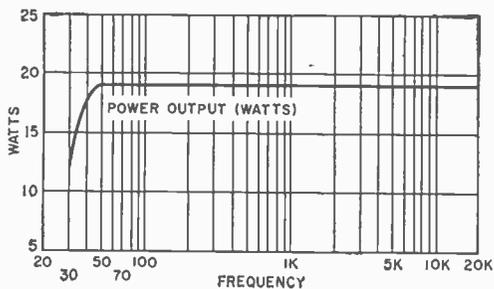Although an octal accessory socket is mounted on the chassis, it need not be wired unless you wish to power auxiliary equipment such as a preamplifier. If you do, connect point *A* to pin 3 of the octal



Power response of amplifier is shown above for a Harmonic distortion of 2%. Note that due to use of a special output transformer the output is flat from 48 to 20,000 cycles. Harmonic distortion at 18 watts output at 30 cycles is less than 3%.

socket and point B to pin 8; these are the 390-volt B+ and ground terminals, respectively. You should also connect pins 4 and 5 of V2's tube socket to pins 2 and 7 of the octal socket to supply 6.3-volt heater current for your accessories. Do not ground either heater lead at the accessory socket since the power trans-

PARTS LIST

- C1, C2—0.047- μ f., 600-volt paper or ceramic capacitor
 C3—250- μ f., 6-volt electrolytic capacitor
 C4, C5—40- μ f., 150-volt electrolytic capacitor
 C6—100- μ f., 500-volt ceramic capacitor
 C7a/C7b/C7c—60/40/20- μ f., 450-volt electrolytic capacitor with insulated mounting flange (Cornell-Dubilier CO365 or equivalent)
 C8—100- μ f., 300-volt electrolytic capacitor with insulated mounting flange (Cornell Dubilier AO340 or equivalent)
 D1, D2—Silicon diode, 750 ma., 600 P.I.V. (Motorola 1N1096 or equivalent)
 F1—3-amp. slow-blow fuse
 J1—RCA phono jack
 L1—2-henry, 200-ma. filter choke (Stancor C2325 or equivalent)
 R1, R2, R7, R8, R9, R10—1-megohm, $\frac{1}{2}$ -watt, 1% resistor
 R3, R4—10-ohm, $\frac{1}{2}$ -watt, 1% resistor
 R5—2200-ohm, $\frac{1}{2}$ -watt, 10% resistor
 R6—330-ohm, $\frac{1}{2}$ -watt, 10% resistor
 R11, R12—1500-ohm, 10-watt, 5% resistor
 R13—5600-ohm, $\frac{1}{2}$ -watt, 10% resistor
 R14—220,000-ohm, $\frac{1}{2}$ -watt, 10% resistor
 R15—6.8-ohm, 1-watt, 10% resistor
 R16—22-ohm, 2-watt, 10% resistor
 T1—Output transformer (Acrosound TO-370)
 T2—Power transformer; 117-volt, 60-cycle primary; 185-volt, 200-ma., and 6.3-volt CT, 4.5-amp. secondaries (Acrosound TP-535)
 TS1—4-lug, screw-type terminal strip
 V1—12AX7 tube
 V2, V3—EL84/6BQ5 tube
 1—Fuse holder
 1—2" x 11" x 7" aluminum chassis (Bud AC-407 or equivalent)
 1— $\frac{1}{8}$ " x 3" fiber insulating sleeve for C8 (Mallory CE-6 or equivalent)
 Misc.—Nine-pin sockets, octal socket, terminal strips, hardware, etc.

HOW IT WORKS

Input stage V1 is used as a combination voltage amplifier and phase inverter. This tube operates with "starved" plate current to achieve maximum amplification, a condition created by the 1-megohm plate resistors (R9 and R10). To obtain best linearity and maximum driving voltage, the heater of the tube is also "starved" by means of dropping resistor R15.

Direct coupling is used between V1 and the push-pull output tubes V2 and V3. The cathode current of each output tube flows through a separate resistor, R3 and R4 respectively, which is coupled to the corresponding grid of V1.

The current feedback through R3 and R4 accomplishes several purposes. First, it stabilizes the cathode current of each output tube under quiescent operating conditions. Secondly, the cathode current is also stabilized under dynamic operating conditions to the point where the stage operates almost completely as class A, resulting in minimum distortion. Finally, the stabilized direct coupling produces an amplifier which has only one principal source of low-frequency phase shift, output transformer T1; this provides perfect low-frequency stability.

In addition to the current feedback, 20 db of voltage feedback is provided by the capacitor-resistor combination C6-R13. The voltage feedback circuit is connected between the secondary of T1 and the cathode of V1a.

Response of transformer T1 drops only 1 db at 5 cps and 60 kc. The primary halves of T1 are tightly coupled for distortionless high-frequency performance. Ultralinear screen taps are provided at the optimum ratio for the output tubes used.

former has a grounded center-tap on the 6.3-volt winding.

When the power supply has been wired, test the resistance between points A and B with a VOM; you should find that it measures well over 1 megohm with the meter connected a few moments. If you get a low reading, reverse the leads to the meter. Should both readings be low, you probably have a defective filter capacitor (C7) or have made a wiring mistake; recheck the wiring against the pictorial and schematic diagrams.

Once the power supply checks out with the VOM, you can give it an operating check. Connect a 5000-ohm, 50-watt resistor between point A and point B. Power the circuit already wired, and test for 390 volts d.c. between points A and B. If the desired voltage is present, the power supply is operating under a load approximating actual operation.

Wiring the Audio Stages. With the power supply wired and tested, proceed with the wiring of the audio circuitry follow-

CASTRO'S RADIO VOICE

AFTER BEING in power for two years, Fidel Castro has started to build a radio propaganda network second to none in Caribbean coverage. Although principally concerned with keeping down unrest in his own country, Castro is obviously propagandizing all of his Latin American neighbors from Guatemala to Venezuela as well. Where will he stop is now the question. Annoyed by *Radio Swan* (see article below), Castro may well switch to English-language broadcasts on both the short-wave and broadcast bands. He has the personnel and he has the equipment.

Fidel, via one Antonio Nunez Jimenez, set up his propaganda network the easy way. Whenever and wherever a radio broadcasting station was needed, the Cuban government simply "borrowed" it. The only "new" link in this network is Jimenez's own station CMBN, *La Voz del INRA*. Remember the initials INRA and the name Jimenez—we may hear much more of them before 1961 has run its course.

Jimenez is the executive director of *Instituto Nacional de Reforma Agraria* (National Institute for Agrarian Reform), which was established as a result

RADIO SWAN

The thorn in Castro's side

PROBABLY no other one thing has frustrated Fidel Castro, Cuba's be-whiskered dictator, as much as a radio station with the picturesque name of *Radio Swan*. Located on a barren piece of Caribbean rock, the station has become a political hot potato. So wacky is the story behind *Radio Swan* that it could easily form the basis for an English political film comedy—another "Mouse That Roared."

Castro's feelings about *Radio Swan* are summed up in this remark which he made before the United Nations on September 26, 1960. As unofficially translated in *The New York Times*, Castro's comments were:

In the Caribbean Islands [is] a territory which belongs to Honduras and which is known as The Swan Islands, [and] the Government of the United States has taken over this island.

It has set up a very powerful broadcasting station which it has placed at the disposal of war criminals and the subversive groups that

are still being sheltered by this country.

The "war criminals" who operate *Radio Swan* are a sedate group of American businessmen whose primary interest is making the station a commercial success. That they tweak Fidel's nose in the process is not of the slightest importance to them. They own the station in the name of the steamship-less Gibraltar Steamship Corporation.

Whose Islands? The Swan Islands are two coral and limestone islands lying at 17°24'N and 83°56'W, or about 97 miles north of Patuca Point, Honduras. The easternmost island, "Little Swan," is uninhabited. The western island, "Great Swan," is 2 miles long by ½-mile wide, and is inhabited by 20 Caymen Islanders—who grow coconuts, six employees of the U.S. Federal Aviation Agency, and about 20 *Radio Swan* operators and engineers.

The Swan Islands were declared a possession of the United States in 1863, although they now seem to be privately owned by a Mr. Sumner Smith of Boston,

By hook or crook, Cuba's Fidel Castro is extending his radio coverage throughout the Caribbean

By C. M. STANBURY II

of Castro's land reform bill of June 3, 1959. In Cuba the word "reform" can cover a tremendous amount of territory. Jimenez is responsible for confiscation of property, breaking up large land holdings, and redistributing them to tenant farmers.

La Voz del INRA. In late October, 1960, CMBN, *La Voz del INRA*, became the hub of Castro's new propaganda network. Residing on 1160 kc., formerly occupied by CMJK (a weak 500 watts), CMBN is destined to be a high-power outlet that will effectively jam *Radio*
(Continued on page 54)



UPI

By TOM KNEITEL, WPE2AB

Mass. Since the island is supposed to be his private property, the various tenants on "Great Swan" pay rent to Mr. Smith for the use of it. But Honduras has been grumbling that it really owns the territory, and recently Nicaragua began laying claim to it as well. *Radio Swan* solved this dilemma for themselves by paying Mr. Smith and not applying to any country for a radio transmitting license.

When *Radio Swan* went on the air in the summer of 1960, its owners began selling commercial time to all comers. They were fairly successful in lining up many sponsors (cigarette companies, a tissue company, etc.) plus a few private political groups—among them some anti-Castro exiles from Cuba and some anti-Trujillo exiles from the Dominican Republic.

Almost immediately, Fidel began raising the roof with his "war criminal" routine. But who could he complain to? He might have questioned the U. S. Government and received the same reply we got from the Federal Communications Commission dated September 16, 1960:

In response to your letter of September 12, 1960, you are advised that the Commission has no information regarding the radio operations to which you refer.

Or he might have asked Honduras and gotten this answer:

In response to your letter of the 12th of this month, we wish to inform you that Radio Swan, located on Honduras' Swan Islands, has neither solicited nor obtained government permission to operate on Honduran territory.

Meanwhile, *Radio Swan* has been going strong with a 50,000-watt broadcast-band transmitter and a 7500-watt short-wave rig.

The whole situation has understandably been pretty embarrassing to the U. S. State Department. Until we broke diplomatic relations with Cuba this past January, Fidel was putting the pressure on the State Department to get *Radio Swan* off the air—which, of course, it was unable to do since the Department felt it

(Continued on page 55)

CASTRO'S VOICE

(Continued from page 53)

Swan, and also be on the air more hours per day than *Radio Swan*.

The choice of call letters for CMBN was unusual since this station is located in Calbarien, in the central Cuban Province of Las Villas, which would not normally have the prefix CMB. Heretofore, the call "CMBN" had been allocated to a station on Isla de Pinos—ironically, an American tourist resort. Station CMBN is using the confiscated channel of CMJK, *La Voz del Camagueyano*, a station best remembered for its companion short-wave outlet on 9625 kc.

Under the enthusiastic guidance of Sr. Adrian Garcia Hernandez, *La Voz del INRA* could give the Soviets lessons in propaganda. Unless you happen to tune in during one of Castro's long emotionally-charged speeches, you could easily mistake CMBN for a commercial Latin American station. There is an abundance of popular Cuban music, news, plays, and even commercials; of course, these are for companies and products seized by the revolutionary government. Station CMBN fills in with very short propaganda blurbs and an occasional long political commentary—plus Castro's harangues.

Other INRA Stations. Of the independent stations now in the INRA propaganda network, CMBL, *Radio Aeropuerto*, (860 kc.), at the Jose Marti airport near Havana, is the most important. It furnishes a valuable short-wave outlet (COBL) on 9833 kc., which cannot be heard too well in the United States because of teletype interference and the 100-kw. signal of *Radio Budapest* on the same channel. It is a safe bet that Castro will soon order COBL to confiscate a new frequency and to up its power.

Meanwhile, CMBL is locked in a new struggle on the 860-kc. channel. This time it is with Trujillo's propaganda voice, *Radio Caribe*, which has unexpectedly taken up residence on this channel and is doing a good coverage job around Santiago, Cuba.



UPI

Another Havana station playing an interesting part in this propaganda war is CMBQ, *Radio Continental*. It has been in and out of Castro's favor since the revolution. Shunted from its strategic 1010-kc. channel to make room for CMZ, it is now spotted on 1150 kc. Station CMZ was inherited by Castro from Batista's Ministry of Education and for some reason still operates independently of INRA and Jimenez.

Station CMBQ is the news source for CMBN, CMBL, and the seven smaller transmitters operated by INRA. Of this latter group only CMGS, *Radio Varadero*, (1580 kc.), can be heard in the eastern United States. Most of North America is blanketed by Canadian Station CBJ, also on 1580 kc.

The INRA network has come up with propaganda especially designed for the Spanish-speaking nations in the Caribbean. It differs little from what they are used to and seem to prefer, but it is in sharp contrast with the dull programming of *Radio Moscow*, *Radio Budapest*, etc. Although *Radio Swan* is a powerful irritant to Castro, the major job of combating Latin American propaganda is being left undone.

—50—



RADIO SWAN

(Continued from page 53)

had no control over the station in the first place.

"Invasion" Party. When the *Radio Swan* situation began to get hectic, a group of Hondurans decided it was time to take a firm stand on the Honduras claim to the Swan Islands. About a dozen brave souls set out from Honduras in a rented boat for an "invasion" of the islands.

After a rough trip, they "took the beach" and asked the boys at *Radio Swan* to give them some seasick remedies and to point out a location where they could run up a Honduran flag. The *Radio Swan* gang gave them a cordial welcome and directed them to an appropriate spot where they proceeded to "fly their colors."

Lunch was served by the *Radio Swan* people, and a parting gift of a bottle of Honduran-made "Scotch" was given to the Swan Islanders by the invasion party before its return to Honduras. A good time was had by all.


Castro, on the other hand, established


his own radio station, CMBN, on *Radio Swan's* channel in an effort to jam the frequency. But this jamming is said to be only mildly effective on an island-wide basis.

As we go to press, *Radio Swan* is still operating without a license and diplomats are still taking tranquilizers over the problem of who really owns the Swan Islands. Castro is still burning about the whole situation, and the land-bound Gibraltar Steamship Corporation is enjoying a profitable business venture.

Reports Welcomed. *Radio Swan* is anxious to receive reception reports from DX'ers, which the station will verify. On the air they announce their address as *Radio Swan*, Box 1247, General Post Office, New York, N. Y., but faster verification can be had if you write to *Radio Swan*, c/o Gibraltar Steamship Corp., 18 East 50th St., New York 22, N. Y. Previously reported addresses are no longer correct.

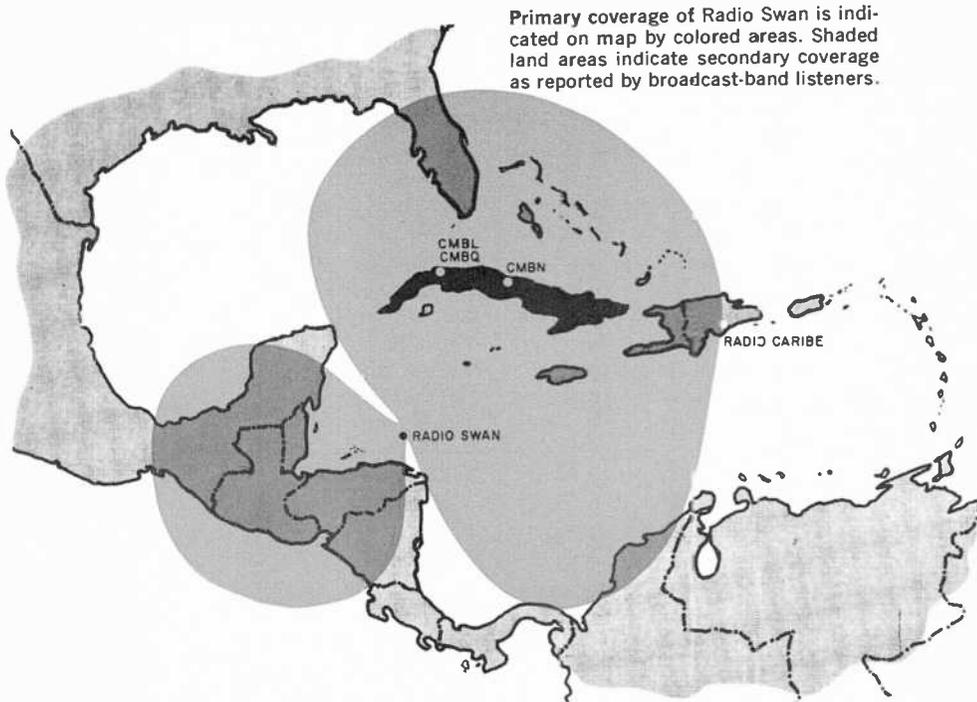The station is scheduled to operate on 1160 kc. at 0500-0715 and 1800-2300 Monday to Saturday, at 1830-2215 on Sundays; and on 6000 kc. at 0800-1015 Monday to Saturday, 1830-2215 on Sundays. All times are EST. -30-



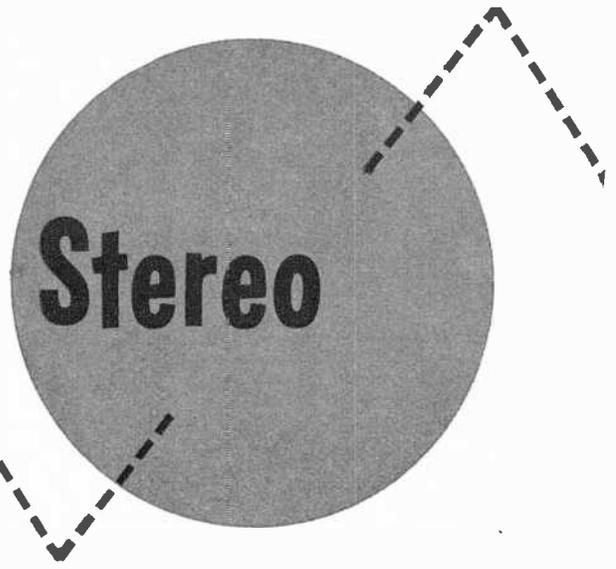

IT HAS BEEN SAID that Americans are a nation of “faddists,” and this philosophy might have a certain germ of truth. There are few of us who can’t recall some of the many fads which have swept the country . . . from the “Charleston” and raccoon coats—through chain letters, bubble gum, and the yo-yo—to the Mayo clinic diet, multi-colored shoe laces, the hula-hoop, and rock n’ roll. Now a restless public has embraced a particular type of stereo recording as one of its latest fads.

The so-called “super” or “spectacular” stereo records are instantly recognizable by their titles, which have spawned a whole new lexicon of musical usage. Since “percussion” seems to be the dominant theme in all these titles, some sociologists have drawn the inference that man is showing an unconscious predilection for this most primitive and basic of all forms of music!


As anyone who is even remotely interested in recorded music knows, we have had stereo records for almost three years. While there were the inevitable early “clinkers,” hundreds of fine stereo discs have been produced. Why then this sudden fad for the new stereo recordings? If we accept their “super” or “spectacular” designations, are we to assume that

other stereo recordings outside this special group are of lesser quality? Let us examine this phenomenon and find a reason for the attraction of the “special stereos” and just how they came into being.

The Stereo Console. It has become almost an axiom that in this country it is the women who “wear the pants.” It is our charming sisters, wives, and mothers who keep a firm grasp on the American purse-strings. Because of their formidable buying power, they exert a tremendous influence on the manufacturers of every product from alphabet soup to zirconium.

Thus, quite early in the stereo era, the stereo console was born. Its design was obviously intended to appeal to the ladies. And it did—ah, they sighed, what lovely Queen Anne styling, what charming Provincial, such Colonial chic, etc., etc. The manufacturers had caught the brass ring again, and the ladies were happy.

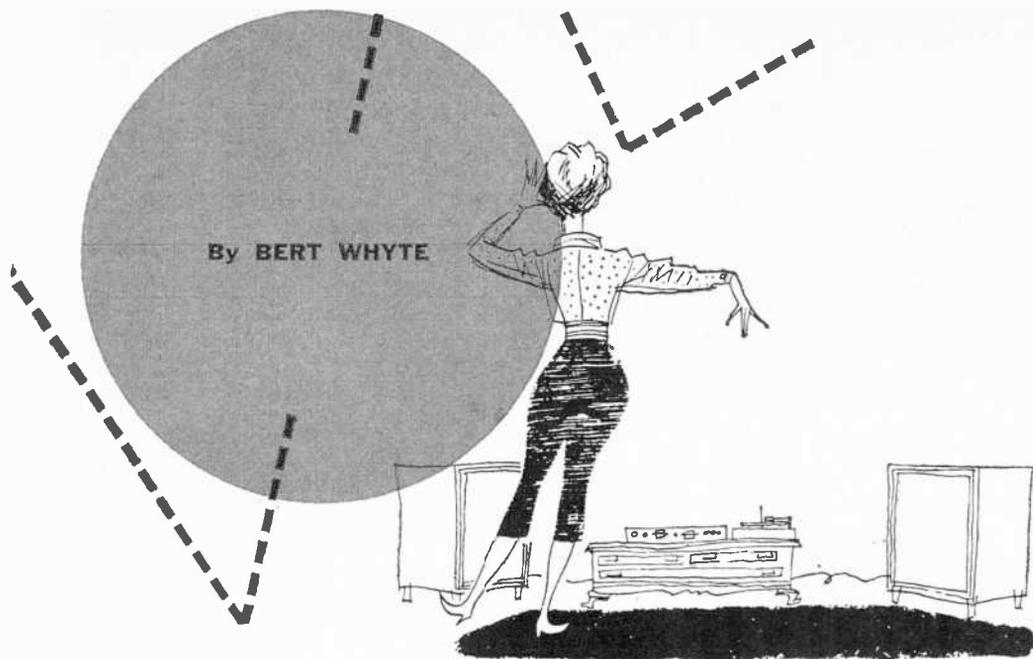Of course, solving this problem simply gave birth to another. The quality and finish of the consoles were equated with size and cost. Since even modest cabinetry is relatively expensive, and since the unit would be used in an average-sized living room, the size of the console



soon became fairly standardized. And so we have the stereo console of today—the regular garden variety of unit that can be seen in almost every department, appliance, and music store across the country.

Premium on "Directionality." Although the ladies and their spouses were happy with the cabinetry, they had been heavily hammered with the glorious virtues of stereo. Therefore, apart from keeping up with the Joneses or filling up a space in the living room, they actually expected to be enthralled by this fabulous new sound. What's more, when our lady-friend and her hubby were buying their unit, they probably were given a sales talk and demonstration by a clerk whose disorientation and lack of knowledge about stereo were only slightly less than theirs. Out of this hubbub of semi-fact and fiction, there lodged in the mind of the clerk and customer alike the term "directionality."

Like some great universal truth, directionality has come to be accepted as the prime function of stereo. Thus armed, our couple turns on their bleached walnut console and eagerly listens for this new miracle to unfold. But since the speakers in their unit are separated by as little as two feet, they strain their ears mightily.

At the distance they are probably sitting from the unit, stereo direction is either barely perceptible or completely absent.

Keenly aware of the stereo console's strengths and deficiencies, Enoch Light, a veteran band leader and the head of several record companies, and a man fairly conversant with modern recording techniques, did some thinking. Along with Bob Fine, the well-known engineer who has been responsible for the superb Mercury classical recordings, he reasoned that to the average person stereo means directionality more than anything else. He knew that the average stereo console was incapable of any significant degree of directionality. Since this was the case, why not produce recordings which would deliberately enhance the directional effects and at the same time take advantage of the other shortcomings in these consoles?

Percussive Magic. Messrs. Light and Fine put in about a year of planning and experimentation, and formed a new company called "Command." Their first stereo disc burst on the public like a bombshell. Entitled *Persuasive Percussion*, it made the heretofore inadequate consoles sit up and do tricks, much to the delight of their owners who now saw the unit as a means of musical enjoyment

as well as a piece of furniture. This successful disc was followed by others in rapid order. Inevitably, more companies jumped on the bandwagon and a flood of similar recordings reached the public.

Like anything else, this type of stereo recording has its good and its bad points. For while they do sound "good" on stereo consoles, these recordings are, by intent, completely contrived and artificial. Theirs is music rigidly confined to the purposes of recording—you could not take the orchestra involved, put it on a stage, and expect to hear in live form what you would hear in the recording.

Question any of the producers of these records and they will candidly admit that they are making the recordings specifically for the "inadequate" stereo units. Rule one, then, is that the various instru-

instruments, a condenser mike on some others, and dynamic mikes on still others. The mikes may have variable patterns, but most likely they are set for the cardioid pickup, again allowing for maximum separation effects.

Depending on the dynamic power of the instrument involved, the mike is set as close as possible to the instrument—in some instances practically on top of it! This setup affords the engineer the best possible signal-to-noise ratio, and the close-up sound has great "presence." Depending on where the recording is made, some engineers will use natural reverb if it is controllable, while others prefer to record "dry" and then add the exact amount of artificial "reverb" or echo they desire. In almost all cases, reverb is considerable, for here again is

an enhancement of stereo perspective and "presence." With a multiplicity of mikes being used, sometimes almost one for each instrument, and with the close pickup employed, the distortion contributed from the mikes and instruments is individually very little. As a result, the recorded sound is remarkably "clean" when suitably reproduced on stereo equipment.



mentalists or instrumental "choirs" are recorded with far greater physical separation than in "normal" setups.

Tricks of the Trade. It is a characteristic of the average stereo console that the best and least distorted reproduction is in the middle ranges; generally there is only fair-to-poor high-frequency response, and not much response at all at the bass end. Rather, there is a more or less deliberate boost of what lows are achieved. Add cabinet resonances to this and the bass is best described as "boomy." Taking power considerations into account and the inherent gain versus hum of the average console, it is always an advantage to play back a recording which has a high sound level, thus keeping the hum down in proportion.


With this knowledge in mind, the "super" stereo engineer sets up microphones whose characteristics are complementary to a given musical instrument. Thus he may use a velocity-type mike on some

Having done about as much as possible in the studio itself, the engineer can also employ other tricks at the mike control mixer or later in re-recording. For example, taking advantage again of the mid-range response of the average console, the mid-frequencies in the music being recorded are boosted a certain number of decibels. This makes everything in that range sound very "forward" and extremely "bright." Equalization is often boosted at the top of the middle range and into the high frequencies to emphasize high strings and such instruments as bells, triangles, vibraphones, and cymbals. The bass range is usually left alone for fear of exciting so much "boominess" that the result would be acoustic "mud."

Another trick is the rapid switching of one group of mikes and instruments to another position—from left to right and vice-versa, for example.

(Continued on page 122)

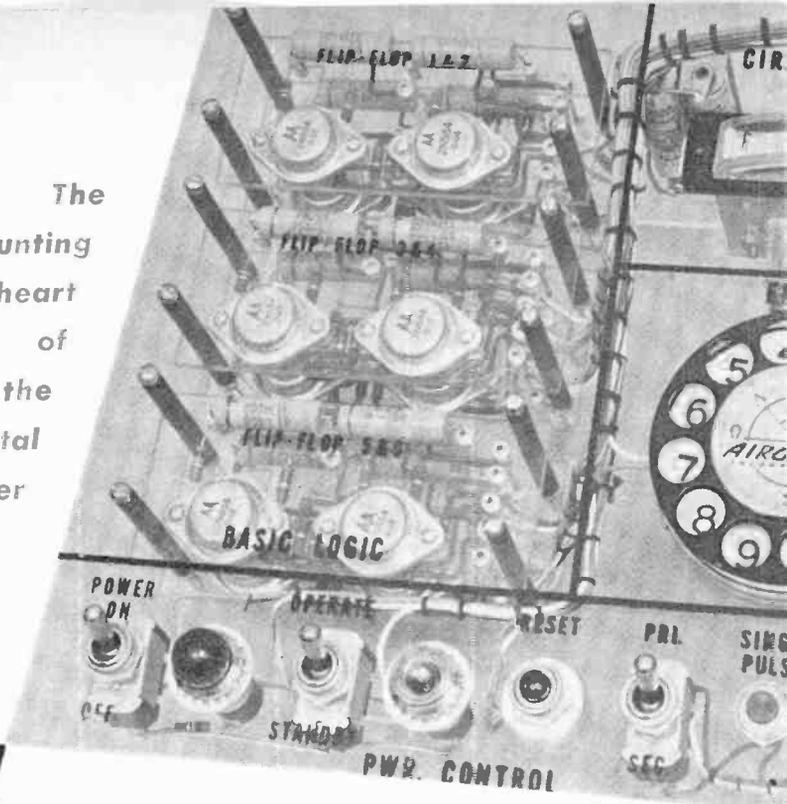The
counting
heart
of
the
digital
computer




FLIP-FLOP CIRCUITS

This article discusses the transistor circuits used in the Digital Computer Demonstrator shown above and on this month's cover. Manufactured by Aironics, Inc., 1035 E. 26th St., Hialeah, Florida, the unit is an educational aid for demonstrating how simple transistor circuits can perform basic computations.

THE digital computer, the electronic brain so widely used in industry and science, is an awesome giant. It's true that some computers—those housed in office-sized desks, for instance—are relatively small physically. But to the untrained eye, their internal workings are a veritable electronic nightmare. Of even more gargantuan concept are the mammoth versions which actually occupy the whole of specially designed, air-conditioned buildings.

On closer inspection, however, the biggest digital computer proves to be only slightly more complex than a brick building. Made up of hundreds, sometimes thousands, of tiny printed-circuit boards—its "bricks," the digital computer also contains such rather unspectacular items as plug-in control panels, tape decks, and

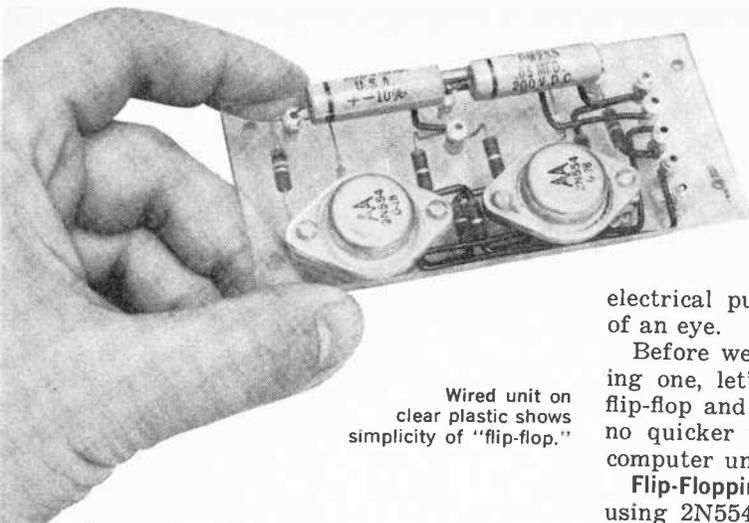By **JULIAN M. SIENKIEWICZ**
Managing Editor



Wired unit on clear plastic shows simplicity of "flip-flop."

typewriter-like read-out machines. Interconnecting its multitude of components are precisely what you might think—miles and miles of wire!

One of the building "bricks" which make up the counting heart of the digital computer is the "flip-flop" circuit, usually tucked away within the computer on a printed-circuit board about the size of a postcard. One such "flip-flop" is the Eccles-Jordan bistable multivibrator. An easy way to visualize its operation is to think of it as an on-off toggle switch. Like the switch, a flip-flop must settle in one of two stable states. But unlike the switch, the "flipping" or "flopping" of the Eccles-Jordan is accomplished by

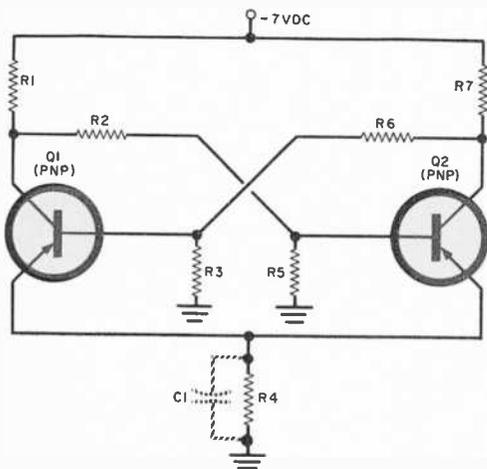


Fig. 1. Typical flip-flop circuit using power transistors. C1 is optional—see text.

electrical pulses quicker than the blink of an eye.

Before we actually set to work building one, let's take a closer look at the flip-flop and see how it is used. There's no quicker way to get on the road to computer understanding.

Flip-Flopping. A typical flip-flop circuit using 2N554 *p-n-p* power transistors is shown in Fig. 1. Whenever power is applied to the circuit, one of the transistors will conduct and the other will be cut off. To understand how this happens, let's assume that transistor *Q1* is conducting ("on") and transistor *Q2* is cut off ("off"). The voltage at *Q1*'s collector is low—less than one volt—due to the large collector current through *R1*.

The current through *Q1* also passes through the common-emitter resistor, *R4*, developing a voltage drop which makes the top end of *R4* more negative than its grounded end. The value of *R4* is such that this would ordinarily make the base of *Q1* more positive than the emitter (reverse bias), preventing *Q1* from conducting. However, the base of *Q1* receives enough negative voltage from the collector of *Q2* to overcome this negative emitter voltage, keeping the base-emitter bias negative and transistor *Q1* conducting.

The voltage at the collector of *Q2* is approximately -7 volts (the same as the power supply voltage), since *Q2* is not conducting and the voltage drop across *R7* is almost zero. There is, however, a small current drain through *R7* due to *R6* and *R3* and collector-emitter leakage in *Q2*.

Transistor *Q2* is held at cutoff because the negative voltage at its emitter—due to the voltage drop across *R4*—is greater than the negative voltage reaching its base from the collector of *Q1*. In other words, the base of *Q2* is positive compared to its emitter (reverse bias) and *Q2* cannot conduct.

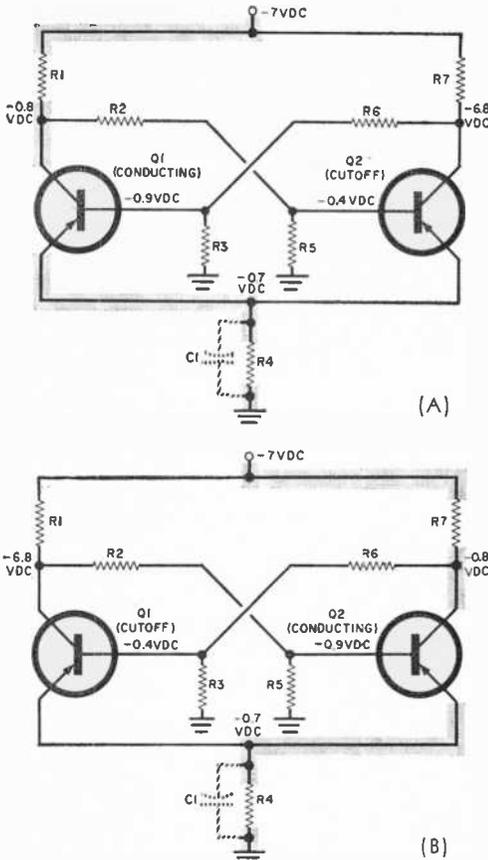


Fig. 2. Shaded lines indicate current path through flip-flop multivibrator when $Q1$ conducts (A) and when $Q2$ conducts (B).

Fig. 3. The circuit of Fig. 1 with two trigger inputs added.

increases to -7 volts. The base of $Q2$, which was positive compared to its emitter, now becomes more negative, because the negative voltage at $Q1$'s collector is passed on to $Q2$'s base through a voltage divider, $R2$ - $R5$. Transistor $Q2$ now conducts heavily and $R7$ drops the voltage at $Q2$'s collector to less than a volt. This low negative voltage is transmitted through $R6$ and $R3$ to the base of $Q1$, permitting $Q1$ to remain in a cut-off state.


The circuit has now "flipped" and the transition period has ended. As before, the flip-flop is in a stable state, but $Q2$ is "on" and $Q1$ is "off." The multivibrator will remain in either stable state until a pulse from an external triggering circuit causes it to flip or flop. Figure 2 (B) shows the current path and circuit voltages when $Q2$ is conducting.

During the transition period, incidentally, when one transistor cuts off and the other is turned on, the voltage drop across $R4$ remains practically unchanged.

Figure 2 (A) shows the current path through the flip-flop multivibrator and d.c. voltages measured to ground when $Q1$ is conducting. The heavy lines show the current path from the -7 volt power supply, through $Q1$, to ground.

This state of affairs— $Q1$ "on" and $Q2$ "off"—will continue indefinitely because the flip-flop circuit is in a stable state. To reverse the transistor conditions—that is, to make the circuit "flip"—let's assume that we momentarily decrease the negative voltage on $Q1$'s base so that the transistor stops conducting. The flip-flop now goes through a transition period of very short duration.

As $Q1$ cuts off, its collector voltage

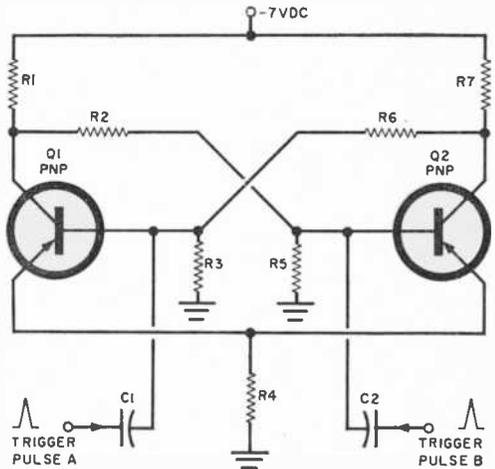

In many flip-flop circuit applications, $R4$ is bypassed by a high-value electrolytic capacitor, $C1$, to insure constant voltage on the emitters of $Q1$ and $Q2$ during the flip or flop of the multivibrator.

Triggering. Before we can put the flip-flop to work for us in a digital computer, some additions to the basic flip-flop circuit are necessary so that we can make either transistor conduct at will. The circuit shown in Fig. 3 is identical to that in Fig. 1 except that two input trigger-

ing signals can now be applied to the base of either transistor through capacitors *C1* and *C2*. By applying a positive pulse to the base of the "on" transistor or a negative trigger pulse to the base of the "off" transistor, the circuit will switch from one state to the other. Let's consider the positive trigger pulse because we will see later that it can be obtained with a simple circuit using only a push-button switch and a resistor.

When *Q1* is conducting (Fig. 3), a positive trigger pulse (*A*) is applied to the base of *Q1*. If this positive pulse is of sufficient amplitude, the base will be driven positive with respect to its collector and *Q1* cut off. The collector voltage of *Q1* will rise rapidly to -7 volts and a part of this voltage will be applied to the base of *Q2* through voltage divider *R2-R5*. Transistor *Q2* will now conduct, its collector voltage will drop to less than a volt, and this voltage will be applied to the base of *Q1* via *R6* and *R3* to hold *Q1* at cutoff when the positive trigger ends.

Obviously, we have just "flipped" the circuit. This same action takes place when a positive trigger pulse (*B*) is applied to *Q2* as this transistor is conducting, although nothing will happen in the event that a positive pulse is applied to

either transistor when it is *not* conducting. This results from the fact that when the transistor is cut off, a positive pulse only helps to keep it in its cut-off state. Therefore, no change will take place.

The flip-flop shown in Fig. 3 requires two trigger signals to "switch" it from one state to the other and back again. With the modified triggering circuit shown in Fig. 4, only one signal source is necessary.

Let's see what happens in the circuit of Fig. 4 when *Q2* is conducting. From Fig. 2 (B) we know that *Q2*'s collector is more positive than its base. Diode *D2*, connected across the base and collector of *Q2* through *R9*, is biased so that it will conduct heavily the instant a positive trigger pulse passes through *C2*. Diode *D1* is wired in the same manner except that its anode is about six volts negative with respect to its cathode. Therefore, a positive trigger pulse must overcome this large negative bias before it can pass through *D1*.

Switch *S1* controls the positive pulse that flips the circuit; note that the junctions of *C1*, *C2*, and *S1* are connected to -7 volts through *R10*. When *S1* is depressed, the -7 volts at this junction are

(Continued on page 104)

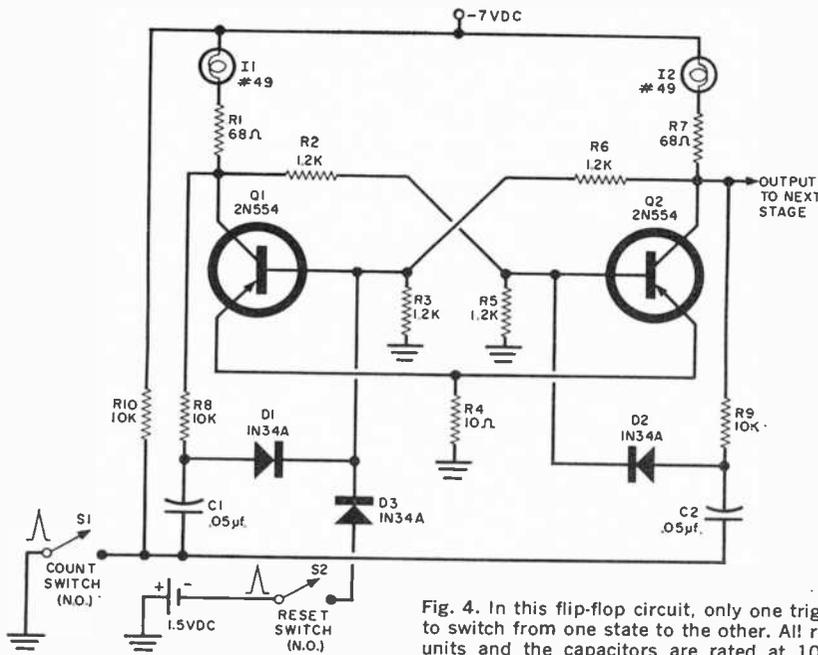


Fig. 4. In this flip-flop circuit, only one trigger input is needed to switch from one state to the other. All resistors are $\frac{1}{2}$ -watt units and the capacitors are rated at 10-w.v.d.c. minimum.

Buying an amplifier?

Then here's what you should know about



CURVES

By G. H. HARRISON

ONE DAY last fall, a fellow we'll call Joe Rodgers caught the hi-fi fever and ran panting—checkbook in hand—to his hi-fi dealer's showroom.

Joe's next-door neighbor, Sam, had a fine system to which Joe had turned an ear on many an occasion. Since everybody said it sounded great, Joe decided to get one just like it. He bought a turntable, arm, cartridge, and speaker just like Sam's. But when he got to the amplifier, his bank balance was running low.

The dealer pointed out another amplifier—with the same power rating—whose price tag was a good bit lower than the amplifier Joe really wanted. But the specifications of the two units were almost identical. "Frequency response flat from 20 to 20,000 cycles, power output 10 watts, harmonic distortion below 1% at full rated power output," ran the spec sheet. Just like the specs of Sam's amplifier, Joe remembered. So he bought the cheaper amplifier.

Later, at home, Joe settled back to enjoy some real music. There was only one trouble—his system didn't sound as good as Sam's! In particular, it didn't produce the rich, satisfying bass Sam's did; and

the highs, especially the violins, didn't sound as crisp and clear as Joe thought they should.

The Whole Story. The mistake our friend made was a common one: he didn't realize that most amplifier "specs" tell only part of the amplifier's story. To find out what's really happening when an amplifier starts hammering watts into a speaker, you need more than the specifications most manufacturers include on the sales brochures: you need *curves*.

Why curves? Because a collection of six or eight accurate curves, covering frequency and power response, distortion at various frequencies and output levels, tone-control characteristics, equalization errors, loudness contours, and so on, can tell you more in a minute than you can learn from studying pages of performance data all day.

As hi-fi fans in general have begun to understand the importance of curves in judging an amplifier's quality, manufacturers have begun to publish them in ever greater quantities. And although you may have to do some digging—not all manufacturers include complete curves with instruction manuals—you

can now find curves for just about any piece of equipment you're interested in.

Curves may at first seem mysterious and complicated, but understanding them is really no trick at all. A curve is simply a visual way of presenting a mass of statistics clearly and graphically.

Frequency Response. Although the frequency response of an amplifier can be shown in tabular form as in Table 1, Fig. 1 shows the same information in curve

freq	db.	freq	db.
20	-.5	800	+.15
50	-.3	1000	0
70	-.2	2000	-.05
90	-.1	3000	-.1
100	0	5000	0
200	+.1	6000	+.05
300	+.2	8000	+.1
500	+.3	10000	+.2
600	+.25	20000	+.4

Table 1.

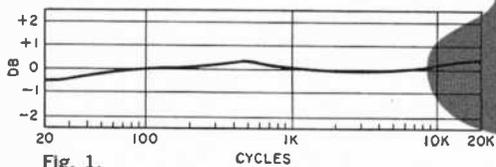


Fig. 1.

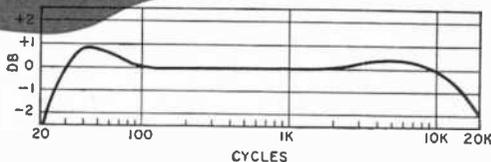


Fig. 2.

form. And a single glance at the curve tells us everything a careful reading of all the figures in the table does. (These figures indicate how many decibels—"db"—the amplifier's gain varies at different frequencies; 1 db is the amount a signal must change for our ears to detect that there has been a change in level.)

The amplifier whose curve is shown in Fig. 1 has a very fine frequency response. Its output is almost "flat" over the entire audible range from 20 to 20,000 cycles, inasmuch as it stays within 0.5 db of the center or "reference" line. And since our ears can't hear a change of less than 1 db, we would be able to hear no change in level over the entire range.

Figure 2 shows the frequency response curve of another amplifier. This one has a pretty good frequency response, but

not as good as the one in Fig. 1. It breaks at 10,000 cycles and is down 2 db at 20,000 cycles.

Frequency response is the amplifier characteristic most frequently shown in curve form. Unfortunately, frequency response curves are probably the least important ones we could see on modern amplifiers. This isn't because good frequency response isn't important, since it is. But output transformers—which once seriously limited frequency response—and amplifier circuitry in general have improved so much that all but the most inexpensive amplifiers now boast excellent frequency response. Consequently,

other curves—ones you don't see nearly so often—can be far more revealing about an amplifier's true quality.

Power Response. Curves showing power response, for instance, tell you a lot about an amplifier's performance that you can't learn easily in any other way. A power response curve simply shows how many actual watts of power an amplifier can deliver over its entire frequency range without producing distortion.

Figure 3 is the power response curve for the amplifier whose frequency response is shown in Fig. 1. Again, this is an excellent amplifier. Its maximum power at 20 cycles is down only about 5 watts from full power. It is up to a full

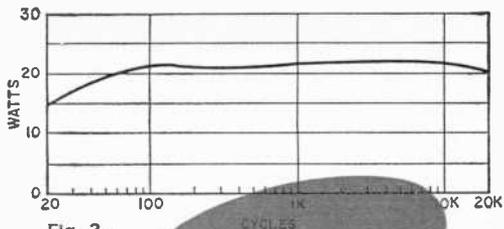


Fig. 3.

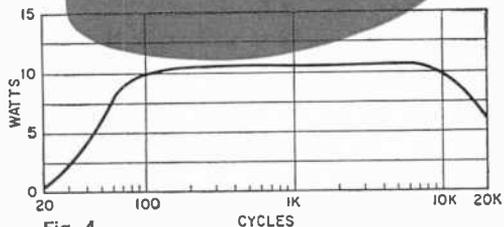


Fig. 4.

20 watts at 50 cycles, and, at 20,000 cycles, the curve has just barely begun to dip.

Figure 4 is the response curve of a considerably less flat but by no means unusual amplifier. As you can see, it doesn't really put out full power below 100 cycles and response begins to fall off pretty sharply above about 8000 cycles. Going back to our friends Sam and Joe, the Fig. 4 amplifier could be the one that Joe bought. Its power output may have been rated the same as Sam's, and both may have had flat frequency response over the audio range. But it's easy to see why Joe's amplifier didn't grind out enough bass to suit him. It just couldn't produce full power below 100 cycles.

Distortion Ratings. Every amplifier specification sheet mentions distortion, usually of two types—harmonic and intermodulation. Although the two types are due to different conditions, they have similar results: more than a tiny amount of either and you get unpleasant sound.

The amazing thing about manufacturers' quoted distortion specifications for many amplifiers—even inexpensive ones—is that they all seem so low. "Less than 1% harmonic and intermodulation

distortion at normal listening levels" is a common claim. But a full picture—such as told by the curves in Fig. 5—is frequently quite different. The "normal listening level" referred to is usually about 1 watt or less. And what happens during climaxes? Just what you think. Distortion rises rapidly, and the music sounds "fuzzy" or otherwise distorted in loud passages.

Figure 5 shows a family of distortion curves for a fairly good 10-watt amplifier. At the 1-watt level, both IM and harmonic distortion—measured at 1000 cycles—are below 1%. But the IM has already climbed to 2% at 3 watts, and to


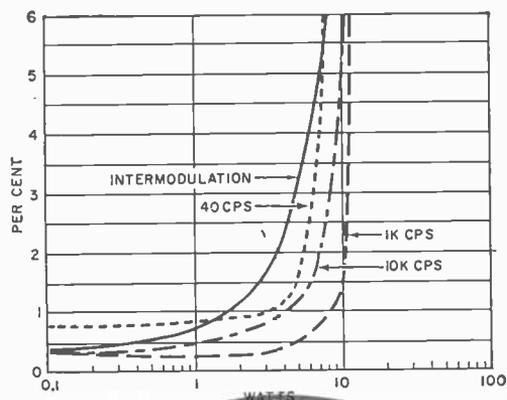


Fig. 5.

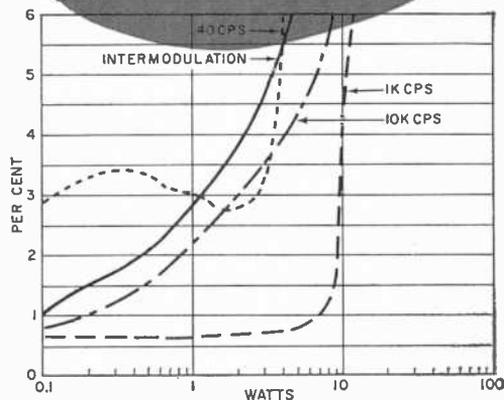

Fig. 5.



6% at 8 watts. Harmonic distortion at 1000 cycles remains low—below 1%—almost to 10 watts. But the figures at 40 and 10,000 cycles again tell a different story.

Figure 6 shows distortion curves for an actual amplifier which is not so good. This is Joe's amplifier, whose power response curve appeared in Fig. 4. The manufacturer probably emphasized the fact that the amplifier's harmonic distortion

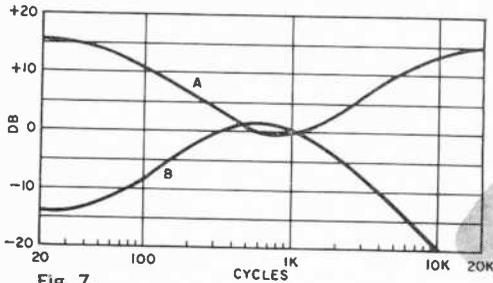


Fig. 7.

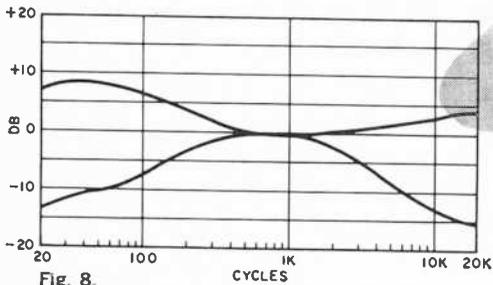


Fig. 8.

tion was below 1% almost all the way to 10 watts. But he probably didn't mention that this was at 1000 cycles only, and that readings at other frequencies were somewhat different, and considerably worse. No wonder Joe felt the fiddles were "fuzzy"—anything over a whisper at high frequencies and distortion begins to soar.

Tone Controls. Curves can tell you quite a lot about the way your tone controls work, too. Figure 7 shows what happens to an amplifier's frequency response with the two tone controls—bass and treble—turned to their extreme positions. When the bass control is turned all the way up, bass response is boosted 16 db at 20 cycles (curve A). With the bass all the way down, response is down 14 db

(curve B). About 15 db of high boost and 29 db of high attenuation can be accomplished with the treble control.

Figure 8 shows the response characteristics of another amplifier with far less effective controls.

You may at times see a so-called

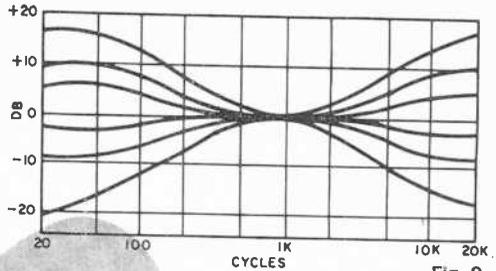


Fig. 9.


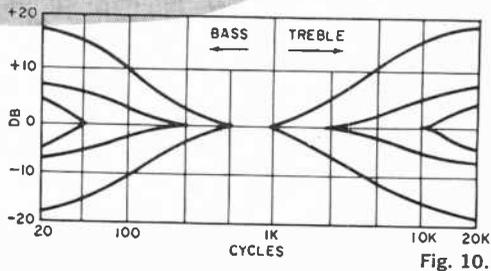


Fig. 10.

"family" of tone control curves, and these can be even more revealing. In Fig. 9 is a family of curves of the conventional "losser" type of tone control, similar to those we have just seen. Three boost and three attenuate curves are shown for each control, that is, three different amounts of bass boost, three of bass attenuation, etc.

Figure 10 is another family with three curves for each function, but note the striking difference from Fig. 9. This is the response characteristic of the famous Baxandall tone control you have probably heard about.

(Continued on page 118)

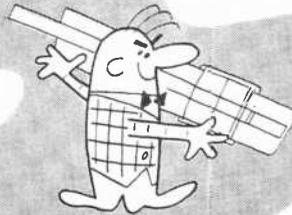

Across the Ham Bands

By
HERB S. BRIER
W9EGQ

TROUBLE-SHOOTING HAM EQUIPMENT

WHAT would you do if your ham transmitter or receiver suddenly stopped working? Among other possibilities, you could send it back to the manufacturer or the dealer from whom you purchased it—after receiving shipping instructions; you could enlist the aid of a local ham expert; or you could repair it yourself.


If the gear is still under guarantee and the trouble seems to be of a major nature, the first course might be the wisest one. However, most ham equipment failures are the result of the breakdown of a single component, such as a tube, capacitor, or a resistor.

Do It Yourself. If you have the instruction manuals and a good volt-ohmmeter, you should be able to run down most causes of trouble in your ham equipment yourself. A tube tester or a set of replacement tubes known to be good is also helpful.

Suppose, for example, that your transmitter has stopped working. You know that the rig is getting power, because its tubes light or it blows fuses. You have tested the tubes or have substituted others that you know to be good. What do you do next?

First, read the entire instruction manual to refresh your memory as to how the equipment is supposed to work and the function of each control. Then locate the circuit diagram, the parts list, and the illustrations showing the position of the various parts. Also, locate the tables showing the resistances and voltages to be expected at specified test points.

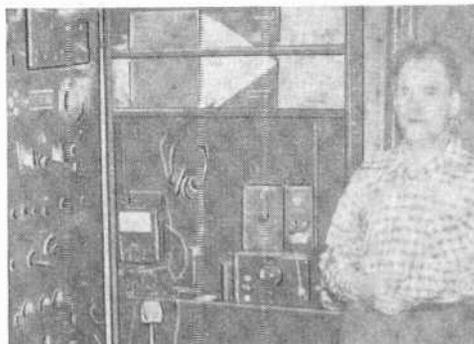Power-Off Tests. With these preliminaries out of the way, pull out the power plug and remove the transmitter from



Ham of the Month

R. B. Smith, VE3CKG, Kingston, Ontario, Canada, became a ham three years ago shortly after a friend lent him a short-wave receiver. "Smitty" operates on all ham bands from 80 to 10 meters from his home and works 75-meter phone from his automobile. He has worked all Canadian provinces and most of the United States, plus many foreign countries. However, he prefers an interesting chat with a local ham station to a hello-and-goodby contact with a rare DX ham.

Smitty likes to build his own ham equipment or to modify war-surplus gear to his needs. His home station is housed in the metal cabinet from a soft-drink dispenser to which he has added shelves to support his equipment. When he is not operating his station, Smitty closes and locks the cabinet door. In this way, he prevents unauthorized persons from tampering with the equipment and either damaging it or injuring themselves.

Interestingly enough, VE3CKG's home-transmitter power is 50 to 75 watts, while his mobile transmitter power is 100 watts. He powers the mobile transmitter from a 117-volt a.c. generator which he constructed from a Ford Model-A "powerhouse"; the generator is driven from the automobile fan belt.

By profession, Smitty is an Area Electrical Inspector for the Ontario Hydro-Electric Power Commission. He is also Activities Chairman for the Kingston Amateur Radio Club.

cabinet. Set it on end, and blow out loose dirt and dust. Then inspect the chassis for obvious troubles, such as broken or burned-out components, dangling wires, and bits of wire or solder lodged between any socket terminals or lugs.

Now, open the instruction manual to the resistance table, and systematically measure the resistances at the specified test points. Compare your measured values with those listed in the proper table. When you find a resistance materially different from the specified one, carefully test all components connected to that point.

Then measure the resistance of all of the capacitors. If a resistance is low, replace the capacitor. A good paper, ceramic, or mica capacitor will show a resistance measured in megohms, and a good electrolytic capacitor will measure over 1/2-megohm after a minute or two.

When you unsolder leads to make measurements, replace them at once so you don't find yourself with a maze of disconnected wires and no idea where they belong. And after replacing a shorted component, check the associated components—the short may have damaged them, as well.

Higher-than-normal resistance readings also call for measuring the resistance of components connected to the test point in question. Compare your measurements with the values indicated in the circuit diagram and parts list. Chokes, coils, and transformer windings usually have quite low resistances.

Power-On Tests. Some defects do not reveal themselves until power is applied. Therefore, if resistance measurements do not turn up anything suspicious, apply power to the transmitter and go through the measuring process again. But this time, measure voltages, and compare them with the values shown in the instruction manual voltage chart.

Be extremely careful while making voltage measurements to avoid a painful or even fatal shock. Also, keep a wary eye open for smoke or other indications


that components are being overheated.

The above procedures will not enable you to find every cause of transmitter and receiver troubles, but they will do the trick most of the time. Try them and see.

TWO-TUBE SCREEN MODULATOR

Ken Kendall, K9EXD, designed and built the two-tube screen modulator at right for his WRL Globe Chief 90A transmitter, but it can be used with any transmitter draining up to 90 watts input to the final. This power input results in a solid 30 watts of well-modulated r.f. power to the antenna.

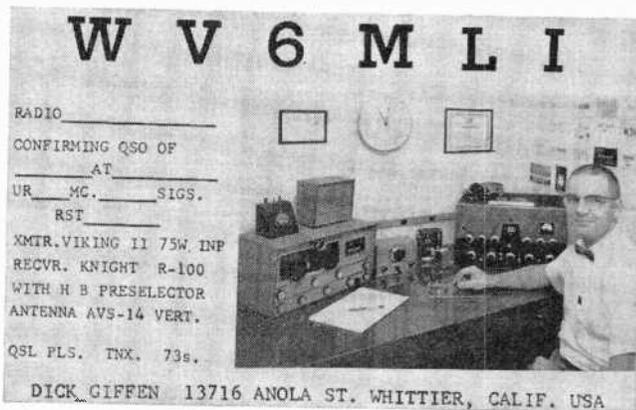Construction. Ken built the modulator on the chassis of his Globe Chief. The modulator is small enough to fit some-




Personalized QSL card used by WV6MLI, who has worked 43 states.

where on the chassis of most transmitters, but it can also be constructed in a 4" x 5" x 3" utility cabinet with attached chassis (Bud C-1795 or equivalent). If you use the cabinet, terminate the external connections in an octal plug and mount a matching socket on the transmitter.

To build the modulator in the "Chief," mount the 12AT7 (V1) and the 12AU7 (V2) tube sockets and the panel controls in the approximate positions shown in the photograph. Locate microphone connector J1, gain control R2, and phone/c.w. switch S1, one above the other, on the right side of the 90A's front panel. Then mount a 5-lug terminal strip (TS1) under the chassis about 1 1/2" in front of



(Continued on page 120)

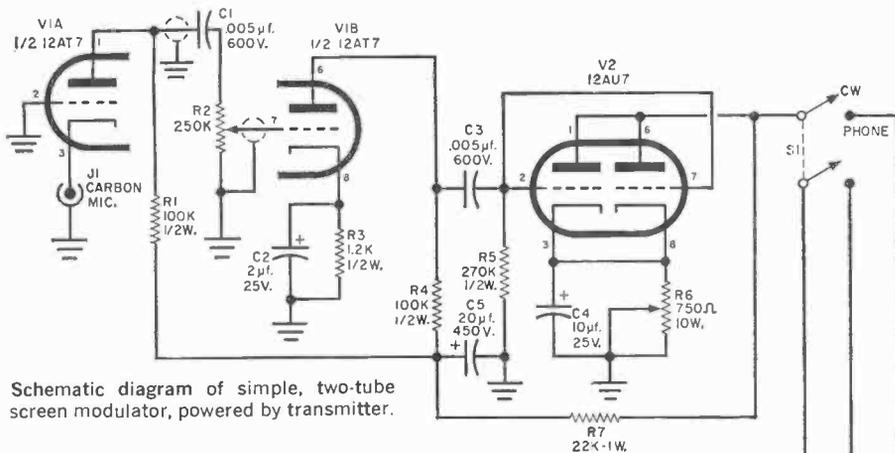

Schematic diagram of simple, two-tube screen modulator, powered by transmitter.

PARTS LIST

- C1, C3—0.005- μ f., 600-volt disc capacitor
- C2—2- μ f., 25-volt electrolytic capacitor
- C4—10- μ f., 25-volt electrolytic capacitor
- C5—20- μ f., 450-volt electrolytic capacitor
- J1—Microphone connector
- R1, R4—100,000-ohm, $\frac{1}{2}$ -watt resistor
- R2—250,000-ohm, audio taper potentiometer
- R3—1200-ohm, $\frac{1}{2}$ -watt resistor
- R5—270,000-ohm, $\frac{1}{2}$ -watt resistor
- R6—750-ohm, 10-watt adjustable resistor (set for approximately 500 ohms—see text)
- R7—22,000-ohm, 1-watt resistor
- S1—D.p.s.t. toggle switch
- TS1—Five-lug terminal strip
- V1—12AT7 tube
- V2—12AU7 tube
- 1—4" x 5" x 3" chassis box (optional—see text)
- Misc.—Hardware, tube sockets, etc.

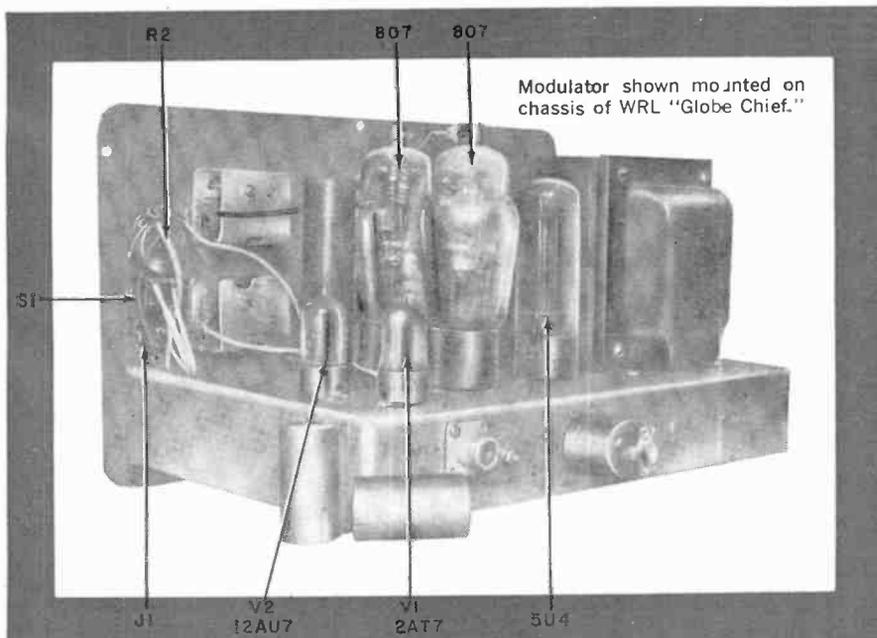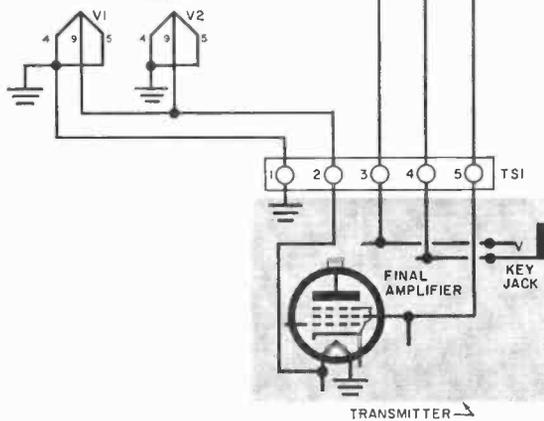

Protect Your Car with this... BURGLAR ALARM SYSTEM

By WILLIAM C. LEWIS

AT ONE TIME OR another, most automobile owners have wondered whether or not the contents of their cars—or even the cars themselves—were safe from theft. Fortunately, it's not too difficult to install a burglar alarm in an automobile if you are handy with tools.

The cost of such a system depends on the type of vehicle involved and the degree of protection desired, but the minimum is generally around \$12 to \$15.




The heart of the system is s.p.s.t. relay *K1* (see diagram) which has one purpose: it prevents the burglar from disabling the alarm. Once energized, it locks itself on so that it cannot be shut off except with a key. Select either a 6- or a 12-volt relay—to match your car's electrical system.

Six s.p.s.t. switches were installed by

the author—on the hood, the trunk, and on all four doors. (The windows are not protected—a potential thief generally breaks a window, then unlocks and opens a door.) If desired, you can even install mercury switches to trigger the alarm if the car moves (in case the car is rolled away), or if a window is broken to admit the thief without opening the door. Simply wire any additional switches in parallel with *S1* through *S6*.

Key-operated switch *S7* will turn the alarm on and off. It should be a good-quality s.p.s.t. switch and have a key that is removable in both the "on" and "off" positions. The cheaper switches generally have simple locks and are easier to "pick."

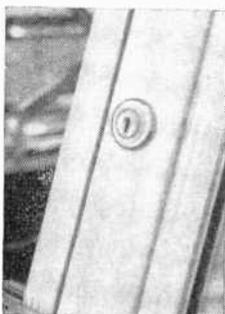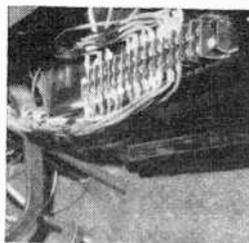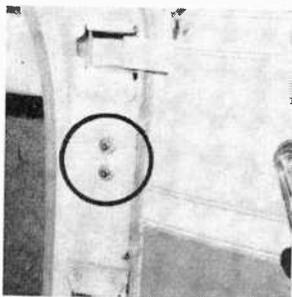Mount on-off switch *S7* in a convenient location, but not where it will fill up



Mounting details of the alarm system are shown in these photographs. Door switch is mounted on frame just below dome-light switch (at left, above). Terminal strip for alarm and accessory wiring is mounted below the dash (center). Alarm siren (at right, above) is located behind the radiator under the hood. The key-operated switch that controls the system (below, left) fits neatly on the doorpost.

HOW IT WORKS

An alarm—siren or auto horn—is connected across the coil of relay *K1*. When a car door is opened, one of the sensing switches (*S1* to *S6*) closes and lights pilot lamp *PL1*. With key-operated switch *S7* closed, *K1* energizes and locks up on its own contacts. With *K1* locked up, the alarm sounds until key-operated switch *S7* is opened. Opening *S7* de-energizes *K1*, and the alarm is silenced.



Pilot lamp *PL1* lights when any sensing switch is closed; the setting of *S7* does not affect its operation. When *PL1* is not lit, all sensing switches are open and the alarm is ready for operation.

with water and freeze during the winter months.

The actual alarm should be loud and have a distinctive sound that you can easily recognize; the cheapest alarm is the existing auto horn. A separate horn or siren can be used, but this boosts the cost somewhat.

As the door switches are operated rather frequently, there is a chance of their failing. There is also a chance that a short will occur in the system wiring and blow a fuse. To avoid the possibility of this happening without the driver knowing about it, a pilot lamp (PL1) is used. It should light whenever any of the doors (or trunk or hood) are opened. If it doesn't light for one door but does for another, check the switch and wiring on the first door. If it doesn't light at all, check fuse F1.

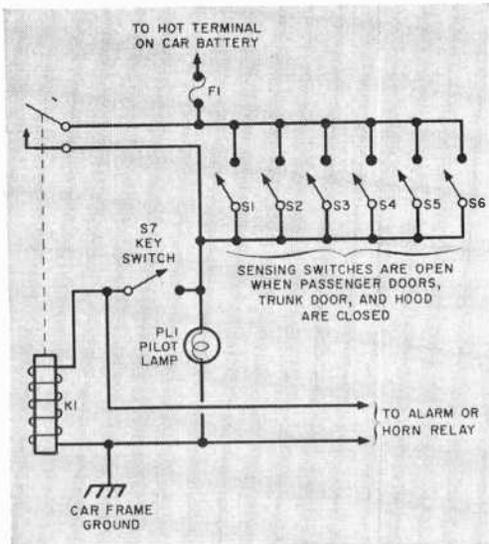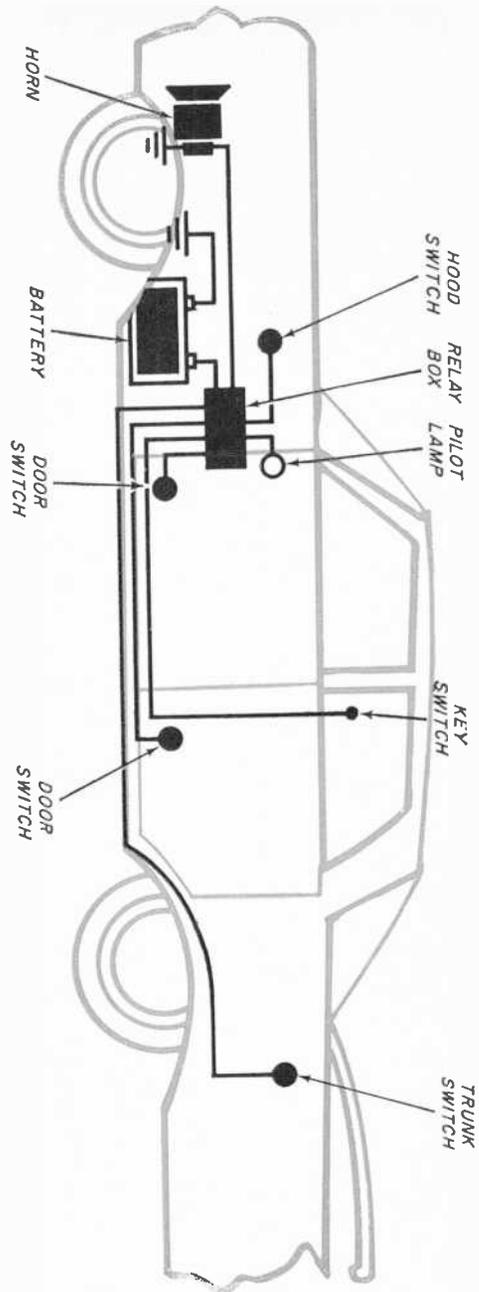
The relay box in the author's system is mounted under the dash along with a terminal strip for the alarm system and accessory wiring. Dress the wiring into existing channels and tunnels to prevent excessive wear and the possibility of a short circuit. The fuse should have a rating high enough to handle the relay, pilot lamp, and alarm. -30-



The alarm operates and relay K1 locks up when both key-operated switch S7 and any sensing switch (S1 to S6) are closed. Sketch at right, above, shows suggested spots for placing sensing switches.

PARTS LIST

- F1—Fuse and inline fuse holder—see text
- K1—S.p.s.t. 6- or 12-volt coil relay (Potter & Brumfield Type AIR or equivalent)
- PL1—6- or 12-volt pilot lamp (No. 47 for 6 volts, No. 1488 for 12 volts) and socket assembly (Dialco No. 111 or equivalent)
- S1-S6—S.p.s.t., normally closed, push-button switch
- S7—S.p.s.t. key-operated switch (J. C. Whitney No. 74437 or equivalent)
- Misc.—Terminal strip, relay box, etc.

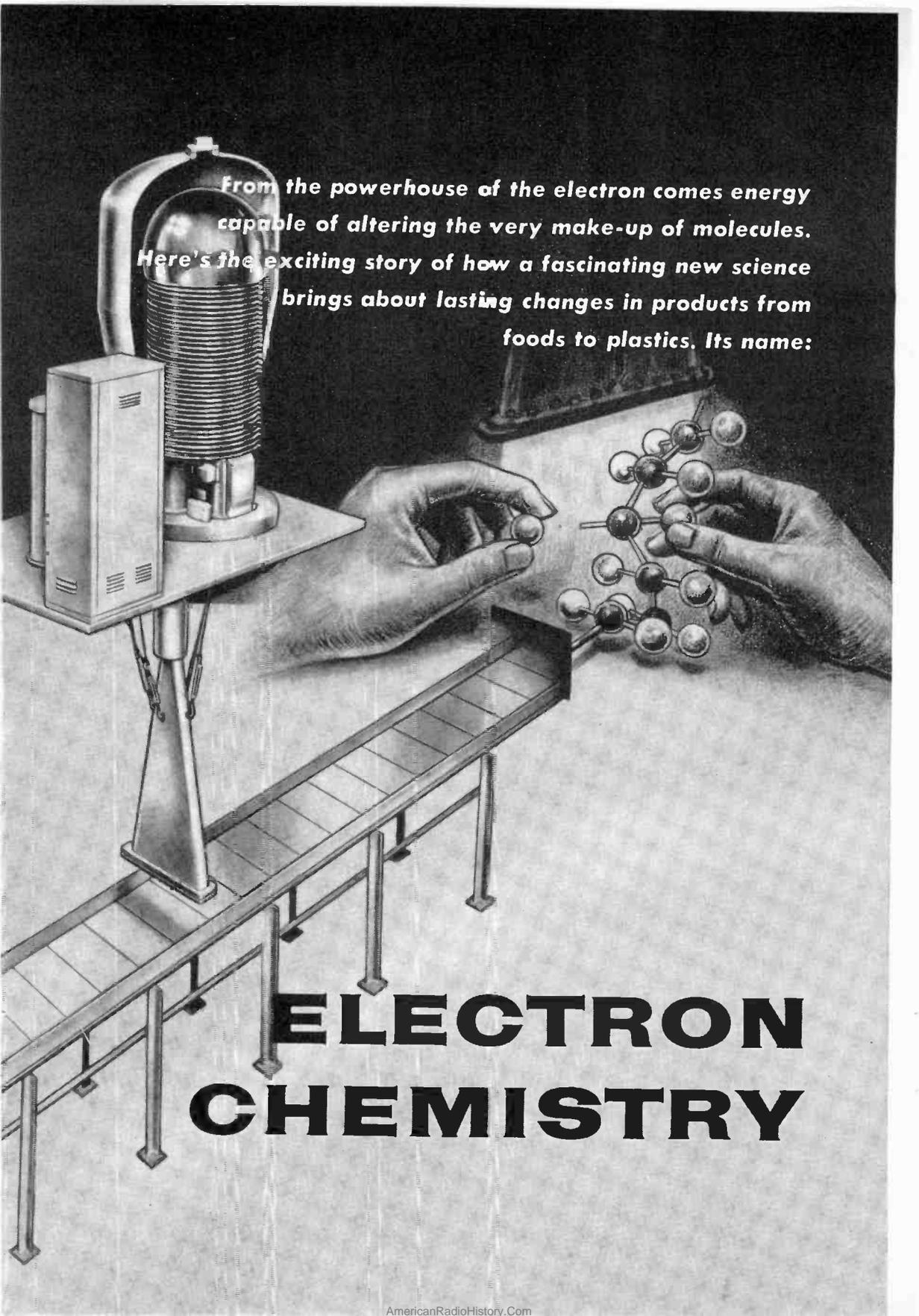

*from the powerhouse of the electron comes energy
capable of altering the very make-up of molecules.
Here's the exciting story of how a fascinating new science
brings about lasting changes in products from
foods to plastics. Its name:*

ELECTRON CHEMISTRY

←High Voltage Engrg. Corp.

READY to irradiate polyethylene with two million volts of electron energy," announced the radiation chemist.

We nodded, and felt strangely excited as we stood in the control room adjoining the thick, concrete-walled irradiation facility. Inside those walls was a two-million-volt electron beam generator.

"Mood music" for the setting was furnished by the whine of a motor-generator set and the sibilant *sh-h-h* of a tube-window cooling blower. These sounds were augmented with a host of visual effects—meters, knobs, and dials galore, bearing such labels as *Megavolts*, *Milhamperes*, *Beam Position*, and *Focus*.

"Look through the window," instructed the radiation chemist. "You'll see something interesting."

Directly behind the radiation-resistant window was a mirror, one of several strategically positioned to provide an image of the irradiation process.

"Beautiful!" we exclaimed at the sight of three polyethylene plastic bottles, all bathed in an eerie blue fluorescence. Directly above the plastic bottles was the funnel-shaped anode of the huge electron-beam generator, looking something like a king-sized water spray attachment.

After the chemist had injected a short "spray" of high-energy electrons, we entered the test cell—but only after harmful ozone had been cleared away by a powerful exhaust system. We picked up a bottle and then—on second thought—dropped it as though it were a lit fire-cracker.

The chemist smiled. "Don't worry—there's no chance of radioactivity. All radiation ceases when the machine is shut off."

"Doesn't seem to be any change," we remarked, turning the bottle over and over cautiously. Again the amused smile—the radiation chemist was obviously enjoying his dramatic role.


"You'll see," he said prophetically, placing the three irradiated bottles along with three non-irradiated bottles in an autoclave steam sterilizer.

We soon stood in awe at the amazing result. After twenty minutes' subjection to a temperature of 250°F, the non-irradiated polyethylene bottles had melted to shapeless blobs. But the irradiated bottles stood proudly erect, unaffected by the heat.

We had just seen one practical application of a revolutionary new science—electron chemistry.

High-Energy Electrons. Scientists define electron chemistry as the use of accelerated high-energy electrons to alter or change the fundamental structure of


General Electric

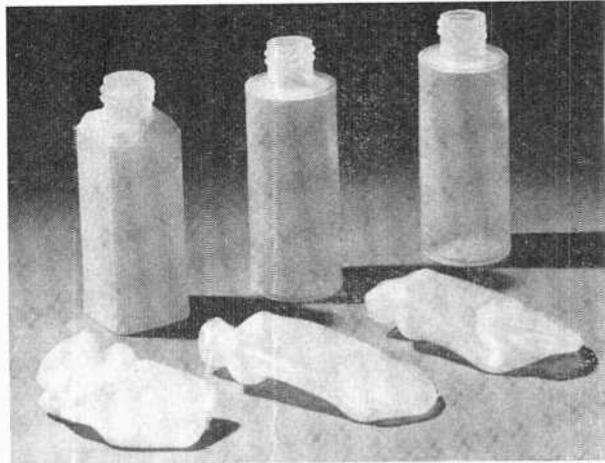

Irradiated polyethylene bottles (top), comprised of "cross-linked" molecules, can withstand prolonged exposure to temperatures as high as 250° F. Non-irradiated bottles (bottom) wilt to shapeless blobs.

matter to create new or improve existing products.

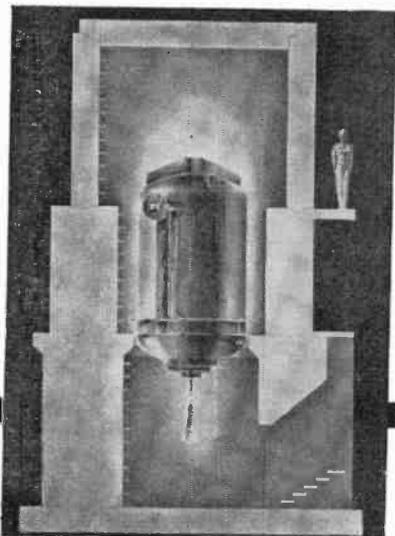This new science uses none of the conventional paraphernalia of chemistry. Absent are acids, bases, salts, and catalysts. Nor are beakers, retorts, or pressure vessels employed. The electron is the "reagent." It was, for example, the high-energy electrons that made a stronger "unmeltable" plastic by altering



Mammoth electron beam generator (left), produced by General Electric, delivers some 3.5 million electron volts. Electrons emerge from thin titanium window at bottom of anode (funnel-shaped structure with cooling fins, above).

the molecular structure of the three polyethylene bottles.

These electrons are, in kind, the same tiny, negatively charged particles which make possible all types of electronic equipment. But here they are "beefed up"—they have "muscle." Traveling at nearly the speed of light, they boast energies in the millions of electron volts.

To understand why high-energy electrons can exert profound chemical changes within a substance, consider, for example, how "weak" the electrons are that bind or hold together atoms and molecules—a feeble ten electron volts, puny energy indeed compared to the one to ten *million* electron-volt "muscle-men" of an electron accelerator!


No wonder these penetrating high-energy electrons can shake up the relatively anemic binding power of electrons in molecules. Naturally, something has to happen when a powerful electrical force meets a small one. In this case, the big guy wins, and ionization or dissociation of the molecule is a result.

Polymerization. What happens is that the molecule takes on some of the energy of the powerful bombarding electron and becomes so disturbed that it throws off a planetary electron. The electron-deficient molecule is now an ion carrying a positive charge of electricity.

These wandering ions and other fragments of the irradiated substance enter into reactions with molecules that were not affected by the electron radiation. The "snipped-off" pieces speedily recombine to form new molecules with new properties.


This "snipping off" of atomic and mole-

General Electric photos


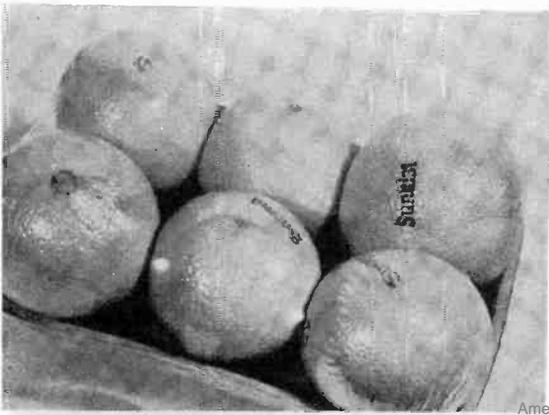


Packaging film made by electron-irradiating low-density polyethylene is clear, strong, and glossy. A blast of hot air shrinks the film to make an attractive, skin-tight wrap that prevents fruit from shifting or being bruised.

POPULAR ELECTRONICS

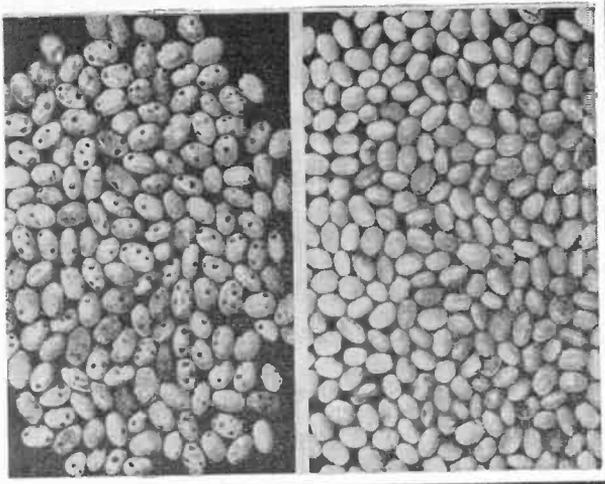

Death rays for food-destroying organisms, high-speed electrons can help preserve a variety of foods. Both bean samples at left, for example, were inoculated with bean weevils, but only the irradiated sample (directly at left) resisted the insects. Applied to potatoes and onions, electrons can inhibit sprouting and greatly increase storage life. Below, left, irradiated bread remains fresh three months after treatment; frankfurters (below, right) look "good enough to eat" 92 days after irradiation.

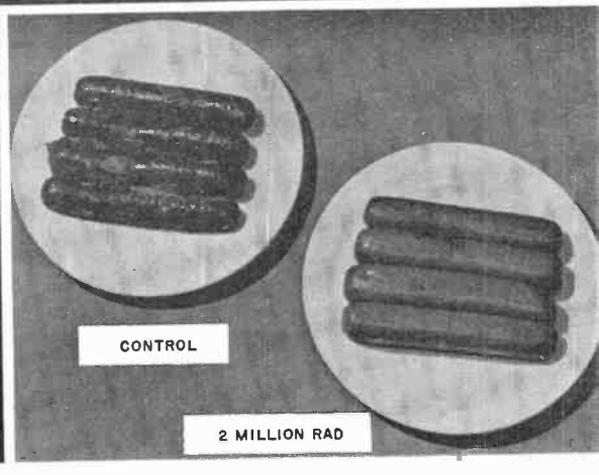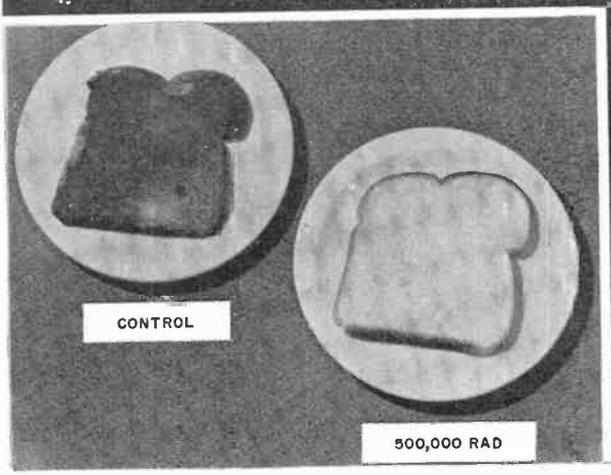


cular parts is often termed "tailoring" by polymer chemists. Polymers, if your high-school chemistry is a bit rusty, are giant molecules composed of thousands of so-called monomer units, the starting substance. In his molecular "tailoring," the radiation chemist uses high-energy electrons to "scissor-off" "parts" of molecules. These "parts" then speedily reassemble to form a new "suit."

Making giant molecules out of little ones is called polymerization. High-energy electrons can polymerize small monomers, such as ethylene gas, into giant polymers—polyethylene in this instance—without chemical assistance. And there are many polymers—rubbers, plastics, glue, and cellulose are but a few examples.

Cross-Linking. If we examine the structure of polyethylene, we can see how "cross-linking" strengthens the substance. Polyethylene is composed of long "chains" of molecules in a random configuration looking much like wet spaghetti. But by "cross-linking" the "chains," the molecules are joined together into a three-dimensional network, effectively bringing order out of chaos and greatly strengthening the polyethylene.

To put it more technically, hydrogen atoms are knocked out of polymer chains or branches, permitting cross-linking or tying of the adjacent chains into one super molecule. In this way, irradiation furnishes the "electronic glue" that

(Continued on page 112)

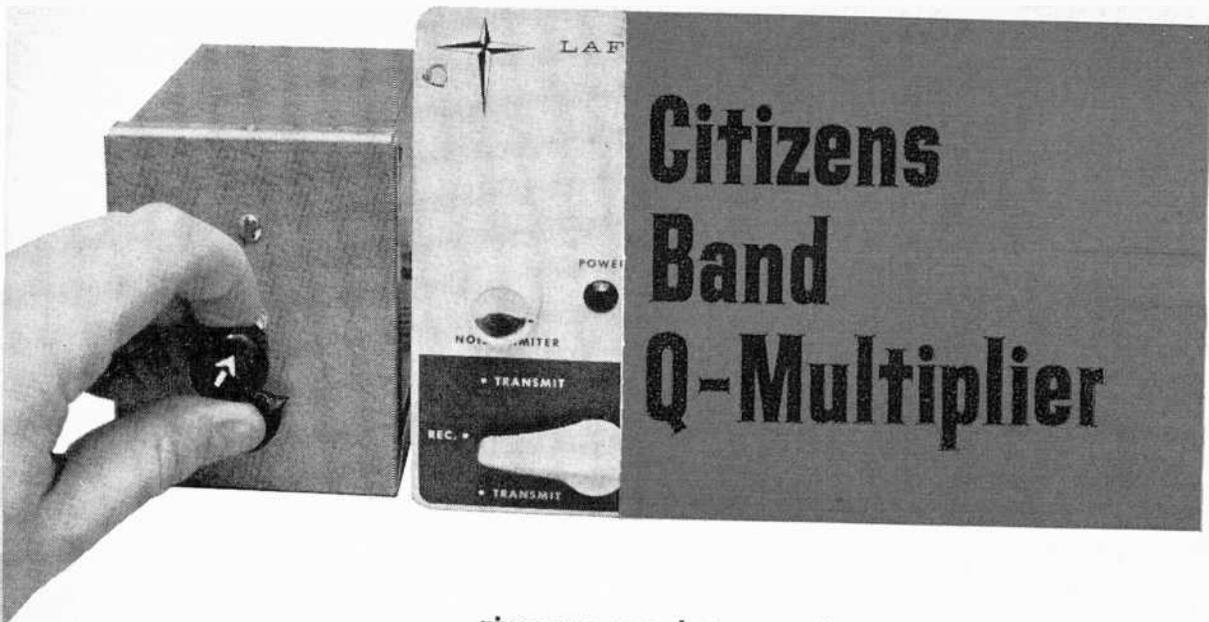

Citizens Band Q-Multiplier

- ... gives any superhet razor-sharp selectivity
- ... cuts down on noise and static pickup

By DONALD L. STONER, 11W1507

CITIZENS BANDERS, hams, or SWL's plagued by interference on the crowded bands can pep up their receivers with an easy-to-build Q-Multiplier.* The unit improves a set's selectivity by narrowing its i.f. bandpass, thus eliminating interfering stations and reducing static and noise pickup.

Since the Q-Multiplier operates on the receiver's i.f. frequency, it can be used with any superhet receiver, including CB, ham, or SWL sets, regardless of its tuning range. However, the receiver must have an i.f. near 455 kc. or between 1300 and 1800 kc.

Completely self-contained, the Q-Multiplier has its own a.c. power supply and requires only a two-wire connection to the receiver. Operation is simple, too; using only two controls, you select the desired station and reject the ones you don't want.

As for construction, there are no expensive parts; with all parts purchased



new, you can build the unit in an evening or so for around \$10.00. The wiring is not critical.

Construction. Build the unit following the layout shown in the pictorial diagram. The tube socket, tuning coil $L1$, and potentiometer $R4$ are fastened to the front panel of the box; however, each requires soldering or modification before mounting.

Bend out the solder lugs on the tube socket before fastening it to the front panel. Then solder a bare wire jumper through the socket's ground sleeve, pin 4, and the socket's mounting flange. Mount the socket so that pins 1 and 7 are pointing to the left when viewed from the front of the box. The socket is fastened to the box by soldering its ground sleeve to a machine screw mounted on the front panel with a nut and lock washer.

If the Q-Multiplier is to be used with a receiver having a 1300- to 1800-kc. i.f., remove 100 turns of wire from the winding of tuning coil $L1$, which is a Miller 2007 ferrite loopstick. For sets with 455-

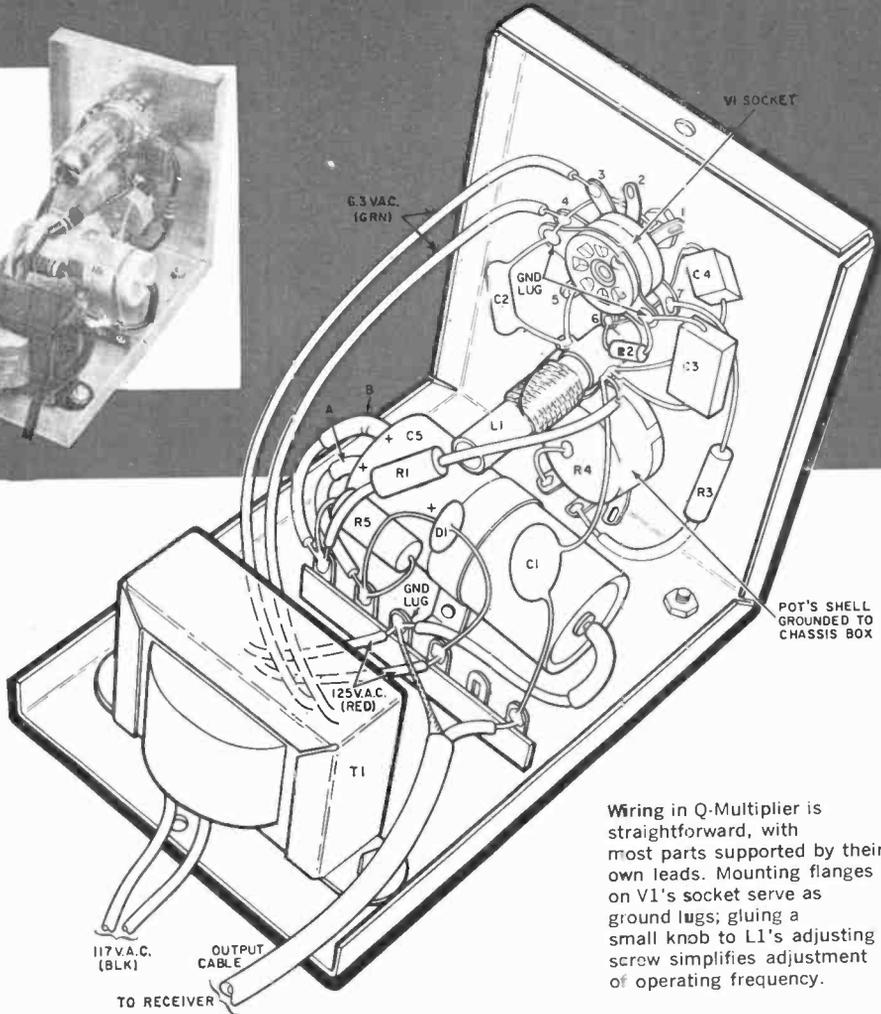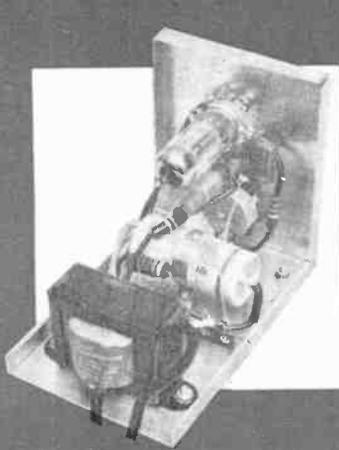
*Developed by O. G. Villard, Jr., the original Q-Multiplier was first described in the engineering monthly "Electronics" in April, 1952.




Wiring in Q-Multiplier is straightforward, with most parts supported by their own leads. Mounting flanges on V1's socket serve as ground lugs; gluing a small knob to L1's adjusting screw simplifies adjustment of operating frequency.

PARTS LIST

- C1—0.005- μ f., 500-volt ceramic disc capacitor
- C2—100- μ f., 500-volt mica capacitor—see text
- C3—500- μ f., 500-volt mica capacitor—see text
- C4—500- μ f., 500-volt mica capacitor
- C5a/C5b—40/40 μ f., 150-volt electrolytic capacitor
- D1—Silicon diode, 200 P.I.V., 200 ma.
- L1—Ferrite loopstick (Miller 2007—see text)
- R1—10,000-ohm, $\frac{1}{2}$ -watt resistor
- R2—2.2-megohm, $\frac{1}{2}$ -watt resistor
- R3—2200-ohm, $\frac{1}{2}$ -watt resistor
- R4—5000-ohm potentiometer, linear taper (Mallory U-14 or equivalent)
- R5—4700-ohm, 1-watt resistor
- T1—Power transformer; 117-volt primary; 125-volt, 15-ma., and 6.3-volt, 0.6-amp secondaries
- V1—6C4 tube
- 1—5" x 4" x 3" aluminum box (LMB 435 or equivalent)
- Misc.—Hardware, R $\frac{5}{8}$ -U coaxial cable, 7-pin tube socket, etc.

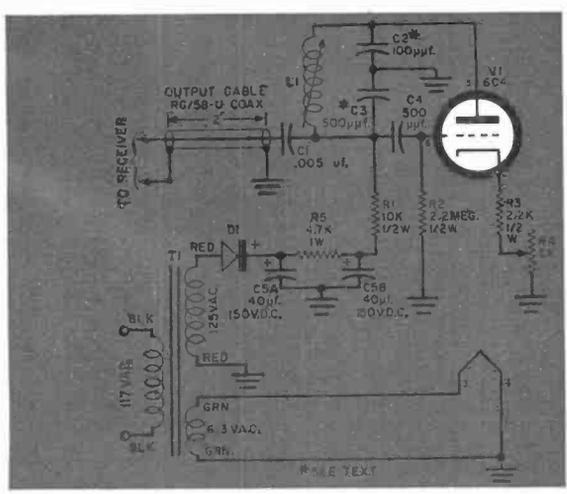

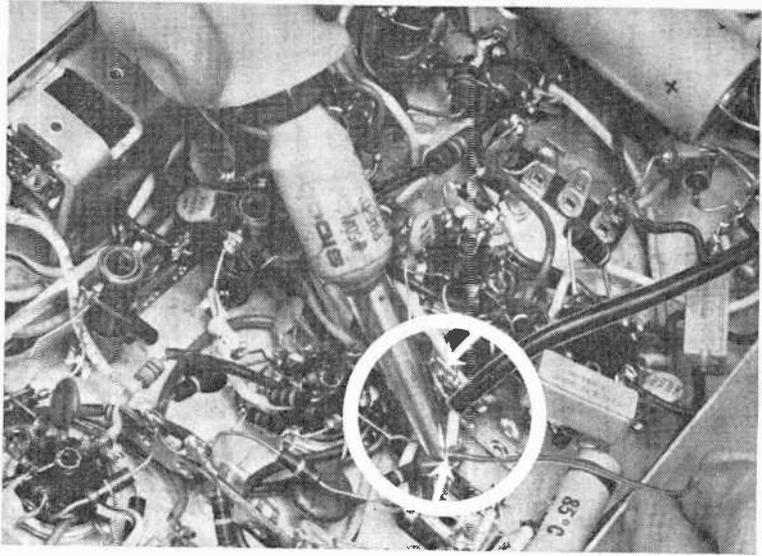Hot lead of Q-Multiplier's output cable can be connected to plate of first i.f. tube at i.f. transformer (lower arrow in photo). Cable's shield should be soldered to ground lug nearby (upper arrow).



kc. i.f.'s, do not modify $L1$, but change capacitors $C2$ and $C3$ to 680 $\mu\text{f.}$ and .0025 $\mu\text{f.}$, respectively.

Ground one lug of potentiometer $R4$ to the shell of the control with a short bare-wire jumper, as shown in the pictorial diagram. Then mount the control.

The remaining wiring is straightforward. However, take care to watch polarities on diode $D1$ and filter capacitor $C5$. Note that the output cable shown on the schematic is a 2' length of RG-58/U coaxial cable.

Connection and Adjustment. If you build the Q-Multiplier to operate on 455 kc., it should be adjusted when you connect it to the receiver. The 1300- to 1800-kc. model requires a preliminary adjustment before being connected. To make the preliminary adjustment, tune the receiver or any broadcast-band set to approximately 1600 kc., and place the hot lead of the Q-Multiplier's output cable near the receiver's antenna. Set selectivity control $R4$ to its minimum resistance position and adjust tuning coil $L1$ until you hear a whistle in the receiver's speaker.

Before hooking up either model to your set, turn off both the receiver and the Q-Multiplier. Then connect the hot lead of the output cable to the plate of the first i.f. tube in the receiver, and solder the output cable's shield to the nearest ground point. If you use the Q-Multiplier with a dual conversion superhet, you must connect the hot lead to the plate

of the i.f. tube which operates in the frequency range of the Q-Multiplier.

Now power the receiver and Q-Multiplier, and set selectivity control $R4$ to its maximum resistance position; this is the point where the Q-Multiplier does not oscillate. When you tune in a station on the receiver in the normal manner, you should notice a considerable reduction in the volume of the received station.

To adjust the 455-kc. Q-Multiplier and to touch up the tuning on the 1300- to 1800-kc. model, set $R4$ to its minimum resistance position. Adjust $L1$ until a strong whistle is heard from the speaker. Now reset $R4$ to maximum resistance. For maximum output, you can repeak the plate tuning adjustment on the first i.f. transformer; a quarter turn in either direction is all that is needed.

Operation. Starting with $R4$ at maximum resistance, slowly decrease the resistance; you will find that the volume of the received station starts to increase as you do so. Soon the volume will increase noticeably, and voice signals will begin to sound rather bassy. Any further decrease in $R4$'s resistance will cause the Q-Multiplier to oscillate and the received station will be blotted out.

Back off $R4$ until the oscillation just stops; this is the most selective point in $R4$'s range. Now adjust both $L1$ and $R4$ slightly, for best results. Whenever you tune in a new station, both of these controls should be readjusted. -50-

On the Citizens Band



By TOM KNEITEL, 2W1965

I'M beginning to feel that a hefty percentage of CB'ers can be sorted into the following categories:

- A. Those who have never read Part 19 of the FCC Rules
- B. Those who have read it, but can't read well
- C. Those who have read it, but couldn't understand it
- D. Those who understood it, but don't give a hoot

Now, your personal opinion of Part 19 is your business—no one will say that you haven't a right to that opinion. And don't think that an IBM machine writes this column every month—I also have my own opinion of Part 19. It may or may not agree with yours. But that's not the point.

You might not like traffic lights but when one turns red you either bring the Model T to a halt or take your chances with getting your lumps from the law. And so it is, dear friends, with CB.

There is no possible excuse, at this stage of the game, for so much flagrant disregard of FCC regulations. And I especially aim a bony accusing finger at you guys with the low call signs who have been around for a while and *do* know better.

No matter how boobish you may think the FCC is (and you evidently do if you are openly ignoring their rules), you can't really think they don't know that your "test" call is a thinly veiled "CQ." You can't really think the FCC monitor is smiling and saying, "Boy, that Elmer is a wonderful CB'er—keeps testing his rig to see if it's operating properly. Guess he's got a licensed technician with him in case the transmitter does need some adjustment."

This goes for playing music over the air, working "skip" DX, jamming with a dead carrier because someone had the nerve to use "your" channel, interjecting

"clever" remarks into other stations' traffic, and other assorted megacycle mayhem common to CB.

Unless you wiseacres cut out the monkeyshines, you're going to have only yourselves to blame when the Day of Reckoning comes and you're sitting with an unlicensed "wasted investment" CB rig. I'd also suggest that good-natured parents who bought "Junior" a CB rig and then obtained "his" license in their own name, take a good look at what "Jr." might be doing to their good name in the community.

Saw some nice "Scotchlite" reflective call letters on a mobile unit the other day. They looked so neat that we asked the CB'er for the scoop on them.

The letters are two inches high and white with a black border to reflect light at night. Each set costs \$1.50, and for



50 cents more you can also get "USA" in reflective letters. If you order two call-letter sets, the "USA" is thrown in at no extra cost. The distributor is Allied-International, CBC Index Div., P. O. Box 112, Prince Station, New York 12, N. Y. Allow two weeks for delivery.

CB for the birds? It has gone to the Portland (Oregon) Zoo, that's for sure. The zoo operates a network of Raytheon

CB rigs between their Tom Thumb kiddie railroad station and the rolling stock of the line (a miniature streamliner and a miniature antique steam train). Just like the for-real railroads, the Tom Thumb Line uses two-way radio to dispatch trains and maintain proper schedules. The trains take the kiddies on a tour through the zoo over a four-mile stretch of track.

We goofed in the January column when we reported that the "Jersey 5 Watters" were soon to become an independent affiliate of another CB club. Jack Orlovsky of the Jersey 5 Watters called us to set the record straight. His club has made no plans to date to team up with any other organization. By the way, if you live out Jersey way and would like to join an active CB club, write to the Jersey 5 Watters, 113 Dailey Ave., Hillside, N. J.

Speaking of clubs, newspapers were received here recently from Cleveland's Hillcrest Citi-Band Club and The Southern California 11 Meter League. Many of the advantages of belonging to a club which takes the trouble to publish a club paper are borne out by these two papers. Technical hints, news of club activities and services, sell and swap items, personal items, etc., are to be found in both. And the Cleveland club has a strong anti-nonsense on-the-air policy which we certainly commend.

A real swingin' club in Syracuse, N. Y., has the interesting name "MCEU," meaning Mobile Civil Emergency Unit. Their fine 14-page newspaper contains information on each of their various chapters around New York State. A look through its pages shows that they aren't

sitting around rag-chewing on the band, but instead are giving the members quite a bit of service for their dues. For instance, they have design contests, supervised "drag" races, advice on the use of CB equipment, barbecues, picnics, etc. MCEU members can be identified by the snazzy window sticker shown here, —most are in the 20W call area. Contact 20W1267 for details.

Up in Holyoke, Mass., CB'ers belong to the Pioneer Valley Five Watters, whose 7-page paper gives details of their PVFW Emergency Net. Write 1W6903 if you're interested.

The Chicago CB gang receives club information from the nifty bulletin of the Citizens Radio League, Inc. The CRL makes good use of humor in its bulletin (and we got a big kick out of it, incidentally) as well as providing interesting information on members and doings. For more data on the CRL, get in touch with 18W5847.

Quite a few readers have written to this column about the taxi cab dispatcher on Channel 11 that goes on hour after hour and never signs a call. Unbeknownst to most CB'ers in the east, this station is audible through the entire midwest and Gulf Coast. It has a woman dispatcher announcing such places as Government Gate, Happy Valley, North Street, Mount Hill, etc. Our Editor, 2W1665, has just returned from Washington and tells me that the station is in Bermuda! It is legit, since the 11-meter band is assigned to such services outside of the U.S.A.


Here's some happy news about the work CB'ers are doing in conjunction with Boy Scouting.

Thirty-two CB mobile units directed a convoy of 550 cars and buses bringing 10,000 Scouts to a Boy Scout powwow in Ottawa, Ill. The whole operation took only 30 minutes, after which the mobile units stayed in operation for the entire three days of the shindig.

Using two control centers on Channel 16, the messages became so numerous that it took two secretaries to log them. By the end of the operation, over 2500 messages had been handled, including eight emergency calls. This traffic-handling involved 1100 man-hours.

The participating CB'ers were members of the Ottawa Five Watters and the Utica Mighty Modulators.

—30—

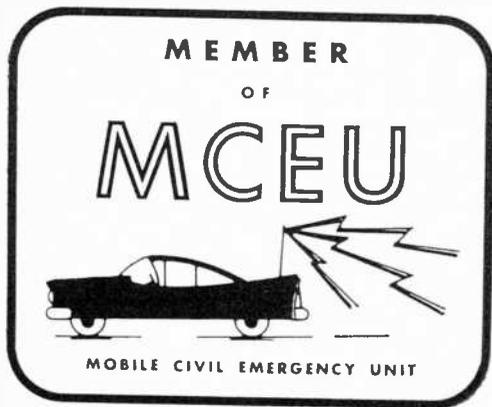

**ADVANCED
EXPERIMENTERS
CORNER**

Radio-Control 11-Meter Receiver

By **PERRY WINTER**
Associate Editor

USING only five transistors, this sensitive R/C receiver is intended to be a companion unit for the 11-meter R/C transmitter described in the February 1960 issue of *POPULAR ELECTRONICS*. But you don't need the companion transmitter if you already have a Citizens Band transmitter—your present CB rig or Part 15 pocket transmitter will operate the receiver on the 27.255-mc. radio-control frequency with only a slight modification. More about that later.


The receiver was designed* to operate on a r.f. signal modulated with a 750- to 1400-cycle tone. This means that nearby transmitters, even diathermy machines operating on the same r.f. frequency as the receiver, won't key the receiver unless they too are modulated with the required tone. The receiver is so sensitive that only 1.2 microvolts at the antenna with a 50% modulation at 1000 cycles will energize the receiver's control relay.

Starting from scratch, all the parts needed to build the receiver cost approximately \$35.00. Wiring in the two r.f. stages of the unit is more or less critical. However, over half the receiver's circuitry operates at audio frequencies and doesn't require any special shielding or wiring precautions.

The construction job should give you

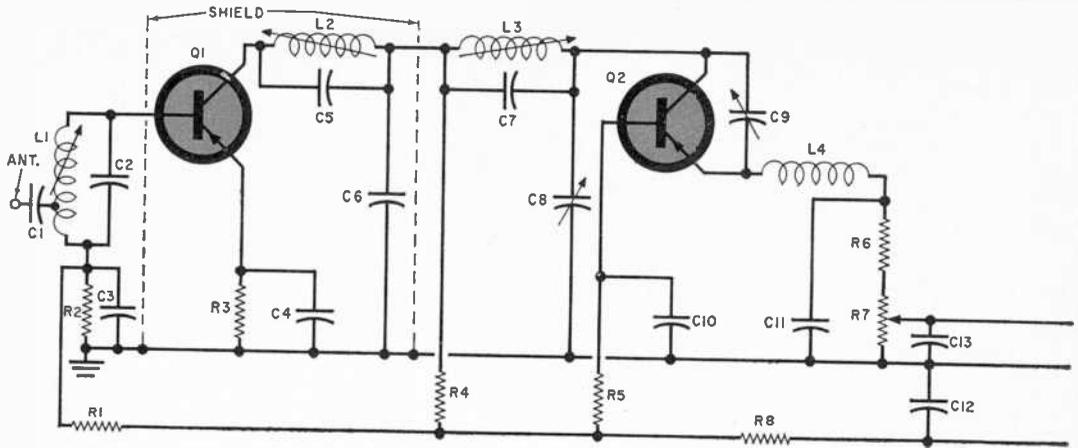*Designed by Texas Instruments Inc., Box 312, 13500 N. Central Expressway, Dallas, Texas.





PARTS LIST

- B1—22.5-volt battery (RCA VSO84, Burgess U15 or equivalent)
- C1, C3, C4—0.01- μ f. ceramic disc capacitor
- C2, C7—18- μ f. mica capacitor
- C5—22- μ f. mica capacitor
- C6—68- μ f. ceramic disc capacitor
- C8, C9—1.5 to 7 μ f. ceramic trimmer capacitor
- C10—0.001- μ f. ceramic disc capacitor
- C11, C15—0.1- μ f. ceramic or paper capacitor
- C12—0.05- μ f. ceramic disc capacitor
- C13, C14—0.02- μ f. ceramic disc capacitor
- C16—0.002- μ f. ceramic disc capacitor—see Alignment/Adjustment Procedure
- C17—5- μ f., 25-volt electrolytic capacitor
- C18—50- μ f., 6-volt electrolytic capacitor
- C19—100- μ f., 25-volt electrolytic capacitor

All capacitors 50 w.v.d.c. unless otherwise specified

- K1—10,000-ohm relay, s.p.d.t. contacts (Potter and Brumfield R55D or equivalent)
- L1, L2, L3—14 turns of No. 25 enameled wire close-wound on Cambridge Thermionic PLS6-2C4L/O or equivalent 30-mc. slug-tuned coil form 27/32" long x 1/4" diameter—coil L1 is center-tapped
- L4—22-microhenry, 2.5-ohm r.f. choke (Delevan 1537-44. Ohmite Z-28 or equivalent)
- L5—25-millihenry choke (Millen 24225 or equivalent)
- L6—8.5-henry choke (Stancor C1279 or equivalent)
- Q1, Q2—2N1107 transistor (Texas Instruments)
- Q3, Q4, Q5—2N185 or 2N1370 transistor (Texas Instruments)
- R1—22,000-ohm resistor
- R2—3900-ohm resistor
- R3, R4, R6—1000-ohm resistor
- R5—220,000-ohm resistor
- R7—100-ohm linear potentiometer (IRC WPK or equivalent)
- R8—3300-ohm resistor
- R9—47-ohm resistor
- R10—6800-ohm resistor
- R11—62,000-ohm resistor
- R12—4700-ohm resistor
- R13—27,000-ohm resistor
- S1—S.p.s.t. switch
- T1—Transistor transformer, 10,000-ohm primary to 2000-ohm center-tapped secondary, CT not used (Thordarson TR-7 or equivalent)
- 1—Aluminum box—see text
- Misc.—Hardware, transistor sockets, feedthrough studs, etc.

All resistors 1/2-watt unless otherwise specified.

Transistorized 11-meter receiver has only two and Q5 operate relay K1 when tone-modulated


no trouble if you are familiar with the short, direct wiring and shielding techniques that are the stock in trade of high-frequency circuits.

Circuit Design. Let's examine some of the design details to see how the receiver does its job. The incoming signal, a tone-modulated carrier on 27.255 mc., is applied to a common-emitter r.f. amplifier (Q1.) While it provides only a little gain, Q1 mainly serves to isolate the superregenerative detector (Q2) from the antenna; the presence of Q1 also makes the detector easier to adjust.

Transistor Q2 operates as a self-quenched superregenerative stage; the r.f. signal is fed into the collector and the audio output is taken from the emitter. A detector of this type is desirable for remote-control equipment because of its high gain and simplicity. The detector's lack of selectivity can be tolerated since it is followed by a high-gain narrow-band audio amplifier (transistors Q3 and Q4).

Detector Q2's output is an ultrasonic quench signal of about 50 kc. mixed with the audio of the detected signal. The quench filter (L5-C13-C14) passes the audio and rejects the quench frequency. Without the filter, the quench signal would overload the audio stages, preventing their proper operation.

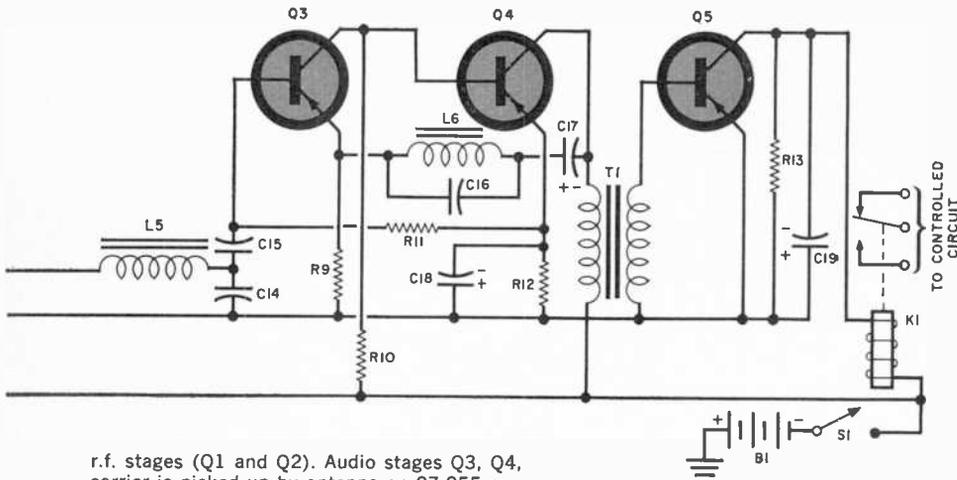The audio signal from the quench filter is then amplified in the two-stage tuned amplifier (Q3 and Q4). Undesired sig-



r.f. stages (Q1 and Q2). Audio stages Q3, Q4, carrier is picked up by antenna on 27.255 mc.

nals outside of the receiver's designed 750- to 1400-cycle bandpass are eliminated in the amplifier; thus, unmodulated stray carriers on the receiver's frequency will not key the receiver.

After amplification, the audio is rectified and re-amplified by Q5 to operate relay K1. The relay contacts can be used to control such equipment as garage door openers, driveway lights, or model boats and trains.

Construction. For valuable construction hints on how to build the receiver, refer to the article on the companion transmitter previously mentioned. In any case, the larger the box you use for the receiver, the fewer the construction problems. With a 7" x 5" x 3" aluminum box (Bud CU-2108A or equivalent), you should have little trouble mounting the parts.

No matter what size box you choose, be sure there is enough room to mount the two interstage shields. One shield is located between transistor Q1 and antenna coil L1, the other between coils L2 and L3. The shields are made from sheets of scrap aluminum and should span the width of the box.

For best results, use a single No. 14 tinned busbar for the ground bus. This busbar should run unbroken from the side of the shield next to Q2, down the length of the receiver to Q5. Only the ends of the busbar should be grounded. A separate ground is made on the other

side of this shield as well as on each side of the shield between Q1 and L1.

Use a second busbar for the B-minus line. Note that this line is interrupted by resistor R8, which isolates the audio and r.f. sections of the receiver. The B-minus bus should be passed through the shields, with insulated feedthrough studs.

Coils L1, L2, and L3 are the familiar slug-tuned coils which are mounted by their threaded screws. All other parts are supported by their leads or are fastened to the box with standard hardware. The transistors are soldered to terminal strips using a heat sink, or sockets can be used, as desired.

Alignment and Adjustment. To speed up alignment and adjustment of the receiver, it's best to have an a.c. VTVM and a 0-5 ma. milliammeter on hand before you start. You'll also need either the modulated version of the companion, Part-15 11-meter transmitter or a CB transmitter equipped with a 27.255-mc. crystal. If you use a Part 15 transmitter, no license is required; but if you use a CB rig, you'll need a Class C (radio-control) license.

With the CB transmitter and the Class C ticket, a pitch-pipe or 1000-cycle generator is also required. To key the receiver, you will have to whistle the tone into the CB transmitter's microphone when called for in the adjustment procedure. (See instructions on next

ALIGNMENT/ADJUSTMENT PROCEDURE

Starting with alignment of the r.f. section, connect a low-impedance (50- to 75-ohm) Citizens Band antenna to the receiver's antenna terminals. Switch on the receiver and proceed as follows:

1. Set coils *L1*, *L2*, *L3* and trimmer capacitors *C8* and *C9* to their mid-range positions.
2. Rotate the arm of potentiometer *R7* to its ungrounded end.
3. Connect an a.c. VTVM, set to a low-voltage scale, between the collector of *Q4* and ground.
4. Temporarily disconnect either side of capacitor *C17* from the receiver's circuit.
5. Adjust trimmer capacitor *C9* until the detector stage (*Q2*) regenerates—oscillation will be indicated by a large increase in the reading of the VTVM.
6. Turn on the transmitter. If you use the companion 11-meter transmitter, remove its antenna and bottom cover—only a weak r.f. signal source is needed for the receiver. If a CB rig is used, no modulation is required in this step.
7. Adjust coil *L3* for a maximum reading on the VTVM.
8. Couple the transmitter closer to the receiver's antenna.
9. Adjust coil *L1* for a maximum reading on the VTVM.
10. Adjust coil *L2* for a maximum reading on the VTVM.
11. Adjust trimmer capacitor *C8* for a maximum reading on the VTVM.
12. Adjust trimmer capacitor *C9* for a maximum reading on the VTVM. If regeneration stops when *C9* is adjusted—this will be indicated by a sudden drop in the VTVM reading—back off on *C9* a bit until oscillation is restored.
13. Repeat steps, 9, 10, 12, and 11, in that order.
14. Reconnect capacitor *C17*. This completes the r.f. alignment.

After r.f. alignment, the audio filter (*L6-C16*) is adjusted to provide best gain and selectivity at 1000 cycles. This is done as follows:

1. Set potentiometer *R7* to its mid-range position.
2. Connect an a.c. VTVM, set to a low voltage scale, between the collector of *Q4* and ground.
3. Turn on the transmitter—the rig should now be modulated with a 1000-cycle tone as described in text.
4. Change the value of fixed capacitor *C16* by substituting different values until the highest reading is obtained on the VTVM. This completes the adjustment of the audio filter.

When both the r.f. alignment and the 1000-cycle filter (*L6-C16*) adjustments have been completed, the sensitivity control, potentiometer *R7*, is then adjusted. To get maximum sensitivity from the receiver, adjust *R7* as follows:

1. Disconnect the receiver's antenna.
2. Insert a 0.5 ma. milliammeter in series with relay *K1* and the B-minus busbar.
3. Adjust *R7* for a 1.5-ma. reading on the milliammeter—this level is approximately 2 ma. less than the required energizing current for relay *K1*.
4. Test the operation of *K1* by connecting the receiver's antenna and by keying the companion transmitter or tone-modulated CB rig. Relay *K1* should energize when the transmitter is keyed and it should de-energize when the transmitter is turned off. With the CB rig, the relay should de-energize when the tone modulation is cut off—the unmodulated carrier, by itself, should not cause *K1* to operate. If relay *K1* does not de-energize in the transmitter-off or modulation-off condition of the respective transmitters, then *R7* should be readjusted slightly until *K1* de-energizes. This step completes the maximum sensitivity adjustment of the receiver.

page.) If you don't have a pitch pipe, connect a calibrated audio generator to the microphone jack.


No external modulation is required if you use the modulated version of the companion transmitter, since a 1000-cycle tone generator is incorporated in it. When this transmitter is keyed on, it will generate a carrier on 27.255 mc. modulated with 1000 cycles.

Operation. Under actual operating conditions, maximum sensitivity of the receiver may not be needed. In fact, high sensitivity may cause control relay *K1* to lock on after the tone-modulated carrier is removed. It is also possible that nearby transmitters on 27.255 mc. could accidentally key the receiver if these transmitters were modulated with an audio tone near 1000 cycles. For example, a 3.7-microvolt r.f. carrier modulated with 750 cycles or a 10-microvolt carrier modulated with 1400 cycles could key the

receiver if it is adjusted for maximum sensitivity.

To avoid accidental keying of the receiver and for operation over short ranges, proceed as follows. Align the receiver's r.f. section and the 1000-cycle filter (*L6-C16*), as described above. Then, mount the receiver and its antenna in their permanent locations. Connect the antenna to the receiver using RG-58/U or RG-59/U coaxial cable, and switch on the receiver.

Place the transmitter at the maximum range from which operation is desired. If you are going to operate your garage door or driveway lights with the contacts of relay *K1*, for example, locate the transmitter in your driveway. Now, turn on the transmitter's modulated carrier and adjust *R7* in the receiver until relay *K1* just "pulls in." Turn off the transmitter. Relay *K1* should now be de-energized; if it does not de-energize, readjust *R7*. —50—

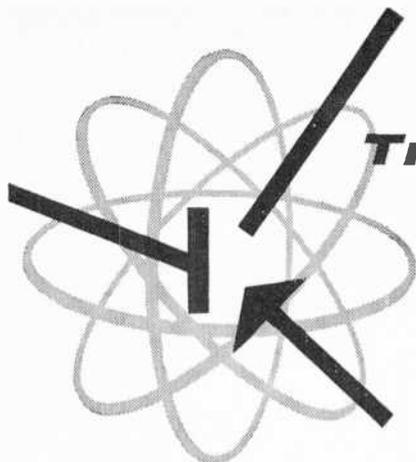

Transistor Topics

By LOU GARNER

ALTHOUGH chill breezes continue to howl over many parts of the nation and snow is still piled high in some areas, it's not too early to start shaping up your plans for spring and summer. Boating enthusiasts, particularly, may want to review their sea-going electronic gear with a view toward adding a few new items—and if these items are to be assembled from kits, *now* is a good time to start wiring them to insure shipshape equipment when launching time arrives.

Perhaps the most valuable item a boat owner can add to his vessel is a good radio direction finder. This instrument can be

used for entertainment purposes, as a source of weather news, and—when you're out of sight of familiar landfalls—as a real aid to navigation.

Heath's DF-3 "Mariner" combines most of the features desired in a radio direction finder. Available in both kit and factory-assembled form through locally franchised dealers as well as direct from the Heath Company, Benton Harbor, Mich., the DF-3 is a fully transistorized, battery-powered, three-band superhet receiver. With an i.f. of 455 kc., the instrument tunes

Heath DF-3 "Mariner"


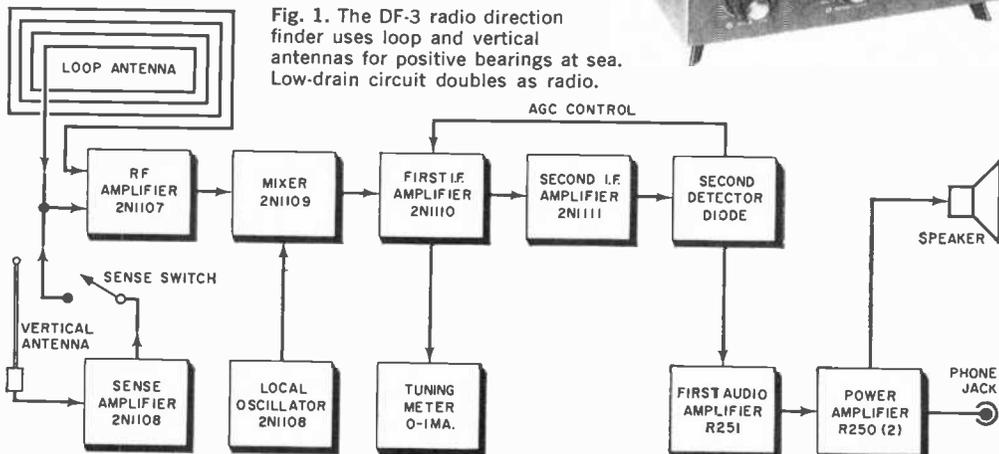


Fig. 1. The DF-3 radio direction finder uses loop and vertical antennas for positive bearings at sea. Low-drain circuit doubles as radio.

Fig. 2. Operation of a radio direction finder can be explained by analyzing the pickup patterns of two different types of antennas. A loop antenna (A) has maximum pickup in directions A and B, minimum pickup in directions X and Y; a vertical antenna (B) has a uniform sensitivity pattern. Combining the two antennas (C) provides maximum sensitivity in direction A only.

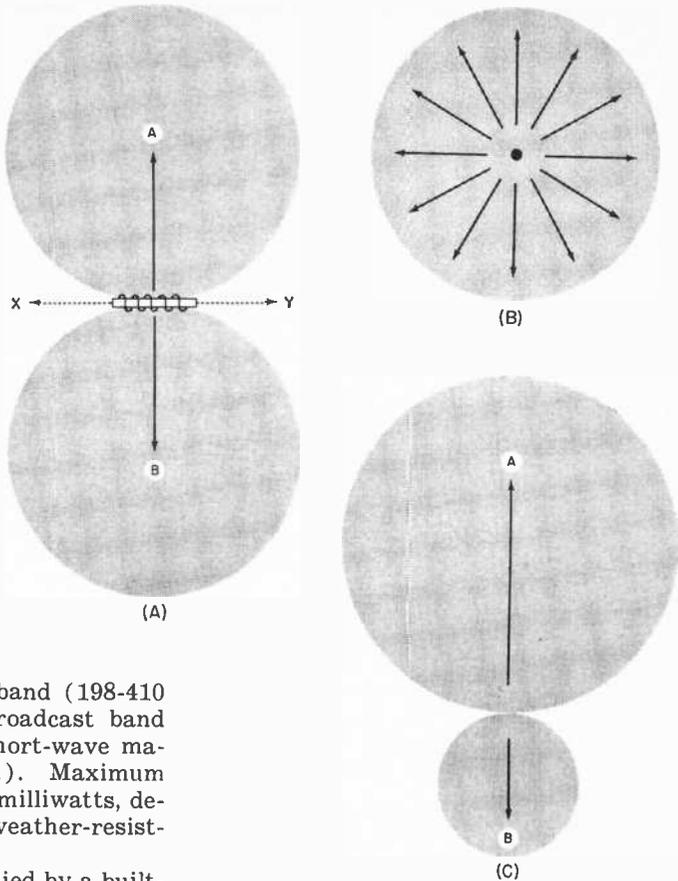

the low-frequency beacon band (198-410 kc.), the standard AM broadcast band (535-1620 kc.), and the short-wave marine band (1650-3450 kc.). Maximum audio output power is 380 milliwatts, delivered to a 4" x 6" oval weather-resistant PM loudspeaker.

Operating power is supplied by a built-in power pack made up of six standard size-"D" flashlight cells supplying a total of 9 volts. Current drain is approximately 20 ma. at a 50-milliwatt output level, giving an average battery life of from 500 to 1000 hours. Physically, the DF-3 measures 8" high by 9" deep by 10" wide and weighs 9¼ pounds (with batteries installed).

A block diagram of the receiver is given in Fig. 1; *p-n-p* transistors in the common-emitter arrangement are used in all stages.



In addition to the familiar loop antenna, a vertical whip antenna and broadband untuned r.f. amplifier are provided. The vertical antenna and r.f. amplifier combination can be connected in addition to the receiver's loop antenna, and serves to add a directional "sense" to the instrument's indicated heading. To see why the additional circuit is needed, and how it works, refer to Fig. 2.

In its basic form, a loop-type antenna has a sensitivity pattern resembling a

figure "8," as shown in Fig. 2(A). Maximum sensitivity is at *right angles* to the plane of the loop (or bar), with minimum sensitivity along a line *through* the bar. Thus, maximum signal pickup is in directions "A" and "B" and minimum pickup in directions "X" and "Y." This directional characteristic is well known, and can be demonstrated quite easily with *any* portable receiver using a loop-type antenna. Simply tune in a weak station and rotate the set slowly, noting increases and decreases in receiver volume.

Although the simple loop can be used for directional indication by rotating it for maximum (or minimum) pickup from a station, it suffers from a serious disadvantage—the station may be located on either side of the loop. (It was this disadvantage, according to many authorities, which caused the crew of that ill-fated World War II bomber, the "Lady Be Good," to overshoot its base and crash in the Libyan desert.) A vertical or

Fig. 3. Two circuits submitted by reader A. Ravindranathan, of India, are essentially the same but are used for different purposes. In his first circuit (A), capacitor C1 and switch S2 convert a standard audio amplifier into an oscillator. In the second circuit (B), light falling on the sun battery PC1 energizes relay K1. See text.

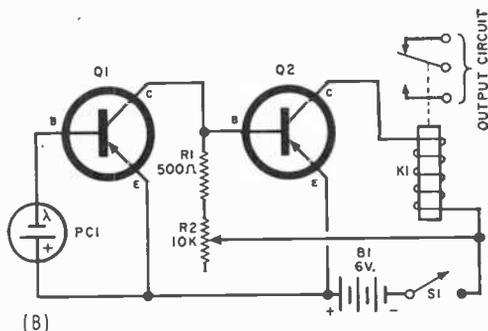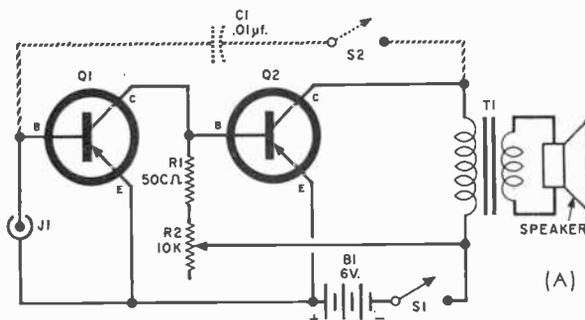

“whip” antenna, in contrast to the loop, has an omnidirectional pattern; as shown in Fig. 2(B), it picks up signals equally well from *all* directions.

When the signals picked up by both loop and vertical antennas are combined, the resulting pattern is that of a somewhat distorted figure “8,” shown in simplified form in Fig. 2(C). This pattern results because the signals picked up in one direction from the loop are out-of-phase (and tend to cancel) with the signals picked up by the vertical antenna, while signals picked up on the opposite side of the loop are in-phase with (and reinforce) the signals picked up by the vertical antenna. Thus, when both antennas are used together, maximum signal pickup is in direction “A”—see Fig. 2(C)—and adjustment of the loop for a given directional heading will provide an accurate indication.

In the DF-3, the vertical “sense” antenna is used only when needed for position and heading checks. It is not needed when the receiver is used as a simple broadcast set for entertainment, or for weather or news reception.

Many potential assemblers of the DF-3 will be pleased to hear that Heath has pre-assembled, wired, and *prealigned* the entire “front-end,” including the r.f., mixer,


and local oscillator circuits. The rest of the receiver is comparatively easy to assemble and adjust using the large-size pictorial diagrams and step-by-step instructions furnished.

Readers' Circuits. Many overseas readers complain that they have difficulty securing transistors, diodes, and other U. S.-made components for their projects—a number of them rely on friends in this country to help them obtain parts. In view of this situation, yours truly was pleasantly surprised by a recent letter from a Mr. A. Ravindranathan in India. Mr. Ravindranathan enclosed several interesting circuits he had developed using standard (U. S.) components, two of which are shown schematically in Fig. 3. These circuits are essentially alike, featuring a pair of *p-n-p* transistors as direct-coupled common-emitter amplifiers. A combination audio amplifier and oscillator is shown in Fig. 3(A), and a light-controlled relay in Fig. 3(B).

In operation, signals applied to transistor *Q1*'s base-emitter circuit are amplified by this stage and applied directly to transistor *Q2*'s input circuit. The amplified output signal from *Q2*, in turn, is applied to the output load device—the primary of audio transformer *T1* in Fig. 3(A) or electromagnetic relay *K1* in Fig. 3(B). Transistor *Q1*'s adjustable collector load resistor, *R1-R2*, serves both to determine *Q2*'s fixed base bias and to control *Q1*'s effective stage gain. In both circuits, *Q1* is an RCA Type 2N215, *Q2* a Type 2N217. Resistor *R1* is a 500-ohm, 1/2-watt unit, and *R2* is a standard 10,000-ohm potentiometer.

In the amplifier-oscillator circuit, *J1* is a standard phono jack, capacitor *C1* a 0.01- μ f. ceramic or paper unit, switch *S2*

(Continued on page 114)

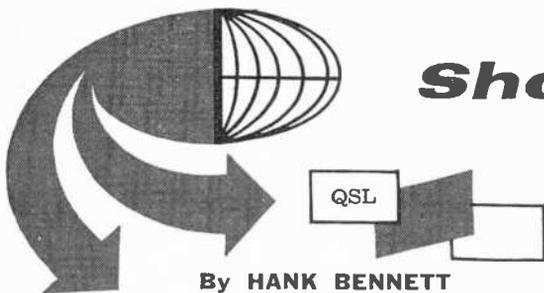

Short-Wave Report

By **HANK BENNETT**
W2PNA/WPE2FT

GEORGE and Nancy Ann Wlodarski—a brother-sister DX'ing team—live at 4337 289th St., Toledo 11, Ohio. Nancy is 17 years old, a sophomore in high school, and holder of the call WPE8BOO. George, 22 years old, and the operator of amateur station K8ABR, was just recently discharged from the U. S. Air Force where he specialized—for four years—in radio and radio repair.

The line-up of equipment at the Wlo-

and 6000 kc., respectively) and, in addition, she is very much interested in the long-wave band from 10 to 100 kc. (Brother George has just completed construction of a converter to cover this band.) Her favorite programming—musical—comes from Stockholm, Warsaw, Berne, and Copenhagen. Moscow also rates as a favorite, for Nancy is able to obtain news from the Iron Curtain standpoint and use some of it in her classes at school.

When George takes over on two-way communications, Nancy's activities are hampered somewhat—her future plans



Nancy Wlodarski and her brother George, who holds amateur call K8ABR, share the same listening post. The Wlodarski's have quite an array of equipment, only part of which is shown here.

darski's is formidable, and in all likelihood is in operation more than it is off. The bank of receivers consists of three Hallicrafters units: an SX-99, an S-38D, and an SX-140. All three of the receivers operate from one antenna, a Mosley vertical mounted 20 feet above the top of the house.

Nancy is the real SWL of the family, for it is she who has compiled a log of 20 countries heard, 8 verified. She has been SWL'ing for nearly two years. In all, she has a total of 20 verifications, and the list is growing steadily. Her best veri to date is from OZF, *The Voice of Denmark*, Copenhagen.

Nancy's favorite short-wave bands center around 19 and 49 meters (15,000



call for an amateur license of her own. If George looks familiar to you, it may be because you saw his picture in last month's *Across the Ham Bands*, together with the Wlodarski equipment.

In Libya, three years ago, George operated with the call 5A3TF and worked

(Continued on page 124)



By
JOHN T. FRYE
W9EGV

Carl and Jerry

A Low Blow

IT WAS two whole weeks since Carl and Jerry had talked face to face. Jerry had been home from school sick with influenza, and the boys' parents had kept them apart to prevent Carl's catching the virus infection. The two had managed to keep in touch by chatting on the phone, by talking over their ham stations, and—since their bedroom windows faced each other—even by blinking Morse code on flashlights from one window to the other. But Jerry had finally recovered sufficiently to be down in his basement laboratory this warm, windy Saturday morning, and to have Carl visit him.

"Hi, Jer," Carl said gruffly as he came in through the outside basement door. "How's my puny pal? You look kinda pale around the gills."

Jerry turned away from the large, wide-mouthed glass jar sitting on the workbench in front of him to bestow a fierce scowl on his friend.

"Don't 'puny pal' me, you big ox! Disgustingly healthy people make me sick!"

"Now, now, there!" Carl murmured with mocking solicitude. "We mustn't get upset. Remember: we are not well. And what are we doing with that goldfish bowl?"

"I am getting ready to test my infrasonic microphone," Jerry said curtly, turning back to the fishbowl that had a thin membrane of rubber stretched over the top. Inside was a small, brass-topped glass jar containing some transistors and other components mounted on a little circuit board. Two tiny twisted wires of the sort used in record-player tone arms came out of a wax-sealed hole in the

bottom of the jar, ran up over the edge of the bowl beneath the rubber membrane, and were connected to the input of a tape recorder sitting on the workbench.

"I need more information than that," Carl cheerfully confessed. "What is this 'infrasonic' jazz? I've never heard you mention a project like that before!"

"In physics you *should* have learned that sound recognized as such by the human ear goes down in frequency to about 12-15 cycles," Jerry explained; "but there are other compression and rarefaction waves in the atmosphere at much lower frequencies. These are called 'infrasonic waves,' and we are surrounded by them even when our ears hear nothing.



They obey the same laws as sound waves: their speed varies as the product of the square root of the absolute temperature and a constant related to the conducting medium.

"At 32°F," he continued, warming to the subject, "sound travels about 1087

feet per second in air, and the speed increases as the temperature rises. The rate at which sound power is absorbed and dissipated into heat depends on the frequency. The fraction of sound power absorbed per unit distance of propagation is roughly proportional to the square of the frequency. That explains why you hear the bass drum of an approaching band first, and it also means that only low inaudible frequencies can be propagated great distances."

Carl started to say something, but Jerry didn't give him a chance.

"When the volcano Krakatoa exploded in 1883 in the East Indies, inaudible waves from this disturbance traveled around the world several times with a pressure so great that it produced readable deflections on barographs. The impact of the great meteor that fell in Siberia in 1908 had the same result. During World War I, it was noticed that cannon fire could be heard within a radius of 100 kilometers, and often beyond 200 km., but not *between* 100 and 200 km."

"The sound waves must have been skipping the way our radio waves do," Carl noted.

"Exactly! Observers figured that something far above the earth must be deflecting the sound waves back down. The only thing that could do so would be a layer of air warmer than the air at the earth's surface which would speed up the top edge of the sound wave entering it at an angle and bend the wave back toward the earth. By listening for the lowest audible frequencies and by checking the transit time of the wave from the source to the distant observer, those smart cookies figured out *where* and *how warm* that layer of air had to be! Very recent information gathered by our space probes confirmed their calculations.

"As you go up in a quiet atmosphere," Jerry went on, "the temperature falls sharply at first and then zigzags back and forth until you reach an altitude of about 105 km. From that point on up, for at least a considerable distance, the temperature increases steadily, reaching much higher values than here—"

"Just a cotton-picking minute," Carl interrupted. "You didn't know all this when you got sick. How did you get so smart?"

"Some time back," Jerry explained, "I noticed a newspaper article about how the National Bureau of Standards was carrying on experiments on the detection and recording of infrasonic waves. I wrote the Bureau asking for more information, and Mr. Paul Walsh and Mr. Donald M. Caldwell kindly sent me a lot of interesting information about their installation near Washington, D. C."

"How do they work it?"

"They have four infrasonic microphones set up at different locations several miles apart. Signals from each mike are fed to a central location where they are amplified, bandpass-filtered, and recorded as ink-on-paper traces. By noticing the difference in time of the signal's arrival at various mike locations, its speed and source-direction can be determined."

"I can't imagine what sort of mike you'd use to pick up signals of one or two cycles per minute," Carl muttered with a thoughtful frown.

"Neither could I," Jerry agreed, "but the dope I got says the mike is a condenser type with a diaphragm of thin, specially-formed brass mounted on a reference volume. One side of the diaphragm connects to a noise-reducing pickup pipe. Movements of the diaphragm modulate the frequency of an oscillator."

"I see—I think," Carl said doubtfully, "but what's this about a noise-reducing pipe?"

"When the mike diaphragm is exposed directly to the open air, pressures produced by the wind develop a lot of signal-masking noise. These specially designed metal pipes lie on top of the ground and are each about 1000 feet long. Each pipe has 100 small holes distributed along its length. A signal traveling toward the microphone along the length of the pipe is attenuated very little, but random variations in pressure caused by wind turbulence are greatly reduced."

"What sort of sounds, or whatever you call 'em, are picked up?"

"Well, on May 5, 1960, when the weather bureau reported 19 tornadoes and funnel clouds in Oklahoma, Texas, and Kansas in a four-and-a-quarter-hour period, the microphones recorded waves of periods between 12 and 50 seconds

(Continued on page 96)

INTERNATIONAL 1961 CATALOG



FREE

Your
BUYING GUIDE FOR
PRECISION RADIO CRYSTALS
AND QUALITY ELECTRONIC EQUIPMENT.

- COMMERCIAL CRYSTALS • AMATEUR AND
CITIZENS BAND CRYSTALS • AUTO
RADIO CONVERTERS • OSCILLATORS • FREQUENCY
ALIGNMENT EQUIPMENT • TRANSMITTERS
• MODULATORS • POWER SUPPLIES
- TRANSISTOR SUBASSEMBLIES • CITIZENS
BAND TRANSCEIVERS • CITIZENS
BAND ANTENNAS/ACCESSORIES

Specialists in precision radio crystals, Citizens 2-Way radio equipment, and quality electronic products.

INTERNATIONAL
CRYSTAL MANUFACTURING CO., INC.

18 NORTH LEE • OKLAHOMA CITY, OKLA.

AMATEURS —

Complete data on International's all transistor subassemblies; 6 and 2 meter transmitting and receiving gear; crystal controlled converters for 75, 40, 20, 15 and 10 meters.

CITIZEN LICENSEES —

International transceivers, accessories and antennas for dependable 2-Way radio communication. See International's kit for constructing your own Citizens transceiver.

EXPERIMENTERS —

Printed circuit oscillators, RF converters, IF units, audio units, transistor subassemblies, crystals and crystal ovens.

Mail today for your FREE Catalog!

International Crystal Mfg. Co., Inc.
18 North Lee, Oklahoma City, Okla.
Send Free 1961 International Catalog

Name _____


Address _____

City _____ Zone _____ State _____

50-WATT STEREO AMPLIFIER AND CONTROL CENTER

Get the most from your stereo system with this superb unit; power-packed 50 watts (25 w. per channel); complete tone, balance and stereo/mono function controls; five dual-stereo inputs plus separate monophonic mag. phono; mixed-channel center speaker output; luggage-tan vinyl clad steel cover. 31 lbs.

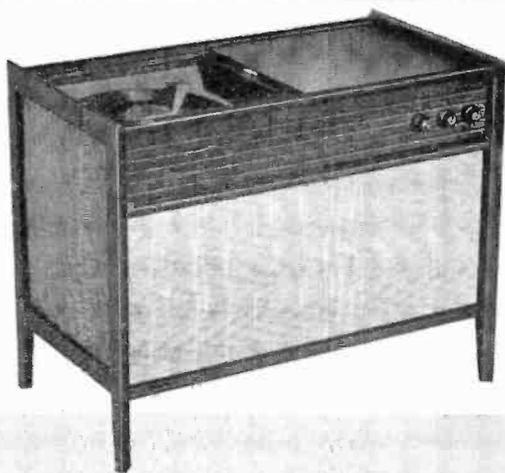Kit Model AA-100 **\$84.95**
 Assembled Model AAW-108 **144.95**



GET BIG STEREO SOUND AT LOWEST COST WITH THIS COMPLETE STEREO-PHONO CONSOLE . . . NOW IN ASSEMBLED OR KIT FORM FROM \$129.95 UP

Modest only in size and price, this new Heathkit Stereo-Phono Console amazes every listener with its room-filling, true-to-life stereo sounds. Proportioned to fit any room, it's less than three feet long and only end-table height, yet it houses a complete stereo-phono system with features usually found only in much larger consoles. There's six speakers . . . two 12" woofers for smooth "lows," two 8" speakers and two 5" cone-type tweeters for "mid-range" and "highs". The 4-speed automatic stereo/mono record changer is equipped with an "anti-skate" device and a turn-over diamond and sapphire styli cartridge. On the front panel are separate, dual bass and treble controls plus a concentric volume control. The handsome cabinet with solid genuine walnut frame, walnut veneer front panel, and matching "wood-grained" sliding top measures just 31 1/4" L x 17 3/8" D x 26 3/4" H. Whether you buy the ready-to-play or kit form, the cabinet is factory assembled and finished. 70 lbs.


Kit Model GD-31 **\$129.95**
 Assembled Model GDW-31 **149.95**


COMPLETE 28-WATT AND 50-WATT STEREO CONSOLES

Enjoy incomparable Heathkit stereo with factory wired components in beautiful preassembled, prefinished cabinets . . . ready to use! The consoles are available in both 28 and 50 watt models, with money-saving optional kit plans. The 28-watt model (HFS-26) contains the Heathkit AJ-10 stereo AM/FM tuner, SA-2 stereo amplifier, AD-50A stereo record changer and two US-3 12" coaxial hi-fi speakers. The 50-watt model (HFS-28) contains the Heathkit AJ-30 deluxe stereo AM/FM tuner; AA-100 deluxe stereo amplifier; AD-60B deluxe stereo record changer; and two Jensen H-223F coaxial 2-way 12" hi-fi speakers. Specify walnut or mahogany.

Assembled Model HFS-26 . . . 215 lbs. **\$475.00**
 Kit Model HFS-27 . . . 215 lbs. **370.00**
 Assembled Model HFS-28 . . . 264 lbs. **675.00**
 Kit Model HFS-29 . . . 264 lbs. **550.00**

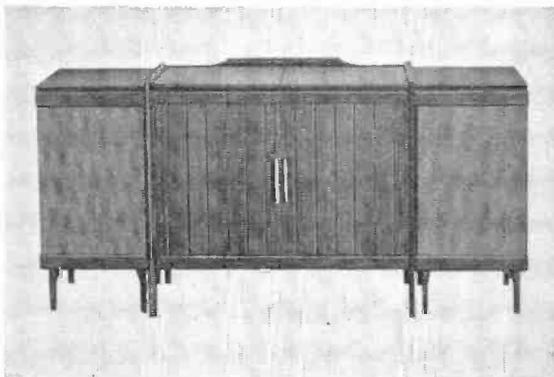(Cabinets available separately, write for information)



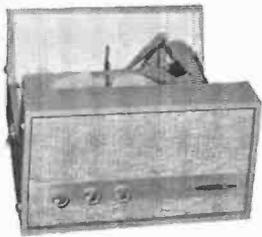

STEREO/MONO PORTABLE PHONOGRAPH

Now you can thrill to magnificent stereo wherever you are, wherever you go! The smartly-styled cabinet with two-tone aqua and white durable vinyl covering comes completely preassembled. In closed carrying position the speaker wing and main cabinet blend into a single handsome unit in dazzling aqua and white vinyl. In use, the detachable speaker-wing top may be spaced at any distance for maximum stereo effect. The completely preassembled automatic changer plays your favorite stereo and mono records at speeds of 16, 33 $\frac{1}{3}$, 45 and 78 rpm, while controls on the amplifier section give you complete command of volume, stereo-balance and tonal quality. 28 lbs.

Kit Model GD-10..... **\$69.95**


Look forward to the happy months ahead
of outdoor living with Heath equipment



PORTABLE 4-TRACK STEREO TAPE RECORDER

Plays and records 4-track stereo tape for endless hours of delight! Can even be used as a hi-fi center to amplify and control tuners, record players, etc. Has "record," "play," "fast-forward" and "rewind"; 2 speeds (3 $\frac{1}{4}$ and 7 $\frac{1}{2}$ IPS); tone balance and level controls; monitoring switch for each channel to let you hear programs as they are recorded; pause button for editing; and two "eye-tube" recording level indicators. Speaker wings are detachable. Cabinet and tape mechanism are preassembled; all amplifiers and speakers included. 49 lbs.

Kit Model AD-40..... **\$179.95**

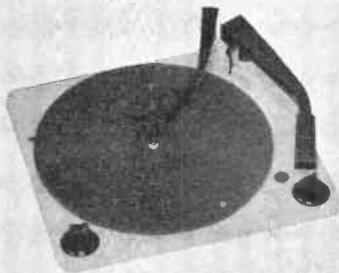

NEW LOW COST STEREO RECORD CHANGER KIT


Here's fine changer features at a budget price . . . oversized 11" turntable, "anti-skate" device, jam-proof mechanism and plug-in cartridge head. 4 speeds with automatic shutoff. Assembles easily, quickly with no special tools. Complete with your choice of three different, famous-name, diamond-styli stereo cartridges. 15 lbs.

Model AD-80C.

Sonotone 8TA4-SD cartridge..... **\$37.95**

Model AD-80A, GE VR-227 cartridge **41.95**

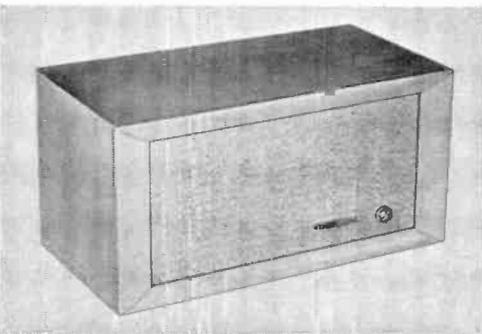Model AD-80B, Shure M&D cartridge **42.95**



REVERBERATION SYSTEM

Add a thrilling new "cathedral" dimension to listening! Reverberation supplies the dimension of spaciousness to sound, as heard in concert halls, etc. where "echoes" enrich and reinforce the original sounds. The GD-61 adds reverberation acoustically, not by electronic mixing, thus it doesn't disrupt your present system and it may be placed anywhere for best listening effect. Can be connected to speaker terminals of hi-fi systems, radios, TV sets, etc. Control lets you add just the right amount of reverberation. The GD-61 consists of Hammond type IV reverberation unit, amplifier with power supply and 8" speaker. Pre-assembled birch cabinets in mahogany or walnut finishes. Measures 11 $\frac{1}{2}$ " H x 23" W x 11 $\frac{1}{4}$ " D. 30 lbs.

Kit Model GD-61M (mahogany) or

GD-61W (walnut) each..... **\$69.95**

NOW ONLY
HEATH
BRINGS YOU
ALL 3!

1. HEATHKIT
for
do-it-yourself
hobbyists.

2. HEATHKIT
factory-built,
ready to use.

3. HEATHKIT
learn-by-doing
Science Series
for youngsters.

HEATH COMPANY / Benton Harbor, Michigan

TWO AND SIX METER TRANSCEIVERS

The "ham on the go" will find the new Heathkit "Shawnee" 6-meter and "Pawnee" 2-meter transceiver kits irresistible! Both of the handsome units offer complete AM and CW facilities with: single knob tuning . . . tracked VFO and exciter stages; 10 watt output; built-in low pass filter; three-way power supply built-in for 117 VAC, 6 VDC or 12 VDC with separate DC and AC plugs and cables included; dual-purpose modulator . . . 10 watts for high level plate modulation or 15 watts for PA operation; double conversion receiver . . . crystal controlled first oscillator; tuning meter . . . auto-switched for received signal strength or relative power output; VFO or crystals . . . front panel switch of VFO or four crystals for novice, CAP, MARS or net operation; "spotting" switch; complete shielding of power supply, final and receiver front end; ceramic microphone . . . push-to-talk with coiled-cord. And many more outstanding features . . . write for information. 34 lbs.

Kit Models HW-10 (6 meter) and HW-20 (2 meter) each . . . \$199.95



look forward to the happy months ahead of outdoor living with Heath equipment

6-TRANSISTOR PORTABLE RADIOS

These award-winning, smartly-styled portables are ready to go anywhere! Both feature vernier tuning; 6-transistor circuit; 4" x 6" speaker for big set tone; prealigned transformers. 6 flashlight cells furnish power. (less batteries).

Kit Model XR-2P (plastic) . . . 6 lbs. . . . \$29.95

Kit Model XR-2L (sim. leather & plastic) . . . 7 lbs. . . . 34.95

"WALKIE-TALKIE"

CITIZEN'S BAND TRANSCEIVER

Ideal companion for the outdoorsman . . . talk to friends up to a mile away. No license required . . . anyone can use it . . . Features 4-transistor circuit, superregenerative receiver, crystal controlled transmitter. Powered by single long-life battery. Case included. 3 lbs. (less battery)

Kit Model GW-30 each . . . \$32.95

Assembled Model GWW-30 each . . . 50.95



"WARRIOR" GROUNDED-GRID KILOWATT LINEAR

Attention Amateurs! Compare it feature for feature, the Warrior paces KW rigs at double this low price! Completely self-contained, the amplifier, HV, filament and bias supplies are built-in. Drives with 50 to 75 watts. no matching or swamping network required. Stable g-g circuit with up to 70% efficiency. Oil-filled capacitor and 5-50 henry swinging choke. Bands: 80 through 10. Max. power input; SSB—1,000 watts PEP; CW—1,000 watts; AM—400 watts (500 using controlled carrier mod.); RTTY—650 watts. Write for information.

Kit Model HA-10 . . . 100 lbs. . . . \$229.95

TRANSISTOR DEPTH SOUNDER

For summer boating fun and safety, the MI-10 is your best buy by far in a dependable depth sounder . . . and you can buy it in kit form or factory wired and tested, ready to use. Gives reliable depth indications to 100' or more over "hard" bottoms; somewhat less over "soft" bottoms. Rotating neon light gives clear indications on hooded dial face. Six long-life flashlight batteries are used for power. Transducer may be mounted through hull, or temporarily outboard. 10 lbs. (less batteries).

Kit Model MI-10 . . . \$ 69.95

Assembled Model MIW-10 . . . 107.95





HEATHKIT BASIC RADIO COURSE

Here's a new 2-part series in basic radio for youngsters and adults. "Basic Radio—Part I" teaches radio theory in everyday language, common analogies, and no difficult mathematics. Experiments performed with radio parts supplied result in a regenerative radio receiver. "Part II" of the series advances your knowledge of radio theory and supplies additional parts to extend your Part I receiver to a 2-band superheterodyne.

- Model EK-2A . . . "Part I" . . . 8 lbs. **\$19.95**
- Model EK-2B . . . "Part II" . . . 4 lbs. **\$19.95**
Available March 24
- Model AK-8 . . . Cabinet for Part II Receiver . . . 4 lbs. **\$3.95**
Available March 24



DELUXE CITIZENS BAND TRANSCEIVER

Get the GW-10 for superior 2-way communication: superheterodyne receiver with switch selection of crystal control of any one channel or continuous vernier tuning of all 23 channels; automatic "series gate noise limiter"; adjustable squelch control; press-to-talk mike with coil cord; illuminated dial. Crystal controlled transmitter has switch selection of 3 crystals (one furnished). Hardware supplied for under dash mounting. Built-in power supply. 117 V. AC and 6 or 12 V. DC models 11 lbs.

- Kit Model GW-10 **\$62.95**
- Assembled Model GW-10 . . . **\$99.95**



3-BAND RADIO DIRECTION FINDER

Now, at big savings, a deluxe completely transistorized portable RDF in your choice of kit or assembled models. The DF-3 operates on marine beacon, standard broadcast and ship-to-shore bands to offer you both portable radio entertainment and reliable direction finding facilities. Featured are: 9-transistor circuit; 6 flashlight battery power supply; preassembled prealigned tuning section; new sense antenna for non-ambiguous bearings; lighted dial and tuning meter. 13 lbs.

- Kit Model DF-3 **\$ 99.95**
- Assembled Model DFW-3 . . . **169.95**



HEATH COMPANY / Benton Harbor 10, Michigan

SEND MY FREE COPY OF YOUR COMPLETE CATALOG

ORDERING INSTRUCTIONS: Fill out the order blank. Include charges for parcel post according to weight's shown. Express orders shipped delivery charges collect. All prices F.O.B. Benton Harbor, Mich. A 30% deposit is required on all C.O.D. orders. Prices subject to change without notice. Dealer and export prices slightly higher.

Please send the following items:

ITEM	MODEL NO.	PRICE

NAME _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____

Order direct by mail or see your Heathkit dealer.
Ship via Parcel Post Express C.O.D. Best Way



Carl and Jerry

(Continued from page 90)

with speeds about equal to that of sound in air and with pressures slightly less than one dyne per square centimeter. Hearing a tornado 1000 miles away is sharp listening! A system of detectors like this could track tornadoes. In fact, another installation is planned near Boulder, Colorado.

"On August 18, 1959," Jerry continued, "sound pressure produced by the big earthquake in Montana was observed at the NBS Washington laboratories. An earthquake wave traveling along the earth's crust moves the surface up and down like the cone of a giant speaker and sends sound waves almost vertically into the atmosphere. Information gleaned from these waves valuably supplements data gathered by seismographs regarding the nature of a quake and its original source.

"Magnetic storms also produce strange 'sound' waves of periods greater than 20 seconds with a trace velocity up to three times the speed of sound. These waves usually arrive from the north during magnetic storms, and they have a large angle to the surface of the earth. The Bureau hopes to study them to learn more about the interaction of the sun and the earth's magnetic field."

HOW did you make your mike, and what are you going to do with it?" Carl asked as the ground shook with a low growl of distant thunder.

"I stretched a diaphragm of very thin brass shim stock tight over a little steel hoop. Another disc of brass mesh wire is separated from the shim stock one by a thin insulating washer. This assembly, mesh disc down, is mounted on top of the little glass jar with an airtight seal. The homemade printed-circuit board inside the jar contains two transistorized crystal oscillators and a diode mixer to combine their outputs. The capacitor formed by the diaphragm and the screen is across one of the crystals. The two oscillators are tuned—you can tune a crystal oscillator a little, you know—so that their frequencies are only one kilocycle apart; and this means that the difference frequency of 1000 cycles comes

out of the mixer. Any movement of the brass diaphragm produced by pressure waves against it is translated into a frequency shift of the crystal oscillator associated with the condenser mike, and an accompanying change in the beat-frequency tone coming out of the mixer."

"Hey, old buddy, that's pretty sharp!" Carl applauded.

"Nothing any bored American boy shot full of antibiotics couldn't do!" Jerry replied modestly. "The roughest job was drilling two holes through the bottom of the glass jar without breaking it. Leads from the mixer come out one, and the other is covered with a brass disc with a very tiny hole punched in it with a needle. That keeps our mike from respond-



ing to very slow pressure changes caused by barometric variations, yet allows it to respond to waves with periods up to several minutes in length."

He switched on the tape recorder, and soon a 1000-cycle note was heard from the speaker. At the same time, a meter connected across the recorder speaker rose to half-scale.

"That's a simple audio frequency meter I've calibrated to indicate frequencies between 100 and 5000 cycles," Jerry answered Carl's questioning look. "We don't have any ink-on-paper recorders, but that meter pointer will swing back and forth in step with any low-frequency waves received. Tape-recording the changes in tone will give us a chance to double-check on any waves we think we observe. Now, let's see what happens when we test it out.

"I drop this little steel ball on the rubber membrane, like so, and this causes a very small increase in the pressure inside the bowl. See that meter kick down? If I've calculated right, it will

start creeping back in a couple of minutes as air leaks through the tiny hole to equalize the pressures on both sides of the diaphragm."

The microphone passed the test with flying colors. It responded to very small changes in pressure; yet, if the pressure was left applied, the tone returned to 1000 cycles in the space of a few minutes.

"Now all you need is that pipe pickup," Carl remarked.

"We've got it!" Jerry said promptly. "Didn't you notice that the men laying that new 8" gas line in the street stopped directly in front of the house last night? Welders will weld the joints together Monday and put the pipe down in the trench, but right now it stretches out to the west on top of the ground for a couple of thousand feet with the joints all neatly butted tight together. I'm hoping small air leaks at these joints will serve as the holes in the pipe used by the National Bureau of Standards.

"The beauty of it all is that the weather bureau has a tornado alert out for the area to the west of us. We may be lucky

enough to hear a tornado! Suppose you go out, Carl, and fasten our mike in the end of the pipe with this wooden collar, and run this twisted pair from it into the cellar window."

CARL carried out the assignment quickly because huge drops of rain had begun spattering down. When the wires were connected to the input of the tape recorder, the meter pointer immediately began to hunt restlessly up and down the scale.


"What we're looking for is a slow, rhythmic swing of the meter pointer," Jerry shouted above the roar of the wind outside, which had begun whipping up the trees and was now pounding furiously at Jerry's house.

But there was nothing slow or rhythmic about the pointer as it swung wildly up and down. Suddenly it began to go up and up, hesitated for a moment, and then fell back to zero and stayed there. The tone disappeared.

"Something's happened to our mike," Jerry shouted as he grabbed up his
(Continued on page 102)

BREAKTHROUGH in KIT DESIGN!

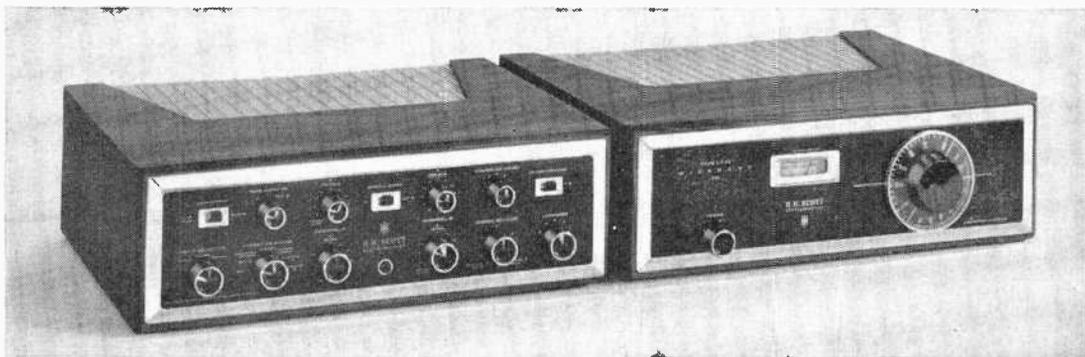H. H. Scott takes totally new approach . . . makes kits easier-to-build, better-performing!



LK-72 72-Watt Stereo Complete Amplifier kit (left), \$149.95, LT-10 Wide-Band FM Tuner kit (2.2µv sensitivity), \$89.95.*

BREAKTHROUGH! Here, for the first time, are kits with the performance, features and handsome good looks of H. H. Scott factory-assembled components . . . kits so expertly designed that you can achieve professional results in just a few hours.

Look at these innovations: ● All mechanical parts such as terminal strips and tube sockets are firmly pre-riveted to chassis. ● Every wire and cable is already cut to exact length and pre-stripped. ● Electronic parts are mounted on special cards in order used. ● Full color diagrams in easy-to-follow instruction book reduce errors. ● New Kit-Pak container acts as worktable.

See new H. H. Scott amplifier and tuner kits at your dealer. Why settle for less?

March, 1961

H. H. SCOTT

H. H. SCOTT Inc. 111 Powdermill Rd., Maynard, Mass.

Rush me complete technical specifications on H. H. Scott kits. Include your new "1961 Guide to Custom Stereo." 520-03

Name _____

Address _____

City _____ Zone _____ State _____

* Prices slightly higher West of Rockies.
Export: Telesco International Corp., 171 Madison Ave., N. Y. C.

A PROPHECY

For men and women with a sincere desire to succeed



“In the years that have passed since my days on the faculty of RCA Institutes, I have become even more firmly convinced that the individual who continues his education . . . particularly his technical education . . . is the individual who profits both as a thinking man and as a working man. Science and industry will reward you for your talents and energy. Out of your efforts may come inventions, new products, processes and services. There is everything good yet to be accomplished in our lives and in our work. What man has done, man can do better.”

David Sarnoff

Chairman of the Board,
Radio Corporation of America

RCA Institutes Offers the Finest of Home Study and Resident Training for Your Career in the Rapidly Expanding World of Electronics

RCA Institutes, founded in 1909, is one of the largest technical institutes in the United States devoted exclusively to electronics. A service of Radio Corporation of America, RCA Institutes offers unparalleled facilities for technical instruction . . . tailored to *your* needs. The very name “RCA”

means dependability, integrity, and scientific advance.

RCA Institutes Home Study School, licensed by the New York State Department of Education, offers a complete program of integrated courses for beginners and advanced students rang-

ing from electronic fundamentals to automation. All courses are designed to prepare you for a rewarding career in the rapidly expanding world of electronics. *The caliber of the training you receive is the finest!* And you get top recognition as an RCA Institutes graduate!

HOME STUDY COURSES in

Electronic Fundamentals • TV Servicing Color TV • Electronics for Automation • Transistors

Voluntary Tuition Plan. The important thing to remember about RCA Institutes Training is the convenient, *no-obligation payment plan*. This plan affords you the most economical possible method of home study training because you pay for each study group only when you order it. If you interrupt your course *at any time, for any reason*, you owe nothing more. You *never* have to pay for the whole course if you don't complete it. No other obligations. No monthly installment payments!



RCA Instruction is Personal. With RCA Home Study training you set *your own pace* in keeping with *your own ability*, finances, and time. The Institutes allows you ample time to complete the course. Your lesson assignments are individually graded by

technically trained personnel, and helpful comments are added where required. You get theory, experiment, and service practice beginning with the very first lesson. All lessons are profusely illustrated. You get a *complete training package* throughout the entire course.

You Get Prime Quality Equipment. All kits furnished with the course are complete in every respect, and the equipment is top grade. You keep all the equipment furnished to you for actual use on the job... *and you never have to take apart one piece to build another!*

* * *

RESIDENT SCHOOLS in

*Los Angeles and
New York City train
you for any field of
Electronics you may
choose!*

No Previous Technical Training Required For Admission. RCA Institutes Resident Schools in Los Angeles and New York City offer training that will prepare you to work in re-

warding positions on research and production projects in fields such as automation, communications, technical writing, television, computers, and other industrial and advanced electronics applications. Even if you did not complete high school, RCA will prepare you for such training with courses specially designed to provide the basic math and physics required for a career in electronics.

Free Placement Service. RCA Institutes graduates are now employed in important jobs at military installations such as Cape Canaveral, with important companies such as IBM, Bell Telephone Labs, General Electric, RCA, and in radio and TV stations all over the country. Many other graduates have opened their own businesses. A recent New York Resident School class had 92.06% of the graduates who used the Free Placement Service accepted by important electronics companies... *and had their jobs waiting for them on the day they graduated!*



Coeducational Day and Evening Courses. Day and Evening Courses are available at Resident Schools in New York City and Los Angeles. You can prepare for your career in electronics while continuing your normal full-time or part-time employment. Regular classes start four times each year.



**SEND POSTCARD FOR FREE
ILLUSTRATED BOOK TODAY!
SPECIFY HOME STUDY OR
RESIDENT SCHOOL**

RCA INSTITUTES, INC. A Service of Radio Corporation of America 350 W. 4th St., N.Y. 14, N.Y. • 610 S. Main St., Los Angeles 14, Calif.



The Most Trusted Name in Electronics

SAVE MORE with

• Tested for mutual con-
ductance in our labs! •
1-Yr. free replacement
guarantee! • Prompt re-
funds on defective mds.

SONAR TUBES

Type		Spec. Pur. & Trmtk.		and Ind. Tubes	
Type	Price	Type	Price	Type	Price
OA2	.60	1N120A	8.50	620H	7.00
OA3	.70	5R4GY	1.00	832	2.00
OA4	.75	6C6	6.50	832A	2.50
OH2	.40	614WA	1.15	806A	1.05
OB3	.60	218	.80	872A	1.05
OC3	.50	5129	.80	884	.80
OD3	.40	750TL	3.00	885	.30
2D21	.55	807	1.00	955	.30
2E26	1.05	813	8.50	955	.30
3A4	.45	815	1.00	955	.30

Type		Price		RECEIVING TUBES	
Type	Price	Type	Price	Type	Price
024	.42	2AP5	.88	51N	.49
1A7GT	.42	3B3C	.48	6U6G	.49
1B3GT	.42	3BZ6	.80	6X4	.49
1B4G	.42	3C26	.40	6V6G	.49
1B5GT	.42	3CF	.41	5V6GT	.45
1L4	.46	3CS6	.42	6Y3GT	.45
1L6	.39	3L4	.49	6Y4G	.45
1N5GT	.42	304	.49	6A4	.44
1Q5GT	.42	354	.44	6A4H	.44
1S5	.44	3V3	.44	6A7	.40
1T4	.39	4BQ7A	.44	6A7F	.40
1U4	.41	5AN8	.65	6AG5	.82
1U5	.41	5AR8	.65	6AG7	.44
1V2	.42	5AV8	.44	6AH6	.55
1V2	.49	5AW4	.44	6AH6GT	.55
2A3	.52	31K7	.39	6AK5	.42
		31K7	.38	6AL7	.49
		31K7	.38	6AV5	.48
		31K7	.38	250L6	.75
		31K7	.38	50C5	.47
		31K7	.38	50L6GT	.48

SONAR
ELECTRONIC TUBE CO.
112 Martin St.
Paterson 3, N. J.

All adv. tubes not nec. new, but may be elec. plet. fac. 21s or used. Ea. clearly marked. All price. incl. 25c ind. chg. Orders under \$5 Inc. 25% dep. on C.O.D.'s. Semi approx. pkg. on Canada & foreign orders. Write for comp. list of tubes & spec. purp. tubes.
89c each

CODE

TELEPLEX METHOD trains you to hear Code signals just as you hear spoken words—because it teaches Code SOUNDS and not dots and dashes. Thirty words with ease. Fifty words not unreasonable. Starts beginner on advances your present speed. Try it for yourself and compare with anything else. 40 years experience teaching Code here made the Teleplex Method far superior to all the cheap "gimmicks" on the market. Write today for details. You be the judge! (Improved cabinet allows new low cost.)



TELEPLEX CO.

739-C Kazmir Court, Modesto, Calif.

Canadian Representative: THE HAM SHACK
1269 Granville St., Vancouver, B.C.

"Blame the Radio Man's," 64 Dey St., New York City

double your income with degree

A college education is a good investment! More rapid advancement, too. Important firms like Tri-State College graduates . . . return regularly to interview seniors on campus. Become an Electronics Engineer. Qualify faster here. Bachelor of Science Degree in 27 Months in Electrical (Electronics or Power major), Mechanical, Chemical, Aeronautical, Civil Engineering. IN 36 MONTHS B.S. in Business Administration (General Business, Accounting, Motor Transport Management majors). For earnest, capable, mature students. Small classes. More professional class hours. Beautiful campus. Well-equipped labs. modernized buildings, new dorms. Year-round operation. Enter June, Sept., Jan., Mar. Founded 1884. Write J. D. McCarthy, Director Admissions, for Catalog and "Your Career in Engineering and Commerce" Book.

TRI-STATE COLLEGE

3631 College Avenue
Angola, Indiana


jacket and headed for the door. At the top of the steps he stopped dead in his tracks and stared up into the northwestern sky. Carl, looking over his shoulder, saw the writhing, twisting, unmistakable shape of a small tornado funnel high above the ground and moving off to the north. Even as the boys watched, the little tornado disintegrated.

They raced over to the pipe and pulled out their mike. The thin brass diaphragm was ruptured, with the jagged corners curled outward somewhat like the petals of a flower.

"Jer, look way down there at the other end of the pipe," Carl said in awe. Jerry followed his pal's pointing finger and saw that the straight line of the pipe was broken four or five blocks away, and the sections of pipe were scattered over the street like jackstraws. A small temporary tool house nearby had been smashed to kindling and the tools strewn about like scraps of paper.

"That little twister must have dabbed down squarely on top of the pipe and then hopped back up," Carl said thoughtfully.

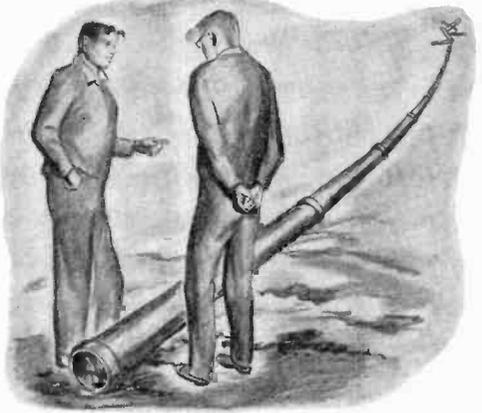"Yeah, and it sucked on that end of the pipe hard enough to bust our mike



diaphragm at this end," Jerry finished. "The tornado dealt us a low blow. We aren't really sure our infrasonic mike works."


"I'm not complaining," Carl said philosophically as he started back for the house. "We're mighty lucky the twister was sucking on *that* end of the pipe and not on *our* end!"



REALISTIC PORTABLE V-O-M TEST KIT
\$12.95
 \$2 down



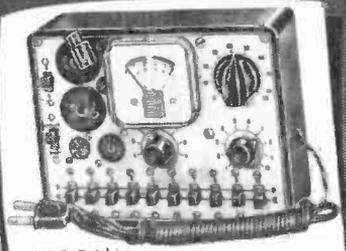Gonset G-11 Citizen's Band 2-Way Radio **\$84.50**
 \$5 down



BARGAIN PORTABLE TUBE CHECKER KIT **\$14.80**
 \$2 down

Our own exclusive low priced portable test instrument kit! Efficient, accurate, stable. Checks batteries, line voltage, tests continuity of circuits. Ideal for home repair of TV, radio, appliances. 4 1/2" easy-to-read meter face dial and 400 μ a movement. 14 AC/DC scales to 5000 V. 8 AC/DC current scales. 3 ohms scales! 6 db scales, 6 output scales. 6 3/4 x 5 1/4 x 3" bakelite case. Simple instructions. Ship. wt. 3 lbs.
No. 7-96L079—Mailable... \$12.95

Exclusive special purchase to sell at \$40 off net price while they last! Famous Gonset "communicator" transmitter transmits, receives within 25-mile range! For car, tractor, boat, plane—or fixed station. Press button to talk, release to listen. Ceramic mike, crystals for 1 channel. Noise eliminator, adjustable "squelch." Mounting bracket. No exam needed—fill out FCC form for license.
No. 7-45DX785—117 VAC 3303 }
No. 7-45DX786—12 VDC 3304 }
 (Express, ship. wt. 10 lbs.)... **\$84.50**

Weights only 2 1/4 lbs., yet performs like larger, costlier units! Tests octal, loc-tal, 9-prong, 7-prong miniature tubes for radio, hi-fi, TV. Tests emission, shorts, leaks, opens, intermittents. Easy-to-read meter. Complete with tube chart, operating manual. Operates on 105-130 VAC, 60 cycles. Precision crafted—ideal for radio-TV servicemen, technicians, amateurs. Wt. 3 lbs. Mailable.
No. 7-94L002—Kit..... \$14.80
No. 7-94L001—Wired.... \$18.80



MERCURY-M TYPE MODEL OUTBOARD MOTOR
99c


This little M bargain turns your model boat into a speed demon! Lightweight die-cast aluminum construction, battery operated on 1.5 to 4.5 volts. Has battery clips, switch lever, swirl mount, stern clamps. 4 in. high.
No. 7-98L366—Ship. wt. 8 oz. Mail .99c

ELECTRONIC PARTS
88c pkg.



50 PIGTAIL RESISTORS—shown. 1/2 watt. size with long axial leads. Std. color code.
No. 7-95L167—Ship. wt. 1 lb... Pkg. 88c
 25 CERAMIC DISCS. Popular sizes. Made by Centralab, Sprague, etc. For all builders.
No. 7-95L283—Ship. wt. 1 lb... Pkg. 88c
 25 MICA CONDENSERS including silver and standard RMA and JAN types.
No. 7-95L146—Ship. wt. 1 lb... Pkg. 88c
 Above packages mailable

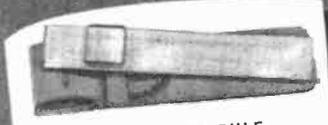Save money ON GUARANTEED EQUIPMENT AND PARTS from RADIO SHACK
 Order Direct from this page



5" POCKET SLIDE RULE In Leather Case **\$2.69**
 Sturdy 9-scale bamboo slide rule by Micronta performs most functions of \$7 rules! Multiplies, divides, calculates squares, sq. roots, cubes, cube roots. Reference equivalents, formulae on back. Wt. 2 oz.
No. 7-97L820—Mail. \$2.69

RADIO SHACK Corporation
 where millions of hobbyists and pros shop by mail
730 Commonwealth Avenue Boston, Massachusetts

Immediate Delivery! Use this handy order blank

RADIO SHACK CORP. Dept. 61C7
 730 Commonwealth Ave., Boston, Massachusetts
 Check or M.O. enclosed for full amount
 Open an Easy Budget Account for me. Check or M.O. enclosed for down payment

Your Name _____ print
 Street _____
 City _____ Zone _____ State _____

Item No.	Quantity	Name of Item	Unit Price	Total

Total cost of items
 (Down Payments: \$2 down on orders up to \$45; \$5 down on orders \$50 to \$180. Add postage charges; all excess refunded. All items mailable except 2-way radio shipped express delivery charges collect.)

Flip-Flop Circuits

(Continued from page 62)

quickly dropped to ground potential because one side of the switch is grounded. The sudden rise in voltage from -7 volts to zero is actually a positive pulse which is coupled through *C2*, and through conducting diode *D2*, to the base of *Q2*.


Although the same positive pulse passes through *C1* to the anode of *D1*, it is not large enough to overcome the negative bias on the diode. When the positive pulse is applied to *Q2*'s base, the circuit switches its conducting state and is ready for the next pulse. Now, a positive pulse will pass through diode *D1* to the base of *Q1* because the voltages

which bulb will light—this will depend solely on which transistor was conducting before the button was depressed.

The reset switch, *S2*, is the answer to our problem. By depressing it before any count is made, we enable *D3* to apply a positive voltage through *D3* to the base of *Q1*, cutting off the transistor. Now, *I1* is out and *I2* is on, indicating a count of "zero." Although *I2* should be in the circuit for balance, you can paint its glass so that it will show no light, since it is not used for counting.

With our flip-flop in operation, pressing *S1* will turn *I1* "on," indicating a count of "one." Pressing *S1* a second time will return the lamp to the "off" state, indicating zero again. Although a single flip-flop such as this one can only

Fig. 5. Seven-volt power supply which can be constructed to power the flip-flop circuit in Fig. 4.

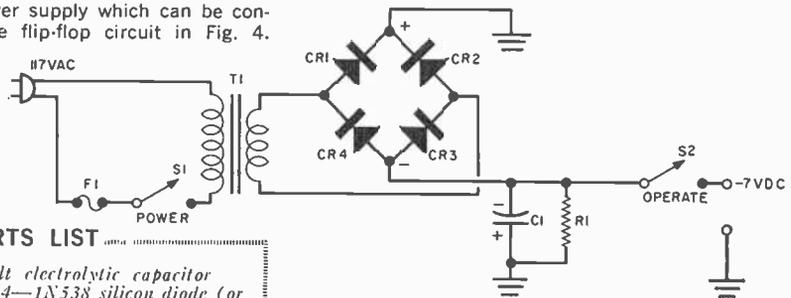

PARTS LIST

- C1*—1000- μ F., 10-volt electrolytic capacitor
- CR1, CR2, CR3, CR4*—1N538 silicon diode (or equivalent)
- F1*—1-amp. fuse
- R1*—10,000-ohm, 1/2-watt resistor
- S1, S2*—S.p.s.t. toggle switch
- T1*—Filament transformer; 117-volt primary; 6.3-volt, 3-amp. secondary. (*T* not used (Knight 62G031 or equivalent))

seen by the diodes are reversed—refer back to Fig. 2 (A). The circuit will continue to flip and flop depending upon the number of positive pulses supplied to it.

Counting. The only things left unexplained about Fig. 4 are the two lamps and the reset circuit. The lamps indicate which transistor is conducting. When *Q1* conducts, the large current passed by it must pass through *I1*. At the same time, *I2* is not illuminated because *Q2* is cut off. These lamps are useful in determining how many positive pulses are supplied by the count switch, *S1*.

Let's assume the count switch is depressed only once. Although one bulb will go out and the other will come on, we as yet have no way of determining

indicate counts of zero and one by itself, other flip-flops can be added to the circuit and higher counts obtained. How this is done will be explained in the next issue of POPULAR ELECTRONICS. Binary counting will also be covered.

Build a Flip-Flop. In the meantime, so that you will fully understand how flip-flop circuits work, we suggest that you build the circuit shown in Fig. 4.

Measure the voltages at the terminals of the transistors and see how they agree with the theory discussed in this article. There may be slight voltage variations between the circuit you build and the values given in Figs. 2 (A) and 2 (B), but this is to be expected due to variations in tolerances of the components. Breadboard your circuit, keeping in mind that you will want to reuse the parts in circuits which will appear next month.

Figure 5 is the schematic diagram of a seven-volt power supply for the flip-flop. If you build it, wire it neatly—you will be using it again.

BUILD 20 RADIO

CIRCUITS AT HOME
with the New Deluxe

PROGRESSIVE RADIO "EDU-KIT"®
A Practical Home Radio Course

ONLY
\$26.95



Reg U.S.
Pat Off.

Now Includes

- ★ 12 RECEIVERS
- ★ 3 TRANSMITTERS
- ★ SQ. WAVE GENERATOR
- ★ SIGNAL TRACER
- ★ AMPLIFIER
- ★ SIGNAL INJECTOR
- ★ CODE OSCILLATOR
- ★ No Knowledge of Radio Necessary
- ★ No Additional Parts or Tools Needed
- ★ EXCELLENT BACKGROUND FOR TV
- ★ School Inquiries Invited
- ★ Sold in 79 Countries

**YOU DON'T HAVE TO SPEND
HUNDREDS OF DOLLARS FOR A RADIO COURSE**

The "Edu-Kit" offers you an outstanding PRACTICAL HOME RADIO COURSE at a rock-bottom price. Our Kit is designed to train Radio & Electronics Technicians, making use of the most modern methods of home training. You will learn radio theory, construction practice and servicing. THIS IS A COMPLETE RADIO COURSE IN EVERY DETAIL. You will learn how to build radios, using regular schematics; how to wire and solder in a professional manner; how to service radios. You will work with the standard type of punched metal chassis as well as the latest development of Printed Circuit chassis. You will learn the basic principles of radio. You will construct, study and work with RF and AF amplifiers and oscillators, detectors, receivers, test equipment. You will learn and practice code, using the Progressive Code Oscillator. You will learn and practice trouble-shooting, using the Progressive Signal Tracer, Progressive Signal Injector, Progressive Dynamic Radio & Electronics Tester, Square Wave Generator and the accompanying Instructional material. You will receive training for the Novice, Technician and General Classes of F.C.C. Radio Amateur Licenses. You will build 20 Receiver, Transmitter, Square Wave Generator, Code Oscillator, Signal Tracer and Signal Injector circuits, and learn how to operate them. You will receive an excellent background for television, Hi-Fi and Electronics. Absolutely no previous knowledge of radio or science is required. The "Edu-Kit" is the product of many years of teaching and engineering experience. The "Edu-Kit" will provide you with a basic education in Electronics and Radio, worth many times the complete price of \$26.95. The Signal Tracer alone is worth more than the price of the entire Kit.

THE KIT FOR EVERYONE

You do not need the slightest background in radio or science. Whether you are interested in Radio & Electronics because you want an interesting hobby, a well paying business or a job with a future, you will find the "Edu-Kit" a worth-while investment. Many thousands of individuals of all

ages and backgrounds have successfully used the "Edu-Kit" in more than 75 countries of the world. The "Edu-Kit" has been carefully designed, step by step, so that you cannot make a mistake. The "Edu-Kit" allows you to teach yourself at your own rate. No instructor is necessary.

PROGRESSIVE TEACHING METHOD

The Progressive Radio "Edu-Kit" is the foremost educational radio kit in the world, and is universally accepted as the standard in the field of electronics training. The "Edu-Kit" uses the modern educational principle of "Learn by Doing." Therefore you construct, learn schematics, study theory, practice trouble-shooting—all in a closely integrated program designed to provide self-learning, thorough and interesting background in radio. You begin by examining the various radio parts of the "Edu-Kit." You then learn the function, theory and wiring of these parts. Then you build a simple radio. With this first set you will enjoy listening to regular broadcast stations, learn theory, practice testing and trouble-shooting. Then you build a more advanced radio, learn more advanced theory and techniques. Gradually, in a progressive manner, and at your own rate, you will find yourself constructing more advanced multi-tube radio circuits, and doing work like a professional radio technician. Included in the "Edu-Kit" course are twenty Receiver, Transmitter, Code Oscillator, Signal Tracer, Square Wave Generator and Signal Injector Circuits. These are not unprofessional "breadboard" experiments, but genuine radio circuits, constructed by means of professional wiring and soldering on metal chassis, plus the new method of radio construction known as "Printed Circuitry." These circuits operate on your regular AC or DC house current.

THE "EDU-KIT" IS COMPLETE

You will receive all parts and instructions necessary to build 20 different radio and electronics circuits, each guaranteed to operate. Our Kits contain tubes, tube sockets, variable, electrolytic, mica, ceramic and paper dielectric condensers, resistors, tie strips, coils, hardware, tubing, punched metal chassis, Instructions Manuals, hook-up wire, solder, selenium rectifiers, volume controls and switches, etc. In addition, you receive Printed Circuit materials, including Printed Circuit chassis, special tube sockets, hardware and instructions. You also receive a useful set of tools, a professional electric soldering iron, and a self-powered Dynamic Radio and Electronics Tester. The "Edu-Kit" also includes Code Instructions and the Progressive Code Oscillator, in addition to F-C-type Questions and Answers for Radio Amateur License training. You will also receive lessons for servicing with the Progressive Signal Tracer and the Progressive Signal Injector, a High Fidelity Guide and a Quiz Book. You receive Membership in Radio-TV Club, Free Consultation Service, Certificate of Merit, Discount Privileges. You receive all parts, tools, instructions, etc. Everything is yours to keep.

FREE EXTRAS

- SET OF TOOLS
- SOLDERING IRON
- ELECTRONICS TESTER
- PLIERS-CUTTERS
- ALIGNMENT TOOL
- WRENCH SET
- VALUABLE DISCOUNT CARD
- CERTIFICATE OF MERIT
- TROUBLE-SHOOTING MANUAL
- HIGH FIDELITY GUIDE + QUIZZES
- TELEVISION BOOK + RADIO
- TROUBLE-SHOOTING BOOK
- MEMBERSHIP IN RADIO-TV CLUB
- CONSULTATION SERVICE + FCC
- AMATEUR LICENSE TRAINING
- PRINTED CIRCUITRY

SERVICING LESSONS

You will learn trouble-shooting and servicing in a progressive manner. You will practice repairs on the sets that you construct. You will learn symptoms and causes of trouble in home, portable and car radios. You will learn how to use the professional Signal Tracer, the unique Signal Injector and the dynamic Radio & Electronics Tester. While you are learning in this practical way, you will be able to do many a repair job for your friends and neighbors, and charge fees which will far exceed the price of the "Edu-Kit." Our Consultation Service will help you with any technical problems you may have.

FROM OUR MAIL BAG

J. Statalis, of 25 Poplar Pl., Waterbury, Conn., writes: "I have repaired several sets for my friends, and made money. The "Edu-Kit" paid for itself. I was ready to spend \$240 for a Course, but I found your ad and sent for your Kit."
Bnn Valerio, P. O. Box 21, Magna, Utah: "The Edu-Kits are wonderful. Here I am sending you the questions and also the answers for them. I have been in Radio for the last seven years, but like to work with Radio Kits, and like to build Radio Testing Equipment. I enjoyed every minute I worked with the different kits; the Signal Tracer works fine. Also like to let you know that I feel proud of becoming a member of your Radio-TV Club."
Robert L. Shuff, 1534 Monroe Ave., Huntington, W. Va.: "Thought I would drop you a few lines to say that I received my Edu-Kit, and was really amazed that such a bargain can be had at such a low price. I have already started repairing radios and phonographs. My friends were really surprised to see me get into the swing of it so quickly. The Troubleshooting Tester that comes with the kit is really swell, and finds most trouble, if there is any to be found."

UNCONDITIONAL MONEY-BACK GUARANTEE

**ORDER DIRECT FROM AD—RECEIVE FREE BONUS
RESISTOR AND CONDENSER KITS WORTH \$7**

- Send "Edu-Kit" postpaid. I enclose full payment of \$26.95.
- I enclose \$5.00. Send "Edu-Kit" C.O.D. for balance plus postage.
- Rush me FREE descriptive literature concerning "Edu-Kit."

Name _____
Address _____

PRINTED CIRCUITRY

At no increase in price, the "Edu-Kit" now includes Printed Circuitry. You build a Printed Circuit Signal Injector, a unique servicing instrument that can detect many Radio and TV troubles. This revolutionary new technique of radio construction is now becoming popular in commercial radio and TV sets. A Printed Circuit is a special insulated chassis on which has been deposited conducting material which takes the place of wiring. The various parts are merely plugged in and soldered to terminals. Printed Circuitry is the basis of modern Automation Electronics. A knowledge of this subject is necessary today for anyone interested in Electronics.

PROGRESSIVE "EDU-KITS" INC.

1186 Broadway, Dept. 578D, Hewlett, N. Y.



Send
POPULAR
ELECTRONICS
Every
Month

name _____
address _____
city _____ zone _____ state _____

- Check one: 3 years for \$10
 2 years for \$7
 1 year for \$4

Payment Enclosed Bill Me

In the U. S., its possessions and Canada, Foreign rates: Pan American Union countries, add .50 per year; all other foreign countries, add \$1 per year.

Mail to: **POPULAR ELECTRONICS**
Dept. PE-361H, 434 S. Wabash Ave., Chicago 5, Ill.

PURCHASING A HI-FI SYSTEM?

TIME PAYMENTS AVAILABLE
Up to 2 Years to Pay!

Send Us
Your List of
Components
For A Package
Quotation

YOU CAN BUY WITH
CONFIDENCE AT AIREX
All merchandise is brand new,
factory fresh and guaranteed.

Free Hi-Fi Catalog

AIREX
RADIO
CORPORATION

85-PE Cortlandt St., N. Y. 7 CO 7-2137

- Jim Lansing*
- Altec Lansing
- Electrovoice
- Jensen • Hartley
- University • Viking
- Acoustic Research
- Janszen • Sperscope
- Wharfedale
- USL Citizen Band
- Gonset • Hallicrafter
- Texas Crystals
- Concertone
- Bell • G.E.
- Weather's
- Harman-Kardon
- Eico • Pilot • Fisher
- ESL • Roberts
- Bogen • Leak • TEC
- Dynakit • H. H. Scott
- Thorens* • Sherwood*
- Dual Changer
- DeWald
- Sony • Challenger
- Wollensak • Pentron
- Garrard • Quad*
- Miracord • Pickering
- Glaser-Steers
- Components
- Rek-O-Kut • Tandberg*
- Audio Tape • Conrac
- Norelco • Magnecord*
- Fairchild • Gray
- Artizan Cabinets
- Rockford Cabinets

*Fair Traded

The Danger of Radar Waves

(Continued from page 45)

turned off, they recovered immediately. Rats reacted the same way.

No one is certain why this strange behavior takes place, but here's the best theory devised to explain it so far. At certain frequencies, signals apparently resonate with certain nerve paths, or the spinal cord, "short-circuiting" the normal electrical signals the brain sends the muscles to control them. The case clearly points up the fact that there are still many unanswered questions about how microwaves affect us.

Safety Pays Off. The fact that only two known cases of death or injury have been reported in this country—and even these are not confirmed—is testimony to the fact that adequate precautions are being taken where hazards exist. Air Force scientists at Rome Air Force Development Center have concluded that no microwave damage of any kind has ever been observed unless the experimental animal was absorbing at least 0.2 watt of microwave energy for every square centimeter of surface area. To put it another way, to be in danger, they had to absorb more than a watt per square inch of exposed skin.

Since 0.2 watt/sq. cm. is the danger level for animals, and man can probably stand more, the Air Force plays it extra safe by specifying that personnel shall be exposed to radiation fields no greater than one-twentieth that amount, or 0.1 watt/sq. cm.

Most companies observe the same standards but a few are even more conservative. Operators of the *Distant Early Warning* radar network which stretches across northern Canada, for example, have set 0.001 watt/sq. cm.—one-tenth as much as the Air Force—as the exposure limit.

Industry and the armed services go to great lengths to protect personnel from radiation exceeding these limits. International Telephone and Telegraph Company, for example, interlocks all dangerous areas. The radar antenna on top of the ITT tower in urban Nutley, N. J., is not dangerous from the ground—but it would be from the radar platform. So the trap door on the roof leading to the

Always say you saw it in—POPULAR ELECTRONICS

antenna is interlocked: open the trap door and you automatically kill the antenna power.

BMEWS Protection System. Undoubtedly the most elaborate preventive measures ever taken are now in effect at the Air Force's BMEWS station in Thule, Greenland. Its huge radars put out pulses of microwave energy at the incredible power level of ten million watts.

The transmitter building is especially shielded to protect technicians from the tremendous radiation. The covered passageways are also solidly shielded—ceiling, walls, even floors—so that crews can go from one building to the other with the radars in operation.

Shielding of the buildings and passageways presented quite a few problems during construction. Even though the walls were made of galvanized steel sheeting, too much radiation energy got through. So first all joints were welded to eliminate cracks. Then, two layers of copper screen were added inside where necessary. And this was topped off in particularly troublesome spots with concrete.

Even small holes in the screen let in too much radiation. Every one of them had to be patched and soldered. Special ventilators that would let in air but not radiation had to be designed and tested.

With all buildings carefully shielded, only one more serious problem remained. Sub-zero temperatures and howling arctic blizzards are prevalent during winter in Greenland. No equipment can stand up forever under such punishment, and outside repairs must be made from time to time. The problem was to figure out a way to make repairs without turning off the radar or cooking the personnel.

The answer: radiation suits designed and built by the Wright Air Development Command especially for BMEWS workers. With this modern-day armor, technicians are able to work safely in r.f. fields that would kill an unprotected man in minutes.

Beneficial Uses. While most of the problems of protecting electronic workers from radiation have now been pretty well solved, scientists are vitally aware that there is a great deal they don't know about radiation and its biological effects. But this knowledge gap is fast being bridged. Both military and civilian scientists are pressing forward at top speed

UNLIMITED OPPORTUNITIES FOR ELECTRO-MECHANICAL TECHNICIANS

DENVER, COLO.

TULSA, OKLA.


FT. WORTH, TEX.

JACKSONVILLE, FLA.

DALLAS, TEX.

OKLAHOMA CITY, OKLA.

WICHITA, KANS.

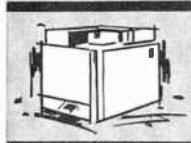

Prepare Now in the Glorious Southland

By training with the most advanced equipment, utilizing latest text materials, under the guidance of top educators, our graduates are qualified to pass F.C.C. examinations for high paying jobs in communications, equipment, etc. and capable of understanding the design, installation, maintenance and repair of ELECTRO-MECHANICAL devices from electrical typewriters to complex computers.

With our training you gain mastery of the technical-engineering areas of Manufacturing Automation, Office Automation, Missile Development, Space Technology, etc.

Class rooms are deliberately kept small for individual career planning of each student. Laboratory work is stressed.

Each of our nationally associated colleges is co-educational and as they are located in the heart of America's fastest growing ELECTRONIC CORE, many students finance their way thru student employment service and industry cooperative programs.

CLASSES NOW STARTING IN

Nationally Recognized curriculum developed by Philco and R.C.A. laboratories and used by leading Service and Academic Colleges Coast to Coast.

If the field of ELECTRO-MECHANICAL is your ambition, if you want top training, quickly, completely, under the most favorable of conditions on an earning, learning, self-supporting basis

MAIL THIS COUPON FOR FREE BOOK

ASSOCIATION OF ELECTRO-MECHANICAL COLLEGES
411-B W. Belknap, Ft. Worth, TEXAS

Please send me free book, full facts. I am especially interested in your school in:

Dallas Denver Tulsa Ft. Worth
 Jacksonville Okla. City Wichita

Name Age.....
Address
City Zone..... State.....

ying to unravel a few of the mysteries ill surrounding the subject.

At the Fourth Annual Tri-Service Microwave Conference held in New York last summer, researchers made some startling disclosures. Lt. Col. Sven A. Bach of the Army Medical Research Laboratory in Fort Knox, Kentucky, for example, told how he had discovered a "profound molecular change" in human gamma globulin which had been subjected to microwave radiation at certain frequencies. Said Bach, the gamma globulin molecules showed "at least a fourfold increase in biological activity."

What does this mean to you? Gamma globulin plays an important part in the body's defenses against disease. Speed up its activity fourfold and it may be four times as effective a disease fighter. Some day your doctor may give you "a shot of microwave" to keep you well.

Dr. Joe Howland of the University of Rochester found that dogs which had been exposed to microwaves were able to withstand heavy doses of X rays far better than dogs not so treated. No spe-

cific application for this technique is now known, but such discoveries frequently lead to undreamed-of advances.

And, finally, some evidence has been gathered to indicate that certain kinds of cells, under the right conditions, will simply disintegrate—fly to pieces—in the presence of the right radiation. But surrounding cells are unaffected. Could such a selective beam ever be used to destroy cancer cells while leaving healthy tissue unaffected? Scientists don't yet know.

Said Col. George M. Knauf, one of the foremost experts on the biological effects of microwaves, speaking of these recent advances, "Our work has progressed sufficiently for us to be fairly certain that the beneficial uses to which this energy may be put will greatly outweigh any harmful results it may produce in men."

All this, of course, does not mean we should forget that uncontrolled microwave energy can be dangerous. But like fire or X rays, microwaves can, when used intelligently and with understanding and respect for the hazards involved, be among man's most valuable tools. —50—

SCIENCE ENGINEERING

B.S. Degree—36 mos. • B.E. degree—27 mos.

Accelerated year-round program. Aero., Chemical, Civil, Elec., Mech., Metallurgical; Math., Chemistry, Physics. Modest rate. Earn board. New classes start March, June, Sept., Jan. Catalog. 2331 E. Washington Blvd., Fort Wayne 2, Indiana.

INDIANA TECHNICAL COLLEGE



HEADS YOU WIN!

Yes, you'll be a winner every time by saving "heap plenty" on all of your high fidelity requirements. Write us and see! Ask too for audio discount catalog A-12.

KEY ELECTRONICS

120 Liberty St., N. Y. 6, N. Y.

NEVER FAIL— ZONE YOUR MAIL

The Post Office has divided 106 cities into postal delivery zones to speed mail delivery. Be sure to include zone number when writing to these cities; be sure to include **your** zone number in **your** return address—after the city, before the state.

new! 7-Band SWL/DX Dipole Kit for 11·13·16·19·25·31·49 meters

Here's a low cost 7-band receiving dipole antenna kit that will pick up those hard-to-get DX stations. Everything included . . . just attach the wires and you're on the air! Weatherproof traps enclosed in Poly-Chem for stable all-weather performance. Over-all length of antenna - 40 feet.

Complete with

8 Trap Assemblies

Transmission Line Connector
Insulators

45 ft. No. 16 Tinned Copper Wire
100 ft. of 75 ohm twin lead

WRITE FOR NAME OF NEAREST DISTRIBUTOR

SWL-7 \$14.75

Mosley Electronics, Inc. 4610 N. Lindbergh • Bridgeton, Missouri

Short-Wave Monitor Registration

If you haven't registered for your Short-Wave Monitor Certificate and call letters, fill out this form and mail it with ten cents in coin to: Monitor Registration, POPULAR ELECTRONICS, One Park Ave., New York 16, N. Y. Include *stamped, self-addressed* envelope so we can mail your certificate at once. If you live outside the United States, send two International Reply Coupons or equivalent value postage stamps. Canadians may send fifteen cents in coin.

(Please Print)

Name

Address City State

Receiver Make Model

Make Model


Principal SW Bands Monitored Number of QSL Cards Received

Type of Antenna Used

Signature Date

TV-RADIO Servicemen or Beginners...

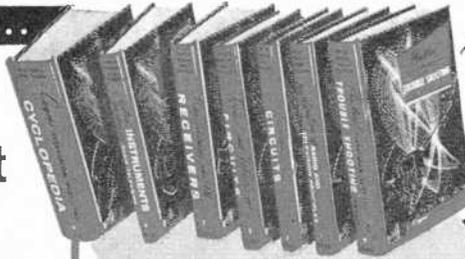Send for *Coyne's*
7-Volume Job-Training Set
on 7-Day **FREE TRIAL!**



The First
Practical
TV-RADIO-
ELECTRONICS
Shop
Library!

Answers ALL Servicing Problems QUICKLY . . .
Makes You Worth More On The Job!

Put money-making, time-saving TV-RADIO-ELECTRONICS know-how at your fingertips—examine Coyne's all-new 7-Volume TV-RADIO-ELECTRONICS Reference Set for 7 days at our expense! Shows you the way to easier TV-Radio repair—time saving, practical working knowledge that helps you get the BIG money! How to install, service and align ALL radio and TV sets, even color-TV, UHF, FM and transistorized equipment. New photo-instruction shows you what makes equipment "tick." No complicated math or theory—just practical facts you can put to use immediately right in the shop, or for ready reference at home. Over 3000 pages; 1200 diagrams; 10,000 facts!

SEND NO MONEY! Just mail coupon for 7-Volume TV-Radio Set on 7-day FREE TRIAL! We'll include the FREE BOOK below. If you keep the set, pay only \$3 in 7 days and \$3 per month until \$27.25 plus postage is paid. Cash price only \$24.95. Or return set at our expense in 7 days and owe nothing. Either way, the FREE BOOK is yours to keep. Offer limited, so act NOW!

Like Having An Electronics Expert Right At Your Side

- VOL. 1—EVERYTHING ON TV-RADIO PRINCIPLES! 300 pages of practical explanations; hundreds of illustrations.
- VOL. 2—EVERYTHING ON TV-RADIO-FM RECEIVERS! 400 pages; fully illustrated.
- VOL. 3—EVERYTHING ON TV-RADIO CIRCUITS! 336 pages; hundreds of illustrations, circuit diagrams.
- VOL. 4—EVERYTHING ON SERVICING INSTRUMENTS! How they work, how to use them, 368 pages; illustrated.
- VOL. 5—EVERYTHING ON TV TROUBLESHOOTING! Covers all types of sets, 437 pages; illustrations, diagrams.
- VOL. 6—TV CYCLOPEDIA! Quick and concise answers to TV problems in alphabetical order, including UHF, Color TV and Transistors; 868 pages.
- VOL. 7—TRANSISTOR CIRCUIT HANDBOOK! Practical Reference covering Transistor Applications; over 200 Circuit Diagrams; 410 pages.

BOOKS HAVE BRIGHT, VINYL CLOTH WASHABLE COVERS

FREE BOOK—FREE TRIAL COUPON!

Educational Book Publishing Division
COYNE ELECTRICAL SCHOOL
1455 W. Congress Parkway, Dept. 31-PE, Chicago 7, Ill.
Yes! Send me COYNE'S 7-Volume Applied Practical TV-RADIO-ELECTRONICS Set for 7-Days FREE TRIAL, per offer. Include "Patterns & Diagrams" book FREE!

Name Age

Address

City Zone State

Check here if you want Set sent C.O.D. Coyne pays postage on C.O.D. and cash orders. 7-Day Money-Back Guarantee.

"LEARNED MORE FROM THEM THAN FROM 5 YEARS WORK!"
"Learned more from your first two volumes than from 5 years work."
—Guy Bliss, New York
"Well set for either the serviceman or the beginner. Every service bench should have one."
—Melvin Masbruch, Iowa.

FREE DIAGRAM BOOK!

We'll send you this big book, "150 Radio-Television Picture Patterns and Diagrams Explained" ABSOLUTELY FREE just for examining Coyne's 7-Volume Shop Library on 7-day FREE TRIAL! Shows how to cut servicing time by reading picture-patterns, plus schematic diagrams for many TV and radio sets. Yours FREE whether you keep the 7-Volume Set or not! Mail coupon TODAY!




Coyne Educational Book Publishing Division
ELECTRICAL SCHOOL
1455 W. Congress Parkway Dept. 31-PE Chicago 7, Illinois




83 YX 929. Stereo Tape Record-Play Preamp Kit. \$79.95 (less case)

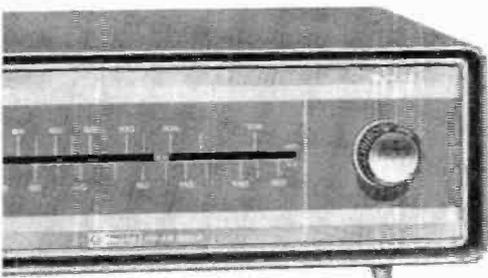One of the many great Knight-Kit stereo component kits. Professional quality; superb performance with virtually any 3-head tape transport; separate dual-channel recording and playback preamps; permits tape monitoring, sound-on-sound and echo effects. Packed with quality features for every possible stereo and monophonic function...



83 YX 928. FM-AM Hi-Fi Tuner Kit. \$49.95

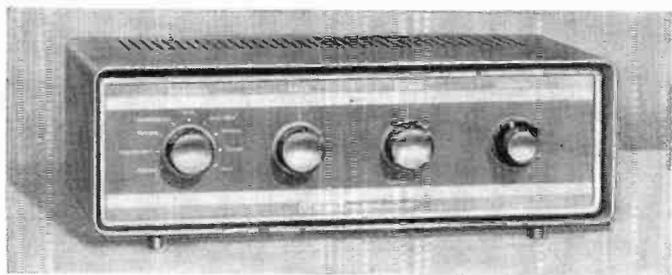Typical Knight-Kit hi-fi value—incomparable at the price. With AFC, tuned RF stage on FM, multiplex jack. Straight FM tuner kit also available at \$38.95. For deluxe Stereo FM-AM and FM tuner kits, see the Allied catalog...



83 YX 927. 20-Watt Stereo Hi-Fi Amplifier Kit. \$39.95


Biggest bargain in quality Stereo hi-fi. Has special clutch-type dual-concentric level control; simplified control facilities; DC preamp filaments. Similarly styled 32-Watt Stereo Amplifier Kit with full frequency center channel available at a low, low \$59.95...

Simply
these and 59
knights
A PRODUCT

a pleasure to build...

The most satisfying do-it-yourself experience awaits you when you build a Knight-Kit! You'll marvel at the sheer ease of assembly, absolutely assured by exclusive "show-how" manuals, wall-sized picture diagrams, step-by-step do-and-check instructions, pre-cut wire, "visi-packed" parts and an engineering perfection that eliminates guesswork. You'll get perfect results. You'll enjoy with pride a true custom-built electronic product, professionally engineered and styled—the best you can own. And to top off your pleasure, you'll save substantially at the unbeatable Knight-Kit price...

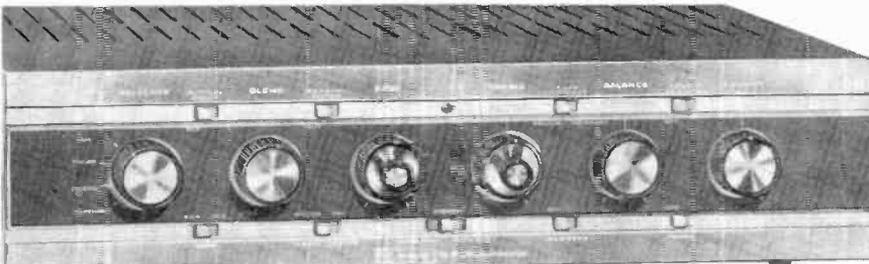83 YU 934. Deluxe 70-Watt Stereo Hi-Fi Amplifier Kit. \$119.95




Super-power to drive any of today's speakers, a do-it-yourself stereo masterpiece, featuring: special "blend" control; full-range center channel; tape-source monitor; dual phasing switches; Stereo paralleling switch. For deluxe 40-watt Stereo amplifier at only \$76.95, and 60-watt Stereo amplifier, see the Allied catalog...



83 YX 712-2. Superhet
Citizen's Band
Transceiver Kit.
\$79.95

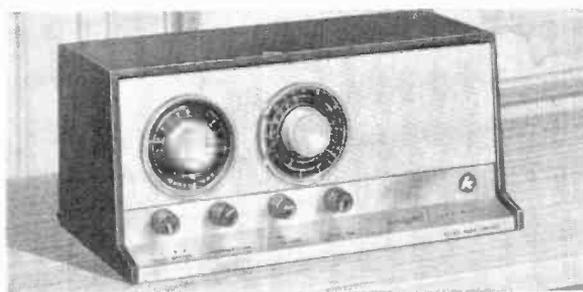Dual-conversion for highest sensitivity and selectivity; crystal-controlled operation on any 2 channels, plus manual tuning. Another Knight-Kit Citizen's Band Transceiver is available at an amazing low \$39.95—see the Allied catalog for full details...




83 YX 258. 4-Band "Span Master"® Receiver Kit. \$25.95

Fabulous performer for world-wide reception; thrilling shortwave adventures, plus fine Broadcast band-switching, 540 KC to 30 MC; with cabinet. For additional receiver kits, radio-intercom, clock-radio, transistor radios, intercom systems, electronic labs and other great hobbyist Knight-Kits, see the Allied catalog...

83 Y 125. Electronic VTVM Kit. \$25.75

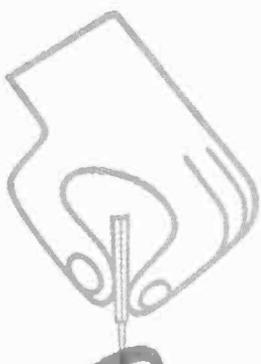High sensitivity general-purpose VTVM; 11 meg input resistance; balanced-bridge circuit; 4 1/2" meter. One of many fine instrument kits including 5" scopes, AC VTVM, tube checkers, signal tracer, audio generator, sweep generator, and others, described in detail in the Allied catalog...



Great!

other money-saving

-kits®

OF ALLIED RADIO

and you own the best

money back guarantee

Every Knight-Kit is unconditionally guaranteed to meet our published specifications for performance or your purchase price is refunded in full.

only \$2 down

It's easy to buy any Knight-Kit: only \$2 down on orders up to \$50; \$5 down up to \$200; \$10 down over \$200—up to 24 months to pay.



Featured

IN THIS VALUE-PACKED 1961
444-PAGE ALLIED CATALOG

Send coupon today for the 1961 Allied electronics catalog (the world's biggest), featuring the complete Knight-Kit line. See the best in electronic kits—save on *everything* in Electronics. Send for your FREE copy now!

also available
in Canada

sold exclusively by

ALLIED RADIO

pioneer in electronic kit development

our 40th year



free

send coupon today!

ALLIED RADIO, Dept. 204-C1
100 N. Western Ave., Chicago 80, Ill.

Send Free 1961 Allied Catalog No. 200

Name _____

PLEASE PRINT

Address _____

City _____ Zone _____ State _____



RECEIVE CITIZENS BAND ON ANY RADIO

Any standard AM broadcast radio (including portables and car radios) can now receive citizens band with the Vanguard C-327 electronic frequency converter.



ONLY
\$22.95

at your dealer
or order direct

The VANGUARD C-327 is preferred by those who know electronics. Check the following features and see why.

- 3 high frequency transistors. R. F. Amplifier, mixer and crystal controlled oscillator.
- Makes any standard radio into a double conversion superhet (known by communications engineers to be the best.)
- All 23 channels can be tuned with sharp selectivity.
- A flick of a switch restores regular broadcast reception.
- Absolutely safe as there are no voltage connections to make connects between your radio antenna.
- Convenient antenna receptacles for quick connections.
- Operates for weeks on low cost self contained 9 volt battery to minimize electrical noise pick-up. Can also be operated from 6 to 12V. D.C. external power source. Consumes only 3 milliamps (3/1000 of an amp.)
- No expense was spared to make the VANGUARD C-327 the "hottest" converter available. Contains over 40 high quality parts.
- 5 year service guarantee.

VANGUARD ELECTRONIC LABS, Dept. E-3

190-48 99th Ave., Hollis 23, N.Y.

FIX ELECTRIC APPLIANCES THAT DON'T WORK PAYS \$3 TO \$5 PER HOUR

FREE BOOK tells about profitable spare-time or full-time business. 400 MIL-LION Appliances now in use. People need them fixed. YOU make good money doing it —

right at home! Easy course trains you for top earnings. At no extra charge you get Appliance Tester. Get **FREE Book, FREE Sample Lesson!** Mail coupon now.

NATIONAL RADIO INSTITUTE, Appliance Division
Dept. D4C1, Washington 16, D. C.

Send **Free Book, Free Appliance Repair Course Lesson.**

Name.....
Address.....
City..... Zone..... State.....

**FREE
BOOK**

**FREE
LESSON**

Experimenters • Amateurs • Hobbyists

Extraordinary values await you in government surplus electronic components. Don't buy anything until you have our "Bargain Bulletin"; new material for mere dimes on the dollar. Remember, everything is brand new; here are typical values:

Stancor P-400 power transformer, \$21 list.....	9 lbs.	\$4.44
Cornell-Dubilier IJL-15100, 10 mfd/1500 v oil.....	4 lbs.	3.19
BC-610 tuning units, specify TU number.....	4 lbs.	3.45
6V6GY vacuum tubes, a dozen for.....	3 lbs.	3.95
5 vct fil xlmr, 15 KV ins, 220-240/60 pri.....	19 lbs.	6.45
Auto xfmr, 110/60 to 220/60, 90 watts.....	7 lbs.	2.29
Sealed 115 v/60 cyc relay, DPDT rated 5 amps.....	10 oz.	1.95
Astatic 400-D tone arm with dual sapphires, cer.....	1 lb.	7.45
455 KC 1Fs, National or equal.....	10 oz.	.79
Electrolytic, 3 x 20/400 volts—8 oz, 59¢.....	10 for	4.95

WRITE TODAY FOR FREE GOVERNMENT SURPLUS BARGAIN BULLETIN

JOE PALMER

P.O. Box 6188 CC,
Sacramento, California

Electron Chemistry

(Continued from page 75)

makes a much stronger polyethylene than the non-irradiated, many-branched ordinary molecular structure. Actually, it was this cross-linking process that strengthened the three polyethylene squeeze bottles of our illustration.

Food Preservation. Electron irradiation of food has been called the most significant advance since Nicholas Appert discovered canning and heat sterilization in 1809. Its great appeal lies in the negligible amount of heat required. As a result, undesired effects of prolonged heating are greatly minimized, if not entirely eliminated.

Irradiation destroys bacteria, sterilizes the food, and greatly extends shelf life. Foods can be kept fresh for months, sometimes years, at room temperature or economical above-freezing refrigeration temperatures.

Drug Sterilization. Heat sterilization produces undesired effects in drugs, especially in sensitive hormones, antibiotics, vaccines, vitamins, anticoagulants, proteins, and alkaloids. Some of these untoward effects are discoloration, chemical changes, precipitation, and loss of potency.

Electron irradiation is "cold sterilization." Some two or three million rads from an electron-beam generator will safely destroy the microorganisms in almost any drug. (The rad is the basic unit of radiation dosage, a measurement of the absorption of 100 ergs of energy per gram).

Another exciting use of irradiation is the all-important cold sterilization of delicate human tissue for surgical transplant. And while more expensive than heat sterilization, the cold sterilization of heat-sensitive catgut sutures by irradiation is a routine practice today. Advantages cited are minimum damage to the sutures, sterilization in the final sealed container, better packaging, and continuous rather than batch processing.

Electron-Beam Generators. Although nuclear reactors, isotopes, and waste fission products can be used as gamma-ray sources for irradiation, special electron machines are still the most dependable source and will likely continue to be

widely used for production processes. Typical high-energy electron machines include the Van de Graaff, linear, and Dynamitron accelerators, as well as the standard electron-beam generator.

An important feature of the electron-beam generator is its resonant transformer. Designed without an iron core, the resonant transformer uses an air-core secondary coil tuned to the primary frequency of 180 cycles. Inductive and capacitive reactances cancel out, leaving energy free to oscillate at this resonant frequency without the need for a continuous iron core. Output voltages range from 1 million to 3.5 million volts.

The resonant transformer furnishes this super-high voltage to a permanently evacuated electron beam tube. A hot-wire filament serves as the source for electrons; high voltage is applied to the accelerating electrodes of the tube, causing the electrons to gain speed and energy. Traveling at nearly the speed of light, electrons emerge from a 0.0075-inch thick titanium "window" to the product treatment area. The electron

beam is deflected over a wide area to distribute the electrons evenly.

Danger—Radiation! The familiar emblem signifying radiation hazard is always in evidence during electron irradiation. An analytical reader might well inquire: why the need for heavy concrete walls for radiation protection when it is well known that electrons can only penetrate matter a few tenths of an inch for each million volts of accelerating potential?

The answer lies in the fact that X rays are produced wherever electrons are stopped. And since X rays have great penetrating power, poured concrete or solid block concrete walls as much as seven feet thick may be required.

We have barely scratched the surface of electron chemistry. Staggering the imagination, as we have seen, are the many possibilities in food preservation, drug sterilization, polymerization and cross-linking of plastics. And with hundreds of materials being subjected to the magic of the electron beam, more and better products will ultimately result from this most exciting new science. —30—

EA. JUMBO PAK HAS OVER 400 Pcs. IN ALL. CERAMICS, DISCS, TUBULARS, PRECISIONS

FREE!! JUMBO PAK

WITH ANY \$10 ORDER

EA. JUMBO PAK REG. SELLS FOR (\$3.00) YOURS FREE WITH \$10 ORDER

POLY PAKS®

70 MICA CONDENSERS
Incl: silters tool .00025 to .01 to 600V. Worth \$20. **\$1**

30 SILVER MICAS
1 & 5% ast. values. Finest mica made. Worth \$8. **\$1**

60 Plugs & Receptacles
Incl: power, audio, battery etc. Worth \$8. **\$1**

50 HI-Q CONDENSERS
Asst. Finest made. Porcelain bodies. **\$1**

2 NPN TRANSISTORS
Worth \$3 ea. 100's of uses. **\$1**

30 PRINTED CIRCUITS
Combination resistor & condenser coupling networks for submini. work. Worth \$15. **\$1**

10 VOLUME CONTROLS
Asst. to 1 meg. Some with switch. Worth \$15. **\$1**

60 RADIO 'N' TV KNOBS
Asst: colors, sizes, shapes; **\$1**

10 Electrolytic Cnd'n'rs
Incl: can & paper types. Duals too! To 1000 mfd to 450 V. **\$1**

12S Ceramic Condensers
Incl: discs too! Wide variety of types & values. Worth \$10. **\$1**

12 GERMANIUM DIODES
Glass-sealed, similar to 1N44; hobbyists' note! **\$1**

15 AC-DC LINE CORDS
2-conductor with molded plugs, rubber insulated short lengths. **\$1**

SALE

10 PANEL SWITCHES
Micros. power, rotary types. Exc. variety. Worth \$10. **\$1**

GIANT SUN BATTERY
For 100's of lite sensitive ckts. 2x1" size. Unmounted. Worth \$4. **\$1**

Transistor Radio Basic
Incl: translator, socket, 100-sticks, diode, case. Worth \$3. **\$1**

3 HOBBY TRANSISTORS
PNP's, etc. Similar to CK-722. Worth \$3. **\$1**

10 PANEL SWITCHES
Toggle type. SPST, DPDT, etc. A shop must. 115V AC **\$1**

15 ROTARY SWITCHES
Asst. gangs, contacts; for power & circuit changing. Worth \$17. **\$1**

2000 OHM PHONE
With cord & plug. Hearing-aid type, with ear loop. Worth \$3. **\$1**

6S RESISTOR SPECIAL
Carbons, precisions, hi-Q. W-W, carb-films, to 50W. 1% too. Worth \$10. **\$1**

POLY PAKS®

12S RESISTORS
30 values, incl. 1% too. carbons! 70 1 meg, 1/2, 1W. Worth \$10. **\$1**

15 "POLY" BOXES
Snap-top covers; sizes to 4". For parts & radio basics. **\$1**

70 COILS & CHOKES
RF, ant. osc, slug-tuned, I.F. Wonderful shop asst. **\$1**

40 Transistor Resistors
Asst: colors, insulation. 1/2, 1W. Color coded. Worth \$1. **\$1**

300-FT. HOOKUP WIRE
Asst: colors, insulation. **\$1**

60 TERMINAL STRIPS
1 to 10 tie points. Used in every type of prof. Worth \$1. **\$1**

7 SILICON DIODES
1N21, 1N23, 1N23, etc. Some worth \$10 ea. **\$1**

40 TUBE SOCKETS
4 to 12 prongs, some ceramic & mica filled, & mini types. **\$1**

8 TRANSISTOR SOCKETS
Fit all types of transistors **\$1** and mini tubes, too.

\$25 SURPRISE PAK
Wide variety of usable radio-TV-hobby parts. **\$1**

1 1/2 LBS. HARDWARE
Nuts, bolts, etc. Wide variety. Handy shop asst. **\$1**

10 RCA PLUG'N'JACK
Sets for amps, tuners, recorders etc. Worth \$3. **\$1**

6S CONDENSER SPECIAL
Incl: discs, ceramics, molded, mica, papers, oils, etc. Worth \$12. **\$1**

CRYSTAL PHONE
Sensitive! 100's transistor proj., w/cord & plug. **\$1**

50 DISC CONDENSERS
Asst. .0001 to .01 to 1000V. Worth \$10. **\$1**

70 Tubular Condensers
Papers, molded, oils, ceramic! .0001 to 1 mfd to 600V. **\$1**

35 POWER RESISTORS
Asst. 5 to 50W to 10,000 ohms. Vitreous types too. **\$1**

100 Half-Watt Resistors \$1

70 One-Watt Resistors \$1

40 Two-Watt Resistors \$1

4 Output Transformers
50:0, etc. Open frame types. Worth \$8. **\$1**

70 Insulated Resistors
IRC, Allen Bradley, Stackpole makers. 1/2, 1W, 100 ohms to 1 meg, 1%, 5% too. **\$1**

50-pc. COBALT MAGNET SET!
For 100's of magnetic hobbies. For home & shop, tool **\$1**

BUY 'EM BY THE POUND

JUMBO PAKS \$3.00

MONEY BACK GUARANTEE—100's SOLD

1 POUND Precision Resistors (Worth \$100)...now

1 POUND Disc Condensers (Worth \$50)...now

1 POUND Ceramic Condensers (Worth \$25)...now

1 POUND Discs & Ceramics (Worth \$75)...now

1 POUND Diodes, Ceramics, Precisions (Worth \$70).....now

PER POUND

BUY 4 PAKS FOR \$11

MINI-MUM ORDER \$2.00

LEKTRON

245 EVERETT AVE.
CHELSEA 50, MASS.
Write for Free Catalog


HOW TO ORDER: Avg. wt. per pak 1 lb. Send check of M.O. including postage; excess returned. (C.O.D. orders, 25% down; rated, net 30 days. Include Postal Zone in address.

Transistor Topics

(Continued from page 87)

a s.p.s.t. toggle switch or conventional hand-key. Almost any standard transistor output transformer may be used for *T1*—suitable types are the Stancor TA-42, the Thordarson TR-114, or the Argonne AR-164. (Since each of these three transformers is a center-tapped unit, use the primary connections that give optimum results.) Any 6-8 ohm PM loudspeaker can be used, although you'll find that larger (6" or 8") units are more efficient than the miniature speakers generally used in transistor circuits. The power switch, *S1*, can be a toggle, slide, or rotary switch, as you prefer.

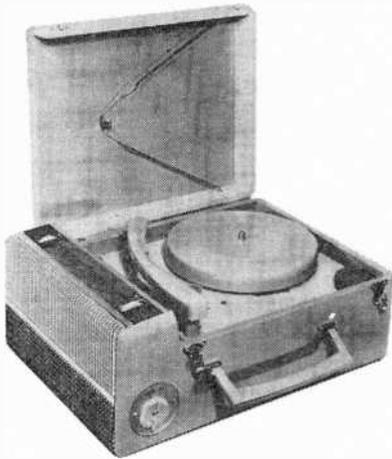The feedback circuit (broken lines in diagram) converts the amplifier into a code practice oscillator and is an optional feature. Therefore, capacitor *C1* and



Portable radio-phonograph introduced by Lafayette Radio—the FS-225—is fully transistorized. See page 115 for details.

switch *S2* can be omitted if you want to use the circuit as a straightforward audio amplifier.

The light-controlled relay circuit is almost identical to that of the amplifier, but with the feedback feature omitted; photocell *PC1* is used instead of input jack *J1*, and a sensitive relay, *K1*, instead of output transformer *T1*. Mr. Ravindranathan did not specify the type of relay used in his model, but any relay requiring less than 10 ma. (at 6 volts)

for operation should give satisfactory results; an Advance Type SO/1C/1000D relay should work nicely, although you may have to adjust armature-spring tension for best performance.

With commercial parts in limited supply, Mr. Ravindranathan used a rather unique photocell in his model. Experimenting with a defective 2N217 transistor, he found that this unit made an acceptable photocell when its outer case was removed so that the germanium junction could be exposed to light. Connections were made to the base and collector electrodes. As an alternative unit, an International Rectifier Type B2M photocell should give excellent results.

Either of the two circuits can be assembled on a conventional metal chassis, on a plastic or fiber board, or built breadboard fashion on perforated Masonite. Neither layout nor lead dress should be critical. Power can be supplied by a single 6-volt battery, such as a Burgess Type Z4, or by a power pack made up of four penlight or flashlight cells connected in series. After assembly, *R2* is adjusted for best performance. In the audio amplifier, *R2* acts as a limited range volume control; in the light-operated relay circuit it serves as a sensitivity control.

Overseas News. From Japan comes news of all-electronic refrigerators and water-coolers using semiconductor thermoelectric elements. Thus far, only handmade prototypes have been assembled, but both units compare favorably in performance with conventional equipment using compressor-type cooling devices. The manufacturer? Tokyo Shibaura Electric Company, Tokyo, Japan.

Transistorized television is making news all over the world—at least two major firms are producing these sets in the U.S., another in Japan, and still another in Germany. With summer approaching, and the resulting increased interest in battery-powered equipment, watch for the announcement of new models by several manufacturers.

Our forward-looking South American neighbor, Brazil, has started transistor production in a big way. One local firm is making transistors under U. S. patents, while several foreign-based producers are planning to open local facilities. A high percentage of currently produced units is for internal consumption, but

with rising production, Brazil will probably export to other Latin American nations.

Product News. Lafayette Radio (165-08 Liberty Ave., Jamaica 33, N. Y.) has introduced a fully transistorized portable radio-phonograph. The radio section features seven transistors, one diode and a thermistor. The phonograph tone arm is equipped with a flip-over cartridge, while the turntable can be switched for 33 1/3-, 45-, and 78-rpm records; a speed compensation control permits a fine adjustment of turntable speed to allow for battery wear. The unit, stock No. FS-225, sells for \$52.50, less batteries, F.O.B. New York City.

A Philadelphia firm, the Navigation Computer Corporation (1621 Snyder Ave., Philadelphia 45, Pa.), is now manufacturing a line of miniature felt discs for use as soldering heat sinks. The felt discs are fitted over transistor leads and saturated with a volatile fluid. During soldering operations, the evaporating fluid absorbs heat from the transistor leads, preventing internal damage. These discs sell for \$5.00 per 100 in quantities of less than 1000, or for \$3.00 per 100 in large quantities. Minimum order is 100 discs.

From the West Coast comes news of a power transistor capable of delivering respectable amounts of power at frequencies up to 30 mc. Pacific Semiconductors, Inc. (1255 Chadron Ave., Hawthorne, Calif.) is in pilot-line production of a triple-diffused silicon mesa transistor which can deliver 5 watts at 30 mc. with a power gain of 10 db. This expensive unit, Type PT-530, presently sells for \$125.00 each in small quantities.

Several new items have been announced by RCA's Semiconductor Division (Somerville, N.J.): a low-cost *p-n-p* power transistor suitable for high-fidelity sound equipment, and two new computer transistors—Types 2N414 and 2N1450. In addition, RCA's Electron Tube Division (Lancaster, Pa.) is now marketing a solid-state high-frequency oscillator; featuring a tunnel diode, the unit delivers almost a milliwatt over the range of 1100 to 1400 megacycles.


That's "all she wrote" for the present, fellows—I'll be back next month with more news.

—Lou

NOW— YOU CAN BUILD YOUR OWN DIGITAL NETWORKS!

USING DIGIBITS*

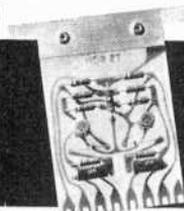For the first time transistorized digital packages, designed and manufactured by professional suppliers to the computer industry, are available to the serious experimenter.



WRITE TODAY FOR BOOKLET DESCRIBING OPERATION & APPLICATION ONLY \$1.00

Create your own computer, counter, or special-purpose network in your own home or lab using Digibits* expandable all-purpose kits. Digibits start at the low price of \$8.95. Complete line of accessories available. Guaranteed performance. (Booklet gives complete instructions.)

WRITE FOR FREE PRICE LIST

TECH SERV

DEPT. D-1
4911 COLLEGE AVE.
COLLEGE PARK, MD.

DEALERSHIPS AVAILABLE

COLLEGE-LEVEL
ELECTRONICS

STUDY ÷

÷ WORK ÷

ASSOCIATE DEGREE
2-YR. RESIDENCE

÷ PLAY ÷

IN

STUDY for CAREER
in Industrial Field

BEAUTIFUL
COLORADO

- MISSILES
- COMPUTERS
- RADAR
- AUTOMATION
- MICROWAVE
- TRANSISTORS
- SERVOMECHANISMS
- CO-EDUCATIONAL
- DORMITORIES
- AT FOOT OF ROCKIES

— MAIL NOW FOR FREE INFORMATION —

NAME _____ AGE _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____

INTERESTED IN RESIDENT HOME STUDY

COLORADO TECHNICAL INSTITUTE
P. O. BOX 7757 DENVER 15, COLO.

ELECTRONICS

BOOK SERVICE

will send you your choice of these selected electronics and hi-fi books for a 7-DAY FREE EXAMINATION!

Here are some of the world's greatest electronics and hi-fi books...chosen carefully by Ziff-Davis Electronics Book Service as among the best in their fields. You'll find top-notch texts and manuals on theory and instruction...important volumes covering radio and TV servicing, electricity and appliances...reference books to help you understand such fields as computers, electronics experimentation and books on hi-fi and tape.

Each volume is designed to help you get more know-how, greater enjoyment from your electronics specialty or hi-fi hobby—and each is yours for 7 days FREE! Simply write your choices on the coupon below and mail it today. When your books arrive, read and enjoy them for seven full days. If, after that, you don't agree that they are everything you want, return them and owe nothing. Here is the perfect way to build the library every man in electronics must have.



2500. BASIC ELECTRONICS, Grob

An introductory text on the fundamentals of electricity and electronics for technicians in radio, television and industrial electronics. \$9.25



2511. UNDERSTANDING RADIO, 3rd Ed., Watson, Welch and Eby

For those with little or no technical knowledge who wish to know the fundamentals of radio theory and servicing. \$8.25



2404. FM RADIO SERVICING HANDBOOK, King

A practical guide to FM V.H.F. receivers, their design, construction, alignment and repair. \$5.00



2442. BASIC ELECTRONIC TEST INSTRUMENTS, Turner

Over 60 instruments described, their uses fully explained, and valuable work-saving short-cuts outlined. \$6.25



2425. ELEMENTS OF TELEVISION SERVICING FOR BENCH AND FIELD, Marcus and Gendler

Up to date discussion of installation, servicing and repair of T.V. receivers designed for the practicing serviceman. \$8.15

2407. HOW TO GET AHEAD IN THE TELEVISION AND RADIO SERVICING BUSINESS, Marcus

Shows the easy way to get started as a TV-Radio repairman, how to earn while you learn, how to get and keep customers. \$3.50



2415. MANDL'S TELEVISION SERVICING, Mandl

This standard text book in the T.V. servicing field provides clear descriptions of the fundamentals of T.V., and practical instruction on the diagnosis and correction of typical trouble. \$7.50

2803. BASIC MATHEMATICS FOR ELECTRICITY, RADIO AND TELEVISION, Singer

Here, mathematical principles are presented as dynamic tools for solving electrical problems. A practical course for students as well as an excellent refresher course for skilled technicians. \$8.25



2651. MAJOR APPLIANCE SERVICING, Brockwell

Gives essential information for a career in major appliance servicing. Explains methods of repairing appliances, organizing and managing a service business. \$5.95

2667. ELECTRIC MOTOR REPAIR, Rosenberg

All details of modern motor repair work. Actual demonstrations of what to do and why. Designed for bench use with a duospiral binding that lies flat. \$9.25



2011. STEREO & HI-FI DIRECTORY, 1961, Ziff-Davis

New! Over 1200 component listings, 800 photos; latest models, prices! Entire sections on every phase of stereo and monaural high fidelity. \$1.00



2010. AUDIO YEARBOOK, 1961, Ziff-Davis

Brand new edition. Advanced discussions and instructions on every phase of audio. Special features make this an excellent guide for the advanced audiophile. \$1.00



2755. THE PRACTICAL HI-FI HANDBOOK, King

A guide to high fidelity sound reproduction for the service engineer and amateur. Chapters on amplifiers, loudspeakers, pickups, microphones, record players, disc, tape and stereo. \$5.95



2765. YOUR TAPE RECORDER, Marshall

This book helps to eliminate trial and error under all conditions. Includes illustrations of 55 magnetic recorders with specifications. \$4.95



2750. ELEMENTS OF MAGNETIC TAPE RECORDING, Haynes

How to get professional results with tape the way the experts do. Basic techniques, how to splice and edit, how to repair and maintain your recording equipment. \$7.95

Curves

(Continued from page 66)

The difference is simply this. In the lossier type, there is a tone control "mid-point," and every tone control frequency response curve slants up or down starting from this point (in Fig. 9, the mid-point falls at about 1000 cycles). But in the Baxandall circuit, if you turn up the bass boost just a little, only the frequencies below 50 cycles are boosted, as in Fig. 10, and the response is still flat between 1000 and 50 cycles. Turn it up a little more and it boosts everything below 200 cycles, and so on.

In other words, the Baxandall circuit varies not only the amount of boost or cut, but the frequency at which boost or cut begins as well. In action, the two different kinds of tone control circuits—lossier and Baxandall—can sound quite different, and a family of curves will quickly tell you which an amplifier has.

Equalization. A curve that will indicate quite a lot about how records played on your system will sound is called the "equalization error" curve. To understand it, let's talk a little first about equalization in general.

When a record is made, engineers find it necessary to attenuate the low frequencies and boost the highs. They cut down on the lows because the wide swings of the cutting stylus at full power at these frequencies would slash deeply into the groove walls; if not attenuated, such low frequencies would interfere with the adjacent grooves, and perhaps even cut all the way through the walls. And the highs have to be boosted, since surface noise at high frequencies is enough to drown out the music unless the highs are amplified more, or, as the engineers say, given "pre-emphasis."

Curve A in Fig. 11 is the standard RIAA (Recording Industry Association of America) recording curve. At 20 cycles, the bass is down 20 db; and at 20,000 cycles, the treble is up 20 db.

A recording with the RIAA equalization would sound pretty funny if we played it back on a perfectly flat amplifier. The highs would seem shrill and piercing; the bass, very weak. So all preamplifiers designed for record playing have built-in equalization networks to

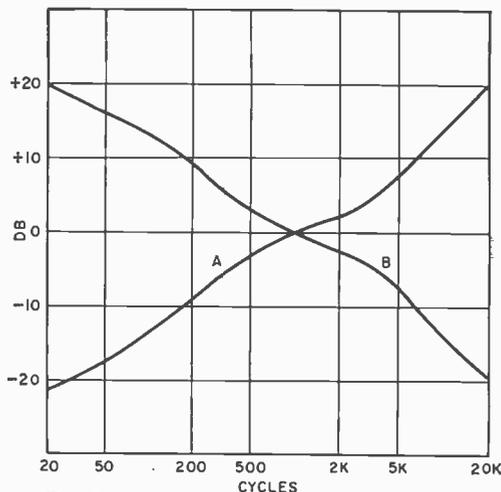


Fig. 11.

correct this situation by attenuating the treble and boosting the bass. If this circuit were perfect, its characteristic curve would be the exact opposite of curve A in Fig. 11 and would look like curve B.

As is usually the case in electronics, the actual circuit is never perfect. An equalization error curve (Fig. 12) shows just how much the equalization is off at each frequency over the audio range. If this curve is reasonably flat—within a db or so at all frequencies, then your equalization network is doing the job it is meant to do, and doing it well.

Figure 13 shows a poor equalization error curve—it varies 8 db from one extreme to the other—displayed by one amplifier on the market.

Loudness. An amplifier you are considering buying may have a "loudness"

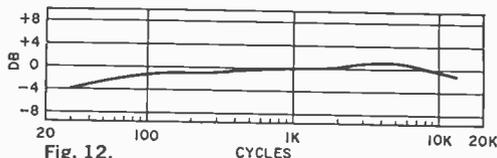


Fig. 12.

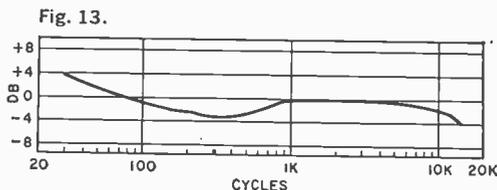


Fig. 13.

control. This circuit attempts to compensate for the fact that our ears have different frequency response characteristics at different sound levels.

A loudness control is often necessary for the simple reason that music is seldom reproduced at its original volume. As many authorities have pointed out, it's impossible to place an orchestra in the average living room.

But while we almost invariably listen to records at less than their original volume, by making use of some rather ingenious loudness circuits we can counteract our ears' deficiencies and make all music sound balanced over the entire range at whatever level we play it. Figure 14 shows a set of loudness curves for one popular amplifier.

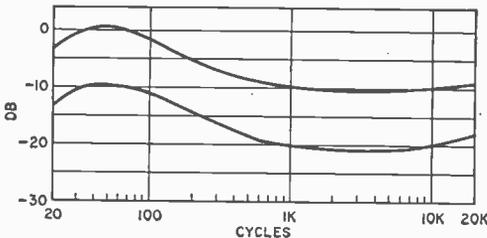


Fig. 14.

Other Curves. There are many other curves: sensitivity, which tells us how much input signal at each frequency it takes to drive an amplifier to full power output; tape equalization, similar to record equalization, but with a shape of its own; channel separation, which charts the channel-to-channel crosstalk over a wide range of frequencies for stereo amplifiers; rumble, scratch, and "presence" curves; to name a few. But if you understand those we've discussed so far, you're well on your way to being able to separate the sheep from the goats—in amplifiers, that is—with only a quick glance at the curves.

Now it's clear why Joe went wrong back at the beginning of our story. He didn't know that two amplifiers with the same or similar specifications could have very different curves and sound quite different as well. If you examine carefully the curves of any amplifier you may be thinking of buying, you won't make the same mistake.

-30-

HERMAN
HE
ELECTRONICS

SOUTHEAST
HEADQUARTERS
FOR

SWL-AMATEUR

538E HALLICRAFTERS \$59.95
Other models in stock

NC-60 NATIONAL 59.95

NC-270 NATIONAL 249.95

G-33 GONSET 89.50

723K EICO 49.95
Transmitter kit

65B HY-GAIN 18.95
5 element — 6 meter beam

HERMAN ELECTRONICS, INC.
1365 N.W. 23rd ST. MIAMI 42, FLORIDA

Please send me your free 1961 catalog

NAME _____

ADDRESS _____


CITY _____ ZONE _____ STATE _____

voices
from
outer space...
SPECIAL
OFFER,
25¢

Dramatic Events Recorded First Time From Short Wave Radio!

President's voice from outer space... police capture of a gunman... radio contact with record altitude flight! Many other fascinating, historic events—ships, planes, foreign stations—all transcribed on a limited-edition recording, "The Amazing World of Short Wave Listening," narrated by world-famous newscaster Alex Dreier. If you're alert, adventuresome, send for this remarkable recording today!

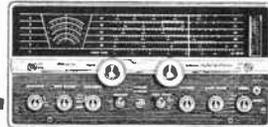As heard on Hallicrafters precision
receivers, \$59.95 to \$395.00.



hallicrafters

Department 21,
Chicago 11, Ill.

Enclosed is 25¢. Please rush my copy of "The Amazing World of Short Wave Listening."

NAME _____

ADDRESS _____

CITY _____ STATE _____



SELL YOUR USED EQUIPMENT Through POPULAR ELECTRONICS' Classified Columns!

The 400,000 purchasers of **POPULAR ELECTRONICS** are always interested in good used equipment or components. So, if you have something to sell, let PE readers know about it through our classified columns. It costs very little: just 50¢ a word, including name and address. Minimum message: 10 words.

For further information write:

Martin Lincoln
POPULAR ELECTRONICS
One Park Avenue
New York 16, N. Y.



Earn BIG MONEY

Learn **TELEVISION, RADIO ELECTRONICS, RADAR, SONAR** in your spare time at home. Earn as you learn.
CTS OFFERS COMPLETE TRAINING Why be satisfied with less? Christy's Shop Method Home Training System speeds your learning. Makes learning fun.
19 TRAINING KITS SENT! Multi-tester, Oscillator, Signal Tracer, Oscilloscope, Signal Generator, Electronic Timer, Regenerative Radio, Giant-sized Television Receiver (optional). Do hundreds of exciting experiments.
FREE BOOK—TWO SAMPLE LESSONS together with Pay later form sent on request. **CHRISTY TRADES SCHOOL, Dept. T-914, 3214 W. Lawrence, Chicago 25.**

TRAINING KIT FURNISHED

WALKIE TALKIE RADIO SENDING SET



YOUR OWN POCKET SIZE RADIO STATION Talk to any house or car radio without wires or hookups of any kind! Built-in antenna. Self-contained flashlight batteries—Power transistor! Talk to radios in the same building and to cars or between cars up to one block or more away—depending on local conditions. No license or permit needed! **SEND ONLY \$3.00** (cash, ck, mo) and pay postman only \$9.95 plus COD postage or send \$12.99 for postpaid delivery. Shipped complete ready to operate. Order yours now—Today! Available only from: **WESTERN RADIO, Dept. TEL-3, Kearney, Nebr.**



SHIRT POCKET TRANSISTOR RADIO Built-in Ferrite Antenna—Tiny 1/2" Speaker! **WORLD'S SMALLEST REAL RADIO!** Smaller than a pack of cigarettes! Uses double reflexed TRANSISTORS. Guaranteed to receive local stations anytime, anywhere! Uses standard 1.5c flashlight battery. American made and service guaranteed for one year.
SEND ONLY \$3.00 (cash, ck, mo) and pay postman \$6.99 plus postage, or send \$9.99 for postpaid delivery. Sent complete. Ready to play! Available only by mail from:
MIDWAY COMPANY
Dept. REL-3 Kearney, Nebraska

Across the Ham Bands

(Continued from page 69)

the tube sockets; *TS1* serves as an input and output tie point for the modulator. You should also place a couple of solder lugs under nearby mounting screws for ground terminals. If necessary, move the antenna coil under the chassis a bit to give yourself a little more working area.

Wiring of the modulator in the "Chief" is point-to-point, with the resistors and capacitors supported by their leads; slip spaghetti tubing over their leads to prevent shorts. Be careful to observe polarity when installing the electrolytic capacitors. Use shielded wire between the microphone connector (*J1*) and the gain control (*R2*) and between *J1* and the 12AT7 (*V1*); use tube shields on both *V1* and *V2* to minimize feedback.

Connect the heater lead (lug No. 2 on *TS1*) to the ungrounded heater terminal of the nearest 807 in the Globe Chief, and connect lug No. 5 on *TS1* to the screen-grid terminal (pin 4 of the 807). Also, connect lugs 3 and 4 on *TS1* across the transmitter's key jack; switching *S1* to "phone" automatically closes the key circuit for phone work.

Operation. Place *S1* in the c.w. position and tune up the transmitter in the normal manner; first tune for maximum r.f. output and then increase the antenna loading to reduce the output a trifle. Now, note the r.f. amplifier plate current and set *S1* to the phone position.

Adjust the slider on resistor *R6* until the amplifier plate current drops to half of the value noted. (Be sure to turn off the transmitter and discharge the Chief's filter capacitor before adjusting *R6*.) Then adjust the gain control (*R2*) so that talking into the microphone at your normal speaking level will cause the amplifier plate current indicator to kick slightly on occasional voice peaks.

News and Views

Bob Effrain, WV2NOH, 62-14 80th St., Middle Village 79, N. Y., is studying madly for his General ticket—his father has promised him \$200.00 for a beam and a rotator when he gets it! Bob uses a Sonar SRT-120 transmitter held down to 75 watts, and he receives on a Hallcrafters SX-110. This combination and a 15-meter doublet gave him 25 contacts his first two weeks on the air. When you work

Always say you saw it in—POPULAR ELECTRONICS

WV2NOH, ask Bob about his 2-meter "walkie-talkie." . . . **Gerald Finn, KN7KRB**, 721 N. Delaware, Chandler, Ariz., excites the ether on 40 and 15 meters with an EICO 720 transmitter and receives on a Hallicrafters SX-99 aided by an RME DB-23 preselector. His brag list shows more than 200 contacts all over the mainland, Canada, Alaska, and Hawaii. . . . Looking for Delaware? Well, look for **John Rhoads, KN3MXJ**, Ten Granite Road, Wilmington, on 7160 kc. He uses a Heathkit DX-40 feeding a 40-meter dipole, and will hear you on a National NC-66.

Jeff Kadet, K1MOD, 501 Greendale Ave., Needham 92, Mass., parlayed his Novice license, a Johnson Adventurer transmitter feeding a 40-meter dipole, and a Hallicrafters SX-100 receiver into 25 countries worked and 47 states confirmed. Not bad for a lad just turned 13. The three states he still needs are Utah, Arkansas and Delaware. . . . **Carlton Carlson, WV2LYP**, 28 Country Club Dr., Mount Marion, N. Y., combines a yen for building his own ham equipment with good operating. His home-brew, 45-watt transmitter, a long-wire antenna, and a six-tube, home-brew receiver worked 420 contacts in 18 states, all on 80 meters. California was his best DX. . . . Bob Anderson, WPE1BDB, reported for his friend **Joel Wilks, K1PCE**, 82 Wilcox St., New Britain, Conn. Joel just received his Conditional license and works mostly 15 and 20 meters with a Heathkit DX-20 transmitter feeding a 20-meter dipole. He receives on a Heathkit AR-3, plus a Q-Multiplier, Twenty-

two states confirmed, Canada, Puerto Rico, and Venezuela comprise his Novice record.

Jimmy Owen III, K4CGY, Box 215, Eagle Rock, Va., works all bands from 10 through 75 meters with his Heathkit DX-100B—his favorites are 10 and 75. Jim receives on an SX-99 and transmits on a 75-meter inverted-V antenna. Out of 38 states worked, 36 are confirmed, and he has three countries confirmed. K4CGY QSL's 100% to all hams and SWL's. . . . New hams in the northwest who are interested in learning how to handle messages via amateur radio are invited to join the Northwest Slow Speed Net. It meets daily except Sunday at 2100 PST on 3700 kc., and code speed is kept down to 5 to 8 wpm. For further information, contact **Samuel M. Van Wyck, K7BWV**, P. O. Box 187, Lapwai, Idaho.

Alan A. Memley, WV6MLH, 2609 W. 102 St., Inglewood 4, Calif., works 15 meters with a DX-20 transmitter and a SX-110 receiver. Ready for the day when he gets his General ticket, he has a 3-element tri-band beam. Al also works 2 meters with a Gonset Communicator feeding a ground-plane antenna. . . . **Fred N. Affleck, VE7BED**, 4624 Winnifred St., Burnaby 1, B. C., Canada, runs 85 watts to a home-brew transmitter on 40 and 20 meters. His antenna is a combination 40/20 meter dipole. With them, he has worked 20 states and two provinces. Fred has just finished building a 15-tube receiver.

Why not send us your News and Views picture, and construction project? 73,
Herb, W9EGQ

MOVING?

Make sure you notify our subscription department about any change of address. Be sure to include your postal zone number as well as both old and new addresses. Please allow four weeks' time for processing.

POPULAR ELECTRONICS
434 South Wabash Avenue
Chicago 5, Illinois

find new
adventure in
amateur
radio...

with
Viking
1st choice of
amateurs the
world over!

loaded with features... kit or wired!



ADVENTURER —50 watts CW input 80 through 10 meters. 240-181-1... Kit Am. Net...\$54.95	RANGER —75 watts CW input; 65 watts phone—160 through 10 meters. 240-161-2... Kit Am. Net...\$229.50	VALIANT —275 watts CW and 55B; 200 watts AM—160 through 10 meters. 240-104-2... Kit Am. Net...\$349.50
	240-161-1... Wired Am. Net...\$329.50	240-104-2... Wired Am. Net...\$439.50

FREE CATALOG

E. F. JOHNSON CO.
1233 2nd Ave. S.W. • Waseca, Minn.

Complete specifications and schematics on all Johnson transmitters, amplifiers, station accessories, keys and practice sets!

NAME _____
ADDRESS _____
CITY _____ STATE _____

CITIZEN BAND KIT SALE!!!!

Closing out our stock of citizen band kits. Nationally advertised at \$39.95 and up. Complete with power supply tubes, crystal, cabinet, coils, instructions, etc., less mike. All sales final. Thousands of satisfied users. FCC application included.

110 VOLT CB TRANSCEIVER KITS.....	SALE PRICE \$19.95
12 VOLT CB TRANSCEIVER KITS.....	SALE PRICE \$22.95
6 VOLT CB TRANSCEIVER KITS.....	SALE PRICE \$22.95

GROVE'S BUY OF THE MONTH!!!

GOV'T SURPLUS NOISE PEAK LIMITER.....SALE PRICE \$14.49
(works swell on CB—new—complete with tube and wiring diagram)

SAVE \$\$\$ ON CB ANTENNAS!!!

3-ELEMENT CB BEAM ANTENNA (REG. \$29.95).....SALE \$11.99
(all aluminum, 9 ft. boom, 8 db. gain, directional)

GROUND PLANE ANTENNA . . . (Famous m'f'r).....SALE \$12.98
102" WHIP + BASE + SPRING ASSEMBLY . . .
(st. steel whip).....SALE \$ 7.98
BUMPER MOUNT ANTENNA + SPRING + WHIP
+ MOUNT.....SALE \$ 9.98

ALLIANCE T-12 ANTENNA ROTATOR.....SALE \$20.99
100 FT. ROLL OF RG-58 OR RG-59 COAXIAL CABLE.....SALE \$ 3.99
FAMOUS MAKE CB TRANSMITTING CRYSTALS
(REG. \$3.95).....SALE \$ 1.99
EMC MODEL 211 TUBE TESTER KITS.....SALE \$14.83
EMC MODEL 211 FACTORY WIRED
TUBE TESTERS.....SALE \$18.83

CLEARANCE ON CB MODULAR UNITS!!!

CB CONVERTER KIT: Uses your car radio, compact...SALE \$14.50
TRANSMITTER KIT: + mike, panel meter, etc.....SALE \$34.95
AC POWER SUPPLY KIT: for home operation.....SALE \$16.95
MOBILE POWER SUPPLY KIT: transistorized.....SALE \$22.98
FIELD STRENGTH METER KIT: + antenna +
load box.....SALE \$14.98

SEND FOR OUR LATEST CITIZEN BAND BARGAIN CATALOG
+ BONUS OFFERS!!!

GROVE ELECTRONIC SUPPLY COMPANY

4103 WEST BELMONT CHICAGO 41, ILLINOIS
Include postage for shipping or 50% deposit, balance C.O.D.

The Battery That's Used in Guided Missiles

For Photography, Aircraft, Models, \$1.95 ea. Postpaid
Searchlights, Radios, etc.



Sintered-plate Nickel-Cadmium alkaline storage batteries designed for "NIKE" Missile and now with no known limit of service (over 3000 recharges on test without loss of capacity). Other features: Virtually indestructible, compact & lightweight, withstands heavy shock and vibration. Flat voltage curve during discharge retains charge year or more. High discharge rate up to 50 amps. for this cell, no corrosive fumes to harm clothing or equipment. spill-proof construction, discharge in position. Indefinite storage without deterioration, operates in temperatures -20°F. to +200°F. Each cell is approx. 4 ampere hour capacity. Nominal voltage per cell is 1.2 volts. Cell size 6" H. x 2" W. x 1/2" T. Wt. 6 oz. ea. Uses Potassium-Dioxide (30%) electrolyte. Negligible loss during lifetime service. Add only distilled water once a year. A fraction of Government cost.

Used Test Cells.....\$1.95 ea. Postpaid
Brand New Cells.....2.95 ea. Postpaid
6 V. Battery (5 cells in stainless steel case) Used \$10.00 New \$15.00
12 V. Battery (10 cells in stainless steel case).....Used \$20.00 New \$30.00
24 V. Battery (20 cells in stainless steel case).....Used \$40.00 New \$60.00
6 ampere hour cells size 4 1/2" H. x 2 3/8" W. x 3/4" T. Used test cells \$3.50 New cells \$4.95

ESSE RADIO COMPANY, Dept. J-7, 42 W. South St., Indianapolis 25, Indiana

ALL BAND TRAP ANTENNA!

Reduces interference and noise on All Makes Short Wave Receivers. Makes World Wide Reception Stronger, Clearer on All Bands!

Complete with 87 ft. of 72 ohm balanced feedline. Sealed automatic frequency resonant traps. Excellent for ALL world wide short wave receivers and amateur transmitters. For NOVICE AND ALL CLASS AMATEURS! Eliminates 5 separate antennas with better performance guaranteed. 80-40-20-15-10 meter bands. Complete length 102 ft. \$14.95 40-20-15-10 meter bands, 54 ft. antenna (best for worldwide swl's)

SEND ONLY \$3.00 (cash, ck, mo) and pay postman balance COD plus postage on arrival or send full price for postpaid delivery. WESTERN RADIO Dept. AEL-3 Kearney, Nebraska

Ping-Pong Stereo

(Continued from page 58)

Now enter the musical arrangers. They know that their job is stereo enhancement and the scoring is entirely directed to this end—thus the almost universal use of heavy brass, woodwind aggregations, and the ubiquitous percussion.

The End Results. What kind of results does all this achieve? The degree of "sensationalism" varies widely, depending on the skill of the engineers and the cleverness of the arrangers. As a general rule, nearly all of these recordings give new life and stereo effect to the machines for which they were intended—the "department-store" stereo console. And even a fair percentage of the cheap-

"SUPER" STEREO SAMPLER

- Bongos Bongos Bongos
—Command RS809SD
- Percussion on Stage Camelot
—Time S2022
- Percusive Jazz
—Audio Fidelity DFS7002
- Pertinent Percussion Cha Cha's
—Command RS814SD
- Pinpoint Percussion
—Time S2016
- Provocative Percussion
—Command RS806SD
- Provocative Piano
—Command RS811SD
- The Sound of Dynamic Woodwinds
—Medallion MS7505
- The Sound of a Marching Band
—Medallion MS7507

er component systems are made more "stereostic" and sonically exciting to their owners.

From a strictly musical viewpoint, the recordings have been howled at and condemned by the critics as "flashy trash," "stereo Pabulum for the musical moron," and worse. But one still must tip the hat to the people involved. Make no mistake: it takes a top engineer, a stereo-oriented arranger, the finest equipment, and the best musicians to produce a really prime example of this new type of stereo recording.

Now some observations about these

Always say you saw it in—POPULAR ELECTRONICS

recordings, as heard on a "money-is-no-object" highest-quality component stereo system. For one thing, many of the companies boast on their record jackets about the "great dynamic range" of their discs . . . not so . . . the music itself is dynamic, but they are mistaking high-level recording for dynamic range.

When channel switching is employed, it is easy for a keen ear to detect one channel switched off completely, even to reverb! Needless to say, the stereo directionality becomes almost outrageous in a high-quality component system, especially if strict two-channel "left and right" positioning was cut on the disc. The "hole-in-the-middle" is then about the size of the Grand Canyon!

Depending on whether natural or artificial reverb was used, a curious phenomenon occurs. If natural reverb was used and some very high-level trumpets were being played on the left side, you would hear the fundamental sound from the left; on the right you would hear the same sound as reverb, being picked up by the mikes on the far right. On some setups, such a double image can be very

confusing! If artificial reverb was used, sometimes the amount varies on the channels and the "presence" on one over-rides that of the other.

As for the claims of total frequency response . . . the generally whooped-up mid-range is projected far out of balance on a good system, and on massed strings the results are excruciatingly painful to the ear and the musical sensibilities. The high frequencies are equally out of balance and some of the high percussive transients can almost cut off your ear! The low frequencies usually appear to be somewhat lacking, this partially through intent as explained previously, but most often as a result of the tremendous velocities and high levels recorded on the discs.

How long this type of recording can survive is anybody's guess, although it is currently selling very well. But even if the sound is very artificial, the discs are affording pleasure to a great many people. And while the perspective may be somewhat distorted, they are at least allowing the general public to hear some of the potential of stereo sound. -50-

read


7 OF THE GREATEST SCIENCE FICTION STORIES EVER WRITTEN—IN AMAZING'S 35th ANNIVERSARY ISSUE

Come celebrate the 35th anniversary of the world's first science fiction magazine—in April **AMAZING STORIES**. It's a fabulous 196-page issue—featuring classics of the sf world:

- **TWO** full-length novels (including the *first* Buck Rogers story!)
- **FIVE** short stories by sf greats like Edgar Rice Burroughs, Ray Bradbury, and Edmond Hamilton—all with their original illustrations!

Be sure to get a copy of AMAZING's 35th Anniversary Issue—on sale at your favorite newsstand March 9. Only 50¢

PRINTED CIRCUIT Holding Fixture

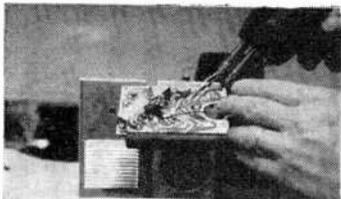

It positions and holds - - - your printed circuits for easy, and better soldering. It pivots horizontally and vertically to position the board for the proper work angle. Price \$1.00

No postage necessary

Cut out and mail with \$1.00 today, for this handy new tool. . . . Please print

Name _____
Street _____
City _____
Zone _____ State _____

Kuhlman Instrument Co. Inc.
52 Woodlawn Ave. Norwalk, Ohio

MAIL COUPON TODAY!

Find out how you can get this book *free!* the V.T.V.M. by Rhys Samuel published at \$2.50—contains a wealth of information on how the V.T.V.M. works . . . how to use it. Send for particulars on how to get this valuable book.

Name _____
Address _____
City _____ Zone _____ State _____

Mail to Dept. P-3 General Techniques, Inc.
Manufacturers of Quality Electronic Kits
1270 Broadway, New York City 1, N. Y.

SHORT WAVE RADIO ADAPTER



ADAPTS ANY HOME, PORTABLE OR CAR RADIO TO RECEIVE SHORT WAVE FOREIGN BROADCASTS, on 31 and 25 meter bands. Gets all over the world day and night! Gets Voice of America, Army and Air Force Broadcasts. Just set NEAR home or portable radio or clip to dash in car. No wiring needed! TRANSISTOR-POWERED with self-contained flashlight battery. Sent complete ready to use with QUICK, EASY INSTRUCTIONS.

SEND ONLY \$3.00 Deposit (cash, ck, mo) and pay postman balance of

\$9.95 on arrival plus COD postnote or send \$12.95 for postpaid insured delivery Guaranteed performance. Available at this low price only from:
WESTERN RADIO Dept. SEL-3 KEARNEY, NEBRASKA

Short-Wave Report

(Continued from page 88)

many stations in the U. S. as well as numerous stations which classify as real DX. He was also able to tune in excellent musical programs from England and Germany. (Your Short-Wave Editor wonders if he ever tuned across the long-wave band from 100 to 500 kc.? While in Germany, we were able to enjoy many fine programs from *R. Luxembourg* and other long-wave stations.)

George originally started out in the radio field back in 1952 by rebuilding and repairing old radio receivers. Before going into the Air Force, he attended night school to study code and to deepen his knowledge of electronics. If you hear him on the air as K8ABR, be sure to send him a report—he will QSL 100%.

Do we have any other brother-sister DX'ing combinations among our readers?

Current Station Reports

Numerous frequency changes are featured in the resume of current reports this month. All times are Eastern Standard and the 24-hour system is used. At time of compilation all reports are as accurate as possible, but stations often change frequency and/or schedule with little or no advance notice. Please send your reports to: Hank Bennett, P. O. Box 254, Haddonfield, N. J. (Requests for Short-Wave Monitor Certificates and call letters *MUST* be sent to: Monitor Registration, POPULAR ELECTRONICS, One Park Ave., New York 16, N. Y. See registration form on page 109.)

Australia—*Radio Australia* plans to add within the next year two 100-kw. xmtrs with calls of VLE and VLF. (*WPE8MS*)

Austria—*Osterreichischer Rundfunk*, Vienna, has test xmns as follows: 0600-0800 on 9770 kc.; 2300-0000 and 0800-1400 on 7245 kc.; 0400-0600 on 7200 kc.; and 0000-0400 and 1400-1600 on 6155 kc. The 0000-0400 mxsn on 6155 kc. is heard best, with waltzes and marches, and anmts in German, Eng. and French. Reports go to Box 700, Vienna 70, Austria. (*WPE1KO*, *WPE2BYI*, *WPE2HF*, *WPE3AGZ*)

Belgium—Brussels is heard well on two new channels: 9765 kc. to N.A. at 1615-1800 and 1815-2000; and 6085 kc. at 2030-2215, in Dutch. (*WPE4FI*)

A mailbag period is conducted on Saturdays at 1530 and 1930. Reports go to Station ORU, P. O. Box 26, Brussels 1, Belgium. (*WPE3BIK*, *WPE5AWL*, *WPE8BXG*)

Canary Islands—*Emissora de la Isla de la Palma*, Santa Cruz de la Palma, has moved from 7390 kc. to 7345 kc. and is heard well at 1600-1805. (*WPE4FI*)

Colombia—A new station is *R. Santa Fe*,

Always say you saw it in—POPULAR ELECTRONICS

Bogota, 4965 kc., noted at 2105-2230 with L.A. music. Reports go to Apartado Aereo 9339, Bogota, Colombia. (WPE1AAC, WPE1BM)

Congo—Leopoldville (*Radio Congo*) is heard well on 11,755 kc. at 1700-1900 with test broadcasts in English; this frequency has caught many DX'ers unaware as the station announces that it is operating on 11,795 kc. There is another Eng. period at 1330-1400 and a test in French to Europe at 1300-1330. Reports go to P. O. Box 3171, Leopoldville. (WPE1AGM, WPE1ASX, WPE1BM, WPE1CAU, WPE1CR, WPE2CKI, WPE2DPD, WPE2DRH, WPE3AK, WPE4BYE, WPE4EC, WPE4FI, WPE4HJ, WPE5XX, WPE6AA, WPE8BYX, WPE8FV, WPE8WT, WPE9KM, WPE0AE, WPE0ATE, WPE0BHG, VE3PE1DO, FE)

Cyprus—The BBC East Mediterranean Station, Limassol, broadcasts in Arabic at 1100-1600 to Iraq and the Persian Gulf on 7130 kc. This frequency replaces 6790 kc. (WPE8MS)

Dominican Republic—*R. Caribe* has opened a new outlet on 15,065 kc. that is operating parallel to 9485 and 6210 kc. despite numerous reports that 6210 kc. has been replaced by the new outlet. The schedule reads 0500-0200. Reports from many DX'ers indicate that reception of the 15,065-kc. broadcasts is excellent during the day and generally poor at night in eastern areas, good to excellent at any time in midwest and western areas. Call-signs are HI3U on 9485 kc., HI2U on 6210 kc.; the call-sign on 15,065 kc. is not known yet. (WPE1BZD, WPE2ANW, WPE2AXS, WPE3AK, WPE3NF, WPE4BC, WPE4FI, WPE6BPN, WPE7AT, WPE8AIJ, WPE9AGK, WPE9KM, WPE0AE, BL)

Ethiopia—*R. Addis Ababa* is heard well at 1315-1345 in Eng. to Europe and at 1515-1545 in Eng. to West Africa on both 11,955 and 17,773 kc. Reports should be sent to P. O. Box 1364, Addis Ababa. (WPE1AGM, WPE1CR, WPE2AXS, WPE4BC, WPE4FI, WPE6EZ, WPE9KM)

Germany—*Deutsche Welle (Voice of Germany)*, Cologne, operates at 1215-1515 to Africa, replacing 11,870 kc. with 11,915 kc., dual to 15,275 kc. (WPE3BSY, WPE4FI)

Greece—*R. Athens* operates at 1215-1245 to France and England on 6075, 9605, 15,345, and 17,720 kc.; at 1400-1500 to Northwest Europe on 9605 and 11,720 kc.; to Greek Mariners at 1700-1730 on 11,720 kc. and at 1800-1830 on 6075 and 9605 kc. All Sunday broadcasts begin 75 minutes earlier. Reports go to Hellenic National Broadcasting Institute, 16 Mourousi St., Athens, Greece. (WPE3BOC, BL)

Guinea Republic—*R. Conakry*, Conakry, has been noted on 4910 kc. at 0145 with Eng. lessons. French news is given at 0200. (WPE0VB)

India—All India Radio stations noted lately, other than those in Delhi, include: Bombay on 7120 kc. at 2030-2230 in native language; Madras on 15,380 kc. at 0630-0730 with Indian music; and Gauhati, 4775 kc., weakly, from 0735 in native language. (WPE3NF, WPE4FI)

Israel—Tel Aviv was noted on 11,922 kc. at 1515 with Eng. news, dual to 9009 kc. Reception of signals from both outlets was excellent. (WPE3NF)

Italy—Add 6010 kc. and delete 11,905 kc. for



NEW!
TRADE MARK
BEST BUY!
UNITED SCIENTIFIC LABORATORIES, INC.

LEADS AGAIN WITH
CITIZENS "RADIO-PHONE"
BAND TR-910 TRANSCEIVER



Amazing at only

99.95
LIST

Furnished with Ceramic Microphone and one Transmitting Crystal

For Communication on the move!

- Push-to-talk with foolproof relay
- Full Squelch control
- Built-in "S" and plate current meter
- 5 channel Transmit
- 22 channel Vernier controlled receive
- Automatic noise limiter

Write for Brochure and Name of Your Nearest Dealer

UNITED SCIENTIFIC LABORATORIES, INC.

35-09 37th AVE., LONG ISLAND CITY 1, N. Y.
Also Mfr's of DeWald HI-FI Stereo Components and FM Radio

BUILD THE PROJECTS DESCRIBED IN THIS ISSUE OF

POPULAR ELECTRONICS

WITH THESE PRODUCTS

DIRECT-COUPLED HI-FI AMPLIFIER
Uses 2" x 11" x 7" aluminum chassis
BUD AC-407—\$1.58

ACROSS THE HAM BANDS—Screen Modulator
Uses 2 1/4" x 2 1/4" x 5" aluminum box
BUD CU-3004A—70¢

CITIZENS BAND Q-MULTIPLIER
Uses 5" x 4" x 3" aluminum box
BUD CU-3005A—96¢

RADIO-CONTROL 11-METER RECEIVER
Uses 7" x 5" x 3" aluminum box
BUD CU-2108A—\$1.65

All Bud products are available for immediate delivery from your Authorized Bud Distributor. They are the best for applications described in these projects.

WATCH FOR THESE LISTINGS EVERY MONTH
IN POPULAR ELECTRONICS

BUD RADIO, INC.
2118 East 55th Street Dept. P.E. Cleveland 3, Ohio

Eng. to N.A. at 1930-1950 and 2205-2225. (*WPE1BDB*, *WPE2DKP*, *WPE4FI*, *WPE6BME*, *WPE8MS*, *WPE9KM*)

Jordan—The 100-kw. xmtr of the Jordan B/C Service, Amman, is heard well on 7155

SHORT-WAVE CONTRIBUTORS

Stanley Schwartz (*WPE1AAC*), Bridgeport, Conn.
 Jim Silk (*WPE1AGM*), Madison, Conn.
 Paul Gough (*WPE1ASX*), West Newton, Mass.
 Robert Anderson (*WPE1BDB*), New Britain, Conn.
 Jerry Berg (*WPE1BM*), W. Hartford, Conn.
 Ubaldo DiBenedetto (*WPE1BZD*), Cohasset, Mass.
 Robert O'Connor (*WPE1CAU*), Holyoke, Mass.
 Jim O'Mara (*WPE1CR*), So. Boston, Mass.
 Edward Bowker (*WPE1KO*), Keene, N. H.
 Vic Travis (*WPE2ANW*), Syracuse, N. Y.
 Robert Newhart (*WPE2AXS*), Merchantville, N. J.
 Albert Mencher (*WPE2BRH*), Bayside, N. Y.
 Steve Bohac (*WPE2BYI*), Fairview, N. J.
 Thomas Campanile (*WPE2CKJ*), Brooklyn, N. Y.
 Joseph Russo (*WPE2CRX*), Toms River, N. J.
 Jeffrey Fritz (*WPE2CYE*), Wantagh, N. Y.
 Michael Baumann (*WPE2DFB*), Binghamton, N. Y.
 Al Burzynski (*WPE2DKP*), Niagara Falls, N. Y.
 Harold Neimans (*WPE2DPD*), Buffalo, N. Y.
 Steve Cosano (*WPE2DRF*), Pleasant Valley, N. Y.
 John Oldham (*WPE2DRH*), Livingston, N. J.
 Ralph Kurtz (*WPE2HIF*), Westfield, N. J.
 Doug Benson (*WPE2MI*), Schenectady, N. Y.
 C. Vernon Hyson (*WPE3IGZ*), Kensington, Md.
 Ed Kowalski (*WPE3AK*), Philadelphia, Pa.
 Charles Craft (*WPE3BIK*), Lansdale, Pa.
 John Brennan (*WPE3BIX*), Baltimore, Md.
 Paul Cherry (*WPE3BOC*), Philadelphia, Pa.
 Robert Dickson, Jr. (*WPE3BSY*), Wilmington, Del.
 George Cox (*WPE3NF*), New Castle, Del.
 Grady Ferguson (*WPE4BC*), Charlotte, N. C.
 John Puckett (*WPE4BNP*), Tampa, Fla.
 Dennis Jarrett (*WPE4BYE*), Ashland, Ky.
 Gary Yarus (*WPE4EC*), Pikeville, Ky.
 Roger Legke (*WPE4FI*), McLean, Va.
 Alan Knapp (*WPE4HJ*), Roanoke, Va.
 William Bing (*WPE5AG*), New Orleans, La.
 Don Kuykendall (*WPE5AHL*), Fort Worth, Texas
 Jack Stephenson (*WPE5XX*), Oklahoma City, Okla.
 Stewart MacKenzie, Jr. (*WPE6IA*), Long Beach, Calif.
 Joe Hypnarowski (*WPE6AZG*), San Diego, Calif.
 Tim Lovatt (*WPE6BME*), Azusa, Calif.
 Shaler Hanisch (*WPE6BNY*), Pasadena, Calif.
 J. Art Russell (*WPE6EZ*), San Diego, Calif.
 Don Beebe (*WPE7AT*), Seattle, Wash.
 David Hillenbrand (*WPE8AII*), Columbus, Ohio
 Jay Owen (*WPE8BXG*), Trenton, Mich.
 Richard St. Amour (*WPE8BYX*), Alpena, Mich.
 Richard England (*WPE8FI*), Columbus, Ohio
 Mike Kander (*WPE8MS*), Dayton, Ohio
 Mark Lewis (*WPE8WT*), Avon Lake, Ohio
 William Berghammer (*WPE9AGK*), Lombard, Ill.
 J. W. Megown (*WPE9DY*), Rolling Meadows, Ill.
 A. R. Niblack (*WPE9KM*), Vincennes, Ind.
 John Beaver, Sr. (*WPE9AE*), Pueblo, Colo.
 Frank Miller (*WPE9AMN*), Richmond, Mo.
 Bill Holscher (*WPE9ATE*), Webster Groves, Mo.
 Gerald Schoenhofen (*WPE9BIIG*), Minneapolis, Minn.
 Ward D. Stewart (*WPE9LVN*), Des Moines, Iowa
 George Buchanan (*WPE9VB*), Webster Groves, Mo.
 Wendell Craighead (*WPE9VU*), Kansas City, Kansas
 William Jacklin (*VE3PE1DO*), Parry Sound, Ont.
 David Digweed (*VE3PE5S*), St. Catharines, Ont.
 Jim Tomkins (*VE5PE2D*), Regina, Sask.
 Richard Lavolette (*VE7PE2M*), Richmond, B. C.
 Fortunato Elia (*FE*), Newark, N. J.
 G. K. Goodrick (*GG*), Bangkok, Thailand
 Bill Lund (*BL*), Santa Monica, Calif.
World Radio Handbook (WRH)

very small power, our station can be heard well in the United States." The letter does not give the actual power but it does state that 20- and 50-kw. xmtrs are expected shortly, at which time additional foreign language broadcasts, including Eng., will be started. Reports should be stamped addressed as follows: *Radio Katanga*, B.P. 1152, Elisabethville, Katanga State, via Brussels and Usumbura. (*WPE1BM*, *WPE0VB*)

Kuwait—*R. Kuwait* operates at 1400-1730 in Arabic with a news and weathercast at 1500-1515. This is a daily xmsn. Power is 5 kw. (*VE7PE2M*)

Malaya—The BBC Far Eastern Relay, Singapore, operates to N. & E. China, Korea, and Japan at 0415-0600 on 11,955 kc.; to Burma and Thailand at 0800-1150 (Saturdays to 1205) on 9690 kc. and at 0845-1150 (Saturdays to

SHORT-WAVE ABBREVIATIONS

anmt—Announcement	L.A.—Latin America
BBC—British Broadcasting Corp.	N.A.—North America
B/C—Broadcasting	R.—Radio
Eng.—English	s/on—Sign-on
ID—Identification	s/off—Sign-off
kc.—Kilocycles	veri—Verification
kw.—Kilowatts	xmsn—Transmission
	xmtr—Transmitter

1205) on 11,955 kc. The 11,820-kc. outlet is heard at 0520-0555 with Eng. variety shows. (*WPE3AGZ*, *WPE6AZG*)

Netherlands—Hilversum now broadcasts at 0900-0950 to S. Asia on 15,445 kc., replacing 15,425 kc., and at 1615-1705 to Europe and N.A. on 11,730 and 9590 kc., replacing 15,220 and 6020 kc. Another N.A. xmsn is scheduled at 2030-2120 on 9590 and 6025 kc. A xmsn in Dutch was noted from 2230 to 2256 s/off and also at 2030-2100 in Dutch on 6085 kc. (*WPE1BM*, *WPE2AXS*, *WPE2BRH*, *WPE2CYE*, *WPE2DFB*, *WPE2DRF*, *WPE6AA*, *WPE9KM*, *VE3PE5S*, *VE5PE2D*)

Nigeria—A veri letter is in from Peter Proudman, General Manager of the Eastern Nigeria B/C Service, P. O. Box 350, Enugu, Nigeria. Their schedule reads: 0000-0300 (Sundays from 0100) and 1030-1730 (Sundays from 1030, Saturdays to 1800) on 4855 kc.; and 0500-0900 (Saturdays to 0930, Sundays at 0330-1000) on 9635 kc. (*WPE1BM*)

Northern Rhodesia—Federal B/C Corp, Lusaka, has news and sports in Eng. at 0000 on 9580 kc. and African music at 0010. The signal is good at first but rapidly deteriorates after 0015. (*WPE9VU*)

Panama—The following short-wave stations are currently inactive: HOM50, 5995 kc.; HP5K, 6005 kc.; HORT, 6060 kc.; HOO, 6090 kc.; HP5H, 6122 kc.; HOQQ, 6140 kc.; HP5G, 6175 kc.; and HOJ53, 9645 kc. (*WRH*)

Paraguay—ZPA1, *R. Nacional del Paraguay*, Asuncion, is testing on 15,135 kc. at 1930 in Spanish. Reports go to Cnel. Martinez 224, Asuncion. (*WPE9AGK*)

Philippine Islands—The Far Eastern B/C Corp., Manila, gives a partial Eng. schedule as follows: 1600-1845 and 2030-0715 on DZH9, 15,300 kc.; 1600-1900 and 2030-1130 on DZ18, 21,515 kc.; 1830-2000 on DZF3, 15,385 kc.; 2130-0400 on DZH8, 11,855 kc., and DZ16, 17,805 kc.; 0230-0400, 0700-0815, and 1100-1130 on DZH7,

kc. at 2230-2240 with an all-Arabic xmsn. This frequency replaces 9530 kc. (*WPE4FI*, *WPE0VB*)

Katanga—*R. Katanga*, Elisabethville, 11,865 kc., has native music with French ID and anmts at 2306-2320. A veri letter from the station reads in part: "We are very pleased to know that, although we are emitting with

9730 kc.; 0400-0500 on DZH6, 6030 kc.; and 0715-1130 on DZF2, 11,920 kc. (WPE3AK)

Portugal—The latest schedule from *Emissora Nacional*, Lisbon, reads: to U.S.A., East Coast, at 1900-2300 on 11,875 kc. and at 1945-2300 on 9750 kc.; to U.S.A., West Coast, at 2100-2300 on 9740 kc.; to Brazil at 0930-1200 on 21,700 kc. (Sundays only on 17,895 kc.), at 1430-2045 on 17,895 kc., and at 1645-2100 on 15,125 kc. Another new channel is 6025 kc., noted at 1630-1700 and at 2100-2300 with the station's usual format. (WPE2AXS, WPE2MI, WPE8AIJ, WPE8FV, WPE9KM)

Portuguese India (Goa)—According to the only Eng. newspaper in Goa, *The Voice of Goa* is now on 21,580 kc. with xmsns to Africa at 1030-1130 in Portuguese and at 1130-1230 in Concani. (WPEIAC)

South Africa—Paradys has opened 21,495 kc. at 0700-1130, replacing 21,525 kc. and 17,855 kc. at 1130-1500, dual to 15,265 kc. In addition, 11,935 kc. is now assigned to Eng. to Africa on Tuesdays, Thursdays, and Saturdays, Afrikaans on remaining days at 1300-1500. (WPE4FI, WPE0AE)

Sweden—R. Sweden, Box 955, Stockholm 1, operates in Eng. at 0730-0845 to Far East on 15,420 and 7230 kc.; at 1115-1145 to Middle East on 15,240 and 11,705 kc.; at 0945-1015 to S. Asia on 15,240 and 9605 kc.; at 1245-1315 and 1445-1515 to Africa on 11,705 kc.; at 1530-1600 to Europe on 7210 kc.; at 0900-0930 to Eastern N.A. on 17,840 kc. and at 2045-2115 on 9725 kc.; and at 2215-2245 to Western N.A. on 9725

kc. (WPE2BRH, WPE3BIX, WPE3BSY, WPE4BNP, WPE4FI, WPE8MS, WPE0LN)

Tanganyika—Dar-es-Salaam is operating daily at 2215-0000, 0830-1415 (Saturdays to 1430) and Saturdays and Sundays at 0400-0530 on 5050 kc.; 0400-0615 on 7277 kc.; 1130-1415 (Saturdays and Sundays to 1430) on either 4845 or 4785 kc. (WPE8MS)

Thailand—Bangkok operates to N.A. at 2315-0015 on 11,910 kc. with news at 2325-2340. The General Service is aired at 0625-0757 with an Eng. newscast at 0530-0545 on the same channel. (WPE5AG, GG)

Togo Republic—Radiodiffusion du Togo, Lome, operates on 5047 kc. from 0100 s/on with an anthem to past 0145. A newscast in French is given at 0130. (WPE0VB)

Tunisia—Tunis is heard at 0700-1100 in Arabic on 17,720 kc. This replaces the former 17,705-kc. outlet. (WPE4FI)

United Arab Republic—Cairo has moved to 11,745 kc. from 11,675 kc., but more checking is required to determine whether this is a permanent move. It was noted at 2200 s/on in the usual Arabic. (WPE9KM)

Windward Islands—St. Georges, Grenada, now operates at 1600-1745 on 15,395 kc. after previous use of 15,400 kc. (in November), 15,150 kc. (in October), 15,370 kc. (in September), and 15,085 kc. (in August). It moves to 11,715 kc. at 1800-2115. (WPE1CR, WPE2CRX, WPE3AK, WPE3BSY, WPE4BC, WPE4FI, WPE4HJ, WPE8AIJ, WPE9CDY, WPE9KM, WPE0AMN)

-50-

GET INTO ELECTRONICS

V.T.I. training leads to success as technicians, field engineers, specialists in communications, guided missiles, computers, radar, automation. Basic & advanced courses in theory & laboratory. Assoc. degree in 29 mos. B. S. obtainable. ECPD accredited, G.I. approved. Graduates with major companies. Start Sept., Feb. Dorms, campus. H. S. graduates or equivalent. Catalog

VALPARAISO TECHNICAL INSTITUTE

Dept. PE VALPARAISO, INDIANA

2 WAY PORTABLE RADIO SET



Sends-receives-your voice 1/2 to 10 miles as shown with built-in antenna—depending on location—more with outside antenna. No permits, license, age limit or restrictions on gov't appt. "11 Mir LP Band." Complete ready to operate—nothing else to buy. Guaranteed to work. 110 volt "plug-in" ANY-WHERE, ANYTIME! 2 or more sets can be used together. "Times in" all Citizens Band Channels.

SEND ONLY \$5 deposit for each set and pay postman balance of \$24.95 COD plus postage or send \$29.95 for postpaid insured delivery, free circular. Available only from: **WESTERN RADIO Dept. HPE-3 KEARNEY, NEBRASKA**



Bargain Meter!
Super-sensitive!
Multi-purpose!

It's NEW! 20,000 OHMS PER VOLT!

Can out-perform meters twice the size and three times the price! What a range! Measures DC Voltage, AC Voltage, DC Current, Resistance, Capacitance, and Decibels! Super sensitive. Easy-to-read. Latest wide gentle arc-shaped face. Size: 3 3/4" x 4 1/2" x 1 1/16". Anyone can use it. Full instructions included. Get it TODAY for only **\$12.95**

Add 25c for postage and handling. Send check with order. Satisfaction guar. Calif. residents add 4% tax. For latest service write to Dept. PE 031.

KORD CO.

3366 SCADLOCK LANE
SHERMAN OAKS, CALIF.

Hear 'Em — Work 'Em Better with BROWNING CB Equipment

R-2700 CB RECEIVER
\$149.00

S-NINE CB TRANSMITTER
\$119.50



Make your CB base station a real communications center with this Browning team. Highly sensitive and selective R-2700 Receiver delivers sharp, noise-free reception on all CB channels. Overcomes even the most severe atmospheric and man-made interference. Browning S-NINE Transmitter allows full power transmission on all channels — introduces new features and advanced design never previously utilized in CB communications.

Also Available
R-2700 Receiver PLUS
T-2700 Transmitter
SPECIAL PACKAGE PRICE

Send for Free Literature



browning
101 UNION AVE., LACONIA, N.H.

SATISFACTION GUARANTEED FOUR CONVENIENT PURCHASE PLANS

POPULAR ELECTRONICS

Advertisers' Index

MARCH 1961

ADVERTISER	PAGE NO.	ADVERTISER	PAGE NO.
A.E.S., Inc.	23	Lafayette Radio	29
Acro Electronic Products Co.	24	Lektron	113
Airex Corporation	106	Midway Company	120
Allied Radio	21, 110, 111	Milwaukee School of Engineering	38
Association of Electro-Mechano Colleges	107	Mosley Electronics, Inc.	108
Audio Devices, Inc.	37	Moss Electronic, Inc.	3rd, 4th COVER
Bailey Technical Schools	26	Multi-Products Company	18
Blonder-Tongue	22	National Radio Institute	33, 34, 112
Browning	127	National Technical Schools	13
Bud Radio, Inc.	125	North American Philips Co., Inc.	12
Burstein-Applebee Co.	36	Olson Electronics	128
Cadro Industries Corp.	15	Palmer, Joe	112
Capitol Radio Engineering Institute	31	Picture Tube Outlet	36
Christy Trades School	120	Progressive "Edu-Kits", Inc.	105
Cleveland Institute of Electronics	17	RCA Institutes, Inc.	98, 99, 100, 101
Colorado Technical Institute	115	Rad-Tel Tube Co.	132
Coyne Electrical School	11, 109	Radio Corporation of America	2nd COVER
DeVry Technical Institute	5	Radio Shack Corp.	103
EICO	40	Radio-Television Training School	7
Electro-Voice, Inc.	1	Rider Publisher, Inc., John F.	14
Electronics Book Service	116, 117	Schober Organ Corp., The	16
Esso Radio Co.	122	Scott, Inc., H. H.	97
General Techniques, Inc.	124	SoNar Electronic Tube Co.	102
Grantham School of Electronics	19	Standard Kollsman Industries, Inc.	27
Greenlee Tool Co.	24	Tech-Serv., Inc.	115
Grove Electronic Supply Company	122	Teleplex Co.	102
Hallcrafters	119	Thorens	25
Heath Company	92, 93, 94, 95	Tri-State College	102
Herman Electronics, Inc.	119	Tru-Vac	32
Holt, Rinehart and Winston, Inc.	28	United Scientific Laboratories, Inc.	125
Indiana Technical College	108	University Loudspeakers, Inc.	20
International Crystal Mfg. Co., Inc.	39, 91	Valparaiso Technical Institute	127
Johnson Co., E.F.	30, 121	Van Nostrand Company, Inc., D.	3
Key Electronics	108	Vanguard Electronic Labs	112
Kord Co.	127	Vocaline Company of America	10
Kuhlman Instrument Co., Inc.	124	Western Radio	120, 122, 124, 127
Kuhn Electronics, Inc.	30		

CUT OUT AND MAIL TODAY



8 FREE
BIG ISSUES

OLSON CATALOGS

TYPICAL VALUE

DIAL TELEPHONE

\$7.93

No. PH-31

Standard phone
company model.



We will send you a new issue every 6 weeks for a full year - NO CHARGE! Compare our World Famous Values.

SEND FREE CATALOGS

Send Dial Telephone @ \$7.93, plus postage

MAIL TO: **OLSON ELECTRONICS**


(Formerly Olson Radio)
817 S. Forge St., Akron 8, Ohio

NAME _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____

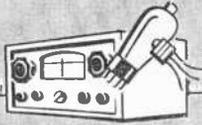Always say you saw it in—POPULAR ELECTRONICS



ELECTRONICS MARKET PLACE

RATE: 60¢ per word. Minimum 10 words prepaid. May issue
POPULAR ELECTRONICS, 1 Park Ave., New York 16, N. Y.

closes March 5th. Send order and remittance to Martin Lincoln.

FOR SALE

SURPLUS Tech Manuals—APR/1, ARC-5 VHF Units, ARN-5, APN 1, 4, 9, ARN-14, ARC-5 LFMHF, TS-34, TS-375, \$7.00 Each Postpaid—Many others, write your needs, We Buy Too. Propagation Products Co., Box 2513, Norfolk, Va.

RUBBER Stamps—Your call letters, name and address on your own rubber stamp \$1.65 postpaid. Name and address alone \$1.50. Hamstamp, 186 Linden Ave., Glen Ridge, N. J.

16 Tested Transistor plans, Flyer, catalog—all 25c. Laboratories, 1131-L Valota, Redwood City, California.

AUTO Radio Distributor. Selling, Servicing, Becker Blaupunkt, FM-AM, other European, American Sets. Save 30%+! Square Electronics, 150-60 Northern Blvd., Flushing, N. Y.

CITIZENS' BAND! Add a Hushpuppy noise suppressor to your Heathkit, Lafayette, Globe, etc. transceiver. Squelch Action! Completely Wired. Guaranteed. \$4.98. Western Mass. Electronics, Great Barrington 1, Mass.

TUBES—TV and Radio tubes. Guaranteed—Save up to 80%—Write: Emkay Electronics, P.O. Box 142, Blythebourne Station, Brooklyn 19, N. Y.

WPE-SWL-CB-QSL Cards — Samples 10¢ — "Brownie" W3CJ1, 3110A Lehigh, Allentown, Penna.

DIAGRAMS for repairing radios. Television \$2.00. Give make, model. Diagram Service, Box 672-PE, Hartford 1, Conn.

CITIZEN-Banders! Too much commotion? An OZCO "Snoozer" squelches everything except conversation. Easily installed by insertion in speaker leads. Time-proved circuit now features exclusive matched resistors and factory test for guaranteed satisfaction. Fairly priced. Only \$2.00 each, \$3.95 pair, postpaid, tax included. Order today from OZCO Sales, Canaan, Connecticut.

GOVERNMENT Surplus Receivers, Transmitters, Snopescopes, Parabolic Reflectors, Picture Catalog 10¢. Meshna, Malden 48, Mass.

PARTY Records—Sampler, catalog \$1.00. 3 different \$3.00 postpaid. DRC-11024 Magnolia, No. Hollywood, Calif.

SOMETHING for sale? Place a classified ad in this section. Low-cost, fast results. It's easy.

TV Tuners—Rebuilt or Exchanged \$9.95 complete—all types—fast, guaranteed service. Send tuner with all parts to: L.A. Tuner Exchange, 4611 West Jefferson Blvd., Los Angeles 16, California.

ELECTRONIC Automobile Ignition Lock. Never worry about losing your ignition keys. Only the foolproof combination will switch your ignition on. Detailed construction plans \$1.00. C & M Enterprises, Apalachin, N. Y.

BE A Spy. Correspondence course on wire tapping, bugging, telescopic sound pickup, recording techniques, microphotography, and invisible photography. Lessons in surveillance, tailing, and use of equipment. Complete course \$22.50. C. Carrier Co., 5880 Hollywood Blvd., Hollywood 28, Calif.

TV Tape Recorder. Build your own Video Recorder. Complete correspondence course and construction details. \$22.50. C. Carrier Co., 5880 Hollywood Blvd., Hollywood 28, Calif.

COLOR TV. Convert your black and white TV to color. Completely Electronic. No mechanical gadgets. Costs about \$35. Complete construction details \$4.75. DB Enterprises, 8959 Wonderland Ave., Hollywood 46, Calif.

JUNK Your Distributor and Voltage Regulator. Improve automobile mileage and performance. Construction details for transistorized distributor and voltage regulator. \$4.75. No moving parts. DB Enterprises, 8959 Wonderland Ave., Hollywood 46, Calif.

TELEPHONE Voice Switch (LS-500). Actuates automatically and unattended any tape or wire recorder. Pictorial installation instructions included. \$23.75. Post Paid US. WJS Electronics, 1130 N. Highland Ave., Los Angeles 38, Calif.

TELEPHONE Extension In Your Car. Answer your home telephone by radio from your car. Complete diagrams and instructions \$2.00. C. Carrier Co., 5880 Hollywood Blvd., Hollywood 28, Calif.

EAVESDROP with a pack of cigarettes. Miniature transistorized FM Radio Transmitter. Complete diagrams and instructions \$2.00. C. Carrier Co., 5880 Hollywood Blvd., Hollywood 28, Calif.

SOUND Operated Relay—For dictating or private use—Actuate recorder only when sound is present—literature and price. W.J.S. Electronics, 1130 North Highland Ave., Hollywood 38, Calif.

TV Camera. Build for less than \$50. Construction Details \$4.75. DB Enterprises, 8959 Wonderland Ave., Hollywood 46, Calif.

INVESTIGATORS! Do your own sound work. Write for free brochure of latest electronic equipment. WJS Electronics, 1130 N. Highland Ave., Los Angeles 38, Calif.

SCHEMATICS For Repairing, Wiring, Government Surplus Receivers, Transmitters, Test Sets \$1.00 Each. (Give Model) Free List, Bill Step Company, Drawer 178PE, Ellenton, Florida.

HAMS Experiment With Ratty, Buy a Complete Teletype Machine. Write: Hedeem, 1322 Sharon Rd., Tallahassee, Fla.

"DIAGRAMS and service information for any radio, television or amplifier \$1.50 per each. Audio Center, P.O. Box 326, Denison, Texas."

GOVERNMENT Sells Surplus: Electronics; Oscilloscopes; Transceivers; Test Equipment; Radar; Sonar; Walkie-Talkies; Boats; Jeeps; Aircrafts; Misc.—Send for "U.S. Depot Directory & Procedures"—\$1.00—Brody, Box 425(PE), Nanuet, New York.

INFRA-Red!! Snooperscopes, Optics, Lamps, Parts. World's largest stock Infra-red components. Write for FREE Infra-red Catalog. McNeal Electric and Equipment, Dept. PE-3, 4736 Olive, St. Louis, Mo.

SCIENCE Project Materials Surplus Optics, Electronics Hard To Get Materials. Catalog 25¢. Wabash Instruments & Specialties, Inc., P.O. Box 194, Wabash, Indiana.

"SPECIAL! WPE-SWL-CB-QSL Cards, 3 colors, \$2.50 per 100. Free Samples, Garth Company, Jutland, New Jersey.

CITIZENS Band; Lafayette HE-15, 15A owners, hear only the channel you tune. Dual Conversation Adapter reduces bandwidth to 5KC @ 6DB, 12KC @ 20DB. Send your unit (in working order) and \$39.95 check or money order. We will promptly install and return prepaid. Or send no money and we will return C.O.D. \$39.95 plus postage. Adapter fully guaranteed. Adapter in kit form and modifications for other units available. Send for free literature. Bainbridge Radio, 2649 Bainbridge Ave., New York 58, N. Y.

CITIZEN Band! Call Books and Equipment. Send your name, address, for Free Information. Werholm Electronics, 4432 Shephard Street, Oakland, California.

DUMONT—Hytron Electronic Receiving Tubes. Also other bargains. Sonoret, 36 Woodbury, Wilkes-Barre, Penna.

KIT of 100 1/2 Watt Resistors, \$3.95. 75 600 Volt Capacitors .001 MFD to .1 MFD, \$4.98. All new first quality American components. Wy'ie Products, Box 8615, Dallas 16, Texas.

"C.B. or Ham call letter plates for your car in beautiful Anodized Aluminum, only \$3.98. Free brochure. P.O. Box 1159, New York 1, N. Y."

CITIZENS Band! Add a squelch to your transceiver. \$2.25 kit. \$3.50 wired. Mark, Box 182, Branford, Connecticut.

MBF-Collins-11 Meters-International Executives-Globes-Cititones Used trade ins—Perfect condition—reasonable. Fox Radio Service, 5610 Gifford, Maywood, California.

POLICE Radar Detector. Stop before those radar speed traps. Fool proof, legal system. Complete diagrams and instructions \$2.75. C. Carrier Co., 5880 Hollywood Blvd., Hollywood 28, Calif.


BALANCE Your Stereo from Across the Room—How it sounds where you sit—that's what counts! Remote volume and balance control works with any system using separate preamplifier and power amplifier or any tape deck with cathode follower outputs. Small control (5 x 3 x 2 inches) can be placed as far as 30 feet away. \$26.95 in walnut or mahogany housing, \$19.95 in metal. Sun Radio Service, 320 Chestnut Street, Kearny, New Jersey. WY 1-0564.

WANTED

BUY, Sell or trade. Short-wave ham & citizens receivers, transmitters. Trigger-W9IVJ, 7361 1/2 W. North Ave., River Forest, Ill. Chicago # TUXedo 9-6429, Mon-Fri., 12N-9PM; Sat., 9AM-5PM.

WANT to buy good equipment and accessories? Place a low-cost classified ad in this space. For information, write: Martin Lincoln, Popular Electronics, One Park Avenue, New York 16, N. Y.

HIGH-FIDELITY

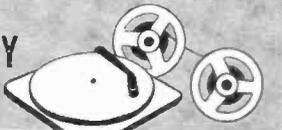

DON'T Buy Hi-Fi Components, Kits, Tape, Tape Recorders until you get our low, low return mail quotes: "We Guarantee Not To Be Undersold." Wholesale Catalog Free. Hi-Fidelity Center, 1797PC First Avenue, New York 28, N. Y.

PRICES? The Best! Factory-Sealed Hi-Fi Components? Yes! Send for free catalog. Audion, 25P Oxford Road, Massapequa, N. Y.

DISGUSTED with "Hi" Hi-Fi Prices? Unusual discounts on your High Fidelity Requirements. Write Key Electronics, 120 Liberty St., New York 6, N. Y. Cloverdale 8-4288.

RECORDERS, components. Free wholesale catalogue. Carston, 125-P East 88, N. Y. C. 28.

ARE prices on Hi-Fi components too high? Write Dixie Hi-Fi, 12402 Connecticut Avenue, Silver Spring, Maryland.

PROMPT Delivery, We Will Not Be Undersold. Amplifiers, Tape Recorders, Tuners, Etc. No Catalogs, Air Mail Quotes. Compare. L. M. Brown Sales Corp. Dept. P, 239 E. 24 St., N.Y. 10, N.Y.

TAPE & RECORDERS


NEW Self-Hypnosis Tape! Free literature. McKinley Co., Box 3038, San Bernardino, Calif.

AMPEX, Concertone, Magnecord, Presto, Bogen, Tandberg, Pentron, Sherwood, Rek-O-Kut, Scott, Shure, Dynakit, others. Trades. Byonton Studio, Dept. PE, 10 Pennsylvania Ave., Tuckahoe, N. Y.

TAPE Recorders, Hi-Fi components, Sleep Learning Equipment, tapes, Unusual Values. Free Catalog. Dressner, 69-02F, 174 St., Flushing 65, N. Y.

SOMETHING for sale? Place a classified ad in this section. Low-cost, fast results. It's easy.

INSTRUCTION

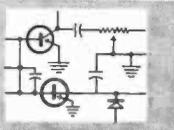

MOTION Pictures, 16mm Sound, for Teaching Electronic Theory and Application—Covers Tubes, Antennas, Transistors, Test Equipment, Etc.—Many Titles, Detailed and Descriptive Lists 25c. Propagation Products Co., Box 2513 Norfolk, Virginia.

BE a Jet Engine Specialist! Earn high wages. New course on Ramjets, Pulsejets, Turbojets, Rockets, Compressors, Turbines, Afterburners, Ignition, etc. Fully illustrated. Complete, only \$14.95. Afraid of Girls? Stop! Improve yourself. Know "What" to do. Develop "Winning Ways." New confidential kit, only \$9.95. Be a Detective! Know secrets of Criminology, Fingerprinting, Tracing, Tailing, etc. Develop your "Deductive Skills." Complete course, only \$5.95. Special! All three, \$25.00. Satisfaction guaranteed. Wilford's, 7400 Benjamin Franklin Station, Washington 4, D. C.

ENGINEERING Education for the Space Age. Northrop Institute of Technology is a privately endowed, nonprofit college of engineering offering a complete Bachelor of Science Degree Program and Two-Year accredited technical institute curricula. Students from 50 states, many foreign countries. Outstandingly successful graduates employed in aeronautics, electronics, and space technology. Write today for catalog—no obligation. Northrop Institute of Technology, 1179 West Arbor Vitae Street, Inglewood 1, California.

LEARN all types drawing, reading blueprints schematic wirings. Send 2 dollars chapter. Louis Prior, 2309 169th Street, Whitestone, New York.

EXPERIMENT with nature's electronics. Instructions—Stillwater, Box 337E, Morris Plains, New Jersey.

BOOKS

BOOKS—All 10¢, 2000 titles, all subjects, catalog free. Cosma, Clayton, Ga.

WRITE Martin Lincoln, Popular Electronics, One Park Avenue, New York 16, N. Y. for information on how to place a classified ad in this section.

BUSINESS OPPORTUNITIES

GOOD Profits in packaging & distributing small new product. Forward \$3.25 M.O. for unit to C.P. Enterprise, Box 541, Moline, Ill.

JAPAN Directory. 145 Japanese manufacturing exporters, Japan and Hong Kong trade journal information. Asia opportunities. \$1.00 today. Nippon Annai, Box 1150 T, Spokane 10, Washington.

SOMEONE "borrowing" your personal copy of Popular Electronics each month? You ought to be taking advantage of Popular Electronics' convenient re-sale plan. Sell copies in your store . . . perform a good service for your customers . . . with no risk involved. For details, write: Direct Sales Department, Popular Electronics, One Park Avenue, New York 16, New York.

INVENTIONS WANTED

INVENTIONS wanted. Patented; unpatented. Global Marketing Service, 2420-P 77th, Oakland 5, Calif.

INVENTIONS Wanted for immediate promotion! Patented, unpatented. Outright cash; royalties! Casco, Dept. BB, Mills Building, Washington 6, D. C.

INVENTORS! Stymied by engineering solutions to ideas? Graduate help now, available. Drawings also made upon request. Complete rights guaranteed by disclosure certificate. Send \$1.00 for details. Devco Lab, Box 26, Hazlewood, Missouri.

MISCELLANEOUS

UNUSUAL Electrical Devices Wholesale. Literature 25¢. Wellco, Box 3055, North Hollywood, California.



SHOPPING GUIDE

Classified

A HANDY REFERENCE TO PRODUCTS AND SERVICES NOT NECESSARILY ELECTRONIC, BUT OF WIDE GENERAL INTEREST

STAMPS & COINS

FREE! \$1.00 worth, your choice, from first stamp selection. No strings! Adults only. Rush request now. Philatelics, Dept. EMG-F, New Paltz, N. Y.

50 WORLD Wide Stamps, many exciting commemoratives, for only 10¢ and stamped self-addressed envelope. No approvals will be sent. Popular Electronics, Box 105, 1 Park Avenue, New York 16, New York.

OVER 400,000 buyers and sellers will read your ad when placed in this space. It costs only 60¢ per word; minimum of 10 words including your name and address. Send order and remittance to: Martin Lincoln, Popular Electronics, One Park Avenue, New York 16, N. Y.

PHOTOGRAPHY—FILM EQUIPMENT, SERVICES

OPTICAL-Science-Math Bargains—Request Free Giant catalog "CJ"—128 pages—Astronomical Telescopes, Microscopes, Lenses, Binoculars, Kits, Parts, Amazing war surplus bargains. Edmund Scientific Co., Barrington, New Jersey.

FREE! New 1961 catalog of all photographic books available. For your copy, send postcard with name and address to Catalog Popular Photography Book Service, One Park Ave., New York 16, N. Y.

PLASTICS

NEW Liquid Casting Plastic, clear, colors. Embed real flowers, butterflies, photos, coins. Send 25¢ for two handbooks "How to Cast Liquid Plastics" and "How to Make Extra Money at Home." Castolite, Dept. C-108, Woodstock, Illinois.

LEATHERCRAFT

FREE "Do-It-Yourself" Leathercraft Catalog. Tandy Leather Company, Box 791-H-39, Fort Worth, Texas.

BUSINESS OPPORTUNITIES

GROW Mushrooms. Cellar, shed and outdoors. Spare, full time, year round. We pay \$4.50 lb. dried. We have 29,000 customers. Free Book. Mushrooms, Dept. 334, 2954 Admiral Way, Seattle, Wash.

MAKE \$25-\$50 Week, clipping newspaper items for publishers. Some clippings worth \$5.00 each. Particulars free. National, 81-DG, Knickerbocker Station, New York.

VENDING Machines—No Selling. Operate a route of coin machines and earn amazing profits. 32-page catalog free. Parkway Machine Corporation, Dept. 12, 715 Ensor St., Baltimore 2, Md.

BUY Direct from factories. Appliances, cameras, watches! Free details! Cam Co., 6810PE 20th Ave., Brooklyn 4, N. Y.

WRITE Martin Lincoln, Popular Electronics, One Park Avenue, New York 16, N. Y. for information on how to place a classified ad in this section.

EDUCATIONAL OPPORTUNITIES

BE A Real Estate Broker. Insure security for yourself and your family. Study at home. Prepare for state examination. GI approved. Write for free book today. Weaver School of Real Estate. 2024 J. Grand, Kansas City, Missouri.

FREE L.P. Record and book gives instructive facts about Sleep-Education and the Audio Educator—the short cut method to learning and self-development—no obligation—SDRF—Dept. L 3, 104 East 40th Street, New York 16, N. Y.

DETECTIVE Profession. Home Study. Badge, Certificate, Future. 4563-AG York, Los Angeles 41, Calif.

EMPLOYMENT INFORMATION

HIGH Paying Jobs in Foreign Lands! Send \$2.00 for complete scoop! Foreign Opportunities, Box 172, Columbus 16, Ohio.

EARN Extra money selling advertising book matches. Free samples furnished. Matchcorp, Dept. MD 31, Chicago 32, Illinois.

35,048 job openings paying up to \$25,000. U. S. and abroad (215 in South Pacific alone). Interview, moving expenses paid on 15,000. Sure-fire formula for successful resume. \$1. Money-back guarantee. Who's Hiring Who. Dept. PE, 2020 M St., Washington 6, D. C.

EXCLUSIVE Employment Information Free. 50,000 Jobs Open. High Pay. Nationwide-Worldwide. Elsing, Box 12, Detroit 13, Michigan.

MISCELLANEOUS

"WINEMAKING, Beer, Ale." Highest powered methods. Illustrated. \$2.20. Eaton Bookstore, Box 1242-C, Santa Rosa, California.

WHATEVER your needs, Popular Electronics classified can solve them. Simply place an ad in these columns and watch your results pour in.

SEND me your name and I'll tell you about a method that lets you take giant bass out of waters that other folks say are "fished out". Facts free. Write Eric R. Fare, Highland Park 22, Illinois.

"HOMEBREW." Make it yourself. Complete instructions \$1.75. Homecrafts, Box 587-A, Bellevue, Nebraska.

LETTERHEADS, Billheads, Envelopes. Surprise deal. Free Samples. Okayprint, Martins Ferry, Ohio.

SOMEONE "borrowing" your personal copy of Popular Electronics each month? You ought to be taking advantage of Popular Electronics' convenient re-sale plan. Sell copies in your store . . . perform a good service for your customers . . . with no risk involved. For details, write: Direct Sales Department. Popular Electronics, One Park Avenue, New York 16, New York.

THE SIGN OF RAD-TEL'S QUALITY PERFORMANCE

BUY DIRECT FROM RAD-TEL!!
ORDER RAD-TEL'S FIRST QUALITY TUBES TODAY!

NOT USED!! NOT PULLED OUT OF SETS!!

SERVICEMEN: HUGE SAVINGS!! COMPARE!!
FAST ONE DAY SERVICE.

GUARANTEED ONE FULL YEAR UP TO 75% OFF ON BRAND NEW TUBES

SEND FOR FREE TROUBLE SHOOTER GUIDE AND NEW TUBE & PARTS CATALOG



TRANSISTORS — AT FABULOUS DISCOUNTS					
PRICE	TYPE	RATING	ELECTRICAL CHARACTERISTICS		life
<input type="checkbox"/> RF 49 ea.	GE PNP ALLOY JUNCTION GENERAL PURPOSE RF/AF	200 mW	1CB0 max.	1EB0 max.	VCE — 1.5 lb = 5 ma 20 min
<input type="checkbox"/> AF 39 ea.			20 ma VCB — -3V	20 ja VEB — -3V	
<input type="checkbox"/> 80 ea.	Power AF Mgd. Freq. to 3		20 ma VCB — -16V	20 ma VEB — -16V	VCE — 1.5 lb = 1 ma 40 min
<input type="checkbox"/> 140 ea.	Hi Power 15 AMP to 36	MIN. POWER OUTPUT 2.25 W	40 ma VCB — -100	40 ma VEB — -100	VCE — 1.5 lb = 1 ma 30 min

SILICON RECTIFIER

35 AMP 50 PIV (max. 20 ma)

\$2.50 ea.

Lots of 10 \$2.25 ea. (No Hardware)

EACH TUBE INDIVIDUALLY & ATTRACTIVELY BOXED

Qty. Type	Price	Qty. Type	Price	Qty. Type	Price
0Z3M	.79	6AW8	.89	12AF6	.49
1AX2	.62	6AX4	.65	12AJ6	.46
1B3GT	.79	6AX7	.64	12AL5	.45
1DMS	.55	6BA6	.49	12AL8	.95
1G3	.73	6BC5	.54	12A05	.52
1J3	.73	6BC7	.84	12A16	.43
1K3	.73	6BC8	.97	12A17	.76
1L6	1.05	6B06	.51	12A06	.50
1LMS	.59	6BE5	.55	12A07	.60
1RS	.62	6BF6	.44	12AV5	.97
1SS	.51	6BG6	1.66	12AV6	.41
1T4	.58	6BH6	.65	12AV7	.75
1U4	.57	6B8B	.87	12AX4	.67
1U5	.50	6B16	.62	12AX7	.63
1X2B	.82	6BK7	.85	12AZ7	.86
2AF4	.96	6BL7	1.00	12B4	.63
3AL5	.42	6BN4	.57	12BAG	.50
3AU6	.51	6BN6	.74	12B06	.50
3AV5	.41	6B05	.65	12B66	.53
3BA5	.51	6B06GT	1.05	12B76	.44
3BC5	.54	6B07	.95	12B97	.73
3BE5	.52	6BR8	.78	12B16	.66
3BN5	.76	6BR8	.70	12B06	1.06
3BU8	.78	6BY6	.54	12B77	.74
3BY6	.55	6BZ6	.54	12B27	.75
3BZ6	.55	6BZ7	.97	12C5	.59
3CB6	.54	6C4	.43	12CA5	.56
3CF6	.60	6CB6	.54	12CN5	.56
3CE5	.52	6C06	1.42	12CR6	.54
3CV5	.71	6CF6	.64	12C05	.58
3OK6	.60	6CG7	.60	12C16	1.05
3OT6	.50	6C08	.77	12C76	.51
3Q5	.80	6C07	.66	12D85	.69
3S4	.61	6C7	.65	12D8	.75
3V4	.58	6CR6	.51	12D18	.85

4BC5	.56	6CS6	.57	12DM7	.67
4BC8	.96	6CU5	.58	12D06	1.04
4BNE	.75	6CUE	1.08	12O57	.79
4BQ7	.96	6CV5	.70	12D26	.56
4BS5	.98	6CY7	.71	12EL6	.50
4BU8	.71	6DA4	.68	12E66	.54
4BZ6	.58	6DB5	.69	12E26	.53
4BZ7	.96	6DF6	.58	12F5	.66
4CS6	.61	6DCE	.59	12F8	.65
4DE6	.62	6D06	1.10	12FM6	.46
4DK6	.60	6DT5	.76	12K5	.65
4DT6	.55	6DT6	.53	12SA7M	.86
5AM8	.79	6E08	.79	12SK7GT	.77
5AN8	.86	6E8	.79	12SN7	.64
5A05	.52	6HG7	.58	12S07M	.73
5AT8	.80	6I5GT	.51	12U7	.62
5BK7A	.82	6J6	.67	12V6GT	.53

5BQ7	.97	6K6	.63	12W6	.69
5BR8	.79	6S4	.48	12X4	.38
5CG8	.76	6SA7GT	.76	17AX4	.67
5CL8	.76	6SK7	.74	17B06	1.09
5E8	.80	6SL7	.80	17C5	.58
5E08	.80	6SN7	.65	17CA5	.62
5I6	.68	6S07	.73	17D4	.69
5I8	.81	6T4	.99	17D06	1.06
5J4	.60	6U8	.78	17L6	.58
5U8	.81	6V6GT	.54	17W6	.70
5V6	.56	6W4	.54	19A14	.83
5X8	.78	6W6	.69	19B6G	1.39
5Y3	.46	6X4	.39	19T8	.80
6AB4	.46	6X5GT	.53	21E6	1.49
6AC7	.96	6X8	.77	25B06	1.11
6AF3	.73	7AU7	.61	25C5	.53
6AF4	.97	7A8	.68	25CA5	.59

6AG5	.65	7B6	.69	25C06	1.44
6AH6	.99	7Y4	.69	25C06	1.11
6AK5	.95	6AB8	.83	25D16	1.42
6AL5	.47	6AW8	.93	25EH5	.55
6AM8	.78	6B05	.60	25L6	.57
6AN4	.95	6CC7	.62	25W4	.68
6AN8	.85	6CM7	.68	25Z6	.66
6A05	.50	6CN7	.97	35C5	.51
6AR5	.55	6CX8	.93	35L6	.57
6AS5	.60	6E8B	.94	35W4	.52
6AT6	.43	11CY7	.75	35Z5GT	.60
6AT8	.79	12A4	.60	50B5	.60
6AU4	.82	12AB5	.55	50C5	.53
6AU6	.50	12AC6	.49	50D4	.37
6AU7	.61	12AD6	.57	50EH5	.55
6A08	.87	12AE6	.43	50L6	.61
6AV6	.40	12AF3	.73	11Z7	.81



NOT AFFILIATED WITH ANY OTHER MAIL ORDER TUBE COMPANY

RAD-TEL TUBE CO.

55 CHAMBERS STREET, NEWARK 5, N. J. DEPT. PE-361

TERMS: 25% deposit must accompany all orders, balance COD. Orders under \$5: add \$1 handling charge plus postage. Orders over \$5: plus postage. Approx. 8 tubes per 1 lb. Subject to prior sale. No COD's outside continental USA.

PRINTED IN U.S.A.

SHIPPED ON APPROVAL NO MONEY WITH ORDER - NO C. O. D.

Superior's New Model 85—a DYNAMIC type TRANS-CONDUCTANCE

TUBE TESTER



Model 85—Trans-Conductance Tube Tester. Total Price—\$52.50.

Terms: \$12.50 after 10 day trial, then \$8.00 monthly for 5 months if satisfactory. Otherwise return, no explanation necessary.

• Employs latest improved TRANS-CONDUCTANCE circuit. Tests tubes under "dynamic" (simulated) operating conditions. An in-phase signal is impressed on the input section of a tube and the resultant plate current change is measured as a function of tube quality. This provides the most suitable method of simulating the manner in which tubes actually operate in radio, TV receivers, amplifiers and other circuits. Amplification factor, plate resistance and cathode emission are all correlated in one meter reading.

• **SYMBOL REFERENCES:** For the first time ever in a trans-conductance tube tester, Model 85 employs time-saving symbols (%, +, ●, ▲, ■) in place of difficult-to-remember letters previously used. Repeated time studies proved to us that use of these scientifically selected symbols speeded up the element switching step. As the tube manufacturers increase the release of new tube types, this time-saving feature becomes more necessary and advantageous.

• **THE "FREE-POINT" LEVER TYPE ELEMENT SWITCH ASSEMBLY** marked according to RETMA basing, permits application of test voltages to any of the elements of a tube. The addition of an extra switch position permits the application of the necessary grid voltage needed for dynamic testing and insures against possible obsolescence due to changes in basing design.

• **NEW IMPROVED TYPE METER** with sealed air-damping chamber provides accurate, vibrationless readings.

• **FREE FIVE (5) YEAR CHART DATA SERVICE.** The chart provided with Model 85 includes easy-to-read listings for over 1,000 modern tube types. Revised up-to-date subsequent charts will be mailed to all Model 85 purchasers at no charge for a period of five years after date of purchase.

• **SPRING RETURN SAFETY SWITCH** guards Model 85 against burn-out if tube under test is "shorted."

• **7 AND 9 PIN TUBE STRAIGHTENERS** have been included on the front panel to eliminate possibility of damaging tubes with bent or out-of-line pins.

• **AN ULTRA-SENSITIVE CIRCUIT** is used to test for shorts and leakages up to 5 megohms between all tube elements.

Model 85 comes complete, housed in a handsome portable cabinet with slip-on cover. Only.....

\$52.50



Model 77—VACUUM TUBE VOLT-METER. Total Price...\$42.50

Terms: \$12.50 after 10 day trial, then \$6.00 monthly for 5 months if satisfactory. Otherwise return, no explanation necessary.

Superior's New Model 77

VACUUM TUBE VOLTMETER WITH NEW 6" FULL-VIEW METER

Compare it to any peak-to-peak V. T. V. M. made by any other manufacturer at any price!

• Extra large meter scale enables us to print all calibrations in large easy-to-read type.
• Employs a 12AU7 as D. C. amplifier and two 9006's as peak-to-peak voltage rectifiers to assure maximum stability. • Meter is virtually burn-out proof. The sensitive 400

AS A DC VOLTMETER: The Model 77 is indispensable in Hi-Fi Amplifier servicing and a must for Black and White and color TV Receiver servicing where circuit loading cannot be tolerated.

AS AN ELECTRONIC OHMMETER: Because of its wide range of measurement leaky capacitors show up glaringly. Because of its sensitivity and low loading, Intermittents are easily found, isolated and repaired.

AS AN AC VOLTMETER: Measures RMS values if sine wave, and peak-to-peak value if complex wave. Pedestal voltages that determine the "black" level in TV receivers are easily read.

micro-ampere meter is isolated from the measuring circuit by a balanced push-pull amplifier. • Uses selected 1% zero temperature coefficient resistors as multipliers. This assures unchanging accurate readings on all ranges.

SPECIFICATIONS

• DC VOLTS—0 to 3/15/75/150/300/750/1,500 volts at 11 megohms input resistance.
• AC VOLTS (RMS)—0 to 3/15/75/150/300/750/1,500 volts. • AC VOLTS (Peak to Peak)—0 to 8/40/200/400/800/2,000 volts.
• ELECTRONIC OHMMETER—0 to 1,000 ohms/10,000 ohms/100,000 ohms/1 meg-ohm/10 megohms/100 megohms/1,000 meg-ohms. • DECIBELS: -10 db to +18 db, +10 db to +38 db, +30 db to +58 db. All based on 0 db = .006 watts (6 mw) into a 500 ohm line (1.73v). • ZERO CENTER METER—For discriminator alignment with full scale range of 0 to 1.5/7.5/37.5/75/150/375/750 volts at 11 megohms input resistance.

Comes complete with operating instructions, probe leads, and streamlined carrying case. Operates on 110-120 volt 60 cycle Only.....

\$42.50

We invite you to try before you buy any of the models described on this page and the following page. If after a 10 day trial you are completely satisfied and decide to keep the Tester, you need send us only the down payment and agree to pay the balance due at the monthly indicated rate.

NO INTEREST OR FINANCE CHARGES ADDED!

If not completely satisfied, you are privileged to return the Tester to us, cancelling any further obligation.

**SEE OTHER
SIDE**

CUT OUT AND MAIL TODAY! ▶

MOSS ELECTRONIC, INC.

Dept. D-860 3849 Tenth Ave., New York 34, N. Y.

Please send me the units checked an approval. If completely satisfied I will pay on the terms specified with no interest or finance charges added. Otherwise, I will return after a 10 day trial positively cancelling all further obligation.

Model 77 Total Price \$42.50
\$12.50 within 10 days. Balance
\$6.00 monthly for 5 months.

Model TV-50A Total Price \$47.50
\$11.50 within 10 days. Balance
\$6.00 monthly for 6 months.

Model 85 Total Price \$52.50
\$12.50 within 10 days. Balance
\$8.00 monthly for 5 months.

Model 70 Total Price \$15.85
\$3.85 within 10 days. Balance
\$4.00 monthly for 3 months.

Name

Address

City Zone State

All prices net, F.O.B., N. Y. C.

SHIPPED ON APPROVAL NO MONEY WITH ORDER — NO C. O. D.

Superior's New Model 70 UTILITY TESTER®

FOR REPAIRING ALL ELECTRICAL APPLIANCES and AUTOMOBILE CIRCUITS



As an electrical trouble shooter the Model 70:

- Will test Toasters, Irons, Broilers, Heating Pads, Clocks, Fans, Vacuum Cleaners, Refrigerators, Lamps, Fluorescents, Switches, Thermostats, etc.
- Measures A.C. and D.C. Voltages, A.C. and D.C. Current, Resistances, Leakages, etc.
- Will measure current consumption while the appliance under test is in operation.
- Incorporates a sensitive direct-reading resistance range which will measure all resistances commonly used in electrical appliances, motors, etc.
- Leakage detecting circuit will indicate continuously from zero ohms to 5 megohms (5,000,000 ohms).

As an Automotive Tester the Model 70 will test:

- Both 6 Volt and 12 Volt Storage Batteries • Generators • Starters • Distributors • Ignition Coils • Regulators • Relays • Circuit Breakers • Cigarette Lighters • Stop Lights • Condensers • Directional Signal Systems • All Lamps and Bulbs • Fuses • Heating Systems • Horns • Also will locate poor grounds, breaks in wiring, poor connections, etc.

INCLUDED FREE This 64-page book—practically a condensed course in electricity. Learn by doing.



Just read the following partial list of contents: What is electricity? • Simplified version of Ohms Law • What is wattage? • Simplified wattage charts • How to measure voltage, current, resistance and leakage • How to test all electrical appliances and motors using a simplified trouble-shooting technique. • How to trace trouble in the electrical circuits and parts in automobiles and trucks.

Model 70 comes complete with 64 page book and test leads

\$15⁸⁵
Only

Model 70—UTILITY TESTER
Total Price...\$15.85—
Terms: \$3.85 after 10 day trial,
then \$4.00 monthly for 3 months,
if satisfactory. Otherwise return, no
explanation necessary.

Superior's New Model TV-50A GENOMETER

7 Signal Generators in One!

- ✓ R.F. Signal Generator for A.M.
- ✓ R.F. Signal Generator for F.M.
- ✓ Audio Frequency Generator
- ✓ Marker Generator
- ✓ Bar Generator
- ✓ Color Dot Pattern Generator
- ✓ Cross Hatch Generator

This Versatile All-Inclusive GENERATOR Provides ALL the Outputs for Servicing:

- A.M. RADIO • F.M. RADIO • AMPLIFIERS • BLACK AND WHITE TV • COLOR TV

R. F. SIGNAL GENERATOR: 100 Kilo-cycles to 60 Megacycles on fundamentals and from 60 Megacycles to 180 Megacycles on powerful harmonics.

VARIABLE AUDIO FREQUENCY GENERATOR: Provides a variable 300 cycle to 20,000 cycle peaked wave audio signal.

MARKER GENERATOR: The following markers are provided: 189 Kc., 262.5 Kc., 456 Kc., 600 Kc., 1000 Kc., 1400 Kc., 1600 Kc., 2000 Kc., 2500 Kc., 3579 Kc., 4.5 Mc., 5 Mc., 10.7 Mc., (3579 Kc. is the color burst frequency).

BAR GENERATOR: Pattern consists of 4 to 16 horizontal bars or 7 to 20 vertical bars.

DOT PATTERN GENERATOR (FOR COLOR TV): The Dot Pattern projected on any color TV Receiver tube by the Model TV-50A will enable you to adjust for proper color convergence.

CROSS HATCH GENERATOR: The pattern consists of non-shifting horizontal and vertical lines interlaced to provide a stable cross-hatch effect.

Complete with shielded leads

\$47⁵⁰
Net



Model TV50-A—Genometer
Total Price \$47.50
Terms: \$11.50 after 10 day trial,
then \$6.00 monthly for 6 months
if satisfactory. Otherwise return,
no explanation necessary.

TRY FOR 10 DAYS BEFORE you buy! THEN if satisfactory

pay in easy, interest free, monthly payments. See coupon inside.

We invite you to try before you buy any of the models described on this and the preceding page. If after a 10 day trial you are completely satisfied and decide to keep the Tester, you need send us only the down payment and agree to pay the balance due at the monthly indicated rate. (See other side for time payment schedule details.)

**NO INTEREST
OR FINANCE
CHARGES ADDED!**

If not completely satisfied, you are privileged to return the Tester to us, cancelling any further obligation.

**SEE OTHER
SIDE**

CUT OUT AND MAIL TODAY!

FIRST CLASS

Permit No. 61430

New York, N. Y.

VIA AIR MAIL

BUSINESS REPLY CARD

No Postage Stamp Necessary if Mailed in the U. S.

POSTAGE WILL BE PAID BY —

MOSS ELECTRONIC, INC.

3849 TENTH AVENUE

NEW YORK 34, N. Y.