

**BUILD A LOGIC PROBE**

MAY 1997

# Popular Electronics®

## Kirlian Photography

Take exciting electrophotographs without spending lots of money

### Land Warrior


Learn how technology is helping soldiers return home safely

### Build a DC Motor-Speed Controller


Finally, speed adjustment made simple
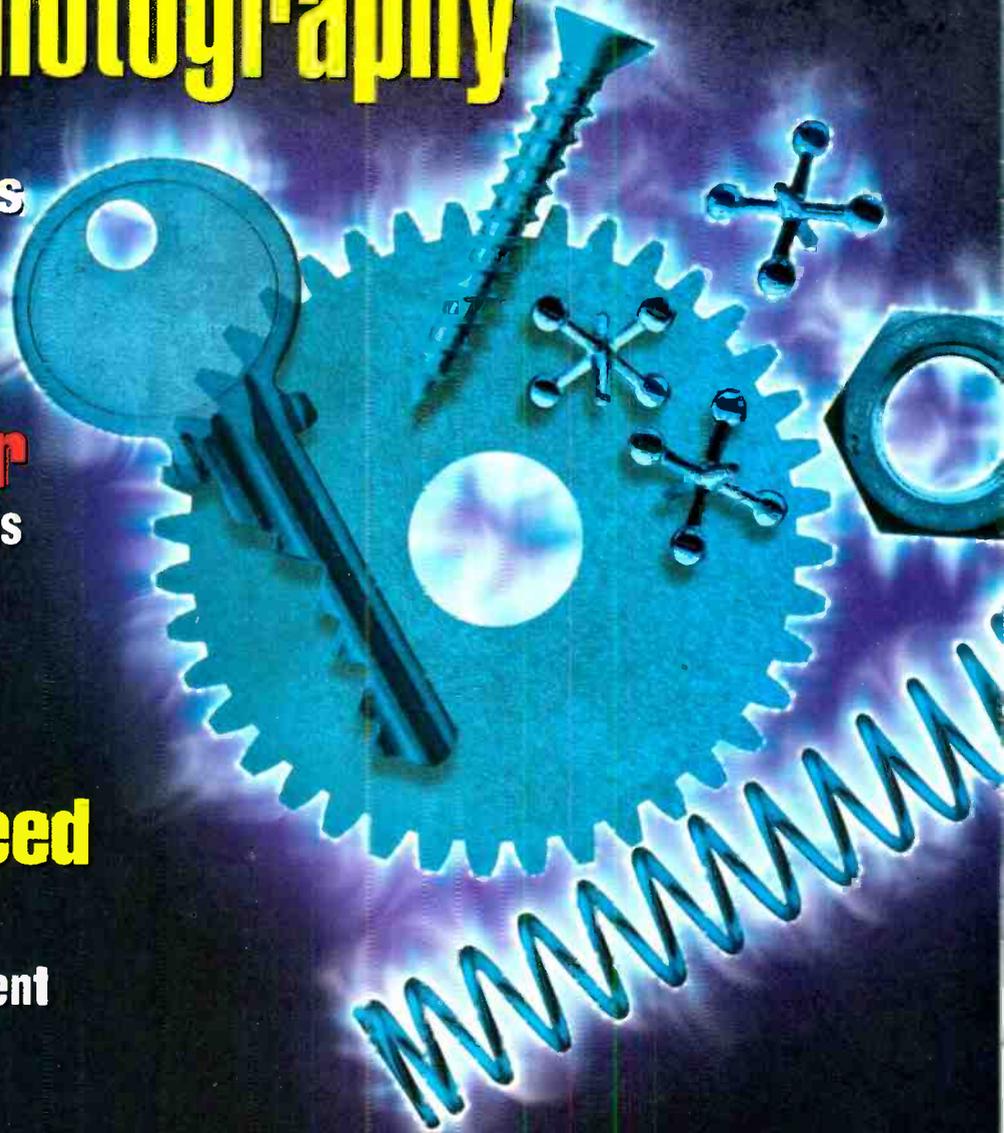
### Build a Duty-Cycle Monitor

Make real-time measurements of a waveform's duty cycle



\$3.99 U.S.  
\$4.50 CAN.

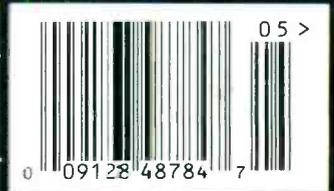


# NEW VERSION!

Electronics Workbench Version 5 with analog, digital and mixed A/D SPICE simulation, a full suite of analyses and over 4,000 devices. Still the standard for power and ease of use. Now ten times faster. Still the same low price.

Join over 75,000 customers and find out why more engineers and hobbyists buy Electronics Workbench than any other SPICE simulator. You'll be working productively in 20 minutes, and creating better designs faster. We guarantee it!

# \$299

**SAME GREAT PRICE!**

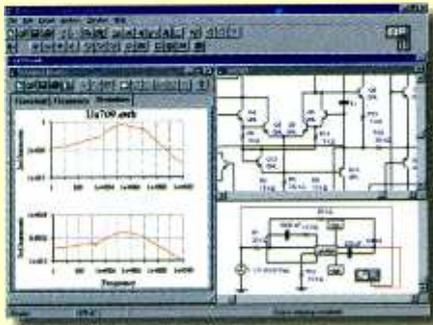

## High-End Features

TRUE MIXED ANALOG/DIGITAL	YES
FULLY INTERACTIVE SIMULATION	YES
ANALOG ENGINE	SPICE 3F5, 32-BIT
DIGITAL ENGINE	NATIVE, 32-BIT
GMIN STEPPING	YES
TEMPERATURE CONTROL	EACH DEVICE
PRO SCHEMATIC EDITOR	YES
HIERARCHICAL CIRCUITS	YES
VIRTUAL INSTRUMENTS	YES
ON-SCREEN GRAPHS	YES
ANALOG COMPONENTS	OVER 100
DIGITAL COMPONENTS	OVER 200
DEVICE MODELS	OVER 4,000
MONEY-BACK GUARANTEE	30-DAY
TECHNICAL SUPPORT	FREE

## Powerful Analyses

DC OPERATING POINT	YES
AC FREQUENCY	YES
TRANSIENT	YES
FOURIER	YES
NOISE	YES
DISTORTION	YES

**30-DAY MONEY-BACK GUARANTEE**  
VERSION 5.0 FOR WINDOWS 95/NT/3.1.  
Upgrades from previous versions \$79.

## FEATURES OF ELECTRONICS WORKBENCH VERSION 5

### WHAT'S NEW

Now 10 times faster. Handles 3 times larger circuits. More and better device models. New thermal modeling. New on-screen graphs. New analyses (Fourier, Noise and Distortion). 25 new components including vacuum tubes, arbitrary sources. 50 new ICs. Improved accuracy. Improved schematic editor with zoom and growing pages. Improved printing. Improved fonts. Improved interface. Redesigned word generator and logic analyzer.

### GENERAL

Integrated Tool: Fully integrated schematic editing, SPICE simulation and waveform generation and analysis. Supports modifications to the circuit during simulation. Circuit analysis through virtual test instrument, or six analyses listed below.  
Simulation Engine: Interactive 32-bit SPICE 3F5 enhanced with native-mode digital and mixed analog/digital support. Automatic insertion of signal translation interface. Supports multiple reuse of hierarchical blocks. GMIN stepping for better convergence. No preset limits on circuit size or complexity.  
Schematic Capture: Click-and-drag interface. Hierarchical work space. Automatic wire routing with automatic reference designation.  
Analysis: Six analyses for quick and simple analysis. Six analyses for on-screen graphs and more (described below).  
Simulation: All design information, including simulation parameters, setup and series of all models stored in a design file to be reused.  
Compatibility: Support standard SPICE models and netlists into reusable Electronics Workbench components. Exports to standard PCB layout packages such as OrCAD, Protel and Tango.

### ANALYSES

DC Operating Point: Calculates DC operating point and reports voltage at each node.  
Transient: Circuit voltages and currents over time of any number of nodes. Specify start and stop times.  
AC Frequency Sweep: Small signal gain and phase over range of AC frequencies at any number of nodes. Specify range, type (decade, octave or linear) and resolution (number of steps) of frequency sweep.  
Fourier: Magnitude and phase of DC and Fourier spectral components of transient response. Specify fundamental frequency and an unlimited number of harmonics.  
Noise: Resistor and semiconductor noise contribution reported as RMS sum. Specify device of interest, output and reference nodes, and range, type and resolution of frequency sweep.  
Distortion: Small signal steady-state harmonic and intermodulation products over a range of frequencies. Specify any number of nodes and sweep range, type and resolution. Optionally exclude devices on an individual basis.

### VIRTUAL TEST INSTRUMENTS

Digital: Models for ICs, Gates and Flip-Flops in HC, LS, CMOS, EPLD, and PAL families. Includes 4008, 4011, 4012, 4013, 4503, 4512, 4516, 41013.

# POWERFUL NEW VERSION!

### MODELS

Digital: Models for ICs, Gates and Flip-Flops in HC, LS, CMOS, EPLD, and PAL families. Includes 4008, 4011, 4012, 4013, 4503, 4512, 4516, 41013.

# Electronics Workbench

VERSION 5

INTERACTIVE IMAGE TECHNOLOGIES LTD., 908 Niagara Falls Boulevard, #068, North Tonawanda, New York 14120-2060/Telephone 416-977-5550  
TRADEMARKS ARE PROPERTY OF THEIR RESPECTIVE HOLDERS. OFFER IS IN U.S. DOLLARS AND VALID ONLY IN THE UNITED STATES AND CANADA. ALL ORDERS SUBJECT TO \$13 SHIPPING AND HANDLING CHARGE.

CALL 800-263-5552

Fax: 416-977-1818 Internet: <http://www.interactiv.com> CompuServe: 71333,3435/BBS: 416-977-3540/E-mail: [ewb@interactiv.com](mailto:ewb@interactiv.com)  
CIRCLE 13 ON FREE INFORMATION CARD

## COVER STORY

### 33 Poor Man's Kirlian Photography

You can now take electrophotographs using fax machine paper in a rather unorthodox fashion, thereby eliminating the need for film developing—*Nick Cinquino*

## CONSTRUCTION

### 40 Build a Logic Probe

With just a couple of chips and a handful of support components, you can assemble one of the most useful test instruments in digital electronics—*Carl J. Bergquist*

### 45 Build a Duty-Cycle Monitor

Using a few simple, easy-to-get components, you can assemble this useful little monitor, and save your oscilloscope or frequency counter for some other task—*Skip Campisi*

### 56 Build a DC Motor Speed Controller

This easy-to-build circuit allows you to control the rotational speed of a DC motor without wasting any of the input power—*Marc Spiwak*

## FEATURES

### 43 Land Warrior

Learn about how present and emerging technologies are helping to ensure that our foot soldiers will return home from their missions around the world—*Bill Siuru*

### 48 Electronics Technician's Day


In recognition of the skilled electronics technicians of the world, who keep our increasingly electronic dependent world humming right all, the Society of Certified Electronics Technicians has proclaimed April 22, 1997 International Electronics Technician's Day—*Barbara Rubin*  
(Turn page)



Page 33



Page 43

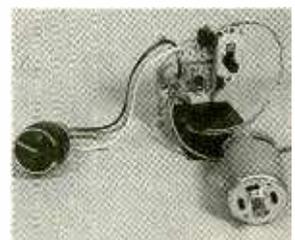

Page 56

POPULAR ELECTRONICS (ISSN 1042-170-X) Published monthly by Gernsback Publications, Inc. 500 Bi-County Boulevard, Farmingdale, NY 11735. Second-Class postage paid at Farmingdale, NY and at additional mailing offices. One-year, twelve issues, subscription rate U.S. and possessions \$21.95, Canada \$28.84 (includes G.S.T. Canadian Goods and Services Tax Registration No. R125166280), all other countries \$29.45. Subscription orders payable in U.S. funds only. International Postal Money Order or check drawn on a U.S. bank. U.S. single copy price \$3.50. Copyright 1997 by Gernsback Publications, Inc. All rights reserved. Hands-on Electronics and Gizmo trademarks are registered in U.S. and Canada by Gernsback Publications, Inc. Popular Electronics trademark is registered in U.S. and Canada by Electronics Technology Today, Inc. and is licensed to Gernsback Publications, Inc. Printed in U.S.A.

Postmaster: Please send address changes to Popular Electronics, Subscription Dept., P.O. Box 338, Mount Morris, IL 61054-9932

A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

As a service to readers, Popular Electronics publishes available plans or information relating to newsworthy products, techniques, and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, Popular Electronics disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this magazine.

PRODUCT REVIEWS

**23 Gizmo**

CPR Prompt Home Learning System, CPR Prompt Rescue and Practice Aid Model CPR 100, Force X Force-Feedback Joystick, The 1997 Consumer Electronics Show, and much more!

COLUMNS

**8 Multimedia Watch**

The PC-TV Merger—*Marc Spiwak*

**12 Net Watch**

Pay Channels Online—*Dan Karagiannis*

**59 Ham Radio**

Going for Gigahertz—*Joseph J. Carr*

**61 Circuit Circus**

Junkbox Goodies—*Charles D. Rakes*

**64 Computer Bits**

Completing Your Greatest Hits Page—*Jeff Holtzman*

**65 DX Listening**

Listening From Another Locale—*Don Jensen*

**67 Think Tank**

Another Winner—*John Yacono*

**71 Antique Radio**

Mailbag Time—*Marc Ellis*

**73 Scanner Scene**

Variety is the Spice of Scanning—*Marc Saxon*

DEPARTMENTS

**4 Editorial**

**6 Letters**

**19 New Products**

**22 Electronics Library**

**75 Popular Electronics Market Center**

**110 Advertiser's Index**

**TIA Free Information Card**

**Larry Steckler**, EHF, CET  
editor-in-chief and publisher

EDITORIAL DEPARTMENT

**Dan Karagiannis**, managing editor

**Teri Scaduto**, assistant editor

**Evelyn Rose**, editorial assistant

**Joseph J. Carr, K4IPV**,  
contributing editor

**Marc Ellis**, contributing editor

**Jeffrey K. Holtzman**,  
contributing editor

**Don Jensen**, contributing editor

**Charles D. Rakes**,  
contributing editor

**Marc Saxon**, contributing editor

**Marc Spiwak**, contributing editor

**John Yacono**, contributing editor

PRODUCTION DEPARTMENT

**Ruby M. Yee**, production director

**Ken Coren**,  
desktop production director

**Lisa Baynon**, desktop production

**Kathy Campbell**,  
production assistant

ART DEPARTMENT

**Andre Duzant**, art director

**Russell C. Truelson**, illustrator

CIRCULATION DEPARTMENT

**Theresa Lombardo**

circulation manager

**Gina L. Gallo**

circulation assistant

**Michele Torriolo**,

POPULAR ELECTRONICS bookstore

BUSINESS AND EDITORIAL  
OFFICES

Gernsback Publications, Inc.

500 Bi-County Blvd.

Farmingdale, NY 11735

1-516-293-3000

FAX: 1-516-293-3115

President: **Larry Steckler**

SUBSCRIPTION  
CUSTOMER SERVICE/  
ORDER ENTRY

1-800-827-0383

7:30 AM - 8:30 PM EST

Advertising Sales Offices  
listed on page 110

Composition by Mates Graphics

Cover by Loawy Design

Cover illustration by Chris Gould



Since some of the equipment and circuitry described in POPULAR ELECTRONICS may relate to or be covered by U.S. patents, POPULAR ELECTRONICS disclaims any liability for the infringement of such patents by the making, using, or selling of such equipment or circuitry, and suggests that anyone interested in such projects consult a patent attorney.

# How to make your car invisible to radar and laser...legally!

Rocky Mountain Radar introduces a device guaranteed to make your car electronically "invisible" to speed traps—if you get a ticket while using the product, the manufacturer will pay your fine!

by Phil Jones



**The Phazer will "jam" both radar and laser guns, preventing police from measuring your speed.**


If your heart doesn't skip a beat when you drive past a speed trap—even if you aren't speeding—don't bother reading this. I can't tell you how many times that has happened to me. Driving down the interstate with my cruise control set at eight miles over the limit, I catch a glimpse of a police car parked on the side of the road. My heart skips a beat and for some reason I look at my speedometer. After I have passed the trap, my eyes stay glued to my rear view mirror, praying the police officer will pass me up for a "bigger fish."

It seems that as speed-detection technology has gotten more and more advanced, speeding tickets have become virtually unavoidable. And although devices exist that enable motorists to detect these speed traps, they are outlawed in many states... including mine.

**The solution.** Today, Rocky Mountain Radar offers drivers like me a perfect solution—the Phazer. Combining a passive radar scrambler with an active laser scrambler, the Phazer makes your automobile electronically "invisible" to police speed-detecting equipment.

The radar component works by mixing an X, K or Ka radar signal with an FM "chirp" and bouncing it back at the squad car by way of a

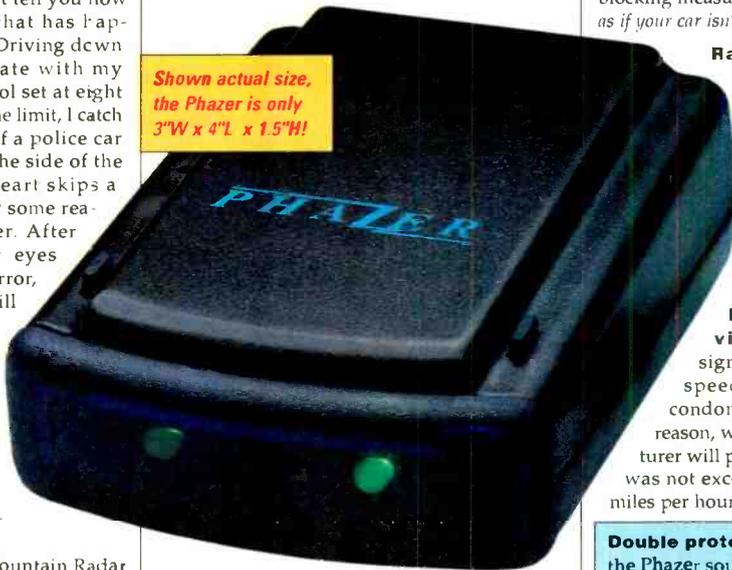waveguide antenna, effectively confusing the computer inside the radar gun. The laser component transmits an infrared beam that has the same effect on laser Lidar units.



Shown actual size, the Phazer is only 3"W x 4"L x 1.5"H!

**Perfectly legal.** Some radar devices have been outlawed because they transmit scrambling radar beams back to the waiting law enforcement vehicle. The Phazer, however, reflects a portion of the signal plus an added FM signal back to the police car. This, in effect, gives the waiting radar unit an electronic "lobotomy."

Best of all, unless you are a resident of Minnesota, Oklahoma or Washington, D.C., using the Phazer is completely within your legal rights.



**The Phazer makes your car invisible to police radar and lasers or the manufacturer will pay your speeding ticket!**

**How it scrambles radar.**

Police radar takes five to 10 measurements of a vehicle's speed in about one second. The Phazer sends one signal that tells the radar the car is going 15 m.p.h. and another signal that the car is going 312 m.p.h. Because police radar can't verify the speed, it displays no speed at all. To the radar gun, your car isn't even on the road.

**Works with laser, too!** The Phazer also protects your vehicle from Lidar guns that use the change in distance over time to detect a vehicle's speed. The Phazer uses light-emitting diodes (LEDs) to fire invisible infrared pulses through the windshield. Laser guns interpret those pulses as a false indication of the car's distance, blocking measurement of your speed. Again, it's as if your car isn't even on the road.

**Range up to three miles.**

The Phazer begins to scramble both radar and laser signals as far as three miles away from the speed trap. Its range of effectiveness extends to almost 100 feet away from the police car, at which point you should be able to make visual contact and reduce your speed accordingly.

**Encourage responsible driving.**

While the Phazer is designed to help you (and me) avoid speed traps, it is *not* intended to condone excessive speeding. For that reason, within the first year, the manufacturer will pay tickets where the speed limit was not exceeded by more than 30%, or 15 miles per hour, whichever is less.

**Double protection from speed traps.**

If the Phazer sounds good, but you prefer to be notified when you are in range of a police radar, the Phantom is for you. The Phantom combines the Phazer (including the Ticket Rebate Program) with a radar detector. It's legal in every state except Minnesota, Oklahoma, Virginia and Washington, D.C. Ask your representative for more details!




4"W x 4"L x 1.5"H

**Risk-free.** Thanks to Rocky Mountain Radar, speed traps don't make my heart skip a beat anymore. Try the Phazer or the Phantom yourself. They're both backed by our risk-free trial and three-year manufacturer's warranty. If you're not satisfied, return them within 90 days for a full "No Questions Asked" refund.

**The Phazer** ..... \$199 \$14 S&H  
**The Phantom** ..... \$349 \$18 S&H  
 Please mention promotional code 1906-10517.

For fastest service call toll-free 24 hours a day  
**800-399-7863**

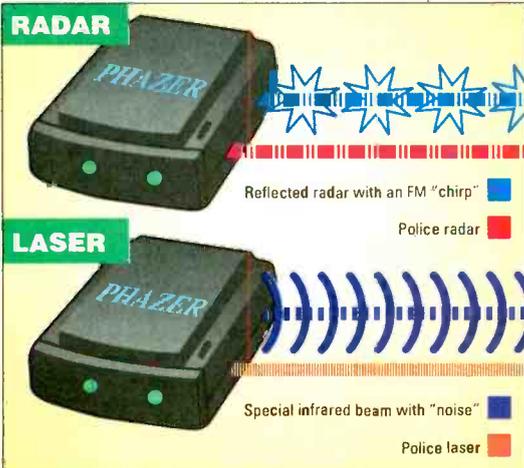**comtradindustries**  
 2820 Waterford Lake Drive, Suite 102 Midlothian, VA 23113



**HOW TO MAKE YOUR CAR DISAPPEAR**

Radar and laser scramblers are devices that foil speed traps by making vehicles electronically "invisible" to police radar. Radar scramblers mix a portion of the radar signal with background clutter and reflect it back to the squad car. This technique, pioneered by Rocky Mountain Radar, creates an unreadable signal that confuses the computer inside the radar gun.

The laser scrambler in the Phazer works in a similar manner. It transmits a special infrared beam with information designed to scramble the laser signal. The result? Readouts on police radar and laser guns remain blank. As far as the police officer is concerned, your vehicle is not even on the road.

# EARN YOUR B.S. DEGREE IN COMPUTERS OR ELECTRONICS



## By Studying at Home

Grantham College of Engineering, now in our 47th year, is highly experienced in "distance education" – teaching by correspondence – through printed materials, computer materials, fax, modem, and phone.

No commuting to class. Study at your own pace, while continuing on your present job. Learn from easy-to-understand but complete and thorough lesson materials, with additional help from our instructors.

Grantham offers three separate distance-education programs, leading to the following accredited degrees;

(1) The B.S.E.T. with Major Emphasis in Electronics. (2) The B.S.E.T. with Major Emphasis in Computers. (3) The B.S.C.S. – the Bachelor of Science in Computer Science.

**The B.S.E.T. programs now include Electronics Workbench Professional 5.0.**

An important part of being prepared to *move up* is holding the right college degree, and the absolutely necessary part is knowing your field. Grantham can help you both ways – to learn more and to earn your degree in the process.

Write or phone for our free catalog. Toll free, 1-800-955-2527, or see mailing address below.

Accredited by  
the Accrediting Commission of the  
Distance Education and  
Training Council

**GRANTHAM**  
**College of Engineering**  
Grantham College Road  
Slidell, LA 70460

# Editorial

## The Fun Is In Working

This great computer age in which we are now living is not so great after all. What was once lots of fun is rapidly diminishing. By the time I became a DOS expert, in came Windows. Even Windows had a rebirth—Windows 95. Windows 97 is now in the wings. Of course the Internet opened vast new spaces to enlighten me and offer practically unlimited knowledge. But I've got to be honest with you. I've given up cigarettes. Gone are regular coffee and colas; and so is the keyboard and mouse. I was addicted to both of them!

That's what makes Popular Electronics so valuable to me. I burned a hole in my pants last week with hot solder. I scraped skin cutting a chassis box to size. I snaked a coaxial cable through the walls of my house. I spent hours thumbing catalogs and magazines looking for a supplier for some CMOS chips. I spent over sixty dollars to build a project that sells for forty dollars. I am alive again and very happy!

The hams can tell a similar story. They would build most of their equipment many years ago. Then came cheap, quality communication appliances and that equipment changed the entire hobby. Hamdom is reverting somewhat. Amateur TV is still a build-it group that looks down on appliances. The flea-power QRP group likes to build some gear. The hams are finding the workbench again and enjoying it.

So it will be for everyone when all the homes in the North American continent have two or three computers with network ties. What will be new and what will be exciting? You may have guessed it. The excitement will be in building and applying electronics for a new generation of projects. Using your brains and handicraft can be rewarding and a lot of fun. That's why going to work every weekday is a fun-filled adventure, and I wouldn't miss it for the world!


Julian S. Martin  
Working Editor

# Your Ultimate Source!

For Quality Electronic Components

Internet Access...

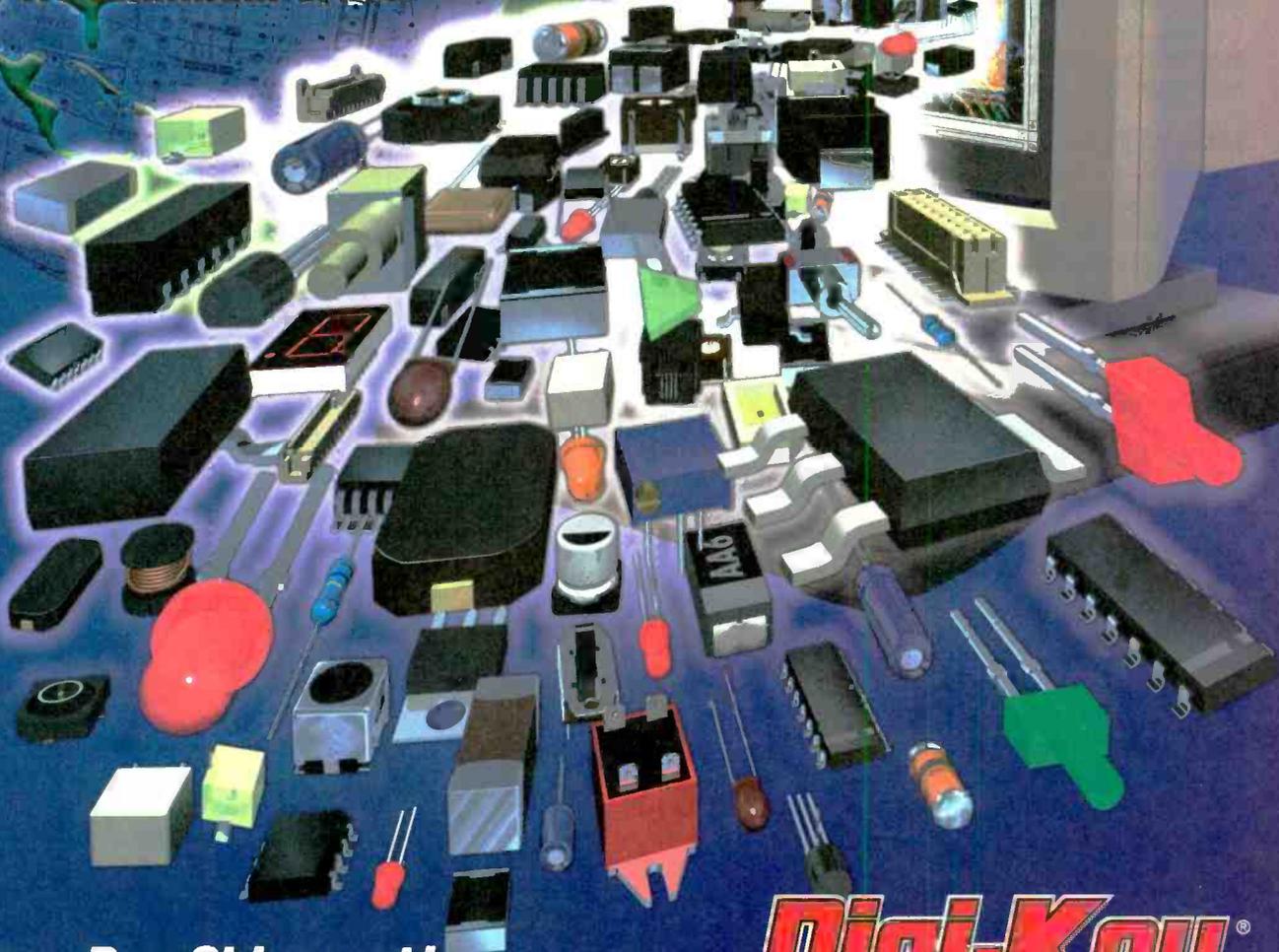- 24 hours-a-day, 7 days-a-week!
- Online ordering & stock status!
- Fast, efficient parts search!
- No minimum order!



**Same-Day Shipment!**

on orders entered by 5:00pm central (M-F)

**Digi-Key®**

[www.digikey.com/cx](http://www.digikey.com/cx)



# LETTERS

## Decoding the Decode

### A CORRECTION

I have some corrections to make to the schematic of my Infrared Decoder article, which appeared in the February 1997 issue of **Popular Electronics**.

For starters, pin 11 of the 8031 must be connected to pin 11 of the MAX232. Also, C5 and C10 are reversed; in other words, they are showing the wrong polarity in the schematic.

The Parts List calls out a 27256 EPROM; the schematic is wired for a 2764. A 27256 can be used if pins 26 and 27 are connected to ground.

Sorry for any inconvenience this may have caused you.

—Stuart R. Ball

### MUSIC FOR PLEASURE

Thanks so much for publishing the 22-Watt Amplifier in your February issue. I built two right away and got them to work in my Jeep on the first try.

What a sound! I tested it with a tape of my favorite band, The Damned, and cranked it up really loud. I'm sure my neighbors heard it in their living rooms.

Please keep publishing such useful projects in the future. How about a graphic equalizer?

D.V.

Los Angeles, CA

*Thanks for writing. We appreciate your happiness with our cover story. As for your suggestion, we'd love to publish a graphic equalizer. However, as with most of our stories, they are generated out of house. That basically means we can only publish it if someone out there designs it and writes it up.*

*Any takers?*

—Editor

### PAGER DECODER PRAISE

I just got my March issue of **Popular Electronics** and I have to say I'm impressed. The cover story, which shows you how to build an alphanumeric pager decoder, is amazing!

Innovative stories like this are the reason that I got into electronics in the first place. I'm looking forward to building my own unit and getting it up and running.

I was also glad to notice that files are being posted to the Gernsback FTP site now. It looks like the bell is finally tolling for BBSes, which add up long-distance bills quite fast.

B.R.

Philadelphia, PA

*We're glad you like the story. And to be honest with you, I agree about the phone bills incurred through BBSing. Before the days of the Internet I received quite a few shocking bills myself!*

—Editor

### MS-TRAP

I bought a new computer. It's a P-166 because I wanted the price to be reasonable, but I did get all the bells and whistles. It came loaded with Windows 95 and the OEM CD disk was provided. I figured to load my old computer with Windows 95 in place of the old Windows, but to no avail. Microsoft locked me out! What do I do?

J.J.

Sparks, NV

*Oh, boy! Did you read the license agreement before you unpacked the Windows 95 packet? I believe you*

### KEEP IN TOUCH

Now there are more ways than ever to contact us at **Popular Electronics**.

You can write to:

*Letters*

**Popular Electronics**

500 BI-County Blvd.

Farmingdale, NY 11735

Or you can send e-mail to:

[peeditor@gernsback.com](mailto:peeditor@gernsback.com)

And don't forget to visit to our Web site at:

<http://www.gernsback.com>

*cannot load a second computer; one is the limit. I could be wrong. I imagine that a single user may load two or more machines provided only that person use those computers. Does anyone know?*

*If the MS answer is yes to my question, the best thing to do is reformat the C drive and load everything again. Be sure you got MS-DOS handy and the CD-ROM drive disk available. Be sure to save your old files.*

### HELP

Does anyone out there know of a good Pinochle program? Also, what is the best Bridge game program you ever used? Please drop a note to the Editor. Thank you.

### HAVES AND NEEDS

I'm looking for PC boards for a Tripp Lite battery backup unit, model number SB/BC 2000 LAN. The PC board numbers are 16-942, 16-891, 16-895, and 16-893M.

Thank you in advance for your time and any help your readers could provide.

Marc De Loach

P.O. Box 107

Hewitt, NJ 07421

I recently saw a band called Bell, Book & Candle in concert and the singer was playing a strange instrument I later learned was a Theremin. Does anyone out there know of any clubs or organizations that offer information on this strange instrument?

I'd like to find out what different types of Theremins there are, and if any are commercially available. I know that *Electronics Now* recently ran an article on one, but I'm new to electronics and I don't think I'd like to try building such an obviously sensitive device just yet.

Can anyone out there help me? I'd really appreciate any help you can give me. Thanks.


Dave V. Ania

P.O. Box 86

Lindenhurst, NY 11757

**Study at home with the**

# **Electronics Technician CD-ROM**

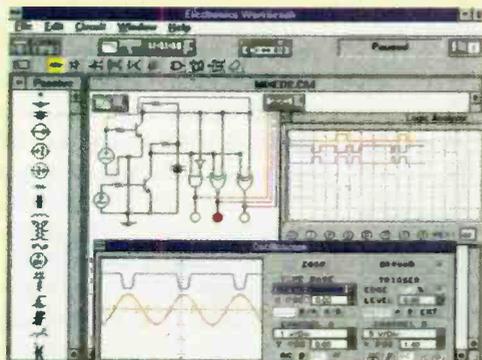

## **The only product of its kind**

This unique CD-ROM based learning program includes 23 courses which are equivalent to a two-year Electronics Technician program and is recognized as the standard for Certified Electronics Technician programs across North America.

## **Purchase the CD-ROM separately or earn College credits.**

The choice is yours. Buy the CD-ROM and use it as the ultimate electronics reference tool to refresh your knowledge of electronics, or enroll in the program and earn College credits. The course material is delivered using video, text, 2-D and 3-D animations color photos, audio, and over 450 laboratory projects. Use the CD-ROM in the home, office, or shop as a troubleshooting/design tool and reference guide.

## **Industry Recognition**

The course content for the CD-ROM was developed in association with some of the top corporate trainers in North America, and focuses on practical applications and troubleshooting techniques.

## **Best Price**

The CD-ROM costs \$249 and comes with **ElectronicsWorkbench** the laboratory software simulation package. Complete all 23 courses on the CD-ROM and receive certification as an Electronics Technician. The total tuition for the 23 courses is \$1150, and includes computer-based tests, tutorial support via 1-800 numbers and the internet.

## **Public Sector Standards**

The CD-ROM was designed by George Brown College, one of the largest and most innovative community colleges in North America. Graduates of the program can continue their studies towards an undergraduate degree through the Minnesota State University (Bemidji) distance education program.

## **Easy at-home learning**

All you need is the CD-ROM, no expensive books or lab equipment is required. Complete each course at your own pace, schedule the time that's best for you and decide how quickly you complete each course. The typical completion time is 48 weeks of part-time study, but there are no time limits.

## **Call now!**

Call our 24-hour toll-free hotline and find out more about the Electronics Technician CD-ROM or the distance education program.

**1-888-553-5333**

# MULTIMEDIA WATCH

## The PC-TV Merger

BY MARC SPIWAK  
TECHNICAL EDITOR  
WINDOWS MAGAZINE

People keep talking about the merger between PCs and home entertainment systems, when in fact it has already happened. With a push from Microsoft, PC manufacturers are equipping computer systems with hardware that makes the merge possible. PC TV tuners have been available for years, and systems are starting to ship with them. These are basically just video-capture cards with built-in TV

game playing. Pretty soon most graphics accelerators will have a TV output. I've been playing with a lot of very affordable video conferencing packages. You can buy them with or without a video camera, because you can use a camcorder if you have one. Video-conferencing kits that include a color camera already sell for under \$500. New transmission standards let you video conference with people on the Internet

ally as good as NTSC, a format we're on the verge of abandoning. Yes, the hardware merger has already taken place. But the change we're really waiting for will take place very soon.

An agreement has recently been reached regarding an HDTV signal standard for the United States. This is the high-resolution, wide-screen picture we've all been waiting for. HDTV sets will be out before you know it, and wide-screen monitors are already available for both PCs and home video systems. The last missing link is DVD, which is the storage solution for high-definition video. Once DVD player/recorders are a standard item, the final "marriage" between the TV and the PC will have taken place. You'll then be able to record and play the same discs on either system. But you'll still want to have two separate systems. One with a 17- to 20-inch display that's easy on the eyes when used close-up, and another with a big, wide-screen display to watch movies on.

### ANOTHER FORM OF PC

I recently saw a demonstration of Xybernaut's Mobile Assistant II. This is basically notebook-computer hardware rearranged so that you can wear it. It's a voice-activated, 75-MHz belt-worn Pentium with a head-mounted display that is suspended in front of one eye only. The whole system weighs only a few pounds and costs around \$7995.

Understand, however, that this is not your next PC. Rather, this is intended for remote technicians who need to access data while keeping their hands free. For example, an airplane mechanic might need to access blueprints or schematics to complete a repair. A front-line medic might need to look up someone's medical files or other critical data before administering treatment. I imagine that in time, we'll see an entire computer built into a pair of glasses.

### SOME NEAT ACCESSORIES

I recently received some very useful



*The Mobile Assistant II is a voice-activated Pentium system that you wear.*

tuners. They usually accept an NTSC, PAL, SECAM, or S- video input, and convert the signal into one you can watch in a window on your PC. Software lets you capture still images, video clips, closed-captioned text, and more. I have a TV tuner card made by Philips that includes an infrared remote control.

We're even starting to see merged hardware packages on the market. Gateway 2000's Destination system is essentially a PC with a built-in TV tuner and a hybrid monitor that's good for both PC and video use. TV Internet boxes have also hit the scene, for web-surfing without a PC.

More recently, graphics accelerators have started to include a TV output, which lets you connect your computer to your big-screen TV for enhanced

who have similar hardware. But these hardware packages are really just another variation of video-capture. In reality, the hardware necessary for the PC-TV merger to take place has been around for quite some time. It's the computers that have finally caught up to the task at hand.

Today's PC also ships with a multi-gigabyte hard drive, so it's essentially the equivalent of a digital VCR. You can't really store all that much video on one of these hard drives, but at least you have plenty of editing room. But a hardware or software MPEG encoder, along with a CD-R drive, lets you put your own edited movies on CD.

The main reason for not wanting to dive into this right now is that the picture quality on a PC (MPEG-1 or some other compression scheme) isn't usu-

# Take This Giant Circuit Library For Only \$14.95

when you join the  
**Electronics Engineers' Book Club®**

Hundreds of circuit ideas  
alphabetically arranged—from  
Alarm circuits to Zero  
crossing detector circuits!

"...includes schematics for the latest electronics  
circuits from industry leaders..."—Popular Electronics

Turn to this comprehensive circuit library for hundreds of project ideas...and concise pinout diagrams and schematics. In each volume you'll find more than 700 electronic and integrated circuits and 100+ circuit categories right at your fingertips to give you ideas you can use on the job or at your workbench.

If coupon is missing, write to: **Electronics Engineers' Book Club®** A Division of The McGraw-Hill Companies P.O. Box 549, Blacklick, OH 43004-9918

## The Encyclopedia of Electronic Circuits Volumes 1-4

by Rudolf F. Graf



### As a member of the Electronics Engineers' Book Club...

you'll enjoy receiving Club bulletins every 3-4 weeks containing exciting offers on the latest books in the field at savings of up to 50% off the regular publishers' prices. If you want the Main Selection, do nothing and it will be shipped automatically. If you want another book, or no book at all, simply return the reply form to us by the date specified. You'll have at least 10 days to decide. If you ever receive a book you don't want due to late delivery of the bulletin, you can return it at our expense. Your only obligation is to purchase 3 more books during the next 2 years, after which you may cancel your membership at any time. And you'll be eligible for FREE BOOKS through our Bonus Book Program. Publishers' Prices Shown © 1997 EEBC

## **ELECTRONICS ENGINEERS'** BOOK CLUB®

A Division of The McGraw-Hill Companies, P.O. Box 549, Blacklick, OH 43004-9918

**YES!** Please send me *The Encyclopedia of Electronic Circuits-Vols. 1-4* (5861488), billing me just \$14.95, plus shipping/handling & tax. Enroll me as a member of the **Electronics Engineers' Book Club** according to the terms outlined in this ad. If not satisfied, I may return the books without obligation and have my membership cancelled.

Name \_\_\_\_\_


Address/Apt.# \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_

Zip \_\_\_\_\_ Phone \_\_\_\_\_

Valid for new members only, subject to acceptance by EEBC. Canada must remit in U.S. funds drawn on U.S. banks. Applicants outside the U.S. and Canada will receive special ordering instructions. A shipping/handling charge & sales tax will be added to all orders.

PIIF597

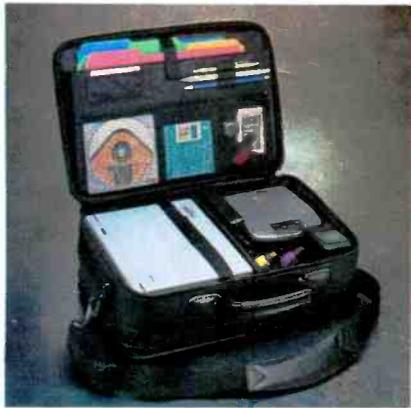

The NC-3 Commuter Notebook Computer Case is a pleasure to travel with.

computer accessories from Case Logic. For \$69.95, the NC-3 Commuter Notebook Computer Case is a great bag to travel with. It's rugged and water-repellent. (I also have a beautiful leather notebook bag that's a bit too nice to jam under an airplane seat, and it doesn't like to be rained on.) The padded nylon NC-3 has plenty of room for a notebook computer and all of its accessories, with adjustable straps and barriers to hold everything in place. It also has all of the nooks and crannies you'd expect in a briefcase, and then some. Zippered interior mesh pockets let you see what's in them, and there's a pouch for a cellular phone. There's a ticket pocket, pen loops, and a key ring. Pleated compartments can hold plenty of files, magazines, or whatever. I've traveled with this bag, and it was a pleasure.

I also received some more unusual product samples that I didn't know I needed until I saw them. Among various CD-carriers, including padded pouches of different sizes, there's a CDV-12 CD Visor that mounts on your car's sun visor. For \$9.95 it puts 12 discs without the jewel boxes easily in reach while driving, and there's also a mesh pocket and pen loop. I particularly like using the Gel-eez Wrist Rest mouse pad. I tend to lean on my hand when I'm using my mouse, and the Gel-eez has a gel-filled cushion that makes it a lot more comfortable. Also useful are the Cable Ties, which sell for \$2.99 a six-pack. These Velcro straps quickly wrap around and tame wires for storage in a closet or travel bag.

## NEW STUFF

Solar System Explorer is the latest product from Maris Multimedia. This neat title lets you explore our solar system from the pilot's seat of the Explorer, mankind's most advanced spacecraft-in the year 2019, that is. You can fly to any planet, experience atmospheric storms on Jupiter, see what the Magellan space probe saw when it orbited Venus, and a whole lot more. You're the pilot, researcher, and scientist, so it's up to you to plot interplanetary courses, fly famous missions, launch probes, and basically run the show. There's a huge scientific database for you to access whenever necessary, panoramic views, relief

## WHERE TO GET IT

**Case Logic, Inc.**  
6303 Dry Creek Parkway  
Longmont, CO 80503  
<http://www.casellogic.com>

**CIRCLE 60 ON FREE INFORMATION CARD**

**Discovery Channel Multimedia**  
7700 Wisconsin Avenue  
Bethesda, MD 20814  
<http://multimedia.discovery.com>

**CIRCLE 65 ON FREE INFORMATION CARD**

**Maris Multimedia**  
4040 Civic Center Drive, Suite 200  
San Rafael, CA 94903  
<http://www.maris.com>

**CIRCLE 61 ON FREE INFORMATION CARD**

**Mattel Media**  
333 Continental Blvd.  
El Segundo, CA 90245  
<http://www.mattel.com>

**CIRCLE 62 ON FREE INFORMATION CARD**

**The Voyager Company**  
578 Broadway, Suite 406  
New York, NY 10012  
<http://www.voyagerco.com>

**CIRCLE 63 ON FREE INFORMATION CARD**


**Xybernaut Corporation**  
12701 Fair Lakes Circle, Suite 550  
Fairfax, VA 22033  
<http://www.xybernaut.com>

**CIRCLE 64 ON FREE INFORMATION CARD**

maps, 3D models, and so on. Virtual reality finally puts the planets within reach of the average couch potato. You can set your sights on the planets with Solar System Explorer for \$45.95.

New from The Voyager Company comes Sound Toys, a very bizarre multimedia title that lets you compose and record your own unique music. You don't have to be a musician to play it either-the program translates intuitive visual gestures into music. There are over three hundred original samples including harmonica, wooden flute, bells, marimba, drums, and acoustic and electric guitar. You can create endless combinations of loops and solos by sliding and clicking the mouse. But, as warned on the CD case, this game can soak up a lot of your time if you really get into it. If you play it at work, your productivity will suffer. Sound Toys has a suggested retail price of \$19.95.

If you've ever dreamed about freely

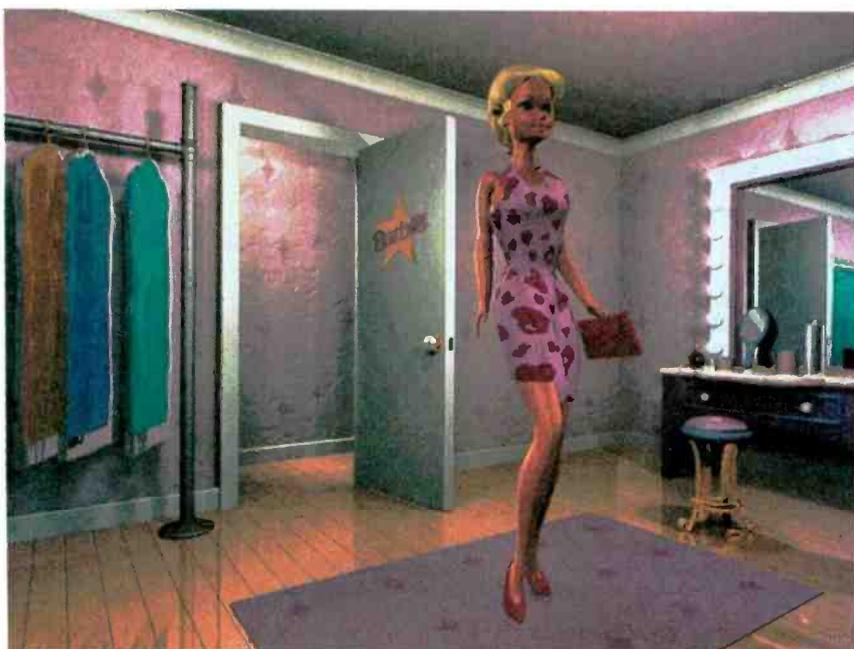

roaming around a 95,000 ton nuclear-powered aircraft carrier, then Discovery Channel Multimedia's Carrier: Fortress At Sea is a title you'll be interested in. You get a pass from the captain for an unescorted tour of the ship. You can explore every crevice of a 3D model of the USS Carl Vinson, the vessel which led the U.S. battle group in the Operation Desert Strike missile launch against Iraq. 85 video locations let you meet the virtual crew of this floating city, and there's also a comprehensive database of carrier facts and statistics and briefings on carrier history. Once you feel comfortable on board the ship, you can take the controls of an F-14 Tomcat and land it on the flight deck if you're skilled enough. This title has an estimated street price of \$40.


Also new this month from Discovery Channel Multimedia for kids ages 9 and up is Animal Planet, a new CD-ROM that's much more than an animal encyclopedia. It features stunning graphics and in-depth information on more than 1,100 animals. Beautiful 3-D vistas range from mountain tops to the ocean depths to the frozen polar regions. Animal Planet also offers instant access

to the World Wide Web with its Bio Web feature, a direct link to over 1,000 animal websites on the Internet. Updated quarterly, the Bio Web offers plenty of information-rich websites, ranging from official museum, aquarium, and zoo sites to those written by veterinarians. A short description of each site is provided as well as a rating.

Many of the toy companies we remember from childhood are still around today in a big way, and multimedia is the new name of the game. I have a bunch of new titles from Mattel Media. Mother Goose's Farm 4 Learning teaches kids ages 3 to 6 arithmetic, reading, rhythm, rhyming, and more. With four separate discs, there's enough here to keep kids busy for months.

Mattel is also on track to produce lots of software intended for girls, and to start off with there's a bunch of Barbie titles. Barbie is celebrating her 37th anniversary, and it makes sense that girls would be interested in Barbie software. Barbie Fashion Designer lets girls create original fashion designs that their Barbie dolls can actually wear. Patterns can be printed on printer-compatible

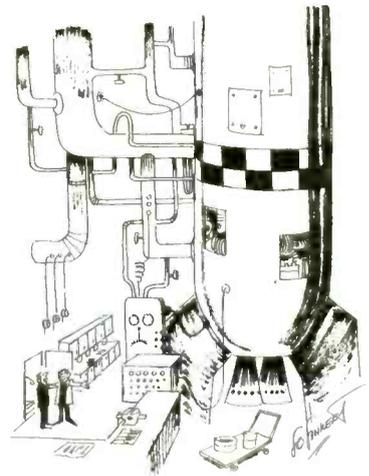
fabric. No sewing is required. Barbie Storymaker lets girls create their own Barbie movies using different locations, scenery, sound effects, and characters. Barbie Print 'n Play lets girls produce their own custom stationary, calendars, and stickers. Of course boys are welcome to play with the software, too—they probably just won't tell their friends about it. ■



"Bob, you have a lovely hobby-room!"


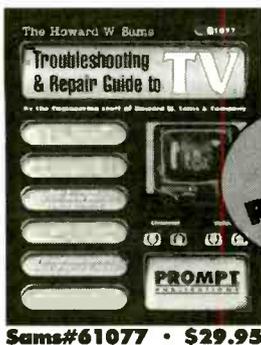
# Proven Products at Popular Prices

From schematics to technical books,  
Howard W. Sams can supply the information  
you need to get the repair job done.



**TV  
Repair**

Sams#61077 • \$29.95

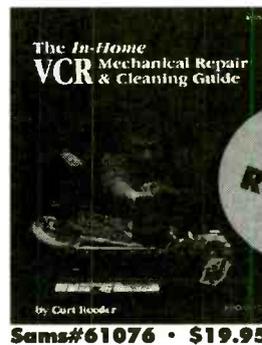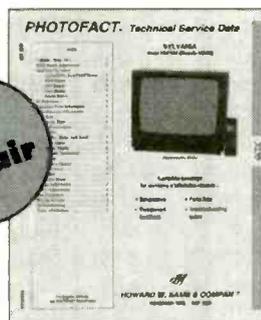

**VCR  
Repair**

Sams#61076 • \$19.95



Call today for your  
**FREE book catalog.**

**800-428-7267**  
Howard W. Sams  
**www.hwsams.com**

CIRCLE 176 ON FREE INFORMATION CARD

# NET WATCH

## Pay Channels Online

BY DAN KARAGIANNIS

Whether you have cable or digital-satellite television, you're paying for programming. As you probably know, having dozens of channels to choose from can be both fun and frustrating, but always better than using "rabbit ears" to tune in a few local stations. But what exactly are you paying for?

In a word: Content.

Whether you love having lots of

to flourish, so I figured we'd add a few more this time around.

### THE WEATHER CHANNEL

Here's a site that everyone can benefit from, whether they have pay TV or not (I know, I just mentioned that this certainly isn't the intention of the channels, but "I call them as I see them"). If you ever care about what Mother Nature has in store for you—

International Conditions & Forecasts, read some Text-Only Conditions & Forecasts, examine US Maps or International Maps, visit some other Weather Links, or take a look at The Weather Channel City of the Day.

At the bottom of this page, as well as on the main page, you can choose from a scrolling list of states. This feature is basically the heart of The Weather Channel site. Why? Because once you pick a state, you can then choose from a list of cities that have local radar and weather stations.

The best way to really experience the significance of this is to go to the site itself, but I'll try and give you an idea of how useful this feature is. Imagine selecting the city you live in (or one close enough to make no difference) and instantly being provided with current conditions, a graphical five-day outlook, regularly updated radar images, weather warnings and watches, and descriptive forecasts.

Whether you'd like to stay informed of what your current surroundings will be like for days to come, or are planning on visiting a certain city in the near future, you'll find yourself bookmarking this feature of the site and returning to it regularly. I love to travel and have not only my own hometown bookmarked, but several other favorite destinations as well.

Having written this column in February, the Weather Channel site had a few winter-related seasonal links that I won't go into simply because they'll most likely be gone by the time you ever see these words. Just to give you an idea (now that winter's just about gone as you read this), the site had Winter Weather and Check on the Slopes links, to name a few. Start looking for thunderstorm, tornado, and eventually hurricane information.

And finally, although they do give away a bit too much at their site, do check out the Weather Channel if it's available in your viewing area. As hooked on the Net as I am, I still check out this channel in the mornings before I start my commute. After all, signing



The Weather Channel website brings you so much useful information that you might never tune in to the channel again!

movies at your disposal, or enjoy choosing from several documentaries and information sources, a cable- or satellite-equipped TV brings quite a lot to your living room. In this month's column we'll look at a couple of information pay channels that have brought some of their content online. Though they're certainly not trying to get people to tune out their broadcasts, these channels have found the Internet to be a great medium for bringing viewers complementary information.

Some of you might recall that when this column first started I covered the Sci-Fi Channel's Dominion at <http://www.scifi.com>. That site has continued

and few can honestly claim not to—then you might want to point your web browser to the Weather Channel's excellent Net presence.

When you first access the opening page, you're provided with several choices, some permanent, some seasonal. On the left there's a vertical banner that lets you select from the all-year links; the seasonal ones are arrayed around the channel's logo.

The permanent link on the top of the banner is called, simply, The Weather. When you click it on, you are presented with a great wealth of information. You can take graphical views of US Conditions & Forecasts or

# What's better than speed reading? *Speed Learning.*

Speed Learning has replaced speed reading. It's a whole new way to read and learn. It's easy to learn...lasts a lifetime... applies to everything you read. It may be the most productive course you've ever taken.

Do you have too much to read and too little time to read it? Do you mentally pronounce each word as you read? Do you frequently have to go back and reread words, or whole paragraphs, you just finished reading? Do you have trouble concentrating? Do you quickly forget most of what you read?

If you answer "Yes" to any of these questions — then here at last is the practical help you've been waiting for. Whether you read for business or pleasure, school or college, you will build exceptional skills from this major breakthrough in effective reading, created by Dr. Russell Stauffer at the University of Delaware.

**Not just "speed reading" — but  
speed reading — thinking —  
understanding — remembering —  
and — learning**

The new *Speed Learning Program* shows you, step-by-proven step, how to increase your reading skill and speed, so you understand more, remember more and use more of everything you read. The typical remark from over one million people taking the *Speed Learning* program is, "Why didn't someone teach me this a long time ago." They were no longer held back by their lack of skills and poor reading habits. They could read almost as fast as they could think.

### What makes *Speed Learning* so successful?

The new *Speed Learning Program* does not offer you a rehash of the usual eye-exercises, timing devices, and costly gadgets you've probably heard about in connection with speed reading courses, or even tried and found ineffective.

In just a few spare minutes a day of easy reading and exciting listening, you discover an entirely new way to read and think — a radical departure from anything you have ever seen or heard about. *Speed Learning* is the largest selling self-study reading program in the world. Successful with Fortune 500 corporations, colleges, government agencies and accredited by 18 professional societies. Research shows that reading is 95% *thinking* and only 5% eye movement. Yet most of today's speed reading programs spend their time teaching you rapid eye movement (5% of the problem), and ignore the most important part, (95%) *thinking*. In brief, *Speed Learning gives you what speed reading can't.*

Imagine the new freedom you'll have when you learn how to dash through all types of reading material at least twice as fast as you do now, and with greater comprehension. Think of being able to get on top of the avalanche of newspapers, magazines and correspondence you have to read...finishing a stimulating book and retaining facts and details



**FOR FASTER SHIPMENT CALL 1-800-729-7323 OR FAX 1-609-273-7766**

more clearly, and with greater accuracy, than ever before.

### Listen — and learn — at your own pace

This is a practical, easy-to-learn program that will work for you — no matter how slow a reader you think you are now. The *Speed Learning Program* is scientifically planned to get you started quickly...to help you in spare minutes a day. It brings you a "teacher-on-cassettes" who guides you, instructs, and encourages, explaining material as you read. Interesting items taken from *Time Magazine*, *Business Week*, *Wall Street Journal*, *Money*, *Reader's Digest*, *N.Y. Times* and many others, make the program stimulating, easy and fun...and so much more effective.

Executives, students, professional people, men and women in all walks of life from 15 to 70 have benefited from this program. *Speed Learning* is a fully accredited course...costing only 1/4 the price of less effective speed reading classroom courses. Now you can examine the same easy, practical and proven methods at home...in your spare time...without risking a penny.

### Examine *Speed Learning* RISK FREE for 15 days

You will be thrilled at how quickly this program will begin to develop new thinking and reading skills. After listening to just one cassette and reading the preface, you will quickly see how you can achieve increases in both the speed at which you read, and in the amount you understand and remember.

You must be delighted with what you see, or you pay nothing. Examine this remark-

able program for 15 days. If, at the end of that time you are not convinced that you would like to master *Speed Learning*, simply return the program for a prompt refund. (See the coupon for low price and convenient credit terms.)

### RISK-FREE ORDER FORM

**YES!** I want to try *Speed Learning* for 15 days without risk. Enclosed is the first of 4 monthly payments of \$32.25\*. If I'm not completely satisfied, I may return it for a prompt refund.

**SAVE \$8.00!** I prefer to pay the \$129.00 now, and save the \$8.00 shipping & handling charge. I may still return the program for a full refund.

**Method of payment:** (Federal Tax Deductible)

Check or money order payable to Learn Incorporated  
 Charge to:  Visa  MC  Am Ex  Discover

Card # \_\_\_\_\_ Exp. \_\_\_\_\_

Signature \_\_\_\_\_

Phone (\_\_\_\_\_) \_\_\_\_\_

Name \_\_\_\_\_


Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_


\*Plus \$8.00 shipping and handling. U.S. funds only. For New Jersey residents, sales tax will be added.

**learn** Dept. LPE-01, 113 Gaither Drive,  
INCORPORATED Mt. Laurel, NJ 08054-9987

# Recoton wireless speakers blanket your

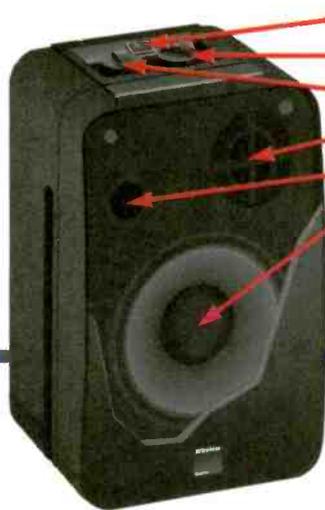

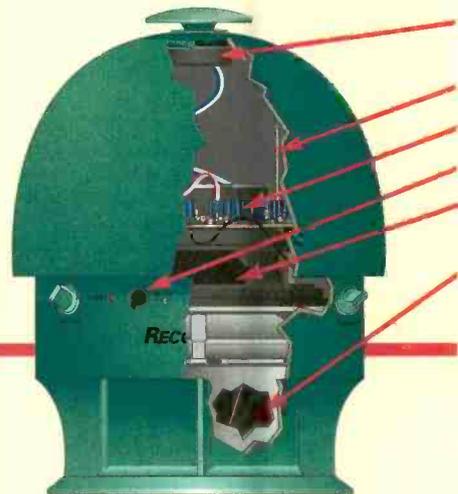
- Power control
- Tuning control
- Volume control
- Two-inch tweeter
- Tuned ports
- Four-inch woofer
- Individual left, right and mono switch and Individual bass boost control (on back)



In June of 1989, the Federal Communications Commission allocated a band of radio frequencies stretching from 902 to 928 MHz for wireless, in-home product applications. Recoton utilized this new technology to introduce this whole new generation of powerful wireless speakers that rival the sound quality of expensive wired speakers. From high-fidelity sound to weather resistance to
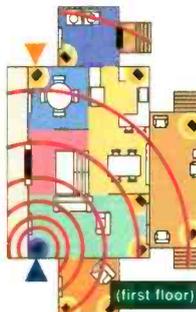
## BLANKET YOUR HOME WITH MUSIC

One Recoton transmitter will broadcast to any number of speakers, up to 150 feet away...through walls, ceilings and floors...indoors or out!



being totally cordless, this line of wireless speakers from Recoton is the perfect solution for listening to music anywhere you want in your home.

**Superior sound anywhere.** Each of these speakers let you listen to your stereo, TV, VCR or CD player in any room of your home—even outdoors—without running miles of speaker wire. You'll never have to worry about range because the new 900 MHz technology allows stereo signals to travel up to 150 feet through walls, ceilings and floors!

*The Recoton transmitter will operate any combination of these speakers, wirelessly, from up to 150 feet away...through walls, ceilings and floors!*



## RECOTON W440s

**Full dynamic range.** The W440s are set in a bookshelf-sized acoustically constructed cabinet, providing a two-way bass reflex design for individual bass boost control. Full dynamic range is achieved with a two-inch tweeter and four-inch woofer. Automatic digital lock-in tuning guarantees optimum reception and eliminates drift. The new technology provides static-free sound in virtually any environment. The W440s are self-amplified; they can't be blown out no matter what your stereo's wattage.

**Stereo or hi-fi, you decide.** The W440s have the option of either stereo or hi-fi sound. Use two speakers (one set on right channel and the other on left) for full stereo separation. Or, if you just want to add an extra speaker to a room, set it on mono and listen to both channels on one speaker. Mono combines both left and right channels for hi-fi sound.

**Special offer.** These speakers are the perfect addition to any audio lineup. And for a limited time, we're offering a special discount. Individually, this speaker costs \$89, but if you buy more than one W440, you can get them for just \$69 each!




Until now, there was no such thing as a completely weatherproof and wireless 900 MHz outdoor speaker. Today there is—introducing the new Recoton W410.

## How omnidirectional speakers work.

You'll never again fret over where to put speakers so you can hear them outside because Recoton's W410s deliver extraordinary omnidirectional sound out-of-doors. Within the green weatherproof housing, a two-inch tweeter and a six-inch woofer deliver 10 watts per channel of clear, strong sound. The tweeter fires upward and the sound is dispersed by the dome-shape of the speaker itself. The woofer, which fires downward, bounces sound waves off of the ground (or whatever surface the speaker is on) to disperse the sound, resulting in intense omnidirectional sound.

**Totally weatherproof.** The W410s are the first speakers of their kind to combine the best features of both indoor and outdoor speakers. They have the power and sound quality of indoor speakers and the wireless convenience and complete weatherproofing that is required in outdoor speakers. In addition, their unique design makes the W410s a discreet addition to your yard, patio or pool—you can enjoy music outdoors without a clutter of unsightly speakers!

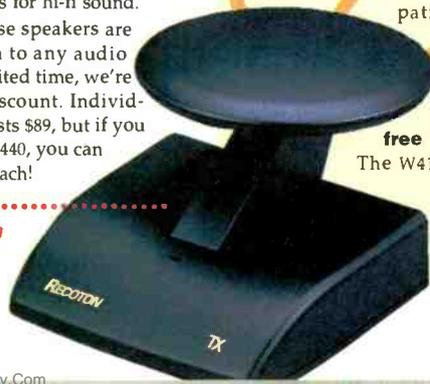**Powerful, static-free high-fidelity sound.** The W410s combine left and right channels for rich, high-fidelity sound. The six-inch full-range speaker



# home (and yard) with high-fidelity sound!

- Two-inch tweeter
- Copper wire antenna
- Capacitors
- Charging port
- Six-inch woofer
- Lead-acid rechargeable battery



## RECOTON W410s

has both treble and bass and provides an above-average bass response. The speakers produce a frequency range from 30 Hz to 19.5 KHz. Since we hear from 20 Hz to 20 KHz, that means the sound produced covers virtually all of our hearing range. With 10-watt RMS output and 20-watt peak output, the W410s provide powerful, static-free sound.

The W410s have a lead-acid rechargeable battery that gives 18 hours of straight play on a full charge. An AC adapter lets you listen to your speakers indoors and charge your battery at the same time!

**Use them anywhere.** The W410s are extremely versatile. While they were designed for outdoor use, they can also be used indoors. Their stylish design will match almost any decor!

**Don't wait! Special offer.** These wireless 900 MHz outdoor speakers are what you've been looking for to enjoy your favorite music on your deck, patio, around the pool... wherever you want. And for a limited time, we're offering a special discount. Buy one W410 for just \$149 and get additional W410s for \$99—that's a \$50 savings on each additional speaker. Call us now!

Recoton's wireless headphones make a great addition to any audio set-up. Look for our special headphone package offer!



- Power-saving low-battery light
- Robust 10-watt RMS amplifier
- Automatic shut-off/bass boost circuitry
- Dynamic tweeter
- Power option battery compartment
- Extended-range woofer
- Pulsating tuned bass port
- Individual control panel (on back)



Recoton's line of wireless speakers just got better. Now you can truly listen to music anywhere because where you put these W445s isn't limited to where you have an outlet!

**No speaker wires. No power cords. No kidding.** The W445s are the ultimate in wireless speakers, because they are also cordless. They are powered by eight "D" batteries, an optional rechargeable lead-acid battery or AC power. Put these cordless speakers anywhere you want within the 150-foot range of the transmitter, indoors or out...and enjoy!

A timer automatically cuts the speaker off 20 to 30 minutes after the music stops, or if the battery voltage drops too low. These speakers also have a built-in handle for easy carrying.

**Super sound quality.** Like the W440s, the W445s provide a two-way bass reflex design for individual bass boost control, full dynamic range and automatic digital lock-in tuning that guarantees good reception and eliminates drift.

With static-free sound in virtually any environment, the W445s are also self-amplified. So no matter what your stereo's wattage, they can't be blown out. In addition, these speakers have a feature that automatically "mutes" the speaker when the music stops playing so no noisy hiss is heard.

**Stereo or hi-fi.** The W445s also give you the option of either stereo or hi-fi sound. You can put two speakers, one set on right channel and the other on left, in the den for full stereo separation. Or add one speaker, set on mono, in the kitchen and listen to both channels at once for hi-fidelity sound. Recoton gives you music how you want it, where you want it!



## RECOTON W445s

**Special offer.** Our factory-direct pricing lets us sell more wireless speakers than anyone! For this reason, if you purchase two or more W445s, they're just \$99 each (save \$30 each!).

*It's time you surround yourself with music throughout your home. All of these products are backed by Comtrad's 90-day risk-free trial and a 90-day manufacturer's warranty. Try them in your home! If you're not thrilled with their quality and versatility (which we're sure you will be), return them for a full refund.*


- Recoton transmitter . . . . . \$69 \$8 S&H
- Recoton W440 speaker . . . \$99 \$9 S&H
- Buy two or more 440s for just \$69 each!
- Recoton W410 speaker . . \$149 \$9 S&H
- Additional W410s . . . . . \$99 \$9 S&H
- Recoton W445 speaker . . \$129 \$9 S&H
- Buy two or more 445s for just \$99 each!

Wireless headphones . . . . \$149 \$9 S&H  
Buy a transmitter and any two speakers and get the headphone system for \$49!  
Mention promotional code 2221-10518.

For fastest service call toll-free 24 hours a day

**800-992-2966**

comtrad

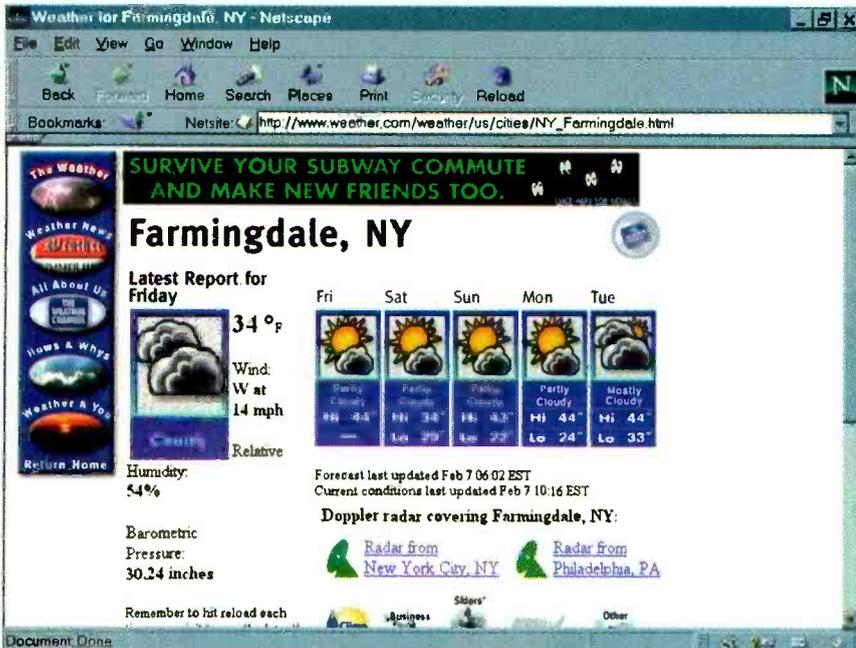

Here's the weather outlook at the time of this writing for the *Popular Electronics* offices. What's it like in your neck of the woods? Finding out is easy with *The Weather Channel's* site.


on to your online account is a bit difficult when you first open up your eyes in the morning.

## DISCOVERY CHANNEL

If you have children and want them watching some really educational quality programming, or are just interested in learning more about the world you live in yourself, the Discovery Channel is hard to beat. There's something of interest to practically everyone

on this station every day, and the same holds true for the channel's impressive website, Discovery Channel Online.

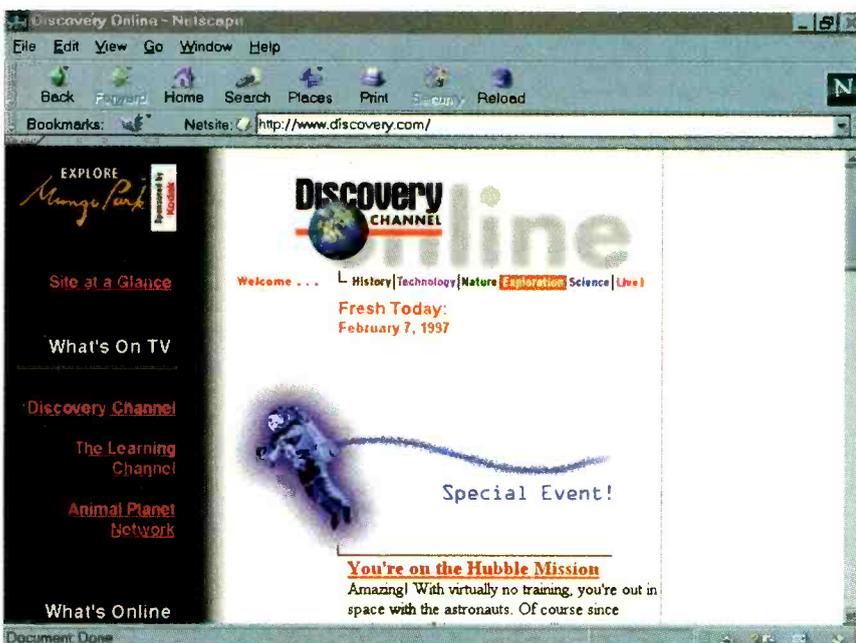Like other sites based on channels, the Discovery Channel Online provides you with information on what shows you can expect to tune in. Of course, this information always changes so we won't deal with it here more than to say that you'll always know what's on, regardless of where you live.



The Discovery Channel Online lets you know what's on the tube and links you to equally fascinating web material.

A great feature of this online presence is that it also gives you current articles of interest to viewers. For example, when I visited the site I found a fascinating link to the Hitchhiker's Guide to the Hubble. Here you can download video footage and information relating to various space missions. As I've said before, I love amateur astronomy, and it's refreshing to get this close to the cosmos on occasion.

You'll also find regular sections of the site dealing with History, Technology, Nature, Exploration, and Science. All of these are pretty self-explanatory and relate to current features on the channel dealing with each category. There's also a great search engine that lets you look for programming related to whatever text you enter.

### HOT SITES

**The Weather Channel**  
<http://www.weather.com>

**The Discovery Channel Online**  
<http://www.discovery.com>

In short, this site has plenty to offer, but it's very timely. The content changes daily and as a result I can only encourage you to check it out for yourself before you waste time searching through a TV guide of some type. Who knows how many fascinating, yet awkwardly scheduled programs we've all missed by relying on such a scanning method in the past.

Sites like these are an innovation that couldn't have come sooner. In these days of media overload, it's nice to be able to find out what's on of interest. Channel surfing can sometimes get you nowhere, but Net surfing is thankfully providing an option.

That's all for this month. Until next time, feel free to drop me a line via snail mail at *Net Watch*, **Popular Electronics**, 500 Bi-County Blvd., Farmingdale, NY 11735. I'll be publishing a new e-mail address next time; please be sure to look for it. ■



# NEW PRODUCTS

## "PLUG & PLAY" PHONE SYSTEMS

TMC Corporation's SOHO family of multi-line, "plug & play" phone systems are specifically designed for the small-office/home-office (SOHO) market. The six models are compatible with each other and with a host of add-on feature modules to provide small-business professionals with telephone systems to meet their particular needs.



The plug & play design, in which the "brains" are built into each phone, ensures that there is no complicated wiring or expensive controller unit. Up to 24 extensions can share the same system, with full access to all lines and features. A full-featured intercom lets you call any extension in the system at the touch of a button and answer intercom calls via speakerphone. Toll restriction allows you to prevent unauthorized long-distance calls, and call privacy lets you prevent others from listening to your conversations unless you include them in a conference call. Off-hook voice announce enables discreet intercom announcements to others without interrupting their calls in progress. Each phone offers a personal 34-number memory dial; 40 more numbers can be added to extension number one for system-wide use. Several models are equipped with a two-line, 16-character, pivoting LCD that includes clock, day and date, call-timer, number dialed, and internal messages.

Optional add-on modules include music on hold, which allows you to connect a radio or tape player to the system; a compatibility box to provide "line-in-use" indicators on all system phones when a line has been accessed by a standard telephone, and allows you to take calls off hold from any standard phone; caller ID


(with the service from the phone company); external paging, which allows you to connect to the system a door intercom speaker, as well as a magnetic door lock that can be opened from any extension; and a cordless phone adapter.

**CIRCLE 80 ON FREE  
INFORMATION CARD**
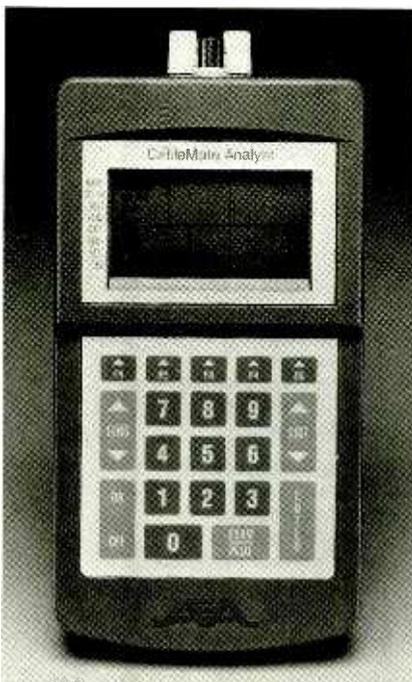
## MICROWAVE TESTER ACCESSORY HEAD

Intended for use by field-service or repair-depot technicians, the AMD1 accessory head from Fieldpiece is specifically designed to test microwave ovens for catastrophically failed diodes. When attached to a digital multimeter's test leads or to a Fieldpiece stick-style DMM, the head allows a meter to measure voltage across a resistor in series with the diode. The AMD1 identifies forward and reverse opens and shorts. In the forward direction, it can distinguish between a diode conducting current properly and a shorted diode. Diodes should be tested without connection to live circuits, as the accessory supplies adequate power to perform the test.

The AMD1 installs on top of the Fieldpiece Stick meter via jacks in a recessed housing. Those industry-stan-



dard jacks also accept Fieldpiece's deluxe test leads for remote testing versatility and compatibility with most other DMMs.

The AMD1 microwave tester accessory head costs \$18.95. For additional information, contact Fieldpiece Instruments, 231 Imperial Highway, Suite 250, Fullerton, CA 92635; Tel. 714-992-1239; Fax: 714-992-6541.

**CIRCLE 81 ON FREE  
INFORMATION CARD**

## SELF-SETTING ALARM CLOCK

*The Time Machine™* from Oregon Scientific always provides the most accurate time possible. The alarm clock sets itself automatically by receiving radio-frequency time signals from the U.S. Atomic Clock. One of the most accurate clocks in the world, the Atomic Clock is located in Boulder, Colorado, and is operated by the U.S. Department of Commerce's National Institute of Standards and Technology.



The Atomic Clock's signal was previously available only for use by commercial and industrial applications, including aircraft and ship navigation, broadcasting stations, and scientific facilities. Now, however, the Time Machine's internal omnidirectional antenna can pick up Atomic Clock signals from anywhere in the continental United States. (A small external antenna is provided for use in urban areas

and high-rise buildings where RF interference can be a problem.) The Time Machine not only sets itself to synchronize its digital time and date display with the Atomic Clock's signals, it also automatically adjusts for daylight-savings time. Once the Atomic Clock is up and running, so is the accurate time.

The Time Machine's oversized LCD readout features bright-blue "HiGlo" illumination, activated by pressing a large bar on top of the clock, for night-time viewing. A map icon on the display indicates which of the four U.S. time zones has been selected by the user. A radio-tower icon indicates reception of the Atomic Clock signal.


The Time Machine has a suggested retail price of \$99.95. For more information, contact Oregon Scientific, 18383 SW Boones Ferry Road, Portland, OR 97224; Tel. 800-869-7779 or 503-639-8883; Fax: 503-684-8883.

**CIRCLE 82 ON FREE INFORMATION CARD**
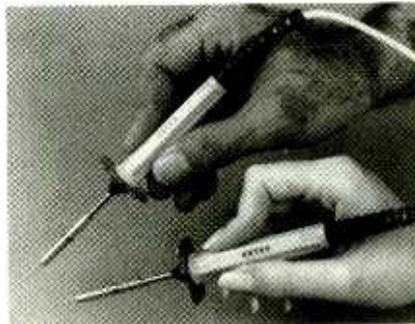
### CABLE CHECKER

With on-screen menus and help functions, the handheld *CableMate* time-

domain reflectometer (TDR) from *Advanced Electronic Applications* makes easy work of pinpointing faults in coaxial and two-wire cables. It can



be used for detecting breaks in cables that are buried or otherwise hidden, and for measuring a length of cable whether it is installed or still on the spool. The *CableMate*'s large LCD device graphically indicates the severity of faults and the distance from the user end to the fault. It displays the distance in feet or meters, and the amplitude in decibels down from the injected pulses.

A built-in table of more than 65 common cable types makes it easy to


choose characteristic impedance and velocity factor. The table has room for a total of 96 cable types. The user can add or delete cables, and give a description up to 14 characters long. The *CableMate* can also measure the velocity factor of a known length of cable. In addition, as many as 15 plots and their parameters can be saved in nonvolatile memory for later reference. Each plot can be assigned a name that appears whenever the plot is displayed.

The *CableMate* is equipped with a computer serial port. The optional *CableCon* serial cable and software package allows the *CableMate* device to be linked to a PC for real-time remote control and display, uploading and downloading plots and cable lists, and for printing plots.

The *CableMate* time domain reflectometer costs \$499. For more information, contact *Advanced Electronic Applications*, P.O. Box C2160, Lynnwood, WA 98036; Tel. 206-774-5554; Fax: 206-775-2340; Web: <http://www.aeainc.com>.

**CIRCLE 83 ON FREE INFORMATION CARD**

## ELECTRONIC COMPONENTS

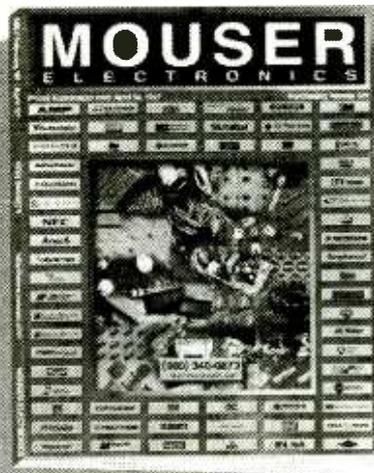

Call for your **FREE 340** page catalog **TODAY!**

- 68,138 Products
- 128 Manufacturers
- All Orders Ship Same Day
- No Minimum Order

**800-992-9943** FAX: 817-483-0931  
<http://www.mouser.com> [catalog@mouser.com](mailto:catalog@mouser.com)

958 North Main St., Mansfield, TX 76063

**CIRCLE 164 ON FREE INFORMATION CARD**

## Turn Your Multimedia PC into a Powerful Real-Time Spectrum Analyzer

### Features


- 20 kHz real-time bandwidth
- Fast 32 bit executable
- Dual channel analysis
- Up to 65,536 pt FFT
- Octave analysis (1/1 - 1/24)
- THD, IMD, SNR measurements
- Signal Generation
- Digital Filtering
- Triggering, Decimation
- Transfer Functions, Coherence
- Dynamic Data Exchange (DDE)
- Time Series, Spectrum Phase, Spectrogram and 3-D Surface plots
- Real-Time Recording and Post-Processing modes

### Applications

- Distortion Analysis
- Frequency Response Testing
- Vibration Measurements
- Acoustic Research
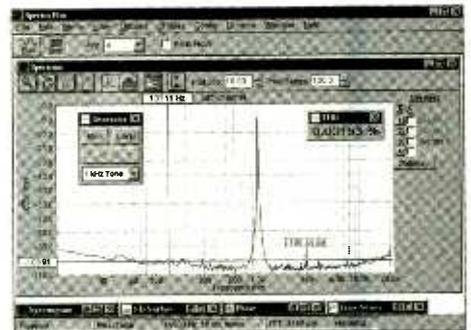
### System Requirements

- 486 CPU or greater
- 8 MB RAM minimum
- Win. 95, NT, or Win. 3.1 + Win.32s
- Mouse and Math coprocessor



Real-Time FFT Analyzer (single channel)	\$299
Options:	
Dual Channel Operation	\$99
Recording, Post-Processing Modes	\$99
Signal Generator	\$99
Professional Quality Sound Cards Available	Call

**DOWNLOAD FREE 30 DAY TRIAL!**

[www.telebyte.com/pioneer](http://www.telebyte.com/pioneer)

**PHS**

Pioneer Hill Software  
24460 Mason Rd. N.W.  
Poulsbo, WA 98370

Sales: (360) 697-3472

Fax: (360) 697-7717

e-mail: [pioneer@telebyte.com](mailto:pioneer@telebyte.com)

**Spectra Plus 4.0**  
Affordable Signal Processing Software

**CIRCLE 175 ON FREE INFORMATION CARD**

# Budget Project and Computer Books

**BP317—Practical Electronic Timing \$6.95.** Time measurement projects are among the most constructed gadgets by hobbyists. This book provides the theory and backs it with a wide range of practical construction projects. Each project has how-it-works theory and how to check it for correct operation.

**BP415—Using Net-scape on the Internet** **BRAND NEW** **\$7.95.** Get with the Internet and with surfing, or browsing, the World Wide Web, and with the Netscape Navigator in particular. The book explains: The Internet and how the World Wide Web fits into the general scenario; how do you go about getting an Internet connection of your own; how to download and install the various versions of Netscape browsing software that are available; and how to use Netscape Navigator to surf the Web, and to find and maintain lists of useful sites. There's a heck of a lot more, too!

**BP325—A Concise User's Guide to Windows 3.1 \$7.95.** Now you can manage Microsoft's Windows with confidence. Understand what hardware specification you need to run Windows 3.1 successfully, and how to install, customize, fine-tune and optimize your system. Then you'll get into understanding the Program Manager, File Manager and Print Manager. Next follows tips on the word processor, plus how to use Paintbrush. There's more on the Cardfile database with its auto-dial feature, Windows Calendar, Terminal, Notepad, etc.

**BP327—DOS: One Step at a Time \$5.95.** Although you spend most of your time working with a word processor, spreadsheet or database, and are probably quite happy using its file management facilities, there will be times when you absolutely need to use DOS to carry out 'house-keeping' functions. The book starts with an overview of DOS, and later chapters cover the commands for handling disks, directories and files.

**PCP119—Electronic Music and Midi Projects \$14.95.** Save cash by building the MIDI gadgets you need. Want a MIDI THRU box, program change pedal, Metronome, analog echo unit, MIDI patchbay or switcher? Over 16 practical and very useful music and MIDI projects—all in this book! The projects are explained in detail with full instructions on assembly.

**PCP120—Multimedia on the PC! \$14.95.** What is Multimedia? What can it do for you? It can do lots of nice things! This 184-page book helps you create your own multimedia presentation. Multimedia applications by people like you can revolutionize educational and business applications as well bring more fun, fun, fun into your leisure computer activities.

**BP404—How To Create Pages for the Web Using HTML \$6.95.** Companies around the world, as well as PC users, are fast becoming aware of the World Wide Web as a means of publishing information over the Internet. HTML is the language used to create documents for Web browsers such as Mosaic, Net-scape and the Internet Explorer. These programs recognize this language as the method used to format the text, insert images, create hypertext and fill-in forms. HTML is easy to learn and use. This book explains the main features of the language and suggests some principles of style and design. Within a few hours, you can create a personal Home Page, research paper, company profile, questionnaire, etc., for world-wide publication on the Web.



**BP377—Practical Electronic Control Projects \$6.95.** Electronic control theory is presented in simple, non-mathematical terms and is illustrated by many practical projects suitable for the student or hobbyist to build. Discover how to use sensors as an input to the control system, and how to provide output to lamps, heaters, solenoids, relays and motors. Also the text reveals how to use control circuits to link input to output including signal processing, control loops, and feedback. Computer-based control is explained by practical examples.

**BP411—A Practical Introduction to Surface Mount Devices \$5.95.** This book takes you from the simplest possible starting point to a high level of competence in working with Surface Mount Devices (SMD's). Surface mount hobby-type construction is ideal for constructing small projects. Subjects such as PCB design, chip control, soldering techniques and specialist tools for SMD are fully explained. Some useful constructional projects are included.

**BP136—25 Simple Indoor and Window Aerials \$5.50.** Many people live in flats and apartments where outdoor antennas are prohibited. This does not mean you have to forgo shortwave listening, for even a 20-foot length of wire stretched out under a rug in a room can produce acceptable results. However, with experimentation and some tips, you may well be able to improve further your radio's reception. Included are 25 indoor and window antennas that are proven performers. Much information is also given on shortwave bands, antenna directivity, time zones, dimensions, etc. A must book for all amateur radio enthusiasts.

**BP336—A Concise User's Guide to Lotus 1-2-3 Release 3.4 \$7.25.** Discover how to use a three-dimensional Lotus spreadsheet in the shortest and most effective way. The book explains how: to generate and manipulate 3-dimensional worksheets and how to link different files together; to generate and add graphs to a worksheet, edit them, and then preview and print the worksheet; to use the SmartIcons and become more productive with your time; to use the WYSIWYG add-in to produce top quality screen and printed displays; and much more.

**BP379—30 Simple IC Terminal Block Projects \$6.50.** Here are 30 easy-to-build IC projects almost anyone can build. Requiring an IC and a few additional components, the book's 'black-box' building technique enables and encourages the constructor to progress to more advanced projects. Some of which are: timer projects, op-amp projects, counter projects, NAND-gate projects, and more.

**BP401—Transistor Data Tables \$6.95.** The tables in this book contain information about the package shape, pin connections and basic electrical data for each of the many thousands of transistors listed. The data includes maximum reverse voltage, forward current and power dissipation, current gain and forward transmittance and resistance, cut-off frequency and details of applications.

**BP403—The Internet and World Wide Web Explained \$6.95.** You've heard about the Information Superhighway. Sort of makes you feel timid about getting on the Web. Put your fears aside! This book eliminates the mystery and presents clear, concise information to build your confidence. The jargon used is explained in simple English. Once the tech-talk is understood, and with an hour or two of Web time under your belt, your friends will call you an Internet guru!

**BP92—Electronics Simplified: Crystal Set Construction \$2.69.** This book is written for those who wish to participate in electronics more through practical construction than by theoretical study. It is designed for all ages upwards from the day when one can read intelligently and handle simple tools. The crystal set projects are designed to use modern inexpensive components and home-wound coils. A book highly recommended for all newcomers.

**ETT1—Wireless & Electrical Cyclopedic \$5.75.** Step back to the 1920's with this reprinted catalog from the Electro Importing Company. Antiquity displayed on every page with items priced as low as 3 cents. Product descriptions include: Radio components, kits, motors and dynamos, Leyden jars, hot-wire meters, carbon mikes and more. The perfect gift for a radio antique collector.

**ELECTRONIC TECHNOLOGY TODAY INC.**  
P.O. BOX 240, Massapequa, NY 11762-0240

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

**SHIPPING CHARGES IN USA AND CANADA**

\$0.01 to \$5.00.....	\$2.00
\$5.01 to \$10.00.....	\$3.00
\$10.01 to \$20.00.....	\$4.00
\$20.01 to \$30.00.....	\$5.00
\$30.01 to \$40.00.....	\$6.00
\$40.01 to \$50.00.....	\$7.00
\$50.01 and above.....	\$8.50

**SORRY No orders accepted outside of USA & Canada**

**No. of Books Ordered**

Total price of books ..... \$ \_\_\_\_\_  
Shipping (see chart) ..... \$ \_\_\_\_\_  
Subtotal ..... \$ \_\_\_\_\_  
Sales Tax (NYS only) ..... \$ \_\_\_\_\_  
**Amount Enclosed** ..... \$ \_\_\_\_\_

All payments must be in U.S. funds!

NW2

Allow 6-8 weeks for delivery


May 1997, Popular Electronics

# ELECTRONICS LIBRARY
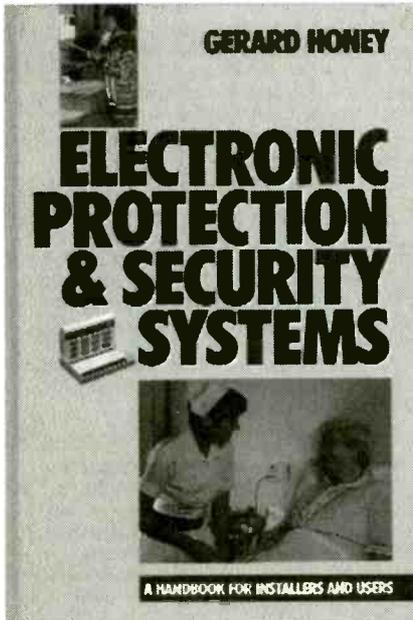
## ELECTRONIC PROTECTION & SECURITY SYSTEMS: A Handbook for Installers and Users

by Gerard Honey

This book presents an overview of the many electronic alarm systems available today. It is intended to help security professionals, system designers, installers, and users to protect the people and property under their care—from looking after children to infirm or elderly people, and securing buildings from homes to industrial installations or shopping centers.



The book examines the large and growing selection of intruder alarms, and presents ways to correctly choose and use the most appropriate ones. System layouts and wiring diagrams are provided where appropriate. Wireless systems are covered in detail. The book also covers fire alarms, call systems, access control, vehicle protection, emergency and security lighting, closed-circuit TV, and intercoms.

*Electronic Protection & Security Systems costs \$39.95 and is published by Butterworth-Heinemann, 313 Washington Street, Newton, MA 02158-1626; Tel. 617-928-2500; Fax: 617-928-2620.*


CIRCLE 90 ON FREE INFORMATION CARD

## COMPUTERS & YOUR HEALTH: The Essential Manual for Every Computer User

by Joanna Bawa

An awful lot of us spend hours a day in front of a computer, both at home and at work. We use PCs to write memos or novels, handle financial records for large corporations or the family check-book, play games against the computer or with other on-line gamers, shop, bank, conduct research, and surf the 'Net.

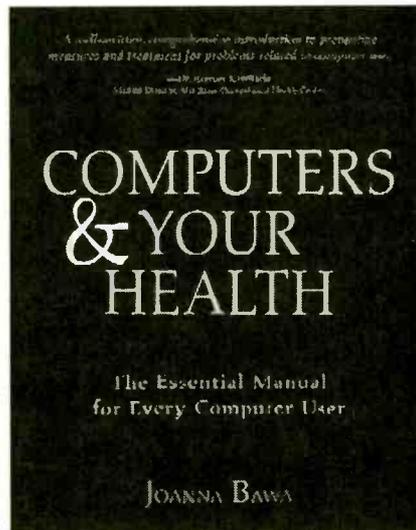This holistic handbook examines the ways in which extensive computer use can affect your health and well-being. The comprehensive guide draws upon the expertise of physical therapists, optometrists, osteopaths, and ergonomists, with the goal of creating a healthier work and home environment.



The book includes information about well-known hazards, such as repetitive strain injuries, electromagnetic radiation, and eye strain. It also looks at the psychological side of frequent computer use, examining such phenomena as video-game addiction and the effect of software design on our mental well-being. The book offers advice on how to manage your children's computing time and how to cope with stress. It suggests specific accessories—ergonomic keyboards, lighting, and furniture.

*Computers & Your Health: The Essential Manual For Every Computer*


*User costs \$12.95 and is published by Celestial Arts, P. O. Box 7123; Berkeley, CA 94707; Tel. 800-841-2665; Fax: 510-559-1600.*

CIRCLE 91 ON FREE INFORMATION CARD
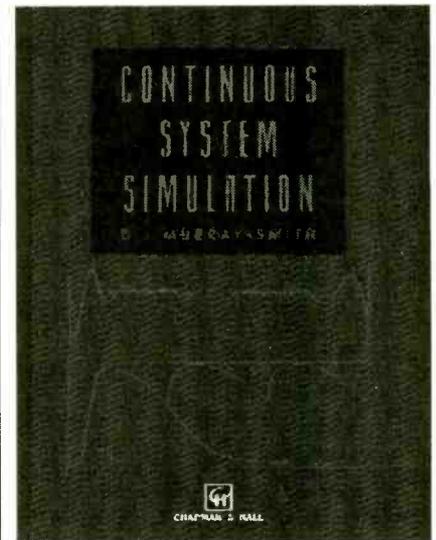
## CONTINUOUS SYSTEM SIMULATION

by D.J. Murray-Smith

This book provides an introduction to modern methods for computer simulation of systems involving continuous variables. Aimed at students, engineers, and scientists, it explains both the theory and the practice of those techniques. Taking a practical approach, the book places particular emphasis on the use of simulation languages and other software tools widely used in the field.



A simple simulation language is provided on disk with the book and used with examples and case studies from control, aeronautical, and biomedical engineering applications. Commercially available software is also described and applied. Model validation and real-time simulation techniques and applications are covered in detail.

*Continuous System Simulation costs \$59.95 and is published by Chapman and Hall, One Penn Plaza, 41st Floor, New York, NY 10119; Tel. 212-564-1060.*

CIRCLE 92 ON FREE INFORMATION CARD

# GIZMO®

## Life Saver


**CPR PROMPT HOME LEARNING SYSTEM.** Manufactured by County Line Limited, Health & Safety Products Division, 4543 Taylor Lane, Warrensville, OH 44128; Tel. 216-765-1234 or 888-728-4533; Fax: 216-765-0278. Price: \$59.95.

How would you feel if your toddler swallowed a Lego piece and you didn't know how to make her cough it up? If your neighbor's child fell into your pool and wasn't breathing when you pulled him out? If your spouse suffered a heart attack? Could you do anything to help besides calling 911—and then waiting those seemingly endless minutes until help arrives?

There's no reason for you to be so helpless. You could—and should—know how to perform some basic life-saving procedures.

In a medical emergency, minutes literally can mean life or death. It takes only four to six minutes after breathing stops for brain damage or death to occur. In fact, the American Heart Association (AHA) estimates that between 100,000 and 200,000 lives could be saved each year in the United States by the timely use of CPR, or cardio-pulmonary resuscitation. CPR keeps blood and oxygen circulating through the brain and other vital organs—in effect, keeping those organs alive and functioning—until professional help can get to the scene. And studies have shown that victims' chances for survival improve up to ten-fold when CPR is started immediately instead of six minutes later.

We've always thought that it would be neat to know CPR and other life-saving techniques—to be able to save someone who was choking in a restaurant or had suffered a heart attack. But our reasons for wanting to learn have become a bit more personal and immediate. Since the birth of our son, almost two years ago, we haven't felt fully qualified as parents because we haven't known what to do in an emergency medical situation. Taking a CPR course has

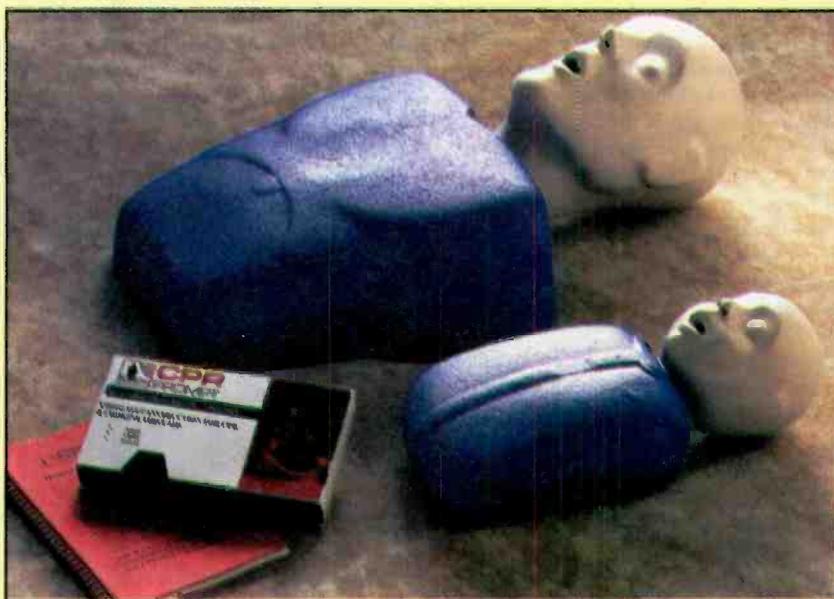

been on our list of New Year's Resolutions two years running.

On our doctors' advice, we took just about every pre-natal course offered to expectant parents, from Lamaze to diaper-changing. Yet no one suggested that we enroll in a CPR class, and we didn't think of it ourselves until after we brought the baby home from the hospital. Unfortunately, as any working parent of small children knows, fitting CPR classes into days already bursting with office hours, long commutes, business trips, bath time, and play time can be next to impossible.

We can't keep cutting the baby's food into little tiny pieces forever—nor can we continue feeling anxious every time he eats a whole grape. We try to keep him away from toys with tiny parts that might be swallowed, but it's impossible to completely baby-proof any environment. Yet every time a CPR course has been offered by the local library or hospital, the class times have conflicted with a business trip or our daily work schedules.

That's why we were so glad to hear about *County Line Limited's CPR Prompt Home Learning System*. The system allows us to learn CPR at home, when time permits. There's no need adjust our hectic

schedules to meet the class offerings—we could study during nap time or after the baby is in his crib for the night. The system costs less than what a couple would have to pay to take the CPR course offered at our library—and the baby's grandparents can learn, too.

The CPR Prompt system follows the American Heart Association's guidelines, which are intended to give rescuers every possible advantage in an emergency situation. The Home Learning System includes an instructional videotape, practice "manikins" that provide feedback to let you know if you're doing it right, and a supplemental study manual that answers some common questions about CPR. The booklet also offers advice on baby-proofing to avoid accidents, and describes the early warning signs of heart attacks and even strokes.

We began by assembling the two manikins—a large one that is used for learning the procedures for adults as well as for children aged one through eight years old, and a small one for infants under the age of one. Each comes in two pieces: a hard plastic head and a blue foam-covered torso. In addition, the system includes two different sizes of plastic bags that simulate

lungs. When you are breathing into the manikin correctly, the bag expands and makes the chest rise visibly. (For health reasons, the bags should be changed, and the heads washed, when more than one person is using the manikins.) Three bags of each size are included; extra bags can be ordered.

After washing the heads (in the dishwasher or by hand), it took less than five minutes to attach the bags, position the heads atop the torsos, and latch them on. We were then ready to begin watching the video.

Nine different life-saving techniques are demonstrated. The three basic procedures—CPR and rescue breathing, saving a conscious choking victim, and saving an unconscious choking victim—vary depending on the age of the victim—adult, child, or infant. The video is color- and number-coded so that you can easily find and repeat the subjects that most interest you, or that require more practice. A competent-looking man and woman guide you through the steps you need to learn—and make it look very easy.


In fact, the demonstrated procedures are quite easy to learn. As the video instructors are fond of repeating, "It's a matter of A, B, C." A for airway, B for breathing, and C for circulation. The tape clearly demonstrates precisely how to tilt the manikin's head back to open an airway; check for breathing and, if necessary, give rescue breaths; and check for a pulse and, if needed, perform chest compressions. The video shows how to apply all of those basic practices in a real-life emergency, including when to call for help, how to position the victim, and what to do in a variety of scenarios (restored pulse but no breathing, blocked airway, etc.). It also shows you how to determine if a person is choking, and how to respond properly depending on the victim's size and condition.

The instructors provide clear, straightforward directions, and the manikins are designed to provide immediate feedback. When you properly breathe into the mouth of either manikin, the lung bag inflates and the chest rises. If you correctly compress the chest of the adult/child manikin, you will hear a clicking sound at each press. (Inside the manikin is a pump, or piston, that can be adjusted between adult and child modes. Different amounts of pressure are required in each.) A chest plate inside the infant manikin prevents you from pressing too hard.

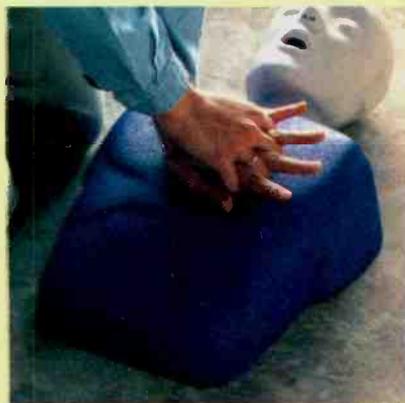**Gizmo is published by Gernsback Publications, Inc., 500-B Bi-County Blvd., Farmingdale, NY 11735. Senior Writers: Christopher Scott and Teri Scaduto. Copyright 1997 by Gernsback Publications, Inc. Gizmo is a registered trademark. All rights reserved.**

The manikins also offer some anatomical pointers. The infant manikin has nipples, and a raised bar runs down the middle of its chest. About an inch below the nipple line, the bar is interrupted—that spot is where you should press. Of course, a real infant has no such bar, but the instructional tape advises you to find the right spot by measuring down one adult finger's width. On the adult/child manikin, the bottom of the rib cage is clearly visible, as is the navel, and the video explains how to place your hand in relation to both when trying to dislodge an object that is obstructing breathing.

We were surprised at how easy it is to master the basics of CPR, the Heimlich Maneuver, and abdominal thrusts. In fact, the tape is only about 40 minutes long. It will take you at least twice that amount of time to gain some working knowledge of the



**When you properly apply chest compressions to the adult/child manikin, a pump inside the unit provides positive feedback by audibly clicking.**

procedures. It is recommended that you watch a segment of the tape, then rewind and carry out the procedures on your manikin while they do it on screen. After each segment, you are instructed to pause the tape and practice the techniques you've just been taught. When you hit PLAY again, you are given a brief quiz to test your mastery of the subject. You can then repeat it or move on to the next portion of the tape. And, of course, practice is vital to properly learning these techniques.

We were equally surprised to learn how physically demanding CPR is. The cycle of two breaths/15 compressions (one breath/five compressions for children and babies) can quickly wear out a person who is not used to physical activity. Even the relatively light pressure applied with two fingers to the infants' chest causes a strain in your hand in a couple of minutes. And you'll find that you must apply quite a bit of force to the adult manikin's chest before you hear the click that means you're doing it right.

One of the few complaints we had about

the CPR Prompt Home Learning System was that it raised several questions that went unanswered by the videotape or the Supplemental Learning Guide. How old do you have to be to perform CPR? Why are the techniques and procedures for different aged victims so different? We wished for a more extensive Supplemental Learning Guide, or at least a list of suggested reading.

We gave County Line Limited a call, and their representative graciously answered most of our inquiries. For instance, we learned that the American Heart Association says that children as young as 7 or 8 years old can learn CPR—as long as they are strong and heavy enough to perform the techniques. Even if they lack the muscles and body weight to do chest compressions on an adult, they should be able to perform CPR on an infant or another child. And, as the AHA stresses, in most cases any trained intervention is better than doing nothing at all.

We were also curious about the differences in the techniques used for resuscitating adults and children—15 compressions and two breaths for adults, 5 compressions and one breath for children and infants. It seems that children's hearts beat faster and they breathe more frequently than adults. Finally, why are you supposed to call 911 immediately if an adult stops breathing, but perform CPR for one minute before calling for help if you are alone with a young victim? According to the AHA, it is common for a child's breathing problems to be caused by a blocked airway, which can be corrected quickly by a trained lay person. There's a good enough chance that you can get the child breathing again on your own that it's worth trying for a minute before calling in the pros. With adults, however, cardiac arrest is likely to be the problem, and the time it takes the paramedics to arrive with their portable defibrillator can be even more crucial than the few seconds it might take you to get to a phone to call for help.

When you're watching the video, or even practicing on your own, it's easy to remember just how many breaths to give, how many chest compressions, when to call 911, and all the other variables. But practice is vital if you want to keep your skills sharp. So, now that we can cross "Learn CPR" of our resolutions list, we find ourselves adding a new entry: "Hold regular CPR practice sessions."

If "Learn CPR" wasn't one of your resolutions, maybe you should rethink your priorities. We would highly recommend that every able-bodied person take the time to learn the techniques that could save a life. And we would highly recommend the CPR Prompt Home Learning System to help you become proficient at these important techniques. ■

## Prompt Assistance

CPR PROMPT RESCUE AND PRACTICE AID MODEL CPR100. Manufactured by County Line Limited, Health & Safety Products Division, 4543 Taylor Lane, Warrensville, OH 44128; Tel. 216-765-1234 or 888-728-4533; Fax: 216-765-0278. Price: \$99.95.

Considering the fact that learning CPR is one of the very few New Year's resolutions we have ever kept, we have doubts about whether we would stick with our new-found resolve to practice the rescue techniques often. That's why we're happy to hear that *County Line Limited* also offers the *CPR Prompt Rescue and Practice Aid (Model CPR100)*, a handheld device that actually talks trained rescuers through any of twelve different CPR and choking emergencies. If you're out of practice—or if everything you ever knew about CPR flies right out of your head in the face of an actual emergency—the portable device can calmly guide you through the proper rescue procedure.

The Practice Aid is an FDA-registered Class I medical device. It measures about 8 × 3½ × 2 inches, and is intended to be wall-mounted in the home—preferably next to a telephone at which emergency numbers have been clearly posted. Mounting hardware is included.

The unit uses four "AA" batteries, which are not included. The batteries should be checked every 45 days, and a green LED lights 45 days after the unit was last used to remind you to do so. If batteries are low, when the power is turned on, the unit will say: "Warning. Replace batteries."

There's a round speaker at the top of the Rescue and Practice Aid, with the ON/OFF button located directly below it. A horizontal row of round buttons labeled A - ADULT, B - BABY, and C - CHILD is used to select the age category of the victim. A row of buttons numbered 1 through 4, running down the center of the device, is used to choose the condition requiring treatment. To the left of each rescue/condition button is a written description of the problem (from top to bottom: choking/conscious, choking/unconscious, pulse OK/no breathing, and no pulse/no breathing). To the right of each button is a written description of the proper response (Heimlich maneuver, abdominal thrusts, rescue breathing, and CPR) as well as a drawing illustrating the technique to be used. A PAUSE button rounds out the front-panel controls.

A volume control on the right side of the unit has two settings, which sounded to our ears like loud and louder. The softer of the two is intended for use during practice ses-



sions; the louder during emergencies when, presumably, there might be other people making phone calls or just making various types of noise.

During an actual emergency, there is likely to be quite a bit of confusion, if not actual panic. The Rescue and Practice Aid provides a calm voice of reason, giving the rescuer the confidence to carry out the necessary procedures. The first words it utters are "Remain calm." It then instructs you to select the age of the victim. If you don't immediately press one of the rescue/condition keys, the CPR100 gives you instructions for selecting the right procedure to follow.

When you select one of the rescue/condition keys, the device walks you through the entire procedure in real time, keeping accurate count of rescue breaths and chest compressions. In the case of a child or infant, it lets you know when one minute has elapsed and it is time to phone for professional help. If the victim's condition changes, you can simply press a different key to hear a new set of instructions. In rescue mode, the unit will keep repeating the directions until you turn it off, or the batteries run out.

During practice sessions, the Model CPR100 provides a straightforward—though dull—reminder of precisely how each rescue procedure should be performed. The digital voice, which is soothingly steady during an emergency, is annoyingly monotonous during practice

sessions. We would certainly prefer to use the Home Learning System and practice on our manikins, following along with the video. The question is: Would we remember to pull the kit out of the closet or attic every few months and actually do it? Unfortunately, being very ordinary folks, we probably would not.

Would we practice CPR every 45 days when the Rescue and Practice Aid reminded us to? Again, the answer is probably not. All the more reason to keep the unit conspicuously mounted in a convenient location, where we could find it immediately when needed.

We worry, however, about gaining a false sense of security. It's reassuring to have "someone" on hand to guide us in the event of a real emergency. But what if the crisis occurred away from our home and the trusty CPR100?

If used properly—as a practice aid as well as an emergency tool—the CPR100 will keep you as prepared as possible to save a life in several different emergency situations, wherever they might occur. And having it on hand during an emergency could help you stay composed and focused, better able to do whatever was needed to keep a victim alive until professional help arrived.

With that in mind, we'd rank the CPR Prompt Rescue and Practice Aid right up there with smoke detectors—essential to both our family's safety and peace of mind. ■



## Shake, Rattle, and Roll

**FORCE FX FORCE-FEEDBACK JOYSTICK.** From CH Products, 970 Park Center Drive, Vista, CA 92083. Tel. 619-598-2518; Web: <http://www.chproducts.com>. Price: \$249.95.

Do you like playing computer games? We don't—as surprising as that might sound. Although we've found a few strategy games that are enjoyable—and waste more of our time than we like to admit—most action games just leave us flat. They have nothing to draw us in. They just don't seem real.

At least they didn't, before we tried the *Force FX* force-feedback joystick from *CH Products*.

The *Force FX* adds a whole new dimension to game play. Now, as you bank your jet fighter for a better shot at the bad guy, you have to struggle with the stick to retain control of the jet. When you fire your missiles, the controller will recoil. Climb too steeply, and the control stick will buffet as your engines begin to stall.

Whether your favorite game is a flight

simulator, a shoot 'em up, or a racing, sport, or combat simulator, you'll enjoy it more with force feedback.

*Force FX* won't work with just any game—the game must be written to support it. As of this writing there are nine titles that either support the joystick outright or that can be updated to do so with a patch.

We received “*The Need for Speed SE*,” from Electronics Arts, with our evaluation joystick. The racing simulation game allows players to feel vibrations from driving on rough roads, g-forces from hard cornering, and collisions with cars, curbs, road signs, and other obstacles.

“*Descent II*,” from Parallax Software, allows players to feel explosions, force fields, and other robots. A patch is required to add force-feedback compatibility.

Flight simulators “*Jet Fighter III*” (Mission Studios and Interplay), “*Warbirds*” (ICI Games), “*Flying Nightmares 2*” (Domark UK), “*Silent Thunder*” (Sierra Online, requires patch), and “*Fighter Duel SE*” (Philips Media Games) all let players feel g-forces and combat explosions.

“*Unnecessary Roughness '96*” (Accolade) and “*Monday Night Football*” (Overtime Sports) turn the computer football game into the contact sport it should be. Both titles require patches.

Future games that will support the *Force FX* are: “*Confirmed Kill*” (Domark UK), “*Red Baron 2*” (On-Line), “*Air Warrior II*” (Kesmai), “*Mag Zone*” (Trimark Interactive), and “*Rocket Jockey Sierra*” (Rocket Science Games). And this is just the beginning—many other future games are expected to add the force-feedback support as well.

Developers have many options to choose from when implementing force-feedback into their games, and those choices will determine whether the game is really improved by the technology.

As mentioned previously, we received “*The Need For Speed SE*” with our joystick. We've never found driving games to be too compelling on the PC. We normally don't drive with a joystick, after all. The addition of force feedback did absolutely nothing for us.

But a silly little demo program supplied to test the stick was actually kind of fun to play with. It was simply an elastic sling and a ball that you could throw and catch with it. The mass of the ball, the gravity, and the sling's damping were adjustable. That's it—it was just a simple demo, and not a game. But it sure did feel real, as the ball flew up, then landed in the sling, stretching it taut before rebounding up into the air again.

At a trade show, when we had our first encounter with a CH force-feedback prototype, we played a game of “*Pong*”—the first home videogame—that had been retrofitted with force-feedback drivers. “*Pong*” is a simple enough game, something we would not usually find compelling. But with force feedback, it turned into a whole new experience.

The developer of the new version of “*Pong*” is Immersion Corp, the same company whose I-Force technology makes possible the *Force FX* joystick. I-Force allows six effects to be built into the joystick: jolt, vector force, vibration, spring, button reflex, and buffeting.

A jolt command causes a jolt or whack to be felt on the joystick. Jolt parameters include magnitude, direction, and duration. A game developer would use it when a plane is hit, when a car bumps into another car, or when a spaceship hits an asteroid.

The reflex jolt command causes the joystick to react in response to a specific joystick button press. The advantage of the reflex jolt over the standard jolt command is that it allows the stick to produce the desired jolts by itself. For example, the joystick can be set up to give a jolt of a given magnitude and direction whenever the trigger button is pulled. A different type of jolt can be set up for whenever a second button is pushed. The host computer doesn't have to monitor what the joystick is doing (with respect to jolts), so the jolts can be produced without consuming any process-

(Continued on page 31)

# Report from Las Vegas

## THE 1997 WINTER CONSUMER ELECTRONICS SHOW

As we joined the throng at the crowded Las Vegas Convention Center for this year's Winter Consumer Electronics Show, we found ourselves wondering if some enterprising manufacturer had managed to invent a working time machine—we were that sure we'd been transported back to *last year's* show. The signs of the past were all around us: Coming Soon—DVD! Internet-Convergence Technologies!

As soon as we got back to New York, we checked out last year's "Report from Las Vegas" (*Gizmo*, *Popular Electronics*, May 1996), and verified that we had not just experienced a four-day case of *deja vu*. There it was in black-and-white: "RCA DVD player, debuting at a store near you by Labor Day." "Toshiba unveiled plans for two players ... available this fall." "Sony ... plans to market DVD players later this year, with DVD-ROM drives to follow shortly thereafter."

One year later, those same manufacturers and more were demonstrating not prototypes, but actual products. Can you go out and buy a DVD player? Not as we go to press, but—maybe, just maybe—by the time this magazine hits the newsstands DVD will have hit the shelves of a store near you.

Why would you want to buy a DVD player? The format provides laser-quality video and Dolby Digital sound on a five-inch disc. Each disc has the storage capacity for a full-length movie, and then some. Software providers can opt to include subtitles and/or soundtracks in several different languages, add biographical information on the stars, present the movie in two or more aspect ratios (4:3 and widescreen), or in versions edited for different ratings, and even throw in the director's cut—a version of the film that the viewing public rarely gets to see. DVD is not just for video, however; DVD-ROM drives will bring increased storage capacity to PCs. (We won't go into the technical details on DVD here. Check out the "DVD Basics" box for a brief overview, or pull out the May 1996 issue for the whole DVD story.)

The DVD format has a lot going for it—including the support of virtually the entire consumer-electronics industry. So what's the holdup?

Two thorny issues are at the root of the delay: copy-protection and regional coding. The first has been tackled time and again—remember when the motion-picture industry was up in arms against VCRs, fearing that profits would take a nose dive

when folks watched films at home? Those fears were put to rest years ago, as video sales and rentals proved a gold mine for the studios. (According to Julie B. Schwerin founder and CEO of the electronic-media market research firm InfoTech, "In the 15 year period between 1980 and 1995 in which the home video industry grew into a \$15 billion industry, box office receipts doubled. It's in Hollywood's best interests to maintain as many channels of distribution as possible.") But new technology breeds new problems.

Everyone agreed from the get-go that some form of DVD copy protection was necessary, particularly with DVD home recorders looming on the not-too-distant horizon. Unfortunately, the original proposed copy-protection scheme had a disastrous effect on the performance of DVD-ROM drives—too much CPU horsepower was required to decrypt the data encoded on the disc. The computer industry quite rightly cried foul, and a new system had to be developed.

It wasn't until the end of October—well after the anticipated DVD player release dates—that the Consumer Electronics Manufacturers Association (CEMA) announced that the multi-industry Copy Protection Technical Working Group (CPTWG) had devised a new system to prevent the unauthorized duplication of movies and other entertainment of prerecorded DVD discs. The new scrambling technique will encrypt the contents of the discs—not the entire contents, but strategically chosen frames that would make a copied disc unusable. In addition, CPTWG will push for Congressional legislation prohibiting "the circumvention of the copy control technology and other technologies as they are developed and implemented."

The second issue slowing the introduction of DVD was the need for some sort of regional coding. Just as major motion pictures are often premiered in a few big cities before they begin playing "at a theater near


you," there are worldwide time frames for film releases. For example, a film is released first to theaters in the U.S. After the theater run is complete, the pay-per-view window opens. After that, the films make it to premium movie channels and video distribution. All that happens before the movie makes it to Europe and other parts of the world. The movie studios wanted to protect that tiered release schedule.


The solution they came up with was regional coding. Six geographical zones were created. Discs that play in one zone will not play on machines sold in another.

With those two issues resolved, the motion-picture industry is ready to back DVD—although not with the whole-hearted commitment that hardware manufacturers were expecting. At DVD's projected April roll-out at the end of April, you might have more DVD players to choose from than DVD movies to play.
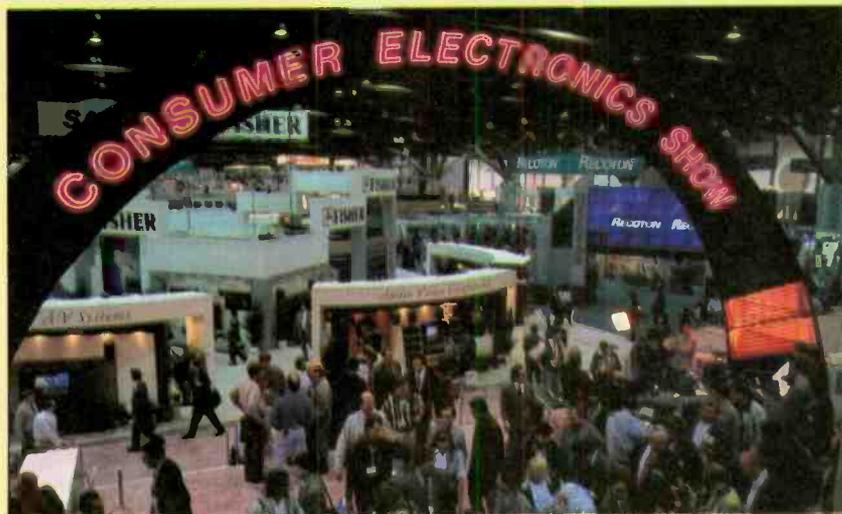
### THE FIRST WAVE

Toshiba is introducing two DVD players in the first quarter of 1997: the \$599 SD-2006 and the \$699 SD-3006. Long-time laserdisc champion Pioneer Electronics is rolling out two lines of combi players. Under the Pioneer label, the DV-500 DVD/CD player will carry a \$599 price tag, while the DV-700DVD/LD/CD player will cost \$999. The Pioneer Elite DVL-90 DVD/LD/CD player is expected to retail for a whopping \$1750. Thomson, whose DVD offering is the only one priced at less than \$500, plans to follow the same marketing strategy it used for DSS—an initial limited market-by-market rollout this spring, followed in the fall by a full nationwide approach. Matsushita, which previously had been hedging its bets on the new format, announced at WCES that it had set a March 1 delivery date on its two Panasonic DVD players, the \$600 DVD-A100 and the \$750 DVD-A300. Denon's initial entry into the DVD market is the DVD-200, priced at \$999. Zenith's 2000



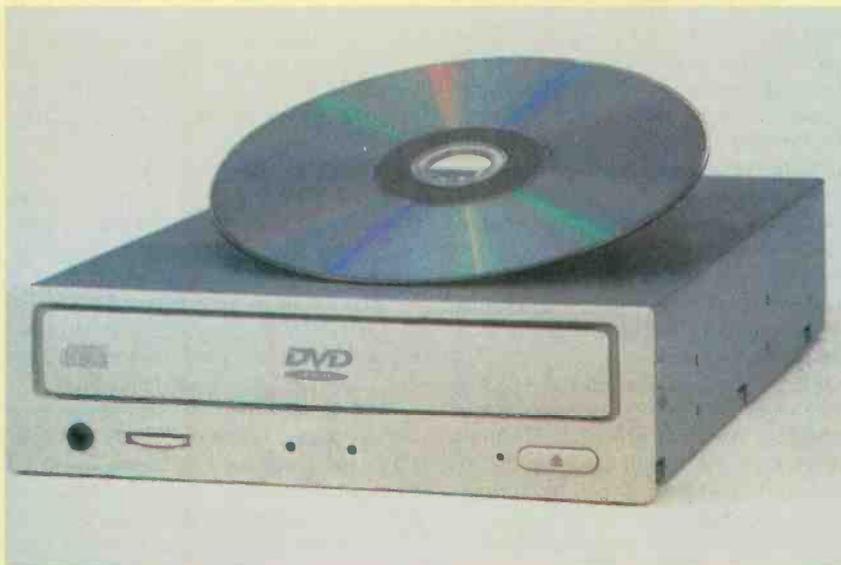

Sony began shipping sample units of its DVD-ROM drive to OEM PC manufacturers in January. It will be available in Sony PCs this summer.

DVD player will cost \$749. Prices have yet to be announced for DVD players from Zenith Inteq, Harmon Kardon, and Philips Magnavox.

While the strategy—at least among most of the big players—is to attract the mass market by keeping introductory prices at a palatable \$500–\$700, Sony has taken a different stance. Billing its DVP-S7000 DVD/CD player as a “reference standard” deck and pricing it at \$1000, Sony is targeting serious videophiles and music enthusiasts. The player uses Sony’s own MPEG IC to provide accurate MPEG decompression, and a 10-bit video D/A converter to minimize digital artifacts. The 32-bit RISC processor allows Smooth Scan™ operation in forward or reverse, in high-speed, slow-motion, or frame-by-frame mode. On the audio side, The DVP-S7000 features current-pulse D/A converters, a 45-bit “Full Feed Forward” digital filter for high music resolution, and a Dual Discrete™ optical pickup with both 650nm red laser and 788nm laser diodes to optimize the tracking of different substrate thicknesses and pit sizes in CD and DVD discs. The DVP-S7000 can be coupled with Sony’s SDP-EP9ES Dolby Digital™ AC-3 decoder processor (\$800). The company is depending upon highly satisfied early adopters to tout the new format, leading to increased demand from your average Joe.

Sony is providing some added incentives for those early adopters. The DVP-S7000 will come bundled with four free software discs. And the company announced a deal with Blockbuster in which buyers of the Sony DVD deck will receive coupons good for free DVD rentals at Blockbuster. Sony DVD demonstration kiosks will also appear in about 50 Blockbuster stores in select major markets.

Software introductions, timed to coin-



Toshiba plans to begin selling its Model SD-3006 DVD player in April at a suggested retail price of \$699.

cide with the spring hardware releases, were announced by Columbia TriStar Home Video, Sony Music Video, Warner Home Video, New Line Home Video, and MGM Home Entertainment. In an attempt to gauge the market, most are planning a mix of new releases, old favorites, and children’s films. From Columbia TriStar Home Video, expect to see *Close Encounters of the Third Kind: Special Edition*, *Fly Away Home*, *In the Line of Fire*, *Jumanji*, *Legends of the Fall*, *Matilda*, and *Taxi Driver*. Sony Music will offer *Beavis and Butt-head’s Final Judgment*, *Sesame Street’s 25th Birthday: A Musical Celebration*, and *Tony Bennett Unplugged*. The ten April DVD releases from MGM Entertainment—*The Wizard of Oz*, *Get Shorty*, *Rocky*, *Singin’ in the Rain*, *Midnight Cowboy*, *Casablanca*, *The Birdcage*, *Species*, *GoldenEye*, and *Raging Bull*—will be followed by 30 more DVD titles by the end of 1997.

Warner and New Line Home Video are sticking with more recent fare. Warner will debut DVD versions of *Twister*, *The Bridges of Madison County*, *Heat*, *Eraser*, *A Time to Kill*, and *Space Jam* this spring, to be followed by films currently in the theaters—*Mars Attacks*, *Michael*,

*Michael Collins* and *Sleepers*—available at the same time they are released on VHS. The six titles announced by New Line are *Dumb and Dumber*, *Mortal Kombat*, *The Player*, *The Mask*, *Rumble in the Bronx*, and *Seven*. Polygram (Philips) announced that it will be releasing several titles this spring, but did not name names.

Prices for DVD discs are expected to be affordable—although no one was willing to reveal specific numbers. The general consensus was that DVD films would be priced—for sale and for rent—somewhere between the prices of VHS tapes and laserdiscs.

## FORMAT FORTUNE-TELLING

With everything in place for a spring launch of this new video format, what does the future hold for DVD? It depends on who you ask.

Warner hired the research firm Vantis International to gauge DVD’s potential. Vantis, which compared the launch to that of DSS, predicted that as many as three-million DVD players could sell in the U.S. in the first twelve months, and as many as 12 million by the end of the third year. Those numbers assume, of course, that the studios get behind the format wholeheartedly. According to the combined results of five Vantis surveys, in which more than 4000 consumer whose demographics categorized them as early adopters were interviewed, “consumer purchase interest” in DVD “is 2½ times greater than that of DSS” back in 1994, when DSS was at a comparable same stage of development. Thomson sold a million DSS receivers in the first year.

Toshiba, one of the more optimistic DVD manufacturers, predicts that first year U.S. sales will be between 650,000 and one million units. Sony, on the other hand, is more conservative, predicting first year U.S. sales of DVD players of a modest 500,000 units. The company does not expect DVD to be an overnight sensation; at its WCES press conference, Sony executives kept tossing around the word “evolution.” Sony hopes to duplicate its highly successful launch 13 years ago of the CD format, which, remember, caught on like wildfire—three or four years after its initial release.

InfoTech, a Woodstock, Vermont-based electronic-media market-research firm, projects worldwide sales of 820,000 DVD players in the first year, but believes that the quick acceptance of DVD-ROM by computer users will drive down costs of shared components. That will likely result in a \$250 mass-market price point by the year 2000, “stimulating a tenfold increase in demand and culminating in a worldwide installed base of over 80 million units by 2005.”

Addressing the problem of limited software ability at introduction, Julie Schwerin of InfoTech noted, “What tends to be forgotten is that the most successful consumer

electronics product of the 1980's, CD-Audio, was launched with a handful of titles, while VHS had none. Our analysis shows that it is far more critical that a large catalog of titles be in place when hardware prices fall from the high end to the mid-market."

The InfoTech study also foresaw a peaceful coexistence between VHS and DVD—likening the relationship to that of analog cassettes and CD. Instead, the report found that DVD's biggest competition "will come from digital transmission formats such as pay-per-view movies available from Digital Satellite System services." Fortunately, the market is robust enough to support both digital formats. In fact, when recordable DVD players become available, they might be used to record such digital satellite transmissions. Due to complex technical, cost, and copy-protection issues, however, mass-market DVD recorders are not expected for several years to come.

### COMMITTED TO CONVERGENCE

The next biggest story at the Winter Consumer Electronics Show was convergence. Last year's highly touted merger of the television and the PC was translated by at least a dozen of TV manufacturers to mean the merger of the channel surfer and the 'Net surfer. Several phone manufacturers and videogame companies also joined the fray.

It seemed as if *everybody* was showing some sort of TV-based Web-browser. And most of the manufacturers were spouting the same marketing strategy: They plan to target non-PC households, and to get viewers to consider the Internet simply another stop on the television "dial." To that end, both format and content will be designed to look and feel like traditional video.

The first to market were Sony and Philips, both of which began shipping their WebTV set-top boxes last fall. Sony wouldn't reveal any sales figures, except to note that they had "met or exceeded all of our sales targets" for the first three months.

The Magnavox-brand WebTV, a.k.a. Internet TV Terminal, actually has been selling at its suggested list price—certainly not normal practice in consumer electronics.

At the show, Thomson announced plans to introduce this spring a set-top Internet-access box costing about \$300. It will be the first in a family of interactive products that would allow people to surf the Web, send and receive e-mail, shop or bank at home, and participate in other interactive activities. The device was developed with Oracle subsidiary Network Computer, Inc. (NCI); NetChannel, Inc. will be the exclusive Internet service provider (ISP) in the RCA-brand devices. Several concept products were unveiled at WCES, including an under-counter kitchen device and a small-screen device for use in kids' bedrooms or home offices for low-cost word processing, information retrieval, and communications.

The prototype displayed at the Sharp



Sony's "reference-standard" DVD-player will cost \$1000 when it debuts this spring.



DVD packaging prototypes from Columbia TriStar Home Video.

booth—for which no concrete pricing or marketing plans were offered—was a wide-screen, Internet-ready TV, NTSC/VGA monitor/receiver that allowed side-by-side viewing of video and Web pages. We liked the concept for two reasons. First, you could use the 90% of your brain that's not required for television viewing to surf the 'Net simultaneously, and be entertained while waiting for pages to download. Second, in Web-only mode, you could get PC quality on your TV—no eyestrain when reading on-screen text.

(By the way, a *real* product available from Sharp doesn't provide Internet access, but does allow a computer image to be projected onto a large screen using a SharpVision video projector. The \$649 AN-SC1000 is an add-on RGB-to-NTSC converter that does not require a software driver, making it easy to connect your PC to your home-theater system.)

Zenith has promised that its NetVision line will be the first TVs with integrated Web browsers to hit the market—even though the introduction was delayed into the first half of 1997, due to "changing market dynamics" and the need to "incorporate the latest technology." The company plans to add some computer functions that will enhance the sets' entertainment value. Under the Zenith label, the first NetVision set will be a 27-inch table model with a retail price of about \$1100. Zenith will also launch 27- and 35-inch models under its new Inteq brand.

Products from several manufacturers, including Mitsubishi's DiamondWeb™ TV, a set-top device from Boca Research, and Sega's Net Link, will use View-Call America's On-TV™ service. On-TV provides e-mail, information tailored to viewer needs, and general Web access. The service offers content from USA Today, Yahoo!, InfoSpace, Reuters, TV Data, Sports Ticker, Interactive Imaginations, and American Express Travel, among others. ViewCall America also announced a partnership with Hitachi Home Electronics, and is working with several manufacturers to create open TV-HTML™ standards intended "to enhance a consumer's Internet experience" with "TV-based Web extensions, which will combine the power of multimedia Internet content with live television signals."

Sega was the first to market a game-based Internet-access device. Last November, the company began selling Net Link, which plugs into the Sega Saturn game console and lets game-players access the Web via their TVs. The game console and Net Link add-on cost less than \$400—and you get to play games, too. Sega marketing plans focus, understandably, on multi-player online gaming. The device will also offer e-mail and localized information on TV programming, news, weather, sports, and entertainment.



David Spomer, Thomson vice president of DBS and DVD product management, demonstrates the RCA-brand DVD player at WCES.

## DVD BASICS

A DVD disc might look like a standard compact disc, but there's a world of difference. A CD has a maximum capacity of 650 megabytes (MB). The most basic DVD has a capacity about seven times as much—4.7 gigabytes (GB).

That higher capacity was achieved mainly by reducing the size of the pits on the disc's reflective layer that represent the digital information. On a standard CD, the smallest pit has a length of 0.83 micrometers or microns. A DVD, by contrast, has a minimum pit length of 0.4 microns. The distance between each track was similarly reduced by about a half, from 1.6 to 0.74 microns. The DVD laser, which reads the information encoded in the pits, has a shorter wavelength, which enables it to resolve the smaller features.

Until recently, even DVD's enormous capacity wouldn't have been able to deliver more than about four minutes of full-motion, full-screen video with sound. The magic of MPEG-2 video compression is what makes the capacity of DVD stand up to the task.

MPEG-2 is a standard for video compression or bit-rate reduction developed by the Moving Pictures Experts Group of the International Standards Organization. It works basically by eliminating repetition or redundancy in video. Instead of repeating information in future frames, only descriptions of changes are described by the data. This works because there is more redundancy in video than you might think—a typical movie scene really changes very little from one frame to the next.

MPEG-2 Intra, or I-picture, frames contain all the information to describe the frame. Predictive, or P-picture, frames describe changes relative to the last I-picture. DVD's copy-protection scheme encrypts only the Intra frames to reduce the number-crunching that's required.

On a CD, all audio is encoded the same. Ten seconds of silence requires as much space as ten seconds of the

"1812 Overture." The average rate at which data is read from a DVD disc is about 3.5 megabits per second (Mbps). However, rates as low as 1 Mbps and higher than 10 Mbps are supported.

Other factors that affect the data rate—and therefore the time capacity of the disc—are the length of the movie and the number of audio and subtitle channels required. Each audio channel requires 384 kilobits per second (Kbps), and each subtitle language requires 10 Kbps.

The basic DVD specification assumes that a typical disc will have three separate audio channels, four subtitle channels, and video encoded at an average rate of 3.5 Mbps. The resulting capacity would then be 133 minutes. A disc manufacturer could, however, play around with the disc's contents and, for example, reduce the number of languages to one audio channel plus one subtitle channel, and increase the capacity to 160 minutes.

But what about *Gone with the Wind*, which would exceed even that? Disc producers hate the idea of distributing films on two discs. An ingenious solution was developed to almost double the capacity of a single-sided disc to 8.5 gigabytes. The information is stored on two layers. The topmost layer is semi-transparent, allowing the laser to focus on either the top or bottom layer to read the information encoded there. The shift from one layer to the next should appear seamless to the viewer, because players will contain buffer memories so that they can output a continuous stream of data even as the laser re-focuses to the next layer.

With so much capacity on a single-sided disc, you'll never have to get up and flip over a disc in the middle of a scene the way you must with today's laserdiscs. However, the DVD format does allow for double-sided discs, including double-sided, dual-layer discs with a capacity of 17 GB—enough for more than eight hours of video. ■

Thomson is not the only manufacturer that will be using Oracle's Network Computer open-architecture system, which—unlike proprietary systems such as that used in WebTV—allows the manufacturers to select their own Internet service providers (ISP). Akai, Curtis Mathes, Funai, Proton, Uniden, and Zenith also announced partnerships with NCI.

## ROOFTOP MODEM

As far as Hughes Network Systems is concerned, the sky's the limit when it

comes to convergence. At WCES '97, the company announced plans to merge two of their very successful products: DSS and DirecPC. A pioneer in satellites, Hughes is a supplier of DSS systems, with their 18-inch dishes, as well as the 21-inch elliptical dishes and ISA cards required for the DirecPC Turbo Internet service. DirecPC allows customers to download information from the 'Net at speeds of up to 400 kilobits per second (Kbps)—more than three times faster than ISDN and 14 times as fast as standard 28.8 modems. The hardware costs

\$499 (instant \$100 cash rebates are currently being offered), and various subscription plans are available.

Hughes' new product is the Convergence Antenna for all-in-one satellite delivery of the more than 200 channels of digital TV from DirecTV and USSB, as well as DirecPC Turbo Internet service. The Convergence Antenna is identical to the 21-inch elliptical DirecPC dish—the difference lies in its much larger "tri-mode" LNB. The LNB actually picks up signals from two different satellites. Up to three cables run from the LNB into the home. One runs to the ISA-card-equipped PC for DirecPC. The other two are for DSS receivers.

When you buy the Convergence Antenna, which will be available in April, you have a few options. Traditional consumers



Thomson's RCA/NC Internet-access device connects to the family TV to provide e-mail, on-line banking and shopping, and other interactive functions.



Sharp has yet to announce marketing plans for its Internet-ready widescreen NTSC/VGA receiver/monitor, whose prototype is shown here.



Several manufacturers will use View Call's On-TV service to bring the Internet to the family television.

might want to buy the dish and a DSS receiver, then decide to buy the DirecPC adapter card later. Techies might do just the opposite. Or you can buy the whole kit-and-kaboodle. Prices won't be announced until closer to the launch date.

#### CALLING ALL WEB SITES

Can't stand the idea of seeing your TV screen monopolized by Web pages? Don't want to spring for a PC? Don't worry, you can still get on the Internet—just dial it up on the telephone. Several companies—including Cidco, IntelliData, Nortel, Philips Home Services, and Uniden—displayed “smart phones” at the Winter Consumer Electronics Show. Built-in software from various Internet Service Providers allow Web access via integrated screens and keyboards. Most, however, provide text only.

Philips Home Services demonstrated its P200, which features a 32-bit RISC CPU, a 16-line by 40-character backlit LCD, a QWERTY keyboard, a built-in Smart Card reader, 1MB of flash memory, and 2 MB of RAM (up to 64 MB of memory can be added with plug-in Miniature Cards). A high-speed auxiliary connector allows a printer, scanner, or digital camera to be attached. The phone provides access to Internet services including Philips Multimedia Center's Planet Search web search engine, adaptations of InfoSpace's popular Internet directories. Users can send and receive e-mail to and from other screen phones, PCs, WebTV terminals, and pagers; access on-line banking, news headlines, and weather reports; and control home automation devices. It supports all type-3 ADSI (Analog Display Services Interface) services, including Call Waiting with Caller ID, and is expected to retail later this year



The Convergence Antenna from Hughes Network can receive signals from two satellites simultaneously, allowing users to pick up DSS TV programming and DirecPC Turbo Internet access from a single dish.



Uniden's Axis offers cordless, computer-less connection to the Internet.

for about \$350.

The Intelifone from IntelliData is another ADSI-based entry. It offers most advanced telephone features, organizer functions that can be integrated with Caller ID call logs, and Web-based e-mail and information services (weather, stock quotes, sports scores, etc.). It is currently shipping with a suggested retail price of \$299.

Uniden is offering two models of the



The iPhone from Cidco can display complete Web pages—text and graphics—on its LCD readout.

Axis. For \$399, you can buy a 900-MHz cordless phone coupled with an Internet access device; the corded version costs \$299. While they are compatible with virtually all Internet and on-line service providers, both models are preconfigured with CompuServe Network Services, which charges \$4.95 for e-mail services.

Cidco's iPhone provides full Internet access—graphics as well as text. The high-end speaker phone offers e-mail, graphical access to the Web, and advanced telephony features for less than \$500. A 7.4-inch touch screen, embedded on the face of the iPhone, allows users to access Internet services by touching the softkeys. A QWERTY keyboard slides out from under the console for typing in e-mail and commands. The iPhone's full VGA screen lets a complete Web page be viewed without scrolling. With its 16-bit gray-scale display and software preprocessing of some data, the 14.4 modem functions at speeds comparable to a 28.8 modem. A serial port for a printer is included. The iPhone is expected to be available at mid-year.

#### THAT'S NOT ALL, FOLKS!

Convergence products and DVD might have dominated the show, but there was plenty more to see and hear on the floor of the Las Vegas Convention Center. Audio, video, home theater, and personal electronics were all represented in full force. For a glimpse of some of the products shown at WCES that won Innovations 97 awards—and a few more worthy of a mention—keep an eye on these pages. ■

#### FORCE FX JOYSTICK

(Continued from page 26)

ing power. The command includes a parameter that describes the repeat rate, which causes a rapid series of jolts when the button is held down. It allows easy implementation of automatic-weapon fire sensations. Other parameters include the button assignment, direction, magnitude, and duration.

The vibration command establishes a vibration of a given frequency and magni-

# RETAILERS THAT SELL OUR MAGAZINE MONTHLY

## Alaska

Frigid North Co.  
1207 W. 36th Avenue  
Anchorage, AK 99503

## California

California Electronics  
221 N. Johnson Ave.  
El Cajon, CA 90202

Ford Electronics  
8431 Commonwealth Avenue  
Buena Park, CA 90621

All Electronics  
14928 Oxnard Street  
Van Nuys, CA 91411

Gateway Electronics of CA  
9222 Chesapeake Drive  
San Diego, CA 92123

Mac's Electronics  
191 South "E" Street  
San Bernardino, CA 92401

Electronics Warehouse  
2691 Main Street  
Riverside, CA 92501

Orvac Electronics  
1645 E Orangethorpe Ave.  
Fullerton, CA 92631

Sav-On Electronics  
13225 Harbor Blvd.  
Garden Grove, CA 92643

JK Electronics  
6395 Westminster Blvd.  
Westminster, CA 92683

Marvac Dow Electronics  
980 S. A Street  
Oxnard, CA 93030

Kandarian Electronics  
1101 19th Street  
Bakersfield, CA 93301

Whitcomm Electronics  
105 W. Dakota #106  
Clovia, CA 93612

Marvac Dow Electronics  
265-B Reservation Road  
Marina, CA 93933

Minuteman Electronics  
37111 Post St., Suite 1  
Fremont, CA 94536

HCS Electronics  
6819 S. Redwood Drive  
Cotati, CA 94931

Halted Specialties Co.  
3500 Ryder Street  
Santa Clara, CA 95051

Metro Electronics  
1831 J Street  
Sacramento, CA 95814

The Radio Place, Inc.  
5675-A Power Inn Road  
Sacramento, CA 95824

HSC Electronics  
4837 Amber Lane  
Sacramento, CA 95841

## Colorado

Gateway Electronics of CO  
2525 Federal Blvd.  
Denver, CO 80211

## Connecticut

Signal Electronics Supply  
589 New Park Avenue  
W. Hartford, CT 06110

Cables & Connectors  
2198 Berlin Turnpike  
Newington, CT 06111

Electronic Service Prod.  
437 Washington Avenue  
North Haven, CT 06473

## Georgia

Norman's Electronics, Inc.  
3653 Clairmont Road  
Chamblee, GA 30341

## Illinois

Tri State Elex  
200 W. Northwest Hwy.  
Mt. Prospect, IL 60056

## Maryland

Mark Elec. Supply Inc.  
5015 Herzel Place  
Beltsville, MD 20705

Amateur Radio Center  
1117 West 36th Street  
Baltimore, MD 21211

## Massachusetts

U-Do-It Electronics  
40 Franklin Street  
Needham, MA 02194

## Michigan

Purchase Radio Supply  
327 East Hoover Avenue  
Ann Arbor, MI 48104

The Elec. Connection  
37387 Ford Road  
Westland, MI 48185

## Minnesota

Acme Electronics  
224 Washington Avenue N.  
Minneapolis, MN 55401

## Missouri

Gateway Electronics Of MO  
8123-25 Page Blvd.  
St. Louis, MO 63130

William Elec & Ind Supply  
803 Davis Blvd.  
Sikeston, MO 63801

## New Jersey

Lashen Electronics Inc.  
21 Broadway  
Denville, NJ 07834

## New York

Sylvan Wellington Co.  
269 Canal Street  
New York, NY 10013

R&E Electronics  
4991 Rt. 209  
Accord, NY 12404

Unicorn Electronics  
Valley Plaza  
Johnson City, NY 13790

## Ohio

Philcap Electronic Suppliers  
275 E. Market Street  
Akron, OH 44308

## Oregon

Norvac Electronics  
7940 SW Nimbus Avenue  
Beaverton, OR 97005

## Pennsylvania

Business & Computer Bookstore  
213 N. Easton Road  
Willow Grove, PA 19090

## Texas

Mouser Electronics  
2401 Hwy. 287 N  
Mansfield, TX 76063

Tanner Electronics  
1301 W Beltline  
Carrollton, TX 75006


Electronic Parts Outlet  
3753 B Fondren  
Houston, TX 77063

Electronic Parts Outlet  
17318 Highway 3  
Webster, TX 77598
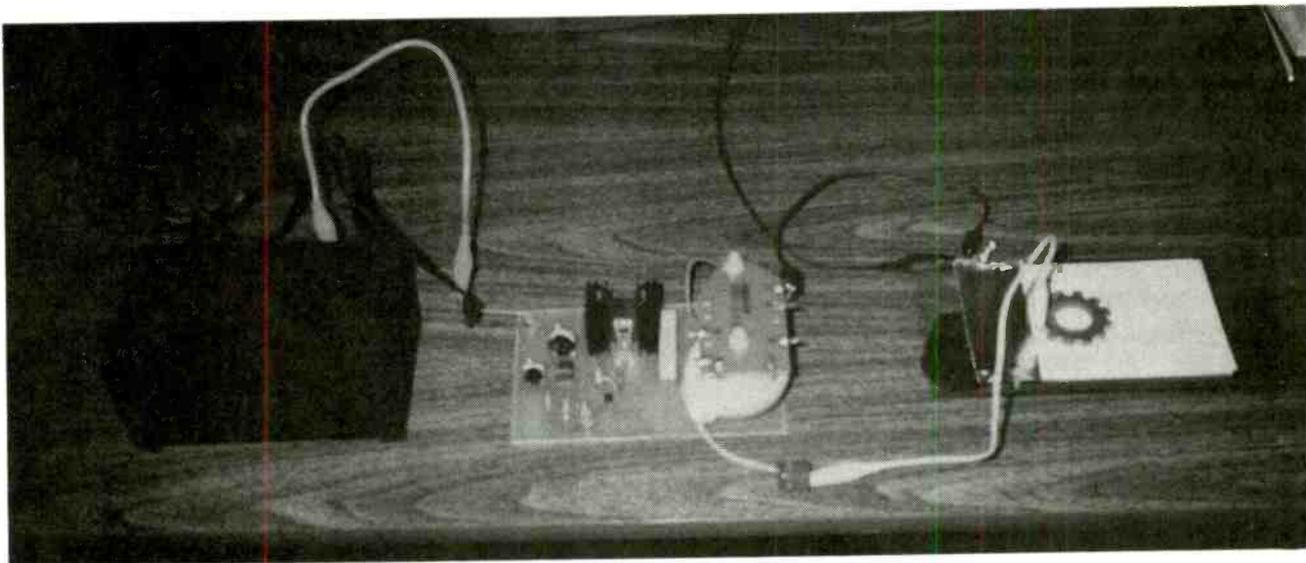
## Washington

Amateur Radio Supply Co.  
5963 Corson Ave., Ste 140  
Seattle, WA 98108

**If you'd like to sell our magazine in your store,  
please circle 180 on Free Information Card.**



# POOR MAN'S KIRLIAN PHOTOGRAPHY

*Take electrophotographs the inexpensive way with this radical new method that requires no film developing.*

By NICK CINQUINO

**M**any electronics experimenters dabble in the field of high-voltage circuit design. Also, many hobbyists understand the basic idea behind Kirlian photography or electrophotography, as it's often called. However, few actually get around to producing their own electrophotographs.

Why is that? Well, producing standard electrophotographs can be a pretty complicated task. It's also expensive. That's why this month we're bringing you a simple and affordable alternative: build the *Poor Man's Kirlian Photography* unit described in this article.

But before we get to why the Poor Man's project is such a great introduction to electrophotography, let's take a closer look at just what Kirlian photography really is.

## Basics of Electrophotography.

Standard Kirlian photography uses high voltage to cause an object to emit a corona discharge. The discharge pattern and colors are photographed using ordinary photographic film. A wide variety of sub-

jects are possible, such as gears, keys, coins, leaves, twigs, heatsinks, and anything else of reasonable

size that will sit still during the exposure. The discharge and photographic exposure are greatest near

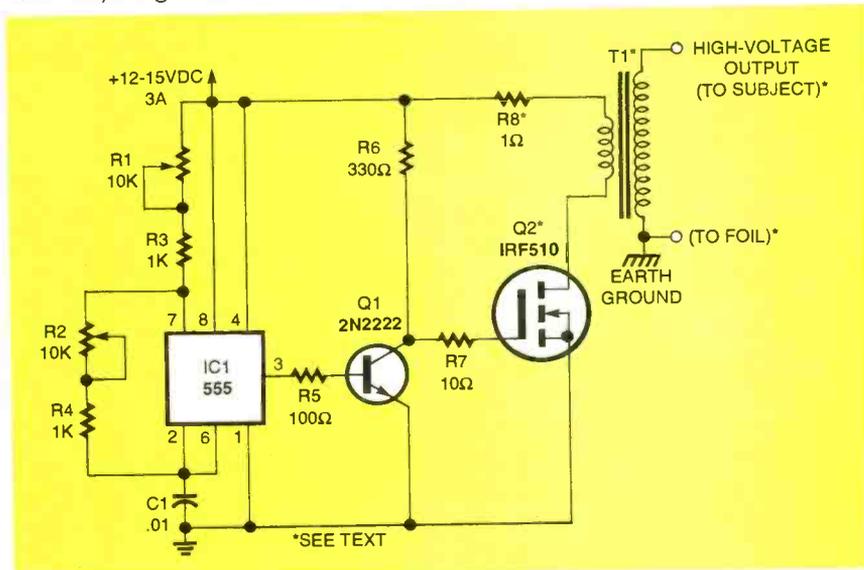


Fig. 1. This simple high-voltage supply will provide the "juice" for your electrophotographs.

an object's sharp points or edges.

Semyon and Valentina Kirlian are generally considered the originators of electrophotography, and most likely they were the first to use film or photographic emulsions for the process in the late '30s. Some of their findings were and still are controversial; for example, they claimed that electrophotographs of living things could indicate disease, or impending disease. They also apparently originated the "phantom leaf" claim, in which an electrophotograph of a trimmed leaf appears whole.

But if you research back to the late 1700's, you'll find that Georg Christoph Lichtenberg produced related images by the scattering of dust around a charged object. His basic techniques are still used, in fact. "Lichtenberg figures" aid in the study of corona loss from high-voltage wires. Other types of electrophotography have been used to check factors such as weld quality.

**Drawbacks and a Simpler Way.** In a typical electrophotography setup, you need to either severely modify a normal camera, or obtain sheets of unexposed film. Both choices offer big headaches. For example, if you elect to modify a regular camera, the camera is no longer usable for anything other than electrophotography. Also, your subject is severely limited in size to the film itself, such as 35mm or 11mm. If you choose sheet film, size is no longer a major limiting factor, but now you'll need to develop the exposed film yourself. So the project is doubly compounded by darkroom necessities like chemicals, trays, timers, plumbing, and of course the darkroom itself. And if those problems weren't enough, the photos require exact exposure times.

Now it's not that the author's a terribly lazy person or anything, but like many hobbyists he's constantly on the lookout for shortcuts to make life easier. In this case, the thought of demolishing a camera to electrophotograph tiny objects, and filling a basement with scary-sounding darkroom chemicals was-

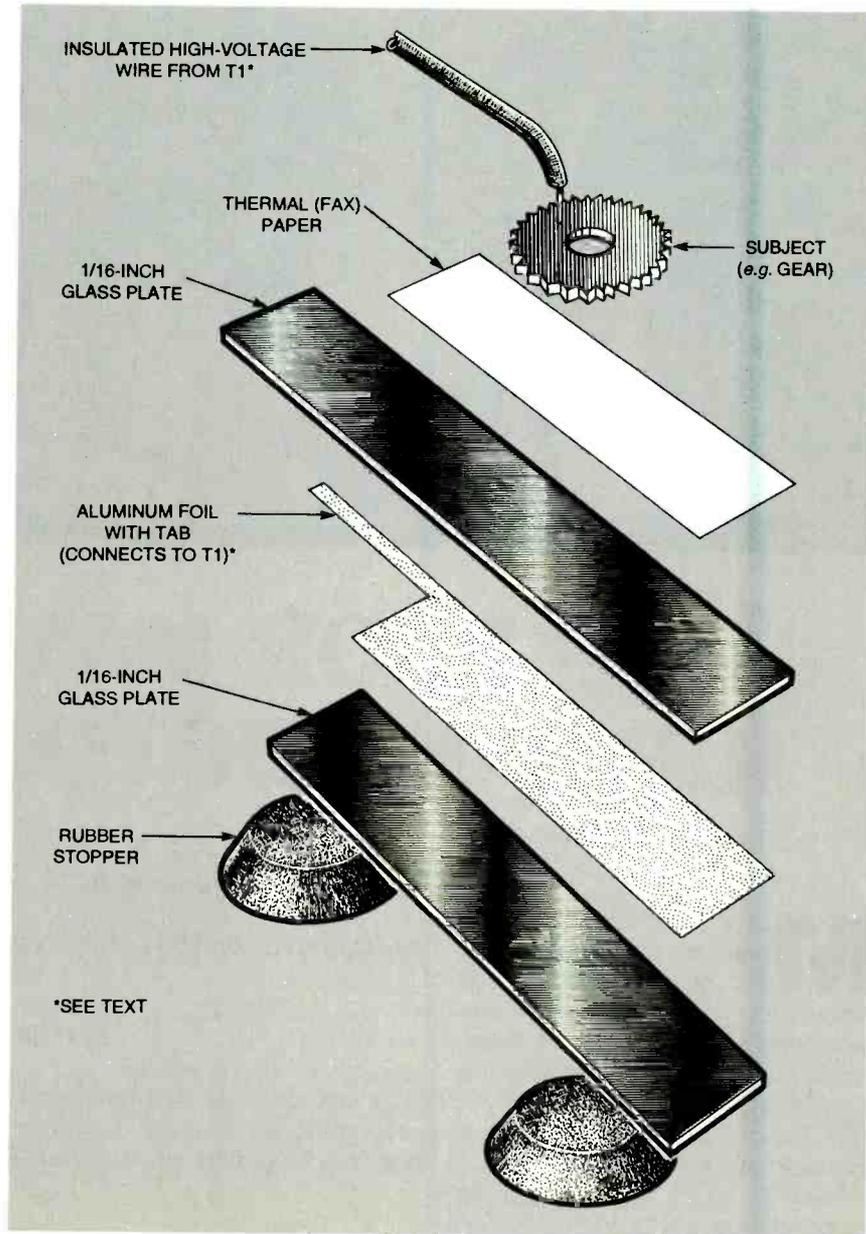


Fig. 2. As you can see, the physical stage required for electrophotographs is easy to assemble.

n't very appealing.

Because Mr. Lichtenberg's method proved that a form of electrophotography can be done without necessarily using film, the author decided to find a modern way to use his ideas. After rejecting a few absurd ideas, he came up with thermal paper as a possible medium; that's the type of paper used in older fax machines. Sure enough, thermal paper, it turns out, is a great way to make simple electrophotographs.

Thermal paper is dirt cheap, readily accessible from the nearest

fax machine, and can be used in ordinary room light to make an exposure. You can watch the paper and the developing image to get exactly the exposure you want. And while you'd expect the image to be monochromatic, a close inspection of the image reveals faint color/gray scale variations, for reasons unknown.

How does the corona form an image on thermal paper? We're not exactly sure! Is it strictly a thermal effect, or is UV light and/or ozone also involved? Try it yourself and find out.

# It's Not Just Training...

*"I needed a refresher in fundamentals and a piece of paper that said I had a degree. CIE gave me both."*

**Louis P Briant**  
Senior Engineer  
Sentel Corp.

*"CIE allowed me to use my G.I. Bill benefits and independent-study allowed me to continue my studies while employed."*

**Charles Hopper**  
Electronics Senior Chief  
U.S. Navy

*"The fact that I intended to continue pursuing my Associate Degree with CIE was a key factor in being considered for my current position."*

**Annamarie Webster**  
Project Engineer -  
Instrumentation  
Ketchikan Pulp

*"My associates at work recommended CIE... The lessons were structured so they were easy to comprehend"*

**Vincent R. Buescher**  
Communications Technician  
AT&T

*"I reenrolled and received my A.A.S. degree from CIE because of the good experiences I had in one of CIE's career courses."*

**Maurice M. Henchorn, Jr.**  
Electronic Technician  
The Denver Post

Independent study from CIE will give you the skills you need to win your own independence in a successful career.

At CIE, we pride ourselves in keeping pace with the latest developing technologies. In turn, this assures our students that upon graduation they can mesh seamlessly into a variety of exciting and rewarding technology-based careers.

Back in the 1930's, we specialized in teaching radio and television sciences. Today, it's computer technology, programming, robotics, broadcast engineering, information systems management, and the electronics behind it all.

But some things have not changed, like the desire of CIE's faculty and staff to see their graduates succeed.

That is why at CIE we teach not only the hands-on, practical aspects of electronics technology, but also delve into the "why" behind today's technology. Why does it work the way it does?

The insights to be gained from such a broad, rich and comprehensive

education at CIE matches or exceeds those gained through

traditional commuter institutes while providing an education schedule to match your commitments and lifestyle.

Our patented learning program is specifically tailored for independent study and backed up by a caring team of professional educators who are at your call whenever you need their help.


At CIE, we'll match our training with your background and career goals and help you decide which of the many career courses that we offer suits you best. We offer an Associate Degree Program and through our affiliation with World College a Bachelor Degree

Program.

If you have the sincerity, the smarts and the desire, CIE can make it happen. CIE is already the institute of choice for many Fortune 1000 companies. Why shouldn't you be next?



**Computer Programming**

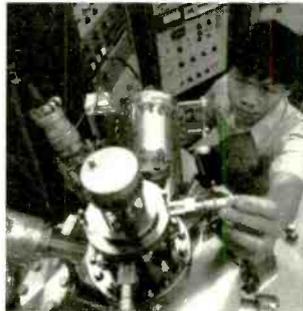

**Electronics Technician**

# ...It's an Education.



1776 East 17th Street  
Cleveland, OH 44114  
(216) 781-9400 • 1-800-243-6446

**YES!** Please send me more information on:

- CIE's Associate Degree Program
- CIE's Career Courses
- World College's Bachelor Degree Program

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Phone: \_\_\_\_\_

Check for G.I. Bill  Active Duty  Veteran

AH92

**Circuit Description.** Many varieties of high-voltage/high-frequency power supplies have been presented in this magazine over the years. If you happen to have a spark-gap or tube-type Tesla coil, you need look no further for a power supply for this project. If not, you will need a simple solid-state flyback or trigger-coil high-voltage power supply. The schematic of the one used in the author's prototype is shown in Fig. 1. The circuit delivers about 10 kV at 50 kHz.

Power for the circuit is provided by a 12- to 15-volt DC supply capable of delivering 3 amperes. A 555 timer, IC1, generates a frequency-adjustable squarewave, which is buffered by Q1, a general-purpose NPN transistor.

The squarewave switches Q2, an IRF510 MOSFET, on and off, thereby allowing high-current pulses through the primary of T1, an ordinary TV flyback transformer (more on T1 later). The flyback's secondary output rings or resonates at a high voltage in response to the primary input, and

output is directly applied to the electrophotography subject.

**Construction.** Before you can build the Kirlian Photography unit, you will need to select and prepare a flyback transformer for use in the circuit. Make sure the flyback has no rectifier diode. Flybacks of this type are available from old TV sets and TV repair shops. Once you have a transformer, remove any preexisting primary (which is a turn or two opposite the "ball of wax") and wind ten turns of 14-gauge wire at the same area.

Wire the circuit on a piece of perforated board, beginning with a socket for IC1. Go on to connect the potentiometers, resistors, capacitor, and transformer. Then solder Q1 and Q2 to the circuit, making sure both are wired correctly. Insert the IC into its socket, making sure it is oriented properly.

Before continuing to assemble the electrophotograph stage (more on that in a moment), connect power to the circuit. Adjust

## PARTS LIST FOR POOR MAN'S KIRLIAN PHOTOGRAPHY

### SEMICONDUCTORS

IC1—555 timer, integrated circuit  
Q1—2N2222 NPN general-purpose transistor  
Q2—IRF510 MOSFET

### RESISTORS

(All fixed resistors are 1/4-watt, 5% units.)  
R1, R2—10,000-ohm potentiometer  
R3, R4—1000-ohm  
R5—100-ohm  
R6—330-ohm  
R7—10-ohm  
R8—1-ohm

### ADDITIONAL PARTS AND MATERIALS

C1—0.01- $\mu$ F, ceramic-disc capacitor  
T1—Flyback transformer (see text)  
Perforated board, rubber stoppers (2), 1/16-inch glass plates (2), aluminum foil, thermal paper, metal subject (gear, etc.), insulated wire, solder, hardware, etc.

potentiometers R1 and R2 until you hear a high-pitched whistle. Now, check carefully for a spark output by bringing a grounded wire to within an 1/8 inch or so of the high-voltage output wire. Once an arc starts, you should be able to draw it out to about a 1/2 inch.

You're now ready to build the setup for exposing the thermal paper. This assembly, shown in Fig. 2, is nearly identical to that used for photographic sheets. The first step is to make an insulating base from rubber stoppers (you could get away with ceramic blocks or glass as well). On top of these, place a small glass plate measuring 1/16 by 4 by 7 inches. On this, place a slightly smaller piece of aluminum foil with a tab sticking out for the connection shown in Fig. 1. On this, place another plate of 1/16-inch glass.

The next layer of the setup is the thermal paper itself, followed by the subject, which in the diagram is shown to be a small gear. Finally, attach the subject to the high-voltage wire from T1 (as shown in Fig. 1).

### Making an Electrophotograph.

Connect a subject to the setup just described. Make sure the area

*continued on page 63*


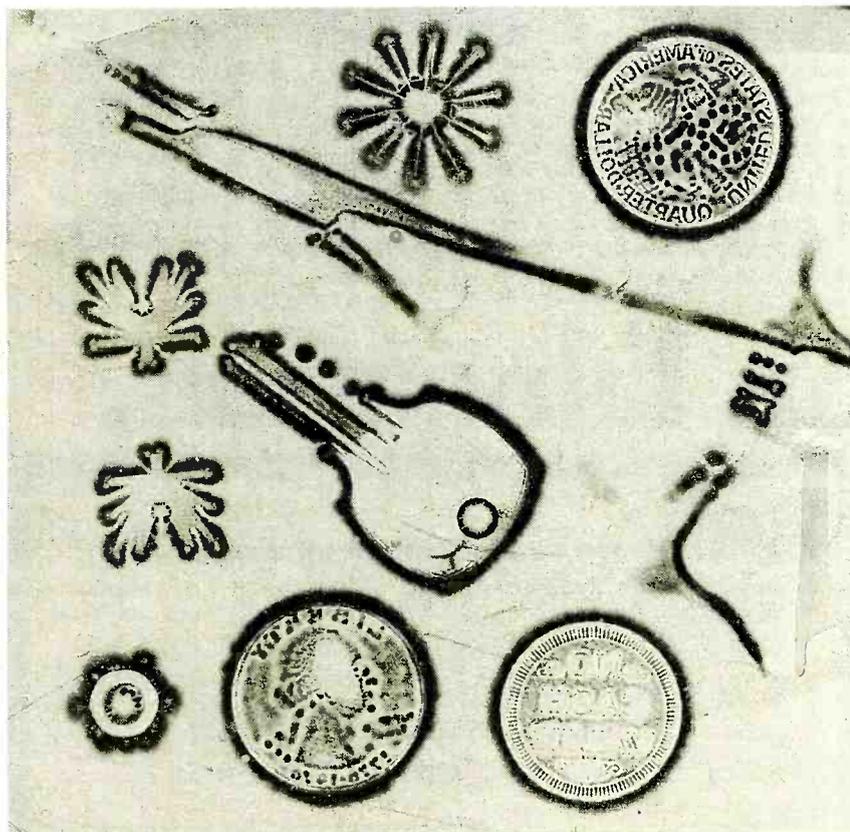


Fig. 3. Here are some sample, multi-exposure electrophotographs. Can you recognize all the objects?

# Hobbyist's Paperback Budget Books

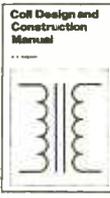

**BP80/98—Popular Electronic Circuits-Books 1 and 2...\$11.90.** Contains a wide range of circuits which are accompanied by text giving a brief introduction, circuit description and special notes on construction and setting-up that may be necessary.



**#160—Coil Design and Construction Manual...\$5.95.** A complete book for the home builder on how to make RF, IF, audio and power chokes and transformers. Practically every possible type is discussed and calculations are explained in detail.



**BP271—How to Expand, Modernize and Repair PC's and Compatibles...\$7.75.** All the practical information you are likely to need to upgrade your PC and compatible. Also contains useful information and illustrations to help you with repairs.



**BP276—Shortwave Superhet Receiver Construction...\$6.95.** Provides construction details, including coil winding, of a number of advanced-design receivers which should have performance levels at least equal to commercial sets of similar complexity.



**#223—50 Projects Using IC CA3130...\$5.00.** One of the more practical and useful operational amplifiers (opamp), the CA3130 integrated circuit chip is the heart of several easy-to-assemble projects covered in the book. The projects are divided into five categories: audio projects, RF projects, test equipment, household projects and a catch-all miscellaneous group. Ideal for all skill levels.



**BP122—Audio Amplifier Construction...\$5.75.** Practical designs are featured and include circuit diagram and description, Veroboard or printed-circuit board layout and construction notes. The text is divided into two parts. The first deals with many types of preamplifiers. The second covers power amplifiers from a simple low-power battery type to a 100-watt DC-coupled amplifier using four MOSFETs in the output stage.



**BP107—30 Solderless Breadboard Projects-Book 1...\$5.95.** Each project is designed to be built on a "Verobloc" breadboard and is presented with a brief circuit description, circuit diagram, component layout diagram and components list. Notes on construction and applications are provided. Wherever possible, the components are common to several projects to keep project costs down.



**BP266—Electronic Modules and Systems for Beginners...\$7.25.** Shows the reader how to build a number of simple analog and digital circuit modules, all suitable for battery operation, and all based on only 1 or 2 transistors or ICs.



**BP329—Electronic Music Learning Projects...\$6.25.** A beginner's book that will assist you in assembling such projects as the Elexylophone, Gildaphone, Melody Ranger, Cordmaker, Appealing Handbells, Electronic Sol-Fa, Tune-up Box and more.



**BP319—Making MS-DOS Work for You...\$6.50.** What you need to know first, comes first, however the text is written in a circular style so that the reader can start anywhere in the text. This book is relevant to all versions of both MS-DOS and PC-DOS.



**BP303—Understanding PC Software...\$6.95.** Covers main types of PC software, giving details of typical uses, the basics of how they are used and their limitations. Each chapter covers popular software and programs of a similar type.



**BP105 Aerial (Antenna) Projects...\$5.50.** In this book the author has considered practical antenna designs, including active, loop and ferrite antennas which perform well and are relatively simple and inexpensive to build. The complex theory and mathematics of antenna design have been avoided. Also included are construction details of a number of antenna accessories including a pre-selector, attenuator and filters.



**BP33—Electronic Calculator Users Handbook...\$5.75.** The book eliminates the mysteries of the calculator and offers unique ideas for the simplest to most complex calculators. Covers the basic functions plus trigonometric, hyperbolic, logarithms, square roots and powers. Included are formulas and data for VAT, discounts, and mark up, currency conversion, interest, binary and octal numbers, and much more!



**BP125—25 Simple Amateur Band Antennas...\$5.50.** Plans to build antennas that are simple and inexpensive to construct and perform well. From the simple dipole to beam, triangle and even mini-rhombic types made from four TV masts and about 400 feet of wire. After the antenna discussion you will find a complete set of dimension tables that will help you "tune" an antenna on a particular frequency.



**BP263—A Concise Introduction to dBASE...\$6.95.** The most popular data-base program, dBASE, is difficult to master without help. This book helps you spend your time using dBase, not setting it up. A user's guide that covers all the basics up to dBase IV.



**PCP104—Electronics—Build and Learn...\$9.95.** Construction details are given to build a circuit demonstrator that is used throughout the book to introduce common electronic components and how these components are built up to useful circuits.



**BP302—A Concise User's Guide to Lotus 1-2-3 Release 3.1...\$6.25.** Written to help existing spreadsheet users upgrade to 1-2-3 Release 3.1, which has the ability to work 3-dimensionally with both multiple worksheets and files.



**BP146—The Pre-BASIC Book...\$6.95.** Another book on BASIC but with a difference. It concentrates on introducing technique by looking in depth at the most frequently used and more easily understood computer instructions.

## Just What the Project Builder Is Looking For!

- |   |  |
|---|--|
| <input type="checkbox"/> #160—Coil Design and Construction Manual .....\$5.95           | <input type="checkbox"/> 1596T—24 Silicon-Controlled Rectifier Projects.....\$9.95 |
| <input type="checkbox"/> #219—Solid State Novelty Projects .....\$4.95                  | <input type="checkbox"/> BP58—50 Circuits Using 7400 Series ICs .....\$5.50        |
| <input type="checkbox"/> #222—Solids State Shortwave Receivers for Beginners.....\$5.50 | <input type="checkbox"/> BP69—Electronic Games.....\$5.50                          |
| <input type="checkbox"/> #223—50 Projects Using IC CA3130.....\$5.00                    | <input type="checkbox"/> BP71—Electronic House Projects .....\$5.00                |
| <input type="checkbox"/> #225—Practical Introduction to Digital ICs.....\$5.25          | <input type="checkbox"/> BP84—Digital IC Projects.....\$5.50                       |
| <input type="checkbox"/> PCP111—Electronic Test Equipment Handbook.....\$13.95          | <input type="checkbox"/> BP93—Electronic Timer Projects.....\$5.50                 |

**ELECTRONIC TECHNOLOGY TODAY INC.**  
P.O. BOX 240, Massapequa, NY 11762-0240

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_  
PE5 Allow 6-8 weeks for delivery

**SHIPPING CHARGES IN USA AND CANADA**  
\$0.01 to \$5.00 .....\$2.00  
\$5.01 to \$10.00 .....\$3.00  
\$10.01 to 20.00 .....\$4.00  
\$20.01 to 30.00 .....\$5.00  
\$30.01 to 40.00 .....\$6.00  
\$40.01 to 50.00 .....\$7.00  
\$50.01 and above.....\$8.50


**SORRY No orders accepted outside of USA & Canada**

Total price of merchandise ..... \$ \_\_\_\_\_  
Shipping (see chart) ..... \$ \_\_\_\_\_  
**Subtotal** ..... \$ \_\_\_\_\_  
Sales Tax (NYS only)..... \$ \_\_\_\_\_  
**Total Enclosed** ..... \$ \_\_\_\_\_

**All payments must be in U.S. funds!**
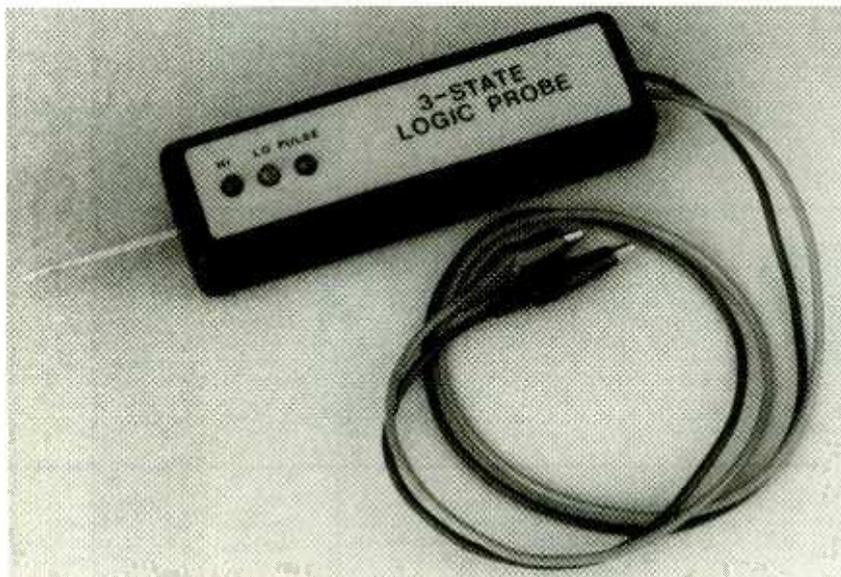
# Build A Logic Probe

*Here's a useful device that every hobbyist needs on their workbench.*



If you enjoy experimenting with digital electronics, or work with such circuits professionally, you are probably well aware of the value of logic probes. These test instruments come in a variety of shapes, sizes, and price ranges, and can be as simple as a single transistor, configured as a switch, to systems employing several integrated circuits.

Widely regarded as the consummate digital diagnostic tool, a logic probe is a device that's prudent to keep on the work bench. Now, while commercial models are by no means prohibitive in cost, we find there's always satisfaction in building your own.

So, if you're ready to tackle the task, the *Logic Probe* described in this article is for you; the unit features a two-IC design that will indicate high, low, and pulse signals. It only takes about two hours to build the probe, and once you have it in hand, you'll no doubt be pleased you made the effort.

**Circuit Description.** The schematic diagram for the Logic Probe is shown in Fig. 1. A test signal is introduced to the input of one of six inverters in a

BY CARL J. BERGQUIST

74LS04 chip (IC1). This inverter, IC1-a, inverts the signal, and sends it to three additional sections: the inputs of IC1-b and IC1-c, and the enable input, pins 3 and 4, of IC2.

The output of IC1-b goes to the cathode of LED1, the "low" indicator; the anode of LED1 is tied to the +5-volt supply. Meanwhile, the output of IC1-c is sent to the input of IC1-d, and IC1-d's output is connected to the cathode of LED2, which indicates a "high" signal. There, the anode of LED2 is pulled high, through a dropping resistor (R2).

The final stage of the Probe employs a 74121 monostable multivibrator, IC2, which is used to detect a pulsing input. In this application the input signal acts as a trigger, while the negative output, pin 1, is tied to the cathode of LED3. Note that LED3's anode is also connected to the positive voltage supply.

In each stage, the output has to be low for the respective LED to light, so, let's take a look at how this is achieved. When a low signal is introduced to the probe, IC1-a inverts this to a high, and IC1-b

inverts it back to a low. Applying this low to the cathode of LED1, lights the diode.

In the case of a high signal, IC1-a inverts it to a low, IC1-c changes the signal to a high, and IC1-d inverts it back to the needed low. This in turn illuminates LED2.

When the input is a pulse, multivibrator IC2 detects this, and activates its outputs for a time constant set up by C1 and R4. The negative or "not Q" output, pin 1, then lights LED3. The indicated values of C1 and R4 are chosen to keep the time constant short, which results in a rapid set/re-set action. With some help from persistence of vision, LED3 appears to be "on" continuously.

So, as can be seen, this is really a very simple system. Simple, yet effective in determining the status of digital signals.

**Construction.** The author's prototype for the Logic Probe was built on a printed-circuit board, though most any form of assembly can be used. If you'd like to build the circuit on a PC board, a full-size template of the board is available in Fig. 2.

For those building the circuit on a PC board, a parts-placement

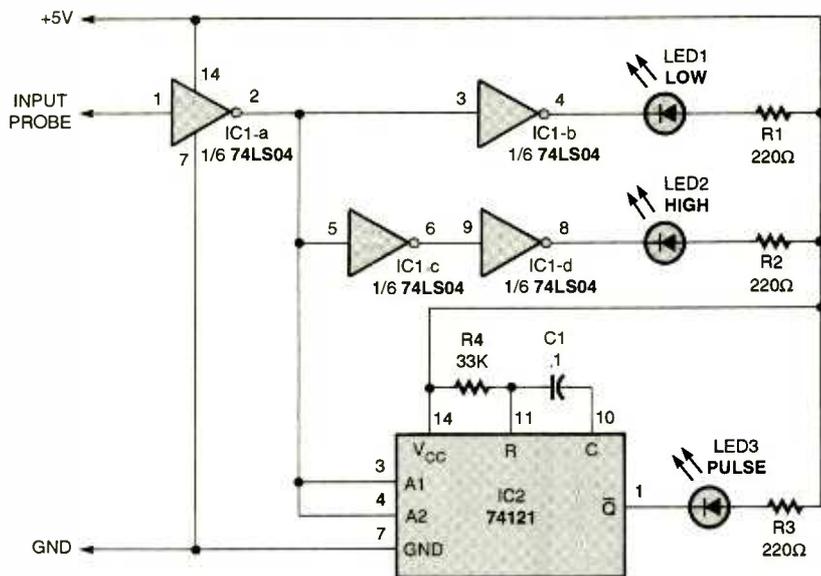


Fig. 1. As the schematic for the Logic Probe shows, this two-IC design provides an extremely low parts count.

diagram is shown in Fig. 3. If you don't use a PC board, be sure to ground the inputs of the unused inverters (pins 11 and 13). This is done to reduce power consumption and prevent the circuit from picking up extraneous noise.

The use of IC sockets, for IC1 and IC2, is not essential, but highly recommended; these should go on the board first. Then install the resistors and jumpers.

Solder the LEDs to the board next, making sure they are oriented properly. Mount the base of each

LED  $7/16$ -inch off the board. This will make it possible to use the enclosure mentioned in the Parts List. In this design, the LEDs are three different colors, with red indicating "high," green representing "low," and orange signifying "pulse."

Next, connect 24-inch lengths of red and black probe wire to the +5V and GND PC-board pads, respectively. Solder small alligator clips to the opposite ends *after* the leads are run through the proper holes in the case. As with most logic probes, this unit is powered by the circuit under test, and these leads will provide the positive and ground/negative connections.

Finally, connect a short section of wire from the input pad to the probe tip. The tip can be fashioned from a variety of materials, but the prototype uses a  $1\frac{1}{2}$ -inch "common" iron nail. Once the electrical connection is made, you'll have to secure the nail with epoxy to whatever case you'll use.

As for the case, it can be whatever is on hand. The author's prototype uses the housing from a surplus remote control (see the Parts List), and the foil pattern is customized for this case. However, a variety of different enclosures can be used, with little, or no, modification to the board.

Once the case has been selected, simply, drill holes for the LEDs, power leads, and probe tip. Label the high, low, and pulse diodes, with dry-transfer lettering. Mount the circuitry and remember to connect those alligator clips. You're now ready to proceed to the testing phase.

**Checkout and Use.** Before installing the integrated circuits, connect the red and black alligator clips to +5 volts and ground. Check

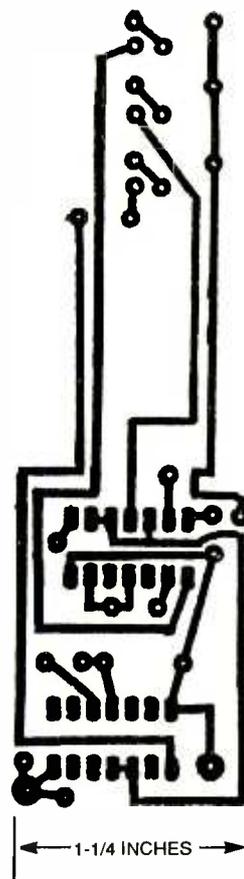


Fig. 2. Here's a full-size template for the Probe's PC board.

pin 14 of the sockets for both IC1 and IC2; make sure they have the proper voltage. If all is well, disconnect the power, install the ICs (observing proper orientation), and close up the case. The unit is ready for use.

To use the Probe, merely determine the +5-volt source and ground of the circuit to be tested, and attach the alligator clips. Now,

when you touch the tip to any point within the circuit, the LEDs will indicate the logical status of that point.

At power up, the high LED (LED2) will light; this is normal. If you place the probe tip on a test point, and there is no change in the LEDs, you have a high signal. When there is a low present, the low indicator (LED1) will illuminate, and LED2 will extinguish.

For pulsed inputs, a slow pulse, say one or two hertz, will result in the high LED staying on constantly, while the low and pulse LEDs flash in sequence with the signal swinging from positive to negative, and back. With fast pulses, the high will, again, remain on, and there will be a slight glow to the low LED, and a bright glow to the pulse indicator. A point to remember is that the pulse LED will not react unless a pulsing

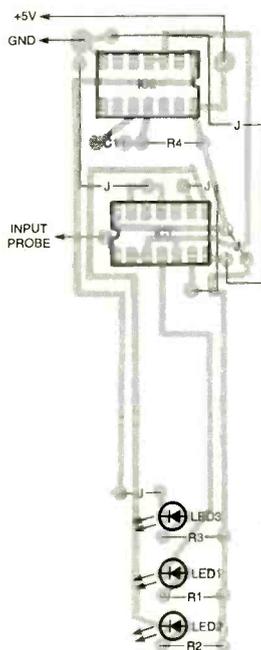


Fig. 3. If you're building the Probe on a PC board, use this parts-placement diagram as a guide.

signal is encountered.

If you have never used a logic probe, you'll be amazed at how handy this little test instrument can be. If you have used one, then you'll appreciate how well our Logic Probe performs. Building this project is well worth the time, materials, and effort required, as the Probe can quickly diagnose many seemingly difficult problems. With a little practice, you'll be able to analyze the operation of any digital device; a process extremely helpful in pinpointing trouble.

Additionally, the design easily lends itself to modification. For example, instead of standard LEDs, you can hardwire small, seven-segment displays to read "H," "L," and "P," or you could add audio annunciation. But even "as is," we're sure you'll be using your Logic Probe quite often. ■

## FORCE FX JOYSTICK

(Continued from page 26)

tude on one or both axes. A game developer would use the vibration command for simulating the feel of driving over rough terrain or the hum of an airplane engine. The command's parameters are magnitude, direction, and frequency.

The buffeting command is similar to the vibration command, but varies the direction and magnitude simultaneously. The sensation is similar to what you expect when flying a plane through turbulence.

The vector force command outputs a force of a given magnitude on a given axis. Its parameters are magnitude and direction. It's a basic command, but it can create a wide variety of force sensations such as g-forces when a plane makes a tight turn, strong cross-winds while flying, or driving into a wall at an angle.

More than one force effect can be active simultaneously, so for example, if you were to get blasted from the left and behind simultaneously, you would be able to feel both effects. By varying the magnitude of the effects, and by combining them in different ways, game developers can create a virtually unlimited variety of effects.

I-Force allows force effects to be generated with little burden on the game or

other host application because the joystick contains an on-board microcontroller. It receives only high-level commands from the host PC, and then produces all force-feedback effects independently. For example, the host computer might request the high-level command Vibration and specify the magnitude, frequency, and duration.

Immersion's I-Force force reflex is an automatic reaction that occurs on the joystick and does not require any supervision by the host. Those reflexes can be configured by the host to allow for custom force effects, but once set up, the host hands all responsibility for those force reflexes over to the on-board microprocessor for extended periods of time. The end result is that game play is just as fast as with a standard joystick.

With I-Force, many reflexes can be pre-programmed on the joystick, and they will remain active during game play. Reflexes can be modified or disabled at any time to allow the joystick to react appropriately as game conditions change.

Another powerful feature of the I-force architecture is the ability to download "Force Feedback Profiles" to the stick. The profiles allow custom force effects to be created by both game developers and game players. A utility supplied with the joystick setup software provides a way to experi-

ment with different effects. A developer who has designed a game with some new super weapon can make it have a signature feel when it is fired—say, a subtle vibration followed by a substantial kick to the left. The custom force profile can be downloaded to the joystick, and called with a simple instruction.

Installing the joystick is a rather simple affair. Its basic requirements are a PC with a 386 or better processor, a gameport, and—because two-way communication is essential—an available serial port. Because the joystick has two internal motors that create the feedback forces, it requires connection to a power supply as well.

The stick features two 4-way switches, five fire buttons, a trigger, and trim controls. It's completely backward-compatible with all the games for which you currently use a joystick. Even better, it allows you to add some effects to your existing non-feedback games. A LOADFX utility supplied with the joystick allows game players to get limited effects by programming the stick directly with custom effects.

When done right, force feedback makes game play compelling even for people who usually don't like playing games. Unlike other joysticks that have crossed our desks, this one is staying connected—we have no plans to unplug it anytime soon. ■



# LAND WARRIOR

*Learn how technology is helping ensure our foot soldiers will come home safely.*

BY BILL SIURU

It is the year 2003. Sergeant Comfort is on a peacekeeping patrol in a Middle Eastern country. Moving through hostile territory in near total darkness he can spot possible trouble through the Monocular Night Vision Sensor mounted on his helmet. Glancing in another direction he views another helmet-mounted display showing infrared images from the Thermal Weapon Sight (TWS), or pictures from the video camera mounted on his M4/M16 rifle. Clicking another control, he calls up a detailed digitized map on the display from the computer worn on his back. His precise position is pinpointed on the map by a Global Positioning System (GPS).

While patrolling he receives a call from another squad member,

Corporal Best, over his Squad Radio. Best has spotted the location of a sniper who has fired a few shots at him. Not wanting to expose himself to fire at the sniper, Best "passes off" the target location determined by Best's weapon-mounted Laser Rangefinder/Digital Compass to Sergeant Comfort. Comfort locates the target on his display and fires a couple of rounds at the designated target. Even though he never sees the sniper, Comfort silences him.

In our little futuristic scenario, Comfort and his platoon are operating in dangerous territory. But soldiers like them will probably be confident that they will return safely from patrol. That is because these soldiers of the future will be equipped with the Land Warrior

System that will be issued to U.S. soldiers around the year 2000. The Land Warrior System is currently being developed for the U.S. Army Soldier Command in Natick, MA by lead contractor Hughes plus Motorola, Honeywell, Battelle, Gentrex, Arthur D. Little, and several other subcontractors.

**An Integrated Approach.** While soldiers have used thermal sensors, laser rangefinders, computers, night-vision equipment, and other advanced technologies for years, such devices were usually issued on a piecemeal basis. These anything-but-seamless bundles of technology added immensely to the soldier's workload (especially under the stress of combat), not to mention that they greatly increased the physical load he had to carry. All that is about to change.

The Land Warrior System is the first totally integrated, high-tech "fighting system" for the foot soldier.



*This soldier is equipped with the Land Warrior System. A computer, radios, GPS receiver, antennas, and batteries are carried in a compact backpack.*

It integrates the latest in communications, sensor, computer, and materials technologies, as well as, wherever possible, off-the-shelf and commercial hardware to keep costs down.

**The Framework.** Physical damage is a main concern for a foot soldier. For this reason the Land Warrior System will feature a Protective Clothing and Individual Equipment Subsystem (PCIE) featuring modular body armor plus clothing, gloves, boots, and other similar items for protection against head-to-toe chemical and biological warfare. The PCIE is the platform that integrates all the pieces of the Land Warrior System.

A main component is the Load Carrying Equipment (LCE), which features a flexible frame allowing it to fit and function like part of the body. The unique design means one frame size fits all soldiers from the 5th to 95th percentile body size. The LCE's design allows redistribution of the load between the shoulder and waist to improve comfort even while the soldier is on the move. This frame serves as the support structure for the back-mounted Computer/Radio Subsystem.

Another great feature of the LCE

is that various packs can be quickly attached to it for different missions; a soldier can therefore plan ahead for varying degrees of assault. Soldiers can even rapidly shed bulky components in an emergency. The frame and LCE also houses and protects the integrated wiring harness that ties together all the electronic hardware.

**Heads Up.** As hinted in the scenario at the beginning of this article, another key component of the Land Warrior System is the Integrated Helmet Assembly Subsystem (IHAS). Beside providing head protection, the open face helmet supports detectors, sensors, and displays. A microphone is integrated into the chinstrap and speakers are built into the helmet suspension system.

The helmet's design truly makes a soldier's time in the field easier. For starters, the helmet is made of lightweight materials to keep its weight down. Designers decided to go a step further, though, and added the unique suspension to provide a stable platform for the optical devices attached to it.

These optical devices include a Monocular Night Vision Sensor for 60 degrees field-of-view under nighttime conditions. The helmet's flat panel display presents images from the video camera and Thermal Weapon Sight mounted on the soldier's weapon; there are also four laser detectors located on the helmet that provide the back-mounted computer with a 360-degree "field-of-view." All these devices can be used even when NBC (nuclear/biological/chemical), BLEEP (ballistic/laser eye protection), and other types of protective gear are donned.

**Computer Backbone.** As mentioned, the Land Warrior is based on a back-mounted computer. The Computer uses an IBM-compatible processor, PC-cards, and is setup for easy future upgrades. This backbone of the System controls various peripherals. Let's look at some of these.

First there's the Computer/Radio Subsystem (C/RS), which includes two radios: a Squad Radio for platoon-level communications and a Soldier Radio for communications with other soldiers within a squad. Both systems have the capability for both voice and data communications, are based on commercial Personal Communications Systems radio technology, and can have their communications encrypted for security.

Antennas for radios and the GPS are embedded in the load-carrying equipment frame. The very versatile C/RS also includes Mission Configurable Electronics and Removable Soldier Access and Mission Modules. Access to the computer and radios is via the Remote Input Pointing Device or a

*continued on page 52*



*Here are some typical video and digital map displays available on the Land Warrior helmet-mounted display.*

**A**re your squarewaves really "square?" Does your pulse train have the proper on/off ratio? The only way to be sure of the answers to such questions when working with a waveform is to measure its duty cycle.


An accurate measurement of a pulse train's duty cycle, or mark/space ratio, is usually a tedious matter. First the period of the train must be measured along with the pulse width, and then the duty cycle must be calculated using those figures. Generally, an oscilloscope or a frequency counter incorporating time-period capability is required to do this.

If you have struggled with these techniques, you can put away your oscilloscope or counter and build the Duty-Cycle Monitor described in this article. It's simple enough to assemble in one weekend. This is a stand-alone instrument that displays a real-time duty-cycle reading of 0% to 100% on its built-in analog meter.

Using a 100-microamp-meter movement allows a direct reading of the duty cycle without using a multiplier (for example, a 45 microamp reading indicates a 45% duty cycle). The circuit is accurate to within 1% of full scale over the range of about 30 Hz to 100 kHz or higher, within an input voltage range of +1.5 to +15 volts, which covers most logic families. Maximum input voltage should be restricted to  $\pm 50$  volts peak. The input impedance is about 100,000 ohms, so circuit loading is not a problem.

**Circuit Description.** As you can see on the schematic diagram (see Fig. 1), the circuit is extremely simple, utilizing only two ICs and a handful of passive components. Power is obtained from a standard 9-volt battery, B1. Current drain is limited to about 10 to 15 milliamps total. The circuit is based on old-style, automotive "dwell meters," which performed a similar function at lower frequencies.

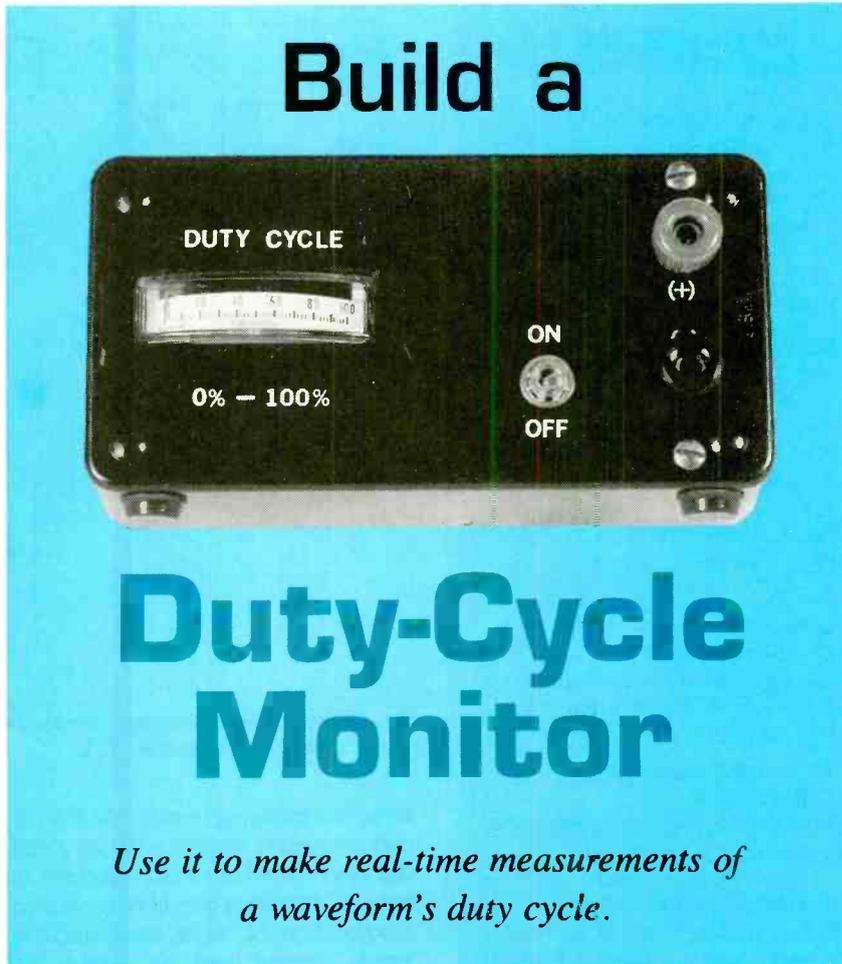The input pulses are applied to IC1, an LM319 dual comparator, via R1, with C1 providing the necessary compensation for the capacitance appearing at the inputs of IC1. You may elect to adjust C1's value slightly to



display even higher frequency ranges. A yellow LED (LED1) provides input overvoltage protection and sets the minimum input level. Diode D1 provides reverse polarity protection for the comparators, while D2 and D3 supply the 1.3-volt threshold reference to IC1's inputs.

The comparator outputs drive display-meter M1 in a push-pull fashion. In other words, while IC1-a is high, IC1-b is low, thus completing the circuit through the meter. When the outputs are in the inverse state, D4 prevents current flow through the meter. The output pulse follows the input pulse timing exactly; therefore, when the input pulse goes high, M1 conducts for the pulse duration at its full-scale rating of 100 microamperes. When the input pulse goes low M1 is not conducting any current.

This on/off current through M1 is averaged by the inherent "damping" of the mechanical meter movement. As a result, M1 responds linearly with the input waveform's duty cycle. A stable display of the duty cycle appears

at frequencies above 30 Hz, while lower frequencies cause the meter needle to oscillate (with a swing determined by the damping effect that's caused by the torque required to move the needle).

The meter used in the prototype was a high-torque type that gave superior low-frequency stability down to 10 Hz. However, this higher damping itself causes small errors to appear: When calibration is done at a 50% duty cycle, signal displays below 50% d.c. "lag" and signal displays above 50% d.c. "lead." For example, an input at 10% d.c. reads between 9% to 10%, and an input of 90% d.c. reads between 90% to 91% duty cycle. If you are more interested in ultimate accuracy, use a low-torque meter movement. This is one case where the less expensive (low-torque) meter might be a better choice, if it has good DC linearity!

A LM78L05 voltage regulator, IC2, supplies +5 volts to IC1, and assures calibration stability within the limits of the circuit. Resistors R4 and R5 prop-

## PARTS LIST FOR THE DUTY-CYCLE MONITOR

### SEMICONDUCTORS

IC1—LM319 dual comparator, integrated circuit

IC2—78L05 5-volt regulator, integrated circuit

D1—D4—1N4148 silicon diode

LED1—Light-emitting diode, yellow

LED2—Light-emitting diode, red

### RESISTORS

(All fixed resistors are 1/4-watt, 5% units.)

R1—100,000-ohm

R2—22,000-ohm

R3—50,000-ohm trimmer potentiometer

R4, R5—1000-ohm

R6—3900-ohm

R7—2700-ohm

### CAPACITORS

C1—10-pF, ceramic-disc

C2, C5—0.1- $\mu$ F, ceramic-disc

C3—1- $\mu$ F, 16-WVDC, electrolytic

C4—10- $\mu$ F, 16-WVDC, electrolytic

### ADDITIONAL PARTS AND MATERIALS

M1—0- to 100-microampere analog panel meter

S1—SPDT toggle switch

B1—9-volt alkaline battery

Perforated board, enclosure, binding posts, battery connector, 22-gauge stranded insulated wire, hookup wire, solder, hardware, etc.

erly load the comparator outputs so that their rise and fall response times match within about 50 nanoseconds, thus assuring linear high-frequency response.

**Construction.** Before you begin assembling the Duty-Cycle Monitor,

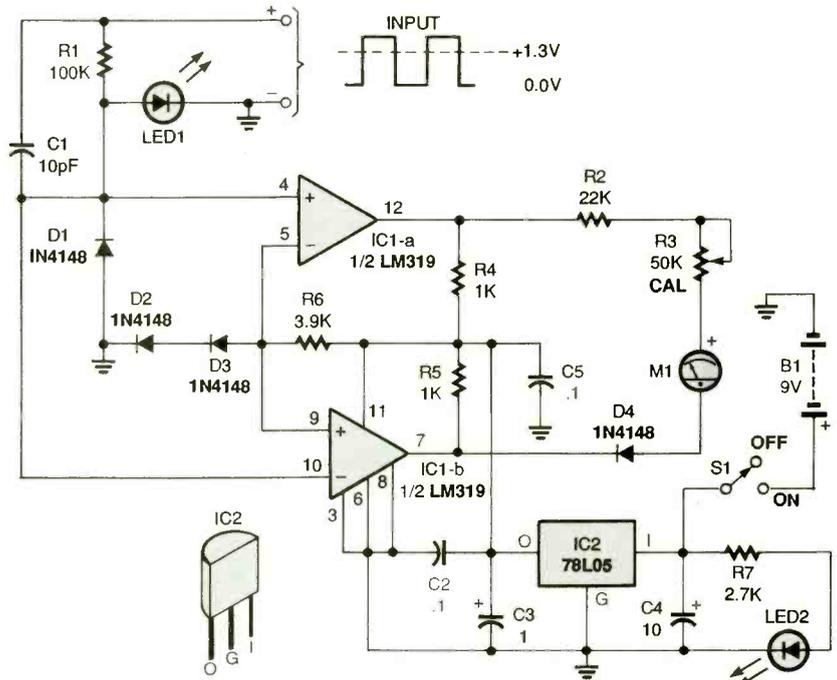


Fig. 1. This is the schematic for the Duty-Cycle Monitor. Note the three-dimensional pinout of the 78L05 regulator, IC2.

keep the following in mind: As this circuit processes signals with very fast rise and fall times, it is important to keep signal leads relatively short and isolated from DC leads. Also, keep the inputs isolated from the outputs, including the meter. The input leads to the binding posts can be standard clip leads about 12- to 18-inches long, terminated with banana plugs.

Begin assembly by dry fitting the panel meter and battery (in its holder) in your enclosure to estimate how much you will need to cut down your PC board for a good fit. The size of the meter you select will determine the actual enclosure you can use: the author's prototype was built in a 2½- ×


5½- × 1½ plastic cabinet to house the meter. The perforated board used in the assembly was cut to 1¾ × 2¼ inches, which allowed more than ample room for the board circuitry. With a larger cabinet, you may not have to cut down your board.

Once you have the board sized, locate and drill or punch two mounting holes in the corners of the board. Using the board as a template, scribe the holes in the cabinet at its appropriate mounting location and set the cabinet aside.

Install a 14-pin DIP socket for IC1 in about the center of the board. Then mount IC2 and add the remaining components, except for the binding posts (the + and - open input circles), S1, LED2, R7, and M1, making the connections illustrated in the schematic diagram. Using 22-gauge stranded hookup wire, connect 6-inch leads to the board as follows: two wires for the signal input, two wires for the output, and two wires for the power input. Install IC1 in the socket and set the board aside.

Lay out and cut the hole in the cabinet for the meter, along with its mounting holes. Locate and drill the mounting holes for the binding posts, power switch, and LED2. The author's prototype had these four compo-

(Continued on page 52)

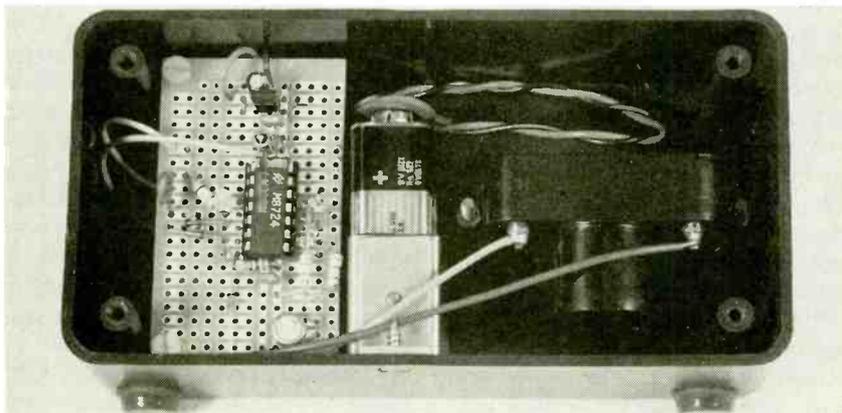

As you can see, a nice and neat assembly is possible using perforated board building techniques.

# The Electronics Industry is looking for a lot of good people!

Here is your chance to get in on the ground floor as an Associate CET. Is your job title "Electronics Service Technician?" Would you like to have that title? You can prove you qualify for the title with a CET Associate Certificate. It can be your career door-opener and begin your rapid advancement!

A technician or student of electronics with less than a total of four years of basic experience may take the Associate Level Exam. The exam is the basic electronics portion of the full-credit CET exam. The 75-question, multiple-choice test covers basic electronics, math, DC and AC circuits, transistors and semiconductors, instruments, measurements and troubleshooting. A successful Associate CET will receive a wall certificate valid for four years and is eligible to join ISCET as an Associate Member. ISCET is the International Society of Certified Electronics Technicians.

The ISCET Computer-Aided Associate-Level Study Guide prepares you for the Associate CET Certificate by randomly selecting sample questions with appropriate diagrams, provides multiple-choice answers, grades the test and provides a summary of your strong and weak points.

Diskette requires IBM computer or compatible with VGA color monitor, 3.5-in. drive and a hard-disk drive.

**CLAGGK INC. - CET Computer-Aided Study Guide Offer**  
**PO Box 4099, Farmingdale, New York 11735**

**YES**, I want to step up to a career in servicing. Here is my order for the CET Computer-Aided Study Guide on a 3.5 diskette. I am enclosing \$39.95 (price includes shipping and handling charges) in U.S. funds.

Bill my  VISA  MasterCard Expire Date \_\_\_/\_\_\_/\_\_\_  
 USA Bank Check  US or International Money Order

Card No. \_\_\_\_\_

Signature \_\_\_\_\_

Name (Please Print) \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

New York residents add local sales taxes. Canadians add \$6.00 per order. No foreign orders. Do not send cash. Checks drawn on US Bank and International Money Orders in US funds only. Credit card users may telephone or FAX orders. Telephone 516-293-3751 or FAX 516-293-3115. Price subject to change. Allow 6 to 8 weeks for delivery.

CB06


## Proof Positive that you are a Certified Electronics Technician



**A New**
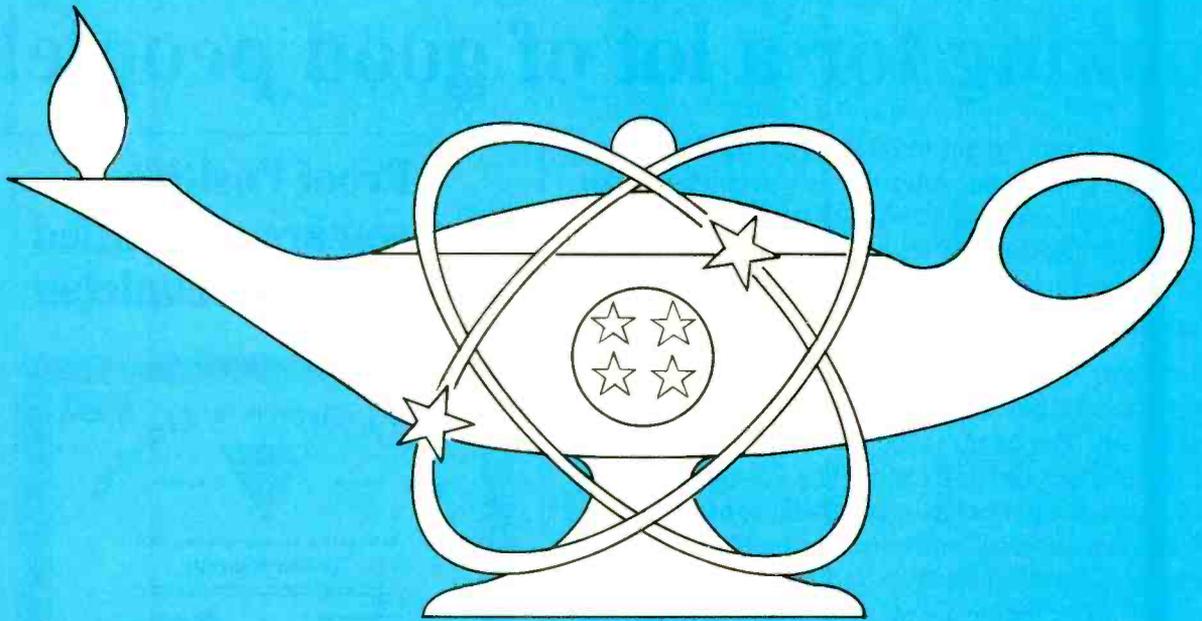
### Computer Software Program — ISCET Computer-Aided Associate-Level Study Guide

Prepare yourself for the 75-question CET Associate Examination. Model examinations provide the technician with a study program and introduction to the actual examinations. The model examinations are automatically graded in decimal numbers and bar graphs that can be outputted on your printer. The questions for each exam are selected randomly from a loaded data base—no two exams are exactly the same. When you answer a question, the correct answer is displayed and an explanation is given. From the print-outs you will determine whether you need more practice and in which topic areas, or if you are ready to take the real test and continue to promote your electronics career today!



# NATIONAL ELECTRONICS TECHNICIANS DAY

*A day to honor those electronics professionals that have demonstrated their mettle—  
and an opportunity to join their ranks*

More than ever, electronics touches nearly every aspect of human activity, and its influence is expanding at a near explosive rate. For example, the latest innovations in banking, business, communications, entertainment, finance, industry, medicine, military systems, and transportation all center around electronics devices and systems, and most of those make extensive use of microprocessors or microcontrollers.

That's also true of the products each of us use every day. Increasingly, cars, cameras, dish-washers, refrigerators, telephones, and TVs—to mention but a few—make use of microprocessors or some other type of "intelligent"

**BY BARBARA RUBIN**  
ISCET Director of Member Services

controller. And the personal computer is fast becoming a standard appliance in many households. With the increasing popularity of the Internet, that's a trend that is likely to continue.

All of that creates a tremendous opportunity for those with an affinity for electronics. The combination of a growing worldwide demand for electronics products, and the rising complexity of those products and systems, has increased the demand for professionals trained in developing, integrating, maintaining and repairing high-tech hardware.

Expert electronics technicians participate in the development, prototyping, and testing of new products. They also integrate and maintain all kinds of electronics systems and networks. And they are the people you call when today's generally reliable electronics products malfunction or fail. Their years of professional training and experience permit them to make needed repairs in a timely and economical manner.

In recognition of the skilled electronics technicians of the world, the International Society of Certified Electronics Technicians (ISCET) has proclaimed April 22, 1997 as International Electronics Technicians Day. In addition, the

entire week of April 20 through April 26, has been set aside as a National Testing Week for technician certification.

ISCET's professional certification of electronics technicians has been recognized internationally for more than 32 years; possession of ISCET certification indicates that the holder has met the highest professional performance standards. The voluntary certification program also helps employers to differentiate between qualified applicants and those with less training and skills.

So far, more than 150 ISCET Certification Test Administrators have volunteered to serve during National Testing Week. They will offer CET, CAT, and FCC testing from April 20 through April 26. A complete list of test sites (including **Popular Electronic's** editorial offices in Farmingdale, NY) are presented elsewhere in this article.

**CET, CAT and FCC Exams.** A wide range of CET, CAT and FCC examinations are now available through ISCET. To become fully certified by ISCET, an electronics technician must have at least four years of formal electronics training and experience. In addition, the demanding criteria for certification requires technicians to be knowledgeable in both fundamental electronics and the more advanced theory applicable to their specialty. To demonstrate that, he or she must pass both a 75-question Associate test, covering basic electronics fundamentals, and a 75-question Journeyman test, covering the applicant's area of specialization. The passing grade for each of the multiple-choice exams is 75%. An electronics technician or student with less than four years of experience may apply for Associate-level certification.

The Associate exam requires a broad knowledge of electronics plus the ability to analyze and troubleshoot circuit problems. The basic subjects on which the candidate will be examined include: electronics math, DC and AC circuits, transistors and semiconductors, elec-

tronic components, instruments, tests and measurements, and troubleshooting. A technician may also use an Associate exam issued by the Electronics Technician Association (ETA) to qualify to take one of the Journeyman Options.

Individual Journeyman exams focus on many different electronic specialties. The present set includes:

• **Audio**—The questions cover amplifiers and sound quality, system integration, speaker installation, servicing audio products, and troubleshooting audio systems. The exam includes questions on both digital and analog audio.

• **Communications**—The questions address communications circuits and transmission systems, AM and FM transmitters and their adjustment, receiver adjustment, and the servicing and troubleshooting of systems.

• **Computers**—The questions cover binary mathematics, logic gates, the basics of digital electronics and computers, local-area network organization, input and output peripherals, memory, elementary programming, and the troubleshooting of computer systems.

• **Consumer**—The questions cover both digital and analog circuits in consumer electronics products. There are, for example, specific questions on the troubleshooting and servicing of televisions and VCRs, and the operation of applicable service test instruments.

• **Industrial**—The questions cover DC and AC power supplies, transducers, sensors, switches, differential amplifiers, logic circuits, analog and digital circuitry, microprocessors and computer systems, and circuit analysis and troubleshooting of industrial electronic systems.

• **Medical**—The questions cover the principles of electrical safety, basic circuitry, the operation of electronic test instruments, telemetry, and the calibration of typical biomedical instrumentation.

• **Radar**—The questions cover both pulse and continuous-wave radar operation, radar transmitters and receivers, CRT display systems,

radar power supplies, antennas, and the principles of transmission lines.

• **Video**—The questions cover the basics of video, knowledge of NTSC standards, test-signal generation, the principals of video tape recording, VCR tape-drive mechanisms, camcorders, TV cameras and monitors, and the microprocessor as it applies to video.

ISCET is also in the process of developing specialized endorsements to the Journeyman Options that signify advanced expertise in a specific field. Endorsements presently available are VCR and Camera, Camcorder, 8mm, Endorsements will soon be available for Monitors, Data communications, FAX, and Cellular.

**CAT Testing.** CAT (Certified Appliance Technician) testing opens a whole new field for the trained and certified technician. Whether it's a microwave oven, washing machine, dishwasher, or air conditioner, it's likely to include electronic circuits—perhaps even a microcontroller. The appliance service technician who service that equipment must learn about electronics as well as learning how to make the electrical and mechanical repairs they have traditionally made.

The Certified Appliance Technician examination is independent of the CET Associate or Journeyman certifications. However, just as for the Journeyman CET option, four years of practical, hands-on experience are required. The CAT examination consists of 100 multiple-choice questions on such subjects as electrical circuits and components, basic electronics, and the operating principles and repair practices for appliances such as refrigerators, ranges, ovens, dishwashers, and trash compactors. Appliance technicians who pass the ISCET CAT are eligible to join ISCET.

**FCC Testing.** ISCET test administrators can give tests covering FCC elements 1, 3, 5, 6, 7, 8 and 9. Element 1 is Basic Radio Law and Operating practice. Element 3 is

## VOLUNTEER EXAMINERS

Cindy Johnson, CA  
280 West Vly Ave  
Birmingham, AL 35209  
(205) 916-2800  
Fax (205) 916-2807

David Bryan, CET, CA  
AL Aviation College  
Box 1209  
Ozark, AL 36360  
w-(205) 774-5113  
h-(205) 774-0163

Rt Van Iderstine, CET, CA  
14563 South Blvd  
Silverhill, AL 36576  
(334) 945-5942

Daniel McCann, CET, CA  
30949 Wellington Ct  
Spanish Ft, AL 36527  
(334) 633-4300, ext. 2047  
h-(334) 621-8163

Tony Jetton, CET, CA  
Wallace St College  
Box 2000  
Hanceville, AL 35077-2000  
(205) 352-8160

Roy Yonce, CA  
Box 723  
Bentonville, AR 72712  
(501) 273-9319  
(918) 865-2569

Dennis Blum, CET, CA  
8730 W Hazelwood  
Phoenix, AZ 85037  
Schemati@aztec.asu.edu  
(602) 872-8564  
(602) 279-9700  
Fax (602) 279-2999

HJ Paine, CET, CA  
4631 E 8th St  
Tucson, AZ 85711  
Kirshna@azstamet.com  
(520) 881-6784  
Fax (520) 795-1209

Jerry Mendoza, CET, CA  
4601 Lexington #111  
Los Angeles, CA 90029  
(213) 677-1732

Gerald Eggers, CET, CA  
Practical Schools  
900 E Ball Rd  
Anaheim, CA 92805  
(714) 535-6000

Don Winchel, CET, CA  
M & D Elect  
Box 123  
Smartville, CA 95977  
(916) 639-2477

David Marson, CET, CA  
Mac Doctor  
1040 W Kettleman  
Ln#1b339  
Lodi, CA 95240-6056  
Macdoc@calweb.com  
(209) 944-6191 ext. 6698

Michael Miller, Vo Instr  
St of CA-Dept of  
Corrcrts/CMC  
PO Box 8103  
Sio, CA 93403-8103  
(805) 547-7900, ext. 7143

Billy Edmonds, CET, CA  
1311-16th St  
Baywood Pk, CA 93402  
(805) 528-8523  
(805) 528-2513

Peter Moreno, CET, CA  
ITT Tech Inst  
630 E Brier Dr #150  
San Bernardino, CA 92408  
(909) 889-3800

John Craig, CET, CA  
531 W Hueneme Rd  
Oxnard, CA 93033  
(805) 982-5228

Howard Bardach, CET, CA  
13251 Ventura Blvd #D  
Studio City, CA 91604-1838  
(818) 995-8648

Parviz Shams, CA  
So Ca Inst of Tech  
1900 W Cresent, Bldg B  
Anaheim, CA 92801  
(714) 520-5552

Steven Thomas, CET, CA  
2306 Marilyn Ave  
Redding, CA 96002  
(916) 222-2541

Charles Trout, CET, CA  
563 N Fairview St  
Santa Ana, CA 92703  
(714) 836-4981  
Fax (714) 569-0204

Jon Sturtz, CET, CA  
10840 Alandale Way  
Rancho Cordova, CA 95670  
(916) 635-6000

George Shaiffer, CET, CA  
100 N Dartmouth  
Colorado Spgs, CO 80911  
(719) 540-7458  
Fax (719) 540-7453

Daniel Shea, CET, CA  
CT School of Elect  
586 Ella T Grasso Blvd  
New Haven, CT N6519  
(203) 624-2121

Alan Besore, CET, CA  
27 Centennial Ct  
Deerfield Bch, FL 33442  
(305) 360-7978

Robert Laquerre, CET, CA  
New England Inst of Tech  
1126-53rd Court  
W Palm Beach, FL 33407  
Boblaq@earthlink.net  
(561) 842-8324

Karl Hunter, CET, CA  
13850 Ketch Cv Dr  
Jacksonville, FL 32224-1143  
w-(904) 633-8143  
h-(904) 223-5289  
Fax (904) 633-8105

Dennis Abell, CET, CA  
3433 Royal Oak Dr  
Titusville, FL 32780  
(407) 269-4208

Dan Mundy, CET, CA  
Norman's Elect  
3653 Clairmont Rd Ne  
Atlanta, GA 30341  
71241.336@compuserv.com  
(404) 373-8037

Joe Reese, CET, CA  
Reese Elect Inc-Box 499  
301 South Main St  
Swainsboro, GA 30401  
Jreese@pinelani.net  
(912) 237-7010  
Fax (912) 237-7463

James Vansant, CET, CA  
Pickens Tech  
100 Pickens Tech Dr  
Jasper, GA 30143  
Jvansant@admin1.pickens1  
ec.ga.  
(706) 692-4500  
Fax (706) 692-4510

John Carolus, CET, CA  
Matsushita Scv Co  
1225 Northbrook Pkwy 2-  
380  
Suwanee, GA 30174-2933  
(770) 338-6875

Leonard Bowdre, CET, CA  
125 SE Thornton Ave  
Des Moines, IA 50315  
lebowdre@dmarc.cc.ia.us  
w-(515) 964-6484  
h-(515) 282-3028

Bruce Tietjen, CET, CA  
204 Northgate Mile  
Idaho Falls, ID  
(208) 523-5045

Paul R Trowblidge, CA  
Drive Controls Inc  
3232 Skokie Rd  
Highland Park, IL 60035  
(847) 433-0755  
(847) 662-1563

Eddie Lane, CET, CA  
1501 Honeysuckle  
Champaign, IL 61821  
w-(217) 333-1070  
h-(217) 356-6996

Fred Schwarzkoﬀ, CET, CA  
3708 W 83 Place  
Chicago, IL 60652  
(773) 767-4126 ext. 563

Paul Tan, CET, CA  
915 Augusta St #1  
Oak Park, IL 60302-1678  
(708) 848-6327

Don Williams, CET, CA  
Vincennes Univ/TB10  
1002 N First St  
Vincennes, IN 47591  
(812) 885-5801  
(812) 922-5670

Paul F. Maglinger, CET, CA  
901 Dover Ct  
Evansville, IN 47710  
Pmaling@c1techno1.com  
(812) 464-2523  
Fax (812) 421-2170

Richard Ackerman, CET, CA  
4107 Meader Bnd  
Indianapolis, IN 46268  
ack@indy.net  
(317) 876-7826

Christopher Smith, CA  
Purdue Univ-N Central  
1401 South US 421  
Westville IN 46391  
csmith@purdue.nc.edu  
(219) 785-5256  
Fax (219) 785-5539

Keith Knos, CET, CA  
Knos Elect  
1206 Elm Blvd  
Liberal, KS 67901  
(316) 624-5908

Stanley Creitz, CET, CA  
Rt. 4 Box 72  
Beloit, KS 67420  
Screitz@nckcn.com  
(913) 738-5095

Jesse Adkison, CET, CA  
Inst of Elect Tech  
509 S 30th St  
Paducah, KY 42001  
(502) 444-9676  
(502) 345-2061

Donald Johnson, CA  
Inst of Elect Tech  
509 S 30th St  
Paducah, KY 42001  
(502) 444-9679

John Hardin, CET, CA  
KY Tech-Ashland Campus  
4818 Roberts Dr  
Ashland, KY 41102  
(606) 928-6427  
(606) 329-7136

Jerry Sipes, CA  
Lexington Elect Inst  
3340 Holywyn Rd  
Lexington, KY 40505  
(606) 223-9608

Danny Keeton, CET, CA  
55 W Airview Dr  
Elizabethtown, KY  
(502) 769-6606  
(502) 769-8278

Edward Kimmel, CET, CA  
Kimmel Elect  
2061 Eastern Pkwy  
Louisville, KY 40204  
(502) 451-3457

Lamarr Ritchie, CET, CA  
Hazard Reg Tech Cntr  
101 Vo-tech  
Hazard, KY 41701  
hazrct@eastky.com  
(606) 435-8101  
Fax (606) 435-6088

Dr. I. F. Creel, CET, CA  
Sullivan Tech Inst  
1710 Sullivan Dr  
Bogalusa, LA 70427  
Fcreel@nl-inc.com  
(504) 732-6640  
(504) 839-2019  
Fax (504) 732-6603

Don Creech, CET, CA  
712 Ronson Dr  
Kenner, LA 70065  
(504) 467-4644

Frank Serra, CET, CA  
159 Mass Ave  
Arlington, MA 02174  
(617) 648-2430  
(617) 395-6304  
Fax (617) 648-2431

Robert Braunston, CET, CA  
RETS Elec Sch  
965 Commonwealth Ave  
Boston, MA 02215  
(617) 783-7197

Earl Tickler, CET, CA  
RETS Tech Trng Cntr  
1520 S Caton Ave  
Baltimore, MD 21227  
(410) 644-6400  
Fax (410) 644-6481

Richard Vigue, CET, CA  
Rt 1 Box 4150  
Oakland, ME 04963-9631  
(207) 465-2682  
(207) 873-0102

Electronic Fundamentals and Techniques Required to Adjust, Repair, and Maintain Radio Transmitters and Receivers. By passing both of those tests, the candidate will qualify for an FCC General Radiotelephone License.

The total gamut of FCC license exams include tests needed for a First Class Radiotelegraph Operator's Certificate (Telegraphy Elements 3 and 4 and written Elements 1, 5, and 6), Second Class Radiotelegraph Operator's Certificate (Telegraphy Elements 1 and 2 and written Elements 1 and 5), Third Class Radiotelegraph Operator's Certificate (Telegraphy Elements 1 and 2 and Written Elements 1 and 5), General Radiotelephone

License (Written Elements 1 and 3), Marine Radio Operator Permit (Written Element 1), GMDSS (Global Maritime Distress and Safety Systems) Radio Operator's License (Written Elements 1 and 7), and GMDSS Radio Maintainer's License (Written Elements 1, 3 and 9).

The FCC released its first question pool to examiners on September 6, 1993. The first technician to be FCC certified by IS CET was Antonio C. Gomez of Santa Isabel, Puerto Rico. All FCC Question Pools were upgraded at the beginning of 1995.

**In The Beginning.** IS CET was founded in 1970 by a committee of Certified Electronics Technicians.

Their main purpose was to foster respect and recognition for their profession. By maintaining the rigorous standards of its certification program, IS CET can identify and recognize highly skilled and knowledgeable technicians. Membership is open only to those technicians who have passed the Journeyman CET exam, the CAT exam, or the Associate CET exam.

In addition to receiving regular newsletters and magazines, members are informed about IS CET-sponsored conventions and technical-training seminars. Members also receive frequent updates on new technology, an annual directory of industry information, and many other valuable benefits available

## VOLUNTEER EXAMINERS

Gerald Heyn, CET, CA  
132 Blueberry  
Gwinn, MI 49841  
(906) 346-6396  
(906) 277-2926

Waiter Reilly, III, CET, CA  
5355 Wildoak  
E Lansing, MI 48823-7201  
(517) 485-1737  
Fax (517) 485-9555

John Thennes, CET, CA  
2102 10th Ave S  
Escanaba, MI 49829  
(906) 786-1413

Larry Geissler, CET, CA  
3706 Chambersburg  
Duluth, MN 55811  
(218) 722-9356

Michelle A. Stein, CA  
Moberly Area Vo Tech  
1625 Gratz Brown  
Moberly, MO 65270  
(816) 269-2690

William Tharp, CET, CA  
Grand River Tech Sch  
1200 Fair  
Chillicothe, MO 64601  
Grtech@vax2.rain.gen.mo.us  
(816) 646-3414

Marion Denny, CET, CA  
Rapid TV/Elect Repair  
1909-6th St  
Meridan, MS 39301  
(601) 485-8451  
Fax (601) 485-2102

Joseph Sloop, CET, CA  
Surry Comm Collg  
Dobson, NC 27017  
(910) 386-8121 ext. 301

Earl Fosler, CET, CA  
Rt. 2 Box D  
Milford, NE 68405  
efosler@sccm.cc.ne.us  
(402) 761-8266  
Fax (402) 761-2324

Anthony Baratta, CET, CA  
RETS Inst  
103 Park Ave  
Nutley, NJ 07110  
(201) 661-0600 ext. 30

Fred Freeman, Jr., CA  
550 Tabany Ave  
Henderson, NV 89015  
(702) 564-9163

Gregory Reiber, CET, CA  
9553 Bantry Rd  
Brewerton, NY 13029-6543  
(315) 668-9936

David Law, CET, CA  
Alfred St Collg  
221 Brown Hall  
Alfred, NY 14802  
Lawd@asc.edu  
(607) 587-3468  
(716) 593-4091  
Fax (607) 587-3291

Larry Steckler, EHF, CET,  
CA  
Gernsback Publications Inc.  
500 Bi-County Blvd  
Farmingdale, NY 11735  
lartronic@aol.com  
(516) 293-3000, ext. 2C1

Carl Meyer, CET, CA  
11 Hemlock Dr  
West Seneca, NY 14224  
(716) 835-6664

Christina Estrada, CA  
Gernsback Publications Inc.  
500 Bi-County Blvd  
Farmingdale, NY 11735  
(516) 293-3000, ext. 209

Hubert West, CET, CA  
20 Schuyler St  
Lake George, NY 12845  
Hwest789@concentric.net  
(518) 668-9285

Lawrence Delonais, CET, CA  
NEC  
1660 Martin Rd  
Mogadore, OH 44260  
(330) 923-9959

Joseph Carney, III, CET, CA  
Malthus Diagnosi  
35888 Center Ridge Rd  
N Ridgeville, OH 44039  
JoeCarney@aol.com  
(216) 327-2585  
Fax (216) 327-7286

James Shambow, CET, CA  
ITTES  
6035 NE 78th Ct  
Portland, OR 97218-2854  
(503) 255-6500

William Margut, CA  
Elect Inst  
19 Jamesway Plaza  
Middletown, PA 17057-4851  
(717) 944-2731

Gene Hedgepeth, CET, CA,  
CMAT  
Techtronics Svcs  
2165 Alberdeen Rd  
Moulaintop, PA 18707-9059  
(717) 868-6566  
Fax (717) 868-3444

Thomas Gaudiello, CET, CA  
Chi inst (RETS Campus)  
W Chester Pike/Malin Rd  
Broomall, PA 19008  
Tomg@inet.net  
(610) 353-7630

Thomas Plant, CET, CA  
ETG of Rhode Isl  
29 Dean St  
Pawtucket, RI 02861  
(401) 725-8719

Stanley Salter, CET, CA  
Stan Salter Music Svc  
826 Bay Blossom  
Sumter, SC 29150  
(803) 469-3022

Harry McCall, CET, CA  
280 Old Farns Bridge Rd  
Greenville, SC 29611  
(864) 294-0280

Don Multerer, CET, CA  
Sencore Inc  
3200 Sencore Dr  
Sioux Falls, SD 57107  
(605) 339-0100

Gordon Osthus, CA  
Lake Area Tech Inst  
Box 730  
Watertown, SD 57201  
(605) 882-5284

William Warren, CET, CSM,  
CA  
Warren Elect Syc  
2540 Sutherland Ave  
Knoxville, TN 37919  
WSWARREN@aol.com  
(423) 546-1128

Ronald Rackley, CET, CA  
TN Inst of Elect  
3203 Tazewell Pike  
Knoxville, TN 37918-2530  
(423) 688-9422  
Fax (423) 688-2419

Arthur Ruppert, CET, CA  
30217 St Andrews  
Georgetown, TX 78628  
(512) 863-9157

James Harris, CET, CA  
1505 Tanglewood Dr  
Harker His, TX 76548  
Harris@hood-  
emh3.army.mil  
(817) 698-2331  
(817) 526-1257

Gerald Martin, CET, CA  
Lucent Technologies  
107 W Nakoma  
San Antonio, TX 78216  
gimartin@lucent.com  
(210) 527-3347  
Fax (210) 527-3343

Gordon Davis, CA  
6934 Drowsy Pine  
Houston, TX 77092  
(713) 462-8764

Tom Underwood, CET, CA  
Tomtronics Inc  
10424 Remington Ln  
Dallas, TX 75229  
Tomund@aol.com  
(214) 357-0644

John Weaver, CA  
3334 Nonesuch Rd  
Abilene, TX 79606-1924  
Jweaver@tstc.edu  
(915) 698-5785

Earl Hines, CET, CA  
1710 Lamar Lot#2  
Sweetwater, TX 79556  
EHines@selib.tstc.edu  
(915) 235-1849

Dickie Lide, CET, CA  
TX St Tech College  
3801 Campus Dr, Bldg 7-05  
Waco, TX 76705  
(817) 867-4883  
Fax (817) 867-3631

Robert Griffin, CET, CA  
TCJC  
5301 Campus Dr  
Ft Worth, TX 76119  
(817) 531-4529

Henry Corrie, CET, CA  
1460 Cr 3413  
Chandler, TX 75758  
(903) 852-4140

Dick Kimberley, CA  
Salt Lake Comm Collg  
4600 S Redwood Fd  
Salt Lake City, UT 84130-  
0808  
(801) 957-4235  
(801) 280-9590

Charles Spiro, CET, CA  
Lord FairFax Comm Collg  
Box 47  
Middletown, VA 22645  
Cspiro@shentel.net  
(540) 869-1120  
Fax (540) 8697881

Ted Rodriguez, CET, CA  
Skagit Valley College  
2405 College Way  
Mt Vernon, WA 98273  
Rodriguez@skagit.ctc.edu  
(360) 416-7757  
Fax (360) 416-7843

Carl McDonald, CET, CA  
417 S 6th  
Sunnyside, WA 98344  
(509) 837-8800  
Jacob Klein, CET, CA  
Northcentral Tech Collg  
1000 W Campus Ave  
Wausau, WI 54401  
(715) 675-3331

David Bates, CET, CA  
Western WI Tech College  
304 N 6th St  
Lacrosse, WI 54602  
(608) 785-9290

Duane Busby, CET, CA  
BC&D Ent  
2027 Sherman Ave  
Madison, WI 53704-5934  
(608) 244-0339

Jeff Paschke, CET, CA  
1011 Jefferson St  
New London, WI 54961  
JPASC5871@aol.com  
(414) 982-3641

David Nida, CA  
NEC  
5514 Big Tyler Rd  
Cross Lanes, WV 25313  
(304) 776-6290

Richard Evans, CET, CA  
Box 217  
Wilkenson, WV 25653  
(304) 752-7267

Gary Memory, CET, CA  
American Embassy-Paris  
PSC-116 Rm# A314  
APO AE 09777  
33-1-47.53.82.55

Egon Strauss, CET, CA  
V. De Obligado 2376  
Buenos Aires  
Argentina 1428  
(541) 781-8564

Antonio M Avellanosa, CA  
MPITI  
Presan Bldg/Gen Luna Rd  
Baguio City  
Philippines 2600  
(74) 442-8170  
Fax (74) 442-6532

Julius Bissessar, CET, CA  
Quarry Vlg P.O.  
Quarry Vlg-via Siparia  
Trinidad/Tobago West Indies  
(809) 649-6127

only to members. ISCET members also receive access to the ISCET Web site, which can be found at <http://www.iscet.org>. At the annual National Professional Service Convention (NPSC), technicians receive the latest in advanced-technology training from knowledgeable, expert instructors.

The members are also invited to attend the annual ISCET membership meetings. During NPSC, some members are selected to participate in ISCET's Product Serviceability Program.

ISCET's main function is the direction and administration of the CET program, developed to measure the theoretical knowledge and technical proficiency of prac-

ticing technicians. Responsible industry executives recognize a technician with CET certification as one who possesses professional training, experience, and competence in his specialty area.

Since its creation in 1965 by the National Electronic Association, the CET program has been widely recognized by technicians, Government agencies, manufacturers, and consumers. Many electronics companies encourage their technicians to qualify for ISCET certification and some even require it. Almost technicians have proven their ability by earning the coveted ISCET certification.

**Exam Fees.** The fee for the CET

exam is \$50; that includes both the Associate exam and one Journeyman option. The fee for the Associate exam is \$30. If the Journeyman option is taken separately from the Associate exam, the fee \$35. The fee for the 100-question CAT exam is \$35. If a candidate fails any of these exams, the first retake is \$15 (one test) or \$25 (both tests), following a 60-day waiting period.

There is a different set of fees for the FCC exams, but the minimum fee is \$25 for one session. The fee for Element 1 is \$25, and the fee for Element 3 is \$30. If the two examinations for the General Radio-telephone Operator's License are taken in a single session, the fee is

only \$35. There are other combinations of elements and fees for the other elements. .

**Preparing For An Exam.** The best way to prepare for any of these exams is to study the available background subject material. IS CET offers excellent, inexpensive study materials that will help all candidates prepare for each of its exams. If you are at the entry level, the Study Guide for the Associate CET Test will give you an excellent review for this first test. The 96-page booklet is priced at \$10. The Software Study Guide and Practice Test with 300 sample questions is price at \$39.95 plus \$2 shipping. In addition, IS CET offers practice tests for most of the Journeyman options as well as excellent review texts on each of those options.

The FCC examinations are assembled from questions in a published question pool. By making the complete question pool available, the FCC has defined the limits of the basic knowledge that it expects each successful candidate to have. The availability of the pool also assures all persons taking the test that there will be no nasty surprises. A study guide and compete question pools for Elements 1, 3, and 8 is available for \$29.95 plus \$3 for shipping and handling costs. In addition, self-test computer software packages are available. Not surprisingly, being well prepared for all examinations can make the difference between passing and failing!

If, after reading this, you decide that you would like to take the CET CAT, or any of the FCC exams, contact one of IS CET's volunteer test administrators listed elsewhere in this article for details. As stated earlier, the exams are scheduled for the week of April 20 through April 26. For additional information, or to obtain an order form listing all of the available guidance and help materials, contact IS CET directly at 2708 West Berry St., Fort Worth, TX 76109; Tel: 817-921-9101, FAX 817-921-3741.

See you at Testing Week 97, and on Electronics Technicians Day! ■

## LAND WARRIOR

(continued from page 44)

separate, hand-held QWERTY keyboard. The C/RS can capture and transmit still-frame video.

At the heart of the Land Warrior is the Software System. This provides navigation, digitized map display, location databases, laser detection and warning, command and control, fire control, and communications capabilities.

Finally there is the Weapon Subsystem featuring a modified M4/M16. The Thermal Weapon Sight attached to the weapon can detect targets out to 1000 meters through fog, smoke, dust, and other obscurants, at day or night. The Laser Rangefinder/Digital Compass Assembly provides the ability to accurately and rapidly pass off targets for indirect fire support when linked to the computer, GPS, and radio. Being able to view outputs of these devices on the helmet displays means the wearer can "see" without exposing his position.

All these electronics are powered by a non-rechargeable battery that provides 12 hours of operation. Batteries can be quickly changed in the field where recharging of batteries is not really practical. However, rechargeable batteries are used during training. Even with all this sophistication, the Land Warrior's weaponry still includes a bayonet.

With the Land Warrior System, soldiers will always have answers to the questions, "Where Am I?, Where is the Enemy?," and "Where are other friendly troops?" ■



## DUTY CYCLE MONITOR

(Continued from page 46)

nents mounted behind the circuit board. Drill the battery-holder mounting hole, and the already scribed board-mounting holes. Install the meter, binding posts, LED2, battery holder, and power switch in cabinet.

Connect R7 from the anode lead of LED2 to one lug on the power switch. Connect the positive lead from a 9-volt battery "snap" connector to the other switch lug, and the negative lead to the cathode of LED2, using shrink tubing on each LED lead. Cut down the 6-inch wires on the circuit board as short as possible for ease of connection and installation of the board on spacers. Connect these leads as follows: the two signal input leads go to the binding posts, the two output leads go to the meter, and the positive power lead goes to the S1/R7 lug connection, with the negative power lead going to the cathode of LED2. Observe proper polarity on all connections. Install the board on the spacers, place the battery in its holder and attach the battery connector.

**Calibration and Use.** A very simple and fairly accurate method of calibrating the unit is to connect the positive-input binding post to +5 volts at the output of IC2. Turn on the power and adjust trimmer potentiometer R3 for a reading of just a "hair" over full scale (about 101 microamps) on your meter. (**Note:** Make sure that the meter is mechanically zeroed before calibration.) That method will get you within about 1%, but for best accuracy, input a signal of about 1 to 10 kHz from a flip-flop configured in its "toggle" mode, and adjust R3 for a 50-microamp or 50%-duty-cycle reading. An oscilloscope or counter along with a pulse generator could also be used to complete this task.

To use the Duty-Cycle Monitor, input any rectangular pulse waveform to the binding posts observing proper polarity and the voltage range of the device. The pulse has to cross the 1.3-volt threshold for proper operation. Read the duty cycle directly in percentages: 100 microamperes equal a 100% duty cycle. The input is fully protected for reverse-polarity and over-voltage conditions. ■

# GET 5 BOOKS FOR ONLY \$4.95

WHEN YOU JOIN THE **Electronics Book Club®**

VALUES TO \$213.80


The leading source of information for electronics hobbyists for over 30 years!



0053146 \$24.95




036432X \$29.95  
Hardcover

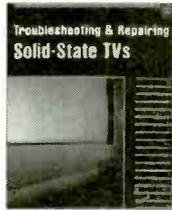


0157537-XX \$44.95  
Hardcover/Counts as 2




0487375 \$24.95

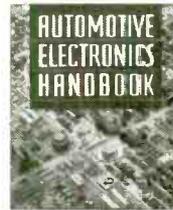

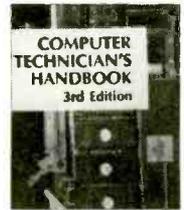
0331898-XX \$89.50  
Hardcover/Counts as 2




1575472 \$27.95

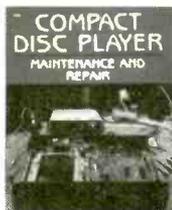

1570519 \$17.95

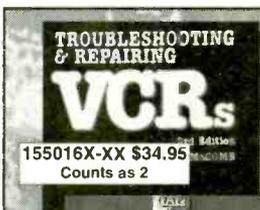


155016X-XX \$34.95  
Counts as 2

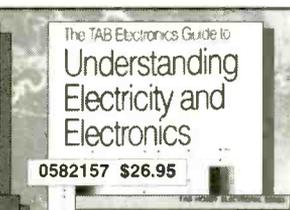


0582157 \$26.95




0157642 \$44.95  
Hardcover

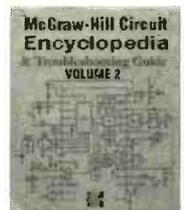


0376115-XX \$36.95  
Counts as 2

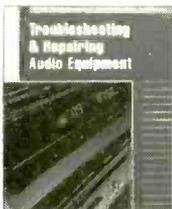


0157553 \$44.95  
Hardcover

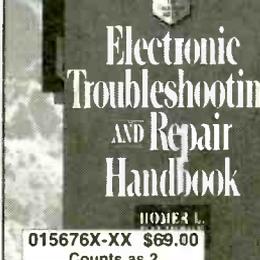

015676X-XX \$69.00  
Counts as 2

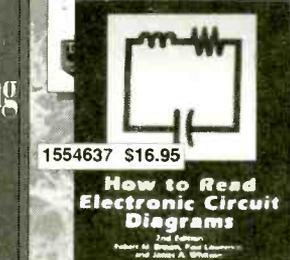


1554637 \$16.95

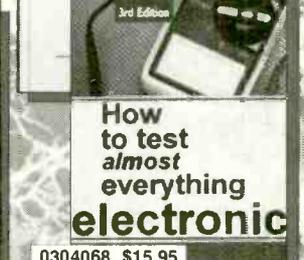

0304068 \$15.95




0535469 \$29.95

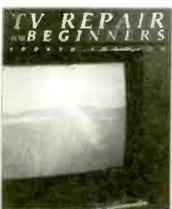


073092X \$19.95




1577564 \$22.95

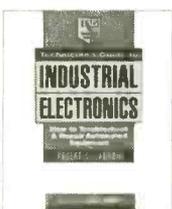

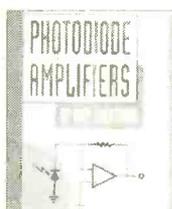0112738-XX \$45.00  
Hardcover/Counts as 2




024247X \$49.00

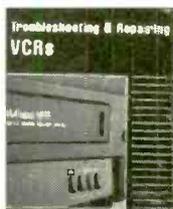


0241996 \$44.95  
Hardcover



5869179 \$12.95

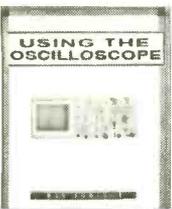


5872625-XX \$30.00  
Counts as 2

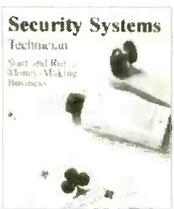

0717753 \$19.95



0052387 \$28.95  
Hardcover

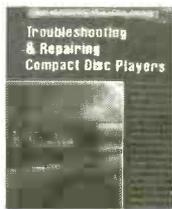

0157626 \$24.95



1574875 \$19.95



0650780 \$24.95

**As a member of the ELECTRONICS BOOK CLUB®...** you'll enjoy receiving Club bulletins every 3-4 weeks containing exciting offers on the latest books in the field at savings of up to 50% off the regular publishers' prices. If you want the Main Selection, do nothing and it will be shipped automatically. If you want another book, or no book at all, simply return the reply form to us by the date specified. You'll have at least 10 days to decide. If you ever receive a book you don't want due to late delivery of the bulletin, you can return it at our expense. Your only obligation is to purchase 3 more books during the next 12 months, after which you may cancel your membership at any time. And you'll be eligible for FREE BOOKS through our Bonus Book Program.

A shipping/handling charge and sales tax will be added to all orders. All books are softcover unless otherwise noted. (Publishers' Prices Shown)


PE597

May 1997, Popular Electronics

55

If coupon is missing, write to: Electronics Book Club® A Division of The McGraw-Hill Companies, P.O. Box 549, Blacklick, OH 43004-9918

# BUILD A DC-MOTOR SPEED CONTROLLER

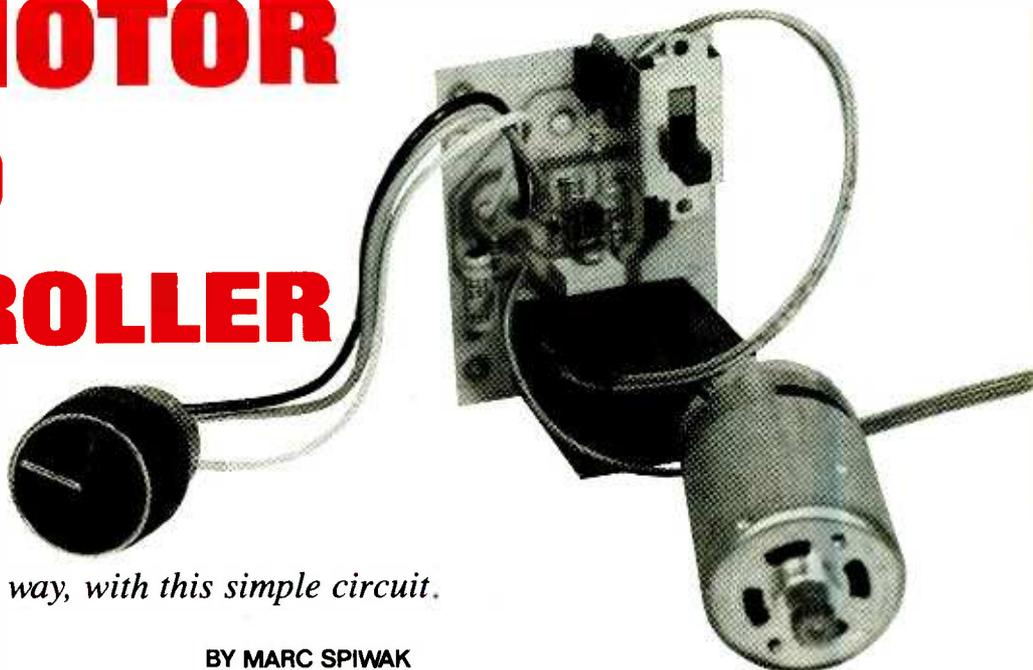

*Vary the speed of a DC motor, the right way, with this simple circuit.*

BY MARC SPIWAK

Everyone who reads this magazine probably played with DC motors as a kid; they were just too fascinating to throw away like other broken appliances. Motors are magical—connect a battery and away they go. Controlling their speed, though, is a bit trickier.

While I had a nice collection of motors going by the age of 10, I never had an electronic speed controller. The best I could come up with at the time was a wire-wound pistol-grip speed controller from an old slot-car set. I actually built my own "radio control" car, which contained two motors, using that very same speed controller.

Back then I connected a rack-and-pinion steering mechanism, that I made from the geared-down starter motor taken from a defunct Visible V8 Engine model, to the chassis of an old Cox car, which had steerable front wheels. With the Cox car's original rear wheels removed (they came off with the engine/tranny combo, which never lasted more than a few hours), I installed a new motor/gearbox/rear-wheel package made from Capsela pieces. A long, four-conductor wire then let me drive the car forward and reverse in variable speed, and make left and right turns, all with a controller box that I made from a couple of power-reversing switches and the

slot-car power supply. Sure the car was tethered to the controller, but I had made it myself. It was a lot of fun to play with, and it didn't cost me anything. I guess that's why I got into electric radio-control cars once I was earning enough money to afford them! But I digress.

Still, DC motors are used in many different devices—pretty much anything that moves. And one of the main design consideration problems is

controlling the speed of a motor. Simple resistive speed controllers can be used, but these waste a lot of energy in the form of heat. In addition, it's not easy to precisely control the speed of a motor with such a simple type of controller.

The best kind of speed controller is an electronic one—a device that basically chops up the DC power and feeds it to the motor in a pulsed form. Very little power is wasted, and none

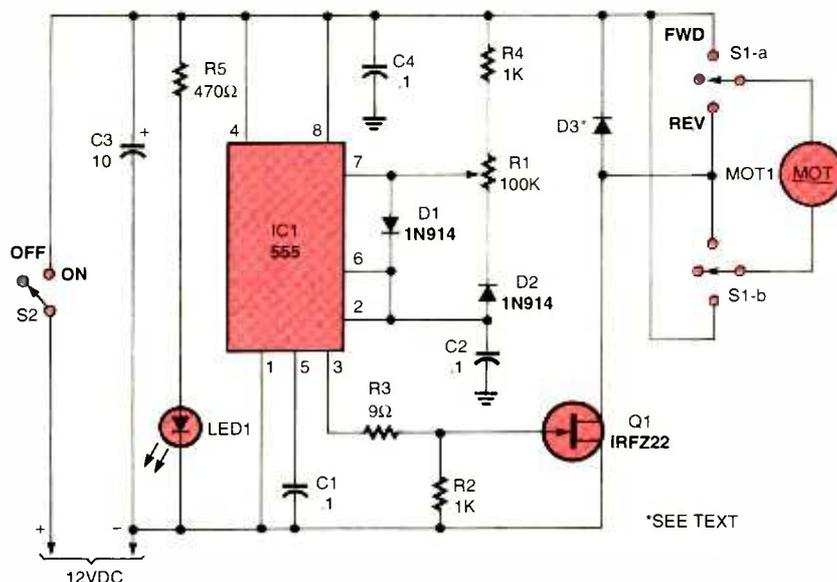


Fig. 1. Here's the schematic for the DC-Motor Speed Controller. At its heart is a 555 timer circuit, which oscillates at a frequency determined by capacitor C1 and potentiometer R1.

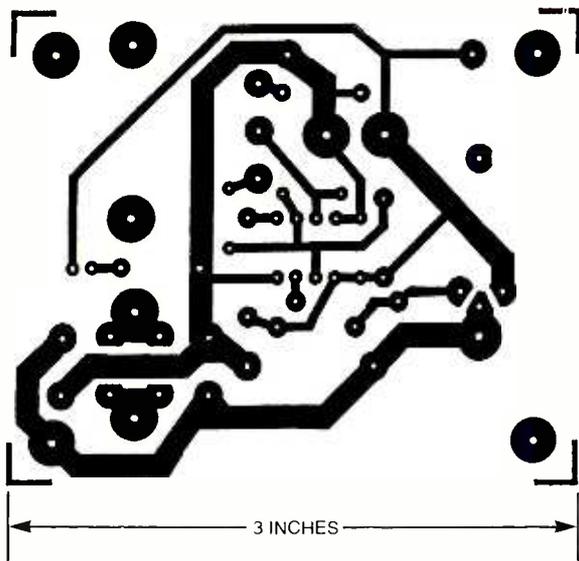


Fig. 2. You can make your own PC board for the Speed Controller using this foil pattern. It is shown full size.

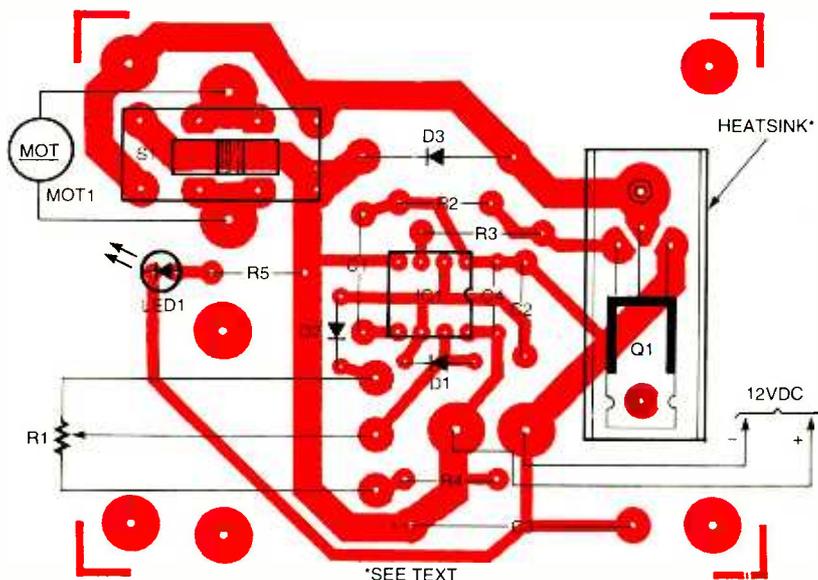


Fig. 3. If you're building the circuit on a PC board, use this parts-placement diagram as a guide.

of it is simply burned up across a resistor. The power output from such an electronic speed controller is basically a squarewave with a variable duty cycle. The more time the voltage output stays high, the higher the average voltage that's fed to the motor. The higher the voltage, the faster the motor spins. Conversely, the less time that the squarewave output stays high, the lower the average voltage and the slower the motor runs.

The DC-Motor Speed Controller described in this article is just such a device, which gives an approximate 5% to 98% control range of a motor. You

can build the simple circuit in an hour or so from parts you probably have lurking in your junk box. If you don't have a good collection of parts, however, don't worry. There's a kit available from the source mentioned in the Parts List that includes a PC board and a nice big motor, plus all the necessary parts. All you have to provide then, besides some solder and tools, is a 12-volt battery or power supply.

**Circuit Description.** The schematic for the Speed Controller is shown in Fig. 1. The circuit is centered around a 555 timer circuit that runs at a fre-

## PARTS LIST FOR THE DC-MOTOR SPEED CONTROLLER

### SEMICONDUCTORS

IC1—555 timer, integrated circuit  
 Q1—IRFZ22 MOSFET or equivalent  
 D1, D2—1N914 or 1N4148 silicon diode  
 D3—3-ampere, 300-volt diode  
 LED1—Light-emitting diode, any color

### RESISTORS

(All fixed resistors are 1/4-watt, 5% units.)  
 R1—100,000-ohm potentiometer  
 R2, R4—1000-ohm  
 R3—9-ohm  
 R5—470-ohm

### ADDITIONAL PARTS AND MATERIALS

C1, C2, C4—0.1- $\mu$ F, ceramic-disc capacitor  
 C3—10- to 15- $\mu$ F, 50-WVDC, electrolytic capacitor  
 MOT1—12-volt DC hobby motor  
 S1—2P3T switch  
 S2—SPDT switch  
 Printed-circuit materials, 12-volt battery pack or power supply, heat sink for MOSFET Q1, hardware, wire, solder, etc.


**Note:** The following is available from Marlin P. Jones & Associates, Inc. (P.O. Box 12685, Lake Park, FL 33403-0685; Tel. 800-652-6733): kit for the Speed Controller (Kit # 4057-MD) including a PC board, all components, and a 12-volt DC motor—\$15.95 plus \$5 shipping and handling. Florida residents please add appropriate sales tax.

quency determined by capacitor C1 and potentiometer R1. Varying R1 changes the discharge rate of the oscillator circuit and the output signal at pin 3. That output turns power MOSFET Q1 on an off, thereby supplying power to the motor (MOT1). As hinted at earlier, the longer the MOSFET is turned on, the higher the average DC voltage applied to the motor, and the faster it will run.

The circuit requires a 12-volt battery pack or power supply that can supply up to 10 amperes (depending on what you are going to use it for). Switch S2 applies power to the circuit and light-emitting diode LED1 indicates when power is turned on. The other switch, S1, toggles the polarity of the power applied to the motor, thus

# You can Build Gadgets!

## Here are 3 reasons why!

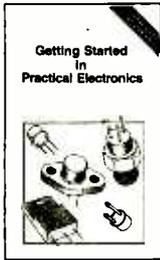


**BP345—GETTING STARTED IN PRACTICAL ELECTRONICS \$5.95**

If you are looking into launching an exciting hobby activity, this text provides minimum essentials for the builder and 30 easy-to-build fun projects every experimenter should toy with. Printed-circuit board designs are included to give your project a professional appearance.

.....


**BP349—PRACTICAL OPTO-ELECTRONIC PROJECTS \$5.95**

If you shun opto-electronic projects for lack of knowledge, this is the book for you. A bit of introductory theory comes first and then a number of practical projects which utilize a range of opto devices, from a filament bulb to modern infrared sensors and emitters—all are easy to build.

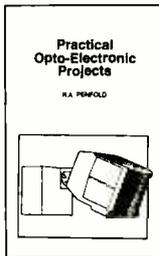

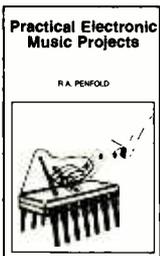**BP363—PRACTICAL ELECTRONIC MUSIC PROJECTS \$5.95**

The text contains a goodly number of practical music projects most often requested by musicians. All the projects are relatively low-in-cost to build and all use standard, readily-available components that you can buy. The project categories are guitar, general music and MIDI.



Mail to:  
**Electronic Technology Today, Inc.**  
**P.O. Box 240**  
**Massapequa Park, NY 11762-0240**

**Shipping Charges in USA & Canada**

\$0.01 to \$5.00.....\$2.00	\$30.01 to \$40.00.....\$6.00
\$5.01 to \$10.00.....\$3.00	\$40.01 to \$50.00.....\$7.00
\$10.01 to \$20.00.....\$4.00	\$50.01 and above.....\$8.50
\$20.01 to \$30.00.....\$5.00	

Sorry, no orders accepted outside of USA and Canada. All payments must be in U.S. funds only.

Number of books ordered.

Total price of books.....	\$ _____
Shipping (see chart).....	\$ _____
Subtotal.....	\$ _____
Sales Tax (NYS only).....	\$ _____
Total enclosed.....	\$ _____

Name \_\_\_\_\_  
 Address \_\_\_\_\_  
 City \_\_\_\_\_ State \_\_\_\_\_ ZIP \_\_\_\_\_

Please allow 6-8 weeks for delivery.

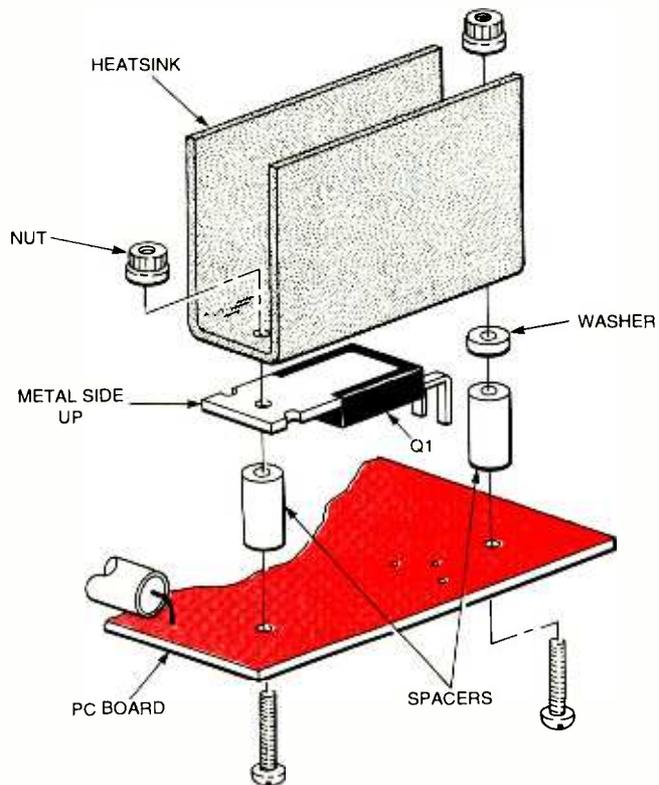


Fig. 4. The heatsink mounts above MOSFET Q1 on spacers with Q1 bent over forward.

changing its direction of rotation between forward and reverse.

**Construction.** If you're building the circuit from scratch, and would like to use a printed-circuit board, you can make your own from the foil pattern provided in Fig. 2. You can also order a board as part of the kit mentioned earlier. Otherwise, you can build the circuit on a piece of perforated construction board and use point-to-point wiring.

If you're going the PC-board route use the parts-placement diagram shown in Fig. 3 as a guide when assembling the circuit. Solder the parts to the board basically in size order, starting with the fixed resistors. The 555 timer IC, diodes, and capacitor C3 must be mounted with the indicated proper polarity. Solder the motor leads to the board before installing switch S1 or else they will be difficult to insert. All leads should be fairly heavy gauge and capable of handling 10 amperes, simply because the circuit is capable of supplying it. The polarity of the motor leads isn't really all that important since you can reverse it with switch S1.

The DPDT switch included with the

kit has an extra row of pins that must be cut off for it to fit the PC board. Position the switch for best fit before cutting off the extra pins. Be careful of the polarity when connecting the power-input leads.

The MOSFET must be heatsinked. The kit includes a heatsink that mounts above the MOSFET bent over forward as shown in Fig. 4. If you're building from scratch, just use any decent-sized heat sink that fits the MOSFET. Some thermal grease applied to the MOSFET tab isn't a bad idea either. After building the circuit be sure to check your soldering and parts placement.

When you are sure the board is in tip-top shape, you can apply power. If all goes well, the motor should start to run and you'll be able to control the speed of it by adjusting potentiometer R1. The board is now ready to be installed in something. Your own model car, perhaps, or maybe some exotic robot to be!

Wherever you use it, and most important when using batteries, the circuit is going to save as much power as possible. That translates into more run time!

# HAM Radio

## Going for Gigahertz

JOSEPH J. CARR, K4IPV

Many readers are familiar with the Mini-Circuits MAR-x devices (they have been covered in this column in the past). Those devices are monolithic microwave integrated circuits (MMIC) that work over frequency ranges of DC to 1000 MHz or DC to 2000 MHz, depending on the model.

Now Mini-Circuits has expanded their MMIC line with a new series that works to 3 gigahertz (GHz), 4 GHz, 6 GHz, or 8 GHz, depending on the type number. The series is called the ERA-x amplifiers, where "x" indicates the specific device. For those who came in late, 1 GHz is 1000 MHz, so 8 GHz is 8000 MHz!

### ERA-x

Figure 1 shows a greatly blown up view of the ERA-x package. The actual size of the plastic package is about the size of the MAR-x package, or about 2-3 mm, but the leads are only about two thirds as long. Also, while the type number can be detected by the color of the dot that indicates lead 1, on the ERA-x they are all red.

One aspect of the MMIC type of device is that the internal circuitry sets the input and output impedances. While most RF devices have a natural input or output impedance that is anything but the standard RF system impedance of 50 ohms, the MMIC devices, including both MAR-x and ERA-x devices, have inherent 50-ohm input and 50-ohm output impedances. As a result, these devices can be used as "drop-in" amplifiers over their entire range of frequency.

Note that there are two ground leads on the ERA-x devices. You must use both grounds. The reason why they do this on RF devices is to prevent lead inductance from causing ground loop problems. A pair of parallel ground leads effectively reduces the apparent lead inductance.

Figure 2 shows the standard circuit for both ERA-x and MAR-x devices. Note that the DC power is applied to the device through the output terminal (pin 3), rather than through any special

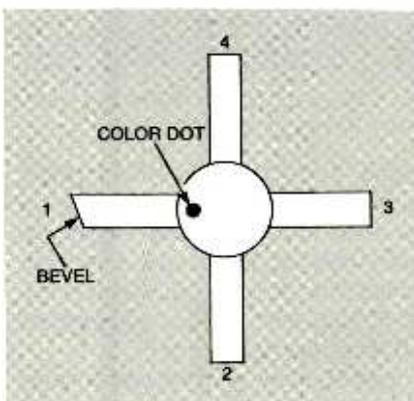


Fig. 1. The package for an ERA-x device is smaller than a MAR-x package, but otherwise similar.

DC terminal. The +5 VDC voltage required at pin 3 by the ERA-x devices (MAR-x devices may use either +5 VDC or +3.5 VDC, depending on type) is derived through the bias resistor, R1. The value of R1 depends on the value of current required by the ERA-x device, which is dependent on the type. The value for each amplifier can be found on the Mini-Circuits spec sheet for the ERA-x devices (see below for details on how to contact them). Let's suppose, for the sake of example, that the desired current is 40 mA (0.040 A). The resistor, R1, must drop  $V+$  to +5 VDC at the desired current level, so by Ohm's law, and assuming  $V+ = 9$  VDC:

$$R1 = ((V+) - V1) / I = (9\text{VDC} - 5\text{VDC}) / 0.040 = 4 / 0.040 = 100 \text{ ohms}$$

The value of R1 will be different for other devices, so please check the spec sheet for the device that you want to use. Table 1 lists some of the devices that are available.

The RF choke (L1) in Fig. 2 is optional, and sometimes causes problems in wideband amplifiers. If the choke is self-resonant at a frequency that is within the amplifier's capability, then the amplifier might oscillate. For VHF/UHF and up, it is recommended that you use a ferrite bead slipped over a short (0.25 to 0.50 inch) length of 22-gauge solid hook-up wire. Suitable ferrite beads can be obtained from sources that also sell toroid cores.

The DC blocking capacitors, C1 and C2, set the lower end of the frequency response curve. Generally, you will use 0.1  $\mu\text{F}$  for the lowest frequencies (<1 MHz), 0.01  $\mu\text{F}$  for 10 MHz, 0.001  $\mu\text{F}$  for 100 MHz, 100 pF for 500 MHz, and 10 pF for above 500 MHz. For frequencies above about 200 MHz, don't use ceramic-disc capacitors because they tend to have a self-resonant frequency that is set by the lead inductance. For those frequencies use surface-mount "chip" capacitors. Below 200 MHz, however, quality ceramic-disc units should work fine.

As mentioned earlier, Table 1 shows some of the devices in the ERA-x line. Note that surface mount versions are also available, and are indicated by an "SM" on the end of the part number (e.g. an ERA-4 is "ERA-4SM" in surface-mount packaging).

The ERA-x devices, like the MAR-x devices, can be used for frequencies from near-DC to the maximum frequency for the device. Keep in mind, however, that not all capacitors (for C1 and C2) are created equal. If you want to have a low-end frequency of around 100 MHz, then a 0.001- $\mu\text{F}$  ceramic-disc capacitor will do nicely at that frequency, but will fall off in performance (or cause problems) at some frequen-

TABLE 1

Type	Gain	-1 dB Comp.	TOIP	NF	Freq. (GHz)
ERA-1	11.8 dB	13 dBm	26 dBm	7 dB	8
ERA-2	14.9 dB	14 dBm	27 dBm	6 dB	6
ERA-3	20.2 dB	11 dBm	23 dBm	4.5 dB	3
ERA-4	11 dB	19.1 dBm	36 dBm	5.2 dB	4
ERA-5	16 dB	19.6 dBm	36 dBm	4 dB	4

cy above 200 MHz because of self-resonance. And those 0.01- $\mu$ F and 0.1- $\mu$ F capacitors used at lower frequencies might look more like blocks of wood than capacitors to GHz-level frequencies. Make sure the capacitor you select works over the entire range.

The DC decoupling capacitor, C3, is nominally set at 0.1  $\mu$ F, but at higher frequencies a value similar to C1 and C2 can be used. In some cases, it is wise to use two capacitors for C3, one being a 0.1- $\mu$ F unit and the other being a 100-pF chip capacitor for the higher frequencies.

Mini-Circuits can be contacted via mail at P.O. Box 350166, Brooklyn, NY, 11235-0003; via phone at 718-934-4500; via FAX at 718-332-4661; or on the Internet at <http://www.minicircuits.com>. Their WWW site allows you to download a complete spec sheet for the ERA-x devices. While you are at the Mini-Circuits website, also download the spec sheets for the POS-x series of RF voltage-controlled oscillators.

## 11-METERS

In this column and elsewhere I have told you that hams lost the 11-meter "ham band" to CBers back in 1957. That's not quite right. A friend at ARRL headquarters (225 Main Street, Newington, CT, 06111; e-mail [hq@arrl.org](mailto:hq@arrl.org)) wrote and reminded me that 11-meters was never a ham band. Hams were *allowed* to operate on the 27 MHz 11-meter band, but only on a shared basis. It was a multi-use band for scientific, industrial, and other devices. Early medical diathermy and industrial-induction heating equipment operated (at high power levels!) on the 11-meter band.

My own 11-meter experience was on CB in the late 1950's to mid-1960's (I got off when it got popular), and medical diathermy noise chewed up a lot of spectrum space on that band. Driving by certain doctors' offices (even many blocks away), or near a hospital, causes a raucous raw interference (caused by the fact that medical diathermy tended to operate using unfiltered pulsating DC on the anodes of the power amplifiers). Fortunately, medical diathermy went into the UHF band a long time ago.

Even though it wasn't a "ham band," we did have a "Save Eleven" contest back in 1956 or 1957. Of

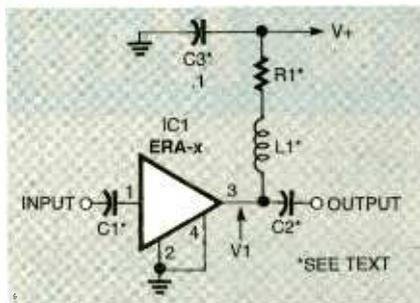


Fig. 2. Here's a circuit for ERA-x and MAR-x devices. See text for component values.

course, a lot of hams disdained CBers, but in the earliest of the early days a few of us in Bruno Paras' electronics shop class at Washington-Lee High School (Arlington, VA) converted a few BC-603/BC-604 military transmitters and receivers for CB use.

Indeed, early in World War II hams who were experimenting with what was then called "UHF" (everything above 25 MHz) heard German language voices on 11-meters. They reported it to the FBI, who found out that the 5-watt transmitters in Rommel's *Afrika Korps* panzers were skipping into Massachusetts quite easily from North Africa.

## OTHER STUFF

A long period of illness in 1994-1995 kind of crimped my book writing, but now there are several new ones on the market that may interest readers of this column. Butterworth-Heinemann, a British publisher that also operates in the USA from Newton, MA, just published *Microwave and Wireless Communications Technology*. It contains a lot of stuff about microwave devices and systems. TAB/McGraw-Hill just published *Secrets of RF Circuit Design-2nd Edition*, and *Technician's Guide to DC Power Supplies*.

Butterworth-Heinemann also published my books *Linear Integrated Circuits* and *Designer's Guide to Applications of Linear ICs* in United Kingdom, but they should be available in the USA soon. Search for the various B-H web sites by typing "Butterworth-Heinemann" into your favorite web search engine.


I can be reached by snail mail at P.O. Box 1099, Falls Church, VA, 22041, or by e-mail at [carrj@aol.com](mailto:carrj@aol.com). I appreciate your mail or e-mail, and much of what I hear from you winds up in this column. It is, after all is said and done, my goal to be of service to you. ■

## ANTIQUE RADIO CLASSIFIED

Free Sample!

Antique Radio's  
Largest Circulation Monthly.  
Articles, Ads & Classifieds.  
6-Month Trial: \$18.95. 1-Yr: \$36.95 (\$53.95-1st Class).  
A.R.C., P.O. Box 802-L16, Carlisle, MA 01741  
Phone:(508) 371-0512 VISA/MC Fax:(508) 371-7129
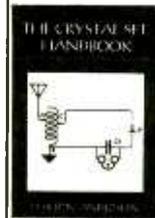
## Get your copy of the CRYSTAL SET HANDBOOK



Go back to antiquity and build the radios that your grandfather built. Build the "Quaker Oats" type rig. Wind coils that work and make it look like the 1920's! Only \$10.95 plus \$4.00 for shipping and handling. Clagg Inc., P.O. Box 4099, Farmingdale, NY 11735. USA Funds ONLY! USA and Canada—no foreign orders. Allow 6-8 weeks for delivery. MA01

## SILICON-CONTROLLED RECTIFIER PROJECTS

1586T—From TAB Books. A treasure trove of exciting projects using SCR's and other low-cost thyristor devices for power-control applications. Includes a sophisticated burglar-alarm system, an SCR-based smoke-alarm system, a remote-control garage-door opener, and a high-tech light dimmer that uses the output from your stereo to modulate the intensity of your lights. And then there are 20 more. To order—ask for book 1586T, and include your check for \$12.95 (includes s&h) in US and Canada, and order from — Electronic Technology Today Inc., P.O. Box 240, Massapequa Park, NY 11762-0240. US funds only, use US bank check or International money order. Allow 6-8 weeks for delivery. MA09



## THE COLLECTED WORKS OF MOHAMMED ULLYES FIPS

#166—By Hugo Gernsback. Here is a collection of 21 April Fools Articles, reprinted from the pages of the magazines they appeared in, as a 74-page, 8 1/2 x 11-inch book. The stories were written between 1933 and 1964. Some of the devices actually exist today. Others are just around the corner. All are fun and almost possible. Stories include the Cordless Radio Iron, The Visi-Talkie, Electronic Razor, 30-Day LP Record, Teleyeglasses and even Electronic Brain Servicing. Get your copy today. Ask for book #166 and include \$16.00 (includes shipping and handling) in the US and Canada, and order from CLAGG Inc., P.O. Box 4099, Farmingdale, NY 11735-0793. Payment in US funds by US bank check or International Money Order. Allow 6-8 weeks for delivery. MA05



# Circuit Circus

## Junkbox Goodies

BY CHARLES D. RAKES

Welcome back, circueteers. This month we're going to stir the pot and pull out a number of simple circuits that you might be able to put to use in a present or upcoming project.

As you might have guessed from the title of this column, a good junkbox should have the majority of the parts needed for the goodies included here. So warm up your soldering iron, and let's get started.

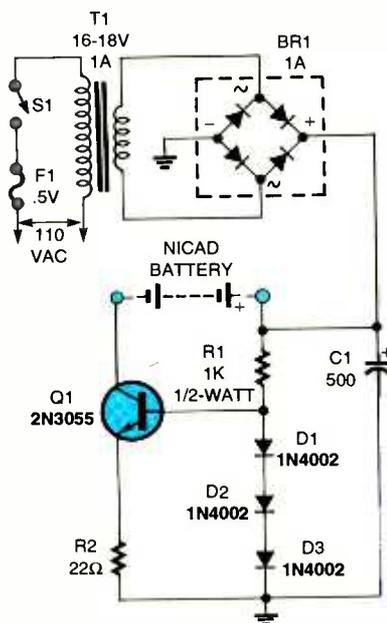


Fig. 1. This constant-current circuit can recharge 1.5- to 12-volt nicad batteries.

### PARTS LIST FOR THE NICAD CHARGER (Fig. 1)

#### SEMICONDUCTORS

Q1—2N3055 NPN power transistor  
BR1—1-ampere full-wave bridge rectifier  
D1-D3—1N4002 silicon diode

#### ADDITIONAL PARTS AND MATERIALS

R1—1000-ohm,  $\frac{1}{2}$ -watt, 5% resistor  
R2—22-ohm,  $\frac{1}{2}$ -watt, 5% resistor  
C1—500- $\mu$ F, 35-WVDC, electrolytic capacitor  
T1—16- to 18-volt, 1-ampere transformer  
S1—SPST toggle switch  
F1—0.5-ampere fuse  
AC line cord with plug, wire, solder, etc.

## NICAD CHARGER

Our first entry, see Fig. 1, features a few inexpensive components connected together to form a useful nicad-battery charger circuit. The charger is a constant-current circuit that can re-energize nicad batteries with voltages as high as 12 volts.

Diodes D1-D3 operate as a low-voltage Zener, setting Q1's base at a 2-volt reference level. Resistor R2's value sets the constant-current charging rate. With a 22-ohm resistor used, the current is close to 50 ma. A 10-ohm resistor will raise the charging rate to around 100 ma.

Most nicads can safely be charged at a rate equal to ten percent of their discharge rating. A battery with a one-amp rating should have no trouble taking a 100-ma charging current. If possible, check the manufacturer's specifications and follow their charging data.

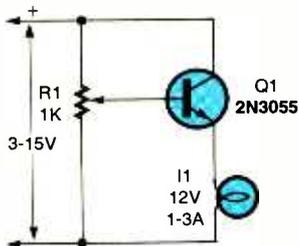


Fig. 2. Discharge nicad batteries with this circuit to help them "remember" what charge they're supposed to hold.

### PARTS LIST FOR THE NICAD DISCHARGER (Fig. 2)

Q1—2N3055 NPN power transistor  
R1—1000-ohm potentiometer  
I1—12-volt, 1 to 3-ampere auto lamp  
Wire, solder, etc.

## NICAD DISCHARGER

Our next circuit (see Fig. 2) is designed to discharge nicad batteries. Nicads can often develop a discharge memory and become "lazy." This basically means that they will not supply their rated output. Sometimes it helps

to zap such a lazy nicad at a safe discharge rate and recharge it again. In some cases this will turn the battery around and make it useful again. Facing the expense of replacing a battery makes it worth trying this rejuvenation trick. (The circuit may also be used in testing the regulation qualities of a power supply.)

A 2N3055 power NPN transistor, Q1, is connected in an emitter follower circuit with an auto lamp, I1, operating as the load resistance. A 1000-ohm potentiometer, R1, varies the transistor's base voltage and the load current. Using the auto lamp is less expensive than replacing it with a 20- or 30-watt resistor.

Before connecting a battery or power source to the circuit, it would be a good idea to heatsink the transistor. This is because Q1 is actually operating as a part of the load.

## POWER-LATCHING SWITCH

A power-latching circuit is shown in Fig. 3. Here we have an SCR connected in series with a power source and the operating circuitry. When S1 is

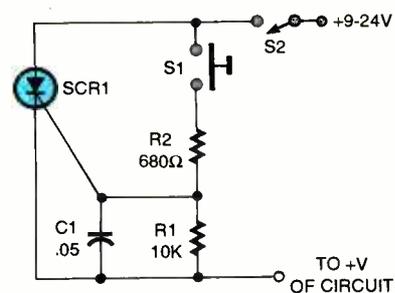


Fig. 3. When S2 is closed and S1 is momentarily pressed, power will stay on with this latching circuit.

### PARTS LIST FOR THE POWER-LATCHING SWITCH (Fig. 3)

SCR1—See text  
R1—10,000-ohm,  $\frac{1}{4}$ -watt, 5% resistor  
R2—680-ohm,  $\frac{1}{4}$ -watt, 5% resistor  
C1—0.05- $\mu$ F, ceramic-disc capacitor  
S1—Normally open pushbutton switch  
S2—SPST toggle switch  
Wire, solder, etc.

momentarily closed the SCR turns on supplying power to the connected circuit. The power remains on until the circuit is broken.

The attached circuitry must draw more current than the SCR's minimum holding current rating or the circuit will not latch. For this reason you will need to decide which SCR to use with your particular circuit.

One application that comes to mind is to use the latching switch to activate and keep an alarm operating until it's reset by a key switch. A tilt or mercury switch could replace S1 for a similar alarm application.

## 15-VOLT DC SUPPLY

If you need a 15-volt DC power supply, but don't have a 20- or 24-volt transformer handy, then take a look at the solution offered in Fig. 4. Here a common 12-volt transformer is connected to a two-diode, two-capacitor, voltage-doubler circuit. The doubled voltage is fed to a 7815 regulator, IC1, producing a 15-volt, 1-ampere regulated power supply.

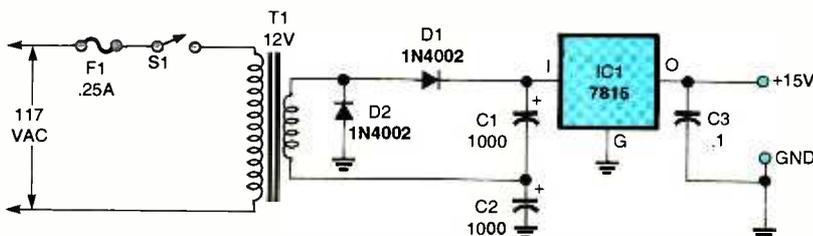


Fig. 4. If you need a 15-volt DC power supply, but don't have a 20- or 24-volt transformer handy, try this circuit.

### PARTS LIST FOR THE 15-VOLT DC SUPPLY (Fig. 4)

IC1—7815 voltage regulator, integrated circuit  
 D1-D2—1N4002 silicon diode  
 C1, C2—1000-µF, 35-WVDC, electrolytic capacitor  
 C3—0.1-µF, ceramic-disc capacitor  
 T1—12-volt, 1-ampere, transformer  
 F1— $\frac{1}{4}$ -ampere fuse  
 S1—SPST switch  
 AC line cord with plug, wire, solder, etc.

Most any 12-volt transformer will work for T1 as long as its current rating is at least 1 ampere. Larger-value filter capacitors may be used but must match each other in value.

## NEGATIVE SUPPLY

The circuit shown in Fig. 5 takes a positive voltage and turns it upside

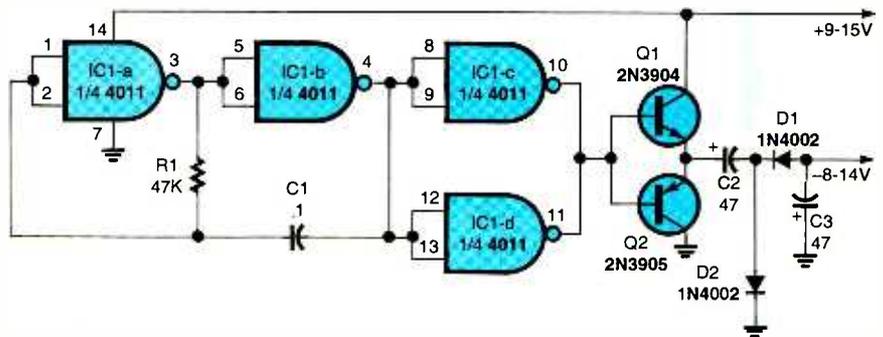


Fig. 5. This circuit takes a positive voltage and turns it "upside down" to produce a negative power supply.

### PARTS LIST FOR THE NEGATIVE SUPPLY (Fig. 5)

#### SEMICONDUCTORS

IC1—4011 quad two-input NAND gate, integrated circuit  
 Q1—2N3904 NPN transistor  
 Q2—2N3905 PNP transistor  
 D1, D2—1N4002 silicon diode

#### ADDITIONAL PARTS AND MATERIALS

R1—47,000-ohm,  $\frac{1}{4}$ -watt, 5% resistor  
 C1—0.1-µF, ceramic-disc capacitor  
 C2, C3—47-µF, 35-WVDC, electrolytic capacitor  
 Wire, solder, etc.

negative output. As you can see in the schematic, this negative output voltage will be slightly lower than the positive supply voltage.

## ISOLATED SUPPLY

In some circuits a separate power source is necessary to help isolate one sensitive circuit from interfering with another. The circuit shown in Fig. 6 generates just such an isolated positive power source.

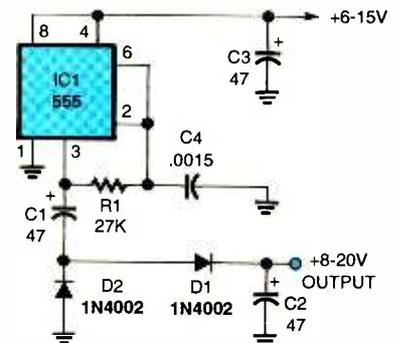


Fig. 6. If you need a separate power source to isolate one sensitive circuit from interfering with another, build this circuit.

### PARTS LIST FOR THE ISOLATED SUPPLY (Fig. 6)

IC1—555 timer, integrated circuit  
 D1, D2—1N4002 silicon diode  
 R1—27,000-ohm,  $\frac{1}{4}$ -watt, 5% resistor  
 C1-C3—47-µF, 35-WVDC, electrolytic capacitor  
 C4—0.0015-µF, Mylar or similar capacitor  
 Wire, solder, etc.

A 555 timer, IC1, is connected in an audio-oscillator circuit with R1 and C4 setting the operating frequency. A squarewave output is fed from pin 3 of IC1 to the input of a dual-diode voltage-doubler circuit. The DC output can supply several milliamperes of current to an isolated circuit.

## LED POLARITY TESTER

Our next entry, see Fig. 7, is a circuit for testing and determining the polarity of "orphan" LEDs. A 6-volt transformer, T1, supplies power to operate the test circuit. Just about any 6-volt transformer will do that can supply at least 20-milliamperes of current to the test circuitry.

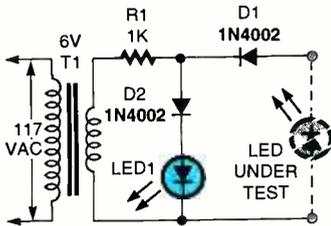


Fig. 7. Use this circuit to test and determine the polarity of "orphan" LEDs.

### PARTS LIST FOR THE LED POLARITY TESTER (Fig. 7)

LED1—Light-emitting diode, any color  
 D1, D2—1N4002 silicon diode  
 R1—1000-ohm, 1/4-watt, 5% resistor  
 T1—6-volt transformer  
 AC line cord with plug, wire, solder, etc.

Resistor R1 limits the total test current to a safe level that's under 10 milliamperes. Without an LED connected to the test terminals, LED1 receives current through diode D2 on each positive cycle. On the negative cycle LED1 is protected from receiving a reverse voltage by the blocking effect of D2.

When an LED is placed across the test terminals as shown in the schematic, and it is in good operating condition, it will light during the negative half cycle. If the LED leads are reversed, nothing happens. An open or shorted LED will indicate so by not giving off a glow. The circuit is obviously not designed to test IR LEDs, because they produce no visible light.

## PROPER-POLARITY ENSURER

Our next entry (see Fig. 8) is a very simple but useful circuit. The four-diode bridge circuit can be used to direct the proper polarity of a DC battery or supply to a circuit. How many times have you said, "Oh darn!" and had to fan the smoke away because you accidentally reversed a battery's connections? If that happens to you this circuit could be the cure.

The 1N4004 diodes indicated in the

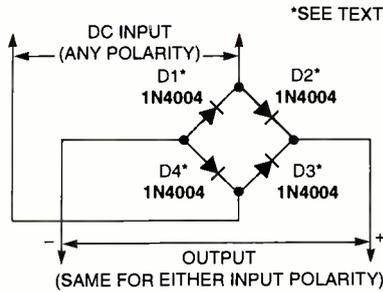


Fig. 8. With this diode bridge, incorrect battery polarity will never harm one of your circuits again.

### PARTS LIST FOR THE PROPER-POLARITY ENSURER (Fig. 8)

D1-D4—1N4004 silicon diode; see text  
 Wire, solder, etc.

schematic will work fine for operating currents below the one-ampere level. Always select diodes with a current and voltage rating greater than your circuit requires. We certainly don't want the cure to become another problem.

Oh, by the way, there is one downside to this circuit. The circuit being supplied with power will lose about 1.2 volts of the power source because of the diodes' forward-voltage drop. Keep that in mind when deciding on what source you'll use.

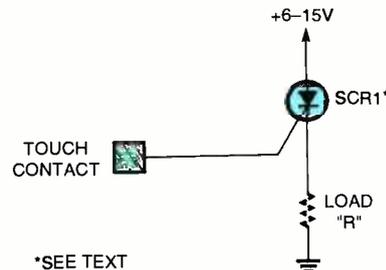


Fig. 9. Need an easy-to-build touch-activated switch? You can't find a simpler one than this one-component circuit.

### PARTS LIST FOR THE TOUCH SWITCH (Fig. 9)

SCR1—See text  
 Touch-contact material, wire, solder, etc.

## TOUCH SWITCH

Our last entry is another simple SCR circuit, which is shown in Fig. 9. Here we have a sensitive gate SCR connected in series with a power

source and a load. When you touch the contact connected to SCR1's gate, the thyristor turns on supplying current to the connected load. As long as the load current is greater than the SCR's holding-current rating the load will receive power.

Any sensitive gate SCR with a current rating suitable for the load can be used. For example, the 2N5060 and 2N5064 types are rated at a maximum load current of 0.8 ampere. Check your component catalogs and you will find a number of sensitive gate SCRs that you can use.

Well it looks like time is running short. So until next month, good circuitry. ■

## KIRLIAN PHOTOGRAPHY


(continued from page 38)

around the entire Kirlian unit is well ventilated. Then stand clear and apply power.

You should hear a hissing sound coming from the electrophotograph stage; that's ozone. Soon you'll see the paper begin to darken in the vicinity of the subject's edges. After 30 to 60 seconds, or when you determine the exposure is long enough, disconnect power, wait a few seconds, and carefully remove the paper (you'll find that residual static charges make the paper stick to the glass plate).

Several exposures can be easily made on one piece of thermal paper, which would be incredibly tricky with regular photographic film. Figure 3 contains a few such sample multi-exposures.

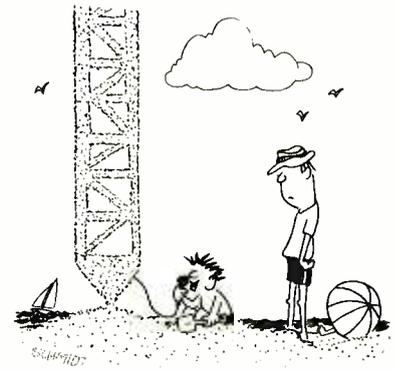And that's all there is to this Poor Man's Kirlian Photography method. Enjoy! ■



# COMPUTER BITS

## Completing Your Greatest Hits Page

BY JEFF HOLTZMANN

This is part three of a series on putting HTML to practical use. Last time we discussed the basis of all Web hyperlinking: the anchor (A NAME) and reference (A HREF) tags. We'll wrap up this series by showing you how to create basic HTML tables, and show an image of the page in action. We'll also draw some conclusions about what we've learned, and discuss a historical milestone reached this issue.

### HTML TABLES

The beginning of each table looks like this:


```
<H3><A Name = "ShareWare Sites">ShareWare Sites</A></H3>
<TABLE BORDER WIDTH=50%>
<TR>
<TH>Description</TH>
<TH>URL</TH>
</TR>
```

The first line says that the display will be in Heading 3 (H3) format. The anchor tag marks where in this HTML file the point called "ShareWare Sites" is located. The next line specifies the beginning of a table, where the table is to use half the width of the browser window. You can also specify an exact width, but I'll leave the details to you.

Line three specifies the beginning of a row in the table. Lines four and five specify two cells, each in the table heading format, which is typically rendered as centered, bold text in the default font. Line six signifies the end of the row.

Each subsequent row in the table looks like this:
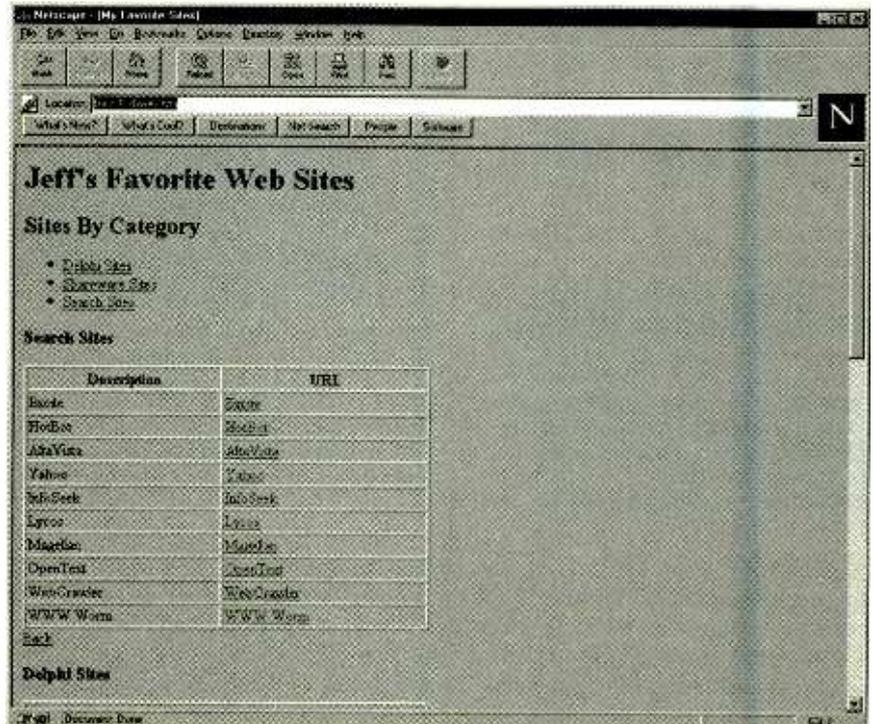
```
<TR>
<TD>Windows95.COM</TD>
<TD><A HREF="http://www.windows95.com/">Win95.COM</A></TD>
>
</TR>
```



Create a "home" page like this for your browser. You'll learn something about the intricacies of HTML coding, and get something useful as well.

Each TD tag specifies a table cell in the default format: normal text, left justification. As we learned last time, the "A HREF" tag in line three specifies an Internet location where a document is located. The "in-between" text, here "Win95.COM," is what is actually displayed, usually underlined and in an alternate color.

Then we see several more table rows; finally, we close out the table as follows:

```
</TABLE>
<A HREF = "#TOP">Back</A>
```

Line one specifies the end of the table; line two provides a link back to the table of contents at the top of the page.

The rest of the file is then just a series of similar tables, with column one containing some descriptive text, and column two a URL.

### USING IT

The simplest way to use this page is to put a shortcut to it on your desktop. Then, whenever you double-click the icon, your browser will load the page. Assuming your Internet dialer is configured correctly, all you'll have to do is click on the desired links.

You can also designate it as your browser's "home" page, the page that will automatically be loaded whenever you run your browser or click the Home button. In Internet Explorer 3.0, choose View, Options, Navigation, and specify the page as your start page. Or you may want to link it to the Search button or one of the Quick Links. In any case, you'll always be no more than a click away from your favorite sites. In Navigator 3.0, choose Options, General Preferences, Appearance. Then, in Browser Starts With, click Home Page

*continued on page 66*

# DX LISTENING

## Listening From Another Locale

BY DON JENSEN

Most of us do our listening from one place. We quickly become familiar with the shortwave bands as they appear to us as we listen from our homes. But if, for example, we should move, say from New York to California, we would find things have changed dramatically.

We would find, perhaps, certain sig-

During his recent visit, he refreshed his recollections by tuning my receiver in my home.

"What are the differences," I asked him, "between listening to shortwave radio in Brazil and the U.S., particularly the DX-filled 60 meter band, the so-called 'tropical' frequencies just above and below 5,000 kHz?"

for some time now. Some in Colombia, others in Nicaragua and other parts of Central America or the Dominican Republic, just do not come through, or are not heard well, in Brazil, mostly because some strong local SW station is on the channel."

Another factor is the noise level from non-man-made sources.

"I was quite surprised to read, some time ago, that in the Amazon region of Brazil, at every single moment, there are more than 200 thunderstorms going on.

"So if you are, as in Sao Paulo, a few hundred miles from that region, you hear on your radio as static and noise the countless electrical discharges from these storms. It is almost like machine-gun bursts!"

North American SWLs may experience, to a lesser degree, those static crashes during summer T-storms. But in Brazil, a level of background noise can be year-round.


"I remember so darned well my time living in Milwaukee. Those cold winter nights were so quiet for DXing. You can turn your volume way up and really hear those weak stations without much static at all. The signal-to-noise ratio was very favorable, whereas at home, you turn the gain up, the amount of noise is just tremendous."

Finally, Jack observes, it seems better to tune low-frequency shortwave stations located toward the east, rather than to the west.

"It seems to have to do with propagational factors, but from my experience it is true. And for listeners in the U.S., and particularly in the Midwest and West, most South American stations are to the southeast."

In Brazil, on the other hand, SW stations in Bolivia, Peru, Ecuador, Colombia and Central America, are located to the north and west.

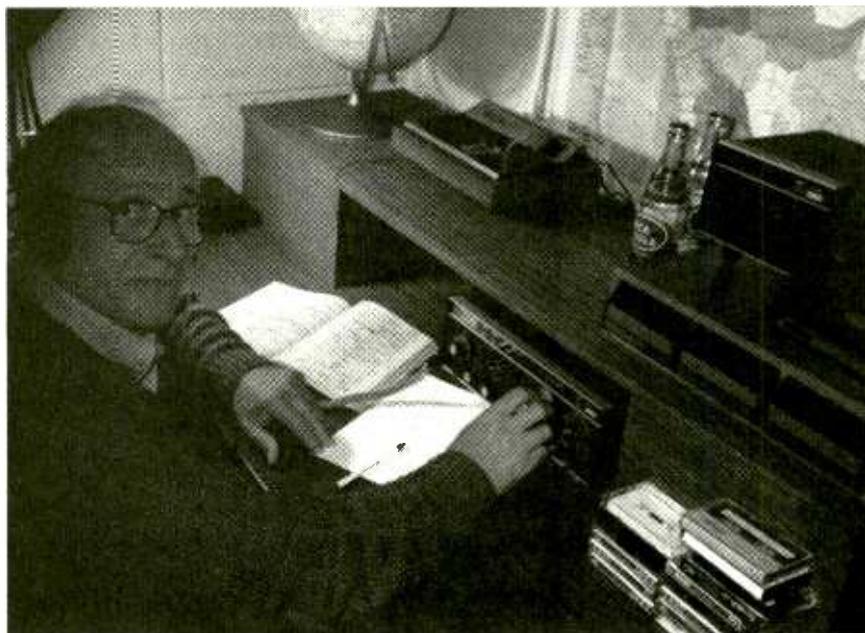All in all, says Jack Perolo, when it comes to tuning in the lower-powered "tropical band" domestic shortwave stations of Latin America, the major tuning challenges of the southern hemisphere, Yankee SWLs may be much luckier than they think.



Here's a photo of Brazilian shortwave DXer Giacomo "Jack" Perolo at his listening post.

nals fade in earlier, or later. Interference may be a problem to a greater or lesser extent. Some SW stations that are commonly heard on the east coast may be difficult, even impossible to hear, on the west.

Imagine the differences in shortwave reception if the comparison points are farther apart, continents apart in opposite hemispheres.

Recently, I was visited by a long-time friend and expert DX listener, Giacomo "Jack" Perolo of Sao Paulo, Brazil. Jack once lived in the U.S. for several years, so he has experience in shortwave listening in Yankeeland.

(CREDITS—Bob Fraser, MA; Harold Levison, PA; Marie Lamb, NY; Ed Newbury, NE; Benton Owsley, CA; North American SW Association, 45 Wildflower Road, Levittown PA 19057)

"There are a number of broadcasting stations in Brazil with relatively high power that operate in these frequencies. They broadcast for long periods causing considerable interference.

"For instance, Radio Aparacida, 5,035 kHz. Depending on the time of night, its strong signal will block with interference a rather wide channel. It will display a rather bad side splash."

American SWLs may look with some envy on Jack's Brazilian location, believing that its proximity to other Latin American countries would make it easier to log some regional broadcasters rarely heard here in North America.

Not necessarily, states Jack.

"There are certain stations that I have been trying for, unsuccessfully,

## TARGET: ICELAND

Not an easy shortwave catch, but one well worth the tuning effort is Ríkisutvarpid RUV, the Icelandic National Broadcasting Service. Not easy because it uses only 10 kilowatts of power on SW and broadcasts in the upper sideband transmission mode. Not easy because it has no English programming. Not easy because its schedule is rather brief.

Still with some effort, and a good bit of patient tuning, logging this broadcaster surely is possible. This is especially the case in the eastern half of North America.

Iceland, of course, is an island of about 40,000 square miles, a bit smaller than Kentucky, located in the far North Atlantic, midway between Europe and Greenland. First settled by Norse colonists about a thousand years ago, the republic has a long history of representative, democratic government.

Ríkisutvarpid, broadcasting since 1930, is an independent public service, owned by the Icelandic government. However, it derives most of its operating funds from domestic listener license fees and advertising.

The broadcasting organization is headquartered in the Icelandic capital of Reykjavik. It has one television channel and two medium-wave stations that cover the whole of the country, plus local radio services for the northern, eastern, and western regions. There also are a number of short-range local FM outlets.

The station is chartered by law with promoting the Icelandic language and the nation's cultural heritage and history. Unfortunately, the former—limiting its SW programming to the Icelandic language—somewhat hampers the promotion of the latter—telling English-speaking listeners about the country's rich historical traditions.

Despite this, the Icelandic National Broadcasting Service is interested in overseas listeners and has an International Relations Department, headed by Dora Ingvadottir.

SW programs are directed toward North America from 1410 to 1440 UTC; 1935 to 2010 UTC; and 2300 to 2335 UTC. The service does tend to alter its frequency selection rather frequently. But during the first two transmission periods, 13,800 and 15,070 kHz seem good bets.

Other registered frequencies worth

trying include: 9,380, 11,580, 11,710 and 15,100 kHz.

Since several of these frequencies are well off the beaten path, if you should come across an upper sideband signal with Nordic-sounding language programming, chances are you've snared this bit of DX.

Your reports can be mailed to Ms. Ingvadottir in care of the International Relations Department, Icelandic National Broadcasting Service, Efstaleiti 1, 150 Reykjavik, Iceland. The e-mail address is [isradio@ruv.is](mailto:isradio@ruv.is).

## DOWN THE DIAL

This month, as every month, we offer a selection of shortwave stations, some easy, some hard to hear, for you to try. You are hearing other SW stations, no doubt, so why not write to get the rest of us know about your current loggings. Or, if you have a question or two about SWling or some special station you've been trying, without success, to hear, why not drop a line to *DX Listening*, **Popular Electronics**, 500 Bi-County Blvd., Farmingdale, NY 11735.

For now, check out these:

**BRAZIL**—15,265 kHz. Radio Nacional do Brasil was heard around 1835 UTC with an English-language program about the Brazilian economy.

**CHILE**—6,090kHz. Radio Esperanza has been heard around 0745 UTC with a recorded religious program in English. Later, Spanish programming resumes, with station identification and religious music.

**CROATIA**—5,895 kHz. Croatian Radio has been logged at 0300 UTC on this frequency with a program of English news, followed by station identification and an interval tuning signal. Programming in Croatian follows.

**NORTH KOREA**—6,575 kHz. Radio Pyongyang's English broadcast was noted shortly before 1200 UTC with a woman announcing station identification. The program continued with march music.

**NORWAY**—9,560 kHz. Radio Denmark's English service is relayed by Radio Norway International's shortwave transmitters. This relay signs off at 0255 UTC. It also can be heard at the same time on 7,465 kHz.

**SWITZERLAND**—13,635 kHz. Swiss Radio International has an English language commentary at 1500 UTC. The signal often is excellent. ■

## COMPUTER BITS

(continued from page 64)

Location. Then enter the URL to where the file is stored on your system. For example, assuming you call your file `faves.htm` and put it in the root of your C drive, enter the following:

```
file://C:\faves.htm
```

There is an old saying to the effect that the teacher always learns more than the students. I certainly learned a few things from doing this series. One thing that surprised me is that doing HTML by hand is no fun. Before beginning this project, I thought that all those WYSIWYG editors like PageMill and FrontPage were for wimps, that a good text editor should suffice for anyone with half a brain. I was wrong. It certainly is possible to write HTML by hand. I now recommend a WYSIWYG HTML editor. Anyway, it worked.

## MILESTONE

That's it for HTML. This, by the way, was the 100th installment of this column by yours truly for this magazine. The timestamp on column one reads 10/17/88, which appeared in the February 1989 issue. The subject of column one was buying your first computer. At that time, there were three levels to choose from: 8088, 80286, and 80386. There was also a newly introduced 80386sx, a hybrid 16/32-bit CPU. The screamers of the day ran at 16 MHz, and had maybe four megabytes of RAM. Both Windows and OS/2 were available.

Today, I'm writing this on a 180-MHz Pentium Pro system with 64 megabytes of RAM, and a 1.6-GB hard drive. The CPU clock is more than ten times faster, the data bus is twice as wide, there is sixteen times as much memory, and sixteen times more disk space on this machine than a 1989 hotrod. In other words, that's  $10 \times 2 \times 16 \times 16$  or roughly  $5 \times 103$  times more powerful. Few in 1989 would have predicted 5000 times the power in only eight years. What do you think will happen in our industry by the time column 200 hits the stands? Hint: Moore's law, which states that semiconductor density doubles every eighteen months, is expected to continue unabated for another 20 years before real physical limits are reached. ■

# Think Tank

## Another Winner

BY JOHN J. YACONO  
TECHNICAL EDITOR  
WINDOWS MAGAZINE

Carlos Eduardo Corpeno Dubon has sent in more than enough good circuits to fill this month's column. He'll be rewarded with the customary MCL1010 chip and a kit, in addition to the book we award for single submissions. If you'd like to take a shot at a book or the whole sha-bang, send a schematic and complete description of your circuit(s) to *Think Tank*, Popular Electronics, 500 Bi-County Blvd., Farmingdale, NY 11735.

Before we get to Carlos' circuits, let's continue our discussion on diodes. As I've mentioned in the past, although they're typically used to rectify current (permitting it to flow in only one direction), they can also be used as voltage sources, control-signal generators, or voltage references.

One rudimentary way to make a diode voltage source is to tap an ordinary diode's barrier potential—the voltage that develops across when it's forward biased. The barrier potential is around 0.7 volts for silicon-based diodes and 0.3 volts for germanium units. Note I said "around." In the real world, the potential is not a precise value. It changes with temperature, manufacturing processes, and other factors. So this method doesn't generate a precise or even constant voltage. But that's sometimes okay to power a forgiving analog circuit. It's also useful for generating voltages of an approximate value to signal the presence of current flow in a circuit, perhaps to trigger another circuit. In this context, the diode generates a control signal of some acceptable value, rather than a precise voltage.

To help visualize the concept, take a look at Fig. 1. Figure 1A shows a simple circuit in which an LED will light to indicate when the load receives at least enough current to illuminate the LED. The indicator is useful to signal when the voltage source switches on or off, or when the load resistance drops enough to permit sufficient current flow. (Note the LED just represents any current-sensitive indicator or circuit you want to activate when suffi-

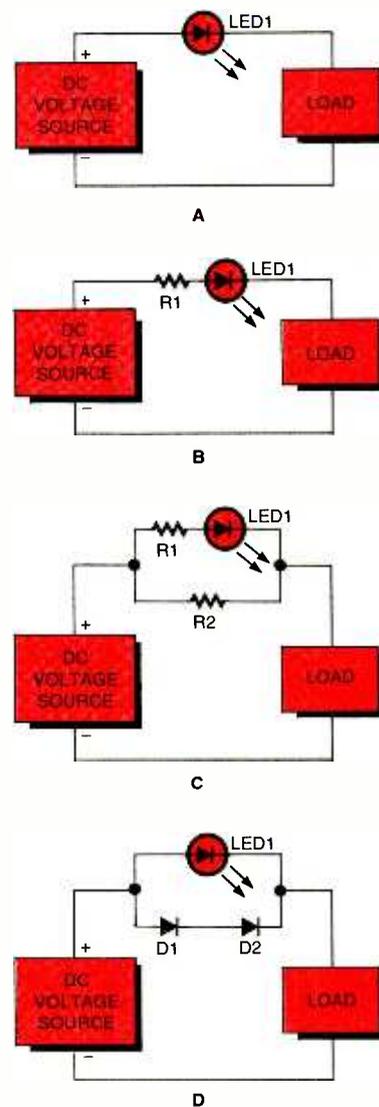


Fig. 1. Here are some ways to connect an LED as an indicator that a load is receiving current: with the LED alone (A), with a resistor in series (B), with a resistor in series and one in parallel (C), and with two diodes in parallel (D). See text for how each configuration works.

cient current flows to the load.)

In this scenario the indicator circuit is both activated and powered by the current to the load, which could present a problem: If the load/source combination in question typically produces more current than the LED can stand, the circuit will surely blow the LED.

Placing a current-limiting resistor of

the right value in the circuit, as shown in Fig. 1B, can reduce the current flow to a safe value for the LED. Unfortunately, it'll also deprive the load of the current it requires for normal operation. So what's obviously needed is to separate the current paths of the load and LED.

To that end, in Fig. 1C we add another resistor (with a value lower than R1's) to permit sufficient current to the load. Another way to look at it is we are using the voltage drop across R2 as a power supply for the R1/LED1 pair. This solution is fine except in circuits where the load current varies to the point it becomes impossible to specify values for R1 and R2 to suit both the current-sensing device (in this case the LED) and the load. It's also not suitable if the load current is so great R2 must be a low-resistance, high-wattage unit that wastes too much power.

What's clearly needed in that circumstance is a voltage that's generated by current flowing to the load, but still fairly independent of the actual value of load current. Something that's better behaved and more predictable would be nice, too, especially if the voltage is to trigger some circuit, rather than just powering a resistor/LED pair.

To that end, check out Fig. 1D. Resistor R2 has been replaced by silicon diodes D1 and D2, while R1 has been dropped altogether. Now when current flows to the load, the barrier potential of the diodes produces a voltage drop across them, rather like the voltage drop across R2. The voltage drop is about 0.7 volts each and since they're in series, the voltage drops combine to supply the LED with around 1.4 volts—regardless of the load or voltage source. If current flows, provided the voltage is sufficient to bias the diodes, the LED will light. You can string more diodes together if a higher signal/supply voltage is needed for the circuit to be triggered/powered.

We'll continue this discussion on using diodes as voltage references and sources next time. Let's turn to the letters now.

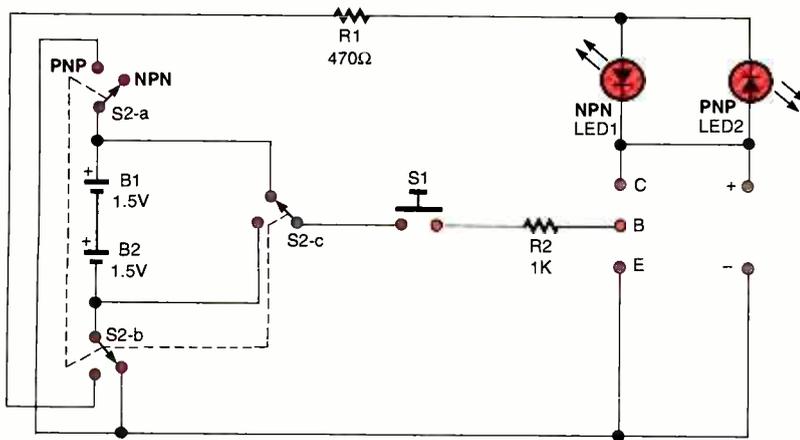


Fig. 2. This circuit is a great component checker that works by lighting corresponding LEDs.

## COMPONENT CHECKER

The circuit in Fig. 2 is a great component checker that works by lighting corresponding LEDs. If you insert a transistor's B and E leads (or a shorted transistor) to the C and E sockets, an LED will light, but you will know that the transistor is placed in the wrong position because the proper LED should light only when you press S1. You may want to use 5 sockets placed "C-E-B-C-E" to avoid bending the transistor leads. A bi-color LED may be used instead of the two plain LEDs shown.

With the transistor-lead sockets you can also check SCRs, LEDs, etc. For SCRs, place the polarity switch in the NPN position, and insert the A, K, and G leads in the C, E, and B sockets, respectively. Momentarily press S1 and the "NPN" LED should light and stay on when you release the switch. To check LEDs, place the polarity switch in the NPN position, and insert the LEDs anode and cathode in the B and E sockets, respectively. Pressing

S1 should cause a good LED under test to light.

There are two more sockets, labeled "+" and "-", which can be used to check diodes, continuity, capacitors, etc. To check a diode, place the polarity switch in the NPN position, insert the diode placing its anode and cathode into the + and - sockets. Press S1, the "NPN" LED should light. To check continuity, place the polarity switch in any position, insert test leads into the + and - sockets, press S1, and a polarity LED should light if the path under test conducts.

To check capacitors, insert the capacitor leads with the correct polarity in the + and - sockets. Then rapidly change the polarity to PNP, then to NPN, then back to PNP. The LEDs should light alternatively. This test only checks charge and discharge, not capacitance value.

—Carlos Eduardo Corpeno Dubon, Comayaguela, Honduras

For this type of test circuit, I like using SIP sockets to accept test leads.


A strand of 5 positions for the C-E-B-C-E socket and 2 separate sockets for the + and - terminals. Alternatively, you can chop up an IC socket with a hacksaw or MotoTool to make the strips you need.

## REMOTE CONTROL

Figure 3 shows a remote-control transmitter and receiver. The theory of the circuit's operation is very simple. The transmitter (Fig. 3A) generates IR light pulses at a frequency of 320 Hz (set in part by R2). The pulses arrive at the collector of the phototransistor and are amplified by the 2N2222 transistor. An NE567, IC2, is tuned to 320 Hz (by R6), so if pulses of any other frequency arrive at the phototransistor, the NE567 recognizes this frequency and pulls its output low.

If you wish to change the NE567's operating frequency, you'll have to adjust R2 and R6 to the same value. Keep in mind that the NE567 will work between 100 Hz and 1 kHz. You can also add more resistors (for more frequencies) instead of R2, and more NE567s tuned at the desired frequencies in order to make a multi-channel remote control system.

If you want to control a DC motor, a momentary load or an on/off load, there are some useful interface circuits in Fig. 4. Figure 4A shows a DC-motor controller that requires the outputs of two different channels (CH1 and CH2). Note that it doesn't matter if the channel outputs are active low or high; what matters is that CH1 must be different from CH2 for the motor to be energized. The circuits in Figs. 4B and 4C are momentary load controllers for

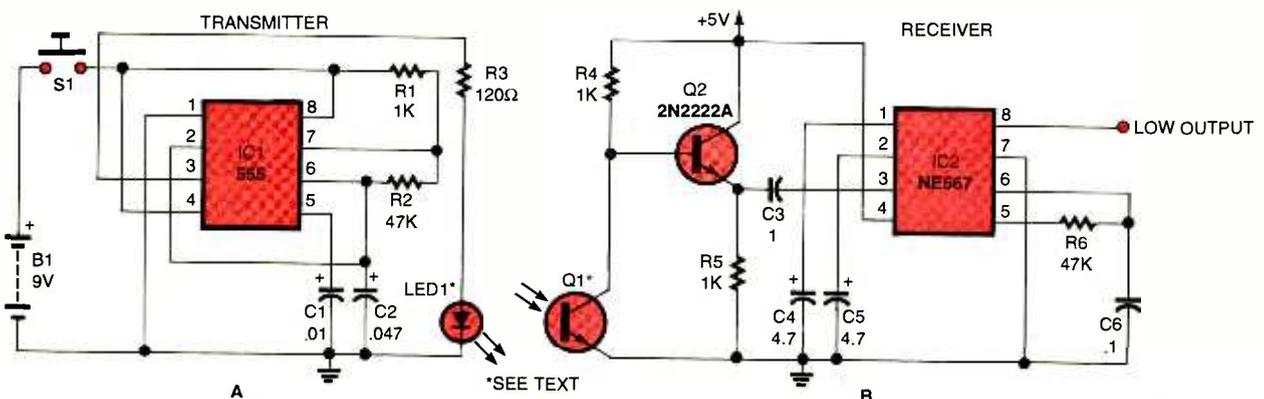

both active high and low channel outputs, respectively. The circuit in Fig. 4D is a toggled-load controller. If you have an active-high channel output, you must add the inverter shown.

—Carlos Eduardo Corpeno Dubon, Comayaguela, Honduras

I'd recommend a lens system for the transmitter and receiver. Also be sure the IR components are a matched pair.

## LOGIC PROBE

Figure 5 shows the schematic for a versatile logic probe. The Zener diode clamps the input signal just above the TTL inverter's 2.2-volt trigger voltage. Zener-diode D1 can be left out if the probe is going to be used on only TTL circuits.

The logic probe is based mainly on inverters IC1-a and IC1-b, which are sections of a 7404 integrated circuit. Depending on whether the input is high or low, the inverters enable AND gate IC2-a or IC2-b, which are sections of a 4081. Each AND gate is connected to an oscillator, one low-frequency the other high. When an AND gate is made high, it passes the frequency of its oscillator to the Piezo buzzer (BZ1). Whenever there's a high at the input, the buzzer will produce the high tone, whenever there's a low at the input, the buzzer will sound the low tone.

With switch S2 in the "pulse" position, if there are pulses present at the input, a yellow LED will light and the buzzer will sound at the frequency of the pulses.

The CMOS/TTL switch selects the voltage from the circuit under test or the voltage from the 7805 regulator. Note that when this switch is in the TTL position, it can only work with 5-volts DC, but when the switch is in the CMOS position, it can work from 7.5- to 35-volts DC.

Since this circuit is intended for TTL and CMOS circuits, a 4049 can be used instead of the 7404, simplifying all the CMOS/TTL switching. But the only inverter available at the time of construction was the 7404.

—Carlos Eduardo Corpeno Dubon, Comayaguela, Honduras

A pulse stretcher at the input would be a nice addition for detecting brief pulses. A latch circuit at the output would also be useful for catching intermittent events.

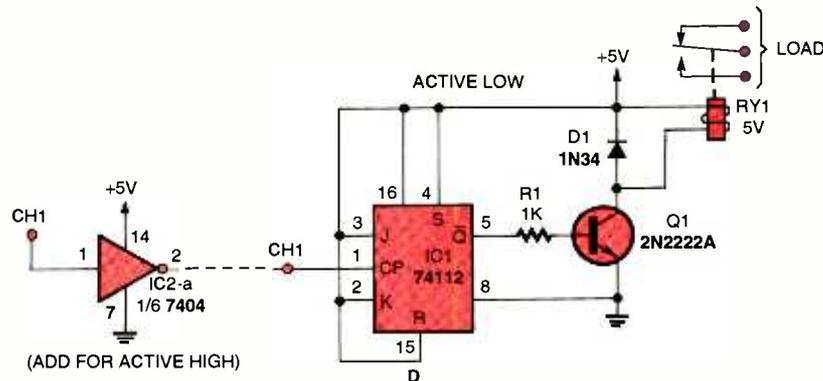
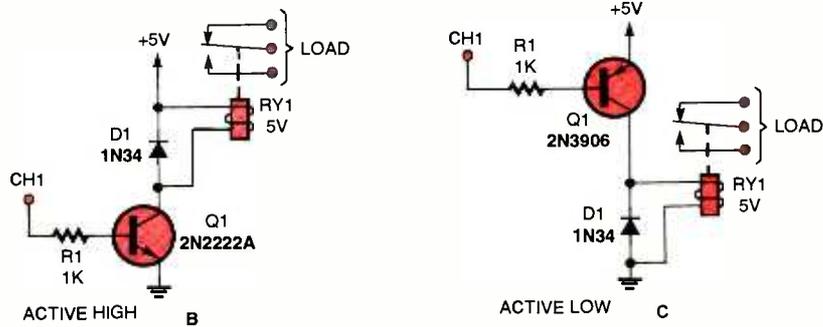
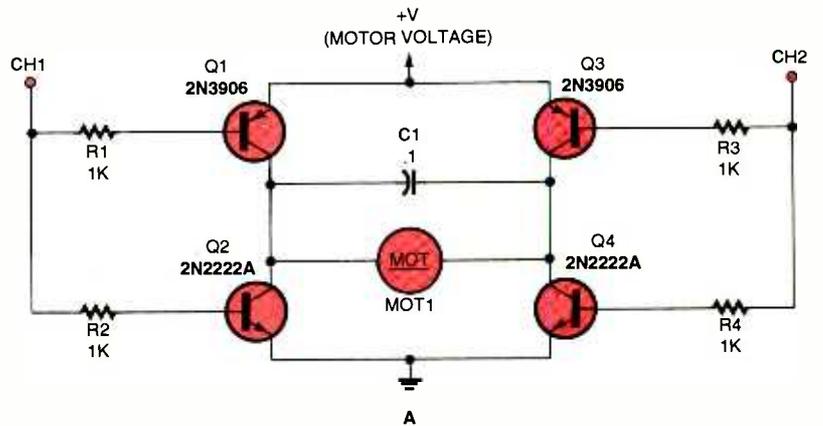


Fig. 4. These circuits work with the remote control in Fig. 3. There's a DC-motor controller, momentary load controllers for both active high- (B) and low-channel (C) outputs, and a toggled-load controller (D).

## MODEM PROTECTOR

A common problem in modem communication is that family members often pickup extensions during a modem call. In order to prevent this problem, I looked for modem-protection circuits, but all I found was a semiconductor (apparently an SBS), which had to be connected in series with each phone extension. I tried that semiconductor, but sometimes it just didn't work. So, I made the circuit in Fig. 6 because I thought it would be better to completely disconnect all the other phones whenever I'd like to use my modem.

The purpose of the LED is to indicate when S1 is in the Modem position but there's no modem connection. This LED is included because sometimes I left home with the switch in the Modem position, leaving my family phoneless! The LED is off when S1 is in the Telephone position or if the modem's in use. The indicator will also light alternatively if you've got S1 set to modem during an incoming call, letting the user know that the phone should be ringing.

Note that this circuit induces some noise when the switch is moved to a different position; however, this noise,

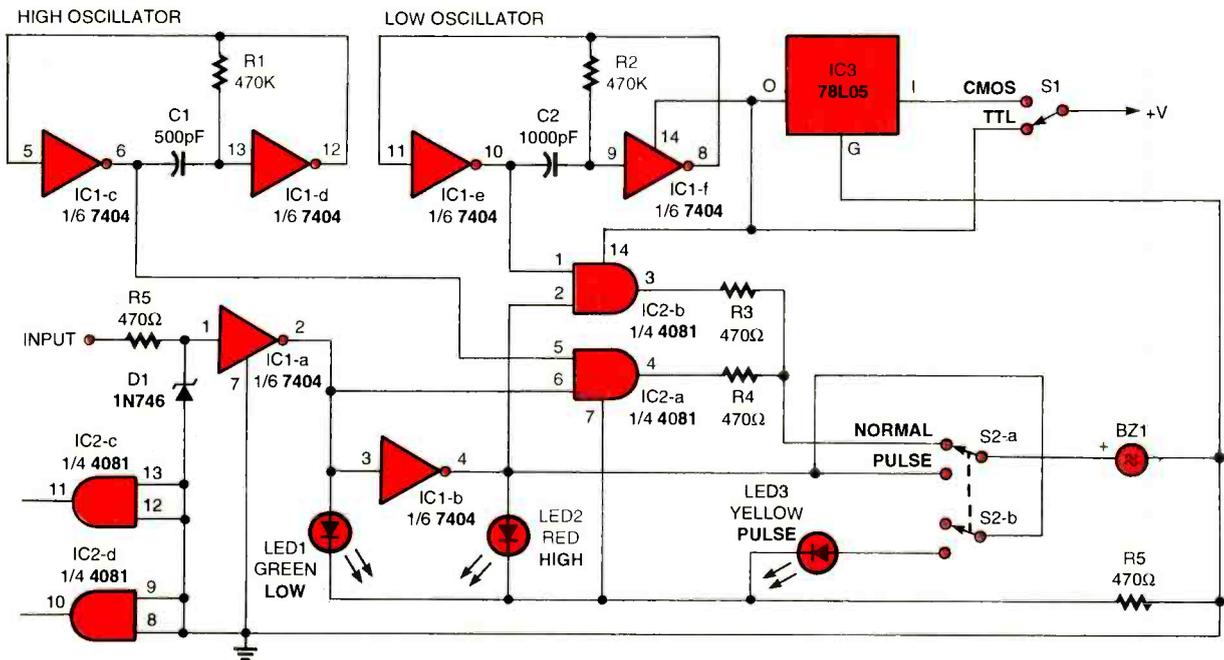


Fig. 5. Here's a versatile logic probe that's sure to impress any hobbyist.

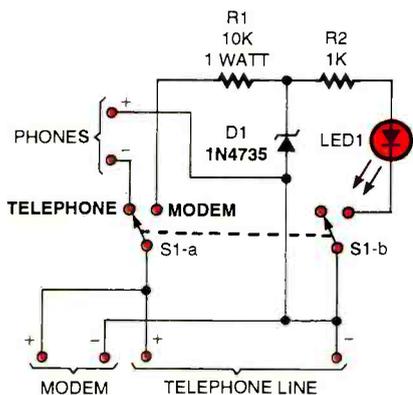


Fig. 6. Forget about having your downloads messed up by someone lifting a phone. This circuit completely disconnects all phones on a line when you are using a modem.

unlike the phone-pickup noise, doesn't make a pulse. So, if you have a pulse line, it's OK to switch while dialing. But remember never to move the switch while using your modem, always do it before dialing instead.

—Carlos Eduardo Corpeno Dubon, Comayaguela, Honduras

*Nice thinking. One last thing, this circuit should obviously be installed in front of the first telephone in the home circuit.*


### DESIRED-WAVEFORM GENERATOR

I designed the circuit in Fig. 7 with a friend of mine. It is a filtered step-func-

tion generator in which the wave amplitude at each step is set by a linear potentiometer (R1-R4). By arranging the potentiometers in time order and side-by-side (the way they are in a graphic equalizer) the position of the knobs describe the output waveform.

The 555 oscillator, controlled by R5 and C1 or C2, sets the duration of each step, and therefore also the wave frequency. Potentiometer R5 controls the step frequency and the capacitors define the frequency range. If you wish to extend the frequency range, you may want to add some more capacitors, switched by a switch with more

*continued on page 74*

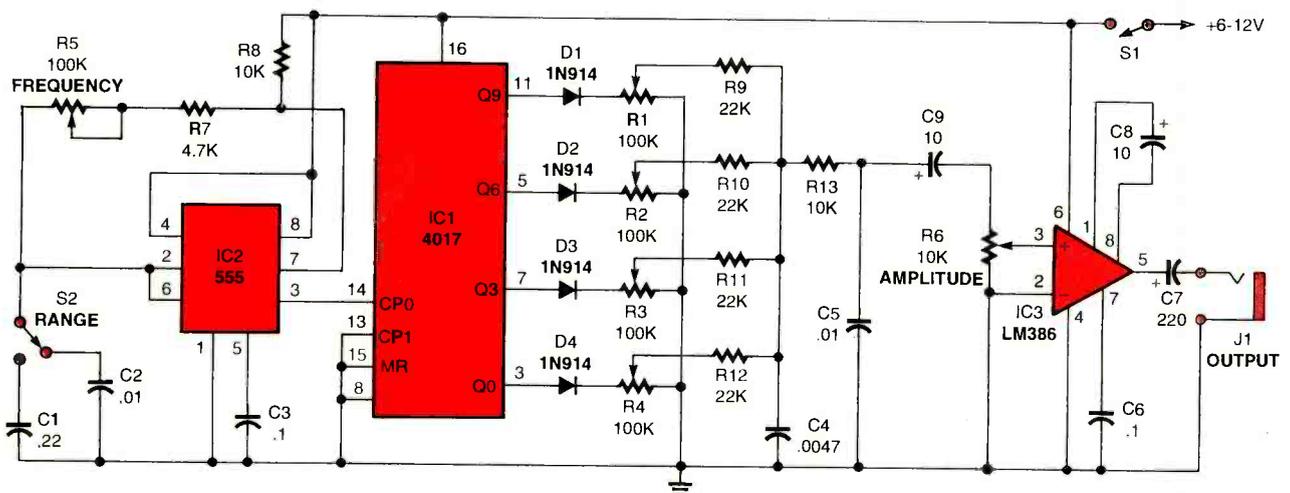

# ANTIQUE Radio

## Mailbag Time!

BY MARC ELLIS

It's been a while since we looked at the mailbag, so let's go through it now and see what's been piling up!

### STAR ROAMER MEMORIES

A good place to start, I think, would be with the comments that have accumulated on the recent Star Roamer restoration. Here's a quote from reader Dean Huster (Oklahoma City, OK):

receivers: the *middle of the line* Star Roamer, The R-55A, and the R-100A. (You may have been confused by the advertising, which may have emphasized the R-55A and R-100A as ham-band receivers. I assure you that they were general-coverage receivers with ham-band-only bandspread dials.)"

Dean's analysis of my thinking was accurate. I was comparing the Star Roamer with simple regenerative

The Star Roamer probably had appeal for both groups, although, as Dean suggests in his interesting letter, it had serious shortcomings as a ham set.

The Star Roamer series also resonated for Ron Rumble (Schaumburg, IL) because he built one in 1964 and has recently gone over the old kit and upgraded the circuitry. He substituted a full-wave rectifier for the selenium stack, put in larger filter capacitors, and installed a Zener-stabilized supply to supply key plate and screen voltages. Several improvements were made in the audio circuitry, and a serious noise-limiter circuit from an ARRL handbook replaced the perfunctory original hookup.

He also mounted the broadcast loopstick antenna on standoffs *outside* the perforated back (actually, I mounted mine similarly, assuming it was the original position). Moving that antenna further from the metal cabinet greatly increased sensitivity. A small winding was also added to the "cold" end of the loop to allow for the use of an outside antenna—an option not originally available on the broadcast band.

Talking about his modifications, Ron says: "This is what I would have done when I assembled the kit, had the technology been available 30 years ago. Granted, this is something like upgrading a Ford Model A to a Ford Escort engine, 12-volt electrical system, and hydraulic brakes. Some people wouldn't like the result, but I would rather use a *new* Model A to take me to and from work every day."

Howard Krausse (Ann Arbor, MI) writes that the Star Roamer was his first shortwave radio as well as his first electronic kit. He was so excited when he got the kit (he was 12 years old at the time) that he began working on it minutes after it arrived at the house, and continued non-stop until it was done. It worked well, and he's never forgotten the thrill of receiving those first shortwave stations.


Later, Howard (reluctantly) sold the Star Roamer for \$15, which he put toward his first ham station (he is now



One of the three "low-end" regenerative receiver kits offered by Allied in the 1960's.

"I have to take exception with your statement that the Knight Kit Star Roamer 'was the top of the line of Knight shortwave receiver kits.' ... At the time, Knight-Kit made three decent

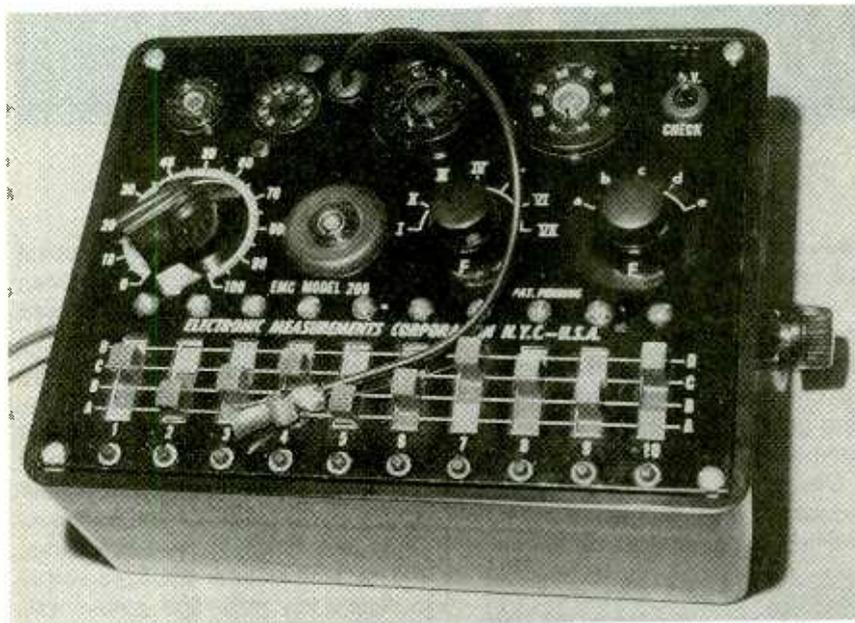Knight Kit receivers such as the Span Master, Ocean Hopper, and Space Spanner—which were aimed at the less well-heeled shortwave listener rather than the ham-radio operator.



Can anyone help Doug Fox with the data on this cute little EMC 208 tube tester? (See text for details.)

KE8M). Last year, he had an opportunity to buy a mint Star Roamer, also for \$15, at the Dayton Hamvention and snapped it up. Says Howard, "The set works as well or better than my original, and the stations it picks up are somehow more exciting than the ones I receive on my fancy Japanese rig!"

Don Rapp (Ste. Genevieve, MO) acquired his Star Roamer as a Christmas gift when he was about 13. He still has the set, which he credits with sparking his interest in an electrical engineering career. Don replaced the filter caps about 15 years ago, and still takes out the set from time to time to do some listening. He has some interesting things to say about the therapeutic value of working with the technology of a less frantic era:

"Although I work with computers and do industrial controls professionally, there is something missing in the level of understanding associated with the new technology .... Knowledge and technology turn over in shorter and shorter time periods such that we are now in what seems like a perpetual learning curve to the future. I enjoy learning, but when you have to spend all your waking hours in pursuit of techno-knowledge, even the enjoyable can become a burden."

Thanks also to Earl Amdale (Palmer, AK), who sent along Star Roamer information and offered assistance. And a bit thank-you to Larry Cook (362 East South Street, Richland

Center, WI 53581-2721), who has a complete Star Roamer manual and offers to make copies for anyone needing one.

## BOAK CARTER REPRISE

W.R. Cobb (Laguna Hills, CA) writes: "I hate to keep harping on the subject of Boak Carter, but errors must be corrected before they become Gospel. You stated that he was a local New York City reporter (*Antique Radio*, July, 1996), but we regularly listened to him in Portland, Oregon. He was as well known as *Walter Winchell*."

G.L. Johnson (Wonewoc, WI) tells us that Boak was heard in the Milwaukee area in the later 1930's, probably on a Chicago station. His accent sounded "English" to the youthful Johnson's ears, and his standard sign-off was a grave and dignified "... and so Philco and I say to you, cheerio."

And, finally, here are some comments from reader L.D. Kelsey, NP4RH (Old San Juan, PR): "I recall clearly that Boak Carter was definitely on a nationwide hookup in the 1930's and part of the 40's. I regularly listened to him in the San Francisco area at about the same time in the afternoon as H. Von Kaltenborn and others did their broadcasts. Boak Carter was one of our better news commentators during the period when the nation was gradually awakening from its isolationist phase ..."

## LITERATURE AND PARTS FOR SALE

Because of the fairly long interval between our "mailbag" columns, and the fact that some three months go by between the time I write this column and the time it appears in print, the items below might no longer be available. Still, if you are interested, it would be worth the price of a postcard to inquire.

John K. Walcott (1862 Spruce Lane, Benbrook, TX 76126) has a large collection of radio parts dating from the late 1920's through the '40's. He has no use for the parts and would like to put them in the hands of people who share his interest in preserving things of the past. John would like to make contact with a radio-collector's club in his area to arrange a deal. Price is negotiable but he'd like it to be fair. Because his own collecting interests center around antique tools, there might be an opportunity for some horse trading.

Old literature enthusiasts might want to contact H.H. Bloom (Soundmaster, Ltd., 386 MacLaren Street, Ottawa, Canada K2P 0M8). He is interested in selling a collection of many old and well-preserved electronic catalogs.

## HELP WANTED!

When he was a boy, Bob Firhau (108 South Ellyn Street, Glenn Ellyn, IL 60137) built a "pocket" shortwave radio from plans in a circa-1934 issue of *Short Wave Craft*. It used a type 30 tube. The whole thing was housed in a Gorton's Codfish box that measured about 4x6x2 inches. Four-prong plug-in coils, wound on old '80 tube bases covered the broadcast band through 19 meters. Power came from two "D" cells and a small 45-volt battery.

Bob heard World War II unfold on this hot little set, which picked up a good selection of Allied and Axis stations. He'd like to recreate it—if he could find the original construction article. He'd also like to find a source for a type 30 tube or suggestions for transistorizing the circuit.

Julio Diaz Gonzalez (RR#3, Box 5022, Rio Piedras, San Juan, PR 00926) is looking for a good source of old radio parts, particularly five-prong tube sockets. Coincidentally, around the same time I received a letter from

*continued on page 74*

# SCANNER SCENE

## Variety is the Spice of Scanning

BY MARC SAXON

**R**adioShack has brought forth a nifty new mobile MHz inhaler dubbed the PRO-2046. It's amazing how these small mobile scanners can now incorporate many of the sophisticated and advanced features that once were the in the exclusive realm of desktop units.

Basically, the PRO-2046 provides 100 memory channels plus 10 more monitor channels. The frequency coverage takes in the 29- to 54-, 137- to 174-, and 806- to 956-MHz FM bands

The IF frequencies are 10.85 MHz and 450 kHz. Selectivity at  $\pm 11$  kHz is  $-6$  dB; at  $\pm 15$  kHz, it's  $-50$  dB. Sensitivity is rated at  $0.7 \mu\text{V}$  between 137 and 512 MHz, at  $0.5 \mu\text{V}$  below 54 MHz, and  $0.8 \mu\text{V}$  above 806 MHz. In the VHF aeronautics band, it is  $2.0 \mu\text{V}$ .

The PRO-2046 comes in a slick-looking package that weighs a tad over two pounds. This is a lot of radio for any mobile unit. You might want to check it out at your nearest RadioShack.



RadioShack's PRO-2046 packs a lot of features into a mobile scanner.

(except for the cell phone bands). It also receives the 108- to 137-MHz VHF aeronautics band. The memories, which are set up in 10 banks of 10 channels each, will retain stored data for at least 14 days without power.

Front-panel buttons permit instant scanning of preset VHF police, fire, emergency, Department of Transportation, highway, and other public-service channels. Of course, you can search out new frequencies, too. The PRO-2046 allows you to do it in 12 preset frequency ranges. While it's searching, it can skip over unwanted data signals plus any 20 other user-selected frequencies. Normal search/scan speed is 50 channels per second, but while searching it will do 100 channels per second and, between 29 and 54 MHz and 137 and 174 MHz, it will sort through up to 300 channels per second.

### WHICH ARE YOU?

Ron Cunningham, of Ontario, Canada, wrote to say that his friends sometimes tell him that they have become bored with scanning. He thinks it's because folks seem to get locked into one type of listening out of habit, forgetting that there are variations on a theme. He suggests that if you sometimes think that you're getting into a scanning rut, try mixing in one or more other approaches to the hobby, just to add some spice.

You say there's only one approach? No way!

One popular way to use a scanner is to spend most of the time monitoring the same group of agencies or frequencies in order to monitor their communications traffic.

Another way is to look up the frequencies of specific agencies and

companies that you have never before monitored, especially ones that are semi-local to you. Then see if you can receive them. Are your skills and equipment good enough to drag in those stations from the surrounding counties? You don't necessarily have to be fascinated by the contents of the communications traffic. Just pull it in and log it.

Then, another way to enjoy a scanner is by entering low and high frequency limits so that the radio can search through the spectrum, rooting out previously unknown stations and frequencies. Who knows what amazing new things you might discover, particularly in those bands that you seldom or never tune—such as 30-44, 72-76, and 148-150 MHz. Search in segments of no more than 1 MHz at a time, and plan to spend at least an hour or two before moving on to the next segment.

A worthy way to participate in the monitoring hobby is to concentrate one's efforts on a particular category of stations, seeing how many you can log. For instance, how many different law-enforcement agencies can you monitor from your location? How many hospitals? How many private security forces? There you go!

### V-LINK COMMUNICATORS

Several requests have come in asking if we know of the frequencies used by the 19-channel V-Link handheld communicators—license-free units intended to look like cellular phones. They are said to be sold for about \$70 at WalMart and several other large chains, including Toys-R-Us.

Actually, we did not know the frequencies for the V-Links. But reader Larry Burkett, of Lexington, Kentucky, was kind enough to send in a listing of all 19 V-Link channels. That solved our dilemma, so be sure to keep this information handy.

Beginning with Calling Channel 1,

and going through to Calling Channel 19, the frequencies are: 916.875, 915.8625, 915.00, 914.0875, 913.3375, 912.000, 910.9125, 910.2375, 909.3375, 908.500, 907.6625, 907.000, 906.3375, 905.6625, 904.500, 903.4865, 903.000, and 902.500 MHz. Yes, it looks odd, but it's not an error! Calling Channel 1 is the highest frequency, and the frequencies descend to the lowest one at the highest numbered Calling Channel.

## MAIL SACK

A note from David W. Jones, of Citrus Heights, California, provides information on the local U.S. Postal Service motor-vehicle services channel (on-the-road vehicles, mechanics, fleet control). The frequency is 164.985 MHz. David also mentions that the U.S. Postal Inspection Service tactical and surveillance frequencies in his area (see above) are 488.225 and 488.675 MHz, and notes that the operations are in WFM mode.

## AN OLD CUSTOM

If you have ever monitored 165.2375 MHz, then you've heard one of the busy operational channels of the U.S. Customs Service. Field portable and mobile units on the frequency identify by coded unit numbers that denote their type. According to the Radio Monitors Newsletter of Maryland (P.O. Box 394, Hampstead, MD 21074-0394), Alpha numbers are individual Customs Service agents, while India series numbers represent Customs Inspectors. Lima numbers are Customs aircraft, Mike units are vessels, and Papa numbers denote vehicles. If you hear a Kilo number on the Customs channel, it's an FBI aircraft.

It might be worth noting that FBI aircraft operating on FBI and other frequencies usually identify with Idaho numbers. In addition, U.S. Customs aircraft on surveillance missions often identify by the code name Omaha followed by numerals.

That's a wrap for this month, but be sure to join next time. We are always looking forward to hearing from you with information or questions about our hobby, reports on new frequencies you have discovered, suggestions or whatever. If it relates to VHF/UHF monitoring or scanning, write to *Scanner Scene*, **Popular Electronics**, 500 Bi-County Blvd., Farmingdale, NY 11735. ■

## ANTIQUÉ RADIO

(continued from page 72)

Dave Eley (Surrey, BC, Canada) recommending Steinmetz Electronics (7519 Maplewood Avenue, Hammond, IN 56324; Tel: 219-931-9316) as a gracious and resourceful parts source. Steinmetz welcomes inquiries for odd-ball items, but asks that they be accompanied by a #10 self-addressed stamped envelope.

New to the antique-radio hobby, 17-year-old Sean Barton, KB0OVD (RT-1 Box 247, Troy, MO 63379) has requested help with a couple of specific problems: 1) What markings were originally around the knobs of the Philco 39-35, and where can one obtain "Philco Style" square rubber shock mounts; and 2) Can someone supply a description or a good photo of the unusual grille cloth used on the Grigsby-Grunow Majestic 130A?

Joseph T. Coyle (1 South Maple Street, Corning, NY) accidentally left his AK Model 36 on all night and experienced a power-supply meltdown. The result: potting goo running all over the place. Joe's idea is to build a replacement supply. He wants to know how to determine the operating voltages to be placed on the 13-lead "umbilical" cable. An experienced restorer might be able to help Joe salvage the original supply.

Another person who sounds as if he is just getting his feet wet in the antique-radio hobby is about to come into possession of an early 1920's radio (not specified) and a 1940's Philco console. He has asked for advice on parts sources and restoration procedures. Stan Dereska lives at 5912 Dinwiddie Street, Springfield, VA 22150. Please contact him if you'd like to share your knowledge.

R. Buchborn (Astabula, OH), Phil Fries (Bayside, NY), and anyone else who would like to know more about the "full wave" crystal set, discussed in the October 1996 *Antique Radio* column, might like to try contacting the builder directly by mail. He is Gustaf O. Linja (848 Eighth Street, Lake Linden, MI 49945). Be sure to enclose a self-addressed stamped envelope if a reply is expected.

That's all for now. In the meantime, let us know about the pieces you have found or added to your collection. See you next month! ■

## THINK TANK

(continued from page 70)

poles than S2. (If you want to change the frequency, remember that the 4017 works up to a few MHz.)

The output of the 555 is applied to the clock input for the 4017 decimal counter, which activates its outputs one at a time. The linear potentiometers divide the voltage of each output, and thus determine the output voltage at a given step point. The schematic only shows potentiometers in Q0, Q3, Q6, and Q9, but for smoother waveforms there should be potentiometers at all the outputs except the Carry-Out pin. The composite waveform is now purified by the filter formed by R13, C4, and C5, so the output will be rounded.

The amplitude is controlled by the LM386 audio amplifier's input. If you're going to use the circuit for high frequencies, I recommend replacing the amplifier with a 741 or other high-frequency op-amp, provided you change some of the op-amp's external components.

—Carlos Eduardo Corpeno Dubon, Comayaguela, Honduras

*That's a real neat concept. Note that if you want more steps it is possible to wire in another 4017 and some logic so that each counter takes a turn counting. Hint: each counter's halt input (pin 13) should be connected to its tenth output (pin 11). That output should not have a linear potentiometer. Also, each chip's tenth output should supply a reset pulse to the other chip through some kind of pulse generator.*

That's all for this month. See you next month with more interesting circuits and such. ■



*"No, I didn't bring extra batteries. These are rechargeable types!"*


# Market Center <sup>TM</sup>

## Paperback Books

GREAT BOOKS AT BUDGET PRICES



**100 RADIO HOOKUPS**  
—#7—\$3.00

First published in May, 1923 this popular booklet went into reprint editions nine times. It is packed with circuits, theory, antenna installation and tips on consumer radio receivers that were popular in the early 1920's. Antique radio buffs and those inquisitive about the early days of radio will find this booklet an exciting, invaluable and excellent reference into the minds of early-day radio listeners. Sorry, we cannot honor the original 25-cent cover price.

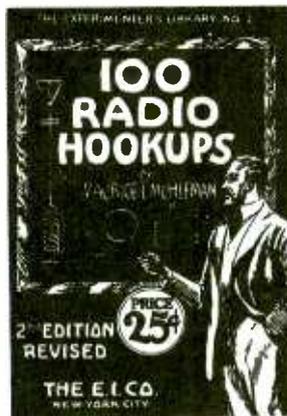


**INTERNATIONAL RADIO STATIONS GUIDE—BP255**  
—\$9.95

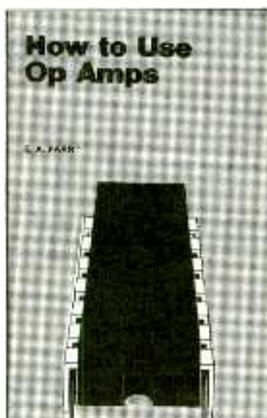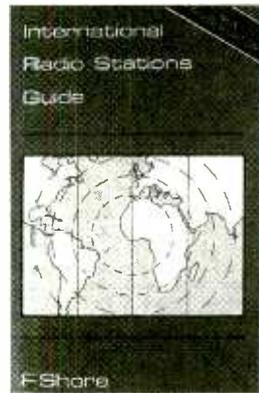Provides the casual listener, amateur radio DXer and the professional radio monitor with an essential reference work designed as a guide for listening to the complex radio bands. Includes coverage on Listening to Shortwave Radio, ITU Country Codes, Worldwide Radio Stations, European Long Wave and Medium Wave Stations, Broadcasts in English and more.



**HOW TO USE OP AMPS**  
—BP88—\$5.95

The engineer's best friend is the op amp. This basic building block is found in many circuits, analog and digital alike. The op amp finds many useful purposes such as: oscillators, inverters, isolators, high- and low-filters, notch and band-pass filters, noise generator, power supplies, audio, MIDI, and much more. Prepared as a designer's guide, some limited math is used, however engineers and hobbyists alike find it a useful text for their design needs.

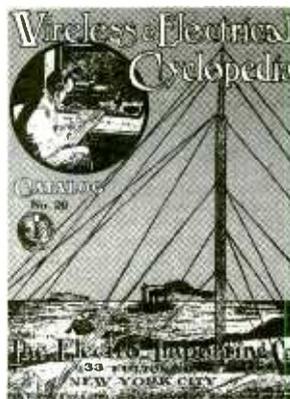

**WIRELESS & ELECTRICAL CYCLOPEDIA**  
—ETT1—\$5.75

A slice of history. This early electronics catalog was issued in 1918. It consists of 176 pages that document the early history of electricity, radio and electronics. It was the "bible" of the electrical experimenter of the period. Take a look at history and see how far we have come. And by the way, don't try to order any of the radio parts and receivers shown, it's very unlikely that it will be available.

**ELECTRONIC TECHNOLOGY TODAY INC.**  
P.O. BOX 240, Massapequa, NY 11762-0240

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

**SHIPPING CHARGES IN USA AND CANADA**

\$0.01 to \$5.00 .....	\$2.00
\$5.01 to \$10.00 .....	\$3.00
\$10.01 to 20.00 .....	\$4.00
\$20.01 to 30.00 .....	\$5.00
\$30.01 to 40.00 .....	\$6.00
\$40.01 to 50.00 .....	\$7.00
\$50.01 and above .....	\$8.50

**SORRY No orders accepted outside of USA & Canada**

Total price of merchandise ..... \$ \_\_\_\_\_  
Shipping (see chart) ..... \$ \_\_\_\_\_  
**Subtotal** ..... \$ \_\_\_\_\_  
Sales Tax (NYS only) ..... \$ \_\_\_\_\_  
**Total Enclosed** ..... \$ \_\_\_\_\_

Number of books ordered

**All payments must be in U.S. funds!**

ET01

### SPECIAL PROJECTS



We design/build/modify/repair/consult on any device / system / process / project electronic / computer / mechanical / optical (eg. phone/auto/security/Radionic/lab/energy/HV/EM/RF/radar/ultrasonic/IR/UV/commo) for business and personal/invention needs. Describe & include nonrefundable \$30 pre-engineering fee. Time & cost estimates sent in 7-10 days. Confidentiality guaranteed!

### OFF-THE-SHELF HARDWARE

Van Eck Systems ★ Data Card Reader/Writers ★ RF/EM/μWave/Radar/Ultrasonic/IR/Light/Sound Detectors/Xmitters/Jammers/Blasters ★ Security/Surveillance ★ EM Weapon Countermeasures ★ Neurophone/Rife/Crystal Radionics ★ Bug ★ Tap Detectors/Blasters ★ Lineman's Handsets ★ Phone Color Boxes ★ Voice Disguisers ★ ESS Infinity Devices ★ DTMF Decoders ★ Child Finder ★ Panic Button ★ Slot Machine Masters ★ Subliminal Mixer/Amps (Ultrasonic/Infrasonic) ★ TENS ★ Hearing Assistors ★ Electronic Dowzers ★ Shriek Modules ★ Ghost Detectors ★ Vortex Generators ★ Alien Braizblasters ★ 6th Sense Communicators ★ More! Order Catalog Today!!

### AUTOMATIC TELLER MACHINES



ATM crimes, abuses, vulnerabilities and defea exposed! 100+ methods detailed, include: Physical, Reg. E, cipher, PIN compromise, card counterfeiting, magnetic stripe, false front, TEMPEST, Van Eck, tapping, spoofing, inside job, super-cool, vibration, pulse, high voltage-others. Case histories, law, countermeasures, detailed security checklist, labeled internal photos, figures. ATMs contain up to \$250,000 in cash!

### PAGER (BEEPER) MANUAL



Describes in detail how Pagers work, different types and uses, frequencies, advantages over and uses with cellphones, and tips and tricks. Few Pagers are hacked and countermeasures. Includes plans for a Personal Pocket Paging System (xmitter and receiver).

### HACKING FAX MACHINES



Describes in detail how Fax Machines are hacked and countermeasures. Includes G3 Fax protocols, comono parameters, compression algorithms, Class 1 & Class 2 commands, Spy Fax Switcher, Fax Servers, FODs/FOCs, and Makeup/Terminating Codes. And insights into designing Fax interception devices and modifying existing Faxes into Stealth Faxes. Eye-popping and invaluable!

### PBX HACKING



PBXs are hacked to the tune of about \$8 Billion/yr! "PBX Hacking" exposes all issues relating to PBX hacking, including countermeasures. This manual was featured in Forbes Magazine! Shocking!

### VOICE MAIL HACKING



Exposes how Voire Mail Box systems are used and specific ways they are hacked. Includes ASPEN, MESSAGE CENTER, BIX, GENESIS, RSVP, CENTAGRAM, EZ, AUDIX, SYDNEY, PHONE MAIL, CINDY, SPERRY LINK, etc. A must for all users, hackers, and security personnel!

# TOP SECRET



NOT FOUND IN BOOKSTORES!

## CONSUMERTRONICS

P.O. Drawer 537 Alamogordo, NM 88311

### ORDER TODAY! 505-439-1776

Fax: 505-434-0234 (ORDERS ONLY)

Web Adventure: [www.tsc-global.com](http://www.tsc-global.com)

Established in 1971. Featured on CBS "60 Minutes," Forbes, New York Times. Add \$5 total S/H (US, Canada). Sold for educational purposes only. Postal M.O. is fastest. VISA, MCOCK. COD (\$49-\$999), add \$6.

### STOPPING POWER METERS



As reported on "60 MINUTES"! How devices can slow down (even stop) watt-hour meters - while loads draw full power! Device plugs into one outlet and normal loads into other outlets. Describes meter creep, overload droop, etc. Plans!

**THE I.G. MANUAL:** External magnetic ways (applied to meter) to slow down and stop power meters while drawing full loads. Plans. \$25.

**KW-HR METERS:** How watt-hour meters work, calibration, error modes (many), ANSI Standards, etc. Demand and Polyphase Meters. Experimental results to slow and stop meters by others. A real eye-opener! \$25.

Special! All 3 (above), Only \$59!

### BEYOND PHONE COLOR BOXES



Dozens of PCB's described - many circuits. Plus Call Forwarding, Conferencing, Phreak History, Glossary, Diverters, Extenders, Loops, REMOBS, Bridging Heads & Cans, Optocom, 3rd Party and many other non-box methods - more! \$29.

### MIND CONTROL



Fear increases over EM and ultrasonic mind control technologies - especially implants! Many more lies published than facts. Secret agents are often used for reporting back to covert organizations. Learn shocking truth about this bizarre phenomena! \$39.

### HACKING ANSWERING MACHINES



All the known ways answering machines are hacked to listen to and erase messages, and to convert them into mini-VMBs. Plus countermeasures - protect yourself from hackers/thieves! \$29.

### UNDER ATTACK!



Electromagnetic weapon attacks cause cancer, birth defects, and profound psychological and neurological disorders! This manual includes actual cases of EM attacks (we investigated)! Includes how to tell if you are under an EM attack, and specific countermeasures. Much more! Shocking! \$29.

### PHREAKING CALLER ID & ANI



Details on how they work and dozens of effective ways of defeating Caller ID, ANI, \*69, \*57, Call Blocking, \*67 etc. Also describes Caller ID, Orange, Beige, Cheese & CF Boxes, ESS, SS7, E-911, various Class services, CN/A, Non Pub DA, CAMA, DNR, 800-ECR, Diverters, LD Extenders, Centrex - much more! \$29.

### BY AN ORDER OF THE MAGNITUDE



The most comprehensive, hard-hitting, hi-tech survival book ever written! Topics include electronic, computer, comomo, chemistry, weaponry, cryptography, energy, concealment, revenge, alarm, disguise & ID change. Designs, tactics & strategies to survive an increasingly dangerous and brutal world. Field-expedient use of technology in various threat and conflict environments and scenarios. \$49.

### CELLULAR AND CORDLESS MODS

So explosive we can't even tell you what it's about! See our Catalog for our infamous cellphone mod guide - detailed, comprehensive, covers most makes - 10 times more info than any competitors' manual!

### THE ULTIMATE SUCCESS MANUAL



How to lie, cheat, steal, influence, and intimidate your way to success! Underpaid? Overworked? Harassed? Manipulated? Forget job performance. This manual outlines what it really takes to make it to the top in today's corporate BS world! \$19.

### INTERNET CONS & SCAMS



Net cons and related frauds now rake in \$2+Billion annually! Most are done with little fear of prosecution. Detailed, + countermeasures. \$29

### INTERNET TRACKING & TRACING



The Net is infected with spammers, stalkers, scammers, infectors, and other wrongdoers who hide behind its anonymity. Learn how to trace them down in this comprehensive, eye-popping manual! \$39

### COMPUTER PHREAKING



Describes in detail how computers penetrate each other, and how VIRUSES, TROJAN HORSES, WORMS, etc are implemented. Dozens of computer crime and abuse methods and countermeasures. Includes disk filled with hacker text files and utilities, and the legendary FLUSHOT+ protection system. Internet advice, password defeats, glossary - much more! Manual + PC Disk! \$39

### BEYOND VAN ECK PHREAKING



Eavesdropping on TV and computer video signals using an ordinary TV described in detail. Includes security industry reports. Range up to 1 KM. Plans include both the Consumertronics and the original Top Secret Van Eck designs! \$29

### CREDIT CARD SCAMS



Completely describes every known means of credit card fraud and scams, + countermeasures. Protect yourself! \$29

## OTHER EXCITING TITLES!

### CONS & SCAMS \$34

Most comprehensive manual on C&S available! Details 100s, their many variations, and countermeasures!

### STEALTH TECHNOLOGY \$29

Every known police radar error - stealth method and material used to minimize radar and laser reflections - tactic and strategy to fight speeding tickets!

### THE PLACAK REPORT \$39

How to read and decrypt the magnetic flux-reversals on popular credit and debit card magnetic stripes. How to determine the decrypted PIN, PAN, bank number, dates, number of uses remaining. No hardware needed!

### HIGH VOLTAGE DEVICES \$29

Many HV device plans: Stun Gun, Taser, Prod, Cane, Flasher, Blaster, Zapper, Radar Jammer, Jacob's Ladder, Fence Charger, Geiger Counter, Fish Stunner, much more!

### RADIONICS MANUAL \$29

Exciting electromagnetic therapeutic, diagnostic devices (mostly experimental). Descriptions, plans, availability.

### ROCKET'S RED GLARE \$29

The most definite and comprehensive source on solid-propellant survival and amateur rocketry! Many plans!

### FREE! \$19

How you can get FREE money, jobs, land, housing, meals, medical care, equipment, merchandise, much more!

### POLYGRAPH DEFEATS \$19

How anyone can tell "the truth" to a "lie detector". Many proven methods to beat the test, and what to avoid.

## SHOCKING!



ALL-NEW TOP SECRET CATALOG. FEATURES 200+ SURVIVAL PRODUCTS! WILL BLOW YOUR MIND! MAIL \$3, OR \$1 WITH ORDER!

### ORDER TODAY!!

Save up to **41%** POPULAR ELECTRONICS READERS! on select items! Take advantage of this tremendous offer. Call today, time is limited!

To take advantage of this offer, you must supply this special price code:

# MCM ELECTRONICS®

CODE: POP40

## Value And Selection From One Source...

- Test Equipment from Tenma, Fluke, Hitachi, Leader, B+K
- Name Brand and Low Cost Generic Technician's Tools
- OEM and Generic TV/VCR repair parts, and over 10,000 Semiconductors
- Gaming and Amusement Repair Parts and Accessories, Computer Hardware, Software, LAN Products and Printer Repair Parts

MCM offers a comprehensive line of tools and test equipment engineered for the repair of computers, TVs, VCRs and more. In addition, you will find a wide variety of OEM and low cost generic TV/VCR parts, passive components, Japanese and American semiconductors, over 30,000 items in all, stocked and ready to ship.

SAVE **34%**



### Aluminum Tool Case

Heavy-duty case is made of lightweight aluminum and designed to take rough field use. Attractive black finish holds up after years of use. Measures 19" x 14" x 6".

#21-3460 Reg. \$49.95 Sale **\$32.95**

SAVE **20%**



### RF Demodulator

The perfect solution to today's home theater applications. RF demodulator receives channel 3 in and gives you audio/video line level out. Operates on 16VDC, with included adaptor. Use your equipment to its fullest.

#33-2060 Reg. \$49.95 Sale **\$39.95**



TENMA®

### Autoranging DMM

3½ digit LCD DMM features 34 segment bargraph, AC/DC voltage measurement to 600V, AC/DC current to 10A and resistance to 32Mohm. Includes protective holster. Input Impedance 10Mohm. Requires 9V battery.

#72-2050 Reg. \$62.95 Sale **\$39.95**

SAVE **37%**

TENMA® Digital

### Solder Station

Ideal for most soldering applications including static sensitive devices. Closed loop control and digital readout offer precise operation from 320-900° F. A variety of replacement tips are available.

#21-1590 Reg. \$119.00 Sale **\$69.95**

SAVE **41%**



Prices Effective March 19, 1997 through May 31, 1997

Hours: M-F 7 a.m.-9 p.m., Sat. 9 a.m.-6 p.m., EST.

For complete information on the items listed, or a free catalog, call...

**1-800-543-4330**



MCM ELECTRONICS®  
650 CONGRESS PARK DR.  
CENTERVILLE, OH 45459  
A PREMIER FARNELL Company

FREE Catalog



MCM Electronics is now ISO 9002 Certified.



Certificate No. RS#35690

Authorized  
**Panasonic**  
Quasar/Technics  
Original Parts Distributor

CODE: POP40

REI/GE  
Premier Distributor

### Same Day Shipping!

In stock orders received by 5:00 p.m. (YOUR TIME), are shipped the same day from distribution centers near Reno, NV and Dayton, OH.

CIRCLE 149 ON FREE INFORMATION CARD

# AMAZING ELECTRONIC & SCIENTIFIC DEVICES

Lasers, Tesla, Ions, Anti-Gravity, Magnetics & More!

Plans • Ready-to-Use • Easy-to-Build Kits

**Laser Ray Gun**  
Handheld, battery operated. Produces an intense burst of light capable of burning holes.  
LAGUN2 Plans ..... \$20.00  
LAGUN2K Kit / Plans ..... Price on Req



**250KV Tesla Coil**  
10-14" of Explosive Bolts of Lightning!  
• Transmit Wireless Energy  
• Ion Motors  
• Anti-Gravity  
• Strange and bizarre pyrotechnical effects  
• Many other experiments shown in detail  
• Award winning science project!  
BTC3 Plans ..... \$15.00  
BTC3K Kit/Plans with coil ..... \$299.50  
BTC30 Assbl'd Ready to Use ..... \$399.50  
BTC4 Plans, 500KV unit ..... \$20.00



**ATTENTION: Experimenters & Researchers!**  
Anti-Gravity, Rail & Coil Guns, Mass Warping, Levitation Research, Exploding Water, Propulsion Drivers, Lattice Snapping, EMP etc. Loss-less Energy Charger with triggered spark switch. • Adjustable 500 to 3KV out • Charges up to 25KJ • Programmable Output  
HEP1 Plans ..... \$15.00  
HEP1K Kit/Plans with 500J ..... \$399.50  
HEP10 Lab Assembled - to your spec's.  
Write, call or fax for price & delivery



HEP10  
...shown connected to potential rail gun system


**Visible Beam Gas Lasers**  
Millions degree temp equiv. Illuminates low level clouds  
• Light Shows  
• Window Listener  
• Optical Projects  
• 12/115V  
• Science Project  
LAS1KM 1 mw, low cost Kit ..... \$69.50  
LGU6K 2-3mw Kit ..... \$119.50  
HNE70 5-7mw, ready to use ..... \$299.50



**Gravity Generator**  
Levitate an object!  
Great science fair project!  
GRA1 Plans ..... \$15.00  
GRA1K Power Supply Kit/Plans ..... \$99.50  
GRA10 Assbl'd Kit/Plans ..... \$149.50  
Includes text book on Anti-Gravity theory!



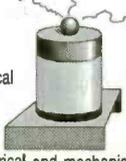**Solid State Tesla Coil**  
• Generate fiery electrical plasma discharge  
• Powers light and objects without contact  
• Experiment with electrical and mechanical fields. TCL5 Plans ..... \$8.00  
TCL5K Kit/Plans 12VDC ..... \$49.50



**Pioneer a Futuristic Weapon!**  
Electric Gun - prototype designed in our lab - Join the research!  
• Ballistic Velocities  
• Handheld • Battery Operated  
• Labelled as DANGEROUS Product  
Experiment now before it is classified as a firearm! EGUN1 Plans ..... \$20.00  
(Must be 21 for purchase of hardware)



**Ion Ray Gun**  
Project Energy!  
Star Wars technology demonstrates weapons potential. IOG7K Kit/Plans \$99.50



**"Talking" Plasma Globe**  
Spectacular color. Pulsates to music, sounds!. 8-9", with intensity and sound controls. PLASMA1 Ready to Use . \$79.50



**Electronic Hypnotizer** *Caution Required*  
Control their minds! Programmable audible and visual stimuli induces hypnotic trances. HYP2K Kit with Book ..... \$39.95  
EH2 Hypnosis Book & Plans ..... \$14.95



**We can design and build high voltage systems - to your specs!**  
Call or fax us with your requirements!

## TACTICAL ELECTRONICS

**Cybernetic Ear!**  
Enhances normal hearing 3-4 times!  
Adjustable volume control, fits easily into either ear. Many, many uses.  
Ready to Use!  
CYBEREAR .... \$19.95



**ALL NEW Telephone Line Grabber/Infinity Transmitter**  
Use tone phone anywhere in the world to:  
• Monitor your premises - avoid break-ins  
• Access ongoing calls - longwinded kids  
• Control up to 8 appliances in your home!  
• Re-direct costly toll calls from pay phones!  
TELCON3 Plans (credit to purch) .. \$ 10.00  
TELCON3K Plans/Kit ..... \$99.50  
TELCON30 Ready to Use ..... \$149.50



**Long Range "Ultra-Ear"** Parabolic Mic can hear a distant whisper!  
20" dish uses satellite technology to capture distant sounds. PMS5 Plans ..... \$ 8.00  
PMS5K Kit/Plans ..... \$149.50  
• Optional Wireless Retrofit transmits captured sounds to an FM radio.  
WM5K Kit for Wireless Option .... \$29.50



**Phasor Sonic Blast Pistol**  
Rids areas of unwanted pests. Trains and conditions wild and domestic animals. Great for barns, attics, cellars, gardens.  
PPP1K Kit/Plans ..... \$39.50



**3 Mi Telephone Xmitter**  
• Tune-able 80-130 Mhz • Undetectable  
• Only transmits when phone is used  
VWPM7K Kit/Plans ..... \$39.50



**3 Mi Voice Transmitter**  
• Ultra-Sensitive Mike  
• Crystal Clear  
• Tunes 80-130 Mhz.  
FMV1K Kit/Plans ..... \$39.50



**FireBall Gun**  
Shoots flaming ball - two shot capacity. Great for special effects and remote fire starting. CAUTION REQUIRED!  
FIREBALL Plans (dangerous product) . \$10.00



**Shocker Force Field/Vehicle Electrifier**  
Make hand and shock balls, shock wands and electrify objects. Great payback for those wiseguys!  
SHK1K Easy to Assemble Kit ..... \$19.50



**Extended Play Telephone Taping System**  
• Tapes Phone Conversation • Extends Tape X4 • Check Local Laws before using!  
TAP30X Ready to Use ..... \$84.50



**"Drop-In" (Imi) Telephone Transmitter**  
Easily tunable over FM radio. Never needs battery! #DROPIN Kit/Plans ..... \$ 19.95



**See In Total DARKNESS!**  
• High Quality IR Night Vision Scope with IR illuminator.  
SD10 Ready to Use ..... \$199.50



**Electric Charge Gun**  
Life is Precious - PROTECT IT!  
Stuns & immobilizes attackers 15 feet away! Check your state laws for legality. More knockdown power than most handguns. No permanent injury. ID coded.  
ECG1 Data (Creditable to purch) ..... \$10.00  
ECG10 Charge Gun, Ready to Use, Includes FREE Stun Gun! ..... \$249.50  
STUN GUNS - sold separately:  
STUN100 100,000 Volts ..... \$34.50  
STUN200 200,000 Volts ..... \$49.50



**3 Mi Tracker Transmitter**  
• Tunable Output  
• Uses FM Radio  
• Excellent Signal Beacon  
HOD1K Kit/Plans ..... \$39.50



**MIND CONTROL!**  
Places subjects under your control. Programmable audible & visual stimuli with biofeedback. Induces strange & bizarre hallucinations without drugs. Caution - not FDA approved.  
MIND2 Plans ..... \$15.00  
MIND2K Kit and Plans ..... \$49.50  
MIND20 Assembled Unit ..... \$69.50



**FANTASTIC BRIGHTNESS!**  
High Quality Laser Pointer  
LAPN64 15mw equiv, 2000' ..... \$39.50  
LAPN61 50mw equiv, 4000' ..... \$84.50



**Window Bounce Laser Listener**  
Aim at window and listen to sounds from reflected light. -CAUTION- Not for illegal use. LWB3 Plans ..... \$10.00  
LWB3K Kit/Plans (req's vid tripod) ..... \$149.50



**1000' Potato Cannon**  
Not a Toy! Uses electronic or piezo ignition. CAUTION REQUIRED!  
POT1 Plans (dangerous product) ... \$10.00



**VISIT US ON THE WEB!**  
<http://www.amazing1.com>

**INFORMATION UNLIMITED**

Dept PEM-7, Box 716, Amherst, NH 03031  
Phone: 603-673-4730 FAX: 603-672-5406  
MC, VISA, COD, Checks accepted Please add \$5.00 S & H

**CATALOG!**  
FREE with Order or send \$1 P&H

24 Hour Phone  
**800-221-1705**  
Orders Only Please!

# DALBANI




CALL TOLL FREE  
1-800-325-2264

**\$20 MINIMUM ORDER  
CALL NOW FOR YOUR  
232 PAGE FREE CATALOG  
1-800-325-2264**

## HOT PRICES ON POPULAR SEMI'S

Order N°	Brand	Min	Price
BU-208	TESLA	10	\$1.49
BU-208/O	TOSHIBA	1	4.50
2N-3055	TESLA	10	0.60
2N-3773	TESLA	5	1.20
2SD-1398	SANYO	10	1.49
2SD-1650	SANYO	5	1.69
STRD-1005	SANKEN	1	4.15
STR-30130	SANKEN	1	2.66
STRS-6301	SANKEN	1	8.50
TA-7777N	TOSHIBA	1	6.96
TDA-2005	SGS	5	1.49

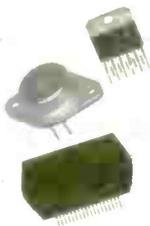

## COLOR CODED LEADS HEAVY DUTY ORDER N° 56-500

- 11" Long Wire Lead
- Insulated 1 1/2" Alligator Clips
- 20 Gauge Wire Size • 10 Leads
- BLACK, GREEN, RED, YELLOW, WHITE

**\$2.82**



## SOLDER WICK

- Solder Remover
- Length 5 Feet

**85¢**

Min. 2 pcs.



## TEMPERATURE CONTROLLED SOLDERING STATION

- Adjustable Temp.: 300°F - 790°F - 150°C - 480°C
- Grounded Tip for Soldering : Static Sensitive Devices, Heater Aid.
- Led Power Temperature Indicator
- Overheat Protection W/ Temperature Control
- Auxiliary Grounded Terminal
- Comes in digital LED display
- 48 Watts soldering iron

**\$64.00**



ORDER N° 51-1035

## CODE PE96

**PLEASE MENTION  
WHEN ORDERING**

Items are subject to availability.  
Prices are subject to change without  
any prior notice.

## FLYBACK TRANSFORMERS



**\$12.50**

Replaces  
GOLDSTAR 154-074R  
ORDER N° 63-0189

## TUN-O-WASH® ORDER N° 30-0100

**\$7.50**

(CFC Free)

Fast drying electronics  
grade cleaner for tuners,  
controls and PC boards.

TUN-O-WASH is excellent cleaner and  
degreaser for tuners, controllers and PC boards.

- Designed for cleaning and degreasing consumer electronics • Cleans in one step, no rinsing required • Contains no ozone depleting compounds • CFC and HCFC free
- Not for use on energized equipment
- 12.5 Oz aerosol (12 cans per case)

Chemtronics



## VCR ALIGNMENT TOOL KIT

ORDER # 50-888

The most popular

**\$24.99**

- VCR Head puller
- Retaining ring remover
- Spring hook
- Micro screwdriver
- Hex key set • Fitted vinyl • Soft zippered case
- Dimensions: 9 1/2"(W) X 12 1/4"(L)
- 7 Assorted head & guide aligners
- 3 Reverseable screwdrivers (Small-Flat-Philips)



## UNIQUE REALTIME OSCILLOSCOPE BUILT-IN FUNCTION GENERATOR

Order N° 50-820



1 MHZ FUNCTION  
GENERATOR

### Features

- Wider than specified frequency response • High deflection factor of 1mV/div. • Wide dynamic range up to 30MHz without waveform distortion • Algebraic sum of CH1 and CH2 • Low drift with compensation circuit • Superb trigger sensitivity • Maximum sweep rate of video signals with internal TV sync. separator • Jitterless trigger circuitry • CH1 signal output terminal available • Variable trigger hold-off • High precision X-Y phase difference measurement up to 50kHz • Built-in function generator with BNC output of 50Ω and TTL • Three kinds of waveform are available with 50Ω output • Flat output waveform frequency up to 1MHz

### Specifications:

- Vertical deflection: • Bandwidth: DC coupled (DC to 20MHz normal), AC coupled : (10Hz to 20MHz normal) • Deflection factor: 5mV/div to 5V/div in 10 calibrated steps of 1-2-5 sequence • Rise time: 17.5nS or less
- Horizontal deflection: • Time Base A: 0.2μs to 0.2S/div in 19 calibrated steps. 1-2-5 sequence • Uncalibrated continuous control between steps of at least 1: 2.5.



Manuf # OS-9020G

20MHz 2-CH DUAL TRACE



**\$498.00**

## DIGITAL MULTIMETERS

NEW! Digital

- Overload protect 1000VDC or peak AC on all other ranges
- Input Impedance 10M Ohm on all ranges • Base accuracy range ± 0.5 % to ± 1.0 % • Resistance 200Ω, 2K, 20K, 200K, 2M, 20M
- Audible continuity response lower than 50Ω • DC Voltage 200mV, 2V, 20V, 200V, 1000V
- AC Voltage 200mV, 2V, 20V, 200V, 700V

ORDER N° 50-815

## DALCO



**\$19.95**

## LOGIC Probe

ORDER N° 51-1015

- Length: 8 inches
- Range: 4.5 To 15 VDC
- Includes Test Leads • Compatible With TTL, DTL, RTL, HTL, CMOS, NMOS Logic

**\$8.99**

## SOLDER ROLL

- 1 LB Spool
- 370 deg F melting point
- Fastest solder
- Alloy 60/40, tin lead, non corrosive flux, Diam. 1.2mm

ORDER N° 51-1005

**\$3.95**



## Universal Audio/video Remote

ORDER N° 82-1055

- Controls basic functions of TV, VCR, cable box, and CD or laser player • Ergonomic design! Main buttons are in line with natural thumb motion • Two-minute memory allows time to replace batteries without re-programming • Programming reminder sticker inside battery compartment • Sleep time for 60, 30, or 15 minutes (according to your TV) • Set key recessed to prevent accidental deprogramming • Spanish instruction included. • Requires four AAA Batteries (not included)



## MAGNAVOX

Smart. Very smart

**\$9.95**

- Cable (11 brands)
- VCR (68 brands)
- TV (77 brands)
- Compact disc and Laser Disc (94 brands)

4225 N.W. 72nd AVE MIAMI, FLORIDA 33166 TEL : (305) 716-1016 FAX : (305) 594-6588

CIRCLE 48 ON FREE INFORMATION CARD


# WORLD'S SMALLEST

## Wireless Video Transmitters

Used by hundreds of hobbyists and professionals alike in R/C models, Robots, Surveillance Video, movie Special Effects, and Law Enforcement.

"... previously, I used expensive wireless units from Pelco, MVP, and Supercircuits. Nothing approaches the VidLinks in power, picture quality, size, and value. Thank you." *R. Leslie, CCTV Installer, NY.*  
 "The best... Incredible color, resolution... very easy to use... cool." *P. Davis, Movie Props, CA.*

**Actual Size!!!**

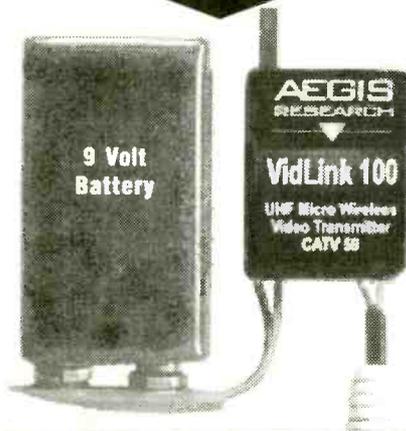

## Live Remote Video From \$99.00

- Full 100 mW RF Power. Range 500ft. to 1/2mile •
- Crystal Controlled •
- High-Resolution Full Color/ B&W video •
- Fully epoxy encased- no exposed components •
- Fully assembled- only two wires to attach •
- MONEY BACK GUARANTEE. •

VidLink 100: 100mW Power- upto 1/4 Mile  
**\$199.00** New! High-Power!

VidLink 15: 15mW Power- upto 150 Feet  
**\$99.00** New! Low Price- Same Size!

Covert Camera: 1 1/4" sq. Pinhole Lens  
**\$169.00** Pro Grade Japanese Quality!

\*\*\* Audio Module Now Available. Call. \*\*\*

Check/MO, COD +\$5.00, S&H \$5.50

**AEGIS**  
 RESEARCH

#671-1225 E. Sunset Dr.  
 Bellingham, WA  
 98226-3529 USA

**1-604-224-0416**

Visit our virtual catalog on the INTERNET at:  
<http://www lynx.bc.ca/virtualspy>



**Are you overpaying . . .**  
 . . . your cable company?

**You are if . . .**   
 . . . you are leasing their equipment.

- Forest Electronics, Inc. offers a complete line of New Cable Decoders and Converters that are fully Compatible with your cable system.
- All systems come with: Remote Control, & Parental Guidance Feature. Volume Control is also available.
- All Equipment is fully guaranteed & comes with a 30 day money back option.

For More Information Call Us 24 Hours a Day At:

**800-332-1996**

**FAX: 813-376-7801**

**ARE YOU LOOKING FOR NEW AND MOST INNOVATIVE PRODUCTS?**  
 hard to find  
 world wide products unique

IF SO, WE HAVE JUST THE RIGHT PRODUCTS FOR YOU! PRODUCTS FOR ALL AGES CAN BE FOUND IN OUR CATALOGS THE BEST KNOWN BRANDS SUCH AS IBM, ACER, ARMNOTE, TOSHIBA, NUREALITY, QUORUM, FUJI, PANASONIC, AND SO MUCH MORE! WE ALSO CARRY A WIDE RANGE OF PRODUCTS LIKE COMPUTERS, KEYBOARDS, MODEMS, MONITORS, MOTHERBOARDS, ELECTRONIC COMPONENTS, CHIPS, CABLES, PLUGS, HARD DRIVES, ADAPTERS, CD ROMS, SCANNERS, LAPTOPS, FAXES, TOYS, BUSINESS OPPORTUNITIES, SECURITY ALARM SYSTEMS.

ALL YOU HAVE TO DO IS SEND \$9.00 U.S. \$15.00 CND TO BECOME A LIFETIME MEMBER OF THE GREAT SELECTION OF PRODUCTS THAT MANA ELECTRONICS HAS TO OFFER! INSTEAD OF SEARCHING, WE SEND IT RIGHT TO YOUR HOME! PRODUCTS ARE FACTORY FRESH, WARRANTIED AND REFUNDABLE. WE OFFER DEALS, DISCOUNTS, PROMOTIONAL GIFT ITEMS TO OUR MEMBERS WHILE YOU ARE CURRENTLY UPDATED WITH CATALOGS OF THE NEWEST AND MOST INNOVATIVE ELECTRONIC PRODUCTS AVAILABLE TODAY!

only \$9.00 U.S. \$15.00 CND 30 DAY REFUND.

order now! AND GET A FREE PEN!



SEND CHECK OR MONEY ORDER TO

**MANA ELECTRONICS**

P.O. Box 67002 RPO Maples  
 Winnipeg MB R2P 2T3  
 (204)-697-3488



# ALFA ELECTRONICS

HIGH QUALITY TEST EQUIPMENT  
BEST PRICE



## DMM 89 \$179.00

### Most Advanced DMM

-80.7 to 81.4 dBm with 4Ω-1200Ω  
20 reference impedances  
True RMS  
Frequency counter: 100 Hz -10MHz  
Capacitance: 5nF-50mF  
Measure AC volt to 20kHz  
5000 counts, 0.1% basic accuracy  
Auto/manual range, fast bar graph  
Min/Max/Ave/DH/Relative/Zoom  
Auto power off  
Input warning  
Splash proof  
Volt, amp, ohm, logic, diode, continuity  
Ruggedized case  
Rubber holster included



## DMM A91

\$49.95

NOW \$39.00

### Plus Free Case

### Solar Cell Powered Large Display

Diode, Continuity  
Volt, Amp, Ohm  
Data Hold  
Auto power off  
7 functions, 19 ranges  
3.5 Digit, 0.8% accuracy  
Auto/Manual ranging  
Energy saver  
Student & hobbyist's favor



## DMM 20

\$74.95

Inductance: 2mH-20H  
Capacitance: 2nF-200uF  
Resistance: 200-200MΩ  
Frequency: 2kHz-20MHz  
3.5 Digit, 0.5% accuracy  
DC/AC Current and Volts  
Transistor hFE, diode est  
Continuity, Duty %  
Peak hold/Max  
Ruggedized case  
Rubber holster \$8.00

Full line of DMMs,  
economy, compact,  
ruggedized, solar cell,  
automotive, heavy duty,  
industrial, electrical  
starts from \$19.95

## Fluke Multimeter

Fluke 12 \$84.95  
Holster C-10 10  
Fluke 70 II \$75.95  
Fluke 73 II \$97.50  
Fluke 75 II \$129  
Holster C70 \$16  
Fluke 77 II \$155  
Fluke 79 II \$175  
Fluke 29 II \$175  
Fluke 76 \$175  
Fluke 87 \$287  
Fluke 867 \$1199  
Scope Meter  
Fluke 97 \$1785  
Fluke 105 \$2799



## LCR Meter 131D

\$229.95

### Most Advanced LCR

Dual display: L/Q or C/D  
Inductance: 10mH-10,000H  
Capacitance: 10nF-10mF  
Resistance: 10Ω-10MΩ  
Auto/manual range  
Dissipation factor & Q factor  
Serial & parallel mode  
Relative mode for comparison  
and to remove parasitics  
Statistics, tolerance,  
Best for design, incoming  
testing & production  
SMD and chip component  
test probe \$25.00



## LCR Meter 814

\$189.95

### Best Resolution LCR

Inductance: 200uH-200H  
Capacitance: 200pF-20,000uF  
Resistance: 2Ω-20MΩ  
Resolution of 0.1uF, 0.1pF, and  
1mΩ are useful for high frequency  
and SMD  
Dissipation factor indicates leakage  
in capacitor and Q factor in inductor  
Zero adjustment to reduce parasitics  
Best for high frequency RF  
SMD and chip component test probe  
\$25.00  
Padded deluxe case \$8.00




## Frequency Counter

FC-1200 \$129.95

Frequency: 10Hz-1.25GHz  
Display: 8 digit LCD  
Period: 0.1μs-0.1s  
Records Max/Min/Average  
Data hold, relative mode  
Telescoping antenna \$8.00  
Deluxe case \$5.00
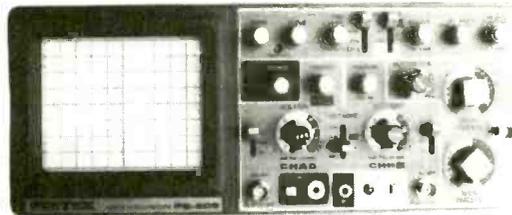
### Also Available:

AC/DC clamp meter, Light meter,  
Thermometer, pH meter, High voltage  
Probe, Digital Calliper, Anemometer,  
Electronic scale, Force Gauge,  
Tachometer, Stroboscope, Humidity  
& EMF adapter, Sound level meter,  
Frequency counter, SWR/field  
strength/power meter, Dip meter



## 20 MHz Oscilloscope with Delay Sweep PS-205 \$429.95


Dual Trace, Component test, 8" CRT, X-Y Operation, TV  
Sync, Z-Modulation, CH2 Output, Graticule Illum, 2 probes  
each has x1, x10 switch. Best price with delay sweep.  
PS-200 20 MHz DUAL TRACE \$339.95  
PS-400 40 MHz DUAL TRACE \$484.95  
PS-405 40 MHz DELAY SWEEP \$589.95  
PS-605 60 MHz DELAY SWEEP \$789.95  
PS-1000 100 MHz DUAL TRACE \$989.95  
Scope Probe: 60MHz x1, x10 \$15, 100MHz x1, x10 \$22  
250MHz x1, x10 \$29, 250MHz x100 \$39

## Digital Storage Scope

DS-303 30MHz, 20M Sample/sec \$849.95

DS-303P w/ RS-232 Interface \$1,049.95

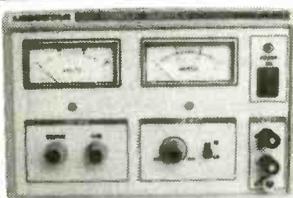
Switchable between digital and analog modes  
2 K word per channel resolution  
8 bit vertical resolution (25 Level/div)  
Expanded Timebase 10ms/div - 0.5 s/div  
Refresh, Roll, Save all, Save CH2, Pre-Trig  
Plotter control



## DC Power Supply

PS-303 \$159.00

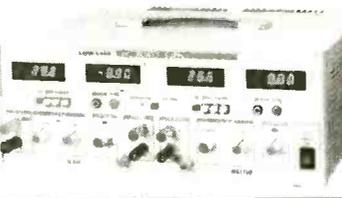
0-30 VDC, 0-3A output  
Constant voltage & constant current mode  
0.02% + 2mV line regulation  
0.02% + 3mV load regulation  
1 mVrms noise and ripple  
Short circuit and overload protected  
PS-8200 with digital voltmeter \$179.00  
Also available: 30V/5A, 60V/3A, 60V/5A  
16V/10A, 30V/10A


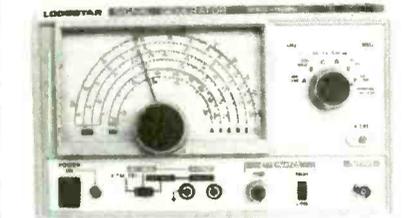
## DC Power Supply Triple

Output PS-8202 \$499.95

Two 0-30 VDC, 0-3A outputs  
One fixed 5VDC, 3A output  
Capable of independent or tracking operation  
Constant voltage and constant current mode  
Four digital meters for volt and current display  
Excellent regulation and low ripple  
Short circuit and overload protected  
Also available: 30V/5A, triple output \$549.95  
Dual tracking 30V/3A, 30V/5A, 60V/3A, 60V/5A



## RF Signal Generator

SG-4160B \$124.95

100 kHz-150MHz sinewave in 8  
ranges  
RF Output 100mVrms to 35 MHz  
Internal 1kHz, External 50Hz-  
20kHz  
AM modulation  
Audio output 1 kHz, 1 Vrms  
Output Impedance: 50 Ohm  
Size: 5.9"H x 9.8"W x 8.1"D

## Audio Generator

AG-2601A \$124.95

10Hz - 1MHz in 5 ranges  
Output: 0-8Vrms sinewave  
0-10Vp-p squarewave  
Synchronization: ±3% of oscillation  
frequency per Vrms  
Output distortion:  
0.05% 500Hz - 50kHz  
0.5% 50Hz - 500kHz  
Output impedance: 600 ohm

## Function Generator

FG-2100A \$169.95

0.2 Hz - 2 MHz in 7 ranges  
Sine/square/triangle/pulse/ramp  
Output: 5mV-20Vp-p  
1% distortion, DC offset ± 10V  
VCF: 0-10V control freq. to 1000:1

## Function Gen./Counter

FG-2102AD \$229.95

Generates signal same as FG-2100A  
Frequency counter 4 digits  
Feature TTL and CMOS output

## Sweep Function

Gen./Counter \$329.95

0.5Hz to 5 MHz in 7 ranges  
Sweep: Linear 10:1 Log 10:1 20ms-2s  
AM Modulation  
Gated Burst, Voltage Control Gener.  
Generator Control Voltage & 8 digit  
counter 1Hz-10MHz for internal &  
external sources



## RF Signal Generator

Counter SG-4162AD

\$229.95

Generates RF signal same as  
SG-4160B  
6 digit frequency counter 1Hz -  
150 MHz for internal and external  
source Sensitivity <50mV

## Audio

Generator/Counter

AG-2603AD \$229.95

Generates audio signal same as  
AG-2601A  
6 digit frequency counter 10Hz-  
150MHz for internal and external  
sources Sensitivity <50mV

ALFA ELECTRONICS

P.O. BOX 8089, Princeton, NJ 08543-8089

(800) 526-2532/(609) 897-1135

FAX: (609) 897-0206

Visa, Master Card, American Express, COD, Purchase Order Welcome

1 YEAR PARTS AND LABOR WARRANTY

CALL / WRITE / FAX FOR FREE CATALOG

CIRCLE 26 ON FREE INFORMATION CARD

# ALL ELECTRONICS

C O R P O R A T I O N

QUALITY PARTS

FAST SHIPPING

DISCOUNT PRICING

CALL, WRITE, FAX  
or E-MAIL For A  
**Free 64 Page**  
CATALOG.  
Outside the U.S.A.  
send \$2.00 postage.

## Low Low Price! 25' BNC-BNC CABLE



25 foot RG58-A/U, 50 ohm co-ax cable with male BNC connectors molded with strain reliefs on both ends. Ideal for studio, lab or communications use. Inquire for quantity pricing.

**\$4.75**  
each

CAT# CBL-25  
10 for \$45.00

## SPECIAL PRICE! TWIST ON F-56 CONNECTOR

We recently made a large purchase of this twist-on co-ax connector for RG-6 cable. Special pricing while the supply lasts.



100 for \$15.00  
500 for \$50.00  
1000 for \$70.00

CAT #FTO-56R

## S-VHS VIDEO CORD



4' cable with miniature 4 pin mini DIN plugs on both ends.

CAT# CB-363


**\$3.00**  
each

10 for \$25.00  
100 for \$150.00
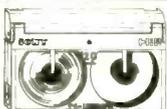
## "HI-8" VIDEO CASSETTE (USED)

SONY Hi-8

Top quality, metal particle 120 minute video cassettes. Used for a short time, then bulk-erased. Each cassette has its own plastic storage box. Satisfaction Guaranteed.



**\$3.00**  
each

CAT # VCU-8

10 for \$28.00 • 100 for \$250.00

## NOTEBOOK COMPUTER CARRYING CASE

Great looking, padded carrying case, suitable for most notebook computers or similar equipment.



Black leatherette exterior with separate zippered compartment for papers or accessories. Detachable nylon web shoulder strap. Interior space is 13.5" X 9" X 2.5"

CAT # CSE-12

**\$9.75**  
each

## EDGEVIEW PANEL METER FS=1 MILLIAMPS

Beautifully constructed edgeview meter movement. 2.75" X 0.8" face. Scale is labeled "BEATS/MINUTE" and is calibrated from 50-150. It can be easily removed or reversed to create a blank scale. The black bezel is 3.53" X 1.33" and can be adjusted or removed. 0.1" thick clear plexiglass case. Maximum case size behind mounting plane: 2.75" X 1.18" X 2.18". Solder lug terminals.



**\$5.50**  
each

CAT # MET-48

## 3 WAY CROSSOVER, INFINITY

Designed for Infinity Studio Monitor, "SM-112", 3 way, 8 ohm speaker system. Rated for 10-175 watts. Crossover frequencies at 900 Hz and 5,500 HZ. Auto-reset circuit breaker protection.

Matte black plastic front panel assembly is 6.75" X 3.6" and has a control for tweeter level adjustment. Fits a cut-out of 5.4" X 2".

**\$7.50**  
each

CAT# LX-112

## THE INSULTINATOR A Programmable Electronic Insult Machine

"You're A Completely Slobbering Greasy Dweeb!"

"You're a totally ugly gross boring nerd!"

"You're A Totally Freaky Wacky Bonehead!"



Hand-held voice synthesizer plays a variety of insults which can be altered by selecting various programming buttons. Thousands of possible insults. Even though no profanity is used, a major nationwide retailer rejected these as being too insulting for their customers. Will green and black case with belt or pocket clip. Includes 3 AA batteries. Attractive display package.


**\$4.95**  
each

case of 24  
\$4.50 each

CAT# INS-5
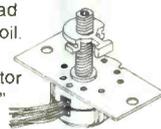
## SMALL STEPPER MOTOR

Unipolar, two phase, 6 lead stepper motor. 53 ohm coil. Operates well on 12 Vdc. 15 degrees per step. Motor body is 1" diameter X 0.5" 0.08" (2mm) diameter shaft is 0.365" long. The shaft is covered with a threaded plastic sheath (0.25" dia X 0.75" long) which acts as a worm gear. This mechanism, is easily removable. Rectangular mounting bracket, 1.73" X 1.10".



**\$1.50**  
each

CAT# SMT-21

10 for \$12.50

## NEODYMIUM MAGNET

Aprox. 1.86" X 1.02" X 0.08" thick.



CAT# MAG-26

**\$1.50**  
each

25 for \$31.25  
100 for \$100.00

ORDER TOLL FREE

**1-800-826-5432**

MAIL ORDERS TO:  
**ALL ELECTRONICS CORP.**  
P.O. BOX 567  
VAN NUYS, CA 91408-0567


FAX (818) 781-2653 • INFO (818) 904-0524  
INTERNET <http://www.allcorp.com/>  
E-MAIL [allcorp@allcorp.com](mailto:allcorp@allcorp.com)



NO MINIMUM ORDER • All Orders Can Be Charged to Visa, Mastercard, American Express or Discover • Checks and Money Orders Accepted by Mail • Orders Delivered in the State of California must include California State Sales Tax • NO C.O.D. • Shipping and Handling \$5.00 for the 48 Continental United States • ALL OTHERS including Alaska, Hawaii, P.R. and Canada Must Pay Full Shipping • Quantities Limited • Prices Subject to change without notice.

**MANUFACTURERS - We Purchase EXCESS INVENTORIES... Call, Write, E-MAIL or Fax YOUR LIST.**

CIRCLE 28 ON FREE INFORMATION CARD

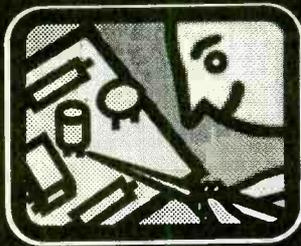

# RAINBOW KITS

Many of our kits are available completely built!

## WIRELESS FM MICROPHONE

Small but mighty this little jewel will out perform most units many times its price. It really stomps out a signal. The WM-2 kit is a buffered wireless

microphone that operates from 80MHz to 120MHz FM, the frequency of any broadcast FM radio. Includes a mini-electret mike. 6 to 12v DC. SIZE: 1.25" x 1

WM2 **KIT \$14.95**

## MICRO-MINIATURE PHONE TRANSMITTER

We haven't seen a smaller phone transmitter than the MMPT2 kit. Powered by the phone, it requires no battery. Transmits both sides of a phone conversation to an FM radio up to a 1/4 mile away. Tunable from 88 to 108MHz FM. Attach it to one phone or add it to the line to pick up all incoming calls. The MMPT2 is undetectable if properly installed. Unit has surface mounted parts, you install the leaded parts. Size .45" x .6"

MMPT2 **KIT \$29.95**

## MICRO-MINIATURE WIRELESS MIKE

So small you could hide this one on some real bugs! It's the smallest we've ever seen. With it's super sensitive mike it transmits a whisper or a room of conversation to an FM radio, tunable from 88 to 108MHz FM. With a proper antenna it transmits about 1/2 mile. The kit is made with surface mounted parts, we have already mounted these parts. You install the leaded parts. Power requirement 6 to 12v DC. Size .35" x .9"

MMWM5 **KIT \$34.95**


## STROBE LIGHT

Do you need an attention getter, warning light, or flashing light for model airplanes? Then this kit is for you. Use it as an emergency light for your auto,

radio tower, even use it on your bicycle. Has a variable flash rate. Power requirement 6 or 12v DC. Size 3.5" x 1.9"

ST-1 **KIT \$11.95**

## FM STEREO TRANSMITTER

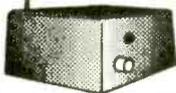

Own your own FM radio station. Any stereo signal you plug into the FMST-100 will be transmitted to any FM radio

tunable from 76 to 108MHz FM. Transmit a wireless link through an auditorium, from your car to your camper, listen to your CD's while mowing the lawn. Play music on one channel sing on the other. Clarity is excellent, approx. 40dB stereo separation. Length of antenna determines the distance of transmission. Complete with stereo input level controls & crystal for stereo separation. 9v battery operation. SIZE: 1.5" x 2.5" x 3"

FMST-100 Cabinet \$8.95 **KIT \$29.95**

## TV NOTCH FILTERS FOR CHANNELS 2 thru 22 ONLY




Our TV filters eliminate unwanted TV channels or interference that alters both sound and video with a beep beep beep. Works on cable channels (2 thru 22) only.

NOTE: All TV Filter Kits are sold for educational purposes only. You must obtain permission from your local cable company before using these filters on your cable system.

DF-222

**KIT \$14.95**

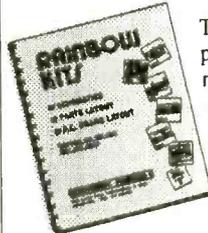


This Manual contains schematics, parts lists & P.C. board layouts for many of the Rainbow Kits. Use your own parts to construct our kits.

**KIT BOOK \$14.95**  
\$9.95 with the purchase of any kit.
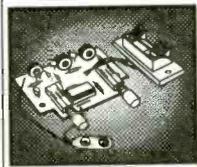
## INDUCTANCE METER

This is the kit everyone has been asking for. Turn your digital volt ohm meter into an inductance meter. It will read inductors 3uH to 7MH. Power requirement 9v DC. SIZE: 1.75" x 2.5"

IA-1 **KIT \$14.95**  
IA-1 CABINET **\$8.95**



## DIGITAL THERMOMETER

The DT-3 kit will turn your digital volt ohm meter into an accurate digital thermometer with .1 degree resolution. Measure temperatures from -40° to 250F°. The remote sensor is .25" sq. and can be mounted many feet from the meter. Power requirement 9V DC. SIZE: 2" x 1.35"

**KIT \$8.95**



DT-3

## CAPACITANCE METER

This kit will turn your digital volt meter into a capacitance meter. Turn that junk box of unmarked capacitors into a fortune of usable parts. Measure capacitors from <2.2pF to 2.2uF. Power requirement 9v DC. SIZE: 1.80" x 2"

**KIT \$12.95**



CA-1

## TEMPERATURE GENIE



Ever lost frozen food because your freezer stopped? The TC-2 kit would have saved you money. An alarm activates when the temperature reaches a critical point. Turn ceiling fans on automatically when it gets too hot. This kit gives you 100mA of output. SIZE: 2" x 1.4" Power requirement 6 to 15V DC.

If you want to switch more power see our Triac (TP-1) or Relay (RP-1) Power kit.

TC-2

**KIT \$7.95**

## PHONE TRANSMITTER




Small but mighty, it fits anywhere. Phone line powered, never needs batteries. Transmits both sides of a phone conversation loud and clear, wireless, to any FM radio at great distances. Variable tunes from 70MHz to 130MHz FM. You can also use it as a speaker phone. SIZE: 1.25" x .6"

TEL-B1

**KIT \$12.95**

## SUPER SNOOPER BIG EAR

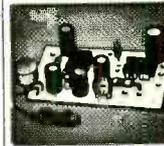


Listen through walls, hear conversations across the room. Add a parabolic reflector and hear blocks away. The BIG EAR can be hidden about anywhere. Makes an ultra sensitive intercom. Can be used as a 1.5W AMP. We supply a mini-electret mike in the kit. Power requirement 6 to 12v DC. SIZE: 1.75" x 1"

AA-1

BUILT \$29.95

**KIT \$10.95**

## RELAY POWER KIT

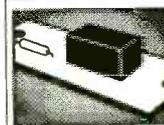


Increase the output of any kit from 100mA to 3 Amps. If you need to switch more power, up to 300 Watts, with the Light Genie,

Temperature Genie, Timer or Vox kits, use the Relay Kit. We supply a two pole relay 1.5 Amps ea., tie both poles together and get 3 Amps. Size .75" x 2"

RP-1

**KIT \$9.95**

## WIDE BAND PRE-AMP

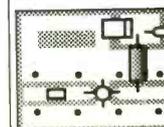

Uses PCB and surface mount technology for better performance. Use for scan-

ners, HT's, Frequency counters, Satellite Receivers. It amplifies low-level (weak) signals. If the signal is extremely low, two amplifiers can be used in a series.

- 1MHz to 2.5 GHz 2.8dB NF
- 1dB compression=OdBm
- Gain: 1MHz- 20dB to 2.5GHz-6dB
- Power requirement: 12v @ 6Ma

WBA-6

**KIT \$19.95**



**ELECTRONIC RAINBOW**

Please add sufficient postage First lb \$5.00 Canada \$7.00  
Additional LB. Add \$1.00 US FUNDS ONLY  
We will accept telephone orders for Visa or Mastercard

**Electronic Rainbow Ind., Inc.**  
6227 Coffman Rd. Indianapolis, IN 46268

**CALL 317-291-7262 FAX 317-291-7269**  
INTERNET: www.rainbowkits.com



6N

**CALL TOLL FREE**  
**(800) 292-7711 orders only**  
**Se Habla Español**

**C&S SALES**  
**EXCELLENCE IN SERVICE**

**CALL OR WRITE FOR**  
**A FREE 60 PAGE**  
**CATALOG!**  
**(800) 445-3201**

**XK-550 Digital / Analog Trainer**

Elenco's advanced designed Digital / Analog Trainer is specially designed for school projects. It is built on a single PC board for maximum reliability. It includes 5 built-in power supplies, a function generator with continuously sine, triangular and square wave forms. 1560 tie point breadboard area.

**XK-550**  
**Assembled and Tested**  
**\$169.95**

**XK-550K - Kit**  
**\$139.95**

Tools and meter shown optional



**TK-3000**  
**\$89.95**

**Tools Included:**

- SR-2 - Deluxe Soldering Iron
- SH-1 - Soldering Iron Stand
- ST-1 - Diagonal Pliers
- ST-2 - Long Nose Pliers
- ST-30 - Deluxe Wire Stripper
- SE-1 - Solder Ease Kit
- ND-3 - 3 pc. Nut Driver Set
- TL-8 - Precision Screw Drivers
- ST-5 - Screw Driver Slotted 3/16"
- ST-6 - Screw Driver #1 Phillips
- ET-10 - IC Puller
- SP-2 - Solder Pump
- ST-20 - Safety Goggles
- ST-9 - Pocket Screw Driver
- ST-4 - Solder Tube
- SW-3 - Solder Wick



A professional technician service tool kit in a metal reinforced tool case with heavy-duty handle and locks. A removable pallet handles most of the tools listed with more room for tools and parts in the lower half.

**GF-8026 w/ Frequency**

- Linear and Log Sweep
  - .02Hz to 2MHz
  - Counter Range 1Hz to 10MHz
  - 4 Digit Display
- \$225**



**MX-9300 Four Functions in One**

- One instrument with four test and measuring systems:
- 1.3GHz Frequency Counter • 2MHz Sweep Function Generator
- Digital Multimeter • Digital Triple Power Supply (0-30V @ 3A, 15V @ 1A, 5V @ 2A)



**\$479.95**

**Model XP-581**

**4 Fully Regulated DC Power Supplies In One Unit**  
 4 DC voltages: 3 fixed - +5V @ 3A, +12V @ 1A, -12V @ 1A  
 1 Variable - 2.5 - 20V @ 2A

**\$85**



**Auto Ranging Hand-Held DMM w/ Bar Graph Model EDM-163**

**\$99.95**

7 Functions with data hold  
 Compares to Fluke Model 77II

**Digital Multimeter Model M-1700**

**\$39.95**

11 functions including freq to 20MHz, cap to 20µF. Meets UL-1244 safety specs.



**Fluke Multimeters**

**70 Series**

- Model 701I ..... \$69.95
- Model 731I ..... \$97.50
- Model 751I ..... \$135.00
- Model 771I ..... \$154.95
- Model 791I ..... \$175.00

**80 Series**

- Model 83 ..... \$235.00
- Model 85 ..... \$269.00
- Model 87 ..... \$289.00

**B&K Precision Multimeters**

- Model 391 ..... \$159.00
- Model 390 ..... \$139.00
- Model 389 ..... \$109.00
- Model 388A ..... \$99.00
- Model 2707 ..... \$79.00
- Model 2860A ..... \$85.00

**Kit Corner**

over 100 kits available

**PT-223K**

**\$15.95**

Phone kit with training course.



**Fiber Optics Technology**

with training course  
**Model FO-30K**

**\$19.95**



**Model AM/FM-108K Transistor Radio Kit**

with training course

**\$29.95**



**M-1005K Compact Multimeter Kit**

**\$19.95**

6 Functions & Transistor Test



**Model M-6100**

**Programmable DMM**

Includes **FREE** Computer Interface and **FREE** Software

- Analog Bar Graph
- Large 3 3/4" LCD Display
- Menu Driven
- Triple Display
- RS-232 Interface
- True RMS
- 9 Basic Functions including cap. & freq.
- Auto Power Off
- Easy-to-use

**\$125**



**WE WILL NOT BE UNDERSOLD**

**C&S SALES, INC.**

150 W. CARPENTER AVENUE  
 WHEELING, IL 60090  
 FAX: (847) 520-9904 (847) 541-0710  
[http://www.elenco.com/cs\\_sales/](http://www.elenco.com/cs_sales/)



**15 DAY MONEY BACK GUARANTEE**

**FULL FACTORY WARRANTY**

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

**FREE PROBES  
WITH ALL  
SCOPES**

# OSCILLOSCOPES

**Lowest Prices of the Year!**

**CALL OR WRITE FOR  
A FREE 60 PAGE  
CATALOG!  
(800) 445-3201**

## B&K Precision Scopes

### 60MHz ANALOG WITH DIGITAL STORAGE

Model 2560

- Cursors and readouts
- RS-232 port
- 20MHz analog bandwidth
- 1GHz equivalent time sampling (at 0.1µs/div.)
- Prints via RS-232 port to any HP-GL printer

**\$1995**

### 20MHz ANALOG WITH DIGITAL STORAGE

Model 2522A

- 20MHz analog bandwidth
- 20MS/s sampling rate
- 2K memory per channel
- 300MHz equivalent time sampling
- Pre-trigger capture

**\$869.95**

### 100MHz THREE-TRACE

Model 2190A

- 1mV/division sensitivity
- Sweeps to 5nd-division
- Dual time base
- Signal delay line
- 15KV accelerating voltage

**\$1379.95**

### 60MHz DUAL-TRACE

Model 2160A

- 1mV/division sensitivity
- Sweeps to 5nd-division
- Dual time base
- Signal delay line
- V mode-displays two signals unrelated in frequency
- Component tester

**\$949.95**

### 40MHz DUAL-TRACE

Model 1511C

- 1mV/division sensitivity
- Video sync separator
- Z-axis input
- Single Sweep
- V mode displays two signals unrelated in frequency
- Component tester

**\$695**

### 60MHz, CURSORS & READOUTS, DUAL TIME BASE

Model 2260

- Cursors and readouts
- 1mV/div sensitivity
- 23 calibrated ranges - main time base
- 18 calibrated ranges - delayed time base
- Signal delay time
- V mode - displays 2 signals unrelated in frequency
- Component tester
- Z-axis input
- Single sweep

**\$1225**

### 20MHz DUAL-TRACE

Model 2120 - 2 Year Warranty

**Special \$389.95**

Model 2125 with delayed sweep

**\$539.95**

- 1mV/division sensitivity
- AUTO/NORM triggered sweep operation
- AC, TVM, TVM and line coupling
- Calibrated 10 step time-base with x10 magnifier
- Compact low-profile design

## Quality Scopes by Elenco



### 60MHz

**DS-603 \$1350**

- Analog / Digital Storage
- 20MS/s Sampling Rate

**S-1360 \$749**

- Analog with Delayed Sweep

### 40MHz

**S-1345 \$569**

- Analog with Delayed Sweep

**S-1340 \$475**

- Analog

### 25/30MHz

**DS-303 \$1095**

- Analog / Digital Storage

**S-1330 \$439**

- 25MHz Analog
- Delayed Sweep

**S-1325 \$325**

- 25MHz Analog

**2 Year  
Warranty**

### OSCILLOSCOPE SELECTION CHART

ANALOG Model		Bandwidth MHz	Sensitivity (max) mV/div	No. of Channels	Sweep Rate Max ns/div	Delayed Sweep	Video Sync	Component Tester	Beam Find	Time Base
S-1360	60	1mV/div	2	10ns/div	Yes	Yes	Yes	Yes	2	
S-1345	40	1mV/div	2	10ns/div	Yes	Yes	Yes	Yes	2	
S-1340	40	1mV/div	2	10ns/div	No	Yes	No	No	1	
S-1330	25	1mV/div	2	10ns/div	Yes	Yes	Yes	Yes	2	
S-1325	25	1mV/div	2	10ns/div	No	Yes	No	No	1	

DIGITAL STORAGE Model		Bandwidth MHz	Analog Sen (max) mV/div	No. of Channels	Sampling Rate	Memory Channel	Internally Backed Up	Pretrigger %	Output
DS-303	30	1mV/div	2	20MS/S	2K	Yes	0, 25, 50, 75	RS232	
DS-603	60	1mV/div	2	20MS/S	2K	Yes	0, 25, 50, 75	RS232	

## Affordable Spectrum Analyzers by B&K

### 500MHz Series

Model 2615 - \$1595  
Model 2620 w/ tracking generator - \$1895

### 1.05GHz Series

Model 2625 - \$2395  
Model 2630 w/ tracking generator - \$2995



**WE WILL NOT BE UNDERSOLD**

UPS SHIPPING: 48 STATES 5%  
OTHERS CALL FOR DETAILS  
IL Residents Add 8% Tax

**HURRY... AT PRICES THIS LOW THEY'LL BE GONE FAST!**  
**HITACHI SCOPES**  
Inventory Reduction Sale  
Lowest Prices of the Decade!

V-209 - 20MHz Battery Operated  
Was \$1505, NOW \$1095 Save \$410

V-695 - 60MHz w/ Cursors  
Was \$1815, NOW \$1395 Save \$420

V-422 - 40MHz Was \$965,  
NOW \$765 Save \$200

V-1065A - 100MHz w/ Cursors  
Was \$2139, NOW \$1565 Save \$574

V-525 - 10MHz w/ Cursors  
Was \$1355, NOW \$955 Save \$400

V-1560 - 100MHz Was \$1790,  
NOW \$1490 Save \$300

V-552 - 50MHz Was \$1195,  
NOW \$850 Save \$345

V-1565 - 100MHz w/ Cursors  
Was \$1960, NOW \$1595 Save \$365

V-555 - 50MHz w/ Cursors  
Was \$1375, NOW \$975 Save \$400

V-252 - 20MHz **\$419**

## Fluke Scopemeters



91 ..... \$1225  
92B ..... \$1445  
96B ..... \$1695  
97 ..... \$1795  
97A ..... \$2945  
99B ..... \$2095

Call or write for complete specs.

**15 DAY MONEY BACK  
GUARANTEE**

**FULL FACTORY WARRANTY**  
PRICES SUBJECT TO CHANGE WITHOUT NOTICE

## C&S SALES, INC.

150 W. CARPENTER AVENUE  
WHEELING, IL 60090  
FAX: (847) 520-9904 (847) 541-0710  
[http://www.elenco.com/cs\\_sales/](http://www.elenco.com/cs_sales/)



CIRCLE 32 ON FREE INFORMATION CARD

# EARN MORE MONEY!

## Be an FCC LICENSED ELECTRONIC TECHNICIAN!



Earn up to \$60 an hour and more!

Learn at home in spare time. No previous experience needed!

No costly school. No commuting to class. The Original Home-Study course prepares you for the "FCC Commercial Radio-telephone License." This valuable license is your professional "ticket" to thousands of exciting jobs in Communications, Radio-TV, Microwave, Maritime, Radar, Avionics and more...even start your own business! You don't need a college degree to qualify, but you do need an FCC License.

**No Need to Quit Your Job or Go To School**  
This proven course is easy, fast and low cost! **GUARANTEED PASS**—You get your FCC License or money refunded. **Send for FREE facts now. MAIL COUPON TODAY!**

Or, Call 1-800-932-4268 Ext. 240

**COMMAND PRODUCTIONS**  
FCC LICENSE TRAINING, Dept. 240  
P.O. Box 2824, San Francisco, CA 94126  
Please rush **FREE** details immediately!

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

## CABLE BOX EXPRESS

CALL 1-888-561-4796

FOR ALL YOUR CABLE TV NEEDS

### GET THE COMPLETE PICTURE


ORIGINAL EQUIPMENT

TEST ACTIVATORS

FILTERS (97,106,108,110)

REPLACEMENTS FOR ALL SYSTEMS

HAVE MAKE AND MODEL NUMBER READY!

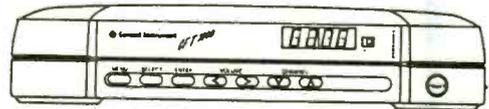

GUARANTEED LOW PRICE!

\*\*SAME DAY SHIPPING\*\*

CALL NOW 1-888-561-4796


1 YEAR WARRANTY ON ALL PRODUCTS

VOID WHERE PROHIBITED

Anyone implying theft will be denied assistance

Low Cost CAD Software  
for the IBM PC and Compatibles

Now In Windows™

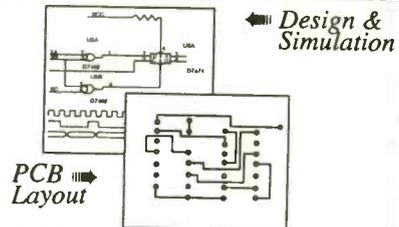

- Easy to use schematic entry program (SuperCAD) for circuit diagrams, only \$149. Includes netlisting, bill of materials, extensive parts libraries, More parts, and automatic wiring available in enhanced CAD package (SuperCAD+) for only \$249.
- Powerful, event-driven digital simulator (SuperSIM) allows you to check logic circuitry quickly before actually wiring it up. Works directly within the SuperCAD editor from a pull-down menu and displays results in "logic analyzer" display window. Starting at \$149 this is the lowest cost simulator on the market. Support for PALs, a larger library, and a separate interactive logic viewer are available in full-featured SuperSIM+ for only \$399. Library parts include TTL, CMOS and ECL devices.
- Circuit board artwork editor and autorouter programs (SuperPCB), starting at \$149. Produce high quality artwork directly on dot matrix or laser printers. You can do boards up to 16 layers including surface mount. Includes Gerber and Excellon file output. Autorouter accepts netlists and placement data directly from the SuperCAD schematic editor.
- Low cost combination packages with schematics and PCB design: 2-layer for \$399, 16-layer for \$649.
- DOS version available.

Write or call for free demo disks:

**MENTAL AUTOMATION, INC.**

5415 - 136th Place S.E.

Bellevue, WA 98006

(206) 641-2141 • BBS (206) 641-2846

<http://www.mentala.com>



**FREE CATALOG  
CALL TOLL FREE  
1-800-338-0531**

E-Mail: [xpress@parts-express.com](mailto:xpress@parts-express.com)



**Parts  
Express™**

**UNBELIEVABLE  
VALUE!**

**X10 POWERHOUSE**

Check our catalog for a full line of X10 Home Security and Home Automation products.



**Weller WLC100 Soldering Station**

The Weller WLC100 solder station is ideal for the professional, serious hobbyist, or kit builder who demands higher performance than usual of a standard iron, but without the high cost of an industrial unit. Power is adjustable from 5 to 40 watts. Includes 40 watt pencil iron. UL approved. Net weight: 1-3/4 lbs.



**\$39<sup>95</sup>** EACH

**"The Sound Bridge" FM Stereo  
Wireless Transmitter**

The Sound Bridge is a mini FM wireless transmitter that can be used to broadcast stereo sound from any audio source like portable CD players, TVs, electronic games, CD-ROM, even computer soundcards, to your home stereo receiver! Adjustable from 89 to 95.5 MHz.



**\$14<sup>95</sup>** EACH

**HOT  
NEW  
ITEM!**

**3 Way Indoor/Outdoor  
Speaker System**

These are the best sounding little speakers you can find anywhere near this price! Perfect for rear channel use in a home theatre system or for outdoor use. Features 4" polypropylene woofer, 2" polycone midrange, 3/4" dome tweeter housed in a weatherized polystyrene enclosure. Frequency response: 90-20,000 Hz. Impedance: 4 ohms. Power handling: 30 watts RMS/60 watts max. Mounting brackets included. 7-1/4" H x 4-5/8" W x 4-3/8" D. Net weight: 6 lbs.



**#PO-319-020 (Black)**

**#PO-319-025 (White)** ..... **\$45<sup>00</sup>** PAIR

Compare To

**Special  
\$29<sup>95</sup>** PAIR

**Home Theatre In-Floor Subwoofer**

To fully appreciate the potential of movie soundtracks, a dual voice coil subwoofer is a must! Many film special effects are extremely demanding in the low frequency range and require a subwoofer that can duplicate explosions, earthquakes, even the footsteps of Tyrannosaurus Rex! This subwoofer fits the bill by featuring a 10" dual voice coil woofer for true stereo operation and high pass filters for your main speakers. The most unique feature of this subwoofer is the fact that it is designed to be mounted in between the floor joists in new and existing home constructions. Simply mount the in-floor sub to the joists and mount a heat register grill above opening in subwoofer front enclosure. The subwoofer is now totally out of view and ready to rumble! Includes detailed installation manual.



**Specifications:** 10" dual voice coil treated paper cone woofer with poly foam surround • Frequency response: 30-100 Hz • Nominal impedance: 8 ohms per coil • Power handling: 100 watts RMS channel/140 watts max • SPL: 89 dB 1W/1m • Dimensions: 27" D x 14-5/8" W x 9" H • Net weight: 29 lbs.

**#PO-300-445** ..... **\$139<sup>95</sup>** EACH

**Peak Instrument Co.**

**"The Woofer Tester"**

Peak Instrument Co. proudly introduces "The Woofer Tester". Just ask any loudspeaker engineer, and they will tell that the only way to design enclosures of the correct size and tuning is to measure the Thiele-Small parameters for the actual drivers to be used. The reason? Manufacturers published specs can be off by as much as 50%! But until now, measuring the parameters yourself required expensive test equipment and tedious calculations, or super expensive measurement systems (\$1,200 to \$20,000). The Woofer Tester changes all that. Finally, a cost effective, yet extremely accurate way to derive Thiele-Small parameters, in only minutes! The Woofer Tester is a combination hardware and software system that will run on any IBM compatible computer that has EGA or better graphics capability and an RS232 serial port. The Woofer Tester will generate the following parameters. Raw driver data: Fs, Qms, Qrs, Qts, Vas, BL, SPL @ 1W/1m, Mmd, Cm, and Rm. Sealed box data: Fsb and system Q. Vented box data: Fsb, ha, alpha, and Q loss. The Woofer Tester system includes hardware, test leads, serial cable, AC wall adaptor, detailed instructions, and software.




**QUICK! AND  
ACCURATELY  
MEASURES Fs,  
Qms, Qrs, Qts,  
Vas, BL, SPL @ 1W/1m,  
Mmd, Cm, and Rm  
IN MINUTES!**

◆ 30 DAY  
MONEY BACK  
GUARANTEE  
◆ 1 YEAR WARRANTY ◆ SAME DAY SHIPPING

**#PO-390-800** ..... **\$249<sup>00</sup>** EACH

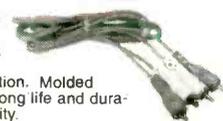**5 Foot Stereo RCA Patch Card**

High quality, Japanese made patch cord features color coded RCA plugs on each end for easy polarity identification. Molded strain reliefs for extra long life and durability. Limited availability.



Part #	Description	Price (1-9)	Price (10-UP)
PO-189-070	Red/white plugs	\$1.20	\$ .95
PO-189-072	Yellow/black plugs	1.20	.95

**Copper Clad PC Board**

Now's the perfect time to start building your own PC boards! A factory buyout enables us to bring you this premium quality copper clad PC boards at unheard of low prices. Each board is coated with .0014" copper and is at least .060" thick. Limited availability.



Part #	Description	Price (1-9)	Price (10-UP)
PO-055-204	6" x 18" single sided	\$1.50	\$1.35
PO-055-206	6" x 21" single sided	1.75	1.55
PO-055-222	8" x 24" single sided	2.65	2.40
PO-055-252	6" x 18" double sided	2.25	2.00

**Speaker  
Surround  
Repair Kits**



- ◆ Do it yourself
- ◆ Save Money
- ◆ Complete instructions
- ◆ Wide variety of sizes and styles
- ◆ Hard to find Advent Woofer and Red Foam kits available

**CALL NOW FOR  
SIZES AND MORE  
INFORMATION**

**900 MHz Wireless Speaker System**

- ◆ 900 MHz technology sends signal up to 180 ft., through walls, floors and ceilings
- ◆ Ideal for use as rear surround speakers or for adding wireless sound to every room in the house!
- ◆ Full range, bass reflex design with built-in high power, low distortion amplifier.
- ◆ Weather resistant cabinet for outdoor use.
- ◆ Selectable battery (six C size for each speaker) or AC operation, adaptor included. Built-in recharging circuitry for ni-cad batteries.
- ◆ System includes: 900 MHz transmitter, wireless speaker pair, AC adaptors, and all cables necessary to hook up system.
- ◆ Limited availability. ◆ Net weight 9 lbs.
- ◆ Frequency response: 20-18KHz.



**#PO-319-030** ..... **\$169<sup>95</sup>** EACH



◆30 day money back guarantee ◆\$20.00 minimum order ◆We accept Mastercard, Visa, Discover, and company C.O.D. orders ◆24 hour shipping ◆Shipping charge = UPS chart rate + \$1.90 (\$5.00 minimum charge) ◆Hours 8:00 am - 8:00 pm ET, Monday - Friday ◆9:00 am - 5:00 pm Saturday. Mail order customers, please call for shipping estimate on orders exceeding 5 lbs. ◆Foreign destination customers please send \$5.00 U.S. funds for catalog. ◆Quantity pricing available.  
CIRCLE 146 ON FREE INFORMATION CARD

**1-800-338-0531**

340 E. First St., Dayton, OH 45402-1257  
Phone: 937-222-0173 ◆ Fax: 937-222-4644

# USE POPULAR ELECTRONICS

READ BY BUYERS OF ELECTRONIC EQUIPMENT ACCESSORIES AND PARTS

## INSTRUCTIONS FOR PLACING YOUR AD!

### HOW TO WRITE YOUR AD

**TYPE or PRINT** your classified ad copy **CLEARLY** (not in all capitals) using the form below. If you wish to place more than one ad, use a separate sheet for each additional one (a photo copy of this form will work as well). Place a category number in the space at the top of the order form (special categories are available). If you do not specify a category, we will place your ad under miscellaneous or whatever section we deem most appropriate.

We cannot bill for classified ads. **PAYMENT IN FULL MUST ACCOMPANY YOUR ORDER.** We do permit repeat ads or multiple ads in the same issue, but, in all cases, full payment must accompany your order.

### WHAT WE DO

The first word and company name of each ad are set in bold caps at no extra charge. No special positioning, centering, dots, extra space, etc. can be accommodated.

### RATES

Our classified ad rate is \$1.75 per word. Minimum charge is \$26.25 per ad per insertion (15 words). Any words that you want set in bold are each .40 extra. Indicate bold words by underlining. Words normally written in all caps and accepted abbreviations are not charged anything additional. State abbreviations must be post office 2-letter abbreviations. A phone number is one word.

If you use a **Box** number you must include your permanent address and phone number for our files. **ADS SUBMITTED WITHOUT THIS INFORMATION WILL NOT BE ACCEPTED.**

For firms or individuals offering Commercial products or Services. **Minimum 15 Words.** 5% discount for same ad in 6 issues within one year; 10% discount for same ad in 12 issues. **Sorry, no discounts on credit-card orders. Boldface (not available as all caps), add .40 per word additional. Entire ad in boldface, add 20%. Tint screen behind entire ad, add 25%. Tint screen plus all boldface ad, add 45%. Expanded type ad, add \$2.25 per word.**

**General Information:** A copy of your ad must be in our hands by the 13th of the fourth month preceding the date of issue (i.e. Sept issue copy must be received by May 13th). When normal closing date falls on Saturday, Sunday or Holiday, issue closes on preceding work day. Send for the classified brochure.

### DEADLINES

Ads not received by our closing date will run in the next issue. For example, ads received by November 13 will appear in the March issue that is on sale January 17. **POPULAR ELECTRONICS** is published monthly. No cancellations permitted after the closing date. No copy changes can be made after we have typeset your ad. **NO REFUNDS, advertising credit only. No phone orders.**

### CONTENT

All classified advertising in **POPULAR ELECTRONICS** is limited to electronics items only. All ads are subject to the publishers approval. **WE RESERVE THE RIGHT TO REJECT OR EDIT ALL ADS.**

**AD RATES:** \$1.75 per word, Minimum \$26.25

Send you ad payments to:

**POPULAR ELECTRONICS 500 Bi-County Blvd, Farmingdale, NY 11735-3931**

### CATEGORIES

100 - Antique Electronics	270 - Computer Equipment Wanted	450 - Ham Gear Wanted	630 - Repairs-Services
130 - Audio-Video Lasers	300 - Computer Hardware	480 - Miscellaneous Electronics For Sale	660 - Satellite Equipment
160 - Business Opportunities	330 - Computer Software	510 - Miscellaneous Electronics Wanted	690 - Security
190 - Cable TV	360 - Education	540 - Music & Accessories	710 - Telephone
210 - CB-Scanners	390 - FAX	570 - Plans-Kits-Schematics	720 - Test Equipment

### CLASSIFIED AD COPY ORDER FORM

Place this ad in Category # \_\_\_\_\_

Special Category \$20.00 Additional \_\_\_\_\_

1 - \$26.25	2 - \$26.25	3 - \$26.25	4 - \$26.25
5 - \$26.25	6 - \$26.25	7 - \$26.25	8 - \$26.25
9 - \$26.25	10 - \$26.25	11 - \$26.25	12 - \$26.25
13 - \$26.25	14 - \$26.25	15 - \$26.25	16 - \$28.00
17 - \$29.75	18 - \$31.50	19 - \$33.25	20 - \$35.00
21 - \$36.75	22 - \$38.50	23 - \$40.25	24 - \$42.00
25 - \$43.75	26 - \$45.50	27 - \$47.25	28 - \$49.00

29 - \$50.75	30 - \$52.50	31 - \$54.25	32 - \$56.00
33 - \$57.75	34 - \$59.50	35 - \$61.25	36 - \$63.00
37 - \$64.75	38 - \$66.50	39 - \$68.25	40 - \$70.00

Total words \_\_\_\_\_ \$1.75 per word = \$ \_\_\_\_\_

Bold Face \_\_\_\_\_ \$0.40 per word = \$ \_\_\_\_\_

Special Heading \_\_\_\_\_ \$20.00 = \$ \_\_\_\_\_

Other \_\_\_\_\_ = \$ \_\_\_\_\_

Total classified ad payment \$ \_\_\_\_\_ enclosed

**TOTAL COST OF AD \$ \_\_\_\_\_**

Check  Mastercard  Visa  Discover

Card # \_\_\_\_\_ Expiration Date \_\_\_\_/\_\_\_\_

Signature \_\_\_\_\_

Name \_\_\_\_\_ Phone \_\_\_\_\_

Address \_\_\_\_\_ City State Zip \_\_\_\_\_

Digital Entertainment  
also available through  
**Skyvision®**



USA SB



AlphaStar

4D TV  
FOR C-BAND



## BEST Values from Skyvision!

**Receivers**  
from \$259  
including 4DTV

**Actuators**  
12" to 52" for all  
C- and Ku-band dishes

**LNBS**  
All kinds  
to heat up your picture

**Tune-Up Kits**  
for C/Ku band & DBS

**Programming**  
Save 30% - 50% with Skypac™

**Support**  
Customers enjoy toll-free technical help

Keep your C-band System Running Strong

Everything on the air for complete variety

Enjoy debut of new channels  
Often in the clear for months

Wild feeds... Action as it happens

Programming you want at a price  
you can afford to pay

Whether you're considering your first  
satellite TV entertainment system or  
looking for an upgrade to your  
current system, Skyvision provides  
the best in hardware, technical  
support, convenience,  
low cost and service.

1048 Frontier Drive  
Fergus Falls, MN 56537

Fax 218-739-4879 Int'l 218-739-5231

All marks shown are registered trademarks  
of their respective owners.

1-800-334-6455  
www.skyvision.com

**Skyvision®**

Our Complete Catalog is now online

<http://www.cir.com>

**CIRCUIT SPECIALISTS INC.**

**Check Out What We Have To Offer:**

**Fantastic DMM Offer!!!**

Don't let the price fool you. This meter is a digital multimeter designed for engineers and hobbyists. Equipped with 5 functions and 19 ranges. Each test position is quickly and easily selected with a simple turn of the FUNCTION/RANGE selector rotary switch.

**Rubber Boot Included**

**General**  
 Display: 3-1/2 Digit LCD, 21mm Figure Height with Automatic Polarity  
 Overrange Indication: 3 Least Significant Digits Blank  
 Temperature for Guaranteed Accuracy: 23°C±5°C RH<75%  
 Temperature Ranges:  
 Operating: 0°C to 40°C (32°F to 104°F)  
 Storage: -10°C to 50°C (14°F to 122°F)  
 Power: 9V Alkaline or Carbon-Zinc Battery (NEDA 1604)  
 Low Battery Indication: BAT on Left of LCD Display  
 Dimensions: 188mm long x 87mm wide x 33mm thick  
 Net Weight: 400g



Our Best Offer Ever on a

High Quality Full Sized DMM

**\$19.00** any qty

**DC Voltage (DCV)**

Range: Resolution: Accuracy:  
 200mV 100µV  
 2000mV 1mV  
 20V 10mV ±(1%rdg+2dgts)  
 200V 100mV  
 1000V 1V

Maximum Allowable Input: 1000V DC or Peak AC.

**DC Current (DCA)**

Range: Resolution: Accuracy:  
 200µA 100nA  
 2000µA 1µA ±(1.2%rdg+2dgts)  
 20mA 10µA  
 200mA 100µA  
 10A 10mA ±(1.2%rdg+2dgts)

Overload Protection: mA Input, 2A/250V fuse.

**AC Voltage (ACV)**

Range: Resolution: Accuracy:  
 200V 100mV ±(1.2%rdg+10dgts)  
 750V 1V

Frequency Range: 45Hz-450Hz  
 Maximum Allowable Input: 750V rms  
 Response: Average Responding, Calibrated in rms of a Sine Wave.

**Resistance (Ω)**  
 Range: Resolution: Accuracy:  
 200Ω 100mΩ  
 2000Ω 1Ω  
 20KΩ 10Ω ±(1.2%rdg+2dgts)  
 200KΩ 100Ω  
 2000KΩ 1KΩ  
 20MΩ 10KΩ ±(2%rdg+10dgts)  
 Maximum Open Circuit Voltage: 2.8V

**Diode Test**

Measures forward voltage drop of a semiconductor junction in mV test current of 1.5mA Max.

**ohFE Test**

Measures transistor hFE.

CAT NO	DESCRIPTION	PRICE
9300G	Rugged High Quality DMM with Rubber Boot	\$19.00

**Switchable Scope Probe Sets**

(Selectable X1/Ref/X10) These high quality scope probe sets are for oscilloscopes up to 60MHz (model HP 9060) or 50MHz (model HP9150). Both sets include a handy storage pouch and include an IC test-hook adapter for the probe. The BNC connector rotates to avoid cable tangle or kink. Cable length is 1.4 meters.

CAT NO	DESCRIPTION	1	10	100
HP-9060	Scope Probe Set DC~60MHz	\$16.49	\$14.49	\$11.58
HP-9150	Scope Probe Set DC~150MHz	24.95	21.95	18.62

**Etching Chemicals/Ferric Chloride**

A dry concentrate that mixes with water to make 1 pint of etchant, enough to etch 400 sq. inches of 1oz board.

CAT NO	DESCRIPTION	1	5
ER-3	Makes 1 pint	\$3.50	\$2.75



**Positive Photo Resist Pre-Sensitized Printed Circuit Boards**



These pre-sensitized printed circuit boards are ideal for small production runs. They provide high resolution and excellent line width control. High sensitive positive resist coated on 1oz. copper foil allows you to go direct from your computer plot or art work layout. No need to reverse art.

CAT NO	DESCRIPTION	PRICE EACH		
		1	10	50
PP101	100mm x 150mm/3.91" x 5.91"	\$2.55	\$1.90	\$1.70
PP114	114mm x 165mm/4.6" x 6.6"	2.98	2.45	1.98
PP152	150mm x 250mm/5.91" x 9.84"	5.40	3.98	3.60
PP153	150mm x 300mm/5.91" x 11.81"	6.15	4.48	4.10
PP1212	305mm x 305mm/12" x 12" <b>NEW!</b>	12.78	10.65	8.52

CAT NO	DESCRIPTION	PRICE EACH		
		1	10	50
GS101	100mm x 150mm/3.91" x 5.91"	\$ 3.90	\$2.98	\$2.60
GS114	114mm x 165mm/4.6" x 6.6"	4.80	3.49	3.20
GS152	150mm x 250mm/5.91" x 9.84"	8.69	5.98	5.78
GS153	150mm x 300mm/5.91" x 11.81"	10.20	7.20	6.80
GS1212	305mm x 305mm/12" x 12" <b>NEW!</b>	18.88	15.73	12.59

CAT NO	DESCRIPTION	PRICE EACH		
		1	10	50
GD101	100mm x 150mm/3.91" x 5.91"	\$ 5.07	\$3.68	\$3.38
GD114	114mm x 165mm/4.6" x 6.6"	5.95	4.29	3.99
GD152	150mm x 250mm/5.91" x 9.84"	10.47	7.39	6.98
GD153	150mm x 300mm/5.91" x 11.81"	11.95	8.69	8.30
GD1212	305mm x 305mm/12" x 12" <b>NEW!</b>	22.09	18.35	14.68

**Developer** This product is used as the developer on our positive photo-resist printed circuit boards. Includes instructions. 50 gram package, mixes with water, makes 1 quart.

CAT NO	DESCRIPTION	PRICE EACH		
		1	10	25
POSDEV	Positive Developer	\$.95	\$.80	\$.50

**Etching Tank** This handy etching system will handle PC boards up to 8" x 9", two at a time. Ideal for etching your PCB's! System includes an air pump for etchant agitation, a thermostatically controlled heater for keeping etchant at optimum temperature and a tank that holds 1.35 gallons of etchant. A tight fitting lid is also supplied to prevent evaporation when system is not being used. Typical etching time is reduced to 4 minutes on 1oz. copper board!




**REDUCES ETCHING TIME!**

CAT NO	DESCRIPTION	PRICE
12-700	Etch Tank System	\$37.95

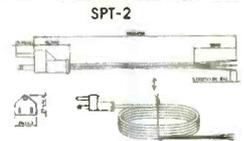
**AC Power Cords**

Our power supply cords are economical and practical for OEM and replacement applications. We stock 6' lengths, with the open end conveniently stripped and tinned (5mm).



CAT NO	SIZE	TYPE	RATING @ 125V (A)				LENGTH (ft)	COLOR	TEMP
			10	10	10	10			
SPT-1BLACK	18/2	SPT-1	10	6	6	6	Black	60°	
SPT-1GRAY	18/2	SPT-1	10	6	6	6	Gray	60°	
SPT-2BLACK	18/3	SPT-2	10	6	6	6	Black	60°	


CAT NO	DESCRIPTION	PRICE EACH			
		1	10	100	500
SPT-1BLACK		\$.88	\$.57	\$.51	\$.46
SPT-1GRAY		.92	.61	.55	.49
SPT-2BLACK		1.97	1.21	1.07	.97

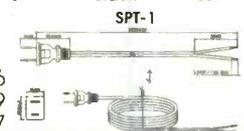

**SEE OUR ON-LINE CATALOG AT**  
<http://www.cir.com>
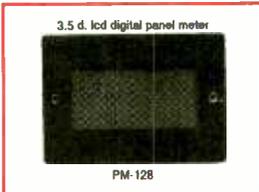
## Digital Panel Meters (LCD & LED)

Don't let the prices fool you. These digital panel meters are not surplus, so even if you design them into an ongoing manufactured product, you can be assured of continued availability. These high quality digital panel meters are decimal point selectable with guaranteed zero reading at zero volts input.



## 3-1/2 Digit LCD 3-1/2 Digit LED 4-1/2 Digit LCD

PM-328: 4-1/2 Digit LCD Digital Panel Meter

### Features

- 200.00mV Full Scale Input Sensitivity
- Single 9V DC Operation
- Decimal Point Selectable
- 11mm LCD Figure Height
- Automatic Polarity Indication
- Low Battery Detection and Indication
- High Input Impedance (>100 Mohm)

### Applications include:

- Voltmeter
- Thermometer
- pH Meter
- dB Meter
- Watt Meter
- Current Meter
- Capacitance Meter
- LUX Meter
- LCR Meter
- Other Industrial & Domestic Uses

### PM-128: 3-1/2 Digit LCD Digital Panel Meter

### PM-129: 3-1/2 Digit LED Digital Panel Meter

### Features

- 200mV Full Scale Input Sensitivity
- PM-128 - Single 9VDC Operation
- PM-129 - Single 9VDC Operation
- Decimal Point Selectable
- PM-128 - 13mm Figure Height
- Automatic Polarity Indication
- Guaranteed Zero Reading for 0 Volt Input
- High Input Impedance (>100Mohm)

### Specifications - PM-128/PM-129

Maximum Input	: 199.9mV DC
Maximum Display	: 1999 counts (3-1/2 Digits) w/Automatic Polarity Indication
Indication Method	: PM-128 - LCD Display PM-129 - LED Display
Measuring Method	: Dual-Slope Integration A/D Converter System
Overrange Indication	: '1' Shown in the Display
Reading Rate Time	: 2-3 Readings per sec.
Input Impedance	: >100 Mohm
Accuracy	: +/-0.5% (23+5°C, <80% RH)
Power Dissipation	: PM-128 - 1mA DC PM-129 - 60mA DC
Decimal Point	: Selectable w/Wire Jumper
Supply Voltage	: PM-128 - 9V DC PM-129 - 9V DC
Size	: 67mm x 44mm

### Specifications - PM-328

Maximum Input	: 199.99mV DC
Maximum Display	: 19999 counts (4-1/2 Digits) w/Automatic Polarity Indication
Indication Method	: LCD Display
Overrange Indication	: '1' Shown in the Display
Input Impedance	: >100 Mohm
Accuracy	: +/-0.05% (23+5°C, <80% RH)
Power Dissipation	: 1mA DC
Decimal Point	: Selectable w/Wire Jumper
Supply Voltage	: 9V DC
Size	: 67mm x 44mm

**AS LOW AS \$5.25 ea.**

CAT NO	DESCRIPTION	PRICE EACH				
		1	10	25	100	250
PM-128	3-1/2 Digit LCD Panel Meter	\$ 9.90	\$ 7.09	\$ 6.40	\$ 5.86	\$ 5.25
PM-129	3-1/2 Digit LED Panel Meter	11.49	9.54	8.67	7.95	6.95
PM-328	4-1/2 Digit LCD Panel Meter	19.88	16.40	14.90	13.66	11.93



**Ball Bearing 12V DC Fans** These High Quality Fans feature Ball Bearings and Brushless DC Motors. All of them are designed to meet UL, CSA & VDE Standards. Design these fans into power supplies, computers or other equipment requiring additional air flows for heat removal. These fans are regular Circuit Specialists stock items — they are not surplus.

**INDUSTRY BEST PRICING!**

CAT NO	PRICE EACH			
	1	10	25	100
CSD 4010-12	\$ 9.88	\$ 6.38	\$ 5.48	\$ 4.87
CSD 6025-12	9.38	5.91	5.41	4.71
CSD 8025-12	8.88	5.85	5.19	4.49
CSD 9225-12	8.95	6.14	5.29	4.59
CSD 1225-12	11.45	8.96	7.82	6.85

### Specifications

CAT NO	DIMENSIONS (MM)	RATED VOLTAGE (V)	START VOLTAGE (V)	INPUT CURRENT (A)	AIR FLOW (CFM)	STATIC PRESSURE (INCH-H <sub>2</sub> O)	SPEED (RPM)	NOISE LEVEL (dB)	WEIGHT (g)
CSD 4010-12	40x40x10mm	12	7	0.06	5.1	0.19	5,500	26	20
CSD 6025-12	60x60x25mm	12	5	0.13	13.7	0.165	4,500	28	65
CSD 8025-12	80x80x25mm	12	5	0.16	37.8	0.177	3,000	31	80
CSD 9225-12	92x92x25mm	12	5	0.32	42	0.18	2,800	37	95
CSD 1225-12	120x120x25mm	12	5	0.35	62	0.180	2,500	42	135

- SOLDER • SOLDER • SOLDER • SOLDER
- SOLDER • SOLDER • SOLDER • SOLDER

Weststock high quality 60/40(Sn%/Pb%), .031" and 63/37, .031" diameter. This is prime JIS certified solder that we maintain as a regular stock item (It is not "Left-overs, Rejects or Surplus") and you can buy it from us at a fraction of the price that you are used to.



**Tired of Paying Inflated Prices for Solder?**

CAT NO	DESCRIPTION	PRICE EACH		
		1	10	25
RH60-1	1-lb. Spool, .031", 60/40	\$ 6.90	\$ 5.96	\$ 5.30
RH63-1	1-lb. Spool, .031", 63/37	6.95	6.10	5.41
RH60-4	4.4-lb. Spool, .031", 60/40	24.00	21.90	17.92
RH60-TUBE	6-oz. Tube, .031", 60/40	.99	.89	.79

CAT NO	DESCRIPTION	PRICE EACH	
		1	5
CA-H34A	PCB Mounted IRCCD Camera	\$99.00	\$85.00
A34	Power Supply Regulating Kit	\$6.95	---

### CCD Camera - IR Responsive As Low As \$85!!

This black and white monochrome CCD Camera is totally contained on a PCB (70mm x 46mm). The lens is the tallest component on the board (27mm high from the back of the PCB) and it works with light as low as 0.1 lux. It is IR Responsive for use in total darkness. It comes with six IR LED's on board. It connects to any standard monitor, AUX or video input on a VCR or through a video modulator to a TV. Works with a REGULATED 12V power supply (11V-13V). Hooks up by connecting three wires: red to 12V, black to ground (power & video) and brown to video signal output.



**Power Supply Regulating Kit for CA-H34** This simple kit is designed to fit onto the back of the CA-H34 CCD camera. It resolves the problem of hooking up the camera to an UNREGULATED supply (which damages the camera) by providing safe regulated power from any 12V-14V DC supply. It also provides regulated 12V DC from a 12V AC source.

**SEE OUR ON-LINE CATALOG AT <http://www.cir.com>**

## CIRCUIT SPECIALISTS, INC.

SINCE 1971  
**800-811-5203**  
**602-464-2485**  
**602-464-5824(FAX)**

**WE ACCEPT:**



### RECEIVE OUR LATEST 132 PAGE CATALOG!


It's chock full of all types of electronic equipment and supplies. We've got I.C.'s, capacitors, resistors, pots, inductors, test equipment, breadboarding supplies, PC supplies, industrial computers, data acquisition products, personal computers and computer parts, plus much, much more. FAX us your name and address or call **800-811-5203, ext. 5**, to leave a message on our catalog request line.



**CABLE TV CHANNELS**  
EQUIPMENT Direct!  
**GUARANTEED**  
SAVE \$1000's  
The Nationwide source for cable TV equipment.  
"BUY WHERE THE DEALERS BUY."  
TV Cable Descramblers, Converters and Magic Box Catalog. Open Every Day!  
**FREE**  
Your VCR TAPES CAN PLAY AS CLEAR AS DAY!  
Eliminates copy protection on any tape  
ENJOIN NOW WITH Video Decoder  
Copy any rerec'd tape  
Power Cord and RC Plug included  
2 Year Warranty  
**CALL NOW!**  
Member Better Business Bureau  
**MEGA ELECTRONICS!**  
1-800-676-6342  
FREE 30 Day Trial!  
VISA • MC • COD

# Discover DC Electronics

17-Module Course -- Only \$49.95

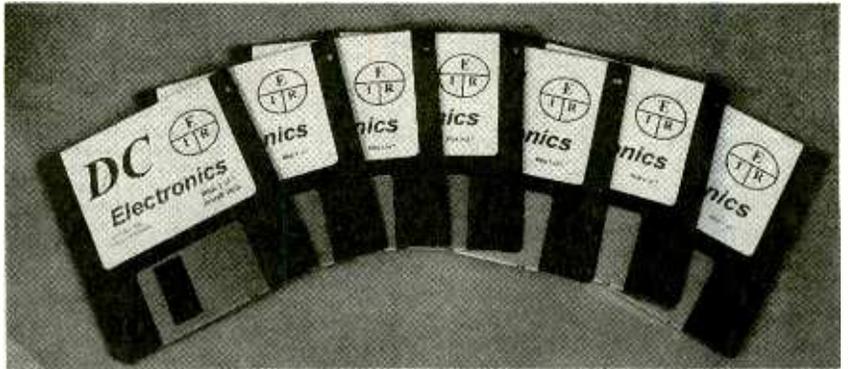

Contains everything you ever needed to know about DC electronics. Whether you are a professional working in electronics and you want a review of the basics, or a student or hobbyist new to this field and need a good self-paced course, this is the perfect way to get started.

The course starts with basics and assumes you know nothing about electronics. It teaches the required math, how to use a scientific calculator, and the metric notation system. Each module has been written by an electronics instructor, and will directly from a floppy or from a menu-driven system on your hard drive. Every module includes a review, summary, quiz, and a final exam that can be printed out. Important points are animated to make the explanation clear.

System requirements: IBM Compatible, 512K RAM, VGA Color, Hard Drive and DOS 3.2 or newer.



## Here are the Modules

1. Atoms and Electrons
2. Volts / Current / Resistance
3. Numbers greater than one  
Scientific - metric notation
4. Numbers less than one  
Scientific - metric notation
5. Resistor Color Codes
6. Using Calculators
7. Ohms Law and Power
8. Series Circuits
9. Parallel Circuits
10. Series / Parallel Circuits
11. Voltage Dividers
12. Kirchhoff's Law
13. Advanced DC Circuit Analysis
14. Capacitors / RC Time Constants
15. Introduction to Magnetism
16. Inductors and L/R Time Constants
17. Volt/Ohm/Current Meters

Claggk Inc. P.O. Box 4099, Farmingdale, NY 11735

Send me my course, today! Charge me the special introductory price!

Name \_\_\_\_\_ \$49.95 + \$4.95 shipping

Address \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_

Zip \_\_\_\_\_

Payment Enclosed \$ \_\_\_\_\_

Check  Money Order  Credit Card

New York residents add local sales taxes. Canadians add \$6

per order. Credit card orders by phone or fax. Automated

telephone orders 516-293-3751. Fax 516-293-3115.

Allow 4 to 6 weeks for delivery.

### Credit Card Info

MC  Visa


Card # \_\_\_\_\_

Exp Date \_\_\_\_\_

Signature \_\_\_\_\_
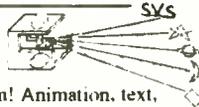
## \$139\* Laser LightShow

Draw with a laser beam! Animation, text, music & more! Includes galvos, mirrors, servo amp, demo software disk, analog and digital computer interface. Use an inexpensive pen pointer or high power gas laser.



## Computerized Motors \$39\*

Includes: 2 Stepper motors, 2 DC motors, computer interface, training manual, & demo software disk. Expandable! Up to 12 motors, up to 3 amps per phase.

Now with 4 Axis Linear Interpolation

\* Add \$6 for shipping. Computer with parallel printer port & cable assembly, power supply, & laser arc required

## FREE FLYER

Voice 510-582-6602 Fax 510-582-6603



1273 Industrial Pkwy West Bldg. 460  
PO Box 55125 Hayward CA 94545-0125

<http://www.xtronics.com/kits.htm>

Electronic Kits! As Seen on our WEB site!

Solderless Kits	Other Kits
Crystal radio \$5.75	FM Microphone \$6.95
Metal Detector \$8.50	Ultrasonic Translator (Hear \$18.50
MW IC Radio \$9.50	Ultrasonic-sound) \$18.50
Bend Wire Game \$7.95	Glitter-Globe Buckminster Fuller
Audio Amplifier \$8.50	sphere 64 LEDs EN1292 \$45.00
Home Alarm \$12.00	Deluxe IC Radio \$11.95
Rain-Flood Alarm \$7.95	Merchandise alarm \$14.95
Test Equipment Kits	Train Sound Module \$3.80
Function Gen w/FM \$28.00	Sound operated control \$3.90
Function Generator \$14.95	Light Receiver module \$3.90
Pulse Generator \$28.00	IR Receiver module \$3.90
RF Sig Generator \$28.00	IR Transmitter \$3.90

3209 W. 9th Street  
Lawrence, KS 66049



Transtronics

ph 913 841 3089  
FAX 913 841 0434  
See more kits at:

Minimum Order \$20.00  
Shipping \$5.00 COD + \$2.00  
Free shipping if over \$40.00  
We ship over seas!

<http://www.xtronics.com/kits.htm>

**FM TRANSMITTERS!  
FUN PROJECTS!  
AND MORE!**

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

**ELECTRONIC  
KITS!**

TOLL FREE ORDER LINE: 1-800-336-7389

FAX LINE: 1-602-731-4748

TECH SUPPORT NUMBER: 1-602-829-0755

XANDI ELECTRONICS, INC.

YOUR MANUFACTURER OF HIGH QUALITY KITS!

**143.775 MHz CRYSTAL CONTROLLED TRANSMITTER KITS**



**XTR300EZ** \$79.95  
**XTL3000EZ** \$99.95  
**XTL1000EZ** \$69.95

**XTR300 TRACKING TRANSMITTER KIT**  
Transmits continuous beep-beep-beep  
Ideal for locating lost or stolen items  
Range up to 1 mile

**XTL3000 LONG RANGE TRANSMITTER KIT**  
Sensitive built in microphone  
Range up to 1 mile  
Custom frequencies available

**XTL1000 TRANSMITTER KIT**  
Sensitive built in microphone  
Range up to 1/2 mile  
Custom frequencies available

**CRYSTAL TRANSMITTER KITS**

- Ultra-miniature surface mount construction.
- E-Z kit approach makes assembly a snap.
- Miniature battery and holder will mount directly to the circuit board.
- Transmit to any scanner type receiver

**BUG DETECTOR**

**XBD500**  
**\$129.95**

- Professional quality.
- Assembly is a snap.
- Covers 1 to 2,000MHz.
- Uses new Microwave Integrated Circuit amplifier.
- Adjustable sensitivity.
- Audic jack for privacy ear phone.



Any intercepted signal causes an audio tone that increases from a low pitched growl to a high pitched squeal as the signal strength increases.

**88-108 MHz FM RECEIVER**

**XMR2000**  
**\$29.95**

- Worlds smallest FM radio.
- As small as a hearing aid.
- Weighs less than 1/4 oz.
- Digital touch tuning.
- Ideal for use with our 88-108MHz FM transmitters



**88-108 MHz FM TRANSMITTER KITS**



**XST 500EZ** \$49.95  
**XWB 1000EZ** \$46.95  
**XFM 100C** \$21.95



**XSP 250EZ** \$34.95  
**XTR 100C** \$29.95  
**XTT 100C** \$19.95

**XST 500** Voice transmitter. Range up to 1 mile. Supersensitive mic. Uses 9 volt battery. Uses surface mount components.

**XWB 1000** Voice transmitter. Range up to 1/2 mile. Includes mic and battery on circuit board. Uses surface mount components.

**XFM 100** Voice transmitter. Range up to 1 mile. 9 v battery and leaded components.

**XSP 250** Super-miniature telephone transmitter. Range 1/4 mile. Powered by phone line. Uses surface mount component.

**XTR 100** Tracking transmitter. Range up to 1 mile. Uses 9 volt battery. Transmits a BEEP - BEEP - BEEP tone

**XTT 100** Telephone transmitter. Range up to 1 mile. Uses 9 volt battery.

**NEW!!**



**XPC 200 PIN HOLE CAMERA**  
**400 LINE RESOLUTION**

- Audio and Video outputs.
- See entire room through pin sized hole.
- Use with any TV or VCR with audio & video input connectors.
- Other models available.

Assembled **\$169.95**

**XVS100 TV TRANSMITTER**

- Use with XVC200, VCR, Camcorder, etc.
- Power cube included.
- Uses VHF TV Band.
- Transmits video & audio.
- Up to 100 foot range.

E-Z Kit **\$29.95**

**"THE ENFORCER!"  
NEW!**

**XXE-1000**  
as a kit **\$39.95**  
assembled **\$49.95**

Use it to test radar detectors in other cars from your own vehicle! 10.450 to 10.550 GHz hand held transmitter. Extra high output level. Includes an input connector for keyed amateur band operation.

**PHONE VOICE CHANGER KIT**

16 levels of digital voice changing. Sound tougher, older or younger, female or male.

**NEW!!**

Works with regular or multi-line phones. Connects between handset and phone. Note: will not work with cordless or cellular type telephones.



**XVC-2005C**  
**\$59.95**

**XANDI ADVANCED HOBBY KITS**



**XPS 1000C**  
**\$55.95**

**TELEPHONE SNOOP KIT**

- Dial home from anywhere and hear inside your home.
- TouchTone coded for secure operation.
- Stop burglars and intruders.
- Reliable 24 hour protection.



**XLC 900C**  
**\$49.95**

**SCANNER CONVERTER KIT(800-950MHZ)**

- Uninterrupted coverage of the 800 to 950 MHz band.
- Works with any 400-550MHz scanner.
- Gain: 6 dB typical.
- Noise figure: 3 dB typical.



**XVA 250C**  
**\$49.95**

**VOICE-STRESS ANALYZER KIT**

- See at a glance if your being lied to!
- Subject need not be present. Works with voices from recordings, TV or radio.
- Has built-in microphone.
- Easy to use LED display output.



**XFS 108C**  
**\$39.95**

**88-108 MHz FM STEREO TRANSMITTER KIT**

- Separate level control for both left and right channels.
- Output level circuit with test points for quick and easy tuning.
- Transmit from any stereo audio source to most any FM stereo receiver.

Serving the public since 1981

**XANDI ELECTRONICS, INC.**  
1270 E Broadway Rd. # 113  
Tempe AZ 85282

WE ACCEPT CHECK, VISA, MC, MO, COD  
SHIPPING & HANDLING EXTRA



**CALL FOR YOUR FREE CATALOG**

SEND MAIL ORDERS TO:  
XANDI ELECTRONICS, INC.  
BOX 25647  
TEMPE, AZ 85285-5647

CIRCLE 134 ON FREE INFORMATION CARD

## LEARN ELECTRONICS!

Home study. Make excellent money. Repair and install camcorders, TVs, VCRs, stereos, sound and lighting, alarm systems, and more!

**FREE LITERATURE: 800-223-4542**

Name \_\_\_\_\_ Age \_\_\_\_\_  
 Address \_\_\_\_\_ Phone (\_\_\_\_) \_\_\_\_\_  
 City/State \_\_\_\_\_ Zip \_\_\_\_\_  
 School of Electronics, Dept. ELF341, PCDI, 6065 Roswell Rd., Atlanta, GA 30328

## BUGGED??

**EAVESDROPPING** is unbelievably widespread! Electronic Devices with amazing capabilities can be monitoring your telephone and room conversations **RIGHT NOW!** Are you sure you're safe? **FREE CATALOG** tells you fast! Includes Free Bonus details on fantastic opportunities now open in Counter-Surveillance field. Exciting, immensely interesting and **EXTREMELY** profitable (up to \$250 hr) full/part-time income. Call Now!

**1-800-732-5000**

## CABLE T.V.

### Converters & Equipment WISE PRODUCTS

30-day money back  
1-year warranty

Dealers  
Welcome!

**1-(800) 434-2269**

Visa, MC, Amex, COD



## Radiotelephone - Radiotelegraph

# FCC Commercial License

### Why Take Chances?

Discover how easy it is to pass the exams. Study with the most current materials available. Our **Homestudy Guides, Audio, Video or PC "Q&A"** pools make it so fast, easy and inexpensive. No college or experience needed. The new commercial FCC exams have been revised, covering updated Aviation, Marine, Radar, Microwave, New Rules & Regs, Digital Circuitry & more. We feature the Popular "Complete Electronic Career Guide" 1000's of satisfied customers **Guarantee** to pass or money back. Send for **FREE DETAILS** or call **1-800-800-7588**

WPT Publications  
4701 N.E. 47th Street  
Vancouver, WA 98661

Name \_\_\_\_\_  
 Address \_\_\_\_\_  
 City \_\_\_\_\_ St. \_\_\_\_\_ Zip \_\_\_\_\_

**1-800-800-7588**

## Smart Battery Charger



**JUN 87 QST**  
**BY WARREN DION N1BBH**

**FOR GEL-CELLS or LEAD ACID BATTERIES.** Features: Precision temperature tracking voltage reference & three mode charging sequence. Standard kit is for 12V @ 1/2 or 1 Amp, user selectable. Can be connected to the battery indefinitely, will not overcharge. Weighs 2 pounds and measures 4"W x 5 1/2"D x 2 1/2"H. Finished enclosure included in kit.

**Complete Kit Only ..... \$59.95**  
**Assembled & Tested ..... \$79.95**

CA Residents add 7.75% sales tax. S&H: \$5.00 (Insured). Foreign orders add 20%. For more info or price list; send legal size SASE (52¢) to:

**A&A Engineering**   
 2521 W. La Palma #K • Anaheim, CA 92801  
 (714) 952-2114 • FAX: (714) 952-3280

## VIDEO SYNC GENERATOR



### Restores Horizontal and Vertical Sync Lines from Distorted Analogue Video Formats

For Free Information Package on Completed Units and Pricing

 • **Call 219-236-5776** • 

L.C. Distributing • PO Box 552 • South Bend, IN 46624

### Quality Microwave TV Systems

**WIRELESS CABLE - ITFS - MMDS**  
**ATV • INTERNATIONAL • S-BAND**  
 Amplifiers • Antennas • Books • Components  
 Filters • Systems • Video Products

- RF Frequency 1990 - 2700 MHz
- Cable Ready - VHF - UHF Outputs
- SASE For "FREE" Catalog or Send \$1

**PHILLIPS-TECH ELECTRONICS**  
 PO Box 8533 • Scottsdale, AZ 85252

**ORDER LINE 800-880-MMDS**  
**CATALOG/INFO 602-947-7700**  
**FAX LINE 602-947-7799**

CHALLENGER SYSTEM  
 33-Channel 52dB Gain  
 Complete Grid \$265  
 Five Year Warranty  
**FREE SHIPPING** Visa • MC • Amx • Disc • COD's • Qty Pricing

**CIRCLE 145 ON FREE INFORMATION CARD**

## ELECTRONICS WORK at HOME

Part time/ Full time **up to \$35/hour**

Be your own boss & get out of the rat race NOW! JUST Published. Comprehensive GuideBook tells how to get started. Use your technical skills to make big money NOW! 250+ pages of info/sources Send \$19.95+\$3 S&H

DCP Enterprises	24hr Recording & Faxback	CA only add Tax
15 Mayflower	800-326-4560 x 201	Limited time offer
Aliso Viejo, CA 92656		30 day MONEY BACK GUARANTEE



## CONTROL YOUR WORLD

# 32K HC11 ModCon

Low Cost Microcontroller boards & kits + Applications

**ZORIN** <http://zorinco.com>  
 or call (206) 282-6061

# CABLE DIRECT

## CONVERTERS DESCRAMBLERS VIDEO STABILIZERS FILTERS



**100% MONEY BACK GUARANTEE!**

**30 DAY FREE TRIAL!**

**FREE Cable TV Catalog.**

Now you can tune-in your favorite cable TV programming and **SAVE \$100'S - EVEN \$1000'S** on premium **CABLE TV EQUIPMENT.**

# MODERN ELECTRONICS

**1-800-906-6664**  
 2125 S. 156TH CIRCLE • OMAHA, NE 68130

## BROADCAST TRANSMITTER

The FMS2 studio quality transmitter is **FULLY** crystal controlled and programmable to any FM broadcast frequency.

Unit features: ALC, 2:1 compressor, audio buffer / amplifier, pre-emphasis, roll off filter, stereo generator, digital PLL tuning, 75 MHz-125MHz bandwidth, 500mW power output and a special introductory price of only \$295.00

SCHEMATICS FOR UNIT \$27 CATALOG 800-504-1178  
 FAX POLL INFO 416-243-1067 TEK LINE 416-243-2260 

## PROTOTYPES

Or large runs. PCBs, wave soldering, cabinets and other metal parts, silk screen printing, plastic injection, xformer/coil winding, etc. Assembly, wiring. Very low prices! Twin plant in Mexico. We ship to your door. V&V. PH. (713) 537-7518 Fax. 011 (525) 361-5996.

## New Surveillance Devices!

**Smoke Alarm and Table Clock Video Cameras** Ultra miniature video cameras hidden in smoke alarm or alarm clock - your choice. Wide field of View and super .1 lux low light sensitivity. Undetectable!

**SC-600** High quality B/W with 420 lines of resolution for ultra sharp images. Direct output of video and audio. **\$189.95 ea.**

**Best price on surveillance cameras anywhere!**

**Telephone Transmitter Kit** hidden in dual modular adaptor. Transmits both sides of conversation to any FM radio up to 1/4 mile. "SnapKit" technology. Uses phone line for power and antenna. Goes completely unnoticed. **MA-100 \$25.95**

High quality cassette deck plugs directly into telephone Jack! Records up to 12 hours of conversations on a single cassette. Recording starts and stops automatically when phone is used! **Visa/MC (800) 594-1047**

**THR-1x 12 Hour Telephone Recorder \$99.95** Free shipping! Check/MO Question line: (972) 255-7480

**Seymour-Radix Inc. Box 166055-E Irving, TX 75016**  
 Now you can visit us on the internet at: <http://www.why.net/home/sr/>

# 9 out of 10 mice prefer it.

Catch the free Consumer Information Catalog online and you'll get the latest info from the U.S. Government. Just point and click your way to [www.pueblo.gsa.gov](http://www.pueblo.gsa.gov) and you'll find more than 250 free publications ready to read or download.

Or, order the Catalog by mailing your name and address to **Free Catalog, Pueblo, CO 81009**. Scurry, this info's the cat's meow.

U.S. General Services Administration



[www.pueblo.gsa.gov](http://www.pueblo.gsa.gov)



## Imagine Little Red Riding Hood without a forest.



PLEASE be very careful with matches. Because without the forests, life is unimaginable.

Only You Can Prevent Forest Fires.



USDA Forest Service and your State Forester.

## PROGRAMMERS OVER 40 MODELS

ADVANTECH EETOOLS NEEDHAMS DATA VO ICE TECHNOLOGY HILO SYSTEM GENERAL CHROMA MODULAR CIRCUIT TECHNOLOGY XELTEK



PROMAX EMP-20 MEGAMAX MEGAMAX4 SIMM/SIP TESTER EMUPA

CALL ADVANTECH LABTOOL	599 EETOOLS SIMMAX
629 ICE TECH MICROLV	795 CHROMA SIMM/SIP
650 EETOOLS ALLMAX +	359 MOD-MCT-EMUPA/R
409 EETOOLS MEGAMAX	279 MOD-MCT-EMUP/R
509 EETOOLS MEGAMAX4	49 EPROM 1G TO 512K
369 XELTEK SUPERPRO II	69 EPROM 1G TO 1MEG
409 XELTEK SUPERPRO II P	99 EPROM 4G TO 1MEG
249 XELTEK SUPERPRO L	199 EPROM 16G TO 1 MEG
165 XELTEK ROMMASTER II	89 EPROM 1G TO 8MEG
479 MOD-MCT-EMUPA	129 EPROM 4G TO 8MEG
739 STAG ORBIT-32	250 EPROM 8G TO 8MEG




LABTOOL48 MICROMASTER SUPERPRO ALLMAX PLUS ROMMASTER2

### General Device Instruments

Sales 408-241-7376 Fax 241-6375 BBS 983-1234  
Web [www.generaldevice.com](http://www.generaldevice.com) E-Mail [icdevice@best.com](mailto:icdevice@best.com)
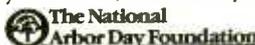
## Trees Make a World of Difference

Find out how trees can make a world of difference for you, and your neighborhood. For your free brochure write: Trees For America, The National Arbor Day Foundation, Nebraska City, NE 68410.



## Learn MICROCONTROLLERS EMBEDDED SYSTEMS and PROGRAMMING...

...with the AES learning system/embedded control system. Extensive manuals guide you through your development project. All programming and hardware details explained. Complete schematics. Learn to program the LCD, keypad digital, analog, and serial I/O. for your applications.



**THREE MODELS AVAILABLE. Choose from an Intel 8051, Intel 8088, or Motorola 68HC11 based system. All models come with:**

- 32K Byte ROM, 32K Byte RAM • 2 by 16 Liquid Crystal Display • 4 by 5 Keypad • Digital, Analog, and Serial I/O • Interrupts, timers, chip-selects • 26 pin expansion connector • Built-in Logic Probe • Power Supply (can also be battery operated) • Powerful ROM MONITOR to help you program • Connects to your PC for programming or data logging (cable included) • Assembly, BASIC, and C programming (varies with model) • Program disks with Cross Assembler and many, well documented, program examples • User's Manuals cover all details (over 500 pages) • Completely assembled and ready to use • Source code for all drivers and MONITOR • Optional Text Book

Everything you need. From \$279. Money Back Guarantee

Call for Free Info Pack, or see WEB at <http://www.aesmicro.com>  
714-550-8094 FAX 714-550-9941



**Call 1-800-730-3232**

AES 970 W. 17TH STREET, SANTA ANA, CA 92706, USA

## The Pocket Programmer

**\$129.95**



The portable programmer that uses the printer port of your PC instead of an internal card.

Easy to use software that programs E(E)prom, Flash & Dallas Ram. 27(C)/28(C)(F)/29(C)(F)/25 series from 16K to 8 Megabit with a 32 pin socket. Adapters available for MCU's 874X, 875X, Pic, 40-Pin X 16 & Serial Eprom's, PLCC, 5-Gang and Eprom Emulator to 32K X 8.

**Same Name, Address & Phone # for 13 Years.... Isn't it Amazing ?**

**Intronics, Inc.**  
Box 13723 / 612 Newton St.  
Edwardsville, KS 66113 Add \$4.75 COD  
Tel. (913) 422-2094 Add \$4.00 Shipping  
Fax (913) 441-1623 Visa / Master Charge

## Be a PC repair expert!


Approved home study. Learn to troubleshoot, repair, install, upgrade, and service computers. **Free literature: 800-223-4542**

Name \_\_\_\_\_ Age \_\_\_\_\_  
Address \_\_\_\_\_ Phone (\_\_\_\_) \_\_\_\_\_  
City/State \_\_\_\_\_ Zip \_\_\_\_\_  
School of PC Repair, DEPT JF341, PCDI  
6065 Roswell Road, Atlanta, Georgia 30328


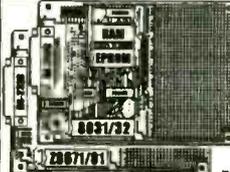
## CABLE TV CONVERTERS

Equipment & Accessories  
Wholesalers Welcome  
Call C&D ELECTRONICS  
1-800-310-1153 M-F 10a-6p



**Prototype it FAST!**  
With Protoboard 8081 or 23  
Fully assembled 8081 or 23 89C  
4.5 x 8 inch board w/ large proto area  
Supports up to 32K EPROMS - 32K RAM  
Chips in sockets - No R separation  
Operates in EPROM w/ source and a pen  
Full docs w/ schematic - no royalties  
Ready to run... **\$99.00 ea.**

Software Science  
3760 Roundbottom Rd.  
Cincinnati, Ohio 45244  
**1-800-561-2060**

## "FULL VIEWING" CABLE BOXES

**FREE**

Converter Box Catalog  
Open Every Day!

**LOWER YOUR CABLE  
BILL NOW!**

**CHANNEL SURFERS**

**1-800-447-7634**

## IMPROVE YOUR IMAGE! WITH OUR VIDEO STABILIZERS

BEFORE

AFTER



**SUPER VHS  
MODEL  
AVAILABLE!**

The clearest picture possible  
playing back movies.  
**GUARANTEE**  
to eliminate copy protection.


- No Rolls/Jitters/Flickers/Fading
- Works on all TV's, VCR's Beta & Cable
- Gold Video Connectors & Cables Included
- 2 Year Warranty
- Money Back Guarantee



**VISION  
ELECTRONICS**


**1-800-562-2252**

2125 S. 156TH CIRCLE • OMAHA, NE 68130

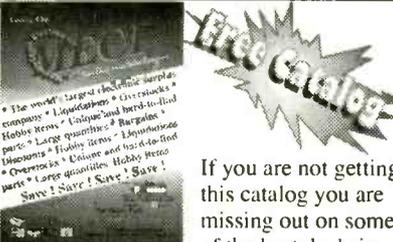

If you are not getting this catalog you are missing out on some of the best deals in electronics today! We have thousands of items ranging from unique, hard-to-find parts to standard production components. Call, write, or fax today to start your free subscription to the most unique catalog in the industry, filled with super values on surplus electronic and hobbyist type items. If you have a friend who would like to receive our catalog, send us their name and address and we will gladly forward them a complimentary 100 page catalog.

Why pay more? Call today.

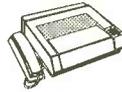

340 East First Street Fax Order Line  
Dayton, Ohio 45402 1-800-344-6324

Order Toll-Free  
**1-800-344-4465**

CIRCLE 147 ON FREE INFORMATION CARD

## WE HAVE IT ALL! Surveillance

- Infinity Transmitters
- FM Wireless Transmitter Kits
- Vehicle Tracking Systems
- Bug Detectors • Caller I.D.
- Telephone Register with Printer
- Long-play Recorders
- Wired Mikes • Shotgun Mikes
- Telephone Recording Adapters
- Alcohol Testers • Drug Testers
- Telephone Scramblers
- Hidden Video Cameras
- Telephone Tap Detectors
- MUCH, MUCH, MUCH MORE.**

**Our 27th Year!**

Small catalog FREE. Larger catalog send \$5.  
Mail Order only. Visa, MasterCard and  
C.O.D. accepted for equipment only.  
Inquire for dealers' prices.

**A.M.C. SALES, INC.**

193 Vaquero Dr. • Boulder, CO 80303  
Mon.-Fri. 8 a.m.-5 p.m. Mtn. Time  
**800-926-2488**

(303) 499-5405 • Fax (303) 494-4924  
Internet: [http://www.siteleader.com/  
catalogdepo/AMCSC-home.html](http://www.siteleader.com/catalogdepo/AMCSC-home.html)  
E-mail: [amc-sales@siteleader.com](mailto:amc-sales@siteleader.com)

## WHOLESALE PRICES STARTING AS LOW AS \$99.00

# CABLE TV DESCRAMBLERS CONVERTERS FILTERS • VIDEO STABILIZERS

1 Year Warranty on All Products.  
Affordable Extended Warranty.  
**FREE CATALOG!**



Call the Cable Professionals 24 Hours A Day!

**Orion  
Electronics**

**1-800-379-3976**

[HTTP://WWW.ORION-ELECTRONICS.COM](http://www.orion-electronics.com)

## KEEP YOUR C-BAND SYSTEM RUNNING STRONG!

Free Buyer's Guide

**BEST VALUES ON...**

- Receivers, including 4DTV
- Dish Movers & LNB's, all kinds
- Tune-up Kits, Tools & Parts
- Skypac™ Programming
- Toll Free Technical Help



Int'l 218-739-5231 Fax: 218-739-4879

**800-334-6455**  
[www.skyvision.com](http://www.skyvision.com)

**Skyvision**

Picture the Seven  
Dwarfs without  
a forest.

Only You Can Prevent Forest Fires.



USFA Forest Service and your State Forester.

## SMART & PHOENIX

**CABLE DIAGNOSTIC UNITS  
(JERROLD COMPATIBLE ONLY)**

**EXTERNAL FTG  
ACTIVATOR/TESTER/PROGRAMMER  
MULTI-FREQUENCY AND MULTI-MODE.  
WIRELESS, SMALL IN SIZE AND  
BATTERY OPERATED. STATE OF THE  
ART SMD TECHNOLOGY. PROVEN  
OUTSTANDING PERFORMANCE.**

**CALL MAKFIT RESEARCH:**

**1-800-220-3643** AFTER 10 AM P.B.T.

<http://ourworld.com/userve.com/homepages/makfit>  
QUALIFIED TECHNICIANS ONLY. NO CA SALES

# CONTROL MEASURE INPUT

RELAYS • LIGHTS • MOTORS  
TEMPERATURE • PRESSURE • LIGHT LEVELS • HUMIDITY  
SWITCH POSITIONS • THERMOSTATS • LIQUID LEVELS

**MODEL 30 . . . . . \$79**



- PLUGS INTO PC BUS
- 24 LINES DIGITAL I/O
- 8 CHANNEL
- 8 BIT A/D IN
- 12 BIT COUNTER
- UP TO 14K BMP/SEC

**MODEL 45 . . . . . \$189**




- RS-232 INTERFACE
- 8 DIGITAL I/O
- 8 ANALOG INPUTS
- 2 ANALOG OUTPUTS
- 2 COUNTERS-24 BIT

**MODEL 100 . . . . . \$279**



- 12 BIT 1-MHZ A/D
- 4 ANALOG OUTPUTS
- 3 TIMER/COUNTERS
- 24 DIGITAL I/O

**MODEL 60 . . . . . \$179**

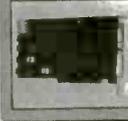

- 8 2-AMP RELAYS
- 16 DIGITAL I/O
- 1 8-BIT ANALOG INPUT

**MODEL 40 . . . . . \$99**



- RS-232 INTERFACE
- 28 LINE DIGITAL I/O
- 8 ANALOG INPUTS
- PWR OUTPUT
- OPTIONAL 12 BIT A/D

**MODEL 70 . . . . . \$239**



- RS-232 INTERFACE
- 18 BIT A/D
- 5.5 DIGIT
- UP TO 60 BMP/SEC

**NEED A CUSTOM PCB? TRY US.**



**PRAIRIE DIGITAL, INC.**  
PHONE 608-643-8599 • FAX 608-643-6754  
846 SEVENTEENTH STREET • PRAIRIE DU SAC, WISCONSIN 53578

CIRCLE 45 ON FREE INFORMATION CARD
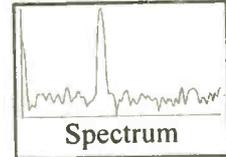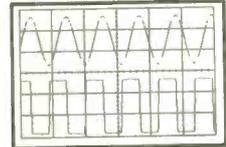
# OSCILLOSCOPES

from \$169 !!!

ATC O-Scope uses printer port to turn PC-AT into Digital Storage Oscilloscope, Spectrum Analyzer, Freq. Counter, Logger, DVM. DC-500KHz



- Print, log to disk, or export data
- Accepts standard scope probes
- Uses standard printer port
- Small and portable
- Works with laptops
- Same day shipping
- Made in U.S.A.
- Single channel units from \$169
- Dual channel units from \$349

**Options:**  
• Probe sets  
• Automotive probes  
• Battery packs


Order yours today.

800 980 9806 MC/Visa/Amex  
Allison Technology Corporation  
8343 Carvel, Houston, TX 77036 USA  
PH: 713 777 0401, FAX: 713 777 4746, BBS: 713 777 4746  
<http://www.atcweb.com>

CIRCLE 137 ON FREE INFORMATION CARD
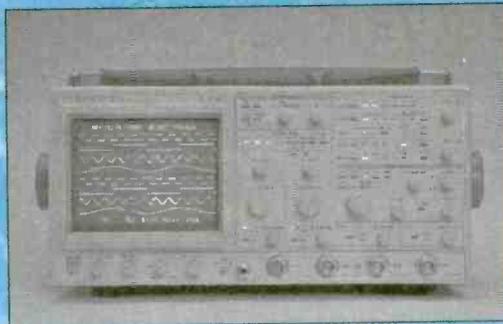
# TEST INSTRUMENT CATALOG !!!

Call, fax or email today for your free copy of our test instrument catalog, jam-packed with the **BEST VALUES** in test and measurement instruments available today!!!



**PRINT**™  
Products International

8931 Brookville Rd \* Silver Spring, MD, 20910 \* 800-638-2020 \* Fx 800-545-0058 \*  
Email: [SMPRODINTL@aol.com](mailto:SMPRODINTL@aol.com)

CIRCLE 46 ON FREE INFORMATION CARD



# CABLE TV Converters & Descramblers

Compatible with  
**Jerrold, Scientific Atlanta,  
Pioneer, Oak, & Hamlin**  
Equipment

**BRAND NEW!**  
6-MONTH GUARANTEE  
**LOWEST PRICES**  
Volume Control & Parental Lockout Available

**Greenleaf Electronics**  
**1-800-742-2567**  
NO ILLINOIS SALES

It is not the intent of Greenleaf Electronics to defraud any pay television operator and we will not assist any company or individual in doing the same.

**AT LAST! DC-20 MHz SYNTHESIZED PERFORMANCE FOR ONLY \$795!**

- DC-20 MHz, 1 Hz resolution, DC offset
- Linear/Log Sweep
- Internal/External AM
- Internal/External FM
- Internal/External PM
- Internal/External SSB
- Internal/External BPSK
- Dualtone Generation
- Internal/External FSK
- Burst
- DTMF Generation
- DTMF Detection
- Power Level Measmt

**Arbitrary Waveform  
Generation Now  
Available!**



The SG-100 gives you clean 1 Hz synthesized precision and a wide diversity of modulation functions all of which can be performed using an internally generated or externally applied signal. You also get signal analysis functions that are just not offered on any other signal source such as DTMF Detection and Power Level Measurement. And because you can download new instrument functions to Flash memory, you can ensure that your SG-100 will never become obsolete.

Call, email, or fax us for your free information kit. Visit us on the web for specs and applications.

**Telulex Inc.**

2455 Middlefield Way S, Mountain View, Ca. 94043  
Fax: (415) 938-0241 <http://www.telulex.com>



C.O.D. P.O.

(415) 938-0240  
email sales@telulex.com

CIRCLE 143 ON FREE INFORMATION CARD

## ❖ ATTENTION CABLE VIEWERS ❖

**CABLE VIEWERS... get back to your BASIC Cable Needs**

**Call 800-577-8775**

For information regarding all of your BASIC cable needs.

**5 GOOD REASONS TO BUY OUR FAR SUPERIOR PRODUCT**

- ❖ PRICE
- ❖ EFFICIENT SALES AND SERVICE
- ❖ WE SPECIALIZE IN 5, 10 LOT PRICING
- ❖ ALL FUNCTIONS (COMPATIBLE WITH ALL MAJOR BRANDS)
- ❖ **ANY SIZE** ORDER FILLED WITH SAME DAY SHIPPING

We handle NEW equipment ONLY - Don't trust last year's OBSOLETE and UNSOLD stock  
**COMPETITIVE PRICING—DEALERS WELCOME**

**HOURS: Monday-Saturday 9-5 C.S.T.**

It is not the intent of B.E.S.W. to defraud any pay television operator and we will not assist any company or individual in doing the same.  
\*Refer to sales personnel for specifications.

**BASIC  
ELECTRICAL  
SUPPLY &  
WAREHOUSING  
CORPORATION**

**P.O. Box 8180 ■ Bartlett, IL 60103 ■ 800-577-8775**

# NOW MAKE AN EXTRA \$600 PART TIME WEEKENDS -- UP TO \$2,000 A WEEK FULL TIME IN *Explosive* SATELLITE DISH TV/ELECTRONICS FIELD!

## Hottest Career Opportunity Since Invention of the VCR!

### See How Fast The Money Rolls In!

**Part time:** *Here's what you can earn  
over a typical weekend:*

Install 2 Satellite dish systems at \$200	= \$400
Repair 4 TV's at \$50 each	= \$200

**Total Weekend Income = \$600**

**Full time:** *Working just five days a week  
you could easily earn:*

Install 5 Satellite dish systems at \$200	= \$1,000
Repair 10 TV's, average \$50 each	= \$500
Clean and adjust 10 CD players, average \$35 each	= \$350
Service 2 Home entertainment centers at \$75	= \$150

**Total Weekly Income = \$2,000**

**In addition you can make big extra profits  
on other supplies you furnish!**

## Get in *THE FAST LANE* on the NEW "INFORMATION SUPERHIGHWAY" Everyone's Talking About!

It's exciting! It's gigantic! The technology of tomorrow is here today! You've been reading and hearing about the amazing Information Superhighway. It's so new that few technicians are equipped to service

this fast emerging field! Foley-Belsaw gives you Satellite dish technology (including new mini-dish) along with the electronic expertise you need to make big money servicing TVs and other electronic equipment.

**Be your own boss!** It's quick and easy to become an expert at home in your spare time. Earn really BIG money adjusting, installing and repairing • *Satellite dish systems* • *TVs* • *Amplifiers* • *CD players* • *AM/FM tuners* • *Home entertainment centers*. Every home, every business, every office in your area desperately needs your expertise!


Your timing just couldn't be better! Never before and probably never again will you have a ground-floor opportunity like this to get into a booming business of your own, make really big money starting right away, be your own boss and enjoy financial freedom and security. The fact you're reading this message shows you're smart enough to realize this!

Satellite dish/TV/Electronics is easy

to learn in your spare time at home. This modern, practical hands-on course combines simple step-by-step lessons with easy-to-follow video cassette guidance. No special experience or electronics background is necessary. Just average mechanical aptitude and the ability to follow simple A-B-C repair procedures that are clearly outlined for you.

And when you complete the course you will receive Foley-Belsaw's official diploma attesting to your expertise.

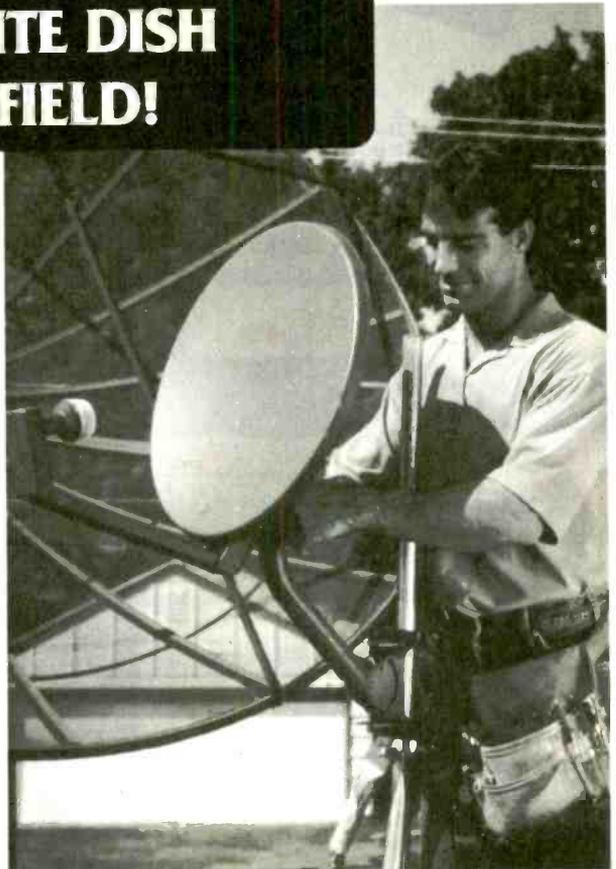**30-DAY  
NO RISK TRIAL**  
Send for details



## Send coupon today for FREE Fact Kit. No obligation.

Don't miss out on this once-in-a-lifetime opportunity. Send in the coupon NOW. Get all the facts and study them in the privacy of your own home. There's absolutely no obligation and no salesman will call on you. So don't delay. Mail the coupon today!

### MAIL TODAY FOR FREE INFORMATION PACKAGE

**Foley-Belsaw Institute**  
6301 Equitable Road  
Kansas City, MO 64120-1395



- YES!** Without obligation send free information kit so I can learn how to become a professional Satellite Dish/TV/Electronics Specialist, in order to earn high extra income. Dept. 31413
- VCR Repair**-Unlimited profits in this growing field. Dept. 62641
- Interested in an exciting, money making career in **Computer Repair, Maintenance and Upgrade?** Dept. 64538
- Personal Computer Programming**-Learn fast at low cost for big earnings. Dept. 35359

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

**Call toll-free 1-800-487-2100**

Zenith Test Chips

# Notch Filters

Beep-Beep



Buzz-Buzz

www.tvfilter.com

Assembled	Kits
1 to 2 \$30 each	1 to 2 \$20 each
3 to 9 \$25 each	3 to 9 \$15 each
10 to 49 \$16 each	10 to 20 \$9 each
50 or more \$14 each	21 or more \$7 each

### Video Media

P.O. Box 93/6025

Margate, Fl. 33093-6025

(954)-752-9202 Fax (954)-340-5201

## Timid about getting on the... World Wide Web?

You've heard about the *Information Superhighway* and all the hype that goes with it! Sort of makes you feel timid about getting on the Web. Put your fears aside! A new book, *The Internet and World Wide Web Explained*, eliminates all the mystery and presents clear, concise information to build your confidence. The jargon used is explained in simple English. Once the tech-talk is understood, and with an hour or two of Web time under your belt, your friends will believe you are an Internet guru!

To order Book #403 send \$6.95 plus \$3.00 for shipping in the U.S. and Canada only to Electronics Technology Today Inc., P.O. Box 240, Massapequa Park, NY 11762-0240. Payment in U.S. funds by U.S. bank check or International Money Order. Please allow 6-8 weeks for delivery.

## WINDOWS 95 —One Step at a Time

Don't know what to do when confronted with Microsoft's Windows 95 screen? Then you need a copy of *Windows 95—One Step at a Time*. Develop your expertise with the straight-forward presentation of the frequently-used features that make Windows 95 so valuable to the PC user.



To order Book BP399 send \$6.95 plus \$3.00 for shipping in the U.S. and Canada only to Electronics Technology Today Inc., P.O. Box 240, Massapequa Park, NY 11762-0240. Payment in U.S. funds by U.S. bank check or International Money Order. Please allow 6-8 weeks for delivery.

## OWN A MACHINE SHOP

The Smithy  
3-in-1  
lathe-mill-  
drill  
gives

you all 3  
basic  
machine

tools in one easy-to-use  
benchtop machine. Save time &  
money. For home or business.



Call for your FREE Info Pak.

1-800-345-6342

FREE  
Info Pak

Ask for  
Operator PE5  
or write

Dept. PE5  
PO Box 1517  
Ann Arbor, MI  
48106-1517

Smithy



In 1872, J. Sterling Morton gave the world a great idea. He created a holiday unlike any other, Arbor Day.

This is the 125th Anniversary of Arbor Day, the tree planters' holiday. This year The National Arbor Day Foundation asks you to plant Trees for America, and provide for their care.

Trees Make a World of Difference. Trees conserve energy, beautify our neighborhoods, and bring songbirds close by. Every tree you plant cleans the air and leaves your mark on the Earth.

This year, plant Trees for America. For your free brochure, write: Trees for America, The National Arbor Day Foundation, Nebraska City, NE 68410.



The National  
Arbor Day Foundation<sup>SM</sup>  
www.arborday.org

## CABLE TV CONVERTERS

Equipment & Accessories  
Wholesalers Welcome

Call C&D ELECTRONICS

1-800-310-1153 M-F 10a-6p

## Pete's Wholesale

Wholesale distributors of cubes and one  
piece units works on all major systems  
call us last for the best price!

800-763-7277

# Arbor Day... A Great Idea GROWS

## Medical miracles start with research

American Heart  
Association<sup>SM</sup>  
Fighting Heart Disease  
and Stroke





One tree can make 3,000,000 matches.



One match can burn 3,000,000 trees.



A Public Service of The Magazine of The Advertising Council

## Don't rent own! Cable TV Descramblers We'll beat Any Price!

- Same Day Shipping!
- 30 Day Money Back Guarantee!
- Credit Cards/C.O.D.

Have make and model number of equipment used in your area

**REPLACEMENTS FOR MOST SYSTEMS**

CALL TOLL FREE

### CABLE DISCOUNT

## 1-800-684-9135

NO NEW JERSEY SALES!

Anyone implying theft of service will be denied assistance.

Since 1965, we've worked to make sure all children have the opportunity to learn valuable lessons during the years when it's easiest for them to learn.

To find out how you can help, call your local Head Start.



Nurture the future  
BE A HEAD START VOLUNTEER



# Zenith ST 1000's \$25.00

## Zenith Jerrold Tocom Pioneer Panasonic & Scientific Atlanta


All converters unmodified

## KABLEWORKS 1-800-899-5000

[www.kableworks.com](http://www.kableworks.com)

# New and Pre-Owned Test Equipment

## Goldstar

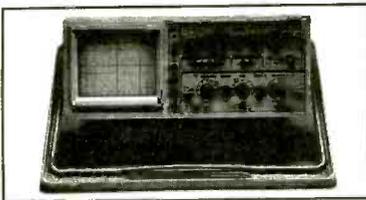

Model OS-9100P → **\$899.00**

### Full 100 MHz Bandwidth!

- Dual-Channel, High Sensitivity
- TV Synchronization Trigger
- Calibrated Delayed Sweep
- Includes Two Probes, 2 Year Warranty

**FREE SHIPPING!**  
ON GOLDSTAR EQUIPMENT  
ANYWHERE IN THE U.S.  
Excluding AK & HI



**BK PRECISION**  
MAXTEC INTERNATIONAL CORP.

Model 4040 \$499.00

### 20 MHz Sweep/Function Generator

- 0.2 Hz to 20 MHz, 5 digit LED Display
- AM & FM Internal or External Modulation
- Sine, Square, Triangle, TTL, CMOS Outputs
- Burst Operation
- External 30 MHz Frequency Counter

**NEW!**

See us on the Web!  
[www.fotronic.com](http://www.fotronic.com)

1-800-996-3837



## TOLL FREE 1-800-99-METER

## Pre-Owned Oscilloscope Specials

B + K Precision 1476 10 MHz \$229.00  
*Great Starter Scope!*

Tektronix 465	100 MHz	\$599.00
Tektronix 465B	100 MHz	\$699.00
Tektronix 475	200 MHz	\$799.00
Tektronix 475A	250 MHz	\$899.00

- The Industry Standard of Oscilloscopes
- Dual Channel, Calibrated Delayed Sweep
- Professionally Refurbished
- Aligned & Calibrated to Original Specifications
- 6 Month Warranty - The Longest Available!

### LOWEST PRICES EVER!

**NEW FLUKE MULTIMETERS & TEKTRONIX OSCILLOSCOPES**

The Industry Standard in Multimeters

Fluke Model 87 ...\$285.00

**TEKTRONIX TDS SERIES  
ON SALE!**

## Test Equipment Depot

A FOTRONIC CORPORATION COMPANY

P.O. BOX 708 Medford, MA 02155

(617) 665-1400 • FAX (617) 665-0780

email: [afoti@fotronic.com](mailto:afoti@fotronic.com)

## CABLE T.V. EQUIPMENT

Friendly, Knowledgeable Service



**ORDERS CALL:**  
1-800-361-4586



- All Equipment New
- Convertors & Descramblers
- 30 Day Money Back Guarantee
- 6 Month Warranty
- Visa, MC, C.O.D. Welcome

**KDE ELECTRONICS, INC.**

P.O. Box 1494  
Addison, IL 60101

Info. 630-889-0281 HRS: Mon-Fri, 9-6 CST  
Fax 630-889-0283 Sat, 9-3 CST

## TRIDENT



**\$699<sup>00</sup>**  
SV150

**1000KHz to 1.00GHz  
Spectrum Analyzer System  
Up to 500MHz Span. Two bands.**

All the advantages of a Spectrum Analyzer at a very affordable price. Great for interference and signal hunting. RS232 connect for logging signals to disk. Real time display sweep outputs on any X,Y scope. Variable span and sweep rate. Marker function and selectable bandwidth. Demods in AM/NFM/WFM plus BFO for CW/SSB modes. For instant information use our fax back service at 317 849 8683, #405. Or, email Scanns@www.acecomms.com . <http://www.acecomms.com/Scanns>.



**Order Line: 1 888 445 7717**

10707 E. 106th, Fishers, IN 46038 International: 317 842 7115  
Fax 317 849 8794 Email: Scanns@www.acecomms.com

CIRCLE 25 ON FREE INFORMATION CARD

# RS-232 Networkable Devices



DISPLAY INCLUDED

NEW: RS-232 programmable 240x64 Graphic Display Module. Upload your BMP/GIF Image Files at 9600/19200 Baud. Complete Support for 30x8 and 40x8 Text. Documentation and QBasic Software Gets You Running FAST!!! Counts as 2 Devices on the NCD RS-232 Network, Combine up to 8 GDSPs on a Single Serial Line. GDSP Intro: \$279. Fully equipped: \$349.

Includes Drivers in QBasic, Mac & Amiga Software Also Supported.


National Control Devices  
Contact Ryan Sheldon  
Phone: (404) 244-2432  
FAX: (417) 646-8302

Include \$5 Shipping  
Visa/MC Accepted.


NCD, Box 384, Osceola, MO 64776



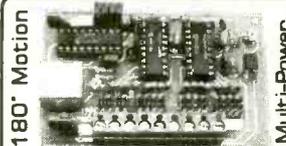
High-Power DC Motor Controller; 9-12 Volt Operation for Motors Up to 4 Amps. Forward/Reverse 64 Speeds. With Infrared Receiver. Hexfet H-Bridge Driver stage.  
NCD-M1 Kit \$129 Asm \$159



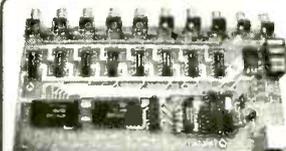8/16 Hobby Servo Controller. Futaba-J Compatible, Infrared Receiver Included with SV16 upgrade. Perfect in all animatronic applications.  
SV8 Kit \$79 Asm \$99  
SV16 Upgd Kit \$39 Asm \$59



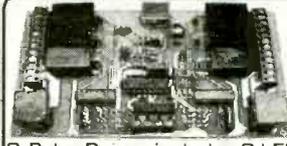Audio/Video Switcher: 8 Inputs, 2 Outputs, Infrared Controllable, Routes Any Input to Any Output. 12-18 volt DC operation. For Low-Power (Line-Level) Signal Switching.  
AVS8 Kit \$129 Asm \$179



8-Relay Driver; includes 8 LED Status Lights. 12V Operation. Includes Infrared Receiver for Remote Operation. With Omron Mechanical Relays. Call for info on our 4-Relay Model.  
R85 (5A) Kit \$109 Asm \$139  
R810 (10A) Kit \$129 Asm \$159




LCD Display Driver; for Displays up to 40x2 (not inc). Two AUX outputs for Relay & Light. Connect up to 16 Displays per RS-232 port.  
NCD-LCD Kit \$34 Asm \$44

Infrared Transceiver for Remote RS-232 Communication with 16 IR Controllable Devices. IRTA Kit \$39 Asm \$49  
RSB Serial Booster Gives your RS-232 Port the Power It Needs to Drive 16 NCD Devices. RSB Kit \$29 Asm \$34

On-Line Catalog: <http://members.aol.com/ncdcat/index.html> E-mail: [ncdryan@aol.com](mailto:ncdryan@aol.com)

# Electronic Training Videos

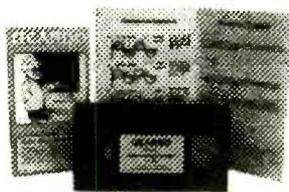

Learn electronics quickly and easily with UCANDO's computer-animated training videos. Students can learn at their own pace and professionals will find the UCANDO videos to be a valuable source of reference material. If these videos aren't the best learning tools you've ever seen, return them within 30 days for a complete refund. These videos are being used by Tech-Schools, CET's, Military Branches, Ham Operators, Industries, and more, across the United States and around the world. Order today and see how UCANDO is ...

*"Changing The Way The World Learns Electronics."*

VCR Maintenance & Repair ... \$29.95      All others ... \$44.95 each  
 • Intro to VCR Repair • Direct Current • Alternating Current • Semiconductors • Power Supplies • Amplifiers • Oscillators • Digital 1 • Digital 2 • Digital 3 • Digital 4 • Digital 5 • Digital 6 • AM Radio • FM Radio Part 1 • FM Radio Part 2 • TV Part 1 "Intro to TV" • TV Part 2 "The Front End" • TV Part 3 "Audio" • Fiber Optics • Laser Technology •

SAVE!!! 6 videos for only \$240 or 12 videos for only \$450



**1-800-678-6113**

or mail check or money order to:

UCANDO Videos

P.O. Box 928

Greenville, OH 45331



**FREE Shipping ... FREE Catalog**

CIRCLE 136 ON FREE INFORMATION CARD

# Cable TV

Descramblers • Converters

**FREE**  
30 Day Trial



**"Full Channel Viewing"**

**Movies \* Fights \* Events**

**Call Now - Save \$\$\$**

**One Year Warranty**

Credit  
Cards

**800-299-7985**

C.O.D.

**QUALITY ELECTRONICS**

# LEADER

For Professionals Who Know The Difference

- Oscilloscopes
- Video Sync/Test Generators
- Waveform Monitors/Vectorscopes
- EFP/ENG Instruments
- RF Signal Level Meters
- Audio Generators & Meters
- Frequency Counters
- Meters & Bridges
- Power Supplies
- Function Generators
- RF Generators

**PRINT™**  
Products International




Test Instruments, Equipment, Tools & Supplies For Electronic Production, Maintenance & Service  
 8931 Brookville Road, Silver Spring, MD, 20910 \* 800-638-2020 \* Fax 800-545-0058

CIRCLE 47 ON FREE INFORMATION CARD



Call, fax or email for your free test and measurement instrument catalog today!  
 800-638-2020 \* Fax 800-545-0058  
 Email: [SMPRODINTL@aol.com](mailto:SMPRODINTL@aol.com)

# Fix It Yourself!

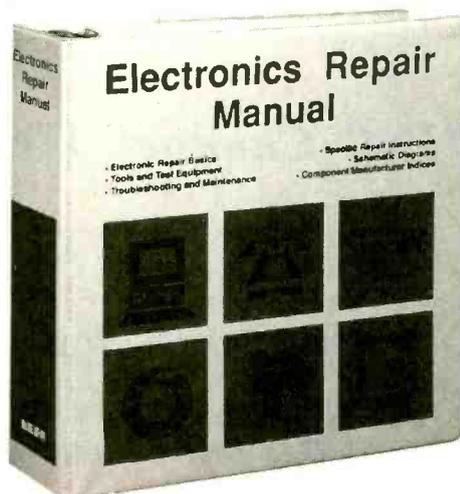

- Hands-on, detailed, troubleshooting instructions
- "How to" primer for test equipment: oscilloscopes, frequency counters, video analyzers, etc.
- Schematic diagrams
- Trouble analysis flowcharts
- Preventive maintenance techniques
- Safety precaution checklists
- Comprehensive replacement parts list
- Directory of manufacturers

**It's easy, fast, and rewarding to repair it yourself with the Electronics Repair Manual!**

### Leading Manufacturers Represented...

- Emerson • Nintendo • RCA • Technics
- Hitachi • Panasonic • Sanyo • Toshiba
- IBM • Pioneer • Sharp • Zenith
- NEC • Quasar • Sony and others!

### ✓ Dozens of Fix-It-Yourself Projects for...

- |   |  |
|---|--|
| <input type="checkbox"/> CD Players         | <input type="checkbox"/> Amplifiers      |
| <input type="checkbox"/> VCRs               | <input type="checkbox"/> Car Radios      |
| <input type="checkbox"/> Televisions        | <input type="checkbox"/> Home Appliances |
| <input type="checkbox"/> Camcorders         | <input type="checkbox"/> AM/FM Tuners    |
| <input type="checkbox"/> Computer Equipment | <input type="checkbox"/> Thermostats     |
| <input type="checkbox"/> Fax Machines       | <b>...and more!</b>                      |
| <input type="checkbox"/> Telephones         |  |

**30-Day Free Trial!**



### Keep Your Skills Up-to-Date!

*The Electronics Repair Manual and the Modern Manual Electronics Manual will be a valuable reference for years to come. Supplements, each containing over 125 pages, add new repair projects, valuable insights into new technologies, diagnostic and repair techniques, electronics projects, and more schematic diagrams into your manual. Just \$35 each for Electronics Repair and \$49.50 each for Modern Electronics plus shipping and handling. Supplements are sent 4-5 times a year and are fully guaranteed. Return any supplements you don't want within 30-days and owe nothing. Cancel anytime.*



# MANUFACTURER

## AI-6600 PHONE TAP DETECTOR

DETECTS:

- Radio Frequency Taps
- Series and Parallel Taps
- Line Impedance Taps
- Extension Phone Listeners



**\$149<sup>95</sup>**

## AI-2100 VIBRATING TRANSMITTER DETECTOR

DETECTS:

- Body Wires
- FM Wireless Mics
- AM Transmitters
- UHF Transmitters



**\$189<sup>95</sup>**

## AI-5500 COMPLETE SAFETY SYSTEM

DETECTS:

- All Phone Taps and Extension Phone Listeners,
- All Body Wires, Wireless Mics, AM/FM and UHF Transmitters

DEFEATS:

- All Body Wires, Transmitters and Distance Microphones with its built-in white noise generator



**\$379<sup>95</sup>**



## TRVD-900 TRANSMITTER / TAPE RECORDER & VIDEO DETECTION SYSTEM

DETECTS:

- Body Wires
- FM Wireless Mics • AM Transmitters • UHF Transmitters
- Tape Recorders • Video Equipment

Alerts User By Vibrating and/or Illuminated LEDs

**\$495<sup>00</sup>**

## WSS-100 WIRELESS SURVEILLANCE SYSTEM SEES & HEARS EVERYTHING!

FEATURES:

- 2.4 GHz Video / Audio Transmitter
- 4 Channel Receiver • 300' Transmission Range
- Black & White CCD w/ Auto-Iris Lens • 410(H) TV Line Resolution
- FCC Approved Frequency



**\$649<sup>95</sup>**

Items May Be Purchased by Credit Card, Certified Check, Money Order or C.O.D.

Send \$6.00  
for 32-Page  
Catalog  
(FREE w/ Purchase)

## AMERICAN INNOVATIONS, INC.

119 ROCKLAND CENTER ~ SUITE 315 • MANUET, NY 10954

VOICE: (914) 735-6127 • FAX: (914) 735-3560

HTTP://WWW.SPYSITE.COM • E-MAIL: AMERICAN@SPYSITE.COM

Quantity  
Discounts  
Available

Whaddya Say To  
A Guy Who's Had  
The Same Job  
For 50 Years,  
Has Never Called  
In Sick Or  
Showed Up Late,  
Never Taken A  
Vacation Or A  
Holiday, Never  
Asked For A  
Raise Or Griped  
About His Bonus  
And, Believe It Or  
Not, Has No  
Plans For  
Retirement?



Thanks.

Remember - only you can prevent forest fires.

# ROBOTIC MACHINING

ROUTE, MILL, DRILL, CARVE, ENGRAVE, PAINT . . . .  
IN WOOD, PLASTIC, VINYL, PC BOARD, & LIGHT METALS!

- 4 & 5 MOTOR GANTRY MILL CONFIGURATIONS
- PC COMPUTER CONTROLLED CNC/DNC
- IMPORT/ EXPORT FILES TO OTHER CADS
- AUTO-BACKLASH COMPENSATION
- PRE-MACHINED HEAVY CASTINGS
- SIMULTANEOUS 4 AXIS MOTION
- FREE 3D CAD/CAM SOFTWARE
- AVAILABLE IN KITS OR ASSEMBLED
- EXPEDITE SERVICE ALSO AVAILABLE
- OPTIONAL ALUMINUM WAY COVERS
- .0005" RESOLUTION / AMERICAN MADE



STARTING AT  
\$695.00

3 & 4 AXIS UNITS  
FROM 12" X 12" TO  
66" X 66" MACH. AREA

U.S. CYBERLAB, INC. 14786 SLATE GAP RD., WEST FORK, AR 72774

CALL NOW FOR INSTANT SPECS 501-839-8293 24 HR. FAX-BACK

# EPROM+ PROGRAMMING SYSTEM USES PARALLEL PORT

**EPROMS** (24,28,32 & 40 PIN)\*+27C AND 25XX  
1702\*, 2708, TMS2716\*, 32,32A, 64, 64A, 128, 128A  
256, 512, 513, 011, 010, 101, 1001, 1000, 1024, 210, 020  
2001, 220, 2048, 4001/2, 040, 080, 240, 4096, 68764/66  
**FLASH EPROMS** 28F256, 28F512, 28F010  
28F020, 29C257, 29C010, 29C040, 29F010, 29F040  
**EEPROMS & NVRAMS** (18,24 & 28 PIN+CXX)  
2210, 2212, 2804, 2816, 2816A, 2817, 2864, 2865-  
28256, 28C010, DS1220, DS1225, DS1230  
**SERIAL EEPROMS\*** (8 & 14 PIN PLUS CXX)  
BR1400, MS8657, 2401, 02, 04, 08, 16, 32, 65, 2444  
59C11, 80011A, 9306, 46, 56, 66, 8572, 82, 92, 168, 9XX  
**BIPOLAR PROMS\*** (16 THROUGH 24 PINS)  
74SXXX AND 82SXXX FAMILY  
**MICROCONTROLLERS\*** 8741, 42, 48, 49, 8751  
C51, 52, C52, 87C5XXX, 87C75X, 89C5X, 68705  
68HC705, 68HC711E9, PIC16CXX, TMS7742  
\*ADAPTER REQUIRED - DIAGRAMS INCLUDED

**SOFTWARE** - READ, VERIFY, PROGRAM, COPY  
DISK FILE LOAD/SAVE, CHECKSUM, FULL  
SCREEN BUFFER EDITOR W/20 COMMANDS  
**READS** HEX, S-RECORD AND BINARY FILES  
**FAST-DEVICES** PROGRAM IN UNDER 20 SEC  
**RUGGED** (9"X6"X3") ENCLOSURE W/HANDLE  
**MADE IN USA** - 1 YEAR WARRANTY

ANDROMEDA RESEARCH, P.O. BOX 222, MILFORD, OH 45150  
(513) 831-9708 FAX (513) 831-7562



**SYSTEM INCLUDES:**  
PROGRAMMING UNIT  
PRINTER PORT CABLE  
POWER PACK, MANUAL  
AND SOFTWARE.

## \$289

ADD \$5.00 SHIPPING  
\$5.00 C.O.D.  
VISA/MASTERCARD

# HOME AUTOMATION

## World's Largest Selection!

### Widest Selection of X-10 Devices Available

Hundreds of hard-to-find automation, X-10 and wireless control products. Computer interfaces, software, development tools, lighting control, telephone systems, security systems, surveillance cameras, infra-red audio/video control, HVAC, pet care automation, wiring supplies, books and videos and much more!



Packed with Pictures  
& Diagrams

**HOME AUTOMATION SYSTEMS, INC.**

Questions: 714-708-0610 Fax: 714-708-0614  
e-mail: catalog@smarthome.com  
http://www.smarthome.com/smarthome

**Lowest Prices  
Guaranteed!**

24 Hours **Call 800-SMART-HOME** 800-762-7846

# Weeder Technologies

Add \$4  
Ship/Hand  
US & Canada

**FREE  
CATALOG!**



# Pro-Kit™

PO Box 421, Batavia, OH 45103

weedtech@iglou.com

513-752-0279

### Home Automation

Connects between a TW523 and an RS-232 serial port. Use your PC/Mac to receive and transmit all X-10 commands. Create your own program to control your home automation system, turning on/off any device plugged into an electrical outlet with response to time/date, other X-10 transmissions or any other computer input stimuli. **\$38.50**

### Caller ID / RS-232

Connects between a telephone wall jack and an RS-232 serial port. Decodes the caller ID data sent over the phone line and sends it to your PC/Mac. In a pre-formatted ASCII character string. Create your own program to log the name, number, date, and time of all incoming calls. Block out unwanted callers to your BBS/modem. **\$34.50**

### Telephone Call Restrictor

Connects to telephone wall jack. Disables all phones on the line if attempting to either: dial a number that has been stored in memory 'Block' mode or, dial a number that has not been stored in memory 'Allow' mode. Use touch-tone phone to enter telephone numbers into memory, and choose mode. Program from any phone on the line using your password. **\$35.00**

### 50 MHz Frequency Counter

Reads frequency from 1Hz to 50MHz and displays up to 7 digits on a 16x1 character LCD display. Auto-range feature provides floating decimal point and automatic placement of suffix (Hz, KHz, or MHz). Microcontroller based provides for very small parts count, only 2" x 3" big. **\$48.50**

### Telephone Scrambler

Scrambles your voice before sending it over the telephone line. Prevent eavesdropping from an extension or tap. Connects between your telephone and wall jack. No modifications are required to your telephone. Full duplex operation. **\$43.00**

### IR Remote Control Receiver


Learns and records the data patterns emitted by standard infrared remote controls used by TVs, VCRs, Stereos, etc. Lets you control all your electronic projects with your TV remote. Seven individual I/O pins can be assigned to any button on your remote, and can be configured for either 'toggle' or 'momentary' action. **\$32.00**

### RS-232 Digital I/O

Give your home-brewed PC/Mac programs a link to the outside world! 12 I/O pins can be configured individually for input or output. Turn on/off relays, triacs, etc. Respond to button presses, switch changes, 4x4 matrix decoding with auto-debounce. Stack up to 16 units on the same serial port for a total of 192 I/O points. **\$32.00**
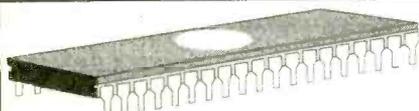
### DTMF Decoder/Logger

Keep track of all numbers dialed or entered from any phone on your line. Connects to your telephone wall jack. Decodes all 18 touch-tones and displays them on an LCD display. Holds the last 240 digits in a non-volatile memory. Scroll through and view all telephone numbers dialed, credit card numbers entered, etc. **\$54.50**



## CABLE CONVERTER DIAGNOSTIC TEST CHIP

**LOAD FULL ACTIVATION OF CABLE CONVERTER**

**WE STOCK A COMPLETE LINE OF CHIPS, TOOLS, WIRELESS QUICK INSTALL TEST BOARDS AND DIAGNOSTIC CUBES FOR ALL CONVERTERS!**

**\*\*\*ANYONE IMPLYING ILLEGAL USE WILL BE DENIED SALE. WE SELL PRODUCTS ONLY TO TECHNICIANS OR CABLE REPAIR FACILITIES!\*\*\***

**#1 IN CUSTOMER SERVICE & TECH. SUPPORT!**

**\*ALL ORDERS SHIP WITHIN 24HRS, UPS/ FED-EX.**

**\*PRIORITY NEXT DAY SHIPPING AVAILABLE!**

**\*SALE= BUY 5 TEST BOARDS AND GET 1 FREE.**

**\*MON-FRI - 8AM-7PM - SAT 10AM-2PM EST.**

**\*WEB PAGE HTTP://WWW.800-GOCABLE.COM**

**VISA MASTERCARD VISUAL**

**COMMUNICATIONS INC.**

**ORDERS/CATALOG 1-800-GO-CABLE**

**TECHNICAL SERVICE DEPT. 717-620-4363 EST. 1976**

### Debco Is a Kit Builders Paradise

Electronic Kits - Plans - Parts - Computers - Amateur Radio



Call Debco today for  
your **FREE** copy of

The Electronic Experimenter's Journal

## 1 800 423 - 4499

Debco Electronics 4025 Edwards Rd. Cincinnati, OH 45209

Only You Can Prevent Forest Fires.



## BE AN ELECTRICIAN!

Home study. Maintain and install electrical systems, wiring, utilities, phones, and more.  
**FREE LITERATURE: 800-223-4542**

Name \_\_\_\_\_ Age \_\_\_\_\_  
Address \_\_\_\_\_ Phone \_\_\_\_\_  
City/State \_\_\_\_\_ Zip \_\_\_\_\_  
The Electrician School, PCDI, DEPT EE341  
6065 Roswell Road, Atlanta, Georgia 30328



# CABLE TV CONVERTERS AND DESCRAMBLERS

**WE CARRY A FULL LINE OF  
CONVERTERS AND DESCRAMBLERS  
COMPATIBLE WITH MOST  
MAJOR BRANDS INCLUDING:**

- Scientific Atlanta™
- Jerrold™
- Tocom™
- Zenith™
- Pioneer™

**30 DAY MONEY BACK GUARANTEE  
BEST PRICES FREE CATALOG**

## ALLSTAR ELECTRONICS 800-782-7214

**HOURS: 9-6 M-F 10-3 Sat EST**

It is not the intent of Allstar Electronics to defraud any pay TV operator. Anyone implying theft of service will be denied assistance. All brand names are registered trademarks of their respective owners & are used for reference only. 110-54 Queens Blvd., #465, Forest Hills, NY 11375. NO NYS SALES.

NEW DX SERIES DMMs

**3 YEAR WARRANTY**  
COVERS FULL PERFORMANCE



Bel MERIT DX Series DMMs have best values for performance, features and dependability with 3 year warranty.

Each DX model has standard DMM measurements with a set of additional capabilities; diode, continuity, TRhFE, capacitance, inductance, frequency, logic and temperature.

Additional features include auto power-off, data hold, annunciator, and input warning beeper & peak hold (DX451/DX460L only)

Deluxe holster, safety test leads and thermocouple probe (DX360T) supplied as standard accessories.

MODEL	DX350	DX360T	DX400	DX405	DX451	DX460L
AC/DC Voltage (750V/1000V)	*	*	*	*	*	*
AC/DC Current (10A)	20µA	*	*	*	*	*
Resistance (20MΩ)	20Ω	2000M	*	*	2000M	2000M
Continuity Beeper/Diode	*	*	*	*	*	*
Temperature w/Probe, Type K	*	*	*	*	*	*
TRhFE	*	*	*	*	*	*
Capacitance (20µF)	*	*	*	*	*	2000µ
Frequency (20MHz)	*	*	*	*	*	*
Logic (TTL & CMOS)	*	*	*	*	*	*
Inductance (20H)	*	*	*	*	*	*
Auto Power-Off	*	*	*	*	*	*
Input Warning Beeper	*	*	*	*	*	*
Data Hold	*	*	*	*	*	*
Peak Hold	*	*	*	*	*	*
Protective Holster	*	*	*	*	*	*
Suggested Resale Price	49.95	64.95	64.95	69.95	89.95	109.95

**• Lots more High Standard Test Instruments available**

All in One Instrument, Oscilloscope, Power Supply, Function Generator, Frequency Counter, Multimeter, Capacitance, Engine Analyzer, Clamp-On, Electrical Tester and More.

**• See your local distributors or Call for Catalog**

**Bel MERIT 1-800-532-3221**  
SOLUTIONS FOR THE TEST INSTRUMENT (714) 586-2310 • FAX (714) 586-3399  
P.O. Box 744, Lake Forest, CA 92630

**THE 3rd HAND**

EVER NEED A 3rd HAND WHILE TRYING TO SOLDER 2 PIECES TOGETHER? SO YOU LAY THE SOLDERING IRON ON THE TABLE AND PUT A WEIGHT ON IT. NOT ONLY DOESN'T IT WORK BUT ITS DANGEROUS. TRY OUR SOLUTION. A WELL BUILT BASE THAT HOLDS THE IRON IN PLACE TO FREE YOUR HANDS. FULLY ADJUSTABLE. WILL FIT MOST IRONS.



KIT INCLUDES BASE AND SOLDERING IRON & COMPLETE INSTRUCTIONS  
TO ORDER OR MORE INFORMATION MAIL TO R & S

2788 C.R. 135  
DOLA OHIO, 45835  
TEL : 419/759-2558 FAX : 419/365-5112

MASTERCARD - VISA

**CABLE TV**

**CABLE descrambling, new secret manual.** Build your own descramblers for cable and subscription TV. Instructions, schematics for SSAVI, gated sync, sinewave, some free methods (HBO, Cinemax, Showtime, UHF, Adult) \$12.95, \$2.00 postage. **CABLETRONICS**, Box 30502PE, Bethesda, MD 20824.

**CABLE TV equipment & accessories.** Wholesalers welcome! 30 day moneyback guarantee! Free catalog! **PROFORMANCE ELECTRONICS, INC.**, 1 (800) 815-1512.

**CABLE descrambler!** Anyone can build in seven steps with Radio Shack parts. Plans/kit from \$5.00. plus free bonus. 1 (800) 818-9103.

**DESCRAMBLE cable using simple circuit.** E-Z to follow instructions. \$10.00. Complete kit with free "Bullet Stopper". \$20.00. 1 (800) 522-8053.

**CABLE "Bullet Terminator and I.D. Blocker".** Electronically shields yourself and your box. Free Hackers Guide included. Lifetime guarantee. Wholesale prices. 1 (800) 820-9024.

**BIG Sale!! Notch filters \$18.00. External Activators \$125.00. Descramblers from \$99.00.** Test chips from \$5.00. **Bullet/I.D. \$10.00.** Name brand cable descramblers from \$135.00. Let us beat your best price. 1 (800) 449-9189 Anytime.

**CABLE TV, descramblers, converters.** Quantity discounts. 30 day free trial. Competitive prices. Call now! 1 (800) 322-0921 **REGAL SALES, INC.**

**CABLE TV descramblers.** One piece units. Pioneer 6310's, Scientific Atlanta 8580's, DPV7's and others. Lowest prices. Money back guarantee. Houston, TX (713) 691-4610.

**CABLE - test chips; Jerrold; Pioneer; Tocom; Scientific Atlanta, Zenith, Jerrold cubes; Pioneer programmable cubes; HUDSON, 1 (800) 863-3237.**

**DESCRAMBLE cable with simple circuit added to Radio Shack RF modulator and using VCR as tuner, instructions \$10.00. TELCOM, Box 832P05, Brusly, LA 70719.**

**ZENITH compatible test chips-activates full test mode.** All except PZ1. \$24.95 **REALVIEW (888) 732-5843 Visa/MC/Cod.**

**"UNIVERSAL" descrambler - Works with virtually any system.** Fully assembled. \$129.95 + \$5.00 S&H. **"Bullet" Buster** - Protect your cable box against the infamous "bullet", ID and "cuckoo" signals. \$19.95 + \$3.00 S&H. **Cable-Safe.** Guarantee cable privacy. The one-way valve for your cable TV signal. \$29.95 + \$3.00 S&H. **"Cable Unscrambled"** - Everything you want to know about cable, but are afraid to ask. \$10.00. **"Descrambler Schematics Revealed"** - A powerful guide to descrambling schemes. \$10.00. **"Baseband Video Explained"** - Discover what a baseband signal is and how it's constructed. \$10.00. Special offer - Get all three booklets for only \$25.00! **VISA/MC/AMEX. ELECTROMAN, Box 24474, New Orleans, LA 70184. (504) 482-3017. Free Catalog.**

**FULL line of cable descramblers and accessories for all types of systems.** Test kits. Auto multimode. Etc... Everything you need. Call (808) 735-9988. Best price guaranteed.

**CABLE Descramblers - Why rent! Own your cable TV equipment.** Access all premium and basic channels. All makes and models available. Please have model number of cable box when calling. **CABLE CONNECTION** at 1-888-83-CABLE.

**CABLE TV notch filters.** Request our free brochure today! Voicemail: 1 (800) 433-6319. Address: **STAR CIRCUITS, PO Box 94917, Las Vegas, NV 89193.**

**SECURITY**

**HIDDEN** miniature camera inside wall clock, or smoke detector with video transmitter. For a full catalog send \$5.00. **THE SPY MASTERS**, Suite 109, 4949 Dempster, Skokie, IL, 60077. Web site <http://members.aol.com/thspymastr/catalog>

## COMPONENTS

**STEPPER IC:** EDE1200 is perfect for robotics, etc. **E-LAB DIGITAL ENGINEERING, INC.** (712) 944-5344. [www.netins.net/showcase/elab](http://www.netins.net/showcase/elab)

## TEST EQUIPMENT

**TEST Equipment for sale:** Quality reconditioned Tektronik, HP, Boonton, Fluke, Wavetek etc. Contact: **AST GLOBAL MARKETING**, 11365 Airport Rd., Meadville, PA 16335. Ph. (814) 336-2138. Fax (814) 337-7920. E-mail [astmrktg@wrench.toolcity.net](mailto:astmrktg@wrench.toolcity.net)

**WANTED:** Used test equipment. **AST GLOBAL MARKETING**. Ph. (814) 336-2138/Fax (814) 337-7920. E-mail [astmrktg@wrench.toolcity.net](mailto:astmrktg@wrench.toolcity.net)

## BUSINESS OPPORTUNITIES

**START** your own technical venture! Don Lancaster's newly updated **Incredible Secret Money Machine II** tells how. We now have autographed copies of the Guru's underground classic for \$18.50. **SYNERGETICS PRESS**, Box 809-C, Thatcher, AZ 85552. (520) 428-4073. Visa/MC.

**SATELLITE Television pays!** 18" minidish sales force needed. **STAR VISION DIRECT:** (800) 899-9707, 8am-10pm Pacific.

## EDUCATION

**FCC/CET software.** General Radiotelephone, CET preparation. Five 3.5 inch diskettes. Q/A format: interactive, comprehensive. EGA/VGA. Complete program, \$35.00. **TUTOR-TECH**, 170 Locksunart Way, #2, Sunnyvale, CA 94087. (408) 481-9543.

**RECEIVE** your certified electronics technician license guaranteed or money back. Manual, simulated exams and tutoring. \$24.95 covers all costs. Check or money order to: **MASS INSTITUTE OF ELECTRONICS**, P.O. Box 1213, Northampton, MA 01060.

## SATELLITE EQUIPMENT

**VIDEOCYpher II** descrambling manual. Schematics, video and audio. Explains **DES, EPROM, CloneMaster, Pay-per-view (HBO, Cinemax, Showtime, Adult, etc.)** \$16.95, \$2.00 postage. Schematics for Videocypher Plus, \$20.00. Schematics for Videocypher 032, \$15.00. Collection of Software to copy and alter EPROM codes, \$25.00. **VCII Plus EPROM**, binary and source code, \$30.00. **CABLETRONICS**, Box 30502FE, Bethesda, MD 20824.

**IDSS Hacking:** How to construct and program smart cards, w/pic16C84, software. Complete DSS system schematics. \$16.95. **CABLETRONICS**, Box 30502R, Bethesda, MD 20824.

**OBTAINING Sound** for your **VCII** and **VCII Plus** is easy. No codes needed. Also **DSS Test Card** information. **Details: 1 (800) 211-5635.**

**IMPROVE** your satellite picture. Focus Maximizer is a diagnostic tool that optimizes feedhorn spacings. \$26.50. Free brochure. **WATERSHED ELECTRONIC DEVELOPMENT (800) 756-7854.**

**MINIDISH satellite systems**, surround sound, big TVs, total home entertainment systems. Discount prices. Free information. **STAR VISION DIRECT:** (800) 899-9707, 8am-10pm Pacific.

**ECHO Star Satellite Dish Networks** for sale, so call about these state of the art systems at (812) 295-4240.

**BEST pricing** on 18" satellite TV systems for home and RV. DSS, DISH Network programming, multi-room viewing options, accessories. Call **SKYVISION® 1 (800) 500-9264.** [www.skyvision.com](http://www.skyvision.com).

## MISCELLANEOUS ELECTRONICS FOR SALE

**THE Case Against Patents.** Thoroughly tested and proven alternatives that work in the real world. \$28.50. **SYNERGETICS PRESS**, Box 809-C, Thatcher, AZ 85552. (520) 428-4073. Visa/MC.

**FM Micro-Broadcasting 88-108MHz.** Assembled PLL transmitters and rf amps mono/stereo 1/2-100 watts. Photo catalog/info call (250) 642-2859. **R. SCOTT COMMUNICATIONS, LTD.** We ship world wide from Canada.

**PRESECTOR Preamp/Filter** 530-1600 khz. Improves dynamic range. Gets remote stations. \$55.00. Box 1625, Frazier Park, CA 93225.

**INTERNATIONAL clients wanted.** "Can do" engineer locates, purchases, ships U.S. technical products, systems, services worldwide. Our job: Get the facts; get you what you want! Professional, confidential, discreet. Fax today: (806) 792-0207. Or, write **TESCO TECH** Box 53743, Lubbock, Texas, 79453, USA.

## PLANS-KITS-SCHEMATICS

**TRANSISTOR Data Tables** — Given are the basic electronic parameters for the worlds popular transistors in one volume. A must for servicemen, hobbyists and engineers. Order "Transistor Data Tables" (BP401) for only \$9.95 (price includes shipping) from **ELECTRONIC TECHNOLOGY TODAY, INC.**, PO Box 240, Massapequa Park, NY 11762-0240. USA and Canada only. US funds.

**CRYSTAL Set Handbook** — Visit antiquity by building the radios your grandfather built. Assemble a "Quaker Oats" rig, wind coils that work and make it look like the 1920's! Only \$10.95 plus \$4.00 for shipping and handling. **CLAGGK INC.**, PO Box 4099, Farmingdale, NY 11735. US funds only! USA and Canada — no foreign orders.

**HEATH COMPANY** is selling photocopies of most Heathkit manuals. Only authorized source for copyright manuals. Phone: (616) 925-5899, 8-4 ET.

**ELECTRONIC Project Kits.** [www.qkits.com](http://www.qkits.com). 1 (888) GO-4-KITS, 292 Queen St., Kingston, ON., K7K 1B8. **QUALITY KITS.**

**MONITORS made simple.** Learn to repair computer monitors! Case studies, illustrations, parts sources, manufacturers included! 136 pages, softcover. \$19.95 + \$2.50 shipping. Order today! Send check or money order to **PIKES PEAK PRESS**, 321 W. Henna Ave., P.O. Box 1801, Woodland Park, CO 80866. (719) 687-1499.

**TRANSFER paper** for printed circuits with laser or copier, excellent quality. 30 sheets 8.5 X10 with instructions \$24.00, send check or money order to **G. SANTA MARIA**, 1602-A Washington Ave., Suite #915, Miami Beach, FL 33139.

**ALL-in-one catalog**, 60 mouth-watering pages. CB/HAM/audio/TV/spy/broadcast/science projects, micropower broadcasting, broadcast transmitters, amplifiers, antennas, "secret books", start your own radio station and more. Send \$1.00 to **PAN-COM INTERNATIONAL**, PO Box 130-PS, Paradise, CA 95967.

**AWESOME Kits:** Voice changers, levitators, lasers, gas sensors and more! Catalog \$1.00. **LNS TECHNOLOGIES**, 20993 Foothill Blvd., Suite 307P, Hayward, CA 94541. [www.ccnnet.com/~lnstech](http://www.ccnnet.com/~lnstech)

**BIO-Stimulator** featured in PE June issue. Tones muscles, relieve aches and pains with electronic acupuncture. Updated kit with enclosure \$40.00 plus \$2.50 S&H. **RAH PROJECTS**, P.O. Box 15904, N.E., California 92659.

**FREE catalog** of fascinating electronics! 3D stereo, detectors, testers, tesla, jammers, robotics, much more! **QUANTUM RESEARCH**, 17919-77 Ave., Edmonton, Alberta T5T 2S1.

**HOME Automation Ideas.** Ideas, construction projects: speaker switch, vehicle detection, interactive control, speech recordings, more! Send \$15.00 to: **CREATIVE CONTROL**, 937 S. Leyden St., Denver, CO 80224.

## Converters & Descramblers Call 1-800-715-6789

30 Day Money Back Guarantee

FREE Catalog



Millennium  
ENTERPRISES

...It's Full of Stars

- Panasonic®
- Zenith®
- Jerrold®
- Scientific Atlanta®
- Pioneer®

ALL MAJOR CREDIT CARDS ACCEPTED

13492 Research Blvd • Suite 120-113 • Austin, TX 78750

## NEW EASY PC


BRITISH  
DESIGN  
AWARD

### SCHEMATIC and PCB C.A.D.

ONLY \$135

Includes

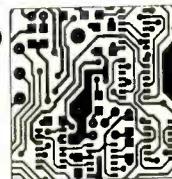- MGA, CGA, EGA & VGA compatible.
- Design large multi layer boards.
- One level pull down menu and quick keys for fast layout.
- Dot matrix, laser, plotter, Gerber & N.C. drill output.



- 6 Month Free update
- Free Demo

7840 ANGEL RIDGE ROAD  
ATHENS, OHIO 45701  
(614) 592-1810

Visa & MasterCard Accepted

## SURVEILLANCE

### The Latest High Tech Professional Electronic Devices

Our latest catalog offers a **HUGE** selection of surveillance, counter-surveillance/privacy devices: hidden video equipment, pinhole camera w/audio \$159<sup>00</sup>, electronic kits, telephone recording systems: 7-Hour \$125<sup>00</sup>—16-Hour \$199<sup>00</sup> touch tone decoders, scanners, bug/phone tap detectors, voice disguisers, telephone scramblers, locksmithing tools, and more.

Catalog \$5.00

### SPY OUTLET

P.O. Box 337, Buffalo, NY 14226  
(716) 691-3476/(716) 695-8660

## ADVERTISING INDEX

Popular Electronics does not assume any responsibility for errors that may appear in the index below.

Free Information Number	Page	Free Information Number	Page
— A&A Engineering	94	— KDE Electronics	102
25 Ace Communications	102	— Learn Inc.	13
— Aegis Research, Canada	80	— Mana	80
— AES	95	149 MCM Electronics	77
26 Alfa Electronics	81	— Mega Electronics	92
28 All Electronics	82	147 Mendelson's	96
137 Allison Technology	97	— Mental Automation	86
— Allstar Electronics	107	171 MicroCode Engineering	CV3
— AMC Sales	96	— Millennium Enterprises	109
— American Innovations	106	— Modern Electronics	94
— Andromeda Research	107	164 Mouser Electronics	20
— Basic Electrical Supply	98	— National Control Devices	102
— Bel Merit	108	— NRI Schools	17
32 C&S Sales, Inc.	84	— Ohio Automation	109
— Cable Discount	101	— Oldaker Mfg. Corp.	108
— Circuit Specialists	90	43 Optoelectronics	CV4
— Cleveland Institute of Electronics	37	— Orion Electronics	96
— Command Productions	86	146 Parts Express	87
— Comtrad Industries	3, 14	175 Pioneer Hill Software	20
— Consumertronics	76	45 Prairie Digital Inc.	97
48 Dalbani	79	46 Print	97
— DC Electronics	92	47 Print	103
173 Digi-Key Corp.	5	— Quality Electronics	103
— EDE Spy Outlet	109	— RC Distributing	94
148 Electronic Rainbow	83	— Silicon Valley Surplus	92
— Electronic Technology Today	21, 75	— Skyvision	89
— Foley-Belsaw	99	— Smithy Company	100
— Forest Electronics	80	— Tab Books	9, 55
— Fotronic Corporation	101	— T.C. Tronics	86
— General Device Instruments	95	143 Telulex	98
— George Brown College	7	— Transtronics	92
— Grantham College of Engineering	4	136 UCANDO Videos	103
— Greenleaf Electronics Inc.	98	— US Cyberlab	106
— Home Automation Systems	107	— Vision Electronics	96
— Howard W. Sams & Company	11	— Visual Communications	107
— Information Unlimited	78	— Weeder Technologies	107
13 Interactive Image Technologies	CV2	— Weka Publishing	104
— Intronics, Inc.	95	— WPT Publications	94
— Kableworks	101	134 Xandi Electronics	93

### ADVERTISING SALES OFFICES

**Gernsback Publications, Inc.**  
**500 Bi-County Blvd.**  
**Farmingdale, NY 11735-3931**  
**1-(516) 293-3000**  
**Fax 1-(516) 293-3115**

**Larry Steckler, EHF/CET**  
 President (ext. 201)  
 e-mail advertising@gernsback

**Christina Estrada**  
 Assistant to the President (ext. 209)

**For Advertising ONLY**  
**1-516-293-3000**  
**Fax 1-516-293-3115**

**Larry Steckler**  
 publisher

**Arline Fishman**  
 advertising director (ext. 206)

**Michele Torrillo**  
 advertising assistant (ext. 211)

**Adria Coren**  
 credit manager (ext. 208)

**Subscription/  
 Customer Service/  
 Order Entry**  
 1-800-827-0383  
 7:30 AM - 8:30 PM EST

### ADVERTISING SALES OFFICES EAST/SOUTHEAST

**Stanley Levitan**  
 Eastern Sales  
 1 Overlook Ave.  
 Great Neck, NY 11021-3750  
 1-516-487-9357, 1-516-293-3000  
 Fax 1-516-487-8402  
 slevitan26@aol.com


### MIDWEST/Texas/Arkansas/ Oklahoma, Colorado, Arizona

**Ralph Bergen**  
 Midwest Sales  
 One Northfield Plaza, Suite 300  
 Northfield, IL 60093-1214  
 1-847-559-0555  
 Fax 1-847-559-0562  
 bergenrj@aol.com
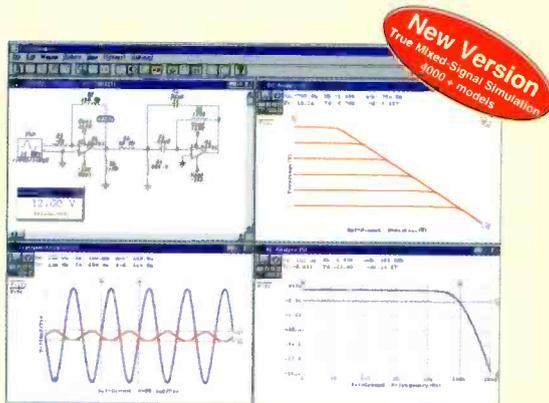
### PACIFIC COAST/Mountain States

**Anita Bartman**  
 Hutch Looney & Assoc., Inc.  
 6310 San Vicente Blvd.  
 Suite 360  
 Los Angeles, CA 90048-5426  
 1-213-931-3444 (ext. 227)  
 Fax 1-213-931-7309

The **Only** Complete Virtual Electronics Lab™




**New Version**  
True Mixed-Signal Simulation  
4000+ models

**CircuitMaker 5**

**The Fastest, Most Accurate,  
True Mixed-Signal SPICE Simulator**

CircuitMaker is a virtual electronics lab where you can quickly and easily design and verify digital, analog and true mixed-mode circuits. You layout your circuit design as a schematic, connecting an assortment of over 4000 indestructible components. Click on the simulation button and view the results as if you were looking at real laboratory instruments. It really is that easy!

New users love CircuitMaker's user friendly environment and short learning curve. Experienced users appreciate its time saving features and respect its accurate simulation and numerous in-depth analysis capabilities. No matter what level of electronics you are at, CircuitMaker, The Virtual Electronics Lab, will match your needs. We are so confident you will love its performance that we back every copy with our iron clad satisfaction guarantee!

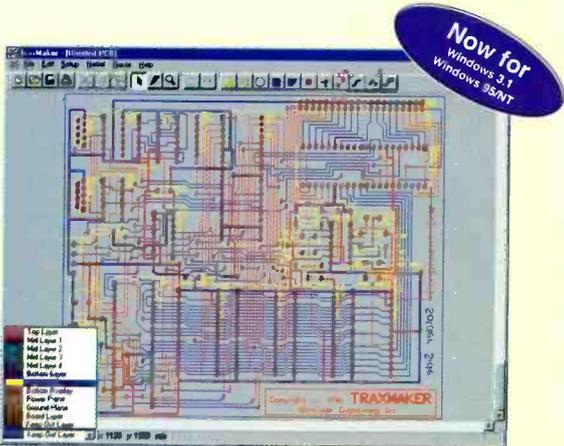


**Now for**  
Windows 3.1  
Windows 95/NT

**TraxMaker 2**

**The Most Affordable,  
Professional Quality, PCB Design Tool**

TraxMaker is a Printed Circuit Board (PCB) layout program with advanced features such as a built-in autorouter, 8 layer capability, support for surface mount devices, and full design rule checking. Most importantly, TraxMaker provides these features while remaining exceptionally easy to use.

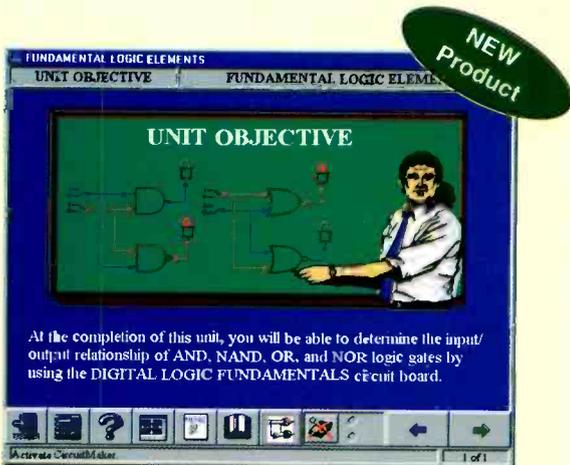TraxMaker is a truly cost effective package which is sure to handle your most demanding PCB design tasks. TraxMaker can be used as a stand-alone product or with compatible schematic capture products. When used in conjunction with CircuitMaker, TraxMaker completes a powerful start to finish circuit design system. TraxMaker provides more power than any other product in its class!



**NEW Product**

**CircuitMaker CBT**

**Electronics Training Featuring  
An Award Winning Curriculum**

MicroCode Engineering and Lab-Volt Systems present CircuitMaker CBT comprising 28 analog and digital lessons organized into four modules covering DC Concepts, AC Concepts, Analog Device Concepts and Digital Device Concepts. This is not another one of those "textbooks on a computer", rather it is an interactive presentation in an intuitive multimedia CD ROM format providing over 200 virtual labs simulated in CircuitMaker.

The award winning curriculum provides the most powerful teaching/learning tool for electronics available today. This complete electronics program includes on-line instruction and testing, workbooks, and virtual labs. Best of all, you do not have to purchase any expensive laboratory equipment to have an exciting and accurate electronics training program. CircuitMaker CBT will help the user learn and understand electronics and troubleshooting of both analog and digital circuits. We guarantee it!

**Total Customer Satisfaction**

At MicroCode Engineering we are committed to total customer satisfaction. When you purchase one of our products you have the confidence of knowing that a trained staff of professionals is available to serve you after the sale. Our free unlimited customer service is second to none! Whether you have general or technical questions they will be answered promptly by a knowledgeable representative.

**FREE Functional Demo**

Additional literature and free functional demos of our products are available on the Internet at <http://www.microcode.com> and on CompuServe (GO MICROCODE).

CircuitMaker - \$299 TraxMaker - \$299

CircuitMaker CBT - \$75 per module

**Call now to order or  
request additional information  
800-419-4242**



# Reaction Tune

Connect the SCOUT with your AOR AR2700\*

The Scout, with its revolutionary Reaction Tune feature, can tune the AOR Model AR2700 to the frequency it captures in less than one second. No more scanning through an entire band of frequencies, hoping to find that one elusive unknown signal. The Scout will lock onto and capture into memory all nearfield frequencies, up to 400, while simultaneously tuning the AR2700 to the recorded frequency. Take it along to a sporting event, amusement park, shopping mall, or downtown, and start building your own frequency database. See below for list of other compatible Scout Reaction Tune receivers.

- ☐ Automatically tunes the AR2700 to the frequency captured
  - ☐ Takes guess work out of scanning for active frequencies
  - ☐ Records and saves up to 400 frequencies in memory
  - ☐ Records up to 255 hits on each frequency in memory
  - ☐ Interface to a PC for frequency download using the optional Optolinx PC Interface
  - ☐ Distinctive beeps indicate frequency hits, pager style vibrator for discreet recording
  - ☐ Automatic EL backlight for night operation
  - ☐ 16 segment RF signal strength bargraph
  - ☐ Frequencies are automatically saved when unit is turned off
- 10MHz-1.4GHz Frequency Range

Also Reaction Tunes: AOR AR8000  
 ICOM R7000, R7100, and R9000. Radio  
 Shack Pro 2005/2006 (OS456 installed)  
 and Radio Shack Pro 2035/2042 (OS535  
 installed)

\*Modification to AR2700  
 required for Reaction tune.  
 Instructions included in  
 Scout manual.

## Free Accessories

Purchase the Scout  
 and receive **FREE**  
 DB32 Antenna  
 CC30 Carry Case  
 Spectrum CD Rom  
 \$67.00 Value



Spectrum FCC Database CD



DB32 Antenna



CC30 Carry Case



AOR AR2700 scanner not sold by Optoelectronics

**\$449**  
 Scout including 3  
 Free Accessories

**Order  
 now!**

**FACTORY DIRECT ORDER LINE 800-327-5912**

# OPTOELECTRONICS

5821 NE 14th Avenue • Ft. Lauderdale, FL • 33334

Visa • Mastercard • C.O.D. • Prices and Specifications

are subject to change without notice or obligation

TEL (954)•771•2050 FAX (954)•771•2052 Email [opto@igc.net](mailto:opto@igc.net)

Internet: [www.optoelectronics.com](http://www.optoelectronics.com)

CIRCLE 43 ON FREE INFORMATION CARD

INNOVATIVE PRODUCTS  
 FOR A  
 MODERN PLANET

