

Better Designs - Faster

With the Personal Design Solution


The Design Solution Includes: Electronics Workbench Personal Edition + EWB Layout

Electronics
Workbench
Personal Edition

Electronics
Workbench *Layout*
Personal Edition

Full-featured schematic capture and SPICE 3F circuit simulation!

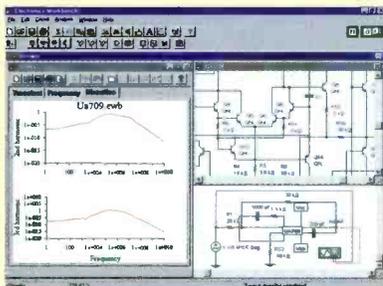
The world's best selling circuit design software. With analog, digital and mixed A/D SPICE simulation, a full suite of analyses and over 4000 devices. Imports netlists. Seamlessly integrated with EWB Layout or exports to other popular PCB programs. Still the standard for power and ease of use. Still the same effective price.



\$299
Version 5

Power-packed PCB layout with autorouting and real-time DRC!

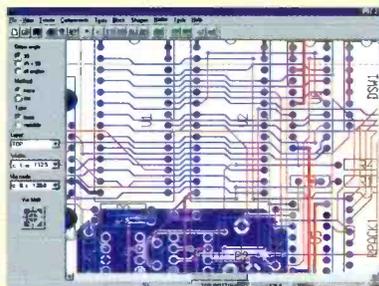EWB Layout is a powerful board layout package for producing high-quality, multi-layer printed circuit boards. Offering tight integration with our schematic capture program, you can incorporate board layout and design and quickly bring well-designed boards to production.



\$299
Version 5

HIGH-END FEATURES

TRUE MIXED ANALOG/DIGITAL	YES
FULLY INTERACTIVE SIMULATION	YES
PRO SCHEMATIC EDITOR	YES
HIERARCHICAL CIRCUITS	YES
VIRTUAL INSTRUMENTS	YES
ON-SCREEN GRAPHS	YES
ANALOG AND DIGITAL MODELS	OVER 4,000
FREE TECHNICAL SUPPORT	YES
DC OPERATING POINT	YES
AC FREQUENCY	YES
TRANSIENT	YES
FOURIER	YES
NOISE	YES
DISTORTION	YES

POWER-PACKED FEATURES

AUTOROUTING	YES
REROUTE WHILE MOVE	YES
LAYERS	32 ROUTING LAYERS
BOARD SIZE	50" X 50"
LIBRARY SHAPES	OVER 3,500
BLIND AND BURIED VIAS	YES
EXTENSIVE OUTPUT	YES
SELECTIVE NET HIGHLIGHTING	YES
USER DEFINED PADS	YES
REAL TIME DESIGN RULE CHECK	YES
DENSITY HISTOGRAMS	YES
FREE TECHNICAL SUPPORT	YES

**30-DAY MONEY-BACK
GUARANTEE**

*Join over 85,000 customers
and find out why more circuit designers
buy Electronics Workbench than
any other circuit design tool.*

**CALL FOR INFORMATION
AND PRICING ON OUR
PROFESSIONAL EDITION.**

ELECTRONICS WORKBENCH Personal Edition \$299.00

EWB LAYOUT Personal Edition \$299.00

**BUY
BOTH
AND
SAVE**

PERSONAL DESIGN SOLUTION

~~\$598.00~~
\$548.00

CALL 800-263-5552

**For a free demo, visit our website
at <http://www.interactiv.com>**

INTERACTIVE IMAGE TECHNOLOGIES LTD., 908 Niagara Falls Boulevard,
#068, North Tonawanda, New York 14120-2060 / Telephone 416-977-5550.
TRADEMARKS ARE PROPERTY OF THEIR RESPECTIVE HOLDERS. OFFER IS IN U.S. DOLLARS AND VALID ONLY
IN THE UNITED STATES AND CANADA. ALL ORDERS SUBJECT TO \$15 SHIPPING AND HANDLING CHARGE.
Fax: 416-977-1818 E-mail: ewb@interactiv.com
CompuServe: 71333,3435 / BBS:416-977-3540



CIRCLE 14 ON FREE INFORMATION CARD

Popular Electronics®

MAY 1998

Vol. 15, No. 5



COVER STORY

21 A Beginner's Guide to Radio Propagation

This article presents some of the basic principles of RF propagation and gives some pointers on how you can use this information as a radio amateur or SWL—*Karl T. Thurber, W8FX*

CONSTRUCTION

39 Build this Portable CD Amp

With nothing more than a pair of low-wattage speakers and this little amplifier, you can use your portable CD player to fill your patio, backyard, or any room in your home with your favorite music—*Homer L. Davidson*

FEATURES


33 National Electronics Technician's Day

Join the ranks of the electronics professionals


PRODUCT REVIEWS

8 Gizmo

Gizmo goes to Vegas!—A look at the hot new products and technologies shown at the 1998 International Consumer Electronics Show

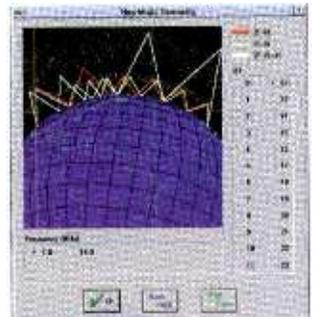

Page 21

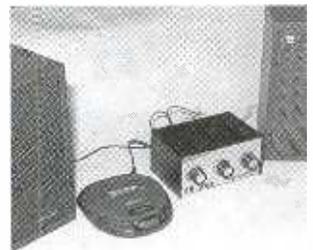

Page 39



Page 8

POPULAR ELECTRONICS (ISSN 1042-170-X) Published monthly by Gernsback Publications, Inc., 300 Bi-County Boulevard, Farmingdale, NY 11735. Periodicals postage paid at Farmingdale, NY and at additional mailing offices. One-year, twelve issues, subscription rate U.S. and possessions \$21.95, Canada \$28.84 (includes G.S.T., Canadian Goods and Services Tax Registration No. R125166280), all other countries \$29.45. Subscription orders payable in U.S. funds only, International Postal Money Order or check drawn on a U.S. bank. U.S. single copy price \$4.50. Copyright 1998 by Gernsback Publications, Inc. All rights reserved. Hands on Electronics and Gizmo trademarks are registered in U.S. and Canada by Gernsback Publications, Inc. Popular Electronics trademark is registered in U.S. and Canada by Electronics Technology Today, Inc. and is licensed to Gernsback Publications, Inc. Printed in U.S.A.

Postmaster: Please send address changes to Popular Electronics, Subscription Dept., P.O. Box 338, Mount Morris, IL 61054-9932.

A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

As a service to readers, Popular Electronics publishes available plans or information relating to newsworthy products, techniques, and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, Popular Electronics disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this magazine.

C O L U M N S

- 43 Computer Bits**
Microcontrollers II—*Jeff Holtzman*
- 44 Multimedia Watch**
A DVD ROM Kit, a Wireless PC, and New Software
—*Marc Spiwak*
- 47 Net Watch**
Sites for Movie Buffs—*Konstantinos Karagiannis*
- 49 Ham Radio**
The Quad Loop Revisited—*Joseph J. Carr*
- 52 Circuit Circus**
AM Receiver Improvements—*Charles D. Rakes*
- 55 Think Tank**
Something for Everyone—*Alex Bie*
- 59 Scanner Scene**
Base-Station Trunking Scanner—*Marc Saxon*
- 60 DX Listening**
Shortwave Newscasts—*Don Jensen*
- 62 Antique Radio**
How Many Volts to Light a Tube?—*Marc Ellis*

D E P A R T M E N T S

- 4 Editorial**
- 6 Letters**
- 36 Electronics Library**
- 37 New Products**
- 65 Popular Electronics Market Center**
- 92 Advertising Index**
- 92A Free Information Card**

Larry Steckler, EHF, CET,
editor-in-chief and publisher

EDITORIAL DEPARTMENT

Edward Whitman, managing editor
Julian Martin, editorial advisor
Robert Young, technical editor
Evelyn Rose, assistant editor
Teri Scaduto, assistant editor
Debbie Cybula, editorial assistant
Alex Bie, contributing editor
Joseph J. Carr, K4IPV,
contributing editor
Marc Ellis, contributing editor
Jeffrey K. Holtzman,
contributing editor
Don Jensen, contributing editor
Konstantinos Karagiannis,
contributing editor
Charles D. Rakes, contributing editor
Marc Saxon, contributing editor
Marc Spiwak, contributing editor

PRODUCTION DEPARTMENT

Ruby M. Yee, production director
Ken Coren, desktop production director
Lisa Baynon, desktop production
Melissa Giordano, desktop production
Kathy Campbell, production assistant

ART DEPARTMENT

Andre Duzant, art director
Russell C. Truelson, illustrator

CIRCULATION DEPARTMENT

Theresa Lombardo,
circulation manager
Gina L. Gallo, circulation assistant

REPRINT DEPARTMENT

Christina M. Estrada, Reprint Bookstore

BUSINESS AND EDITORIAL OFFICES

Gernsback Publications, Inc.
500 Bi-County Blvd
Farmingdale, NY 11735
516-293-3000
FAX: 516-293-3115

President: Larry Steckler
Vice-President: Adria Coren
Vice-President: Ken Coren

SUBSCRIPTION
CUSTOMER SERVICE/
ORDER ENTRY

800-827-0383
7:30 AM - 8:30 PM EST

Advertising Sales Offices
listed on page 92

Composition by Mates Graphics
Cover illustration by David Miller



Since some of the equipment and circuitry described in POPULAR ELECTRONICS may relate to or be covered by U.S. patents, POPULAR ELECTRONICS disclaims any liability for the infringement of such patents by the making, using, or selling of such equipment or circuitry, and suggests that anyone interested in such projects consult a patent attorney.

One scientist's vision revolutionizes the hearing industry, benefiting millions of people...

Crystal Ear® uses sophisticated electronics to provide affordable, cosmetically-pleasing and easy-to-use hearing amplification.


by Harold Sturman

One day a friend asked my wife Jill if I had a hearing aid. "He certainly does," replied Jill, "Me!" After hearing about a remarkable new product, Jill finally got up the nerve to ask me if I'd ever thought about getting a hearing aid. "No way," I said. "It would make me look 20 years older and cost a fortune." "No, no," she replied. "This is entirely different. It's not a hearing aid...it's Crystal Ear!"

No one will know. Jill was right. Crystal Ear is different—not the bulky, old-styled body-worn or over-the-ear aid, but an advanced personal sound system so small it's like contacts for your ears. And Crystal Ear is super-sensitive and powerful, too. You will hear sounds your ears have been missing for years. Crystal Ear will make speech louder, and the sound is pure and natural.

I couldn't believe how tiny it is. It is smaller than the tip of my little finger and it's almost invisible when worn. There are no wires, no behind-the-ear devices. Put it in your ear and its ready-to-wear mold fits comfortably. Since it's not too loud or too tight, you may even forget that you're wearing it! Use it at work or at play. And if your hearing problem is worse in certain situations, use Crystal Ear only when you need it.

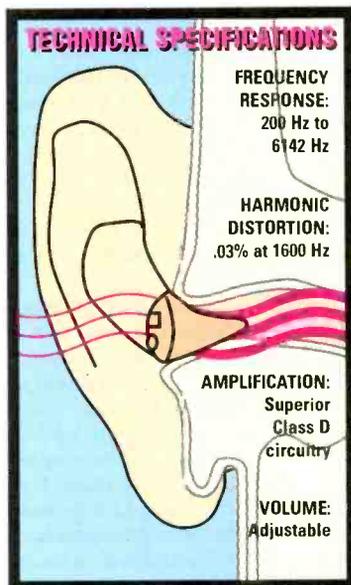A fraction of the price. Hearing loss is the world's number-one health problem, but in



Innovative, breakthrough technology solves common problem...

Hearing loss, which typically begins prior to teenage years, progresses throughout one's lifetime. Nearly 90 percent of people suffering the type of loss Crystal Ear was designed for choose to leave the problem untreated. Crystal Ear is now available to help these people treat their hearing loss with a small and very affordable Class I in-the-canal hearing amplifier.


most cases it goes completely untreated. For many millions of people, hearing devices are way too expensive, and the retail middlemen want to keep it that way. What's more, treating hearing loss the old retail way can involve numerous office visits, expensive testing and adjustments to fit your ear. Thanks to Crystal Ear, the "sound solution" is now affordable and convenient. Almost 90% of people with mild hearing loss, and millions more with just a little hearing dropoff, can be dramatically helped with Crystal Ear. Plus, its superior design is energy-efficient, so batteries can last months, not just weeks.

You'll feel years younger! Wear Crystal Ear indoors, outdoors, at home and at work. Crystal Ear arrives ready to use, complete with batteries, two different fitting sleeves, a cleaning brush and even a carrying case. Crystal Ear is a breakthrough advance in the hearing device field. It is made in the USA, using state-of-the-art micro-manufacturing techniques that cut costs dramatically—savings that we can

pass on to you. The conventional companies, domestic and foreign, don't like that! **Don't be fooled by high prices.** No hearing device, no matter how expensive, can eliminate background noise, despite claims by the manufacturers. Crystal Ear does not promise miracles—just an affordable, sound solution to many common hearing problems.

DON'T TAKE OUR WORD FOR IT...

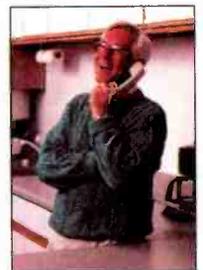"My father spent over \$5000 on another brand. I showed him my Crystal Ear, he tried it, and he decided it worked better than his brand, even though it was a small fraction of the cost!"



—A satisfied Crystal Ear user

"Over 32 million Americans experience some loss of hearing. Though most cases go untreated, over 90 percent of these people would be disappointed to learn from their doctor that there is no medical or surgical cure. There is, however, an effective treatment: electronic amplification."

—Dr. Dale Massad, MD

Risk-free. Try Crystal Ear and hear what you've been missing. It comes with a 90-day manufacturer's limited warranty as well as our risk-free home trial. If you're not satisfied, return it within 30 days for a full refund.

Crystal Ear®:

Three credit-card payments of \$99.95 \$12 S&H If not purchasing a pair, please specify right or left ear.

Please mention promotional code 3461-12617.

For fastest service, call toll-free 24 hours a day

800-992-2966



comtrad industries

2820 Waterford Lake Dr., Suite 102
Midlothian, Virginia 23113

COMPARE CRYSTAL EAR AND SEE THE DIFFERENCE

	MOST IN-CANAL BRANDS	CRYSTAL EAR
Require fitting	Yes	No
Require testing	Yes	No
Battery life	160 hours	320 hours
Impact resistance	Average	Excellent
Whistling/feedback	Frequent	Limited
Telephone use	Yes	Excellent
Retail price	\$1,000-2,000	\$299.85

Accredited B.S. Degree in Computers or Electronics

by studying at Home

Grantham College of Engineering
offers 3 distance education programs:

- B.S.E.T. emphasis in Electronics
- B.S.E.T. emphasis in Computers
- B.S. in Computer Science

NEW! Electronics Workbench Professional 5.0
included in our B.S.E.T. curriculums
-Approved by more than 200 Companies,
VA and Dantes, (tuition assistance avail.)

For your free catalog of our programs dial
1-800-955-2527

<http://www.grantham.edu>

GCE

Your first step
to help yourself
better your future!



Grantham College of Engineering
34641 Grantham College Road
Slidell, LA 70460-6815

ANTIQUE RADIO CLASSIFIED Free Sample!

Antique Radio's
Largest Circulation Monthly
Articles, Ads & Classifieds.
6-Month Trial: \$18.95. 1-Yr: \$38.95 (\$55.95-1st Class).
A.R.C., P.O. Box 802-L18, Carlisle, MA 01741
Phone:(508) 371-0512 VISA/MC Fax:(508) 371-1219

!!! BROADCAST FARTHER !!!

The model 220 is an 80-110 MHz RF amplifier that connects to mono or stereo FM transmitters and produces a powerful 2-15 watt signal which could broadcast up to 5 miles or more! Requires 50-150 mW drive.
Step by step plans complete with part source information and antenna designs... ONLY \$14 PLUS \$2 S&H NO C.O.D.'S
Progressive Concepts
BOX 588 STREAMWOOD, IL 60107
(630)736-9822 FAX:(630)736-0353

POPTRONIX®

Online
Edition

We're on the web **FREE**

<http://www.poptronix.com>

EDITORIAL

They're Baaaack!

What's back? *Terminator II*, the ghosts from *Poltergeist*? No...it's the sunspots! That's right, after being relatively dormant for about five years, old Sol is finally starting to come back to life. Our cover story, opening on page 21, features "A Beginner's Guide to Radio Propagation"—just to whet your appetite to discover more about this amazing Earth phenomenon.



Funny, when DXers get together amongst themselves they talk about rare countries, DXpeditions, band openings, and of course, the sunspots. Some old-timers recall past sunspot cycles with such reverence, it almost sounds like war veterans recalling their fiercest campaigns. Let me tell you about my "campaign."

I was fortunate to have gotten started in ham radio at the onset of one of the highest sunspot cycles in recent times (Cycle 19). My friend Mike and I had just got our Novice licenses, and we hung out mainly on the 80- and 40-meter bands. We had an on-going competition on who could work the furthest "DX" from Brooklyn, NY. We were both on a somewhat even playing field. He was running a *Heathkit* AT1, about 40 watts to a 100-foot end-fed antenna on top of a two-story home. I was pushing about the same power from my *Johnson Viking Adventurer* on the roof of a six-story apartment house, to a "sort of" 80-meter dipole. I say "sort-of" because the wire ran zig-zag through the TV antennas on the roof (let's not talk about TVI at this time!). I believed the antenna favored the east-west direction (I used the light towers of *Ebbets Field* as my reference).

Mike and I had not yet worked anyone west of the Mississippi at that time. We would track our "DX" on his wall map and stick colored pins in some of our further contacts. Then one day Mike called me and said he had just worked a station in St. Louis, MO. I was devastated—I couldn't get past Chicago. One afternoon after school, I was experimenting with my rig and noticed that I could load up on the relatively new 15-meter Novice band (my frequency was 21,150 kHz exactly—Novices were crystal-controlled then). I listened around this frequency, called a slow CQ (in Morse code, of course) and listened—nothing but noise. Over the next few afternoons I actually worked a few stations, but all local contacts. The following weekend I called CQ and listened patiently. Out of the noise, I heard a slow methodical (--- • •--- ••• -). He repeated his callsign about a dozen times. I was panicky, I never copied a station that did not start with a K or W. I composed myself, acknowledged his call, exchanged some information, and he faded away. I looked at my station notebook and saw I copied the call OE1FT, name Franz, and QTH (location) Vienna—in AUSTRIA!

I ran over to Mike's house, and when I told him I just worked Vienna, he replied, "Sure Vienna, Virginia!" He disbelieved me and said, "Where's his QSL card?" I ran to the library, looked up OE1FT's address in the callbook and sent him my QSL card...and waited. Over the next few weeks I worked stations in FA8 (Algeria), ON4 (Belgium), PAØ (Netherlands), G3 (England) and EA1 (Spain). Mike's walls of disbelief were gradually eroding. Then the *coup d'état*—OE1FT's QSL card arrived. My pin was off the map! As the other QSLs arrived, our DX competition was over—I had won. I never realized until later how important sunspots are to amateur radio, and how lucky I was to get on a great DX band just as the solar flux was on a major upswing. By the way, Mike (who now lives in California) and I still keep in contact on the air. He never got into DX, but works 2 meters.


For those hams out there, tune your rigs to the 15- and 10-meter bands and work the world. And for SWLs—for the thrill of a lifetime, get your ham license and participate in the last sunspot roller coaster ride of this millennium—Cycle 23.

Ed Whitman
Managing Editor

The U.S. Government always knows exactly what time it is...do you?

New clock from Arcron uses radio signals from the U.S. Atomic Clock in Colorado to display the precise time, within a billionth of a second.

by Jake Prine

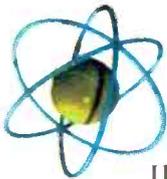


These days, timing is everything. Between meetings and appointments, deadlines and conference calls, my schedule requires that

I know the time down to


the minute. Even on weekends, I've got Little League games to coach, shows to tape and planes to catch. If I'm late, I'm sunk. The problem is that it's hard if my clocks aren't correct. Even the digital clocks can display time inaccurately. Power outages, dead batteries, time changes...any of these can cause a clock to be inaccurate. The next thing you know, you're strolling into that important conference...an hour late. Now there's no need to worry, because advanced radio technology has produced a clock which gets the time directly from the U.S. Atomic Clock in Fort Collins, Colorado, the standard for time-keeping the world over. The Atomic Clock by Arcron is the most accurate, reliable and convenient timepiece you can buy.

The most accurate clock on Earth.

Every morning at 1:00 a.m., this "smart" clock tunes in to the radio time signal emitted by the U.S. Atomic Clock in Colorado and automatically resets itself to the exact hour, minute and second. The U.S. Atomic Clock is accurate to ten billionths of a second per day. Using molecular technology, it measures the vibration rate of atoms—a constant—to calibrate time. This means that the clock deviates less than one second over a one million year peri-

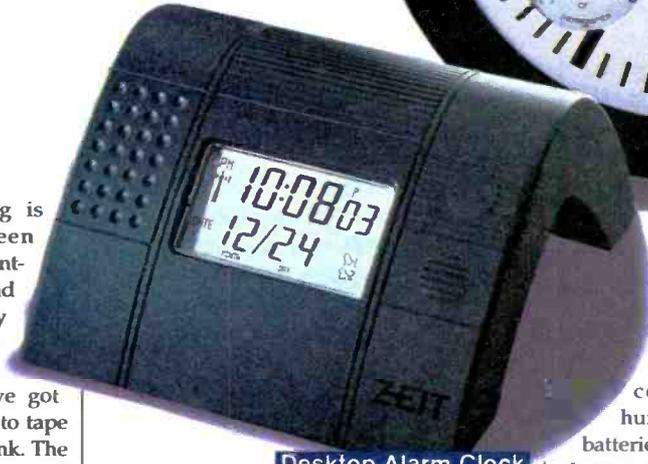

Desktop Alarm Clock

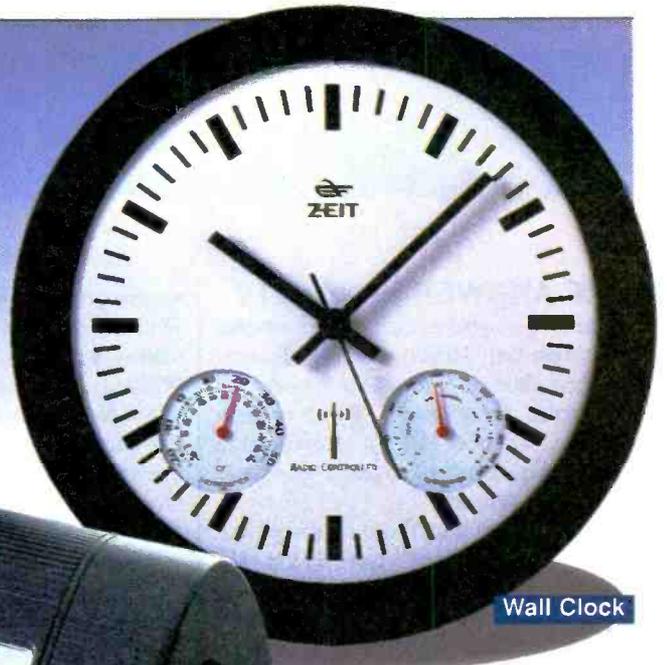

Wall Clock

clock. It also has dual alarms, perfect for couples, and one-touch illumination for nighttime viewing.

The handsome wall clock comes with temperature and humidity gauges. After you install the batteries, watch the hands spin at 20 times their normal rate, until the clock has adjusted to the precise time. Both the executive desktop and the wall model have an internal antenna for superior reception sensitivity, without unattractive wires.

Imagine having the ability to know the exact time, all the time. The Atomic Clock probably costs less than most of the clocks and watches you own, but you'll be able to use it to set them all correctly. Isn't it about time you had a clock you can trust?

The time to buy is now! Act now and you can own the world's most precise timepiece. Both the executive desktop and the wall model come with a one-year manufacturer's limited warranty and Comtrad's risk-free home trial. If you are not completely satisfied, return your purchase within 90 days for a full "No Questions Asked" refund.

od! The Atomic Clock even adjusts automatically for daylight savings time, so you don't have to remember to "spring forward" or "fall back". This clock is the only atomic clock with an internal calibrator that creates "intelligent" adjustments based on the latest signal readings. The desktop model is the only clock that will not lose time with low power or when you change its batteries.

An easy time. The most accurate clock in the world is of no use if it is difficult to operate. The Arcron Atomic Clock is engineered in Germany using the latest scientific technology. It comes in two styles, the wall clock and the executive desktop model. Both are designed to be functional and easy to use.

The desk clock's display features the exact time (in hours, minutes and seconds), month and date, or you can choose to display any two U.S. or world time zones. It features a sleek, European design, and, at only eight ounces, is the perfect travel

Every morning at 1:00 a.m., this "smart" clock tunes in to the radio time signal emitted by the U.S. Atomic Clock in Colorado and automatically resets itself to the exact hour, minute and second. The U.S. Atomic Clock is accurate to ten billionths of a second per day.



Atomic Wall Clock \$99 \$8 S&H

Atomic Desktop Alarm Clock . . . \$99 \$8 S&H

Please mention promotional code 2761-12618.

For fastest service call toll-free 24 hours a day

800-992-2966



To order by mail, send check or money order for the total amount including S&H. To charge it to your credit card, enclose your account number and expiration date.

Virginia residents only—please add 4.5% sales tax.

comtrad industries
 2820 Waterford Lake Dr., Suite 102
 Midlothian, Virginia 23113

LETTERS

THE ANSWER IS SAFETY

In the *Letters* column (**Popular Electronics**, March 1998), Joseph Carr, author of the article "Safety for Electronic Hobbyists" (**Popular Electronics**, October 1997), answered a reader's question on grounding. I have a different answer.

"Why is the center tap on the power service grounded?" **SAFETY!!** My teacher in school (a long time back) explained it this way.

Let's look at what could happen if this 110/120-volt system is ungrounded. The power line feeds several homes. In your home, the power system is now floating—there should be no shock hazard touching any line to ground. Let's say now, that your neighbor has a defective appliance. The appliance shorts one end of the service to ground; no fuses blow or circuit breakers trip. Back at your home, everything looks normal, but, unknown to you, you now have a lethal situation at some outlets in your home. Instead of having a maximum of 110V to ground (hazardous—yes, lethal—occasionally), you now have 220 volts to ground (hazardous—yes, lethal—yes). That was how he explained it.

E.M.

via e-mail

UNSUNG INVENTOR

I've just read Larry Lisle's article "Before Their Time" (**Popular Electronics**, March 1998). One other inventor whose idea fell by the wayside was Professor Woodyard of University of California-Berkeley (UCB).

In 1942, he put two points onto a piece of germanium and found he was getting a larger signal out of it than he was putting in. In other words, he had made a solid-state amplifier. He submitted a patent application through UCB's legal department. Since UCB was only interested at that time in cyclotrons, the reaction was what does a germanium amplifier have to do with cyclotrons? And no revelation of his solid-state amplifier (later called a solid-state transistor) was announced.

I came to learn about this at an IEEE

meeting in 1967 in Palo Alto, CA on the 20th anniversary of the invention of the silicon transistor. On the panel were William Shockley *et. al.*, plus Dr. Woodyard, who told this story of how the transistor was really invented about five years earlier than its official date.

R.G.R.

Phoenix, AZ

A FLYBACK TESTER, ANYONE?

Every month I look forward to receiving my copy of **Popular Electronics** because it presents such an interesting overview of developments in the electronics field. As I am an electronics technician with my own repair shop, I especially appreciate the unique projects offered in each issue. I would like to suggest a project for future publication.

I repair audio/video equipment with television comprising a large portion of my business. In talking with fellow repairmen, I can attest that there is a definite need for a reliable flyback tester. While there are such testers currently available, they are either cost-prohibitive for the small businessman or, when they are economical to obtain, they simply don't work properly. Since a flyback tester is also an integral component of computer monitor repair, instructions for building one's own tester would probably be greatly appreciated by those in the computer industry.

Thank you in advance for considering this idea.

D.B.

Kenmore, NY

Well, here is another possible construction idea for those "would-be" designers out there. Add this project to the list started in the March Letters column.—Editor

BATTERY QUESTION

I found January's issue of your product test review on AA alkaline batteries to be very informative. You provided a concise, unbiased review on a number of the leading battery suppliers. The data presented was more

than superficial, but not detailed to the depth which required an engineering degree. I look forward to similar reviews on other battery cells/types in the future.

I do have one question, however, which I have never seen addressed. I usually use the *Duracell*-brand of alkaline cell (which came out the best in your tests) in a number of toys and electrical gadgets in my house. It seems that after a few weeks of use, the metal contacts on the battery holder in the toys start building up some corrosion, or chemical reaction, with the battery terminals. This requires me to remove the battery and clean off these contacts. This effect is not noticed with similar batteries from other manufacturers. Do you have any suggestions?

J.S.

Lauderdale Lakes, FL

We are not sure what this chemical reaction could be caused by with the Duracell brand of alkaline cells. Perhaps the humid conditions of Florida might have an effect on this corrosion, or maybe it is some strange reaction with the battery-holder material. We do know that Duracell, along with all the major battery manufacturers, has removed mercury from their alkaline cells, making them safer for the environment, but we are not experienced in identifying possible chemical effects between battery terminals and the holder. Readers—any similar experiences or possible explanations on this effect?—Editor

GUITAR AMPLIFIER IMPROVEMENTS

I really enjoyed the "Guitar Amplifier" article by Rodrick Seely (**Popular Electronics**, December 1997). I remember the first guitar amplifier project you did: the "MM/M Instrument Amplifier" in the April and May 1968 issues—and each one you publish gets better. It is a shame you did not provide a circuit description for the complementary-symmetrical power amplifier section of Mr. Seely's design, since it is quite interesting. In addition to the

short-circuit protection provided by Q5 and Q6, he uses a differential input stage consisting of Q2 and Q3, with Q2 cascoded by transistor Q1. Instead of just using diodes to bias the output stage transistors, he incorporates Q4 as a V_{BE} multiplier, which allows precise adjustment of the output stage bias current. These features are not always incorporated even in professional units, and they can greatly improve the performance of an audio amplifier.

One standard circuit which I noticed was not included is a Zobel network across the speaker. A loudspeaker is a series R-L circuit whose impedance increases with frequency. While the amplifier can drive a resistive load without any problems, inductive loads can cause an amplifier to oscillate at high frequencies because the inductance appears as an open circuit. This is aggravated because there is no capacitor across R21 to roll-off the high frequency response. A Zobel network is a series RC compensation circuit which is connected across the speaker. With properly selected resistor and capacitor values (a stable film capacitor should be used), the impedance seen by the amplifier output stage can be made to appear constant. This can be shown specifically in the formula, $C_z R_z = L_s / R_s$ —where the subscript "z" represents the Zobel values and the subscript "s" refers to the speaker values.

As an example, let's assume the speaker has a DC resistance of 8 ohms and an inductance of 10 μ H (the actual values should be available from the speaker supplier). In order to have the amplifier load appear as a constant 8 ohms, you select:

$$C_z = L_s / (R_z R_s) = 10 \mu\text{H} / (8 \times 8) = 0.156 \mu\text{F}$$

Thus, by connecting a series combination of an 8-ohms resistor and 0.15- μ F capacitor across the speaker, the amplifier will be unconditionally stable at all frequencies.

C.H.

Tinton Falls, NJ

HAVES & NEEDS

I would like to ask my fellow **Popular Electronics** readers for some help. I am looking for a circuit diagram for a device that indicates when the telephone line is busy.


Any response will be greatly appre-

ciated. Thank you for any help you can give me.

Brenden McNeil
203 S. Cleveland Ave.
Elsmere, DE 19805
e-mail: brenden_mcneil@hotmail.com

I am looking for a circuit which shows you how to interconnect two telephones to make an intercom. I think I saw something in **Popular Electronics** about ten years ago. Any references provided will be appreciated.

Al Conforti
via e-mail: xalbex@aol.com

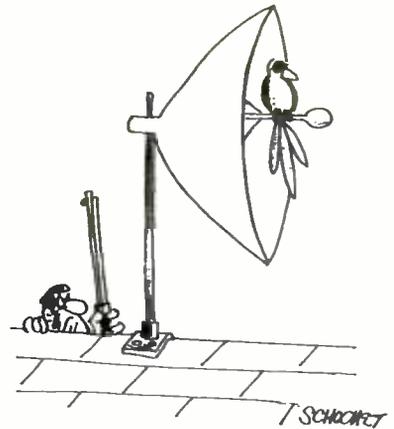

PC-BOARD DESIGN

made easy



EAGLE 3.5


Schematic Capture • Board Layout
Autorouter

for Windows® 95/NT

Windows 95 and Windows NT are registered trademarks of Microsoft Corporation.

Why have more than 25,000 pc board designers chosen EAGLE as their layout tool?

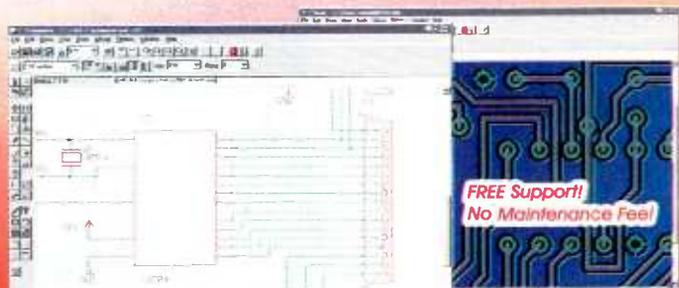Mainly because EAGLE is so easy to use that you can start designing your own boards within a few hours. But there are many other good reasons! Check out our Web Site for a free demo and more detailed information.



EAGLE Standard

Board Size: 6.3 x 4 inches
4 Signal Layers
99 Sheets per Schematic

398\$

EAGLE Light

Board Size: 4 x 3.2 inches
2 Signal Layers
1 Sheet per Schematic

100\$

EAGLE Professional

Board Size: 64 x 64 inches
16 Signal Layers
99 Sheets per Schematic

798\$

Order a FREE demo today and experience EAGLE first hand. You will be surprised!

800-858-8355
www.cadsoftusa.com

CadSoft Computer, Inc., 801 S. Federal Highway, Delray Beach, FL 33483
Hotline (561) 274-8355, Fax (561) 274-8218, E-Mail: info@cadsoftusa.com

These prices include Schematic Capture and Board Layout. The Autorouter Module is available for \$40/199/299\$. Pay the difference for Upgrades.

GIZMO®

GIZMO GOES TO VEGAS!

A look at the hot new products and technologies shown at the 1998 International Consumer Electronics Show

Amidst the hustle and bustle, hype and hoopla of the 1998 International Consumer Electronics Show (ICES) this January in Las Vegas, video technologies took center stage. Don't get us wrong; there was plenty happening in the worlds of audio, computers, telecommunications, and personal electronics. Throughout the Las Vegas Convention Center, the Sands Convention Center, and several surrounding hotels, manufacturers displayed a huge variety of consumer-electronics gear, ranging from such mundane items as carrying cases and home-theater furniture to high-end audio and video products. But you couldn't turn around without coming face to face with demonstrations of Digital TV (DTV) and High-Definition TV (HDTV)—often displayed on large-screen, hung-on-the-wall plasma-display monitors that are as little as 4-inches thick.

In our ICES 98 roundup, we'll take close-up looks at DTV, HDTV, and plasma-display devices, and then describe some of the other neat technologies displayed at the show. Next month, we'll present a broader picture of ICES with a special "Wish List" of products that brought home Innovations 98 awards in various product categories.

HDTV VS. DTV

Drawing crowds to more than a dozen booths at ICES 1998 were high-definition televisions that were showing actual, real-time, real-life HDTV broadcasts, provided by two local stations: KLAS-TV (CBS) and KLVX (PBS). At previous shows, HDTV sets displayed prerecorded Japanese pro-



Displays of HDTV sets drew crowds at a dozen booths in the Las Vegas Convention Center, including Pioneer's, shown here.

gramming. The 1998 ICES marked the debut of the first live U.S. HDTV broadcasts, generating plenty of excitement and more than a little confusion.

The experimental HDTV feeds are forerunners of the HDTV rollout that's scheduled to begin this fall, which is also when the first HDTV sets are expected to



The Consumer Electronics Manufacturers Association hopes the new DTV certification logo, which signifies that a product is capable of receiving and displaying all ATSC video formats, will help reduce consumer confusion. A CEMA/ATSC certification program will allow manufacturers to assess their products for conformance to the ATSC standard.

become available. That doesn't necessarily mean that you'll be able to see any HD broadcasts, however, even if you do have the big bucks needed to buy one of the first-generation HDTVs. First, initial broadcasts will reach only the top ten U.S. markets (Atlanta, Boston, Chicago, Dallas, Detroit, New York, Philadelphia, Los Angeles, San Francisco, and Washington, D.C.). Second, no one has quite reached a consensus on HDTV standards (although the finalized HDTV standards might be released by the time you read this). Third, broadcasters must decide how much bandwidth they're willing to allocate to HDTV and how much to digital standard-definition TV (SDTV).

As we go to press, this much is known: HDTV will deliver about twice the resolution of National Television Systems Committee (NTSC) TVs. At the minimum, HDTV will offer a vertical display resolution of 720 progressive/1080 interlace (or higher): the ability to display a 16:9 image at that resolution; the ability to receive all Advanced Systems Television Committee (ATSC) table formats; and the ability to receive, reproduce, and/or output Dolby Digital (AC-3) audio. The Federal Communications Commission has mandated that broadcasters must begin the transition to digital in the top ten markets by May 1999 and in the top 30 markets by November 1999. Analog signals will continue to be sent at least through 2006. Some cable operators, such as HBO, and satellite providers, such as DirecTV, have announced that they will broadcast HDTV

Gizmo is published by Gernsback Publications, Inc., 500 Bi-County Blvd., Farmingdale, NY 11735. Senior Writers: Christopher Scott and Teri Scaduto. Copyright 1998 by Gernsback Publications, Inc. Gizmo is a registered trademark. All rights reserved.



Thomson's ProScan PS3800 multimedia monitor is an interim product, providing peak video performance from today's DVD players and Internet access devices, and tomorrow's digital set-top converters.

programming later this year.

But the "transition to digital" doesn't necessarily mean the broadcasting of HDTV. Digital TV is a broad umbrella term that encompasses not only HDTV, but also digital standard definition TV and several other potential systems. The SDTV format, as you'd expect, delivers lower resolution than HDTV and doesn't have a specified aspect ratio. An SDTV product or system must have the ability to receive all ATSC Table III formats and to produce "usable audio" and "a usable picture." There is no specified aspect ratio for SDTV.

Under the FCC ruling, broadcasters must switch to digital. However, they still have a lot of options. For example, given its new channel assignments, a TV station could choose to broadcast one or two high-definition signals, or multiple SDTV signals. It boils down to quality vs. quantity, because several SDTV broadcasts take up the same bandwidth as one HDTV signal. Will HDTV stations demand (and get) higher advertising revenues? Or will broadcasters fare better economically with more stations and less resolution? Those questions are yet to be answered.

What does all this mean to you as a consumer? First, if your old TV is on the fritz, or you've been considering making the move to a big-screen set, don't put off the purchase while awaiting a digital set. Television sets have an average life-span of 8 years. So if you buy one now, by the time it needs replacing, DTV sets will be a well-established, and perhaps even reasonably priced, commodity. (Right now, they're running from \$2000 to \$5000 more than comparable analog models. Current estimated prices for first-generation HDTVs are even more prohibitive, with starting prices between \$8000 and \$10,000! Consumer-electronics products

generally cost half their "introductory" price—in some recent instances, much less—by their tenth anniversary.) If digital TV really takes off in the meantime, you'll be able to buy a less expensive set-top converter box that will allow your 1998 or older set to receive digital broadcasts as well as analog ones.

Keep in mind that it was a full decade after color TV's introduction that the one-millionth color set was sold. HDTV is expected, by some, to have a much slower acceptance rate due to initially prohibitive retail costs, limited programming options, and the fact that today's viewers, who already enjoy better pictures and sound than ever before from a range of digital sources, don't perceive the same urgent need that spurred color-TV sales.

According to the Consumer Electronics Manufacturers Association (CEMA), conservative estimates predict that 30% of U.S. households will have digital sets by 2006. On the other hand, consumer acceptance of such formats as digital satellite transmissions, DVD, and Dolby Digital might indicate that we are getting primed for HDTV.

The consumer-electronics and broadcasting industries face a number of hurdles in the race to deliver HDTV to the American viewing public. First and foremost, perhaps, is convincing less technologically aware viewers that they might want and need digital TV—a challenge in light of the fact that, according to a study on DTV conducted by the Verity Group, most Americans have little or no idea what DTV is and what HDTV can mean to them, and that some confuse DTV with other technologies, such as DVD and Digital Satellite System (DSS). Clearly, an all-out public-education campaign is needed. The Verity study also found that if peo-

ple are going to spend the money on a DTV set, enhanced picture quality is not enough. The set had better offer increased functionality—for instance, computer capabilities and interactivity—and improved sound quality, as well as excellent programming choices, or the buying public won't buy.

Broadcasters, on the other hand, face huge initial expenses in building large HDTV transmission towers and purchasing the necessary equipment, and have worries about new interference sources. Perhaps that's why, out of all the stations in the top ten markets, only 26 have adopted the accelerated production schedule needed to begin digital broadcasting by year's end.



Sharp's 36-inch DTV-ready analog set has 800 lines of resolution, and component video inputs for use with DVD players and DTV converters.

What if you just *have* to be the first one on your block to have a digital TV or HDTV set—and you have deep pockets or a terrific credit line? If you can wait until the fall, you're in luck. More than a dozen manufacturers showed prototypes or actual products or announced marketing plans for such. To resolve the current standards confusion, virtually all of the DTVs shown have the ability to receive 1080i HDTV signals as well as the 17 other formats that fall under the DTV heading. (No, 1080i is not another form you have to complete and mail to the IRS by April 15. It refers to 1080 interlaced lines of resolution—as compared to today's 525 interlaced lines—and if it's not found in a DTV's specifications, that set is not HDTV compatible.)

Thomson Consumer Electronics not only showed HDTV hardware but, along with DirecTV, hosted a demonstration of the first-ever HDTV direct-to-home satellite feed. DirecTV announced that it would begin transmitting two HDTV channels nationwide over the DSS satellite system sometime this year. At the joint press con-

ference, the companies pointed out that if just one percent of the current 4 million DSS subscribers decided to purchase a high-definition television, that would translate to 40,000 sets. Thomson hopes some of those bought will be its ProScan 61000 61-inch, 2,073,600-pixel (1920 × 1080 interlaced) HDTV set. The 61000 HD set has a suggested retail price of \$8000. Thomson also displayed two ProScan multimedia TVs that are converter-box-ready and offer data-grade picture tubes. They will be available later this year at prices yet to be announced.

Mitsubishi hopes to introduce three or four models in its HD-1080 series before the end of this year. The mid- to large-screen sets will have suggested retail prices ranging from \$8000 to \$11,000. In addition to 1080i HDTV signals, the sets will provide full Dolby Digital 5.1 channel output, and enhanced NTSC processing to dramatically improve analog images.

Sharp was displaying a variety of DTV prototypes on the show floor. Said Robert Scaglione, director of product planning, "We are taking a broad approach that will provide consumers with a variety of options, from set-top boxes that will let consumers receive DTV signals on their existing sets to widescreen HDTV projection sets capable of tapping DTV's full potential. Prototypes displayed at the show included a 1080i front projector with a 100-inch screen, digital set-top boxes, and direct-view and rear-projection DTVs." In terms of real products, Sharp plans to make available early this year DTV-ready component-input analog televisions, in 27- to 36-inch sizes, as well as several DTV-ready SharpVision LCD projectors.



Zenith's digital HDTV receiver/decoder (top), combined with the company's Pro900 high-definition front-projection monitor (bottom), provides a full HDTV home-theater or commercial package, delivering high-definition images up to 200 inches diagonal.

Zenith is also taking several different approaches to HDTV. The company plans to begin marketing its Digital HDTV Receiver/Decoder this spring. The Zenith-Inteq model IQADTV1W is a stand-alone unit that includes the Zenith-developed vestigial sideband (VSB) demodulation system, MPEG-2 video decoding, and



The Zenith-Inteq 64-inch widescreen HDTV set will be available this fall.

Dolby Digital audio decoding. Combine it with Zenith's PRO900 high-definition front-projection monitor for a complete HDTV package, with images up to 200 inches diagonal. The company's first integrated HDTV set is a 64-inch diagonal widescreen rear projector, Zenith-Inteq model IQA64W10W, which will be available this fall for "more than \$10,000." It will provide 1920 × 1080 HDTV resolution, Dolby Digital audio processing, and a 15-pin VGA computer input (along with three S-Video jacks, 15 composite video jacks, and four RF inputs).

John Briesch, president of Sony's Consumer Audio/Video Products Group, speaking from Sony's "unique vantage point as the only company involved in virtually every aspect of the digital television chain—from broadcasting and content creation to TV set manufacturing" noted, "We believe the transition to digital TV ... will not take place overnight. It will certainly be more complex than when consumers switched from black-and-white TVs to color sets." During the transition period, Sony plans to introduce a "total range of home entertainment solutions" including HDTV products this fall in the ten markets scheduled to receive HDTV broadcasts, converter boxes, and a flat-display

Over 5000 IC's, components and much more!

JAMECO's 25th Year of Serving You

Special Prices for Popular Electronics Readers. Please mention VIP #5P!

Component Cabinet Kits

Kits include the most popular components with extra space for your customized expansion. Each kit includes a 20 drawer component cabinet.



More kits available - call for details!

Part No.	Description	Price
84953	330 pc. 7400 series IC kit	\$159.95
84961	420 pc. 74LS series IC kit	\$119.95
84970	300 pc. CD4000 series IC kit	\$84.95
84988	385 pc. Linear series IC kit	\$159.95
108329	540 pc. 1/8 watt Resistor kit	\$29.95
81832	540 pc. 1/4 watt Resistor kit	\$28.95
107879	540 pc. 1/2 watt Resistor kit	\$32.95
108433	2200 pc. Electr. Hardware kit	\$39.95
81867	110 pc. Radial Capacitor kit	\$34.95
81859	320 pc. Ceramic Capacitor kit	\$29.95
81883	160 pc. Mylar Capacitor kit	\$34.95
81841	129 pc. Tantalum Capac. kit	\$49.95
82587	270 pc. Diode kit	\$39.95
82595	180 pc. Transistor kit	\$49.95

75MHz Barebones Pentium®




Monitor, video card and hard drive not included

- 16MB of RAM upgradeable to 128MB
- 256KB cache RAM, upgradeable to 512KB
- Hard disk and floppy I/O controller card
- Four exposed bays (two 5.25", two 3.5"); one internal 3.5" bay • 3.5" floppy drive
- Includes keyboard, mouse and cables
- Four PCI slots and three ISA slots

Part No.	Description	Price
146499	75MHz Pentium® Sys.	Special \$299.95

Ultrasonic Motion Detector Kit

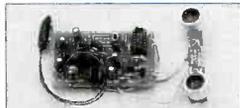

- Detects motion from 4-7m away
- Switchable latch, red LED indicator
- Solder pad output to drive external relay or circuits
- Requires 9V battery (not included)

Part No.	Description	Price
125090	Ultrasonic alarm kit	\$29.95

DC to Pulse Width Modulator

The circuit converts a DC voltage into a series of pulses, such that the pulse duration is directly proportional to the value of the DC voltage.

Part No.	Product No.	Price
120539	K8004	\$20.95

JE 2206 Function Generator Kit

Produces sinusoidal, triangular (saw-tooth), and square waveforms at frequencies continuously variable from 1Hz to 100kHz. Requires 12VDC supply or ±6VDC split supply.

Part No.	Description	Price
20685	Function generator	\$19.95

METEX® 3 1/2-Digit Digital Multimeter


- 3 1/2-digit LCD (.5" high digits)
- AC voltage: 200mV, 2V, 20V, 200V, 700V
- DC voltage: 200mV, 2V, 20V, 200V, 1000V
- AC & DC current: 20µA, 200µA, 2mA, 20mA, 200mA, 2A, 20A
- Resistance: 200Ω, 2KΩ, 20KΩ, 200KΩ, 2MΩ, 20MΩ • Input impedance: 10MΩ
- Auto zeroing • One-year warranty



Part No.	Product No.	1-4	5-9
27115	M3800	\$39.95	\$35.95

Muscle Wires Project Book & Deluxe Kit

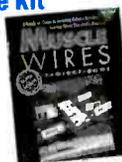
Get the facts behind the unusual properties of Muscle Wires. Study their uses in heat engines, industrial, medical and aerospace applications, electronic and mechanical devices, prosthetic limbs, robotics, virtual reality systems, and more!



Part No.	Description	1-4	5-9
141348	Muscle Wires kit	\$59.95	\$53.95

VITRAX Programmable Controller

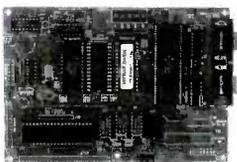
Control, Measurement, Data Collection Self-Contained Development System



- Kit or Fully Assembled
 - 24 digital I/O lines
 - Two serial channels to 19.2K baud; DE9 interface
 - Four external interrupts for instant response
 - 8KB RAM (expand to 32KB)
 - 16KB EPROM space for application code
 - Built-in EPROM programmer
 - Optimized BASIC language in ROM—fast! - 80 commands
 - sup. float point, strings, integers, arrays
 - interrupt service commands
 - serial channel data manager and buffer
 - Power: 5VDC regulated; 250mA
 - Size: 4.5" L x 6.5" W • One-year warranty
- | Part No. | Description | Price |
|----------|------------------------------------|----------|
| 148700 | VITRAX controller kit | \$129.95 |
| 148697 | VITRAX - assembled | \$159.95 |
| 148734 | A/D converter module, 10-bit, 8-ch | \$9.95 |
| 148726 | RealTime calendar clock module | \$9.95 |
| 148718 | LCD interface port: 2 x 7 pin mod. | \$19.95 |
| 134658 | Novation power supply | \$6.95 |

mission technology PC-Multiscope 2

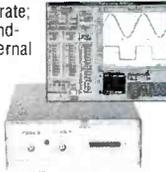- 20MHz sampling rate; 10Mhz analog bandwidth; built in external trigger
- 1mV/div to 10V/div; built in adjustable DC power supply output
- Frequency analyzer (FFT) and transient signal modes



Part No.	Description	Price
142834	PC-Multiscope 2	\$399.95

Hand-held EPROM Programmer/Emulator

- 512Kbits of RAM
- Supports EPROMs, EEPROMs and Flash memories up to 8Mbits
- Self-powered and completely portable - ideal for field service work
- Maximum pins: 32



Part No.	Description	Price
124003	EPROM programmer	\$749.95

AXIOM 48-Bit Digital I/O Card

- Low cost IBM PC/XT/AT compatible D/I/O card
- 48 TTL/DTL compatible digital I/O lines arranged into 8-bit ports
- Software programmable for inputs/outputs
- Emulates 8255 PPI mode 0



Part No.	Description	Price
136784	48-bit digital I/O card	\$99.95

PARALAX Basic Stamps



127693 130892

Basic Stamps are small computers using a variation of Basic, called PBASIC to control execution of many applications. The BS-1-IC has 8 I/O lines, while the BS-2-IC has 16 I/O lines which can be connected directly to buttons, LEDs, registers, and many other TTL level devices. • One-year warranty

Part No.	Description	Price
127693	Basic stamp BS-1-IC	\$34.95
130892	Basic stamp BS-2-IC	\$49.95

Easy Photo Reader Scanner

- 133 dpi color optical resolution
- Up to 1200 dpi color enhanced resolution
- 24-bit true color
- TWAIN compliant
- Single pass scanning
- Photo reader with feeder 5.5" x 6" x 3", feeds up to a 5" x 7" photo
- Easily plugs into a parallel port



Part No.	Description	Price
147264	Photo scanner	Special \$69.95

Hyper Peppy Robot Kit

- Changes course when it comes in contact with an object or hears a loud sound



Part No.	Description	Price
140863	Robot kit	Special \$19.95

Jameco Solderless Breadboards

- Low static plastic body - CMOS safe
- Nickel plated clips designed to withstand up to 5,000 insertion cycles



Part Number	Contact Points	Size L x W	1-9	10-49
94457	100	6.5 x 0.4	\$2.49	\$2.25
20600	400	3.3 x 2.1	4.95	4.49
136901	1,600	5.5 x 2.3	SAL 19.95	
20669	630	6.5 x 1.4	5.49	4.95
20722	830	6.5 x 2.1	7.95	6.95
20757	1,360	6.5 x 3.1	11.95	10.95
20773	1,660	6.5 x 4.3	17.95	15.95
20790	2,390	6.9 x 5.8	22.95	20.49
20811	3,220	7.3 x 7.5	30.95	27.95

EDWin NC (CAD/CAE) Software

The first truly seamlessly integrated suite of software running in all Windows® formats...Simulation, schematics, and PCB design. Large start-up libraries.



Part No.	Description	1-4	5-9
141680	EDWin NC	\$149.95	\$134.95

Weller® 40-Watt Electronic Soldering Station

- 40 watts, 120V @ 60Hz
- Lighted on/off switch
- Adjustable power from 5 watts - 40 watts
- Temperature is electronically controlled from 350°F to 850°F • UL listed
- Includes ST3 1/8" screwdriver tip, soldering station, soldering handle and manual



Part No.	Description	Price
146595	40 watt soldering station	\$44.95

Power Authority II

- Master power switch and 5 auxiliary switch for each outlet
- Heavy duty 8' cord with 3 line AC protection
- Ground indicator • EM/RFI filtering
- Static discharge plate (will eliminate static charge once touched)
- UL approved telephone line protection
- Maximum spike current @ 96,000 amps
- UL1499 clamping voltage: 330 volts
- \$15,000 connected equipment manufacturer's warranty



Part No.	Description	Price
147011	Power base	Special \$24.95

SHARP Camera Board

- EIA system 512(H) x 492(V)
- Composite output - 380 lines resolution
- 1/50 to 1/1000 sec. shutter speed
- 2.1mm female center positive



Part No.	Description	1-4	5-9
127263	Camera board	\$129.95	\$116.95

JAMECO
ELECTRONIC COMPONENTS
COMPUTER PRODUCTS

© 1998 Jameco 5/98
Order Toll Free 24-Hours
7-Days a Week!

1355 Shoreway Road
Belmont, CA 94002-4100
FAX: 1-800-237-6948 (Domestic)
FAX: 650-592-2503 (International)
E-mail: info@jameco.com
http://www.jameco.com

Call for your FREE catalog!



Mention V.I.P.# 5P8

Call 1-800-831-4242 day or night!



Philips' 64-inch rear-projection HDTV set features full ATSC and NTSC decoding, maximum display of 1080 × 1925 interlaced lines of resolution, and Dolby Digital surround sound.

Trinitron "Wega" TV.

Philips Consumer Electronics Company president and CEO, Robert Minkhorst, expressed a more optimistic view: "1998 will be a historical year as the television industry enters the Digital Era, and Philips is excited to be a leader in this transition with our first HDTV offering"—a 64-inch widescreen rear projection set slated for fall availability. "The transition to digital marks a paradigm shift in how consumers will experience television in their homes—much the same way that the transition from black-and-white to color changed television in the 1950s and 60s."

Panasonic, which had already introduced a "digital-ready" SVGA TV/monitor, displayed at ICES a prototype 36-inch widescreen direct-view DTV, a 56-inch widescreen rear-projection TV, and a set-top converter box, all still under development but expected to be available this fall. JVC's top-of-the-line front-projector will be capable of delivering HDTV signals. Samsung's SVP-555JHD 1080i HDTV features an MPEG-2 video decoder, a universal format converter to translate any DTV or NTSC signal to 1080i or 720 or 480 progressive scan, and a Dolby Digital decoding system for HDTV and DVD.

Unity Motion, which bills itself as "HDTV programmers and equipment integrators," plans to provide both HDTV programming and a satellite dish capable of receiving it, along with direct-view and rear-projection HDTV sets. Initial tests are slated to begin in February, four to six channels are expected by summer, and as many as a dozen by fall. The company will market complete packages, consisting of, for instance, a 28-inch widescreen set, Ku-band dish, and integrated receiver-

decoder (IRD) (\$5500). Substitute the 72-inch rear-projector, and the price jumps to about \$10,000. Programming will run about \$50 a month.

In other HDTV satellite news, EchoStar reacted to the DSS HDTV demo with an "anything you can do we can do better" attitude. EchoStar is currently the only U.S. Direct Broadcast Satellite (DBS) provider to use an MPEG2 world standard transport. It also claims "twice" the capacity of any of its competitors, even before the March 1998 launch of another satellite. EchoStar promises to begin HDTV transmissions as soon as the digital TV sets and programming are out there.

On the business end of DTV, Philips Semiconductors demonstrated the first in a series of TriMedia DTV reference platforms, a complete reference design for developing Advanced Television Systems Committee (ATSC) TVs, set-top boxes, and PCs, supporting all 18 ATSC standards from SDTV to HDTV and easily programmed to provide custom features and to support additional applications such as video e-mail, video telephony, Internet access, and communications. The platform includes both hardware and software to allow manufacturers to quickly develop ATSC products. So far, Philips Electronics Sound & Vision Group and Samsung Information Systems America have announced plans to use the TriMedia DTV reference platform.



Philips Semiconductors' TriMedia programmable DTV reference platforms allow hardware and software manufacturers to quickly develop ATSC products.

Zenith chose the ICES venue to declare its collaboration with Intel Corporation in the development of demodulator cards that will allow PCs to receive DTV broadcasts, including data services. Intel's Tom Galvin, director of market development, digital broadcast and broadband, said the joint development effort "supports Intel's vision of bringing exciting digital content and broadband services to millions of Intel Architecture-based computers around the world." Intel has integrated Zenith's VSB



The electronics for Philips FlatTV plasma television are housed in a separate unit, shown in front. The 4.5-inch thick set features data/video display capability, multi-standard display compatibility, and a 160-degree viewing angle.

technology into a prototype PCI board design for cost-effective PC implementation. Zenith's VSB digital transmission system was adopted by the FCC as part of the ATSC DTV broadcast standard. Any consumer product that receives an ATSC DTV signal will use Zenith's patented technology. Now, in addition to licensing VSB to DTV manufacturers, Zenith plans to license its DTV technology to the PC industry, under terms that have yet to be disclosed.

Just before the Consumer Electronics Show, Sony announced that it plans to work with NextLevel Systems Inc. to jointly develop digital TV technologies and HDTV products for cable TV users. At its ICES presentations, Sony emphasized its deep involvement in behind-the-scenes aspects of DTV, from supplying broadcasters with HD cameras, monitors, editing and special-effects equipment to transferring an archive of more than 200 films to high-definition digital video.

What does it all come down to? The technologies are there, ready for use. And the end result is terrific. (We particularly enjoyed Runco's elaborate high-definition home theater. Granted, all its varied components probably cost more than the average house, and the speaker arrays were the size of a small car. Even the non-HDTV digital source material (DVD) looked and sounded great, but the step up to HDTV was a noticeable improvement.) But it will take several more years, at best, for HDTV to hit the mainstream. Meanwhile, we'll be hearing a lot more about digital and high-definition television, as the consumer-electronics indus-

5 Reasons why NRI Training in PC Servicing puts the emphasis on you

**Real-World Technology...
New Course Features...
Hands-On Experience...
Service...
Convenience**



Real-World Technology

- You get a customized 200 MMX Pentium® computer to train with and keep.
- You use your new computer's 33,600 baud or faster fax/modem in conjunction with Netscape Navigator™ Web browser software.
- You train with a digital multimeter, for quick and easy testing.
- You learn to take advantage of PC communications and the Internet.

New Course Features




- You can move up to an even more feature-packed computer system at special student prices, with NRI's new PC Options Plan.
- You get a free upgrade to Windows 98.
- You receive an exciting multimedia CD-ROM from Norton Interactive
- You gain computer

aided electronics troubleshooting experience with diskettes covering four key areas: AC electronics, DC electronics, semiconductors, and electronic circuits.

Hands-On Experience

- You establish a solid foundation with a review of basic electronics.
- You learn how to troubleshoot and maintain today's sophisticated PCs.
- You train with the NRI Discovery Lab to experience circuit design and modification.
- You explore the features you've chosen for your computer, from memory chips to high-speed CD-ROM drive.
- You explore the applications and accessories of Windows 95, then move up to new Windows 98.

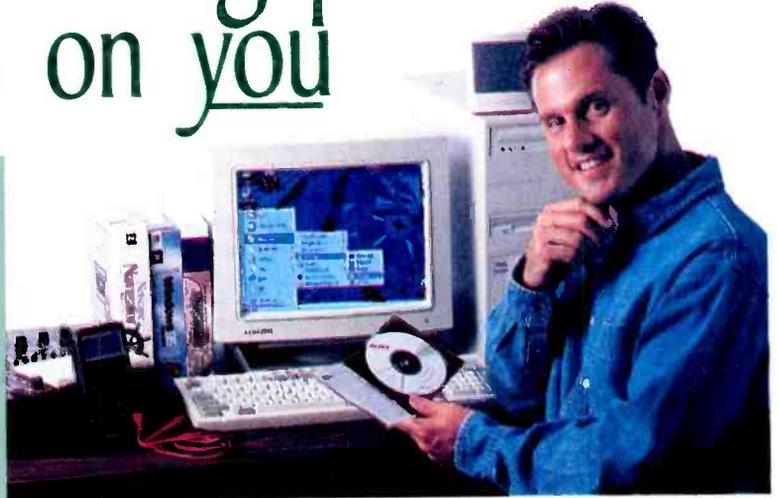

Service

- You work one-on-one with an experienced instructor.
- You can call NRI's TeleService hotline, for 24-hour answers to your questions.
- You get immediate feedback with NRI's TeleGrading service, featuring 24-hour exam grading.
- You can continue receiving advice and feedback from your instructor after you graduate.
- You can turn to NRI for letters of recommendation, transcripts, tips on resume writing, and more.

Convenience

- You don't need any experience to get started.
- You study at home, at your own pace.
- Your company may pay for all or part of your tuition.
- You can reach your instructors easily by mail, phone, fax, or online.
- You can tailor your training to meet your immediate interests or professional goals.



CALL 1-800-321-4634 FOR FREE CATALOG!

NRI Schools

4401 Connecticut Avenue,
NW, Washington, DC 20008

Ask for Ext.3004

Check one FREE catalog only

PC SERVICING

Game Programming Fundamentals

Troubleshooting Personal Computers

Computer Programming

TV/Video/Audio Servicing

Desktop Publishing with PageMaker

Networking with Windows NT

Bookkeeping and Accounting

Mastering Microsoft Office

Multimedia Programming

Name _____ (please print)

Age _____

Address _____

City _____

State _____

Zip _____

A Division of The McGraw-Hill Companies

Accredited Member, Distance Education and Training Council

0018-0598

MANUFACTURERS

ADCOM

10 Timber Lane
Marlboro, NJ 07746
Tel: 732-390-1130
Web: www.adcom.com

AUDIO DESIGN ASSOCIATES (ADA)

602-610 Mamaroneck Avenue
White Plains, NY 10605
Tel: 914-946-9595
Web: www.ada-usa.com

BOSTON ACOUSTICS

300 Jubilee Drive
P.O. Box 6015
Peabody, MA 01961-6015
Tel: 978-538-5000
Web: www.bostonacoustics.com

CONSUMER ELECTRONICS MANUFACTURERS ASSOCIATION (CEMA)

2500 Wilson Boulevard
Arlington, VA 22201-3834
Tel: 703-907-7674
Fax: 703-907-7690
Web: www.eia.org/cema

DENON ELECTRONICS

222 New Road
Parsippany, NJ 07054
Tel: 973-575-7810
Web: www.denon.com

DIREC TV, INC.

2230 East Imperial Highway
El Segundo, CA 90245
Tel: 310-726-4656
Web: www.directv.com

DOLBY LABORATORIES LICENSING CORP.

100 Potrero Avenue
San Francisco, CA 94103-4813
Tel: 415-558-0200
Web: www.dolby.com

ECHOSTAR COMMUNICATIONS CORPORATION

90 Inverness Circle East
P.O. Box 6552
Englewood, CO 80155
Tel: 303-799-8222
Web: www.dishnetwork.com

FISHER

21604 Plummer Street
Chatsworth, CA 91311
Tel: 818-998-7322
Web: www.audvidfisher.com

FUJITSU GENERAL AMERICA, INC.

353 Route 46W
Fairfield, NJ 07004
Tel: 888-888-3424
Web: www.plasmavision.com

HITACHI HOME ELECTRONICS (AMERICA)

3890 Steve Reynolds Blvd.
Norcross, GA 30093
Tel: 770-279-5600
Web: www.hitachi-ce.com

JAMO HI-FI USA, INC.

1177 Corporate Grove Drive
Buffalo Grove, IL 60089
Tel: 847-465-0005
Web: www.jamospeakers.com

JVC COMPANY OF AMERICA

41 Slater Drive
Elmwood Park, NJ 07407
Tel: 201-794-3900
Fax: 201-523-3601
Web: www.jvc.com

LEXICON, INC.

3 Oak Park Street
Bedford, MA 01730-1141
Tel: 781-280-0300
Web: www.lexicon.com

LUCASFILM LTD, THX DIVISION

P.O. BOX 10327
San Rafael, CA 94912
Tel: 415-492-3900
Web: www.thx.com

MADRIGAL AUDIO LABORATORIES

2081 South Main Street
Middletown, CT 06457-0781
Tel: 860-346-0896
Web: www.madrigal.com

MARANTZ AMERICA INC.

440 Medinah Road
Roselle, IL 60172-2330
Tel: 630-307-3100
Web: www.marantzamerica.com

MCINTOSH SALES CORPORATION

661 West Redondo Beach Blvd.
Gardena, CA 90247-4201
Tel: 888-979-3737
Web: www.mcintoshlabs.com

MERIDIAN AUDIO

3800 Camp Creek Parkway
Building 2400, Suite 122
Atlanta, GA 30331
Tel: 404-344-7111
Web: www.meridian-audio.com

MITSUBISHI ELECTRIC AMERICA

5665 Plaza Drive
Cypress, CA 90630
Tel: 800-823-6372
Web: www.mitsubishi-tv.com

PANASONIC CONSUMER ELECTRONICS COMPANY

One Panasonic Way
Secaucus, NJ 07094-2999
Tel: 201-348-7000
Web: www.panasonic.com/pcec

PHILIPS ELECTRONICS, N.V.

64 Perimeter Center East
Atlanta, GA 30346-6401
Tel: 770-821-2400
Web: www.philipsmagnavox.com

PHILIPS TRIMEDIA

811 East Arques Avenue
Sunnyvale, CA 94088
Tel: 408-991-2646
Web: www.semiconductors.philips.com

PIONEER ELECTRONICS (U.S.A.) INC.

2265 East 220th Street
Long Beach, CA 90810-1639
Tel: 310-952-2260
Web: www.pioneerelectronics.com

RUNCO INTERNATIONAL

2463 Tripaldi Way
Hayward, CA 94545
Tel: 510-293-9154
Web: www.runco.com

SAMSUNG ELECTRONICS AMERICA, INC.

105 Challenger Road
Ridgefield Park, NJ 07660
Tel: 201-229-4000
Web: www.sosimple.com

SHARP ELECTRONICS CORPORATION

Sharp Plaza
Mahwah, NJ 07430
Tel: 201-529-8200
Web: www.sharp-usa.com

SHERWOOD AMERICA

14830 Alondra Blvd.
La Mirada, CA 90638
Tel: 714-521-6100
Web: www.sherwoodusa.com

SONANCE

961 Calle Negocio
San Clemente, CA 92673
Tel: 714-492-7777
Web: www.sonance.com

SONY ELECTRONICS INC.

One Sony Drive
Park Ridge, NJ 07656-8003
Tel: 201-930-1000
Web: www.sony.com

TECHNICS (see PANASONIC)

THOMSON CONSUMER ELECTRONICS

10330 North Meridian Street
INH-310
Indianapolis, IN 46290
Tel: 317-587-3000
Web: www.rca-electronics.com

UNITY MOTION

1201 Crooked Creek Drive
St. Charles, MO 63304
Tel: 314-447-0524
Web: www.unitymotion.com

ZENITH ELECTRONICS CORPORATION

1000 Milwaukee Avenue
Glenview, IL 60025
Tel: 847-391-7000
Web: www.zenith.com

try puts its public awareness campaigns into full swing.

VIDEO HANG-UPS

Another one of those technologies that the industry has been promising for decades now is a television that is flat enough to hang on the wall like a picture. Well, they're here. Flat-screen TVs were hanging from the walls at booths all around ICES 98. The good news is: They look really great—wide screen, slim profile, very high “cool” factor. The bad news is: The picture quality still ranges from so-so to very good (with high-definition feeds), and the price is still sky high.



A sampling of some of the MD products Sony is rolling out in 1998, which it has dubbed “the year of the MiniDisc.”

Basically, a plasma set uses a layer of fluorescent gas sandwiched between two thin glass panels in which rows and columns of electrodes are embedded. When a relative low-voltage is applied to the electrodes, the pixels at their junctions emit light, the color of which is determined by which phosphor pigment (red, green, or blue) is being addressed. The result is a very flat array of individually addressable pixels, providing for precise image control. The depth requirements of a traditional cathode-ray tube or CRT—with its electron gun and large, heavy glass envelope required to contain a high vacuum—are eliminated. Thus, plasma sets can use much thinner, lighter, flatter screens. That, combined with the fact that light is evenly distributed all over the entire screen, allows the flat TVs to be viewed from angles of up to 180 degrees.

Various manufacturers are involved in the development of a number of different gas plasma technologies. A hybrid technology known as PALC, (for plasma-addressed liquid crystal) was developed originally by Tektronix and has been licensed by Sony, Sharp, and Philips. Those companies are now striving to create a flat-screen display that will be less expensive to produce than similar plasma or thin-film transistor (TFT) LCD monitors while offering better picture quality.

It was difficult to turn around on the



Sharp's MD-X8 minisystem lets you download audio from the Internet and record it to a MiniDisc. An optional digital sound card is required for connection to a PC or laptop, which can then be used to control the music system and to edit and title discs and tracks.

show floor without encountering flat-screen TV. Mitsubishi, Fujitsu, Hitachi, JVC, Thomson, Sony, Philips, Panasonic, Sharp, Samsung, and Pioneer were all showing them, although not all of the demo models are currently available to the public or even have definite marketing plans.

Fujitsu, the first company to sell plasma displays in the U.S., unveiled its second-generation Plasmavision 42 at ICES 98. It offers a 400:1 contrast ratio (the original model was only 70:1), component video input, SVGA compatibility, 42-inch-wide screen (diagonal) and is less than 6 inches deep. Its suggested list price is \$10,999.

Test marketing of Mitsubishi's DiamondPanel Television began last Christmas. Two dealers in Los Angeles were offering the 40-inch-wide, 4-inch thick, flat-panel plasma-display TVs (a wall-mount and a table-mount)—the first to be marketed in the U.S.—for about \$10,000 apiece. A separate control unit functions as the TV tuner, input selector, and audio amplifier. At ICES, Mitsubishi displayed a 46-inch DiamondPanel DTV-ready television, which will be ready in the second half of 1998.

Philips' 42-inch widescreen FlatTV Plasma television is 4.5-inches thick and has a 160-degree viewing angle. It offers video and data display capability and a complete Dolby Pro Logic surround-sound system with nine speakers built into a frame around the display (a stand-alone subwoofer and rear speakers are also included). Compatible with NTSC, PAL, and SECAM standards, the FlatTV is HDTV-ready with the addition of a set-top converter box. The electronics, power supply, and connectors are housed in a separate TV receiver. The complete system is

slated for delivery early this year, with a suggested retail price of \$14,999.

Thomson's prototype plasma TV has a depth of just 4-inches. Intended for both home-theater and conference-room use, the set is scheduled to reach dealers in time for Christmas 1998, with prices to be announced.

Sharp displayed a 42-inch PALC-based set, which the company hopes to market this fall, followed by a high-definition version by the end of 1999. Sony, which is already selling PALC-based Plasmatrons in Japan, took a different route at ICES 98, introducing the “Wega” (pronounced “Vega”) Trinitron, a flat-screen tube-based set. It uses the FD Trinitron tube, which is flat both horizontally and vertically for



Philips Audio CD Recorder, which premiered in “select” audio shops last fall, will be available through mainstream retailers this year at a suggested retail price of \$649.

“minimal glare and virtually no distortion.” A larger deflection yoke and longer electron gun than those found in previous Trinitron sets promise precise corner-to-corner focus. Wega also uses two new Sony technologies: Direct Reality Creation, said to “effectively double a picture's horizontal and vertical resolution,” and Multi Image Driver, which converts most standard video source signals to a



The DR-700 CD-R/CD-RW recorder from Marantz offers direct-to-digital and analog dubbing capabilities on record-once and re-writeable CDs.



The first Dolby Digital-equipped audio minisystem is Sharp's CD-C492, with 240-watt amp, three-disc CD changer, AM/FM digital tuner, double cassette deck, and six speakers.

higher resolution level.

Cool as they might look, don't expect plasma sets to make any inroads on traditional CRT and projection sets in the next few years.

THE HEAR AND NOW

Meanwhile, back in the real world, several new and not-so-new technologies are being refined and even redefined. Hot audio technologies include recordable digital audio and a slew of home-theater audio solutions.

DIGITAL RECORDING OPTIONS

Sony has declared 1998 "the year of the MiniDisc"—which basically means it's spending big bucks to promote a format that has, so far, been less than a roaring market success in the U.S. We've always liked the format for its sound quality, portability, and, of course, recordability. So have consumers in Japan and Europe. But, other than a prototype of a computer-based CD-to-MD recording/editing system, Sony displayed revamped and expanded lines of the basic home, car, and portable models.

Sharp, on the other hand, was showing (and is currently selling) a truly innovative (and is currently selling) a truly innovative 18 MD product. Its MD-X8 minisystem

allows users to digitally download and store audio from the Internet to a MiniDisc. Record companies and music services offer music on their home pages, and more than 40,000 Web sites broadcast Real Audio and Webcasts. You can find simulcast concerts, college sporting events, and recording samples of signed and unsigned bands on the Internet. The MD-X8 connects to a computer through an optional PCMCIA adapter. Once connected, the PC or laptop can be used to control many of the minisystem's functions, and to edit and title tracks using the computer keyboard. The system can also record music from other digital sources, such as DSS, Digital-Audio Tape (DAT), and, of course, CDs. The MD-X8, with three-disc CD changer, AM/FM digital tuner with 40 presets, front-loading MD player/recorder, and 80 watts of total power, has a suggested retail price of \$899.95. The Digital Sound Card with cable costs \$299.95.

One of the reasons that consumers have been reluctant to buy MiniDisc products is their unwillingness to begin collecting another whole set of hardware and software—car, home, and portable tape decks, CD players, and MD recorder/players. Now, however, it's possible to record your own CDs and play them back, with no loss of quality, on the equipment you already own. CD-Recordable (CD-R) recorders are still scarce, but they're out there, as are

CD-ReWritable (CD-RW) devices.

Although they offer CD-quality sound, in contrast with MiniDisc's "near-CD quality," CD-RWs can't match the editing or playback capabilities of MDs. For example, you can only re-write the last track on the disc—to replace an earlier track, you have to also erase all the tracks that follow it on the disc. Worse yet, because of CD-RW discs' low reflectivity, they can't be played back on most conventional CD players. (CD-Rs don't have that problem.)

Starting next year, Philips plans to redesign its whole line of CD players so that they will be MultiRead-compatible and will play CD-RWs. Pioneer's new DVD players also will play back CD-RWs (and presumably other manufacturers will follow suit). So, if you really want to buy a CD-RW recorder now, you can use it to record CD-Rs until you are ready to buy, and the manufacturers to sell, a new CD or DVD player that is compatible with CD-RW media. Finally, consumer audio CD-RW machines (but not PC CD-RW drives) require the use of special "consumer" blank discs that are more expensive because their cost includes a royalty payment. They also contain some anti-piracy features to prevent digital bootlegging.

Philips' Audio CD-Recorder, which has been available since last fall, allows you to make your own CD mixes, is compatible with both CD-R and CD-RW media, and has a suggested price of \$649. Philips also exhibited its OMNIwriter/12 CD-ReWritable storage solution at ICES 98. The PC peripheral device allows users to read, write, and rewrite their CDs, and also can be used for true backup of large-capacity media. OMNI/12 can create CD-R and CD-RW audio discs, and can read CD-ROMs. CD-RW media can be read by DVD-ROM drives and can record DVD readable discs. The OMNI/12 has a suggested list price of \$499.

Pioneer, which has been selling CD-R recorders for the last four years, introduced the PD-R55RW re-writeable CD recorder at ICES. The unit features a sampling frequency converter for easy digital-to-digital recording of non-CD sources, such as MD, Digital-Compact Cassette (DCC), and DAT, and track-by-track digital synchronization. When recording from analog sources, an automatic level control system maintains a steady input level. The PD-R55RW is expected to be available this summer.

Marantz also introduced a CD-R/CD-RW deck. The DR-700 CD recorder automatically converts digital audio recorded at

different sampling rates to the 16-bit, 44.1 kHz CD standard when transferring data to disc. Optical and coaxial digital inputs and outputs are provided, as are analog connections for recording tapes or LPs. The DR-700 will ship in mid-1998; prices have yet to be announced.

HOME THEATER— SOUNDING GOOD!

Other audio news at ICES revolved around home-theater sound: Dolby Digital, THX, DTS, and Virtual Dolby.

The big news in 5.1-channel Dolby Digital is price drops. Sherwood, for instance, plans to have a \$399 Dolby Digital receiver on the market in late summer. Several other companies have models with expected street prices of less than \$450. Sharp displayed the first Dolby Digital mini-system. The CD-C492 features a 240-watt amplifier, a three-disc CD carousel changer, AM/FM digital tuner, double cassette deck, and six speakers. It will be available in May with a suggested retail price of \$699.95. Dolby Digital-



Technics' SH-AC500D can decode both Dolby Digital- and DTS-encoded source materials for playback through an audio system with 5.1 discrete channels.

ready receivers were also seen in abundance, with street prices as low as \$199.

DTS, or Digital Theater System, is making some inroads in the home-theater market. DTS delivers six channels of master-quality audio. The DTS algorithm encodes six channels of 20-bit digital audio information into the space previously allotted for only two channels of 16-bit linear PCM. Then, during playback, the DTS decoder reconstructs the original six channels of 20-bit digital audio, said to be audibly superior to a CD's 16-bit linear PCM audio.

Dolby Digital is a standard audio type in the DVD-Video format, which means that all DVD players are DD-ready (although not all of them feature on-board Dolby Digital decoders, and not all DVD discs feature Dolby Digital soundtracks). DTS, on the other hand, is an option that is available to the developers of DVD discs.

Technics unveiled its SH-AC500D DTS/Dolby Digital Decoder, which, when connected to a DTS-ready source and an

audio system with 5.1 discrete channels (left, center, right, left surround, right surround, and subwoofer), will deliver six channels of "sonic excellence" from any DTS-encoded DVD, Laser Disc (LD), or CD. A DD-ready sound system and a DD-encoded source are required to hear Dolby Digital material. The DTS/DD decoder will be available in May with a suggested retail price of \$399.99.

Meanwhile, the first DTS-capable DVD players were introduced at ICES 98. The DVD-890 from Marantz, for instance, can handle both Dolby Digital 5.1-channel soundtracks and six-channel DTS-encoded DVD, when the player is hooked up to a DD- and/or DTS-equipped receiver. (The first DTS-encoded DVDs are currently becoming available.) The DVD-890, with a suggested price of \$699.99, will be shipping in the second quarter of 1998.


Also unveiled at ICES 98 were a variety of THX-certified Dolby Digital/DTS products—and Dolby Digital and DTS are credited with spurring the awareness, acceptance, and even sales of Home THX products. "As more and more Dolby Digital and DTS products come to market, it's interesting—and encouraging—to see that a growing proportion of those products are part of the Home THX Program," noted Marc Spector, director of marketing for the THX Division of Lucasfilm Ltd. "It certainly seems that manufacturers are responding to the growing sophistication of the home-theater market by further enhancing the sophistication of their products with THX Certification."

A small sampling of the new THX-certified products include DVD players from Denon, Meridian, Pioneer, and Runco, which showed a 200-disc DVD changer with PC-based controller; Dolby Digital/DTS-capable system controllers from Adcom, Audio Design Associates (ADA), Lexicon, Madrigal, McIntosh, and Meridian; an integrated Dolby Digital home theater system from Denmark-based Jamo, which includes six active speakers and a digital controller; and in-wall speakers from the newest THX licensee, Sonance.

In related news, Lucasfilm announced its intentions to introduce later this year a new set of THX certification standards that could be applied to mid-priced audio products. Spector said that the new standards, still in the development phase, might have a different logo than that carried by standard THX-certified products.

What if you want the home-theater experience without the fuss, the muss—or the alphabet soup? Two companies dis-

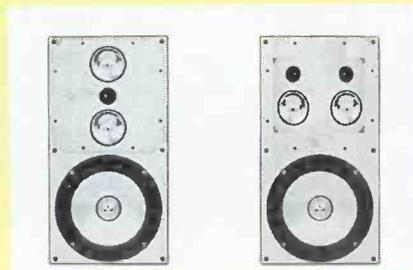played "simple solutions" to home theater. Boston Acoustics' SoundBar Cinema places three speakers (right, left, and center) in a rectangular set-top box that also contains amplification, equalization, a Dolby Pro Logic Decoder, and Q-Sound processing, which widens the front image. A single separate speaker handles the surround channel. The SoundBar Cinema,



Sonance has joined the roster of THX licensees and is offering a pair of THX-certified in-wall home-theater speaker systems featuring polypropylene and aluminum cone drivers, plus a directable midrange tweeter assembly.

with preprogrammed remote control, is available at a suggested list price of \$799.

Each of the two initial offerings in Pioneer's SimpleSolution HTV Series consists of a single slim-line unit that sits atop a TV and uses Virtual Dolby to create the illusion that specific sounds come from any point surrounding the listener. The main unit contains two high-power amplifiers that power two full-range speakers and a subwoofer. The HTV-1, with a 30-watt-per-channel amplifier and a 60-watt amp for the subwoofer, and a preset remote control, will be available in June with a suggested price of \$429. The 40/120-watt HTV-2, with learning remote, will be available in September with a suggested price of \$499.

DVD-AUDIO

During the 1998 ICES, the DVD WG-4 Audio Working Group announced that it had released a draft of its DVD audio specifications to DVD Consortium members, major music industry associations, the Recording Industry Association of America (RIAA), the Recording Industry Association of Japan, the International Federation of the Phonographic Industry, and WG-4 members. The Group hopes that feedback from those associations will help shape the final specifications for the DVD-Audio format, which will have to address copy-protection issues in a manner that is acceptable to the recording industry



You can enjoy DVD video on-the-go with Panasonic's DVD-L1 portable DVD player with built-in 5.8-inch widescreen LCD monitor.



Sharp's small-footprint DVD player is designed to go with the company's Dolby Digital minisystem.

as well as consumers.

WG-4's goal is to "create the music industry's next-generation format using the superior disc storage capacity of DVD." In contrast to the current DVD format, the audio specifications utilize the disc capacity by emphasizing improved next-generation digital sound quality rather than the playback of 135 minutes of video. When the specifications are finalized, DVD Audio will join DVD Video and DVD ROM as a "compatible family of formats."

DVD AND DIVX NEWS

DVD video hardware and software have been selling quite well for a new product category, although sales have not been as brisk as manufacturers had initially hoped. From last March, when they were introduced, through the end of 1997, manufacturers shipped more than 300,000 DVD players. It is estimated that 40% to 45% of those units were actually purchased, which means that about 125,000 U.S. households now have DVD players. For comparison's sake, 35,000 CD players sold in 1983, the first year they were on the market; VCRs were introduced in 1975 and the 200,000th unit sold in 1977.

At least a dozen manufacturers were exhibiting DVD players at ICES 98. Most showed second-generation units, although there were some new players in the DVD field, including Hitachi and Sharp. Some of the latest DVD players feature DTS-compatibility, others add virtual surround-sound enhancements to two-channel audio, and several offer component video

outputs. There are also a couple of new DVD product categories: portables and changers.

Panasonic's DVD-L1 is a portable DVD player with a 5.8-inch widescreen LCD and built-in stereo speakers. It offers 10-bit video DAC and 96 kHz/24-bit DAC for linear PCM audio. Its rechargeable battery provides two hours of play time, and an included AC adapter allows it to be used as a home DVD player as well. Available this spring, the DVD-L1 has a suggested retail price of \$1299.

Samsung calls its P-Theater "the world's smallest portable DVD player." We won't argue with that, considering it weighs in at two pounds and measures approximately 8 × 6½ × 2 inches. Resembling a portable CD player, the P-Theater comes with a headset viewer, similar to virtual-reality goggles, that is said to create the sensation of looking at a 40- to 70-inch screen. The P-Theater will ship later this year; no price has been announced.

Sharp's DVD-550 is not portable, but it is smaller than most. Designed as a companion piece to the company's Dolby Digital minisystem, mentioned above, it has a 270mm-wide footprint. The player has a built-in Dolby Digital decoder, and component-video and digital optical outputs. It will be available this spring at a suggested price of \$749.

At the show, Runco debuted its THX-certified SAR-200, a 200-disc DVD changer that comes with the Runco Theater Manager, a single-zone controller for home multimedia systems. Compatible

with CDs as well as DVDs, the SAR-200 is currently available at a suggested retail price of \$14,995. A 60-disc DVD changer from Fisher will ship to the professional and institutional markets this fall, at a price that has yet to be announced.

Also making news—and waves—at ICES 98 was Digital Video Express, a.k.a. Divx. The company was at the show promoting its pay-per-view version of DVD, which is backed by Circuit City. Divx displayed prototypes in a nearby hotel suite, and manufacturers including Zenith, Panasonic, and Thomson announced plans to sell Divx players this year.

Divx DVD players are compatible with all DVD titles and CD audio discs, but Divx discs won't play on today's "open" DVD players. Divx movies will be available as rentals, costing between \$5 and \$7 for a 48-hour period, during which time they can be watched as often as you like. After that, you can keep the disc. But if you want to watch it again, you must pay for each additional 48-hour viewing period. An on-screen menu and on-board modem will allow you to order more time, and view your billing record, and will allow the authorization center to "unlock" the disk.

Said Divx chairman Richard Sharp, who is also the chairman of Circuit City, "Divx is a feature and not a format. A Divx player starts as a fully functioning DVD player, and adds this capability to it." It allows the consumer to "watch movies at home in a substantially different model," he added.


IT'S A WRAP!

All this talk of new technologies barely scratches the surface of the Consumer Electronics Show. Computers, communications, home-office products, accessories, mobile electronics, home theater, camcorders, and much more are all represented at the show. For a glimpse at the "best of the rest," see next month's Innovations '98 Wish List round-up. ■

A BEGINNER'S GUIDE TO RADIO PROPAGATION

How do radio waves get from here to there? In this article we will present some of the basic principles of RF propagation and give pointers on how you can use this information as a radio amateur or SWL.

KARL T. THURBER, W8FX

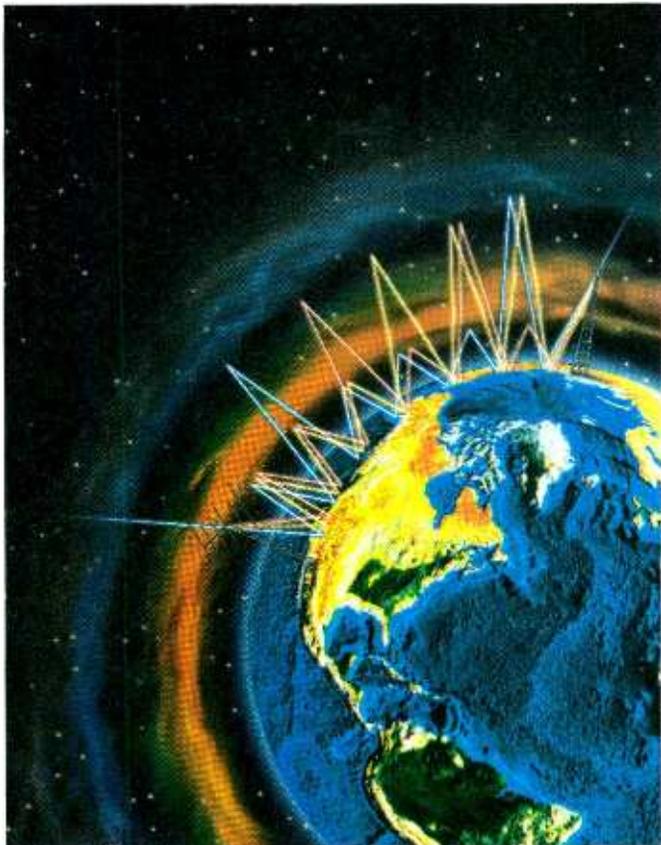

Have you ever wondered why a signal generated several hundred or thousand miles away reaches your location without the aid of connecting wires? After reading this article you should have a pretty good understanding of how and why this is possible. In addition to discussing basic radio propagation principles and techniques, we will also cover the electromagnetic spectrum; the nature of radio waves; the regions of the Earth's atmosphere; sunspots and how the sun affects propagation; radio propagation modes and parameters; VHF and UHF propagation modes; using propagation charts and making forecasts; the role of personal computers (PCs) in forecasting; and sources of solar, geomagnetic, and propagation indices and data. Before we get into propagation details, let's start with what constitutes the electromagnetic spectrum.

The Electromagnetic Spectrum.

The radio spectrum extends from a frequency of a few hertz (Hz), or 10^8 meters in wavelength, to about 300 gigahertz (GHz), or 1 mm (10^{-3} m).

That is but a small part of the total electromagnetic spectrum, which extends to about 1 attometer (10^{-18} m), or a wavelength of one-quintillionth of a meter. Figure 1 shows the total electromagnetic spectrum in terms of increasing wavelength (or decreasing frequency).

Frequency-wise, those frequencies in the lowest portion of the spectrum (ranging from zero to 3 Hz) are known as ultra-low frequencies (ULF). Just above ULF lies another band called extremely low frequencies (ELF), which cover a range of 3 Hz to 3 kHz. Above that grouping, ranging from 3 kHz to 30 kHz, is the very low-frequency (VLF) range. Next are the low frequencies (LF), from 30 kHz to 300 kHz. The medium frequencies (MF) extend from 300 kHz to 3000 kHz (3 MHz).

From 3 MHz to 30 MHz are the high frequencies (HF). Above HF are the very high frequencies (VHF), from 30 MHz to 300 MHz. The ultra-high frequencies (UHF) extend from 300 to 3000 MHz, or 3 GHz. From 3 GHz to 30 GHz are the super high frequencies (SHF), and from 30 GHz to 300 GHz, the extremely high frequencies (EHF).

In this article, we'll be concerned with but a small portion of the total electromagnetic spectrum—covering long wave (LF) through the AM broadcast band and medium wave (MF), shortwave, VHF and UHF, and the microwave frequencies (low end starts at about 1 GHz).

The Fundamental Nature of Radio Waves. Radio communication is accomplished via electromagnetic waves, which travel through the Earth's atmosphere. Like light, radio waves are propagated as electromagnetic radiant energy.

Reflection, refraction, and diffraction, or some mix thereof, play an important role in radio-wave propagation. Reflection can occur at any boundary between materials with a different dielectric (non-conducting) constant. Radio waves can be reflected by ionized atmospheric layers, buildings, air mass boundaries, water, or the ground. Atmospheric reflection plays a large part in communication. Without an atmosphere, such as on the Moon or on other planets, we would not be able to enjoy the type of radio propagation we currently experience.

Refraction—the bending of radio waves as they pass at an angle from one medium to another—is common at boundaries between air masses; it is particularly noticeable at VHF, UHF, and microwave frequencies.

The term diffraction refers to the irregular spreading of waves due to interference of one part of the wave with another part. It also describes a change in the direction and intensity of radio waves as they pass by an obstacle or aperture. Diffraction is related to scattering—a “disordered” change in the direction of propagation when waves encounter matter, something like what happens when light tries to penetrate fog.

A practical way to classify radio waves is by propagation: ionospheric, tropospheric, or ground waves. Ionospheric waves (also known as sky waves) make up most of the transmitted electromagnetic radiation. HF radio waves are propagated as sky waves or ground waves, or a combination of both modes. Sky waves reflected from the ionosphere can traverse great distances, and enable global communication. Ground wave refers to signals that travel close to the Earth (though not necessarily touching it) and do not leave the lower atmosphere. Ground waves, which can include waves that follow the Earth’s curvature by bending in the lower atmosphere or troposphere—a propagation form known as tropospheric bending—are not very

useful for long-distance communication because they are greatly attenuated if they travel more than few dozen miles.

The term surface wave often is considered synonymous with ground wave, but, strictly speaking, the surface wave is a wave that travels in contact with the Earth’s surface. Because of high attenuation, its propagation range is limited to about 100 miles or so, depending on wavelength and several other factors. Since attenuation increases with frequency, surface waves are of little value on HF. Such waves are most useful for low- and medium-frequency transmissions, such as the standard AM broadcast band.

The Earth’s Lower Atmosphere.

The Earth’s atmosphere is the body of air surrounding the Earth, reaching elevations of more than about 500 statute miles. The atmosphere is divided into several regions or layers—the troposphere, stratosphere, and ionosphere. (There are other layers, but those listed are the ones with which we are most concerned.) Beyond the ionosphere lies the magnetosphere, as shown in Fig. 2. (All distances and distance conversions listed are approximate.) For the moment, we will concern ourselves with only the two lowest regions; the troposphere and the stratosphere.

The troposphere—which lies between the surface of the Earth and the tropopause (the region that separates the troposphere

from the stratosphere and varies in height from about 5 miles at the poles to 11 miles at the equator)—is the lowest layer of the atmosphere. The troposphere plays a major role in VHF and higher frequency propagation. Immediately above the troposphere lies the stratosphere, a relatively calm region of the atmosphere that is located from about 5–30 miles above the Earth’s surface. The stratosphere shows little temperature change throughout its height. About 99 percent of all atmospheric gases are found within the troposphere and the stratosphere.

The Upper Atmosphere.

The ionosphere is divided into three major regions or layers: D, E, and F, in order of increasing altitude and electron density. Each layer plays a distinct role in ionospheric propagation, and each reflects or refracts radio waves depending upon the frequency and angle of arrival of the incident energy. The two lower layers of the ionosphere, the D and E regions, are absorbing layers, while the F layers are reflecting layers. The D layer—whose electron density is under direct solar control and in proportion to the sun’s height or zenith angle—forms at from 30 to 55 miles above the Earth in daylight. The D layer peaks at about noon and mostly dissipates after sunset; it is also higher in summer than in winter. The D layer absorbs energy at the low end of the HF spectrum. The signal-strength reduction can be considerable.

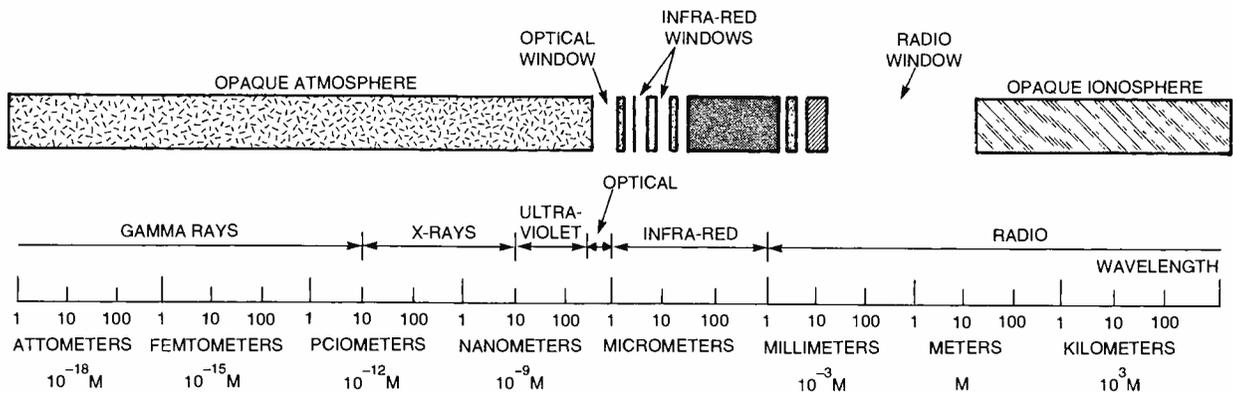


Fig. 1. The electromagnetic spectrum is an array of radiant energies. In order of increasing wavelength (smallest to longest) or decreasing frequency (highest to lowest), the types of electromagnetic radiation are gamma radiation, x-rays, ultraviolet radiation, visible light, infrared radiation, microwaves, and radio waves. The illustration shows the total spectrum in terms of wavelength and depicts the atmosphere’s relative transparency—very important in understanding propagation concepts.

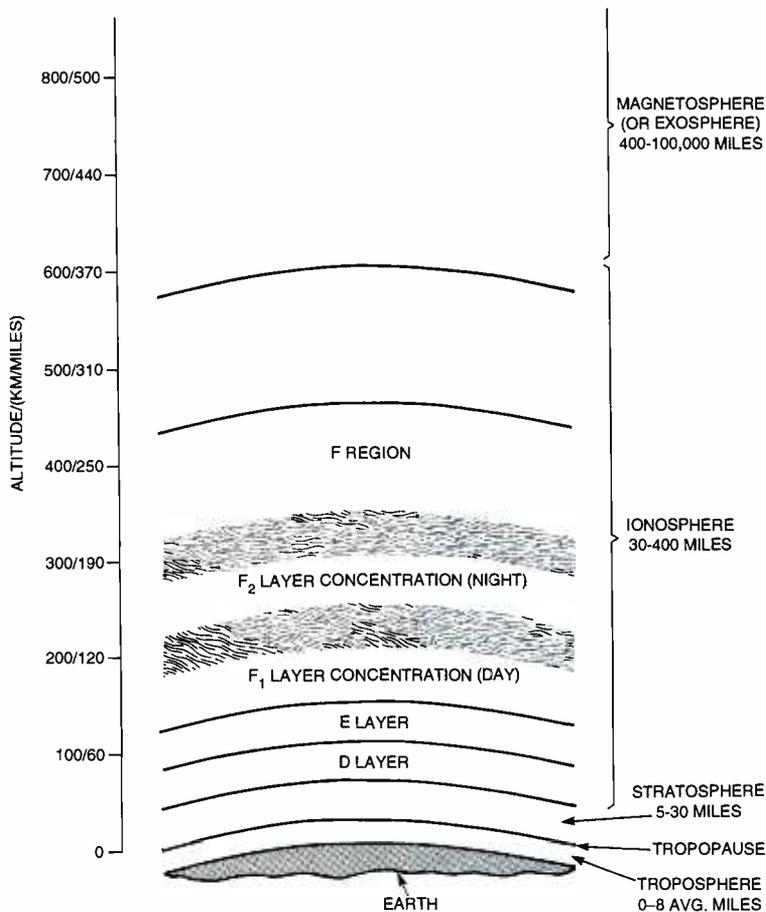


Fig. 2. Depicted here are the major regions of the Earth's atmosphere—ranging from the troposphere (the lowest region) through the stratosphere, ionosphere, and magnetosphere.

especially during daytime.

The E layer—the lowest layer that can refract HF signals—develops during the day at between about 60 to 70 miles above the Earth. It, too, is under strong solar control, with its ionization density reaching its maximum after noon and falling to a low nighttime level after sunset. However, the E layer does not completely disappear at night. The E layer has daily and seasonal variations that are similar to those exhibited by the D layer. Signals can propagate between two points via the E layer, as they do via the F layers. However, the maximum ground distance in one E-layer hop is only about 1200-1300 miles. Thus, more hops are usually required on DX paths. The DX, or long-distance HF communication, often is the result of both the F and E layers getting into the act in a variety of "mixed" propagation modes.

At elevations ranging between about 130 and 260 miles above the

Earth's surface, the F layer is the highest ionospheric region. Long-distance HF communication is most influenced by F-layer ionization. In the daytime, the F layer splits into two parts: F₁ (at roughly 140 miles), and F₂ (at about 200 miles). At night and during the wintertime, the F₁ and F₂ layers recombine into a single F layer.

The F₁ layer, like the E layer, is under strong solar control and reaches maximum ionization about an hour after noon. When the F₁ region exists as a separate layer, its propagational effects are similar to those of the E layer. The F₂ layer is the highest layer. It usually has the highest electron density and is of great value in HF ionospheric propagation, but it is characterized by much variability. The height of the F₂ layer and its density depend on a variety of factors, including local time, season, sunspot cycle, latitude, and longitude. The maximum electron density of the F₂ layer usually occurs well

after noon, sometimes even in the evening. The layer decays slowly at night. At mid-latitudes, the height of maximum electron density is higher at night than in the daytime, while at equatorial latitudes, the opposite occurs. The maximum Earth distance of one F₂ layer hop is about 2500 miles, readily enabling global communication via multiple hops.

While we're most concerned with the ionosphere, let us not forget what lies beyond—the magnetosphere, at roughly 400 to 100,000 miles above the Earth. This shell is an asymmetrical magnetic envelope which shelters the Earth from solar wind (a stream of ionized particles ejected from the Sun at high speeds) by deflecting it into space. The ionosphere lies closer to the Earth, but there is considerable coupling (both electric and magnetic) between these two layers.

How The Sun Affects Propagation.

Solar dynamics have everything to do with propagation, just as they have a great deal to do with everything on Earth. The density and nature of the ionosphere is directly dependent on the amount of solar radiation that reaches the Earth. Sunspots are the sun's easiest-observed characteristic. (You may even have seen these dark spots or blemishes that appear periodically in groups on its surface.) They are probably caused by intense, localized magnetic fields trapped below the sun's surface. Sunspots are the source of flares, which are violent solar events that produce a variety of radiation, including high-energy particle cosmic radiation, low-energy particle radiation, and electromagnetic radiation, each of which has an effect on propagation.

Since the earliest days of observing solar activity, our measure of that phenomena has been based on counting sunspots. Radio propagation conditions vary with sunspot number and size, affecting both maximum usable frequency (which is the upper frequency at any given time for which a particular propagation path is possible) and signal absorption (which increases as the ionizing radiation increases). The sunspot number and solar flux are used as indirect

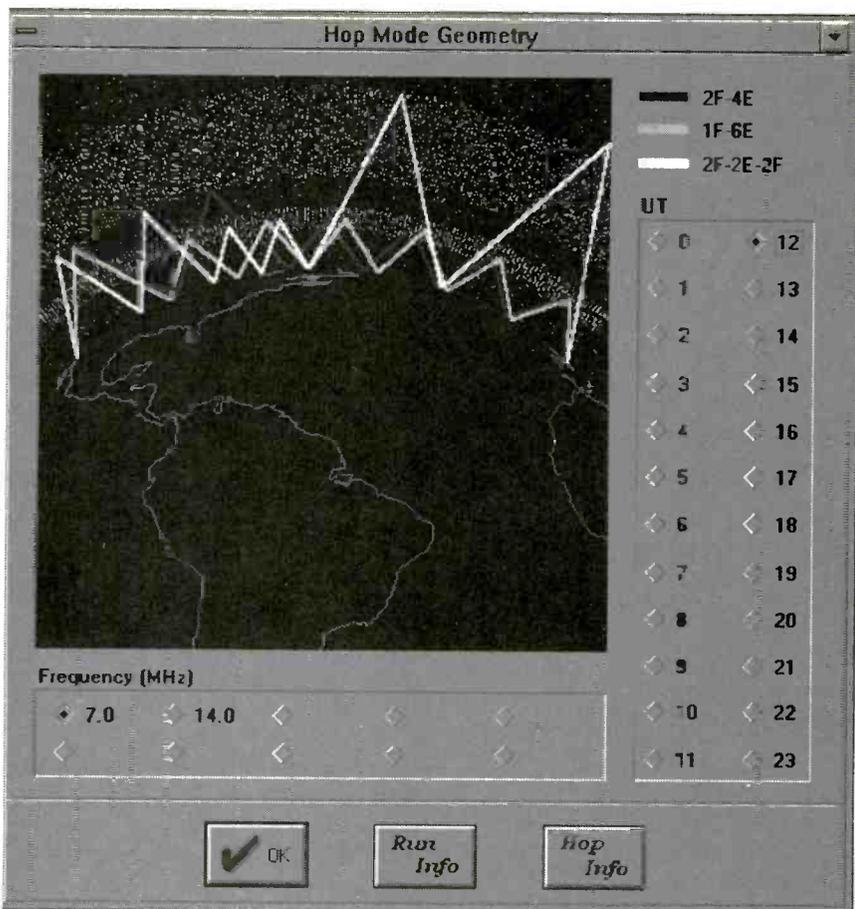


Fig. 3. Pacific-Sierra Research's HFX is a popular Windows HF propagation prediction program. The HFX Hop Mode model generates field strength, mode, availability, and signal-to-noise ratio (S/NR) for a given date, transmitter and receiver pair, frequency, and antenna type. The program displays the data in several formats, including a graphic of sky wave ionospheric hops for each frequency at one-hour intervals, as shown here.

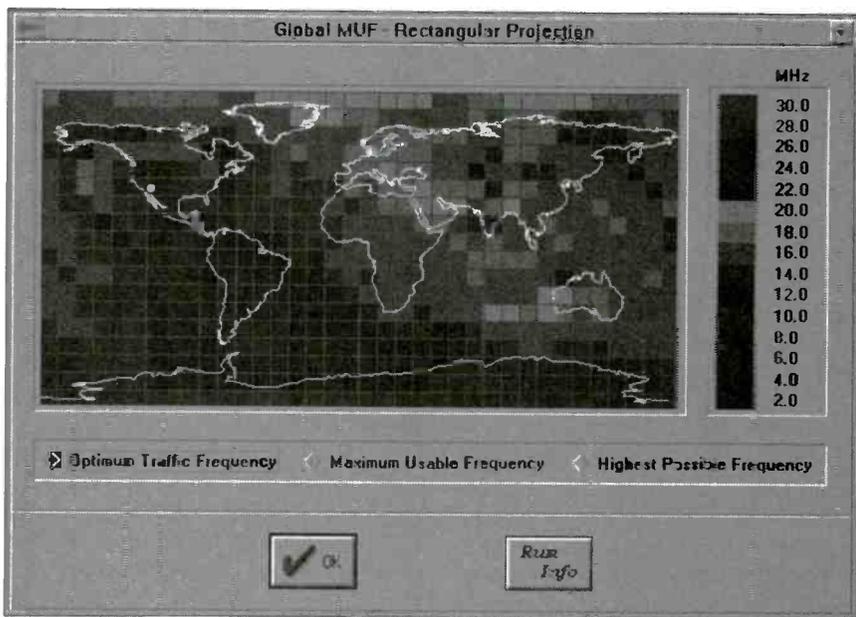


Fig. 4. The HFX Global MUF model generates a color map of Maximum Usable Frequency (MUF), Frequency of Optimum Traffic (FOT), or Highest Possible Frequency (HPF). Using this model, you can determine the best frequencies to reach any part of the world. Global MUF geometry is depicted here on a rectangular projection.

measures of that radiation.

The International Sunspot Number (ISN) is used as an approximation of general solar activity. However, the ISN isn't just a simple count of visual spots, but instead involves a complex formula that takes into account other factors, such as sunspot grouping and size. The variation of ISN falls into well-documented long-term yearly patterns or sunspot cycles. The ISN can vary from near zero at sunspot minima to well over 200 at the peak. Most propagation models and programs require that the sunspot number be specified, while others let you use solar flux. Generally, the 2800 MHz (10.7 cm) solar flux, which varies from about 60 to 300, is considered to be a somewhat more dependable (yet still indirect) measure of radio noise coming from the sun.

Although both sunspot number and solar flux are used as activity measures, there isn't an exact mathematical relationship, especially if daily data is examined. But there is a fairly close correlation between the two if a 12-month running average (smoothed sunspot number, or SSN) for both sunspots and solar flux is used. Episodes of solar activity have a number of terrestrial effects. Ionospheric propagation is susceptible to several kinds of short-term disturbances, which upset the ionospheric electron configuration, thereby affecting propagation. The disturbances weaken signal levels and, in some cases, make them disappear entirely. A sudden ionospheric disturbance or SIDs—which can last from just a few minutes to several hours—or shortwave fadeout (SWF) occurs when x-rays emitted by a solar flare reach the sunlit portion of the D layer, increasing the electron density and absorption rate of that layer.

An event known as Polar Cap Absorption (PCA), caused by high energy protons from large solar flares, occurs as a result of intense ionization of the polar ionosphere. PCAs, which begin about 15 minutes to several hours after protons are ejected from the Sun, may last from about an hour to 60 hours or more. Ionospheric storms are caused by a variety of solar phenomena, such as coronal holes, coronal mass ejections, and solar flares. The storms last

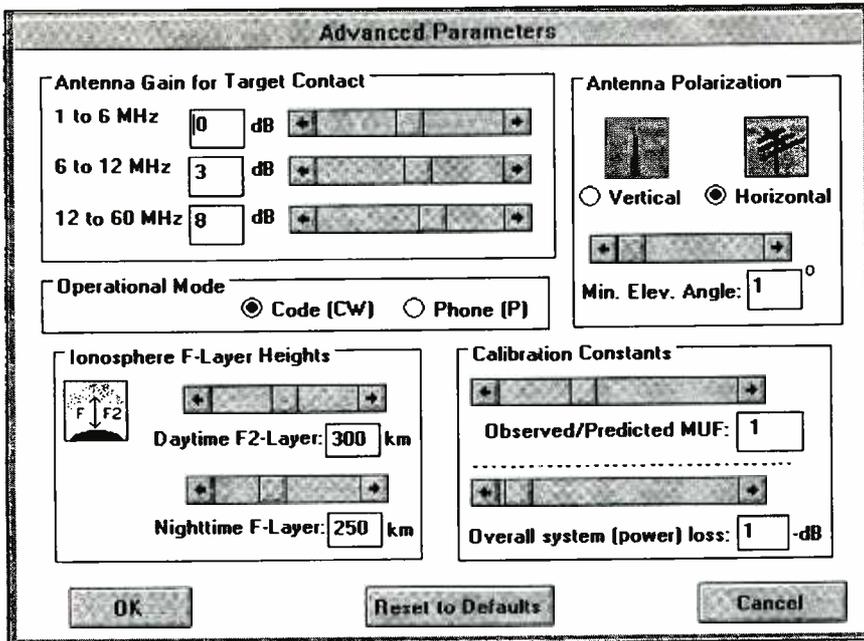


Fig. 5. SKYCOM 2.0, from Fuentz Systems Concepts, Inc., is an easy-to-use Windows program that presents a "quick-look" prediction for "yes-no-maybe" contact possibilities; you can also obtain a detailed report. Shown here is the Advanced Parameters Window, where you can fine tune the program to better reflect prevailing conditions or set up "what if" scenarios.

from a few hours to several days, and some disturbances recur in step with the Sun's 27.5-day rotation on its axis. Although ionospheric storms are difficult to predict, they occur in conjunction with geomagnetic storms, so geomagnetic field disturbances are an indicator of ionospheric disturbances. Severity is indicated by the A and K indices included in the geophysical alert (Geolert) broadcasts from the National Institute of Standards and Technology (NIST) radio stations WWV and WWVH. In general, maximum usable frequencies or MUFs decrease and absorption increases as geomagnetic field activity increases. Ionospheric and magnetic disturbances may be accompanied by visible auroras. Solar radiation is not constant by any means. There are both relatively short- and long-term solar cycles that must be dealt with.

Sunspot Cycles. The first solar cycle is short-term, based on the sun's own approximate 27.5-day rotation period, which can be observed visually by noting the periodic appearance of sunspots on the surface. Generally, sunspots reappear every 27.5 days, so that ionospheric propagation conditions tend to recur with that cycle. Since both

geomagnetic activity and solar flux reflect the rotation period, you can make good short-term predictions for up to about a month in advance.

The number of sunspots reaches a maximum every 11 years (10.7 years to be precise), although the period varies from about 7 to 17 years. Cycle 19, which peaked in 1958, was the highest cycle recorded, with an average SSN of over 200. Experts generally agree that we passed through the trough or low point between Cycle 22 (which began in September 1986) and the current dawning Cycle 23, in mid-1996. Presently sunspots are again beginning their awaited climb, and DX conditions are starting to improve.

Long term predictions, such as deciding when a sunspot cycle has ended and another has begun, or even forecasting next year's conditions, is problematic. Doing so is a complex scientific endeavor that involves a variety of sophisticated techniques, all of which are beyond the scope of this article. Luckily, forecasting the next day's, week's, or month's radio conditions isn't all that difficult. The task has been simplified by easy-to-use propagation charts in popular radio journals, as well as

some excellent computer software developed for that purpose.

High Frequency Communications.

Most long-distance HF communication depends on the bending (refraction) of waves in the ionosphere, which consists of ionized regions caused by the Sun's x-ray and UV radiation. That ionization is intense enough to affect the properties of electromagnetic waves propagated through it. Upon entering the ionosphere, HF waves are refracted in proportion to the layer's ionization and the signal's wavelength. If the ionization is large enough, waves reaching the ionosphere are bent back toward the Earth as if they had been reflected, thereby enabling distant reception. However, there is a maximum frequency, at a given elevation angle, for which a transmitted signal will be refracted back to Earth. Higher frequencies, at the same elevation angle, penetrate this layer and may travel into space.

The highest frequency at which a wave is returned to Earth at vertical incidence (at ninety degrees or zero ground distance) is known as the vertical incidence critical frequency (or simply critical frequency). For communication between two points on Earth, vertical incidence serves no purpose—oblique propagation is necessary, and this method is directly related to the critical frequency. At transmissions above the critical frequency, the steepest angle at which a signal is reflected back to Earth is called the critical angle. Signals transmitted at angles greater than the critical angle pass through the ionosphere and do not return to Earth. Thus, depending on the critical angle and signal frequency, there is some distance beyond which there are no signal return, hence no sky wave. The area between the limit of ground wave range and the innermost edge of signal returned from the ionosphere is called the skip region (also known as the skip zone or dead zone), since sky wave signals simply skip over it.

The length of the skip zone is the skip distance—i.e., the shortest distance that can be reached by a refracted wave at a given frequen-

FOR MORE INFORMATION

Suggested Readings

The ARRL Antenna Book, Eighteenth Edition, 1997. The American Radio Relay League, Inc., Newington, CT.

The ARRL Handbook for Radio Amateurs, Seventy-Fifth Edition, 1998. The American Radio Relay League, Inc., Newington, CT.

The ARRL Operating Manual, Sixth Edition, 1997. The American Radio Relay League, Inc., Newington, CT.

Boithias, Lucien. *Radiowave Propagation*, 1988. McGraw-Hill, Inc., New York.

CQ Amateur Radio Almanac, 1997. CQ Communications, Inc., Hicksville, NY
Davies, K. *Ionospheric Radio*, 1990. Peter Peregrinus, Ltd., London, U.K.

Fiedler, LTC David M. and Ed Farmer, AAZM. *Near Vertical Incidence Skywave Communication*, Worldradio Books, P.O. Box 189490, Sacramento, CA 95818.

Jacobs, George. W3ASK. Theodore J. Cohen. N4XX, and Robert B. Rose. K6GKU. *The NEW Shortwave Propagation Handbook*, 1995. CQ Communications, Inc., Hicksville, NY.

Lee, J.G., W6VAT. *An Introduction to Radio Wave Propagation*, 1991. Bernard Babani Ltd., London, U.K. (distributed by Electronic Technology Today Inc., Box 240, Massapequa Park, NY 11762—reference publication BP293).

McNamara, L. F. *Radio Amateurs Guide to the Ionosphere*, 1994 Melbourne. FL: Krieger Publishing Co.

NIST Special Publication 432, *NIST Time and Frequency Services*. Boulder, CO. Time and Frequency Division, National Institute of Standards and Technology, June 1991.

NISTIR 5042-2, *NIST Time and Frequency Bulletin*. Boulder, CO: Time and Frequency Division, National Institute of Standards and Technology, February 1996 (published monthly).

NOAA Technical Memorandum ERL SEL-80. *A Radio Frequency User's Guide to the Space Environment Services Center Geophysical Alert Broadcasts*. Boulder, CO. Space Environment Laboratory, June 1990.

Pocock, Emil, W3EP. *Beyond Line of Sight: A History of VHF Propagation from the Pages of QST*, 1992. The American Radio Relay League, Inc., Newington, CT.

Thurber, Karl T., Jr. "Long Delayed Echoes: Fact or Fancy?" **Popular Electronics**, August 1995.

Names and Numbers

Here are the names, addresses, and telephone numbers for related products and services. Also included is contact information on several popular propagation prediction software programs (note the several programs with similar names)—information may be subject to change.

Collins Avionics & Communications Division, 350 Collins Road N.E., Cedar Rapids, IA 52498. Tel. 800-321-2223. (*PropMan* program).

Jacques d'Avignon, VE3VIA, 965 Lincoln Drive, Kingston, ON Canada K7M 4Z3. Tel. 613-634-1519. (North American distributor for the ASAPS program developed by IPS Radio and Space Services, P.O. Box 5606, West Chatswood, N.S.W. 2057, Australia).

Engineering Systems, Inc., P.O. Box 939, Vienna, VA 22180. Tel. 703-687-3000. (*Skycom*, DOS-based program).

Fuentez Systems Concepts, Inc., 11781 Lee Jackson Highway, Suite 700, Fairfax, VA 22033. Tel. 800-989-1447. (*SKYCOM 2.0*, Windows-based program).

Kangaroo Tabor Software, Rt. 2, Box 106, Farwell, TX 79325. e-mail: ku5s@wrtt.net. Web: www.wrtt.net/~ku5s. (*Wizard2*, Communications analysis prediction).

Pacific-Sierra Research Corporation, 2901 28th Street, Santa Monica, CA 90405. Tel. 800-820-4PSR. Web: www.psrv.com/hfx/. (*HFX* program).

Skywave Technologies (Jacob Handwerker, W1FM), 17 Pine Knoll Road, Lexington, MA 02173; Tel. 617-862-6742. (*IONSOUND* and *IONSOUND PRO* programs).

W6EL Software, Sheldon C. Shallon, 11058 Queensland St., Los Angeles, CA 90034. (*MINIPROP PLUS* program).

Xantek, Inc., P.O. Box 834, Madison Square Station, New York, NY 10159. Tel. 212-566-8240. (*Super DX EDGE* grayline computer program and slide rule based grayline calculator).

Websites

<http://solar.uleth.ca/solar/>—Solar Terrestrial Dispatch (in Canada), home page

www.dvle.com/solar/—for various solar activity reports (courtesy DX Listeners Club of Norway)

www.ngdc.noaa.gov—National Geophysical Data Center

www.sel.noaa.gov/—Space Environment Center

Also check numerous programs found on assorted ham-related bulletin boards.

cy, or the distance between the transmitter site and the ionospheric signal return. To reach shorter distances, you must use lower frequencies, although the signal may be heard weakly within the zone due to scattering effects.

Radio Propagation Modes and Parameters.

Signals can travel from transmitter to receiver by one, two, or multiple hops. Propagation configuration modes can involve one or more F-layer (F_2) hops, one or more E-layer hops, or a combination of the two, with a ground reflection between adjacent hops. If the wave simply is reflected midway between points, it is referred to as one-hop mode. Two-hop mode is when the signal is reflected twice by the ionosphere and once by the ground. The reflecting layer can be the F_2 or the E layer—the E layer often is ionized sufficiently to reflect waves at low frequencies. Over long distances, different ionospheric conditions exist at each reflection point, so multiple hops can be quite complex.

Multihop paths that span the day/night boundary often involve a combination of E- and F-layer reflections, and are referred to as either F-layer modes, E-layer modes, or mixed modes. Recall that the maximum single-hop F_2 -layer distance is about 2500 miles, while E-layer reflection is about 1250 miles; longer paths require multiple hops.

The range of frequencies that support communication between two particular points are of great interest to radio amateurs and shortwave listeners (SWLs). The MUF—which is influenced by absorption, transmitter power, antenna gain, receiver characteristics, type of service, and noise conditions—is the highest frequency at which a radio wave can propagate between two points at a given time by ionospheric refraction alone. Because of the great variability in the Earth's ionosphere, predicted MUFs on a given path aren't absolute values; rather, they are statistical. Predicted MUFs are median values: the actual value exceeds the predicted MUF 50 percent of the time; the other 50 percent of the time, it is less than that predicted. In general, transmission just below the MUF for a particular

It's Not Just Training...

"I needed a refresher in fundamentals and a piece of paper that said I had a degree. CIE gave me both."

Louis P. Briant
Senior Engineer
Sentel Corp.

"CIE allowed me to use my G.I. Bill benefits and independent-study allowed me to continue my studies while deployed."

Charles Hooper
Electronics Senior Chief
U.S. Navy

"The fact that I intended to continue pursuing my Associate Degree with CIE was a key factor in being considered for my current position."

Annamarie Webster
Project Engineer -
Instrumentation
Ketchikan Pulp

"My associates at work recommended CIE... The lessons were structured so they were easy to comprehend."

Vincent R. Buescher
Communications Technician
AT&T

"I reenrolled and received my A.A.S. degree from CIE because of the good experiences I had in one of CIE's career courses."

Maurice M. Henthorn, Jr.
Electronic Technician
The Denver Post

Independent study from CIE will give you the skills you need to win your own independence in a successful career.

At CIE, we pride ourselves in keeping pace with the latest developing technologies. In turn, this assures our students that upon graduation they can mesh seamlessly into a variety of exciting and rewarding technology-based careers.

Back in the 1930's, we specialized in teaching radio and television sciences. Today, it's computer technology, programming, robotics, broadcast engineering, information systems management, and the electronics behind it all.

But some things have not changed, like the desire of CIE's faculty and staff to see their graduates succeed.

That is why at CIE we teach not only the hands-on, practical aspects of electronics technology, but also delve into the "why" behind today's technology. Why does it work the way it does?

The insights to be gained from such a broad, rich and comprehensive

education at CIE matches or exceeds those gained through traditional commuter institutes while providing an education schedule to match your commitments and lifestyle.

Our patented learning program is specifically tailored for independent study and backed up by a caring team of professional educators who are at your call whenever you need their help.

At CIE, we'll match our training with your background and career goals and help you decide which of the many career courses that we offer suits you best. We offer an Associate Degree Program and through our affiliation with World College a Bachelor Degree



Computer Programming



Electronics Technician

Program.

If you have the sincerity, the smarts and the desire, CIE can make it happen. CIE is already the institute of choice for many Fortune 1000 companies. Why shouldn't you be next?

...It's an Education.



1776 East 17th Street
Cleveland, OH 44114
(216) 781-9400 • 1-800-243-6446

YES! Please send me more information on:

- CIE's Associate Degree Program
- CIE's Career Courses
- World College's Bachelor Degree Program

Name _____

Address _____

City _____ State _____ Zip _____

Phone: _____

Check for G.I. Bill Active Duty Veteran

AH 116

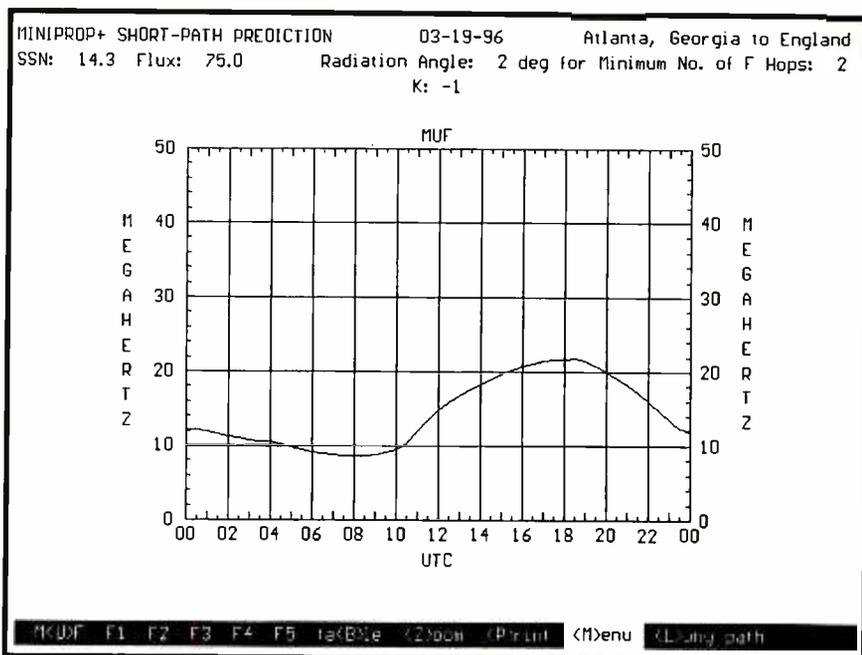


Fig. 6. MINIPROP PLUS 2.5 has significant graphical capabilities. Shown here a display of predicted MUF with a resolution of 30 minutes. The prompt line selections on the graph screen also allow you to view a graph of predicted signal levels or signal-to-noise ratio (SINR) on each prediction frequency.

path produces the strongest signals. But for long paths, the true feasibility of communication is determined mainly by the MUFs of hops close to the transmitter and receiver. The MUF for the entire path is the lowest MUF.

There are also lower limits to useful communications frequencies over a given path. The lowest usable frequency (LUF)—which is determined by many of the same types of factors that govern the MUF—is the lowest frequency that is effective for ionospheric propagation between two points. If the LUF exceeds the MUF, you have a “radio blackout” and will probably be unable to maintain communication over the path.

The highest possible frequency (HPF) is often given in addition to the MUF. The predicted frequency supported by the ionosphere is higher than the predicted MUF 10 percent of the time. Ninety percent of the time the predicted frequency is lower than the MUF and is called the frequency of optimum traffic (FOT).

Unusual HF Propagation Modes.

Here you have the basic modes of propagation; however there are some unusual propagation phenomena—such as F-layer grayline and long path propagation, non-

reciprocal communication, ionospheric fading, auroral propagation, backscatter, sidescatter, and ducting, to name just a few—that may be encountered.

F-layer grayline propagation is a special form of propagation surrounding the unusual ionospheric configuration along the fuzzy “twilight zone” between day and night. The grayline (terminator), which generally runs north-south but can vary, extends completely around the Earth. Grayline propagation is very efficient, so it can be one of the best HF-communication modes, even with low power transmitters and modest antennas. However, at any given location, grayline conditions exist for only about two hours a day: when one station is in sunrise and the other in sunset (or *vice versa*)—one hour in the morning (plus and minus 30 minutes from sunrise) and one hour in the evening (plus and minus 30 minutes from sunset).


Usually, long-distance HF communication takes place along the shortest great circle path (the “short path”) between points, which is always less than about 12,400 miles, or half the Earth’s circumference. But you can sometimes make contact in the opposite direction, the long way around the Earth (“long

path”). Although the great circle distance traveled by the radio waves may be longer, the absorption is less (due to the path traveled being in darkness). That type of propagation can be useful if the short path isn’t open for communication. However, when both paths are open at the same time, you may hear an echo in the received signal due to the phase differences between the paths traveled by the incoming waves.

Normally, radio propagation is a two-way street. But because of atmospheric anomalies, especially differences in the junctions between ionospheric layers at the path ends, it is possible for signals to travel only one way over the path; that phenomenon is called non-reciprocal communication, or one-way skip. It is more common to have a significant difference in signal strength at one end of the path, rather than the complete absence of the signal.

Ionospheric fading is the variation in signal strength caused by a gradual change in the nature of the transmission medium, where signals rise and fall over a few seconds to a few minutes. That phenomenon is usually caused by the interaction of several radio waves from the same source arriving (essentially out of phase) via different propagation modes. Stronger signals result from radio waves that arrive in phase and thus combine, while weaker signals are a result of out-of-phase signals arriving together. A variety of ionospheric phenomena can cause fading. Even signals arriving over a single path can fade due to changes in the ionospheric medium over the path.

Auroral propagation (aurora) is caused by sudden outbursts of solar activity wherein particles are ejected from the Sun. Some of those particles reach the Earth’s atmosphere about 24 to 36 hours later, where they are channeled to the polar regions by the Earth’s magnetic field. That causes a reaction with the Earth’s magnetosphere and its magnetic field. The upshot often is a visible auroral display (the northern and southern lights) as well as a radio aurora—a sort of fluorescence of the E layer which tends to reflect radio signals above about 20 MHz.

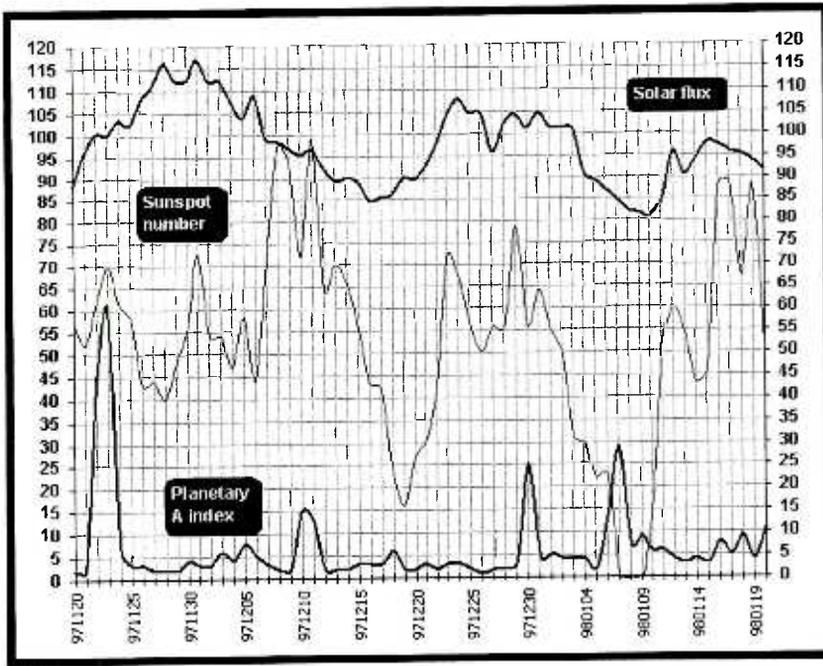

The solar terrestrial activity report (updated January 21 1998 at 0410 UTC)—downloaded (www.dxlc.com/solar) partially from data of the Sunspot Index Data Center in Brussels, and reproduced courtesy of Jan Alvestad.

Backscatter—the scattering of a signal at the point where the ionospherically propagated signal arrives—helps to fill in skip zones. Sidescatter is similar, but the groundscatter zone is somewhat off the direct line between the two stations. Both effects are particularly noticeable on the amateur 10-meter (28-MHz) band.

Ionospheric and magnetospheric ducting also may occur. In ionospheric ducting, signals may even become trapped in a duct (similar to a waveguide), possibly between the E and F layers, perhaps circling the world several times, traveling from one end of the ionospheric duct to the other. That phenomenon may be a major cause of so-called “Long Delayed Echoes” (LDEs) on HF signals. Ducting on VHF, UHF, and microwave signals may occur in the magnetosphere, rather than in the ionosphere, which largely is transparent to such higher frequencies.

VHF and UHF Propagation Modes.

At one time people believed that communication on VHF and higher frequencies would be strictly line-of-sight, but that belief has been proven wrong. Many tropospheric and ionospheric modes and phenomena tend to make VHF and

higher frequency propagation very exciting. Certain weather conditions can cause tropospheric refraction, producing greatly increased VHF and UHF signal coverage, and stronger signals than expected. The tropospheric phenomenon known as ducting takes place when refraction is so high that radio waves are bent back to the Earth. Ducting tends to occur when weather conditions involving temperature inversions are present.

All radio waves propagate at least partly through the troposphere, where they are subject to refraction, scattering, and other phenomena. While tropospheric conditions usually are not very significant below about 30 MHz, they’re quite important at VHF and higher frequencies. You’ll find a common but highly significant form of tropospheric propagation to be tropospheric scatter, sometimes called troposcatter. In fact, most VHF communication beyond the radio horizon out to about 300 miles is the result of signal scattering in the troposphere. One of the best features of troposcatter is that it is present most of the time, and it doesn’t necessarily require special equipment—although high-gain directional antennas and high

transmitter power are helpful.

The ionosphere’s layers are most important at HF, but some ionospheric irregularities and modes are significant at VHF, especially in the range 30–100 MHz. One of these is D-layer ionospheric forward scatter. That mode is fairly uncommon and usually causes weak signals, but it can produce VHF communication of up to about 1000 miles. It is most noticeable when other forms of propagation aren’t present.

Embedded at times within the E layer is the sporadic-E layer—an anomalous ionization layer that is sometimes patchy and irregular and, at other times, as smooth as silk. Many experts believe that intense sporadic-E ionization is caused by wind shear. Sporadic-E layer properties vary greatly with latitude and time of day. “Short-skip” openings on the amateur 6- and 2-meter bands often result from one-hop sporadic-E ionization.

Another E-layer propagation phenomenon is auroral E, which is noticeable on the amateur 28-, 50-, and (sometimes) 144-MHz bands. It is common across the northern third of the US and southern Canada at about the same time as auroral activity is diminishing. Signals, much like sporadic-E, sometimes have a “hollow” sound. Effects are found mostly on east-to-west paths over distances up to about 1400 miles. Auroral E openings usually last for an hour or two.

F-layer trans-equatorial spread-F, sometimes known as trans-equatorial (TE) propagation—possibly due to irregular “bulges” in the F₂ layer near the equator—can result in signals propagating between 3100 and 5000 miles across the equator; the signals tend to move westward with the setting sun. The effects have been noticed as low as the 10-meter amateur band and as high as 432 MHz. Trans-equatorial signals have a rough, auroral character, sometimes called “flutter fading,” which some texts describe as trans-equatorial field-aligned irregularities.

Large numbers of meteors, or “shooting stars,” enter the atmosphere every day. The number increases at certain periods of the year during “meteor showers.” The larger meteors leave a long, ionized

trail behind them, especially prominent in the E layer, which allows the reflection or scattering of VHF signals. Meteor-burst openings affect VHF to 200 MHz signals or higher traveling at altitudes between 300 and 1450 miles. You'll find meteor scatter contacts usually very short. It is not too difficult to literally bounce VHF and higher frequency signals off the moon (over what are known as Earth-Moon-Earth, or EME paths) across a wide range of VHF, UHF, and microwave frequencies. In fact, it's been done by amateurs since 1960 (1953 if you count "one-way" EME echoes of an amateur's own signals). Since the moon reflects only a few percent of the signal that reaches it, high-power and high-gain antennas on both ends generally are needed for success.

Using Propagation Charts And Making Forecasts.

All this knowledge is little more than academic esoterica unless you have some idea of how to convert theory into practice. Amateur-radio operators, SWLs, VHF/UHF scanner buffs, and others are all interested in predicting ionospheric radio conditions. An easily-obtained solar flux or sunspot number is all that's needed to plug into a propagation prediction program to see when and if the band(s) will be open to a given location. Some like to keep up with expected conditions via the propagation column of their favorite amateur radio magazine. Still others like to have the raw data to "roll their own" propagation estimates.

However, predicting propagation conditions is something like predicting the weather—it is not an exact science. Particularly daunting is that the underlying phenomena and relationships are complex and involve many variables. Experience and a knowledge of predicted and actual propagation conditions are required to make realistic and useful forecasts.

Luckily most of us focus on practical, short-term forecasting, since it's impossible to accurately predict propagation conditions far ahead. We're interested in whether today or this week or this month is going to give us conditions good enough to warrant participating in a DX radio

contest, or we want to know what time of day we're likely to hear or "work" a DX station. Several vehicles exist for doing this.

Direct observation, although not really forecasting, is a technique that requires you to scan the band(s) of interest to see what DX is rolling in, and where it is coming from. It is similar to the meteorologist looking out his window to check the weather. That method is fine as a real-time technique and for extrapolating very near-term conditions, but reveals little about radio conditions in a few hours or days. Direct observation works well for real-time SWLing (provided that you know which stations from which areas should be on the air at a given time). However, that technique has a disadvantage for radio amateurs. For hams, conditions might be open to particular areas of the world, but no one is transmitting from them. Thus a band may appear "dead" when it's really just dozing.

A more polished form of direct observation involves systematically scanning known operational HF beacon stations in various areas of the world. A variety of organizations operate beacons, which are mostly clustered on the 10- and 20-meter amateur bands; many are on 6 meters. For example, the Northern California DX Foundation (NCDXF) operates a network of beacons on 14.100 MHz in the 20-meter band, and the International Telecommunication Union (ITU) operates beacons in Australia and Norway on frequencies adjacent to several HF amateur bands.

Using Computers In HF Propagation Prediction.

Until recently, radio hamshack and SWL PC software was focused mainly on QSO (contact) and contest logging. Today, however, software has been developed that lets your PC perform many other chores, and most can be customized for your QTH. You can even produce timely predictions of sky wave conditions (or MUF) between any two points. Some programs can handle such chores as estimating LUF and other propagation parameters such as HPF and FOT, as well as signal strength, signal-to-noise ratio (S/NR), number and

configuration of hops, long- and short-path distance and heading, radiation angle, time zones, and other parameters.

Pacific-Sierra Research's *HFX* is a popular Windows HF propagation prediction program. The HFX Hop Mode model generates field strength, mode, availability, and S/NR for a given date, transmitter and receiver pair, frequency, and antenna type. The program displays the data in several formats, including a graphic of sky wave ionospheric hops for each frequency at one-hour intervals, as shown in Fig. 3.

The HFX Global MUF model generates a color map of maximum usable frequency, frequency of optimum traffic, or highest possible frequency, as shown in Fig. 4. Using this model, you can determine the best frequencies to reach any part of the world. Global MUF geometry is depicted here on a rectangular projection.

SKYCOM 2.0, from Fuentez Systems Concepts, Inc., is an easy-to-use Windows program that presents a "quick-look" prediction for "yes-no-maybe" contact possibilities; you can also obtain a detailed report. Shown in Fig. 5 is the Advanced Parameters Window, where you can fine tune the program to better reflect prevailing conditions or set up "what if" scenarios.

MINIPROP PLUS 2.5 has significant graphical capabilities. Shown in Fig. 6 is a display of predicted MUF with a resolution of 30 minutes. The prompt line selections on the graph screen also allow you to view a graph of predicted signal levels or signal-to-noise ratio (S/NR) on each prediction frequency.

Summary. We have covered some of the more basic aspects of radio wave propagation: the electromagnetic spectrum; the nature of radio waves; the regions of the Earth's atmosphere; sunspots; propagation modes; the role of personal computers in forecasting; etc. This primer wasn't intended to make you a propagation pro, but with the information we've presented, you should be well on the way to understanding how propagation works and making the most of your newfound skills. ■

NATIONAL ELECTRONICS TECHNICIAN'S DAY

National Electronics Technician's Day is the perfect time to join the ranks of the certified service professionals.

For over 30 years, the International Society of Certified Electronics Technicians (ISCET), has developed and implemented programs and services to help the working technician remain competent and to continue to develop skills and technical expertise. During that time, ISCET has certified over 44,000 technicians nationwide and in over 40 foreign countries, provinces, and territories, while continu-

ing to set industry standards to assure this country's continued technological and economic leadership. To recognize that achievement, to honor the technicians who have demonstrated their skill and high performance by becoming Certified Electronics Technicians (CETs), and to encourage working technicians to join the ranks of their colleagues who have attained the CET designation, ISCET established

National Electronics Technicians Day in 1986 as a special day set aside for the certification of technicians worldwide. For this year, that special day, officially declared as "T-DAY," is set for Tuesday, April 21, 1998.

ISCET invites all technicians to celebrate National Electronics Technicians Day during the Week of April 21 through April 25, 1998, which has been designated T-WEEK. If you are planning to take

VOLUNTEER CET EXAMINERS

Cindy Johnson, CA
280 West Vly Ave
Birmingham, AL 35209
205-916-2800
205-916-2807

Alfred Jones, CET, CA
Lawson St Comm College
3060 Wilson Rd
Birmingham, AL 35221
205-925-2515
DJones@kibanet.com

James Lockhart, CET, CA
ITT Tech Inst
500 Riverhills Business Pk
Birmingham, AL 35242
205-991-5410
205-991-5025

Susan Gann, CA
ITT Tech Inst
500 Riverhills Business Pk
Birmingham, AL 35242
205-991-5410
205-991-5025

Tony Jetton, CET, CA
Wallace St College
Box 2000
Hanceville, AL 35077-
2000
205-352-8160

Ricky Reaves, CET, CA
Shoals Comm College
Box 2545
Muscle Shoals, AL 35662
205-331-5201
205-331-5200
205-331-5222
800-645-8967

David Bryan, CET, CA
AL Aviation College
Box 1209
Ozark, AL 36360
W-205-774-5113
H-205-774-0163

R.T. Van Iderstine, CET,
CA
14563 South Blvd
Silverhill, AL 36576
334-945-5942

Daniel McCAnn, CET, CA
QMS Inc
30949 Wellington Ct
Spanish Ft, AL 36527
W-334-633-4300 X-2047
H-334-621-8163
dmcCAnn@rd.qms.com

Kristi Lashlee, CA
PO Box 909
Searcy, AR 72143
501-268-6191

Dennis Blum, CET, CA
8730 W Hazelwood
Phoenix, AZ 85037
602-872-8564
602-279-2999
schemati@aztec.asu.edu

HJ Paine, CET, CA
4631 E 8th St
Tucson, AZ 85711
520-881-6784
520-795-1209
kirshna@azstamet.com

Parviz Shams, CA
So CA Inst Of Tech
1900 W Crescent-Bldg B
Anaheim, CA 92801
714-520-5552

Romualdo Malarayap,
CET, CA
4249 Filhurst
Baldwin Park, CA 91706
626-962-3631

Jim Hines, CA
Fresno Tech
731 W Shaw Ave
Clovis, CA 93612-3217
209-442-3500

Michael Maxwell, CET, CA
St Agnes Med Cntr
1303 E Herndon Ave
Ms 040
Fresno, CA 93720
209-449-3512
209-449-3030
maxwm@samc.com

David Marson, CET, CA
Mac Doctor
1040 W Kettleman
Ln#1b339
Lodi, CA 95240-6056
209-944-6191 X6698
Maddoc@CAIweb.com

Jerry Mendoza, CET, CA
4601 Lexington #111
Los Angeles, CA 90029
213-667-1732

Michael Miller, Vo Instr
1205 Bay Oaks Dr
Lososos, CA 93402
805-547-7900 X 7143

John Craig, CET, CA
NSWC
531 W Hueneme Rd
Oxnard, CA 93033
805-982-9803
805-986-2504

George M Kirby, CA
ITT Tech Inst
10863 Gold Center Dr
Rancho Cordova, CA
95670-6034
916-851-3900
916-851-9225
gjkir@inreach.com

Jon Sturtz, CET, CA
10840 Alandale Way
Rancho Cordova, CA
95670
916-635-6000

Steven Thomas, CET, CA
2306 Marilyn Ave
Redding, CA 96002-2304
916-222-2541
916-243-2267
pilotst@nstate.net

Peter Moreno, CET, CA
ITT Tech Inst
630 E Brier Dr #150
San Bernardino, CA
92408
909-889-3800

Dr Kenneth Wilson, CET,
CA
San Diego Cty College
1313 12th Ave
San Diego, CA 92101
619-230-2601

Charles Trout, CET, CA
Service Concepts Inter Inc
563 N Fairview St
Santa Ana, CA 92703
714-836-4981
714-569-0204

Don Winchel, CET, CA
M & D Elect
Box 123
Smartville, CA 95977
530-639-2477
530-639-2477
dwinchel@mako.com

Howard Bardach, CET,
CA
13251 Ventura Blvd #D
Studio City, CA 91604-
1838
818-995-8648
818-995-8647

Marjorie Lona, CA
Colorado Aero Tech
10851 West 120th Ave
Broomfield, CO 80021
303-466-1714 X-273
800-888-3995

Ken Hill, CET, CA
400 CR 230
Durango, CO 81301
970-247-3032
970-565-8457

George Shaiffer, CET, CA
38 N Dartmouth
Widfield, CO 80911
719-540-7458
719-392-1000
719-540-7453

Daniel Shea, CET, CA
CT School Of Elect
586 Ella T Grasso Blvd
New Haven, CT 06519
203-624-2121

Scott Latino, CET, CA
Bombardier Aviation Serv
1 Bradley Internationl
Airport
Windsor Locks, CT 06096
860-292-7219

Albert Moses, CET, CA
Box 188
Cheswold, DE 19936
W-302-736-3816
H-302-653-5648

Karl Hunter, CET, CA
13850 Ketch CV Dr
Jacksonville, FL 32224-
1143
W-904-633-8143
H-904-223-5289

Edward Guary, Sr, CET, CA
Eddy's Car Radio
2505 US 60 E
Lake Wales, FL 33853
941-679-7507

John S Richards, CET, CA
ITT Tech Inst
2600 Lake Lucien Dr
Ste 140
Maitland, FL 32751
407-660-2900
407-660-0694
wizsteve@gte.com

James Sullivan, CET, CA
ITT Tech Inst
7955 NW 12th St #119
Miami, FL 33126
305-477-3080
305-477-7561

James D Drennen, CET, CA
Pensacola Jr College
1000 College Blvd
Pensacola, FL 32504
904-484-2592
850-484-2597
jdrennen@pic.cc.fl.us

Ronald Handlon, CET, CA
Tampa Tech Inst
2410 E Busch Blvd
Tampa, FL 33617
W: 813-935-5700
H: 813-898-3970

Dennis Abell, CET, CA
3433 Royal Oak Dr
Titusville, FL 32780
407-269-4208

Alan Besore CET, CA
New England Inst Of Tech
1126 53rd Ct
W Palm Beach, FL 33407
800-826-9986
561-842-9509

VOLUNTEER CET EXAMINERS

Robert Laquerre, CET, CA
New England Inst Of Tech
1126-53rd Court
W Palm Beach, FL 33407
561-842-8324
boblaq@earthlink.net

Donald K Dahms, CA
Atlanta Tech Inst
1560 Metropolitan Pkwy
SW
Atlanta, GA 30310
404-756-3786
404-752-0180
ddahms@admin1.Atlanta.
Tec.ga.us

Dan Mundy, CET, CA
Norman's Elect
3653 Clairmont Rd NE
Atlanta, GA 30341
404-373-8037
71241.336@COM
PUSERV.COM

James Vansant, CET, CA
Pickens Tech
100 Pickens Tech Dr
Jasper, GA 30143
706-692-4500
706-692-4510
jvansant@admin1.pick
ens.tec.ga.us

John Carolus, CET, CA
Matsushita
1225 Northbrook Pkwy
2-380
Suwanee, GA 30174-
2933
770-338-6875

Joe Reese, CET, CA
Reese Elect Inc
Box 499
301 South Main St
Swainsboro, GA 30401
912-237-7010
912-237-7463
jreese@pineian1.neti

William Doi, CET, CA
Doi's Elect Svc
105-a N Kainalu Dr
Kailua, HI 96734
808-261-6911

Leonard Bowdre, CET, CA
125 SE Thornton Ave
Des Moines, IA 50315
W-515-964-6484
H-515-282-3028
lebowdre@dmrc.cc.ia.us

Donnin Custer, CET, CA
West IA Tech Comm
College
Box 265-4647 Stone Ave
Sioux City, IA 51102-0265
712-274-8733 X-1392

Bruce Tietjen, CET, CA
204 Northgate Mile
Idaho Fis, ID 83401
208-523-5045

Dr Harvey Franklin, CA
500 Eighth Ave
Lewiston, ID 83501
208-799-2220

Eddie Lane, CET, CA
1501 Honeysuckle
Champaign, IL 61821
W-217-333-1070
H-217-356-6996

Fred Schwarzkopf, CET, CA
3708 W 83 Place
Chicago, IL 60652
773-767-4126 X-563

Paul R Trowbidge, CA
Drive Controls Inc
3232 Skokie Rd
Highland Park, IL 60035
847-433-0755
847-662-1563

Paul Tan, CET, CA
915 Augusta St#1
Oak Park, IL 60302-1678
708-848-6327

Lonnie Lewellen, CA
Ivy Tech State College
4475 Central Ave
Columbus, IN 47203
812-372-9925

Matthew A Dillman, CA
Ivy Tech State College
3501 First Ave
Evansville, IN 47710
812-429-1479

Paul F Maglinger, CET, CA
901 Dover Ct
Evansville, IN 47710
812-464-2523
812-421-2170
pmagling@clrtechnol.com

Don Williams, CET, CA
Vincennes Univ-TB10
1002 N First St
Vincennes, IN 47591
812-885-5801
812-922-5670

Christopher Smith, CA
Purdue Univ-N Central
1401 South US 421
Westville, IN 46391
219-785-5256
219-785-5539
csmith@purdueuc.edu

Stanley Creitz, CET, CA
Comm Services
Rr 4 Box 72
Beloit, KS 67420
913-738-5095
screitz@nckcn.com

Keith Knos, CET, CA
Knos Elect
1206 Elm Blvd
Liberal, KS 67901
316-624-5908

Sharon West, CA
Johnson Cnty Comm
College
12345 College Blvd
Overland Park, KS 66210
913-469-4439

John Hardin, CET, CA
KT Tech-Ashland Rtc
4818 Roberts Dr
Ashland, KY 41102
606-928-6427
606-329-7136

Danny Keeton, CET, CA
55 W Airview Dr
Elizabethtown, KY 42701
502-769-6606
502-769-8278

Lamarr Ritchie, CET, CA
Hazard Reg Tech Cntr
101 Vo-tech Dr
Hazard, KY 41701
606-435-6101
606-476-8714
lamarr@geocitlps.com

Jerry Sipes, CA
Spencerian Colge-
Lexington
3330 Partner Pl Ste 1
Lexington, KY 40503
606-223-9608
606-224-7744
S4744@gte.com

Edward Kimmel, CET, CA
Kimmel Elect
2061 Eastern Pkwy
Louisville, KY 40204
502-451-3457

Donald Johnson, CA
Inst Of Elect Tech
509 S 30th St
Paducah, KY 42001
502-444-9679

Jesse Adkison, CET, CA
Inst Of Elect Tech
509 S 30th St
Paducah, KY 42001
502-444-9676
502-345-2061

Michael Dixon, CET, CA
KY Tech-Somerset
Campus
230 Airport Rd
Somerset, KY 42501
606-679-4303

Dr I F Creel, CET, CA
Louisiana Tech College
1710 Sullivan Dr
Bogalusa, LA 70427
504-732-6640
504-732-6603
fcreel@communique.net

Don Creech, CET, CA
712 Ronson Dr
Kenner, LA 70065
504-467-4644

Jeffrey Luminais, CET, CA
4014 Arkansas
Kenner, LA 70065
504-888-6848

James Sorrels, CET,
csm, CA
Polytronics
8101 Kingston Rd #102a
Shreveport, LA 71108-5745
318-688-2952
318-688-4888
polytronics@internetcni.
com

Frank Serra, CET, CA
AudioSonics Inc
159 Mass Ave
Arlington, MA 02174
781-648-2430
781-648-2431

Don Harris, CA
RETS Elec Sch
965 Commonwealth Ave
Boston, MA 02215
617-783-1197

Robert Braunston, CET, CA
RETS Elec School
965 Commonwealth Ave
Boston, MA 02215
617-783-7197

Earl Tickler, CET, CA
RETS Tech Trng Cntr
1520 S Caton Ave
Baltimore, MD 21227
410-644-6400
410-644-6481

Carl Miller, CET, CA
TESST
5122 Baltimore Ave
Hyattsville, MD 20781
301-864-5750

Bob Bellers, CET, CA
Washtenaw Comm
College
4800 E Huron Riv Dr
Ann Arbor, MI 48106
313-973-3316
BBEL373@orchard.washt
enow.cc.mi.us

Naomi Ludman, CA
Southwestern Michigan
Colge
58900 Cherry Grove Rd
Dowagiac, MI 49047
616-782-1329

John Thennes, CET, CA
2102 10th Ave S
Escanaba, MI 49829
906-786-1413

Gerald Heyn, CET, CA
WNMU-TV, WNMU-FM
132 Blueberry
Gwinn, MI 49841
906-346-6396H
gheyn@nmu.edu

Walter Reilly, III,
CET, CSM, CA
WER Inc
2727 E Kalamazoo
Lansing, MI 48912
517-485-1737
517-485-9555
RS2K23A@PRODIGY.COM

Larry Geissler, CET, CA
3706 Chambersburg
Duluth, MN 55811
218-722-9356
lgeiss@theonramp.net

Jim Hunsucker, CET, CA
N Cntrl Area Vo Tech
Hwy 69 Spur N
Bethany, MO 64424
816-425-2196
jhunsucker@shr2.k12.mo.
us

William Sharp, CET, CA
Grand River Tech Sch
1200 Fair
Chillicothe, MO 64601
816-646-3414
816-646-3568
sharpbil@grt.chillicothe.k12
.mo.us

Annabel Gooch, CA
MAVTS
905 N Wade St
Mexico, MO 65265
573-581-0752
573-581-7084
AGOOCH@mexicok12.m
o.us

Michelle A Stein, CA
Moberly Area Vo Tech
1625 Gratz Brown
Moberly, MO 65270
816-269-2631
816-269-2692

Marlon Denny, CET, CA
Rapid TV-Elect Repair
1909 6th St
Meridian, MS 39301
601-485-8453
601-485-2102
rpdptr@intop.net

Joseph Sloop, CET, CA
Surry Comm College
Dobson, NC 27017
910-386-8121 X-301

Linda Dickinson, CA
Craven Comm College
Ste 22 E Plaza
Professional Cnt
Havelock, NC 28532
919-444-6005
919-444-1918

Earl Fosler, CET, CA
Southeast Comm College
4236 Ridge Lea Rd
Milford, NE 68405
402-761-8266
402-761-2324
ertfosler@sccm.cc.ne.us

Jack Hopson, CET, CA
First Telev Svc
5214 Center
Omaha, NE 68106
402-556-4018
402-551-4870

Franklin Davy, CET, CA
PO Box 1889
Hillsboro, NH 03244-1889
603-478-5716

Edward Leduc, CET, CA
319 S Hall St
Manchester, NH 03103-
3955
603-669-1533

Joseph Szumowski, CET,
CA
JTS Elect
412 Pomona Rd
Cinnaminson, NJ 08077
609-829-9669
cintron@aol.com

Anthony Baratta, CET, CA
RETS Inst
103 Park Ave
Nutley, NJ 07110
973-661-0600 X-30
973-661-2954

Antonio Mares, CET, CA
Luna Vo Tech Inst
PO Box 2969
Las Vegas, NM 87701
505-425-5600

Fred Freeman, Jr, CA
550 Tabany Ave
Henderson, NV 89015
702-564-9163

David Law, CET, CA
Alfred St College
222 Brown Hall
Alfred, NY 14802
607-587-3468
607-587-3291
LawL@alfredtech.edu

Carl Meyer, CET, CA
AFPS Inc Test Lab
4236 Ridge Lea Rd
Amherst, NY 14226
716-835-6664

Gregory Reiber, CET, CA
9553 Bantry Rd
Brewerton, NY 13029-
9543
315-668-9936

Larry Steckler, EHF,
CET, CA
Gernsback Publications
500 Bi-County Blvd
Farmingdale, NY 11735
516-293-3000 X-201

Hubert West, CET, CA
20 Schuyler St
Lake George, NY 12845
518-668-9285
hwest789@concentric.net

Richard Mildenerger,
CET, CA
Quaritus TV
147 Merrick Ave
Merrick, NY 11566
516-379-3970

Gary Rathbun, CET, CA
Cleveland Inst Of Elect
1776 E 17th St
Cleveland, OH 44114
216-781-9400
216-781-0331
instruct@cie-wc.edu

Richard Ackerman,
CET, CA
3603 Steeplechase Ln #3d
Loveland, OH 45140-3246
W-513-573-4704
H-513-583-1402

Lawrence Delonais, CET,
CA
NEC
1660 Martin Rd
Mogadore, OH 44260
330-923-9959

Joseph Carney, III,
CET, CA
Malthus Diagnosis
35888 Center Ridge Rd
N Ridgeville, OH 44039
330-327-2585
330-327-7286
Joecarney@aol.com

Michael Beaver, CET, CA
Univ Of Rio Grande
School Of Technolgy
Rio Grande, OH 45674
740-245-7314
740-245-7440
mbeaver@urgrcc.edu

A C Falcone, CET, CA
Falcon Elect Inc
3266 Kent Rd
Stow, OH 44224
330-688-2451
330-688-8747

Joe Harris, CA
Tulsa Tech Cntr
3850 N Peoria
Tulsa, OK 74106-1691
918-428-2261 X-264

Noah Harrelson, CAI, CA
Tulsa Tech Cntr
3850 N Peoria
Tulsa, OK 74106-1691
918-428-2261 X-241

Roy Yonce, CA
5103 S Sheridan Rd #214
Tulsa, OK 74145-7627

Vern Hartshorn, CET, CA
Mt Hood Comm College
26000 SE Stark St
Gresham, OR 97030
503-667-7117

VOLUNTEER CET EXAMINERS

James Shambow, CET,
CA
ITTES
6035 NE 78th Ct
Portland, OR 97218-2854
503-255-6500
800-234-5488

Thomas Gaudiello, CET,
CA
Chi Inst (RETS Campus)
W Chester Pike/Malin Rd
Broomal, PA 19008
610-353-7630
tomg@inet.net

L.A. Leibensperger, CET,
CA
5225 Camp Meeting Rd
Center Vly, PA 18034
610-866-4114

William Margut, CA
Elect Inst
19 Jamesway Plaza
Middletown, PA 17057-
4851
717-944-2731

Gene Hedgepeth, CET,
CA, CMAT
Techtronics Svcs
2165 Alberdeen Rd
Moutaintop, PA 18707-
9059
717-868-6566
717-821-0509
717-868-3444

Thomas Plant, CET, CA
ETG Of Rhode Isl
29 Dean St
Pawtucket, RI 02861
401-725-8719

Stanley Salter, CET, CA
Stan Salter Music Svc
826 Bay Blossom
Sumter, SC 29150
803-469-3022

Don Multerer, CET, CA
Sencore Inc
3200 Sencore Dr
Sioux Falls, SD 57107
605-339-0100
800-736-2673

Ronald Rackley, CET, CA
Tenn Inst Of Elect
3203 Tazewell Pike
Knoxville, TN 37918-2530
423-688-9422
423-688-2419

William Warren, CET,
CSM, CA
Warren Elect Svc
2540 Sutherland Ave
Knoxville, TN 37919
423-546-1128
423-524-5362

John Weaver, CA
3334 Nonesuch Rd
Abilene, TX 79606-1924
915-698-5785
915-622-7091
jweaver@tstc.edu

Francis E Cave, CET, CA
6303 Lotus Dr
Arlington, TX 76001
817-468-8706
817-640-7100
cave@arlington.net

Fred Duck, CET, CA
Austin Comm College
1212 Rio Grande
Austin, TX 78701-1785
512-223-3044
512-247-5763
512-495-7400
Duck2021@juno.com

Alan Green, CET, CA
ITT Tech Inst
6330 Hwy 290 East
Austin, TX 78723-1061
512-467-6800

Henry Corrie, CET, CA
1460 CR 3413
Chandler, TX 75758
903-852-4140
903-593-0220

Tom Underwood, CET, CA
Tomtronics Inc
10424 Remington Ln
Dallas, TX 75229
214-357-0644
jomund@aol.com

Rodger W Minatra, CA
Grayson Cnty College
6101 Grayson Dr
Denison, TX 75020-8299
903-463-8670
903-463-5284
rminatra@grayson.edu

Robert Griffin, CET, CA
TCJC
5301 Campus Dr
Ft Worth, TX 76119
817-531-4529

Arthur Ruppert, CET, CA
30217 St Andrews
Georgetown, TX 78628
512-863-9157

James Harris, CET, CA
1505 Tanglewood Dr
Harker Hts, TX 76548
817-698-2331
817-526-1257
harrisj@hood-
emh3.Army.MIL

Alden Walther, CA
ITT Tech Inst
2950 S Gessner Rd
Houston, TX 77063-3751
713-952-2294

Gordon Davis, CA
6934 Drowsy Pine
Houston, TX 77092
713-462-8764

Frank Ureno, CA
Texas A&M Univ-Kingsville
Box 122
Kingsville, TX 78363
512-593-2111
512-593-3605
fureno@tamuk.edu

Marilyn A Hendershot, CA
1317 East Hulsache
Kingsville, TX 78363
H-512-592-0853
W-512-592-3608

Gerald Martin, CET, CA
Lucent Technologies
107 W Nakoma
San Antonio, TX 78216
210-527-3347
210-527-3347
glmartin@lucent.com

Earl Hines, CET, CA
1710 Lamar Lot#2
Sweetwater, TX 79556
915-235-1849
915-235-7404
915-235-7369
ehines@selib.tstc.edu

Sandra Woodman, CA
TSTC
300 College Dr
Sweetwater, TX 79556
915-235-7406
800-592-8783

Dickie Lide, CET, CA
Texas State Tech College
3801 Campus Dr
Bldg 7-05
Waco, TX 76705
254-867-4883
254-867-3631

Sandra L Herinckx CET
CA
Texas State Tech College
3801 Campus Dr Bldg 7-5
Waco, TX 76705
254-867-4883
254-867-3631
sherinck@tstc.edu

Dick Kimberley, CA
Salt Lake Comm College
4600 S Redwood Rd
Salt Lake City, UT 84130-
0808
801-957-4235
801-280-9590
801-965-8008

Norman F Gresley, CET,
CA
52 Hancock PINE
Leesburg, VA 22075
703-443-0185
540-347-8978

Charles Spiro, CET, CA
Lord Fairfax Comm
College
Box 47
Middletown, VA 22645
540-869-1120
540-869-7881
cspiro@shentel.net

Ted Rodriguez, CET, CA
Skagit Vly College
2405 College Way
Mt Vernon, WA 98273
360-416-7757
360-416-7843
rodriguez@skagit.ctc.edu

Roberta Wells, CA
ITT Tech Inst
N 1050 Argonne Rd
Spokane, WA 99212
509-926-2900

Del Dressel, CET, CA
Oakland Radio & TV
3901 S Center St
Tacoma, WA 98409-3148
206-840-4975
206-840-5099

David Bates, CET, CA
Western WI Tech College
304 N 6th St
Lacrosse, WI 54602
608-785-9290
608-785-9407
BatesD@western.tec.wi.us

Duane Busby, CET, CA
BC&D Ent
2027 Sherman Ave
Madison, WI 53704-5934
608-244-0339

Jeff Paschke, CET, CA
1011 Jefferson St
New London, WI 54961
414-982-3641
414-982-3641
JPASC5871@aol.com

Jacob Klein, CET, CA
Northcentral Tech College
1000 W Campus Ave
Wausau, WI 54401
715-675-3331 X-4395
715-675-4917

C Stephen Triplett, CA
NITC
5514 Big Tyler Rd
Cross Lanes, WV 25313
304-776-6290
304-776-6262

David L Woodruff, Jr
NITC
5514 Big Tyler Rd
Cross Lanes, WV 25313
304-776-6290

Egon Strauss, CET, CA
V. De Obligado 2376
Buenos Aires
Argentina 1428
541-781-8564
541-782-2088
egon@lauquen.com.ar

Richard M Hopkins CA
Napanee Dist School
245 Belleville Rd
Napanee, Ontario
Canada K7J 3M7
613-354-3381

Gary Memory, CET, CA
Amer Emby
Paris, France
PSC-116 Rm# A314
APO AE 09777
33-1-47.53.82.55
101365.1113@com
puserve.com

Antonio M Avellanosa, CA
MPITI
45 Tecson St
Baguio City, Philippines
2600
74-442-8170
74-442-6532

Jose M T Bigornia, CA
o/o Cebu Tech Sch
Osmena Bw
Cebu City, Philippines
6000
(063-32) 2542434
(063-32) 2538797
ctsinc@webllnq.com

Julius Bissessar, CET, CA
Quarry Vlg P.O.
Quarry Vlg-Via Siparia
Trinidad-Tobago,
West Indies
809-649-6127

the CET exams, now is the time as during T-WEEK, ISCET's dedicated network of Certified Test Administrators will be providing opportunities for interested technicians to obtain their certification. Whether you are interested in completing your Associate or Journeyman Certificate, gaining continuing education units, or want to sit for one of many FCC elements, call one of the examiners listed below for assistance. These test administrators are dedicated to the continued growth of the CET program and anxiously await your calls.

For more information on the CET program, visit ISCET's home page at www.iscet.org.




"No! No! No! That's not what I meant by trouble-shooting!"

ELECTRONICS LIBRARY

ALTERNATIVE ENERGY: AN INTRODUCTION TO ALTERNATIVE & RENEWABLE ENERGY SOURCES

by Mark E. Hazen

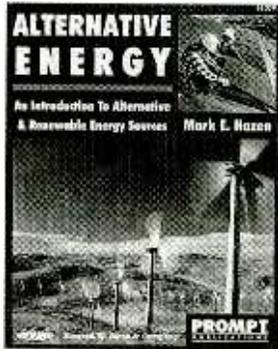The world's energy needs are greater than ever before as populations increase and Asian countries awaken industrially and economically. As the demand for oil-based energy is increasing, the world supply is decreasing. Demand for fuel is outpacing the world's ability to produce it. Now more than ever, it is important to understand the energy problem and the alternatives that are available.



The author begins with a broad overview of electricity, explaining its various mechanisms from electro-mechanical and electromagnetic to thermo-, photo-, and piezo-electric. The second chapter defines energy and discusses the basics of potential, kinetic, thermal, chemical, and nuclear energy. Further chapters go into depth on these topics, introducing the reader to energy sources that draw from such supplies as wind, sun, water stored in reservoirs, ocean tides, ocean currents, ocean heat storage, and more.

Organized in a very clear, easy-to-read manner, each chapter has review questions and Web sites relevant to the subject of that chapter. An excellent reference, the book provides a comprehensive listing of Web sites about alternative forms of energy and the organizations devoted to them, a glossary of terms, an index, and a bibliography.

Alternate Energy costs \$18.95 and


is published by Prompt Publications, Howard W. Sams & Company, 2647 Waterfront Parkway, East Drive, Indianapolis, IN 46214-2041; Tel. 800-428-7267 or 317-298-5400; Fax: 317-298-5604; Web: www.hwsams.com.

**CIRCLE 90 ON FREE
INFORMATION CARD**

I WANT MY WEB TV

by David Fox

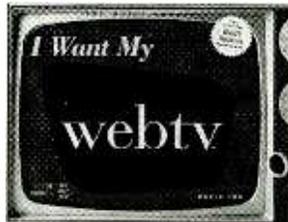Designed for anyone who has a television and wants to hook up to the Web, this book is written in a witty and conversational style. An invaluable road map explaining what Web TV is and how to navigate it, it shows readers how to tune in, turn on, and hook up within minutes. The author also gives advice on surfing the Web, exploring cutting-edge places that Web TV can go.



Advanced features are covered, such as using e-mail, searching, creating favorites lists, blocking mature screens, and how to use credit cards safely on the Web. Guidance is provided on exploring travel, games, entertainment, news, sports, and shopping on the Web.

I Want My Web TV costs \$19.99 and is published by Waite Group Press, 200 Tamal Plaza, Corte Madera, CA 94925; Tel. 415-924-2575; Fax: 415-924-2576; Web: www.waite.com/waite.


**CIRCLE 91 ON FREE
INFORMATION CARD**

BooksNow To order books in this magazine or, any book in print. Please call anytime day or night: **(800) BOOKS-NOW (266-5766)** or (702) 258-3338 ask for ext. 1454 or visit on the web at <http://www.BooksNow.com/popular-electronics.htm>.

LASERS, RAY GUNS & LIGHT CANNONS: PROJECTS FROM THE WIZARD'S WORKBENCH

by Gordon McComb

In this 413-page book, there are over 88 laser and optics projects. Hobbyists, either expert- or student-level, are shown how to build the fun projects, using inexpensive, easy-to-obtain components. Projects include putting on a professional light show, creating holograms, performing dozens of experiments, and building a laser-ray gun. In other construction projects, the reader will learn how to detect intruders around a perimeter, measure precisely the speed of light, perform laser "snooping," transmit data with lasers, and carry voices over a beam of light.

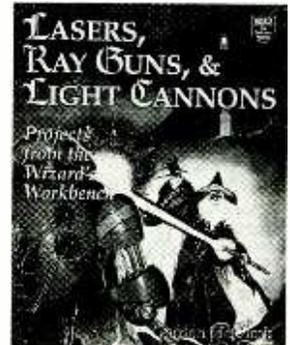

Organized into 25 independent modules, the book presents the scientific history and theory, as well as both basic and advanced instructions for the projects themselves. In addition, there are chapters on tools for laser experimentation, buying laser parts, and computer-controlled laser projects.

Lasers, Ray Guns & Light Cannons: Projects from the Wizard's Workbench costs \$21.95 and is published by McGraw-Hill, Inc., 11 West 19th St., New York, NY 10011; Tel. 800-2MCGRAW or 212-337-5951.

**CIRCLE 92 ON FREE
INFORMATION CARD**


**1997/98 ELECTRONIC
INTERCONNECT GUIDE**
from 3M Electronics Division

This 116-page catalog is a condensed
(Continued on page 42)

NEW PRODUCTS

COMPUTER MONITOR

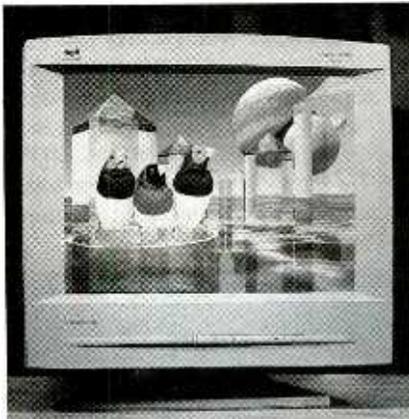In keeping with concerns for environment issues, ViewSonic Corporation's G773 17-inch Monitor meets the safety, emissions and power management standards set by TCO '95 and NUTEK. Designed for SOHO and business graphics users, this monitor offers excellent screen performance and implements automatic power-savings mode during periods of inactivity.



With its super-fine 0.26mm dot pitch and Invar shadow mask, the View Sonic G773 produces clear, sharp images. This clarity is enhanced by advanced SuperClear screen technology that combines exceptional focus found in high-contrast conventional CRTs with the bright, vivid colors associated with aperture grille CRT monitors, creating crisp, color-rich images. A special screen treatment reduces annoying glare and reflection.

Featuring a horizontal scan rate of 30–70 kHz, a vertical scan rate of 50–160 Hz, and a refresh rate of 87Hz at a resolution of 1024 × 768, this monitor operates in both PC and Mac environments. The G773 offers easy-to-use controls, a user-friendly on-screen menu for all screen adjustments, and Plug&Play+, which supports Windows 95 requirements, for easy configuration and set up.

The estimated street price is \$510. For more information, contact ViewSonic Corporation, 20480 Business Parkway, Walnut, CA 91789; Tel. 800-888-8583 or 909-869-7976; Fax: 909-468-3756; Web: www.viewsonic.com.


**CIRCLE 80 ON FREE
INFORMATION CARD**

UNIVERSAL HORIZONTAL ANALYZER

This product-test equipment works with all computer monitors, televisions, projection TVs, and other CRT video displays—all in one instrument. Providing everything you need to localize horizontal and B+ supply defects in computer monitors, the HA2500 Universal Horizontal Analyzer does it in less time and more efficiently than ever before.

The HA2500 offers a unique frequency lock and variable horizontal frequency system that allows quick servicing of all horizontal circuits no matter the frequency (15 kHz to 125 kHz). It also provides a "Horizontal Output Load Test" that makes set up and testing a snap, allowing a circuit to be tested without even applying AC power. This guarantees accurate estimates, reduces the number of damaged replacement parts, and speeds the technician's diagnosis and repair.

In addition, the unit incorporates a patented "Ring" test for analyzing IHVTs, flybacks, and yokes in seconds. The "Dynamic Tests" feature analyzes horizontal circuits in a powered-up condition to catch even subtle defects in the power supply and drive signal. This test can eliminate call-backs and reworks associated with horizontal circuits. A special variable-current limited and protected B+ substitute supply is bundled with the HA2500, and this allows the technician to test and troubleshoot even when the power supply of the unit being tested is dead.

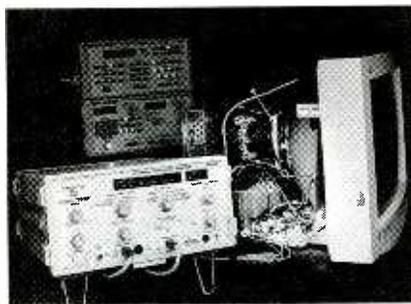


The HA2500 Universal Horizontal Analyzer costs \$2895. Contact Sencore, Inc., 3200 Sencore Drive, Sioux Falls, SD 57107; Tel. 800-SEN CORE or 605-339-0100; Fax: 605-339-0317.

**CIRCLE 81 ON FREE
INFORMATION CARD**

AN INTERFACE MULTIMETER

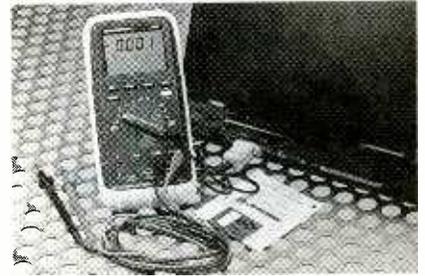Permitting data logging directly to a personal computer via a built-in RS-232 interface port, the handheld Model 2880 digital multimeter is an all-in-one instrument. The 2880 DMM measures true RMS values and is a cost-effective device.



The triple LCD display with 4000 count resolution and a fast update analog bargraph that are incorporated makes measurements easy to read. Min, Max, and Present readings can be displayed simultaneously, or the mode can be changed to display Min, Max, and Average readings simultaneously instead. The triple display function can also be used in the Compare Mode, where high and low limits may be set and displayed, while the main display indicates PASS or FAIL when measurements are compared to the preset limits. In the Dual Display Mode, the LCD can also simultaneously display AC voltage and Frequency (200 Hz–200 kHz with 20,000 count display).

Measurement functions include AC/DC volts, AC/DC current, resistance (auto/manual ranging), continuity and diode test, capacitance (400 nF–40 μF) 10-megohm input impedance, and overload protection at 1000-volt peak (600-volt peak on 40-mV range.) Priced at \$189, the Model 2880 DMM comes with software diskette, as well as the RS-232 interface cable.

All B&K Precision products are available worldwide through a global network of authorized distributors. For more information, contact B+K Precision, 4353 W. Lawrence Avenue, Chicago, IL 60630; Tel. 773-725-9252; Fax: 773-725-9385; Web: www.bkprecision.com.

**CIRCLE 82 ON FREE
INFORMATION CARD**

CAMERA/CAMCORDER BAGS

Designed specifically for customers seeking specialty equipment storage and portability, these five nylon camera/camcorder bags are loaded with pockets that carry 35mm SLR cameras or compact camcorders, and all the accessories the photographer needs. The *CBV-1* and *CBV-2* Camera/Video bags are padded for extra protection, feature a shoulder strap, compartments for film, and adjustable dividers.



The *CBV-10*, *-11*, and *-12* are targeted for camcorder users. Features include thick padding, a panel for business cards, inner panel pockets, nylon mesh pockets on both ends for batteries and film, and a protective armored and waterproofed bottom. In addition, the *CBV-11* has a detachable case so when all the extra accessories aren't needed, the camcorder carrier can be used alone. The *CBV-12* offers extra protection with pull-over security flaps and safety buckles.


Prices range from \$19.99 for the *CBV-1* to \$49.99 for the *CBV-12*. Contact Case Logic, 6303 Dry Creek Parkway, Longmont, CO 80503; Tel: 800-925-8111 or 303-530-3800; Fax: 303-530-3822; Web: www.caselogic.com for more information.

CIRCLE 83 ON FREE INFORMATION CARD

SCOPE ON A DISK

The *uScope* is one of a series of eight multifunctional computer-controlled measuring instruments available from *T P Engineering*. It is a single-channel unit with eight-bits resolution that plugs into the printer port of a desktop, laptop, or notebook computer. Measurements are derived by sampling the input signal; digitizing the values; and processing, saving, and displaying them.

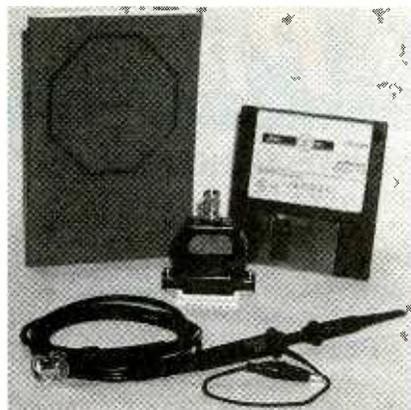Performing effective sampling at 100,000 samples per second, the *uScope* can be used as an oscilloscope, storage oscilloscope, spectrum



analyzer, true RMS voltmeter, or transient recorder—with the accompanying software. Other values, such as temperature, pressure, and frequency, can be measured as well, since the software allows the instrument to be reconfigured to do so.

The program can be controlled by mouse or by cursor keys. Collected data can be directly recorded onto disk or printed out. There is an option to write additional software in C, Pascal, or Basic.

The *uScope* with disk and manual costs \$170. For more information, contact T P Engineering, 239 Park Avenue, Berkeley Heights, NJ 07922; Tel: 908-464-5486.

CIRCLE 84 ON FREE INFORMATION CARD

ACCESSORY KITS

ITT Pomona recently introduced an assortment of *Test Companion Kits* specially designed for the most popular Fluke, Hewlett-Packard, Tektronix, and Wavetek benchtop DMMs. The durable, lightweight accessory pouch mounts easily on top of the instrument. Multiple zippered compartments for convenient accessory storage are included.



The 6176 *Test Companion Kit* is specifically designed for use with Fluke 45, 8840, 8842, and PM2525 benchtop multimeters. The kit includes a safety


sheath style flexible test lead set, test probe handle set with banana plug tip, medium alligator clip set, Maxigrabber with pincer tip, and insulated spade lug set. The 6177 *Test Companion Kit*, which is compatible with the same Fluke multimeters, includes a wider selection of lab and benchtop accessories.

The *Test Companion Kits* range in price from \$88 to \$112. Contact ITT Pomona Electronics, 1500 E. Ninth Street, Pomona, CA 91766-3835; Tel: 909-469-2900; Fax: 909-629-3317; Web: www.ittpomona.com.

CIRCLE 85 ON FREE INFORMATION CARD

MINI-STICK METERS

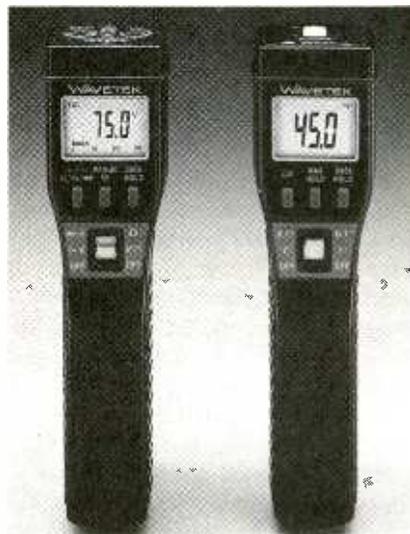
Traditional handheld DMMs have to be laid aside while the technician is holding the test leads. *Wavetek's* uniquely shaped digital multimeters, the *ST75* and *TM45*, allow the user to simultaneously hold the meter safely and read the display.



A complete volt/ohm stick DMM, the *ST75* features digital and analog bargraph display, 3200-count resolution, autoranging, data hold, quick continuity checking, and diode testing. It measures DC and AC voltage up to 600 volts and resistance up to 32 megohms. Geared to commercial and industrial applications, the *TM45* is a digital thermometer with a wide temperature range up to 2000° Fahrenheit and 1300° Celsius and is capable of data and maximum display hold. Temperature measurement is switchable between Fahrenheit and Celsius, and the device is compatible with Type K-thermocouples.

(Continued on page 54)

BUILD THIS PORTABLE CD AMP

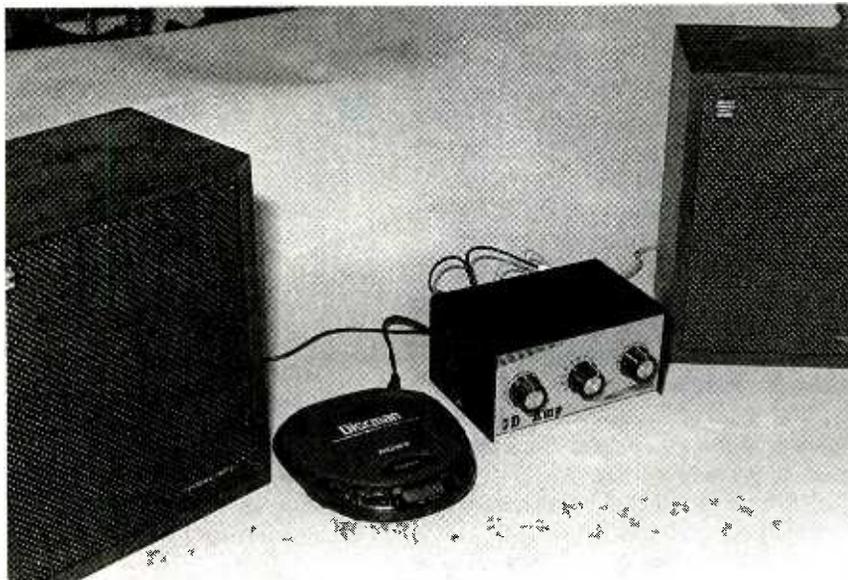

With nothing more than a pair of low-wattage speakers and this little amplifier, you can use your portable CD player to fill your patio, backyard, or any room in your home with your favorite music.

HOMER L. DAVIDSON

Like the Walkman, personal CD players have become an intricate part of the exercise regimen of the health conscious. But once you've finished that two mile jaunt, it would be nice to just sit back and, while unleashed from your CD player, listen to some good music. Of course, portable CD players can be connected to your full-size audio-component system. But that often requires climbing over furniture or moving furniture around in order to get at the line inputs at the rear of your audio system. And what if you want to sit out on the patio or in your backyard while you relax to some soothing sounds—do you lug your full-size speakers, connected to your in-house stereo system through about a "mile and a half" of speaker cable, out back so that you can lounge in your hammock while the music takes you away?

With the *Portable CD Amp* described in this article, you needn't deal with any of the difficulties that might be encountered when trying to connect a portable CD to a stationary audio system. The stereo outputs of the Portable CD Amp pumps out plenty of volume for its size—four watts of crisp clean audio that can be used to drive a

pair of small 8-ohm speakers—and features a dual-tone control. Best of all, this small amplifier, which can be built for less than 20 bucks, allows you to enjoy your portable CD player unencumbered by its "mooring lines."

Circuit Description. A schematic diagram of the Portable CD Amp is shown in Fig. 1. At the heart of the circuit is an LM2877 dual four-watt audio power amplifier (IC1), which is designed to deliver 4 watts of continuous power per channel into an 8-ohm load. Each of the amplifiers within that single-inline monolithic chip—which can be operated from a 12- to 20-volt power source and requires few external components—is biased from a common internal regulator to provide high power-supply rejection.

The stereo output of the portable CD player is applied to the Portable CD Amp through a stereo patch cord that connects to J1 and J2 (the left and right channel inputs to the stereo amplifier). The volume for the two channels is controlled via a pair of 100k potentiometers (R1 for the left channel and R10 for the right channel). From the volume controls, the left- and right-channel

signals are coupled through a pair of capacitors (C1 and C6) to pins 4 and 8 of IC1. Those capacitors allow the audio signals to pass, while blocking any DC component that may be present in the audio input. Note that the input to IC1-a is applied to its inverting-input terminal at pin 4, while the input to IC1-b is applied to its non-inverting terminal at pin 8.

The other inputs to the two amplifiers (at pin 5 and pin 7) are connected to a dual tone-control circuit—one built around R3-a (the left channel) and the other built around R3-b (the right channel). Since the two channels are nearly identical (except that one channel uses the non-inverting input to the amplifier, while the other uses the amplifier's inverting input), from here we'll refer only to the left channel of the circuit. However, anything said about the left channel also applies to the right channel.

The output of the amplifier (IC1-a) divides along two paths. In one path, the amplified output of IC1 is fed back to the left channel tone-control network, which is comprised of R2, R3-a, R4-R6, and C2-C4. The circuit, which is essentially a variable passive RC filter, is used to select the

frequency of the feedback signal. The selected feedback frequency is applied to the non-inverting input of IC1-a at pin 5. That decreases that frequency's presence in the output signal. (In the right channel, the feedback signal is applied to the inverting input at pin 7, and the direct signal is applied to the non-inverting input at pin 8 and produces a similar effect in that channel.) In the other path, the frequency-adjusted output of the amplifier at pin 2 is fed through a 470- μ F capacitor (C12) to the output jack (J3), and is used to drive an 8-ohm speaker.

The Portable CD Amp can be powered from an appropriate 12-volt battery source or from a DC power supply like that shown in Fig. 2, which is comprised of a 12-volt, step-down transformer (T1), a full-wave bridge rectifier (consisting of four 1N4002 1-amp, 100-PIV rectifier diodes, D1-D4), and a 6800- μ F filter capacitor (C16). The circuit in Fig. 2 provides an output of 18.6 volts to

operate the Portable CD Amp (draws under 100 mA at mid-volume). You can build a similar power supply or operate the circuit from a plug-in DC power pack. When S1 is closed, power is fed through the switch to pin 11 of IC1, energizing the circuit.

Construction. The Portable CD Amp was assembled on a printed circuit board, measuring 3 by 5 1/16 inches. A template of the author's printed-circuit layout is shown in Fig. 3. That layout can be copied from the page and used to etch your own printed-circuit board. Once you've etched your board and obtained all of the components listed in the Parts List, construction can begin.

The parts-placement diagram for the author's printed-circuit layout is shown in Fig. 4. Start by installing the passive components, and then connect lengths of hookup wire where off-board components are indicated.

Carefully mount and solder IC1

to the circuit board in the location indicated in the parts-placement diagram. IC1 is soldered directly to the printed-circuit board. All of the components, with the possible exception of the LM2877, can be found at your local electronic sup-

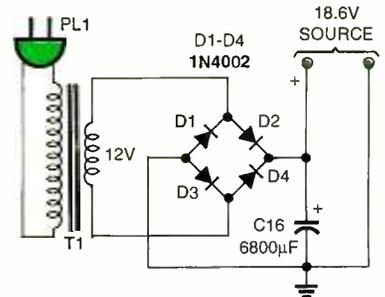


Fig. 2. The author's version of the Portable CD Amp was powered from a 12-volt DC power supply comprised of T1 (a 12 volt, step-down transformer), D1-D4 (four 1N4002 1-amp, 100-PIV rectifier diodes, which form a full-wave bridge rectifier), and C16 (a 6800- μ F filter capacitor).

PART LISTS FOR THE PORTABLE CD AMP

RESISTORS

(All fixed resistors are 1/2-watt, 5% units.)
 R1, R10—100,000-ohm, audio-taper potentiometer (see text)
 R2, R13—1000-ohm
 R3—100,000-ohm dual-gang potentiometer (see text)
 R4, R14—10,000-ohm
 R5, R12—470,000-ohm
 R6, R11—51,000-ohm
 R7, R8—1-megohm
 R9, R15—2.7-ohm

CAPACITORS

C1, C6, C13, C14, C15—0.1- μ F, ceramic-disc
 C2, C7—100- μ F, 35-WVDC, electrolytic
 C3, C8—0.33- μ F, ceramic-disc
 C4, C9—0.033- μ F, ceramic-disc
 C5—47- μ F, 35-WVDC, electrolytic
 C10—3300- μ F, 35-WVDC, electrolytic
 C11, C12—470- μ F, 35-WVDC, electrolytic
 C16—6800- μ F, 50-WVDC, electrolytic

ADDITIONAL PARTS AND MATERIAL

IC1—LM2877 dual 4-watt, audio-power amplifier, integrated circuit
 J1-J4—Shielded RCA jack
 J5—Insulated power jack
 S1—SPST switch (part of R1, see text)
 Printed-circuit material, pair of 4 \times 6-inch (or larger) 8-ohm speakers, 3 1/16 \times 6 1/4 \times 4 1/8-inch metal enclosure, heatsink, wire, solder, hardware, etc.

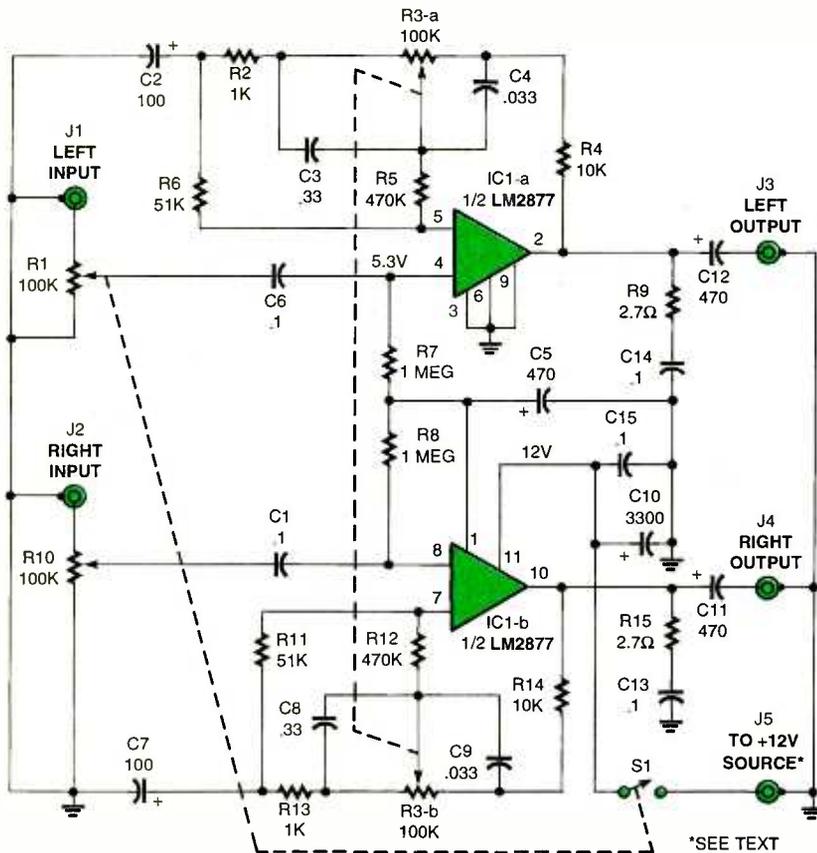


Fig. 1. At the heart of the Portable CD Amp is an LM2877 dual four-watt audio-power amplifier (IC1), a single-inline monolithic chip that requires few external components and can be operated from supply voltages ranging from 12- to 20-volts.

ply house. If your local supplier does not carry the LM2877, it can be obtained by mail-order from either Digi-Key Corporation (701 Brooks Avenue South, Thief River Falls, MN 56701-0677, Tel. 800-344-4539) or Jameco Electronic Components (1355 Shoreway Road, Belmont, CA 94002-4100, Tel. 800-831-4242). After soldering IC1 to the printed-circuit board, check between each terminal with an ohmmeter for shorted connections. You should have no measurement below 1k between any two terminals. If you find two terminals that are soldered together, remove the excess solder with the soldering iron and solder wick. Once that is done, connect the tab of the IC to a large heatsink with a couple of screws and secure the heatsink to the board with appro-

priate hardware.

Next wire the off-board components to the circuit through appropriate lengths of hookup wire. Note that while R1, R3, and R10 have the same value, they are not interchangeable; R3 is a dual-gang 100k unit, R10 is a plain ol' vanilla component, and R1 has switch S1 piggy-backed to it. Of course, the R1/S1 combination could be replaced by separate units if desired. The choice is yours. In any event, connect a pair of RCA jacks (for J1 and J2) to one end of both R1 and R10, and ground the other ends of the potentiometers as well as the free terminals of the jacks. Then connect the wipers of the two potentiometers to the appropriate points on the circuit board. Connect another pair of RCA jacks to the circuit where J3

and J4 are indicated. Connect the final jack (J5) to S1.

Testing. Double check all wiring before testing the amplifier. Apply a +12-volt source to J5. Connect a pair of 8-ohm speakers to the left- and right-channel outputs, J3 and J4. Always have both speakers connected before powering up the Portable CD Amp as the CM2877 may be damaged if the volume is turned up and the speakers are missing. Set the volume controls to about midrange, and flip S1 to the on position. You should hear a very low hum in each speaker. Lightly touch one of the shielded input jacks (J1 or J2). Touching the jack should cause the volume of the hum in that channel to increase. Test the second channel input in the same manner.

If the circuit does not respond as expected—i.e., no hum is heard at either speaker—check the voltage at the positive terminals of C10 and C15; you should get a reading of 12 volts at both points. Suspect a leaky IC or improper IC connections if the voltage at pin 11 is low. If you get a proper reading, check the voltage at each terminal of IC1. The voltage at pins 5 and 7 should be 5.9 volts; pins 4 and 8 should be at 5.3 volts; and pins 2 and 10 should be at 5.97 volts. If those points check out, turn off the power and measure the circuit's resistance from the power supply input (J5) to ground; you should get a reading of over 5k. Check the printed-circuit wiring for poor solder connections. When one channel is dead or has minimum volume, suspect a defective IC, connecting part, or improper connection. The voltage and resistance should be the same for each channel.

Once the circuit is functioning properly, prepare the enclosure that will house the circuit board. The author's unit was housed in a $3\frac{1}{16} \times 6\frac{1}{4} \times 4\frac{1}{8}$ -inch metal cabinet. Three appropriate sized holes were drilled in the front panel of the enclosure to accommodate the three potentiometers, R1, R3, and R10. Five holes were drilled in the rear panel to accommodate the jacks: four for the left and right channel input and output jacks, and one for the power jack. Additional holes were drilled in

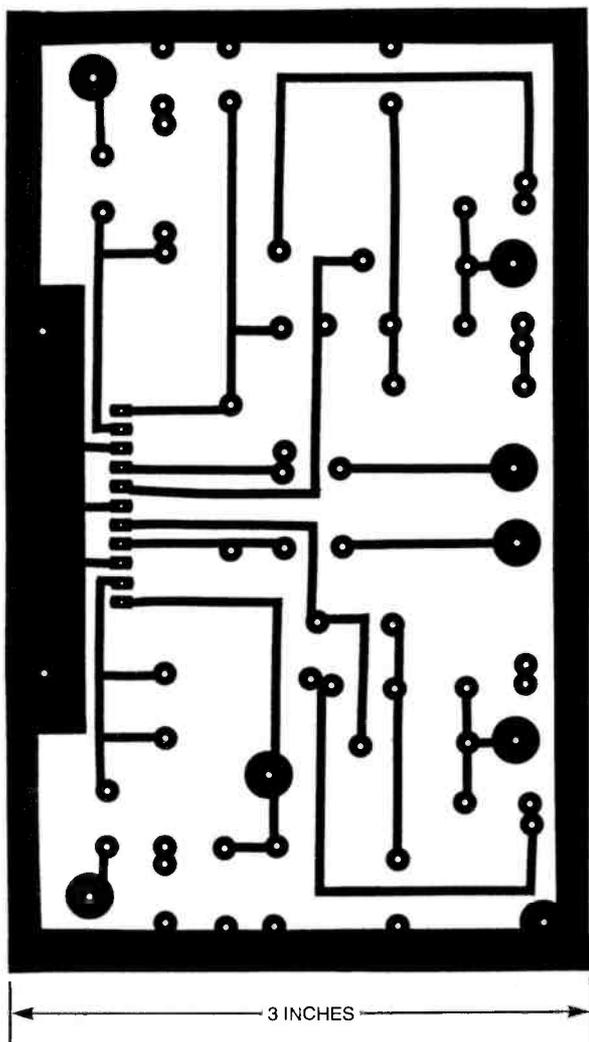


Fig. 3. The Portable CD Amp was assembled on a printed-circuit board, measuring 3 by $5\frac{1}{16}$ inches. A template of the author's printed-circuit layout is shown here full-size.

the floor of the enclosure for mounting hardware for the printed-circuit board. The board was mounted on 1/4-inch spacers to the bottom of the cabinet.

The front and rear panels of the

Portable CD Amp's enclosure can be labeled using dry-transfer lettering. Labeling the rear panel jacks will help to prevent the amplifier from being hooked up improperly. Labeling the front and rear panels

of the unit helps to enhance its appearance.

Once the circuit has been tested and mounted in its enclosure and you have made any cosmetic adjustment that you care to make to the enclosure, the Portable CD Amp is ready to pump out your favorite tunes in any location that you choose. ■

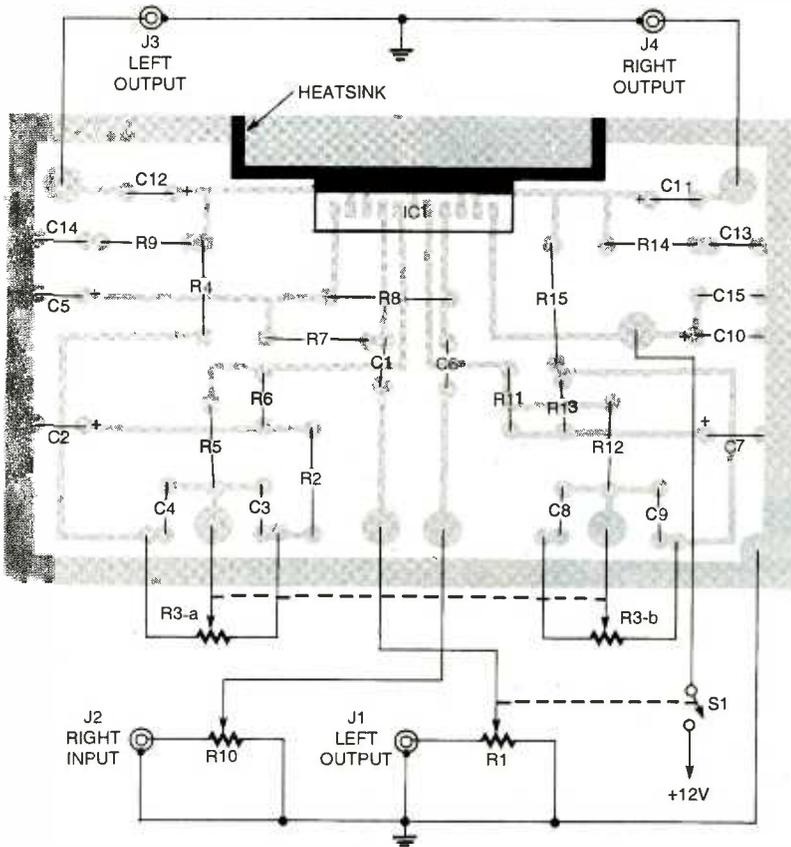


Fig. 4. Assemble the Portable CD Amp guided by this parts-placement diagram. Since the LM2877 is mounted directly to the board, be careful the chip is properly oriented before soldering it into place; when soldering the IC to the circuit board, be extra careful not to overheat the leads of the component, as overheating the leads can cause damage to the chip.




When taking resistance measurements, be sure to turn power to the Portable CD Amp off; failing to do so will damage the resistance measuring circuitry of the meter. When taking voltage measurements be sure that the meter is set to the DC scale and on a range that is higher than the anticipated voltage in the circuit.

ELECTRONICS LIBRARY

(continued from page 36)

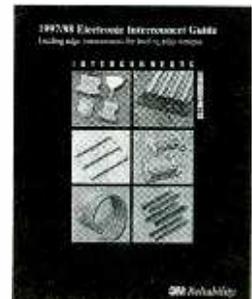version of the full 3M catalog. It has information on interconnect system connectors; assembly equipment; cable; fiber-optic products; heat-shrink products; tape, terminals, and tools; wire connectors; and wire identification products. It includes product descriptions and photos, as well as complete ordering information. The catalog is three-hole drilled for convenient storage.



Organized by application, it includes 3M distributor and international location contact information. The catalog contains several indexes for ease of use, including a part number index, a general index, and a technical service drawing index. For those who require them, the latest technical service drawings can be downloaded from the 3M Web site.

1997/98 Electronic Interconnect Guide is free upon request and is published by 3M Electronic Products Division, 6801 River Place Blvd., Austin, TX 78726-9000; Tel. 800-328-0016, ext. 114; Web: www.mmm.com/interconnects. ■

BooksNow

To order books in this magazine or, any book in print. Please call anytime day or night: (800) BOOKS-NOW (266-5766) or (702) 258-3338 ask for ext. 1454 or visit on the web at <http://www.BooksNow.com/popular-electronics.htm>.

COMPUTER BITS

Microcontrollers II

JEFF HOLTZMAN

My original concept for this series on microcontrollers was to cover the extremely popular PIC series. However, I am unquestionably late to the party. There is lots of good information to be had on the PIC, including the books (discussed last month) published by Square One Electronics, and tons of sources all over the Internet.

Instead, I have decided to change gears and talk about a different chip family: Atmel's AVR series, in particular, the AT90S1200. I didn't pick that device at random. The chip itself has an amazing set of capabilities, it is (relatively) new, and it hasn't been fully dissected like the PIC family. This month I'll give an overview of the 1200. Next time—I promise—we will start getting our hands dirty.

OVERVIEW

The AT90S1200 is a 20-pin device available in 0.3-inch Dual-In-Line Package (PDIP) form, in Shrink Small Outline Package (SSOP), and in Small Outline Integrated Circuit (SOIC) packages. It is fully CMOS—the clock may range from 0–16 MHz, and power source ranges from 2.7–6.0 VDC.

Other features include a built-in 1-MHz (approximate) RC oscillator (so the chip can literally run stand-alone, with no external components), and optional operation with a crystal or ceramic resonator. In addition, the 1200 includes: 15 latched general-purpose I/O lines (each with 20 mA of current-sinking capability, or 140 mA total), 1K bytes of flash, 64 bytes of EEPROM, internal and external interrupts, a watch-dog timer, an 8-bit counter/timer (with prescaling), two low-power modes, and an analog comparator.

Architecturally, the 1200 contains 32 8-bit registers, an 8-bit data bus, and a three-level hardware stack (I hate that). It has four separate memory spaces: flash (where programs run); EEPROM (data storage); and an I/O space for accessing interrupt control registers, port control registers, timer/counter, watch-dog timer, comparator functions,

and so on. The fourth memory space contains three registers with device-code information, such as manufacturer, device type, and flash size. The program space (flash) is 16 bits wide, so the 1K of flash is somewhat misleading. It actually provides 512 words of program code. The program counter is 9-bits wide, as is the stack.


The 1200 can be programmed in two ways—via serial (SPI) and parallel interfaces. Serial mode is designed for in-circuit updates; only normal V_{CC} is required. Parallel mode requires a +12-VDC source (used as an enable signal and not to power anything heavy-duty), provides faster operation, and allows

access to the 1200's "fuse bits," which cannot be changed otherwise.

The fuse bits (RCEN and SPIEN) control two aspects of operation. RCEN enables the on-board RC oscillator. SPIEN enables serial programming mode. By default, RCEN is erased, disabling the oscillator, and SPIEN is programmed, enabling serial programming. The 'A' version of the 1200 comes with RCEN programmed.

A separate set of bits provides three program locking modes: unlocked (default), locked, and locked plus verify disabled. When locked, flash cannot be programmed. The program memory

(Continued on page 46)

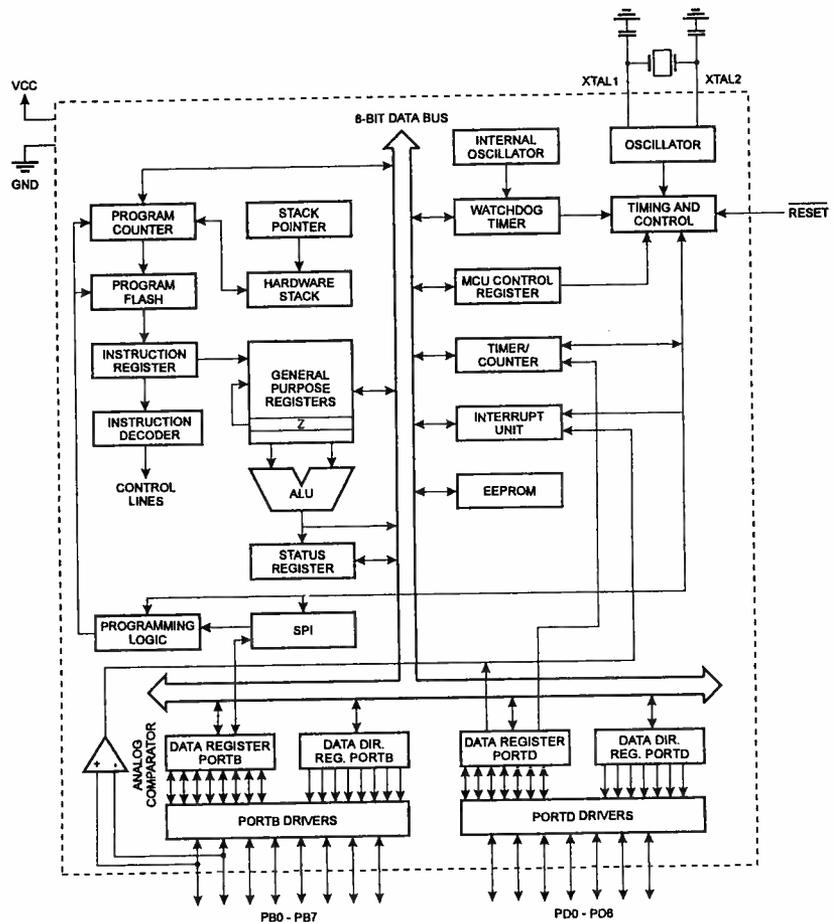

The Atmel/MVS 1200 microcontroller block diagram. This microcontroller can run with no (!) external components, provides 15 bits of I/O, has 512 words of flash program memory, 64 bytes of EEPROM, an analog compactor, and supports in-circuit programming. With care, you can program it directly via the serial or parallel port of a PC.

Multimedia Watch

A DVD-ROM Kit, a Wireless PC, and New Software

MARC SPIWAK
ASSOCIATE TECHNICAL EDITOR
COMPUTER RESELLER NEWS


As I've mentioned before, one of the best things about writing this column is getting all of the new equipment to test. But the downside is that I usually have to return the hardware. Such was the case with my *Hi-Val DVD* upgrade kit that I had to return recently. That single package let me play DVD movies on my PC, transmit them to my home entertainment system and watch them on a big-screen TV.

Fortunately for me, I'm always getting new gadgets, and the new stuff is usually better than what it replaces. I recently received two new products that let me duplicate the functions of the *Hi-Val DVD* kit, and do a lot more as well. I'm talking about Creative Labs' *PC-DVD Encore Dxr2* DVD-ROM kit and RF Link Technology's *Wireless PC@TV* system.

PC-DVD ENCORE DXR2

Creative Labs' new *PC-DVD Encore Dxr2* is a complete DVD upgrade kit for the PC. It includes a second-generation DVD-ROM drive that runs at 2× (for DVD that is), and it also doubles as a 20× CD-ROM drive that can read CD-R discs as well as most other formats. It also has a fast access time of 100 milliseconds. The DVD-ROM drive in the *Hi-Val* kit was a first-generation 1× DVD-ROM drive that could not read CD-R discs, and its maximum CD-ROM speed was only 8×. I receive a lot of software on CD-R discs, so it's a real pain in the neck for me if a drive can't read them. The drive in the Creative bundle can substitute for a regular CD-ROM drive.

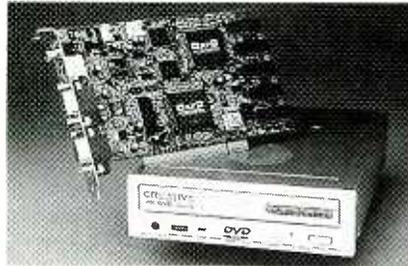Creative's DVD-ROM drive is bundled with a PCI-based Dxr2 card that includes MPEG-2 and Dolby Digital decoding plus picture enhancement technology. DynamicXtended Resolution (Dxr2) uses vertical and horizontal interpolation filters and double-scanning up to 60 fields/second to eliminate artifacts at Windows resolutions up to 1280 × 1024. The Dxr2 card also



Creative Labs' *PC-DVD Encore Dxr2* includes a second-generation DVD-ROM drive that runs at 2× (for DVD) and doubles as a 20× CD-ROM drive that can read CD-R discs.

provides Dolby Digital AC-3 audio decoding for cinema-like surround-sound. The audio is down-mixed to two channels on a PC, or it can be decoded into 5.1-channel surround sound, using a Dolby Pro Logic decoder.

Creative's *Encore* bundle is a DVD player for a PC, with a resolution-enhanced image that plays in a resizable window. But it's also a DVD player for a TV, because the Dxr2 card has S-video and composite outputs. Connectors on the card bracket include an RCA jack S/PDIF output, a VGA output, VGA input, and S-Video and composite video outputs. There are onboard connectors for an audio output to a sound card, an audio input from the DVD-ROM drive, and an audio input from a regular CD-ROM drive. An easy-to-use software control panel features a directional pad, status display, playback buttons, volume control, and menus for customizing settings such as audio, color, and display mode. DVD-ROM games such as *Claw* and *Wing Commander IV* are bundled with the package. The Creative DVD bundle will run you \$379.99.

WIRELESS PC@TV

Creative Labs' DVD bundle puts me back in business as far as DVD is concerned, but it can't transmit video to my TV, and it comes with a relatively short video output cable for connecting to a TV. Enter RF Link Technology and its


Wireless PC@TV. This package includes the same Wavecom Sr. wireless audio/video transmitter that came with the *Hi-Val DVD* kit, so I can again broadcast DVD video—or any video—to my TV set. But the *Wireless PC@TV* bundle also lets me enjoy the Internet, computer games, and more, all on my TV set.

The *Wireless PC@TV* bundle includes the wireless audio/video transmitter and a wireless keyboard/mouse. Wavecom Sr. transmits a computer's video and audio through walls to a television in another room. One of the Wavecom Sr.'s more advanced features is that it can also relay infrared remote control signals to a device in another room. *PC@TV* takes advantage of that feature by sending commands from a wireless keyboard to the PC. So the user can sit in the living room watching the video output from the PC on a big-screen TV while controlling the PC with the wireless keyboard and its built-in mouse. Special software by Vidam Communications, Inc. conditions web pages and text for clear viewing on a TV set.

Aside from being couch-potato friendly, *Wireless PC@TV* is also very useful for delivering business presentations. It has a transmission range of up to 100 feet through walls, floors, and ceilings, and the *PC@TV* bundle includes all necessary hardware, software, and accessories. It's a very useful bundle for \$599.99.

SLIMSCSI

Notebook computers are quite powerful these days, and it would be nice if you could use fast desktop SCSI peripherals with them. Of course you can, with Adaptec's *SlimSCSI 1480* PC Card SCSI adapter. It connects to any SCSI device and delivers PCI desktop performance to the portable PC with data transfer rates up to 20 MB/second with UltraSCSI devices, and up to 10 MB/second with Fast SCSI devices. Up

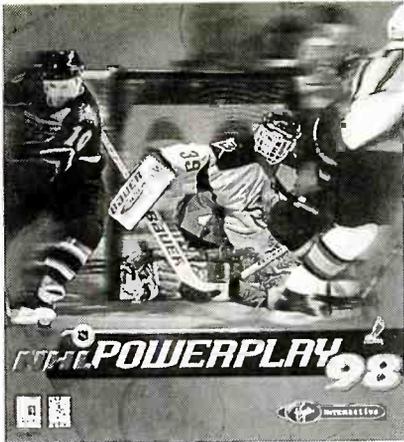

NHL Powerplay '98 features the actual styles and abilities of every player in the NHL. Accurate skating physics create realistic action.

to three SCSI devices can be daisy-chained. The Type II PC Card will work in any notebook computer with a CardBus-enabled PC Card slot. It's not every day that I need to use *SlimSCSI*, but if I ever need to connect a tape backup, CD-R drive, or other SCSI peripheral to my notebook computer, *SlimSCSI* will let me do it. The manufacturer's suggested retail price (MSRP) is \$239.

NEW SOFTWARE

Symantec's *Norton Uninstall Deluxe* is a safe way to make changes on any Windows 95 or Windows NT 4.0 system, including both removing and adding programs and files. InstallGuard lets you remove the last installation and return a system to its original state. SafetyScan ensures accurate knowledge of your system and configuration for a safe and complete Remove, Move, Copy and Store of all applications and files—even ones that were on the system before Norton Uninstall Deluxe. Autoclean automatically frees up space on a hard disk by removing unnecessary files each time the system boots. This program will remove \$39.95 (MSRP) from your wallet.

If you've had your share of computer problems, *CheckIt* (version 5) for Windows 95 from TouchStone Software provides tools to help pinpoint and solve those problems, backup and restore system files, install new hardware, uncover conflicts, and optimize system performance. *CheckIt* offers comprehensive information displays identifying everything users need to know about their motherboard, memory, modem, drives, video, ports, printer,

and Internet connections. *CheckIt* monitors all system resources, highlights conflicts, and guides the user through the repair. *CheckIt* automatically saves Windows Registry and critical system files so users always have a recent backup. *CheckIt* version 5 is \$49.95.

If you like to play Monopoly but would rather watch Star Wars, then maybe *Star Wars Monopoly* can pry you away from the big screen. This neat game from Hasbro Interactive has you playing a multimedia version of the famous real-estate trading game. But instead of trading depression-era real estate on earth, you are in a galaxy far, far away, vying for your favorite Star Wars real estate on a quest to conquer the galaxy. C-3PO is there in his ever-polite form as an intergalactic banker. Galaxy trading starts at \$49.99.

Sabre Ace: Conflict Over Korea from Virgin Interactive gives you a chance to

be a fighter pilot during the Korean War. Battle in an F-86 Sabre jet or choose from four other planes: the F-51 Mustang, the F-80 Shooting Star, the MiG-15, or the YAK-9. You fly as a U.S. fighter pilot in the Mustang, Shooting Star, and Sabre, or in the Soviet military aboard the YAK-9 and MiG-15. You can even engage in dogfights with friends via modem, serial, or LAN connections. Design your own dogfights or jump right into combat—it's all up to you. For an estimated street price (ESP) of \$44.99, you too can enter the dogfights.

NHL Powerplay '98, also from Virgin, is just what hockey fans have been waiting for. This sequel to *NHL Powerplay '96* is better than ever. Different players have their own particular styles in the game, and the action is modeled after the real players' styles. The actual styles and abilities of every player in the NHL delivers the most realistic PC hockey

WHERE TO GET IT

Activision

11601 Wilshire Blvd., Suite 1000
Los Angeles, CA 90025
310-255-2000
www.activision.com

**CIRCLE 60 ON FREE
INFORMATION CARD**

Adaptec, Incorporated

691 South Milpitas Boulevard
Milpitas, CA 95035
408-945-8600
www.adaptec.com

**CIRCLE 61 ON FREE
INFORMATION CARD**

Creative Labs

1901 McCarthy Blvd.
Milpitas, CA 95035
800-998-5227, 408-428-6600
www.creativelabs.com

**CIRCLE 62 ON FREE
INFORMATION CARD**

Hasbro Interactive

50 Dunham Road
Beverly, MA 01915
508-921-3700
www.hasbro.com

**CIRCLE 63 ON FREE
INFORMATION CARD**

LucasArts Entertainment Company

PO Box 10307
San Rafael, CA 94912
415-472-3400
www.lucasarts.com

**CIRCLE 64 ON FREE
INFORMATION CARD**

RF Link Technology, Inc.

411 Amapola Ave.
Torrance, CA 90501
310-787-2328
www.rlinktech.com

**CIRCLE 65 ON FREE
INFORMATION CARD**

Symantec Corporation

10201 Torre Avenue
Cupertino, CA 95014
800-441-7234
www.symantec.com

**CIRCLE 66 ON FREE
INFORMATION CARD**

TouchStone Software

2124 Main Street
Huntington Beach, CA, 92648
800-932-5566, 714-969-7746
www.touchstonesoftware.com

**CIRCLE 67 ON FREE
INFORMATION CARD**

Virgin Interactive Entertainment

18061 Fitch Avenue
Irvine, CA 92714
714-833-8710
www.vie.com

**CIRCLE 68 ON FREE
INFORMATION CARD**

VtechSoft

5 Corporate Park Drive, Suite 210
Irvine, CA 92606
800-742-1050
www.vtechsoft.com

**CIRCLE 69 ON FREE
INFORMATION CARD**

game ever created. Accurate skating physics create realistic action, and there are five playable camera angles to select from. A multiplayer mode lets you play with up to five friends. The ESP for this game is \$34.99.

Fans of Lucasarts' first two Monkey Island games will find more of the same good fun in *The Curse of Monkey Island*. This time buccaneer LeChuck is attempting to woo Elaine into becoming his undead bride. But a cursed ring slipped on her finger turns her into a gold statue. LeChuck must find a way to remove the curse while battling villains and pirates. This third installment of the Monkey Island game series has players finding objects and solving puzzles in order to finish the game. This installment costs about \$39.95 ESP.

Activision's *Zork Grand Inquisitor* centers around restoring magic to the ailing Great Underground Empire so its inhabitants may be freed from the Dark Ages of Zork. Magic has been outlawed, so players must join forces with the Magic Resistance to battle the Grand Inquisitor's regime. Players travel back to classic Zork eras to recover three magical treasures—the Skull of Yoruk, the Cube of Foundation, and the Coconut of Quendor. *Grand Inquisitor* has a suggested retail price of \$49.95.

Also from Activision comes *Dark Reign* (MSRP of \$49.95), a sci-fi adventure where two armies duel for interplanetary domination. Set in a distant future, players are immersed in a struggle of war, loyalty, and rebellion. Another game from Activision, *Net Storm*, integrates leading-edge game design and sophisticated online capability. The MSRP is \$39.95.

VtechSoft's *Book Buddies* presents classic animated tales to children ages 4 to 7. The CD-ROM features Jack & the Beanstalk, The Three Little Pigs, Three Billy Goats Gruff, and Little Red Riding Hood. The package also includes a 5 1/2-inch plastic figurine character from each story. The characters stand on top of a speaker base that plugs into your sound card, and your PC speakers plug into the base. Somehow the base cuts out the signal going to your speakers at times, and only the character speaks with its voice coming from the base. Kids can also print coloring books, board games, and recipes. *Book Buddies* costs \$39.95.

That's about it for this month—see you in my next column. ■

COMPUTER BITS

(continued from page 43)

lock bits can only be erased (thereby unlocking program memory) via a Chip Erase operation, which can only be performed in parallel programming mode.

The hardware required to implement either serial or parallel programming is simple. In fact, it is possible to implement programming solutions simply by connecting the appropriate lines of the 1200 to the correct pins of a standard serial or parallel port. Not to forget software, of course—details on this next time.

FOR MORE INFORMATION

Atmel Corporation

2325 Orchard Parkway
San Jose, Ca 95131
Tel. 408-441-0311
Web: www.atmel.com

MVS

Box 850
Merrimack, NH 03054 Tel. 508-792-9507
Web: www.star.net/people/~mvs

COMPETITION

The 1200 competes against the PIC family by providing in-circuit programming, more versatile memory, more registers, more I/O, and higher speed. Architecturally, the 1200 is simpler. For example, PICs typically require bank switching to access various memory pages; the 1200 provides free access to all memory at all times.

On the other hand, PICs have plain RAM for temporary storage. However, the 1200's 32 registers compensate pretty well for that. The 1200's 64-byte EEPROM space might seem comparable, but it cannot be accessed at clock speed; typical read and write time runs 2–4 ms, depending on supply voltage. PICs also have an eight-level stack (whew!), as compared with the 1200's three-level stack.

It seems that every microcontroller must have some curious architectural lapse. So far, the only one I've found for the 1200 is that it has no command to load a register from program memory. It can load an "immediate" value, which is really encoded by an assembler as part of the opcode. But there is no way to

create a table of data and index through it. That is a bad characteristic. Why, with so much else going for it, would the designers of this chip do such a thing? Ah well.

WHERE DO I GET IT?

Sound good? I thought so. Now you want to know how to buy one. Getting an Atmel chip may not be so easy. However, a company called MVS is selling, in small (and large) quantities, a variant known as the *MVS1200*. According to an MVS spokesperson, the *MVS1200* is "backwards-compatible" with Atmel's variant. Both devices are based on the same basic design; the MVS version adds a few instructions, but is otherwise totally compatible. We'll be looking more at the differences in future installments; for now, the *MVS1200* will suit our purposes just fine. The *MVS1200* comes with RCEN programmed, so you can literally apply power and run the chip. Contact MVS directly for details and ordering information.

Also, check Atmel's Web site at www.atmel.com for data sheets and application notes. MVS's documentation is Spartan at best, but the Atmel information is pretty well done. See you next time. Meanwhile I will be posting information and links on my Ingeneering Web site (www.ingeninc.com), or contact me at jeff@ingeninc.com. ■



A public service of this magazine

NET WATCH

Sites for Movie Buffs

KONSTANTINOS KARAGIANNIS

We all love movies right? They're a part of our pop culture, an integral piece of our history, and a perfect way to tell a story in a dramatic way. And, oh yeah, there are a *lot* of them out there. Whether you're planning on doing the whole dinner-and-a-movie outing, trying to decide which summer blockbuster to see, or just want a good video to rent, you could easily find yourself overwhelmed with all the choices. Friends' recommendations can only go so far, no?

This month we'll take a look at some great sites on the Net that are so full of film information, it would take an entire lifetime to read just a fraction of the information found on them! And, as films keep coming out, the sites are being updated.


Want to see what movies a particular actor is in? Enjoy a particular director's style and feel like checking out his or her other work? You'll be amazed at how easy the Web makes tasks like these. Further, as we hinted at a moment ago, deciding what movie to see can be difficult at times. That's where reviews come in. Sure, new films are reviewed in just about every newspaper, but what about the ones you missed in the theater?

Enough preamble, though, Hollywood's a fast-paced place, so let's get rolling!

INTERNET MOVIE DATABASE

While there are few sites you can say this about, I find myself tempted to say this of the Internet Movie Database (or IMDb)—if you can't find it here, it might not be out there.

This is the absolute largest database of film information on the Internet and is basically the first place I ever look if I want to know who was in what, *etc.* The opening page might not look like a whole lot graphically, but the site makes up for it with a killer amount of info. As it says at the top of the home page, the site has data on over 120,000 movies! I found it hard to believe there were even

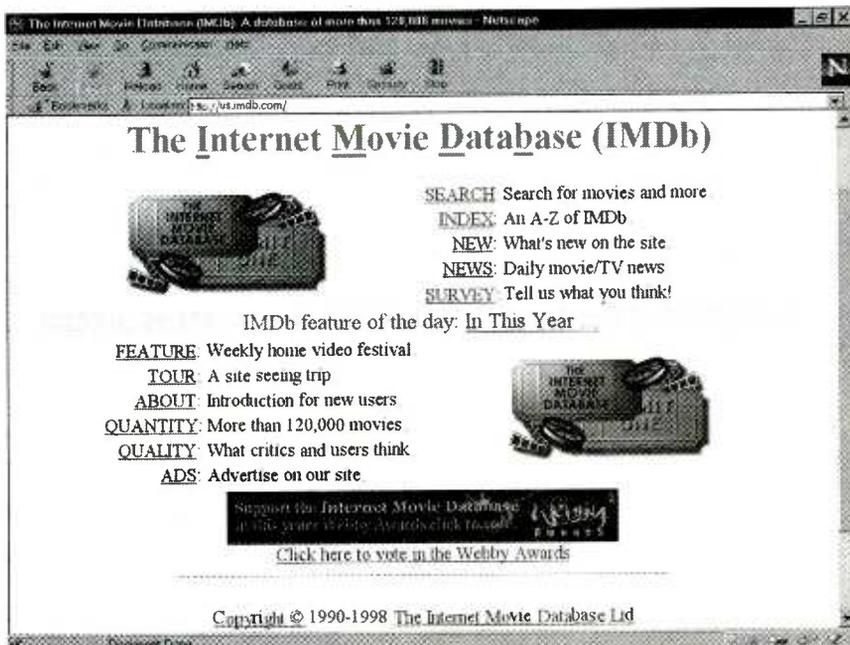

It may not look like much at first, but the Internet Movie Database houses more film information than you could read in a lifetime.

that many films in existence when I first read the figure.

Like all good databases, online or not, the IMDb has an excellent search engine. Click on Search and choose what type of information you are looking for. You can enter title words, actors, directors, and even genre with an amazing amount of specificity allowed (*i.e.*, you can type in "vampire movie" and not just "horror").

When you finally find the movie you're looking for, you'll usually find that there's a plot synopsis/review. A few obscure movies don't have this, but you could always add your own. Some of the descriptions are a little vague, but

as we just implied, they aren't written by pros. Anyone can submit opinions and corrections. It's amazing all the fine details the site crams into each film's description. You can learn the name of most everyone in the cast, and even find out who the people behind the scenes were.

Next time someone tells you there was this great action movie with so-and-so in it, that came out in such-and-such a year, look no further than the IMDb. I don't think I've ever been able to stump it with a query, and I've searched for some pretty bizarre low-budget films, too.

Finally, there's a neat rating system used at the site. Rather than accepting what one critic decided should be the film's star rating (for example, five stars for excellent), the site uses a one through ten system based on people's votes. Could the majority be wrong about a film? Well, okay, they could be, but it's still safer than trusting one person.


The biggest drawback to the site is it doesn't have any images. In this mul-

HOT SITES


Internet Movie Database
www.us.imdb.com

Boxoffice Online
www.boxoff.com

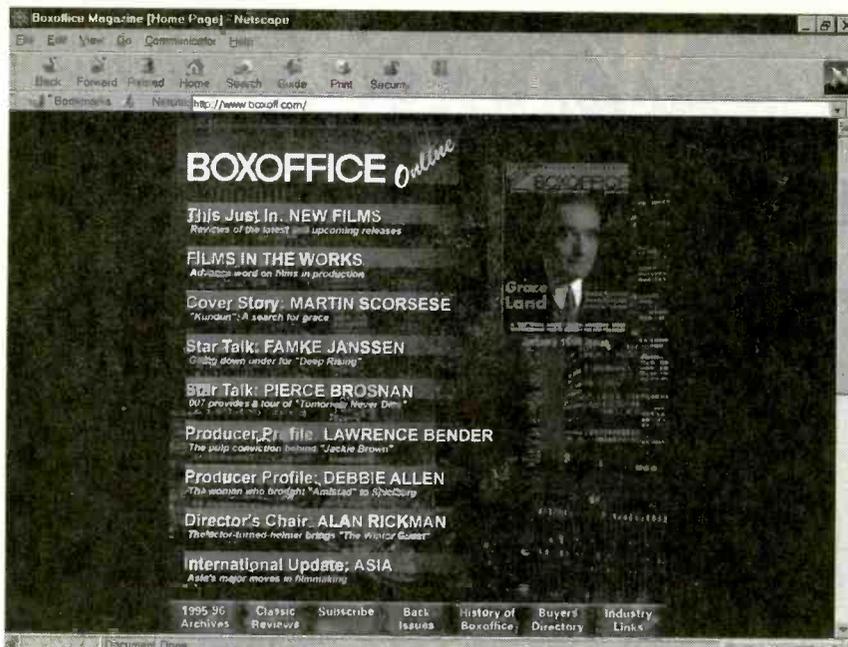99 Lives: The Video Magazine
www.99lives.com



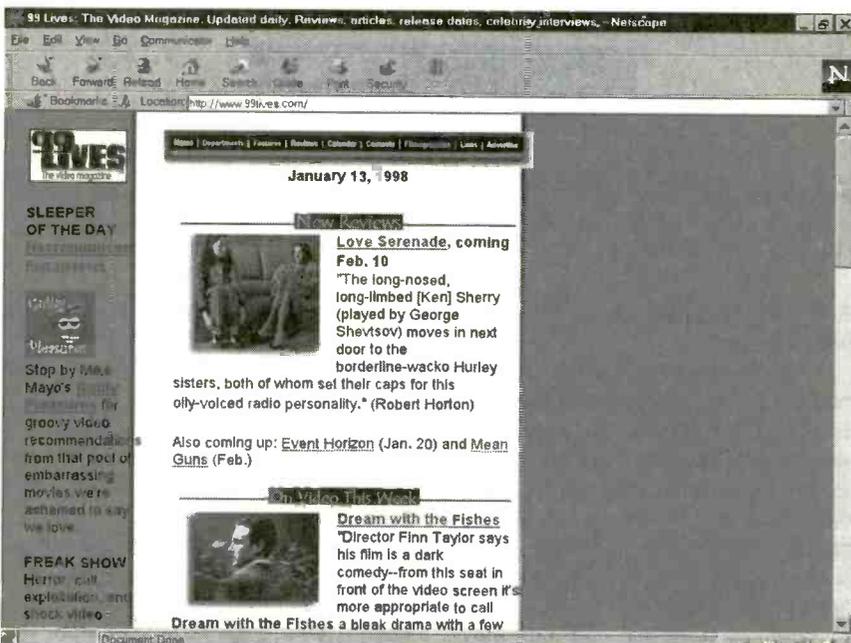Get current or old movie reviews and a whole lot more at the Boxoffice Online site. The articles and interviews are definitely worth a visit.



For those who like to watch movies at home, 99 Lives: The Video Magazine is the site to visit. You'll find release dates, reviews, and articles about the people making movies of all types and budgets.

timedia age, Web surfers just love eye candy or maybe even sound clips. But we'll give the Database a little leeway here—housing multimedia files for over 120,000 movies would challenge even the most impressive Web servers.

BOXOFFICE ONLINE

Sometimes you want deeper information about movies than just who's in them. Want to get more of an inside track to what's happening in Hollywood, check out Boxoffice On-line, the Web

presence of *Boxoffice* magazine. The site contains most of the content from the past three years' worth of issues. Each online issue has articles about up-and-coming films (the link called FILMS IN THE WORKS), and the ones making news today (click NEW FILMS). The Cover Story focuses on a big name or big movie phenomenon in the industry. Star Talk articles are interviews with actors, while Producer Profile and Director's Chair are chats with, well, producers and directors.

If you don't feel like searching through past issues online, you can simply go to the 1995–1997 Review Archives. Or, to speed things up even more, try the downloadable Infoscout software. It's an offline movie-review browser that works with *Internet Explorer*. New reviews are automatically downloaded regularly into the program, allowing you to search reviews offline at your leisure. The Infoscout software and service is free for 30 days and then costs a one-time license fee of \$14.95.

99 LIVES

A similar site to Boxoffice Online is 99 Lives: The Video Magazine. As you might have gathered from the title, there is a significant difference between the two—99 Lives is devoted to movies that are now available on videotape, laser disc, and DVD.

Here's the perfect site to consult before heading out to the video store. Most useful is the site's Calendar, which tells you what movies are coming out on video on what day. It looks as if the site gets its information rather quickly and updates it frequently. In other words, if a release date has been set for a particular title, there's a good chance you'll learn about it here. To help you pick which of these new releases (or old ones) you should get, the site also has Reviews. They're written in a more, shall we say, "hip" style than Boxoffice.

The Features here might seem dated in that they're articles about movies that came out half a year to several years ago, but remember, this is a video magazine. When you head out to *Blockbuster*, you're not looking for information about what's in the theaters. And the Features are pretty interesting. They're usually relevant to the week's new releases, and I think they do a good job of generating a fresh interest in movies just coming out on video.

Some of the articles even deal with technology. I also liked the non-techie Wish List, which is a list of hard-to-find favorites on video and how you can go about actually finding them.

Until next time, hope you have some good experiences checking out the big screen and avoiding the box-office flops. Feel free to e-mail me at netwatch@comports.com or send snail mail to *Net Watch*, **Popular Electronics**, 500 Bi-County Blvd., Farmingdale, NY 11735.

The Quad Loop Revisited

JOSEPH J. CARR

The quad loop antenna (Fig. 1) is a square loop that can be fed on either a horizontal edge (horizontal polarization) or vertical edge (vertical polarization). This type of loop is a "large loop" because it has an overall perimeter of at least one-half wavelength at the frequency of interest. When the loop is this size, the current in the loop is not constant, but rather varies over the length of the wire (as does the voltage). The example shown in Fig. 1 has a total length of 1λ , and is positioned for horizontal polarization.

These antennas were developed in the late 1930s and continue to be popular today. The large loop came into prominence when Clarence Moore, an engineer at missionary shortwave radio station HCJB in Quito, Ecuador, tried to solve a problem with arcing off the ends of half wavelength elements used in Yagi beams. The thin air of the mountain location of HCJB caused corona to develop, and it destroyed the tips of the antenna elements. The antenna designed by Moore was a two element beam made of square quad loops.

Large loop antennas are commonly found in circular, triangular, and square geometries. The square loop is shown here and is the subject of this column; it is probably the most popular because of its relative ease of construction. It has a gain slightly less than 1.8 dB above isotropic (dBi), which means that it exhibits a bit less than the gain of a half wavelength dipole. The feedpoint impedance is close to 110 ohms. The performance difference between square and circular form factors is small, so it is common in antenna engineering books to see the circular analysis being used as an approximation for the square analysis.

The quad loop also produces (like the dipole) a figure-8 azimuthal pattern, and, at higher frequencies, can be easily made rotatable.

FEEDING THE QUAD LOOP

There are two basic feed configurations for the square loop (Fig. 2). In each case, the loop is fed in the center

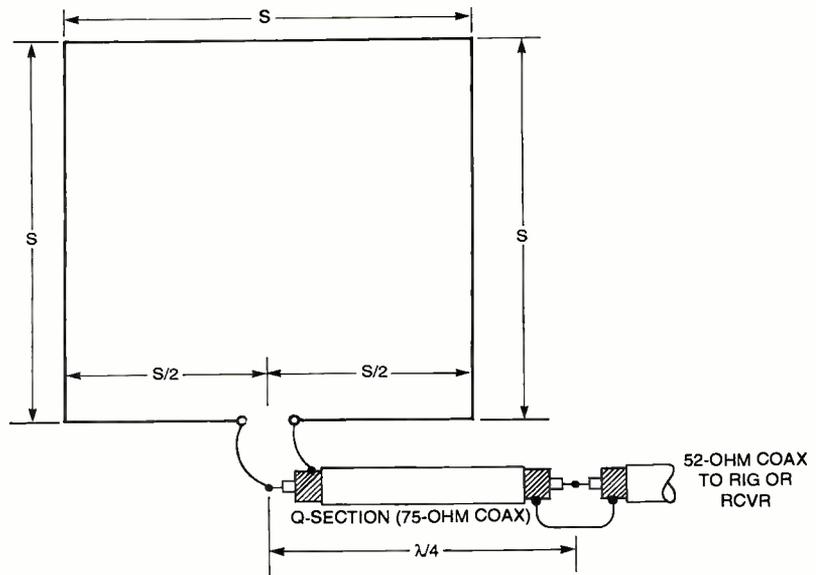


Fig. 1. The one wavelength quad loop antenna is horizontally fed and uses a $(\lambda/4)$ Q-section for matching to 52-ohm coax transmission line.

of one side, which becomes a *de facto* current node. The other current node will appear at the middle of the opposite length, while the voltage nodes appear at the middle of the adjacent lengths. If horizontal polarization of the antenna is preferred, then feed the antenna along either the top or bottom horizontal length (Fig. 2A). Alternatively, vertical polarization occurs when the antenna is fed along either vertical length (Fig. 2B).

The feedpoint impedance of the 1λ loop varies from about 100 ohms to 130 ohms. If we feed these antennas directly with 75-ohm coaxial cable, the VSWR will vary from 1.33:1 to 1.7:1. This range is well within what is normally acceptable for a receiver, and with a line flattener antenna tuning unit (ATU), this antenna can be used with a transmitter.

Because the feedpoint impedance of the square loop is a bit over 100 ohms, using 75-ohm coaxial cable in a "Q-section" (or quarter-wave section of electrical length $\lambda/4$) impedance transformer, creates a decent match to 52-ohm coaxial cable. The coaxial cable is connected to the center point of the bottom

edge (the top edge could also be used). The center conductor of the coax is connected to one side of the loop, while the shield of the coax is connected to the other side of the loop.

The length of each side (S in Fig. 1) is one-quarter wavelength, so the overall length, or perimeter (L), is one wavelength ($L = 4S$). This antenna can be built using 14 gauge copper antenna wire. The values of the lengths are:

$$L = 1005/f_{\text{MHz}}$$

$$S = L/4 = 251.25/f_{\text{MHz}}$$

If you don't care to calculate the lengths, then values across the HF amateur bands are given in Table 1. The values for the sides (S), and overall length, L , where $L = 4S$, are listed (in feet) every 250 kHz. If you want to pick a frequency between these values, then interpolate (split the difference proportionally).

Q-SECTION IMPEDANCE TRANSFORMER

The feedpoint impedance of the one

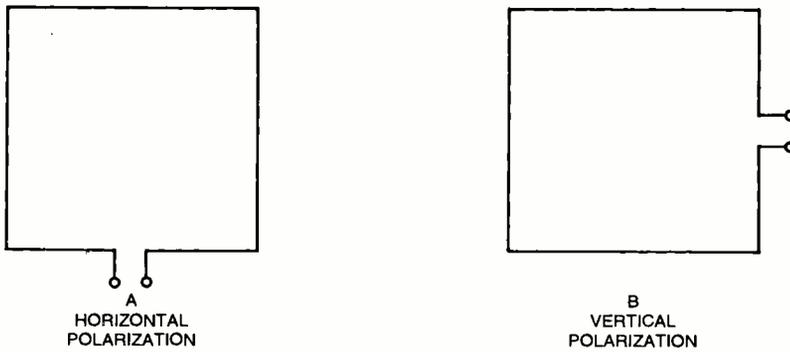


Fig. 2. By feeding the square loop in either horizontal side, as in A, the quad exhibits horizontal polarization; when the feed is changed to either side, as in B, vertical polarization occurs.

wavelength square loop is about 105 ohms, more or less. If you use 75-ohm coaxial cable to feed the antenna, then the VSWR will be (105/65):1 = 1.4:1. This is a reasonable match, and if any particular transmitter is sensitive to this value it can be tuned out using any standard "line flattener" coax-to-coax antenna tuner. If you use 52-ohm coax, the VSWR goes up to 2.1:1.

If you want to make the impedance match closer, then use the Q-section impedance transformer as shown in Fig. 1. The value of the Q-section characteristic impedance is 75 ohms, and the impedance of the line to the transmitter or receiver is 52 ohms. For any Q-section, the value of the impedance required of the coax is:

$$Z_s = \sqrt{Z_o Z_L}$$

where

Z_s is the impedance of the Q-section coax

Z_o is the impedance of the coax to the rig

Z_L is the feedpoint impedance of the antenna

If you work the numbers with $Z_L = 105$ ohms, and $Z_o = 52$ ohms, then the value required of the Q-section (Z_s) is 73.9 ohms, which is close enough to 75 ohms to be considered "right on."

The electrical length of the Q-section is one-quarter wavelength at the frequency of interest. The physical length, however, is a bit less because of the velocity factor of the coaxial cable used for making the Q-section. The velocity factor of polyethylene dielectric coax (the oldest form) is 0.66, while for polyfoam dielectric it is 0.80. Table 2 shows the physical lengths (in feet) for Q-sections at some amateur

radio HF frequencies, for both 0.66 and 0.80 velocity factor coaxial cable.

The quad loop antenna is relatively easy to construct, although more difficult than most dipoles, but a little tricky "to get up in the air." In order to maintain the geometry of the loop, use must be made of dielectric materials or spreaders to support the wire loop above the ground. Many amateurs use the following materials (listed in order of strength and durability): bamboo (cheapest), fiberglass (most popular), or "surplus" pole-vauling poles (expensive and difficult to find).

THE CUBICAL QUAD BEAM

The quad loop antenna can be formed into a beam antenna by adding a second element. Two forms of constructions are seen, although one is more common than the other. The most common form (Fig. 3) places a second element, a parasitic element, in front of, or behind, the *driven element* (which is like Fig. 1). If the parasitic element is in front of the driven element (Fig. 3A), then it is a *director*, and is about 3 percent shorter than the driven element. If the additional element is placed behind the driven element (Fig. 3B), then it is called a *reflector* (about 3 percent longer than the driven element). In both Figs. 3A and 3B the direction of radiation is shown by the arrow.

The other method of construction places the two loops side-by-side and feeds them in parallel, but 180° out of phase. The loops are generally fed from a 1:1 balun transformer through equal lengths of 300-ohm twin-lead transmission line. Twist the line once on each end to provide the phase reversal.

Put all these three elements together

TABLE 1—QUAD LOOP DIMENSIONS (FEET) VS. FREQUENCY

f/MHz	L	S
7.00	143.57	35.89
7.25	138.62	34.66
7.50	134.00	33.50
10.00	100.50	25.13
10.25	98.05	24.51
14.00	71.79	17.95
14.25	70.53	17.63
14.50	69.31	17.33
18.00	55.83	13.96
18.25	55.07	13.77
21.00	47.86	11.96
21.25	47.29	11.82
21.50	46.74	11.69
24.75	40.61	10.15
25.00	40.20	10.05
28.00	35.89	8.97
28.25	35.58	8.89
28.50	35.26	8.82
28.75	34.96	8.74
29.00	34.66	8.66
29.25	34.36	8.59
29.50	34.07	8.52
29.75	33.78	8.45

(reflector, driven element, director) and you have a 3-element quad beam—which some hams say works better than a 4-element Yagi beam.

MY HOBBY HORSE

If you have read my columns over the years you know that I am fond of science fairs for high school and junior high school students. When I was in 7th through 12th grades I entered science fairs (and even took some "paper" home). I now judge science fairs, have counseled a couple of science fair students, and generally support the science fair movement. Recently, a fellow contacted me about the general lack of electronics science fair projects. He is the coordinator of an eight-school district area fair, and a ham radio operator. Although there are lots of computer projects (mostly programming), if it is like our local fair, the number of electronics projects entered is diminishing year after year.

What to do about it? If you are a teacher, or have some other role in the local middle and high schools, then encourage students. If you are a parent or friend of a youngster in the correct age range, then you can also encourage them—and within the limits of the

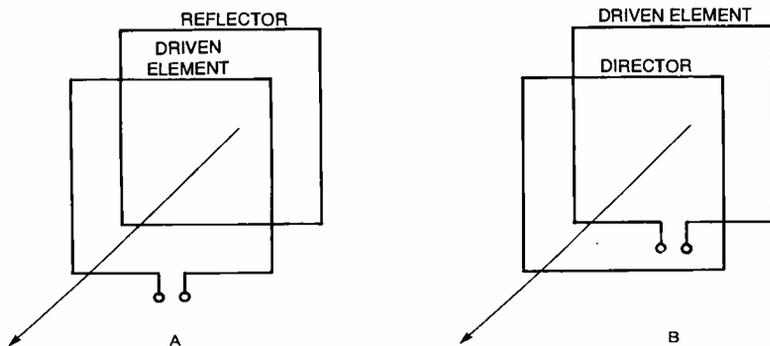


Fig. 3. A two-element cubical quad antenna consists of the driven element and a parasitic element. When the parasitic element is placed in back of the driven one, as in A, it is called a reflector. With the parasitic element placed in front, as in B, it is called a director. Electrical characteristics of both configurations are essentially the same—main beam is perpendicular to the plane of the loops in the direction shown.

TABLE 2—Q-SECTION LENGTH (FEET) VS. FREQUENCY

f _{MHz}	V = 0.66	V = 0.80
7.00	23.19	28.11
7.25	22.39	27.14
7.50	21.65	26.24
10.00	16.24	19.68
10.25	15.84	19.20
14.00	11.6	14.06
14.25	11.39	13.81
14.50	11.20	13.57
18.00	9.02	10.93
18.25	8.90	10.78
21.00	7.73	9.37
21.25	7.64	9.26
21.50	7.55	9.15
24.75	6.56	7.95
25.00	6.49	7.87
28.00	5.80	7.03
28.25	5.75	6.97
28.50	5.70	6.91
28.75	5.65	6.85
29.00	5.60	6.79
29.25	5.55	6.73
29.50	5.50	6.67
29.75	5.46	6.62

rules—assist them in designing and executing a project. This year's science fair season is over by only a few weeks, but the time to start a youngster planning for next year is just beginning.

Even if you are not a teacher or parent of science fair age kids, you can still assist. Contact the science department of your local school, or the science (or science fair) coordinator of your local school board. Schools rarely shun volunteers who want to serve as advisors

or judges.

It is no secret that amateur radio is seeing declining numbers, and that the average age of ham operators is increasing (my average age is certainly increasing!). Technically inclined kids today gravitate towards computers rather than ham radio. Perhaps encouraging the kids to do electronics projects, or better yet radio projects, will help some of them see ham radio as a potential hobby.

I can be reached by snail mail at P.O. Box 1099, Falls Church, VA, 22041, or by e-mail at carrij@aol.com. ■



"To satisfy my taste for adventure, I roam the Internet."

BUGGED??

FAVEDROPPING is unbelievably widespread! Electronic Devices with amazing capabilities can be monitoring your telephone and room conversations RIGHT NOW! Are you sure you're safe? **FREE CATALOG tells you fast!** Includes Free Bonus details on fantastic opportunities now open in Counter-Surveillance field. Exciting, immensely interesting and EXTREMELY profitable (up to \$250/hr) full/part-time income. Call Now! **1-800-732-5000**

CABLE TV CONVERTERS

Equipment & Accessories
Wholesalers Welcome
Call **C&D ELECTRONICS**
1-888-615-5757 M-F 10a-6p

WINDOWS 95 —One Step at a Time

Don't know what to do when confronted with Microsoft's Windows 95 screen? Then you need a copy of **Windows 95—One Step at a Time**. Develop your expertise with the straight-forward presentation of the frequently-used features that make Windows 95 so valuable to the PC user.



To order Book BP399 send \$8.99 plus \$3.00 for shipping in the U.S. and Canada only to **Electronics Technology Today Inc.**, P.O. Box 240, Massapequa Park, NY 11762-0240. Payment in U.S. funds by U.S. bank check or International Money Order. Please allow 6-8 weeks for delivery.

Circuit Circus

AM Reception Improvements

CHARLES D. RAKES

Circuiteers, get ready for some radio fun and adventure here at the *Circus*, as we look over a number of loop antennas, pre-amps, and other receiver enhancement circuits. There's no limit to the information that's flowing around us everywhere in the radio medium, and the easiest way to experience the adventure is on the standard AM broadcast band, where thousands of stations are operating. But, by no means do you have to limit yourself to this very small segment of the radio spectrum. There is information abound from near-audio frequencies to light waves that are just waiting to be tapped. Radio monitoring is a giant wide-open hobby that can supply hours and hours of fun and adventure to all. Buckle your seat belts, and make ready for a journey into radio wonderland!

FULL-SIZE LOOP ANTENNAS

To capture all those radio waves we need antennas, and antennas require a lot of space. Space is the basic requirement for that dream antenna farm we would all love to have, but most of us will have to take our limited area; maximize its use by constructing smaller, more efficient antennas; and use electronic enhancement circuits.

The full-wave horizontal loop antenna is one of the best, least expensive, most efficient, and quiet, multiband receiving or transmitting antennas you can put up. Bar none! Again SPACE is the only real problem with the full-wave loop, as it can take up a large area when designed for the AM broadcast frequencies. However, as the frequency goes up, the size of the loop goes down. Also a higher frequency loop can be "tuned" with an antenna tuner or Transmatch ("Transmitter Matching") for lower frequency operations. If there's any way you can manage to fit one on your property—do it, because once you've put one up and used it, I don't believe you will ever take it down—unless you have figured out how to put up a larger loop in its place.

circular loop antenna. The math for figuring the loop's total length, or circumference, in feet, is $1005/f$ (where f is the operating frequency in MHz). The loop's total length for receiving an AM broadcast station operation on a frequency of 1 MHz would be $1005/1$, or a total loop circumference of 1005 feet! Granted this would not be practical in most cases, but if the frequency you wanted to receive happened to be 10 MHz, the total length of the loop would be a manageable 100.5 feet. Since it's configured as a square loop, we divide this length by four (see Figure 1B), and each side only takes up about 25 feet—also do-able.

The ideal construction form for the loop would be a circle, but that is not practical because it would take an infinite number of supports around the loop to maintain the circle pattern. The

next best and most practical form is the square, where the loop is divided into four equal sides. The loop's actual shape can vary somewhat without greatly affecting its performance, and the feed point can be in any of the corners as well.

I've seen some small lots with a full 80-meter loop and a very small lot supporting a full 40-meter loop. To make it fit on your property, you can even have your house in the middle of the loop. The higher up you place the loop the better it works, but don't let that bother you too much—my full-length, 80-meter loop is only about 15 feet above ground, built on a slope where it performs like gangbusters on all the HF ham bands.

The loop can be used on lower bands and even the AM broadcast band, by tying the ends of the loop together and feeding with a single wire to the receiver's antenna input (see Fig. 1C).

SMALL LOOP

If you have never played with loop antennas, the one shown in Fig. 2 is a good one to try first. This indoor loop may be wound on the outside of a door facing, or supported in mid-air from the ceiling, or any other method you chose. The dimensions and number of turns are not set because it is not likely that any two would be the same. No matter what support method you use, try and keep it away from metal objects; so don't use a door facing that surrounds a metal door. If a door facing is the winding support, try about four turns of any size insulated wire from #12 to #26 gauge.

Connect both sections of an old radio broadcast tuning capacitor (365-pF or larger) in parallel and across the coil. Then place a plastic case AM transistor radio in the loop so the radio's internal loop is parallel to the large loop. Tune the radio to a weak station anywhere in the mid-dial position and adjust the large loop's capacitor for maximum audio output. If the loop's tuning range covers the frequency your radio is tuned to, the audio output and quality will greatly be

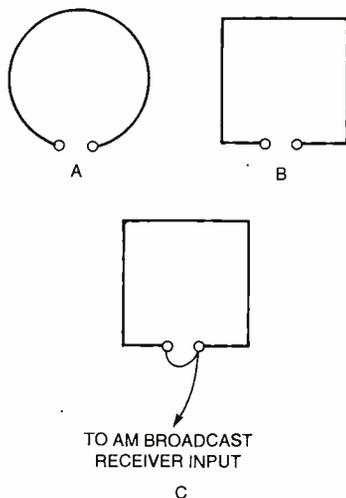


Fig. 1. This figure illustrates three configurations of loop antennas. The balanced loop is circular in (A) and rectangular in (B). In (C), a rectangular loop is shown fed as a single-ended source using ground as a return path.

PARTS LIST FOR FULL-SIZE LOOP ANTENNAS (FIG. 1)

Antenna wire—14-gauge, 7-strand copper (Radio Shack has 70-foot rolls that work great in full-length loops—part number 278-1329)

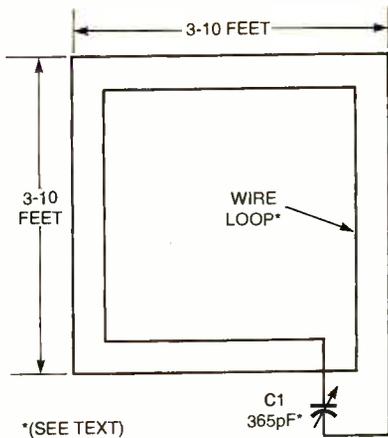


Fig. 2. This indoor loop can be wound on the outside of a door facing or supported in mid-air from the ceiling. It will work wonders in improving AM reception.

PARTS LIST FOR SMALL LOOP ANTENNA (FIG. 2)

Antenna wire—Any size copper wire from #12 to #26 gauge
 C1—365-pF or larger tuning capacitor

enhanced. If the loop and capacitor combination won't tune to the radio's frequency, the loop's induction might be too small or not have enough turns. Either add a turn or add a 330-pF capacitor across the coil and retune.

SMALLER, ACTIVE LOOP CIRCUIT

Our next loop in Fig. 3 is smaller—and to help make up for its reduced size, an RF amplifier is added. The loop is five turns of #22 plastic insulated copper wire, close wound on a 3-foot diameter wood frame. If a circle frame is not available, use a 3-foot square wood frame. The tuning range will depend on the loop's actual size and the value of capacitance of C1. One of the old AM tube-type tuning capacitors (365-pF or larger) with two variable sections tied together is an excellent choice for C1. If a large value tuning capacitor is not available, additional capacitance can be switched across the loop to lower the tuning range. Add capacitance in steps of about 330 pF to cover the lower frequency range of the AM broadcast band.

Transistor Q1, a MPF102 FET, amplifies the tuned RF signal, and its output is buffered by Q2, a 2N2222 transistor, connected in an emitter-follower circuit. Resistor R2 sets the gain of the RF amplifier and drives the signal into the receiver's antenna input terminal.

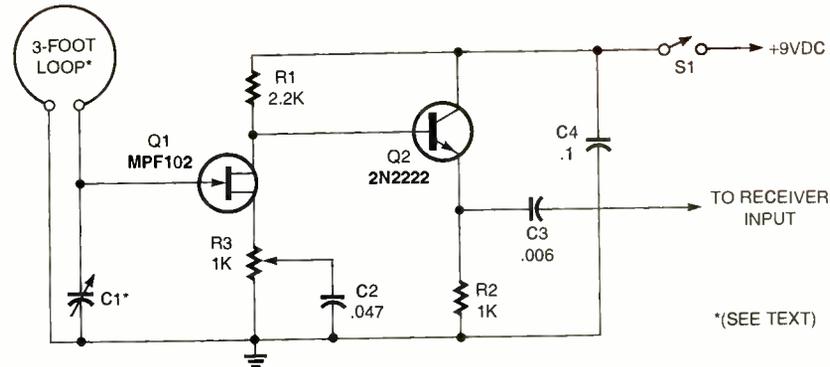


Fig. 3. Short of antenna space? Try this active antenna circuit. The RF amplifier boosts up the gain to reasonable levels.

The amplified loop is best used with a radio that has an external antenna input, but if it doesn't, connect the output to a pull-up antenna. If the receiver has neither an external antenna input or a pull-up antenna, add the coupling coil shown in Fig. 4.

The actual size and number of turns on L1 isn't too important, but the type of ferrite used should be of the same material as found in most AM transistor radios. The ferrite core can be salvaged from most any non-working transistor portable radio. It can be either a round or rectangle-shaped core.

Align the coupling coil on the outside of the radio's case in parallel with the radio's internal antenna coil. Locating L1 for its best position should be done when receiving a weak signal. Move L1 around the area where the radio's internal loop is located and tape it in place where the greatest output signal is produced.

GETTING THE MOST FROM YOUR AMPLIFIED LOOP

The loop should be positioned vertically to match the polarization of the AM broadcast stations and aimed with the plane of either side of the loop toward the station you want to receive, as shown in Fig. 5A. One of the loop's best features is its ability to null out noise and unwanted stations. Select a station that you don't want to receive and rotate the plane of the loop perpendicular to the direction of that station, and the signal will null to a low signal level (see Fig. 5B). Also the loop may be tilted to help in nulling unwanted signals as well as increasing desired ones.

MICRO-ANTENNA FOR LONGWAVE RECEPTION

As the length of an antenna is reduced, the signal sent to the receiver

PARTS LIST FOR SMALLER, ACTIVE LOOP CIRCUIT (FIG. 3)

C1—365-pF or larger tuning capacitor
 C2—0.047- μ F, 50-WVDC, ceramic-disc or similar capacitor
 C3—0.005- μ F, 50-WVDC, ceramic-disc or similar capacitor
 C4—0.1- μ F, 50-WVDC, ceramic-disc or similar capacitor
 Q1—MPF102 JFET (RadioShack 276-2062, or equivalent)
 Q2—2N2222 NPN transistor (NTE123A, SK3444, or equivalent)
 R1—2200-ohm, $\frac{1}{4}$ -watt, 5% resistor
 R2—1000-ohm, $\frac{1}{4}$ -watt, 5% resistor
 R3—1000-ohm potentiometer
 S1—SPST switch
 Antenna loop—see text

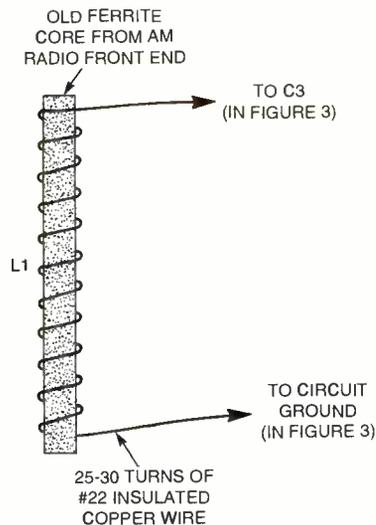


Fig. 4. Without an external or pull-up antenna? Use this coupling antenna as an alternative.

PARTS LIST FOR COUPLING COIL (FIG. 4)

L1—Old ferrite loop core removed from AM transistor radio (see text)

er is also reduced. An amplifier can be added to electronically stretch the antenna's length and bring the RF sig-

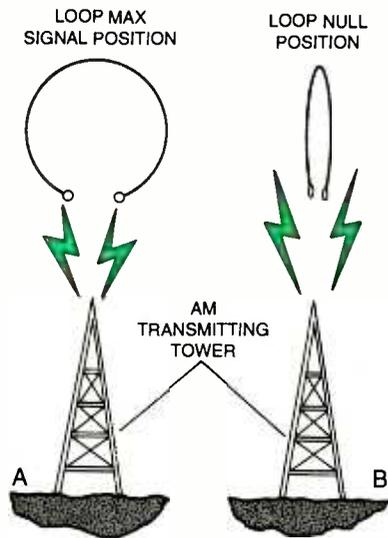


Fig. 5. This figure illustrates the proper positioning for a loop antenna. In (A) when the loop antenna is broadside (maximum area exposed to the incoming RF energy), the reception will be maximized. As the plane of loop is rotated 90 degrees, as in (B), the signal strength is minimized, or nulled out.

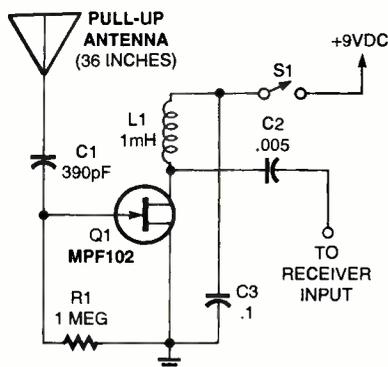


Fig. 6. Here's a simple broadband low-frequency active antenna circuit useful for AM reception.

PARTS LIST FOR MICRO ANTENNA FOR LONGWAVE RECEPTION (FIG. 6)

- C1—390-pF, 50-WVDC, ceramic-disc or similar capacitor
- C2—0.005-μF, 50-WVDC, ceramic-disc or similar capacitor
- C3—0.1-μF, 50-WVDC, ceramic-disc or similar capacitor
- Q1—MPF102 JFET (RadioShack 276-2062, or equivalent)
- L1—1-mH RF choke
- R1—1-megohm, 1/4-watt, 5% resistor
- S1—SPST switch
- Antenna—36-inch pull-up replacement antenna

nal level back up to a level near that of a longer antenna.

A simple broadband low-frequency (AM broadcast band) amplified antenna is shown in Fig. 6. A MPF102 JFET amplifies the RF signals picked up by the 36-inch pull-up antenna and passes it on to the receiver. Since the amplifier is a broadband device, all RF signals, including noise, within the bandwidth of the amplifier is fed to the receiver. If the receiver has a very good front end with excellent selective and dynamic range, the amplifier will help. But if the receiver happens to have a weak front end, look out; the amplified antenna could cause more grief than good.

In any case, the circuit won't cost you too much to build. Experiment with it to see if it can help pull in that desired AM station. The amplifier's gain can be changed somewhat by raising and lowering the pull-up antenna. This could allow the amplifier to be used with a low-cost receiver.

Looks like it's time to go, so until next month—great listening on the AM band. ■

NEW PRODUCTS

(continued from page 38)

The small, thin style of the meters makes them easy to carry in tool belts or to fit easily into tool boxes. They measure approximately 6³/₄-inches high by 1⁵/₈-inches wide at the widest point. Designed especially for electricians, plant and maintenance engineers, and other who need a compact tool, Wavetek's ST75 and TM45 are very useful for applications where space is tight, for quick tracing on wiring panels and circuits, and for blower and motor circuit troubleshooting.

Priced at \$99.95, the meters come complete with batteries, test leads, probes, and a protective carrying case and are available from local distributors and national catalogs. Contact Wavetek Corporation, Instrument Division, 9405 Balboa Avenue, San Diego, CA 92123; Tel. 619-279-2200; Fax: 619-565-9558.

CIRCLE 86 ON FREE INFORMATION CARD

MODERN RABBIT-EAR ANTENNA

The TV15 from TERK Technologies offers the ideal combination of exceptional reception performance on all TV

broadcast frequencies, elegant styling, compact-size (5¹/₄-inches high and 25-inches wide), and durability. It is compact enough to use in almost any AV cabinet.

For optimum efficiency, the length of an antenna's element should be a specific percentage of the wavelength of each broadcast frequency. Outdoor antennas accomplish this with multi-element arrays consisting of longer elements for the lower frequencies, and shorter elements for the higher frequencies. In the 1930s, rabbit-ear indoor antennas were developed to duplicate the physics of the outdoor antenna by permitting the user to physically vary the length of the two telescoping arms. However, rabbit ear antennas have inherent problems. TERK has developed the TV15 to resolve these problems.



This horizontally arrayed non-telescoping dual-rod antenna utilizes newly developed Advanced Frequency Matching Technology, which involves the use of tuned circuits in each arm of the TV15. These circuits extend the effective length of each arm electrically at the lower frequencies, while reducing their effective length for reception of higher frequencies. For even greater efficiency and selectivity, TERK added an additional stage of Pin-Dot Pre-Tuning. Adjustable via a five-position switch on the antenna base, the Pre-Tuning stage enables the user to minimize ghosting and other artifacts in difficult reception conditions. The semi-circular base has a curved surface that allows easy access to the Pin-Dot Pre-Tuning control and the Antenna/Video source selector. The two-position source selector makes it easy to switch between off-air reception and other video sources, such as satellite, video games, or camcorders.

The TV15 retails for \$39.95. Contact TERK Technologies, 63 Mall Drive, Commack, NY 11725; Tel. 516-543-1900; Fax: 516-543-8088; Web: www.terk.com.

CIRCLE 87 ON FREE INFORMATION CARD ■

Think Tank

Something for Everyone

ALEX BIE

In this month's column, we continue exploring the basics of electrical devices—namely the semiconductor. One of the fundamental structures within semiconductor technology is the PN junction (see Fig. 1). It has the valuable property that electrons only flow in one direction across it, and as a result, it acts as a rectifier. This means that the PN junction is widely used both with integrated circuits and also as a discrete device for more conventional circuits.

WHAT IS A PN JUNCTION?

In its basic form a PN junction is manufactured from one piece of semiconductor material by making one end P-type and the other end N-type. This means that both ends have different characteristics. One end has an excess of electrons while the other end has a surplus of holes. Where the two areas meet, the electrons fill the "holes," and there are no free holes or electrons. No holes means that there is no way for current to flow in this region. As the area where the two semiconductor types meet is depleted of charge carriers, *i.e.* there are no holes or electrons, it is called the depletion region.

Even though the depletion region at the junction is very thin, often only a few thousandths of a millimeter, current cannot flow in the normal way. Different effects are noticed depending upon the way in which the DC voltage is applied to the junction. If a voltage is applied (as shown in Fig. 2A) such that the P-type area becomes positive and the N-type becomes negative (forward bias), holes are attracted towards the negative voltage and are forced to jump across the depletion layer. Similarly, electrons move towards the positive voltage and jump the depletion layer. Even though the holes and electrons are moving in opposite directions, they

carry opposite charges and as a result they represent a high current flow in the same direction.

If the voltage is applied to the PN junction (as shown in Fig. 2B) in the opposite sense, very little current flows. The reason for this is that the holes are attracted towards the negative potential, which is applied to the P-type region. Similarly the electrons are attracted towards the positive poten-

tial, which is applied to the N-type region. In other words the holes and electrons are attracted away from the junction itself, the depletion region increases in width and forms a potential barrier.

Not Ideal Characteristics

The PN junction is not an ideal rectifier having infinite resistance in the reverse direction and no resistance in the forward direction. Instead it has a characteristic like that shown in Fig. 3. From the diagram you'll see that a small amount of current flows in the reverse direction. It has been exaggerated to show it on the diagram, and in normal circumstances it's very much smaller than the forward current. Typically it may be picoamps (pA) or microamps (μA) at the most. However, it's worst at higher temperatures and it's also found that germanium is not as good as silicon. For example, a standard 1N4001 silicon rectifier has an average forward current rating of 1A (I_F) and a reverse current of 30 μA (I_R).

The reverse current results from what are called minority carriers. They are a very small number of electrons found in a P-type region or holes in a N-type region. Nowadays though, the manufacture of semiconductor materials is very much better and the number of minority carriers is much reduced, as are the levels of reverse currents.

Junction Barrier Voltage

In the forward direction it can be seen from Fig. 3 that very little current flows until a certain voltage has been reached. This represents the work that is required to enable the charge carriers to cross the depletion layer. The junction barrier voltage varies from one type of semiconductor to another. For germanium it is around 0.2 or 0.3 volts and for silicon it is about 0.6 volts.

In fact, it is possible to measure a voltage of about 0.6V across most small current diodes when they are forward biased. Power rectifier diodes normally have a larger voltage across them

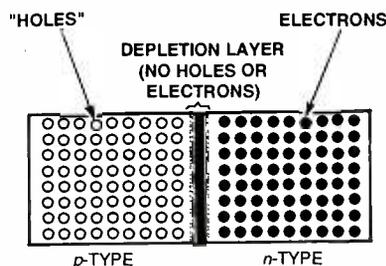


Fig. 1. A PN junction with no voltage applied.

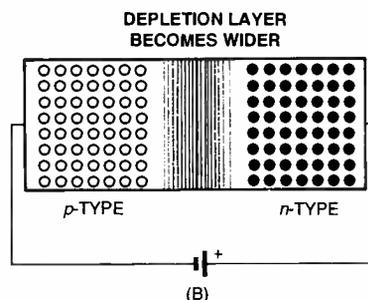
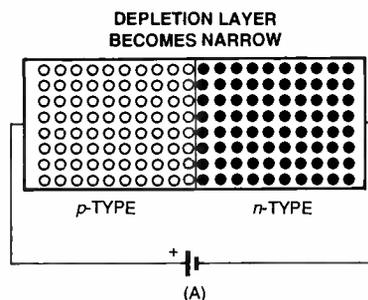


Fig. 2. When a positive voltage is applied (forward bias), as shown in (A), the depletion region becomes narrow and a high forward current flows; when this voltage is reversed (reverse bias), as in (B), the depletion layer becomes wider and very little current flows.

("What is A...?" series reprinted by permission from *Practical Wireless*, Arrowsmith Court, Station Approach, Broadstone, Dorset BH18 8PW, England.)

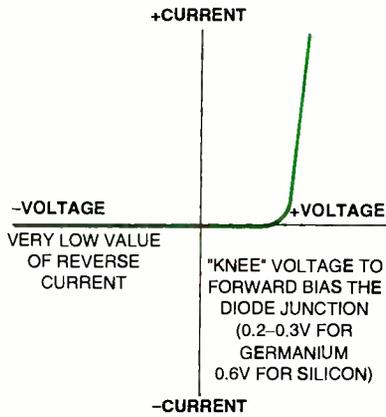


Fig. 3. Voltage-current characteristics of a typical diode.

but this is partly due to the fact that there is some resistance in the silicon, and partly due to the fact that higher currents are flowing and they are operating further up the curve (as shown in Fig. 3).

The PN junction is widely used as a rectifier in a number of applications, but it also has a number of other uses. In the coming months, we will be taking a look at some of these uses before moving on to some other interesting devices. But right now let's get to our readers' circuits. We have different circuits for different folks—in short, something for everyone!

LOW-DISTORTION, LOW-LEVEL AMPLITUDE MODULATOR

This simple diode modulator delivers excellent results when used for high percentage amplitude modulation (AM) at low signal levels. The parts shown in Fig. 4 are designed for an RF carrier input of 10 MHz. With a different tank circuit (L1/C1), this modulator will give excellent results at any frequency below 100 MHz (limited to the characteristics of D1). I used the Hewlett Packard 5082-2800 Schottky barrier diode; however, a standard fast silicon diode, such as the 1N4148 (equivalent NTE519), could also be used. A shunt resistor placed across the tank circuit reduces the "Q" of the circuit. This would permit a high percentage modulation without appreciable distortion.

—Alex Belenky, Brooklyn, NY

Simple but interesting circuit, Alex. By the way, the relationship between the variable capacitor and inductor determines the resonant frequency of the tank circuit ($f = 1/\sqrt{2\pi LC}$).

"PESKY CRICKET" CIRCUIT

The cricket is well-known for the chirping sound made by the males. They make their distinctive sound by rubbing an up-turned scraper on one forewing against a row of 50–250 teeth on the bottom of another forewing, producing a triple-modulated sound in the 1500–10,000-Hz frequency range. The circuit shown in Fig. 5 produces a pretty authentic triple-modulated cricket-chirp, but like a real cricket prefers to oscillate only in the dark. As you can imagine, this circuit makes an excellent practical joke, as your victim discovers a cricket in a room and will stop at nothing to locate and silence the little pest.

In operation, the cadmium sulfide (CdS) photoresistor monitors the light level, and then outputs a voltage to the 555 timer, IC1, which is set up as a Schmidt trigger to turn on the rest of the

circuit if it is dark and to turn it off under lighted conditions. Timer IC2 is an astable multivibrator, adjusted for 1.8 Hz. It modulates IC3, another 555, also configured astable operation and running at 50 Hz. The modulated output of IC3 powers an ordinary piezo-buzzer, which typically has an operating frequency in the 2–3 kHz range, just right for a fairly large cricket! Feed your cricket with a 9-volt battery.

When completed, just place the circuit in a hidden but not too dark spot in a room, and wait for your victim to ask for a flashlight and bug spray! To optimize the circuit for stealthy pranks, choose the smallest possible CdS photo cell and piezo-buzzer, and use surface-mount components, so the board is the same size as the 9-volt battery. Care to make this circuit more authentic? Replace the 100k resistor of IC2 with a thermistor in the 100k range, and you now have a "thermometer cricket," whose chirp rate is proportional to the ambient temperature!

—Nick Cinquino, Schaumburg, IL

I can see lots of fun with this neat circuit, Nick. To make the circuit even smaller, what about using a 556 dual timer or even a 558 quad timer? However, if the configuration gets too authentic you better watch out that you don't attract all the female crickets in the neighborhood!

SIMPLE AUDIO TONE-CONTROL CIRCUIT

A better alternative to all the tone-control circuits I have seen in recent years is the Signetics TDA1524 IC. This chip is supplied in a conventional 18-pin package and requires only a handful of support components. The circuit shown

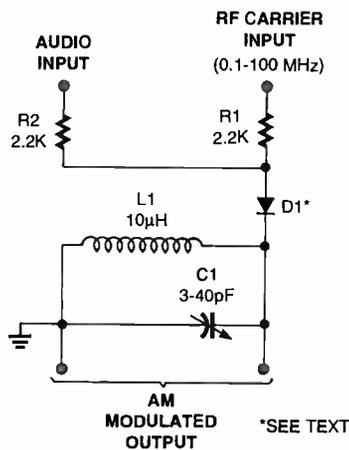


Fig. 4. This simple circuit is a great way to produce amplitude modulation. Experiment with the diode for best mixing characteristics.

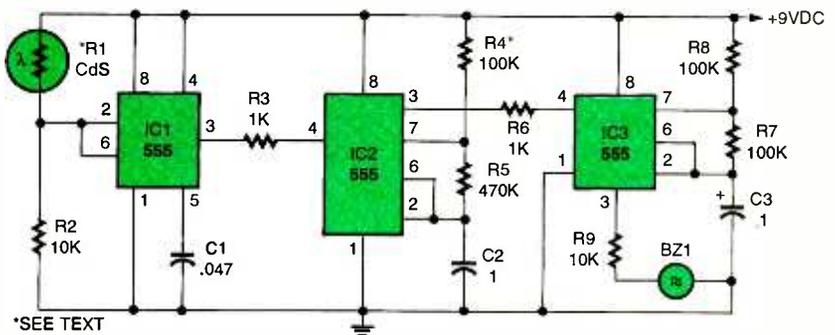


Fig. 5. This fun circuit simulates the chirp of a cricket—complete with a photo cell, which shuts down the circuit when a light shines on the "cricket!"

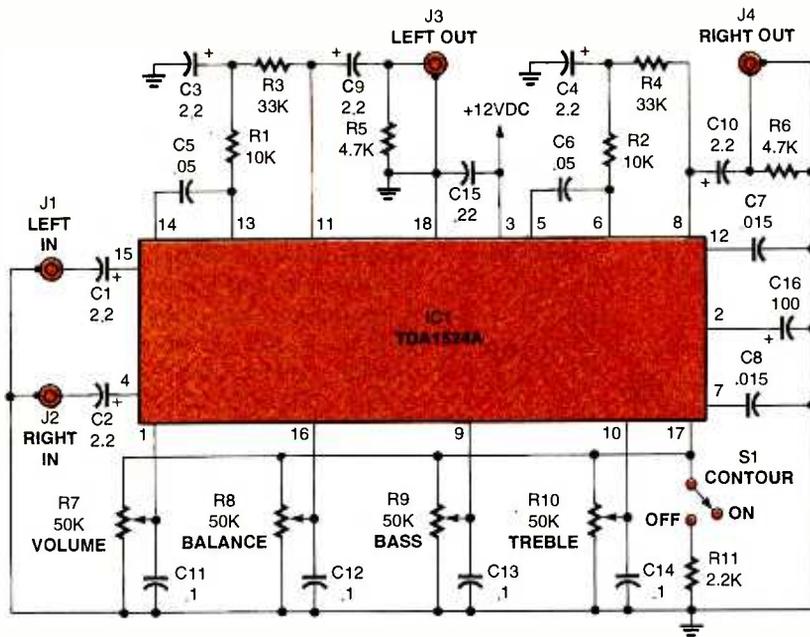


Fig. 6. This simple circuit uses the TDA1524 stereo audio control system IC as the only active component in this great amplifier add-on.

in Fig. 6 shows the TDA1524 in a typical design configuration that provides tone control for stereo inputs. The volume, bass, treble, and balance controls are single 50k linear potentiometers. A feature not found in other tone-control circuits is the loudness contour, which can be switched on or off, depending upon your audio requirements. With a 12-volt DC supply, volume control at maximum, and bass and treble controls centered, an audio input signal of 120 mV will produce a 1.5-volt output. The bass and treble controls allow about 14-dB boost or drop at 100 and 10 kHz, respectively.

I constructed the circuit on a small PC board to keep everything neat and compact. All the input/output jacks were RCA-type panel mounts. Since I wanted a stand-alone unit, the board was installed in a metal cabinet along with a small DC supply. This TDA1524 circuit makes an excellent companion to the TDA1554 power amp described in the February 1997 *Think Tank* column.

Robert O. Barg, Rochester, NY

Thanks for this neat circuit, Robert. I am sure that all those audiophiles will want to use this circuit in their stereo system. By the way, Robert indicated that he was able to pick up the TDA1524 IC from DC Electronics for \$5.95, Tel. 800-467-7736. The cross-reference to this IC is the SK9884 (stereo audio control system).

AUTOMATED MOTOR PUMP SWITCH

I designed a circuit to automatically fill a watering tank to the right level. I do not have a tank, but I tested the circuit using a pail with water, and it works just fine. As you can see from Fig. 7, the circuit is designed around a 2N5060 SCR and a few other components. The secondary of the step-down transformer, T1, is rated at 12-volts, 500-mA minimum and the rectifier assembly, BR1, can be a modular type or derived from 1N4001 diodes.

When switch S1 is closed, if the water is below the level of the lower electrodes, there is no conduction through these electrodes. Since AC line voltage is applied to the pump terminals through the normally closed relay contacts, the motor pump is turned on to start filling the tank with water. When the level reaches the lower electrodes, conduction begins, and the anode of the SCR connects to the positive supply. The SCR is now in its standby mode. When the water level finally reaches the upper electrodes, a new conduction path through these electrodes is formed. The trigger pin of the SCR is now connected to a positive voltage, and the SCR is triggered. At the same instant, relay RY1 is energized, and its contacts pull in, disconnecting one line of the motor pump from the AC potential. The motor pump

is therefore turned off, which stops the water flow. The LED now turns on, indicating that there is plenty of water in the tank. Should the water level fall below the upper electrodes, LED1 and relay RY1 remain latched on by the SCR. When water falls below the lower electrodes, the relay de-energizes and the LED indicator turns off. The water pump is turned on again to repeat this cycle.

Reset switch S2 is used if a black-out occurs. When the electricity comes back, the pump turns on if the water level is between the lower and upper electrodes. To stop the pump, just press S2 to turn it off and activate the LED indicator. Before you go on a vacation, open switch S1, which isolates the circuit from the 117-volt AC line. Switch S3 is for a lamp installed near the motor pump to provide light for repairs.

You can place switches S1, S2, and S3 on the project enclosure, so it will be easier to use them. For the electrodes, use 4- \times 4-inch PCBs or plain aluminum stock. You can install the lower electrodes, say, 1-foot from the bottom of the tank. That way you still have some water when the LED indicates an empty tank. Secure each pair of electrodes close to each other for best conduction. All the circuit parts are available at RadioShack.

—Jose Ignatius A. Alea, Cebu, Philippines

The lamp is a nice touch. I would connect S3 to the other side of S1 instead. That way you can deactivate the circuit (by switching off S1) for safety, but still use the lamp.

MAILBAG, ETC.

Here's some corrections, suggestions, etc. to recent *Think Tank* circuits.

In the January 1998 *Think Tank*, page 68, Fig. 2, the component for "D1" is a 1N5464B (equivalent NTE612) or MV2107 (equivalent NTE, SK3326) variable capacitance diode (varactor). The 1N4817 (a standard recovery rectifier diode) shown in the circuit is incorrect.—Editor

I think there is an error in Alex Belinky's, "Twenty-Watt Audio Amplifier" circuit in the July 1997, *Think Tank*, page 65. In Fig. 2, a short is shown from the top of C1 to the R2, D1 junction, which essentially shorts out R2—does it belong there? Also would a 2N3904 transistor, or 2N2222, substitute for the

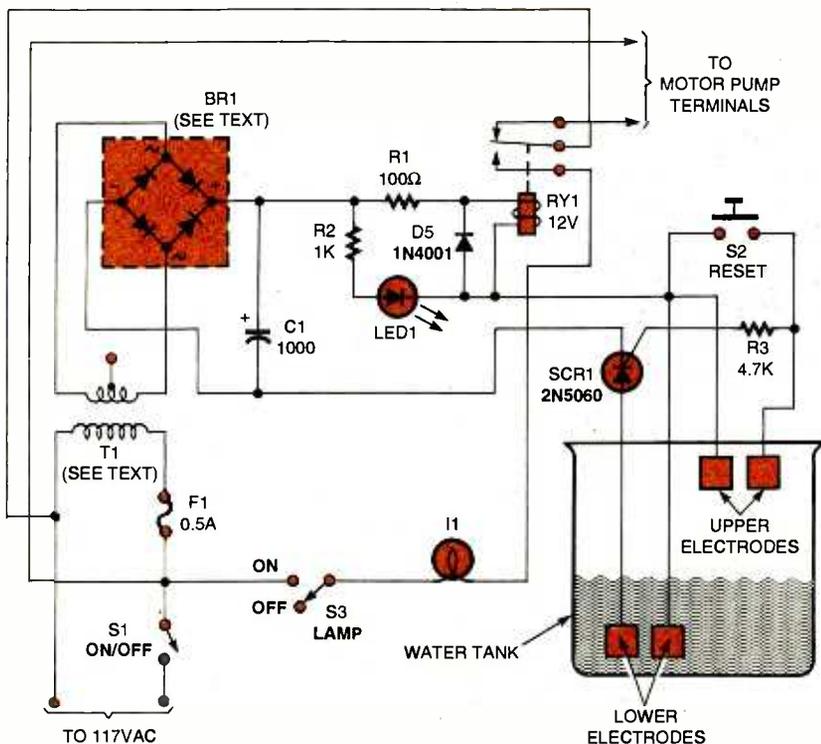


Fig. 7. Here's a useful circuit around the homestead that will always ensure a full water tank. It takes a little skill to set up and adjust those electrodes. Equivalent electrical parts for the circuit are RadioShack 276-1067 for SCR1 and RS 276-1101 for the 1N4001s. You can always use their modular rectifier unit, such as the RS 276-1146, to save some space.

2N5961? Finally, are the internal diodes in the SE9401 Darlington transistors something special, or could 1N4002 diodes be used if different Darlington (without internal diodes) were substituted?

—Dennis Share, Plainview, NY

Here are the responses we received from Alex: About that short, it should be removed, sorry! As far as the substitute for the 2N5961, I believe the 2N3904 would be a better choice—but I never tried it. Lastly, I believe the internal diodes of the SE9401 Darlington are especially made for this transistor (temperature-compensated, etc.). But like I said for the transistor substitution, it would not hurt if you experimented with other parts, just make sure they can handle the requirements of the amplifier. via e-mail (<http://idt.net/~alexbel>)

In the September 1997 *Think Tank*, page 74, a question arose as to a quad-package equivalent to the *National Semiconductor* LF353 dual JFET op-amp used in the "Four-Channel Audio Mixer" circuit (Fig.2). There are actually a few good quad op-amps for audio

available. The oldest is the *Texas Instrument* TL074. The problem with the FET input LF353 and the TL074 is the propensity for latch-up and/or input inversion when the input signal exceeds the power supply rails. This is a possibility when the power supply is only ± 9 -volts DC. For this reason, it is a good idea to clamp the inputs to the power supply rails with 1N4148 diodes. *National* also makes two JFET quads, designed about the same time as their LF353, which are also suitable—the LF347N and the LF444CAN.

There are newer BiFET devices, which can withstand input peaks greater than their supply voltages and are suitable for high-quality audio use. The *Analog Devices* AD713KN (available from *Jameco*, Tel. 800-831-4242) and the *Linear Technology* LT1058CN (available from *Digi-Key*, Tel. 800-344-4539) are two I have used with great success. They have the added advantage in that the input offset voltage is less than 1 mV, so you can direct couple the signals after the input stage and save quite a few film capacitors. For stability reasons, the four input stages should have their high-frequency gains

rolled off at 200 kHz, or so, by adding a high quality 10pF capacitor (polystyrene or NPO ceramic) across the 100k resistors (R3, R7, R11, R14 of Fig. 2).

If the input impedance does not have to be so high, there are also a number of suitable bipolar input quad op-amps. Bipolars tend to have lower input noise, although given the high resistances needed for battery power, the resistor noise may be the higher noise source. Some of these quad audio bipolar op-amps are as follows: *PMI(ADC)* OP-471GP, *National* LM837N, *NECE* μ PC4574C, and the *Motorola* MC3408AP.

—Charles Hanson, Tinton Falls, NJ

Well, that's about it for circuits and comments for this month's column. Just a reminder, as soon as we verify any corrections, we will post them on our Web site: www.gernsback.com, under the **Popular Electronics**, Forum link. Remember—this is **your** column—keep those circuits and ideas coming in.

Write me—Alex Bie, *Think Tank*, **Popular Electronics**, 500 Bi-County Blvd., Farmingdale, NY 11735. ■



"How could she fail me for that essay? I copied it right from the Internet."

Get your copy of the CRYSTAL SET HANDBOOK

Go back to antiquity and build the radios that your grandfather built. Build the "Quaker Oats" type rig, wind coils that work and make it look like the 1920's! Only \$10.95 plus \$4.00 for shipping and handling. **Clagge Inc., P.O. Box 4099, Farmingdale, NY 11735.** USA Funds ONLY! USA and Canada—no foreign orders. Allow 6-8 weeks for delivery. MA01

SCANNER SCENE

Base Station Trunking Scanner

MARC SAXON

You said you wanted a base station scanner that could wrestle with UHF trunked systems. You've got it! It's *Uniden's Bearcat BC-895XLT Trunk Tracker*, and it's brimming over with features.

There are 300 memory channels in ten banks. The unit covers from 29 to 512 MHz and 806 to 956 MHz (minus the cellular bands, which are permanently factory-blocked as per FCC edict). The BC-895XLT normally searches and scans at nearly 100 channels per second, but can zip through them at an incredible 300 channels per second when placed in Turbo mode.

The unit gives instant one-button access to scanning all NOAA weather channels, and it provides a severe weather alert warning tone. There are service search access buttons for aeronautical, police and fire/emergency services. Users can select ten priority channels, as well as program 20 skip channels for service search scan, plus another 20 for regular search scan. The BC-895XLT allows manual channel access, directly to any specific desired frequency. It provides the option of stepping through the channels or using the rotary tuning control.

The Uniden BC-895XLT scans regular VHF/UHF communications, plus it can also efficiently track Motorola 800 MHz trunked systems. It is not designed to track 400 MHz bond trunked systems, nor GE trunked systems. It can search for all channels used in trunked systems, tracking those used as many as 50 channels. You get to hear both sides of trunked system conversations, even if the trunking frequencies change between replies.

How about a signal strength meter? And a built-in CTCSS (PL tone) board that lets you read the tones that may be in use on the channel being monitored. There's an RS232C port to allow computer control of this scanner, using readily available software/hardware.

The Bearcat BC-895XLT is a good-looking top-grade scanner for the serious user. It's available from Uniden Bearcat dealers nationwide.



Uniden's new Bearcat BC-895XLT Trunk Tracker base station scanner continuously covers 29 through 512 MHz and 806 to 956 MHz.

SCANNER FAMILY TREES

Some scanners look identical from the outside, such as the RadioShack PRO-2005 and PRO-2006, even though they aren't quite the same internally. Others vastly differ physically or mechanically from one another, but may practically be clones from an electronics point of view. Did you know that? This amusing but confusing aspect of scanner technology has vexed members of the hobby for a while, so we thought it might be of interest to pass along some of the family secrets of scanners.

There are major external but only minor internal differences between the PRO-2004 and PRO-2005, yet a few small changes were made to make the PRO-2006 slightly different from its (externally) identical twin, the PRO-2005. The handheld PRO-43 is a close relative of these scanners, but the later identical base station scanners, PRO-2035 and PRO-2042, are even closer in their circuitry to the PRO-2004/5/6 series.

The RadioShack PRO-26 is essentially the same internally as a Uniden Bearcat BC-3000XLT. Other nearly *identical twins* are the PRO-32 and the PRO-2021, the PRO-34 and the PRO-2022, the PRO-39 and the PRO-2032, and the PRO-64 and the PRO-2041. The PRO-62 is most likely a double of the PRO-2037, while the PRO-2035 matches up rather closely with the PRO-2042, with the exception of some CPU differences.

Uniden Bearcat's BC200XLT is the same as the BC-205XLT and the Regency R-4030. Their BC590XLT is identical to the BC-600XLT. Uniden Bearcat's BC-760XLT is a twin to their

BC-950XLT and the Regency R-1600.

This information may be useful when evaluating or modifying scanners.

MAILBAG

A reader in New Jersey reports monitoring several DEA surveillance chopper pilots communicating with one another on 120.775 MHz, while directing ground surveillance vehicles on 418.75 MHz. According to the authoritative "*Top Secret*" *Registry of U.S. Government Radio Frequencies, 8th Ed.* (CRB Research), 120.775 MHz is a standard DEA air surveillance channel. The book suggests you also try 120.375 MHz for similar traffic. CRB Research's address is P.O. Box 56, Commack, NY 11725. A free catalog is available. Their phone number is 516-543-9169, the e-mail address is crbbooks@aol.com, while their Web site has a URL of www.crbbooks.com.

Many readers who live in Florida, or plan on visiting there, write to ask if we can offer a basic listing of good frequencies to monitor during Space Shuttle launches. Here are some suggestions for the areas of Patrick AFB and Kennedy Space Center that are being reported as active and interesting: 126.65, 133.75, 139.05, 141.30, 143.45, 163.4875, 164.7, 173.025, 259.7, 284.0, 294.6, 344.6, and 372.2 MHz. Undoubtedly there are dozens of other frequencies in use locally during a launch, and you can easily find them by search-scanning. The orbiter uses 259.7 MHz.

Here are two scanner tricks from Pete Levine of Utah. Pete says that on a certain channel he monitors, he wishes that the scan delay function operated for a bit longer than only two seconds. He solved this by programming the desired channel into his scanner (with the delay on) in two different memory positions ten slots apart. This gives the scanner another shot at picking up the reply, if it's just beyond the heels of the first channel's two second delay limit.

Pete's second trick is even better.

(Continued on page 64)

DX LISTENING

Shortwave Newscasts

DON JENSEN

Beginning, I guess, back in the 1930s, news junkies have relied on shortwave radio to tell them what in the world is going on. Even the American radio networks would monitor SW broadcasts from foreign capitals to flesh out their own newscasts with the latest worldwide information. But technology has turned that old world upside-down. CNN and satellite links, "live-from-whenever" video, and the Internet have transformed the way we receive information. So, one might think, the old-fashioned shortwave news broadcast is as out-dated as great-granddad's buggy-whip. One might think that... but, apparently, one would be wrong!

Based on the mail received and contacts I have with SWLs here and overseas, listeners still have plenty of interest in tuning in SW news broadcasts from around the globe. Why, given the virtually instantaneous breaking news capabilities of, say, CNN, do listeners still tune to SW newscasts? Perhaps there are many answers, but a couple seem apparent.

First, there is viewpoint. TV may already be there with live pictures, but how is the big news event playing in Tokyo, in Teheran, in Jerusalem? For that perspective, it helps to listen in to a number of individual newscasts from different countries on shortwave to get a composite "big picture" view.

Secondly, shortwave can offer the "little picture" as well, covering news stories of purely regional or even local impact that global TV newscasts ignore or overlook. Political unrest in Papua New Guinea; stock market skid in South Africa; soccer cup results from Spain—these events may barely flicker the TV screen in the U.S. and Canada,

(CREDITS—Bran Boulden, CA; Bob Fraser, MA; Mark Humenyk, ONT; David Krause, OH; Harold Levison, PA; William McGuire, MD; Jim Moats, OH; Jay Novello, NC; Denis Pasquale, PA; Ed Rausch, NJ; Jim Renfrew, NY; Chuck Rippel, VA; North American SW Association, 45 Wildflower Road, Levittown, PA 19057).

but knowing about them can, perhaps, make us better informed about the world we live in.



Fifty years ago, Norwegian King Haakon VII spoke to listeners abroad, officially opening the shortwave service known today as Radio Norway International.

It is noteworthy that the respected shortwave annual, *Passport to World Band Radio* (or PWBR—and available from Universal Radio, 6830 Americana Pkwy., Reynoldsburg, OH 43068. Tel. 800-431-3939), includes several news broadcasts among its ten top shortwave programs of 1998. "World band radio is the nerve center for the world's news—real news from everywhere," the publication says. And one of the best is the British Broadcasting Corporation's World Service, "Newshour."

"No other broadcaster offers the same depth and breadth of coverage of what is happening in the world," PWBR says. "And amidst this wealth of riches, the jewel in the crown is 'Newshour,' 60 minutes of news and reports from around the globe. The choice of subjects is wide-ranging and includes national, regional, and international stories. Fast-breaking news is

regularly updated throughout the program, with in-depth analysis of major topics being a regular feature. Not all is politics and crises—lighter stories also are offered, and there are business updates and news of major sporting events. There are two separate daily editions, at 1300 and 2000 UTC."

Those times, of course, are listed in UTC, or universal time, equivalent to Eastern Standard Time+5 hours, CST+6 hours, MST+7 hours, or PST+8 hours. Thus, 1300 and 2000 UTC are the same as 8 AM and 3 PM EST, 7 AM/2 PM CST, 6 AM/1 PM MST, or 5 AM/12 noon PST.

The BBC often changes SW frequencies with the season, but there are a number of channels in use at any given time, and finding one which offers decent signals is not too difficult. Some of the frequencies you may wish to try include 6195, 9410, 9515, 9590, 9740, 11865, 12095, 15220, 15575 and 17640 kHz at 1300 UTC. At 2000 UTC, check out the following—6180, 6195, 7325, 9410, 12095 and 15575 kHz.

REGIONAL COVERAGE

Also making the PWBR's top ten SW program list this year is "NewsLink" on Germany's international broadcaster, Deutsche Welle. It offers, the publication says, good regional—"that mid-ground between national and international reporting"—coverage of Europe.

"Deutsche Welle...has always leaned heavily toward coverage of European affairs, and its pioneering 'European Journal' has been a valuable source of continental news and analysis. Playing to this success in 1997, the station decided to merge its two main news programs—'European Journal' and 'Newsline Cologne'—into the new and more streamlined 'NewsLink.'"

"The result is a fast-moving 25-minute show with the accent squarely on Europe. Granted, important interna-

(Continued on page 64)

RETAILERS THAT SELL OUR MAGAZINE MONTHLY

California

California Electronics
221 N. Johnson Ave.
El Cajon, CA 90202

Ford Electronics
8431 Commonwealth Avenue
Buena Park, CA 90621

All Electronics
14928 Oxnard Street
Van Nuys, CA 91411

Gateway Electronics of CA
9222 Chesapeake Drive
San Diego, CA 92123

Mac's Electronics
191 South "E" Street
San Bernardino, CA 92401

Electronics Warehouse
2691 Main Street
Riverside, CA 92501

Orvac Electronics
1645 E Orangethorpe Ave.
Fullerton, CA 92631

Sav-On Electronics
13225 Harbor Blvd.
Garden Grove, CA 92643

JK Electronics
6395 Westminster Blvd.
Westminster, CA 92683

Kandarian Electronics
1101 19th Street
Bakersfield, CA 93301

Whitcomm Electronics
105 W. Dakota #106
Clovis, CA 93612

Minuteman Electronics
37111 Post St., Suite 1
Fremont, CA 94536

HCS Electronics
6819 S. Redwood Drive
Cotati, CA 94931

Halted Specialties Co.
3500 Ryder Street
Santa Clara, CA 95051

Metro Electronics
1831 J Street
Sacramento, CA 95814

HSC Electronics
4837 Amber Lane
Sacramento, CA 95841

Colorado

Gateway Electronics of CO
2525 Federal Blvd.
Denver, CO 80211

Connecticut

Cables & Connectors
2198 Berlin Turnpike
Newington, CT 06111

Electronic Service Prod.
437 Washington Avenue
North Haven, CT 06473

Georgia

Norman's Electronics, Inc.
3653 Clairmont Road
Chamblee, GA 30341

Illinois

Tri State Elex
200 W. Northwest Hwy.
Mt. Prospect, IL 60056

Kansas

Electronic Hobby Shop
309 E. McKay
Frontenac, KS 66763

Maryland

Mark Elec. Supply Inc.
5015 Herzel Place
Beltsville, MD 20705

Amateur Radio Center
1117 West 36th Street
Baltimore, MD 21211

Massachusetts

U-Do-It Electronics
40 Franklin Street
Needham, MA 02194

Michigan

Purchase Radio Supply
327 East Hoover Avenue
Ann Arbor, MI 48104

The Elec. Connection
37387 Ford Road
Westland, MI 48185

Minnesota

Acme Electronics
224 Washington Avenue N.
Minneapolis, MN 55401

Missouri

Gateway Electronics Of MO
8123-25 Page Blvd.
St. Louis, MO 63130

New Jersey

Lashen Electronics Inc.
21 Broadway
Denville, NJ 07834

New York

R&E Electronics
4991 Rt. 209
Accord, NY 12404

Unicorn Electronics
Valley Plaza
Johnson City, NY 13790

Ohio

Philcap Electronic Suppliers
275 E. Market Street
Akron, OH 44308

Oregon

Norvac Electronics
7940 SW Nimbus Avenue
Beaverton, OR 97005

Taztronics
257 N. Wasson St.
Coos Bay, OR 97420

Pennsylvania

Business & Computer Bookstore
213 N. Easton Road
Willow Grove, PA 19090

Texas

Mouser Electronics
958 N. Main Street
Mansfield, TX 76063

Tanner Electronics
1301 W Beltline
Carrollton, TX 75006

Electronic Parts Outlet
3753 B Fondren
Houston, TX 77063

Electronic Parts Outlet
17318 Highway 3
Webster, TX 77598

Washington

Amateur Radio Supply Co.
5963 Corson Ave., Ste 140
Seattle, WA 98108

If you'd like to sell our magazine in your store,
please circle 180 on Free Information Card.

ANTIQUE Radio

How Many Volts to Light a Tube?

MARC ELLIS

I was originally going to cover this topic in a full-length feature article to be published in a future issue of **Popular Electronics**. But since we've just finished a very long restoration project (*Freed Eisemann NR-5*), I'd like to talk about something other than nuts and bolts for now, and I'll bet most of you would agree. The time seems ripe for something more general, so let's go for it!

FILAMENTS VS. HEATERS

Before getting into the story, we'll take a minute to talk terminology. When an incandescent element directly supplies the electrons required to establish a plate current in a tube, it is called a *filament*. The original filaments were quite visible in the tube and very similar to the fiber or wire filaments Edison used in the first electric lamps—hence the name.

When the incandescent element in a tube is arranged to heat up a surrounding element, termed a *cathode*, which in turn becomes the electron source for the tube, it is called a *heater* (though it is still essentially a wire filament). The heater passes through channels inside the cylindrical cathode. It is usually out of sight except for a glowing section visible at the top.

Filamentary tubes were in common use during the battery-set era (most of the 1920s). Tubes with heaters and cathodes were introduced with the first AC ("plug-in") sets, which appeared in the late 1920s. I'll try to be conscientious about my language in referring to the "heating devices" for these two tube types.

Since we will be talking about a transitional era when battery and AC design practices were used in the same radio, and since this is a story about filament (or heater!!) voltages, I'll be discussing both types of tubes frequently, often in the same sentence. Now that you know this, you won't be surprised when I switch back and forth with dizzying frequency between the terms for the two different primary sources of electrons in a vacuum tube.

VOLTAGES AND MORE VOLTAGES!

The battery radios of the 1920s used tubes of various filament voltages, though generally all of the tubes in a specific set were the same type, or at least operated from the same voltage. Commonly used tubes were the 11 and 12 (1.1 volts), 99 and 120 (each 3.0–3.3 volts), and 01-A (5 volts). On the other hand, the early-1930s' battery sets intended for use on farms still not hooked up to rural electrification used tubes with 2.0-volt filaments, such as the types 30, 31, and 32.

Many of you may have noticed there seems to be an unusual and unnecessary variation in the filament or heater voltages required to light the tubes found in the early AC ("plug-in") sets—especially the first ones to come on the market in the late 1920s. To illustrate this point, I've included a detail from the schematic drawing of the power supply for the RCA Radiola 17, an AC receiver that appeared about 1927.

Notice that the power transformer has no less than *four* filament or heater windings. One lights the filament of the UX-280 rectifier tube. The other three power the filaments or heaters, respectively, of the UX-226, UY-227, and UX-171-A tubes used in the radio proper (we'll refer to these tubes by their more-modern, abbreviated designations: 80, 26, 27, and 71-A from here on out).

Notice also that the RCA draftsman has been conscientious in his use of the terms filament and heater in the labels for the windings. (The single type 27 in this radio is the only tube to have a cathode—and therefore a heater).

The type 80 filament, which operates from 5 volts, must be powered by a separate transformer winding to isolate the set's plate voltage from the rest of the circuitry. But why three windings to power the other tubes? It turns out that the three types used require different heater or filament voltages. The type 26 needs 1.5 volts; the type 27, 2.5 volts; the type 71-A, 5 volts. Most other AC sets of this era had a similar

tube complement and required two or more transformer windings, in addition to the one for the rectifier for filament/heater power.

In more modern transformer-powered sets, say from the late 1930s, the power transformer typically had just two filament or heater windings: one for the rectifier tube (usually 5 volts) and the other for the remainder of the tubes in the radio (all operating from 6.3 volts). Other, non-transformer-powered, sets of the thirties and forties used tubes with heaters operating from much higher voltages, such as 12, 25, 35, or 50 volts.


Why were so many different voltages chosen to light these tubes? Well some of the reasons have been lost in the mists of time. However, I think we can make quite a lot of sense out of what at first may seem to have been a whimsical and arbitrary selection process.

STORAGE BATTERY TUBES

We will start with the tubes for battery sets because the logic behind the voltages used to light their filaments is fairly apparent. In the days before radios could be powered from a wall plug, there were two main sources of power for radio tube filaments: (1) the rechargeable auto-style 6-volt storage battery or (2) the large No. 6 1.5-volt dry cells, sometimes called "ignition cells," commonly used to power doorbells in homes without electricity, magneto-phone sets in rural areas and, I suppose, ignition systems in primitive stationary gas engines.

The storage battery was heavy and clumsy, and contained corrosive acid that could ruin floors and carpets. It had to be lugged down to the corner gas station every once in a while for recharging (at least in the days before the trickle charger became a popular living-room accessory). Dry cells were much lighter and far less messy, but were probably more expensive to use because they were not rechargeable and had to be discarded when exhausted.

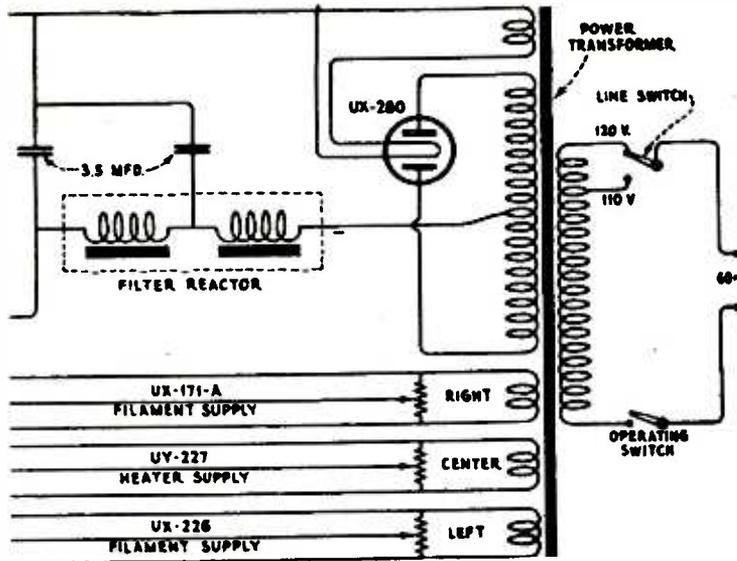The storage battery was the filament power source of choice for larger sets,



Detail from schematic of RCA Radiola 17 power supply reveals that power transformer had no less than four (!) filament windings.

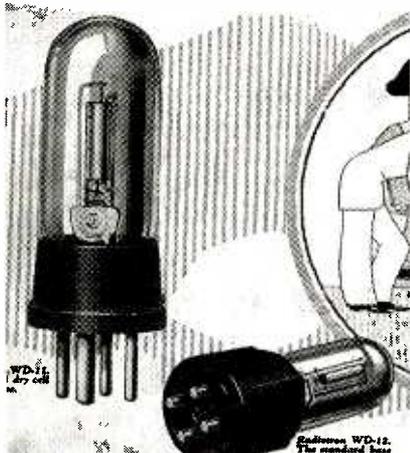


Illustration from 1925 ad for RCA Radiotrons shows type 11 (left) and 12 dry-cell tubes.

and the tube developed for storage battery use was the familiar 01-A with its 5-volt filament. Why 5 volts for a 6-volt battery? The reason is based on the fact that an auto-style storage battery can deliver usable power even when discharged to the point where it is delivering only five volts.

To get maximum usage between charges, radios were equipped with rheostats for cutting back the voltage of a new battery to this value. As battery voltage declined, the listener would cut more and more resistance out of the circuit to maintain the filament voltages at 5 volts. Once the voltage dipped below five, it was recharging time.

DRY BATTERY TUBES

The selection of filament voltages for

dry-cell tubes followed a similar logic. Two voltage standards eventually emerged. The type 11 (and the identical, but differently based, type 12), intended for smaller sets, was designed to be operated from a single 1.5-volt dry cell. As such, it was designed to have a filament voltage of 1.1, leaving leeway for rheostat adjustment as battery voltage declined.

The type 99, which tended to be used with multi-tube sets, was designed to be used with three 1.5-volt dry cells in series—delivering 4.5 volts. Its filament was built for 3.0-volt operation (later upped to 3.3) to give plenty of “rheostat leeway.”

Battery sets were quickly replaced with plug-in models when the technology became generally available in the late 1920s. However, they remained in use quite a bit longer on farms, many of which did not have access to commercial electricity until late in the 1930s. And so, for these farm sets, battery-radio technology had some time to evolve a little further.

For filament power, these “second generation” battery sets used a new dry battery developed by *Eveready*. The *air cell*, as it was called, was similar to the “ignition cell” we just discussed, except that its chemical processes required oxygen that was absorbed from the outside air via perforations in its case. The case was made of hard rubber, similar to that of a storage battery, but the air cell was not rechargeable and was discarded after exhaustion.

The air cell delivered two volts at its terminals, and this voltage remained essentially constant throughout its useful life. Power rating was 600 ampere-hours, which meant that a radio drawing 0.25 amperes could be operated for 2400 hours. The cost of a similar period of operation using No. 6 dry cells was about double. Of course, the special range of tubes developed for air cell use (types 30, 31 and 32) had two-volt filaments.


THOSE EARLY AC TUBES

In order to develop radios that would draw their power from the wall socket rather than from batteries, designers had to find ways to power tube filaments from alternating current. Most battery tubes, such as the heavily used 01-A, would introduce excessive hum into the received signal if operated from an AC source.

One exception was the type 71-A “power amplifier.” This tube was designed towards the end of the 1920s to get more punchy sound from storage battery sets. It was intended to replace the 01-A used as a second audio amplifier, and so of course it had a 5-volt filament. The 71-A found little use for its intended purpose because battery sets were on the way out. However, it worked very well with AC on its filament in the non-critical second audio position, and so was pressed into service as the second audio tube in most of the early AC sets.

Another exception was the rectifier tube (almost always a type 80). Its job was simply to turn high-voltage AC into DC for the receiver plate supply, and it was no way part of the path traveled by the signal through the receiver. Thus it could have AC on its filament with no consequences. Its 5-volt rating was probably selected to match that of the type 13, which it replaced. And the 13’s rating was probably selected by analogy with the type 01-A, which was certainly dominating the tube manufacturing industry in 1925 when the 13 was introduced.

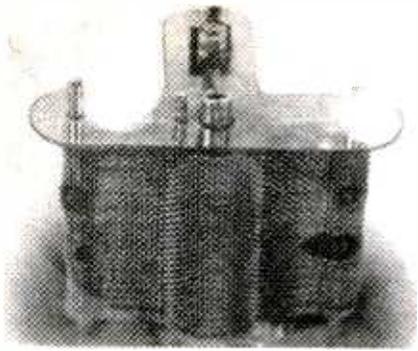The first tube especially designed to have an AC-powered filament was the type 26, developed as a replacement for the 01-A. In creating this first AC tube, designers found that they could minimize introduced hum by carefully balancing the current passing through the filament with the voltage across it. Their best results were obtained with



Close-up of type 27's innards. Top of cathode can be seen poking through plate-support structure.

1.5-volts at 1.5 amperes, and that is the rating of the filament that was put into the type 26. The 26 replaced the 01-A quite successfully as an RF and first AF amplifier, but it introduced too much hum when used in the highly critical detector stage. For that, a new tube design would be needed—one that would be even more efficient in suppressing AC hum than the type 26.

The result was the type 27, the first tube with a cathode—an innovation so successful that virtually all AC tubes from that time on would incorporate it. More on the type 27 and subsequent tube developments, next month.

In the meantime, we'd like to hear from you! While letters cannot be answered directly, your comments and questions are considered very seriously. Most are printed in this column for response by the readership at large. Write me at *Antique Radio, Popular Electronics*, 500 Bi-County Blvd., Farmingdale, NY 11735. ■

SCANNER SCENE

(continued from page 59)

Spread out with, say, a separation of 100 channels or more between two entries of the same frequency, it becomes almost the same as adding another priority channel, and less annoying than a regular priority channel inasmuch as it doesn't keep up that infernal "flashing." This way, you'll scan your desired frequency twice as often as normal. Fact is, you can do this fake priority channel trick with several frequencies you want to carefully watch. Are our readers clever, or what?

Our direct e-mail address here is Sigintt@aol.com, or you're invited to snail mail *Scanner Scene* in care of **Popular Electronics**, 500 Bi-County Blvd., Farmingdale, NY 11735. ■

DX LISTENING

(continued from page 60)

tional stories are not ignored, but it is European news and reports which hold center stage. 'NewsLink' is simply invaluable as a source of information for followers of the European scene."

Look for the North America SW newscast Tuesday through Saturday on 6040, 6085, 6145, 9640, or 11810 kHz at 0106 UTC (which is Monday through Friday evenings in the U.S.—local time). There is a second transmission on 6085, 6185, 9535, 9615, or 9640 kHz at 0306 UTC, and a third airing, perhaps the best bet for West Coast U.S. listeners, on 5960, 6045, 6185, or 9515 kHz at 0506 UTC.

Other SW stations broadcasting in English which tend to include more regional or national news include:

Voice of Greece, Athens, with about 10 minutes of news at 0130 UTC on frequencies which may include 6260, 7448, 9420, 9935, or 11645 kHz.

Albania's Radio Tirana, also with about 10 minutes of English news from this little-known Balkan country at 0145 UTC on 6115 and 7160 kHz.

R.A.E., Radio Argentina al Exterior, airing English news and short features on life in Argentina during its 0200 UTC hour on 11710 kHz.

Kol Israel, with 15 minutes of news in English from Israel Radio's domestic network at 0400 UTC on 7465, 9435, and 17545 kHz.

South Africa's Channel Africa focuses on news affecting and involving that continent. This station can be heard in English at 0500 UTC on 9675 and 11900 kHz.

HAPPY BIRTHDAY NRK

Radio Norway International celebrates its 50th birthday this year. It was on January 3, 1948, when the Norwegian monarch, King Haakon VII officially opened the international broadcasting station. Though Radio Norway International operates on a smaller scale than other European SW broadcasters, this Nordic nation has invested in some high-powered transmitting equipment necessary to provide solid signals to listeners around the world. Programs are broadcast via transmitters based in Sveio, and Kvitsøy, on Norway's west coast.

Its broadcasts are aimed mostly at

Norwegian-speaking listeners abroad, including its own merchant seamen. But it airs a weekly half-hour English program on Sundays only. The program, "Norway Now," is broadcast at 0100 UTC (9 PM EST Saturday night) on 7465 and 7545 kHz; 0200 UTC on 7565 kHz; 0400 UTC on 7520 kHz; 1300 and 1600 UTC Sunday on 13805 kHz, and at 1900 UTC on 9960 kHz. Reception reports may be sent to Radio Norway International, NRK, N-0340, Oslo, Norway; or via e-mail to radionorway@nrk.no.

DOWN THE DIAL

Here are some other SW stations for you to tune:

ARGENTINA—11710 kHz, RAE in Buenos Aires has English at 0205 UTC. This station has been heard advising listeners how to send for a QSL card.

BELGIUM—9925 kHz, Radio Vianaanderan, broadcasting in English from Brussels at 2330 UTC, has news, a DX program, mailbag, commentary, and identification.

BRAZIL—11805 kHz, Radio Globo, in Portuguese, has been heard with morning programming at 1105 UTC, with an echo announcement, many commercials, and IDs.

FINLAND—15400 kHz, Radio Finland has English programming at about 1240 UTC, with a weather report and regional news and an identification.

HUNGARY—6120 kHz, Radio Budapest has English programming at 0100 UTC, including a station identification and newscast.

PERU—9675 kHz, Radio del Pacifico in Lima can be heard here with all Spanish programming from 1600 UTC, with a local listener phone-in program, identification, frequency, and a string of commercials.

SAUDI ARABIA—11870 kHz, the Broadcasting Station of the Kingdom of Saudi Arabia is noted here with its 500-kilowatt transmitter. Programming, beginning at about 0300 UTC, is in Arabic.

SLOVAKIA—5930 kHz, Radio Slovakia International can be heard on this frequency after 0100 UTC, with identification and frequencies, then news in English.

SOLOMON ISLANDS—5020 kHz, Solomon Islands Broadcasting Corp. has been noted with fair signals, featuring island music and talk, at about 1045 UTC. ■

Market Center TM

ROBOTIC MACHINING

ROUTE, MILL, DRILL, CARVE, ENGRAVE, PAINT
IN WOOD, PLASTIC, VINYL, PC BOARD, & LIGHT METALS!

STARTING AT
\$695.00

- 4 MOTOR GANTRY MILL CONFIGURATIONS
- PC COMPUTER CONTROLLED CNC/DNC
- IMPORT/ EXPORT FILES TO OTHER CADS
- AUTO-BACKLASH COMPENSATION
- PRE-MACHINED HEAVY CASTINGS
- SIMULTANEOUS 3 AXIS MOTION
- FREE 3D CAD/CAM SOFTWARE
- AVAILABLE IN KITS OR ASSEMBLED
- EXPEDITE SERVICE ALSO AVAILABLE
- OPTIONAL ALUMINUM WAY COVERS
- .001" RESOLUTION / AMERICAN MADE



3 AXIS UNITS
FROM 12" X 12" TO
66" X 66" MACH. AREA

<http://www.uscyberlab.com>

U.S. CYBERLAB, INC. 14786 SLATE GAP RD., WEST FORK, AR 72774

CALL NOW FOR INSTANT SPECS 501-839-8293 24 HR. FAX-BACK

Weeder
Technologies

Add \$4
Ship/Hand
US & Canada

FREE
CATALOG!



Pro-Kit

PO Box 2426, Ft. Walton Beach, FL 32549

850-863-5723

Stackable RS-232 Kits

Digital I/O - 12 I/O pins individually configurable for input or output. DIP switch addressable; stack up to 16 modules on same port for 192 I/O points. Turn on/off relays. Sense switch transitions, button presses, 4x4 matrix decoding using auto-debounce and repeat. **\$32.00**

Analog Input - 8 input pins. 12-bit plus sign self-calibrating ADC. Returns results in 1mV steps from 0 to 4095. Software programmable alarm trip-points for each input. DIP switch addressable; stack up to 16 modules on same port for 128 single-ended or 64 differential inputs. **\$49.00**

Home Automation (X-10) - Connects between a TW523 and your serial port. Receive and transmit all X-10 commands with your home-brewed programs. Full collision detection and auto re-transmission. **\$38.50**

Caller ID - Decodes the caller ID data and sends it to your serial port in a pre-formatted ascii character string. Example: '12/31 08:45 850-863-5723 Weeder, Terry <CR>'. Keep a log of all incoming calls. Block out unwanted callers to your BBS or other modem applications. **\$34.50**

Touch-Tone Input - Decodes DTMF tones used to dial telephones and sends them to your serial port. Keep a log of all outgoing calls. Use with the Caller ID kit for a complete in/out logging system. Send commands to the Home Automation or Digital I/O kits using a remote telephone. **\$33.50**

Telephone Call Restrictors

Two modes of operation; either prevent receiving or placing telephone calls (or call prefixes) which have been entered into memory, or prevent those calls (or call prefixes) which have 'not' been entered.

Block out selected outgoing calls. Bypass at any time using your password. **\$35.00**

Block out selected incoming calls. Calls identified using Caller ID data. **\$46.00**

Phone Line Transponder

7 individual output pins are controlled with buttons 1-7 on your touch-tone phone. Automatically answers telephone and waits for commands. Monitor room noises with built in mic. 'Dial-Out' pin instructs unit to pick up phone and dial user entered number(s). Password protected. **\$49.00**

IR Remote Control Receiver

Learns and records the data patterns emitted by standard infrared remote controls used by TVs, VCRs, Stereos, etc. Lets you control all your electronic projects with your TV remote. 7 individual output pins can be assigned to any button on your remote, and can be configured for either 'toggle' or 'momentary' action. **\$32.00**

DTMF Decoder/Logger

Keep track of all numbers dialed or entered from any phone on your line. Decodes all touch-tones and displays them on a 16 character LCD. Holds the last 240 digits in a non-volatile memory which can be scrolled through. Connect directly to radio receiver's speaker terminals for off-air decoding of repeater codes, or numbers dialed on a radio program. **\$54.50**

CABLE T.V. EQUIPMENT

Friendly, Knowledgeable Service



ORDERS CALL:
1-800-361-4586



- All Equipment New
- Convertors & Descramblers
- 30 Day Money Back Guarantee
- 6 Month Warranty
- Visa, MC, C.O.D. Welcome

KDE ELECTRONICS, INC.

P.O. Box 1494
Addison, IL 60101

Info. 630-889-0281 HRS: Mon-Fri, 9-6 CST
Fax 630-889-0283 Sat, 10-2 CST

EPROM+ The Professionals Choice!

A DEVICE PROGRAMMER FOR BENCH AND FIELD

Uses parallel printer port!
Excellent software!
Supports all standard parts!



- FIRST GENERATION EPROMS** 2708, TMS2716*, 25XX
SECOND GENERATION EPROMS (24, 28, 32 PIN) 2716 - 27C080 (8 MEG) *ADAPTER REQUIRED DIAGRAMS INCLUDED
16 BIT EPROMS (40, 42 PIN) 27C1024 - 27C160 (16 MEG)
FLASH EPROMS (28, 32 PIN) 28F, 29C, 29EE, 29F FAMILIES PLUS BOOT BLOCK DEVICES
EEPROMS/NVRAMS (24, 28, 32 PIN) 28C014 - 28C016, X2216/12, ER5901, PLUS DALLAS 12XX
SERIAL EPROMS* (8, 14 PIN) 17XX, 24XX, 25XX, 35XXX, 59XX, 85XX, 93XX, 95XX+ER1400
BIPOLAR PROMS* (16 - 24 PIN) 74SXXX AND 82SXXX FAMILIES
MICROCONTROLLERS* (ALL FAMILIES) 874X, 875X, 87C5XX, 87C75X, 89C5X, 89CX051, 68705, 68711, PIC12XXX - 16CXXX, 17C4X PLUS FLASH AND 14000
- READ, PROGRAM, COPY, COMPARE FILE LOAD/SAVE (PLUS MUCH MORE!)
 - FULL SCREEN EDITOR W/25 CMDS + BYTE/WORD MODES
 - RUNS UNDER DOS, WIN3.1/95 ON ANY SPEED MACHINE
 - SUPPORTS INTEL HEX, S-RECORD AND BINARY FILES
 - MADE IN USA - 30 DAY MONEY BACK GUARANTEE

\$289

SYSTEM INCLUDES: PROGRAMMING UNIT, PRINTER \$5.00 SHIPPING + \$5.00 C.O.D. PORT CABLE, POWER PACK, SOFTWARE & MANUAL VISA*MASTERCARD*AMEX

ANDROMEDA RESEARCH, P.O. BOX 222, MILFORD, OH 45150
(513) 831-9708 FAX (513) 831-7562

The Greatest Thing Since Sliced Bread

Our free Consumer Information Catalog lists more than 200 free and low-cost government booklets that are helpful and practical. To get your free copy, send your name and address to:

**Consumer Information Center
Department GT
Pueblo, Colorado 81009**

AUTOMATIC TELLER MACHINES

ATM crimes, abuses, vulnerabilities and defeats exposed! 100+ methods detailed, includes: Physical, Reg. E, cipher, PIN compromise, card counterfeiting, magnetic stripe, false front, TEMPEST, tapping, spoofing, inside job, vibration, pulse, high voltage - others, con jobs. Histories, law, security checklist, internal photos, figures. *More!* \$39.

CELLPHONE PHREAKING GUIDE

How cellphones operate and are modified. Vulnerabilities to hack attack and countermeasures. Details on programming NAMs, ESNs, etc (cloning), control data formats, computing encoded MINs, ESNs, SIDHs, operating systems, PROM programming, forcing ACK, test mode and resets, cable diagrams, scanning, tracking, scanner restorations, freq allocations, roaming, Step-by-steps to keypad-reprogram 100+ popular cellphones. *More!* \$59

PAGER / BEEPER MANUAL

How Pagers work, different types and uses, freqs, advantages over and uses with cellphones, and tips and tricks. How Pagers are hacked/countermeasures. And plans for a **Personal Pocket Paging System** (transmitter and receiver). *More!* \$29

PHREAKING CALLER ID & ANI

How they work and dozens of ways of defeating Caller ID, ANI, *69, *57, Call Blocking, *67 etc. Describes ESS, SS7, CNA, CAMA, DNR, Diverters, Centrex - *more!* \$19.

BEYOND VAN ECK PHREAKING

Eavesdropping on TV and computer video signals using an ordinary TV described in detail. Includes security industry reports. Range up to 1 KM. Plans include both the ours and the original Top Secret Van Eck designs! \$29.

HACKING THE INTERNET

The latest tricks and methods being used on the Net to pirate software (warez) and the newest hacking websites. *Updated every two months.* Includes examples, countermeasures, password defeats, UNIX, Sprintnet, brute force methods, lots of tips, *and more!* \$25.

COMPUTER PHREAKING

Describes in detail how computers penetrate each other, and how VIRUSES, TROJAN HORSES, WORMS are implemented. Dozens of computer crime and abuse methods and countermeasures. Includes disk filled with hacker text files and utilities, and the legendary FLUSHOT+ protection system. Internet advice, password defeats, glossary - *much more!* Manual + PC Disk! \$39.

OTHER EXCITING TITLES

Call For Descriptions

- Hacking Fax Machines - \$29
- PBX Hacking - \$19
- Voice Mail Hacking - \$29
- Beyond Phone Color Boxes - \$29
- Hacking Answering Machines - \$19
- By an Order of the Magnitude - \$49
- Ultimate Success Manual - \$15
- Internet Cons & Scams - \$19
- Internet Tracking & Tracing - \$29
- Cookie Terminator - \$19
- Casino Hacking - \$18
- Credit Card Scams - \$29
- Radionics Manual - \$29
- Heal Thyself - \$19
- Stealth Technology - \$24
- High Voltage Devices - \$29
- The Hacker Files - \$39
- Cons & Scams - \$29
- Cryptanalysis Techniques - \$29
- Secret & Survival Radio - \$24
- Secret & Alternate IDs - \$15
- Rocket's Red Glare - \$29
- Mind Control - \$29
- EM Brainblaster - \$29

SPECIAL PROJECTS SERVICES

We will build just about anything. Ask about our application form!



STOPPING POWER METERS
As reported on "60 MINUTES"! All-new 6th Edition!! Over 45 pages jam-packed with how devices can slow down (even stop!) watt-hour meters - while loads draw full power! Device plugs into one outlet and normal loads into other outlets. Describes meter creep, overload droop, etc. Plans only! \$29.

THE I.G. MANUAL: External magnetic ways (applied to meter) to slow down and stop power meters while drawing full loads. Plans \$25.

KW-HR METERS: How watt-hour meters work, calibration, error modes (many), ANSI Standards, etc. Demand and Polyphase Meters. Experimental results to slow and stop meters by others. \$25.

All 3 (above), Only \$59! (Add \$20 for Video)

MAIL \$3 FOR OUR LATEST CATALOG TO: (free w/order)



CONSUMERTRONICS

P.O. Box 23097 ABQ, NM 87192-1097

ORDER TODAY! 505-237-2073

Fax: 505-292-4078 Web Adventure: www.tsc-global.com

Established in 1971. Featured on CBS "60 Minutes," Forbes, New York Times. Add \$5 total S/H (US, Canada). Sold for educational purposes only. Postal M.O. is fastest. VISA, MC OK. COD (\$49-\$999), add \$7.

NEW S.P.M. THE VIDEO!! \$39



Now its easier to learn about KW-HR Power Meters than ever before! This educational video shows you how they work and their anatomy. Demonstrates SPM device and external magnetic methods used to slow and stop meters! Hosted by a top expert in the field. From the novice to the pro, an excellent source of info on these exciting devices! Great in combo with our SPM related manuals!

Only \$49 for SPM video + SPM manual!!

MCM ELECTRONICS[®]


The Source For
All Of Your
Electronics Needs

Prices Effective March 19
through May 29, 1998

When ordering, please
provide this code: ▼

SOURCE CODE: POP52

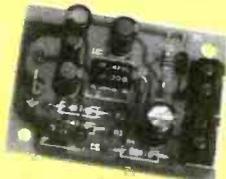These pre-assembled circuit modules are ideal for repairing or refurbishing old equipment, prototype work or hobby applications.



One Watt Single Channel Audio Amplifier

Accepts line level input, 50mV, 100Kohm. Output impedance 4-8ohm. Operates with supply voltage from 4-14VDC, 200mA. Optimum 12VDC. Board dimensions 50mm x 35mm x 20mm. Many larger amplifier modules are available.

Order # (ea.)
28-4795 \$7.49



Microphone Preamp Module

May be used any amplifier with line level input. Gain is adjustable via board mounted potentiometer. Input level 560ohm, 5mV. Output level 1Kohm, 300mV. Operates with supply voltage from 6-18VDC, 5mA. Board dimensions 50mm x 35mm x 20mm.

Order # (ea.)
28-4805 \$8.95



**FREE
Catalog!**

Call for information on many other types of pre-assembled modules including timers, counters, temperature controls, VOX relays, Programmable LCD displays and power supplies.

1-800-543-4330

www.mcmelectronics.com

Hours: M-F 7 a.m.-9 p.m., Sat 9 a.m.-6 p.m., EST.

**Same Day
Shipping!**

In stock orders
received by 5:00 p.m.
(YOUR TIME), are
shipped the same day.



MCM ELECTRONICS[®]
850 CONGRESS PARK DR.
CENTERVILLE, OH 45459
A PREMIER FARNELL Company


SOURCE CODE: POP52



Programmable LCD Single Line Display

One or two line x 16 character display is fully programmable and stores up to 14 alpha numeric messages. Backlit display allows viewing in any light. Messages can be individually displayed by closing specific contacts on terminal strip mounted to the board. Programming is easily done via a menu programming, similar to that of VCR or camcorder text. Data can be sent between multiple units to allow fast programming of a many units. Requires 12VDC, 300mA.

Order #	Description	(ea.)
28-4765	Single line	\$115.00
28-4766	Two line	140.00

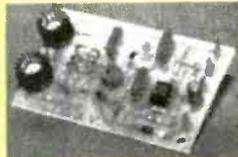

High Power FM Transmitter

Accepts line level input (300mV), and transmits audio to any standard FM radio. Output frequency can be adjusted anywhere in the 88-108MHz FM band. Requires 9-15VDC supply, 150mA. Board dimensions 50mm x 65mm x 20mm.

Order # (ea.)
28-4851 \$24.95

Two Digit LED Counter

Provides digital count from 0 to 99. Contact closure input provides one count up and reset-to-zero function. Each digit is 0.5" high. Requires 12VDC, 100mA. Dimensions 70mm x 52mm x 46mm.

Order # (ea.)
28-4785 \$14.95



Voice Activation (VOX) Relay

5A output relay is energized when audio signal level is detected. Input level 50mV, 10Kohm. Sensitivity is adjusted via a board mounted potentiometer. Requires 12VDC, 50mA. Board dimensions 75mm x 40mm x 30mm.

Order # (ea.)
28-4825 \$17.95



On Delay Timer Module

Provides precision time delay for a variety of uses. Upon contact closure, the output relay remains open, until a predetermined amount of time passes, then closes. The relay remains closed for a predetermined amount of time, then opens again. Both predetermined times are independently adjustable by two board mounted potentiometers. Relay contacts 5A. Requires 12VDC, 500mA. Board dimensions 43mm x 75mm x 30mm.

Order #	Delay Time	(ea.)
28-4750	1-180 second	\$19.95
28-4751	2-45 minute	19.95

Need a convenient power supply?

This 13.5VDC, 1 amp AC adaptor is perfect for many hobby applications.

Order # (ea.)
58-3330 \$3.99



CALL TOLL FREE
(800) 292-7711 orders only
Se Habla Español

C&S SALES
EXCELLENCE IN SERVICE

LOOK FOR OTHER
MONTHLY SPECIALS
ON OUR WEBSITE

NEW XK-700 Digital / Analog Trainer

Elenco's newest advanced designed Digital / Analog Trainer is specially designed for school projects. It is built on a single PC board for maximum reliability. It includes 5 built-in power supplies, a function generator with continuously sine, triangular and square waveforms and a 1560 tie point breadboard area. Tools and meter shown optional. (Mounted in a professional tool case made of reinforced metal).

XK-700
Assembled and Tested
\$189.95

XK-700 - SEMI KIT
w/ Fully Assembled PC Board
\$174.95

XK-700K - Kit
\$159.95



Made in the USA

Volt Alert™ By FLUKE

Volt Alert™ is the new pocket-sized AC line voltage detector from Fluke. Easy to use - just touch the tip to an outlet or cord. When it glows red, you know there's voltage in the line.

Electrician's, maintenance, service, and safety personnel can quickly test for energized circuits and defective grounds on the factory floor, in the shop, or at home.

• Fits in shirt pocket for convenience.

• All outer surfaces are unconductive for safety.

Detects voltage metallic contact.

#1AC \$19.50



DIGITAL LCR METER

Model LCR-1810

NEW

\$99.95



- Capacitance -1pF to 20µF
- Inductance 1µH to 20H
- Resistance .01Ω to 2000MΩ
- Temperature -20°C to 75°C
- DC Volts 0 - 20V
- Frequency up to 15MHz
- Diode/Audible Continuity Test
- Signal Output Function
- 3 1/2 Digit Display

20MHz Sweep / Function Generator with Freq Counter

B&K 4040

- 0.2Hz to 20MHz
- AM & FM modulation
- Burst Operation
- External Frequency counter to 30MHz
- Linear and Log sweep

10MHz B&K 4017 \$309
5MHz B&K 4011 \$239



\$399



Model M-6100

The M-6100 is Elenco's most sophisticated meter with almost every possible feature available. The M-6100 even has a computer interface for viewing and storing data on a personal computer. It comes complete with software, RS-232 cable, test leads and manual.

\$125

Model XP-581

4 Fully Regulated DC Power Supplies in One Unit
 4 DC voltages: 3 fixed - +5V @ 3A, +12V @ 1A, -12V @ 1A
 1 Variable - 2.5 - 20V @ 2A

\$89.95



SATELLITE FINDER

Model SF-100A

- Aligns Satellite Dishes
- Range 950-2050MHz
- Audio Tone
- Compact Size
- Self Power Check



\$39.95

Digital Multimeter

Model M-1700

\$39.95

11 functions including freq to 20MHz, cap to 20µF. Meets UL-1244 safety specs.



Technician Tool Kit TK-1500

28 tools plus a DMM contained in a large flexible tool case with handles ideal for everyone on the go.



\$49.95

Kit Corner

over 100 kits available

AK-700

\$14.95

Phone kit with training course.



RADIO CONTROL CAR KIT

MODEL AK-870

- 7 functions
- Remote control included

\$24.95

No Soldering Required



Model AM/FM-108K Transistor Radio Kit

with training course

\$29.95



35mm Camera Kit

Learn all about photography

AK-540

\$14.95

No Soldering Required



The New DMM900 Series Handheld Digital Multimeters


For high-performance digital multimeters that are accurate, reliable, and rugged, the DMM900 Series extends the Tektronix line of already affordable DMMs. Twice the accuracy. Up to 10 times the resolution. And a full range of capability that spans voltage, current, digital multimeters features a dual numeric display, 3-year warranty, and autoranging capability. All backed by the reliability of the Tektronix brand.

Features


DMM912, DMM914,

DMM916

- 40,000 Count Display
- 0.06% Basic DC Volts Accuracy (DMM916)
- DC Voltage Ranges from 400mV to 1,000V
- AC Voltage Ranges from 4V to 750V (True RMS)
- AC and DC Current Ranges from 10,000µA to 10A
- Resistance Ranges from 400Ω to 40MΩ
- Capacitance Ranges from 4nF to 40µF
- Frequency Ranges from 400Hz to 2MHz
- Temperature Measurements from -50°C to +98°C (DMM916, DMM914)
- 3 Year Warranty
- CE Marking

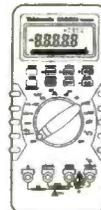

DMM 912
\$189

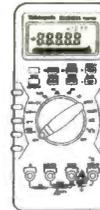

DMM 914
\$235



DMM 916
\$275

GUARANTEED LOWEST PRICES ON TEK DMMs

WE WILL NOT BE UNDERSOLD C&S SALES, INC.

150 W. CARPENTER AVENUE

WHEELING, IL 60090

FAX: (847) 541-9904 (847) 541-0710

http://www.elenco.com/cs_sales/



15 DAY MONEY BACK GUARANTEE

FULL FACTORY WARRANTY

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

Same Day
Shipping

C & S SALES
Your one stop source for
all your electronic needs!

CALL OR WRITE FOR OUR
NEW FREE 64 PAGE
CATALOG!
(800) 445-3201

Fluke Scopemeters



- 123...NEW.....\$950
- 92B.....\$1445
- 96B.....\$1695
- 99B...NEW....\$2095
- 105B.....\$2495

**ALL FLUKE
PRODUCTS
ON SALE**

**B & K PRECISION
SCOPES**

100MHz THREE-TRACE

Model 2190A



- 1mV/division sensitivity
- Sweeps to 5ns/division
- Dual time base
- Signal delay line
- 15kV accelerating voltage

\$1295.00

60MHz DUAL-TRACE

Model 2160



- 1mV/division sensitivity
- Sweeps to 5ns/division
- Dual time base
- Signal delay line
- V mode displays two signals unrelated in frequency
- Component tester

\$895.00

40MHz DUAL-TRACE

Model 1541C



- 1mV/division sensitivity
- Video sync separators
- Z-axis input
- Single Sweep
- V mode displays two signals unrelated in frequency
- Component tester

\$695

60MHz, CURSORS & READOUTS, DUAL TIME BASE

Model 2260



- Cursors and readouts
- 1mV/div sensitivity
- 23 calibrated ranges - main time base
- 19 calibrated ranges - delayed time base
- Signal delay time
- V-mode - displays 2 signals unrelated in frequency
- Component tester
- Z axis input
- Single sweep

\$1225

20MHz DUAL-TRACE

Model 2120B - 2 Year Warranty

Special \$375

Model 2125A with delayed sweep

\$539.95



- 1mV/division sensitivity
- AUTONORM triggered sweep operation
- AC, TVH, TVV and line coupling
- Calibrated 19 step time-base with x10 magnifier
- Compact low-profile design

**Affordable Spectrum
Analyzers by B&K**

500MHz Series

- Model 2615 - \$1595
- Model 2620 w/ tracking generator - \$1895

1.05GHz Series

- Model 2625 - \$2395
- Model 2630 w/ tracking generator - \$2995



Quality Scopes by Elenco

Lowest Prices of the Year!



60MHz

DS-603 \$1350

- Analog / Digital Storage
- 20MS/s Sampling Rate

S-1360 \$749


- Analog with Delayed Sweep

100MHz

S-1390 \$995

- Analog

Includes
Free Dust
Cover and
Probes

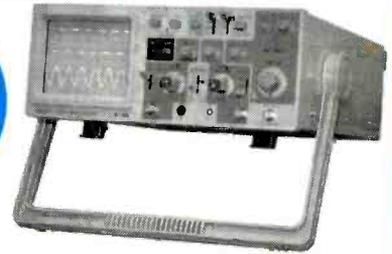

25/30MHz

DS-303 30MHz \$1095

DS-203 20MHz \$725

- Analog / Digital Storage

S-1330 \$439

- 25MHz Analog
- Delayed Sweep

S-1325 \$325

- 25MHz Analog

**2 Year
Warranty**

SIMM MODULE TESTER

B & K 898

\$625

- Tests 72 and 30-pin SIMMs to 36 bits.
- Stand alone and portable. No other equipment required.
- Automatically identifies width, depth and speed of SIMMS.
- 10 built-in tests identify most memory defects. Preheat cycle prior to test.



PORTABLE SEMICONDUCTOR TESTER

B&K 510

- In or out-of-order circuit tests for transistor, FETs, SCRs and diode ratings.



\$199.00

Fluke Multimeters

Model 70III	\$85	Model 83	\$235
Model 73III	\$115	Model 85	\$269
Model 75III	\$139	Model 87	\$289
Model 77III	\$154	Model 863E	\$475
Model 79III	\$175	Model 867BE	\$650

B&K Precision Multimeters

Model 391	\$143	Model 388A	\$99
Model 390	\$127	Model 2707	\$75
Model 389	\$109	Model 2860A	\$79
Model 5390	\$295	Model 5370	\$219
Model 5380	\$265	Model 5360	\$195

MX-9300

Four Functions in One Instrument

Features:

- One instrument with four test and measuring systems:
 - 1.3GHz Frequency Counter
 - 2MHz Sweep Function Generator
 - Digital Multimeter
 - Digital Triple Power Supply
- 0-30V @ 3A, 15V @ 1A, 5V @ 2A



\$459⁹⁵

GUARANTEED LOWEST PRICES

C & S SALES, INC.

150 W. CARPENTER AVENUE
WHEELING, IL 60090
FAX: (847) 541-9904 (847) 541-0710
http://www.elenco.com/cs_sales/



**15 DAY MONEY BACK
GUARANTEE**

FULL FACTORY WARRANTY
PRICES SUBJECT TO CHANGE WITHOUT NOTICE

UPS SHIPPING: 48 STATES 5%
OTHERS CALL FOR DETAILS
IL Residents add 8.25% Sales Tax

ALL ELECTRONICS

C O R P O R A T I O N

QUALITY PARTS

FAST SHIPPING

DISCOUNT PRICING

CALL, WRITE, FAX
or E-MAIL For A
Free 96 Page
CATALOG.
Outside the U.S.A.
send \$3.00 postage.

Stepper Motor Controller IC



E-Lab # EDE-1200
Controller IC for unipolar stepper motors. Designed to interface a logic-level signal to a stepper motor. Also capable of running independently (self-clocking). Allows for half-stepping and directional control. TTL/CMOS compatible inputs. TTL-level outputs. 18 pin DIP package. 5 vdc operation. Works for most unipolar stepper motors. Includes specs and hook-up diagram.
CAT# EDE-1200 \$12.50 each

Shielded Woofer

Designed for use in Infinity center channel video sound systems. These well constructed woofers have shielded magnets to prevent interference with picture quality.

5 1/4" 6 OHM
1" voice coil. 8 oz. magnet. 50 watts max power. 3.125" deep.



CAT # SK-7346
\$10.00 each

12 for \$96.00

RED Ultrabright LED

PAINFULLY BRIGHT RED LED
2500 to 4000 mcd @ 20 ma. These T 1 3/4 (5 mm diameter) red LEDs are significantly brighter than conventional LEDs. At close range, they are painful to look at. They are great for attention getting displays that can be seen from a distance. Water clear in off-state.

CAT # LED-42
2 for \$1.20
10 for \$5.00
100 for \$45.00
1000 for \$400.00



High Brightness FLASHER LEDs

T 1 3/4 (5mm) high brightness RED LEDs with built-in flasher unit.
3-5 Vdc operation

CAT # LED-4 2 for 90¢
100 for \$40.00 - 1000 for \$300.00



Stepper Motor


Airpax # LB82246
Unipolar, two-phase, 6 lead stepper motor. 500 ohm coil. 7.5 degrees per step. 1.4" dia. X 0.7" body. Oval mounting flange has holes on 1.65" ctrs. 0.08" (2mm) dia. shaft is 0.4" long and is fitted with a 0.31" dia. gear with 18 teeth. 15" leads.



CAT # SMT-28 \$2.00 each

"HI-8" Video Cassette

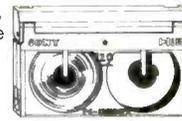SONY Hi-8 Top quality, metal particle 120 minute video cassettes. Used for a short time, then bulk-erased. Each cassette has its own plastic storage box.



CAT # VCU-8
10 for \$28.00
100 for \$250.00

PRICE REDUCTION! SL WABER "PowerMaster" Surge/Noise Suppressor

Protect your computer, phone, VCR, TV and stereo equipment from damaging transient voltage surges. Just plug in, and you've got full 3-line protection. Visual indicator lets you know that the device is functioning.
UL, CSA listed.
CAT # PW-103 \$2.75 each
Formerly \$3.75



S-VHS Tape (Used)



Super VHS tape users! Save a bundle on name-brand S-VHS, T-120 tapes. These tapes were used for a brief period, then bulk erased. The record-protect tabs have been broken out, so you will have to cover the notch with a piece of tape, but they work great and cost a fraction of the "new" price. Try some, you'll be back for more.

CAT #S-VHS \$3.00 each
10 for \$28.00 • 100 for \$250.00

Miniature Temperature Sensor (THERMISTOR)

Keystone (Similar to #RL0503-17-56K-96-MS) 30K ohms @ 25 degree C. (77 degree F.) Negative temperature coefficient. 0.2" long X 0.09" diameter, epoxy insulated bead. 1.13" long teflon insulated AWG#30 wire leads. Prepped with 0.75" long metal tabs.



CAT# THR-19
2 for \$1.50

box of 264
\$150.48
(57¢ each)

3 Volt Lithium Coin Cell

Panasonic # BR2330-1GU
3 volt, 255 mAh coin cell. Lithium batteries have a very long shelf life and are great for memory back-up protection. 0.9" diameter x 0.12" thick. 0.7" between positive and negative pc leads.



CAT #LBAT-16
2 for \$1.50
20 for \$12.00
100 for \$45.00
1K for \$300.00

Ferrite Bead

TDK # HF70RH 16X28X9
1.1" x 0.63" od x 0.35" id.
CAT # FB-24 \$1.00 each
10 for \$8.50 - 100 for \$70.00



ORDER TOLL FREE

1-800-826-5432

MAIL ORDERS TO:
ALL ELECTRONICS CORP.
P.O. BOX 567
VAN NUYS, CA 91408-0567

FAX (818) 781-2653 • INFO (818) 904-0524
INTERNET <http://www.allcorp.com/>
E-MAIL allcorp@allcorp.com



NO MINIMUM ORDER • All Orders Can Be Charged to Visa, Mastercard, American Express or Discover • Checks and Money Orders Accepted by Mail • Orders Delivered in the State of California must include California State Sales Tax • NO C.O.D • Shipping and Handling \$5.00 for the 48 Continental United States - ALL OTHERS including Alaska, Hawaii, P.R. and Canada Must Pay Full Shipping • Quantities Limited • Prices Subject to change without notice.

MANUFACTURERS - We Purchase EXCESS INVENTORIES... Call, Write, E-MAIL or Fax YOUR LIST.

Our Complete Catalog is now online  www.csi.com

Circuit Specialists Inc.

SINCE 1971

Check Out What We Have To Offer:

Fantastic DMM Offer!!!

Don't let the price fool you. This meter is a digital multimeter designed for engineers and hobbyists. Equipped with 5 functions and 19 ranges. Each test position is quickly and easily selected with a simple turn of the FUNCTION/RANGE selector rotary switch.

General Rubber Boot Included

Display: 3-1/2 Digit LCD, 21mm Figure Height with Automatic Polarity
Overrange Indication: 3 Least Significant Digits Blank

Temperature for Guaranteed Accuracy:

23 C 5 C RH<75%

Temperature Ranges:

Operating: 0 C to 40 C (32 F to 104 F)

Storage: -10 C to 50 C (14 F to 122 F)

Power: 9V Alkaline or Carbon-Zinc Battery (NEDA1604)

Low Battery Indication: BAT on Left of LCD Display

Dimensions: 188mm long x 87mm wide x 33mm thick

Net Weight: 400g

DC Voltage (DCV)

Range: Resolution: Accuracy:

200mV 100 V (1%rdg+2dpts)

2000mV 1mV (1%rdg+2dpts)

20V 10mV (1%rdg+2dpts)

200V 100mV (1%rdg+2dpts)

1000V 1V (1%rdg+2dpts)

Maximum Allowable Input: 1000V DC or Peak AC.

DC Current (DCA)

Range: Resolution: Accuracy:

200 A 100mA (1.2%rdg+2dpts)

2000 A 1 A (1.2%rdg+2dpts)

20mA 10 A (1.2%rdg+2dpts)

200mA 100 A (1.2%rdg+2dpts)

10A 10mA (1.2%rdg+2dpts)

Overload Protection: mA Input. 2A/250V fuse.

\$19.00 any qty



Our Best Offer Ever on a

High Quality Full Sized DMM

Resistance (Ω)

Range: Resolution: Accuracy:

200Ω 100mΩ (1.2%rdg+2dpts)

2000Ω 1Ω (1.2%rdg+2dpts)

20KΩ 10Ω (1.2%rdg+2dpts)

200KΩ 100Ω (1.2%rdg+2dpts)

2000KΩ 1KΩ (1.2%rdg+2dpts)

20MΩ 10KΩ (1.2%rdg+2dpts)

Maximum Open Circuit Voltage: 2.8V

Diode Test

Measures forward voltage drop of a semiconductor junction in mV test current of 1.5mA Max.

hFE Test

Measures transistor hFE.

Frequency Range: 45Hz-450Hz

Maximum Allowable Input: 750V rms

Response: Average Responding. Calibrated in rms of a Sine Wave.

AC Voltage (ACV)

Range: Resolution: Accuracy:

200V 100mV (1.2%rdg+10dpts)

750V 1V (1.2%rdg+10dpts)

CAT NO	DESCRIPTION	PRICE
9300G	Rugged High Quality DMM with Rubber Boot	\$19.00

20 AMP Switching Power Supply

A very special Circuit Specialists offer. This 20 amp continuous switching power supply is available at this fantastic low price!

Specifications
Input Voltage: AC 110V +/- 15%, 50Hz/60Hz
Output Voltage: DC9V 15V variable
Polarity: Negative ground
Current (13.8V): 25A peak, 20A continuous
Overvoltage Protection
Cooling fan inside chassis



CAT NO	DESCRIPTION	PRICE
SPS-1020G	20 Amp Switching Power Supply	\$99.00



Developer This product is used as the developer on our positive photo-resist printed circuit boards. Includes instructions, 50 gram package, mixes with water, makes 1 quart.

CAT NO	DESCRIPTION	1	10	25
POSDEV	Positive Developer	\$.95	\$.80	\$.50

Etching Chemicals/Ferric Chloride

A dry concentrate that mixes with water to make 1 pint of etchant, enough to etch 400 sq. inches of 1oz board.

CAT NO	DESCRIPTION	1	5
ER-3	Makes 1 pint	\$3.50	\$2.75



Positive Photo Resist Pre-Sensitized Printed Circuit Boards



These pre-sensitized printed circuit boards are ideal for small production runs. They provide high resolution and excellent line width control. High sensitive positive resist coated on 1oz. copper foil allows you to go direct from your computer plot or art work layout. No need to reverse art.

Single-Sided, 1oz. Copper Foil on Paper Phenolic Substrate

CAT NO	DESCRIPTION	1	10	50
PP101	100mm x 150mm/3.91" x 5.91"	\$2.55	\$1.90	\$1.70
PP114	114mm x 165mm/4.6" x 6.6"	2.98	2.45	1.98
PP152	150mm x 250mm/5.91" x 9.84"	5.40	3.98	3.60
PP153	150mm x 300mm/5.91" x 11.81"	6.15	4.48	4.10
PP1212	305mm x 305mm/12" x 12"	12.78	10.65	8.52

Single-Sided, 1oz. Copper Foil on Fiberglass Substrate

CAT NO	DESCRIPTION	1	10	50
GS101	100mm x 150mm/3.91" x 5.91"	\$ 3.90	\$2.98	\$2.60
GS114	114mm x 165mm/4.6" x 6.6"	4.80	3.49	3.20
GS152	150mm x 250mm/5.91" x 9.84"	8.69	5.98	5.78
GS153	150mm x 300mm/5.91" x 11.81"	10.20	7.20	6.80
GS1212	305mm x 305mm/12" x 12"	18.88	15.73	12.59

Double-Sided, 1oz. Copper Foil on Fiberglass Substrate

CAT NO	DESCRIPTION	1	10	50
GD101	100mm x 150mm/3.91" x 5.91"	\$ 5.07	\$3.68	\$3.38
GD114	114mm x 165mm/4.6" x 6.6"	5.95	4.29	3.99
GD152	150mm x 250mm/5.91" x 9.84"	10.47	7.39	6.98
GD153	150mm x 300mm/5.91" x 11.81"	11.95	8.69	8.30
GD1212	305mm x 305mm/12" x 12"	22.09	18.35	14.68



Etching Tank This handy etching system will handle PC boards up to 8" x 9", two at a time. Ideal for etching your PCB's! System includes an air pump for etchant agitation, a thermostatically controlled heater for keeping etchant at optimum temperature and a tank that holds 1.35 gallons of etchant. A tight fitting lid is also supplied to prevent evaporation when system is not being used. Typical etching time is reduced to 4 minutes on 1oz. copper board!

REDUCES ETCHING TIME!	CAT NO	DESCRIPTION	PRICE
	12-700	Etch Tank System	\$37.95

1/3" CCD Board Cameras

Available with PINHOLE LENS with AUDIO: STANDARD LENS with AUDIO: and STANDARD LENS with INFRA-RED. These are the world's smallest commercially available CCD board cameras!


World's Smallest B&W Board Cameras

Specifications

Image Pick-Up Device	1/3" CCD area Sensor
Picture Elements	EIA=512(H) x 492(V)
Pixel Pitch	EIA=9.6UM (H) x 7.5UM (V)
Scanning System	2 : 1 Interface
Scanning Frequency	EIA=525 lines, 60 field/sec (II) 15.750 KHz x 60 HK
Resolution	430 Lines
Minimum Illumination	0.03 LUX
S/N Ratio	45DB
Lens Mounting	4.3mm standard, 5mm pinhole
Video Output	1.0 VP-P/750OHM composite signal
Power Requirement	8-12 VDC (9VDC standard)
Power Consumption	100mA
Operating Temperature	-20C → 70 C RH 95% Max
Storage Temperature	-40C → 85 C RH 95% Max
Audio Pick-Up Sensitivity	-60 DB (ODB = 1B/UBAR. 1KNZ)
Audio Frequency Range	20 Hz to 20KHz
Audio S/N Ratio	More than 35DB
Audio Output Level	1VP-P/600 OHM

Dimensions	WDP-2000	WDS-2005	WDI-4000	PRICE EACH
	30mm (H) x 30mm (W)	30mm (H) x 30mm (W)	44mm (H) x 30mm (W)	1 5

CAT NO	DESCRIPTION	1	5
WDP-2000	1/3" B&W Pinhole Lens with Audio	\$89.00	\$77.00
WDS-2005	1/3" B&W Standard Lens with Audio	89.00	77.00
WDI-4000	1/3" B&W Infra-RED (no audio)	89.00	77.00
WDPH-558W	Plastic Housing Option for B&W Board Cameras (WDP-2000 & WDS-2005 ONLY)	13.00	12.00

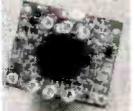

CIRCUIT SPECIALISTS, INC.

SINCE 1971
800-811-5203
602-464-2485
602-464-5824(FAX)

WE ACCEPT:   

RECEIVE OUR LATEST 132 PAGE CATALOG!

It's chock full of all types of electronic equipment and supplies. We've got I.C.'s, capacitors, resistors, pots, inductors, test equipment, breadboarding supplies, PC supplies, industrial computers, data acquisition products, personal computers and computer parts, plus much, much more. FAX us your name and address or call 800-811-5203, ext. 5, to leave a message on our catalog request line.



EARN MORE MONEY!

Be an FCC LICENSED ELECTRONIC TECHNICIAN!



Earn up to \$60 an hour and more!

Learn at home in spare time. No previous experience needed!

No costly school. No commuting to class. The Original Home-Study course prepares you for the "FCC Commercial Radio-telephone License." This valuable license is your professional "ticket" to thousands of exciting jobs in Communications, Radio-TV, Microwave, Maritime, Radar, Avionics and more...even start your own business! You don't need a college degree to qualify, but you do need an FCC License.

No Need to Quit Your Job or Go To School
This proven course is easy, fast and low cost! **GUARANTEED PASS**—You get your FCC License or money refunded. **Send for FREE facts now. MAIL COUPON TODAY!**


Or, Call 1-800-932-4268 Ext. 240

COMMAND PRODUCTIONS

FCC LICENSE TRAINING, Dept. 240
P.O. Box 2824, San Francisco, CA 94126
Please rush FREE details immediately!

NAME _____
ADDRESS _____
CITY _____ STATE _____ ZIP _____

Low Cost CAD Software Now In Windows™95

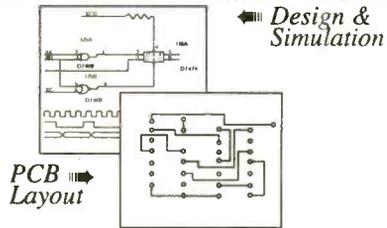

- Easy to use schematic entry program (**SuperCAD**) for circuit diagrams, only \$149. Includes netlisting, bill of materials, extensive parts libraries.
- Digital simulator (**SuperSIM**) allows you to check logic circuitry quickly before actually wiring it up. Works directly within SuperCAD and displays results in "logic analyzer" display window. Starting at \$149 this is the lowest cost simulator on the market. Library parts include TTL, and CMOS devices.
- Analog simulator (**mentalSPICE**) for \$199. Allows AC, DC and transient circuit analysis. Includes models of transistors, discretes, and op amps.
- Circuit board artwork editor and autorouter program (**SuperPCB**), starting at \$149. Produce high quality artwork directly on dot matrix or laser printers. You can do boards up to 16 layers including surface mount. Includes Gerber and Excellon file output. Autorouter accepts netlists and placement data directly from the SuperCAD schematic editor.
- New!--Complete electronic design package (**mentalMAX**) including schematic editor, analog and digital circuit simulation, and printed circuit board layout with autorouter for only \$549!

Write or call for free demo disks:
MENTAL AUTOMATION, INC.
5415 - 136th Place S.E.
Bellevue, WA 98006
(425) 641-2141
Internet: <http://www.mentala.com>

Learn MICROCONTROLLERS EMBEDDED SYSTEMS and PROGRAMMING...

...with the AES learning system/ embedded control system. Extensive manuals guide you through your development project. All programming and hardware details explained. Complete schematics. Learn to program the LCD, keypad digital, analog, and serial I/O. for your applications.



THREE MODELS AVAILABLE. Choose from an Intel 8051, Intel 8088, or Motorola 68HC11 based system. All models come with:

- 32K Byte ROM, 32K Byte RAM • 2 by 16 Liquid Crystal Display • 4 by 5 Keypad • Digital, Analog, and Serial I/O • Interrupts, timers, chip-selects • 26 pin expansion connector • Built-in Logic Probe • Power Supply (can also be battery operated) • Powerful ROM MONITOR to help you program • Connects to your PC for programming or data logging (cable included) • Assembly, BASIC, and C programming (varies with model) • Program disks with Cross Assembler and many, well documented, program examples • User's Manuals: cover all details (over 500 pages) • Completely assembled and ready to use • Source code for all drivers and MONITOR • Optional Text Book

Everything you need. From \$279.
Money Back Guarantee

Call for Free Info Pack, or see
WEB at <http://www.aesmicro.com>
714-550-8094, FAX 714-550-9941



Call 1-800-730-3232

AES 575 ANTON BLVD., SUITE 300, COSTA MESA, CA 92626, USA

Learn quick, low cost, in spare time at home.

10 EXCITING WAYS YOU CAN EARN UP TO \$2,000 A WEEK IN YOUR OWN BUSINESS. *and more*

How would you like to be your own boss! Call all the shots! Set your own hours! Enjoy financial security and a better life for you and your family! Be highly respected! It's easier and quicker than you think ... With Foley-Belsaw's help.

Here are 10 of the hottest career opportunities of the '90s! Choose any one and you'll be well on your way to owning your own profitable Big Money-Making Business. Thanks to Foley-Belsaw and their easy-to-follow hands-on do-it-yourself technical service training, you can learn at low cost in your spare time at home and start making big money quick! No previous experience or special education necessary.

This is a once-in-a-lifetime opportunity. Take that first step now. Pick the business that interests you the most and send in the coupon for Free Information today! No obligation. No salesman will call. Don't put it off and let your future slip through your fingers!



BE YOUR OWN BOSS
Earn Big Money as a
Modern-day Service Technician.



1. LOCKSMITHING With rising crime rates, people are seeking more protection than ever before. Professional locksmiths are in great demand. Course in Burglar and Fire Alarm Systems included at no extra cost.

2. SMALL ENGINE REPAIR There's an acute shortage of qualified Small Engine Repairers—many technicians have found this to be a profitable business 52 weeks a year.

3. SAW & TOOL SHARPENING 90 cents out of every dollar you take in is cash profit! The work is easy—machines do the work for you.

4. UPHOLSTERY Instead of buying new furniture, more and more people are re-upholstering to save money. And repairing damaged furniture will add additional big profits in both commercial and consumer markets.

5. WOODWORKING Build over \$3,000 worth of fine furniture while you learn. Create heirloom-quality furniture for customers or to sell. Save thousands on your own home repairs alone.

6. GUNSMITHING Collectors and hunters pay big money for professional expertise to keep their guns in tip-top condition. Law enforcement officers have their weapons serviced regularly.

7. VCR REPAIR Our unique "Fundamentals Method" concentrates on the mechanics involved in 90% of all repairs, without wasting time learning unnecessary electronics. Our way is faster, simpler, lower cost.

8. COMPUTER REPAIR There are over 60 million personal computers in service, 50,000 new ones sold every day! There are just not enough technicians to service them. Customers will pay you big bucks to keep their PCs running.

9. SATELLITE DISH/TV/ELECTRONICS SPECIALIST Few technicians are equipped to service this fast emerging field. Foley-Belsaw gives you Satellite Dish technology (including new mini-dish), along with electronic expertise to make big money servicing TVs and other devices.

10. PERSONAL COMPUTER PROGRAMMING Drastic shortage of qualified computer programmers can mean big earnings in a career for you. Learn fast at low cost.

MAIL TODAY FOR FREE INFORMATION.

Foley-Belsaw Institute 6301 Equitable Road
Kansas City, MO 64120-1395



YES! Without obligation send me the following free information kit (please check only one). I understand no salesman will call.

- | | |
|--|---|
| <input type="checkbox"/> Locksmithing Dept. 13091 | <input type="checkbox"/> Gunsmithing Dept. 92591 |
| <input type="checkbox"/> Small Engine Repair Dept. 52963 | <input type="checkbox"/> VCR Repair Dept. 62787 |
| <input type="checkbox"/> Saw & Tool Sharpening Dept. 21898 | <input type="checkbox"/> Computer Repair Dept. 64689 |
| <input type="checkbox"/> Upholstery Dept. 81500 | <input type="checkbox"/> Satellite Dish/Electronics Dept. 31558 |
| <input type="checkbox"/> Woodworking Dept. 43830 | <input type="checkbox"/> P.C. Programming Dept. 35505 |

Name _____

Address _____

City _____ State _____ Zip _____

Call TOLL-FREE 1-800-487-2100

May 1998, Popular Electronics


WORLD'S SMALLEST

Wireless Video Transmitters

Used by hundreds of hobbyists and professionals alike in R/C models, Robots, Surveillance Video, movie Special Effects, and Law Enforcement.

"... previously, I used expensive wireless units from Pelco, MVP, and Supercircuits. Nothing approaches the VidLinks in power, picture quality, size, and value. Thank you." *R. Leslie, CCTV Installer, NY.*
"The best... Incredible color, resolution... very easy to use... cool." *P. Davis, Movie Props, CA.*

Actual Size!!!

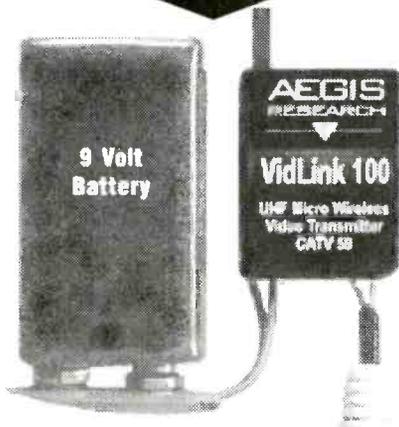

Live Remote Video From \$99.00

- Full 100 mW RF Power. Range 500ft. to 1/2mile •
 - Crystal Controlled •
- High-Resolution Full Color/ B&W video •
- Fully epoxy encased- no exposed components •
- Fully assembled- only two wires to attach •
- **MONEY BACK GUARANTEE.** •

VidLink 100: 100mW Power- upto 1/4 Mile
\$199.00 New! High-Power!

VidLink 15: 15mW Power- upto 150 Feet
\$99.00 New! Low Price- Same Size!

Cover Camera: 1 1/4" sq. Pinhole Lens
\$169.00 Pro Grade Japanese Quality!

*** Audio Module Now Available. Call. ***
Check/MO, COD +\$5.00, S&H \$5.50

**AEGIS
RESEARCH**

#671-1225 E. Sunset Dr.
Bellingham, WA
98226-3529 USA

1-604-224-0416

Visit our virtual catalog on the INTERNET at:
<http://www lynx.bc.ca/virtualspysp>



Are you overpaying . . .
... your cable company?

You are if . . . 
... you are leasing their equipment.

- Forest Electronics, Inc. offers a complete line of New Cable Decoders and Converters that are fully Compatible with your cable system.
- All systems come with: Remote Control, & Parental Guidance Feature. Volume Control is also available.
- All Equipment is fully guaranteed & comes with a 30 day money back option.

For More Information Call Us 24 Hours a Day At:


800-332-1996

FAX: 813-376-7801

Digital Oscilloscope 100 MSa/s



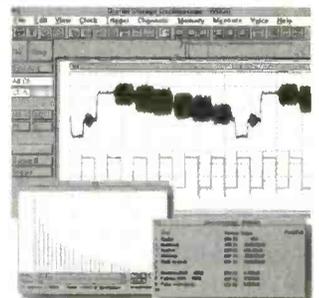- 2 Ch. Digital Oscilloscope
- 100 MSa/s max single shot rate on both channels
- 32K samples per channel
- Advanced Triggering
- Easy to use Windows and DOS software included
- Small and Lightweight (9 oz and 6.3" x 3.75" x 1.25")
- Parallel Port interface to Laptop or Desktop PC
- Optional FFT Spectrum Analyzer, Advanced Math and TVLine Trigger.




For \$499 you get the model DSO-2102S Oscilloscope, Probes, Interface Cable, Power Adapter, and Windows and DOS Software.



Link Instruments (973) 808-8990

369 Passaic Ave. • Suite 100 • Fairfield, NJ 07004
www.LinkInstruments.compe5 • Email: Sales@LinkInstruments.com

AMAZING PRODUCTS!

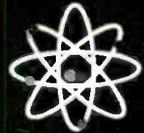

ELECTRONIC & SCIENTIFIC DEVICES

ALL NEW! LASER WINDOW BOUNCE SCIENCE PROJECTS

Remarkable concept allows user to hear sounds within a premise over a beam of laser light reflected from a window or similar surface. Experimental device provides hours of interesting and educational use. Utilizes a visible red laser that simplifies alignment and discourages illegal use. Usable range will vary-expect about 20 to 50 meters. Optional lens will increase range 200 to 400 meters! Further range requires expensive optics. Requires a sturdy video tripod (not incl.). Caution-check local law in your state if planning to use for accessing oral communication. **REQUIRES OPTICAL ALIGNMENT**



- LWB5 Plans.....\$20.00
- LWB5K KIT/PLANS.....\$149.50
- LWB50 Ready to Use With Selected Laser Pointer.....\$199.50
- LWB70 Above With High Performance Laser Gun Sight, Long Range Extender Lens and Cushioned Headsets.....\$299.50

USES SCATTERED AND DIRECT REFLECTIONS

WIRELESS LAB KITS

ALL PARTS TO BUILD 6 EXCITING TRANSMITTER PROJECTS

- 1 Super Sensitive Ultra Clear 1Mile+ Voice Transmitter
- 2 1 Mile + Telephone Transmitter
- 3 Beeper Alert for Above Telephone Transmitter
- 4 Tracking/Homing Beacon "Beeping Transmitter"
- 5 Transmitter Rebroadcast Video or Audio Outputs
- 6 Short Range TV/FM Disrupter NEAT FRANK!!! Discretion Advised

All 6 Above Kits Plus FREE Info Data Pack on "HELPFUL HINTS" Building and Tuning Wireless Devices

COMBO Kits and Plans.....\$59.50

ULTRA BRIGHT LASERS

4 to 7x brighter 650-630 nm Radiation

ALL METAL CONSTRUCTION
1 YEAR WARRANTY

BATTERIES INCLUDED

- LAPN65 15mw equiv 2000 ft.....\$29.95
- LAPN63 30mw equiv 3000 ft.....\$69.95

FOCUSABLE LASER POINTER

LAPN65F Focusable Above LAPN65...\$39.95

TRANSISTORIZED TESLA COIL

Turns a Light Bulb into a Spectacular Plasma Display

Transmits Wireless Energy
Noiseless Operation
Pyrotechnic Effect
12 VDC/5 Amps or Battery
115 VAC Optional Converter
Adjustable Frequency
Control Far Effect



- TCL5 Plans.....\$8.00
- TCL5K Kit/Plans.....\$59.50
- TCL50 Ready to Use.....\$99.50
- 12DC/7 12VDC@7Amps.....\$39.50

NEW CYBERNETIC EAR!

Use For Courtesy Lowering of TV Volume Control etc. Detect Rattles and Other Mechanical Abnormalities, Leaking Gases, A/c, or Carbons. Great Safety Aid for Shop etc. Enhances Most Hearing 3 to 4 Times! Adjustable Volume Control. Fits Easily into Either Ear. Many Many Uses!

CYBEREAR Ready to use...\$19.95

3 MI TELEPHONE TRANSMITTER

Tunable On FM Broadcast. Excellent Telephone Project. Only Transmits When Phone is Used

VWPM7 Plans Only.....\$7.00

Uses Readily Available Parts and Pieces

ELECTRIC CHARGE GUN

WITH 15 FOOT RANGE!!

Stuns and Immobilizes Attackers From a Distance. More Knockdown Power than a Handgun!

Check Your State Legality

FREE!!! 100KV Stun Gun

ECG10 With STUN100.....\$249.50

STUNGUNS SOLD SEPERATELY

STUN200 200KV StunGun.....\$49.50

STUN300 300KV StunGun.....\$69.50

JACOBS LADDER

Observe a pyrotechnical display of "traveling" fiery plasma. Starts off as 1/2" arc and expands to over 3" before evaporating into space. This is an excellent attention getting display as well as a winning science project!! With arc control.

- JACK1 Plans.....\$8.00
- JACK1K Kit Minus Case.....\$129.50
- JACK10 Ready to Use.....\$249.50

- 12KVGEN20 Pwr Supply Only.....\$99.50
- 12KVGEN2K Kit of Pwr Supply.....\$79.50

250KV TESLA COIL

10-14' of Explosive Bolts of Lightning

Transmit Wireless Energy Strange and Bizarre pyrotechnical effects. Ion Motors Anti-Gravity Size 20" H x 8" Sq Weight - 25 Pounds 115 Volts/2 Amps AC Labeled "Use Caution"

- BTC3 Plans.....\$15.00
- BTC3K Kit/Plans.....\$349.50
- BTC30 Ready to Use.....\$449.50
- BTC4 Plans. 500kv Unit.....\$20.00

HIGH CRIME AREA SECURITY!

INFINITY+ TRANSMITTER

ROOM MONITOR/ LINE GRABBER/CONTROLLER

- MONITOR YOUR PREMISES Avoid ambushes and break ins.
- ACCESS ON GOING CALLS Longwinded teenagers!
- CONTROL 8 APPLIANCES Remote control your hotmail!!!
- EXTRA ADDED FEATURE!!! Selects Those "CON HANGERS" Toll Calls Made From Pay Phones!

- TELCON3 Plans.....\$10.00
- TELCON3K Kit/Plans.....\$99.50
- TELCON30 Ready to Use.....\$149.50

Programmed With built in BEEPER ALERT

PHASOR BLAST WAVE PISTOL

130 db of Directional Sonic Shock Waves Energy Handheld and Battery Operated

- PPP1 Plans.....\$8.00
- PPP1K Kit/Plans.....\$49.50
- PPP10 Ready to Use.....\$79.50

ATTENTION! HIGH VOLTAGE EXPERIMENTERS

Battery Powered Mini Sized Modules for research in: HOVERCRAFT, ION GUNS FORCE FIELDS, SHOCKERS etc

MINIMAX4 4KV@10ma.....\$19.50

BURNING LASER RAY GUN

UTILIZES LOSSLESS ENERGY CHARGING

All Parts Available

LAGUN2 Plans.....\$20.00

BURNING CO2 BENCH LASER

HOTTER THAN MOST TORCHES!

- All Parts Available
- LC7 Plans.....\$20.00

KINETIC ELECTRIC GUN

PIONEER A FUTURISTIC WEAPON!

500 Joules Energy Storage
Constant Current Charging
Triggered Spark Switch
Ballistic Velocities
Handheld Battery Operated
Labeled A Dangers product

EGUN1 Plans with Parts List.....\$20.00

All Parts are Individually Available

3MI FM BC TRANSMITTER

Safety Product Allows Listening to Children or Invalids in Hazardous Areas, Pools, Ponds etc. Great Security Intrusion Alert! Uses FM Table Top Radio.

FMV1K Kit/Plans.....\$39.50

ION RAY GUN PROJECTS ENERGY!

Star Wars Technology Demonstrates Weapons Potential!

IOG7K Kit/Plans.....\$99.50

GRAVITY GENERATOR

Demonstrates a unique phenomena of electrical reactions that produce the effect of "anti-gravity". You build and levitate a small mock space ship from simple materials. Excellent scientific demonstration of a fascinating method of levitation. *Levitate an Object!*

- GRA1 Plans and Book.....\$20.00
- GRA1K Pwr Sup Kit/Plans.....\$99.50
- GRA10 Assbled Pwr Sup...\$149.50

ELECTRONIC HYPNOSIS AND MIND CONTROL

Generates Highly Effective Audible and Visual Stimuli With Bio-Feedback That Can Induce Hypnotic as Well as ALPHA Relaxed States of the Mind. Place Subjects "Under" Your Control. Enhances Hidden PSYCHIC Ability in Many People!

- MIND Plans.....\$15.00
- MIND2K Kit and Plans.....\$49.50
- MIND20 Assembled.....\$79.50

TELEPHONE TAPING SYSTEM

EXTENDED X4 PLAY

Tapes Phone Conversation 20 Mega Input Z1 Check Laws!

TAP30X Ready to Use.....\$84.50

BEEP10 Beeper Alert.....\$29.95

SHOCK FORCE FIELD/VEHICLE OBJECT ELECTRIFIER

Hand Shock Balls, Wanda, Electrify Objects. Great Payback for Those Who Buy!!

SHK1K Kit of Pwr Module....\$19.50

ATTENTION!! RAILGUN EXPERIMENTERS

HIGH ENERGY PULSER

RAIL GUN, COIL GUN, EXPLODING WATER, ANTIGRAVITY, MASS WARPING, LEVITATION, PLASMA PROPULSION, LATTICE SNAPPING, EMP etc

- Lossless Energy Charging
- Programmable Voltage to 2 KV and Energy Control to 3 KJ
- Triggered Spark Switch (IKJ)
- Universal 12 VDC or 115 VAC
- 7.5 X 7.5 X 7" Light weight

- HEP3 Plans High Energy Pulser/Ignitor.....\$15.00
- HEP3K Kit/Plans (Minus Energy Storage).....\$199.50
- HEP30 Assembled (Minus Energy Storage).....\$299.50
- HEPCAP 800 Joules Energy Storage.....\$199.50

INFORMATION

UNLIMITED DEPT PE 1097
BOX 716 AMHERST, N.H. 03031

24 Hr Toll FREE "Orders Only" Line 1-800-221-1705

Fax Your Order to 1-603-672-5406

9 to 5 pm EST Information Line 1-603-673-4730


See Our Web Site at <http://www.amazing1.com>

We Accept MC, VISA, Cash, MO, Checks. Please add \$5.00 Shipping. COD Orders Add Additional \$4.75. REQUEST A FREE CATALOG!!

May/1998, Popular Electronics

New and Pre-Owned Test Equipment

Goldstar

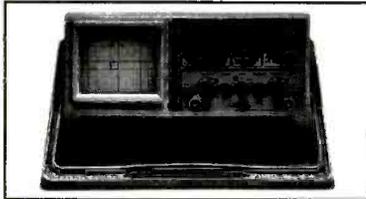

Model OS-9100P → **\$899.00**

Full 100 MHz Bandwidth!

- Dual-Channel, High Sensitivity
- TV Synchronization Trigger
- Calibrated Delayed Sweep
- Includes Two Probes, 2 Year Warranty

FREE SHIPPING!
ON GOLDSTAR EQUIPMENT
ANYWHERE IN THE U.S.
Excluding AK & HI



BK PRECISION
MAXTEC INTERNATIONAL CORP.

Model 4040 \$499.00

20 MHz Sweep/Function Generator

LOWEST PRICES EVER!

NEW FLUKE MULTIMETERS & TEKTRONIX OSCILLOSCOPES

The Industry Standard in Multimeters

Fluke Model 87 \$285.00 !!!



TOLL FREE 1-800-99-METER

Pre-Owned Oscilloscope Specials

Tektronix 2215	60 MHz	\$549.00
Tektronix 465	100 MHz	\$579.00
Tektronix 465B	100 MHz	\$729.00
Tektronix 475	200 MHz	\$829.00
Tektronix 475A	250 MHz	\$929.00
Tektronix 2465	300 MHz	\$2,499.00

- Professionally Refurbished
- Aligned & Calibrated to Original Specifications
- The Industry Standard of Oscilloscopes
- 6 Month Warranty - The Longest Available!

See us on the Web!

www.fotronic.com

Test Equipment Depot

A FOTRONIC CORPORATION COMPANY

P.O. BOX 708 Medford, MA 02155


(617) 665-1400 • FAX (617) 665-0780

email: afoti@fotronic.com

LEADER

For Professionals Who Know The Difference

- Oscilloscopes
- Video Sync/Test Generators
- Waveform Monitors/Vectorscopes
- EFP/ENG Instruments
- RF Signal Level Meters
- Audio Generators & Meters
- Frequency Counters
- Meters & Bridges
- Power Supplies
- Function Generators
- RF Generators

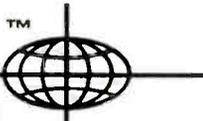PRINT™ 
Products International



Call, fax or email for your free test and measurement instrument catalog today!

800-638-2020 * Fax 800-545-0058

Email: SMPRODINTL@aol.com

Test Instruments, Equipment, Tools & Supplies For Electronic Production, Maintenance & Service
8931 Brookville Road, Silver Spring, MD, 20910 * 800-638-2020 * Fax 800-545-0058

CIRCLE 47 ON FREE INFORMATION CARD

**OVER
30,000
ITEMS
IN STOCK**

Dalbani®

The Ultimate Saving Source

**LARGE VARIETY
SAME DAY SHIPPING**


Over 6,000 new items

SHIP UP TO
51bs
FOR ONLY

\$3.95



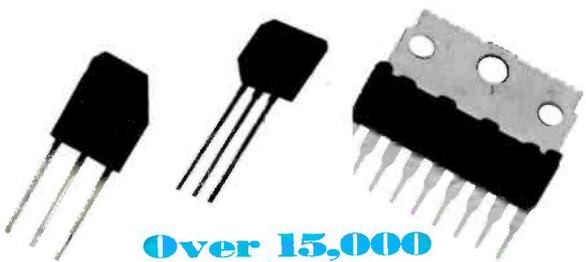- Audio/Video Service Parts**
- Audio/Video Accessories**
- Professional Audio**
- Security Products**
- Connectors**
- Technician Aids**
- Chemicals**
- Test Equipments**
- Soldering Equipment**
- Automotive Products**
- Automotive Installation Kits**



**Over 15,000
Original SEMI in stock.**

Dalbani®

4225 NW 72ND AVE. MIAMI, FLORIDA 33166
TEL : (305) 716-1016 ----- FAX : (305) 594-6588

TO ORDER A CATALOG CALL "258"

1-800-325-2264

COPY RENTAL TAPES

WITH OUR VIDEO STABILIZERS

BEFORE

AFTER



FREE CABLE TV CATALOG!

The clearest picture possible playing back movies. **GUARANTEED** to eliminate copy protection.

- No Rolls/Jitters/Flickers/Fading
- Works on all TV's, VCR's Beta & Cable
- Gold Video Connectors & Cables Included
- 1 Year Warranty
- Money Back Guarantee

to eliminate copy protection.

VISION ELECTRONICS

1-800-562-2252

2609 S. 156TH CIRCLE • OMAHA, NE 68130
<http://www.modernelectronics.com>

Cable TV Outlet



Get the Clearest Coverage of Sports, Movies, News, Main Events and Adult!

- Unbeatable Wholesale Pricing-
- Converters/Descramblers-
- Filters and Accessories-
- Premium Channel Coverage-
- Full Satisfaction Guaranteed-

QB VIDEO

Open M-F 9a to 5p (CT)

1-800-249-3025

Visa, MC & C.O.D.'s Welcome

PROGRAMMERS OVER 50 MODELS

ADVANTECH EETOOLS NEEDHAMS DATA I/O ICE TECHNOLOGY HILO SYSTEM GENERAL CHROMA MODULAR CIRCUIT TECHNOLOGY XELTEK



PROMAX EMP-20 MEGAMAX MEGAMAX4 SIMM/SIP TESTER EMUPA

- | | |
|--------------------------|------------------------|
| CALL ADVANTECH LABTOOL | 599 EETOOLS SIMMAX |
| 629 ICE TECH MICROV | 795 CHROMA SIMM/SIP |
| 650 EETOOLS ALLMAX + | 359 MOD-MCT-EMUPA/R |
| 409 EETOOLS MEGAMAX | 279 MOD-MCT-EMUP/R |
| 509 EETOOLS MEGAMAX4 | 49 EPROM 1G TO 512K |
| 369 XELTEK SUPERPRO II | 69 EPROM 1G TO 1MEG |
| 409 XELTEK SUPERPRO II P | 99 EPROM 4G TO 1MEG |
| 249 XELTEK SUPERPRO L | 199 EPROM 16G TO 1 MEG |
| 165 XELTEK ROMMASTER II | 89 EPROM 1G TO 8MEG |
| 479 MOD-MCT-EMUPA | 129 EPROM 4G TO 8MEG |
| 739 STAG ORBIT-32 | 250 EPROM 8G TO 8MEG |




LABTOOL.48 MICROMASTER SUPERPRO ALLMAX PLUS ROMMASTER

General Device Instruments

Sales 916-393-1655 Fax 916-393-4949 BBS 983-1234
 Web www.generaldevice.com E-Mail icdevice@best.com

SURVEILLANCE HIDDEN CAMERAS

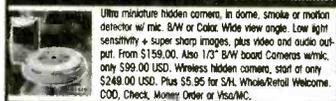DIRECT FROM MANUFACTURER—BEST PRICE IN THE MARKET



Ultra miniature hidden camera. In dome, smoke or motion detector w/ mic. B/W or Color. Wide view angle. Low light sensitivity + super sharp images, plus video and audio output. From \$159.00. Also 1/3" B/W board cameras w/mic. only \$39.00 USD. Wireless hidden camera, start at only \$249.00 USD. Plus \$5.95 for S/H. Wholesale/Rental Welcome. C.O.D., Check, Money Order or Visa/MC.

BOLIDE INTERNATIONAL CORPORATION
 PH: (800) 355-8895 or (818) 575-8178
 9660 Flair Drive #318, El Monte, CA 91731
<http://www.bolideamazingproducts.com>

Cable TV Converters

Save \$100 Dealers Welcome

30 Day Money Back

Call Us Last!

We will beat any advertised price

2 Pc. Combo \$95.⁰⁰


Minimum 10 Lot

1-800-842-9670

T.C.V.

7 SECOND IC REMOVER

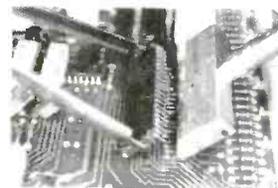Remove 100's of good IC's per hour
 Won't damage IC's or circuit boards



- 8 Desoldering Tools (Remove 6 thru 40 pin IC's) \$ 89.95
- 10 Desoldering Tools (Remove 6 thru 64 pin IC's) \$114.95

FRANKS ELECTRONICS

P. O. BOX 357 — GLEN, MISS. 38846
 Orders By Mail Only. No COD's.

ADAPT-11 68HC11 Modules for Solderless Breadboards

- miniature 2.0" by 2.8" module
- plugs vertically into solderless breadboard for easy development
- BOOT/RUN switch for easy programming via PC serial port
- all I/O lines on dual row connector



Complete modular prototyping system! Expansion accessories available!

For just US\$74.95, our Starter Package (AD1ISP) provides everything you need to get going fast. Now you can harness the power of the popular 68HC11 in your projects! Includes ADAPT-11 with 68HC11E2, providing 2K EEPROM (re-programmable), 8 channel 8-bit Analog-to-Digital Converter (ADC), hardware timers, counters, interrupts, Serial Peripheral Interface (SPI), Serial Communications Interface (SCI), and more! On-board RS-232 Interface (cable included), 5-volt regulator, 8MHz crystal, reset circuit, and convenient program/run switch. Comes with non-commercial versions of '11C11 Assembler, BASIC, & C, as well as handy utilities & example code. Includes Motorola 68HC11 Pocket Programming Reference Guide and manual with schematic. All you need is a PC to write & program your software, a DC power supply, and a solderless breadboard (or protoboard) to build your application circuits on for use our modular accessories!

Visa • MasterCard • American Express • Discover
TECHNOLOGICAL ARTS
 309 Aragona Blvd., Suite 102, Box 418, Va. Beach, VA 23462
 1844 Bayview Avenue, Box 1794, Toronto, ON M4G 3C2
 voice/fax: (416) 963-8996 www.interlog.com/~techart

Slot Machines \$ 449.00



- Free Shipping
- Slot Machine Demo Video \$ 5.99
- 40 - Minutes
- Brochure \$ 1.00
- Magic Box
- Test Chips
- Filter Kits
- Beep - Beep
- Buzz - Buzz
- Notch Filters

Video Media www.nutnet.com
 P.O. Box 93/6025
 Margate, FL 33093
 (954)-752-9202



Popular Electronics, May 1998

BE A LOCKSMITH!

Home study. Learn locksmithing for a great career, or to start your own at-home business. **FREE LITERATURE: 800-223-4542**

Name _____ Age _____
 Address _____ Phone _____
 City _____ State _____ Zip _____
The School of Locksmithing, Dept. LKF341
 PCDI, 6065 Roswell Rd., Atlanta, GA 30328

WORK AT HOME!

LEARN ELECTRONICS!

Home study. Make excellent money. Repair and install camcorders, TVs, VCRs, stereos, sound and lighting, alarm systems, and more! **FREE LITERATURE: 800-223-4542**

Name _____ Age _____
 Address _____ Phone (____) _____
 City/State _____ Zip _____
School of Electronics, Dept. ELF341 PCDI, 6065 Roswell Rd., Atlanta, GA 30328

ALFA ELECTRONICS, INC.

HIGH QUALITY TEST EQUIPMENT PROVIDER

1-800-526-2532 (526-ALFA)

15 Days Money Back Guarantee!

	<h3>DMM</h3> <p>DMM-18 (\$19.95) 3 1/2 digit, DC/AC V, Ω, hFE, diode, signal output(+3V, -0.5Vsq, 50% duty)</p> <p>DMM-17B (\$39.95) 3 1/2 digit, DC/ACV, contin., DC/ACA, Ω, Capacitance, hFE, diode, Freq</p> <p>DMM-20 (\$74.95) AC/DC (V, A), Freq, cont., Capac, Induct., Ω, hFE, diode, duty cycle</p> <p>DMM-22 (\$89.95) 4000counts, bar graph, Freq, AC/DC(V,A), Ω, Capacitance, diode, contin.</p> <p>DMM-23T (\$99.95) 4 1/2 digit, high resol. (10uV, 10nA, 10mΩ), hFE, diode, contin., true rms</p> <p>DMM-89S (\$179.00) true rms, AC/DC (V,A), Ω, bar graph, freq., capac., dBm, logic, diode</p>		<h3>LCR METER</h3> <p>CAP-15 (\$49.95) 3 1/2 digit, 0.1pF-20mF, 9 Ranges, 0.1pF resolution zero adjustment.</p> <p>LCR-195 (\$89.95) 1uH-200H (induct.), 0.1pF-200uF(Capac.), 0.01Ω-20M Ω(resistance)</p> <p>LCR-814 (\$189.95) 0.1uH-200H, 0.1pF-20mF, 0.1Ω-20MΩ, Q Factor, dissipation, zero adjust</p> <p>LCR-131D (\$229.95) autorange, 0.1uH-10kH, 0.1pF-10mF, 1mΩ-10MΩ, Q Factor, serial/parallel, 120Hz/1kHz testing mode</p>	<h3>FREQ. COUNTER</h3> <p>FC-1200 (\$129.95) 1.25GHz Handheld, 8 digits display, 10ppm accuracy, sensitivity 5mV (130-350MHz), 30mV (440MHz), 22m (800MHz), batteries or 9V adapter.</p> <p>FC-2500 (\$179.95) 2.5GHz Handheld, 8 digits display, 4ppm accuracy, sensitivity <50mV, batteries or 9V adapter.</p> <p>FC-5270A (\$149.95) 1.2 GHz bench type, 8 digit, 10 ppm, 35mV sensitivity, 10Vp-p max. input, power by 9V adapter.</p> <p>FC-5700 (\$329.95) 1.3GHz bench type, 8 digit, 1 ppm accuracy, 20mV sensitivity, period 0.1us to 100ms. Ideal for test & repair of audio instrument.</p>																		
	<p>DMM-113 (\$24.95) Pocket Size, DC/ACV, Ω, diode, Continuity beeper</p> <p>DMM-120 (\$24.95) economy type, DCV, ACV, DCA, Ω, hFE, diode</p> <p>DMM-122 (\$59.95) DC/AC(V,A), Ω, hFE, diode, capacitance, freq, logic, continuity</p> <p>DMM-123 (\$44.95) DMM + capacitance, DC/AC(V,A), Ω, hFE, diode, continuity</p> <p>DMM-124 (\$69.95) Electrical+Temp, DC/ACV, capacitance, freq, 3 phase, diode, contin.</p> <p>DMM-125C (\$54.95) Autorange + bar graph, DC/ACV, Cap, Ω, diode, continuity beeper</p>		<h3>FLUKE DMM</h3> <table border="1"> <tr> <th>HandHeld</th> <th>Scope Meter</th> </tr> <tr> <td>12 \$ 84.95</td> <td>92B \$1,399</td> </tr> <tr> <td>70-II \$ 75.95</td> <td>96B \$1,699</td> </tr> <tr> <td>73-II \$ 97.95</td> <td>99B \$1,999</td> </tr> <tr> <td>75-II \$129.00</td> <td>105B \$2,499</td> </tr> <tr> <td>76-II \$175.00</td> <td>863E \$469</td> </tr> <tr> <td>77-II \$155.00</td> <td>867E \$659</td> </tr> <tr> <td>79/29-II \$175.00</td> <td></td> </tr> <tr> <td>87 \$287.00</td> <td></td> </tr> </table>	HandHeld	Scope Meter	12 \$ 84.95	92B \$1,399	70-II \$ 75.95	96B \$1,699	73-II \$ 97.95	99B \$1,999	75-II \$129.00	105B \$2,499	76-II \$175.00	863E \$469	77-II \$155.00	867E \$659	79/29-II \$175.00		87 \$287.00		<h3>SPECIALTY</h3> <ul style="list-style-type: none"> • Sound Meter \$169.95 • EMF Tester \$69.95 • Conductivity \$169.95 • Thermometer \$69.95-\$89.95 • Humid/Temp meter \$169.95 • Press. meter \$299.95 • Electr. scale \$89.95 • Watt Meter \$129.95 • High Voltgae Probe \$59.95 • pH Meter \$79.95 • Light Meter \$80-\$90 • Light Adapter \$49.95 • Anemometer \$179.95 • Anemometer adapter (And More) \$89.95
HandHeld	Scope Meter																					
12 \$ 84.95	92B \$1,399																					
70-II \$ 75.95	96B \$1,699																					
73-II \$ 97.95	99B \$1,999																					
75-II \$129.00	105B \$2,499																					
76-II \$175.00	863E \$469																					
77-II \$155.00	867E \$659																					
79/29-II \$175.00																						
87 \$287.00																						

OSCILLOSCOPE

Dual Trace, Component Test, 6" CRT, X-Y Operation, TV Sync, CH2 Output, Graticule Illum, 2 Probes(x1,x10)

- PS-200 20 MHz Dual Trace \$339.95
- PS-205 20 MHz Dual w/ Delay Sweep \$429.95
- PS-400 40 MHz Dual Trace \$494.95
- PS-405 40 MHz Dual w/ Delay Sweep \$569.95
- PS-605 60 MHz Dual w/ Delay Sweep \$769.95
- PS-1000 100MHz Dual Trace \$999.95

Digital Scope

- DS-303 30MHz Digital, 20 Samples/sec \$849.95
- DS-303P RS-232 interface, 30Mhz \$1,049.95

Scope Probe

- HP-9060 (60MHz) \$15, HP-9150 (150MHz) \$22, HP-9250 (250MHz) \$29, HP-9258 (250MHz, 100:1) \$39

AUDIO/RF/FUNCT. GENERATOR

RF Generator

- SG-4160 (\$124.95) 100kHz-150MHz sinewaves in 8 ranges, 100mV at 35MHz
- SG-4162 (\$229.95) Generate same signal as SG-4160, but with int. counter (150MHz).

Audio Generator

- AG-2601 (\$124.95) 10Hz-1MHz, 0-8Vpp sine, 0-10Vpp squarewave
- AG-2603 (\$229.95) Same as AG-2601, but with additional counter and digital display.

Function Generator

- FG-2100A (\$169.95) 2Hz-2MHz, 5mV-20Vpp
- FG-2102AD (\$229.95) same as FG-2100A, but with int. counter and TTL, CMOS output.
- FG-2103 (\$329.95) Sweep 0.5Hz-5MHz, linear/log, VCG, GCV, and int. counter

POWER SUPPLIES	Single Output DC Power Supplies	Dual Tracking	Triple Output
<ul style="list-style-type: none"> • Short Circuit and overload protected • Constant current, constant voltage mode • 0.02%+2mV line regulation; 0.02%+2mV load regulate <p>Analog Meters Display</p> <ul style="list-style-type: none"> PS-303 (\$159.00) 30V/3A PS-305 (\$219.95) 30V/5A PS-8110 (\$289.95) 60V/5A PS-8112 (\$399.95) 60V/5A PS-1610 (\$289.00) 16V/10A PS-8107 (\$399.95) 30V/10A <p>Digital Voltage, Analog Current</p> <ul style="list-style-type: none"> PS-8200 (\$179.95) 30V/3A PS-8201 (\$239.95) 30V/5A <p>Digital Volt & Current Display</p> <ul style="list-style-type: none"> PS-8300 (\$199.95) 30V/3A PS-8301 (\$259.95) 30V/5A 	<ul style="list-style-type: none"> • Short Circuit & overload protected • Constant current & constant mode • Independent or Tracking <p>Dual Tracking (Analog V & I Displays)</p> <ul style="list-style-type: none"> PS-303D (\$314.95) 30V/3A/30V/3A PS-305D (\$399.95) 30V/5A/30V/5A PS-8108 (\$549.95) 60V/3A/60V/3A PS-8109 (\$699.95) 60V/5A/60V/5A 	<ul style="list-style-type: none"> • One fixed 5VDC, 3 Amp output • Parallel to double current output (PS-8102 & PS-8103 only) <p>Triple Output (Analog displays)</p> <ul style="list-style-type: none"> PS-8102 (\$399.95) 30V/3A/30V/3A PS-8103 (\$489.95) 30V/5A/30V/5A <p>Digital Displays</p> <ul style="list-style-type: none"> PS-8202 (\$499.95) 30V/3A/30V/3A PS-8203 (\$549.95) 30V/5A/30V/5A 	

INSTEK® Test & Measuring Instrument

ISO 9002 Cert. #934163 (2 Years Warranty)

OSCILLOSCOPE	DC POWER SUPPLIES	FUNCTION GENERATOR	BENCHTOP DMM
<p>OS-653 \$699.95 50MHz Triggering</p> <p>OS-622B \$399.95 20 MHz Oscilloscope</p>	<p>Triple Output</p> <p>PC-3030 (\$499.95)</p> <p>PC-3030D (\$549.95)</p> <p>Single Output</p> <p>PS-1830 (\$209.95) 18V/3A</p> <p>PS-1850 (\$219.95) 18V/5A</p> <p>PS-3030 (\$224.95) 30V/3A</p> <p>PS-6010 (\$209.95) 60V/10A</p> <p>PR-3060 (\$314.95) 30V/6A</p> <p>PR-6030 (\$314.95) 60V/3A</p> <p>Programmable</p> <p>PPS-1860G (\$1,099.95)</p> <p>PPS-3635G (\$1,099.95)</p> <p>PPT-6020G (\$1,099.95)</p> <p>PPT-1830G (\$1,399.95)</p> <p>PPT-3615G (\$1,399.95)</p> <p>FG-830 (\$1,499.95) 30MHz Synthesized Function Gen.</p> <p>• Output: sine, tri., square, sync out, arb. waveform</p>	<p>FG-8015G (\$189.95) Sweep 0.02Hz-2MHz, no counter</p> <p>• Sine/Squ/Tri/pulse/Ramp</p> <p>FG-8016G (\$239.95)</p> <p>0.02Hz-2MHz w/ counter</p> <p>• Pulse, function generator</p> <p>FG-8017G (\$249.95) Sweep Sine/Tri/Squ/TTL/CMOS</p> <p>0.02Hz-2MHz, FM mod.</p> <p>FG-8019 (\$399.95) Sweep 0.02Hz-2MHz w/counter</p> <p>• INT/EXT AM/FM mod</p> <p>FG-8019 (\$209.95)</p> <p>0.02Hz-2MHz w/counter</p> <p>FG-8050 (\$499.95) Sweep 0.05Hz-5MHz w/counter</p> <p>• INT/EXT AM/FM mod</p> <p>• 20MHz Freq. resolution</p> <p>• Linear/log sweep</p> <p>• Arbitrary modulation</p> <p>• RS232, IEEE-488(option)</p>	<p>DM-8034 (\$179.95) 3 1/2 dgt</p> <p>• AC/DC(V,A), Ω, diode</p> <p>1000V, 20A, 0.5% accu.</p> <p>DM-8040 (\$339.95) 3 1/2 dgt</p> <p>• ACV to 50kHz, true rms</p> <p>DM-8055 (\$649.95) 5 1/2 dgt</p> <p>• 0.006% basic accuracy</p> <p>• 1uV, 1mΩ, 1nA resolution</p> <p>• dBm, auto, REL, min/max</p> <p>DM-8055G (\$889.95) GPIB</p> <p>• Same funct. as DM-8055</p> <p>Frequency Counters</p> <p>FC-8131 (\$469.95) 1.3GHz</p> <p>FC-8170 (\$629.95) 7GHz</p> <p>UC-2010G (\$294.95)</p>

Programable Electronic Load (PEL-300)
(Patent No. 5,101,812A4)

- Operating Rating: voltage 3-60V, current 6mA-60A, power 300W, temp 0-40C(operate)-10-70C (store)
- Over voltage, over current, over power protection
- Operation mode: constant voltage, current, resistance
- Transient Gen. Frequency 1Hz-1kHz, duty 10-90%
- High Resolution: 20mV, 0.2mA, 0.3m Ω
- Self-Test and Software Calibration
- Meet UL CSA IEC Safety regulation

*** NEW * \$1409.95**

ALFA ELECTRONICS P.O. BOX 8089 PRINCETON, NJ 08543

TEL: (800)526-ALFA(2532) / (609)897-1135

FAX: 609-897-0206

Email: alfa0168@aol.com

Call/Write/Fax/Email for **FREE CATALOG**

Visa, MC, AMEX, COD, PO Accepted. OEM Welcome.

1 Year Warranty (2 Years for Instek)

May 1998, Popular Electronics

USE POPULAR ELECTRONICS

READ BY BUYERS OF ELECTRONIC EQUIPMENT ACCESSORIES AND PARTS

INSTRUCTIONS FOR PLACING YOUR AD!

HOW TO WRITE YOUR AD

TYPE or PRINT your classified ad copy **CLEARLY** (not in all capitals) using the form below. If you wish to place more than one ad, use a separate sheet for each additional one (a photo copy of this form will work as well). Place a category number in the space at the top of the order form (special categories are available). If you do not specify a category, we will place your ad under miscellaneous or whatever section we deem most appropriate.

We cannot bill for classified ads. **PAYMENT IN FULL MUST ACCOMPANY YOUR ORDER.** We do permit repeat ads or multiple ads in the same issue, but, in all cases, full payment must accompany your order.

WHAT WE DO

The first word and company name of each ad are set in bold caps at no extra charge. No special positioning, centering, dots, extra space, etc. can be accommodated.

RATES

Our classified ad rate is \$1.75 per word. Minimum charge is \$26.25 per ad per insertion (15 words). Any words that you want set in bold are each .40 extra. Indicate bold words by underlining. Words normally written in all caps and accepted abbreviations are not charged anything additional. State abbreviations must be post office 2-letter abbreviations. A phone number is one word.

If you use a **Box number** you must include your permanent address and phone number for our files. **ADS SUBMITTED WITHOUT THIS INFORMATION WILL NOT BE ACCEPTED.**

For firms or individuals offering Commercial products or Services. **Minimum 15 Words.** 5% discount for same ad in 6 issues within one year; 10% discount for same ad in 12 issues. **Sorry, no discounts on credit-card orders.** **Boldface** (not available as all caps), add .40 per word additional. **Entire ad in boldface**, add 20%. **Tint screen behind entire ad**, add 25%. **Tint screen plus all boldface ad**, add 45%. **Expanded type ad**, add \$2.25 per word.

General Information: A copy of your ad must be in our hands by the 13th of the fourth month preceding the date of issue (i.e. Sept issue copy must be received by May 13th). When normal closing date falls on Saturday, Sunday or Holiday, issue closes on preceding work day. Send for the classified brochure.

DEADLINES

Ads not received by our closing date will run in the next issue. For example, ads received by November 13 will appear in the March issue that is on sale January 17. **POPULAR ELECTRONICS** is published monthly. No cancellations permitted after the closing date. No copy changes can be made after we have typeset your ad. **NO REFUNDS**, advertising credit only. No phone orders.

CONTENT

All classified advertising in **POPULAR ELECTRONICS** is limited to electronics items only. All ads are subject to the publishers approval. **WE RESERVE THE RIGHT TO REJECT OR EDIT ALL ADS.**

AD RATES: \$1.75 per word Minimum \$26.25

Send you ad payments to:

POPULAR ELECTRONICS 500 Bi-County Blvd, Farmingdale, NY 11735-3931

CATEGORIES

100 - Antique Electronics	270 - Computer Equipment Wanted	450 - Ham Gear Wanted	630 - Repairs-Services
130 - Audio-Video Lasers	300 - Computer Hardware	480 - Miscellaneous Electronics For Sale	660 - Satellite Equipment
160 - Business Opportunities	330 - Computer Software	510 - Miscellaneous Electronics Wanted	690 - Security
190 - Cable TV	360 - Education	540 - Music & Accessories	710 - Telephone
210 - CB-Scanners	390 - FAX	570 - Plans-Kits-Schematics	720 - Test Equipment

CLASSIFIED AD COPY ORDER FORM

Place this ad in Category # _____ Special Category \$20.00 Additional _____

1 - \$26.25	2 - \$26.25	3 - \$26.25	4 - \$26.25	29 - \$50.75	30 - \$52.50	31 - \$54.25	32 - \$56.00
5 - \$26.25	6 - \$26.25	7 - \$26.25	8 - \$26.25	33 - \$57.75	34 - \$59.50	35 - \$61.25	36 - \$63.00
9 - \$26.25	10 - \$26.25	11 - \$26.25	12 - \$26.25	37 - \$64.75	38 - \$66.50	39 - \$68.25	40 - \$70.00
13 - \$26.25	14 - \$26.25	15 - \$26.25	16 - \$28.00	Total words _____ \$1.75 per word = \$ _____			
17 - \$29.75	18 - \$31.50	19 - \$33.25	20 - \$35.00	Bold Face _____ \$0.40 per word = \$ _____			
21 - \$36.75	22 - \$38.50	23 - \$40.25	24 - \$42.00	Special Heading _____ \$20.00 = \$ _____			
25 - \$43.75	26 - \$45.50	27 - \$47.25	28 - \$49.00	Other _____ = \$ _____			

Total classified ad payment \$ _____ enclosed **TOTAL COST OF AD \$ _____**

Check Mastercard Visa Discover Card # _____ Expiration Date ___/___

Signature _____

Name _____ Phone _____

Address _____ City State Zip _____

PARTS EXPRESS

ELECTRONICS & MORE


**FREE
244 PAGE
CATALOG**



**UNBELIEVABLE
VALUE!**

4 Way Speaker Switch

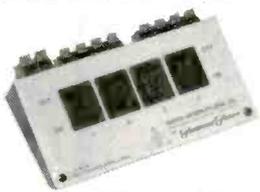Control up to 4 pairs of speakers with this compact speaker selector switch. Features circuit protector, heavy duty rocker switches, spring loaded terminals, and silver plated switch connectors. Includes one pair of amplifier inputs. Load to amplifier is minimum 4 ohms (with 8 ohm speakers) or 220 ohms with all speakers switched off. Net weight: 1 lb.



WAS \$22⁵⁰ EACH NOW \$15⁰⁰ EACH

#PO-309-030

Peak Instrument Co.

"The Woofer Tester"

Peak Instrument Co. proudly introduces "The Woofer Tester". Just ask any loudspeaker engineer, and they will tell that the only way to design enclosures of the correct size and tuning is to measure the Thiele-Small parameters for the actual drivers to be used. The reason? Manufacturers published specs can be off by as much as 50%! But until now, measuring the parameters yourself required expensive test equipment and tedious calculations, or super expensive measurement systems (\$1,200 to \$20,000). The Woofer Tester changes all that. Finally, a cost effective, yet extremely accurate way to derive Thiele-Small parameters, in only minutes! The Woofer Tester is a combination hardware and software system that will run on any IBM compatible computer that has EGA or better graphics capability and an RS232 serial port. The Woofer Tester will generate the following parameters. Raw driver data: Fs, Qms, Qes, Qrs, Vas, BL, Re, Le, SPL @ 1W/1m, Mmd, Cm, and Rm. Sealed box data: Fsb and system Q. Vented box data: Fsb, ha, alpha, and Q loss. The Woofer Tester system includes hardware, test leads, serial cable, AC wall adaptor, detailed instructions, and software.



QUICKLY AND ACCURATELY MEASURES:
Fs, Qms, Qes, Qrs, Vas, BL, Re, Le, SPL @ 1W/1m, Mmd, Cm, and Rm IN MINUTES!

30 DAY MONEY BACK GUARANTEE

1 YEAR WARRANTY SAME DAY SHIPPING

#PO-390-800 \$249⁰⁰ EACH

"The Sound Bridge" FM Stereo Wireless Transmitter

The Sound Bridge is a mini FM wireless transmitter that can be used to broadcast stereo sound from any audio source like portable CD players, TVs, electronic games, CD-ROM, even computer soundcards, to your home stereo receiver! Adjustable from 89 to 95.5 MHz.



**HOT
NEW
ITEM!**

\$14⁹⁵ EACH

#PO-249-220

Weller Professional Irons

Weller

Perfect for a variety of electronic soldering work, this top quality iron features a long life, double coated tip and a quick change, plug-in heater element. Lightweight handle includes a comfortable cushioned grip. Net weight: 1/2 lb.

#PO-372-110 (25 Watt) \$30⁰⁰ (1-3) \$28⁵⁰ (4-UP)

#PO-372-112 (35 Watt) \$38⁰⁰ (1-3) \$34⁹⁵ (4-UP)

900 MHz. Wireless Speaker System

- ◆ 900 MHz technology sends signal up to 180 ft., through walls, floors and ceilings.
- ◆ Ideal for use as rear surround speakers or for adding wireless sound to every room in the house!
- ◆ Full range, bass reflex design with built-in high power, low distortion amplifier.
- ◆ Weather resistant cabinet for outdoor use.
- ◆ Selectable battery (six C size for each speaker) or AC operation, adaptor included. Built-in recharging circuitry for ni-cad batteries.
- ◆ System includes: 900 MHz transmitter, wireless speaker pair, AC adaptors, and all cables necessary to hook up system.
- ◆ Limited availability. ◆ Net weight 9 lbs.
- ◆ Frequency response: 20-18KHz.



#PO-319-030 \$169⁹⁵ EACH

Home Theatre In-Floor Subwoofer

To fully appreciate the potential of movie soundtracks, a dual voice coil subwoofer is a must! Many film special effects are extremely demanding in the low frequency range and require a subwoofer that can duplicate explosions, earthquakes, even the footsteps of Tyrannosaurus Rex! This subwoofer fits the bill by featuring a 10" dual voice coil woofer for true stereo operation and high pass filters for your main speakers. The most unique feature of this subwoofer is the fact that it is designed to be mounted in between the floor joists in new and existing home constructions. Simply mount the in-floor sub to the joists and mount a heat register grill above opening in subwoofer front enclosure. The subwoofer is now totally out of view and ready to rumble! Includes detailed installation manual.



Specifications: 10" dual voice coil treated paper cone woofer with poly foam surround ◆ Frequency response: 30-100 Hz ◆ Nominal impedance: 8 ohms per coil ◆ Power handling: 100 watts RMS channel/140 watts max ◆ SPL: 89 dB 1W/1m ◆ Dimensions: 27" D x 14-5/8" W x 9" H ◆ Net weight: 29 lbs.

#PO-300-445 \$139⁹⁵ EACH

Dayton Loudspeaker Co.®



◆ 30 day money back guarantee ◆ \$20.00 minimum order
◆ We accept Mastercard, Visa, Discover, and company C.O.D. orders ◆ 24 hour shipping ◆ Shipping charge = UPS chart rate + \$1.90 (\$5.00 minimum charge) ◆ Hours 8:00 am - 8:00 pm ET, Monday - Friday ◆ 9:00 am - 5:00 pm Saturday. Mail order customers, please call for shipping estimate on orders exceeding 5 lbs. ◆ Foreign destination customers please send \$5.00 U.S. funds for catalog. ◆ Quantity pricing available.

1-800-338-0531

340 E. First St., Dayton, OH 45402-1257
Phone: 937-222-0173 ◆ Fax: 937-222-4644
E-Mail: sales@parts-express.com

CIRCLE 146 ON FREE INFORMATION CARD

CABLE TV CHANNELS

EQUIPMENT *Direct!* **GUARANTEED**

FREE 30 DAY TRIAL

SAVE \$1000's

The Nationwide source for cable TV equipment.

"BUY WHERE THE DEALERS BUY."

TV Cable Descramblers, Converters and Magic Box Catalog. Open Every Day!

FREE

YOUR VCR TAPES CAN PLAY AS CLEAR AS DAY!

Eliminates copy protection on any tape

UNJAM NOW WITH Video Decoder

• Copy any rental/bought tape
• Power Cord and RC Plugs included

2 Year Warranty

CALL NOW!

Member Better Business Bureau

MEGA ELECTRONICS

1-800-676-6342

VISA • MC • COD

FREE 30 Day Trial!

Expandable 8051 SBC, Multi-Tasking PC WatchDog, PC & Printer Port Data Acq...

Remotely Downloadable, Expandable SBC starts at \$99. Stack on cards expand SBC to fit your needs. Use our I/O cards, our proto board or design your own cards. Projects up in no time!

- Atmel's 89C5X, 11.059MHz, 4.75" x 3.15"
- Load program via RS232 then run, its that simple!
- RS232 & RS485. Has 5 External Interrupts
- Cards: A/D, D/A, D/I/O, LCD/Keypad, Counter.
- FREE Assembler, Disassem, Simulator, Basic, C.

We also have...

- ◆ **UNIQUE PC WATCHDOG..** monitors up to 4 programs, resets PC if any one fails. Only \$80.
- ◆ 8 chan A/D, 24 D/I/O, counter for a PC \$65.
- ◆ **PRINTER PORT**, 8 channel 8 bit A/D, 8 TTL D/I, 8 D/O @ 35mA. \$87

Innovation West (626) 309-6085
Fax: 309-9972 inowest@aol.com
<http://members.aol.com/inowest/>

VIDEO INVERTER
Create & Restore Inverted Video

R.C. Distributing
PO Box 552 • South Bend, IN 46624
Website: www.south-bend.net/rcd

For Free Information Package on Completed Units and Pricing
Call 219-236-5776

Smithy / 3-in-1 Lathe•Mill•Drill

Benchtop machine shop

- Make your own parts and repairs
- Easy to use, free training
- Work metal, wood, or plastic

4 models starting at **\$995**

FREE Info Dept. PE, PO Box 1517
Ann Arbor, MI 48106-1517
Call 1-800-345-6342

Do You Repair Electronics?

Repair Databases for TV, VCR, Monitor, UL Audio, FCC, and more.	- Over 76,000 records - Private user forums - Live on-line chat rooms
---	---

RepairWorld.com
Electronics Corp. 1 Herald Sq. Fairborn, OH 45324 (937) 878-9878

PCB TONER TRANSFER PAPER

PRINT-IRON-PEEL-ETCH
No need to soak off transfer!

Brand new paper - based transfers with advanced coating for use with laser printers or photocopiers.

RT SIMPLE, QUICK & INEXPENSIVE!
\$7.95 US / 10 Sheets

ROSS TECHNOLOGIES - BOX 26021 WINDSOR, ONT. CANADA N9A-7E9
Soak your laundry ... not your printed circuit boards!

ATTENTION CABLE VIEWERS

CABLE VIEWERS... get back to your BASIC Cable Needs

Call 800-577-8775

For information regarding all of your BASIC cable needs.

5 GOOD REASONS TO BUY OUR FAR SUPERIOR PRODUCT

- ❖ PRICE
- ❖ EFFICIENT SALES AND SERVICE
- ❖ WE SPECIALIZE IN 5, 10 LOT PRICING
- ❖ ALL FUNCTIONS (COMPATIBLE WITH ALL MAJOR BRANDS)
- ❖ **ANY SIZE ORDER FILLED WITH SAME DAY SHIPPING**

We handle NEW equipment ONLY - Don't trust last year's OBSOLETE and UNSOLD stock!
COMPETITIVE PRICING—DEALERS WELCOME

HOURS: Monday-Saturday 9-5 C.S.T.

It is not the intent of B.E.S.W. to defraud any pay television operator and we will not assist any company or individual in doing the same.
*Refer to sales personnel for specifications.

BASIC ELECTRICAL SUPPLY & WAREHOUSING CORPORATION

P.O. Box 8180 ■ Bartlett, IL 60103 ■ 800-577-8775

SEC Sun Equipment Corporation

P. O. Box 97903, Raleigh, NC 27624 E-mail: sunequipco@ipass.net
To request FREE CATALOG, please call, fax, write, or e-mail us.

Quality Test Equipment for Cost-Minded People

LODESTAR Lodestar Electronics Corp. Since 1979

One Year Warranty. 15 Day Money Back Guarantee. OEM WELCOME.

School purchase order accepted. Bids accepted.

SALES REP/DISTRIBUTORS/OEM WANTED.

1-800-870-1955 / (919)870-1955 Fax: (919)870-5720

VISA Mastercard

Discover, AmrExp

DC POWER SUPPLY (CC/CV)

All models: protection of short ckt, overload, reverse polarity, over-voltage; Constant Current & Voltage (CC/CV) are fully adjustable. Regulation: $\pm 0.1\% + 3mV$ (line); $\pm 0.1\% + 3mV$ (load); $\pm 1mV$ ripple.

SINGLE OUTPUT

Analog Displays

- PS-303 \$159.00, 30V/3A
- PS-305 \$219.95, 30V/5A
- PS-1610S \$289.00, 16V/10A
- PS-2243 \$139.00, 12V/24V select, 3A
- PS-2245 \$159.00, 12V/24V select, 5A
- 8107 \$399.95, 30V/10A
- 8110 \$289.95, 60V/3A
- 8112 \$399.95, 60V/5A

Digital Voltmeter & Analog Ammeter

- 8200(8201) \$179.95 (\$239.95), 30V/3A(5A)
- Digital Displays 8210/8300 \$199.95, 30V/3A
- 8211/8301 \$259.95, 30V/5A

DUAL OUTPUTS

Independent/Tracking

Analog Displays

- 8108 \$549.95, 60V/3A
- 8109 \$699.95, 60V/5A

PS-303D \$314.95, 30V/3A

TRIPLE OUTPUTS, a fixed 5V/3A output, Independent/Tracking

- Digital Displays 8202(8203) \$499.95(\$549.95), dual 30V/3A(5A)
- Analog Displays 8102(8103) \$399.95(\$489.95), dual 30V/3A(5A), with Parallel (30V/6A) and Series (60V/3A) Mode operation

NTSC/PAL TV COLOR BAR GEN.

CPG-1366A \$159.95, VHF NTSC;

Freq.: 45.75, 175.25, 187.25 MHz;

RF Output: 10mV.

Impedance: 75 Ohm;

Video Output: BNC, 1V_{p-p}

CPG-1367A \$159.95, VHF PAL.

SWR/RF/mW POWER METER

310 \$89.95, 1.8-150MHz, RF Power

0.4W/20W/200W 3 ranges; SWR

Measurement: 1.0-∞, 4W minimum.

Accuracy: 5%-10%; Insert Loss: 3dB

Input/Output Imp.: 50Ω; SO-239 plug

320 \$89.95, 130-520MHz. Spec. 310.

330 \$119.95, 1.8-520MHz. Spec. see 310.

SWR-3P \$26.95 1.7-150MHz;

RF Power: 0.5-10W, 0.5W-100W.

SWR-2P \$22.95, 1.7-30MHz; RF Power: 0.5-10W.

mW RF Power Meter 340 \$219.00, 1.8-500MHz, RF

Power: 20mW/200mW/2W 3 ranges; Imped.: 50Ω; Accuracy:

$\pm 10\%$ full scale. SWR < 1.15 . N-type connector. BNC type output.

FM STEREO MODULATOR

AG-2011A \$549.00

RF SECTION:

Carrier: 98MHz ± 2 MHz;

Output: 10mV, 1mV & 0.1mV

COMPOSITE SIGNALS:

Pilot: 19KHz ± 2 Hz, 0.8Vrms

INT. MODULATION: 400KHz,

1KHz $\pm 1\%$, 1Vrms, distortion $< 5\%$; L-R Separation: > 50 dB

EXT. MODULATION: Freq.: 50Hz-15KHz

L-R Separation: > 45 dB 100Hz-3KHz; > 35 dB 50Hz-15KHz.

TOOLKITS - ELECTRONIC/PC

9245 \$29.99 U.S. Patented, 45-pos. Contents: IC inserter/extractor with securers & bows, 3-prong part retriever, #0 phillips screwdriver, 1/8" flat screwdriver, self-hold tweezers, metal tweezers, extra parts tube, soldering iron, solder, crimping tool, long-nose plier, cutting plier, zipper vinyl case. Bits include: Phillips #0/#1/#2/#3; Flat: 1/8"/3/16"/1/4"/9/32"; PZ1/PZ2; T8/T9/T10/T15/T20/T25/T27/T30/T40/T45; Hex: 5/64"/3/32"/1/8"/5/32"/3/16"; Sockets: 3/16" (5mm)/7/32" (5.5mm)/1/4" (6mm)/9/32" (7mm)/5/16" (8mm). 8G23 \$34.99 23-pos Contents: IC inserter/extractor with securer & bows, 3-prong part retriever, 3/16"/1/4" nutdriver, 3/16"/1/8" slotted screwdriver, #0/#1 phillips, reversible T10/T15 bits, re-reversible #2 phillips/1/4" slotted bits, tweezers, long-nose plier, cutter, 6" adj. wrench, soldering iron, solder, crimping tool, zipper case, manual. Different packages available, call/write/e-mail/fax for detail.

STEREO/ALIGNMENT/SWEEMAR SCOPE

STEREO SCOPE OS-7505B \$369.00, 0-10MHz/20mV.

ALIGNMENT SCOPE OS-7001A \$369.00, 0-200KHz/1mV.

SWEEMAR SM-6225B/C \$1999.95

Freq Range: (AM)490KHz, (FM)10-11.4MHz, Accuracy: $\pm 0.1\%$; Marker:

(AM)455KHz, ± 5 KHz, ± 10 KHz;

(FM)10.7MHz, ± 7.5 KHz, ± 150 KHz.

RF SIGNAL GENERATOR



SG-4160B \$124.95, 100KHz-150MHz up to 450MHz on 3rd harmonics in 6 ranges; AM modulation, Accuracy: $\pm 5\%$. RF Output: 100mVrms to 35 MHz; Modulator: Int. 1KHz (AM) $\pm 30\%$, Ext. 50Hz-20KHz, at least 1V_{min} input; Audio Output: 1KHz, 2V_{min} minimum.

SG-4162AD (with Freq. Counter) \$229.95, Spec. see SG-4160B. COUNTER SECTION: 10Hz-150MHz, Max. Input: ≤ 3 V effective Gate Time: 1, 1sec. Input Sensitivity: 35mV, 10Hz-200MHz. Input Impedance: 1MΩ(HF), 50Ω(VHF). Display: 7-digit LEDs.

AM/FM STD SIGNAL GEN.

SG-4110A \$1799.00, Freq: 0.1-110MHz, Display: 6-digit LED; Resolution: 100Hz (0.1-34.999MHz); 1KHz (35MHz-110MHz). Accuracy: $< 5 \times 10^{-1} \pm 1$ count; Output: -19dBu-99dBu, 1dB steps. Impedance: 50Ω VSWR 1.2; 100 preset frequency & store functions.

AUDIO GENERATOR

AG-2601A \$124.95, 10Hz-1MHz in 5 ranges; Output: sinewave 0-8V_{max}, square 10V_{p-p}, 600 Ohm. Output Imped: 600 Ohm. Distortion: $< 0.05\%$ 500Hz-50KHz, $< 0.5\%$ 50KHz-500KHz.

AG-2603AD \$229.95, with 6-digit, Int/Ext. Freq. Counter, 10Hz-150MHz. Output Control: 0/20-40dB & Fine adjuster. Spec. see AG-2601A.

FUNCTION GENERATOR

FG-2100A \$169.95, 0.2Hz-2MHz in 7 ranges; sine, square, triangle, pulse & Ramp; Output: 5mV_{p-p}-20V_{p-p}, 1% distortion. VCF 0-10V/freq. to 1000.1. FG-2102AD \$229.95 see FG-2100A; 4-digit counter display, TTL & CMOS outputs, 30ppm ± 1 count accuracy.

FG-2020B \$159.00 0.5Hz-500KHz, Sine, Square, Triangle. FG-2103 \$229.95, Digital sweep generator, 0.5Hz-5MHz in 7 ranges. Operating Mode: sweep, AM, gated burst, VCG. Freq. Counter: Int. 0.5Hz-5MHz, Ext. 5Hz-10MHz. FG-513 \$769.95, 13 MHz, Microprocessor embedded digital sweep; Sine, Square, Triangle, Pulse, Ramp, TTL & DC; $\pm 0.1\% + 1$ digit. Freq. Counter & TCXO: 5Hz-100MHz, 6.5 digits $\times 1/2 \times 20$ attenuator.

AC MILLIVOLT METER

MV-3100A \$159.95 wide band 5Hz-1MHz; 3 scales, mV, dB & dBm; 300μV-100V in 12 ranges, 10μV resolution, -70-40dB in 12 ranges, 0dB=1Vrms, 0dBm=0.775V; $\pm 3\%$ accuracy; Input impedance 10MΩ; Noise $< 2\%$. MV-3201B \$309.95 dual channels, simultaneous measurement.

OSCILLOSCOPES

OS-7305B \$249.00 DC-7MHz, 3" CRT, Horiz: 25V/div, 10Hz-100KHz in 4 ranges; Vert: 10mV/div; Int. & Ext. Sync.; Input: 1MΩ/35pF. OS-7010A \$299.95 10MHz, 5" CRT, Horiz: 2V/div, Vert: 10mV-10V/div. OS-622G \$389.95 20MHz, 2 CH X-Y

Alt trigger, trigger lock, hold OFF, TV syn., 8x10 div., 1mV/div., Horiz: 2μs-5s/div., Vert: 1mV-5V/div. OS-653G \$699.95 50MHz, 2 CH/delay sweep, Alt trigger, TV syn. OS-6101G \$1499.95 100MHz, 4ch/8 traces, delay sweep, cursor readout. 2 years warranty for OS-622G, OS-653G, & OS-6101G.

UHF ATTENUATORS

RT-8815L (50Ω) \$299.00 / RT-8817U (75Ω) \$299.00, 950MHz, 81dB, 0.5W max; Steps: 1/2/3/5/10/20/20/20, 8 switches. 085E-2 (50Ω) \$399.00 / 087E-2 (75Ω) \$399.00, 950MHz, 81dB, 0.5W max; Steps: 10dB+7.1dBx10. Electronic adjustment knob.

MICROPROCESSOR TRAINER

BCC-8088 \$699.00, learn computer theory. Excellent for school & individual who want to learn about ROM, RAM, I/O ports, programming, & run a 8088 Microprocessor. An easy to understand step-by-step manual guides you to achieve your goal. 56-key keyboard, LCD display, RS-232, UART.

GRID DIP METER

DM-4061 \$89.95 1.5-250MHz, 6 bends; 6 plug-in coils, 2 transistor, and 1 diode. Modulation: ≈ 2 KHz Sinewave. Crystal Oscillator: 1-15MHz. Wave absorption meter. 9VDC battery.



FREQUENCY COUNTER

FC-5250C \$119.95 10Hz-220MHz (HF) 10Hz-20MHz (VHF) 10-200MHz. Gate Time: 1, 1sec. Max. Input: 10V_{p-p}. Input Sensitivity: 35mV/10Hz-200MHz. Input Imped.: 1MΩ(HF), 50Ω(VHF). Display: 7-digit LEDs, 9V adapter (\$6).

FC-5260A \$129.95

10Hz-600MHz, 7-digit LEDs

FC-5270 \$149.95

10Hz-1.2GHz, 8-digit LEDs.

FC-5600B \$229.95

10Hz-600MHz; 10-digit LEDs.

FC-5700 \$299.95 10Hz-1.3GHz, 10-digit LEDs. Period measure.

SIGNAL TRACER/INJECTOR

SE-6100 \$134.95 (9VDC adapter, \$6.0) TRACER: Gain 60dB maximum. Attenuation: 0/20/40/60dB. Input Imped.: 100KΩ; Meter: Vu 100μA. Output Imped.: 600Ω; Speaker: 8 Ω. INJECTOR: ≈ 1 KHz Squarewave; Output Level: Continuously variable 0-4.5V, 9V battery/adaptor.

LCR METERS

MIC-4070D \$179.95, Induct.: 0.1μ-200H, Capacit.: 0.1p-20mF, Resist.: 1mΩ-20MΩ, 2Ω range, Dissipation factor measurement, Zero adjust, Surface mount device (SMD) test probe: LT-06 \$21.95

DIGITAL MULTIMETER

DMM-120 \$24.95, 3 1/2 digit, 600VDC, 2ADC 500VAC, 2MΩ, hFE/diode/continuity test. DMM-123+Capacitance \$44.95, 3 1/2 digit, 600VDC/600VAC, 10ADC/AC, 2GΩ, 20μF, hFE/diode test, continuity beeper. DMM-124+Cap.+Temp.+Freq Cntr \$69.95, 3 1/2 digit, 600VDC/500VAC, -58-752°F, 2GΩ, 20mF, 200KHz, 3φ phase/diode/continuity test. DMM-125 \$54.95, Autorange/Bar Graph, 32MΩ, 600VDC/AC, 10ADC/AC, diode/continuity test. MIC-35 \$59.95, Autorange, 3 1/2 digit LCD, 1000VDC/750VAC, 20MΩ, 20ADC/AC, diode/continuity check, data hold, free holster. MIC-39 \$129.95, Autorange/Bar Graph, True RMS, 3 1/2 digit LCD, 480MΩ, 40μF, 1000VDC/750VAC, 20ADC/AC, 600KHz freq. cntr, data hold, drop-prove, sleep mode, memory, read functions, holster.

AUTO. CAPACITANCE METER

CM3300A \$139.00 10 ranges, 99.9pF - 99.9mF, fully automatic. Resolution: 0.1pF lowest, 0.1% full scale. Accuracy: 0.5% of full scale ± 1 digit to 99.9μF, 1% of full scale ± 1 digit to 99.9μF. Display: 3 digit LED. Units: pF, nF, μF, mF, Overrange indicators.

AUTO DISTORTION METER

DM-3104A \$799.95 DISTORTION MEASURE Range: 0.01% to 30%, 0.1/0.3/1/3/10/30% 6 ranges. Freq: 400Hz-10%, 1KHz-10%(HPF). Input: 3mV-100V; Ratio measure 20dB. Auto. Freq. Switching Ranges: Fundamental Freq. = (fo) $\pm 10\%$; Fund. Rejection: > 80 dB at (fo) $\pm 5\%$, > 70 dB at (fo) $\pm 10\%$; Harmonic Accuracy: ± 0.5 dB, 1.8/(fo)-20KHz. LEVEL MEASURE Range: 0 to 100V in 0.3/1/3/1/3/10/30/100V. Freq Response: ± 0.5 dB/20-50KHz, ± 1 dB/20-100KHz. DM-3204 \$1,599.00 dual channels, Spec see DM-3104A.

WOW-FLUTTER METER

WF-3103A \$699.95 Freq Range: 3KHz-10% JIS/CCIR, 3.15KHz $\pm 10\%$ DIN. Measurements: 0.3/1/3/1/3/3% full scale. Accuracy: $\pm 5\%$ of full scale. WF-3105A \$799.95, digital display; Function: LIN/WOW/Flutter/WT. Freq Counter: 10Hz-9.99MHz. Indication: CCIR/DIN/JIS.

Modern computing and standard surge suppressors...a recipe for disaster.

Almost all surge protection devices use MOV's (metal oxide varistors) as their active element. MOV's are sacrificial/wear/limited life components. Surge suppressors based on this technology are doomed to failure. These surge "suppressors" also don't suppress a thing. They divert powerline surges equally to the ground and neutral wire. When you put current on the common ground wire of interconnected equipment some of that current will flow (through the inherent ground loops) to the data lines. This is a major cause of lock-ups and misoperations that plague today's computer environments. Another fact; all modern computers use switch mode power supplies. During surges the power supply capacitors must charge to the clamping level of the MOV before the MOV turns on. A recent study has shown that it takes a 3000A surge 15 microseconds (15,000 nanoseconds) to charge the typical capacitors of these power supplies to that level. The surge is virtually over before the MOV reacts. (See *five things you probably don't know about your surge suppressor at www.fivethings.com*.)

THE POINT: Standard surge suppressors allow too much current to hit the computer. Standard surge suppressors divert surge current to the ground wire and disrupt data transfer. Standard surge suppressors eventually fail without warning. Modern computers have logic voltage levels (the signals that transmit the data) and power supply voltages that are dramatically lower than that of their recent predecessors. Modern computers use integrated circuits with transistors of ever decreasing physical geometries. Modern computers are virtually always interconnected to other computers or peripheral equipment. The bottom line; *modern computers are much more sensitive and susceptible to powerline anomalies.*

INTRODUCING BRICK WALL SURGE FILTERS. . . The World's Best Surge Suppressor

Initially engineered for critical, non-fail industrial applications, this patented device protects indefinitely and sets a new standard for every measure of surge suppressor and powerline filtering performance.

A Brick Wall 1) Utilizes NO MOV'S or Any Other Sacrificial Components (a two pound inductor and nine capacitors are the heart of the unit) 2) Has No Joule Rating or Surge Current Limitations 3) *HAS BEEN TESTED AND CERTIFIED BY UL TO THE MOST DEMANDING CLASSIFICATION OF A NEW GOVERNMENT SPECIFICATION; CLASS I, GRADE A. Which Means: UL PUT ONE THOUSAND 3000A, 6000V SURGES (this is the largest surge an interior environment can experience) THROUGH A UNIT (at 60 second intervals) AND DOCUMENTED NO FAILURE OR PERFORMANCE DEGRADATION OF ANY KIND WHATSOEVER.*

i.e.: A Brick Wall Will Not Fail.

We know of no cord connected, MOV based surge protection device that has, or can pass this test.

A Brick Wall possesses UL's lowest Suppressed Voltage Rating (let-through voltage) of 330V. This is the lowest rating they will grant. In that test of one thousand 6000V, 3000A surges, *UL NEVER SAW THE LET-THROUGH VOLTAGE EXCEED 290V. YOU CANNOT DO BETTER THAN THIS FOR A POINT-OF-USE SURGE PROTECTION DEVICE.* Once again, we know of no other surge protection device that could come close to this performance level.

A Brick Wall is a current activated *Series Mode* device. *Since it is not wired in parallel, nor voltage activated, it does not have to wait for the capacitors of the power supply to charge before it becomes effective. YOUR EQUIPMENT IS PROTECTED INSTANTANEOUSLY (and indefinitely).*

These devices were engineered utilizing a current limiting/surge filtering technology. *THEY DO NOT DIVERT ANY SURGE CURRENT TO THE GROUND WIRE. They Will Not Cause Your Computer System To LOCK-UP, CRASH OR MISOPERATE as a consequence of surge diversion. Your current surge "suppressor" will.*

Powerline Filtering

In addition to all this, Brick Wall Surge **FILTERS** are the best AC powerline filters you can buy (that we have been able to find anyway). Industrial machinery, copiers, coffee makers, laser printers, fluorescent lights, refrigerators, etc., all cause powerline noise that can cause your computer to misoperate. A Brick Wall Surge Filter will make powerline noise related problems disappear.

You Can't Buy a Better Surge Protection/Powerline Filtering Device...Anywhere.




**BRICK WALL DIV.,
PRICE WHEELER CORP.
1-800-528-0313**

Fax: 1-800-528-6623 E-Mail: info@brickwall.com

Web: www.brickwall.com

Visa - MC - AMEX

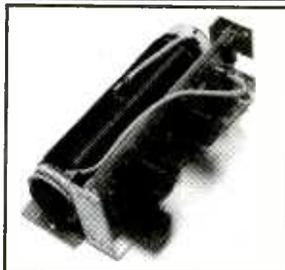

Available in Modular Form

ASK ABOUT OUR NEW IN-LINE UPS/SERVER PROTECTOR



If he weren't constantly hungry
he might never be called
"Shrimp."

Over 12 million children in America
are suffering from hunger.
Hunger that is stunting their growth.
We can help them grow.
Simply by feeding them.
Call Second Harvest,
America's food bank network,
at 1-800-532-2673.



**SECOND
HARVEST**
TOGETHER WE
HUNGER'S HUNGER

www.secondharvest.org

Buy recycled.




It would mean
the world to them.

Recycling keeps working to protect
their future when you buy products
made from recycled materials. For
a free brochure, write *Buy Recycled*,
Environmental Defense Fund, 257
Park Avenue South, New York, NY
10010, or call 1-800-CALL-EDF.



Xcelite Wheeled Tool Case!!!

- Super tough, black polyethylene rotationally molded for maximum strength.
- 53 individual hand tools, 31 Series 99 interchangeable screwdriver/nutdriver blades and handles, and two specialized screwdriver/nutdriver kits.
- Extra large (3-5/8") roller bearing wheels with wide base for maximum stability and easy transport over rough pavement or stairs.
- Extra wide, comfortable extension handle is molded into case to prevent wear.
- Dimensions: 18" x 15" x 8" deep.
- Extension handle locks into place automatically when extended and retracted. Easy one-handed release.
- Two spring loaded tote handles for convenience.
- "D" ring provided for Bunji cords to carry other cases on top.
- 3-panel hinged tool pallet in lid plus additional pallet in bottom.
- Extra large all new screen mesh literature/utility pocket.
- Extra large storage space for additional equipment.

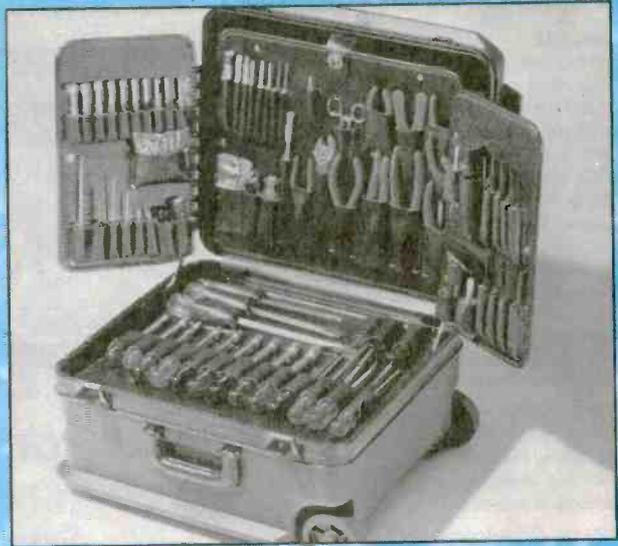

Xcelite

MODEL TCMB-100/STW
Suggested Price \$1109.80
SUPER SPECIAL \$ 695.00!!!



Products International

8931 Brookville Rd * Silver Spring, MD, 20910 * 800-638-2020 * Fx 800-545-0058
Email: SMPRODINTL@aol.com

CIRCLE 46 ON FREE INFORMATION CARD

The Pocket Programmer

\$129.95



The portable programmer that uses the printer port of your PC instead of an internal card.

Easy to use software that programs E(E)prom, Flash & Dallas Ram. 27(C)/28(C)(F)/29(C)(F)/25 series from 16K to 8 Megabit with a 32 pin socket. Adapters available for MCU's 874X, 875X, Pic, 40-Pin X 16 & Serial Eprom's, PLCC, 5-Gang and Eprom Emulator to 32K X 8.

Same Name, Address & Phone # for 13 Years.... Isn't it Amazing ?

Intronics, Inc.

Box 13723 / 612 Newton St.
Edwardsville, KS 66113 Add \$4.75 COD
Tel. (913) 422-2094 Add \$4.00 Shipping
Fax (913) 441-1623 Visa / Master Charge

BEST DEALER PRICING!

CABLE DIRECT

CONVERTERS • FILTERS
DESCRAMBLERS

IMPROVE YOUR IMAGE WITH
VIDEO STABILIZERS

**FREE
CABLE TV
CATALOG!**

**00%
MONEY BACK
GUARANTEE!**



Now you can tune-in your favorite cable TV programming and **SAVE \$100'S - EVEN \$1000'S** on premium CABLE TV EQUIPMENT.



MODERN ELECTRONICS

1-800-906-6664

2609 S. 156TH CIRCLE • OMAHA, NE 68130
<http://www.modernelectronics.com>



The world's largest electronic surplus company • Liquidators • Overstocks • Hobby Stores • "Unique" and hard-to-find parts • Large quantities • Liquidations • Electronics • Hobby items • Hardware • Overstocks • Unique and hard-to-find parts • Large quantities • Hobby items • Save! Save! Save! Save!

If you are not getting this catalog you are missing out on some of the best deals in

electronics today! We have thousands of items ranging from unique, hard-to-find parts to standard production components. Call, write, or fax today to start your free subscription to the most unique catalog in the industry, filled with super values on surplus electronic and hobbyist type items. If you have a friend who would like to receive our catalog, send us their name and address and we will gladly forward them a complementary 100 page catalog.

Why pay more? Call today.



340 East First Street Fax Order Line
Dayton, Ohio 45402 1-800-344-6324

Order Toll-Free
1-800-344-4465

CIRCLE 151 ON FREE INFORMATION CARD

VIDEO SYNC GENERATOR



Restores Horizontal and Vertical Sync Lines from Distorted Video



Lost Sync



Restored Sync with VSG

For Free Information Package, and Pricing

Call 219-236-5776
www.south-bend.net/rcd

R.C. Distributing, PO Box 552, South Bend, IN 46624

Turn Your Multimedia PC into a Powerful Real-Time Audio Spectrum Analyzer

Features


- 20 kHz real-time bandwidth
- Fast 32 bit executable
- Dual channel analysis
- High Resolution FFT
- Octave Analysis
- THD, THD+N, SNR measurements
- Signal Generation
- Digital Filtering
- Triggering, Decimation
- Transfer Functions, Coherence
- Dynamic Data Exchange (DDE)
- Time Series, Spectrum Phase, Spectrogram and 3-D Surface plots
- Real-Time Recording and Post-Processing modes

Applications

- Distortion Analysis
- Frequency Response Testing
- Vibration Measurements
- Acoustic Research

System Requirements

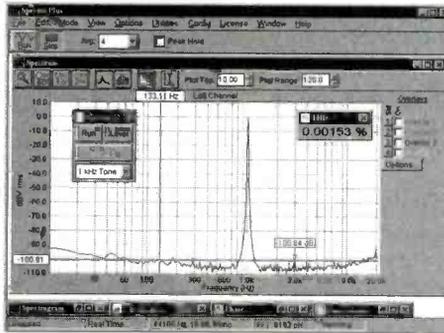- 486 CPU or greater
- 8 MB RAM minimum
- Win. 95, NT, or Win. 3.1 + Win.32s
- Mouse and Math coprocessor
- 16 bit sound card



Priced from \$299

(U.S. sales only – not for export/resale)

Professional Quality Sound Cards Available...Call

DOWNLOAD FREE 30 DAY TRIAL!

www.telebyte.com/pioneer

PHS

Pioneer Hill Software
24460 Mason Rd. N.W.
Poulsbo, WA 98370

Spectra Plus 4.0
Affordable Signal Processing Software

Sales: (360) 697-3472

Fax: (360) 697-7717

e-mail: pioneer@telebyte.com

Introducing Eagan Technical Services, Inc.

Surface Mount Rework System

The Eagan Technical Services SMT Rework System and Procedures were developed to meet the needs of several high volume computer repair facilities and provide an efficient and economical method for removal and installation of Surface Mount devices. The system includes all tools, supplies, and materials required to perform nondestructive removal and installation of most package/types of surface mount components.

Just \$249.95!



- SMT Reflow Gun
- Reduction Nozzle
- Set of 3 Probes
- Set of 2 Tweezers
- Cleaning Sponge
- Illuminated Magnifier
- Water-Soluble Flux
- Organic Core Solder
- Flux Applicator
- Tool/Parts Box
- Instructional Video
- Practice PC Board
- Instruction Booklet



Eagan Technical Services, Inc.
1408 Northland Drive, Suite #304
Mendota Heights, MN 55120

Phone: 612.688.0098 Fax: 612.688.7829

Toll Free: 800.285.1873 Internet Address: www.eagantech.com

<http://www.xtronics.com/kits.htm>

Join the exciting and profitable world of factory automation via PLCs. First, buy the *PLC Primer*, a great intro to PLCs & ladder logic programming. It ships with student PLC software and a PLC manual for \$37.94. Next, get our PLC starter kit. It comes with an 8(+2 Pot) 8 out Toshiba PLC, cable, software (Win95 & 3.1 w/o support) for \$295.00!!

Electronic Kits!
See these and more on our WEB site!



Crystal radio	\$5.75	Glitter-Globe Buckminster Fuller	
Function Gen w/FM	\$28.00	sphere 64 LEDs EN12/92	\$45.00
Function Generator	\$14.95	Deluxe IC Radio	\$11.95
Pulse Generator	\$28.00	World Radio	\$25.95
RF Sig Generator	\$28.00	Train Sound Module	\$3.80
FM Microphone	\$6.95	IR Receiver or Xmitter	\$3.90
Ultrasonic Translator - Hear		Assembled Metal	
ultrasonic-sound	\$18.50	Detectors from	\$18.50!!

Transtronics

Free catalog

ph 785 841 3089
FAX 785 841 0434

3209 W. 9th Street
Lawrence, KS 66049
Minimum Order \$20.00 +
Shipping - up to 4 lb \$5.00
We ship over seas!

**WHOLESALE PRICES
STARTING AS LOW AS \$99.00**

**CABLE TV
DESCRAMBLERS
CONVERTERS
FILTERS · VIDEO STABILIZERS**



1 Year Warranty on All Products.
Affordable Extended Warranty.
FREE CATALOG!

30 Day
FREE
TRIAL

Call the Cable Professionals 24 Hours A Day!

**Orion
Electronics**

1-800-379-3976

[HTTP://WWW.ORION-ELECTRONICS.COM](http://WWW.ORION-ELECTRONICS.COM)

SURVEILLANCE


**The Latest High Tech
Professional Electronic Devices**

Our latest catalog offers a HUGE selection of surveillance, counter-surveillance/privacy devices: hidden video equipment, pinhole cameras \$149⁰⁰, telephone recording systems: 12-Hour \$139⁰⁰ 16-Hour \$199⁰⁰ touch tone decoders, scanners, bug/phone tap detectors, voice disguisers, telephone scramblers, locksmithing tools, and more.

Catalog \$5.00

SPY OUTLET

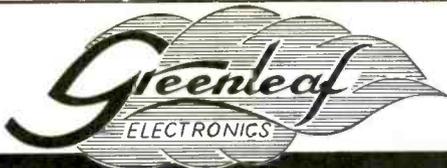P.O. Box 337, Buffalo, NY 14226
(716) 695-8660/(716) 691-3476



CABLE TV Converters & Descramblers

Compatible with
**Jerrold, Scientific Atlanta,
Pioneer, Oak, & Hamlin
Equipment**

BRAND NEW!

6-MONTH GUARANTEE

LOWEST PRICES

Volume Control & Parental Lockout Available

Greenleaf Electronics

1-800-742-2567

NO ILLINOIS SALES

It is not the intent of Greenleaf Electronics to defraud any pay television operator and we will not assist any company or individual in doing the same.

The World's Largest Source for Home Automation

- The Best & Most Comprehensive Home Automation Catalog in the Industry.
- Best Customer Service & Technical Support

FREE
144 page full
color catalog!

Thousands of hard-to-find automation, X-10 and wireless control products. Computer interfaces, software, development tools, lighting control, telephone systems, security systems, surveillance cameras, infrared audio/video control, home theater, touchscreen control, HVAC, pet care automation, wiring supplies, books and videos and much more!

World's Largest Selection!

Lowest Prices Guaranteed!

HOME AUTOMATION SYSTEMS, Inc.

Questions: 714-708-0610 Fax: 714-708-0614

e-mail: catalog@smarthome.com

www.smarthome.com

Call for a **FREE** Catalog! 800-762-7846

800-SMART-HOME

Dealers/Resellers ask about our
HASPRO Dealer Program 800-949-6255

Help protect our nation's soil and water.
Call for your free action packet.

1-800-THE-SOIL
WE OWE IT TO OUR CHILDREN

United States Department of Agriculture
Soil Conservation Service


CONTROL RELAYS • LIGHTS • MOTORS MEASURE TEMPERATURE • PRESSURE • LIGHT LEVELS • HUMIDITY INPUT SWITCH POSITIONS • THERMOSTATS • LIQUID LEVELS

MODEL 30 \$79



- PLUGS INTO PC BUS
- 24 LINES DIGITAL I/O
- 8 CHANNEL, 8 BIT A/D IN
- 12 BIT COUNTER
- UP TO 14K SMP/SEC

MODEL 45 \$189*

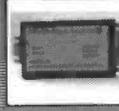

- RS-232 INTERFACE
- 8 DIGITAL I/O
- 8 ANALOG INPUTS
- 2 ANALOG OUTPUTS
- 2 COUNTERS-24 BIT

MODEL 100 \$279



- 12 BIT 100 KHZ A/D
- 4 ANALOG OUTPUTS
- 3 TIMES COUNTERS
- 24 DIGITAL I/O

MODEL 150-02 \$179



- RS-232 INTERFACE
- TRMS, 25 AMPS
- 12 BIT I/O
- OPTO-ISOLATED
- COMPLETE DMM

MODEL 40 \$99



- RS-232 INTERFACE
- 28 LINES DIGITAL I/O
- 8 ANALOG INPUTS
- PWM OUTPUT

MODEL 70 \$239



- RS-232 INTERFACE
- 18 BIT A/D
- 9.5 D16T
- UP TO 50 SMP/SEC

Prairie Digital, Inc.

PHONE 608-643-8595 • FAX 608-643-6754

846 SEVENTEENTH STREET • PRAIRIE DU SAC, WISCONSIN 53578

CIRCLE 45 ON FREE INFORMATION CARD

WIN LOTTO!

**GAIL HOWARD'S
SMART LUCK® SOFTWARE LOTTERY SYSTEMS**

**Won 59 Lotto Jackpots
Worth 97.4 Million Dollars!**
The ONLY Systems with *documented* JACKPOT WINNERS!

LOTTO HOW TO WHEEL A FORTUNE

This 397 page book contains the world's most successful lottery wheeling systems including ALL the systems used by Gail's biggest jackpot winners. Has 162 systems with specific win guarantees. Easy to use as A-B-C. \$24.00 (\$19.50 + \$4.50 S/H)

LOTTERY MASTER GUIDE

The most comprehensive book on lottery strategy ever written. A virtual library of indispensable lottery information - everything serious players need to know to win pick-5 and pick-6 Lottos. Identifies the winning patterns that produce winning numbers and tells how to spot the Hot Numbers of tomorrow...TODAY!! \$29.00 (\$24.50 + \$4.50 S/H)

ADVANTAGE PLUS™

Complete drawing results for all 64 pick 5, 6 and 7 Lotto games FREE • Over 50 scientific charts / reports to zero in on the winners • Automatic SMART PICKS selects best Lotto #'s instantly • Test past accuracy with one key stroke • Detailed 88 page manual shows how to identify winning patterns • Use Advantage Plus and you'll trash all of your other lottery software • A \$295.00 value. Your introductory price for a limited time only: \$79.50 + \$3.00 S/H.

COMPUTER WHEEL™

Easy to use scientific systems that reduce the odds • Has 252 Lotto Wheeling Systems with specific win guarantees • Wheels up to 40 of your Lotto numbers • Optimizing feature makes best possible sums of your chosen numbers • Tell how many times each number position is in the wheel • Saves up to 500 wheels for win checking • All flawless • Find one system that fails its win guarantee and you'll get DOUBLE your money back! \$39.50 + \$3.00 S/H

ADVANTAGE PLUS™ and COMPUTER WHEEL™

Save \$20! Buy BOTH for only \$99.95 + \$3.00 S/H 3.5" IBM/Comp unless you request 5.5".




1-800-945-4245
SMART LUCK® SOFTWARE



Dept RE-1, P.O. Box 1519 • White Plains, NY 10602-1519
FAX: 904-426-8705

Visit Our Web Site at: www.smartluck.com

A WHOLE NEW WORLD IN SCIENCE KITS.

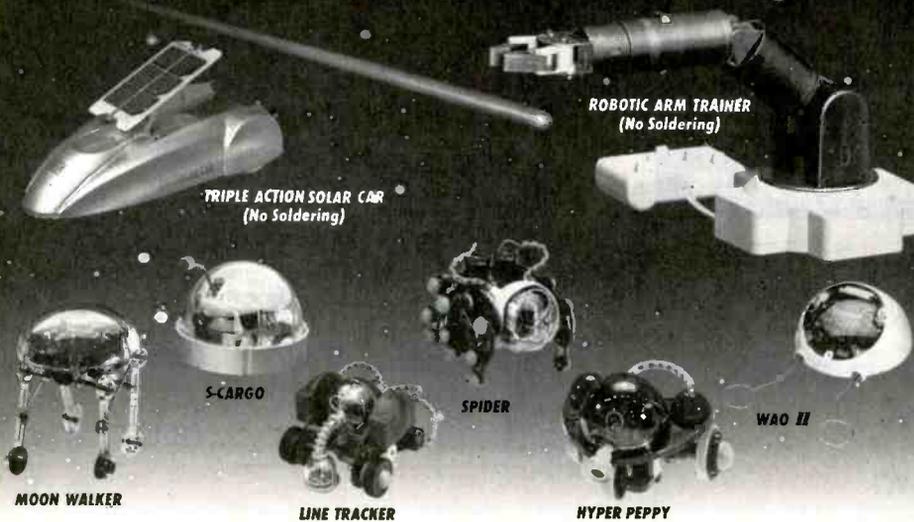

OWI's "Next Generation" of affordable, rugged Robot Kits challenge the enthusiast to solder circuit boards and/or mechanically assemble.

Each OWIKIT also incorporates the basic principles of robotic experiments, sensing and locomotion, guaranteeing an exciting, hands-on adventure of knowledge and fun!

But remember! OWI is the recognized founder and leader in Educational Robot Kits. ACCEPT NO IMITATIONS.

Visit our homepage
@ <http://www.owirobot.com>



1160 Mahalo Place, Suite B
Rancho Dominguez, CA 90220-5443
(310) 638-7970
Fax: (310) 638-8347



Order M - F: 8a.m. - 4p.m. PST

ROBOTIC ARM TRAINER	OWI-007	5 Axis Control	Avail. Aug. '98	69.95
TRIPLE ACTION SOLAR CAR	OWI-685	Solar Sensor	28 pg. Book	39.95
S-CARGO	OWI-936K	Sound Sensor	47 Pg. Book	36.95
WAO II	OWI-961K	Programmable - Graphic	59 Pg. Book	69.95
SPIDER	OWI-962K	Infrared Sensor	49 Pg. Book	49.95
LINE TRACKER	OWI-963K	Infrared Sensor	48 Pg. Book	49.95
HYPER PEPPY	OWI-969K	Sound / Touch Sensor	46 Pg. Book	24.95
MOON WALKER	OWI-989K	Solar Sensor	10 Pg. Book	34.95

Whaddya Say To
A Guy Who's Had
The Same Job
For 50 Years,
Has Never Called
In Sick Or
Showed Up Late,
Never Taken A
Vacation Or A
Holiday, Never
Asked For A
Raise Or Griped
About His Bonus
And, Believe It Or
Not, Has No
Plans For
Retirement?



Thanks.

Remember - only you can prevent forest fires.

Call For **FREE** Catalog!

CABLE TV BONANZA

LOW PRICES!
GREAT SERVICE!

FULL VIEW CABLE BOXES
WHOLESALE PRICES!
30 Day Free Trial!
1 Year Guarantee!

- VIDEO STABILIZERS—Removes video tape copy protection
- TEST CHIPS, DEVICES, FILTERS AND ACCESSORIES

FREE BULLET BUSTER
with cable box purchase (REG.\$9.95)
Anyone implying theft of service will be denied assistance

N.S. INTERNATIONAL

OPEN DAILY 9am - 11pm (EST) **1-800-449-9189** C.O.D. or Credit Cards

\$139* Laser LightShow

Draw with a laser beam! Animation, text, music & more! Includes galvos, mirrors, servo amp, demo software disk, analog and digital computer interface. Use an inexpensive pen pointer or high power gas laser.

Computerized Motors \$39*

Includes: 2 Stepper motors, 2 DC motors, computer interface, training manual, & demo software disk. Expandable! Up to 12 motors, up to 3 amps per phase.

Now with 4 Axis Linear Interpolation

* Add \$6 for shipping. Computer with parallel printer port & cable, assembly, power supply, & laser are required.

FREE FLYER

Voice 510-582-6602 Fax 510-582-6603

SVS 1273 Industrial Pkwy West Bldg. 460
PO Box 55125 Hayward CA 94545-0125

POPTRONIX®

Awaiting your call! **Online Edition**

<http://www.poptronix.com>

Cable T.V. Converters & Equipment

Lower Prices
Dealer Discounts
30-Day Money back
1-year warranty
MC, Visa, AE, COD

No Florida Sales

www.cable4you.com

1-(800) 888-5585

Electronic Training Videos



Learn electronics quickly and easily with UCANDO's computer-animated training videos. Students can learn at their own pace and professionals will find the UCANDO videos to be a valuable source of reference material. If these videos aren't the best learning tools you've ever seen, return them within 30 days for a

complete refund. These videos are being used by Tech-Schools, CET's, Military Branches, Ham Operators, Industries, and more, across the United States and around the world. Order today and see how UCANDO is ...

"Changing The Way The World Learns Electronics."

VCR Maintenance & Repair ... \$29.95 All others ... \$44.95 each
 • Intro to VCR Repair • Direct Current • Alternating Current • Semiconductors • Power Supplies • Amplifiers • Oscillators • Digital 1 • Digital 2 • Digital 3 • Digital 4 • Digital 5 • Digital 6 • AM Radio • FM Radio Part 1 • FM Radio Part 2 • TV Part 1 • Intro to TV • TV Part 2 • The Front End • TV Part 3 • Audio • Fiber Optics • Laser Technology •

SAVE!!! 6 videos for only \$240 or 12 videos for only \$450



1-800-678-6113

or mail check or money order to:

UCANDO Videos

P.O. Box 928

Greenville, OH 45331





FREE Shipping ... FREE Catalog

CIRCLE 136 ON FREE INFORMATION CARD

OSCILLOSCOPES

from \$169 !!!

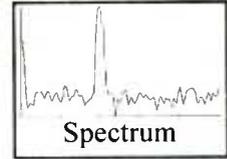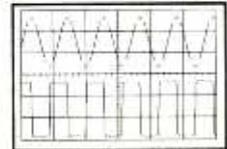ATC O-Scope uses printer port to turn PC-AT into Digital Storage Oscilloscope, Spectrum Analyzer, Freq. Counter, Logger, DVM. DC-500KHz



- Print, log to disk, or export data
- Accepts standard scope probes
- Uses standard printer port
- Small and portable
- Works with laptops
- Same day shipping
- Made in U.S.A.
- Single channel units from \$169
- Dual channel units from \$349

Options:

- Probe sets
- Automotive probes
- Battery packs

Order yours today.

800 980 9806

MC/Visa/Amex

Allison Technology Corporation

8343 Carvel, Houston, TX 77036 USA

PH: 713 777 0401, FAX: 713 777 4746, BBS: 713 777 4746

<http://www.atcweb.com>

Any waveform you want!




Starting at

\$795


Quantity 1

Money back guarantee

Telulex Inc. model SG-100

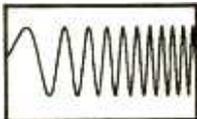


DC to 20 MHz linear and log sweeps

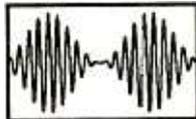


Int/Ext AM, SSB, Dualtone Gen.



Int/Ext FM, PM, BPSK, Burst

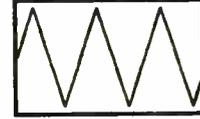


Ramps, Triangles, Exponentials

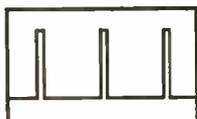


Pulse Generator



Noise

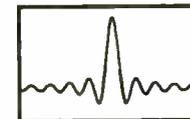

Arbitrary Waveforms

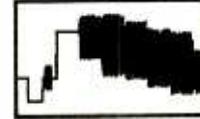

Unlimited Possibilities!

- **Synthesized Signal Generator**
Clean sinewaves DC-20 MHz with .001% accuracy!
.1 Hz steps. DC Offset. RS232 remote control.
- **Arbitrary Waveform Generator**
40 Megasamples/Second. 32,768 points. 12 bit DAC
- **Function Generator**
Ramps, Triangles, Exponentials & more to 2 MHz!
- **Pulse Generator**
Digital waveforms with adjustable duty cycle

Telulex Inc.

2455 Old Middlefield Way S Tel (415) 938-0240 <http://www.Telulex.com>

Mountain View, CA 94043 Fax (415) 938-0241 Email: sales@Telulex.com

CIRCLE 142 ON FREE INFORMATION CARD

Call Today And
SAVE!


**Unbeatable
PRICES!**

CABLE TV

**DESCRAMBLERS
CONVERTERS · FILTERS
VIDEO STABILIZERS**

FREE ➤ 30 Day Trial
FREE ➤ Product Catalog
FREE ➤ 1 Year Warranty

100% MONEY BACK GUARANTEE

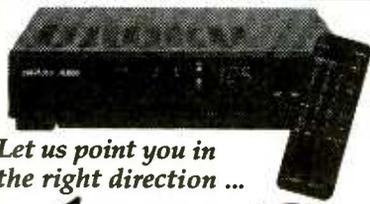

Let us point you in
the right direction ...




Omaha, Nebraska

**TOLL FREE
888-554-ARROW**
888-554-2776



ELECTRONIC COMPONENTS

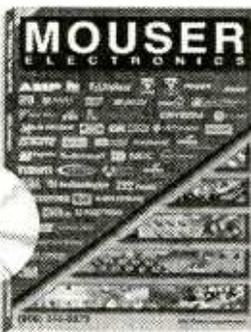

Visit our web site!
www.mouser.com

FREE catalog is available on the
internet, CD-ROM, or in paper!

- 70,000+ Products • 145 Suppliers
- Same Day Shipping • No Minimum Order

800-992-9943

817-483-6828 Fax: 817-483-0931
www.mouser.com catalog@mouser.com

958 North Main St., Mansfield, TX 76063

CLASSIFIED

MISCELLANEOUS ELECTRONICS FOR SALE

PLANS-KITS-SCHEMATICS

FREE CATALOG: Cable Descramblers, Notch Filters, Wireless Microphones, Telephone Bugs, Plans, Products, Information. **TINKERTRONICS** PO Box 270786, Corpus Christi, TX 78427 Rodgersd@juno.com

AUDIO-VIDEO-LASERS

CABLE TV

CABLE TV descramblers. One piece units. Pioneer 6310's, Scientific Atlanta 8580's, DPV7's and others. Lowest prices. Money back guarantee. **Precision Electronics**, Houston, TX (888) 691-4610.

CONFUSED Descramblers. Will explain all your options, all makes and models. Wholesale and retail. Open 6 days a wk 9AM - 8 PM Est. Best tech support and friendly service. Toll free 1 (888) 238-0967 **ROYAL ENGINEERING INC.**

CABLE descramblers and converters. 10 lot decoders \$38.00 ea. 10 lot converters \$57.00 ea. Visa and Mastercard accepted. (304) 337-8027.

CABLE DESCRAMBLERS AND CONVERTERS SHOP NO MORE, BEST PRICES AND TECH SUPPORT. EXTREME ELECTRONICS 1-888-609-4910

Free Cable Descrambler Plans, For Details Write: Sierra Publishing, 909 E. Yorba Linda Blvd., Suite H-181, Dept PEQ, Placentia, CA 92870

Signal Eliminator can block severe TV interference or unwanted channels! Order by channel number - 0 thru 36 available. Only \$30.00 each plus \$4.00 S/H. Quantity discounts. Money Back Guarantee. Prepay, Visa or Mastercard. COD \$5.00 additional. Visit us on the web today at <http://starcircuits.com/tvfilter>. Star Circuits, PO Box 94917, Las Vegas, NV 89193. 1-800-433-6319

CABLE Descrambling, New secret manual. Build your own Descramblers for Cable and Subscription TV. Instructions, schematics for SSAVI, Gated Sync, Sinewave, some free methods \$12.95, \$2.00 postage. **CABLETRONICS**, Box 30502PE, Bethesda, MD 20824.

CABLE TV EQUIPMENT & ACCESSORIES. Wholesalers Welcome! 30 Day Moneyback Guarantee! Free Catalog! **PROFORMANCE ELECTRONICS, INC.** 1-800-815-1512.

BIG SALE!! NOTCH FILTERS \$18.00. EXTERNAL ACTIVATORS and DESCRAMBLERS FROM \$99.00. Test chips from \$5.00. **BULLET/I.D. \$10.00.** Name Brand Cable Descramblers from \$135.00. **LET US BEAT YOUR BEST PRICE. 1-800-449-9189 ANYTIME. SE HABLE ESPANOLE**

CABLE "BULLET TERMINATOR/I.D. BLOCKER". Electronically shields yourself and your box. Free Hackers Guide included. **LIFETIME GUARANTEE. Wholesale prices. 1-800-820-9024.**

CABLE DESCRAMBLER!! ANYONE CAN BUILD IN SEVEN STEPS with RADIO SHACK PARTS. PLANS/KIT from \$5.00 PLUS FREE BONUS!! 1-800-818-9103

Descramble cable with simple circuit added to Radio Shack RF modulator and using VCR as tuner instruction \$10.00 **TELCOM**, Box 832 P-5 Brushly, LA 70719

36 Channel Jerrold JSX manual converters five for \$10.00. **McCullough**, Box 57 Salem, AR 72576. 1-870-895-2528

CABLE BOXES-ALL MODELS-ALL CHANNELS. Jerrold Impulse Dp, DPV & DPBB's, Pioneer or Scientific Atlanta - Lowest Prices in U.S. - \$175.00 including remote, batteries and cable. Call for 10 lot pricing. Toll Free (888) 689-0779.

SATELLITE EQUIPMENT

VIDEOCYpher II descrambling manual. Schematics, video and audio. Explains DES, EPROM, CloneMaster, Pay-per-view \$16.95, \$2.00 postage. Schematics for Videocypher Plus, \$20.00. Schematics for Videocypher 032, \$15.00. Collection of software to copy and alter EPROM codes, \$25.00. **VCI Plus EPROM**, binary and source code, \$30.00. **CABLETRONICS**, Box 30502PE, Bethesda, MD 20824.

DSS Hacking: How to construct and program smart cards, w/pic16C84, software. Complete DSS system schematics \$16.95. **CABLETRONICS**, Box 30502PE, Bethesda, MD 20824.

FREE DSS Test Card information package. Works on new system and turns on all channels including PPV, adult and sports channels. Write **SIGNAL SOLUTIONS**, 2711 Buford Rd., Suite 180, Richmond, VA 23235.

SKYVISION! Your Satellite Home Entertainment Source. **Best values:** DBS and C/Ku-band equipment, including 4DTV. Most complete selection: Parts-Tools-Upgrades-Accessories! **Free Discount Buyer's Guide.** Call 800-543-3025. International 218-739-5231. www.skyvision.com.

DSS TEST CARD authorizes all channels for information. Call toll free 1-888-416-7296. Plus Free Bonus!

BUSINESS OPPORTUNITIES

\$\$\$ Millions in Scrap Gold from old electronics, computers, circuit boards, jewelry, 24 hours: (603) 645-4767.

ELECTRONIC ENTERPRISES, Home Based, Part/Full time. 250pg. Comprehensive Guidebook, insider information, 24hr recording (800) 326-4560 x145.

Inventions/new products. ISC, America's leading invention firm, helps submit to companies. Patent Services. 1-800-288-IDEA.

EASY WORK! EXCELLENT PAY! Assemble Products At Home. Call Toll Free 1-800-467-5566 EXT. 5730

ATTN: CONSUMER ELECTRONICS TECHNICIANS RentWay, Inc., America's leader in the rental/purchase industry is rapidly expanding nationwide and needs experienced audio/video repair technicians. Openings exist in IN, OH, NY, CO, MD, SC and several other eastern states. Our compensation package includes an attractive starting salary, 401K, company vehicle and a monthly bonus program. An ability to relocate is an advantage. For more information: **Fax your resume to 814-836-5008 or E-mail us at Alevenson@rentway.com.**

Satellite Television Pays! 18" minidish sales force needed. **START VISION DIRECT:** (800) 899-9707, 8am-10pm Pacific.

COMPUTER SOFTWARE

FREE!! IBM Shareware and CD-Rom Disk Catalog. **MOM 'N' POP'S SOFTWARE**, POB 15003-E, Springhill, FL 34609. 1-352-688-9108, momn-pop@gate.net.

EDUCATION

FIBER OPTIC EDUCATIONAL EXPERIMENTS KIT, Includes: tutorial w/experiments, 40ft. fiber assortment, +cutting tool. \$19.95+S/H 800-373-7078

SEIZED CARS:

SEIZED CARS FROM \$175. Porsches, Cadillacs, Chevs, BMW's, Corvettes. Also Jeeps, 4WD's your area. Toll free 1-800-218-9000 Ext. A-14087 for current listings.

FORECLOSE:

GOV'T FORCLOSED homes from pennies on \$1.00. Delinquent Tax, Repo's. REO's. Your area. Toll free (1)800-218-9000 Ext. H-14087 for current listings

GRAVITY THEORIES

Gravity Reversal Theory. A manuscript revealing reversal of gravity by altering the cause of gravity. \$19.95 U.S. Dollars to Schwab Inc., 11221 Manchester Rd., Suite 306, St. Louis, MO 63122

BEST BY MAIL

Rates: Write National, Box 5, Sarasota, FL 34230

EDUCATION

HIGH SCHOOL DIPLOMA Fast, Accredited, Member Christian Schools International. 1-800-470-4723.

FINANCIAL

CASH NOW FOR FUTURE PAYMENTS! We buy payments from Insurance Settlements, Annuities, and Casino Winnings. We also buy Owner Financed Mortgages. Call R&P Capital Resources at 1-800-338-5815, X500.

"LIVE LIKE A KING" Experience Financial Freedom! Quickly and Easily Become Debt Free! Enjoy The Benefits Of Wealth! Call 1-800-968-1732. www://realnetnw.com/innovative/index.htm

SAVE HUNDREDS! TEN Major Corporations offer stock without typical brokerage fees! Information \$20.00. Paul's, 412 Bigwoods Circle, Belton, SC 29627.

TOP \$\$\$s FOR TD's, Contracts, Mortgage Notes. 1-888-544-4089.

MONEYMAKING OPPORTUNITIES

MAKE \$500 - \$8,000 Weekly! Using the newspaper. Amazing 24 hr. info. 602-351-8667.

OF INTEREST TO ALL

YOU MUST BE DREAMING! Talk to exciting women! 24 hours a day. One on one. 1-900-255-0900, Ext 8551. \$3.99 per minute. Must be 18 years. Serv-U (619) 645-8454.

Plast-a-id™ Unique VERSATILE NEW PRODUCT. Hardens quickly to Strong, Durable Plastic. You can Bond many Unlike Materials or Make New Plastic Parts. Special \$19.95. LEW WEST Co., Dept. PE, 9115 W. 73rd Ave. Arvada, CO 80005. Write or FAX: 303-456-9640 for details.

PSYCHIC & ASTROLOGY

BECOME PSYCHIC! Course detailing simple, straightforward techniques shows you how. Satisfaction guaranteed. Send \$24.95. MCR, PO Box 32455, Newark, NJ 07102.



ATTENTION CABLE VIEWERS
Own Your Own Unit Today
Cable TV Converters &
Descramblers
All Makes / All Models

Call 1-800-577-8775

Technical Info: 847-584-2099

Debco is a Kit Builders Paradise

Electronic Kits - Plans - Parts - Computers - Amateur Radio

Call Debco today for your FREE copy of The Electronic Experimenter's Journal

1 800 423 - 4499

Debco Electronics 4025 Edwards Rd. Cincinnati, OH 45205

Quality Microwave TV Systems

WIRELESS CABLE - ITFS - MMDS
ATV - INTERNATIONAL - S-BAND
Amplifiers • Antennas • Books • Components
Filters • Systems • Video Products
• RF Frequency 1990 - 2700 MHz
• Cable Ready - VHF - UHF Outputs
• SASE For "FREE" Catalog or Send \$1

PHILLIPS-TECH ELECTRONICS

PO Box 8533 • Scottsdale, AZ 85252

ORDER LINE 800-880-MMDS

CATALOG/INFO 602-947-7700

FAX LINE 602-947-7799

Visa • M/C • Amx • Dlac • COD's • Qty Pricing

CHALLENGER SYSTEM
33-Channel 52dB+ Gain
Complete Grid \$265
Five Year Warranty
FREE SHIPPING

CABLE TV CONVERTERS

Equipment & Accessories
Wholesalers Welcome

Call C&D ELECTRONICS

1-888-615-5757 M-F 10a-6p

Interactive catalog: www.tokview.com

**TV
cable
CONVERTERS
&
EQUIPMENT**



- * 30 days money back guarantee
- * 1 yr warranty
- * Quantity Discounts
- * Dealers Welcome!

VISA MC AMEX C.O.D.

(800)739-2253

TokView Electronics

5 Axis Robotic Arm Kit \$195.00



Build your own functional Robotic Arm

The kit comes complete with all hardware, base enclosure, structural components, 6 Hitec servos, Mini SSC II servo controller, Quick Basic software and an illustrated assembly manual. This robotic arm can be controlled from any micro with a serial port! It makes an excellent addition to a small mobile robot base. It is a great foundation for artificial intelligence experiments and teaching motion control. Check out our web site for more information and other robot kits.

- 3 Axis Version \$155.00
- Mobile Version \$250.00
- Mobile Robots Book \$48.00

Quantity discounts available. \$7.50 Shipping & Handling for USA, call for international and quantity shipping charges. IL residents add 6.25% sales tax to total.

Many more robot kits, ask for our free catalog!

Technical Service & Solutions
104 Partridge Road
Pekin, IL 61554-1403 USA



Tel: 309-382-1816
Fax: 309-382-1254
www.lynxmotion.com
jfrje@lynxmotion.com

Super Savings!!! Super Savings!!!



10 Watt Multimedia Speakers
Amplified speaker system features 10 watt max. power

output, 80Hz-20KHz frequency response, 0.5% THD, 40dB signal-to-noise, 2" x 4" full range speaker. Separate controls for volume and power. Includes cables and wall transformer. Size: 3-7/8" (D) x 3-1/2" (W) x 5-1/2" (H).

Retail Price: \$34.95

No. 220-0201.....\$9.95 (per pair)



50 Watt Multimedia Speakers
Amplified speaker system features 50 watt max. power

output, 80Hz-20KHz frequency response, 3" magnetically shielded full range speaker. Separate controls for power, volume and tone. Includes LED power indicator and front headphone jack. Includes cables and wall transformer. Size: 5-1/8" (D) x 4-1/2" (W) x 7" (H).

Retail Price: \$79.95

No. 220-0203.....\$29.95 (per pair)



20 Watt Multimedia Speakers
Amplified speaker system features 20 watt max. power

output, 80Hz-20KHz frequency response, 0.3% THD, 45dB signal-to-noise, 3" full range speaker. Separate controls for volume, power and tone. LED power ON indicator. Includes cables and wall transformer. Size: 5-1/2" (D) x 3-3/4" (W) x 7-1/8" (H). Retail Price: \$59.95

No. 220-0202.....\$19.95 (per pair)

Super CHARGER™

Alkaline and Ni-Cd Charger for AAA, AA, C and D Cell batteries. Incredible space-age technology automatically and safely recharges regular alkaline (1.5V) and nickel cadmium (1.2V) batteries. Mfg: Buddy L. Model #8000. *Repackaged*



No. 140-0140.....\$7.95 (ea)

MECI
340 E. 1st St.
Dayton, Ohio
45402
Call for a free catalog

Order Toll-Free
1-800-344-4465
Fax Order Line
1-800-344-6324

CIRCLE 150 ON FREE INFORMATION CARD

ADVERTISING INDEX

Popular Electronics does not assume any responsibility for errors that may appear in the index below.

Free Information Number	Page	Free Information Number	Page
— Aegis Research, Canada	74	153 MCM Electronics	67
— AES	72	— Mega Electronics	82
26 Alfa Electronics	79	150 Mendelson's	91
28 All Electronics	70	151 Mendelson's	85
— Allison Technology	89	— Mental Automation	72
— Andromeda Research	66	16 MicroCode Engineering	CV4
— Arrow Electronics	90	— Modern Electronics	85
— Basic Electrical Supply	82	152 Mouser	90
130 C&S Sales, Inc.	68	— NRI Schools	15
13 CadSoft	7	— NS International	88
— CD Electronics	78	— Orion Electronics	86
— Circuit Specialists	71	— OWI	88
— Cleveland Inst. of Electronics	29	146 Parts Express	81
— Command Productions	72	— Pioneer Hill Software	86
— Comtrad Industries	3, 5	45 Prairie Digital Inc.	87
— Consumertronics	66	— Price Wheeler	84
39 Dalbani	77	46 Print	85
— Eagan Technical Services	86	47 Print	76
— EDE Spy Outlet	86	— Pro Planet	88
— Foley-Belsaw	73	— QB Video	78
— Forest Electronics	74	— RC Distributing	82
— Fotronic Corporation	76	— Ross Technologies	82
— Franks Electronics	78	— Silicon Valley Surplus	88
— General Device Instruments	78	— Skyvision Inc.	78
29 George Brown College	CV3	— Smart Luck Software	87
— Grantham College of Eng.	4	— Sun Equipment	83
— Greenleaf Electronics Inc.	87	— Technological Arts	78
— Home Automation Systems	87	— Tek View	91
— Information Unlimited	75	142 Telulex	89
— Innovation West	82	— Transtronics	86
14 Interactive Image Technologies	CV2	136 UCANDO Videos	89
— Intronics, Inc.	85	— US Cyberlab	65
— Jameco	11	— Video Media	78
— KDE Electronics	66	— Vision Electronics	78
— Link Instruments	74	— Weeder Technologies	65
— Lynxmotion	91		

ADVERTISING SALES OFFICES

Gernsback Publications, Inc.
500 Bi-County Blvd.
Farmingdale, NY 11735-3931
1-(516) 293-3000
Fax 1-(516) 293-3115

Larry Steckler, EHF/CET
 President (ext. 201)
 e-mail advertising@gernsback

Adria Coren
 Vice-President (ext. 208)

Ken Coren
 Vice-President (ext. 267)

Christina Estrada
 Assistant to the President (ext. 209)

For Advertising ONLY
1-516-293-3000
Fax 1-516-293-3115

Larry Steckler
 publisher

Arline Fishman
 advertising director (ext. 206)

Marie Falcon
 advertising assistant (ext. 211)

Adria Coren
 credit manager (ext. 208)

**Subscription/
 Customer Service/
 Order Entry**
1-800-827-0383
7:30 AM - 8:30 PM EST

ADVERTISING SALES OFFICES EAST/SOUTHEAST

Stanley Levitan
 Eastern Sales
 1 Overlook Ave.
 Great Neck, NY 11021-3750
 1-516-487-9357, 1-516-293-3000
 Fax 1-516-487-8402
 slevitan26@aol.com

**MIDWEST/Texas/Arkansas/
 Oklahoma, Colorado, Arizona**


Ralph Bergen
 Midwest Sales
 One Northfield Plaza, Suite 300
 Northfield, IL 60093-1214
 1-847-559-0555
 Fax 1-847-559-0562
 bergenrj@aol.com

PACIFIC COAST/Mountain States

Anita Bartman
 Hutch Looney & Assoc., Inc.
 6310 San Vicente Blvd.
 Suite 360
 Los Angeles, CA 90048-5426
 1-213-931-3444 (ext. 227)
 Fax 1-213-931-7309

Study at home with the

Electronics Technician CD-ROM

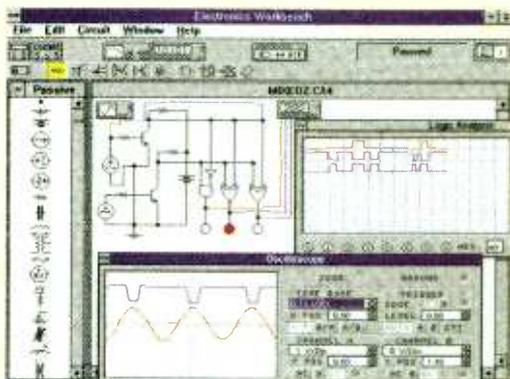

The only product of its kind

This unique CD-ROM based learning program includes 23 courses which are equivalent to a two-year Electronics Technician program and is recognized as the standard for Electronics Technician programs across North America.

Purchase the CD-ROM separately or earn College credits.

The choice is yours. Buy the CD-ROM and use it as the ultimate electronics reference tool to refresh your knowledge of electronics, or enroll in the program and earn College credits. The course material is delivered using video, text, 2-D and 3-D animations color photos, audio, and over 450 laboratory projects. Use the CD-ROM in the home, office, or shop as a troubleshooting/design tool and reference guide.

Industry Recognition

The course content for the CD-ROM was developed in association with some of the top corporate trainers in North America, and focuses on practical applications and troubleshooting techniques.

Best Price

The CD-ROM costs \$249 and comes with **ElectronicsWorkbench** (Student Edition), laboratory software simulation package. Complete all 23 courses on the CD-ROM and receive an Electronics Technician certificate.

Public Sector Standards

The CD-ROM was designed by George Brown College, one of the largest and most innovative community colleges in North America. Graduates of the program can continue their studies towards an undergraduate degree through the Minnesota University (Bemidji State) distance education program.

Easy at-home learning

All you need is the CD-ROM, no expensive books or lab equipment is required. Complete each course at your own pace, schedule the time that's best for you and decide how quickly you finish each course. The typical completion time is 48 weeks of part-time study, but there are no time limits.

Call now! Toll Free!


Call our 24-hour toll-free hotline to find out more about the Electronics Technician CD-ROM or the distance education program.

1-888-553-5333

George Brown College
160 Kendall Avenue
Toronto, Canada M5R 1M3
Fax: 416-415-4727
web site: <http://www.gbrownc.on.ca>


Professional Power at a hobbyist price.

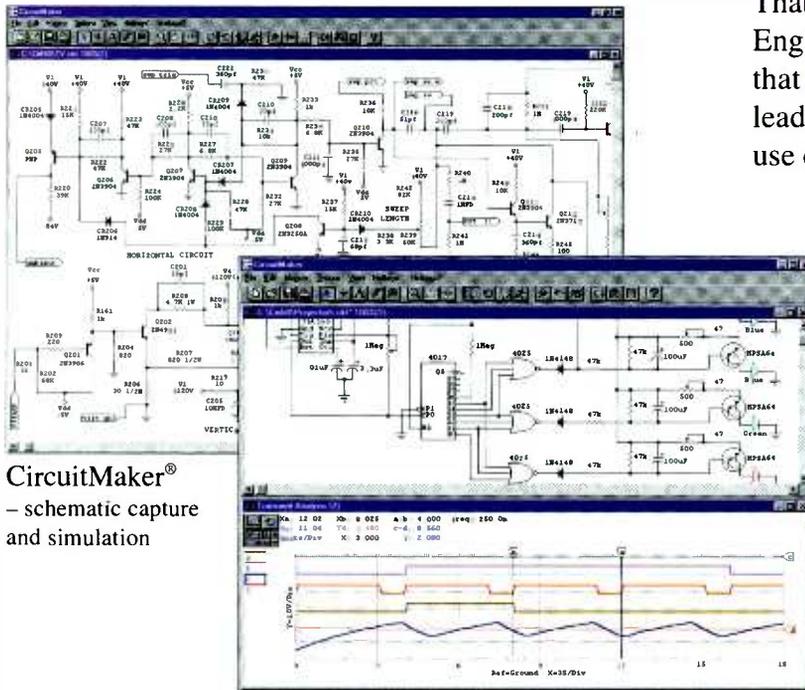That has been our philosophy at MicroCode Engineering since 1987. So it's no surprise that **CircuitMaker** and **TraxMaker** are the leading software tools for affordable, easy-to-use circuit design, simulation and PCB layout.



CircuitMaker®
– schematic capture
and simulation

TraxMaker® – PCB layout and autorouting

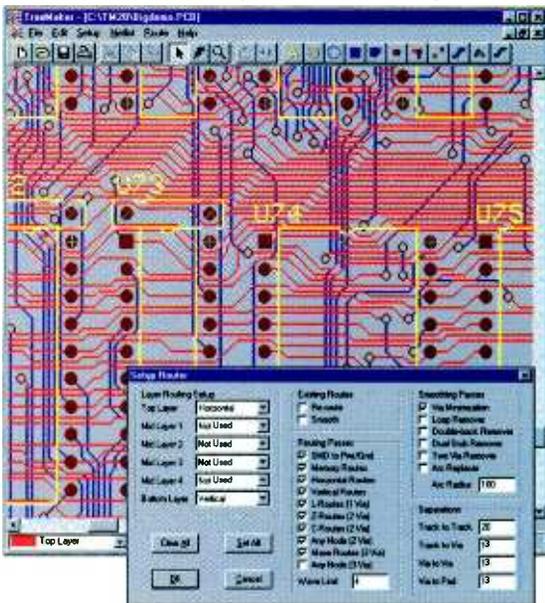

QUICKLY DESIGN analog, digital or mixed analog/digital circuits with CircuitMaker's advanced schematic features. You fully control the wiring, device placement, annotation and colors. And the Symbol Editor and macro features let you create unlimited custom devices and symbols.

SIMULATE and ANALYZE what you create – try all the “what if” scenarios with:

- Fast, proven 32-bit SPICE 3f5/XSpice simulator
- True mixed analog/digital simulation
- Fully interactive digital logic simulation
- 4,000-device library
- AC Frequency Analysis
- DC Operating Point Analysis
- DC Transfer Function
- Transient Analysis
- Step Function – step component values and sources over a user-definable range

TAKE MEASUREMENTS at any point in the circuit with a click of the Probe tool. Results appear immediately on virtual instruments like the Digital Oscilloscope, Curve Tracer, Digital Multimeter and Bode Plotter. No other simulator lets you take measurements as quickly and easily as CircuitMaker.

COMPLETE the design process with TraxMaker, a professional printed circuit board layout program with built-in autorouter. Import netlists from CircuitMaker and other schematic programs, or design boards from scratch.

- Includes autorouter, auto component placement and Design Rules Check
- Supports up to 8 copper layers, board sizes up to 32 x 32 inches
- Surface mount and through-hole components from a customizable library
- Outputs your PCB as a Gerber file, Excellon N/C drill file, and prints to any Windows-selectable printer or plotter

RELY ON free technical support from qualified engineers. And every MicroCode product is backed by our **30-day Money-Back Guarantee** if it does not live up to your expectations.

Call **800-419-4242** for more information and free demos
(or download from www.microcode.com)
CIRCLE 171 ON FREE INFORMATION CARD

CircuitMaker Version 5	\$299
TraxMaker Version 2	\$299
CircuitMaker Design Suite™ (CircuitMaker and TraxMaker)	\$549