

Radio-Electronics

JAPANESE TRANSISTOR REPLACEMENTS

75¢ ■ AUG. 1975

Radio-Electronics®

THE MAGAZINE FOR NEW IDEAS IN ELECTRONICS

COLOR TV CAMERA
Build It Yourself

HI-FI LAB TESTS

- Kenwood KR-5400 Receiver
- Crown VFX-1 Filter/Crossover

MATV SPLITTERS
See How They Work

TAPE DECK ELECTRONICS
Make The Reels Go Round
Without Jamming The Tape

USING YOUR SCOPE
To Speed Service Jobs



A
GERNSBACK
PUBLICATION


LIQUID-CRYSTAL CLOCK
Has 2-Inch Readouts

642220 RHM R0001A96 14 A FEB76
 A. L. RUMMEL
 RT 1
 HOLLSOPPLE PA 15935

Clinic
shooting Charts ★ State-Of-Solid-State

PTS ELECTRONICS

Precision Tuner Service

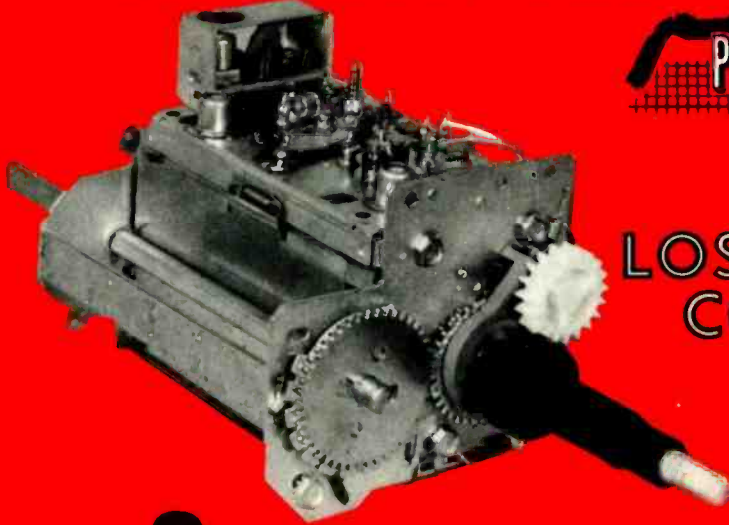

is proud to announce the
GRAND OPENING

of our new Service Centers in
LOS ANGELES
COLUMBUS, OHIO
PHOENIX
BOSTON
NORFOLK
MILWAUKEE

Fast 8 hr. Service!

LET US TAKE CARE OF YOUR TUNER PROBLEMS...

PTS will repair any tuner—no matter how old or new. Fastest Service—8 hour—in and out the same day. Overnight transit to one of our strategically located plants. Best Quality—you and your customers are satisfied.

PTS uses only ORIGINAL PARTS! No homemade or make-do, inferior merchandise (this is why we charge for major parts!). You get your tuner back in ORIGINAL EQUIPMENT condition.

PTS is recommended by more TV Manufacturers than any other tuner company and is overhauling more tuners than all other tuner services combined.

VHF, UHF \$10.95
UV-COMBO 17.95
IF-SUBCHASSIS 12.50

Major parts and shipping charged at cost. (Dealer net!)

PTS ELECTRONICS, INC.

HOME OFFICE	BLOOMINGTON, INDIANA 47401	5233 S. HIGHWAY 37	812-824-9331
ALABAMA	BIRMINGHAM, ALABAMA 35222	524 32ND ST. SO.	205-323-2657
ARIZONA	PHOENIX, ARIZONA 85061	2412 W. INDIAN SCHOOL RD.	602-279-8718
CALIFORNIA CENTRAL	LOS ANGELES, CA. 90023	4184 PACIFIC WAY	213-266-3728
CALIFORNIA NORTH	SACRAMENTO, CA. NO. 95841	4611 AUBURN BLVD.	916-482-6220
CALIFORNIA SOUTH	SAN DIEGO, CA. SO. 92105	5111 UNIVERSITY AVE.	714-280-7070
COLORADO	ARVADA, COLORADO 80001	4958 ALLISON ST.	303-423-7080
FLORIDA NORTH	JACKSONVILLE, FLA. NO. 32210	1918 BLANDING BLVD.	904-389-9952
FLORIDA SOUTH	MIAMI, FLA. SO. 33168	12934 N.W. 7TH AVE.	305-685-9811
INDIANA	BLOOMINGTON, IND. 47401	5233 S. HIGHWAY 37	812-824-9331
KANSAS	KANSAS CITY, KANSAS 66106	3116 MERRIAM LANE	913-831-1222
LOUISIANA	METAIRIE, LA. 70003	2914 WYTTCHWOOD DR.	504-885-2349
MARYLAND	SILVER SPRINGS, MD. 20910	1105 SPRING ST.	301-565-0025
MASSACHUSETTS EAST	SOMERVILLE, MASS. 02144	52 HOLLAND ST.	617-666-4770
MASSACHUSETTS WEST	SPRINGFIELD, MASS. 01103	191 CHESTNUT ST.	413-734-2737
MICHIGAN	DETROIT, MICH. 48235	13709 W. 8 MILE RD.	313-862-1783
MINNESOTA	MINNEAPOLIS, MINN. 55408	815 W. LAKE ST.	612-824-2333
MISSOURI	ST. LOUIS, MO. 63130	8456 PAGE BLVD.	314-428-1299
NEW JERSEY	E. PATERSON, N. JERSEY 07407	158 MARKET ST.	201-791-6380
NEW YORK	BUFFALO, NEW YORK 14212	993 SYCAMORE ST.	716-891-4935
NORTH CAROLINA	CHARLOTTE, N. CAR. 28205	724 SEIGLE AVE.	704-332-8007
OHIO SOUTH	CINCINNATI, OHIO 45215	8180 VINE ST.	513-821-2298
OHIO CENTRAL	COLUMBUS, OHIO 43227	4003 E. LIVINGSTON AVE.	614-237-3820
OHIO NORTH	PARMA, OHIO 44134	5682 STATE RD.	216-845-4480
OKLAHOMA	OKLAHOMA CITY, OK. 73106	3007 N. MAY	405-947-2013
OREGON	PORTLAND, OREGON 97213	5220 NE SANDY BLVD.	503-282-9636
PENNSYLVANIA WEST	PITTSBURGH, PA. 15202	257 RIVERVIEW AVE. W.	412-761-7648
PENNSYLVANIA EAST	UPPER DARBY, PA. 19082	1742-44 STATE RD.	215-352-6609
TENNESSEE	MEMPHIS, TENN. 38118	3614 LAMAR AVE.	901-365-1918
TEXAS SOUTH	HOUSTON, TEXAS 77032	4324-26 TELEPHONE AVE.	713-644-6793
TEXAS NORTH	LONGVIEW, TEXAS 75601	MOPAC RD.	214-753-4334
VIRGINIA	NORFOLK, VA. 23504	3118 E. PRINCESS ANNE RD.	804-625-2030
WASHINGTON	SEATTLE, WASH. 98108	432 YALE AVE.	206-623-2320
WISCONSIN	MILWAUKEE, WIS. 53215	3509 W. NATIONAL	414-643-8800

We offer you finer, faster...

... Precision
Tuner Service



ELECTRONICS, INC....

... Number ONE and still trying harder!
(Not a Franchise Company)

**1 YEAR
GUARANTEE**


**P
T
S
No.
1**

Circle 1 on reader service card

World's Most Inexpensive BASIC Language System

\$995

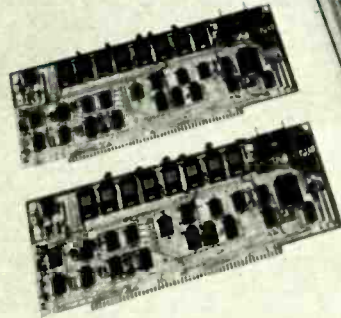
Limit one per customer.
OFFER expires September 15, 1975



Two 4,096 word Memory Boards (kit)




Altair 8800 Computer Kit

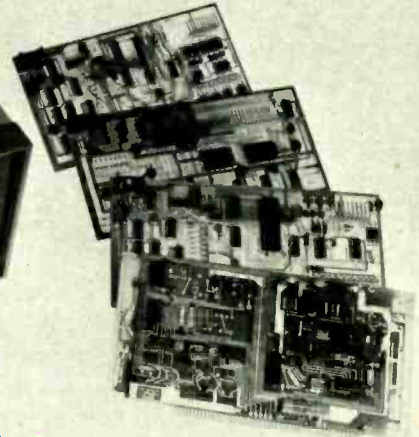

Your choice of Interface Boards (kit)

Altair 8K BASIC Language

Altair 8K BASIC Language. This language was chosen for the Altair Computer because of its versatility and power and because it is easy to use (comes with complete documentation). Altair 8K BASIC has many features not normally found in BASIC language including an OUT statement and corresponding INPut function that allows the user to control low speed devices (machine control without assembly language). Leaves 1750 words in 8K machine for programming and storage.

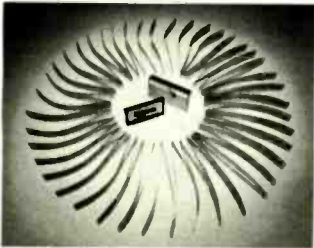

NOTE: Altair BASIC comes in either paper tape or cassette tape. Specify when ordering.

electrical signals from the computer to audio tones. It can be used to store unlimited amounts of information coming out of the computer and it can be used to put information back into the computer.

PRICES:

Altair Computer kit with complete assembly instructions	\$439
Assembled and tested Altair Computer	\$621
1,024 Word Memory Board	\$176 kit and \$209 assembled
4,096 Word Memory Board	\$264 kit and \$338 assembled
Full Parallel Interface Board	\$92 kit and \$114 assembled
Serial Interface Board (RS232)	\$119 kit and \$138 assembled
Serial Interface Board (TTL or TTY - teletype)	\$124 kit and \$146 assembled
Audio Cassette Interface Board	\$128 kit and \$174 assembled
4K BASIC language (when purchased with Altair, 4,096 words of memory and Interface Board)	\$60
8K BASIC language (when purchased with Altair, two 4,096 word memory boards and Interface Board)	\$75
COMTER II	\$780 kit
Teletype ASR-33	\$1500 (assembled only)

Interface Board Options. The *Parallel Interface Board* is used to connect the Altair 8800 to external devices that send and receive parallel signals. Many line printers require a *Parallel Interface Board*. The *RS232 Serial Board* is used to connect the Altair 8800 to external devices that send and receive RS232 serial signals. Most computer terminals require an *RS232 Serial Interface Board*. The *TTY Serial Interface Board* is used to connect the Altair 8800 to an ASR-33 or KSR-33 teletype (20 milliamp current loop). The *TTL Serial Interface Board* is for custom interfacing. The *Audio Cassette Interface Board* is used to connect the Altair 8800 to any cassette tape recorder. It works by changing the

Input Output Devices. The *Comter II Computer Terminal* has a full alpha-numeric keyboard and a highly-readable 32-character display. It has its own internal memory of 256 characters and complete cursor control. Also has its own built-in audio cassette interface that allows you to connect the *COMTER II* to any tape recorder for both storing data from the computer and feeding it into the computer. Requires an *RS232 Interface board*.

The *Standard ASR-33 Teletype* prints 10 characters per second. It has a built-in paper tape reader and punch. Has standard 120 day Teletype warranty. Requires a *Serial TTY Interface board*.

NOTE: The Altair 8800 can be connected to any number of input/output devices other than the ones listed above.

MAIL THIS COUPON TODAY

Enclosed is check for \$ _____

BankAmericard # _____ or Master Charge # _____

* \$995 BASIC System Special with following Interface Board: Parallel Serial RS232 Serial TTY Serial TTL Audio Cassette

Altair 8800 Kit Assembled Options (list on separate sheet)

Include \$8 for postage and handling

Please send free Altair System Catalog

NAME _____

ADDRESS _____

CITY _____ STATE & ZIP _____

Credit Card Expiration date _____

MIT S/6328 Linn. NE, Albuquerque, NM 87108 505/265-7553

Warranty: 90 days on parts for kits and 90 days on parts and labor for assembled units. Prices, specifications and delivery subject to change.

MIT S

"Creative Electronics"

6328 Linn, N.E., Albuquerque, NM 87108 505/265-7553

Circle 2 on reader service card



Whistles while you work.



We're taking a big part of the nuisance out of the spaghetti bowl of tangled wires that haunts every soundman. With the Shure A15TG Tone Generator, tracing a lost connection through a clutter of cables strung between microphones, mixers and amplifiers becomes an easy job. Simply plug the self-powered A15TG on one end of a cable and it puts a tone on that particular line. To find the other end, simply monitor the lines until you find the one that whistles. It's that easy. This new Tone Generator is only one of the many problem solvers in the Shure A15 Series. For more information about this series, write us. Or buy a Shure A15TG Tone Generator and just whistle.

Shure Brothers Inc.
222 Hartrey Ave., Evanston, IL 60204
In Canada: A. C. Simmonds & Sons Limited



Manufacturers of high fidelity components, microphones, sound systems and related circuitry.

Circle 3 on reader service card

Radio-Electronics®

THE MAGAZINE FOR NEW IDEAS IN ELECTRONICS

More than 65 years of electronics publishing

AUGUST 1975 Vol. 46 No. 8

BUILD ONE OF THESE

- 33 **Giant Liquid-Crystal Clock**
One IC and 2-inch high readouts combine to create a very simple digital clock. *by George J. Whalen*
- 42 **Color TV Camera Costs About \$400**
Part II—Circuit details and camera-head adjustments. by Gary Davis

TELEVISION

- 24 **Equipment Report**
Miller-Stephenson Cobra Spray attachment
- 58 **Step-By-Step Troubleshooting Charts**
Color problems don't have to be difficult. *by Stan Prentiss*
- 63 **Service Clinic**
Scan-derived DC power supplies. *by Jack Darr*
- 69 **Reader Questions**
R-E's Service Editor solves reader problems.

HI-FI AUDIO STEREO

- 36 **R-E Tests The Kenwood KR-5400**
A very special kind of Lab-Tested report we think is the most complete one you can find. *by Len Feldman*
- 39 **R-E Tests The Crown VFX-2**
Electronic crossover for bi-amplification and tri-amplification hi-fi systems. *by Len Feldman*
- 45 **Tape Deck Electronics**
How to make the reels go round without jamming the tape. *by Len Feldman*

TEST EQUIPMENT

- 22 **Equipment Report**
B&K 520 transistor tester
- 24 **Equipment Report**
Heath IO-4530 10-MHz triggered-sweep scope
- 52 **All About Oscilloscopes**
Part III: Operating your scope properly, plus measurements you can make. by Charles Gilmore

GENERAL ELECTRONICS

- 4 **Looking Ahead**
What's new in the world of electronics. *by David Lachenbruch*
- 55 **State-Of-Solid-State**
A new monolithic power amplifier and a monolithic function generator. *by Karl Savon*
- 60 **R-E's Transistor Replacement Directory**
More substitutes for Japanese Transistors. *by Elizabeth & Robert F. Scott*

DEPARTMENTS


- | | | | |
|-----|---------------------------|-----|---------------------|
| 106 | Advertising Index | 87 | New Literature |
| 12 | Advertising Sales Offices | 78 | New Products |
| 88 | Books | 95 | Next Month |
| 14 | Letters | 109 | Reader Service Card |
| 6 | New & Timely | 96 | Service Questions |

ON THE COVER

If you've always wanted to build a digital clock, but thought they were too complicated, try this one. It's a snap to assemble and has giant 2-inch high numerals. . . . see page 33



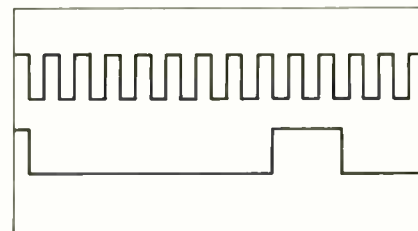INSIDE THE KENWOOD KR-5400 receiver. For all the facts on how well it works see our complete lab-test report on page 36.



INPUT AND OUTPUT WAVEFORMS from a BCD counter are only one of the things you'll learn to measure with your scope. . . . see page 52

Radio-Electronics, Published monthly by Gernsback Publications, Inc., 200 Park Avenue South, New York, NY 10003. Phone: 212-777-6400. Second-class postage paid at New York, NY and additional mailing offices. One-year subscription rate: U.S.A., U.S. possessions and Canada, \$8.75. Pan-American countries, \$10.25. Other countries, \$10.75. Single copies 75c. © 1975 by Gernsback Publications, Inc. All rights reserved. Printed in U.S.A.

Subscription Service: Mail all subscription orders, changes, correspondence and Postmaster Notices of undelivered copies (Form 3579) to Radio-Electronics Subscription Service, Boulder, CO 80302.

A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

As a service to readers, Radio-Electronics publishes available plans or information relating to newsworthy products, techniques and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, Radio-Electronics disclaims any responsibility for the safe and proper functioning or reader-built projects based upon or from plans or information published in this magazine.

looking ahead

Conservation sacrifice

Two controversial "improvements" in color-TV sets may be sacrificed on the altar of energy conservation. These are the power race, which is seeing ever-increasing high-voltage to force more brightness from the picture tube, and the trend toward 110-degree wide-angle short picture tubes. The nation's television manufacturers have met with Commerce Department officials and have been assigned the "voluntary" goal of reducing the power consumption of the average television set—both color and monochrome—by 40% below the 1972 level by 1976. The original goal was 25%, easily accomplished by the already nearly complete switch to solid-state. But government officials changed their tune and persuaded the industry to switch to the far tougher target of 40%. In the opinion of some top industry engineers, this means changing priorities for the near future.

The high-power race is something which most manufacturers haven't been too excited about anyway—it's been a defensive maneuver to avoid being out-brightened by the competition. The eventual switch to 110-degree tubes in color has always been a foregone conclusion. It happened in black-and-white, resulting in more compact cabinets. In Western Europe, 110-degree tubes are the general rule. But the wider deflection angle requires higher power, and although there will be some 110-degree tubes introduced in the near future, it's now probable that the majority of television manufacturers will stick predominantly with 90-degree deflection in order to meet the government guidelines.

VTR tape economy

Speaking of Sony, last month I reported on its Beta-

max home videocassette recorder. Now it has been introduced into the United States market. The first unit to be sold here will be a combination videocassette recorder and 19-inch color-TV set, with a list price of \$2,295, to be offered in a few large cities here this fall. It's now learned that one of the secrets of Betamax's extreme conservation of magnetic tape is the elimination of the guardband between the diagonal video tracks. The color phase-polarity is reversed on every other line, permitting the tracks to abut directly against one another. Any remaining cross-talk between tracks is eliminated by the use of a comb filter.

In videotape, particularly videotape designed for the home, the name of the game is economy of tape. Last month I gave some examples of the tape economy of various systems, and mentioned the fact that RCA's developmental MagTape Selecta-Vision had undergone a major revision which almost doubles its tape economy. (The figure given last month was for the original system.) The home videocassette race may well be won by the unit that gobbles up the least area of tape per hour, whether it's 1/4-inch, 1/2-inch or 3/4-inch tape. Therefore, I've prepared the following table, based on published specs, of the various videocassette and cartridge systems in the order of increasing approximate usage of tape to record for an hour. The systems marked with asterisks are developmental and subject to change. They are all helical scan except the German BASF Longitudinal Video Recording (LVR) system that lays down 28 longitudinal tracks on 1/4-inch tape, and American Videonetics that uses an eight-head assembly revolving at 7,200 rpm, laying down a track nearly perpendicular to the tape. The Akai 1/4-inch unit, although still an open-reel machine, is included here because the tape could easily be placed in a cassette or cartridge. EIA-J

Type I is the standard Japanese cartridge recorder.

System	Speed (ips)	Tape Width	Sq. ft./hour
Sony Betamax	1.57	1/2"	20.6
*BASF LVR	120.00	1/4"	26.8
*RCA MagTape	1.53	3/4"	28.7
V-Cord (Japan)	3.75	1/2"	46.9
Cartrivision	3.8	1/2"	47.5
*Amer. Videonetics	2.88	3/4"	54.0
Akai	10.0	1/4"	62.5
Philips VCR	5.6	1/2"	70.0
Sony U-Matic	3.75	3/4"	70.3
EIA-J Type I	7.5	1/2"	93.8

New TV projectors

Sony, the mini-TV specialist, has introduced two maxi-TV projection systems—one for home and the other for industrial-educational use. Scheduled for immediate marketing in New York, Chicago and Los Angeles is a one-piece furniture-housed home projection TV with a Kodak Ektalite screen that measures 40 inches diagonally. The picture is projected from a special 12-inch Trinitron receiver through a lens-and-mirror system. The receiver is housed in a pull-out drawer. When the set is not in use, a vertical flexible tambour door—like that used on a roll-top desk—covers the screen. Sony says the brightness is 20 foot-lamberts, adequate for viewing in a dimly lit room and nearly twice the brightness of Sony's earlier industrial-institutional unit with a slightly smaller screen. The price is \$2,500. Two other home projection systems are on the market—the Muntz Home TV Theater with a 30 x 40-in. screen (about 35 inches diagonally) at \$1,995, and the Advent Videobeam two-piece unit whose screen measures about seven feet diagonally.

The other Sony projection system has a screen measuring 12 feet diagonally and uses three specially made 12-inch Trinitron picture tubes as light sources—one for each color. The green tube projects directly onto the screen through a lens system, while

the red and blue images are combined using a dichroic mirror and projected through a second lens system. Altogether, the system uses 13 lenses. This system is claimed to have a projected picture more than 20 foot-lamberts in brightness. The screen is placed 11.5 feet from the projector. The system costs about \$23,300, as compared with \$44,000 for the G-E Light-valve projector, with which it competes.

Quintaphonics

The first movie claiming to have "Quintaphonic sound" is the Columbia release, "Tommy." The sound system, developed by John Mosley, uses a QS matrix to produce four channels from two magnetic sound tracks, feeding speakers at the corners of the theatre. A third track provides the fifth channel, which is fed to a speaker system directly behind the screen. Over 50 theaters have been equipped with decoders and additional amplifiers and speakers.

Pay-TV via bird

United Artists-Cablevision, which owns cable TV systems serving 182,000 subscribers, plans to feed special closed-circuit pay-TV programming to its system by space satellite. It will install earth stations at each of its system locations to receive programming from the Home Box Office, a pay-TV network. The first earth station will serve CATV systems in Fort Pierce and Vero Beach, FL, later this year. It will be followed in 1976 by installations serving Fort Smith, AR; Laredo, TX; Yuma, AZ; El Centro, CA, and Pasco and Kennewick, WA.

by DAVID LACHENBRUCH
CONTRIBUTING EDITOR

New Mallory Ni-Cad Batteries. Rechargeable 1000 times.



Economical recharging —
Mallory BC-1 Charger draws only two watts.

Team these long-life nickel-cadmium cells with an automatic Mallory Charger, and you can recharge them 1000 times, or more.

You'll be sure of having fresh D, C, and AA batteries, while saving money, time and trouble. Mallory Rechargeable Nickel-Cadmium Batteries keep on coming back for more in electronic calculators, tape recorders, radios, cameras, toys, other battery-powered products.

Keep a spare set of Mallory Ni-Cads on hand,

and you'll never run out of battery power again. They recharge to full strength, two or four at a time. And unlike ordinary dry cells that lose voltage during discharge, Mallory Ni-Cads with a full charge maintain operating voltage during the entire work cycle. You get maximum power, continuously, for top product performance.

For the long run, Mallory Rechargeable Ni-Cads . . . the 1000-time batteries. Get them now at your Mallory Distributor.

MALLORY

MALLORY DISTRIBUTOR PRODUCTS COMPANY

a division of P. R. MALLORY & CO. INC.

Box 1284, Indianapolis, Indiana 46206; Telephone: 317-856-3731

Batteries • Capacitors • Controls • Security Products • DURATAPE® • Resistors • Semiconductors • SONALERT® • Switches • Fastening Devices

DURATAPE® and SONALERT® are registered trademarks of P. R. Mallory & Co. Inc.

Circle 4 on reader service card

new & timely

New non-impact printer writes with laser beam

A new non-impact printer just tested by RCA for the US Army uses a laser to transfer digital communications alphanumeric characters onto ordinary paper. The messages are transferred by a process in which the laser scans its beam across a dye-coated plastic ribbon in contact with the paper. Called TLP (tactical line printer), the system has seven speeds—55, 110, 220 and 440 lines-per-minute for serial input and 273, 605 and 900 lines-per-minute for parallel input.

The TLP is interfaced to receive digital communications from a wide variety of sources, including satellite ground terminals. It decodes the digital data received and stores it in a buffer memory one line at a time. It then produces an electrical signal that modulates the laser's intensity as it scans the plastic ribbon, producing a series of dots. The dots form the characters as the laser continues to scan, reproducing a line in 19 horizontal scans.

Advantages of the TLP are claimed to be less maintenance, since a laser has no moving parts to break down; cost savings through use of ordinary paper, and quietness, since the printer is a non-impact type.

Dr. Coolidge, inventor of tungsten filament, X-ray, dies at age 101

Dr. William D. Coolidge, retired General Electric vice president and director of research, died February 3 after a short illness. He was 101 years old last October.

Born on a small farm in Massachusetts, Coolidge attended the Massachusetts Institute of Technology. He graduated in 1896, \$4,000 in debt for the money borrowed to put him through college. He then worked as an assistant in physics at M.I.T. Obtaining a scholarship, he studied in Germany, receiving his PhD (summa cum laude) from the University of Leipzig in 1899. Returning to M.I.T., he taught until 1905, leaving to join General Electric.

Within two years, Dr. Coolidge succeeded in producing a ductile form of the notoriously brittle and unworkable metal, tungsten. Drawn into thin filaments, it became the ideal material for electric lamp filaments. By 1911 it had replaced the brittle and short-lived materials heretofore used and ushered in an era of cheap, long-life electric lamps that could be used in any position and that would withstand the shock of automobile operation and other rough usage.

The tungsten filament led to another

invention—the Coolidge X-ray tube. A cold-cathode, gaseous type of X-ray tube already existed—mostly as a laboratory curiosity. The tubes were erratic and tended to change their characteristics each time they were used. The Coolidge tungsten filament hot-cathode tube could be evacuated to a high vacuum and the output predetermined and accurately controlled. Patented in 1916, the new Coolidge tubes also used tungsten in the "target" or anode.



DR. COOLIDGE as he appeared at 81.


During World War I, Drs. Coolidge and Irving Langmuir—also of General Electric—developed the first successful submarine detector. After the war, he went on to develop new high-voltage X-ray tubes, with potentials up to 2 million volts.

Dr. Coolidge became director of the General Electric Research Laboratory in 1932. Under his direction, the laboratory developed, among other things, the sodium vapor lamp, Fernico glass seals for vacuum tubes, the electric blanket, "invisible" glass, new permanent magnet alloys and high-quality magnetic steel.

During World War II, he was associated with the atomic bomb project. He retired in 1944, having remained two years beyond normal retirement age because of the need for top scientists during the early stages of the war.

On his 100th birthday, G-E employees presented Dr. Coolidge with a huge birthday cake decorated with 100 tiny tungsten lamps (*Radio-Electronics*, March 1974, page 12) and with the tungsten anode of an early Coolidge X-ray tube at its center.

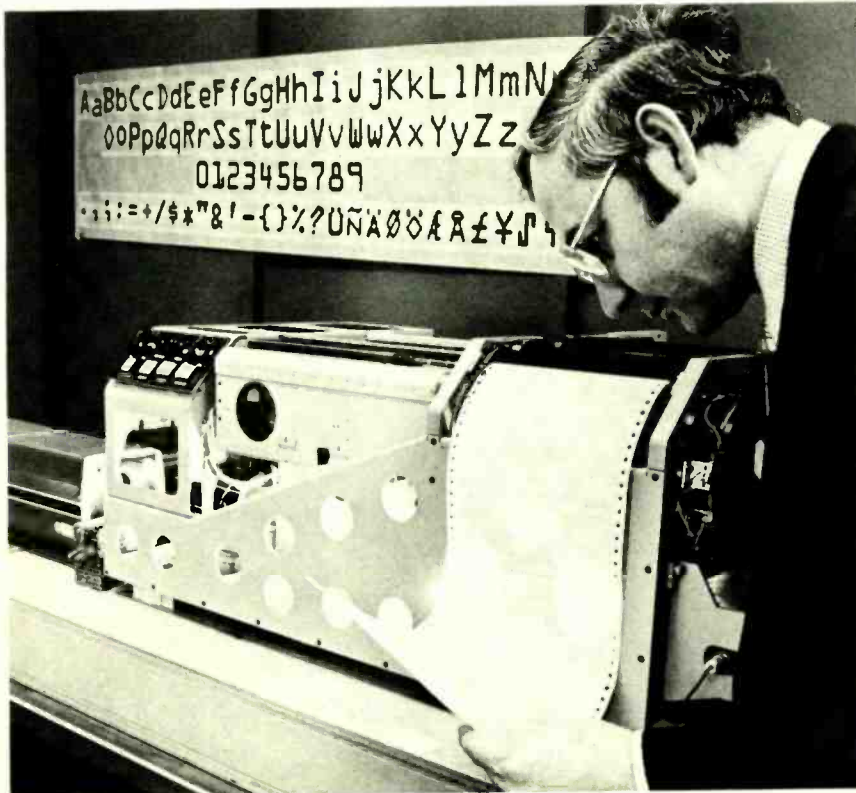Besides his PhD from Leipzig (renewed with a Golden Anniversary PhD in 1949),
(continued on page 12)



MARTIN L. LEVINE OF RCA EXAMINES COPY FROM THE NEW PRINTER that uses a laser. An enlarged view of the characters is shown in the background.

Get the news before it's news... with a "behind-the-scenes" Scanner Radio from Radio Shack!

Pocket-size Realistic scanners seek and lock-in on exciting police, fire and emergency calls, even continuous weathercasts.* There's one to cover the action in your area — 11 models in all.

PRO-6 — VHF-Hi and VHF-Low

Electronically scans up to 4 crystal-controlled channels on 148-174 or 30-50 MHz. Stops on each active channel until conversation ends, then resumes scanning. You don't miss a thing—it's like 4 radios in one. Lighted channel indicators, switches for bypassing any channels, scan/manual switch, variable volume and squelch, built-in antenna, earphone jack. With 4 "AA" cells. Requires up to 4 crystals. #20-171. **119⁹⁵**


PRO-4A — VHF-Hi Band

Like the PRO-6, but covers VHF-Hi only. #20-174 **99⁹⁵**

PRO-5 UHF "Metro" Band

Same as the PRO-4A, but covers 450-470 MHz used in many larger cities. #20-169. **119⁹⁵**

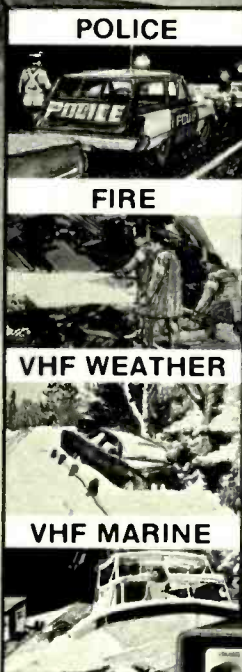Accessories Available. Plug-in antenna. 12VDC adapter, AC adapter/battery charger, rechargeable batteries.



*On VHF-Hi band in over 70 localities

NEW PRO-16A — Super Scanner for the ultimate at-home or mobile listening post



With
Extended UHF
Coverage

Scans up to 16 crystal-controlled channels, in any combination, on 30-50 and 148-174 MHz VHF and 450-512 MHz UHF. Like having 16 radios in one! Lockout buttons and indicator lights for each channel, manual selector, squelch, variable scan rate, scan-delay in/out button, 12VDC/120 VAC operation, mobile mounting bracket. Requires up to 16 crystals. U.L. listed. #20-165. **229⁹⁵**

Police-frequency listening may be regulated by local authorities

FREE New 1976 Radio Shack Catalog

OVER 2000 PRODUCTS
EXCLUSIVES ON EVERY PAGE
BEAUTIFUL FULL COLOR

Stereo • Quadraphonic • Phonographs
TV Antennas • Radios • Citizens Band
Kits • Recorders • Tape • Tools
Auto Tune-Up • Electronic Parts
Test Instruments • More!



164 pages of the finest in home and hobby electronics. Respected brand names like Realistic, Micronta, Archer, Science Fair — and they're available only at Radio Shack stores and dealers nationwide! See what's really new in electronics by getting this catalog now.

SEND FOR YOURS TODAY!
FILL OUT COUPON BELOW

1976 Mail to Radio Shack, P. O. Box 1052, 541
Catalog Ft. Worth, Texas 76101. (Please print.)

Name _____ Apt. No. _____

Street _____

City _____

State _____ ZIP _____



Master Charge or
Bank Americard at
participating stores

REALISTIC® at Radio Shack®


A TANDY CORPORATION COMPANY

OVER 3000 STORES • 50 STATES • 7 COUNTRIES
Retail prices may vary at individual stores

Circle 5 on reader service card

Prepare for a high-paying career in Complete Communications

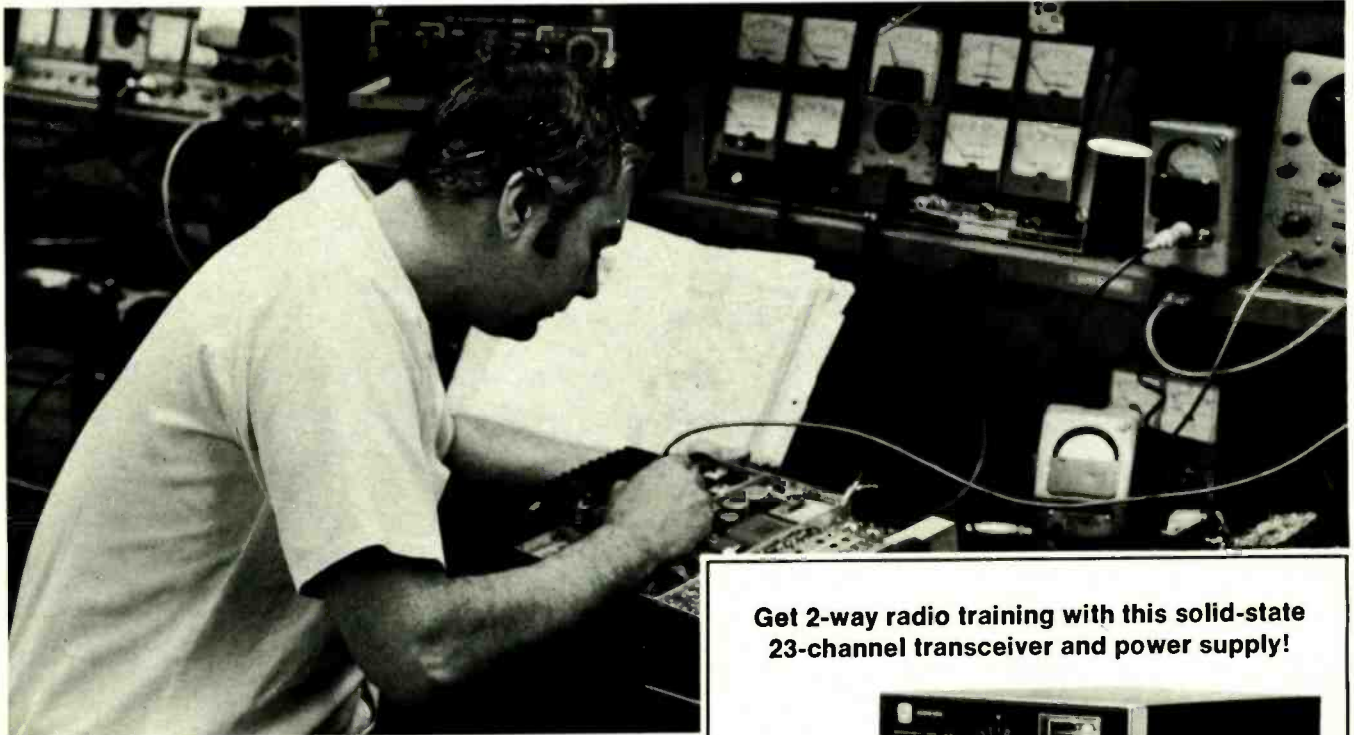Including CB design, installation
and maintenance...in actual practice



The field of communications is bursting out all over. In Citizens Band alone, estimates predict a growth in equipment sales from \$514 million in 1973 to \$1.2 billion dollars in 1982! That means a lot of openings in service and maintenance jobs. NRI can train you at home to fill one of those openings... including your FCC license and solid-state 2-way radio service.

NRI's Complete Communications Course will qualify you for a First Class Commercial License or you get your money back! It covers AM and FM Transmission Systems, Teletype, Radar Principles, Marine Electronics, Mobile Communications, and Aircraft Electronics.

You will learn to service and/or adjust CB equipment... using your own 23-channel Johnson Transceiver and AC power supply for hands-on experience as well as your own personal use.

With NRI's training program, you can learn this important skill easily, at home in

Get 2-way radio training with this solid-state 23-channel transceiver and power supply!



Your CB training will be up-to-the-minute when you experiment with this solid-state transceiver unit. Mount it in your car or use it with your AC power as a base station. You get "hands-on" experience that puts your course theory into practice the practical way.

your spare time. You get 8 training kits, including your own 3½ digit digital multimeter for digital experiments and precise measurements. You'll learn from bite-size lessons, progressing at your own speed to your FCC license and then into the communications field of your choice.



Only NRI offers five choices in TV/Audio Servicing



NRI can train you at home to service and repair commercially-built color and black-white TV, hi-fi equipment, AM-FM radios and sound systems. You can choose from 5 courses, starting with a basic servicing course with 65 lessons... up to a Master Color TV course, complete with 25" diagonal solid state color TV in handsome woodgrain cabinet. All courses are available with low down payments and convenient monthly payments to fit your budget. And all courses provide professional equipment along with NRI-designed kits for hands-on training. With the Master Course, for instance, you receive your own 5" wide band, solid-state triggered sweep oscilloscope, TV pattern generator, 3½ digit digital multimeter, and a high quality NRI 25" diagonal solid state television receiver expressly designed for color TV training.

YOU PAY LESS WITH NRI TRAINING AND YOU GET MORE FOR YOUR MONEY

NRI employs no salesmen, pays no commissions. We pass the savings on to you in reduced tuition costs and extras in the way of professional equipment, testing instruments, etc. You can pay more, but you can't get better training.

Step into the digital age with NRI's Complete Computer Electronics Course



Digital electronics is the career area of the future... and the best way to learn it is with NRI's Complete Computer Electronics Course. You can become a computer or digital technician with NRI's unique and fascinating home training... while you build and use a real digital computer in your home! This is no beginner's "logic trainer". It's a complete programmable digital computer. And it's just one of ten kits you receive, including a professional digital multimeter for experiments and precise measurement. It's the quickest and best way to learn digital logic, and computer operation.

NEARLY ONE MILLION STUDENTS IN 60 YEARS HAVE LEARNED AT HOME THE NRI WAY...

Mail the insert card and discover for yourself why NRI is the recognized leader in home study training. No salesman will call. Do it today and get started on that new career.

APPROVED UNDER GI BILL

For the career minded, we are approved for veterans benefits. Check box on card for details.

MAIL THE INSERT CARD FOR YOUR FREE NRI CATALOG

No salesman will call



NRI SCHOOLS
McGraw-Hill Continuing Education Center
3939 Wisconsin Avenue,
Washington, D.C. 20016

Hugo Gernsback (1884-1967) founder

M. Harvey Gernsback
editor-in-chief and publisher

Larry Steckler, CET, editor

Robert F. Scott, W2PWG, CET,
technical editor

Arthur Kleiman, associate editor

Jack Darr, CET service editor

Leonard Feldman
contributing high-fidelity editor

David Lachenbruch, contributing editor

Karl Savon, semiconductor editor

Vincent P. Cicenia, production manager

Sarah Martin, production assistant

Harriet I. Matysko, circulation director

Arline R. Bailey, advertising coordinator

Cover photo courtesy Walter Herstatt

Cover design by Louis G. Rubsamen

Radio Electronics is a member of the *Institute of High Fidelity* and is indexed in *Applied Science & Technology Index* and *Readers Guide to Periodical Literature*.



Radio-Electronics is published by Gernsback Publications, Inc. 200 Park Ave. S. New York, NY 10003 (212) 777-6400

President: M. Harvey Gernsback

Secretary: Bertina Baer

ADVERTISING SALES

EAST

Stanley Levitan, Sales Manager
Radio-Electronics
200 Park Ave. South
New York, NY 10003
(212) 777-6400

MIDWEST/Texas/Arkansas/Okla.

Ralph Bergen
The Ralph Bergen Co.
6319 N. Central Ave.
Chicago, IL 60646
(312) 792-3646

PACIFIC COAST/Mountain States

Jay Eisenberg
J.E. Publishers Representative Co.,
8732 Sunset Blvd.,
4th Floor,
Los Angeles, CA 90069
(213) 659-3810

Sales Mart Building
1485 Bayshore Blvd., Box 140
San Francisco, CA 94124
(415) 467-0125

Dr. Coolidge held honorary doctorates from at least half a dozen universities in North and South America. He held 83 patents, was a member or honorary member of a large number of scientific societies and received numerous awards and medals from institutions and societies in the United States, Britain, Chile and other countries, including the honorary M.D. degree of the University of Zurich, an honor seldom bestowed on an American layman.

Night-vision bifocals help firefighters

Helicopter fire-fighters of Los Angeles County have been made more effective in forest-fire missions with the help of special night-vision goggles.

Helicopters have proved their worth in daytime fire-fighting, especially in fighting forest fires. They can be even more effective at night, when temperatures and wind speeds often drop and fire spread is slower. But while a fire itself is conspicuous, it does a poor job of lighting up its surroundings. Ability to see the area and size-up the situation gives the fire-fighter an edge he cannot have if "working in the dark."

The two-pound goggles, made by ITT Electro-Optical Products Division, Roanoke, VA, use any low-level light source—firelight, starlight, moonlight or artificial light—to give the wearer an electronically amplified picture of whatever's beneath. The goggles are bifocal, so the pilot can read his instrument panel as well as study the terrain below.

In more than 50 missions to date, the Los Angeles County Fire Department reports, the fires have been brought under control sooner than would have been possible under daytime flying conditions.

One cable for power and video in latest CCTV camera

The recently introduced RCA VidiPlex CCTV camera, model TC1025, has made installation easier by using a common cable for the video signal and power supply. The camera consists of two units—a camera head and power supply connected by an RG-59/U cable. The single conductor carries 24-volts DC to the camera head and the video to the monitor.



LATEST IN RCA'S TC1000 FAMILY has 2:1 interlace and one cable for video and power.

A 2:1 interlace scanning network, as used in standard broadcast work, improves vertical resolution and prevents picture crawl, often objectionable in random-interlace surveillance cameras. Images from several cameras can be presented simultaneously on the same screen, and cameras can be locked together. **R-E**



FIRE-FIGHTING HELICOPTER PILOTS of Los Angeles County wear these bifocal light-amplifying goggles that permit them to see at night while flying over dangerous mountain terrain to fight forest fires, while at the same time keeping an eye on the cockpit instruments.

no strings attached


NEW **Weller**[®] CORDLESS SOLDERING IRON GOES ANYWHERE

A professional quality tool, Weller's feather-light and fingertip-handly WC-100 Cordless Soldering Iron allows you to make connections anywhere...without dependence on an AC cord and outlet.

The heart of the WC-100 is its high-energy, long-life, nickel-cadmium battery which springs into action at the touch of your finger, heating the tip to over 700°F in just 6 seconds. And no danger of accidental discharge. Weller's exclusive sliding safety switch breaks the circuit when your finger is removed, won't lock in "on" position, and does lock in "off" position for added safety while restoring energy with fast-power recharger (UL listed).

Loosen two slotted set screws and you've got instant choice of four tips... regular, long-reach, fine-point, or miniature... each mounted on an extra-strong stainless tube to resist bending. Tip is continuously illuminated by the built-in light which focuses on the work area, a special advantage under poor lighting conditions.

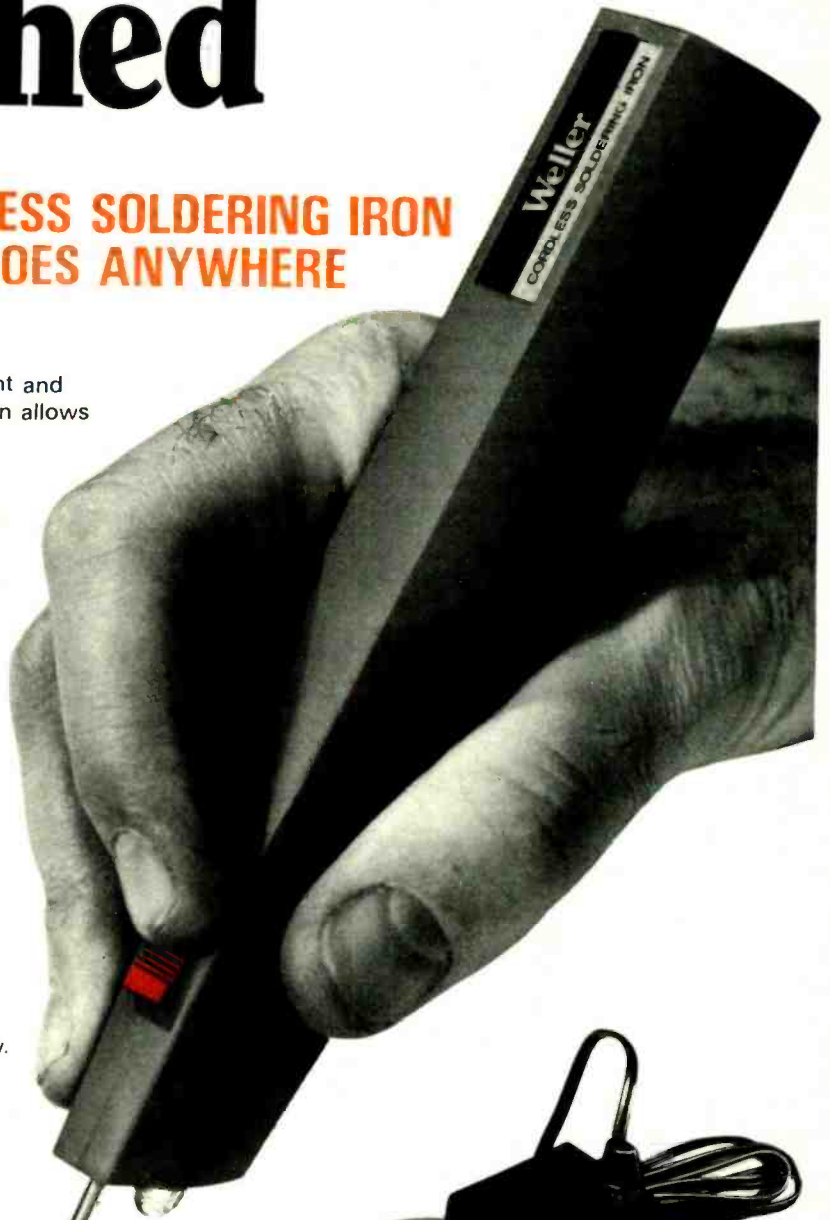Try this for size! It's a full-scale photo of the compact WC-100. And the real thing is waiting for you at your dealer or distributor...right now. Need to know more? Request literature.



Weller-Xcelite Electronics Division
The Cooper Group

P. O. BOX 728, APEX, NORTH CAROLINA 27502

Circle 6 on reader service card

BUILD & TEST CIRCUITS AS FAST AS YOU THINK!

- POWER FOR THE PROFESSIONAL
- ECONOMY KITS FOR THE HOBBYIST
- A MODEL AND A PRICE FOR EVERYONE



PROTO BOARD 203

Breadboard Prototyping with 5 Volt, 1 AMP Regulated Power Supply included! A total ready-to-use power breadboard prototest device with a built-in regulated, short-proof power supply. Just plug-in and start building! 2 extra floating 5-way binding posts for external signals. Self-contained with power switch indicator lamp and power fuse. 24-14 pin DIP capacity. Attractive two-tone quality case. All metal construction. 9 $\frac{3}{4}$ " L x 6 $\frac{1}{2}$ " W x 2 $\frac{3}{4}$ " H. 5 lbs. Order today!

\$75

Add \$2.50 shipping/handling

A modestly priced kit for the economy-minded experimenter . . .

PROTO BOARD 100

A low cost, big 10 IC capacity breadboard kit with all the quality of QT sockets and the best of the Proto Board series . . . complete down to the last nut, bolt and screw. Includes 2 QT-35S Sockets; 1 QT-35B Bus Strip; 2 5-way binding posts; 4 rubber feet; screws, nuts, bolts; and easy assembly instructions.

19⁹⁵

Add \$1.50 shipping/handling.

PROTO-CLIP
for Power-On,
Hands-Off Signal
Tracing. No more
shorting leads.
Costs less than . . .

\$5

Bring IC leads from pc board for fast signal tracing and troubleshooting. Inject signals. Wire unused circuits into boards. Scope probes and test leads lock onto Dynagrip inset (see circle) for hands-off testing. Plastic construction eliminates springs, pivots. Non-corrosive nickel/silver contacts for simultaneous low resistance connections.

PC-14, 14-pin Proto Clip, \$4.50 ea.
PC-16, 16-pin Proto Clip, \$4.75 ea.

Add 75¢ shipping/handling.

Order today off-the-shelf from CSC or local distributor. Charge: BAC, MC, AX. Write for free catalog. Free English/Metric Slide Rule with each order. Dealer inquiries invited.

Foreign Orders add 15%.

Patents Pending Made in USA
Prices subject to change

CSC Continental Specialties Corp.

Box 1942, New Haven, CT 06509 • 203/624-3103

W. Coast Off.: Box 7809, S. Francisco, CA 94119 • 415/383-4207
Canada: Available thru Len Finkler Ltd., Ontario

Circle 7 on reader service card

letters

PERIPHERALS

With the rapid development of homebrew computer systems, the need for peripheral devices is sure to grow. Readers may be mystified about sources of paper-tape readers, card reader/punches, tape drives, etc. With the prices as they are, and the mechanical complexity of these devices, it may be cheaper to buy than build.

I thought other readers might be interested in a company that specializes in used computer equipment. Write to: American Used Computer Corporation, Post Office Box 68, Kenmore Station, Boston, MA 02215.

This company sells used micro (and macro) computers, central processors, memories, etc., in addition to peripherals. Since the equipment is used, the prices tend to be reasonable.

Keep the computer projects coming, they are fulfilling the dream of "a computer in every home."

STEVEN C. HORII
New York, NY

City of New York
Department of Consumer Affairs
80 Lafayette Street
New York, N.Y. 10013
Elinor Guggenheimer,
Commissioner

Dear Ms. Guggenheimer:

Since you have taken office, it is obvious you have gone out of your way to make life unbearable for the hard working, law abiding citizen. The actions of your office in recent months, if allowed to continue, will cause mass bankruptcy and emigration from New York City of all types of independent service personnel.

To be more specific, I would like to call your attention to the havoc and mass hysteria you are inflicting upon the television service industry, of which I am a member. First, I would like you to explain why you singled out this industry for licensing, ignoring a multitude of others, equally deserving. If you really wanted to remove the rotten apples from the barrel (of each servicing field) and work for the public good (as you were appointed to do), you would have instituted similar licensing requirements for all industries which deal with the public. WHY HAVEN'T YOU?

Of course there are television repairmen who are dishonest and take advantage of the public. Licensing here may have cut down on the dishonest techniques of a select few, but due to excessive fees and an over-burdening of paperwork, you have forced most television service technicians to either raise their prices or go out of business. Is this

(continued on page 16)

REPLACEMENT SK Series

Fix it with SK. The RCA quality replacement.

Count on top quality in SK replacement semi-conductors. Because they carry the name RCA, a top manufacturer of OEM devices. Same strict AQL standards, same strict Director of Quality Assurance. That's how we protect you from callbacks, so you can make more profitable use of your time. RCA's higher-than-ever 410 to 1 replacement ratio will help you save time too. Your key to fast, easy replacement is RCA's new 1975 SK Replacement Guide. Get your copy at the RCA distributor where you buy SK parts.

RCA Solid State, Box 3200, Somerville, N.J. 08876.



It's OK if it's **sk**

Circle 8 on reader service card

FAST RELIEF FROM SOLID STATE HEADACHES



**STOCK
THIS
FAST
SELLER**

Now with
E-Z Hook leads!

There's nothing else like the Hickok Model 215 Pocket Semiconductor Tester.

- It's simple to use — no set up — no data books.
- It automatically determines lead configuration.
- LED displays indicate if semiconductor is GOOD or BAD and identifies base lead (gate for FET's) and whether NPN or PNP.
- Operates on 9V batteries.
- Weighs only 12-ounces and fits in your pocket.

We back the Model 215 with the best warranty in the business — two full years.

The Model 215 or our bench Model 220 are values you have to see to believe. Ask your Hickok distributor for a demonstration or contact us for more information.

SUMMER SPECIAL **\$124⁰⁰**

HICKOK

the value innovator

INSTRUMENTATION & CONTROLS DIVISION
THE HICKOK ELECTRICAL INSTRUMENT CO.
10514 Dupont Avenue • Cleveland, Ohio 44108
(216) 541-8060 • TWX: 810-421-8286

Circle 9 on reader service card

LETTERS

(continued from page 14)

in the interest of the public good?

Suppose a customer takes me to court on fabricated charges. Assuming I am innocent and no conviction takes place, who compensates me for the time and income I lost as a result of being unable to work? Who protects me from members of the public (and there are many) whose hobby it is to take advantage of servicemen? **THE POLICIES OF YOUR OFFICE ARE TOO ONE-SIDED!** Why don't you introduce an amendment to current licensing regulations that would force the complainant to compensate the technician for his lost time and income if no criminal acts have been proven beyond doubt?

Your recent proposal that would allow the customer to sue the serviceman because he could not keep an appointment is sheer lunacy. If this becomes law, one of two things will take place. One possibility is that the large majority of independent servicemen will leave New York City, thus leaving the major service companies in control. I need not mention that their service rates are often more than twice those of many independents, but, as in the past, this should not interest you. Have you never heard of dishonest service procedures among the major companies? For your information, it is widespread. **WHY HAVEN'T THEY BEEN LICENSED?**

The other alternative is that the independent technicians will change their style of business from repairing the television receiver in the customer's house whenever possible to a pickup and delivery service. This will have to be done so as not to be late for appointments made hours or even days ago. Neither the technician nor the customer would like this arrangement. Prices will inevitably have to be raised because of the increased expense of transit.

First and foremost, you must keep in mind the fact that it is impossible for a service technician (especially television) to predict accurately how long a service call will take. It could be as short as fifteen minutes, or as long as five hours, depending on the difficulty of the repair (which is almost always unpredictable). Therefore, when a service technician prepares his daily schedule of appointments, he can only estimate the part of the day he will *probably* be at each customer's house (early or late afternoon, etc.). No matter how well planned a daily work schedule is, a longer stay than anticipated at the home of one or more customers due to unexpected repair problems encountered on one of the many highly inferior television receivers presently on the market can totally destroy the rest of the day's schedule.

In conclusion, therefore, I would like you to consider the aforementioned reasons and how they would make your recent proposal (allowing consumers to sue servicemen for missed appointments in the already overcrowded court system) impractical, unfeasible, UNBEARABLE, economically disastrous and just plain stupid. **THERE IS NO NEED TO**

WAGE YOUR PERSONAL VENDETTA AGAINST SERVICE TECHNICIANS!! However, I am sure you will find that as you increase your attacks on the television and other service industries, you are only hurting the public, who you were appointed to protect. Service organizations will oppose you every step of the way with increased strength as you continue to rob the livelihood of their members. The majority of people in the television service industry (contrary to the picture you and your office have drawn) are honest and very hard working. The last thing they want to do is take advantage of the public, since respect and proper treatment of them keeps my fellow technicians and I in business.

JACK BERGER
JACK'S TV
Brooklyn, NY

COSMOS BURGLAR ALARMS

Regarding your article on COSMOS Burglar Alarms Part 1, appearing in the April issue of *Radio-Electronics*, I would like to see the following features added to your list of "requirements of the ideal burglar alarm."

The alarm should automatically reset after the Auto-Turnoff has occurred. If the alarm was falsely triggered, it would remain off after resetting. But if a door is left open, the alarm should reset after auto-turnoff and then trip again and remain on continuously until someone shuts off the power to the alarm or shuts the door.

It should have a time-delay turn-on connected through one door to allow the user to set the alarm inside the home and have 20-30 seconds to exit. It should also have the same delay when returning to enter the home through the selected door without triggering the alarm.


The control and electronic alarm generator should operate from the same 12 VDC battery supply.

There should be a means of tripping both a 12 VDC electronic alarm generator and a 120 VAC circuit to turn on lights by use of solid-state electronics, such as solid-state relays using LED triggering, rather than mechanical relays. The battery powered alarm should be backed up by a 120 VAC combination 12 VDC, 4A regulated and filtered charger/eliminator to charge a gelled cell or nickel cadmium type battery.

If these features are included in the circuitry, you truly have the "ideal burglar alarm system."

DAVID BLUM
Philadelphia, PA

R-E

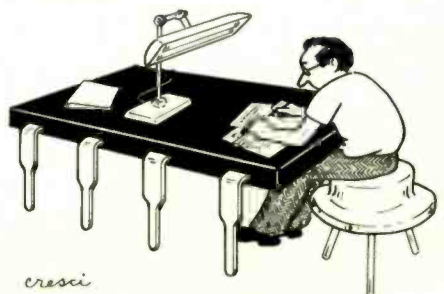

crisci

RALLY IV

DIGITAL STOPWATCH KIT

STURDY ANODIZED ALUMINUM CASE PHOTOGRAPHED

ACTUAL SIZE

ASSEMBLED \$99.95

PLUS \$2.95 P & H



- ★ BRIGHT 6 DIGIT LED DISPLAY 1/100 SEC. TO ONE HOUR
- ★ HIGH ACCURACY .003% CRYSTAL CONTROLLED
- ★ 4 FUNCTIONS STANDARD, SPLIT, RALLY AND SEQUENTIAL FOR SINGLE, MULTI-LEG, OR INTERRUPTED EVENTS
- ★ 24 HOUR TIMEKEEPING CAPABILITY
- ★ OPTIONAL NICADS AND CHARGER \$10.00 ADDITIONAL

\$ 69⁹⁵

SIMULATED DISPLAY

ONE EVENING ASSEMBLY

PLUS 2.95 POSTAGE AND HANDLING FLORIDA SALES ADD 4% TAX



ALPHA ELECTRONICS DEPT. 2

P.O. BOX 1005 MERRITT ISLAND FLA. 32952

305-636-6951



TELEPHONE IN YOUR 'ALPHAKIT' ORDER



DIGITAL MULTIMETER


NEW FEATURES AND PRICE

BRIGHT YELLOW 3 1/2 DIGIT DISPLAY

FEATURED COVER DECEMBER '74 POPULAR ELECTRONICS

AUTO ZERO AUTO POLARITY

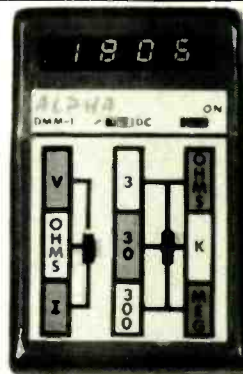- ★ FIVE FUNCTION DC VOLTS 1MV TO 600V, AC VOLTS 1MV TO 300V, DC CURRENT 1μA TO 2A, AC CURRENT 1μA TO 300MA, OHMS 1 OHM TO 6M
- ★ EXCEPTIONAL ACCURACY .1% OHMS & DC VOLTS, 1% AC/DC CURRENT & ACV
- ★ OPERATES ON 5 VOLTS, 4 AA NICADS
- ★ COMPLETE KIT OF PARTS LESS TEST LEADS & BATT.



KIT **79⁹⁵**

+2.95 P & H FLA. SALES ADD 4% TAX

MODEL DMM-1ER

Circle 10 on reader service card

The whole neighborhood wondered what Frank Mallon was up to in his workshop.

Word had it he was up to something mighty peculiar. And when he didn't show up for bowling practice one Wednesday night, the Wabash Cannonballs (that was the name of his neighborhood team) began to wonder, too.

So it was that a bunch of the boys decided to pay their "star" a visit, and talk him out of his workshop and back into action.

It didn't happen that way, though.

Matter of fact, it was Frank Mallon who talked the Wabash Cannonballs out of their bowling night and down into his workshop. What was it... what could be exciting enough to keep a bunch of ten-pin tigers from their favorite pastime? One of the most fascinating learn-at-home programs in the world, that's what!

Actually build and experiment with the new generation color TV in Bell & Howell Schools' fascinating learn-at-home program. It will help you develop new occupational skills as an electronics troubleshooter.

You'll set up your own electronics laboratory to learn first-hand, the technology behind such innovations as digital-display wristwatches and tiny pocket calculators.

In fact, as part of the program, you'll actually build and experiment with a 25" diagonal color TV incorporating digital features.

But most important of all will be the new skills you'll develop all along the way... the kind of skills that could lead you in exciting new directions. While we cannot offer assurance of income opportunities, once you've completed the program you can use your training:

1. To seek out a job in the electronics industry.
2. To upgrade your current job.
3. As a foundation for advanced programs in electronics.

Go exploring at home, in your spare time. No traveling to class. No lectures. No one looking over your shoulder.

Bell & Howell Schools wants to introduce you to the modern way to learn. It means you'll be able to develop new skills in your own home—on whatever days and hours you choose. So you don't have to give up your present job or paycheck just because you want to learn new occupational skills.

What's more, we believe that when you're exploring a field as fascinating as electronics, reading about it is just not enough.

That's why you'll get lots of "hands on" experience with some of the most impressive electronic training tools you've ever seen.

No electronics background necessary.

That's one of the advantages of this program. We start you off with the basics and help you work your way up, one step at a time. In fact, with your first lesson you receive a Lab Starter Kit to give you immediate working experience on equipment.

You build and perform exciting experiments with Bell & Howell's Electro-Lab®, an exclusive electronics training system.

First comes the design console. After you assemble it, you'll be able to set up and examine circuits without soldering.

Next, you'll put together a digital multimeter. This instrument measures voltage, current and resistance, and displays its findings in big, clear numbers like on a digital clock.

Then comes the solid-state "triggered sweep" oscilloscope. An instrument similar in principle to the kind used in hospital operating rooms to monitor heartbeats. You'll use it to analyze the "heartbeats" of tiny integrated circuits. The "triggered sweep" feature locks in signals for easier observation.

You'll build and work with Bell & Howell's new generation color TV... investigating digital features you've probably never seen before!

This 25" diagonal color TV has digital features that are likely to appear on all TV's of the future.

As you build it, you'll probe into the technology behind all-electronic tuning. And into the digital circuitry of channel numbers that appear right on the screen! You'll also build in a remarkable on-the-screen digital clock that will flash the time in hours, minutes and seconds.

And you'll program a special automatic channel selector to skip over "dead" channels and go directly to the channels of your choice.

You'll also gain a better understanding of the exceptional clarity of the Black Matrix picture tube, as well as a working knowledge of "state-of-the-art" integrated circuitry and the 100% solid-state chassis.

After building and experimenting with this TV, you'll be equipped with the kinds of skills that could put you ahead of the field in electronics know-how.

We try to give more personal attention than other learn-at-home programs.

1. Toll-free phone-in assistance. Should you ever run into a rough spot, we'll be there to help. While many schools make you mail in your questions, we have a toll-free line for questions that can't wait.

2. In-person "help sessions". These are held in 50 major cities at various times throughout the year, where you can talk shop with your instructors and fellow students.

So take a tip from Frank Mallon. Find out more about the first learn-at-home program that could stir up your neighborhood!

Mail this postage-paid card today for full details!

Taken for vocational purposes, this program is approved for Veterans' Benefits.

If card has been removed, write:

An Electronics Home Study School
DEVRY INSTITUTE OF TECHNOLOGY



ONE OF THE
BELL & HOWELL SCHOOLS

4141 Belmont, Chicago, Illinois 60641

"Electro-Lab®" is a registered trademark of the Bell & Howell Company.


696R3



On-screen digital clock




Channel numbers that flash on the screen

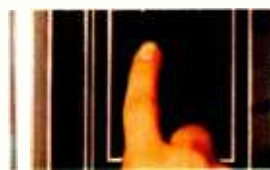

Automatic pre-set channel selector



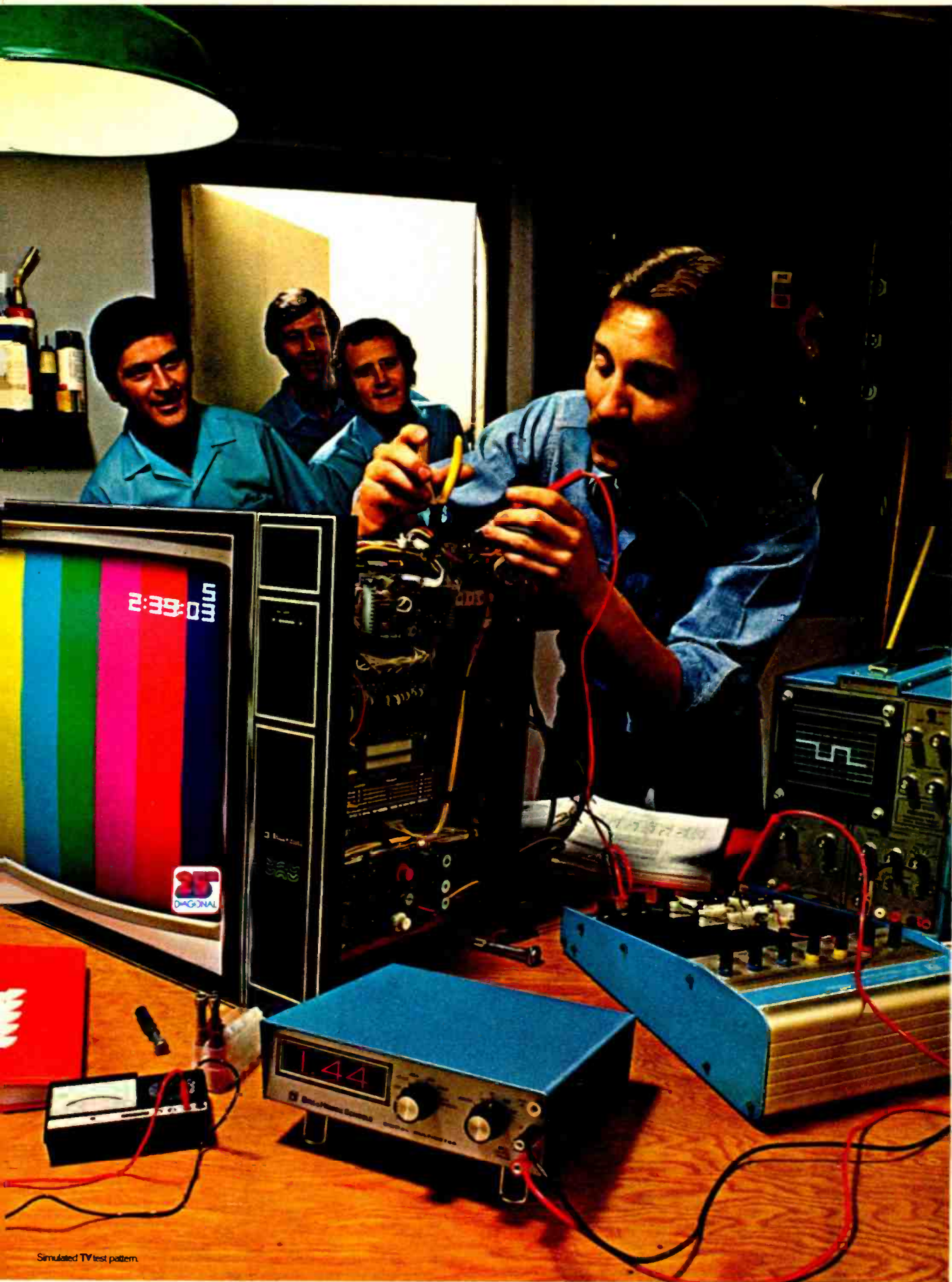

Simulated TV test pattern

Super quality SPRAY AIDS!



Imported line
from famed

KONTAKT CHEMIE

WEST GERMANY

16 formulations in handy aerosol cans that clean, protect and insulate in the repairing and service fields, and during electronic and electrical equipment production. Call or send for catalog and price information. Liberal quantity discounts.

**REGMO DATA
CORPORATION**

"Authorized
United
States
Distributors"

612/925-3800

6992 Oxford St., Mpls., MN 55426

Circle 11 on reader service card

equipment reports

B & K Model 520 Transistor Tester



Circle 107 on reader service card

THE B & K MODEL 520 IS AN INNOCENT-looking piece of test gear. Nice cabinet, dark panel with plain lettering, and three test leads with little blobs on the end. (Remember these blobs; they are something.) Inside the case, all kinds of things happen. This is a fully automatic transistor tester, in-circuit or out. Well, maybe not fully automatic; you do have to hook it up and turn it on. After that, things happen all by themselves.

The big problem in transistor testing has always been "Which connection is which?" These black beasts with three legs are all too often completely unidentified. To make a test, we must know which is which. The model 520 will tell you, and then test the transistor for the things we need to know. All you do is hook it up, and then move one switch. This will tell you whether it's good or not. Move another one, and it'll tell you what kind it is, and then read the leakage.

Those blobs are very special test leads. Each one has a tiny hook on the end, spring-loaded. The tips are so small that you can get into practically any transistor chassis and make connections to the leads. The hooks hold firmly, so that the rest of the job is "hands-off." For those chassis where they jammed the transistor tightly against the PC board, you can use the special probe with sharp pointed tips and get it from the wiring side.

The first test is for quality. All you have to do is move the TEST switch to each of its six positions. This changes the three connections around to every possible combination. The arrangement is shown by colored triangles, visible in a window on the panel. When you hit the right one, the

520 says "Beep!", and a LED on the panel lights up. This tells you that it's good and that it's either a PNP or NPN. No beep, no go; the transistor is either shorted or open.

This test can be made either in-circuit or out. The only time you'll have troubles in-circuit is in circuits where the transistor is shunted by a very small resistor or a big capacitor.

After this, leave the TEST switch in the correct position. Turning the FUNCTION switch to the left will tell you whether this transistor is silicon or germanium; two more LED's read this out. Turn the FUNCTION switch to the right, and it reads the leakage— I_{CES} or I_{RES} for bipolar transistors, and I_{DSS} for FET's. The meter scale is specially designed non-linear type, so that you can read a wide range of currents on a single scale.

There are four scales; small-signal silicon, power silicon, small-signal germanium and power germanium. The acceptable minimum leakage for each type is shown. Leakage in-circuit is not significant, due to shunting. Out-of-circuit leakage tests are definite. For out-of-circuit tests you can use the test leads or a socket on the panel.

The model 520 will test all bipolar transistors, including one that has been very hard to check—the Darlington-pair transistors in a single case. It will also check FET's, SCR's and diodes of any kind. Fine for matching diodes for AFC, etc.

For either in or out of circuit tests, you can identify the base arrangement of the transistor by looking at the little window. This shows the color of the lead connected to each element. This can be a very valuable feature, not only for transistor testing per se, but for identification of circuit test points that you need to know! The same test can be used to check diode rectifiers and detectors. It will identify the cathode lead on those unmarked diodes! This can be very handy. Video detector diode and similar types can be checked for leakage. This can cause a very fine "dog" symptom.

Quite by accident, I discovered another test. I was going through a small stereo amplifier, with a one-channel dead complaint. I hooked the 520 probes to an output transistor, and found that it would also check speakers! I could hear the "puttering" sound of the clock oscillator in the speaker. (Scared me for a minute!)

This one can turn out to be a real time-saver in any kind of solid-state work. Nowadays, that is definitely the name of the game.

R-E

(continued on page 24)

New 21" (diag.) Heathkit digital-design Color TV

Popular Electronics editors called the digital-design GR-2000 "the color TV of the future." Now you can enjoy the same technology and features in the new GR-2050 with the convenient, popular 21-inch picture tube.

On-screen electronic digital channel numbers—big, bright, bold, and easy to read, even from across the room. **On-screen electronic digital clock time**—low cost insurance against missed programs. In 12 or 24 hour format, 4 or 6 digits. **Silent, electronic, touch-tuning**, thanks to the combination VHF-UHF varactor tuner. No knobs to turn, nothing to wear out. Just touch to tune... on the front panel or the Remote. **Programmable digital counter/channel selector**—a computer-like programming board for you to pre-program any 16 stations, UHF or VHF, or both, in any order, even repeating if you wish. Touch the tune button and the counter silently sweeps up or down through all 16 channels, stopping when you release the button.

Exclusive fixed ten-section LC bandpass filter—does away with adjusted traps yet eliminates interference from adjacent channel, etc. And it never needs instrument alignment.


100% solid-state—with more ICs than any other set and a black negative matrix picture tube for brighter, more vivid pictures.

Easy to build with modular circuits. Easy to service with built-in digital dot generator, check-out meter, and slide-out service drawer. Build the GR-2050 TV of the future... Remote, \$89.95. Cabinets from \$119.95*



New 2½-digit Heathkit DMM—only \$79.95

Full function capability. Four overlapping AC & DC voltage & current ranges plus five resistance ranges with accuracy of 1% on DCV, 1.5% on ACV, 1.5% on AC & DC current, and 2% on resistance. Ranges: (full scale) DCV, 2, 20, 200, 1000V; ACV, 2, 20, 200, 700V rms (25 Hz to 10 kHz); DC current, 2, 20, 200, 2000 mA; AC current, 2, 20, 200, 2000 mA (25 Hz to 10 kHz); Ohms, 200, 2k, 20k, 200k, 2000k ohms. Lighted panel indicators show overrange, positive and negative DC voltages and current at a glance. All solid-state design uses IC circuitry for a clear non-blinking display with up-date every 16 msec. One megohm input impedance with overload protection on all ranges; automatic decimal positioning; isolated floating ground; universal banana jack inputs; 120 or 240 VAC operation; one circuit board for easy assembly; blue & white heavy-duty metal case. Kit IM-1212, \$79.95; Assembled SM-1212, \$125*.

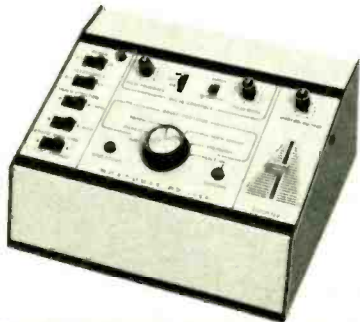

New Model Railroad Control Center/Power Supply provides acceleration and braking of unsurpassed realism plus power for two HO or N-gauge engines and accessories. Throttle slide control plus 5-position Brake switch (Run, Release, Normal, Quick-Service, Emergency), and Mode switch (Momentum or Direct). Adjustable pulse width and frequency allow accurate control at low speeds, eliminate "jack rabbit" starts. Voltage control optimizes for each engine. One circuit board; builds in two evenings. Kit RP-1065, \$79.95*.



New Digital Tachometer is faster than any meter-type tach. Numbers whirl by to show peak performance level your engine reaches. Great for monitoring best cruising RPM for your car, camper, boat (inboard or outboard), planes, cycles, mowers, tractors, even stationary engines. 2-digit electronic readout shows RPMs from 100 to 9900 in 100 RPM steps. For 4, 6, or 8 cyl., 4-cycle engines; 2, 3, or 4 cyl. 2-cycle engines; 2, 3, or 4-rotor Wankel engines; conventional, C-D, or factory electronic ignitions (12 v. neg. grd. only). Black die-cast case with bracket. Kit CI-1079, \$49.95*.



New Breakerless Ignition Adapter develops timing signal electronically so your car is timed correctly at all speeds and stays correct for longer periods. For use with C-D ignition systems only, it replaces the points of all pre-1975 GM V-8 and V-6 engines, and all AMC V-8s with external dwell adjustment. Unit mounts under hood; sensor mounts in distributor without removing points (switch returns engine to point timing when you wish). Operates from -37.2°C to +85°C. Easy to build. Kit CP-1051, \$44.95*.

HEATHKIT ELECTRONIC CENTERS—
Units of Schlumberger Products Corporation
Retail prices slightly higher.

ARIZ.: Phoenix; CALIF.: Anaheim, El Cerrito, Los Angeles, Pomona, Redwood City, San Diego (La Mesa), Woodland Hills; COLO.: Denver; CONN.: Hartford (Avon); FLA.: Miami (Hialeah), Tampa; GA.: Atlanta; ILL.: Chicago, Downers Grove; IND.: Indianapolis; KANSAS: Kansas City (Mission); KY.: Louisville; LA.: New Orleans (Kenner); MD.: Baltimore, Rockville; MASS.: Boston (Wellesley); MICH.: Detroit; MINN.: Minneapolis (Hopkins); MO.: St. Louis (Bridgeton); NEB.: Omaha; N.J.: Fair Lawn; N.Y.: Buffalo (Amherst), New York City, Jericho (L.I.), Rochester, White Plains; OHIO: Cincinnati (Woodlawn), Cleveland, Columbus, Toledo; PA.: Philadelphia, Pittsburgh; R.I.: Providence (Warwick); TEXAS: Dallas, Houston; VA.: Norfolk (Va. Beach); WASH.: Seattle; WIS.: Milwaukee.

Send for
FREE
Catalog



HEATH		Heath Company,	
Schlumberger		Dept. 20-08	
		Benton Harbor, MI 49022	
Please send my free 1975 Heathkit Catalog.			
NAME _____			
ADDRESS _____			
CITY _____		STATE _____	ZIP _____
<small>*PRICES ARE FACTORY MAIL ORDER, FOB</small>			
<small>PRICES & SPECIFICATIONS SUBJECT TO CHANGE WITHOUT NOTICE.</small>			
			CL-568

Circle 100 on reader service card

AUGUST 1975

NEW

from endeco



The Pencil Soldering Iron with Operating Light, 2 Heats and On/Off Switch

\$10.95
NET

Model 540S
Soldering Iron
Length 8 1/2"
Weight 2 oz.



- Light shows when it's on
- 2 heats—20w and 40w—for any job
- Ironclad tips for longer life
- Cool, unbreakable polycarbonate handle
- Burn-resistant neoprene cord
- Converts to a desoldering iron with low cost attachment

The Pencil Desoldering Iron with Operating Light, and On/Idle/Off Switch

\$15.95
NET

Model 510
Desoldering Iron | Length 8 1/2"
Weight 3 1/2 oz.



- Light shows when it's on
- Operates at 40w; idles at 20w for longer tip life
- 8 tip sizes available to handle any job
- Cool, unbreakable polycarbonate handle
- Burn-resistant neoprene cord
- Exclusive new bracket insures alignment, prevents damage

New kits also available!

- Soldering Kits • Desoldering Kits
- Soldering/Desoldering Kits

See your distributor or write



5127 EAST 65TH ST.
INDIANAPOLIS,
INDIANA 46220
PHONE 317 / 251-1231


enterprise
development
corporation

Circle 13 on reader service card

EQUIPMENT REPORTS

(continued from page 22)

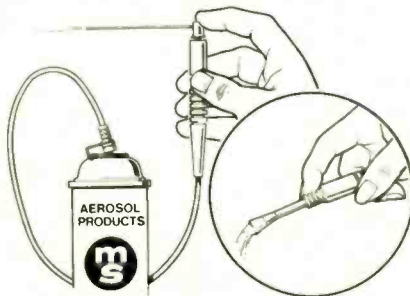Miller-Stephenson Chem. Co. Products With Cobra Extension Nozzle



Circle 108 on reader service card

THE MILLER-STEPHENSON CHEMICAL CO. (Box 628, Danbury, CT 06810) has come up with some goodies for the TV-radio technicians, including one really ingenious, and very handy, new device. This company makes a long line of chemical compounds for industrial use, of all kinds, even "canned air" (for cleaning delicate instruments, etc.) and a static eliminator, *En-Stat*, plus a cleaner for plastics, metal and glass.

The goodies include *Contact Re-Nu*, a very effective contact cleaner. There is a magnetic head cleaner for all kinds of tape-heads—from computers down to 8-track stereo's. There is also a *Quik-Freeze* spray for those thermal intermittents, and a pure *Freon Degreaser* for cleaning up those filthy PC boards. There are others, including a flux-remover for PC boards that would be useful either in service or production work. This comes in two strengths—normal and heavy duty for those really dirty jobs.

The new device is their handy *Cobra* extension-nozzle kit. This has a small plastic tube, about 30 inches long, and a handle about the size of a felt-tip pen. A standard spray-nozzle with a 6-inch tube can be slipped over this. You hook it on the spray-can by pushing the coupler over the little metal pipe you see when you pull the nozzle that comes with the can off. Special latches hold it in place. To turn the *Cobra* on, just push it to one side and latch it.

To spray, just push the end of the *Cobra* handle to one side. The small size plus the long tubing makes it very easy to get into tight places in TV sets. I cleaned up a very dirty CONTRAST control in the tuner mounting assembly of an old set; it was so well concealed that I could barely see the thing.

For cleaning up spots on PC boards so that you can see your work, read color codes, etc., or for cleaning entire boards, there is a pure Freon Degreaser compound. This can be used with the *Cobra* extension nozzle. A special brush-handle can be plugged onto the *Cobra* handle. This is how; by pushing the handle, the solvent can be applied as needed while the brush loosens caked deposits and dirt. I cleaned up a couple of sets that were really dirty, and the boards looked like new. For cases where you suspect leakage across a board in a sensitive area, this is

a dandy.

These products can be a real time-saver for the professional radio-TV and electronics man. They come in 16-ounce cans, which last a long time. They're available at many radio-TV supply houses, especially the Industrial Electronics suppliers. **R-E**

Heathkit IO-4530 10-MHz Triggered-Sweep Oscilloscope



Circle 100 on reader service card

IT'S TIME TO REPLACE YOUR VENERABLE but time-worn multi-tube oscilloscope with a more reliable solid state instrument. If your scope is devoted to TV servicing or other limited bandwidth lab work, the new Heathkit 4530 is a good candidate.

For \$300 a single-trace 10-MHz 3-dB bandwidth scope can be assembled with good sensitivity and a choice of XY operation or calibrated, automatically triggered horizontal sweep. The 4530 has a device complement of 44 transistors, 22 diodes, and 9 integrated circuits.

The vertical or Y channel input feeds an attenuator with a parallel, 1 megohm-40pF input impedance. A series of ceramic trimmer capacitors compensate the attenuator over each decade of its 10mV/cm to 20 V/cm range. Following the attenuator, an FET source follower is used as the vertical amplifier input device. The high gate impedance of the follower prevents loading and inaccuracies of the input attenuator. There are a total of 11 vertical gain positions in a 1-2-5 sequence. DC coupling is used over the entire input level range. The AC coupling switch position rolls off the response 3 dB at 2 Hz.

The horizontal X amplifier has a 1-MHz 3-dB bandwidth with a sensitivity range of 0.02 to 2 V/cm in three decade steps. A compensated attenuator is also used in the horizontal channel with a similar 1 megohm-40 pF input impedance.

One of the strongest features of the 4530 is its modern triggered sweep. Trigger inputs are conditioned by filtering options and then switch a 741 op-amp discrete FET current source combination to generate an accurate linear sweep. A transistor switch discharges the time-base capacitor to ground during retrace, and the constant current source charges it negatively during trace. TTL 7400 gates and a 72710 voltage comparator are set up to trigger in the automatic mode at zero crossings of the sync input waveform. Trace scan begins on either the positive or negative slope of the sync waveform by inserting the right number of

(continued on page 26)


LIVE IN THE WORLD OF TOMORROW... TODAY!

And our FREE 180 PAGE CATALOG is packed with exciting and unusual values in electronic, hobby and science items — plus 4,500 finds for fun, study or profit... for every member of the family.

A BETTER LIFE STARTS HERE

4 1/4" ASTRONOMICAL TELESCOPE

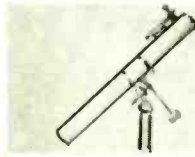See moon craters, rings of Saturn, double stars. New equatorial mount. f/10, 1/4 wave mirror (Pyrex®). Gives theoretical limit of resolution. Rack & pinion focusing. Aluminum tube, 6X finder. 1" F.L. 45X Kellner achromatic eyepiece and Barlow lens to double & triple power up to 135X. Free Star Chart plus 2 Books.



- Stock No. 85,105EH... (Shipping Wt. 42 lbs.) \$149.50 FOB
- 4 1/4" WITH CLOCK DRIVE #85,107EH \$189.50 FOB
- 6" REFLECTOR TELESCOPE (48X to 360X) #85,187EH \$249.50 FOB
- 6" WITH CLOCK DRIVE #85,086EM \$285.00 FOB
- 3" DELUXE REFLECTOR (30 to 90X) #80,162EM \$ 79.95 Ppd.
- STANDARD 3" REFLECTOR #85,240EM \$ 49.95 Ppd.

AM RADIO FITS IN/ON YOUR EAR!

Wear it inconspicuously everywhere. Listen as you work (lawn, yard, office), watch (game, beach) or wait. Instant music, news, sports. No gimmick, our 6/10 oz. Technological wonder has integrated circuit, 11 transistors, patented ferrite antenna/tuner/volume dial. Uses normal silver oxide hearing aid batt. (incl) for approx. 100 hrs. playing. New batt. to slip in avail. at drug stores (about 50c). No lengthy wires, bulky cases, or power-packs!



Stock No. 42,275 EH \$14.95 Ppd.

NEW VISUAL EFFECTS PROJECTOR

Revolutionary 2-WHEEL set lets you create wild far-out visual effects with no worry about nuts & bolts—you change programming as fast as you drop in a new disc! Attach any 35mm slide you have, or use your 35mm camera to program. Make rotating images, bleemer effects, Kaleidoscopic patterns, 3-D plus mind-blowing Moiré effects right on your screen. Incl 2 internal drive motors, 3-way Kaleidoscope Lens, Hexidoscope, Lenticular Wheel, Moiré Wheel, instrs.



Stock No. 72,071EH \$99.95 Ppd.


WHICH ARE YOUR CRITICAL DAYS?

Can Bio-rhythm tell you? We're not sure, but we're told that vast mood shifts are caused by your body's internal Time Clock whose rhythms can be charted ahead to possibly warn you of "critical" days. Some are great, some blah. Maybe it's your physical, emotional & intellectual rhythms converging at the right or wrong time. Compute your cycles with our Bio-rhythm kit and judge for yourself. Incl Charting kit, metal Dialgraf Calc. instrs.



Stock No. 71,949 \$11.50 Ppd.
1 YR. PERSONALIZED REPORT — BY COMPUTER \$15.95 Ppd.
Stock No. 19,200 (Send Birthdate)

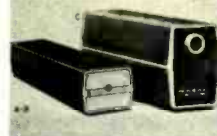WHEN YOU COME TO PHILADELPHIA BE SURE TO SEE
FREE BICENTENNIAL LIGHT SHOW
IN BARRINGTON, N. J. ONLY 10 MINUTES AWAY AT
EDMUND FACTORY STORE



He-Ne LASERS... \$115.00 up!

Top quality lasers feature TEM₀₀ mode, internal mirror plasma tubes w/10,000 hr. life, self-starting cold aluminum cathodes, low noise & ripple, guaranteed output, power stability and more for demanding lab work. 18-mo. mfr. wty. 115v AC

- (A) 0.5mW... 0.88 Beam Dia., 1 mRad Diverg. #79,070 EH (2.6x8.5x14.8") \$115.00 Ppd.
- (B) 1.0mW... (as above) #79,073 EH \$150.00 Ppd.
- (C) 4.0mW... 0.8 Beam Dia., 1.1 mRad Diverg. #79,079 EH (3.9x5.5x15.6") \$485.00 Ppd.



QUALITY DETECTOR UNDER \$40

New Edmund developed, fully transistorized BFO unit capable of locating quarter at 18"—powerful 6 trans. oscillator-amplifier circuit. Easily compares to others priced 50% higher! Aluminum pole and housing—not plastic! 6" waterproof search coil (Faraday shielded to elim. outside interference); long 50 hr battery (9V) life; powerful 2" speaker; 1-knob on-off tune control. Perfect balance; lightweight (2 lb). Great buy!

Stock No. 80,222EH \$ 39.95 Ppd.
Deluxe Unit w/Earphones, Meter No. 80,134EM (11" Coil) \$169.00 Ppd.



SOLAR ENERGY CUBE!

Unique demonstrator dramatically shows how sunlight converts to kinetic energy. Clear plastic Solar Energy Cube placed in the sun with its 3 highly efficient silicon solar cells powers the motor to whirl the propeller! Unit actually produces 1.5v DC, 825ma. Same cells found in our mighty panels. Speed directly related to sunlight available. Nothing to wear out! Great for executives, hobbyists, teachers.

No. 42,287EH... (4X4X4") \$19.95 Ppd.



NEW! KIRLIAN PHOTOGRAPHY KIT!

Experiment in the fascinating new field of "Kirlian electrophotography"—images obtained on film without camera or lens by direct recording of electric charge transmitted by animate & inanimate objects. Each "aura" differs—animate aura said to change corresponding to physical changes. Kit incl portable darkroom, double transformer isolated from power source; instructions.


- No. 71,938 EH \$49.95 Ppd.
- "HIGH VOLTAGE PHOTOGRAPHY" by H. S. Dakin No. 9129 EH (60-PG.) PPBK BK.) \$5.00 Ppd.
- DELUXE KIRLIAN PHOTOGRAPHY SET No. 72,053 EH \$399.00 Ppd.



KNOW YOUR ALPHA FROM THETA!

For greater relaxation, concentration, listen to your Alpha-Theta brainwaves. Ultra-sensitive electrode head-band slips on/off in seconds—eliminates need for messy creams, etc. Atch'd to amplifier, filters brainwaves, signals beep for ea. Alpha or Theta wave passed. Monitoring button simulates Alpha sound; audio & visual (L.E.D.) feedback. Reliable, easy-to-use unit—comparable to costlier models. Completely safe. Comprehensive instruction booklet.

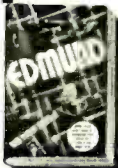- No. 1635 EH (8x3x4"; 24 oz.) \$134.50 Ppd.
- LOW COST "STARTER" UNIT No. 71,809 EH \$55.00 Ppd.
- DELUXE "ON" TIME MONITOR MEASURES & RECORDS % No. 1652 EH \$349.50 Ppd.



MAIL COUPON FOR GIANT FREE CATALOG!

180 PAGES • MORE THAN 4500 UNUSUAL BARGAINS

Completely new 1975 edition. New items, categories, illustrations. Dozens of electrical and electromagnetic parts, accessories. Enormous selection of Astronomical Telescopes. Unique lighting and ecological items. Microscopes, Binoculars, Magnifiers, Magnets, Lenses, Prisms. Hard-to-get surplus bargains. Ingenious scientific tools. 1000's of components.

EDMUND SCIENTIFIC CO.
300 Edscorp Building, Barrington, N.J. 08007
Please rush Free Giant Catalog "EH".

Name _____
Address _____
City _____ State _____ Zip _____



COMPLETE AND MAIL WITH CHECK, M. O. OR CHARGE NO.

EDMUND SCIENTIFIC CO. 300 Edscorp Building, Barrington, N.J. 08007

How Many	Stock No.	Description	Price Each	Total
<input type="checkbox"/>		PLEASE SEND GIANT FREE CATALOG "EH"		
<input type="checkbox"/>		Charge my BankAmericard*		
<input type="checkbox"/>		Charge my Master Charge*		
Add Handling Chg.: \$1.00, Orders Under \$5.00 50¢, Orders Over \$5.00				
Interbank No. _____				
My Card No. Is _____				
I enclose <input type="checkbox"/> check <input type="checkbox"/> money order for TOTAL \$ _____				

Card No. _____ Signature _____

Card Expiration Date _____
30-DAY MONEY-BACK GUARANTEE. You must be satisfied or return any purchase in 30 days for full refund. *\$15.00 minimum

Name _____
Address _____
City _____ State _____ Zip _____

EQUIPMENT REPORTS

(continued from page 24)

inversions in the signal path. The sync can be derived from the vertical input channel, through the external trigger connector, or from the 60-Hz line from a tap on a power transformer winding.

Like its big brothers, in the automatic trigger mode the 4530 displays a base line in the absence of a trigger signal. If the trigger source is idle, the automatic baseline generator initiates sweep at a 40-Hz rate. To synchronize below 40 Hz, the trigger level switch is advanced from its detented position selecting the NORMAL sync mode. Auto-baseline circuitry is disabled and the trigger level is continuously variable over the range of -0.6 to $+0.6$ volts. As you might guess, these limits are determined by forward-biased silicon diode junctions. Sweep speed range is from 0.2 sec/cm to 200 ns/cm in seven decade steps. The 5X magnifier pull-out switch increases the gain of the horizontal amplifier five times by reducing the emitter resistance of the output differential cascode amplifier. DC, AC, and TV sync coupling is selected by a front panel switch. The TV position inserts an integration network to filter out the vertical sync. Video signals can then be locked in easily at a frame or field rate.

Regulated low voltage power supplies use a 4501 dual regulator IC for plus and minus 15 volts. Zener diodes drop these potentials to lower 5- and 12-volt sources for the TTL logic and comparators. The

CRT voltages are all derived from a 1375-volt Zener stack.

Kit construction went smoothly. About half of twenty plus hours were spent putting together the main circuit board. It holds everything but the high voltage power supply and the front panel components. The three large vertical gain, horizontal gain, and sweep speed rotary switches are printed circuit types and mount directly on the main board without cluttered wiring. The low-capacitance switch inputs are brought out on non circuit board terminals so they can be routed to the input connectors by non-deviuous routes.

Separate assembly and operating manuals are included with extensive calibration and troubleshooting procedures. Detailed flow charts attempt to cover the majority of circuit problems. Our sample did not trigger horizontally when first completed. The trouble was traced to a defective holdoff monostable IC. A second fault impaired the retrace blanking. This problem was caused by an intermittent Zener diode. It is to Heath's credit that the only malfunctions in such a complex kit were due to two easily replaced components and not to a miswiring or a design related problem.

The scope appearance is quite professional and it is obvious it was meant to emulate well-known top drawer lab equipment. BNC connectors are used for the X, Y, and trigger inputs. An 8×10 cm graticule and CRT window cover the face of the 5 inch round CRT. About half of the four corner reticle squares are not

scanned because of the tube shape. The CRT is surrounded by a substantial shield as well as mu-metal wrapping around the gun.

The IO-4530 measures $6.937 \times 12.8 \times 19.2$ inches ($17.7 \times 32.5 \times 49$ cm) not including its detented dual-purpose carrying and support handle. It weighs 22.5 pounds (10.2 Kg). Power consumption is 65 watts from 120 or 240 volt nominal supplies.

The new Heath scope will be a welcome addition to the low budgeted service or circuit development organization by bringing a good deal of the feel of a high grade lab instrument within its grasp. It does not have the high brightness or VHF bandwidth of a \$3000 Tektronix or Hewlett Packard scope, but it does have the same basic functional control philosophy with solid no-nonsense operating ease. I think Heath has been successful with the IO-4530 by providing the most instrument per dollar they know how. **R-E**



Automatic transistor tester works in-circuit when others can't



BK PRECISION
520 Dynapeak™
\$150.00

TESTS IN ONLY 9 SECONDS Tests diodes, SCR's and unijunctions, too. Avoids time wasting unsoldering of good transistors that tested bad in circuit and then good out-of-circuit because of erroneous testing. B&K-Precision 520 Dynapeak™ even tests automatically in-circuit with shunts of 10 ohms or 50 mfd. Random lead connection; turn the switch—the rest is automatic: Pulsating audio tone and LED indicates good device; PNP/NPN, Ge/Si shown by LED. No-charts leakage tests. Tests transistor action, not just junction or diode characteristics. Write today!

BK PRECISION
PRODUCTS OF DYNASCAN

1801 W. Belle Plaine Avenue • Chicago, IL 60613

Circle 14 on reader service card

Portable Digital Multimeter at an Analog Price

MODEL 280
\$99⁹⁵



Enjoy the benefits of auto-polarity digital read-out plus full overload protection and high-low power ohms for accurate tests in solid-state circuits.

Accuracy better than analog VOM's!

22 RANGES

Reads in decades: AC and DC volts and mA, 1-1000; ohms, 100-10 meg. Resolution: 1mV, 1mA, 0.1 ohm.

Accuracy: DC typically $\pm 1\%$ F.S.; AC and ohms typically $\pm 2\%$ F.S. except $\pm 2.5\%$ on highest range. Uses "C" cells. Optional AC adapter/charger.


In stock at your local distributor

BK PRECISION
PRODUCTS OF DYNASCAN

1801 W. Belle Plaine Avenue Chicago, IL 60613

Circle 15 on reader service card

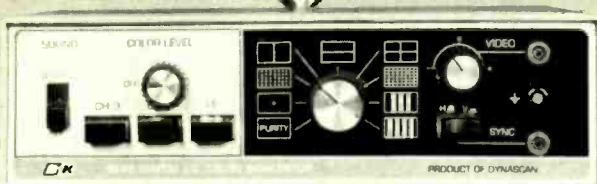
Color Generator doubles as portable Analyst



MODEL 1248 \$175

Now you can localize TV problems at the customer's location without bench equipment! Service CCTV and Videotape too! The 1248 is a rock-steady nine-pattern IC color generator—with RF, IF, video, sync and sound outputs that let you substitute signals to find the problem. Digitally generated patterns. Crystal-controlled IF and RF outputs. With carrying case; dependable AC operation.

In stock at your distributor.

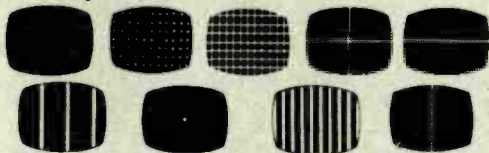

B+K PRECISION

PRODUCTS OF DYNASCAN
1801 W. Belle Plaine Avenue • Chicago, IL 60613

Circle 16 on reader service card

10MHz 5" scope with easier calibration and voltage measurement



Model 1465 \$428

Here are some B&K extra touches. Besides DC-to-10MHz bandwidth, triggered sweep, automatic sync, 16.6mV/cm vertical sensitivity, DC-coupled amplifier and front-panel Vectorscope capability, Model 1465 also has 5X magnification to increase sweep speed to 0.2usec/cm for complex waveform analysis. And Cali-Brain®, which collapses horizontal sweep to let you measure instantaneous peak-to-peak voltage easily while simultaneously displaying the full-scale voltage range. Now in stock at your local distributor or write Dynascan.

B+K PRECISION

PRODUCTS OF DYNASCAN
1801 W. Belle Plaine Ave.
Chicago, IL 60613 • (312) 327-7270

Circle 17 on reader service card

Reliable dual-trace scope useful to 30MHz.



MODEL 1472 \$599

We nominally rate the 1472 at 15MHz (−3dB), but it easily syncs and displays a 30MHz signal with sure triggering. It automatically selects chopped or alternate trace display to avoid flickering at any sweep speed . . . so even with 11 sensitivity ranges from 10mV to 20V/cm and 19 sweep ranges from 0.5μSEC to 0.5SEC/cm, it's easier to use than most scopes. The 1472 has 24nSEC risetime and can be used in X-Y mode with matched phase-shift and sensitivity inputs.


In stock at your distributor.

B+K PRECISION

PRODUCTS OF DYNASCAN
1801 W. Belle Plaine Avenue • Chicago, IL 60613

Circle 18 on reader service card

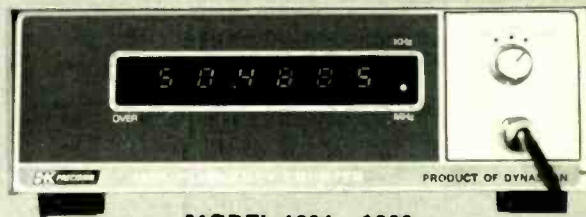Affordable frequency counter for jobs that have always needed one



MODEL 1801 \$230

With a good autoranging frequency counter you can watch oscillator adjustments, monitor RF and audio frequencies precisely, do fast production testing, check critical countdown chains, calibrate signal generators, check pull-in range of AFT circuits and CB frequencies accurately. The 1801 is good because its accuracy is typically better than 10PPM; it typically reads 10Hz-60MHz and is guaranteed to read 20Hz-40MHz. It's automatic—there's just one control and gate times, decimal points and scalings are automatically selected for best speed and accuracy. And it's fast—the display is refreshed up to 5 times per second.

In stock at your distributor.

B+K PRECISION

PRODUCTS OF DYNASCAN
1801 W. Belle Plaine Avenue Chicago, IL 60613

Circle 19 on reader service card

If you've ever said...

"There must be a better

Send for a free Career Guidance Booklet that could start you on the road to success in a rewarding new career.

It happens to all of us, sooner or later. No matter what kind of job we have.

One day, it suddenly strikes home that we're going to have to work for a living, the rest of our lives. And most of us are horrified at the thought of forever being locked into the jobs we now hold.

"Surely," we tell ourselves, "there must be a way to get more satisfaction out of working. Surely, there must be a way to find a job that's more rewarding."

"Surely," in other words, "there must be a better way to earn a living!"

If you, too, have been thinking these same thoughts, you'll find one of our free Career Guidance Booklets very helpful at this time. We invite you to send for one.

Your free booklet will describe the opportunities for higher income and greater job security you might expect in one of the career fields listed on card or coupon. It will also explain why ICS can prepare you for this new career field...right in your own home...in your spare time...regardless of your education or past experience.

Of course, no school — not even ICS — can guar-



way to earn a living..”

antee you a better job. We can't make you smarter than you already are, and we can't make you ambitious if you're lazy.

But ICS *can* give you the first-rate training you need — especially if you're interested in one of the growing careers where ICS concentrates its training. Like Electrician. Engineer. Auto Mechanic. TV Repairman. Air Conditioning Serviceman. (Check your choice on card or coupon.)

Along with your Career Guidance Booklet, you'll also receive a free Demonstration Lesson that lets you see for yourself why preparing for a more rewarding career — the ICS way — may be a lot easier than you think.

Please bear in mind that ICS has a long and distinguished record of success. In fact, since 1890, millions of men and women around the world have turned to ICS for career training.

More than 70 of America's largest 100 corporations (including Ford, U.S. Steel, Mobil Oil, GE and RCA) use ICS training for their own employees.

Earn a College Degree

You could even earn a college degree from the ICS Center for Degree Studies, which is authorized by the Pennsylvania Department of Education to grant the Associate in Specialized Business Degree in Accounting and Business Management.

These are growing career fields in which job openings are expected to increase in the years ahead.

ICS Associate Degree programs are the basic equivalent of most four-year college programs in Accounting or Business Management — minus liberal arts courses and electives. If you already have some college education, you may be able to receive advanced standing toward your degree. With a degree from ICS, you'll be able to apply with pride for jobs that call for college training.

An Ideal Way to Learn

Whether you choose a degree program or a non-degree program, as an ICS student, you study at home, on your own schedule. You waste no time traveling to and from class. And you never have to miss a paycheck.

But you're never alone. Skilled instructors are

always ready to help you.

If you ever have doubts or problems or just want to talk to an instructor, you can call ICS from anywhere in the continental United States, day or night, using our special toll-free Dial-a-Question® service.

So if you want more — more money, more security, more day-to-day satisfaction and more future — our free Career Guidance Booklet and free Demonstration Lesson can help you get started in the right direction. Just check the box next to the field that interests you most and mail the postpaid card or coupon today. There's no obligation.

Remember, it's your life. You might as well make the most of it.

© 1975 Intext, Inc.

ICS	International Correspondence Schools	B
Scranton, Pa. 18515	XA812G	
Please mail me the Free Career Guidance Booklet and Free Demonstration Lesson for the field I have checked below. I understand I am under no obligation.		
<input type="checkbox"/> Electrician	<input type="checkbox"/> Automotive Mechanics	
<input type="checkbox"/> Engineering	<input type="checkbox"/> Business Management	
<input type="checkbox"/> Accounting	<input type="checkbox"/> Civil Engineering	
<input type="checkbox"/> Drafting	<input type="checkbox"/> Interior Decorating	
<input type="checkbox"/> Electronics Technician	<input type="checkbox"/> Restaurant/Club Mgt.	
<input type="checkbox"/> TV Service and Repair	<input type="checkbox"/> Income Tax	
<input type="checkbox"/> Airline/Travel	<input type="checkbox"/> Motel/Hotel Management	
<input type="checkbox"/> Surveying and Mapping	<input type="checkbox"/> Mechanical Engineering	
<input type="checkbox"/> Construction Electrician	<input type="checkbox"/> ICS High School Diploma	
<input type="checkbox"/> Diesel Mechanic	<input type="checkbox"/> High School Equivalency	
<input type="checkbox"/> Air Conditioning and Refrigeration		
Name _____	Age _____	
Address _____		
City _____	State _____	Zip _____
Telephone _____		
Earn A College Degree		
The ICS Center for Degree Studies is authorized by the Pennsylvania Department of Education to offer college programs at home leading to Associate in Specialized Business Degrees. For more information at no cost or obligation, check the degree of your choice.		
<input type="checkbox"/> Accounting Degree		
<input type="checkbox"/> Business Management Degree		
<small>Canadian residents use Scranton, Pa. address for service from ICS Canadian, Ltd. In Hawaii: 931 University Ave., Honolulu, Hawaii 96814.</small>		

APPROVED FOR VETERANS' TRAINING. APPROVED FOR FEDERALLY INSURED STUDENT LOANS. ACCREDITED MEMBER NATIONAL HOME STUDY COUNCIL.

We'll give you a treat if you pick up the tab.



This year—20 bonus tabs for color picture tubes.

Sav-a-Tab '75 is now under way, so we hope you've been saving Sylvania tube box tabs all along—the tabs marked "WALTHAM" at the end of each box.

And this year we're adding a new dimension. One serial number label from a color-tube carton will earn you the equivalent of 20 receiving tube tabs. (You'll find the label on the upper left-hand

corner of every color-tube carton.)

Sav-a-Tab '75 ends at midnight, Nov. 30, so get your catalog of treats right now. See your local Sylvania distributor or write Sylvania Award Headquarters, P.O. Box 1000, Fenton, Missouri 63026.

GTE SYLVANIA

Giant LCD Clock



Two-inch high numerals sandwiched between two clear glass panels makes this liquid crystal display a magical mystery and the clock a real conversation piece

by **GEORGE J. WHALEN**

BLACKSTONE AND HOUDINI, THE MASTER illusionists, would have been baffled by the high-technology legerdemain that makes the Magi-clock work! On a clear panel, transparent as a sheet of glass, the time of day mysteriously appears in two-inch high whitish numerals. Two digits accurately report the hours and two digits mark the passage of the minutes. Yet, there is no sign of wires or connections to the "floating" numerals! While the Magi-clock *tells* the time, it keeps the way it works a *secret*.

In just one enjoyable evening, you can assemble this extraordinary time-keeping conversation piece. Construction is made easy by the use of a single LSI integrated circuit, requiring but a handful of external components, and a large liquid crystal display that plugs into a mating connector on the printed circuit board. Powered directly from the AC line without bulky, heavy transformers, the Magi-clock is compact and light enough to build into any enclosure you can conceive of. And, its accuracy is as good as the closely-controlled 60-Hz power line frequency. The line frequency is held to $\pm .02$ Hz, $-.05$ Hz. Thus, the Magi-clock can deliver better than 0.1% accuracy over time periods up

to an hour. Long time accuracy is maintained because accumulated cycles-per-second errors are periodically corrected by the power company.

The time-keeping heart of the Magi-clock is a type C1200 monolithic MOS integrated circuit manufactured by LSI Computer Systems, Inc. (see Fig. 1). Time set, logic, dividing for seconds, minutes, and hours, seven-segment decoding, and display drivers and switches, are all built into this unique "chip." Circuit functions use MOS p-channel enhancement and ion-implanted depletion mode devices.

The liquid-crystal display panel (LCD) is an optically-transparent "sandwich" that has many components that don't meet the eye at first glance. Figure 2-a reveals its inner secrets. Two glass panels (called front-plane and back-plane) make up the front and back of this device. The inner faces of the two panels are thin-film metallized with tin oxide or indium oxide. On one, the film has been deposited to produce the seven-segment patterns of the numerals, as well as a colon and starburst, together with thin-film metal conductors that lead down to a "connector" edge. Thus, each film-metallized segment is individu-

ally addressable (Fig. 2-b). The other glass panel is metallized over its entire inner surface.

The two metallized glass panels don't touch. They are separated by a normally transparent fluid called a *nematic liquid*.^{*} A seal about the outer edge keeps the panels separated and prevents the liquid from leaking out. The assembled LCD appears to be transparent when not excited, since the metallizing film on the glass plates and the nematic liquid have about the same refraction index.

The LCD "sandwich" is a *field-effect device*. (Fig. 3.) Applying an electric field between the back metallized panel and any front metallized segment causes a molecular reorganization of the "crystalline" structure of the nematic liquid. Normally,

^{*}An LCD's performance is based on the behavior of certain organic chemicals which simultaneously exhibit both liquid and crystal properties. These *nematic liquids* are transparent in the liquid state until their thread-like molecules are disturbed by the presence of an electrical field—a phenomenon discovered in 1888, but regarded as a laboratory curiosity until late in the 1950's when investigations of practical uses began.

these long, cigar-shaped molecules are in a parallel alignment and are free to slide past each other. In this unperturbed state, the crystal molecules don't scatter light, and so, the liquid appears transparent. However, when disturbed by an electric field, the well-ordered structure is upset; molecules organize randomly, thus scattering light passing through the LCD sandwich. This causes the affected area of the LCD to turn milky white. Thus, the LCD, when properly "addressed" by the output of the clock IC, provides an easily seen display of time by *scattering light*, rather than emitting light, as in other forms of digital readout devices.

The process of cycling the transmissivity of the crystals produces *dynamic scattering*, so that the LCD's light transmission properties at any instant depend upon the voltage applied between the front-plane and back-plane electrodes.

How it works

Components external to the clock IC are shown in Fig. 4. AC power is applied to a voltage divider (R1-R4), that supplies an 11-volt RMS 60-Hz count input to pin 22 of the IC, provides the input to a full-wave rectifier (D1-D4) and filter (C1) to supply DC operating potential to the IC, and supplies a nominal 40-volt RMS potential for excitation of the LCD segments, with transient over-voltage protection afforded by Zener diodes D5 and D6.

Referring now to Fig. 1 for events going on inside the IC; the 60-Hz line frequency signal goes from pin 22 to the TIMING CHAIN, where it is divided several times to generate binary coded decimal (BCD) equivalents of seconds, minutes and hours pulses that are fed to the SEVEN-SEGMENT MATRIX to be decoded. Outputs from the matrix go to the HIGH-VOLTAGE DRIVERS that control the ANALOG SWITCHES. The SEVEN-SEGMENT MATRIX is a complex decoder/driver. Here, the inputs from the timing chain, which are in the form of four BCD inputs for the first significant digit of the minute display, are decoded to excite the right number segments. For the second significant digit of the minute display, only three BCD inputs are needed, for here we are only counting from zero thru five, rather than from 0 to 9 as in the first significant digit. BCD outputs from the hours section of the timing chain are similarly decoded by the matrix.

The TIME SET GENERATOR receives a 2-Hz input from the TIMING CHAIN, and, depending on whether you close MINUTE SET switch S2 or HOUR SET switch S1, it generates a signal that advances the minutes or hours portion of the display at a 2-Hz rate.

The *carry inhibit* signal from the TIME SET GENERATOR serves a very important function. It makes sure that setting the minutes does not affect the hours display and vice versa. In other words, the minutes display goes to 00 after it reaches 59, but does not advance the hours setting. Simi-


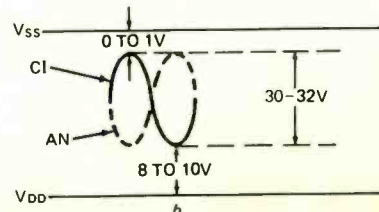
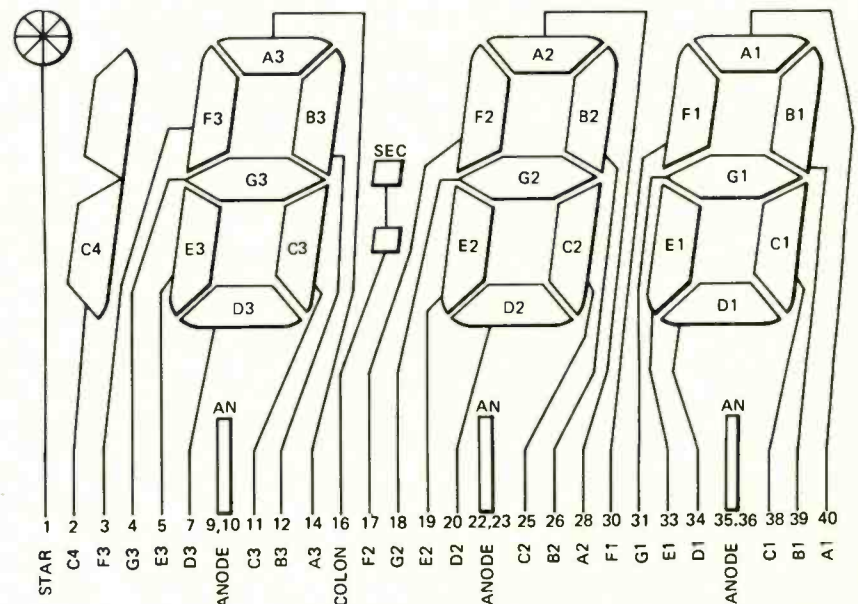
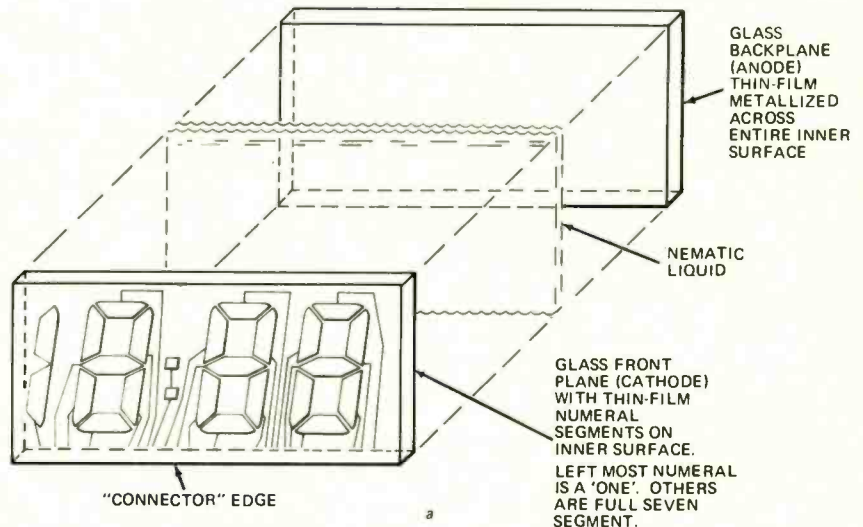
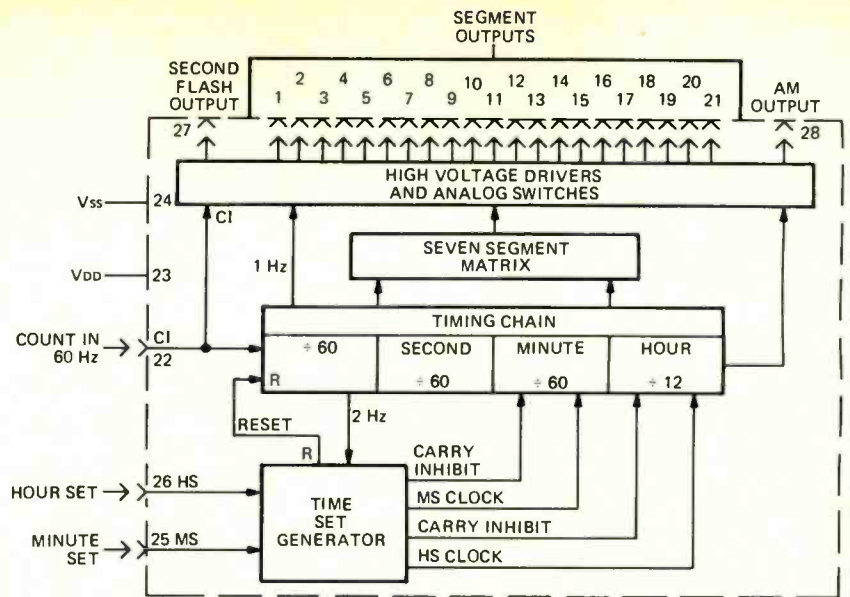


FIG. 1—BLOCK DIAGRAM of LSI Computer Systems Inc. C1200 clock IC.

FIG. 2 (right)—CONSTRUCTION of liquid crystal display device is shown in a. Metallizing pattern and connections of liquid crystal display with diagram of voltages applied to the cathode (front-plane) and the anode (back-plane) is shown in b.

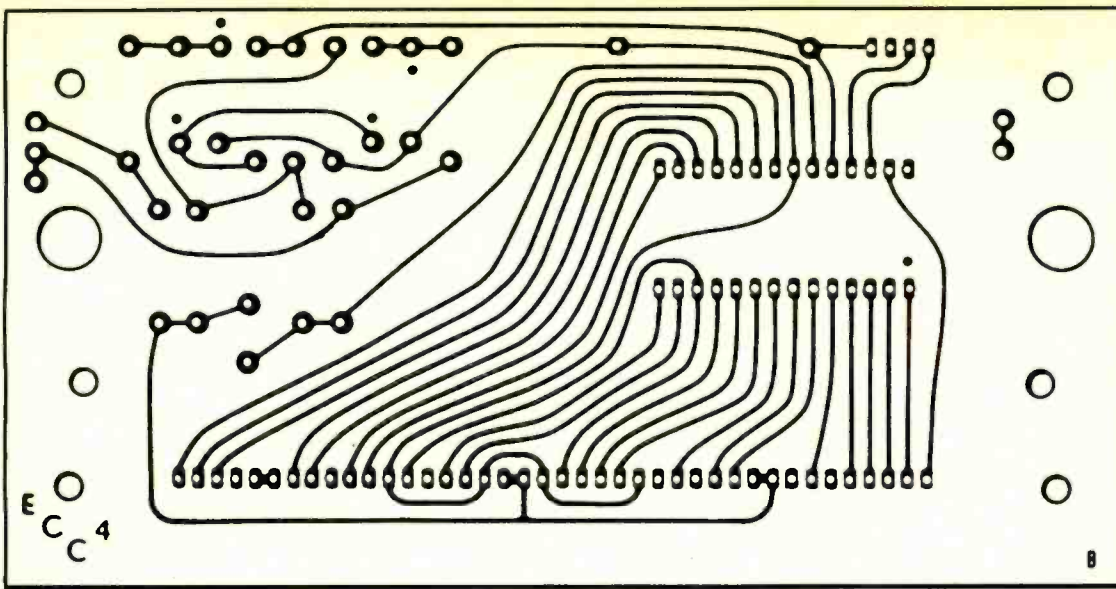

FOIL PATTERN for the printed circuit board shown full-size.

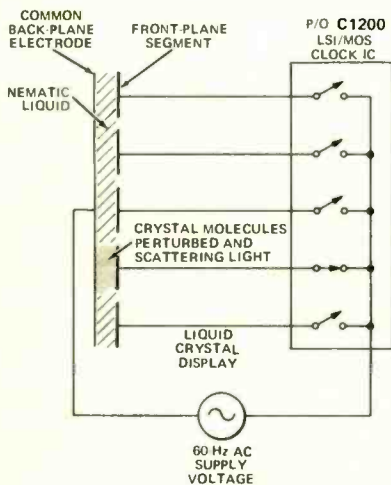


FIG. 3 (top)—THE CRYSTAL MOLECULES in the nematic liquid are disorganized by an electric field.


FIG. 5 (right)—PIN CONNECTIONS for LSI Computer Systems Inc. C1200 MOS clock IC.

Pin No.	Function
1	G4
2	F3
3	G3
4	E3
5	D3
6	C3
7	B3
8	A3
9	F2
10	G2
11	E2
12	D2&A2
13	C2
14	B2
15	F1
16	G1
17	E1
18	D1
19	C1
20	B1
21	A1
22	CI
23	VDD
24	VSS
25	MS
26	HS
27	SEC
28	AM

PIN CONNECTIONS C1200

LCD SEGMENT OUTPUTS

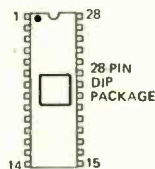60 Hz COUNT INPUT
SUPPLY
MINUTE SET INPUT
HOUR SET INPUT
ONE SECOND FLASH OUTPUT
AM OUTPUT (NOT USED)



PARTS LIST

- R1, R4—8200 ohms, 1/4 W, 5%
- R2, R3—2000 ohms, 1/4 W, 5%
- R5, R9—2000 ohms, 1 W, 5%
- R6—680 ohms, 1/2 W, 5%
- R7—1500 ohms, 1/2 W, 5%
- R8—2200 ohms, 1/2 W, 5%
- C1—25 μ F, 50 V, electrolytic
- C2—.05 μ F, 50 V, ceramic
- D1, D2, D3, D4—1N916 or equal
- *D5, *D6—Zener diode, 51V, 10%, 1W (1N4757 or equal) (Part MGC-51)
- *IC1—C1200 (LSI MOS clock IC) (Part MGC-C1200)
- S1, S2—spsst, momentary contact (see text for details)
- *LCD1—Liquid crystal display (Part MGC-50)
- *Socket for display (Part MGC-116)
- *28-pin IC socket (Part MGC-28)
- *Circuit board (Part MGC-48-7)
- AC line cord with plug
- *These parts are available from Inventive Electronics, Box 53, Wykagyl Station, New Rochelle, NY 10804. Price of the partial kit containing all parts marked with an asterisk is \$65 postpaid.

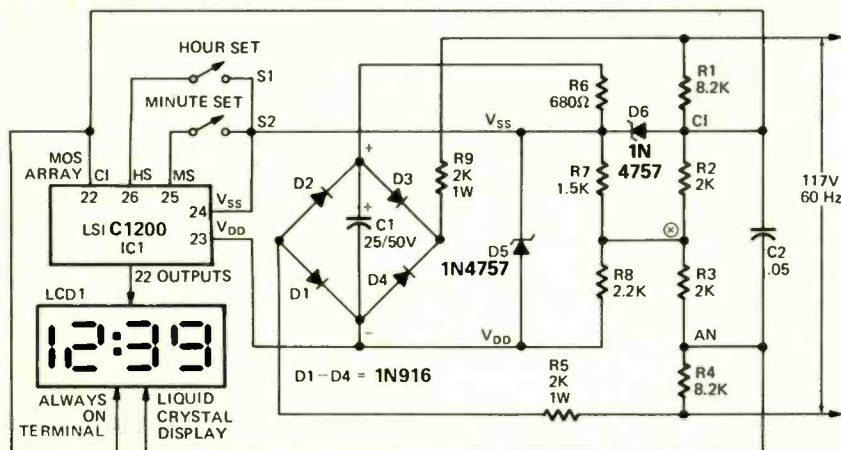


FIG. 4—SCHEMATIC DIAGRAM shows the C1200 IC and the external components necessary for the clock.


larly, the seconds input to the minutes portion of the TIMING CHAIN has no effect when MINUTE SET switch S2 applies a signal to pin 25.

The reset output of the TIME SET GENERATOR is used when the IC is used as an elapsed time indicator. To do this, HOUR SET S1 and MINUTE SET S2 must be

closed at the same time. This automatically generates a reset pulse which sets the timing chain—subseconds, seconds, minutes and hours—to zero. When both switches are released, simultaneously, the chip starts from an all-zero reference and counts "up", to add one minute to the time displayed every sixty seconds.

The cathode (front-plane) voltage input to the LCD goes through the ANALOG SWITCH that is ON at any given time so AC is applied to the appropriate segment of the LCD. The anode (back-plane) voltage is applied via three contacts on the display (see Fig. 2-b). Cathode and anode voltages are always 180° out of phase and identical in amplitude. There is no DC component present, for the life of an LCD is appreciably reduced if it is operated from a DC source, or from AC with a DC component. However, DC is required to perform the logic operations in the chip and is supplied from the full-wave supply consisting of low voltage diodes, D1, D2, D3, D4 and filter capacitor C1.

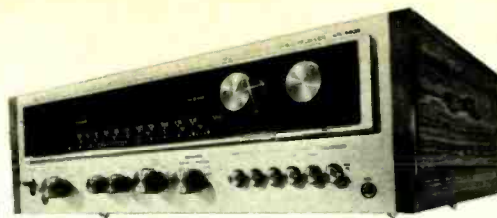The two Zener diodes (D5, D6) are required for over-voltage protection of the IC. D5 limits the supply to 51 volts and D6 limits the voltage applied to the HOUR SET and MINUTE SET inputs (pins 26 and 25) to 51 volts, peak-to-peak. C2 acts as a high-frequency filter. It eliminates the high-frequency component of transients on the AC line. (continued on page 92)



Tests Kenwood KR-5400

by **LEN FELDMAN**
CONTRIBUTING HI-FI EDITOR

THE KENWOOD MODEL KR-5400 2-CHANNEL receiver is a medium priced model in that company's broad line of stereophonic all-in-one receivers. The unit just above it in price and power (at 50 watts continuous power-per-channel) is their model KR-6400, which costs \$70 more. The next lowest unit in power and price would be the KR-4400, with an output of 25 watts-per-channel and a retail price of \$299.95. At its price, the KR-5400 offers a variety of control features that should appeal to the serious audiophile who requires this amount of power in an all-in-one receiver.

The Kenwood model KR-5400 is shown in Fig. 1. The upper section of the panel has a long, blacked-out dial scale area which becomes illuminated in soft blue when power is applied. The signal-strength meter, located at the upper right of this area is only illuminated when AM or FM reception is selected, and the dial pointer itself becomes illuminated in red when radio reception is selected by means of the program selector switch. The FM and AM dial scales are well calibrated with notations at every 2 MHz for the perfectly linear FM dial scale and a reference logging scale located below the AM and FM scales. To the right of the dial scales are the large tuning knob coupled to an effective flywheel tuning system, and a dual concentric master volume and balance control. The balance control section of this dual control takes the form of a lever that can be swung to favor left or right channel output. A mechanical detent helps establish its center position. This lever tends to be hidden because of the color scheme of the panel and its position under the master volume control and the user who fails to read the owner's manual might well wonder, at first, if balancing facilities were overlooked entirely.

The lower section of the gold colored aluminum panel has a rugged looking lever-type power on off switch at the left. This is followed by a six-position speaker selector switch (which includes an off position for headphone listening as well as choices for any one of three pairs of speakers which can be connected to the receiver or combinations of main and either remote pair of speakers operating together), separate bass and treble tone controls, a mode switch (with settings for left, right, stereo, reverse and mono-mix), a program selec-

tor switch and six push buttons. The buttons are used to actuate either of the two tape monitor circuits, FM muting, low-and high-cut filters and loudness circuitry. Along the lower edge of the panel there is the usual headphone connection jack as well as a microphone input jack. Only a single microphone can be connected to the receiver and its signal will be reproduced monophonically through both speakers.

The cabinetry of the KR-5400 consists of a pair of walnut side panels mounted to

a metal enclosure, the top surface is well ventilated with slots. The rear panel of the receiver is shown in Fig. 2, and a diagram illustrating all the various components which can be used with the unit and how they are connected is shown in Fig. 3. The rear panel is equipped with the usual input and output jacks (two turntables can be connected), antenna terminals for FM and AM external antennas, an FM detector output jack (for future use with FM four-channel adaptors), in and out jacks for the

TABLE I
RADIO-ELECTRONICS PRODUCT TEST REPORT

Manufacturer **Kenwood** Model **#KR-5400**

FM PERFORMANCE MEASUREMENTS

	R-E Measurement	R-E Evaluation
SENSITIVITY, NOISE AND FREEDOM FROM INTERFERENCE		
IHF sensitivity, Mono (μV)	3.0	acceptable
Sensitivity, Stereo (μV)	16.0	acceptable
50 dB quieting signal, Mono (μV)	4.0	very good
50 dB quieting signal, Stereo (μV)	35.0	good
Maximum S/N ratio, Mono (dB)	69	very good
Maximum S/N ratio, Stereo (dB)	59	good
Capture ratio (dB)	1.5	very good
AM suppression (dB)	65	excellent
Image rejection (dB)	72	very good
IF rejection (dB)	90	excellent
Spurious rejection (dB)	85	excellent
Alternate channel selectivity (dB)	63	very good

FIDELITY AND DISTORTION MEASUREMENTS

	R-E Measurement	R-E Evaluation
Frequency response, 50Hz to 15 kHz (\pm dB)	+0, -2.0	good
Harmonic distortion, 1kHz, Mono (%)	0.1	excellent
Harmonic distortion, 1kHz, Stereo (%)	0.2	excellent
Harmonic distortion, 100 Hz, Mono (%)	0.07	excellent
Harmonic distortion, 100 Hz, Stereo (%)	0.45	good
Harmonic distortion, 6 kHz, Mono (%)	0.20	very good
Harmonic distortion, 6 kHz, Stereo (%)	2.0	acceptable
Distortion at 50 dB quieting, Mono (%)	1.75	good
Distortion at 50 dB quieting, Stereo (%)	0.40	excellent

STEREO PERFORMANCE MEASUREMENTS

	R-E Measurement	R-E Evaluation
Stereo threshold (μV)	16.0	acceptable
Separation, 1 kHz (dB)	44	excellent
Separation, 100 Hz (dB)	35	excellent
Separation, 10 kHz (dB)	33	excellent

MISCELLANEOUS MEASUREMENTS


	R-E Measurement	R-E Evaluation
Muting threshold (μV)	20	acceptable
Dial calibration accuracy (\pm kHz @ MHz)	200	acceptable

EVALUATION OF CONTROLS, DESIGN, CONSTRUCTION


	R-E Evaluation
Control layout	very good
Ease of tuning	good
Accuracy of meters or other tuning aids	good
Usefulness of other controls	very good
Construction and internal layout	good
Ease of servicing	good
Evaluation of extra features, if any	good

OVERALL FM PERFORMANCE RATING



good

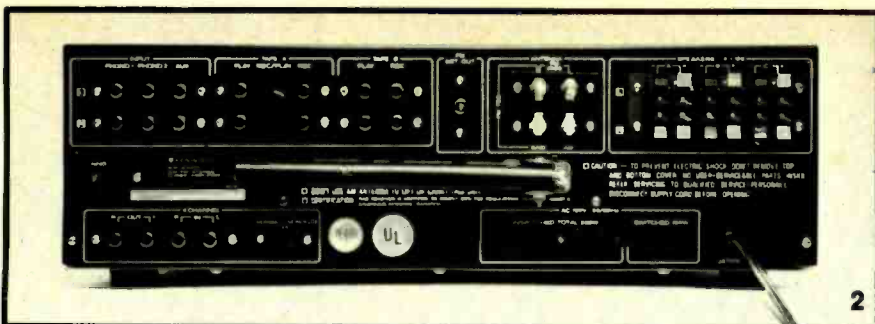


2

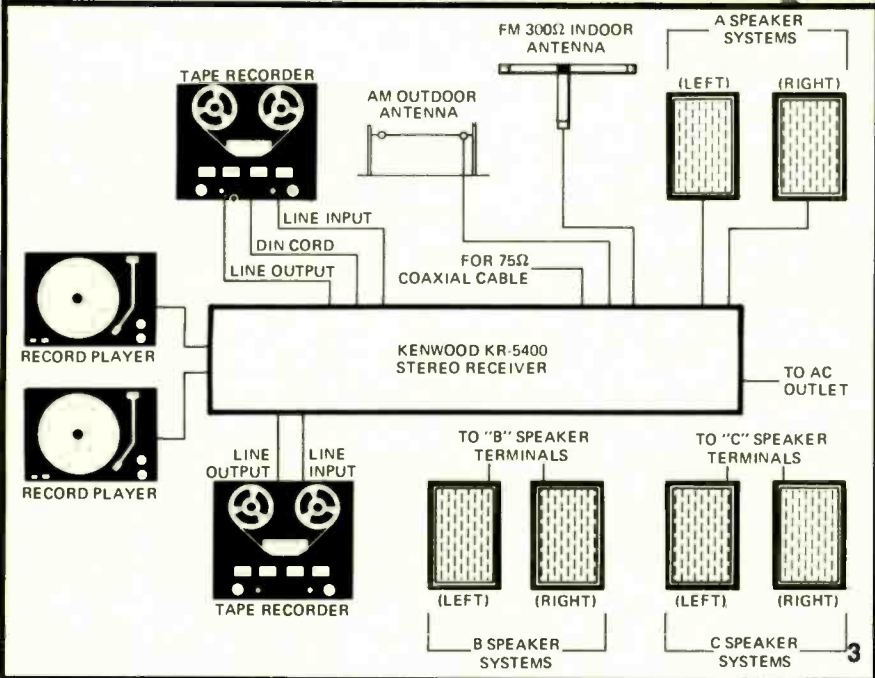

3

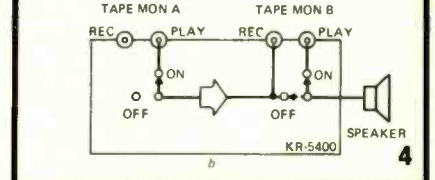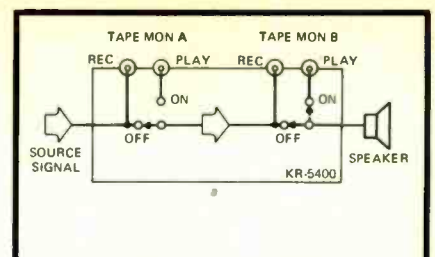

4

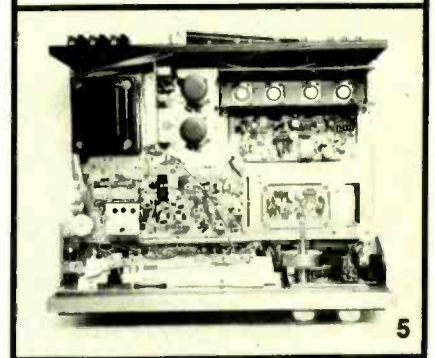

5

Kenwood KR-5400 Stereophonic AM/FM Receiver

SUMMARY OF MANUFACTURER'S PUBLISHED SPECIFICATIONS:

TUNER SECTION (FM)

IHF Sensitivity: 1.9 μV . S/N Ratio: 68 dB. Quieting Slope: 48 dB at 4 μV ; 60 dB at 10 μV ; 68 dB at 50 μV . Selectivity: 65 dB. Capture Ratio: 1.5 dB. Image Rejection: 70 dB. IF Rejection: 90 dB. Spurious Rejection: 90 dB. Harmonic Distortion: (mono): 0.3%; (Stereo): 0.5%. Stereo FM Separation: (1kHz): 35 dB; (10 kHz): 27 dB.

TUNER SECTION (AM)

Sensitivity: (ext. antenna): 18 μV . Selectivity: 30 dB. Image Rejection: 60 dB. IF Rejection: 40 dB. S/N Ratio: 45 dB.

AUDIO AMPLIFIER SECTION

Continuous Power Output: (Both channels driven, 8 ohm loads, 20 Hz to 20 kHz): 35 watts-per-channel. Rated Harmonic Distortion: 0.5%. Rated IM Distortion: 0.5%. Frequency Response: 10 Hz to 40,000 Hz ± 1 dB. Phono Equalization: RIAA ± 1 dB. Damping Factor: 50 (at 8 ohms). Input Sensitivity: (Phono): 2.5 mV; (Aux & Tape): 150 mV. Record Output Level: 150 mV. Hum and Noise: (Phono 1 & 2): 70 dB ("A" Weighting); (High Level Inputs): 90 dB ("A" Weighting). Tone Control Range: (Bass): ± 10 dB @ 100 Hz; (Treble): ± 10 dB ± 10 kHz. Low Filter: -5 dB @ 100 Hz. High Filter: -10 dB @ 10 kHz.

GENERAL SPECIFICATIONS

Power Requirements: 120 V, 50/60 Hz, 240 watts maximum consumption. Dimensions: 18-15/16 \times 5-15/16 high \times 13-9/16 deep. Weight: 25.4 lbs. Retail Price: \$379.95.

two tape monitor circuits (as well as a DIN connector for one of those monitoring circuits) and two unswitched plus one switched AC convenience receptacles. Speaker terminals for three possible pairs of speakers are of the spring-loaded piano key type that require only the simple insertion of stripped wire ends into a tiny hole that appears when the terminal keys are depressed.

Four additional jacks at the lower left of the rear panel are labelled 4-CHANNEL IN

and OUT. They are, in reality, the components of a third tape monitor circuit and permit the user to introduce a 4-channel matrix decoder without giving up either of the other two front-panel actuated tape monitor circuits. To use this facility, it is necessary to move a rear panel slide switch to the position identified as "separate". This circuit interruption should not be confused with the preamp-amp separating switches which are supplied on some costlier receivers. The circuit separation in this

case occurs ahead of all tone control and volume or balance control action, whereas the preamp-amp arrangements on some receivers actually occur after all preamplification and control functions have taken place.

The two tape monitoring circuits of the Kenwood KR-5400 provide a high degree of versatility for the serious recordists. You can record any program source onto one or two tape recorders simultaneously (See Fig. 4A) or you can dub from one tape recorder to another (See Fig. 4B) and monitor recorded results on the second recorder. When recording to two recorders at once, only the recorder connected to the "Tape Mon B" jacks can be simultaneously monitored.

Circuit configuration and features

An internal view of the chassis of the KR-5400 is shown in Fig. 5. Eight separate circuit modules are used in its construction, of which three major ones can be seen in the photograph. The entire FM tuner circuitry is contained on one large PC board. This circuit contains the front end, which consists of an FET RF amplifier plus two conventional transistors used as local oscillator and mixer circuits. Tuning is by means of a three-gang variable capacitor. A two-gang capacitor is used for AM tuning and bi-polar discrete transistors are used for the AM front-end circuitry. Some of the IF FM section is shared by the AM IF circuits, and a total of four bipolar transistors followed by an IC and a conventional ratio detector are used in this section. All but one stage of the IF section are tuned by means of conventional interstage transformers. The multiplex stereo decoder consists essentially of a single IC circuit which includes a phase-locked-loop arrangement and requires no adjustable tuned circuits for optimizing separation.

Phono and microphone preamplification

is accomplished by IC's on a separate well shielded module, with equalization selectable depending upon the setting of the program selector switch. Thus, microphone use, besides being limited to monophonic reproduction, cannot be "mixed" with any other program source. Tone control circuits also use IC's (one for each channel) and are of the popular negative feedback type. Both power amplifier circuits are mounted on a single PC board which includes the output transistors (complementary-symmetry NPN-PNP pairs) that mount through a single large heat sink directly to the PC board itself. Input stages are differential amplifiers and each power amplifier is completely direct coupled.

FM tuner measurements

Results of our FM performance measurements are tabulated in Table I, and readers can compare measured results with manufacturer's published claims, where applicable. Although IHF sensitivity fell short of the 1.9 μ V claimed, we cannot fault tuner performance on this score, since with only 4 μ V applied, S/N ratio reached an acceptable 50 dB. We were also rather surprised at the better than average selectivity measured for this tuner that, after all, uses a "bare minimum" three-gang tuning capacitor and a not terribly sophisticated IF design. What did disturb us somewhat was the rather high level of sub-carrier product output from the stereo FM section, which was only about 45 dB below full modulation. Kenwood claims carrier suppression of 60 dB. Of course, this high frequency output is not audible, nor will it adversely affect tweeters (the energy is too low), but it may cause some problems with tape recorders having lower than usual bias frequencies. While stereo separation was excellent, the presence of "beats" when attempting to measure THD at high audio frequencies in the stereo mode resulted in the rather high 2.0% reading shown in Table I.

Amplifier performance measurements

Amplifier measurements are tabulated in Table II. Specifications quoted by Kenwood are in complete compliance with the new FTC rules on power disclosure, and these numbers more than met in our individual measurements. Had Kenwood wanted to be a bit less conservative, they could well have elected to rate the power output of each channel at 37 watts instead of 35 and still met FCC requirements. In fact, in just about all respects, the amplifier section of the KR-5400 rates a bit better than the tuner section. The only criticism we might levy against the unit is in its equalization characteristics, which departed from correct RIAA values by as much as 3 dB at the low end, providing more bass boost at 50 Hz and 30 Hz than is called for. Slight counterclockwise rotation of the bass control easily rectifies this discrepancy. If phono reproduction seems excessively bassy to you.

Since Kenwood elected to quote hum-and-noise figures using an "A" weighting network (which takes into account the audibility factor of hum-and-noise), we did likewise and came up with 72 dB as opposed to the 70 dB claimed. Even without this correcting network, the phono

TABLE II
RADIO-ELECTRONICS PRODUCT TEST REPORT

Manufacturer **Kenwood**

Model **#KR-5400**

AMPLIFIER PERFORMANCE MEASUREMENTS



	R-E Measurement	R-E Evaluation
POWER OUTPUT CAPABILITY		
RMS power/channel, 8-ohms, 1 kHz (watts)	39	good
RMS power/channel, 8-ohms, 20 Hz (watts)	37	excellent
RMS power/channel, 8-ohms, 20 kHz (watts)	38	very good
RMS power/channel, 4-ohms, 1 kHz (watts)	50	very good
RMS power/channel, 4-ohms, 20 Hz (watts)	45	very good
RMS power/channel, 4-ohms, 20 kHz (watts)	49	very good
Frequency limits for rated output (Hz-kHz)	18-23	excellent
DISTORTION MEASUREMENTS		
Harmonic distortion at rated output, 1 kHz (%)	0.14	very good
Intermodulation distortion, rated output (%)	0.55	good
Harmonic distortion at 1 watt output, 1 kHz (%)	0.10	good
Intermodulation distortion at 1 watt output (%)	0.05	excellent
DAMPING FACTOR, AT 8 OHMS	50	excellent
PHONO PREAMPLIFIER MEASUREMENTS		
Frequency response (RIAA \pm ___ dB)	3.0	acceptable
Maximum input before overload (mV)	135	very good
Hum/noise referred to full output (dB) (at rated input sensitivity)	72	excellent
HIGH LEVEL INPUT MEASUREMENTS		
Frequency response (Hz-kHz, \pm ___ dB)	10-40, 1	excellent
Hum/noise referred to full output (dB)	87	excellent
Residual hum/noise (min. volume) (dB)	90	very good
TONAL COMPENSATION MEASUREMENTS		
Action of bass and treble controls	See Fig. 6	good
Action of secondary tone controls	
Action of low frequency filter(s)	See Fig. 7	good
Action of high frequency filter(s)	See Fig. 7	acceptable
COMPONENT MATCHING MEASUREMENTS		
Input sensitivity, phono 1/phono 2 (mV)	2.5/2.5	
Input sensitivity, auxiliary input(s) (mV)	143	
Input sensitivity, tape input(s) (mV)	143	
Output level, tape output(s) (mV)	143	
Output level, headphone jack(s) (V or mW)	N/A	
EVALUATION OF CONTROLS, CONSTRUCTION AND DESIGN		
Adequacy of program source and monitor switching		very good
Adequacy of input facilities		excellent
Arrangement of controls (panel layout)		very good
Action of controls and switches		very good
Design and construction		good
Ease of servicing		very good
OVERALL AMPLIFIER PERFORMANCE RATING		very good

hum measured a very high 65 dB referred to full output and based on the 2.5 mV input sensitivity.

Tone control range is plotted in Fig. 6 and is typical of this type of circuitry. Action of the low- and high-cut filters is plotted in Fig. 7 and, while the choice of cut-off and slope of the low filter helps to correct for rumble problems without seriously affecting musical bass response, the same is not true of the treble cut filter which does little more than duplicate the action available from the regular treble control.

Utilization and listening tests

As is true of all honestly designed power amplifiers, the Kenwood KR-5400 "sounds" more powerful than it really is. We had no trouble driving low-efficiency acoustic suspension speaker systems to 100 dB sound-pressure-level in our 14 x 21 foot listening room. Action of all controls is smooth and there is no turn-on popping noise, thanks to a relay which is included in the protection circuitry of the receiver that delays application of audio signals to the speakers for a few seconds after

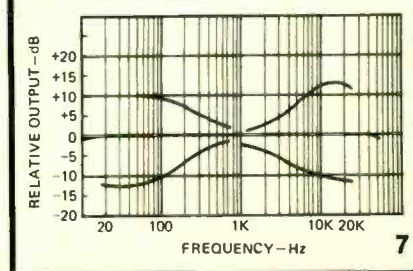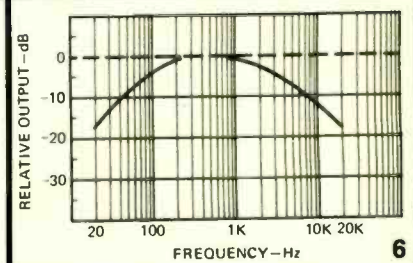

turn-on.

FM reception was good, at least in our location, using a 5-element outdoor antenna. The signal-strength meter is not of great help in proper tuning (a center-of-

TABLE III
RADIO-ELECTRONICS PRODUCT TEST REPORT
OVERALL PRODUCT ANALYSIS

Manufacturer **Kenwood**

Model **#KR-5400**

Retail Price
 Price Category
 Price/Performance Ratio
 Styling and Appearance
 Sound Quality
 Mechanical Performance

\$379.95
Medium
very good
excellent
very good
good

Comments:

The amplifier performance of the Kenwood KR-5400 merits a higher rating than does the tuner performance of this receiver. Its power output capability (for this price category) is high, and adequate reserve power is available at the important low-frequency extremes. High cut filter action is no more useful than the treble control, however, because of its low turnover point and its minimal 6 dB/octave slope.

Given the option of only one tuning meter, we would have preferred to see a center-of-channel meter for FM tuning. Tuning feel, however, is very smooth and in typical moderate to strong signal locations, FM performance will be adequate, despite the rather sparse front-end design and the use of conventional interstage tuned transformers in the IF section. The stereo multiplex section is extremely stable and separation was excellent, though the presence of high amounts of sub-carrier products in the output may create problems when taping FM programs on some recorders. We recommend using the high-cut filter for such taping operations if audible "beats" are encountered in completed recordings. The phase-lock-loop circuit used in the stereo MPX section will insure continued stable separation and no alignment should be necessary for this section. The FM IF section may need periodic alignment, however.

The linear FM dial scale (present on all Kenwood receivers and tuners) is a welcome feature and makes station finding easier.

Compared to some phono preamp IC's we have tested in other receivers, the one used in the KR-5400 has excellent overload capabilities and, with the low residual phono hum measured, record reproduction will have adequate, if not superb, dynamic range. The slightly exaggerated bass equalization can be compensated for by a slight bass-cut setting on the bass control. In summary, an excellent amp-preamp section plus an adequate tuner.

channel meter would have been preferred), but tuning is nevertheless relatively easy and bandwidth seems great enough so that the lowest distortion settings are consistently obtained without using any auxiliary equipment as a check. Calibration was off by about 200 kHz at the low end of the dial, but right on target from about 94 MHz up to 108 MHz. Stereo switching occurs at about the right signal strength, though muting threshold is adjusted a bit too high for our taste. By not using the muting feature we were able to receive about three additional stations with acceptable quieting that would otherwise have been blocked by the muting circuit.

Our capsule summary, along with overall comments, is tabulated in Table III. No unusual heat problems were encountered while operating the Kenwood KR-5400 for extended time periods and it passed its FTC pre-conditioning tests easily. While lacking some of the circuit sophistication of more expensive receivers, the Kenwood performed well in its price category and compares very favorably with competitive units in that same price range. **R-E**

Radio-Electronics®

Tests Crown VFX-2



by **LEN FELDMAN**
 CONTRIBUTING HI-FI EDITOR

AUDIO PERFECTIONISTS HAVE LONG RECOGNIZED the virtues of bi-amplification and tri-amplification in high fidelity sound reproducing systems. For the uninitiated, bi-amplification means using two separate amplifiers to drive the woofer and tweeter of a loudspeaker system, or as many as

three or four power amplifiers if three- and four-way speaker systems are used. By doing away with the usual passive crossover network normally included with multi-driver speaker systems, certain problems of phase distortion and IM distortion are often eliminated and, in many cases, a better balance between low-, mid- and high-frequency sonic energy can be created in the listening room.

In addition to requiring two or more stereo amplifiers for such an arrangement, an electronic crossover must be used. This device channels required bands of audio frequencies to the respective amplifiers and, in some cases, adjusts the level of signals going to each amplifier. One such product is Crown's Model VFX-2, shown in Fig. 1. It contains enough circuitry for a bi-amplification two-channel system and

can be interconnected to provide tri-amplification facilities for a single audio channel. So, if you plan to use three-way speaker systems with an electronic crossover (and three power amplifiers per channel), two of these Crown units would be required for stereo reproduction. Figure 2 shows how the device would be interconnected in a two-way speaker system set-up. Figure 3 shows a single channel of amplification connected to feed a three-way speaker system.

The front panel of the VFX-2 contains eight rotary controls; four for each stereo channel. A selector switch either removes a given filter from the circuit (in its "off" position) or chooses a frequency multiplication factor of $\times 10$, $\times 100$ or $\times 1000$. Adjacent to each selector switch is a rotary control calibrated from 2 to 20. Thus, low- and high-pass corner frequencies (frequencies at which response is down 3 dB) can be adjusted from 20 Hz to 20,000 Hz.

As a first experiment, we adjusted the low- and high-pass controls of channel-one so that the corner frequencies coincided at 1000 Hz and plotted the response from the output jacks labelled LOW PASS OUTPUT and HIGH PASS OUTPUT. The frequency response observed at each output are combined in the graph shown in Fig. 4.

While this is perhaps the most popular application of the VFX-2, it can also be used as an audio bandpass filter, thanks to a novel switching arrangement available on the rear panel (see Fig. 5). The rear panel includes a pair of balanced or unbalanced inputs at the right, with adjacent screwdriver controls which permit adjustment from unity gain to $+15.5$ dB and a pair of unity gain inputs (with no gain adjustments). There are pairs of normal and inverted high-pass output and pairs of normal and inverted switchable outputs that, depending upon the setting of the pair of adjacent slide switches, provide either a low-pass output or bandpass output.

The reason for the normal or inverted output becomes clear when you consider that the power amplifiers used with the system may or may not have equal numbers of phase-inverting amplifier stages. If the number is unequal, then applying in-phase signals to the bass and treble amplifiers in a bi-amplified system would result in out-of-phase outputs to the speakers. By providing normal and inverted outputs on the VFX-2, this problem is easily solved.

Additional possible response curves and applications, together with front panel control settings and rear panel required connections and switch positions are illustrated in Fig. 6.

Circuit Description

The Crown VFX-2 Electronic Filter/Crossover consists primarily of two identical channels of active IC operational amplifier tunable filters. A schematic of one of the channels is shown in Fig. 7. Operational amplifier IC1-a, functions as a balanced gain amplifier. The unity-gain output of IC1-b is applied to the input circuit of IC2-a (high-pass filter) only or to that circuit plus the input circuit of IC4-a (low-pass filter) depending upon the position of the crossover-filter switch. The output from IC1-b can also go directly to

SUMMARY OF MANUFACTURER'S PUBLISHED SPECIFICATIONS

Frequency Response: 18 Hz to 38 kHz ± 0.5 -dB into 600-ohm load.

Inputs: Bridging input, 20K ohm balanced or 10K ohm unbalanced, and 1M ohm unbalanced; both using 1/4 in. standard phone jack.

Output: 10 volts maximum before overload; 2.5 volts rated.

Gain: 0 to 15.5 dB from balanced/unbalanced input.

Hum and Noise: More than 100-dB below rated output, with 0-dB gain, over entire audio spectrum from 20 Hz to 20 kHz.

IM Distortion: Less than 0.01% at rated output

Filter Characteristics: Separate 18-dB Butterworth highpass and lowpass, with adjustable corner frequencies. Can be internally cascaded to form band pass and band reject filters.

Controls: (front panel) Range and vernier controls for corner frequencies (high and low pass), power on/off switch. (rear panel): Screwdriver-adjustable input attenuators for each channel.

Dimensions: 19-in. wide (standard rack mount) \times 3 1/2-in. high \times 5 3/4-in. deep.

Power Requirements: 2 watts at 120 or 240 VAC, 50-400 Hz.

Weight: 6 lbs. Retail Price: \$249.00

RADIO-ELECTRONICS PRODUCT TEST REPORT

OVERALL PRODUCT ANALYSIS

Manufacturer **Crown International**


Model **#VFX-2**




Retail Price
Price Category
Price/Performance Ratio
Styling and Appearance
Sound Quality
Mechanical Performance

\$249.00
Medium
Good
Excellent
Excellent
Good

Comments:

As might be expected, based on the dynamic range capabilities and low distortion measurements made, the VFX-2 introduces no audible distortion or noise of any kind. We would have liked to see some sort of level controls for regulating low-amplifier output relative to high-amplifier output. Since such controls are not provided, readers who plan to use the VFX-2 in a home audio system should make certain that their individual stereo power amplifiers have input level controls so that woofer and tweeter levels can be adjusted. A study of the internal construction and layout of the VFX-2 indicated that it is built to professional standards, uses top grade components, and should remain trouble free for many years. Even used as a simple bandpass filter (for high-cut scratch filtering and/or low cut rumble filtering), the unit proved far more effective than the usual "high cut" and "low cut" filters normally found in integrated amplifiers or receivers, thanks to its steeper (18 dB-per-octave) slopes and more precise filter action.


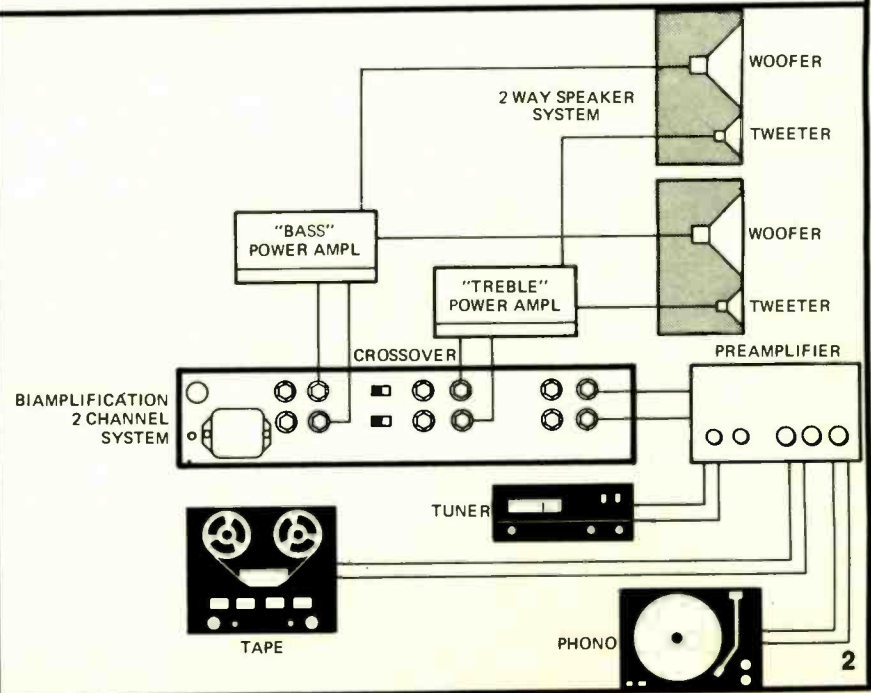


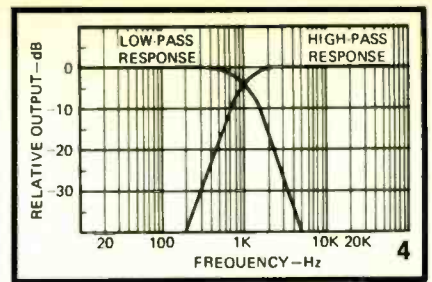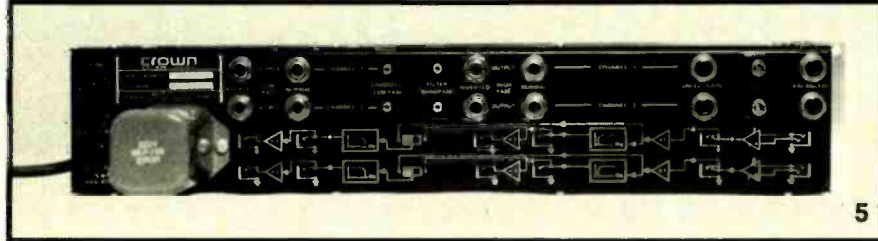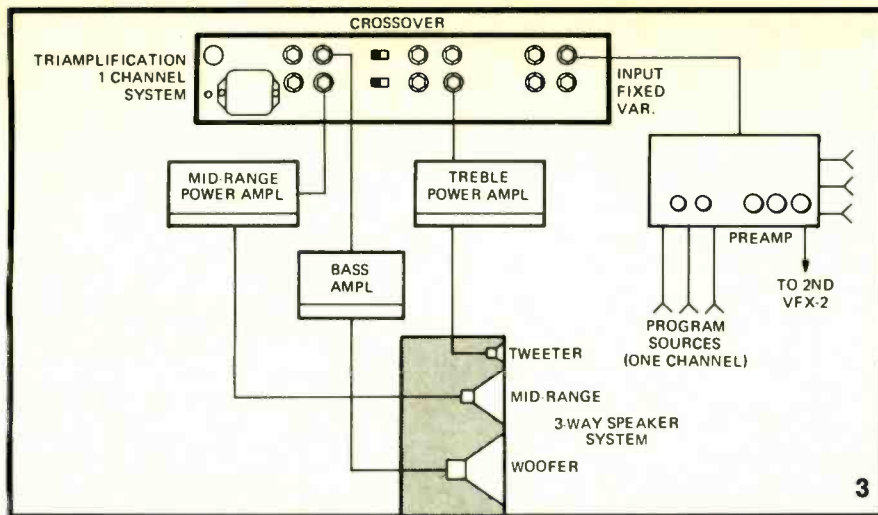

the LOW PASS OUTPUT jack depending upon the position of the RANGE switch.

The RANGE switch determines the appropriate group of 5% matched capacitors to be used in the filter stages. High-vernier potentiometer (R14, R16, R18) and low-vernier potentiometer (R23, R25, R27) are matched sets of three 15K ohm resistive elements used to determine the corner frequency of each filter. The signal from IC1-b is applied through selected RC filter components to dual operational amplifier IC2-a that, along with IC2-b and IC3-a, forms a 3-pole high-pass 18 dB/octave Butterworth filter. This delivers the non-inverted high-pass output, while operational amplifier IC3-b delivers the high-pass inverted output.

(continued on page 73)

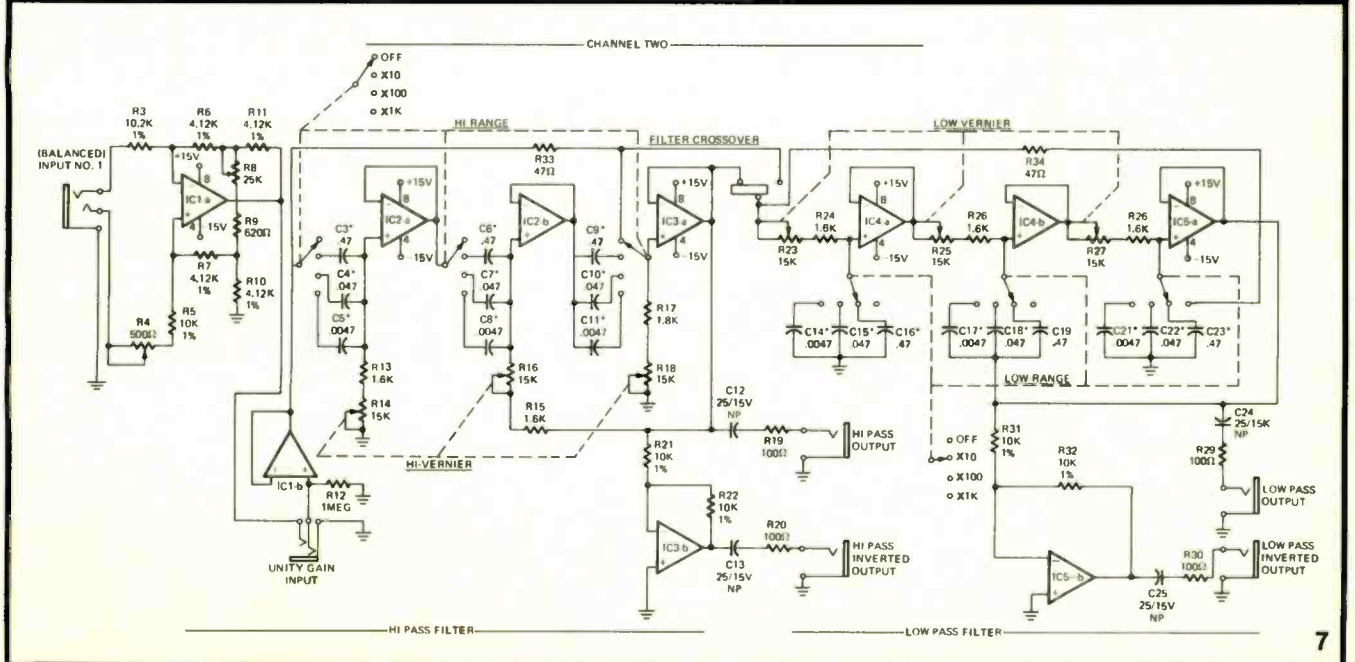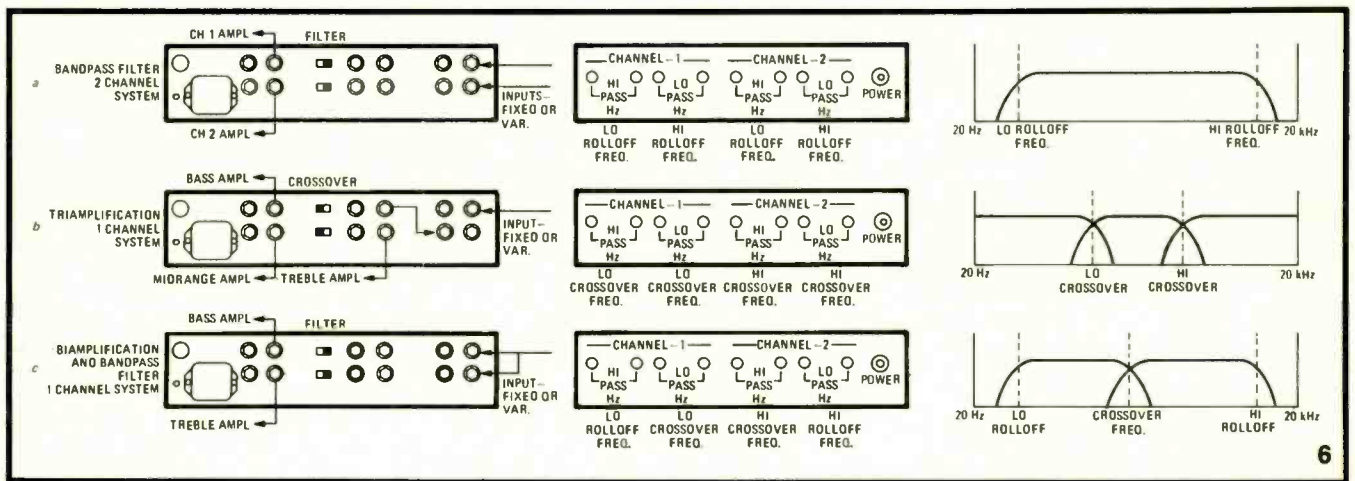

BUILD

this COLOR TV for about

This month the circuit head adjustments are we'll show you how to connect

by GARY DAVIS

LAST MONTH WE PRESENTED THE color processing, block diagram, and general layout of a low-cost color TV camera. This month we will cover the camera heads in detail, including adjustments and registration.

The vidicon tube

Each camera head consists of three basic units. The vidicon-tube assembly,

the video preamp and the deflection components. Before we discuss the camera circuitry, let's briefly examine the operation of a vidicon image pickup tube. The tube contains a signal plate of a conducting metallic film, so thin that it is transparent. One side of this plate is coated with a thin layer of photo-conductive material, such as amorphous selenium. The optical

image is focused on the opposite side of the signal plate. The photo-conductive material is scanned with an electron beam originating at the vidicon cathode.

The scanning beam deposits just enough electrons on each spot that it touches, to reduce the potential of that side of the metallic film to the cathode potential. However, during the interval


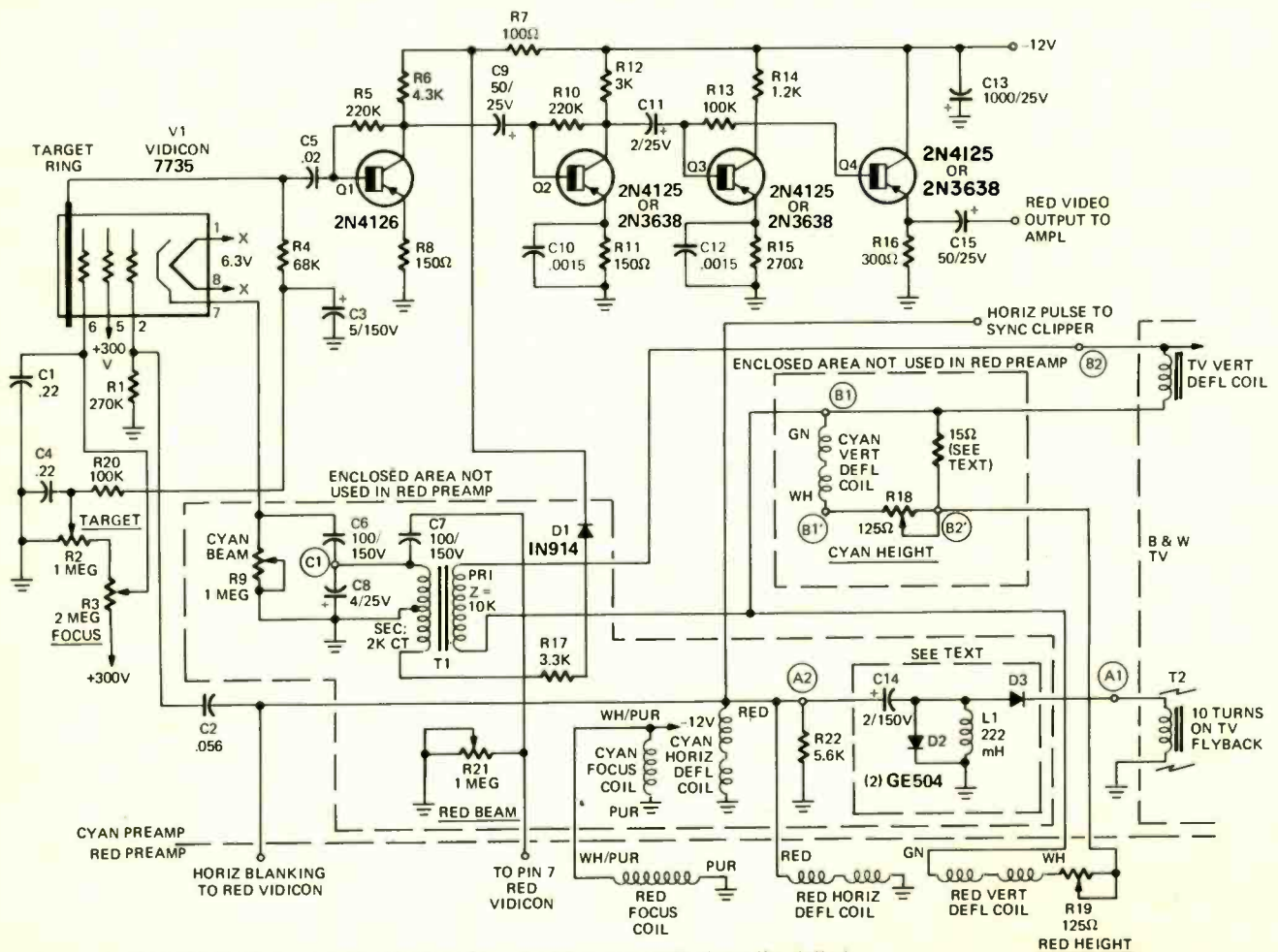


FIG. 2—PREAMPLIFIER for the cyan and red video channels. All components above the dotted line, except where noted, are duplicated for red video channel. A black-and-white TV receiver supplies the operating voltages, sync and blanking signals to the camera head.

CAMERA \$400

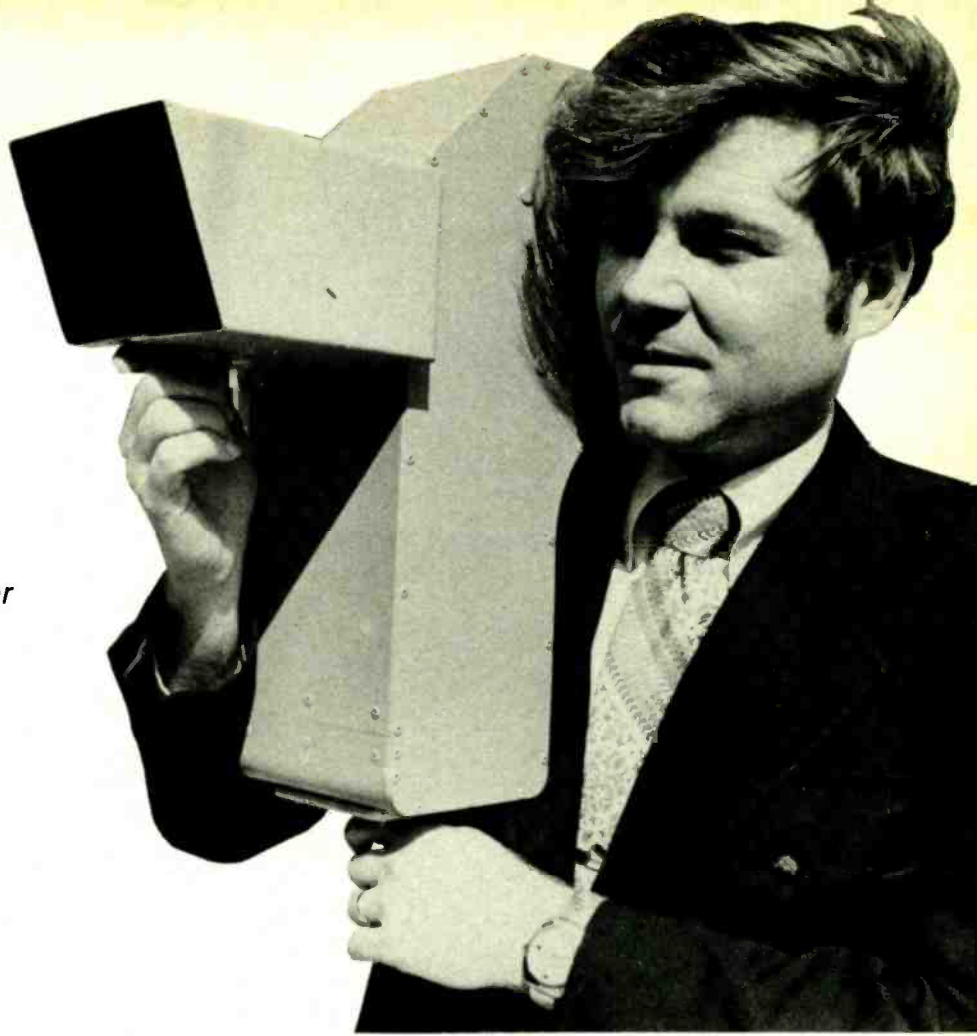details and camera covered. Next month, the camera head to a color monitor



between successive scans, a charge leaks through the photo-conductive material in proportion to the illumination. The charge deposited on any particular spot of the photo-conductive material the next time it is scanned, is enough to replace those electrons that have been lost by leakage since the last passage of the beam. The total current of the electron beam and the capacitance of the photo-conductive material is in series with the external load resistors.

The preamp

In this camera so much light is absorbed by the color filters and prism, that only a very low level of light actually strikes the vidicon photo-conductive surface. Therefore, the video amplifier must work with a very low signal-to-noise ratio. The schematic diagram of the preamp circuits are shown in Fig. 2. Transistor Q1 should be a low-noise type 2N4126, and may

have to be individually selected for low-noise content after the camera is in operation. One should not be satisfied with the signal-to-noise ratio until with sufficient illumination, the pictures are about as noise-free as those received from a local commercial TV station. It will probably not be necessary to individually select the other amplifier transistors.

The video amplifier should be mounted inside a metal box to shield the amplifier from extraneous signals. It is important to use short leads and the amplifier should be mounted on the focus coil assembly so that the signal lead from the vidicon target connector to the video preamplifier input is no longer than one inch in length. In dealing with low signal levels at the vidicon output, ground loops and sufficient grounding between components becomes extremely critical. A general rule would be to ground everything possible with short ground leads, including the lens mount and the lens. Good results with my camera were obtained with an unshielded wire for a target lead. However, in metropolitan areas or areas with strong RF signals, a shielded wire may be necessary.

Vertical sync is added to the cyan signal through diode D1 at Q1. The addition of vertical sync slightly tilts the video waveform. However, it has negligible shading affect on the picture. Capacitors C10 and C12 boost the high-frequency response to increase the upper frequency limit of the entire video amplifier. Low-frequency negative feedback is introduced to each stage individually by connecting the bias resistor to the collector load resistance. This arrangement further en-

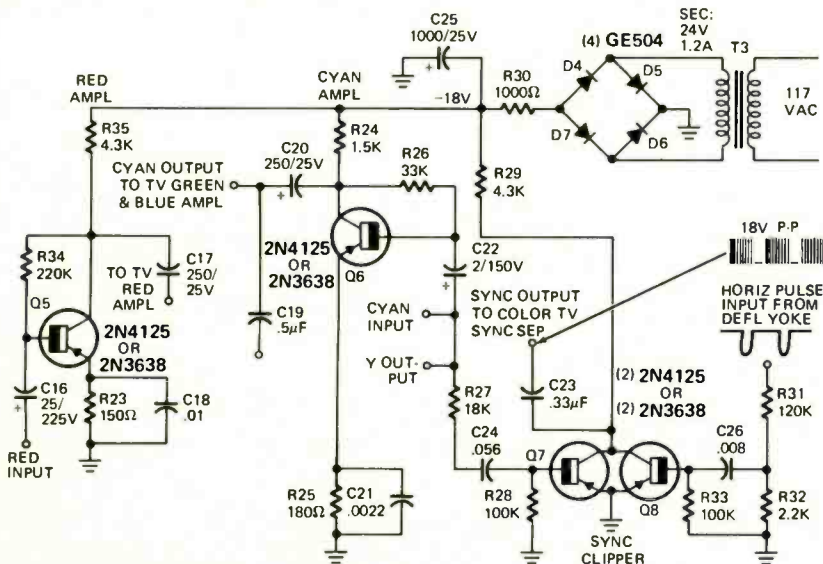


FIG. 3—COLOR AMPLIFIERS and sync circuit. The video and sync outputs are connected directly to the color difference amplifiers and sync separator of the color monitor.

hances the relative high-frequency response of each stage. The entire video amplifier has a voltage gain of approximately 300. The color amplifier and sync circuits are shown in Fig. 3.

Deflection and focus assembly

Due to the fact that the red camera head sees a mirror image of the actual scene, the phase of the deflection signal to the red yoke must be taken into

consideration. Focus coil windings for both vidicon tubes should have the purple wire grounded (see Figs. 2 and 4), and the white/purple wires connected to $-12V$. On the vertical windings, yellow is not used. White wires are connected to their respective height controls R18 and R19. The green wires are connected together and common to T1. On the horizontal windings, the red wires are connected together. The cyan black wire is connected to point A2. The red channels' black wire is grounded. Both gray wires of the electrostatic shield should also be grounded. The blue wires are not used. With this wiring arrangement, the deflection assembly should be mounted with the focus coil lead exit-holes for the cyan channel opposite the mounting board. The red-channel focus coil lead exit holes should be next to the mounting board. This arrangement applies to type CY101-1547 deflection assembly available from Denson Electronics.

The vertical deflection coils require 6 V P-P for proper deflection as shown on waveform B1. Each horizontal deflection coil requires 30 to 40 V P-P as shown on waveform A2. It should be noted that for proper operation, the camera requires waveforms and voltage amplitudes as shown. They are supplied by a small B/W monitor.

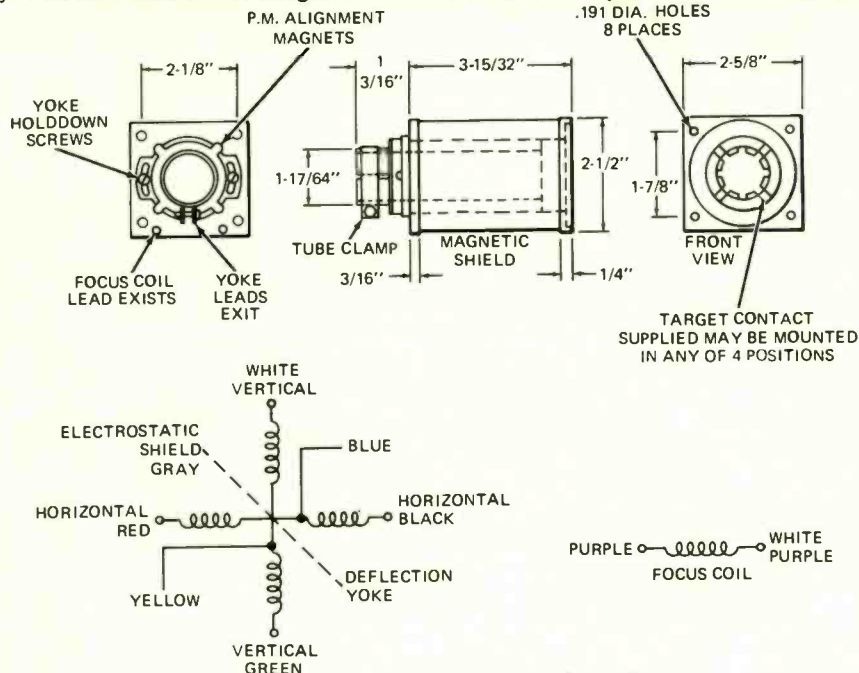


FIG. 4—DEFLECTION ASSEMBLY of type CY101 for 1-inch vidicon tubes.

PARTS LIST

All resistors are 1/2-watt 10% unless noted

- *R1—270,000 ohms
- *R2, R9, R21—potentiometer, 1 megohm, linear taper
- *R3—potentiometer, 2 megohms, linear taper
- *R4—68,000 ohms
- *R5, *R10, R34—220,000 ohms
- *R6, R29, R35—4300 ohms
- *R7—100 ohms
- *R8, *R11, R23—150 ohms
- *R12—3000 ohms
- *R13, *R20, R28, R33—100,000 ohms
- *R14—1200 ohms
- *R15—270 ohms
- *R16—300 ohms
- R17—3300 ohms
- R18, R19—potentiometer, 125 ohms, wirewound
- R22—5600 ohms
- R24—1500 ohms
- R25—180 ohms
- R26—33,000 ohms
- R27—18,000 ohms
- R30—1000 ohms
- R31—120,000 ohms
- R32—2200 ohms
- *C1, *C4—.22 μF , 300V
- *C2, C24—.056 μF , 200V
- *C3—5 μF , 150V, electrolytic
- *C5—.02, 100V
- C6, C7—100 μF , 150V, electrolytic
- C8—4 μF , 25V, electrolytic
- *C9, *C15—50 μF , 25V, electrolytic
- *C10, *C12—.0015 μF , 25V
- *C11—2 μF , 25V, electrolytic
- *C13, C25—1000 μF , 25V, electrolytic
- *C14, C22—2 μF , 150V, electrolytic
- C16—25 μF , 225V, electrolytic
- C17, C20—250 μF , 25V, electrolytic

- C18—.01 μF , 50V
- C19—.05 μF , 200V
- C21—.0022 μF , 50V
- C23—.33 μF , 150V
- C26—.0082 μF , 150V
- D1—1N914 diode
- D2-D7—400PIV, 2.5A rectifier (GE504 or equal)
- *Q1—2N4126 transistor
- *Q2, *Q3, *Q4, Q5-Q8—2N4125 transistor
- L1—222 mH inductor
- *V1—7735 vidicon tube
- T1—10K-2K impedance matching transformer (Radio Shack No. 2731378 or equal)
- T2—10-turns on TV flyback (see text)
- T3—117V primary; 24V, 1.2A secondary
- Vidicon filament transformer 117V primary; 6.3V CT, 3A secondary
- *Two each of the components are required to construct both video channels.
- MISC—two 4 \times 2 1/2 \times 1 1/8 in. aluminum mini-boxes (Bud no. CU3002A) 1/2 in. plywood mounting board, aluminum sheet metal for camera case, lenses, yokes, deflection coils, lens mounts, vidicon sockets, color filters, prism, wire, solder, etc.
- NOTE: the following parts are available from Denson Electronics, P.O. Box 85, Longview St., Rockville, CN 06066. Two yokes and focus coils no. CY101-1547, two vidicon sockets, two Comsicar 32939 lenses, two size C lens mounts. The following parts are available from Edmund Scientific Co., 91 Edscorp Bldg., Barrington, N.J. 08007. One 2x2 in. Plexiglas red no. 2423 color filter, two 2x2 in. Plexiglas green no. 2414 color filters, one cube prism.**

Blanking and sync

Transformer T1 supplies both the vertical sync and the vertical blanking signal. The center tap of the 2K secondary is grounded. Phasing should be observed with an oscilloscope insuring that the positive going pulse is applied to test point C1. Capacitor C8 stretches the pulse and sets the amplitude to 7 V P-P. Capacitors C6 and C7 then apply the blanking pulse to cut off the vidicon cathodes during vertical retrace. C8 may have to be selected for use with some types of vidicons if black retrace lines appear in the picture. The other half of the secondary feeds a negative-going vertical sync pulse to diode D1. Polarity of diode D1 should be observed as shown on the schematic. A horizontal sync pulse is taken from point A2 and fed to the monitor separately.

Initial vidicon tube adjustments

The following adjustments are made with all voltages and scanning signals applied to the camera from the B/W monitor. Potentiometer R3 serves as a focus control. Initially, the beam control R9 should be adjusted for maximum resistance. The target control should be adjusted for about 40 to 50 volts at the center terminal. The focus control should be set about midway. The beam control should be adjusted until blobs of light and dark areas ap-

(continued on page 74)

To meet the severe demands placed upon today's tape transports, manufacturers have, among other things, introduced logic control. Here's how they work.

inside today's tape transports

by LEN FELDMAN
CONTRIBUTING HI-FI EDITOR



LAST MONTH I DISCUSSED TAPE EQUALIZATION AND BIAS AND their effect on frequency response, signal-to-noise ratio and distortion of a tape recorder. These, and other purely electronic characteristics of tape recording and playback have been thoroughly covered in the high-fidelity literature in recent years. Considerably less emphasis has been given to the tape transport mechanism itself—the elements in a tape deck that mechanically position and move the magnetic tape over the tape heads.

Actually, the demands made upon a high-quality tape transport mechanism are much more severe than those upon a phonograph turntable of equivalent quality. The turntable is called upon simply to turn at a constant speed. The tape transport, in addition to moving tape at relatively slow speeds, must also be able to rewind or forward wind large and small reels of tape at very fast speeds and must be able to bring all motion to a safe stop without spilling, ripping or in any way damaging the tape.

From the earliest, purely mechanical, one-motor transport systems equipped with all kinds of friction-braking devices, multiple belts and other schemes subject to wear and misadjustment, the tape recording industry has progressed to a variety of fail-safe all-electronic, computer-logic activated transport systems that have no brake shoes or other friction devices—no mechanical linkages or gadgets to wear out.

A typical example of sophisticated electronics brought to bear on the mechanical functioning of a tape transport is to be found in Crown International's 800 series tape transport (Fig. 1). Its belt-driven capstan is powered by a hysteresis synchronous motor. In addition, two reel motors take care of tape-up and tape-feed tension, fast forward, rewind and braking.

In PLAY, take-up tension is controlled by an AC voltage applied to the take-up motor, while feed tension is controlled by an AC voltage applied to the tape-feed motor. In FAST FORWARD or REWIND, the pulling motor is fed a full 117 VAC while the opposite motor has only 35 VAC applied for a slight holdback tension. All of these actions, including automatic shut-off whenever tape runs out or whenever a transparent segment of tape passes through, are governed by fully electronic command signals derived from digital electronic circuitry that is detailed in the schematic diagram of Fig. 1. Crown's excellent owner's manual gives the user a complete insight into the functioning of the transport and its electronics, and from it we were able to derive the following explanation of the various sections of the circuitry.

Tape sensing

The tape sensor feeds a "stop" command to the computer

(commands, memory and gates sections) whenever the tape runs out or a transparent length of tape is sighted. This is done by positioning a photocell (PC1) on one side of the tape path and a lamp on the other (See Fig. 1.). Light reaching the photocell causes its resistance to decrease, turning on transistor Q11 and presenting a low ("0") voltage to the input of inverter IC1-f. The output of this inverter is then a high ("1") voltage which gives the "stop" command through transistor Q12.

The tape sensor circuitry also incorporates a dual-speed function. A longer time span, is required before the stop command is issued when the transport is in PLAY than when it is in FAST-WIND since the tape is moving at a slower rate. When operating in PLAY, transistor Q10 is turned on, placing capacitor C19 in the photocell circuit and increasing its time constant. In any mode but PLAY, the circuit senses a transparent length of tape or senses when the tape runs out in from 1 to 3 milliseconds. In PLAY, it takes more than 10 ms for the stop command to be issued. This prevents an erroneous stop command caused by poor splices or pinholes in the tape.

Motion and direction sensing

Since the direction and speed of the tape has a direct bearing on reel tensions and reel braking, a system of motion and direction sensing had to be devised for the transport. Circuitry for this function is shown in the upper left block of Fig. 1. Mechanically, the motion sensor uses a pair of slotted discs that modulate a light beam in front of one of two photocells (PC2 and PC3). The first disc rotates with the tape-feed reel motor shaft and causes the light to flash on the photocell whenever this shaft rotates. The second disc forms an aperture



TRANSPORT SECTION of Crown series 800 tape recorders. Audio electronics is a separate circuit.


**Communications
Engineering**

**Aeronautical
& Navigational**


**Television
Engineering**



**Automatic
Control
Engineering**

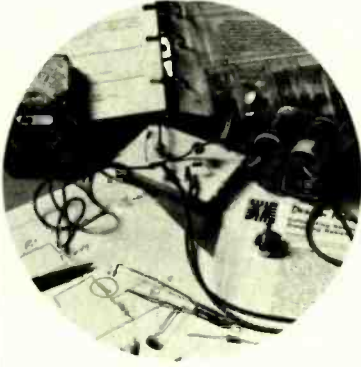


**Missile &
Spacecraft
Guidance**

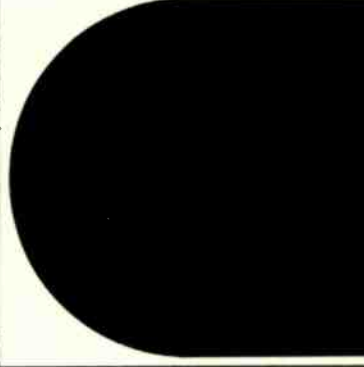


**Radar &
Sonar
Engineering**




**Digital
Communications**

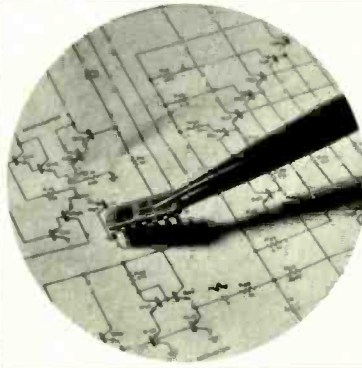

**Industrial
Electronics**

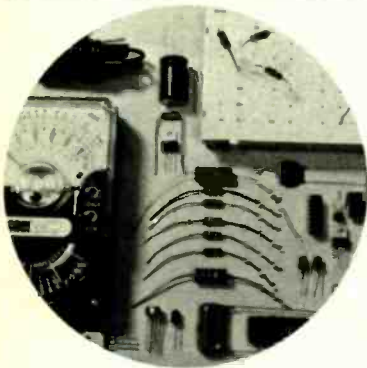


**Microwave
Engineering**

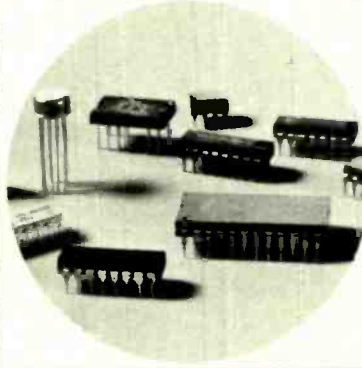

**Satellite
Communications**




**Cable
Television
Engineering**

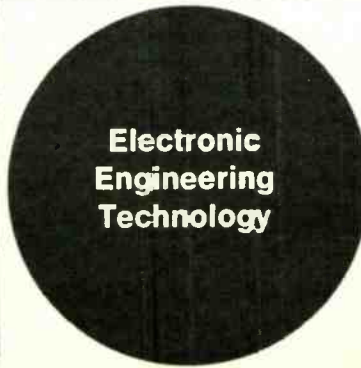

**Electronic
Engineering
Technology**

**Nuclear
Instrumentation
& Control**

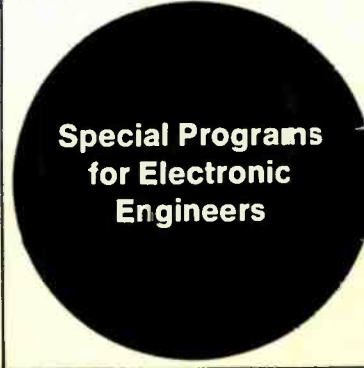

**Special Programs
for Electronic
Engineers**

ADVANCED ELECTRONICS CAREER TRAINING AT HOME

Computer
Engineering

If you are too busy to go to college to learn advanced electronics, CREI brings college level training to you. CREI programs give you practical engineering training that you can apply in your work to move ahead to higher paying jobs. And CREI lets you specialize in exactly the area of electronics you want. You have a choice, depending on your qualifications, of 18 different programs.

Not only are CREI programs college-level but arrangements are available for you to earn college credit applicable to advanced degrees.

Only CREI offers you a choice of 18 programs in advanced electronics

Electronic
Systems
Engineering

For over 45 years CREI programs have been recognized by leading technical organizations as effective home study training in advanced electronics.

NEW OPTIONAL LAB PROGRAM



CREI now offers a supplementary ELECTRONIC DESIGN LABORATORY PROGRAM to make learning advanced electronics easier and to give you actual experience to use in your work. Only CREI offers this complete college type laboratory program. You learn to actually design electronic circuits. At the same time you get extensive experience in tests and measurements, breadboarding, prototype building and other areas important to your career.

Qualifications to Enroll. To qualify for enrollment in a CREI program, you must be a high school graduate (or equivalent). You should also be working in electronics or have previous training in this field.

Send for FREE book. If you are qualified, send for CREI's newly published book describing your career opportunities in advanced electronics. This full color book is filled with facts about career opportunities for you.

Nuclear
Engineering
Technology



Accredited Member, National Home Study Council

CREI, Dept. E-1408-F
3939 Wisconsin Avenue
Washington, D.C. 20016

Rush me your FREE book describing my opportunities in advanced electronics. I am a high school graduate.

Name _____ Age _____

Address _____

City _____ State _____ ZIP _____

If you have previous training in electronics, check here

Employed by _____

Type of Present Work _____


Veterans and servicemen, check here for G. I. Bill information

Special Programs
for
Non Electronic
Engineers

CREI

**CAPITOL
RADIO
ENGINEERING
INSTITUTE**

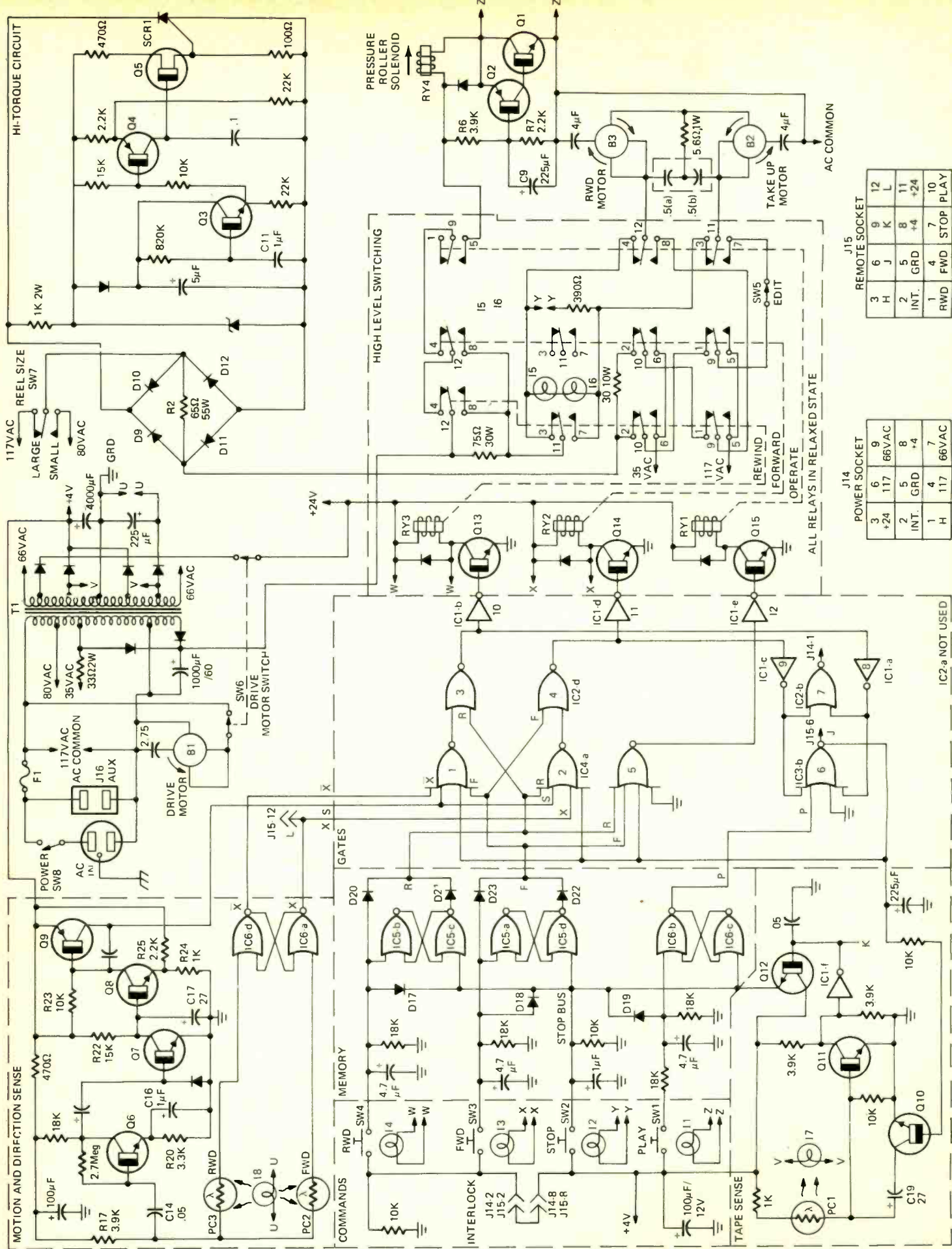A Division of McGraw-Hill
Continuing Education Co.
3939 Wisconsin Avenue,
Washington, D. C. 20016



J14
POWER SOCKET

3	+24	9	66VAC
2	INT.	8	GRD +4
1	H	7	66VAC

J15
REMOTE SOCKET

3	H	9	L
2	INT.	8	+24
1	RWD	4	FWD
		10	STOP
		11	PLAY

FIG. 1—ELECTRONIC CONTROL section of the transport system.

between the first wheel and the photocells, masking one cell while revealing the other. This second disc is fastened to a ball bearing that rides the rotating shaft and is free to turn with it until it encounters a stop where it exposes either the forward or the rewind photocell, depending upon the direction of motor rotation.

The photocells have one common lead that supplies power to them. Each cell is connected to the input of a set-reset direction-sensing flip-flop (IC6-a and IC6-d). This flip-flop stores the direction information received from the last light pulse seen by the photocells. If the last photocell illuminated was the forward cell then the flip flop remains in the set state. Storing this direction information makes it available even during the dark half of a light flashing sequence. When light flashes on one of the photocells, its resistance changes, developing a pulsating DC voltage on supply resistor R17. This voltage is coupled via C14 to Q6 where it is amplified. Because the photocell output decreases with increasing frequency, emitter resistor R20 is bypassed by C16 to increase the gain of Q6 at higher frequencies.

Transistor Q6 drives a detector circuit that provides a low voltage ("0") when pulsating DC is detected. A threshold detector made up of Q8, Q9, R23, R24 and R25 measures the voltage stored on capacitor C17. As motion occurs, transistor Q7 is intermittently turned on by the pulsating DC voltage from Q6. This causes C17 to be discharged at a rate higher than it is being charged by R22, turning off the threshold detector. Time constants are arranged so that motion can be sensed almost immediately. But to sense a lack of motion (stop condition), a short delay formed by the time constant network R22 and C17 must elapse. This permits high braking to continue even after rotation has slowed down to a rate too low to be detected by the motion sensor.

Tape lifter and pressure roller pull in

Tape guides and heads are positioned so moving tape does not contact the heads except when the transporter is in PLAY. A tape-lifter assembly provides enough tape to the head con-

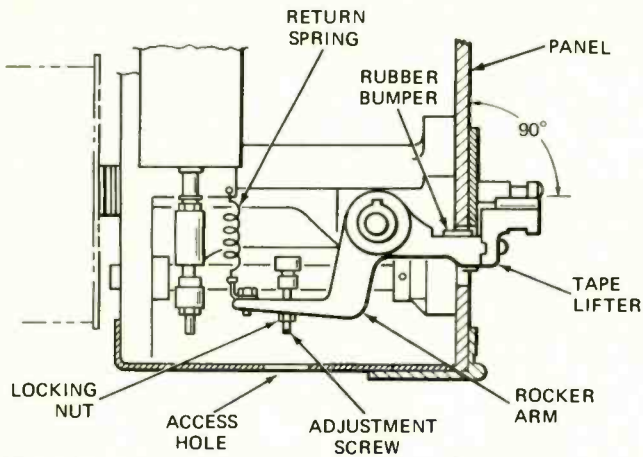


FIG. 2—Tape lifter assembly moves tape against the heads during play mode.

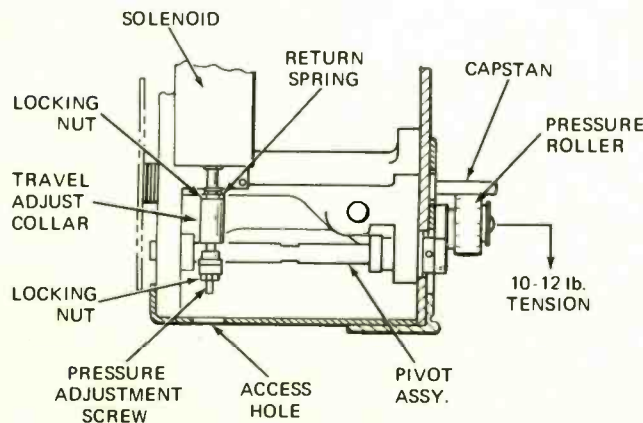


FIG. 3—SAME SOLENOID used in tape lifting also applies the pressure roller against the tape capstan during the play mode.

tact area when the transport is in PLAY. A cross section of the tape lifter assembly is in Fig. 2, while Fig. 3, shows the same tape lifter solenoid applying the tape pressure roller during PLAY. Powered through relays from the same power supply that is used for the braking system, the pressure roller and tape-lifter solenoid relaxes after pull-in due to an electronic circuit in series with the solenoid coil.

The voltage drop across transistor Q1 (see Fig. 1) is essentially the same as the voltage on capacitor C9. At turn on, C9 is at zero volts and begins charging towards a value determined by voltage divider R6 and R7. During the beginning of this charge cycle, the solenoid becomes seated. Once seated, its power requirements are substantially reduced. For this purpose, lamp I1 (shown in the "commands" section of Fig. 1) is wired in parallel with Q1. If the "play" lamp (I1) is on, it indicates proper operation of the solenoid relaxing circuit, in addition to its more obvious indicating function.

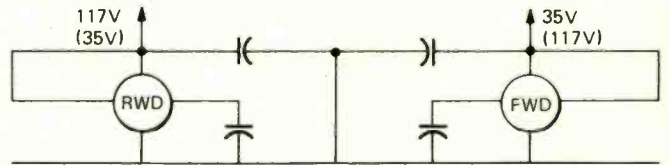


FIG. 4—VOLTAGES SHOWN without parentheses are applied to reel motors during rewind. Voltages in parentheses are applied during fast forward.

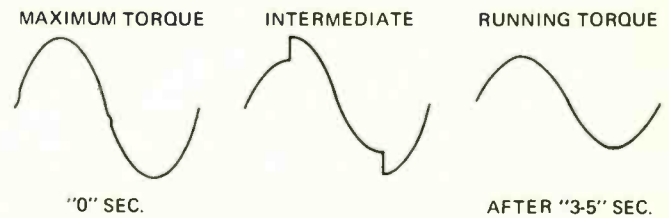


FIG. 5—VOLTAGE WAVEFORM sequence for high starting torque.

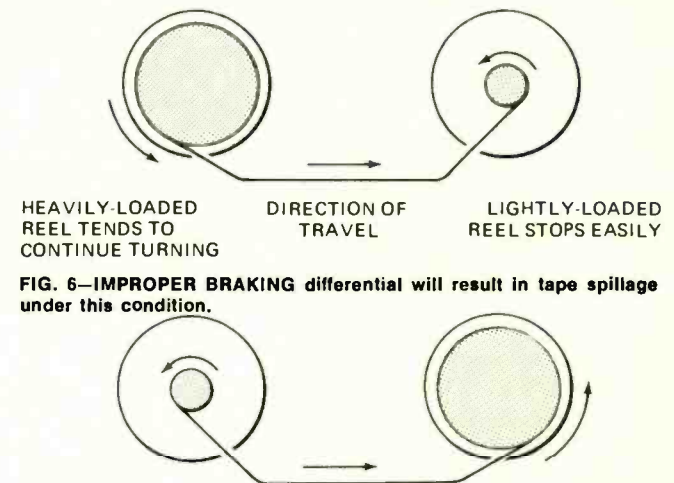


FIG. 6—IMPROPER BRAKING differential will result in tape spillage under this condition.

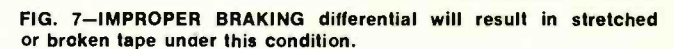


FIG. 7—IMPROPER BRAKING differential will result in stretched or broken tape under this condition.

Powering the reel motors

During FAST REWIND and FAST FORWARD, full 117 VAC is applied to that reel motor which is doing the pulling, while the trailing motor is fed approximately 35 VAC, as in Fig. 4.

To get fast, smooth starting when going into PLAY, extra power is applied to the reel motors to help them overcome stationary inertia. If this extra torque is not reduced gradually, a wobble appears in the tape motion. To provide this drop-back, a two terminal network is placed in series with the reel motors. The impedance of this network is very low for a second or so, increasing to its maximum value after about three seconds. The network consists of resistor R2 shunted by an

(continued on page 89)

All About OSCILLOSCOPES

*PART III—Operating the oscilloscope properly
is covered plus several measurements
that can be made*

by CHARLES GILMORE*

USING MOST TEST-EQUIPMENT IS STRAIGHT-forward and little knowledge is required by the user when moving from one manufacturer's product to another or when performing simple tasks. The oscilloscope does not follow this pattern.

The many types of oscilloscopes available and the relative complexity of all oscilloscopes in comparison to other test-instruments make it necessary for the user, especially the casual or infrequent one, to follow some simple initial operating rules. If they are not followed, you'll waste a lot of time and effort while attempting the apparently simplest of procedures. Therefore, in this article we will establish initial operating rules for an oscilloscope. Once mastered, you'll know how to use a seemingly more complicated and sophisticated instrument such as a triggered scope.

A trace on the screen

When using a new or unfamiliar oscilloscope, the first step is to get a trace. Plug in scope. Turn it on and let it warm up. Some oscilloscopes, especially those using vacuum tubes, require as much as one to two minutes before any trace can be obtained. All scopes should be allowed additional warm-up time before use to eliminate trace drift. After warm-up, set the time base (horizontal or sweep frequency) switch to a medium sweep-speed and place the AUTO/NORMAL switch (triggered oscilloscopes) in the AUTO position. Turn up the intensity control with the vertical and horizontal position controls set at the center of rotation. A trace in the form of a horizontal line, should appear. If, at full intensity, there is no trace, look for a general lighting or glow at one of the edges. This gives an indication of the off-screen direction of the trace. Then use the vertical and horizontal position controls to center the trace on the screen.

If this technique does not work, a more systematic approach may be used. Return the vertical and horizontal position controls to their midway points. Now systematically rotate the horizontal position control in small increments. After each correction of the horizontal position control, move the vertical-position control through its entire range to locate the trace. Do not rotate the vertical-position control quickly or the beam may cross the CRT face too rapidly to be seen.

*Design Engineer Heath Company, Benton Harbor, Mich.

Beam adjustments

Once you've got the trace, switch the time base to the external horizontal position. A dot rather than a line should now appear on the face of the CRT. Adjust the focus, intensity and astigmatism controls for the smallest roundest dot possible. This procedure insures the sharpest trace. The FOCUS, INTENSITY, and ASTIGMATISM controls all interact. When in use, trace brightness variations may require refocusing.

Displaying a waveform

Adjust the vertical and horizontal position controls to center the trace vertically and to start the trace at the left side of the CRT. Set the time base at a mid-range position, for internal trigger or synchronization (either + or -). Triggered scopes should be in the auto mode.

Once you have a trace, a signal must be connected to the scope to observe a waveform. Obviously, you need some form of cable or probe to connect the signal to the vertical input jack. Then the vertical input switch is used to select the AC or DC position, depending upon the information desired from the trace. A common error is to leave the vertical input selector AC-DC-GROUND switch in the GROUND position. If uncertain about the relative amplitudes of AC and DC components of the input waveform, use the AC position first. Select an attenuator setting commensurate with the expected input signal amplitude. If the amplitude is unknown, use the *highest* attenuation level (lowest sensitivity) possible. Adjust the attenuator to produce a trace from $\frac{1}{2}$ to $\frac{3}{4}$ of screen height. When performing initial adjustments, keep both the vertical attenuator and the horizontal-variable controls in their calibrated positions. Leaving these controls in their uncalibrated positions is a frequent source of error.

Once you have a trace, set the time-base switch to display a few cycles of the input waveform. The trace may not be stable at this time; however, you should be able to see enough of the unstabilized trace to determine an approximate time-base setting. With this setting, a triggered scope in the auto position may need level-control adjustment to produce a stable pattern. Some scopes use the level control in the AUTO position and some do not. With the recurrent-sweep oscilloscope, the coarse and fine time-base controls are set to produce the desired number of cycles of display.

If there is a sync-level control, you may have to adjust it to stabilize the trace.

Triggering in the automatic mode

The auto mode of triggering is the one that is most frequently used. Auto triggering has the advantage of maintaining a trace (baseline) when triggering is lost because of low-signal levels.

Auto trigger is designed to trigger relatively simple waveforms above 100 Hz to an upper-frequency limit near that of the scope's vertical bandwidth. If the frequency of the waveform is out of this range or the waveform is complex, normal mode is preferred.

In the AC-coupled auto mode, a trigger signal is generated when the displayed waveform passes through the zero voltage point of the AC portion of the waveform. AC-coupling should be used, as the auto mode is not designed for low-frequency work. Below the frequency that is the automatic trigger-rate of the baseline generator, the automatic baseline generator takes over between cycles of the displayed waveform. When this occurs, normal mode should be used.

When DC-coupled automatic triggering is used (not available on all oscilloscopes), a triggering signal is generated as the displayed waveform passes through an imaginary line representing zero volts. The user must be sure that the signal does pass through this zero-volt line to get triggering. To determine where this imaginary line is, set the vertical input selector switch to the ground position. This operates the automatic baseline generator and establishes a trace whose position is the zero-volt imaginary line. Varying the vertical position control varies this line that represents the triggering point. DC-coupling of the automatic mode may be required when examining signals with low duty cycles, or those with a DC offset greater than their AC amplitude. Figure 14 shows the effect of varying the vertical position control with AC and DC trigger coupling in the automatic mode.

If AC/DC trigger coupling is not available on a particular oscilloscope and DC coupling is necessary to properly trigger the waveform, switch to normal triggering. Such scopes consider auto triggering AC-coupled and normal triggering DC-coupled.

Slope control

The SLOPE control permits the user to

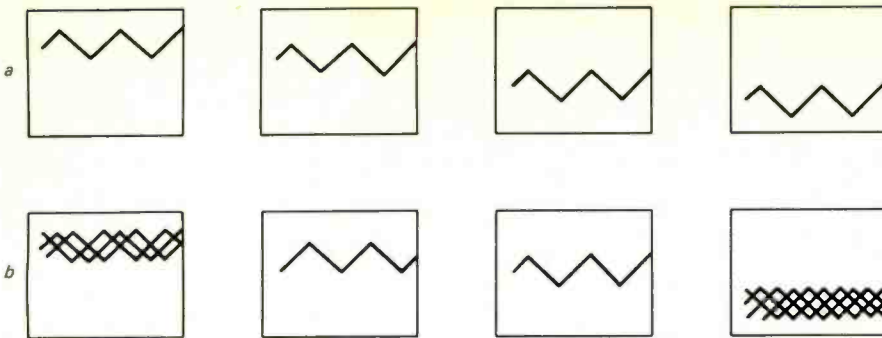


FIG. 14—WAVEFORMS shown in a are AC triggered. Waveforms in b are triggered via DC coupling.



FIG. 15—EFFECT OF TRIGGERING on positive edge is shown in a, while negative edge is shown in b.

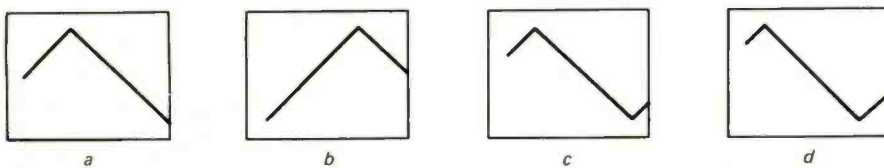


FIG. 16—THE EFFECT of varying the trigger level control while observing a triangle waveform.

select triggering on either the positive- or the negative-going slope of the waveform. Figure 15 shows the effects of slope adjustment. One of the most important uses of the SLOPE switch is when examining pulses where the desired point for observation is on one edge or another of the waveform. Slope selection followed by trace expansion with the time-base control will permit detailed examination as shown in Figure 15. The SLOPE control is independent of trigger mode or coupling.

Triggering in the normal mode

Normal mode triggering is useful when you want to trigger at a specific point on the displayed waveform. When normal mode is used, the LEVEL control is used as well as the COUPLING and SLOPE controls. Figure 16 shows the effect of varying the LEVEL control on a triangle waveform. The NORMAL mode is needed only when the signal cannot be properly triggered in the AUTO mode. An oscilloscope being used at the limits of its frequency capability requires the normal mode for good triggering.

At the opposite end of the frequency spectrum, the NORMAL setting is also required. As noted above, the automatic baseline generator may interfere with low-frequency triggering in auto mode, and on some oscilloscopes there is no way to truly DC-couple the trigger signal in the auto mode. In this case, signals that are extremely low in frequency or those having DC-offsets greater than their AC amplitude must be triggered in the normal mode. This is especially true of older scopes. In some modern oscilloscope designs, the difference between automatic and normal

modes is simply one of an automatic baseline generator. In these instruments, the reason for using the normal mode may be no more than keeping a trace off the CRT when no signal is applied or for very high frequency operation.

Vertical measurements

The simplest of all vertical measurements is peak-to-peak amplitude. Figure 17 shows a waveform with a 3-cm vertical

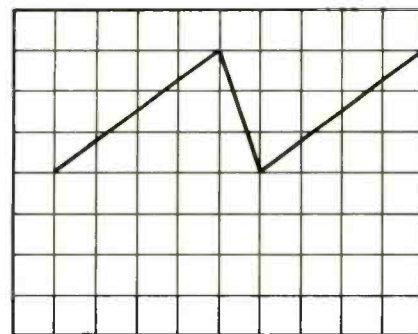


FIG. 17—A RAMP SIGNAL displayed on an oscilloscope with a calibrated vertical attenuator.

amplitude. The vertical attenuator is set at 0.2 volts-per-cm to produce this display; therefore, the waveform amplitude is 0.6 volts ($3\text{cm} \times 0.2\text{ V/cm}$). Remember, the measurements are peak-to-peak voltage measurements. An oscilloscope cannot make RMS or average measurements directly. Such measurements must be calculated by knowing the peak-to-peak amplitude and dividing by 2.828 (for triangle waveforms only) to arrive at an RMS value.

For the square wave (50% duty cycle), the peak-to-peak value is its RMS value. However, with more complex waveforms, conversions involve extensive calculations.

If the oscilloscope has DC-coupling, DC voltages can be measured. A measurement of a DC plus an AC voltage can also be determined. Figure 18-a shows AC-coupling with the waveform centered on the screen. The oscilloscope is set to 10 mV/division. A sinewave signal is measured at 60 mV peak-to-peak. In Figure 18-b, the

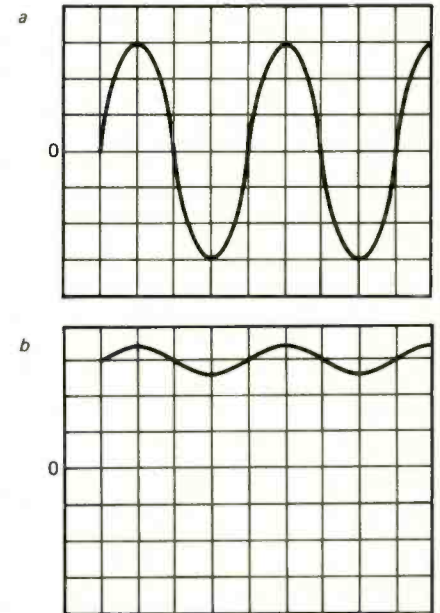


FIG. 18—MEASUREMENT of the peak-to-peak amplitude of an AC signal riding on a DC offset voltage.

input attenuator reduces the sensitivity of the oscilloscope to 1 V/division. DC coupling shows the AC waveform to be riding on a DC signal of 3 volts. Using the ground position of the vertical input coupling switch is a common way to establish the zero-volt reference line.

Horizontal measurements

While vertical measurements yield signal amplitude, horizontal measurements give a measurement of time. Most triggered oscilloscopes with calibrated time bases specify the time-per-division. As most measurements involve more than one division, a multiplication of the time-per-division settings and the number of divisions involved is required.

If the magnifier is used, the final period measurement must also include the magnifier multiplier.

The period of a waveform is defined as the time required for the waveform to completely repeat itself. With a triggered oscilloscope having a calibrated time base, this measurement can be easily made. Suppose that the length of a sawtooth waveform is 5 divisions. The time base setting for the display is 0.5 ms-per-division. The period of the waveform is 0.5 ms-per-division multiplied by 5 divisions, or 2.5 ms. The reciprocal of period will yield frequency, in this example, 400 Hz.

Risetime measurements

As previously indicated, risetime is the time required for the leading (positive

going) or trailing (negative going) edge of a wave to pass from 10% to 90% of its full amplitude. When measuring rise-time, it is preferable to expand the trace, by adjusting the timebase, to spread the rise or fall of the signal over as many horizontal divisions as possible. A slope of 45° is the most desirable although it is not always achievable.

The signal should also be spread over as many vertical divisions as possible. Use the variable vertical attenuator to reduce the amplitude of the signal to an integral number of divisions (five for example.) Such an adjustment facilitates measuring the 10% and 90% amplitude points. Using the variable vertical attenuator may introduce some error in the risetime measurements. Do not use this adjustment if extreme accuracy is desired, or if the measurement is near the risetime specification of the oscilloscope.

Dual-trace measurements

When using a dual-trace scope, the operator must decide on alternate or chopped mode and trigger source selection (channel 1, channel 2, or mixed).

Some dual-trace scopes require the operator to select between chopped and alternate modes. Other scopes do this automatically. The optimum point to switch from chopped to alternate mode will vary slightly with the waveforms to be observed. However, changeover as the timebase reaches 1 ms-per-division is a good choice.

Chopped mode at fast timebase rates will produce a square wave on the CRT with no signals applied to the oscilloscope. This can be confusing. Triggering selection usually offers the alternatives of one of the two vertical input channels, or the combination of both channels. If the two signals to be observed are time (phase) related, but have a frequency difference, triggering should be selected from the lowest frequency channel. For example, Figure 19 shows a dual-trace display of the

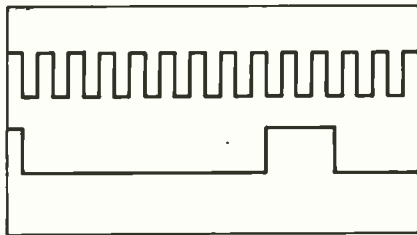


FIG. 19—INPUT AND OUTPUT waveforms from a BCD counter. Triggering is on the trailing edge of output waveform.

input and output waveforms of a BCD TTL counter. The upper trace is the input and the lower is the output. Triggering is selected to be on the negative slope of the lower waveform, thus insuring only one sweep for each output pulse.

If two signal channels have no time or phase relationship and may have a frequency difference, the combination mode may be desired.

One of the most common uses of the dual-trace scope is to compare an output waveform to an input waveform for general changes in the wave-shape. The position controls may be used to superimpose

the input and output waveforms, making differences quite noticeable.

Another useful dual-trace measurement is to determine time differences. Figure 20 shows 300-ns delay between the leading edge of the upper and the leading edge of the lower pulse. A common source of error in time measurements is improper trig-

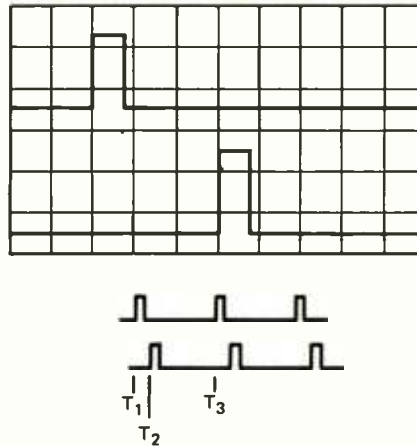


FIG. 20—MEASUREMENT of delay time between two pulses. Triggering must be from upper waveform.

gering source selection. The triggering must be made from the start signal. Using the stop signal as a trigger source would yield a measurement of stop to start time, which may or may not have meaning. Think in terms of cause and effect when selecting the trigger source for such measurements.

X-Y frequency measurements

An application that is older than the oscilloscope itself is a measurement of frequency by the use of the Lissajous pattern. It can be shown geometrically, that plotting two sinewaves of the same frequency, but with a 90° phase-shift, will result in a circle. This leads to a technique for frequency measurement. A reference frequency is applied to the horizontal axis of an oscilloscope (operated in the X-Y mode) and an unknown frequency of the same amplitude is applied to the vertical axis. When a perfect circle or, for all practical purposes, something close to a perfect circle, is achieved, the two frequencies are identical.

The difference between the frequencies of the X and Y signals, for small differences, may be measured by watching the circle alternately collapse and expand (rotate). Two circles will be produced each second for each cycle of difference. For example: suppose the horizontal axis is supplied with a 100 kHz reference frequency and the unknown frequency is applied to the vertical axis. If, in the course of 10 seconds, four perfect circles are made, there is a two cycle per 10 seconds or 0.2 Hz difference between the two frequencies. The measurement does not determine whether the reference frequency is higher or lower in frequency.

This technique does determine that the frequency difference is less than a certain amount. Such a technique is frequently used for setting oscillator frequencies within a certain tolerance. The upper-frequency limit of this technique is depen-

dent on the reference frequency available and the horizontal frequency capability of the oscilloscope.

The Lissajous technique may be expanded to measure frequency ratios. Figure 21-a shows the pattern created when the vertical frequency is twice that of the horizontal frequency. Figure 21-b shows

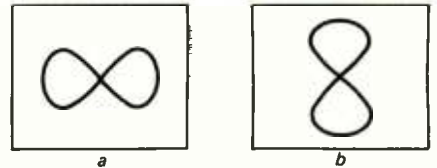


FIG. 21—LISSAJOUS PATTERNS for a two-to-one frequency relationship between horizontal and vertical signals.

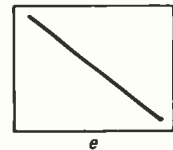
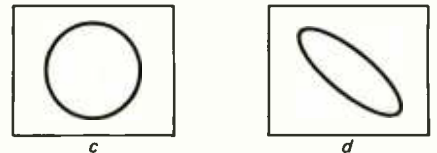
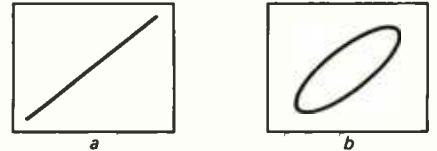


FIG. 22—LISSAJOUS PATTERNS FOR (a) 0°, (b) 45°, (c) 90°, (d) 135°, and (e) 180°.

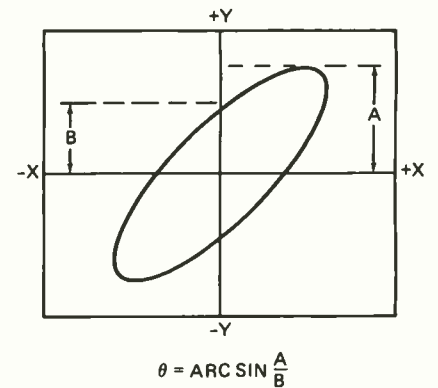


FIG. 23—PHASE ANGLE measurement. The X and Y amplitudes must be equal for the relationship to hold.

the opposite case, where the horizontal frequency is twice that of the vertical frequency. Fairly complex frequency ratios may be measured by this technique, but as the ratios grow larger, it is more difficult to maintain sufficient pattern stability long enough to determine the ratio. For most cases, limits of 5 to 1 are fairly reasonable. Lissajous patterns do represent a fairly realistic form of frequency measurement. The 60 cycle power line provides a reference with frequency stability in the order of .1 to .01%. (continued on page 86)

State of SOLID STATE

This month we will look at a monolithic power amplifier and a monolithic function generator.

by KARL SAVON
SEMICONDUCTOR EDITOR

THE INTEGRATED-CIRCUIT AUDIO POWER amplifier has been kicking around for a few years now. It's only recently though, that the full potential of the IC has been used. The beauty of the latest circuits is that they have effective burn-out protection built right in. They are *nearly* impossible to destroy. Nearly, because there is always someone who with seemingly little effort can do the impossible. Even though an amplifier is protected against shorts and elevated temperature, it can never be protected against excessively high power supply voltage. If a power supply is connected to an IC terminal and the control knob turned high enough, something is going to break down and pfft, there goes the IC. Cooking an amplifier chip beyond the maximum allowable junction temperature with an outside heat source is another way to destroy it.

When a manufacturer says an amplifier is fully protected, he means it will not be destroyed within the bounds of reasonable, sometimes unstated common sense qualifications. Usually the conditions are listed under the absolute maximum ratings. And if you expect 7 watts of audio out of a 14- or 16-pin dual-in-line package, and you forget to attach it to a large enough heat sink, the amplifier may not burn out, but neither will it amplify.

The nice thing about self-protected amplifiers is that you don't have to get carried away overdesigning heat sinks to protect against what might happen under abnormal conditions.

SGS-ATES 10-watt fully protected amplifier

The TCA940 monolithic power amplifier is perfect for low-cost stereo, tape recorder and radio applications. It typically delivers 10 watts into 4 ohms, but at 10% distortion. A more practical rating is 7 watts into 4 ohms at 1% THD. Working into an 8-ohm load the power output for 1% dis-

ortion is about 5 watts.

Two separate protection systems are built into the chip. One responds to accidents, the kind that happen when your screwdriver shorts the amplifier output terminals. You knew you shouldn't have been working with the amplifier turned on, but then you are a meticulously careful worker. . . . The other guards against the longer lasting problem, like external component failure. It reacts to chip overheating.

A short-circuit protection circuit limits the peak current in the output transistors. The schematic diagram in Fig. 1 doesn't show the protection cir-

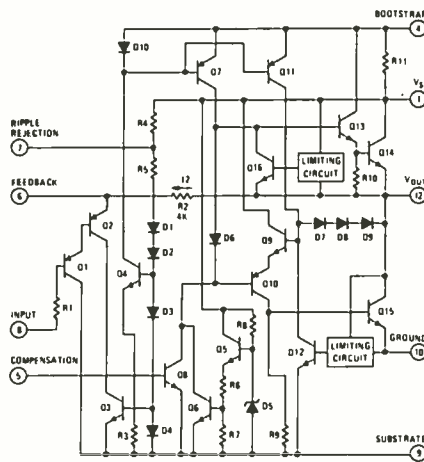


FIG. 1—TCA940 SCHEMATIC DIAGRAM. V_{out} is biased at precisely $V_{cc}/2$.

cuit details but shows a limiting circuit block connected across both the upper and lower output transistors Q14 and Q15. They are also connected in series with the bases of pull-down devices Q12 and Q16. In most IC audio amplifiers only the upper output transistor is protected. It is the one subjected to the most abuse.

The usual output short is to ground and it is the upper transistor that is overloaded. The lower transistor limiting circuit in the TCA940 gives protection against shorting the output

terminal to the power supply. Shorts on the speaker side of the output coupling capacitor will also overload Q15. Trying to force the output voltage to follow a decreasing input swing, the lower output transistor attempts to absorb the large amount of charge on its now purely capacitive load.

The only other thing known about the limiting circuit is that it controls peak power. As the collector-to-emitter voltage across either output transistor increases, the limiting current decreases. Fig. 2 shows this characteris-

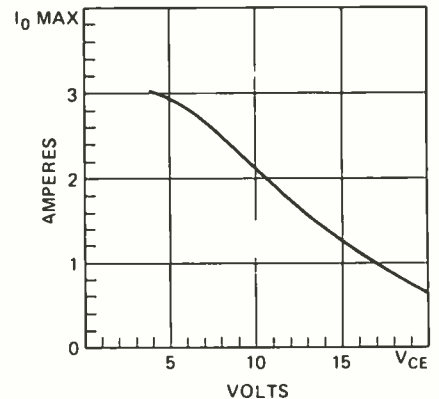


FIG. 2—GRAPH FOR THE TCA940 shows the current limiting vs. collector voltage.

tic. At 7 volts, the limiting current is 2.6 amps, and the power is $7 \times 2.6 = 18.2$ watts. At 14 volts, the limiting current is 1.4 amps, and the power is $14 \times 1.4 = 19.6$ watts, pretty much the same. I know 19 watts is much higher than the 8-watt absolute maximum power dissipation rating of the TCA940.

Remember though, that this is a short-circuit protection scheme. It limits the peak dissipation of the output transistors to prevent destruction of the transistors before the chip temperature has had time to change. It protects against failure due to local destruction of the devices or the metalization. The circuit has thermal

capacitance, the ability to soak up short bursts of peak energy. The transient-power capability of the circuit is much greater than its steady-state limitations.

If the overload is continuous or has a high duty cycle, the temperature of the chip rises rapidly and the second



SGS-ATES TCA940 monolithic power amplifier delivers 10 watts into 4 ohms.

protection system comes into play. With a 4-ohm load and 110°C chip temperature, the power output is sharply restricted, and it is completely shut down if the temperature gets as high as 125°C. The protection knee and final shutdown temperatures increase to 125°C and 135°C when working into 8 ohms. Q6 is the temperature sensing transistor which is located close to the output transistors. Zener D5 and emitter follower Q5 bias the base of Q6 through resistor divider R6-R7 at a voltage which is below the turn-on threshold of Q6.

The base-to-emitter junction voltage of a silicon transistor has a negative temperature coefficient; the turn-on threshold reduces at about 2-mV per °C. When the chip warms up, Q6 will turn on as its threshold voltage decreases below the voltage across R7. The collector current in Q6 pulls down

the drive to the base of output driver Q13 through D6.

Figure 3 shows the IC connected to the external components and power supply making a complete audio amplifier. C_r and C_e are frequency compensation capacitors. C_r is five times C_e 's value and C_e 's capacitance depends on the bandwidth and the AC coupled feedback resistor R_r . A graph on the data sheet gives the component values.

In the schematic (see Fig. 1) you can see R2, a 4K resistor, connected between the output pin 12 and the pin 6 feedback emitter of Q2. The typical open-loop gain of the amplifier is 75 dB or about 5600 times. For normal closed-loop gain in the range of 40 dB, the gain can be calculated by taking the inverse of the feedback factor $R_r / (R_r + R_2)$ which is $1 + R_2 / R_r$. R2 has a tolerance of $\pm 30\%$ plus a positive temperature coefficient of 0.2% per degree C.

The gain of the amplifier changes almost as the resistor does. If better gain stability is needed, an external resistor can be connected from the feedback resistor to the output load, shown by the dotted lines in Fig. 3. The added resistor R_c shunts the internal R2 lowering the parallel combination of the two. Choosing the external resistor at least ten times smaller than R2 makes the gain mostly dependent on the ratio of R_r and R_c .

To keep the gain up when the low external series feedback resistor is used, the value of R_r must also be lowered. Adding R_c gives a gain stability of ± 1 dB. Cd, the 100 μ F DC blocking capacitor, keeps the DC feedback from being affected by manipulations in AC feedback components. Notice that the amplifier does not have a differential input stage arrangement. The internal biasing of the amplifier sets the DC output at pin 12 at precisely one-half of the power supply voltage. Input terminal 8 is returned to ground through a 100K resistor. Since the bias current in the base of Q1 is only 0.5 μ A, the drop across the resistor is negligible and the base can be considered grounded. One end of R2 is returned to V_{out} and the other is 2 V_1 (junction-voltage-drops) above ground because of the series aiding Q1-Q2 base-emitter junctions. V_1 is the nominal 0.7 volt PN junction voltage.

The current in R2 is then $I_2 = (V_{out} - 2V_1) / R_2$. I_2 flows through Q2 into Q3. The current in Q3 is the same as the current in D4 which is $(V_s - 4V_1) / (R_4 + R_5)$. Setting $V_{out} = V_s / 2$ we get: $(V_s / 2 - 2V_1) / R_2 = (V_s - 4V_1) / (R_4 + R_5)$ Multiplying the top and bottom of the left hand expression by 2: $(V_s - 4V_1) / 2R_2 = (V_s - 4V_1)$

$/(R_4 + R_5)$ and the necessary biasing condition is: $R_4 + R_2 = 2R_2$ and $R_2 = R_4 = 4000$ ohms.


R_s and C_s is a Boucherot Cell for high-frequency stability, and bootstrap coupling capacitor C_s raises the input impedance to the upper output transistor to keep the upper part of the output waveform symmetrical.

The TCA940 is mounted in a 12-pin dual-in-line plastic package with two large tabs that conduct heat from the chip to an external heat sink. SGS-ATES calls it the FIN DIP package. In small quantities the TCA940 costs \$5.25 each.

More information including a printed board layout is available from SGS-ATES Semiconductor Corp., 435 Newtonville Avenue, Newtonville MA 02160.

EXAR monolithic function generator

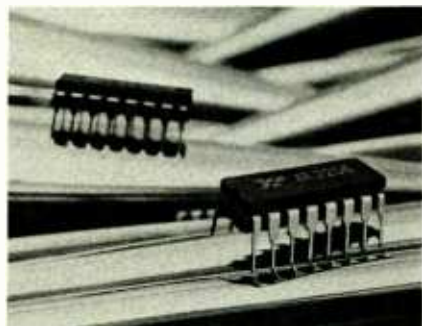A function generator is a versatile general-purpose signal source. It has a choice of output waveforms including sine wave, square, pulse and triangle signals. The linear triangle wave is



EXAR's XR2206C FUNCTION GENERATOR is capable of AM, FM, FSK, and PSK.

great for checking amplifier linearity or measuring triggering points of level sensitive trigger circuits. Sine waves of course are the common denominator source for most frequency and distortion measurements. Pulse and square waves give quick checks on transient response. Did you ever wish you could check a TV yoke but you didn't own a yoke tester, well I have. Drive the yoke from the pulse output of a waveform generator through an isolating resistor. The damped response displayed on a scope will tell you the condition of the coils.

The heart of modern function generators is a wideband voltage-controlled oscillator or VCO. One type of oscillator linearly charges and discharges a capacitor with constant current sources and sinks. Square and pulse waveforms are byproducts of this oscillator; they are used to switch between the charge and discharge cycles. Emitter-coupled astable oscillators with current source emitter loads are popular forms of this oscillator.

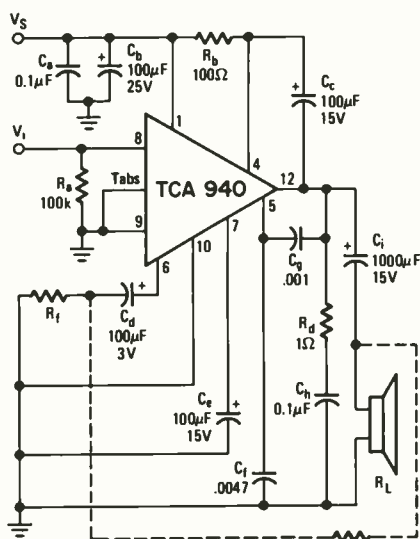


FIG. 3—TCA940 IN AUDIO AMPLIFIER application. Resistor R_c is connected for gain stabilization.

Step-by-step

TV Troubleshooters Guide

Color problems are not difficult if you follow a logical step-by-step troubleshooting procedure and circuit analysis.

by STAN PRENTISS

THE TWO PROBLEMS THAT STUMP SERVICE technicians the most are undoubtedly high voltage and color. Either one is solvable with a little patience, proper circuit analysis, and good test equipment. For instance, if a color receiver is hybrid or all tubes, the horizontal output tube drive voltage will have an exponential shape and usually measure about 250 volts AC. A transistorized horizontal output stage, being current driven, will have a rectangular shaped voltage, probably with a few transient spikes, and an amplitude of perhaps 10 volts fully loaded as it passes through the inevitable current-driver transformer to the base of the horizontal output transistor. If there is no high voltage and the drive waveforms are good, or the luminance section isn't driving the picture tube to cutoff, then the problem is with the horizontal output tube or transistor, a B-boost or shunt capacitor, the deflection yoke, or possibly the flyback trans-

former itself. Standard voltage and waveform checks will usually isolate the trouble. At the moment, however, we've got a color problem. The problem is not too difficult to solve if handled systematically.

When color comes & goes

The complaint on this Sears 562-10481 amounted to the simple statement that the "color comes and goes." And, indeed, a look at the picture tube with an on-the-air colorcast confirmed the obvious: color most assuredly came and went, and even when it remained for a few minutes, the color control could, by no means, produce saturation. Tint responded reasonably well but would not phase fully from flesh tones through green and magenta. So here were a pair of puzzlers worth attention.

A schematic of the chroma section is shown in Fig. 1. There's an L501 chroma takeoff coil—centertapped for

better impedance matching; a pair of chroma bandpass transistor amplifiers (Q501, Q502) their transformers (T501-T502) plus burst and the subcarrier oscillator. Of course there are the usual demodulators and RGB-Y outputs in this hybrid receiver but, in this instance they are eliminated from our search by immediate voltage checks and prompt tube substitutions. There was a slight increase in overall waveform amplitude, but nothing worthwhile, and cathode, grid, and plate potentials were well within the 10-15% tolerance. So it's back to the chroma and color sync circuits for investigation and analysis. And since these are basically transistor amplifiers, the only real way to do this is by examining signal passage, beginning with the 8KR8 (V201-a) video amplifier. First, however, I decided to do something a little different—and that was to quickly decide whether the problem is in the subcarrier portion of the color

TROUBLESHOOTING CHART (color problems)


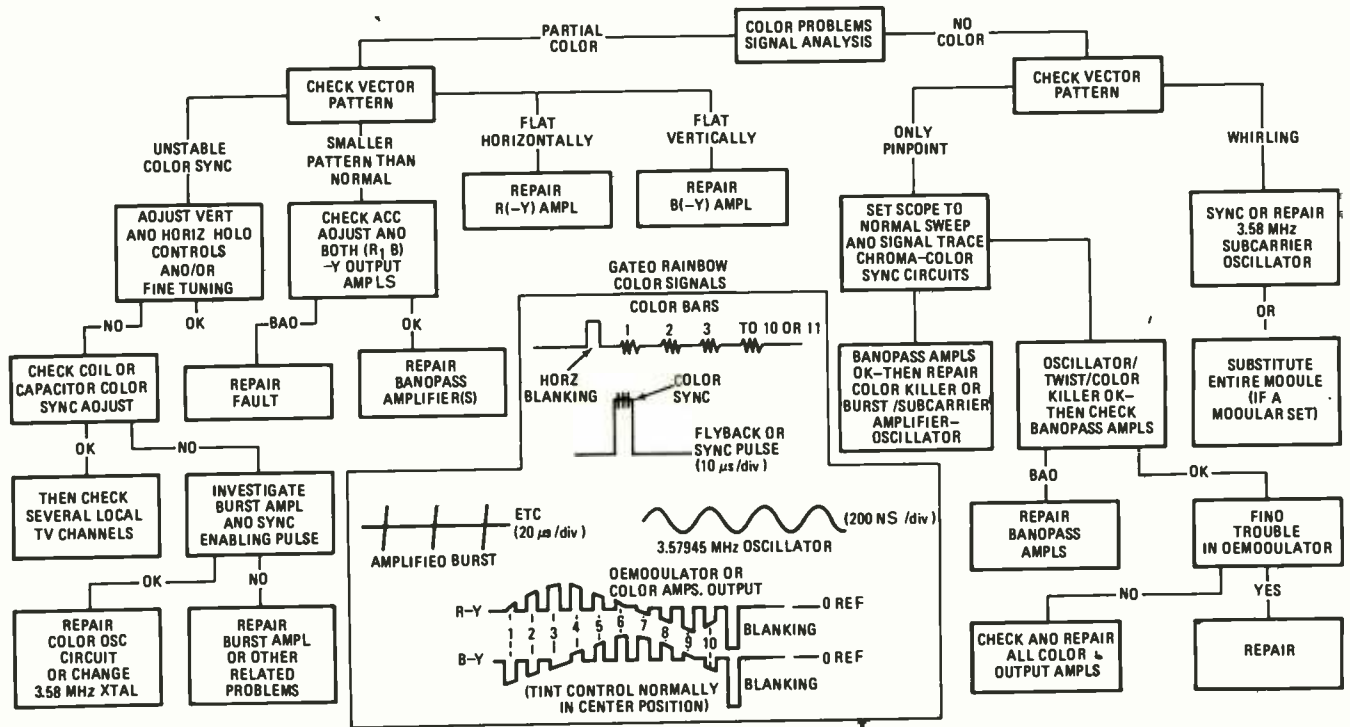


FIG. 1—SEARS MODEL 562.10481 hybrid color television receiver.

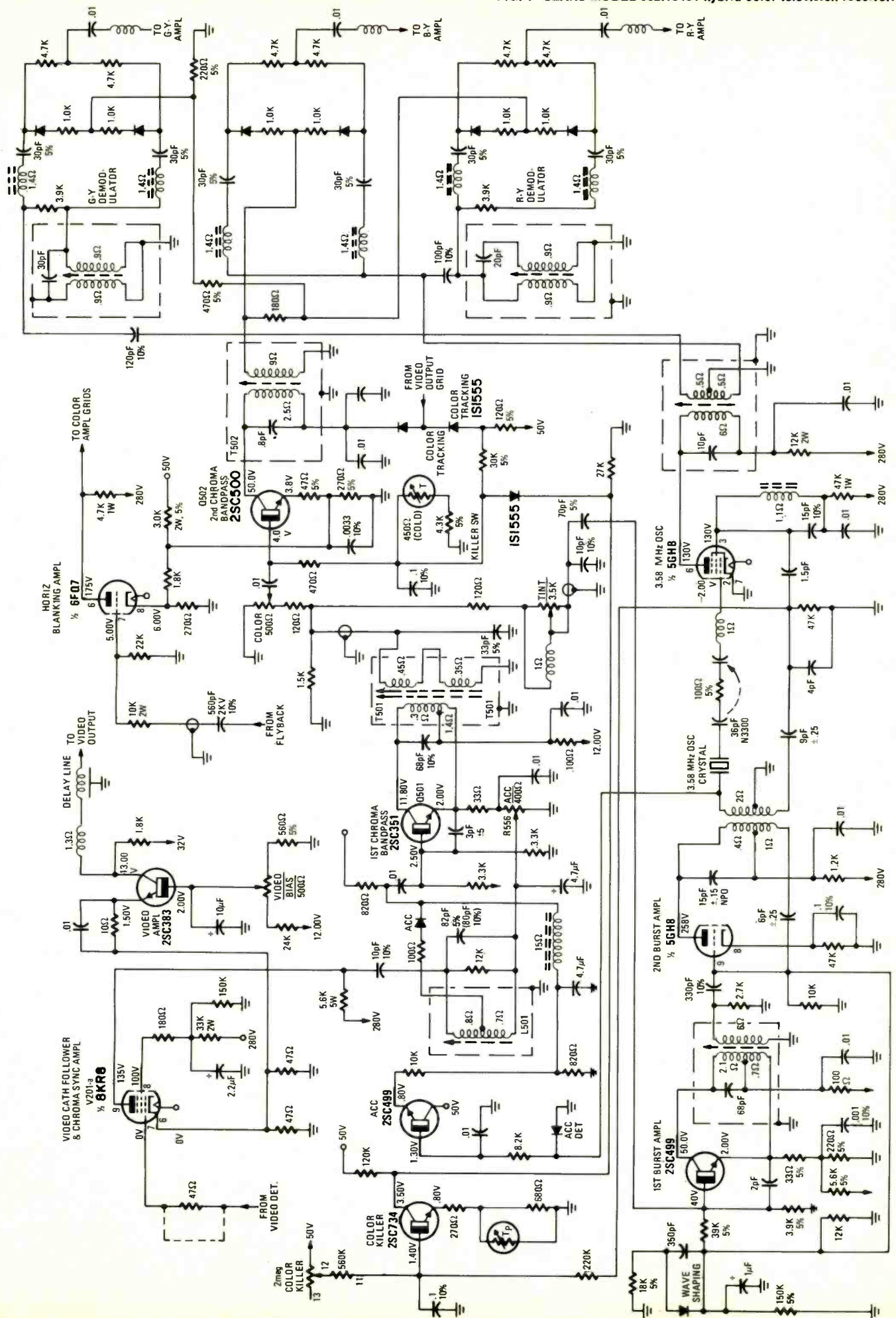

circuits or in the bandpass amplifiers.

Identifying the problem

So why not hook up a dual-trace oscilloscope at the R-Y and B-Y grids of the picture tube, put a *clean* color bar signal through the tuner, and see what the Y-Y (some say X-Y) vector pattern (Fig. 2) looks like. Since, with this method, you can actually see the entire operation of the chroma circuits. Therefore, with the scope's vertical amplifiers set for 20 volts/division, the pattern is very small, has lots of looped petals in the wrong places, and the blanking pulse is smeared. True, some of these contortions can be forced with misadjusted fine tuning, but that isn't our basic problem. The chroma amplifiers, themselves, are adding to the collective woes with low voltage output, although the subcarrier oscillator remains steady and in sync. Out of sync, the patterns spin, and if the color oscillator quit, there would be no vector pattern at all. Now both output amplifiers seem to be operating satisfactorily because neither the red vertical nor blue horizontal portions are affecting the small but relatively stable oval display. So our problem really becomes threefold: we want to straighten up the pattern with fine tuning, troubleshoot the chroma *amplifiers*, probably re-align the chroma amplifiers and touch-up the burst transformer for at least an overall 70-degree phase shift. This really isn't as difficult as it sounds—so let's go.

Signal analysis

With a 2-volt input into the 8KR8 chroma-sync amplifier from the video detector—as specified by the schematic—you want maximum swing from the plate of V201a to drive the 1st chroma bandpass transistor Q501. So a new 8KR8 (if this one's an original) often helps. The ACC potentiometer R556 can next be adjusted for Q501 maximum output. Now, if these changes don't do the trick, and the vector pattern hasn't expanded considerably in all directions, return the scope to normal operation and go after both bandpass amplifiers.

Since the input signal at the base of Q501 is only 30 mV and that at the base of second chroma bandpass amplifier Q502 has no visible amplitude, let's go to the *collectors* of both transistors and look at the AC waveforms as well as the DC levels simultaneously. The upper trace of Fig. 3, shows an amplitude of less than 1 volt at the collector of Q501, but with a normal DC collector operating potential of some 11 volts. There's about the same condition at the collector of Q502, shown in the lower trace of Fig. 3. Here the scope's vertical setting amounts to 10 volts/division, and exhibits an AC amplitude of a little over 8 volts, with

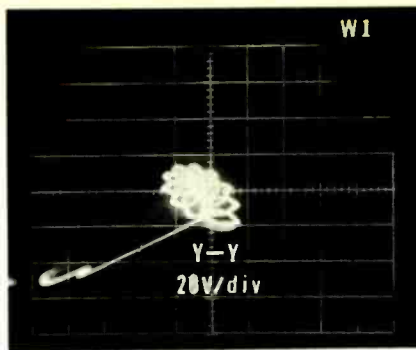


FIG. 2—POOR VECTOR PATTERN and distorted blanking bar was taken with a sensitivity of 20 V/div including the X10 attenuation of the low-capacity probes.

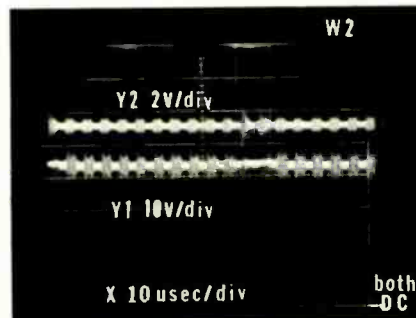


FIG. 3—COLLECTOR WAVEFORM of transistor Q502 is shown in the upper trace. Lower trace shows the waveform at the collector of Q501.

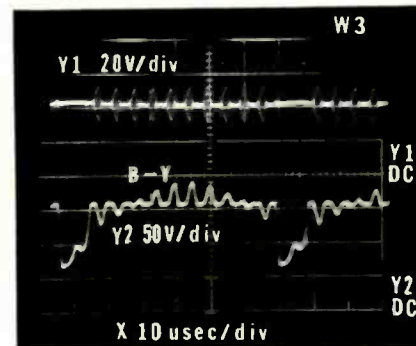


FIG. 4—NORMAL WAVEFORM at the collector of Q502 is shown in upper trace. Normal B-Y waveform is shown in lower trace.

a DC output of 45 volts. There are also DC readings of 5.9 volts at the base and 5.2 volts at Q502's emitter. These "slightly-off" base-emitter measurements, however, are nothing to become excited about since you don't know either the accuracy of the original meter readings, or whether a low impedance shunt may have taken place when the meter—whatever it was—was connected across the lower junctions of the transistor. But collector readings are usually pretty well on target, with one outstanding exception: instead of Q502's collector amplitude being 20 volts AC as specified, the output is less than half, even with bandpass transformer T502 impedances included. So, both the first and second chroma bandpass amplifiers—as the vectorscope indicated—seem to have AC problems.

Of course, it could be worse. For the most part, DC voltages are holding, so the power supplies are fine, and passive components such as bypass and coupling capacitors, resistors, and transformers are doing their filtering, signal flow, and impedance matching jobs. A quick ohmmeter shunt across the color control—with the set off, of course—verifies there are no problems here. Consequently, there remains but one principal action to take, and that is change one or both transistors since apparently there is leakage.

Cleaning up

Cross referencing the 2SC351 and 2SC500 in the transistor stock lists produces substitutes. Now, there's little to do but wick off all old solder about the original units with a 40-watt iron and some braid, and the new semiconductors are ready for insertion. This is easily done when the chassis bottom screws have been removed, along with the paper side chassis insulator. When both transistors are soldered securely, and

(continued on page 76)

R-E's Substitution guide for replacement transistors

PART XXIX

by ROBERT & ELIZABETH SCOTT

- ARCH—Indicates the Archer brand of semiconductors sold only by Radio Shack and Allied Radio stores. Allied Radio Shack, 2725 W. 7th St., Ft. Worth, Texas 76107
- DM—D. M. Semiconductor Co., P.O. Box 131, Melrose, Mass. 02176
- G-E—General Electric Co., Tube Product Div., Owensboro, Ky. 42301
- ICC—International Components, 10 Daniel Street, Farmingdale, N.Y. 11735
- IR—International Rectifier, Semiconductor Div., 233 Kansas St., El Segundo, Calif. 90245
- MAL—Mallory Distributor Products Co., 4760 Kentucky Ave., Indianapolis, Ind. 46241
- MOT—Motorola Semiconductors, Box 2963, Phoenix, Ariz. 85036
- RCA—RCA Electronic Components, Harrison, N.J. 07029
- SPR—Sprague Products Co., 65 Marshall St., North Adams, Mass. 01247
- SYL—Sylvania Electric Corp., 100 1st Ave., Waltham, Mass. 02154
- WOR—Workman Electronic Products, Inc., Box 3828, Sarasota, Fla. 33578
- ZEN—Zenith Sales Co., 5600 W. Jarvis Ave., Chicago, Ill. 60648

Radio-Electronics has done its utmost to insure that the listings in this directory are as accurate and reliable as possible; however, no responsibility is assumed by Radio-Electronics for its use. We have used the latest manufacturers material available to us and have asked each manufacturer covered in the listing to check its accuracy. Where we have been supplied with corrections, we have updated the listing to include them. The first part of this Guide appeared in March 1973.

	ARCH	DM	G-E	ICC	IR	MAL	MOT	RCA	SPR	SYL	WOR	ZEN
2S351B	NA	NA	NA	NA	TR-17	PTC 107	NA	NA	RT-183	ECG 160	NA	NA
2S363	NA	NA	GE-20	NA	TR-21	PTC 136	NA	NA	RT-114	ECG 123A	NA	NA
2S375	NA	NA	NA	NA	NA	PTC 109	NA	NA	NA	ECG 102	NA	NA
2S381	NA	NA	NA	NA	TR-21	NA	NA	NA	RT-107A	ECG 123A	NA	NA
2S471-1	NA	NA	GE-50	NA	TR-17	PTC 107	NA	NA	RT-183	ECG 160	NA	NA
2S494	NA	NA	NA	NA	NA	NA	NA	SK 3114	RT-115	ECG 159	NA	NA
2S501	RS276-2009	T-50	GE-61	ICC-50	TR-21	PTC 139	HEP-50	SK 3122	RT-102	ECG 123A	WEP 736	ZEN 100
2S502	RS276-2009	T-50	GE-61	ICC-50	TR-21	PTC 139	HEP-50	NA	RT-102	ECG 123A	WEP 736	ZEN 100
2S503	RS276-2009	T-50	GE-62	ICC-50	TR-21	PTC 139	HEP-50	SK 3122	RT-102	ECG 123A	WEP 736	ZEN 100
2S512	RS276-2023	T-52	GE-20	ICC-52	TR-53	PTC 133	HEP-52	SK 3039	RT-113	ECG 108	WEP 56	NA
2S608	NA	NA	NA	NA	TR-21	NA	NA	NA	RT-107A	ECG 123A	NA	NA
2S644	NA	NA	GE-16	NA	TR-51	NA	NA	NA	RT-127A	NA	NA	NA
2S701	RS276-2021	T-51	GE-60	ICC-51	TR-53	PTC 132	HEP-51	SK 3124	RT-100	ECG 123	WEP 53	ZEN 101
2S702	RS276-2021	T-51	GE-60	ICC-51	TR-53	PTC 132	HEP-51	SK 3124	RT-100	ECG 123	WEP 53	ZEN 101
2S703	RS276-2021	T-51	GE-60	ICC-51	TR-53	PTC 115	HEP-51	SK 3124	RT-100	ECG 123	WEP 53	ZEN 101
2S711	RS276-2009	T-53	GE-18	ICC-53	TR-25	PTC 125	HEP-53	SK 3124	RT-100	ECG 123	WEP 53	ZEN 102
2S712	RS276-2009	T-53	GE-18	ICC-53	TR-25	PTC 125	HEP-53	SK 3124	RT-100	ECG 123	WEP 53	ZEN 102
2S731	RS276-2023	T-52	GE-17	ICC-52	TR-25	PTC 101	HEP-52	SK 3122	RT-102	ECG 123A	WEP 53	NA
2S732	RS276-2023	T-52	GE-17	ICC-52	TR-25	PTC 101	HEP-52	SK 3122	RT-102	ECG 123A	WEP 53	NA
2S733	RS276-2023	T-52	GE-17	ICC-52	TR-65	PTC 101	HEP-52	SK 3122	RT-102	ECG 123A	WEP 53	NA
2S741	RS276-2021	T-51	GE-11	ICC-51	TR-87	PTC 139	HEP-51	SK 3024	RT-114	ECG 128	WEP 243	ZEN 101
2S742	RS276-2021	T-51	GE-63	ICC-51	TR-87	PTC 117	HEP-51	SK 3024	RT-114	ECG 128	WEP 243	ZEN 101
2S743	NA	NA	GE-18	NA	TR-78	PTC 117	NA	SK 3045	RT-110	ECG 154	WEP 712	NA
2S744	RS276-2021	T-51	GE-11	ICC-51	TR-87	PTC 139	HEP-51	SK 3025	RT-114	ECG 128	WEP 243	ZEN 101
2S745	RS276-2021	T-51	GE-63	ICC-51	TR-87	PTC 117	HEP-51	SK 3024	RT-114	ECG 128	WEP 243	ZEN 101
2S746	NA	NA	GE-18	NA	TR-78	PTC 117	NA	SK 3045	RT-110	ECG 154	WEP 712	NA
2S828(Q)	NA	NA	NA	NA	TR-21	NA	NA	NA	RT-107A	NA	NA	NA
2S838(E)	NA	NA	NA	NA	TR-724	NA	NA	NA	NA	NA	NA	NA
2S930C	NA	NA	NA	NA	TR-51	NA	NA	NA	RT-172	ECG 160	NA	NA
2S930(D)	NA	NA	NA	NA	TR-51	NA	NA	NA	RT-172	NA	NA	NA
2S930(E)	NA	NA	NA	NA	TR-24	NA	NA	NA	RT-114	ECG 108	NA	NA
2S945	NA	NA	NA	NA	TR-21	NA	NA	NA	RT-107A	ECG 123A	NA	NA
2S1014D1	NA	NA	NA	NA	TR-76	NA	NA	NA	RT-197	ECG 152	NA	NA
2S1760	NA	NA	GE-2	NA	NA	NA	NA	NA	RT-123	ECG 102	NA	NA
2S3010	NA	T-715	GE-21	ICC-715	TR-88	NA	HEP-715	SK 3025	RT-115	ECG 129	WEP 242	ZEN 106
2S3020	NA	T-715	GE-21	ICC-715	TR-52	NA	HEP-715	SK 3114	RT-115	ECG 159	WEP 717	ZEN 106
2S3021	NA	T-52	GE-22	ICC-52	TR-52	NA	HEP-52	SK 3114	RT-115	ECG 159	WEP 717	NA
2S3030	NA	T-722	GE-22	ICC-722	TR-52	NA	HEP-722	SK 3114	RT-115	ECG 159	WEP 717	ZEN 110
2S3040	NA	T-717	GE-22	ICC-717	TR-52	NA	HEP-717	SK 3114	RT-115	ECG 159	WEP 717	NA
2S3187	NA	NA	NA	NA		PTC 102	NA	NA	NA	NA	NA	NA
2S3210	RS276-2023	T-52	GE-21	ICC-52	TR-52	NA	HEP-52	SK-3114	RT-115	ECG 159	WEP 717	NA
2S3220	RS276-2023	T-52	GE-21	ICC-52	TE-52	NA	HEP-52	SK 3114	RT-115	ECG 159	WEP 717	NA
2S3221	RS276-2023	T-52	GE-22	ICC-52	TR-20	NA	HEP-52	SK 3114	RT-115	ECG 159	WEP 717	NA
2S3230	RS276-2023	T-52	GE-22	ICC-52	TR-52	NA	HEP-52	SK 3114	RT-115	ECG 159	WEP 717	NA
2S3240	RS276-2023	T-52	GE-22	ICC-52	TR-52	NA	HEP-52	SK 3114	RT-115	ECG 159	WEP 717	NA
2S3324	NA	NA	NA	NA	TR-05	PTC 102	NA	NA	NA	ECG 105	NA	NA
2S3370	NA	NA	GE-52	NA	TR-05	PTC 102	NA	NA	RT-123	ECG 105	NA	NA
2S3734Y	NA	NA	NA	NA	TR-87	NA	NA	NA	RT-187	ECG 128	NA	NA
2S6344	NA	NA	NA	NA	TR-21	NA	NA	NA	RT-107A	ECG 123A	NA	NA
2S6371	NA	NA	NA	NA	TR-21	NA	NA	NA	RT-107A	ECG 123A	NA	NA
2S6387	NA	NA	NA	NA	TR-83	NA	NA	NA	NA	NA	NA	NA
2S6856	NA	NA	NA	NA	NA	NA	NA	SK 3040	RT-110	ECG 154	NA	NA
2SA01	NA	NA	NA	NA	TR-11	NA	NA	NA	NA	NA	NA	NA
2SA12	RS276-2004	T-253	GE-50	ICC-253	TR-12	PTC 109	NA	SK 3005	RT-123	ECG 102A	WEP 250	ZEN 304
2SA12(D)	NA	T-253	NA	NA	TR-12	PTC 109	HEP-253	NA	RT-123	ECG 158	NA	NA
2SA12A	RS276-2004	T-253	GE-1	ICC-253	TR-12	PTC 109	HEP-253	SK 3006	RT-188	ECG 102A	WEP 250	ZEN 304
2SA12B	NA	T-253	GE-50	ICC-253	TR-12	PTC 109	HEP-253	SK 3008	RT-123	ECG 102A	WEP 250	ZEN 304
2SA12C	RS276-2004	T-253	GE-1	ICC-253	TR-85	PTC 109	HEP-253	SK 3006	RT-188	ECG 102A	WEP 250	ZEN 304
2SA12D	NA	T-254	GE-50	ICC-254	TR-85	PTC 109	HEP-254	SK 3006	RT-188	ECG 102A	WEP 250	ZEN 305
2SA12H	RS276-2004	T-250	GE-50	ICC-250	TR-85	PTC 109	HEP-250	NA	RT-123	ECG 102A	WEP 250	ZEN 302
2SA12V	NA	T-253	NA	ICC-253	TR-12	PTC 109	HEP-253	SK 3006	RT-188	ECG 102A	WEP 250	ZEN 304
2SA13	RS276-2004	T-250	GE-50	ICC-250	TR-17	PTC 109	HEP-250	SK 3005	RT-183	ECG 160	WEP 637	ZEN 302
2SA14	RS276-2004	T-250	GE-1	ICC-250	TR-17	PTC 109	HEP-250	SK 3005	RT-183	ECG 160	WEP 637	ZEN 302
2SA15	RS276-2004	T-250	GE-50	ICC-250	TR-85	PTC 107	HEP-250	SK 3005	RT-123	ECG 102A	WEP 250	ZEN 302
2SA15-6	NA	NA	NA	NA	NA	PTC 107	NA	SK 3005	NA	ECG 100	NA	NA
2SA15H	RS276-2004	T-250	GE-50	ICC-250	TR-85	PTC 109	HEP-250	NA	RT-123	ECG 102A	WEP 250	ZEN 302
2SA15R	NA	NA	NA	NA	TR-05	PTC 107	NA	SK 3005	RT-117	ECG 100	NA	NA
2SA15V	RS276-2003	T-635	GE-1	ICC-250	TR-17	PTC 107	HEP-250	SK 3005	RT-118	ECG 100	WEP 254	ZEN 311
2SA15V/ R	NA	T-253	ICC-253	TR-85	PTC 107	HEP-253	SK 3005	RT-117	ECG 100	WEP 254	ZEN 304	
2SA15Y	NA	T-635	GE-2	ICC-635	TR-85	PTC 107	HEP-635	SK 3005	RT-123	ECG 102A	WEP 250	ZEN 302
2SA16	RS276-2004	T-250	GE-50	ICC-250	TR-85	PTC 107	HEP-250	SK 3005	RT-123	ECG 102A	WEP 250	ZEN 302
2SA17	RS276-2021	T-251	GE-1	ICC-251	TR-85	PTC 145	HEP-251	SK 3005	RT-123	ECG 102A	WEP 250	ZEN 303
2SA17H	RS276-2021	T-251	GE-50	ICC-251	TR-85	PTC 109	HEP-251	NA	RT-123	ECG 102A	WEP 250	ZEN 303
2SA18	RS276-2021	T-251	GE-50	ICC-251	TR-85	PTC 109	HEP-251	SK 3005	RT-123	ECG 102A	WEP 250	ZEN 303

NA=NOT AVAILABLE

(turn page)

AUGUST 1975

ARCH DM G-E ICC IR MAL MOT RCA SPR SYL WOR ZEN

2SA18H	RS276-2021	T-251	GE-50	ICC-251	TR-85	PTC 107	HEP-251	NA	RT-123	ECG 102A	WEP 250	ZEN 303
2SA19	RS276-2003	T-639	GE-51	ICC-639	TR-17	PTC 107	HEP-639	SK 3008	RT-119	ECG 126	WEP 635	ZEN 314
2SA20	RS276-2003	T-639	GE-57	ICC-639	TR-17	PTC 107	HEP-639	SK 3008	RT-119	ECG 126	WEP 635	ZEN 314
2SA21	RS276-2003	T-639	GE-51	ICC-639	TR-17	PTC 107	HEP-639	SK 3008	RT-119	ECG 126	WEP 635	ZEN 314
2SA22	NA	NA	GE-51	NA	NA	NA	NA	NA	RT-188	NA	NA	NA
2SA23	NA	NA	GE-51	NA	NA	NA	NA	NA	RT-188	NA	NA	NA
2SA24	NA	NA	GE-50	NA	TR-12	NA	NA	NA	RT-188	NA	NA	NA
2SA25	NA	NA	GE-50	NA	NA	NA	NA	NA	NA	NA	NA	NA
2SA26	RS276-2004	T-250	GE-1	ICC-250	TR-05	PTC 109	HEP-250	SK 3005	RT-118	ECG 100	WEP 254	ZEN 302
2SA27	NA	NA	GE-51	NA	NA	NA	NA	NA	RT-188	NA	NA	NA
2SA28	RS276-2003	T-639	GE-51	ICC-639	TR-17	PTC 109	HEP-639	SK 3005	RT-188	ECG 126	WEP 635	ZEN 314
2SA29	RS276-2003	T-639	GE-51	ICC-639	TR-17	PTC 109	HEP-639	SK 3008	RT-119	ECG 126	WEP 635	ZEN 314
2SA29-3	NA	T-53	NA	ICC-53	NA	NA	HEP-53	NA	NA	NA	NA	NA
2SA30	RS276-2003	T-637	GE-50	ICC-637	TR-17	PTC 107	HEP-637	SK 3005	RT-188	ECG 126	WEP 635	NA
2SA31	RS276-2005	T-254	GE-50	ICC-254	TR-05	PTC 107	HEP-254	SK 3005	RT-118	ECG 100	WEP 254	ZEN 305
2SA32	RS276-2004	T-250	GE-53	ICC-250	TR-85	PTC 109	HEP-250	SK 3005	RT-123	ECG 102A	WEP 250	ZEN 302
2SA33	RS276-2004	T-250	GE-1	ICC-250	TR-85	PTC 109	HEP-250	NA	RT-123	ECG 102A	WEP 250	ZEN 302
2SA35	RS276-2003	T-637	GE-50	ICC-637	TR-85	PTC 109	HEP-637	SK 3005	RT-188	ECG 126	WEP 635	ZEN 305
2SA36	RS276-2003	T-254	GE-50	ICC-254	TR-05	PTC 107	HEP-254	SK 3005	RT-118	ECG 100	WEP 254	ZEN 305
2SA37	RS276-2004	T-250	GE-51	ICC-250	TR-17	PTC 107	HEP-250	SK 3005	RT-188	ECG 126	WEP 635	ZEN 302
2SA38	RS276-2004	T-250	GE-51	ICC-250	TR-17	PTC 107	HEP-250	SK 3005	RT-188	ECG 126	WEP 635	ZEN 302
2SA39	RS276-2004	T-250	GE-51	ICC-250	TR-17	PTC 107	HEP-250	SK 3005	RT-188	ECG 126	WEP 635	ZEN 302
2SA40	RS276-2005	T-254	GE-1	ICC-254	TR-05	PTC 109	HEP-254	SK 3005	RT-118	ECG 100	WEP 254	ZEN 305
2SA41	RS276-2007	T-631	GE-51	ICC-631	TR-17	PTC 109	HEP-631	SK 3005	RT-183	ECG 160	WEP 637	ZEN 307
2SA42	RS276-2007	T-631	GE-51	ICC-631	TR-17	PTC 109	HEP-631	SK 3123	RT-136	ECG 160	WEP 637	ZEN 307
2SA43	RS276-2005	T-638	GE-51	ICC-638	TR-17	PTC 107	HEP-638	SK 3007	RT-188	ECG 126	WEP 635	ZEN 313
2SA44	RS276-2004	T-253	GE-2	ICC-253	TR-05	PTC 102	HEP-253	SK 3005	RT-118	ECG 100	WEP 254	ZEN 304
2SA45	NA	T-635	GE-51	ICC-635	NA	NA	HEP-635	SK 3006	RT-188	ECG 126	WEP 635	ZEN 311
2SA45-1	NA	T-635	GE-51	ICC-635	TR-17	PTC 107	HEP-635	SK 3006	RT-188	ECG 126	WEP 635	ZEN 311
2SA45-2	NA	T-635	GE-51	ICC-635	TR-17	PTC 107	HEP-635	SK 3006	RT-188	ECG 126	WEP 635	ZEN 311
2SA45-3	NA	T-635	GE-51	ICC-635	TR-17	PTC 107	HEP-635	SK 3006	RT-188	ECG 126	WEP 635	ZEN 311
2SA48	NA	NA	GE-51	NA	NA	NA	NA	NA	NA	NA	NA	NA
2SA49	RS276-2003	T-639	GE-51	ICC-639	TR-17	PTC 109	HEP-639	SK 3005	RT-188	ECG 126	WEP 635	ZEN 314
2SA50	RS276-2003	T-632	GE-53	ICC-632	TR-17	PTC 109	HEP-632	SK 3005	RT-123	ECG 102A	WEP 250	ZEN 308
2SA51	RS276-2004	T-250	GE-51	ICC-250	TR-17	PTC 109	HEP-250	SK 3005	RT-183	ECG 160	WEP 637	ZEN 302
2SA52	RS276-2003	T-639	GE-51	ICC-639	TR-17	PTC 109	HEP-639	SK 3003	RT-188	ECG 126	WEP 635	ZEN 314
2SA53	RS276-2003	T-639	GE-51	ICC-639	TR-17	PTC 109	HEP-639	SK 3005	RT-188	ECG 126	WEP 635	ZEN 314
2SA54	RS276-2003	T-3	GE-1	ICC-3	TR-17	PTC 109	HEP-3	SK 3005	RT 183	ECG 160	WEP 637	ZEN 301
2SA55	RS276-2004	T-253	GE-2	ICC-253	TR-05	PTC 102	HEP-253	SK 3005	RT-118	ECG 100	WEP 254	ZEN 304
2SA56	RS276-2003	T-1	GE-1	ICC-1	NA	PTC 109	HEP-G0008	NA	NA	ECG 160	WEP-637	NA
2SA56A	NA	NA	GE-22	NA	NA	NA	HEP-S0019	NA	RT-126	NA	NA	NA
2SA57	NA	T-639	GE-51	ICC-639	TR-17	PTC 107	HEP-G0008	SK 3008	RT-119	ECG 126	WEP-635	ZEN 314
2SA58	RS276-2003	T-639	GE-51	ICC-639	NA	PTC 107	HEP-G0008	SK 3006	RT-188	ECG 126	WEP-635	ZEN 314
2SA58G	NA	T-639	NA	NA	NA	NA	HEP-G0008	NA	RT-183	NA	NA	NA
2SA59	RS276-2003	T-639	GE-51	ICC-639	TR-12	PTC 107	HEP-G0008	SK 3007	RT-183	ECG 126	WEP-635	ZEN 314
2SA60	RS276-2003	T-639	GE-51	ICC-639	TR-05	PTC 107	HEP-G0008	SK 3006	RT-188	ECG 126	WEP-635	ZEN 314
2SA60G	NA	T-639	NA	NA	NA	NA	HEP-G0008	NA	RT-183	NA	NA	NA
2SA61	RS276-2003	T-637	GE-2	ICC-367	TR-17	PTC 102	HEP-G0003	SK 3005	RT-183	ECG 160	WEP-637	NA
2SA64	RS276-2004	T-250	GE-52	ICC-250	IRTR-85	PTC 107	HEP-G0005	SK 3008	RT-121	ECG 102A	WEP-250	ZEN 302
2SA64B	NA	NA	NA	NA	NA	NA	HEP-S0019	NA	RT-126A	NA	NA	NA
2SA65	RS276-2004	T-250	GE-2	ICC-250	IRTR-85	PTC 102	HEP-G0005	SK 3005	RT-121	ECG 102A	WEP-250	ZEN 302
2SA66	RS276-2004	T-250	GE-2	ICC-250	TR-06	PTC 102	HEP-G0005	SK 3006	RT-188	ECG 126	WEP-635	ZEN 302
2SA67	RS276-2004	T-250	GE-2	ICC-250	TR-17	PTC 107	HEP-G0008	SK 3006	RT-188	ECG 126	WEP-635	ZEN 302
2SA69	RS276-2003	T-640	GE-50	ICC-640	TR-17	PTC 107	HEP-G0008	SK 3006	RT-188	ECG 126	WEP-635	ZEN 302
2SA70	RS276-2003	T-640	GE-50	ICC-640	TR-17	PTC 107	HEP-G0008	SK 3006	RT-188	ECG 160	WEP-637	NA
2SA70-08	NA	NA	GE-50	NA	TR-17	PTC 107	NA	SK 3006	RT-188	NA	NA	NA
2SA70F	NA	T-636	GE-50	ICC-633	TR-17	PTC 107	HEP-G0008	SK 3006	RT-188	ECG 160	WEP-637	ZEN 312
2SA70L	RS276-2003	T-637	GE-51	ICC-637	TR-17	NA	HEP-G0003	NA	RT-188	ECG 160	WEP-637	NA
2SA70MA	RS276-2003	T-637	GE-50	ICC-637	TR-17	PTC 107	HEP-G0003	SK 3006	RT-188	ECG 160	WEP-637	NA
2SA70-OB	NA	NA	NA	NA	NA	NA	NA	SK 3006	RT-188	NA	NA	NA
2SA70-8	NA	NA	NA	NA	NA	NA	NA	NA	NA	NA	NA	NA
2SA70Y	NA	NA	GE-50	NA	TR-17	PTC 107	NA	SK 3006	RT-188	NA	NA	NA
2SA71	RS276-2003	T-640	GE-50	ICC-670	TR-17	PTC 107	HEP-G0008	SK 3006	RT-188	ECG 126	WEP-635	NA
2SA71A	NA	T-253	GE-50	ICC-253	TR-17	PTC 107	HEP-G0005	SK 3006	RT-188	ECG 126	WEP-635	ZEN 304
2SA71AB	NA	T-639	GE-50	ICC-639	TR-17	PTC 107	HEP-G0008	SK 3006	RT-188	ECG 126	WEP-635	ZEN 314
2SA71AC	NA	T-640	GE-50	ICC-640	TR-17	PTC 107	HEP-G0008	SK 3006	RT-188	ECG 126	WEP-635	NA
2SA71B	NA	T-635	GE-50	ICC-635	TR-17	PTC 107	HEP-G0001	SK 3006	RT-188	ECG 126	WEP-635	ZEN 311
2SA71BS	NA	T-635	GE-50	ICC-635	TR-17	PTC 107	HEP-G0001	SK 3006	RT-188	ECG 126	WEP-635	ZEN 311
2SA71D	NA	T-635	NA	ICC-635	IRTR-85	NA	HEP-G0001	SK 3006	RT-188	ECG 126	WEP-635	NA
2SA71Y	NA	T-635	GE-50	ICC-635	TR-17	PTC 107	HEP-G0001	SK 3006	RT-188	ECG 126	WEP-635	ZEN 311
2SA72	RS276-2003	T-639	GE-51	NA	TR-17	PTC 107	HEP-G0008	SK 3006	RT-183	ECG 126	WEP-635	ZEN 314
2SA72	BLU	RS276-2003	NA	ICC-640	IRTR-85	NA	HEP-G0008	SK 3006	RT-183	ECG 126	WEP-635	NA
2SA72	BLU-BLU	RS276-2003	NA	ICC-640	IRTR-85	NA	HEP-G0008	SK 3006	RT-183	ECG 126	WEP-635	NA

NA=NOT AVAILABLE

(continued next month)

R-E's Service Clinic

Scan-derived DC power supplies

They're easy to service if you know how they work

by JACK DARR
SERVICE EDITOR

SEVERAL OF THE LATER MODEL solid-state color-TV chassis have come up with an interesting feature. This is called by quite a few different names (one even calls it an "electronic power supply!"). Probably the most descriptive term is Admiral's "scan-derived power supply." It's really simple; all it means is that some or all of the operating DC voltage supplies do not come

set.

In many sets, especially those with remote control and/or Instant-On, the set is never completely turned off. When the switch is turned off, the power supply to the horizontal oscillator and output is not cut off, but reduced. So, a lower DC voltage is present to keep the remote control units working and the picture tube heater

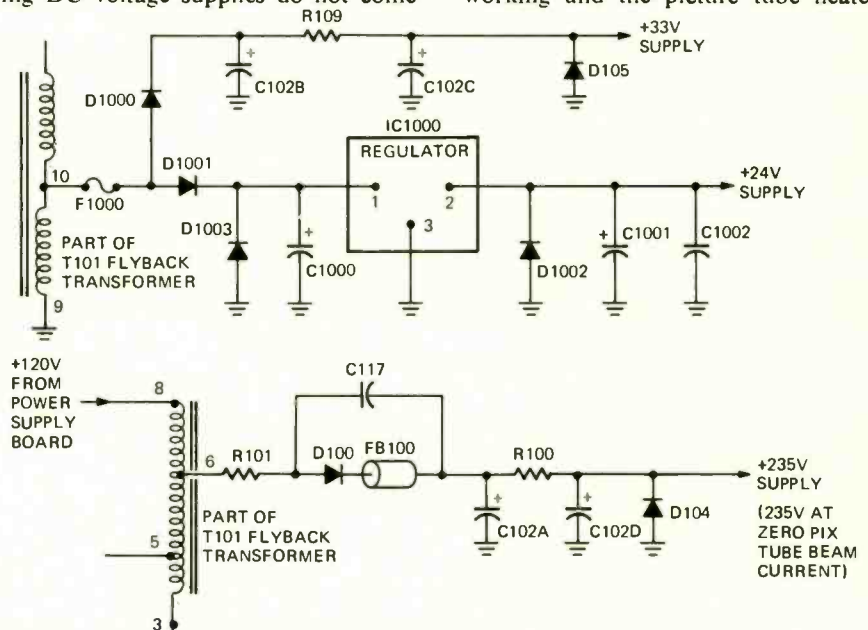


FIG. 1—DC VOLTAGES are derived from flyback.

directly from the AC line through a rectifier, but originate in the horizontal output transformer. One little Sony portable supplies the picture tube heater from a winding on the horizontal driver transformer!

There is a good reason for this. Since the operating frequency is so much higher, the transformer can be made much smaller. Filtering is also simplified. You can use a much smaller capacitor at 15.75 kHz than you need at 60 Hz. Since the voltages needed for solid-state circuits are lower, it's not nearly as hard as it sounds.

The actual power used does come from the AC line, of course. This can be as simple as a half-wave rectifier often fed directly from the AC line, sometimes from a power transformer. Here, the power transformer could be a simple 1:1 isolation transformer. This DC supply feeds the horizontal oscillator and output stage. Extra windings on the flyback transformer provide the operating voltages for the rest of the

warm. The high-voltage and sound circuits are "turned down" to the point where they stop working.

Admiral's M10 chassis is a good example of this type of circuit. Figure 1 shows the three scan-derived DC power supplies. The +120 volts comes from a regulated DC power supply, fed by the +145 volts DC from the AC line circuit. This +120 volts drives the horizontal oscillator and output stages. At turn-on, this is the only DC voltage present. As soon as the oscillator starts driving the output stage, everything else starts too. In a solid-state circuit, this is almost instantaneous.

The +235 volt supply provides the higher voltages needed for the picture tube grids and the three video driver stages. The picture tube screen grids are fed from a tap on the focus voltage, which in turn comes from a tap on the voltage tripler used in the high-voltage supply.


The +33 volt supply is fed by a posi-
(continued on page 68)

This column is for your service problems—TV, radio, audio or general and industrial electronics. We answer all questions individually by mail, free of charge and the more interesting ones will be printed here.

If you're really stuck, write us. We'll do our best to help you. Don't forget to enclose a stamped, self-addressed envelope. If return postage is not included, we cannot process your question. Write: Service Editor, Radio-Electronics, 200 Park Ave. South, N.Y. 10003.

Have you ever asked yourself, "Can I make it in Electronics?"

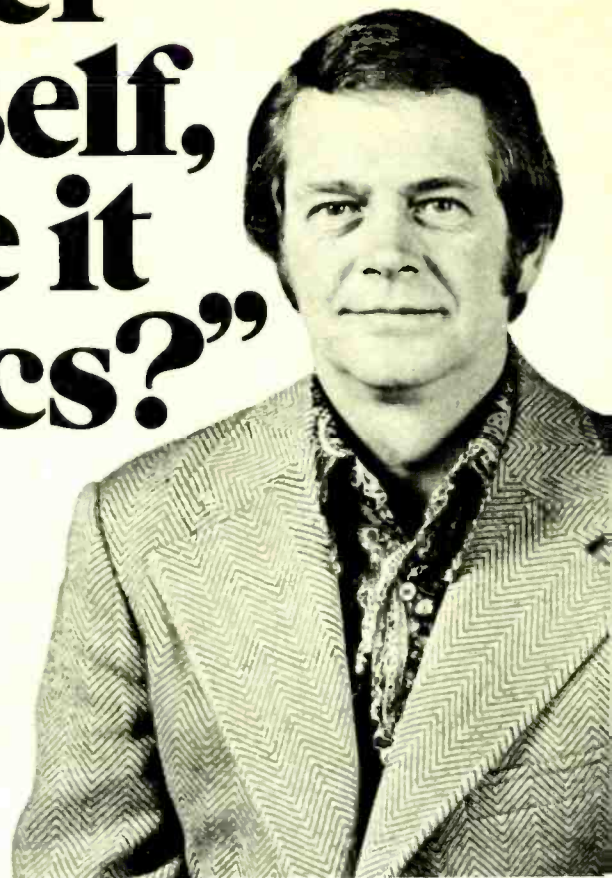CIE may be the answer if you have a technical aptitude and a serious desire to get ahead.



Right now, you're reading a technical magazine with articles that require a certain amount of electronics know-how. And that says a couple of things about you.

First, you're involved in Electronics . . . on the job, or as a hobby.

Second, you obviously realize the importance of staying up-to-date on the latest technical applications and developments. Reading a technical magazine *helps*, but it takes more than that to get you where *you* want to be . . . if you're serious about Electronics.

How can you afford

. . . *not* to continue with your electronics training?

You know the answer to that as well as we do.

To achieve continuing success, you have to keep building more knowledge into the Electronics background and experience you already have. You have to sharpen the tech skills you've already got and add new ones.

And one of the most logical ways for you to get what you need is to seriously consider an in-depth electronics training program that could help you achieve your ambitions in Electronics.

How can you afford

. . . the time and trouble of going back to school?

An excellent and *convenient* way for you to develop and expand your electronics knowledge is to "let the *school* come to *you*."

CIE's independent education plan does just that. Because we can effectively train you with an "education by mail" electronics training program that makes sense. And it makes sense for these reasons:

You can master *career* Electronics without missing one day of work. Without sacrificing one paycheck! Because you study in your free time . . . setting the study pace that best fits your schedule. *You* decide when and where *you* want to study. So you can go right on enjoying your leisure time because there are no *rigid* classroom schedules to be met. *You're* in control!

How can you afford

. . . the expense of the additional education you need?

A lot depends on which CIE course best fits your educational goals and background. We have a variety of electronics courses at beginner, intermediate, and advanced college-level. And there's a convenient payment plan available for every course. But, one way to evaluate your investment in CIE is this . . . you can *graduate* from CIE for about the cost of one year's tuition at some colleges or universities.

How can you afford

. . . to learn Career Electronics from anyone other than an electronics *specialist*?

If you are *serious* about your career in Electronics, you owe it to yourself to investigate *the* home study school that devotes its entire curriculum and instructional efforts to Electronics. That's CIE — Cleveland Institute of Electronics.

We have *specialized exclusively* in Electronics education-by-mail for more than 40 years. Just Electronics. Nothing else. And, the courses we offer today are the result of these years of teaching experience and proven methods of training . . . all based on the expert guidance of our



specialized Electronics Instruction Staff. Our lessons reflect this specialized experience. No frills. No unnecessary fancy stuff. Instruction is thorough . . . designed to meet the demands of electronics employers.

Each CIE course is built on the principle that the best way for you to *learn* and *retain* what you've learned is to *explain*; then to *check* your understanding; then to *reinforce* your comprehension with practical applications. In some courses, you will perform experiments and tests with your CIE Experimental Electronics Laboratory using authentic electronic components and gear. And, if you select a course that includes Color TV technology, you will not only build and keep a big screen Color TV which features digital circuitry . . . you'll also learn how to troubleshoot your TV.

The course you select will be a complete educational program, designed by *experts* to give you the best in Electronics independent home-study education. It will not be a "snap" course. No easy exams. It will make you work . . . and think. So that when you've earned your CIE Diploma, you'll *really* know your stuff.

In education just like in the "real world" of Electronics, your success depends on you and the effort you make. That's a real plus in CIE independent home-study . . . you build a strong foundation of self-discipline. And *that* pays off!

How can you afford . . . to stop now?

There is a lot more to CIE than this advertisement can tell you. And because you're looking for the *best*, we think it's well worth your while to find out what CIE is

all about. Detailed Courses of Study outlines. In-depth training programs in Electronics Technology, Broadcasting, Industrial, Color TV, Engineering, and 1st Class FCC License preparation. Special CIE Student Services.

All this information is available to you, **FREE**, when you mail the card or coupon to us. For your convenience, we'll try to have a school representative contact you to review the benefits of CIE training and assist in course selection. And as soon as we hear from you, we'll mail a complete package of information, including our school catalog, G. I. Bill details, special FCC License information. All the facts you need to start your Electronics career program with CIE.

Send TODAY for CIE'S FREE information.

CIE Cleveland Institute of Electronics, Inc.	
1776 East 17th Street, Cleveland, Ohio 44114	
Accredited Member National Home Study Council	
Yes, I want your FREE school catalog and career information package today.	
I am especially interested in: RE-57	
<input type="checkbox"/> Electronics Technology	<input type="checkbox"/> Industrial Electronics
<input type="checkbox"/> FCC License Preparation	<input type="checkbox"/> Electronics Engineering
<input type="checkbox"/> Color TV Maintenance	<input type="checkbox"/> Other _____
<input type="checkbox"/> Mobile Communications	_____
Print Name _____	
Address _____ Apt. _____	
City _____	
State _____ Zip _____ Age _____	
Check box for G.I. Bill information. <input type="checkbox"/> Veteran <input type="checkbox"/> On Active Duty	

AUGUST 1975

is all right, but you have no +24 volt supply, the driving pulse must be there. You would have something like a bad rectifier diode, faulty IC regulator, etc. If the 1.5A fuse F1000 is open, this will kill both of the low-voltage supplies. This would point to something like a short in either one, or a short in one of the loads fed from them. These can be checked out in a short time by disconnecting things.

For a complete description of these circuits, see Admiral's Service News Letter, January and March 1975. For the complete schematic, Admiral Service Data S1349. Thanks, Admiral! R-E

reader questions

INTERCHANGEABLE TUBES?

This Dumont 41P01 portable looks just like the picture in Sams, on the outside. When I took the back off, I found the enclosed tube layout pasted inside. Sams shows a 5HA7/5HC7 tube, and this one has a 6LX8. A factory man says that it should be one of these two; he has no record of a 6LX8. Sams does show a 6LX8 as an alternate. Who's

right here?—H.P., Brooklyn, NY.

Sams is. If your set has a 6LX8, and it is obviously a "factory job", this was a modification at the factory. Incidentally, in this set, you must use the type of tube you found in there! The 5HA7 and 5HC7 are not interchangeable, I'm fairly sure! The tube manual says these are "dual dissimilar triodes" and the triodes are reversed between the 12FQ base of the 5HA7 and the 12FR base of the 5HC7. The 6LX8 is a triode-pentode with a 9DC base (9-pin).

NO HIGH VOLTAGE, HOT 6JE6

There is no high voltage in this Emerson 822A and the 6JE6 gets red-hot when the high-voltage lead is connected to the picture tube. Disconnected, this lead checks 25-30 kV. Everything around the high-voltage circuit seems OK. Help would be appreciated.—S.M., Wilmington, DE.

Help is on the way! Take the high-voltage lead off the picture tube and tuck it away somewhere. Now measure all of the DC voltages on the picture tube base, especially the cathode and control grid voltages. From the reaction, your picture tube is biased so much positive on the grids that it's

drawing far too much beam current. This can be due to the control grid voltages being too much positive, or to the cathodes being too far negative! You might have an open video peaker, L17, in the cathode circuit. This has happened.

(Feedback from reader; this was it! Replaced by Miller 7600, and it worked. Even a blind pig gets an acorn once in a while!)


SKILL IS ALL RIGHT IN ITS PLACE

I need a power transformer for a Tonecrest radio-stereo. No numbers at all on the chassis, and it's made in Canada. I've looked everywhere but can't find any information. The owner is bugging me for this; help!—F.Y., Los Angeles, CA.

Check the Sams Photofact Folder 673-6 for a Clairtone C303. The power transformer has exactly the same part number and the tube lineup is the same as the one you sent! Unbelievably, this was in the *second* folder I checked. I crossed the name Tonecrest and got Clairtone and some more, and started looking. Skill is all right in its place, but a little luck beats it any day! Try a Triad R127A or Thordarson 26R112. Should match perfectly.

(continued on page 77)

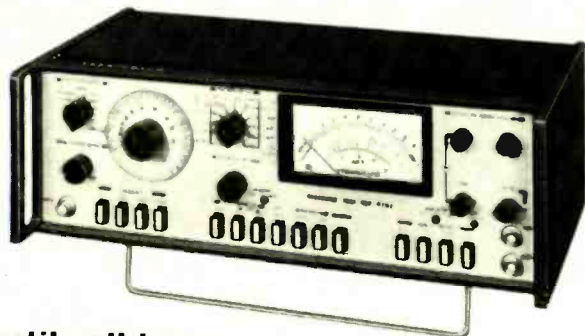Everything you need for complete tape recorder testing. Ferrograph RTS-2 with Auxiliary Unit




Versatile all-in-one precision test system

It's a Sine Wave generator . . .
Millivoltmeter . . . Wow & Flutter bridge
. . . Harmonic Distortion analyzer that you can learn to use in minutes. Requiring only two leads, setup time is minimal. Pushbutton controls provide rapid, precise operation. Compact and lightweight, it's ideal for recording and broadcast studios, testing labs and service shops.

Vastly expanded operation

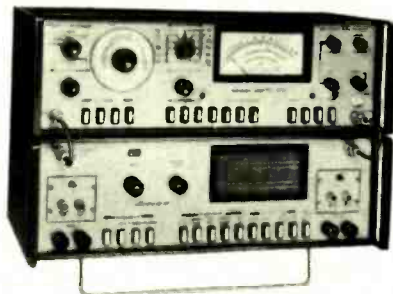By combining the RTS-2 with the ATU Auxiliary Unit, you're ready for the most sophisticated audio testing. • Monitors pre-recorded test alignment tape with



RTS-2 Test Set — \$1300
ATU Auxiliary Unit — \$550
Combination offer (both units) — \$1800
Carrying cases optional


built-in speaker unit • Balanced and unbalanced input/output. Switches between left/right input/output channels. Provides matching impedances for 8Ω, 200Ω, 600Ω impedances, or unloaded. • Compares input/output signals • NAB weighted noise filter network for S/N measurements • Oscillator output may be set in 10dB increments over 40dB range by pushbuttons • Designed for use with virtually any test equipment.

New, Convenient Payment Plan!

Try this unique, complete test system Free for 30 days. Write for details.

ELPA MARKETING INDUSTRIES, INC., New Hyde Park, N.Y. 11040

Circle 22 on reader service card

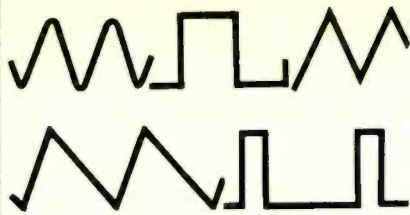

0.1 Hz. to 100 KHz.



For only \$39.95

Our new FG-2 Function Generator kit gives you all five of the most useful waveforms for design and testing at one fourth the cost of previous similar instruments. Thanks to improved IC's the FG-2 now features amplitude stability of ± 1 db over any range, Sine wave distortion of less than 1% from 20 Hz. to 20,000 Hz. and an output of 4.0 Volts peak-to-peak with adjustable offset. The offset selector lets you put the positive peak, negative peak, or the center of the waveform on DC ground. The DC coupled circuit keeps the waveforms in exactly the same position no matter what the level control setting.

Gray impact plastic case 5" x 6" x 2".
115 Volts 60 cycle power supply included.


FG-2 Function Generator Kit
shipping weight 3.0 lbs.....\$39.95 PPd

GET OUR
NEW 1975
CATALOG

listing this and other unique kits

"FREE"

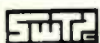by simply circling our number
on the reader service card.



SOUTHWEST TECHNICAL
PRODUCTS CORPORATION

DEPT. PE

219 W. Rhapsody
San Antonio, Texas 78216

Circle 23 on reader service card

MATV Splitters


Splitters are relatively simple devices, but they are a potent weapon in the MATV system designers arsenal.

by JAMES E. KLUGE*

SPLITTERS, LIKE THEIR NAME IMPLIES, divide a signal voltage into two or more identical parts. Each part contains all the information that was contained in the original signal before splitting. All that is lost in the splitting process is power level.

Branching feeder lines

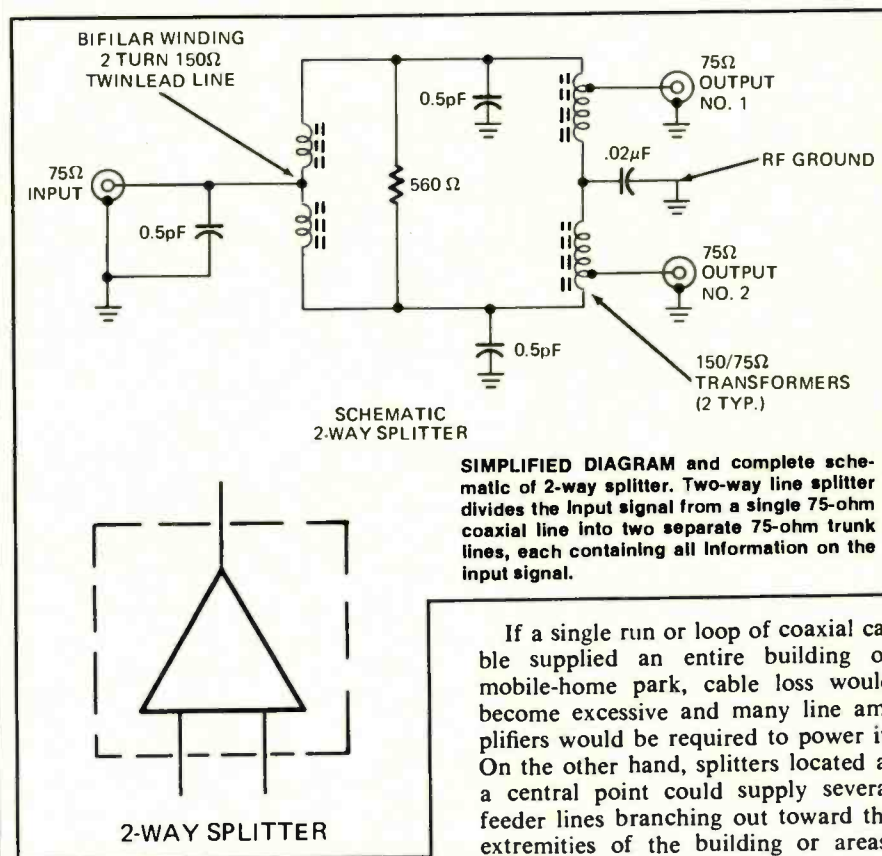Splitters provide a way to branch an MATV system into several routes or feeder lines. Each feeder then services a portion of a building, such as a wing or a floor or a row of mobile homes if in a large mobile-home park.



SIMPLIFIED DIAGRAM and complete schematic of 2-way splitter. Two-way line splitter divides the input signal from a single 75-ohm coaxial line into two separate 75-ohm trunk lines, each containing all information on the input signal.

If a single run or loop of coaxial cable supplied an entire building or mobile-home park, cable loss would become excessive and many line amplifiers would be required to power it. On the other hand, splitters located at a central point could supply several feeder lines branching out toward the extremities of the building or areas. Cable loss, then, would be limited only to the longest feeder line.

Insertion loss

Since a whole equals the sum of its parts, a signal split into two parts has half the power in one part, the other half in the other part. Thus, a signal reduced from full power to half power experiences a 3-dB loss. Likewise, the dual outputs of a 2-way splitter should be 3-dB less than the input signal. Actually, the loss measures 3.5 to 4.0 dB depending on frequency. In addition, to the 3-dB splitter loss, high-frequency losses in the splitter components account for another 0.5 to 1.0 dB.

Isolation

Because line splitters employ transformer action, high isolation exists between outputs. The high isolation helps prevent interference, spurious signals and reflections that appear on one output line from getting onto the other output line. Typical isolation value for a good splitter is 18 to 20 dB between outputs.

2-, 4-, and 8-way splitters

Basically, the splitter is a 2-output device. Four-way splitters consist of a

*Technical Editor
Winegard Company

now available for the telephone experimenter

COMPLETE CONSTRUCTION PLANS

TELEPHONE PLANS: \$3.00 each.
 Answering Device, Automatic Dialer, "Black Box", Call Diverter, Call Limiter, Conference Bridge, Central Dial Exchange, Music Ringing Generator, Recorder-Actuator, Remote Control, Schematics, Speakerphone, Teletalk Burglar Alarm, Voice Scrambler, Dial/Tone Converter, Tone/Dial Converter.
 MISC. PLANS: \$6.00 each.
 Biofeedback Conditioner, Multifrequency Encoder Network, Horticulture Simulator, Undershedron Speaker Enclosure, Photographic Pinhole Camera.

ALL OF THE CONSTRUCTION PLANS ABOVE: \$24.95 AIRMAILED.

LEARN THE SECRETS OF YOUR TELEPHONE



Have you ever wondered what lies behind that telephone dial? Now you can learn the tricks of the telephone trade. Get the inside story of telephone systems—their quirks and flaws, and remain up to date on vital occurrences within the telephone industry. TELEPHONE ELECTRONICS LINE is a publication designed for the telephone enthusiast, phone phreak and experimenter, containing interesting articles which offer a wealth of hard to find information. Technical theory is also discussed, among the following items:
Current News Items • Code Numbers Illustrations • Games • Facts • Plans Projects • History • Comics • Stories Facts previously Tel. Co. confidential is now published in TEL!
 One year subscription rate: United States \$6.00, Canadian & foreign \$8.00.

ALL OF THE CONSTRUCTION PLANS ABOVE PLUS A ONE YEAR SUBSCRIPTION TO TELEPHONE ELECTRONICS LINE: \$36.95 AIRMAILED.


THE LEGAL ASPECTS OF INTERCONNECTION

\$19.95 AIRMAILED.
 The complete reference book to your LEGAL RIGHTS as a telephone subscriber. Study toll evasion, tariffs, wiretapping, customer provided equipment, and many more!

ALL OF THE CONSTRUCTION PLANS ABOVE AND A ONE YEAR SUBSCRIPTION TO TEL PLUS "THE LEGAL ASPECTS OF INTERCONNECTION": \$49.95 AIRMAILED.

TELEPHONICS COMPANY OF AMERICA
 22035 BURBANK BLVD., WOODLAND HILLS CA 91384 USA

Circle 24 on reader service card

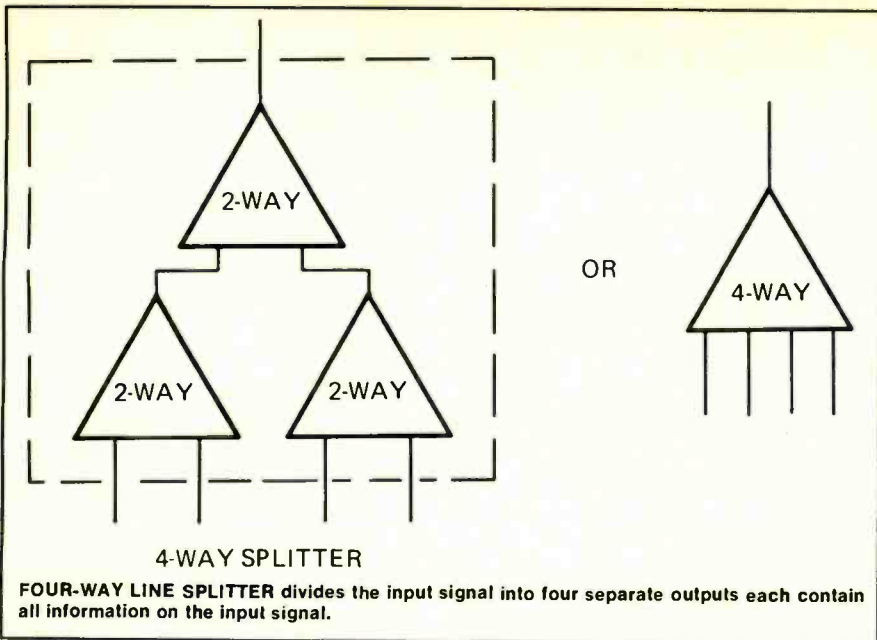


BOOSTER COUPLER CONTAINS broadband amplifier feeding a 4-way line splitter. Power cord goes to 118V, 60 Hz source providing power to amplifier.

pair of 2-way splitters fed from each of the two outputs of another 2-way splitter. Such an arrangement gives us four outputs from one input. The insertion loss doubles but the isolation

CASH IN ON THIS NEW MINI-SCOPE AT \$495.00

IT'S THE WORLD'S BEST SCOPE VALUE!

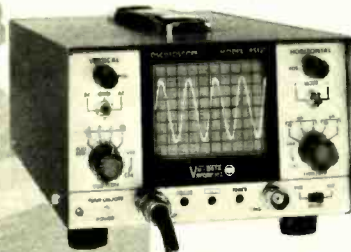- DC - 5 MHz bandwidth
- Only 3" high X 5" wide
- Weighs less than 5 lbs
- Triggered sweep
- All solid state design
- Lab accuracy & quality
- 8 X 10 div display area
- Fits in a tool kit or brief case
- Compact, rugged construction
- Up to 100 nsec/div sweep rate
- 1 year warranty
- 50 mV/div sensitivity




From a Leader in Mini-Portable Oscilloscopes



INTERESTED? Call Hal Wardein at (714) 279-6572, or write to us at 7170 Convoy Court, San Diego, CA 92111.

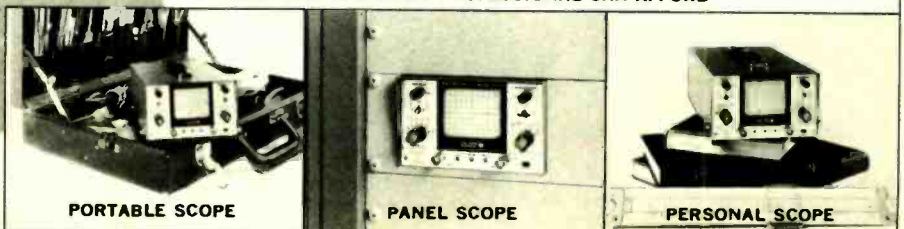PS121A—A SCOPE EVERY PROFESSIONAL CAN AFFORD



PORTABLE SCOPE

PANEL SCOPE

PERSONAL SCOPE

Distributors Wanted

Circle 25 on reader service card

FREE burglar — fire alarm catalog



over 500 systems, detectors, controls, sounders, tools, locks, supplies

TO PROTECT HOMES, BUSINESSES, INDUSTRY

Huge selection of hard-to-find security equipment from stock. 96 fact-filled pages loaded with 100's of highest quality professional alarm products, technical notes, diagrams.

ONE-STOP SUPERMARKET SELECTION INCLUDES:

ultrasonics, radar, infrared, undercarpet mats, magnetic contacts, smoke & heat detectors; Controls; Alarms: bells, sirens, phone dialers, lights, guard panels. Large selection of tools, relays, wire, holdup alarms, books. Fills need for industry, alarm cos., businesses, homes, institutions. Order your copy today.



mountain west alarm
4215 n. 16th st.
phoenix, az. 85016
(602) 263-8831

Circle 26 on reader service card

FREE catalog over 2000




unique tools, handy kits, precision instruments, technical supplies.

Our 23rd year of service to the World's finest craftsmen and technicians.

A carefully selected and tested assortment of unique, hard-to-find tools, clever gadgets, precision instruments, bargain kits. One-stop shopping for the technician, craftsman, hobbyist, lab specialist, production supervisor. Many tools and measuring instruments available nowhere else. One of the most unusual and complete tool catalogs anywhere. Get your copy of the NC FLASHER today.

National Camera 2000 West Union Ave., Dept. GBA
Englewood, Colorado, 80110
Phone (303) 789-1893

Circle 27 on reader service card

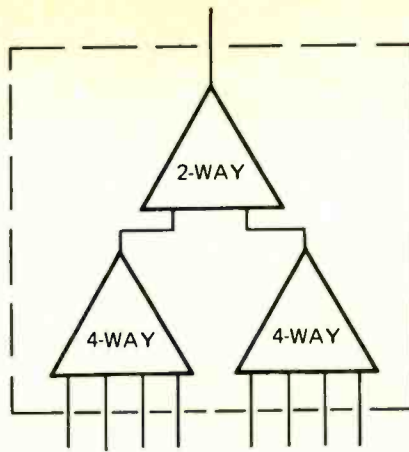


8-WAY SPLITTER


EIGHT-WAY LINE SPLITTER divides the input signal into eight individual signals each containing all information on the input signal.

remains the same. Likewise, an 8-way splitter has two 4-way splitters fed from each of two outputs of a 2-way splitter.

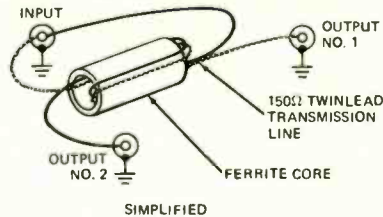Splitters can also be inverted to combine two signals into one. Applications include combining two antenna down-



SIMPLIFIED

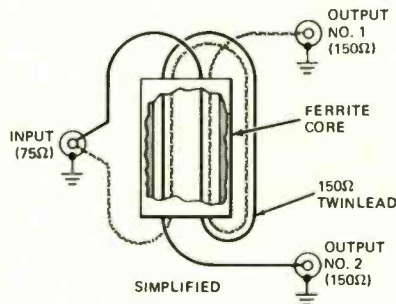

SIMPLIFIED


SIMPLIFIED SCHEMATICS of two different inductive two-way splitters are shown in the diagram above.

leads into one or the outputs of two amplifiers into one line.

Splitters are commonly available in 2-way and 4-way versions with 8-way types being less common. However, most any combination can be had by combining 2-way and 4-way splitters in cascade.


Booster couplers

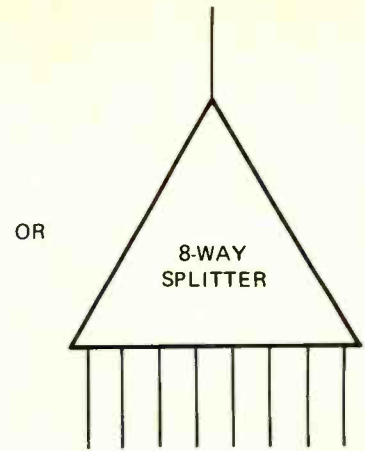If splitter loss (insertion loss) is a problem, you may want to consider booster couplers. A booster coupler is simply a broadband amplifier followed by a splitter, usually a 4-way. Most booster couplers have a high input capability of the order of +34 dBmV for 7 VHF channels and 5 UHF chan-



OR


8-WAY SPLITTER

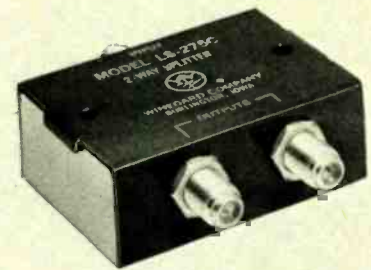

WINEGARD MODEL LS-275C two-way splitter.

nels. The gain, usually 6 dB between the input and each output, overcomes the cable and splitter losses to maintain high line levels.

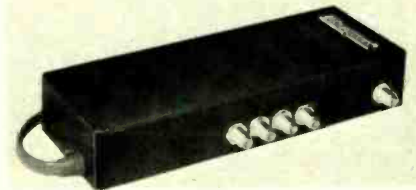Most splitters and booster couplers are 82-channel VHF/UHF types.



WINEGARD MODEL LS-475C amplified 4-way splitter.

There are VHF-only types also available. Booster couplers require 117V, 60 Hz AC power, restricting their location somewhat while line splitters, being passive can be located anywhere. **R-E**




HI-FI LAB TESTS

(continued from page 41)


The high-pass output signal from IC3-a is also applied through the crossover-filter switch to the selected RC filter components. Operational amplifiers IC4-a, IC4-b and IC5-a form a three-pole, low-pass 18 dB/octave Butterworth filter. This filter produces the non-inverted low-pass output, while operational amplifier IC5-b creates the low pass inverted output.

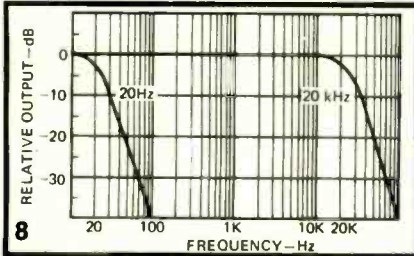Measurements of primary interest in a product of this type are accuracy of filter response characteristics, distortion, and phase response. Figure 8 is a plot of response of the high pass filter section for




two extreme settings of corner frequencies, namely 20 Hz and 20 kHz. Figure 9 shows the response characteristics of the low-pass filter section when it is set to these same frequencies. Superimposing the plots will show that the -3dB point in both cases corresponds exactly to the 20 Hz or 20 kHz points desired.

IM distortion was measured for each of

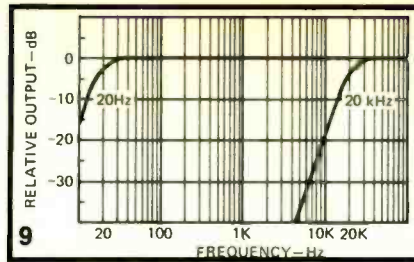

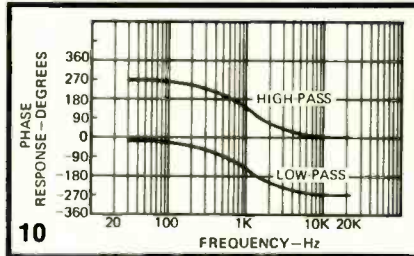the two channels. In both cases we measured less than 0.01% at 9 volts output and this reading (the limit of our test equipment) remained constant down to outputs of as low as 30 millivolts or so, increasing to about 0.02% for lower outputs. Signal to noise ratio for unity gain in each channel measured 107 dB, prob-



ably a good deal better than the S/N ratio of any power amplifier.

Phase response of the low- and high-pass filters, when set for a corner frequency of 1 kHz, is plotted in Fig. 10 and is typical of the phase characteristic that one would expect from a 3-pole Butterworth filter configuration. **R-E**

the audio amateur ?

The brain boggles at what old Johann could have done with his own console, preamp, 8-in-2 out mixer, octave equalizer, electrostatic speakers, or 24 inch woofer.

Come boggle with us.

the Audio Amateur


Box 30R
Swarthmore, Pa.
19081

Craig Stark of STEREO REVIEW says:
"Top quality, only U.S. publication devoted to the serious audiophile constructor."

Name
Street
City State
Zip

Circle 28 on reader service card

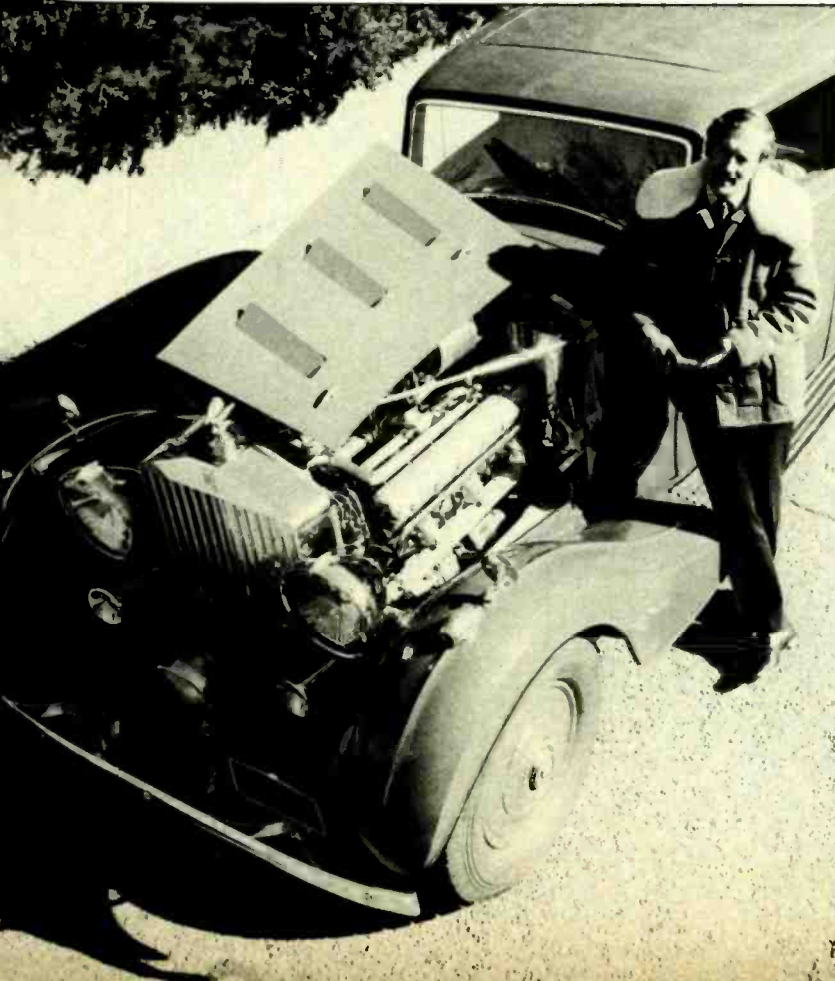You don't have to buy a new car to get an electronic ignition.



Let's face it. After 37 years, even a Phantom III can use a lift. That's why I put a Delta Mark Ten B Capacitive Discharge Ignition on my Phantom . . . to give her a spark I'd pit against any '75 model car. I went to Delta because they aren't Johnny-come-latelys. Delta's been making electronic ignition systems for over a decade.

Whatever kind of car you drive, you can give it the same great Delta performance I gave mine.

- Mark Ten B Capacitive Discharge Ignition Systems are manufactured by Delta Products, Inc., a company with a conscience, and with a proven record of reliability both in product and in customer relations.

- The Mark Ten B really does save money by eliminating the need for 2 out of 3 tune-ups. Figure it out for yourself. The first tune-up or two saved pays for the unit, the rest is money in your pocket. No bunk!

- Because the Mark Ten B keeps your car in better tune, you actually can save on expensive gasoline.

- With a Mark Ten B, spark plugs stay clean and last longer . . . fouling is virtually eliminated.



I want to know more about Mark Ten B CDI's. Send me complete no-nonsense information on how they can improve the performance of my car.

Name
Address
City State Zip



DELTA PRODUCTS, INC.

P.O. Box 1147, Dept. RE, Grand Junction, Colo. 81501
303-242-9000

Mark Ten B, assembled \$64.95 ppd	Standard Mark Ten, assembled \$49.95 ppd
Mark Ten B, klt \$49.95 ppd	Deltakit® \$34.95 ppd

Circle 29 on reader service card

COLOR TV CAMERA

(continued from page 44)

pear on the monitor screen. Adjustment of the focus control R3, the optical lens focus and the target control R2, should bring the scene into sharp focus with sufficient contrast. Due to the series arrangement of R3 and R2, some interaction will be encountered. The focus control should always be the last one adjusted. In normal operation, only the focus controls will have to be re-adjusted.

Initial adjustments of the deflection assembly

If the camera images appear off-center and cannot be brought into registration with the PM alignment magnet adjustments (see Fig. 4), the yoke windings must be demagnetized. Momentarily, connect the yoke windings across a variable DC voltage power supply set to about 12 volts. Reverse the leads and lower the power supply setting about 1 volt. Keep reversing the windings and momentarily magnetizing the yoke at decreasing 1 volt increments. At below the 1 volt point, the residual magnetism that remains should be within the corrective range of the yoke PM alignment magnets.

The objective of this process is to get the magnetism levels at a low enough point so that all registration and centering adjustments for both the yokes can be made by simply rotating the alignment rings. With both camera heads in proper focus optically and electrically, it will be necessary to loosen the yoke hold-down screws, Fig. 4, to allow rotation of the yoke within the focus coil, to correct for vertical axis errors. It should also be remembered that exact positioning of the lens mount will alter the axis of the lens, changing the apparent vertical or horizontal centering in relation to the other channel.

The best construction approach will probably be to simply build each camera head as a black and white unit, thoroughly testing it without using the prism or color filters. When results are satisfactory, initial color registration can be attempted. Insert the color filters behind the lens mount. The edges can simply be taped in place. Be sure to allow the camera to warm up sufficiently before performing registration adjustments. Place the test pattern in front of the prism at the minimum distance at which you want the camera to focus. Adjust both lenses for nearest focus. Slide the cyan vidicon tube back and forth until the sharpest focus is

attained. Re-adjust the electrical focus for sharpest image. Then using the adjusted cyan image as a reference, slide the red vidicon back and forth for best focus. Tighten the vidicon tube clamp (see Fig. 4). Adjust red electrical focus for sharpest image. Adjust the red alignment magnets to bring both images in register. It will be necessary to rotate yoke, adjust vertical scan amplitude and perhaps select values for resistor R22 for best registration. It will be necessary to repeat adjustments several times initially. The above adjustments can be made while viewing the picture in either cyan or red. When it is necessary to view a single channel, simply close the iris on the undesired channel.

Final color adjustments

As mentioned last month, the easiest way to adjust color is by adjusting the lens iris controls on a white test pattern with color stripes. Both images together should produce a good white from the test pattern. When the proper levels are set, the other colors should appear in the correct order. The only discrepancy will be with yellow, which may appear as a yellowish-beige. To insure good color fidelity, the red, blue and green controls on the color monitor must be adjusted to produce a per-

KICK OUT THOSE "TOUGH DOG" TIME CONSUMING AM-FM STEREOS BEFORE THEY EAT UP ALL YOUR PROFITS.



RADIO-ELECTRONICS


NOW
Backed By Sencore's
100% Made Right
Life Time Guarantee

SG165
ONLY \$595

WITH THE ONLY COMPLETE AM-FM STEREO ANALYZER ON THE MARKET TODAY... WITH ALL SIGNALS AT BETTER THAN FCC SPECS

ALL 12 SIGNALS THAT YOU NEED TO WALK THE TROUBLE OUT OF ANY AM, AM-FM, AUTO RADIO, OR THE BIGGEST HI FI IN THE BUSINESS.

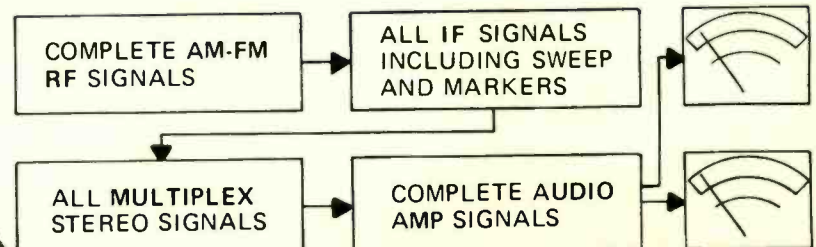TAKES THE FEAR OUT OF STEREO SERVICING BY ISOLATING PROBLEMS IN MINUTES WITH:



MONITORED BY DUMMY LOADS AND 2 D'ARSONVAL METERS FOR POWER OUTPUT AND TRUE SEPARATION TESTS.

SEE YOUR SENCORE FLPD DISTRIBUTOR FOR A 10 DAY FREE TRIAL.

SENCORE 3200 SENCORE DRIVE,
SIOUX FALLS, SOUTH DAKOTA 57107

Circle 30 on reader service card

fect gray raster with the camera on and operating, but with both iris controls closed. These adjustments will of course, be critical due to the fact that the tint control has no effect with this particular set up. Due to the high amount of light loss through the prism (each tube receives only 30% of incoming light), a very high amount of illumination will be required for good color fidelity. I use No. 2 photo-flood blubs. If the scene has a slight pinkish cast, or the yellow appears too pink, it is possible the light bulb is too close to the subject. The camera sensitivity could be greatly increased with a higher efficiency prism or perhaps a mirror optic system which would overcome much of the light loss encountered with the present prism.

It is anticipated that some camera builders may be able to locate high efficiency prisms or low light loss semi-silvered mirrors. It is possible by using a more complex mirror arrangement to put both camera heads in line, thereby making a somewhat smaller and more compact camera. Inasmuch that this is the first known home experimenter or amateur type of live color camera, it is recognized that many modifications, changes and improvements could be incorporated by individual camera builders. For example, by using the camera in conjunction with a commercial N.T.S.C. color encoder, some inherent color deficiencies may be correctable.

Next month we will cover construction of the color monitor sync circuits, red and cyan amplifiers, as well as modification of the two TV sets for use with the camera. **R-E**

Ultrasonic measurement system will aid medical researchers

A new ultrasonic measuring system developed recently by RCA will provide medical researchers with previously unavailable precise measurements of ultrasonic diagnostic devices. In so doing, it may increase and speed up the use of ultra-high-frequency sound in detecting malignancies in human tissue.

Ultrasonic techniques have been preferred for many types of research because they enable body tissue features to be observed that can't be seen by X-ray or optical techniques. But up to now, researchers had no way of knowing precisely the intensity of the waves they were using. This created difficulties in determining exactly what effect increasing or decreasing the intensity or frequency of the sonic waves had in detecting malignancies or tissue malformations.

To measure the output of an ultrasonic transmitter with the new technique, it is placed in a water tank containing a gold-plated pellicle 15-cm in diameter and a few millionths of a meter thick. The pellicle, or membrane, is so thin as to be transparent to sound and follows exactly the microscopic motions of the

water that make up the sound waves passing through it, vibrating in proportion to the intensity of the sound waves reaching it.

Its motions are sensed by scanning a laser beam across the pellicle horizontally and vertically. The reflected beam is minutely altered (phase-modulated) by the pellicle's vibrations. An interferometer compares the modulated beam with an unmodulated reference laser beam and produces electric signals that can be measured by conventional electric meters.

When the system is used to measure ultrasonic waves passing through tissue, the waves are transmitted through or reflected from the specimen and imaged, or

focused, onto the pellicle by plastic acoustic lenses. The pellicle is so tightly coupled to the water that its vibrations at any point are determined by the amount of sound that reaches that point. That amount depends on how much sound was imaged through the specimen. Mapping the small motions of the pellicle with the laser interferometer technique provides an image of the specimen on the cathode-ray display tube.

With a 15-milliwatt laser, the system has a potential sensitivity of about 5 nanowatts-per-square-centimeter, corresponding to a membrane displacement of .007 angstroms at 1.5 MHz. The system has a wide frequency response—about 0.5 MHz to approximately 10 MHz. **R-E**

INTERNATIONAL
FM 2400CH

FREQUENCY METER for testing mobile transmitters and receivers

- Tests Predetermined Frequencies 25 to 1000 MHz
- Extended Range Covers 950 MHz Band
- Pin Diode Attenuator for Full Range Coverage as Signal Generator
- Measures FM Deviation



The FM-2400CH provides an accurate frequency standard for testing and adjustment of mobile transmitters and receivers at predetermined frequencies.

The FM-2400CH with its extended MHz. The range covers 25 to 1000 frequencies can be those of the radio frequency channels of operation and/or the intermediate frequencies of the receiver between 5 MHz and 40 MHz.

Frequency Stability: $\pm .0005\%$ from $+50^\circ$ to $+104^\circ\text{F}$.
Frequency stability with built-in thermometer and temperature corrected charts: $\pm .00025\%$ from $+25^\circ$ to $+125^\circ$ (.000125% special 450 MHz crystals available).

Self-contained in small portable case. Complete solid state circuitry. Rechargeable batteries.

FM-2400CH (meter only)\$595.00
RF crystals (with temperature correction) ... 24.00 ea.
RF crystals (less temperature correction) 18.00 ea.
IF crystalscatalog price

Write for catalog!



Circle 61 on reader service card

DELUXE DIGITAL COLOR CONVERGENCE GENERATOR

NOW AT A PRICE EVERYONE CAN AFFORD

ROCK SOLID PATTERNS
ALL IC COUNTDOWN CIRCUITS
QUARTZ CRYSTAL OSCILLATORS
2 FULL YEARS' WARRANTY




MODEL SG-200 \$99⁹⁵

10 Patterns: Full & Gated Rainbow, 4 Crosshatch, 4 Dot, Die Casted 1/8" Aluminum Case.



MODEL SG-150 \$75⁹⁵

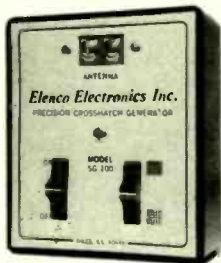10 Patterns: B&W Bars, White Field, 4 Crosshatch, 4 Dot.



MODEL SG-100

ONLY \$59⁹⁵

2 Patterns: 20 x 16 Crosshatch, 320 Dots, weight only 17 oz.

FULL 15 DAYS MONEY BACK GUARANTEE

See Your Distributor or Write:

ELENCO ELECTRONICS INC.
8744 W. North Ter., Niles, Ill. 60648

312-564-0919 MODEL SG-_____

- My check or money order enclosed.
 COD—Add \$2.50 mailing & handling.

NAME _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

DISTRIBUTORS' INQUIRIES INVITED

Circle 62 on reader service card

STEP-BY-STEP

(continued from page 60)

the receiver again plugged into a line isolation transformer, the waveforms swing out tall and steady. Top trace in Fig. 4, now has more than 20 volts AC swing with a DC level in excess of 40 volts, and with the color control only half open. This waveform should swing to 40 volts with the color control turned fully clockwise—and it does. As a backup, and without using double photo exposure, the B-Y output of this set is also shown in the lower trace of Fig. 4 at 50 volts/division. Therefore, it is riding at a DC level of just over 150 volts, the 3rd and 9th bars are at zero reference, and the overall waveform, including the 10- μ s blanking pulses amounts to a total amplitude of 120 volts.

Now, with the tuner set on channel 3—which accommodates most color bar generators—the vector pattern turns out as shown in Fig. 5. Naturally I did a little fine tuning immediately after transistor replacement, and touched up the two bandpass transformers and chroma input coil L501 for best waveform symmetry, no petal crossovers, and put the R-Y third bar at about 90 degrees. You may enlarge this pattern, of course, by merely adjusting your oscilloscope's vertical amplifiers—if you have a modern scope. The smaller display, however, looks cleaner, and makes a somewhat better photograph than does a more spread out pattern. In vector-aligning chroma stages, you *always* start with the chroma takeoff coil, get your narrow petal width, then continue with the first and second bandpass transformers, in that order. Usually, the entire pattern is shaped by these three circuits, with burst and the 3.58 MHz coils having to operate on tint phase settings and R-Y, B-Y demodulator references that select color injection into the various segments of the combined luminance-chroma picture. Consequently, since this is an RBG-Y color difference set where luminance goes to the cathodes of the picture tube and chroma to its grids, the color-video mix takes place in the tube itself.

Color faults aren't that tough

Color problems aren't really all that difficult, if you'll remember there are three basic signal paths that must be operated on in the chroma sections. These signal paths are as follows:

1. The 3.08-4.08 MHz, 1 MHz color bandwidth information.
2. Burst amplifier enabling pulses from either the sync separator (Japanese sets) or from the fly-back (U.S. sets).
3. Burst, itself, that normally enters the first bandpass amplifier (along

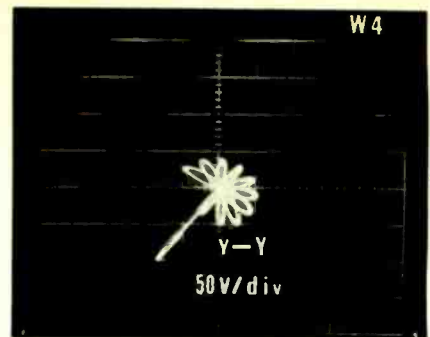


FIG. 5—NORMAL VECTOR PATTERN is shown aligned and with full amplitude.

with color), is amplified and *then* put to the burst amplifier for color sync processing.

If all three inputs are identified and followed through their respective stages of amplification and demodulation, there is no way you can miss finding a chroma problem. But digging with an aged VOM or VTVM, especially in solid state circuits, won't resurrect the dead. You'll find it takes an oscilloscope—and a very good one—every time. In chroma circuits, your AC amplitudes—let's forget the term peak-to-peak, it's confusing—and your DC levels should be investigated simultaneously for competent signal analysis. And a good vectorscope will tell all. The final waveform, Fig. 5, now has scope amplifiers set at 50 volts/div., for R-Y, B-Y picture tube inputs, where they should be for most *all* color receivers. If you have to drop to 20 volts, as we did in Fig. 2, somebody's in trouble . . . Let's hope it isn't you. But even troubles like this are simple if logical troubleshooting procedures are followed.

R-E

HELP AMERICA WORK.

Hire the disabled vet.

He can handle most jobs as well as anyone else. Maybe even better. So if you have a job to give, call the National Alliance of Businessmen.

Get people off the welfare rolls, and on the payrolls.

 **The National Alliance of Businessmen**

READER QUESTIONS

(continued from page 69)

TRANSISTOR REPLACEMENT?


I need a horizontal output transistor for a Westinghouse V-2483-1 chassis. The part number is 29V069C01, and it isn't listed. No one seems to know what to use in here. Can you help?—W.M., Pittsburgh, PA.

You're right; this one isn't listed in any of my seven transistor guides either. However, from the schematic and the ratings, something like an RCA SK-3111 ought to do, or a Motorola HEP-S7005. Both of these seem to have ample safety factors. For the best way, use a variable-voltage line transformer when you turn it on the first time, with current meters, etc. Saves a lot of trouble!

A ROLLS-ROYCE RADIO RELAY?

I want a relay circuit, like the one used in Rolls-Royce cars, that will switch the speakers from radio to tape automatically when the tape deck is turned on. Do you know where I could get this?—L.G., Astoria, NY.

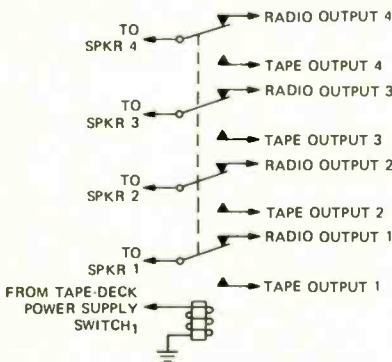You'll need a 12-volt DC, 4PDT relay. Hook it up as shown. The relay connects the four speakers to the radio



when it is not energized. Connect the relay coil lead to the tape-deck motor connection so that when the tape-deck is turned on, it energizes the relay.

WHERE'S THE OTHER TRANSISTOR?

I can't find the other transistor in the horizontal output stage of this little GE TA chassis. It shows it on the print I have, but I can't find it in the schematic! What's going on?—A.B., Key West, FL.

You have the horizontal output transistor in there. There are no more transistors in this circuit. You're being caught by one that's got a lot of people. What you're looking for is the damper diode! In this set, this is a GE Part ET57X34, and it is in a TO-3 transis-

tor case! It is mounted right alongside the horizontal output transistor, on the heat-sink.

NO HIGH VOLTAGE

If I take the plate-cap off the horizontal output tube in this Zenith 19CC19, all voltages are normal except the high voltage, of course. If I put this cap back on, everything goes to pieces. It squeals, the high voltage starts to build up and the 26LX6 gets red hot. Horizontal frequency goes away off. Can't get any help from anyone else; how about you?—P.K., Cherry Hill, NJ.

We'll sure give it a good try! This sounds familiar. These are exactly the kind of symptoms you get when you have a filter capacitor open in the wrong place (meaning the B+ feed to the horizontal oscillator/output stages. This allows a feedback to be set up. This can cancel out the horizontal oscillator, cause a loss of drive and all of the other goodies you see.

Easy check; just scope all of the DC voltage supply lines. You should see nothing at all on them, except a nice straight line. Any horizontal-frequency pulses mean trouble. Replace capacitors. R-E

BARGAIN BONANZA

OF

EDLIE

HIGHEST QUALITY

KITS

ONLY NEW PRODUCTS

LED's — IC's

- (CT7001) CLOCK \$5.95
Alarm & date. With data.
- (MM5314) CLOCK \$4.95
6 digit, hold count, w/data.
- (8038) VOLT. CONT. OSC. \$4.95
With data.
- (LM309K) 5 volt 1 amp REGULATOR \$1.20
- (E293) SEVEN SEGMENT LED's \$1.00
14 pin DIP guar.
- (E102) CALCULATOR KEYBOARD \$3.95
Wild Rover C-1380. Can be used with CT5001. 4 function, clear, clear entry and constant. 7 cm x 9 cm.
- (E223) 10 ASST. LED's guaranteed \$1.00
- (E242) 3 LED's Yellow or green (specify) guar. \$1.00
- (E001) 5 RED LED's guaranteed \$1.00

- (E175) 70 1/2w CARBON RESISTORS \$1.00
Asst. values. Some 5%.
- (E154) 150 CUT LEAD RESISTORS \$1.00
Carbon, all leads long enough for soldering.
- (E149) 20 POLYSTYRENE TOP GRADE CAPACITORS \$1.00
Popular sizes.
- (E253) 7 AMP POWER TRANSISTOR \$1.49
SI NPN. Similar to SK3054. 90v, 90w.
- (E132) 20 DUAL POTENTIOMETERS \$1.00
Asst. ohmages.
- (E138) 10 SLIDE SWITCHES \$1.00
All types: DPDT, SPST, etc.
- (E134) 8 ROTARY SWITCHES \$1.00
Some multiple gang.
- (E125) 4 TRANSFORMERS \$1.00
Some power, filament, output, worth up to \$10 each.
- (E144) TRANSISTOR REPAIR KIT \$1.19
Various parts used to repair transistorized devices.
- (E137) 10 INSTRUMENT KNOBS \$1.00
Made by Rathcon, etc. With set screws. "1/4" shaft."
- (E164) 4 ROLLS OF WIRE \$1.00
Approx. 25 ft. per roll, 20-28ga.
- (E148) 4 ROCKER SWITCHES \$1.00
Assorted.

- (E141) 6 RCA JACK STRIPS \$1.00
From 2-6 per strip.
- (E142) 50 PRECISION RESISTORS \$1.00
All 1%, 1/2w and 1w, low and high ohmages.
- (E128) 13 MINIATURE ELECTROLYTIC CAPACITORS \$1.00
Axial & upright, popular values.
- (E150) 15 HI-FI KNOBS \$1.00
Every one superb! Purchased from Harmon Kardon, Fisher, etc.
- (E156) 60 DISC CAPACITORS \$1.00
Asst. from .0001 to .1, most 600v, 25U, NPO, N750, etc.
- (E147) 4 lb. GRAB BAG SPECIAL \$1.00
Full of exotic and exciting electronics parts.
- (E155) TUBE BONANZA! \$1.00
20 asst. popular tubes, untested.

MONEY BACK GUARANTEE

Terms: Minimum order \$4.00. Include postage. Either full payment with order or 20% deposit, balance C.O.D.

WRITE FOR FREE VALUE PACKED CATALOG

Listing thousands of components, tubes, transistors, IC's, kits, test equipment.

BONUS

FREE CAPACITOR KIT

With Every \$5 Purchase

SURPLUS TUBES

All guaranteed for 1 full year.

ANY 3 FOR \$1.25

Acquired from U.S. Defense depots or removed from equipment (new and used). These are laboratory tested and guaranteed for one full year. Most are of such standard makers as RCA, GE, etc.

3A3	6A05	6DE4	6X4
3AF4	6A07	6DR7	10EW7
3BN6	6A76	6DW4	12AE7
3DG4	6AU6	6EA8	12AL5
3EJ7	6AV6	6EB8	12AL11
3KT6	6AV11	6EJ7	12AT7
3Q4	6AX4	6EM7	12AU7
4BC5	6AX5	6ER5	12AV6
4BN6	6AY3	6EY6	12BE6
4BU8	6AY11	6GF7	12BH7
4BZ7	6BA6	6GH8	12C8
4CY5	6BG6	6GN8	17JZ8
4HA5	6BJ8	6GU7	18FW6
5V6	6B06	6K6	21KQ6
5Y3	6B26	6K11	25L6
6AC7	6CB6	6LB6	35EH5
6AF4	6C67	6SN7	3Z5
6AG5	6CL6	6T8	36AM3
6AG7	6CM7	6V6	50A5
6AL5	6DA4	6W4	50L6
6AL7			

- (E140) TAPE RECORDER SPARE PARTS KIT \$2.95
Parts for repairing most tape recorders: capacitors, meter, pilot lamp, jacks, and MUCH MORE.
- (E167) 10 MINIATURE POTENTIOMETERS \$1.00
For transistor applications.
- (E145) 50 TIE LUGS \$1.00
From 2 lugs up.
- (E182) 2 MISC. METERS \$1.00
Miniature.
- (E222) 20 DIODES 1A 50V-IP. Epoxy, guar.
- (E126) 10 HUM BALANCERS \$1.00
Asst. values.
- (E575) BATTERY CLIPS \$.15
For stand. 9v battery.
- (E1094) DISPENSER PACK SOLDER \$.59
60/40 Rosin Core, .04" x 110".
- (E174) 20 SCREW TERMINAL BOARDS \$1.00
Speaker type, from 2-8 term.
- (E136) 50 RADIO KNOBS \$1.00
Asst. shapes, sizes, colors.
- (E377) SMALL PHONO ARM \$.99
Complete with cartridge. Used in many children's phonos.
- (E005) 50 FEET SHIELDED CABLE \$1.00
- (E006) SHIELDED WIRE KIT \$1.00
10 pcs. of heavy gauge 28" cable.


EDLIE ELECTRONICS, INC., 2700-E HEMPSTEAD TPKE., LEVITOWN, N.Y. 11756

Circle 63 on reader service card

new products

More information on new products is available from the manufacturers of items identified by a Reader Service number. Use the Reader Service Card inside the back cover.

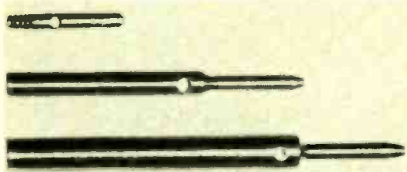
SOLDERING IRON TIPS. Vented Tunnel Tips solder and desolder, all with the same tip. New design optimizes capillary action to enable both functions alternately and continuously. Only the use of "flux" is essential to maintain capillary action. The unique design



permits the tip to surround the connection to both solder and desolder. Tips range in price from \$1.98 each to \$2.28 each and are available for American Beauty, Ungar, Hunter, Esico, Kwickie, Wall-Lenk and Weller soldering irons.—Joe Nicosia, c/o Gunmaster, Box 743, Kings Park, NY 11754.

Circle 31 on reader service card

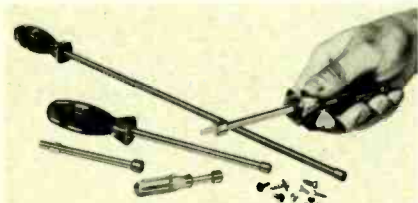MAGNETIC NUTDRIVERS. With fixed handles are available in four styles, each in two sizes. The line also includes two sizes of interchangeable shanks which fit in all Series-99 handles, both regular and ratchet types. The permanent Alnico magnet in the



insulated socket holds fasteners firmly for easy, one-hand driving. Styles range from a 3½ in. midget pocket clip to a super long 20¾ in. driver, all in ¼ and 5/16 in. hex openings. Intermediate lengths are 7 and 10 in. Handles are color-coded red or amber.—Xcelite, Apex, NC 27502.

Circle 32 on reader service card

3½ DIGIT DVM, model DVM32. Portable unit is powered by standard "C" cells, rechargeable, or optional 115/230V line-cord power-adaptor. "Auto-off" circuit turns the LED display off between measurements on any range, when in the AUTO position. A continuous display is available in the normal ON position. The unit has a basic 0.5% DC volts accuracy with 1 mV resolution backed by a 15-megohm input impedance. A 200K isolation resistor in the probe further reduces potential loading error. DVM Lo Power ohms mode uses .08V test voltage that will not trigger semiconductor junctions during resistance measurements. Accessory high-voltage probe will extend the 2000V range to 40kV for complete measuring capabilities.

Specifications: **DC VOLTS:** 4 Ranges; 0 to

1.999, 19.99, 199.9, 1999. **AC VOLTS:** 4 Ranges; 0 to 1.999, 19.99, 199.9, 1000 volts RMS. Accuracy: 1.5% at 60 Hz from ¼ scale to full scale, 3% from 1/10 to ¼ scale plus or minus 1 dB from 40 Hz to 3 KHz. Input Impedance: 1.8 megohms shunted by 18pF. **OHMS:** Low Power: 5 Ranges; 0 to 199.9 ohms, 1.999K, 19.99K, 199.9K, 1.999 meg-



ohms. Accuracy: 1%. Maximum Test Voltage: 80 millivolts. **OHMS:** High Power: 5 Ranges; 0 to 1.999K, 19.99K, 199.9K, 1.999 megohms, 19.99 megohms. Accuracy: 1% on all ranges except 5% on 19.99 megohms. Maximum Test Voltage: 800 millivolts. **DC CURRENT:** 4 Ranges; 0 to 1.999, 19.99, 199.9, 1999 milliamps. Accuracy: 1%. **AC CURRENT:** 4 Ranges; 0 to 1.999, 19.99, 199.9, 1999 milliamps. Accuracy: Same as AC volts.

Unit weighs 2¼ lbs., measures 7 in. wide × 5 in. high × 4 in. deep. Complete with direct-input probe. The price is \$198.00.—Sencore, 3200 Sencore Drive, Sioux Falls, SD 57107.

Circle 33 on reader service card

DIGITAL MULTIMETER KIT, model 1M-2202. 3½ digit display features automatic polarity indication and decimal point placement. Continuous rotation range switch and four pushbutton function switches select any of the ranges. Portable unit is powered by four rechargeable nickel-cadmium batteries and




a built-in charging circuit for up to eight hours of continuous operation. The unit can also be operated from 110 or 220 VAC. 26 ranges include full scale ranges of 100 mV to 1000 volts DC, 100 mV to 750 volts AC, 100 µA to 1000 mA and 100 ohms to 1000K ohms. 100% overrange capability allows measurements up to 1.999 on all ranges except 1000 VDC and 750 VAC, giving full 2A or 2 megohm capability. Overage is auto-

matically indicated by a flashing "1" display.

If Lab standard is used for calibration, DC accuracy is ±0.2%. For AC, accuracy with a lab standard is ±0.5% to 10 kHz. Internal standards supplied with the kit allow easy field calibration to ±0.5% for DC and ±1% for AC. Heath Company, Benton Harbor, MI 49022.

Circle 100 on reader service card

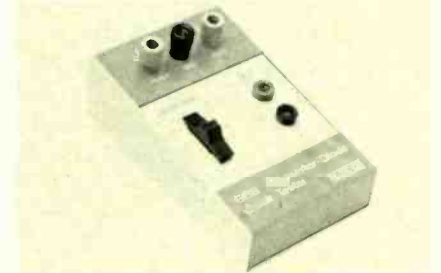TRANSISTOR CHECKER, model 688. Test semiconductors in or out of circuit. Use this unit with your oscilloscope and touch the semiconductor with the probe. The waveform tells its condition at a glance. Switch



selection for "in" or "out" of circuit testing. Checks all diodes and transistors (except MOS FETS). 5-Way binding posts for inter-connection to the scope. Prices: \$14.95 kit, \$22.95 assembled.—Eico Electronics, 283 Malta Street, Brooklyn, NY 11207.

Circle 34 on reader service card

TEST JIG CABLE AND ADAPTER KITS. Six new models, one each for servicing RCA, Admiral, Magnavox, Philco, Sylvania and Zenith color-TV. Use with RCA color test jig. Each adaptor packed in plastic case that's



stackable. Shoe box size cases have sliding drawer to make handy storage assembly when no longer needed for the storage of the test jig kit.—RCA Distributor and Special Products Div., P.O. Box 100, Deptford, NJ 08096.

Circle 35 on reader service card

DIGITAL MULTIMETER, model PM2513. LSI circuit performs part of the analog circuit functions, the A/D conversion and the digital signal evaluation, reducing the total number of circuit components. A 3½ digit, seven segment LED display with automatic decimal point. Functions selected by push-buttons, ranges with a rotary switch. AC and DC voltages are measured in 5 ranges, from 0.1 to 600V and 0.1 to 1000V, respectively. Resolution is 100 µV in the 0.1V range and accuracy is ±0.2% full-scale ±0.3% of reading for DC and ±0.2% full-scale ±1% of

reading for AC. Errors due to the instrument loading are reduced by a 10 megohm input impedance. Five AC and DC current ranges extend from 100 μ A to 1A full-scale, with a resolution of 100 μ A in the lowest range. Accuracy for both current and resistance measurements is 0.2% full-scale \pm 1.5% of reading.

Unusual feature is built in provision for temperature measurements which can be



made with an optional probe. Surface temperature measurements cover -50° C to $+200^{\circ}$ C, with a resolution of 0.1 $^{\circ}$ C and an accuracy of \pm 1 $^{\circ}$ C.

Unit is powered by 6 standard 1.5V size C batteries. To increase battery life, the circuitry is normally at rest and switched on by means of a special push button for 25 seconds each time a measurement is taken. Optional rechargeable battery pack or normal line voltage is available. Unit measures 7.3 in. high \times 6 in. wide \times 2.6 in. deep and weighs 3 pounds including batteries. Price is \$245.00. The optional temperature probe, model PM9247 is \$75.00, a rechargeable battery pack is \$15.00.—**Philips Test & Measuring Instruments, Inc.**, 400 Crossways Park Drive, Woodbury, NY 11797.

Circle 36 on reader service card

CASSETTE DECK WITH DOLBY. model CT-F6161. New cassette deck offers front panel access for cassettes and all operating controls. As a result, the newly designed unit can be mounted in only 5 1/2 inches of shelf height or may be stacked above or below other components. Designed for use with available cassette tapes, the unit presents low distortion and high signal-to-noise ratio and dynamic range. Transport system is




powered by an electronically controlled DC servo motor for high starting torque and is immune to voltage or load fluctuations. Features include built-in selectable Dolby noise reduction for up to 10 dB signal-to-noise improvement. Separate bias and equalization switches for standard, low noise, Chrome and Ferri-Chrome tapes. Illuminated VU level meters plus record mode indicator light. Automatic stop at end of tape travel in play, record and fast wind modes. Three-digit tape counter. Pause control, separate dual mic and line inputs, line outputs and DIN connector. Built-in monitoring amplifier and headphone jack. Specifications include: Frequency response: 30 to 13,000 Hz (40 to 11,000 Hz \pm 3 dB, standard tape); 30 to

16,000 Hz (40 to 12,000 Hz \pm 3 dB Chromium Dioxide tape). Signal-to-noise ratio: 58 dB with Dolby on; 48 dB Dolby off (standard tape). Wow and flutter: Less than 0.12% (WRMS). Equalization: Standard or 70 μ S (Chrome), selectable. Fast forward or rewind time: Less than 80 seconds (C-60 tape). Input sensitivity: 0.2 mV or 90 mV, Mic; 60 mV to 9 V, Line; 6 mV to 2.7 V DIN. Output level: 300 mV, Line and DIN; 40 mV/8 ohms, Headphone output. Power Requirements: 120V, 60 Hz, 16 watts. Size. 17-13/32 in. W \times 5-7/16 in. H \times 13 in. D. Price: \$299.95.—**U.S. Pioneer Electronics Corp.**, 75 Oxford Drive, Moonachie, NJ 07074.

Circle 37 on reader service card

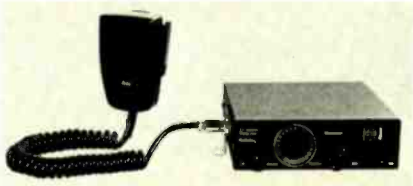
23-CHANNEL CB TRANCEIVER. model CB 720. One of two new entries in the CB field features automatic noise limiter, rotary volume on/off control, public address push-button control, illuminated signal-radio frequency meter, rotary squelch control, built-in



noise suppression and color-coded channel selector with lighted channel-indicator. Mobile unit will work with either positive or negative ground, has an external speaker jack, a quick mount snap on microphone bracket, and a very convenient antenna connector. Comes complete with all necessary wiring and mounting hardware. **Boman Industries**, 9300 Hall Road, Downey, CA 90241.

Circle 38 on reader service card

BUBBLE ETCHER. Designed to satisfy the printed circuit requirements of small shops. The bubble etcher offers semi-automatic operation and requires only periodic inspection of the board. Vigorous bubbling action provides fast etching while reducing the possibility of staining or undercutting. Unit consists of an etching tray connected to an aquarium air pump that provides bubble agitation of the etchant. The tray and bubble

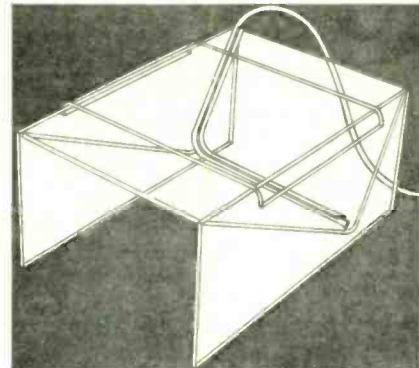


source are designed to maximize etching rate as determined by the pressure and velocity of the bubbles. The unit is built of 1/8" acrylic which allows etchant temperatures of up to 200 $^{\circ}$ F. The unit measures 11 \times 5 \times 7 1/4 inches which permits etching of boards up to 6 \times 8 inches. A splash guard protects the surroundings. The unit comes complete and ready to use, except for an easily obtainable aquarium pump. The price is \$12.00 excluding pump, \$17.50 including pump.—**Trumbull**, 833 Balra Drive, El Cerrito, CA 94530.

Circle 39 on reader service card

Swap 75 GE flaps for one book S&H Green Stamps. Offer ends November 30.

TAKE GE and Award Yourself!

BOTTOMS dΩ

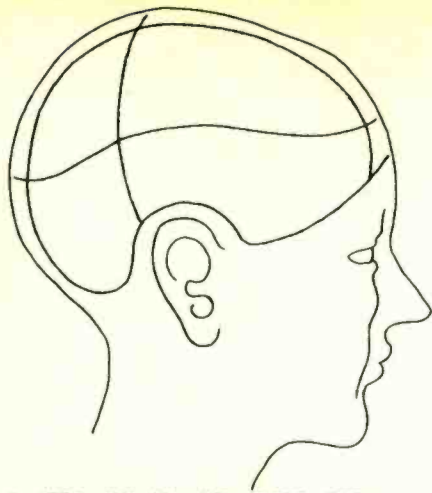

'GET INTO YOURSELF'

Discover your Alpha Brainwaves with this professional Biofeedback System.

Lowest Cost Brainwave Monitor

EICO introduces a price breakthrough in the fantastic new field of brainwave biofeedback... a completely safe, battery operated, biofeedback system that offers features and sensitivity comparable to professional models costing much more.

You Will Be Amazed At What You Hear

The BW-300 will detect your alpha brainwaves (which occur when you are totally relaxed) and produce a tone varying in frequency according to your mental state.

100% Solid State Circuitry

Reliable All Solid State IC Circuit Design features an active filter that isolates alpha brainwaves and a high-gain low-noise amplifier providing 5-microvolt sensitivity for easy alpha recognition. The BW-300 is supplied with stethoscopic earphones, electrodes headband, contact cream and instructions.

KIT 3495
WIRED 59.95

FREE EICO CATALOG

For latest EICO Catalog on Test Instruments, Automotive and Hobby Electronics, Eicocraft Project kits, Burglar-Fire Alarm Systems and name of nearest EICO Distributor, check reader service card or send 50¢ for fast first class mail service.

EICO—283 Malta Street, Brooklyn, N.Y. 11207

Leadership in creative electronics



Circle 64 on reader service card

CHECK-A-COLOR JIG. model CK 3000, is factory tested, fully assembled and ready to use. It can be used on the bench with 48 separate brand name TV sets with anode voltages up to 30,000 volts, and permits fast efficient servicing of 7,000 different solid-state, tube and hybrid color-television chassis. The jig can handle 70° and 90° tubes,



hybrid, transistor and SCR circuitry with a wide range of impedances. A built-in alternate focus supply also permits testing of focus voltages as low as 4.5 kV. A complete set of programmers for the patented yoke circuit is furnished for correct matching to six different receiver deflection outputs. The unit contains a 90° slotted-mask, in-line color picture tube with 13 inches of viewable area and leaded strontium X-ray inhibiting glass. The self contained unit is portable, weighing less than 25 pounds, making it easy to move from one bench to another. Available as optional accessories are adapter kits for the seven most popular TV brands and discrete adapters for 41 more. GTE Sylvania, 70 Empire Drive, West Seneca, NY 14224.

Circle 40 on reader service card

CASSETTE EDIT/REPAIR KIT. Permits recordists to repair a broken cassette tape, yet avoid the almost impossible problems associated with disassembling sealed or screw-held shells. Repairs can be made without disturbing the cassette components. The handy kit can repair most tape breaks. How-



ever, it cannot fix mishaps in which the tape has pulled free from the hub or broken within six inches of a hub. The kit doubles as a precision editing block. One side has a diagonal cutting guide for normal splicing and a butt cutting guide for close editing. A five-inch channel groove holds the tape. Six adhesive-tipped polyester picks for retrieving tape ends lost inside the cassette housing and six pieces of 150-mil splicing tape, pre-cut to proper length are contained inside the kit along with a fully illustrated instruction booklet. Price: \$3.10.—ERK, Dept. MA, Box 33600, St. Paul, MN 55133.

Circle 41 on reader service card



THOUSANDS OF BARGAINS—TOP VALUES IN Electronic Parts

Transistors, Modules, Speakers, Stereo, Hi-Fi, Photo Cells and thousands of other Electronic Parts. Send for **FREE** Catalog




ELECTRONIC DISTRIBUTORS INC.
Dept. TA-2, 4900 Elston
Chicago, Ill. 60630

RUSH CATALOG

Name _____

Address _____

City _____ State _____ Zip Code _____

Circle 65 on reader service card

3

Don't cut yourself out of a career as a two-way radio technician...

MTI offers the only training for professional FM two-way radio available. Qualified technicians are employed in government, industry, and public service. But training is your key.


You could cut out a career as a two-way radio technician by cutting out this coupon. We'll send you information on how you can learn more about this specialized field, at home, for only \$345.

Name _____

Address _____

City/State/Zip _____

I am a veteran or serviceman on active duty.



formerly

MOTOROLA TRAINING INSTITUTE

College Hill, Summerdale, Pennsylvania 17093

Circle 66 on reader service card


CURVE TRACER, model IT-1121. Accurately displays operating parameters of virtually all types of semiconductors including bipolar transistors, diodes, SCR's triacs, FET's, etc. Intended for use by TV service technicians, hobbyists and anyone else who works with



electronic circuits. A semiconductor curve tracer is a valuable aid in selecting devices for specific applications or for sorting, inspecting and testing. It's particularly useful in identifying unknown semiconductors. Price: \$89.95 as a kit.—Heath Company, Benton Harbor, MI 49022.

Circle 100 on reader service card

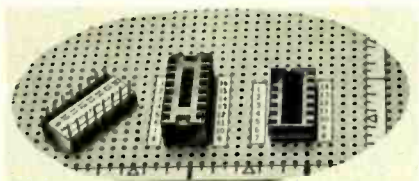PRESS ON LABELS identify DIP socket pins and circuit board hole locations quickly and easily. The 14-pin DIP markers, models MS-9, have double sequential number lines from 1 to 7 on one side and from 8 to 14 on the adjacent side. They're all printed on 0.1-in. centers to match the lead spacing of conventional DIP components. Similar strips are



available for 16-pin DIP's (MS-10) and pairs of single line strips, numbered 1 to 7 and 8 to 14 for 14-pin DIP's (MS-9A), as well as 1 to 8 and 9 to 16 for 16-pin DIP's (MS-10A). All strips are adhesive-backed and self adhering. They come on backing cards. Prices vary from \$1.98 for the MS-9 and MS-10 for a package of 36, to \$2.45 for the MS-9A and MS-10A for a package of 36.—Vector Electronic Co., Inc., 12460 Gladstone Avenue, Sylmar, CA 91342.

Circle 47 on reader service card

BATTERY CHARGER, model GP-1044. A 15A automatic battery charger that can deliver dead battery starts within one minute. A practical solution to dead battery problems in cars, boats and campers using 12-volt lead-acid batteries of automobile size or larger. Unit is completely automatic in the



normal mode, bringing the battery to full charge then automatically shutting down, turning on again only to compensate for normal battery leakage. Pressing a spring loaded switch for not more than one minute gives a 50A boost-surge that puts enough energy into a dead battery to start an

(continued on page 86)

LEADER

Automatic

Dual Channel/Dual Trace

5" Scope/Vectorscope



- Automatic Trigger
- Automatic Horizontal Sweep
- Automatic Vertical Input

And that means virtually error-free, easy operation. You can even read between ranges in any position as with analog VTVM's. Features: separate and simult. sweep display, Ch 1 & 2 - alternate, chopped, auto/normal trigger; 10MHz b'width; 10mVp-p/cm to 20Vp-p/cm vert. sen-

sitivity, 11 calib. steps; 0.5μS/cm to 0.2S/cm sweep range, 18 steps calib; X5 sweep mag.; XY & vectorscope display. Compact, lightweight with low power consumption.

\$569 95

Complete with probes, terminal adapters, test leads.

MODEL LBO-506

LEADER "Put Us To The Test"

Instruments Corp. 151 Dupont St. Plainview, L.I., N.Y. 11803 (516) 822-9300

Circle 67 on reader service card

Now...the most enjoyable

do-it-yourself project

of your life—a Schober

Electronic Organ!


You'll never reap greater reward, more fun and proud accomplishment, more benefit for the whole family, than by assembling your own Schober Electronic Organ.

You need no knowledge of electronics, woodwork or music. Schober's complete kits and crystal-clear instructions show you — whoever you are, whatever your skill (or lack of it) — how to turn the hundreds of quality parts into one of the world's most beautiful, most musical organs, worth up to twice the cost of the kit.

Five superb models with kit prices from \$575 to around \$2,300, each an authentic musical instrument actually superior to most you see in stores, easy for any musically minded adult to learn to play, yet completely satisfying for the accomplished professional. And there are accessories you can add any time after your organ is finished — lifelike big auditorium reverberation, automatic rhythm, presets, chimes, and more.

Join the thousands of Schober Organ builders who live in every state of the Union. Often starting without technical or music skills, they have the time of their lives — first assembling, then learning to play the modern King of Instruments through our superlative instructions and playing courses.

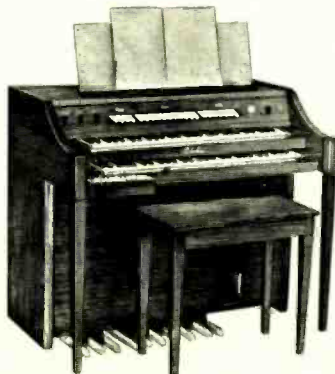Get the full story FREE by mailing the coupon TODAY for the big Schober color catalog, with all the fascinating details!



The Schober Organ Corp., Dept. RE-141
43 West 61st Street, New York, N. Y. 10023




- Please send me Schober Organ Catalog.
- Enclosed please find \$1.00 for 12-inch L.P. record of Schober Organ music.

NAME _____
ADDRESS _____
CITY _____ STATE _____ ZIP _____

Circle 68 on reader service card

The better the training the better you'll

Send for
FREE
illustrated
career
guide

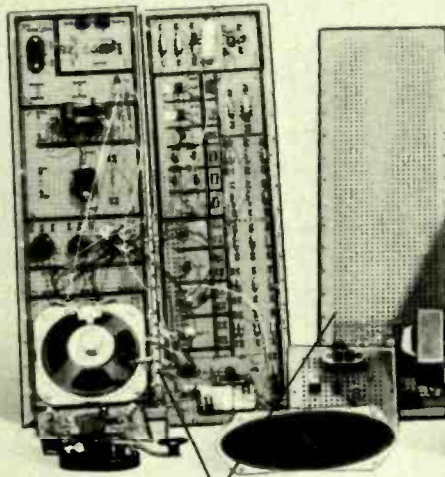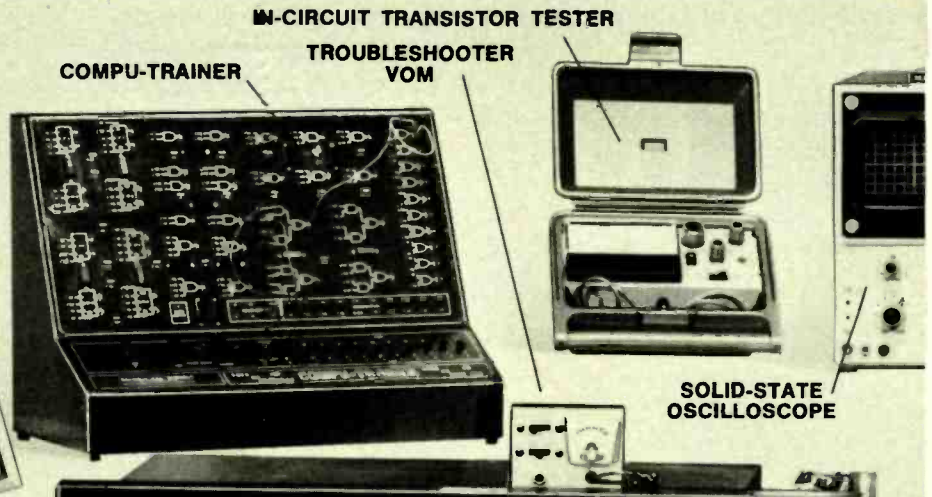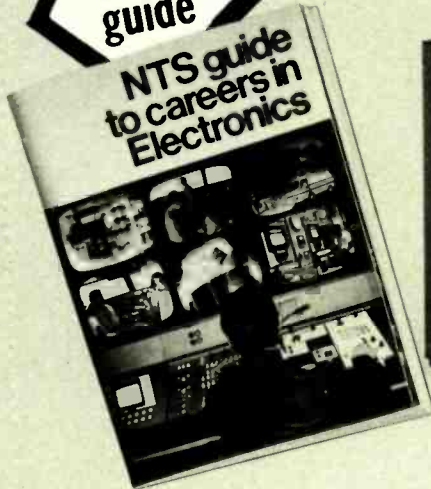

(Simulated TV Reception)

ELECTRO-LAB

As an NTS student you'll acquire the know-how that comes with first-hand training on NTS professional equipment. **Equipment you'll build and keep.** Our courses include equipment like the **NTS/Heath Digital GR-2000 Solid State color TV** with first-ever features like silent varactor diode tuning; digital channel selection, (with optional digital clock), and big 315 sq. in. ultra-rectangular screen.

Also pictured above are other units — 5" solid state oscilloscope, vector monitor scope, solid-state stereo AM-FM receiver with twin speakers, digital multimeter, and more. It's the kind of better equipment that gets you better equipped for the electronics industry.


This electronic gear is not only designed for training; it's field-type — like you'll meet on the job, or when you're making service calls. And with NTS easy-to-read, profusely illustrated lessons you learn the theory behind these tools of the trade.

Choose from 12 NTS courses covering a wide range of fields in electronics, each complete with equipment, lessons, and manuals to make your training more practical and interesting.

Compare our training; compare our lower tuition. We employ no salesmen, pay no commissions. You receive all home-study information by mail only. All Kits, lessons, and experiments are described in full color. Most liberal refund policy and cancella-

and the equipment be equipped.

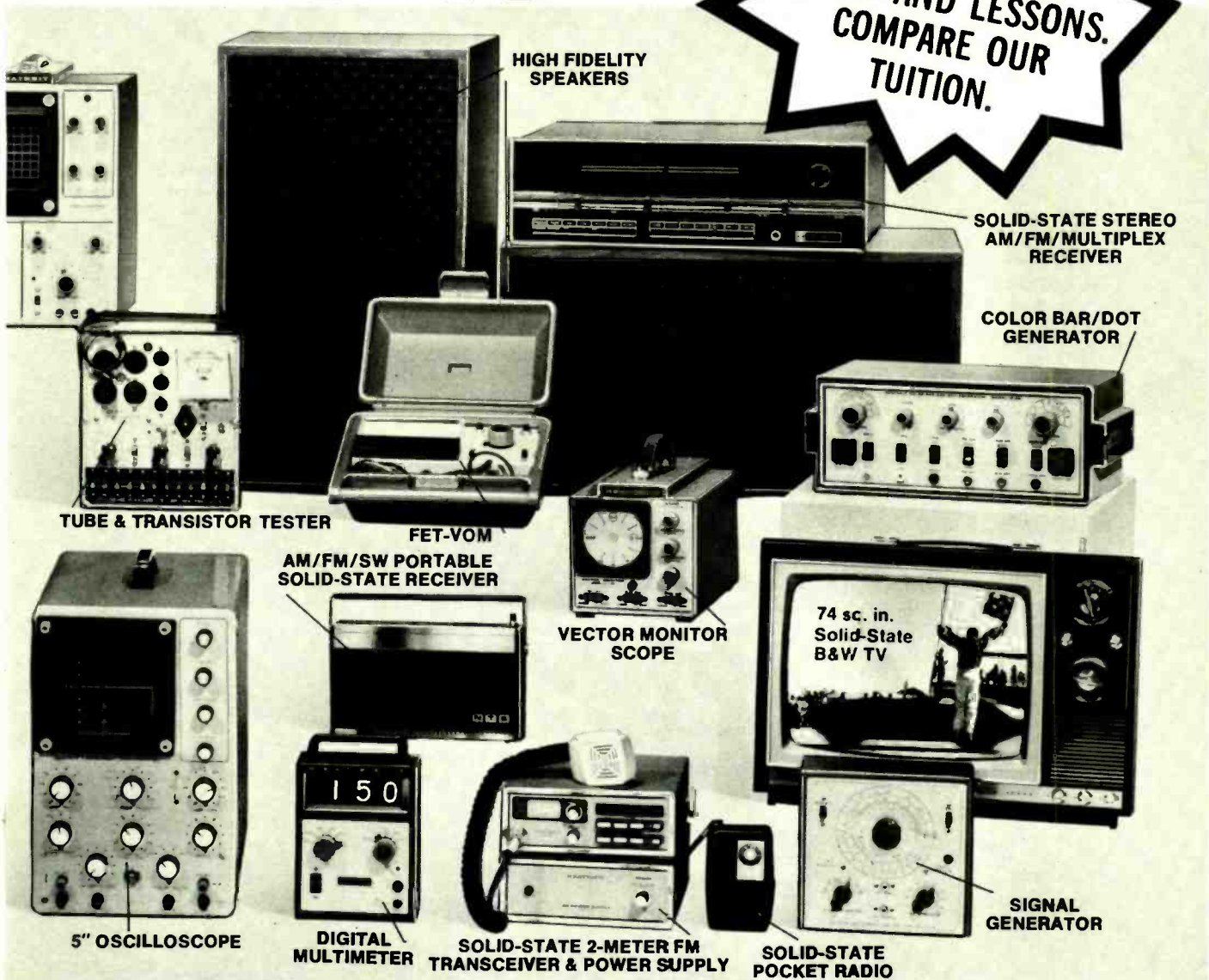**COMPARE OUR
KITS AND LESSONS.
COMPARE OUR
TUITION.**



tion privileges spelled out. Make your own comparisons, your own decision. Mail card today, or clip coupon if card is missing.

NO OBLIGATION. NO SALESMAN WILL CALL

APPROVED FOR VETERAN TRAINING

Get facts on new 2-year extension

NATIONAL TECHNICAL SCHOOLS

TECHNICAL-TRADE TRAINING SINCE 1905

Resident and Home-Study Schools

4000 So. Figueroa St., Los Angeles, Calif. 90037

NATIONAL TECHNICAL SCHOOLS Dept. 206-085

4000 South Figueroa St., Los Angeles, Calif. 90037

Please send FREE Color Catalog and Sample Lesson.
NO OBLIGATION. NO SALESMAN WILL CALL.

- | | |
|---|--|
| <input type="checkbox"/> Color TV Servicing | <input type="checkbox"/> Electronics Technology |
| <input type="checkbox"/> B & W TV and Radio Servicing | <input type="checkbox"/> Computer Electronics |
| <input type="checkbox"/> Electronic Communications | <input type="checkbox"/> Basic Electronics |
| <input type="checkbox"/> FCC License Course | <input type="checkbox"/> Audio Electronics Servicing |


NAME _____ AGE _____

ADDRESS _____ APT # _____

CITY _____ STATE _____

Please fill in Zip Code for fast service _____

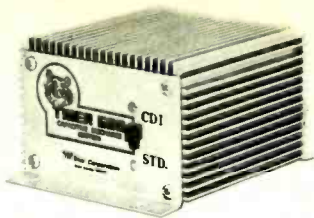- Check if interested in G.I. Bill information.
 Check if interested ONLY in classroom training in Los Angeles.



12 REASONS YOUR CAR NEEDS TIGER CDI

Instant starting in any weather - Eliminates tune-ups - Increases gas mileage - Increases horsepower 15% - Improves acceleration and performance - Spark plugs last up to 70,000 miles - Reduces engine maintenance expense - Amplifies spark plug voltage to 45,000 volts - Maintains spark plug voltage to 10,000 RPM - Reduces exhaust emissions - Dual ignition switch - An Unconditional LIFETIME GUARANTEE - Installs in 10 minutes on any car with 12 volt negative ground - No rewiring - Most powerful, efficient and reliable Solid State Ignition made.

SATISFACTION GUARANTEED or money back

TIGER 500 assembled \$53.95
TIGER SST assembled \$42.95
Post Paid in U.S.A.

Send check or money order with order to:

Tri-Star Corporation

P. O. Box 1727 B
Grand Junction, Colorado 81501

DEALER INQUIRIES INVITED

Circle 69 on reader service card

RGS ELECTRONICS

008A MICROCOMPUTER KIT

8008 CPU, 1024 X 8 memory; memory is expandable. Kit includes manual with schematic, programming instructions and suggestions; all ICs and parts supplied except cabinet, fuses and hardware.

Includes p.c. boards *\$375.00
MANUAL ONLY, \$25.00
(No Discount on Manual)

008A-C AUDIO CASSETTE ADAPTER KIT

Kit includes all ICs, p.c. board, schematic and instructions. Will interface most audio cassette recorders to the 008A Micro-computer. NOT intended to interface with any other computer.

*\$100.00

008A-K ASCII KEYBOARD INPUT KIT

Kit includes keys, p.c. board, ICs, schematic and instructions. This kit is intended to interface ONLY with the RGS Electronics 008A Microcomputer *\$135.00

TRANSISTORS

NPN General purpose TO-92 \$.08; \$5.95/100
PNP General purpose TO-92 \$.08; \$5.05/100

Other transistors and JFETS available at our usual low prices; all are tested, good units. Specs available in our flyer.

RGS ELECTRONICS, 3650 Charles St. Ste K, Santa Clara, CA 95050 (408) 247-0158

We sell many ICs and components not listed in this ad, included most of the 7400 series; send a stamp for our free flyer.

TERMS OF SALE: All orders prepaid; we pay postage on all U.S. orders. Handling charge of \$1.00 on U.S. orders under \$10.00, foreign orders under \$25.00. California residents please include sales tax. Please include name, address, and zip code on all orders and flyer requests.

*DISCOUNTS: 10% OFF ORDERS OVER \$25.00 - 20% OFF ORDERS OVER \$250.

PRICES SUBJECT TO CHANGE WITHOUT NOTICE.

Circle 70 on reader service card

NEW PRODUCTS (continued from page 81)

operable engine. A thermo-sensing automatic-resetting circuit breaker protects against over-charging in the boost mode. Price: \$49.95 as a kit.—Heath Company, Benton Harbor, MI 49022.

Circle 100 on reader service card


SOLDERING IRONS. Featherweight units have heat-resistant or shielded pencil-like handles and extra long cords. Weight varies from 1 3/4 oz. to less than 1 lb, even in the



heavy-duty models. Pre-tinned lips of plated copper are replaceable and range from 25 to 175 watts. Price is from \$5.50 to \$14.00. Weller, The Cooper Group, Apex, NC 27502.

Circle 48 on reader service card

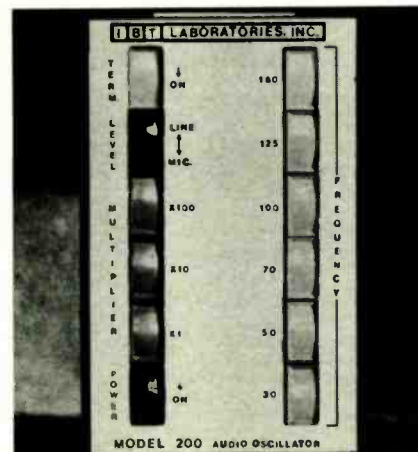OSCILLATOR, model 200. Battery-powered audio (sinewave) test oscillator is housed in extruded aluminum case and features 21 pushbutton selectable frequencies that range from 30 Hz to 20 kHz. Output levels of 0 dBm or -50 dBm are available by



pushbutton selection with level tracking of ± 0.5 dB over entire frequency range. Output is transformer isolated, balanced, floating and presents an impedance of 600 ohms at the high level setting and 150 ohms at the low level setting. 2 1/4 x 4 x 3 3/4 in.; \$129.95.—IBT Laboratories, Inc., 5200 Myer Court, Rockville, MD 20853.

Circle 49 on reader service card

ELECTRONIC WATCHDOG. Provide insurance for yourself when out of town. If the door of your hotel or motel is opened, a piercing alarm will sound. If the intruder tries to deactivate the unit by standing it upright again or by pushing the only button visible, the unit will not shut off. You are the only one who knows the secret of deactivation. 100% solid-state circuit; elec-

tronic oscillator (2900 Hz) produces over 80 dB audio alarm; battery powered with



two 9-volt transistor batteries; 2 X 9 in.; less than 8 oz.; \$30.00.—Harris Electronics, 271 Mimosa Way, Portola Valley, CA 94025.

Circle 50 on reader service card

SCOPES

(continued from page 59)

X-Y phase measurements

Within the frequency limitations of the horizontal and vertical amplifiers, the X-Y oscilloscope can be used to make phase measurements. The phase measurement technique is similar to the Lissajous frequency measurement. To measure phase, horizontal and vertical amplitude measurements are taken, from which phase angle is computed. For phase measurements, horizontal and vertical display amplitudes must be identical and horizontal and vertical frequencies the same. Independently adjusting each channel, using the variable attenuator, to set the display amplitude at an equal number of divisions is a simple method of assuring identical amplitudes. Figure 22 shows the various 45° phase relationships.

As shown in Figure 23, the exact phase

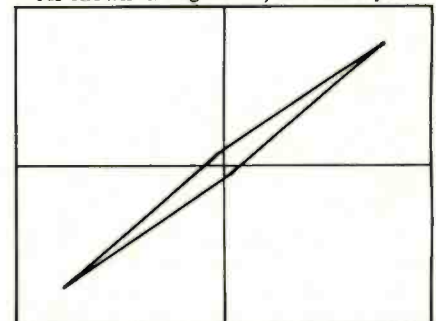


FIG. 24—A 1° PHASE SHIFT measured on an X-Y oscilloscope.

relationship may be calculated. Phase measurements made on an X-Y oscilloscope must include any phase difference between the X and Y channels of the oscilloscope at the measurement frequency. For comparison purposes, Figure 24 shows a 1° phase-shift.

(continued next month)

IGR
EMPLOYER SUPPORT OF
THE GUARD & RESERVE

new lit

All booklets, catalogs, charts, data sheets and other literature listed here with a Reader Service number are free. Use the Reader Service Card inside the back cover.

FM TWO-WAY RADIO correspondence course is described in this 8-page pamphlet. The booklet outlines the contents of 40 lessons and 13 reference texts are included with the course offered by Motorola Training Institute. The course covers FM two-way radio from the service technicians point of view.—MTI, College Hill Rd., Summerdale, PA 17093.

Circle 42 on reader service card

MICROPHONE SELECTION AND APPLICATION GUIDE. The *Music-Maker's Manual of Microphone Mastery* presents tips from leading sound engineers on how to select and use microphones plus guidelines for on-stage miking situations. The brochure describes in non-technical terms how to professionally mike voices and instruments with listings of soundman-proved techniques for handling especially troublesome sound pickup situations. Also featured are recommended microphones for specific instrumental and vocal styles, microphone positioning hints and a description of a variety of accessories that professional entertainers find helpful—Shure Brothers Inc., 222 Hartrey Avenue, Evanston, IL 60204.

Circle 43 on reader service card

RECORD CARE BOOK. *Just For The Record.* A 28-page book that deals with topics such as the problems of dust and static, how to handle records properly, playing records with changers and automatic turntables, rejuvenating old records, the treatment of 4-channel records, and many other areas that will prove invaluable to anyone who collects and plays records. In addition to offering specific tips on record cleaning, storage and maintenance, the book presents data on stylus and turntable platter care. It also explains the effects of record cleanliness on tracking force. Methods of static elimination are also described.—Eipa Marketing Industries, Inc., New Hyde Park, NY 11040.

Circle 44 on reader service card

A REVOLUTION IN IGNITION SYSTEMS. A 24-page booklet that traces the history of conventional ignition systems describes component functions and details the relatively recent move to electronics. The balance of the book describes the manufacturer's Tiger capacitive discharge ignition system and presents comparative data on transistor and conventional ignition systems.—Tri-Star Corp., P.O. Box 1727, Grand Junction, CO 81501.

Circle 45 on reader service card

BREADBOARDING DEVICES is the subject of this 14-page colorful brochure. The full line of this manufacturer's breadboarding products range from a \$5 Proto-clip for power-on-hands-off signal tracing through a logic monitor and on to a variety of breadboarding assemblies. All should be of interest to both the experimenter and industrial technician.—Continental Specialties Corp., 44 Kendall St., New Haven, CT 06512.

Circle 46 on reader service card



LOOKING FOR INNOVATION? LOOK TO PAIA KITS.

Some recent examples . . .

The GNOME. The only Electronic Music Micro-Synthesizer available in a hand held, battery powered package.

\$48.95 shipping wt. 4 lbs.

The PYGMY, battery powered practice/headphone/stage amp. 8 watts peak power driving super-efficient 5" accoustic suspension speaker.

\$39.95 shipping wt. 6 lbs.

NEW 24 HOUR DEMO-LINE for a one-minute recorded demo of PAIA Synthesizers (405) 843-7396. Catalog requests or charge orders also acceptable.

FREE CATALOG

PAIA Electronics, Dept. R 1020 W. Wilshire Blvd., Oklahoma City, OK 73116

Circle 71 on reader service card

MATHEMATICS ELECTRONICS

We are proud to announce two great new courses for the electronic industry.

These unusual courses are the result of many years of study and thought by the President of Indiana Home Study, who has personally lectured in the classroom to thousands of men, from all walks of life, on mathematics, and electrical and electronic engineering.

You will have to see the lessons to appreciate them!

NOW you can master mathematics and electronics and actually enjoy doing it!

WE ARE THIS SURE: you sign no contracts—you order your lessons on a money-back guarantee.

In plain language, if you aren't satisfied you don't pay, and there are no strings attached.

Write today for more information and your outline of courses.

You have nothing to lose, and everything to gain!

The INDIANA HOME STUDY INSTITUTE

DEPT. RE-875 | P.O. BOX 1189
PANAMA CITY, FLA 32401

Circle 72 on reader service card

New Value For The Cost- Conscious Buyer \$995.00 includes:

- 10 MHz at 10 mV/div •Dual Trace
- Compact Size (4" X 9" X 11") •Probes and Batteries



If your requirement dictates a portable oscilloscope with dual trace and 10 MHz at 10 mV/div sensitivity, but your budget demands frugality, then you should consider the new TELEQUIPMENT D32. It offers 10 mV/div to 5 V/div in 9 calibrated steps, automatic selection of chopped or alternate mode, depending on sweep speed setting, plus automatic selection of tv line or frame display. It also offers a choice of battery or ac line operation . . . with up to 4 hours continuous operation from 6 rechargeable, 'D' cell batteries. The batteries, two probes, and a molded front-panel protective cover are all included as standard equipment.

We feel the D32, at only 10 lbs., is well suited as a servicing tool. Especially for industrial manufacturing, computer peripherals, and voice communication equipment. And it should be considered for servicing the rapidly increasing number of consumer electronic products.

If you agree and would like a demonstration at your convenience and in your environment, or simply additional information, contact your local Tektronix Field Office or write: Tektronix, Inc., P.O. Box 500, Beaverton, Oregon, 97077.



TEKTRONIX®
committed to
technical excellence

Circle 90 on reader service card

Circle 73 on reader service card for demonstration

SONY PIONEER

Sansui

WE'LL SAVE YOU MONEY
ON FAMOUS BRAND
NATIONALLY ADVERTISED
STEREO COMPONENTS,
VIDEO & PROFESSIONAL
PRODUCTS EQUIPMENT
WRITE TODAY FOR OUR QUOTE AND
OUR COMPLETE PRICE CATALOG.
FAST DELIVERY IN FACTORY SEALED CARTONS
FOR IMMEDIATE QUOTE
CALL (202) 723-6066


THE COST OF YOUR CALL WILL BE DEDUCTED
FROM ANY ORDER OVER \$200.00.

A.D.R. AUDIO VIDEO
6200 CHILLUM PLACE N.W.
WASHINGTON, D.C. 20011

Master Charge/BankAmericard Honored on Mail Orders

Circle 74 on reader service card

A Major Advance...

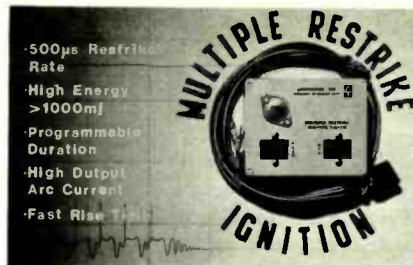

- *500µs Restrike Rate
 - *High Energy >1000mj
 - *Programmable Duration
 - *High Output Arc Current
 - *Fast Rise Time
- *INSURES PROPER COMBUSTION
 - *EASIER STARTING
 - *LONGER POINTS and PLUG LIFE
 - *INCREASE MILEAGE up to 40%
 - *EASY INSTALLATION (12v neg. gnd.)

Labtronics' Multiple Restrike (M-R) Ignition produces a high energy repetitive spark on each power stroke to effectively ignite the air/fuel mixture. M-R statistically insures more complete combustion - resulting in greater energy and increased efficiency. Send for Labtronics' free literature on the M-R system. Better yet, experience M-R and enjoy the pleasure and the economy of a well-performing engine.

- Model VI \$79.95 • 1 Year Warranty •
- Model VI-B \$59.95
- Brochure • 30 Day Money Back Guarantee
- P.P.D. In U.S.A.
- Send Check or Money Order to:

Labtronics, Incorporated
3635 Hillside, Ypsilanti, Michigan 48197

DEDICATED TO EFFICIENCY
Circle 75 on reader service card

books

MODEL SAIL & POWER BOATING... BY REMOTE CONTROL, by George Siposs. TAB Books, Blue Ridge Summit, PA 17214. 192 pp. 8½ x 5¼ in. Hardcover \$7.95; Softcover \$4.95.

This handbook covers all types of model boating—sail and powered, electric and internal-combustion engines. There is no attempt to teach the reader how to assemble one particular type of boat model and it doesn't advocate one specific method of construction. Instead, the author considers all modern techniques and includes enough theory to insure that the reader will understand the basic principles behind the operations of various models and systems. The principles of radio control and radio-control signals are explained in non-technical language. The basics of a control system are enumerated and techniques such as installation, isolating trouble and repairing water damage are covered too. Sail boats, electric-powered boats and internal-combustion engine-powered boats are all covered. To help the beginning hobbyist, there is a chapter on the workshop including recommendations for tools and other useful gadgets.

ELECTRONIC MUSIC PRODUCTION, by Alan Douglas, TAB Books, Blue Ridge Summit, PA 17214. 148 pp. 8½ x 5¼ in. Hardcover \$7.95; Softcover \$3.95.

Although relatively in its infancy, electronic music has already had considerable influence on musicians and composers in all fields. In this book, the tremendous potential of electronic music is described in its freedom from the limitations of conventional instruments and notation. The author suggests rather than displacing human performers, electronic music will provide the basis of a completely new art form in its own right with its own language, performers and devotees. The book deals first with the properties of conventional music, going on to show how their limitations may be overcome by electronic means. The three principal methods of synthesizing music electronically are described with examples of the latest equipment.

AUTO STEREO SERVICE & INSTALLATION, by Paul L. Dorweiler & Harry E. Hansen. TAB Books, Blue Ridge Summit, PA 17214. 252 pp. 8½ x 5¼ in. Hardcover \$8.95; Softcover \$5.95.

For the service technician eyeing the growing field of auto stereo system installation and service, this is an extremely useful book. It covers every phase of installation including mounting and adjustment of FM stereo receivers and tape players and it tells how to get rid of troublesome interference caused by the automotive environment. Also included are 48 complete schematics representing 13 major manufacturers plus many other servicing diagrams and sketches. The largest part of the book is devoted to servicing. The subject of general maintenance covers the mechanical aspects which consume much of the technician's time—dial cord and lamp replacement (illustrated, of course), replacing controls, cleaning and adjusting tape players, demagnetizing and tape splicing.

R-E

TeleMatic MJ-195

MASTER TEST RIG

FOR TUBE AND SOLID STATE SERVICING

\$149.95
less 19" picture tube

- 30 KV CAPACITY
- METAL CABINET
- SPEAKER BUILT IN
- HIGH VOLTAGE METER
- STATIC CONVERGENCE
- FRONT PANEL CONNECTIONS

TeleMatic 2245 Pitkin Ave., Brooklyn, N.Y. 11207

FREE! Adaptor Quick Reference Chart
Circle 76 on reader service card

(continued from page 51)

SCR circuit placed in a full-wave bridge D9 through D12 (See "Hi-Torque Circuit" section of Fig. 1). The SCR is fired during the starting interval, applying full voltage to the appropriate motor. As capacitor C11 charges, transistors Q3 and Q4 reduce the triggering rate of Q5 which fires the SCR. This reduces the SCR's duty cycle until ultimately, Q5 ceases to trigger the SCR completely as the collector current of Q4 becomes zero. The voltage waveforms at the output of the SCR go through the progression shown in Fig. 5 in from three to five seconds, but the final waveform is sinusoidal which results in smooth motor operation.

Electrical braking

When attempting to bring the reels to a stop, a differential braking action must be used. This means that the reel which is feeding out tape should have greater braking action applied to it than the reel which is taking up the tape. Figures 6 and 7 show two typical conditions requiring differential braking. In Fig 7, a heavily loaded tape feed reel would tend to continue its rotation if stopped in FAST FORWARD, while the takeup reel, having little momentum, would stop almost immediately. This would cause tape spill. Conversely, in Fig. 8, a heavily loaded takeup reel would tend to continue rotating longer than the lightly loaded feed reel and this might stretch or even tear the tape. Some manufacturers have solved the problem by eliminating braking completely from the takeup reel. However, this creates a great deal of tension on the tape unless very soft braking is applied and reel size is limited to 7".

Obviously, in a differential braking system such as the one in the Crown 800 transport, more braking must be applied to the tape feed reel than to the takeup reel, but this differential must have specific limits. It must be great enough to prevent a loop from forming under the conditions shown in Fig. 5 but not so great that the tape can stretch or tear under the conditions shown in Fig. 8. Furthermore, because fast winding must take place in both directions, the function of tape-feed and takeup reels must be reversible. In Fig. 8-a, tape is travelling from left to right and the left reel should have the higher braking force. In Fig. 8-b, tape is running from right to left and the right reel is now the tape feed reel and should have the higher braking force.

The electrical braking system of the transport operates by feeding direct current through the reel motors (DC "freezes" these motors while AC makes them turn). DC is provided for

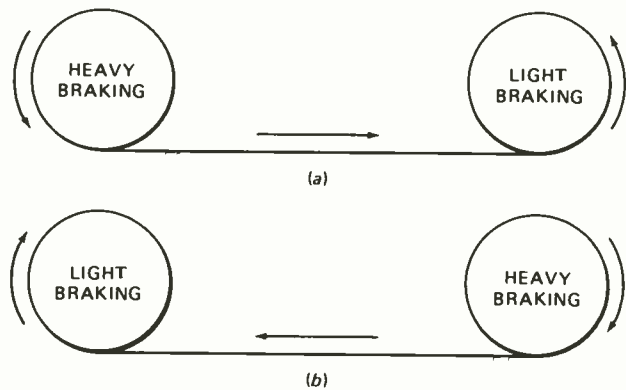


FIG. 8—IN FORWARD direction of tape travel (a), heavier braking is required on the tape-feed reel, while in the rewind mode (b), heavier braking must be applied to the take-up reel.

the motors in both the STOP and STANDBY modes, but the "stop" current is higher. This is done by shorting a series resistor. The required differential action is provided by placing a lesser voltage on the takeup motor than on the tape-feed motor.

Since the stopping torque of such a motor with DC applied is proportional to its rate of rotation, stopping tension due to the differential DC voltage is greater at the start of the braking interval than when the tape has nearly stopped. This means that ideally, the amount of differential voltage should be automatically variable during the braking cycle. One way to do



Think of it as the best tester in your bag. Only \$299

Now you can get a high performance Model 8000A Digital V.O.M. from Fluke, America's foremost maker of quality digital multimeters, especially designed for TV, radio, stereo and audio service. No other digital V.O.M. gives you the resistance range to check breakers and switches, the high resolution voltage to look at emitter base and other transistor voltages, excellent ac accuracy and full accuracy with a 30 second warm-up.

Measures in 26 ranges 100 μ V to 1200 V, 0.1 μ A to 2A, and 100 milli Ω to 20 meg Ω with a basic dc accuracy of 0.1%. Full year guarantee. Low cost options include rechargeable battery pack, printer output, deluxe test leads, HV, RF & 600-amp ac current probes, carrying case, and rack mount. Unique self zero eliminates offset uncertainty. Electronics securely mounted in high-impact case. Service centers throughout U.S., Canada, Europe and Far East for 48-hour turnaround repair.



P. O. Box 7428, Seattle, Washington 98133.

Get all the details from your nearest Fluke sales office. Dial toll-free 800-426-0361 for address of office nearest you.

Circle 77 on reader service card

Accuracy like a VTVM... Convenience like a VOM...

NEW BATTERY-OPERATED FET SOLID-STATE VOLT-OHMMETER #116

Easy-to-build KIT

\$36.90 =116K

Factory-Wired & Tested

\$49.49 =116W



Now you can get all the benefits of a VTVM (laboratory accuracy, stability and wide range) but with its drawbacks gone: no plugging into an AC outlet, no waiting for warm-up, no bulkiness. New Field Effect Transistor (FET) design makes possible low loading, instant-on battery-operation and small size. Excellent for both bench and field work.

Compare these valuable features:

- High impedance low loading: 11 meg-ohms input or DC, 1 megohm on AC
- 500-times more sensitive than a standard 20,000 ohms-per-volt VOM
- Wide-range versatility: 4 P-P AC voltage ranges: 0-3.3, 33, 330, 1200V; 4 RMS AC voltage ranges: 0-1.2, 12, 120, 1200V; 4 DC voltage ranges: 0-1.2, 12, 120, 1200V; 4 Resistance ranges: 0-1K, 0-100K, 0-10 meg., 0-1000 meg.; 4DB ranges: -24 to +56DB.

Sensitive easy-to-read 4 1/2" 200 micro-amp meter. Zero center position available. Comprises FET transistor, 4 silicon transistors, 2 diodes. Meter and transistors protected against burnout. Etched panel for durability. High-impact bakelite case with handle useable as instrument stand. Kit has simplified step-by-step assembly instructions. Both kit and factory-wired versions shipped complete with batteries and test leads. 5 1/4"H x 6 3/4"W x 2 7/8"D. 3 lbs.

Send FREE catalog of complete EMC line and name of nearest distributor. RE-8

Name _____

Address _____

City _____

State _____ Zip _____

EMC

ELECTRONIC MEASUREMENTS CORP.
625 Broadway, New York, N.Y. 10012

this is to have the series resistor value increase with time as the tape is stopping. Crown provides this effect very simply as shown in Figs. 10-a and 10-b, by using a device with a high positive-temperature-coefficient—an incandescent lamp assembly.

High-level relay switching

Three relays control the high-level AC line voltage used in the reel motors and in the pressure-roller (tape lifter) solenoid. The relays are all controlled by the logic circuits. Table I shows

MACHINE MODE	RELAYS			TYPICAL VOLTAGES		
	Op.(RY1)	FWD.(RY2)	(RWD)(RY3)	TU Motor	PO Motor	Sol.(RY4)
STANDBY	0	0	0	+6 VDC	+16.5 VDC	0
PLAY (LG reel)	1	0	0	112 VAC 80 VAC	100 VAC 71 VAC	54 VDC 34.5 VDC
PLAY (SM reel)	1	0	0	78 VAC 55 VAC	69 VAC 49 VAC	54 VDC 34.5 VDC
F. RWD	1	0	1	37 VAC	117 VAC	0
F. FWD	1	1	0	117 VAC	37 VAC	0
RWD BRAKES	0	0	1	+52 VDC	+13 VDC	0
FWD BRAKES	0	1	0	+13 VDC	+52 VDC	0
RWD & FWD (Jockeying)	1	1	1	117 VAC	117 VAC	0

Test Conditions:
 "0" = Relaxed State Line Voltage = 117 VAC No accessories being powered
 "1" = Pulled-in State Reels unloaded and free Meter - 20,000 Ω/volt VOM

TABLE I—Condition of the three high-level switching relays shown in Fig. 1 during various operating modes of the transport.

what happens in each of the machine's operating modes and how each relay applies the proper voltages to each reeling motor and the solenoid. The "operate" relay (RY1) is energized for all tape-moving modes. This relay determines whether the reel motors are powered by AC (moving) or DC (braking) voltages, and switches on the pressure roller/tape lifter solenoid when the other interlocking relays are de-energized. The rewind relay (RY3) chooses the proper braking differential and reel voltages for rewind, interlocks solenoid power, and activates

the high-rewind braking mode. The forward relay (RY2) selects proper voltages for fast-forward, interlocks solenoid power, and activates the high-forward braking mode.

The logic circuitry

The logic circuits of the 800 transport use six Motorola MC-700P series IC's, ten transistors and eight diodes. Figure 10

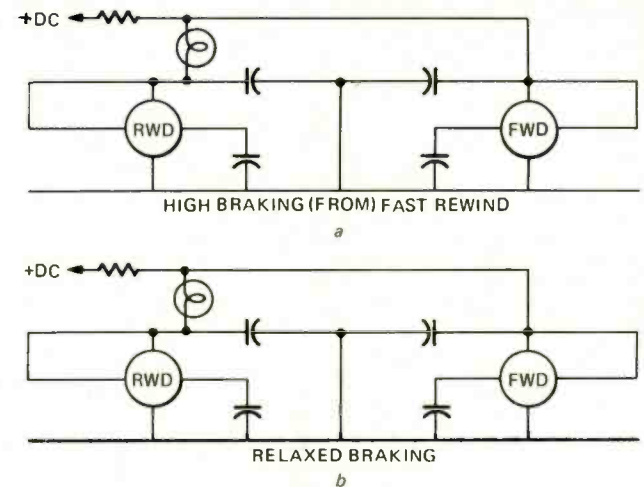


FIG. 9—DURING HIGH BRAKING (a), or relaxed braking (b), the differential voltage between reel motors varies automatically as the resistance of the incandescent lamp changes after a DC voltage has been applied.

is a block diagram of the controlling elements of the machine. The memory section of the computer takes and stores, in three flip-flops (IC5-b, -c; IC5-a, -d and IC6-b, -c), the last command given to it while erasing all previous commands. The stop bus is used to erase previous commands by resetting all three flip-flops to their standby state. Set-reset flip-flops are made of the MC-724P two-input gates by cross coupling their inputs and outputs, as shown in Fig. 11.

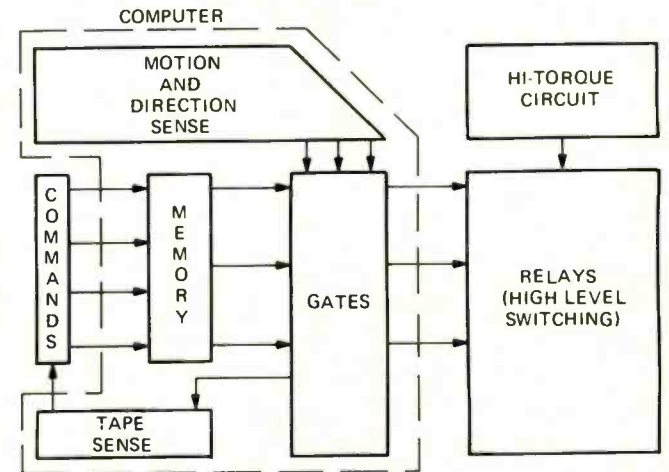


FIG. 10—CONTROLLING ELEMENTS of the Crown 800 tape transport.

The appropriate diode (D17, D18 or D19—Fig. 1), coupled from the play, rewind or forward commands provides a signal to the stop bus for each of these commands. In addition to furnishing the reset signal, the diode also causes the flip-flop to go to the desired state upon removal of the command because the reset command extinguishes before the input command, due to the forward voltage drop of the diode.

The "on" state of the rewind and fast forward flip-flops gives a high voltage output ("1") while the operate flip-flop provides a low voltage ("0") when in the "on" state. For any command other than stop, both flip-flop outputs are an "0". This is because both set and reset inputs of the associated flip-flop are activated—one by the command; the other by the stop bus. Therefore,

(continued on page 93)

4½ digit multimeter to go battery and line operated



\$295.

Model 245 4½ digit DMM offers 21 range versatility, 100% overrange, line and battery operation, (DC/AC volts, ohms, DC/AC amps) .005% resolution with ±.05% basic accuracy for only \$295 including battery module, charger, in-pot probes, carrying case and full documentation.

Truly portable, pocket size
1 3/4" X 3 1/2" X 5 1/2".

Fully protected to 1000 Volts
Data Precision Corporation
Audubon Road, Wakefield, Mass. 01880
(617) 246-1600

DATA PRECISION®
...years ahead

Distributed nationally.
Call your local office
for a demonstration.

- AL (205) 533-5896
- AZ (602) 994-9519
- CA (N) (408) 733-8690
- CA (S) (714) 540-7160
- CO (303) 449-5294
- CT (203) 525-7647
- FL (S) (305) 525-9767
- FL (N) (813) 294-5815
- GA (404) 457-7117
- HI (808) 262-6286
- IL (312) 593-0282
- IN (317) 293-9827
- MA (617) 273-0198
- MD (301) 792-8661
- MI (313) 482-1229
- MN (612) 781-1611
- MO (W) (816) 737-0066
- MO (E) (314) 731-2331
- NC (919) 787-5818
- NJ (S) (215) 925-8711
- NJ (N) (201) 863-5660
- NM (505) 266-6471
- NY (N) (315) 446-0220
- NY (S) (516) 482-3500
- OH (N) (216) 725-4560
- OH (S) (513) 433-8171
- OR (503) 238-0001
- TX (N) (214) 234-4137
- TX (S) (713) 461-4487
- UT (801) 268-3181
- WA (206) 763-2210

- CAN (E) (416) 275-2270
- CAN (E) (514) 695-9787
- CAN (W) (604) 879-9161

Circle 78 on reader service card


BLOCKBUSTER VALUES

FREE \$1 BUY WITH EVERY 10 YOU ORDER
Only applies to "\$1" Buys

FREE GIFT WITH EVERY ORDER

CANADIANS: Ordering is easy—we do the paperwork—try a small order

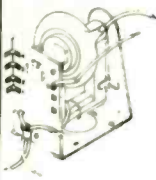RCA 110° FLYBACK TRANSFORMER
We scooped the Market. Latest type standard for all 110° TV's (Blk. & Wht.). RCA's design of large Coil produces 18KV—assuring adequate width incl. Schematic Diagram application for any TV.
List price \$13.90 **395**
Your price **10%** off in lots of 3.



WESTINGHOUSE
ALL TRANSISTOR HOME/OFFICE MESSAGE CENTER
Leaves messages for other for replay . . . Built in speaker/microphone for talk-into convenience . . . Records up to 3 minutes of messages . . . Illuminated signal shows when a message is waiting. Control adjusts playback volume without affecting recording volume . . . Capstan Drive: **795**
BRAND NEW SOLD AS IS

SHANNON MYLAR RECORDING TAPE

3" — 225'	.19	CASSETTE C-60	.59
3 1/4" — 600'	.78	CASSETTE C-90	1.19
5" — 600'	.82	CASSETTE C-120	1.97
5" — 900'	.90	8-Track — 64 Min.	1.29
5" — 1200'	1.49	8-Track — 80 Min.	1.59
5" — 1800'	1.89	8-Track — Cleaner	1.49
7" — 1200'	.97	3" TAPE REEL	.09
7" — 1800'	1.32	3 1/4" TAPE REEL	.12
7" — 2400'	1.99	5" TAPE REEL	.29
7" — 3600'	3.49	7" TAPE REEL	.35

- 6-TRANSISTOR RADIO EARPIECES wires complete with plug **1.00**
- 7-TV ELECTROLYTIC CONDENSERS desirable types **1.00**
- 25—.0033 DISC CERAMIC CAPACITORS C. R. I. **1.00**
- 50-ASST. TERMINAL STRIPS all types, 1-lug to 6-lug **1.00**
- UNIVERSAL 4" PM SPEAKER Top Quality **1.00**
- ZENER DIODE - MOTOROLA HEP 103 1 Watt—6.2 Volts **1.00**
- CAR POWER ADAPTOR 12 Volt In—6V, 7.5V, 9 Volt Out—300MA **4.95**
- 50-ASST. TUBULAR CONDENSERS Popular values **1.00**
- TRANSISTOR RADIO asst type good, bad, broken, as-is, potluck **1.50**
- TAPE RECORDER assorted types good, bad broken, as-is, potluck **4.00**
- 200 ASST. 1/2 W RESISTORS Top Brands, Short Leads, Excellent Selection **1.00**
- 75-ASST 1/4 WATT RESISTORS stand, choice ohmages, some in 5% **1.00**
- 100-ASST 1/2 WATT RESISTORS stand, choice ohmages, some in 5% **1.00**
- 70-ASST 1 WATT RESISTORS stand, choice ohmages, some in 5% **1.00**
- 35-ASST 2 WATT RESISTORS stand, choice ohmages, some in 5% **1.00**
- 50-PRECISION RESISTORS asst. list-price \$50 less 98% **1.00**
- 20-ASSORTED WIREWOUND RESISTORS, 5, 10, 20 watt **1.00**
- 10-ASST SLIDE SWITCHES SPST, SPDT, DPDT, etc. **1.00**
- 25-SYLVANIA HEAT SINKS For Transistors **1.00**
- 20-ASSORTED TV COILS I.F. VIDEO, sound radio, etc. **1.00**
- 1-ELECTROLYTIC COND. 200/300/100/100 MFD—25V **1.00**
- 1-ELECTROLYTIC COND. 100 MFD—300V **1.00**
- 3-ELECTROLYTIC COND. 20/20 MFD—450V **1.00**
- 40-ASST. TUBE CARTONS Most popular types **1.00**
- 2-ELECTROLYTIC Condensers 300 mfd—200V, 300/60 mfd—150V **1.00**
- 4-ELECTROLYTIC COND. 75/30mfd—150V **1.00**
- ELECTROLYTIC CONDENSERS 200/200 mfd.—200V **1.00**
- 2-ELECTROLYTIC COND. 1000 mfd.—25V **1.00**
- 250-ASST SOLDERING LUGS best types and sizes **1.00**
- 250-ASST WOOD SCREWS finest popular selection **1.00**
- 250-Asst Self Tapping SCREWS #8, #8, etc. **1.00**
- 100-ASST 6/32 SCREWS and 100-6/32 HEX NUTS **1.00**
- 100-ASST 8/32 SCREWS and 100-8/32 HEX NUTS **1.00**
- 100-ASST 2/56 SCREWS and 100-2/56 HEX NUTS **1.00**
- 100-ASST 4/40 SCREWS and 100-4/40 HEX NUTS **1.00**
- 100-ASST 5/40 SCREWS and 100-5/40 HEX NUTS **1.00**
- 500-ASSORTED RIVETS most useful selected sizes **1.00**
- 300 ASSORTED WASHERS most useful selected sizes **1.00**
- 100-ASST RUBBER BUMPERS for cabinet bottoms—other uses **1.00**
- 100-ASST RUBBER GROMMETS best sizes **1.00**
- 15-DIPPED MYLAR CAP. .01—600V **1.00**
- 15-DIPPED MYLAR CAP. .033—600V **1.00**
- 15-DIPPED MYLAR CAP. .0033—1000V **1.00**
- 15-DIPPED MYLAR CAP. .047—400V **1.00**
- 15-Molded Tubular Capacitors .056—400V **1.00**
- 15-DIPPED MYLAR Condensers .0039 400V **1.00**

Test Equip. Special Discount Prices

BK TEICO Leader SENCORE

- MERCURY COMPACT TUBE TESTER Model #990 Miniature-sized Specra Saver Full sized in performance **49.95**
- TELMATIC Tuner-Mate KT-730 Portable "Substi-Tuner"—Instant Tuner Check **42.50**
- TELEMATIC Test Jig Model—EJ-190—Master Riggs—Combo Riggs—Econo Riggs **49.95**

KLEPS "CLEVER" TEST PRODS
"Third-hand" test prods. reach into out of way places - insulated - cannot slip - accommodates bare wire or banana plug—no soldering.

- PRUF 10—Versatile Test Probe **89¢**
- KLEPS 10—Boathook Clamp 4 1/4" long **1.99**
- KLEPS 20—Boathook Clamp 7" long **1.49**
- KLEPS 30—flexible-forked Tongue 6" long **1.79**
- KLEPS 40 FLEXIBLE-PC Board Terminals 6 1/4" long **2.59**
- KLEPS 1-ECONOMY Kleps for Light Work **99¢**

- 4 - TV ALIGNMENT TOOLS most useful assortment #1 **1.00**
- 4 - TV ALIGNMENT TOOLS For Color TV #2 **1.49**
- 6 - TV COLOR ALIGNMENT TOOLS Most popular type **2.79**
- TV TWIN LEAD-IN 300 ohm 500'—\$7.100'—\$1.50, 50' CO-AX CABLE RG59U (Black) 250'—\$10, 100'—\$4.50, 50' **2.69**
- 5-DUAL DIODE—MOST POPULAR TYPES Common cathode or Series connected **2.50**
- CONVERGENCE RECTIFIER—For COLOR TV 4 Cell—Used in RCA—Philco, etc. **1.00**
- TV DAMPER DIODE Single—Replace RCA part #120818 Dual—RCA part #135928 **\$2.29 \$3.95**
- COLOR POWER TRANS. —Good for most sets 26R1150 List Price—\$36.75 **6.95**
- 6-Top Brand Silicon RECT. 1 amp., 1000 PIV **1.00**
- 5-PNP TRANSISTOR general purpose, TO-5 case **1.00**
- 5-NPN TRANSISTORS general purpose, TO-5 case **1.00**
- 25-ASSORTED TRANSISTORS big factory scoop—sold as-is **1.00**
- 5-9 VOLT MOTORS Excellent for hobbyist **1.00**
- 2-ELECTROLYTIC CONDENSERS Axial leads—500—25V **1.00**
- ELECTROLYTIC CONDENSER 300 mfd.—200V **1.00**
- 2-ELECTROLYTIC CONDENSERS 80/100/80 MFD—160V **1.00**
- 2-ELECTROLYTIC COND. 200/30/4—mfd—350V **1.00**
- 3-ELECTROLYTIC COND. 100 mfd.—100V, 50 mfd.—75V **1.00**
- 4-ELECTROLYTIC COND. 40 mfd—500V, 40 mfd—400V **1.00**
- 50-ASST. CERAMIC CONDENSERS—Most desirable values **1.00**
- 4-50' HANKS Hook-Up Wire assorted colors **1.00**
- 10-SETS PHONO PLUGS & PIN JACKS RCA type **1.00**
- 8-MINI PILOT BULBS With 8" Leads—8.3V 30MA (5000 Hrs) **1.00**
- 8-MINI PILOT BULBS With 12" Leads—6.3V, 150MA (5000 Hrs.) **1.00**
- 37-TESTY PROD WIRE **1.00**
- DELUXE QUALITY red & black **1.00**
- 10-MINI ELECTROLYTIC Cond For Transistor & miniature work **1.00**

- 110° TV DEFLECTION YOKE for all types TV's incl schematic **4.95**
- "COMBINATION SPECIAL" RCA 110° FLYBACK plus 110° DEFLECTION YOKE **6.95**
- 90° FLYBACK TRANSFORMER for all type TV's (Blk. & Wht.) **2.95**
- 90° TV DEFLECTION YOKE for all type TV's (Blk. & Wht.) **3.95**
- 70° FLYBACK TRANSFORMER for all type TV's (Blk. & Wht.) **2.00**
- 70° TV DEFLECTION YOKE for all type TV's (Blk. & Wht.) **2.00**
- OLYMPIC & SHARP FLY-BACK Part #81T592 Equip. Stancor #HO-408—Thordarson #Fly339 **2.00**
- 90° COLOR YOKE For all Rectangular 19 to 25" Color CRT's **7.95**
- 70 COLORE YOKE For all round color CRT's **8.95**
- DELMONICO NIVICO COLOR FLYBACK Part #A20411-B **7.95**

SARKES TARZIAN TUNER
41mc
Latest Compact Model good for all 41 mc TV's. BRAND NEW —



Best TUNER "SARKES TARZIAN" ever made — last word for stability, definition & smoothness of operation. An opportunity—to improve and bring your TV Receiver up-to-date. **795**
Complete with Tubes

- WESTINGHOUSE FM TUNER #476-V-015D0 1 Transistor **3.99**
- WESTINGHOUSE FM TUNER (12DT8 Tube) **1.00**
- UHF TUNER—Transistor Type Used in all TV sets **3.95**
- G.E. UHF TUNER—TRANSISTOR TYPE Model #85N4 **3.95**
- ADMIRAL TV TUNER Model #94C393-1 (2HA5-4LJ8) Model #T94C41-3 (Transistor) **7.95**
- WELLS GARDNER TUNER Part #7A 120-1 (4GS7-2HA7 Tubes) **7.95**
- G.E.—TV TUNER (2GK5-4LJ8) Model #EP 86x11 **7.95**
- PHILCO UHF/VHF TUNER Transistorized **9.95**
- GE TV TUNER 82T 86x196, (6GK5-6BL8) **5.95**
- UNIVERSAL TV Antenna Back of set mounting, 5 section rods **2.99**
- BLUE LATERAL Magnet Assy. Replacement for most color TV's **1.79**
- 5-10K—2 WATT BIAS POTS Used in solid state application **1.00**
- COLOR CONVERGENCE Assy. Universal type—good for most sets **2.49**
- COLOR-TV RECTIFIER—Used in most color sets—6500 kv 3 for 2 COLOR-TV CRT SOCKETS **1.95**
- Wired leads, for all color TV's **1.00**
- 3-RCA 110° CRT SOCKETS Wired leads, for all TV's **1.00**
- 4-36" Hi-Fi CABLES RCA Molded Phone plug at one end stripped and tinned leads on other end **1.00**
- 3-Polarized CHEATER CORD Brown **1.00**
- 70° COLOR TUBE **3.95**
- BRIGHTNER **1.00**
- 90° COLOR TUBE **4.95**
- BRIGHTNER 2-Colorburst Quartz-Crystal For most color TV sets 3579.545 KC **1.89**
- Popular replacements for most COLOR TV **1.00**
- UHF or VHF Matching Trans. Simple Pool-proof Installation **1.00**


- MARKET SCOOP COLUMN**
- 7 TUBE AM-FM STEREO AMPLIFIER CHASSIS Completely assembled—AS IS needs slight adjustments **22.50**
 - KANDU—Printed Circuit Kit Trace & Etch your own circuits easy to use instructions **9.95**
 - 15-ASSORTED IC'S For Experimenters **1.00**
 - TRANSISTOR RADIO - NEW Excellent value **3.95**
 - Silicon NPN HV TRANSISTOR RCA—SK-3021—Hep-240 RCA—SK-3026—Hep-241 Transistor Specials—Your Choice SK3006, SK3018, SK3020 SK3122, SK3124 **1.00 ea.**
 - Transistor Specials—Your Choice SK3009, SK3024, SK3040 **1.98**
 - TACHOMETER 2 1/4" Sq. Panel Meter 1-VDC, full scale 33 Ohm coil resistance 0-6000 R.P.M. **2.00**
 - 1-CASSETTE type dynamic Mike with universal plugs—200 Ohms VU 1" PANEL METER 0-20 db Scale **2.99**
 - 100' GREY SPEAKER WIRE 2 Cond. mini zip, 101 uses **2.00**
 - WAHL-CORDESS SOLOER IRON Complete with Auto Charger—Fast Heating—Compact **15.95**
 - 5-Audio Output TRANSFORMER Sub-min for Trans Radios **1.00**
 - 5-I.F. Coil TRANSFORMERS 456-ke for Transistor Radios **1.00**
 - 8" UNIVERSAL SPEAKER Top quality Special buy **1.59**
 - 12" UNIVERSA SPEAKER Top Quality Large Magnet **5.89**
 - 10" PHILCO SPEAKER Top Quality Large Magnet **3.95**
 - 8" UNIVERSAL SPEAKER Large Magnet—Special Buy **2.99**
 - 3" UNIVERSAL TWEETER 1 oz. Magnet **1.29**
 - 2 1/2"x4" SPEAKER Special Buy 10 for \$5 **69¢**
 - 4"x6" "QUAM" 16 OHM SPK. Large magnet . . . Special BUZ (10 for \$15.00) **1.79**
 - 8" HEAVY DUTY 10Z. SPEAKER Ceramic Type—8 Ohm 1-6"x9" Heavy Duty 10 oz. Speaker Ceramic Type . . . 8 Ohm (1-5"x7" UNIVERSAL SPK. (10-20-40 OHM Imped.) **4.50**
 - 3 SPEAKER—7 WAY SELECTOR SWITCH Wall Mount STANCOR POWER TRANSFORMER 115V-50—60 Cycle—Pri. Sec. 12.6 Cent. Tap 2 Amp. POWER TRANSFORMER (PT-48)—110V Pri.—12V Sec. Used in many transistor Power supplies **3.29**
 - COMPLETE CONVERGENCE ASSY.—Inc. Yoke, Board & Plug Conn. Adaptable to most 8" sets **3.95**
 - COLOR DELAY LINE—Used in most color sets **1.89**
 - 7-ASSORTED VOLUME CONTROLS with switch **1.00**
 - 10-ASSORTED VOLUME CONTROLS less switch **1.00**
 - 15-ASST. ROTARY SWITCHES All popular types—\$20 value **1.00**
 - DELUXE PILLOW SPEAKERS With plug & volume control **2.49**
 - 2-12BMT RCA TUBES **1.00**
 - 10-ASST DIODE CRYSTALS 1N34, 1N48, 1N60, 1N64, etc. **1.00**
 - TUBE & CONTINUITY CKR. Model FT425 (Tests fuses, heaters, lamps, Etc.) **1.98**
 - VARGO Stereo Cartridge-CN-72 With mounting bracket, flipover needle **2.95**
 - Stereo Headphones HI-FI Quality Complete with Stereo plug **5.95**
 - 10-STANDARD TRANSISTORS NPN & PNP 2N404, 2N414, etc. **1.00**
 - 25' Shielded MIKE CABLE Grey 25/1 **1.89**

IMMEDIATE DELIVERY . . . Scientific light packing for safe delivery at minimum cost. HANDY WAY TO ORDER . . . Send check or money order, add extra for shipping. Lists of new offers will be returned in your order. Please specify refund on shipping overpayment desired: CHECK POSTAGE STAMPS MERCHANDISE (our choice) with advantage to customer


BROOKS RADIO & TV CORP., 487 Columbus Ave., New York, N.Y. 10024 TELEPHONE 212-874 5600

Circle 79 on reader service card

MODE 4

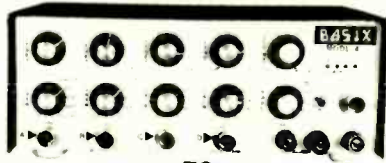

TO

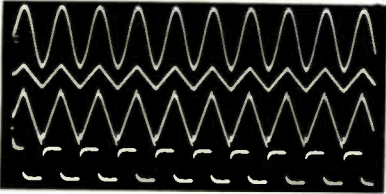

YOUR SCOPE

Lack of multi-channel capability on an otherwise good scope can cost many expensive and frustrating hours when working with modern electronic circuits or servicing complex equipment. Combining the latest in linear and digital semiconductor technology, MODE 4 will permit your unmodified single-channel scope to display up to 4 channels of analog or digital signal — at a fraction of the single-channel scope price.


- Gain (individual channels): x .01 to x 100
In decade steps
- Frequency Response: DC to 10 MHz
- Serial or parallel multiplexing capability
- Z_{in}: 300 K / 20 pf
- Display Modes: From 1 to 4 channels
- V_{in}: 100 v p-p / 100 vdc max.
- Size: 3" H. x 8" W. x 5" D

MODE 4 price \$189.00 including standard I/O cables and test clips [Shielded I/O and min. coax connectors \$10 more.]

BASIX, 1067 Seneca Street, Bethlehem, Pa. 18015

Circle 80 on reader service card

THE MEAN LITTLE KIT

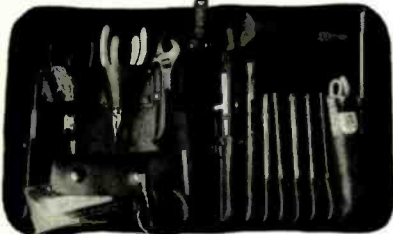

New compact 24-piece kit of electronic tools for engineers, scientists, technicians, students, executives. Includes 7 sizes screwdrivers, adjustable wrench, 2 pair pliers, wire stripper, knife, 2 alignment tools, stainless rule, hex-key set, scissors, 2 flexible files, burnisher, miniature soldering iron, solder aid, coil of solder and desoldering braid. Highest quality padded zipper case, 6 x 9 x 1 3/4" inside. Satisfaction guaranteed. Send check, company purchase order or charge BankAmericard or Mastercharge. We pay the shipping charges.

JTK-6 TOOL KIT.....\$49.00

FREE CATALOG

112 pages of hard-to-find precision tools. Also contains 10 pages of useful "Tool Tips" to aid in tool selection. Send for your free copy today!



JENSEN TOOLS and ALLOYS
4117 N. 44TH STREET, PHOENIX, ARIZONA 85018

Circle 81 on reader service card

DIGITAL CLOCK

(continued from page 35)

Obtaining parts

The liquid-crystal display and the C1200 LSI Computer Systems clock IC are specially designed components, not easily obtained through usual distribution channels. Accordingly, arrangements have been made to supply, by mail, a kit containing these special and other hard-to-get components of the Magiclock to readers of **Radio-Electronics**. The kit includes the etched and drilled printed-circuit board (MGC 48-7), Liquid-Crystal Display (MGC-50), 40-pin connector (MGC-116), C1200 MOS/LSI clock integrated circuit, 28-pin IC socket (MGC-28), and two 51-volt Zener diodes (MGC-51). The Magiclock kit, priced at \$65.00, postpaid, is available from: Inventive Electronics, Box 53 Wykagyl Station, NY 10804.

Other components of the Magi-clock are available locally at any electronics distributor. Do not substitute values for those given, as voltage division is quite critical to proper operation.

Construction

Begin by laying out and soldering-in components other than the IC. Leave this component in its protective foam until everything else has been wired. (Be sure to read the precautions in handling before you attempt to install the IC.)

The use of a PC board makes construction easy. The sockets for the LSI integrated circuit and for the display, as well as all other components (except for D5 and D6) mount flat on top of the PC board, as shown in Fig. 5. Carefully observe the polarities of the six diodes and

to proper operation of the clock.

Checkout

Perform these checks before installing IC1 or the LCD. *Do not install either of these components until everything is checked.*

After connecting the socket, the line cord, the wires to the switches, and all other components, give the PC board a careful visual once-over. Look for cold solder joints and potentially destructive solder or rosin bridges between pads. Protect your investment by making sure that the right resistor is in the right place. (Remember: you can blow the IC in a few microseconds if something's wrong and you don't bother to check.) If everything looks OK, you're ready for the recommended voltage checkout, which *must be done before you install the IC and the LCD in their respective sockets.*


AC voltage checks

Plug the line cord into a 117-volt AC outlet and measure the voltage across R2 and across R3. You should read between 9 and 12 volts AC across each resistor, and the two readings should be about equal. If these voltages aren't right, remove power and check resistors R1, R2, R3, and R4. One or more may be the wrong value or out of tolerance.

Now, plug the line cord in again and measure the voltage across R1 and across R4. Each reading should be not less than 42, nor more than 48 volts AC. If either voltage is out of tolerance, remove power and thoroughly check resistance values in the divider.

DC voltage checks

Measure the voltage from the junction

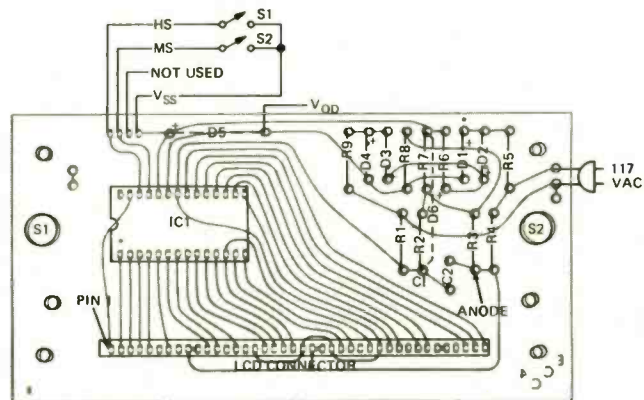

NOTE:
C2 IS NOT ON COMP SIDE
OF BOARD, CONNECTS
FROM IC1 TO ANODE.

FIG. 5—COMPONENT LAYOUT of printed circuit board. An IC socket is used for easy assembly.

note that the two Zeners are soldered in place on the underside of the board. The display socket must be inserted with its part number facing the edge of the PC board so the display can plug in correctly. For S1 and S2, you can use either toggle switches or momentary-contact, normally open, pushbutton switches. For our Magiclock, we used toggle switches that nest neatly into cavities cut in the two wooden cleats, that support the PC board. Switch location is optional and not at all critical

of R2 and R3 noted as point X on the schematic, to the VDD point on the PC board (see Fig. 4) You should read about -28 volts DC. (VDD is negative with respect to X.) Next, measure from the VSS point to X. You should read about +19 volts DC. (VSS is positive with respect to point X.) Now, measure from VDD to VSS. The meter should indicate the sum of the two previous readings (approximately 47 volts DC) with VSS positive with respect to VDD. (Continued page 94)

(continued from page 90)

in the case of the rewind and fast forward flip-flops, where a "1" output is necessary, diode OR gates are used to feed the commands around the flip-flops during the command (reset) interval. Diodes D20, D21, D22 and D23 do this job.

Each of the command inputs to the memory circuit has a capacitor to ground placed across it to protect the input from stray pulses and to assure that there is enough time for proper

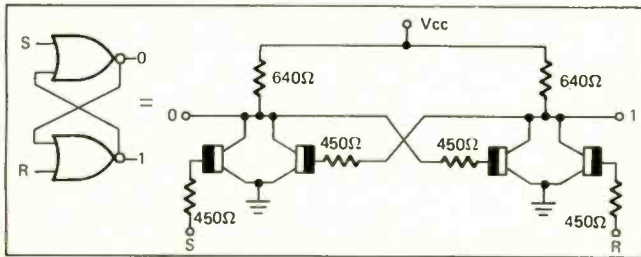


FIG. 11—A PAIR of two-input gates of a Motorola MC-724P IC are cross-connected as shown to form set-reset flip-flops.

setting of the flip-flop after removal of the command. Resistors are also used to shunt any external leakage currents to ground and to hold each input's stray positive pulse immunity at a maximum.

Each of the three high-level switching relays previously discussed is controlled by a transistor (Q13, Q14 or Q15) that in turn is controlled by its associated gating circuit. The 12 IC gates are the heart of the computer's interlocking and coordinating system. Each gate in Fig. 1 is identified by a number. If the gate is on in a given mode, its output is called "0" (low voltage); if off, it is assigned a "1" (high voltage) in Table II.

MACHINE MODE	GATES											
	1	2	3	4	5	6	7	8	9	10	11	12
STANDBY	0s Possibly \bar{x}	0s Possibly x	1	1	1	0p	1	0 ₃	0 ₄	0 ₃	0 ₄	0 ₅
PLAY	0 _{6x}	0 ₆	1	1	0 ₆	1	1	0 ₃	0 ₄	0 ₃	0 ₄	1
REWIND	1	0 _{Rx}	0 _{1R}	1	0 ₅	0 _{p8}	0 ₈	1	0 ₄	1	0 ₄	1
FORWARD	0 _{Fx}	1	1	0 _{2F}	0 _F	0 _{p9}	0 ₉	0 ₃	1	0 ₃	1	1
REWIND BRAKES	1	0 _x	0 ₁	1	1	0 _{p8}	0 ₈	1	0 ₄	1	0 ₄	0 ₅
FORWARD BRAKES	0 _x	1	1	0 ₂	1	0 _{p9}	0 ₉	0 ₃	1	0 ₃	1	0 ₅
RWD & FWD (Jockeying)	0 _F Possibly \bar{x} and/or s	0 _R Possibly x and/or s	0 _R	0 _F	0 _{Rf}	0 _{p89}	0 ₈₉	1	1	1	1	1

TABLE II—On or off state of each of the twelve logic gates is tabulated for the various operating modes of the Crown 800 transport.

Whenever a gate output is "0", the set of numbers or letters following the "0" indicate which gate or control sources had supplied the necessary "1" output to its input to cause it to be "0". The letters of the control sources used in the table correspond to:

- R=Rewind flip-flop in the memory circuit (1 = RWD)
- F=Forward flip-flop in the memory circuit (1 = FWD)
- P=Play flip-flop in the memory circuit (0 = FWD)
- X=Direction sense circuitry (1 = RWD, 0 = FWD)
- X=Direction sense circuitry (1 = FWD, 0 = RWD)
- S=Motion Sense circuitry (1 = stop, 0 = Motion)


Because the last direction of machine motion is not unique in the standby or jockeying (fast forward followed quickly by fast rewind) states, gates 1 and 2 have X or \bar{X} possible. Also, since there may not be any motion at all during jockeying, S is possible during this mode.

What does it all mean?

Clearly, modern electronic techniques, and particularly those from the world of digital electronics, play a vital part in the operation and performance of a top-performing tape transport such as Crown's 800.

R-E

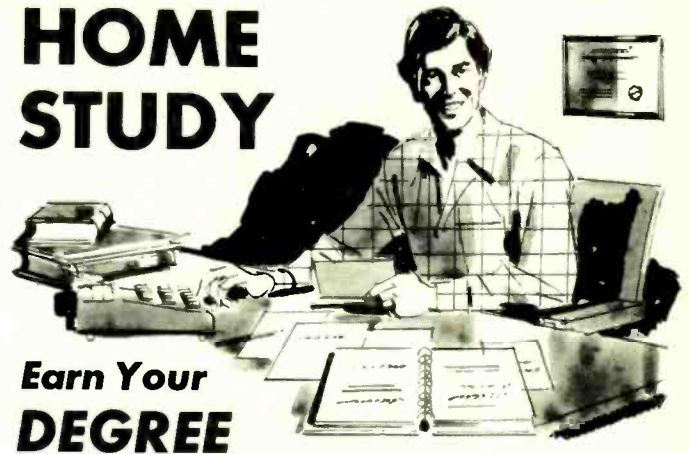Put Professional Knowledge and a COLLEGE DEGREE in your Electronics Career through HOME STUDY



Earn Your DEGREE

by correspondence, while continuing your present job. No commuting to class. Study at your own pace. Learn from complete and explicit lesson materials, with additional assistance from our home study instructors. Advance as fast as you wish, but take all the time you need to master each topic. Profit from, and enjoy, the advantages of independent study.

The Grantham correspondence degree program in electronics is comprehensive. It begins with basics, written in very simple language, and continues through the B. S. E. E. degree level. Throughout the entire program, heavy emphasis is placed on clear explanations written in great detail, progressing from the simple to the complex, in easy steps.

Our free bulletin gives complete details on the curriculum, the degrees awarded, the requirements for each degree, and how to enroll.

GRANTHAM SCHOOL OF ENGINEERING

2000 Stoner Ave., Los Angeles CA 90025

● Telephone (213) 477-1901 ●

Worldwide Career Training thru Home Study

Mail the coupon below for free bulletin.

Grantham School of Engineering RE 8-75
2000 Stoner Ave., Los Angeles, CA 90025

I have been in electronics for _____ years. Please mail me your free bulletin which gives details concerning your electronics degree programs.

Name _____ Age _____

Address _____

City _____ State _____ Zip _____

Circle 82 on reader service card

**We carry
B&K, EICO,
RCA,
SENCORE,
FLUKE,
HICKOK and
LEADER.**

**We sell them
at *% off.**

*Our prices are so low the manufacturers forbid us to advertise them. Write and find out how much you can save

Complete line of tubes,
tools and electronic supplies

**FREE CATALOG
FORDHAM**

RADIO SUPPLY CO., INC.

558 Morris Ave., Bronx, N.Y. 10451
Tel: (212) 585-0330

Circle 83 on reader service card

MACHINE LANGUAGE PROGRAMMING

for the
8008

(and SIMILAR MICROCOMPUTERS)

Written to provide you with the detailed knowledge you need to know in order to successfully develop your own MACHINE LANGUAGE PROGRAMS! This information packed publication discusses and provides numerous examples of algorithms and routines that can be immediately applied to practical problems. Coverage includes:

DETAILED PRESENTATION OF THE '8008' INSTRUCTION SET • FLOW CHARTING • MAPPING • EDITING AND ASSEMBLING • DEBUGGING TIPS • FUNDAMENTAL PROGRAMMING TECHNIQUES: LOOPS, COUNTERS, POINTERS, MASKS • ORGANIZING TABLES • SEARCH AND SORT ROUTINES • MATHEMATICAL OPERATIONS • MULTIPLE-PRECISION ARITHMETIC • FLOATING-POINT PACKAGE • MAXIMIZING MEMORY UTILIZATION • I/O PROGRAMMING • REAL-TIME PROGRAMMING • PROGRAMMING FOR "PROMS" • CREATIVE PROGRAMMING CONCEPTS.

Virtually all techniques and routines illustrated also applicable to '8080' and similar types of micro/minicomputers, with appropriate machine code substitution. Orders now being accepted for immediate delivery at the LOW price of just \$19.95.* Add \$3.00 if PRIORITY mailing service desired. (*Domestic prices.) Order direct from—

SCELBI COMPUTER CONSULTING, INC.

1322 REAR • BOSTON POST ROAD
MILFORD, CONNECTICUT 06460

MASTER CHARGE ACCEPTED. MASTER CHARGE customers must submit Card #, Bank #, Expiration Date, and card holder's personal signature.

DON'T DELAY—ORDER TODAY!

DIGITAL CLOCK

(continued from page 92)

Finally, measure the voltage drop across R6. The reading should be at least 8 volts, DC, but not more than 9 volts, DC.

If any reading is not in tolerance, carefully check each resistor value and replace any that are out of spec.

Installing the liquid crystal display

Disconnect the AC plug and carefully insert the LCD panel into its socket. Line it up so that contact areas on the lower edge of the glass are exactly opposite the spring contacts of the socket. In this way, you make sure that when the display is firmly seated, all socket contacts will properly mate with the LCD's connector edge. *Don't insert the IC yet.*

Plug in the AC line cord. If the LCD is properly inserted, the colon will appear on the display. If it doesn't, the LCD is not making proper contact. Reinsert the LCD or move it slightly to one side or the other, until the colon lights. Now pull out the AC plug again.

Installing the LSI clock chip

Having come this far, you are within minutes of seeing your Magi-clock in operation. Don't rush things now! Read and heed the next paragraph's precautions as you prepare to install IC1.

Any MOS IC device must be handled carefully, for it can be damaged by high-

removing the IC from its protective foam, touch a grounded object to discharge any body capacitance charge. *Never, never, never attempt to insert or remove the MOS IC while power is on.* If you need to resolder a connection after the IC is plugged-in, run a ground wire to the iron's tip to drain away destructive charges. Follow these precautionary steps and your IC is sure to survive.

After pulling out the power line plug, wait a few seconds for filter capacitor C1 to dissipate its charge through R6, R7 and R8. Now insert the integrated circuit into its socket. *Be sure to plug it in correctly as shown in Fig. 5.* If you insert the socket incorrectly, you'll damage it the instant power is applied—so, do it right the first time.

Connect the AC line cord. A random number display will appear on the LCD. It may even flash at a 1-Hz rate. Now, you're ready to set the time and that is very simple.

Setting time and using your clock

Close the MINUTE SET switch and you will see the minutes change rapidly—two minutes each second. As the correct minute digit appears, open the switch. The hour digits are set the same way with the HOUR SET switch and that is all there is to it!

The clock can be set precisely from the time signal sent over the radio or telephone. Close the HOUR SET and MINUTE SET switches at the same time. Release them both at the instant the time signal is heard. Then set the minutes and hours independently to the correct time as before. The clock is now accurately synchronized to the time tone.

For elapsed time indication close both switches and release them simultaneously. The display will start from 0:00 and count elapsed time in one minute steps.


If there has been a power interruption (as is theoretically the case when the clock is first plugged in) the entire display may flash at a 1-Hz rate signalling that the time displayed is not correct. When either time set switch is activated, the display will stop flashing.

If you plug in the clock immediately after bringing it indoors on a very cold day, the display may not read correctly—one or more "extra" segments may light up. This happens because of condensation between the IC or LCD sockets' closely spaced "lands" on the PC board, or moisture between the contact areas on the LCD itself. Normal drying in warm room air should alleviate the problem. Plug in the clock and let it operate for 15 to 30 minutes to restore normal operation.

Back-lighting the display

If you add a small fluorescent or incandescent light source *behind* the LCD the visibility of the large time numerals will improve. The light should be mounted out of direct line of sight, so as to cast light on the display, without the light-source itself being visible through the LCD panel. An angle-mounted plane mirror is a good choice for reflecting light onto the display. Choose one about the same width as the LCD panel and about half its height. Alternatively, aluminum foil can be used as a flexible, easily worked reflector. R-E

PIN CONNECTIONS C1200

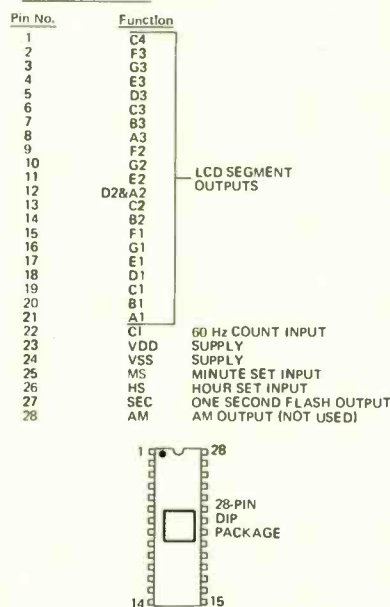

PIN FUNCTION and pin identification for the C1200 clock chip from LSI Computer Systems.

voltage static charges produced by casual, ordinary handling. For this reason, it is shipped with all of its pins pressed into a piece of conducting foam rubber, where it should remain until you're ready to plug it into the socket on the PC board. Don't handle the device immediately after you walk across a dry rug with rubber-soled shoes, comb your hair or put on a nylon sweater, for you can easily build up static charges of several thousand volts and unwittingly ZAP the IC. Before

next month

SEPTEMBER 1975

■ Build This Electronic Doorbell

IC project uses a PROM to "record" up to 32 musical notes. Two circuit boards make the unit easy to build and you program the particular music you want your unit to play.

■ Installing TV-MATV Antennas

Put antenna theory to practical use to solve reception problems when you put up that next TV-MATV antenna system.

■ All About Oscilloscopes

Part IV: The final section of this article describes many interesting oscilloscope applications. Bet you'll find at least one you've never seen before.

■ Hi-Fi Lab Test Reports

Two more new reports on some of the latest hi-fi gear around.

■ Signal-To-Noise—What does it mean?

If you have always wondered what signal-to-noise ratio is and how it affects hi-fi sound, don't miss this article by Len Feldman, R-E's Contributing High-Fidelity Editor.

PLUS

Jack Darr's Service Clinic

Step-By-Step Troubleshooting Charts

State-Of-Solid-State

Radio-Electronics' Replacement
Japanese Transistor Directory


CALECTRO® DIGITAL DISPLAYS AND LOGIC

ATTENTION HOBBYISTS!

BUILD THIS DIGITAL COUNTER/ L.E.D. DISPLAY KIT.



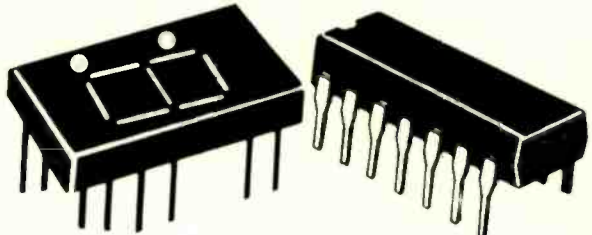Everything needed to build a complete decade counter (0-9) including a printed circuit board. Operates from a 5 Volt D.C. supply. Can be used in hundreds of applications.



See your nearby CALECTRO distributor for all the most popular digital displays and integrated circuits. Also, get your copy of the new CALECTRO DIGITAL PROJECTS HANDBOOK!



GC ELECTRONICS

DIVISION OF HYDROMETALS, INC.
ROCKFORD, ILLINOIS 61101 U.S.A.

Polaris

40 KV

DUAL RANGE

Probe

Current & Voltage Reading
For Today...
And Tomorrow!

MODEL \$29⁹⁵
651

RANGE NO. 1: 40,000 VOLTS DC
RANGE NO. 2: 0-400 MA DC

Send literature and name of my distributor.

Polaris New York
2862 FULTON STREET
BROOKLYN, N.Y. 11207

Name _____
Address _____
City _____ State _____
Zip _____

Circle 84 on reader service card

MOVING?

Don't miss a single copy of **Radio-Electronics**. Give us:

Six weeks' notice

Your old address and zip code

Your new address and zip code

ATTACH LABEL HERE

name (please print)

address

city state zip code

Mail to: Radio-Electronics
SUBSCRIPTION DEPT., BOULDER, COLO.
80302

service questions

NO SYNC'S

This was one of mine. "Friend" (?) brought in large Quasar TS-938. Says "I've changed all the boards that would have anything to do with it, and I've still got problems!". It looked as if there was no horizontal or vertical sync. So, we drove it into the shop. "Up scope!".

I found plenty of horizontal sync on Q5, the sync separator; also at the output of the sync amplifier. However, it was jittering badly. The video signal to the sync separator was also jittering. The scope showed an odd glitch on the horizontal sync. However, the oscillator itself was apparently in good condition. The picture never fell into slanting lines, just floated back and forth.

I saw what seemed to be enough horizontal sync at the output terminal on the sync panel, so let's see if it is getting to the horizontal-output panel. Tracing this through the cabling, I pulled the output panel. Oh, oh! One of the numerous contact pins in the vertical array on the left side was *pushed back* at least half an inch. Tilting the panel, my little flashlight showed that the contact this was supposed to make was plainly labelled HOR SYNC INPUT! A little tricky work with a pair of long-noses pushed the pin back in line with the rest. Putting the board carefully back, the trouble was over! Evidently this pin had been slightly bent, and when the board was replaced, it got pushed back far enough so that it wasn't making contact at all. The jitter of the video signal was probably due to the upsetting of the AGC.

ELECTRIC FENCE

My solid-state electric fence charger went out. I found an open electrolytic capacitor; the one that discharges to produce the shock. It's a 100-mF 150 volt type. I replaced it with a 150-mF 200-volt type. Is this OK? Seems to work about the same as it did.—B.R., Temple, TX.

I'd buy that any day. You can never go wrong by choosing a replacement capacitor with a higher voltage rating than the original. In most applications, you can generally use a larger capacitance than the original. Just don't use a smaller one or one with a lower voltage rating.

R-E

312 FASCINATING PAGES!

A FLICK OF THE SWITCH

new 1930-1950 book

- Re-live the great days of radio broadcast and the beginnings of TV-electronics.
- Browse through 1,000 pictures and interesting old ads.
- Discover the rewards of radio collecting and restoration.
- Own a First Edition of this valuable reference book.

This new book includes broadcasting, home radio-TV, Amateur radio, World War II radio-electronics, the radioman, collecting and "how it works." \$9.95 hard-cover, \$6.95 handbook.

Other valuable books are Vintage Radio (1887-1929) \$7.95 hard-cover, \$5.95 handbook; Radio Collector's Guide (1921-1932) \$4.95; 1927 Radio Encyclopedia \$12.95 hard-cover, \$9.95 soft-cover; 1926-1938 Radio Diagrams, \$7.00. Also, we'll furnish any pre-1951 diagram for \$3.50. 10-day return privileges.

Send today to Vintage Radio, Dep't R, Box 2045, Palos Verdes Peninsula, CA., 90274. Postage paid. Cal. residents add 6% tax.

_____ \$ _____
 _____ \$ _____
 _____ \$ _____
 TOTAL _____

Name _____
 Address _____
 City _____ St. _____ Zip _____

FREE Radio Age Guide with each order FREE

NEW VINTAGE RADIO BOOK

For
faster
service

USE
ZIP
CODE

on
all
mail

Market Center

CLASSIFIED COMMERCIAL RATE (for firms or individuals offering commercial products or services). \$1.40 per word . . . minimum 15 words.

NONCOMMERCIAL RATE (for individuals who want to buy or sell personal items) 85¢ per word . . . no minimum.

ONLY FIRST WORD AND NAME set in bold caps. Additional bold face (not available as all caps) at 10¢ per word. Payment must accompany all ads except those placed by accredited advertising agencies. 10% discount on 12 consecutive insertions, if paid in advance. All copy subject to publisher's approval. Advertisements using P.O. Box address will not be accepted until advertiser supplies publisher with permanent address and phone number. Copy to be in our hands on the 26th of the third month preceding the date of the issue (i.e. August issue closes May 26). When normal closing date falls on Saturday, Sunday or a holiday, issue closes on preceding working day.

BUSINESS OPPORTUNITIES

TV Sales & Service, established 23 years. Annual Gross: \$24,000.00. Free with purchase of prime property in heart of Pasadena. Beautiful climate. Reasonable. Owner retiring. P. O. BOX 4162, Pasadena, CA 91106

OWN YOUR OWN PICTURE TUBE REBUILDING BUSINESS
With Lakeside Industries re-building equipment you can rebuild any picture tube!

For complete details send name, address, zip code to
LAKESIDE INDUSTRIES
3520 W. Fullerton Ave.
Chicago, Ill. 60647
Phone: 312-342-3399



PLANS & KITS

FREE catalog. Most unusual electronic kits available. Music accessories, surf, wind synthesizers, wind chimes, many others. **PAIA ELECTRONICS**, Box B14359, Oklahoma City, OK 73114

CIRCUIT collections: 20 useful circuits you can build. Includes schematics, parts list, description. \$3.98. **RJE COMPANY**, 28 Park Street, Jamestown, NY 14701

F.C.C. EXAM MANUAL

PASS FCC EXAMS! Memorize, study—Tests—Answers for FCC 1st and 2nd class Radio-telephone licenses. Newly revised multiple choice questions and diagrams cover all areas tested in FCC exams, plus Self-Study Ability Test. \$9.95 postpaid. Money-back guarantee.



COMMAND PRODUCTIONS P.O. Box 26388 E
RADIO ENGINEERING DIV. SAN FRANCISCO, CAL. 94126

UNIVERSAL TTL/DTL CMOS IC tester; 100,000 test operations in 0.66 seconds. Will test 16/14 pin digital IC's. Circuit is easy to understand and build. IC's needed cost less than \$20.00; all are TTL. Plans \$1.35, **NORTHSTAR ENGINEERING**, 3617 North Crede Drive, Charleston, WV 25302

CONVERT any television to sensitive, big-screen oscilloscope. Only minor changes required. No electronic experience necessary. Illustrated plans \$2.00. **SANDERS**, Dept. A-25, Box 92102, Houston, TX 77010

BUILD that electronic organ you always wanted at a price you can afford. Third edition of "Organ Builder's Guide", pictured product kit line, circuits, block diagrams, design rationale using IC divider and independent generators with diode keying. \$3.00 Postpaid. Also, free brochure on keyboards. **DEVTRONX ORGAN PRODUCTS**, Dept. B, 5872 Amapola Drive, San Jose, CA 95129

UNUSUAL digital plans for games, test equipment, others. Free info. T. WONG, 103 E. Broadway, Dept. 4A, New York, NY 10002

EDUCATION & INSTRUCTION

LEARN design techniques. Electronics design Newsletter. Digital, linear construction projects, design theory and procedures. Annual subscription \$6.00, sample copy \$1.00. **VALLEY WEST**, Box 2119-A, Sunnyvale, CA 94087

FREE educational electronics catalog. Home study courses. Write to: **EDUKITS WORKSHOP**, Dept. 270G, Hewlett, NY 11557

WANTED

QUICK cash for your used Altair 8800, TV Typewriter, interfaces, software, etc. Contact us for service, parts, and free applications information. **ALCOVE**, 230 Main, North Reading, MA 01864, (617) 664-4271

QUICK cash . . . for electronic equipment, components, unused tubes. Send list now! **BARRY**, 512 Broadway, New York, NY 10012, 212 Walker 5-7000

WANTED qualified, experienced electronics instructor to prepare correspondence lessons on radio, transistor TV, color TV. Instructor can do the job right at his home. Apply by Air-mail. State remuneration required. **UNIVERSAL RADIO INSTITUTE**, P.O. Box 42, Owen Road, Singapore, 8.

ELECTRONIC ENGINEERING & INSTRUCTION

SELF-STUDY CB radio repair course. There's money to be made repairing CB radios. This easy-to-learn course can prepare you for a career in electronics enabling you to earn as much as \$16.00 an hour in your spare time. For more information write: **CB RADIO REPAIR COURSE**, Dept. RE-075, 531 North Ann Arbor, Oklahoma City, OK 73127

FOR SALE

ELECTRONIC Ignition: Capacitor, transistor, pointless. Auburn sparkplugs. Information 10¢. **ANDERSON ENGINEERING**, Epsom, NH 03234

ELECTRONIC Components: Premium grade at minimum cost. Wide selections purchased from liquidating companies. Send 25¢ to **CLOSEOUT BULLETIN**, 340 Vivian St., Longmont, CO 80501

LOW-noise resistors—1/4W, 5%, carbon film from 10-3.3 megohms for 3 1/2¢ each. Fifty of one value for \$1.25. 1N4148 diodes for 6¢. 75¢ postage. Free samples/specifications. **COMPONENTS CENTER—RE**, Box 134, New York, NY 10038

QUALITY ELECTRONIC COMPONENTS — SAME DAY SERVICE —

NEW DISCOUNT SCHEDULE SAVES YOU EVEN MORE!

1024 BIT STATIC MOS RAM

2102 . . . \$3.50

INTEGRATED CIRCUITS — TTL, CMOS, LINEAR & MOS

7400N	24c	7453N	22c	74153M	.77c	40194A	.58c	4518AE	\$1.28
7401A	24c	7454A	22c	74156A	.77c	4020AE	\$1.67	4520AE	\$1.28
7402N	24c	7460N	22c	74157N	.68c	4021AE	\$1.50	4527AE	\$2.36
7403N	24c	7470N	34c	74169N	\$1.19	4022AE	\$1.25	4528AE	\$1.94
7404A	24c	7472N	34c	74181A	\$1.11	4023AE	.79c	4534DL	\$2.08
7405A	24c	7473A	34c	74182A	\$1.19	4024AE	.79c	4535AE	\$1.87
7406A	24c	7474A	31c	74183A	\$1.19	4025AE	.79c	4536AE	\$1.87
7407N	24c	7475N	51c	74164A	\$1.28	4026AE	\$1.67	4535SV	.66c
7408N	24c	7480A	34c	74165A	\$1.09	4027AE	.65c	4536AE	.86c
7409N	24c	7480M	.68c	74159A	\$1.07	4028AE	\$1.09	4536B	\$3.83
7410N	24c	7482N	.68c	74180N	.77c	4029AE	\$1.42	4536B	\$3.83
7411A	24c	7483N	.68c	74181N	\$2.13	4030AE	.79c	4536B	\$3.83
7412N	24c	7485A	\$1.11	74182N	.85c	4031AE	\$1.67	4536A	\$1.45
7413N	24c	7486A	.61c	74190A	.79c	4032AE	\$3.34	4536B	\$1.45
7414A	\$1.02	7489N	\$2.13	74191A	\$1.45	4033AE	\$1.42	4536N	\$1.36
7416A	24c	7490N	.68c	74192N	\$1.10	4034A	\$1.67	4536CA	.42c
7417N	24c	7491N	.77c	74193N	\$1.11	4034AE	.92c	4536CA	.28c
7420N	24c	7492N	.65c	74194A	\$1.11	4034E	.84c	4537CA	.37c
7421N	24c	7493A	.68c	74195A	\$1.11	4034E	.67c	4537CA	.60c
7422N	24c	7494A	.65c	74196A	.77c	4034E	.67c	4537CA	.60c
7426A	24c	7495N	.85c	4000AF	.79c	4040AE	\$1.51	4537CA	.68c
7428N	.63c	7496N	.77c	4000AE	.79c	4040AE	\$1.51	4537CA	.68c
7429N	.31c	74102A	.64c	4002AE	.79c	4040AE	\$1.51	4537CA	.68c
7437N	24c	74107N	.31c	4006AE	\$1.50	4051AE	\$1.50	1129	\$1.25
7438N	24c	74108A	.34c	4007AE	.34c	4052AE	\$1.50	1130	\$1.25
7440N	24c	74129A	.43c	4008AE	\$1.17	4053AE	\$1.50	1131	\$1.25
7441N	\$1.11	74130A	.78c	4009AE	.67c	4064AE	\$1.67	1209N	\$1.00
7442N	24c	74131A	.61c	4010AE	.67c	4064AE	\$1.67	1209N	\$1.00
7443N	.61c	74132A	.73c	4011AE	.79c	4071AE	.30c	4536CA	\$1.25
7444N	.61c	74133A	.73c	4012AE	.79c	4072AE	.30c	4536CA	\$1.25
7445N	.77c	74134A	.94c	4013AE	.61c	4073AE	.30c	4536CA	\$1.25
7446N	.77c	74135A	\$1.16	4014AE	\$1.67	4074AE	.30c	4536CA	\$1.25
7447N	.77c	74136A	\$1.36	4015AE	\$1.37	4081AE	.30c	4536CA	\$1.25
7448N	.77c	74137A	.85c	4016AE	\$1.34	4082AE	.30c	4536CA	\$1.25
7449N	.77c	74138A	.85c	4017AE	\$1.34	4083AE	\$1.38	4536CA	\$1.25
7450N	.77c	74139A	\$1.36	4018AE	\$1.67	4511AE	\$1.70	7107	\$3.50

SILICON TRANSISTORS

EN918	21c	10/51.00	1C/517.85	2N3640	21c	10/52.00	1C/517.85
EN930	16c	10/51.55	1C/513.60	2N3641	16c	10/51.55	1C/513.60
MP5900	16c	10/51.55	1C/513.60	2N3643	16c	10/51.55	1C/513.60
MP2922	16c	10/51.55	1C/513.60	2N3645	16c	10/51.55	1C/513.60
MP2222A	16c	10/51.55	1C/513.60	2N3645	21c	10/52.00	1C/517.85
EN2369A	16c	10/51.55	1C/513.60	2N3646	21c	10/52.00	1C/517.85
MP5399A	16c	10/51.55	1C/513.60	2N3904	16c	10/51.55	1C/513.60
MP5717	16c	10/51.55	1C/513.60	2N3904	16c	10/51.55	1C/513.60
EN2907	16c	10/51.55	1C/513.60	2N4124	16c	10/51.55	1C/513.60
MP52907A	16c	10/51.55	1C/513.60	2N4126	16c	10/51.55	1C/513.60
2N3911A	21c	10/52.00	1C/517.85	2N4401	16c	10/51.55	1C/513.60
2N3927	16c	10/51.55	1C/513.60	2N4443	16c	10/51.55	1C/513.60
MP5392	16c	10/51.55	1C/513.60	2N5007	16c	10/51.55	1C/513.60
2N3393	16c	10/51.55	1C/513.60	2N5089	16c	10/51.55	1C/513.60
MP5393	16c	10/51.55	1C/513.60	2N5129	21c	10/52.00	1C/517.85
1N4017	16c	10/51.55	1C/513.60	2N5926	16c	10/51.55	1C/513.60
MP5394	16c	10/51.55	1C/513.60	2N5134	21c	10/52.00	1C/517.85
MP5395	16c	10/51.55	1C/513.60	2N5137	21c	10/52.00	1C/517.85
2N3653	21c	10/52.00	1C/517.85	2N5138	21c	10/52.00	1C/517.85
2N3655	21c	10/52.00	1C/517.85	2N5139	21c	10/52.00	1C/517.85
2N3638	16c	10/51.55	1C/513.60	2N5210	16c	10/51.55	1C/513.60
2N3638A	16c	10/51.55	1C/513.60	2N5457	52c	10/54.88	1C/544.20
MP5363BA	16c	10/51.55	1C/513.60	2N5457	52c	10/54.88	1C/544.20
				MP5-A13	80c	10/53.75	1C/534.00

ELECTROLYTIC CAPACITORS

Radial Lead			Axial Lead				
1uF/50V	8c	10/46c	1C/5 5.41	10uF/50V	14c	10/51.13	1C/5 9.56
2.2uF/50V	8c	10/46c	1C/5 5.41	22uF/16V	12c	10/96c	1C/5 8.31
3.3uF/50V	8c	10/46c	1C/5 5.41	33uF/16V	12c	10/96c	1C/5 8.31
4.7uF/50V	8c	10/46c	1C/5 5.41	33uF/25V	12c	10/101.13	1C/5 8.48
10uF/25V	8c	10/67c	1C/5 5.66	33uF/25V	14c	10/113.13	1C/5 9.56
10uF/50V	10c	10/77c	1C/5 5.66	47uF/16V	14c	10/113.13	1C/5 9.56
3.3uF/50V	9c	10/72c	1C/5 6.09	47uF/25V	12c	10/93.13	1C/5 8.74
22uF/50V	12c	10/11.00	1C/5 8.48	100uF/16V	17c	10/51.32	1C/5 11.22
100uF/6.3V	9c	10/74c	1C/5 6.32	100uF/25V	20c	10/51.57	1C/5 11.30
100uF/16V	11c	10/86c	1C/5 7.28	100uF/50V	29c	10/57.32	1C/5 11.70
100uF/25V	13c	10/110.08	1C/5 9.15	220uF/16V	29c	10/57.32	1C/5 11.70
Axial Lead			Axial Lead				
1uF/50V	11c	10/90c	1C/5 7.65	330uF/16V	29c	10/52.35	1C/5 11.96
2.2uF/50V	12c	10/92c	1C/5 7.82	330uF/25V	32c	10/57.34	1C/5 12.67
470pF/500V	4c	10/36c	2C/5 6.09	470uF/16V	32c	10/57.34	1C/5 12.67
1000pF/500V	4c	10/37c	2C/5 6.22	470uF/25V	37c	10/52.98	1C/5 12.25
2200pF/500V	4c	10/37c	2C/5 6.22	6.32 1/4 Screw	.99c	C	\$ 7.30/M
4700pF/500V	4c	10/32c	2C/5 5.41	6.32 1/2 Screw	.88c	C	\$ 7.00/M
61uF/500V	6c	10/54c	2C/5 5.55	6.32 3/8 Screw	\$1.05c	C	\$ 8.40/M
.01uF/50V	3c	10/24c	2C/5 8.05	8.32 5/8 Screw	\$1.05c	C	\$ 8.00/M
.022uF/25V	3c	10/28c	2C/5 7.43	2.56 Hex Nut	\$1.35c	C	\$10.80/M
.047uF/25V	5c	10/42c	2C/5 7.17	4.40 Hex Nut	\$1.45c	C	\$11.60/M
1uF/25V	8c	10/62c	2C/5 10.57	6.32 Hex Nut	\$1.45c	C	\$11.70/M
				8.32 Hex Nut	\$1.50c	C	\$11.80/M
				No. 2 Lock Washer	.45c	C	\$ 3.50/M
				No. 4 Lock Washer	.45c	C	\$ 3.50/M
				No. 6 Lock Washer	.45c	C	\$ 3.50/M

DISC CAPS

100pF/500V	4c	10/36c	2C/5 6.09	2.56 1/4 Screw	.90c	C	\$ 7.20/M
220pF/500V	4c	10/36c	2C/5 6.09	2.56 1/2 Screw	.96c	C	\$ 7.80/M
470pF/500V	4c	10/36c	2C/5 6.09	4.40 1/4 Screw	.96c	C	\$ 7.80/M
1000pF/500V	4c	10/37c	2C/5 6.22	4.40 1/2 Screw	.96c	C	\$ 7.80/M
2200pF/500V	4c	10/37c	2C/5 6.22	6.32 1/4 Screw	.99c	C	\$ 7.30/M
4700pF/500V	4c	10/32c	2C/5 5.41	6.32 1/2 Screw	.88c	C	\$ 7.00/M
61uF/500V	6c	10/54c	2C/5 5.55	6.32 3/8 Screw	\$1.05c	C	\$ 8.40/M
.01uF/50V	3c						

FOR SALE

MANUALS for Govt. surplus radios, test sets, scopes, List 50¢ (coir). BOOKS, 7218 Roanoke Drive, Washington, DC 20021

PRINTED CIRCUIT

PHOTO ETCH KITS; DATA PRODUCTS; TAPE RESIST; ALPHA NUMERIC COMPONENT DESIGNATIONS; ARTWORK; CARBIDE DRILL BITS; BUBBLE ETCHERS SEND S.A.S.E. FOR FLYER TRUMBULL 833 BALRA DR., EL CERRITO, CA 94530

BURGLAR alarm dialing unit automatically calls police. \$29.95. Free literature. S&S SUPPLY, Box 12375G, North Kansas City, MO 64116

TV transmitter. RCA TT-2AH. Excellent condition. Reasonable. P. O. BOX 4162, Pasadena, CA 91106

FREE catalog. IC's, Semi's. CORONET ELECTRONICS, 649A Notre Dame W., Montreal, Que. Canada, H3C-1H8. US Inquiries

RADIO & TV tubes 36¢ each. One year guaranteed. Plus many unusual electronic bargains. Free catalog. CORNELL, 4217-E University, San Diego, CA 92105



MINIATURE TRANSMITTER WIRELESS MICROPHONE

Among world's smallest. Improved solid state design. Picks up and transmits most sounds without wires thru FM radio up to 300 ft. Use as mike, music amp., baby sitter, burglar alarm, hot line, etc. For fun, home and business. Batt. incl. Money back guar. B/A, M/C cds. COD ok. Only \$14.95 plus 50¢ Post and hdg. AMC SALES, Dept. 19, Box 928, Downey, Ca. 90241.

Size 2-1/4 x 3/4 x 1/2"

CANADIAN discount and factory clearouts catalog. Top brand stereo equipment, calculators, test gear, CB & communications, telephones. Factory dumps—government surplus. Amazing bargains. Unusual items. Rush \$1. ETCO-RE, 521 5th Ave., NYC, 10017

MEMORY SYSTEM \$125.00

1024 core memory system, 1024 words memory, 8, 9, or 10 bits/word. Random access, with all logic, register, timing, control, core select and sense functions in one package. New, with 60 page booklet includes schematics. Measures only 9x4x1 inches. Good start for mini-computer.

TOUR GEN. BOARD

3 Octave tone gen. board from Magnus Organ. Unused with instructions & amp. \$9.95 2 for \$18.

PIANO KEYBOARD \$9.95

2 Octave keyboard For use with above organ or synthesizer, etc.

MULTI-USE XFMR \$8.95

Output 18 V @ 6 amp; 17 V @ 6 amps; 10 V @ 10 amp. Brand new. \$8.95 ea., 2 for \$15; 10 for \$50.

BELLTONE PAGER

Made for Bell System. Clip-on belt or pocket pager-receiver. Used condition, complete radio receiver on freq. of 35 Mhz with reed-decoder tone alert. An interesting & useful experimenters gadget. Limited quantity.

#SP-125 \$5.00 each 6/\$25

Please add shipping cost on above.

FREE catalog

Meshna SURPLUS ELECTRONIC MATERIAL

P.O. Box 62

19 ALLERTON STREET
E. LYNN MASS. 01904

Circle 101 on reader service card

New Canadian Magazine, "Electronics Workshop", \$5.00 yearly, sample \$1.00. ETHCO, Box 741 "A", Montreal

SURPRISE! Build inexpensively, the most unusual test instruments, futuristic gadgets using numerical readouts! Catalogue free GBS, Box 100B, Greenbank, WV 24944

CATALOG

GOVERNMENT SURPLUS ELECTRONIC EQUIPMENT For 1975

FREE PUNION REQUEST! Write for Copy of Catalog WS-75 Now! Address: Attention Dept. RE

FAIR RADIO SALES

1016 E. EUREKA • Box 1105 • LIMA, OHIO • 45802

JEEPS \$52.50! Cars \$31.50! 100,000 Items!—Govt. surplus complete information—Your area \$2.00 money back guarantee!!! GOVT. INFO. SERVICE, Dept RE-7, Box 623, South San Francisco, CA 94080

RECONDITIONED test equipment. \$0.50 for catalog. WALTER, 2697 Nickel, San Pablo, CA 94806

PHOTOGRAPHIC timer digital readout, crystal time base, alarm, footswitch, guaranteed. CASCADE LABS, 5637 Bayview Ave., Richmond, CA 94804

UNDERSTAND digital electronics—calculators, microprocessors, clocks. New programmed learning courses. Design of Digital Systems, 6 volumes, only \$14.95. Digital Computer Logic, 4 volumes, \$9.95. Both \$19.95. Unconditional refund if dissatisfied. CAMBRIDGE LEARNING ENTERPRISES, Box 428, FDR Station, New York, NY 10022

INTEL 8080 CPU \$165.00
8008 8 BIT MICRO PROCESSING CHIP (with Data Book) \$ 35.00
2102-2 1024 BIT RAM \$ 5.00
5202A UV PROM \$ 19.00
MM5203 UV PROM \$ 19.00

MINIATURE TRIM POTS
5K, 10K, 25K, 50K, 100K, 200K
\$.75 ea. \$3/2.00

MULTI-TURN TRIM POTS
Similar to Bourans 3010 style, 1/4" x 5/8" x 1 1/4"; 50, 100, 2000, 5000 ohms \$1.50

LIGHT ACTIVATED SCR'S
TO-18, 200V 1A \$1.75

PRINTED CIRCUIT BOARD
4 1/2" x 6 1/2" single sided epoxy board, 1/16" thick, unetched
\$.50 ea. 5/\$2.20

CONDUCTIVE ELASTOMETER
LOW PROFILE CALCULATOR
KEYBOARD \$6.00
2N 5460 P FET \$.45
TIS 73 N FET \$.45
2N 4891 UJT \$.45
ER 900 TRIGGER DIODES 4/\$1.00
2N 6028 PROG. UJT \$.65

VERIPAX PC BOARD

This board is a 1/4" single sided paper epoxy board, 4 1/2" x 6 1/2". DRILLED and ETCHED which will hold up to 21 single 14 pin IC's or 8, 16 or LSI DIP IC's with busses for power supply connector. \$5.25

RED/GREEN BIPOLAR LED \$1.30
MT-2 PHOTO TRANS \$.60
GREEN OR YELLOW LED \$.30
RED GAP OSL-3 LED \$.20
14 PIN DIP SOCKETS \$.40
16 PIN DIP SOCKETS \$.50
MOLEX PINS 100/\$1.00
1000/\$8.00
8 PIN MINI DIP SOCKETS \$.32
4 WATT IR LASER DIODE \$7.95
10 WATT ZENERS
3.9, 4.7 OR 18V \$7.5 EA.
1. WATT ZENERS 5.6,
10, 12, 15, 18, OR 22V \$4.0 EA.

Silicon Power Rectifiers

PRV 1A 3A 12A 50A
100 .06 .14 .30 .80
200 .07 .20 .35 1.15
400 .09 .25 .50 1.40
600 .11 .30 .70 1.80
800 .15 .35 .90 2.30
1000 20 .45 1.10 2.75

REGULATED MODULAR POWER SUPPLIES

+15VDC AT 100ma \$24.95
115VAC INPUT \$19.95
5VDC AT 1A, 115VAC INPUT \$24.95
12V .6A \$24.95
IN 4148 (IN914) 14/\$1.00
1103 1024 bit RAM \$4.75
NEC 6003 2048 bit RAM \$9.50
1101 256 bit RAM \$1.75
8223 PROM \$4.75
7489 RAM \$2.40

Terms: FOB Cambridge, Mass. Send Check or Money Order. Include Postage. Minimum Order \$5.00. COD's \$20.00.

TRANSISTOR SPECIALS

2N1546 PNP GE TO-3	\$.95
2N5086 PNP Si TO-92	4/\$1.00
2N4898 PNP TO-66	\$.60
2N404 PNP GE TO-5	5/\$1.00
2N3919 NPN Si TO-3 RF	\$1.50
MPSA13 NPN Si TO-92	3/\$1.00
2N3767 NPN Si TO-66	\$.70
2N2222 NPN Si TO-18	5/\$1.00
2N3055 NPN Si TO-3	\$.80
2N3904 NPN Si TO-92	5/\$1.00
2N3906 PNP Si TO-92	5/\$1.00
2N5296 NPN Si TO-220	\$.50
2N6109 PNP Si TO-220	\$.55
2N3866 NPN Si TO-5 SI RF POWER	\$.75
MJ252 NPN Si TO-66	\$.90
2N3638 NPN Si TO-5	5/\$1.00
2N6517 NPN TO-92 Si	3/\$1.00

CAPACITORS

35V at 47 uf TANT 5/\$1.00
35V at 6.8 uf TANT 3/\$1.00
20V at 150 uf TANT \$.40
6V 30 uf TANT 5/\$1.00
12V 200 uf ELEC \$.30
200V 4.7 uf ELECT \$.30

FPA 711-7 LEVEL Diode Array Optical Tape Readers \$5.95

Low cost Digital Volt Meter Kit. Kit contains Integ. Circuit Schem. Pwr. Board, LED Displays, Regulator, Resistors, Capacitors and Transistors. Outer case and battery not supplied. Accurate to ± one count. has range of 1 mv to 1,000 V AC. Overall dimensions 1 1/2" x 3" x 5". \$62.00

TTL IC SERIES

74L00—30	7476—45
7400—14	7480—60
7401—17	7483—80
7402—14	7485—1.10
7403—17	7486—40
7404—21	7490—60
7405—20	7491—1.00
7406—35	7492—75
7407—37	7493—60
7408—18	7495—80
7410—17	7496—85
7411—27	8267—1.95
7412—45	74107—40
7413—72	74121—50
7416—37	74123—90
7417—37	74125—65
7420—17	74126—70
7425—36	74150—99
7426—27	74151—84
7427—31	74153—1.05
7430—17	74154—1.49
7432—27	74155—1.05
7437—36	74157—1.17
7438—35	74163—1.45
7440—17	75164—1.75
7441—95	74165—1.75
7442—90	74173—1.55
7445—1.05	74175—1.60
7446—1.10	74177—1.50
7447—1.00	74181—3.00
7448—1.00	74192—1.40
7472—33	74193—1.28
7473—38	74195—80
7474—35	74196—1.85
7475—60	75491—1.10

8038 IC VOLT CONT. OSC \$4.50
5311 or 5316 CLOCK CHIPS ea. \$4.75
C77001 CALENDAR ALARM CLOCK CHIP \$6.95
10 PIN TO-5 TEFLON PC SOCKETS \$.60

C/MOS (DIODE CLAMPED)

74C02 \$.55	CD4019 \$.58
74C10 \$.60	CD4022 \$1.25
74C157 \$2.15	CD4023 \$.30
74C165 \$3.50	CD4024 \$1.00
CD4001 \$.30	CD4025 \$.30
CD4002 \$.30	CD4026 \$1.67
CD4006 \$1.50	CD4027 \$1.20
CD4007 \$.30	CD4028 \$1.09
CD4009 \$.67	CD4029 \$1.42
CD4010 \$.65	CD4030 \$.30
CD4011 \$.30	CD4035 \$1.42
CD4012 \$.30	CD4042 \$.84
CD4013 \$.53	CD4046 \$2.50
CD4015 \$1.17	CD4047 \$3.10
CD4016 \$.65	CD4050 \$.58
CD4017 \$1.35	CO4055 \$2.70

DO-33-A 3 DIG. LED ARRAY READOUT \$1.65

MAN-1 READOUT \$1.75	Full Wave Bridges
MAN-3 READOUT \$1.00	PRV 2A 6A 25A
MAN-4 READOUT \$1.30	200 .95 1.25 4.00
MAN-7 READOUT \$1.25	400 1.15 1.50 5.00
SLA-3 \$4.50	600 1.35 1.75 6.00

2516—64x68 CHARACTER GEN. \$9.95

CD 110 LINEAR 256 XI BIT SELF SCANNING CHARGED COUPLED DEVICE, WITH DATA \$150.00

SANKEN AUDIO POWER AMPS

Si 1010 G 10 WATTS	\$ 6.90
Si 1020 G 20 WATTS	\$13.95
Si 1050 G 50 WATTS	\$24.95

LINEAR CIRCUITS

LM 309K 5V 1A REGULATOR	\$1.50
723—40 +40V REGULATOR	\$.58
301/748-Hi Per. Op. Amp.	\$.30
LM 320—5 or —15 V REG.	\$1.75
LM 376—V to 37V POS REG.	\$.58
741A or 741C OP. AMP.	\$.31
709C OPER. AMP.	\$.25
340T-5, 8, 12, 15, 18, 24V POS. REG. TO-220	\$1.75
101 OPER. AMP. HI PERFORM.	\$.75
LM 308 Oper. Amp., Low Power	\$1.05
747—DUAL 741	\$.65
556—DUAL TIMER	\$1.30
537—PRECISION OP. AMP.	\$2.80
LM 3900—QUAD OP. AMP.	\$.49
LM 324—QUAD 741	\$1.70
560—PHASE LOCK LOOP	\$2.80
561—PHASE LOCK LOOP	\$2.80
565—PHASE LOCK LOOP	\$1.75
566 FUNCTION GEN.	\$2.50
567—TONE DECODER	\$2.00
703—RF-IF AMP.	\$.41
LM370—AGC SQUELCH AMP.	\$1.15
555—2 μs—2 HR. TIMER	\$.65
553 QUAD TIMER	\$3.50
FCO 810 OPTO-ISOLATOR	\$1.35
1456 OP. AMP.	\$.95
1458 DUAL OP. AMP.	\$.65
LM 380—2W AUDIO AMP.	\$1.29
LM 377—2W Stereo Audio Amp.	\$2.50
LM 381—STEREO PREAMP	\$1.69
LM 382—DUAL AUDIO PREAMP	\$1.69
LM 311—HI PER. COMPARATOR	\$.95
LM 319—Dual HI Speed Comp.	\$1.15
LM 339—QUAD COMPARATOR	\$1.25

TRIACS

PRV 1A 10A 25A	1.5A 6A 35A
100 .40 .70 1.30	.40 .50 1.20
200 .70 1.10 1.75	.60 .70 1.60
400 1.10 1.60 2.60	1.00 1.20 2.20
600 1.70 2.30 3.00	3.00

Send 20¢ for our catalog featuring Transistors and Rectifiers 145 Hampshire St., Cambridge, Mass.



SOLID STATE SALES

P.O. BOX 740
SOMERVILLE, MASS. 02143 TEL. 617 547-4005

WE SHIP OVER 95%
OF OUR ORDERS THE
DAY WE RECEIVE THEM



IMPORTED JAPANESE TRANSISTORS

ALL TRANSISTORS ORIGINAL FACTORY MADE

2SA100	\$.65	2SB370	\$1.25	2SC778	\$4.75
2SA101	.70	*2SB405	1.15	2SC781	3.50
2SA102	.65	*2SB415	1.20	2SC799	4.50
2SA103	.70	2SB463	1.75	*2SC828	.80
2SA234	.80	*2SB473	1.75	*2SC829	.85
2SA341	1.05	*2SB474	1.85	2SC839	.95
2SA342	1.05	*2SB481	1.75	2SC945	.65
2SA350	.80	*2SB492	1.35	2SC1000	.75
2SA353	.80	2SC281	.80	2SC1014	1.35
2SA495	.75	2SC371	.80	2SC1018	1.85
2SA564A	.85	2SC372	.80	*2SC1030	3.50
*2SA634	1.50	2SC373	.80	2SC1060	1.80
2SA636	1.45	2SC374	.80	2SC1061	1.80
2SA640	.70	2SC380	.80	*2SC1096	1.35
*2SA643	.95	2SC394	.80	2SC1098	1.30
2SA670	1.95	2SC454	.80	2SC1173	1.50
2SA671	1.95	*2SC458	.80	*2SC1226A	1.35
*2SA683	.85	*2SC460	.80	2SC1237	2.15
*2SA699A	1.45	2SC461	.80	2SC1239	5.75
2SA706	1.95	2SC482	1.75	2SC1306	5.75
2SB22	.75	2SC517	4.75	2SC1307	6.50
2SB54	.80	2SC535	.80	2SC1377	6.75
2SB56	.80	*2SC536	.75	*2SC1383	.85
2SB156	1.05	*2SC537	.75	2SC1384	.85
2SB171	.65	2SC538A	.80	*2SD72	1.15
2SB172	.65	2SC632A	1.15	2SD77	1.05
2SB173	.65	2SC634A	1.15	2SD178	1.45
2SB175	.65	2SC644	.65	2SD186	.80
2SB178	1.15	*2SC710	.75	2SD218	4.25
2SB185	.70	*2SC711	.80	2SD226A	1.75
2SB187	.70	2SC732	.80	2SD234	1.65
2SB303	.75	2SC733	.80	2SD235	1.35
*2SB324	1.15	2SC734	.80	*2SD261	.90
*2SB337	2.25	2SC735	.80	2SK19	1.35
2SB367	1.75	2SC776	3.50	2SK30	1.45

► KIT TR24 \$23.28
Kit Contains 24 (*)Mark Transistors. YOU SAVE 20%

SPECIAL ► 8-TRACK HEAD \$3.95

Playback Replacement Head for Practically All Auto and Home 8-Track Tape Players.

Orders Less Than \$10.00 Add \$1.00—Others Postpaid. Calif. Residents Please Add 6% Sales Tax. Send Order and Make Check or Money Order to:

West Pacific Electronics
P.O. BOX 25837
W. LOS ANGELES, CALIF. 90025

Circle 106 on reader service card

LISTEN TO

Spectacular 4-Channel Sound!

Vista SQ Decoder
Exclusive
CBS Licensed

IC's FOR
SUPERB FIDELITY AND
CHANNEL SEPARATION
WITH FULL LOGIC AND
WAVE MATCHING

FIXED BLEND KIT SQ-1 VARIABLE BLEND KIT SQ-3

\$40⁰⁰ **\$55⁰⁰**

All Parts Except Case and Power Supply.

+20V 75mA IC Regulated Power Supply Kit Available. Only \$5.00 when ordered with a decoder kit.

Shipped prepaid in USA NY State add Tax
\$2.00 additional for CANADA

PHOTOLUME CORPORATION
118 East 28th STREET, New York, N.Y. 10016

Circle 105 on reader service card

ALTAIR 8800 USERS!!

FREE SOFTWARE!... well, almost free. We will send octal & Assembly language listings to anyone sending \$3 per package for postage & handling. If you buy one of our modules, we'll send them FREE.

Package 1: Resident assembler, system monitor, and text editor for the Altair 8800. Really an OS for Assembly language! For example, you can store and call programs by name.

Package 2: BASIC language interpreter—this one should be ready by Oct. 75. We are working very hard at putting the Monitor, Assembler into a fast 16K ROM module for delivery in Oct. 75. SEND FOR OUR FREE SOFTWARE BROCHURE.

OUR HARDWARE

Remember, if you don't continue to buy our neat modules we won't be able to provide FREE software. All our modules just plug into the 8800 bus. Check these. 2KRO — Erasable, reprogrammable PROM module. Kit, \$50; assembled, \$75.

3P+S — I/O module, 2 parallel I/O's plus a serial interface for TTY and RS232. Kit, \$125; assembled, \$165.

4KRA — 4096 word STATIC high speed memory. Kit, \$225; assembled, \$280. MB1 — Mother board, 16 card slots, rugged. Kit, \$35.

BT1 — Bus Terminator module. Kit, \$30. 100PC — 100 pin edge connector, \$8.50. COMING SOON!!

MMM-1 — The first in a series of Music Maker Modules will provide two computer controlled tones that go directly to an audio amplifier! Free driving software.

PPM — Smart PROM programmer. Let us know if you need to program 1702A's or 5203's or both. About \$150. 8800 Plug-in. TC+1 — Fully computer controlled cassette transport and controller/interface. This is a really nice one! About \$300 kit.

TTK — True Timekeeper Module, date and time down to .01 sec. Alarm and Real Time Interrupt too! About \$100.

VTM — Video Terminal Module. 16 or more, if we can do it, lines of 64 characters to a video monitor Smart memory allocation & very fancy text editing software included. About \$125!

Send for our FREE flyer or order now from:
PROCESSOR TECHNOLOGY CO.
Dept. R, 2465 4th St., Berkeley, CA 94710
(415) 549-0857

Circle 104 on reader service card

CB SPECIALS

2SC517	4.75	2SC781	3.25	2SC1237	2.00	2SC1678	5.75
2SC710	.70	2SC799	4.25	2SC1239	2.80	2SC1679	5.75
2SC711	.70	2SC1013	1.50	2SC1243	1.50	2SC1957	3.50
2SC735	.70	2SC1014	1.50	2SC1306	5.25	2SD235	1.00
2SC756	1.50	2SC1017	1.50	2SC1307	6.25	MRF8004	3.00
2SC773	.85	2SC1018	1.50	2SC1377	6.75	4004	3.00
2SC774	1.75	2SC1173	1.25	2SC1449	3.50	4005	3.00

OEM SPECIALS

1N270	.06	2N630	3.10	2N1540	.90	2N2325	2.10	2N3247	3.50	2N3856	.20	2N4403	.19
1N749.A	.16	2N677C	5.00	2N1543	3.00	2N2326	3.00	2N3250	4.00	2N3866	.90	2N4409	.19
1N750.A	.16	2N706	2.00	2N1544	80	2N2327	4.00	2N3375	4.95	2N3903	.19	2N4410	.19
1N751.A	.16	2N706B	35	2N1549	1.05	2N2328	4.25	2N3393	1.90	2N3904	.19	2N4416	.75
1N914	.06	2N711	35	2N1551	3.50	2N2329	6.00	2N3394	1.90	2N3905	.19	2N4441	.85
1N4148	.06	2N711B	50	2N1552	3.50	2N2368	.25	2N3414	22	2N3906	.19	2N4442	.90
1N4746	.50	2N718	18	2N1554	1.75	2N2369	.19	2N3415	25	2N3924	3.25	2N4443	1.25
1N4747	.50	2N718A	25	2N1557	1.50	2N2484	20	2N3416	28	2N3925	4.50	2N4452	.60
1N4749	.50	2N720A	1.35	2N1560	3.00	2N2712	.25	2N3417	30	2N3954	4.50	2N5061	.25
1N5355	.75	2N759A	90	2N1605	.35	2N2894	.40	2N3442	1.90	2N3954A	4.50	2N5064	.40
1N5357.A,B,75	2N760	40	2N1613	30	2N2903	3.50	2N3553	1.50	2N3955	2.50	2N5130	.19	
1N5358.A,B,75	2N877	2.25	2N1671	1.00	2N2904	.19	2N3563	18	2N3955A	2.90	2N5133	.15	
1N5359.A,B,75	2N894	1.75	2N1711	30	2N2904A	.25	2N3565	18	2N3957	1.30	2N5138	.15	
2N173	2.00	2N918	1.90	2N1907	4.25	2N2905	.19	2N3642	.18	2N3958	1.20	2N5154	6.25
2N178	.90	2N930	19	2N2080	1.90	2N2905A	.25	2N3642	19	2N4037	.60	2N5157	8.95
2N327A	1.25	2N956	20	2N2102	40	2N2906	.19	2N3643	15	2N4093	.90	2N5198	3.85
2N334	1.25	2N960	40	2N2218	20	2N2906A	20	2N3645	15	2N4124	.18	2N5294	.60
2N336	.90	2N962	40	2N2218A	25	2N2907	.19	2N3646	10	2N4126	.23	2N5296	.45
2N338A	1.10	2N967	40	2N2219	20	2N2907A	.25	2N3730	1.25	2N4141	.23	2N5306	.20
2N398B	.90	2N1136	1.25	2N219A	25	2N2913	.75	2N3731	1.65	2N4142	.16	2N5354	.25
2N404	.20	2N1137A	1.65	2N2219	19	2N2914	1.25	2N3740	1.00	2N4143	.15	2N5369	.20
2N443	1.05	2N1143	1.75	2N2221A	19	2N2916A	3.75	2N3771	1.90	2N4220A	.90	2N5400	.50
2N456	1.15	2N1143	1.75	2N2222	19	2N3019	1.25	2N3772	2.00	2N4234	1.25	2N5401	.50
2N501A	3.50	2N1302	25	2N2222A	19	2N3053	.19	2N3773	2.10	2N4235	1.60	2N5457	.35
2N508A	.35	2N1305	30	2N2270	30	2N3054	.70	2N3819	25	2N4400	.19	2N5458	.35
2N512B	2.50	2N1377	1.25	2N2322	1.50	2N3055	.75	2N3823	60	2N4401	.19	2N5467	28.00
2N555	.45	2N1420	18	2N2323	1.60	2N3227	2.10	2N3843	.25	2N4402	.19	C106B1	.45
2N652A	.90	2N1483	1.00	2N2324	2.00								

JAPANESE TRANSISTORS

2SA52	.60	2SB370	1.10	2SC478	.80	2SC829	.75	2SC1509	1.25
2SA101	.70	2SB379	.65	2SC482	1.75	2SC833	70	2SC1569	1.25
2SA103	.70	2SB380	.70	2SC491	2.50	2SC838	70	2SC1756	1.25
2SA221	.60	2SB405	1.00	2SC495	70	2SC839	85	2SD30	.95
2SA473	.85	2SB407	1.20	2SC497	1.60	2SC940	65	2SD45	2.00
2SA495	.65	2SB415	1.05	2SC515	80	2SC935	65	2SD64	.75
2SA497	.55	2SB461	1.25	2SC535	95	2SC1010	80	2SD65	.75
2SA505	.65	2SB463	1.65	2SC536	.65	2SC1012	80	2SD68	.70
2SA562	.70	2SB471	1.75	2SC537	.70	2SC1013	1.50	2SD72	1.50
2SA607	2.25	2SB474	1.75	2SC563	2.50	2SC1014	1.50	2SD88	1.00
2SA613	1.00	2SB481	2.10	2SC564	.70	2SC1018	1.50	2SD120	.85
2SA643	.85	2SB492	1.25	2SC568	.70	2SC1030	3.25	2SD130	1.50
2SA647	2.75	2SB495	95	2SC582	.85	2SC1051	2.50	2SD141	2.25
2SA673	.85	2SB605	2.00	2SC591	2.50	2SC1061	1.65	2SD151	2.50
2SA679	2.25	2SB606	2.00	2SC605	1.00	2SC1079	3.95	2SD170	2.00
2SA682	.95	2SC15	.65	2SC619	.70	2SC1096	1.20	2SD180	3.00
2SA699	1.30	2SC24	.65	2SC620	.80	2SC1098	1.15	2SD198	2.50
2SA699A	2.00	2SC32	.65	2SC627	1.75	2SC1115	2.75	2SD201	2.50
2SA705	.55	2SC33	.65	2SC644	.70	2SC1166	.70	2SD218	5.00
2SA714	2.50	2SC41	4.00	2SC645	.85	2SC1170	4.00	2SD235	1.00
2SA720	.70	2SC49	80	2SC681	2.50	2SC1172B	4.25	2SD261	.80
2SA733	.65	2SC56	95	2SC684	2.10	2SC1173	1.25	2SD291	.85
2SB22	.65	2SC143	3.50	2SC687	2.50	2SC1213	.75	2SD292	.85
2SB54	.70	2SC154	3.75	2SC696	2.35	2SC1226	1.25	2SD300	2.50
2SB56	.70	2SC162	3.75	2SC710	.70	2SC1237	2.00	2SD313	1.20
2SB77	.70	2SC163	4.50	2SC711	.70	2SC1239	2.80	2SD315	.75
2SB128	2.50	2SC185	1.00	2SC712	.70	2SC1293	.85	2SD318	.95
2SB135	.95	2SC202	1.00	2SC713	.70	2SC1308	5.00	2SD341	.95
2SB152	4.50	2SC206	1.00	2SC732	.70	2SC1317	.60	2SD350	3.50
2SB172	.55	2SC240	1.10	2SC733	.70	2SC1325	5.00	2SD352	.80
2SB173	.55	2SC261	.65	2SC735	.70	2SC1347	.80	2SD380	6.00
2SB175	.55	2SC291	.65	2SC739	.70	2SC1377	6.75	2SD389	.95
2SB178	1.00	2SC320	.75	2SC756	1.50	2SC1383	.75	2SD390	.75
2SB186	.60	2SC352	.75	2SC774	1.75	2SC1393	.60	2SD437	6.00
2SB187	.60	2SC353	.75	2SC775	2.00	2SC1409	2.75	2SD458	.80
2SB235	1.95	2SC371	.70	2SC778	3.00	2SC1410	2.75		

5% OFF ON ORDERS OVER \$50.00
10% OFF ON ORDERS OVER \$100.00
15% OFF ON ORDERS OVER \$250.00

TTL

7400	\$.16	7451	\$.21	74154	\$ 1.25
7401	.17	7453	.20	74155	1.07
7402	.17	7454	.17	74156	1.07
7403	.17	7460	.17	74157	.99
7404	.19	7464	.35	74158	1.19
7405	.20	7465	.35	74160	1.39
7406	.35	7470	.30	74161	1.25
7407	.35	7472	.30	74162	1.39
7408	.19	7473	.35	74163	1.39
7409	.23	7474	.35	74164	1.59
7410	.16	7475	.57	74165	1.59
7411	.26	7476	.39	74166	1.49
7413	.55	7483	.99	74170	2.30
7415	.35	7485	1.10	74173	1.49
7416	.35	7486	.40	74174	1.62
7417	.35	7489	2.48	74175	1.39
7420	.17	7490	.62	74176	.89
7422	.26	7491	.97	74177	.84
7423	.29	7492	.71	74180	.90
7425	.27	7493	.60	74181	2.98
7426	.26	7494	.94	74182	.79
7427	.29	7495	.79	74184	2.29
7430	.20	7496	.79	74185	2.29
7432	.23	74100	1.30	74187	5.95
7437	.35	74105	.44	74190	1.35
7438	.35	74107	.40	74191	1.35
7440	.17	74121	.42	74192	1.25
7441	.98	74122	.45	74193	1.19
7442	.77	74123	.85	74194	1.25
7443	.87	74125	.54	74195	.89
7444	.89	74126	.71	74196	1.25
7445	.89	74141	1.04	74197	.89
7446	.93	74145	1.04	74198	1.79
7447	.80	74150	.97	74199	1.79
7448	1.04	74151	.79	74200	5.90
7450	.20	74153	.99		

LOW POWER TTL

74L00	\$.25	74L51	\$.29	74L90	\$ 1.49
74L02	.25	74L55	.33	74L91	1.45
74L03	.25	74L71	.25	74L93	1.69
74L04	.25	74L72	.39	74L95	1.69
74L06	.25	74L73	.49	74L98	2.79
74L10	.25	74L74	.49	74L164	2.79
74L20	.33	74L78	.79	74L165	2.79
74L30	.33	74L85	1.25		
74L42	1.49	74L86	.69		

HIGH SPEED TTL

74H00	\$.25	74H21	\$.25	74H55	\$.25
74H01	.25	74H22	.25	74H60	.25
74H04	.25	74H30	.25	74H61	.25
74H08	.25	74H40	.25	74H62	.25
74H10	.25	74H50	.25	74H72	.39
74H11	.25	74H52	.25	74H74	.39
74H20	.25	74H53	.25	74H76	.49

8000 SERIES

8091	\$.53	8214	\$ 1.49	8811	\$.59
8092	.53	8230	1.49	8812	.89
8095	1.25	8230	2.19	8822	2.19
8121	.80	8520	1.16	8830	2.19
8123	1.43	8551	1.39	8831	2.19
8130	1.97	8552	2.19	8836	.25
8200	2.33	8554	2.19	8880	1.19
8210	2.79	8810	.69	8263	5.79
				8267	2.59

9000 SERIES

9002	\$.35	9309	\$.79	9601	\$.89
9301	1.03	9312	.79	9602	.79

Data sheets supplied on request.
 Add \$.50 ea. for items less than \$1.00

CMOS

4000A	\$.39	4019A	\$.69	4066A	\$ 1.19
4001A	.39	4020A	1.98	4068A	.49
4002A	.39	4021A	1.89	4069A	.49
4006A	1.95	4023A	.39	4071A	.40
4007A	.40	4024A	1.45	4072A	.40
4008A	1.98	4025A	.39	4073A	.40
4009A	.69	4027A	.98	4075A	.40
4010A	.69	4028A	1.69	4078A	.40
4011A	.39	4030A	.79	4081A	.40
4013A	.69	4035A	1.89	4082A	.40
4014A	1.98	4042A	1.89	4528A	1.60
4015A	1.98	4049A	.79	4585A	2.40
4016A	.69	4050A	.79	4047A	2.75
74C00	\$.22	74C74	\$ 1.04	74C162	\$ 2.93
74C02	.26	74C76	1.34	74C163	2.66
74C04	.44	74C107	1.13	74C164	2.66
74C08	.68	74C151	2.61	74C173	2.61
74C10	.35	74C154	3.15	74C195	2.66
74C20	.35	74C157	1.76	80C95	1.35
74C42	1.61	74C160	2.48	80C97	1.13
74C73	1.04	74C161	2.93		

5203

2048 bit programmable ROM UV erasable \$14.95

MAN3M LED DISPLAY

RH dec comm cathode .12" character 12 for \$1.98

9 DIGIT LED DISPLAY

On multiplexed substrate, comm. cathode compatible with all 8 digit calculator chips. 7 segment right hand decimal, red with clear magnifying lens. .12" character, 1 to 4 MA, 1.8V typ 2 1/2" x 1/4" x 1/16" high \$3.95

CLOSEOUT ON CALCULATOR CHIPS

These early model calculator chips have been superseded and are now offered at this lowest price ever. Complete with data.

- CT5001 12 digit display and calculate, 4 function, chain operation, fixed dec. 40 pin package \$1.95
- CT5002 Same as 5001 except battery operation \$2.95
- CT5005 12 digit display and calculate, 4 function plus memory. 28 pin package \$3.49

WITH PURCHASE OF ANY OF THE ABOVE —

MAN 3M led display, RH common cathode, .12" character 12 for \$1.70

AUGUST SPECIALS

DIGITAL CIRCUITS (DIP PKG)

7448	BCD - 7 seg Decoder/Driver (30V)	\$.89
7474	Dual D flip-flop	.29
74107	Dual J-K flip-flop	.33
74123	Retrig monostable multivib w/clr	.69

LINEAR CIRCUITS (DIP PKG)

380	2 watt audio amplifier	\$1.09
3900	Quad amplifier	.29

POCKET CALCULATOR KIT

5 function plus constant — addressable memory with individual recall — 8 digit display plus overflow — battery saver — uses standard or rechargeable batteries — all necessary parts in ready to assemble form — Instructions included.



CALC KIT	\$12.95
ASSEMBLED	14.95
SET OF ALKALINE BATT.	2.00

OUR 10% DISCOUNT HAS BEEN DEDUCTED FROM ALL PRICES REGARDLESS OF AMOUNT OF ORDER.

MEMORIES

1101	256 bit RAM MOS	\$ 1.50
1103	1024 bit RAM MOS	3.95
2102	1024 bit static RAM	5.55
5203	2048 bit UV eras PROM	17.95
5260	1024 bit RAM	2.49
5261	1024 bit RAM	2.69
5262	2048 bit RAM	5.95
7489	64 bit ROM TTL	2.48
8223	Programmable ROM	1.69
74200	256 bit RAM tri-state	5.90

CALCULATOR & CLOCK CHIPS

S001	12 DIG 4 funct fix dec	\$3.45
S002	Same as S001 exc btry pwr	3.95
S005	12 DIG 4 funct w/mem	4.95
MM5725	8 DIG 4 funct chain & dec	1.98
MM5736	18 pin 6 DIG 4 funct	4.45
MM5738	8 DIG 5 funct K & Mem	5.35
MM5739	9 DIG 4 funct (btry sur)	5.35
MM5311	28 pin BCD 6 dig mux	4.45
MM5312	24 pin 1 pps BCD 4 dig mux	3.95
MM5313	28 pin 1 pps BCD 6 dig mux	4.45
MM5314	24 pin 6 dig mux	4.45
MM5316	40 pin alarm 4 dig	5.39

LED's

MV10B	Red TO 18	\$.22
MV50	Axial leads	.18
MV5020	Jumbo Vls. Red (Red Dome)	.22
	Jumbo Vls. Red (Clear Dome)	.22
ME4	Infra red diff. dome	.54
MAN1	Red 7 seq. .270"	2.19
MAN2	Red alpha num. 32"	4.39
MAN4	Red 7 seq. .190"	1.95
MAN5	Green 7 seq. .270"	3.45
MAN6	6" high solid seq.	4.25
MAN7	Red 7 seq. .270"	1.19
MAN8	Yellow 7 seq. .270"	3.45
MAN64	4" high solid seq.	2.95
MAN66	6" high spaced seq.	3.75
MCT2	Opto-iso transistor	.61

SHIFT REGISTERS

MM 5013	1024 bit accum. dynamic	mDIP	\$1.75
MM 5016	500/512 bit dynamic	mDIP	1.59
MM 5058	1024 bit static	DIP	3.45
SI 5-4025	Dual 64 bit static	DIP	1.39

DTL

930	\$.15	937	\$.15	949	\$.15
932	.15	944	.15	962	.15
936	.15	946	.15	963	.15

Satisfaction guaranteed. Shipment will be made via first class mail within 3 days from receipt of order. Add \$.50 to cover shipping and handling for orders under \$25.00. Minimum order \$5.00. California residents add sales tax.

INTERNATIONAL ELECTRONICS UNLIMITED

P.O. BOX 1708/ MONTEREY, CA. 93940 USA
 PHONE (408) 659-3171



2102-2 MOS 1024 BIT MEMORY

FULLY DECODED STATIC RANDOM ACCESS MEMORY
DIRECTLY TTL COMPATIBLE INPUTS AND OUTPUT
SINGLE 5V SUPPLY - - NO CLOCKS OR REFRESH

\$6.95 EA. (DIP) 8 FOR \$49.95

Numeric Display
1/4" Single Digit
GaAsP LED



COMMON CATHODE WITH RH DECIMAL

Compact—10 digits in 3" panel width

Highly legible—bright red 1/4" character easily read within 10 feet over a wide viewing angle
125 mW per digit at typical brightness

SUPER SPECIAL \$7.75
TEN for \$5.95

SPECIAL
8223
PROM



8 BIT
32 WORD
MEMORY

***\$3.00 EA.**
10 - *\$29

WE PROGRAM
FOR *\$5 EACH

CD-2 COUNTER KIT

Unit includes board, 7490, 7475, quad latch, 7447 seven-segment driver, and RCA DR2010.



COMPLETE KIT only \$11.95; FULLY-ASSEMBLED \$15.00; boards can be supplied separately at \$2.50 per digit.

RCA 2010

Numitron Digital Display Tube, incandescent 5-volt 7-segment:

.6" High numeral visible from 30 ft
Standard 9-pin base (solderable)

Left-hand decimal point

EACH \$5.00 5 FOR \$20.00

CMOS

CD4000	\$.55	CD4016	1.00
CD4001	.45	CD4019	1.00
CD4002	.45	CD4023	.45
CD4007	1.00	CD4024	1.60
CD4008	3.25	CD4025	.45
CD4009	.75	CD4027	1.00
CD4010	.75	CD4030	1.00
CD4011	.45	74C20	.65
CD4012	.45	74C42	2.00
CD4013	1.00	74C157	2.50
CD4015	3.00	74C161	3.00
		74C195	2.00

TRANSISTOR SPECIAL

2N3568-HEP73B
TOP2 PLASTIC
NPN 300MW
60V 40-120B
EACH \$.15
TEN 1.00
100 9.00
1000 80.00

NEW-TELEDYNE
MARKED T3568



POTTER BRUMFIELD

Type KHP Relay
4 PDT 3A Contacts

24 VDC (650 coil) \$1.50 EA.

120 VAC (10.5 MA coil) \$1.75 EA.

SEND FOR FREE FLYER!

C.O.D. PHONE ORDERS
ACCEPTED--\$10 MINIMUM

All IC's new and fully tested, leads plated with gold or solder. Orders for \$5.00 or more are shipped prepaid, smaller orders--add 55¢. California residents add Sales Tax.....IC's shipped within 24 hours.

BABYLON ELECTRONICS

P.O. BOX 41727
SACRAMENTO, CA
95841

916 334 2161

TTL DIP


7400	.20
74H00	.25
7401	.20
74H01	.25
7402	.25
7403	.25
7404	.25
74H04	.30
7405	.30
7406	.40
7408	.30
7400	.20
7410	.20
7413	.75
7417	.40
7420	.20
74L20	.30
74H20	.30
74H22	.30
7430	.20
74H30	.30
74L30	.30
7440	.20
74H40	.30
7442	1.00
7447	1.50
7450	.20
74H50	.30
7451	.20
74H51	.25
7453	.20
7454	.20
74L54	.25
74L55	.25
7460	.16
74L71	.25
7472	.40
74L72	.60
7473	.35
74L73	.75
7474	.45
74H74	.75
7475	.80
7476	.55
74L78	.70
7480	.50
7483	.70
7489	3.00
7490	1.00
7492	.65
7493	1.00
7495	.65
74L95	1.00
74107	.50
74145	1.25
74180	1.00
74193	1.50
74195	.80

FANTASTIC BOARD SET



This unusual set of 5 boards contains a wide variety of late parts, including the following: 3reed relays, including a latching relay, over 90 small signal diodes, over 30 rectifier diodes, 11 2N5061 SCRs, many transistors including 2N6027, 2N6028, 2N4401, 2N5088, 2N3903, 2N3905. 2 bridge rectifiers, 46 Teledyne HiNIL high noise immunity integrated circuits, G.E. SCRs, and TI power transistors, plus many capacitors, etc.
STOCK NO.R5277 set of 5 boards \$6.00 10/11.00

ANOTHER GIANT SOPHISTICATED BOARD

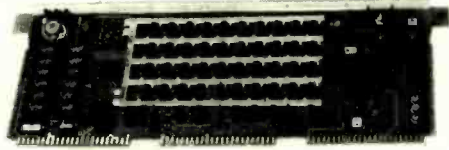

Super board has 13 reed relays, designed for 12 or 24 volts. 1 SPDT reed relay, LM-309 regulator, 49 TTL & DTL ICs, 2 TO-5 linear ICs, 11 2N5061 SCRs, transistors, diodes, capacitors and much more. We supply data on most of the parts. 7"x18 1/2"

STOCK NO.R9228 14.95 ea. 2/28.00

TRANSFORMER

R9906 35 Vct 6 A. & 10 V 10 A. 8.95 ea. 2/16.00

Enclose sufficient postage. Excess will be refunded. Send for our new catalog 14. 64 pages of electronic bargains.



DELTA ELECTRONICS CO.

BOX 1, LYNN, MASSACHUSETTS 01903
Phone (617) 388-4705

Circle 93 on reader service card

LOOK FOR
THE
SEPT.
ISSUE OF
RADIO-
ELECTRONICS
AT YOUR
NEWSDEALER

AUG. 19

1st prize: **CAVE**
16 bit microcomputer chip
CONTEST!

2nd prize: 8080 cpu 3rd prize: 8008 cpu

We were the 1st to offer the 8008 to hobbyists over 16 months ago; now we're setting the pace again with a powerful new 16 bit microcomputer IC in a 40 pin DIP, made by:

the Secret Microcomputer Co!

GODBOUT

BILL GODBOUT ELECTRONICS
BOX 2355, OAKLAND AIRPORT, CA 94614

YOU MAY WIN ONE OF THESE CHIPS -- JUST:

- 1) Reveal the Secret Microcomputer Co.'s true identity
- 2) Tell us in 25 words or less why you should receive a free chip

If you can convince our jaded judges, in a form suitable for use in this magazine. YOU WIN!

GOOD LUCK!!

FINE PRINT: ALL ENTRIES MUST BE POSTMARKED BY AUG 31 AND BE IN OUR HANDS BY SEP 7, 1975; ENTRIES BECOME PROPERTY OF BILL GODBOUT ELECTRONICS. ALL CONTESTANTS RECEIVE A DATA SHEET ABOUT OUR FIRST PRIZE. WINNER WILL BE NOTIFIED BY OCT 1, 1975. IF YOU DON'T WIN ANYTHING THIS TIME AROUND, DON'T FEEL TOO BAD; ENTER OUR COMING CONTEST FOR A COMPLETE 16 BIT MICROCOMPUTER KIT. THESE CONTESTS SPOTLIGHT PRODUCTS WE'RE INTRODUCING FOR FALL '75. SEND ENTRIES TO "16 BIT CONTEST", BOX 2355, OAKLAND AIRPORT, CALIFORNIA 94614.

March ad error: memory board from Solid State Music
Circle 96 on reader service card

LINEAR INTEGRATED CIRCUITS

GENERAL PURPOSE AMPLIFIERS		1-24	25-99	100 up
SL2018	GP amp/plier	4.01	3.51	3.01
SL201C	GP amp/plier	1.87	1.64	1.40
MATCHED NPN TRANSISTORS				
SL301A	Matched pair	2.72	2.46	1.40
SL301B	Matched pair	2.42	2.14	1.72
SL303A	Matched tripl	4.47	4.78	4.09
SL303B	Matched tripl	3.93	3.43	3.93
SL306B	Dual matched pairs	7.37	6.44	5.52
SL312B	Matched pair w/all	2.85	2.56	2.27
SL354B	Matched pair	1.93	1.68	1.43
SL360C	2.8GHz match w/all	0.93	0.86	0.81
SL362C	2.5GHz low noise pr	16.26	14.20	12.14
SL3045C	Transistor array	1.77	2.43	2.09
SL145C	2.8GHz trans. array	14.78	12.94	11.09
AUDIO CIRCUITS				
SL414A	3W audio amplifier	4.22	3.70	3.17
SL418A	5W audio amplifier	5.49	4.81	4.12
POWER CONTROL CIRCUITS				
SL440	Power control circuit	5.49	4.81	4.12
TRANSISTOR ARRAYS				
SL3046	Five-transistor array	1.85	1.61	1.37
LINEAR RF AMPLIFIERS				
SL501A	RF amplifier	19.26	16.84	14.44
SL501B	RF amplifier	5.91	5.17	4.44
SL502A	RF amplifier	14.58	13.04	11.17
SL502B	RF amplifier	3.88	3.49	3.09
SL503A	RF amplifier	16.50	14.78	13.07
SL503B	RF amplifier	4.12	3.70	3.27
SL551A	RF amplifier	18.82	16.87	14.92
SL551B	RF amplifier	5.89	5.28	4.67
SL552A	RF amplifier	18.82	16.87	14.92
SL552B	RF amplifier	5.89	5.28	4.67
SL553A	RF amplifier	21.09	19.00	16.71
SL553B	RF amplifier	4.28	3.82	3.36
SL510C	RF det. & video amp	25.34	22.18	19.00
SL511C	RF det. & video amp	25.34	22.18	19.00
LIMITING WIDEBAND AMPLIFIERS				
SL521A	Limiting RF amp	27.72	24.26	20.80
SL521B	Limiting RF amp	17.58	15.58	13.57
SL521C	Limiting RF amp	10.59	9.27	7.95
SL571A	Limiting RF amp	37.80	33.08	28.35
SL571B	Limiting RF amp	23.39	20.46	17.53
SL571C	Limiting RF amp	17.48	15.29	13.09
SL528C	Wideband amplifier	5.80	5.20	4.60
SL530C	Logarithmic amp	17.58	15.58	13.57
SL550C	200MHz wideband amp	26.19	21.81	18.16
SL1030C	200MHz wideband amp	29.57	25.87	22.18
RADIO COMMUNICATIONS CIRCUITS				
SL510C	RF amplifier	4.07	3.56	3.06
SL511C	RF amplifier	4.07	3.56	3.06
SL512C	RF amplifier	4.07	3.56	3.06
SL513C	Line amp/demod.	8.66	7.58	6.49
SL520C	VOGAD	6.15	5.39	4.62
SL521C	AGC generator	6.15	5.39	4.62
SL522C	AF amp/VOGAD	15.21	13.31	11.41
	diodes amp/plier			

PLESSEY SEMICONDUCTORS

SL623C	AM det./AGC amp/PL	11.19	9.79	8.40
SL624C	SSB demod.			
SL624C	Mod/mods det AF amp	5.70	5.00	4.28
SL630C	AF amplifier	3.85	3.38	2.90
SL640C	Dbl. bal. modulator	7.55	6.60	5.65
SL641C	Receiver mixer	7.85	6.60	5.65
SL645C	Quadr. lev. device	7.85	6.60	5.65
SL650B	Mod./phase loc. loop	10.86	9.31	7.76
SL650C	Mod./phase loc. loop	8.00	5.83	4.86
SL651B	Mod./phase loc. loop	12.06	10.34	8.62
SL651C	Mod./phase loc. loop	7.56	6.84	4.40
OPERATIONAL AMPLIFIERS				
SL701B	Op. amplifier	7.13	6.23	5.39
SL701C	Op. amplifier	3.56	3.12	2.67
SL702B	Op. amplifier	7.13	6.23	5.39
SL702C	Op. amplifier	3.56	3.12	2.67
SL717A	Dual comparator	10.35	9.06	7.76
SL717C	Dual comparator	6.67	5.76	4.94
SL751B	Op. amplifier	8.37	7.50	6.63
SL751C	Op. amplifier	4.81	4.30	3.80
TELECOMMUNICATIONS CIRCUIT				
SL1001A	Linear mod/demod.	3.22	2.83	2.43
SL1001B	Linear mod/demod.	3.22	2.83	2.43
SL1020A	Lin. amp/remote con	7.18	6.26	5.36
TELEVISION CIRCUITS				
SA4570	Limit. IF amp/PMF det.	4.22	4.22	3.30
SA6611	Limit. IF amp/PMF det.	4.73	4.73	3.70
SA7000	Signal processor	10.14	10.14	7.92
SBA550	Signal processor	10.14	10.14	7.92
SBA750	Limit. IF amp/PMF det.	4.73	4.73	3.70
SL4372	Limit. IF amp/PMF det.	4.73	4.73	3.70
SL437C	IF & AGC for PNP tuners	13.52	13.52	10.56
SL437D	IF & AGC for PNP tuners	13.52	13.52	10.56
SL442	Switch control power	9.24	7.92	6.60
SL450	Power sup. & Syn. sep.	11.09	9.50	7.92
SL456A	TV IF system	7.39	6.34	5.28
SL456B	TV IF system	7.39	6.34	5.28
SL457A	TV IF system	7.39	6.34	5.28
SL457B	TV IF system	7.39	6.34	5.28
SL9001	Color demodulator	10.14	10.14	7.92
SL917	Color decoder	13.52	13.52	10.56
DIGITAL INTEGRATED CIRCUITS				
Description: 1-24 25-99 100 up				
PROCESS CONTROL CIRCUITS				
SP520	Gray code counter	13.94	12.49	11.04
SP521	8214 register multipl.	13.94	12.49	11.04
SP522	Phase loc. & com.	13.94	12.49	11.04
PECL II - SP1000 SERIES				
SP1004B	Dual 4 I/P OR/NOR gate	1.71	1.48	1.25
SP1005B	Dual 4 I/P OR/NOR gate	1.71	1.48	1.25
SP1006B	Dual 4 I/P OR/NOR gate	1.71	1.48	1.25
SP1007B	Triple 3 I/P NOR gate	1.71	1.48	1.25
SP1008B	Triple 3 I/P NOR gate	1.71	1.48	1.25
SP1009B	Triple 3 I/P NOR gate	1.71	1.48	1.25
SP1010B	Dual 2 I/P NOR gate	1.71	1.48	1.25
SP1011B	Dual 2 I/P NOR gate	1.71	1.48	1.25
SP1012B	Dual 2 I/P NOR gate	1.71	1.48	1.25
SP1013B	Dual 2 I/P NOR gate	1.71	1.48	1.25
SP1014B	Dual 2 I/P NOR gate	1.71	1.48	1.25
SP1015B	Dual 2 I/P NOR gate	1.71	1.48	1.25
SP1016B	Dual 2 I/P NOR gate	1.71	1.48	1.25
SP1017B	Triple 3 I/P NOR gate	1.71	1.48	1.25
SP1018B	Triple 3 I/P NOR gate	1.71	1.48	1.25
SP1019B	Triple 3 I/P NOR gate	1.71	1.48	1.25
SP1020B	Dual 4 I/P OR/NOR gate	2.17	1.86	1.55
SP1021B	Dual 4 I/P OR/NOR gate	2.17	1.86	1.55
SP1022B	Dual 4 I/P OR/NOR gate	2.17	1.86	1.55
SP1023B	Dual 4 I/P OR/NOR gate	2.17	1.86	1.55
SP1024B	Dual 4 I/P OR/NOR gate	2.17	1.86	1.55
SP1025B	Dual 4 I/P OR/NOR gate	2.17	1.86	1.55
SP1026B	Dual 4 I/P OR/NOR gate	2.17	1.86	1.55
SP1027B	Triple 3 I/P NOR gate	1.71	1.48	1.25
SP1028B	Triple 3 I/P NOR gate	1.71	1.48	1.25
SP1029B	Triple 3 I/P NOR gate	1.71	1.48	1.25
SP1030B	Dual 2 I/P NOR gate	1.71	1.48	1.25
SP1031B	Dual 2 I/P NOR gate	1.71	1.48	1.25
SP1032B	Dual 2 I/P NOR gate	1.71	1.48	1.25
SP1033B	Dual 2 I/P NOR gate	1.71	1.48	1.25
SP1034B	Dual 2 I/P NOR gate	1.71	1.48	1.25
SP1035B	Dual 2 I/P NOR gate	1.71	1.48	1.25
SP1036B	Dual 2 I/P NOR gate	1.71	1.48	1.25
SP1037B	Triple 3 I/P NOR gate	1.71	1.48	1.25
SP1038B	Triple 3 I/P NOR gate	1.71	1.48	1.25
SP1039B	Triple 3 I/P NOR gate	1.71	1.48	1.25
SP1040B	Dual 4 I/P OR/NOR gate	2.17	1.86	1.55
SP1041B	Dual 4 I/P OR/NOR gate	2.17	1.86	1.55
SP1042B	Dual 4 I/P OR/NOR gate	2.17	1.86	1.55
SP1043B	Dual 4 I/P OR/NOR gate	2.17	1.86	1.55
SP1044B	Dual 4 I/P OR/NOR gate	2.17	1.86	1.55
SP1045B	Dual 4 I/P OR/NOR gate	2.17	1.86	1.55
SP1046B	Dual 4 I/P OR/NOR gate	2.17	1.86	1.55
SP1047B	Triple 3 I/P NOR gate	1.71	1.48	1.25
SP1048B	Triple 3 I/P NOR gate	1.71	1.48	1.25
SP1049B	Triple 3 I/P NOR gate	1.71	1.48	1.25
SP1050B	Dual 2 I/P NOR gate	1.71	1.48	1.25
SP1051B	Dual 2 I/P NOR gate	1.71	1.48	1.25
SP1052B	Dual 2 I/P NOR gate	1.71	1.48	1.25
SP1053B	Dual 2 I/P NOR gate	1.71	1.48	1.25
SP1054B	Dual 2 I/P NOR gate	1.71	1.48	1.25
SP1055B	Dual 2 I/P NOR gate	1.71	1.48	1.25
SP1056B	Dual 2 I/P NOR gate	1.71	1.48	1.25
SP1057B	Triple 3 I/P NOR gate	1.71	1.48	1.25
SP1058B	Triple 3 I/P NOR gate	1.71	1.48	1.25
SP1059B	Triple 3 I/P NOR gate	1.71	1.48	1.25
SP1060B	Dual 4 I/P OR/NOR gate	2.17	1.86	1.55
SP1061B	Dual 4 I/P OR/NOR gate	2.17	1.86	1.55
SP1062B	Dual 4 I/P OR/NOR gate	2.17	1.86	1.55
SP1063B	Dual 4 I/P OR/NOR gate	2.17	1.86	1.55
SP1064B	Dual 4 I/P OR/NOR gate	2.17	1.86	1.55
SP1065B	Dual 4 I/P OR/NOR gate	2.17	1.86	1.55
SP1066B	Dual 4 I/P OR/NOR gate	2.17	1.86	1.55
SP1067B	Triple 3 I/P NOR gate	1.71	1.48	1.25
SP1068B	Triple 3 I/P NOR gate	1.71	1.48	1.25
SP1069B	Triple 3 I/P NOR gate	1.71	1.48	1.25
SP1070B	Dual 2 I/P NOR gate	1.71	1.48	1.25
SP1071B	Dual 2 I/P NOR gate	1.71	1.48	1.25
SP1072B	Dual 2 I/P NOR gate	1.71	1.48	1.25
SP1073B	Dual 2 I/P NOR gate	1.71	1.48	1.25
SP1074B	Dual 2 I/P NOR gate	1.71	1.48	1.25
SP1075B	Dual 2 I/P NOR gate	1.71	1.48	1.25
SP1076B	Dual 2 I/P NOR gate	1.71	1.48	1.25
SP1077B	Triple 3 I/P NOR gate	1.71	1.48	1.25
SP1078B	Triple 3 I/P NOR gate	1.71	1.48	1.25
SP1079B	Triple 3 I/P NOR gate	1.71	1.48	1.25
SP1080B	Dual 4 I/P OR/NOR gate	2.17	1.86	1.55
SP1081B	Dual 4 I/P OR/NOR gate	2.17	1.86	1.55
SP1082B	Dual 4 I/P OR/NOR gate	2.17	1.86	1.55
SP1083B	Dual 4 I/P OR/NOR gate	2.17	1.86	1.55
SP1084B	Dual 4 I/P OR/NOR gate	2.17	1.86	1.55
SP1085B	Dual 4 I/P OR/NOR gate	2.17	1.86	1.55
SP1086B	Dual 4 I/P OR/NOR gate	2.17	1.86	1.55
SP1087B	Triple 3 I/P NOR gate	1.71	1.48	1.25
SP1088B	Triple 3 I/P NOR gate	1.71	1.48	1.25
SP1089B	Triple 3 I/P NOR gate	1.71	1.48	1.25
SP1090B	Dual 2 I/P NOR gate	1.71	1.48	1.25
SP1091B	Dual 2 I/P NOR gate	1.71	1.48	1.25
SP1092B	Dual 2 I/P NOR gate	1.71	1.48	1.25
SP1093B	Dual 2 I/P NOR gate	1.71	1.48	1.25
SP1094B	Dual 2 I/P NOR gate	1.71	1.48	1.25
SP1095B	Dual 2 I/P NOR gate	1.71	1.48	1.25
SP1096B	Dual 2 I/P NOR gate	1.71	1.48	1.25
SP1097B	Triple 3 I/P NOR gate	1.71	1.48	1.25
SP1098B	Triple 3 I/P NOR gate	1.71	1.48	1.25
SP1099B	Triple 3 I/P NOR gate	1.71	1.48	1.25
SP1100B	Dual 4 I/P OR/NOR gate	2.17	1.86	1.55
SP1101B	Dual 4 I/P OR/NOR gate	2.17	1.86	1.55
SP1102B	Dual 4 I/P OR/NOR gate	2.17	1.86	1.55
SP1103B	Dual 4 I/P OR/NOR gate	2.17	1.86	1.55
SP1104B	Dual 4 I/P OR/NOR gate	2.17	1.86	1.55
SP1105B	Dual 4 I/P OR/NOR gate	2.17	1.86	1.55
SP1106B	Dual 4 I/P OR/NOR gate	2.17	1.86	1.55
SP1107B	Triple 3 I/P NOR gate			

COAX CONNECTOR KITS . . . BY MAIL.

Finest quality. Solderless. Made by AMP . . . the world's foremost name in connectors and application tooling of all types. Kits assembled by AMP Special Industries, especially for R&D lab technicians, maintenance personnel, and other communications installation and repair people. Three different kits, each with its own crimping tool and supply of connectors in a sturdy metal box. Connectors may be reordered by mail as required. Total satisfaction, or money instantly refunded at any time. An unbeatable value!



Specify quantity of each kit by kit number. Send check, purchase order or BankAmericard number. Be sure to include applicable sales tax. Postpaid. Free catalog with each order or circle Reader Service Number.

KIT NUMBER	TYPE	PRICE
1-601834-0	BNC for RG-58 Cable (Tool + 20 connectors)	\$49.95
1-601834-3	BNC for RG-59 Cable (Tool + 20 connectors)	\$49.95
1-601834-6	UHF for RG-58, RG-59 Cable (Tool + 25 connectors)	\$49.95



AMP SPECIAL INDUSTRIES

Division of AMP Products Corporation
Valley Forge, Pa. 19482
A subsidiary of AMP Incorporated.

Circle 88 on reader service card

COMPARE OUR PRICES WITH OTHERS!

CLOCK CHIPS

MM 5314	\$3.50
MM 5316	\$4.00
CT 7001	\$6.50

MEMORIES

1103A	1024 bit RAM MOS	\$2.20
2101-2	1024 bit 650 US	\$4.00
8080	COMPUTER ON CHIP	\$120.00

HP 0.3"	7 SEGMENTS LED DISPLAYS	\$1.60
---------	-------------------------	--------

FAIRCHILD FND70 0.275"	7 SEGMENT DISPLAYS	\$1.00
------------------------	--------------------	--------

DL 747 0.6"	DISPLAY	\$2.60
DL 707 0.3"	DISPLAY	\$2.00

ALSO IN STOCK—ALL TYPES OF CMOS, TTL, IC, TRANSISTORS, CAPACITORS, RESISTORS, DIODES, SCR AND TRIAC AT THE LOWEST PRICES!

MAIL ORDER ACCEPTED

FORMULA INTERNATIONAL INC.

12603 CRENSHAW BLVD.,
HAWTHORNE, CA. 90250

For Information PLEASE CALL
(213) 679-5162

Circle 95 on reader service card

ADVERTISING INDEX

RADIO-ELECTRONICS does not assume responsibility for any errors which may appear in the index below.

READER SERVICE CARD NO.	PAGE
74	A.D.R. Audio 88
21	Allison Automotive 68
10	Alpha Electronics 17
28	Audio Amateur 73
80	Basix 92
14,15,16,17,18,19	B & K Division of Dynacorn Corp. 26, 27
	Bell & Howell Schools 18-21
79	Brooks Radio & TV Corp. 91
87	Castle TV Tuner Service Corp. Cover IV
20	CIE, Cleveland Institute of Electronics 64-67
7	Continental Specialties Corp. 14
	CREI, Division of McGraw-Hill Continuing Education Center 46-49
78	Data Precision Corp. 90
29	Delta Products Corp. 73
65	EDI, Electronic Distributors Inc. 80
63	Edlie Electronics 77
12, 85	Edmund Scientific 25, 108
64	EICO, Electronic Instrument, Inc. 80
62	Elenco Electronics Inc. 76
22	Elpa Marketing 69
	EMC, Electronics Measurement Corp. 89
13	Enterprise Development Corp. 24
77	Fluke 89
83	Fordham Radio Supply Co. 94
	GC Electronics 95
	General Electric Co., Tube Div. 79
82	Grantham School of Electronics 93
	GTE Sylvania Electronic Components 32
100	Heath Co. 23
9	Hickok Electrical Co. 16
	ICS, International Correspondence Schools 28-31
72	Indiana Home Study Institute 87
61	International Crystal Mfg. Co. 75
81	Jensen Tools & Alloys 92
86	Jerrold Electronics Cover III
75	Labtronics, Inc. 88
67	Leader 81
4	Mallory Distributor Co. 5
2	MTS, Micro-Instrumentation Telemetry Systems, Inc. 1
66	MTI, Motorola Training Institute 80
26	Mountain West Alarm Supply Co. 72
27	National Camera Co. 72
	National Technical Schools 82-85
	NRI Schools, Division of McGraw-Hill Continuing Education Center 8-11
71	PAIA Electronics 87
84	Polaris, NY 96
1	PTS Electronics Cover II
5	Radio Shack 7
8	RCA Solid State Division 15
11	Regmo Data Corp. 22
70	RGS Electronics 86
	Scelbi Computer Consulting, Inc. 94
68	Schober Organ 81
30	Scorcere 74
3	Shure Bros. 2
23	Southwest Technical Products 70
76	Telematic 88
73, 90	Tektronix, Inc. 87
24	Teletronics Company of America 71
69	Tri-Star 86
	Vintage Radio 96
25	Vu-Data Corp. 71
6	Weller-Xcelite Electronics Division 13
	MARKET CENTER
	READER SERVICE CARD NO. PAGE
	AMC Sales 100
88	AMP Special Industries 106
89, 91	Anconra Corp. 105, 107
	ATV Research 106
92	Babylon Electronics 104
	Command Productions 97
93	Delta Electronics 104
94	Digi-Key 97
	Fair Radio Sales 100
95	Formula International, Inc. 106
96	Bill Godbout Electronics 104
	Gunmaster 106
97	International Electronics Unlimited 103
98	James Electronics 98
	Lakeside Industries 97
	Lesco Electronics 106
101	Meshna Electronics, John Jr. 100
99	New-Tone Electronics 102
105	Photolum Corp. 102
102, 103	Poly Paks 99, 101
104	Processor Technology Co. 102
	Saxitone Tape Sales 106
	Solid State Sales 100
	Trumbull 100
106	West Pacific Electronics 102

500-MHz prescaler assembled and tested complete with cabinet and power supply \$99.95. 200-MHz counter kit less cabinet \$139.95. DAVIS ELECTRONICS, 636 Sheridan Dr., Tonawanda, NY 14150. (716) 879-5848-9

CASSETTES

Plain white cassette labels. Norelco cassette cleaners, famous brand cassettes. Send for open reel and cassette discount catalog.

1-9	10-99	100	1000	10M
Cassette Labels (Multiples of 10)	.02	.015	.01	.006
Norelco Cassette Cleaner	.65	.60	.55	.50
*Scotch Cassette SC90HE	2.72	2.55	2.44	

*Buy 10, SC90HE, get 5 free.
Plus Postage by Weight and Zone. Minimum Order \$5.00

OPEN REEL STEREO TAPE BUYERS!

At last! An open reel catalog, including titles, songs, etc. of 95 long play, 2-3 hour albums by American Airlines or Ampex 4 track stereo tapes. Send \$1.00—and we will also mail you a 140-page Harrison stereo tape guide—so you'll get both for \$1.00—and this \$1.00 is refundable on your first \$10.00 purchase of open reel stereo tapes at our 30% discount.

We've Got the "Spirit" The Prices And The Address To Prove It

Saxitone's Bicentennial Tape Shoppe
1776 Columbia Rd., N.W., Wash. D.C. 20009

BUILD YOUR OWN TV CAMERA! — Ideal for home & business —

THE ECONOMICAL ANSWER TO HOME MONITORING OF NURSERIES, ENTRANCES, DRIVEWAYS, BUSINESS and INDUSTRIAL SURVEILLANCE. TV AMATEUR TV PLUS HUNDREDS OF OTHER APPLICATIONS. MODEL XT-1A, SERIES D - KIT FORM \$185 ASSEMBLED \$275. SOLID-STATE WORKS ON ANY TV SET. OPTIONAL SOUND KIT \$29.95. PHONE or WRITE for catalog. Dial 402-987-3771

BOX 453-RE ATV Research DAKOTA CITY, NE 68731

MOSTEK MK50250 "beeper" alarm clock IC \$5.95—Jumbo 0.6" 747 LED display \$1.95—0.33" 707 display 85¢—Complete clock kits including power supply and PC boards available. All new, guaranteed parts. Catalog 25¢, redeemable. DIAMONDBACK ENGINEERING, PO Box 194, Spring Valley, IL 61362

INTEL 8080, 8-bit CPU: \$155. Intel 8008, 8-bit CPU: \$26.50. MM5203Q-1, 2K bit EPROM: \$12.50. 2102-2, 1K RAM: \$4.50. AY5-1008, TTY terminal RX: \$5.50. AY5-1010, TTY terminal TX: \$5.50. AY5-2376, 9-bit KYBD ENCOD: \$9.50. XR205, function generator: \$10.50. XR210, FSK mod/demod: \$6.00. XR2240, Prog. timer: \$4.75. SP425-09, 9-digit display: \$2.50. VA210C, 10-GHz Klystron: \$30.00. Main & Memory PCB. (TVT-II): \$39.50. Catalog 10¢. ELECTRONIC DISCOUNT SALES, Dept. RE, 138 N. 81st, Mesa, AZ 85207

ELECTRONIC ignitions—Mark 10B \$36.95. Tri-Star: SST—\$27.95, 500—\$33.95. Satisfaction guaranteed. G.E.E. SALES, 12525 SE 188th Pl., Renton, WA 98055

A NEW INSTRUMENT TO USE WITH YOUR SCOPE



MULTITRACER

Use with your present Oscilloscope to trace Resistors, Capacitors, Transformers, Diodes, Transistors, Zeners, Triodes, most Semiconductors, IC's, etc. Also shows continuity of circuit and pin-to-pin checks. Complete with diagrams and instructions. No internal scope connections. For medium or small production runs or for biologist, experimenter, engineer, or hobbyist.

ONLY \$19.95—CHECK OR MONEY ORDER
WAY #58-109E

BOX 14, LESCO ELECTRONICS, SKOKIE, ILL. 60076

SOLDERING IRON USERS NEW! SAME SOLDER TIP

• SOLDERS • DESOLDERS • RESOLDERS

EXCELLENT FOR P.C. WORK

Type A 1/8" dia., 6-32 threads	\$1.98
Type F 3/8" dia., Plug Type Tip	2.13
Type H 1/4" dia., Plug Type Tip	2.28

GUNMASTER, Box 743, Kings Park, N.Y. 11754

ELECTRONIC parts! New! Solid State devices. Free flyer: DARTEK ELECTRONICS, Box 2460, Dartmouth, Nova Scotia, Canada U.S. inquiries



The American
Red Cross.
The Good
Neighbor.

C-MOS

4000AE	.26	.25
4001AE	.26	.25
4002AE	.26	.25
4004AE	5.83	5.82
4006AE	1.36	1.34
4007AE	.26	.25
4008AE	1.79	1.78
4009AE	.60	.59
4010AE	.59	.58
4011AE	.26	.25
4012AE	.26	.25
4013AE	.47	.46
4014AE	1.49	1.48
4015AE	1.26	1.25
4016AE	.56	.55
4017AE	1.20	1.19
4018AE	1.49	1.48
4019AE	.52	.51
4020AE	1.49	1.48
4021AE	1.34	1.33
4022AE	1.11	1.10
4023AE	.26	.25
4024AE	.90	.89
4025AE	.26	.25
4026AE	3.72	3.70
4027AE	.60	.59
4028AE	.98	.97
4029AE	1.27	1.26
4030AE	.44	.43
4031AE	3.01	3.00
4035AE	1.27	1.26
4040AE	1.49	1.48
4041AE	4.06	4.05
4042AE	.75	.74
4043AE	.60	.59
4044AE	.60	.59
4047AE	3.84	3.83
4048AE	1.43	1.42
4049AE	.52	.51
4050AE	.52	.51
4051AE	1.34	1.33
4052AE	1.34	1.33
4053AE	1.34	1.33
4055AE	2.68	2.58
4056AE	3.43	3.39
4060AE	1.50	1.49
4066AE	.90	.89
4069AE	.78	.77
4071AE	.26	.25
4076AE	1.68	1.48
4081AE	.26	.25
4508AE	2.30	2.20
4510AE	1.98	1.78
4516AE	2.30	2.20
4518AE	3.28	2.98
4520AE	1.88	1.68
4528AE	2.30	2.20
4901AE	.43	.36
4911AE	.43	.36



7400N TTL

7400N	\$.14	7444N	\$1.05	7496N	\$.85	74161N	1.28
7401N	.17	7445N	.93	74100N	1.30	74162N	1.50
7402N	.14	7446N	1.10	74104N	1.25	74163N	1.48
7403N	.17	7447N	.88	74105N	.45	74164N	1.22
7404N	.20	7448N	1.00	74107N	.40	74165N	1.78
7405N	.20	7450N	1.55	74109N	.75	74166N	1.50
7406N	.30	7451N	.20	74110N	.72	74170N	2.50
7407N	.30	7453N	.20	74111N	.92	74173N	1.66
7408N	.18	7454N	.26	74114N	.92	74174N	1.20
7409N	.22	7455N	.37	74115N	.92	74175N	1.60
7410N	.18	7460N	.25	74118N	1.51	74176N	1.30
7411N	.27	7462N	.37	74121N	.37	74177N	1.50
7412N	.52	7464N	.37	74122N	.37	74180N	.73
7413N	.65	7465N	.37	74123N	.90	74181N	3.20
7414N	.18	7470N	.30	74125N	.48	74182N	.75
7415N	.37	7471N	.49	74126N	.64	74184N	2.90
7416N	.22	7472N	.32	74128N	.94	74185N	2.29
7417N	.34	7473N	.38	74132N	1.74	74188N	4.90
7418N	.17	7474N	.33	74136N	.92	74190N	1.49
7419N	.60	7475N	.60	74140N	2.50	74191N	1.20
7420N	.27	7476N	.33	74141N	1.19	74192N	1.40
7421N	.48	7477N	.55	74145N	1.08	74193N	1.00
7422N	.48	7478N	.56	74147N	2.35	74194N	1.35
7423N	.34	7480N	.60	74148N	2.20	74195N	.80
7424N	.25	7481N	1.19	74150N	.99	74196N	1.90
7425N	.31	7482N	.90	74151N	.75	74197N	.80
7426N	.52	7483N	.65	74152N	1.50	74198N	2.00
7427N	.74	7484N	2.50	74153N	1.05	74199N	2.09
7428N	.62	7486N	.36	74154N	1.48	74200N	5.90
7429N	.36	7489N	2.40	74155N	1.08	74221N	1.75
7430N	.35	7490N	.54	74156N	1.18	74251N	1.95
7431N	.39	7491N	1.00	74157N	1.18	74278N	2.95
7432N	.16	7492N	.61	74158N	1.44	74279N	.95
7433N	.98	7493N	.50	74160N	1.50	74293N	8.00
7434N	.69	7494N	1.20			7552-2CPE	8.00
7435N	.95	7495N	.80				

DECODED READ/WRITE RAM

P1103 \$6.20

SCHOTTKY TTL

74500N	.45	74574N	1.30	745158N	2.40	745160N	4.70
74502N	.80	74585N	6.10	745174N	3.30	745161N	4.70
74503N	.75	74586N	2.70	745175N	3.30	745162N	5.10
74504N	.75	745112N	2.20	745181N	10.20	745163N	5.10
74508N	.80	745133N	1.50	745189N	5.10	745164N	3.30
74510N	.85	745133N	3.60	745194N	3.30	745165N	3.30
74511N	.65	745133N	.90	745195N	3.30	745166N	2.40
74520N	.80	745138N	2.40	745215N	2.40	745167N	2.40
74530N	.80	745139N	2.40	745253N	2.40	745168N	2.40
74532N	.80	745140N	.90	745257N	2.40	745169N	2.40
74540N	.80	745151N	2.40	745258N	2.40	745170N	2.40
74551N	.80	745153N	2.40	745260N	.90	745171N	2.40
74564N	.80	745187N	2.40	745280N	5.70		

LOW POWER TTL

74L00N	.34	74H00N	.34	74H53N	.36
74L02N	.34	74H02N	.25	74H54N	.36
74L03N	.39	74H03N	.30	74H55N	.36
74L04N	.39	74H04N	.38	74H60N	.36
74L10N	.34	74H05N	.37	74H61N	.36
74L20N	.39	74H08N	.40	74H62N	.36
74L42N	1.62	74H10N	.36	74H71N	.80
74L51N	.34	74H11N	.36	74H72N	.74
74L73N	.74	74H20N	.36	74H73N	.90
74L74N	.89	74H21N	.36	74H74N	.87
74L90N	1.62	74H30N	.36	74H101N	.80
74L93N	1.74	74H40N	.36	74H102N	.80
74L95N	1.62	74H50N	.36	74H103N	1.10
93L00	1.50	74H61N	.36	74H106N	.98
93L01	1.60	74H52N	.36		
93L08	3.20				
93L09	1.80				
93L10	2.80				
93L11	4.20				
93L12	1.80				
93L14	1.70				
93L16	3.20				
93L18	3.50				
93L21	1.50				
93L22	1.80				
93L24	2.80				
93L28	3.70				
93L34	4.00				
93L38	4.20				
93L40	6.50				
93L41	6.50				
93L60	3.00				
93L66	2.70				

BIPOLAR MEMORY

C3101	6.50
P3101	4.90
C3101A	7.30
P3101A	6.90
IM5501CDE	7.30
IM5501CPE	5.80
MM5560N	5.80
DM8999N	5.80
93403PC	6.80
1506	4.00
1507	4.00
1602	33.00
1702	33.00
C2102	8.00
P2102	4.95

TWO-PHASE MOS CLOCK DRIVER

MM0026CN \$8.50

COMPUTER INTERFACE

DM8820N	2.40
DM8820AN	6.90
DM8830N	2.40
DM8831N	5.20
DM8832N	6.00
N8726B	4.40
9600PC	1.30
9601PC	1.20
9602PC	2.10
9614PC	2.30
9615PC	2.40
9616DC	4.40
9617PC	3.50
9620PC	4.00
9621PC	4.00

PULSE GENERATOR

Interdesign 1101: 0.1Hz-2MHz, 0.5V Output, var. width, line or battery operation. \$159.00

WAVEFORM GENERATOR

XR205K KIT Only \$25.00
Here's a highly versatile lab instrument at a fraction of the cost of conventional units. Kit includes two XR205 IC's, date & application, PC board, etched & drilled, ready for assembly) and detailed instructions.

DUAL LOW NOISE OP AMP

LM331N: $V_{io} = 6mV$, $I_{io} = 1000 nA$, $I_{sp} = 1.5dB$, \$2.20

DISPLAYS

OPCA	
SLA1	Red 2.25
SLA11	Green 3.50
SLA21	Yellow 3.50
DL87	Red 1.60
LITRONIX	
DL80	Red 6.00
DL81	Red 6.00
DL10	Red 6.00
DL10A	Red 4.00
DL101	Red 4.90
DL57	Red 9.90
DL61	Red 12.00
DL33	Red 4.00
DL44	Red 6.00
DL402	Red 4.00
DL701	Red 3.40
DL704	Red 2.25
DL707	Red 2.35
DL747	Red 2.50
XCITON	
XAN72	Red 2.00
XAN52	Green 2.00



CALCULATORS (Limited Qty.) \$19.00

1024-BIT N-Channel RAM

2601-1	11.40
2601-21	11.40
2602B	8.00
2602-18	8.00
2602-28	8.00
MK4102P	11.40
7552-1CPE	8.00
7552-2CPE	8.00

LEDs

EP 9125	
8-DIGIT DISPLAY	\$7.90
1/8" character height	
compact, thin PC package	
wide viewing angle	
MONSANTO	
MCT2	1.35
LITRONIX	
IL1	1.30
IL12	1.40
IL16	1.80
IL74	1.38
ILD74	1.75
ILD74	3.40



209 Red	\$.25
209 Yellow	.35
209 Green	.35
216 Red	.28
216 Yellow	.30
216 Green	.30
220 Red	.26
220 Yellow	.30
220 Green	.30
226 Red	\$.25
226 Yellow	.30
226 Green	.30
226 Orange	.30
5053 Yellow	.35
5053 Green	.40
5053 Orange	.40
216 = MV5024	
5053 = MV5053	
MV50 Red	\$.30

1-AMP RECTIFIERS

1N4001	1.00	7.00	60.00
1N4002	1.10	8.00	70.00
1N4003	1.20	9.00	80.00
1N4004	1.30	10.00	90.00
1N4005	1.40	11.00	100.00
1N4006	1.50	12.00	110.00
1N4007	1.60	13.00	120.00

PHASE-LOCKED LOOPS

LM567CM Mini-dip .80

PREMIUM QUALITY COMPONENTS

We've been buying and selling top quality components for nearly ten years. Our annual volume exceeds \$3 million. We handle only original parts, from the world's leading manufacturers and our customers include some of the largest and most quality-conscious companies. Now you can take advantage of our component buying skills and power and select from a broad range of advanced circuits.



AUDIO AMPS

Type	V	W	Ω	Price
LM352	6-15	1.15	8	1.60
LM354A	6-27	2.80	8	2.50
TA6611B12	6-15	1.15	8	1.60
TA6621A12	6-27	2.80	8	2.00
TBA641B11	6-18	2.20	4	3.00
TBA800	5-30	4.70	8	2.20
TBA810AS	4-20	2.50	4	3.00
TBA820	3-16	0.75	17	0
TCA830	5-20	2.00	4	2.20
TCA940				

LIVE IN THE WORLD OF TOMORROW... TODAY!

And our FREE 180 PAGE CATALOG is packed with exciting and unusual values in electronic, hobby and science items — plus 4,500 finds for fun, study or profit... for every member of the family.

A BETTER LIFE STARTS HERE

3-CHANNEL COLOR ORGAN KIT

Easy to build low-cost kit needs no technical knowledge. Completed unit has 3 bands of audio frequencies to modulate 3 independent strings of colored lamps (i.e. "lows"-reds, "middles"-greens, "highs"-blues. Just connect hi-fi, radio, power lamp etc. & plug ea. lamp string into own channel (max. 300w ea.) Kit features 3 neon indicators, color intensity controls, controlled individ SCR circuits; isolation transformer; custom plastic housing; instructions.



Stock No. 41,831 EH \$18.95 Ppd.

AM RADIO FITS IN/ON YOUR EAR!

Wear it inconspicuously everywhere, listen as you work (lawn, yard, office), watch (game, beach) or wait. Instant music, news, sports. No gimmick — 6/10 oz. technological wonder w/integrated circuit, 11 transistors, patented ferrite antenna/tuner/volume dial. Works best outdoors. Uses hearing aid batt. (incl)—up to 100 hrs. playing. New batt. to slip in avail. at drug stores (about 50¢). No lengthy wires, bulky cases, or power-packed!



Stock No. 42,275 EH \$14.95 Ppd.

PRO ELECTRONIC SOUND CATCHER

Parabolic mike w/18 3/4" reflecting shield & 2 i.c.'s in amplifier magnifies signals 100X that of omni-directional mikes. Catch a songbird 1/2 mile off; QB's huddle strategy; sounds never before heard. Super directivity gives highest signal to noise ratio poss. Safe: auto. cuts off ear damaging noises. Earphones, tape recorder output, tripod socket. Req. two 9v trans. batt. (not incl).



No. 1649 EH (5 1/2 LB.) \$299.00 Ppd.
BIG EAR "TOY" MODEL # 80,176 EH \$32.25 Ppd.

AN ALPHA MONITOR FOR \$34.95?

Yes, because you built it! Use your ability to tune in your brainwaves, an aid to relaxation, concentration. Kit incl. everything you need (except 9v trans. batt.) to own a portable self-cont. BIOFEEDBACK unit for a pittance: steth. earphones, electrode headband, solid-state circuitry; 5 microvolt sensitivity, more! Compl. assembly instructions & op. manual. With basic electronics knowledge, you can do it!



No. 61,069 EH (KIT) \$34.95 Ppd.
No. 71,809 EH (FULLY ASSEMBLED) \$55.00 Ppd.

WHEN YOU COME TO PHILADELPHIA, BE SURE TO SEE
FREE BICENTENNIAL LIGHT SHOW
IN BARRINGTON, N.J. ONLY 10 MINUTES AWAY AT
EDMUND FACTORY STORE

RUN A WORKING STEAM ROLLER!



Authentic English hand-crafted model made of heavy-gauge metal, powered by steam so you can run it forward, backward, regulate speed, pull other models, lock roller and run engine independently. Just set steering or use the 12" extension steering rod and drive it yourself! The fun even can power the mighty whistle. To run, fill the safe vaporizing spirit lamp w/wood alcohol (not incl).

No. 71,934 EH (4 lb.; 10 1/4x6x7") \$35.00 Ppd.

TOTAL KIRLIAN PHOTOGRAPHY SET



Explore "aura" photography w/ superb new self-contained Kirlian Electrophotography Research Unit. Terrific value — introduced at \$99.95 (\$140 in Sept.)! Has everything but vinyl photo changing bag. Ideal for color or b&w 35mm, sheet or Polaroid film for photos up to 5x7" all without camera or lens. Variable voltage 12v to 32kv. Ultimate safety design—fully encased in plastic; patented electronics. Instrs.

No. 72,104 EH (3x5 1/4x7 1/4") \$99.95 Ppd.
No. 42,240 EH (CHANGING BAG) \$6.50 Ppd.

LOW COST 7X INFRARED VIEWER



For Infra-red crime detection surveillance, security system alignment, I.R. Detection, laser checking, nite wildlife study, any work req. I.R. detection & conv. to visible spectrum. Self cont. scope w/everything incl. I.R. light source. 6v or 12v power, 6032 I.R. converter tube, f/4.5 objective lens, adjust. triplet eyepiece. Focuses from 10' to infinity.

No. 1659 EH (11x14 1/4x3") \$275.00 Ppd.
WITHOUT LIGHT SOURCE
No. 1648 EH \$225.00 Ppd.

SUPER POWER FOR ANY AM RADIO



New antenna assist turns a tiny transistor into a tiger, has pulled in stations 1000 miles away! Just set it beside your radio (no wires, clips, grounding) and fine-tune Select-A-Tenna's dial to same frequency — "Gangbusters"! Terrific for sportsmen, vacationers. Great for clearing weak signals in radio depressed areas, off-coast islands, stations in crowded frequencies. Solid state—uses no electricity, batts., tubes. Works almost forever.

Stock No. 72,095 EH \$15.95 Ppd.

ELECTRONIC DIGITAL STOPWATCH: \$69.95



A price breakthrough! New pocket size 4 oz. timer acc. to ± 2% of last digit (1/100 sec. increments). Compares with others twice the price! Instant error-free read-outs to 9999.99 sec. (over 2 1/4 hr.). Starts, stops, re-starts (accumulates).

Mechanical pushbutton & electrical remote on/off w/ any 3.5-150v AC/DC source. Plug-in jack. Incls. 9v batt. Solid state.
No. 1943 EH (2 1/4x4 1/2x7 1/8") \$69.95 Ppd.
DELUXE 2 EVENT STOPWATCH (± 0.01% OF LAST DIGIT)
No. 1653 EH (PRICE UP IN SEPT.!) \$120.00 Ppd.



MAIL COUPON FOR GIANT FREE CATALOG!

180 PAGES • MORE THAN
4500 UNUSUAL BARGAINS

Completely new 1975 edition. New items, categories, illustrations. Dozens of electrical and electromagnetic parts, accessories. Enormous selection of Astronomical Telescopes. Unique lighting and ecological items. Microscopes, Binoculars, Magnifiers, Magnets, Lenses, Prisms. Hard-to-get surplus bargains. Ingenious scientific tools. 1000's of components.

EDMUND SCIENTIFIC CO.
300 Edscorp Building, Barrington, N.J. 08007
Please rush Free Giant Catalog "EH".

Name _____
Address _____
City _____ State _____ Zip _____




COMPLETE AND MAIL WITH CHECK, M. O. OR CHARGE NO.
EDMUND SCIENTIFIC CO. 300 Edscorp Building, Barrington, N.J. 08007

How Many	Stock No.	Description	Price Each	Total
<input type="checkbox"/>		PLEASE SEND GIANT FREE CATALOG "EH"		
<input type="checkbox"/>		Charge my BankAmericard *		
<input type="checkbox"/>		Charge my Master Charge *		
Add Handling Chg.: \$1.00, Orders Under \$5.00 50¢, Orders Over \$5.00				
Interbank No. <input type="text"/>				
My Card No. Is <input type="text"/>				
I enclose <input type="checkbox"/> check <input type="checkbox"/> money order for TOTAL \$ <input type="text"/>				
Card Expiration Date _____ Signature _____				

30-DAY MONEY-BACK GUARANTEE. Name _____
You must be satisfied or return Address _____
any purchase in 30 days for full refund. *\$15.00 minimum City _____ State _____ Zip _____

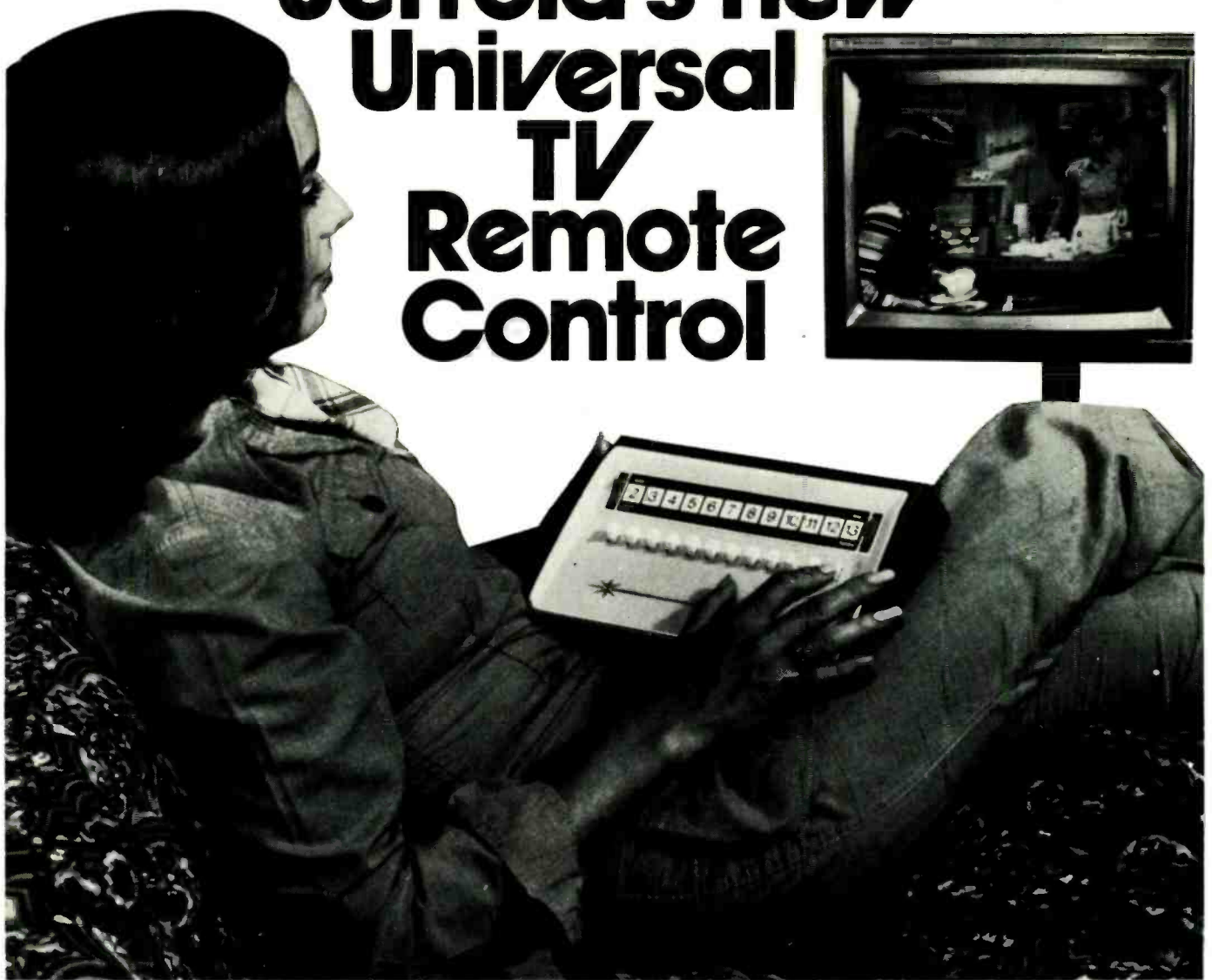Jerrold's new Universal TV Remote Control



The Hottest New Product Since The Calculator...

Makes every set on your floor a remote control model

Universal— Attaches to any set in minutes

Changes channel instantly and fine tunes

Turns set on/off

Silent push-button varactor— diode tuning— 12 channels

Amplifies signal and eliminates direct pick up ghosts

For homes, apartments, bars, hotels/motels, schools, hospitals and nursing homes.

Packaged in a sturdy, colorful, self-selling carton



JERROLD



a GENERAL INSTRUMENT company

HEADQUARTERS & EASTERN OFFICE 200 Witmer Rd., Horsham, Penna. 19044, (215) 674-4800

SOUTHERN OFFICE 1 Perimeter Place, Suite 101, Atlanta, Georgia 30339, (404) 432-3102

WESTERN OFFICE 1255 Veterans Blvd., Redwood City, Calif. 94063, (415) 365-5050

MIDWESTERN OFFICE 1334 Atlantic Street, North Kansas City, Mo. 64116, (816) 842-1555

Circle 86 on reader service card



The Tuner People

Pioneers of TV Tuner Overhauling Originators of Complete TV Tuner Service

Castle offers the following services to solve ALL your television tuner problems.

Universal Replacements from \$8.95

These universal replacement tuners are all equipped with memory fine tuning and uhf position with plug input for uhf tuner. They come complete with hardware and component kit to adapt for use in thousands of popular TV receivers.

STOCK No.	HEATERS	SHAFT		I.F. Snd.	PRICE
		Min.*	Max.*		
CR6P	Parallel 6.3v	1 3/4"	3"	41.25	8.95
CR7S	Series 600mA	1 3/4"	3"	41.25	9.50
CR9S	Series 450mA	1 3/4"	3"	41.25	9.50
CR6XL	Parallel 6.3v	2 1/2"	12"	41.25	10.45
CR7XL	Series 600mA	2 1/2"	12"	41.25	11.00
CR9XL	Series 450mA	2 1/2"	12"	41.25	11.00

Castle Replacements

\$15.95

Castle custom replacements made to fit in place of original tuner. Purchase outright . . . no exchange needed. Write for current list of Castle replacements, or request the part number you require (use number on ORIGINAL TUNER ONLY; do not use service literature numbers). Available for many of the popular models of following manufacturers: Admiral, Curtis Mathes, Emerson, GE, Heathkit, Magnavox, Motorola, Muntz, Philco, RCA, Sears, Sylvania, Westinghouse, Zenith and many private labels.

Overhaul Service

\$9.95

This is the service pioneered by Castle! We are now in our third decade of serving the TV Service Industry

Service on all makes and models, vhf or uhf, including transistor and color tuners . . . one price \$9.95 Overhaul includes parts, except tubes and transistors.

Remember!

Castle overhaul service is as near as your post office

Simply send us the defective tuner complete; include tubes, shield cover and any damaged parts with model number and complaint. Your tuner will be expertly overhauled and returned promptly, performance restored, aligned to original standards and warranted for 90 days.

Dismantle tandem uhf and vhf tuners and send in defective unit only. Remove all accessories . . . or dismantling charge will apply.

Custom Exchange Service

\$17.95

When our inspection reveals that original tuner is unfit for overhaul, and it is not available from our stock of outright replacements, we offer to make a custom replacement on exchange basis. Charge for this service is \$15.95 for uhf tuner and \$17.95 for vhf tuner.

If custom replacement cannot be made we will custom rebuild the original tuner at the exchange replacement price.

All replacements are new or rebuilt. All prices are f.o.b. our plant. Add shipping and handling of \$1.25 on all prepaid orders. We will ship C.O.D.

CASTLE TV TUNER SERVICE, INC.

5715 N. Western Ave., Chicago, Ill. 60645 • Ph. 312-561-6354

Circle 87 on reader service card

