

48783

# Radio - BUILD A HI-TECH X-MAS TREE

\$2.25 DEC. 1987  
IN CANADA \$2.75

# Electronics®

TECHNOLOGY - VIDEO - STEREO - COMPUTERS - SERVICE

## BUILD A DIGITAL IC TESTER

COMPUTERIZED TESTER WORKS  
IN OR OUT OF CIRCUIT

## THE EARLY DAYS OF RADIO

A NOSTALGIC LOOK AT  
IMPROVEMENTS IN AUDIO

## ANALYZING WAVEFORMS

THE RIGHT WAY TO USE  
AN OSCILLOSCOPE

## STRAIN-GAGE TRANSDUCERS

THE THEORY YOU NEED TO  
PUT THEM TO WORK

## COMPUTERDIGEST

FLOPPY-DISK DATA STORAGE  
BUILD A 68000-BASED COMPUTER

# CLEAN UP THE MACROVISION MESS

## REMOVE COPY PROTECTION FROM VIDEO CASSETTES FOR A BETTER PICTURE



A  
**GERNSBACK**  
PUBLICATION

# NEW FROM TEK AT JUST \$995!

**Light weight** makes the 2225 easy to carry even to remote servicing sites.


**Fully segmented graticule lines** ease the way for quick, accurate voltage and time measurements.

**Bright, full-size CRT** with minimal geometric distortion and crisp, small spot size delivers sharp trace definition.

**One-button beam finder** locates off-screen signals, even when intensity is turned down.

**Proven design and rugged construction** offer reliability at its best. And the Tek reputation for meeting rigid environmental requirements means confidence in your measurements—and in knowing that his scope is built to last.

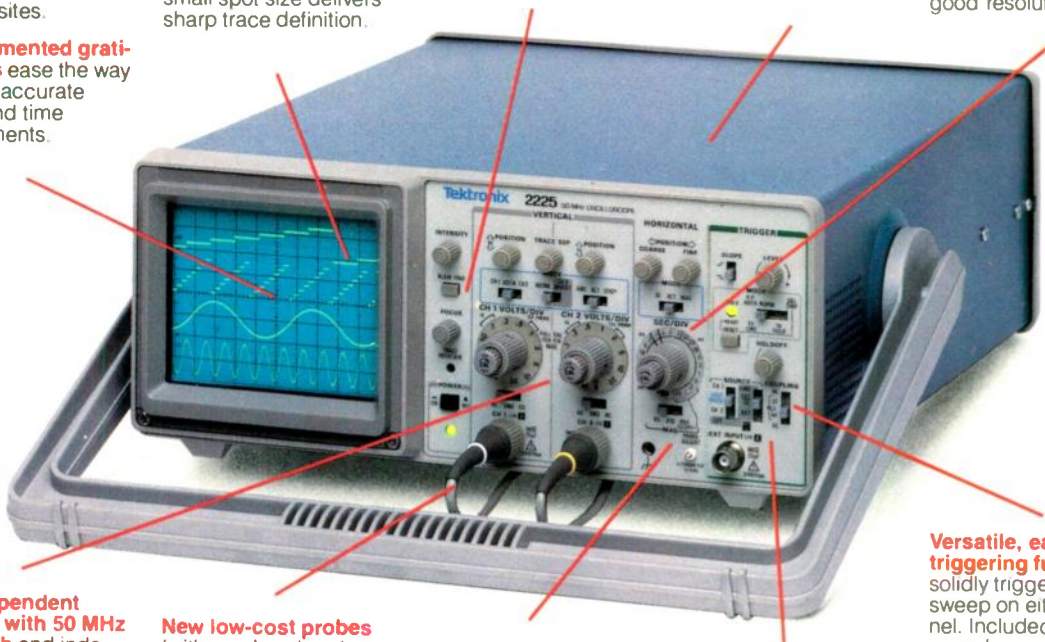**Sweep speeds to 5 ns/div** are fast enough for making accurate pulse and timing measurements on most digital logic families, with good resolution.



**Two independent channels with 50 MHz bandwidth** and independent bandwidth limiting on each channel to 5 MHz, 500  $\mu$ V/div sensitivity for low-level signal measurements and differential applications.

**New low-cost probes** (with nearly unbreakable tips) complement the rugged scope design. Compensation adjustments in the probe body itself eliminate the bulky compensation box at the front panel. Scope and probes are a perfect match!

**Fast, accurate alternate horizontal magnification** lets you choose any of three expansion levels to magnify any part of the normal waveform display—including the trigger point and end of sweep.

**Now for the first time! Two vertical-channel inputs and an external Z-axis input all on the front panel.** An excellent combination for manufacturing test stations and rackmount applications. And at the simple flip of a switch you can trigger on the Z-axis signal.

**Versatile, easy-to-use triggering functions** solidly trigger the sweep on either channel. Included are asynchronous triggering capability; flexible coupling via DC, AC, HF and LF reject filtering; hands-free triggering from virtually any signal; plus independent selection of either TV line or TV field triggering regardless of time-base setting.

**Now, the professional quality and performance you expect from Tektronix... at an unexpected price: \$995 for scope, probes, 3-year warranty and 30-day free trial on approved credit.** No portable in its class can match the Tek 2225 for features, versatility, convenience and value. It's the easy, economical answer to scope needs at bench and field sites, on the manufacturing floor and in the classroom. Call Tek to order, for application assistance or to get the name of your nearest Tek representative or distributor.



Call Tek direct: 1-800-426-2200



**Tektronix**  
COMMITTED TO EXCELLENCE

# December 1987 **Radio Electronics**

Vol. 58 No. 12

## BUILD THIS

- 47 ELECTRONIC CHRISTMAS TREE**  
Blinking LED's make this a unique holiday decoration.  
**Thomas L. Jozwiak**
- 49 MACROVISION STABILIZER**  
Clean up your VCR's picture.  
**D. Dupre**
- 55 IN-CIRCUIT DIGITAL-IC TESTER**  
Part 2. Build the tester and put it to work.  
**Bill Green**
- 67 R-E ROBOT**  
Part 12. An electronic eye.  
**Steven E. Sarns**
- 69 PC SERVICE**  
Foil patterns for Macro-Scrubber, Christmas Tree, and IC Tester.

## TECHNOLOGY

- 59 HOW TO ANALYZE WAVEFORMS**  
Digital readouts make waveform analysis a snap.  
**Gregory D. Carey, CET**

## CIRCUITS AND COMPONENTS

- 61 STRAIN-GAGE TRANSDUCERS**  
A look at how they work and how you can use them.  
**Clinton M. Wood**
- 64 THE EARLY DAYS OF RADIO**  
Part 5. More nostalgia.  
**Martin Clifford**

## DEPARTMENTS

- |   |  |
|---|--|
| <b>12 VIDEO NEWS</b><br>What's new in video.<br><b>David Lachenbruch</b>      | <b>42 STATE OF SOLID STATE</b><br>An electronic potentiometer.<br><b>Robert F. Scott</b> |
| <b>35 EQUIPMENT REPORTS</b><br>Mark V Professional Color<br>Light Controller. | <b>74 SATELLITE IV</b><br>What's next?<br><b>Bob Cooper, Jr.</b>                         |
| <b>40 AUDIO UPDATE</b><br>Can you believe your ears?<br><b>Larry Klein</b>    | <b>77 DRAWING BOARD</b><br>Designer RAM<br><b>Robert Grossblatt</b>                      |



**PAGE 86**



**PAGE 47**

## AND MORE

- 126 Advertising and Sales Offices**
- 126 Advertising Index**
- 101 Annual Index**
- 15 Ask R-E**
- 4 Editorial**
- 127 Free Information Card**
- 24 Letters**
- 105 Market Center**
- 32 New Products**
- 6 What's News**

## ON THE COVER



Copy protection is commonplace in today's movie industry. The *Macrovision* encoding process is used on many new video tape releases, and some cable companies have expressed interest in it as well. Its advocates claim that *Macrovision* affords unimpaired viewing of the original tape while making it impossible to copy it. However, many sets are unable to process the encoded signal correctly—resulting in a clouded picture that might also roll or flash. If your TV is one of those that can't handle the encoded picture, our Macro-Scrubber can help. It eliminates only the *Macrovision* encoding, with no effect on normal video signals. For a clean picture all the time, build the Macro-Scrubber. The story begins on page 49.

## COMING NEXT MONTH

**THE JANUARY ISSUE  
IS ON SALE  
DECEMBER 3**

### NATIONWIDE PAGING SYSTEM

Wherever you are, you'll get your message.

### BUILD AN UNINTERRUPTABLE POWER SUPPLY

A 40-watt unit keeps going when your power company quits.

### SEMICONDUCTOR TESTING

How to test TTL devices.

### COMPUTER DIGEST

Get your PT-68K up and running.

As a service to readers, RADIO-ELECTRONICS publishes available plans or information relating to newsworthy products, techniques and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, RADIO-ELECTRONICS disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this magazine.

Since some of the equipment and circuitry described in RADIO-ELECTRONICS may relate to or be covered by U.S. patents, RADIO-ELECTRONICS disclaims any liability for the infringement of such patents by the making, using, or selling of any such equipment or circuitry, and suggests that anyone interested in such projects consult a patent attorney.

**RADIO-ELECTRONICS, (ISSN 0033-7862) December 1987.** Published monthly by Gernsback Publications, Inc., 500-B Bi-County Boulevard, Farmingdale, NY 11735 Second-Class Postage paid at Farmingdale, NY and additional mailing offices. Second-Class mail registration No. 9242 authorized at Toronto, Canada. One-year subscription rate U.S.A. and possessions \$16.97. Canada \$22.97. all other countries \$25.97. All subscription orders payable in U.S.A. funds only, via international postal money order or check drawn on a U.S.A. bank. Single copies \$1.95. © 1987 by Gernsback Publications, Inc. All rights reserved. Printed in U.S.A.

**POSTMASTER:** Please send address changes to RADIO-ELECTRONICS, Subscription Dept., Box 55115, Boulder, CO 80321-5115.

A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

## Radio-Electronics

Hugo Gernsback (1884-1967) founder  
M. Harvey Gernsback,  
editor-in-chief, emeritus

Larry Steckler, EHF, CET,  
editor-in-chief and publisher

### EDITORIAL DEPARTMENT

**Art Kleiman**, editorial director  
**Brian C. Fenton**, managing editor  
**Carl Laron**, WB2SLR, associate editor  
**Jeffrey K. Holtzman**,  
assistant technical editor  
**Marc Spiwak**, associate editor  
**Robert A. Young**, assistant editor  
**Julian S. Martin**, editorial associate  
**Byron C. Wels**, editorial associate  
**M. Harvey Gernsback**,  
contributing editor  
**Jack Darr**, CET, service editor  
**Robert F. Scott**,  
semiconductor editor  
**Herb Friedman**,  
communications editor  
**Bob Cooper, Jr.**, satellite-TV editor  
**Robert Grossblatt**, circuits editor  
**Larry Klein**, audio editor  
**David Lachenbruch**,  
contributing editor  
**Richard D. Fitch**,  
contributing editor  
**Teri Scaduto**, editorial assistant

### PRODUCTION DEPARTMENT

**Ruby M. Yee**, production director  
**Robert A. W. Lowndes**,  
editorial production  
**Andre Duzant**, technical illustrator  
**Ronald Dee**, assistant technical  
illustrator  
**Karen Tucker**, advertising production  
**Marcella Amoroso**, production traffic

### CIRCULATION DEPARTMENT

**Jacqueline P. Cheeseboro**,  
circulation director  
**Wendy Alanko**,  
circulation analyst  
**Theresa Lombardo**,  
circulation assistant

Typography by Mates Graphics  
Cover photos by Nick Koudis

Radio-Electronics is indexed in  
*Applied Science & Technology Index*  
and *Readers Guide to Periodical Literature*.

Microfilm & microfiche editions are  
available. Contact circulation depart-  
ment for details.

Advertising Sales Offices listed  
on page 126.



CIRCLE 205 ON FREE INFORMATION CARD

**HANDHELD DIGITAL IC COMPARATOR/TESTERS FEATURE 20 CHANNEL LOGIC MONITOR**

B&K-PRECISION's Model 550 and 552 IC Comparator Tester/Logic Monitors test IC's by comparison to a known good reference in one simple operation. As logic monitors, they simultaneously indicate the logic states of up to 20 IC pins. They test most 14 to 20 pin, 54 and 74 Series TTL (Model 550) or 4000 and 74C Series CMOS (Model 552) devices. Both models are available from distributors at \$395. Contact your local distributor or: B&K-PRECISION, Dynascan Corp., 6460 W. Cortland St., Chicago, IL 60635. (312) 889-9087.




**LOGIC/PULSER PROBES HELP LOCATE DIGITAL FAULTS IN LAB OR IN FIELD SERVICE**

B&K-PRECISION now offers logic and pulser probes to fill the needs of engineers and technicians. The DP-21 is a 20 MHz probe that also displays pulse presence and logic status. Both LED and audible logic state indicators are featured. The DP-31 pulser probe can be used alone or with a logic probe or scope. It produces a 10µS pulse at 0.5 or 400 PPS rates and features an external square wave and synchronizing terminal. Both probes are multi-family compatible. The DP-21 is \$32. The DP-31 is \$33. Contact your local distributor or: B&K-PRECISION, Dynascan Corp., 6460 W. Cortland St., Chicago, IL 60635. (312) 889-9087.



CIRCLE 77 ON FREE INFORMATION CARD

CIRCLE 206 ON FREE INFORMATION CARD

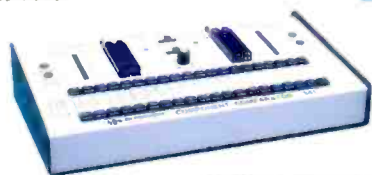

**NEW COMPARATOR ADDS IC/COMPONENT TESTING TO SCOPE**

Test virtually any type of passive or active component or module with B&K-PRECISION's new 541 Component Comparator. The 541 is designed for use with the 540 component tester or virtually any x-y oscilloscope. It is well suited for both in-circuit and out-of-circuit tests. It's fast and easy to use. Unlike single function testing, the 541 can be used on series, parallel or series/parallel circuits. \$395. Contact your local distributor or: B&K-PRECISION, Dynascan Corp., 6460 W. Cortland St., Chicago, IL 60635. (312) 889-9087.



**NEW COMPONENT TESTER LOCATES FAULTS ON UNPOWERED BOARDS IN FIELD OR PLANT**

The new Model 540 component tester is an extremely cost effective, highly flexible trouble-shooting aid that can assist in rapidly locating faults on unpowered boards. Faults can be traced to the component level without specific circuit knowledge. Individual components can also be tested. Test results are displayed as a curve on a built-in CRT display. Curve tracing allows matching of components. Two channels allow production testing against known good boards. Ideal for field service or production testing. \$995. Contact your local distributor or: B&K-PRECISION, Dynascan Corp., 6460 W. Cortland St., Chicago, IL 60635. (312) 889-9087.



**PROGRAMMABLE IC TESTER TESTS TTL, CMOS, RAM AND ROM IC'S, IN OR OUT-OF-CIRCUIT**

Called the "first cost-effective way to test IC's both in and out-of-circuit," the new B&K-PRECISION Model 560 fills the void between basic component testers and costly ATE systems. Over 1500 different 14 to 24 pin devices can be tested, including TTL and CMOS digital IC's, RAMs and ROMs. The 560 speeds testing, simplifies diagnostics and doesn't require prior test skills. Plain-English user prompts guide every step of operation. Test results are displayed as positive "pass" or "fail." Test results can be fed to a printer. Applications include incoming inspection, QC, production line testing and troubleshooting faulty products. \$3,500. Contact your local distributor or: B&K-PRECISION, Dynascan Corp., 6460 W. Cortland St., Chicago, IL 60635. (312) 889-9087.

CIRCLE 207 ON FREE INFORMATION CARD

CIRCLE 208 ON FREE INFORMATION CARD

# B&K-PRECISION has what you need for fast, cost-effective IC or board testing.

Check it out

- Programmable in/out-of-circuit IC tester
- Portable curve-tracing component tester
- Portable IC comparator tester/ logic monitors
- Benchtop IC component comparator tester
- Multi-family compact pulser probes
- Memory-mode multi-family logic probes

Whether your needs are for production board testing, incoming inspection or field service, B&K-PRECISION has you covered with time saving, accurate digital test products.

The Model 560 Programmable In/Out-of-circuit IC Tester is the first cost-effective way to rapidly test IC's both in and out-of-circuit. Punch up the number you need from a resident memory of over 1500 TTL, CMOS IC's, RAM's and ROM's.

The Model 540 Component Tester locates faults on unpowered boards down to the component level. Curve-tracing method also allows fast comparison of components or boards.

The Model 541 Component Comparator is a companion instrument for use with your scope or the 540. It tests IC's, semiconductors, capacitors, inductors, transformers and more.

The Models 550 and 552 IC Comparator Tester/Logic Monitors are hand-held portables for TTL and CMOS applications. In-circuit dynamic tests compare a known-good IC to an on-board IC. A 20-channel logic monitor is built-in.

The B&K-PRECISION digital test line-up is rounded out by convenient and economical pulser and logic probes.

For immediate delivery or complete specifications and applications information, call your local distributor or B&K-PRECISION.



**BK PRECISION**

**DYNASCAN CORPORATION**  
6460 West Cortland St. • Chicago, IL 60635 • 312-889-9087  
International Sales: 6460 W. Cortland St., Chicago IL 60635

Canadian Sales, Atlas Electronics, Ontario  
South and Central American Sales, Empire Exporters, Plainville, NY 11803

---

---

# EDITORIAL



## Where is ComputerDigest going?

It's been almost four years since the first issue of **ComputerDigest** appeared inside **Radio-Electronics**. We have proven wrong the thousands of readers who felt that we would soon become "just another computer magazine." We have proven that **Radio-Electronics** is dedicated to covering the entire scope of electronics from satellite TV to antique radio, from digital audio tape to computers.

We hope you've noticed that **ComputerDigest** has changed during the last year. We've been taking our coverage of computers more seriously, and we've been covering more serious computers.

We've seen how computers can be used to design printed-circuit boards, and we've seen how graphics coprocessors work to make CAD programs faster and more powerful. We've looked at the computers of tomorrow with reports on IBM's PS/2. And, although we got off to a false start, we've begun to show you how to build a computer based on Motorola's powerful 68000 microprocessor.

Our hands-on reviews have kept you on top of the latest hardware and software. And we hope that our in-depth product comparisons have helped make your buying decisions easier by keeping you informed.

The construction projects have ranged from a clock board for your PC to a complete, powerful, yet low-cost 68000-based machine. We have also shown you how to install a 3-1/2-inch disk drive, and how you can dramatically increase the performance of your PC.

But that's enough talk about 1987. As we prepare our first issue for next year, we wonder how we can make **ComputerDigest** better. What type of articles do you want to see in 1988? More reviews? More construction? More industry news? Only *you* know how **ComputerDigest** can serve you better. Please don't keep it to yourself—we need to know. Write to us at 500-B Bi-County Blvd., Farmingdale, NY 11735. Let us know what computers you use and how you use them, and share your views with us..

Thanks for making 1987 a successful year for **Radio-Electronics**. We hope your holiday season is happy, and we wish you all the best for the new year.

A handwritten signature in black ink, which appears to read "Brian C. Fenton". The signature is stylized and fluid.

BRIAN C. FENTON  
Managing Editor

# Your Best Source for Banana Plugs and Adapters is POMONA ELECTRONICS

**STANDARD DOUBLE BANANA  
PLUG: MODEL MDP**



**BNC FEMALE TO STANDARD  
DOUBLE BANANA PLUG:  
MODEL 1269**



**STANDARD DOUBLE BINDING  
POSTS TO BNC MALE:  
MODEL 1296**



**DOUBLE BANANA JACK:  
MODEL 2269**



**FREE 1987 GENERAL CATALOG**



**ITT** Pomona Electronics  
1500 E. Ninth St., Pomona, CA 91766  
Tel: (714) 623-3463

**SINGLE BINDING POST TO BNC  
MALE: MODEL 3430**



**STANDARD BINDING POST:  
MODEL 3760**



**CONNECTOR TEST ADAPTERS:  
SOCKET TYPE (LEFT) MODEL  
4690; PIN TYPE (RIGHT)  
MODEL 4691**



**BNC FEMALE TO PHONO PLUG:  
MODEL 2957**



Our Products are available through your favorite electronics parts distributor.

CIRCLE 101 ON FREE INFORMATION CARD

# WHAT'S NEWS

## Novel developments in artificial intelligence

In spite of fantastic advances, computers remain remarkably stupid about certain things. In particular, their language level is below that of a two-year-old child. And they are notoriously poor at finding things only slightly different from those asked for. Another weakness of computers is overprecision—without the exact information the computer cannot reach a conclusion. (An officer on the battlefield, on the other hand, must make instant decisions based on incomplete—and sometimes conflicting—information.)

Scientists at the General Electric Research and Development Center recently presented eight papers aimed at those problems at the Tenth International Conference on Artificial Intelligence,

held in Milan, Italy. Possibly the most topical were two papers by Dr. Urik Zernik of the Center. Both of them were based on attempts to answer two questions: How do human beings learn language?" and "How can the process be taught to computers?"

Past computer-language programs have followed academic models—the computer is "taught" a vocabulary (or fitted with a "dictionary") and given a set of grammatical rules. But humans don't learn a language that way, says Dr. Zernik. They learn with everyday experience with new words, phrases, and idioms.

His solution is to equip his program (called RINA) with a "dynamic lexicon" containing entire phrases (including idioms). RINA


is also equipped with a set of mathematical instructions that tell the computer how to work with the lexicon and how to use it to gain new knowledge.

As an example, the computer was given the statement: "Israel and Egypt buried the hatchet." The computer interpreted that as "The nations buried a knife", but it rejected the phrase; in its experience, nations do not bury physical objects. The user helped out: "Israel and Egypt were in a long conflict, they signed a peace agreement." The computer, correctly deducing the meaning of the idiom, then replied: "They buried the hatchet; they terminated the conflict." Later, given the idiom in a totally different context, it responded correctly by applying what it had learned.

A system that is designed to enable a computer to make decisions based on incomplete information was described by Dr. Piero Bonissone, in a paper detailing RUM (*Reasoning with Uncertainty Module*). The system helps the computer to make sense out of fuzzy terms, like "almost" or "probably" and to weigh the similarities and differences of the current situation against a previous one.

Another paper, by GE scientist Van-Duc Nguyen, describes advances in image understanding—a computer's ability to recognize objects shown by the lines and angles of their outlines. (See "What's News" *Radio-Electronics*, April 1987). That process of "line labeling", or identification, is improved by adding information showing all lines as either concave, convex, or occluding.


R-E

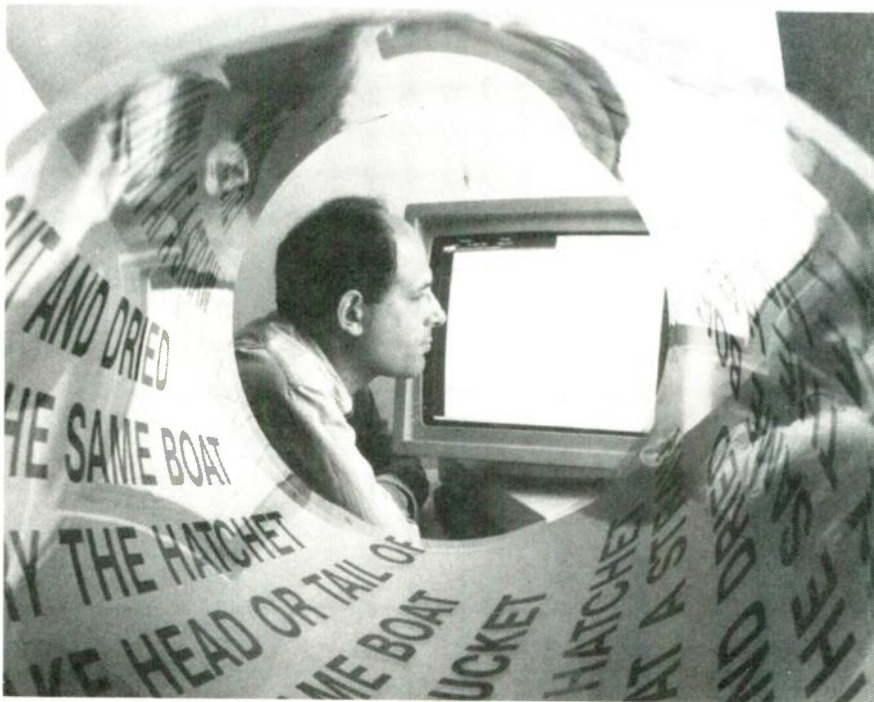

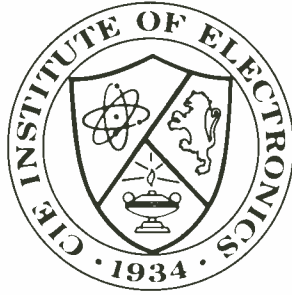
DR. URI ZERNIK, General Electric scientist, with a few of the idioms that his language, RINA, helps the computer to figure out.







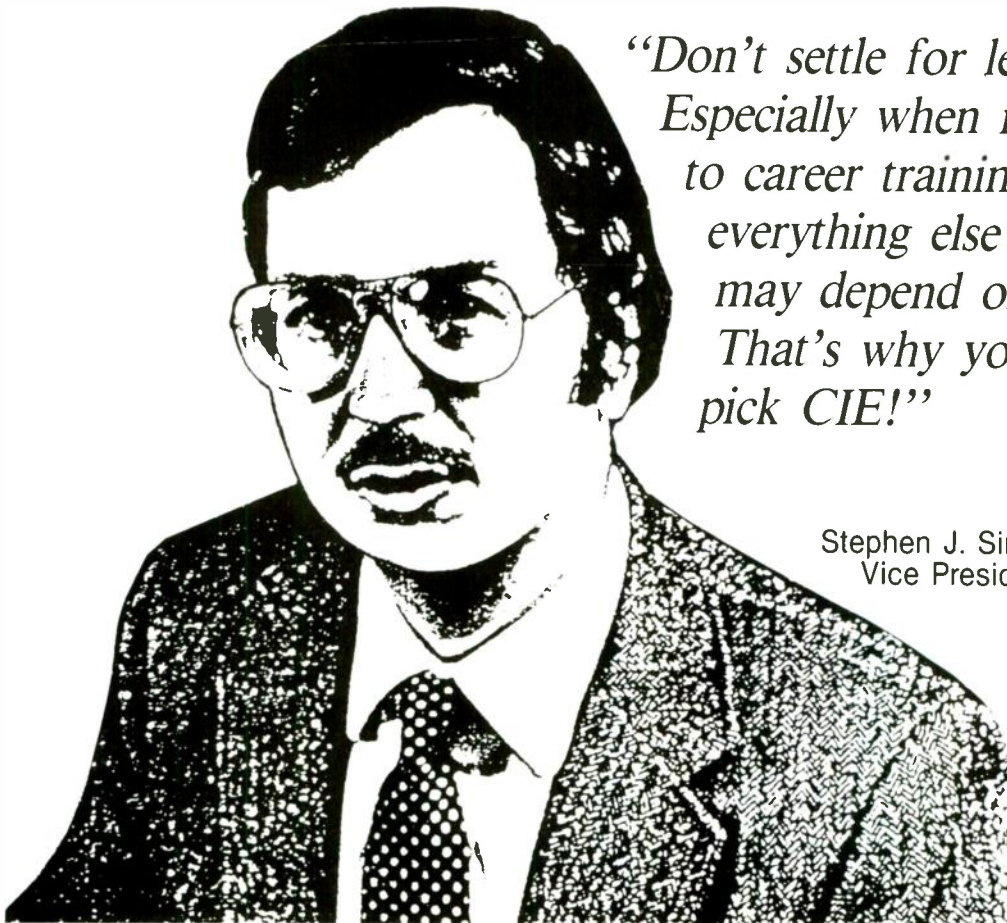“If you’re going to learn electronics, you might as well learn it right!”



*“Don’t settle for less.  
Especially when it comes  
to career training...because  
everything else in your life  
may depend on it.  
That’s why you ought to  
pick CIE!”*

Stephen J. Simcic  
Vice President, Academic Affairs

**Y**ou've probably seen advertisements from other electronic schools. Maybe you think they're all the same. They're not!

CIE is the largest independent home study school in the world that specializes exclusively in electronics.

### Meet the Electronics Specialists.

When you pick an electronics school, you're getting ready to invest some time and money. And your whole future depends on the education you get in return.

That's why it makes so much sense to go with number one . . . with the specialists . . . with CIE!

### There's no such thing as bargain education.

If you talk with some of our graduates, chances are you'd find a lot of them shopped around for their training. Not for the lowest priced but for the best. They pretty much knew what was available when they picked CIE as number one.

We don't promise you the moon. We do promise you a proven way to build valuable career skills. The CIE faculty and staff are dedicated to that. When you graduate, your diploma shows employers you know what you're about. Today, it's pretty hard to put a price on that.

### Because we're specialists we have to stay ahead.

At CIE, we've got a position of leadership to maintain. Here are some of the ways we hang onto it . . .

### Programmed Learning

That's exactly what happens with CIE's Auto-Programmed Lessons. Each lesson uses famous "programmed learning" methods to teach you important principles. You explore them, master them completely, before you start to apply them. You thoroughly understand each step before you go on to the next. You learn at your own pace.

And, beyond theory, some courses come fully equipped with electronics gear (the things you see in technical magazines) to actually let you perform hundreds of "hands-on" experiments.

### Experienced specialists work closely with you.


Even though you study at home, you are not alone! Each time you return a completed lesson, you can be sure it will be reviewed, graded, and returned with appropriate instructional help. When you need additional individual help, you get it fast and in writing from the faculty technical specialist best qualified to answer your question in terms you can understand.

### Pick the pace that's right for you.

CIE understands people need to learn at their own pace. There's no pressure to keep up . . . no slow learners hold you back. If you're a beginner, you start with the basics. If you already know some electronics, you move ahead to your own level.
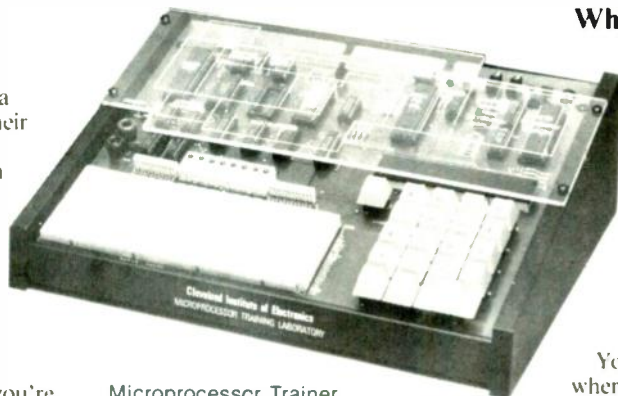
### Enjoy the promptness of CIE's "same day" grading cycle.

When we receive your lesson before noon Monday through Saturday, we grade it and mail it back the same day. You find out quickly how well you're doing!



Microprocessor Trainer

### State-of-the-art Laboratory Equipment

Some courses feature the CIE Microprocessor Training Laboratory. An integral part of computers, microprocessor technology is used in many phases of business, including service and manufacturing industries.

The MTL gives you the opportunity to program it and interface it with LED displays, memory devices, and switches. You'll gain all the practical experience needed to work with state-of-the-art equipment of today and tomorrow.

### CIE offers you an Associate Degree.

One of the best credentials you can have in electronics — or any other career field — is a college degree. That's why CIE gives you the opportunity to earn an Associate in Applied Science in Electronics Engineering Technology. Any CIE career course can offer you credit toward the degree — more than half of the number needed in some cases.

*"Cleveland Institute of Electronics is the only accredited institution of higher learning offering an Associate Degree program with tuition based on actual study time used. The faster you complete your degree assignments, the less your overall tuition."*

Steve Simcic  
Vice-President Academic Affairs

### Which CIE Training fits you?

Beginner? Intermediate? Advanced? CIE home study courses are designed for ambitious people at all entry levels. People who may have:

1. No previous electronics knowledge, but do have an interest in it;
2. Some basic knowledge or experience in electronics;
3. In-depth working experience or prior training in electronics.

You can start where you fit and fit where you start, then go on from there to your Diploma, Associate Degree, and career.

### Today is the day. Send now.

Fill in and return the postage-free card attached. If some ambitious person has removed it, cut out and mail the coupon. You'll get a FREE school catalog plus complete information on independent home study. For your convenience, we'll try to have a CIE representative contact you to answer any questions you may have.

Mail in the coupon below or, if you prefer, call toll-free 1-800-321-2155 (in Ohio, 1-800-523-9109).

ARE-74

## CIE Cleveland Institute of Electronics, Inc.

1776 East 17th Street, Cleveland, Ohio 44114

Accredited Member National Home Study Council

YES...I want to learn from the specialists in electronics — CIE. Send me my FREE CIE school catalog...including details about the Associate Degree program... plus my FREE package of home study information.

Print Name \_\_\_\_\_

Address \_\_\_\_\_ Apt. \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Age \_\_\_\_\_ Area Code/Phone No. \_\_\_\_\_/\_\_\_\_\_

Check box for G.I. Bill bulletin on Educational Benefits:  Veteran  Active Duty

**MAIL TODAY!**

CIRCLE 60 ON FREE INFORMATION CARD

---

---

# VIDEO NEWS



**DAVID LACHENBRUCH,**  
CONTRIBUTING EDITOR

• **What's in a name?** Not much, evidently. Take RCA, for example: In 1986, it was sold to General Electric, which was one of the original founders of RCA. General Electric then sold off RCA Records to German publisher Bertelsmann, which not only continues to use the RCA name but has restored the old RCA "meatball" trademark—R, C, and A in a circle, with a lightning bolt at the bottom of the A. Then GE proceeded to sell both GE and RCA consumer electronics to France's giant Thomson combine. Now the RCA initials will be used on records by a German company and on TV's by a French one. The David Sarnoff Research Center (once called RCA Laboratories) was donated to SRI International, which still calls it by the name of RCA's guiding genius.

Or take Philips, the worldwide tradename of the Dutch electronics giant. In the early days of electronics, the company reached an agreement to keep the Philips name out of the United States because it might be confused with Philco, which was here first. Philco was sold to Ford, Ford sold it to GTE, and GTE sold it to North American Philips, which in turn was absorbed by Dutch Philips. So Philips ended up owning Philco, which, not surprisingly, no longer had any objection to the use of the Philips name. Thus, the Philips name finally has come to America on lightbulbs and appliances, and soon on electronics, including TV sets.

Good old names never seem to die; but sometimes they go to sleep for a while. That's what's now happening to Pilot, a historic name. It was Pilot Radio that introduced the first big-selling component FM tuner, the *Pilotuner*. Then in 1948 Pilot brought out the first portable TV (it was in a large suitcase and had a 3-inch picture); that was also the first TV set with a list price under \$100. Pilot went through a number of permutations, and eventually when audio marketer Morse sold out to Curtis Mathes, Pilot was one of the names that went with it. Curtis Mathes tried selling Pilot audio equipment for a while, but phased out the line this year. So Pilot is now in limbo, but the brand will probably make a comeback sometime soon, like oldtimers such as

Capehart, Emerson, Symphonic, and DuMont; all of those are still around, but the equipment is being manufactured by companies that have no connection to the brand's originator.

• **Zenith goes digital.** Apparently encouraged by the success of its original digital offerings last year, Zenith has introduced 15 new TV sets with all-digital signal processing, in 20- and 27-inch sizes, all with built-in TV stereo and teletext reception. That's far more digital models than any other TV manufacturer will be selling in the U.S. In other introductions, Zenith became the first American manufacturer to offer a TV set with a 35-inch tube (the tube is Japanese). Also, Zenith has introduced a new vertical VCR about six-inches wide by 12-inches tall, designed for bookshelves and other tight places. One 27-inch TV set has a removable panel that conceals a compartment just the right shape to hold Zenith's vertical VCR—and nobody else's. For its lower-priced sets, Zenith has introduced the new highly automated *Duratech* chassis, which contains 46% surface-mount parts, 80% machine-inserted components, 20% fewer connectors, and is 100% computer tested and aligned.

• **Compact disc-video postponed.** If you've been looking for those Compact Disc-Video (CD-V) records and players (**Radio-Electronics**, August 1987), you'll have to wait a little longer. Although they were formally "introduced" last summer, nothing has come on the market, and they're now scheduled for a new launch early in 1988. The CD-V format is an overall name given to the old Laservision videodisc, as well as the new five-inch discs that play five minutes of analog video and 20 minutes of digital audio. Pioneer has introduced combination players that will play the 5-inch discs as well as 8- and 12-inch ones, and others are due soon. CD-V's sponsors want to go through the hoopla of a launch after they have about 200 music-video titles in the 5-inch size. At press time, fewer than 100 selections had been committed to the short audio-video singles.

**R-E**

# TEST EQUIPMENT THAT MEASURES UP TO YOUR SPECIFICATIONS



**DMM-300 \$79.95**  
3.5 DIGIT DMM / MULTITESTER

Our best model. A highly accurate, full function DMM loaded with many extra features. Audible continuity, capacitance, transistor, temperature and conductance all in one handheld meter. Temperature probe, test leads and battery included.

- Basic DC accuracy: plus or minus 0.25%
- DC voltage: 200mv — 1000v, 5 ranges
- AC voltage: 200mv — 750v, 5 ranges
- Resistance: 200 ohms — 20M ohms, 6 ranges
- AC/DC current: 200uA — 10A, 6 ranges
- Capacitance: 2000pf — 20uf, 3 ranges
- Transistor tester: hFE test, NPN, PNP
- Temperature tester: 0° — 2000° F
- Conductance: 200ms
- Fully over-load protected
- Input impedance: 10M ohm



**DMM-200 \$49.95**  
3.5 DIGIT FULL FUNCTION DMM

High accuracy, 20 amp current capability and many range settings make this model ideal for serious bench or field work. Tilt stand for hands-free operation. 2000 hour battery life with standard 3v cell. Probes and battery included.

- Basic DC accuracy: plus or minus 0.25%
- DC voltage: 200mv — 1000v, 5 ranges
- AC voltage: 200mv — 750v, 5 ranges
- Resistance: 200 ohms — 20M ohms, 6 ranges
- AC/DC current: 200uA — 20A, 6 ranges
- Fully over-load protected
- Input impedance: 10M ohm
- 180 x 86 x 37mm, weighs 320 grams



**DMM-700 \$49.95**  
3.5 DIGIT AUTORANGING DMM

Autorange-convenience or fully manual operation. Selectable LO OHM mode permits accurate in-circuit resistance measurements involving semi-conductor junctions. MEM mode for measurements relative to a specific reading. Probes and battery included.


- Basic DC accuracy: plus or minus 0.5%
- DC voltage: 200mv — 1000v, autoranging or 5 manual ranges
- AC voltage: 2v — 750v, autoranging or 4 manual ranges
- Resistance: 200 ohms — 20uΩ ohms, autoranging
- AC/DC current: 20mA — 10A, 2 ranges
- Fully over-load protected
- Audible continuity tester
- Input impedance: 10M ohm
- 150 x 75 x 34mm, weighs 230 grams



**DMM-100 \$29.95**  
3.5 DIGIT POCKET SIZE DMM

Shirt-pocket portability with no compromise in features or accuracy. Large, easy to read 5" LCD display. 2000 hour battery life with standard 9v cell provides over two years of average use. Probes and battery included.

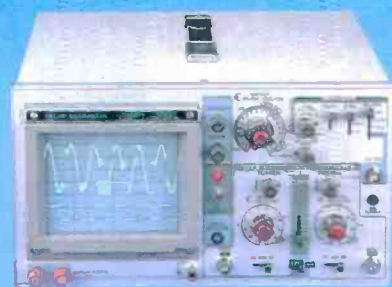- Basic DC accuracy: plus or minus 0.5%
- DC voltage: 2v — 1000v, 4 ranges
- AC voltage: 200v — 750v, 2 ranges
- Resistance: 2k ohms — 2M ohms, 4 ranges
- DC current: 2mA — 2A, 4 ranges
- Fully over-load protected
- Input impedance: 10M ohm
- 130 x 75 x 26mm, weighs 195 grams



**MODEL 2000 \$349.95**  
20 MHz DUAL TRACE OSCILLOSCOPE

Model 2000 combines useful features and exacting quality. Frequency calculation and phase measurement are quick and easy in the X-Y Mode. Service technicians will appreciate the TV Sync circuitry for viewing TV-V and TV-H as well as accurate synchronization of the Video Signal, Blanking Pedestals, VITS and Vertical/Horizontal sync pulses.

- Lab quality compensated 10X probes included
- Built-in component tester
- 110/220 Volt operation
- X-Y operation • Bright 5" CRT • TV Sync filter



**MODEL 3500 \$499.95**  
35 MHz DUAL TRACE OSCILLOSCOPE

Wide bandwidth and exceptional 1mV/DIV sensitivity make the Model 3500 a powerful diagnostic tool for engineers or technicians. Delayed triggering allows any portion of a waveform to be isolated and expanded for closer inspection. Variable Holdoff makes possible the stable viewing of complex waveforms.

- Lab quality compensated 10X probes included
- Delayed and single sweep modes
- Z Axis intensity modulation
- X-Y operation • Bright 5" CRT • TV Sync filter




**DPM-1000 \$54.95**  
3.5 DIGIT PROBE TYPE DMM

Autoranging, pen style design for the ultimate in portability and ease of use. Custom 80 pin LSI chip increases reliability. Audible continuity tester and data hold feature for added convenience. Case, test leads and batteries included.

- Basic DC accuracy: plus or minus 1%
- DC voltage: 2v — 500v, autoranging
- AC voltage: 2v — 500v, autoranging
- Resistance: 2k ohms — 2M ohms, autoranging
- Fully over-load protected
- Input impedance: 11M ohm
- 162 x 28 x 17mm, weighs 75 grams

**2 YEAR WARRANTY ON ALL MODELS**

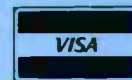

**JDR INSTRUMENTS**

110 Knowles Drive, Los Gatos, CA 95030  
(408) 866-6200 • FAX (408) 378-8927 • Telex 171-110

COPYRIGHT 1984 JDR MICRODEVICES  
THE JDR INSTRUMENTS LOGO IS A REGISTERED TRADEMARK OF JDR MICRODEVICES.  
JDR INSTRUMENTS IS A TRADEMARK OF JDR MICRODEVICES.

**ORDER TOLL FREE 800-538-5000**


OR VISIT OUR RETAIL STORE  
1256 SOUTH BASCOM AVE.  
SAN JOSE, CA. (408) 947-8881  
CIRCLE 59 ON FREE INFORMATION CARD

# IF YOU WANT A BETTER COMPUTER BUILD IT YOURSELF.

Heath makes building the powerful 386 computer quick, fun, easy... and a great value.


Now you can own the fastest, most powerful home computer available today - at an affordable cost. Just by building it yourself.

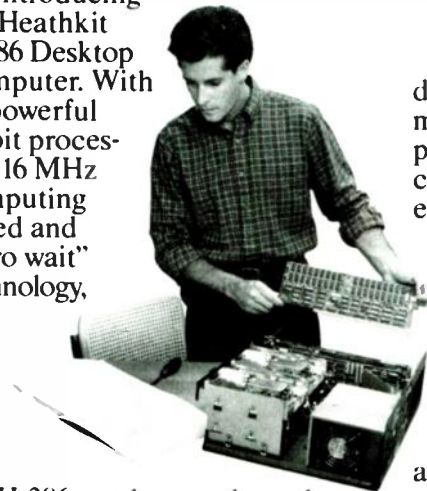Introducing the Heathkit H-386 Desktop Computer. With its powerful 32-bit processor, 16 MHz computing speed and "zero wait" technology,



the H-386 can breeze through complex calculations in seconds.

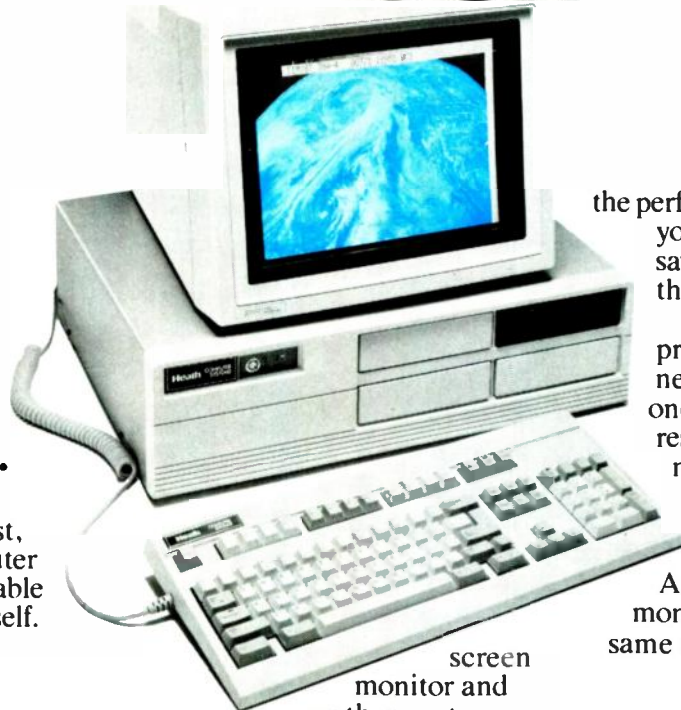Every INTEL 80386 microprocessor used in our H-386 is 100% tested for all functions. And you get superb graphics because one video port provides dazzling 640-by-480 color on Zenith's new flat



screen monitor and another port drives EGA, CGA and TTL monochrome monitors. Both ports automatically emulate common video formats for easy system configuration.

Designed for people using large spreadsheets, CAD/CAM or other computation-intensive applications, or anyone who simply wants to own the newest, most powerful hardware on the market, the Heathkit H-386 can be assembled easily and quickly. One or two evenings is all it takes, and no special tools or equipment are required.

In the bargain, you get the satisfaction of having built a powerful computer system all by yourself, and the confidence that this exciting product will deliver all

the performance and dependability you expect. At a significant savings over comparable off-the-shelf brands.

What's more, all Heathkit products are backed by a newly extended, limited one-year warranty, highly respected manuals and technical consultation service.

So if you want a better computer, build it yourself. Impress your friends.

And save money at the same time.



To order the new Heathkit H-386 Desktop Computer, simply call toll-free 1-800-253-0570. Ask for operator 312. Use your Visa, MasterCard or Heath Revolving Charge. Or call 616-982-3614 for the Heath/Zenith Computers and Electronics store location nearest you.

For more information on all our quality kits, send now for your free four-color Heathkit catalog. Write Heath Company, Dept. 020-604, Benton Harbor, MI 49022.

Prices, product availability and specifications are subject to change without notice.

**Heathkit®**  
Heath  
Company

Heathkit is a registered trademark of Heath Company, a subsidiary of Zenith Electronics Corporation.

© 1987, Heath Company.

CIRCLE 86 ON FREE INFORMATION CARD

# ASK R-E

WRITE TO:


ASK R-E  
Radio-Electronics  
500-B Bi-County Blvd.  
Farmingdale, NY 11735

# TALK IS CHEAP.

Have you heard? For less than \$90 your AT or XT-compatible computer can talk! All it needs is the HV-2000 Computer Voice Kit from Heathkit.

Reading letters, transcriptions and computerized instruction can be easier and quicker than you ever thought possible. Computer games gain a new dimension. Your computer can even entertain children with stories and songs.

**\$89.95**

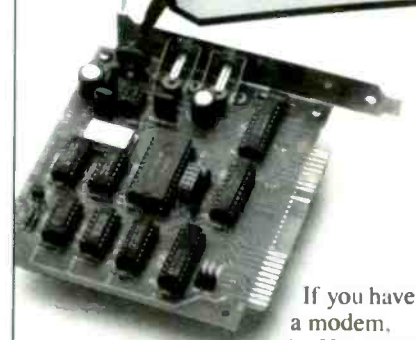

If you have a modem, the HV-2000

Computer Voice will allow your computer to recite reference and research information from time-sharing services. Or, speak radio transmitted ASCII information.

The HV-2000 Computer Voice Card, containing speech synthesizer and audio amplifier, plugs into any AT or XT-compatible computer's expansion slot. An external speaker is also included. Versatile. Heath-developed software gives you a wide variety of voices and easy interface to high and low level languages.

The HV-2000 Computer Voice. At less than \$90, talk IS cheap. To order, call toll-free 1-800-253-0570. Ask for operator 312. Use your Visa, MasterCard or Heath Revolving Charge card. Or call 616-982-3614 for the nearest store location.

**Heathkit**  
Heath  
Company

Benton Harbor, MI 49022

Prices, product availability and specifications are subject to change without notice.

© 1987, Heath Company.

CIRCLE 86 ON FREE INFORMATION CARD

DECEMBER 1987

15

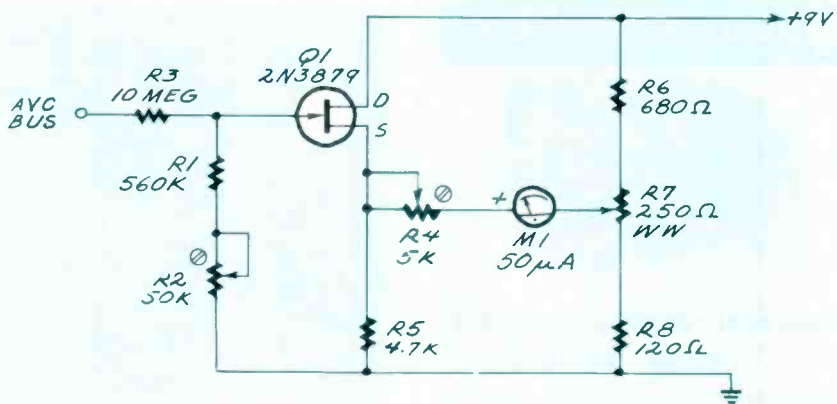


FIG. 1

## S-METER AND HEADPHONE JACK

Please show the circuit of a signal-strength meter for an AM radio. Also describe how I can add a headphone jack that will automatically silence the speaker when the phones are plugged in.—J.D., Turnersville, NJ.

I don't know anything about the radio you're modifying, so the best bet for a signal-strength indicator is an FET DC voltmeter (Fig. 1) connected to the set's AGC bus. As shown, the meter reads upward when connected to a positive-going AGC. If the radio uses tubes or has a negative-going AGC, completely isolate the voltmeter's positive and negative leads from

the receiver and then reverse the meter movement's connections so it responds to a negative voltage input. Or, do as was often done on communications receivers: Turn the meter upside down so a declining voltage input will cause the meter to appear to read up-scale.

Figure 2 shows how low-impedance headphones can be connected into the audio output circuit of the radio. Inserting the phone plug connects the phones across the audio output while disconnecting the speaker.

## PRECEDENCE DETECTOR

We are planning to update the indicator system used in our "Scholastic Bowl" events. The present system uses relays and we want to use solid-state circuitry.

The moderator or quiz-master asks a question and the first contestant to believe that he has the answer presses a pushbutton switch that causes his indicator lamp to light, and, at the same time, locks out the indicators of the other contestants. The judge determines the winner and then resets the system.—J.R., Cuba, IL.

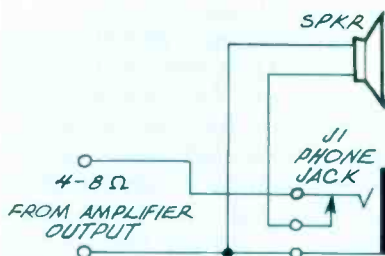


FIG. 2

# HITACHI SCOPES AT DISCOUNT PRICES!

20MHZ



Model V212 \$475

Model V-212 20MHZ Dual Channel (1mV Sens.) \$475  
 Model V-422 40MHZ Dual Channel (1mV Sens.) \$699  
 Model V-425 40MHZ Dual Channel (with cursor) \$795  
 Model V-660 60MHZ Dual Channel (Delayed Sweep) \$999  
 Model V-1060 100MHZ Dual Channel (Delayed Sweep) \$1,375  
 All above scopes have a 3 year warranty on parts and labor


100MHZ



Model V1060 \$1,375

15-25%  
OFF LIST  
PRICE

# ELENCO PRODUCTS AT DISCOUNT PRICES!

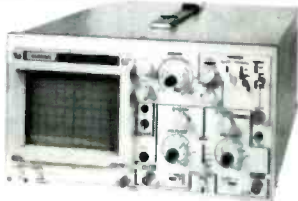

40MHZ  
DELAYED  
SWEEP  
MO-1253  
\$550



20MHZ DUAL TRACE OSCILLOSCOPE  
\$359 MO-1251

35MHZ DUAL TRACE OSCILLOSCOPE  
\$498 MO-1252

Top quality scopes at a very reasonable price. Contains all the desired features. Elenco's 2 year guarantee assures you of continuous service. Two 1x, 10x probes, diagrams and manual included. Write for specs.  
 100 MHz Test Probes, 1X, 10X, Ref. (Complete with 5 accessories) Fits Most Scopes - \$22

MULTIMETER with CAPACITANCE AND TRANSISTOR TESTER  
 Model CM-1500A \$58  
 Reads Volts, Ohms, Current, Capacitors, Transistors & Diodes W/Case

TRUE RMS 4 1/2 DIGIT MULTIMETER  
 Model M-7000 \$135  
 .05% DC Accuracy  
 1% Resistance with Freq. Counter & Deluxe Case

Auto Ranging plus Manual Ranging  
 3 1/2 Digit Meter  
 28 Functions Fully protected  
 M-1180 7% Acy \$36.95  
 M-1182 25% Acy \$39.95  
 M-1181 1% Acy \$42.95

GF-8016 FUNCTION GENERATOR with Freq. Counter  
 \$239  
 • Sine, Square, Triangle  
 • Pulse, Ramp, .2 to 2MHz  
 • Frequency 1 thru 10MHz  
 GF-8015 without Freq. Meter \$179

10MHz OSCILLOSCOPE \$239  
 Model S-3000  
 • 10MHz DC or AC  
 • Triggered Sweep  
 • Calibrated Vert & Hor  
 • Reads Volts & Freq

BREADBOARD  
 Model 9436 Shown  
 9430 1,100 pins \$15  
 9434 2,170 pins \$25  
 9436 2,860 pins \$35

DIGITAL TRIPLE POWER SUPPLY  
 Model XP-765 \$239  
 0-20V @ 1A  
 0-20V @ 1A  
 5V @ 5A  
 Fully Regulated, Short Circuit Protected with 2 Limit Cont. 3 Separate Supplies  
 XP-860 with Analog Meters \$169.50

DIGITAL LCR METER \$148  
 Model LC-1800  
 Measures: Inductors, Capacitors, Resistors

50MHz LOGIC PROBE 20 nsec with memory LP-700  
 \$23  
 Logic Pulsar LP-800 \$23

DIGITAL 3 AMP POWER SUPPLY  
 Model XP-750 \$175  
 0-40V @ 1.5A  
 0-20V @ 3A  
 Fully regulated, short circuit protected current limit control  
 XP-850 with Analog Meters \$129.50

MULTI-FUNCTION COUNTERS  
 F-1000 1.2GH \$259  
 F-100 120MH \$179  
 Frequency, Period, Totalize, Self Check with High-Stabilized Crystal Oven Oscillator, 8 Digit LED Display

C&S SALES INC., 1245 ROSEWOOD DRIVE, DEERFIELD, IL 60015 800-292-7711 (312) 459-9040 ASK FOR CATALOG 15 DAY MONEY BACK GUARANTEE

2 Year Limited Guarantee! Add 5% for Postage (\$10 max), IL Res., 7% Tax CIRCLE 109 ON FREE INFORMATION CARD

Our files contain a number of precedence-detector circuits that indicate which of two pushbuttons is pressed first. One circuit, which uses incandescent lamps for high visibility, is shown in Fig. 3.

The circuit, which was described by M. Jennings in the English magazine *Radio & Electronics Constructor*, is designed for SCR switching. The SCR's, of which there is one per "player," remain off until one of them is turned on when a player momentarily closes his pushbutton switch. The switch

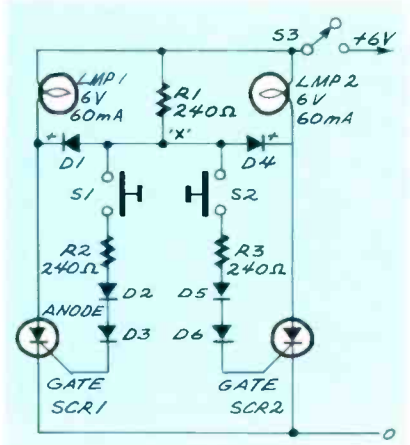



FIG. 3

closure produces a positive trigger pulse on the gate of the corresponding SCR, turning it on. As soon as one SCR turns on, its corresponding indicator lamp lights and the other SCR is locked out so that it cannot fire.

Any number of switching circuits can be added to the detector by duplicating the circuitry to the right of point "X". The SCR's are low-power types such as the Radio Shack 276-1020 and the diodes are silicon rectifiers such as the 1N4002. Switches S1 and S2 are normally-open pushbuttons. Switch S3 is used by the judge or referee to apply power and to reset the precedence detector. That switch may be a single-pole push-on/push-off type.

The precedence detector works this way: Even with S3 closed to energize the detector, the SCR's do not conduct because their gates are isolated from a positive voltage source. Assume that two (or more) players hit their push-buttons at almost the same instant, but contestant No. 1 closes his switch (S1) a fraction of a sec-





# Nine Test Probes with only one difference between them and your scope's original equipment

Manufacturers Scope	Original Probe	Price	Coline/TPI Equivalent	Price	Manufacturers Scope	Original Probe	Price	Coline/TPI Equivalent	Price	
<b>TEKTRONIX</b> 2300 Series	P6101A	\$53	M12X1	<b>\$38</b>	<b>PHILIPS</b> PM3267	PM8294	\$60	M12X1	<b>\$38</b>	
	P6108A	\$75	M12X10	<b>\$62</b>		& PM3256	PM8926	\$70	P100	<b>\$38</b>
	2200 Series	P6121	\$100	M12X10AP			<b>\$68</b>	PM8928	\$95	M12X10
		P6122	\$58	P100	<b>\$38</b>	<b>HITACHI</b> V-1100A V-670 V-509	AT-10AL15	\$64	SP100	<b>\$43</b>
	2400 Series	P6131	\$140	M15X10HFAP	<b>\$87</b>					
		P6133	\$115	M12X10AP	<b>\$68</b>					
400 Series	P6105A	\$93	M12X10AP	<b>\$68</b>						
	P6106A	\$140	M15X10HFAP	<b>\$87</b>	<b>HEWLETT PACKARD</b> 1715A 1722B 1725A 1740 Series	10018A	\$135	M20X10	<b>\$68</b>	
	P6130	\$130	M12X10AP	<b>\$68</b>		10017A	\$130	M15X10HF	<b>\$79</b>	
<b>IWATSU</b> SS-5321	SS-0014	\$92	M12X10	<b>\$62</b>		10017A	\$130	M15X10HF	<b>\$79</b>	
SS-5711	SS-0012	\$77	M12X10	<b>\$62</b>	10041A	\$135	P100	<b>\$38</b>		
<b>LEADER</b> LBO-315	LP-060X	\$60	SP100	<b>\$43</b>	10021A	\$85	IP20	<b>\$29</b>		
LBO-518	LP-100X	\$76	SP100	<b>\$43</b>						

Take up the Coline TPI challenge and compare our prices with the probes you currently use. In many cases you can replace both probes on your dual trace scope at the cost of one probe from the scope manufacturer. Plus, bandwidth and overall performance of the TPI probe typically exceed that of the original equipment. Satisfaction is guaranteed with a ten day return privilege. Coline TPI - Specialists in probes for over 15 years.

Available from your local distributor.

**TOLL FREE INFORMATION LINE**  
**1-800-368-5719, 1-800-643-8382 in California**

**Coline TPI**  
TEST PROBES INC.

9178 Brown Deer Road, San Diego CA, 92121 Phone: (619)535 9292  
CIRCLE 123 ON FREE INFORMATION CARD

Send to: 9178 Brown Deer Road, San Diego CA, 92121  
 Please send full line catalog  
Name \_\_\_\_\_  
Company \_\_\_\_\_  
Address \_\_\_\_\_  
Phone: \_\_\_\_\_

# Train with NRI for a servicing

**NEW!**


Train with the newest Sanyo 880 Series Computer—it's fully IBM-compatible and runs almost twice as fast as the IBM PC!

## Get started now by building this fully IBM PC compatible computer

Now you get it all . . . training for America's fastest growing career opportunity . . . training to service all computers . . . training on the newest total computer system, the Sanyo 880. Only NRI can give you the well-rounded training you need, because only NRI gives you a complete computer system . . . computer, monitor, disk drive, software, even test instruments like a digital multimeter and logic probe to work with and keep. It all adds up to training that builds the knowledge, competence, and ability you need to succeed as a computer service specialist.
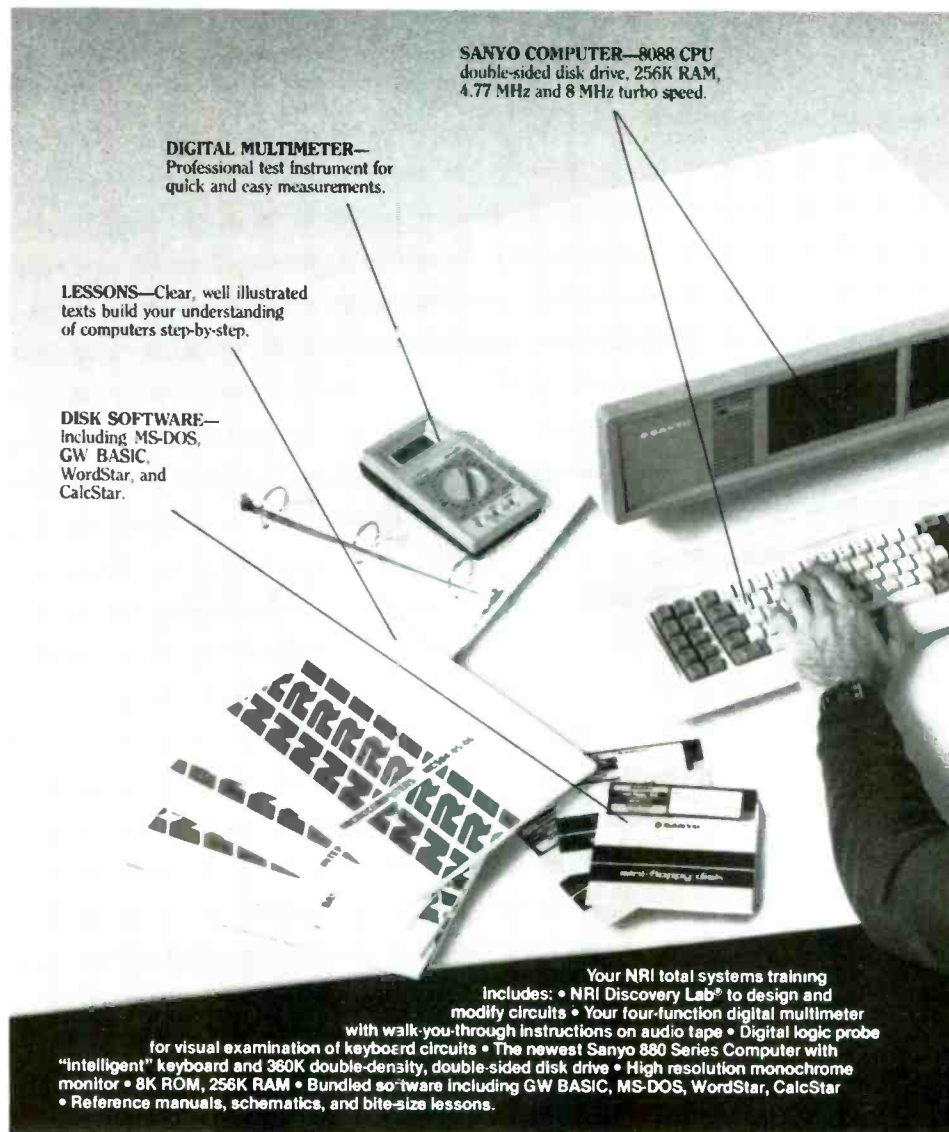
### Get inside the newest, fully IBM PC compatible Sanyo Microcomputer

As an NRI student, you'll get total hands-on training



**SANYO COMPUTER**—8088 CPU, double-sided disk drive, 256K RAM, 4.77 MHz and 8 MHz turbo speed.

**DIGITAL MULTIMETER**—Professional test instrument for quick and easy measurements.

**LESSONS**—Clear, well illustrated texts build your understanding of computers step-by-step.


**DISK SOFTWARE**—Including MS-DOS, GW BASIC, WordStar, and CalcStar.

Your NRI total systems training includes: • NRI Discovery Lab® to design and modify circuits • Your four-function digital multimeter with walk-you-through instructions on audio tape • Digital logic probe for visual examination of keyboard circuits • The newest Sanyo 880 Series Computer with "Intelligent" keyboard and 360K double-density, double-sided disk drive • High resolution monochrome monitor • 8K ROM, 256K RAM • Bundled software including GW BASIC, MS-DOS, WordStar, CalcStar • Reference manuals, schematics, and bite-size lessons.

as you actually build your own latest model Sanyo 880 Series computer from the keyboard up. It's fully IBM PC-compatible and, best of all, it runs programs almost twice as fast as an IBM PC. As you assemble the Sanyo 880, you'll perform

demonstrations and experiments that will give you a total mastery of computer operation and servicing techniques. You'll do programming in BASIC language—even run and interpret essential diagnostic software.

# high paying career computers

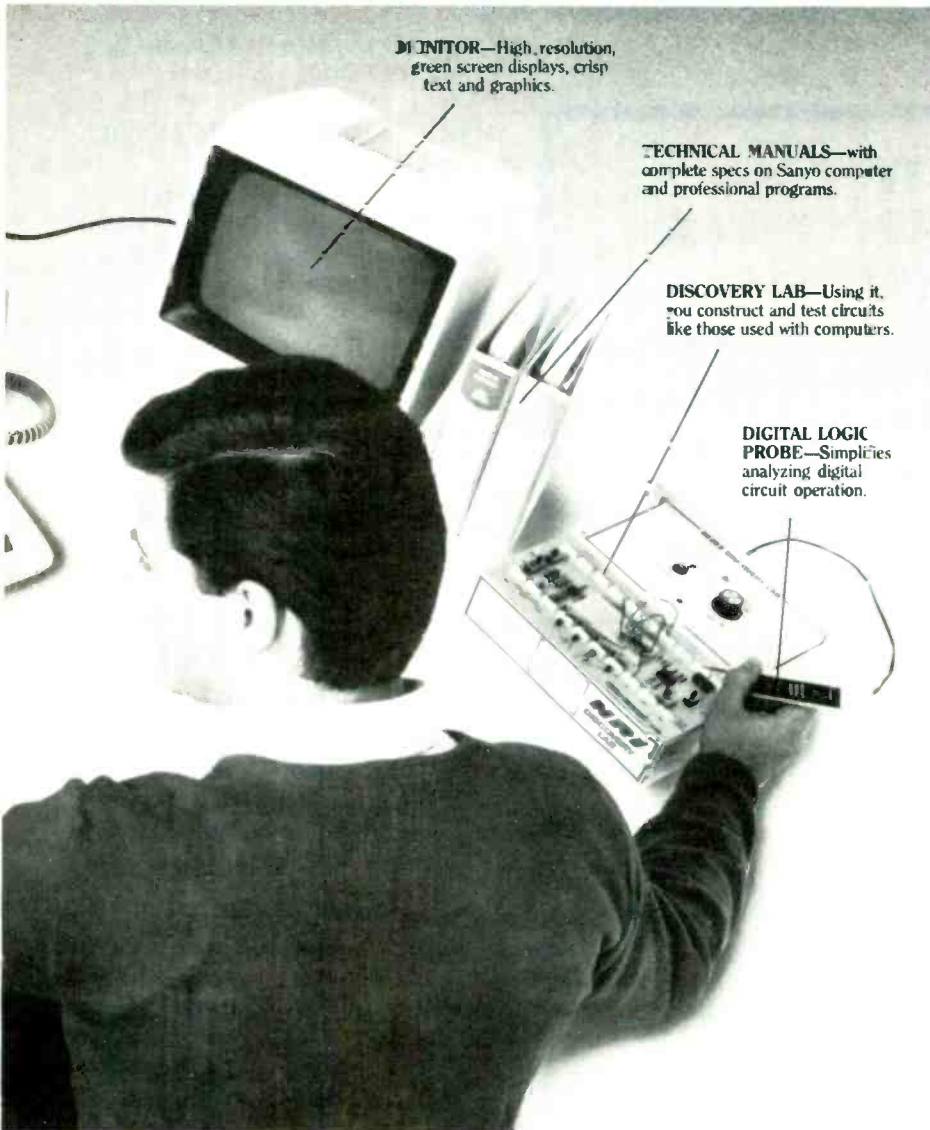

## Understanding you get only through experience

You need no previous knowledge to succeed with NRI. You start with the basics, rapidly building on the fundamentals of electronics with bite-size lessons. You perform hands-on experiments

with your NRI Discovery Lab and then move on to master advanced concepts like digital logic, microprocessors, and computer memories.

## Learn at home in your spare time

You train in your own home

at your own convenience, backed at all times by your own NRI instructor and the entire NRI staff of educators and student service support people. They're always ready to give you guidance, follow your progress, and help you over the rough spots to keep you moving toward your goal.

## 100 page free catalog tells more . . . send today

Send the postage-paid reply card today for NRI's 100 page catalog that gives all the facts about computer training, plus career training in robotics, data communications, TV/audio/video servicing, and many other fields. If the card is missing, write to NRI at the address below.



**NRI** SCHOOLS  
McGraw-Hill Continuing Education Center  
3939 Wisconsin Avenue  
Washington, DC 20016  
We'll give you tomorrow



ond before any of the others. At the instant S1 closes, gate current flows through R1, S1, and diodes D2 and D3, so SCR1 conducts. Its anode current flows through indicator lamp LMPI, and the anode voltage falls to around 0.6 volt—the anode-cathode voltage drop across SCR1. That causes D1 to be forward-biased, so it also conducts, dropping point X to 1.2 volts—the sum of the diode-voltage drops across SCR1 and D1.

With point X at 1.2 volts, all the

other circuits are locked out, because when any other pushbutton is pressed, the two series-connected silicon diodes (D5, D6, etc.) are not sufficiently forward-biased to pass the gate current needed to fire the associated SCR. After determining the winning contestant, the umpire resets the board by pushing S3 once to turn off the conducting SCR, and again to restore power.

The indicator lamps should be low-current types—drawing ap-

proximately 60 mA or so. If you use higher current types make sure that their cold resistance (as measured with an ohmmeter) is high enough to limit the initial inrush of lamp current to the maximum surge-current rating of the SCR.

If you need something more elaborate, consider building the "Electronic Umpire" described in the December 1970 issue of *Radio-Electronics*. It handles two teams of three players each, and indicates the order of response for the first four contestants.

#### USING AN OPTOELECTRONIC COUPLER

I am trying to design a circuit that uses a Motorola MOC7811 slotted opto-coupler as a sensor, but I can't locate any applications data. Can you help?—B.J.D., Peoria, AZ .

Slotted couplers in that series consist of an infrared-emitting diode and a photodetector facing each other across a slot in the housing, as shown in Fig. 4. The slot provides a means of interrupting the path between the infrared source and its detector.

We don't have any idea as to

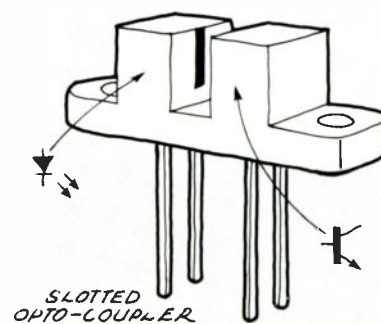


FIG. 4

what you want to accomplish, so your best bet is to seek applications data from Motorola Semiconductors, 616 West 24th St., Phoenix, AZ 85282. For typical circuits and additional applications information, see one or more of the following: *General Electric Optoelectronics Manual*, the *Motorola Optoelectronics Device Data book*, or *The Optoelectronics Data Book for Design Engineers* from Texas Instruments.

#### WHAT KIND OF RESISTORS

I'm interested in resistors and want information on the differences

### CABLE TV SPECIALS CONVERTERS



	JRX-3 DIC—6 Channel Corded Remote . . .	\$139.95
	JSX-3 DIC—36 Channel Set Top . . . . .	\$129.95
	SB-3 — 'The Real Thing' . . . . .	\$109.95
	SB-M-Refurbished . . . . .	\$89.95
	DRZ-3D1C—68 Channel Wireless with Decoder . . . . .	\$199.95
ZENITH:	Z-TAC Cable Add-On . . . . .	\$199.00
VIEW STAR:	EVSC-2010—60 Channel Wireless— with Parental Lockout . . . . .	\$ 99.00
	EVSC-2010 A-B—Same as above with A-B Switch . . . . .	\$109.00
	View Star 2501—60 Channel Wireless . . . . . with Volume . . . . .	\$119.00
	Unika MR-702—72 Channel Wireless with Parental Lockout . . . . .	\$89.95

### MISCELLANEOUS

OAK:	N-12 Mini-Code . . . . .	\$ 89.00
	N-12 Mini-Code Vari-Sync . . . . .	\$99.95
	N-12 Mini-Code Vari-Sync Plus Auto On-Off . .	\$159.95
JERROLD:	400 & 450 Handheld Transmitters . . . . .	\$ 29.00
HAMLIN:	MLD-1200 . . . . .	\$ 99.00
NEW ITEMS:	Ripco Tape Copy Stabilizer . . . . .	\$109.95
	Scientific Atlanta SA-3 . . . . .	\$139.95
OAK:	E-13 Mini-Code Substitute . . . . .	\$ 79.95
	E-13 Mini-Code W/Vari-Syn . . . . .	\$ 89.95

ALL UNITS GUARANTEED. QUANTITY PRICES AVAILABLE.

### UNITED ELECTRONIC SUPPLY

P.O. BOX 1206 • ELGIN, ILLINOIS 60121 • 312-697-0600

between a thermistor, thermister, thyristor, and varistar. I have found some definitions, but they are conflicting. I'm particularly interested in the thermistor because one is used in my oscilloscope's power supply.—B.C., San Diego, CA.

The word "thermistor" is an acronym for *Thermally-Sensitive Resistor*. A thermistor is a ceramic semiconductor whose resistance varies greatly with changes in its temperature. The change in temperature may be due to internal heating due to current flow, or to heat from an external source. Thermistors are available with either positive or negative temperature coefficients. The NTC (*Negative Temperature Coefficient*) device is one that exhibits a *decrease* in resistance with *increases* in body temperature. A PTC device is one that develops an *increase* in resistance with an *increase* in temperature.

"Thermister" is a misspelling or corruption of the correct spelling.

I never heard of a "varistar." Perhaps the word you are looking for

is "varistor"—meaning a two-terminal voltage-sensitive semiconductor whose resistance decreases rapidly as the applied voltage is increased.

A thyristor is a stable (two-state) semiconductor device having three or more junctions. It can be rapidly switched between its *off* and *on* states. The term "thyristor" is often used to include SCR's and gate-controlled switches.

### UNLOADED VACUUM-TUBE AMPLIFIERS

I've serviced car stereo and home hi-fi equipment for more than ten years. Occasionally, an old tube-type amplifier is brought in for service. Recently, a new service manager "hit the roof" when he found me working on a vacuum-tube power amplifier when I had not connected a load to its outputs. He says that I could have destroyed the amplifier, but won't explain how or why. What's the problem?—B.F., Mamaroneck, NY.

Solid-state power amplifiers can be run without a load on their out-

puts but can be damaged if a short circuit is inadvertently connected across the output terminals. Conversely, a vacuum-tube power amplifier can be damaged if you "crank up the power" before connecting a speaker or resistor load across the secondary of the output transformer.

Here's what happens: Without a load on the secondary winding, the primary winding appears as a very-high impedance and the audio voltages across it can rise to very-high values. The peak voltages can be high enough to cause arcing in the output tubes or cause a breakdown in the insulation between turns in the primary winding.

Whether the voltage peaks do or don't cause catastrophic tube or transformer failure depends on such factors as the transformer's design and the amplifier's output power. You have been lucky thus far, so follow the service manager's instructions and always keep a load on the output of a vacuum-tube power amplifier. R-E

# NEW RUGGEDIZED SCOPE PROBES

Just a phone call away.

**\$35** P6103

50 MHz 10x  
Compensation Range  
15 to 35 pF

**\$58** P6109

150 MHz 10x  
Compensation Range  
18 to 22 pF


These new passive voltage probes can be used with any oscilloscopes having matching compensation ranges.

Screw in tips mean easy repair, no downtime.

To order call toll free **1-800-426-2200**

In Oregon, call collect (503) 627-9000.

VISA and MasterCharge accepted.

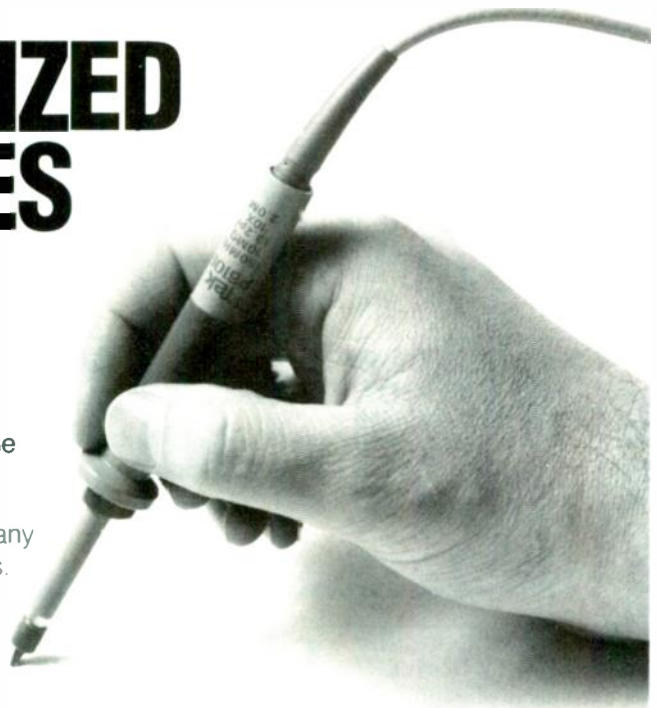

**Tektronix**  
COMMITTED TO EXCELLENCE

# LETTERS



## ON ARTIFICIAL INTELLIGENCE

I read your article, "Artificial Intelligence," in the May 1987 issue of *Radio-Electronics*, and I was amazed that nothing was mentioned about the following:

Democratic electronic circuits or systems would consist of not only series/serial circuits, but parallel as well. That type of system would also include analog chips and circuits, which convey data based on the degree that a circuit is on—in short, waveforms—and not just based on electronic

switching chips or circuits. Those analog chips would simulate how the neurons work in the brain. They would probably be called *almost* and *nalmost* chips, or *maybe on* and *not maybe on* chips. Chips and circuits such as those would make it possible for a computer to learn, memorize, and understand, and to relate or think—to *know*.

*Interface data bridges* would allow the thousands of neuron microprocessors in the computer to have the same data stored in each

one as the entire computer has stored in its memory bank overall. Those would make it possible for the computer to have a holographic memory bank, just as the brain has.

A circuit that performs like an electronic mirror, composed of a simulated *data-constructed model* of reality, would enable a computer to compare incoming data with that data model for analysis and interpretation. Within that index memory bank should be a form of self-consciousness, so that the

Send Purchase Order, Check, Money Order, or C.O.D. or Call Toll Free  
**800-223-0826**  
 In N.Y. State (212) 865-5580

## #1 IN CABLE BOXES SPECIAL!

### JERROLD CORDLESS CABLE TV CONVERTER

MODEL DRX3-105/400

## \$59.95/10 UP

\$69.95/1-9

- 58 channels
- Remote channel changing
- Remote on/off switch
- Remote fine tuning
- Compatible with descramblers



### JERROLD CORDLESS CABLE TV CONVERTERS

MODEL STARCOM-460

## \$99.95/3 UP

\$109.95/1-2

- Instant channel recall
- Programmable to go on at a particular channel and off automatically
- Compatible with descramblers



VOLUME CONTROL

\*ADD 5% FOR VISA OR MASTER CARD

### JERROLD CORDED CABLE TV CONVERTER

MODEL JRX3-105

## \$29.95/10 UP

\$39.95/6-9  
\$49.95/1-5



### SCIENTIFIC ATLANTA CORDLESS CABLE TV CONVERTER

MODEL SA-550

## \$79.95/10 UP

\$89.95/1-9

- 83 channels
- Automatic fine tuning
- parental control
- programmable channeling
- compatible with descramblers

NEW!

# OMNITRON

## ELECTRONICS

770 Amsterdam Ave., New York, NY 10025

Write for  
**FREE CATALOG**  
136 page

SHIPPING CHARGES

For Orders	
\$25-100	Add \$6.50
\$100-500	\$8.50
\$500-750	\$10.50
\$750 and up	\$20.00

MASTER CARD     VISA

RADIO-ELECTRONICS


# Your Career in **ELECTRONICS** or **COMPUTERS**

Add prestige and earning power to your technical career by earning your Associate or Bachelor's Degree in electronics or computers—through independent home study.

No commuting to class. Study at your own pace, while continuing on your present job. Learn from easy-to-understand lessons, with help from your Grantham instructors when you need it.

Grantham College of Engineering is a specialized institution catering to adults who are employed in electronics and allied fields such as computers. These fields are so enormous that opportunity for advancement is always present. Promotions and natural turn-over make desirable positions available to those who are prepared to move up!

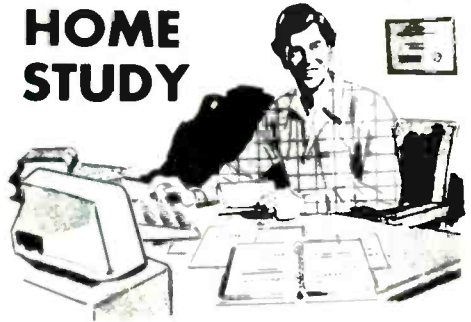Put Professional Knowledge and a  
**COLLEGE DEGREE**  
in your Technical Career through  
**HOME STUDY**



*NHSC Accredited*

**Grantham College of Engineering**  
**10570 Humbolt Street**  
**Los Alamitos, California 90720**

*Write for our free catalog*  
(see coupon below) or phone  
(213) 493-4423 (no collect calls)  
and ask for our "degree catalog."

Grantham offers two B.S. degree programs — one with major emphasis in **ELECTRONICS** and the other with major emphasis in **COMPUTERS**. Either program can be completed by correspondence (also known as "distance education.") An A.S. degree is awarded along the way in each B.S. program, but the B.S. program is not complete without the A.S. part. Our catalog gives complete details.

*Now in Our*  
**37th Year**

**Grantham College of Engineering**

has conferred on

**John Doe**

the degree of

**Associate in Science in Engineering Technology**  
*with major emphasis in Computers*

**Grantham College of Engineering**

has conferred on

**John Doe**

the degree of

**Bachelor of Science in Engineering Technology**  
*with major emphasis in Computers*

*In witness thereof, this diploma duly signed has been issued by the College Administration upon recommendation of the Faculty, at the College in*

**Grantham College of Engineering**

has conferred on

**John Doe**

the degree of

**Associate in Science in Engineering Technology**  
*with major emphasis in Electronics*

**Grantham College of Engineering**

has conferred on

**John Doe**

the degree of

**Bachelor of Science in Engineering Technology**  
*with major emphasis in Electronics*

*In witness thereof, this diploma duly signed has been issued by the College Administration upon recommendation of the Faculty, at the College in Los Alamitos, California, on this day of March 1, 1987.*

**Grantham College of Engineering**  
P.O. Box 539, Los Alamitos, CA 90720

Please mail me your free catalog which explains your distance-education degree programs.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_


STATE \_\_\_\_\_

ZIP \_\_\_\_\_

R-12-87

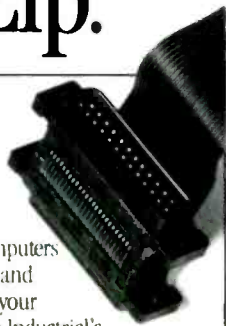
# Test RS232C In A Zip.

Test RS232C data communications interfaces—like computers to printers, computers to modems, and computers to computers—fast and easy in the palm of your hand with Beckman Industrial's low-cost, easy-to-use line of testers. Each is self-contained in a Toughpak case, including five models in a durable zippered pouch, and a 10-year warranty on every model. Prices start as low as \$49.95.



See your nearest Beckman Industrial distributor today, or send for free brochure. We'll send it to you in a zip.

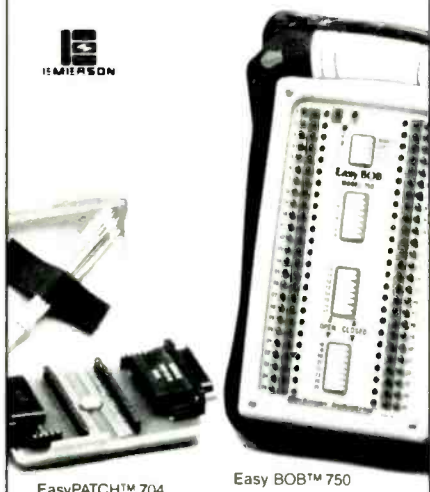- Quick Cable Customizing
- Fast RS232C Interfacing and Testing
- LED Identification of Cable Configurations
- Pocket and Hand-held Compactness
- Speeds Up Trouble Shooting
- 10 Standard, Low-Cost Models



EasyPATCH™ 704

Easy BOB™ 750

**In Service  
Instruments,  
We're The One.**

**Beckman Industrial™**

Beckman Industrial Corporation Instrumentation Products Division  
A Subsidiary of Emerson Electric Company  
5883 Ruffin Rd. San Diego, California 92123-1898  
(619) 565-4415 • FAX: (619) 268-0172 • Tlx: 249031

© 1987 Beckman Industrial Corporation

computer can know itself better and have an identity. That would allow it to relate itself better to the outside world.

Circuits such as those would enable a computer to mimic the brain realistically. They would be able to modify and re-program themselves relative to outside circumstances and basic built-in programming, for survival and the expansion or evolution of consciousness. The circuits would be flexible and therefore capable of change and growth.

Today's computers are nothing more than inert slave mechanisms—like electronic slide rules, card catalogs, or books. We need computers that have more feedback in them.

HERBERT D. STAFFIERI  
*Bridgeport, CT*

## MICRO-FLOPPY RETROFIT

Before I read the article, "Micro-floppy Retrofit," in the August 1987 *ComputerDigest*, I converted my XT B: drive to 3½ inch, using the

Toshiba ND-354A with their "Universal Kit." The kit is very inexpensive and complete, with accessories for the PC, XT, AT, Compaq2, AT&T PC6300, and compatibles. Besides costing less than the IBM kit, the Toshiba kit has the advantage of not requiring the IBM's 37-pin D-connector.

My original configuration was one half high 5¼ FDD and one half-height 20-megabyte hard disk. The half height 3½-inch disk drive fits very nicely on top of my A: drive.

I am using PC DOS 3.2, and to format 3½ inch disks at 720K I used the undocumented DOS command called DRIVPARM in my CONFIG.SYS file. The complete command is DRIVEPARM =/D:1/F:2, where /D:1 is the drive number (B:) and /F:2 indicates the 3½-inch drive type.

Having a 3½ inch drive is necessary for me to maintain compatibility with the new IBM computers at work—and it is nice to have 720K floppy storage.

RICHARD F. PELLY  
*Huntington Beach, CA*

## AMPLIFIER DESIGN

I enjoy Radio-Electronics very much—in fact, I can barely wait for the next issue. I want to thank you for including computer program listings with some of your articles. I find them almost as much fun as the projects.

The article, "Transistor Amplifier Design," by Jack Cunkelman in the August 1987 issue was a great source of information on common emitter amplifiers. Maybe he could do more on common-base and common-collector amps.

Line 280 in the program listing reads:

$$R2 = IZ * RE * 100 / ((RE * 100) - IZ)$$

Two problems were solved when I changed line 280 to read:

$$R2 = INT(IZ * RE * B / ((RE * B) - IZ))$$

First, the formula now considers the "input" value for beta. And I no longer get a negative result for R2 with certain "input" data.

I hope that is useful to other readers, and thanks again.

MICHAEL H. PERKINS  
*Louisville, KY*

*continued on page 37*

## Be an FCC LICENSED ELECTRONIC TECHNICIAN!

Learn at home in spare time.  
No previous experience needed.

No costly school. No commuting to class. The Original Home-Study course prepares you for the "FCC Commercial Radiotelephone License". This valuable license is your "ticket" to thousands of exciting jobs in Communications, Radio-TV, Microwave, Computers, Radar, Avionics and more! You don't need a college degree to qualify, but you do need an FCC License.

**No Need to Quit Your Job or Go To School**  
This proven course is easy, fast and low cost! **GUARANTEED PASS** - You get your FCC License or money refunded. **Send for FREE facts now. MAIL COUPON TODAY!**

**COMMAND PRODUCTIONS**  
FCC LICENSE TRAINING, Dept 90  
P.O. Box 2223, San Francisco, CA 94126  
Please rush FREE details immediately!

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_



# ONE FOR ALL,




# AND ALL FROM ONE.

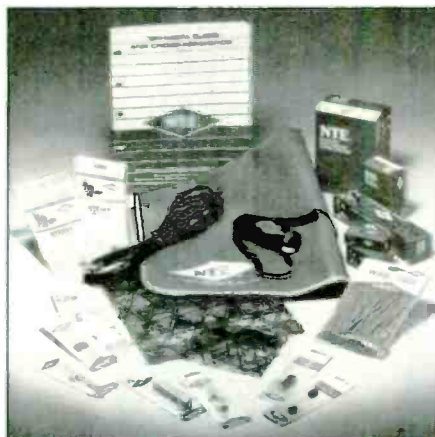**An extensive line of capacitors for both standard and high voltage applications from NTE Electronics.**

NTE, the name you've come to trust for all your replacement semiconductor needs, now has a line of subminiature aluminum electrolytic capacitors.

These quality capacitors are available with both radial and axial leads and are dependable over a broad temperature range. Ratings include capacitance of 0.1  $\mu\text{F}$  to 10000  $\mu\text{F}$ , tolerance of  $\pm 20\%$  ( $-10\%$  to  $+50\%$  for the high voltage line), and voltage range of 6.3 to 100 volts (160 to 450 for the high voltage line), making them ideal for the most demanding applications.



**LOOK FOR THE FULL LINE OF QUALITY NTE REPLACEMENT PARTS AND PRODUCTS:**

- Transistors
- Thyristors
- Integrated Circuits
- Rectifiers and Diodes
- High Voltage Multipliers and Dividers
- Optoelectronic Devices
- Zeners
- Microprocessors and Support Chips
- Memory ICs
- Thermal Cut-Offs
- Bridge Rectifiers
- Unijunctions
- RF Transistors
- Microwave Oven Rectifiers
- Selenium Rectifiers
- Flameproof Resistors
- Wire Ties
- Electrolytic Capacitors
- Static Control Products

For more information or the name of your local distributor, call or write NTE.




**NTE ELECTRONICS, INC.**


44 Farrand Street, Bloomfield, New Jersey 07003 (Outside N.J.) 1-800-631-1250 • (N.J. only) 1-800-624-2624

CIRCLE 71 ON FREE INFORMATION CARD

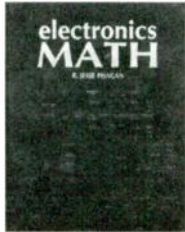
Please note: some books count as 2 selections



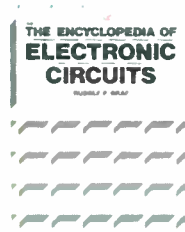**Electronics Math**  
Pub. Price \$22.95  
Club Price \$18.95  
Book #7205



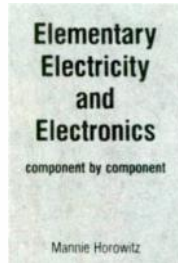**The Encyclopedia of Electronic Circuits**  
Pub. Price \$50.00  
Club Price \$39.95  
Book #7014  
COUNTS AS 2 SELECTIONS



**Elementary Electricity and Electronics**  
component by component  
Mannie Horowitz  
Pub. Price \$23.95  
Club Price \$19.15  
Book #7285




**Handbook of Computers and Computing**  
Pub. Price \$77.50  
Club Price \$62.35  
Book #7072  
COUNTS AS 2 SELECTIONS



**The Illustrated Dictionary of Microcomputers**  
Pub. Price \$24.95  
Club Price \$19.95  
Book #7246



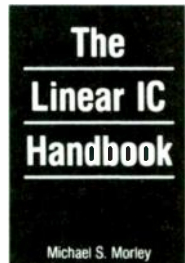
**Industrial Robotics**  
Pub. Price \$43.95  
Club Price \$35.15  
Book #7211  
COUNTS AS 2 SELECTIONS




**The Linear IC Handbook**  
Michael S. Morley  
Pub. Price \$49.95  
Club Price \$39.95  
Book #7214  
COUNTS AS 2 SELECTIONS



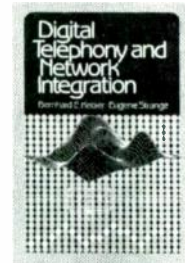**Cost Estimating with Microcomputers**  
Pub. Price \$29.95  
Club Price \$23.95  
Book #7037



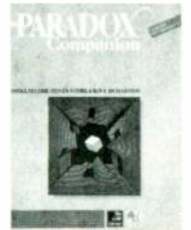**Digital Telephony and Network Integration**  
Pub. Price \$44.50  
Club Price \$35.95  
Book #7204  
COUNTS AS 2 SELECTIONS




**The Paradox Companion**  
Pub. Price \$24.95  
Club Price \$19.95  
Book #7245



**Semiconductor Power Electronics**  
Pub. Price \$46.95  
Club Price \$37.55  
Book #7267  
COUNTS AS 2 SELECTIONS



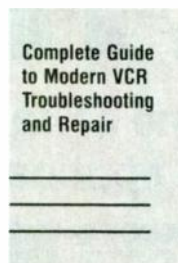**Software Engineering Environments**  
Pub. Price \$38.95  
Club Price \$31.15  
Book #7247



**Complete Guide to Modern VCR Troubleshooting and Repair**  
Pub. Price \$38.33  
Club Price \$31.15  
Book #2126




**Discovering Electronics With Useful Projects and Applications**  
Pub. Price \$29.95  
Club Price \$23.95  
Book #4560



**Complete TV Servicing Handbook**  
Pub. Price \$33.00  
Club Price \$26.35  
Book #7385



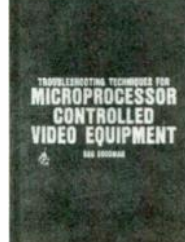**The Complete Compact Disc Player**  
Pub. Price \$33.00  
Club Price \$26.35  
Book #7389




**Troubleshooting Techniques for Microprocessor Controlled Video Equipment**  
Pub. Price \$24.95  
Club Price \$19.95  
Book #7599



**Electronic Connections**  
Pub. Price \$28.67  
Club Price \$23.15  
Book #2808



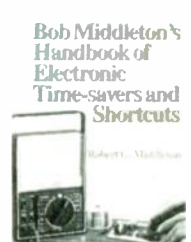**Handbook of Video Camera Servicing and Troubleshooting Techniques**  
Pub. Price \$29.95  
Club Price \$23.95  
Book #4213



**Bob Middleton's Handbook of Electronic Time-savers and Shortcuts**  
Pub. Price \$29.95  
Club Price \$23.95  
Book #4595

# Until you write them yourself, you won't find better books than these...or a better deal!

Take any 3 books for just \$1.00 each.  
Take 1 more at our special Club Price.

*Not only will you save as much as \$120.63 off publishers' list prices on 4 of the most popular — and indispensable — technical books in print today... but also fulfill half the usual 2-book purchase obligation — automatically!*

**Examine your 4 books FREE for 15 days!**

EBS is the professional service designed specifically to keep you on top of everything new in electronic theory and application. Every book is reviewed and approved by our Technical Advisory Board. And every month we bring you the kind of information you want — and need — to know in the field of advanced electronics... access to new thoughts on systems design, op amps, TTL, bit-slice microprocessors, circuits, LSI/VLSI, optoelectronics, satellite communications, LANs, linear control, feedback, instrumentation, A/D crossovers and more. Everything it takes to keep you going *and successful* throughout your career!

## 6 Unbeatable Reasons for Joining Electronics Book Service

**1. Our Introductory Offer** — 3 books for just \$1.00 each... a 4th at our special Club Price — a savings of as much as \$120.63 off publishers' list prices.

**2. Automatic Fulfillment of half the usual 2-book purchase obligation** — Once you have selected and paid for your 4 introductory selections, you *automatically* fulfill half of EBS's usual 2-book purchase obligation. Your only obligation is to then purchase 1 additional book — at Member discounts — during the first year of your Membership. You may cancel any time after that.

**3. Original publishers' editions** — Never cheaply-made reprints.

**4. A complete book store by mail** — Choose from the best, most popular books in your field — by mail and from the comfort and convenience of your home or office. Here's how it works: Every 3-4 weeks (15 times a year) you'll receive the *Bulletin* describing a new Main Selection and several Alternates. If you want the Main Selection, do nothing. It will be shipped automatically. If you prefer an Alternate — or no

book at all — simply indicate your choice on the order card always provided and return it by the date indicated. You'll always have 10 days to decide whether or not you want a Main Selection.

**5. Special Member Discounts** — 20% to 30% — and more — off regular list prices. A small shipping and handling charge is added to all orders.

**6. The Electronics Book Service Guarantee** — You never buy books you don't want. If you ever receive a book that does not live up to your expectations, return it for full credit.



Say YES and  
become an electronics  
know it all!

Send this coupon today!

### Electronics Book Service

A Prentice Hall Book Club  
P.O. Box 10621, Des Moines, IA 50380-0621

YES! Please enroll me as a trial Member of Electronic Book Service and send me the 3 books listed below for just \$1.00 each and 1 more book for the special Club Price plus postage and handling and applicable state sales tax. I understand the Membership Plan as described in this ad and that by accepting your offer, I automatically fulfill half the usual 2-book purchase obligation. I agree to then purchase 1 additional book — at Member discounts — during the first year of my Membership. If not completely satisfied with my introductory selections I may return them within 15 days and owe nothing.

Send me these 3 books for  
\$1.00 each:

Book # \_\_\_\_\_

Book # \_\_\_\_\_

Book # \_\_\_\_\_

PLUS... Send me this book at  
the special Club Price

Book # \_\_\_\_\_

(Please note that some books count  
as 2 selections)

Name \_\_\_\_\_

Address \_\_\_\_\_

City/State/Zip \_\_\_\_\_

Signature \_\_\_\_\_

(not valid without signature)

Offer good for new Members only in the continental US and Canada.

All applications subject to credit approval.

87T51

# ELECTRONIC COMPONENTS CATALOG

... yours **FREE**  
by dialing

**1-800-992-9943**

In Texas: 817/ 483-4422

Call Today for your **FREE** subscription to the 1988 Mouser Electronics Catalog. Contains 176 pages featuring over 16,000 in-stock, quality electronic components.

..PLUS..Mouser's proven service and prompt delivery.  
(Outside U.S.A., Send \$2.)

**MOUSER ELECTRONICS**



**MOUSER ELECTRONICS**

2401 Hwy 287 North  
Mansfield, Texas 76063

**DISTRIBUTION CENTERS NATIONWIDE**

CIRCLE 117 ON FREE INFORMATION CARD

## CABLE-TV



**signal remover**  
50dB NOTCH FILTER

Any\* signal coming in on your cable can be completely "removed" with this powerful filter. Particularly useful on "pay" channels. Also can be used to eliminate any\* over-the-air signal which prevents normal reception. The filter's external adjustments allow precise tuning to any frequency required.

\*AVAILABLE FOR THE FOLLOWING CHANNELS:

MODEL 26 - For any channel between 2 and 6  
(Tuning range 54 - 108 Mhz)

MODEL 713 - For any channel between 7 and 13  
(Tuning range 174 - 216 Mhz)

MODEL 1422 -For any channel between 14(A) and 22(I)  
(Tuning range 120 - 174 Mhz)

★★ ONLY \$30 EACH ★★ 30 DAY FREE TRIAL ★★  
To order, send \$30 check or money order. Specify Model. If not completely satisfied, simply return within 30 days for a full and speedy refund.

★ All models in stock ★ One year warranty  
★ Fast, free delivery ★ Quantity discounts to 50%

**STAR CIRCUITS/DEPT.1-R**  
P.O. BOX 8332, PEMBROKE PINES, FL 33084

# NEW PRODUCTS



CIRCLE 10 ON FREE INFORMATION CARD

### FM DUAL-BAND TRANSCEIVER.

The Kenwood *TW-4100A* is rated for 45 watts on 2 meters and 35 watts on 70 cm. It features selectable full-duplex cross-band ("telephone-style") operation. Cross-band repeater operation is also possible. (A control operator is needed for repeater operation.) In addition, there are programmable band scan and memory scan with

memory-channel lock-out features.

The model *TW-4100A* is 5.9 × 1.97 × 7.87" and weighs less than four pounds. Frequency coverage is 142-149 MHz (allows operation on certain MARS and CAP frequencies), and 440-449.995 MHz. The suggested price is \$649.95. —Kenwood, 2201 E. Dominguez Street, Long Beach, CA 90810.

**DIGITAL MULTIMETER.** The Beckman *DM71* is a handheld pen-type meter that features a 3½-digit display with 0.7% accuracy (2-mV DC range) and auto-ranging; it fits easily into a shirt pocket.

The meter has been designed for ease of use, having a rotary function dial instead of the usual combination-pushbutton operation. A DATA HOLD function allows

the user to manually freeze the display so that it can be read without rushing, or under better lighting conditions. The unit features a 90-hour battery life.


The model *DM71* has a suggested retail price of \$49.94. —Beckman Industrial Corporation, 3883 Ruffin Road, San Diego, CA 92123-1898.



CIRCLE 11 ON FREE INFORMATION CARD

**SWITCH MODULE.** The Iec *SNAP-TEC* is a new approach to mounting data-entry switches directly onto a printed-circuit board without the need for soldering.

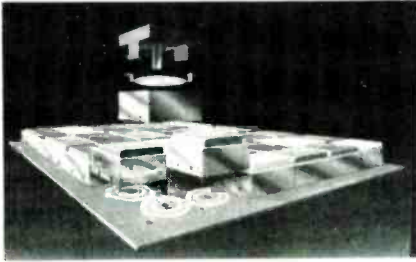Designed for low- to medium-speed switching applications, the *SNAP-TEC* uses a stainless-steel snap-dome mounted in a plastic housing along with a plastic key-cap/actuator. The switch module snaps into two holes in a .062-inch



CIRCLE 12 ON FREE INFORMATION CARD

PC board directly over mating contact circuitry.


Available in a variety of colors and keycap styles, the **SNAP-TEC** can be mounted on .500-inch centers. Custom-designed keycaps are also available. Actuation force is 220 grams with a 0.015-inch nominal travel. The price per unit is under \$0.30 each when purchased in quantities of 1000.—**Tec, Incorporated**, 2727 North Fairview Avenue, P.O. Box 5646, Tucson, AZ 85703.

**CABLE TIES.** Two new cable ties from Panduit, the **PAN-TY** (shown) and the **STA-STRAP**, are double-loop ties whose bent tips provide faster orientation.

Both types are made of natural 6/6 nylon (white), which is U.L. 94-V2 self-extinguishable. They are also available in heat-stabilized nylon (black) and weather resistant outdoor nylon (black). Temperature ranges are  $-40^{\circ}\text{F}$  to  $+221^{\circ}\text{F}$  for heat-stabilized materials and  $-40^{\circ}\text{F}$  to  $+185^{\circ}\text{F}$  for the other two materials.

**PAN-TY** double-loop cable ties are one-piece construction; two sizes are available for up to a maximum combined bundle diameter of 3.8". They have a minimum loop tensile strength of 50 pounds. Prices, which depend on size, start at \$10 per 100.

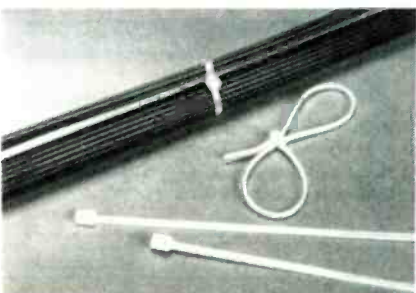**STA-STRAP** double-loop cable ties have a two-piece design, which allows the first loop to be



CIRCLE 13 ON FREE INFORMATION CARD

released prior to final tensioning. That design has zero insertion force and can be hand-installed only. Maximum combined bundle diameter is 1.25"; minimum loop tensile strength is 30 pounds. Pricing depends on size.—**Panduit Corp.**, 17301 Ridgeland Avenue, Tinley Park, IL 60477-0981.

**DEDICATED ADAPTER.** The Program Automation *Surface Mount Adapter*, for Data I/O's 120/121A programmers, can program 10 de-



CIRCLE 14 ON FREE INFORMATION CARD

vices at a time on the upper and/or lower 10 sockets of the programmer, and uses all standard programmer instructions and readouts. For added throughput, two adapters can be used to program 20 devices at a time.

Immediate Delivery

FLUKE

DMM's at SALE PRICES!

**3 1/2 DIGIT 3200 COUNT ANALOG/DIGITAL MULTIMETERS**

**Model 73**  
Value Leader-World's Most Popular DMM-Autoranging  
**\$69** reg. \$79

**Model 75**  
Autoranging + Range Hold Audible Continuity Function  
**\$95** reg. \$109

**Model 77**  
Touch-Hold Feature + Features of Model 75  
**\$125** reg. \$145

**Model 37**  
Bench/Portable, 0.1 VDC Accuracy 10 A Range 2 yr. Warranty  
**\$199** reg. \$229

**4 1/2 DIGIT TRUE RMS HAND HELD**

**Model 8060A**  
Measures True RMS AC Volts & Amps, dB + Frequency from 12 Hz to 200 kHz, Resistance to 300 M  
**\$315** reg. \$359

**Model 8062A**  
Same as 8060A, but Less Frequency & dB  
**\$265** reg. \$295

**40th Year Anniversary Sale**

**Model 77**  
**Model 80218**

**3 YEAR WARRANTY**

**FREE SHIPPING!**  
FREE SHIPPING ON FLUKE TO UPS SHIPPABLE DESTINATION.

**3 1/2 DIGIT HIGH-ACCURACY HAND HELD**

**Model 80218**  
0.25% DC Accuracy, Audible Continuity Function  
**\$149** reg. \$169

**Model 80208**  
0.1% DC Accuracy, Audible Continuity & Conductance Function  
**\$175** reg. \$199

**Model 80248**  
0.1% DC Accuracy, 11 Functions Peak Hold, Temperature  
**\$219** reg. \$249

**Model 80268**  
0.1% DC Accuracy True RMS AC Volts & Current  
**\$195** reg. \$219

**TRUE RMS BENCH DMM'S**

**Model 4010A**  
3 1/2 Digit 10 AMP Range  
**\$255** reg. \$289

**Model 4010A-01**  
With Rechargeable Battery  
**\$295** reg. \$329

**Model 4012A**  
3 1/2 Digit Two Low Ranges  
**\$319** reg. \$359

**Model 8012A-01**  
With Rechargeable Battery  
**\$355** reg. \$399

**Model 8050A**  
4 1/2 Digit Relative Ref. Function 0.03% DC Accuracy  
**\$355** reg. \$399

**Model 8050A-01**  
With Rechargeable Battery  
**\$389** reg. \$439

\*True RMS AC TO 50/ kHz  
\*Conductance Function Checks High Resistance

Send for FREE 480 page "Industrial Products Catalog". I understand it is FREE with any order or if requested on company letterhead. (Otherwise, \$4.95 to cover catalog and shipping costs.)

ORDER TOLL FREE  
**1-800-323-5925**  
IN ILLINOIS  
**312-297-4200**

SINCE 1947

**Joseph Electronics**



**JOSEPH ELECTRONICS, INC.**

8830 N. Milwaukee Ave. Dept. R  
Niles, IL 60648

Rush merchandise per attached order.  
I understand rated accounts are shipped open account; otherwise send per credit card.  
 Visa  Master Card  Discover  
 Check  Money Order  Rush Catalog

Card No. \_\_\_\_\_ Exp. Date \_\_\_\_\_

Name \_\_\_\_\_

Company \_\_\_\_\_

Street Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

IL Res. 7% Tax

# CONNECTION PROTECTION

SWITCHES & RELAYS  
EDGE CONNECTORS  
PLUGS & SOCKETS  
POTENTIOMETERS

CONNECTING CABLES  
TERMINAL STRIPS  
GOLD PLATED CONNECTORS  
BATTERY CONTACTS



## C RAMOLIN®

Even the finest equipment in the world cannot guarantee noise-free operation. One "dirty" connection anywhere in the electrical path can cause unwanted noise or signal loss.

**"MORE THAN A CONTACT CLEANER"**

**C RAMOLIN®** is a fast-acting, anti-oxidizing lubricant that cleans and preserves all metal surfaces, including gold.

When applied to metal contacts and connectors, **C RAMOLIN®** removes resistive oxides as it forms a protective molecular layer that adheres to the metal surfaces and maintains maximum electrical conductivity.

**C RAMOLIN®** - USED BY THOSE WHO DEMAND THE BEST:

Bell & Howell	Hewlett Packard	MC(Sony)	Nakamichi
Boeing	John Fluke Mfg.	Motorola	RCA
Capitol Records	McIntosh Labs	NASA	Switchcraft
			SINCE 1956

**CAIG LABORATORIES** INC.

1175-O Industrial Ave., (P.O. Box J) - Escondido, CA 92025-0051 U.S.A. \* (619) 743-7143

CIRCLE 50 ON FREE INFORMATION CARD

Features include: easy drop-in lock-in adapter; pop-out ejector after programming; vertical sockets for ease of handling and insertion; sockets designed to meet manufacturer's specs and ensure coplanarity; small footprint for ease of handling.

The *Surface Mount Adapter* can be used for production planning of OTP PICC EPROMS, for incoming inspection of preprogrammed parts, and in a maintenance environment for checking questionable parts. It is priced at \$2000.00—**Program Automation, Inc.**, 22706 Aspan, Suite 308, El Toro, CA 92630.

**PRECISION ALIGNMENT KIT.** The Jensen Y23B840 kit contains a selection of precision tools that are manufactured to extremely fine tolerances and are designed for adjustments of VHS and Beta video-cassette recorders.

The kit includes a base-plate reference jig and a height gauge (used for precision height adjustment of the reel discs, guide posts, *continued on page 38*

## NRI's At-Home Training in Electronic Design Technology Can Put You in a High-Paying Career as an In-Demand Design Technician

The best jobs in electronics today go to the people who have the skills to think and work creatively. Conceive and design circuits and equipment. Initiate ideas and carry them through. Now NRI can help you be one of these people—design technicians who command up to \$22,000 as starting salaries, earn \$35,000 or more with experience.

NRI's Electronic Design Technology course starts you with the fundamentals and builds from there to prepare you for an electronics career with real growth potential!

### No Previous Experience Necessary

Even if you've never had any previous training in

electronics, you can succeed with NRI training. You start with the basics, then rapidly build on them to master advanced electronics concepts.

### NRI Circuit Designer Gives You Invaluable Hands-On Experience

The heart of your lab training is the exclusive NRI Circuit Designer you build. It's a totally unique instrument with full breadboarding capability, built-in multiple power supplies, and a multifunction signal generator for circuit testing. Fast, simple connections let you create prototype circuits, immediately check them out for function or faults. Your Circuit Designer will handle both linear and digital integrated circuits as well as discrete components such as transistors and diodes.

### Send for FREE Catalog

Send the coupon today for NRI's free catalog that gives you all the details about the Electronic Design Technology course. If the coupon is missing, please write to



NRI School of Electronics, 3939 Wisconsin Avenue, Washington, DC 20016.

Send coupon today for free NRI catalog.

**NRI** SCHOOL OF ELECTRONICS

McGraw-Hill Continuing Education Center  
3939 Wisconsin Ave. Washington, D.C. 20016


Please send information about NRI training in Electronic Design Technology.

Name \_\_\_\_\_ (Please Print) \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City/State/Zip \_\_\_\_\_ 10-127

Your hands on training includes all this: the unique NRI Circuit Designer, a solderless breadboarding system you build and use for circuit design, prototype construction, component evaluation, and testing... the NRI Model 2500 10 MHz triggered sweep oscilloscope, invaluable in electronic troubleshooting... a TI-30 calculator for fast, accurate computations... and 3 1/2 digit, hand-held digital multimeter you learn to use as professionals do to perform electronic tests and measurements.

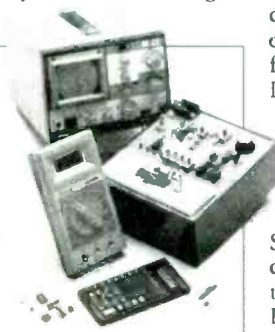


# EQUIPMENT REPORTS
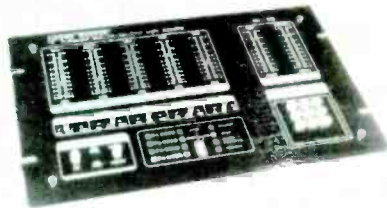
## Mark V SM-328 Professional Color Light Controller

*Control your lights for  
excitement*

IF YOU ARE A PROFESSIONAL DJ—OR IF you just want to pretend you are—you'll be interested in the SM-328 professional light controller from Mark V Electronics, Inc. (248 E. Main Street, Suite 100, Alhambra, CA 91801). The SM-328 can be used for dance-hall lighting, to add chasing lights to advertising dis-



CIRCLE 20 ON FREE INFORMATION CARD

plays, or just to add a new dimension to your parties. The 4-channel controller is a distant relative of the color organs you might remember from the 1960's. It has a power output of better than 1000 watts per channel, so it can be used to control more than forty 100-watt spotlights or more

than 800 5-watt bulbs! But whatever lighting array you choose, there are three main ways that the SM-328 can control it: It can run its own chaser programs, it can control the lights based on an external audio signal, or it can use a combination of the input signal and the chaser program.

### Chaser programs

The SM-328 can run four chaser programs, which can be used for dramatic displays of chasing lights. The first program lights each channel in sequence, with one channel active at a time. The second program does the opposite. It darkens each channel in sequence, while the other three channels appear lighted. The third

## HAMEG

Instruments

**HM 205-2**  
the new Digital Storage Oscilloscope  
with 5 MHz sampling rate and 2 x 1024 / 8 bit storage  
realtime bandwidth DC-20 MHz **\$888.00**

**HM 8148**  
the new intelligent Graphic Printer  
firmware for time, date, interval, linear interpolation  
zooming function **\$788.00**

**DSO Software**  
with 13 programs  
incl. IEEE BUS card **\$480.00**

**call toll free**  
**(800) 247-1241**  
**HAMEG, Inc.**  
88-90 Harbor Road · Port Washington, N.Y. 11050  
Phone (516) 883-3837 · Telex (023) 497.4606

CIRCLE 62 ON FREE INFORMATION CARD

# Test VCR Mechanics Fast and Easy!

Take the guesswork and hassles out of VCR  
mechanical problem diagnosis!  
Four Universal, Powerful Tools for VCR Service

**Tape Tension Gauge:** The Tentelometer® is the world's most universal method of measuring hold back tension. Calibration can easily be checked in the "field". Merely slide the probes over tape to measure tape tension directly in grams. Illustrated instruction manual included. This is the back tension gauge referenced by many of the VCR service manuals, and it will work on all VCRs.

T2-H7-UM \$295



**Video Head Protrusion Gauge:** Universal, fast, safe method of measuring the amount of video head tip wear. Measures in microns and ten-thousandths of an inch. Allows accurate predictions of remaining head life. Head wear provides useful information regarding VCR condition and wear on other components. Stop guessing about head wear. Accessory "S1" stand allows use on any VCR.

HPG-1 \$479 S1 \$95



**Spindle/Elevator Gauge:** The TSH gauge inserts into the VCR just like a cassette. The new TSH-V5 performs 6 critical measurements to eliminate tape binding and edge damage. This gauge quickly locates problems that can't even be detected by other methods. Fully illustrated instruction manual is included.

TSH-V5 for VHS: \$395



**Torque Gauge:** A universal, inexpensive, accurate torque gauge for VHS and Beta VCRs. Calibrated in Gram-Centimeters both clockwise and counterclockwise. Complete with easy-to-follow, detailed instruction manual for VHS recorders. Includes a modified VHS cassette for ease-of-use.

Complete System  
TQ-600 \$139



Tentel® provides the most powerful, easy-to-use, field calibratable, universal VCR test equipment available for various mechanical tests. Call our application engineers today for answers to your questions. Ask about the combination discount when ordering all 4 gauges.

**Tentel Corp.**

1506 Dell Avenue  
Campbell, CA 95008

(800) 538-6894  
(408) 379-1881  
in California

CIRCLE 198 ON FREE INFORMATION CARD

## SUPER LONG PLAY TAPE RECORDERS

10 Hour Model - \$95.00\*  
14 Hour Model - \$159.00\*

Modified Panasonic Slimline,  
high quality, AC-DC  
Recorders provide 5 or 7  
continuous hours of quality  
recording & playback on  
each side of cassette for a  
total of 10 or 14 hours  
depending on model. Built-in  
features include: • Voice  
level control. • Digital  
counter, etc. TDK DC 180  
Cassette Furnished.



### PHONE RECORDING ADAPTER

Records calls automatically. All Solid  
state connects to your telephone  
jack and tape recorder. Starts  
recording when phone is lifted.  
Stops when you hang up.

\$24.50\*

FCC APPROVED

### VOX VOICE ACTIVATED CONTROL SWITCH

Solid state. Self contained. Adjust-  
able sensitivity. Voices or other  
sounds automatically activate and  
control recorder. Uses either re-  
corder or remote mike.

\$24.95\*

\*Add for ship & hdg. Phone Adapter & Vox \$1.50 ea.  
Recorders \$4.00 ea. Cal. Res. add tax. Mail order, VISA,  
MIC, COD'S OK. Money Back Guarantee. Qty. disc.  
avail. Dealer Inquiries invited. Free data.  
AMC SALES, Dept. A 9335 Lubec  
St., Box 928, Downey, CA  
(213) 90241 Phone  
869-8519

## ATTENTION! ELECTRONICS TECHNICIANS

EARN YOUR  
**B.S.E.E.  
DEGREE**



### THROUGH HOME STUDY

Our New and Highly Effective Advanced-Place-  
ment Program for experienced Electronic Tech-  
nicians grants credit for previous Schooling and  
Professional Experience, and can greatly re-  
duce the time required to complete Program and  
reach graduation. No residence schooling re-  
quired for qualified Electronic Technicians.  
Through this Special Program you can pull all of  
the loose ends of your electronics background  
together and earn your B.S.E.E. Degree. Up-  
grade your status and pay to the Engineering  
Level. Advance Rapidly! Many finish in 12  
months or less. Students and graduates in all 50  
States and throughout the World. Established  
Over 40 Years! Write for free Descriptive Lit-  
erature.

## COOK'S INSTITUTE OF ELECTRONICS ENGINEERING



347 RAYMOND ROAD  
P.O. BOX 20345  
JACKSON, MISSISSIPPI 39209

CIRCLE 189 ON FREE INFORMATION CARD

program lights two channels at a time and alternates back and forth between them. Finally, the fourth program also lights two channels at a time, but in a sequence of 1-2, 2-3, 3-4, 4-1. The speed of the chasing is controlled by a lighted slide potentiometer.

The chaser program and its operating modes are selected via a 9-button keypad. For example, an AUTO control mode can be selected to automatically vary the time that each channel remains lighted; or, a slide potentiometer can be used to manually control the on-off timing. The direction of the chase is also controlled from the keypad.

### Music control

By connecting the SM-328 in parallel with one of your loudspeakers, you can use the audio signal fed to the speaker as the controlling source for the lights. The actual audio level is unimportant because the SM-328 will accept signals ranging from 100 millivolts to 28 volts (or a maximum of 100 watts of audio power). Since the SM-328 has a high impedance (bridging) input it has no effect on either the speaker or its associated amplifier.

A MASTER LEVEL control allows the user to adjust the overall brightness of the lamps in proportion to the volume of the music input. Alternately, the user can create unusual or customized lighting effects, even "ride gain" on the effects, because each channel has its own level control—a lighted slide control.

The output of each channel's level control feeds an op-amp filter that determines the channel's frequency response. One channel responds to treble frequencies, one to midrange frequencies, and two channels respond equally to bass frequencies. The op-amps, in turn, control optically-coupled Triacs. In addition to a level control, each channel features a three-position slide switch that can be used to instantaneously dim or cut the light.

Some of the most interesting and eye-catching lighting displays can be obtained by using a music signal to control the execution of the light-chaser programs.



## Good layout

The front panel is specifically designed to be used in dim lighting—even in virtual darkness. For example, only those potentiometers that can be used in a given mode are lighted in that mode. Also, the brightness of the level-control potentiometers changes with the music signal in its channel. But while the LED's that illuminate the potentiometers can be used for quick set-up adjustments, they aren't adequate for use as an overall lighting guide; for *precise* lighting control it's still necessary to view the actual lights.

We found the keypad switches difficult to use. Their tactile feedback was very poor, and the keys did not always do what they were supposed to. However, we were able to clear up the problem by disassembling the case and cleaning the switch contacts. Other than the keypad, the SM-238 is solidly constructed, and its solid metal 14-inch rack-mount case can take a good amount of abuse. The controller carries a suggested list price of \$150. R-E

## LETTERS

*continued from page 26*

### SCA RECEIVER

I'm glad to see that **Radio-Electronics** is showing an interest in FM subcarriers, with "Build This SCA Receiver" in the August 1987 issue. The authors mention that SCA is inherently "noisy." However, with the Signetics' 565 PLL (whose basic design the authors follow) most of the noise is due to the unnecessarily wide bandwidth inherent in the SCA receiver design published in the Signetics' application notes.

Ironically, that wide-bandwidth noise shows up mostly in more advanced SCA receivers, such as the one featured in **Radio-Electronics**, that amplify the signal before input to the PLL. Below 100 mV, the lock range (thus, the capture range as well) decreases with decreasing input voltage. Therefore, a simple receiver accepting a weak SCA signal of 10-20 mV has build-in bandwidth limiting. In general, however, increased input voltage will improve the 565's demodulation characteristics (AM reception,

etc.).

Fortunately, there is a simple solution to the wide-bandwidth-noise problem in advanced SCA receivers: reduce the lock range by connecting a 25K potentiometer between pins 6 and 7 of the 565. While some people will enjoy having direct control of the bandwidth from the "front panel," it turns out that simply shorting pins 6 and 7 (minimum lock range) gives acceptable results.

I have one more suggestion: substituting a 470-pF capacitor for C43 and a 4.7K resistor for R55 will give the 10K potentiometer (R72) sufficient range to tune both the 92-kHz and the 67-kHz SCA subcarriers.

The above discussion notwithstanding, designing an SCA receiver with the Signetics 565 is much more straightforward than with Exar's XR2211. But I did find the reward—a portable receiver that works from a single supply of 4.7-6 Volts—to be worth the effort of using Exar's model.

GIL ROBERTS  
Duarte, CA

## Need Quick Turnaround on CRYSTALS?

Try Our E.O.D.  
(Emergency Order Dept.)

and get

**JAN QUALITY  
and STABILITY  
PLUS Low Prices!**



You benefit from 21 years of manufacturing quality crystals for industry, military services, radio amateurs, citizen band and experimenters.

To Get Free Catalog  
Call or Write

**JAN CRYSTALS**  
P.O. Box 06017  
Ft. Myers, FL 33906  
(813) 936-2397

CALL 1-800-237-3063  
FREE (Except Florida)

CIRCLE 104 ON FREE INFORMATION CARD

# Performance Tools.

**Our AR-130A is always ready**—thanks to intelligent Auto-Power-Off circuitry.

- Ideal multi-purpose meter
- 20 Amp AC/DC capability
- Transistor hFE measurement
- Gold plated PC board reliability



AR-130A

**Our AR-170 NI sets new standards**—

- in telecommunications & audio equipment testing.
- Direct dBm reading (600 ohms) of systems noise level measurement
- True RMS AC measurement
- High accuracy: 20 mV, 20  $\mu$ A and 20 ohm range
- 1% DC accuracy



AR-170 NI

**Our AR-460 D is an advanced ICR meter**

- rivaling bench instruments in both accuracy and cost—
- Directly measures "dissipation", leakage in a capacitor and Q in an inductor
- Ideal for QA and engineering labs
- Inductance to 2H, capacitance to 200  $\mu$ F, resistance to 20 Mega Ohms



AR-460D

**THE American Reliance line of Test and Measurement Equipment has been getting the job done all over the world for nearly a decade. For the location of a distributor in your area, call us for more information.**

**800-654-9838**

American Reliance Inc., 9241 E. Valley Blvd.  
Rosemead, CA 91770 • FAX: (818) 287-8855



ARI/VALUE BEYOND MEASURE

CIRCLE 195 ON FREE INFORMATION CARD

**AMERICAN  
RELIANCE INC.**

## 87" HI-TECH SALE

**Cobra Stun Gun** generates 45,000 volts of stopping power, the Cobra also delivers a burst of high intensity light directly into an attackers eyes. Chances are that his optic nerves will be so overdosed with excess light energy that he will not be able to see you let alone continue the attack. If he does, the Cobra delivers its painful bite, leaving him dazed and confused. \$49.95. With NiCad battery & charging kit \$59.95 + \$3.74 shp.

### Centron Security Light

The Centron security light puts unwelcome visitors in the spotlight... instantly! This smart lighting system's infrared sensors guards your yard or driveway when you're away or home alone. It senses the presence of people or cars by changes in temperature patterns and instantly floods the area with bright light. It guides your guest to your door and scares away would-be prowlers \$55.00 plus \$4.99 shipping.

### Remote Control Pen.

Not only is it a hand-some high quality ball point writing pen, but a powerful remote-control device. Effective at distances up to 75 yds, the Remote Control Pen is perfect for turning on or off any 120 volt appliance or alarm system. Think of the possibilities. \$39.00 shipping \$3.74.

### The Private Eye Motion Detector.

Alarm warns you to the presence of an intruder but the intruder doesn't know he has been detected. No wires just plug it in and it works. Information travels from the detector to the receiver via the electrical system. \$63.00 shipping \$5.40

World's smallest dialer \$49.95 Alcohol Breath Analyzer \$59.00  
Levigator \$79.95 Telemonitor 2000 ..... \$175.00  
Pistol Cross Bow \$59.95 Remote Car starter..... \$225.00

**\*\*All products ready to use and Guaranteed\*\***


ORDERS CALL TOLL FREE 1-800-624-1150 For information or free catalog call 402-554-0383 or write United Imports & U.S. Mfg. 6846 Pacific St. Omaha, Nebraska 68106



CIRCLE 53 ON FREE INFORMATION CARD

## NEW PRODUCTS

continued from page 34

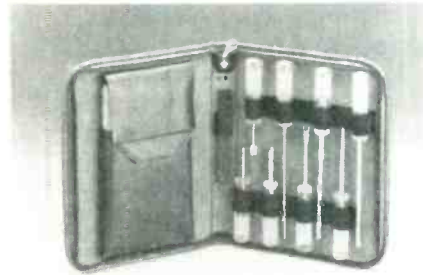


CIRCLE 15 ON FREE INFORMATION CARD

tape transport, pinch wheel audio, synchronization, and erase heads), and an eight-piece driver/wrench set with precisely configured bits for adjusting the tape-teed guide, tape-tension heads, tape transport, audio, and control heads.

The tools are furnished in a padded, vinyl zipper case having elastic straps to hold the drivers and the height gauge. A velcro-closure pouch holds the base-plate reference jig. Case size is 10 × 8 × 1½".

The kit is priced at \$169.00—Jensen Tools, Inc., 7815 S. 46th St., Phoenix, AZ 85044.

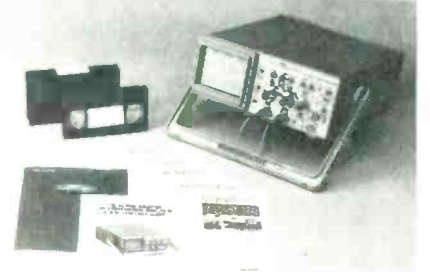**PORTABLE OSCILLOSCOPE.** The Tektronix 2225 is a 50-MHz scope, and comes with a library of support material that includes a demonstration video tape, a full-color



CIRCLE 16 ON FREE INFORMATION CARD

brochure, a 36-page primer (*The XYZ's of Using a Scope*) and five technical briefs on oscilloscope measurements.

Viewers of the video tape will see demonstrations of the model 2225's dual-channel operation, alternate horizontal magnification, 500-microvolt sensitivity, and extensive triggering features. The

# Fluke breaks the old mold.



Dollar for dollar the Fluke 37 breaks into the market with more features for the money than any other bench DMM. It's bold new design includes built-in handle and storage compartment, and it has all the high performance features of the world's best, most reliable 3½-digit DMMs.

Autoranging, to eliminate guesswork. Audible Continuity, so you don't have to look at the display. An exclusive analog and digital display. Superior EMI shielding. Plus a two-year warranty.

And, how many other bench/portable meters give you these features? Min-Max recording, for monitoring signals. 38 components dedicated exclusively to input protection. Relative mode, to help you calculate changes in readings. And Fluke's patented Touch Hold, to give you an extra set of hands when you're taking critical measurements.

None. Only the Fluke 37.

For more information call 1-800-426-0361.



© 1986, Fluke


CIRCLE 121 ON FREE INFORMATION CARD

# Walk "Tough Dog" Troubles Out Of Any TV & VCR In Half The Time . . . Guaranteed!

primer provides a study guide that expands on all aspects of the scope's operation and use. The technical briefs provide further details on specific measurement methods—period, frequency, phase, risetime, amplitude, etc.

The model 2225 is priced at \$995.00.—Tektronix, P.O. Box 500, Beaverton, OR 97077.

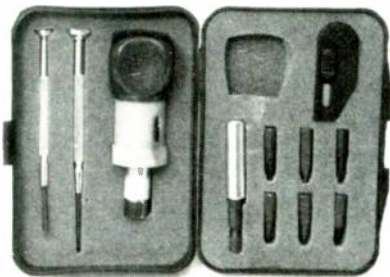**RATCHET TOOL SET.** Electronic Technology Today's Cuecraft 716 consists of a reversing and locking ratchet handle having an integral 1/4-inch socket wrench/driver-holder and a fingertip shaft-spinner, number 1 and 2 Phillips-head drivers, 3/16" and 1/4" flat-blade drivers,



CIRCLE 18 ON FREE INFORMATION CARD

and two Torx drivers in sizes that are commonly used in automobiles and appliances. A 2 3/8-inch handle extension is also provided for the times when you need a little extra reach or torque.

The set also includes 3/16" and 1/8" flat-blade screwdrivers for miniature screws, and a fingertip slide-knife. All parts fit inside a form-fitted, foam-lined 4 3/8" x 3 3/16" x 1 1/16" hard-plastic travel case.

Price is \$12 postpaid. New York residents must add appropriate sales tax.—Electronic Technology Today, Inc., P.O. Box 240, Massapequa Park, NY 11762-0240



with the exclusive, patented  
VA62 Universal Video Analyzer™ . . . \$3,495

Would you like to . . .

**Reduce your analyzing time?** Isolate any problem to one stage in any TV or VCR in minutes, without breaking a circuit connection, using the tried and proven signal substitution method of troubleshooting.

**Cut costly callbacks and increase customer referrals by completely performance testing TVs and VCRs before they leave your shop?** Own the only analyzer that equips you to check all standard and cable channels with digital accuracy. Check complete, RF, IF, video and chroma response of any chassis in minutes without taking the back off the receiver or removing chassis, plus set traps dynamically and easily right on the CRT.

**Reduce costly inventory from stocking yokes, flybacks, and other coils and transformers for substitution only, with the patented Ringing Test?** Run dynamic proof positive test on any yoke, flyback, and integrated high voltage transformer.

**Protect your future by servicing VCRs for your customers before they go to your competition?** Walk out "tough dog" troubles in any VCR chrominance or luminance circuit to isolate problems in minutes. Have proof positive tests of the video record/play heads before you replace the entire mechanism.

**Have one piece of test equipment that doesn't need replacing every time technology changes?** Be able to service Stereo TVs & VCRs profitably, and get in on the ground floor of this growing market with exclusive phase-locked accessories.

**Find out how the VA62 Universal Video analyzer will make servicing easier and more profitable in your shop?** Call WATS Free 1-800-843-3338 and ask your area Sales Engineer for a "Try before you buy" 10 Day Self Demo or a full color brochure and join the many servicers already on the road to more profitable servicing with the VA62.

Universal Video Analyzer is a trademark of Sencore, Inc.



WATS Free 1-800-843-3338 In Canada WATS Free 1-800-851-8866

## SENCORE

**Means Success In Electronic Servicing**

3200 Sencore Drive, Sioux Falls, South Dakota 57107

Call Collect 605-339-0100 In SD & AK

CIRCLE 176 ON FREE INFORMATION CARD

# AUDIO UPDATE

## Can you believe your ears?



LARRY KLEIN,  
AUDIO EDITOR

THE TERM "PSYCHOACOUSTICS" HAS recently become a prominent part of the audio vocabulary. But despite the fact that its use seems mostly reserved for those devices that are designed, electrically or acoustically, to enhance stereo imaging, as we've discussed in previous columns, the term covers much more than that. The study of psychoacoustics specifically involves the relationship of the *subjective* sensations of the human ear/brain mechanism to *objective* acoustical events.

The significant differences between the subjective and objective worlds of sound are illustrated nicely by the inconsistent ways in which the ear responds to frequency and intensity—or in psychoacoustic terms, *pitch* and *loudness*. Three examples: (1) More than fifty years ago Harvey Fletcher demonstrated that the subjective judgment of the pitch of a pure tone can be shifted as much as 10% by simply varying the intensity of the sound. (2) Aside from the pitch shift, as shown in Fig. 1, the human ear's sensitivity to low- and high-frequency ranges diminishes disproportionately as the volume (intensity) of the sound is reduced. The loudness controls found on most amplifiers and receivers are meant to compensate for that fact. (3) Most of us are aware that the ear does not respond linearly to increases in the intensity of the stimulus. For example, the measured acoustic power of a sound has to be raised about *ten times* before the average person hears it as merely *twice* as loud.

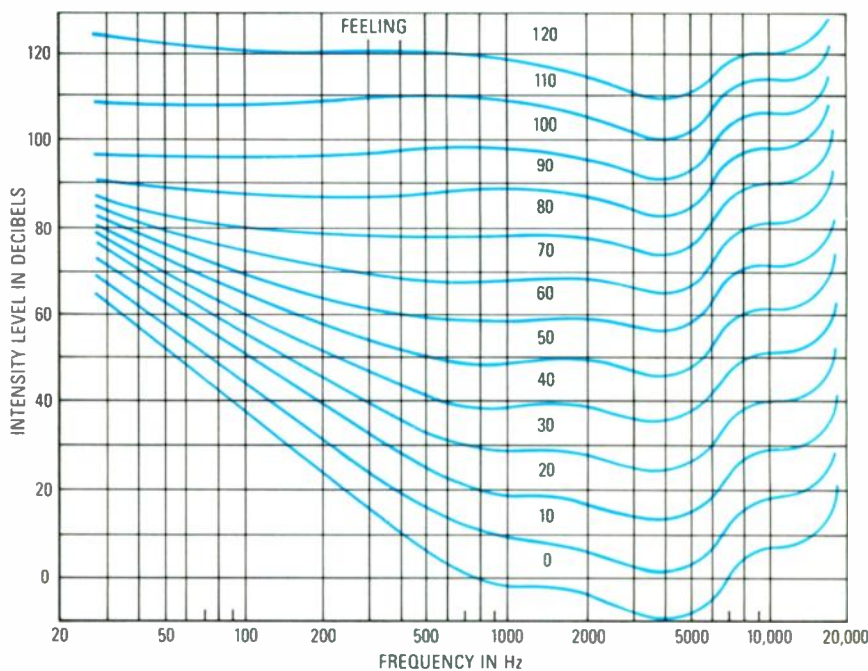


FIG. 1

Those are only three of the psychoacoustic peculiarities of human hearing, and I'm sure that most of you have read discussions of such matters before. But what is not generally appreciated is that the stereo-reproduction process itself is a totally artificial phenomena dedicated to deceiving the ear's psychoacoustic sound-localization process. Think about it—where in nature do you encounter two widely spaced, discrete sound sources each producing a portion of the sound that is heard as coming from *between* them?

### Localization

Two main differences between the sounds reaching each ear are

used for localization: time-of-arrival differences, and sound-pressure-level (SPL) differences. In general, differences in arrival times are used to localize the lower-frequency sound sources, SPL differences are used for the higher frequencies; the crossover point between the two is about 1,200 Hz.

There's a good reason why the ear/brain uses (actually, needs) at least two different sound cues for localization. For high- to mid-frequency audio wavelengths, your head is an acoustic barrier that partially blocks the sound reaching the ear most distant from the sound source. The measured difference at the ears is something like 16 dB at 5,000 Hz, falling to

Discover How The World's Only  
**100% Automatic, Dynamic, & Portable**  
**LC Analyzer Gives You Total Confidence**  
**In Your Cap/Coil Testing . . .**  
**Call 1-800-843-3338 Today!**



**LC77 AUTO-Z™**  
**Automatic Capacitor and Inductor Analyzer**  
**Double Patented \$1,895**      **IEEE - 488**

The first cap/coil analyzer guaranteed to reliably test anywhere, without calculations, look-up tables, or error — 100% automatically so you're confident of your accuracy.

Do you want to eliminate doubt from your cap/coil testing? The LC77 AUTO-Z tests all key parameters with results anyone can understand. Automatic good/bad results eliminate the guesswork for error-free analysis. Touch-sensitive keypad and one-two-three setup makes your AUTO-Z the easiest and fastest LC analyzer on the market.

Are you frustrated trying to test the new high-tech caps/coils used in modern electronics? Only the LC77 AUTO-Z allows you to test them all. Test capacitors from 1 pf to 20 farads, with leakage tests to 1000 V and ESR to 2000 ohms for locating failures other testers miss. Inductor value from 1 uh to 20 H and a patented ringing test for dependable, error-free coil testing every time.

Do you need the freedom of a battery-operated portable LC meter? The LC77 is 100% battery portable for use in the field or factory. The full power and potential of the LC77 AUTO-Z is packed into a light-weight, portable package. The AUTO-Z puts the complicated electronics on the inside for ease of operation on the outside.

Do you want maximum efficiency with a bus compatible LC testing system? Your LC77 AUTO-Z is IEEE 488 compatible for automated cap/coil analysis for data collection, incoming inspection, and quality assurance tests.

Be satisfied that you can meet all the challenges new technology brings. Call WATS Free 1-800-843-3338 today and tell your Area Sales Engineer you want to "try before you buy" with Sencore's exclusive 10 Day Self Demo.

AUTO-Z is a trademark of Sencore, Inc.

WATS Free 1-800-843-3338 In Canada WATS Free 1-800-851-8866



**SENCORE**

**Means Success In Electronic Servicing**

3200 Sencore Drive, Sioux Falls, South Dakota 57107  
 Call Collect 605-339-0100 In SD & AK

CIRCLE 177 ON FREE INFORMATION CARD

about 7 dB at 1,000 Hz. When the frequency is low enough (the wavelengths long enough), the head is no longer an adequate baffle and approximately the same signal level is heard by both ears. However, your brain is still sensitive to the relative timing of the signals reaching each ear, even though there's only about a 0.6-millisecond difference when the source is located fully on one side of your head. That fraction of a millisecond difference provides the brain with the data needed for localization. When the audio wavelengths get very long—below 200 Hz or so—arrival time differences also disappear and localization is completely lost. That, by the way, explains why subwoofers operating below 200 Hz can be installed almost anywhere in the room without confusing the directional information.

**Sonic masking**

Most noise-reduction techniques rely on psychoacoustic masking to help achieve their ends. Masking describes the ear's loss in sensitivity to sounds in one frequency area when there are louder sounds within the same, or adjacent octaves. Hiss is not heard when there is a lot of music going on in the octaves at or adjacent to the hiss frequencies. Only when the musical frequencies are low (a drum or cello solo), intermittent (a solo piano or guitar), or absent, does hiss become obtrusive. Obviously, the task of a noise-reduction circuit is eased if it has to cope with hiss only in the absence of masking musical sounds.

Masking can be a severe problem in a car because the music gets obscured by wideband wind and tire noises, rather than vice versa. The soft passages in a wide-dynamic-range compact disc will inevitably be masked unless player volume is turned up high enough to override the road noise. But with the volume turned up that high, the louder passages are likely to be unbearably loud! I've not seen any indication that the manufacturers of CD car units recognize the problem and are about to install switchable dynamic-range attenuator (compression) circuits

*continued on page 45*

# STATE OF SOLID STATE

An electronic potentiometer



ROBERT F. SCOTT,  
SEMICONDUCTOR EDITOR

UPON HEARING OR READING THE words potentiometer or *pot*, we immediately think of a variable resistor having a rotary control shaft. But this is the age of electronics, and a potentiometer need no longer be a mechanical device adjusted by turning a shaft; it can be an electronic device that uses small voltages to emulate a potentiometer. One kind of device that can do that is Xicor's *E<sup>2</sup>POT* Digitally Controlled Potentiometer, which is available in several different versions as the X9MME 8-pin miniDIP series of solid-state non-volatile potentiometers. Basically, the device functions as a digitally-controlled trimmer resistor.

A digitally-controlled potentiometer can be adapted to many applications where mechanical potentiometers or digital-to-analog circuits cannot be used, or would be inconvenient to use. For example:

- It provides for automatic potentiometer calibration or adjustment on an assembly line.
- It eliminates the need for manual adjustments of mechanical potentiometers.
- It makes possible remote control via a keyboard of variable adjustments, such as volume and brightness.
- It simplifies adjustment or control of a remote device via a radio, LAN, or modem link.

## 99 resistors

The device is essentially an array composed of 99 resistive elements with 100 tap points that are accessible to the "wiper" element. (100

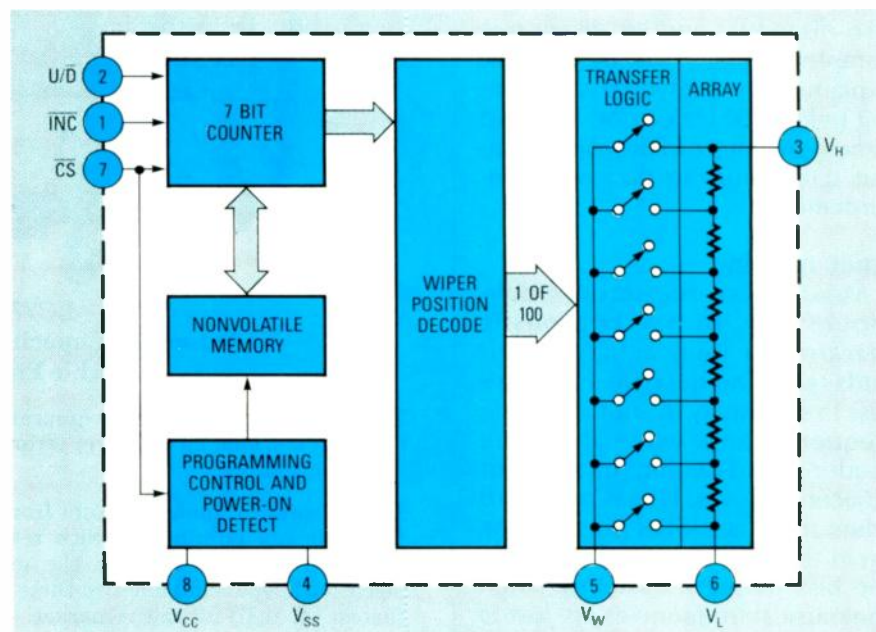


FIG. 1

TABLE 1

Mode Selection	Mode	Power
CS   INC   U/D		
L   $\sim$   H	Wiper Up	Active
L   $\sim$   L	Wiper Down	Active
$\sim$   H   *	Store Wiper Position	Active

\* equals high or low

points because the taps are located between adjacent resistor elements and at each end of the resistor string.) The X9MME's functional diagram and pinout are shown in Fig. 1. The wiper's position is digitally controlled by TTL-Level voltages on the  $\overline{CS}$ ,  $U/D$ , and

$\overline{INC}$  inputs. Table 1 shows the mode selection. The position data is stored in a non-volatile memory and is automatically recalled on power-up. The memory is capable of retaining the wiper position data for 100 years.

The X9MME *E<sup>2</sup>POT* is available in three versions, each having different value ranges. The X9103P is 10K, the X9503P is 50K, and the X9104P is 100K. The resolution—the value between tap points—equals the maximum end-to-end resistance divided by 99, or 101, 505, and 1010 ohms for the X9103P, X9503P, and X9104P, respectively.

Other *E<sup>2</sup>POT*'s features include:

- Single-chip MOS implementation
- Three-wire TTL control

- Operation from a 5-volt supply
- Analog voltage range of  $\pm 5$  volts
- Temperature compensation for  $\pm 20\%$  of end-to-end resistance range
- Wiper current of 1-mA maximum
- Typical wiper resistance 40 ohms at 1 mA
- Resolution 1% of resistance

For information on pricing and availability of the E<sup>2</sup>POTS's, write to *XICOR INC.*, 851 Buckeye Court, Milpitas, CA 95035.

### New 8-bit D/A converter

The ZN438 is a new low-cost monolithic D/A converter that requires only two external passive components for full 8-bit conversion. Features include a trimmable 2.5-volt bandgap reference, which is also available externally for use as a system reference. A trim pin can be left floating to provide the nominal 2.5 volts, or it can be connected to a 10K potentiometer to provide a  $\pm 5\%$  trim range. The ZN438 has a settling time to  $\pm 0.5$  LSB of 1.25  $\mu$ sec.

The ZN348E device is available for commercial applications in a 16-lead plastic DIP package, and is priced at \$5.44, in 1000-piece lots. The ZN348J is ceramic packaged and operates in the military temperature range. Price is \$10.37 each, in 1000-piece lots. For additional information, contact *Ferranti Semiconductors*, 87 Modular Avenue, Commack, NY 11725.

### CMOS megabit memory

In the Mega-Project, in conjunction with Philips, Siemens is producing the first laboratory samples of a CMOS memory chip with more than 4-million bits of storage capacity. The project's 1-Megabit DRAM will be mass-produced at Siemens' Regensburg facility this year; followed by the 4-Megabit DRAM in 1989. The 4-Megabit chip stores 4,194,304 bits on a surface of 91 mm<sup>2</sup> (6.5 mm  $\times$  14 mm). It features the novel "trench cell"—a trench not wider than 1  $\mu$ m (1/1000 mm) etched 4  $\mu$ m deep into the silicon.

### 1987 data book

The 320-page *1987 Data Converters and Voltage References* data book features information on 27 A/

Call 1-800-843-3338 today  
to start thoroughly analyzing  
and pinpointing any trouble in any  
**TV-RF distribution system,**  
automatically to FCC specifications . . .



with the All New  
**FS74 CHANNELIZER SR.™ TV-RF Signal Analyzer**  
Patents Pending \$3495

Does your success in servicing RF distribution systems depend on locating problems quickly and accurately? If so, here's why your all new Sencore FS74 CHANNELIZER SR. will mean success for you . . .

**Quickly tune in all TV/FM channels from 5 MHz to 890 MHz.** Exclusive all channel, microprocessor-controlled digital tuner checks every standard and cable channel with better than FCC accuracy to fully analyze any system.

**Exclusive 5 microvolt sensitivity to bring in even weak signals.** Autoranged attenuator automatically selects the best sensitivity for simplifying your VHF, UHF, or FM signal measurements like never before possible.

**Automatic hassle-free S/N ratio, A/V ratio, and hum level tests.** Exclusive on-channel signal-to-noise ratio test eliminates time-consuming signal comparison and chart reading. Exclusive audio-to-video ratio test measures directly in dB for easy comparison to specifications.

**Exclusive checks for ghosts, co-channel interference, line reflections, and other signal quality checks.** Portable 4 MHz wideband battery-operated monitor lets you finally check the quality of your cable or MATV system and stop annoying callbacks.

**Built-in autoranging AC/DC volt/ohmmeter makes troubleshooting a snap.** Exclusive all-weather design holds tighter than FCC specifications from  $-4^{\circ}$ F to  $+104^{\circ}$ F. Truly portable, field-tested tough for dependable ease of use.

Begin successfully locating TV-RF signal problems more quickly and accurately than ever before possible, with the new FS74 CHANNELIZER SR. Call WATS Free 1-800-843-3338 today for a free Product Guide or an industry exclusive "Try before you buy" 15 Day Self Demo.

"CHANNELIZER SR." is a trademark of Sencore, Inc.



WATS Free 1-800-843-3338 In Canada WATS Free 1-800-851-8866

**SENCORE**

**Means Success In Electronic Servicing**

3200 Sencore Drive, Sioux Falls, South Dakota 57107

Call Collect 605-339-0100 In SD & AK

CIRCLE 178 ON FREE INFORMATION CARD

# Crystek Crystals

**FOR OPTIMUM STABILITY  
AND RELIABILITY IN  
FREQUENCY MANAGEMENT**

## QUARTZ CRYSTALS FOR

### Industrial Equipment/Instrumentation

- Micro-processor control
- Computers/Modems
- Test/Measurement
- Medical



### General Communications

- Channel element Service (VHF/UHF)
- Land Mobile 2-way
- Marine
- Aircraft
- Telemetry
- Monitors/Scanners/Pagers



### Amateurs/2-Meter/General Coverage CB/Hobblist/Experimenter



## The Pulse of Dependable Communications

Crystek Crystals offers their new 16 page FREE catalog of crystals and oscillators. Offering state of the art crystal components manufactured by the latest automated technology. Custom designed or "off the shelf." Crystek meets the need, worldwide. Write or call today!

## CRYTEK CORPORATION

DIVISION OF WHITEHALL CORPORATION

2351/2371 Crystal Drive • Ft. Myers, FL 33907  
P.O. Box 06135 • Ft. Myers, FL 33906-6135

**TOLL FREE 1-800-237-3061**

**PH 813-936-2109/TWX 510-951-7448/FAX 813-939-4226**

**TOLL FREE IN THE U.S.A. EXCEPT FLORIDA, ALASKA, HAWAII**

CIRCLE 187 ON FREE INFORMATION CARD

## MOVIE TIME



V-7200



## CABLE CONVERTERS

### 72 Channel Wireless Remote Cable Converter

Remote Fine Tuning . . . Fine Tune Centering . . . Last Channel Recall  
Favorite Channel Memory . . . HRC/Standard Switch . . . 2/3 Switchable  
90 Minute Sleep Timer . . . Switchable AC Outlet . . . 12 Mo. Warranty  
Compatible with all CABLE DECODERS . . . . . ONLY \$79.95

V-430 Video Control Center wireless Remote Switcher, with 4 Inputs and 3 Outputs . . . . . \$79.95

### MOVIE TIME, V-7800

78 Channel Remote Converter (same features as the V-7200) + Parental Control and built in 10 DB Amplifier. 24 Mo. Warranty . . . . . \$89.95

Replacement Hand Units for the JERROLD 400 or 450 . . . . . \$24.95

Shipping Charge \$5.50 per order. We accept AMERICAN EXPRESS, COD or Personal Checks. Checks must clear prior to shipping.

**Dealer Inquiries Welcome  
Call 1-305-652-3971**

### MOVIE TIME

**1-305-652-1981 20203 NE 15 Ct.  
1-800-843-9845 Miami, FL 33179**

30 DAY MONEY BACK GUARANTEE

CIRCLE 199 ON FREE INFORMATION CARD

D converters (including 16 new devices), 20 new D/A converters, and 11 voltage references from Maxim Integrated Products. A complete product listing, converter selector guides, and package information selector guides, and package information sections are also included.

For a free copy of the 1987 *Data Converters and Voltage References* data book, contact a Maxim sales representative or distributor, or call Customer Service direct at 408/737-7600. *Maxim Integrated Products* 510 N. Pastoria Avenue, Sunnydale, CA 94086.

### New Hall-effect switches

Sprague has developed a new sensor chip that makes possible the new UGN/UGS-3119, UGN/UGS-3120, and UGN/UGS-3140 monolithic Hall-effect switches that are less susceptible to mechanical stress and have better stability over their operating temperature ranges than earlier Hall-effect devices.

The 3119 is recommended for applications that provide steep magnetic slopes and low residual levels of magnetic flux density. The 3120 is for applications that require precise switch points. The 3140 is for use with small inexpensive magnets or for applications where there are relatively large distances between the magnet and the Hall cell.

The UGN types are rated for operation over the  $-20^{\circ}\text{C}$  to  $+85^{\circ}\text{C}$  temperature range. The UGS series has an operating range of  $-40^{\circ}\text{C}$  to  $+125^{\circ}\text{C}$ . All types are offered in two 3-pin plastic SIPS—a 60-mil thick (1.54 mm) "U" package and a 80-mil-thick (2.03 mm) "T" package. They also come in SOT 89 (TO-24AA) packages and in hermetically sealed 3-pin ceramic packages.

The UGN-3119, -3120, and -3140 are priced at \$0.47, \$0.50, and \$0.81, respectively in lots of 100. The UGS-3119; -3120, and -3140 are priced at \$0.79, \$0.90, \$1.20 each, respectively.

For detailed technical information, request Data Sheets 26621, 27622, and 27627 from Technical Literature Service, *Sprague Electric Co.*, P.O. Box 9120, Mansfield, MA 02048-9120.

R-E



## AUDIO UPDATE


continued from page 41

in their players; but it seems to me that they are a necessity. The compression circuit could even be controlled by the brake system and arranged so that compression would be *off* when the car is stopped and *on* when it is moving. Or better yet, let's stay with cassettes—which to my mind are far more sensible for car use. At least one manufacturer (NAD) is producing a cassette deck with a novel car-tape recording feature. When the circuit is switched in, cassettes are recorded with both compression and equalization to compensate for both the noise and the special acoustics of the automotive environment.

As might be surmised, I'm all for psychoacoustic manipulation of the stereo signal if greater realism can be achieved. I've long since given up any hope of being able to provide facsimile reproduction in my home of an original acoustical event. I would be content with a reproduced musical performance that sounded *plausible*. In other words, it might have been heard that way live in some other acoustic space and time. Plausible reproduction, in my use of the term, is not easy to achieve. Perhaps half a dozen times in my 30 years of audio involvement have I experienced the acoustic illusion "I am there" or "they are here." And in almost every case, for it to succeed, the illusion required multiple channels or binaural headphone reproduction.

I hope this brief guided tour through some of the mysteries of psychoacoustics has been interesting, instructive, and has provoked some appreciation of what it takes to delude your ears into believing that they are hearing music freshly produced without artificial preservatives. Psychoacousticians are well aware that they do not as yet have all the answers as to how to hear. However, I'm convinced that there's an R&D *Twilight Zone* inhabited by a few special psychoacoustically-oriented equipment designers from whose joint efforts the audio millennium will one day emerge. R-E
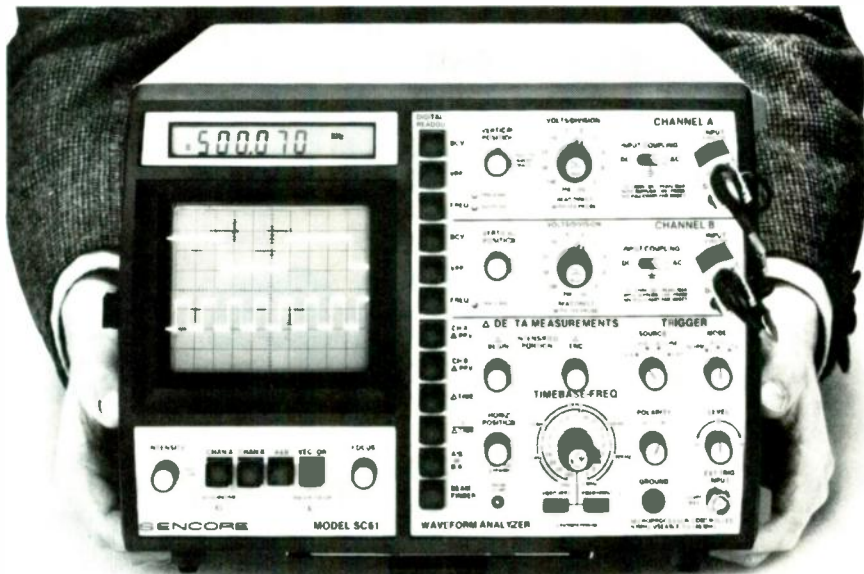
## Analyze defective waveforms faster, more accurately, and more confidently — every time or your money back



with the SC61 Waveform Analyzer  
Patented \$2,995

If you value your precious time, you will really want to check out what the exclusively patented SC61 Waveform Analyzer can do for you. 10 times faster, 10 times more accurate, with zero chance of error.

**End frustrating fiddling with confusing controls.** Exclusive ultra solid ECL balanced noise cancelling sync amplifiers, simplified controls, and bright blue dual trace CRT help you measure signals to 100 MHz easier than ever.

**Accurately and confidently measure waveforms from a tiny 5 mV all the way to a whopping 3,000 V without hesitation** with patented 3,000 VPP input protection — eliminates expensive "front end" repairs and costly equipment downtime.

**Make only one circuit connection and push one button for each circuit parameter test:** You can instantly read out DC volts, peak-to-peak volts and frequency 100% automatically with digital speed and accuracy. It's a real troubleshooting confidence builder.

**Confidently analyze complex waveforms fast and easily.** Exclusive Delta measurements let you intensify any waveform portion. Analyze glitches, interference signals, rise or fall times or voltage equivalents between levels; direct in frequency or microseconds.

**Speed your digital logic circuit testing.** Analyzing troublesome divide and multiply stages is quicker and error free — no time-consuming graticule counting or calculations. Simply connect one test lead to any test point, push a button, for test of your choice for ERROR FREE results.

To see what the SC61 can do for your troubleshooting personal productivity and analyzing confidence, CALL TODAY, WATS FREE, 1-800-843-3338, for a FREE 15 day Self Demo.



Call Today Wats Free 1-800-843-3338

**SENCORE**

3200 Sencore Drive  
Sioux Falls, SD 57107  
605-339-0100 In SD Only

*innovatively designed  
with your time in mind.*

CIRCLE 179 ON FREE INFORMATION CARD

# Information radio is on the air.



**B**efore you hear about it on your old radio, hear it live on your new Informant Information Radio. Whether it's an all-points-bulletin from the State Police, the dispatcher for the city's Fire Department, an ambulance racing to the hospital or a National Weather Service report, the new Informant from Regency makes you a part of all the action... instantly.

*Breakthrough Technology. Instant Information.*

Informant Information Radio uses a revolutionary new technology that allows you to constantly monitor your police, fire and



emergency frequencies, as well as NOAA weather information channels in all 50 states. All pre-programmed. This new Information Radio utilizes a principle similar to the seek and scan feature found on expensive AM/FM radios. Your information radio scans the public service channels in the area, locates the active signals, locks in and broadcasts all the information right to you. With revolutionary TURBO-SCAN speed!

*Hear Your Hometown Like You've Never Heard it Before.*

Just turn it on. As easy to use as your AM/FM radio. Instantly, you're tuned into real life adventures. One touch control lets you select and hold police, fire and emergency broadcasts so you don't miss a single minute of the action.

Hear the amazing Information Radio today. Take it home and be a part of the action tonight!!



*Information Radio for Real Life Adventure*



# BUILD THIS

THOMAS L. JOZWIAK

# ELECTRONIC XMAS TREE




*This pocket-size electronic Christmas tree will give your holiday lighting a new and festive look.*

FOR ABOUT \$10 YOU CAN BUILD A UNIQUE high-tech Christmas tree that will add a new and festive look to both your home and office holiday decorations. And because it's powered by two AA batteries, if you can't be home for the holidays you can pack one along in a suitcase to remind you of your loved ones.

The electronic Christmas tree is really a 6½-inch high tree-shaped printed-circuit board that's outlined by what appears to be randomly-blinking red, green, and yellow LED's. The tree's trimming is the components for the electronic circuit that makes the LED's wink and blink. The Christmas tree's base consists of two AA-size battery holders cemented together with the tree's PC board sandwiched between the two. A little imaginative spray painting before the components are installed puts a realistic finishing touch to the Christmas-tree project.

Because the LED's are continuously cycled *on* and *off*, two alkaline batteries provide more than 300 hours of continuous operation: that's enough to provide almost two full weeks of window display or entertainment before the batteries need to be replaced.

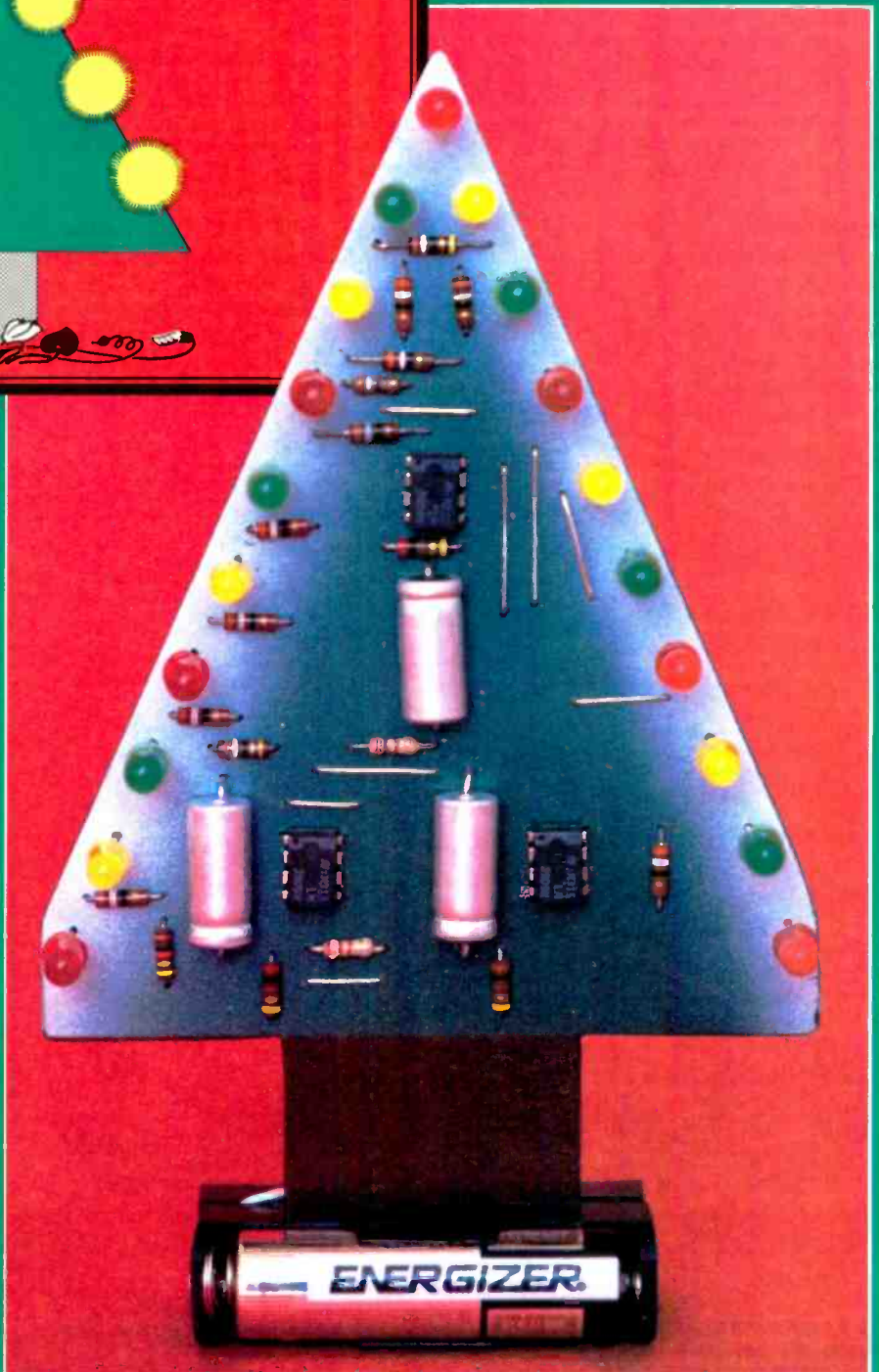

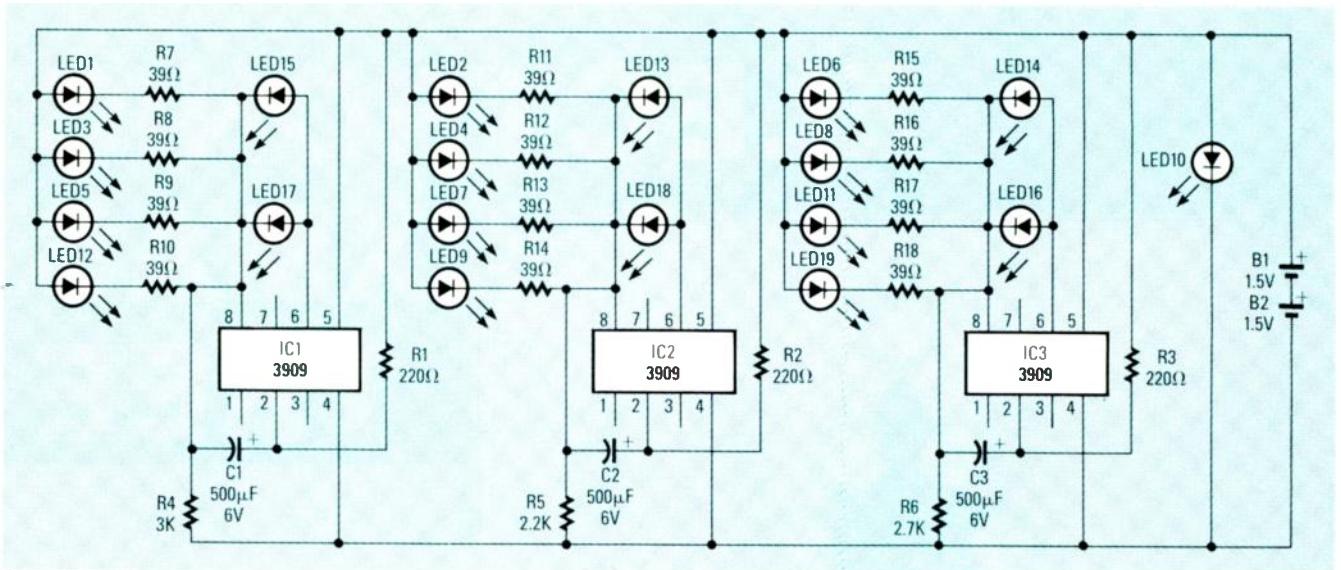


FIG. 1—THREE INDIVIDUAL FLASHER CIRCUITS having unrelated flash rates create a pseudo-random blinking of the LED's because the LED's from each individual circuit are intermixed around the edges of the tree.

### How it works

As shown in Fig. 1, three individual flashing circuits that use an LM3909 LED flasher/oscillator IC create the appearance of a pseudo-random firing order. The combination of C1-R4, C2-R5, and C3-R6 control the blink rate, which is between .3 and .8 second, while the inherent wide

tolerance range ( $-20\%$  to  $+80\%$ ) of standard electrolytic capacitors add to the irregularity of the blink cycles. The continuous current drain is about 10 mA; however, if you decrease the values of R4-R6 or C1-C3 in order to increase the blink rate, the current will then increase proportionately.

### PARTS LIST

All resistors are 1/4-watt, 5%.

R1-R3—200 ohms

R4—3000 ohms

R5—2200 ohms

R6—2700 ohms

R7-R18—39 ohms

#### Capacitors

1-C3—500  $\mu$ F, 6 volts, electrolytic

#### Semiconductors

IC1-IC3—LM3909, LED flasher

LED1, LED4, LED7, LED13, LED16, LED19—Red, diffused 5-mm LED

LED2, LED5, LED6, LED11, LED14, LED17—Yellow, diffused 5-mm LED

LED3, LED6, LED9, LED12, LED15, LED18—Green, diffused 5-mm LED

LED10—Red flasher LED (Radio Shack 270-401 or equivalent)

#### Other Components

B1, B2—1.5-volt AA alkaline battery

Miscellaneous: battery holders, PC board, wire, solder, etc.

**Note:** An etched and drilled PC board is available for \$10 postpaid from Fen-Tek P.O. Box 5012, Babylon, NY 11707-0012. NY residents must add appropriate sales tax.

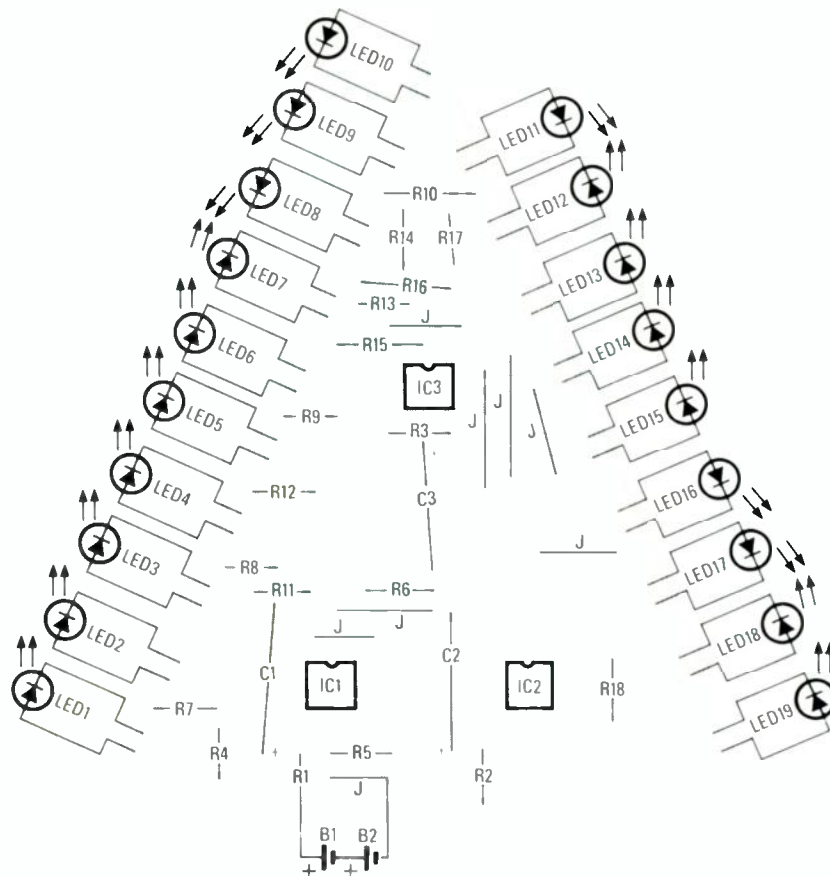


FIG. 2—TAKE EXTRA CARE THAT THE LED'S are installed with the correct polarities. If you want to decorate the "tree", do it before drilling the mounting holes for the components.

Note in particular that external current-limiting resistors aren't needed for LED13 through LED18; the resistors are built into the IC's. LED10, which serves as the tree's "star," is a special kind of flashing LED that blinks continuously at a fixed rate.

Power can be turned off by simply removing either battery, or by slipping a small piece of paper between any battery and either of its battery-holder terminals. Of course, a switch can also be added.

*continued on page 82*



## MACROVISION STABILIZER

*Are copy-protected video tapes also mucking-up normal viewing on your TV? Then use a Macro-Scrubber to make the picture squeaky-clean.*

D. DUPRE

YOU ARE PROBABLY ALREADY AWARE that the movie industry has launched a new front against video tape copying with a new "encoding" scheme called *Macrovision*. Although many new releases from Embassy, CBS/Fox, MGM/UA, HBO/Cannon, MCA, and Disney have been protected with it, its use is generally not advertised on the label. However, you can easily identify a *Macrovision*-processed tape by turning the vertical hold control on your TV (if your set has one) so that the black bar across the top of the picture becomes visible. If the signal contains *Macrovision* encoding, you will see five or six gray or white pulsating "boxes" on the left side of the black bar.

According to a top *Macrovision* executive, plans are already in the works to transmit *Macrovision*-encoded signals through cable systems.

The basic idea behind the *Macrovision* process is to render the program material uncopyable to a VCR while allowing the unimpaired viewing of the original tape (a goal not achieved by the original *CopyGuard* system, which has since passed away). Although some proponents of the *Macrovision* process claim that the system meets those goals, numerous consumers who have either purchased or rented a number of *Macrovision*-encoded tapes can attest to the contrary. That is evidenced by the large influx of letters to

magazines predominant in the video field, and by continuous complaints to video rental and retail stores.

Both the users and developers of the *Macrovision* process admit that some TV's and VCR's are adversely affected in the PLAY mode, but that that percentage is very small. So, if you are one of the "small percentage" you probably have a significant sum of money invested in the best features that state-of-the-art video has to offer; yet with it you wind up watching a dark, murky picture that may be flashing, rolling or streaking as well.

If you're among the users who have discovered that your VCR or TV equipment simply can't handle the so-called

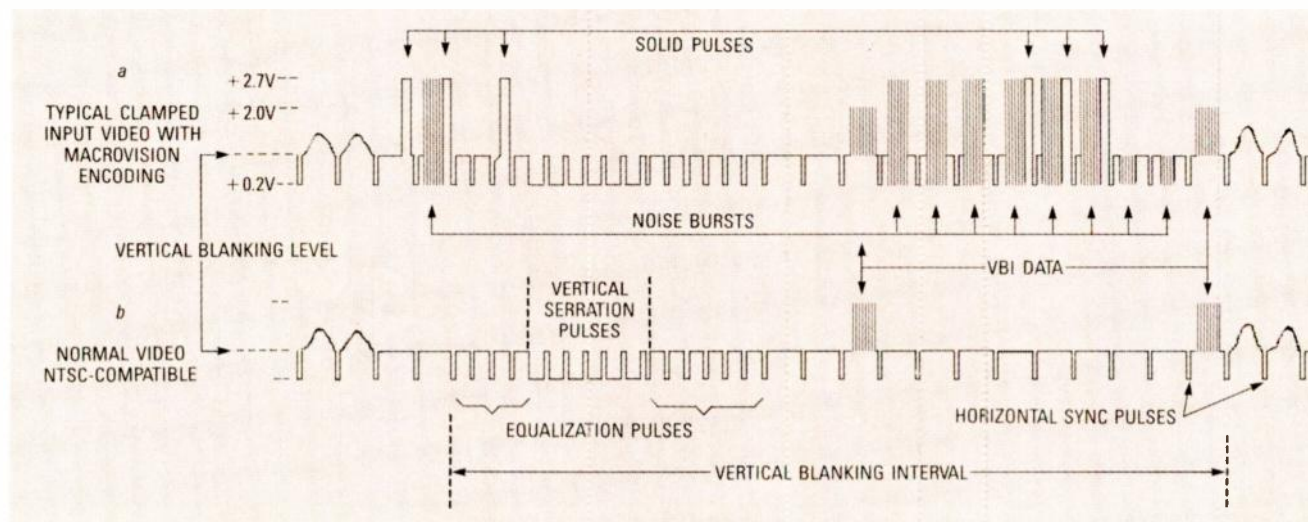


FIG. 1—MACROVISION DELIBERATELY injects interference during the vertical-blanking interval (a). The Macro-Scrubber restores the signal to standard NTSC (b).

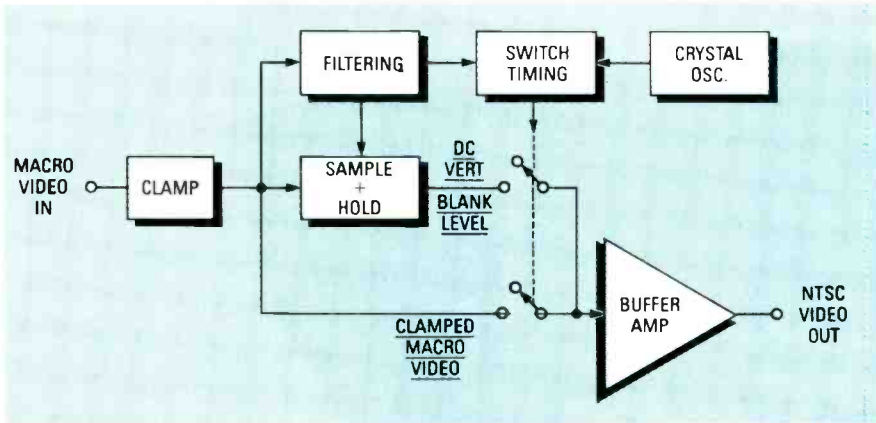


FIG. 2—AN ELECTRONIC DPDT SWITCH is used to restore the video signal to the conventional NTSC format.

“invisible” Macrovision encoding, then you need the Macro-Scrubber, a device that simply eliminates the encoding. Plug the device between your VCR and its TV or monitor and you won’t know that Macrovision even exists.

### Macrovision encoding

Macrovision is not an encoding process at all. If it were, then an appropriate decoder would have to be made available to the consumer just so he could view a Macrovision-encoded tape. In fact, the video information remains intact and unmodified in the signal, as does the audio. The encoding is really a disturbance in the TV signal’s vertical-blanking interval that is supposed to affect only a VCR attempt-

ing to copy the tape. Unfortunately, the encoding also affects some TV’s. By simply eliminating the disturbance and returning the offending signal to normal NTSC standards you can view a completely normal picture while playing a Macrovision-processed tape.

As shown in Fig. 1, the Macrovision process merely injects noise bursts and solid pulses into the signal during selected line times within the vertical blanking interval. One possible form of Macrovision encoding is shown in Fig. 1-a; the same signal in conventional NTSC form is shown in Fig. 1-b. The peak level of the bursts is randomly varied from black to white. Sometimes the bursts are pumped between two or three different levels; at

### WARNING

Duplication of copyright material is prohibited by law. The Macro-Scrubber is recommended for use only between a VCR and its TV or monitor as a solution to viewing problems that are generated within the TV or the monitor by Macrovision encoding.

other times the burst level is ramped slowly up and down. The location of the injected noise is also randomly alternated between the available line times; however, the location and level of solid pulses usually remains constant for the duration of a particular title—thus all copies of a particular title have the same encoding.

The Macrovision irregularities created during the vertical retrace time are intended to upset a VCR’s record-mode AGC circuit so that it records an unviewable picture. Since a VCR is designed to record only the NTSC video signal—which contains no noise transitions during the vertical blanking interval—any fast irregularities in the vertical blanking interval cannot be tracked by the AGC.

The effectiveness of the Macrovision anti-copying system varies with the type of VCR used, but in general, synchronization is lost, leaving an unviewable picture on the attempted copy. At best, the resulting dubbed copy will exhibit erratic brightness changes. Sometimes the picture will roll vertically due to a noise burst injected just before vertical sync.

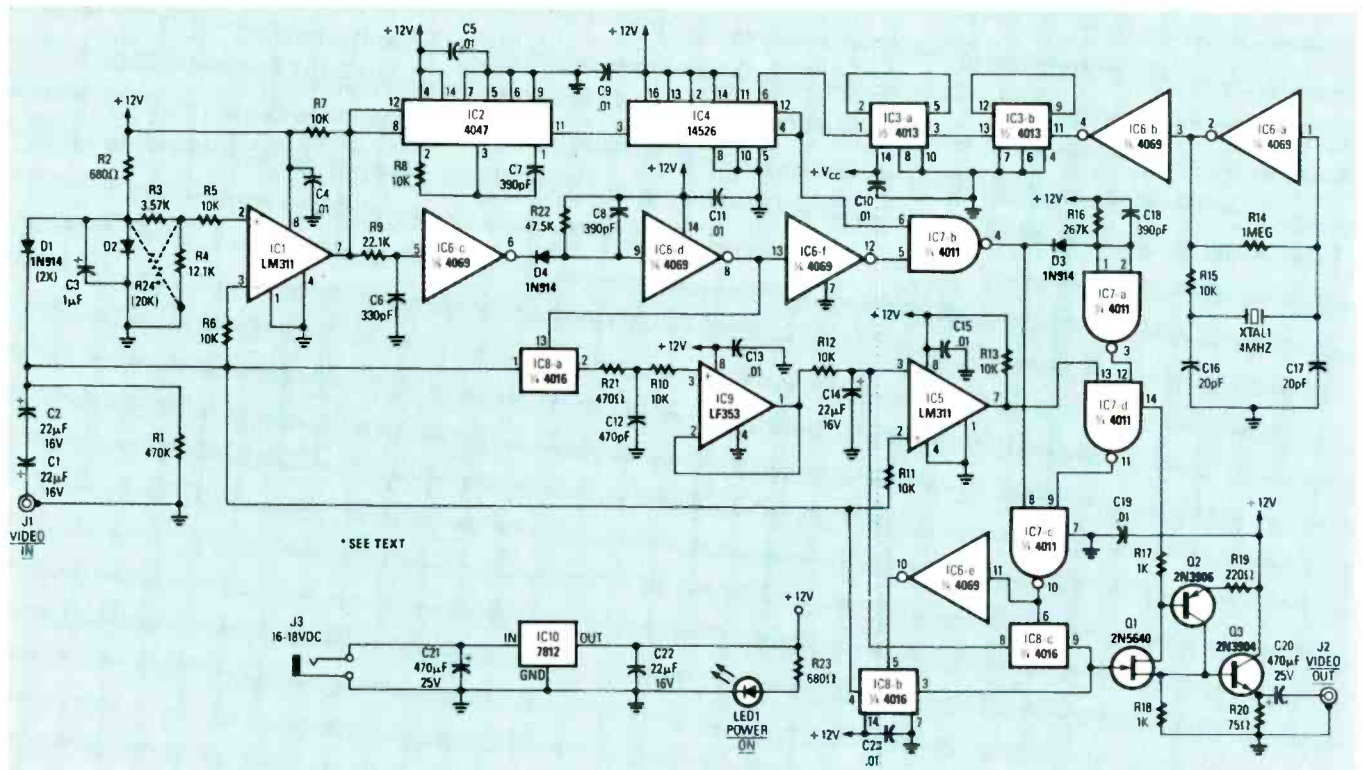


FIG. 3—THE INPUT-SIGNAL LEVEL must be within a specified range for the Macro-Scrubber to work properly. If there is some problem with the input-signal level it is suggested that R24—shown with dashed lines—be substituted for R3 and R4.

## COMPLEX IS REALLY BETTER

The majority of devices sold with a purpose similar to that of the Macro-Scrubber either blank or clip the entire vertical-blanking interval, which also removes any other VBI data (color correction signals, closed captions, teletext, etc.). They then attempt to economically reconstruct the entire vertical-blanking interval, including horizontal sync, equalization, and serration pulses. From a technical viewpoint, that is often not very successful because the characteristics of the reconstructed pulses are usually set to some form of "standard" value, and as such do not really match the actual input signal. Since those units do not actually detect and selectively remove the *Macrovision* noise, they also strip the vertical-blanking interval of a normal TV signal if not bypassed or removed from the system.

Many models also require factory-type calibrations of numerous timing potentiometers. Their new blanking level is either preset to some kind of standard value or an external adjustment is provided to compensate for signals from different video tapes or sources.

What makes the Macro-Scrubber unique, when compared to the restoration devices, is that there are no precision adjustments; digital filters remove only the *Macrovision* pulses and pass the original vertical-blanking interval data and sync pulses, while sample-and-hold circuits reproduce the correct vertical-blanking level, which is switched into the output signal in place of *Macrovision* pulses. Also, the use of a crystal oscillator eliminates the need for timing adjustments. And since the Macro-Scrubber has no effect on normal video signals, there is no need to switch the Macro-Scrubber out of the system for normal viewing.

Unfortunately, similar symptoms sometimes are experienced when merely playing the original tapes on some VCR/TV combinations.

### A logical solution

In comparing Figs. 1-a and 1-b, you can

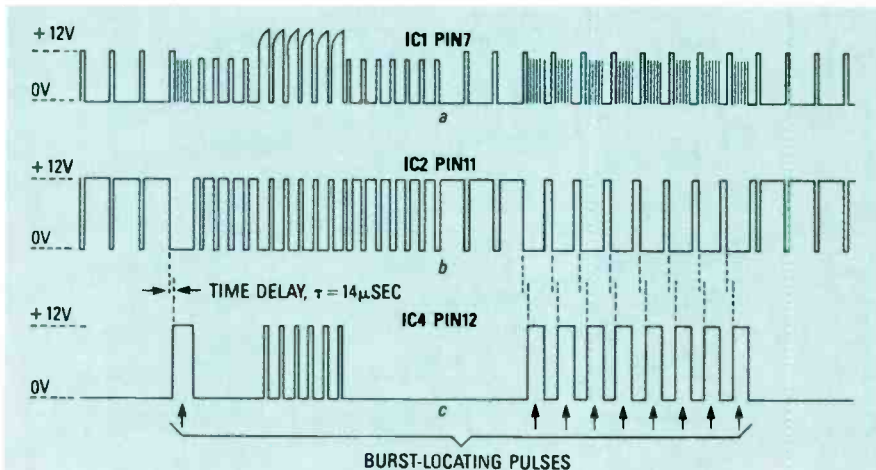


FIG. 4—THE MACRO-SCRUBBER GENERATES noise pulses which are used to locate and suppress the *Macrovision* noise-burst interference.

see that a normal NTSC video waveform is held at the vertical blanking level during times when injected noise exists in the *Macrovision*-encoded waveform. By locating the individual noise bursts and solid pulses, and by connecting the output to a DC voltage that is equivalent to the vertical blanking level at those times, we can essentially recreate the NTSC version of the waveform. When no encoding signals are present, we connect the output to the clamped video input.

Figure 2 shows a block-diagram of how the encoding can be removed. First, the incoming video signal is clamped to hold the negative sync tips at the same level, thereby removing any AC hum or other time-varying offset from the signal; that step is critical for detecting signal transitions against a fixed reference level. The clamped video is then sent to a filtering circuit to accurately locate the noise bursts and the solid pulses from which the switch-timing and the control signal are created. (A crystal oscillator is used so that timing adjustments aren't necessary.)

The sample-and-hold circuit continuously samples the video waveform to generate a DC voltage equivalent to the vertical blanking level of the incoming signal. That assures that the switched-in blanking level is always correct for the actual input signal applied and eliminates the need for any manual adjustment. Finally, an electronic double-pole, single-throw switch that is controlled by the noise-locating signal connects either the clamped input video or the reproduced blanking level to the output buffer amplifier. In so doing, *Macrovision* noise is eliminated and the signal is restored to normal NTSC video.

### Circuit description

Figure 3 shows Macro-Scrubber's circuit. The *Macrovision*-encoded video signal is applied to jack J1 and is fed through back-to-back capacitors C1 and C2 to a resistor/diode network that clamps the negative sync tips close to ground poten-

## PARTS LIST

All resistors are 1/4-watt, 5% unless otherwise noted.

R1—470,000 ohms  
R2, R23—680 ohms  
R3—3,570 ohms, 1%  
R4—12,100 ohms, 1%  
R5—R7, R10—R13, R15—10,000 ohms  
R8—10,000 ohms, 1%  
R9—22,100 ohms, 1%  
R14—1 Megohm  
R16—267,000 ohms, 1%  
R17 R18—1,000 ohms  
R19—220 ohms  
R20—75 ohms  
R21—470 ohms  
R22—47,500 ohms, 1%  
R24—20,000 ohms, trimmer potentiometer

### Capacitors

C1, C2, C14, C22—22  $\mu$ F, 16 volts, electrolytic  
C3—1  $\mu$ F, 35 volts, electrolytic  
C4, C5, C9—C11, C13, C15, C19, C23—0.01  $\mu$ F, ceramic disk  
C6—330 pF, NPO  
C7, C8, C18—390 pF, silver mica  
C12—470 pF, polypropylene  
C16, C17—20 pF, NPO  
C20, C21—470  $\mu$ F, 25 volts, electrolytic

### Semiconductors

IC1, IC5—LM311 comparator  
IC2—4047B multivibrator  
IC3—4013B dual D flip-flop  
IC4—4526B binary counter  
IC6—4069B hex inverter  
IC7—4011B quad NAND gate  
IC8—4016B quad analog switch  
IC9—LF353 dual JFET op-amp  
IC10—7812, 12-volt regulator  
Q1—2N5640, JFET transistor  
Q2—2N3906, PNP transistor  
Q3—2N3904, NPN transistor  
D1—D4—1N914, switching diode  
LED1—Light-emitting diode

### Other components

XTAL1—4-MHz crystal, AT cut (parallel), HC-18 package

J1, J2—RCA-type phono jacks

Miscellaneous: PC board materials, 16-18-volt, 200-mA AC adapter, etc.

**Note:** A complete Macro-Scrubber kit, model MAK-7, which includes the PC board, cabinet, all components, and an AC adapter, is available for \$52.95 plus \$3.00 shipping and handling from: The Hobby Helper, P.O. Box 308, Bridgewater, MA. 02324. (617) 339-1026. Massachusetts residents must add appropriate sales tax.

tial (approximately 0.2 volt). The clamped video input applied to IC1's inverting input (pin 3) resembles the waveform shown in Fig. 1-a. A DC reference voltage derived from diode D2 is fed to IC1's non-inverting input (pin 2). Since the DC reference is slightly higher than the clamped video input, IC1's output goes positive whenever the input signal is lower than the reference signal. As shown in Fig. 4-a, IC1 outputs a waveform that is normally low (0 volts) with high-going pulses con-

current with negative-going pulses below the vertical-blanking level (i.e. horizontal-sync pulses, equalization pulses, vertical-serration pulses, and *Macrovision* noise bursts).

The clamped video signal is also delivered to the input of a sample-and-hold circuit, which consists primarily of analog switch IC8-a, hold capacitor C12, and op-amp IC9. The switch is driven in such a way that it samples the level of the video signal only during vertical-sync time at the peaks of the vertical-serration pulses. The output of IC9 is a DC voltage equal to the vertical-blanking level, which will be switched into the output waveform in place of the *Macrovision* noise bursts and solid pulses.

Clamped input video is fed to the input of analog switch IC8-b, and the DC output voltage from IC9 is fed to the input of analog switch IC8-c. Notice that the outputs of analog switches IC8-b and IC8-c are connected together, and that because of inverter IC6-e, their control inputs at pins 5 and 6 respectively are driven 180° out of phase. That arrangement creates the electric equivalent of a single-pole, double-throw switch, with either the clamped input video or a DC voltage that is equal to the vertical-blanking level being fed to buffer amplifier Q1 at any one time.

It is through control of the electronic DPDT switch shown in Fig. 2 that the encoded video is restored to a normal NTSC signal. All that is needed is a proper signal to pin 6 of IC8.

The signal from IC1 pin 7 (Fig. 4-a), which contains pulses that correspond to the sync and the *Macrovision* noise pulses, is fed to IC2 pins 8 and 12. IC2 is a multivibrator that is configured as a digital low-pass filter. The time constant determined by R8 and C7 causes frequencies greater than twice the horizontal frequency to be filtered out. IC2's output at pin 11 looks like a squared-up and inverted version of its input, except that the high-frequency pulses corresponding to the *Macrovision* noise bursts have been filtered out, leaving a low level for each burst duration. (See Fig. 4-b).

The filtered signal is fed to pin 3 (ENABLE) of binary counter IC4. A 4-MHz crystal-oscillator circuit feeds dual flip-flop IC3, which divides the crystal frequency by four, yielding a 1-MHz clock input to IC4 pin 6. When the input at IC4 pin 3 goes high, that counter is asynchronously preset to the binary value determined by preset lines P3, P2, P1, and P0 (pins 2, 14, 11, and 5 respectively). With the connections shown in Fig. 3, the preset count is 14 decimal (1110 binary). Whenever the count is not zero, the counter decrements once for each clock pulse it sees on pin 6 while pin 3 remains low. Thus, 14  $\mu$ s after the leading, negative-going edge of the input signal on pin 3 goes low, the count reaches 0 and the counter's output switches high. The high output is fed back to pin 4, the INHIBIT line, which prevents any further counting.

When the input signal at pin 3 returns high, the counter is again preset to a 14 count and the output returns to its low preset state. Low input pulses having a duration less than 14  $\mu$ sec are ignored because the counter is preset before the count ever reaches zero.

The resulting output signal at IC4 pin 12 is normally low, with high-going pulses that start 14  $\mu$ s after the beginning of each horizontal-sync pulse that precedes a *Macrovision* noise burst. The 14  $\mu$ sec delay forces the horizontal sync pulses (and color-bursts) to be switched into the output waveform. Each of the noise-burst locating pulses returns to a low at the end of the corresponding *Macrovision* burst. Those pulses, as shown in Fig. 4-c, define the points in time when the bursts occur, with one exception. Concurrent with the vertical-serration pulses, there are a string of pulses that must be removed in order to create a signal that will totally isolate the *Macrovision* noise. In order to remove those pulses we must create a gating signal with a single pulse that lasts only for the duration of the vertical sync pulse in each frame. To do that, sync and noise pulses from IC1 pin 7 (Fig. 4-a) are fed to a low-pass filter consisting of R9 and C6.

Narrow, positive-going pulses are attenuated because C6 never gets a chance to charge to a logic-high level unless the pulses are long compared to the time constant determined by R9 and C6. The only pulses wide enough to allow C6 to charge

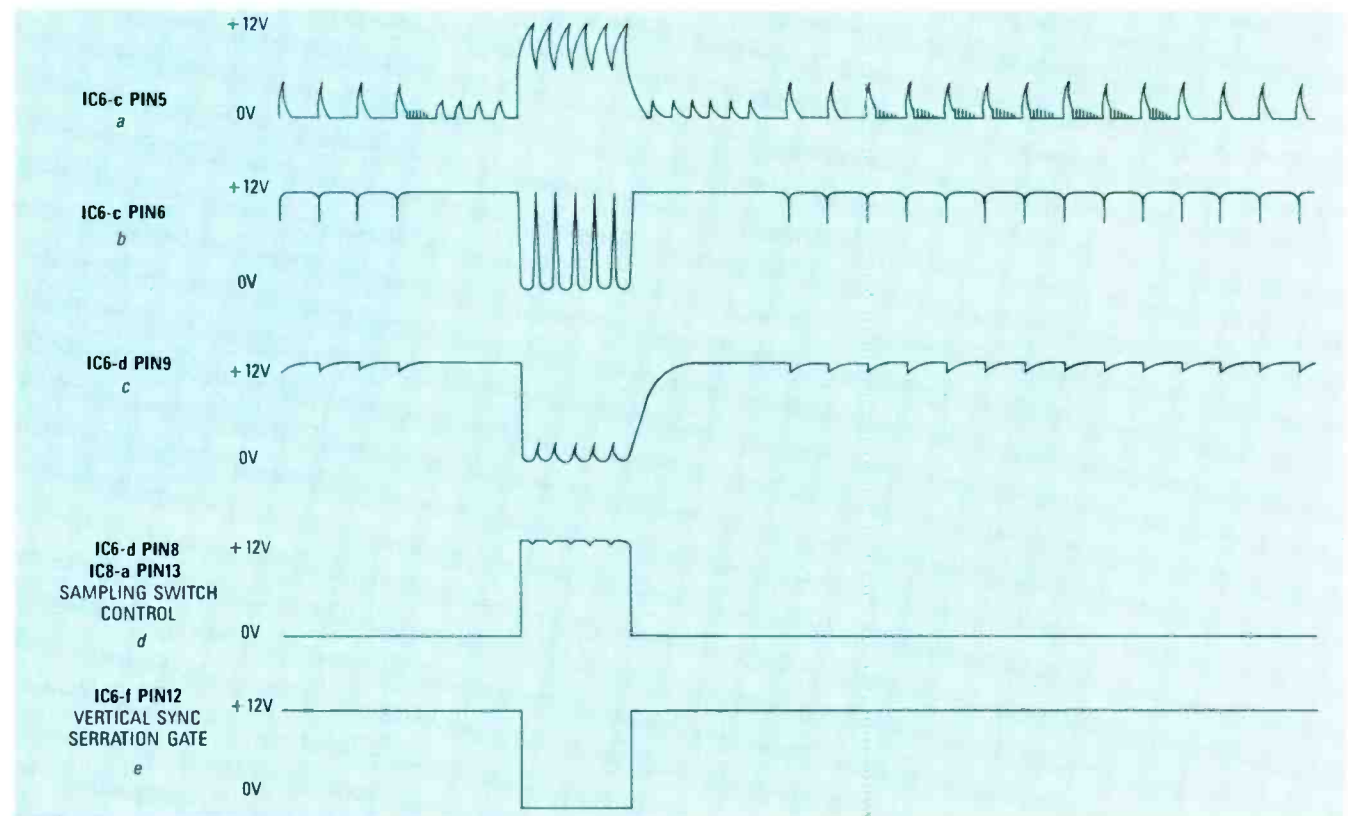


FIG. 5—VERTICAL SYNC AND BLANKING level sampling pulses are derived from the *Macrovision*-induced noise bursts.



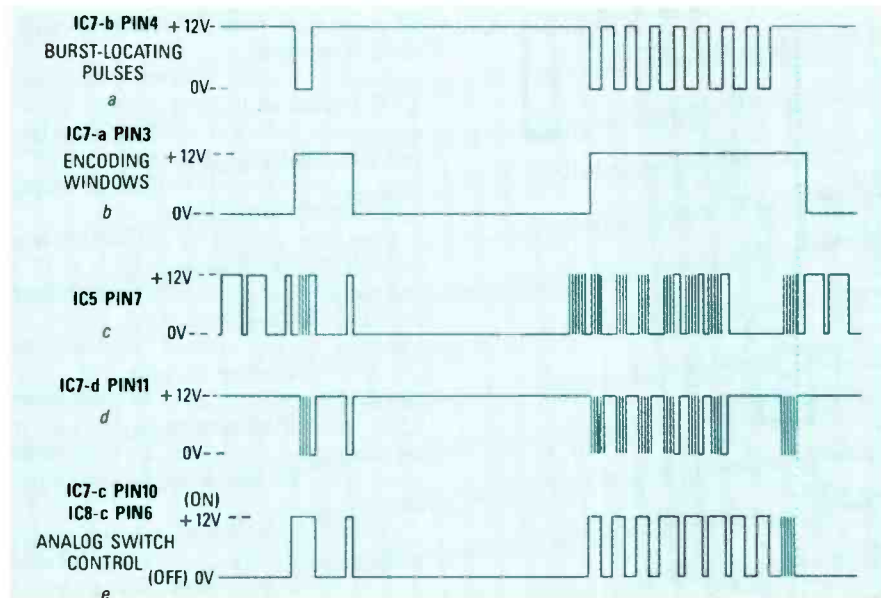


FIG. 6—WINDOWS DERIVED FROM the burst-location pulses provide the switch control signals that eliminate the Macrovision interference from the output signal.

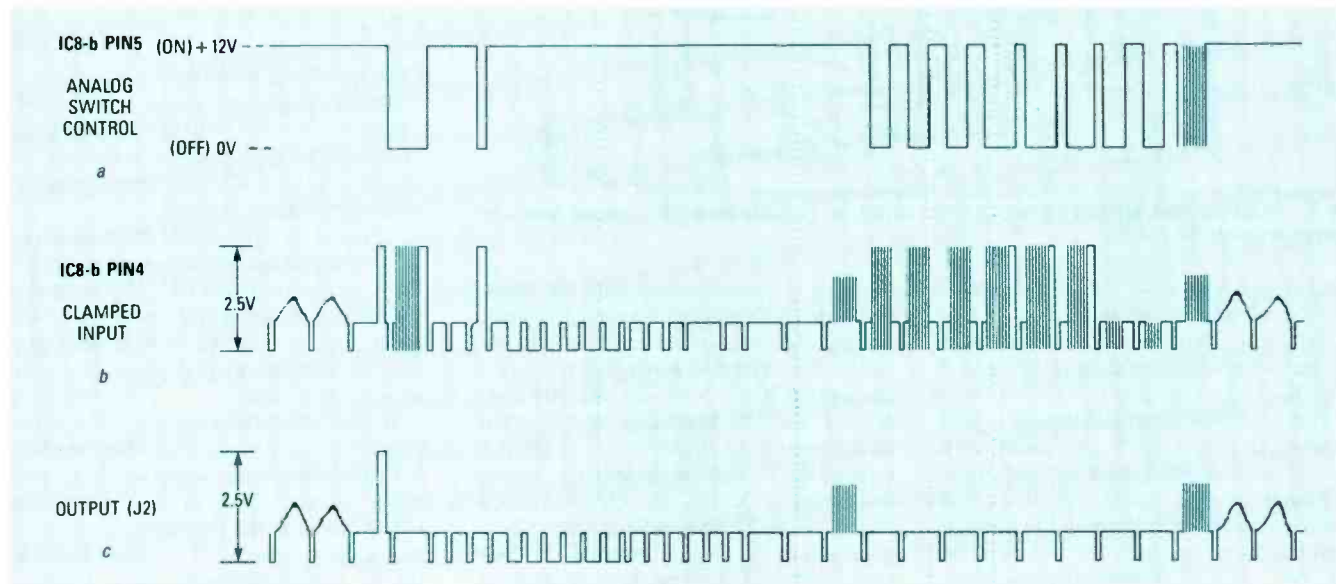


FIG. 7—THE NTSC SIGNAL IS CREATED by selectively switching the encoded input and the sampled vertical-blanking level into the output.

to a logic-high value are those corresponding to the vertical serration pulses.

Therefore, as shown in Fig. 5-a, at IC6-c pin 5 we have a signal that has +5-volt pulses corresponding to the horizontal sync pulses, and +12-volt pulses concurrent with the serration pulses during vertical-sync time.

Inverter IC6-c discriminates farther, since input pulses lower than a logic high (approximately +7V for a +12V supply) will not trigger output pulses. Therefore, as shown in Fig. 5-b, at inverter IC6-c pin 6 we have a normally high signal with low-going pulses occurring only during the vertical sync period. When that signal goes low, diode D4 becomes forward-biased and inverter IC6-d pin 9 is immediately pulled low as well. When IC6-c pin 6 goes high, D4 is reverse-biased, so

that pin 9 charges to a logic-high level at a rate determined by R22 and C8. (See Fig. 5-c.) Again, narrow pulses are ignored and, as shown in Fig. 5-d, the inverter's output (IC6-d pin 8) is normally low with logic-high sync pulses.

The inverter's output signal turns on sampling-switch IC8-a during the vertical-serration time, and C12 charges to the vertical blanking level. The high input impedance of op-amp IC9, and IC8-a in its off state, prevent the charged voltage on C12 from leaking off between samples. Unity-gain amplifier IC9 feeds C12's DC-voltage level to analog switch IC8-c, where it will be switched into the output waveform in place of the Macrovision noise.

As shown in Fig. 5-e, the vertical-sync signal at IC6-d pin 8 is inverted by IC6-f,

and is then fed to NAND gate IC7-b to gate the burst-locating signal from IC4 pin 12 (Fig. 4-c). The output signal at IC7-b pin 4 (Fig. 6-a), is normally high, with logic-low pulses that last for the duration of the corresponding Macrovision noise burst.

Notice, from Fig. 1-a, that some Macrovision bursts are followed by a solid pulse that doesn't have a negative transition. Since the Macrovision noise-locating pulses shown in Fig. 6-a were created by detecting high-frequency bursts below the blanking level, they do not locate the solid pulses without affecting any non-Macrovision pulses we must: 1) detect positive transitions above the vertical blanking level that occur during the Macrovision-encoded areas of vertical blanking, and 2) combine the new signal that locates the Macrovision solid pulses with the signal that locates the Macrovision noise bursts at IC7-b pin 4.

Macrovision-encoded areas of the sig-

nal are defined by feeding the signal at IC7-b pin 4 (Fig. 6-a) to a low-pass filter consisting of D3, R16, C18, and IC7-a. The resulting waveform at IC7-a pin 3 contains wide pulses, or windows, that define the time periods in which the Macrovision encoding is present. That signal is shown in Fig. 6-b.

The DC output voltage from the sample-and-hold circuit is fed to the inverting input of comparator IC5, while the clamped video input signal is fed to IC5's non-inverting input. A train of high-going pulses appears at IC5 pin 7 that corresponds to all transitions above the blanking level; including video, vertical-blanking interval data and Macrovision pulses. See Fig. 6-c.

The signal from IC5 pin 7 (Fig. 6-c) is gated by the window pulses from IC7-a

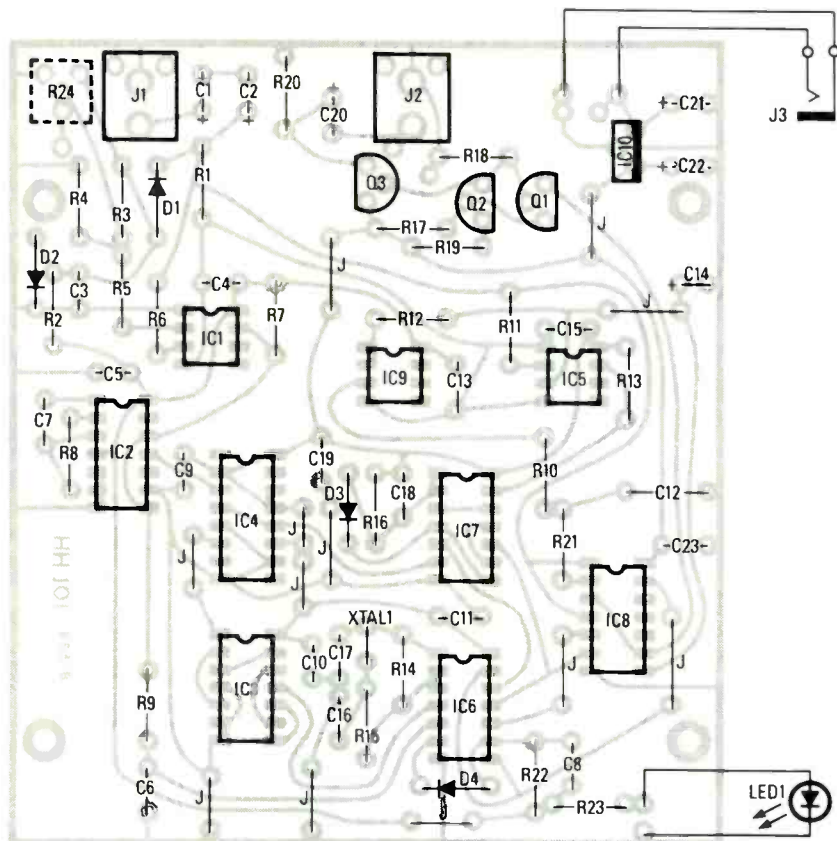


FIG. 8—RESISTOR R24, SHOWN BY THE DOTTED LINES, isn't usually used. If it is needed, you must remove resistors R3 and R4.

pin 3 (Fig. 6-b) at NAND gate IC7-d, yielding the waveform shown in Fig. 6-d at IC7-d pin 11. That signal is combined with the burst-locating signal from IC7 pin 4 (Fig. 6-a) by NAND gate IC7-c.

The final *Macrovision*-locating signal appears at IC8-c pin 6 and looks very similar to an inverted version of the original burst-locating signal (Fig. 6-a), but the pulses have been stretched to include both the bursts and the solid pulses. (See Fig. 6-e.) Notice that no locating pulse exists to remove the single solid pulse occurring at the start of the vertical blanking shown in the sample input waveform (Fig. 1-a). That is because there is no preceding negative noise burst that can be used to locate the solid pulse. As a result, that pulse will remain in the output waveform (Fig. 7-c), but it doesn't cause a problem because it is narrow and is not pumped.

The signal shown in Fig. 6-e directly feeds the control input, IC8-c pin 6, and an inverted form of the signal (Fig. 7-a) feeds analog switch IC8-b via inverter IC6-e.

The removal of the *Macrovision* encoding signal works as follows: During video time, horizontal-sync time, vertical-serration time, and all non-*Macrovision*-encoded vertical-line times, the control input of analog switch IC8-c is low—the switch is open. At the same time, the control input of analog switch IC8-b is

high—it is closed, connecting the clamped-video video (Fig. 7-b) to Q1's gate. During *Macrovision* noise times, the situation is reversed. Switch IC8-b is open and switch IC8-c is closed, thereby connecting the DC blanking voltage from sample-and-hold amplifier IC9 to Q1. An impedance-matching amplifier stage, consisting of Q1, Q2, and Q3, provides a match for the 75-ohm video output. Thus, as shown in Fig. 7-c, a "normal" NTSC-compatible video signal is reconstructed at the output, eliminating only the *Macrovision* noise.

### Construction

The circuit is assembled on a printed-circuit board. The foil pattern for that board is provided in PC Service. The parts-placement diagram for that PC board is shown in Fig. 8.

Begin stuffing the printed-circuit board by first installing all resistors, diodes, and capacitors. Make sure that all of the electrolytic capacitors and the diodes are installed with the proper polarity. Save the clipped component leads for use as jumpers.

Capacitor C12 must be a "polypropylene" type because the extremely low-leakage characteristic of the material prevents the vertical-blanking hold voltage from sagging between samples. As correct R-C time constants are critical to the proper operation of the circuit, use of

the component values shown in the schematic is essential.

The PC board's spacing for crystal XTAL1 is for an HC-18 package. Values specified in the Parts List for resistors R14 and R15, and capacitors C16 and C17, must be used in order to insure proper operation of the oscillator.

Mount the transistors and voltage regulator IC10 next. Transistor Q1 is an FET and should be handled with proper regard for static charges. A heatsink should be mounted on the voltage regulator, especially if the circuit is housed in a case that has limited ventilation. Potentiometer R24, which is indicated by dashed lines in the schematic, is not normally used, so its holes in the PC board will remain empty. (We'll explain R24 later.)

Finally, mount the IC's, using proper precautions for static electricity because most of them are CMOS. Sockets aren't necessary, but using them would make any troubleshooting or repair easier. The project will fit nicely into a PAC-TEC CM5-125 case.

### Checkout and hookup

Apply power and check that the AC adapter's output voltage is between 14–24-volts DC when it is powering the circuit, and that IC10's output voltage is +12-volts DC,  $\pm 0.6$  volt.

Connect an input signal and monitor or a TV to the Macro-scrubber. Connect the VCR's video output to J1. If you have a video monitor or a TV having a video input, connect the Macro-scrubber's output, J2, directly to that piece of equipment's video input.

If your equipment lacks a video input, you'll need an RF modulator for the channel you normally use when watching your VCR (channel 2, 3, or 4). Connect the video output to the modulator's video input. Connect the VCR's audio output to the RF modulator's audio input. Connect the modulator's RF output to the TV's antenna-input jack or terminals.


Play a video tape that you have already identified as containing *Macrovision* pulses. The picture you see should now be free of interference.

If the *Macrovision*-related viewing problems still exist, or if part of the picture is blanked out, the input-signal level from your VCR may be excessively high or low. In that case, a pattern of holes has been provided in the PC pattern so that fixed resistors R3 and R4 can be replaced with a 20,000-ohm potentiometer. The potentiometer is shown in the schematic by dashed lines, and is identified in the schematic and on the PC placement diagram as R24. (Remember, if you install R24 you must remove R3 and R4.)

To adjust R24, play a *Macrovision* tape, and while observing the TV picture, adjust R24 until the picture appears to be normal—interference-free. **R-E**

## In-Circuit Digital IC Tester

BILL GREEN

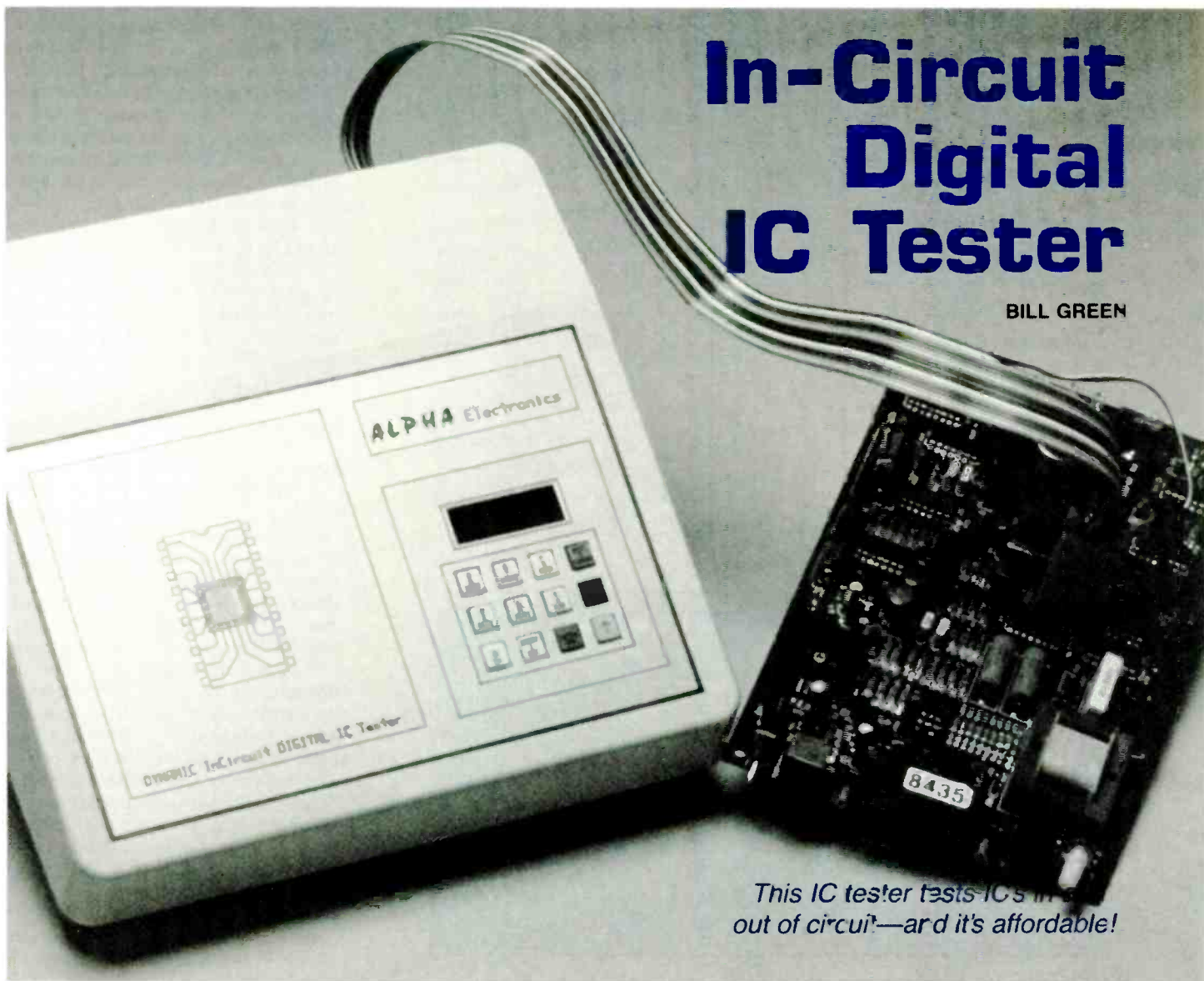

*This IC tester tests ICs in-circuit—and it's affordable!*

**Part 2** LAST MONTH WE BUILT the tester and discussed basic test methodology. Now we'll go on and provide specific examples showing how to set up your own test routines on paper and by computer, and how to send those files to and from your desktop computer.

Before we get started, let's correct a few errors from last month. The schematic of the driver board incorrectly identified P2 and P4. Also, the ordering information should have noted that IC16 and IC17 are not included in the partial kit.

### 7404 test data

Here is how to generate test data. This procedure applies whether data is entered via external computer using the data-entry routine discussed later, or is entered via the tester's keyboard.

Our first example illustrates the process for a 7404 hex inverter. First, obtain the pin numbers for inputs, outputs,  $V_{CC}$ , and

ground, and the functional description (or truth table) from the device's data sheet.

To ease the process of generating the test data, make a copy of the template shown in Fig. 7; then fill in the blanks for the part number, number of pins, and group number. You must make a template for each test group if you need more than one. You may also sketch the part's logic diagram in the box on the template.

Next fill in the data blanks, leaving room to write eight binary digits at each pin that must be tested. If we put a 1 into an inverter, we should get a 0 out of it. So put a 1 in the blank for pin 1, and a 0 by pin 2. Repeat the procedure with the remaining five inverters. Then put an X at pins 7 and 14 to indicate that they will be ignored. Now we have all data for the first test cycle.

There is a total of eight test cycles, so now place a 0 at each input and a 1 at each output. (The X's should remain by pins 7 and 14.) That accounts for two of the eight

bits in this test group's byte, so duplicate the bit pairs four times. Then convert the eight-bit data, four bits at a time, to two hexadecimal digits using the binary/hexadecimal chart at the bottom of the template. The completed test form is shown in Fig. 8.

The test information, along with the part number and the number of pins, is then stored in the tester's memory using the procedure outlined last time. There is no need for more than one test group to test a 7404 completely.

### In-circuit example

The data for an in-circuit IC depends on how the IC is connected. For example, input pins may be tied to  $V_{CC}$  or to ground, so we tell the tester to ignore those pins. Or, if the IC's input is connected to one of its outputs, ignore the input, because its data will be supplied by the output it's connected to. A sample chart is shown in Fig. 9.

## TEST ROUTINE TEMPLATE

PART NUMBER (8 Alphanumeric Digits Maximum): \_\_\_\_\_  
 NUMBER OF PINS (2 Digits Maximum, Even Numbers 4 to 24): \_\_\_\_\_  
 GROUP NUMBER (1 to 5): \_\_\_\_\_  
 REMARKS: \_\_\_\_\_

Binary Data	Hex	Funct	Pin#	Pin#	Binary Data	Hex	Funct
_____	=	_____	_____	_____	_____	=	_____
_____	=	_____	_____	_____	_____	=	_____
_____	=	_____	_____	_____	_____	=	_____
_____	=	_____	_____	_____	_____	=	_____
_____	=	_____	_____	_____	_____	=	_____
_____	=	_____	_____	_____	_____	=	_____
_____	=	_____	_____	_____	_____	=	_____
_____	=	_____	_____	_____	_____	=	_____
_____	=	_____	_____	_____	_____	=	_____
_____	=	_____	_____	_____	_____	=	_____
_____	=	_____	_____	_____	_____	=	_____
_____	=	_____	_____	_____	_____	=	_____
_____	=	_____	_____	_____	_____	=	_____
_____	=	_____	_____	_____	_____	=	_____
_____	=	_____	_____	_____	_____	=	_____
_____	=	_____	_____	_____	_____	=	_____
_____	=	_____	_____	_____	_____	=	_____
_____	=	_____	_____	_____	_____	=	_____

### BINARY TO HEXADECIMAL CONVERSION TABLE

BINARY	HEX	BINARY	HEX
0000	0	1000	8
0001	1	1001	9
0010	2	1010	A
0011	3	1011	B
0100	4	1100	C
0101	5	1101	D
0110	6	1110	E
0111	7	1111	F

FIG. 7—COPY THIS TEMPLATE to simplify generating your own test routines.

## Multiple test groups

IC's with pins that can function as both inputs and outputs can be tested as follows. We'll use a 74LS245 octal bus transceiver for illustration. That IC is commonly used to buffer data into and out of a microprocessor; direction of data flow is controlled by a single DIR input (pin 1).

The data for testing the IC in send mode is shown in Fig 10; the data for testing it in receive mode is shown in Fig. 11. Notice that the data in both cases is identical except for the setting of the direction line.

The enable line of a registered (latched) IC must be toggled to ensure that the IC responds when it is enabled, and does not respond when it is not enabled. Fig. 12 shows the test pattern for a 74LS373 octal data latch. The outputs should follow the inputs when the enable line (pin 11) is high, and shouldn't change otherwise.

## Clocked logic

A clocked IC that has no means of setting or clearing its outputs will have an indeterminate state before it is clocked. Therefore, all outputs must be listed as indeterminate (D). The first state of a pin defined as indeterminate will be cleared to zero. (Only outputs can be indeterminate.) The remaining 7 states of the group will be processed normally. If more than one test group is needed, the first state of each additional group will not be indeterminate and should be defined as Output. Note in the test data that the clock line goes high in the odd-number cycles (1, 3, 5, and 7). The outputs will only change on those cycles, because the 74LS374 changes state during the leading clock edge. Test data is shown in Fig. 13.

## Multiple-output-state devices

An IC with many inputs or outputs may require more than one test group. (Remember that there is a maximum of five test groups per part number). For exam-

PART NUMBER (8 Alphanumeric Digits Maximum) 7404  
 NUMBER OF PINS (2 Digits Maximum, Even Numbers 4 to 24) 14  
 GROUP NUMBER (1 to 5): 1  
 REMARKS HEX INVERTER

Binary Data	Hex	Funct	Pin#	Pin#	Binary Data	Hex	Funct
_____	_____	_____	_____	_____	_____	_____	_____
_____	_____	_____	_____	_____	_____	_____	_____
_____	_____	_____	_____	_____	_____	_____	_____
_____	_____	_____	_____	_____	_____	_____	_____
0101 0101	55	I	1	14	_____	_____	X
1010 1010	AA	O	2	13	0101 0101	55	I
0101 0101	55	I	3	12	1010 1010	AA	O
1010 1010	AA	O	4	11	0101 0101	55	I
0101 0101	55	I	5	10	1010 1010	AA	O
1010 1010	AA	O	6	9	0101 0101	55	I
_____	X	_____	7	8	1010 1010	AA	O

FIG. 8—TEST DATA FOR A 7404 hex inverter. All states are redundantly checked four times.

PART NUMBER (8 Alphanumeric Digits Maximum) 7404  
 NUMBER OF PINS (2 Digits Maximum, Even Numbers 4 to 24) 14  
 GROUP NUMBER (1 to 5): 1  
 REMARKS IN-CIRCUIT

Binary Data	Hex	Funct	Pin#	Pin#	Binary Data	Hex	Funct
_____	_____	_____	_____	_____	_____	_____	_____
_____	_____	_____	_____	_____	_____	_____	_____
_____	_____	_____	_____	_____	_____	_____	_____
_____	_____	_____	_____	_____	_____	_____	_____
0101 0101	55	I	1	14	_____	_____	X
1010 1010	AA	O	2	17	_____	_____	X
_____	X	_____	3	12	0000 0000	00	O
0101 0101	55	O	4	11	0101 0101	55	I
_____	X	_____	5	10	1010 1010	AA	O
1010 1010	AA	O	6	9	0101 0101	55	I
_____	X	_____	7	8	1010 1010	AA	O

FIG. 9—TEST DATA FOR AN IN-CIRCUIT 7404. Input pins 3, 5, and 13 are marked X, for "ignore." Those pins might be hard-wired to ground, V<sub>CC</sub>, or elsewhere in an actual circuit.

PART NUMBER (8 Alphanumeric Digits Maximum) 74LS245  
 NUMBER OF PINS (2 Digits Maximum, Even Numbers 4 to 24) 20  
 GROUP NUMBER (1 to 5) 1  
 REMARKS: SEND MODE

Binary Data	Hex	Funct	Pin#	Pin#	Binary Data	Hex	Funct
11111111	FF	I	1	5A	V <sub>CC</sub>		
0101 0101	55	I	2	1A	E	19	0000 0000
0101 0101	55	I	3	2A	1B	18	0101 0101
0101 0101	55	I	4	3A	2B	17	0101 0101
0101 0101	55	I	5	4A	3B	16	0101 0101
0101 0101	55	I	6	5A	4B	15	0101 0101
0101 0101	55	I	7	6A	5B	14	0101 0101
0101 0101	55	I	8	7A	6B	13	0101 0101
0101 0101	55	I	9	8A	7B	12	0101 0101
	X		10	GND	8B	11	0101 0101

FIG. 10—TEST SETUP FOR A 74LS245 octal bus transceiver in send mode.

PART NUMBER (8 Alphanumeric Digits Maximum) 74LS245  
 NUMBER OF PINS (2 Digits Maximum, Even Numbers 4 to 24) 20  
 GROUP NUMBER (1 to 5) 1  
 REMARKS: RECEIVE MODE

Binary Data	Hex	Funct	Pin#	Pin#	Binary Data	Hex	Funct
0000 0000	00	I	1	5A	V <sub>CC</sub>		
0101 0101	55	O	2	1A	E	19	0000 0000
1101 0101	55	O	3	2A	1B	18	0101 0101
0101 0101	55	O	4	3A	2B	17	0101 0101
0101 0101	55	O	5	4A	3B	16	0101 0101
0101 0101	55	O	6	5A	4B	15	0101 0101
0101 0101	55	O	7	6A	5B	14	0101 0101
0101 0101	55	O	8	7A	6B	13	0101 0101
0101 0101	55	O	9	8A	7B	12	0101 0101
	X		10	GND	8B	11	0101 0101

FIG. 11—TEST SETUP FOR A 74LS245 octal bus transceiver in receive mode.

ple, the 74154 4-to-16 line decoder has four address inputs (pins 20–23), two active-low gate inputs (pins 18 and 19), and 16 outputs, one of which goes low when both gate inputs are low, depending on the state of the four address inputs. Figures 14, 15, and 16 show the data required to test the IC completely.

### Advanced commands

After generating test data you'll probably want to store it in your desktop computer. The tester provides storage for as many as 105 test routines, which you may upload to and download from the tester's internal memory.

After entering test data, if you wish to store it, press the Store key, and the data will be stored in memory for future use under the part number that is entered with the data.

To load a test routine from the tester's local memory, press Load and then enter

the part number. If a corresponding routine is in memory, *CLEAR OR ENTER?* will appear on the display. Press Clr to erase the entry from memory, or press Enter to leave the data in the test buffer for testing or transfer to the external computer. To upload the data, press Send. To download it, press Recv. If you wish to retain a received file, press Store. Use the BASIC programs shown in Listings 1 and 2 to send and receive programs.

### Remote data generation

The BASIC program shown in listing 3 can be used to create test patterns somewhat more conveniently than on the tester itself. It is important to note that when using the program to generate test files, only hex characters (0–9, A–F) may be used in the part number (TF\$) if the file is to be stored in the Tester's memory. The reason for this is that the Tester's keyboard has no other characters to access the test

routine in its memory. Therefore you would not be able to load or delete the test routine. For example, a part entered as 74LS138 would be inaccessible because there is no L or S on the Tester's keyboard.

### Usage hints

First a few words of caution. Never connect the test clip to an IC that has power on it unless the tester is on and *COMMAND?* is scrolling in the display. Conversely, never shut the tester off when the clip is connected to a powered IC. And always make sure when testing in-circuit IC's that the tester and the DUT (*Device Under Test*) share a common ground. Connect the black test hook clip to a ground on the board near the IC's to be tested.

The test drivers (IC7–IC15) are rated at 7 volts maximum, so be careful what you connect the test clip to. A powered RS-232 driver might have ±12 volts, or even more, and voltages at those levels

PART NUMBER (8 Alphanumeric Digits Maximum) 74LS373  
 NUMBER OF PINS (2 Digits Maximum, Even Numbers 4 to 24) 20  
 GROUP NUMBER (1 to 5) 1  
 REMARKS: OCTAL TRANSPARENT LATCH

Binary Data	Hex	Funct	Pin#	Pin#	Binary Data	Hex	Funct
0000 0000	00	I	1	OE	V <sub>CC</sub>		
1001 0001	91	O	2	1G	8Q	19	1001 0001
1001 1001	99	I	3	1D	8P	18	1001 1001
1001 1001	99	I	4	2D	7D	17	1001 1001
1001 0001	91	O	5	2Q	7Q	16	1001 0001
1001 0001	91	O	6	3Q	6Q	15	1001 0001
1001 1001	99	I	7	3D	6D	14	1001 1001
1001 1001	99	I	8	4D	5D	13	1001 1001
1001 0001	91	O	9	4Q	5Q	12	1001 0001
	X		10	GND	E	11	1011 0011

FIG. 12—TEST SETUP FOR A 74LS373 octal transparent data latch. Whenever the enable line (pin 11) is high, each output follows the corresponding input.

PART NUMBER (8 Alphanumeric Digits Maximum) 74LS374  
 NUMBER OF PINS (2 Digits Maximum, Even Numbers 4 to 24) 20  
 GROUP NUMBER (1 to 5) 1  
 REMARKS: OCTAL D EDGE-TRIGGERED FF

Binary Data	Hex	Funct	Pin#	Pin#	Binary Data	Hex	Funct
0000 0000	00	I	1	OE	V <sub>CC</sub>		
1001 1000	9B	D	2	1Q	8Q	19	1001 1000
1100 1100	CC	I	3	1D	8D	18	1100 1100
1100 1100	CC	I	4	2D	7D	17	1100 1100
1001 1000	9B	D	5	2Q	7Q	16	1001 1000
1001 1000	9B	D	6	3Q	6Q	15	1001 1000
1100 1100	CC	I	7	3D	6D	14	1100 1100
1100 1100	CC	I	8	4D	5D	13	1100 1100
1001 1000	9B	D	9	4Q	5Q	12	1001 1000
	X		10	GND	CLK	11	1010 1010

FIG. 13—TEST SETUP FOR A 74LS374 octal D flip-flop. Data on each input is clocked into the corresponding output on the leading edge of each clock pulse. Clock pulses are applied to pin 11.

PART NUMBER (8 Alphanumeric Digits Maximum): 74154  
 NUMBER OF PINS (2 Digits Maximum, Even Numbers 4 to 24): 24  
 GROUP NUMBER (1 to 5): 1  
 REMARKS: 4-70-16 LINE DECODER

Binary Data	Hex	Funct	Pin#	Pin#	Binary Data	Hex	Funct
0000	0	0	Q0	V <sub>CC</sub>	24		X
0001	1	0	Q1	A	23	0101	5
0010	2	0	Q2	B	22	0110	6
0011	3	0	Q3	C	21	1000	8
0100	4	0	Q4	D	20	0000	0
0101	5	0	Q5	G2	19	0000	0
0110	6	0	Q6	G1	18	0000	0
0111	7	0	Q7	Q15	17	1111	F
1000	8	0	Q8	Q14	16	1111	F
1001	9	0	Q9	Q13	15	1111	F
1010	A	0	Q10	Q12	14	1111	F
1011	B	0	Q11	Q11	13	1111	F
1100	C	X					

FIG. 14—A 74154 demultiplexer has six inputs and 16 outputs, so it requires three test groups to test all combinations. Group 1 is shown here.

PART NUMBER (8 Alphanumeric Digits Maximum): 74154  
 NUMBER OF PINS (2 Digits Maximum, Even Numbers 4 to 24): 24  
 GROUP NUMBER (1 to 5): 2  
 REMARKS: 4-70-16 LINE DECODER

Binary Data	Hex	Funct	Pin#	Pin#	Binary Data	Hex	Funct
0000	0	0	Q0	V <sub>CC</sub>	24		X
0001	1	0	Q1	A	23	0101	5
0010	2	0	Q2	B	22	0110	6
0011	3	0	Q3	C	21	1000	8
0100	4	0	Q4	D	20	1111	F
0101	5	0	Q5	G2	19	0000	0
0110	6	0	Q6	G1	18	0000	0
0111	7	0	Q7	Q15	17	1111	F
1000	8	0	Q8	Q14	16	1111	F
1001	9	0	Q9	Q13	15	1111	F
1010	A	0	Q10	Q12	14	0111	7
1011	B	0	Q11	Q11	13	1011	B
1100	C	X					

FIG. 15—GROUP TWO OF THE 74154 TEST set is shown here.

PART NUMBER (8 Alphanumeric Digits Maximum): 74154  
 NUMBER OF PINS (2 Digits Maximum, Even Numbers 4 to 24): 24  
 GROUP NUMBER (1 to 5): 3  
 REMARKS: 4-70-16 LINE DECODER

Binary Data	Hex	Funct	Pin#	Pin#	Binary Data	Hex	Funct
0000	0	0	Q0	V <sub>CC</sub>	24		X
0001	1	0	Q1	A	23	1111	F
0010	2	0	Q2	B	22	1111	F
0011	3	0	Q3	C	21	1111	F
0100	4	0	Q4	D	20	1111	F
0101	5	0	Q5	G2	19	1111	F
0110	6	0	Q6	G1	18	1111	F
0111	7	0	Q7	Q15	17	1111	F
1000	8	0	Q8	Q14	16	1111	F
1001	9	0	Q9	Q13	15	1111	F
1010	A	0	Q10	Q12	14	1111	F
1011	B	0	Q11	Q11	13	1111	F
1100	C	X					

FIG. 16—GROUP THREE OF THE 74154 TEST set is shown here.

could damage the drivers easily. The display will probably dim if you inadvertently connect the test clip to an IC incorrectly, or if you have entered test data incorrectly. If the display does become

## PARTS LIST

All resistors are 1/4-watt, 5% unless otherwise noted.

R1—22,000 ohms

R2—330 ohms

R3—R6—1000 ohms

Capacitors

C1, C8—1000 μF, 16 volts, electrolytic

C2, C4—C7, C9—C17—0.1 μF, 10 volts, ceramic disc

C3—10 μF, 16 volts, electrolytic

Semiconductors

IC1—Z80 microprocessor

IC2—DS1230-104 32K nonvolatile RAM

IC3—MAX233 RS-232 interface

IC4—75499 custom decoder

IC5—75498 custom decoder

IC6—75500 custom decoder

IC7, IC10, IC13—NE591 open-emitter

octal driver

IC8, IC11, IC14—NE590 open-collector octal driver

IC9, IC12, IC15—74LS373 octal latch

IC16—7805 5-volt regulator

IC17—2-Mhz crystal oscillator

D1—1N4001 rectifier

DISP1—DL1414 16-segment decoder/driver/display

Other components

F1—1-amp pigtail fuse

J1—9-pin D connector

P1, P2—right-angle double-row 20-pin male header strips

P3—right-angle double-row 26-pin male header strips

S1—miniature SPDT toggle switch

S2—momentary SPST pushbutton

S3—S14—momentary SPST keyboard switches

T1—Transformer, 9.5–12-volts, 1-amp, wall-mount

Miscellaneous: One 10-pin, two 20-pin and one 26-pin double-

row female IDC header connectors. Two 12-pin single-row female IDC header connectors. Flat ribbon cable and test clips.


Note: The following are available from: ALPHA Electronics

Corporation, P.O. Box 1005, Merritt Island, Florida 32952-1005, (305) 453-3534: Kit of parts for \$299.00 + \$6.00

P&H. Includes all parts, punched and screened panel, case, and labeled keys. Test cable and clips not included.

Completely assembled tester for \$399.00 + \$6.00 P&H. Includes test cable with 16-, 20-, and 24-pin IC test clips.

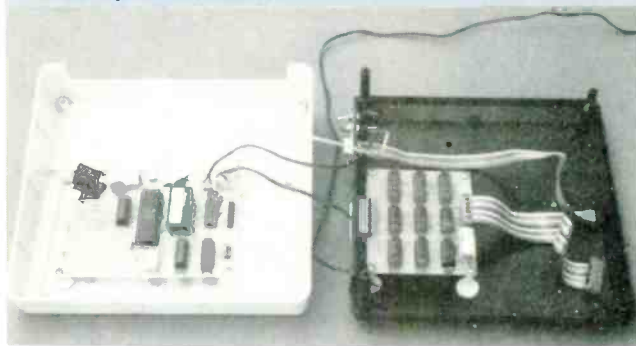Partial kit, including all IC's (except IC16 and IC17), display, and PC boards for \$199.00 + \$5.00 P&H. Three custom IC's (75498, 75499 and 75500) for \$60.00 + \$4.00 P&H. Florida customers please add 5% State sales tax. Canadian customers please add \$3.00 additional postage to all orders. All foreign orders add appropriate postage for Air shipping and insurance.



INSIDE THE IC TESTER. Last time we showed you how to build the project; this month we show you how to use it.

dim, disconnect the test clip and remove power immediately.

In addition to testing IC's both in and out of circuit, the tester can also be used as a simple logic analyzer to test as many as twenty four points in a digital circuit. Simply replace the DIP clip with individual test-hook clips. Some lines would be used as outputs to stimulate the circuit, and others would be used as inputs to read the results.

R-E

An oscilloscope is an indispensable troubleshooting tool. Adding a digital readout makes it ideal.

## How to Analyze Waveforms

GREGORY D. CAREY, CET

AN OSCILLOSCOPE IS LIKE AN ELECTRONIC stethoscope—it allows you to confirm a circuit's "health" by examining the signals flowing through it. Whether you are designing a circuit, building a project from a magazine, or repairing circuits for a living, the ability to analyze waveforms quickly, accurately, and without mistakes can let you make the most of your technical skills. Unfortunately, many technicians only use their scopes when absolutely necessary. Because of that, they often are unfamiliar with the unit's operation, making waveform interpretation seem difficult. Combining a digital readout with the scope's graphic display, eliminates most of the problems of waveform interpretation.

### What is a waveform?

Before we go on, let's be certain that you understand what the waveform on an oscilloscope's CRT screen represents. The CRT graphically displays the relationship between the voltage and time at the test point you're measuring. The vertical movement (deflection) indicates the signal's voltage, with more deflection representing larger voltages. Simultaneously, the beam is moving horizontally at a constant rate, so that each horizontal division on the CRT represents a constant time interval.

Analyzing the signal helps identify

which components are responsible for circuit problems. Let's look at how each part of the waveform helps find different component problems.

### The seven waveform parameters

The seven parameters shown in Fig. 1 fully define any signal. Four of those parameters apply to any signal, and the other three apply to complex signals. We will explain how to interpret each parameter and which components are most likely to affect each one.

(1) **Waveshape:** The signal's waveshape confirms the general operation of a circuit. Waveform distortion is often caused by a problem in a reactive compo-

nent, such as a coil or a capacitor. Waveform clipping ("flat-topping") may be caused by saturation of a stage or a power supply with low output. After discovering a waveshape problem, other parameters can be used to provide additional clues about the circuit's operation.

(2) **DC level:** The DC bias at a test point is such an important troubleshooting parameter that many people use their voltmeters as their main piece of test equipment. DC problems may be responsible for problems with any of the other parameters, including distorted waveshape, or incorrect amplitude or frequency. DC problems may be caused by power-supply problems or an open or shorted

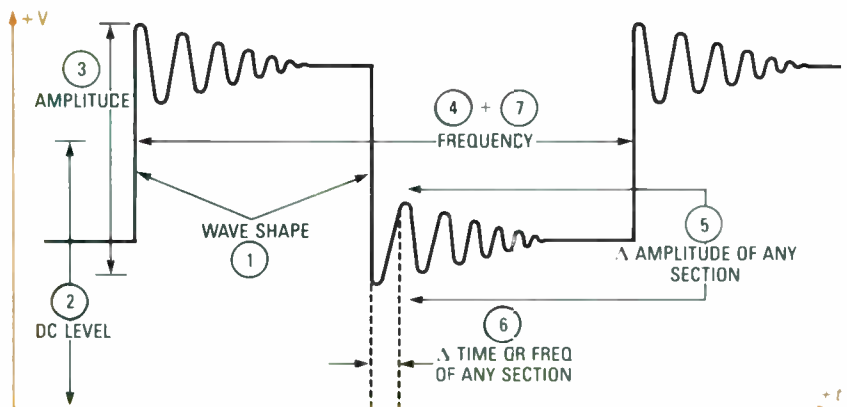


FIG. 1—TO FULLY ANALYZE A WAVEFORM, these seven parameters must be measured or observed.

component somewhere in the circuit. A DC-coupled scope, especially one with a digital readout, allows you to measure DC bias directly, while simultaneously observing the signal's waveshape. The DC and waveform readings also work together when a power supply has excessive ripple, even though its DC output is correct.

**(3) Amplitude:** The next test is to confirm that the signal has the correct peak-to-peak voltage. Low signal amplitude may be caused by low stage gain or by excessive loading. Poor gain often results from a defective transistor or IC, low power-supply voltage, or a defective emitter-bypass capacitor. Excessive loading may be the result of a component that has shorted or has changed value.

**(4) Frequency:** Some circuits, such as oscillators, generate signals for use by later stages. Other stages may be referenced to an external source, such as in VCR servo circuits, phase-locked loops, digital counter stages, or television sweep circuits. Testing the frequency of those circuits confirms whether they are working correctly.

#### Delta measurements

The previous four tests will fully analyze a signal if you are testing a simple waveshape, such as a sine wave or square wave. If, on the other hand, you are testing a complex signal, you may need to know the details of the secondary parts of the signal to complete the analysis. Those added tests are called *delta* measurements. There are three types of delta measurements as follows:

**(5) Delta amplitude:** The peak-to-peak voltage test covered earlier measured the total amplitude from the signal's lowest to its highest points. But many signals have additional signals buried within them. For example, an incorrect color-burst level on a composite video waveform (see Fig. 2) may cause color

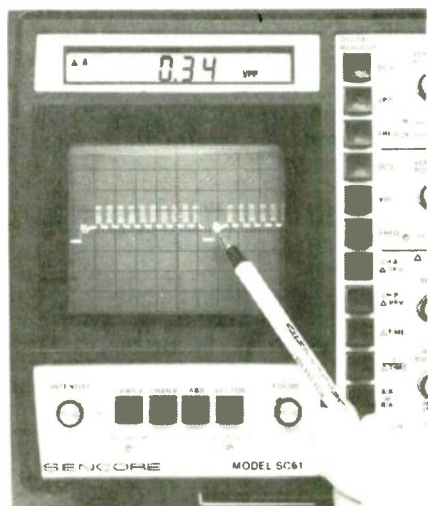


FIG. 2—PERFORMING A DELTA PEAK-TO-PEAK measurement confirms that the color burst of a composite video signal has the correct amplitude.

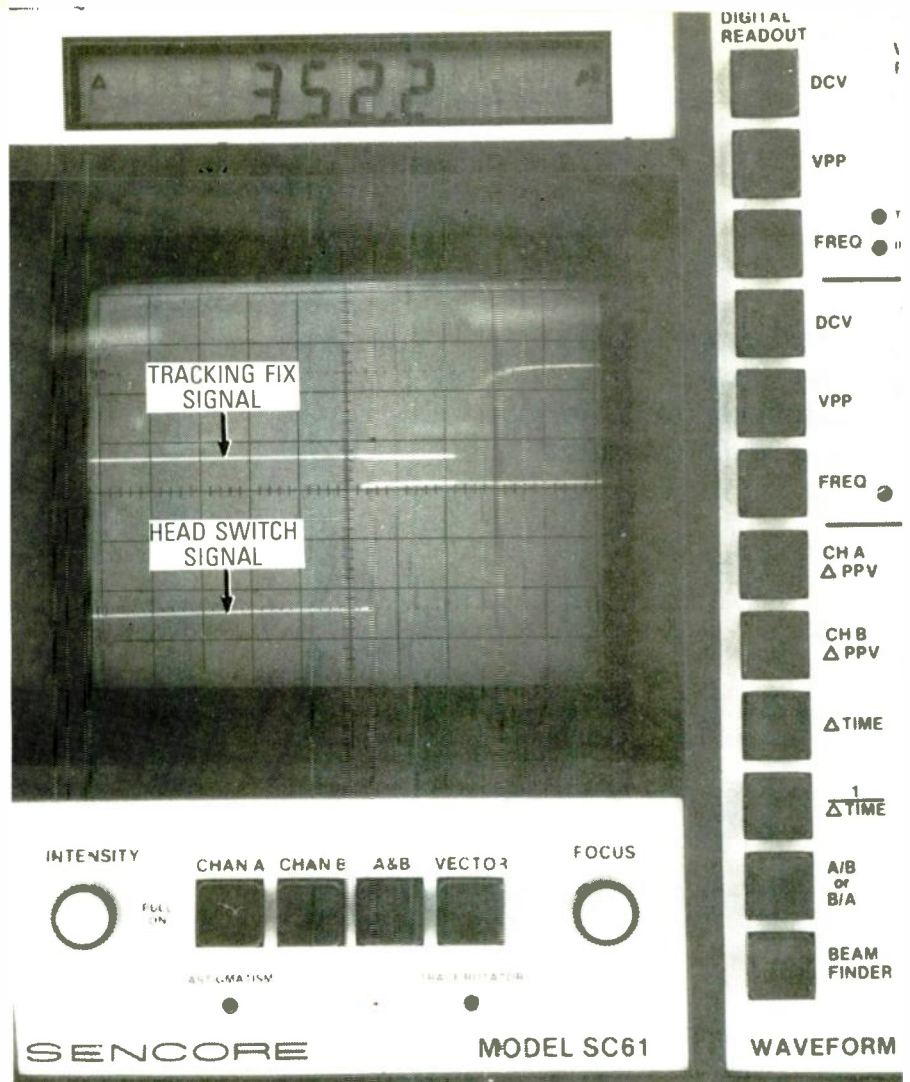


FIG. 3—MAKING A DELTA-TIME MEASUREMENT shows that the difference between a tracking fix and a head-switch signal has to be 352  $\mu$ s; factory specifications call for a 400  $\mu$ s delay.

problems. An incorrect sync-pulse level on the same composite signal may cause sync instability. Ripples or glitches, riding along the top of digital squarewaves may cause later circuits to operate incorrectly. Those conditions can be detected by using delta peak-to-peak voltage measurements, which allow the level of secondary signals to be measured independently of the main signal level.

**(6) Delta time:** Time measurements fall into two categories: those that are part of one signal, and those involving the time difference between two signals. An example of time within one signal would be the duty cycle of a switching power supply, where the "on-time" compared to the "off-time" determines the power delivered to the load. The time delay between two signals is important in many VCR servo adjustments. See Fig. 3. Either of those applications uses a point on the waveform as a reference for a delta-time measurement.

**(7) Reciprocal time measurements:** You can determine the approximate frequency of a signal by measuring the time for a single cycle and then inverting the time measurement mathematically. You can use that method to determine the time constant of circuits responsible for ring-

ing, or the frequency of an interfering signal to determine its source.

#### Digital measurements

You make all seven of those measurements every time you fully analyze a signal with an oscilloscope. Conventional scopes require you to make every parameter reading by measuring beam displacement on the CRT, and multiplying that by the settings of the vertical or horizontal circuit controls. Some scopes with microprocessor-controlled measuring circuits, such as the Sencore SC61 shown in the opening of this article, allow every parameter to be converted to a direct digital reading. The CRT is then only used to display the overall shape of the signal.

A digital readout offers three advantages over using the CRT for measurements: Speed, accuracy, and freedom from errors. Let's look at each of those advantages in a little more detail.

**Speed:** You may begin to appreciate the time that direct digital readings save when you look at the number of steps needed to make a single measurement on a conventional CRT. Those steps are outlined in Table 1. If you use an oscilloscope often, you perform those steps without even

*continued on page 82*



## Strain-Gage Transducers

CLINTON M. WOOD

*Strain gages can be used to measure virtually any force-related physical property. In this article we'll see how those versatile devices work.*

STRAIN-GAGE TRANSDUCERS, USED IN EVERYTHING from automobiles to zinc plants, have found their way into our homes, our supermarkets, our factories, and our hospitals. They're commonly used in nearly every branch of science and technology, including research, space flight, product development, robotics, automation, energy production, agriculture, and consumer products. They can be used to measure a wide range of force-related physical properties like weight, acceleration, pressure, volume, liquid level, flow rate, and velocity. Further, they are accurate, durable, inexpensive, linear, and inherently simple to use.

Since strain-gage transducers are linear, it's easy to determine the value of a force-related input. All that's required is to divide the output voltage by the transducer sensitivity as shown in Fig. 1. That's because the input and output are related by a simple linear equation. In this article we'll see where that equation comes from, and, in the process, learn something about the underlying principles that are common to all strain-gage transducers. Toward that end, we have divided the strain-gage transducer into three components: 1) the spring element, 2) the strain gage, and 3) the bridge circuit. We'll take a look at each of those compo-

nents to see what they contribute to the operation of the transducer. Then we'll put them back together to see how the complete transducer works.

### The spring element

The principle of elasticity, that is the tendency of solids to deform or change dimensions when subjected to an external force, is central to the operation of the strain-gage transducer. It makes no difference whether the force is from a weight, a fluid pressure, or even mechanical inertia; the result is the same.

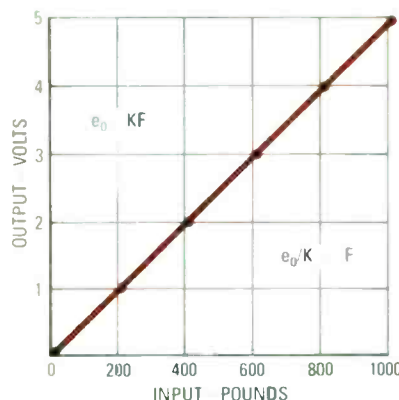


FIG. 1—IN A STRAIN-GAGE TRANSDUCER the relationship between the applied force and the output voltage is linear.

As an example, Fig. 2 shows a steel bar subjected to a force in the form of a weight. In Fig. 2-a the bar is unloaded and has a length of  $L$ . In Fig. 2-b, the bar is anchored at the top, and the weight is attached to the bottom. In that case, the resulting deformation will appear as an increase in length. In Fig. 2-c, the weight is placed on top of the bar. That will result in a decrease in length. Note that no matter how the bar is loaded, it will return to its original length when the weight is removed, provided that the applied force was not so large as to cause the bar to permanently stretch or break. The change in length resulting from an applied force is known as strain. For metallic solids like steel or aluminum, the maximum allowable strain before deformation is in the range of a few thousandths of an inch.

The property of elasticity is widely used in the manufacture of instruments because there is a linear relationship between strain and the applied force. This relationship can be expressed as

$$S = kF \quad (1)$$

where  $F$  is the applied force,  $S$  is the resulting strain, and  $k$  is the spring-element constant; the value of  $k$  depends on a number of things like the geometry and type of material, and the direction of the

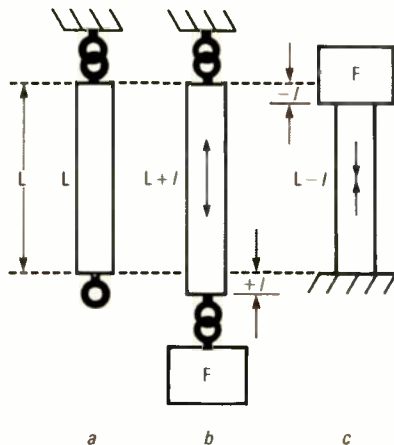


FIG. 2—IF A STEEL BAR (a) is loaded, its length will change. Depending on the placement of the load, the bar will either expand (b) or contract (c).

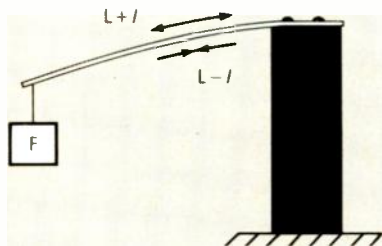


FIG. 3—WHEN FORCE IS APPLIED to the free end of the arm, the upper surface will expand and the bottom surface will contract.

applied force. That relationship, known as Hooke's Law, was originally applied to coil springs for use as a measure of weight. But we have since recognized that, within limits, it is essentially true for all solids.

The spring element is the foundation of the strain-gage transducer. It is an elastic solid (usually metallic) designed to linearly translate an applied force into an equivalent strain. Its size and shape depend on the magnitude and type of force that the transducer is to sense. A spring element could be as simple as the steel bar in Fig. 2, but a design of that type provides only one direction of strain in response to an applied force. If the applied force can produce two equal strains that are opposite in direction, the resulting transducer will be more accurate. That is often done by applying a force to the spring element in a way that will make it bend.

Figure 3 shows one way that can be done. A rectangular steel bar is anchored at one end in a cantilever configuration. The force is applied to the free end of the bar, perpendicular to the axis, rather than along the axis as in Fig. 2. As a result, the upper surface of the bar will stretch, and the bottom surface will compress. The surface strain will vary along the bar, from a maximum near the end that is anchored, to zero at the other end. But at any given position along the bar, the strain of the

upper and lower surfaces will be equal in magnitude and opposite in direction. Later we will see that those opposing strains can help stabilize the transducer against varying environmental conditions that may occur.

Some commercial transducers use spring elements that are similar to the cantilever configuration, but there are a great many other designs that are used as well—in fact, too many to discuss here realistically. Fortunately, a study of the design variations is unnecessary as long as you remember that a spring element is a structural component designed to provide a linear deformation in response to an applied force.

### The strain gage

The purpose of the strain gage is to convert the strain of the spring element into an equivalent change in resistance. A strain gage is just a metallic conductor that is bonded to the spring element, stretching and compressing in the same way as the spring element. We know from basic electricity that the resistance of a conductor depends on its length. And, we know that if we place it in tension its length will increase as the steel bar did in Fig. 2. Since resistance is proportional to length, that stretching will result in an increase in resistance. If we turn that around and put the conductor into compression, its resistance will decrease.

Figure 4 shows a typical commercial strain gage. It consists of a thin foil conductor bonded to a plastic backing material. The backing, which serves as a carrier for the metal foil and provides insulation from the spring element, must be flexible enough to follow the spring element, yet tough enough to transfer the strain to the metal foil. The foil conductor is usually made of an alloy having a low temperature coefficient, like constantan. To keep the strain gage reasonably short, the foil has been laid out in a criss-cross pattern over the surface of the backing material. At one end, the foil expands to form two solder tabs which are used to attach lead wires to the strain gage. Although the design shown in Fig. 4 is typical, a number of other designs are available, including multiple gages on a single backing and circular gages for use with diaphragm-type pressure transducers. A number of designs from one supplier, Transducers Inc. (14030 Bolsa

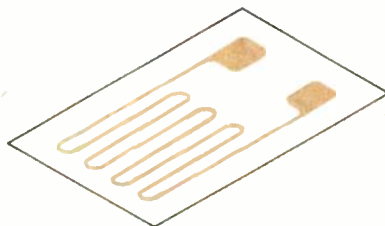


FIG. 4—A TYPICAL strain-gage design.

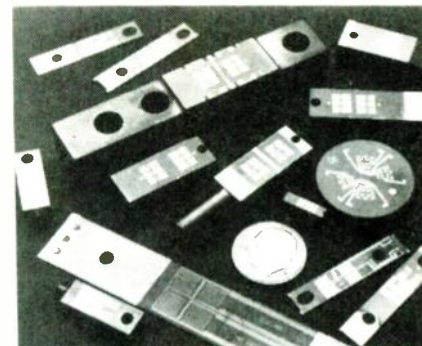


FIG. 5—STRAIN GAGES are made in a number of configurations and designs for different applications.

Ln., Cerritos, CA 90701), are shown in Fig. 5.

The strain gage is usually bonded to the spring element with an adhesive like epoxy. The quality of the bond is critical since the adhesive must accurately transfer any spring-element deformation to the strain gage. A poor bond will result in "creep"—a slippage between the strain gage and the spring element. That will make it look as if the input is slowly changing when, in fact, it is not.

The change in strain-gage resistance is related to strain by the gage factor, that is defined as the ratio of the unit change in resistance to the strain, or:

$$G = (r/R)/S \quad (2)$$

where  $G$  is the gage factor,  $R$  is the initial (unstrained) resistance of the gage,  $S$  is the strain, and  $r$  is the change in resistance resulting from a change in length. Most strain gages have an initial resistance of 120 or 350 ohms. For most metal-foil strain gages, the gage factor is usually between 2 and 3; the precise value depends on the composition of the alloy used for the foil conductor.

The last equation can be rewritten in terms of  $r$ , or:

$$r = GRS \quad (3)$$

That shows that, since both  $R$  and  $G$  are constants of the strain gage, the change in resistance is proportional to the strain.

Most strain-gage transducers use metal-foil strain gages. However, transducers using semiconductor strain gages are gaining popularity. Instead of a metal alloy, they are built using semiconductor material. Functionally, they are similar to metal-foil gages, but they have a higher initial resistance and a larger gage factor. Since they can be made very small, they are often used in miniature transducers.

### The bridge circuit

So far, we've seen that the change in strain-gage resistance is proportional to the change in the length of the spring element. And we've seen that the change in the length of the spring element is proportional to the applied force. Since both of those relationships are linear, we can

say that the change in resistance is proportional to the applied force. But a resistance change itself is not always a convenient parameter to measure because data loggers, computers, and process controllers usually require a voltage or current signal.

We could convert the resistance change into a voltage change by connecting a resistor in series with the strain gage and applying a DC voltage across the pair. If we used a series resistor of the same value as the strain gage and applied 5-volts DC, the voltage at the junction of the strain gage and the resistor would be 2.5 volts. A change made in the strain-gage resistance would then produce a change in that voltage.

Notice that it is the change in voltage that we want, because it is the change in voltage that is proportional to the change in resistance. But the change will be very small compared to the initial value of 2.5 volts. It's as if the desired signal voltage has been summed with a large, unwanted DC bias voltage. We can't amplify the small change until we eliminate the initial 2.5 volts. In transistor amplifiers, DC bias is often removed with a coupling capacitor, but we can't use that technique here because we want the steady-state voltage change as well as the dynamic change. What we need is some way to null out the initial voltage level.

One approach would be to configure the strain gage in a resistance bridge, as shown in Fig. 6. If the three resistors and the strain gage were all of the same resistance, the voltage at the junction of each pair would be the same. As a consequence, the voltage difference from one junction to the other would be zero. If we consider that voltage difference to be the output, ( $e_o$ ) then we have effectively nulled out the initial voltage but preserved the DC response of the strain gage. We have also re-invented the Wheatstone bridge.

Unlike the Wheatstone bridge, though, balancing serves only to null out the initial voltage level. To make a measurement with that type of circuit, the bridge must

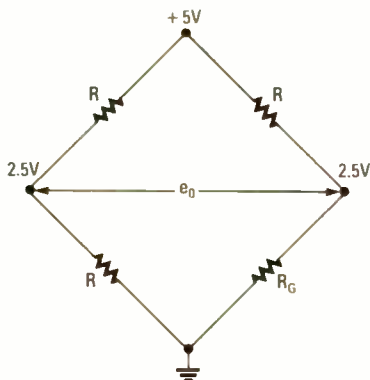


FIG. 6—USING A BRIDGE CIRCUIT allows us to null out the bridge supply voltage and only see the DC response of the strain gage.

be unbalanced by a change in the strain-gage resistance. That will cause a change in voltage difference across the bridge. We can use that change as an indication of the change in strain-gage resistance.

In the circuit of Fig. 6, you will find that for very small resistance changes, the output voltage appears to be a linear function of the change in resistance. But, as the change becomes larger it is no longer linear. We could limit the non-linearity to an acceptable level by limiting the change in resistance. But there is a better way.

Non-linearity can be eliminated entirely by building the bridge from four identical strain gages, instead of just one. The resulting circuit, which is known as a *four-arm, fully-active bridge*, is shown in Fig. 7.

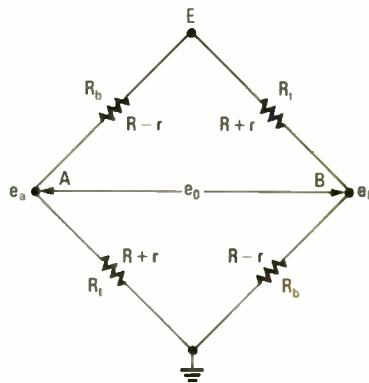


FIG. 7—A FOUR-ARM, FULLY-ACTIVE BRIDGE is made up of four identical strain gages.

The output of that bridge is a linear function of the change in strain-gage resistance, provided that the change in each strain gage is identical and that the change in two of the gages will result in an increase in resistance while the change in the other two will result in an identical decrease. In addition to being linear, the output of the circuit is higher and less sensitive to environmental changes than that of the single-gage bridge configuration. That type of circuit is used almost exclusively in strain-gage transducers.

To see how it works, let's use the spring element again as shown in Fig. 8. At some point near the fixed end of the bar, we will bond two of the strain gages to the upper surface, and the other two directly below them on the lower surface. In Fig. 8,  $R_t$  refers to the gages on top of the spring element and  $R_b$  refers to those on the bottom. When no force is applied to the bar, the top and bottom surfaces will be the same length. Since all four of the strain gages have the same initial resistance, the bridge will be balanced and the potential difference across the bridge will be zero. If we now apply a force to the end of the bar, the upper strain gages will increase in length and the lower gages will decrease. That is shown in Fig. 8 as  $R + r$

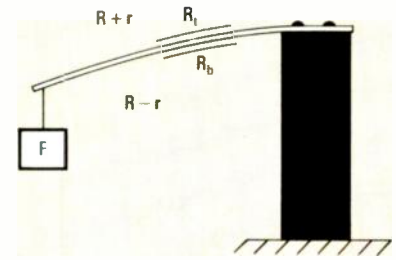


FIG. 8—WHEN FORCE IS APPLIED to the end of the spring arm, the resistance of the strain gages on its upper and lower surfaces change by equal but opposite amounts.

and  $R - r$ . Note that since the upper and lower strains are equal,  $r$  is the same for all four gages. But, since they are opposite in direction,  $r$  is then added to the gages on top and subtracted from the gages on the bottom.

We can show that the relationship between the voltage difference across the bridge and the change in resistance is linear. The first step is to find an expression for the voltage at point A ( $e_a$ ) of the bridge (as shown in Fig. 7) as a function of the change in resistance. If we look at the bridge circuit as the parallel combination of two series resistances, we can see that the voltage at point A is given by:

$$e_a = I(R + r) \quad (4)$$

where  $I$  is the current in the left leg of the bridge. But  $I$  can be expressed as:

$$E / [(R - r) + (R + r)] = E / (2R) \quad (5)$$

where  $E$  is the bridge supply voltage. Combining those equations yields:

$$e_a = E(R + r) / (2R) \quad (6)$$

We can find an expression for the voltage at point B of the bridge in the same way, which yields:

$$e_b = E(R - r) / (2R) \quad (7)$$

Since  $e_a$  and  $e_b$  are both referred to ground, the difference in potential ( $e_o$ ) between point A and point B is just the difference between  $e_a$  and  $e_b$ , or:

$$e_o = e_a - e_b = E[(R + r) / (2R)] - E[(R - r) / (2R)] \quad (8)$$

That can be further reduced to:

$$e_o = Er / R \quad (9)$$

The last equation shows that the bridge output voltage is directly proportional to the change in strain-gage resistance.


The four-arm fully-active bridge has another advantage over the single strain-gage bridge. While the single strain gage is mounted on the spring element, the other three resistors must be mounted in a strain-free location. That means that the strain gage could be subjected to temperature changes that are different from those seen by the other three resistors. Since a temperature change will cause a

continued on page 83

## The Early Days of RADIO

*More nostalgia  
from radio's  
pioneer days.*

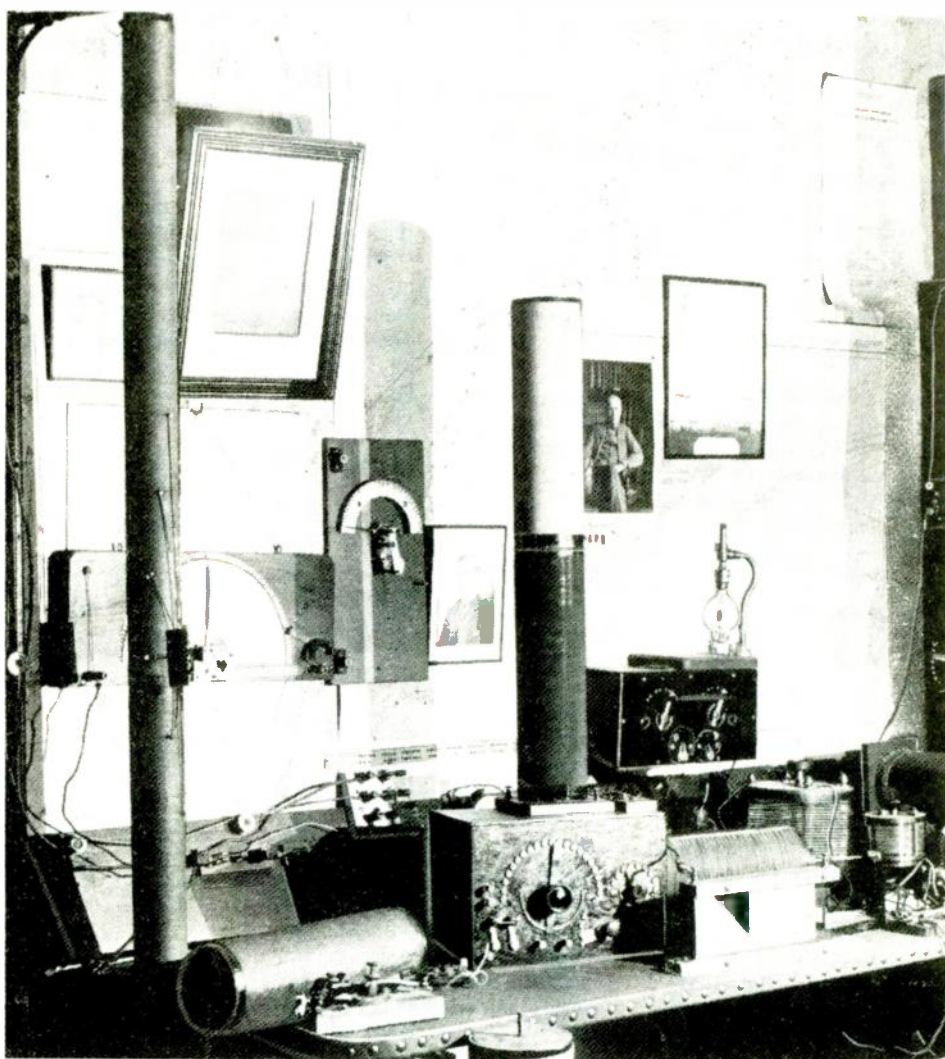**Part 5** AS IMPORTANT AS AMPLIFICATION was during radio's early days, an even more important receiver criterion was selectivity. Selectivity is a measure of the ability to receive closely spaced signals without interference from each other. Improved selectivity was usually attained by using taps on the antenna coil to increase its Q through better impedance matching on both sides of the antenna coil. Figure 1 shows two "selective" circuits used by the early radio experimenters. In Fig. 1-a the taps on both the primary and the secondary of antenna coil L1 are adjusted for best reception or minimum interference. In Fig. 1-b a separate tapped antenna loading coil (L2) is used to peak the antenna itself for a particular range of frequencies, and a tapped inductor (L3) increases the



impedance that L1 "sees" when looking into the rectifier.

But better selectivity created an unforeseen problem: insufficient receiver sensitivity. Being able to tune between the local powerhouse signals allowed the listener to partially hear much weaker signals from far-away places, and so was born "DX'ing"—DX'ing meaning the reception of distant signals. Unfortunately, crystal detectors could not provide sufficient volume from the weak DX stations. The need for more volume, coupled with a sharp decrease in the price of vacuum tubes, sounded the death knell for the crystal receiver. At first, only one tube was used for amplification; then, two; and finally three or more as designers learned how to build multi-stage amplifiers that didn't break into self-oscillation if the canary chirped.

### Audio coupling

As shown in Fig. 2, early audio amplifiers used transformer coupling between

stages, starting at the crystal detector. The transformers provided an amplifier's plate load, DC blocking, and AC coupling into the following stage. Though the transformer simplified interstage connections, the DC current flowing in the primary winding of the amplifier-output transformers caused core saturation, which reduced the effective inductance of the transformer—thereby producing a distorted sound. Known as *hysteresis* distortion, it marked the beginning of awareness of the need for better sound quality.

Various attempts were made to get around core saturation. The most effective, of course, was to use a transformer with "more iron," but this led to transformers that weighed more than a small boat anchor. The next attempts at reducing core saturation were the circuits shown in Fig. 3, where the transformer was isolated from the DC circuit. The tube got its plate voltage either through an adjustable power resistor (R in Fig. 3-a) or through

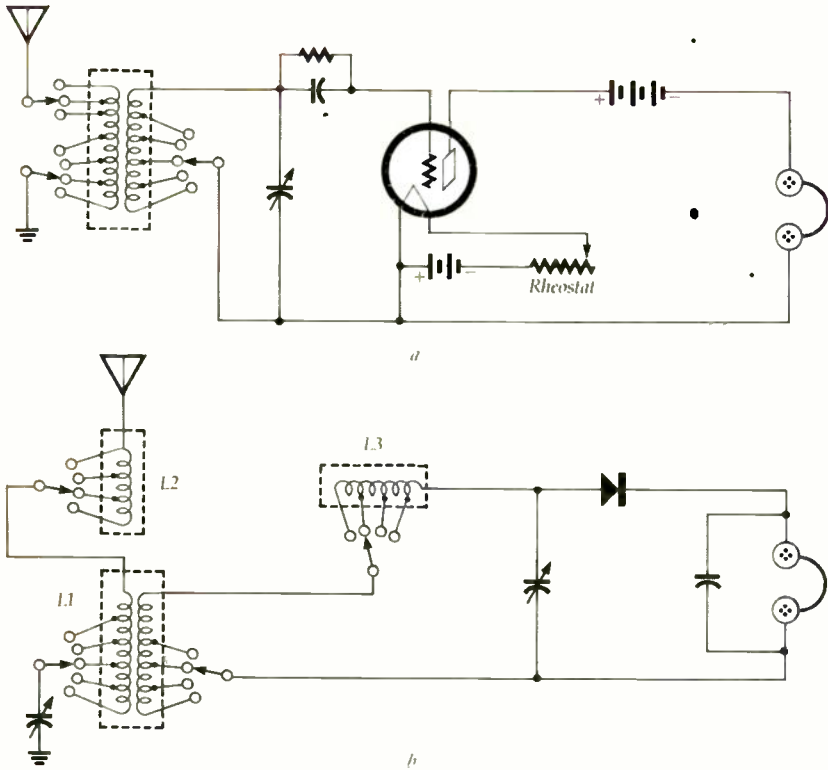


FIG. 1—SIMILAR TUNING METHODS were used for both single-tube and crystal receivers.

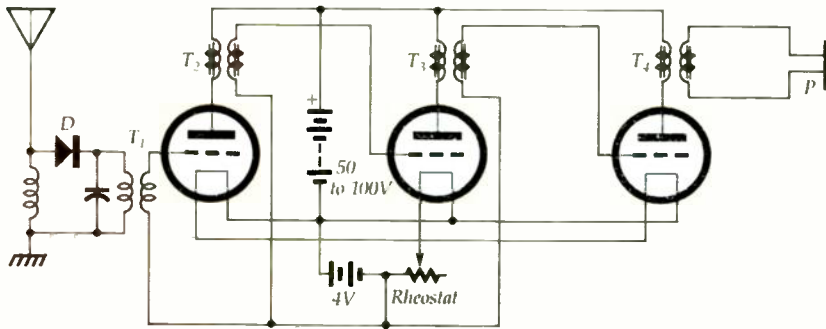


FIG. 2—INITIALLY, A CRYSTAL receiver's multistage audio amplifier was transformer coupled.

an inductor ( $L$  in Fig. 3-*b*). In both instances, capacitor  $C$  effectively isolates interstage transformer  $T$  from the DC plate voltage/current.

Neither circuit became popular because resistor  $R$  required a larger-than-usual battery voltage, while inductor  $L$  was frequency-selective.

One of the first attempts to eliminate the interstage transformer completely was the impedance-coupling circuit you'll find shown in Fig. 4. Unlike the interstage transformer, it did not supply voltage step-up. Also, as with other attempts to use an inductor as the plate load, coil  $L$  was frequency-selective.

### Resistance coupling

The really big breakthrough in both performance and production cost was the re-

sistance-coupled circuit shown in Fig. 5. It was inexpensive to build, had no inductors or transformers to saturate, and was not frequency-selective. Hence, it resulted in better sound quality. The disadvantage of resistance coupling was that the voltage drop across plate load-resistor  $R$  necessitated a higher battery voltage to make up for the voltage drop.

The disadvantages of resistance, transformer, and impedance coupling were overcome in 1931 by the invention of the first practical direct-coupling system by E.H. Loftin and S.Y. White. As shown in Fig. 6, in the direct-coupled amplifier the plate of one stage was directly connected to the grid of the following stage. Its advantages were its low manufacturing cost, and the possibility of greater fidelity, because it contained no frequency-discrimi-

nating components. Early units had a flat frequency-response capability of 30 Hz to 7,000 Hz, with the possibility of extending the upper limit to 10,000 Hz, which was an upper limit for those days.

### Electron flow

Prior to the invention of the diode and

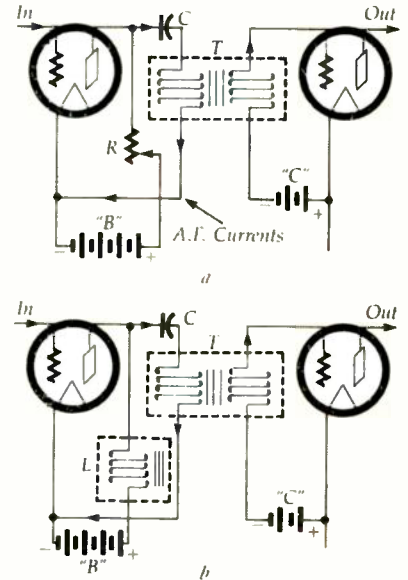


FIG. 3—THESE ARE TWO WAYS by which DC was kept out of the interstage transformer.

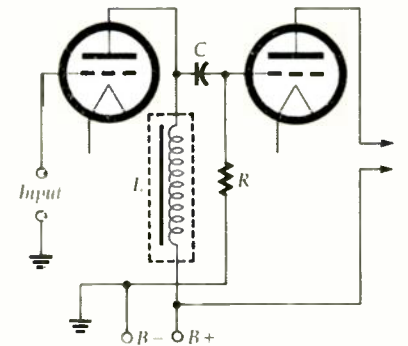


FIG. 4—IMPEDANCE COUPLING eliminated the interstage transformer, but still used an inductor ( $L$ ) for the plate load.

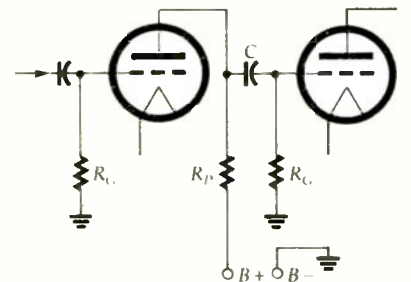


FIG. 5—IN RESISTANCE COUPLING there is neither a transformer nor an inductor. Resistors  $R_p$  and  $R_c$  and capacitor  $C_3$  provide the interstage coupling.

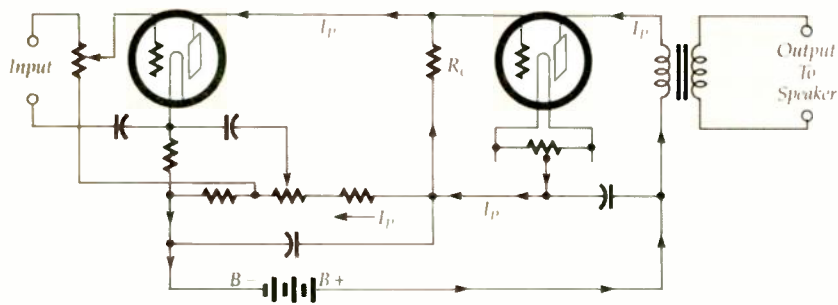


FIG. 6—DIRECT INTERSTAGE COUPLING provided the best fidelity. Note that the direction of the arrows indicates what is called "conventional current flow"; something that never really existed.

were held together with string or a rubber band (Fig. 7-b). The value of the capacitance thus achieved was unknown, but it didn't matter because it was usually used for a non-critical receiver circuit.

### Headphones and speakers

As shown in Fig. 8, headphones evolved from the telephone industry; in fact, the first earphone was the "roaring twenties" standard telephone receiver, and its spin-off *watchcase* receiver (Fig. 8-a)—which was specifically designed for use with a radio. Although both types worked with radio receivers, they had two problems: (A) they were fatiguing because they had to be supported by hand, as shown by the complete radio in Fig. 8-b; (B) they had a very low impedance of approximately 75 ohms. Eventually, their

rows shown in Fig. 6, an original drawing of the Loftin-White direct-coupled amplifier, indicates conventional current flow.

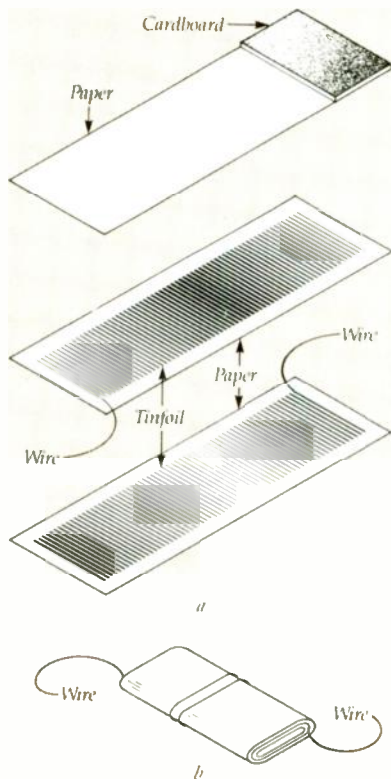


FIG. 7—EXPERIMENTERS MADE CAPACITORS from interleaved strips of tinfoil and paper held together by a rubber band or string.

triode tubes, the movement of an electron current was thought to be from positive to negative, a concept based on the ideas of Benjamin Franklin, who, having a 50-50 chance of guessing right, guessed wrong. Current flow in a vacuum tube clearly showed that current moved from a negative filament (cathode) to a plate (anode) that carried a positive charge. Although correct, the electron concept confused many experimenters, technicians, and engineers who had adopted the positive-to-negative concept and were most unwilling to give it up. Consequently, the electric and electronic industries compromised, and positive-to-negative current flow was called *conventional current flow*, while negative-to-positive current flow was called *electron flow*. For example, the ar-

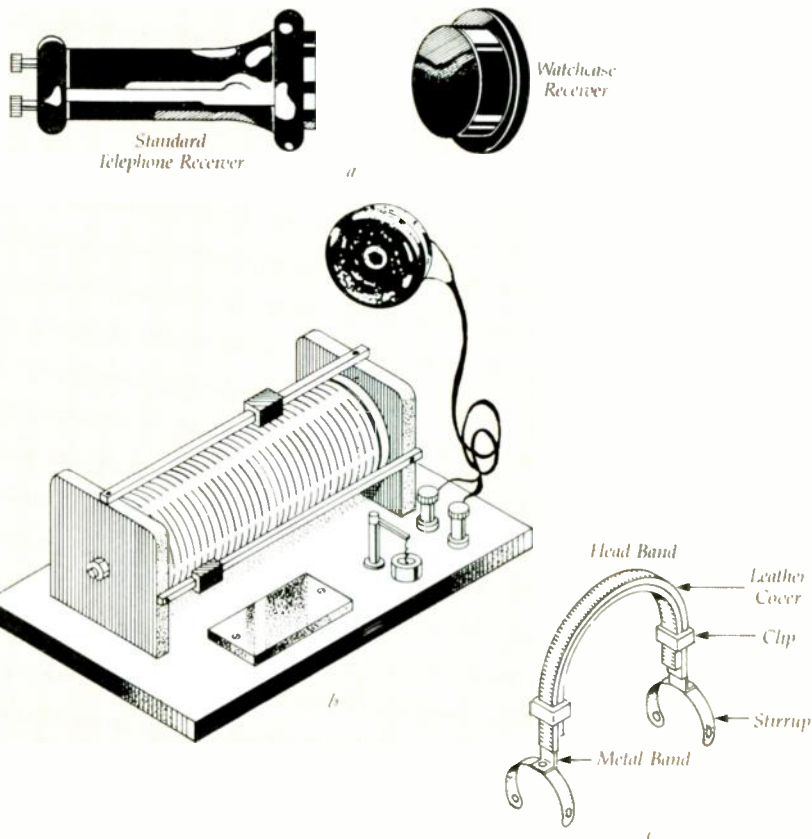


FIG. 8—THE DEVELOPMENT OF HEADPHONES: It started with a conventional telephone receiver, and ended in a headband.


### Capacitors

In the early days of radio, to avoid the relatively high cost of capacitors, many experimenters and hobbyists "rolled their own" using the tinfoil from a pack of cigarettes and small sheets of paper. As shown in Fig. 7-a, alternate layers of foil formed the plates of the capacitor, whereas the paper was used for the dielectric. The interleaved sheets of tinfoil and paper

impedance was increased to about 100 ohms, and finally to about 1000-3000 ohms. Fatigue was mitigated when the headband shown in Fig. 8-c was invented. It allowed the user to literally "wear" the receiver. When one or two receivers were mounted in a headband the entire assembly was called a "headphone," "headphones," or "headset."

*continued on page 76*

# R-E ROBOT

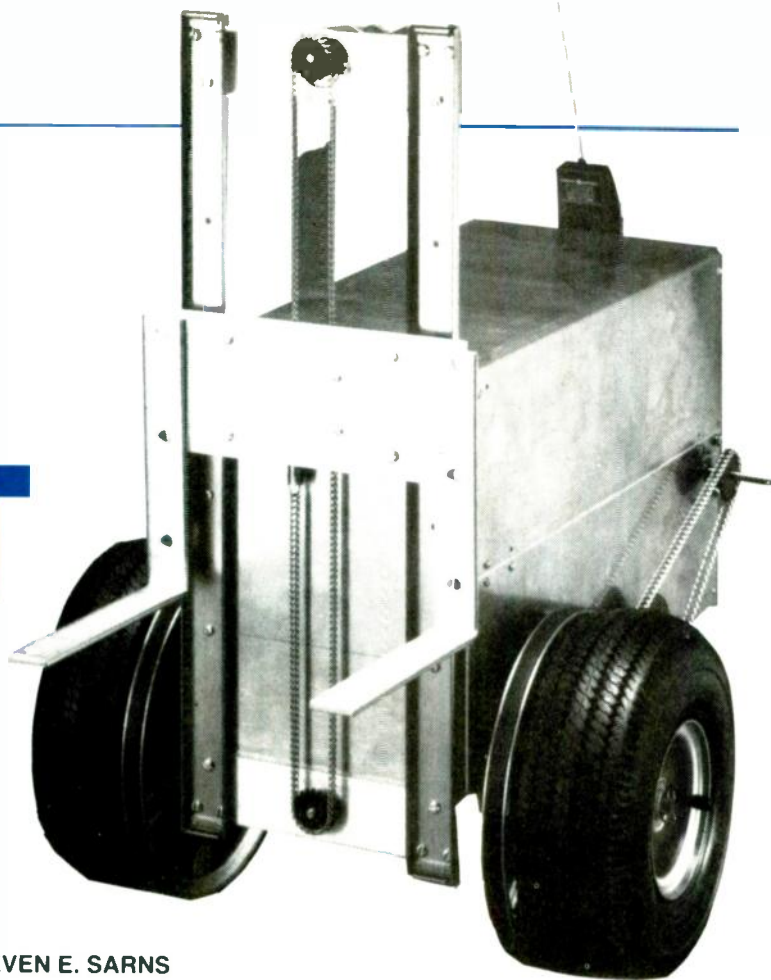

*This month, we add the first of the R-E Robot's sensors—an electronic eye.*

**Part 12** AT THIS POINT, OUR robot is an efficient tractor unit, moderately intelligent, with plenty of pulling power. He can carry items from place to place, and can understand complex instructions. However, he is also as blind as a bat. To make the unit as useful as possible, we must give it a way to see.

You can fully appreciate the severity of the problem by imagining the following example: You are at the end of a hallway. Several doors can be chosen. Look carefully, close your eyes and, without touching or peeking, walk forward and turn into a doorway.

That is what we were asking the robot to do when we programmed the MAILBOT example in Part 9 of this series (**Radio-Electronics**, August 1987). Instructions like "Go forward 10 steps, turn right, and then go forward again 10 steps" seem clear enough on paper, but what if you did not turn exactly 90 degrees? What if your steps were short for some reason? Worst of all, what if you lost your bearing and had to start over, all without peeking?

To make it easier for the robot to get around, we will give it the ability to detect and track light sources. That capability will allow the robot to follow a light beam or an optical stripe on the floor.

Ideally, we also would like to provide the robot with the capacity to determine the distance to a light source and to triangulate its position using several light sources. Unfortunately, the software required to perform those last two tasks is quite formidable, and at this time is far from being fully developed. For now, we will discuss the problems involved in giv-

STEVEN E. SARNS

ing the robot those capabilities, and the hardware needed to input the data that future software will require.

The robot eye will eventually be mounted on a rotating platform, or "head." The head will contain the electronics for a number of the robot's sensors and will be discussed in more detail in the next installment of this series. The head will move the eye through a few degrees, mapping light intensities at several points. The data collected in that way will be used by all of our navigation schemes.

### Navigation schemes

The navigation scheme that we will implement now permits the robot to track a light beam. The robot will rotate the eye until a light-intensity maxima is determined. The robot will then angle toward that maxima.

For the future, position-finding is merely an extension of that navigation technique. By mapping the maxima of several known light sources, the robot can determine its position fairly accurately using triangulation.

For range-finding, we will need to add a second eye to the head. Then, the robot can use parallax to determine the distance between it and an unknown light source. The parallax principal, in which the difference in viewing angle at two points that are equidistant from the third are used to determine the distance to that point, is

what provides humans with depth perception; the two equidistant viewing points are our two eyes. See Fig. 1. Note that the technique is only good at relatively close ranges. But remember that even humans lose their depth perception at distances beyond 30 feet.

### The human eye

In terms of design, the human eye is difficult to match. The spectral response is not too wide, ranging from 360 to 780 nanometers, but color is of secondary importance to other factors. The eye is capable of resolving details as small as one minute of arc ( $1/60$  of a degree). And most importantly, the eye can operate in a very wide range of light intensities, ranging from star-lit night to bright sunlight. If those light levels are quantized, you will find that the range is on the order of 180 dB, or a billion to one.

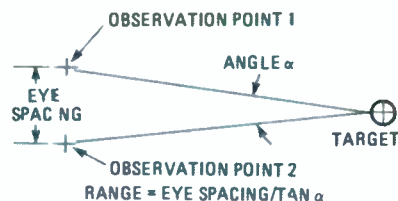


FIG. 1—USING PARALLAX to determine the distance to an object.

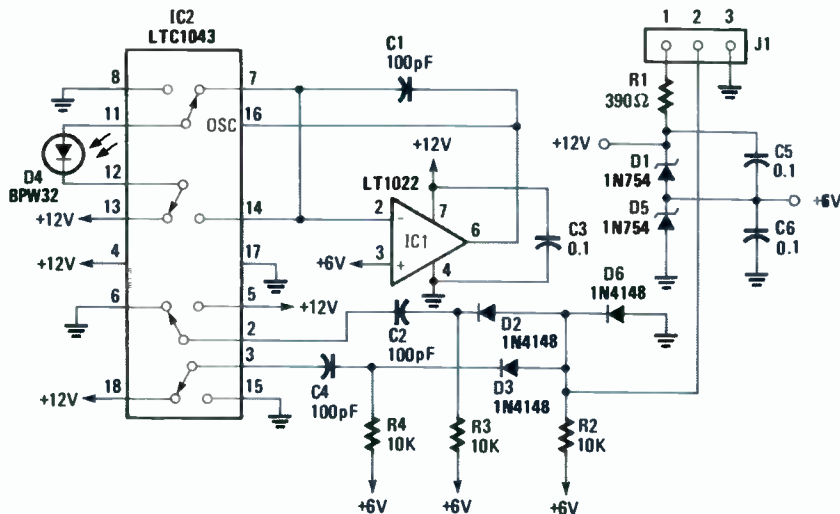


FIG.2—THE ROBOT'S EYE. The photodiode, D4, can be configured to source or sink current by IC2.

### The robot eye

Our design goal was to make the robot's eye useful over as wide a range of light conditions as possible. While it is unlikely that you will need to have the robot navigate by starlight, giving the robot low-light capabilities will increase its distance range. Since light follows the inverse square law, that is, the illumination is inversely proportional to the square of the distance, light levels fall rapidly as you move away from the source. At the same time, operation at conventional ambient light-levels must be possible, and the robot should be able to deal with most common light sources.

Therefore, we feel that the minimum acceptable range should span at least 4 orders of magnitude (10,000:1 or 80 dB); that corresponds (using the inverse square law) to tracking an ideal light source over a 100:1 distance range. The maximum possible dynamic range using readily available components is about 120 dB. That corresponds to a light range of 1,000,000:1, or a distance range of 1000:1.

We choose .01 lux as the lowest light level that we wish the sensor to respond to. A lux is the amount of light falling on

one square meter from a candle located one meter away. That is at the extreme low-end of most detectors so to improve performance we will enhance the unit's light-gathering power with a Fresnel lens. Focusing a 4-square-inch Fresnel lens will amplify the light level by a factor of 100. If we were to focus such a lens on the sensor, a light level of .01 lux at the lens will result in a light level of 1 lux at the sensor. Most detectors can work with such a light level.

As we mentioned earlier, future range-finding requires that the robot be equipped with two eyes. Those will be mounted 10-inches apart on the head. If the robot can locate a light source to within 5 degrees of arc, that spacing will allow range finding at distances of up to 30 feet.

### Selecting a sensor

Many different sensors for measuring illumination are available. Phototransistors, photodiodes, and PIN photodiodes are all common and well understood.

If our prime design criteria is dynamic range, then we must choose the device with the largest sensitivity range. The key parameter in determining a unit's sensitivity is its *dark current*; that is the leakage current that flows when no light reaches the device. In general, photodiodes have the greatest ratio between dark current and high-illumination output. One, the Siemens BPW32 has a rated dark current of less than 10 pA and a high-level output at 10,000 lux of 100  $\mu$ A. Those figures represent a dynamic range of 140 dB. Typical output currents of that photodiode for various light levels are shown in Table 1.

Note that the photodiode's output current becomes non-linear above 1,000 lux and below .001 lux. Also, remember that linearity can also be affected by the supporting circuitry. If you can not locate the

Light Level	Photodiode Current
10,000 lux	100 $\mu$ A
1,000 lux	10 $\mu$ A
100 lux	1 $\mu$ A
10 lux	100 nA
1 lux	10 nA
0.1 lux	1 nA
0.01 lux	100 pA
0.001 lux	10 pA
0.0001 lux	1 pA

## PARTS LIST

All resistors are 1/4-watt, 5%

R1—390 ohms

R2—R4—10,000 ohms

Capacitors

C1, C2, C4—100 pF, ceramic disc

C3, C5, C6—0.1  $\mu$ F, ceramic disc

Semiconductors

IC1—LT1022 op amp (Linear Technology)

IC2—LTC1043 IC switch (Linear Technology)

D1, D6—1N754 Zener diode

D2, D3, D5—1N4148 diode

D4—BPW32 photodiode (Siemens)

Other components

J1—male header

Miscellaneous: Fresnel lens, PC board, wire, solder, etc.

The 2.3-inch Fresnel lens can be ordered for \$10.00 each, plus \$6 postage and handling, from Edmund Scientific Company, 101 East Gloucester Pike, Barrington, N.J. 08007, (609) 573-6250. The part number is E32,589. NJ residents must add appropriate sales tax.

A bare printed-circuit board for the eye can be obtained from Vesta Technology Inc., 7100 W. 44th St., Wheatridge, CO 80033, (303) 422-8088, for \$19 each. An assembled and tested eye PC board, Fresnel lens not included, is available for \$59. CO residents must add appropriate sales tax.

Siemens component, a suitable substitute is NEC's PH201A photodiode.

### The circuit

A schematic diagram of the eye circuit is shown in Fig. 2. The BPW32 photodiode, D4, provides an output current that is proportional to the illumination level. That small current will span a range of 10 million to one. If we were to convert the current into a voltage and the voltage into a binary number with an analog-to-digital converter, we would need a 23-bit unit! For example, if the full-scale voltage was 5, then the least significant bit would be 5 microvolts. Such a unit, if you could find one, would cost thousands of dollars.


Instead, we will convert our current into a frequency and use the RPC (Robotic Personal Computer) to determine the period of the frequency. That will give us the dynamic range that we need, since a 140-dB range can be accommodated using a frequency band of 0.1 Hz to 1 MHz. The circuit will output approximately 200 kHz when held 3 inches away from a 60-watt light bulb in a reflective lamp. The circuit will output 0.5 Hz when illuminated by the trace of an oscilloscope 2 feet away.

The frequency range used is critical. The eye must rotate a small amount, take a reading and repeat the process continu-


*continued on page 84*



# PC SERVICE

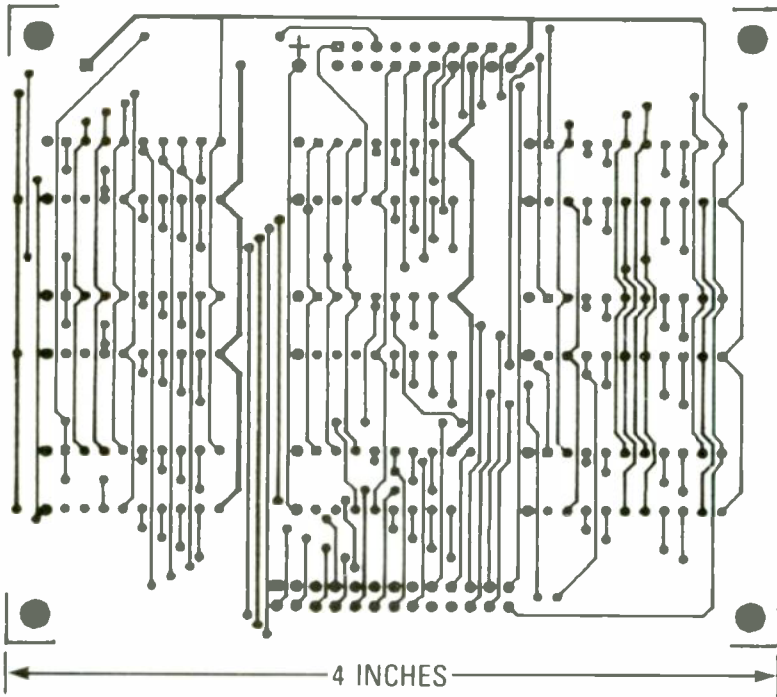

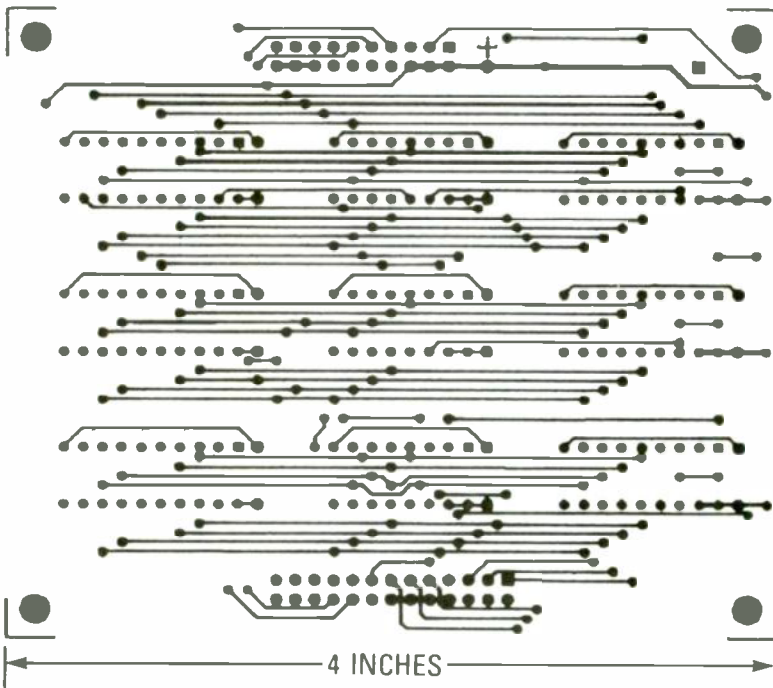THE IC TESTER'S DRIVER BOARD. The foil side is shown here.



MOUNT THE COMPONENTS ON THIS SIDE of the IC Tester's driver board. The PC pattern for the main board will be shown next time.

One of the most difficult tasks in building any construction project featured in **Radio-Electronics** is making the PC board using just the foil pattern provided with the article. Well, we're doing something about it.

We've moved all the foil patterns to this new section where they're printed by themselves, full sized, with nothing on the back side of the page. What that means for you is that the printed page can be used directly to produce PC boards!

**Note:** The patterns provided can be used directly only for *direct positive photoresist methods*.

In order to produce a board directly from the magazine page, remove the page and carefully inspect it under a strong light and or on a light table. Look for breaks in the traces, bridges between traces, and in general, all the kinds of things you look for in the final etched board. You can clean up the published artwork the same way you clean up your own artwork. Drafting tape and graphic aids can fix incomplete traces and doughnuts, and you can use a hobby knife to get rid of bridges and dirt.

An optional step, once you're satisfied that the artwork is clean, is to take a little bit of mineral oil and carefully wipe it across the back of the artwork. That helps make the paper translucent. Don't get any on the front side of the paper (the side with the pattern) because you'll contaminate the sensitized surface of the copper blank. After the oil has "dried" a bit—patting with a paper towel will help speed up the process—place the pattern front side down on the sensitized copper blank, and make the exposure. You'll probably have to use a longer exposure time than you are used to.

We can't tell you exactly how long an exposure time you will need as it depends on many factors but, as a starting point, figure that there's a 50 percent increase in exposure time over lithographic film. But you'll have to experiment to find the best method for you. And once you find it, stick with it.


Finally, we would like to hear how you make out using our method. Write and tell us of your successes, and failures, and what techniques work best for you. Address your letters to:

**Radio-Electronics**  
Department PCB  
500-B Bi-County Blvd.  
Farmingdale, NY 11735

---


---

# PC SERVICE

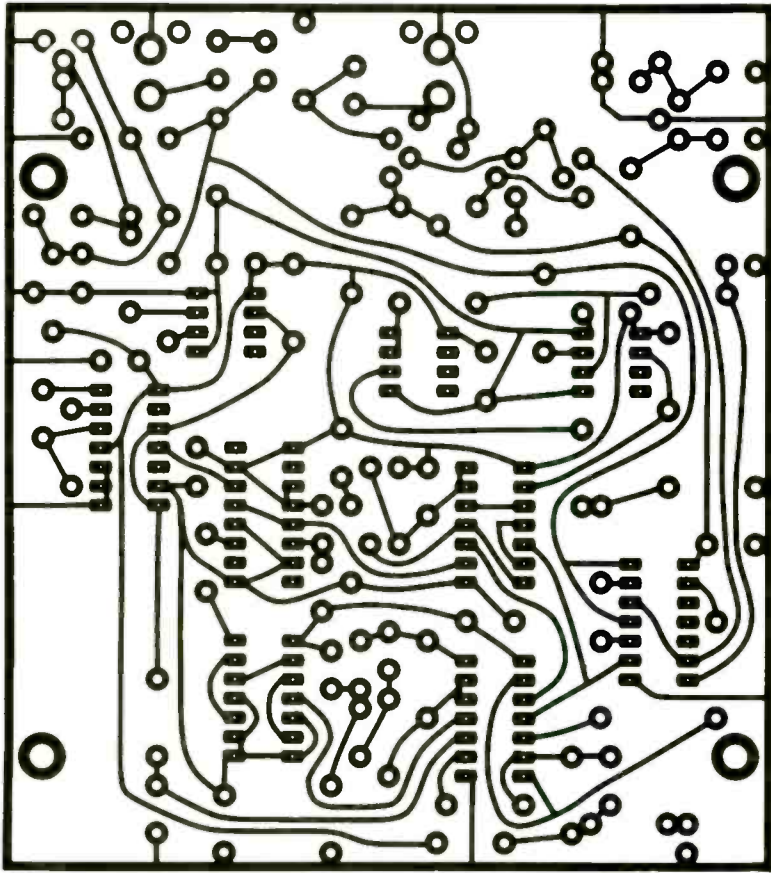


4 INCHES

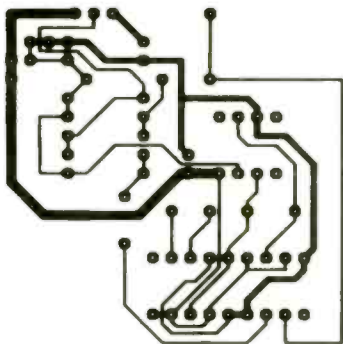BUILD THE MACROSCRUBBER using this board.



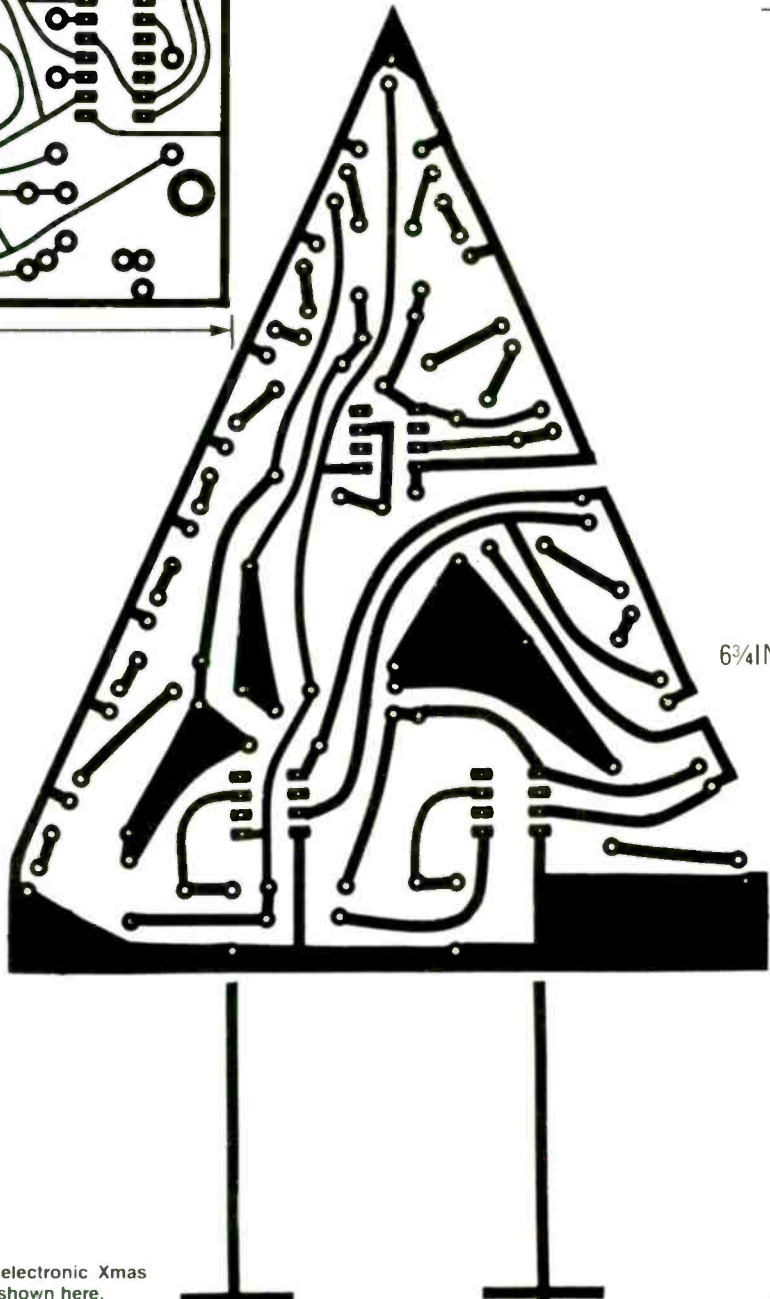2.3 INCHES

THE ROBOT EYE'S PC board is shown here. Remember that the components mount on the foil side.



6 3/4 INCHES


LIGHT UP THE HOLIDAYS with the electronic Xmas tree. The PC board for that project is shown here.

# PC SERVICE
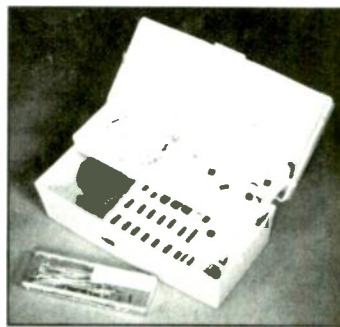
# EIA/CEG AUGMENTS DIGITAL AND MICROPROCESSOR COURSE HIGH TECH PARTS KITS NOW AVAILABLE

The members of the Electronic Industries Association Consumer Electronics Group (EIA/CEG) through the Product Services Committee, has marketed the illustrated parts kit for vocational schools, educators and technicians. This is the same material used in the Digital and Microprocessor Course during EIA's summer workshop programs. These workshops are organized by the Consumer Electronics Group and co-sponsored by national service organizations and state departments of vocational education.

Parts and components are contained in a lightweight tool box with individual compartments. It includes a breadboard, power supply, pre-dressed jumpers, resistors,



capacitors, and integrated circuits to perform all digital exercises 1 through 25 of the Digital/Microprocessor course book listed in the table of contents. Some parts have been included for the microprocessor section but other components will have to be acquired (as listed in the Introduction to Exercises 26-31).

Individual and classroom size quantities are available at the following cost: quantities 1-9, \$69.95 each, quantities 10-19, \$67.95 each, and for quantities 20 or more, \$64.95 each (cost includes shipping and handling). The kits will also include the Digital and Microprocessor Course book. Additional books are available at the cost of \$2.00 per copy.

## PLEASE COMPLETE ORDER FORM FOR PARTS KITS AND BOOKS

Send to: EIA/CEG, Department PS, P.O. Box 19100, Washington, D.C. 20036

**ORDER FORM**

Parts Kit	Quantity	Amount	Total
1-9 .....	_____	\$69.95 each	_____
10-19 .....	_____	\$67.95 each	_____
20 or more .....	_____	\$64.95 each	_____
<b>Additional Digital/Microprocessor Course Books</b> .....	_____	\$2.00 per copy	_____
<b>Total Amount Enclosed</b>			_____

Name																		
Title																		
Firm																		
Address																		
City											State			Zip				

---

---

# SATELLITE TV



**BOB COOPER, Jr.**  
SATELLITE-TV EDITOR

## What's next?

BY THE MOST ACCURATE COUNT, THE home-dish industry was producing, selling, and installing as many as 70,000 home-dish systems per month in the fall of 1985. Now, the most accurate figures suggest that fewer than 12,000 home-dish systems are being sold per month at the present time.

Those numbers mean different things to different groups. The cable-television industry sees a "thriving low-power satellite broadcasting business". The home-satellite industry, the people who manufacture, distribute, and install such systems "sees a business on the verge of collapse". Both of the preceding quotes appeared in the July 20, 1987 issue of *Broadcasting Magazine*, which contained a full report on the status of the home-dish industry.

### Death of an industry

Which view is correct? One only has to peruse the few remaining trade publications serving the TVRO market, or to attend an electronic flea market to witness the depth of the industry's doldrums. Complete home systems with 10-foot dishes are wholesaling for under \$400; individual parts, such as 70° Kelvin LNB's are selling for as little as \$40. Much of the merchandise warehoused in the spring of 1986 for the anticipated 1986 is still there.

Several pieces of legislation have been introduced to provide some form of assistance to an ailing industry and a stunted communications medium. Hearings in support of that legislation were

held, but the legislation was never enacted. And even if it were, at best it would have made it *slightly* more difficult for satellite programmers and cable-television-system operators to maintain their present monopolistic control over programming access.

Control over programming—how it is distributed to home-dish owners and what it costs per service per month—is the central issue. Some say it is the *only* issue. Cable programmers and cable operators have married one another at the corporate level. TCI, the largest cable-system owner in the world, has bought substantial stock in services such as WTBS/CNN and others. Virtually every programmer making a profit has some or all of its stock owned by its customers, the cable system owners.

Home-dish proponents believe that such cross ownership has worked against the development of a "competitive delivery system". As David Wolford, a publisher in the home-dish industry told Congress: "Programmers such as HBO and Showtime/Viacom derive the vast majority of their revenue from cable operators. Are they really going to undercut the prices of their primary customers? The market is moving into a dangerous situation. If present conditions are allowed to continue, satellite TV will (end up being) controlled by its one and only natural competitor, cable TV."

Programmers such as HBO and Showtime have refused to date to allow anyone but themselves or their cable affiliates to market pro-

gramming to home-dish owners. Cable operators are further controlled by specified geographical territories outside of which they cannot sell to home-dish owners. That has resulted in a form of price control because there are no competitive forces at work. If you live within a cable franchise area and want HBO, you *must* buy from the local-cable HBO affiliate. If you live outside a cable franchise area, you *must* buy from HBO directly.

Cable trade-association head James Mooney told Congress: "Cable programming is readily available to home-dish owners at prices less than those paid by the average cable subscriber for the same service."

Others, such as Bob Phillips of the National Rural Telecommunications Corporation testified that his firm has not been able to buy cable programming for resale to home-dish owners at all, or in the best case they are paying 500% to 700% more per home than cable systems are paying for the identical programming service.

Stephen Shulte of Viacom/Showtime has his own pet theory as to why the home dish industry suddenly dried up and quit functioning. He told Congress: "The infrastructure of the (TVRO) industry grew up during a time when the basic selling argument (to would-be consumers) was erroneous...that cable programming was available at no charge (with a dish). When services started to scramble (their programming), the sales were simply no longer great enough to support the industry that had been created."

Charles Rule, acting assistant attorney general for the antitrust division of the Department of Justice seemed to agree with that assessment when he told Congress "(our) investigation has not uncovered the existence of any illegal concerted activity among cable operators (or programmers)."

### The next generation

Is this to be the end of direct broadcasting satellites for North America, an industry that did too well, too fast, and then was ill-equipped to face its adversaries? Probably not, but a significant period of readjustment is certainly ahead. Even the most optimistic cable-system operators admit that when the cable-television industry has completed the "wiring of America" between ten million and twenty million homes will still be without the magical cable interface. Would those homes be sufficient to support a direct-to-home satellite industry?

The answer of course is yes. But not using the present C-band satellites or frequencies. All planning for the future centers on the use of the 11-12 GHz band, generally called the K or Ku band. Several large firms, such as Comsat, have planned satellites to operate in those frequency bands. Most of those firms have suspended work on the project. Hubbard Broadcasting, a Minnesota-based television and radio station owner has plans to make use of that band. Hughes, the same people who pushed C-band satellite technology to new limits, plans a 1991 launch of a pair of satellites for Ku band as well; those satellites are intended specifically for direct-to-home broadcasting. RCA(GE)-Americom, in conjunction with HBO/Time-Life, also plans to launch Ku-band satellites sometime between 1989 and 1990.

But none of those would-be satellite operators has yet been successful in attracting programming to their satellites. Americom might have a slight advantage here; they have an investment in programming through their association with HBO and could at least fill up some channels from their own stock. But Hubbard and Hughes are offering some attractive finan-

cial deals to cable programmers such as Showtime, Turner, or ESPN.

For now, the route to the next generation of home-satellite broadcasting is not clearly marked. Nor is there any certainty that it will happen unless programmers such as Showtime feel comfortable that an offering on the Ku band will not in any way anger their existing cable-TV clients. HBO is even now trying to head off future problems by offering their

present cable customers exclusive rights to the sale of Ku-band programming within their cable-franchise territories. That of course translates to monopolistic control of programming rates and terms; the very thing that has stifled C-band sales and growth. **R-E**

### SCRAMBLE FACTS 718-343-0130

3 minutes of industry news, technical tips, and new product information.



## IF YOU LIVE IN THE CARIBBEAN, CENTRAL AMERICA, NORTHERN S. AMERICA or FLORIDA . . .

### WIN A PARACLIPSE HOME DISH SYSTEM!

Bob Cooper's **CARIBBEAN ELECTRONICS MAGAZINE** is giving away 12 complete Paraclipse 12' home dish systems between September 1, 1987 and August 31, 1988. **FREE.** No obligation of any kind! If you are an amateur radio operator in the 'qualifying area' (see map), simply send us your Ham radio QSL card. If you are in electronics but not a licensed amateur, send your business card. You may enter once per month for each of the 12 months but no more than once per month. The home dish system winners are announced in 'CEM' monthly starting with the November 1987 issue.

**PLUS** - when we receive your QSL card or business card, we will send you a **FREE** sample copy of the most exciting electronics magazine in the Caribbean; Caribbean Electronics. CEM covers every aspect of communications and broadcasting, just for those who live in the Caribbean and countries surrounding the Caribbean. And we do it in English and Spanish with special Spanish summaries for all feature articles.

**OUR** twelve **FREE** home dish systems feature the highly acclaimed Paraclipse 12 foot dish with tuned feed, state-of-the-art solid state actuator/controller, and the top-rated by test AVCOM 2 series receiver system with remote control. This is the best, quality system for home or commercial use in the Caribbean. Find out how our CEM Lab rates everything from power line filters to VCRs, shortwave radios to home computers for Caribbean use in Caribbean Electronics Magazine. Send us your QSL card or business card today!

**CARIBBEAN ELECTRONICS MAGAZINE**  
P.O. Box 100858, Ft. Lauderdale, FL 33310 USA  
Telephone: 305/733-9955; in Florida 800-367-8150

## 117 PRACTICAL IC PROJECTS YOU CAN BUILD

2645T—117 PRACTICAL IC PROJECTS YOU CAN BUILD..... \$10.95. Dozens of fully-tested, ready-to-build circuits you can put together from readily-available, low cost IC's! There are a total of 117 IC circuits ranging from an audio mixer and a signal splitter to a tape-deck amplifier and a top-octave generator organ! From TAB Books. To order your copy send \$10.95 plus \$2.75 shipping to Electronic Technology Today Inc., P.O. Box 240, Massapequa Park, NY 11762-0240



## FCC LICENSE PREPARATION


The FCC has revised and updated the commercial license exam. The NEW EXAM covers updated marine and aviation rules and regulations, transistor and digital circuitry. THE GENERAL RADIOTELEPHONE OPERATOR LICENSE - STUDY GUIDE contains the necessary preparation for ONLY \$25.00.

WPT PUBLICATIONS  
979 Young Street, Suite E  
Woodburn, Oregon 97071  
Phone (503) 981-6122

CIRCLE 186 ON FREE INFORMATION CARD
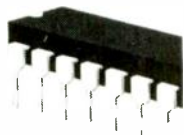
## LINEAR IC EQUIVALENTS & PIN CONNECTIONS

Linear IC  
Equivalents  
and Pin  
Connections




BP141—Shows equivalents & pin connections of a popular user-oriented selection of European, American and Japanese linear IC's 320 pages, 8 x 10 inches. \$12.50 Plus \$2.75 shipping. ELECTRONIC TECHNOLOGY TODAY INC., PO Box 240, Massapequa Park, New York 11762-0240.



HANDHELD GENERATOR/TESTER KITS • Function Gen. 1HZ to 300KHZ \$79.95 • Audio Gen. 8 steps 40HZ to 20KHZ \$69.95 • IF Gen. 455KHZ & 10.7MHZ, internal modulation \$59.95 • Transistor Tester, Tests PNP, NPN \$34.95 • FM Gen. 80 to 120MHZ, internal modulation \$59.95 • All kits include test leads. Any kit assembled & tested add 25%. Send \$1 for complete catalog & coupon. SEL LABS, 22848 LEADWELL ST., CANOGA PARK, CA 91307. (818) 347-1960.

CIRCLE 184 ON FREE INFORMATION CARD

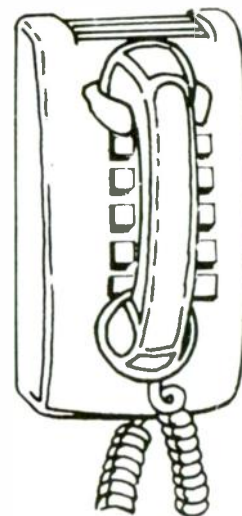

## CALL NOW AND RESERVE YOUR SPACE

- 6 x rate \$800.00 per each insertion.
- Reaches 245,824 readers.
- Fast reader service cycle.
- Short lead time for the placement of ads.

Call 516-293-3000 to reserve space. Ask for Arline Fishman. Limited number of pages available. Mail materials to: Engineering Admart, RADIO-ELECTRONICS, 500-B Bi-County Blvd., Farmingdale, NY 11735.

## EARLY RADIO

*continued from page 66*

There were two types of headphones used in the early 20's. One type had an iron armature that was mechanically connected to a mica or composition diaphragm. In the other, an electromagnet was used to attract an iron diaphragm that was supported around its circumference. An unusual design, called a "Baldwin receiver," used a fiber diaphragm; a later model had a diaphragm made of aluminum. Compared to speakers that were used during the early 1920's, a Baldwin-type headphone rendered superior sound.

The earliest speaker was a headphone put into a resonant chamber such as a glass bowl or a wood box. Subsequently, an enterprising experimenter developed a horn with tubular extension arms to ac-



FIG. 9—ONE OF THE EARLIEST ATTEMPTS to get more volume was a small horn that fitted over an earphone.

commodate a headset (Fig. 9).

Commercial horn speakers were soon manufactured. Some were little more than oversized headphone units attached to curved metal or paper-mache funnels (or even to brass automobile horns). Others, like the Magnavox (first to introduce the voice coil) with a 6-volt, 1-ampere field coil, and the Western Electric, produced very good sound.

Later in the 20's cones came into use. Most of the early ones were "balanced-armature" types like a Baldwin headphone. A stylus from the armature connected to the center of the cone.

These were superseded by the "dynamic speaker," still in use. A voice coil in a strong magnetic field is connected across a low-impedance winding on the receiver's output transformer. The coil and the cone moves in and out of the field in accordance with the signal.

R-E



# DRAWING BOARD

## Designer RAM



ROBERT GROSSBLATT,  
CIRCUITS EDITOR

EVER SINCE CP/M BEGAN TO DECLINE, people have been saying that the days of the Z80 were numbered—don't you believe it. It's true that you won't see many new computer designs done around a Z80, but it's also true that the Z80 has too much muscle to wind up on the silicon scrap heap. It's still one of the microprocessors of choice to use as a dedicated controller.

Building our dynamic-RAM system around a Z80 makes sense because the chip's built-in features relieve us of the burden of implementing much of the design in external hardware. We'll still need glue to put all the pieces together,

but not anywhere as much if we were building the whole circuit from gates alone.

There are four Z80 control signals that are critically important in the construction of our circuit. Understanding what they are, how they work, and what their timing relationships are, is the first step in the design. The four signals, all of which are active low, are:

- Memory Request ( $\overline{MREQ}$ ), pin 19
- Read ( $\overline{RD}$ ), pin 21
- Write ( $\overline{WR}$ ), pin 22
- Refresh ( $\overline{RFSH}$ ), pin 28

Let's discuss them one at a time.

$\overline{MREQ}$  is a control signal that is active whenever the Z80 has been

instructed to perform an operation that involves external memory. As soon as the Z80 has an address ready to put out on the bus it brings this line low. That happens for *all* memory operations: read, write, and refresh.

$\overline{RD}$  goes low when the Z80 wants data from the outside world, which can be from either a memory location or an I/O port. Therefore a request for a read from memory must be sensed by watching  $\overline{MREQ}$  as well as  $\overline{RD}$ .

$\overline{WR}$  is the opposite of  $\overline{RD}$ . When it goes low, the Z80 has data that it wants to send to either memory or an I/O device. Just as with  $\overline{RD}$ , the destination is determined by watching the  $\overline{MREQ}$  line.

$\overline{RFSH}$  is the signal that keeps the Z80 popular. When it goes low it signals that the microprocessor has incremented its internal refresh counter and has put the new refresh address on the lower seven bits of the address bus (A0-A6). By combining  $\overline{RFSH}$  signal with  $\overline{MREQ}$ , you can determine exactly when a refresh operation must take place in your system.

All memory operations require two Z80 control signals, so it's important that we have a good understanding of the timing relationships between them. And any discussion of timing must start with a look at the basic heartbeat of the Z80: the instruction cycle.

### M and T cycles

Figure 1 is a representation of the two fundamental parts of all Z80 instruction cycles: the M (machine) cycle, and the T (time, or clock) cycle. Every instruction that

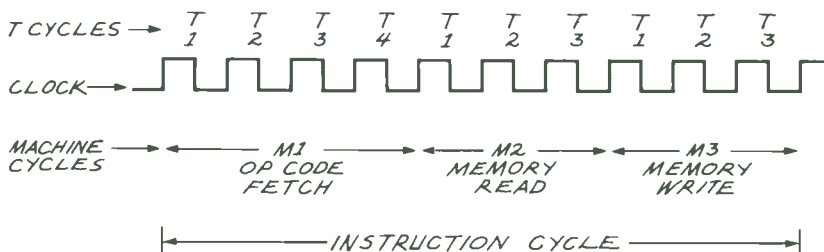


FIG. 1

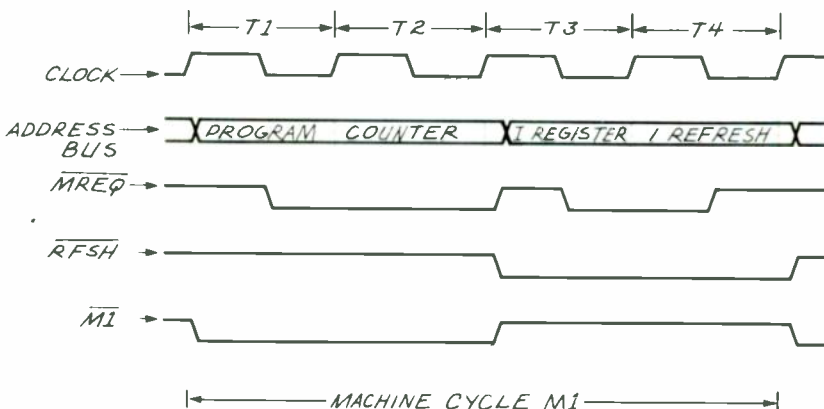


FIG. 2



**THE MOST POPULAR  
WIRE-WOUND CB ANTENNAS  
IN THE WORLD**

*Because...they perform!*

**FACT**

When CB was legalized in England, 'Firestik' antennas were barred from sale because the emitted signal was too strong. Fortunately, no other country including the U.S... limits antenna efficiency.

**YOU CAN HAVE SECOND  
BEST OR, 'Firestik'!**

Call or Write for **FREE** Catalog  
'Firestik' Antenna Company  
2614 East Adams  
Phoenix, Arizona 85034  
(602) 273-7151

**MILLIONS OF SATISFIED OWNERS**

CIRCLE 100 ON FREE INFORMATION CARD

You Can Be  
One Of The  
20,000 Technicians  
Certified BY ISCET



The International Society Of Certified Electronics Technicians offers permanent certification by administering the CET exam with the FCC recognized communications option for \$20. A second exam on FCC regulations for a \$10 fee is required for a Radiotelephone License. Upon passing, technicians receive both a permanent Radiotelephone Operator Certificate and a CET Certificate issued by ISCET.

**ISCET Offers License Renewal**

ISCET has developed a program for registration of those who currently hold a valid Radiotelephone Operator License. By sending a completed application, a photocopy of your FCC License, and \$10 your license will be renewed with the assurance of a recognized national technicians association behind it.

For More Information Contact:  
ISCET 2708 W. Berry, Ft. Worth, TX  
76109. (817) 921 - 9101

the Z80 executes requires from one to six machine cycles, M1-M6. During M1 the Z80 fetches the op-code of the next instruction. If the op-code is more than one byte long there will be more than one M1 cycle. In addition, it's during M1 that the Z80 handles refresh addressing. By the way, as shown in the figure, M2 and M3 are used for reads and writes.

Figure 2 is an expanded look at the M1 cycle. During T1 and T2, the Z80 places the contents of the program counter on the the address bus to get the next op-code. The microprocessor uses the next two T cycles, T3 and T4, to decode the op-code; it doesn't need the bus during that time. So, during T3 and T4, the address bus is divided in half to provide two kinds of data. The upper eight bits, A7-A15, have the contents of the I (index) register, and the lower seven bits, A0-A6, have the contents of the R, or refresh, register.

When the refresh address stabilizes, both  $\overline{MREQ}$  and  $\overline{RFSH}$  go low. That combination of signals is therefore a guaranteed-stable refresh address that can be used to systematically refresh dynamic memory.

In case you missed it, what the Z80 is doing for us is to eliminate the need for the external counters and logical glue that used to be necessary to ensure that dynamic memory would be refreshed at the right time and in the right order.

Now that you understand how much work the Z80 is ready to do for us, let's see what we have to do to take advantage of it.

**Putting it to work**

In using dynamic RAM with a Z80, the most important design task is to ensure that the memory is fast enough to work in the amount of time available for refresh. In our circuit we'll use a Z80B and run it at a maximum speed of 2.5 MHz, which translates into 400 nanoseconds ( $1/(2.5 \times 10^6)$ ) per T cycle, or 800 ns to complete one refresh. In fact, however, we can't count on having the full 800 nanoseconds. Some time is eaten by delays internal to the Z80; more is needed to allow for propagation delays in our support circuitry; and all dynamic RAM

needs a refresh "precharge" time. Keeping that in mind, let's see how much of the 800 nanoseconds we actually have for refresh.

Even though Fig. 2 is only a representation of actual timing, it's clear that there are delays associated with the memory-control signals generated by the Z80. It takes about three quarters of a T cycle for the Z80 to put the program counter on the address bus and then guarantee that the memory control signals ( $\overline{MREQ}$  and  $\overline{RD}$ ) are stable. And after the op-code appears on the data bus, we also must allow for settling time on the data bus.

Assuming the maximum clock speed of 2.5 MHz, we can expect to see the following timing for the whole op-code fetch cycle, (T1-T2):

$$\begin{aligned} T(\text{OP-CODE}) &= (T1 + T2) - T(\text{ADDRESS/SIGNAL}) - T(\text{DATA}) \\ &= 800 - 300 - 50 \\ &= 450 \text{ nanoseconds} \end{aligned}$$

The amount of time needed for a memory read is also an important consideration, but it is usually longer than the time needed for an op-code fetch. For our 2.5 MHz system, a memory read requires about 650 nanoseconds. Not only is that longer than an op-code fetch, but both numbers are well within the bounds of the modern 150-nanosecond (and faster) RAM.


The logic that we'll need to make our system work also has built-in delays. Each of the buffers and gates that comprise the circuit contributes to the total amount of time the circuit needs to operate. TTL and fast CMOS parts have very small propagation delays, but if you add enough of them together you can wind up with a circuit that is too slow. A worst-case analysis might look like this:

- 40 ns for memory buffer delays
- 40 ns for data buffer delays
- 30 ns for gating delays
- 40 ns for Z80 buffer delays

That's a total circuit-propagation delay of 150 ns.

Those figures are not exact, but if you look through a TTL or CMOS data book, you'll see that I've overestimated the maximum possible times by a large margin.

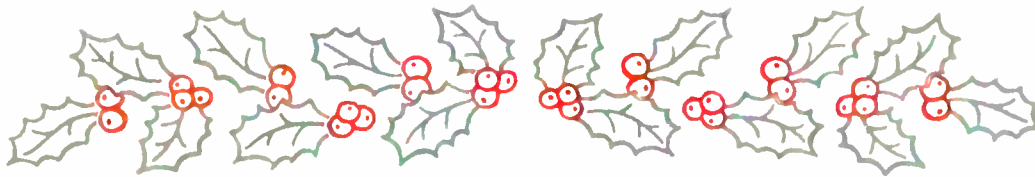Now that we have all the numbers worked out, we also have the maximum access time for the RAM



# Plug a Friend into Radio-Electronics this Christmas ... and Save \$12!

**This Christmas give an electrifying gift ... plug a friend into Radio-Electronics and brighten his whole new year! Whether electronics is his livelihood or his hobby, your gift will sharpen his focus and illuminate the whole spectrum of electronics throughout the coming year.**

Radio-Electronics will keep him informed and up-to-date with new ideas and innovations in all areas of electronic technology ... computers, video, radio, stereo, solid state technology, satellite TV, industrial and medical electronics, communications, robotics, and much, much more.

He'll get complete plans and printed circuit patterns for building valuable test equipment and electronic devices for home and car — practical money-savers like these ... a TV signal descrambler ... a video test generator ... an auto exhaust analyzer ... a clockboard for his PC ... a radio commercial zapper ... a solid state barometer ... a working robot ... and many others!


**PLUS ... equipment repair and troubleshooting ... circuit design ... new**

product news and buyer's guides ... service clinics ... equipment test reports ... a special "Computer Digest" section ... regular columns on video, stereo, radio, circuits, solid state, satellite TV and robotics ... and lots more exciting features and articles.

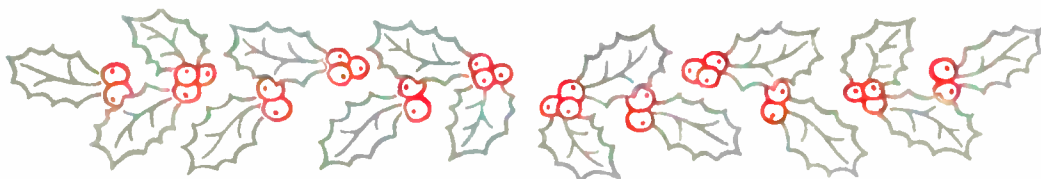**SAVE \$12 ... OR EVEN \$24 ... For each gift of Radio-Electronics you give this Christmas, you save a full \$12.00 off the newsstand price. And as an R-E gift donor, you're entitled to start or extend your own subscription at the same Special Holiday Gift Rate — you save an additional \$12.00!**

No need to send money ... if you prefer, we'll hold the bill till January, 1988. But you must rush the attached Gift Certificate to us to allow time to process your order and send a handsome gift announcement card, signed with your name, in time for Christmas.

So do it now ... take just a moment to fill in the names of a friend or two and mail the Gift Certificate to us in its attached, postage-paid reply envelope. That's all it takes to plug your friends into a whole year of exciting projects and new ideas in Radio-Electronics!



# Radio-Electronics mini-ADS

we'll need. You don't need a lot of equipment to see that even if we used some slow 250-nanosecond RAM, the total circuit delay time would only be 400 (150 plus 250) ns. Most mail-order houses don't even stock 250-ns parts. The bottom line is that by using 150-ns RAM we can eliminate all the potential problems that would be caused by timing restrictions.

## System design

There are a couple of things to keep in mind when using a Z80 to control a RAM system. All of them come from one general principle: *If the Z80 stops running, all our memory data will be history.*

That principle is of critical importance and it's also really easy to forget. As long as the Z80 is executing instructions it will continue putting out new refresh addresses during each M1 cycle. However, anything that puts the Z80 to sleep will also trash the memory. Fortunately, there are only a few circumstances in which that can happen:

- A reset pulse longer than 1 millisecond.
- A wait state longer than 1 millisecond.
- A DMA operation longer than 1 millisecond.

In our system, all memory access will be done through the Z80, we don't have to worry about the last two on the list. DMA simply won't be used in our system; any external request to store or retrieve data will be done by loading latches and then asking the Z80 to perform a read or a write. Similarly, we simply don't have any wait states.

Any slow I/O device using our memory system will talk to buffers and latches, not directly to memory. Some memory systems (like that of the IBM PC) must place wait states into every memory request because there isn't enough time for the "precharge time" required by the dynamic RAM. As we've seen from the mathematical analysis above, we surely don't have that problem.

Next month we'll start building the circuit. If you haven't done so already, you should get good data sheets on the Z80 and dynamic RAM. R-E



**THE MODEL WTT-20 IS ONLY THE SIZE OF A DIME**, yet transmits both sides of a telephone conversation to any FM radio with crystal clarity. Telephone line powered - never needs a battery! Up to ¼ mile range. Adjustable from 70-130 MHZ. Complete kit \$29.95 + \$1.50 S + H. Free Shipping on 2 or more! COD add \$4. Call or send VISA, MC, MO. **DECO INDUSTRIES, Box 607, Bedford Hills, NY 10507. (914) 232-3878.**

CIRCLE 127 ON FREE INFORMATION CARD




**ZENITH SSAV1 from \$169, UHF INPUT**, reconditioned. Level II modules available for SSAV1s. UHF SSAV1 project handbook \$6.50 ppd. Sylvania 4040 \$169. Z-TAC, N-12, MLD-1200s. Converters, amplifiers and accessories. Satellite components. Radar speed guns for car/boat racing, bowling, skiing; baseball, etc. from \$275 used. Professional police models. IBM-compatible computer systems from \$895. Catalog \$1. **AIS SATELLITE, INC., P.O. Box 126-E, Dublin, PA 18917. (215) 249-9411.**

CIRCLE 81 ON FREE INFORMATION CARD



**TOOLS & TEST EQUIPMENT.** Contact East's latest catalog contains many new and innovative products for testing, repairing, and assembling electronic equipment. A full selection of test instruments, precision hand tools, tool kits, and soldering supplies are just some of the products featured. Products are shown in full color with detailed descriptions, pricing and a 100% satisfaction guarantee. **CONTACT EAST, P.O. Box 786, No. Andover, MA 01845. Call (800)-225-5370**

CIRCLE 55 ON FREE INFORMATION CARD

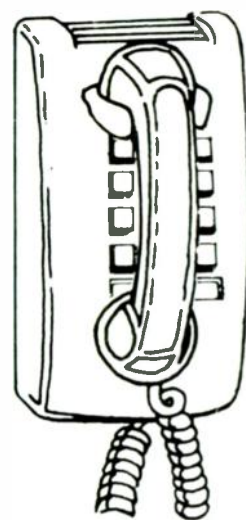

## CALL NOW AND RESERVE YOUR SPACE

- 6 x rate \$745.00 per each insertion.
- Reaches 245,824 readers.
- Fast reader service cycle.
- Short lead time for the placement of ads.


Call **516-293-3000** to reserve space. Ask for Arline Fishman. Limited number of pages available. Mail materials to: Computer Admart, **RADIO-ELECTRONICS, 500-B Br-County Blvd., Farmingdale, NY 11735.**



**DECODE NEARLY ANY SINGLE LEVEL GATED PULSE SIGNAL.** New circuit works with Hamlin, Jerrold, Sylvania, and Eagle systems. Decodes In-band, Out-band, AM or FM reference. Complete educational kit including P.C. board, parts, case, and 40 page gated pulse theory booklet is only \$47.00 plus \$3.00 shipping. Order no. 1PFD-1K. **ELEPHANT ELECTRONICS INC. P.O. Box 41865-R, Phoenix, AZ 85080. (602) 581-1973**


CIRCLE 120 ON FREE INFORMATION CARD

# Radio-Electronics mini-ADS

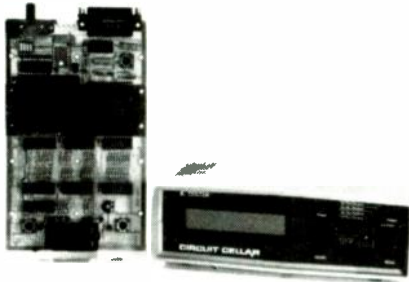


**BUILD STEVE CIARCIA'S NEW SUPER IC TESTER** Tests over six hundred 7400-series TTL, L, S, H, C, HC, HCT, F, AS, and ALS devices, 4000-series CMOS and PALs. Identifies unmarked chips and bad IC pins. User definable test sequence and user expandable ROM library. Tester operates standalone with LCD display, or with IBM PC or terminal. Partial kit—\$99. Full board kit—\$179. CCI, 4 Park St., Suite 12, Vernon, CT 06066. (203) 875-2751.

CIRCLE 52 ON FREE INFORMATION CARD

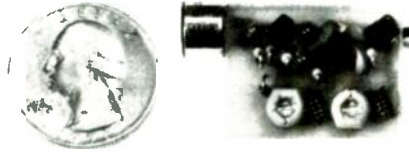


**SIMPLY SNAP THE WAT-50 MINIATURE FM TRANSMITTER** on top of a 9v battery and hear every sound in an entire house up to 1 mile away! Adjustable from 70-130 MHz. Use with any FM radio. Complete kit \$29.95 + \$1.50 S + H. Free shipping on 2 or more! COD add \$4. Call or send VISA, MC, MO. DECO INDUSTRIES, Box 607, Bedford Hills, NY 10507. (914) 232-3878.

CIRCLE 127 ON FREE INFORMATION CARD

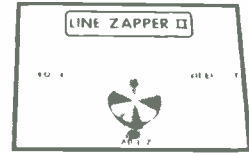

**CHRISTMAS SALE** on the Line Zapper II. During Nov. and Dec. only, the complete KIT (not recommended for the beginner) is only \$49.95 and the fully assembled unit is only \$89.95 (add \$3.00 ea. postage). Decode the Marco-Mess and start watching recent video tape movie releases without the flashing, jumping jittering and video noise. **ELEPHANT ELECTRONICS INC.**, P.O. Box 41865, Phoenix, AZ 85080 (602) 581-1973

CIRCLE 180 ON FREE INFORMATION CARD

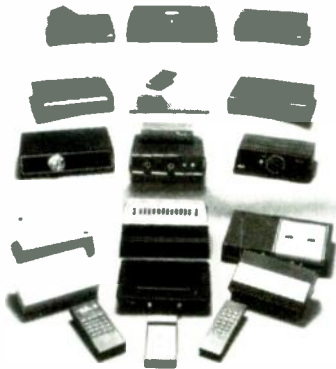

**CABLE TV CONVERTERS AND DE-SCRAMBLERS.** Large selection of top quality merchandise. Low prices. Quantity discounts. We ship COD. Most orders are shipped within 24 hrs. Send \$2.00 for catalog. **CABLETRONICS UNLIMITED**, P.O. Box 266 Dept. R, S. Weymouth, MA 02190 (617) 843-5191

CIRCLE 188 ON FREE INFORMATION CARD

## CALL NOW AND RESERVE YOUR SPACE


- 6 - rate \$745.00 per each insertion
- Reaches 245,824 readers.
- Fast reader service cycle.
- Short lead time for the placement of ads.

Call 516-293-3000 to reserve space Ask for Arline Fishman. Limited number of pages available. Mail materials to: Computer Admart, RADIO-ELECTRONICS, 500-B Bi-County Blvd., Farmingdale, NY 11735.



**FREE 24 PAGE OCTE CATALOG!** Cable TV converters, hand controls, stereo decoders and switching centers. Negative cable TV traps and noise filters. Descrambler books, schematics and parts. SCA books and kits. Nite viewers. Microwave downconverters. Telephone privacy assurance devices and automatic conversation recorders. Bug and tap detectors. Parabolic microphones. Power supplies. Surplus electronics parts. **OCTE ELECTRONICS**, Box 276, Alburg, VT 05440. (514) 739-9328.

CIRCLE 80 ON FREE INFORMATION CARD

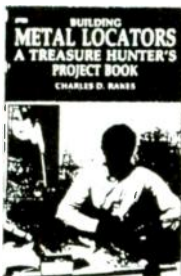


**2706T—BUILDING METAL LOCATORS, A Treasure Hunter's Projects Book.....\$9.95.** Build your own high-quality metal detector for a fraction of the factory-built cost! The detectors described in this unique project guide will locate anything from coins and jewelry to gold and silver—and can be built quickly and easily! From TAB Books. Get your copy today. Send \$9.95 plus \$1.75 shipping to Electronic Technology Today Inc., P.O. Box 240, Massapequa Park, NY 11762-0240.



**PANASONIC CABLE CONVERTERS.** Wholesale and Retail. Scientific Atlanta and Pioneer Cable Converters in stock. Panasonic model 130N 68 channel converter \$79.95, Panasonic Amplified Videc Control Switch Model VCS-1 \$59.95. Scientific Atlanta Brand new Model #8528 550MHZ 80 Channels Converter \$89.95. Video Corrector (MACRO, CCPYGUARD, DIGITAL) ENHANCER \$89.95. We ship to Puerto Rico, Caribbean countries, & So. Amer. Write or call **BLUE STAR IND.**, 4712 AVE. N, Dept 105, Brooklyn, NY 11234. Phone (718) 258-9495.

CIRCLE 85 ON FREE INFORMATION CARD

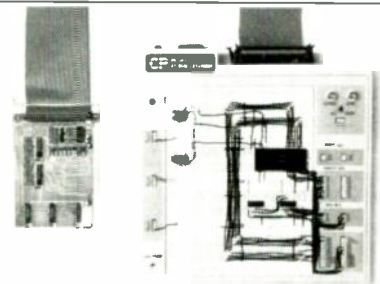

**PC-601 XT BUS EXTENDER BREADBOARD LAB** connects to any IBM PC compatible computer and extends all PC electrical bus connections out to the PC-601 for easy circuit prototype connection, testing and troubleshooting. Includes large 3060 tie-point breadboard. • 5V and • 12Vdc AC line powered power supplies. Includes buffer card, 2' ribbon cable & 1-Year warranty. Price: \$369.95 **CHENESKO PRODUCTS**, 21 Maple St., Centereach, NY 11720. 516-736-7977, Fax: 516-732-4650

CIRCLE 193 ON FREE INFORMATION CARD

## XMAS TREE

*continued from page 48*

### Construction

The PC board can be made photographically using the foil pattern shown in PC Service, or the pattern can be used as a guide for applying liquid and tape resist by hand. Although the foil pattern itself is only 5-inches high, the PC board material must be 6¼ inches high because the tree's 1¼-inch trunk is part of the PC board. Since etching large copper areas not only takes excessive time but also shortens the life of the etchant, we suggest you trim away the unwanted PC board material before you etch the board. Or, if you prefer to cut the tree to size after the pattern is etched, protect the foil of the large unused trunk area with resist and simply let the copper remain. As long as the trunk's foil doesn't come in contact with any of the circuit traces it makes no difference whether it's there or not.

If you want to decorate the front of the tree, do it before the holes for the components are drilled. For example, the author sprayed the component side with a bright automotive metallic-green paint. To prevent a defined line, a cardboard mask was held about ½ inch above the board. Then, the edge of the PC board was "dusted" with a fine mist of white paint to simulate snow. After allowing for adequate drying, again using a cardboard mask, the trunk portion of the board was painted with a metallic-brown paint.

Allow the decorative paint to dry overnight before drilling the component mounting holes. Then install and solder the eight jumpers, the resistors, the IC's, and the capacitors. Then insert all the LED's, observing the polarities shown in Fig. 2. Position the LED's so that they are raised approximately ½ inch off the board. To do that, turn the board over and lay it down on a flat surface, being careful not to allow any LED's to fall out; that can be done easily by holding a piece of stiff cardboard against the LED's while turning the board over. Keeping the board parallel to your work surface, solder one lead of each LED. Turn the board over and carefully look across the surface to see whether the LED's are straight and at the same height. If not, correct as needed. When you're satisfied with their alignment, solder the other lead of each LED.

### Adding the base

Prepare the surfaces of the battery holders and the PC board for gluing by sanding the back of each holder and a ⅜-inch strip on both sides of the circuit board at the bottom of the trunk. Mix a small amount of a 5-minute epoxy and apply some to the ⅜-inch strip on both sides of the circuit board. With the battery polarities opposite

each other, sandwich the PC board between the holders. Hold the assembly firmly on a flat surface that's covered with a piece of wax paper. You will have a few minutes working time before the epoxy sets to ensure proper alignment. Make certain that the holders are even and that the circuit board is centered and upright between the holders. In about 5 minutes the glue will have set up sufficiently, and the tree can be lifted from the wax paper. Use acetone or flux remover to clean excess glue from the bottom of the battery holders. As with most other cleaners, be careful not to touch the painted surface.

After allowing at least one hour for the epoxy to cure, solder a jumper wire at one end of the battery holders, across the adjacent positive and negative terminal lugs. From the battery source ends, solder the positive and negative leads directly to the foil traces—as shown in Fig. 2. The LED's will start to flash as soon as the batteries are installed. Any LED that fails is most likely defective, or installed with reversed polarity.

When you're certain the project is working, you can add a final "dress up" by gluing a colorful felt material over foil traces on the back of the board. **R-E**

## ANALYZE WAVEFORM

*continued from page 60*

thinking about them, but you do go through them.

A properly designed digital readout reduces each measurement to simply pushing a button and reading a number, including the correct decimal placement and the range multiplier. Since the tests are so much easier to do, you will probably analyze waveforms more often, instead of using less effective troubleshooting methods.

**Accuracy:** Digital readings provide much higher accuracy than a CRT. Most people don't think much about the accuracy of a reading, but errors can add up quickly when using a standard oscilloscope. First, no scope reading can be more accurate than the calibration of the vertical and horizontal circuits. Published accuracies range from 2% to 5%, but only if the scope has been recalibrated within the past few months. If not, the circuit errors may be higher.

Next, consider the errors in determining the displacement of the trace on the CRT. A typical CRT trace has 8 major vertical divisions, each divided into 5 minor divisions. If a waveform is 4 major divisions tall (one-half the screen height), it covers a total of 20 minor divisions. Since the width of the trace is about 1 minor division, the trace thickness adds an extra 5% error to the calibration uncertainty. When we add interpolation and

**TABLE 1**  
**Peak-to-peak volts**

1. Turn vertical vernier to CAL.
2. Lock waveform and adjust horizontal circuits until desired number of waveforms appear.
3. Adjust VOLTS/DIVISION control until waveform is 2 to 4 divisions tall.
4. Adjust VERT POSITION control until the bottom of waveform sits on a horizontal graticule line.
5. Adjust HORIZ POSITION control until tallest portion of waveform is on center CRT graticule.
6. Count divisions between bottom and top of waveform.
7. Multiply number of divisions times VOLTS/DIVISION setting.
8. Multiply times 10 if a  $\times 10$  probe is used and input is calibrated for direct readings.

### DC volts

1. Set vertical vernier to CAL.
2. Lock waveform and adjust horizontal circuits until desired number of waveforms appear.
3. Adjust VOLTS/DIVISION setting until waveform is 2 to 4 divisions tall.
4. Set INPUT COUPLING switch to ground.
5. Adjust VERT POSITION control until line is on a horizontal graticule line.
6. Move INPUT COUPLING switch to the DC position.
7. Readjust VOLTS/DIVISION switch if has trace moved off screen.
8. Estimate vertical midpoint of waveform.
9. Count number of divisions from reference in step 5 to midpoint of step 8.
10. Multiply number of divisions by the VOLTS/DIVISION setting.
11. Multiply by 10 if a  $\times 10$  probe is used and input is calibrated for direct readings.

### Time or frequency

1. Turn horizontal vernier to CAL.
2. Lock waveform and adjust horizontal circuits until desired number of waveforms appear.
3. Adjust the HORIZ POSITION control until left edge of signal touches a vertical graticule line.
4. Adjust VERT POSITION control until right edge of signal crosses center CRT graticule.
5. Count number of divisions between left and right edge of waveform.
6. Multiply number of divisions by the setting of the TIMEBASE-FREQ switch.
7. Divide by 10 if the horizontal  $\times 10$  expander is on.
8. For frequency, invert results.

parallax errors, a scope reading will only be accurate to within 10% to 20%.

Digital scope readouts offer a much higher degree of accuracy. For instance, the peak-to-peak voltage function of the Sencore SC61 is accurate to 2%. The accuracy improvements are even greater for frequency measurements; that is because

*continued on page 84*

## STRAIN GAGE

continued from page 63

resistance change, any difference in temperature between the strain gage and the other resistors could look like a legitimate output. But when four strain gages are used, and all are mounted on the spring element, they all see the same temperature variations. Then they will all increase or decrease by the same amount, thereby preserving the bridge balance and producing no output.

### Putting it together

We are now in a position to say that the bridge output voltage is directly proportional to the force applied to the spring element. To find out what that relationship looks like all we have to do is combine equations 1, 3, and 9. Reviewing what we've learned so far:

$$e_o = E(r/R), r = (GS)R, \text{ and } S = kF$$

By substituting  $kF$  for  $S$  in the gage-factor equation and then substituting  $(GkF)R$  for  $r$  in the bridge equation we find that:

$$e_o = (EGk)F \quad (10)$$

You may recognize that as the equation of a straight line that passes through the

origin. The applied force,  $F$ , is the independent variable and the bridge output voltage,  $e_o$ , is the dependent variable. The slope of the line is represented by the three constants,  $E$ ,  $G$ , and  $k$ . They are shown in parentheses because once the transducer has been assembled and supplied with a suitable operating voltage, they can be treated as a single constant. The slope of the line is also known as the sensitivity of the transducer. We must know the sensitivity of the transducer in order to determine the applied force. We can make that conversion simply by dividing the output voltage by the sensitivity.

Strain-gage transducers can be purchased with or without built-in amplification. The transducer's sensitivity is specified a little differently in each case. First of all, a transducer with built-in electronics is usually provided a fixed bridge-supply voltage and enough gain to bring the maximum output up to some standard level. Adding that additional gain to equation 10 will result in:

$$e_o = (AEGk)F \quad (11)$$

where  $A$  is the gain of the built-in amplifier. Since the gain and the bridge supply voltage, as well as the gage factor and spring constant, are all fixed at the time of assembly, they can all be combined into one constant as the transducer sensitivity.

But, rather than specifying transducer sensitivity outright, transducer manufacturers often list the maximum value of the input force and the corresponding maximum output-voltage level. Both of those specifications are important in themselves, and the sensitivity is implied in the two numbers. Since equation 10 defines a line that passes through the origin, all we have to do is divide the full-scale output voltage by the full-scale input force to determine the sensitivity. A typical value for the maximum output might be 5 volts. If the maximum input force is 500 pounds, then the sensitivity of the transducer would be 5-volts/500 psi = 0.01-volts/psi.

If the transducer does not have built-in electronics, it is up to the user to provide the bridge supply voltage and whatever gain may be required. Since the output voltage is a linear function of both the applied force and the bridge supply voltage, sensitivity is then specified as output volts per bridge supply volts per input force. The maximum output voltage corresponding to a maximum input is listed for a bridge supply of one volt. That way we can determine what the maximum output voltage will be when some other value of supply voltage is used by simply multiplying the listed maximum by the supply voltage actually used. R-E

## HITACHI COMPACT SERIES OSCILLOSCOPES



V-1065 DC to 100MHz With Cursor Readout  
**\$1595. Save \$200!**

- 6" CRT with Internal Graticule
- Dual Channel X-Y Display
- Sweep Time Autoranging
- 400V High Input Voltage Protection
- TV Sync Trigger Circuit
- Delayed Sweep • CRT Readout
- Single Sweep • ±3% Accuracy
- Trigger Lock • Bandwidth Limiter

V-1060 DC to 100MHz  
**\$1345. Save \$150!**

V-665 DC to 60MHz

**\$1145. Save \$150!**

V-660 DC to 60MHz

**\$970. Save \$125!**

**Instant Hard Copy!!  
From Oscilloscopes**

**POLAROID®  
DS-34  
CAMERA**



**Save \$135! \$290.**

- 5", 6" and 7" Hoods (Available separately @ \$51 ea. Please Specify size)
- Pistol Grip For Ease of Operation
- Works on Any Make of Oscilloscope
- Three Full Year Warranty

### Dual Channel 6" CRT Scopes

V-425 DC to 40MHz, CRT Readout  
**\$845. Save \$150!**

V-423 DC to 40MHz, Single Time Base Delayed Sweep

**\$745. Save \$250!**

V-422 DC to 40MHz, DC Offset

**\$795. Save \$130!**

V-225 DC to 20MHz, CRT Readout

**\$720. Save \$75!**

V-223 DC to 20MHz, Delayed Sweep

**\$695. Save \$100!**

V-222 DC to 20MHz, DC Offset

**\$515. Save \$200!**

V-212 DC to 20MHz

**\$440. Save \$175!**

### Dual Channel Mini-Portable Scopes

V-509 DC to 50MHz, Delayed Sweep

**\$1195. Save \$250!**

V-209 DC to 20MHz

**\$822. Save \$175!**

### Quad Channel Multi-Function Scopes

V-1150 DC to 150MHz, Delayed Sweep

**\$2650. Save \$300!**

V-1100AU DC to 100MHz, Delayed Sweep

**\$2240. Save \$250!**

### Digital Storage Scope

V-6020 1MHz Sampling, Dual Channels

**\$1750. Save \$200!**

### NTSC Waveform Monitors

V-079 6" CRT

**\$1625. Save \$125!**

V-099 3.5" CRT

**\$950. Save \$300!**

### NTSC Vector Scopes

V-069 6" CRT

**\$1825. Save \$125!**

V-089 3.5" CRT

**\$1284. Save \$400!**

**PROBES INCLUDED WITH ALL HITACHI  
SCOPES AT-NO EXTRA CHARGE!**



**WM. B. ALLEN  
SUPPLY COMPANY**

**ALLEN SQUARE**

300 Block North

Rampart Street

New Orleans

Louisiana 70112

TOLL FREE 800 535-9593 • LA 800 462-9520

NEW ORLEANS 504 525-8222 • FAX 504 525-6361

• American Express • Visa • MasterCard •  
928 pg Catalog FREE with your order

## R-E ROBOT

continued from page 68

ously throughout a full 360° rotation of the head. Under low-light conditions the output of the eye will be a low frequency. If the eye is operating at 1 Hz and light readings are taken every 5°, it will take over a minute to rotate the head. Obviously, then, the higher the frequency output of the eye, the better. We can always divide the frequency down to get it in a range that the RPC will be able to process effectively; however, we cannot multiply a low-frequency input to obtain information faster.

The active integrator used in the circuit is based on a simple, classic design. The photodiode's output current is used to charge a capacitor; the charging time, of course, is the integral of the input voltage. A novel twist, however, is that we will use the photodiode to both charge and discharge the capacitor. A newly developed IC from Linear Technology Corporation, the LTC1043, will be used to switch the photodiode from a current-sourcing to a current-sinking configuration. That IC is also used to convert the output of the integrator to a frequency signal for input to the robot's RPC.

The integrator is built around op-amp IC1, a Linear Technology LT1022. That op-amp is chosen for its high-speed operation, modest input-bias current, and low cost. Other operational amplifiers can be substituted, but be aware that any increased input-bias current will degrade the low-light performance, and decreased output slew-rate will degrade high-light-level performance.

### Construction

The PC-board's design is somewhat different in that all of the components except J1 are mounted on the *foil side* of the board; the PC pattern can be found in PC Service, and the parts-placement diagram is shown in Fig. 3. The components are mounted in that way so that the PC board can be used as one side of a light-tight structure supporting the Fresnel lens as shown in Fig. 4. Placing the traces on the inside of the box protects them somewhat from contamination; over time, that contamination can build up on the circuitry and affect performance. The completed board can also be covered with a conformal coating (that's a coating that closely conforms to the surface that it is applied to) or potted to minimize any contamination problems.

The printed circuit board is 2.3 inches by 2.3 inches. Those are the same dimensions as the Fresnel lens available from the supplier mentioned in the Parts List. Use screws or standoffs to mount the lens 1.3 inches from the photodiode. That is the

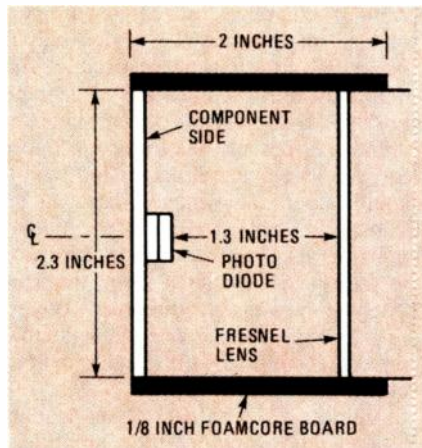


FIG. 3—ALL OF THE COMPONENTS, except J1, mount on the foil side of the PC board.

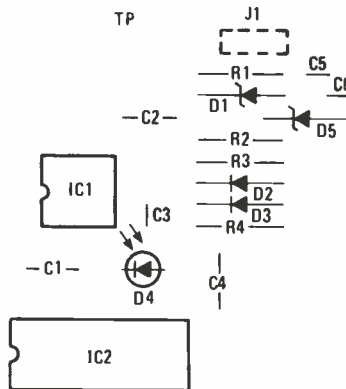


FIG. 4—A FRESNEL LENS is used to concentrate the light on the photodiode.

focal distance of the lens and will result in maximum light gathering power. To fine-focus the lens, attach an oscilloscope to the photodiode and, with the eye pointed towards a light source located several feet away, adjust the lens supports for maximum frequency output. If you find that your eye saturates too quickly, you can simply defocus the lens slightly to reduce the light level that reaches the photodiode.

After the lens has been focused, cut and mount the remaining sides of the box. Cardboard or a similar material is suitable for that; the author used Foamcore board, which is available at art supply stores. Hot-melt glue is a handy means of attaching the sides.

Paint the cardboard sides black to reduce the amount of light entering the eye except through the lens. That won't do much to stop infrared light, however. If interference due to infrared noise becomes a problem, laminate a layer of aluminum foil to the sides.

### Next time

That completes the eye's construction. Now it's time to hook it up and test it. Unfortunately, at the moment there's nothing to hook it up to. That shortcoming will be taken care of next time when we show you the robot's rotating head. R-E

## ANALYZE WAVEFORM

continued from page 82

a 0.001%-accurate frequency counter replaces the 10 to 20% errors associated with CRT-based frequency measurements.

**Freedom from errors:** The third difference may have even more impact than the first two. That's because an error in counting or multiplication—or forgetting to set the horizontal or vertical vernier to the CAL position—may lead you down a completely wrong path.

What is worse is that you won't realize that you've made the error until some time later when you re-test a signal. A direct-reading digital readout prevents that because it gives accurate results independently of display settings.

Other problems can happen, too. The verniers can be out of their calibrated position; the signal can be off of the CRT; or the triggering circuits can even be out of sync. But none of those problems will affect the digital readings.

Digital readings make it easier to use waveform analysis for more and more of your troubleshooting. You can lock the waveform onto the CRT when you want to fully analyze all seven parameters of complex waveforms. When making general tests, however, you don't even need to adjust the CRT circuits, if DC voltage, peak-to-peak voltage, or frequency readings are enough to tell you whether the circuits are operating correctly. Such general testing can speed your circuit analysis even more. And, what service technician or engineer could possibly argue with that?

R-E



"Next year we get a computer."



# COMPUTER DIGEST

VOL. 4 NO. 12 DEC. 1987

A NEW KIND OF MAGAZINE FOR ELECTRONICS PROFESSIONALS

## FLOPPY DISKS

Bits, bytes, and copy protection

## 68000 COMPUTING

The big moment

```
2DA3:0108 EB 35 54 6F 74 61 6C 28-6D 65 6D 6F 72 79 3A 28 15Total memory 65536
2DA3:0110 38 38 38 28 48 42 28 28-28 28 4D 65 6D 6F 72 79 800 KB Mem@28C0
2DA3:0120 28 61 76 61 69 6C 61 62-6C 65 3A 28 38 38 28 available: 00
2DA3:0130 48 42 24 00 00 00 00 EB-17 08 A1 33 01 BF 18 01 KB@.....13.7
NOT SAMPLE
AX=0000 CX=0000 DX=0000 SP=FFFF BP=0000 SI=0000 DI=0000
DS=2DA3 ES=2DA3 SS=2DA3 CS=2DA3 IP=0108 FL=0246 MV UP EI PL ZR NA PE M
X1
SAMPLE:
2DA3:0108 EB05 JMP START
TOTAL:
2DA3:0102 54 PUSH SP
2DA3:0103 6F OUTSW
2DA3:0104 7461 JZ CONVERT
2DA3:0106 6C INSB
2DA3:0107 286D65 AND [DI+65],CX
UT-- In C:\PERIN\ROM.COM
Y*
```

The commands are: Assemble (A AJ), Breakpoint (BA BB BC BI BL BP BR BU BV  
BX), Compare (C), Display (DA DB DD DE DI DL DM DR DS DW DZ), Enter (E EA ES),  
Fill (F), Go (G G= GA GM GT), Hex (H), In (I IR IS), Jump (J JL), Klear (K KJ),  
Load (LA LF LS), Move (M), Name (N), Out (O), Quit (Q), Register (R RR RS),  
Search (S SA SC SD SR SU), Trace (T TB TR TU) Unassemble (U UA UB US), View (V  
VS), Write (WA WF WS), Xlate (XA XD XH), Options (O OE ON OS OT OU OV OX)

## DEBUGGING TOOLS


Hands-on report

```
Line-Stat B29-1 File:memory TURBOsmith Source Code
1: 0:
while true do begin
  i := i + 1;
  writeln(i);
  a;
end;
Machine Code
AX=0000 SP=FFFF DS=2DA3
CX=2E77 SI=2D9C ES=FFFF
DX=0000 DI=2D9C IP=2E30
AZ NC MC MV UP NA PE EI
77F5:2E30 B00000 MOV AX,0000h
77F5:2E40 A30002 MOV [02A0h],AX
77F5:2E43 B90100 MOV AX,0001h
77F5:2E46 B0C3 OR AX,AX
77F5:2E48 7503 JNE 2E4Bh
77F5:2E4A B72000 JMP 2E75h
77F5:2E4D A16002 MOV AX,[0258h]
Level Program [Main] Variable View
Memory: Integer?? (Special System Parameter) 0000h
BufLen: Byte 126
: Integer 0
```

```
10 end;
11 h;
12 writeln;
13 end;
begin
14 i := 0;
while true do begin
15 i := i + 1;
16 writeln(i);
17 a;
18 end;
19 end;
20 end;
Source: Memory T-DebugPLUS 2.00
SACRS:SomeA 10 0F0E 100E1F0E 10 0E 0 0 0 0 0 0 0 0
SACRS:SomeA 0' 0021h 0 1 0101 P1 00,EE-4Copyright (C) 1985 BORLAND In.
-> Memory
watch variables are removed.
VD [(parameter)] - Redraw/resize windows. (parameter) is now row for
the Window Divider. Default setting is row 14.
X [(parameter)] - Translate. If (parameter) is a symbol or statement number,
returns an address; if a hexadecimal offset, returns a statement number.
* 4a cs:0100
*
```



# EDITOR'S WORK- BENCH

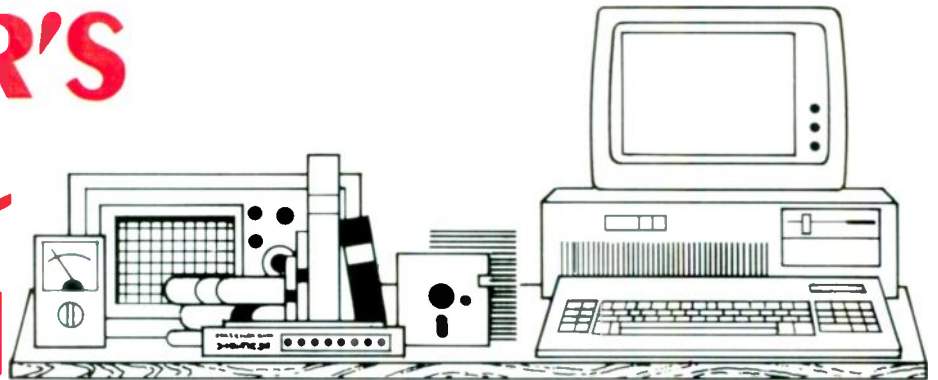

## Periscope

**D**ebug is the standard MS-DOS machine-language debugger. It is included with every copy of DOS, so every programmer, hacker, and hobbyist is familiar with it. Debug is useful for tracing and analyzing both software you write yourself, and software written by others. And with care you can even use it to create short programs without the aid of an external assembler.

However, you don't have to use the program for very long to realize that it has limitations, the most severe of which are limited breakpoint facilities, lack of windowing, and lack of support for the symbols generated by the assembler or compiler you use to generate object code.

Attempting to remedy those deficiencies, the Periscope Company sells a line of high-quality debugging tools with varying capabilities. The latest incarnation includes an expansion card that allows you to trap bus events in real time, thereby providing many of the capabilities of a development system for about 10% of the cost.

Actually, there are four models of Periscope, which differ mainly in the hardware included.

- Periscope I (\$345) includes a memory board with 56K of write-protected memory and a break-out switch. The memory is installed outside of the 640K DOS limit (usually in segment D000 or E000), the Periscope software runs from that memory. Pressing the break-out switch at any time—even when the system is apparently locked-up—generates a hardware interrupt that activates the Periscope software.

- Periscope II (\$175) includes just the break-out switch; the software runs from normal DOS memory, so it may be overwritten by a run-away program. In that case you may not be able to regain control of a hung system. The break-out switch does not require an expansion slot; a small finger slips in an in-use slot between the expansion card and the connector's own finger.

- Periscope II-X (\$145) includes just the software and no hardware. You may use your own break-out switch or a keyboard hot-key to activate the software.

- Periscope III (\$995) is a full-length expansion card (shown in Fig. 1) that includes 64K of write-protected memory, a break-out switch, and additional circuitry that continuously monitors the expansion bus and allows you to create breakpoints that are activated when memory locations, I/O ports, or microprocessor registers attain certain values. A small module must be inserted into your motherboard's 8087 (or 80287) socket.



FIG. 1—The Periscope board.

The software functions pretty much the same for all versions, given the hardware differences. In fact, the same software is included with all versions; during the installation you must specify your hardware configuration.

### How to use it

The Periscope software comes in two parts: PS.EXE, the 50K debugger, and RUN.COM, a 7K program that loads and runs your software. First you run PS, which lies dormant in memory until you run a program. When you do, the Periscope screen comes up, a register dump is displayed, and the first instruction is disassembled. You can then execute your program in various ways.

To ease the learning process, Periscope duplicates many Debug commands, so you can Trace a single instruction or a group thereof, or Go, starting at an address you

specify, with breakpoints at addresses you specify. In addition, you can Dump memory in the standard Debug format, Read and Write files and disk sectors, Unassemble, Examine, Search, and Fill memory, etc.

Normally, all output scrolls up the screen in standard fashion. However, you can open windows (see this month's cover for an example) that maintain information in fixed places on the screen, thereby making that information much easier to find and assimilate. Window size and color is easily specified, windows may contain registers, memory dumps (in several formats), disassembled instructions, stack dump, and a text file dump. Pressing Ctrl-F9 or Ctrl-F10 brings up default windows for mono and color windows, respectively.

The disassembly will contain the symbols and high-level instructions of your program, if an appropriate .MAP file is available. (Most assemblers and linkers can generate such a file.) For example, the program shown in Fig. 2 is written in Turbo Pascal; a utility sold by Turbo Power created the required .MAP file. Note that both Turbo source lines and the generated object code are shown. See this month's software reviews for more information.

You can add your own labels to programs and save them separately. That capability is useful when disassembling third-party software.

### Breakpoints and program tracing

You can set an almost bewildering variety of breakpoints with Periscope. BC sets a Code Breakpoint, activated when your program tries to execute code at the specified address. That address may be specified using Hex notation or symbolically. BI sets an Interrupt Breakpoint, activated when a software interrupt is executed. For example, to stop execution any time a DOS function (interrupt 21h) was to be executed, you'd type

BI 21

You can also set breakpoints on source-

```

29A9:0100 E9 79 2C 90 90 CD AD 43-6F 70 79 72 69 67 68 74 19.. P+Copyright
29A9:0110 20 20 43 29 20 31 39 38-35 20 42 4F 52 4C 41 4E (C) 1985 BOBLAN
29A9:0120 44 20 49 6E 63 02 04 00-B1 57 00 3C 33 00 00 00 D Inc 1W (3...
29A9:0130 00 00 00 00 00 00 00 00-00 00 00 00 00 00 00
DBT
AX=0000 BX=0000 CX=2D7F DX=0000 SP=FFFF BP=0000 SI=0000 DI=0000
DS=29A9 ES=29A9 SS=29A9 CS=29A9 IP=2D7C FL=0246 NU UP EI PL ZR NA PE MC
R1-- WR SS:FFFF = 1787
A1: var i : integer.
29A9:2D7C E857DD CALL 0AD6
29A9:2D7F 06 PUSH ES
29A9:2D80 00773D ADD [BX+3D],DH
29A9:2D83 37 AAA
29A9:2D84 47 INC DI
29A9:2D85 E0227 CALL 548A
29A9:2D88 0000 ADD [BX+SI],AL
UF-- In C:\PERI\RUN.COM
>t
Source file for module A ? \pascal\test.pas

```

FIG. 2—The Periscope debugging screen.

code line numbers (BL), memory addresses (BM), I/O port addresses (BP), registers (BR), user-specified conditions (BU), memory contents (BW), and subroutine exit (BX). Note that those are not hardware-activated breakpoints, so execution must be started via the GT command, in which machine instructions are executed one at a time, breakpoint settings are examined, and then control reverts either to Periscope or to the user program, depending on whether the breakpoint conditions were met.

Each of the breakpoint commands may be cleared by entering the command with an asterisk. In addition, breakpoints of a particular type may be enabled (by typing +), disabled (by typing -), or displayed (by typing ?).

### Hardware control

All of the commands discussed thus far may be used on any version of Periscope. Periscope III enables an additional set of breakpoint, trace, and display commands that let you execute your program in real time until a specified condition is met. The HB command, for example, sets a breakpoint when a specific bit pattern appears on the data bus. Values of 0, 1, and X (don't care) are legal. You can also trap memory and port reads or writes (or either) using the HM and HP commands, respectively. Further, using the JD command you can qualify the breakpoint so that execution will continue until data within a specified range, and at the specified address is accessed.

Periscope III's hardware buffer has sufficient memory to trap 8192 bus events. When defining a breakpoint, you can instruct the hardware to save the 8K events preceding the breakpoint, the 8K following it, or 4K on either side. You can also set up a pass count, so that, for example, the breakpoint will not be executed until the fifth time an 0Dh is output to port 61h. The HC (Hardware Control) command sets those modes

Operation on an AT is somewhat more complicated. For example, when setting a bit breakpoint, you must specify the upper or lower half of the bus (or both). In addition, you can force a hardware breakpoint to be executed when memory beyond the one-megabyte area is accessed, again using the HC command.

### Hardware buffer display

There are four commands for displaying the contents of the hardware buffer; a fifth (DW) saves the buffer to disk (or memory) for future examination. The display commands are as follows.

The HR command provides a full-screen display of the raw contents of the hardware buffer. Each line contains an address, data, operation type (input, output, read, write, DMA, instruction pre-fetch), plus an address symbol, if available. A sequence number that corresponds to the 8K of stored data is also displayed. You can scroll through the buffer and search for address, data, and operation types.

HS displays a single line in the same format as the HR command.

HT and HU provide a full-screen display of the hardware buffer, but in a more digestible format. HT provides a disassembly (with labels) plus the operation types (in, out, etc.), and HU provides just the disassembly.

### Other goodies

Naturally, Periscope includes a built-in assembler. The surprise is that you can use symbols for address references—those from your program's MAP file, or those that you've defined within Periscope (using ES).

There is also (optional) on-line help. Pressing ? brings up a list of commands; pressing ? plus a command brings up a brief summary of that command.

Periscope can use two monitors—one for your program's output, and one for the Periscope debug display. When used with

an EGA and enhanced color display, the Periscope display can optionally run in the 43-line mode.

The Periscope command line is fully editable, and the program maintains a stack of recently issued commands, which you can scroll through and then edit and execute the new line. Limited macro-type facility is available, and you can repeat the last command executed by pressing F4.

A word about the break-out switch: If you run the following piece of code under Debug, the only way to regain control of your machine would be by resetting:

```
XXXX:0100 JMP 0100
```

A break-out switch will, however, allow you to escape from the loop.

### Conclusions

With or without a break-out switch, Periscope impresses us as one of the finest pieces of development software we've ever seen. It will be part of our tool kit for years to come. The hardware models aren't cheap, but if you need one, you need it bad, so cost should be no object. If you're on a tight budget, you can buy the software-only version and add your own break-out switch.

### Turbo Pascal Debuggers

Turbo Pascal, when it was introduced some four years ago, laid to rest forever the notion that serious software development could only be done by means of the traditional and time-consuming edit-compile-link-test-repeat loop. Comprising less than 40K of code, and widely available at well under \$100, Turbo Pascal also dispelled the notion that a professional compiler had to be big or expensive. In addition, it's available for a number of operating systems (CP/M, CP/M-86, and MS-DOS).

The only thing missing from Turbo Pascal was a symbolic source-level debugger of the type that companies like Periscope (see this month's hardware review) have been selling for some time.

That lack was addressed a few years ago when a program called TDebug appeared on BBSes across the nation. Since then, the product has gone commercial; the commercial implementation, called T-DebugPlus, adds a host of new features and several extremely useful utility programs.

TurboSmith, a latecomer, provides many of the features of T-DebugPlus, as well as several unique ones, including an integrated machine-language debugger.

### TurboSmith

The program is contained in a single 120K file (TSM.EXE). In keeping with the Turbo philosophy, TurboSmith costs \$69. It's writ-

ten entirely in assembly language, and requires 512K of free RAM to run. In fact, TurboSmith really needs most of 640K to function properly; it wouldn't work at all on a 3Com network station, which gobbles about 200K of memory for device drivers.

You run TSM to get into Turbo; TSM loads Turbo and adds a new item, Trace, to Turbo's main menu. (See Fig. 3.) The editor and compiler functions work just as they do without TSM; the new Trace option compiles the current program and then brings up the debugging screen. (See Fig. 4.)

That screen can display as many as three windows simultaneously. One is the source-code window, which is always displayed. The other two may contain program variables, a hex/ASCII memory dump, or a machine-language control window.

You switch among windows cyclically by pressing the F10 key; pressing F2 inside any window brings you to a command line where you can initiate various operations. For example, by typing Q you return to the Turbo menu. A full range of line-editing functions is available at each command line.

Other non-command-line operations are initiated by Ctrl-key and Alt-key combinations, and the commands work as much alike as possible inside different windows. For example, pressing Alt-B inside either the source or the machine-code window sets a breakpoint where the program will stop when it tries to execute that Pascal statement or that machine-language instruction, respectively.

In either program-control window you can execute a single statement or instruction by pressing the + key by the numeric keypad. Or press Alt-X (eXecute) to execute full-speed until a breakpoint is reached or Alt-S (Stop) is pressed. Another way of starting executing is to press Alt-A (Auto single-step). In that mode, a statement or instruction is executed, the screen is updated, and then the next program ele-

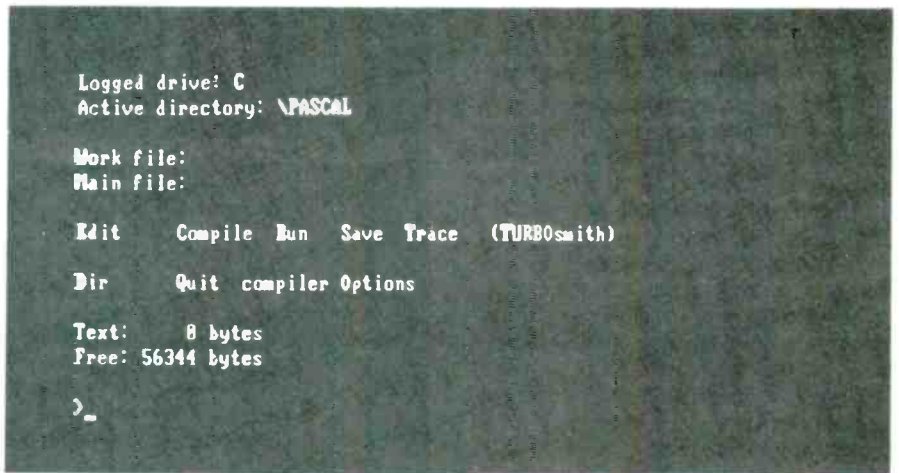


FIG. 3—TurboSmith adds a new item to the Turbo menu.

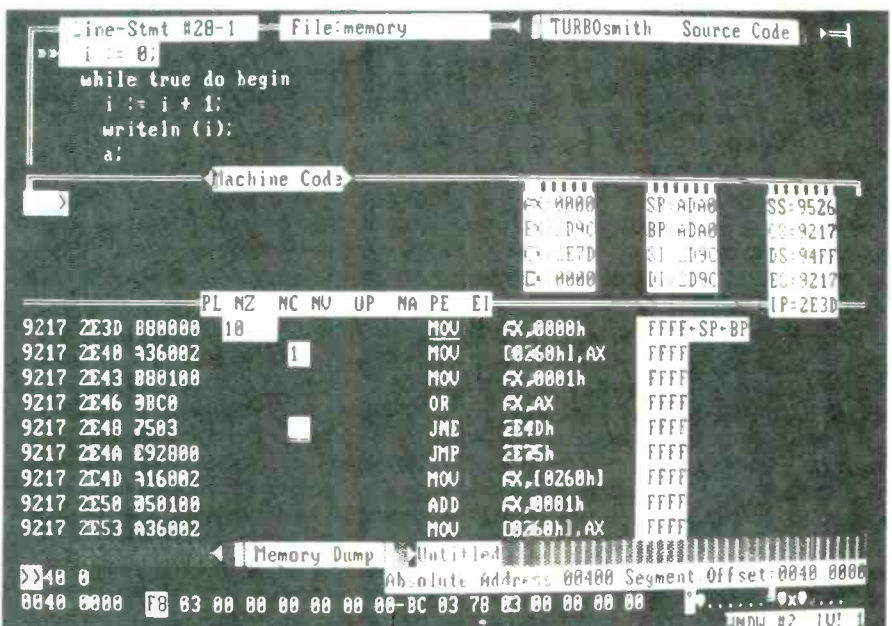


FIG. 4—The TurboSmith debugging screen.

ment is executed. Terminate Auto mode by pressing any key. Auto mode is not as useful as it might be because you can't control the speed at which statements are executed. You might want to slow execution in order to get the feel of how a loop was executing, for example.

The Variables window displays the values of all global variables, Turbo's internal variables as well as your own. You can only view variables inside a nested procedure or function when the program is executing that procedure or function. Further, you can open as many as eight window levels, each of which overlays one of the three on-screen windows. You cycle among displayed windows by pressing F10, and among levels by pressing F9. You are free to change the values of variables within any window.

Version 2.1 (which was not available in time for this review) should automatically open variable windows in nested procedures and functions.

### Screen swapping

Most programs produce some sort of screen output; TSM can deal with screen output in two ways. First, and best, you can use two monitors, one mono (IBM or Hercules) and one color (CGA or EGA). In that case, program output must go to the mono screen; the debugging windows come up on the color screen. Otherwise, on a single-monitor system, you can use screen swapping, wherein TSM maintains memory images of both the debugging data and the program's output data, swapping them at the press of a key.

One useful feature is that TSM will respond to a break-out switch. If your program gets locked in a loop and the keyboard won't respond, chances are the break-out switch will allow you to regain control and continue debugging. See this month's hardware review for more information or break-out switches.

TSM's machine-language debugger provides powerful breakpoint facilities. You

### Products Evaluated

- TurboSmith (\$69), Visual Age, 642 N. Larchmont Blvd., Los Angeles, CA 90004, 800-732-2345, 213-534-4202 (CA).

CIRCLE 31 ON FREE INFORMATION CARD

- T-DebugPlus (\$60), Turbo Power, 2109 Scotts Valley Drive, Scotts Valley, CA 95066, 408-438-8608.

CIRCLE 32 ON FREE INFORMATION CARD

- Turbo Pascal (\$99.95), Borland International, 4585 Scotts Valley Drive, Scotts Valley, CA, 800-255-8008, 408-438-8400 (CA).

CIRCLE 33 ON FREE INFORMATION CARD

- Periscope (price varies according to model), The Periscope Company, 14 Bonnie Lane, Atlanta, GA 30328, 404-256-3860.

CIRCLE 34 ON FREE INFORMATION CARD

can set *passpoints*, breakpoints that will occur only when an instruction has been executed a number of times (ranging from 1 to 65535). In addition, you can tag an instruction or a group of instructions with a number ranging from 1 to 99; you can then set, clear, or disable breakpoints by tag number. The ML debugger also provides DEGUG-like facilities for searching, filling, moving, and disassembling memory, computing hex values, inputting and outputting values to I/O ports, etc. You can also append comments to disassembled instructions, but the comments may not be saved. A macro facility allows you to record sequences of keystrokes and assign them to any key. Macros may not be saved. TSM will also accept keystrokes from a file.

In the machine-code window, you can use a non-symbolic assembler to enter assembly-language instructions into your program in one of two ways. First, by pressing Ctrl-A, you enter an overwrite mode in which your instructions overwrite whatever instructions currently reside in memory. Second, by pressing Ctrl-P, you enter a patch mode in which your instructions are inserted *between* current instructions—even if there is no space for them!

You can also patch memory in the memory-dump window, in either hex or ASCII notation. You can also force the memory-dump window to track the machine-code window, so that any time you execute a machine instruction that accesses memory, that area of memory will be displayed.

One deficiency is that you can't use TSM to debug graphics programs. Future versions of the program may correct that deficiency, but for now, you'll have to stick to text-mode debugging. Our only other complaint is that window position is hard to control; by contrast, some machine-language debuggers allow window placement by screen line number.

### T-DebugPlus

Turbo Power has been selling Turbo enhancements for a long time, and the company has a number of products, including T-DebugPlus; Turbo Extender, which allows you to create very large (greater than 64K) Turbo programs; Turbo Optimizer, which allows you to compact the size of run-time files and to create and link libraries of often-used routines; and Programmer's Utilities, which contains a program structure analyzer, an execution timer and profiler, pretty printer, and several file-management utilities. Source code is available for all programs, all of which are written in Turbo Pascal.

T-DebugPlus is contained in one .COM file and one overlay file, which together occupy about 100K of disk space. To run T-DebugPlus you need about 256K of free memory. The main features that distinguish T-DebugPlus from TSM are that (a) the program is written in Turbo Pascal, and the source is included; (b) the program has no

```

11  b;
12  writeln;
13  end;

      begin
14  i := 0;
15  while true do begin
16    i := i + 1;
17    writeln (i);
18    a;
19  end;
Source: Memory | T-DebugPLUS 2.00 |
$667D:$0260 1 | $001F 00000000 00011111 31
Watch
watch variables are removed.
WD [<parameter>] - Redraw/resize windows. <parameter> is new row for
the Window Divider. Default setting is row 14.
X [<parameter>] - Translate. If <parameter> is a symbol or statement number,
returns an address; if a hexadecimal offset, returns a statement number.
* p
* #
MaxAvail 234672 bytes (14667 paragraphs)
MemAvail 234672 bytes (14667 paragraphs)
Actual 234928 bytes
* #

```

FIG. 5—The T-DebugPlus debugging screen.

built-in machine-language debugger; (c) the program does support graphics modes; (d) program and debug screens can appear on either mono or color monitors in a dual-monitor system. T-DebugPlus also has a screen-swapping mode.

In addition, T-DebugPlus includes several useful utilities, including TMAP, which generates a .MAP file for use with an external symbolic machine-language debugger; TMERGE, which allows T-DebugPlus to debug large Turbo programs (when used in conjunction with Turbo Extender), and two program-listing programs, one of which generates a symbolic disassembly. In addition, several files contain information about various routines in Turbo's run-time library; that information is extremely useful for learning about how Turbo works. All source files are contained in a single .ARC file on the distribution disk.

To use T-DebugPlus, you run the program, which, like TurboSmith, loads and runs Turbo for you. When you Run your program from Turbo's menu, T-DebugPlus's debugging screen comes up. (See Fig. 5). There you can single-step individual statements and entire functions and procedures. You can set breakpoints that become active when a variable changes or becomes equal to a specified value, or when a particular memory location is altered. You can also set breakpoints by line number and by routine name. A breakpoint may also include passpoint count values, so that the breakpoint would be executed after a routine was executed the specified number of times. In addition, you can open a memory-dump window in one of several formats, display "watch" variables, whose values are updated on the screen each time a breakpoint is reached, and examine and change the values of variables.

All commands are executed from a com-

mand line, which can be edited. No macros are allowed, but the function keys provide shortcuts to the most common commands, and F4 repeats the last command.

Although T-DebugPlus has no built-in machine-language interface, it can be used in conjunction with an external debugger—even Debug. The DG command will drop you into your debugger. Source-level debugging is not possible in that manner. However, you can use TMAP, one of the utilities included with the package, to generate a .MAP file, which most source-level debuggers can use to link source code and machine instructions.

Several miscellaneous commands provide useful functions. For example, a brief command summary is available by pressing F1. In addition, the X command allows you to find the machine addresses of variables, source-code line numbers, procedures, and functions. Conversely, you can find the nearest statement to a specified address.

### Conclusions

T-DebugPlus and TurboSmith are both extremely useful accessories to anyone programming in Turbo Pascal.

Points to keep in mind, however, are that T-DebugPlus does graphics, has full dual-monitor support, and slightly more convenient breakpoint facilities (at the source level). In addition, it requires less memory, and its documentation is more concise and better produced. For beginners and those not needing full machine-language support, it may be the better choice. TurboSmith's strength are its windows, its built-in machine-language interface, and its ability to work with a break-out switch. But considering the reasonable prices of these packages, you may want to get copies of each. ♦♦♦

# FLOPPY-DISK DATA STORAGE

*Learn all about Apple and IBM disk formatting—including copy protection!*



**ROBERT GROSSBLATT**

**N**o matter what you use your computer for, it's safe to say that you spend a great deal of time dealing with floppy disks and floppy-disk drives. Loading programs and saving data are such common operations that we tend to forget how fragile the whole system is. But all it takes is one disk disaster to remind us of that fragility.

Of course, there are ways of protecting against those types of disasters, and other ways of dealing with them when they do occur. Performing regular backups is the best protection, but even that is not fail-safe. What happens if a disk crashes during a backup procedure?

In order to have any chance at all of recovering that data, as well as to back up copy-protected software, you need to know how data is stored on your disks. The more of the process you understand, the better your chances of successfully recovering a crashed disk. So in this article we'll examine how data is stored on both IBM and Apple floppy disks. The information provided will put you far on the road toward being a real "disk jockey."

## Tracks and sectors

The standard 5¼-inch floppy disk consists of a disk of magnetically coated plastic that is contained in a jacket, as shown in Fig. 1-a. In order for your computer to use the disk, it must have a way of finding its way around the magnetic coating on the surface. It does so by treating the disk as a group of tracks that are divided into sectors. As shown in Fig. 1-b, the tracks are a series of concentric circles, each of which is divided into a number of segments, the sectors. In addition to tracks and sectors, disks also have two sides, as shown in Fig. 2. Not all disk

control hardware and software can use both sides, however.

The number of tracks and sectors determines how much data will fit on the disk. That amount is dependent on your computer's hardware and disk operating system (DOS). The numbers vary among computers and disk sizes, but the basic principles of operation are the same.


When you tell your computer to format a disk, the hardware moves the read/write head to track zero, the outermost track, and then forces it to deposit information on the surface of the disk that indicates the sector locations. The process is repeated for each track until the last track has been formatted.

Standard 5¼-inch Apple disks have 35 tracks on one side of the disk only, and the most common IBM format has 40 tracks on each side of the disk. Double-sided 3½-inch and 8-inch disks have 77 tracks per side, and the AT's quad-density 5¼-inch disks have 80 tracks on each side.


DOS (IBM or Apple) uses tracks and sectors to organize the disk's surface. At the DOS level, to find a particular piece of information, all you need are two pieces of information: track and sector numbers. With double-sided disks, you must also specify the head number.

The number of tracks per disk is usually a function of the hardware. The DOS talks to the disk controller, which, in turn, talks to the stepper motor in the drive and tells it to move the head in or out the desired number of tracks.

The number of sectors, however, is controlled by the DOS. IBM's DOS, for example, can format for eight or nine sectors per track, but standard Apple disks have sixteen sectors per track. So you can have more small sectors or fewer large sectors.

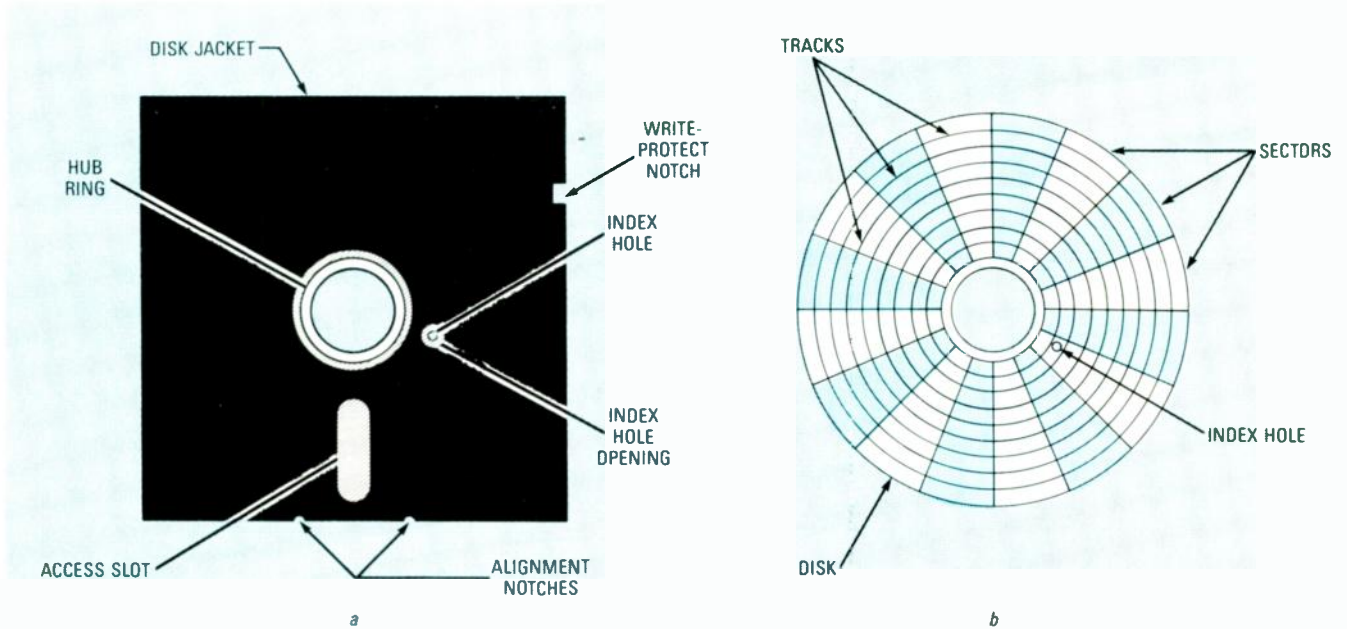

**FIG. 1—DISK CONSTRUCTION:** The magnetically coated disk is contained in a jacket (a), and is formatted to contain tracks and sectors (b).

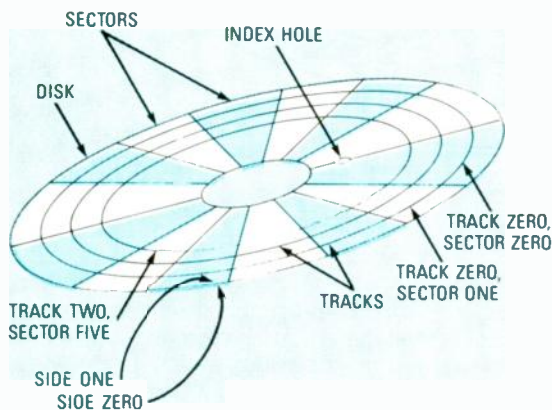

**FIG. 2—BOTH SIDES** of a disk are used by some disk control hardware and software.

### Disk formatting

When a track is formatted, DOS writes three kinds of information in each sector: ID bytes, sync bytes, and gap bytes. The exact format of those bytes differs from computer to computer, but the same sort of scheme is used by every DOS. The reason is that DOS must have a way of determining exactly which sector it's looking at. Not only that, but there must be a way of ensuring that the special formatting bytes are never overwritten by data. If that does happen, DOS has no way to identify the sector and the result is what you might expect—a crashed disk.

There are actually two kinds of ID bytes on a sector—one is the signpost that marks the sector's location on the disk, and the other lets DOS know that it's looking at the beginning of the data stored in the sector.

Figure 3-a shows a dump of an Apple DOS 3.3 sector, and Fig 3-b shows a dump from an IBM DOS 3.1 sector. At first glance, they both look meaningless—clearly different but equally meaningless. Those disk formats are the two most popular, and both the hardware and the software used to create them are

totally incompatible. It's even more interesting, therefore, to see that they use similar schemes to write disk data.

The ID marks on the IBM sector are written in hex on the disk; you'll find them in Fig. 3-b at offset 00A1h. The first three bytes (00, 00, and 01) show that you're looking at track 0, side 0, sector 1. The next byte (02) shows that the sector can hold 512 bytes.

Other sector sizes can be accommodated, as shown in Table 1. Normally, a maximum of about 6000 bytes can be written per track, so the final entry in the table may seem questionable. On the other hand, perhaps IBM has something up its sleeve.

The two bytes following the ID bytes contain a special error-detecting code called a CRC (cyclic redundancy check). The CRC is used by DOS to make sure that data read from the disk is correct. If the CRC calculated from the data that is read from the disk doesn't match the four CRC bytes in the header, DOS considers the data corrupt. Every time you change the data in a sector, DOS recalculates the CRC and writes it to the disk.

In order to keep those bytes from being overwritten accidentally, DOS uses sync bytes to mark the location of the ID bytes. When the floppy-disk controller writes a data byte on the disk, it sends out a steady clocked stream of ones and zeros. The Apple, for example, writes bytes to the disk at intervals of 32 microseconds. Sync bytes, however, are written at a different interval so they're easy to spot on the disk. Apple sync bytes are written in 40-microsecond intervals, and each sync "byte" is 10 bits long.

IBM sync bytes differ. The IBM sector in Fig. 3-b shows that there are three bytes containing a value of A1 beginning at offset 9D. Those are the specially written sync bytes that the floppy-disk controller uses to mark the location of the ID bytes. The twelve 00 bytes preceding the A1 bytes are also sync bytes. You can understand how they're used by tracing through the mechanics of a normal disk read.

When an IBM controller must read data, the first thing it does is make sure that it's looking at the right sector. It starts reading data, watching for a stream of 00 sync bytes, which lets it know that there's a chance that A1 sync bytes will follow. If they do, DOS knows that the following bytes are ID bytes.

Although ID bytes are used to mark both the signposts and your data, DOS can tell the difference by looking at the byte immediately following the A1 bytes. If it's an FE, the ID bytes are signposts, but if it's an FB then it's data. The amount of data is





FIG. 3—SECTOR DUMP of an Apple disk (a) and an IBM disk (b).

known because the sector size is specified in the signpost. The last non-data byte on the disk is called a gap byte. Gap bytes are insurance against worst-case operation. They're needed because not all disk drives turn at the same speed, so there's no way to guarantee that writing a new block of data to a sector won't overwrite existing ID and sync bytes. A disk drive only has one head per surface, so there's no way to read and write simultaneously. As long as drive speed is within tolerance, the DOS standards have been set so that there's no possibility of destroying any of the critical bytes needed to read the sector. On an IBM disk, the gap bytes usually have a value of 4E. Apple, on the other hand, uses 10-bit FF "bytes."


As for data bytes, if the sector hasn't been used, it will be filled with the DOS formatting bytes. IBM uses F6, Apple uses 96, and CP/M uses E5.

TABLE 1—IBM SECTOR SIZE ENCODING

ID Byte	Bytes/Sector
\$00	128
\$01	256
\$02	512
\$03	1024
\$04	2048
\$05	4096
\$06	8192

TABLE 2—APPLE DISK ENCODING

One Byte Volume Number	= B7 B6 B5 B4 B3 B2 B1 B0
Two Byte Disk Encoding	= \$FF FE
	= 11 11 11 11 11 11 11 10
Apple's Encoded Format	= 1B7 1B5 1B3 1B1 1B6 1B4 1B2
	= 1B0
Decoded Binary Number	= 1 1 1 1 1 1 1 0
Volume Number	= \$FE
	= 254
One Byte Track Number	= B7 B6 B5 B4 B3 B2 B1 B0
Two Byte Disk Encoding	= \$AB AE
	= 10 10 10 11 10 10 11 10
Apple's Encoded Format	= 1B7 1B5 1B3 1B1 1B6 1B4 1B2 1B0
Decoded Binary Number	= 0 0 0 0 0 1 1 0
Track Number	= \$06
	= 6
One Byte Sector Number	= B7 B6 B5 B4 B3 B2 B1 B0
Two Byte Disk Encoding	= \$AE AF
	= 10 10 11 10 10 10 11 11
Apple's Encoded Format	= 1B7 1B5 1B3 1B1 1B6 1B4 1B2 1B0
Decoded Binary Number	= 0 0 0 0 1 1 0 1
Sector Number	= \$0D
	= 13

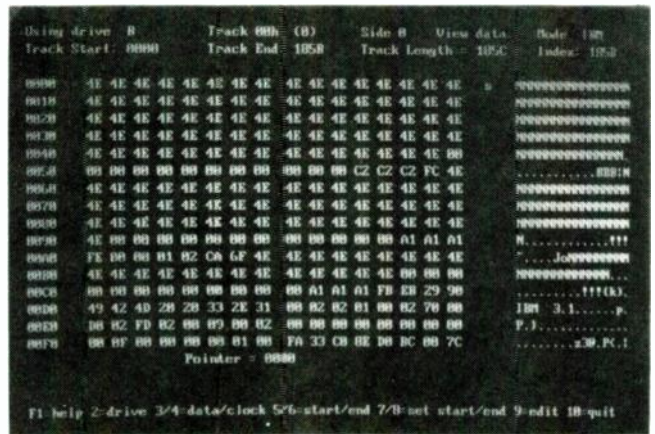

Although Apple's disk format is structurally similar to IBM's, the details are different because Apple's disk control hardware and software are unique. Most disk controllers store data in un-encoded format, so that a dump of an ASCII text file, for example, will be comprehensible. The Apple hardware, however, limits the values that can be stored on disk. The high bit of each byte must be set, there can't be more than two adjacent zero bits, and at least two adjacent bits must be set in each byte. Some values are reserved for use as ID bytes, and hardware restrictions eliminate many others, so there are only 64 possible values that can be written to the disk to represent your data.

So, in order to be able to write all 256 combinations of eight bits, it's clear that the data must be encoded. In fact, Apple has gone through three major revisions of their encoding scheme. However, that's not a subject that can be covered here; see the books in the References sidebar for more information.

**Apple format**


Apple's sector format is somewhat different. Referring back to Fig. 3-a, the signpost ID bytes are located at offset 0013h after the series of FF sync bytes. The signpost bytes always begin with a prologue (D5 AA 96), which serves the same purpose as the FE marking the IBM signpost. The next eight bytes are encoded versions of the disk volume number, track, sector, and checksum. As shown in Table 2, by decoding them we see we're looking at volume 254, track 6, sector 13. The checksum is calculated by sequentially XORing all data bytes in that sector together.

Following that information is an epilogue, which can be seen beginning at offset 0C1Eh. It marks the end of the signpost area and has no counterpart on an IBM disk. The epilogue is there so that DOS can make sure it's been reading the correct signpost marks and that it is still in sync with the disk. They're not really necessary, but remember that the Apple system was devised in the late seventies when disk drives were not as reliable as they are today.

Following another group of sync bytes comes the data bytes. At offset 0028h is the prologue (D5 AA AD); then follow 342 bytes of data. Apple stores 56 bytes of data in each sector, but, because the data is encoded, 342 bytes are needed to do it. A checksum is calculated for the data and stored at the end of the data space along with the epilogue (DE AA EB).

**Sector numbering**

Although sectors are numbered sequentially, often they're not stored sequentially. When DOS looks for a particular sector, it must locate the signpost markers, read them, verify the read, and then see if they're the ones it was looking for. All that takes time, but meanwhile the disk keeps spinning, so there's a good chance the next sector will have passed beneath the read/write head while the previous sector was being analyzed.

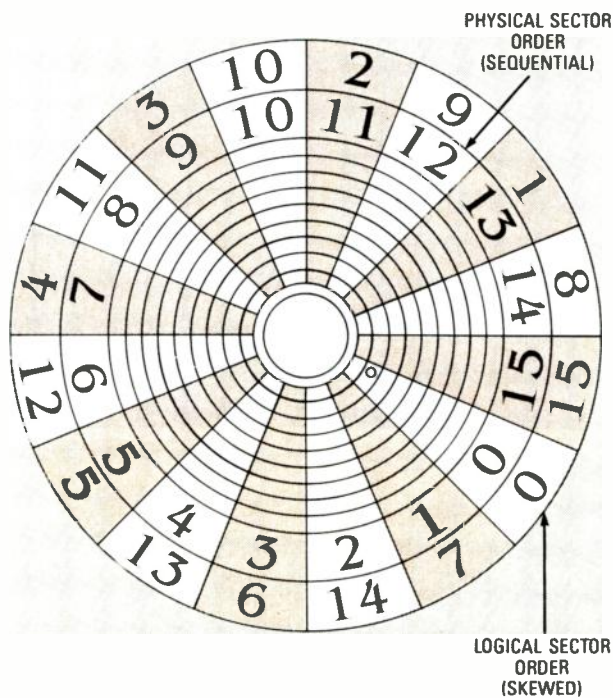

**FIG. 4—LOGICAL AND PHYSICAL sector orders are not necessarily the same.**

So, to make things more efficient, the sectors are interleaved, or skewed, as shown in Fig. 4. The inner circle indicates physical sector numbering; the outer circle indicates logical sector numbering.

### Disk organization

Now that we know how data is stored on the disk, the next step is to see how it's organized. Once again, although the details vary from computer to computer, the basic method is the same. Let's look at the general principles and then see how they're actually applied in both Apple and IBM systems.

DOS divides the disk into four areas: System, Directory, Table of Contents, and Data. Any disk operation makes use of the information stored in all four areas.

DOS itself is stored in the System area of the disk—the first few tracks on the disk. The number of tracks depends on the size of DOS and the type of computer. The very first sector on the first track is called the *boot sector* and it's used whenever you boot a disk. It has a short machine-language program that tells the computer how to go about loading DOS from the disk. In addition, in some systems it contains data related to the directory structure, disk format, and so on.

When you boot your computer, the disk controller reads the boot sector into memory. Then the computer turns control over to the program, called the bootstrap loader, that is contained in that sector. Things are done that way because the controller can read in only a sector at a time. You can read in more than one sector at a time—but that's DOS's job. So it's a chicken-and-egg problem: you need DOS to read multiple sectors and you can only read in multiple sectors by using DOS. But because DOS is located in a specific place on the disk, the bootstrap loader knows how to transfer it to the computer's memory.

The Directory and the Table of Contents go hand in hand. The former is a list of the files stored on the disk, and the latter is a list of sectors telling DOS where to find them. Every time you tell DOS to access a particular file, it first goes to the Directory to see if the file exists and, if it does, DOS then turns to the Table of Contents to get the file's location on the disk.

As you might have guessed, the Data space is where DOS stores your data.

IBM stores DOS in three disk files: IBMBIO.COM, IBMDOS.COM, and COMMAND.COM. (Clones running MS-DOS store the first two of those programs under different names.) In order for the computer to load DOS from the disk, IBMBIO.COM and IBMDOS.COM must be the first two files on the disk. If they're not, the bootstrap loader won't be able to find them, and you'll get the infamous "NON-SYSTEM DISK OR DISK ERROR" message. Those two files contain the routines the computer uses to control the disk hardware. The third file, COMMAND.COM, is loaded after the first two and it's the part of DOS that executes internal DOS commands (DIR, REN, DEL, etc.), external programs, and batch files.

IBM's Table of Contents is called the FAT (file allocation table). It's used to keep track of where each chunk of each file is stored on the disk, which sectors are available for use, which sectors are bad, and so on. The basic unit of the FAT is called the cluster, and it represents a variable number of disk sectors, depending on the operating system and on the format of the disk. For example, single-sided IBM disk clusters are one sector long, double-sided IBM disk clusters are two sectors long, and higher density disks have even larger clusters.

The Directory is also located on track 0, right after the FAT. It stores the names of your files, their attributes, the date and time they were created, their size, and the location of the file's first entry in the FAT. The rest of the disk is set aside for your data. When you change anything on the disk by writing new data, DOS must update the Directory and the FAT, because they work together to keep your files organized.

The Apple also has a boot sector to start the process of loading DOS into the computer. The actual contents of the boot sector (as well as the organization of the disk) depends on which Apple DOS you're using. Both systems, however, differ from the IBM version in that the only job of Apple's boot sector is to start the process of loading in DOS.

There are major differences in the two current Apple operating systems, DOS 3.3 and ProDOS. Although the basic sector formatting is the same, the organization of the disk is quite different. The older system, DOS 3.3, stores the System on the first three tracks, and the directory on track 11h (in the middle of the disk). That was done, the reasoning went, because, on average, the head would have less distance to travel to get to the directory than if the directory had been located in track 0, as on the IBM. Less distance means less time, so that wasn't bad reasoning.

ProDOS, on the other hand, has a closer resemblance to the IBM system in that the directory is stored in the lower tracks. Disk space is allocated a sector at a time under DOS 3.3, and a block at a time under ProDOS. (A block equals two consecutive sectors.) The Table of Contents is called the Volume Table of Contents in DOS 3.3 and the Volume Bit Map in ProDOS.

Both are similar to the IBM's FAT in that each contains a table that DOS uses to keep track of which sectors are free, which are reserved, and which are otherwise used. Each file on the disk reserves a track-and-sector list sector (or block) that contains a list of the sectors where each file's data is stored. Overall, the Apple has to do about the same amount of housekeeping as the IBM. It must update the directory, the table of contents, and the track/sector list for each file you use.

### Copy protection

With those facts in mind, let's examine various copy-protection schemes. But before we get into the details, let's talk about the philosophy behind copy protection. Both software publishers and software owners make strong arguments about protecting their investment—and they're both right. Nobody wants to get ripped off, so publishers should be able to make money, and owners should be able to make legitimate backup copies of software they have purchased. Of course, there is much

*continued on page 100*

# BUILD THE PT-68K

*The big moment:  
add the microprocessor.*

PETER STARK, STARK SOFTWARE SYSTEMS CORPORATION



© 1987, Peter A. Stark

**Part 3** In the first installment of the **Computer Digest Classroom**, we presented an overview of the PT-68K. In part two, we built clock, reset, and test circuits. Now let's install the 68000 and start learning how it works.

## Step 7: hardware basics

The pinout of the 68000 microprocessor is shown in Fig. 1. Though it's a 64-pin IC and looks complex, it really is straightforward. Let's go over it pin by pin.

In the figure, notice first the data bus, with its 16 lines labeled D0-D15, and the address bus, with its 23 lines labeled A1-A23. In case you're wondering, there is no A0—see below.

The remaining signals are known collectively as the control lines; let's look at them in more detail. Each control line is labeled with an arrow to indicate whether it is an input, an output, or, in some cases, both.

The three active-high output lines FC0, FC1, and FC2 output a function code that can be decoded to indicate what the 68000 is doing internally; the function code can also be used to increase the 68000's addressable memory to 64 megabytes.

The enable line ( $\bar{E}$ ), the valid memory address line ( $\bar{VMA}$ ), and the valid peripheral address ( $\bar{VPA}$ ) line are all useful when the 68000 is used with older input-output IC's, particularly those originally intended for use with Motorola's 6800 processor. Also,  $\bar{VPA}$  provides some interrupt information.

IPL0, IPL1, and IPL2 are interrupt-level inputs. We will discuss interrupts later; for now let us just say that an event such as a keypress can interrupt the 68000, cause it to stop whatever it's doing, and then respond to the interrupt. The three interrupt inputs tell the 68000 whether an interrupt is being asked for, and what kind of an interrupt it is.

The RESET and HALT inputs come from the 555 circuit shown in Part 2, Fig. 6. Note, however, that those two pins are also outputs. That explains why an open-collector 7406 inverter was used to drive them; occasionally the 68000 may output a low on one of those lines, and that would conflict with the normally high output of a standard inverter (such as a 7404).

BR, BG, and BGACK are used with DMA circuitry, which is used to transfer blocks of data without help from the microprocessor. If DMA were used, the DMA controller would send a bus request ( $\bar{BR}$ ) signal to the 68000, which would release the data and

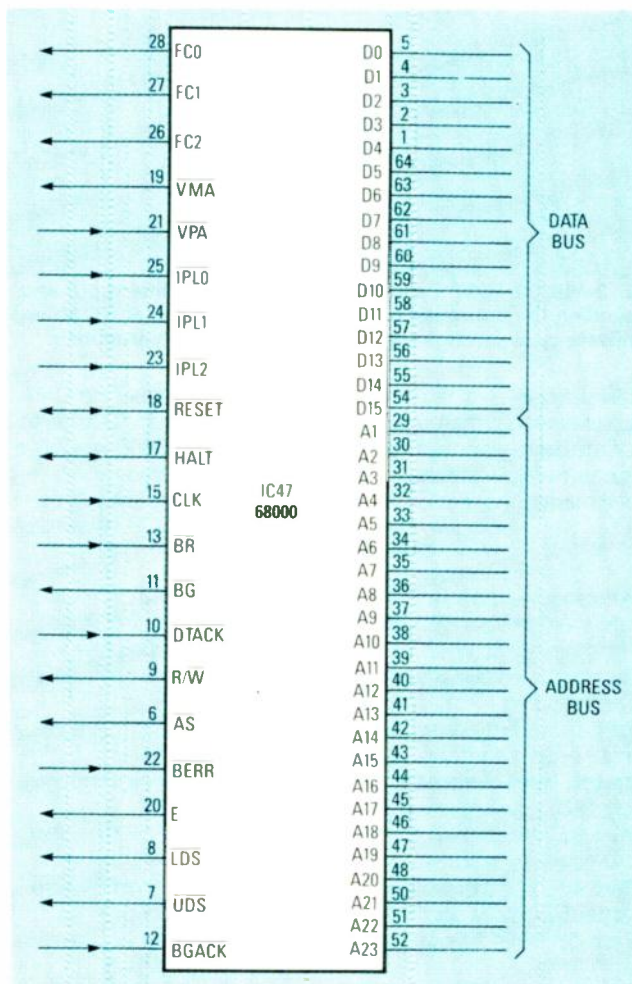


FIG. 1—THE 68000 MICROPROCESSOR has sixteen data lines, 23 address lines, and 21 control lines.

DECEMBER 1987

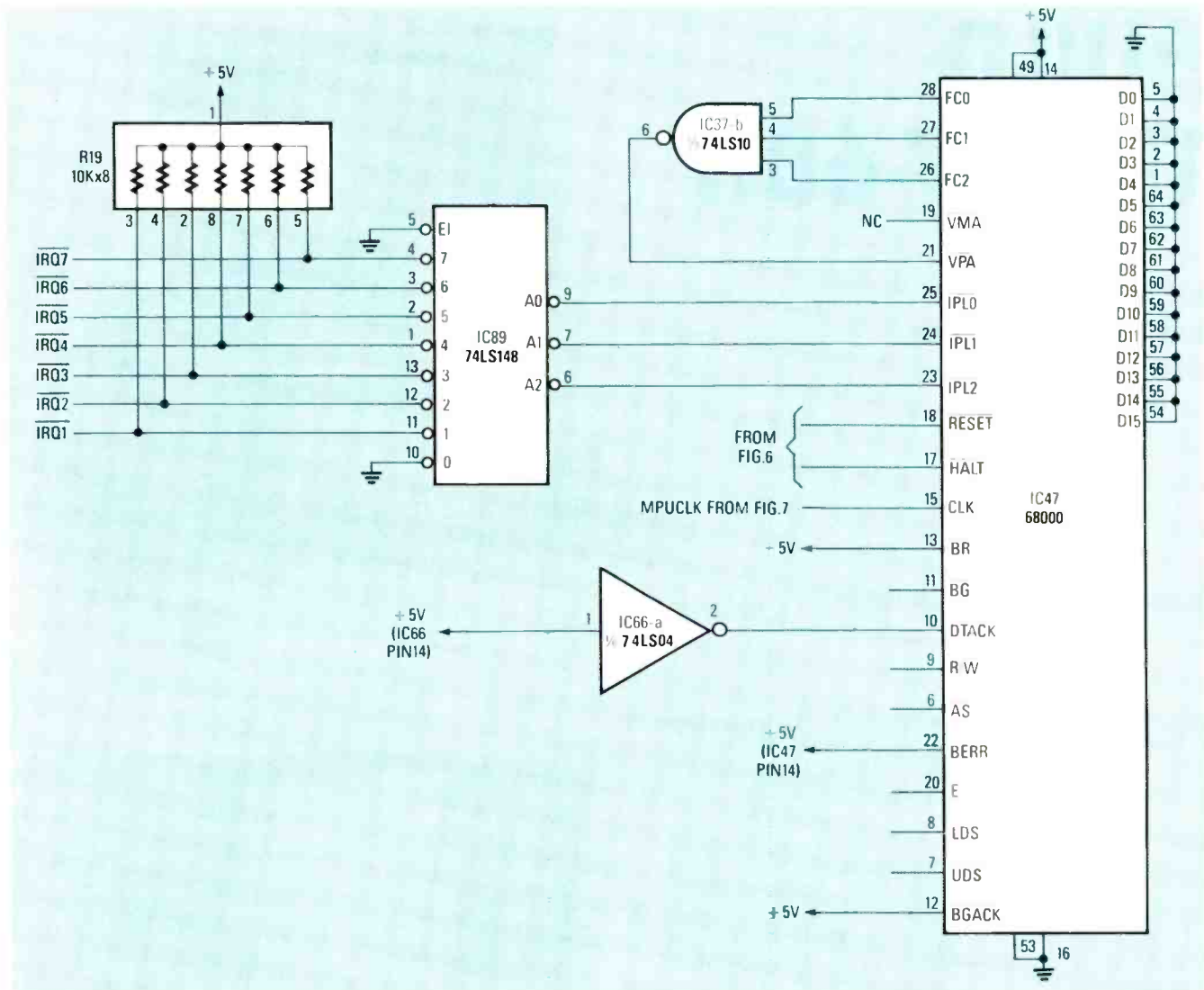


FIG. 2—68000 TEST CIRCUIT. By disabling all interrupts and grounding the entire data bus, you can force the 68000 to repetitively cycle through four million "phantom" instructions.

address buses and return a bus granted ( $\overline{BG}$ ) signal. The DMA controller would then send a bus grant acknowledge ( $\overline{BGACK}$ ) to confirm that it has control of the buses. Then the 68000 would sit back and wait while the DMA controller did its thing.

We mentioned that  $\overline{LDS}$  and  $\overline{UDS}$  replace address line A0; they

**Past, present, future**

What follows is a listing of the contents of past and projected future articles in the **Computer Digest** 68000 Classroom. The precise number of articles—and their contents—will depend on your response, so *let us know what you're interested in!*

- Part 1:** System overview, block diagram, parts list, memory map, ordering information.
- Part 2:** Parts-placement diagram, power connector mounting, LED, speaker, reset, and clock circuits.
- Part 3:** Introduction to the 68000, test circuit, EPROM and RAM circuits, address-bus waveforms.
- Part 4:** Logic symbols,  $\overline{MAP}$  circuit, address decoding,  $\overline{BERR}$  and  $\overline{DTACK}$ , RAM and ROM, HUMBUG.
- Part 5:** Serial interfacing and IBM-compatible expansion slots.
- Part 6:** Dynamic RAM.
- Part 7:** Disk control hardware and software. SK\**DOS*.

do so in an interesting way. The 68000 has a 16-bit data bus, but memory is organized as eight-bit bytes. Even so, the data bus can access two bytes at a time. The memory is wired so that half of memory—the odd-numbered locations—connects to the lower part of the data bus (bits D0–D7), and the other half of memory—the even-numbered locations—connects to the upper part of the data bus (bits D8–D15). The 68000 asserts  $\overline{LDS}$  when it wants to use the lower half of the data bus,  $\overline{UDS}$  if it wants to use the upper half of the data bus, or both if it wants to transfer 16 bits on the entire data bus. Thus an odd address turns on  $\overline{LDS}$ , and an even address turns on  $\overline{UDS}$ . The overall effect is similar to that provided by address line A0 in other microprocessors, where A0 is low for an even address and high for an odd address.

$\overline{AS}$  is an address strobe which is generally asserted by the 68000 at the same time as either  $\overline{LDS}$  or  $\overline{UDS}$ ; it simply tells external circuitry (address decoders, for example) that there is a valid address on the address bus. That's an important point, because the address bus often carries data that is meaningless;  $\overline{AS}$  provides a way of preventing decoders from responding to invalid addresses.

Next comes the read/write line ( $R/\overline{W}$ ), which is used by the 68000 to tell other circuitry whether it wants to read data in (when  $R/\overline{W}$  is high) or write data out (when  $R/\overline{W}$  is low). In other words,  $R/\overline{W}$  is high when data goes from RAM or ROM to the

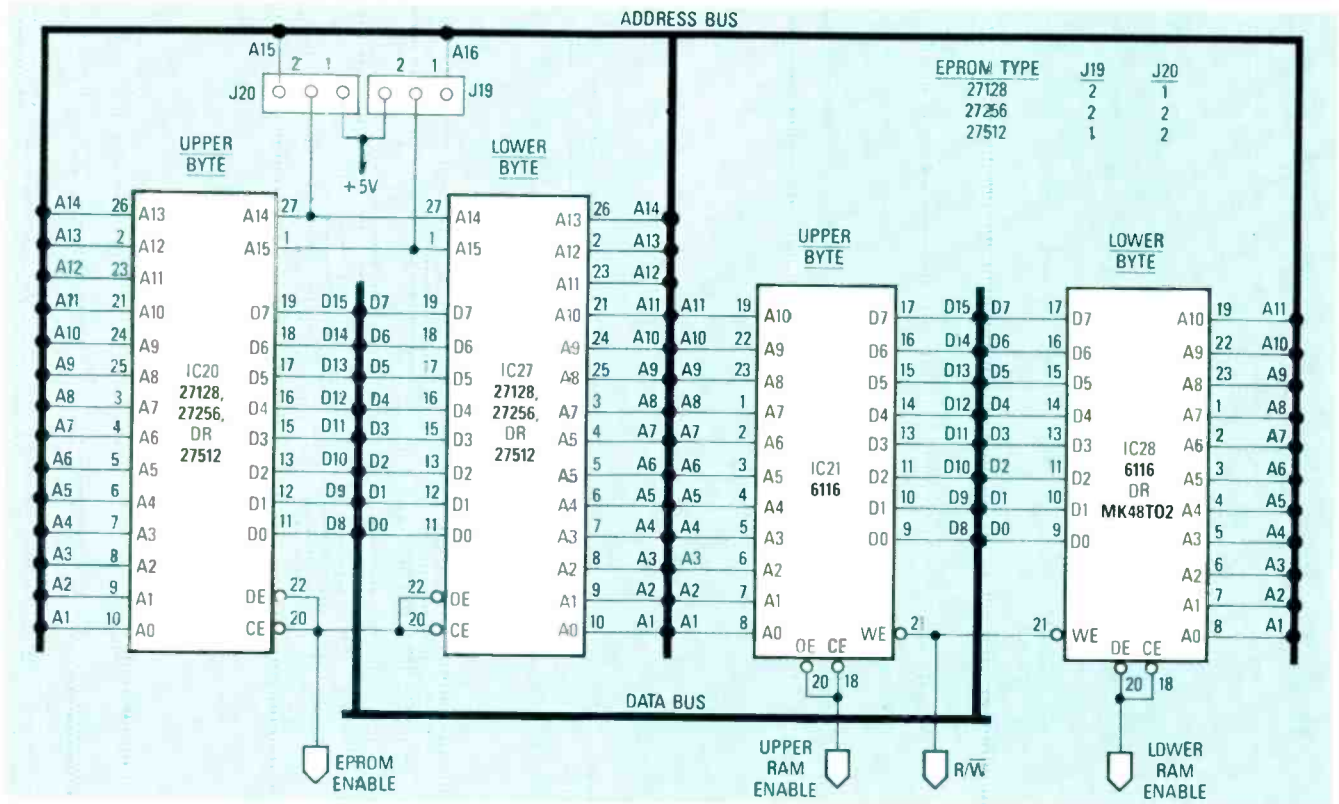


FIG. 3—EPROM AND STATIC-RAM WIRING is shown here.

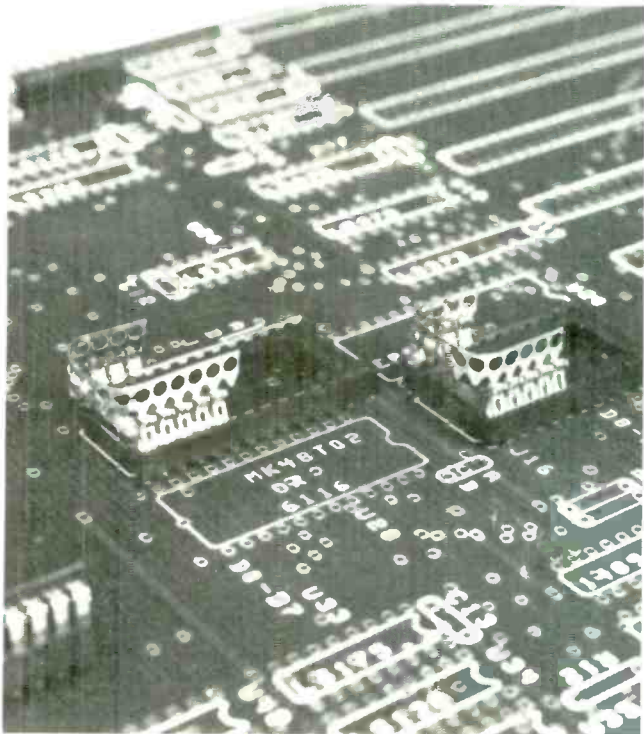


FIG. 4—USE MOLEX SOLDERCON PINS to ground all data lines without soldering.

### Thanks

I'd like to thank Fred Brown of Peripheral Technology, Inc., kit supplier for this CD Classroom series. Fred is the wizard who designed the hardware of the PT-68K; without his assistance, the project would never have gotten off the ground.

68000, and low when data goes from the 68000 to RAM. Normally we don't write to a ROM.

$\overline{BERR}$  is an input to the 68000 that external circuitry uses to tell the 68000 when something has gone wrong on one of the buses. We will see how that is done later.

Last,  $\overline{DTACK}$  stands for data transfer acknowledge. Whenever the 68000 wants to read or write to memory (or an I/O device), it (a) puts the address on the address bus, (b) puts a high or low on  $R/\overline{W}$ , (c) asserts  $\overline{AS}$ , (d) asserts  $\overline{UDS}$ ,  $\overline{ODS}$ , or both, and (e) waits until either  $\overline{DTACK}$  is asserted, indicating that the transfer has completed successfully, or  $\overline{BERR}$  is asserted, indicating that something went wrong. When  $\overline{DTACK}$  is received, the 68000 goes on to the next instruction. We'll discuss what happens if  $\overline{BERR}$  is asserted later.

If  $\overline{DTACK}$  were permanently grounded, the 68000 would assume that all transfers finished quickly, so it would zip along at maximum speed. In most cases, though,  $\overline{DTACK}$  is generated by an external timer that gives memory and I/O just enough time to finish their jobs. And if a memory or I/O device is particularly slow,  $\overline{DTACK}$  can then be delayed so that the 68000 will wait for it to finish.

In practice, each 68000 memory or I/O access takes a specific amount of time, which is measured in clock cycles. If  $\overline{DTACK}$  is delayed, for even an instant, the 68000 lets an extra clock cycle slip by and checks again. If  $\overline{DTACK}$  is still off, the 68000 waits another clock cycle, and so on. Each of those clock cycles is called a *wait state*. Ideally, everything would be fast enough so that the 68000 could continue processing without wait states. However, some computers have slow memory or I/O devices, and therefore run with one or even more wait states, which obviously slows everything down. You'll be happy to know that the PT-68K runs with no wait states!

### 68000 test circuit

Last time we built the clock and reset circuits, and now that we have some basic familiarity with the 68000, it's time to get the system running. Normally, you need quite a bit of external hardware to get a 68000-based computer running, but there is a

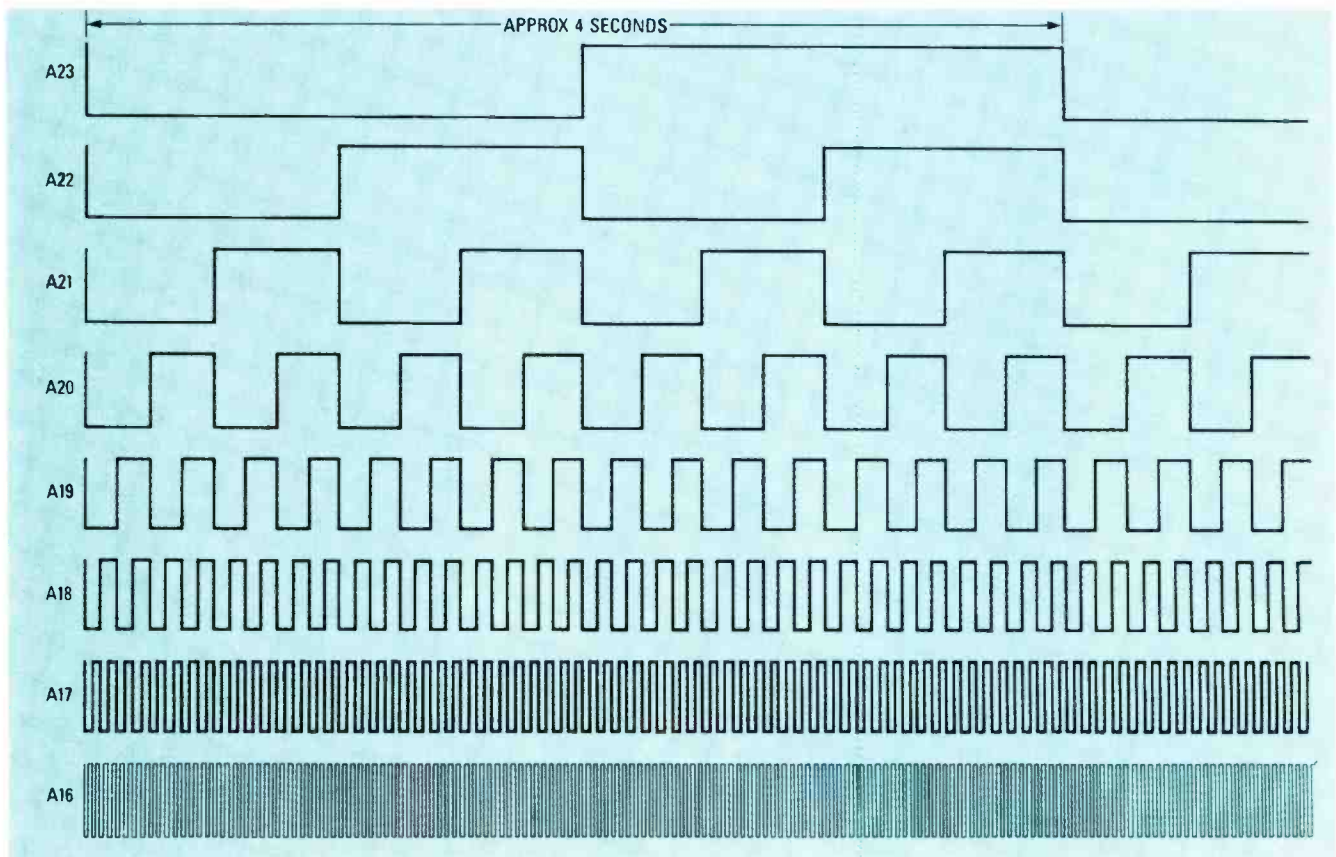


FIG. 5—EACH SUCCESSIVE ADDRESS LINE runs at half the frequency of its predecessor.

way of fooling the microprocessor into thinking the necessary support circuitry is connected, even though it isn't. Figure 2 shows how. Basically, the circuit ensures that interrupts are disabled and jams the data bus with "phantom" instructions that the 68000 will execute over and over.

In order to minimize the amount of extra wiring we have to do, we will take advantage of circuitry already on the printed-circuit board (which will be needed later anyway). For example, we can use  $\overline{\text{RESET}}$ ,  $\overline{\text{HALT}}$ , and  $\text{CLK}$  as-is.

The circuit works like this: IC37-b is a NAND gate that asserts  $\overline{\text{VPA}}$  when  $\overline{\text{FC0}}$ ,  $\overline{\text{FC1}}$ , and  $\overline{\text{FC2}}$  are all high, and negates  $\overline{\text{VPA}}$  at all other times. That is done because  $\overline{\text{VPA}}$  is used only during interrupt processing; for now, we need to force it high.

Also dealing with interrupts is IC89, a priority-encoder IC. In normal operation, when an interrupt request appears on one of the  $\overline{\text{IRQ}}$  lines ( $\overline{\text{IRQ0}}-\overline{\text{IRQ7}}$ ), IC89 functions as a traffic cop that determines which line has the highest priority.  $\overline{\text{IRQ7}}$  has a higher priority than  $\overline{\text{IRQ6}}$ , which is in turn higher than  $\overline{\text{IRQ5}}$ , and so on. Depending on which interrupt lines are active, IC89's three outputs send a binary number corresponding to the highest priority interrupt to the  $\overline{\text{IPL0}}$ ,  $\overline{\text{IPL1}}$ , and  $\overline{\text{IPL2}}$  lines of the 68000. For example, if the highest priority interrupt request is  $\overline{\text{IRQ4}}$ , U89 sends the binary number 100 (4) to the 68000 by forcing  $\overline{\text{IPL2}}$  high and the others low.

In our test circuit, however, the seven resistors in R19 are pulling all of the  $\overline{\text{IRQ}}$  lines high. Therefore, IC89 sees no interrupt request, so it sends the binary number 000 to the 68000, telling it that there are no interrupt requests.

By the way, we could have achieved the same result by grounding the three  $\overline{\text{IPL}}$  pins of the 68000 and by tying  $\overline{\text{VPA}}$  high. However, we can save ourselves extra labor by installing R19, IC89, and IC37, which we'll have to do eventually anyway.

Two of the inputs, labeled  $\overline{\text{BR}}$  and  $\overline{\text{BGACK}}$ , are already tied high, and a number of other pins are unconnected.

That leaves the data bus,  $\overline{\text{BERR}}$ , and  $\overline{\text{DTACK}}$  to contend with.

First,  $\overline{\text{BERR}}$  must be tied high so that the 68000 won't think a bus error has occurred. That is easily done by installing a short jumper between pins 14 and 22 of the 68000, on the foil side of the board.

Normally  $\overline{\text{DTACK}}$  will carry a meaningful signal, but for now we want to ground it to make the 68000 think that all is well on the outside. The inverter (IC66-a) that drives  $\overline{\text{DTACK}}$  was installed previously, so force the input high by installing a jumper from pin 1 to pin 14 of that IC on the foil side of the board.

Last, as shown in Fig. 2, we want to ground all sixteen data lines. The reason is that, when the 68000 is running normally, it fetches instructions and addresses from memory, so we have to provide it with some apparently meaningful data. By grounding the entire data bus, every time the 68000 tries to read anything from memory it will read the number 0000. As it turns out, that is a valid 68000 machine-language instruction, which is written:

OR.B #0,D0

That instruction tells the microprocessor to or a 0 to register D0; the instruction consists of four 00 bytes.

Though that OR instruction seemingly does nothing, the 68000 thinks that all 16 megabytes of memory are filled with 4 million OR instructions, and so it starts executing them one after another. When it gets to the top of memory at \$FFFFFF, it simply "wraps around" and starts over at \$000000.


### Fire it up

Now let's wire up the circuit and see what happens. Install the following components: sockets for IC37, IC47, and IC89; R19, a 10K single-in-line package. Pin 1 of R19, identified by a white line or dot, should point toward J25. Then install C14, C48, and C66 (0.1  $\mu\text{F}$  disc capacitors), and last jumpers from pin 14 to pin 22 of IC47 and from pin 1 to pin 14 of IC66. Both jumpers will be removed later, so install them neatly and in a way such that they can be removed easily.

Grounding all sixteen lines of the data bus at the micro-
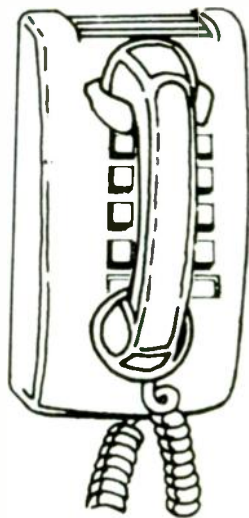
# R-E Computer Admart

Rates: Ads are 2 1/4" x 2 7/8". One insertion \$825. Six insertions \$800 each. Twelve insertions \$775. each. Closing date same as regular rate card. Send order with remittance to **Computer Admart**, Radio Electronics Magazine, 500-B Bi-County Blvd., Farmingdale, NY 11735. Direct telephone inquiries to Arline Fishman, area code-516-293-3000. **Only 100% Computer ads are accepted for this Admart.**



## CALL NOW AND RESERVE YOUR SPACE

- 6 - rate \$800.00 per each insertion.
- Reaches 245,824 readers.
- Fast reader service cycle.
- Short lead time for the placement of ads.

Call 516-293-3000 to reserve space. Ask for Arline Fishman. Limited number of pages available. Mail materials to: Computer Admart, RADIO-ELECTRONICS, 500-B Bi-County Blvd., Farmingdale, NY 11735.

### COMPUTER ASSEMBLY MANUALS



Eliminate Guesswork! Build with Confidence!

**BIG BLUE SEED for IBM™ BUILDERS!** Parts list, placement diagrams, instructions, mods, for assembling over 90 IBM-compatible bare cards. Latest version with guides for 640K, Turbo, AT & Baby AT MthBds. **\$17.95**

**APPLE™ BUILDERS NEED APPLE SEED!** Instructions for assembling over 90 Apple-compatible bare cards including II+ & IIe MthBds. For ALL Apple enthusiasts and hobbyists **\$14.95**

**SAVE 10% - ORDER TWO OR MORE MANUALS OVER 40 BARE IBM & APPLE CARDS IN STOCK** (MthBds - Disk - Video - Burner - MultiFn - I/O - Modem - Proto - etc)

Check Money-order, VISA, MasterCard to: **NuScope Associates\*, Dept RE**  
In U.S.A. In CANADA  
P O Box 790 P O Box 742, Stn B  
Lewiston, NY 14092 Willowdale, Ont M2K 2R1  
\*A Division of Kosmic MicroTech Inc.

CIRCLE 194 ON FREE INFORMATION CARD

### LASER PRINTER\* P.C. COPIER OWNERS



\*H.P., Apple, OASYS, OMS, and more  
**Recharge Your Used Toner Cartridges.**

RECHARGING	PRINTER COPIER	
BLACK	\$45	\$40
DK BLUE BROWN	\$65	\$60
NEW CARTRIDGE	\$89	

(RETURN SHIPPING INCLUDED)

**20 Years of Laser Printing and Xerography Experience -Unconditional Guarantee-**

**LASER EDGE**

800 W. Burlington, Fairfield, IA 52556  
(800)635-8088 (515)472-7850

CIRCLE 197 ON FREE INFORMATION CARD

### CHRISTMAS SPECIAL

12-16-20 MHZ.  
HIGH SPEED  
TURBO-286/386



- ▶ CPU-286-12/386-16 MHZ.
- ▶ 287/387 and 16-20 MHZ. opt.
- ▶ 1 MGB. on board. Max. 16 MGB.
- ▶ 2 Teac 1.2, or 360/3.5/720.
- ▶ 60 MGB. 28 MLS. with W.D. Contr.
- ▶ I/O, Serial, Parallel, Game.
- ▶ PGA, EGA, CGA, MGA, HERC. S. Sw.
- ▶ Deluxe Keybrd. 102/12 Funct. Keys.
- ▶ 200 W.P.S. Case, Digital Display.
- ▶ ☆ **TURBO-XT-W/Monitor...\$899.00**

**TURBO-286/386-\$2,499.00/\$3,499.00**  
**COMPSTAR, INC.**  
**(818) 842-4606**

239 E. Alameda Ave., Burbank, CA 91502  
TELEX: 797196 FAX: (818) 845-0739

CIRCLE 202 ON FREE INFORMATION CARD

### ICs PROMPT DELIVERY!!!

SAME DAY SHIPPING (U.S. ONLY)

24251213, 2411 2412, 2413, 2414, 2415, 2416, 2417, 2418

OUTSIDE OKLAHOMA: NO SALES TAX

DYNAMIC RAM		
1Mbit	1000Kx1	100 ns \$27.50
1Mbit	256Kx4	120 ns 32.00
51258	*256Kx1	80 ns 7.40
4464	64Kx4	150 ns 3.60
41256	256Kx1	80 ns 5.50
41256	256Kx1	100 ns 4.85
41256	256Kx1	120 ns 3.95
41256	256Kx1	150 ns 3.50
41264	2 PORT	120 ns 5.25
EPROM		
27C101	1000Kx1	150 ns \$45.00
27C256	32Kx8	250 ns 6.75
27256	32Kx8	250 ns 5.60
27128	16Kx8	250 ns 5.35
STATIC RAM		
43256L-12	32Kx8	120 ns \$11.75
6264LP-15	8Kx8	150 ns 3.50

OPEN 6 1/2 DAYS, 7-30 AM-10 PM SHIP VIA FED-EX OR SAT.

SUNDAYS & HOLIDAYS - SHIP OR DELIVERY VIA U.S. EXPRESS MAIL

SAT DELIVERY INCLUDED ON FED-EX ORDERS RECEIVED BY 10:30 AM \$4.18 (H.P. \$10.50 2 lbs)

MAJORS AND VISA AT 110% (ASHI 1.2%)

Factory New, Prime Parts 24/7

MICROPROCESSORS UNLIMITED INC

31000 S. Florida Ave. (918) 267-4961

BEAUGIS (IN 7424)

No minimum order

Orders received by 8 PM CST can usually be delivered the next morning via Federal Express Standard Air - \$4.00, or guaranteed next day Priority One - \$10.50

CIRCLE 61 ON FREE INFORMATION CARD



### IBM PC/COMPATIBLES

- TEN PROGRAMS
- 100% BASIC
- EASY TO LEARN
- EASY TO USE
- WRITTEN BY EMERALD DIRECT
- SINCE 1981

### NOT COPY PROTECTED

CA RESIDENTS \$49.95 + \$2 USA ONLY ADD STATE TAX SHIP/DEL. HANDLING

BLECHMAN ENTERPRISES  
7217 BERNADINE AVE #10  
CANOGA PARK CA 91307

INFO/ORDER 9AM 5PM M SAT PACIFIC TIME

818-346-7024

### TURBO CHARGE YOUR PC WITH THE ACCELERATOR 286

Replaces your PC, XT, or compatibles 8088 with an 80286 processor. It includes 8K of zero-wait-state cache memory, and your software can run up to 7 times faster. So why buy an AT? Upgrade your PC with the Accelerator. **\$275**

### VIDEO SHARING DEVICE

**\$59.95**

Transmits color computer/VCR signal to any TV at home without cables. Simply plug it into computer's composite outlet or VCR's jacks. This is the least expensive way of upgrading your system to color without buying a color monitor. Minor assembly required.

**PC Plus Corp.** Monterey Park  
710 E. Garvey Ave.  
California 91754 (818)571-6991

CIRCLE 201 ON FREE INFORMATION CARD

processor's socket could lead to problems later, so we'll do it another way. The data bus is more accessible at the two EPROM sockets (IC20 and IC27) and at the two static RAM sockets (IC21 and IC28). The wiring diagram of the EPROM and static-RAM circuitry is shown in Fig. 3. Install a 28-pin socket at IC27 and a 24-pin socket at IC21.

The D0-D7 lines of the data bus are connected to IC27 via pins 11-13 and pins 15-19, and pin 14 is conveniently grounded. So we need to short pins 11-19 together. In the same way, the D8-D15 lines of the data bus are connected to IC21 via pins 9-11 and 13-17, and pin 12 is conveniently grounded. So we need to together pins 9-17 together.

On both IC21 and IC27, those are the bottom four pins on the left and the bottom five pins on the right. Instead of soldering any wires, take a strip of Molex Soldercon pins and insert them into the sockets as shown in Fig. 4, with four pins on the left, five pins on the right, and a section of six or so pins bent in a U shape below. Molex pins are normally sold as an inexpensive substitute for sockets; they consist of individual clips joined by a perforated carrier strip that is normally broken off after soldering the pins to the PC board. In our case, we insert the thin pins into the socket, and use the entire strip as one big short circuit.

Now plug in the IC's, being careful not to bend pins, and turn on the power. Connect your LED probe to pin 52 of the 68000,

### Ordering Information

Complete details were given in part one (in the October issue). To summarize: The basic kit (PT1, \$200) contains all parts except power supply, case, and video terminal or personal computer to get a small system (ROM monitor, 2K RAM) up and running. The full basic system (PT68K, \$460) includes 512K of dynamic RAM, floppy-disk controller, parallel port, battery-backed clock/calendar, and three PC-compatible expansion slots. To order, or for more information, contact Peripheral Technology, 1480 Terrell Mill Road #870, Marietta, GA 30067, (404) 984-0742.

which is address line A23. If all is well, the LED will light for about 2 seconds, go off for about 2 seconds, and so on. (That flashing rate will be faster if your PT-68K's clock is faster than 16 MHz.)


If the LED does not flash at the expected rate, recheck the signal at every pin of the 68000. Look especially for a low on  $\overline{DACK}$ , lows on all data lines, highs on  $\overline{BERR}$ ,  $\overline{HALT}$ , and  $\overline{RESET}$ . When looking at the clock signal, the LED should be slightly dim.

If the LED flashes as expected, all is probably well. What's happening is that the 68000 is racing through memory (or what it thinks is memory, all 16 megabytes worth), executing or instructions at maximum speed, one instruction per microsecond. One complete run through four million instructions (4,194,304 instructions, to be exact) therefore will take slightly more than four seconds.

During that time, the address bus is counting off the addresses where the 68000 thinks those instructions are coming from. If you look at the address bus you see that A1 alternates 0, 1, 0, 1, 0, 1, .... A2 also alternates, but slower: 0, 0, 1, 1, 0, 0, ...; and so on.

Figure 5 shows the waveforms present on the upper eight bits of the address bus. When the LED probe is connected to A23, it flashes on and off once every four seconds. If it is connected to A22, it repeats once every two seconds; on A21 it repeats once per second. As we go down to A20, A19, and so on, it flashes faster and faster, until at A16 (pin 44) it flashes so fast (about 32 times per second) that we can barely see it flicker; A15, flashing about 64 times per second, looks absolutely steady.

Last, if you have access to an oscilloscope or frequency counter, examine each address line to make sure that its frequency is half that of its next higher neighbor. This ensures that there are no shorts between adjacent address lines. If you use a frequency counter, keep in mind that real-world waveforms are not as well defined as the idealized ones shown in Fig. 12, so some counters may have difficulty properly counting the frequency of such a square wave.)

Next time we'll add address decoders, ROM and RAM. See you then. 

## FLOPPY-DISK DATA STORAGE

continued from page 94

illegitimate software floating around, so it seems that something has to be done about basic human nature before copy protection will cease to be an issue.

Even though there are obvious (and subtle) differences between the hardware and software comprising various types of computers, the basic approach to copy protection is the same: Make the disk unreadable by the standard DOS. It's easy to do because any DOS must make a number of assumptions about disk format before it tries to read or write information. It must assume, for example, that it's going to find tracks formatted in a particular way, that each one will contain a specific number of sectors, and that those sectors will contain data written in a predefined fashion. If any of those conditions aren't met, DOS will throw in the towel, and, instead of data, all you'll get is an error message. The point is that any disk that has data organized in a non-standard way must also have a non-standard way to read that data.

When Apple introduced its disk system in the late seventies, the company emphasized software rather than hardware. That was a departure from the norm, because most disk systems were and are built around a single-IC LSI controller. As a result, Apple disks were (and still are) unreadable by most other machines. However, Central Point Software's Option Board allows an IBM to read Apple disks, and many others as well.

Doing most of the disk control in software makes it simple to

upgrade DOS. It also makes it easy for creative programmers to write copy-protection schemes that do strange things with the disk. That dependence on software, as we'll see, has produced methods of copy protection that are unique to the Apple.

### Non-standard data formats


There are many methods of storing data in a non-standard format; we'll examine several in what follows. The most popular methods are these:

- Oddball track formatting
- Nibble counting
- Modified DOS
- Non-standard sectoring
- Unique data encryption
- Synchronized tracks
- Quarter tracks
- Spiral tracking

Of course, there are variations on those methods, and they're often used in combination. But attaining a good understanding of them will help you unravel any copy-protection scheme likely to come your way.

Those methods of copy protection are used on the Apple; due to differences in the IBM's disk-control hardware, it has fewer means of copy-protecting a disk. For example, the IBM cannot do quarter tracking. The most popular methods are:

- Oddball formatting
- Weak bits
- Laser burning

We'll examine those and other means of copy-protecting software next time. 



# 1987 ANNUAL INDEX

## Radio Electronics<sup>®</sup> Volume 58 and COMPUTER DIGEST Volume 4

Abbreviations: (AR)Antique Radio; (ARE) Ask Radio-Electronics; (AUD)Audio Update; (C)Construction; (COMC)Communications Corner; (D)Department; (DB)Drawing Board; (DN)Designers Notebook; (ED)Editorial; (ER)Equipment Report; (LTR)Letter; (NI)New Ideas; (PCS)PC Service; (SC)Service Clinic; (SQ)Service Questions; (SOSS)State Of Solid State; (STV)Satellite TV

### A

Acid Rain Monitor(C)(Scott) Apr 48  
Air Ionizers(ARE) Jun 10  
All About A-to-D Converters(Trietley) Feb 71  
**Amplifier**  
Transistor Design(Cunkelman) Aug 55  
Broadcast Band RF(NI)(Housley) Mar 42  
Another Attack on Home Taping(ED)(Home Recording Rights Coalition) Oct 4  
**Antennas**  
Marconi Lucked Out(COMC)(Friedman) Jun 82  
Antique Radio Clubs May 120  
**Antique Radios(D)(Fitch)** Jan 74, Feb 88, Mar 86  
Jun 80, Nov 39, (LTR) Sep 13  
Inventors and Inventions Mar 86  
Portables Jan 74  
Restoring a Classic Jun 80  
Restoring a Classic, Part 2 Nov 39  
The Telegraph and WWI Feb 88  
Arm, Robot(C)(Sarns) Oct 56  
Artificial Intelligence, The Future of(Heilmeier) May 85  
**Ask R-E(D)** Feb 12, Mar 12, Apr 8,  
May 10, Jun 10, Jul 7,  
Aug 8, Oct 10, Dec 15  
110-Volt Devices on 220? May 10  
CATV Lingo, Understanding Mar 12  
Crossover Networks Jul 7  
DC-to-DC Converter May 10  
Electronic Motor Controls Feb 12  
Helical Resonator Trap Mar 12  
Motor-Speed Control, More On Apr 8  
Optoelectronics Coupler, Using An Dec 15  
Pest Repellers, More On Mar 12  
Precedence Detector Dec 15  
Reversing Motors Oct 10  
Rhombic Antenna Impedance Oct 10  
SCA Decoder Jun 10  
Scanner, Booster for Mar 12  
S-Meter and Headphone Jack Dec 15  
Solid-State Tube Substitutes Apr 8  
Speakers Jul 7  
Stereo Spread Circuit Feb 12  
Sunrise Sunset Simulator Aug 8  
Timing Light Modification May 10  
Unloaded Vacuum-Tube Amplifiers Dec 15  
What's a Gate-Turnoff May 10  
A-to-D Converters, All About(Trietley) Feb 71  
Audible Logic Tester(NI)(Kane) Sep 32  
**Audio**  
Amplifier, Miniature Wideband(C)(Clawson) May 45  
**Audio Update(D)(Klein)** Jan 72, Feb 85,  
Mar 80, Apr 68, May 74,  
Jun 78, Aug 32, Oct 83,  
Nov 33, Dec 40  
Audio Answerman, The Aug 32  
Can You Believe Your Ears? Dec 40  
Joys of Equalization, The Feb 85  
Magnetically Shielded Loudspeakers Oct 83  
Psychoacoustics and Stereo Imagery Mar 80  
Resurgence of Surround Sound, The May 74  
Signal Processors Jan 72  
Stereo Spatial Imaging Nov 33  
Unwanted Sounds Jun 78  
Why Stereo Doesn't Work Apr 68  
Commercial Zapper for Your Radio(C)(Rumreich) Apr 45  
Digital Audio Tape(Fenton) Oct 45  
Great Installations(Vizard) Jul 39  
Great Systems(Vizard) Jul 31  
**Stereo**  
Imagery and Psychoacoustics(AUD)(Klein) Mar 80  
Spatial Imaging(AUD)(Klein) Nov 33

Spread Circuit(ARE)(Scott) Feb 12  
TV Decoder(C)(Templin) Jan 37, Feb 51, (PCS) Feb 79  
Why Stereo Doesn't Work(AUD)(Klein) Apr 68  
Why Digital Audio Tape Isn't Here(ED)(Fenton) Jun 4  
**Automotive**  
Automotive World of the 21st Century, The(Petersen) May 91  
**Digital**  
Speedometer for Your Car(C)(Ortman) Jul 47  
(PCS)Jul 79, (LTR)Nov 8  
Tachometer for Your Car(C)(Ortman) Jun 45  
(PCS)Jun 71, (LTR)Nov 8  
**Great**  
Installations(Vizard) Jul 39  
Systems(Vizard) Jul 31  
Avcom PSA-35A Portable Spectrum Analyzer(ER) Jul 15

Noise Isn't Always Bad Mar 44  
Think Ferrite May 127  
Turnable IF Jan 86  
Communications in 2001 The Third Age of Video (Ju Jice) May 102  
Inside Cellular Telephone(Bernard) Sep 53  
Compact Disc, Philips Test Set(ER) Feb 27  
**Computer**  
All About A-to-D Converters(Trietley) Feb 71  
Artificial Intelligence, The Future of(Heilmeier) May 85  
Computer Board, 80188-Based for R-E Robot (C) Sarns) Apr 39, (PCS) Apr 65, (PCS) May 67  
Orchid PCTurbo 286E IBM-PC Accelerator Card(ER) Feb 24  
Pencept Penpad 320(ER) Jan 22  
Conductive Inks and Adhesives(Mims) Nov 81

### B

Base Unit, R-E Robot(C)(Sarns) Mar 52  
**Battery**  
Backup for CMOS-Based Circuits(DN) (Grossblatt) Apr 79  
Over-Voltage Indicator(DN)(Grossblatt) Oct 10  
Using the Polapulse(Blechnan) Feb 61  
Beckman Industrial DM 800 DMM(ER) Jan 71  
**Biometal**  
Mondo-Tronics Space Wings Robotics Kit(ER) Oct 22  
Black Vertical Bars(Shane) Jun 70  
Blue Box and Ma Bell, The(Friedman) Nov 49  
Broadcast-Band RF Amplifier(NI)(Housley) Mar 42  
**Bulletin Board Service**  
Using the RE-BBS May 122  
Buyer's Guide to Camcorders(Vizard) Mar 47

Acid Rain Monitor(C)(Scott) Apr 48  
Amplifier, Miniature Wideband(C)(Clawson) May 45,  
(PCS) May 67  
Commercial Zapper for Your Radio(C)(Rumreich) Apr 45  
**Descrambling**  
Tri-Mode Cable-TV(C)(Coffell) Feb 43  
(LTR) May 13, (PCS) Feb 78  
TV Signal Descrambling(C)(Sheets and Graf) Jan 53,  
Mar 63, Jul 58, (PCS) Mar 73  
Digital Speedometer for Your Car(C)(Ortman) Jul 47,  
(PCS)Jul 79, (LTR)Nov 8  
Digital Tachometer for Your Car(C)(Ortman) Jun 45,  
(PCS)Jun 71, (LTR)Nov 8

### C

Camcorders, Buyer's Guide to(Vizard) Mar 47  
**Car Audio**  
**Great**  
Installations(Vizard) Jul 39  
Systems(Vizard) Jul 31  
Cassette Fidelity(LTR) Apr 12  
CATV Lingo, Understanding(ARE) Mar 12  
Cellular Telephone, Inside(Bernard) Sep 53  
Certification for Electronic Technicians(Small) Aug 52  
Clock Module, TSM 201 Nov 122  
CMOS Circuits, A Battery Backup For(DN) (Grossblatt) Apr 79  
**Color-Bar Generator**  
NCM's Video Wonderbox(ER) Nov 14  
Commercial Zapper for your Radio(C)(Rumreich) Apr 45  
**Communications**  
**Corner(D)(Friedman)** Jan 86, Feb 94, Mar 44,  
May 127, Jun 82, Oct 31  
Diversity Microphone Transmission Aug 26  
Image Interference Feb 94  
Light Makes the Perfect Wire Oct 31  
Marconi Lucked Out Jun 82

**Electronic**  
Digital Lock(C)(Renton) Nov 107  
Xmas Tree(C)(Jozwiak) Dec 47, (PCS) Dec 69  
IC Tester, In-Circuit Digital(C)(Green) Nov 43, Dec 55,  
(PCS) Dec 69  
Laser Listener(C)(Pearson) Oct 39, (LTR) Nov 8  
Macrovision Stabilizer(C)(Dupre) Dec 49, (PCS) Dec 69  
New Life for Old Car Radios(C)(McClellan) May 42,  
Jun 50, (PCS) Jun 71,  
(LTR) Jul 12, (LTR) Oct 15,  
Jan 57,  
Nov 57,  
Nov 87  
Nine-Station Intercom(C)(Morrison) (PCS) Jan 67  
Phonik Interactive Remote Control(C)(Roseth) May 39,  
Jun 53, (PCS) Jun 71  
R-E Robot(C)(Sarns) Jan 42, Feb 48, Mar 52,  
Apr 39, May 62, Jun 58,  
Jul 44, Aug 57, Sep 56,  
Oct 56, Dec 67,  
(LTR) Jul 12, (LTR) Oct 15  
(PCS) Apr 65, (PCS) May 67  
SCA FM-Stereo Receiver(C)(Sheets and Graf) Aug 39,  
Sep 46, (LTR) Oct 15  
(PCS) Sep 69  
SMT Project Business-Card Tone Generator(C)(Mims) Nov 85  
SMT Project I-R Remote on a Keychain(C)(Mims) Nov 77  
SMT Project LED Flasher(C)(Mims) Nov 73  
SMT Project Light Meter(C)(Mims) Nov 75  
Stereo TV Decoder(C)(Templin) Jan 37, Feb 51  
Versatile Digital Timer(C)(Ortman) Aug 45  
Video Effects Generator(C) (Sheets and Graf) Sep 41, Oct 48  
(PCS) Oct 75  
Crossover Networks(ARE)(Scott) Jul 7

### D

Data Sheets of RF Power Transistors, Understanding(Dye) Nov 109

- DC-to-DC Converter(ARE) May 10  
Dear Sue...(Oliver) May 84  
Decoder, Stereo TV(C)(Templin) Feb 51, (PCS) Feb 79  
Delay Circuit, A Very Simple(DN)(Grossblatt) Sep 34  
**Designer's Notebook(D)(Grossblatt)**  
Battery Backup for CMOS-Based Circuits, A Apr 79  
CMOS Oscillator, A Simple Feb 96  
Delay Circuits, Very Simple Sep 34  
Logic-Family Translation Aug 30  
Over-Voltage Indicator Oct 101  
Trigger Pulses May 121  
Under-Voltage Monitor, An Nov 41  
**Descrambling**  
Practical Descrambling(STV)(Cooper) Feb 83  
Tri-Mode Cable-TV Scrambling(C)(Coffell) Feb 43,  
(PCS) Feb 79, (LTR) May 13  
TV Signal Descrambling(C)  
(Sheets and Graf) Jan 53, Jul 58  
Why Videocipher is Dead(STV)(Cooper) Mar 78  
Zombies, Zits, and Zoweee(STV)(Cooper) May 77  
**Digital**  
**Audio Tape**  
Another Attack on Home Taping(ED)(Home  
Recording Rights Coalition) Oct 4  
Digital Audio Tape(Fenton) Oct 45  
Why Digital Audio Tape Isn't Here(ED)(Fenton) Jun 4  
**Circuitry**  
Logic-Gate Fundamentals(Marston) Apr 50  
Flip-Flops, Working With(Marston) Jun 64  
In-Circuit IC Tester Nov 43, Dec 55, (PCS) Dec 69  
Multimeter(SEE TEST EQUIPMENT)  
Speedometer for Your Car(C)(Ortman) Jul 47,  
(PCS) Jul 79, (LTR) Nov 8  
Tachometer for Your Car(C)(Ortman) Jun 45,  
(PCS) Jun 71, (LTR) Nov 8  
Timer, Versatile(C)(Ortman) Aug 45, (PCS) Aug 75  
**Drawing Board(D)(Grossblatt)** Jan 82, Mar 82,  
Apr 76, May 123,  
Jul 26, Dec 77  
Designer RAM  
DTMF Receiver, A Mar 82  
Dynamic Memory Jul 26  
Output Decoder, An Apr 76  
Remote Control Transmitter  
Which Memory? Jan 82  
May 123  
Drive System, R-E Robot(C)(Sarns) Feb 48, Mar 52  
**DTMF**  
Receiver, A(DB)(Grossblatt) Mar 82  
Transmitter-Receiver Output Decoder, An(DB)  
(Grossblatt) Apr 76  
**E**  
Early Days of Radio, The(Clifford) Apr 59, Jul 52, Dec 64  
Editorial(D) Jan 12, May 4, Jun 4,  
Oct 4, Dec 4  
Another Attack on Home Taping(Home  
Recording Rights Coalition) Oct 4  
Home Appliances(Kleiman) Jan 12  
Welcome to the Twenty-First Century(Fenton) May 4  
Why Digital Audio Tape Isn't Here(Fenton) Jun 4  
**EEPROM's**  
Non-Volatile Memory IC's(Grossblatt) Oct 60  
**Electronic**  
Digital Lock(C)(Renton) Nov 107  
Christmas Tree(C)(Jozwiak) Dec 47, (PCS) Dec 69  
Eye, R-E Robot(C)(Sarns) Dec 67  
Motor Controls(ARE)(Scott) Feb 12  
**Energy**  
Storage in 2001: Superconductivity(LTR) Jun 14  
Technology in the 21st Century(Kuznetsov) May 107  
**Equipment Reports(D)** Jan 22, Feb 24, Mar 28,  
Apr 24, May 24, Jun 21,  
Jul 15, Aug 16, Sep 22,  
Oct 22, Nov 14, Dec 35  
Avcom PSA-35A Portable Spectrum Analyzer Jul 15  
Beckman Industrial DM 800 DMM Jan 71  
Fluke LCA-10 Line Current Test Adapter Mar 28  
Leader LCD-100 Portable DMM Storage  
Oscilloscope Jun 21  
Mark V Professional Color Light Controller Dec 35  
Mondo-Tronics Space Wings Robotics Kit Oct 22  
NCM's Video Wonderbox Nov 14  
Onkyo Unifler Universal Programmable  
Remote Control Sep 22  
Orchid PCTurbo 286E IBMM-PC Accelerator  
Card Feb 24  
Pencept Penpad 320 Jan 22  
Philips Compact Disc Test Set Feb 27  
Regency Informant Scanning Receiver Aug 16  
Sencore LC75 "Z Meter II" Apr 24  
TI/P-CAD PAL Starter Kit Mar 32  
Universal Wireless Remote-Control/Stereo  
TV Tuner May 24  
Evolution of VHSIC, The(Grossblatt) Mar 59  
**F**  
**Fiber Optics**  
Light Makes the Perfect Wire(COMC)(Friedman) Oct 31  
Finding Cable Faults(Martin) Mar 66  
Flasher, Sequential(NI)(Circ) Feb 36  
Flip-Flops, Working With(Marston) Jun 64, (LTR) Oct 15  
Fluke LCA-10 Line Current Test Adapter(ER) Mar 28  
FM Commercial Zapper for Your  
Radio(C)(Rumreich) Apr 45, (LTR) Sep 13  
Future of Artificial Intelligence, The(Heilmeyer) May 85  
**G**  
Gated-Pulse Decoder(C)(Sheets and Graf) Jan 53,  
(PCS) Mar 73, (LTR) Apr 12  
Gravity Waves(LTR) Jan 18  
**Great**  
Installations(Vizard) Jul 39  
Systems(Vizard) Jul 31  
**H**  
Hand-Soldering SMC's(Mims) Nov 71  
Headlight Alarm(NI)(Lowell) Apr 67  
Helical Resonator Trap(ARE) Mar 12  
**HDTV**  
High-Definition DBS(STV)(Cooper) Jul 62  
Is HDTV the Key to an International  
Standard?(STV)(Cooper) Aug 28  
High Definition TV(Bernard) Aug 48  
**History(See also ANTIQUE RADIO)**  
Early Days of Radio, The(Clifford) Apr 59, Jul 52, Dec 64  
**Home**  
Appliances(ED)(Kleiman) Jan 12  
Of the Future, The(MacFadyen) May 115  
**How to**  
Analyze Waveforms(Carey) Dec 59  
Apply For a Patent(Sweeney) Jan 48, (LTR) Apr 12,  
May 13  
Design Oscillator Circuits(Carr) Jan 65, (LTR) Mar 16  
Humidity Monitor(LTR) Jan 18  
**I**  
IC Tester, Digital In-Circuit(C)(Green) Nov 43, Dec 55,  
(PCS) Dec 69  
I-R Remote on a Keychain, SMT Project(C)(Mims) Nov 77  
Industrial SMT Assembly(Mims) Nov 65  
**Inside**  
Cellular Telephone(Bernard) Sep 53  
The Telephone(LTR) Feb 16, (LTR) Mar 16  
Introduction to SMT(Mims) Nov 59  
**K**  
Kit Report: TSM 201 Clock Module Nov 122  
**L**  
Laser Listener(C)(Pearson) Oct 39, (LTR) Nov 8  
Latching Continuity Tester(LTR) Jan 18  
Leader LCD-100 Portable DMM Storage  
Oscilloscope(ER) Jun 21  
LED Flasher, SMT Project(C)(Mims) Nov 73  
**Letters(D)** Jan 18, Feb 16, Mar 16,  
Apr 12, May 13, Jun 14,  
Jul 12, Aug 12, Sep 13,  
Oct 15, Nov 8, Dec 24  
**Light**  
Controller, Outdoor(NI)(Holke) Oct 104  
Color Controller, Mark V(ER) Dec 35  
Meter, SMT Project(C)(Mims) Nov 75  
Lock, Electronic Digital(C)(Renton) Nov 107  
Logic-Family Translation(DN)(Grossblatt) Aug 30  
Logic-Gate Fundamentals(Marston) Apr 50  
Logic Tester, Audible(NI)(Kane) Sep 32  
Looking Into the Future(Clarke) May 81  
LORAN, Learning About(Sweeney) May 5  
**M**  
Macrovision Stabilizer(C)(Dupre) Dec 49, (PCS) Dec 69  
Mark V Professional Color Light Controller(ER) Dec 35  
**Medical Technology in the 21st Century(Fish)** May 112  
Miniature Wideband Amplifier(C)  
(Clawson) May 45, (PCS) May 67  
Mondo-Tronics Space Wings Robotics Kit(ER) Oct 22  
Monitor, Acid Rain(C)(Scott) Apr 48  
Multi-Tone Generator, Simple(NI)(Khan) Nov 31  
**N**  
NCM's Video Wonderbox(ER) Nov 14  
**New**  
**Ideas(D)** Feb 36, Mar 42, Apr 67, Jun 40,  
Sep 32, Oct 104, Nov 31  
Audible Logic Tester(Kane) Sep 32  
Broadcast-Band RF Amplifier(Housley) Mar 42  
Headlight Alarm(Lowell) Apr 67  
Outdoor Light Controller(Holke) Oct 104  
Sequential Flasher(Circ) Feb 36  
Simple Multi-Tone Generator(Khan) Nov 31  
Sound-Effects Generator(Tupue) Jun 40  
Life for Old Car Radios(C)(McClellan) May 42, Jun 50,  
(PCS) Jun 71, (LTR) Jul 12,  
(LTR) Oct 15  
**LiI(D)** Aug 21, Sep 31  
**Products(D)** Jan 30, Feb 34, Mar 36,  
Apr 30, May 30, Jun 30,  
Jul 21, Aug 24, Sep 24,  
Oct 26, Nov 22, Dec 32  
Nine-Station Intercom(C)(Morrison) Jan 57, (PCS) Jan 67  
Non-Volatile Memory IC's(Grossblatt) Oct 60  
**O**  
On Electrons(LTR) Jun 14  
110-Volt Devices on 220?(ARE) May 10  
Onkyo Unifler Universal Programmable  
Remote Control(ER) Sep 22  
Op-Amp, Micropower(SOSS)(Scott) Sep 94  
Orchid Technology PCTurbo 286E IBM-PC  
Accelerator Card(ER) Feb 24  
Oscillator, A Simple CMOS(DN)(Grossblatt) Feb 96  
Oscilloscopes(See TEST EQUIPMENT)  
Out-Band Decoder(C)(Sheets and Graf) Mar 83,  
(PCS) Mar 73  
Outdoor Light Controller(NI)(Holke) Oct 104  
Output Decoder, An(DB)(Grossblatt) Apr 76  
Over-Voltage Indicator(DN)(Grossblatt) Oct 101  
**P**  
PC Boards, Making(LTR) Nov 8  
**PC Service(D)** Jan 67, Feb 78, Mar 73,  
Apr 65, May 67, Jun 71,  
Jul 79, Aug 75, Sep 69,  
Oct 75, Nov 127, Dec 69  
Patent, How to Apply For A (Sweeney) Jan 48, (LTR) Aug 12  
Pencept Penpad 320(ER) Jan 22  
Personal Computer, R-E Robot(C)(Sarns) Jan 42  
Pest Repellers, More on(ARE) Mar 12  
Philips Compact Disc Test Set(ER) Feb 27  
Phonlink Interactive Remote Control(C)  
(Roseth) May 39,  
Jun 53, (PCS) Jun 71  
Piezoelectric Plastic Film(Iovine) Mar 57  
Polapulse Battery, Using the(Blechman) Feb 61  
Poor Man's Storage Scope(Bernard) Nov 113  
Programmable Array Logic  
TI P-CAD PAL Starter Kit(ER) Mar 32  
**R**  
**Radio(see also ANTIQUE RADIOS, COMMUNICATIONS**  
**CORNER)**  
Antique Radio Clubs, Listing May 120  
Commercial Zapper for Your Radio(C)(Rumreich) Apr 45  
Early Days of Radio, The(Clifford) Apr 59, Jul 52, Dec 64  
LORAN, Learning About(Sweeney) May 51  
Life for Old Car Radios(C)(McClellan) May 42, Jun 50,  
(PCS) Jun 71, (LTR) Jul 12,  
(LTR) Oct 15  
Razor-Blade Radio (LTR) Apr 12, (LTR) Jul 12  
Regency Informant Scanning Receiver(ER) Aug 16  
SCA FM-Stereo Receiver(C)(Sheets and Graf) Aug 39,  
Sep 46, (PCS) Sep 69  
Spread Spectrum Communications,  
All About(McDermott) Apr 55  
**RAM**  
Which Memory?(DB)(Grossblatt) May 123  
Dynamic Memory(DB)(Grossblatt) Jul 26  
**R-E Robot(C)(Sarns)** Jan 42, Feb 48, Mar 52,  
Apr 39, May 62, Jun 58,  
Jul 44, Aug 57, Sep 56,  
Oct 56, (LTR) Jul 12,  
(LTR) Oct 15, (PCS) Apr 65,  
(PCS) May 67, (PCS) Dec 69  
R-E BBS, Using the Mar 83, May 122  
Regency Informant Scanning Receiver(C) Aug 16  
**Remote Control**  
Phonlink Interactive(C)(Roseth) May 39, Jun 53,  
(PCS) Jun 71  
DTMF Receiver, A(DB)(Grossblatt) Mar 82  
Remote Control Transmitter(DB)(Grossblatt) Jan 82  
Reversing Motors (LTR) May 13, (ARE) Oct 10  
RFI, The Reasons Behind(LTR) Mar 16  
Rhombic Antenna Impedance(ARE) Oct 10  
**Robotics**  
**Kit**  
Mondo-Tronics Space Wings(ER) Oct 22  
**R-E Robot**  
Applications(C)(Sarns) Sep 56  
Brain(C)(Sarns) Jan 42  
Command Language(C)(Sarns) Aug 57  
Control Board(C)(Sarns) Jul 44  
Control Electronics(C)(Sarns) Jun 58  
Electronic Eye(C)(Sarns) Dec 67  
Personal Computer(C)(Sarns) Apr 39, (PCS) Apr 65,  
May 67  
Robot in the 21st Century, The(Asimov) May 99

# S

<b>Satellite TV(D)(Cooper)</b>	Jan 4, Feb 83, Mar 78, May 77, Jul 62, Aug 28, Sep 87, Oct 80, Dec 74	Feb 16, Nov 81, Nov 71, Nov 65, Nov 59
High-Definition DBS	Jul 62	Nov 85
International Connection. The Is HDTV the Key to an International Standard?	Sep 87, Oct 80	Nov 77
Practical Descrambling	Aug 28	Nov 73
Videocipher Has Been Cracked	Feb 83	Nov 75
What's Next	Jan 4	Nov 89
Why Videocipher is Dead	Dec 74	Nov 32
Zits Fraud, The	Mar 78	May 74
Zombies, Zits, and Zoweee!	Jan 76, May 77	
<b>SCA</b>		
Decoder(ARE)	Jun 10	
FM-Stereo Receiver(C)(Sheets and Graf)	Aug 39, Sep 46, (PCS) Sep 69	
	(LTR) Oct 15	
<b>SCR's</b>		
Using Tracs and SCR's(Marston)	Sep 64	
Working with Tracs and SCR's(Marston)	Oct 64	
<b>Scanner</b>		
Booster for(ARE)	Mar 12	
Regency Informant Scanning Receiver(C)	Aug 16	
Seismic Discussion Net(LTR)	May 13	
Semiconductors, Testing(Byers)	Feb 58, Mar 71, Apr 62, May 59, Jun 61, Aug 12, Sep 61, Nov 115	
	(LTR) Aug 12, (LTR) Nov 8	
Sendore LC75 Z Meter II(ER)	Apr 24	
Sequential Flasher(NI)(Circic)	Feb 36	
<b>Service</b>		
<b>Clinic(D)(Darr)</b>	Jan 88, May 125, Sep 30	
Funny Pictures	May 125	
Leakage and Psychology	Jan 88	
Quirks and Querries	Sep 30	
<b>Questions(D)(Darr)</b>	Jan 90	
Log: Surface-Mount Components(Poe)	Nov 32	
<b>Shortwave Converter</b>		
New Life for Old Car Radios(C)(McClellan)	May 42, Jun 50, (PCS) Jun 71, (LTR) Jul 12, (LTR) Oct 15	
Simple Multi-Tone Generator(NI)(Khan)	Nov 31	
<b>Smart House</b>		
Home of the Future. The(MacFadyen)	May 115	
<b>SMT Projects(See SURFACE MOUNT TECHNOLOGY)</b>		
Soldering: Old Techniques and New Technology(Martin)	May 47, (LTR) Aug 12, (LTR) Sep 13	
<b>Solid-State (See also STATE OF SOLID STATE)</b>		
Technology in the 21st Century(Gregory)	May 97	
Tube Substitutes(ARE)	Apr 8	
Sound-Effects Generator(NI)(Tupue)	Jun 40	
<b>Soundproofing</b>		
Unwanted Sounds(AUD)(Klein)	Jun 78	
Speakers, Magnetically Shielded(AUD)(Klein)	Oct 83	
Spectrum Analyzer, Portable(See TEST EQUIPMENT)		
Speedometer, Digital(C)(Ortman)	Jul 47, (PCS) Jul 79, (LTR) Nov 8	
Spread Spectrum Communications, All About(McDermott)	Apr 55	
<b>State of Solid State(D)(Scott)</b>	Feb 92, Mar 84, Apr 80, May 129, Jun 87, Sep 94, Nov 124, Dec 42	
Bang-Bang IC. A Electronic Potentiometer, An Instrumentation Amplifiers	Nov 124, Dec 42	
Long-Time Timer	Jun 87	
Micropower Op-Amp	May 129	
Temperature Transducer	Sep 94	
Tone Generator IC's	Mar 84	
Transformerless 5-Volt Regulator	Apr 80, Feb 92	
<b>Stereo(See also AUDIO)</b>		
Imagery and Psychoacoustics(AUD)(Klein)	Mar 80	
Spatial Imaging(AUD)(Klein)	Nov 33	
Spread Circuit(ARE)(Scott)	Feb 12	
TV Decoder(C)(Templin)	Jan 37, Feb 51	
Why Stereo Doesn't Work(AUD)(Klein)	Apr 68	

Strain-Gage Transducers(Wood)	Dec 61
Sunrise Sunset Simulator(ARE)(Scott)	Aug 8
<b>Surface-Mount Technology</b>	
Surface-Mounted Components(LTR)	Feb 16
Conductive Inks and Adhesives(Mims)	Nov 81
Hand-Soldering SMC's(Mims)	Nov 71
Industrial SMT Assembly(Mims)	Nov 65
Introduction to SMT(Mims)	Nov 59
<b>SMT Project</b>	
Business-Card Tone Generator(C)(Mims)	Nov 85
I-R Remote on a Keychain(C)(Mims)	Nov 77
LED Flasher(C)(Mims)	Nov 73
Light Meter(C)(Mims)	Nov 75
Resource Directory	Nov 89
Service Log(Poe)	Nov 32
Surround Sound, Resurgence of(AUD)(Klein)	May 74

# T

Telegraph, and WWII(AR)(Fitch)	Feb 88
<b>Telephone</b>	
Blue Box and Ma Bell, The(Friedman)	Nov 49
Inside Cellular Telephone(Bernard)	Sep 53
Nine-Station Intercom(C)(Morrison)	Jan 57, (PCS) Jan 67
Phonlink Interactive Remote Control(C)(Roseth)	May 39, Jun 53, (PCS) Jun 71
Television(See VIDEO)	
Tesla, Father of Radio	(LTR) Jun 14
<b>Test Equipment</b>	
Avcom PSA-35A Portable Spectrum Analyzer(ER)	Jul 15
Beckman Industrial DM 800 DMM(ER)	Jan 71
Finding Cable Faults(Marin)	Mar 66
Fluke LCA-10 Line Current Test Adapter(ER)	Mar 28
How to Analyze Waveforms(Carey)	Dec 59
In-Circuit Digital IC Tester(C)(Green)	Nov 43
Leader LCD-100 Portable DMM	Jun 21
Storage Oscilloscope(ER)	Nov 14
NCM's Video Wonderbox(ER)	Nov 14
Oscilloscopes, Using the New Generation(Diller)	Feb 55
Philips Compact Disc Test Set(ER)	Feb 27
Poor Man's Storage Scope(Bernard)	Nov 113
Sendore LC75 Z Meter II(ER)	Apr 24
Temperature Transducer(SOSS)(Scott)	Mar 84
Testing Semiconductor(Byers)	Feb 58, Mar 71, Apr 62, May 59, Jun 61, Aug 12, Sep 61, Nov 115
	(LTR) Aug 12, (LTR) Nov 8
TIP-CAD PAL Starter Kit(ER)	Mar 32
Timer, Versatile Digital(C)(Ortman)	Aug 45, (PCS) Aug 75
Timing Light Modification(ARE)	May 10
Tone Generator IC's(SOSS)(Scott)	Apr 80
Tool Organizer, Maszota(LTR)	Mar 16
Transducers, Strain-Gage(Wood)	Dec 61
Transformerless 5-Volt Regulator(SOSS)(Scott)	Feb 92
Transistor Amplifier Design(Cunkelman)	Aug 55
<b>Triacs</b>	
Using Triacs and SCR's(Marston)	Sep 64
Working With Triacs and SCR's(Marston)	Oct 64
Tri-Mode Cable-TV Scrambling(C)(Coffell)	Feb 43, (PCS) Feb 78, (LTR) May 13
Trigger Pulses(DN)(Grossblatt)	May 121
TSM 201 Clock Module	Nov 122
Tunable IF(COMC)(Friedman)	Jan 86
TV Signal Descrambling(C)(Sheets and Graf)	Jan 53, Mar 63, Jul 58
<b>2001</b>	
Automotive World of the 21st Century. The(Petersen)	May 91
Communications in 2001: The Third Age of Video(Judice)	May 102
Dear Sue....(Oliver)	May 84
Energy Technology in the 21st Century(Kuznetsov)	May 107
Home of the Future. The(MacFadyen)	May 115

Looking Into the Future(Clarke)	May 81
Medical Technology in the 21st Century(Fish)	May 112
Robot in the 21st Century. The(Asimov)	May 99
Solid-State Technology in The 21st Century(Gregory)	May 97
Future of Artificial Intelligence. The(Helmeier)	May 85
Welcome to the Twenty-First Century(ED)(Fenton)	May 4

# U

Under-Voltage Monitor, An(DN)(Grossblatt)	Nov 41
Understanding Data Sheets of RF Power Transistors(Dye)	Nov 104
Universal Wireless Remote Control/Stereo TV Tuner(ER)	May 24
<b>Using</b>	
New Generation Oscilloscopes. The(Diller)	Feb 55
Polapulse Battery. The(Blechman)	Feb 61, (LTR) Jun 14
RE-BBS. The	May 122
Triacs and SCR's(Marston)	Sep 64

# V

Vacuum Tubes(LTR)	Feb 16
Versatile Digital Timer(C)(Ortman)	Aug 45, (PCS) Aug 75
VHSIC. The Evolution of(Grossblatt)	Mar 59
<b>Video</b>	
Communications in 2001-The Third Age of Video(Judice)	May 102
Black Vertical Bars(Shane)	Jun 70
Buyer's Guide to Camcorders(Vizard)	Mar 47
Effects Generator(C)(Sheets and Graf)	Sep 41, Oct 48, (PCS) Oct 75
Palette(C)(Sheets and Graf)	Sep 41, Oct 43, (PCS) Oct 75
High Definition TV(Bernard)	Aug 48
<b>News(D)(Lachenbruch)</b>	Jan 16, Feb 6, Mar 6, Apr 7, May 8, Jun 8, Jul 6, Aug 6, Sep 6, Oct 6, Nov 6, Dec 12
	Jan 37, Feb 51, Feb 43, (PCS) Feb 79, (LTR) May 13
TV Signal Descrambling(C)(Sheets and Graf)	Jan 53, Mar 63, (PCS) Mar 73, Jul 58
Universal Wireless Remote Control/Stereo TV Tuner(ER)	May 24
VHSIC. The Evolution of(Grossblatt)	Mar 59
<b>Videocipher</b>	
Practical Descrambling(STV)(Cooper)	Feb 83
The Zits Fraud(STV)(Cooper)	Jun 76
Videocipher Has Been Cracked(STV)(Cooper)	Jan 4
Why Videocipher is Dead(STV)(Cooper)	Mar 78
Zombies, Zits, and Zowee!(STV)(Cooper)	May 77
Voltage Transformers(LTR)	Aug 12

# W

Waveforms, How to Analyze(Carey)	Dec 59
Welcome to the Twenty-First Century(ED)(Fenton)	May 4
<b>What's</b>	
A Gate-Turnoff Rectifier?(ARE)	May 10
New in Solid State(Scott)	Jan 14, Feb 4, Mar 4, Apr 4, May 6, Jun 6, Jul 5, Aug 4, Sep 4, Nov 4, Dec 6
<b>News(D)</b>	Jan 14, Feb 4, Mar 4, Apr 4, May 6, Jun 6, Jul 5, Aug 4, Sep 4, Nov 4, Dec 6
Working With Tracs and SCR's(Marston)	Oct 64

# COMPUTER DIGEST Volume 4

January 1987 — December 1987

Abbreviations: (C)Construction; (D)Department; (Ed)Editorial; (EW)Editor's Workbench; (HWR)Hardware Review; (LTR)Letter; (SWR)Software Review

## A

Add a Disk Drive(Friedman)(C) Apr 96  
All About Interfacing Part 2 (Holtzman) Jan 13  
Apparat Limbo II(EW) Mar 94

## B

Biofeedback(L) Feb 102  
Books(EW) May 137, Nov 93  
Brooklyn Bridge(EW) Sep 74  
**Build**  
Clock Board for Your PC. A(C)(Martin) Mar 97  
MC68000. The(C)(Schrader, Koenig, Voelzke) Mar 101  
PT-68K. The(C)(Stark) Oct 90

## C

**CAD**  
Computer-Assisted Regulator Design (Cunckelman) Feb 110  
Designing PC Boards on Your Computer (Grossblatt) Jun 97  
Aug 69  
CD-ROM (EW) Mar 94, (EW) Mar 95, (EW) Apr 90  
Cauzin Softstrip System, The(Holtzman) Apr 93  
Central Point Software: The Option Board(EW) Oct 87  
Certificate Maker(SWR) Feb 103

**Clock**  
Board for Your PC (C)(Martin) Mar 97, (PCS) Mar 73  
Circuit for the PT-68K(C)(Stark) Nov 101

**Clones**  
IBM-Compatible Clone Computer(C)(Flack) Feb 104  
COMDEX Report(EW) Sep 73  
Commodore Pulse Generator(C)(Barbarelo) Oct 96  
CompDes(EW) May 136  
Computer Products(D) Jan 4, Feb 102  
Computer-Assisted Regulator Design(Cunckelman) Feb 110

**Computer-Controlled Robot(C)**  
(Barbarelo) May 144, (PCS) May 67  
Concurrency(Stern) Feb 112

**Construction**  
Add a Disk Drive(C) (Friedman) Apr 96  
Clock Board for Your PC (C)(Martin) Mar 97, (PCS) Mar 73  
Commodore Pulse Generator(C)(Barbarelo) Oct 96  
Computer-Controlled Robot(C) (Barbarelo) May 144, (PCS) May 67  
IBM Incompatible, Build This(C)(Holtzman) Apr 98  
MC68000, Build The(C) (Schrader, Koenig, Voelzke) Mar 101, May 138  
Micro-Floppy Retrofit(C)(Friedman) Aug 67  
PT-68K. Build the(C)(Stark) Oct 90, Nov 101, Dec 95

**Copy Protection**  
The Beginning of the End (ED)(Wels) Jan 3

## D

Data Storage. Floppy-Disk(Grossblatt) Dec 91  
**Debugging(EW)**  
T-DebugPlus(EW) Dec 87  
Turbo Pascal(EW) Dec 87  
TurboSmith(EW) Dec 87  
Designing PC Boards on Your Computer(Grossblatt) Jun 97, Aug 69  
Direc-Link(EW) Sep 74  
Do Me a Favor (ED)(Wels) Feb 101

## E

**Editorial**  
Do Me a Favor...(ED)(Wels) Feb 101  
The Beginning of the End...(ED)(Wels) Jan 3  
**Editor's Workbench**  
Mar 93, Apr 85, May 135, Jun 93, Jul 66, Aug 63, Sep 73, Oct 87, Nov 93, Dec 87  
Apparat Limbo II Mar 94  
Books May 137, Nov 93  
Brooklyn Bridge Sep 74  
CD-ROM Mar 94, Mar 95, Apr 90  
Central Point Software: The Option Board Oct 87  
COMDEX Report Sep 73  
CompDes May 136  
Debugging Dec 87  
Direc-Link Sep 74  
Graphics Sep 73  
Groler's Electronic Encyclopedia Apr 90  
Hardware Reviews Mar 93  
Healthkit SK-203 Printer Buffer Sep 76

Hercules Graphics Card Plus IBM Apr 85  
Models 30 and 50 PCs Aug 63  
Operating Systems: The M&M's Personal System 2 Jun 93  
Keyboards Jul 66  
Masters' Visible Computer: 8088 Jun 95  
Memory Expansion Mar 93  
Microsolutions' Matchpoint Jun 94  
Mycroft Labs' Mile Oct 88  
Orchid's Conquest Mar 93  
PC-Sigs  
Command-Line Editor Mar 95  
PC-Outline Mar 94  
PS 2 Sep 73  
Portable Computers(Holtzman) Nov 93  
Product Reviews Mar 96, Apr 92, Jun 96, Oct 89, Nov 94  
68000 Update Aug 63  
T-DebugPlus Dec 87  
Tseng Lab's EVA 480 May 135  
Turbo Pascal Dec 87  
TurboSmith Dec 87  
Vercomp's Breakthru(PC) Mar 94

5-Volt Only: The Max 232(Kreuter) Jan 10  
From Keypress to Scan Code(Holtzman) Jul 70

## F

## G

Graphics(EW) Sep 73  
Graphics Co-Processors(Bernard) Sep 82  
Groler's Electronic Encyclopedia(EW) Apr 90

## H

**Hardware**  
Add a Disk Drive(C)(Friedman) Apr 96  
All About Interfacing Part 2(Holtzman) Jan 13  
Build the MC68000(C) (Schrader, Koenig, Voelzke) Mar 101, May 138  
Build the PT-68K(C)(Stark) Oct 90, Nov 101, Dec 95  
Cauzin Softstrip System, The(Holtzman) Apr 93  
Commodore Pulse Generator(C)(Barbarelo) Oct 96  
Concurrency(Stern) Feb 112  
Editor's Workbench(EW) Mar 93  
Graphics Co-Processors(Bernard) Sep 82  
IBM-Compatible Clone Computer(C)(Flack) Feb 104  
IBM Incompatible, Build This(C)(Holtzman) Apr 98  
Floppy-Disk Data Storage(Grossblatt) Dec 91  
MC68000, Build the(C) (Schrader, Koenig, Voelzke) Mar 101, May 138  
Micro-Floppy Retrofit(C)(Friedman) Aug 67  
Portable Computers(Holtzman) Sep 77  
Healthkit SK-203 Printer Buffer(EW) Sep 76  
Hercules Graphics Card Plus(EW) Apr 85

## I

**IBM**  
-Compatible Clone Computer(C)(Flack) Feb 104  
-Incompatible, Build This(C)(Holtzman) Apr 98  
Models 30 and 50 PCs(EW) Aug 63  
Operating Systems: The M&M's(EW) Jun 93  
Personal System 2(EW) Jul 66  
Interfacing. All About: Part 2(Holtzman) Jan 13

## J

J&M's Memory Minder(EW) Aug 63

## K

**Keyboards**  
Editor's Workbench Jul 66  
From Keypress to Scan Code(Holtzman) Jul 70  
Working with Surplus Keyboards(Grossblatt) Jul 74  
Keptom, The(Holtzman) Jun 100

## L

**Letters(D)**  
Jan 4, Feb 102  
Look Inside the 6502. A(Solomon) May 141

## M

Max 232: 5-Volt Only(Kreuter) Jan 10  
MC68000. Build the(C) (Schrader, Koenig, Voelzke) Mar 101, May 138  
Memory Expansion(EW) Mar 93  
Micro-Floppy Retrofit(C)(Friedman) Aug 67  
Microsolutions' Matchpoint(EW) Jun 94  
**Multitasking**  
Concurrency(Stern) Feb 112  
Mycroft Labs' Mile(EW) Oct 88

## O

Orchid's Conquest(EW) Mar 93

## P

PC Boards, Designing on Your Computer(Grossblatt) Jun 97  
PC-Sigs  
Command-Line Editor(EW) Mar 95  
PC-Outline(EW) Mar 94  
Periscope Software(EW) Dec 87  
Portable Computers(Holtzman) Sep 77, (EW) Nov 93  
Product Reviews(EW) Mar 96, Apr 92, Jun 96, Oct 89, Nov 94

**Programs**  
Commodore Pulse Generator(C)(Barbarelo) Oct 96  
Computer-Assisted Regulator Design (Cunckelman) Feb 110  
TV Channel Frequency Program(Kiley) Jan 12  
TVRO Antenna Pointer(Tyson) PS 2(EW) Sep 73  
PT-68K, Build the(C)(Stark) Oct 90, Nov 101, Dec 95

## R

Robot, Computer-Controlled(C) (Barbarelo) May 144, (PCS) May 67

## S

**Software**  
Editor's Workbench Mar 94, Apr 90, May 136, Jun 93, Aug 63, Sep 74, Oct 88, Nov 93, Dec 87  
Designing PC Boards on Your Computer: Part 2(Grossblatt) Aug 69  
Masters' Visible Computer: 8088(EW) Jun 95  
Periscope(EW) Dec 87  
Pirates, Sinking the(Holtzman) Jun 100  
Review(D) Jan 5, Feb 103  
Certificate Maker(SWR) Feb 103  
Webster's On-Line Thesaurus(SWR) Jan 5

**6800**  
MC68000. Build the(C) (Schrader, Koenig, Voelzke) Mar 101, May 138  
PT-68K. Build the(C)(Stark) Oct 90, Nov 101, Dec 95  
68K Update(EW) Aug 63  
6502. A Look Inside the(Solomon) May 141

## T

**Test Equipment**  
Commodore Pulse Generator(C)(Barbarelo) Oct 96  
Tseng Lab's EVA480(EW) May 135  
TV Channel Frequency Program(Kiley) Jan 12  
TVRO Antenna Pointer Program(C)(Tyson) Jan 6

## V

Vercomp's Breakthru PC(EW) Mar 94

## W

Webster's On-Line Thesaurus(SWR) Jan 5  
Working with Surplus Keyboards(Grossblatt) Jul 74

# MARKET CENTER

## FOR SALE

**REPAIR your own TV...it's easy.** Write RESEARCH, Rt. 3, Box 601BR, Colville, WA 99114.

**CIRCUIT boards, kits, & assemblies** for QST magazine articles. For price list SASE to: A & A ENGINEERING, 2521 W. La Palma Ave., Anaheim, CA 92801. (714) 952-2114.

**RESTRICTED technical information:** Electronic surveillance, schematics, locksmithing, covert sciences, hacking, etc. **Huge selection. Free brochure.** MENTOR-Z, 135-53 No. Blvd., Flushing, NY 11354.

**TV tunable notch filters, free brochure.** D.K. VIDEO, Box 63 6025, Margate, FL 33063. (305) 752-9202.

**DESCRAMBLER catalog.** All brands Special combo Jerrold 400 and SB3 \$165. Descrambler kit \$39.00 (assembles in half hour) Send \$1.00. **MJ INDUS\*RY**, Box 531, Bronx, NY 10461.

**IS it true...Jeeps for \$44 through the government?** Call for facts! 1 (312) 742-1142, ext. 4673.

**OLDTIME radio programs** on high quality tapes. Comedy! Adventure! Music! Free catalog. **CARL F. FROELICH**, Heritage Farm, New Freedom, PA 17349.

**TEST equipment, reconditioned.** For sale. \$1.25 for catalog **WALTER'S**, 2697 Nickel, San Pablo, CA 94806. (415) 724-0587.

## CLASSIFIED AD ORDER FORM

To run your own classified ad, put one word on each of the lines below and send this form along with your check to:

**Radio-Electronics Classified Ads**, 500-B Bi-County Boulevard, Farmingdale, NY 11735

**PLEASE INDICATE** in which category of classified advertising you wish your ad to appear. For special headings, there is a surcharge of \$23.00.

( ) Plans/Kits ( ) Business Opportunities ( ) For Sale  
( ) Education/Instruction ( ) Wanted ( ) Satellite Television

Special Category: \$23.00

### PLEASE PRINT EACH WORD SEPARATELY, IN BLOCK LETTERS.

(No refunds or credits for typesetting errors can be made unless you clearly print or type your copy.) Rates indicated are for standard style classified ads only. See below for additional charges for special ads. **Minimum: 15 words.**

1	2	3	4	5
6	7	8	9	10
11	12	13	14	15 (\$42.75)
16 (\$45.60)	17 (\$48.45)	18 (\$51.30)	19 (\$54.15)	20 (\$57.00)
21 (\$59.85)	22 (\$62.70)	23 (\$65.55)	24 (\$68.40)	25 (\$71.25)
26 (\$74.10)	27 (\$76.95)	28 (\$79.80)	29 (\$82.65)	30 (\$85.50)
31 (\$88.35)	32 (\$91.10)	33 (\$94.05)	34 (\$96.90)	35 (\$99.75)

We accept MasterCard and Visa for payment of orders. If you wish to use your credit card to pay for your ad fill in the following additional information (Sorry, no telephone orders can be accepted.):

Card Number \_\_\_\_\_ Expiration Date \_\_\_\_\_

Please Print Name \_\_\_\_\_

Signature \_\_\_\_\_

**IF YOU USE A BOX NUMBER YOU MUST INCLUDE YOUR PERMANENT ADDRESS AND PHONE NUMBER FOR OUR FILES. ADS SUBMITTED WITHOUT THIS INFORMATION WILL NOT BE ACCEPTED.**

**CLASSIFIED COMMERCIAL RATE:** (for firms or individuals offering commercial products or services) \$2.85 per word prepaid (no charge for zip code)...**MINIMUM 15 WORDS.** 5% discount for same ad in 6 issues; 10% discount for same ad in 12 issues within one year; if prepaid. **NON-COMMERCIAL RATE:** (for individuals who want to buy or sell a personal item) \$2.30 per word, prepaid...no minimum. **ONLY FIRST WORD AND NAME** set in bold caps at no extra charge. Additional bold face (not available as all caps) 50¢ per word additional (20% premium). Entire ad in boldface, add 20% premium to total price. **TINT SCREEN BEHIND ENTIRE AD:** add 25% premium to total price. **TINT SCREEN BEHIND ENTIRE AD PLUS ALL BOLD FACE AD:** add 45% premium to total price. **EXPANDED TYPE AD:** \$4.30 per word prepaid. All other items same as for STANDARD COMMERCIAL RATE. **TINT SCREEN BEHIND ENTIRE EXPANDED TYPE AD:** add 25% premium to total price. **TINT SCREEN BEHIND ENTIRE EXPANDED TYPE AD PLUS ALL BOLD FACE AD:** add 45% premium to total price. **DISPLAY ADS:** 1" x 2 1/4" — \$320.00; 2" x 2 1/4" — \$640.00; 3" x 2 1/4" — \$960.00. General information: Frequency rates and prepayment discounts are available. **ALL COPY SUBJECT TO PUBLISHERS APPROVAL. ADVERTISEMENTS USING P.O. BOX ADDRESS WILL NOT BE ACCEPTED UNTIL ADVERTISER SUPPLIES PUBLISHER WITH PERMANENT ADDRESS AND PHONE NUMBER.** Copy to be in our hands on the 12th of the third month preceding the date of the issue. (i.e., Sept. issue copy must be received by May 12th). When normal closing date falls on Saturday, Sunday or Holiday, issue closes on preceding working day.

## CB RADIO OWNERS!

We specialize in a wide variety of technical information, parts and services for CB radios. 10M-FM conversions, repairs, books, plans, kits, high-performance accessories. Our 11th year! Catalog \$2.

**CBC INTERNATIONAL, P.O. BOX 31500RE, PHOENIX, AZ 85046**

**TUBES** new, unused. Send self-addressed, stamped envelope for list. **FALA ELECTRONICS**, Box 1376-2, Milwaukee, WI 53201.

**PHOTOFACT** folders, under #1400 \$3.00. Others \$5.00. Postpaid **LOEB**, 414 Chestnut Lane, East Meadow, NY 11554.

**TI-99/4A** software hardware bargains. Hard-to-find items. Huge selection. Fast service. Free catalog. **DYNA**, Box 690, Hicksville, NY 11801.

**FLASHLIGHT** that needs no batteries measures 5" x 3" ideal for every situation, money back guarantee \$10. — **SAMUELS ENTERPRISES**, 724 East 231 Street, Bronx, NY 10466.

**CUSTOM** front panel nameplates for your projects. For details: **J & E ENTERPRISES**, 2457 N. Mar-mora, Chicago, IL 60639.

**FREE power supply (\$7.95 value) with ASSORTMENT #103**, (February '84 article) printed circuit, **toko coils, transistors, IC's, diodes \$25.00.** Five: \$12.50. Shipping \$3.00. **JIM RHODES INC.**, P.O. Box 3421, Bristol, TN 37625.



**Quality Microwave TV Antennas**

Multi-Channel 1.9 to 2.7 GHz 40dB Gain  
12-Channel System complete \$104.95  
2-Channel System complete \$84.95  
Dealerships, Qty. Pricing, Replacement Parts

**Philips-Tech Electronics**  
P.O. Box 8523 • Scottsdale, AZ 85225  
(602) 947-7700 (300 Credit all phone orders!)

LIFETIME WARRANTY  
MasterCard • Visa • C.O.D.

**COMMODORE** chips repairs C-64 repair \$39.95 complete. We sell chips at low cost (eg. 6526 6510-\$9.95 and many others) C-64 P.S. \$27.95. "Commodore Diagnostician," a complete chart for diagnosing faulty IC's \$6.95 + postage. Send for catalog. **KASARA MICROSYSTEMS, INC.**, 33 Murray Hill Drive, Spring Valley, NY 10977. (800) 642-7634 (outside NY) or (914) 356-3131.

**NEW 30 channel** microwave TV antenna—complete \$149.95. Standard 2 channel \$99.95. Lifetime warranty—dealer pricing—C.O.D.—**MC—VISA—HIGH-TECH ELECTRONICS**, 337 Vineyard Ave., Suite 300, Ontario, CA. 91764. (714) 391-1655.

# AMAZING SCIENTIFIC & ELECTRONIC PRODUCTS

**PLANS**—Build Yourself—All Parts Available In Stock

- LC7—BURNING CUTTING CO<sub>2</sub> LASER \$ 20.00
- RUB4—PORTABLE LASER RAY PISTOL 20.00
- TCC1—3 SEPARATE TESLA COIL PLANS TO 1.5 MEV 20.00
- IOG1—ION RAY GUN 10.00
- GRA1—GRAVITY GENERATOR 10.00
- EML1—ELECTRO MAGNET COIL GUN/LAUNCHER 6.00

**KITS**

- MFT1K—FM VOICE TRANSMITTER 3 MI RANGE 49.50
- VVPM5K—TELEPHONE TRANSMITTER 3 MI RANGE 39.50
- BTC3K—250.00 VOLT 10-14" SPARK TESLA COIL 199.50
- LHC2K—SIMULATED MULTICOLOR LASER 39.50
- BLS1K—100.000 WATT BLASTER DEFENSE DEVICE 69.50
- ITM1K—100.000 VOLT 20" AFFECTIVE RANGE INTIMIDATOR 69.50
- PSP4K—TIME VARIANT SHOCK WAVE PISTOL 59.50
- PTG1K—SPECTACULAR PLASMA TORNADO GENERATOR 149.50
- MVIK SEE IN DARK KIT 169.50

**ASSEMBLED**

- PG70H—MULTICOLORLED VARIABLE MODE PLASMA GLOBE "7" 425.00
- BTC10—50.000 VOLT—WORLD'S SMALLEST TESLA COIL 44.50
- LGU40—1MW HeNe VISIBLE RED LASER GUN 299.50
- TAT20 AUTO TELEPHONE RECORDING DEVICE 24.50
- GPV10—SEE IN TOTAL DARKNESS IR VIEWER 299.50
- LIST10—SNOOPER PHONE INFINITY TRANSMITTER 169.50
- IPG70—INVISIBLE PAIN FIELD GENERATOR—MULTI MODE 74.50

• CATALOG CONTAINING DESCRIPTIONS OF ABOVE PLUS HUNDREDS MORE AVAILABLE FOR \$1.00 OR INCLUDED FREE WITH ALL ABOVE ORDERS

PLEASE INCLUDE \$3.00 PH ON ALL KITS AND PRODUCTS PLANS ARE POSTAGE PAID. SEND CHECK, MO, VISA, MC IN US FUNDS

**INFORMATION UNLIMITED**  
P.D. BOX 716 DEPT. RE. AMHERST, NH 03031

**CABLE TV converters.** "new" Zenith flash, Scientific Atlanta, Jerrold, Oak, Zenith, Hamlin. Many others. "New" video hopper "The Copy Killer". Visa, M/C & Amex 1 (800) 826-7623. B & B Inc., 10517 Upton Circle, Bloomington, MN 55431.

**TUBES** 59¢. Year Guarantee. Free catalog. Tube tester \$8.95. CORNELL, 4215 University, San Diego, CA 92105.

**OAK 56 channel wireless remote converter/descrambler.** original refurbished equipment, exceptional video, \$175.00; legal to own your equipment, however, Federal law prohibits hookup without cable company permission. **PONDEROSA**, (303) 661-1659. (We ship C.O.D.)!

**FREE remote control converter** with any descrambler below: Oak VN12 \$85.00; new Hamlin MLD1200 \$90.00; new SB3 \$89.00; new Trimode/Bistate \$125.00; Starcom-6 system \$125.00; Zenith cable \$175.00; legal to own your equipment, however, Federal law prohibits hookup without cable company permission. **PONDEROSA**, (303) 661-1659. (We ship C.O.D.)!

**ADD 5 important features to your home telephone.** SASE (805) 583-4272. **B & M ENGINEERING**, Box 823, Simi Valley, CA 93062.

WRITE FOR  
**McGEE'S**  
**SPEAKER & ELECTRONICS CATALOG**  
1001 BARGAINS IN SPEAKERS  
toll free 1-800-346-2433 for ordering only.  
1901 MCGEE STREET KANSAS CITY, MO. 64108

**CABLE TV equipment S.A., Jerrold, Zenith, Hamlin, Oak, Eagle, filters, remotes and more.** Best prices C.O.D.'s accepted dealers needed. Ours work where others failed and we guarantee it! **TRANS-WORLD CABLE CO.**, (218) 543-6671.

**TUBES**, name brands. New. 80% off list. **KIRBY**, 298 West Carmel Drive, Carmel, IN 46032.

**TRANSISTORS-tubes:** MRF421 \$24.00, MRF454 \$15.00, MRF455-MRF477 \$12.00, MRF492 \$16.95, SRF2072 \$13.50, 3800 \$18.95, 2SC2879 \$25.00, 6LF6-6LQ6-6JS6 \$10.95, 8950 \$15.95. New Ranger AR3500 all mode 10 meter transceiver \$319. Quantity discounts! Best prices on hard-to-find parts, antennas, mics, power supplies, & equipment! Catalog \$1.00 (refundable), or free with order. **RFPC**, Box 700, San Marcos, CA 92069. For information or same day shipment—call (619) 744-0728. Visa MC/C.O.D.

**CIRCUIT board assembly** at 60¢ per hour. **FABRICANTS ELECTRONICS**, Apartado 391 Pavas, Costa Rica, C.A. Ph 320074.

**SATELLITE & cable equipment.** We have those hard-to-find units ready to go. Tired of junk that dont work properly, try our 10 day satisfaction guarantee & 90 day warranty (wholesale only) **HI TEC ELECTRONICS**, PO Box 42423, Detroit, MI 48242. (313) 722-9381.

**TUBES - 2000 TYPES DISCOUNT PRICES!**  
Early, hard-to-find, and modern tubes. Also transformers, capacitors and parts for tube equipment. Send \$2.00 for 20 page wholesale catalog.  
**ANTIQUE ELECTRONIC SUPPLY**  
688 W. First St. • Tempe, AZ 85281 • 602/894-9503

**PLASMA sphere** colorful bottled lighting, low cost prefilled 5" globes used in easily built for \$60 complete detailed plans \$10, kits, complete 5" & 9" units also available, info \$2. **RIESS**, Box 54625, Phoenix, AZ 85078.

**ALARM do-it-yourself** and save. Send SASE: **ERIC'S ALARM**, P.O. Box 8331, Bossier, LA 71113-8331.

**TUBES:** "oldest," "latest." Parts and schematics. SASE for list. **STEINMETZ**, 7519 Maplewood Ave., R.E. Hammond, IN 46324.

**HACKING**, crashing, pirating, and phreaking. Who's doing it, why they're doing it, and how they're doing it. Sample programs, phone numbers, and the tools of the trade. **Hacker's Handbook**, \$12.95. **Computer Underground**, \$14.95. \$1 postage to **CABLETRONICS**, Box 30502R, Bethesda, MD 20814.

**Cable Converters & Decoders**

	1	10
* Jerrold S.B. Add On.....	\$89.00	\$58.00
* Jerrold Tri-Bi Add On.....	\$98.00	\$78.00
Jerrold Starcom CSV.....	\$139.95	Call
MTS Converter + Remote.....	\$85.00	\$69.00
Jerrold 450 DRZ-3A.....	\$95.00	\$79.00
Parental Control MTS Plus.....	\$100.00	\$85.00
Hamlin MLD 1200-3.....	\$98.00	\$58.00
Scientific Atlanta Add On.....	\$140.00	\$99.00
M-35 B Combo With VariSync.....	\$99.00	\$69.00
Mini Code N-12 VariSync.....	\$99.00	\$58.00
442 VariSync (N-12 Substitute).....	\$89.00	\$58.00
Wireless Video Sender.....	\$45.00	Call

\*S.B. TRI-BI Flashing Got You Down? Try original Jerrold Equipment it might just solve your problems. Call or write for Free Catalog. All products Guaranteed 90 days plus.  
**M.D. Electronics** 5078 So. 108th Suite 115  
Omaha NE, 68137 Phone (402) 554-0417

**LASER**, components and accessories. Free catalog. **M.J. NEAL COMPANY**, 6672 Mallard Court, Orient, OH 43146.

**MODULES.** Build professional, custom, audio-music electronic devices easily. Catalog \$1.00 (refundable). **TONIX**, Box 770, Vernon, NJ 07462-770.

**INTRODUCTORY offer:** 100 pack 4 inch wire ties, one-piece molded 6/6 nylon, self-locking adjustable \$1.99. Product and price listing free with order or send \$1.00 refundable with first order. **NUTTER RIDGE PURVEYORS**, Star Route Province Road, Strafford, NH 03884.

**DESCRAMBLER** parts: I.C.'s, I.F. transformers, transistors, coils, capacitors, misc. Send S.A.S.E. to: **T-ROY**, P.O. Box 597 Marine City, MI 48039.

**ELECTRONICS** components, lowest prices. Free flyer. send SASE. **SANTECH ELECTRONICS**, 11 Revere, Tappan, NY 10983. (914) 359-1130.

**SAMS** photo facts under #1300 \$2.99 post paid. "SURPLUS," P.O. Box 219, Edgewood, NM 87123-0219.

**NUTS & VOLTS** MAGAZINE  
P.O. Box 1111-E  
Piscataway, CA 98670  
714-632-7721

GIVE YOURSELF A BREAK—A PRICE BREAK!  
NUTS & VOLTS WILL SAVE YOU MONEY ON ELECTRONIC PARTS & EQUIPMENT. **Just SHOW US WHERE TO FIND UNIQUE, UNUSUAL AND HARD-TO-FIND ITEMS.**

**SUBSCRIBE TODAY!**

Subscription Rates	U.S. Funds Required
1 Year	\$10.00
2 Year	\$18.00
3 Year	\$25.00
4 Year	\$32.00
5 Year	\$40.00
6 Year	\$48.00
7 Year	\$56.00
8 Year	\$64.00
9 Year	\$72.00
10 Year	\$80.00

A National Publication For The Buying And Selling Of Electronic Equipment

**PHOTOVOLTAIC** battery chargers by Arco solar. Cars, RVs, marine, etc. From \$49.50. Brochure. **SUN POWER-TEXAS**, P.O. Box 2788A, Freepost, TX 77541.

**USED** books: electronics, physics, mathematics, mechanics, etc; big list: \$1.00 in stamps: **SOFTWARE**, 1515 Sashabaw, Ortonville, MI 48462.

**INTERCOM 2001**—An inexpensive home intercom and control system that utilizes existing touch tone telephones and their associated wiring! Easy to install and easy to use! \$499.95. **JACKSON COMMUNICATION PRODUCTS**, 604 Burnham Road, Phila., PA 19119.

**PLANS AND KITS**  
**HI-FI speaker systems**, kits and speaker components from the world's finest manufacturers. For beginners and audiophiles. Free literature. **A&S SPEAKERS**, Box 7462, Denver, CO 80207. (303) 399-8609.

**VOICE** disguisers! FM bugs! Telephone transmitters! Phone snoops! More! Catalog \$1.00 (Refundable); **XANDI ELECTRONICS**, Box 25647, Dept. 60V, Tempe, AZ 85282.

**DEAR SANTA**  
WITH THE WORLD POPULATION AT IT'S HIGHEST EVER I FIGURED YOU COULD STAND TO SAVE A BUCK OR 2! BELOW IS MY SHOPPING LIST FROM SILICON VALLEY SURPLUS' HOLIDAY SALE

**MSDOS BOOK SET** \$13.99  
This four book set for vers 2.11c have the following titles User's Guide, Debug Utility, Programmers Reference, & Pivot Enhancements

**MACINTOSH NOTEBOOKS** \$12.00  
A well illustrated 3 book set by Prentice Hall each book is 8 by 11 by 3/4" A separate book for Macpaint, Macwrite, & Multiplan

**Multitech KEYBOARDS FOR IBM® A.T.**

Works on the P.C. or the A.T. but not the XT. If you do not like the "feel" return it within 15 days for a refund, limited quantity on hand  
84 KEYS KB084 \$34.00  
reg 39.00

**15 no hassle money back trial**

**IBM COMPATIBLE FLOPPY DISK CONTROLLER WITH CENTRONICS PORT** \$12.00  
Printer assignment LPT 1 cannot be changed on this 3/4 size card  
REG 19.00  
Tandon pcba 188400

this sale will be over before we can process the bingo cards... call for fast service

Call for a copy of 15 day trial agreement. Tax & freight extra. Send check or add 1.90 for COD. Price may change. Store Price may differ. While supplies last. No P.O.s, terms, or credit cards

**Silicon Valley Surplus** OPEN 10am-6pm CLOSED SUN & MON  
415-261-4506  
4401 OAKPORT OAKLAND CA, 94601  
CALL OUR BBS 415-261-4513

CIRCLE 51 ON FREE INFORMATION CARD



# DO YOU REALLY GET THE BEST BUY FROM THEM?

Let's face it: There will always be some outfit that can undercut a published price. They do it by having no overhead, and no responsibility to you, the consumer.

"So, you want that Jerrold 450 combo? The one that Pacific Cable Co., Inc., is offering for \$199<sup>00</sup>?"

Well, that's a good price, but here's what I'll do..." What may happen is that you may save a

couple of bucks at the time. But suppose

there's a problem (and it happens to the best of them,) and you call that "Dealer"... This could be what you'll hear:

"No, Steve isn't here. He moved out, the bum! And he owes me \$437<sup>00</sup> on the phone bill! No, I don't know about any guarantees on your Gerald, who's that? Listen, if you see that creep..." etc.

At Pacific Cable Co., you've got an established company who will be here for you, time after time. We may be tough competitors, but we've got a soft spot for our clients! Try us, and be treated right—and we'll prove it by giving a one-year warranty on everything we sell.

### Check our prices on Scientific Atlanta Units!

ITEM	1 UNIT	10 OR MORE	ITEM	1 UNIT	10 OR MORE
RCA 36 Channel Converter (Ch 3 output only)	29 00	18 00	*Mimicode (N-12)	89 00	58 00
Panasonic Wireless Converter (our best buy)	88 00	69 00	*Mimicode (N-12) with Var Sync	99 00	62 00
400 or 450 Converter (manual line tune)	88 00	69 00	*Mimicode VarSync with Auto On-Off	145 00	105 00
*Jerrold 400 Combo	169 00	119 00	Econocode (mimicode substitute)	79 00	52 00
Jerrold 400 Hand Remote Control	29 00	18 00	Econocode with VarSync	89 00	56 00
*Jerrold 450 Combo	199 00	139 00	*MLD-1200-3 (Ch 3 output)	99 00	58 00
*Jerrold 450 Hand Remote Control	29 00	18 00	*MLD-1200-2 (Ch 2 output)	99 00	58 00
Jerrold SB-Add-On	89 00	58 00	*Zenith SSAVI Cable Ready	175 00	125 00
*Jerrold SB-Add-On with Trimode	99 00	70 00	Interference Filters (Ch 3 only)	24 00	14 00
*M-35 B Combo unit (Ch 3 output only)	99 00	70 00	*Eagle PD-3 Descrambler (Ch 3 output only)	119 00	65 00
*M-35 B Combo unit with VarSync	109 00	75 00	*Scientific Atlanta Add-on Replacement Descrambler	119 00	75 00

CHECK US OUT—WE'LL MEET OR BEAT THE OTHER'S ADVERTISED WHOLESALE OR RETAIL PRICES!



## Pacific Cable Co., Inc.

7325½ Reseda Blvd., Dept. R-12  
Reseda, CA 91335  
(818) 716-5914 • (818) 716-5140

• NO COLLECT CALLS! •

**IMPORTANT** • When ordering, please have the make and model number of the equipment used in your area—Thank you!

\*Call for availability

Prices subject to change without notice

Jerrold is a registered trademark of General Instruments Corp

Quantity	Item	Output Channel	Price Each	TOTAL PRICE

California Penal Code #593-D forbids us from shipping any cable descrambling unit to anyone residing in the state of California.

Prices subject to change without notice

PLEASE PRINT

Name \_\_\_\_\_

Address \_\_\_\_\_ City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_ Phone Number ( ) \_\_\_\_\_

Cashier's Check     Money Order     C O D     Visa     Mastercard

Acct # \_\_\_\_\_ Exp Date \_\_\_\_\_

Signature \_\_\_\_\_

#### FOR OUR RECORDS

**DECLARATION OF AUTHORIZED USE** — I, the undersigned, do hereby declare under penalty of perjury that all products purchased, now and in the future, will only be used on cable TV systems with proper authorization from local officials or cable company officials in accordance with all applicable federal and state laws

Dated \_\_\_\_\_ Signed \_\_\_\_\_

## A SINGER'S DREAM!

**REMOVES VOCALS FROM RECORDS!**  
Now You can sing with the world's best bands!  
The Thompson Vocal Eliminator can remove most or virtually all of a lead vocal from a standard stereo record and leave the background!  
Write or call for a free brochure and demo record.  
**LT Sound, Dept. R-1, P.O. Box 338, Stone Mountain, GA 30086 (404) 493-1258**

**STRANGE stuff** Plans, kits, new items. Build satellite dish \$69.00. Descramblers, bugs, adult toys. Informational photo package \$3.00 refundable. **DIRIJO CORPORATION**, Box 212, Lowell, NC 28098.

**DETECTIVES**, experimenters. Exciting new plans. Hard-to-find micro and restricted devices. Large catalog \$5.00, refundable on 1st order. **WILSON**, P.O. Box 5264, Augusta, GA 30906.

**VIDEOCIPHER II** manual 120+ pages/Oak Orion™ 120+ pages, either—\$27.45—both \$49.95. Plans, kits, descrambling books. Catalog—\$2.00. **MICROTRONICS**, P.O. Box 6426, Yuma, AZ 85364-0840.

**PLANS**. Plasma display, H.V. generator, CB modulator, linear amplifiers, pain field generators, shock sensor. Plans for all \$20.00 complete. **AET**, Suite 173, 5800-A North Sharon, Amity Rd., Charlotte, NC 28215.

**NOVELTY** type electronics projects for the gadgeteer. Unusual, fascinating, and fun. Free information. **TAYLOR ELECTRONICS**, P.O. Box 1612, Destin, FL 32541.

**BUILD** this five-digit panel meter and square-wave generator including an ohms, capacitance and frequency meter. Detailed instructions \$2.50. **BAGNALL ELECTRONICS**, 179 May, Fairfield, CT 06430.

**CATALOG**: hobby/broadcasting/1750 meters/ham/CB: transmitters, antennas, scramblers, bugging devices, more! **PANAXIS**, Box 130-F12, Paradise, CA 95967.

**CRYSTAL** radio sets, plans, kits, catalog \$1.00. **MIDCO**, 660 North Dixie Highway, Hollywood, FL 33020.

**DECODING** plans and theory booklets. Video tape copy protection, removes flashing and jitter, 30 pages, \$15.45. Jerrold DI and DIC decoder theory, 12 pages, \$6.95. Gated pulse decoding plus new universal single level suppression decoder, works on Hamlin, Jerrold, Sylvania, Eagle, 39 pages, \$15.00. Video scrambling techniques, the original secret manual, sinewave and Zenith SSAVI, 57 pages, \$14.95. Hidden signals on satellite TV, 178 pages, \$16.95. PC board and kits available. **ELEPHANT ELECTRONICS INC.**, P.O. Box 41865-J, Phoenix, AZ 85080. (602) 581-1973.

## FINALLY!

An interesting and worthwhile project. This **EASY-TO-BUILD** circuit lets you use any regular TV set as a simple **OSCILLOSCOPE**. Build for less than \$10. **NO MODIFICATIONS TO TV!** Single or dual trace. Send for **FREE CATALOG** of other plans and kits.

**TV-SCOPE**  
Detailed Plans: \$4.95  
**PENN RESEARCH**, Box 3543  
Williamsport, PA 17701

**FREE CATALOG 99-cent kits**—audio, video, TV, computer parts. **ALLKIT**, 434 W. 4th St., West Islip, NY 11795.

**PROJECTION TV**. Convert your TV to project 7 foot picture. Results comparable to \$2,500 projectors... Total cost less than \$30.00. Plans and 8" lens \$21.95... Illustrated information **Free**... **MACROCAM-GD**, Washington Crossing, PA 18977. Credit card orders 24hrs. (215) 736-3979.

**ELECTRONIC House** Bimonthly magazine covering smart houses, integrated electronics, security, energy, sensors, more. Send \$14.95 for one year subscription to: **ELECTRONIC HOUSE**, Dept. RE, 524 East McKinley, Mishawaka, IN 46545. (219) 256-2060.

**SURPLUS SATELLITE EQUIPMENT**

**SPARTAN DISTRIBUTING**  
PO BOX 7 BIXBY, OK 74008

**NEW SURPLUS INVENTORY FROM SATELLITE EQUIP. MANUF.**

**COMPLETE PLANS TO BUILD A HIGH QUALITY SATELLITE BLOCK RECEIVER. KIT INCLUDES SCHEMATICS, PARTS LIST, METAL CASE, SILK-SCREENED FRONT PANEL, PRINTED CIRCUIT BOARD WITH CONTROLS ATTACHED.**

**\$35.00 + 2.50 SHIP. MONEY ORDERS OR CASHIERS CHECK ONLY.**

SEND STAMPED ENVELOPE FOR LIST OF OTHER EQUIP AVAILABLE

**TOP quality** imported, domestic kits, surplus, discount electronics, computer components. **free catalog**. **TEKTRASONIX**, 1120 Avenue of the Americas, 11th suite 4038, New York, NY 10036.

**PLANS**. Car radio amplifiers, 50W, 100W, 200W per channel. Plans for all \$10.00 complete. **DBS**, P.O. Box 261632, Tampa, FL 33685.

**SELECT TV** patents plus complete explanations of authorization, polarity status, audio, sync modifications \$14.00. **SIGNAL**, Box 2512-R, Cuiver City, CA 90231.

**PLANS**: solar, wood differential thermostat; wood-stove audible blower control; microprocessor AC DC controller; auto tremble alarm; VLF receiver \$5.00 each. **AUTOMATION CONTROL SYSTEMS**, 823 W. Durham, Cary, NC 27511.


CPU'S & CHIPS		RAM'S	
V205	10.95	2016	1.50
V208	14.95	2016-3	.70
Z8001 CPU	1.75	2101A-4	1.50
Z8008 CPU	3.75	2111A	1.75
Z8011 CPU	1.95	2121-1	1.95
Z8012 CPU	1.95	2121-2	1.95
Z8013 CPU	1.95	2121-3	1.95
Z8110 CPU	1.95	2121-100	1.95

TRANSISTOR SPECIAL		SCR'S		TRIACS		74HC SERIES	
2N1307 PNP GP TD 5	\$4.00	1.5A	6A	PRV 1A	10A	74HC00	25
2N1307 PNP GP TD 5	\$4.00	100	35	100	35	74HC01	25
2N1307 PNP GP TD 5	\$4.00	200	40	200	40	74HC02	25
2N1307 PNP GP TD 5	\$4.00	400	60	400	60	74HC03	25
2N1307 PNP GP TD 5	\$4.00	600	80	600	80	74HC04	25
2N1307 PNP GP TD 5	\$4.00	800	100	800	100	74HC05	25
2N1307 PNP GP TD 5	\$4.00	1000	120	1000	120	74HC06	25
2N1307 PNP GP TD 5	\$4.00	1200	140	1200	140	74HC07	25
2N1307 PNP GP TD 5	\$4.00	1400	160	1400	160	74HC08	25
2N1307 PNP GP TD 5	\$4.00	1600	180	1600	180	74HC09	25
2N1307 PNP GP TD 5	\$4.00	1800	200	1800	200	74HC10	25
2N1307 PNP GP TD 5	\$4.00	2000	220	2000	220	74HC11	25
2N1307 PNP GP TD 5	\$4.00	2200	240	2200	240	74HC12	25
2N1307 PNP GP TD 5	\$4.00	2400	260	2400	260	74HC13	25
2N1307 PNP GP TD 5	\$4.00	2600	280	2600	280	74HC14	25
2N1307 PNP GP TD 5	\$4.00	2800	300	2800	300	74HC15	25
2N1307 PNP GP TD 5	\$4.00	3000	320	3000	320	74HC16	25
2N1307 PNP GP TD 5	\$4.00	3200	340	3200	340	74HC17	25
2N1307 PNP GP TD 5	\$4.00	3400	360	3400	360	74HC18	25
2N1307 PNP GP TD 5	\$4.00	3600	380	3600	380	74HC19	25
2N1307 PNP GP TD 5	\$4.00	3800	400	3800	400	74HC20	25
2N1307 PNP GP TD 5	\$4.00	4000	420	4000	420	74HC21	25
2N1307 PNP GP TD 5	\$4.00	4200	440	4200	440	74HC22	25
2N1307 PNP GP TD 5	\$4.00	4400	460	4400	460	74HC23	25
2N1307 PNP GP TD 5	\$4.00	4600	480	4600	480	74HC24	25
2N1307 PNP GP TD 5	\$4.00	4800	500	4800	500	74HC25	25
2N1307 PNP GP TD 5	\$4.00	5000	520	5000	520	74HC26	25
2N1307 PNP GP TD 5	\$4.00	5200	540	5200	540	74HC27	25
2N1307 PNP GP TD 5	\$4.00	5400	560	5400	560	74HC28	25
2N1307 PNP GP TD 5	\$4.00	5600	580	5600	580	74HC29	25
2N1307 PNP GP TD 5	\$4.00	5800	600	5800	600	74HC30	25
2N1307 PNP GP TD 5	\$4.00	6000	620	6000	620	74HC31	25
2N1307 PNP GP TD 5	\$4.00	6200	640	6200	640	74HC32	25
2N1307 PNP GP TD 5	\$4.00	6400	660	6400	660	74HC33	25
2N1307 PNP GP TD 5	\$4.00	6600	680	6600	680	74HC34	25
2N1307 PNP GP TD 5	\$4.00	6800	700	6800	700	74HC35	25
2N1307 PNP GP TD 5	\$4.00	7000	720	7000	720	74HC36	25
2N1307 PNP GP TD 5	\$4.00	7200	740	7200	740	74HC37	25
2N1307 PNP GP TD 5	\$4.00	7400	760	7400	760	74HC38	25
2N1307 PNP GP TD 5	\$4.00	7600	780	7600	780	74HC39	25
2N1307 PNP GP TD 5	\$4.00	7800	800	7800	800	74HC40	25
2N1307 PNP GP TD 5	\$4.00	8000	820	8000	820	74HC41	25
2N1307 PNP GP TD 5	\$4.00	8200	840	8200	840	74HC42	25
2N1307 PNP GP TD 5	\$4.00	8400	860	8400	860	74HC43	25
2N1307 PNP GP TD 5	\$4.00	8600	880	8600	880	74HC44	25
2N1307 PNP GP TD 5	\$4.00	8800	900	8800	900	74HC45	25
2N1307 PNP GP TD 5	\$4.00	9000	920	9000	920	74HC46	25
2N1307 PNP GP TD 5	\$4.00	9200	940	9200	940	74HC47	25
2N1307 PNP GP TD 5	\$4.00	9400	960	9400	960	74HC48	25
2N1307 PNP GP TD 5	\$4.00	9600	980	9600	980	74HC49	25
2N1307 PNP GP TD 5	\$4.00	9800	1000	9800	1000	74HC50	25
2N1307 PNP GP TD 5	\$4.00	10000	1020	10000	1020	74HC51	25
2N1307 PNP GP TD 5	\$4.00	10200	1040	10200	1040	74HC52	25
2N1307 PNP GP TD 5	\$4.00	104					



If you would like to know more about these Tenma products, ask for our free catalog...  
**Call TOLL-FREE 1-800-543-4330**  
 In Ohio call 1-800-762-4315  
 In Alaska or Hawaii 1-800-858-1849

**TENMA** 

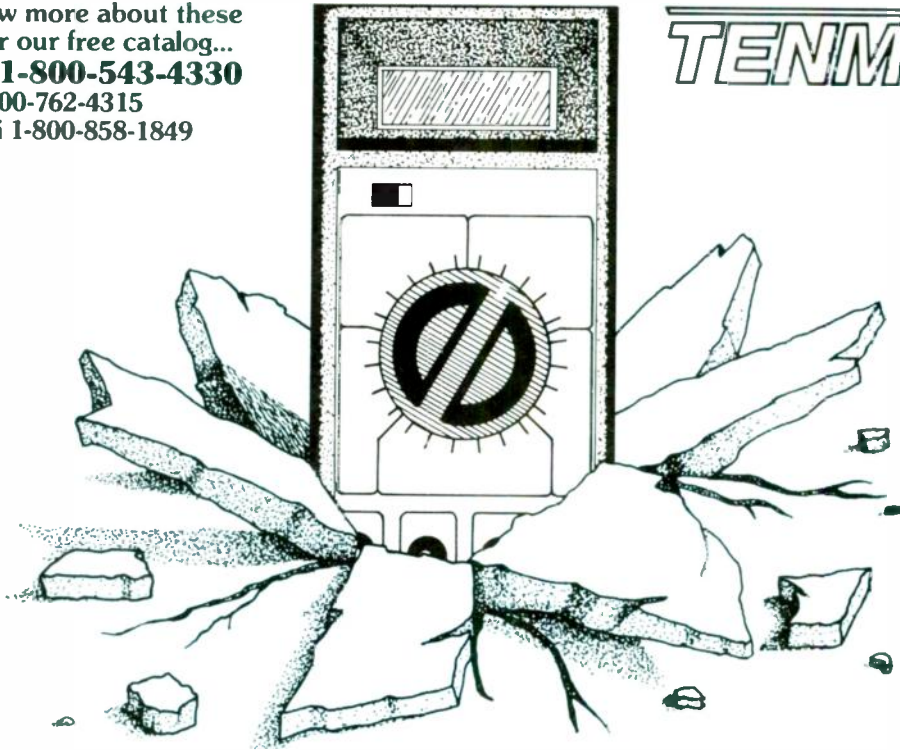

# Earth Shattering Products



## #72-370 Tenma LCR Meter

- Measures inductance from 1 $\mu$ H-200H in six ranges
- Measures capacitance from .1pF-200 $\mu$ F in seven ranges
- Measures resistance from .01ohm-20Mohm in seven ranges
- 3 $\frac{1}{2}$  digit LCD display
- Fuse protected
- Low battery indicator
- Comes complete with test leads, carrying case and owners manual



## #72-445 Tenma Compact DMM/Logic Probe

- 3 $\frac{1}{2}$ " shock-mounted LCD display
- Transistor gain and diode test
- Audible continuity test
- Overload protection
- Low battery indicator
- Comes complete with test leads, carrying case and owners manual



## #72-040 Tenma Capacitance Meter

- 3 $\frac{1}{2}$  digit LCD display
- Zero adjustment
- In or out of circuit measurements
- Fuse protected
- Low battery indicator
- Comes complete with test leads, carrying case and owners manual



## #72-050 Tenma 3 $\frac{1}{2}$ Digit LCD Multimeter

- Transistor gain and diode test
- 10Mohm input impedance
- AC and DC current up to 10A
- Low battery indicator
- Overload protection
- Comes complete with test leads, carrying case and owners manual



## #72-045 Tenma Combination DMM/Capacitance Meter

- Measures capacitance from 1pF-20 $\mu$ F
- 10Mohm input impedance
- Transistor gain and diode test
- Audible continuity test
- AC and DC current up to 10A
- Resistance up to 20Mohm
- Overload protection
- Auto-polarity
- Comes complete with test leads, carrying case and owners manual



## #72-058 Tenma Autorange DMM

- 3 $\frac{1}{2}$  digit LCD display
- 10Mohm input impedance
- Auto/manual range selector
- Audible continuity tester
- AC and DC current up to 10A
- Switchable Lo/Hi power ohms for in-circuit resistance tests
- Overload protection
- Low battery indicator
- Auto-polarity
- Comes complete with test leads, carrying case and owners manual



## #72-060 Tenma Compact DMM

- 3 $\frac{1}{2}$ " shock-mounted LCD display
- Transistor gain and diode test
- Overload protection
- Low battery indicator
- Comes complete with test leads and owners manual



## #72-075 Tenma Rotary Dial DMM

- AC and DC current up to 20A
- 10Mohm input impedance
- Overload protection
- Auto-polarity
- Low battery indicator
- Comes complete with test leads, carrying case and instruction manual



## #72-430 Tenma True RMS DMM/Frequency Counter

- 4 $\frac{1}{2}$  digit LCD display
- True RMS AC voltage and current measurement
- 10Mohm input impedance
- Frequency counter
- Data hold
- Audible continuity test
- AC and DC current measurements up to 10 amps
- Overload protection
- Diode test
- Auto-polarity
- Comes complete with test leads, carrying case and owners manual

Note: All products shown have a 1 year limited warranty.



**MCM ELECTRONICS**

858 E. CONGRESS PARK DR.  
 CENTERVILLE, OH 45459

A PREMIER Company

SOURCE NO. RE-39

**REMOVE** vocals the easy way from records. Mono-cable complete with instructions \$12.95. **TRONCO**, Box 453, California, MD 20619.

**ULTRASONIC** ranging system measures distances from 6" to 35". I/O is TTL compatible, can be connected directly to most computers. Experimenter's kit includes one SN28827 ranging module, one Polaroid 50KHz electrostatic transducer, and user's manual with data sheets. Great for alarms, computer mapping, robotics, etc. \$59.95 + \$2.00 postage, \$2.50 for COD. I.O. **MICRODEVICES**, P.O. Box 2386, Canoga Park, CA 91306. (818) 348-8312.

**DESCRAMBLING**, new secret manual. Build your own descramblers for cable and subscription TV. Instructions, schematics for SSAVI, gated sync, sinewave. (HBO, Cinemax, Showtime, etc.) \$8.95, \$1 postage. **CABLETRONICS**, Box 30502R, Bethesda, MD 20814.

**Multi-Channel Microwave T.V. Receivers**  
1.9-2.7 GHz Parabolic Dish 40-dB Gain  
**LIFETIME WARRANTY**  
Complete System \$89.95 (Shipping Incl.)  
Dealer Rates, Replacement Components  
& Expert Repairs Available

**K & S ELECTRONICS** Call now for same  
P.O. BOX 34522 (day shipping)  
PHOENIX, AZ 85067 (602) 230-0640

VISA/MC/COD \$2 credit on phone orders!

### SATELLITE TV

**SATELLITE TV** receiver kits! LNA's! Instructions! Schematics! Catalog \$1.00 (refundable): **XANDI ELECTRONICS**, Box 25647, Dept. 21Y, Tempe, AZ 85282.

**SATELLITE TV** equipment. Buyers guide, discount prices. \$2.00 **N.E.C.S. INC.**, Box 22808-R4, Little Rock, AR 72221.

### Cable TV Converters

Why Pay A High Monthly Fee?

Jerrold Products include "New Jerrold Tri-Mode," SB-3, Hamlin, Oak VN-12, M-35-B, Zenith, Magnavox, Scientific Atlanta, and more. (Quantity discounts) 60 day warranty. For fast service C.O.D. orders accepted. Send SASE (60 cents postage) or call for info (312) 658-5320. **Midwest Electronics, Inc.**, **HIGGINS ELECTRONICS**, 5143-R W. Diversey, Chicago, IL 60639. MC/Visa orders accepted. No Illinois orders accepted. Mon.-Fri.-9 A.M.-6 P.M. CST

**CABLE TV Secrets**—the outlaw publication the cable companies tried to ban. HBO, Movie Channel, Showtime, descramblers, converters, etc. Suppliers list included \$8.95. **CABLE FACTS**, Box 711-R, Pataskala, OH 43062.

**DESCRAMBLER**. Build our low cost satellite TV video only descrambler for all major movies and sports. Uses all Radio Shack parts. Order P.C. board and instructions by sending check, money order, or Visa for \$35.00 U.S. funds to: **VALLEY MICROWAVE ELECTRONICS**, Bear River, Nova Scotia, Canada. BOS-1BO. (902) 467-3577.

**SEE "after dark" with TELEASE-MAST assortment #301** (October '86 article) printed circuit, IC's, transistors, diodes. \$25.00. Shipping \$3.00. **JIM RHODES, INC.**, P.O. Box 3421, Bristol, TN 37625.

**DESCRAMBLERS** for movies, networks. \$149. video only. \$399 complete. Catalog \$4. **SKYWATCH**, 238 Davenport Road, Toronto, Ontario, Canada. M5R-1J6.

**SATELLITE** antenna special, 6 1/2 foot, mesh construction, polar mount. UPS shippable. \$159. **D.N.F.**, (313) 437-5565.

**SATELLITE descrambling manual**, Video Cypher II. Schematics, thorough explanation of digital audio encoding, EPROM code, DES. (HBO, Cinemax, Showtime.) \$10.95, \$1 postage. **CABLETRONICS**, Box 30502R, Bethesda, MD 20814.

**\*\*\*SCRAMBLING NEWS\*\*\***  
**PAY TV AND SATELLITE DESCRAMBLING**

Schematics, theory, bypasses, 13 cable, 7 satellite. New SA turn-on, MLD-1200-3 \$14.95. Experiments With Videocipher Cloning musketeering \$14.95. Cable TV Security design \$12.95. MDS, MMS Handbook Microwave hacking \$9.95. Build Satellite Systems Under \$600 \$12.95. Any 3 S27 Scrambling News. Monthly Feature articles, product reviews, law history, patents \$24.95 yr. Sample \$5. Winter catalog \$1.

**Shojiki Electronics Corp.** 1327A Niagara St.,  
Niagara Falls, NY 14303. COD's 716-284-2163

### BUSINESS OPPORTUNITIES

**YOUR own radio station!** AM, FM, cable. Licensed or unlicensed. **BROADCASTING**, Box 130-F12, Paradise, CA 95967.

**EARN** thousands with your own part time electronics business. I do. Free proof, information. **INDUSTRY**, Box 531, Bronx, NY 10461.

**DEALERS** wanted. Notch filters for any channel. Send for further information or \$15 for sample unit (specify output channel of converter). **DB ELECTRONICS**, P.O. Box 8644, Pembroke Pines, FL 33084.

**HOME** assembly. Assemble PC boards for video accessories. We supply materials. No experience needed \$7.50 per hour. Send self-addressed stamped envelope, to: **MICRON-ELECTRONICS**, Box 4716 Akron, OH 44310.

**SUPER SAVINGS - SHOP G.E.I.**

**MULTI NI-CAD BATTERY CHARGER**  
Recharge 2 or 4 NI-CAD "AA Batt" or "AAA Batt"  
**10.00 each**

**COMMODORE 64 CARTRIDGES**  
• Num. Nabber • Star Post  
• Financial Advts. • Frog Master  
• Super Smash • Avenger • Radar Rat  
• Jupitree Landing • Megic Compos  
• Dragons Den • Simon Basic  
• Viduzzies • Star Ranger  
• Golf • Blue Print • ABC Voice  
• Sales Demo  
**\$1.50 ea. (10 pc. min.)**

**POWER SUPPLY FOR THE COMMODORE AMIGA**  
+5VDC @ 8 Amps  
+12VDC @ 1 Amp  
-5VDC @ 1/2 Amp  
**\$39 ea.**

**MINI FLOPPY DISK DRIVE**  
by Shugart #SA465-3AA  
1/2 height  
Quad Density  
5 1/4 Inch  
**Ea \$65**

**PATCH CORDS**  
5 ft dual RCA  
color coded, stereo cords  
**99c Each**

**OPEN FRAME MONITORS**  
12" monitor 40-80 column display  
composite Green screen 18 Mhz Bandwidth  
**\$20 Ea.**

**Plug in WALL TRANSFORMER**  
Quantity Pricing Available  
• 9.5 VDC @ 1 Amp \$3.00  
• 19 VAC @ 300 MA \$1.50  
• 25.4 VAC @ 1 Amp \$1.95  
• 14 VDC @ 200 MA \$1.00  
**\$24 ea.**

**REGULATED LINEAR POWER SUPPLY**  
Computer Grade  
+5VDC @ 8 Amps  
+12VDC @ 8 Amps  
-5VDC @ 0.5 Amps  
Bench Style/Great for Hobbies  
**\$24 ea.**

**PASSIVE INFRARED MOTION DETECTOR**  
It can pick up any moving human body heat or moving vehicle with sensing range (40 x 60 ft), and turn on the light.  
**\$60 Each**

**GET**  
19 Freeman St., Newark, N.J. 07105  
TOLL FREE 800/645-9060  
201/344-8183 Fax # 201/344-3282

**Parts Express** INTERNATIONAL INC.  
**HARDWARE AND ELECTRONICS**

<b>PIONEER</b> 12" POLY WOOFER Clear ribbed polypropylene cone. 65 watts RMS, 11 oz magnet Ferro fluid cooled 1" voice coil. Trimming incooled. 25-2500 Hz. #290-100 \$15.50 (1-3) #290-055 \$20.50 (1-3) #290-160 \$30.95 (1-3) #290-055 \$18.95 (4-UP) #290-160 \$28.40 (4-UP)	<b>PIONEER</b> 8" POLY WOOFER Clear ribbed polypropylene cone. 60 watts RMS, 90 watts max power. 20 oz magnet. 35-2500 Hz. 4-8 ohm impedance. #290-055 \$20.50 (1-3) #290-160 \$30.95 (1-3) #290-055 \$18.95 (4-UP) #290-160 \$28.40 (4-UP)	<b>PIONEER</b> 15" WOOFER 20 oz magnet, 60 watts RMS, 90 watts max. 8 ohm impedance. 1" voice coil. 25-2000 Hz. #290-160 \$30.95 (1-3) #290-055 \$18.95 (4-UP) #290-160 \$28.40 (4-UP)
<b>MOTOROLA</b> PIEZO TWEETER Mfg #KSN1005A. 3" x 3". No crossover required. 50 watts maximum input power. #270-010 \$4.95 (1-79) #270-050 \$6.50 (1-9) #270-050 \$5.90 (10-UP)	<b>PIONEER</b> HORN TWEETER 3" wide dispersion horn tweeter. 1800-15,000 Hz response. 35 watts RMS. 50 watts max. 8 ohm impedance. #270-050 \$6.50 (1-9) #270-050 \$5.90 (10-UP)	<b>PIONEER</b> 5 1/4" CUP MIDRANGE Tuned cup. Paper cone. 1" voice coil. 9.3 oz magnet. 50 watts RMS. 70 watts max. Response: 320-6000 Hz. 8 ohm impedance. #280-020 \$11.50 (1-9) #280-020 \$9.95 (10-UP)
<b>CROSSOVERS</b>		
2-Way, 30 watt #260-190 \$3.95		
3-Way, 60 watt #260-200 \$7.50		
3-Way, 100 watt #260-210 \$12.50		
<b>FREE CATALOG</b>		
Call or write today for your free catalog containing speakers, semi-conductors, CATV products, tools, hardware, TV-VCR parts, and more.		
		
<b>CALL TOLL FREE 1-800-255-3525</b> In Ohio: 1-800-322-3525 Local: (513) 222-0173		
<ul style="list-style-type: none"> <li>• 15 day money back guarantee.</li> <li>• \$10.00 minimum order.</li> <li>• COD orders accepted.</li> <li>• 24 hour shipping.</li> <li>• Shipping charge: UPS chart rate (\$2.50 minimum charge). Hours 8:30 a.m. - 6 p.m. EST M-F.</li> </ul>		
<b>PARTS EXPRESS INTL. INC.</b> 340 East First St Dayton, Ohio 45402		
 		

RADIO-ELECTRONICS

**PERSONAL** computer owners can earn \$1000 to \$5000 monthly selling simple services part time. Free list of 100 services. **A.I.M.J.K.**, Box 60369, San Diego, CA 92106-8369.

**PROJECTION TV**...Make \$\$\$'s assembling projectors...easy...results comparable to \$2,500 projectors...Total cost less than \$30.00...Plans, 8" lens and dealers information \$20.50...Illustrated information free...**MACROCOMA-GDX**, Washington Crossing, PA 18977. Credit card orders 24hrs. (215) 736-2880.

**CRT** equipment rebuilds Sony color tubes other **CRT SYSTEMS**, 633 North Semoran, Orlando, FL 32807. Call (305) 275-9543.

**MICRO-Electronics** engineer to design and manufacture receiver. **JPH**, 4218 Bunker Hill, Bettendorf, IA 52722. (319) 355-2927.

## WANTED

**INVENTORS!** AIM wants—ideas, inventions, new products, improvements on existing products. We present ideas to manufacturers. Confidentiality guaranteed. Call toll free 1-(800) 225-5800 for information kit.

**INVENTIONS**, ideas, new products wanted! Industry presentation/national exposition. Call free 1-(800) 288-IDEA. Canada, 1-(800) 528-6060. X831.

**WANTED** excess inventories of I.C.s, disk drives, circuit boards, computers, etc. **WESTERN TECH.**, (818) 882-1355 (CA).

## INVENTORS

**INVENTORS!** Can you patent and profit from your idea? Call **AMERICAN INVENTORS CORPORATION** for free information. Over a decade of service. 1-(800) 338-5656. In Massachusetts or Canada call (413) 568-3753.

**BIG PROFITS**

## ELECTRONIC ASSEMBLY BUSINESS

Start home spare time investment knowledge or experience unnecessary. **BIG DEMAND** assembling electronic devices. Sales handled by professionals. Unusual business opportunity.

**FREE: Complete illustrated literature**  
EARTA RE-0 Box 248  
Walnut Creek Calif 94597

## DESCRAMBLER MODULE

**COMPLETE** cable-TV decoder in a mini-module. Latest technology upgrade for Jerrold SB-3 or Radio-Electronics Feb. 1984 project. Versatile, sophisticated, and low cost. For literature, **SOUTHTECH DISTRIBUTING**. (813) 222-3293.

## NOTCH FILTERS

**THE Positrap Cookbook:** build 50-60dB notch filters for pennies. Construction, alignment, fixed, tunable, trimable. **Comprehensive cable TV scrambling and descrambling theory and practice.** Identifying various systems. \$9.95. **CLEARVIEW CABLE COMPANY**, P.O. Box 207, Sterling Heights, MI 48311.

## EDUCATION & INSTRUCTION

**F.C.C. Commercial General Radiotelephone license.** Electronics home study. Fast, inexpensive! "Free" details. **COMMAND**, D-176, Box 2223, San Francisco, CA 94126.

**SUPERFAST Morse Code** supereasy. Subliminal cassette. \$10. Learn Morse Code in 1 hour. Amazing new supereasy technique \$10. Both \$17. Moneyback guarantee. Free catalog: **SASE. BAHN**, 2549-E7 Temple, Palmbay, FL 32905.

# LEARN TV/VCR REPAIR

**N**ow you can train at home in spare time for a money-making career as a TV/VCR Repair Specialist. No previous experience necessary. No need to quit your job or school. Everything is explained in easy-to-understand language with plenty of drawings, diagrams and photos. We show you how to troubleshoot and repair video-cassette recorders and TV sets, how to handle house calls and shop repairs for almost any make of television or VCR. Tools are included with your course so you can get "hands-on" practice as you follow your lessons step by step. Send for free facts about the exciting opportunities in TV/VCR Repair and find out how you can start making money in this great career. **MAIL COUPON TODAY!**

**ICS SCHOOL OF TV/VCR REPAIR, Dept. DE0B7**  
Since 1981, Scranton, Pennsylvania 18515

Please send me full information and color brochure on how I can learn TV/VCR Repair at home in my spare time. I understand there is no obligation and no salesman will visit me.

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City/State/Zip \_\_\_\_\_

Phone ( \_\_\_\_\_ ) \_\_\_\_\_

**FCC Commercial General Radiotelephone license** correspondence course, 60 individual lessons for \$89.50. Payment plan. Results guaranteed! Details free. **AMERICAN TECHNICAL INSTITUTE**, Box 201, Cedar Mountain, NC 28718.

**RECORD** changer repairing is very profitable. Be an expert. Learn at home. Info—**R.C.T.G.**, P.O. Box 1503, Leesburg, FL 32748.

**CHANGING** careers? Complete handbook shows you how. \$5.00. Easy steps. **MBL**, P.O. Box 12002, Akron, OH 44312.

# BUY BONDS

**508 Central Ave.**  
**Westfield, N.J. 07090**  
**(201) 654-8008**

TTL SERIES				74LS SERIES				LINEAR				TRANSISTORS & DIODES			
7400	25	74396	80	74LS164	45	4012	25	LM137	25	74LS11	25	2N4348	25	1N914	25
7401	25	74393	80	74LS165	60	4013	25	LM138	25	74LS12	25	2N4350	25	1N915	25
7402	25	75324	20	74LS166	45	4014	25	LM139	25	74LS13	25	2N4351	25	1N916	25
7403	25	74624	80	74LS167	45	4015	25	LM140	25	74LS14	25	2N4352	25	1N917	25
7404	25	74644	80	74LS168	60	4016	25	LM141	25	74LS15	25	2N4353	25	1N918	25
7406	20	74122	25	74LS169	60	4017	25	LM142	25	74LS16	25	2N4354	25	1N919	25
7407	25	74124	80	74LS170	60	4018	25	LM143	25	74LS17	25	2N4355	25	1N920	25
7408	20	74126	80	74LS171	60	4019	25	LM144	25	74LS18	25	2N4356	25	1N921	25
7409	20			74LS172	60	4020	25	LM145	25	74LS19	25	2N4357	25	1N922	25
7410	25			74LS173	60	4021	25	LM146	25	74LS20	25	2N4358	25	1N923	25
7411	25	74LS200	20	74LS174	60	4022	25	LM147	25	74LS21	25	2N4359	25	1N924	25
7412	25	74LS201	20	74LS175	60	4023	25	LM148	25	74LS22	25	2N4360	25	1N925	25
7413	25	74LS202	20	74LS176	60	4024	25	LM149	25	74LS23	25	2N4361	25	1N926	25
7414	25	74LS203	20	74LS177	60	4025	25	LM150	25	74LS24	25	2N4362	25	1N927	25
7415	25	74LS204	20	74LS178	60	4026	25	LM151	25	74LS25	25	2N4363	25	1N928	25
7416	25	74LS205	20	74LS179	60	4027	25	LM152	25	74LS26	25	2N4364	25	1N929	25
7417	25	74LS206	20	74LS180	60	4028	25	LM153	25	74LS27	25	2N4365	25	1N930	25
7418	25	74LS207	20	74LS181	60	4029	25	LM154	25	74LS28	25	2N4366	25	1N931	25
7419	25	74LS208	20	74LS182	60	4030	25	LM155	25	74LS29	25	2N4367	25	1N932	25
7420	25	74LS209	20	74LS183	60	4031	25	LM156	25	74LS30	25	2N4368	25	1N933	25
7421	25	74LS210	20	74LS184	60	4032	25	LM157	25	74LS31	25	2N4369	25	1N934	25
7422	25	74LS211	20	74LS185	60	4033	25	LM158	25	74LS32	25	2N4370	25	1N935	25
7423	25	74LS212	20	74LS186	60	4034	25	LM159	25	74LS33	25	2N4371	25	1N936	25
7424	25	74LS213	20	74LS187	60	4035	25	LM160	25	74LS34	25	2N4372	25	1N937	25
7425	25	74LS214	20	74LS188	60	4036	25	LM161	25	74LS35	25	2N4373	25	1N938	25
7426	25	74LS215	20	74LS189	60	4037	25	LM162	25	74LS36	25	2N4374	25	1N939	25
7427	25	74LS216	20	74LS190	60	4038	25	LM163	25	74LS37	25	2N4375	25	1N940	25
7428	25	74LS217	20	74LS191	60	4039	25	LM164	25	74LS38	25	2N4376	25	1N941	25
7429	25	74LS218	20	74LS192	60	4040	25	LM165	25	74LS39	25	2N4377	25	1N942	25
7430	25	74LS219	20	74LS193	60	4041	25	LM166	25	74LS40	25	2N4378	25	1N943	25
7431	25	74LS220	20	74LS194	60	4042	25	LM167	25	74LS41	25	2N4379	25	1N944	25
7432	25	74LS221	20	74LS195	60	4043	25	LM168	25	74LS42	25	2N4380	25	1N945	25
7433	25	74LS222	20	74LS196	60	4044	25	LM169	25	74LS43	25	2N4381	25	1N946	25
7434	25	74LS223	20	74LS197	60	4045	25	LM170	25	74LS44	25	2N4382	25	1N947	25
7435	25	74LS224	20	74LS198	60	4046	25	LM171	25	74LS45	25	2N4383	25	1N948	25
7436	25	74LS225	20	74LS199	60	4047	25	LM172	25	74LS46	25	2N4384	25	1N949	25
7437	25	74LS226	20	74LS200	60	4048	25	LM173	25	74LS47	25	2N4385	25	1N950	25
7438	25	74LS227	20	74LS201	60	4049	25	LM174	25	74LS48	25	2N4386	25	1N951	25
7439	25	74LS228	20	74LS202	60	4050	25	LM175	25	74LS49	25	2N4387	25	1N952	25
7440	25	74LS229	20	74LS203	60	4051	25	LM176	25	74LS50	25	2N4388	25	1N953	25
7441	25	74LS230	20	74LS204	60	4052	25	LM177	25	74LS51	25	2N4389	25	1N954	25
7442	25	74LS231	20	74LS205	60	4053	25	LM178	25	74LS52	25	2N4390	25	1N955	25
7443	25	74LS232	20	74LS206	60	4054	25	LM179	25	74LS53	25	2N4391	25	1N956	25
7444	25	74LS233	20	74LS207	60	4055	25	LM180	25	74LS54	25	2N4392	25	1N957	25
7445	25	74LS234	20	74LS208	60	4056	25	LM181	25	74LS55	25	2N4393	25	1N958	25
7446	25	74LS235	20	74LS209	60	4057	25	LM182	25	74LS56	25	2N4394	25	1N959	25
7447	25	74LS236	20	74LS210	60	4058	25	LM183	25	74LS57	25	2N4395	25	1N960	25
7448	25	74LS237	20	74LS211	60	4059	25	LM184	25	74LS58	25	2N4396	25	1N961	25
7449	25	74LS238	20	74LS212	60	4060	25	LM185	25	74LS59	25	2N4397	25	1N962	25
7450	25	74LS239	20	74LS213	60	4061	25	LM186	25	74LS60	25	2N4398	25	1N963	25
7451	25	74LS240	20	74LS214	60	4062	25	LM187	25	74LS61	25	2N4399	25	1N964	25
7452	25	74LS241	20	74LS215	60	4063	25	LM188	25	74LS62	25	2N4400	25	1N965	25
7453	25	74LS242	20	74LS216	60	4064	25	LM189	25	74LS63	25	2N4401	25	1N966	25
7454	25	74LS243	20	74LS217	60	4065	25	LM190	25	74LS64	25	2N4402	25	1N967	25
7455	25	74LS244	20	74LS218	60	4066	25	LM191	25	74LS65	25	2N4403	25	1N968	25
7456	25	74LS245	20	74LS219	60	4067	25	LM192	25	74LS66	25	2N4404	25	1N969	25
7457	25	74LS246	20	74LS220	60	4068	25	LM193	25	74LS67	25	2N4405	25	1N970	25
7458	25	74LS247	20	74LS221	60	4069	25	LM194	25	74LS68	25	2N4406	25	1N971	25
7459	25	74LS248	20	74LS222	60	4070	25	LM195	25	74LS69	25	2N4407	25	1N972	25
7460	25	74LS249	20	74LS223	60	4071	25	LM196	25	74LS70	25	2N4408	25	1N973	25
7461	25	74LS250	20	74LS224	60	4072	25	LM197	25	74LS71	25	2N4409	25	1N974	25
7462	25	74LS251	20	74LS225	60	4073	25	LM198	25	74LS72	25	2N4410	25	1N975	25
7463	25	74LS252	20	74LS226	60	4074	25	LM199	25	74LS73	25	2N4411	25	1N976	25
7464	25	74LS253	20	74LS227	60	4075	25	LM200	25	74LS74	25	2N4412	25	1N977	25
7465	25	74LS254	20	74LS228	60	4076	25	LM201	25	74LS75	25	2N4413	25	1N978	25
7466	25	74LS255	20	74LS229	60	4077	25	LM202	25	74LS76	25	2N4414	25	1N979	25
7467	25	74LS256	20	74LS230											

**SCIENTIFIC ATLANTA & SB-3**

SCIENTIFIC Atlanta models 8500—8550, remote included...\$250.00. SB-3's...\$74.00. TRI-BI's...\$95.00. SBSA-3's...\$99.00. Zenith (Z-Tac) Descramblers...\$169.00. N-12 (Vari-sync)...\$89.00. M-35 B (Vari-sync)...\$99.00. Jerrold-550 converters...\$95.00—\$99.00. Dealer discount on 5 units. Brochure available. Call...N.A.S. INTERNATIONAL. (213) 631-3552.

**CABLE TV TURN-ON'S**

"TURN-ON" boards & kits for Jerrold 400; Jerrold 450 (all models—no internal modification); Tocorn 5504 & 5503. Special requests no problem. Let us know what make and model you are interested in. Fully guaranteed. Call or write for information and prices. VIDEO SOLUTIONS, 3938 E. Grant, Suite 236, Tucson, AZ 85712. (602) 323-6072.

**VIDEO TAPE COPYGUARD**

Eliminate the latest copyguard problems units from \$59<sup>95</sup> to \$169<sup>95</sup>

*Deluxe Electronics* ..... (714) 998-6866  
1432 Heim Wy., Orange, Ca. 92665

THIS IS AN EXPANDED-TYPE AD WITH A TINT SCREEN. See how it jumps out on the page. To order your ad in this format calculate the cost at \$4.30 per word for the expanded-type and add 25% for the tint background.

**You can help us raise the colorectal cancer cure rate.**

When detected early, the cure rate for colorectal cancer is very high. That's why we urge regular checkups for men and women 50 and over.

Warning signs are a change in bowel habits, blood in the stool.

Your doctor can perform the digital and procto exams, and you take care of the stool blood test at home.

- Checkup Guidelines for men and women over 50 without symptoms:
- digital exam annually
  - stool blood test annually
  - procto exam every 3 to 5 years after 2 negative tests 1 year apart

No one faces cancer alone.

AMERICAN CANCER SOCIETY

CALL FOR FREE CATALOG

**TEXT TO SPEECH BOARD!**

PC/XT COMPATIBLE. MAKE YOUR COMPUTER TALK! A VERY POWERFUL AND AMAZING SPEECH CARD. USES THE NEW GENERAL INSTRUMENTS SPO256-AL2 SPEECH CHIP AND THE CTS256A-AL2 TEXT TO SPEECH CONVERTER.

THIS BOARD USES ONE SLOT ON THE MOTHERBOARD AND REQUIRES A COM SERIAL PORT. BOARD MAY ALSO BE USED IN A STAND ALONE ENVIRONMENT WITH ALMOST ANY COMPUTER THAT HAS A RS232 SERIAL PORT. FEATURES ON BOARD AUDIO AMP OR MAY BE USED WITH EXTERNAL AMPS.

DEMONSTRATION SOFTWARE AND A LIBRARY BUILDING PROGRAM ARE INCLUDED ON A 5 1/4 INCH PC/XT DISKETTE. FULL DOCUMENTATION AND SCHEMATICS ARE ALSO INCLUDED.



**NEW!** PRICE CUT! **\$69<sup>95</sup>** ASSEMBLED & TESTED

**NEW! IC TESTER! \$149.00**

SIMILAR TO BELOW EPROM PROGRAMMER. PLUGS IN TO YOUR PC OR XT. TESTS ALMOST ALL 14, 16, AND 20 PIN 74XX SERIES. INCLUDES STANDARD POWER, "S" AND "LS" DEVICES. ALSO TESTS CD4000 SERIES CMOS. SOFTWARE INCLUDED CAN EVEN DETERMINE PART NUMBERS OF MOST UNMARKED AND HOUSE NUMBERED DEVICES WITH SIMPLE MOD. THIS UNIT CAN ALSO TEST 6.4K AND 256K DRAMS WITH MANUAL AND SOFTWARE. \$149. PERFECT FOR SCHOOLS.

**PC/XT EPROM PROGRAMMER \$169**



ASK ABOUT OUR NEW PAL PROGRAMMER!

• LATEST DESIGN • PROGRAMS UP TO 4 DEVICES AT ONE TIME • FEATURES EASY TO USE MENU DRIVEN SOFTWARE THAT RUNS UNDER PC OR MS-DOS. • USES AN INTELLIGENT PROGRAMMING ALGORITHM FOR SUPER FAST (8X) EPROM BURNING. • THIS PLUG-IN BOARD ATTACHES TO AN EXTERNAL MINI CHASSIS CONTAINING 4 TEXTUOL Z.I.F. SOCKETS. • NO PERSONALITY MODULES REQUIRED • AUTOMATIC VPP SELECTION: 12.5V, 21V, OR 25V. • EPROM DATA CAN ALSO BE LOADED FROM OR SAVED TO A DISKETTE. • PROGRAMMING SOFTWARE SUPPORTS: 2716, 2732, 2732A, 2764, 2764A, 27128, 27128A, 27256, 27256A, 27512, AND 27512A. • ASSEMBLED AND TESTED, BURNED, IN WITH MANUAL. \$169 WITH SOFTWARE.

JUST RECEIVED. SAME AS ABOVE PROGRAMMER, BUT PROGRAMS 8 UNITS AT ONE TIME - \$299.

**Digital Research Computers**

P.O. BOX 381450 • OUNCANVILLE, TX 75138 • (214) 225-2309

TERMS: Add \$3.00 postage. We pay balance. Orders under \$15 add 75¢ handling. No C.O.D. We accept Visa and MasterCard. Texas Res. add 6-1/4% Tax. Foreign orders (except Canada) add 20% P & H. Orders over \$50 add 85¢ for Insurance.

# Copies of articles from this publication are now available from the UMI Article Clearinghouse.

For more information about the Clearinghouse, please fill out and mail back the coupon below.

## UMI Article Clearinghouse

Yes! I would like to know more about UMI Article Clearinghouse. I am interested in electronic ordering through the following system(s):

- DIALOG/Dialorder
- OnTyme
- Other (please specify) \_\_\_\_\_
- ITT Dialcom
- OCLC ILL Subsystem
- I am interested in sending my order by mail.
- Please send me your current catalog and user instructions for the system(s) I checked above.

Name \_\_\_\_\_  
 Title \_\_\_\_\_  
 Institution/Company \_\_\_\_\_  
 Department \_\_\_\_\_  
 Address \_\_\_\_\_  
 City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_  
 Phone (\_\_\_\_\_) \_\_\_\_\_

Mail to: University Microfilms International  
 300 North Zeeb Road, Box 91 Ann Arbor, MI 48106

RADIO-ELECTRONICS  
 ALL SALES SUBJECT TO THE TERMS OF OUR 90 DAY LIMITED WARRANTY. FREE COPY UPON REQUEST.


# Electronics Paperback Books
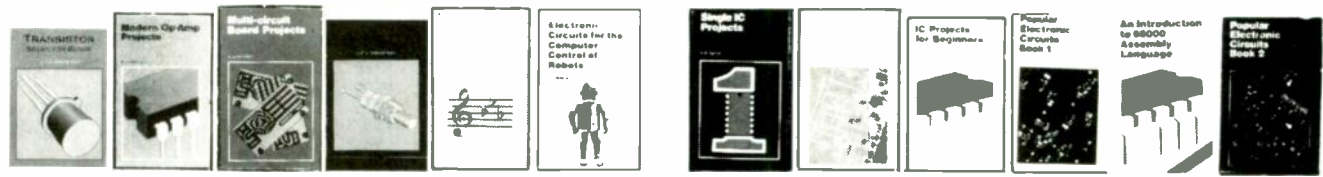
## GREAT ELECTRONICS PAPERBACKS FROM ETT



- BP125—25 SIMPLE AMATEUR BAND ANTENNAS.....\$5.00. All are inexpensive to build, yet perform well. Diodes, beams, triangle and even a mini rhombic.
- BP128—20 PROGRAMS FOR THE ZX SPECTRUM AND 16K ZX82.....\$5.75. Included with each program is a flow chart and a description of what happens. Notes for converting programs for use on other computers are also included.
- BP235—POWER SELECTOR GUIDE.....\$10.00. Complete guide to semiconductor power devices. More than 1000 power handling devices are included. They are tabulated in alpha-numeric sequence, by technical specs. Includes power diodes, Thyristors, Triacs, Power Transistors and FETs.
- BP234—TRANSISTOR SELECTOR GUIDE.....\$10.00. Companion volume to BP235. Book covers more than 1400 JEDEC, JIS and brand-specific devices. Also contains listing by case type, and electronic parameters. Includes Darlingtons, transistors, high-voltage devices, high-current devices, high power devices.
- BP99—MINI-MATRIX BOARD PROJECTS.....\$5.00. Here are 20 useful circuits that can be built on a mini-matrix board that is just 24 holes by ten copper-foil strips.
- BP157—HOW TO WRITE ZX SPECTRUM AND SPECTRUM · GAMES PROGRAMS.....\$5.95. A crystal-clear step-by-step guide to writing your own graphics games programs.
- BP117—PRACTICAL ELECTRONIC BUILDING BLOCKS—Book 1.....\$5.75. Oscillators, Timers, Noise Generators, Rectifiers, Comparators, Triggers and more.
- BP184—INTRO TO 68000 ASSEMBLY LANGUAGE.....\$6.50. The 68000 is a great new breed of microprocessor. Programming in assembly language increases the running speed of your programs. Here's what you need to know.
- BP179—ELECTRONIC CIRCUITS FOR THE COMPUTER CONTROL OF ROBOTS..... \$5.00. Data and circuits for interfacing the computer to the robots motors and sensors.
- BP126—BASIC & PASCAL IN PARALLEL.....\$4.95. Takes these two programming languages and develops programs in both languages simultaneously.
- 224—50 CMOS IC PROJECTS.....\$5.25. Includes sections on multivibrators, amplifiers and oscillators, trigger devices, and special devices.
- 225—A PRACTICAL INTRODUCTION TO DIGITAL IC'S.....\$4.95. Mainly concerned with TTL devices. Includes several simple projects plus a logic circuit test set and a digital counter timer.
- BP170—INTRODUCTION TO COMPUTER PERIPHERALS.....\$5.95. Shows how to use a variety of co computer add-ons in as non-technical a way as possible.
- 227—BEGINNERS GUIDE TO BUILDING ELECTRONIC PROJECTS.....\$5.00. How to tackle the practical side of electronics so you can successfully build electronic projects.
- BP169—HOW TO GET YOUR COMPUTER PROGRAMS RUNNING.....\$5.95. Shows how to identify error in program and what to do about them.
- BP194—MODERN OPTO DEVICE PROJECTS.....\$6.25. Crammed with great projects for the experimenter. Includes sections on Fiber optics, passive Infra-Red detectors, plus an assortment of miscellaneous projects.
- BP180—ELECTRONIC CIRCUITS FOR THE COMPUTER CONTROL OF MODEL RAILROADS.....\$6.25. It's easy to interface home computers to model railroad control. The main problem is in interfacing the computer to the system.
- BP110—HOW TO GET YOUR ELECTRONIC PROJECTS WORKING.....\$5.00. How to find and solve the common problems that can occur when building projects.

- BP33—ELECTRONIC CALCULATOR USERS HANDBOOK.....\$5.75. Invaluable book for all calculator owners. Tells how to get the most out of your calculator.
- BP36—50 CIRCUITS USING GERMANIUM, SILICON & ZENER DIODES.....\$5.00. A collection of useful circuits you'll want in your library.
- BP37—50 PROJECTS USING RELAYS, SCR'S & TRIACS.....\$5.00. Build priority indicators, light modulators, warning devices, light dimmers and more.
- BP39—50 FET TRANSISTOR PROJECTS.....\$5.50. RF amplifiers, test equipment, tuners, receivers, tone controls, etc.
- BP42—SIMPLE LED CIRCUITS.....\$5.00. A large selection of simple applications for this simple electronic component.
- BP127—HOW TO DESIGN ELECTRONIC PROJECTS.....\$5.75. Helps the reader to put projects together from standard circuit blocks with a minimum of trial and error.
- BP122—AUDIO AMPLIFIER CONSTRUCTION.....\$5.75. Construction details for preamps and power amplifiers up through a 100-watt DC-coupled FED amplifier.
- BP92—CRYSTAL SET CONSTRUCTION.....\$5.00. Everything you need to know about building crystal radio receivers.
- BP45—PROJECTS IN OPTOELECTRONICS.....\$5.00. Includes infra-red detectors, transmitters, modulated light transmission and photographic applications.
- BP48—ELECTRONIC PROJECTS FOR BEGINNERS.....\$5.00. A wide range of easily completed projects for the beginner. Includes some no-soldering projects.
- BP49—POPULAR ELECTRONIC PROJECTS.....\$5.50. Radio, audio, household and test equipment projects are all included.
- BP51—ELECTRONIC MUSIC AND CREATIVE TAPE RECORDING.....\$5.50. Shows how you can make electronic music at home with the simplest and most inexpensive equipment.
- BP56—ELECTRONIC SECURITY DEVICES.....\$5.00. Includes both simple and more sophisticated burglar alarm circuits using light, infra-red, and ultrasonics.
- BP59—SECOND BOOK OF CMOS IC PROJECTS.....\$5.00. More circuits showing CMOS applications. Most are of a fairly simple design.
- BP72—A MICROPROCESSOR PRIMER.....\$5.00. We start by designing a small computer and show how we can overcome its shortcomings.
- BP74—ELECTRONIC MUSIC PROJECTS.....\$5.95. Provides the experimenter with a variety of practical circuits including a Fuzz Box, Sustain Unit, Reverberation Unit, Tremolo Generator and more.
- BP91—AN INTRODUCTION TO RADIO DXING.....\$5.00. How you can tune in on those amateur and commercial broadcasts from around the world in the comfort of your home.
- BP94—ELECTRONIC PROJECTS FOR CARS AND BOATS.....\$5.00. Fifteen simple projects that you can use with your car or boat. All are designed to operate from 12-volt DC supplies.



**ELECTRONIC TECHNOLOGY TODAY INC.**  
 P.O. Box 240, Massapequa Park, NY 11762-0240

Name \_\_\_\_\_  
 Address \_\_\_\_\_  
 City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

SHIPPING CHARGES IN USA & CANADA

\$0.01 to \$5.00	\$1.00
\$5.01 to \$10.00	\$1.75
\$10.01 to \$20.00	\$2.75
\$20.01 to \$30.00	\$3.75
\$30.01 to \$40.00	\$4.75
\$40.01 to \$50.00	\$5.75
\$50.01 and above	\$7.00

**SORRY** No orders accepted outside of USA & Canada

Number of books ordered

Total price of merchandise \$ \_\_\_\_\_  
 Sales Tax (New York State Residents only) \$ \_\_\_\_\_  
 Shipping (see chart) \$ \_\_\_\_\_

All payments must be in U.S. funds

Total Enclosed \$ \_\_\_\_\_

H1287

## NEC V20 & V30 CHIPS

Replace the 8086 or 8088 in Your IBM-PC and Increase its Speed by up to 40%!

Part No.	Price
UPD70108-5 (5MHz) V20 Chip. . . . .	\$ 8.75
UPD70108-8 (8MHz) V20 Chip. . . . .	\$10.75
UPD70108-10 (10MHz) V20 Chip. . . . .	\$29.95
UPD70116-8 (8MHz) V30 Chip. . . . .	\$13.75
UPD70116-10 (10MHz) V30 Chip. . . . .	\$29.95

## 7400

Part No.	1-9	10+	Part No.	1-9	10+
7400	29	19	7485	65	55
7402	29	19	7486	45	35
7404	29	19	7489	2.05	1.95
7405	35	25	7490	49	39
7406	39	29	7493	45	35
7407	39	29	74121	45	35
7408	35	25	74123	55	45
7410	29	19	74125	55	45
7414	49	39	74126	69	59
7416	39	29	74143	3.95	3.85
7417	39	29	74150	1.35	1.25
7420	35	25	74154	1.35	1.25
7430	35	25	74158	1.59	1.49
7432	39	29	74173	85	75
7438	39	29	74174	59	49
7442	55	45	74175	59	49
7445	79	69	74176	99	89
7446	89	79	74181	1.95	1.85
7447	79	69	74188	1.95	1.85
7448	2.05	1.95	74193	79	69
7472	89	79	74198	1.85	1.75
7473	39	29	74221	99	89
7474	39	29	74273	1.95	1.85
7475	49	39	74365	65	55
7476	45	35	74367	65	55

## 74LS

74LS00	29	19	74LS165	75	65
74LS02	29	19	74LS166	99	89
74LS04	35	25	74LS173	59	49
74LS05	35	25	74LS174	49	39
74LS06	1.09	99	74LS175	49	39
74LS07	1.09	99	74LS189	4.59	4.49
74LS08	29	19	74LS191	59	49
74LS10	29	19	74LS193	79	69
74LS14	49	39	74LS221	69	59
74LS27	35	25	74LS240	69	59
74LS30	29	19	74LS243	69	59
74LS32	35	25	74LS244	69	59
74LS42	49	39	74LS245	89	79
74LS47	99	89	74LS259	99	89
74LS53	39	29	74LS273	89	79
74LS74	35	25	74LS279	49	39
74LS75	39	29	74LS322	4.05	3.95
74LS76	55	45	74LS365	49	39
74LS85	59	49	74LS366	49	39
74LS86	35	25	74LS367	49	39
74LS90	49	39	74LS368	49	39
74LS93	49	39	74LS373	79	69
74LS123	59	49	74LS374	79	69
74LS125	49	39	74LS383	89	79
74LS138	49	39	74LS390	6.05	5.95
74LS139	49	39	74LS624	2.05	1.95
74LS154	1.09	99	74LS629	2.95	2.85
74LS157	45	35	74LS640	1.09	99
74LS158	45	35	74LS645	1.09	99
74LS163	59	49	74LS670	1.09	99
74LS164	59	49	74LS688	2.39	2.29

## 74S/PROMS\*

74S00	29	74S188*	1.49
74S04	29	74S189	1.69
74S08	35	74S196	2.49
74S10	29	74S240	1.49
74S32	35	74S244	1.49
74S74	45	74S253	1.49
74S85	79	74S287*	1.49
74S86	49	74S288*	1.49
74S124	2.75	74S373	1.49
74S174	79	74S374	1.49
74S175	79	74S472*	2.95

## 74F

74F00	29	74F139	69
74F04	29	74F157	69
74F08	29	74F193	2.95
74F10	29	74F240	99
74F32	29	74F244	99
74F74	39	74F253	69
74F86	39	74F373	99
74F138	69	74F374	99

## CD—CMOS

CD4001	19	CD4076	59
CD4008	69	CD4081	25
CD4011	69	CD4082	25
CD4013	29	CD4093	35
CD4016	29	CD4094	39
CD4017	49	CD40103	2.49
CD4018	59	CD40108	7.49
CD4020	59	CD40109	7.49
CD4024	49	CD4510	69
CD4027	35	CD4511	69
CD4030	29	CD4520	75
CD4040	65	CD4522	79
CD4049	29	CD4538	89
CD4050	29	CD4541	89
CD4051	59	CD4543	79
CD4052	59	CD4553	4.95
CD4053	59	CD4555	79
CD4063	1.49	CD4559	7.95
CD4066	2.49	CD4566	2.49
CD4067	1.29	CD4583	89
CD4069	25	CD4584	39
CD4070	25	CD4585	89
CD4071	25	MC14411P	8.95
CD4072	25	MC14490P	4.49

## MICROPROCESSOR COMPONENTS

MISCELLANEOUS CHIPS		6500/6800/68000 Cont.		8000 SERIES Cont.	
Part No.	Price	Part No.	Price	Part No.	Price
D765AC	4.95	6845	3.95	8228	2.95
WD9216	6.95	6850	1.95	8237-5	4.95
95H90	9.95	6852	1.49	8243	2.25
Z80	1.25	MC68000LB	11.95	8250A	6.49
Z80-CTC	1.79	MC68000L10	13.95	8250B (For IBM)	6.95
Z80-DART	4.95	MC68010L10	8.95	8251A	1.89
Z80-PIO	1.79	MC68020RC12B	16.95	8253-5	1.95
Z80A	1.69	MC68881RC12A	14.95	8254	4.95
Z80A-CTC	1.79	8001	3.95	8255A-5	1.89
Z80A-DART	4.95	80031	9.95	8257-5	1.95
Z80A-PIO	1.69	80035	1.95	8259-5	2.25
Z80A-SIO/O	5.75	80073	9.95	8272	4.95
Z80B	3.49	8080A	2.95	8275-5	2.95
Z80B-CTC	3.95	8085A	2.49	8741	9.95
Z80B-PIO	4.29	8086	5.95	8742	29.95
8008-2	6.95	8086-2	6.95	8748 (25V)	9.95
8008-2 (8MHz)	129.95	8087-1 (10MHz)	229.95	8748A (HMOS) (2V)	9.95
8087-1 (10MHz)	229.95	8087-2 (8MHz)	169.95	8751	39.95
8087-2 (8MHz)	169.95	8088	6.49	8755	14.95
8088	6.49	8088-2	8.95	DATA ACQUISITION	
8089-2	4.95	8116	4.95	ADC0804LCN	3.19
8155-2	2.49	8155	2.49	ADC0808CCN	5.95
8156	3.95	8156-2	3.49	ADC0809CCN	3.95
8202	3.95	8156-2	3.49	ADC1205CGJ-1	19.95
8203	3.95	8202	3.95	DAC0808LCN	1.95
8212	1.75	8203	3.95	DAC1008LCN	4.95
8214	1.79	8212	1.49	AY-3-1015D	4.95
8224	2.25	8224	2.25	AY-5-1013A	2.95

## MICROPROCESSOR SALE!

Part No.	Price
8052AHBASIC CPU w/BASIC Interpreter. . . . .	\$ 29.95
MC68000L8 32-Bit MPU (8-Bit Data Bus). . . . .	\$ 19.95
MC68701 8-Bit EPROM Microcomputer . . . . .	\$ 14.95
MC68705P3S 8-Bit EPROM Microcomputer . . . . .	\$ 14.95
MC68705U3L 8-Bit EPROM Microcomputer . . . . .	\$ 10.95
80286-10 16-Bit Hi Performance MPU. . . . .	\$ 99.95
80287-8 Math Co-processor (8MHz). . . . .	\$299.95
80287-10 Math Co-processor (10MHz). . . . .	\$329.95
80387-16 Math Co-processor (16MHz) <sup>GRID ARRAY</sup>	\$494.95

## DYNAMIC RAMS

Part No.	Price
4116-15	16,384 x 1 (150ns) . . . . . 89
4128-20	131,072 x 1 (200ns) (Piggyback) . . . . . 3.25
4164-120	65,536 x 1 (120ns) . . . . . 1.75
4164-150	65,536 x 1 (150ns) . . . . . 1.25
4164-200	65,536 x 1 (200ns) . . . . . 99
TMS4416-12	16,384 x 4 (120ns) . . . . . 3.49
81118	16,384 x 1 (120ns) . . . . . 49
41256-100	262,144 x 1 (100ns) . . . . . 4.95
41256-120	262,144 x 1 (120ns) . . . . . 3.95
41256-150	262,144 x 1 (150ns) . . . . . 3.25
50464 15	65,536 x 4 (150ns) (4464) . . . . . 4.95
511009P-10	1,048,576 x 1 (100ns) 1 Meg . . . . . 34.95
514256P-10	2,097,152 x 4 (100ns) 1 Meg . . . . . 29.95

## STATIC RAMS

2016-12	2048 x 8 (120ns) . . . . . 1.69
2018-45	2048 x 8 (45ns) . . . . . 6.25
2102-2L	1024 x 4 (250ns) Low Power . . . . . 1.95
2114N	1024 x 4 (450ns) . . . . . 99
2114N-2L	1024 x 4 (200ns) Low Power . . . . . 1.49
21C14	1024 x 4 (200ns) (CMOS) . . . . . 49
2149	1024 x 4 (45ns) . . . . . 2.49
5101	450ns CMOS . . . . . 1.89
6116P-3	2048 x 8 (150ns) CMOS . . . . . 1.89
6116LP-3	2048 x 8 (150ns) LP CMOS . . . . . 1.95
6264LP 12	8192 x 8 (120ns) LP CMOS . . . . . 4.25
6264P-15	8192 x 8 (150ns) CMOS . . . . . 3.49
6264LP-15	8192 x 8 (150ns) LP CMOS . . . . . 3.75
6514	1024 x 4 (350ns) CMOS . . . . . 3.49
43256-15L	32,768 x 8 (150ns) CMOS Low Power . . . . . 11.95

## EPROMS

TMS2516	2048 x 8 (450ns) 25V. . . . . 6.95
TMS2532	4096 x 8 (450ns) 25V. . . . . 6.95
TMS2532A	4096 x 8 (450ns) 21V. . . . . 5.95
TMS2564	8192 x 8 (450ns) 25V. . . . . 9.95
TMS2716	2048 x 8 (450ns) 3 Voltage . . . . . 9.95
1702A	256 x 8 (1µs) . . . . . 6.95
2708	1024 x 8 (450ns) . . . . . 4.95
2716	2048 x 8 (450ns) 25V . . . . . 3.75
2716-1	2048 x 8 (350ns) 25V . . . . . 4.25
27C16	2048 x 8 (450ns) 25V (CMOS) . . . . . 5.49
2732	4096 x 8 (450ns) 25V. . . . . 3.95
2732A-20	4096 x 8 (200ns) 21V. . . . . 4.25
2732A-25	4096 x 8 (250ns) 21V. . . . . 3.95
27C32	4096 x 8 (450ns) 25V (CMOS) . . . . . 5.95
2764-20	8192 x 8 (200ns) 21V. . . . . 4.25
2764-25	8192 x 8 (250ns) 21V. . . . . 3.75
2764A-45	8192 x 8 (250ns) 12.5V. . . . . 3.95
2764A-25	8192 x 8 (450ns) 21V. . . . . 2.95
27C64-15	8192 x 8 (150ns) 21V (CMOS) . . . . . 6.49
27128-20	16,384 x 8 (200ns) 21V. . . . . 6.95
27128-25	16,384 x 8 (250ns) 21V. . . . . 5.95
27128A-25	16,384 x 8 (250ns) 12.5V. . . . . 5.25
27C128-25	16,384 x 8 (250ns) 21V (CMOS) . . . . . 6.95
27256-20	32,768 x 8 (200ns) 12.5V. . . . . 6.95
27256-25	32,768 x 8 (250ns) 12.5V. . . . . 5.95
27C256-25	32,768 x 8 (250ns) 12.5V (CMOS) . . . . . 7.95
27512-20	65,536 x 8 (200ns) 12.5V. . . . . 13.49
27512-25	65,536 x 8 (250ns) 12.5V. . . . . 11.95
68764	8192 x 8 (450ns) 25V. . . . . 13.95

## EEPROMS

2816A	2048 x 8 (350ns) 5V Read/Write . . . . . 5.95
2817A	2048 x 8 (350ns) 5V Read/Write . . . . . 7.95
2865A	8192 x 8 (250ns) 5V Read/Write . . . . . 9.95
52B13 (21V)	2048 x 8 (350ns) 5V Read Only . . . . . 1.49

## COMMODORE CHIPS

WD1770	11.95
S13052P	2.49
6502	2.65
6504A	1.95
6507	4.39
6510	9.95
6520	1.95
6525	3.95
6526	14.95
6529	2.95
6532	6.49
6545-1	4.95
6551	4.49
6560	10.95
6567	14.95
6569	24.95
6572	8.95
6581 (12V)	14.95
6582 (9V)	14.95
8360	14.95
8501	10.95
8502	


# Worldwide • Since 1974

• QUALITY COMPONENTS • COMPETITIVE PRICING  
• PROMPT DELIVERY

Mail Order Electronics • Worldwide  
**Jameco**  
ELECTRONICS

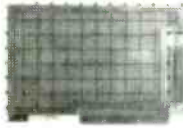
## Jameco NEW! General Purpose Prototype PC Boards

- Wire Wrap
- Component Testing
- Point-to-Point Wiring
- 31/62 Connection



JE417 (Pictured)

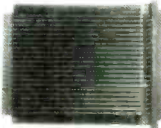- JE411 (6 1/2", No Pads, Gen. Purp.) . . . \$12.95
- JE415 (6 1/2", No Pads, PC/XT) . . . \$14.95
- JE417 (6 1/2", Plated w/Pads, PC/XT) . . . \$19.95



### Extender Boards Designed for Troubleshooting and Testing

JE419 (Pictured)


- JE419 (5" Extender, 22/44 Connector) . . \$19.95
- JE421 (4" Extender, 31/62 Connector) . . \$19.95

### Accessories for Commodore VIC-20, C-64 & C-128

JE232CM (Pictured)

- \*CM1 (300B Modem VIC-20, C-64) . \$19.95
- \*JE232CM (RS232 Inter. VIC-20, C-64) . \$39.95
- CPS10 (C-64 Power Supply) . . . \$39.95
- CPS128 (C-128 Power Supply) . . . \$59.95

## ZUCKERBOARD

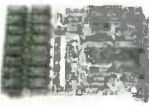

### TANDY 1000 Expansion Memory Half Card

Expand the memory of your Tandy 1000 (128K Version) to as much as 640K. Also includes DMA controller chip.

- TE512 Includes 512K RAM. . . \$119.95
- TANC Plug-in Clock option chip (only) . . . \$39.95

### 20Meg Hard Disk

- T20MB 20MB Hard Disk Drive Board for Tandy 1000. . . \$494.95
- SX20MB 20MB Hard Disk Drive Board for Tandy 1000SX. . . \$499.95



### TANDY 1000 Multifunction Board with Clock Calendar

Expand the memory on your Tandy 1000 (128K Version) to as much as 640K. Complete with an RS232 port, clock/calendar, RAM Disk, Printer Spooler and on-board DMA controller chip.

- MT512 Includes 512K RAM. . . \$199.95

## DATA TRONICS

### 2400/1200/300 Modems



• Hayes command compatible • Built 103/212A compatible • Auto-dial/auto-answer • FCC approved • 1-year warranty • The 1200H & 2400S include MaxMite Communication Software • The 1200C & 2400E do not include software

- 1200H 1200/300 Baud Internal Modem. . . \$ 79.95
- 2400S 2400/1200/300 Internal Modem. . . \$174.95
- 1200C 1200/300 Baud External Modem. . . \$119.95
- 2400E 2400/1200/300 External Modem . . . \$219.95

## INTRODUCING JAMECO'S NEW COMPUTER KITS!!

### Jameco's IBM™ AT Compatible Kit! Mini-286 6/8/10/12 MHz Kit!

EGA Monitor  
TE5154 \$399.95  
EGA Card  
JE1055 \$149.95  
(not included)



Part No.	Description	Price
JE1043	1.2M/360K Floppy Control.	\$ 49.95
JE1015	XT/AT Style Keyboard	\$ 59.95
41256-120	512K RAM (18 Chips)	\$ 71.10
JE1012	Baby AT Flip-Top Case	\$ 69.95
JE1032	200W Power Supply	\$ 89.95
JE1022	5 1/4" High Density Disk Drive	\$109.95
JE1003	Baby AT Motherboard (Zero-K RAM-incl. Award BIOS ROM)	\$399.95

Regular List \$850.80  
**SAVE \$50.85!**

### JE1008 IBM™ AT Compatible Kit. . . . . \$799.95

### Jameco's IBM PC/XT Compatible Kit

Part No.	Description	Price
4164-150	128K RAM (18 Chips)	\$22.50
JE1040	Floppy Controller Card	\$29.95
JE1010	Flip-Top Case	\$34.95
JE1015	XT/AT Style Keyboard	\$59.95
JE1030	150 Watt Power Supply	\$69.95
JE1050	Mono/Graph. Crd. w/PPort	\$59.95
JE1020	5 1/4" DSDD Disk Drive	\$89.95
GREEN	12" Mono. Green Monitor	\$99.95
JE1000	XT Motherboard (Zero-K RAM-incl. Award BIOS ROM)	\$89.95

**FREE! QUICKSOFT PC  
WRITE WORD PROCESSING  
SOFTWARE INCLUDED!**

Regular List \$557.10

### JE1004 (IBM™ PC/XT Compatible Kit) . . . . . \$479.95

### Jameco's 4.77/8MHz Turbo IBM Compatible Kit

Same as JE1004 except comes with 640K RAM, JE1001 (Turbo) 4.77/8MHz motherboard, JE1071 multi I/O with controller and graphics, and AMBER monitor.

SAVE \$70.70 Regular List \$670.65

### JE1005 (IBM™ PC/XT Turbo Compatible Kit) . \$599.95

### IBM Compatible Motherboards

- 4.77/8MHz operation (Turbo only)
- 8087 Math Co-processor capability
- BIOS ROM included

- JE1001 4.77/8MHz . . . \$129.95 \$104.95
- JE1000 4.77MHz . . . \$409.95 \$ 89.95

### Additional Add-Ons Available!

#### Color Graphics Card for PC/XT/AT



- Text 40 or 80 x 25 • Graphics 320 or 640 x 200 • Parallel Printer Port • Manual included
- JE1052 . . . . . \$49.95

#### EGA Card for PC/XT/AT



- Graphics 720 x 348 • 16 out of 64 colors • Manual included
- JE1055 . . . . . \$149.95

#### I/O Cards for PC/XT/AT




- Printer Port
- RS232 Port
- Game Port
- Manual included
- JE1060 (Pictured)
- JE1060 I/O for XT. . . . . \$59.95
- JE1065 I/O for AT. . . . . \$59.95

#### Multi I/O w/Controller & Graphics for PC/XT



- Printer port • RS232 port • Floppy controller • Graphics • Manual included
- JE1071 . . . . . \$119.95

## Jameco Solderless Breadboard Sockets

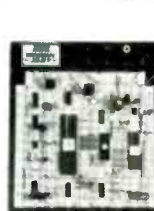

Part No.	Dim. L x W	Contact Points	Binding Posts	Price
JE20	6 1/2" x 3 1/4"	200	0	\$ 2.29
JE21	3 1/4" x 2 1/8"	400	0	\$ 4.49
JE22	6 1/2" x 1 3/8"	630	0	\$ 5.95
JE23	6 1/2" x 2 1/8"	830	0	\$ 7.49
JE24	6 1/2" x 3 1/8"	1,360	2	\$14.95
JE25	6 1/2" x 4 1/4"	1,660	3	\$22.95
JE26	6 1/2" x 5 1/4"	2,390	4	\$27.95
JE27	7 1/4" x 7 1/2"	3,220	4	\$37.95

## Jameco Extended 80-Column Card for Apple IIe



• 80 Col /64K RAM • Doubles amount of data your Apple IIe can display as well as its memory capacity • Ideal for word processing • Complete with instructions

### JE864 \$49.95

### ADD12 (Disk Drive II, II+, IIe) \$99.95

### Additional Apple Compatible Products Available

## NEW! Seagate 20, 30 & 40MB Half Height Hard Disk Drives



ST225K (Pictured)

- ST225 20MB Drive only (PC/XT/AT) . . . \$269.95
- ST225K 20MB w/Controller (PC/XT) . . . \$319.95
- ST23E 30MB Drive only (PC/XT/AT) . . . \$299.95
- ST238K 30MB w/Cont. (PC/XT/AT) . . . \$339.95
- ST251 40MB Drive only (PC/XT/AT) . . . \$469.95
- ST251XT 40MB w/Cont. Card (PC/XT) . . . \$549.95
- ST251AT 40MB w/Cont. Card (AT) . . . \$589.95



JE1022 (Pictured)

- JE1020 (360K Drive, PC/XT/AT) . . . \$ 89.95
- JE1022 (1.2MB, AT Compatible) . . . \$109.95

### DATA BOOKS

- 30003 National Linear Data Book (82) . . . \$19.95
- 30005 Logic Data Book - Vol. II (84) . . . \$319.95
- 30005 Intersil Data Book (87) . . . \$14.95
- 21398 CMOS Cookbook (86) . . . \$39.95
- 210830 Intel Memory Handbook (87) . . . \$17.95
- 230843 Intel Microsystem Hndbk. Set (87) . . . \$24.95

### MUFFIN/SPRITE-STYLE FANS



- TA450S. . . . . \$11.95
- Tonn Industries (4 6/8" sq., 50 cfm)
- SU2A1. . . . . \$11.95
- EG&G Rotron (3 1/2" square, 34 cfm)

U.S. Funds Only  
Shipping: Add 5% plus \$1.50 Insurance

California Residents:  
Add 6%, 6 1/2% or 7%  
Sales Tax  
FAX 415-592-2503

12/87

1355 SHOREWAY RD., BELMONT, CA 94002 • FOR ORDERS ONLY 415-592-8097 • ALL OTHER INQUIRIES 415-592-8121

\$20 Minimum Order  
IBM is a registered trademark of International Business Machines



Data Sheets — 50¢ each  
Prices Subject to Change

Send \$1.00 Postage for a  
FREE 1988 CATALOG

Telex: 176043

©1987 Jameco Electronics

# 256K STATIC 150ns \$1295 256K DRAMS 150ns \$295

32K X 8

256K X 1

## STATIC RAMS

2112	256x4	(450ns)	2.99
2114	1024x4	(450ns)	.99
2114L	1024x4	(200ns)(Low Power)	1.49
TMM2016-100	2048x8	(100ns)	1.95
HM6116-4	2048x8	(200ns)(CMOS)	1.79
HM6116-3	2048x8	(150ns)(CMOS)	1.85
HM6116LP-4	2048x8	(200ns)(CMOS)(LP)	1.85
HM6116LP-3	2048x8	(150ns)(CMOS)(LP)	1.90
HM6116LP-2	2048x8	(120ns)(CMOS)(LP)	2.45
HM6264LP-15	8192x8	(150ns)(CMOS)(LP)	3.95
HM6264LP-12	8192x8	(120ns)(CMOS)(LP)	4.49
HM43256LP-15	32768x8	(150ns)(CMOS)(LP)	12.95
HM43256LP-12	32768x8	(120ns)(CMOS)(LP)	14.95
HM43256LP-10	32768x8	(100ns)(CMOS)(LP)	19.95

## DYNAMIC RAMS

4116-250	16384x1	(250ns)	.49
4116-200	16384x1	(200ns)	.89
4116-150	16384x1	(150ns)	.99
4116-120	16384x1	(120ns)	1.49
MK4332	32768x1	(200ns)	6.95
4164-150	65536x1	(150ns)	1.29
4164-120	65536x1	(120ns)	1.55
MCM6665	65536x1	(200ns)	1.95
TMS4164	65536x1	(150ns)	1.95
4164-REFRESH	65536x1	(150ns)(PIN 1 REFRESH)	2.95
TMS4416	16384x4	(150ns)	3.75
4112B-150	131072x1	(150ns)	5.95
TMS4464-15	65536x4	(150ns)	4.95
41256-150	262144x1	(150ns)	2.95
41256-120	262144x1	(120ns)	3.95
41256-100	262144x1	(100ns)	4.95
HM51258-100	262144x1	(100ns)(CMOS)	4.95
1MB-120	1048576x1	(120ns)	19.95
1MB-100	1048576x1	(100ns)	24.95

## EPROMS

2708	1024x8	(450ns)	4.95
2716	2048x8	(450ns)(5V)	3.49
2716-1	2048x8	(350ns)(5V)	3.95
TMS2532	4096x8	(450ns)(5V)	5.95
2732	4096x8	(450ns)(5V)	3.95
2732A	4096x8	(250ns)(5V)(21V PGM)	3.95
2732A-2	4096x8	(200ns)(5V)(21V PGM)	4.25
27C64	8192x8	(250ns)(5V)(CMOS)	4.95
2764	8192x8	(450ns)(5V)	3.49
2764-250	8192x8	(250ns)(5V)	3.69
2764-200	8192x8	(200ns)(5V)	4.25
MCM68766	8192x8	(350ns)(5V)(24 PIN)	15.95
27128	16384x8	(250ns)(5V)	4.25
27C256	32768x8	(250ns)(5V)(CMOS)	7.95
27256	32768x8	(250ns)(5V)	6.95
27512	65536x8	(250ns)(5V)	11.95
27C512	65536x8	(250ns)(5V)(CMOS)	12.95

5V Single 5 Volt Supply      21V PGM: Program at 21 Volts

## \*\*\*\*\* HIGH-TECH \*\*\*\*\*

### HM43256LP-15 \$12.95

- \* 32K x 8 STATIC RAM
- \* LOW POWER CONSUMPTION
- \* HIGH SPEED — 100ns AVAILABLE
- \* LOW STAND-BY CURRENT (2ma MAX.)
- \* TTL COMPATIBLE INPUT AND OUTPUTS

## \*\*\*\*\* SPOTLIGHT \*\*\*\*\*

### CMOS

4001	.19	4049	.29
4011	.19	4050	.29
4012	.25	4051	.69
4013	.35	4052	.69
4015	.29	4053	.69
4016	.29	4060	.69
4017	.49	4066	.29
4018	.69	4069	.19
4020	.59	4070	.29
4021	.59	4081	.22
4023	.25	4093	.49
4024	.49	14411	9.95
4025	.25	14433	14.95
4027	.39	14497	6.95
4028	.65	4503	.49
4040	.69	4511	.69
4042	.59	4518	.85
4044	.69	4528	.79
4046	.69	4538	.95
4047	.69	4702	12.95

### HIGH SPEED CMOS

74HC00	74HC00	74HC00	74HC00
74HC00	21	74HC02	25
74HC02	21	74HC02	25
74HC04	25	74HC04	27
74HC08	25	74HC08	27
74HC14	35	74HC14	27
74HC32	35	74HC32	45
74HC74	35	74HC138	55
74HC86	45	74HC161	79
74HC138	45	74HC240	89
74HC139	49	74HC244	89
74HC151	59	74HC245	99
74HC154	1.09	74HC273	99
74HC157	55	74HC373	99
74HC244	85	74HC374	99
74HC245	85	74HC393	99
74HC273	69	74HC401	1.19
74HC373	69	74HC4040	99
74HC374	69	74HC4060	1.49

## 74LS00

74LS00	16	74LS112	29	74LS241	69
74LS01	18	74LS122	45	74LS242	69
74LS02	17	74LS123	49	74LS243	69
74LS03	18	74LS124	2.75	74LS244	69
74LS04	16	74LS125	39	74LS245	79
74LS05	18	74LS126	39	74LS251	49
74LS08	19	74LS132	39	74LS259	49
74LS09	18	74LS133	49	74LS257	39
74LS10	16	74LS136	39	74LS258	49
74LS11	22	74LS138	39	74LS259	1.29
74LS12	22	74LS139	39	74LS260	49
74LS13	26	74LS145	99	74LS266	39
74LS14	39	74LS147	99	74LS273	39
74LS15	26	74LS148	99	74LS279	39
74LS20	17	74LS151	39	74LS280	1.98
74LS21	22	74LS153	39	74LS283	59
74LS22	22	74LS154	1.49	74LS290	89
74LS27	23	74LS155	59	74LS293	89
74LS28	26	74LS156	49	74LS299	1.49
74LS30	17	74LS157	35	74LS322	3.95
74LS32	18	74LS158	29	74LS323	2.49
74LS33	29	74LS160	29	74LS365	39
74LS37	26	74LS161	39	74LS367	39
74LS38	26	74LS162	49	74LS368	39
74LS42	39	74LS163	39	74LS373	79
74LS47	75	74LS164	49	74LS374	79
74LS48	85	74LS165	65	74LS375	95
74LS51	17	74LS166	95	74LS377	79
74LS52	18	74LS168	69	74LS381	1.19
74LS53	24	74LS173	49	74LS393	79
74LS75	29	74LS174	39	74LS451	1.49
74LS76	29	74LS175	39	74LS624	1.95
74LS83	49	74LS191	49	74LS640	99
74LS85	49	74LS192	69	74LS645	99
74LS86	22	74LS193	69	74LS670	89
74LS89	39	74LS194	69	74LS682	3.20
74LS92	49	74LS195	69	74LS688	49
74LS93	39	74LS196	59	74LS783	22.95
74LS95	49	74LS197	59	25LS2521	2.80
74LS107	36	74LS221	59	26LS31	1.95
74LS109	34	74LS240	69	26LS32	1.95

# TOLL FREE U.S. & CANADA (800) 538-5000

### 8000

8031	3.95
8035	1.49
8039	1.95
8052AH BASIC	34.95
8080	2.49
8085	1.95
8086	6.49
8087 5V/Hz	159.95
8087-2 8MHz	159.95
8088	5.99
8088-2	7.95
8155	2.49
8155-2	2.49
8741	9.95
8748	7.95
8749	12.95
8755	14.95
80286	79.95
80287 6MHz	179.95
80287-8 8MHz	249.95
80287-10MHz	309.95

### 6500 1.0 MHz

6502	2.25
65C02 (CMOS)	7.95
6520	1.65
6522	2.95
6526	13.95
6532	5.95
6545	2.95
6551	2.95

### 2.0 MHz

6502A	2.69
6520A	2.95
6522A	5.95
6532A	11.95
6545A	3.95
6551A	6.95

### 3.0 MHz

6502B	4.25
-------	------

### Z-80 2.5 MHz

Z80-CPU	1.25
Z80A-CPU	1.29
Z80A-CTC	1.69
Z80A-DART	5.95
Z80A-DMA	5.95
Z80A-PIO	1.89
Z80A-SIO 0	5.95
Z80A-SIO 1	5.95
Z80A-SIO 2	5.95

### 6.0 MHz

Z80B-CPU	2.75
Z80B-CTC	4.25
Z80B-PIO	4.25
Z80B-DART	6.95
Z80B-SIO 0	12.95
Z80B-SIO 2	12.95
Z8671 ZILOG	9.95

### DISK CONTROLLERS

1771	4.95
1791	9.95
1793	9.95
1795	12.95
1797	12.95
2791	19.95
2793	19.95
2797	29.95
8272	4.39
UPD765	4.39
MB8876	12.95
1691	6.95
2143	6.95
9216	6.29

### V 20 SERIES

V20* 5 MHz-z	8.95
V20* 8 MHz-z	10.95
V30 8 MHz-z	13.95

\*Replaces 8088 to speed up your PC by 10 to 40%

### CRYSTALS

32.768 KHz	95
1.0 MHz	2.95
1.8432	2.95
2.0	1.95
2.4576	1.95
3.57954E	1.95
4.0	1.95
5.0	1.95
5.0688	1.95
6.0	1.95
6.144	1.95
8.0	1.95
10.0	1.95
10.73863E	1.95
12.0	1.95
14.31818	1.95
16.0	1.95
18.0	1.95
18.432	1.95
20.0	1.95
22.1184	1.95
24.0	1.95
32.0	1.95
74F64	55
74F74	39
74F86	55
74F138	79
74F139	79
74F253	89
74F157	1.69
74F240	3.29

### LINEAR

LM567	79
NE570	2.95
NE592	98
LM733	49
LM733	98
LM301	79
LM309K	1.25
LM311	59
LM311H	89
LM317K	3.49
LM317T	69
LM318	1.49
LM319	1.25
LM320	7900
LM323K	3.49
LM332	34
LM333	3.95
LM334	1.19
LM335	1.79
LM336	1.75
LM338K	4.49
LM339	59
LM340	7800
LF353	59
LF356	99
LF357	99
LM358	59
LM380	89
LM383	1.95
LM386	89
LM393	45
LM394H	5.95
TL494	4.20
TL497	3.25
LM555	2.9
NE556	49
NE558	79
NE564	1.95
LM565	35
LM566	1.49
NE590	2.50
ULN2003	79
KR2206	3.95
KR221	2.95
LM2917	1.95
CA3046	89
CA3146	1.29
LM3373	1.29
LM338K	4.49
LM339	59
LM340	7800
LF353	59
LF356	99
LF357	99
LM358	59
LM380	89
LM383	1.95
LM386	89
LM393	45
LM394H	5.95
TL494	4.20
TL497	3.25
NE555	2.9
NE556	49
NE558	79
NE564	1.95
LM565	35
LM566	1.49
NE590	2.50
H-T-O-5 CAN, K-T-O-3, T-T-O-220	

### 8200

8203	14.95
8205	3.29
8212	1.49
8216	1.49
8224	2.25
8228	2.25
8237	3.95
8237-5	4.75
8243	1.95
8250	6.95
8251	1.29
8251A	1.69
8253	1.59
8253-5	1.95
8255	1.49
8255-5	1.19
8259	1.95
8259-5	2.29
8272	4.39
8275	16.95</



# 20 MEG HARD DISK DRIVE ON A CARD \$349!

## CAPACITORS

TANTALUM					
1.0 $\mu$ F	15V	.12	47 $\mu$ F	35V	.39
6.8	15V	.42	1.0	35V	.45
10	15V	.45	2.2	35V	.19
22	15V	.39	4.7	35V	.39
22	35V	.15	10	35V	.69

## DISC

DISC					
10 $\mu$ F	50V	.05	680	50V	.05
22	50V	.05	001 $\mu$ F	50V	.05
27	50V	.05	0022	50V	.05
33	50V	.05	.005	50V	.05
47	50V	.05	.01	50V	.07
68	50V	.05	.02	50V	.07
100	50V	.05	.05	50V	.07
220	50V	.05	1	12V	.10
560	50V	.05	1	50V	.12

## MONOLITHIC

01 $\mu$ F	50V	.14	1 $\mu$ F	50V	.18
047 $\mu$ F	50V	.15	47 $\mu$ F	50V	.25

## ELECTROLYTIC

RADIAL					
1 $\mu$ F	25V	.14	1 $\mu$ F	50V	.14
2.2	35V	.11	10	50V	.16
4.7	50V	.11	22	16V	.14
10	50V	.11	47	50V	.19
47	35V	.13	100	35V	.19
100	16V	.15	220	25V	.25
220	35V	.20	470	50V	.29
470	25V	.30	1000	16V	.29
2200	16V	.70	2200	16V	.70
4700	25V	1.45	4700	16V	1.25

## FRAME STYLE TRANSFORMERS

12.6 Volts AC	2 Amps	(CT)	5.95
12.6 Volts AC	4 Amps	(CT)	7.95
12.6 Volts AC	8 Amps	(CT)	10.95
25.2 Volts AC	2 Amps	(CT)	7.95

## 36 PIN CENTRONICS MALE

IDCEN36	RIBBON CABLE	3.95
CEN36	SOLDER CUP	1.85

## FEMALE

IDCEN36 F	RIBBON CABLE	4.95
CEN36PC	RT. Angle PC Mount	1.85

## EDGE CARD CONNECTORS

100 Pin Solder Tail S-100	125	3.95
100 Pin Wirewrap S-100	125	4.95
62 Pin Solder Tail IBM PC	100	1.95
50 Pin Solder Tail APPLE	100	2.95
44 Pin Solder Tail STD	156	1.95
44 Pin Wirewrap STD	156	4.95

## IDC CONNECTORS

DESCRIPTION	ORDER BY	CONTACTS					
		10	20	26	34	40	50
SOLDER HEADER	IDHxxS	.82	1.29	1.68	2.20	2.58	3.24
RIGHT ANGLE SOLDER HEADER	IDHxxSR	.85	1.35	1.76	2.31	2.72	3.39
WIREWRAP HEADER	IDHxxW	1.86	2.98	3.84	4.50	5.28	6.63
RIGHT ANGLE WIREWRAP HEADER	IDHxxWR	2.05	3.28	4.22	4.45	4.80	7.30
RIBBON WIREWRAP SOCKET	IDSxx	.63	.89	.95	1.29	1.49	1.69
RIBBON HEADER	IDMxx	---	5.50	6.25	7.00	7.50	8.50
RIBBON EDGE CARD	IDExx	.85	1.25	1.35	1.75	2.05	2.45

FOR ORDERING INSTRUCTIONS, SEE D-SUBMINIATURE CONNECTORS BELOW

## D-SUBMINIATURE CONNECTORS

DESCRIPTION	ORDER BY	CONTACTS						
		9	15	19	25	37	50	
SOLDER CUP	MALE	DBxxP	.45	.59	.69	.69	1.35	1.85
	FEMALE	DBxxS	.49	.69	.75	.75	1.39	2.29
RIGHT ANGLE PC SOLDER	MALE	DBxxPR	.49	.69	---	.79	2.27	---
	FEMALE	DBxxSR	.55	.75	---	.85	2.49	---
WIREWRAP	MALE	DBxxPWW	1.69	2.56	---	3.89	5.60	---
	FEMALE	DBxxSww	2.76	4.27	---	6.84	9.95	---
IDC RIBBON CABLE	MALE	IDBxxP	1.39	1.99	---	2.25	4.25	---
	FEMALE	IDBxxS	1.45	2.05	---	2.35	4.49	---
HOODS	METAL	MHOODxx	1.05	1.15	1.25	1.25	---	---
	GREY	HOODxx	.39	.39	---	.39	.69	.75

ORDERING INSTRUCTIONS: INSERT THE NUMBER OF CONTACTS IN THE POSITION MARKED \* OF THE ORDER BY PART NUMBER LISTED. EXAMPLE: A 15 PIN RIGHT ANGLE MALE PC SOLDER WOULD BE DB15PR

## MOUNTING HARDWARE 59C

## DIP CONNECTORS

DESCRIPTION	ORDER BY	CONTACTS								
		8	14	16	18	20	22	24	28	40
TOOLED SOLDER TAIL IC SOCKETS	AUGATxxST	62	.79	.89	1.09	1.29	1.39	1.49	1.69	2.49
TOOLED WIREWRAP IC SOCKETS	AUGATxxWW	1.30	1.80	2.10	2.40	2.50	2.90	3.15	3.70	5.40
COMPONENT CARRIES (DIP HEADERS)	ICCxx	.49	.59	.69	.99	.99	.99	.99	1.09	1.49
RIBBON CABLE DIP PLUGS (IDC)	IDPxx	.95	.49	.59	1.29	1.49	---	.85	1.49	1.59

FOR ORDERING INSTRUCTIONS, SEE D-SUBMINIATURE CONNECTORS ABOVE

CALL FOR VOLUME QUOTES

## VOLTAGE REGULATORS

TO-220 CASE				TO-3 CASE			
7805T	49	7805K	1.59	7905K	1.69		
7808T	49	7812K	1.39	7912K	1.49		
7812T	49						
7815T	49						
7905T	59						
7908T	59						
7912T	59	78L05	.49	79L05	.69		
7915T	59	78L12	.49	79L12	1.49		

LM323K 5 VOLTS, 3 AMPS, TO-3 4.79  
LM338K ADJUSTABLE, 5 AMPS, TO-3 6.95

## RESISTOR NETWORKS

SIP 10 PIN	9 RESISTOR	.69
SIP 8 PIN	7 RESISTOR	.59
DIP 16 PIN	8 RESISTOR	1.09
DIP 16 PIN	15 RESISTOR	1.09
DIP 14 PIN	7 RESISTOR	.99
DIP 14 PIN	13 RESISTOR	.99

## BYPASS CAPACITORS

.01 $\mu$ F CERAMIC DISC	100	\$5.00
.01 $\mu$ F MONOLITHIC	100	\$10.00
.1 $\mu$ F CERAMIC DISC	100	\$6.50
.1 $\mu$ F MONOLITHIC	100	\$12.50

## DISCRETE

1N751	15
1N759	15
1N4148	25 1.00
1N4004	10 1.00
1N5402	25
KBPO2	55
KB08A	.95
MDA990-2	35
N2222	.25
PN2222	.10
2N2905	.50
2N2907	.25
2N3055	.79
2N3904	.10
4N26	.69
4N27	.69
4N28	.69
4N33	.89
4N37	1.19
MCT-2	.59
MCT-6	1.29
TIL 111	2.25
2N3906	.10
2N4401	.25
2N4402	.25
2N4403	.25
2N6045	1.75
TIP31	.49

## IC SOCKETS

SOLDER TAIL	1.99	100-
8 PIN ST	1.10	10
14 PIN ST	1.10	.09
16 PIN ST	1.10	.10
18 PIN ST	1.15	.13
20 PIN ST	1.15	.15
22 PIN ST	1.15	.12
24 PIN ST	2.20	.15
28 PIN ST	2.22	.16
40 PIN ST	3.30	.22
64 PIN ST	1.95	1.49

WIREWRAP	8 PIN WW	59	69
14 PIN WW	69	52	
16 PIN WW	69	58	
18 PIN WW	99	90	
20 PIN WW	1.09	.98	
22 PIN WW	1.39	1.28	
24 PIN WW	1.49	1.35	
28 PIN WW	1.69	1.49	
40 PIN WW	1.99	1.80	

ZERO INSERTION FORCE	16 PIN ZIF	4.95	CALL
24 PIN ZIF	5.95	CALL	
28 PIN ZIF	6.95	CALL	
40 PIN ZIF	9.95	CALL	

## WISH SOLDERLESS BREADBOARDS

PART NUMBER	DIMENSIONS	DISTRIBUTION STRIP(S)	TIE POINTS	TERMINAL STRIP(S)	TIE POINTS	BINDING POSTS	PRICE
WBU-D	38 x 6.50"	1	100	---	---	---	2.95
WBU-T	1.38 x 6.50"	---	---	---	---	---	6.95
WBU 204-3	3.94 x 8.45"	1	100	2	1260	2	17.95
WBU 204	5.13 x 8.45"	4	400	2	1260	3	24.95
WBU 206	6.88 x 9.06"	5	500	3	1890	4	29.95
WBU-208	8.25 x 9.45"	7	700	4	2520	4	39.95

## EXTENDER CARDS FOR IBM

EXT-8088 \$29.95  
EXT-80286 \$39.95



## SHORTING BLOCKS

.1" CENTERS  
GOLD CONTACTS  
5/\$1.00

WHY THOUSANDS CHOOSE JDR  
\* QUALITY MERCHANDISE  
\* COMPETITIVE PRICES  
\* MOST ORDERS SHIPPED IN 24 HOURS  
\* FRIENDLY, KNOWLEDGEABLE STAFF  
\* MONEY BACK GUARANTEE (ASK FOR DETAILS)  
\* TOLL FREE TECHNICAL SUPPORT  
\* EXCELLENT CUSTOMER SERVICE



## WIREWRAP PROTOTYPE CARDS

FR-4 EPOXY GLASS LAMINATE WITH GOLD-PLATED EDGE-CARD FINGERS  
XT  
BOTH CARDS HAVE SILK SCREENED LEGENDS AND INCLUDES MOUNTING BRACKET

IBM-PR1 WITH 5V AND GROUND PLANE \$27.95  
IBM-PR2 AS ABOVE W/ DECODING LAYOUT \$29.95

## AT

IBM-PRAT LARGE 5V & GROUND PLANES \$29.95

## S-100

P100 1 BARE NO FOIL PADS \$15.15  
P100 2 HORIZONTAL BUS \$21.80  
P100 3 VERTICAL BUS \$21.80  
P100 4 SINGLE FOIL PADS PER HOLE \$22.75

## APPLE

P500 1 BARE NO FOIL PADS \$15.15  
P500 3 HORIZONTAL BUS \$22.75  
P500 4 SINGLE FOIL PADS PER HOLE \$21.80  
7060-45 FOR APPLE IIe AUX SLOT \$30.00

## PAGE WIRE WRAP WIRE PRECUT ASSORTMENT

IN ASSORTED COLORS \$27.50  
100ea 5.5" 6.0" 6.5" 7.0"  
250ea 2.5" 4.5" 5.0"  
500ea 3.0" 3.5" 4.0"

## SPOOLS

100 feet \$4.30 250 feet \$7.25  
500 feet \$13.25 1000 feet \$21.95  
Please specify color:  
Blue, Black, Yellow or Red

## SOCKET-WRAP I.D.™

\* SLIPS OVER WIRE WRAP PINS  
\* IDENTIFIES PIN NUMBERS ON WRAP SIDE OF BOARD  
\* CAN WRITE ON THE PLASTIC, SUCH AS AN IC #

Pins	Part #	Pck. of	Price
8	IDWRAP 08	10	1.95
14	IDWRAP 14	10	1.95
16	IDWRAP 16	10	1.95
18	IDWRAP 18	5	1.95
20	IDWRAP 20	5	1.95
22	IDWRAP 22	5	1.95
24	IDWRAP 24	5	1.95
28	IDWRAP 28	5	1.95
40	IDWRAP 40	5	1.95

PLEASE ORDER BY NUMBER OF PACKAGES (PCK. OF)

## EPROM ERASERS

### SPECTRONICS CORPORATION

Model	Timer	Chgp Capacity	Intensity (uW/cm²)	Unit Cost
PE 140	ND	9	8,000	589
PE 140T	YES	9	8,000	\$139
PE 240T	YES	12	9,600	\$189

## DATASE \$34.95

\* ERASES 2 EPROMS IN 10 MINUTES TIME  
\* VERY COMPACT - NO DRAWER  
\* THIN METAL SHUTTER PREVENTS UV LIGHT FROM ESCAPING

## LIGHT EMITTING DIODES

### LED DISPLAYS

FND-357(359)	COM CATHODE	362"	1.25
FND-500(503)	COM CATHODE	5"	1.49
FND-507(510)	COM ANODE	5"	1.49
MAN-72	COM ANODE	3"	.99
MAN-74	COM CATHODE	3"	.99
TIL-313	COM CATHODE	3"	.45
TIL-311	4x7 HEX W LOGIC	270"	10.95

### DIFFUSED LEDS

JUMBO RED	T1 1/2	1.99	100-UP
JUMBO GREEN	T1 1/2	.10	.09
JUMBO YELLOW	T1 1/2	.14	.12
MOUNTING HDW	T1 1/2	.10	.09
MINI RED	T1	.10	.09

## SWITCHES

SPDT	MINI-TOGGLE ON ON	1.25
DPDT	MINI-TOGGLE ON ON	1.50
DPDT	MINI-TOGGLE ON/OFF ON	1.75
SPST	MINI-PUSHBUTTON N/O	.39
SPST	MINI-PUSHBUTTON N/C	.39
BCD OUTPUT	10 POS. 6 PIN DIP	1.95

## DIP SWITCHES

4 position	85	7 position	95
5 position	90	8 position	95
6 position	90	10 position	1.29

## "SNAPABLE" HEADERS

CAN BE SNAPPED APART TO MAKE ANY SIZE HEADER, ALL WITH 1" CENTERS

1x40	STRAIGHT LEAD	.99
1x40	RIGHT ANGLE LEAD	1.49</

**4164 150ns \$129**

**41256 150ns \$295**

**MONITOR STANDS**

- MODEL MS-100 \$12.95**  
 • TILTS & SWIVELS • STURDY PLASTIC CONSTRUCTION
- MODEL MS-200 \$39.95**  
 • TILTS AND SWIVELS • BUILT-IN SURGE SUPPRESSOR  
 • BUILT-IN POWER STATION INDEPENDENTLY CONTROLS UP TO 5 120 VOLT AC OUTLETS • UL APPROVED



**NASHUA DISKETTES**

- BOXES OF 10**
- 5 1/4" DS DD 360K \$9.95  
 5 1/4" DS HD 1.2M \$24.95  
 3 1/2" DS/DD 720K \$16.95
- 5 1/4" DS/DD SOFT SECTOR  
**49¢ea 39¢ea**  
 BULK QTY 50 BULK QTY 250

**5 1/4" DISKETTE STORAGE FILE \$8.95**

- HOLDS 70 5 1/4" FLOPPIES  
 • STURDY, ATTRACTIVE SMOKED ACRYLIC CASE  
 • COMPLETE WITH HINGED DIVIDERS
- VERSION FOR 3 1/2" FLOPPIES AVAILABLE \$9.95**



**2 WAY SWITCH BOXES \$39.95**

- CONNECT 2 PRINTERS TO 1 COMPUTER OR VICE VERSA  
 • SERIAL & PARALLEL MODELS AVAILABLE  
 • ALL LINES SWITCHED  
 • GOLD PLATED CONNECTORS & QUALITY SWITCHES



**6' INTERFACE CABLES**

- MEETS FCC REQUIREMENTS 100% SHIELDED
- IBM COMPATIBLE PARALLEL PRINTER \$9.95  
 CENTRONICS (MALE TO FEMALE) \$15.95  
 CENTRONICS (MALE TO MALE) \$14.95  
 IBM COMPATIBLE MODEM CABLE \$7.95  
 RS232 SERIAL (MALE TO FEMALE) \$9.95  
 RS232 SERIAL (MALE TO MALE) \$9.95  
 COILED KEYBOARD EXTENDER \$7.95

**JOYSTICK \$19.95**

- SET X-Y AXIS FOR AUTO CENTER OR FREE MOVEMENT  
 • FIRE BUTTON FOR USE WITH GAME SOFTWARE  
 • INCLUDES ADAPTOR CABLE FOR IBM



**SWITCHING POWER SUPPLIES**

- PS-135 \$59.95**  
 • FOR IBM XT COMPATIBLE  
 • UL APP. 135 WATTS  
 • 5V 15A, 12V 4.2A  
 • 5V 5A, 12V 5A  
 • ONE YEAR WARRANTY
- PS-150 \$69.95**  
 • FOR IBM AT COMPATIBLE  
 • 200 WATTS  
 • 5V 22A, 12V 8A  
 • 5V 5A, 12V 5A  
 • ONE YEAR WARRANTY



**MONITORS**

**SAMSUNG MONOCHROME**

- IBM COMPATIBLE TTL INPUT  
 • 12" NON-GLARE, LOW DISTORTION, AMBER SCREEN  
 • RES. 720 x 350  
 • SWIVEL BASE  
 • 1 YEAR WARRANTY

**\$119.95**



**MULTISYNC BY NEC \$549.95**

- ORIGINAL CGA EGA PGA COMPATIBLE MONITOR  
 • AUTO FREQUENCY ADJUSTMENT  
 • RESOLUTION AS HIGH AS 800 x 560

**EGA BY CASPER \$399.95**

- 15.75 21.85 KHZ SCANNING FREQUENCIES  
 • RES. 640 x 200 350 • 31mm COT PITCH  
 • 14" BLACK MATRIX SCREEN • 16 COLORS FROM 64

**RGB BY CASPER \$279.95**

- COLOR GREEN AMBER SWITCH • RES. 640 x 240  
 • RGB IBM COMPATIBLE • 14" NON-GLARE SCREEN  
 • .39mm DOT PITCH • CABLE FOR IBM PC INCLUDED

**MONOCHROME BY HYUNDAI \$69.95**

- IBM COMPATIBLE TTL INPUT  
 • 12" NON-GLARE AMBER SCREEN  
 • ATTRACTIVE CASING WITH A TILT SWIVEL BASE

**TOLL FREE U.S. & CANADA (800) 538-5000**

**20MB HARD DISK ON A CARD**



- SAVES SPACE AND REDUCES POWER CONSUMPTION  
 • IDEAL FOR PCs WITH FULL HEIGHT FLOPPIES  
 • LEAVES ROOM FOR A HALF LENGTH CARD IN ADJACENT SLOT

**\$349**

**RITEMAN II PRINTER**



- 160 CPS DRAFT, 32 CPS NLQ MODE  
 • SUPPORTS EPSON IBM GRAPHICS  
 • 9 x 9 DOT MATRIX  
 • FRICTION AND PIN FEEDS  
 • VARIABLE LINE SPACING & PITCH

**\$219.95**

- IBM COMPATIBLE PRINTER CABLE \$9.95  
 REPLACEMENT RIBBON CARTRIDGE \$7.95

**DISK DRIVES**

**5 1/4" SEAGATE HARD DISK DRIVES**

- ST-225 HALF HEIGHT 20MB 65ms \$259  
 ST-238 HALF HEIGHT 30MB 65ms (RLL) \$299  
 ST-251 HALF HEIGHT 40MB 40ms \$469  
 ST-277 HALF HEIGHT 60MB 40ms (RLL) \$649  
 ST-4038 FULL HEIGHT 30MB 40ms \$559  
 ST-4096 FULL HEIGHT 80MB 28ms \$895

**1/2 HEIGHT FLOPPY DISK DRIVES**

- 5 1/4" TEAC FD-55B DS/DD 360K \$109.95  
 5 1/4" TEAC FD-55F DS/QUAD 720K \$124.95  
 5 1/4" TEAC FD-55GFV DS/HD 1.2M \$154.95  
 5 1/4" MITSUBISHI DS/HD 1.2M \$119.95  
 5 1/4" DS/DD 360K \$69.95  
 3 1/2" MITSUBISHI DS/DD (AT OR XT) \$129.95

**DISK DRIVE ACCESSORIES**

- TEAC SPECIFICATION MANUAL \$5.00  
 TEAC MAINTENANCE MANUAL \$25.00  
 1/2 HT MOUNTING HARDWARE FOR IBM \$2.95  
 MOUNTING RAILS FOR IBM AT \$4.95  
 1/2" POWER CABLE FOR 5 1/4" FDDs \$2.95  
 5 1/4" FDD POWER CONNECTORS \$1.19

**DRIVE ENCLOSURES WITH POWER SUPPLIES**

- CAB-2SV5 DUAL SLIMLINE FOR 5 1/4" \$49.95  
 CAB-1FH5 FULL HEIGHT FOR 5 1/4" \$69.95  
 CAB-2SV8 DUAL SLIMLINE FOR 8" \$209.95  
 CAB-2FH8 DUAL FULL HEIGHT FOR 8" \$219.95

**EASYDATA MODEMS**

All models feature auto-dial answer/redial on busy, power up self test, touchtone or pulse dialing, built-in speaker. Hayes and Bell Systems 103 & 212A compatible. Full or half duplex. PC Talk III Communications software with internal models and more.



**INTERNAL**

- 12H 1200 BAUD 1/2 CARD \$69.95  
 24B 2400 BAUD FULL CARD \$179.95

**EXTERNAL**

- (NO SOFTWARE INCLUDED)
- 12D 1200 BAUD \$119.95  
 24D 2400 BAUD \$219.95


**COMPUTER CASES**

Attractive sturdy steel cases fit the popular sized motherboards and include speakers, faceplates, expansion slots and all necessary hardware.



- XT STYLE FLIP-TOP \$34.95  
 XT STYLE SLIDE-TOP \$39.95  
 AT STYLE SLIDE-TOP \$89.95

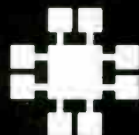- FRONT PANEL KEYLOCK AND LED INDICATORS
- JR. AT STYLE FLIP-TOP \$149.95  
 • INCLUDES 180 WATT POWER SUPPLY  
 • FRONT PANEL KEYLOCK AND LED INDICATORS



Visit our retail store located at 1256 S. Bascom Ave. in San Jose, (408) 947-8881

**JDR Microdevices**

110 Knowles Drive, Los Gatos, CA 95030

Toll Free 800-538-5000 • (408) 866-6200

FAX (408) 378-8927 • Telex 171-110

COPYRIGHT 1987 JDR MICRODEVICES

THE JDR MICRODEVICES LOGO IS A REGISTERED TRADEMARK OF JDR MICRODEVICES. JDR INSTRUMENTS AND JDR MICRODEVICES ARE TRADEMARKS OF JDR MICRODEVICES. IBM IS A TRADEMARK OF INTERNATIONAL BUSINESS MACHINES CORPORATION. APPLE IS A TRADEMARK OF APPLE COMPUTER.

PLEASE USE YOUR CUSTOMER NUMBER WHEN ORDERING

TERMS: Minimum order \$10.00. For shipping and handling include \$2.50 for UPS Ground and \$3.50 for UPS Air. Orders over 1 lb. and foreign orders may require additional shipping charges—please contact our sales department for the amount. CA. residents must include applicable sales tax. All merchandise is warranted for 90 days unless otherwise stated. Prices are subject to change without notice. We are not responsible for typographical errors. We reserve the right to limit quantities and to substitute manufacturer. All merchandise subject to prior sale. A full copy of our terms is available upon request. Items pictured may only be representative.

8087 5MHz \$99<sup>00</sup>

80287 6 MHz \$179<sup>95</sup>

INTERFACE CARDS

FROM MODULAR CIRCUIT TECHNOLOGY

MULTIFUNCTION CARDS

MCT-MF MULTIFUNCTION \$79<sup>95</sup>

- ALL THE FEATURES OF 6 PACK AT HALF THE PRICE
• 0-384K DYNAMIC RAM USING 4164s
• SERIAL PARALLEL GAME PORTS, CLOCK / CALENDAR

MCT-MGMIO MONOGRAPHS I/O \$119<sup>95</sup>

- TOTAL SYSTEM CONTROL FROM A SINGLE SLOT
• 2 FLOPPY CONT, SERIAL, PARALLEL, GAME PORT, CLOCK / CAL
• RUN COLOR GRAPHICS SOFTWARE ON A MONOCHROME MONITOR

MCT-MIO MULTI I/O FLOPPY \$79<sup>95</sup>

- A PERFECT COMPANION FOR OUR MOTHERBOARDS
• SERIAL PARALLEL, GAME PORT, CLOCK / CALENDAR
• SUPPORTS UP TO 2 360K FLOPPIES, 720K WITH DOS 3.2

MCT-IO MULTI I/O CARD \$59<sup>95</sup>

- USE WITH MCT-FH FOR A MINIMUM OF SLOTS USED
• SERIAL PORT, CLOCK / CALENDAR WITH A BATTERY BACK-UP
• PARALLEL PRINTER PORT ADDRESSABLE AS LPT1 OR LPT2

MCT-ATMF AT MULTIFUNCTION \$139<sup>95</sup>

- ADDS UP TO 3 MEGABYTES OF RAM TO THE AT
• USER EXPANDABLE TO 1.5 MB OF MEMORY (ZERO K INSTALLED)
• INCLUDES SERIAL PORT AND PARALLEL PORT

MCT-ATIO AT MULTI I/O \$59<sup>95</sup>

- USE WITH MCT-ATFH FOR A MINIMUM OF SLOTS USED
• SERIAL, PARALLEL AND GAME PORTS
• USES 16450 SERIAL SUPPORT CHIPS FOR HIGH SPEED OPERATION

MEMORY CARDS

MCT-RAM 576K RAM CARD \$59<sup>95</sup>

- A CONTIGUOUS MEMORY SOLUTION IN A SHORT SLOT
• USER SELECTABLE CONFIGURATION AMOUNTS UP TO 576K USING 64K & 256K RAM CHIPS (ZERO K INSTALLED)

MCT-EMS EXPANDED MEMORY CARD \$129<sup>95</sup>

- 2 MB OF LOTUS-INTEL MICROSOFT COMPATIBLE MEMORY FOR XT
• CONFORMS TO LOTUS / INTEL EMS • USER EXPANDABLE TO 2 MB
• EXPANDED / CONVENTIONAL MEMORY, RAMDISK AND SPOOLER

MCT-ATRAM AT 4 MB RAM CARD \$149<sup>95</sup>

- A POWER USER'S DREAM - 4 MB OF MEMORY FOR AT
• BACKFILL TO 640K, FLEXIBLE STARTING ADDRESS
• UP TO 2 MB ON CARD, 4 MB WITH OPTIONAL PIGGYBACK BOARD

MCT-ATEMS AT COMPATIBLE EMS \$139<sup>95</sup>

- CAN BE USED FOR EXPANDED, EXTENDED OR CONVENTIONAL MEMORY
• CONFORMS TO LOTUS / INTEL EMS • USER EXPANDABLE TO 2 MB
• RAMDISK, PRINT SPOOLER AND LIM / EMS SOFTWARE INCLUDED

DRIVE CONTROLLERS

MCT-FDC FLOPPY DISK CONTROLLER \$29<sup>95</sup>

- QUALITY DESIGN OFFERS 4 FLOPPY CONTROL IN A SINGLE SLOT
• INTERFACES UP TO 4 FDDs TO AN IBM PC OR COMPATIBLE
• SUPPORTS BOTH DS / DD AND DS / QD WITH DOS 3.2

MCT-HDC HARD DISK CONTROLLER \$79<sup>95</sup>

- HD CONTROL FOR WHAT OTHERS CHARGE FOR FLOPPY CONTROL
• SUPPORTS 16 DRIVE SIZES INCLUDING 5, 10, 20, 30 & 40 MB
• DIVIDE 1 LARGE DRIVE INTO 2 SMALLER, LOGICAL DRIVES

MCT-FDC-1.2 1.2MB FLOPPY CONTROLLER \$69<sup>95</sup>

- ADD VERSATILITY & CAPACITY TO YOUR XT
• SUPPORTS 2 DRIVES, BOTH MAY BE 360K OR 1.2 MEG
• ALLOWS DATA TO FLOW FREELY FROM XTS TO ATs

MCT-FH FLOPPY/HARD CONTROLLER \$139<sup>95</sup>

- SYSTEM STARVED FOR SLOTS? SATISFY IT WITH THIS TIMELY DESIGN
• INTERFACES UP TO 2 FDDs & 2 HDDs, CABLING FOR 2 FDDs & 1 HDD
• SUPPORTS BOTH DS / DD & DS / QD WITH DOS 3.2

MCT-ATFH AT FLOPPY/HARD CONTROLLER \$149<sup>95</sup>

- FLOPPY HARD DISK CONTROL IN A TRUE AT DESIGN
• SUPPORTS UP TO 2 360K / 720K / 1.2MB FDDs
• AS WELL AS 2 HDDs USING STANDARD CONTROL TABLES

DISPLAY CARDS

MCT-EGA ENHANCED GRAPHICS ADAPTOR \$149<sup>95</sup>

- 100% IBM COMPATIBLE - PASSES IBM EGA DIAGNOSTICS
• 256K OF VIDEO RAM ALLOWS 640 x 350 IN 16 OF 64 COLORS
• COMPATIBLE WITH COLOR AND MONOCHROME ADAPTRs

MCT-CG COLOR GRAPHICS ADAPTOR \$49<sup>95</sup>

- COMPATIBLE WITH IBM COLOR GRAPHICS STANDARDS
• SHORT SLOT SUPPORTS RGB, COLOR & COMPOSITE MONOCHROME
• 640 x 320 x 200 RESOLUTION, LIGHT PEN INTERFACE

MCT-MGP MONOCHROME GRAPHICS \$59<sup>95</sup>

- TRUE HERCULES COMPATIBILITY - SUPPORTS LOTUS 123
• SOFTWARE DRIVER ALLOWS COLOR GRAPHICS PRDGRAMS TO RUN ON A MONOCHROME MONITOR • PARALLEL PRINTER PORT

HALF HEIGHT HARD DISK DRIVES

40 MB \$469

Seagate model ST-251 5 1/4" half height FAST 40ms access time

60 MB \$649

Seagate model ST-277 5 1/4" half height FAST 40ms access time (RLL)

HALF HEIGHT HARD DISK SYSTEMS

20 MB \$289

Systems include Seagate 1/2 height hard drive, hard drive controller, cables and instructions. All drives are pre-tested and warranted for one year.

30 MB \$329

IBM COMPATIBLE MOTHERBOARDS

FROM MODULAR CIRCUIT TECHNOLOGY

MCT-TURBO TURBO 4.77/3 MHz \$109<sup>95</sup>

- 4.77 OR 8 MHz OPERATION WITH 8088 2 & OPTIONAL 8087 2 CO-PROCESSOR
• DYNAMICALLY ADJUSTS SPEED FOR MAXIMUM THROUGH-PUT & RELIABILITY DURING DISK I/O
• CHOICE OF NORMAL / TURBO MODE OR SOFTWARE SELECT PROCESSOR SPEED

MCT-XTMB STANDARD MOTHERBOARD \$97<sup>95</sup>

MCT-ATMB 80286 6/8 MHz \$379<sup>95</sup>

- 8 SLOT (2 EIGHT BIT, 6 SIXTEEN BIT) MOTHERBOARD
• HARDWARE SELECTION OF 6 OR 8 MHz
• 1 WAIT STATE
• KEYLOCK SUPPORTED, RESET SWITCH, FRONT PANEL LED INDICATOR

MCT-BATMB MINI 80286 \$429<sup>95</sup>

- SOCKETS FOR 1 MB OF RAM AND 80287
• BATTERY BACKED CLOCK
• REPLACE VENT BOARD FOR XT STYLE CHASSIS
• OPERATE AT 6 / 10 MHz WITH UP TO 1MB ON-BOARD MEMORY (ZERO K INSTALLED)
• SOCKET FOR 80287 MATH CO-PROCESSOR
• BATTERY BACKED CLOCK
• 8 SLOTS: 2 EIGHT BIT, 6 SIXTEEN BIT
• USES CHIPS & TECHNOLOGY CHIP SET FOR RELIABILITY AND SMALL SIZE

IBM COMPATIBLE KEYBOARDS



MCT-5339 \$79<sup>95</sup>

- IBM ENHANCED STYLE LAYOUT
• SOFTWARE AUTONSENSE FOR XT OR AT COMPATIBLES
• LED INDICATORS
• AUTO REPEAT FEATURE
• SEPARATE CURSOR PAD

MCT-5060 \$59<sup>95</sup>

- IBM AT STYLE LAYOUT
• SOFTWARE AUTONSENSE FOR XT OR AT COMPATIBLES
• LED INDICATORS
• AUTO REPEAT FEATURE

MCT-5150 XT STYLE LAYOUT \$49<sup>95</sup>

MCT-5151 KB5151 EQUIV. \$69<sup>95</sup>

WHY BUY A SYSTEM FROM JDR?

- \* BUILD IT YOURSELF AND SAVE
\* QUALITY COMPONENTS AT COMPETITIVE PRICES
\* TOLL FREE TECHNICAL SUPPORT IN THE U.S. AND CANADA
\* MONEY BACK GUARANTEE (ASK FOR DETAILS)
\* MORE THAN 10,000 SOLD!

I am very pleased with the computer system I purchased from you and all the outstanding support and courteous people on your staff. Your attitude & commitment to customer satisfaction is exceptional. YOUR ATTITUDE SHOULD BE INDUSTRY STANDARD.

Daryl Hammond

BUILD YOUR OWN 256K XT COMPATIBLE

- \* MOTHERBOARD
\* 256K OF MEMORY
\* 135 WATT POWER SUPPLY
\* FLIP-TOP CASE
\* 5060 STYLE KEYBOARD
\* 360K FLOPPY DRIVE
\* DRIVE CONTROLLER
\* MONOCHROME MONITOR
\* GRAPHICS ADAPTOR

FOR ONLY \$499<sup>15</sup>

ANYONE CAN BUILD A SYSTEM IN ABOUT 2 HOURS USING A SCREWDRIVER AND OUR EASY-TO-FOLLOW INSTRUCTIONS!



DEVELOPMENT TOOLS

FROM MODULAR CIRCUIT TECHNOLOGY

MCT-EPROM PROGRAMMER \$129<sup>95</sup>

- PROGRAMS 2716 & 2732 EPROMS UP TO 27512
• SUPPORTS VARIOUS PROGRAMMING FORMATS AND VOLTAGES
• SPLIT OR COMBINE CONTENTS OF SEVERAL EPROMS OF DIFFERENT SIZES
• READ, WRITE, COPY, ERASE CHECK AND VERIFY
• SOFTWARE FOR HEX AND INTEL HEX FORMATS

MCT-EPROM-4 4 GANB PROGRAMMER \$189<sup>95</sup>

MCT-EPROM-10 10 GANB PROGRAMMER \$299<sup>95</sup>

MCT-PAL PAL PROGRAMMER \$269<sup>95</sup>

MCT-MP PROCESSOR PROG. \$199<sup>95</sup>



CALL FOR VOLUME QUOTES

COPYRIGHT 1987 JDR MICRODEVICES

CIRCLE 183 ON FREE INFORMATION CARD

DECEMBER 1987

NATIONAL SEMICONDUCTOR • PANASONIC MACHINE • EVC INC. • INTERTEC • EAC, INC. • J. W. MILLER • AAVID ENGINEER • E. F. JOHNSON • ATLANTIC SEMICONDUCTOR

256K (262,144 x 1) DRAM 150NS \$5.70/1; \$39.95/9

Factory Firsts

DIODES • DIAMOND TOOL • UNGAR • ES • CV INDUSTRIES • AMDEK • G.E. • AR • YAGEO • J. W. MILLER • LUCAS CHEMICALS • ARIES • PLESSEY

### INTEGRATED CIRCUITS

#### 7400 TTL

Part	Price
7400	1.00
7401	1.00
7402	1.00
7403	1.00
7404	1.00
7405	1.00
7406	1.00
7407	1.00
7408	1.00
7409	1.00
7410	1.00
7411	1.00
7412	1.00
7413	1.00
7414	1.00
7415	1.00
7416	1.00
7417	1.00
7418	1.00
7419	1.00
7420	1.00
7421	1.00
7422	1.00
7423	1.00
7424	1.00
7425	1.00
7426	1.00
7427	1.00
7428	1.00
7429	1.00
7430	1.00
7431	1.00
7432	1.00
7433	1.00
7434	1.00
7435	1.00
7436	1.00
7437	1.00
7438	1.00
7439	1.00
7440	1.00

### INTEGRATED CIRCUITS

#### 4000 CMOS

Part	Price
4000	1.00
4001	1.00
4002	1.00
4003	1.00
4004	1.00
4005	1.00
4006	1.00
4007	1.00
4008	1.00
4009	1.00
4010	1.00
4011	1.00
4012	1.00
4013	1.00
4014	1.00
4015	1.00
4016	1.00
4017	1.00
4018	1.00
4019	1.00
4020	1.00
4021	1.00
4022	1.00
4023	1.00
4024	1.00
4025	1.00
4026	1.00
4027	1.00
4028	1.00
4029	1.00
4030	1.00
4031	1.00
4032	1.00
4033	1.00
4034	1.00
4035	1.00
4036	1.00
4037	1.00
4038	1.00
4039	1.00
4040	1.00

### T.I.C. SOCKETS

#### SOLDER TAIL DIP SOCKETS

Standard profile

Universal mounting and packaging capabilities

Compatible with standard DIP sockets

Wide range of sizes to meet your needs

YOUR CHOICE: TIN OR GOLD\*

\*Minimum 1000 sockets per lot

Part #	Description	1	10	100	1000
TS1	8-pin solder tail	1.18	1.18	1.18	1.18
TS2	14-pin solder tail	1.18	1.18	1.18	1.18
TS3	18-pin solder tail	1.18	1.18	1.18	1.18
TS4	20-pin solder tail	1.18	1.18	1.18	1.18
TS5	24-pin solder tail	1.18	1.18	1.18	1.18
TS6	28-pin solder tail	1.18	1.18	1.18	1.18
TS7	32-pin solder tail	1.18	1.18	1.18	1.18
TS8	36-pin solder tail	1.18	1.18	1.18	1.18
TS9	40-pin solder tail	1.18	1.18	1.18	1.18
TS10	44-pin solder tail	1.18	1.18	1.18	1.18
TS11	48-pin solder tail	1.18	1.18	1.18	1.18
TS12	52-pin solder tail	1.18	1.18	1.18	1.18
TS13	56-pin solder tail	1.18	1.18	1.18	1.18
TS14	60-pin solder tail	1.18	1.18	1.18	1.18
TS15	64-pin solder tail	1.18	1.18	1.18	1.18
TS16	68-pin solder tail	1.18	1.18	1.18	1.18
TS17	72-pin solder tail	1.18	1.18	1.18	1.18
TS18	76-pin solder tail	1.18	1.18	1.18	1.18
TS19	80-pin solder tail	1.18	1.18	1.18	1.18
TS20	84-pin solder tail	1.18	1.18	1.18	1.18
TS21	88-pin solder tail	1.18	1.18	1.18	1.18
TS22	92-pin solder tail	1.18	1.18	1.18	1.18
TS23	96-pin solder tail	1.18	1.18	1.18	1.18
TS24	100-pin solder tail	1.18	1.18	1.18	1.18
TS25	104-pin solder tail	1.18	1.18	1.18	1.18
TS26	108-pin solder tail	1.18	1.18	1.18	1.18
TS27	112-pin solder tail	1.18	1.18	1.18	1.18
TS28	116-pin solder tail	1.18	1.18	1.18	1.18
TS29	120-pin solder tail	1.18	1.18	1.18	1.18
TS30	124-pin solder tail	1.18	1.18	1.18	1.18
TS31	128-pin solder tail	1.18	1.18	1.18	1.18
TS32	132-pin solder tail	1.18	1.18	1.18	1.18
TS33	136-pin solder tail	1.18	1.18	1.18	1.18
TS34	140-pin solder tail	1.18	1.18	1.18	1.18
TS35	144-pin solder tail	1.18	1.18	1.18	1.18
TS36	148-pin solder tail	1.18	1.18	1.18	1.18
TS37	152-pin solder tail	1.18	1.18	1.18	1.18
TS38	156-pin solder tail	1.18	1.18	1.18	1.18
TS39	160-pin solder tail	1.18	1.18	1.18	1.18
TS40	164-pin solder tail	1.18	1.18	1.18	1.18
TS41	168-pin solder tail	1.18	1.18	1.18	1.18
TS42	172-pin solder tail	1.18	1.18	1.18	1.18
TS43	176-pin solder tail	1.18	1.18	1.18	1.18
TS44	180-pin solder tail	1.18	1.18	1.18	1.18
TS45	184-pin solder tail	1.18	1.18	1.18	1.18
TS46	188-pin solder tail	1.18	1.18	1.18	1.18
TS47	192-pin solder tail	1.18	1.18	1.18	1.18
TS48	196-pin solder tail	1.18	1.18	1.18	1.18
TS49	200-pin solder tail	1.18	1.18	1.18	1.18
TS50	204-pin solder tail	1.18	1.18	1.18	1.18

### T.I.C. SOCKETS

#### TIN PLATED SOLDER TAIL

Standard profile

Universal mounting and packaging capabilities

Compatible with standard DIP sockets

Wide range of sizes to meet your needs

YOUR CHOICE: TIN OR GOLD\*

\*Minimum 1000 sockets per lot

Part #	Description	1	10	100	1000
TS1	8-pin solder tail	1.18	1.18	1.18	1.18
TS2	14-pin solder tail	1.18	1.18	1.18	1.18
TS3	18-pin solder tail	1.18	1.18	1.18	1.18
TS4	20-pin solder tail	1.18	1.18	1.18	1.18
TS5	24-pin solder tail	1.18	1.18	1.18	1.18
TS6	28-pin solder tail	1.18	1.18	1.18	1.18
TS7	32-pin solder tail	1.18	1.18	1.18	1.18
TS8	36-pin solder tail	1.18	1.18	1.18	1.18
TS9	40-pin solder tail	1.18	1.18	1.18	1.18
TS10	44-pin solder tail	1.18	1.18	1.18	1.18
TS11	48-pin solder tail	1.18	1.18	1.18	1.18
TS12	52-pin solder tail	1.18	1.18	1.18	1.18
TS13	56-pin solder tail	1.18	1.18	1.18	1.18
TS14	60-pin solder tail	1.18	1.18	1.18	1.18
TS15	64-pin solder tail	1.18	1.18	1.18	1.18
TS16	68-pin solder tail	1.18	1.18	1.18	1.18
TS17	72-pin solder tail	1.18	1.18	1.18	1.18
TS18	76-pin solder tail	1.18	1.18	1.18	1.18
TS19	80-pin solder tail	1.18	1.18	1.18	1.18
TS20	84-pin solder tail	1.18	1.18	1.18	1.18
TS21	88-pin solder tail	1.18	1.18	1.18	1.18
TS22	92-pin solder tail	1.18	1.18	1.18	1.18
TS23	96-pin solder tail	1.18	1.18	1.18	1.18
TS24	100-pin solder tail	1.18	1.18	1.18	1.18
TS25	104-pin solder tail	1.18	1.18	1.18	1.18
TS26	108-pin solder tail	1.18	1.18	1.18	1.18
TS27	112-pin solder tail	1.18	1.18	1.18	1.18
TS28	116-pin solder tail	1.18	1.18	1.18	1.18
TS29	120-pin solder tail	1.18	1.18	1.18	1.18
TS30	124-pin solder tail	1.18	1.18	1.18	1.18
TS31	128-pin solder tail	1.18	1.18	1.18	1.18
TS32	132-pin solder tail	1.18	1.18	1.18	1.18
TS33	136-pin solder tail	1.18	1.18	1.18	1.18
TS34	140-pin solder tail	1.18	1.18	1.18	1.18
TS35	144-pin solder tail	1.18	1.18	1.18	1.18
TS36	148-pin solder tail	1.18	1.18	1.18	1.18
TS37	152-pin solder tail	1.18	1.18	1.18	1.18
TS38	156-pin solder tail	1.18	1.18	1.18	1.18
TS39	160-pin solder tail	1.18	1.18	1.18	1.18
TS40	164-pin solder tail	1.18	1.18	1.18	1.18
TS41	168-pin solder tail	1.18	1.18	1.18	1.18
TS42	172-pin solder tail	1.18	1.18	1.18	1.18
TS43	176-pin solder tail	1.18	1.18	1.18	1.18
TS44	180-pin solder tail	1.18	1.18	1.18	1.18
TS45	184-pin solder tail	1.18	1.18	1.18	1.18
TS46	188-pin solder tail	1.18	1.18	1.18	1.18
TS47	192-pin solder tail	1.18	1.18	1.18	1.18
TS48	196-pin solder tail	1.18	1.18	1.18	1.18
TS49	200-pin solder tail	1.18	1.18	1.18	1.18
TS50	204-pin solder tail	1.18	1.18	1.18	1.18

### 5% Carbon Film Resistors

Available in 1/4, 1/2, 1, 2 Watt

Standard values

Part #	Value	1	10	100	1000
R100	100Ω	1.00	1.00	1.00	1.00
R101	100Ω	1.00	1.00	1.00	1.00
R102	100Ω	1.00	1.00	1.00	1.00
R103	100Ω	1.00	1.00	1.00	1.00
R104	100Ω	1.00	1.00	1.00	1.00
R105	100Ω	1.00	1.00	1.00	1.00
R106	100Ω	1.00	1.00	1.00	1.00
R107	100Ω	1.00	1.00	1.00	1.00
R108	100Ω	1.00	1.00	1.00	1.00
R109	100Ω	1.00	1.00	1.00	1.00
R110	100Ω	1.00	1.00	1.00	1.00
R111	100Ω	1.00	1.00	1.00	1.00
R112	100Ω	1.00	1.00	1.00	1.00
R113	100Ω	1.00	1.00	1.00	1.00
R114	100Ω	1.00	1.00	1.00	1.00
R115	100Ω	1.00	1.00	1.00	1.00
R116	100Ω	1.00	1.00	1.00	1.00
R117	100Ω	1.00	1.00	1.00	1.00
R118	100Ω	1.00	1.00	1.00	1.00
R119	100Ω	1.00	1.00	1.00	1.00
R120	100Ω	1.00	1.00	1.00	1.00
R121	100Ω	1.00	1.00	1.00	1.00
R122	100Ω	1.00	1.00	1.00	1.00
R123	100Ω	1.00	1.00	1.00	1.00
R124	100Ω	1.00	1.00	1.00	1.00
R125	100Ω	1.00	1.00	1.00	1.00
R126	100Ω	1.00	1.00	1.00	1.00
R127	100Ω	1.00	1.00	1.00	1.00
R128	100Ω	1.00	1.00	1.00	1.00
R129	100Ω	1.00	1.00	1.00	1.00
R130	100Ω	1.00	1.00	1.00	1.00

### DISC CAPACITORS

Standard values

Part #	Value	1	10	100	1000
C100	100pF	1.00	1.00	1.00	1.00
C101	100pF	1.00	1.00	1.00	1.00
C102	100pF	1.00	1.00	1.00	1.00
C103	100pF	1.00	1.00	1.00	1.00
C104	100pF	1.00	1.00	1.00	1.00
C105	100pF	1.00	1.00	1.00	1.00
C106	100pF	1.00	1.00	1.00	1.00
C107	100pF	1.00	1.00	1.00	1.00
C108	100pF	1.00	1.00	1.00	1.00
C109	100pF	1.00	1.00	1.00	1.00
C110	100pF	1.00	1.00	1.00	1.00
C111	100pF	1.00	1.00	1.00	1.00
C112	100pF	1.00	1.00	1.00	1.00
C113	100pF	1.00	1.00	1.00	1.00
C114	100pF	1.00	1.00	1.00	1.00
C115	100pF	1.00	1.00	1.00	1.00
C116	100pF	1.00	1.00	1.00	1.00
C117	100pF	1.00	1.00	1.00	1.00
C118	100pF	1.00	1.00	1.00	1.00
C119	100pF	1.00	1.00	1.00	1.00
C120	100pF	1.00	1.00	1.00	1.00
C121	100pF	1.00	1.00	1.00	1.00
C122	100pF	1.00	1.00	1.00	1.00
C123	100pF	1.00	1.00	1.00	1.00
C124	100pF	1.00	1.00	1.00	1.00
C125	100pF	1.00	1.00	1.00	1.00
C126	100				

# MERRY CHRISTMAS


### MULTIPURPOSE MELODY GENERATOR TA-50A/B/C

This multipurpose melody generator is made with the latest CMOS LSI technology. Operating on a very low current, it can play 8-10 different songs by using two AA sized batteries (DC3V). Applications include their usage in electronic door bells, musical box and electronic clock alarm and many more. Better still, you can choose between 3 models both containing 8-10 popular, melodious tunes.

- TA 50A**
  - Jingle Bell
  - Silent Night
  - Rudolph, the red nosed reindeer
  - O Come, All ye faithful
  - Santa Claus is coming to town
  - Joy to the world
  - I wish you a merry X'mas
  - Mark, the Herald Angels sing
- TA 50B**
  - London Bridge is falling Down
  - Aire you Slewing
  - Joy Symphonny
  - Waggoned
  - Row your Boat
  - Happy Birthday
  - Home Sweet Home
  - Melody on purple bamboo
- TA 50C**
  - Wedding march
  - Happy Birthday
  - Humoresque
  - Loretta
  - The Last Rose of summer
  - Love Song From Sisking

**TA 50A/B \$10.75**  
**TA 50C \$11.50**

### COLOR LIGHT CONTROLLER TY 238




As a result of the advanced technology, this unit can control various colorful spot lights or bulbs. The visual effect of which is most suitable in places like party, disco, electronic game centre and also in lighting for advertisements. Total output power is 1000W (1000VAC) which can control 30 pieces of 100W or 600 pieces of 5W color light bulbs.

**FEATURES**

- "Music" mode: Audio signal is divided into high, middle and low frequency to drive 3 groups of lights; it has independent controller for sensitivity.
- "Chasing" mode: Electronic circuit automatically control 3 groups of color lights in sequential ON and OFF; also it has a speed controller and shift program "Chasing Mode" on the P.C. Board.

Kit \$65.00 Assembled with tested \$75.00


### 80W+80W PURE DC STEREO MAIN POWER AMPLIFIER TA 802



It uses FET differential input to improve S/N ratio and input impedance. It is compatible with all kinds of pre-amplifier. It has a multi-stage protection system, including high sensitivity DC output protection circuit, high speed output short circuit, overload protection and an automatic temperature control system. It can protect the loudspeakers and amplifier against damage.

Kit \$39.95


### 100W DYNAMIC CLASS "A" MAIN POWER AMPLIFIER TA-1000A



Kit \$51.95  
Metal Cabinet/X'former \$26/ \$16.80

**OVER 5000'S SOLD!**

### HIGH QUALITY PRE-AMPLIFIER WITH 10 BAND EQUALIZER TA-2500



Kit with tested \$90.00

**NEW with CD input stage**

### SUPERIOR ELECTRONIC ROULETTE TY-47



**GREAT CHRISTMAS IDEA**

**BRING 'LAS VEGAS' HOME ONLY**

Kit \$16.92


### BOW + 80W DC LOW TIM PRE-MAIN POWER AMPLIFIER BUILD A 160 W HI-FI STEREO AMP - YOURSELF -



**FREE 1988 MARK V CATALOG**

Kit \$55.38  
Metal Cabinet/X'former \$26/ \$16.80

### LCD THERMOMETER CLOCK



**It reads temp in all sensitive areas**

**NEW**

Features: 0.34" DIGITAL thermometer with Hi & Low temperature alarm function and 12 hours clock combination. Measuring range: 0°F to 160°F or 20°C to +70°C. Resolution reading: ±1.6°F. Dimensions: 3.2" x 0.86" x 2.08"

T-1 with In/Out Door sensor \$20.00  
T-2 with Fahrenheit/Celsius measuring \$18.00

NOT A KIT

### STEREO SIMULATOR TA-3000



Kit only \$25

You can own a stereo TV from today! This simulator is special design of using the most advance analog monopolised LSI. It produced a superior analog stereo effect since the LSI is equalled 60 pcs of LOW NOISE FET & TRANSISTOR. The simulator can even help you to promote your television from a normal one to a special one with a Hi-Fi STEREO function. Our simulator is also applicable to any other mono sources in covering it to ANALOG STEREO. Undoubtedly, it is the most advanced equipment for every family, while it should contribute to your listening pleasure.

Ass. with tested \$30.00

### TALKING CLOCKS that really tell time!



No. 8502 No. 8501 No. 8504

- Talk push button for voice announcement of time
- Parrot twelve hours system display for hour, minute, second (by color flash), AM & PM
- Display three display modes of time, alarm time & date
- Alarm on / off switch with thirty seconds voice alarm
- Snooze / reminder voice alarm of thirty seconds after a minutes of first vocal alarm
- Volume: two level of voice output
- Language available: English

PARROT 8501 \$17.75  
COCKATOO 8502 \$15.90 NOT A KIT!  
MYNAR 8504 \$16.90

**SPECIAL VALUE**

### PROFESSIONAL COLOR LIGHT CONTROLLER SM-328



**FEATURES**

- FOUR GROUPS OF INDEPENDENT OUTPUT SYSTEM 1000W CH MAX 4600W 100 117V
- PROFESSIONAL COLOR CONTROL SYSTEM KEY BOARD T-PE 3
- INDEPENDENT INPUT SIGNAL ADJUSTMENT 4
- FOUR GROUPS OF INDEPENDENT DIMMER CONTROL 5
- SPEED CONTROL CHASER & AUTOMATIC CHASING CONTROL SYSTEM 7
- FOUR KINDS OF SPECIAL CHASING PROGRAM 8
- COMBINATION OF PROGRAM AND MUSIC CHASING EFFECT 9
- FORWARD BACKWARD CHASING CONTROL SM-328 color light controller is specified for ballroom, night club and advertisement lighting. It consists with several color control characteristics, which employ professional color control system and keyboard program selection. Therefore, it is capable of producing lighting effects by using chasing program and fluctuating music signal. There are two kinds of lighting effects. The first type is controlled by music signal. In order to adjust the brightness of four group of lighting, each music signal will be separated into high, medium, low A and low B frequency range. Furthermore, each group of lighting is incorporated with an independent signal adjustment. The second kind is composed of electrical circuits and this is the main part for creating a special lighting effect. It has four chasing programmes.

Dimensions: 14.5" x 16" x 8.15" (H) x 3.31" (D)  
Ass. with tested \$150.00

### ELECTRONIC ECHO AND REVERBERATION AMPLIFIER TA-2400A



Ass. with tested \$99.85

**RECORDS W/ ECHO EFFECT YOURSELF!**

### NF-CR BI-FET PRE-AMP TA-2800



Match with TA-477 or other main power

Kit \$44.50

**WITH TREBLE, MID-RANGE AND BASS 3 WAY TONE CONTROL**

TERMS: \$10 min order • \$20 min charge card order • Check, money order or phone order accepted • We ship UPS Ground • Add 10% of total order (min \$2.50) for shipping, outside USA add 20% (min \$5.00) • Transit insurance add 8% of total (outside USA only) • CA residents add sales tax • All merchandise subject to prior sale • Prices are subject to change without notice • Any goods proved to be defective, MUST BE RETURNED IN ORIGINAL FORM WITH A COPY OF YOUR INVOICE WITHIN 30 DAYS FOR REPLACEMENT.

**OFFICE HOURS: (PACIFIC TIME) MON.-FRI. 9:30 to 5:00 SAT. 10:00 to 5:00**

Model No.	Description	Kit/Assembled	Unit Price	SM 328	PROFESSIONAL COLOR LIGHT CONTROLLER	Assm	\$150.00
TA-006	6W MINI AMPLIFIER	K/It	\$ 4.92	TR-100A	0.15V 2A REGULATED DC POWER SUPPLY	Kit/Assm	\$ 59.50/69.50
TA-007	12W STEREO POWER BOOSTER	K/It	\$ 8.00	TR-355A/B	3.5A REGULATED DC POWER SUPPLY	Kit	\$ 10.68
TA-008	AC/DC SHOULDER AMPLIFIER	Assm	\$ 48.50	TR-503	0.15V/3A POWER SUPPLY WITH SHORT CIRCUIT BREAK & OVERLOAD PROTECTOR	K/It	\$ 17.30
TA-50A/B	MULTI-PURPOSE MELODY GENERATOR	K/It	\$ 10.75	TY-1A MK4	BATTERY FLUORESCENT LIGHT DRIVER	Kit	\$ 3.99
TA-50C	MULTI-PURPOSE MELODY GENERATOR	K/It	\$ 11.50	TY-7	ELECTRONIC TOUCH SWITCH	Kit	\$ 5.50
TA-10	STEREO PRE-AMP WITH MAGNETIC MIC AMP	K/It	\$ 6.00	TY-11A	MULTI-FUNCTIONAL CONTROL SWITCH	Kit	\$ 3.99
TA-120 MK2	PURE CLASS "A" MAIN POWER AMP (MONO)	K/It	\$ 25.00	TY-12A	DIGITAL CLOCK WITH TIME	Kit	\$ 13.95
TA-200	30W MULTI-PURPOSE SINGLE CHANNEL AMP	K/It	\$ 11.07	TY-13	COLOR LED AUDIO LEVEL METER	Kit	\$ 17.50
TA-302	60W VERSATILE STEREO POWER BOOSTER	K/It/Assm	\$ 50.00/60.00	TY-14	ELECTRONIC SHOCK	Kit	\$ 5.00
TA-323A	HIGH QUALITY 30W - 30W STEREO AMP	K/It	\$ 24.60	TY-18	HIGH PRECISION SOUND CONTROL SWITCH	K/It	\$ 7.68
TA-3271	50W - 50W IC STEREO AMP WITH LEVEL DISPLAY	K/It	\$ 29.50	TY-20	5 SHARP COLOR LED LEVEL METER	Kit	\$ 19.50
TA-377A	FULLY COMPLEMENTARY & SYMMETRICAL FET STEREO PRE-AMP	K/It/Assm	\$ 55.00/65.00	TY-23B	COLOR LIGHT CONTROLLER	Kit/Assm	\$ 65.00/75.00
TA-400	40W SOLID STATE MONO-AMP	K/It	\$ 13.84	TY-25	STEREO LOUSPEAKER PROTECTOR	Kit	\$ 11.00
TA-477	120W MOSFET POWER AMP (MONO)	K/It	\$ 81.76	TY-35	PM WIRELESS MICROPHONE	Kit	\$ 7.68
TA-720	72W - 72W AC/DC STEREO HI-FI PA AMP	K/It	\$ 52.00	TY-36	ACID QUARTZ DIGITAL CLOCK	Kit	\$ 18.92
TA-800	80W - 80W DC LOW TIM PRE MAIN POWER AMP	K/It	\$ 55.38	TY-38	SOUND OR TOUCH CONTROL SWITCH	Kit	\$ 10.00
TA-802	80W - 80W PURE DC STEREO MAIN POWER AMP	K/It	\$ 39.95	TY-41 MKV	INFRA RED REMOTE CONTROL UNIT	Kit/Assm	\$ 30.00/45.00
TA-820A	60W - 60W DC/DC PRE MAIN STEREO AMP	K/It	\$ 43.00	TY-42	BAR/DOT LEVEL METER	Kit	\$ 21.00
TA-1005A	1000W DYNAMIC CLASS "A" MAIN POWER AMP (MONO)	K/It	\$ 51.95	TY-43	DIGITAL PANEL METER	Kit	\$ 30.00
TA-1500	100W - 100W NEW CLASS "A" DC STEREO PRE MAIN AMP	K/It	\$ 67.00	TY-45	2C STEPS BAR/DOT AUDIO LEVEL DISPLAY KIT	Kit	\$ 34.95
TA-2400A	ELECTRONIC ECHO AND REVERBERATION AMP	K/It/Assm	\$ 89.00/99.85	TY-47	SUPERIOR ELECTRONIC ROULETTE	Kit	\$ 16.92
TA-2500	HQ MULTI-PURPOSE PRE-AMP WITH 10 BAND GRAPHIC EQ	Assm	\$ 90.00	YAMA TO 4001	LED DIGITAL MULTIMETER	Kit	\$ 21.00
TA-2800	HI-FI BI-FET PRE-AMP WITH 3 WAY TONE CONTROL	K/It	\$ 44.50	T1	TALKING CLOCK WITH IN/OUT DOOR SENSOR	Kit	\$ 33.80
TA-3000	STEREO SIMULATOR	K/It/Assm	\$ 25.00/40.00	8501	LCD THERMOMETER CLOCK WITH IC MEASURING	Kit	\$ 29.00
SM-43	3W MULTI-FUNCTIONAL LED D.P.M	K/It/Assm	\$ 30.00/36.00	8502	TALKING CLOCK (PARROT)	Kit	\$ 17.75
SM-48	4W HI-PRECISION D.P.M	K/It/Assm	\$ 38.00/48.00	8504	TALKING CLOCK (COCKATOO)	Kit	\$ 15.90
SM-48A	4W HI-PRECISION D.P.M WITH DIN STANARD ABS CASE!	K/It/Assm	\$ 43.00/51.00	620	TALKING CLOCK (MYNAR, GOLDEN OR BLACK)	Kit	\$ 16.90
SM-100	150 MC DIGITAL FREQUENCY COUNTER	Assm	\$ 99.00		CORDLESS SOLDERING-IRON (RECHARGEABLE)	Kit	\$ 22.80

WE ALSO SUPPLY HIGH POWER TRANSFORMERS AND PROFESSIONAL LOOKING METAL CABINETS FOR OUR KITS, PLEASE REFER TO OUR CATALOG!

**MARK V ELECTRONICS INC.,** 1-800-423-3483 INFORMATION: 1-818-282-1196  
248 EAST MAIN STREET SUITE 100 TOLL FREE MAIL ORDER: P.O. BOX 6610  
ALHAMBRA, CA 91801 Only for orders paid by Master or Viscard ALHAMBRA, CA 91802  
TELEX 3716914 MARK 5 IN CAL.: 1-800-521-MARK

# What's New at AMERICAN DESIGN COMPONENTS?

"The Source" of the  
electro-mechanical components  
for the hobbyist.

We warehouse 60,000 items at American Design Components - expensive, often hard-to-find components for sale at a fraction of their original cost!

You'll find every part you need - either brand new, or removed from equipment (RFE) in excellent condition. But quantities are limited. Order from this ad, or visit our retail showroom and find exactly what you need from the thousands of items on display.

OPEN MON. - Sat., 9-5

## THERE'S NO RISK.

With our full 90-day warranty, any purchase can be returned for any reason for full credit or refund.

### ADAM COMPUTER


(Less printer)  
No wiring necessary (just plugs together).  
Hook-up diagram included. Includes: Keyboard, 1 cassette digital data drive, 2 game controllers, power supply, & one cassette. Capable of running CP/M, has built-in word processor.



Item #7410 Complete - \$99.00
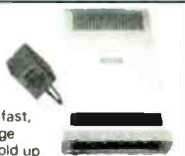
### ADAM 5 1/4" DISK DRIVE

Gives your Adam fast, reliable data storage & retrieval. Can hold up to 160K bytes of information. Uses industry-standard SS/DD disks. Connects directly to your Adam memory console. Comes w/disk drive power supply, Disk Manager disk and owner's manual. Mfr - Coleco, model 7817  
Item #12830 Like New - \$199.00



### ADAM PRINTER



Complete, less top cover plate. Friction feed. Takes standard paper 8 1/2" x 11". (Customer returns; tested - operational.)  
Item #8839 \$69.50

### ADAM Accessories . . .

- Data Drive - Item #6641 \$19.95
- Printer Power Supply - Item #6642 \$14.95
- ASCII Keyboard - Item #6643 \$19.95
- Controllers - (Set of 4) Item #7013 \$9.95
- Adam Cassettes - (Consisting of Smart Basic, Buck Rogers & blank cassette.) Item #7786 BAKER'S DOZEN - \$19.95
- Adam Link Modem - (Software included.) Item #12358 \$29.95
- Auto-Dialer
- Address Book - Item #12365 \$19.95
- Adam Daisy Print Wheel - Item #13305 \$3.95
- Adam Ribbon Cartridge - Item #13306 \$3.95
- Disk Drive Power Supply - Item #14603 \$14.95

### 5 1/4" 10MB HARD DISK DRIVE



(IBM® Compat.)  
Fits standard 5 1/4" spacing. Shock mtd. High speed, low power.  
Mfr - Seagate/Tandon  
Item #13250 \$159.00 New  
Controller Card for above  
Item #10150 \$89.00

### 5 1/4" FLOPPY DISKETTES




Single side/single density; 16 hard sectors. Mfr - Xerox #11R61630  
Item #14537  
Pack of 10 \$9.95 New

### 5 1/4" FULL HT. DISK DRIVES



48 TPI (IBM® Compat.)  
Double sided/double density, full height drive. 48 T.P.I., 80 tracks.  
Mfr - Tandon TM100-2  
Item #7928 \$79.00  
2 for \$150.00  
96 TPI, DS/Quad Density  
Mfr - CDC #9409T  
Item #1893 \$99.00

### 5 1/4" 1/2 HT. DISK DRIVES

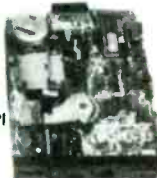

48/96 TPI 1.2 Mb. (AT Compat.)  
DS/single-double density; 80 track. Mfr - Panasonic #JU 475  
Item #10005 \$119.00 New  
96 TPI, DS/Quad Density (DOS 3.2 Compatible)  
Tandon TM55-4; DS/Quad  
Item #1904 \$79.00  
2 for \$150.00

### 5" COMPOSITE VIDEO MONITOR



Power regulated, 12VDC. Mtd. in plastic cabinet, w/brightness control knob. Mfr - Sperry  
OA Dim.: 8" W x 8" H x 8 1/4" deep  
Item #14536 \$24.95

### 115 CFM MUFFIN® FAN With Adjustable Speed Control



115 VAC/60 Hz., 21W., 28A., 3100 RPM; 5-blade model, aluminum housing. Can be mounted for blowing or exhaust.  
Dim.: 4 1/4" sq. x 1 1/2" deep.  
Item #5345S \$8.95

### 27 CFM MINI FANS



115VAC; 50/60Hz.; 12W. Low noise level fans, can be mtd. for blowing or exhaust.  
1 1/2" STANDARD  
7 metal blades  
Dim.: 3 3/8" sq. x 1 1/2" deep  
NEW - Rotron #SU2A1  
Item #5970 \$7.95  
USED - Rotron  
Item #1873 \$5.95

### 12/24 VDC MUFFIN-TYPE FANS



55/100 CFM  
8 W. Can be mounted for blowing or exhaust. Aluminum housing, brushless, ball-bearing type.  
1" Thin: 5 plastic blades with feathered edges.  
Mfr - Centaur #CUDC24K4-601  
Item #8541 \$19.95 New  
1 1/2" Standard: 5 plastic blades  
Mfr - Centaur #CNDK24K4-601  
Item #12109 \$14.95 RFE

### American's IBM PC/XT-COMPATIBLE COMPUTER . . .

- Contains:
- 256K RAM;
  - XT/AT Style Keyboard;
  - 5 1/4" Full-Height Floppy Disk Drive
  - 10Mb Full-Height Hard Disk Drive
  - Hard Disk & Floppy Disk Controller Cards
  - Color/Monochrome Monitor Card (monitor not included).



Item #14331  
\$549.95 New

### MAGNIFYING LAMP




Multi position, 30", completely adjustable swing arm w/3-way metal C-clamp. Has 4" diopter magnifying lens, w/ruler. Porcelain lamp socket, & on/off switch; uses up to a 60W bulb. Color: Beige. UL listed.  
Item #13136 \$24.95 New

### BATTERIES - FANS - BLOWERS

### COLECOVISION GAME

(Factory returns - tested good!)

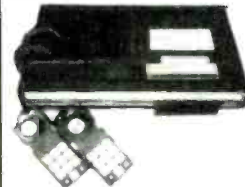


Also includes power supply, instruction manual, modulator, and one Donkey Kong cartridge.  
Item #9918 \$29.95

### COLECOVISION Accessories . . .

- ColecoVision to Adam Expansion Kit  
Just plugs into your ColecoVision.  
Item #9918 \$59.50
- Expansion Module #2  
Incl. Turbo cart.  
Item #13146 \$39.95 New
- Roller Controller  
Incl. Slither cart.  
Item #13147 \$39.95 New
- Super Action Controller Set  
Incl. Baseball cart.  
Item #13148 \$39.95 New
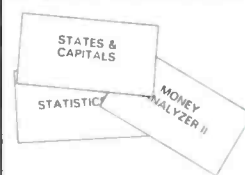
### TIMEX-SINCLAIR 1000 & ZX-81 CASSETTES



Consists of 13 assorted cassettes. May include: Money Analyzer II, States & Capitals, Casino Craps, Statistics, The Carpooler, and others.  
Item #14651  
Set of 13 \$19.95 New

### NEON TRANSFORMER (Hi-Voltage)



7300 VAC @ 5 Ma.  
May be used for powering neon lights, replacing oil burner ignition transformer, building Jacob's ladder (spark gap). A high-volt. output: 1/4" quick connect terminal & case ground input fully enclosed metal case. Weight: 12 lbs.  
Base mount: 4 1/2" H x 5 1/4" W x 6 7/8" D  
Item #151 \$9.95 RFE


### GELL CELL/LEAD ACID BATTERIES . . .

RECHARGEABLE - Used for solar energy storage, alarm systems, remote control boats, robots, etc.



- 6V @ 7.5AH  
Dim.: 5 1/2" L x 3 3/4" H x 2" D  
Mfr - EPC #0031  
Item #13324 \$5.95
- 6V @ 2.6AH  
Dim.: 5 1/2" L x 3 3/4" H x 1 1/4" D  
Mfr - EPC #0027  
Item #13326 \$3.95
- 12V @ 4.5AH  
Dim.: 6" L x 3 3/4" H x 2 1/2" D  
Mfr - EPC #0027  
Item #13325 \$7.95
- 12V @ 2.6AH  
Dim.: 5 1/2" L x 3 3/4" H x 2 1/4" D  
Mfr - EPC #0026  
Item #13323 \$5.95
- 12V @ 1.2AH  
Dim.: 3 1/2" L x 2" H x 1 1/4" D  
Mfr - EPC #0025  
Item #13327 \$3.95

### PLUG-IN POWER SUPPLIES

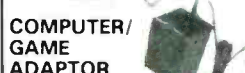

COMPUTER/GAME ADAPTOR  
Output: +5 VDC, .9A  
-5 VDC, .1A  
+12 VDC, .3A  
Input: 120 VAC/60 Hz., .25A  
Mfr - Coleco #55416  
Item #1882 \$4.95 New  
9VDC ADAPTOR  
Input: 115 VAC, 50/60 Hz.  
Output: 9.5V @ 1A.  
Dim.: 2 1/2" W x 3 3/4" H x 2" deep  
Mfr: Commodore #251539-01/02  
Item #9393 \$5.95 New

### NICAD BATTERIES (Rechargeable)



12V @ 450 ma  
Contains 10 AA cells. Recharge rate: 45 ma. 16-18 hours.  
Dim.: 2 1/4" H x 1 1/4" W x 2 1/8" L  
Mfr - GE 123233 or equiv.  
Item #5443 \$5.95 New  
"D" CELLS  
Dual Pack  
2.4V @ 1.2Ah  
2 D cells, stacked & series connected (easily ganged for carrying). Recharge in 12-14 hrs. O.A.  
Dim.: 1 1/2" dia. x 4 1/2" L  
Item #12142 (pack of 2) \$5.95 (Major mfrs.) 5 packs \$25.00




**SEND FOR  
FREE  
1987 CATALOG**  
OUR NEW MAILING  
ADDRESS IS:  
P.O. BOX 567  
VAN NUYS, CA 91408  
800-826-5432

QUALITY PARTS \* DISCOUNT PRICES \* FAST SHIPPING!

# ALL ELECTRONICS CORP.

## ALL ELECTRONICS CORP.

### BLACKLIGHT ASSEMBLY

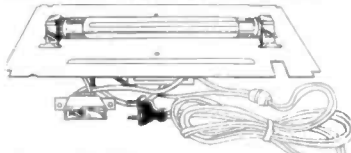

Complete, functioning assembly includes ballast, on-off switch, power cord, sockets and F4T5-BL blacklight. Mounted on a 7 1/8" X 3 1/8" metal plate. Use for special effects lighting or erasing EPROMS.

CAT# BLTA \$10.00 EACH

### 1mA METER

Modutec 0-1 mA signal strength meter with KLM logo. 1 1/4" X 1 3/4" X 7/8" deep.



CAT# MET-2 \$2.00 each

### NI-CAD CHARGER/TESTER

DELUXE universal charger and tester for almost every size Ni-cad battery available.



CAT# UNCC-N \$15.00 each

### RECHARGEABLE NI-CAD BATTERIES

- AAA SIZE 1.25V 180MAH \$2.25
- AA SIZE 1.25V 500MAH \$2.00
- AA with solder tabs \$2.20
- C SIZE 1.2V 1200MAH \$4.25
- SUB-C SIZE solder tab \$4.25
- D SIZE 1.2V 1200MAH \$4.25

### COMPUTER GRADE CAPACITORS

- 1,400 MFD 200 VDC  
2" dia. X 3" high  
CAT# CG-1420 \$2.00
- 7,500 MFD 200 VDC  
3" dia. X 4 3/4" h.  
CAT# CG-75 \$4.00
- 22,000 MFD 25 VDC  
2" dia. X 4 3/4" h.  
CAT# CG-22 \$2.50
- 72,000 MFD 15 VDC  
2" dia. X 4 3/8" h.  
CAT# CG-130 \$3.50

### TRANSISTORS

- 2N2222A 3 for \$1.00
- PN2222A 4 for \$1.00
- 2N2904 3 for \$1.00
- 2N2905 3 for \$1.00
- 2N3055 \$1.00 each
- PN3569 10 for \$1.00

### WALL TRANSFORMER

11.5 Vdc  
1.95 AMP.  
Input:  
120 Vac



SIZE: 3 3/4" X  
2 7/8" X 2 5/8"  
CAT# DCTX-11519  
\$6.50 each

### A/B SWITCH

JVC# PUS3593-2  
High quality  
A/B  
Switch.



Measures:  
3 3/4" X 1 7/16" X 1".  
75 OHMS IN/OUT  
CAT# ABS-2 \$3.50 each

### 13.8 VDC REGULATED POWER SUPPLY

Solid state, fully regulated 13.8 Vdc power supplies. Both feature 100% solid state construction, fuse protection and LED power indicator. UL listed.

- 2 AMP CONSTANT, 4 AMP SURGE  
CAT# DVP-412 \$22.50 each
- 3 AMP CONSTANT, 5 AMP SURGE  
CAT# DVP-512 \$30.00 each



### ELECTRET CONDENSER MIKE



Mouser# 25LMO44 Highly sensitive mini microphone. 6" wire leads. 0.39" dia. X 0.27" high. Omni directional. Operates on 2-10 Vdc @ less than 1 mA. 1K impedance. 50 to 8 K Hz range.

CAT# MKE-1 \$1.00 EACH

### SLIM LINE FAN

TOYO# TF92115A New 115 Vac cooling fan. 3 5/8" square X 1" deep. Metal housing. 8 blade impeller.



CAT# SCFE-115 \$8.50 each

10 for \$75.00

### 2K TO TURN

Multi-turn pot Spectrol# MOD 534-7161



CAT# MTP-10-2 \$5.00 each

### VENTED PROJECT CASE

Bopla #BO 718L Vented top and bottom. Black plastic with removable end panels.



CAT# MB-718 \$12.50 each

### 6-12 VDC MOTOR

Mabuchi # RS-5505 Permanent magnet motor. 1 7/16" dia X 2 1/4" long 2,600 RPM @ 6 Vdc-200 mA 5,300 RPM @ 12 Vdc



CAT# DCM-7 \$3.00 each

### LED'S

- Standard Jumbo Diffused  
T 1-3/4 Size  
10 for \$1.50
- RED 100 for \$13.00  
CAT# LED-1 1000 for \$110.00
- GREEN 10 for \$2.00  
CAT# LED-2 100 for \$17.00  
1000 for \$150.00
- YELLOW 10 for \$2.00  
CAT# LED-3 100 for \$17.00  
1000 for \$150.00

### FLASHING LED

w/ built in flashing circuit operates on 5 Volts...

- RED \$1.00 each  
CAT# LED-4 10 for \$9.50
- GREEN \$1.00 each  
CAT# LED-4G 10 for \$9.50

### BI-POLAR LED

Lights RED one direction, GREEN the other, two leads.

CAT# LED-6 2 for \$1.70

### LED HOLDERS

Two piece holder.  
CAT# HLED 10 for 65c

### CLIPLITE LED HOLDER

Makes L.E.D. look like a fancy indicator

- CLEAR CAT# HLDCL-C
- RED CAT# HLDCL-R
- GREEN CAT# HLDCL-G
- YELLOW CAT# HLDCL-Y
- 4 of one color \$1.00


### 48 KEY ASSEMBLY



NEW T.J. KEYBOARDS. Originally used on computers, these keyboards contain 48 S.P.S.T. mechanical switches. Terminates to 15 pin connector. Frame 4" X 9"  
CAT# KP-48 \$3.50 each
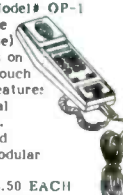
### PUSHBUTTON PHONE

Spectra-phone Model# OP-1 1 piece telephone with rotary (pulse) output. Operates on most rotary or touch tone systems. Feature: fast minute redial and mute button. Includes coil cord with standard modular plug. IVORY.



CAT# PHN-1 \$8.50 EACH  
2 FOR \$15.00

### RELAYS

#### 12 VDC-4PDT

P.C. mount  
5 amp contacts  
150 ohm coil  
Size: 1 1/4" X  
1 3/4" X 7/8"  
CAT# 4PRLY-12PC \$3.50  
10 for \$30.00



#### 10AMP SOLID STATE

Control: 3-32 Vdc  
Load: 10 AMPS,  
120 Vac  
Size: 2 1/2" X  
3/4" X 7/8"  
CAT# SSRLY-10A \$9.50  
10 for \$85.00



#### 25 AMP SOLID STATE

OPTO 2# 240D25  
TTL compatible.  
INPUT: 3-32 VDC  
OUTPUT: 25 AMPS @ 240 VAC  
SIZE: 2 1/2" X 3/4" X 7/8"  
CAT# SSRLY-2524 \$15.00 each



### THIRD TAIL LIGHT


Sleek high-tech lamp assembly. Red lens is 2 3/4" X 5 1/2" mounted on a 4" high pedestal with up-down swivel adjustment. Has 12V replaceable bulb.



CAT# TLB \$3.95 each
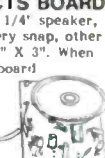
### SOUND EFFECTS BOARD

P.C board with 2 1/4" speaker, 2 LEDs, IC, battery snap, other components 2 3/8" X 3". When switch is pushed board beeps and leds light. Operates on a 9V battery (not included)




CAT# ST-3 \$1.25 each

### XENON FLASH TUBE

3/4" long X 1/8" dia.  
CAT# FLT-1 2 for \$1.00

### VIC 20 MOTHERBOARD

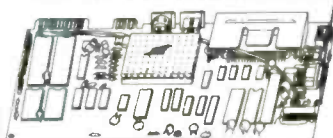

26 IC's including 6502A and 6560. 2 ea. 6522, 2 ea. 8128, 2 ea. 901486, 3 ea. 2114. Not guaranteed but great for replacement parts or experimentation.

CAT# VIC-20 \$15.00 each

### SWITCHING POWER SUPPLY

Compact, well regulated switching power supply designed to power Texas Instruments computer equipment.

INPUT: 14-25 vac @ 1 amp  
OUTPUT: +12 vdc @ 350 ma.  
+5 vdc @ 1.2 amp  
-5 vdc @ 200 ma.

SIZE: 4 3/4" square.  
Includes 18 Vac @ 1 amp wall transformer designed to power this supply.

CAT# PS-TX \$5.00 / set  
10 for \$45.00



### LIGHT ACTIVATED MOTION SENSOR

This device contains a photocell which senses sudden change in ambient light. Could be used as a door annunciator or modified to trigger other devices. 5 1/2" X 4" X 1". Operates on 6 Vdc. Requires 4 AA batteries (not included).



CAT# LSMD \$5.75 per unit

### TRANSFORMERS


- 5.6 VOLT-750ma  
CAT# TX-56 \$3.00
- 12 V.c.t.-1amp  
CAT# TX-121 \$4.00
- 12 V.c.t.-2amp  
CAT# TX-122 \$4.85
- 12 V.c.t.-4amp  
CAT# TX-124 \$7.00
- 18 VOLT-650ma  
CAT# TX-186 \$2.00  
10 for \$18.00
- 24 V.c.t.-1amp  
CAT# TX-241 \$4.85
- 24 V.c.t.-2amp  
CAT# TX-242 \$6.75
- 24 V.c.t.-3amp  
CAT# TX-243 \$9.50
- 24 V.c.t.-4amp  
CAT# TX-244 \$11.00

### SWITCHES

- MINIATURE TOGGLE SWITCHES rated 5 Amps  
S.P.D.T. (ON-OFF)  
Non threaded brushing  
P.C. mount.  
CAT# MTS-40PC 75c each  
10 for \$7.00
- S.P.D.T. (ON-ON)  
Solder lug terminals.  
CAT# MTS-4 \$1.00 each  
10 for \$9.00
- D.P.D.T. (ON-ON)  
Solder lug terminals.  
CAT# MTS-8 \$2.00 each  
10 for \$19.00
- MINI PUSH BUTTON  
S.P.S.T. momentary.  
Push to make  
1/4" brushing.  
Red button.  
CAT# MPB-1 35c each  
10 for \$3.00
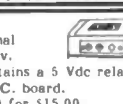
### POLARITY SWITCH

Designed to control an external coaxial relay on a satellite t.v. system. Ideal for parts. Contains a 5 Vdc relay and many other parts on a P.C. board.



CAT# RPDS \$1.75 each 10 for \$15.00

**STORES:**  
LOS ANGELES  
905 S. VERMONT AVE.  
LOS ANGELES, CA 90006  
(213)380-8000  
VAN NUYS  
6228 SEPULVEDA BLVD.  
VAN NUYS, CA 91411  
(818)997-1806

**MAIL ORDERS TO:**  
ALL ELECTRONICS  
P.O. BOX 567  
VAN NUYS, CA  
91408  
TELEX  
TWX-5101010163  
ALL ELECTRONICS  
Foreign Customers  
Send \$1.50 postage  
for FREE Catalog!!

**TOLL FREE**  
800-826-5432  
INFO: (818)904-0524  
FAX: (818)781-2653  
QUANTITIES LIMITED  
MINIMUM ORDERS \$10.00  
CALIF. ADD SALES TAX  
USA: \$3.00 SHIPPING  
NO C.O.D.I.  
FOREIGN ORDERS:  
INCLUDE SUFFICIENT  
SHIPPING

**SOUND AND VIDEO MODULATOR**  
TJ# UN1381-1. Designed for use with T.J. computers. Can be used with video cameras, games or other audio/video sources. Built in A/B switch enables user to switch from T.V. antenna without disconnection. Operates on channel 3 or 4. Requires 12 Vdc. Hook up diagram included.  
CAT# AVMOD \$5.00 each

**TELEPHONE COUPLING TRANSFORMER**  
STANCOR # TTCP-8  
600 ohms c.t.  
to 600 ohms c.t.  
P.C. board mount.  
3/4" X 5/8" X 3/4"  
CAT# TCTXS  
\$2.50 each





# Radio Shack Parts Place™

## HOLIDAY VALUES AT A STORE NEAR YOU



### Special Order Hotline

No Postal or Shipping Charge  
■ Fast Service ■ No Minimum




Your Radio Shack store manager can special order parts and accessories not a part of our regular stock. These items include linear and digital ICs, microprocessors, diodes, semiconductors, tubes, phono styli, crystals and more. We'll call you when it arrives—in about a week.

### FM Receiver on a Chip

**NEW!**

No IF Transformers Needed

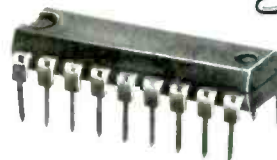

**TDA7000.** Combines RF mixer, IF and demodulator stages in one monolithic IC. Just what you need to build a small, inexpensive mono FM band receiver, repeater monitor or public service band monitor with a minimum of external components. Frequency-locked-loop system with 70 KHz IF. Includes pin-out and application notes. #276-1304 ..... 5.95

### Reference Guide and How-To Books



**NEW!** Essentials For Your Test Bench

**NEW!** 1988 Semiconductor Reference Guide. Over 80,000 types. 288 pages. #276-4011 ..... 3.99  
**Getting Started In Electronics.** Basic electronics projects. 128 pages. #276-5003 ..... 2.49  
**Timer IC Mini-Notebook.** Learn to use the versatile 555 and 556 ICs. 32 pages. #276-5010 ..... 99c

### Add Speech to Your Computer



**SPO256-AL2 Speech Synthesizer.** Easy to interface with most computers. With data. Requires 3.12 MHz crystal (special order). 28-pin DIP. #276-1784 ..... 12.95

**CTS256-AL2 Text to Speech IC.** Translates ASCII characters into control data. Requires 10 MHz crystal (special order). 40-pin DIP. #276-1786 ..... 16.95

### First-Quality ICs

With Pin-Out & Specs

4000-Series CMOS ICs.

Type	Cat. No.	Each
4001	276-2401	.99
4011	276-2411	.99
4013	276-2413	1.19
4017	276-2417	1.49
4049	276-2449	1.19
4066	276-2466	1.19

Line Driver ICs for Data

**MC1488 RS-232 Quad Line Driver.** For sending peripheral data. 14-pin DIP. #276-2520 ..... 1.29

**MC1489 RS-232 Quad Line Receiver.** Use with above. 14-pin DIP. #276-2521 ..... 1.29

CMOS & Bipolar Timers

**TLC555.** Low-power CMOS. Same pin-out as 555 but operates up to 2 MHz. 8-pin DIP. #276-1718 ..... 1.39

Bipolar Resetttable Timers.

Type	DIP	Cat. No.	Each
555 (Single)	8-Pin	276-1723	1.19
556 (Dual)	14-Pin	276-1728	1.49

### Sight 'n Sound



(1) **NEW!** Brilliant Ruby-Red LED With Holder. #276-088 ..... 1.79  
(2) **Tri-Sound-Siren Buzzer.** Three extra-loud outputs. #276-072 ..... 5.95  
(3) **Pulsing Buzzer.** Outputs 80 dB, 2 Hz pulse. #276-058 ..... 2.99

### Project Cases



Blue styrene plastic. Internal slots for PC boards. With screws.

Size	Cat. No.	Each
4 x 2 x 1 3/16"	270-220	1.69
4 x 2 7/16 x 1 1/16"	270-221	1.89
4 3/4 x 2 1/2 x 1 1/16"	270-222	2.19
6 x 3 3/16 x 1 1/8"	270-223	2.69
7 1/2 x 4 1/2 x 2 1/4"	270-224	2.99

### Audio Hookups


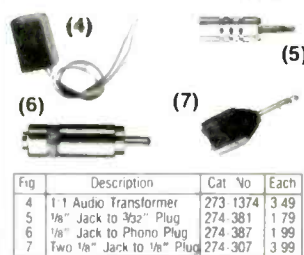


Fig	Description	Cat. No.	Each
4	1:1 Audio Transformer	273-1374	3.49
5	1/8" Jack to 3/32" Plug	274-381	1.79
6	1/8" Jack to Phono Plug	274-387	1.99
7	Two 1/8" Jack to 1/8" Plug	274-307	3.99

### Micro Controls

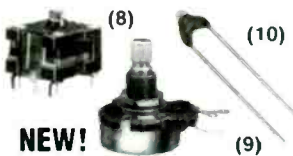


**NEW!** (8) **Variable Tuning Capacitor.** 335 pF. #272-1337 ..... 4.95  
(9) **5-Watt, 25-Ohm Rheostat.** Wire-wound pot. #271-265 ..... 2.99  
(10) **High-Precision Thermistor.** Range -50° to +110°C. #271-110 ..... 1.99

### Parts Bargains



Fig	Description	Cat. No.	Each
11	Circuit Breaker, 2 Amps	270-1310	1.99
12	Fuses Therm	270-1320/1321	.89
13	Pigtail Fuse Adapter Clip	270-1219	.99
14	DPDT Relay, 3 A, 125 AC	270-206	4.99
15	SPST On/Off Switch - Momentary Version	275-617 275-618	1.59 1.49

### RS-232 Hardware

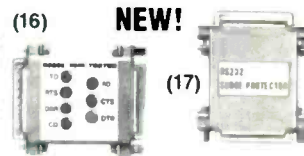

(16) **RS-232 Inline Tester.** Diagnose interface problems in micros and peripherals. #276-1401 ..... 14.95  
(17) **RS-232 Spike Protector.** AC line protection is not enough—Guard each port to be sure! #276-1402 ..... 16.95

### Soldering Tools/Supplies

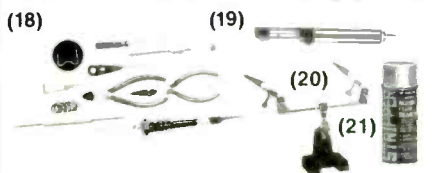


Fig	Description	Cat. No.	Each
(18)	Ten-Piece Electronic Tool Set.	#64-2801	14.95
19	Vacuum Desoldering Tool, Non-Stick Tip	64-2098	4.95
20	Helping Hands, 2 Adjustable Clips	64-2093	7.49
21	Rosin Flux Remover, 6 oz	64-2324	1.89

### Dual-Track Split Supply



Variable 0-15 VDC or series up to 30 VDC. Delivers rock-stable DC at precisely the voltages you need. In tracking mode, a single control lets you adjust both voltages simultaneously. Independent mode to adjust voltages separately. Volt/ammeter. UL listed AC. #22-121

**69<sup>95</sup>**

Choice of Independent Or Slave Operation

### Bench LCD Multimeter



**99<sup>95</sup>**

Low As \$15 Per Month\*

Manual/Auto-ranging • Stores Min/Max Values

The 31-segment analog bar graph displays input peaks and trends. Transistor checker, diode checker, memory function and buzzer continuity checker. Measures to 1000 VDC, 750 VAC, 10 AC/DC amps, 30 megohms resistance. Impedance: 10 megohms. #22-195

Over 1000 items in stock: Binding posts, Books, Breadboards, Buzzers, Capacitors, Chokes, Clips, Coax, Connectors, Fuses, Hardware, ICs, Jacks, Knobs, Lamps, Multimeters, PC Boards, Plugs, Rectifiers, Resistors, Switches, Tools, Transformers, Transistors, Wire, Zeners and more!

**Radio Shack®**  
A DIVISION OF TANDY CORPORATION

\*Revolving credit from Radio Shack. Actual payment may vary depending on purchases. Prices apply at participating Radio Shack stores and dealers

# ADVERTISING INDEX

RADIO-ELECTRONICS does not assume any responsibility for errors that may appear in the index below.

Free Information Number	Page	190	127	82	—	—	71	194	80	110	201	—	56	101	—	78	196	184	176, 177	178, 179	51	74	—	73	92, 185	198	123	199	192	53	186	—
81	A.I.S. Satellite	80	127	82	—	—	71	194	80	110	201	—	56	101	—	78	196	184	176, 177	178, 179	51	74	—	73	92, 185	198	123	199	192	53	186	—
108	AMC Sales	36	127	82	—	—	71	194	80	110	201	—	56	101	—	78	196	184	176, 177	178, 179	51	74	—	73	92, 185	198	123	199	192	53	186	—
107	All Electronics	124	127	82	—	—	71	194	80	110	201	—	56	101	—	78	196	184	176, 177	178, 179	51	74	—	73	92, 185	198	123	199	192	53	186	—
103	Allen W.B.	83	127	82	—	—	71	194	80	110	201	—	56	101	—	78	196	184	176, 177	178, 179	51	74	—	73	92, 185	198	123	199	192	53	186	—
—	Amazing Devices	106	127	82	—	—	71	194	80	110	201	—	56	101	—	78	196	184	176, 177	178, 179	51	74	—	73	92, 185	198	123	199	192	53	186	—
106	American Design Components	123, 122	127	82	—	—	71	194	80	110	201	—	56	101	—	78	196	184	176, 177	178, 179	51	74	—	73	92, 185	198	123	199	192	53	186	—
195	American Reliance	37	127	82	—	—	71	194	80	110	201	—	56	101	—	78	196	184	176, 177	178, 179	51	74	—	73	92, 185	198	123	199	192	53	186	—
—	Amway	99	127	82	—	—	71	194	80	110	201	—	56	101	—	78	196	184	176, 177	178, 179	51	74	—	73	92, 185	198	123	199	192	53	186	—
77, 205,	B&K Precision	3	127	82	—	—	71	194	80	110	201	—	56	101	—	78	196	184	176, 177	178, 179	51	74	—	73	92, 185	198	123	199	192	53	186	—
206, 207	B&K Precision	3	127	82	—	—	71	194	80	110	201	—	56	101	—	78	196	184	176, 177	178, 179	51	74	—	73	92, 185	198	123	199	192	53	186	—
208	B&K Precision	3	127	82	—	—	71	194	80	110	201	—	56	101	—	78	196	184	176, 177	178, 179	51	74	—	73	92, 185	198	123	199	192	53	186	—
98	Beckman Industrial	26	127	82	—	—	71	194	80	110	201	—	56	101	—	78	196	184	176, 177	178, 179	51	74	—	73	92, 185	198	123	199	192	53	186	—
85	Blue Star Industries	81	127	82	—	—	71	194	80	110	201	—	56	101	—	78	196	184	176, 177	178, 179	51	74	—	73	92, 185	198	123	199	192	53	186	—
109	C & S Sales	16	127	82	—	—	71	194	80	110	201	—	56	101	—	78	196	184	176, 177	178, 179	51	74	—	73	92, 185	198	123	199	192	53	186	—
60	CIE	8	127	82	—	—	71	194	80	110	201	—	56	101	—	78	196	184	176, 177	178, 179	51	74	—	73	92, 185	198	123	199	192	53	186	—
188	Cabletronics	81	127	82	—	—	71	194	80	110	201	—	56	101	—	78	196	184	176, 177	178, 179	51	74	—	73	92, 185	198	123	199	192	53	186	—
50	Caig	34	127	82	—	—	71	194	80	110	201	—	56	101	—	78	196	184	176, 177	178, 179	51	74	—	73	92, 185	198	123	199	192	53	186	—
—	Caribbean Electronics	75	127	82	—	—	71	194	80	110	201	—	56	101	—	78	196	184	176, 177	178, 179	51	74	—	73	92, 185	198	123	199	192	53	186	—
193	Chenesko Products	81	127	82	—	—	71	194	80	110	201	—	56	101	—	78	196	184	176, 177	178, 179	51	74	—	73	92, 185	198	123	199	192	53	186	—
52	Circuit Cellar	81	127	82	—	—	71	194	80	110	201	—	56	101	—	78	196	184	176, 177	178, 179	51	74	—	73	92, 185	198	123	199	192	53	186	—
—	Command Productions	26	127	82	—	—	71	194	80	110	201	—	56	101	—	78	196	184	176, 177	178, 179	51	74	—	73	92, 185	198	123	199	192	53	186	—
79	Communications Electronics	7	127	82	—	—	71	194	80	110	201	—	56	101	—	78	196	184	176, 177	178, 179	51	74	—	73	92, 185	198	123	199	192	53	186	—
202	Compstar	99	127	82	—	—	71	194	80	110	201	—	56	101	—	78	196	184	176, 177	178, 179	51	74	—	73	92, 185	198	123	199	192	53	186	—
55	Contact East	80	127	82	—	—	71	194	80	110	201	—	56	101	—	78	196	184	176, 177	178, 179	51	74	—	73	92, 185	198	123	199	192	53	186	—
189	Cook's Institute	36	127	82	—	—	71	194	80	110	201	—	56	101	—	78	196	184	176, 177	178, 179	51	74	—	73	92, 185	198	123	199	192	53	186	—
187	Crystek	44	127	82	—	—	71	194	80	110	201	—	56	101	—	78	196	184	176, 177	178, 179	51	74	—	73	92, 185	198	123	199	192	53	186	—
—	Daetron	126	127	82	—	—	71	194	80	110	201	—	56	101	—	78	196	184	176, 177	178, 179	51	74	—	73	92, 185	198	123	199	192	53	186	—
—	Deco Industries	80, 81	127	82	—	—	71	194	80	110	201	—	56	101	—	78	196	184	176, 177	178, 179	51	74	—	73	92, 185	198	123	199	192	53	186	—
—	Digi-Key	120	127	82	—	—	71	194	80	110	201	—	56	101	—	78	196	184	176, 177	178, 179	51	74	—	73	92, 185	198	123	199	192	53	186	—
—	Digital Research Computers	112	127	82	—	—	71	194	80	110	201	—	56	101	—	78	196	184	176, 177	178, 179	51	74	—	73	92, 185	198	123	199	192	53	186	—
—	Elec. Industry Association	73	127	82	—	—	71	194	80	110	201	—	56	101	—	78	196	184	176, 177	178, 179	51	74	—	73	92, 185	198	123	199	192	53	186	—
—	Electronic Technology Today	113	127	82	—	—	71	194	80	110	201	—	56	101	—	78	196	184	176, 177	178, 179	51	74	—	73	92, 185	198	123	199	192	53	186	—
120, 180	Elephant Electronics	80, 81	127	82	—	—	71	194	80	110	201	—	56	101	—	78	196	184	176, 177	178, 179	51	74	—	73	92, 185	198	123	199	192	53	186	—
100	Firestik II	78	127	82	—	—	71	194	80	110	201	—	56	101	—	78	196	184	176, 177	178, 179	51	74	—	73	92, 185	198	123	199	192	53	186	—
121	Fluke Mfg.	38	127	82	—	—	71	194	80	110	201	—	56	101	—	78	196	184	176, 177	178, 179	51	74	—	73	92, 185	198	123	199	192	53	186	—
—	Fordham Radio	CV4	127	82	—	—	71	194	80	110	201	—	56	101	—	78	196	184	176, 177	178, 179	51	74	—	73	92, 185	198	123	199	192	53	186	—
191	GEL	110	127	82	—	—	71	194	80	110	201	—	56	101	—	78	196	184	176, 177	178, 179	51	74	—	73	92, 185	198	123	199	192	53	186	—
—	Grantham College of Engineering	25	127	82	—	—	71	194	80	110	201	—	56	101	—	78	196	184	176, 177	178, 179	51	74	—	73	92, 185	198	123	199	192	53	186	—
62	Hameg	35	127	82	—	—	71	194	80	110	201	—	56	101	—	78	196	184	176, 177	178, 179	51	74	—	73	92, 185	198	123	199	192	53	186	—
86	Heath	15, 14	127	82	—	—	71	194	80	110	201	—	56	101	—	78	196	184	176, 177	178, 179	51	74	—	73	92, 185	198	123	199	192	53	186	—
—	ISCET	78	127	82	—	—	71	194	80	110	201	—																				

# FOR FREE INFORMATION USE THESE POST-PAID CARDS

**1** Print your name, address and Zip Code on one of the attached postage-paid cards.

**2** Circle the number (or numbers) on the card that matches the number at the bottom of each ad or editorial item that you want information on. Advertisers' free information numbers also appear in the ad index on the facing page.

**3** Mail the card. It's Postage-Paid.

The bottom free-information card is a BUSINESS/PROFESSIONAL CARD. If you use this card you MUST complete the spaces for Company Name, Title, and Phone Number. If these are not filled in, the card will not be processed.

**NOTE:**  
Use the postcard address for Free Product Information only. Address all editorial inquiries to Editor, Radio-Electronics, 500-B Bi-County Blvd., Farmingdale, NY 11735



**Radio Electronics.**  
Your favorite electronics magazine and still getting better

## BUSINESS PROFESSIONAL FREE INFO CARD

Use this card if information requested is for business use. You must fill in company name and phone number.

**Radio Electronics.**

4-1287

Name \_\_\_\_\_ Title \_\_\_\_\_  
 Company \_\_\_\_\_  
 Dept./MS \_\_\_\_\_  
 Daytime Business Phone \_\_\_\_\_  
 Company Address \_\_\_\_\_  
 City \_\_\_\_\_ State \_\_\_\_\_ Zip + 4 \_\_\_\_\_

Unclear or incomplete mailing info will prevent our processing this request.

- 2  Please send me 12 issues of RADIO-ELECTRONICS for \$16.97 and bill me. (Canada \$22.97 - US Funds only)
- 4  Please send me 12 issues of HANDS-ON ELECTRONICS for \$18.95 and bill me. (Canada \$23.95 - US Funds only)

19 37 55 73 91 109 127 145 163 181 199 217 235 253 271  
 20 38 56 74 92 110 128 146 164 182 200 218 236 254 272  
 21 39 57 75 93 111 129 147 165 183 201 219 237 255 273  
 22 40 58 76 94 112 130 148 166 184 202 220 238 256 274  
 23 41 59 77 95 113 131 149 167 185 203 221 239 257 275  
 24 42 60 78 96 114 132 150 168 186 204 222 240 258 276  
 25 43 61 79 97 115 133 151 169 187 205 223 241 259 277  
 26 44 62 80 98 116 134 152 170 188 206 224 242 260 278  
 9 27 45 63 81 99 117 135 153 171 189 207 225 243 261 279  
 10 28 46 64 82 100 118 136 154 172 190 208 226 244 262 280  
 11 29 47 65 83 101 119 137 155 173 191 209 227 245 263 281  
 12 30 48 66 84 102 120 138 156 174 192 210 228 246 264 282  
 13 31 49 67 85 103 121 139 157 175 193 211 229 247 265 283  
 14 32 50 68 86 104 122 140 158 176 194 212 230 248 266 284  
 15 33 51 69 87 105 123 141 159 177 195 213 231 249 267 285  
 16 34 52 70 88 106 124 142 160 178 196 214 232 250 268 286  
 17 35 53 71 89 107 125 143 161 179 197 215 233 251 269 287  
 18 36 54 72 90 108 126 144 162 180 198 216 234 252 270 288

## FREE INFORMATION CARD

VOID after FEBRUARY 29, 1988  
 Allow 6-8 weeks for delivery of first issue

## POSTAGE-PAID FREE INFORMATION CARD

**Radio Electronics.**

3-1287

Name (please print) \_\_\_\_\_  
 Company Name (if applicable) \_\_\_\_\_  
 Address \_\_\_\_\_  
 City \_\_\_\_\_ State \_\_\_\_\_ Zip + 4 \_\_\_\_\_

Unclear or incomplete mailing info will prevent our processing this request.

- 2  Please send me 12 issues of RADIO-ELECTRONICS for \$16.97 and bill me. (Canada \$22.97 - US Funds only)
- 4  Please send me 12 issues of HANDS-ON ELECTRONICS for \$18.95 and bill me. (Canada \$23.95 - US Funds only)
- Is this your personal copy of RADIO-ELECTRONICS?  
 6  Yes 8  No

19 37 55 73 91 109 127 145 163 181 199 217 235 253 271  
 20 38 56 74 92 110 128 146 164 182 200 218 236 254 272  
 21 39 57 75 93 111 129 147 165 183 201 219 237 255 273  
 22 40 58 76 94 112 130 148 166 184 202 220 238 256 274  
 23 41 59 77 95 113 131 149 167 185 203 221 239 257 275  
 24 42 60 78 96 114 132 150 168 186 204 222 240 258 276  
 25 43 61 79 97 115 133 151 169 187 205 223 241 259 277  
 26 44 62 80 98 116 134 152 170 188 206 224 242 260 278  
 9 27 45 63 81 99 117 135 153 171 189 207 225 243 261 279  
 10 28 46 64 82 100 118 136 154 172 190 208 226 244 262 280  
 11 29 47 65 83 101 119 137 155 173 191 209 227 245 263 281  
 12 30 48 66 84 102 120 138 156 174 192 210 228 246 264 282  
 13 31 49 67 85 103 121 139 157 175 193 211 229 247 265 283  
 14 32 50 68 86 104 122 140 158 176 194 212 230 248 266 284  
 15 33 51 69 87 105 123 141 159 177 195 213 231 249 267 285  
 16 34 52 70 88 106 124 142 160 178 196 214 232 250 268 286  
 17 35 53 71 89 107 125 143 161 179 197 215 233 251 269 287  
 18 36 54 72 90 108 126 144 162 180 198 216 234 252 270 288

## FREE INFORMATION CARD

VOID after FEBRUARY 29, 1988  
 Allow 6-8 weeks for delivery of first issue

## BUSINESS REPLY MAIL

FIRST CLASS PERMIT NO 597 BOULDER, COLORADO

**Radio Electronics.**

**SUBSCRIPTION SERVICE**

P.O. Box 51866

BOULDER, COLORADO 80321-1866

NO POSTAGE  
 NECESSARY  
 IF MAILED  
 IN THE  
 UNITED STATES




NO POSTAGE  
NECESSARY  
IF MAILED  
IN THE  
UNITED STATES

**BUSINESS REPLY MAIL**  
FIRST CLASS PERMIT NO. 132 DALTON, MA

POSTAGE WILL BE PAID BY ADDRESSEE

**Radio-  
Electronics**

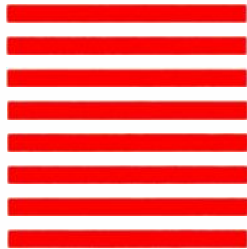FREE PRODUCT INFORMATION  
P.O. Box 388  
DALTON, MA 01226-9990



**For New  
Ideas  
In Electronics  
read Radio-  
Electronics  
every month.**

**During the next  
12 months**

Radio-Electronics will carry up to the minute articles on:

- Computers • Video
- Solid-state technology
- Outstanding construction projects
- Satellite TV • Telephones
- Radio • Stereo • Equipment Reports
- Test equipment • VCR's
- Servicing
- Industrial electronics



**NEW IDEAS AND INNOVATIONS  
IN ELECTRONICS APPEAR IN EVERY  
ISSUE OF RADIO-ELECTRONICS**

**KEEP UP TO DATE! DON'T MISS  
ANY ISSUES!**

**SUBSCRIBE TODAY!**

**USE THE ORDER CARD ON YOUR  
LEFT!**

**Hands-on  
Electronics**

*Formerly Special Projects*

**Delivers construction article after  
construction article....Exciting col-  
umns including Jensen on DXing,  
Freidman on computers, Test bench  
tips, Noll with Calling All Hams, New  
Products and more.**



**SUBSCRIBE TODAY!**

**USE THE REPLY CARDS ON YOUR  
LEFT!**

**Radio-  
Electronics**

4SM73

Subscribe today to the magazine that keeps you up-to-date with the newest ideas and innovations in electronics. (If you already are a subscriber, do a friend a favor and pass this subscription card along to him.)

**check offer preferred**

- 1 Year—12 issues **ONLY \$16.97**       2 Years (**SAVE MORE**)—24 issues \$32.97  
 (You save \$10.03 off single copy price)      (You save \$21.03 off single copy price)
- Canada—12 issues \$22.97       Canada—24 issues \$44.97

ALL SUBSCRIPTIONS PAYABLE IN U.S. FUNDS ONLY

- Payment enclosed       Bill Me       Check here if you are extending or  
renewing your subscription

Name (Please Print) \_\_\_\_\_

Company Name (If applicable) \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Allow 6-8 weeks for delivery of first issue



NO POSTAGE  
NECESSARY  
IF MAILED  
IN THE  
UNITED STATES

**BUSINESS REPLY MAIL**  
FIRST CLASS PERMIT NO. 132 DALTON, MA

POSTAGE WILL BE PAID BY ADDRESSEE

**Radio-  
Electronics**

FREE PRODUCT INFORMATION  
P.O. Box 388  
DALTON, MA 01226-9990




# T S M

2065 BOSTON POST ROAD, LARCHMONT, N.Y. 10538  
TEL 914-937-2447 OR 914-834-7190

## ELECTRONICS KITS

Mike Roth Sales Inc. 1430 South Village #N, Santa Ana, CA 92705
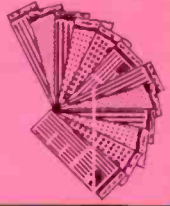
## MECANORMA DIRECT ETCHING TRANSFER SHEETS



### P.C.B. SYMBOLS

	1 in
	2 in
	1.25 in
	1.56 in
	2 in
	0.56 in
	0.15 in
	0.42 in
	2 in
	1 in
	0.37 in
	0.78 in
	3.5 in
	0.15 in
	156 in
	500 in
	63 in
	156 in
	100 in
	0.36 in
	300 in
	100 in
	0.61 in
	300 in
	100 in
	0.314 in
	0.393 in
	0.5 in
	0.799 in
	1 in

## MECANORMA DIRECT ETCHING



### TRANSFER TAPES


	0.314 in
	0.393 in
	0.5 in
	0.799 in
	1 in




**TSM 5A** \$26.30  
AUDIO POWER MODULE 70W PEAK POWER  
35W RMS, INPUT SENSITIVITY 47K/600mV  
OUTPUT 4Ω/8Ω, POWER SUPPLY 39V D.C.  
2.5A



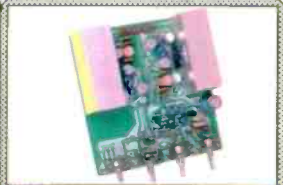
**TSM 9** \$14.00  
AUDIO PREAMPLIFIER FOR GUITAR, INPUT  
SENSITIVITY 47K/5mV, OUTPUT LEVEL  
47K/1.5V, VOLUME CONTROL VARIABLE  
POWER SUPPLY 25V D.C./0.1A



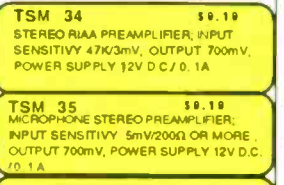
**TSM 67** \$39.74  
STEREO AMPLIFIER 2X40W PEAK POWER  
SENSITIVITY INPUT 47K/300mV, OUTPUT  
2.5/8Ω VOLUME, BALANCE, BASS,  
TREBLE CONTROLS, POWER SUPPLY  
12V D.C./3A



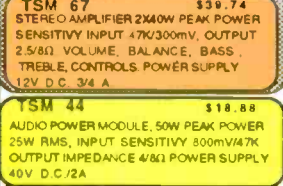
**TSM 34** \$9.19  
STEREO RIAA PREAMPLIFIER, INPUT  
SENSITIVITY 47K/3mV, OUTPUT 700mV,  
POWER SUPPLY 12V D.C./0.1A



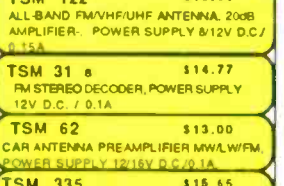**TSM 44** \$18.88  
AUDIO POWER MODULE, 50W PEAK POWER  
25W RMS, INPUT SENSITIVITY 800mV/47K  
OUTPUT IMPEDANCE 4/8Ω POWER SUPPLY  
40V D.C./2A



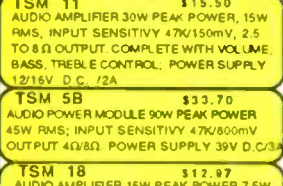
**TSM 122** \$13.95  
ALL-BAND FM/VHF/UHF ANTENNA, 20dB  
AMPLIFIER, POWER SUPPLY 8/12V D.C./  
0.15A




**TSM 11** \$15.50  
AUDIO AMPLIFIER 30W PEAK POWER, 15W  
RMS, INPUT SENSITIVITY 47K/150mV, 2.5  
TO 8Ω OUTPUT, COMPLETE WITH VOLUME  
BASS, TREBLE CONTROL, POWER SUPPLY  
12/16V D.C./2A



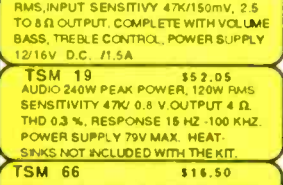
**TSM 62** \$13.00  
CAR ANTENNA PREAMPLIFIER MWLW/FM,  
POWER SUPPLY 12/16V D.C./0.1A



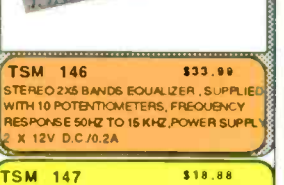
**TSM 5B** \$33.70  
AUDIO POWER MODULE 90W PEAK POWER  
45W RMS, INPUT SENSITIVITY 47K/800mV  
OUTPUT 4Ω/8Ω, POWER SUPPLY 39V D.C./3A



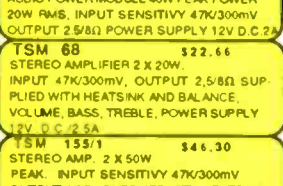
**TSM 335** \$16.65  
PHYSIOLOGIC TONE CONTROL, STEREO,  
INPUT IMPEDANCE 150mV/160K, OUTPUT  
LEVEL 800mV, POWER SUPPLY 25V D.C.



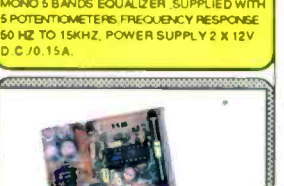**TSM 18** \$12.97  
AUDIO AMPLIFIER 15W PEAK POWER, 7.5W  
RMS, INPUT SENSITIVITY 47K/150mV, 2.5  
TO 8Ω OUTPUT, COMPLETE WITH VOLUME  
BASS, TREBLE CONTROL, POWER SUPPLY  
12/16V D.C./1.5A



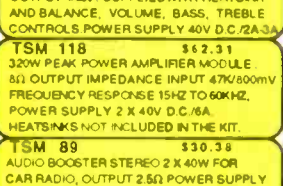
**TSM 146** \$33.99  
STEREO 2X5 BANDS EQUALIZER, SUPPLIED  
WITH 10 POTENTIOMETERS, FREQUENCY  
RESPONSE 50HZ TO 15 KHZ, POWER SUPPLY  
2 X 12V D.C./0.2A




**TSM 66** \$16.50  
AUDIO POWER MODULE 40W PEAK POWER  
20W RMS, INPUT SENSITIVITY 47K/300mV  
OUTPUT 2.5/8Ω, POWER SUPPLY 12V D.C./2A



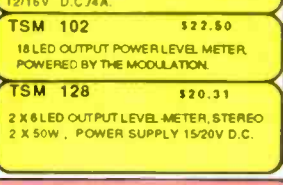
**TSM 147** \$18.88  
MONO 5 BANDS EQUALIZER, SUPPLIED WITH  
5 POTENTIOMETERS, FREQUENCY RESPONSE  
50 HZ TO 15KHZ, POWER SUPPLY 2 X 12V  
D.C./0.15A.



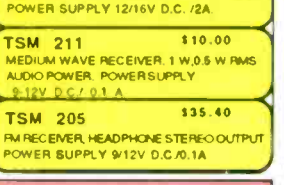
**TSM 89** \$30.38  
AUDIO BOOSTER STEREO 2 X 40W FOR  
CAR RADIO, OUTPUT 2.5Ω POWER SUPPLY  
12/16V D.C./4A



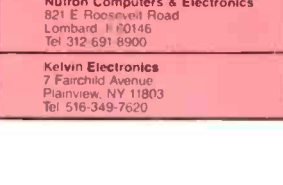
**TSM 61** \$25.48  
FM RECEIVER, OUTPUT 1 WATT 4Ω,  
POWER SUPPLY 12/16V D.C./0.2A



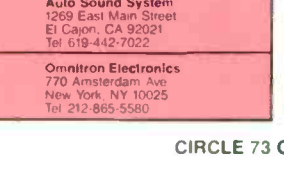**TSM 102** \$22.50  
18 LED OUTPUT POWER LEVEL METER,  
POWERED BY THE MODULATION



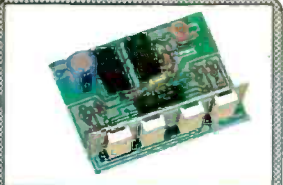
**TSM 211** \$10.00  
MEDIUM WAVE RECEIVER 1 W, 0.5 W RMS  
AUDIO POWER, POWER SUPPLY  
9/12V D.C./0.1A




**TSM 201** \$26.77  
DIGITAL CLOCK, 5/16" READ OUT, POWER  
SUPPLY 12V D.C./0.2A WITH HOUR AND  
MINUTE SETTING CONTROLS



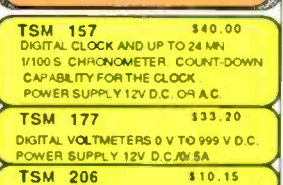
**TSM 212** \$17.50  
LOW OPERATING VOLTAGE  
SPOT TSM 230 AND TSM 221 COMPATIBLE,  
CONTROLLED BY A MICROPHONE,  
POWER SUPPLY 12V/1A, OUTPUT 0.5A  
MODULATOR SAFE 3 CHANNEL LIGHT



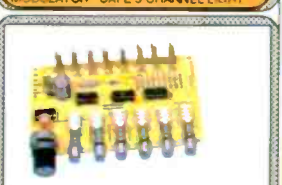
**TSM 157** \$40.00  
DIGITAL CLOCK AND UP TO 24 MIN  
1/100 S CHRONOMETER, COUNT-DOWN  
CAPABILITY FOR THE CLOCK,  
POWER SUPPLY 12V D.C. OR A.C.



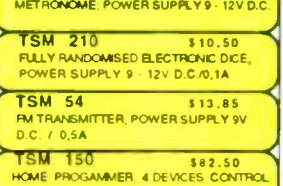
**TSM 177** \$33.20  
DIGITAL VOLTMETERS 0 V TO 999 V D.C.  
POWER SUPPLY 12V D.C./0.5A



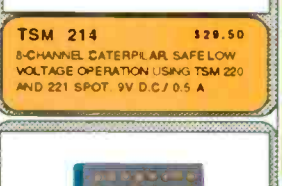**TSM 206** \$10.15  
METRONOME, POWER SUPPLY 9 - 12V D.C.



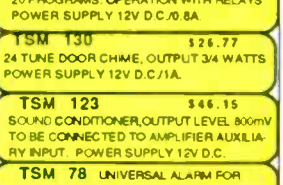
**TSM 214** \$29.50  
8-CHANNEL CATERPILAR SAFE LOW  
VOLTAGE OPERATION USING TSM 220  
AND 221 SPOT, 9V D.C./0.5A




**TSM 210** \$10.50  
FULLY RANDOMISED ELECTRONIC DICE,  
POWER SUPPLY 9 - 12V D.C./0.1A



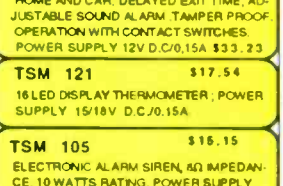
**TSM 54** \$13.85  
FM TRANSMITTER, POWER SUPPLY 9V  
D.C./0.5A



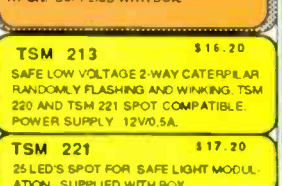**TSM 150** \$82.50  
HOME PROGRAMMER, 4 DEVICES CONTROL  
20 PROGRAMS, OPERATION WITH RELAYS  
POWER SUPPLY 12V D.C./0.8A



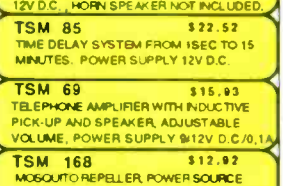
**TSM 130** \$26.77  
24 TUNE DOOR CHIME, OUTPUT 3/4 WATTS  
POWER SUPPLY 12V D.C./1A



**TSM 123** \$46.15  
SOUND CONDITIONER, OUTPUT LEVEL 800mV  
TO BE CONNECTED TO AMPLIFIER AUXILIARY  
INPUT, POWER SUPPLY 12V D.C.



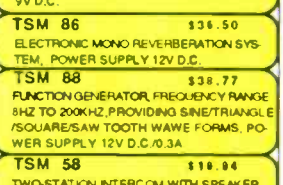
**TSM 78** \$18.45  
UNIVERSAL ALARM FOR  
HOME AND CAR, DELAYED EXIT TIME, AD-  
JUSTABLE SOUND ALARM, TAMPER PROOF  
OPERATION WITH CONTACT SWITCHES,  
POWER SUPPLY 12V D.C./0.15A \$33.23



**TSM 121** \$17.54  
16 LED DISPLAY THERMOMETER, POWER  
SUPPLY 15/18V D.C./0.15A



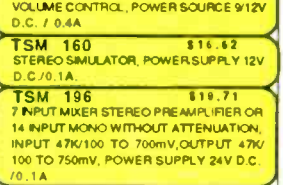**TSM 220** \$25.30  
64 LED'S SPOT FOR SAFE LIGHT MODU-  
LATION, SUPPLIED WITH BOX




**TSM 105** \$16.15  
ELECTRONIC ALARM SIREN, 8Ω IMPEDAN-  
CE, 10 WATTS RATING, POWER SUPPLY  
12V D.C., HORN SPEAKER NOT INCLUDED




**TSM 85** \$22.52  
TIME DELAY SYSTEM FROM 15SEC TO 15  
MINUTES, POWER SUPPLY 12V D.C.



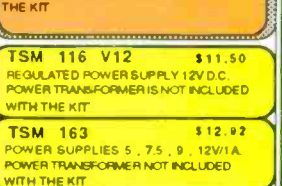
**TSM 69** \$15.93  
TELEPHONE AMPLIFIER WITH INDUCTIVE  
PICK-UP AND SPEAKER, ADJUSTABLE  
VOLUME, POWER SUPPLY 9/12V D.C./0.1A



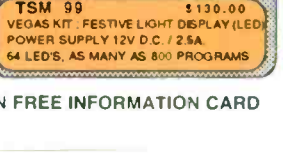**TSM 168** \$12.92  
MOSQUITO REPELLER, POWER SOURCE  
9V D.C.



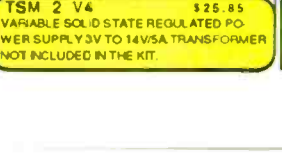**TSM 86** \$36.50  
ELECTRONIC MONO REVERBERATION SYS-  
TEM, POWER SUPPLY 12V D.C.



**TSM 88** \$38.77  
FUNCTION GENERATOR, FREQUENCY RANGE  
8HZ TO 200KHZ, PROVIDING SINE/TRIANGLE  
/ SQUARE SAW TOOTH WAVE FORMS, PO-  
WER SUPPLY 12V D.C./0.3A



**TSM 58** \$18.94  
TWO-STATION INTERCOM WITH SPEAKER  
VOLUME CONTROL, POWER SOURCE 9/12V  
D.C./0.4A



**TSM 160** \$16.62  
STEREO SIMULATOR, POWER SUPPLY 12V  
D.C./0.1A



**TSM 196** \$19.71  
7 INPUT MIXER STEREO PREAMPLIFIER OR  
14 INPUT MONO WITHOUT ATTENUATION,  
INPUT 47K/100 TO 700mV, OUTPUT 47K/  
100 TO 750mV, POWER SUPPLY 24V D.C.  
/0.1A



**TSM 116 V5** \$11.50  
REGULATED POWER SUPPLY 5V D.C.  
POWER TRANSFORMER NOT INCLUDED WITH  
THE KIT



**TSM 116 V12** \$11.50  
REGULATED POWER SUPPLY 12V D.C.  
POWER TRANSFORMER IS NOT INCLUDED  
WITH THE KIT



**TSM 163** \$12.92  
POWER SUPPLIES 5, 7.5, 9, 12V/1A,  
POWER TRANSFORMER NOT INCLUDED  
WITH THE KIT



**TSM 2 V4** \$25.85  
VARIABLE SOLID STATE REGULATED PO-  
WER SUPPLY 3V TO 14V/5A TRANSFORMER  
NOT INCLUDED IN THE KIT.



**TSM 116 V12** \$11.50  
REGULATED POWER SUPPLY 12V D.C.  
POWER TRANSFORMER IS NOT INCLUDED  
WITH THE KIT

**Nutron Computers & Electronics**  
821 E Roosevelt Road  
Lombard, IL 60146  
Tel: 312-691-8900

**Auto Sound System**  
1269 East Main Street  
El Cajon, CA 92021  
Tel: 619-442-7022

**Kelvin Electronics**  
7 Fairchild Avenue  
Plainville, NY 11803  
Tel: 516-349-7620

**Omnitron Electronics**  
770 Amsterdam Ave  
New York, NY 10025  
Tel: 212-685-5580

**SCOPE 3 1/2 Digital Multimeters**



**Model DVM-638**  
**\$8750**

- Test leads included
- 11 function, 38 ranges
  - Logic level detector
  - Audible visual continuity
  - Capacitance and conductance measurement

**Model DVM-636**  
**\$6750**

- 7 function, 32 ranges
- Transistor measurement

**SCOPE 3 1/2 Digit Capacitance Meter**



**Model DCM-602**  
**\$5995**

- Test leads included
- 8 ranges with full scale values to 2000 uF
  - LSI circuit
  - Crystal time base
  - Frequency range 800 Hz to 8KHz

**SCOPE Pocket Sized Audio Signal Generator**



**Model RC-555**  
**\$5995**

- Test leads & 9V battery included
- Low distortion sine-wave signal
  - 46 step selected frequency
  - x1 range 20 Hz to 1.5 KHz
  - x100 range 2 KHz to \*50 KHz

**SCOPE 4 1/2 Digit LCD Bench Digital Multimeter**



**Model DVM-6005**  
**\$21995**

- Test lead set 6, "D" size batteries included
- 0.4" high characters
  - Conversion period: 500 milliseconds
  - Automatic, negative polarity

# Mini-Meters with Maxi-Specs

**SCOPE 3 1/2 Digit LCD with 8 Full Functions**

**Model DVM-632**

**\$4495**  
OUR PRICE

Measures only 5 3/8" x 2 13/16" x 1 1/4"

- Deluxe test leads included
- 0.5% accuracy
  - Transistor gain test
  - Audible continuity checking & diode test
  - 10 Amp measurement

Zipped Carrying Case CC-30 **\$450**



**SCOPE 3 1/2 Digit LCD**



Measures only 5" x 2 1/4" x 7/8"

**Model DVM-630**  
**\$2995**

- OUR PRICE
- Test leads included
  - 0.5% accuracy
  - 6 functions, 19 ranges
  - Automatic zero adjust
  - Low battery indication

Zipped Carrying Case CC-30 **\$450**

ASK FOR FREE CATALOG.

Money orders, checks accepted. C.O.D.'s require 25% deposit.



# Fordham

260 Motor Parkway, Hauppauge, NY 11788

Toll Free  
**800-645-9518**  
In NY State 800-832-1446

**Service & Shipping Charge Schedule Continental U.S.A.**

FOR ORDERS	ADD
\$25-\$100	\$4.50
\$101-\$250	\$6.00
\$251-\$500	\$8.00
\$501-\$750	\$10.50
\$751-\$1,000	\$12.50
\$1,001-\$1,500	\$16.50
\$1,501-\$2,000	\$20.00
\$2,001 and Up	\$25.00