

48783
Radio



**GATED SYNC
DESCRAMBLING**

DECEMBER 1988

Electronics

TECHNOLOGY - VIDEO - STEREO - COMPUTERS - SERVICE

INTERACTIVE TV

Technology lets viewers join in the action

RADIO DATA SYSTEM

Digital data on the FM dial

COMPUTER DIGEST

Universal speech synthesizer lets your computer do the talking

TRUE RMS VOLTMETER

Build an adapter for your DMM

OP-AMP COOKBOOK

17 circuit recipes

PLUS:

- ★ **Hardware Hacker**
- ★ **Video News**
- ★ **Shortwave Radio**
- ★ **Audio Update**

BUILD A VIDEO EDITING CONTROLLER

For clean edits of your home video movies

A
GERNSBACK
PUBLICATION



\$2.25 U.S.
\$2.75 CAN



FLUKE



PHILIPS

How to beat the high cost of cheap meters.



You get what you pay for.
So get the Fluke 70 Series.

You'll get more meter for your money, whether you choose the affordable 73, the feature-packed 75 or the deluxe 77.

All of them will give you years of performance, long after cheaper meters have pegged their fishhook needles for the last time.

That's because they're built to last, inside and out. So they're tough to break. They don't blow fuses all the time. You don't even have to replace batteries as often.

And they're backed by a 3-year warranty. Not the usual 1-year.

Of course, you may only care that the world-champion 70 Series combines digital and analog displays with more automatic features, greater accuracy and easier operation than any other meters in their class.

You may not care that they have a lower overall cost of ownership than all the other "bargain" meters out there.

But just in case, now you know.

For a free brochure or your nearest distributor, call toll-free
1-800-44-FLUKE, ext. 33.

FROM THE WORLD LEADER
 IN DIGITAL MULTIMETERS



FLUKE 73	FLUKE 75	FLUKE 77
\$79*	\$109*	\$159*
Analog/digital display	Analog/digital display	Analog/digital display
Volts, ohms, 10A, diode test	Volts, ohms, 10A, mA, diode test	Volts, ohms, 10A, mA, diode test
Autorange	Audible continuity	Audible continuity
0.7% basic dc accuracy	Autorange/range hold	Touch Hold® function
2000+ hour battery life	0.5% basic dc accuracy	Autorange/range hold
3-year warranty	2000+ hour battery life	0.3% basic dc accuracy
	3-year warranty	2000+ hour battery life
		3-year warranty
		Multipurpose holster

* Suggested U.S. list price, effective October 1, 1988.

FLUKE

December 1988 Radio Electronics

Vol. 59 No. 12

BUILD THIS

- 49 GATED-SYNC DECODER**
How the gated-sync pulses of scrambled TV signals are restored.
Steve Pence
- 57 VIDEO-EDIT CONTROLLER**
Do professional-quality editing with this inexpensive device.
Thomas A. Nery
- 61 TRUE RMS CONVERTER FOR YOUR DMM**
Add this top-of-the-line feature to your VOM or DMM.
Steven A. Brown

TECHNOLOGY

- 45 INTERACTIVE TV**
Compete against game-show contestants, and other viewers, with this exciting new technology!
Brian C. Fenton
- 65 RADIO DATA SYSTEM**
Get a wide range of services from your FM car radio.
Herb Friedman

CIRCUITS

- 69 WORKING WITH A NORTON OP-AMP**
Learn about the LM3900 current-differencing op-amp.
Ray Marston

DEPARTMENTS

- | | |
|---|--|
| <ul style="list-style-type: none">6 VIDEO NEWS
What's new in this fast-changing field.
David Lachenbruch24 EQUIPMENT REPORTS
Amdek Laserdek 1000.33 HARDWARE HACKER
A solid-state digital compass.
Don Lancaster | <ul style="list-style-type: none">38 SHORTWAVE RADIO
Radio station WWV.
Stanley Leinwoll91 AUDIO UPDATE
The Audio Engineering Society.
Larry Klein93 DRAWING BOARD
Seven-segment displays.
Robert Grossblatt |
|---|--|

COMPUTERS

BUILD A SPEECH SYNTHESIZER



ASSEMBLY LANGUAGE PROGRAMMING

PAGE 79

Annual Index
January Thru December 1988
Begins on page 96.

SEASON'S GREETINGS

The editors and staff of 'Radio Electronics join in sending holiday greetings and our best wishes for a happy new year

AND MORE

- 122 Advertising and Sales Offices**
- 122 Advertising Index**
- 12 Ask R-E**
- 123 Free Information Card**
- 14 Letters**
- 101 Market Center**
- 26 New Products**
- 77 PC Service**
- 4 What's News**

ON THE COVER



If you've ever watched a TV game show, you know how difficult it is not to play along—especially when *you* know the answer that is stumping all the contestants! By this time next year, you may be able to do something other than pounding the coffee table. A proposal by the Interactive Game Network would let you play along with your favorite show, and even win prizes.

The interactive home terminals could also be used for public-opinion polling on a scale that simply cannot be done today. For a complete overview of interactive TV technology, turn to page 45.

COMING NEXT MONTH

THE JANUARY ISSUE IS ON SALE DECEMBER 1

CARRIER-CURRENT SPEAKERS

Use your home's power lines to transmit audio.

PROBES

All about oscilloscope probes, how they can affect your measurements, and how to build a low-capacitance scope probe.

Radio-Electronics ADVANCED CONTROL SYSTEM

REACTS returns with a backup power supply.

COMPUTERDIGEST

Inside Intel's 80386.

As a service to readers, RADIO-ELECTRONICS publishes available plans or information relating to newsworthy products, techniques and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, RADIO-ELECTRONICS disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this magazine.

Since some of the equipment and circuitry described in RADIO-ELECTRONICS may relate to or be covered by U.S. patents, RADIO-ELECTRONICS disclaims any liability for the infringement of such patents by the making, using, or selling of any such equipment or circuitry, and suggests that anyone interested in such projects consult a patent attorney.

RADIO-ELECTRONICS, (ISSN 0033-7862) December 1988. Published monthly by Gernsback Publications, Inc., 500-B Bi-County Boulevard, Farmingdale, NY 11735 Second-Class Postage paid at Farmingdale, NY and additional mailing offices. Second-Class mail registration No. 9242 authorized at Toronto, Canada. One-year subscription rate U.S.A. and possessions \$17.97. Canada \$23.97, all other countries \$26.97. All subscription orders payable in U.S.A. funds only, via international postal money order or check drawn on a U.S.A. bank. Single copies \$2.25. © 1988 by Gernsback Publications, Inc. All rights reserved. Printed in U.S.A.

POSTMASTER: Please send address changes to RADIO-ELECTRONICS, Subscription Dept., Box 55115, Boulder, CO 80321-5115.

A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

Radio-Electronics

Hugo Gernsback (1884-1967) founder
M. Harvey Gernsback,
editor-in-chief, emeritus

Larry Steckler, EHF, CET,
editor-in-chief and publisher

EDITORIAL DEPARTMENT

Art Kleiman, editorial director

Brian C. Fenton, editor

Carl Laron, WB2SLR,
editorial associate

Marc Spiwak, associate editor

Jonathan A. Gordon,
assistant technical editor

Teri Scaduto, assistant editor

Jeffrey K. Holtzman,
computer editor

Robert A. Young, assistant editor

Byron G. Wels, editorial associate

Jack Darr, CET, service editor

Robert F. Scott,
semiconductor editor

Herb Friedman,
communications editor

Robert Grossblatt, circuits editor

Larry Klein, audio editor

David Lachenbruch,
contributing editor

Don Lancaster,
contributing editor

Richard D. Fitch,
contributing editor

Kathy Campbell, editorial assistant

Andre Duzant, technical illustrator

Injae Lee, assistant illustrator

PRODUCTION DEPARTMENT

Ruby M. Yee, production director

Robert A. W. Lowndes,
editorial production

Karen Tucker, advertising production

Marcella Amoroso, production traffic

CIRCULATION DEPARTMENT

Jacqueline P. Cheesboro,
circulation director

Wendy Alanko,
circulation analyst

Theresa Lombardo,
circulation assistant

Nancy Estrada, manager,
R-E Bookstore

Typography by Mates Graphics

Cover art by Annette M. Zygarowicz

Radio-Electronics is indexed in
Applied Science & Technology Index
and Readers Guide to Periodical Literature.

Microfilm & microfiche editions are
available. Contact circulation depart-
ment for details.

Advertising Sales Offices listed
on page 122.



Heathkit®



Anyone Can Buy Top Notch Audio. Now You Can Build It.

With Heath's new build-them-yourself stereo components, you create your own sound system.

Specially designed for Heath by industry leader Harman Kardon, our new stereo line exceeds the standards of even the most discerning audiophile. And because most of the components come in kit form, you experience firsthand how electronic craftsmanship results in premium hi-fi performance.

Build the power amplifier, preamplifier and stereo tuner. Prewired and pretested circuit boards and minimal soldering mean each component takes only a few evenings to build.

And, your success is guaranteed. Our precise, step-by-step manuals are industry-recognized, and our technical assistance team is just a phone call away.

To complete your sound system, add the remote control compact disk player, cassette deck and any of our fine speakers and headphones.

See Heath Company's wide assortment of innovative electronic products in our 108-page Heathkit Catalog. For your *FREE* copy, mail the coupon below or call 24 hours a day TOLL-FREE:

1-800-44-HEATH (1-800-444-3284)

Yes, send me a *FREE* Heathkit Catalog.

Send to: **Heath Company, Dept. 020-724**
Benton Harbor, Michigan 49022

Name _____

Address _____ Apt. _____


City _____

State _____ Zip _____

Heath Company

WHAT'S NEWS

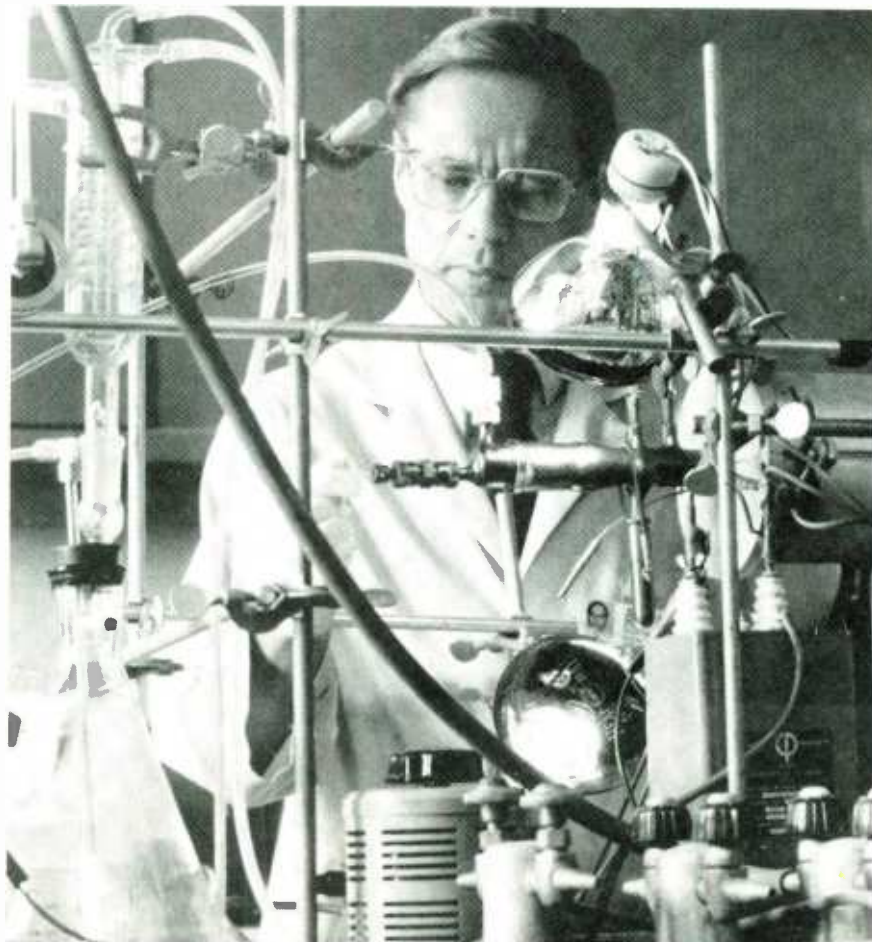Better superconductors from aerosol process



WESTINGHOUSE SCIENTIST DR. ALFRED PEBLER with the equipment used to produce super-high quality yttrium, barium, or copper powders.

Westinghouse scientists have developed a new technology for producing raw materials for the new high-temperature superconductors. The materials are produced in a highly pure powder form that can make superconductor manufacture cheaper while improving the product. "Our particles are so pure and fine that the samples we make from them give us the sharpest transition to the superconductor state that we have seen," states Dr. Alfred Pebler, head of the team working on the new technology. "It occurs at 94°

Kelvin, over a temperature range of at most 3 degrees."

The process starts by dissolving the powders in nitric acid to form a homogeneous solution. Aerosol droplets are then formed from a water solution of the dissolved nitrates and passed through a tubular furnace at temperatures of up to 1,000°C. In the short time while the solution is at that extremely high temperature, the water evaporates, leaving only a metal-oxide compound in the form of a very fine, pure crystalline powder.

News from NPEC '88


At the 1988 National Professional Electronics Convention (NPEC), Larry Steckler CET/EHF was presented with the National Electronics Sales & Service Dealers Association's (NESDA) prestigious "Friend of Service Award," honoring the most significant contribution by a person or company to the advancement of the independent sales and service industry in 1988.

Mr. Steckler, a heavy promoter of the industry's trade associations' causes, owns Gernsback Publications and is the publisher and editor-in-chief of **Radio-Electronics**, **Popular Electronics**, and **Electronics Experimenters' Handbook**. He is a member and chairman of the board of the Electronics Industry Hall of Fame, and also happens to be a participating member of both NESDA and ISCET (International Society of Certified Electronics Technicians).

A recurrent theme at NPEC '88—which was held in St. Charles, IL from August 1-6, and included a wide array of management and technical seminars along with a 2-day trade show—was the need to improve service profitability. Discussions focused on how improved communications between servicers and manufacturers can increase profitability for manufacturers, servicers, and dealers. Also emphasized was the need for dealers to become more familiar with each manufacturer's warranty policies, and for a hard line in negotiating rates with manufacturers annually.


Management seminars covered negotiation techniques and liability traps as well as basic management skills. A variety of technical seminars provided professional instruction in the intricate workings of CD players, digital VCR's, super-VHS VCR's, and camcorders.

R-E

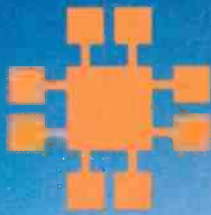

JDR INSTRUMENTS™

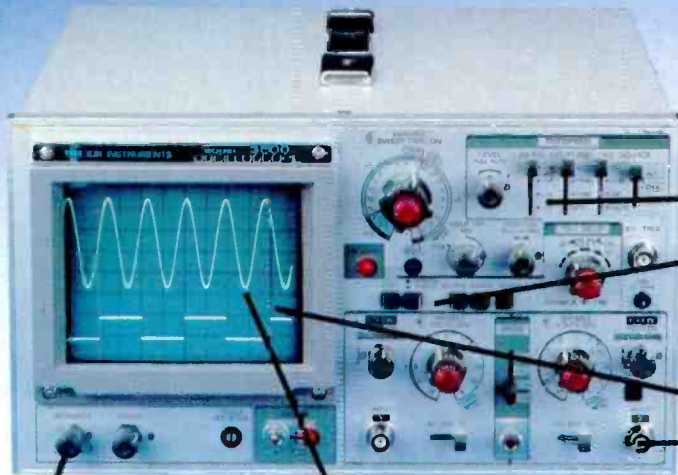Complete customer satisfaction... superior service... friendly, knowledgeable personnel... quality merchandise... providing the best values in leading edge technology.



35 MHZ OSCILLOSCOPE

A remarkable value

\$499⁹⁵

Wide bandwidth and exceptional 1mV/DIV sensitivity make the Model 3500 a powerful diagnostic tool for engineers or technicians at a remarkable price. Delayed triggering allows any portion of a waveform to be isolated and expanded for closer inspection. Variable Holdoff allows stable viewing of complex waveforms.

Z AXIS INTENSITY MODULATION FAST 10NS RISE TIME

TV SYNC FILTER

DELAYED AND SINGLE SWEEP MODES

EXCEPTIONALLY BRIGHT 5" CRT


X-Y OPERATION

DMM-300 \$79.95

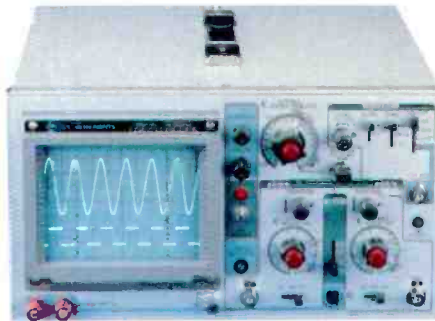3.5 DIGIT DMM/MULTITESTER

This full function 3.5 digit DMM offers highly accurate performance and a host of added features like audible continuity, capacitance, transistor, temperature, and conductance to help you do the job—fast. Temperature probe, test leads and battery included.

- Basic DC accuracy: plus/minus 0.25%
- DC voltage: 200mv–1000V, 5 ranges
- AC voltage: 200mv–750V, 5 ranges
- Resistance: 200 ohms–20M ohms, 6 ranges
- Capacitance: 2000pf–20 µf, 3 ranges
- Transistor Tester: 0–2000°F
- Conductance: 200ns
- Fully overload protected
- Input impedance: 10M ohm.



MODEL 2000 \$389.95

20 MHz DUAL TRACE OSCILLOSCOPE

Model 2000 makes frequency calculation and phase measurement quick and easy. The component tester aids in fast troubleshooting. Service technicians appreciate the TV Sync circuits for viewing TV-V and TV-H and accurate synchronization of the video signal, Blanking, VITS, and V/H sync pulses.

- Exceptionally bright 5" CRT
- Built-in component tester
- TV Sync filter
- X-Y operation 110/220 volts

DMM-100 \$29.95

3.5 DIGIT POCKET SIZE DMM

Perfect for the field service technician. Shirt pocket size without compromising features or accuracy. Large, easy to read 1/2" LCD display. Fully overload protected for safety. 2000 hour battery life with standard 9v cell. Probes and battery included.

- Basic DC accuracy: plus/minus 0.5%
- DC voltage: 2v–1000v, 4 ranges
- AC voltage: 200v–750v, 2 ranges
- Resistance: 2k ohms–2M ohms, 4 ranges
- DC current: 2mA–2A, 4 ranges
- Input impedance: 10M ohm
- Fully overload protected
- Approx. 5" x 3" x 1". Under 7 ozs.



DMM-200 \$49.95

3.5 DIGIT FULL FUNCTION DMM

Get highly accurate performance at a very affordable price. Rugged construction, 20 amp current capability and 22 ranges make it a perfect choice for serious field or bench work. Low battery indicator and tilt-stand. Probes and 2000 hour battery included.

- Basic DC accuracy: plus or minus 0.25%
- DC voltage: 200mv–1000V, 5 ranges
- AC voltage: 200mv–750V, 5 ranges
- Resistance: 200 ohms–20M ohms, 6 ranges
- AC/DC current: 200µA–20A, 6 ranges
- Input impedance: 10M ohm
- Fully overload protected
- Approx. 7" x 3 1/2" x 1 1/2". Wt. 11 ozs.

DPM-1000 \$54.95

3.5 DIGIT PROBE TYPE DMM

Custom 80 pin LSI chip provides accuracy and reliability in such a compact size. Autoranging, audible continuity and data hold feature help you pinpoint the problem quickly. Case and batteries included.

- Basic DC accuracy: plus/minus 1%
- DC voltage: 2v–500v, autoranging
- AC voltage: 2v–500v, autoranging
- Resistance: 2k ohms–2M ohms, autoranging
- Fully overload protected
- Input impedance: 11M ohm
- Approx 6 1/2" x 1" x 3/4". Under 3 ozs.



- ★ 2 YEAR REPLACEMENT WARRANTY
- ★ 30 DAY MONEY BACK GUARANTEE
- ★ TOLL FREE TECHNICAL SUPPORT
- ★ NEXT DAY AIR SHIP AVAILABLE

COPYRIGHT 1987 JDR MICRODEVICES



JDR INSTRUMENTS, 110 KNOWLES DRIVE, LOS GATOS, CA 95030
RETAIL STORE: 1256 SOUTH BASCOM AVE, SAN JOSE, CA (408) 947-8881

ORDER TOLL FREE 800-538-5000

CIRCLE 53 ON FREE INFORMATION CARD

www.americanradiohistory.com

VIDEO NEWS



DAVID LACHENBRUCH,
CONTRIBUTING EDITOR

● **Battle of the Midgets.** The fight between the 8mm-video and VHS-C formats is heating up. Last month I reported that Sony has further miniaturized the 8mm recorder's mechanical transport. While there has been no reported move to further miniaturize VHS-C, Matsushita is working to increase the recording and playing time of that format. One report indicates that there may soon be 30- and 40-minute VHS-C tapes, in addition to the current 20-minute types—presumably through the use of a thinner film base. Since most recent VHS-C camcorders also offer a one-third speed switch, the extended play mode will provide 90- and 120-minute recording time. The 8mm format provides up to two hours recording time on a cassette in the standard play mode and four hours at half speed.

Japanese manufacturers are beginning to introduce Super VHS-C format camcorders with high-fidelity stereo sound. While the 8mm sound is hi-fi, the camcorder models don't provide stereo. Sony is expected to offer a model with digital stereo sound, and some other 8mm adherents are planning analog stereo. To compete with Super VHS, you can expect to see the first models in the new 8mm Hi-Band subformat early in 1989. Hi-Band provides a picture with resolution comparable to S-VHS (*Radio-Electronics*, June 1988).

Sony has already introduced its Video Walkman ("New Products," September 1988), combining a 3-inch LCD color TV set and an 8mm VCR in a 2½-pound package—ideal for watching movies while riding the bus or waiting for the dentist. Not to be outdone, Matsushita has introduced a similar, slightly heavier package using the S-VHS-C format. It's on sale in Japan; there's no word yet on American marketing plans from Panasonic, a subsidiary of Matsushita. Sony's Video Walkman is due on the American market by the time you read this, for approximately \$1,300.

● **Stereo TV All Over.** There are now more than 500 TV stations in North America broadcasting in stereo Multichannel-TV Sound (MTS), according to a survey by *Television Digest*, that turned up 514 MTS-equipped stations. Those

stations are in all of the top market areas, and bring a stereo signal within the tuning range of more than 99% of American TV homes. While the total is still only about 35% of the 1,392 TV stations on the air in the U.S., it contains many of the major outlets. In addition, some 7,362 cable-TV channels carry MTS, according to a survey by the Recoton Corp. Those are all special satellite-delivered channels, and are in addition to those broadcast channels with MTS that the cable systems may be relaying. The 7,362 cable-TV channels constitute only 7.5% of the 97,600 satellite-program channels on the nation's 8,800 cable systems, but most of the stereo-sound channels are believed to be on the larger cable systems. In addition to MTS stereo, many cable systems also use FM signals to relay stereo sound for satellite-TV programs to subscribers. Some systems use both stereo-sound systems on the same channels to cover subscribers who have MTS-stereo TV sets as well as those who don't.


● **Airvision.** You take your seat in the airliner and instead of listening to music or reading a magazine, you flip the switch in the armrest to the TV news, a choice of several movies, language instruction, or a live picture of the plane's takeoff—and watch the small bright color screen embedded in the back of the seat in front of you (or in the between-seats console if you're traveling first class). You might even choose to play an exciting video game or two to while away your travel time.

How far in the future is all of that? Would you believe this year? Philips of the Netherlands and Warner Brothers pictures say the first aircraft equipped with Airvision will have taken off by the time you read this. The viewing screens initially will be three-inch active-matrix back-lighted LCD's; at least five VHS videocassette players in the aircraft will be used as signal sources, with other sources possible. They're proposing the system for buses, taxicabs, trains, and ships, too. And a competing system, ACES (Airborne Cabin services and Entertainment System), with four-inch flat color CRT's has been developed by Sony and Sundstrand Data Control.

ELECTRONICS ENGINEERS & DESIGNERS BOOK CLUB®

Take any 3 books for only \$1.95 (Values to \$198.40)

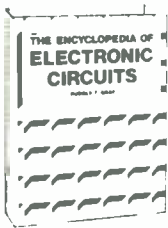SHARPEN YOUR SKILLS—With Quality, Affordable Professional Books



1938 \$60.00
Counts as 2



2888 \$28.95



9825 \$49.95




9808 \$34.95



9788 \$49.50



3019 \$39.95
Counts as 2

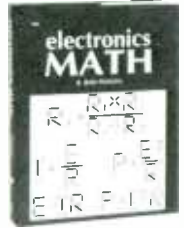


1962 \$22.95



9785 \$79.95



9781 \$68.95

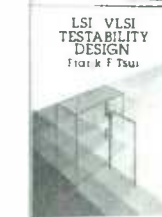

9799 \$49.95




2672 \$49.50
Counts as 2



9832 \$36.95



2720 \$32.50

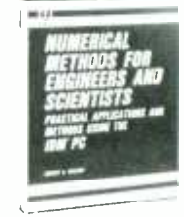

2697 \$19.95



2785 \$39.95
Counts as 2



9794 \$35.95



9083 \$29.95




3002 \$49.50
Counts as 2



2890 \$32.95



2958 \$34.95

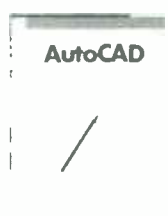

2989 \$29.95



9820 \$46.95




9829 \$45.00



2937 \$29.95



9773 \$44.95

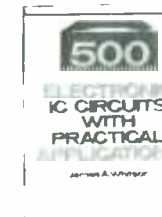

2920 \$28.95

How the Club Works

YOUR BENEFIT: You get 3 books for \$1.95 plus shipping & handling when you join. You keep on saving with discounts from 20 to 50% as a member.

YOUR PROFESSIONAL BOOKSTORE BY MAIL: Every 3-4 weeks, you will receive the EE&D Book Club News describing the Main Selection and Alternates, as well as bonus offers and special sales, with hundreds of titles to choose from.

AUTOMATIC ORDER: If you want the Main selection, do nothing and it will be sent to you automatically. If you prefer another selection, or no selection at all, simply indicate your choice on the reply form provided. As a member, you agree to purchase at least 3 books within the next 2 years and may resign at any time thereafter.

BONUS BOOKS: Starting immediately you will be eligible for our Bonus Book Plan with savings of up to 50% off publishers' prices.

IRONCLAD NO-RISK GUARANTEE: If not satisfied with your books, return them within 10 days without obligation!

EXCEPTIONAL QUALITY: All books are quality publishers' editions especially selected by our Editorial Board.

EE&DBC Blue Ridge Summit, PA 17294-0860

SEND NO MONEY NOW!

INTRODUCTORY 10-DAY FREE EXAMINATION

ELECTRONICS ENGINEERS & DESIGNERS BOOK CLUB®
Blue Ridge Summit, PA 17294-0860

YES! Please accept my membership in the *Electronics Engineers & Designers Book Club®* and send me the volumes I have listed below, billing me only \$1.95 plus shipping and handling charges. I understand that the books are sent on a 10-Day Free Examination basis. If dissatisfied in any way, I may return the books within 10 days and incur no further obligation. Otherwise, I agree to pay the enclosed invoice promptly and to receive regular club bulletins as described in "How the Club Works." To complete my membership obligation I need only purchase 3 additional books at regular members prices during the next 2 years, and may resign at any time thereafter.

NAME _____

ADDRESS _____

CITY _____ STATE/ZIP _____

SIGNATURE _____

Valid for new members only. Foreign applicants will receive special ordering instructions. Canada must remit in U.S. funds. This order is subject to acceptance by the *Electronics Engineers & Designers Book Club®*. DRE-1288

Learn to troubleshoot and service today's computer systems as you build a fully XT-compatible micro, complete with 512K RAM and powerful 20 meg hard drive

Train the NRI Way— and Earn Good Money Servicing Any Brand of Computer

Jobs for computer service technicians will almost double in the next 10 years according to Department of Labor statistics, making computer service one of the top 10 growth fields in the nation.

Now you can cash in on this exciting opportunity— either as a full-time industry technician or in a computer service business of your own—once you've mastered electronics and computers the NRI way.

NRI's practical combination of "reason-why" theory and hands-on building skills starts you with the fundamentals of electronics, then guides you through more sophisticated circuitry all the way up to the latest advances in computer technology. You even learn to program in BASIC and machine language, the essential language for troubleshooting and repair.

Train With a Powerful XT-Compatible — Now With 20 Meg Hard Drive!

To give you hands-on training with the absolute in state-of-the-art computer




You build this powerful Packard Bell VX88 computer, all the while gaining a true mastery of computer electronics. Best of all, it's yours to keep for all your professional and personal computing needs.

technology, NRI includes the powerful new Packard Bell VX88 computer as the centerpiece of your training. As you assemble this fully IBM XT-compatible micro from the keyboard up, you actually see for yourself how every section of your computer works.

You assemble and test your computer's "intelligent" keyboard, install the power supply and 5 1/4" disk drive, then interface the high-resolution monitor. But that's not all.

Your hands-on training continues as you install a powerful 20 megabyte hard disk drive—today's most-wanted computer peripheral—now included in your course to dramatically increase

Your NRI computer training includes all this: • NRI's unique Discovery Lab® for circuit design and diagnosis • NRI's hand-held digital multimeter featuring "talk-you-through" instructions on audio cassette • A digital logic probe that lets you visually examine computer circuits • The new Packard Bell VX88 computer with "intelligent" keyboard, 360K double-sided, double-density disk drive, 512K RAM, 16K ROM • 20 megabyte hard disk drive • Bundled software including MS-DOS, GW-BASIC, word processing, spreadsheet, and database programs • Packard Bell reference manuals with programming guidelines and schematics.

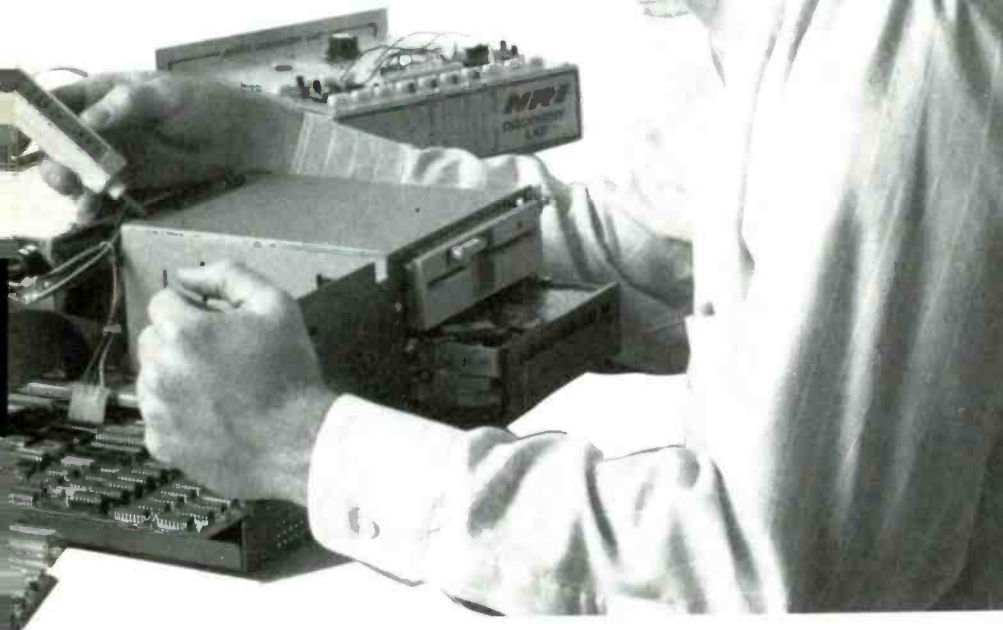

NEW!

Includes 20 meg Hard Drive

throughout your training, you've got the full support of your personal NRI instructor and the NRI technical staff, always ready to answer your questions and help you whenever you need it.

FREE 100-Page Catalog Tells More

Send today for NRI's big, 100-page, full-color catalog that describes every aspect of NRI's innovative computer training, as well as hands-on training in robotics, video/audio servicing, electronic music technology, security electronics, data communications, and other growing high-tech career fields. If the coupon is missing, write to: NRI School of Electronics, McGraw-Hill Continuing Education Center, 3939 Wisconsin Avenue, Washington, DC 20016.

NRI School of Electronics

McGraw-Hill Continuing Education Center
3939 Wisconsin Avenue,
Washington D.C. 20016

IHM is a registered trademark of International Business Machines Corporation



the data storage capacity of your computer while giving you lightning-quick data access. Plus you work with exclusive word processing, database, and spreadsheet software, yours to use for your own professional and personal applications.

As you build your computer, performing key demonstrations and experiments at each stage of assembly, you get the confidence-building, real-world experience you need to work with, troubleshoot, and service today's most widely used computer systems.

No Experience Needed, NRI Builds It In

This is the kind of practical, hands-on experience that makes you uniquely prepared to take advantage of today's opportunities in computer

service. You learn at your own convenience in your own home.

No classroom pressures, no night school, no need to quit your present job until you're ready to make your move. And all

SEND TODAY FOR FREE CATALOG!

NRI

McGraw-Hill Continuing Education Center
3939 Wisconsin Avenue, NW, Washington, DC 20016

For Career courses approved under GI Bill

check for details.

CHECK ONE FREE CATALOG ONLY

- Computer Electronics
- TV/Video/Audio Servicing
- Robotics
- Electronic Music Technology
- Security Electronics
- Digital Electronics Servicing

- Electronic Design Technology
- Industrial Electronics
- Communications Electronics
- Basic Electronics
- Bookkeeping and Accounting
- Building Construction
- Automotive Servicing



- Air Conditioning, Heating & Refrigeration
- Small Engine Repair
- Electrician
- Locksmithing & Electronic Security
- Travel Careers
- Telephone Servicing
- Paralegal

Name (Please print) _____

Age _____

Street _____

City/State/Zip _____

We'll give you tomorrow.

Accredited by the National Home Study Council

3-128

DECEMBER 1988

Ask R-E

WRITE TO:

ASK R-E
Radio-Electronics
500-B Bi-County Blvd.
Farmingdale, NY 11735

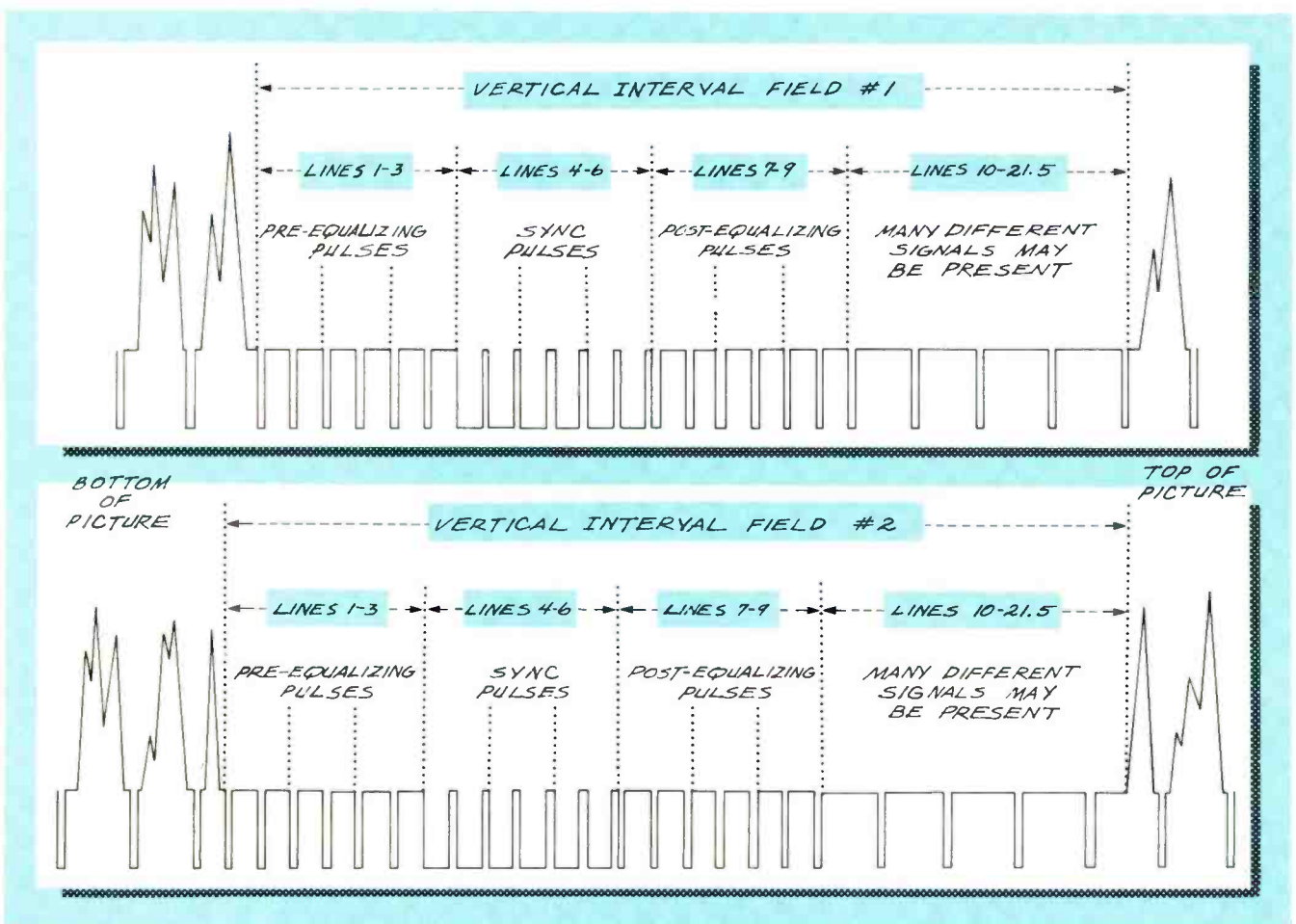


FIG. 1

Automatic editing

I've heard that commercial television sends "station break" signals and other information during the vertical interval. Is there some way that I could take advantage of that to automatically edit commercials when I'm recording off the air?—H. W., Santa Maria, CA

It is with the greatest sorrow and deepest sympathy that I tell you there is absolutely nothing you can be sure of finding in the ver-

tical interval other than equalizing pulses and the vertical-sync pulse. And however bad that sounds, that's only part of it. The complete story is even worse.

Here's the deal: There are actually two vertical intervals, one for each of the two fields of video that make up a full video frame. There are broadcast conventions defining what's on a particular line in each of the fields but they're only conventions—not law.

Figure 1 is the ideal vertical blanking interval as defined by the NTSC. Both fields are very similar in appearance and content but the timing difference between them lets television equipment know which field they're associated with. That information is important because it's used in maintaining sync for interlacing the two fields of standard video.

The vertical interval is defined to be 20½ horizontal lines of video.

The first three lines contain six *pre-equalizing pulses* and their job is to maintain interlace. The next three lines are the actual vertical-sync signal. There are six vertical-sync pulses that most television equipment combines into one long negative pulse. The last three lines have six *post-equalization pulses*, identical to the pre-equalization pulses on the first three lines.

Some of the remaining 11½ lines in the vertical interval are used by broadcasters for other purposes. For example, lines 17 and 18 are where you'll find the VITS (Vertical Interval Test Signal), line 19 is the location for the VIRS, (Vertical Interval Reference Signal), and line 21 is for Closed Caption data. But, sometimes those signals don't exist, so don't count on finding them there. The important thing to remember is that none of those signals will help you eliminate commercials.

But wait. There's even less.

Once upon a time you could build hardware that would automatically edit commercials from black and white broadcasts. The basic idea was that commercials were in color so you could detect the colorburst and use it to put your VCR in pause. After all, the broadcaster would turn off the colorburst during black and white video to keep things like false color and fringing from messing up the picture—but that is not true any more.

WHAT'S A LOCAL-DISTANCE SWITCH?

While watching a "Shoppers Channel" on TV, a radio was mentioned that had a local/distance switch to help pull in distant stations. How does that work? Is it an added amplifier or a stronger antenna?—L.R.G., Franklinville, NC

When designing a high-performance receiver, engineers often have to compromise between high sensitivity, high selectivity, or signal-handling capability. A set designed for high sensitivity may be easily overloaded by strong signals. Radio-frequency amplifiers designed to handle a wide range of signals can greatly increase the cost of the set. So, some designers

include a way to provide high sensitivity when needed, and a way to reduce the sensitivity to prevent circuit overload in the presence of stronger-than-average signals.

Radios that have local/distance switches are especially sensitive, and are easily overloaded by strong signals. When the switch is in the local position, it desensitizes the set by increasing the AGC (Automatic Gain Control) voltage to the RF amplifier or any stage that is ahead of the stage likely to

be overloaded. To receive distant stations, the listener puts the switch in the distance position. That reduces the AGC voltage so that the RF and IF amplifiers will run with maximum gain. Also, in electronically tuned radios, the local/distance switch determines what stations scanning will stop at. For instance, if you were to press the scan button while the radio is set in the local mode, the radio would stop at only the strongest of the received stations. **R-E**

Up to 50% Savings on Probes



Model SP100
Switchable 1X-10X \$ **43.**

Performance
Guaranteed

TEST PROBES, INC. **TPI**

9178 Brown Deer Road
San Diego, CA 92121

Call toll free for information
and free catalog:

1-800-368-5719
1-800-643-8382 in CA

ORDER FROM THESE DISTRIBUTORS

Or Phone Toll Free for the Distributor Nearest You



1-800-535-9593
1-800-462-9520 LA

contact east **Metermaster**

1-800-225-5370
(508) 682-2000 MA

1-800-962-8128
(213) 685-4340 CA



1-800-527-5018
(214) 550-1923 TX



1-800-363-6592 Canada
1-800-363-7601 QUE



(617) 879-7650



JENSEN TOOLS INC.
(602) 968-6231

BCS ELECTRONICS LIMITED
(416) 661-5585

ALLIED ELECTRONICS INC.
A SUBSIDIARY OF HALL SCARF ELECTRONICS CORP.
1-800-433-5700, (817) 336-5401 TX

WESTCON INC.
(503) 283-0132 OR, (206) 223-1133 WA

CIRCLE 123 ON FREE INFORMATION CARD

LETTERS



FROM RUSSIA...

I read G.O.P.'s letter regarding vacuum tubes that appear to be manufactured in the USSR ("Ask R-E," *Radio-Electronics*, October 1988), and your reply. It is quite possible that those tubes are, in fact, made in the USSR; U.S. Customs regulations require the country of origin to be marked on any imported item.

I, too, have been an electronics technician for over ten years; for most of that time, I was with a government agency. I regularly see tubes that are *definitely* manufactured in the USSR and Hungary—I get them through the Federal supply system! I haven't seen any quality problems with those tubes; the ones that I have tested are right in line with the specifications in my old *RCA Receiving Tube Manual*. Those of us who still work with vacuum-tube equipment are going to see more imported ones in the future, for one simple reason: There are many types of tubes that are no longer manufactured in the U.S. Once existing stocks are depleted, they

will all be imported from somewhere—including the Soviet Union.

In my opinion, G.O.P. should have nothing to worry about from "the authorities" by using those tubes. If they are good enough for Uncle Sam, they should be OK for everyone else. Electrons, fortunately, are not political—they don't care who pushes them. Think of it as doing your bit to bring capitalism to the Soviet empire, and to give *perestroika* and *glasnost* a little help.

GRAEME C. PAYNE
Summerville, SC

...WITH...

I hate to burst your bubble, but you didn't do your homework before you answered the inquiry on "Red Star" 6L6's. Without a doubt, the tubes in question were made in Russia.

Because the U.S. and most, if not all, other foreign sources decided to abandon that section of the electronics market, the "Evil Empire" has moved in to fill the void.

Get used to it—in the future, when you need a 6L6, KT66, 6CA7, or whatever to keep your treasured Ultra-Linear Williamson alive, that's where it's likely to come from. And hold your breath when you ask the price!

AL YEAGER
Portsmouth, NH

...TUBES

I'm afraid you really missed the mark with your answer to G.O.P. regarding his question about Russian tubes: The part in question was almost certainly a Commie!


The giveaway on that 6L6 is the overly large plastic base, coupled

with a large glass projection (about 1-inch tall) at the bottom of the envelope. That device is *notorious* in the musical-instrument tech industry—for poor quality. Another problem one can encounter when installing those Russian 6L6's in guitar amps is that most musical-instrument amps operate the tubes in an upside-down position, using a spring-steel clamp to keep the tube in the socket. The Russian tube's base is too large to fit through the tube clamp, so the tech has to squash the clamp down against the chassis, or remove it. Either way, if the tube doesn't fry itself first, it will certainly commit suicide by jumping out of the hole when the amp is transported to jobs. Believe me; I learned that the hard way!

High-power audio-output tubes are getting hard to come by these days, and the importers are turning in droves to the few remaining tube producers. Most of the manufacturers currently producing the 6L6 are in the communist bloc. I've seen that particular tube marked with such brands as RCA, GE, United, Radio Shack, Mullard, and Penta Labs, and it stamped with such countries of origin as USSR, Poland, East Germany, West Germany, Hungary, Yugoslavia, England, France, and even U.S.A.! My contacts in the tube industry tell me that *all* of them, regardless of what's marked on the box or the glass, come out of a shoddy little factory in Yugoslavia.

There are some good tubes to be had from Russia. There is an outfit that imports certain types, screens them extensively, and markets them under the brand name "Virgin Commies" (no kidding). You can find their ads in

CALIBRATE

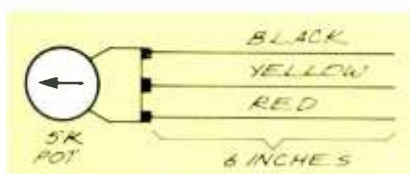

For those of you who were confused on how to calibrate the Breath Alert blood-alcohol monitor (*Radio-Electronics*, October 1988), here's the missing Fig. 9 so you can obtain the correct calibration voltages. We're sorry about the inconveniences.

—Editor

OPTOELECTRONICS INC.

FREQUENCY COUNTERS TO 2.4 GHZ

8 LED DIGITS • 2 GATE TIMES
ALUMINUM CABINET
INTERNAL NI-CAD BATTERIES INCLUDED
AC ADAPTER/CHARGER INCLUDED

EXCELLENT SENSITIVITY & ACCURACY

AC-DC • PORTABLE OPERATION

NEW

POCKET SIZE

SIZE: 4" H x 3.5" W x 1" D
MADE IN USA

#TA-1005



Small enough to fit into a shirt pocket, our new 1.3 GHz and 2.4 GHz, 8 digit frequency counters are not toys! They can actually out perform units many times their size and price! Included are rechargeable Ni-Cad batteries installed inside the unit for hours of portable, cordless operation. The batteries are easily recharged using the AC adapter/charger supplied with the unit.

The excellent sensitivity of the 1300H/A makes it ideal for use with the telescoping RF pick-up antenna; accurately and easily measure transmit frequencies from handheld, fixed, or mobile radios such as: Police, firefighters, Ham, taxi, car telephone, aircraft, marine, etc. May be used for counter surveillance, locating hidden "bug" transmitters. Use with grid dip oscillator when designing and tuning antennas. May be used with a probe for measuring clock frequencies in computers, various digital circuitry or oscillators. Can be built into transmitters, signal generators and other devices to accurately monitor frequency.

The size, price and performance of these new instruments make them indispensable for technicians, engineers, schools, Hams, CBers, electronic hobbyists, short wave listeners, law enforcement personnel and many others.

STOCK NO:

- #1300H/A Model 1300H/A 1-1300 MHz counter with preamp, sensitivity, < 1mV, 27MHz to 450MHz includes Ni-Cad batteries and AC adapter **\$169.95**
- #2400H Model 2400H 10-2400 MHz microwave counter includes Ni-Cad batteries and AC adapter **\$299.95**
- #CCA Model CCA counter/counter, for debugging, ultra sensitive, < 50 micro volts at 150MHz! 1-600 MHz with adjustable threshold, RF indicator LED. Includes Ni-Cad batteries and AC adapter **\$299.95**

ACCESSORIES:

- #TA-1005 Telescoping RF pick-up antenna with BNC connector **\$12.00**
- #P-100 Probe, direct connection 50 ohm, BNC connector **\$20.00**
- #CC-12 Carrying case, gray vinyl with zipper opening. Will hold a counter and #TA-1000S antenna. **\$10.00**



ORDER FACTORY DIRECT
1-800-327-5912

FLA (305) 771-2050



AVAILABLE NOW!

OPTOELECTRONICS INC.

5821 N.E. 14th Avenue
Ft. Lauderdale, Florida 33334

Orders to US and Canada add 5% of total (\$2 min, \$10 max)
Florida residents add 6% sales tax. COD fee \$2.
Foreign orders add 15%

CIRCLE 101 ON FREE INFORMATION CARD

www.americanradiohistory.com

DECEMBER 1988

high-end audio-specialty magazines. Word has it that they reject about 90% of everything they get, though; that might explain their outrageous prices.

W.A. "FAT WILLIE" WHITTAKER, JR.
Denver, CO

PATENTLY MISLEADING

I was dismayed to see Don Lancaster's extremely negative statements about patents ("Hardware Hacker", *Radio-Electronics* Oc-

tober 1988), especially since most of them are untrue. Perhaps he is making a gross overgeneralization because of one unprofitable experience he's had with patents.

His admonition not to even think about patenting is absurd. As a patent attorney, I have several independent-inventor clients who have made handsome profits—over \$1,000,000 in one case—from patents. Consider Polaroid's recent award of over \$10,000,000 from Kodak, for infringement of

Polaroid's instant-camera patents. And don't forget the major drug companies: As soon as a patent on a drug expires, the clones come in and sell what was formerly a 75-cent pill for 20 cents. Does Mr. Lancaster think that any of those patent holders would agree with him?

His statement that three helpline callers are trying to get patents on old ideas may be true. But is it fair to blame the patent system for the patent applicants' failure to make adequate searches before filing?

The Patent and Trademark Office (PTO) does not offer poorer odds than a state lottery—the PTO doesn't offer any odds at all. It simply grants a 17-year monopoly on any invention presented to it (no matter how harebrained) that it finds to be substantially different from the prior art. It has no responsibility for, authority over, or interest in the commercial success of the inventions that it patents. That is totally the responsibility of the inventor. A patent should never be construed as any indication of commercial value—only that the invention is "unobvious" over the "prior art."

Mr. Lancaster's statement that "Not one single patent in one hundred will ever show any positive cash flow" is a gross exaggeration, but has some truth. Probably only one in twenty patents is profitable or covers a commercial product. The low success rate of patented inventions is, again, not due to the patent system, but to the failure of most inventors to adequately investigate their brainchild's commercial prospects before filing, and inadequate promotion thereafter. I have devoted a whole chapter in my book (*Patent It Yourself*, Nolo Press) to the need for stringent commercial evaluation before filing and another chapter to urge vigorous exploitation after filing. However, I admit that many inventors still don't get that important message.

Mr. Lancaster's statement that not one patent in a thousand will stand up if challenged is another wild exaggeration. At present over 60% of all litigated patents are upheld. That doesn't count those that never make it to court be-

★ **CABLE TV SPECIALS** ★

CONVERTERS

	JRX-3 DIC—36 Channel Corded Remote	\$129. ⁹⁵
	RCA 58-3 58 channel set top with Jerrold Decode	\$99. ⁹⁵
	SB-3 — 'The Real Thing'	\$109. ⁹⁵
	SB-3-Taiwan Copy	\$89. ⁹⁵
	DRZ-3D1C—68 Channel Wireless with Decoder	\$199. ⁹⁵
ZENITH:	Z-TAC Cable Add-On	\$169. ⁹⁵
VIEW STAR:	MXC 2001—65 Channel Wireless— with Parental Lockout	\$89. ⁹⁵
	MXC 2001 A-B—Same as above with A-B Switch	\$109. ⁹⁵
	MXC 2501—65 Channel Wireless with Volume	\$119. ⁹⁵
	Universal V7472—72 Channel Wireless Remote MTS Stereo Converter-Full Feature Decoder Compatible	\$129. ⁹⁵
MISCELLANEOUS		
OAK:	ECONO-3V Mini-Code	\$89. ⁹⁵
	ECONO-3V Mini-Code Vari-Sync	\$89. ⁹⁵
	ECONO-3V Mini-Code Vari-Sync Plus Auto On-Off	\$119. ⁹⁵
OAK:	Sine-wave Anti-Jammer Kit	\$39. ⁹⁵
OAK:	M35B 36 Channel Converter— Decoder	\$109. ⁹⁵
JERROLD:	400 & 450 Handheld Transmitters	\$29. ⁹⁵
HAMLIN:	MLD-1200 Channels 2 or 3	\$99. ⁹⁵
NEW ITEMS:	Scientific Atlanta SA-3	\$129. ⁹⁵
GENERAL		
INSTRUMENTS:	VCU Amplified Video Switch Signal Amplifier	\$59. ⁹⁵
ALL UNITS GUARANTEED. QUANTITY PRICES AVAILABLE.		
UNITED ELECTRONIC SUPPLY		
P.O. BOX 1206 • ELGIN, ILLINOIS 60121 • 312-697-0600		

cause the infringer saw the handwriting on the wall and agreed to pay the patent owner royalties.

His claim that the side with the most resources wins in patent litigation has been changed by the reexamination procedure, where the validity of most challenged patents can be decided—economically—by the PTO instead of in an expensive court proceeding. In litigation, the individual inventor has a tremendous advantage: In cases where an individual inventor sues a big company, juries love to find in favor of you-know-who.

It is true that many valuable and successful products, like the Apple and IBM computers, weren't covered by any major patents. But thousands of great products—Dolby noise reduction, floppy disks, and videocassette tapes, to name a few electronic ones—are patented and earn handsome royalties.

It is not true that many large companies won't look at outside ideas for fear of getting sued. Almost every company in the U.S. will be glad to look at an outsider's ideas. They will protect themselves by first having the inventor sign their "waiver" form, that requires the inventor to rely only on his or her patent rights. But they will look. Big companies have one major drawback: the Not-Invented-Here syndrome. That's why I recommend in my book that inventors try only smaller companies, which are more receptive to outside ideas.

Finally, it might surprise Mr. Lancaster to learn that each year the PTO issues about 75,000 patents, and that tens of billions of dollars change hands in the U.S. for the licensing and sale of patent rights—hardly something a hacker can ignore!

DAVID PRESSMAN,
San Francisco, CA

BIOFEEDBACK FEEDBACK

As a subscriber to *Radio-Electronics* for about five years, I've enjoyed each and every issue, and I've even built a few of the projects detailed. The "Biofeedback Monitor" (*ComputerDigest*, October 1988) sounded simple and interesting—like something I'd want to tackle.

Most of the parts needed could

easily be scrounged from my junkboxes; the rest were readily available locally. It went together very easily in one evening—after which, unfortunately, I spent a good deal of time troubleshooting its improper operation.

I set out to use a CMOS NE555C to minimize the draw on my batteries, as I intended to use Ni-Cad rechargeables and wanted them to last as long as possible between charges. Building it with that in mind, I fell victim to a minor

point—missed in the article—that can probably be safely ignored if using a non-CMOS 555. But it really caused me a headache.

The functional block diagram for a 555 shows that pin 4 is called RESET, an active low-input signal. Typically, in non-CMOS applications that input probably floats high. With the indeterminate nature of CMOS inputs, I was getting erratic operation; RESET was preventing the circuit from functioning as intended. That was re-

Get your hands on the standard: POMONA.

Since 1951 POMONA has grown to become the standard of the industry. And for good reason. Our test products assure honest test results because they are the best you can buy. Specify POMONA and get unsurpassed quality, the broadest product line, the greatest selection, the industry standard.




For your FREE 1988 General Catalog, circle reader service number printed below

POMONA
ITT Pomona Electronics

CIRCLE 101 ON FREE INFORMATION CARD

www.americanradiohistory.com

Digital scopes with a

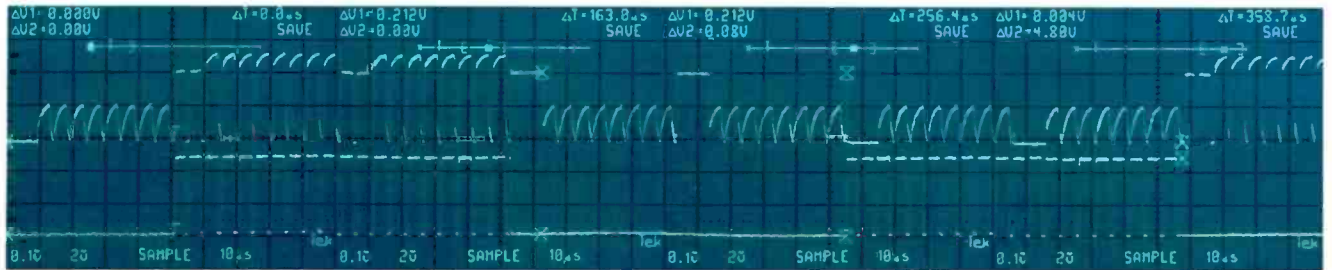

Give up real-time capability for storage? Not with Tek!

That's because analog capability is integral to low-cost Tek digital storage oscilloscopes. So you need only one instrument to make all your measurements efficiently. With no trade-offs.

It's another Tek advantage: analog and digital in one familiar, affordable package.



Select either mode at the push of a button.

With digital storage you can capture events which are difficult if not impossible to see on conventional scopes. Pre and post trigger events. Fast transients.

Single-shot events.
Elusive glitches.
Low-speed phenomena.

Four screen photos spliced end to end illustrate the benefit of full four-screen capture using the 2230's 4K record length.

Any waveform can be viewed for as long as you like. Or stored in 4K of memory for later analysis or comparison to other waveforms. And if there's a question about a digital measurement, just push a button for real-time display analysis.



real-time advantage.

The affordable portables.

These are the world's best-selling digital storage oscilloscopes. And with the new 20 MHz Tek 2201 joining the family, there's now an even better selection—in bandwidth, performance and price.


Select for advanced features such as 100 ns glitch capture at any sweep speed, CRT readout, measurement cursors, multiple acquisition modes and hardcopy output, plus optional GPIB or RS-232-C interfaces and software.

These scopes are perfect for first-time digital users. And seasoned operators will appreciate even more their versatility, convenience and value. All backed

Features	2230	2221	2220	2210	2201 ^{NEW}
Bandwidth	100 MHz	60 MHz	60 MHz	50 MHz	20 MHz
Max. Sampling Speed	20 MS/s	20 MS/s	20 MS/s	20 MS/s	10 MS/s
Vertical Resolution	8-12 bits	8-10 bits	8 bits	8 bits	8 bits
Record Length	1K/4K Selectable	4K	4K	4K	2K
Glitch Capture	100 ns	100 ns	100 ns	No	No
CRT Readout/Cursors	Yes	Yes	No	No	No
GPIB/RS-232-C Options	Yes	Yes	Yes	No	RS-232-C Hardcopy
Warranty	3-years on labor and parts including CRT				
Price	\$4995	\$3995	\$2995	\$2395	\$1495



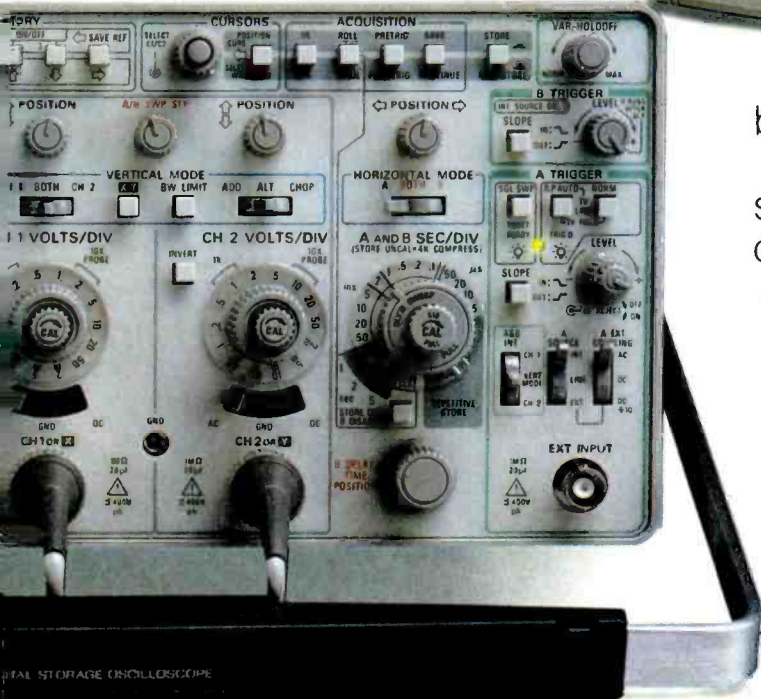Each scope offers a range of capabilities you'd expect to find only in much more expensive instruments.



by Tek quality and a 3-year warranty. Discover the potential. Let Tek show you what you're missing... without making you give up analog to see it. That's the real-time advantage of Tek digital storage.

For easy ordering or more information call Tek Direct:

1-800-426-2200



Tektronix
COMMITTED TO EXCELLENCE

CIRCLE 92 ON FREE INFORMATION CARD

ELECTRONIC COMPONENTS CATALOG

... yours **FREE** by dialing

1-800-992-9943

IN TEXAS, call; 1-800-346-6873

Call Today for your **FREE** subscription to the latest Mouser Electronics Catalog. Contains 192 pages featuring over 17,000 in-stock, quality electronic components. ..**PLUS**.. Mouser's proven service and prompt delivery.

Outside U.S.A., Send \$2.



MOUSER ELECTRONICS
2401 Hwy 287 North
Mansfield, Texas 76063

DISTRIBUTION CENTERS COAST-TO-COAST

CIRCLE 117 ON FREE INFORMATION CARD

DIGITAL VIDEO STABILIZER ELIMINATES ALL VIDEO COPY PROTECTIONS



While watching rental movies, you will notice annoying periodic color darkening, color shift, unwanted lines, flashing or jagged edges. This is caused by the copy protection jamming signals embedded in the video tape, such as Macrovision copy protection. Digital Video Stabilizer: RXII completely eliminates all copy protections and jamming signals and brings you crystal clear pictures.

FEATURES:

- Easy to use and a snap to install
- State-of-the-art integrated circuit technology
- 100% automatic - no need for any troublesome adjustments
- Compatible to all types of VCRs and TVs
- The best and most exciting Video Stabilizer in the market
- Light weight (8 ounces) and Compact (1x3.5x5")
- Beautiful deluxe gift box
- Uses a standard 9 Volt battery which will last 1-2 years.

WARNING :

SCO Electronics and RXII dealers do not encourage people to use the Digital Video Stabilizer to duplicate rental movies or copyrighted video tapes. RXII is intended to stabilize and restore crystal clear picture quality for private home use only.

(Dealers Welcome)

To Order: \$49 ea + \$3 for FAST UPS SHIPPING

1-800-445-9285 or 516-694-1240

Visa, M/C, COD M-F: 9-6 (battery not included)

SCO ELECTRONICS INC.

Dept. C11 62 Marine St. Farmingdale NY 11735

Unconditional 30 days Money Back Guarantee

CIRCLE 200 ON FREE INFORMATION CARD

mediated by adding a pullup here to the supply.

After that small addition, all worked as advertised. My box is a resounding success at the office, where the challenge is to see who can relax the quickest.

MARK J. CULROSS
Fort Worth, TX

ANTIQUe CAR-RADIO REPAIR

"Antique Radios" (Radio-Electronics, July 1988) referred to electronic replacements available for vibrators, but gave the impression that they all required external mounting, gave inferior performance, and would detract from the value of the radio.

We have been manufacturing a direct, electronic plug-in replacement for 6- and 12-volt units for two years. They perform very well and do not require any mounting. They are also economically priced. We repair original vibrators, too.

TERRENCE CHURCHMAN

Radio Resurrection
110 North El Nido Ave.
Monrovia, CA 91016



Prototyping Made Easy. In The Quantities You Require.

Your Electronic Specialty Products distributor has a wide selection of 3M breadboards and prototyping labs in the quantities and styles you desire.

We invented solderless breadboarding with one thought in mind: "make it fast and easy!" And we build these products with American made reliability.

Whether your requirements demand 3M's A·C·E 100 Series solderless breadboards or Powerace prototyping labs with self-contained power supplies, or our newest Powerace labs

with removable boards, you'll find what you need at your authorized 3M Electronic Specialty Products distributor.

For educators, students, hobbyists and even professional designers, 3M prototyping products make circuit building and testing fun and easy. And whether you need one breadboard or a hundred, we've got them packaged as you need them.

Your Electronic Specialty Products distributor also has all the prototyping tools you'll need. Tools such as jumper wires, adaptor pins and patch cords.

For the name of your nearest 3M A·C·E Board and Powerace distributor, call toll free 800-321-9668 or (216) 354-2101 in Ohio.

**Electronic Specialty Products
3M Electronic Products Division**

9325 Progress Parkway
Mentor, Ohio 44060

We've Packaged Our Solutions.



CIRCLE 76 ON FREE INFORMATION CARD

For **SUCCESS** in your Vocation or Profession *LEARNING is Where It's At!*

You'll need a "*Learning Environment*" in your home (or office) to work on your degree with "*the college that comes to you,*"

GRANTHAM COLLEGE OF ENGINEERING



Grantham makes your **understanding** of electronics and computers its most important teaching objective. You are never rushed or held back; you study at your own pace. Learn more by self-paced home study, with Grantham instructors standing by to help you.

Accredited

Now in Our 38th Year

***A.S. and B.S. Degrees
Awarded***

Phone or write for our Home Study Degree Catalog:

Phone 213-493-4421 (no collect calls)

or write

Grantham College of Engineering

10570 Humbolt Street

Los Alamitos, California 90720

Grantham College of Engineering is accredited by the Accrediting Commission of the National Home Study Council in Washington, D.C.

Grantham College of Engineering
P.O. Box 539, Los Alamitos, CA 90720

Please mail me your free catalog with gives details of your home-study degree programs, including enrollment information.

NAME _____

ADDRESS _____

STATE and ZIP _____

R-12-88

EQUIPMENT REPORTS

Amdek's Laserdek 1000

550 megabytes in the space
of a floppy!

CIRCLE 45 ON FREE INFORMATION CARD



IF THE IDEA OF HAVING 550 MEGABYTES of optical storage at your fingertips intrigues you, but the thought of having to buy a high-priced external CD-ROM drive for that privilege turns you off, then you haven't heard about Amdek's half-height CD-ROM for the IBM PC and its clones.

Called the Laserdek 1000, this \$895 CD-ROM drive fits into a single floppy-disk-drive bay. A half-length adapter board controls all CD-ROM functions and an assortment of software utilities put the drive through its paces—including a program that lets you use your CD-ROM drive as if it were an audio CD player.

An obvious advantage of an optical disk is the amount of data that it can store. Because the holes are microscopic in size, much more data can be placed on an optical disk than can be put on a floppy disk. In fact, it takes over 1500 floppy disks to equal the 550-MB capacity of a single CD.

A compact compact

The Laserdek 1000 is the first CD drive to install inside a PC. Previous CD-ROM's, like Amdek's Laserdek 2000, have been full-height external units that must

compete with the PC and other peripherals for desk space.

The Laserdek 1000 can be installed in any IBM PC, XT, AT, or compatible. Installation is equivalent to installing an internal hard disk. The half-length card is inserted into any empty 8-bit expansion slot and the drive is fitted into one of the drive bays; slide rails are available for AT installation. Power is obtained from the PC's power supply via a standard power connector. The drive contains four DIP switches that you don't have to adjust unless you are installing more than one CD-ROM in the system.

The software drivers automatically install themselves onto your hard disk using an installation utility. During the software-installation process, your CONFIG.SYS and AUTOEXEC.BAT files are modified to recognize the presence of the CD-ROM. When the system is rebooted, the Laserdek 1000 appears as a D: drive (or E: drive, if you have two hard disks). You can then access the CD-ROM as you would any other disk drive, which means that you can display a directory of the disk's contents.

Software availability

Within the last year, there has

been a generous offering of general-purpose CD's—including the very popular Microsoft Bookshelf (see the January 1988 issue of "Computer Digest" for a review). There is always the venerable Grolier Electronic Encyclopedia, and Lotus has announced that it will publish a trillion and a half pages of financial data that interfaces with 1-2-3.

The sounds of music

When you're not running Microsoft Bookshelf or some other CD application, you can use your Laserdek 1000 to play Tchaikovsky or Hank Williams. To use the Laserdek 1000 as an audio CD player, simply plug a set of headphones into the front of the drive and run the audio software that comes with the drive. Headphone volume is adjusted by a control that is also located on the front of the drive.

The audio software requires 10K and becomes RAM resident when installed, which means that you can go about your normal PC business while the music plays in the background. An Amdek utility allows you to select specific tunes from the disk, skip around tracks, or program the drive to play a sequence of songs.

If the rather thin sound of the earphones is objectionable, you can run the music through your stereo system by plugging into the jacks provided at the back of the drive. In its current configuration you will need a special connector (available from Amdek) to plug into the drive, but Amdek claims it will soon have standard RCA jacks on the Laserdek 1000 for the audio interface.

Conclusion


While the Laserdek 1000 isn't going to set the world afire at \$895, it

continued on page 105

JANUARY 1989

WATCH FOR THIS

ISSUE

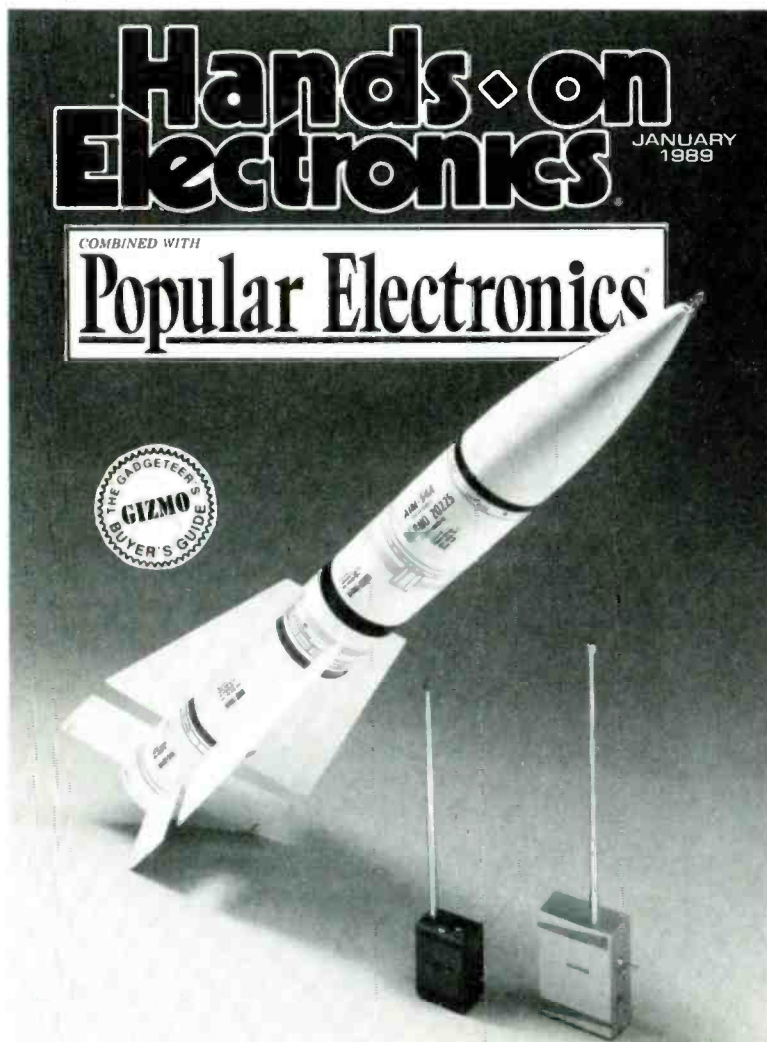

FEATURING:

ROCKET STROBE

Find that model rocket easily, even in tall weeds or at night!

PERSONAL POCKET PAGER

Our build-it-yourself pager lets you stay in touch at home, work, or play!

BUILD THE SPEEDI-WATT

It's a motor controller, a light dimmer, and more!

10-MHz FREQUENCY COUNTER

Build this valuable addition to any hobbyist's workbench!

ON SALE NOVEMBER 22, 1988

ADDITIONALLY:

GIZMO

Our monthly look at what's hot in consumer electronics!

E-Z MATH

An easy-to-understand primer on the numbers of electronics!

CIRCUIT CIRCUS

HAM RADIO

DX LISTENING

COMPUTER BITS

SCANNER SCENE

ANTIQUÉ RADIO

THINK TANK

NEW PRODUCTS



CIRCLE 10 ON FREE INFORMATION CARD

HOME-THEATER SOUND. Pre-recorded video tapes are hot items: American households devote an average of 7.1 hours to watching them every week—spending almost twice as much money on tapes than on going out to the movies. And an increasing percentage of those tapes are encoded for surround sound, as are some current made-for-TV movies.

Shure Brother's *HTS Theater Reference System*, aimed at the top end of that viewing market, is the first complete audio system for home theater.

The system centers around an exceptionally accurate surround-sound decoder, the *HTS5300 Acra Vector Decoder*, with wireless remote.

Three *HTS50SPA Signal Processing Amplifiers*—the direct links between decoder and speakers—balance the entire system. With switchable outputs, the appropriate amount of compensation can

be added to each speaker, greatly reducing distortion.

The system's array of six loudspeakers was designed to provide the best possible sound from the smallest possible speakers. It includes one model *HTS50CF* center-front speaker, four model *HTS50LRS* left-right-surround speakers, and the model *HTS50SW* subwoofer speaker.

The multiple sound sources permit flexible seating arrangements anywhere within the perimeter of the speakers; a large room isn't required for good performance.

The *HTS Theater Reference System*—one decoder, three amplifiers, one center-front speaker system, four left-right-surround speaker systems, and one subwoofer-speaker system—has a suggested retail price of \$9600.00.—**Shure Brothers, Inc.**, Home Theater Sound Division, 222 Hartrey Avenue, Evanston, IL 60202-3696.

SCANNING CABLE TESTER. This microprocessor-based tester automatically tests from one point to all other points of a data-interface cable. It can program itself from a good sample, making it easy to test RS-232 cable prior to installation.

The unit features two rows of 26 LED's and twin 2-digit displays; the scanning sequence for shorts, opens, continuity, and miswiring is quickly identified. The user can choose the SCAN mode to test each cable lead automatically, or the STEP mode for one-step-at-a-time testing.

A loop-back receiver module is included for remote testing of installed cables. The tester "learns" from a good reference cable by storing the complete wiring configuration in memory. Then it sequences a "comparison test" between the cable being tested and the stored memory. A PASS or FAIL determination appears in less than one second, and then the final wiring information appears as LED indications for the user's reference.

The unit comes equipped to test any RS-232 cable using male or female DB-25 connectors; optional adaptor cables for testing DB-9 cables and DB-25 varieties are available. The tester operates from a 115-volt AC source. With the optional purchase of six rechargeable pen cells and battery holder, portable use is possible.




CIRCLE 11 ON FREE INFORMATION CARD

The cable tester, with padded vinyl carrying case, is priced at \$359.00.—L-COM Data Products, 1755 Osgood Street, North Andover, MA 01845.

AM/FM STEREO TUNER. Audio Dynamics' T-2000E programmable, remote-controllable AM/FM tuner combines Schotz noise reduction, efficient interference rejection, and wide separation with attractive, low-profile styling. It allows up to 10 AM and 10 FM stations to be programmed for instant access.

Audiophile-quality features include a 1.5-dB capture ratio over the entire signal-strength range of 25 to 65 dB, providing effective interference control even for weak stations. Separation is well over 30 dB across the entire radio band, and Schotz noise reduction affords quieter stereo reception.

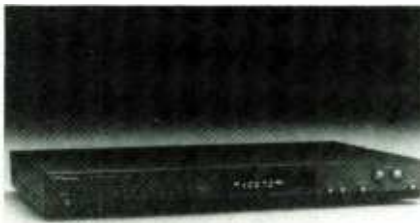The tuner's high performance and clean Euro-style design match Audio Dynamics' CD-2000e CD



CIRCLE 12 ON FREE INFORMATION CARD

player and CA-2000E integrated amplifier. Armchair operation of the tuner is possible with the wireless remote control that is supplied with that amplifier.

The T-2000E has a suggested list price of \$349.00.—Audio Dynamics Corporation, 851 Traeger Avenue, San Bruno, CA 94066.

SOLDER DISPENSER. A product that simplifies a frequently performed task is always welcome. The SOLDERSTAT wrist-strap dispenser falls into that category, by slashing soldering time by as much as 40%.

The spool dispenser is attached to an elastic or Velcro static-control strap, so that up to ¼-pound of solder can be fed out directly from the wrist. The unit unsnaps for easy reloading.



CIRCLE 13 ON FREE INFORMATION CARD

The SOLDERSTAT, with an elas-

tic strap for one-time adjustment, costs \$8.00. With a Velcro strap, it costs \$9.50. Options include an adjustable static-control elastic strap for \$7.00, and a six-foot coiled grounding cord for \$9.50. (Please add \$2.00 for postage and handling to each order.)—SGW Co., 6414 Hallee Road, Joshua Tree, CA 92252; phone 1-800-537-1535.

SCANNER-RECORDING. Electron Processing's TAPE-SAVER TS-1 provides a way for scanner owners to

Special INSTRUMENT SALE!

Joseph Electronics' 40th Anniversary Specials!

Model 2120 Oscilloscope
DC to 20 MHz. Dual Trace, 6" CRT, 1mv Sensitivity.
Reg. \$520 **\$379.40**
40TH ANNIVERSARY PRICE

Model 2125 Oscilloscope
Same great features as 2120, except with delayed sweep
Reg. \$620 **\$519.40**
40TH ANNIVERSARY PRICE

Model 1541A Oscilloscope DC to 40 MHz, Dual Trace, 6" CRT 1mv Sensitivity
Reg. \$845 **\$739.40**
40TH ANNIVERSARY PRICE

Model 2160 Oscilloscope DC-60MHz, Dual Trace, delay sweep, 6" CRT, 1mv. sensitivity
Reg. \$995 **\$839.40**
40TH ANNIVERSARY PRICE

Model 2520 Digital Storage 20MHz, Dual Trace, 2mv Sens
Reg. \$1990 **\$1795.40**
40TH ANNIVERSARY PRICE

Model 2521 Digital Storage 20MHz, Dual Trace CRT Readout, Cursors, RS232 Interface
Reg. \$3050 **\$2745.40**
40TH ANNIVERSARY PRICE

Model 1249 NTSC/RGB Color Bar Generator, Composite Video Output, RF Output
Reg. \$499 **\$419.40**
40TH ANNIVERSARY PRICE

Model 2009 MTS TV Stereo Generator Ideal for Stereo TV, Receivers, VCR's and Stereo Adapter Service
Reg. \$499 **\$419.40**
40TH ANNIVERSARY PRICE

Model 2830 3 1/2 DIGIT LED BENCH Multimeter .5 DCV Accuracy, ALL 33 Ranges and Functions are Push Button Selectable
Reg. \$243 **\$209.40**
40TH ANNIVERSARY PRICE

Model 1045 Telephone Product Tester Provides Basic Operation Tests for Corded and Cordless Telephones, Answering Machines and Automatic Dialers
Reg. \$495 **\$415.40**
40TH ANNIVERSARY PRICE

Model 1803 Frequency Counter 100 MHz, 8 digit display, zero blanking AC or Battery
Reg. \$199 **\$169.40**
40TH ANNIVERSARY PRICE

Model 2005 RF Signal Generator 100 KHz to 150 MHz, in 6 fundamental bands and 450 MHz in harmonics
Reg. \$195 **\$165.40**
40TH ANNIVERSARY PRICE

Model 3011 Function Generator 2 MHz, 4 digit display, TTL & CMOS pulse outputs
Reg. \$239 **\$199.40**
40TH ANNIVERSARY PRICE

Model 1630 DC Power Supply 0-30V, 0-3A, high-low current range, Low ripple
Reg. \$251 **\$209.40**
40TH ANNIVERSARY PRICE

Model 1601 DC Power Supply isolated 0-50V, 0-2A in ranges, fully automatic shutdown, Adj current limit
Reg. \$463 **\$389.40**
40TH ANNIVERSARY PRICE

Model 1650 Triple Output Power Supply two 0-25 VDC @ 5A and 5VDC @ 5A, fully automatic shutdown
Reg. \$489 **\$409.40**
40TH ANNIVERSARY PRICE

Model 1653 AC Power Supply variable isolated 0-150 VAC @ 2A, built-in isolation transformer
Reg. \$200 **\$169.40**
40TH ANNIVERSARY PRICE

NEW! Model 388-HD Hand-held 3 1/2 Digit LCD TEST BENCH
41 voltage ranges, frequency counter, capacitance meter, logic probe, transistor and diode tester. All packed into a drop-resistant case. **SPECIAL PRICE!**
Reg. \$139 **\$119.40**



We are celebrating our 40th Anniversary by offering you huge savings on B&K Test Equipment.

Send for FREE 480 page "Industrial Products Catalog." I understand it is FREE with any order or if requested on company letterhead. (Otherwise, \$4.95 to cover catalog and shipping costs.)

ORDER TOLL FREE
1-800-323-5925
IN ILLINOIS
312-297-4200
FAX: 312-297-6923



JOSEPH ELECTRONICS, INC. Dept. R
8830 N. Milwaukee Ave., Niles, IL 60648

Rush merchandise per attached order
 I understand rated accounts are shipped open account, otherwise send per credit card.

Include \$5.00 per item for shipping and handling

Visa Master Card Discover
 Check Money Order Rush Catalog

Card No. _____ Exp. Date _____

Name _____

Company _____

Street Address _____

City _____ State _____ Zip _____

IL Res. 7% Tax

When performance & price really count...



CRYSTEK CRYSTALS

The pulse of dependable communications

QUARTZ CRYSTALS FOR Industrial Equipment/Instrumentation

- Micro-processor control
- Computers/Modems
- Test/Measurement
- Medical

General Communications

- Channel element Service (VHF/UHF)
- Land Mobile 2-way
- Marine
- Aircraft
- Telemetry
- Monitors/Scanners/Pagers

Amateurs/2-Meter/General Coverage CB/Hobbyist/Experimenter

The Pulse of Dependable Communications...

Crystek Crystals offers their new 16 page **FREE** catalog of crystals and oscillators. Offering state of the art crystal components manufactured

For Optimum
Stability and
Reliability in
Frequency
Management

Custom Made Crystals Catalog

by the latest automated technology. Custom designed or "off the shelf." Crystek meets the need, worldwide. Write or call today!



NEW

CRYSTEK CORPORATION
DIVISION OF WHITEHALL CORPORATION



2351/2371 Crystal Drive • Ft. Myers, FL 33907
P.O. Box 06135 • Ft. Myers, FL 33906-6135
TOLL FREE 1-800-237-3061
PH 813-936-2109/TWX 510-951-7448/FAX 813-939-4226
TOLL FREE IN THE U.S.A. EXCEPT FLORIDA, ALASKA, HAWAII

CIRCLE 190 ON FREE INFORMATION CARD

"MADE IN U.S.A."



We've been supplying quality crystals since 1965...long before the flood of cheap imports.

We're still supplying quality crystals with:

- QUICK TURNAROUND
- LOW PRICE
- HIGH QUALITY

TO SOLVE YOUR
CRYSTAL
PROBLEMS,
CALL OR WRITE
FOR THIS FREE
CATALOG:



JAN CRYSTALS

P.O. BOX 06017
FORT MYERS, FL 33906
(813) 936-2397

TOLL-FREE: 1-800-237-3063

IN FLORIDA: 1-800-226-XTAL
FAX ORDERS: 1-813-936-3750

CIRCLE 104 ON FREE INFORMATION CARD

NEW SUPER LONG PLAY TAPE RECORDERS

12 Hour Model — \$105.00*
USES D-120 TAPE

Modified Panasonic Slimline,
high quality, AC-DC
Recorders provide 6
continuous hours of quality
recording & playback on
each side of cassette for a
total of 12 hours.
Built-in features include
• Voice level control, • Digital
counter, etc. TDK DC 120
Cassette Furnished.



PHONE RECORDING ADAPTER

Records calls automatically. All Solid
state connects to your telephone
jack and tape recorder. Starts
recording when phone is lifted.
Stops when you hang up. \$24.50*
FCC APPROVED



VOX VOICE ACTIVATED CONTROL SWITCH
Solid state. Self contained. Adjust-
able sensitivity. Voices or other
sounds automatically activate and
control recorder. Uses either re-
corder or remote mike. \$24.95*
FCC APPROVED



*Add for ship & hdg. Phone Adapter & Vox \$1.50 ea.
Recorders \$4.00 ea. Cal. Res. add tax. Mail order, VISA,
MIC, COD's OK. Money Back Guarantee. Qty. disc.
avail.. Dealer Inquiries invited, Free data. ©
AMC SALES INC. Dept. 9335 Lubec
St., Box 928, Downey, CA
90241 Phone (213)
869-8519

CIRCLE 108 ON FREE INFORMATION CARD



CIRCLE 14 ON FREE INFORMATION CARD

avoid wasting recording tape during periods of scanner inactivity. The unit connects the tape recorder to the scanner and automatically switches the tape recorder on and off via its remote-control jack. With the "dead time" removed by the *TS-1*, an entire evening's monitoring can be listened to in less than an hour.

Standard mini-plugs are used to connect the scanner and the recorder. A sub-mini plug connects to the recorder for on/off control. The recorder is controlled by a high-quality isolated-reed relay that will accommodate control currents up to 1 amp. An internal speaker is provided so that the unit can be left plugged in during normal use, yet switched off when silent recording is desired. Speaker-mode is controlled from the front panel, which also provides indicators for power and recording. The unit requires 115-volts AC at 4 watts maximum.


The *TAPE-SAVER TS-1* interface costs \$49.95.—**Electron Processing, Inc.**, Sales Dept., P.O. Box 708, Medford, NY 11763.

POWER-LINE MONITORS. *HMC's Model WD121 and WV120C* power-line monitors can save their users' time and money by revealing fluctuations in the line voltage that is



CIRCLE 15 ON FREE INFORMATION CARD

EXPAND YOUR CAREER HORIZONS...

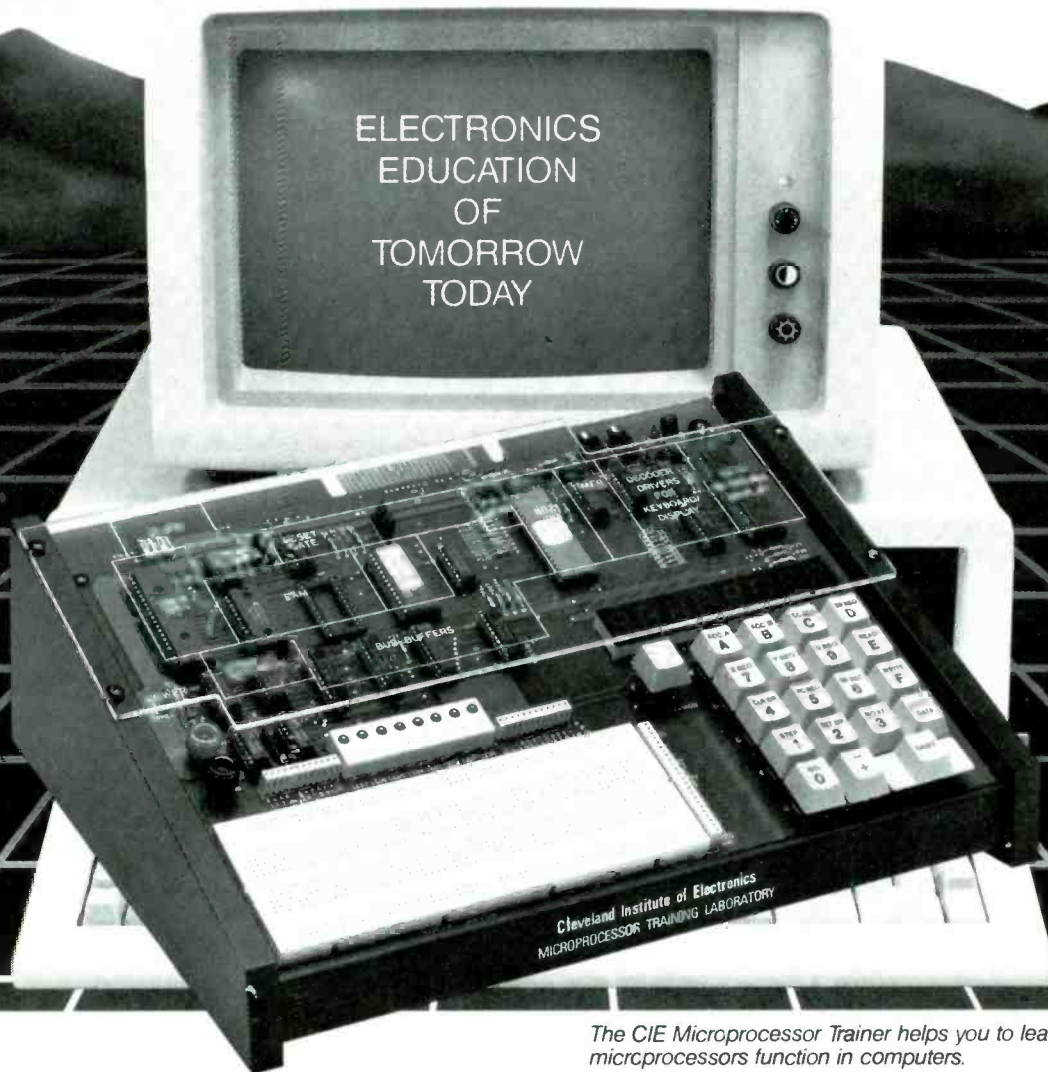

ELECTRONICS
EDUCATION
OF
TOMORROW
TODAY

Cleveland Institute of Electronics
MICROPROCESSOR TRAINING LABORATORY

The CIE Microprocessor Trainer helps you to learn how circuits with microprocessors function in computers.

START WITH CIE.

Microprocessor Technology. Satellite Communications. Robotics. Wherever you want to go in electronics... start first with CIE.

Why CIE? Because we're the leader in teaching electronics through independent study. Consider this. We teach over 25,000 students from all over the United States and in over 70 foreign countries. And we've been doing it for over 50 years, helping thousands of men and women get started in electronics careers.

We offer flexible training to meet your needs. You can start at the beginner level or, if you already know something about electronics, you may want to start at a higher level. But wherever you start, you can go as far as you like. You can even earn your Associate in Applied Science Degree in Electronics.

Let us get you started today. Just call toll-free 1-800-321-2155 (in Ohio, 1-800-362-2105) or mail in

CIRCLE 60 ON FREE INFORMATION CARD

the handy reply coupon or card below to:
Cleveland Institute of Electronics,
1776 East 17th Street, Cleveland, Ohio 44114.

CIE World Headquarters

Cleveland Institute of Electronics, Inc.
1776 East 17th Street • Cleveland, Ohio 44114

Please send your independent study catalog.
For your convenience, CIE will try to have a representative contact you — there is no obligation.

Print Name _____

Address _____ Apt. _____

City _____ State _____ Zip _____

Age _____ Area Code/Phone No. _____

Check box for G.I. Bill bulletin on Educational Benefits

Veteran Active Duty **MAIL TODAY!**

Just call toll-free 1-800-321-2155 (in Ohio, 1-800-362-2105)

ARE-104

DECEMBER 1988

31

Be an FCC LICENSED ELECTRONIC TECHNICIAN!



No costly School. No commuting to class. The Original Home-Study course prepares you for the "FCC Commercial Radiotelephone License". This valuable license is your "ticket" to thousands of exciting jobs in Communications. Radio-TV. Microwave. Computers. Radar. Avionics and more! You don't need a college degree to qualify, but you do need an FCC License. **No Need to Quit Your Job or Go To School** This proven course is easy, fast and low cost! **GUARANTEED PASS**— You get your FCC License or money refunded. **Send for FREE facts now. MAIL COUPON TODAY!**

COMMAND PRODUCTIONS

FCC LICENSE TRAINING, Dept. 90
P.O. Box 2824, San Francisco, CA 94126

Please rush **FREE** details immediately!

NAME _____
ADDRESS _____
CITY _____ STATE _____ ZIP _____


supplied to expensive electronic equipment and by warning of situations that could potentially cause damage.

Digital *Model WD121* features a high-accuracy, 3-digit, .8-inch LCD display. Analog *Model WV120C* features easy-to-read scales. The monitors can be used to monitor the power line only, or they can be installed between the AC line and equipment. Both models measure true-RMS AC voltage. The compact units weigh only 1.5 pounds, with its outside dimensions of 4 x 5 x 3 inches.

The digital unit, *Model WD121*, costs \$138.21; the analog *Model WV120C* costs \$95.36.—HMC, P.O. Box 526, Canton, MA 02021.

DESOLDERING BRAID. *Kwik-Wik* is a line of flux-impregnated copper braid for rapidly desoldering plated-through holes and DIP's. It quickly absorbs solder by capillary action, and eliminates the need for any kind of desoldering tools in many assembly and field-service applications.

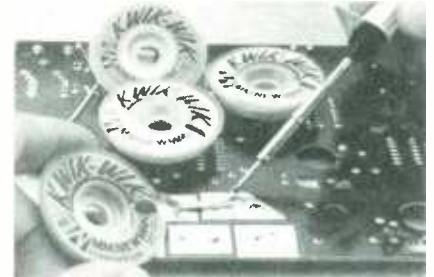
The copper braid is easy to use, by simply placing it on the joint being desoldered and holding the tip of a soldering iron against it. When the braid absorbs the solder



CIRCLE 16 ON FREE INFORMATION CARD

and turns silver it is then snipped off and thrown away.

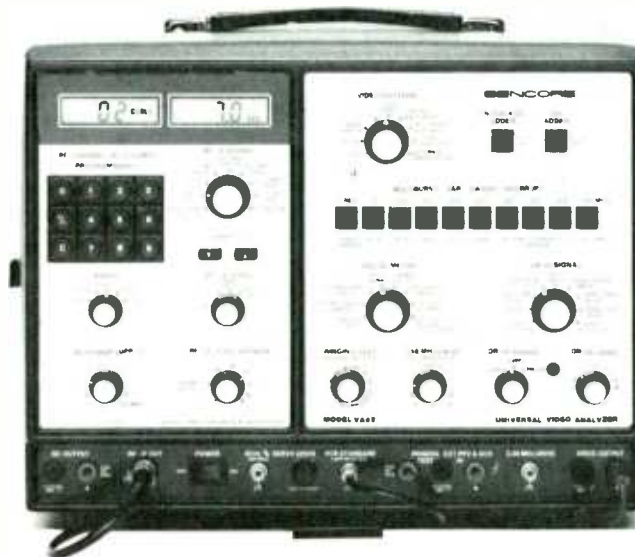Kwik-Wik is available in four sizes: Thin (.03 inch), small (.06 inch), medium (.08 inch), and wide (.10 inch), all on 5-foot spools. It is list priced from \$1.35 per spool in quantities of 11 to 99.—M.M. Newmann Corporation, 24 Tioga Way, P.O. Box 615, Marblehead, MA 01945.



Cut Your Video Servicing Time By 54%

With the Market Proven VA62 Universal Video Analyzing System.

Today's VCRs, TVs, and MTS Stereo TVs require a proven method to quickly isolate the defective component. New technology has made simple problem solving a time-consuming and expensive procedure.

A survey of over 1500 Video Analyzer owners has shown that the VA62's unique signal substitution method has reduced their video servicing time by an average of 54%, and increased their servicing profits.

You can join the successful service centers that have cut their video servicing time and increased their profits with the VA62 Universal Video Analyzing System. Call for a brochure on the VA62. Call **1-800-843-3338**, and increase your profits. In Canada Call **1-800-851-8866**.

SENCORE

3200 Sencore Drive, Sioux Falls, SD 57107

100% American Made

CIRCLE 186 ON FREE INFORMATION CARD

HARDWARE HACKER

Digital compass circuits
The Earth's magnetic field
Measuring magnetic fields
A low-end PostScript driver
Computer model prototypes

A solid-state digital compass

DON LANCASTER

DO YOU REMEMBER THE SANTA CLAUS machine that we looked at a few columns back? Well, it turns out that you can now buy them off the shelf from the *3-D Systems* folks.

The price (a house and two cars) may seem a tad on the steep side at first glance, until you allow for the obvious "Uh - compared to what?" factor. And then you see that it becomes a rather astounding bargain.

What it does is create a plastic prototype from a software data base by the selective laser hardening of a liquid plastic photopolymer. It is particularly good at machining the unmachinable, and can often do so in minutes rather than months.

There are quite a few new hacker opportunities here. One is to start up a prototype "service bureau," similar to the laser-printer rentals at quick-copy centers. Another is to come up with a super-cheap low-end Santa-Claus system that can, in fact, be built on a hacker budget.

Meanwhile, bunches of your helpline callers have been asking for "low-end" PostScript graphics and typesetting routines that will work on dot-matrix printers. Well, to do that would be the equivalent of trying to install a *Porsche* engine on a skateboard.

Nonetheless, *Lasergo* has freshly announced its brand new *Geoscript* software that does give you some PostScript abilities for the cheaper and older printers. Cost is in the \$200 range, and the software is primarily intended for IBM and its many clones.

Our feature distraction this

month involves a new solid-state digital compass. But first, let's take a quick look at . . .

Computer modeling

I must get a dozen calls a week from people that want to build some "simple" custom circuit that usually will involve a keyboard, a display, some I/O, and perhaps some storage. What I will usually do is tell them that the product already exists, that it costs around \$30, and that it is scunging away in their neighbor's driveway.

If you haven't guessed, it is called a *Commodore 64*, and thirty bucks is the typical yard-sale price.

In this day and age, if you are designing *any* circuit that involves more than four chips total, you will save an incredible amount of time, money, and frustration by modeling what it is that you think you want on a personal computer, doing as much as possible with the computer, and as little as possible with external custom hardware.

Even if your ultimate goal is to build and sell a brand new product, starting the project off with a computer model will nearly always get you a better product out the door much faster.

Why bother with a model? First

NEED HELP?

Phone or write your **Hardware Hacker** questions directly to:
Don Lancaster
Synergetics
Box 809
Thatcher, AZ 85552
(602) 428-4073

and foremost, software is far easier to change than hardware. Once you have something doing what you thought you wanted it to, there will be many obvious improvements and changes that will just be crying to be made.

And the chances these days are overwhelming that a RAM-ROM-CPU circuit will be cheaper, have fewer chips, and will end up far more buildable than would a traditional circuit built up out of a handful of CMOS or TTL chips.

Earth's magnetic field

There's an obscure electronics study area that is known as *magneto hydrodynamics*. Basically, if you have a moving and highly conductive pressurized gas or liquid, you can either generate an electrical current by applying a magnetic field, or else you can apply an electrical current and generate a magnetic field.

The liquid iron-nickel core of Earth does indeed qualify as a humongous magneto hydrodynamic generator.

As such, it generates a very large, but rather weak, magnetic field. And that is why compasses point to the north.

Well, sort of.

Actually, that north pole of Earth's electromagnetic field is only roughly at the real north pole, and it wanders around from time to time. It even flops over and reverses itself completely every few tens of thousands of years.

The deviation from true north is called the *magnetic declination*.

Here in Arizona, the magnetic declination is around 14 degrees

easterly. In Kansas, the declination is nearly zero, while on the East Coast, the declination is a few degrees westerly.

You can find the declination for your region from any USGS topographic map. To do that, you take the declination at the time the map was published and add the yearly drift rate to it, and multiply by the map's age. The drift rate is usually negligible, except possibly for the oldest of maps.

It is obviously very important to know whether you are using "true" or "magnetic" north, or very serious errors will result. Many better-grade compasses and survey instruments have adjustment screws that let you preset your declination.

It is also very important to keep your compass or whatever completely and totally level at all times. The magnetic field is also three dimensional. It points "straight up" at the far north, "horizontal" near the equator, and "straight down" near the south pole.

The vertical component of Ear-

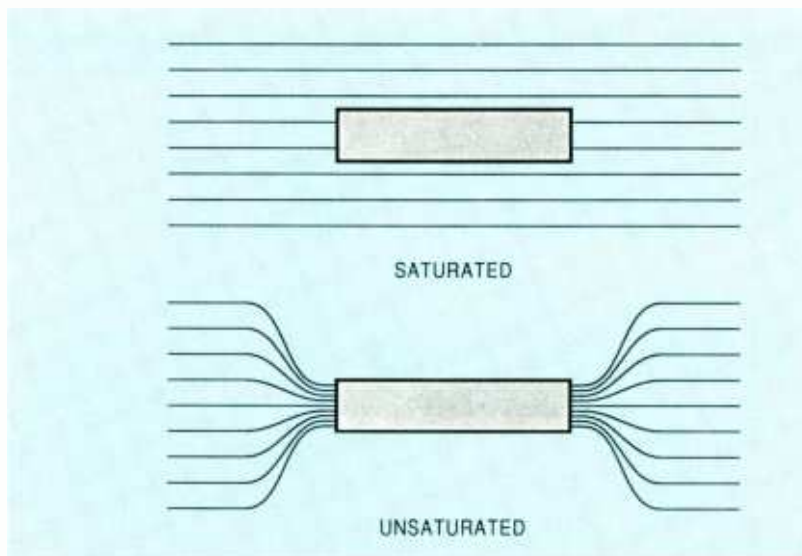


FIG. 1—AN UNSATURATED MAGNETIC MATERIAL will "pull in" the lines of force from Earth's or any other magnetic field. A saturated material will not.

th's field is called the *magnetic inclination*. One instrument to measure that is called a *dipping needle*.

If your compass or whatever is not completely level, then your reading will end up as mix of the horizontal and vertical field components, and will lie like a rug.

It gets nasty fast on an airplane that is not flying level. On a bank, you can get a severe *northerly turning error*. One cure is to use a "floating" compass on gyro that stays level when the plane banks.

Why would you want to hack Earth's magnetic field? Navigating, orienteering, and surveying are the three biggest reasons.

Not getting lost is another.

By carefully measuring the tiny variations over a very accurately gridded area, it is sometimes possible to map buried features such as archaeological sites, lava tubes, ore bodies, or even larger caves.

Further, there are two obscure but highly fascinating scientific fields that are known as *archaeomagnetism* and *paleomagnetism*. They study the history of the magnetic field's wandering, the first over thousands of years, and the second over hundreds of thousands. Accurate absolute dating is one application.

For instance, when a prehistoric fireplace is used, its temperature exceeds the *Curie* point of the magnetic materials in its rocks, and all of the old fields are erased, just like erasing a cassette tape.

As the fireplace cools, it takes an automatic snapshot of the inclination and declination of the field at that instant and preserves it.

By carefully measuring that magnetic snapshot, the last-use time of the fireplace can be accurately and absolutely dated. Even pots can be dated if you assume they were fired right-side up. And anything nearby can be relatively dated through guilt by association.

Similarly, the lava vents that cause sea floor spreading have a neat locked-in history of all the magnetic reversals that took place over time. That lets you accurately date all the extruded lava; and then you can measure the actual spread rate.

But, to hack any of that, we need some way of . . .

Measuring magnetic fields

The strength of Earth's field is roughly one *Gauss*. That is a rather weak field, and special tricks are required if you want to accurately measure it.

Obviously, a compass works like a champ. My favorite here is the good old *Brunton*, which is a cross between a high-end compass and a low-end survey instrument.

You can build your own compass by magnetizing a needle, sticking it through a cork and floating it in a cup of water. Ultra-cheap compasses are available by the bagful through *Edmund Scientific*.

Only there are problems. A compass will give you direction

**NEW FROM
DON LANCASTER**

HANDS-ON BOOKS

Hardware Hacker Reprints II	24.50
Ask The Guru Reprints	24.50
CMOS Cookbook	18.50
TTL Cookbook	16.50
Active Filter Cookbook	15.50
Micro Cookbook vol I or II	16.50
Enhancing your Apple I or II	15.50
AppleWriter Cookbook	19.50
Apple Assembly Cookbook	21.50
Incredible Secret Money Machine	10.50
PostScript Cookbook (Adobe)	16.50
PostScript Ref. Man. (Adobe)	22.50
PostScript Prog. Man (Adobe)	22.50

UNLOCKED SOFTWARE

PostScript Show & Tell (Ile/Mac/PC)	39.50
Intro to Postscript VHS Video	39.50
PostScript Perspective Draw	39.50
PostScript Printed Circuits	39.50
PostScript Technical Illustrations	39.50
Postscript BBS stuff	19.50
Absolute Reset Ile & Iic	19.50
AppleWriter/Laserwriter Utilities	49.50
Apple Ram Card Disassembly Script	24.50
Enhance I or II Companion Disk	19.50
AppleWriter CB or Assy CB Disk	24.50

FREE VOICE HELPLINE VISA/MC

SYNERGETICS
Box 809-RE
Thatcher, AZ 85552
(602) 428-4073

but it will not give you an amplitude. It is also a mechanical device subject to both settling and vibration. Worst of all, it has *damping* problems, as does any other moving mechanism.

The *Hall Effect* is one solid-state way of measuring magnetic fields. That effect will cause a transverse voltage output to be generated in response to an input current in certain solid-state materials. While Hall-Effect devices are low in cost and readily available, most of them are not nearly sensitive enough to use as a solid-state compass.

The *F.W. Bell* people do have some very large and very expensive Hall-Effect devices that do seem to have enough sensitivity, but something better is clearly needed.

Another candidate is known as a *proton precession magnetometer*.

What you do is take a baby bottle full of water and then wind a zillion turns of wire around it. You apply a strong current for a fraction of a second. The current aligns all of the deuterium atoms present in ordinary water into a fixed orientation.

When the current is released, Earth's weaker magnetic field will cause the deuterium atoms to *precess* like miniature gyroscopes.

The precession in turn induces an audio signal of a microvolt or so into the winding. The frequency of that fairly brief resultant signal is proportional to the strength of Earth's field.

One very big limitation to proton-precession magnetometers is that they only measure the total strength of the field, and not its direction. Another drawback is that you are working with extremely small, quite noisy, and rather brief signals.

It sure would be interesting to combine a modern digital signal-processing chip with some better-grade analog integrated circuits and see what could result.

The most practical way of solid-state sensing Earth's magnetic field is with a beastie called a *flux-gate magnetometer*.

Most magnetic materials have what is called a B-H magnetization curve. Up to a certain level, they behave linearly. Above a certain point, they will *saturate* and lose

NAMES AND NUMBERS	
<p>Assoc. of Energy Engineers 4025 Pleasantdale Rd, Suite 420 Atlanta, GA 30340 (404) 447-5083</p>	<p>Lasergo Inc 9235 Trade Place, Suite A San Diego, CA 92126 (619) 530-2400</p>
<p>Autohelm/Nautech Anchorage Park, Eastern Road Portsmouth, Hants PO3 5TD ENGLAND</p>	<p>NASA Langley Research Center Hampton, VA 23665 (804) 865-3281</p>
<p>F.W. Bell 6120 Hanging Moss Rd Orlando, FL 32807 (407) 678-6900</p>	<p>Precision Winding 109 South Knight Wichita, KS 67213 (316) 942-2811</p>
<p>Crystal Semiconductor Box 17847 Austin, TX 78760 (512) 445-7222</p>	<p>Silicon Systems 14351 Myford Road Tustin, CA 92680 (714) 731-7110</p>
<p>Edmund Scientific 101 E. Gloucester Pike Barrington, NJ 08007 (609) 573-6250</p>	<p>Siliconix 2201 Laurelwood Road Santa Clara, CA 95054 (408) 988-8000</p>
<p>Electronic Research P.O. Box 913 Shawnee, KS 66202 (913) 631-6700</p>	<p>Speleonics P.O. Box 5283 Bloomington, IN 47407 (812) 339-7305</p>
<p>Doug Garner NASA Langley, MS 471 Hampton, VA 23665 (804) 865-3506</p>	<p>3 D Systems 12847 Arroyo Street Sylmar, CA 91342 (818) 898-1533</p>
<p>KVH Industries 850 Aquidneck Avenue Middletown, RI 02840 (401) 847-3327</p>	<p>USGS Cartographic Info Box 25046, MS 510 Denver, CO 80225 (303) 236-5829</p>

all of their magnetic properties. What you have done is "filled" them with all the magnetic energy that they can possibly hold.

As Fig. 1 shows us, an ordinary magnetic material in its linear region will "pull in" magnetic lines of force, since the *permeability* of the material is greater than air.

Thus, a local distortion in Earth's magnetic field is created as the lines of force get "sucked in."

On the other hand, if you cause the magnetic material to saturate, there is no attraction or concentration of additional field lines, and Earth's field will ignore the material completely.

So, if you do switch, or *gate* a magnetic material into and out of saturation, you will also alternately concentrate and later ignore Earth's field. Should you now add a

new sense winding, current pulses will be induced into that winding every time Earth's field enters or leaves the material.

The strength of the pulses will be proportional to Earth's magnetic-field strength along the sensing axis.

The trick is to saturate and then unsaturate the fluxgate core without getting any of the drive current into the sense winding. Figure 2 shows us one possibility. A toroid of special magnetic material with a "square" B-H curve is used, along with a toroidal drive winding.

The sense winding is a linear overwrap of the toroid, going in one direction only.

With proper circuit design and a reasonable amount of luck, most of the drive current and its resultant saturating field will stay inside

the toroid and thus not be picked up by the sense winding.

Figure 3 shows us how a second quadrature sense winding can be added, giving us a sine and cosine output of the horizontal field component. We can now work with the ratio of those two signals and can often be more accurate.

Solid-state compasses

A fluxgate magnetometer seems to be the best approach today to building your own solid-state digital compass. Options include working direct or at the second harmonic of the drive frequency,

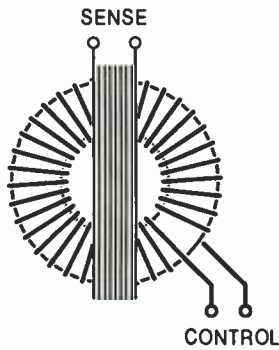


FIG. 2—A FLUXGATE magnetometer is built by using a control winding to alternately saturate and unsaturate a toroidal core. As Earth's magnetic field gets sucked into and out of the core, it induces pulses in the sense winding. All of the introduced pulses are proportional to the strength and the direction of Earth's magnetic field.

CORE: Magnetics 50086-2F
 CONTROL: 143 turns #30
 SENSE: 1000 turns #35

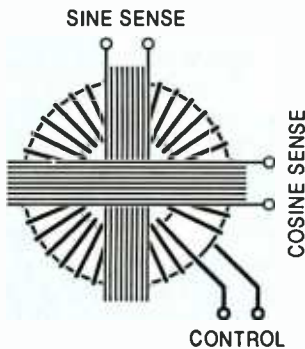


FIG. 3—ADDING A NEW quadrature sense winding will give you both the sine and cosine of the field strength. When one is weak, the other will be strong. The final magnetic bearing is found by dividing the sine output by the cosine output. A list of possible winding details are also shown.

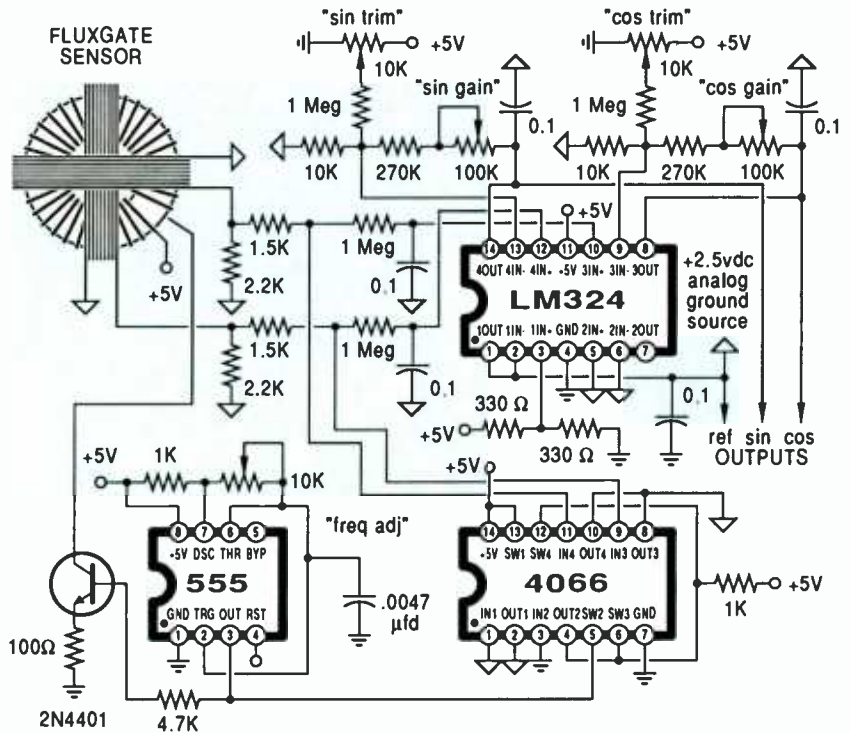


FIG. 4—A SIMPLIFIED SCHEMATIC of a solid-state digital compass. The outputs are A/D-converted and then routed to a microprocessor that handles the bearing calculations and a suitable digital display.

or of using a single or double quadrature sense winding, and of either working with nulls (by rotating the sensor) or by using absolute amplitudes.

In aircraft or radio-control model applications, one single fluxgate magnetometer can replace both the traditional compass and its backup gyro. At the same time, a compensation winding can be added so as to minimize any northerly turning-error problems.

That new approach to navigation is ridiculously cheaper and simpler than others. Figure 4 shows you the circuitry that is involved. What you have here on the driver is a 60-kHz square-wave generator that drives both the magnetometer and a pair of output-sensing gated half-wave demodulators and amplifying integrators.

The two quadrature DC-output signals are proportional to the sine and cosine of the amplitude of Earth's magnetic field. They can be routed through an A/D converter and sent to a microprocessor for further processing. Surprisingly, only a few hundred bytes of very simple code are needed to produce a complete digital compass.

One source of prewound and ready-to-use flux gate cores is *Precision Windings*. Circuit boards and complete kits are available from *Electronics Research*. Further info on licensing for resale or commercial use is available through *Doug Garner*.


For more details on building your own digital compass, see the NASA Tech Brief LAR-13560 on *An Improved Flux-Gate Magnetometer*, and *A Magnetic heading Reference for the Electro/Fluidic Autopilot* from the December 1981 and January 1982 issues of *Sport Aviation*. Updates to that earlier design are once again available through Doug Garner. Ask for the "Oshkosh 1987" and "Sensors Expo 1987" reprints.

Solid-state compasses are also becoming commercially available from other sources at reasonable prices. Do check out your boating-supply store for more details.

Those that I have looked at so far are British made and cost around \$90. Unfortunately, they are not quite accurate enough for cave surveying and they lack a built-in level and inclinometer.

continued on page 96

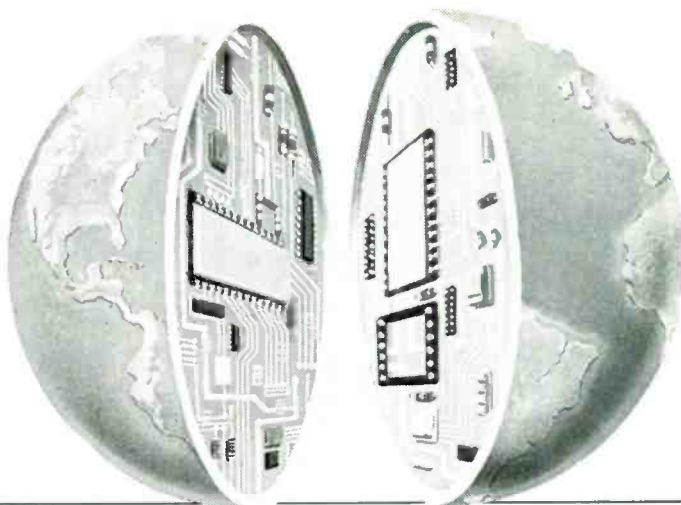WITH CIE, THE WORLD OF ELECTRONICS CAN BE YOUR WORLD, TOO.



Look at the world as it was 20 years ago and as it is today. Now, try to name another field that's grown faster in those 20 years than electronics. Everywhere you look, you'll find electronics in action. In industry, aerospace, business, medicine, science, government, communications—you name it. And as high technology grows, electronics will grow. Which means few other fields, if any, offer more career opportunities, more job security, more room for advancement—if you have the right skills.

SPECIALISTS NEED SPECIALIZED TRAINING.

It stands to reason that you learn anything best from a specialist, and CIE is the largest independent home study school specializing exclusively in electronics, with a record that speaks for itself. According to a recent survey, 92% of CIE graduates are employed in electronics or a closely related field. When you're investing your time and money, you deserve results like that.

INDEPENDENT STUDY BACKED BY PERSONAL ATTENTION.

We believe in independent study because it puts you in a classroom of one. So you can study where and when you want. At your pace, no somebody else's. And with over 50 years of experience, we've developed proven programs to give you the support

such study demands. Programs that give you the theory you need backed with practical experience using some of the most sophisticated electronics tools available anywhere, including our Microprocessor Training Laboratory with 4K of random access memory. Of course, if you ever have a question or problem, our instructors are only a phone call away.



START WHERE YOU WANT, GO AS FAR AS YOU WANT.

CIE's broad range of entry, intermediate, and advanced level courses in a variety of career areas gives you many options. Start with the Career Course that best suits your talents and interests and go as far as you want—all the way, if you wish, to your Associate in Applied Science Degree in Electronics Engineering Technology. But wherever you start, the time to start is **now**. Simply use the coupon below to send for your FREE CIE catalog and complete package of career information. Or phone us, toll-free, at **1-800-321-2155** (in Ohio, 1-800-523-9109). Don't wait, ask for your free catalog now. After all, there's a whole world of electronics out there waiting for you.

CIE

Cleveland Institute of Electronics, Inc.
1776 East 17th Street, Cleveland, Ohio 44114

Member NHSC
Accredited Member National Home Study Council

ARE-106

CIE **Cleveland Institute of Electronics, Inc.**
1776 East 17th Street, Cleveland, Ohio 44114

YES... I want to learn from the specialists in electronics—CIE. Please send me my FREE CIE school catalog, including details about CIE's Associate Degree program, plus my FREE package of home study information.

Name (print): _____

Address: _____

City: _____ State: _____ Zip: _____

Age: _____ Area Code/Phone No.: _____ / _____

Check box for G.I. Bill bulletin on educational benefits:

Veteran Active Duty

**MAIL
TODAY!**

CIRCLE 60 ON FREE INFORMATION CARD

www.americanradiohistory.com

SHORTWAVE RADIO

Radio Station WWV



STANLEY LEINWOLL,
CONTRIBUTING EDITOR

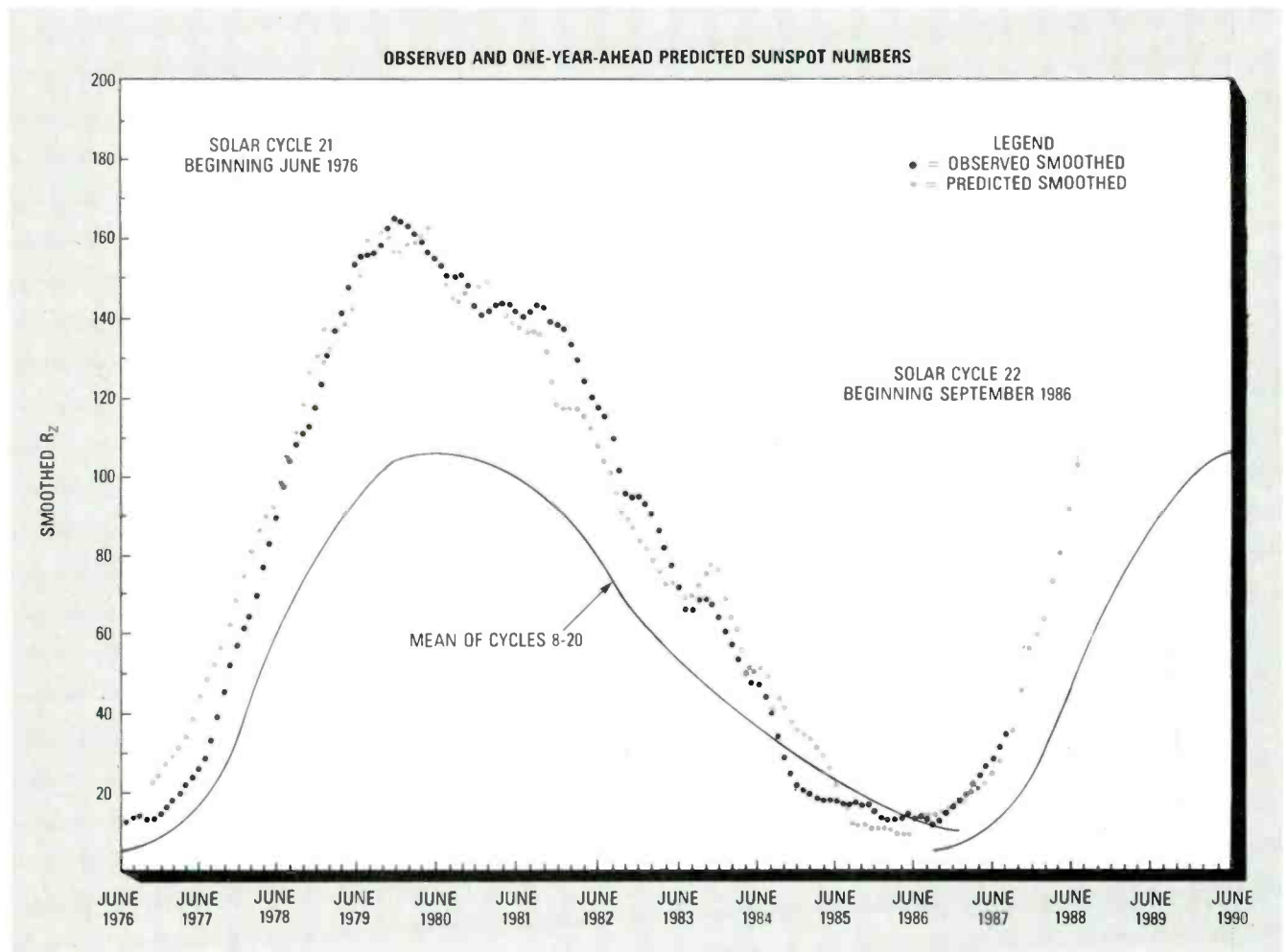


FIG. 1

THE FIRST MAJOR IONOSPHERIC STORM of the current sunspot cycle occurred last May, when a massive flare erupted on the sun, causing a virtual radio blackout throughout the world for several days.

During the early days of radio, before things like solar flares and geomagnetic storms were understood, many radio hobbyists took

their receivers apart during such radio storms looking for bugs that didn't exist, because they thought their receivers weren't working properly.

With increasing sunspot activity there will be more blackout-producing storms, caused by a growing number of solar flares. Before you dismantle *your* receiver, we

suggest you listen to WWV, the National Bureau of Standards time and frequency station, which broadcasts continuously on 2.5, 5, 10, 15, and 20 MHz. In addition to giving the correct time every minute, WWV also broadcasts hourly geophysical alerts that describe radio conditions during the previous 24 hours and give a forecast

Discover—Explore—Experience
Today's Electronics With ...

McGraw-Hill's Contemporary Electronics Series

Now you can meet the challenges of today's electronics quickly and easily. This professional level learning series is as innovative as the circuitry it explains and as fascinating as the experiments you build and explore! And it's for anyone who has an interest in electronics... from the hobbyist to the professional.

Thousands Have Already Experienced the Excitement!

Today's high-tech world demands an entirely new and innovative approach to understanding electronics. That's why McGraw-Hill has developed this unique "hands-on" learning method that brings to life the dynamics of the new electronics. It's a unique combination of interactive materials that gets you involved as you build and experiment with today's latest electronic circuitry.

Just how well this innovative learning approach meets the challenge of the new electronics is confirmed by those who have already completed the Series... "You have put me right into the middle of an extraordinary learning experience. With each lab exercise I have gained a new understanding of the intricacies of today's electronics." Or... "For me, the Series was just the answer. I felt confident within my specialty, but my grasp of other areas of electronics was slipping away. Your Series helped me upgrade my knowledge of the latest electronics concepts." Or this from a company director of training... "We manufacture sophisticated electronic products, with a lot of people in sales, assembly and purchasing. McGraw-Hill has answered a real need in helping our employees see the total picture. They now communicate with customers and each other more effectively."

Your Involvement in the New Electronics Begins Immediately.

You master one subject at a time with 15 McGraw-Hill *Concept Modules*, sent to you one

every 4 to 6 weeks. You waste no time on extraneous materials or outdated history. It's an entertaining, lively, nontraditional approach to the most modern of subject matter.

Your very first module takes you right to the heart of basic circuit concepts and gets you ready to use integrated circuits to build a digital oscillator. Then, you'll verify the operation of different electronic circuits using a light emitting diode (LED).

And each successive module brings you up to speed quickly, clarifying the latest advances in today's electronics... from digital logic and micro-processors to data communications, robotics, lasers, fiber optics, and more.

Unique Combination of Interactive Instruction Materials Makes Learning Easy.

Laboratory experiments, vividly illustrated text and interactive cassette tapes all blend together to give you a clear, simplified understanding of contemporary electronics.

With each module, you receive a McGraw-Hill *Action-Audio Cassette* that brings to life the facts and makes you feel as if you're participating in a lively dialogue with experts.

Your ability to quickly make this knowledge your own is further aided by strikingly *illustrated* texts that use diagrams, explanations, illustrations, and schematics to drive home and rein-

force the meaning of each important point. Carefully indexed binders conveniently house all this material, as well as the instructions that will guide you through your "hands-on" lab experiments.

Throughout your Series, *laboratory experiments* reinforce every significant concept. With this essential "hands-on" experience using actual electronic components, you master principles that apply all the way up to tomorrow's VLSI (Very Large Scale Integrated) circuitry.

Discover, Explore, Experience for Yourself—15-Day Trial.

In all ways, the Contemporary Electronics Series is an exciting learning experience that offers you the quickest and least expensive method available to master today's electronics... and the only one with "hands-on" experience.


To order your first module for a 15-day

trial examination, simply complete the card and send today! If the card is missing, write to us for ordering information.



McGraw-Hill
Continuing
Education Center

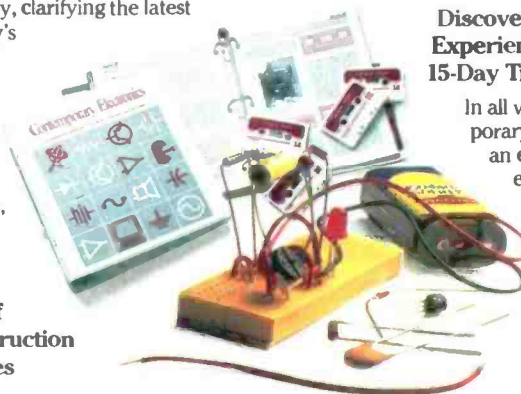3939 Wisconsin Avenue, NW
Washington, DC 20016



With your first module, you'll build this solderless breadboarding system. As you add additional boards, you create increasingly complex circuits easily and quickly, bringing today's electronics concepts to life.

ATTENTION! ELECTRONICS TECHNICIANS

EARN YOUR
**B.S.E.E.
DEGREE**

THROUGH HOME STUDY

Our New and Highly Effective Advanced-Placement Program for experienced Electronic Technicians grants credit for previous Schooling and Professional Experience, and can greatly reduce the time required to complete Program and reach graduation. No residence schooling required for qualified Electronic Technicians. Through this Special Program you can pull all of the loose ends of your electronics background together and earn your B.S.E.E. Degree. Upgrade your status and pay to the Engineering Level. Advance Rapidly! Many finish in 12 months or less. Students and graduates in all 50 States and throughout the World. Established Over 40 Years! Write for free Descriptive Literature.

COOK'S INSTITUTE
OF ELECTRONICS ENGINEERING

CI 4251 CYPRESS DRIVE
JACKSON, MISSISSIPPI 39212

CIRCLE 58 ON FREE INFORMATION CARD



for the following 24 hours. The messages are broadcast at 18-minutes past the hour, every hour, and are updated every three hours.

WWV and its sister stations, WWVB and WWVH, provide numerous other services, including standard time and frequency information, and marine storm warnings. National Bureau of Standards publication 432, entitled *Time and Frequency Dissemination Services*, can be obtained free of charge by writing Diana Gibson, Time and Frequency Division, National Bureau of Standards, Boulder, Colorado 80303.

General Conditions

With sunspot activity relatively high and increasing, daytime DX will be good to excellent, with the 15-, 17-, and 21-MHz bands providing numerous opportunities. The amateur 10-meter band will also open regularly. In addition, DX Citizens Band openings will become more frequent.

At night, conditions will be better than they were last winter,

when only the 6-MHz band was reliable for long periods. This year, the 9-MHz band will be useful for DX; even the 11- and 15-MHz bands will open over long circuits from southerly locations, such as Africa and Latin America.

Because noise levels due to thunderstorm activity are at a minimum in the northern hemisphere during the winter, broadcast-band DX will improve significantly during the hours of darkness.

We are currently in the 22nd recorded sunspot cycle. Based on the average of the first twenty-one sunspot cycles, the following is a general summary of sunspot cycle behavior:

- The average period of a sunspot cycle, from minimum to maximum and back to minimum is 10.7 years.
- The average period from the beginning of a cycle (minimum) to the maximum is about 4 years.
- The average period from the maximum to the minimum of a cycle is approximately 6.7 years.

Figure 1 is a composite drawing, courtesy of the Institute for Telecommunications Sciences, that shows the average of cycles 8-20 (the period during which accurate records have been kept). Superimposed on that, is the complete cycle 21, the last complete cycle we have had. It can be seen that cycle 21 was considerably above average. Its maximum, observed in December 1979, was the second highest ever observed, with a smoothed number of 165.

Sunspot numbers are smoothed because month-to-month averages can vary widely, and scientists have found that by smoothing sunspot numbers, a more accurate assessment of trends can be made. A smoothed number for a given month (R7) can be obtained using the following equation:

$R7 = (N1 + N2... + N7... + N13) / 13$
where N1-N13 are sunspot numbers for 13 consecutive months and R7 is the smoothed number centered on the seventh month of the sequence. It can be observed that a smoothed sunspot number can't be obtained until monthly numbers for six months afterward are available. Monthly numbers are obtained by averaging daily values during each month.

continued on page 95

SHORTWAVE RADIO BOOKS



Discover one of most incredible collections of electricity and electronics books to come along in years. You'll find scores of high quality new books and reprints of rare old books on building and collecting old time radios including spark-gap transmitters, crystal sets, regenerative and other antique receivers, early telephony and television, and more!

Tesla Coils!

Build Tesla coils, induction coils, Wimshurst and other lightning bolt generators! Rewind and repair motors! Design and build electrical generators! Get high power from auto alternators! You'll find quality books on these topics and much more!

RARE! BOOKS



Fringe Science!


You'll even discover a strange collection of books on "Fringe Science" - lost continents, perpetual motion, unusual phenomena recorded throughout the centuries, and much more. Explore the strange world that lies between fact and fiction!

Wide Variety!

You'll find plans and info on all types of unusual equipment from lasers to century-old induction coils! Build equipment your friends haven't even heard of!

Write for a catalog!

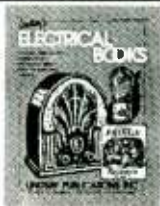Write for your copy of Lindsay's new Electrical Books catalog and see for yourself what you've been missing! Send \$1.00 (US & Canada) or \$3.00 foreign airmail. We'll send your catalog immediately! Write today!



Lindsay's Electrical Books

PO Box 12-WA2, Bradley IL 60915

Enclosed is \$1.00. Send me a copy of Lindsay's Electrical Books catalog via first class mail!

Name _____

Address _____

City _____ St _____ Zip _____

Radio-Electronics mini-ADS



2645T—117 PRACTICAL IC PROJECTS YOU CAN BUILD.....\$10.95. Dozens of fully-tested, ready-to-build circuits you can put together from readily-available, low cost IC's! There are a total of 117 IC circuits ranging from an audio mixer and a signal splitter to a tape-deck amplifier and a top-octave generator organ! From TAB Books. To order your copy send \$10.95 plus \$2.75 shipping to Electronic Technology Today Inc., P.O. Box 240, Massapequa Park, NY 11762-0240




ZENITH SSAVI UHF input from \$169, ch. 3 input \$229, reconditioned. UHF SSAVI hand-book \$6.50 ppd. Used Sylvania 4040 w/remote \$169. New N-12-VS \$99, ch 2 or 3. MLD-1200s ch 2 or 3. Converters & accessories. Satellite systems. New Panasonic 2, 3, 6 or 12 line/8 to 32 extension telephone systems. Systems with key phones: two lines from \$675; three lines from \$1149. catalog \$1. AIS SATELLITE, INC., 106 N. 7th St./D, Perkasia, PA 18944. 215-453-1400.

CIRCLE 192 ON FREE INFORMATION CARD



THE MODEL WTT-20 IS ONLY THE SIZE OF A DIME, yet transmits both sides of a telephone conversation to any FM radio with crystal clarity. Telephone line powered - never needs a battery! Up to ¼ mile range. Adjustable from 70-130 MHZ. Complete kit \$29.95 + \$1.50 S + H. Free Shipping on 2 or more! COD add \$4. Call or send VISA, MC, MO. DECO INDUSTRIES, Box 607, Bedford Hills, NY 10507. (914) 232-3878.

CIRCLE 127 ON FREE INFORMATION CARD

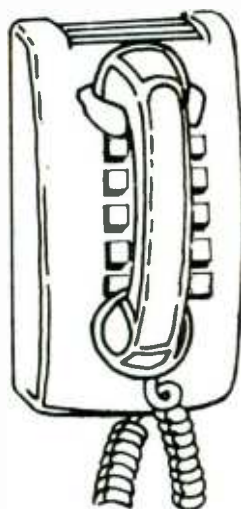

CALL NOW AND RESERVE YOUR SPACE

- 6 x rate \$890.00 per each insertion.
- Fast reader service cycle.
- Short lead time for the placement of ads.
- We typeset and layout the ad at no additional charge.

Call 516-293-3000 to reserve space. Ask for Arline Fishman. Limited number of pages available. Mail materials to: mini-ADS, RADIO-ELECTRONICS, 500-B Bi-County Blvd., Farmingdale, NY 11735.




PANASONIC CABLE CONVERTERS, Wholesale and Retail. Scientific Atlanta and Pioneer Cable Converters in stock. Panasonic model 140N 68 channel converter \$79.95, Panasonic Amplified Video Control Switch Model VCS-1 \$59.95. Scientific Atlanta Brand new Model #8528 550MHZ 80 Channels Converter \$89.95. Video Corrector (MACRO, COPYGUARD, DIGITAL) ENHANCER \$89.95. We ship to Puerto Rico, Caribbean countries, & So. Amer. Write or call BLUE STAR IND., 4712 AVE. N, Dept 105, Brooklyn, NY 11234. Phone (718) 258-9495.

CIRCLE 85 ON FREE INFORMATION CARD



RADAR SPEED SYSTEMS & GUNS. Professional X and K band police models for clocking speeds in car & boat racing, skiing, baseball, etc. Starting at \$269 used, \$350 reconditioned. Moving and stationary units available with dual displays. All units are road tested and have a 30-day warranty. We carry a complete line of TV accessories and Panasonic multi-line business telephone systems. Catalog \$1. AIS SATELLITE, INC., 106 N. 7th St./C, Perkasia, PA 18944. 215-453-1400.

CIRCLE 81 ON FREE INFORMATION CARD

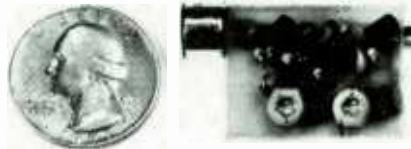

SIMPLY SNAP THE WAT-50 MINIATURE FM TRANSMITTER on top of a 9v battery and hear every sound in an entire house up to 1 mile away! Adjustable from 70-130 MHZ. Use with any FM radio. Complete kit \$29.95 + \$1.50 S + H. Free shipping on 2 or more! COD add \$4. Call or send VISA, MC, MO. DECO INDUSTRIES, Box 607, Bedford Hills, NY 10507. (914) 232-3878.

CIRCLE 127 ON FREE INFORMATION CARD



PROFESSIONAL VIDEO new exclusive color video correlator with unique super comb filter. Allows you to reposition color back inside its boundaries due to poor quality broadcasts and tapes. Restores edge sharpness to near rgb look with reduction of background noise. Black pedestal level set a must for big screens. S-VHS and ED-BETA supported. PR/4 \$299.95 others from \$139.95 DX-TELE-LABS 6601 E. Clinton St. Scottsdale AZ. 85254 (602)998-3966


CIRCLE 194 ON FREE INFORMATION CARD

Cable Checklist

ENJOY CABLE TV MORE THAN EVER



SNOOPER STOPPER/DATA BLOCKER \$39⁹⁵

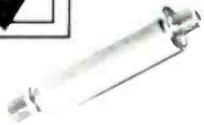

- Prevent cable companies from spying on you to see how many cable converters you have
 - Removes beeping sound from your FM when radio is connected to cable TV
 - Cable TV descramblers are being sold by the thousands, but few people know descramblers can be detected on most addressable systems
- Maintain your privacy with a Snooper Stopper. For more detailed information, send \$2.00 for our "Cable TV Snooper Stopper" article.



MACROVISION... NOW YOU SEE IT, NOW YOU DON'T

MS1-KIT \$29⁹⁵

Includes all the parts, pc board, AC adaptor, and instructions from a published construction article in *Radio Electronics* magazine.



- Remove copy-protection from video cassettes
- Digital filter type; removes only Macrovision pulses

JMAK-4 BLACK BOX \$14⁹⁵

Original box as shown in ad with two feet and four holes to mount pc board.

- No adjustments; crystal controlled
- Compatible with all VCRs
- Uses automatic vertical blanking level
- Assembles in less than three hours

Note: Unauthorized duplication of copyrighted materials is illegal. Use Macro-Scrubber for viewing only.



SIGNAL ELIMINATOR \$29⁹⁵




- Works on cable or broadcast TV
- External adjustments allow precise tuning to any frequency
- Model 26 - Tuneable to channels 2-6 (54-108 Mhz)
- Model 713 - Tuneable to channels 7-13 (174-216 Mhz)
- Model 1422 - Tuneable to channels 14-22 (120-174 Mhz)

ELIMINATE a Channel

that you find unsuitable for family viewing, but is poorly scrambled by your cable company. **OR**

CLEAR UP a Channel

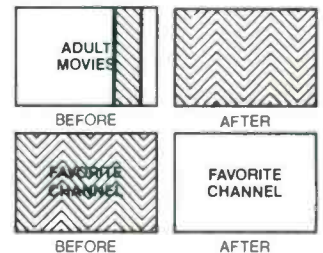
that presently contains severe interference by ELIMINATING whatever signal is causing this.



Note: If picture and sound are equally affected, this IS interference and CAN be removed by our product. If only picture is affected, this usually IS NOT interference and CANNOT be removed by our product.



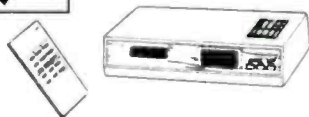72 Channel CABLE CONVERTER with Infra-Red Remote \$79⁹⁵



- Microprocessor controlled PLL operation
- Skip channel memory eliminates unused channels
- Parental control for all channels
- Compatible with all external descramblers
- Last channel recall
- Fine tune memory
- UL listed/FCC approved
- Simple installation with any TV
- Includes battery and 3 foot coax
- Channel output 2 or 3 switchable

Add \$3.50 shipping & handling
\$9.50 Canadian orders

ORDER TOLL FREE ANYTIME 1-800-227-8529

Inside MA: 508-695-8699 Fax: 508-695-9694
Ask for additional free information
Add \$3.00 shipping & handling on all orders unless otherwise noted. \$6.00 Canadian orders.
Visa, MasterCard, or C.O.D.



J & W ELECTRONICS, INC.

P.O. BOX 800 • MANSFIELD, MA 02048

CIRCLE 65 ON FREE INFORMATION CARD

TECHNOLOGY

BRIAN C. FENTON, EDITOR

TELEVISION HAS CHANGED QUITE A BIT since its invention. Compatible color and stereo audio were hailed as major advances that changed the way we look at and listen to TV. Some claim that HDTV will be the next breakthrough. We're looking forward to HDTV, too; but *nothing* promises to be as exciting—and have as much of a sociological impact—as a practical interactive TV system.

We've all had the experience of watching a TV game show and knowing the answer long before any of the contestants—and, we think, before anyone else in the viewing audience. Other than pounding the coffee table, there's not much you can do in such a situation. But next year, if the people at the Interactive Game Network (IGN) have their way, that may change drastically.

Imagine being able to play your favorite game against the contestants, and all other viewers, in real time. The system proposed by IGN would let you prove to the nation that you knew the answer first. And it would open up a whole world of other possibilities, too, including electronic opinion polling, lottery playing, TV auctions, and more.

What is Interactive TV?

The idea of interactive TV is not new. Two-way TV that lets the viewer play an active role has been talked about for years, and it's even been tried before. One of the better known two-way systems was QUBE, an interactive cable system developed by Warner-Amex Cable for distribution in Columbus, Ohio. QUBE was successful in securing more than 300,000 subscribers, but in a 1984 cost-cutting move Warner Communications canceled QUBE's operation.

QUBE failed because the revenues generated did not justify its development costs, or the expenses incurred in laying the two-way cable and obtaining the head-end equipment. IGN's proposed system is significantly different from two-way cable systems. It promises to bring interactivity to *everyone* because its required infrastructure is already in place. IGN's system does not involve any



INTERACTIVE TV

Interactive TV turns armchair spectators into active participants.

new technology nor does it require the development of new equipment. Instead, it is a new combination of the existing technology of computers, FM subcarriers, and TV. It doesn't even require any change in FCC regulations! We're confident that the only things standing in the way of your having interactive TV in your living room are contracts with program suppliers and a massive advertising campaign.

Before we get into the technical details of the system, we should take a realistic look at where the system will go. As of press time (mid September), the system's introduction is *planned*

for August 1989.

NBC is participating with IGN in a joint development agreement to devise interactive sports and game shows. Since NBC owns the rights to the daytime version of *Wheel of Fortune*, we would expect an interactive version of that most popular game show to be among the first.

The major sports leagues have also expressed an interest in working with IGN to develop interactive contests around their televised sports. An "armchair quarterback" game, where viewers try to predict the next play would likely be the first game of that genre.

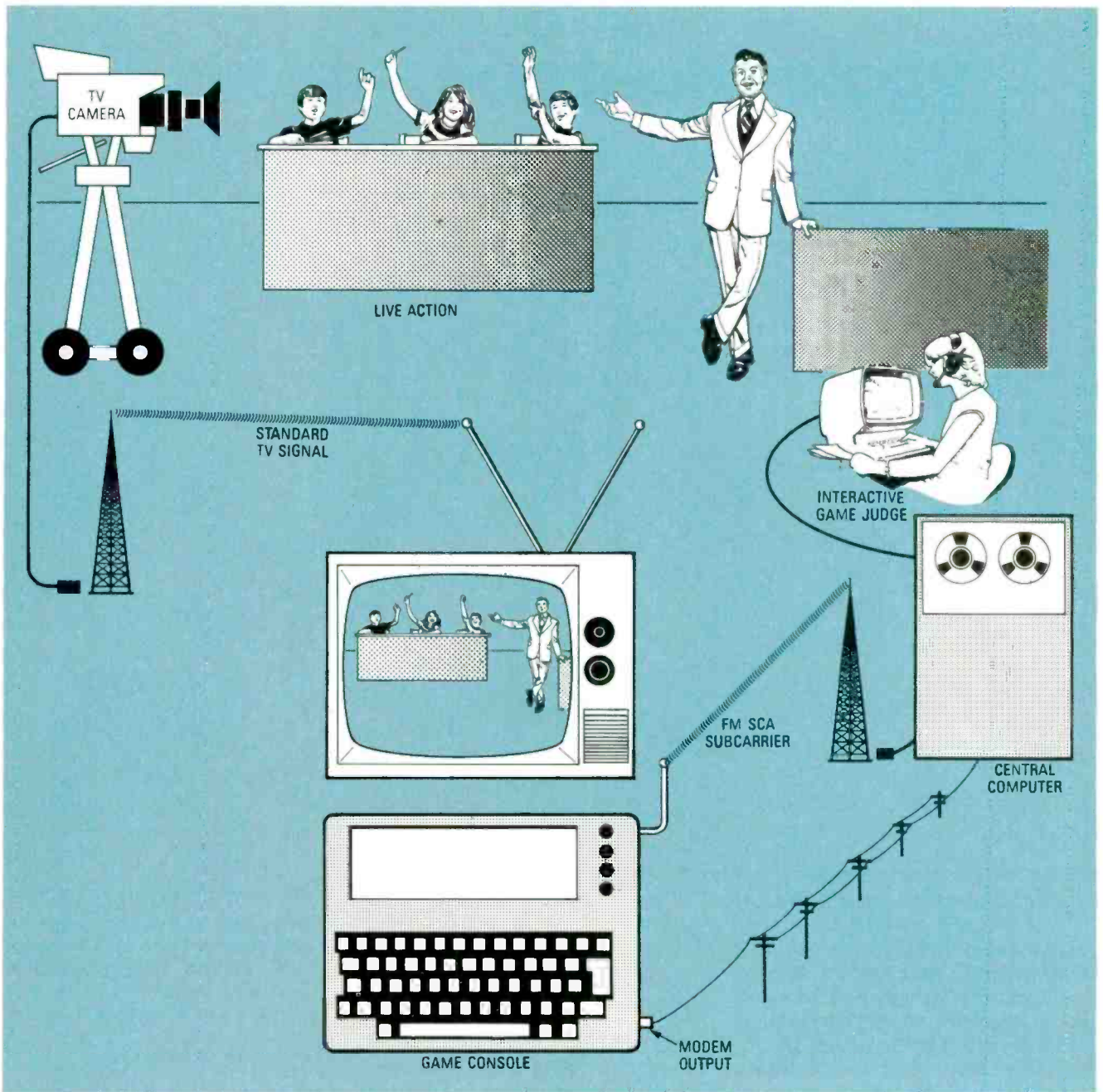


FIG. 1—INTERACTIVE GAME NETWORK'S system consists of a standard TV broadcast coupled with an FM SCA subcarrier transmission. The game consoles receive the questions from the subcarrier, along with the correct answers and a difficulty multiplier. After the game is over, the home player calls the central computer to upload his score. Winners are notified by the subcarrier transmissions.

Figure 1 shows the basic idea of how IGN's interactive TV system works. An event, such as a quiz game, is televised as it is normally. Viewers who are not interactive players enjoy TV normally. However, those who are equipped with an interactive game console receive—via an FM SCA subcarrier—instructions on how to play the game interactively.

When quiz questions are asked, the home game players have an oppor-

tunity to answer the question. In a fast-moving game such as *Jeopardy*, the home game player sees multiple-choice answers on the screen that require only a single keystroke to answer. A slower-moving game, such as *Wheel of Fortune*, requires the player to type in the full answer.

In either case, once the question is answered correctly on TV, a lockout signal is sent via the FM SCA subcarrier to prevent the console from accepting any more answers.

The use of an SCA subcarrier is essential to IGN's system. It's no coincidence that IGN's president, who holds the patent for the interactive system, is David Lockton, the founder of Dataspeed. That company pioneered the use of FM subcarriers to transmit stock quotes around the country.

Of course, not everyone in the U.S. lives within the range of an FM station that will carry IGN's data on a subcarrier. At the outset, FM stations in the top 25 markets will carry IGN's data subcarrier, leaving about 35 percent of the population out of range. Those people have no reason to de-

spair, however. The same information as is transmitted on the subcarrier will be carried on the VBI (Vertical Blanking Interval) of PBS TV stations. An adapter box, tuned to the local PBS station, will translate the data from the VBI to an FM signal, and send it to the game console using a low-power FCC type-approved transmitter.

The game console

As far as the home game player is concerned, the game console is the most important part of the system. Although the console's exact design hasn't been chosen, it will probably look much like a lap-top computer, with a full-size keyboard and a multi-line LCD display. As we mentioned previously, not all games require a full keyboard. Many games can make use of *soft keys*, which are placed along the display and take on the meaning assigned by the display.

The game console features a built-in SCA receiver and a telephone modem. Its block diagram is shown in Fig. 2. We'll continue with our game-show scenario as we discuss its operation.

The heart of the game console is a microprocessor that accepts data from an FM SCA subcarrier and also from keyboard inputs. It presents appropriate information on its display. Say, for example, a game-show question asks for the proper capital of the United States. Assuming that the game show receives rapid-fire answers from its contestants, the display would show four choices alongside four soft keys.

The interactive game judge assigns a *degree of difficulty* multiplier to the question that allows for more difficult question to be worth more. For example, a question that asks for the capital of the republic of Lithuania might be worth three times as much as the previous one. The game console receives, along with the question, the correct answer on the FM subcarrier. If your answer matches, your score is increased, and added to the score stored in your console's memory.

Along with questions, answers, and lock-out signals, the game judge (or, to be more precise, the central computer) also sends random counter-start signals. When those signals are received by the microprocessor, the current time from the microprocessor's real-time clock is transferred to one of ten counters, and a

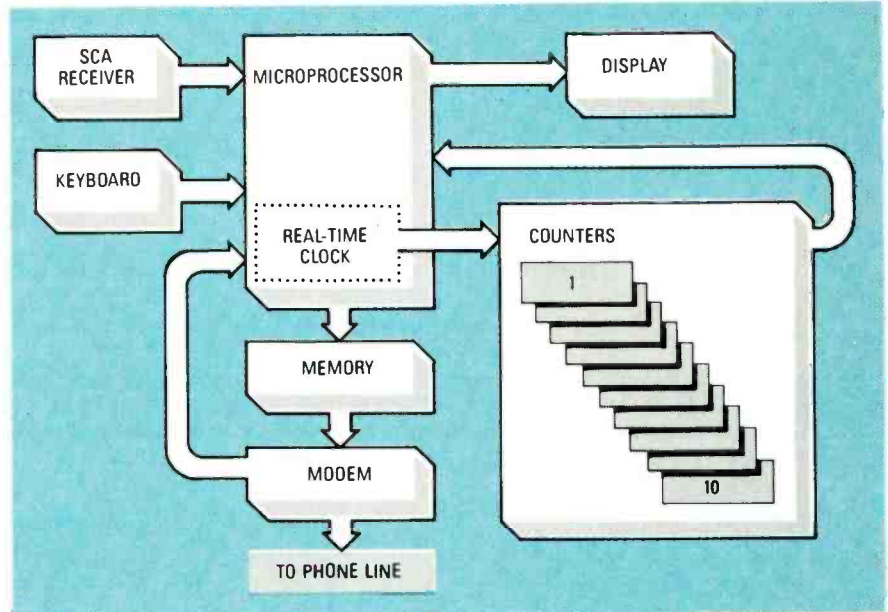


FIG. 2—THE GAME CONSOLE'S HEART is a microprocessor that receives data and time stamps from digital data in an FM subcarrier, and inputs from the keyboard. The time stamps are stored in incrementing counters that are used for verification purposes.

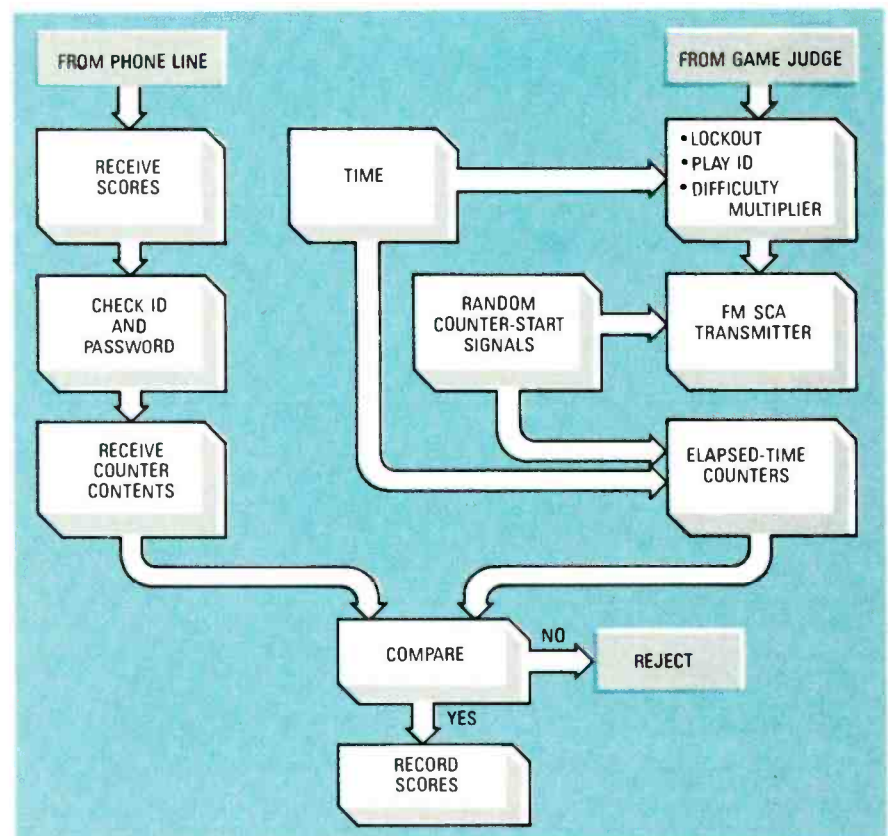


FIG. 3—THE CENTRAL COMPUTER controls the subcarrier transmissions based on inputs received from the game judge. It also generates random time stamps to start the game consoles' counters. Finally, it receives scores from game players, computes their standings, and transmits the results over an FM SCA subcarrier.

count-up operation begins in that counter. That time-stamping operation is very important—it is the main anti-cheating safeguard.

Once the game ends, you can up-

load your score to the central computer, where it is compared against all other players'. The upload process is nothing like what you may be used

continued on page 106

HITACHI SCOPES AT DISCOUNT PRICES



V-212
\$379
List \$560
Save \$181

20MHz Dual Trace Oscilloscope

All Hitachi scopes include probes, schematics and Hitachi's 3 year warranty on parts and labor. Many accessories available for all scopes.



V-425
List \$995 **\$835**

- DC to 40MHz
- Dual Channel
- CRT Readout
- Cursor Meas
- DC Offset
- Alt Magnifier
- Compact Size




V-1060
List \$1595 **\$1,285**

- DC to 100MHz
- Dual Channel
- Delayed Sweep
- CRT Readout
- Sweep Time
- Autoranging
- Trigger Lock
- 2mV Sensitivity

	LIST	PRICE	SAVE
V-223 20MHz	\$770	\$695	\$75
V-422 40MHz	\$875	\$695	\$180
V-423 40MHz	\$955	\$795	\$160
V-660 60MHz	\$1,195	\$990	\$205
V-1065 100MHz	\$1,895	\$1,575	\$320
V-1100A 100MHz	\$2,295	\$1,995	\$300
V-1150 150MHz	\$3,100	\$2,565	\$535

ELENCO PRODUCTS AT DISCOUNT PRICES

20MHz Dual Trace Oscilloscope

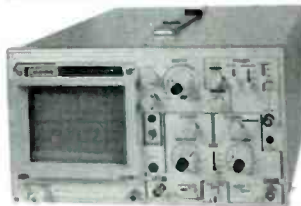

\$349
MO-1251

- 6" CRT
- Built in component tester
- TV Sync

SCOPE PROBES

P-1 65MHz, 1x, 10x	\$19.95
P-2 100MHz, 1x, 10x	\$23.95

with 5 accessories
10 Meg ohm input impedance
Fits all scopes with BNC connector
TL-3 BNC to Minigrabber \$3.49

35MHz Dual Trace Oscilloscope



\$498
MO-1252

- High Luminance 6" CRT
- 1mV Sensitivity
- 6KV Acceleration Voltage
- 10ns Rise Time
- X-Y Operation • Z Axis
- Delayed Triggering Sweep

Top quality scopes at a very reasonable price. Contains all desired features. Two 1x, 10x probes, diagrams and manual. Two year guarantee.

NEW! Autoranging DMM



M-5000
\$45

- 9 Functions
- Memory and Data hold
- 1/2 % basic acc
- 3 1/2 digit LCD



True RMS 4 1/2 Digit Multimeter
M-7000
\$135

- .05% DC Accuracy
- .1% Resistance
- with Freq. Counter and deluxe case



Multimeter with Capacitance and Transistor Tester
CM-1500A
\$55

- Reads Volts, Ohms, Current, Capacitors, Transistors and Diodes with case

Digital Capacitance Meter



CM-1550
\$58.95

- 9 Ranges
- .1pf-20,000ufd
- .5% basic accy
- Zero control with case

Digital LCR Meter



LC-1800
\$138

- Measures Coils 1uH-200H
- Caps .1pf-200uf
- Res .01-20M

NEW! AC Clamp-On Current Adapter



ST-265
\$22

- 0-1000A AC
- Works with most DMM

NEW! Bench DMMS



M-3500
3 1/2 digit
1% accy

M-4500
4 1/2 digit
.05% accy

\$125

\$175

50MHz Logic Probe



LP-700
\$23

Logic Pulsar LP-600 \$23

Solderless Breadboards



- 9430 1,100 pins \$15
- 9434 2,170 pins \$25
- 9436 2,860 pins \$35
- All have color coded posts

9436 SHOWN

Low Cost Multimeter



M-1600
\$25

- 3 1/2 digit LCD
- 1% DC Accy
- 10A Scale
- Auto zero
- polarity

NEW! Wide Band Signal Generators



SG-9000
\$119
RF Freq 100K-450MHz
AM Modulation of 1KHz
Variable RF output

SG-9500 with Digital Display and 150MHz built-in Freq Ctr \$249

3 1/2 Digit Probe Type DMM



M-1900
\$45

- Convenient one hand operation
- Measures DCV, ACV, Ohms
- Audible continuity check, Data hold
- with batteries and case

GF-8016 Function Generator with Freq. Counter



\$239

- Sine, Square, Triangle Pulse, Ramp, 2 to 2MHz
- Freq Counter .1 - 10MHz

GF-8015 without Freq. Meter \$179

Digital Triple Power Supply



XP-765
\$249

- 0-20V at 1A
- 0-20V at 1A
- 5V at 5A

Fully Regulated, Short circuit protected with 2 Limit Cont., 3 Separate supplies

XP-660 with Analog Meters \$175

Quad Power Supply



XP-580
\$59.95

Fully regulated and short circuit protected

- 2-20V at 2A
- 12V at 1A
- 5V at 3A
- 5V at 5A

XP-575 without meters \$44.95

Four-Function Frequency Counters



F-1000 1.2GH
\$259

F-100 120MH
\$179

Frequency, Period, Totalize, Self Check with High Stabilized Crystal Oven Oscillator, 8 digit LED display

NEW!

"GREAT IDEA" FUNCTION BLOX FOR EASY BREADBOARDING

All blox interlock to make your design work a snap. You can change the configuration

9550 7.50
550 tie pts



9600
FUNCTION GENERATOR
1 to 1MHz sine, sq wave




9610
RESISTOR DECADE BLOX
20 resistors 47-1M ohm



9620
CAPACITOR DECADE BLOX
20 capacitors 47pf-10mfd



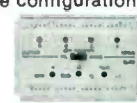9630
DIGITAL CLOCK BLOX
pulses from 1Hz to 50MHz



9640
LOGIC PROBE BLOX
4 logic level ind.



9650
POWER BLOX
5V at 1A - 5 at .4A
12V at .3A



WE WILL NOT BE UNDERSOLD!
UPS Shipping: US 5%
(\$10 Max) IL Res., 7% Tax

C & S SALES INC.
1245 Rosewood, Deerfield, IL 60015
(800) 292-7711 (312) 541-0710

15 Day Money Back Guarantee
2 Year Warranty
WRITE FOR FREE CATALOG


CIRCLE 109 ON FREE INFORMATION CARD

GATED-SYNC DESCRAMBLER

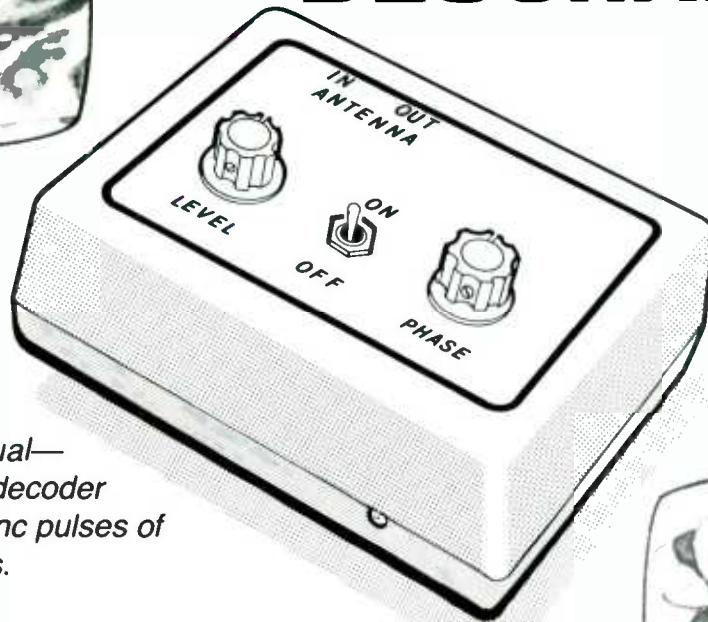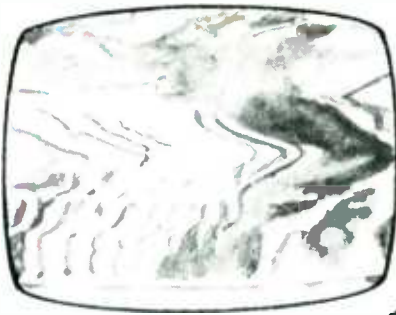

This somewhat unusual—but easily installed—decoder restores the gated sync pulses of scrambled TV signals.

STEVE PENCE

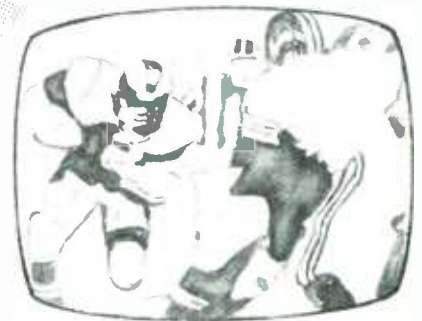

OF THE MANY METHODS USED TO SCRAMBLE a video signal for secure transmission, one of the more popular ones is called *Gated Pulse* or *Gated Sync*. The scrambling is accomplished by applying 6-dB suppression to the video signal's horizontal sync pulses thereby making it impossible for a television set to maintain a synchronized picture on the screen.

Figure 1 shows how gated sync works. Figure 1-a shows a conventional video signal with normal horizontal sync pulses. Notice the colorburst riding on the *back porch* of

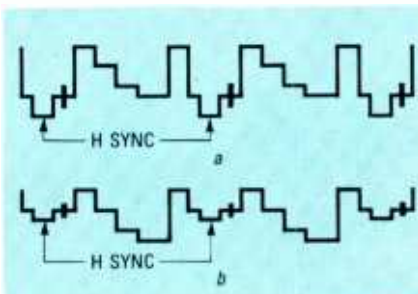


FIG. 1—A CONVENTIONAL TV signal is shown in a. With suppressed sync the signal resembles b.

the horizontal blanking pulse. Figure 1-b shows the same signal with the horizontal sync pulse suppressed 6 dB. Notice that in Fig. 1-b the horizontal sync pulse and its blanking pulse, and the colorburst are all within the video-signal level.

YOU MUST PAY

Please note that the gated-pulse decoder is intended only for those who presently subscribe to a scrambled cable service and are dissatisfied with the picture quality attained from the supplied decoder, or who want to experiment with various decoding devices. If you are not presently a subscriber but want to view scrambled programs using our decoder, you must make subscriber arrangements with the originating program service.

The subscriber arrangement is necessary because the unauthorized reception of cable services is illegal under Federal and State laws.

Federal law renders illegal both the interception and reception of any communications service offered over a cable system, unless those actions have been specifically authorized by the cable operator or by law. Federal law imposes both civil and criminal penalties for violation of the applicable statutes. In addition, states have enacted "theft of cable services" statutes that impose penalties for violations thereof.

The foregoing is not intended to constitute legal advice. Readers are advised to obtain independent advice based upon their individual circumstances and jurisdictions.

Although the gated-sync scrambling technique is basic and straightforward, its exact implementation can vary greatly from one equipment manufacturer to another; which means that each system needs its own particular kind of decoder to regain

the original programming. As a general rule, the variations used to customize gated-sync scrambling usually involve a reference signal of some kind that is either multiplexed onto the audio carrier in some fashion, or onto some kind of outband carrier on an empty channel.

But if we can get around the "misplaced" reference signal, a simple gated-sync decoder is all that's necessary to decode nearly any single-level gated-pulse signal. And that's exactly what our decoder does. It eliminates the need for a reference signal, so it doesn't matter where the scrambling system hides the reference.

As you'll see, our decoder requires no special set-up equipment, although a scope does simplify setting up. Best of all, there's no intricate RF alignment because no RF tuned circuits are used in the decoder.

Pluses and minuses

As with any other decoder, ours has both advantages and disadvantages. Its advantages include: versatility—it

will work on nearly any single-level sync-suppression system and does not need a reference signal to operate; no demodulation of any kind; a simplified circuit design that uses low-cost, readily available parts.

The disadvantages are that the device must be used with a television set—a VCR by itself will not do. The television set must be tuned to the channel that is being decoded, and phase-lock is not automatic—it must be done manually each time the decoder is turned on or when the channel is changed. Also, the decoder will not work on tri-mode systems or any other system that uses more than one level of sync suppression, or on any system that suppresses the vertical sync pulse. Also, the decoder will operate only in the low VHF band; hence it must be used with a cable downconverter that outputs on channels 2, 3, or 4.

How it works

As shown in Fig. 2—a functional block diagram of the decoder and

some of a TV set's circuits—the basic principle used in the gated-sync decoder is that of a phase-locked loop. The loop, which is indicated by the bold lines, is formed by the TV set's sync separator, horizontal AFC circuit, horizontal oscillator and output, and the high-voltage flyback transformer. When all of that circuitry is being fed normal video (containing sync pulses), the loop is closed by taking a pulse from a winding on the flyback transformer and feeding it back to the AFC circuit, where the flyback's pulses and the sync pulses are compared. If they are not in phase, an error voltage is generated that forces the horizontal oscillator to change frequency until the two signals are finally in phase and the picture locks.

If the sync pulses are suppressed, as they are in a gated-sync system, the AFC loop has been opened because the pulses from the flyback transformer have nothing to be compared with; so the horizontal oscillator runs free (unsynchronized).

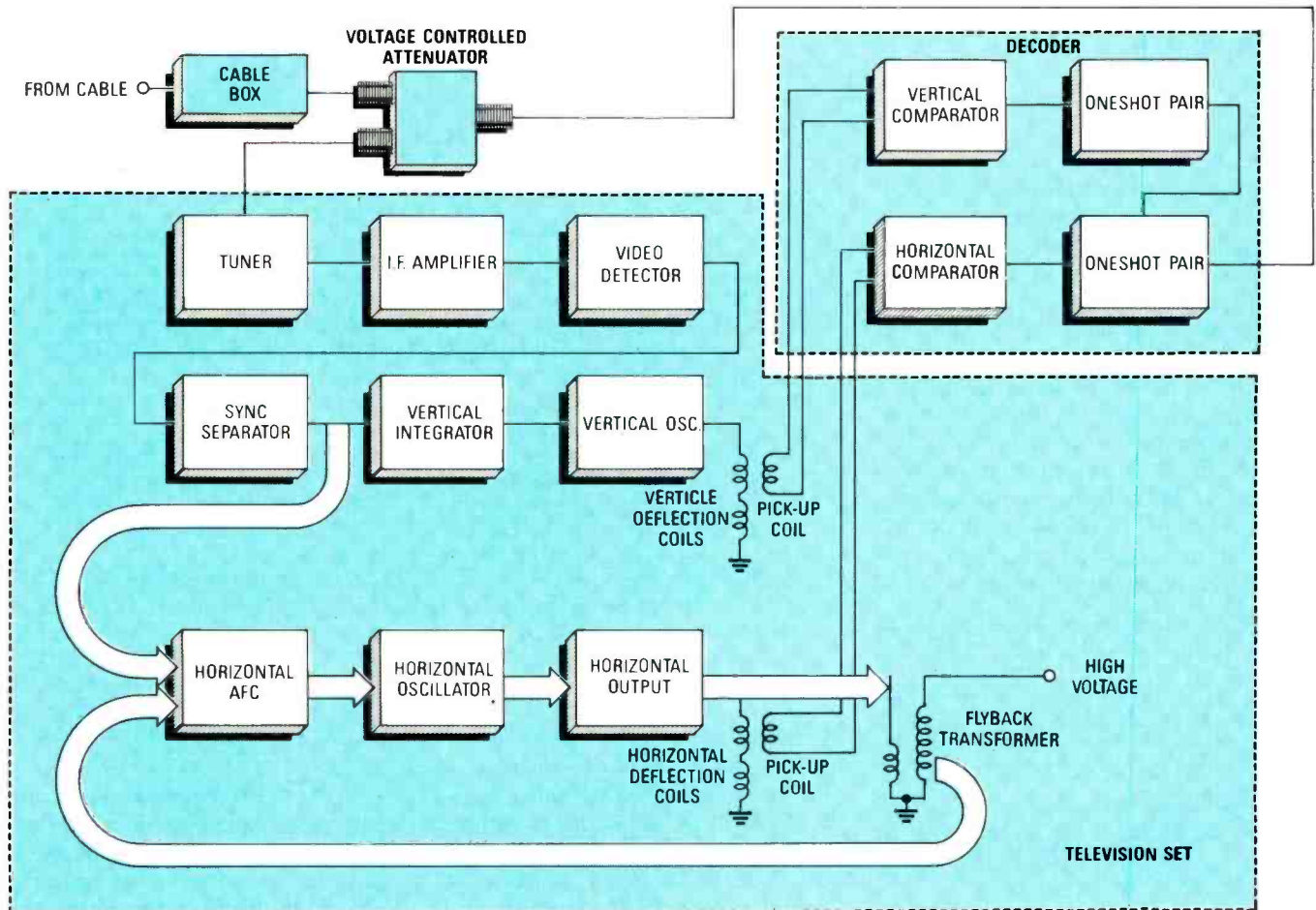


FIG. 2—THE DECODER WORKS by using sync samples from the TV's deflection yoke to control a signal attenuator.

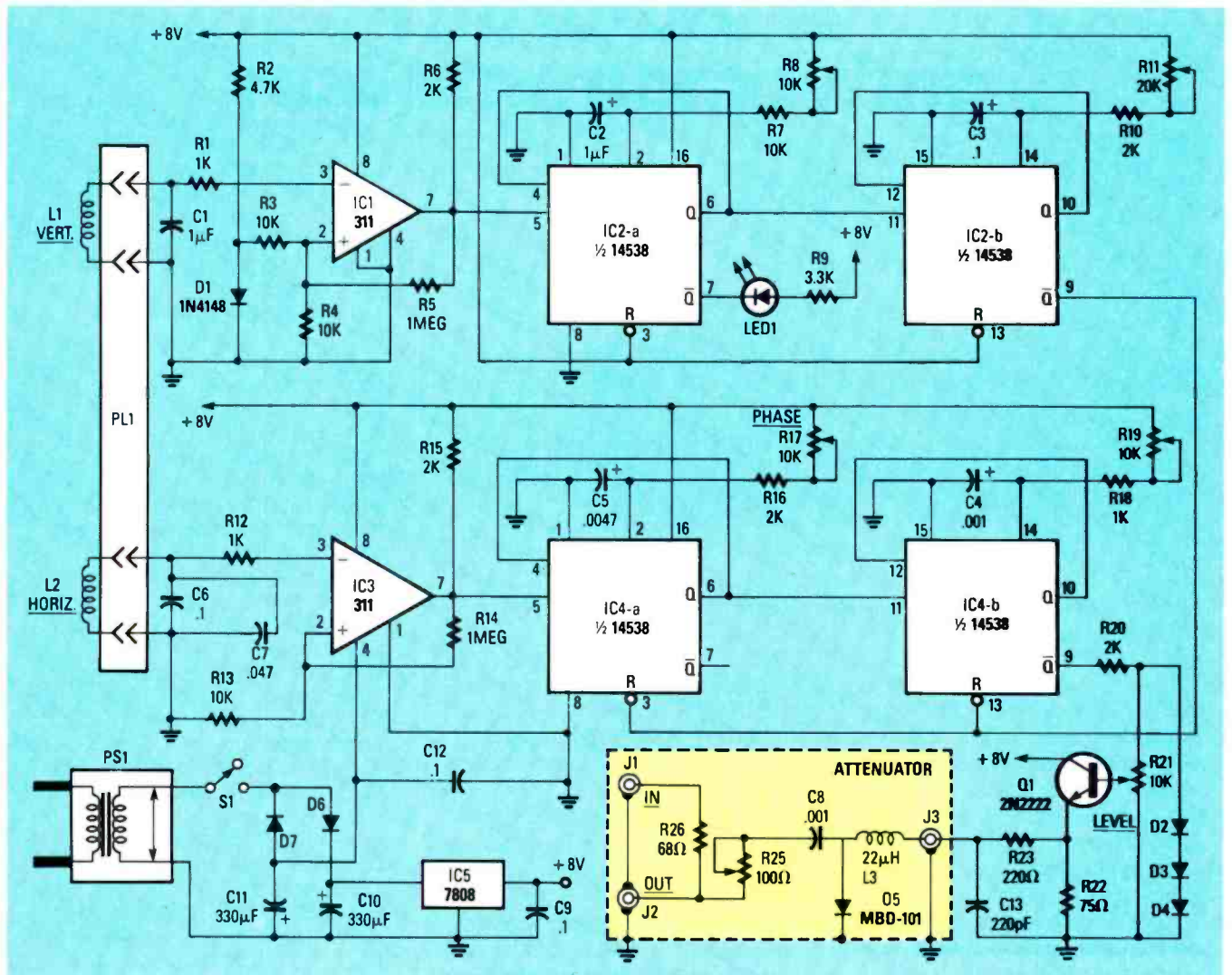


FIG. 3—THE DECODER'S CIRCUIT. The attenuator is built as a separate subassembly.

Closing the loop

Our decoder closes the loop by taking samples of the pulses produced by the horizontal oscillator and feeding them back around to the antenna input to increase the amplitude of the RF envelope during the signal's sync-pulse period. The samples of the TV set's vertical and horizontal sync pulses are obtained by induction from the TV's vertical and horizontal deflection coils.

The sync-pulse reinsertion is accomplished with a voltage-controlled attenuator. The attenuator reduces the amplitude of the RF signal feeding the TV set. Pulses from the decoder cause the attenuator to "unattenuate," thus increasing the signal level during the "unattenuate time"—which is effectively the same thing as re-inserting the sync pulse. Sync pulses are inserted pretty much randomly until the

right combination of horizontal oscillator, decoder oneshot phase delay, and re-insertion level occur. When everything is correct, so that a few sync pulses are inserted at the proper time, the whole system locks up and stability is restored to the picture.

The circuit

The decoder, which is shown in Fig. 3, requires that no direct electrical connection, nor any modification, be made to the TV set. The TV signals are obtained by pickup coils L1 and L2 through inductive coupling; hence, there is no shock hazard during set up as long as the television set is unplugged from the powerline and you touch nothing but the deflection yoke during the installation of the coils. The purpose of the coils—which are taped to the deflection yoke—is to pick up the horizontal and vertical scanning pulses.

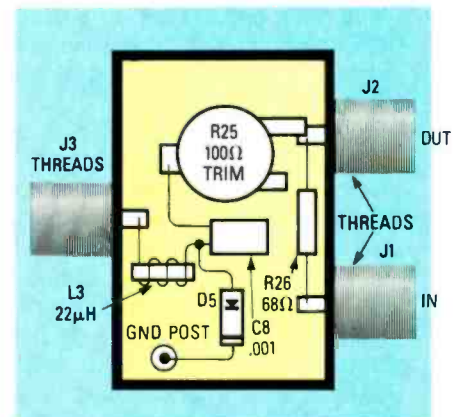


FIG. 4—THE ATTENUATOR is built in a gutted splitter. The assembly will be simplified if you follow this parts layout.

L1 and L2 are identical air-core coils. The vertical coil, L1, is taped to the side of the yoke (either right or left, it doesn't matter). Coil L2 is the horizontal coil, and it is taped to the top of the yoke.

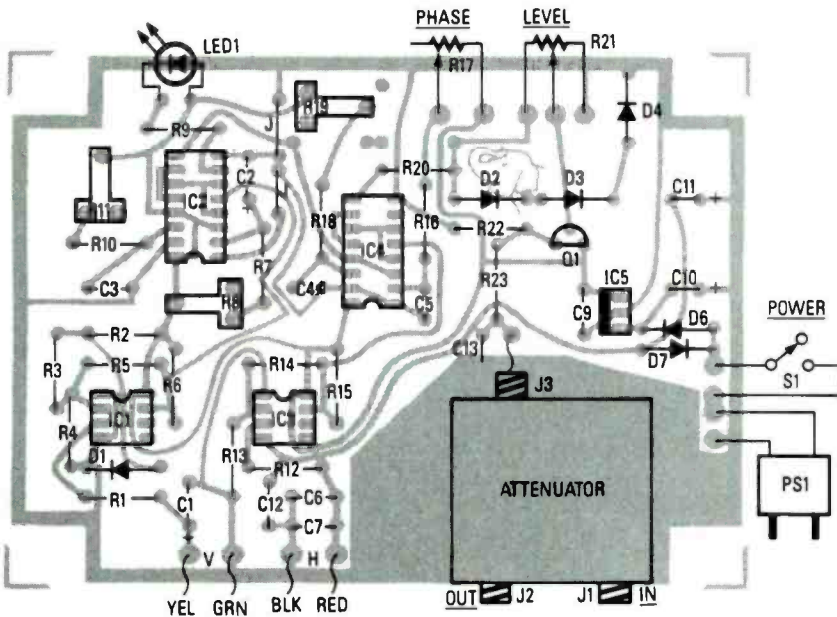


FIG. 5—THE PARTS LAYOUT. The attenuator subassembly is installed directly on the component side of the PC board.

A 15.734-kHz resonant circuit is formed by L2 and C6/C7. The waveform displayed on an oscilloscope that is connected across L2/C6/C7 will be a pure sine wave whose amplitude depends on the size of the picture tube. That's because as the screen gets larger, the yoke scanning current must become larger to deflect the beam.

IC3 is a zero-crossing detector that squares up the sine wave induced in L2 and converts it to single-ended drive for IC4—a CMOS oneshot—that follows. Because the input to IC3 is a sine wave that goes both above and below ground potential, IC3 must

have both a positive and negative supply voltage. The positive voltage is supplied by voltage regulator IC5. IC3's negative voltage is provided by D7 and C11.

IC4-a is used as a phase delay and sync pulse restorer pair. *Phase Adjust* control, R17, can vary the period of IC4 over the range of 9–56 μ s. R17 is installed on the front panel because it is used to phase-lock the decoder when the unit is first powered up, or when the user selects a different television channel.

IC4-b is used as a sync restorer that provides a pulse of 1–11 μ s (set by trimmer-potentiometer R19). The output pulse at pin 9 is normally high; it goes low during the sync pulse. Transistor Q1 is a low-impedance driver for attenuator-diode D5. Diodes D2, D3, and D4 limit the amplitude of the pulse so that D5 (in the attenuator) cannot be overdriven.

A simple shunt attenuator is made up of R25, R26, and D5. The RF signal that is applied to J1 is attenuated at J2 when D5 is forward biased. When the voltage across D5 drops to zero, the RF signal is unattenuated.

Basic circuit

In many instances, only the previously described circuit that is associated with L2 is all that's needed. With some judicious knob twisting, the circuit can be aligned by simply observing the picture to see the effect

PARTS LIST

All resistors 1/4 watt, 5%, unless otherwise specified.

- R1, R12, R18—1000 ohms
- R2—4700 ohms
- R3, R4, R7, R13—10,000 ohms
- R5, R14—1 megohm
- R6, R10, R15, R16, R20—2000 ohms
- R8, R19—10,000 ohms, trimmer
- R9—3300 ohms
- R11—20,000 ohms, trimmer
- R17, R21—10,000 ohms, potentiometer
- R22—75 ohms
- R23—220 ohms
- R24—not used
- R25—100 ohms, trimmer
- R26—68 ohms

All capacitors polystyrene, 25 volts, unless otherwise noted

- C1, C2—1 μ F, 25 volts, tantalum
- C3, C6, C9, C12—0.1 μ F
- C4, C8—0.001 μ F
- C5—0.0047 μ F
- C7—0.047 μ F
- C10, C11—330 μ F, 25 volts, electrolytic
- C13—220 pF

Semiconductors

- IC1, IC3—LM311 voltage comparator
- IC2, IC4—MC14538 dual monostable multivibrator
- IC5—7808, 8-volt regulator
- D1, D2, D3, D4—1N4148 silicon rectifier
- D5—MBD-101 or 1N5817 silicon rectifier
- D6, D7—1N4001 silicon rectifier
- LED1—red light-emitting diode
- Q1—2N2222, NPN transistor

Other components

- Attenuator—see text
- J1, J2, J3—part of attenuator
- PS1—wall transformer, 12 volt, 50mA
- S1—SPST switch
- PL1—Mating DIN connectors

Miscellaneous: Printed-circuit materials, wires, solder, soldering iron, hardware, tools, etc.

Note: The following items are available from Steve Pence, P.O. Box 41850, Phoenix, AZ 85080. The printed-circuit board: \$15.00. A partial kit that includes the PC board, IC's, and coils: \$25.00. The PC board for the April '85 Sync Separator project is available for \$15.00 (the complete kit has been discontinued). Allow 4 to 6 weeks for delivery. We cannot accept orders from Arizona residents. Canadian orders please use postal money orders in U.S. funds and add \$2.00 handling.

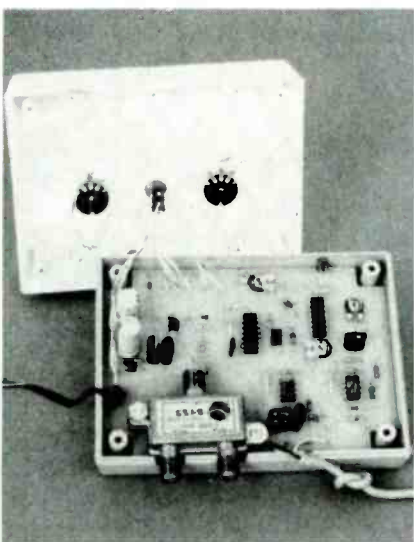


FIG. 6—THE COMPLETED DECODER. The three operating controls are mounted on the cabinet's cover.

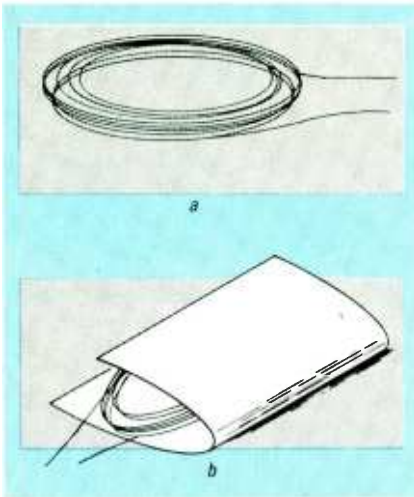


FIG. 7—STRETCH THE COIL into an oval, as shown in *a*. Then cover the coil with tape, as shown in *b*.

of each control. The decoder is connected between the output of a cable box and the antenna input of the television set. If desired, a VCR can be placed between the decoder and the television set, and the effect on the signal can then be observed with a scope by looking at the VCR's video output.

The vertical circuit, composed of L1, IC1, and IC2, locks out IC4 during the vertical interval. The pickup coil, L1, must be taped to the deflection yoke in order to pick up enough of a signal to drive IC1. Capacitor C1, which is connected across L1, serves only as a filter to remove the horizontal hash that is picked up along with the vertical pulse by L1.

The signal across L1 will be polarized, and must be of the correct polarity to drive IC1; hence it may be necessary to reverse the coil's connections. LED1 will light when L1's polarity is correct.

The two sections of IC2 operate the same as they do for IC4, except that they are used for the vertical, rather than the horizontal, sync pulses. IC2 is adjusted by R8 and R11 until the output pulses at pin 9 go low during the time you want the horizontal pulses locked out, which usually occurs during vertical blanking.

Construction

Except for the RF attenuator, construction is non-critical. The author's prototype was first built on a Radio Shack breadboard, and the circuit worked perfectly the first time. For those of you who prefer printed-circuit assembly, we provide a full-scale

template in PC Service. Take note that space and a ground plane are provided on the PC board for the RF attenuator, which, as shown in Fig. 3, is a separate unit.

Figure 4 shows the assembly of the attenuator, which is built inside a gutted two-set coupler. Most couplers are made of aluminum and cannot be soldered to; and most, but not all, will have a solderable ground stud inside. If yours does not, you will have to drill a hole for a machine screw with which you can bolt down your own ground lug. Solder a bare bus wire to the ground lug in the attenuator (the cut-off lead of a resistor or capacitor will do). The wire should exit out the bottom of the attenuator and be snaked through a hole in the PC board that you must drill specifically for the

ground wire. After the module is mounted to the board, solder the wire to the PC board's ground plane.

The reason for the ground wire is because the attenuator module's mounting screws often do not make a good ground connection to its case and the PC board. The ground wire is simply insurance against possible grounding problems.

You should also drill a 3/8-inch hole in the top of the attenuator module directly over where trimmer-potentiometer R25 will be mounted. The hole will allow you to adjust the trimmer without dismounting the module.

Figure 5 shows the parts placement on the PC board. Secure the attenuator case to the PC board with two screws. If the case has a separate external grounding tab, simply cut it

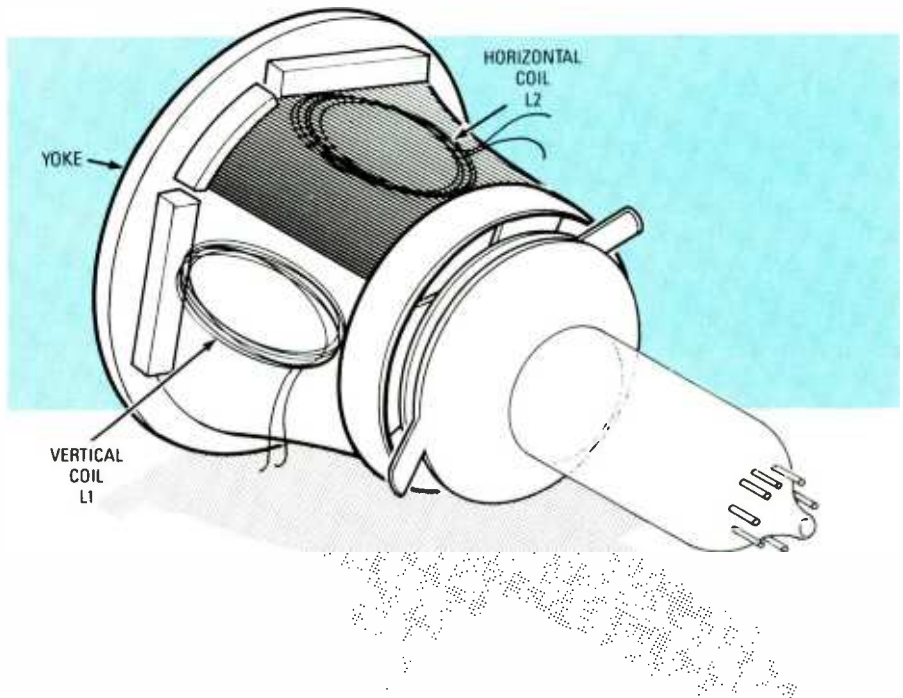


FIG. 8—TAPE THE COILS on the CRT's yoke as shown.

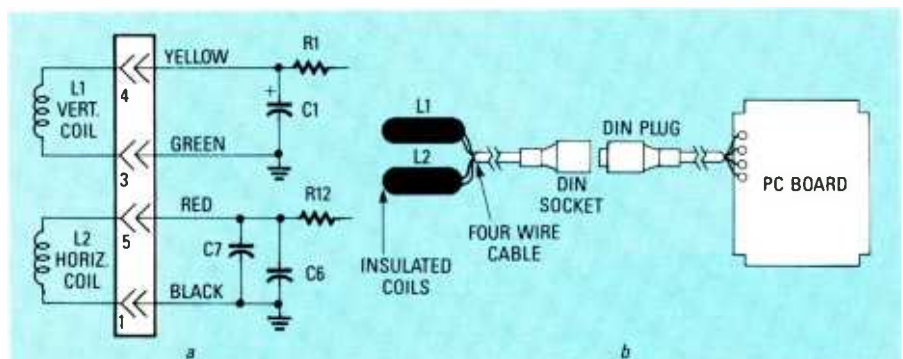


FIG. 9—THE ELECTRICAL COIL connections are shown in *a*. The way they are connected to printed-circuit board is shown in *b*.

off if it gets in the way of anything. Notice that IC1-IC4 are not mounted with the same orientation; that is, all No. 1 pins and/or notches do not face the same direction. Instead, all pin 1's and/or notches face the center of the PC board, as does IC5's metal tab.

Figure 5 also shows color-coding for the wires connected to the vertical and horizontal PC-board connections. The exact colors are unimportant—they will depend on the particular multi-conductor wire that's used. (The colors shown are those of conventional telephone quad.) We only show color-coding to help you integrate the parts placement with the wiring of L1 and L2, which we'll get to in a short while.

At this point the circuit board can be installed in a cabinet, as shown in Fig. 6. The phase (R17) and level (R21) controls, and the power switch (S1), are mounted on the cover.

Making the coils

Coils L1 and L2 are made by scramble-winding 100 turns of No. 28 or No. 30 solid, insulated, magnet wire around a 1/4-inch form. (The author used an empty 35-mm film canister for the form.) As shown in Fig. 7-a, after each coil is wound, slide it off the form and elongate the coil to form an oval. To prevent the coils from becoming unwound or deformed, dip them in hot candle wax or paraffin (available in most hardware stores.)

Make two coils, then attach leads to each coil that are long enough to reach from the inside of the TV set to the decoder. You can use either individual wires, pairs for each coil, or quad (four wires: two for each coil). Sandwich the coil assemblies in white adhesive tape for insulation, making certain that the tape covers the coils and the ends of the heavier hook-up wires. (The tape provides stress relief for the thinner coil wires).

Mount the coils to the yoke of the television set as shown in Fig. 8. The easiest way to do it is to simply hold the coils in place with a strip of adhesive or electrical tape. Snake the wires out of the TV set and connect them to a 5-pin DIN connector as shown in Fig 9. Figure 9-a shows the actual wiring and the DIN-connector numbers. Figure 9-b shows how the coils connect to the PC board.

Tweaking

Due to the differences in inductance that are possible when coils are wound by hand with whatever size wire is readily available, it may be necessary to select the value of C6/C7. The value needed to resonate with L2 will be near 0.15 μ F. After the coils are taped to the yoke, turn on the TV set and use a high-impedance voltmeter or scope to measure the induced voltage across C6/C7. Try different values of capacitance until you attain the maximum peak-voltage reading.

USING A SCOPE

Whenever you work with video, and in particular when working with decoders, you must often correlate the video signal with another signal, such as a sync re-insertion pulse. That is impossible to do if the scope you are using is not set-up to be triggered properly.

The secret is in a setup that allows you to look at only one line of video at a time; each time the scope sweeps, it displays the same line. In other words, if you want to look at scanning line number 32 (that is, the 32nd line of video that occurs after the first field begins), you must make the scope sweep only during the time that line 32 is present.

Most scopes do not easily allow you to trigger that way. Those that can be triggered that way have an extra feature called "delayed sweep." Delayed sweep allows you to trigger on a relatively slow repetitive event like vertical sync, delay out to a specific line of video, then begin a very fast sweep that is set by a second time-base. The delayed sweep allows you zero in on any part of a waveform that occurs after the trigger, and then expand that portion.

A project that provides scope delay was described in the April 1985 issue of **Radio-Electronics**.

Alignment

Ideally, alignment should be done with a scope, using the equipment arrangement shown in Fig. 10. The best scope to use is a dual-trace model having delayed sweep. For those of you without access to such a scope, begin by interconnecting the decoder with your television as shown in Fig. 11 (the VCR is optional). Turn on the TV set and tune the cable box to a non-scrambled station. Adjust the set's vertical-hold control until you can see the vertical-blanking bar: Try to get it to sit still long enough so you can measure the vertical height of the bar with a ruler or a tape measure. Make a note of the height.

Set R8, R11, R17, R19, and R25 to the center of their rotation, and set R21 fully counterclockwise. When you apply power to the circuit the vertical-polarity LED should come on. If it does not, reverse the leads from L1 or physically flip the coil 180°

Slowly adjust R21 clockwise—the picture becomes lighter as the control

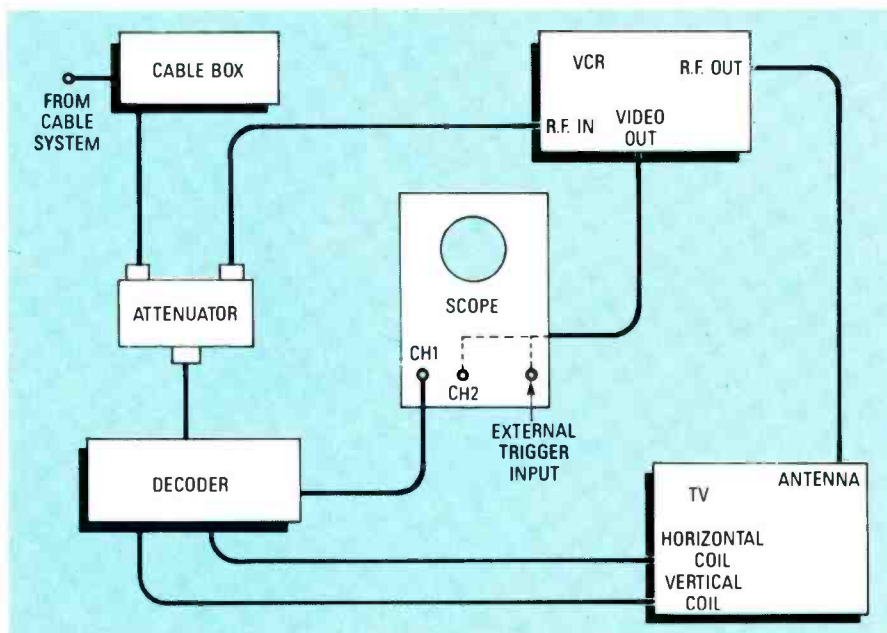


FIG. 10—THIS IS HOW TO CONNECT the equipment when making your checks and adjustments. The VCR is not necessarily required (see text).

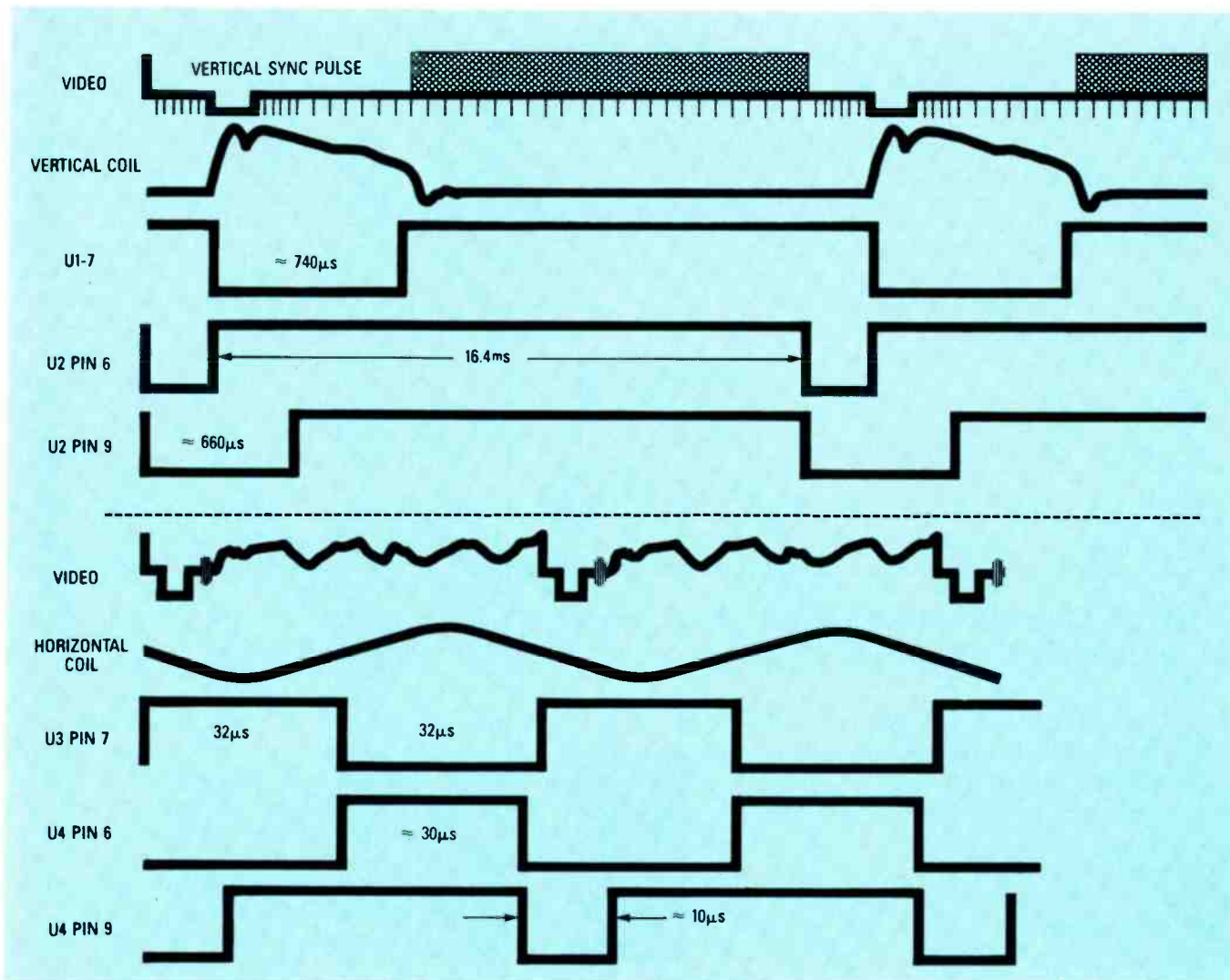


FIG. 11—IF YOU USE A SCOPE for checks and adjustments, this is how the important waveforms will be displayed.

is advanced. You may see a bar near the center of the picture that will be slightly darker than the picture itself. If you do not see the bar, adjust R17 to bring the bar in from either side of the screen. If you cannot make the bar appear from either side, reverse the connections to L2 or flip it over.

Adjust R17 until you can see the full width of the bar; then adjust R8 until you see a clear spot in the vertical bar. Then adjust R11 until the clear spot is just a little wider than the vertical blanking bar was that you measured previously. As R8 is adjusted through its full range, you should be able to make the clear spot appear from either the top or the bottom of the picture. Note where in R8's rotation the spot appears at the top, and where it appears at the bottom of the screen. Set R8 midway between those two points.

Set R17 midway between where the bar disappears on the left and right hand side of the screen. Tune in a scrambled channel and set R21 to about $\frac{3}{4}$ of its clockwise rotation. (That ensures that the attenuator diode is being driven hard.) Adjust R25 until the picture corrects; which will be easiest to do on a brightly lit picture, and nearly impossible to do on a dark picture. R25 should be set so that the picture is somewhat over-corrected and washed out; then adjust R21 for normal brightness and contrast. The three controls—R21 (phase), R19 (pulse width), and R21 (level)—all interact with one another and may require considerable experimentation and knob twisting to get them all correctly adjusted.

Keep in mind that D5 is being used as a switch and not as a diode. That means that it must be driven hard

enough (controlled by R21) to keep it off the sharp knee of its forward-bias curve. If it is allowed to act as a diode, it will also rectify the incoming signals and produce a varying voltage that will also modulate its own forward-bias voltage. That action will produce an interference pattern in the picture.

Once everything is properly optimized, all you should have to do will be to adjust R17 and R21 whenever you turn the decoder on, or after you change channels. In most, but not all, instances, picture-lock will occur automatically when a scrambled channel is selected and a fairly bright scene is available.

If the signal level of your cable system is too low, the 6-dB signal loss caused by the attenuator module will often cause snow in the picture. One solution to the problem is to place a

The Philips ECG DT-205 Digital Thermometer: better value in a more convenient size.

The pocket-sized, easy to use DT-205 has features usually found in more costly instruments. See for yourself:

- built-in retractable 3½" thermocouple probe
- measures in Centigrade or Fahrenheit
- ±1°C, ±2°F accuracy
- built-in pocket clip
- zippered carrying case

Make the smart choice. Contact one of our more than 900 distributors, or call 1-800-225-8326 for the name of the distributor nearest you. It just might be the smartest call you make all week.

CIRCLE 250 ON FREE INFORMATION CARD

The Smart Choice.
PhilipsECG
A North American Philips Company



The ECG pocket-sized DM-51 Multimeter is packed full of features!

The ECG® DM-51 Multimeter is part of our new line of compact multimeters that combine small size with big features. The DM-51 can easily be carried in a repair kit, bag, or even your shirt pocket!

- measures up to 200 MΩ
- up to 10 amps DC
- test batteries—9V, 1.5V
- transistor hFE test
- diode test
- continuity beeper

Contact one of our more than 900 distributors, or call 1-800-225-8326 for the name of the distributor nearest you. It just might be the smartest call you make all week.

CIRCLE 188 ON FREE INFORMATION CARD

The Smart Choice.
PhilipsECG
A North American Philips Company



Keep equipment in top shape with Philips ECG's top of the line Audio/Video products.



The best performance from any piece of equipment. The line-up that delivers it looks like this:

- To measure and adjust frequency response of audio tape decks, the AR20 frequency response cassette
- To accurately adjust audio tape running speed and record/playback head alignment, the AR30 speed and adjustment cassette
- To observe tape travel path in the VCR, the Video tape path view cassette
- To measure torque in play or fast forward/rewind modes, the Video torque meter cassettes

Contact your Philips ECG distributor or call 1-800-225-8326. It just might be the smartest call you make all week.

CIRCLE 68 ON FREE INFORMATION CARD

The Smart Choice.
PhilipsECG
A North American Philips Company

distribution amplifier in the signal chain prior to the decoder.

Scope set up

Begin by interconnecting everything as shown in Fig. 10. Set R8, R11, R17, and R19 to the center of their rotation. Set R21 for zero correction—full counter-clockwise. If the vertical-polarity LED does not come on, reverse the connections to pickup-coil L1 or flip it over and retape it to the yoke. Perform the set-up adjustments with an unscrambled signal.

Adjust R8 and R11 until the vertical-sync waveforms on your scope match those shown in Fig. 11-a. Both comparators of IC2 are triggered on the falling edge. The period of IC2-a is approximately 16.4 milliseconds. It should be adjusted to time out just before the beginning of the next vertical interval.

IC2-b is triggered by the falling edge from the first section. For most gated-pulse systems, its period will be approximately 660 μs. Again it should be set by comparing its pulse width to the video waveform. It should fire just before the vertical sync interval and time out just after the last equalizing pulse.

To set up IC4, compare the sine wave across L2 with the video waveform. The leading edge of the horizontal-sync pulses should correspond to the positive to negative transition of the sine wave through zero volts. If it does not, reverse the connections to L2 or flip the coil over.

Both sections of IC4, like IC2, are negative-edge triggered. Adjust R17 and R19 until they match the waveforms shown in Fig. 11. The output at pin 9 should be set for a starting pulse width of 8–10 μs.

Then, use the same alignment procedure as previously described, starting with the adjustment for R21.

Operating tips

If you can't locate an MBD-101 or a 1N5817 you can use a 1N4148; but if you do, another diode must be connected in series with D2, D3, and D4 to make certain that there will be enough drive voltage for D5.

The 14538 used for IC4 must be manufactured by either Motorola or National. The reason for that is because most other manufacturers do not guarantee operation for pulse widths below 20 microseconds, which is not narrow enough.

R-E

BUILD THIS

THOMAS A. NERY

EXCITING HOME VIDEOS USUALLY REQUIRE heavy editing—leaving the deadly-dull stuff “on the cutting-room floor.” Unfortunately, the commercial video-edit controllers needed for *pro*-quality editing are usually priced beyond the budget of most video hobbyists, which means that most videos usually end up looking like just another home movie—or worse.

But there *is* a low-cost alternative to commercial video editing. It's our video-edit controller; a relatively simple device that requires the use of only two VCR's, or a VCR and camcorder, to edit video tapes electronically like a professional.

Home videos are usually edited by pausing the recording VCR at the point where recording is to begin, and pausing the source (player) VCR at the point where the new video starts. Once satisfied with the edit points, both pause buttons are released simultaneously to allow the playback and recording to start.

Although the procedure for “pause-editing” is theoretically correct, real life proves that theory and practice are not one and the same, because machines—particularly when dealing with precise timing—don't necessarily function the way we would like them to. The variations in the pause-timing characteristics of VCR's and camcorders usually result in several seconds of lost picture at the edit.

Editing controller

But use our video-edit controller and you will eliminate the lost snatches of picture when editing. That's because our controller allows video editing by frames, rather than by time periods.

To understand the operation of the video-edit controller, it's necessary to understand why several seconds of video are lost when using the simultaneous-pause-release method of videotape editing.

When the source (player) VCR's *pause* is released, the machine starts playing slightly after the point where the tape is positioned. The “slightly

after” is a function of the tape getting up to speed before the video is output. The recorder, on the other hand, must synchronize itself to the source. To accomplish that, most newer VCR's—as well as camcorders—use a feature known as *preroll*.

Preroll

Preroll means that the recorder is rewind a predetermined number of frames, put into the play mode, and then shifted into *record* at the point where the recording is actually to start. When editing by dual-pause control, the additive “true start” delays of the source and record machines usually result in several seconds of missed video from the source.

There is also a synchronization problem associated with the dual-pause method of editing. Specifically, the recorder is being asked to synchronize itself to two different sources: the video prior to the source-VCR's getting up to speed, and then the video once speed is attained. That complicates the recorder's operation, and can result in video-breakup at the edit point.

Pro-quality editing

On the other hand, our video-edit controller does not depend on pause

controls: It edits in a way similar to some professional editors. First, it rewinds the source-VCR for a fixed amount of time and then switches the VCR to the *play* mode. At the appropriate time, while the source-VCR is playing, the controller starts the recording VCR. The recording VCR uses up its preroll, comes up to speed, and then switches to the *record* mode. If all the timings are correct, the source-VCR is feeding the selected edit frame at the precise instant that the-recording VCR switches to the *record* mode.

Overall editing accuracy is dependent on the ability of the source- and recording-VCR's to consistently repeat their operations in exactly the same time periods. Since the recording-VCR's preroll is designed by the manufacturer to always start the recording after a fixed time interval, it is the source-VCR that's the main synchronizing problem.

Review to time

But we can make the source-VCR's rewind timing more or less consistent if we use the machine's *review* function—rather than the *rewind* function—to back up the tape. That is due to the fact that *review* is a *capstan*-driven function that always operates at a predetermined multiple of the nor-

VIDEO-EDIT CONTROLLER



Here's a low-cost device for professional-quality video editing.

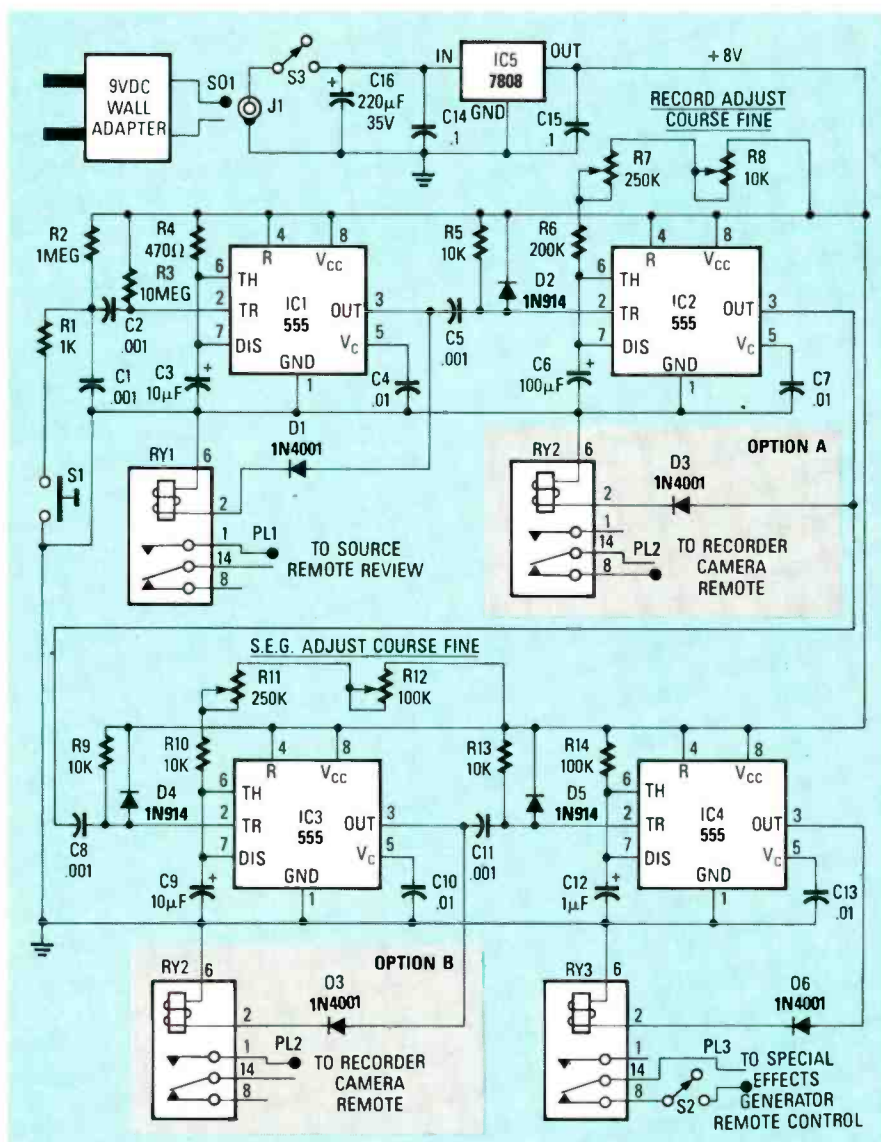


FIG. 1—THE VIDEO-EDIT CONTROLLER basically consists of four similar timer circuits. Both the OPTION A and OPTION B circuits for relay RY2 are built into the PC board. Simply plug the relay into the appropriate socket.

mal play speed. During *review*, the tape is always backed up the same length per period of time; whereas, during *rewind*, the actual amount of tape backed up per unit of time depends on how much tape is left on the supply reel.

In addition to the edit function, the controller also provides a switching circuit for a special-effects generator, such as you might use to cause a fade from, or to, black at the correct time.

How it works

The edit-controller, shown in Fig. 1, consists of four monostable timers. Each timer has the capability to drive a relay, although only three relays are used to interface to the controlled devices. To accommodate different re-

mote-control circuits, relay RY2 can be installed at the locations labeled OPTION A, or OPTION B—more on that later.

The edit operation is started by closing switch S1, which causes a rapid drop to ground of the voltage across capacitor C1. C1's discharge causes a negative-going spike through C2, which triggers timer IC1. The triggering of IC1 causes RY1's contacts to close, and they remain closed during IC1 timing period. The timing period is determined from the equation:

$$\text{time} = 1.1(R4 \times C3)$$

The source-VCR's remote-control *review* jack is connected to RY1's contacts through PL1. The VCR will be

held in the *review* mode during IC1's timing period. At the end of the timing period, RY1 is released, its contacts open, and the VCR automatically switches from the *review* to the *play* mode. Also at the end of the timing period, IC1 triggers timer IC2.

Timers IC2-IC4 operate in a similar manner as IC1, the major difference being that IC2 and IC3 have *coarse* and *fine* adjustments for tweaking the time-period. Also, RY2 can be driven either by IC2 or IC3, depending on the requirements of the recording-VCR. If the recorder is started by opening its remote control, RY2 is installed at the OPTION A location. If the recorder is started by closing its remote control, then RY2 is installed at the OPTION B location.

The editor's timing constants are a function of both the type and the speed of the VCR's. While the principles can be applied to any combination of VCR's and speeds, the prototype assumes VHS machines operating at the SP speed. Should a different combination be desired, it will be necessary to adjust the timing components for the selected speed.

Construction

Before building anything, you must make certain that your source-VCR is compatible with the controller. Place a tape in the VCR and start the play. After about 30 seconds, depress the *pause* button. Once the VCR has come to a complete stop—as indicated by a frozen frame on the screen—press and hold the *review* (or dual-function *review/rewind*) button for about five seconds and then release it. The VCR is compatible with the video-edit controller if it rewinds and then automatically enters the *play* state when the *review* button is released. If releasing the button did not cause the VCR to switch automatically into the *play* mode, then it can't be used with the controller.

If the VCR passes the compatibility test, you must make a review-switch modification. Disconnect the VCR from the powerline, open the VCR's case, and locate the *review* switch's contacts. Use a VOM to verify that you have selected the correct contacts. (In some VCR's the *review* switch has DPST contacts that are wired in parallel.) Solder a pair of thin, insulated, stranded wires (i.e. 22 gauge) to the switch's contacts. Then route the wire to an accessible

blank portion of the VCR's rear apron. Carefully drill a hole in the apron for a miniature phone jack that will mate with PL1. If the cabinet is metal, use two contacts of a 3-circuit jack and change PL1 to a 3-circuit miniature phone jack. (The plug's *sleeve* connection—which is connected to the VCR's grounded cabinet—should not be used.)

Complete the modification by soldering the wire pair to the phone jack. Then, replace the VCR's cover. At that point, the VCR should be tested for normal operation. Check the modification for a short-circuit if the VCR doesn't operate correctly.

The controller is assembled on a PC board, for which a full-scale template is provided in PC service.

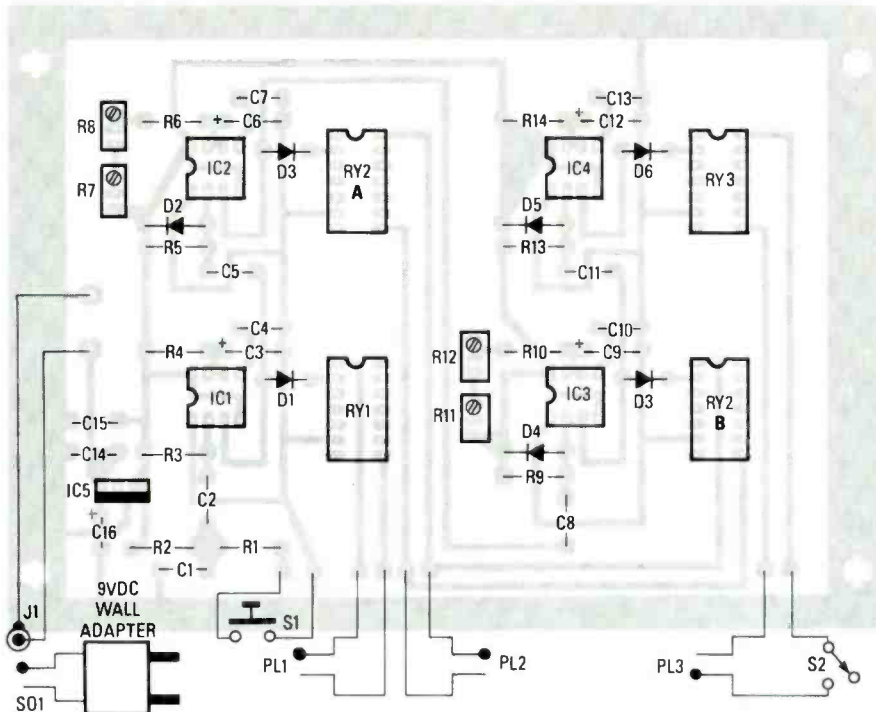


FIG. 2—THE CONTROLLER'S PARTS LAYOUT. Select only one location for RY2; the other remains empty.



FIG. 3—THE PRINTED-CIRCUIT BOARD is mounted in the cabinet using spacers at each mounting screw. Make certain that there is some kind of wire between the PC board's ground trace and the metal cabinet.

PARTS LIST

All resistors 1/4-watt, 10%, unless specified otherwise.

- R1—1000 ohms
- R2—1 megohm
- R3—10 megohms
- R4—470,000 ohms
- R5, R9, R13—10,000 ohms
- R6—200,000 ohms
- R7, R11—250,000 ohms, multiturn potentiometer
- R8, R12—10,000 ohm, multiturn potentiometer
- R10—47,000 ohms
- R14—100,000 ohms

All capacitors rated 10 volts, unless specified otherwise.

- C1, C2, C5, C8, C11—0.001 μ F, disc
- C3, C9—10 μ F, tantalum
- C4, C7, C10, C13—0.01 μ F, disc
- C6—100 μ F, tantalum
- C12—1 μ F tantalum
- C14, C15—0.1 μ F
- C16—1000 μ F, 35 volts, electrolytic

Semiconductors

- IC1—IC4—555, timer
- IC5—7808, 8-volt regulator
- D1, D3, D6—1N4002, silicon rectifier
- D2, D4, D5—1N914, rectifier

Other components

- J1—male power-supply mini-jack to match SO1
- PL1, PL2, PL3—miniature phone plugs to match VCR equipment
- RY1, RY2, RY3—SPDT DIP relay, GORDOS 831A-4
- S1—N.O. momentary switch
- S2, S3—SPST switch
- SO1—power socket, part of 9-volt wall adapter

Miscellaneous

- Printed-circuit materials, WA1—9-volt DC wall adapter, DIP sockets, cabinet, wire, solder, etc.

The parts layout is shown in Fig. 2. Notice that there are two locations—labeled A and B—for RY2. If you use DIP sockets for mounting the relay, you will then be able to switch RY2's location easily to conform with the remote-control circuit of the associated VCR.

Figure 3 shows how the prototype's fully assembled PC board looks when it's finished, and also how it is installed in its cabinet.

VCR modification

The controller requires a special, though quite simple, modification to the source-VCR's *review* switch. But be aware that opening the case of the VCR and installing the modification will void the warranty (if it is still in effect).

Remote jack

The recording-VCR or camcorder should have a camera-controlled remote jack. Also, for best results the recorder should also perform a preroll operation prior to initiating the recording action. That feature can often be verified by the recorder's user's manual.

The recording-VCR will run-record when the camera-controlled remote jack is switched by RY2's contacts. The location of RY2 is determined by the requirements of the remote jack. If recording is started by opening a contact, RY2 should be installed in the **OPTION A** location, which is controlled by IC2. If recording is started by closing a contact, RY2 should be installed in the **OPTION B** location, which is controlled by IC3.

Calibration

The only items required for calibration are two prerecorded tapes. One is a *source* tape, which contains a clean transition of scenes. The tape can easily be made by making an off-the-air recording of about five minute of program up to a commercial, the

commercial, and then five minutes of program. The commercial is only needed so that you can easily recognize a scene transition—from program to commercial and vice versa.

The other tape is the recording tape. It should be pre-recorded with about five minutes of programming.

Connect PL1 to the *review jack* that was added to the source-VCR. Connect PL2 to the recording VCR's camera-controlled remote jack.

Roll the source tape, locate the start of the commercial as closely as possible, and place the source recorder into the *pause* mode.

Then play the second tape in the recording VCR. Locate the end of the recording, set the recorder to *pause*, then activate the record function.

Set the *coarse* adjustment associated with RY2 (R7 or R11) to its smallest value and the *fine* adjustment (R8 or R12) to the center of its adjustment. Press S1. Each of the recorders will do its thing—controlled by the video-edit controller.

After the recording VCR runs for about 30 seconds, stop and rewind its tape to the point where the recording

was inserted and press the *pause* button. Then release the *pause* button and time the playing time from the source-tape's entry point until the source-tape's commercial appears.

Using the equation given earlier, calculate the combined resistance value of R7 and R8 (or R11 and R12) that is needed to eliminate the pre-commercial timing. Set the *coarse* adjustment to that value.

Repeat the procedure until the editing controller correctly locates the edit point within about one-half second. At that point, the procedure should be repeated once more, using the *fine* adjustment, until the edit point is "on the nose."

That completes the calibration. A similar method is used to calibrate the switch-in of a special-effects generator via PL3.


Now you're ready to edit some video tapes, and it may take a few tries to become familiar with the system. However, in no time at all, you'll be getting rid of unwanted commercials, splicing together your favorite movie scenes, or removing scenes that you don't want your kids to see. **R-E**

HOLD IT ANYWHERE YOU WANT IT!


PanaVise electronic work holding systems allow you to position, tilt and rotate your projects without removing them from their holding devices! With over 30 years experience and made-in-USA quality, PanaVise ensures reliable, long-lasting service.



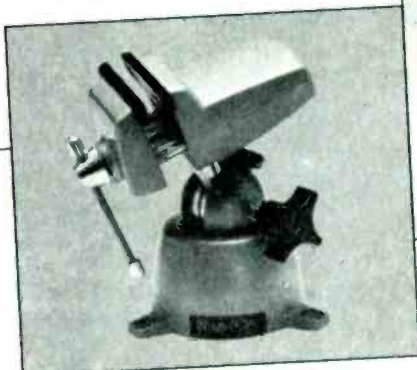MULTI-PURPOSE WORK CENTER: Self-Centering Extra Wide Opening Head (opens to 9"), famous "split ball" Standard Base (moves in three planes), and convenient Tray Base Mount (with parts wells) handle difficult to hold items with ease! Model #350. \$52.95.



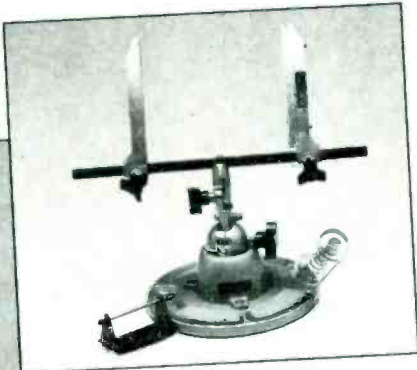STANDARD PANAVISE: Our most popular vise, the Standard PanaVise is an extremely versatile, useful workbench tool. Jaws open a full 2.25" and the patented "split ball" base tilts, turns and rotates through three planes. One convenient control knob locks work into any position! This durable, all-purpose mini-vise stands about 6" tall and will deliver years of rugged service. Model #301. \$33.95.



ELECTRONIC WORK CENTER: A complete combination to make work areas more efficient and manageable! Circuit Board Holder gently, but firmly, holds PCB's up to 12" wide. Add our Standard Base (moves in three planes), Tray Base Mount (with parts wells), and Solder Station (self-centers wire and holds iron at perfect angle) for a great combo! Model #324. \$54.95.



See your local electronics supplier or contact PanaVise for the source nearest you.
PanaVise Products, Inc., 2850 E. 29th Street,
Long Beach, CA 90806; (213) 595-7621

TRUE RMS CONVERTER FOR YOUR DMM

This simple converter will add true-RMS capability to any VOM or DMM and it will only cost you about twenty dollars!



STEVEN A. BROWN

JUST ABOUT ANY VOM OR DMM CAN ACCURATELY measure the RMS voltage of pure sine-wave AC. But true-RMS capability is a feature that is usually found only on top-of-the-line meters.

In the AC mode, the average multimeter (one that does not have true-RMS capability) simply measures the peak rectified value and scales it by a factor of 0.707. Otherwise, they measure the average rectified value and scale it by the factor 1.11, which is the ratio of RMS-to-average, or 0.707/0.636. Introduce some distortion to the sine wave, however, and the reading's accuracy becomes questionable. Try measuring a non-sinusoidal waveform, such as sawtooth or square wave, and the reading can become utterly meaningless.

For example, when measuring a 10%-duty-cycle square wave, the reading on an average meter can be off by more than 100%! For such waveforms, the only reliable measurement of voltage can be made using a voltmeter or multimeter with true RMS capability. That feature is usually found on only the most expensive digital multimeters—until now. In this article, we'll show you how to build

an accurate, low-cost converter that will give true RMS measurement capability to *any* VOM or DMM. Before getting into the details of the circuit though, let's briefly take a look at what RMS means, and why its value is important to know when talking about AC waveforms.

RMS defined

RMS stands for Root Mean Square (the square root of the average of the squared values), a mathematically derived quantity that is taken to be the value of an equivalent DC voltage—one that would produce an equal amount of heat in a resistor or light from a light bulb. In an AC waveform, the instantaneous voltage varies as a function of time. Therefore, the equation that defines the RMS voltage must take into account the functional relationship between those two variables, and it can only be applied if an exact mathematical expression for that relationship is known, which can be “plugged into” the equation. An example of such an expression is the one that gives us the instantaneous voltage (v) at any time (t) for a sine wave is:

$$v = V_{\text{MAX}} \sin \omega t$$

where V_{MAX} is the peak amplitude, ω is the angular frequency in radians-per-second, and t is the elapsed time from the beginning of the cycle. The equation for the RMS voltage of any periodic waveform, where “ V ” is a function of t , is given by:

$$V_{\text{RMS}} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} v^2(t) dt}$$

where T is the total period of time under consideration. For those who are not familiar with calculus, the definite integral under the radical sign, whose symbol resembles a tall thin S , represents the “area under the curve” if v^2 were plotted against t . That quantity, multiplied by $1/T$, is equal to the average value of v^2 during the time period T . The square root of the average value is the RMS voltage.

Though it would be possible to construct a circuit to perform the operation of the second equation, a simpler approach—the one that is used by DMM's that can measure true RMS—is to square the instantaneous input voltage, average that square with a

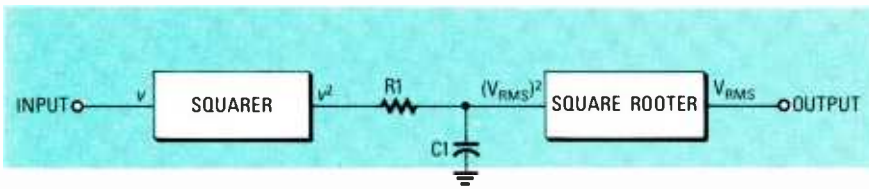


FIG. 1—RMS CONVERTER BLOCK DIAGRAM. This shows how an RMS measurement is obtained.

long time-constant RC network, and take the square root of their average. That sequence of operations is shown in the block diagram of Fig. 1, and can be represented mathematically by the simpler equation:

$$V_{RMS} = \sqrt{\text{Avg.}(v^2)}$$

where v is the instantaneous voltage. The basic difference between that sequence of operations and that of the previous equation lies in the method—but the result is the same. While the previous equation gives the precise net effect of v over a definite time period, the simpler method makes use of the property of a low-pass RC network (Fig. 1) that causes capacitor C1 to drift slowly to, and finally settle at, the long-term average of the instantaneous voltage applied to resistor R1. The time for the C1 to reach that final value, once a steady-state AC voltage has been applied to the network, is approximately equal to five times the RC time constant. By selecting a suitably long time constant, so C1's voltage does not vary significantly during the period of one cycle, a precise average can be obtained.

Stated simply, the RMS voltage of an AC waveform is equal to the square root of the long-term average of the square of the instantaneous voltage. At this point, the reader might ask why the effective value of an AC voltage is not equal to its average value. The answer to that question becomes apparent if one bears in mind that the power delivered to a load is proportional to the square of the applied voltage, in accordance with the familiar equation:

$$P = \frac{V^2}{R}$$

Therefore, in determining the RMS value of an AC voltage, the square of the instantaneous voltage is proportional to the instantaneous power that would be produced in a load. Since the average of the instantaneous power would be equal to the power produced by an equivalent DC voltage, the RMS voltage is found by

averaging the square of the instantaneous voltage over a period of at least one cycle, and taking the square root of that average.

Applications of RMS

Now that we've examined what RMS means, let's take a look at some applications where an accurate RMS measurement becomes an important thing to know.

- To measure the output of motor-speed and light-dimmer controls, where the 60-Hz AC waveform is chopped by SCR or Triac switches.
- To measure pulse-width-modulated waveforms in switching power supplies.
- To measure and adjust the output of a battery charger for optimal rate of charge, where the output is rectified but unfiltered DC.
- To measure the power applied to an audio-speaker system by speech or music. A good approximation of audio power can be found by:

$$P = \frac{V^2}{Z}$$

where V is the RMS voltage measured across the speaker terminals, and Z is the nominal system impedance.

- To measure the effective value of any AC or variable DC waveform.

About the circuit

A complete schematic diagram of the True RMS Converter is shown in Fig. 2, and its specifications can be seen in Table 1. The heart of the circuit is Analog Devices' AD736 true-RMS-to-DC converter IC. Its low power consumption of 1 mW makes it ideal for portable, battery-powered operation. The device can measure inputs of 1-volt RMS or less, but it is most accurate with a 200-mV RMS input. To measure higher voltages, an input attenuator is required.

The input at pin 2 of the AD736 is internally connected to the non-inverting input of an FET buffer which has an impedance of 10^{12} ohms. That makes it well-suited for use with the high-resistance input attenuator, R1. Pin 1 is internally connected to the inverting input of the FET buffer which has an impedance of 8,000 ohms, and it is used to reference pin 2 to ground. When switch S2 is closed (DC mode), pin 1 is connected directly to ground. That makes the converter responsive to both DC and AC components of the input signal. When measuring signals having a very small amplitude, S2 can be opened (AC

TABLE 1—SPECIFICATIONS

Transfer Function: RMS-to-DC voltage
Accuracy: ± 0.5 mV, $\pm 0.5\%$ (1kHz sine-wave, AC-coupled, 0-to-200 mV, 200 mV range)
Input Impedance: 10 megohms
Maximum Input Voltage: 1200 VRMS
Bandwidth: 33 kHz (1% additional error)
190 kHz (± 3 db)

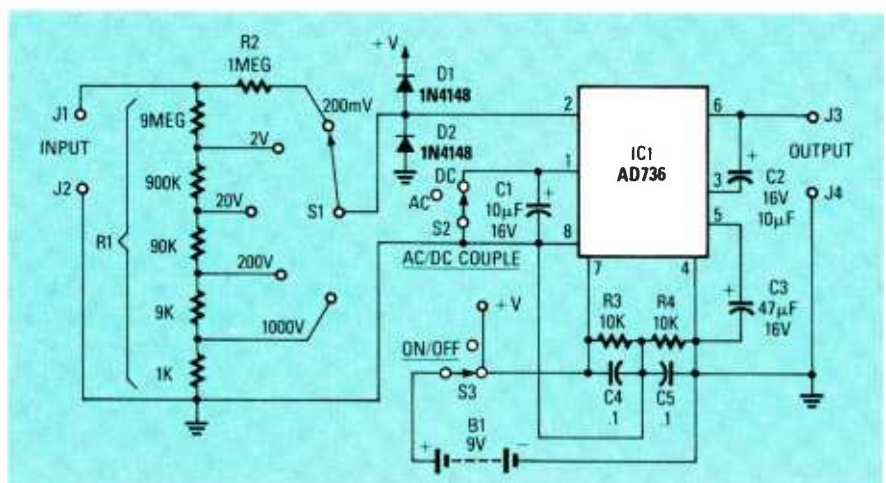


FIG. 2—SCHEMATIC DIAGRAM. The heart of the circuit is the AD736 true-RMS-to-DC converter IC.

PARTS LIST

Resistors

R1—Caddock 1776-C742 5-decade voltage divider

R2—1 megohm, ½-watt, 5%

R3, R4—10,000 ohms, ¼-watt, 5%

Capacitors

C1, C2—10 µF, 16 volts, radial electrolytic

C3—47 µF, 16 volts, radial electrolytic

C4, C5—0.1 µF, 50 volts, 10%, polyester film

Semiconductors

D1, D2—1N4148 diode

IC1—AD736JN RMS-to-DC converter (Analog Devices)

Other components

J1–J4—Insulated binding posts

S1—5-position rotary switch, (Mouser 10YQ025 or equivalent)

S2, S3—SPST subminiature toggle switch

B1—9-volt alkaline battery

Miscellaneous: 9-volt battery connector, 9-volt-battery mounting clip, plastic project case, plastic knob for rotary switch, wire, etc.

Note: A complete kit containing an etched and drilled PC board and all components that mount on it (SPST switches, binding posts, etc., not included) is available for \$19.95 plus \$2.50 for shipping and handling from Andromeda Electronics, 125 N. Prospect St., Washington, N.J. 07882. New Jersey residents must include 6% sales tax. Allow three weeks for delivery.

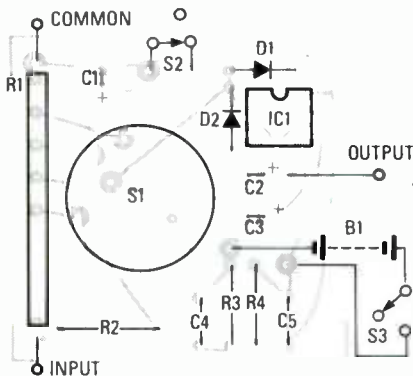


FIG. 3—MOUNT THE COMPONENTS as shown. All other parts mount on the cover of the plastic project case.

mode) and the input thereby becomes AC-coupled. In that mode, signals as small as 100 microvolts RMS can be measured.

Capacitor C3 is the averaging capacitor; C2 removes any residual rip-

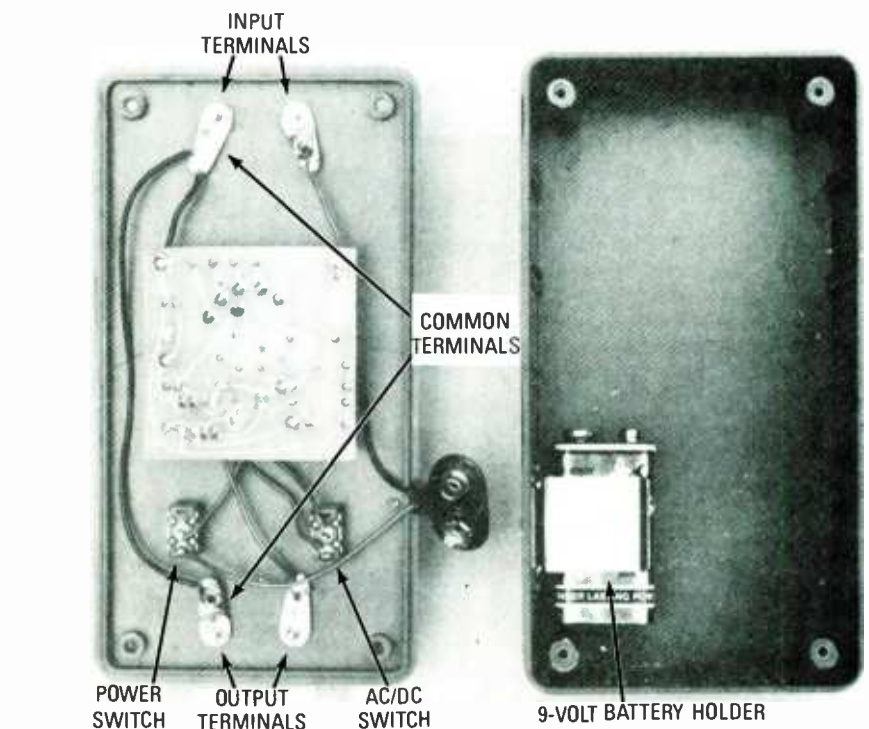


FIG. 4—THIS IS HOW YOUR CONVERTER should look when it's completed. You can see how the common terminal from both the input and the output are wired together.

ple that might be present at the output. The attenuator is a Caddock 1776-C742 precision 5-decade voltage divider with a ratio tolerance of $\pm 0.25\%$. Switch S1 is used to select the tap on the voltage divider that corresponds to the range of voltages to be measured.

The network made up of R2, D1, and D2 prevents overvoltage damage to IC1 by limiting the peak input voltage at pin 2. Resistor R2 has a power rating of ½-watt, so the maximum continuous overvoltage that can be sustained by R2 indefinitely without damage is about 700-volts RMS. Overvoltages up to 1200-volts RMS can be withstood for several seconds. No damage at all can occur to R2 from overvoltage in the 2-volt position and higher.

In the 200-mV position, IC1 reads the full voltage across the input terminals. When S1 is placed in the 2-volt position, all input voltages are divided by 10, and the DC voltage across the output terminals, as read by a DC voltmeter, must be multiplied by 10 to obtain a correct RMS reading. With S1 in the 20-volt position, the output reading must be multiplied by 100; in the 200-volt position, by 1000; and in the 1000-volt position, by 10,000 (Table 2 lists the multiplier values). The maximum continuous input voltage in

TABLE 2—MULTIPLIER VALUES

Range in use	Multiply output by
200 mV	1
2 V	10
20 V	100
200 V	1000
1000 V	10,000

the 1000-volt position should not exceed 1200-volts RMS—the maximum rating of the voltage divider.

An important parameter of AC waveforms is the crest factor, which is defined as the ratio of the peak voltage to the RMS voltage. A sine wave has a crest factor of 1.414, while music with its high transients may have crest factors of 10 or more. The crest factor becomes significant when the peak excursions of the waveform approach the peak transient limits of the input of the measuring device. Peak clipping will occur if either of those limits are exceeded, resulting in a loss of accuracy. For an AD736 that is powered by a 9-volt battery, the peak transient limits of the input at pin 2 are approximately ± 2.5 volts. Therefore, the crest factor of a 200-mV RMS signal, measured on the 200-mV range, would have to exceed 12.5

DAMARK

INTERNATIONAL, INC.

MUST LIQUIDATE AT FAR BELOW DEALER COST!

FREE GIFT with Order!

9 Function Superior Multi-Purpose Swiss Army like knife. Value: \$24.95



MAGNAVOX

VIDEOWRITER/WORD PROCESSOR
A revolution in writing is right at your fingertips! This Magnavox Videowriter/Word Processor is the ideal personal writing system for the novice or seasoned pro. NO TRAINING NECESSARY...built-in instructions appear on the screen while you see what you write!

- Write, insert, delete, move & copy text at any time.
- Built-in 50,000 word dictionary lets you check spelling at any time.
- Built-in type styles: normal, bold, wide, superscript, & subscript.
- Screen splits so you can work on 2 documents at once.
- Displays 18 lines at a time. • Automatically saves each page.
- Automatically indents, centers & justifies right margin.
- Standard 3 1/2" disk holds approx. 75 pages.
- Printer automatically loads standard paper & envelopes.
- Whisper quiet thermal print head. • Includes ribbon, dictionary, storage diskette & paper. • Factory Serviced, but like new!



Mfg. Sugg. Retail: \$799.95
DAMARK \$399
FULL FACTORY WARRANTY!
Order No. B-1004-107763
Insured Ship/Hand: \$14.50

FLYING EAGLE

REMOTE DUNE BUGGY



Enjoy fun in the sand & sun, or out in the yard with this Flying Eagle radio controlled car. Great fun for kids of all ages, from 8 to 80!

- Races over 30 Miles Per Hour!!
- 10 Functions: Forward, backward, stop, left, right, head light, car horn, variable speed, high-speed & low-speed shift gear.
- Balloon Tires.
- Size: 11.75"L x 7.25"W x 5.5"H.
- Full Factory Warranty!
- Factory New!

Factory Perfect! Mfg. Sugg. Retail: \$129.95
DAMARK \$59
Order No. B-1004-105650
Insured Ship/Hand: \$4.50

Advance

QUARTZ MEMORY CARD



Never Worry About Phone Numbers & Addresses Again! You Can Carry A Complete Directory in Your Billfold or Wallet!

- Credit card size.
- Automatic shut off.
- Stores up to 1910 char.
- Full function calculator.
- Long life battery.
- Memo messages alarm.
- Clock.
- Full Factory Warranty!
- Factory New! Factory Perfect!


This powerful credit card-sized Quartz Memory Card and Calculator by Advance stores anything such as names, addresses, & phone numbers. Able to select your own security access code so only you can retrieve the information.

Mfg. Sugg. Retail: \$59.95
DAMARK \$19
Order No. B-1004-104430
Insured Ship/Hand: \$4.00

FOR FASTEST SERVICE CALL TOLL FREE 1-800-950-9090

- Check/Money Order VISA
 MasterCard Discover

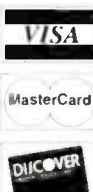
NAME _____
ADDRESS _____
CITY _____ ST _____ ZIP _____
PHONE _____
CARD NO. _____



DAMARK INTERNATIONAL, INC.
6707 Shingle Creek Parkway, Minneapolis, MN 55430
Corporate Offices • 612/560-5415

Please RUSH me:

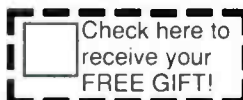MAGNAVOX Video Writer(s) @ \$399 each, plus \$14.50 shipping/handling ea. Order No. B-1004-107763
ADVANCE Memory Card(s) @ \$19 each, plus \$4.00 shipping/handling ea. Order No. B-1004-104430
FLYING EAGLE Dune Buggy(s) @ \$59 each, plus \$4.50 shipping/handling ea. Order No. B-1004-105650
MN res. add 6% sales tax.



EXP. DATE _____

before peak clipping occurs. If a 1-volt RMS signal were measured on that same range, however, 2.5 would be the maximum crest factor beyond which peak clipping would occur. Switching to the 2-volt range would raise the crest-factor threshold of clipping to 25 for the same 1-volt RMS signal.

Construction

The RMS Converter can be installed in any case (preferably plastic) that is large enough to fit the PC board, the battery, and all other associated wiring, switches, etc.

All components except S2, S3, B1, input jacks J1 and J2, and the output jacks J3 and J4 mount directly on the PC board, as shown in Fig. 3. Rotary switch S1 is soldered directly to the PC board, and its bushing provides a rigid mounting to the case.


To accommodate S1's anti-rotation tab, a 1/8-inch diameter hole should be drilled 1/2-inch below S1's mounting hole. Both the input and output common terminals should be wired together (see Fig. 4) and to the IC1 pin-8 PC solder pad. The input and output jacks, as well as S2, S3, and the battery-connector leads, should be connected to the appropriate PC pads indicated in Fig. 3, and secured to the face of the case as shown in Fig. 4. If you like, you can install a battery-mounting clip as shown in Fig. 4.

Operation

As can be seen from Fig. 2, there is no isolation between the input and output common terminals. Therefore, ALWAYS CONNECT YOUR VOM OR DMM TO THE OUTPUT TERMINALS BEFORE YOU CONNECT THE INPUT TERMINALS TO AN AC VOLTAGE.

The True RMS Converter is portable and easy to use. Simply connect the test leads of a VOM or a digital multimeter capable of reading zero to 200 millivolts to the output terminals, and connect a pair of insulated test probes to the input terminals. Connect the test probes to the voltage to be measured, and move the selector switch to the appropriate range so that a reading of at least 50 mV but no more than 500 mV is obtained. Then multiply the reading by the scale factor from Table 2 for the range in use. For inputs that are less than 50 mV, the AC-coupled mode will give the most accurate readings.

R-E

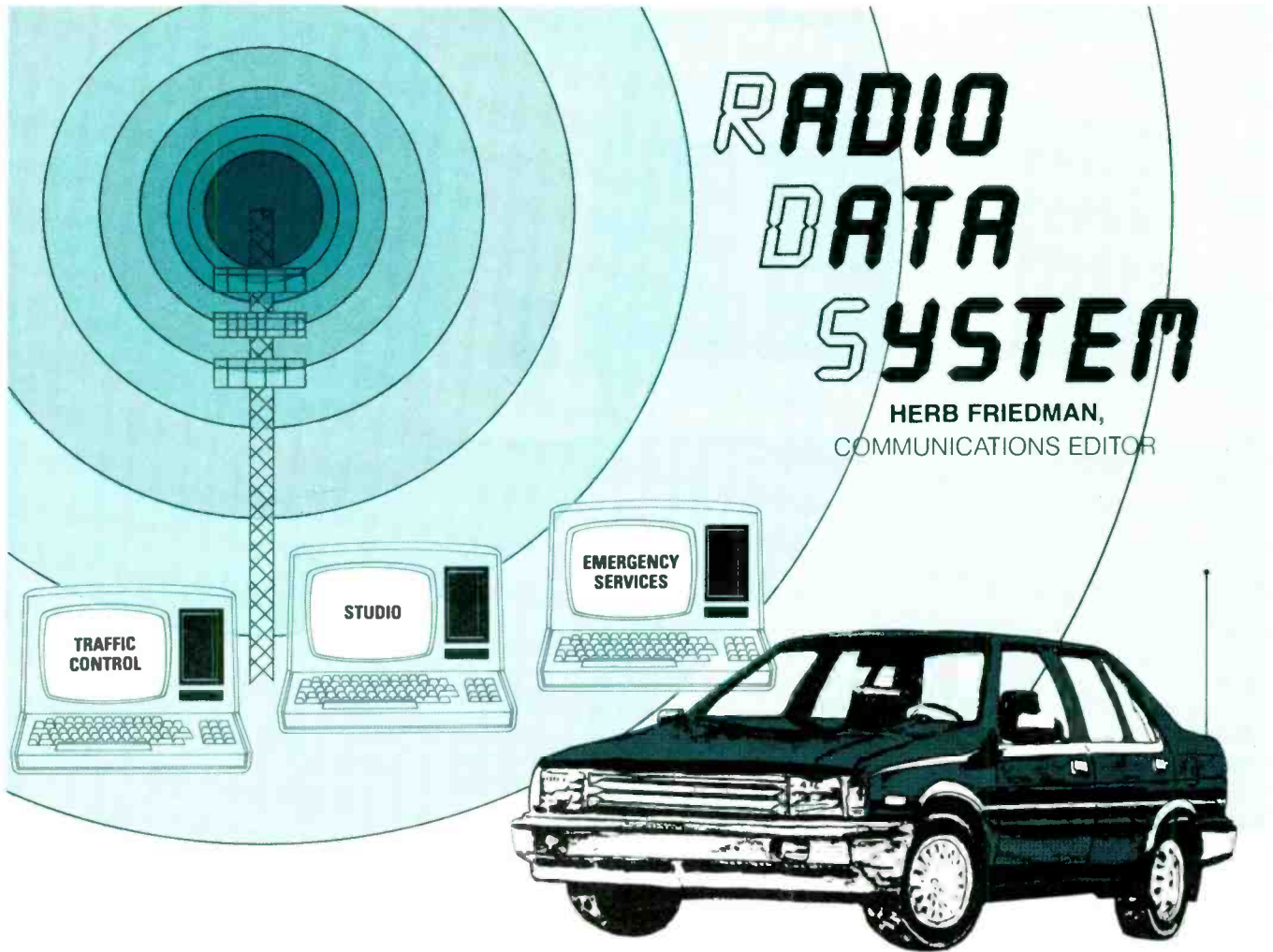

RADIO DATA SYSTEM

HERB FRIEDMAN,
COMMUNICATIONS EDITOR

A Radio Data System FM car radio can automatically locate the kind of programs you like, control the volume and frequency response, display a paging message, and even keep you informed of traffic conditions.

MOST FM LISTENERS, AND EVEN SOME technicians, do not know that many stations routinely use a subcarrier to carry digital data. The data itself might represent stock-market information, telemetry and remote-control signals for the FM transmitter, radiopaging messages, or even data representing computer programs and messages sent from a school system's headquarters to individual schools.

The fact of the matter is that by using digital data just about anything is possible; and it is extremely fast. At approximately 1200 baud, which is a reliable bit rate for FM broadcasting, a burp of data—sounding like nothing more than a blip of static—can convey enough information to satisfy many personal entertainment and safety needs.

And that's exactly what it's used for in Europe, where digital data broadcast on a conventional FM subcarrier is used to provide a driver with many wide-ranging services through his or her car radio.

Radio Data

The data system that we're talking about is known as RDS—which is derived from Radio Data System. Basically, RDS is a European-developed system for the co-transmission of digital data and conventional FM programming. It is presently estimated that all of Europe will be integrated into the RDS system in three to five years. Whether the idea travels across the Big Pond to our side of the world probably depends on the results of RDS experiments conducted in

Canada, because our FCC is not known as "Mister Speedy" when it comes to legitimizing new communication technologies.

Before we get into the bits, bytes, and code groups of the RDS subcarrier modulation, keep in mind that the system must not interfere with existing subcarrier services used in only a few European countries. Eventually, those services will be integrated into the RDS system; but today, RDS must exist side-by-side with services that preceded RDS.

As shown in Fig. 1, the European stereo-FM RDS signal closely resembles U.S. stereo signal that also has subcarrier modulation. The fact that the RDS subcarrier is at 57 kHz shouldn't disturb you because 57-kHz subcarriers are also used in the U.S.,

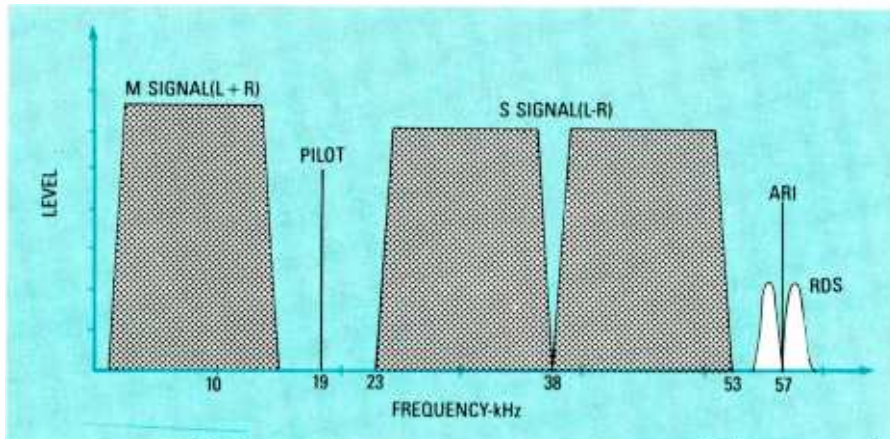


FIG. 1—THE RDS SIGNAL IS PLACED on a 57-kHz subcarrier. If the station also broadcasts an ARI auto-radio information signal on 57 kHz, the RDS signal is applied in quadrature so both can use the subcarrier.

even though a 67-kHz subcarrier is more common here. The Europeans selected 57 kHz because it's a multiple of the 19-kHz stereo pilot, which makes the subcarrier frequency easy to derive and phase-lock.

Note that the RDS 57-kHz subcarrier shows two distinct services: ARI and RDS. That is where "accommodating existing services" comes into play. ARI stands for *Auto Radio Information*; a system used in Germany and other countries to provide up-to-the-minute traffic information. (Actually, ARI stands for the German words that mean "auto radio information." Fortunately, the German and English words have the same initial characters—ARI.)

ARI works this way: The car radio constantly monitors the ARI subcarrier even if the driver is playing a tape. If the station broadcasts a subaudible frequency of approximately 10 Hz to 30 Hz, the tape program is interrupted by the radio so that the driver can hear traffic announcements made over the main channel by the station announcer. If the driver wants peace and quiet but wants to be kept up to date on traffic conditions, he can keep the volume turned down. Reception of an ARI signal automatically raises the volume so that the driver can hear the station's announcements and be aware of any emergency situations.

On the other hand, Sweden uses 57 kHz for its MBS national paging service. You can drive the entire 2000-mile length of Sweden and be paged if your radio is tuned to an FM station. (It is exactly the same as the cue nationwide radio paging system, which we covered in the January '88 issue of *Radio-Electronics*)

Multipath

In order to share the subcarrier with existing ARI 57-kHz subcarrier services in Austria, Germany, and Switzerland, the RDS modulation is applied in quadrature (90° out of phase) with the existing service. An RDS radio can use either quadrature signal. Unfortunately, although the quadrature method works almost exactly the same as our FMX stereo broadcasts, which were discussed in Larry Klein's *Audio Update* column in the June '88 issue of *Radio-Electronics*, quadrature RDS also suffers from the same kind of multipath interference that afflicted early FMX reception. Again, like FMX, multipath interference problems created by quadrature RDS is being reduced. Since, as we'll show, RDS can accommodate both traffic and paging digital data, when RDS is the sole ancillary FM communications system, the multipath problem won't exist because RDS will be the only signal using a 57-kHz subcarrier.

The quadrature modulation is the reason why Fig. 1 shows both the ARI and RDS services sharing the 57-kHz subcarrier. It does not show the Swedish MBS paging signal because that is not compatible with RDS. Sweden is developing an interim system where MBS and RDS will be implemented on individual radio networks. Eventually, MBS will be phased out, and paging will be integrated within RDS.

Digital info

Bear in mind that once we have a digitized source of information, any device associated with the digital data can be made intelligent; which means that the device is capable of making

decisions. In the case of RDS, the intelligent device is the car radio. And before we get into the nuts and bolts of RDS, let's take time out for a few whet-the-appetite examples of what's possible with an intelligent RDS car radio.

Intelligent is a broad term that covers anything and everything. The most recent RDS radios can be programmed on-the-fly by the user for certain functions, such as traffic-information reception, specific programming, etc. A super-intelligent radio—which is what is really envisioned, since an RDS radio has an on-board microprocessor—will resemble the functional block diagram shown in Fig. 2. Other than the power switch, and the manual tuning and volume controls, just about every feature and function can be determined, set, or varied by the digital signal received on the RDS subcarrier. For example, an RDS station might send a signal indicating whether they are broadcasting music or voice. The user can program the radio, through a keypad or other pushbuttons, to automatically raise the volume when music is broadcast, even optimize the radio's frequency response for speech or music, or for a particular kind of music.

If the RDS data signal indicates that speech is being broadcast, the data can be used by the radio's microprocessor to reduce the radio's audio-frequency response to the 250–7500 Hz range for maximum clarity. When the RDS data indicates that music is being broadcast, pre-programming by the user can cause the audio bandwidth to increase to 50–15,000 Hz, with or without Dolby decoding. It is even possible to use the RDS signal to indicate rock, wall-to-wall, or classical music, and then to adjust the radio automatically—for example, the volume level for the specific kind of music being broadcast.

On the other hand, the radio can be user-programmed so that if the RDS signal is an emergency announcement, the driver hears the emergency signal itself—a tone burst, or the volume is automatically increased to the threshold of pain.

User memory

As shown in Fig. 2, the receiver's microprocessor control is what makes both user and automatic feature/function control possible. But also note that the receiver has EPROM memory

and a voice synthesizer. In later RDS receivers, the user will be able to order a custom EPROM; one that is replaceable from the front panel. The first reason for the replaceable EPROM is obvious: The user can change features on demand. The second reason is not so obvious, but it is

ports. Figure 3-b shows the display if a message page, coded specifically for that radio, was received. Figure 3-c shows how the display might appear if a traffic-information bulletin were being transmitted, or scheduled to be transmitted. It might be accompanied by a warning tone; or the mes-

sage might override normal tape or radio reception, with the display serving only to tell the user what the message is about.

The user of an RDS car radio could accommodate possible variations in the RDS data, or a language barrier, by simply substituting the appropriate

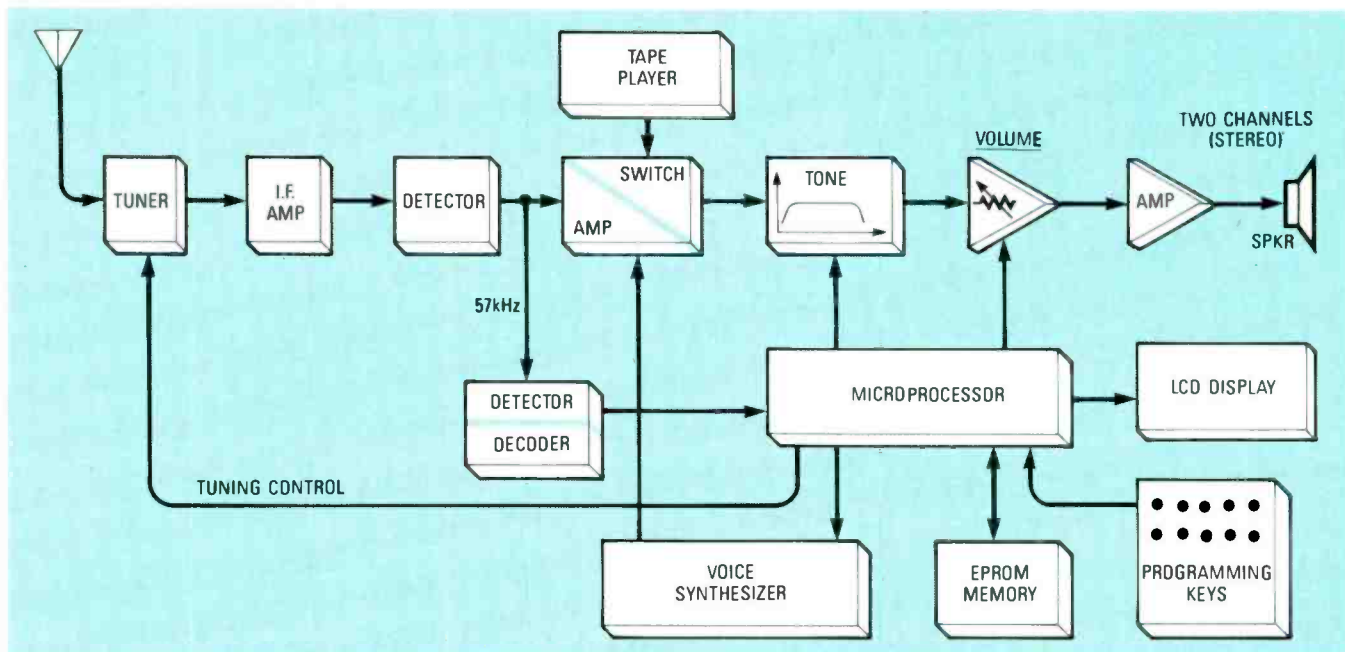


FIG. 2—THE FUNCTIONAL BLOCK DIAGRAM of a super-intelligent RDS receiver. The voice synthesizer allows an emergency or traffic bulletin to be heard in the listener's native language.

probably more important, particularly in Europe where an auto can easily be driven across three or four language borders in a single day.

The EPROM, in conjunction with the voice synthesizer, can be pre-programmed with standardized emergency and road-service phrases in the driver's native language. That means that an RDS signal can force the voice-synthesized announcement to override or replace a received signal, or even a tape playback, with emergency broadcast announcements or a personal-paging message. Either way, regardless of the country of origin of the RDS signal, the driver hears the emergency announcements or the page *in his own language*.

Also, the message or page might be shown on the radio's LCD display. In Fig. 3 we use a conventional RDS receiver to illustrate the kind of display that might be attained on a super-intelligent RDS radio. Figure 3-a shows how the display would appear during the microprocessor's programming if the user wanted the radio to tune only stations broadcasting

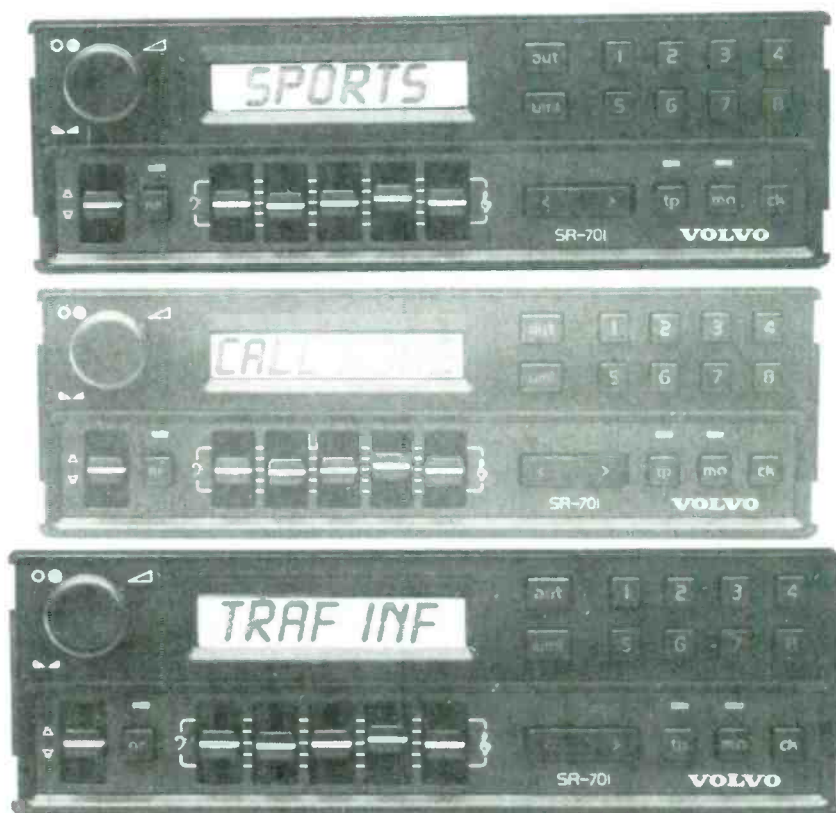


FIG. 3—THE DISPLAYS MIGHT INDICATE: a) the kind of station that the listener wants tuned in; b) a personal paging message; c) traffic information.

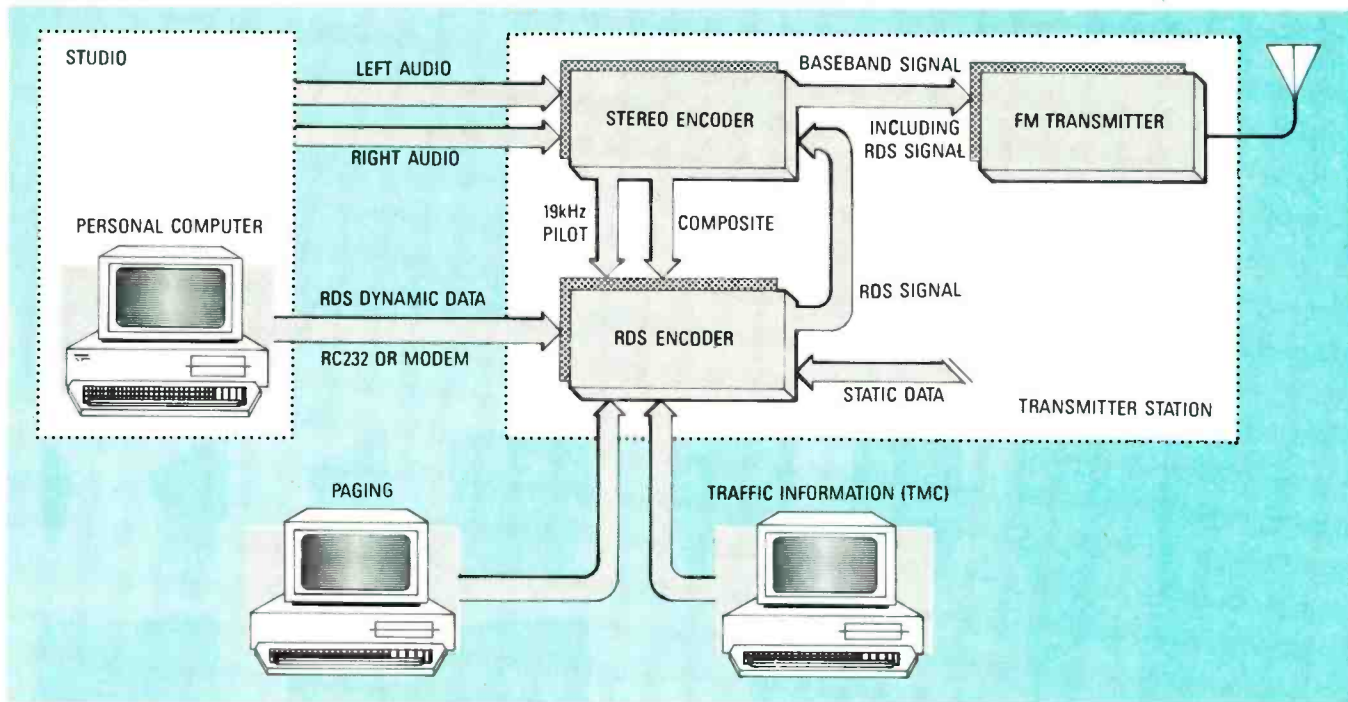


FIG. 4—RDS INFORMATION CAN ORIGINATE from ROM's as static (permanent) data, or from individual computer sources as dynamic data.

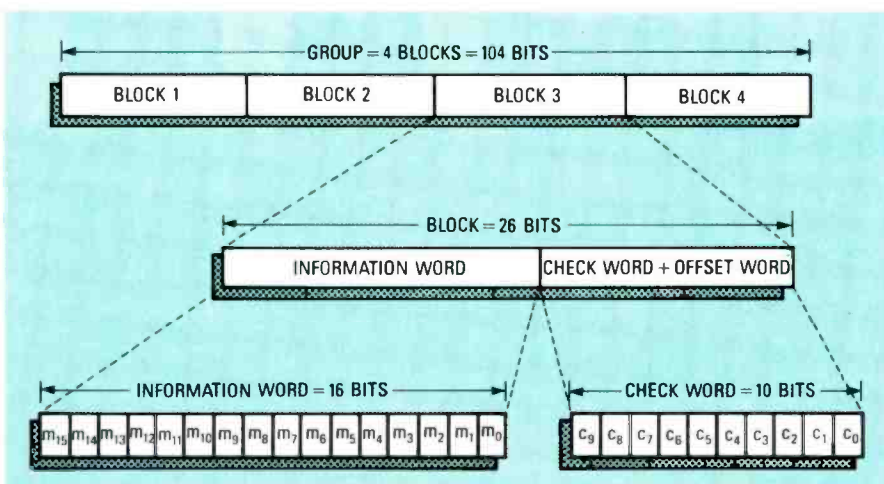


FIG. 5—THE RDS DATA IS TRANSMITTED in groups of 104 bits. Each group consists of four 26 bit blocks. Each block uses 16 bits for information, 10 bits for error-checking. The effective information transmission-rate is 730 bps.

EPROM when the car crossed a country's border. For example, imagine that you're traveling in Italy, the language of which you have little knowledge other than a few words such as pizza and manicotti. You're tooling your Fiat up the Appian Way while listening to your travel-tape of Bruce Springsteen on the car stereo, when suddenly "The Boss" is interrupted by an emergency travel advisory—given in perfect, though computerized English. And while you're hearing the travel bulletin in English, French tourists are hearing the same

bulletin in French, and in another car, filled with visitors from Japan, they are hearing the same bulletin, at the same time, in Japanese.

If user-exchange of the EPROM is needed because you intend to drive through many countries, you simply rent a car having an RDS radio that speaks your language. If you own the car, the voice synthesizer will, of course, be in your native language.

An RDS emergency-announcement uses the same digital code regardless of the country of origin, although there might be exceptions to

handle unusual conditions. For example, it is more likely that the digitized phrase *M1 motorway* rather than *Appian Way* is pre-programmed for car radios intended for Great Britain; while *autobahn* would be used in German radios. To handle unusual traffic conditions, the voice synthesizer might simply contain the equivalent of "Ho Boy! You drivers in the south of England (or wherever) are in for massive tie-ups, so pay attention to local officials."

Static and dynamic

RDS data can be either static or dynamic. Static data can be the station's I.D., automatic time and clock correction (as you drive through different times zones the radio's clock is automatically corrected), the network affiliation, the kind of program being broadcast, etc. For example, in Sweden you can drive 2000 miles and have an RDS radio track the same program even as you drive out of the range of one station into the reception zone of another. If programmed to a particular service or program, such as *sports*, the radio continually searches out the RDS data representing that service or program—automatically adjusting the radio's tuning to the appropriate local station.

Dynamic data is RDS information
continued on page 76

WORKING WITH A NORTON OP-AMP

MOST OPERATIONAL AMPLIFIERS ARE Voltage-Differencing Amplifiers, or VDA's, which have an output that is proportional to the difference between the voltages applied at the two input terminals. But the LM3900 is a Current-Differencing Amplifier, or a CDA; it is also known as a *Norton* op-amp. The device has an output that is proportional to the difference between the currents applied at the two input terminals.

The LM3900, first introduced in the early 1970's, was specifically designed as a low-cost, medium-performance, quad op-amp that could operate off a single-ended power supply and provide a large output-voltage swing. It is the most widely known CDA-type op-amp, containing four identical and independently accessible op-amps, as shown in Fig. 1. The device can operate with any DC supply from 4 + -46 volts, and each op-amp has a unity-gain bandwidth of 2.5 MHz and an open-loop gain of 70 dB.

Basic principles

The LM3900 incorporates four identical op-amps, each having the circuit shown in Fig. 2. To help you understand how that circuit works, it is broken down into four simple stages in Fig 3.

Figure 3-a shows the basic inverting-amplifier circuit. Transistor Q1 is a common-emitter amplifier with a constant-current collector load, providing high-gain inverting action. Transistor Q2 is a non-inverting emitter-follower output buffer with a constant-current emitter load. The upper-frequency response of the resulting high-gain non-inverting amplifier is rolled off by C1 to enhance circuit stability. Note that the output can swing within a few hundred millivolts of ground and the supply voltage.

The overall current gain of the Fig. 3-a circuit is limited to the product of the two individual transistor current gains. Fig. 3-b shows how the current gain can be further increased, with little reduction in the output-voltage swing, by adding transistor Q3.

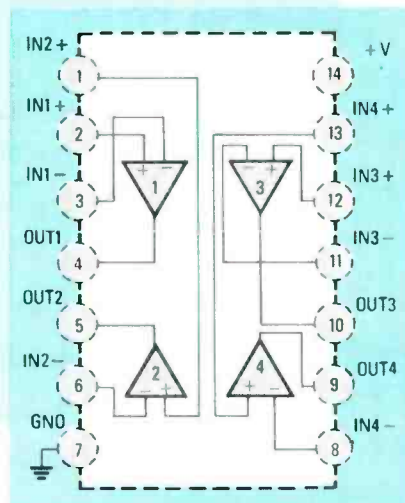


FIG 1—THE LM3900 NORTON OP-AMP contains four identical and independently accessible amplifiers.

The output from the circuit in Fig. 3-b can typically source up to 10 mA, but can sink only 1.3 mA (via the constant-current generator of Q2). Figure 3-c shows how the sink current can be increased by adding Q4, providing class-B operation during the over-drive condition. Also, transistors Q5 and Q6 are used as constant-current generators, which are biased by an internal network in the LM3900 IC.

The circuit in Fig. 3-c is the basis of each of the LM3900 amplifier stages, but it can only provide inverting action. The non-inverting action of the LM3900 is provided by the addition of the current-mirror circuit in Fig. 3-d. That circuit is made up of two identically matched transistors and will draw an output current that is almost identical to the input current. The circuit operates as follows:

The input current to the circuit in Fig. 3-d is applied to the base of each transistor. Suppose that both transistors have current gains of 100, and that both transistors draw base currents of 5 μ A. In that case, the collectors of both transistors will draw 500 μ A. Note, however, that the collector current of Q7 is drawn from the cir-

This month we explore the mysteries of the LM3900 op-amp, and show the many ways of using this versatile device.

RAY MARSTON

cuit's input current, and equals 500 μ A plus ($2 \times 5 \mu$ A), or 510 μ A, and that the collector current of Q8 is the output or *mirror* current of the circuit. The input and output currents are almost identical, regardless of the input-current magnitude.

Finally, if we connect the current-mirror circuit in Fig. 3-d to the circuit in Fig. 3-c, we have the circuit in Fig. 2, where the mirror circuit is driven by the non-inverting input terminal, and the mirror current is drawn from the inverting-input terminal, which is also connected directly to the base of the Q1 amplifier stage. Consequently, the base current of Q1 is equal to the input current at the inverting input, minus the input current at the non-inverting input. The complete amplifier (Fig. 2) thus provides CDA action already mentioned. Note that CDA's can operate like conventional VDA's by wiring high-value resistors in series with the input terminals, so that the input currents are directly proportional to the input-voltage/resistor values.

The output of an LM3900 amplifier will start to swing down through the half-supply point (half of the supply voltage) when the input-bias current

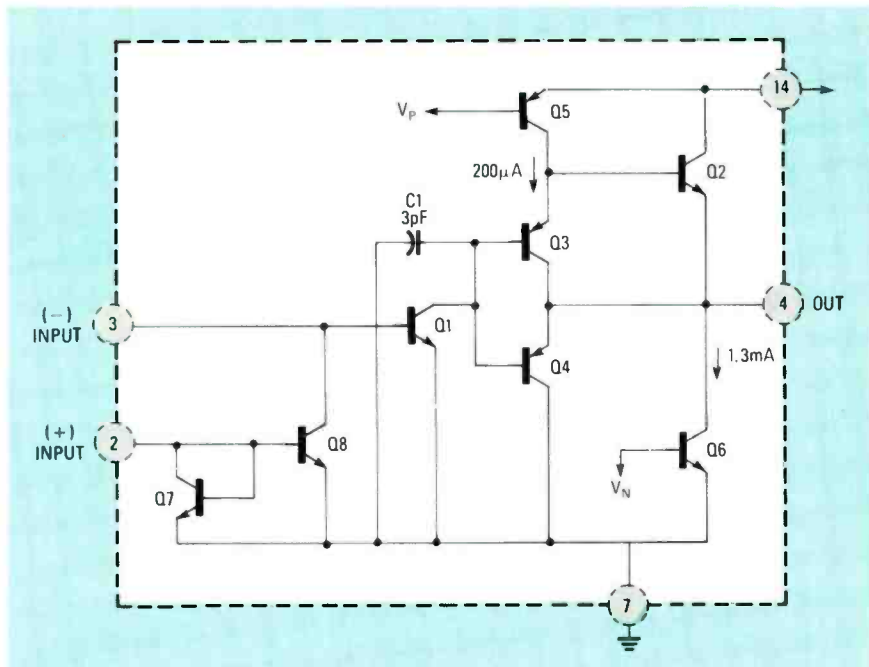


FIG 2—THE CIRCUITRY for each of the four op-amps inside the LM3900 looks like this.

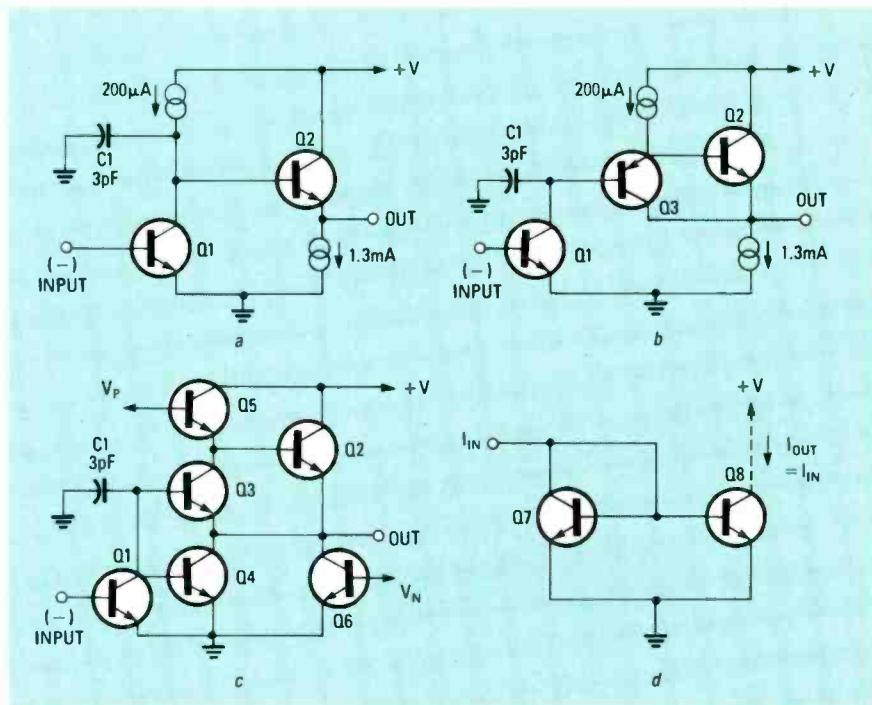


FIG 3—THE BASIC INVERTING AMPLIFIER is shown in a, and an improved inverting amplifier is shown in b. Constant-current generators have been added in c, and the current-mirror circuit is shown in d.

of Q1 rises above 30 nA or so. The input-bias current is normally equal to the difference between the two input-terminal currents, and those currents should normally be restricted to the range from 0.5 μ A to 500 μ A.; an ideal value for the input-bias current of an LM3900 amplifier is usually around 10 μ A.

Linear amplifier circuits

In linear applications, an op-amp is normally biased so that its output takes on a quiescent value of half of the supply voltage to accommodate maximum undistorted signal swings. Also, when an op-amp is biased for linear operation, its output is proportional to its input. The feedback cur-

rent automatically limits the internal Q1 base current, providing a closed-loop gain. In Fig. 4, R1, R2, and C1 generate a decoupled half-supply reference voltage, which applies a reference current to the non-inverting terminal via R3. Also, a negative-feedback current is applied to the inverting terminal via R4, from the op-amp's output.

In Fig. 5, R2 and R3 bias the output to a quiescent half-supply value. The input signal is applied to the inverting

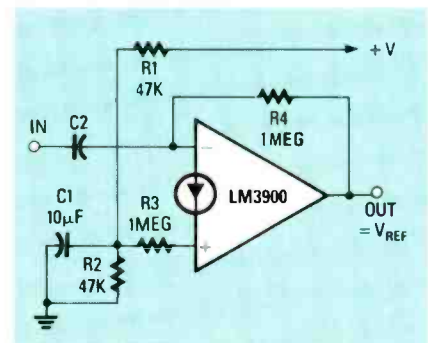


FIG 4—AN OP-AMP CAN BE BIASED so that its output takes on a quiescent value of half of the supply voltage.

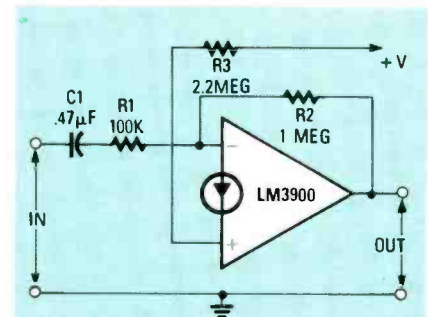


FIG 5—THIS INVERTING AC AMPLIFIER uses supply-line biasing.

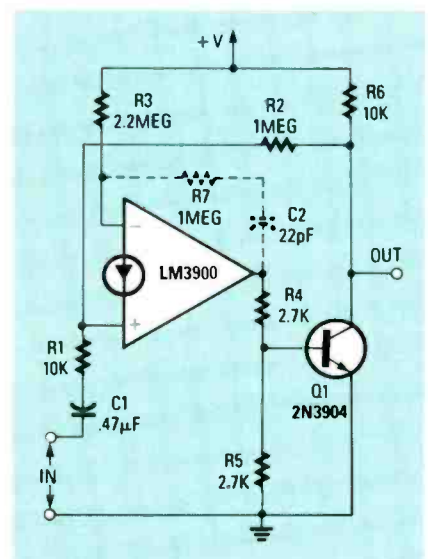


FIG 6—AN IMPROVED BANDWIDTH and high gain are featured in this circuit.

terminal via R1, and the voltage gain is determined by the R2/R1 ratio, so that circuit is set up as a $\times 10$ inverting amplifier.

The op-amps of the LM3900 have slew rates of only $0.5\text{V}/\mu\text{s}$, so they have very restricted useful bandwidths. Figure 6 shows how the useful bandwidth can be increased by connecting a transistor to the output and rearranging the input connections of the standard amplifier circuit to make a $\times 100$ inverting amplifier with a 200-kHz bandwidth. Because of the high overall gain, that circuit may be somewhat unstable. If so, R7 and C2 can be added to slightly reduce the bandwidth and improve overall circuit stability.

The circuit in Fig. 6 can be modified to have a peak-to-peak output swing of 150 volts. That is done by supplying the output transistor with a separate supply of 150 volts DC. The output will then take on a quiescent value of 75 volts, causing $7.5\ \mu\text{A}$ to be fed to the non-inverting terminal of the op-amp. Therefore, in order to have correct biasing, $7.5\ \mu\text{A}$ would also have to be applied to the inverting input.

The LM3900 op-amp can be used as a unity-gain non-inverting buffer amplifier, or voltage follower. That is done by connecting the output to the inverting input with a 1-megohm resistor, and applying the input signal to the non-inverting terminal via an equal-value resistor; that way the circuit will provide unity gain.

Schmitt triggers

The LM3900 op-amp can be used as a voltage comparator by wiring equal-value current-limiting resistors in series with each input, using one resistor as the input, and the other as the sample input. The circuit in Fig. 7 is an inverting voltage comparator, in which the output switches high when V_{IN} falls below V_{REF} .

The circuit in Fig. 7 could also be used as a non-inverting voltage-comparator. That would be done by applying V_{REF} to the inverting input and V_{IN} to the non-inverting input. The output will then switch high when V_{IN} rises above V_{REF} .

The circuit in Fig. 7 can supply output currents of only a few mA. However, the output current can be boosted to tens or hundreds of mA by connecting a transistor to the circuit's output.

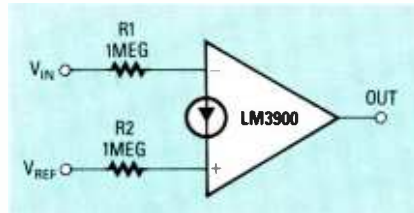


FIG 7—THE CIRCUIT SHOWN HERE is an inverting voltage comparator.

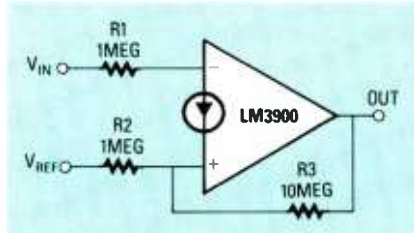


FIG 8—THE CIRCUIT SHOWN HERE is an inverting Schmitt trigger.

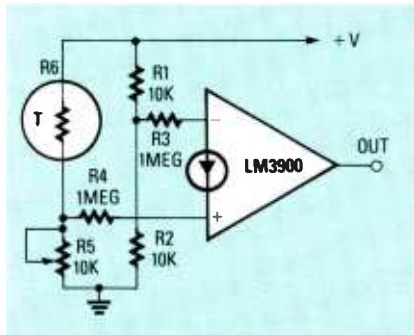


FIG 9—AN OVER-TEMPERATURE SWITCH will trigger its output when a pre-determined temperature is exceeded.

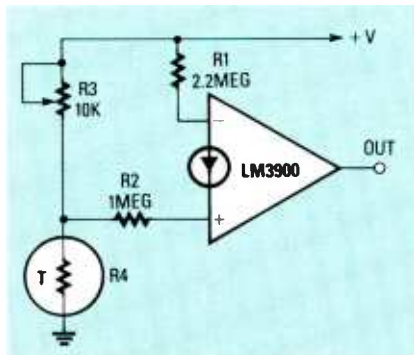


FIG 10—AN UNDER-TEMPERATURE SWITCH will trigger its output when the temperature falls below a predetermined value.

Hysteresis can easily be added to LM3900 voltage-comparator circuits so that they operate as Schmitt triggers. That is done by connecting a high-value resistor between the output and the non-inverting terminal. Figure 8 is an inverting Schmitt trigger, in which the R3/R2 ratio determines the hysteresis magnitude. The circuit becomes a non-inverting Schmitt trigger by transposing the inputs.

Comparator applications

Figures 9–12 show some useful applications for voltage comparators. The circuit in Fig. 9 is an over-temperature switch, where the output goes high when a pre-set temperature is exceeded. A fixed half-supply reference voltage feeds a reference current to the inverting input, and a variable current is fed to the non-inverting input. Resistor R6 is a Negative-Temperature-Coefficient (NTC) thermistor, so the potential at the junction of R5 and R6 rises with temperature. The op-amp will switch high when that voltage exceeds the half-supply value. The trip temperature can be pre-set via R5.

Figure 10 is an under-temperature switch. In that circuit the reference current is fed from the supply voltage via R1, to the inverting terminal, and the variable (non-inverting) current is

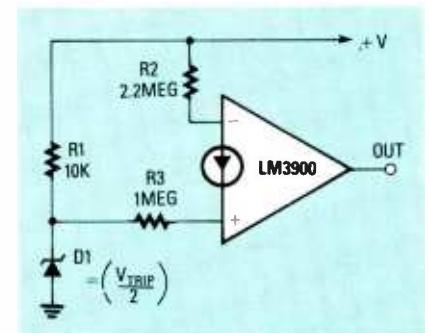


FIG 11—AN UNDER-VOLTAGE DETECTOR can be used to monitor a voltage supply.

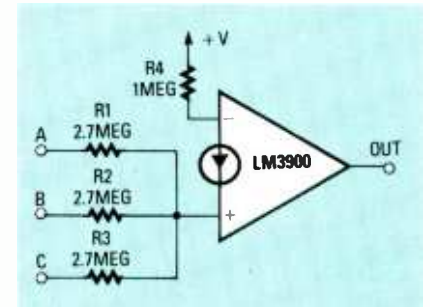


FIG 12—A 3-INPUT and GATE can be converted to a NAND gate by transposing the two inputs.

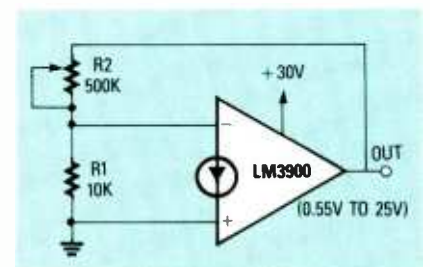


FIG 13—SIMPLE VARIABLE-VOLTAGE reference circuit uses the voltage at its inverting terminal as a reference.

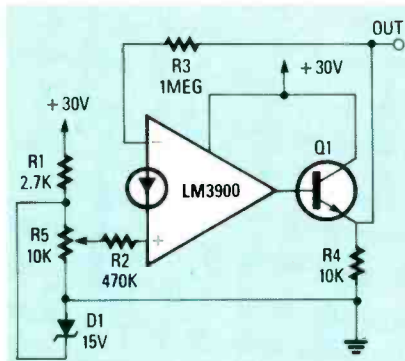


FIG 14—THIS VARIABLE-VOLTAGE REGULATOR has a boosted-current output.

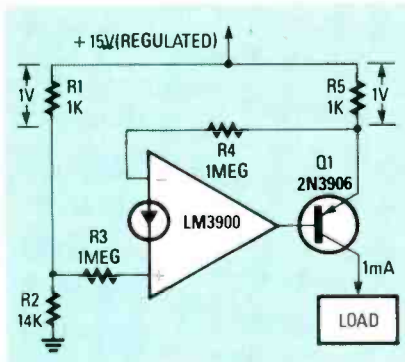


FIG 15—FIXED-CURRENT SOURCE can deliver 1 mA to any load that is from 0 to 14 kilohms.

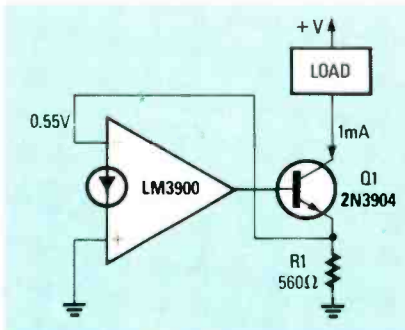


FIG 16—A SIMPLE 1-mA CURRENT SINK will draw 1 mA from any load.

supplied from the junction of R3 and R4. Since the value of R1 is approximately double that of R2, and generates a current that is proportional to the supply voltage, the trip temperature (pre-set via R3) is independent of the supply voltage.

An under-voltage detector is shown in Fig. 11. Its output goes high when the supply falls below a value determined by Zener diode D1. If D1 is a 5.6-volt Zener, the op-amp will switch high when the supply voltage falls below approximately 11 volts. The precise trip point can be varied by replacing R3 with an 820K resistor in series with a 470K potentiometer.

Finally, Fig. 12 shows how a comparator can be used as a 3-input AND gate, having a high output only when all three inputs are high. The non-inverting-input current, when all three inputs are high, must exceed that of the inverting input, as determined by R4. The circuit can be converted to a NAND gate by transposing the two inputs of the op-amp.

Voltage-regulator circuits

There are various applications that can make use of the LM3900 as a voltage regulator or reference. Figure 13 is a variable-voltage reference source. The non-inverting terminal of the op-amp is grounded, and the circuit uses the voltage at the inverting terminal as a reference. Its voltage gain is determined by the R2/R1 ratio. When R2 is set at zero, the circuit has unity gain and a 0.55-volt output. When R2 is set to the maximum value, the circuit has a gain of 50 and an output of about 25 volts. The circuit provides good regulation and can supply output currents of several mA. The output voltage however, is not temperature compensated.

Figure 14 is a variable voltage regulator. The op-amp is wired as a $\times 2$ non-inverting DC amplifier with a gain that is determined by the R3/R2 ratio. The input voltage to the op-amp

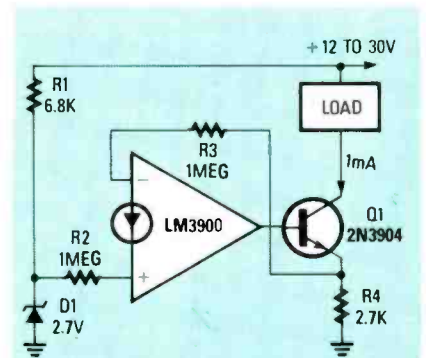


FIG 17—AN IMPROVED CURRENT SINK with a fixed reference of 2.7 volts.

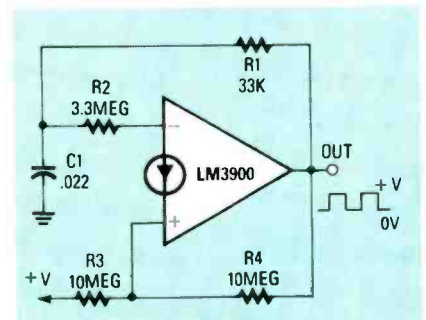


FIG 18—A 1-kHz SQUARE-WAVE generator can be used as a tone generator.

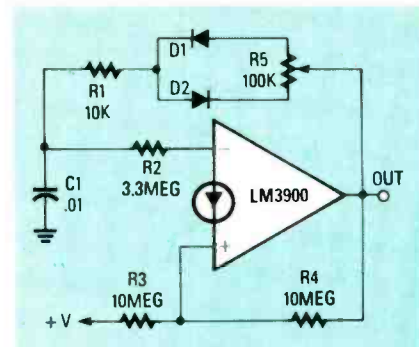


FIG 19—THIS CIRCUIT is a variable duty cycle square-wave generator.

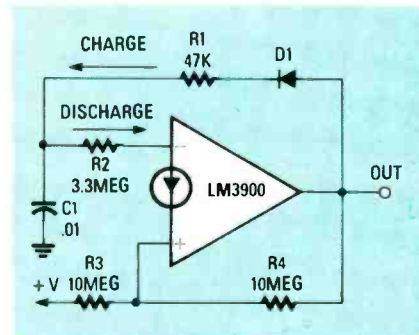


FIG 20—THIS PULSE GENERATOR has a duty cycle of about 1:60.

is variable between 0 and 15 volts via R5. The output voltage is therefore variable over the approximate range from 0.5–30 volts. The available output current has been boosted by adding transistor Q1 to the output.

Current-regulator circuits

The LM3900 can be used as a fixed-current regulator. Figure 15 is a fixed 1-mA current source, which delivers a fixed current to a load connected between Q1's collector and ground; the load can be anywhere in the range from 0 ohms to 14 kilohms. The circuit is powered from a regulated 15-volt supply, and the R1-R2 voltage divider applies a 14-volt reference to R3. The op-amp's output automatically adjusts to provide an identical voltage at the junction of R4 and R5. That produces 1 volt across R5, resulting in an R5 current of 1 mA. Since that current is derived from Q1's emitter, and the emitter and collector currents of a transistor are almost identical, the circuit provides a fixed-current source. The output current can be doubled by halving the value of R5.

Figure 16 shows a simple 1-mA current sink, in which a fixed current flows through any load connected be-

continued on page 76



Plug a Friend into Radio-Electronics this Christmas ... and Save \$11!

This Christmas give an electrifying gift ... plug a friend into Radio-Electronics and brighten his whole new year! Whether electronics is his livelihood or his hobby, your gift will sharpen his focus and illuminate the whole spectrum of electronics throughout the coming year.

Radio-Electronics will keep him informed and up-to-date with new ideas and innovations in all areas of electronic technology ... computers, video, radio, stereo, solid state technology, satellite TV, industrial and medical electronics, communications, robotics, and much, much more.

He'll get complete plans and printed circuit patterns for building valuable test equipment and electronic devices for home and car — practical money-savers like these ... a TV signal descrambler ... a video test generator ... an auto exhaust analyzer ... a clockboard for his PC ... a radio commercial zapper ... a solid state barometer ... a working robot ... and many others!

PLUS ... equipment repair and troubleshooting ... circuit design ... new

product news and buyer's guides ... service clinics ... equipment test reports ... a special "Computer Digest" section ... regular columns on video, stereo, radio, circuits, solid state, satellite TV and robotics ... and lots more exciting features and articles.

SAVE \$11 ...OR EVEN \$22 ... For each gift of Radio-Electronics you give this Christmas, you save a full \$11.00 off the newsstand price. And as an R-E gift donor, you're entitled to start or extend your own subscription at the same Special Holiday Gift Rate — you save an additional \$11.00!

No need to send money ... if you prefer, we'll hold the bill till January, 1989. But you must rush the attached Gift Certificate to us to allow time to process your order and send a handsome gift announcement card, signed with your name, in time for Christmas.

So do it now ... take just a moment to fill in the names of a friend or two and mail the Gift Certificate to us in its attached, postage-paid reply envelope. That's all it takes to plug your friends into a whole year of exciting projects and new ideas in Radio-Electronics!



RADIO DATA SYSTEM

continued from page 68

that is usually input, when needed, from personal computers located at various locations. Figure 4 shows how both static and dynamic data are integrated. The stereo encoder provides a sample of the 19-kHz pilot signal to the RDS encoder for phase-locked generation of the RDS subcarrier. The static data is input to the encoder, as is dynamic data from three independent sources: (1) local announcements from the radio station's studio; (2) paging data from a paging service; (3) emergency and traffic information from the local safety officials (police, fire, etc.).

Actually, to avoid a clash of data if several dynamic sources decide to operate at the same time, all RDS data sources generally pass through some kind of automatic polling or sequencing master-control facility. Also, the master control does not allow an individual operator to create interference to an RDS data source to which he does not have access. In other words, if the master control allows the public-safety computer to give its data precedence by immediately seizing the RDS system, other operators cannot override, delay, or interfere with the public-safety data; nor can they interfere with the paging data, etc. The protection is attained by tagging incoming data with its source or origin, so that the master control knows what signal is coming from where, and its order of precedence.

Data groups

As shown in Fig. 5, RDS data is transmitted in groups of 104 bits divided into four 26-bit blocks. Of the 26 bits, which are transmitted at 1187.5 bps (bits-per-second), the first 16 bits represent information, the remaining 10 bits are checks for error protection. Therefore, the effective information bit-rate $1187.5 \times 16/26$, or 730 bps.

RDS provides for individual identified groups, such as 0A, 0B, 7A, and 15B. The system requires that specific data be placed in specific groups and blocks so that no station creates a Tower of Babel by going its own way. For example, Swedish paging, which allows up to 18 characters per pager, must be in group 7A, while decoder information, which provides informa-

tion on mono/stereo transmission and special noise reduction or encoding is found in groups 0A, 0B, and 15B. A station's program service data, a maximum of 8 ASCII characters (for LCD display) must be transmitted at least once each second on groups 0A and 0B.

Various services and future expansion is built into the group assignments; for example, a 5-bit channel code representing computer-program normal text can be placed in groups 5A and 5B; the music/speech identification bit that enables the radio to switch between two volume levels or tone-control adjustments is transmitted four times per second in groups 0A, 0B, and 15B; the station's automatic telemetering and remote-control signals can be in groups 6A and 6B. It is even possible, within groups 2A and 2B, to display up to 64 characters for say, a program parade (schedule), or program information such as "Verdi - *La Traviata*."

As you can see from the few previous examples, each group can contain the data for several functions because the data can utilize the individual group blocks.

Why not here?

To say that Europe is rushing pell-mell toward total implementation of the system would be an understatement, because almost everything coming from Europe that concerns communications mentions RDS and when it will be totally implemented on a country-by-country basis. The question we should ask is why RDS stops at Land's End in Europe. The U.S. is 3000 miles wide, and while we don't have contiguous government-controlled radio networks that allow the tracking of a single broadcast from coast to coast, and while we also don't have a single paging system, certainly all the other RDS functions would be the ideal thing for the average autosound enthusiast. Its an idea whose time and technology came a long time ago in the U.S. In fact, the equipment is here; the encoding-equipment manufacturer, RE Instruments Corp. (31029 Center Ridge Road, Westlake, OH 44145), has encoding units here that they use for demonstration. It really would be an advantage to the consumer if the FCC allowed FM communications to get ready for the 21st century—it's almost here. **R-E**

NORTON OP-AMP

continued from page 72

tween the positive supply and Q1's collector. The non-inverting terminal of the op-amp is grounded, and negative feedback flows between the output of the circuit (Q1's emitter) and the inverting terminal. The voltage across R1 is thus equal to the voltage at the inverting terminal (approximately 0.55 volt), so a fixed current of about 1 mA flows through the load, Q1's emitter, and R1.


Figure 17 shows another type of current sink, in which the op-amp has a fixed reference of 2.7 volts applied to the non-inverting terminal via R2. Consequently, the circuit automatically adjusts to generate 2.7 volts across R4, which has a value of 2.7K; therefore 1 mA flows through the emitter and collector of Q1

Waveform-generator circuits


Figure 18 is a 1-kHz square-wave generator. When the output is high, R3 and R4 are in parallel, and C1 charges via R1 until the current in R2 equals that the non-inverting terminal. That occurs when C1's voltage rises to $\frac{2}{3}$ of the supply voltage. At that point the circuit switches regeneratively. The output switches low and C1 starts to discharge via R1. Now R4 is effectively disabled and the current to the non-inverting terminal is determined solely by R3, so C1 discharges until the current through R2 falls slightly below that of R3. That happens when the voltage across C1 falls to about $\frac{1}{3}$ of the supply voltage. At that point the circuit again switches regeneratively, and the output again goes high.

The circuit in Fig. 18 is useful for generating symmetrical square waves with maximum frequencies of only a few kHz. And, because of the poor slew-rate characteristics of the LM3900 ($0.5V/\mu s$), the output waveforms have rather slow rise and fall times. In the circuit in Fig. 19, C1 alternately charges via R1-D1 and the upper half of R5, and discharges via R1-D2 and the lower half of R5. The duty cycle can be varied over the range from 1:10 to 10:1 via R5.


Figure 20 is a free-running pulse generator. In that circuit C1 alternately charges via R1-D1 and discharges via R2, producing a duty cycle of about 1:60. **R-E**

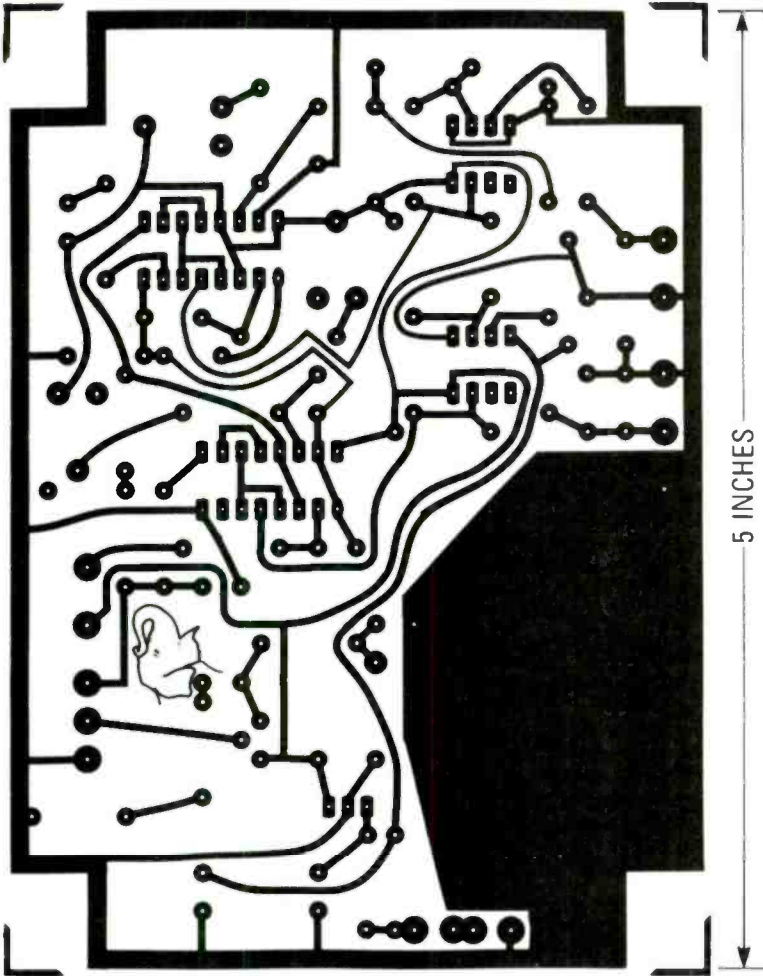

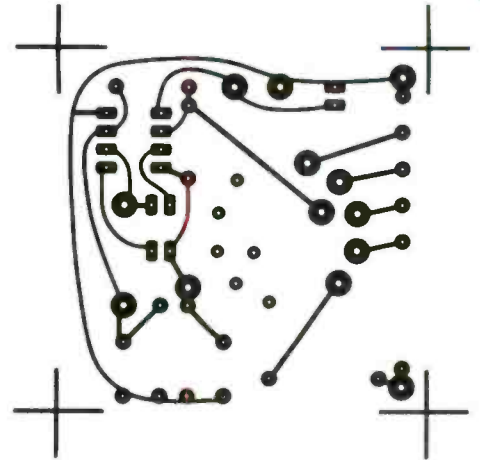
THE GATED SYNC experimenter's descrambler board.



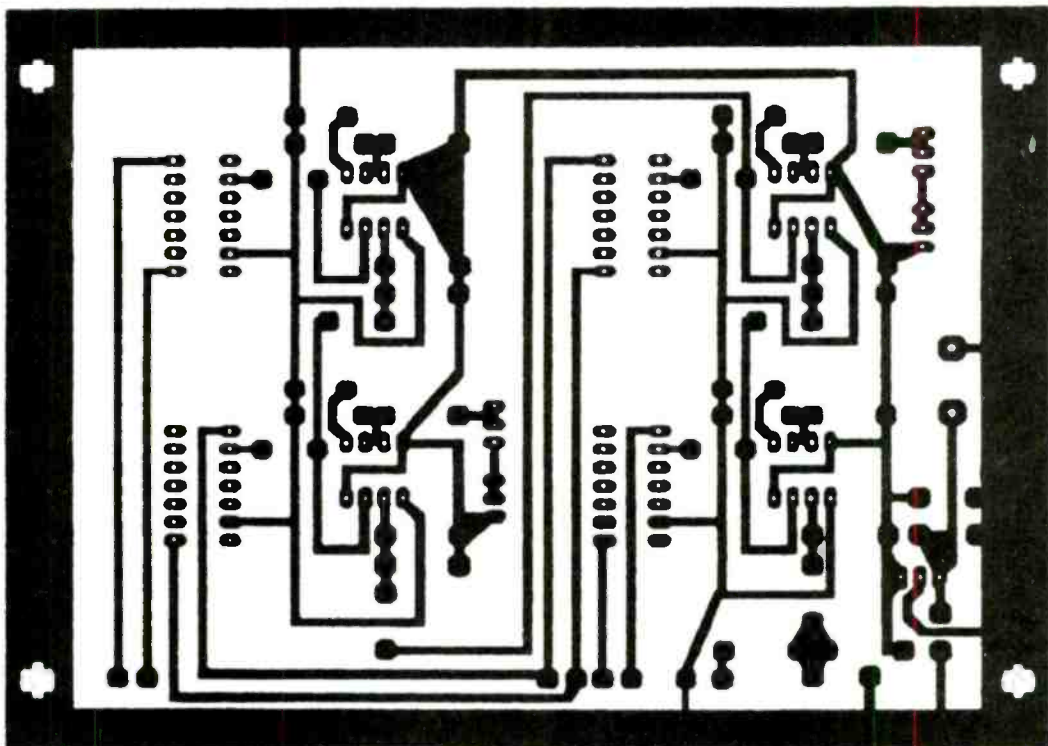
YOU CAN BUILD the RMS adapter using this foil pattern.



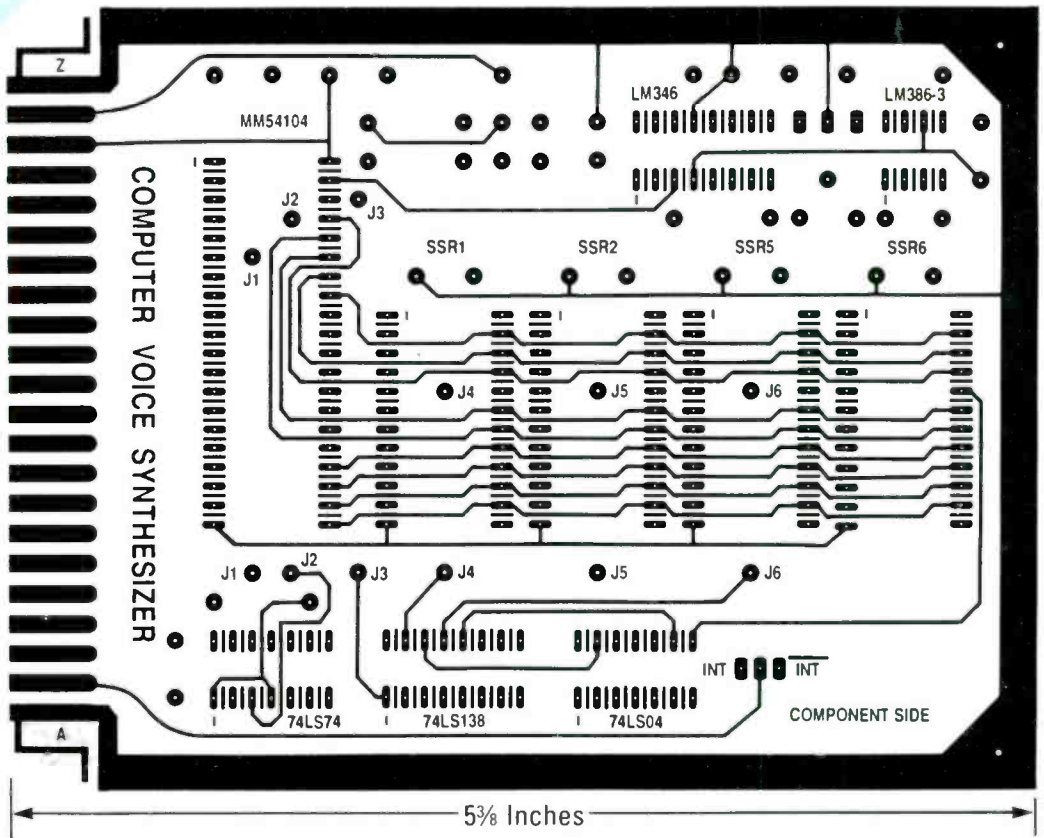FULL SIZE FOIL PATTERN for the video-edit controller.



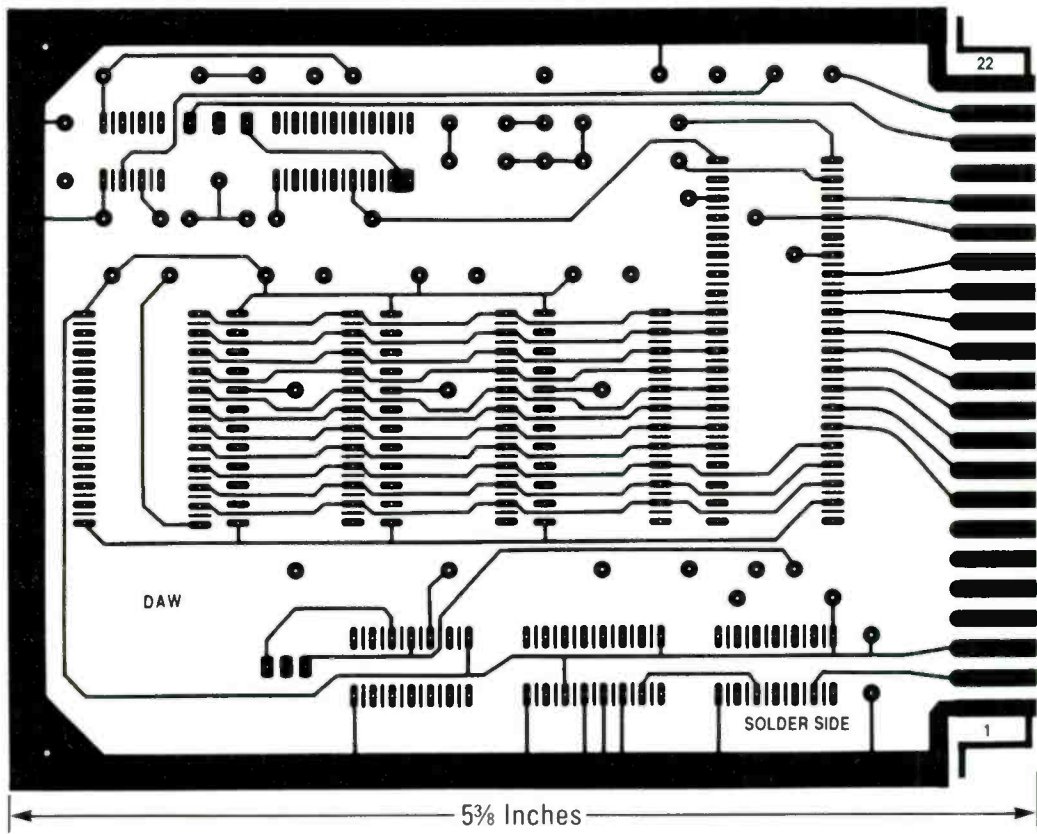THE COMPONENT SIDE of the voice-synthesizer board.



THE SOLDER SIDE of the voice-synthesizer board.

A NEW KIND OF MAGAZINE FOR ELECTRONICS PROFESSIONALS

BUILD A SPEECH SYNTHESIZER

Teach any computer to talk.

Page 80



ASSEMBLY LANGUAGE PROGRAMMING

Programming the 68000

Page 86

BUILD THIS



SPEECH SYNTEHSIZER

DAVID A. WARD

Computerized voice synthesizers are turning up everywhere. Perhaps you've heard one at the grocery store check-out stand, in an automobile, or from an educational toy. Other uses include text-to-speech converters for the visually impaired, talking clocks, calculators, radar detectors, chess and other games, blood-sugar and pressure-monitoring devices, and automotive test equipment.

It's a lot of fun experimenting with voice synthesizers; in fact, the author has built and experimented with four different voice synthesizer IC's, and has listened to at least ten different synthesizers in all.

So that you can share in the fun too, we'll present theory and construction details of a stored-word speech system that you can connect to any personal computer

having a parallel printer port. A simple BASIC program then uses LPRINT statements to create speech output. A number of terms relevant to electronics are included: ampere, kilo, milli, volt, circuit, connect, farad, hertz, meg, mega, micro, nano, ohms, pico, as well as letters of the alphabet, numbers, and numerous others. The project can be built for about \$75.

Speech systems

Most speech synthesis systems operate in one of two ways: the stored-speech method or the allophone method. The allophone method uses *allophones*, little chunks of sound that can be combined to form words. The stored-word system stores entire words and phrases.

Each system has advantages and disadvantages. Allophone synthesis can offer an unlimited vocabulary and yet require very little memory. However, allophone speech synthesis is usually artificial sounding, monotone, and difficult for the untrained ear to understand. Probably the best application for allophone synthesis is in converting text to speech. Text-to-speech conversion can be a great aid for the visually impaired, allowing them to operate word processors and other computer programs.

By contrast, a stored-word synthesizer can offer excellent speech quality with intonation or feeling. However, a stored-word system requires tremendous amounts of memory for just a few minutes of speech. Typically, that limits a stored-word system to a vocabulary of several dozen words. The best application for a stored-word synthesizer is one that requires the clearest possible speech and a limited vocabulary, such as in an automobile, or a supermarket check-out stand. A stored-word

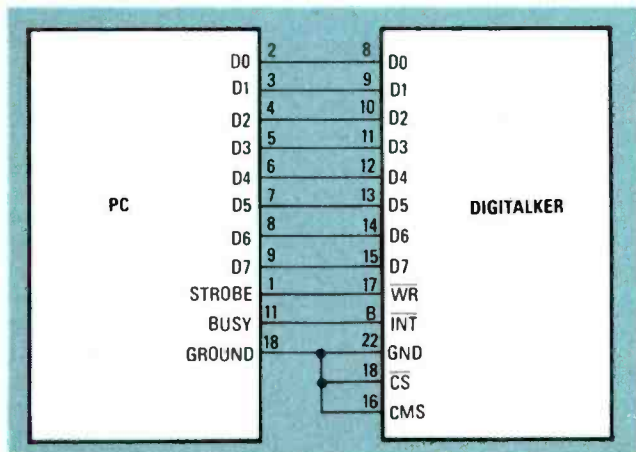


FIG. 1—THE PARALLEL PRINTER PORT of any personal computer can drive the Digitaltalker.

TABLE 1—WORD LIST (SSR1 AND SSR2)

THIS IS	0	Q	48	IS	96
DIGITALKER	1	R	49	IT	97
ONE	2	S	50	KILO	98
TWO	3	T	51	LEFT	99
THREE	4	U	52	LESS	100
FOUR	5	V	53	LESSER	101
FIVE	6	W	54	LIMIT	102
SIX	7	X	55	LOW	103
SEVEN	8	Y	56	LOWER	104
EIGHT	9	Z	57	MARK	105
NINE	10	AGAIN	58	METER	106
TEN	11	AMPERE	59	MILE	107
ELEVEN	12	AND	60	MILLI	108
TWELVE	13	AT	61	MINUS	109
THIRTEEN	14	CANCEL	62	MINUTE	110
FOURTEEN	15	CASE	63	NEAR	111
FIFTEEN	16	CENT	64	NUMBER	112
SIXTEEN	17	400 HZ TONE	65	OF	113
SEVENTEEN	18	80 HZ TONE	66	OFF	114
EIGHTEEN	19	20 mS SILENCE	67	ON	115
NINETEEN	20	40 mS SILENCE	68	OUT	116
TWENTY	21	80 mS SILENCE	69	OVER	117
THIRTY	22	160 mS SILENCE	70	PARENTHESIS	118
FORTY	23	320 mS SILENCE	71	PERCENT	119
FIFTY	24	CENTI	72	PLEASE	120
SIXTY	25	CHECK	73	PLUS	121
SEVENTY	26	COMMA	74	POINT	122
EIGHTY	27	CONTROL	75	POUND	123
NINETY	28	DANGER	76	PULSES	124
HUNDRED	29	DEGREE	77	RATE	125
THOUSAND	30	DOLLAR	78	RE	126
MILLION	31	DOWN	79	READY	127
ZERO	32	EQUAL	80	RIGHT	128
A	33	ERROR	81	SS (NOTE 1)	129
B	34	FEET	82	SECOND	130
C	35	FLOW	83	SET	131
D	36	FUEL	84	SPACE	132
E	37	GALLON	85	SPEED	133
F	38	GO	86	STAR	134
G	39	GRAM	87	START	135
H	40	GREAT	88	STOP	136
I	41	GREATER	89	THAN	137
J	42	HAVE	90	THE	138
K	43	HIGH	91	TIME	139
L	44	HIGHER	92	TRY	140
M	45	HOUR	93	UP	141
N	46	IN	94	VOLT	142
O	47	INCHES	95	WEIGHT	143
P					

NOTE 1: "SS" (#129) can be used to make singular words plural

TABLE 2—WORD LIST SSR5 AND SSR6

ABORT	0	FARAD	44	PER	88
ADD	1	FAST	45	PICO	89
ADJUST	2	FASTER	46	PLACE	90
ALARM	3	FIFTH	47	PRESS	91
ALERT	4	FIRE	48	PRESSURE	92
ALL	5	FIRST	49	QUARTER	93
ASK	6	FLOOR	50	RANGE	94
ASSISTANCE	7	FORWARD	51	REACH	95
ATTENTION	8	FROM	52	RECEIVE	96
BRAKE	9	GAS	53	RECORD	97
BUTTON	10	GET	54	REPLACE	98
BUY	11	GOING	55	REVERSE	99
CALL	12	HALF	56	ROOM	100
CAUTION	13	HELLO	57	SAFE	101
CHANGE	14	HELP	58	SECURE	102
CIRCUIT	15	HERTZ	59	SELECT	103
CLEAR	16	HOLD	60	SEND	104
CLOSE	17	INCORRECT	61	SERVICE	105
COMPLETE	18	INCREASE	62	SIDE	106
CONNECT	19	INTRUDER	63	SLOW	107
CONTINUE	20	JUST	64	SLOWER	108
COPY	21	KEY	65	SMOKE	109
CORRECT	22	LEVEL	66	SOUTH	110
DATE	23	LOAD	67	STATION	111
DAY	24	LOCK	68	SWITCH	112
DECREASE	25	MEG	69	SYSTEM	113
DEPOSIT	26	MEGA	70	TEST	114
DIAL	27	MICRO	71	TH (NOTE 2)	115
DIVIDE	28	MORE	72	THANK	116
DOOR	29	MOVE	73	THIRD	117
EAST	30	NANO	74	THIS	118
ED (NOTE 1)	31	NEED	75	TOTAL	119
ED (NOTE 1)	32	NEXT	76	TURN	120
ED (NOTE 1)	33	NO	77	USE	121
ED (NOTE 1)	34	NORMAL	78	UTH (NOTE 3)	122
EMERGENCY	35	NORTH	79	WAITING	123
END	36	NOT	80	WARNING	124
ENTER	37	NOTICE	81	WATER	125
ENTRY	38	OHMS	82	WEST	126
ER	39	ONWARD	83	SWITCH	127
EVACUATE	40	OPEN	84	WINDOW	128
EXIT	41	OPERATOR	85	YES	129
FAIL	42	OR	86	ZONE	130
FAILURE	43	PASS	87		

NOTE 1: "EDs" 31 and 32 work best with words that end with "T" or "D". "ED" 34 works best with words that end with soft sounds.

NOTE 2: "TH" (#115) can be added to words like: six, seven, and eight to make sixth, seventh, and eighth etc.

NOTE 3: "UTH" (#122) can be added to twenty, thirty, and forty to make twentieth, thirtieth, and fortieth, etc.

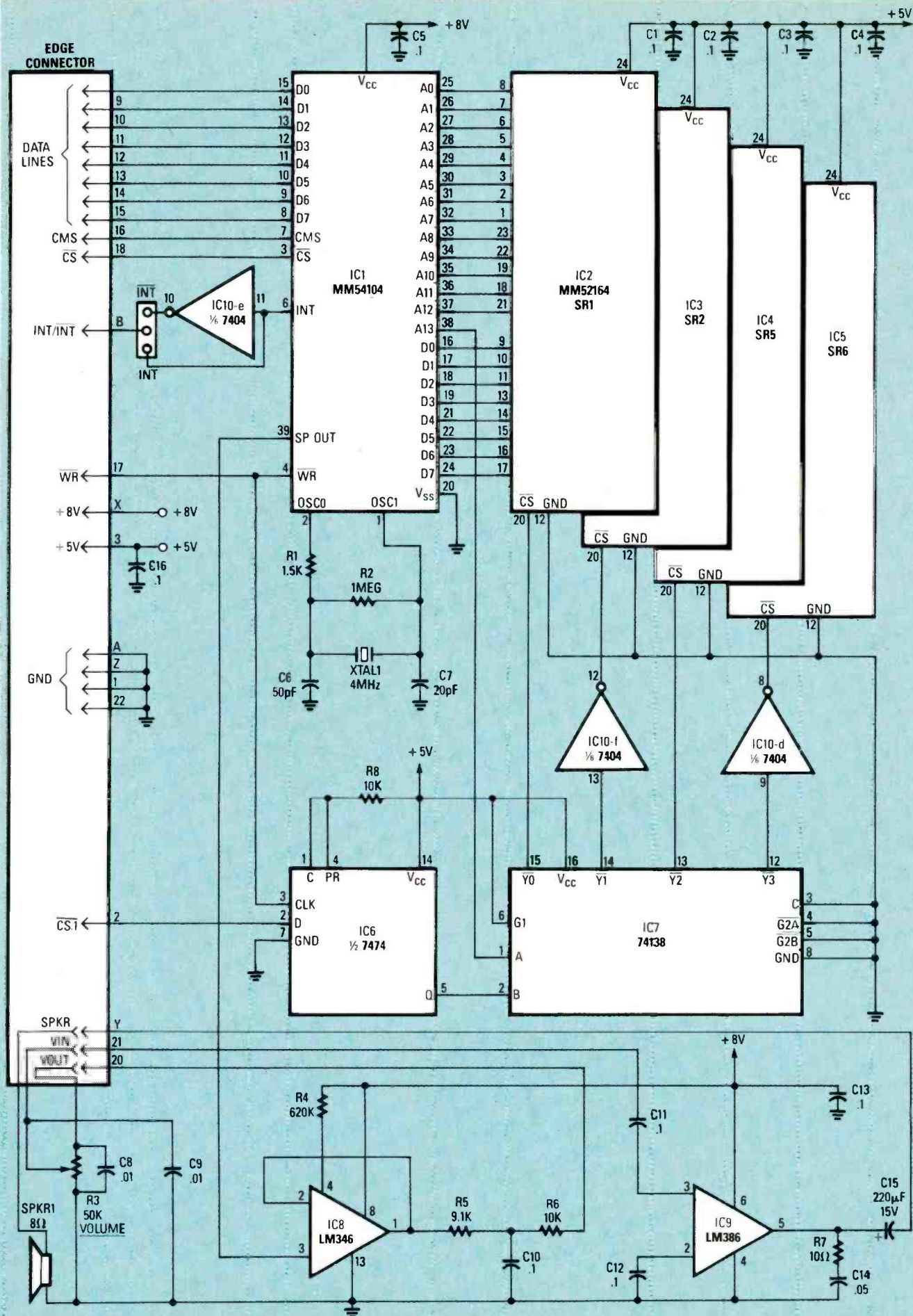


FIG. 2—SCHEMATIC DIAGRAM OF THE DIGITAL TALKER. The speech processor (IC1) reads data from the ROM's (IC2-IC5) and delivers speech output via pin 39.

synthesizer is useless for text-to-speech conversion because of the large amount of memory that would be required.

The Digitalker

National Semiconductor's Digitalker is a stored-word speech synthesis system that produces an exceptionally clear "voice." In fact, the Digitalker's quality exceeds Texas Instrument's *Speak & Spell* speech synthesizer. The Digitalker's voice has intonation or feeling, is not monotone, and even uses a female voice for the phrase "This is Digitalker."

The MM54104 SPC (Speech Processor Chip) is the heart of the Digitalker system. It's a 40-pin IC having 8 data lines (pins 8–15) that can be programmed manually with switches, or by connecting the device to a computer. For best results, a computer should be used to control the SPC so that sentences can be formed by stringing words together rapidly.

The SPC also has 14 ROM address lines (A0–A13, pins 25–38) that are to address ROM's containing speech data. Through those 14 address lines, the SPC can directly access 128K bits of speech data, which is good for about one minute of continuous speech. The SPC receives its data from the ROM's through eight data lines (pins 16–19 and pins 21–24). A number of other lines (pins 3, 4, and 7) are used for handshaking with a host computer, for connecting an external crystal oscillator (pins 1 and 2), and for speech output (pin 39)—which is connected to a filter and an audio amplifier. For more information on the SPC, see National's 1982 Linear Databook.

The right words

One key to a good stored-word speech-synthesis system is to choose the right words to store, convert them from an analog source, and then compress them into digital data suitable for the SPC.

National Semiconductor will convert analog tapes into custom digital data for customers, but that's an expensive proposition for hobbyists. However, the company has developed four general-purpose 64K-bit ROM's that contain data for 273 words, phrases, tones, and pauses. National's Linear databooks list several different ROM sets, but the SSR1, SSR2, SSR5, and SSR6 provide the best selection of words and are easy to obtain. The four ROM's together contain nearly two minutes of continuous speech; the words contained in each ROM set are shown in Tables 1 and 2.

Hooking it up

As shown in Fig. 1, the simplest way to use the Digitalker is to connect it to your computer's printer port. There are several advantages to doing so. First, handshaking between the computer and the Digitalker is automatic, so it isn't necessary to place timing loops in the software.

Second, most printer ports have a STROBE line that goes low when data at the port is valid. The strobe line can be connected to the SPC's \overline{WR} line. When it is asserted, the SPC reads the ROM data for the selected word over its eight data lines (D0–D8), and then delivers the word to the audio output (pin 39).

The SPC's INTR line (pin 6) goes high after the entire word has been pronounced. By connecting the INTR line (or, if necessary, the inverted \overline{INTR}) to the printer port's BUSY input,

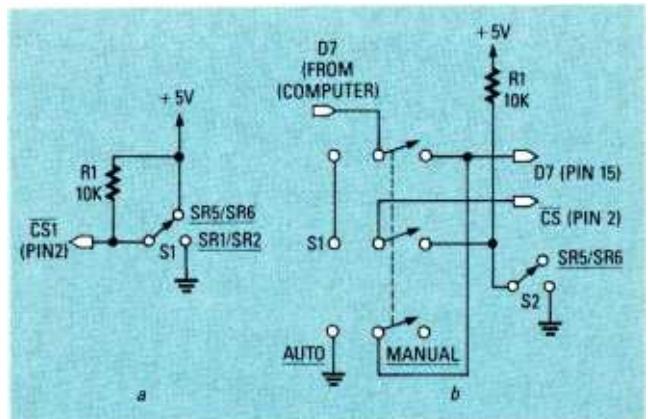


FIG. 3—ROM-SELECT CIRCUITS: Use the circuit shown in (a) to select between ROM sets manually. The circuit shown in (b) allows manual or automatic computer control, but only the first 128 words and phrases are accessible in the auto mode.

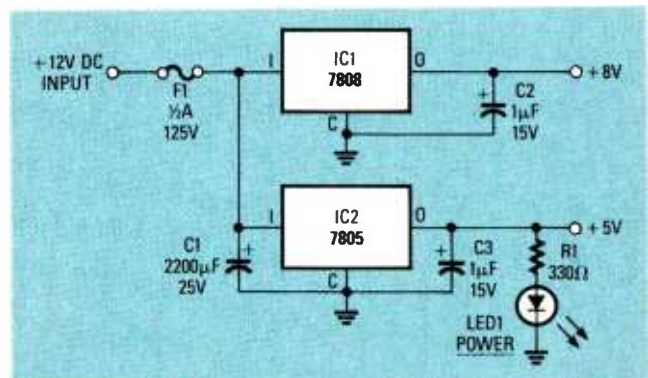


FIG. 4—POWER SUPPLY for the Digitalker. A +12-volt wall transformer provides the raw DC input.

the host computer will wait until each word has been spoken before sending more data to the SPC.

Two SPC pins provide options. First, \overline{CS} is the chip-select line; it must be grounded momentarily when the computer addresses the SPC. \overline{CS} is provided to allow the SPC to share the data bus with other devices.

Second, \overline{CMS} (command select) resets the interrupt and starts a speech sequence when it is low, and only resets the interrupt when it is high.

The PC board layout brings both \overline{CS} and \overline{CMS} out to the edge connector. For normal operation from a parallel-printer port, it's most convenient to ground both pins at the edge-card connector.

Now let's look at the circuit, shown in Fig. 2. The SPC's speech output drives IC8, which buffers the audio signal and drives a volume control. Final audio output is provided by IC9.

Flip-flop IC6 and 3-to-8 line decoder IC7 select the speech ROM's, depending on whether SPC address line AD13 is high or low, and on the state of the \overline{CS} signal (edge connector pin 2). AD13 picks the high or low ROM of a pair, and \overline{CS} picks one pair or the other.

There are several ways to select which ROM pair you want to use. If you have an extra output bit available on your PC (perhaps a bit from a second parallel port), you can program \overline{CS} directly. Otherwise, you can use a manual switch, as shown in Fig. 3-a.

A combination approach is shown in Fig. 3-b. With switch S1 in the Manual position, you can use S2 to switch

between ROM's. But with S1 in the Auto position, you can switch between ROM's using a single eight-bit port. The upper data bit (D7) provides the switching function, so only the first 128 words (0-127) in each ROM set will be accessible using that approach.

The power-supply schematic is shown in Fig. 4. An inexpensive wall transformer provides the raw DC power. Voltage regulators inside the project's cabinet provide the required voltages: +5-volts DC for the digital circuits, and +8-volts DC for the audio circuitry. The entire circuit draws about 300 mA when the volume is turned up, so use a +12-volt DC, 500-mA power supply.

Construction

PC board patterns are shown in PC Service. An etched and drilled PC board is also available from the source given in the Parts List. Figure 5 shows how the parts are mounted on the board. **Note:** six jumper wires must be soldered to the circuit board before the IC sockets are installed. An additional jumper must be soldered from the center INT terminal to either INT or $\overline{\text{INT}}$, depending on the handshaking requirements of your computer's parallel port. Most computers use an active-high busy signal, so try the INT setting first if you're not sure which one to use.

Observe normal precautions when handling the SPC and ROM IC's. Leave the chips in their protective "rugs" until they are ready for use. To protect the components against damage caused by static electricity, make sure to ground yourself before removing the IC's from their rugs, or when handling or moving the PC board.

After mounting all components, check your work carefully for solder bridges and cold joints. Fix any problems before applying power to the board.

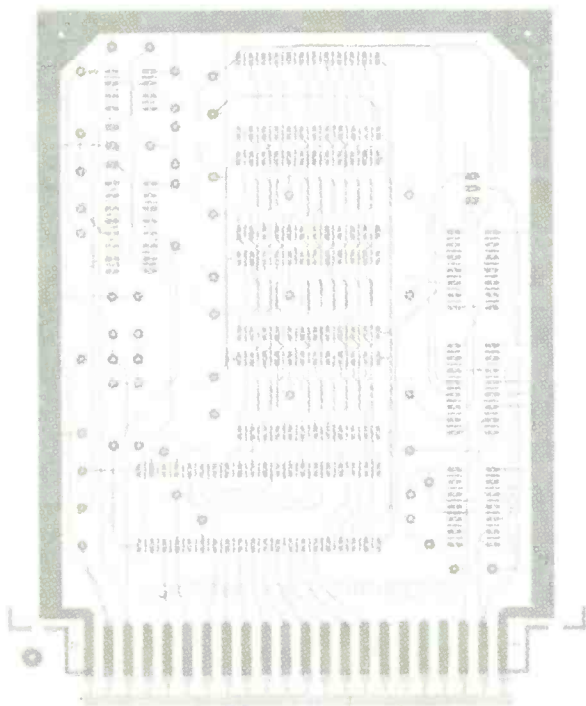


FIG. 5—PARTS LAYOUT: Note that six jumpers must be installed on the component side of the board before installing the IC sockets. (Sockets mount over five of the six jumpers.)

DIGITAL TALKER PARTS LIST

All resistors are 1/4-watt, 5% unless otherwise noted.

- R1—1500 ohms
- R2—1 megohm
- R3—50,000 ohms, potentiometer
- R4—620,000 ohms
- R5—9100 ohms
- R6, R8—10,000 ohms
- R7—10 ohms

All capacitors are rated 15 volts or higher

- C1—C5, C10—C13, C16—0.1 μF , ceramic disc
- C6—50 pF, ceramic disc
- C7—20 pF, ceramic disc
- C8, C9—0.01 μF , ceramic disc
- C14—0.05 μF , ceramic disc
- C15—220 μF , 15 volts, electrolytic

Semiconductors

- IC1—MM54104, speech processor
- IC2—MM52164-SSR1, speech ROM
- IC3—MM52164-SSR2, speech ROM
- IC4—MM52164-SSR5, speech ROM
- IC5—MM52164-SSR6, speech ROM
- IC6—7474, dual D flip-flop
- IC7—74138, 3-to-8 line decoder
- IC8—LM346, programmable op-amp
- IC9—LM386, audio power amplifier
- IC10—7404, hex inverter

Other components

- XTAL1—4.00 MHz crystal

POWER SUPPLY PARTS LIST

- R1—330 ohms
- IC1—7808 8-volt regulator
- IC2—7805 5-volt regulator
- C1—2200 μF , 25 volts, electrolytic
- C2, C3—1 μF , 15 volts, tantalum
- F1—fuse, 0.5 amp, 125 volts
- LED1—light-emitting diode

Note: An etched and drilled PC board is available for \$15.95 from David A. Ward, 2261 W. Skyview, Cedar City, UT 84720-2233. All orders add \$2.00 shipping and handling; Utah residents add 6% sales tax.

LISTING 1

```

10 REM This program will make the
20 REM Digitaltalker pronounce all words
30 REM in SSR1 and SSR2 (CS1 is low)
40 FOR X = 0 to 143
50 LPRINT CHR$(X);
60 NEXT X
70 END

```

LISTING 2

```

10 REM This program will make the
20 REM Digitaltalker pronounce all words
30 REM in SSR5 and SSR6 (CS1 is high)
40 FOR X=0 to 130
50 LPRINT CHR$(X);
60 NEXT X
70 END

```

LISTING 3

```

10 REM REAL TIME CLOCK PROGRAM
20 CLS
30 PRINT"HOW OFTEN DO YOU WANT THE TIME ANNOUNCED?"
40 PRINT:PRINT
50 PRINT"ENTER 1 FOR 1 MINUTE INTERVALS..."
60 PRINT"ENTER 5 FOR 5 MINUTE INTERVALS..."
70 PRINT"ENTER 30 FOR 30 MINUTE INTERVALS..."
80 INPUT" ", I
90 TIMES=TIMES
100 TS=LEFTS(TIMES,2)
110 T1S=MIDS(TIMES,4,2)
120 HS=LEFTS(TS,1)
130 H1S=RIGHTS(TS,1)
140 H=ASC(HS)
150 H1=ASC(H1S)
160 H=H-48
170 H1=H1-48
180 H=H*10
190 HT=H+H1
200 IF HT>12 THEN HT=HT-12:P=47:GOTO 220
210 P=32
220 IF HT=12 THEN P=47
230 IF HT=0 THEN HT=12:P=32
240 MS=LEFTS(T1S,1)
250 M1S=RIGHTS(T1S,1)
260 M=ASC(MS)
270 M1=ASC(M1S)
280 M=M-48
290 M1=M1-48
300 IF M=0 AND M1=0 THEN M=68:M1=68
310 IF M=0 AND M1>0 THEN M=46
320 IF M=1 AND M1=0 THEN M=10:M1=68
330 IF M=1 AND M1=1 THEN M=11:M1=68
340 IF M=1 AND M1=2 THEN M=12:M1=68
350 IF M=1 AND M1=3 THEN M=13:M1=68
360 IF M=1 AND M1=4 THEN M=14:M1=68
370 IF M=1 AND M1=5 THEN M=15:M1=68
380 IF M=1 AND M1=6 THEN M=16:M1=68
390 IF M=1 AND M1=7 THEN M=17:M1=68
400 IF M=1 AND M1=8 THEN M=18:M1=68
410 IF M=1 AND M1=9 THEN M=19:M1=68
420 IF M=2 THEN M=20
430 IF M=3 THEN M=21
440 IF M=4 THEN M=22
450 IF M=5 THEN M=23
460 IF M1=0 THEN M1=68
470LPRINT CHR$(0);CHR$(138);CHR$(67);CHR$(139);CHR$(67);
CHR$(96);CHR$(71);CHR$(HT);CHR$(69);CHR$(M);CHR$(M1);
CHR$(71);CHR$(P);CHR$(44);CHR$(71);CHR$(71);
480 PRINT TIMES
490 GOSUB 510
500 GOTO 90
510 IF I=1 THEN I=60
520 IF I=5 THEN I=300
530 IF I=10 THEN I=600
540 IF I=30 THEN I=1800
550 Z=TIMER
560 Y=TIMER
570 IF Y-Z<I THEN 560
580 RETURN

```

Making the connection

Connecting the Digitalker to your computer is as simple as plugging it into your computer's parallel printer port. For testing purposes, wire a ROM-select switch as shown in Fig. 3-a.

It's easy to program the Digitalker. For example, simply by typing

```
LPRINT CHR$(0);
```

the Digitalker will say the phrase "This is Digitalker" if \overline{CS} is low, or "abort" if \overline{CS} is high.

Listing 1 and Listing 2 are test programs that sequentially pronounce all words contained in the selected ROM set. Both programs were written in GW-BASIC; they were tested on a Kaypro PC.

More sophisticated applications are not difficult. For example, the author has written BASIC programs that do the following; announce the time from the computer's

real-time clock, pronounce the corresponding letter of the alphabet as a key is typed (great for a small child learning his ABC's), pronounce phone numbers as names are typed in, and prompt the user for input in various programs. The talking clock program is shown in Listing 3.

There are a couple of things to be aware of when programming the Digitalker. First, addressing a word with a number higher than that listed in the word lists will produce unintelligible speech, but will not damage the

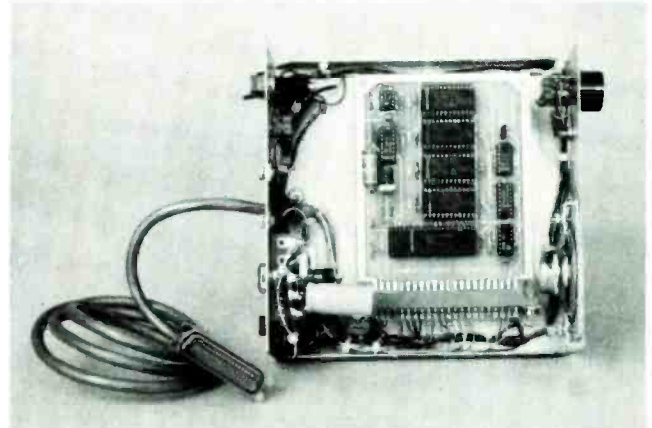


FIG. 6—THE ASSEMBLED SYNTHESIZER with its cover removed.

SPC or ROM chips. Second, the semicolons following the LPRINT statements are essential. If they are not present the Digitalker will pronounce *thirteen* and then *ten* after each word is spoken. That occurs because an ASCII 13 is a carriage return, and an ASCII 10 is a linefeed. The semicolon (;) eliminates the carriage return and linefeed.

Applications ideas

Computer voice synthesis can be a very natural way for computers to communicate with people. For example, a synthesizer could be used to warn a pilot that the plane's altitude is critically low, or that the fuel level is low. A visually impaired person could compose documents with a word processor, or compute math problems with a calculator.

Undoubtedly, there are many other uses for computerized voice synthesis in cash registers, automatic teller machines, emergency warning systems, automobiles, telephone systems, etc. Have fun finding them! ♦♦



"The man at the pet shop said he can store up to 20 separate commands."

68000 ASSEMBLY LANGUAGE

*An introduction to 68000
assembly-language programming.*

PETER A. STARK,
STARK SOFTWARE SYSTEMS CORPORATION

Copyright (C) 1988 by Peter A. Stark



Programming the 68000 in a high-level language (BASIC, C, etc.) is not much different from programming in a high-level language on any other microprocessor. But if you're building the PT-68K computer, we assume that you want to go beneath the surface and learn a bit about the internal structure of the microprocessor, and how to program it in its native language. What follows will serve as a necessarily brief introduction; we'll also provide references for further information.

Even though the 68000 is an extremely versatile and powerful microprocessor, it is still fairly easy to program it in assembly language, especially compared with the difficulty of programming other microprocessors (the Intel family in particular). With some effort, it is even possible to program it in machine language, though one has to be pretty desperate to want to attempt it.

As shown in Fig. 1, Internally, the 68000 has nineteen user-accessible registers; each register is a memory location within the microprocessor that can store a number while it is being used. All registers but one are 32 bits long.

For purposes of experimentation, we'll use HUMBUG, the PT-68K's built-in ROM monitor that allows you to examine and change memory, execute programs at full speed and a step at a time, etc. Start your computer, and when you get the prompt, you can press the letters HE to display a help screen. Each command is a two-character abbreviation for the command.

One useful command is RE (Register Examine). At the prompt, press RE to get a display similar to that shown in Table 1. The line starting D: shows eight 8-digit numbers corresponding to the eight *data registers* (D0–D7); the line starting with A: shows eight 8-digit numbers corresponding to the eight *address registers* (A0–A7). For example, data register D3 is shown on the D: line, under the 3; address register A0 is on the A: line, under the 0.

The last line of Fig. 1 shows four additional registers: the

program counter (PC), the *status register* (SR), the *user stack register* (US), and the *supervisor stack register* (SS, also called the *system stack register*). Actually, only nineteen registers are shown, because one of the registers is shown twice. Register A7 is normally used as the user stack pointer, so the register dump shows that the two registers have identical contents.

Except for SR (the status register), each register contains an eight-digit hexadecimal number. For example, Table 1 shows that D0 contains the number 12121212 (your display will contain different numbers). Each hex digit represents four bits, so each register (other than SR) can contain a 32-bit number.

The SR (status) register differs in that it contains only 16 bits, or four hex digits. In the example, those hex digits are 0000; the periods to the right of the number indicate the status of each bit.

The 68000 can work with an entire register (32 bits), half a register (16 bits), or even a quarter of a register (8 bits) at a time. A two-digit hex number is called a *byte*; a four-digit hex number is called a *word*; an eight-digit number is called a *long word*.

Although instructions in a high-level language may consist of complex mathematical calculations, at the lowest level all microprocessors work with *machine language*, which are usually represented with hex numbers and binary digits. Somewhat more readable (to humans, that is) is *assembly language*, which represents those instructions with words, not just numbers.

Machine- and assembly-language instructions are concerned with relatively small tasks. The most common such task is one that simply moves a number from one place to another. For example, the assembly-language instruction that moves a long word from the D5 register to the A2 register would be written:

```
MOVE.L D5,A2
```

Note that the instruction consists of four parts: MOVE tells

addresses that indicate the location of that data. There are exceptions to that rule, so moving a long word from D5 to A2 is perfectly valid—the 68000 doesn't care whether the number being moved is an address or data. That is why Motorola states that the 68000 has sixteen "general purpose" registers.

The 68000 can directly address as many as 16 million locations; those addresses are numbered consecutively from \$000000 to \$FFFFFF, for a total of just six hex digits. But the registers can hold eight hex digits, not just six. Therefore, in most cases the two left digits of an address will both be 00 (like the A7 and PC registers in Table 1).

Even though the two left digits are not used by the 68000 for addressing, the scheme maintains compatibility with the microprocessor's more powerful siblings, the 68020 and the 68030, both of which allow full eight-digit addresses, thereby allowing as many as four billion locations to be accessed directly.

Here are two other common 68000 assembly-language instructions intended to exemplify the *from, to* structure:

```
MOVE.B D7,$00FF0200
```

moves a byte from register D7 to memory location \$FF0200, and

```
ADD.W $00FF0100,D6
```

adds the number that is stored in memory location \$FF0100 to the contents of data register D6, and leaves the result in that register.

Machine and assembly language

Those instructions are simple examples of assembly language. Unfortunately, microprocessors don't understand assembly language—instead, they require an even more down-to-earth language called machine language, in which the four parts of the above instructions are coded as binary bits. For example, our first example instruction (MOVE.L D5,A2) is actually coded as the 4-digit hex number 2445, which translates to a binary 0010010001000101. Each of the parts of the original assembly-language instruction is carefully preserved in the machine code as well: the first 0010 means "MOVE.L," the next 010001 means "to A2," and the final 000101 means "from D5."

Although the original MOVE.L D5,A2 is understandable to humans, a number like 2445 (or, worse yet, 0010010001000101) doesn't make much sense. If we had to write all our programs in machine language—as either hex numbers or even strings of ones and zeroes—programming would be very difficult indeed. Fortunately, a program called an *assembler* translates from assembly language to machine language for us. SK*DOS includes a 68000 assembler, but you need a built-up PT-68K (one with disk drives and some DRAM) to run it. If you've got only a bare-bones system (one with 2K or 4K of RAM), to assemble programs what you are going to have to do is to try one of the ideas outlined below.

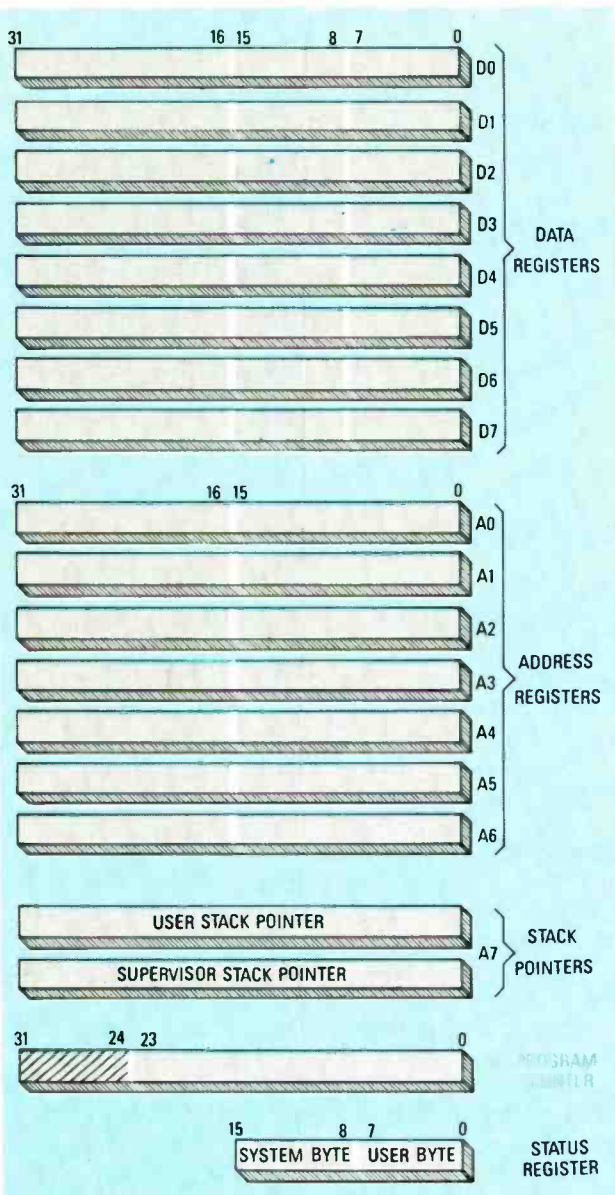


FIG. 1—THE MC68000'S REGISTER MODEL. All registers except the status register (also called the condition code register or CCR) are 32 bits long. A7 is used as the user stack pointer.

what we want to do, .L specifies that a long word (32 bits) is to be moved, D5 (the *source*) tells where the number is to be moved from, and A2 (the *destination*) tells where to move it to. In 68000 programming, the source always comes first, so you may think of the format as *from, to*; that differs from some microprocessor families (notably the Intel family) where the format is *to, from*.

Normally data registers contain numbers used in calculations of some kind, and address registers contain

TABLE 1—HUMBUG'S REGISTER DISPLAY

	0	1	2	3	4	5	6	7
D:	12121212	00000012	00000013	00000014	00000015	00000016	00000017	00000018
A:	98765432	00000099	00000088	00000077	00000066	00000055	00000044	00FF0EFC
PC=	00F00206	SR=0000	=.....0.....		US=00FF0EFC		SS=00FF0DFC	

LISTING 1

```

FF0000                                ORG          $FF0000

FF0000 2002                            START      MOVE.L    D2,D0      Move D2 to D0
FF0002 2401                            MOVE.L    D1,D2      Move D1 to D2
FF0004 2200                            MOVE.L    D0,D1      Move D0 to D1
FF0006 4EF9 00FF 0000                  JMP       START      And repeat

                                END

0 ERROR(S) DETECTED

```

You can, of course, wait until you have installed more memory and a disk interface, at which time you can run the SK*DOS assembler. Alternatively, you could use an assembler that runs on another computer, such as a Macintosh, an Atari ST, or even a PC compatible. (An assembler which runs on a totally different computer is often called a *cross-assembler*.) With the latter approach, you'll have to enter the hex bytes generated by the assembler into your PT-68K by hand.

If you are really persistent, it is possible (though not easy, and definitely not enjoyable) to "hand-assemble" a program—i.e., translate it manually from assembly language to machine language—with the aid of a few good books on 68000 assembly-language programming. Two such books are *The 68000: Principles and Programming*, written by Leo J. Scanlon, and published by Howard W. Sams & Co., and *M68000 16/32-bit Microprocessor Programmer's Reference Manual*, by the Motorola Staff, published by Prentice-Hall Inc. Both books are also available from local Motorola sales offices; the latter book is a "must have" if you intend to do really serious assembly-language programming.

Last, you could send your assembly language program to the PT-68K BBS (at 914-241-3307) by phone; the Sysop will assemble it for you free of charge. Again, you'll have to enter hex bytes by hand.

To get started, let's write a simple program and show you how you could enter it and test it on your computer. Let's start with a simple BASIC program; it's not really useful, but it does make a good introduction to assembly language:

```
ab 10 D0 = D2 ' MOVE D2 TO D0
```

```
ab 20 D2 = D1 ' MOVE D1 TO D2
```

```
ab 30 D1 = D0 ' MOVE D0 TO D1
```

```
ab 40 GOTO 10 ' AND REPEAT
```

The equivalent assembly language program is shown in Listing 1.

The two programs are similar, but there are differences. In BASIC, for example, D0 is a variable (possibly with a decimal point or exponent), whereas in assembly language it represents a binary integer that, in this case, happens to be contained in a specific register.

Assembly-language syntax

In assembly language, any line may consist of four parts: a *label*, an *operation code*, an *operand*, and a *comment*. Not every line will have all four parts; some will have all four, and others will have only one or two. Let's discuss each in turn, using analogies in BASIC where possible.

In most versions of BASIC, every line has a line number, although only line 10 in this example really needs one (because it is referred to in line 40). In assembly language, lines have (optional) labels, rather than numbers. The first line is labeled START, because it is where code begins, and so that the last program line can refer to it.

The operation code (MOVE.L or JMP, for example) tells the microprocessor what to do, and the operand tells the microprocessor what to do it to, or where to do it, or even how to do it. For example, a MOVE instruction must have source and destination registers or memory locations.

As in BASIC, an assembly-language statement can have explanatory comments appended to the end of the line, but in 68000 assembly language, a comment needs no quote (or, as in some versions of BASIC, a :REM).

For an assembler to translate the program into machine language, we must add two more lines. At the top, we add the *assembler directive*

```
ORG $FF0000
```

which tells the assembler where in memory to place the program. It is called an assembler directive because it is an instruction to the assembler, rather than an instruction within the program. We use address \$FF0000 for the beginning of the program, because that is the only place where RAM is installed in a minimal system.

At the end of the program, we place the directive

```
END
```

which tells the assembler to stop translating. The resulting six lines are called the *source program*.

TABLE—ENTERING A SIMPLE PROGRAM

```

*ME ADDRESS: FF0000
00FF0000 00 20
00FF0001 00 02
00FF0002 00 24
00FF0003 00 01
00FF0004 00 22
00FF0005 00 00
00FF0006 00 4E
00FF0007 00 F9
00FF0008 00 00
00FF0009 00 FF
00FF000A 00 00
00FF000B 00 00
00FF000C 00
*HD FROM FF0000 TO FF000B
00FF0000 20 02 24 01 22 00 4E F9 00 FF 00 00
*
```


TABLE 3—SINGLE STEPPING WITH HUMBUG

```

*ST FROM FF0000
00FF0000: 2002
      0          1          2          3          4          5          6          7
D: 22222222 11111111 22222222 33333333 44444444 55555555 66666666 77777777
A: 88888888 99999999 AAAAAAAAA BBBB BBBB CCCCCCCC DDDDDDDD EEEEEEEE 00FF0EFC
PC=00FF0002 SR=0000 =.....0..... US=00FF0EFC SS=00FF0DFC

*SS
00FF0002: 2401
      0          1          2          3          4          5          6          7
D: 22222222 11111111 11111111 33333333 44444444 55555555 66666666 77777777
A: 88888888 99999999 AAAAAAAAA BBBB BBBB CCCCCCCC DDDDDDDD EEEEEEEE 00FF0EFC
PC=00FF0004 SR=0000 =.....0..... US=00FF0EFC SS=00FF0DFC

*SS
00FF0004: 2200
      0          1          2          3          4          5          6          7
D: 22222222 22222222 11111111 33333333 44444444 55555555 66666666 77777777
A: 88888888 99999999 AAAAAAAAA BBBB BBBB CCCCCCCC DDDDDDDD EEEEEEEE 00FF0EFC
PC=00FF0006 SR=0000 =.....0..... US=00FF0EFC SS=00FF0DFC

*SS
00FF0006: 4EF9
      0          1          2          3          4          5          6          7
D: 22222222 22222222 11111111 33333333 44444444 55555555 66666666 77777777
A: 88888888 99999999 AAAAAAAAA BBBB BBBB CCCCCCCC DDDDDDDD EEEEEEEE 00FF0EFC
PC=00FF0000 SR=0000 =.....0..... US=00FF0EFC SS=00FF0DFC

*SS
00FF0000: 2002
      0          1          2          3          4          5          6          7
D: 11111111 22222222 11111111 33333333 44444444 55555555 66666666 77777777
A: 88888888 99999999 AAAAAAAAA BBBB BBBB CCCCCCCC DDDDDDDD EEEEEEEE 00FF0EFC
PC=00FF0002 SR=0000 =.....0..... US=00FF0EFC SS=00FF0DFC
    
```

LISTING 2

FF0000	287C	00FF	0012	START	ORG	\$FF0000	
FF0006	4EB9	00F8	0102		MOVE.L	#STRING,A4	Address of string
FF000C	4EF9	00FF	0000		JSR	\$F80102	Print it
					JMP	START	And repeat
FF0012	48454C4C4F2104			STRING	DC.B	'HELLO!',4	
					END		

0 ERROR(S) DETECTED

We then call the assembler to do the translation; it prints out a listing of both the source program and the translated machine code, which is called the *object program* or *object code*. As shown in Listing 1, the object code is at the left, and the source code is at the right.

At the left side of the listing, the first column of numbers (beginning with FF0000) are the addresses where the program instructions will be stored. (The beginning address was specified in the ORG directive at the beginning of the program. The first instruction (MOVE.L D2,D0), translates into a 2002 machine-language instruction,

which is stored in location FF0000. That instruction occupies two locations in memory, namely FF0000 and FF0001; therefore the second instruction begins at location FF0002. The second instruction also occupies two bytes, so the third instruction begins at FF0004, and so on.

Note that each of the three MOVE instructions take only two bytes, but the JMP instruction (equivalent to BASIC's GOTO) at the end of the program takes six bytes. In general, instructions that involve only internal registers tend to be short (and fast), whereas instructions that involve memory tend to be long (and slow), because

R-E Computer Admart

Rates: Ads are 2 1/4" x 2 7/8". One insertion \$900. Six insertions \$875. each. Twelve insertions \$845. each. Closing date same as regular rate card. Send order with remittance to Computer Admart, Radio Electronics Magazine, 500-B Bi-County Blvd., Farmingdale, NY 11735. Direct telephone inquiries to Arline Fishman, area code-516-293-3000. Only 100% Computer ads are accepted for this Admart.

8051 SIMULATOR

for the IBM PC/XT/AT **\$99**

The 8051SIM software package assists in the debug of 8051 family programs. A screen oriented, menu command driven program, 8051SIM simulates the Intel 8051 family of single chip microcomputers. This learning tool also speeds up the development process.

8031 DryICE \$199

The 8051 Dry ICE is a hardware/software package that allows you to dump and modify memory; execute and trace 8051 family code in your target system. Hardware connects between target system and any serial port.



HiTech Equipment Corporation
9560 Black Mountain Road
San Diego, CA 92126

(619) 566-1892

CIRCLE 183 ON FREE INFORMATION CARD

ICs PROMPT DELIVERY!!!

SAME DAY SHIPPING (USUALLY)
QUANTITY ONE PRICES SHOWN for SEPT. 13, 1988

OUTSIDE OKLAHOMA, NO SALES TAX

DYNAMIC RAM			
SIMM	1Mx9	85 ns	\$495.00
1Mbit	1Mx1	100 ns	38.50
41256	256Kx1	60 ns	14.50
41256	* 256Kx1	80 ns	13.75
41256	256Kx1	100 ns	13.75
51258	* 256Kx1	100 ns	12.95
41256	256Kx1	120 ns	12.75
41256	256Kx1	150 ns	11.75
41264	+ 64Kx4	120 ns	18.95
EPROM			
27C1000	128Kx8	150 ns	\$37.95
27C512	64Kx8	200 ns	13.95
27256	32Kx8	250 ns	7.25
27128	16Kx8	250 ns	6.60
STATIC RAM			
43256L-10	32Kx8	100 ns	\$18.95
6264P-12	8Kx8	120 ns	13.50

OPEN 6 1/2 DAYS, 7:30 AM-10 PM. SHIP VIA FED-EX ON SAT

WE EXPORT ONLY TO CANADA, GUAM, PUERTO RICO & VIRGIN ISLANDS

MasterCard/VISA or UPS CASH COD

Factory New, Prime Parts

MICROPROCESSORS UNLIMITED, INC.

24,000 S. Phoenix Ave.

BEESD, OK 74421

(918) 267-4961

No minimum order. Please note that prices are subject to change. Shipping & insurance extra, \$ up to \$1 for packing materials. Orders received by 4 PM CST can usually be delivered the next morning, via Federal Express Standard Air @ \$4.95, or guaranteed next day Priority One @ \$18.25.

CIRCLE 61 ON FREE INFORMATION CARD

SECRETS OF THE COMMODORE 64

Secrets of the COMMODORE 64



BP135—A beginners guide to the Commodore 64 presents masses of useful data and programming tips, as well as describing how to get the best from the powerful sound and graphics facilities. We look at how the memory is organized, random numbers and ways of generating them, graphics-color-and simple animation, and even a chapter on machine code. Get your copy today. **Send \$5.00 plus \$1.25 for shipping in the U.S. to Electronic Technology Today Inc., P.O. Box 240, Massapequa Park, NY 11762-0240.**

they often require a complete four-byte memory address. Thus JMP translates into 4EF9, followed by 00FF0000, which is the address of the START label.

Without an assembler, you'll have to type the machine-language code in by hand to test and run it. As shown in Table 2, first type in the command ME (which stands for Memory Examine), and then respond with FF0000 (and a space) when HUMBUG asks for an address.

On the second line, HUMBUG prints out the address 00FF0000, followed by the present contents of that address. Although it is shown as 00 in the example, your computer will most likely have some other data there when you begin. You should then type in the number 20, which is the first byte of the first instruction (2002). HUMBUG will then go to the next line and display the contents of the next location; now you should type in the 02. After typing in twelve bytes, just press the Enter key when the program asks for data to place in location 00FF000C.

The last two lines in Table 2 show how to use the HD (Hex Dump) command in order to ensure that the data was entered correctly. The twelve bytes of our program are now neatly displayed, one after another, in consecutive locations.

Now let's test the program. If you look at the original BASIC program, you see that if we typed it in and typed RUN, the program would simply get tied up in a loop and never output a single number. The same would happen with the machine-language program. To avoid that, and to see what is happening, we will trace the program one instruction at a time, rather than run it at normal speed.

As shown in Table 3, start by issuing the ST (STart Stepping) command, and reply FF0000 when HUMBUG asks where to start.

On the next line, HUMBUG prints out the address and operation code of the instruction it is about to perform (in this case, 00FF0000: 2002). Then the instruction is executed, and next the 68000's registers are dumped. (For

purposes of illustration, all registers had been preloaded with distinctive data, thereby making it easy to see that the contents of D2 has been copied into D0.)

In the first register dump, note the item that reads PC = 00FF0002. The PC is the Program Counter, a register in the 68000 that holds the address of the next instruction to be performed. In this case, the next instruction is at location 00FF0002.

Next the SS command was typed in, HUMBUG performed the next instruction, and the registers were dumped again. Now both D1 and D2 contain the number 11111111.

Note what happens after the computer performs the JMP (4EF9) instruction at 00FF0006. This time the data registers do not change; what happens is that the program counter changes to 00FF0000, indicating that the computer will do the instruction at FF0000 next. In that way we see how the JMP instruction causes the program to repeat from the beginning.

For more practice, you can play with the program shown in Listing 2. Here, the second instruction (JSR \$F80102) causes HUMBUG to display the string pointed to by A4, in this case the message "HELLO!" Enter the machine code as before, but don't try to trace through HUMBUG. Just execute the program at high speed (using the command JS FF0000) to see what happens. Then try to figure out how to vary the message.

Conclusions

Assembly-language programming is a complex topic, so we cannot possibly do it justice here. However, we hope that we've given you an idea of what it's like to program in assembly language. If you want to learn more about it, consult your local engineering bookstore, one of the books mentioned above, local computer clubs, and your local college or university. Most important try to get some experience. Good luck.

AUDIO UPDATE



LARRY KLEIN,
AUDIO EDITOR

The Audio Engineering Society—Pt. II

IN LAST MONTH'S COLUMN I WROTE about the Audio Engineering Society and the services it provides to those interested in the technical side of audio. I had mentioned that I've been a member of the AES for some 30 years, and I credit it—through its monthly Journal and meetings—for much of my audio education. Present AES membership includes more than 10,000 engineers, researchers, educators, manufacturers, audio retailers, and students.

Aside from the talks, lectures, and debates scheduled during the regular local section meetings held in many major cities, scores of papers detailing the latest audio research and developments are presented during the annual conventions. For information on becoming a member of the AES and/or a catalog of available papers and special publications, simply write to: Audio Engineering Society, 60 East 42nd Street, New York, NY 10165. Anyway, here's a couple of presentations from the October 1987 meeting that I found particularly interesting.

2504, 0-7

A Musically Appropriate Dynamic Headroom Test for Power Amplifiers, Mitchell.

This paper discusses in depth a matter that I have written about extensively in a variety of publications. It questions the validity of the EIA dynamic headroom test found in the current amplifier standard, which measures an amplifier's ability to provide more

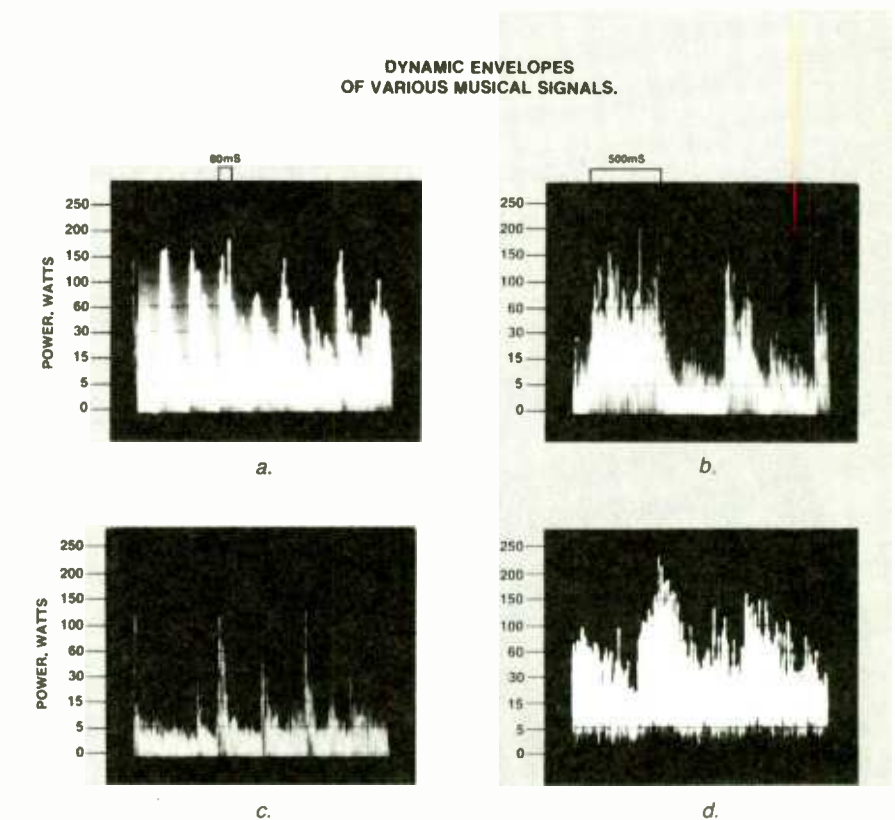


FIG. 1

power for brief peaks than it can on a continuous or sustained basis. The author does not find the concept of dynamic headroom at fault; the problem lies in the specific characteristics of the standard test signal that is used to determine dynamic power, which, in his view (and mine), are inadequately representative of typical music waveforms.

The present amplifier test standard (EIA RS-490) calls for a 1,000-

Hz tone burst of 20-millisecond duration, recurring at half-second intervals. The amplitude of the tone-burst test signal is gradually increased until the output waveform begins to clip. The difference, expressed in dB, between an amplifier's maximum rated output with a continuous signal versus its output with a tone-burst signal is its *dynamic headroom* rating. The dynamic headrooms of today's amplifiers have been mea-

sured as low as 0.25 dB, and as high as 6 dB—or four times the continuous-power rating.

Mitchell's paper includes nine oscilloscope photos (some of them are displayed in Fig. 1) showing the dynamic envelopes for a 2-second period of recorded selections ranging from Genesis and the Bee Gees to Bruckner, Mahler, and Strauss. The scope photos adequately establish that there are substantial musical peaks on compact discs that extend in time far beyond the 20 milliseconds of the EIA standard. Equally interesting are two graphs that illustrate the differences between conventional amplifiers and "commutating" amplifiers that adjust their power-supply voltages to the demands of the output signal. In the latter case, the power supply is operating at a low level most of the time—which minimizes heating and the need for a heavy-duty power supply. When musical tone bursts demand more power, the power supply switches to a higher voltage level.

Mitchell states that the original choice of 20 milliseconds for the tone-burst length was done "somewhat arbitrarily." Not so. As I recall, Edward Foster, who as chairman of the committee had undertaken the task of framing the standard, volunteered to research the question of an appropriate test signal. Only one technical paper bearing on the duration of musical peaks turned up, and our test-signal parameters were based on it.

Mitchell's paper concludes with a suggestion that the audio industry adopt a revised dynamic-headroom rating as its primary standard, because it most closely relates to an amplifier's ability to reproduce music without distortion. That is an interesting suggestion; but my experience as a member of the original IHF committee—which took two years to frame the current dynamic-headroom standards—leads me to believe that changes are unlikely to be agreed upon and adopted, given the nature of today's industry.

2518 C-1

Results of the 1986 AES Audiometric Survey, Martinez, Gilman.

About 25 years ago I visited the sound-mixing department of a major Hollywood motion-picture studio. As I recall, what impressed me most about the facility were the ear-blasting sound-pressure levels that were used for monitoring the mixes.

The sound was so loud that I couldn't see how it was possible to judge the finer points of audio quality while being buffeted by such sonic storms. I was later told that the high volume levels were used to listen for artifacts such as audible tape splices, rather than for nuances of quality. But there's another reasonable—and rather unfortunate—explanation for the high levels used by many audio professionals and musicians: hearing loss.

We'll look at that problem next month before we move on to the topic of amplifier damping factors. R-E

REALMAGIC!

An **ETCHED** circuit board from a Printed **PAGE** in just **3 Hours**

RADIO-ELECTRONICS

The ER-4 PHOTO ETCH KIT gives you the tools, materials and chemicals to make your own printed circuit boards. The patented Pos-Neg™ process copies artwork from magazines like this one without damaging the page. Use the circuit patterns, tapes and drafting film to make your own 1X artwork. Or try the Direct Etch™ system (also included), to make single circuit boards without artwork. The ER-4 is stocked by many electronic parts distributors, or order direct, postpaid.

ER-4 PHOTO ETCH KIT (NJ and CA residents add sales tax) \$38.00
DATAK'S COMPLETE CATALOG lists hundreds of printed circuit products and art patterns. Also contains dry transfer letter sheets and electronic title sets for professional looking control panels. **WRITE FOR IT NOW!**

DATAK Corp. • 3117 Paterson Plank Rd. • N. Bergen, NJ 07047

CIRCLE 182 ON FREE INFORMATION CARD

SCIENTIFIC ATLANTA AND PIONEER CABLE CONVERTORS IN STOCK		
AC/DC — The New Leader in Low Prices		
ITEM	1 UNIT	5+ UNITS
PIONEER ADD ON PD-2	275.00	250.00
PANASONIC WIRELESS CONVERTER 1403M	79.95	68.00
JEHOLD 400 WITH HELMOTE (MANUAL FINE TUNING)	64.95	55.00
JEHOLD 400 COMBO W/ HELMOTE (DIGITAL)	134.95	100.00
JEHOLD 450 COMBO W/ HELMOTE (DIGITAL)	189.95	125.00
JEHOLD 400 OR 450 RE-MOTE 1 HAND UNIT	24.95	15.00
JEHOLD SB ADD ON	74.95	55.00
ORV MANIPULATOR (9-12)	85.00	75.00
JEHOLD SB ADD ON WITH TR-88	84.95	65.00
OAK M 26 COMBO	84.95	59.00
OAK L COMBODE (E-12)	84.95	40.00
HAMILB MLD-1200	64.95	55.00
EAGLE PD 3	89.95	60.00
Z8 WITH SS-8V CABLE READY	149.95	100.00
SCIENTIF ATLANTA SA 3 ADD ON	109.95	60.00
INTELENECE FILTER (CHANNEL 3 OR 6)	24.95	14.00
VIDEO TAP COPY STABILIZER	49.95	45.00
PANASONIC CONVR HIGH W/ VOLUME CONTROL (170 3FB)	109.95	85.00
SCIENTIF ATLANTA 83 CHANNEL CONVR RFL II	89.95	75.00
SCIENTIF ATLANTA 32MATE 18 MOTE	89.95	49.00
PIONEER CONVR HIGH (4036)	89.95	75.00

QUANTITY	ITEM	OUTPUT CHANNEL	PRICE EACH	TOTAL PRICE
NO NEW YORK SALES. It is not the intent of AC/DC to disband any pay telephone operator and we will not attend any company or individual in doing so.			SUBTOTAL	
PLEASE PRINT: <input type="checkbox"/> Cashier's Check <input type="checkbox"/> Money Order <input type="checkbox"/> COD			Shipping Add \$3.00 per Unit	
Name _____			COD: Add 5%	
Address _____			TOTAL	
City / State / Zip _____				
Signature _____			Phone Number () _____	
<p>WAIVER: Since I, the undersigned, fully understand that the ownership of a cable decoder does not give the owner of the decoder the right to decode or view premium cable channels without proper authorization from their local cable company, I hereby declare under penalty of perjury that all products purchased, at any time, will only be used on cable TV systems with proper authorization from local officials or cable company officers in accordance with all applicable federal and state laws. Federal and various state laws provide for substantial criminal and civil penalties for unauthorized use.</p>				
Dated _____		Signed _____		

ATLANTIC CABLE DISTRIBUTING CENTER INC.
P.O. BOX 276 — GREENVALE, NY 11548
516 - 625-3550 [IMPORTANT: Have make and model # of the equipment used in your area.] **516 - 625-3532**

CIRCLE 197 ON FREE INFORMATION CARD

DRAWING BOARD

Seven-segment displays



ROBERT GROSSBLATT,
CIRCUITS EDITOR

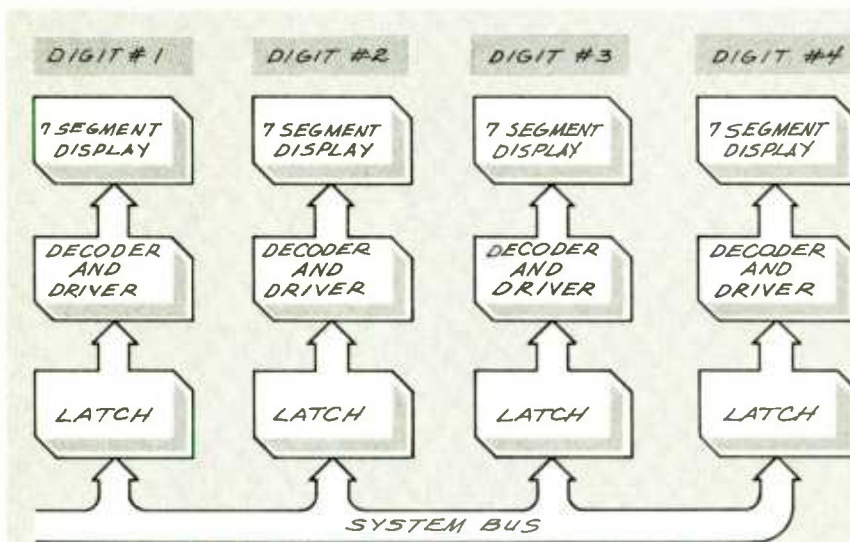


FIG. 1

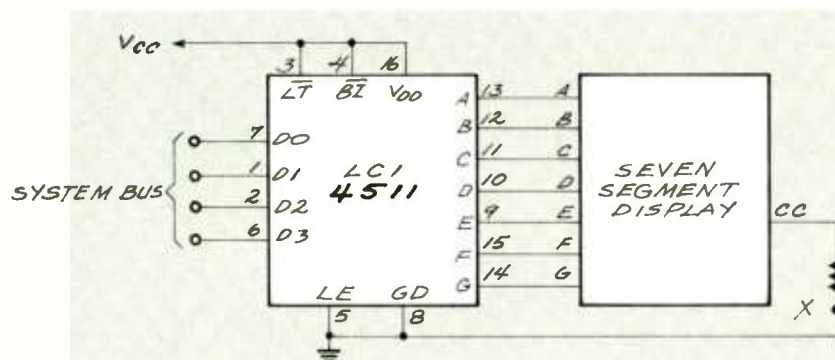


FIG. 2

WE'VE COVERED SOME OF THE BASICS of display multiplexing, but everything we've talked about so far involved single LED's. Not only that, but we've also looked at circuitry that only demonstrated the idea of multiplexing. As everyone knows, there's usually quite a difference between demonstration stuff and reality.

All LED-display multiplexing uses the same basic principle we've been talking about—strobing the LED's fast enough so that it seems as if they're constantly on. But, different circuits may have to be handled in different ways. Now let's try multiplexing a seven-segment display.

The block diagram in Fig. 1 is a

typical setup for a seven-segment display. Each display has a latch-and-decoder combination in front of it, and most circuits will use chips that combine the latch and driver in one package but the operation of the circuit is the same.

A practical implementation of that block diagram is shown in Fig. 2. The only thing that's missing from the display is multiplexing—and that's exactly what we're going to add to it. Although the design considerations are specifically aimed at the circuit that you see in Fig. 2, they're the same for any other circuit.

The first thing we need is a scan oscillator. You can use the one that we put together in the October issue, or any other one that you happen to have around. That isn't as silly as it sounds, because if you're adding display multiplexing to a circuit, the chances are that there already is a clock in that circuit. It's always a good idea to keep the amount of silicon on a board to a minimum, so it makes perfect sense to steal a clock signal from something in the circuit if you can.

The requirements for an oscillator are really minimal. As a matter of fact, there are only two requirements that are absolutely essential: The first is that the frequency be high enough to keep the display from flickering noticeably and the second is that the duty cycle will make the display bright enough.

The minimum frequency needed to avoid flicker depends on several different things—how many display elements are being

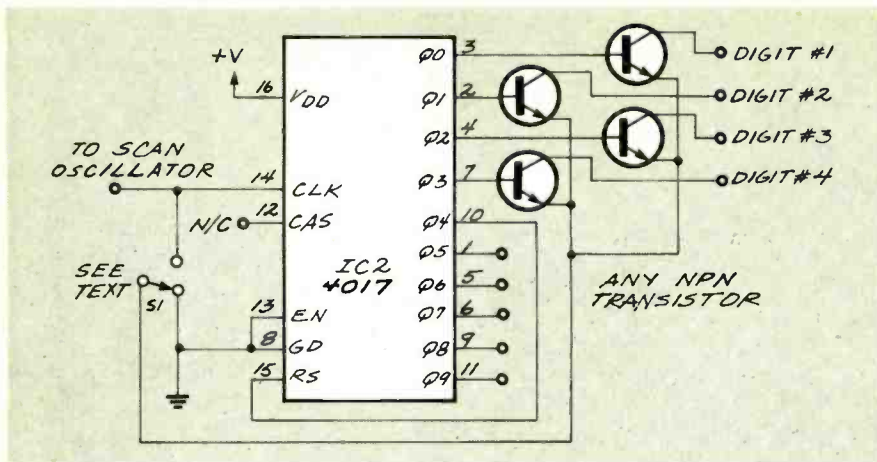


FIG. 3

multiplexed, the characteristics of the particular displays being used, and so on. But as long as you turn on each display at least once every hundredth of a second or so you don't have anything to worry about. You can do it less often but the demonstration circuit we've already discussed should have shown you that the minimum frequency varies from person to person. Most circuit designs that use multiplexing techniques have scan

frequencies of well over 1 kHz to keep the problem from even being considered.

The clock's duty cycle can determine how bright the display is going to be, depending on the particular circuit. The one we're looking at, for example, uses common-cathode displays; the more time the common-cathode terminal spends low, the brighter the display is going to be. If you're stealing a clock signal from an al-

ready-existing circuit, you'll probably be stuck with a given duty cycle. But, if you're generating your own, you have control over everything. Let's do it both ways.

The circuit in Fig. 3 is the same basic one that we used before. A few additions are needed, because the 4017 puts a high on the selected pin and we need a low to light the digit. The transistors are set up as simple switches to invert the 4017 outputs. It may seem as if the circuitry we're adding is unnecessarily cumbersome, but there are reasons for it.

It's true that we could replace the 4017 with a multiplexer that puts a low on the selected output rather than a high. Then we wouldn't need the transistors and we could have the display driven directly by the multiplexer's outputs. On the face of it, that seems like a good idea—fewer parts is a good thing...sometimes.

Using the circuit in Fig. 3 adds complexity but it also gives us two advantages that we'll discuss next month. R-E

TOP OF THE LINE

METERS

FLUKE

3 Years Manufacturers Warranty parts & labor

- 23 3 1/2 Digit DMM ... \$137.
- 73 3 1/2 Digit DMM ... 69.
- 75 3 1/2 Digit DMM ... 99.
- 77 3 1/2 Digit DMM ... 126.
- 83 3 1/2 Digit DMM ... 189.
- 85 3 1/2 Digit DMM ... 219.
- 87 4 1/2 Digit DMM true RMS ... 289.
- 8080A 4 1/2 Digit DMM true RMS ... 323.
- 8062A 4 1/2 Digit DMM true RMS ... 260.
- 37 Bench portable DMS ... 217.
- 8010A Bench portable true RMS ... 255.
- 8050A Bench portable true RMS ... 349.

FULL LINE AVAILABLE

BECKMAN

- DM10 3 1/2 Digit DMM ... \$38.
- DM73 Probe DMM Auto-ranging beeper, data hold ... 65.
- TECH350 Bench DMM with beeper, and more ... 222.
- HD181 Pocket DMM auto-ranging ... 149.
- HD182 3 1/2 Digit DMM auto-rang ... 169.
- HD183 3 1/2 Digit DMM auto-rang ... 199.
- DM850 4 1/2" digit, frequency counter, data hold ... 207.83
- Tech300 Diode Test ... 113.00
- Tech330 True RMS, Diode Test ... 206.00

SCOPES

HITACHI

- V-212 20 MHz dual trace scope ... \$385.
- V-423 40 MHz dual trace delayed sweep scope ... 799.
- V-660 60 MHz dual trace scope ...
- V-665 60 MHz dual trace cursor readout scope ...
- V-1060 100 MHz dual trace scope ...
- V-1065 100 MHz cursor readout scope ...
- V-6020 20 MHz digital storage scope ...

BECKMAN

- 9020 20MHz dual trace scope, component tester, delayed sweep ... 520.

"We ship anywhere. Your satisfaction is our main concern."
Lisa S. Hadar V.P., C.P.A.

—WE CARRY—

- *Soldering Supplies
- *Electronic Parts
- *Electrical Supplies
- *Test Instruments
- *Electronic Kits
- *Printed Circuit Material
- *Tools

IC TESTER

B & K

560 programmable IC tester ... \$297.00

POWER SUPPLIES

VIZ

- WP-703A Single 0-20VDC @ 0-500MA, single meter ... 146.
- WP-704A Single 0-40VDC @ 0-250MA, single meter ... 146.

SOLDERING SUPPLIES

Unger

- UTC 100 Temperature controlled soldering system ... 414.
- 8000 Temperature controlled soldering station ... 206.
- 8970 HD Heat gun (gives 1000 watts) ... 72.
- 1008 heat gun (gives 1000 watts) ... 38.

FREE CATALOG

REGULATED LINEAR POWER SUPPLY

\$24 ea.

Computer Grade
+ 5VDC @ 3 Amps
+ 12VDC @ 6 Amps
-5VDC @ 0.5 Amps
Bench Style/Great for Hobbists

MAGNAVOX AMBER PC MONITOR

\$55

- 12" Tube
- TTL Level Digital VIDED
- 20 MHz Bandwidth

Plug in WALL TRANSFORMER

Quantity Pricing Available

- 9.5 VDC @ 1 Amp '3.00
- 19 VAC @ 300 MA '1.50
- 25.4 VAC @ 300 Amp '1.95
- 14 VDC @ 200 MA '1.00

ASTEC POWER SUPPLY

MODEL #AA12690

INPUT \$19.95

- 1.15V 3.0 Amp
- 230V 1.5V Amp
- 50/60 HZ
- 113 WATT. MAX.

OUTPUT

- 5V 10 Amp
- 12V 2.5 Amp
- 12V 5 Amp UN REG.
- 12V 0.25 Amp

HEAVY DUTY MOTOR

Heavy-duty reversible dual shaft 12 volt P.M. DC Motor. Ideal for Robots & Tools, etc.

\$2.95 ea.

COMMODORE 64 CARTRIDGES

\$1.50 ea.

- Dragons Den • Simon Basic
- Viduzzles • ABC Voice • Easycalc

TOY MOTORS

6 to 12 VDC

50¢ ea.

PATCH CORDS

3 Ft. dual RCA color coded, stereo cords

50¢ ea.

PLUG-IN POWER WALL SUPPLY

Triple Output
+ 5VDC @ .75 Amps
+ 12VDC @ .12 Amps
- 12VDC @ .12 Amps

2.99 ea.

COMMODORE KEYBOARD

C16 4 Plugs

\$2.95 ea.

FANS

115V - 3" & 4" *6.00
24V - 3" & 4" *6.00
220V - 3" & 4" *5.00

TERMS: Minimum order \$10.00
N.J. residents 6% sales tax added.
Please call for shipping charges.

GET

19 Freeman St., Newark, New Jersey 07105

Toll Free: 800/645-9060

201/344-5700 Fax # 201/344-3282

GIANT ELECTRONICS INC.

CIRCLE 193 ON FREE INFORMATION CARD

CIRCLE 198 ON FREE INFORMATION CARD

RADIO-ELECTRONICS

94

www.americanradiohistory.com

SHORTWAVE RADIO

continued from page 42

The highest maximum ever observed was during cycle 19, which started in April of 1954 with a smoothed number of 3.3. Within 2-½ years it exceeded 159, which had been the previous record of cycle 3. By March 1958 the smoothed number was 201.3.

Conditions during the maximum year of cycle 19 have already become legendary. Worldwide ionospheric propagation in the amateur 6-meter band (50 MHz) was observed; the 16-meter (17 MHz) broadcast band was open around the clock on a worldwide basis. From 1957-1959, transatlantic and transcontinental TV DX was commonplace via the ionosphere on channels 2-5.

Cycle 20 was more "normal," reaching a maximum of 111 in November 1968. However, once the cycle began to decline it displayed some unusual characteristics in that it remained confined to the range between 100 and 110 for 21 months, from November 1967, to August 1970. To cycle 20 belongs the distinction of the longest plateau at maximum ever observed. Cycle 20 was also longer (11.5 years) than the average cycle, and took longer (7.4 years) to go from maximum to minimum.

Cycle 21

Cycle 21 began in June 1976 with a smoothed sunspot number of 12.2; many scientists and astronomers were fooled by that cycle, having expected it to be similar in intensity to cycle 20. Some forecasters had predicted that we'd see a maximum smoothed number under 100. However, within 27 months of its start, the smoothed number had already risen above 100, and by November of 1979 had become the second highest cycle ever recorded.

A Look at the Future

If we consider that the sun is about four billion years old, and that we have been keeping records for about 250 of those four billion years, it becomes apparent that we really don't know very much about sunspot cycles. We can, at best,

offer only educated guesses:

- Cycle 22 will reach its maximum in the summer of 1990.
- There is a strong possibility that cycle 22 will peak at 200 or above, and that it will be the highest ever observed.
- That would result in unprecedented radio conditions, including around-the-clock amateur 10-meter and Citizen's Band DX a reality. DX television will be commonplace, and TV interference levels will be significant. 17-MHz short-wave DX is likely to be possible around the clock during the summer months, and 21 MHz will be open for longer periods than ever before.
- During the next three years, short-wave DX will be better than ever before!

We'll have to wait and see, of course, how those predictions turn out. When will it reach its peak, will it be the highest cycle ever to be recorded, and will it reach 200? Those are questions that only time can answer.

Don't forget—you heard it here first!


Get A Complete Course In

ELECTRONIC ENGINEERING

8 volumes, over 2000 pages, including all necessary math and physics. 29 examinations to help you gauge your personal progress. A truly great learning experience.

Prepare now to take advantage of the growing demand for people able to work at the engineering level.

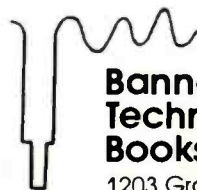Ask for our brochure giving complete details of content. Use your free information card number, or write us directly. \$99.95, Postage Included. Satisfaction guaranteed or money refunded.



**Banner
Technical
Books, Inc.**

1203 Grant Ave.
Rockford, IL 61103

CIRCLE 184 ON FREE INFORMATION CARD

CABLE-TV SIGNAL ELIMINATOR

\$30 each



30 DAY
MONEY-BACK
GUARANTEE

- All models in stock
- Fast, free shipping
- One year warranty
- Quantity discounts to 50%

TO ORDER, SEND CHECK OR MONEY ORDER TO:

STAR CIRCUITS - (DEPT. FJ)

P.O. BOX 8067

PENSACOLA PINES, FLORIDA 33008



ELIMINATE A CHANNEL
that you find unsuitable for family viewing, but is poorly scrambled by your cable company.

or



CLEAR UP A CHANNEL
that presently contains severe interference by ELIMINATING whatever signal is causing this.

NOTE: If picture and sound are equally affected, this is interference and CAN be removed by our product. If only picture is affected, this usually IS NOT interference and CANNOT be removed by our product.

WORKS ON CABLE TV OR BROADCAST TV

EXTERNAL ADJUSTMENTS ALLOW PRECISE TUNING TO ANY FREQUENCY REQUIRED

THREE MODELS AVAILABLE:

MODEL 35-Tuneable to channels 2 thru 5 (54-108 MHz)

MODEL 1022-Tuneable to channels 14(A) thru 22(1) (160-174 MHz)

MODEL 713-Tuneable to channels 7 thru 13 (174-216 MHz)



CHEMICAL SOLUTIONS

FREE CHEMTRONICS CATALOG!

Comprehensive new source for over 200 products used in electronic manufacturing and field service. Precision cleaning agents, flux removers, bulk solvents, circuit refrigerants, precision dusters, non-residual wipers, foam swabs, premoistened pads/swabs, antistatic compounds, conformal coatings, lubricants, adhesives, desoldering braids, rosin core solder and solder masking agents. Complete with technical specifications and application guide.



Chemtronics Inc.
681 Old Willets Path
Hauppauge, N.Y. 11788
516-582-3322

CIRCLE 54 ON FREE INFORMATION CARD

R-E Engineering Admart

Rates: Ads are 2 1/4" x 2 1/4". One insertion \$900. Six insertions \$875. each. Twelve insertions \$845. each. Closing date same as regular rate card. Send order with remittance to Engineering Admart, Radio Electronics Magazine, 500-B Bi-County Blvd., Farmingdale, NY 11735. Direct telephone inquiries to Arline Fishman, area code-516-293-3000. Only 100% Engineering ads are accepted for this Admart.

NO WAITING FOR COMPLETE, LOW PRICED, CHIP COMPONENT KITS

CC-1 Capacitor Kit contains 365 pieces, 5 ea. of every 10% value from 1pf to .33µf. CR-1 Resistor Kit contains 1540 pieces; 10 ea. of every 5% value from 100 to 10 megohm. Sizes are 0805 and 1206. Each kit is ONLY \$49.95 and available for Immediate One Day Delivery!

Order by toll-free phone, FAX, or mail. We accept VISA, MC, AMEX, COD orders, or company P.O.'s with approved credit. Call for free detailed brochure.



COMMUNICATIONS SPECIALISTS, INC.
426 West Telford Avenue • Orange, CA 92665-4296
Local (714) 998-3021 • FAX (714) 974-3420
Entire U.S.A. 1-800-854-0547

CIRCLE 176 ON FREE INFORMATION CARD

FCC LICENSE PREPARATION

The FCC has revised and updated the commercial license exam. The NEW EXAM covers updated marine and aviation rules and regulations, transistor and digital circuitry. THE GENERAL RADIOTELEPHONE OPERATOR LICENSE - STUDY GUIDE contains the necessary preparation for ONLY \$25.00.

WPT PUBLICATIONS
979 Young Street, Suite A
Woodburn, Oregon 97071
Phone (503) 981-6122

CIRCLE 181 ON FREE INFORMATION CARD

MIDI PROJECTS



BP182—MIDI interfacing enables any so equipped instruments, regardless of the manufacturer, to be easily connected together and used as a system with easy computer control of these music systems. Combine a computer and some MIDI instruments and you can have what is virtually a programmable orchestra. To get your copy send \$6.95 plus \$1.25 for shipping in the U.S. to Electronic Technology Today Inc., P.O. Box 240, Massapequa Park, NY 11762-0240.

New Scanner by AOR

100 Channels
800 MHz



• Includes antenna, rechargeable battery, charger/adaptor & belt clip. Full range of optional accessories available.

• Covers 27-54 MHz, 108-174 MHz, 406-512 MHz, and 800-950 MHz.

• 5 Scan Banks and 9 Search Banks.

• 25 Day Satisfaction Guarantee. Full Refund if not Satisfied.

• No Frequencies cut out.

• Size: 2" x 5 1/4" x 1 1/2" wt: 12 oz.

AR900

Total Price, Freight Prepaid
(Express Shipping Optional)

\$299.00



COMMUNICATIONS

10707 E. 106th St. Indpls., IN 46256

Toll Free 800-445-7717

Visa and MasterCard
(COD slightly higher)

In Indiana 317-849-2570 Collect FAX (317) 849-8794

CIRCLE 199 ON FREE INFORMATION CARD

BUY BONDS

HARDWARE HACKER

continued from page 36

Two ready-to-use solid-state digital compasses are now available from *AutoHelm* and *KVH Industries*. Further info on those appears in issue ten of *Speleonics*.

For this month's contest, just tell me something new and unusual that you would do with a solid-state compass, particularly if the compass measured amplitude as well as direction.

There will be the usual *Incredible Secret Money Machine* book prizes, along with an all expense paid (FOB Thatcher, AZ) *tinaja* quest for two for the very best entry of all.

New tech lit

Siliconix has some free samples available on their new ultra-fast DMOS transistors and analog gates. Those dudes switch in less than a nanosecond and can have their on-resistance value as small as 19 ohms. Obvious uses are in video switching and for various special-effect generators.

Crystal Semiconductor has an amazing new 16-bit A/D converter available with pricing in the \$20 range. The part number is CS-5501.

It is very easy to interface with most any personal computer.

The *Silicon Systems* people have a pair of new data books out, one on *Microperipheral Products*, and a second on *Telecommunications*. Products described include modems, call-progress detectors, disk-drive chips, and precision motor controllers.

For information on alternates to traditional power generation that include cogeneration, solar energy, management, conservation, and superconductivity, you might want to check into the *Association of Energy Engineers*.

Turning to my own products, for lots more information on computer-circuit modeling, you might like to try out my *Micro Cookbooks*, volumes I and II. And, yes, we finally have complete sets of edited and up-graded *Hardware Hacker* reprints available, as well as plenty of other great stuff on the *PostScript* language.

Let's hear from you.

R-E



"Help! The laser printer is malfunctioning again!"

1988 ANNUAL INDEX

Radio Electronics Volume 59 and COMPUTER DIGEST Volume 5

Abbreviations: (AR)Antique Radio; (ARE) Ask Radio-Electronics' (AUD)Audio Update; (C)Construction; (CC)Communications Corner; (L)Department; (DB)Drawing Board; (DN)Designers Notebook; (ED)Editorial; (ER)Equipment Reports; (HH)Hardware Hacker; (LTR)Letter; (NI)New Ideas; (PCS)PC Service; (SC)Service Clinic; (SR)Shorwave Radio; (SOSS)State of Solid State

A

AD converter and D/A Conversion(Lancaster)(HH) (Lancaster)(HH)	Sep 68 May 69, Aug 69
A.W. Sperry VH-600 Voltage Detector(ER)	Jun 26
Absolute navigation (Lancaster)(HH)	Jul 69
Acoustics Can you hear the difference?(Klein)(AUD)	Aug 75, Sep 79
Alcohol-level tester(DiLalo)(C)	Oct 51
Amplified Speaker (McClellan)(C)	Sep 41,(PCS)Sep 88
Ampifier, Micro-Sized (Polimene)(C)	Aug 33
Analog computer interfacing (Lancaster)(HH)	Aug 69
Ancient Transformers, Tubes, and Speakers (Fitch)(AR)	Jan 84
Antenna Direction-finder(ARE)	Jul 12
Phantom Hand, The(Friedman)(CC)	Jan 82
Antique Radio Antique Radio(D)(Fitch)	Jan 84, Mar 80, Apr 82, Jun 80, Jul 80,
Ancient Transformers, Tubes, and Speakers	Jan 84
Antique radios for antique autos	Jul 80,(LTR)Sep 16,(LTR)Dec 14
Drawing radio schematics	Jun 80
More on antique parts	Mar 80
Our Readers Write	Apr 82
Early Days of Radio, The(Clifford)	Aug 57
Apple Appletigs monitors(Lancaster)(HH)	Mar 71
-computing books(Lancaster)(HH)	Sep 68
Arkon Wire-Free IR Headphones (ER)	Feb 26
Ask R-E(D)	Jan 22, Feb 12, May 12, Jun 14, Jul 12, Aug 10, Sep 12, Oct 12, Nov 12, Dec 12 (LTR)Oct 16
Atari	
Audio Amplified Speaker(McClellan)(C)	Sep 41
Antique radios for antique autos(Fitch)(AR)	Jul 80
Arkon Wire-Free IR Headphones (ER)	Feb 26
Audio Update(D)(Klein)	Jan 78, Feb 80, Mar 36, Apr 80, May 76, Jun 74, Jul 74, Aug 75, Sep 79, Oct 80, Nov 42, Dec 91
Audio answerman returns, The	Oct 80
Audio Engineering Society, The	Nov 42, Dec 91
Can you hear the difference?	Aug 75, Sep 79
Debunking Audio Myths	Mar 36
Documentation Difficulties	Feb 80
Getting the noise out of FM	Jun 74
History of Hi-Fi	Apr 80
Positive and negative feedback	Jan 78
Predicting the audio future	May 76
Two common record-player problems	Jul 74
Differential Audio- Distortion Analyzer(Friedman)(C)	Oct 62
"hum"(ARE)	Jan 22
Phantom Hand, The(Friedman)(CC)	Jan 82
Scrambling System(Lindell)(C)	Jan 51, (PCS)Jan 67,(LTR)Mar 14
Subwoofer Simulator(Hill)(C)	May 57
Surround Sound Decoder(Hill)(C)	Apr 45
/Video Switcher(Templin)(C)	Feb 65, (PCS)Feb 71,(LTR)Apr 14
Wireless Speaker System (Graf & Sheets)(C)	Aug 37,(PCS)Aug 66
Stereo Link(Graf & Sheets)(C)	Mar 54, Apr 50

Automobile

Automobile Battery Monitor(ARE)	Jan 22
Electronics(Lancaster)(HH)	Jan 71
Radio Data System(Friedman)	Dec 65
Radio for AM DX'ing(ARE)	Oct 12

B

Bar Codes (Lancaster)(HH)	Apr 72
Beckman HD150 Series DMMs (ER)	Aug 20
Blue Boxes	(LTR)Jan 24,(LTR)Mar 14,
Breath-Alert Alcohol Tester (DiLalo)(C)	Oct 51,(PCS)Oct 69
Bulletin Board Using the RE-BBS	May 84

C

CD-I, The Potential of (Fenton)(ED)	Apr 4
Cable-TV converter hum (ARE)	May 12
Calibrating VCR Counters (Blechnan)	Jan 57, (LTR)Apr 14,(LTR)May 16
Calibration (Martin)	Jun 57,(LTR)Aug 12,(LTR)Sep 16
Can you hear the difference? (Klein)(AUD)	Aug 75, Sep 79
Canon FAX-L920 Laser Facsimile (ER)	Dec 24
Car (see Automobile)	
Carbon-filter components (Klein)(AUD)	Oct 80
Cellular phones	(LTR)Jan 24
Cheap Color Fuser, A (Lancaster)(HH)	Nov 32
Clock, I/O and BIOS (Grossblatt)(DB)	Jul 76
Coils, Coping With (Powell)	Nov 67
Command Communications TF500 Autoswitch(ER)	Nov 22
Communications Communications Corner (Friedman)(D)	Jan 82, Feb 32, Mar 33, May 80, Aug 24, Sep 84, Oct 36, Nov 78
Double your modem's data throughput	Nov 78
Hybrid Networks Make Signals Invisible	Mar 33
Multiplexing by color	Oct 36
New way to communicate, A	Sep 84
Phantom Hand, The	Jan 82
Pinning the Blame	Feb 32
Real personal- communications service, A	Aug 24
When a shield isn't a shield	May 80
Facts on Fax, The (Friedman)	Nov 45
ISDN: Telephone of Tomorrow (Summer)	Oct 41,(LTR)Dec 14
Parasitic Signaller (Crooks)(NI)	Feb 98
HFBC 87: Planning the Shortwave Bands (Leinwoll)	Feb 55
National Radio-Paging System, A (Friedman)	Jan 41
Radio Data System (Friedman)	Dec 65
Compact discs, recordable Read/Write Compact Discs(Fenton)	Aug 8
Compass, Solid-State Digital (Lancaster)(HH)	Dec 33
Computer (See Also Computer Digest, page 100) Clock, I/O and BIOS(Grossblatt)(DB)	Jul 76
Copy protection(Grossblatt)(DB)	Sep 82
Fliuke 90 Series	

Microprocessor Board Tester (ER)	May 19
General Purpose Interface Bus (Martin)	Jul 57, Aug 53
Graphics on VCRs	(LTR)Feb 14
Interactive TV (Fenton)	Dec 45
Memory expansion (Lancaster)(HH)	Jun 65
Modeling (Lancaster)(HH)	Dec 33
Multiplexing and Dynamic RAM (Grossblatt)(DB)	Nov 74
Psion Organiser II	
Handheld Computer (ER)	Sep 24
REACTS (Roberts, Tucker & Bybee)(C)	Jan 67, Feb 47, Mar 49, Apr 52, May 50, Jun 51, Jul 46, Aug 45, Sep 45, Oct 65, Nov 65
Seven-segment display (Grossblatt)(DB)	Dec 93
Technology Marketing's PC Weather Pro (ER)	Mar 23
Z80 hardware (Grossblatt)(DB)	Jun 71
Construction Amplified Speaker (McClellan)	Sep 41
Audio Scrambling System(Lindell)	Jan 51
/Video Switcher(Templin)	Feb 65
Breath Alert Alcohol Tester (DiLalo)	Oct 51
Differential Audio-Distortion Analyzer (Friedman)	Oct 62
Digital L/C Meter(Heckt)(C)	Jul 41, Aug 50, (PCS)Jul 66,(LTR)Nov 14 Nov 59, Oct 58
Telephone Lock (Sokolowski)	
Electronic Knighthood(di Zerega)	Apr 35
Thermometer (Spiwak)	Oct 55
Tornado (Iannini)	Mar 43
Gated-Sync Decoder (Pence)(C)	Dec 49,(PCS)Dec 77
In-Circuit Digital IC Tester (Green)	Feb 46, Sep 37,(PCS)Sep 88, Oct 108
Micro-Sized Amplifier (Polimene)	Aug 33
Powerline Monitor (McClellan)	Nov 55
REACTS (Roberts, Tucker & Bybee)(C)	Jan 67, Feb 47, Mar 49, Apr 52, May 50, Jun 51, Jul 46, Aug 45, Sep 45, Oct 65, Nov 65
Radiation Monitor (Sythe)	Jun 41, Jul 51
60-Hz Timebase (Gifford)	Jan 56
Soil Moisture Meter (Jimenez)	Jun 49
Subwoofer Simulator (Hill)	May 57
Surround Sound Decoder (Hill)	Apr 45
True RMS Converter for your DMM (Brown)(C)	Dec 61,(PCS)Dec 77
TV-Derived Frequency Standard (Stroud)	Apr 55
Uninterruptible Power Supply (Perkins)	Jan 44
Versatile Function Generator (Wannamaker)	May 39
Video-Edit Controller (Nery)(C)	Dec 57,(PCS)Dec 77
Wireless Speaker System(Graf & Sheets)(C)	Aug 37, (PCS)Aug 66
Stereo Link (Graf & Sheets)(C)	Mar 54, Apr 50
Consumer Electronics for the Consumer (Fenton)(ED)	Mar 4
Control system, REACTS(Roberts, Tucker & Bybee)(C)	Mar 49, May 50, Jun 51
Coping With Coils (Powell)	Nov 67
Copy protection (Grossblatt)(DB)	Sep 82
"Crowbar" circuits (ARE)	Jan 22,(LTR)Apr 14
CPU board, REACTS(Roberts)(C)	Mar 49
module, REACTS(Roberts)(C)	Apr 52
CRT controller, REACTS(Roberts)(C)	Aug 45
Current-differencing op-amps Norton Op-Amps, Working with(Marston)	Dec 69

D

Databank resources(Lancaster)(HH) Aug 69
 Debunking Audio Myths(Klein)(AUD) Mar 36
 Decoder, Gated-Sync(Pence)(C) Dec 49,(PCS)Dec 77
 Designer's Notebook(D)(Grossblatt) Jan 80
 Sinewave oscillators, making Jan 80
 Desktop publishing (LTR)May 16
 Differential Audio-Distortion Analyzer(Friedman)(C) Oct 62
Digital
 Encoding(Friedman)(CC) Sep 84
 IC tester, In-Circuit(Green)(C) Feb 46, Sep 37,
 (PCS)Sep 88, Oct 108
 Potentiometer(Lancaster)(HH) Jan 71
 L/C Meter(Heckt)(C) Jul 41, Aug 50,
 (PCS)Jul 66, (LTR)Nov 14
 Multimeters
 Beckman HD150 Series DMMs(ER) Aug 20
 Solid-State Compass(Lancaster)(HH) Dec 33
 Tachometer (LTR)May 16
 Telephone Lock(Sokolowski)(C) Oct 58, Nov 59
 Disk storage(ARE) Jun 14
Displays
 Let's think about our display(Grossblatt)(DB) Aug 80
 More on multiplexing(Grossblatt)(DB) Oct 99
 Seven-segment(Grossblatt)(DB) Dec 93
 Documentation Difficulties(Klein)(AUD) Feb 80
 Double your modem's data throughput(Friedman)(CC) Nov 78
Drawing Board(D)(Grossblatt)
 Clock, I/O and BIOS Jul 76
 Copy protection Sep 82
 Let's think about our display Aug 80
 More on multiplexing Oct 99
 Multiplexing and dynamic RAM Nov 74
 Seven-segment display Dec 93
 Z80 hardware Jun 71
 Drawing radio schematics(Fitch)(AR) Jun 80
DX'ing
 Shortwave Radio(D)(Leinwoll) Apr 78, Jun 78, Aug 78
 Oct 39, Dec 73
Dynamic
 Headroom test(Klein)(AUD) Dec 91
 RAM(Grossblatt)(DB) Jun 71

E

Early Days of Radio, The(Clifford) Aug 57
Editorial(Fenton)
 Consumer Electronics for the Consumer Mar 4
 Potential of CD-I, The Apr 4
 Some Happenings at the FCC Jan 4
 Electron flow (LTR)Feb 14
Electronic
 Knighthood(di Zerega)(C) Apr 35, (LTR)Aug 12
 Lock (LTR)Feb 14
 Music circuits(Lancaster)(HH) Feb 73
 References(Lancaster)(HH) Sep 68
 Security Systems(Glasser) Apr 59
 Thermometer(Spiwak)(C) Oct 55, (PCS)Oct 69
 Tomado(Iannini)(C) Mar 43
Equipment Reports
 A.W. Sperry VH-600 Voltage Detector Jun 26
 Arkan Wire-Free IR Headphones Feb 26
 Beckman HD150 Series DMMs Aug 20
 Canon FAX-L920 Laser Facsimile Dec 24
 Command Communications TF500 Autoswitch Nov 22
 Fluke 90 Series Microprocessor Board Tester May 19
 Heath GR-9009 Portable Color TV Jan 32
 Lattice Semiconductor GAL39V18 GAL Development Kit Oct 24
 Philips ECG RCT7501 Remote Control Tester Jul 22
 Psion Organiser II Handheld Computer Sep 24
 Technology Marketing's PC Weather Pro Mar 23
 Videonic's DirectEd Apr 27

F

FCC regulations
 Part 15(Klein)(AUD) Oct 80
 Some Happenings at the FCC(Fenton)(ED) Jan 4
Facsimile
 Canon FAX-L920 Laser Facsimile(ER) Dec 24
 1940 to 1988(Helber) Nov 50
 The Facts on Fax(Friedman) Nov 45
 Fiber optics(Friedman)(CC) Oct 36
 Finding computer parts(Lancaster)(HH) Jun 65
 Fingertip Olympics(Blake)(NI) Jul 34
 Fisher 400 stereo receiver(ARE) Feb 12
 Fluke 90 Series Microprocessor Board Tester(ER) May 19
FM
 hiss(Klein)(AUD) Oct 80
 Radio Data System(Friedman) transmitter Dec 65
 Wireless Stereo Link(Graf & Sheets)(C) Mar 54, Apr 50
 Frequency Standard, TV-Derived (Stroud)(C) Apr 55, (LTR)Jul 14
 Function Generator, Versatile (Wannamaker) May 39, (PCS)May 100
 (LTR)Aug 12, (LTR)Sep 16
 Fuser, A Cheap Color Fuser(Lancaster)(HH) Nov 32

G

GAL development kit, Lattice Semiconductor(ER) Oct 24
 Geiger counter
 Radiation Monitor(Sythe)(C) Jun 41
 General Purpose Interface Bus(Martin) Jul 57, Aug 53
Generator
 60-Hz Timebase(Gifford) Jan 56
 Sinewave, Simple(Nassar)(NI) Apr 77
 Versatile Function(Wannamaker) May 39, (PCS)May 100
 (LTR)Aug 12, (LTR)Sep 16
 Getting the noise out of FM(Klein)(AUD) Jun 74
 Ghost busting(Darr)(SC) May 31
 Groove skipping(Klein)(AUD) Jul 74

H

HDTV Update(Fenton) Jan 16
Haffer test
 (Klein)(AUD) Sep 79
 Differential Audio-Distortion Analyzer(Friedman)(C) Oct 62
Hardware
 Clock, I/O and BIOS(Grossblatt)(DB) Jul 76
 Hardware Hacker(D)(Lancaster) Jan 71, Feb 73, Mar 71
 Apr 72, May 69, Jun 65, Jul 69, Aug 69, Sep 68
 Oct 71, Nov 32, Dec 33
 A/D and D/A Conversion Sep 68
 Cheap Color Fuser, A Nov 32
 Finding parts, computer Communications, and more Jun 65
 Making PC board layouts Jul 69
 Patents and patenting Oct 71, (LTR)Dec 14
 Refilling toner cartridges May 69
 Remote controls and a great A/D converter Aug 69
 Superconductors for the Hacker Feb 73
 Surplus EGR Valves Apr 72
 Tips, Products, and Publications Mar 71
 Welcome to a new column Jan 71
 REACTS(Roberts)(C) May 50, Jun 51, Jul 46
 Head unit, R-E Robot(Sams)(C) Jan 67
 Hear-Ear Amplifier(Polimene)(C) Aug 33
 Hearing aids(ARE) May 12
 Heat pumps
 Thermoelectric Coolers(Shields) May 61
 Heath GR-9009 Portable Color TV(ER) Jan 32
 HFBC 87
 Planning the Shortwave Bands(Leinwoll) Feb 55
History (See also Antique Radio)
 Early Days of Radio, The(Clifford) Aug 57
 Facsimile: 1940 to 1988(Helber) Nov 50
 of Hi-Fi(Klein)(AUD) Apr 80
 Home automation
 REACTS(Bybee)(C) Oct 65, Nov 65
 Hybrid Networks Make Signals(Friedman)(CC) Mar 33

I

IBM video standard(ARE) Jul 12
 In-Circuit Digital IC Tester(Green)(C) Feb 46, Sep 37, (PCS)Sep 88, Oct 106
 IC's, miniature
 Nanoelectronics(Bernard) Sep 49
 Inductance/Capacitance Meter, Digital(Heckt)(C) Jul 41, Aug 50
 Inductors
 Coping With Coils(Powell) Nov 67
Infrared
 Receivers(Lancaster)(HH) Aug 69
 Wireless Speaker System(Graf & Sheets)(C) Aug 37
 Interactive TV(Fenton) Dec 45
Interface
 Bus, General Purpose(Martin) Jul 57, Aug 53
 IBM to Apple(Lancaster)(HH) Mar 71
 Invention protection(LTR) Feb 14
 ISDN: The Telephone of Tomorrow(Summer) Oct 41, (LTR)Dec 14

K

Kit building
 Heath GR-9009 Portable Color TV(ER) Jan 32
 Knight, Electronic(di Zerega)(C) Apr 35
L
 LAN(Lancaster)(HH) Oct 71
 LED
 Bargraph displays, Using(Marston) Mar 59
 Let's think about our display(Grossblatt)(DB) Aug 80
 VU meter(ARE) Aug 10
 Laser Listener (LTR)May 15, Nov 14
 Lattice Semiconductor GAL39V18 GAL Development Kit(ER) Oct 24

L

Let's think about our display(Grossblatt)(DB) Aug 80
 Letters(D) Jan 24, Feb 14, Mar 14, Apr 14
 May 14, Jun 22, Jul 14, Aug 12
 Sep 16, Oct 16, Nov 14, Dec 14
 Linear IC's(SOSS) Jun 38
 Liquid-level detectors(Lancaster)(HH) Feb 73
 LM13600(Marston) Jul 61
Logic
 Circuit Design Basics(Sharp) Sep 57
 Devices
 Lattice Semiconductor GAL39V18 GAL Development Kit(ER) Oct 24
 Low-pressure pneumatics(Lancaster)(HH) Apr 72

M

Macroscrubber (LTR)Apr 14, Jul 14, Aug 12, Nov 14
Magnetic
 Fields(Lancaster)(HH) Dec 33
 Memories, New(Gillette) Apr 65
Making
 PC board layouts(Lancaster)(HH) Jul 69
 Your Own PC Boards(Laron) Feb 51, (LTR)Apr 14, Jul 14
Memory
 Clock, I/O and BIOS(Grossblatt)(DB) Jul 76
 Multiplexing and dynamic RAM(Grossblatt)(DB) Nov 74
 Miniaturization
 Nanoelectronics(Bernard) Sep 49
 Micro-Sized Amplifier(Polimene)(C) Aug 33, (PCS)Aug 66
 Microprocessor fundamentals(Lancaster)(HH) Feb 73
Modem
 Double your modem's data throughput(Friedman)(CC) Nov 78
 Moisture Meter, Soil(Jimenez)(C) Jun 49
 Monostable Multivibrators, Working with(Marston) Apr 65
 More on multiplexing(Grossblatt)(DB) Oct 99
Multiplexing
 and dynamic RAM(Grossblatt)(DB) Nov 74
 by color(Friedman)(CC) Oct 36
 More on multiplexing(Grossblatt)(DB) Oct 99

N

Nanoelectronics(Bernard) Sep 49
 National Radio Paging System, A(Friedman) Jan 41
 New Books(D) Aug 23
 New Ideas(D) Feb 98, Apr 77, Jul 34
 Fingertip Olympics Jul 34
 Parasitic Signaller Feb 98
 Sine-wave Generator, Simple Apr 77
 New Products(D) Jan 34, Feb 32, Mar 26, Apr 36
 May 24, Jun 32, Jul 26, Aug 30
 Sep 32, Oct 32, Nov 24, Dec 26
 New way to communicate, A(Friedman)(CC) Sep 84
 NiCd charging(ARE) May 12
 Non-clone coverage (LTR)Sep 16
 Norton Op-Amps, Working with(Marston) Dec 69

O

Old capacitors, disposing of(ARE) Feb 12
 Omnicron copier(Lancaster)(HH) Nov 32
Op-amps
 Working with OTA's(Marston) May 63, Jul 61
 Working with Norton Op-Amps(Marston) Dec 69
Optical Media
 Read/Write Compact Discs Aug 8
 Oscillators, sinewave(Grossblatt)(DN) Jan 80
 Our Readers Write(Fitch)(AR) Apr 82

P

PA-speaker placement(ARE) Jul 12
 Parasitic Signaller(Crooks)(NI) Feb 98
 Patents and patenting(HH) Oct 71, (LTR)Dec 14
PC boards
 Layouts(Lancaster)(HH) Jul 69
 Making Your Own(Laron) Feb 51
PC Service(D)
 Jan 67, Feb 71, Mar 69, Apr 69
 May 100, Jun 63, Jul 66, Aug 66
 Sep 88, Oct 69, Nov 71, Dec 77
Peltier devices
 Thermoelectric Coolers(Shields) May 61
 Pendulums(ARE) Jun 14, (LTR)Oct 16
 Personalized Cassettes(Klein)(AUD) Nov 42
 Perspective Transforms(Lancaster)(HH) Jun 65
 Phantom Hand, The(Friedman)(CC) Jan 82
 Philips ECG RCT7501 Remote Control Tester(ER) Jul 22
 Pinning the Blame(Friedman)(CC) Feb 32
 Plasma Globe
 Electronic Tornado(Iannini)(C) Mar 43, (PCS)Mar 69

Posistors(Lancaster)(HH) Mar 71
 Positive and negative feedback(Klein)(AUD) Jan 78
 PostScript language(Lancaster)(HH) May 69
 Potential of CD-I, The(Fenton)(ED) Apr 4
 Power Supply, Uninterruptable(Perkins)(C) Jan 44

Powerline
 Interference(ARE) Aug 10
 Monitor(McClellan)(C) Nov 55,(PCS)Nov 71
 Predicting the audio future(Klein)(AUD) May 76

Pressure
 Measurements(Lancaster)(HH) Oct 71
 Transducers(Lancaster)(HH) Apr 72,Oct 71
 Programmable Logic Devices(Meyer) Feb 59,Mar 63
 Propagation, Radio Wave(Leinwoll)(SR) Apr 78

Psion Organiser II
 Handheld Computer(ER)Sep 24
 Psychoacoustics(Klein)(AUD) Aug 75,Sept 79

Pulse generators
 60-Hz Timebase(Gifford) Jan 56
 Working with Monostable Multivibrators(Marston) Apr 65

R

Radalert Radiation Monitor(Sythe)(C) Jun 41,Jul 51,
 (LTR)Sep 16,(LTR)Oct 16,(PCS)Jun 63

Radio
 Data System(Friedman) Dec 65
 Drawing radio schematics(Fitch)(AR) Jun 80
 Early Days of Radio, The(Clifford) Aug 57

General conditions and fundamentals(Leinwoll)(SR) Oct 39
 for July and August(Leinwoll)(SR) Aug 78

HFBC 87: Planning the Shortwave Bands(Leinwoll) Feb 55
 Pinning the Blame(Friedman)(CC) Feb 32
 Station WWV(Leinwoll)(SR) Dec 38

What makes shortwave possible(Leinwoll)(SR) Jun 78
 New Column Debuts, A(Leinwoll)(SR) Apr 78

R-E Robot(Sams)(C) Jan 67,(LTR)Mar 14

REACTS(Roberts, Tucker & Bybee)(C) Jan 67,
 Feb 47,Mar 49,Apr 52, May 50,Jun 51,Jul 46,
 Aug 45,Sept 45, Oct 65,Nov 65

Add X-10 Compatibility(Bybee)(C) Nov 65,(PCS)Nov 71
 Control system(Roberts, Tucker & Bybee)(C) Mar 49,
 May 50,Jun 51,

CPU
 board(Roberts)(C) Mar 49
 module(Roberts)(C) Apr 52,(PCS)Apr 69

CRT Controller(Roberts)(C) Aug 45
 RAM/PROM programmer (Roberts)(C) May 50,(PCS)May 56

Terminal interface(Tucker)(C) Sep 45
 Wireless Home Automation(Bybee)(C) Oct 65
 Universal I/O(Roberts)(C) Jul 46,(PCS)Jul 66

Read/Write Compact Disc(Fenton) Aug 8
 Reader-Help-Reader(D) Aug 102

Real personal-communications service(Friedman)(CC) Aug 24

Refilling toner cartridges, and more(Lancaster)(HH) May 69
 Regulators, battery powered(Lancaster)(HH) Apr 72

Remote controls and a great A/D converter(Lancaster)(HH) Aug 69
 Ring-equivalency numbers(Lancaster)(HH) Jul 69

Robotics
 R-E Robot(Sams)(C) Jan 67,(LTR)Mar 14

RS-232 Interface (See also Computer Digest)
 (Lancaster)(HH) Jun 65
 (PCS) Aug 66,(LTR)Sep 16

Russian tubes(ARE) Oct 12,(LTR)Dec 14

S

Santa Claus machine(Lancaster)(HH) Jan 71

Satellite paging
 National Radio Paging System(Friedman) Jan 41

Scrambling
 Audio Scrambling System(Lindell)(C) Jan 51

Security
 Digital Telephone Lock(Sokolowski)(C) Nov 59
 Electronic Security Systems(Glasser) Apr 59

Semiconductors, Testing(Byers) Jan 63
 Semiconductor replacements(Lancaster)(HH) May 69

Service Clinic(D)(Darr) May 31
 Ghost busting May 31

Servicing
 Ghost busting(Darr)(SC) May 31
 VCRs(Phelps) Sep 53

Seven-segment display(Grossblatt)(DB) Dec 93
 Shielding(Friedman)(CC) May 80

Shortwave converters(ARE) Oct 12
Shortwave Radio(D)(Leinwoll) Apr 78,Jun 78,Aug 78,
 Oct 39,Dec 38

General conditions and fundamentals for July and August Aug 78
 New Column Debuts, A Radio Station WWW Dec 38
 What makes shortwave Possible Jun 78

Sinewave
 Generator, Simple(Nassar)(NI) Apr 77
 Oscillators, making(Grossblatt)(DN) Jan 80

60-Hz Timebase(Gifford) Jan 56
 16-bit converter chips(Lancaster)(HH) Sep 68
 Soil Moisture Meter(Jimenez)(C) Jun 49

Solid-state
 Digital Compass(Lancaster)(HH) Dec 33
 tube replacement(ARE) Sep 12

Some Happenings at the FCC(Fenton)(ED) Jan 4
 Spark-gap capacitor(ARE) Nov 12

Speaker
 Amplified(McClellan)(C) Sep 41
 Impedance(Klein)(AUD) Oct 80
 Leads, small(ARE) Feb 12,(LTR)May 16
 Overload(ARE) May 12

State of Solid State(D)(Scott) Jun 38
 Linear IC's Jun 38

Stereo(See also Audio)
 Can you hear the difference?(AUD) Aug 75,Sept 79
 Debunking Audio Myths(AUD) Mar 36
 Getting the noise out of FM(AUD) Jun 74
 Subwoofer Simulator(Hill)(C) May 57
 Surround Sound Decoder(Hill)(C) Apr 45

Wireless
 Speaker System (Graf & Sheets)(C) Aug 37,(PCS)Aug 66
 Stereo Link(Graf & Sheets)(C) Mar 54, Apr 50

Subwoofer performance(Klein)(AUD) Nov 42
 Subwoofer Simulator(Hill)(C) May 57,(PCS)May 100

Sunspots(Leinwoll)(SR) Oct 39
 Superconductivity Breakthroughs(Fenton) Feb 43
 Superconductors(Lancaster)(HH) Feb 73,Mar 71,Jun 65

Surface-mount technology (LTR)Jan 24,Feb 14
 Letters Aug 33
 Micro-Sized Amplifier(Polimene)(C) Aug 33

Surplus EGR Valves(Lancaster)(HH) Apr 72

Surround Sound
 Decoder(Hill)(C) Apr 45,(PCS)Apr 69,(LTR)Jun 22

Switching Circuits
 Logic Circuit Design Basics(Sharp) Sep 57

Synchronous Inverters (ARE) Feb 12
 (Lancaster)(HH) Sep 68
 Synergy Card(CD) (PCS)Nov 71

T

Technical literature(Lancaster)(HH) Jan 71
 Technology Marketing's PC Weather Pro(ER) Mar 23

Telephone
 Command Communications TF500 Autoswitch(ER) Nov 22

-coupling transformers(Lancaster)(HH) Nov 32
 ISDN: The Telephone of Tomorrow(Summer) Oct 41,(LTR)Dec 14

-line recording phones(Lancaster)(HH) Jul 69
 Ring detectors(Lancaster)(HH) May 69
 Tele-Guard II

Digital Telephone Lock(Sokolowski)(C) Oct 58,Nov 59,(PCS)Nov 71

Television(See Video, see also TV)
 Terminal interface REACTS(Tucker)(C) Sep 45

Test Equipment
 A.W. Sperry VH-600 Voltage Detector(ER) Jun 26
 Beckman HD150 Series DMMs(ER) Aug 20

Digital
 L/C Meter(Heckl)(C) Jul 41,Aug 50
 In-Circuit IC Tester(Green)(C) Feb 48

Powerline Monitor(McClellan)(C) Nov 55
 Fluke 90 Series Microprocessor Board Tester(ER) May 19

Generator
 Sine-wave Simple(Nassar)(NI) Apr 77
 Versatile Function(Wannamaker)(C) May 39

In-Circuit Digital
 IC Tester(Green)(C) Sep 37
 Philips ECG RCT7501

Remote Control Tester(ER)Jul 22
 True RMS Converter for your DMM(Brown)(C) Dec 61,(PCS)Dec 77

TV-Derived Frequency Standard(Stroud)(C) Apr 55
 Testing Semiconductors(Byers) Jan 63,Aug 61

Thermoelectric Coolers(Shields) May 61
 Thermometer, Electronic(Spiwak)(C) Oct 55

Tips, Products, and Publications(Lancaster)(HH) Mar 71
 Touch-sensitive lamp(ARE) Oct 12

True North(ARE) Sep 12,(LTR)Nov 14
 True RMS Converter for your DMM(Brown)(C) Dec 61,(PCS)Dec 77

TTL devices
 Testing Semiconductors(Byers) Aug 61
 Transmission Identification(Friedman)(CC) Feb 32

Transmitter
 FM Wireless Stereo Link(Graf & Sheets)(C) Mar 54,(PCS)Mar 69,Apr 50

TV-Derived Frequency Standard(Stroud)(C) Apr 55,(LTR)Oct 16,(PCS)Apr 69
 TV on RGB monitor(Lancaster)(HH) Nov 32
 Two common record-player problems(Klein)(AUD) Jul 74

U

UV-curing resins(Lancaster)(HH) Feb 73
 Uninterruptable Power Supply(Perkins)(C) Jan 44,(PCS)Jan 67

Universal I/O
 REACTS(Roberts)(C) Jun 51

Using
 Bargraph Displays(Marston) Mar 59
 the RE-BBS May 84

V

Versatile Function
 Generator(Wannamaker)(C) May 39,(PCS)May 100,
 (LTR)Aug 12,(LTR)Sep 16

VCR
 Calibrating VCR Counters(Blechman) Jan 57
 Servicing Basics(Phelps) Sep 53
 Video-Edit Controller(Nery)(C) Dec 57,(PCS)Dec 77
 Videonic's DirectEd(ER) Apr 27

Video
 Audio/Video Switcher(Tomplin)(C) Feb 55
 Calibrating VCR Counters(Blechman) Jan 57

Gated-Sync Decoder(Pence)(C) Dec 49,(PCS)Dec 77
 Ghost busting(Darr)(SC) May 31

HDTV Update(Fenton)Jan 16
 Heath GR-9009 Portable Color TV(ER) Jan 32

IC's(Lancaster)(HH) Mar 71
 -imaging devices(Lancaster)(HH) Apr 72
 Interactive TV(Fenton) Dec 45
 Palette (LTR)Feb 14

Signals(ARE) Jun 14
 Subwoofer Simulator(Hill)(C) May 57

Surround Sound Decoder(Hill)(C) Apr 45
 Video-Edit Controller(Nery)(C) Dec 57,(PCS)Dec 77

Videonic's DirectEd(ER) Apr 27
 VCR Servicing Basics(Phelps) Sep 53
Video News(Lachenbruch)(D) Jan 12,Feb 6,Mar 12,
 Apr 8,May 6,Jun 6,Jul 6,Aug 6,
 Sep 6,Oct 6,Nov 6,Dec 6

W

Weather station
 Technology Marketing's PC Weather Pro(ER) Mar 23

Welcome to a new column(Lancaster)(HH) Jan 71
 What makes shortwave possible(Leinwoll)(SR) Jun 78

What's News(D) Jan 6,Feb 4,Mar 6, Apr 6,
 May 4,Jun 4,Jul 4,Aug 4,
 Sep 4,Oct 4,Nov 4,Dec 4

When a shield isn't a shield(Friedman)(CC) May 80

Wireless
 Speaker System(Graf & Sheets)(C) Aug 37,(PCS)Aug 66
 Stereo Link(Graf & Sheets)(C) Mar 54,(PCS) Mar 69,Apr 50

Working with
 Monostable Multivibrators(Marston) Apr 65
 OTA's(Marston) May 63,Jul 61

Z

Z80
 hardware(Grossblatt)(DB) Jun 71
 reset(Grossblatt)(DB) Sep 82
 upgrade(ARE) Nov 12

COMPUTER DIGEST Vol. 5 January 1988.— December 1988

Abbreviations: (C)Construction; (D)Department; (EW)Editor's Workbench; (HWR)Hardware Review; (LTR)Letter; (SWR)Software Review

A

Accelerator card
 Microsoft's Mach 20(EW) Jul 84
 Baby AT Motherboard(EW) Mar 89
 Address decoding, PT68-K(Stark)(C) Jan 95
 Assembly-language programming,
 PT-68K(Stark)(C) Dec 86
 AST's Premium 386(HWR) Oct 86
 Autodesk
 AutoCAD(EW) Apr 87
 AutoSketch(EW) Apr 87
 AutoSwitch Monochrome EGA(EW) Sep 90

B

Backup Tape Subsystem
 Irwin Model 310(EW) Apr 87
 BASIC 6.0(EW) Sep 90
 Biofeedback Monitor(Barbarelo)(C) Oct 95,(LTR)Dec 14
 Book Review
 Customizing AutoCAD(EW) Sep 90
 OS-2 Programmer's Guide(EW) Jul 84
 Osborne/McGraw-Hill Programming Series(EW) Jan 88
 Brain waves
 Synergy Card for Your PC
 (Warner)(C) Sep 94,Oct 90,Nov 90
 Buttonware, Inc.
 PC-File + (SWR) Oct 86

C

Central Point Software
 Copy II PC Deluxe Option Board(HWR) Nov 84
 Communications
 Line-Carrier Modems
 (Nichols)(C) Jul 87,Aug 88,(PCS)Aug 66
 Configurable motherboard
 Orchard Technology(EW) Aug 82
 CeBIT: The Greatest Computer
 Show on Earth(Endrjonas)(EW) Jul 84
 Comdex
 Report from Atlanta(EW) Aug 82
 Commodore 64,
 Digital IC Tester for(Barbarelo)(C) May 89
 Compaq's 386SX systems(HWR) Oct 86
 Construction
 Biofeedback Monitor(Barbarelo) Oct 95,(LTR)Dec 14
 Digital IC Tester(Barbarelo) May 89
 Line-Carrier Modems(Nichols) Jul 87,Aug 88,
 (PCS)Aug 66
 PT-68K(Stark) Jan 95,Feb 91,Apr 98,May 95,Apr 98,
 May 95,Jun 93,Jul 93,
 Aug 91,Sep 97,Dec 86
 Address decoding
 Assembly-language programming
 DRAM circuits Jun 93,Jul 93,Aug 91
 Controller Sep 97
 Keyboard Feb 91
 Memory Aug 91
 Parallel port Sep 97
 RAM Jan 95
 ROM Jan 95
 Troubleshooting May 95
 Video display Feb 91
 RS-232 Monitor Control System(Frickey) Aug 83
 Serial Printer Multiplexer(Renton) Mar 93,(PCS)Mar 69
 Speech Synthesizer(Ward) Dec 80
 Synergy Card for Your PC(Warner) Sep 94,Oct 90,Nov 90
 Controllers
 Compaticard(EW) Nov 84
 Copy protection
 Floppy-Disk Data Storage(Grossblatt) Jan 90
 Copy II PC Deluxe Option Board(EW) Nov 84
 Customizing AutoCAD(EW) Sep 90

D

Data Encryption(Maniccalco) Apr 93
 Database manager
 PC-File + (SWR) Oct 86
 Desktop Publishing
 (Bernard) Mar 98
 (Holtzman) Feb 85
 DESQview(EW) May 86
 Digital IC Tester(Barbarelo)(C) May 89
 Disk Technician(EW) Apr 87
 DOS version 4.0(SWR) Oct 86
 Dr. Shrink(SWR) Oct 86

E

Editor's Workbench(D) Jan 88,Feb 83,Mar 89,Apr 87
 May 86,Jun 86,Jul 85,Aug 82
 Sep 90,Oct 86,Nov 84

EIA-323-D:
 New & Improved RS-232(Ball) Nov 87

F

Floppy-Disk
 Controller, PT68-K(Stark)(C) Sep 97
 Data Storage(Grossblatt) Jan 90
 formatting(Grossblatt) Jan 90

G

Golden Bow Systems' VOPT(EW) Sep 90
 Graphics
 Boards(EW) Aug 82
 Card: AutoSwitch Monochrome EGA(EW) Sep 90
 conversion: Hijaak(EW) Sep 90
 GrafPlus(EW) Apr 87
 Orchid's Designer VGA(EW) Jul 86
 VGA Plus(EW) Sep 90
 Grandview(EW) Sep 90

H

Hardware Review
 AutoSwitch Monochrome EGA(EW) Sep 90
 Baby AT Motherboard(EW) Mar 89
 Copy II PC Deluxe Option Board(EW) Nov 84
 Irwin Model 310 Backup Tape Subsystem(EW) Apr 87
 Microsoft's Mach 20(EW) Jul 84
 MicroSolution's CompatiCard(EW) Nov 84
 Mothercard 5.0(EW) Sep 90
 No-Slot Clock(EW) Feb 83
 Orchid's Designer VGA(EW) Jun 86
 VGA Plus(EW) Sep 90
 Hemi-sync generator
 Synergy Card for Your PC
 (Warner)(C) Sep 94,Oct 90,Nov 90
 Hijaak, Inset Systems(EW) Sep 90

I

Interface
 New & Improved RS-232(Ball) Nov 87
 RS-232 Monitor Control System(Frickey)(C) Aug 83
 IBM's DOS 4.0(EW) Nov 84
 Inset Systems' Hijaak(EW) Sep 90
 Intel's 80386SX-16(HWR) Oct 86
 Interchange File Exchange System(Byers)(EW) Mar 89
 I/O control system
 RS-232 Monitor Control System(Frickey)(C) Aug 83
 Irwin Model 310 Backup Tape Subsystem(EW) Apr 87

L

Line-Carrier Modems(Nichols)(C) Jul 87,Aug 88,
 (PCS)Aug 66
 Living VideoText, Grandview(EW) Sep 90

M

Microcomputing Mice(Holtzman) Jun 87
 Microsoft
 BASIC 6.0(EW) Sep 90
 Bookshelf(EW) Jan 88
 Excel(EW) Sep 90
 Mach 20(EW) Jul 84
 Windows/286 & 386(EW) Nov 84
 MicroSolution's CompatiCard(EW) Nov 84
 Modems
 Line-Carrier(Nichols)(C) Jul 87,Aug 88,(PCS)Aug 66
 Mothercard 5.0(EW) Sep 90
 Multi-tasking
 DESQview(EW) May 86
 OS-2(EW) May 86
 TaskView(EW) May 86
 ThinkTank(EW) May 86

N

Neuralytic Systems' Dr. Shrink(SWR) Oct 86
 New & Improved RS-232(Ball) Nov 87
 New chips, bus, and DOS(HWR)(SWR) Oct 86

New Riders Publishing
 Customizing AutoCAD(EW) Sep 90
 No-Slot Clock(EW) Feb 83

O

Orchid's Designer VGA(EW) Jun 86
 OS/2
 (EW) May 86
 On an XT Mothercard 5.0(EW) Sep 90
 Outliner, Grandview(EW) Sep 90
 Programmer's Guide(EW) Jul 84
 Report from Atlanta(EW) Aug 82
 Osborne/McGraw-Hill
 Programming Series(EW) Jan 88

P

PageMaker
 Desktop Publishing(Bernard) Mar 98
 Paradise Systems Inc.
 AutoSwitch Monochrome EGA(EW) Sep 90
 VGA Plus(EW) Sep 90
 Parallel port, PT68-K(Stark)(C) Sep 97
 Programming BASIC 6.0(EW) Sep 90
 PC-File + (SWR) Oct 86
 Persoft's IZE(EW) Nov 84

Q

Qualitas' 386MAX(HWR) Oct 86
 Quarterdeck's DESQview(SWR) Oct 86

R

RAM, PT68-K(Stark)(C) Jan 95
 Report from Atlanta(EW) Aug 82
 ROM, PT68-K(Stark)(C) Jan 95
 RS-232 Monitor Control System(Frickey)(C) Aug 83

S

Screen Extender(SWR) Oct 86
 Seaside Software's AskSam(EW) Nov 84
 Serial interfacing
 New & Improved RS-232 Standard(Ball) Nov 87
 Serial Printer Multiplexer(Renton)(C) Mar 93,(PCS)Mar 69
 Software Review
 Autodesk's AutoCAD and AutoSketch(EW) Apr 87
 BASIC 6.0(EW) Sep 90
 DESQview(EW) May 86
 Disk Technician(EW) Apr 87
 Dr. Shrink(SWR) Oct 86
 GrafPlus(EW) Apr 87
 Grandview(EW) Sep 90
 Hijaak(EW) Sep 90
 IBM's DOS 4.0(EW) Nov 84
 Interchange File Exchange System(EW) Mar 89
 Microsoft
 BASIC 6.0(EW) Sep 90
 Bookshelf(EW) Jan 88
 Excel(EW) Sep 90
 Mach 20(EW) Jul 84
 Windows/286(EW) Nov 84
 Windows/386(EW) Nov 84
 OS/2(EW) May 86
 PC-File + (SWR) Oct 86
 Persoft's IZE(EW) Nov 84
 Screen Extender(SWR) Oct 86
 Seaside Software's AskSam(EW) Nov 84
 TaskView(EW) May 86
 ThinkTank(EW) May 86
 Turbo Pascal 4.0(EW) Mar 89
 VOPT(EW) Sep 90
 ZBASIC(EW) Feb 83
 SOTA Technology's Mothercard 5.0(EW) Sep 90
 Speech Synthesizer(Ward)(C) Dec 80
 Stairway Software's Screen Extender(SWR) Oct 86
 Spreadsheets
 Excel(EW) Sep 90
 Synergy Card for Your PC
 (Warner)(C) Sep 94,Oct 90,Nov 90

V

Ventura Publisher
 Desktop Publishing(Bernard) Mar 98
 Video display, PT68-K(Stark)(C) Feb 91
 VGA Plus(EW) Sep 90

MARKET CENTER

FOR SALE

TUBES, name brands, new, 80% off list. **KIRBY**, 298 West Carmel Drive, Carmel, IN 46032.

GREAT buys! Surplus prices, ICs, linears, transformers, PS, stepping motors, vacuum pump, phototransistor, meters, Isase, **FERTIK'S**, 5400 Ella, Phila., PA 19120.

CLASSIFIED AD ORDER FORM

To run your own classified ad, put one word on each of the lines below and send this form along with your check to:

Radio-Electronics Classified Ads, 500-B Bi-County Boulevard, Farmingdale, NY 11735

PLEASE INDICATE in which category of classified advertising you wish your ad to appear. For special headings, there is a surcharge of \$23.00.

() Plans/Kits () Business Opportunities () For Sale
() Education/Instruction () Wanted () Satellite Television

Special Category: \$23.00

PLEASE PRINT EACH WORD SEPARATELY, IN BLOCK LETTERS.

(No refunds or credits for typesetting errors can be made unless you clearly print or type your copy.) Rates indicated are for standard style classified ads only. See below for additional charges for special ads. **Minimum: 15 words.**

1	2	3	4	5
6	7	8	9	10
11	12	13	14	15 (\$42.75)
16 (\$45.60)	17 (\$48.45)	18 (\$51.30)	19 (\$54.15)	20 (\$57.00)
21 (\$59.85)	22 (\$62.70)	23 (\$65.55)	24 (\$68.40)	25 (\$71.25)
26 (\$74.10)	27 (\$76.95)	28 (\$79.80)	29 (\$82.65)	30 (\$85.50)
31 (\$88.35)	32 (\$91.10)	33 (\$94.05)	34 (\$96.90)	35 (\$99.75)

We accept MasterCard and Visa for payment of orders. If you wish to use your credit card to pay for your ad fill in the following additional information (Sorry, no telephone orders can be accepted.):

Card Number

Expiration Date

Please Print Name

Signature

IF YOU USE A BOX NUMBER YOU MUST INCLUDE YOUR PERMANENT ADDRESS AND PHONE NUMBER FOR OUR FILES. ADS SUBMITTED WITHOUT THIS INFORMATION WILL NOT BE ACCEPTED.

CLASSIFIED COMMERCIAL RATE: (for firms or individuals offering commercial products or services) \$2.85 per word prepaid (no charge for zip code)...**MINIMUM 15 WORDS.** 5% discount for same ad in 6 issues; 10% discount for same ad in 12 issues within one year; if prepaid. **NON-COMMERCIAL RATE:** (for individuals who want to buy or sell a personal item) \$2.30 per word, prepaid....no minimum. **ONLY FIRST WORD AND NAME** set in bold caps at no extra charge. Additional bold face (not available as all caps) **50c per word additional.** Entire ad in boldface, \$3.40 per word. **TINT SCREEN BEHIND ENTIRE AD:** \$3.55 per word. **TINT SCREEN BEHIND ENTIRE AD PLUS ALL BOLD FACE AD:** \$4.15 per word. **EXPANDED TYPE AD:** \$4.30 per word prepaid. Entire ad in boldface, \$5.15 per word. **TINT SCREEN BEHIND ENTIRE EXPANDED TYPE AD:** \$5.40 per word. **TINT SCREEN BEHIND ENTIRE EXPANDED TYPE AD PLUS ALL BOLD FACE AD:** \$6.25 per word. **DISPLAY ADS:** 1" x 2 1/4"—\$385.00; 2" x 2 1/4"—\$770.00; 3" x 2 1/4"—\$1155.00. **General Information:** Frequency rates and prepayment discounts are available. **ALL COPY SUBJECT TO PUBLISHERS APPROVAL. ADVERTISEMENTS USING P.O. BOX ADDRESS WILL NOT BE ACCEPTED UNTIL ADVERTISER SUPPLIES PUBLISHER WITH PERMANENT ADDRESS AND PHONE NUMBER.** Copy to be in our hands on the 12th of the third month preceding the date of the issue. (i.e., Aug. issue copy must be received by May 12th). When normal closing date falls on Saturday, Sunday or Holiday, issue closes on preceding working day. Send for the classified brochure. Circle Number 49 on the Free Information Card.

TWO-WAY-RADIO, PC COMPUTERS, UNIDEN SERVICE. General Radiotelephone licensed technician. Catalog-**RAYS**, 2025 Moline, Ft. Worth, TX 76117 (817) 831-7717.

AIDS? Yes we have! Cable aids to help you. Zenith, Jerrold, Scientific Atlanta, Oak, Hamlins, much more. No Michigan sales! **HOTRONICS**, (313) 675-5834.

RESTRICTED technical information: Electronic surveillance, schematics, locksmithing, covert sciences, hacking, etc. **Huge selection. Free brochures.** **MENTOR-Z**, Drawer 1549, Asbury Park, NJ 07712.

TUBES 59¢. Year guarantee. Free catalog. Tube checker \$8.95. **CORNELL**, 4215 University, San Diego, CA 92105.

FAIR prices SB-3, Z-TAC, SA3, TRI-BI, MLD-1200-3. Pioneer, any notch filters. **Small dealer only.** No Michigan sales (313) 979-8356.

DESCRAMBLERS. All brands. Special combo Jerrold 400 and SB3 \$165. Complete cable descrambler kit \$39. Complete satellite descrambler kit \$45.00. Free catalog. **MJM INDUSTRY**, Box 531, Bronx, NY 10461-0531.

TRS-80 color computer software. Low prices! Huge selection! Free catalog. **T&D**, P.O. Box 1256, Holland, MI 49422.

CB RADIO OWNERS!

We specialize in a wide variety of technical information, parts and services for CB radios. 10-Meter and FM conversion kits, repair books, plans, high-performance accessories. Over 12 years of satisfied customers! Catalog \$2.

CBC INTERNATIONAL
P.O. BOX 31500RE, PHOENIX, AZ 85046

IS it true...Jeps for \$44 through the government? Call for facts! 1-(312) 742-1142, ext. 4673.

TUBES. "Oldest," "latest." Parts and schematics. SASE for list. **STEINMETZ**, 7519 Maplewood Ave., R.E. Hammond, IN 46324.

PC products—A/D, D/A, relay, digital I/O cards starting at \$79. Free catalog—parts, kits, computers. **JB COMPU-TRONIX**, 3816 N. Wadsworth Blvd., Wheat Ridge, CO 80033. Call (303) 425-9586

SOLAR electric systems. Discount prices. **SUN POWER-TEXAS**, Dept. 01C, P.O.B. 2788A Freeport, TX 77541. 1-(409) 233-8350.

BANDSTOP Filters—Clear up channels affected by interference. Channels 2, 3, 4, 14, 15, 16, 17, 18, 19, 20, 21 and 22 available. \$20 each—10 for \$130. **dB ELECTRONICS**, P.O. Box 8644, Pembroke Pines, FL 33084.



Quality Microwave TV Antennas

Multi-Channel 1.9 to 2.7 GHz, 40dB Gain
30-Channel System complete \$149.95
12-Channel System complete \$104.95
2-Channel System complete \$79.95

Philips-Tech Electronics
P.O. Box 8533 • Scottsdale, AZ 85262
(602) 947-7700 (\$3.00 Credit all phone orders!)

LIFETIME WARRANTY MasterCard • Visa • C.O.D.'s Quantity Pricing

CATV CONVERTERS & DESCRAMBLERS. Quality Products. Professional Service. Call 1 (800) 541-5487 Visa/M/C Accepted. **MOUNTAINTECH, INC.** Box 5024, Mt. Crested Butte, CO 81225.

CABLE TV CONVERTERS/DESCRAMBLERS Free Catalog **VIDEO MART** 3938 E. Grant #241-C, Tucson, AZ 85712. (602) 721-6557.

RENTAL MOVIE STABILIZER Connect between VCRs or to monitor. Satisfaction Guaranteed. \$59.95, \$4 handling. 1 (800) 338-8751.

3 FOR 1 SPECIAL

ON SUB-MINIATURE VOICE FM TRANSMITTERS. KITS CONTAIN PC BOARDS



***FMX-1 LONG RANGE (3 MI) ULTRA SENSITIVE FM VOICE XMTR** with fine tune, range control plus.....\$24.50



***TELX-1 TELEPHONE FM XMTR (3 MI)** automatically operates when phone is used. Crystal clear clarity with fine tune and range control. Non detectable.....\$24.50




***ATR-1 AUTOMATIC TELEPHONE RECORDING DEVICE** tapes telephone conversation all automatically.....\$19.50

ALL THREE OF ABOVE FOR.....\$49.50

CALL OR SEND VISA, MASTER CHARGE, MONEY ORDER, ETC. TO **AMAZING CONCEPTS**, BOX 716, AMHERST, NH 03031. (603) 673-4730.

CONSOLIDATED ELECTRONICS

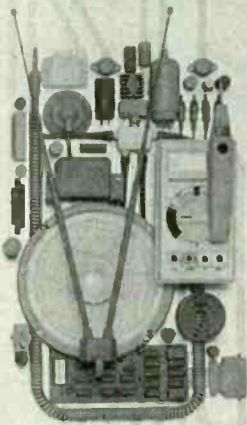

CONSUMER & INDUSTRIAL ELECTRONICS CATALOG • 17TH EDITION

THE ULTIMATE ELECTRONICS CATALOG.

Order your 260 page catalogue packed with over 10,000 money saving electronic parts and equipment. Send \$3.00 check or money order, or call **1-800-543-3568** today and use your Mastercard or Visa. Consolidated Electronics, Incorporated, 705 Watervliet Ave., Dayton, Ohio 45420-2599

NAME _____
 ADDRESS _____
 CITY _____
 STATE _____ ZIP _____

CIRCLE 196 ON FREE INFORMATION CARD

MICROPROCESSOR based prototype board. Zilog Z8, RAM, EPROM, serial/parallel I/O, prototype area. Boards, kits, software from \$49.00. Free catalog with application notes. **SOFTWARE SCIENCE**, 3535 Roundbottom Road, Cincinnati, OH 45244. (513) 561-2060.

ELECTRONIC Test Equipment, parts. Lowest prices. **EF ELECTRONICS**, Box 249, Aurora, IL 60507.

FAIR Pricing 1 (313) 979-8356. Lots 5 and 10; 65 SB 55; 65 MLD 1200 55; 85 TriBi 75; 90 SA 80; 120 SSAVI 110; 130 Pioneer 120; 180 Z-Tac 170; 180 TOCOM 170; 18 Filters Any Channel-15; No. Michigan Sales.

FREE CATALOG

FAMOUS "FIRESTIK" BRAND CB ANTENNAS AND ACCESSORIES. QUALITY PRODUCTS FOR THE SERIOUS CB'er. SINCE 1962
FIRESTIK ANTENNA COMPANY
 2614 EAST ADAMS
 PHOENIX, ARIZONA 85034

TUBES, new, unused. Send self-addressed, stamped envelope for list. **FALA ELECTRONICS**, Box 1376-2, Milwaukee, WI 53201.

PHOTOFACT folders, under #1400 \$4.00. Others \$6.00. Postpaid. **LOEB**, 414 Chestnut Lane, East Meadow, NY 11554.

Free power supply, connectors (\$8.95 value) with TV Project Assortment #103 (February 1984 G. Sync article) contains **PCB TOKO** coils, transistors (BFQ85), IC's, diodes, article reprint. \$25.00. Five \$112.50. Assortment #104, contains all other parts \$10.00. Shipping \$3.00. **MC/VISA, COD** accepted. **Jim Rhodes, Inc.** P.O. Box 3421, Bristol, TN 37625.

LASERS, 1 to 9 milliwatt, from \$30, write **MWK INDUSTRIES**, 9852 W. Katella Suite 340, Anaheim, CA 92804.

Multi-Channel Microwave T.V. Receivers

1.9-2.7 GHz Parabolic Dish 40+ dB Gain
LIFETIME WARRANTY
 Complete System \$99.95 (Shipping Incl.)
 Replacement Components & Expert Repairs Available

K & S ELECTRONICS Call now for same day shipping!
 P.O. BOX 34522 (602) 230-0640
 PHOENIX, AZ 85067
VISA/MC/COD \$2 CREDIT ON PHONE ORDERS

EPROM, Emulator/Programmers. IBM PC/XT compatible. Free info sheet. **SOLICON**, 8825 El Matador Dr., Gilroy, CA 95020.

EARN thousands with your own part time electronics business. I do. Free proof, information. **INDUSTRY**, Box 531, Bronx, NY 10461-0531.

CABLE TV CONVERTERS We sell only the best. Low prices, we ship COD. \$2.00 for catalog. **ACE PRODUCTS** PO Box 582 Dept E. Saco, ME 04072 (207) 967-0726.

ENGINEERING software. IBM/compatibles. CompDes Circuit Design. Basic electricity through circuit designs. CompMath. General mathematics through statistics. CompView. Digital Analysis, waveforms and filters. \$49. (614) 491-0832. **BSOFT SOFTWARE** 444 Colton Road, Columbus, OH 43207.

REMOTE CONTROL KEYCHAIN

Complete w/mini-transmitter and +5 vdc RF receiver. Fully assembled including plans to build your own auto alarm. Quantity discounts available.

\$19.95 Check, Visa or M/C 30 days refund

VISITECT INC. (415) 872-0128
 PO BOX 5442, SO. SAN FRAN., CA 94080

CABLE TV DECODERS, Jerrold, Scientific Atlanta, Zenith, most major brands. Dealer Inquiries Welcome. Visa-M/C Accepted. **E & O VIDEO**, 6691 E. 265th Street, Elko, MN 55020. 1 (800) 638-6898.

LOW prices: ICs, transistors, capacitors, switches. **SASE SANTECH**, 11 Revere Place, Tappan, NY 10983. (914) 359-1130. FAX: (914) 365-0243.

PLANS AND KITS

BUILD this five-digit panel meter and square-wave generator including an ohms, capacitance and frequency meter. Detailed instructions \$2.50. **BAGNALL ELECTRONICS**, 179 May, Fairfield, CT 06430.

ELECTRONIC kits, devices, testers, components, plans, bugs-software. Catalog \$1.00. **EXPO-TRONICS**, 1222 Highland, Berwyn, IL 60902.

VIDEOCIPHER II Manuals. Volume 1—hardware, Volume 2—software. Either \$29.95 both \$49.95! **NEW!** Volume 3—Projects/software—\$39.95. All for \$79.95. CODs—1-(602) 782-2316. Catalog—\$3.00. **TELECODE**, Box 6426-R, Yuma, AZ 85366-6426.

The DECODER. Satellite and cable descrambling newsletter. News-schematics-modifications-reviews. \$24.00/year. Complimentary sample. **TELECODE**, Box 6426, Yuma, AZ 85366-6426.

MICRO-link FM stereo audio transmitter. One chip does it all! Transmit your CD/VCR/Walkman in stereo to any FM radio. Free schematic and info. Send a self addressed/stamped envelope to: **DJ INC.**, 217 E. 85th St., Suite 108, New York, NY 10028.

DESCRAMBLING, new secret manual. Build your own descramblers for cable and subscription TV. Instructions, schematics, for SSAVI, gated sync, sinewave. (HBO, Cinemax, Showtime, etc.) \$8.95, \$2 postage. **CABLETRONICS**, Box 30502R, Bethesda, MD 20814.

BIG PROFITS!

Learn VCR cleaning-repair! Prior experience unnecessary. Need only small hand tools, average mechanical ability. **Big demand** performing VCR cleanings and repairs! **Viejo's 400 page TRAINING MANUAL** (over 500 photos and illustrations!) and companion **VIDEO TRAINING TAPE** contains hundreds of REAL-WORLD examples of VCR malfunctions and their repair solutions. Secrets revealed! Also: business tips for your new service business!

Free INFO: call (toll free) 1-800-537-0589 or write to: **Viejo Publications, Dept. R-E** 217 E. 86th St., STE 272, NY, NY, 10028

TOP quality imported, domestic kits, surplus, discount electronics, computers, components. **Free catalog**. **TEKTRASONIX**, 1120 Avenue of the Americas, 11th Suite 4038, New York, NY 10036.

"CB Trick of the Trade book" learn CB repair tricks and tuning tricks. Send \$19.95 to **MEDICINE MAN**, CB, P.O. Box 37, Clarksville, AR 72830.

FREE kit catalog. Home, auto, industrial kits. **BALCO, INC.**, 148S. Clayton, Lawrenceville, GA 30245. (404) 979-5900.

FM transmitter 88 to 108 MHz kit \$12.95 **Sierra Electronics**. Box 709, Eilers, FL 34680-0709.

POWER Supply Kit: Variable, D/C voltage, fullwave bridge rectification. Complete: Transformer, PC board, meter, cabinet and components. **Satisfaction Guaranteed**. \$29.95 + \$3.00 S/H. **KDC ELECTRONICS**, Box 577, Bloomington, IN, 47401.



DETAILED PLANS: \$4.95

TV-SCOPE

PENN RESEARCH, Box 3543, Williamsport, PA 17701

FINALLY!

An interesting and worthwhile project. This **EASY-TO-BUILD** circuit lets you use any regular TV set as a simple **OSCILLOSCOPE**. Build for less than \$10. **NO MODIFICATIONS TO TV!** Single or dual trace. Send for **FREE CATALOG** of other plans and kits.

CAR Alarms: Schematics, kits. Remote controlled. Info \$1. **KCO 8 Manor House Lane, Uxbridge, MA 01569.**



**SINGERS!
REMOVE VOCALS
FROM RECORDS AND CDs!**

SING WITH THE WORLD'S BEST BANDS!

An Unlimited supply of Backgrounds from standard stereo records! Record with your voice or perform live with the backgrounds. Used In Professional Performance yet connects easily to a home component stereo. This unique product is manufactured and sold Exclusively by LT Sound - Not sold through dealers. Call or write for a Free Brochure and Demo Record.

LT Sound, Dept. RL-3, 7980 LT Parkway
Lithonia, GA 30058 (404) 482-4724
Manufactured and Sold Exclusively by **LT Sound**
24 HOUR PHONE DEMO LINE: 1-404-482-2485

ELECTRONIC Kits! Transmitters! Recorders! Phone Devices! Surveillance items! More! Catalog \$1.00: **XANDI ELECTRONICS**, Box 25647, 60H, Tempe, AZ 85285-5647.

COMPUTER kits, \$49.95 complete. Build your own Sinclair ZX81 with built in BASIC. School discounts available. Add \$3.00 for shipping. Visa/MC. **Zebra Systems, Inc.** 78-06 Jamaica Ave., Woodhaven, NY 11421. (718) 296-2385.

HOW to rewind power transformers to your specs. Instructions \$7.95. **BROSS ELECTRONICS** 350 Tremont Drive, Suite D-51, Dept. R12, Murfreesboro, TN 37130.

CATALOG: Hobby/broadcasting/HAM/CB: Cable TV, transmitters, amplifiers, bugging devices, computers, more! **PANAXIS**, Box 130-F12 Paradise, CA 95967.

PRINTED circuit boards etched & drilled. Free delivery. **K & F ELECTRONICS, INC.**, 33041 Groesbeck, Fraser, MI 48026. (313) 294-8720.

SCRAMBLE FACTS
718-343-0130

PHONE TODAY for 3 minutes of satellite TV industry news, technical tips, and new product information.

SATELLITE TV

CABLE TV Secrets—the outlaw publication the cable companies tried to ban. HBO, Movie Channel, Showtime, descramblers, converters, etc. Supplier's list included \$8.95. **CABLE FACTS**, Box 711-R, Pataskala, OH 43062.

SATELLITE TV receiver kits! Instruction manual, boards, semiconductor parts! 59' LNA's! LNB's! Ku-Band LNB's! Catalog \$1.00 **XANDI ELECTRONICS**, Box 25647, Dept. 21MM, Tempe, AZ 85285-5647.

FREE catalog. Systems, **Upgrades**, Houston, Uden, Chaparral, etc. Save, \$\$\$\$ **SKYVISION**, 2009 Collegeway, Fergus Falls, MN 56537. (218) 739-5231.

SATELLITE descrambling—cable descrambling. Send stamp for catalog. **COMMUNICATIONS ENGINEERING**, 76 Boulevard, Hudson Falls, NY 12839.

FREE catalog 36 pages. Major brands. Nobody undersells **WEST** since 1977. Immediate shipping. Call for prices. 1741 Cedardale Road, Mt. Vernon, WA 98273. (800) 222-9064.

CABLE-TV

**WE'LL MATCH OR BEAT ANYONE'S
ADVERTISED RETAIL OR WHOLESALE PRICES!**

BONANZA!

ITEM	1 UNIT	10 OR MORE
HAMLIN MCC 3000 36 CORDED REMOTE CONVERTER (Ch 3 only)	29 00	18 00
PANASONIC WIRELESS CONVERTER (our best buy)	98 00	79 00
MOVIE TIME VR7200A (manual fine tune)	88 00	69 00
JERROLD 400 COMBO	169 00	119 00
JERROLD 400 HAND REMOTE CONTROL	29 00	18 00
JERROLD 450 COMBO	199 00	139 00
JERROLD 450 HAND REMOTE CONTROL	29 00	18 00
JERROLD 5B ADD-ON	99 00	63 00
JERROLD 5B ADD-ON WITH TRIMODE	109 00	75 00
M-35 B COMBO UNIT (Ch 3 output only)	99 00	70 00
M-35 B COMBO UNIT WITH VARISYNC	109 00	75 00
MINICODE (N-12)	99 00	62 00
MINICODE (N-12) WITH VARISYNC	109 00	65 00
MINICODE VARISYNC WITH AUTO ON-OFF	145 00	105 00
ECONOCODE (minicode substitute)	69 00	42 00
ECONOCODE WITH VARISYNC	79 00	46 00
MLD-1200-3 (Ch 3 output)	99 00	62 00
MLD-1200-2 (Ch 2 output)	99 00	62 00
ZENITH SVAVI CABLE READY	175 00	125 00
INTERFERENCE FILTERS (Ch 3 only)	24 00	14 00
EAGLE PD-3 DESCRAMBLER (Ch 3 output only)	119 00	65 00
SCIENTIFIC ATLANTA ADD-ON REPLACEMENT DESCRAMBLER	119 00	85 00

*CALL FOR AVAILABILITY

Quantity	Item	Output Channel	Price Each	TOTAL PRICE
			SUBTOTAL	
			Shipping Add \$3.00 per unit	
			COD & Credit Cards — Add 5%	
			TOTAL	

California Penal Code #593-D forbids us from shipping any cable descrambling unit to anyone residing in the state of California. Prices subject to change without notice.

PLEASE PRINT

Name _____
 Address _____ City _____
 State _____ Zip _____ Phone Number () _____
 Cashier's Check Money Order COD Visa Mastercard
 Acct # _____ Exp. Date _____
 Signature _____

FOR OUR RECORDS:

DECLARATION OF AUTHORIZED USE — I, the undersigned, do hereby declare under penalty of perjury that all products purchased, now and in the future, will only be used on cable TV systems with proper authorization from local officials or cable company officials in accordance with all applicable federal and state laws. **FEDERAL AND VARIOUS STATE LAWS PROVIDE FOR SUBSTANTIAL CRIMINAL AND CIVIL PENALTIES FOR UNAUTHORIZED USE.**

Dated: _____ Signed: _____

Pacific Cable Company, Inc.
 7325 1/2 RESEDA BLVD., DEPT. #R-12 • RESEDA, CA 91335
 (818) 716-5914 • No Collect Calls • (818) 716-5140

IMPORTANT: WHEN CALLING FOR INFORMATION
 Please have the make and model # of the equipment used in your area. Thank You

© Copyright 1987 PACIFIC CABLE CO., INC.

Cable TV Converters

Why Pay A High Monthly Fee?

Jerrold Products include "New Jerrold Tri-Mode," SB-3. Hamlin, Oak VN-12, M-35-B, Zenith, Magnavox, Scientific Atlanta, and more. (Quantity discounts) 60 day warranty. For fast service C.O.D. orders accepted. Send SASE (60 cents postage) or call for info 1-800-648-3030. **MIDWEST ELECTRONICS, INC.**, 5143-R W. Diversey, Chicago, IL 60639. MC/Visa orders accepted. No Illinois orders accepted. Mon.-Fri. 8 A.M.-5 P.M. CST

DESCRAMBLERS for movies, networks, \$175. video only. \$450 complete. Visa, MC accepted. Catalog \$4. **SKYWATCH**, 238 Davenport Road, Toronto, Ontario, Canada, M5R-1J6.

VIDEOCYPHER II descrambling manual, schematics, video and audio DES, cloning, showkateering, EPROM codes. (HBO, Cinemax, Skysat, adult channels.) \$13.95, \$2 postage. **CABLETRONICS**, Box 30502R, Bethesda, MD 20814.

CAR-STEREO EQUIPMENT

POWER amplifier stereo bridgeable 800W linear class A, 2X400W or use 4X200W \$295.00! Subwoofer speaker systems, Hemholtz enclosure kits, electronic crossovers etc. wholesale prices, free catalog. Information **BOOM-BOOM ELECTRONICS** 2905 Las Vegas Blvd. North #53RE, North Las Vegas, NV 89030 (702) 399-3139.

BUSINESS OPPORTUNITIES

EASY, lucrative. One man CRT rebuilding machinery. Free info: (815) 459-0666 CRT, 1909 Louise, Crystalake, IL 60014.

YOUR own radio station! AM, FM, TV, cable. Licensed/unlicensed. **BROADCASTING**, Box 130-F12, Paradise, CA 95967.

MECHANICALLY inclined individuals desiring ownership of small electronics manufacturing business—without investment. Write: **BUSINESS**, 92.R, Brighton 11th, Brooklyn, NY 11235.

BIG PROFITS ELECTRONIC ASSEMBLY BUSINESS

Start home, spare time. Investment knowledge or experience unnecessary. **BIG DEMAND** assembling electronic devices. Sales handled by professionals. Unusual business opportunity
FREE: Complete illustrated literature
 BARTA, RE-O Box 248
 Walnut Creek, Calif 94597

BURGLAR ALARMS-BOOMING BUSINESS. GET STARTED NOW. INFORMATION \$2.00. DYNAMIC SECURITY POB 1456-M Grand Rapids, MI 49501.

EASY Work! Excellent Pay! Assemble products at home. Call for information. (504) 641-8003 Ext. A-5192.

CABLE TV CONVERTERS

CABLE TV converters. Scientific Atlanta, Jerrold, Oak, Zenith, Hamlin. Many others. "New" Video Hopper "The Copy Killer." Visa, M/C & Amex. 1 (800) 826-7623. **B&B INC.**, 10517 Upton Circle, Bloomington, MN 55431.

EDUCATION & INSTRUCTION

F.C.C. Commercial General Radiotelephone license. Electronics home study. Fast, inexpensive! "Free" details. **COMMAND**, D-176, Box 2223, San Francisco, CA 94126.

MASTER new skills fast through our short specialized home study courses. Condensed and highly effective! Passport to success! 50 choices! Diploma! **CIEE-12**, Box 20345, Jackson, MS 39209.

MICROPROFESSOR 8 bit trainer. Z-80 C.P.U. 158 instruction set, 8K monitor ROM, enter programs in assembly, machine, basic, or forth. \$199.95 and \$7.50 s&h. **ETRONIX** 5326 9th Ave.N.E. Seattle, WA 98105. 1 (800) 426-1044 and (206) 527-5223.

MAGIC! Four illustrated lessons plus inside information shows you how. We provide almost 50 tricks including equipment for four professional effects. You get a binder to keep the materials in, and a one-year membership in the International Performing Magicians with a plastic membership card that has your name gold-embossed. You get a one-year subscription to our quarterly newsletter, "IT'S MAGIC!" Order now! \$29.95 for each course plus \$3.50 postage and handling. (New York residents add applicable state and local sales tax.) **THE MAGIC COURSE** 500-B BiCounty Boulevard, Farmingdale, NY 11735.

DESCRAMBLER MODULE

LATEST technology alternative to Jerrold SB-3 or Radio-Electronics Feb. 1984 project. Featuring electronic tuning, AGC, auto-on/off, AD/DC power, mini-size, A&T, and more. For literature—**SOUTH-TECH DISTRIBUTING**, (813) 527-2190.

AUTO ALARMS

REMOTE auto alarm accessory. Locks/unlocks power doors from remote. Compact kit \$21. (516) 691-4543. Leave address for info.

CALL FOR FREE CATALOG

TEXT TO SPEECH BOARD!

PC/XT COMPATIBLE. MAKE YOUR COMPUTER TALK!
 A VERY POWERFUL AND AMAZING SPEECH CARD. USES THE NEW GENERAL INSTRUMENTS SPO256-AL2 SPEECH CHIP AND THE CTS256A-AL2 TEXT TO SPEECH CONVERTER.

THIS BOARD USES ONE SLOT ON THE MOTHERBOARD AND REQUIRES A COM SERIAL PORT. BOARD MAY ALSO BE USED IN A STAND ALONE ENVIRONMENT WITH ALMOST ANY COMPUTER THAT HAS A RS232 SERIAL PORT. FEATURES ON BOARD AUDIO AMP OR MAY BE USED WITH EXTERNAL AMPS. DEMONSTRATION SOFTWARE AND A LIBRARY BUILDING PROGRAM ARE INCLUDED ON A 5 1/4 INCH PC/XT DISKETTE. FULL DOCUMENTATION AND SCHEMATICS ARE ALSO INCLUDED.




NEW! PRICE CUT! \$69.95 ASSEMBLED & TESTED

NEW! IC TESTER! \$149.00

SIMILAR TO BELOW EPROM PROGRAMMER. PLUGS IN TO YOUR PC OR XT. TESTS ALMOST ALL 14, 16, AND 20 PIN 74XX SERIES. INCLUDES STANDARD POWER, "S" AND "LS" DEVICES. ALSO TESTS CD4000 SERIES CMOS. SOFTWARE INCLUDED CAN EVEN DETERMINE PART NUMBERS OF MOST UNMARKED AND HOUSE NUMBERED DEVICES WITH SIMPLE MOD. THIS UNIT CAN ALSO TEST 6.4K AND 256K DRAMS! WITH MANUAL AND SOFTWARE: \$149. PERFECT FOR SCHOOLS.

PC/XT EPROM PROGRAMMER \$169

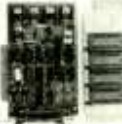

ASK ABOUT OUR NEW PAL PROGRAMMER!

* LATEST DESIGN * PROGRAMS UP TO 4 DEVICES AT ONE TIME * FEATURES EASY TO USE MENU DRIVEN SOFTWARE THAT RUNS UNDER PC OR MS-DOS. * USES AN INTELLIGENT PROGRAMMING ALGORITHM FOR SUPER FAST (8X) EPROM BURNING. * THIS PLUG-IN BOARD ATTACHES TO AN EXTERNAL MINI CHASSIS CONTAINING 4 TEXTPOOL Z.I.F. SOCKETS. * NO PERSONALITY MODULES REQUIRED * AUTOMATIC VPP SELECTION: 12.5V, 21V, OR 25V. * EPROM DATA CAN ALSO BE LOADED FROM OR SAVED TO A DISKETTE. * PROGRAMMING SOFTWARE SUPPORTS: 2716, 2732, 2732A, 2764, 2764A, 27128A, 27128A, 27256, 27256A, 27512, AND 27512A. * ASSEMBLED AND TESTED, BURNED, IN WITH MANUAL. \$169 WITH SOFTWARE.

JUST RECEIVED. SAME AS ABOVE PROGRAMMER, BUT PROGRAMS 8 UNITS AT ONE TIME - \$299.

Digital Research Computers

P.O. BOX 381450 • DUNCANVILLE, TX 75138 • (214) 225-2309

TERMS: Add \$3.00 postage. We pay balance. Orders under \$15 add 75¢ handling. No C.O.D. We accept Visa and MasterCard. Texas Res. add 6-1/4% Tax. Foreign orders (except Canada) add 20% P & H. Orders over \$50 add 85¢ for insurance.

JUST SIMPLY SAID . . .

"When you're looking for a company that provides service and up-to-date technical advances, call us. That's what we're here for."
800-85-AMCOM

CABLE EQUIPMENT		BRAND NEW	T C - V I P																																																													
Super SSAVI ADD-ON ELIMINATES LINE 20 FALSE FLASHING AUTOMATICALLY HANDLES NORMAL & INVERTED VIDEO. NO SWITCHES. FULLY AUTOMATIC \$219.00			CHANNEL #3 IN/CHANNEL #3 OUT. BUILD IT YOURSELF AND SAVE. Assembled and tested \$169.00 Kit includes all parts 109.00																																																													
Standard SSAVI ADD-ON CH #3 IN CH #3 OUT 1 YEAR WARRANTY \$159.00		TEN-TEC DW-12 Metal Enclosure W = 10" L = 10.25" H = 4.50" WITH HARDWARE \$20		"BLASTER" \$25.00 UHF PREAMP KIT 25 db gain with only .5 mV loss - noise made minimal. USES PHANTOM POWER STRIPLINE CIRCUITRY																																																												
INTERFERENCE FILTERS \$15.00 CHANNEL #2, 3, 5, 6, 8, 9, 14, 17, 22 ONLY BI-STATE TRIMODE ADD-ON \$119.00		WALL PWR SUPPLIES 24 VAC 525 MA N/C .50 12 VAC 600 MA W/C 2.00 12 VAC 265 MA W/C 1.75		UHF SSAVI UNIT w/power supply \$50.00 ORIGINAL Z-TAC AND SSAVI POWER SUPPLY \$15.00																																																												
TV TUNER VARACTORS VHF/MID/UHF MITSUMI \$25.00		CALL US!!! WE BUY EXCESS INVENTORY																																																														
<table border="1"> <thead> <tr> <th colspan="2">LINEAR</th> <th colspan="2">CMOS</th> <th>OTHER</th> <th>RARE IC CHIP</th> </tr> </thead> <tbody> <tr> <td>LMS12 .30</td> <td>MC1310 1.00</td> <td>CD4002 .20</td> <td>CD4097 .36</td> <td>CD4000</td> <td>CAMERA SYNC CHIP</td> </tr> <tr> <td>LMS19 .30</td> <td>MC1390 1.75</td> <td>CD4011 18</td> <td>CD4040 .86</td> <td>CD4000</td> <td>SUPPLIES ALL SYNC</td> </tr> <tr> <td>LMS24 .25</td> <td>MC1360 1.25</td> <td>CD4012 25</td> <td>CD4047 .86</td> <td>CD4000</td> <td>AND COLOR INFO</td> </tr> <tr> <td>LF363 .40</td> <td>CA1360 4.00</td> <td>CD4013 25</td> <td>CD4083 .36</td> <td>7480</td> <td></td> </tr> <tr> <td>LMS80 1.75</td> <td>MC1460 2.25</td> <td>CD4016 25</td> <td>CD4088 .36</td> <td>74LS04</td> <td></td> </tr> <tr> <td>LMS82 .60</td> <td>LH1460 7.5</td> <td>CD4016 25</td> <td>CD4090 .36</td> <td>74LS74</td> <td></td> </tr> <tr> <td>LMS88 .25</td> <td>LH1500 1.00</td> <td>CD4017 35</td> <td>CD4077 .29</td> <td>74LS123</td> <td></td> </tr> <tr> <td>LMS92 .75</td> <td>TL082 7.5</td> <td>CD4018 45</td> <td>CD4091 .29</td> <td>74LS24</td> <td></td> </tr> <tr> <td>HMS82 .75</td> <td>TL084 1.25</td> <td>CD4024 40</td> <td>CD4092 .20</td> <td>74LS205</td> <td></td> </tr> </tbody> </table>		LINEAR		CMOS		OTHER	RARE IC CHIP	LMS12 .30	MC1310 1.00	CD4002 .20	CD4097 .36	CD4000	CAMERA SYNC CHIP	LMS19 .30	MC1390 1.75	CD4011 18	CD4040 .86	CD4000	SUPPLIES ALL SYNC	LMS24 .25	MC1360 1.25	CD4012 25	CD4047 .86	CD4000	AND COLOR INFO	LF363 .40	CA1360 4.00	CD4013 25	CD4083 .36	7480		LMS80 1.75	MC1460 2.25	CD4016 25	CD4088 .36	74LS04		LMS82 .60	LH1460 7.5	CD4016 25	CD4090 .36	74LS74		LMS88 .25	LH1500 1.00	CD4017 35	CD4077 .29	74LS123		LMS92 .75	TL082 7.5	CD4018 45	CD4091 .29	74LS24		HMS82 .75	TL084 1.25	CD4024 40	CD4092 .20	74LS205				
LINEAR		CMOS		OTHER	RARE IC CHIP																																																											
LMS12 .30	MC1310 1.00	CD4002 .20	CD4097 .36	CD4000	CAMERA SYNC CHIP																																																											
LMS19 .30	MC1390 1.75	CD4011 18	CD4040 .86	CD4000	SUPPLIES ALL SYNC																																																											
LMS24 .25	MC1360 1.25	CD4012 25	CD4047 .86	CD4000	AND COLOR INFO																																																											
LF363 .40	CA1360 4.00	CD4013 25	CD4083 .36	7480																																																												
LMS80 1.75	MC1460 2.25	CD4016 25	CD4088 .36	74LS04																																																												
LMS82 .60	LH1460 7.5	CD4016 25	CD4090 .36	74LS74																																																												
LMS88 .25	LH1500 1.00	CD4017 35	CD4077 .29	74LS123																																																												
LMS92 .75	TL082 7.5	CD4018 45	CD4091 .29	74LS24																																																												
HMS82 .75	TL084 1.25	CD4024 40	CD4092 .20	74LS205																																																												
DEALERS WANTED!! GREAT QUANTITY PRICES		AMCOM P. O. Box 68391 Virginia Beach, VA 23455 804-456-5505 (TECHNICAL) 800-852-6266 (ORDERS ONLY)		UPS DAILY COD ACCEPTED MINIMUM ORDER \$15.00 PRICES SUBJECT TO CHANGE WITHOUT NOTICE NO INSTANT SALES																																																												

RADIO-ELECTRONICS

CABLE T.V. "BOXES"

Converters—Descramblers
Remote Controls—Accessories

- ★ **Guaranteed Best Prices** ★
- ★ **1 Year Warranty—C.O.D.'s** ★
- ★ **Immediate Shipping** ★
- ★ **FREE CATALOG** ★

Call or Write
TRANS-WORLD CABLE CO.
12062 Southwest 117th Court, Suite 126
Miami, Florida 33186
800-442-9333

NEURAL NETWORKS

AMAZING circuits or computer program simulate thought & sensory processing. Plans \$25. Program \$50. Free Brochure. Author MSEE. LP WEBER, Box 621, Dept. RE-1204, Allenwood, NJ 08720.

HIGH TECH ELECTRONICS

SCRAMBLER PHONES! Phone Bug Detectors! Electronic Countermeasures Equipment! Executive and personal protection products! And much more!!! Catalog \$3.00 (Refundable with first order) **DIVERSIFIED WHOLESALE PRODUCTS**, P.O. Box 1275-RE, Redondo Beach, CA 90278.

DIGITAL CAR DASHBOARDS

BUILD yourself a complete electronic dashboard. Free details, \$1 P&H. **MODERN LABS**, 2900 Ruisseau, St. Elizabeth, QC. JOK 2J0, Canada

WANTED

INVENTORS! AIM WANTS—ideas, inventions, technology, improvements on existing products. We present ideas to manufacturers. Confidentiality guaranteed. Call toll-free in U.S. and Canada 1 (800) 225-5900.

CABLE-TV AT IT'S BEST

SCIENTIFIC Atlanta models 8500—8550 remote included...\$240.00. SB-3's...\$74.00. TRI-BI's...\$95.00. SA-3's...\$99.00. Zenith (Z-Tac) descramblers...\$169.00. N-12 (Vari-sync)...\$89.00. M-35 B (Vari-sync)...\$99.00. Hamlin MLD-1200's...\$89.00. 80-Channel converters...\$95.00. Dealer discount on (5) units. Call—N.A.S. INTERNATIONAL, (213) 631-3552.

SCRAMBLING NEWS

Twenty plus pages of information per month, covering cable, satellite and wireless cable. News, product reviews, feedbacks, features, patents, circuits, turn-ons etc. Current articles Z-TAC, SNAVI SALVAGE? Cable TV, VC and the Self Sufficient. \$24.95/yr. Scrambling News 1987 \$22.95. Sample \$3. Pay TV and Satellite Descrambling Vol 1 or Vol 2 \$14.85 each. Cable TV, Security \$12.95. MDS/MMDS Hacking \$9.95. Satellite Systems Under \$600. \$12.95. Experiments with Videocipher \$14.95. Any 3/\$28 or 6/\$42. ST-1085 descrambler schematic \$15.95. Z-TRAP II eliminates flashing \$15.95. Z-BAG Bogus Address Generator \$19.95. Both \$29.95.

Shojiki Electronics Corp., 1552A Hertel Ave.
Buffalo, NY 14216
CODS 716-874-2088

EQUIPMENT REPORTS

continued from page 24

does represent a major step forward in CD-ROM technology. For the first time you can have a CD in your PC that behaves like and offers the same conveniences of a hard disk. The software drivers are considerably easier to use than in competitive units like the Sony CDU-100, and software installation is a snap. That along with audio-CD capability and Amdek's commitment to CD-software distribution make the Laserdek 1000 one attractive deal. **R-E**

NUTS & VOLTS
MAGAZINE

P.O. Box 1111-E
Piscataway, NJ 08870
714-632-7781

GIVE YOURSELF A BREAK—A PRICE BREAK!
NUTS & VOLTS Will Save You MONEY ON ELECTRONIC PARTS & EQUIPMENT!
Plus SHOW YOU WHERE TO FIND UNIQUE, UNUSUAL AND HARD-TO-FIND ITEMS.

SUBSCRIBE TODAY!

A National Publication For The Buying And Selling Of Electronic Equipment

THIS IS AN ALL BOLD-FACE AD. If you want your entire ad in boldface the cost is \$3.40 per word.

<p>V20-8 14.95 8080A CPU 1.75 2808 CPU 3.75 280A CTC 1.95 280A DAPT 5.25 280A UMA 8.50 280A PFD 1.95 280A SIMA 5.00 2808 SIO 9.95 82C43 2.75 AM02901 4.00 8902 3.25 6522 3.00 6800 1.75 6802 4.50 6803LC 8.00 6809 5.50 6810 1.75 6821 1.75 6845 4.80 6880 1.75 80314M 3.75 8035 1.75 8048 8.00 8049 2.50 8085A 2.75 NS16480 12.95 6800C-12 19.95 68881 95.00</p>	<p>CPU'S & CHIPS 8086 8.00 8088 7.50 8088 2.75 8202 8.00 8203 16.00 8212 1.45 8214 3.75 8216 1.80 8224 2.25 8226 1.60 8227 6.80 8238 3.95 8238 6.75 8243 2.40 8244 1.75 8255 1.85 8257 2.40 8259 2.40 8274 4.80 8275 9.00 8276 2.75 8278 2.75 8284 2.50 8286 4.75 280927NL 9.50 6800BL 8.50</p>	<p>RAM'S 5M4000A-12 30.00 21102-3 7.00 20114-3 6.50 2101A-4 1.50 2111A 1.75 2112-1 1.95 2112-2 1.00 2118-4 1.75 2147-3 2.50 2147-6 6.00 2147-8 1.75 MK4027-3 .85 7M54050NL 1.75 MK4096 11 1.75 1108-9 1.60 4116-2 1.75 4118-4 3.45 4118-5 1.75 4118-6 1.75 4118-7 9.80 4118-12 2.95 41256-12 41256-15</p>	<p>TRANSISTOR SPECIAL</p> <p>TIP 318 NPN S-TO-220 \$ 40 TIP 328 PNP S-TO-220 \$ 40 TIP 33 PNP S-T \$ 95 TIP 111 S-T \$ 50 TIP 122 NPN S-UBA \$ 50 TIP 145 NPN S-UG7 \$120 TIP 145 \$135 2N1307 PNP GE TO-5 \$ 40 DPS7008-DUAL \$3.95 POWER DARL. \$3.95 2N2222 NPN S-TO-92 \$ 781.00 2N2907 PNP S-TO-92 \$ 781.00 2N2955 PNP S-T \$ 70 2N3055 NPN S-TO-3 \$ 50 MJE3055T \$ 60 2N3772 NPN S-TO-3 \$175 2N4304 PNP S-TO-92 \$761.00 2N4306 PNP S-TO-92 \$781.00 2N4901 PNP S-TO-3 \$100 2N8296 NPN S-TO-3 \$ 50 2N8296 PNP S-TO-220 \$ 55 2N8296 PNP S-TO-92 \$781.00 MPS-804 CM FR NPN \$ 75 MPS-842 200V NPN \$81.00</p>	<p>SCR'S 1.5A 6A 35A 75A 100 35 40 140 200 40 50 180 400 60 70 240 90 600 80 100 360 1200</p> <p>TRIAC'S PRV 1A 10A 100 35 60 200 50 80 400 70 100 600 100 360 1200</p>	<p>LINEAR CIRCUITS</p> <p>TLO82C .95 LM393 40 MC1301 1.00 TLO84CN 1.00 LF398A 3.00 1458 .80 TLO12 1.00 LF411 1.25 1468 .50 LM79BCT .60 AD506A 2.90 LM1808 1.75 TLO62 .90 537 1.90 LM2700A 1.75 TLO84 1.00 LM556 29 AD7200 4.95 LM393 1.60 LM565 45 AD9201 .95 LM201 .75 558 1.10 CA3018 1.95 LM301 .35 AD561 3.00 CA3045 1.20 LM307 .45 564 1.75 C8287BRT 1.50 LM308 .65 565 .90 CA3088E 1.75 LM311 .45 566 1.25 CA3094 1.30 LM318 1.00 567 75 CA3130 90 LM307 .45 564 1.75 CA3140 .75 LM324 .35 NE592 .95 SG3543 1.70 LM339 .50 709C 80 SG3544 1.00 LM348 .65 711C 80 UNLDR1E 1.75 LF351 .45 733 .95 LM9000 .50 LF353 .75 739 1.50 4136 .85 LF355 .35 741CV 29 SO8000 1.75 LF356 .85 747 .90 N552A .75 LM388 .45 DAC08C 2.95 NS566A 1.50 LM380 .65 CNDN .85 SO6000 1.00 LM384 1.60 MC1310 1.00 8700C 5.95 LM385 .65 MC1390 .90 LM13080 .80 LM385 .65 MC1395 1.25 76477 2.95</p>	<p>74HC SERIES 74HC00 .35 74HC125 .50 74HC245 .80 74HC02 .35 74HC133 .50 74HC257 .55 74HC04 .35 74HC138 .50 74HC259 .80 74HC08 .35 74HC14 .50 74HC263 .55 74HC10 .35 74HC19 .50 74HC354 .35 74HC11 .40 74HC19 .50 74HC354 .35 74HC12 .35 74HC21 .50 74HC354 .35 74HC13 .35 74HC21 .50 74HC354 .35 74HC14 .35 74HC21 .50 74HC354 .35 74HC15 .35 74HC21 .50 74HC354 .35 74HC99 .35 74HC21 .50 74HC354 .35 74HC00 .35 74HC21 .50 74HC354 .35 74HC01 .35 74HC21 .50 74HC354 .35 74HC02 .35 74HC21 .50 74HC354 .35 74HC03 .35 74HC21 .50 74HC354 .35 74HC04 .35 74HC21 .50 74HC354 .35 74HC05 .35 74HC21 .50 74HC354 .35 74HC06 .35 74HC21 .50 74HC354 .35 74HC07 .35 74HC21 .50 74HC354 .35 74HC08 .35 74HC21 .50 74HC354 .35 74HC09 .35 74HC21 .50 74HC354 .35 74HC10 .35 74HC21 .50 74HC354 .35 74HC11 .35 74HC21 .50 74HC354 .35 74HC12 .35 74HC21 .50 74HC354 .35 74HC99 .35 74HC21 .50 74HC354 .35 74HC00 .35 74HC21 .50 74HC354 .35 74HC01 .35 74HC21 .50 74HC354 .35 74HC02 .35 74HC21 .50 74HC354 .35 74HC03 .35 74HC21 .50 74HC354 .35 74HC04 .35 74HC21 .50 74HC354 .35 74HC05 .35 74HC21 .50 74HC354 .35 74HC06 .35 74HC21 .50 74HC354 .35 74HC07 .35 74HC21 .50 74HC354 .35 74HC08 .35 74HC21 .50 74HC354 .35 74HC09 .35 74HC21 .50 74HC354 .35 74HC10 .35 74HC21 .50 74HC354 .35 74HC11 .35 74HC21 .50 74HC354 .35 74HC12 .35 74HC21 .50 74HC354 .35 74HC13 .35 74HC21 .50 74HC354 .35 74HC14 .35 74HC21 .50 74HC354 .35 74HC15 .35 74HC21 .50 74HC354 .35 74HC16 .35 74HC21 .50 74HC354 .35 74HC17 .35 74HC21 .50 74HC354 .35 74HC18 .35 74HC21 .50 74HC354 .35 74HC19 .35 74HC21 .50 74HC354 .35 74HC20 .35 74HC21 .50 74HC354 .35 74HC21 .35 74HC21 .50 74HC354 .35 74HC22 .35 74HC21 .50 74HC354 .35 74HC23 .35 74HC21 .50 74HC354 .35 74HC24 .35 74HC21 .50 74HC354 .35 74HC25 .35 74HC21 .50 74HC354 .35 74HC26 .35 74HC21 .50 74HC354 .35 74HC27 .35 74HC21 .50 74HC354 .35 74HC28 .35 74HC21 .50 74HC354 .35 74HC29 .35 74HC21 .50 74HC354 .35 74HC30 .35 74HC21 .50 74HC354 .35 74HC31 .35 74HC21 .50 74HC354 .35 74HC32 .35 74HC21 .50 74HC354 .35 74HC33 .35 74HC21 .50 74HC354 .35 74HC34 .35 74HC21 .50 74HC354 .35 74HC35 .35 74HC21 .50 74HC354 .35 74HC36 .35 74HC21 .50 74HC354 .35 74HC37 .35 74HC21 .50 74HC354 .35 74HC38 .35 74HC21 .50 74HC354 .35 74HC39 .35 74HC21 .50 74HC354 .35 74HC40 .35 74HC21 .50 74HC354 .35 74HC41 .35 74HC21 .50 74HC354 .35 74HC42 .35 74HC21 .50 74HC354 .35 74HC43 .35 74HC21 .50 74HC354 .35 74HC44 .35 74HC21 .50 74HC354 .35 74HC45 .35 74HC21 .50 74HC354 .35 74HC46 .35 74HC21 .50 74HC354 .35 74HC47 .35 74HC21 .50 74HC354 .35 74HC48 .35 74HC21 .50 74HC354 .35 74HC49 .35 74HC21 .50 74HC354 .35 74HC50 .35 74HC21 .50 74HC354 .35 74HC51 .35 74HC21 .50 74HC354 .35 74HC52 .35 74HC21 .50 74HC354 .35 74HC53 .35 74HC21 .50 74HC354 .35 74HC54 .35 74HC21 .50 74HC354 .35 74HC55 .35 74HC21 .50 74HC354 .35 74HC56 .35 74HC21 .50 74HC354 .35 74HC57 .35 74HC21 .50 74HC354 .35 74HC58 .35 74HC21 .50 74HC354 .35 74HC59 .35 74HC21 .50 74HC354 .35 74HC60 .35 74HC21 .50 74HC354 .35 74HC61 .35 74HC21 .50 74HC354 .35 74HC62 .35 74HC21 .50 74HC354 .35 74HC63 .35 74HC21 .50 74HC354 .35 74HC64 .35 74HC21 .50 74HC354 .35 74HC65 .35 74HC21 .50 74HC354 .35 74HC66 .35 74HC21 .50 74HC354 .35 74HC67 .35 74HC21 .50 74HC354 .35 74HC68 .35 74HC21 .50 74HC354 .35 74HC69 .35 74HC21 .50 74HC354 .35 74HC70 .35 74HC21 .50 74HC354 .35 74HC71 .35 74HC21 .50 74HC354 .35 74HC72 .35 74HC21 .50 74HC354 .35 74HC73 .35 74HC21 .50</p>
--	--	--	---	---	---	--

INTERACTIVE TV

continued from page 47

to—most of the operation is automatic, and the entire upload takes about five seconds. Once your game console uploads your name, password and score (which are stored in the console's memory), a signal from the control computer instructs the micro-processor to also upload the counter contents.

The central computer

The return link of the interactive system ends at the central computer. Its block diagram is shown in Fig. 3. As we mentioned earlier, the central computer controls the SCA subcarrier transmitter. It receives the questions, the correct answers, and a difficulty multiplier for each question from the interactive game judge. It transmits all the information, via an FM SCA subcarrier to the game console, which keeps its own score.

The SCA transmitter also sends out random counter-start signals, which are sent to the game consoles to start one of the ten counters. An equivalent set of counters in the central computer also receive the start signals.

When the player calls to upload his results, his score is transmitted first, followed by his ID and password, which are checked and, we hope, approved. Then the contents of the consoles's ten counters are uploaded, and are compared with the counters of the central computer. If everything matches, the score is recorded. After the upload time period is over, (say 1/2 hour after the end of the game) the winners will be notified, via the FM subcarrier.

Security

The interactive TV system can be used for a lot more than playing games. Using the game console for placing orders to a home-shopping channel or to order pay-per-view programming are only a couple of the many potential uses. State-lottery

registration might be in the works, also. If IGN's system is going to be used for something as potentially lucrative as winning the state lottery, it had better be secure. There are sure to be more than just high-school kids trying to get through the security measures. All data that is uploaded and downloaded by the game console is encrypted using DES (the Data Encryption Standard). To make it even more of a challenge to would-be hackers, the required software can be changed every day, so that a potential hacker has, at most, 24 hours to crack the security code!

Each console has its own software-encryption key, and thus its own way of sending encrypted data. Since all game players must be subscribers with registered ID's and passwords, it will quickly be obvious who is trying to play around.

Speaking of playing around, the next time you find yourself watching a game show, remember: Now's the time to start getting in shape to win the game of the 1990's. **R-E**

  <p>6" x 9" COAXIAL SPEAKERS Super buyout. Made in Japan by Pioneer for GM. Upgrade auto sound system. 6" x 9" woofer, 2 1/2" cone tweeter. 35 watts RMS, 50 watts max. 12 oz. magnet, Dust cover. Sold in pairs. 8 lbs./pair. Limited quantities.</p> <p>#300-220 \$1450 \$1195 (1-5 prs) (6 prs-up)</p>	<h3>SPEAKERS AND COMPONENTS</h3>     		 <p>EMINENCE Made in U.S.A.</p> <p>18" WOOFER 100 oz. magnet, 3" voice coil. 250 watts RMS, 350 watts max. 8 ohm, 30 Hz resonant frequency, 22-2700 Hz response. Efficiency: 95 dB, 1W/1M. Paper cone treated accordion surround. Net wt: 29 lbs.</p> <p>#290-200 \$9880 \$8950 (1-3) (4-up)</p>
  <p>15" WOOFER 60 watts RMS, 90 watts max. 1 1/2" voice coil. 8 ohm, 25-2500 Hz response. 20 oz. magnet, paper cone with poly foam surround. 93 dB, 1W/1M sensitivity. Net weight: 7 lbs.</p> <p>#290-160 \$2895 Any Qty.</p>	 <p>EMINENCE MADE IN U.S.A.</p> <p>10" WOOFER Super duty 34 oz. magnet, 2" voice coil. Paper cone, treated accordion surround. 100 watts RMS, 140 watts max. 8 ohm, 70Hz resonant frequency, response: 45-4000 Hz. Net weight: 8 lbs.</p> <p>#290-098 \$3150 \$2870 (1-3) (4-up)</p>	 <p>12" POLY WOOFER Super duty, 40 oz. magnet. Polypropylene cone. 100 watts RMS, 145 watts max. 4-8 ohm compatible (6 ohm). 2" voice coil.</p> <p>#290-125 \$3680 \$3450 (1-3) (4-up)</p>	
 <p>WOODGRAIN GRILL CLOTH Authentic woodgrain print design cloth. 36" x 60"</p> <p>#260-340 \$595 Per Yard</p>	<p>12" 3-WAY, 100 WATT SYSTEM Pioneer design engineers carefully evaluated the performance characteristics of this speaker systems to ensure the best full range frequency response.</p> <p>System Includes: (1) #290-125 poly woofer, (1) #280-045 heavy duty 5 1/4" midrange, (1) #270-035 4" soft dome tweeter, (1) #260-210 3-way 100 watt crossover, (2) #260-255 50 watt L-pads, (1) #260-300 terminal, and (1) #260-340 woodgrain grill cloth. Recommended cabinet volume: 3.1 cu ft. Cabinet Kit Available #260-390 \$19.95 each</p> <p>#12-100 \$7395 each</p> <p>Save Over \$1000</p>		  <p>HORN TWEETER Exponential horn design. Mylar dome. 3 1/2" x 3 1/2". 1800-20,000Hz response. 35 watts RMS, 50 watts max.</p> <p>#270-050 \$650 \$590 (1-9) (10-up)</p>
 <p>340 E. First St., Dayton, OH 45402 Local 1-513-222-0173 FAX: 513/222-4644</p>		<p>CALL TOLL FREE 1-800-338-0531</p> <p>* 15 day money back guarantee. * \$10.00 minimum order. * We accept Mastercard, Visa, Discover, and C.O.D. orders. * 24 hour shipping. * Shipping charge = UPS chart rate (\$2.50 minimum charge). * Hours: 8:30 am - 6:00 pm EST, Monday - Friday. * Mail order customers, please call for shipping estimate on orders exceeding 5 lbs.</p>  <p>FREE CATALOG</p>	

Radio Shack Parts Place


GREAT VALUES—AND GIFTS—FOR BUILDERS AND FIXERS!

Novice Ham Study Package

Take Advantage of the New Voice Privileges

19⁹⁵

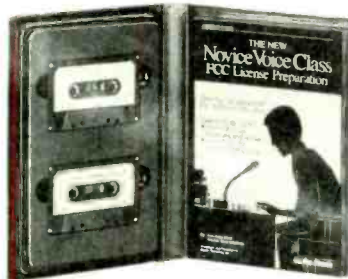Radio Shack's Novice Exam Study Package includes two cassettes for self-paced code learning plus practice exam. #62-2402




Includes Durable Binder

"Hotline" Order Service Saves Time and Postage

Our store manager can order a wide variety of parts and accessories from the Radio Shack warehouse. Fast service, no minimum order!

SAMS Books Now Available

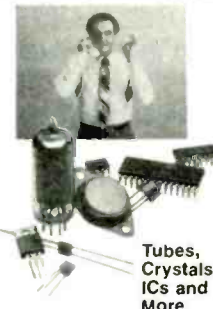We can also order many of the famous SAMS service manuals. Come in for details.




Tubes, Crystals, ICs and More

Electronic Speech Recognition


Design Your Own System

NEW! 9⁹⁵

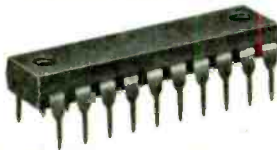

VCP200. Experiment with leading-edge technology—voice recognition! This high-tech IC recognizes spoken commands regardless of the person speaking—five motion commands and two on/off commands. Clipped analog input simplifies circuitry so no external A-to-D conversion is needed. 20-pin DIP with data. #276-1308

Handle RAMS and CMOS the Safe Way

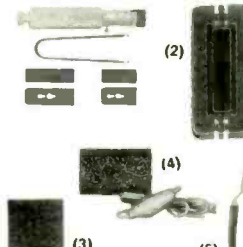

- (1) IC In/Out Tool Kit. For 6 to 40-pin DIPs. #276-1581 6.95
- (2) IC Pin Aligner. Factory-straight pins in a jiffy! #276-1594 2.99
- (3) Conductive Foam. 5 x 5" safety mat for your bench. #276-2400 .. 89¢
- (4) Static-Draining Wrist Strap. 24" ground lead. #276-2399 2.79
- (5) Soldering Heat Sink. Prevents heat damage. #276-1567 1.39

Opto Bargains



- (1) Super-Bright LED. 2000 mcd output! #276-087. . . 1.69
- (2) Jumbo LED. Six LED elements in a single housing! #276-064 3.49
- (3) Flexible Solar Cell. 65 mA at 1.2V. #276-138 .. 5.95

Precision Tool Kit

10⁹⁵

Fitted Case



Top-quality jeweler's-type philips and blade drivers, nutdrivers, hex keys and a torque bar—16 pieces in all. #64-1961

Metal Pocket Flashlight

9⁹⁵



Heavy-Duty Aluminum

Krypton bulb—visible over a mile away! Rotate head to turn on/off and adjust beam width. Batteries extra. #61-2736

Loud Buzzers



- (1) Pulsing or Continuous Buzzer. Piezo type. #273-068 7.95
- (2) Chime. #273-071 8.69
- (3) Mini DC Buzzers. With leads.

VDC	Cat No.	Each
1.5-3	273-053	1.99
6	273-054	1.99
12	273-055	1.99

Megacable™

NEW!

99¢ Per Foot

Our best-ever speaker cable. 12-gauge braided pure copper conductors. #278-1268



6⁴⁹ 4-cond., 5 feet long. #278-355

Thermistor

1⁹⁹

Precision device converts temperature to proportional resistance. -50 to +100° C. Ideal for remote sensing. #271-110

15-Turn Trimmer Pots

- 10% 1.49 Each
- 3/4-Watt 1.49
- 1k. #271-342 1.49
- 10k. #271-343 1.49
- 20k. #271-340 1.49

RF Project Parts

NEW!

- (1) NEW! 95-420 pF Trimmer Capacitor. #272-1336 1.69
- (2) Dual 335 pF Variable Capacitor. #272-1337 4.95

50 Small-Value Caps

NEW! Ceramic discs, 1 to 33 pF, 50WVDC. #272-806, Set 2.99

Studfinder

19⁹⁵

Ends Guessing

Easy to use and saves time! Senses changes in wall density to find wooden studs fast—also locates wires, conduit and pipes. Battery extra. #64-2825

Pro Soldering Station

39⁹⁵

- 15 or 25 Watts
- Grounded Tip

A super value! With a convenient sponge tip-cleaning pad. UL listed AC. #64-2057




Logic Probe and Pulsar

16⁹⁵

Probe. LEDs and tones reveal logic states in TTL, LS and CMOS circuits. #22-303

17⁹⁵

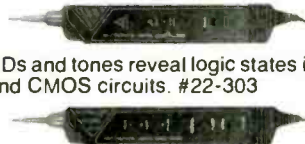Pulsar. Teammate for the probe. Produces a single 5 µs pulse or a continuous pulse train at the push of a button. #22-304



Benchtop Digital VOM

99⁹⁵

Manual or Autoranging

Our best! Has analog display in addition to big LCD digital readout. Built-in transistor gain checker, diode-check, memory function, continuity buzzer and more. Includes probes and illustrated manual. #22-195



Over 1000 Items in stock! Binding Posts, Books, Breadboards, Buzzers, Capacitors, Chokes, Clips, Coax, Connectors, Fuses, Hardware, ICs, Jacks, Knobs, Lamps, Multitesters, PC Boards, Plugs, Rectifiers, Resistors, Switches, Tools, Transformers, Transistors, Wire, Zeners, More!

Prices apply at participating Radio Shack stores and dealers

Radio Shack
The Technology Store™

A DIVISION OF TANDY CORPORATION

CIRCLE 78 ON FREE INFORMATION CARD

JDR Microdevices

• 30 DAY MONEY BACK GUARANTEE • 1 YEAR WARRANTY ON ALL PRODUCTS • TOLL-FREE TECHNICAL SUPPORT

STATIC RAMS

PART	SIZE	SPEED	PRICE
2112	256x4	450ns	2.99
2114	1024x4	450ns	.99
2114L-2	1024x4	200ns	1.49
TC5516	2048x8	250ns	3.95
TMM2016-100	2048x8	200ns	3.25
TMM2016-150	2048x8	150ns	3.29
TMM2016-100	2048x8	100ns	4.29
HM6116-4	2048x8	200ns	4.95
HM6116-3	2048x8	150ns	5.95
HM6116-2	2048x8	120ns	6.45
HM6116LP-3	2048x8	200ns	5.95
HM6116LP-2	2048x8	150ns	6.95
HM6116LP-15	8192x8	150ns	9.95
HM6264LP-12	8192x8	120ns	10.95
HM43256LP-15	32768x8	150ns	12.95
HM43256LP-12	32768x8	120ns	14.95
HM43256LP-10	32768x8	100ns	19.95

CALL TO CONFIRM CURRENT PRICES

DYNAMIC RAMS

PART	SIZE	SPEED	PRICE
4116-200	16384x1	200ns	.89
4116-150	16384x1	150ns	.99
MK4332	32768x1	200ns	6.95
4164-150	65536x1	150ns	2.89
4164-120	65536x1	120ns	3.19
4164-100	65536x1	100ns	3.95
TMS4164	65536x1	150ns	2.89
TMS4416	16384x4	150ns	8.95
41128-150	131072x1	150ns	5.95
TMS4464-15	65536x4	150ns	10.95
TMS4464-12	65536x4	120ns	11.95
41256-150	262144x1	150ns	12.45
41256-120	262144x1	120ns	12.95
41256-100	262144x1	100ns	13.45
41256-80	262144x1	80ns	13.95
HMS1258-100	262144x1	100ns	13.95
1MB-120	1048576x1	120ns	34.95
1MB-100	1048576x1	100ns	37.95

CALL TO CONFIRM CURRENT PRICES

EPROMS

PART	SIZE	SPEED	Vpp	PRICE
2708	1024x8	450ns	25V	4.95
2716	2048x8	450ns	25V	3.49
2716-1	2048x8	350ns	25V	3.95
2732	4096x8	450ns	25V	3.95
2732A	4096x8	250ns	21V	3.95
27C64	8192x8	250ns	12.5V	4.95
2764	8192x8	450ns	12.5V	3.49
2764-250	8192x8	250ns	12.5V	3.69
2764-200	8192x8	200ns	12.5V	4.25
MCM68766	8192x8	350ns	21V	15.95
27128	16384x8	250ns	12.5V	4.95
27128A-200	16384x8	200ns	12.5V	5.95
27C256	32768x8	250ns	12.5V	7.95
27256	32768x8	250ns	12.5V	5.95
27256-200	32768x8	200ns	12.5V	7.95
27512	65536x8	250ns	12.5V	11.95
27C512	65536x8	250ns	12.5V	12.95
27C101-20	131072x8	200ns	12.5V	34.95

CALL TO CONFIRM CURRENT PRICES

CO-PROCESSORS

8087	5 MHz	99.95
8087-2	8 MHz	159.95
8087-1	10 MHz	229.95
80287	6 MHz	179.95
80287-8	8 MHz	249.95
80287-10	10 MHz	309.95
80387-16	16 MHz	499.95
80387-20	20 MHz	799.95
80387-25	25 MHz	999.95



intel
5
YEAR
WARRANTY

INCLUDES MANUAL & SOFTWARE GUIDE

**CALL FOR VOLUME QUOTES
ORDER TOLL FREE**

HIGH-TECH SPOTLIGHT

SCSI HOST ADAPTOR \$49.95

A LOW POWER, SHORT SLOT CARD FOR PC COMPATIBLES THAT CAN CONTROL UP TO SEVEN SCSI DEVICES. THIS POPULAR STANDARD OFFERS SPEED, EXPANDABILITY AND THE ADVANTAGES OF USING A DEVICE INDEPENDENT BUS. INCLUDES CABLES. MCT-SCSI

V-20 SERIES

SPEED UP YOUR PC BY 10 TO 40%!

- HIGH SPEED ADDRESS CALCULATION IN HARDWARE
- PIN COMPATIBLE WITH 8088
- SUPERSSET OF 8088 INSTRUCTION SET
- LOW POWER CMOS

V20*	5 MHz	8.95	V20*	8 MHz	10.95
V20*	10 MHz	12.95	V30*	8 MHz	13.95

VOLTAGE REGULATORS

7805T	.49	7812K	1.35
7808T	.49	7905K	1.69
7812T	.49	7912K	1.49
7815T	.49	7810L	.49
7905T	.59	78L12	.49
7908T	.59	79L05	.69
7912T	.59	79L12	1.49
7915T	.59	LM323K	3.49
7805K	1.59	LM338K	4.49

PALS

16L8	2.95
16R8	2.95
16R6	2.95
16R4	2.95

UARTS

AYS-1013	3.95
AYS-1015	4.95
AY3160	3.95
2651	4.95
IM6402	3.95
IM6403	9.95
INS8250	9.95
NS16450	10.95

INTERFACES

ICL7107	10.95
ICL7660	1.99
ICL8038	3.85
ICM7207A	5.95
ICM7208	15.95

MICROPROCESSORS

6500 8000 8200

6502	2.25	8031	3.95	8253-5	1.95
6502A	2.69	8035	1.49	8254	2.79
6502B	4.25	8039	1.95	8255	1.49
65C02*	7.95	8052AH		8255-5	1.59
6520	1.65	BASIC	34.95	8256	15.95
6522	2.95	8080	2.49	8259	1.95
6522A	5.95	8085	1.95	8259-5	2.29
6526	13.95	8085A-2	3.75	8272	4.39
6532	5.95	8086	6.49	8274	4.95
6545A	3.95	8088	5.99	8275	10.95
6551	2.95	8088-1	12.95	8279	2.49
6551A	6.95	8088-2	7.95	8279-5	2.95
CMOS		8155	2.49	8282	3.95
		8156	2.95	8283	3.95
		8155-2	3.95	8284	2.25
		8741	9.95	8285	3.95
		8742	29.95	8287	3.95
		8748	7.95	8288	4.95

6800

6800	1.95
6802	2.95
6803	2.95
6809	5.99
6809E	5.49
6810	1.95
6820	2.95
6821	1.25
68B21	1.85
6840	3.95
6845	4.95
6847	4.75
6850	1.95
68B50	1.75
68B3	22.95
68000	9.95

Z-80

Z80-CPU	1.25
Z80A-CPU	1.29
Z80B-CPU	2.75
Z80A-CTC	1.69
Z80B-CTC	4.25
Z80B-DART	5.95
Z80B-DART	6.95
Z80A-DMA	5.95
Z80A-PIO	1.89
Z80B-PIO	4.25
Z80A-SIO-0	5.95
Z80B-SIO-0	12.95
Z80A-SIO-1	5.95
Z80B-SIO-2	5.95
Z80B-SIO-2	12.95
Z8671 BASIC	9.95

8200

8205	3.29
8212	1.49
8216	1.49
8224	2.25
8228	2.25
8237-5	4.75
8238	4.49
8243	1.95
8250	6.95
8251	1.29
8251A	1.69
8253	1.59

LINEAR COMPONENTS

TL071	.69	LM380	.89	XR2206	3.95
TL072	1.09	LM383	1.95	XR2211	2.95
TL074	1.95	LM386	.89	LM2917	1.95
TL081	.59	LM393	.45	CA3046	.89
TL082	.99	LM394H	5.95	CA3146	1.29
TL084	1.49	LM399H	5.95	MC3373	1.29
LM301	.34	TL494	4.20	MC3470	1.95
LM309K	1.25	TL497	3.25	MC3480	8.95
LM310	1.75	NE555	.29	MC3487	2.95
LM311	.89	NE556	.49	LM3900	.49
LM311H	.89	NE559	.79	LM3909	.98
LM311K	3.49	NE564	1.95	LM3911	2.25
LM312H	1.75	LM565	.95	LM3914	1.89
LM317T	.69	LM566	1.49	LM3915	1.89
LM318	1.49	LM567	.79	MC4024	3.49
LM319	1.25	NE570	2.95	MC4044	3.99
LM323K	3.49	NE590	2.50	RC4136	1.25
LM324	.34	NE592	.98	RC4558	.69
LM331	3.95	LM723	.49	LM1360	1.49
LM334	1.19	LM733	.98	75107	1.49
LM335	1.79	LM741	.29	75108	1.49
LM336	1.75	LM747	.69	75110	1.95
LM338K	4.49	MC1330	1.69	75150	1.95
LM339	.59	MC1350	1.19	75154	1.95
LF347	2.19	LM1458	.35	75188	1.25
LF353	.59	LM1488	.49	75189	1.25
LF356	.99	LM1489	.49	75451	.39
LF357	.99	LM1496	.85	75452	.39
LM358	.59	ULN2003	.79	75477	1.29

HIGH SPEED CMOS LOGIC

74HC00	.21	74HC244	.85	74HCT138	.35
74HC04	.25	74HC245	.85	74HCT139	.55
74HC08	.25	74HC273	.69	74HCT157	.59
74HC14	.35	74HC367	.69	74HCT161	.79
74HC32	.35	74HC373	.69	74HCT240	.89
74HC74	.35	74HC390	.79	74HCT244	.89
74HC138	.45	74HC374	.69	74HCT245	.99
74HC139	.45	74HC4040	.89	74HCT273	.99
74HC154	1.09	74HC704	.25	74HCT373	8.99
74HC157	.65	74HC704	.27	74HCT374	.99
74HC161	.65	74HC708	.25	74HCT393	.99
74HC164	.65	74HC732	.27	74HCT4040	.99
74HC175	.59	74HC774	.45	74HCT4060	1.49

STANDARD CMOS LOGIC

4001	.19	4028	.65	4069	.19
4011	.19	4040	.69	4070	.29
4013	.35	4042	.59	4081	.22
4015	.29	4044	.69	4093	.49
4016	.29	4046	.69	14411	9.95
4017	.49	4047	.69	74433	14.95
4018	.69	4049	.29	14497	6.95
4020	.59	4050	.29	4503	.49
4021	.69	4051	.69	4511	.69
4023	.25	4052	.69	4518	.85
4024	.49	4053	.69	4528	.79
4025	.25	4060	.69	4538	.95
4027	.39	4066	.29	4702	9.95

7400 SERIES LOGIC

7400	.19	74123	.29	74F240	1.29
7402	.19	74125	.49	74500	.29
7404	.19	74150	1.35	74502	.29
7406	.29	74151	.55	74508	.35
7407	.29	74153	.55	74510	.29
7408	.24	74154	1.49	74532	.35
7410	.19	74157	.55	74574	.49
7411	.25	74159	1.65	74586	.35
7414	.49	74161	.69	745112	.50
7416	.25	74164	.85	745124	2.75
7417	.25	74166	1.00	745138	.79
7420	.19	74175	.89	745153</	

CRYSTALS

32.768 KHz	.95
1.0 MHz	2.95
1.8432	2.95
2.0	1.95
2.4576	1.95
3.579545	1.95
4.0	1.95
5.0	1.95
5.0588	1.95
6.0	1.95
6.144	1.95
8.0	1.95
10.0	1.95
10.738635	1.95
12.0	1.95
14.31818	1.95
16.0	1.95
16.0	1.95
16.432	1.95
20.0	1.95
22.1184	1.95

OSCILLATORS

1.4MHz	5.95
1.432	5.95
2.0	5.95
2.3576	5.95
2.5	5.95
4.0	4.95
5.0	4.95
5.3688	4.95
6.0	4.95
6.144	4.95
8.0	4.95
11.0	4.95
12.0	4.95
14.31818	4.95
13.0	1.95
15.0	4.95
16.432	4.95
20.0	4.95
24.0	4.95

BIT RATE GENERATORS

MC14411	9.95
3R1941	4.95
1702	9.95
COM5010	16.95
COM8116	8.95
MM5307	4.95

DISCRETE

1N751	.49	2N4403	.25
IN5402	.25	2N6045	1.75
IN4004	10/1.00	MPS-A13	.40
IN4148	25/1.00	TIP31	.49
KBP02	.55	4N26	.69
PN2222	.10	4N27	.69
2N2907	.25	4N33	.89
2N3055	.79	4N37	1.19
2N3904	.10	MCT-2	.59
2N3906	.10	MCT-6	1.29
2N4401	.25	TIL-111	.99

CAPACITORS

TANTALUM		ELECTROLYTIC	
1.0µf	15V .12	RADIAL	
6.8	10V .42	1µf	50V .14
10	15V .45	4.7	50V .11
22	15V .99	10	50V .11
2.2	35V .45	47	35V .13
4.7	35V .39	100	16V .15
10	35V .69	220	35V .20
		470	25V .30
		2200	16V .70
		4700	25V 1.45

DISC		AXIAL	
10pf	50V .05	1µf	50V .14
22	50V .05	10	16V .14
33	50V .05	10	50V .16
47	50V .05	22	16V .14
100	50V .05	10	50V .19
220	50V .05	47	50V .19
.001µf	50V .05	100	35V .19
.005	50V .05	470	50V .29
.01	50V .07	1000	16V .29
.05	50V .07	2200	16V .70
.1	12V .10	4700	16V 1.25
.1	50V .12		

BYPASS CAPACITORS

.01xx	CERAMIC DISC	100/5.00
.01xx	MONOLITHIC	100/10.00
.1xx	CERAMIC DISC	100/6.50
.1xx	MONOLITHIC	100/12.50

CLOCK CIRCUITS

MC146818	5.95	MM58174	9.95
MM58167	9.95	MSM5832	2.95

SOLDER STATION


UL APPROVED
 ■ ADJUSTABLE HEAT SETTING
 ■ TIP TEMPERATURE READOUT
 ■ REPLACEMENT TIPS AVAILABLE \$2.95
 168-2C



\$49.95

WIREWRAP PROTOTYPE CARDS

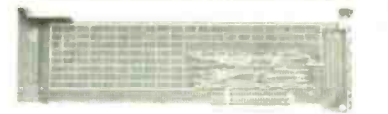FR-4 EPOXY GLASS LAMINATE WITH GOLD PLATED EDGE-CARD FINGERS AND SILK SCREENED LEGENDS.



FOR PS/2		
JDR-PR32	32 BIT PROTOTYPE CARD	69.95
JDR-PR16	16 BIT WITH I/O DECODING LAYOUT	49.95
JDR-PR16PK	PARTS KIT FOR JDR-PR16 ABOVE	15.95
JDR-PR16V	16 BIT FOR VIDEO APPLICATIONS	39.95
FOR AT		
JDR-PR10	16BIT WITH I/O DECODING LAYOUT	34.95
JDR-PR10PK	PARTS KIT FOR JDR-PR10 ABOVE	12.95
FOR XT		
IBM-PR1	WITH +5V AND GROUND PLANE	27.95
IBM-PR2	AS ABOVE WITH I/O DECODING LAYOUT	29.95

FULL 1 YEAR WARRANTY ON EVERY PRODUCT!

POWER SUPPLIES

APPLE TYPE SUPPLY
 ■ APPLE CONNECTOR
 ■ -5V @ 6A, +12V @ 3A, -5V @ 1A, -12V @ 1A
 PS-A \$49.95



75 WATT SUPPLY
 ■ UL APPROVED
 ■ -5V @ 7A, +12V @ 3A, -5V @ 300MA, +12V @ 250MA
 PS-1558 \$34.95

MICRO SUPPLY
 ■ UL APPROVED, 144 WATTS
 ■ -5V @ 18A, -12V @ 4A, +12V @ 500MA
 PS-1554 \$29.95

FLOPPY DRIVE SUPPLY
 ■ +5V @ 2.5A, +12V @ 2A, +12V @ 1A
 ■ +5V @ 5A, IF +12 NOT USED
 PS-ASTEC \$24.95



GENDER CHANGERS

GENDER-FF FEMALE-FEMALE 7.95
 GENDER-MM MALE-MALE 7.95
 GENDER-MF MALE-FEMALE 7.95
 GENDER-NM NULL MODEM 8.95
 GENDER-JB JUMPER BOX 8.95
 GENDER-MT MINITESTER 14.95




DISK CONTROLLERS

1771	4.95	2797	29.95
1791	9.95	8272	4.39
1793	9.95	UP0765	4.39
1795	12.95	MB8876	12.95
1797	12.95	MB8877	12.95
2791	19.95	1691	6.95
2793	19.95	2143	6.95

"SNAPABLE" HEADERS

CAN BE SNAPPED APART TO MAKE ANY SIZE HEADER, ALL WITH 1" CENTERS

1x40	STRAIGHT LEAD	.59
1x40	RIGHT ANGLE LEAD	.49
2x40	2 STRAIGHT LEADS	2.49
2x40	2 RIGHT ANGLE LEADS	2.99

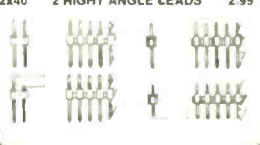


RS-232 BREAKOUT BOX

FOR TROUBLESHOOTING SERIAL COMMUNICATIONS

- OPEN CLOSE INDIVIDUAL CIRCUITS
- 20 JUMPERS CROSS-CONNECT ANY TWO CIRCUITS
- 10 LEDS SHOW CIRCUIT ACTIVITY

GENDER-BO \$34.95

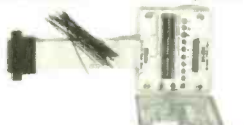

IDC CONNECTORS/RIBBON CABLE

DESCRIPTION	ORDER BY	CONTACTS					
		18	20	26	34	40	50
SOLDER HEADER	IDHxxS	.82	1.29	1.68	2.20	2.58	3.24
RIGHT ANGLE SOLDER HEADER	IDHxxSR	.85	1.35	1.76	2.31	2.72	3.39
WIREWRAP HEADER	IDHxxW	1.86	2.98	3.84	4.50	5.28	6.63
RIGHT ANGLE WIREWRAP HEADER	IDHxxWR	2.05	3.28	4.22	4.45	4.80	7.30
RIBBON HEADER SOCKET	IDSxx	.83	.89	.95	1.29	1.49	1.69
RIBBON HEADER	IDMxx	-	5.50	6.25	7.00	7.50	8.50
RIBBON EDGE CARD	IDExx	.85	1.25	1.35	1.75	2.05	2.45
10" PLASTIC RIBBON CABLE	RCxx	1.60	3.20	4.10	5.40	6.40	7.50

FOR ORDERING INSTRUCTIONS, SEE D-SUBMINIATURE CONNECTORS BELOW

D-SUBMINIATURE CONNECTORS

DESCRIPTION	ORDER BY	CONTACTS						
		9	15	19	25	37	50	
SOLDER CUP	MALE	DBxxP	.45	.59	.69	.69	1.35	1.85
	FEMALE	DBxxS	.40	.69	.75	.75	1.39	2.29
RIGHT ANGLE PC SOLDER	MALE	DBxxPR	.49	.69	-	.79	2.27	-
	FEMALE	DBxxSR	.55	.75	-	.85	2.49	-
WIREWRAP	MALE	DBxxPWW	1.69	2.56	-	3.89	5.60	-
	FEMALE	DBxxSww	2.76	4.27	-	6.84	9.95	-
IDC RIBBON CABLE	MALE	IDBxxP	1.30	1.99	-	2.25	4.25	-
	FEMALE	IDBxxS	1.45	2.05	-	2.35	4.49	-
HOODS	METAL	MHODxx	1.05	1.15	1.25	1.25	-	-
	PLASTIC	HOODxx	.30	.39	-	.39	.60	.75

ORDERING INSTRUCTIONS: INSERT THE NUMBER OF CONTACTS IN THE POSITION MARKED "xx" OF THE "ORDER BY" PART NUMBER LISTED. EXAMPLE: A 15 PIN RIGHT ANGLE MALE PC SOLDER WOULD BE DB15PR.

Mounting Hardware 59¢

IC SOCKETS/DIP CONNECTORS

DESCRIPTION	ORDER BY	CONTACTS								
		8	14	16	18	20	22	24	28	40
SOLDER TAIL SOCKETS	xxST	.11	.11	.12	.15	.18	.15	.20	.22	.30
WIREWRAP SOCKETS	xxWW	.59	.69	.69	.99	1.09	1.39	1.49	1.69	1.99
ZIF SOCKETS	ZIFxx	-	4.95	4.95	-	5.95	-	5.95	6.95	9.95
TOOLED SOCKETS	AUGATxxST	.82	.79	.89	1.09	1.29	1.39	1.49	1.69	2.49
TOOLED WW SOCKETS	AUGATxxWW	1.30	1.80	2.10	2.40	2.50	2.90	3.15	3.70	5.40
COMPONENT CARRIERS	ICxx	.48	.50	.69	.99	.99	.99	.99	1.09	1.49
DIP PLUGS (IDC)	IDPxx	.95	.48	.59	1.29	1.49	-	.85	1.49	1.59

FOR ORDERING INSTRUCTIONS SEE D-SUBMINIATURE CONNECTORS ABOVE

SHORTING BLOCKS

5/91.00



LITHIUM BATTERIES

■ 6.8V FOR 286/386 COMPUTERS
 ■ MOTHERBOARD CONNECTOR
 ■ ADHESIVE VELCRO STRIP FOR EASY MOUNTING

LITHIUM 6.8V \$11.95

LITHIUM-3V 3V COIN TYPE LITHIUM BATTERY \$1.95
 3V-MHW BATTERY HOLDER \$1.49



JDR MICRODEVICES, 110 KNOWLES DRIVE, LOS GATOS, CA 95030
 LOCAL (408) 866-6200 FAX (408) 378-8927 TELEX 171-110
 RETAIL STORE: 1256 SOUTH BASCOM AVE., SAN JOSE, CA (408) 947-8881
 HOURS: M-F 10-7 SAT. 9-5 SUN. 12-4

ORDER TOLL FREE 800-538-5000

COPYRIGHT 1988 JDR MICRODEVICES CONTINENTAL U.S. AND CANADA

TERMS: MINIMUM ORDER \$10.00 FOR SHIPPING AND HANDLING INCLUDE \$2.50 FOR UPS GROUND AND \$3.50 UPS AIR. ORDERS OVER 1 LB. AND FOREIGN ORDERS MAY REQUIRE ADDITIONAL SHIPPING CHARGES—PLEASE CONTACT THE SALES DEPARTMENT FOR THE AMOUNT. CA RESIDENTS MUST INCLUDE APPLICABLE SALES TAX. PRICES ARE SUBJECT TO CHANGE WITHOUT NOTICE. WE ARE NOT RESPONSIBLE FOR TYPOGRAPHICAL ERRORS. WE RESERVE THE RIGHT TO LIMIT QUANTITIES AND TO SUBSTITUTE MANUFACTURER. ALL MERCHANDISE SUBJECT TO PRIOR SALE. A FULL COPY OF OUR TERMS IS AVAILABLE UPON REQUEST. ITEMS PICTURED MAY ONLY BE REPRESENTATIVE.

JDR Microdevices

• 30 DAY MONEY BACK GUARANTEE • 1 YEAR WARRANTY ON ALL PRODUCTS • TOLL-FREE TECHNICAL SUPPORT

2400 BAUD MODEMS

\$129.95



\$169.95



SAVE TIME AND TELEPHONE CHARGES WITH A HIGH SPEED 2400 BAUD MODEM FROM JDR.

INTERNAL 2400 BAUD

- AUTO DIAL ANSWER
- SELF TEST ON POWER-UP
- TOUCHTONE OR PULSE DIALING
- HAYES & BELL SYSTEMS COMPATIBLE
- FULL OR HALF DUPLEX
- MIRROR II COMMUNICATIONS SOFTWARE INCLUDED

MCT-24I 1200 BAUD 1/2 CARD \$129.95

MCT-24M 2400 BAUD FOR PS/2 \$249.95

EXTERNAL 2400 BAUD

- 2400/1200/300 HAYES COMPATIBLE
- 8 EASY-TO-READ STATUS LED'S
- CALL PROGRESS MONITORING & ADJUSTABLE VOLUME
- 2ND PHONE JACK FOR VOICE COMMUNICATIONS
- REQUIRES SERIAL PORT & CABLE (OPTIONAL)

MCT-24E \$169.95

MCT-12E 1200 BAUD EXTERNAL \$99.95

APPLE/MACINTOSH MODEMS

MACINTOSH 2400 BAUD EXTERNAL AS ABOVE WITH CABLE AND PROCOM-M SOFTWARE.


MCT-24EM \$199.95

MCT-24A APPLE II 2400 BAUD MODEM \$179.95

MCT-12A APPLE III/200 BAUD MODEM \$139.95

POCKET MODEM

\$99.95

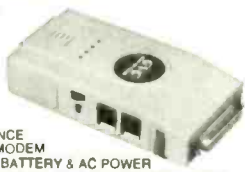

YOU'LL NEVER BE FAR FROM YOUR DATA WITH THIS 6 OUNCE HAND-HELD POCKET MODEM

- 1200/300 BAUD ■ BATTERY & AC POWER
- SERIAL INTERFACE (DB25) ■ 4 STATUS INDICATORS

MCT-12P

KEYBOARDS

MODULAR CIRCUIT TECHNOLOGY

ENHANCED STYLE LAYOUT

- AUTOSENSE FOR XT OR AT COMPATIBLES
- LED INDICATORS ■ AUTO REPEAT FEATURE
- SEPARATE CURSOR PAD

MCT-5339 \$79.95

84 KEY LAYOUT ■ SOFTWARE AUTOSENSE FOR XT OR AT COMPATIBLES

LED INDICATORS ■ AUTO REPEAT \$59.95

MCT-5060

MAXI-SWITCH KEYBOARDS

WITH TACTILE FEEDBACK

MAX-5339 ENHANCED STYLE LAYOUT \$84.95

MAX-5060 84 KEY LAYOUT \$64.95

AUDIBLE "CLICK" KEYBOARD

■ ENHANCED STYLE, 101 KEY KEYBOARD

■ LED INDICATORS ■ AUTO REPEAT

K-103-A \$84.95

HANDY SCANNER

\$249.95



INSTANT SCANNING OF IMAGES UP TO 4" WIDE

- 100, 200, 300, 400 DPI BOTH DIRECTIONS
- B&W AND 3 HALF-TONE MODES
- 32 LEVELS OF GRAY SCALE
- HERCULES, CGA AND EGA COMPATIBLE
- INCLUDES HALO DPE AND IMAGE EDITOR SOFTWARE HS-3000

LOGITECH HIREZ MOUSE

\$129.95



HIGH RESOLUTION BUS MOUSE FOR BETTER RESPONSE AND LESS HAND MOVEMENT. IDEAL FOR CAD WORK

- 320 DPI ■ INCLUDES DRIVER, TEXT EDITOR & POP-UP MENUS ■ NO PAD, POWER SUPPLY OR PORT REQUIRED

LOGITECH 3-BUTTON MOUSE

PC MAGAZINE EDITORS CHOICE! ALL MODELS HAVE SERIAL SUPPORT (COM1/COM2), 200 D.P.I. RESOLUTION, LOTUS 1-2-3 SHELL, SELF-INSTALLING SOFTWARE AND "POINT EDITOR"

LMOUSE \$79.95

LMOUSE-P SERIAL MOUSE W/LOGIPAIN \$99.95

LMOUSE-BP BUS MOUSE W/LOGIPAIN \$99.95

LMOUSE-BPL BUS MOUSE W/PUBLISHER PKG \$139.95

LMOUSE-BPC BUS MOUSE W/LOGIPAIN/CAD \$149.95

CALL OUR 24-HOUR BBS:
(408) 374-2171

FOR TECHNICAL SUPPORT, CONFERENCING,
TIPS AND MORE

CITIZEN PRINTER

\$219.95



A RELIABLE, FAST AND INEXPENSIVE ALL PURPOSE PRINTER THAT'S LOADED WITH FEATURES

- 9 PIN DOT MATRIX PRINT HEAD
- 180 CPS DRAFT MODE, 29 CPS NLQ MODE
- CENTRONICS PARALLEL INTERFACE, SERIAL OPTIONAL
- DUAL PITCH, DOUBLESTRIKE, ITALICS & SUPERSCRIP
- EPSON FX & IBM GRAPHICS
- COMPRESSED, EXPANDED & EMPHASIZED PRINT
- DOT ADDRESSABLE GRAPHICS IN SIX DENSITIES

CITIZEN-180D \$6.95

RC-180D REPLACEMENT RIBBON CARTRIDGE

MOLDED CABLES

CBL-PRINTER PC PRINTER CABLE \$9.95

CBL-PRINTER-25 AS ABOVE - 25 FOOT \$15.95

CBL-PRINTER-RA RIGHT ANGLE PRINTER \$15.95

CBL-DB25-MM DB25 MALE TO DB25 MALE \$9.95

CBL-DB25-MF DB25 MALE TO DB25 FEMALE \$9.95

CBL-9-SERIAL 9 PIN TO 25 PIN SERIAL \$6.95

CBL-KBD-EXT KEYBOARD EXTENSION \$7.95

CBL-CNT-MM 36 PIN CENTRONICS-MM \$14.95

CBL-HD-20 20 PIN HARD DISK CABLE \$3.95

CBL-HD-34 34 PIN HARD DISK CABLE \$4.95

CBL-HD-34D 34 PIN DUAL HARD DISK \$6.95

CBL-FDC-EXT 37 PIN EXTERNAL FLOPPY \$9.95

VGA COMPATIBLE PACKAGE

\$649.00



- 800 X 560 MAXIMUM RESOLUTION
- 640 X 480 IN 16 COLORS
- 320 X 200 IN 256 COLORS
- IBM STYLE ANALOG MONITOR
- FULLY VGA, EGA, CGA, HERCULES & MONOCHROME COMPATIBLE



NEC MULTISYNC II \$599.95

- AUTO FREQUENCY ADJUSTMENT
- RESOLUTION AS HIGH AS 800 X 560

CASPER EGA \$399.95

- 640 X 350 RESOLUTION ■ 31 MM DOT PITCH
- 14" BLACK MATRIX SCREEN ■ 16 COLORS

CASPER RGB \$279.95

- COLOR GREEN AMBER SWITCH ■ 39MM DOT PITCH
- 640 X 240 RESOLUTION ■ 14" NON-GLARE SCREEN

SAMSUNG MONO \$129.95

- 12" NON-GLARE LOW DISTORTION AMBER SCREEN
- 720 X 350 RESOLUTION ■ SWIVEL BASE

MONITOR STANDS

MODEL MS-100 \$12.95

■ TILTS AND SWIVELS

MODEL MS-200 \$39.95

■ TILTS AND SWIVELS ■ BUILT-IN SURGE SUPPRESSOR

■ INDEPENDENTLY CONTROLS UP TO 5 AC OUTLETS

TOWER CASE

\$299.95

SAVE DESKSPACE AND ADD STYLE TO YOUR OFFICE WITH THIS SLEEK UPRIGHT DESIGN

- ACCOMMODATES ALL SIZES OF MOTHERBOARDS
- 250 WATT POWER SUPPLY INCLUDED
- MOUNTS FOR 3 FLOPPY & 4 HARD DRIVES
- TURBO & RESET SWITCH
- SPEED DISPLAY, POWER & DISK LED'S
- MOUNTING HARDWARE, FACEPLATES & SPEAKER INCLUDED

CASE-100 \$34.95

CASE-FLIP FOR 8088 MOTHERBOARDS \$39.95

CASE-SLIDE FOR 8088 MOTHERBOARDS \$89.95

CASE-70 FOR 286 MOTHERBOARDS \$149.95

CASE-JR MINI-286 W/POWER SUPPLY



POWER SUPPLIES

135 WATT \$59.95

- UL APPROVED
- IBM XT COMPATIBLE
- +5V 15A, +12V 4.2A, -5V .5A, -12V .5A

PS-135 \$69.95

PS-150 150W MODEL \$89.95

200 WATT \$89.95

- UL APPROVED
- IBM AT COMPATIBLE
- +5V 22A, +12V 8A, -5V .5A, -12V .5A


PS-200 \$129.95

PS-250 250 WATT MODEL \$129.95



1.44 MB 3 1/2" DRIVE

\$149.95

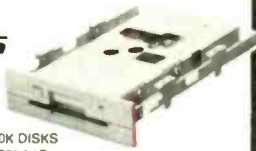

- ULTRA HIGH DENSITY
- ALSO WORKS WITH 720K DISKS
- FDD-1.44X BLACK FACEPLATE
- FDD-1.44A BEIGE FACEPLATE

1 1/2" HEIGHT FLOPPY DISK DRIVES

FD-55B	5-1/4" TEAC DS/DD 360K	\$99.95
FD-55G	5-1/4" TEAC DS/HD 1.2M	\$129.95
M2551A	5-1/4" FUJITSU DS/DD 360K	\$89.95
M2553K	5-1/4" FUJITSU DS/HD 1.2M	\$119.95
FDD-360	5-1/4" DS/DD 360K	\$69.95
FDD-1.2	5-1/4" DS/HD 1.2M	\$109.95
FDD-3.5A	3-1/2" MITSUBISHI DS/DD(BEIGE)	\$129.95
FDD-3.5X	3-1/2" MITSUBISHI DS/DD(BLACK)	\$129.95

TAPE BACK-UP DRIVES

AR5240X	ARCHIVE TAPE DRIVE -XT'S & AT'S	\$369.95
AR5540A	FASTER TAPE DRIVE -AT'S ONLY	\$369.95
AR340	40 MB TAPE CARTRIDGES	\$24.95

DISKETTES

N-MD2D	BOX OF 10 5-1/4" 360K DS/DD	\$6.95
N-MD2H	BOX OF 10 5-1/4" 1.2 MB DS/HD	\$13.95
N-3.5DS	BOX OF 10 3-1/2" 720K DS/DD	\$16.95
N-3.5HD	BOX OF 10 3-1/2" 1.44 MB DS/HD	\$49.95
N-MD2DBULK	360K DS/DD (MIN. 50 DISKS)	EA. 49¢

DRIVE ACCESSORIES

FD-ARAIL	MTG. RAILS FOR AT COMPATIBLE	\$2.95
FD-55FP	BEIGE FACEPLATE FOR TEAC DRIVES	\$2.95
FD-55MHW	HALF-HEIGHT MOUNTING HARDWARE	\$2.95
FD-5Y	Y-POWER ADAPTOR FOR DRIVES	\$2.95

Seagate HARD DISKS

Whatever your hard disk needs, we have reliable, high quality Seagate drives at the lowest prices available. Buy them alone, or with an MCT disk controller for even greater savings!



SIZE	MODEL	AVG. SPEED	HEIGHT	DRIVE ALONE	WITH MCT CONTROLLER			
					HDC	RLL	AFH	AFH-RLL
20MB	ST-225	65 ms	Half	\$225	\$269	-	\$339	-
30MB RLL	ST-238	65 ms	Half	\$249	-	\$299	-	\$389
40MB	ST-251	40 ms	Half	\$429	\$469	-	\$539	-
40MB	ST-251-1	28 ms	Half	\$529	\$569	-	\$639	-
60MB RLL	ST-277	40 ms	Half	\$499	-	\$549	-	\$639
30MB	ST-4038	40 ms	Full	\$559	\$603	-	\$659	-
80MB	ST-4096	28 ms	Full	\$895	\$939	-	\$995	-

INBOARD 386/PC

\$895.00



UPGRADE YOUR XT TO A 386 FOR LESS THAN \$900

- 16 MHZ PROCESSOR REPLACES 8088
- 1 MB MEMORY INSTALLED
- EXPAND TO 3 MB WITH PIGGYBACK CARD
- 5 YEAR WARRANTY

PCIB 1200

PIGGYBACK MEMORY BOARDS

PCIB1210	1 MB INSTALLED	\$649.00
PCIB1220	2 MB INSTALLED	\$1195.00

NEW!! SIGMA VGA CARD

\$279.50



100% REGISTER COMPATIBLE VGA DISPLAY CARD

- VGA, EGA, CGA, HGC & MDA COMPATIBLE
 - 320 X 200 IN 256 COLORS
 - 640 X 480, 800 X 600 IN 16 COLORS
 - 80 X 25, 132 X 44 TEXT MODES
 - SUPPORTS STANDARD DIGITAL & ANALOG MONITORS
 - UTILITY SOFTWARE INCLUDED
- MCT-VGA

INTERFACE CARDS

BY MODULAR CIRCUIT TECHNOLOGY

DRIVE CONTROLLERS

FLOPPY DISK CONTROLLER \$29.95

SINGLE SLOT CONTROL OF 4 FLOPPIES
 ■ INTERFACES UP TO 4 FDD'S TO AN IBM PC OR COMPATIBLE ■ SUPPORTS DS/DD AND DS/QD W/ DOS 3.2
 MCT-FDC

1.2 MB FLOPPY CONTROLLER \$69.95

ADD VERSATILITY AND CAPACITY TO YOUR XT
 ■ SUPPORTS 2 DRIVES, CAN MIX 360K AND 1.2 MB
 ■ ALLOWS DATA TO FLOW FREELY FROM XT'S TO AT'S
 MCT-FDC-1.2

FLOPPY/HARD CONTROLLER \$139.95

XT SYSTEM SHORT OF SLOTS? THIS CARD FREES ONE UP!
 ■ INTERFACES UP TO 2 FDD'S & 2 HDD'S, CABLING FOR 2
 FDD/1HDD ■ SUPPORTS BOTH DS/DD & DS/QD W/ DOS 3.2
 MCT-FH

286/386 FLOPPY/HARD \$149.95

FLOPPY/HARD DISK CONTROL IN A TRUE AT DESIGN
 ■ SUPPORTS UP TO 2 360K/720K/1.2 MB FDD'S
 ■ SUPPORTS 2 HDD'S USING STANDARD TABLES
 MCT-AFH

HARD DISK CONTROLLER \$79.95

HARD DISK CONTROL AT AN ECONOMICAL PRICE
 ■ SUPPORTS 16 DRIVE SIZES INCLUDING 10,20,30 & 40 MB
 ■ DIVIDE 1 LARGE DRIVE INTO 2 LOGICAL DRIVES
 MCT-HDC

RLL CONTROLLER \$119.95

TRANSFER DATA 50% FASTER
 ■ SUPPORTS UP TO 2 RLL HARD DRIVES
 ■ DESIGNED FOR XT COMPATIBLES
 MCT-RLL

286/386 FLOPPY/HARD RLL \$199.95

IMPROVE SPEED AND STORAGE OF YOUR AT COMPATIBLE
 ■ SUPPORTS UP TO 2 RLL HARD DISCS AND 2 FLOPPIES
 ■ SUPPORTS 360/720/1.2 MB FLOPPIES IN 5.25" & 3.5"
 MCT-AFH-RLL

MULTIFUNCTION CARDS

MULTI I/O FLOPPY CONTROLLER \$79.95

A PERFECT COMPANION FOR OUR MOTHERBOARDS
 ■ SUPPORTS UP TO TWO 360K FLOPPIES, 720K W/ DOS 3.2
 ■ SERIAL, PARALLEL, GAME PORT, CLOCK/CALENDAR
 MCT-MIO

MIO-SERIAL—2ND SERIAL PORT \$15.95

MULTI I/O CARD \$59.95

USE WITH MCT-FH FOR MINIMUM OF SLOTS USED
 ■ SERIAL PORT, CLOCK/CALENDAR WITH BATTERY
 ■ PARALLEL PORT ADDRESSABLE AS LPT1 OR LPT2
 MCT-I/O

286/386 MULTIFUNCTION \$139.95

ADDS UP TO 3 MB OF RAM TO YOUR AT
 ■ USER EXPANDABLE TO 1.5 MB OR 3 MB WITH OPTIONAL
 PIGGYBACK BOARD (OK INSTALLED) ■ INCLUDES SERIAL
 AND PARALLEL PORT

MCT-AMF \$29.95

MCT-AMF-MC PIGGYBACK BOARD \$29.95

AMF-SERIAL 2ND SERIAL PORT \$24.95

286/386 MULTI I/O CARD \$59.95

USE WITH MCT-AFH MINIMUM OF SLOTS USED
 ■ SERIAL, PARALLEL AND GAME PORTS ■ USES 16450
 SERIAL SUPPORT CHIPS FOR HIGH SPEED OPS
 MCT-AIO

AIO-SERIAL 2ND SERIAL PORT \$24.95

MEMORY CARDS

576K RAM CARD \$59.95

A CONTIGUOUS MEMORY SOLUTION IN A SHORT SLOT
 ■ USER SELECTABLE CONFIGURATION UP TO 576K
 ■ USES 64K & 256K RAM CHIPS (OK INSTALLED)
 MCT-RAM

EXPANDED MEMORY CARD \$129.95

2MB OF LOTUS INTEL MICROSOFT MEMORY FOR AN XT
 ■ CONFORMS TO LOTUS INTEL EMS ■ USER EXPAND-
 ABLE TO 2 MB ■ CAN BE USED AS EXPANDED OR
 CONVENTIONAL MEMORY, RAMDISK AND SPOOLER
 MCT-EMS
 MCT-AEMS 286/386 VERSION \$139.95

DISPLAY ADAPTORS

MONOCHROME GRAPHICS \$59.95

TRUE HERCULES COMPATIBILITY SUPPORTS LOTUS 1-2-3
 ■ PARALLEL PRINTER PORT CONFIGURES AS LPT1 OR
 LPT2 ■ USES VLSI CHIPS TO ENSURE RELIABILITY
 MCT-MGP

EGA ADAPTOR \$149.95

100% IBM COMPATIBLE PASSES IBM EGA DIAGNOSTICS
 ■ 256K OF VIDEO RAM ALL CWS 640 X 350 IN 16 OF 64
 COLORS ■ COMPATIBLE WITH COLOR AND MONO-
 CHROME ADAPTORS ■ HERCULES COMPATIBLE
 MCT-EGA

COLOR GRAPHICS ADAPTOR \$49.95

COMPATIBLE WITH IBM GRAPHICS STANDARDS
 ■ SUPPORTS RGB, COLOR, & COMPOSITE MONOCHROME
 ■ 640/320 X 200 RESOLUTION, LIGHT PEN INTERFACE
 MCT-CG

MONOGRAPHICS MULTI I/O \$119.75

TOTAL SYSTEM CONTROL FROM A SINGLE SLOT!
 ■ CTRL 2 FLOPPIES, SERIAL, PARALLEL, GAME PORT,
 CLOCK CAL ■ RUN COLOR GRAPHICS SOFTWARE ON A
 MONOCHROME MONITOR
 MCT-MGMI0

286/386 MONOGRAPHICS I/O \$99.95

VIDEO DISPLAY AND I/O FUNCTIONS IN ONE CARD
 ■ 720 X 348 RESOLUTION, 30 & 132 COLUMN TEXT
 ■ PARALLEL, SERIAL & GAME PORTS
 MCT-MGAI0

BARGAIN HUNTER'S CORNER

MULTIFUNCTION CARD

- INCLUDES FULL ONE YEAR WARRANTY
- XT COMPATIBLE
- 2-384K DYNAMIC RAM USING 4164'S
- SERIAL PORT & PARALLEL PRINTER PORT
- GAME CONTROLLER PORT
- CLOCK/CALENDAR
- SOFTWARE FOR RAM DISK, PRINT SPOOLER AND
 CLOCK/CALENDAR

ONLY \$59.95

SPECIAL ENDS 11/30/88



JDR MICRODEVICES, 110 KNOWLES DRIVE, LOS GATOS, CA 95030
 LOCAL (408) 866-6200 FAX (408) 378-8927 TELEX 171-110

RETAIL STORE: 1256 SOUTH BASCOM AVE., SAN JOSE, CA (408) 947-8881
 HOURS: M-F 10-7 SAT. 9-5 SUN. 12-4

ORDER TOLL FREE 800-538-5000

COPYRIGHT 1988 JDR MICRODEVICES

CONTINENTAL U.S. AND CANADA

TERMS: MINIMUM ORDER \$10.00 FOR SHIPPING AND HANDLING INCLUDE \$2.50 FOR UPS
 GROUND AND \$3.50 UPS AIR. ORDERS OVER 1 LB. AND FOREIGN ORDERS MAY REQUIRE
 ADDITIONAL SHIPPING CHARGES—PLEASE CONTACT THE SALES DEPARTMENT FOR THE
 AMOUNT. CA RESIDENTS MUST INCLUDE APPLICABLE SALES TAX. PRICES ARE SUBJECT
 TO CHANGE WITHOUT NOTICE. WE ARE NOT RESPONSIBLE FOR TYPOGRAPHICAL
 ERRORS. WE RESERVE THE RIGHT TO LIMIT QUANTITIES AND TO SUBSTITUTE
 MANUFACTURER. ALL MERCHANDISE SUBJECT TO PRIOR SALE. A FULL COPY OF OUR
 TERMS IS AVAILABLE UPON REQUEST. ITEMS PICTURED MAY ONLY BE REPRESENTATIVE.

BUILD YOUR OWN SYSTEM!

OVER 20,000 JDR SYSTEMS HAVE ALREADY BEEN BUILT. EASY TO ASSEMBLE IN JUST 2 HOURS WITH A SCREWDRIVER. SAVE MONEY AND LEARN MORE ABOUT YOUR COMPUTER AT THE SAME TIME!



VIDEO INSTRUCTIONS

\$4.95 WITH KIT PURCHASE

A JDR EXCLUSIVE! 20-MIN. VHS OR BETA TAPE SHOWS YOU STEP-BY-STEP HOW TO BUILD AN XT COMPATIBLE SYSTEM. W/O KIT \$19.95

10 MHz TURBO 8088

\$661⁰⁰

- INCLUDES SERIAL PORT, 2 PARALLEL PORTS, CLOCK CALENDAR AND GAME ADAPTOR ■ RUNS COLOR GRAPHICS ON A MONOCHROME MONITOR
- MOTHERBOARD ■ 256K RAM MEMORY ■ 135 WATT POWER SUPPLY ■ FLIP-TOP CASE ■ 84 KEY KEYBOARD
- 360K FLOPPY DRIVE ■ MONOGRAPHICS I/O CARD ■ MONOCHROME MONITOR

12 MHz MINI-286

\$1232⁷⁵

- 12 MHz MINI-286 MOTHERBOARD ■ 512K RAM MEMORY ■ MINI CASE WITH POWER SUPPLY
- 84 KEY KEYBOARD ■ MONOCHROME MONITOR
- 1.2 MB FLOPPY DRIVE ■ FLOPPY / HARD CONTROL ■ GRAPHICS ADAPTOR

16 MHz 1 Mb 386

\$2348⁶⁵

- MYLEX 386 MOTHERBOARD ■ 1 MB RAM ON BOARD
- 200 WATT POWER SUPPLY ■ CASE ■ ENHANCED KEYBOARD ■ 1.2 MB FLOPPY DRIVE ■ FLOPPY/HARD CONTROLLER ■ MONOGRAPHICS CARD ■ MONOCHROME-MONITOR

MOTHERBOARDS

TURBO 4.77/8 MHz

\$99.95

- XT COMPATIBLE ■ NORTON SI 1.7 ■ 4.77 OR 8 MHz OPERATION WITH 8088-2 AND OPTIONAL 8087-2 CO-PROCESSOR ■ FRONT PANEL LED SPEED INDICATOR AND RESET SWITCH SET SUPPORTED ■ CHOOSE NORMAL/TURBO MODE OR SOFTWARE SELECT PROCESSOR SPEED

MCT-TURBO

MCT-XMB STANDARD MOTHERBOARD \$87.95

10 MHz TURBO SINGLE CHIP 8088

\$129.95

- XT COMPATIBLE ■ NORTON SI 2.1 ■ USES LESS POWER, IMPROVES RELIABILITY ■ KEY SELECTABLE SPEED, 4.77 MHz OR 10 MHz ■ 2.3 TIMES FASTER THAN A STANDARD ■ RESET SWITCH, KEYLOCK, AND SPEED / POWER INDICATORS SUPPORTED

MCT-TURBO-10

80286 6/10 MHz

\$379.95

- AT COMPATIBLE ■ LANDMARK AT SPEED 10 MHz ■ NORTON SI 10.3 ■ 8 SLOTS (TWO 8-BIT, SIX 16-BIT) ■ HARDWARE SELECTION OF 6 OR 10 MHz ■ FRONT PANEL LED INDICATOR
- SOCKETS FOR 1MB OF RAM AND 80287 ■ ONE WAIT STATE ■ BATTERY BACKED CLOCK ■ KEYLOCK SUPPORTED ■ RESET SWITCH

MCT-286

12 MHz MINI-286

\$399.95

- AT COMPATIBLE ■ LANDMARK AT SPEED 13.2 MHz ■ NORTON SI 11.6 ■ 6 MHz, 10 MHz (0/1 WAIT STATE), 12 MHz (1 WAIT STATE) ■ ZYKOS ASICS FOR FEWER CHIPS, GREATER RELIABILITY ■ SUPPORTS 512K-1024K MEMORY ■ RECHARGEABLE HIGH CAPACITY Ni-CAD BATTERY ■ SIX 16-BIT SLOTS, TWO 8-BIT SLOTS ■ MOUNTS IN STANDARD XT CASE

MCT-M286-12

MCT-M286 6 /10 MHz MINI 80286 BOARD \$389.65

16 MHz MYLEX 386

\$1699.00

- 1 MB RAM ON BOARD ■ 8 SLOTS (TWO 8-BIT, SIX 16-BIT) ■ USES AMI BIOS
- SUPPORTS 80287 MATH CO-PROCESSOR ■ SUPPORTS 80387 WITH ADAPTOR
- 64KB CACHE FOR NEAR 0 WAIT STATE ■ 20 MHz VERSION AVAILABLE

MCT-386MB

MCT-386MB-4 FOUR MB MEMORY INSTALLED \$2999.00

MCT-386MB-MCB MATH CO-PROCESSOR ADAPTOR BOARD \$149.00

16 MHz MYLEX MINI 386

\$1249⁰⁰


- LANDMARK AT SPEED 23.2 MHz ■ NORTON SI 18.7 ■ 64KB HIGH SPEED DIRECT MAPPED STATIC RAM CACHE ■ 1 MB OR 2 MB MEMORY ON STD. MEMORY BOARD ■ UP TO 8 MB OF 32-BIT MEMORY ON PIGGYBACK MEMORY BOARD, FOR TOTAL OF 10 MB ■ AMI BIOS WITH 32 BIT EGA SUPPORT ■ SOCKETED FOR 80387 MATH CO-PROCESSOR ■ ONE 8-BIT, FOUR 16-BIT AND ONE 32-BIT SLOTS ■ DALLAS CMOS /CLOCK DEVICE ON BOARD W/ BATT.

MCT-386 JR (MEMORY CARD REQUIRED)

MCT-386JR20 20 MHz VERSION \$1695.00

MCT-386JR-M 1 TO 2 MB MEMORY CARD (REQUIRED) 0/ INSTALLED \$159.00

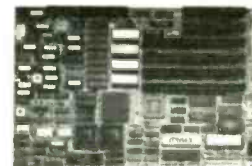MCT-386JR-M8 8 MB PIGGYBACK MEMORY BOARD 0K INSTALLED \$159.00



NEW! MODULAR PROGRAMMERS

THE IDEAL SYSTEM FOR DEVELOPERS. ALL MODULES USE A COMMON HOST ADAPTOR CARD

HOST ADAPTOR CARD **\$29.95**

- A UNIVERSAL INTERFACE FOR ALL THE PROGRAMMING MODULES ■ USER SELECTABLE PROGRAMMABLE ADDRESSES PREVENT ADDRESSING CONFLICTS ■ MENU-DRIVEN SOFTWARE PACKAGE ■ INCLUDES MOLDED CABLE

MCT-MAC

UNIVERSAL MODULE **\$499.99**


- PROGRAMS EPROMS, EEPROMS, PALS, BI-POLAR PROMS 8748 & 8751 SERIES DEVICES ■ TESTS TTL, CMOS, DYNAMIC & STATIC RAMS

MCT-MUP

DIGITAL IC MODULE **\$129.95**

- TESTS TTL, CMOS, DYN. & STATIC RAM ■ AUTO SEARCH

MCT-MIC

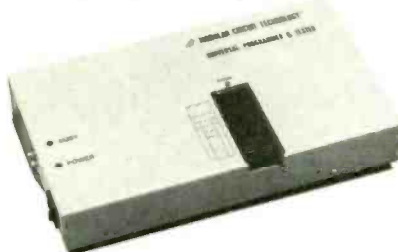

EPROM MODULE **\$119.95**

- PROGRAMS 24-32 PIN EPROMS, CMOS EPROMS AND EEPROMS FROM 16K TO 1024K

MCT-MEP

MCT-MEP-4 FOUR-EPROM PROGRAMMER \$169.95

MCT-MEP-8 EIGHT-EPROM PROGRAMMER \$259.95

PAL MODULE **\$249.95**

- PROGRAMS MMI, NS, TI 20 & TI 24 PIN DEVICES

MCT-MPL

8748 MODULE **\$179.95**

- PROG. 8741, 8742, 8748, 8749 & 8750 EPROMS & PROMS.

MCT-MMP

BI-POLAR MODULE **\$259.95**

- PROG. AMD, MMI, NS, TI & SIGNETICS BI-POLAR PROMS

MCT-MBP

JDR Microdevices®

JDR MICRODEVICES, 110 KNOWLES DRIVE, LOS GATOS, CA 95030

LOCAL (408) 866-6200 FAX (408) 378-8927 TELEX 171-110

ORDER TOLL FREE 800-538-5000

COPYRIGHT 1988 JDR MICRODEVICES

BBS (408) 374-2171




MMC
MEMBER OF
RADIO-ELECTRONICS

CONTINENTAL U.S. AND CANADA

SPECIAL PRODUCTS FROM MCM ELECTRONICS

TENMA Soldering Station

- Adjustable temperature range of 150° - 420°C (300° - 790°F)
- Grounded tip for soldering static sensitive devices
- LED power, heater and temperature indicators
- Overheat protection with closed loop temperature control
- Heat resistant soldering iron cord
- Grounded three wire power cord
- Auxiliary ground terminal
- Built-in tray with cleaning sponge
- Easily accessible fuse holder
- Replaceable iron clad tip
- Improved circuit design for greater temperature stability
- Adjustable temperature, and a variety of available tips make this unit perfect for most soldering applications including SMD

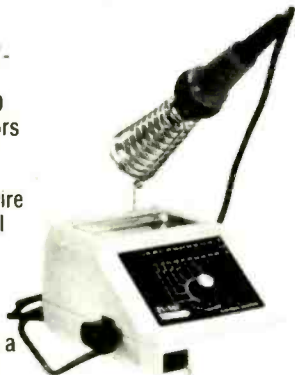

#21-147

TENMA Autorange DMM

The rotary dial design permits rapid selection of functions. Meter automatically selects proper range for most accurate reading.

- 3½ digit LCD display
- Autorange/manual range selector
- Data hold: Holds display reading after meter is removed from circuit
- Memory: Removes stored measurement from future readings
- Audible continuity tester
- Low battery indicator
- Switchable Lo/Hi power ohms
- Comes complete with test leads, carrying case and owners manual



#72-560

Quick Shot Joystick

- Compatible with Nintendo Entertainment System
- Six positive response micro-switches
- Trigger-like primary fire button
- Thumb-activated secondary fire button
- Contoured pistol grip
- Select/start switch
- Auto-fire switch
- Four stabilizing suction cups

#83-0280



Amplified Indoor FM Antenna

- Helps your FM receiver deliver clean undistorted sound
- Adjustable gain
- Improves reception without installing unsightly outdoor antenna
- Black color blends well with any decor

#80-335



MCM ELECTRONICS
858 E. CONGRESS PARK DR.
CENTERVILLE, OH 45459-4072
A PREMIER Company

CIRCLE 87 ON FREE INFORMATION CARD



atus AM300E Stereo Mixer

Top quality rack mountable mixer manufactured by Audio-Technica. Perfect for amateur and professional DJ use.


- Echo circuit with continuously adjustable "repeat" and "delay"
- Built-in five band per channel graphic equalizer with in/out switch
- Ten switchable inputs with five slide and one rotary level controls
- Slide pot for smooth turntable cross-fade
- Six position headphone monitor allows user to cue any input
- Built-in 20dB mute and 10dB microphone "talkover" circuits
- Master output levels are displayed on dual V.U. meters

#80-315

Automatic CD Cleaner

- Motorized chamois cleaning system provides true radial cleaning
- Cleaner automatically stops when finished
- Can be used wet or dry
- 1 oz. bottle of cleaning fluid included
- Operates on four "AA" batteries (not included)

#80-320

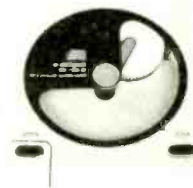

CD 700 Headphones

These lightweight headphones deliver full size sound. Semi-open design earpads are comfortable even during extended listening.

- 30mm dynamic mylar speaker
- 32ohm impedance
- 20-20KHz frequency response
- 10' straight cord with 3.5mm plug
- ¼" adaptor included

#35-320



audio-technica SG750CD Headphones

- Expressly designed for use with digital playback systems
- High sensitivity ensures wide dynamic range
- Earpieces completely cover ears to filter out undesired outside noises
- Speaker: 40mm mylar full range driver
- Frequency response: 20-20,000Hz
- Impedance: 35ohm
- 7½' straight cord with ¼" phone plug for use with all home stereo systems

#35-330



For your FREE copy of our
NEW MCM ELECTRONICS CATALOG,
CALL TOLL FREE 1-800-543-4330

In Ohio, call 1-800-762-4315
In Alaska or Hawaii, call 1-800-858-1849

SOURCE NO. RE-51

What's New at AMERICAN DESIGN COMPONENTS?

We warehouse 60,000 items at American Design Components—expensive, often hard-to-find components for sale at a fraction of their original cost!

You'll find every part you need—either brand new or removed from equipment (RFE) in excellent condition. But quantities are limited. Order from this ad, or visit our retail showroom and find exactly what you need from the thousands of items on display.

OPEN MON.—SAT., 9–5

THERE'S NO RISK!

With our 90-day warranty, any purchase can be returned for any reason for full credit or refund.

COMMODORE COMPUTERS...



★ **PLUS 4 —**
(Cust. Returns — Tested Good!)
Built-in software incl.: a word processor, spread sheet, graphics, & a filing system. Comes complete w/power supply & instruction manual.
★

Item #19202 **\$49.95**
VIC 20 — (Cust. Returns — As Is!)
No guarantee. (Power supply not incl.)
Item #18770 **\$29.95**

COMMODORE 8050 Dual Disk Drive Unit...



The 8050 uses 2 full-height, 100 TPI single-sided disk drives, ea. w/storage cap. of 533,248 bytes. Ea. 8050 diskette has 77 tracks & is read/write compatible w/the 8250 disk drive. Complete w/built-in power supply. Power req.: 115VAC/60Hz. (manuals incl.) Dim.: 13 3/4" W x 13 3/4" D x 6"H.
Item #19313 New — **\$89.95**

ADAM COMPUTER



(Less Printer)
No wiring necessary (just plugs together). Incl. hook-up diagram; Keyboard, 1 cassette digital data drive, 2 game controllers, power supply & 1 cassette. Capable of running CP/M, has built-in word processor.
Item #7410 Complete — **\$99.00**

ACCESSORIES...

DATA DRIVE — Item #6641... **\$19.95**
PRINTER POWER SUPPLY — Item #6642... **\$14.95**
ASCII KEYBOARD — Item #6643... **\$19.95**
CONTROLLERS (Set of 4) — Item #7013... **\$9.95** RFE
ADAM CASSETTES — Incl. Smart Basic, Buck Rogers & blank cassette. Item #7786
Baker's Dozen — **\$19.95**
DISK DRIVE POWER SUPPLY — Item #14603... **\$14.95**
ADAM DAISY PRINT WHEEL — Item #13305... **\$3.95**

COLECOVISION to ADAM EXPANSION KIT

Just plugs into your ColecoVision. W/printer power supply & data drive (both incl.) you will have a working ADAM computer. Adam keyboard, 1 Smart Basic cassette & hook-up diagram also incl.
Item #9918 **\$59.50**

5 1/4" FULL-HEIGHT HARD DISK DRIVES



40Mb (AT/XT Compat.)
High speed, 40 ms. access time. Quantum #Q540
Item #17765 New — **\$379.00**
10Mb (ST412 Compat.)
Major manufacturers — Get them while they last!
Item #17199 **\$99.00** ea.

5 1/4" HALF-HT. 10Mb HARD DISK DRIVES



10Mb (IBM Compatible)
Mfr — NEC #D5124
Item #19704 New — **\$99.00**
20Mb (ST225 Compatible)
Mfr — Olivetti #EM5520/2
Tested—Like New!
Item #20060 New — **\$159.00**

5 1/4" FULL-HEIGHT DISK DRIVE (IBM® Compat.)



48 TPI, 40 Track, Double Side/Double Density
Tandon #TM100-2 or equiv.
Item #7928 **\$79.00** New
2 for **\$150.00** New

5 1/4" 1.2Mb. HALF-HEIGHT FLOPPY DISK DRIVE



IBM® AT Compatible.
48/96 TPI, 1.2 Mb. Double sided, high density; 160 tracks. Mfr — Panasonic #JU-475
Item #10005 New — **\$99.95**

3 1/2" MICROFLOPPY DISK DRIVE



1 Mb (unformatted), 135 TPI, 3 ms. access time. Power requirements: +12, +5 volts. Removed from operational computers — TESTED — LIKE NEW!
Mfr — NEC, model FD1035
Item #17171 **\$79.00** ea.
2 for **\$150.00**

★ 2-WAY, HIGH-TECH, WALL MOUNT SPEAKER SYSTEM (3 1/4" Thin) ★



80W. max., 4/8 Ohm, 150–20,000 Hz.
Cabinet: heavy-duty aluminum, black w/mesh grille cover.
Dim.: 9"H x 13 1/2"W x 3 1/4" deep
Mfr #SB-5000
Item #19634 **\$119.00**/pair

★ EXTERNAL DISK DRIVE CHASSIS ★



With 60W power supply (fan cooled). Can accommodate: 2 full-hr. drives our item #7928 2 floppy drives..... #13250 1 hard drive & 1 floppy..... #13250 Input: 115/230V, 50/60 Hz. Orig. for Burroughs computer. Dim.: 11"W x 8"H x 12" deep
Item #14541 **\$59.50**

115 CFM MUFFIN® FANS



115VAC, 60Hz., 21W., 2BA., 3100 RPM, 5-blade model, aluminum housing. Can be mounted for blowing or exhaust. Dimen: 4 1/8" sq. x 1 1/2" deep
NEW — Mfr: IMC
Item #1864 **\$9.95**
USED — Mfr: Centaur/Howard
Item #5345 **\$5.95**

Call or write with any other requirements...

TTL MONITORS... HI-RES... (Open Frame)



12" — Monitor Kit
Green phosphor. Input: 115VAC. Made up of sub assemblies: CRT, board, & transformer. (Hook-up diagram incl.)
Item #6811 New — **\$19.95**
15" Data Display/Monitor Kit
Alphanumeric & graphics display. Green phosphor. Input power req. 24VDC. Bandwidth: 22–72KHz. Consists of 2 subassemblies: CRT & board. (Hook-up diagram incl.)
Wells Gardner #15V7025
Item #16171 New — **\$24.95**

12/24VDC MUFFIN®-TYPE FANS 55/100CFM



8W. Can be mtd. for blowing or exhaust. Alum. housing. Brushless, ball-bearing type. 1" THIN: 5 plastic blades with feathered edges. Centaur #CUDC24K4-601
Item #8541 New — **\$19.95**
1" STANDARD: 5 plastic blades. Centaur #CNDC24K4-601
Item #12848 **\$14.95** RFE

Free Catalog with every order!

COMPUTER/GAME ADAPTERS...



COMMODORE 64
DC Output: +5VDC @ 7.5W and 9VAC @ 6.7VA
Input: 117VAC, 50/60Hz.
Commodore #310157-02 (black)
Item #19315 New — **\$24.95**
COLECOVISION
DC Output: +5VDC @ 9A -5VDC @ .1A +12VDC @ .3A
Input: 120VAC/60Hz., .25A
Coleco #55416 (black)
Item #1882 New — **\$9.95**

HEAD & SCREEN MAINTENANCE KIT (5 1/4" Diskettes)




Maintain your disk heads & CRT screens. Use regularly to help prevent memory loss & downtime. Protecting users from eye strain. One bottle of head-cleaning fluid, 2 head-cleaning diskettes, & 10 wet/10 dry screen cleaning pads.
Mfr — Dialight #611-0001
Item #19228 New — **\$7.95**

COLECOVISION Accessories...

EXPANSION MODULE #2
Play arcade quality driving & racing games on your ColecoVision. Incl. Turbo cartridge.
Item #13146 New — **\$39.95**
ROLLER CONTROLLER
Gives full 360° game control. High speed action of an arcade. Can be used w/the Adam. Incl. Slither cartridge.
Item #13147 New — **\$39.95**
SUPER ACTION CONTROLLER SET
Gives you indiv. control of 4+ on-screen players. Includes Baseball cartridge.
Item #13148 New — **\$39.95**

RECORDING TAPE 7 1/2" Reel, 2400 ft.

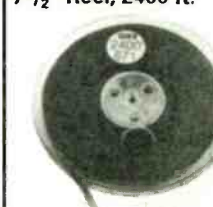

1/4 Mil. Bulk erased. Major mfrs.: Ampex, Scotch, etc. Item #6711.
15 reels for **\$9.95**

HIGH-RESOLUTION INSTRUMENTATION TAPE




1/2" tape on 14" reels; 9200/rev. Wide band, highly conductive tape, w/magnetic oxide surface (makes it ultrasmooth for chart-wave recording). Orig. used in gov't & other critical instrument applications. Standard hub size.
Mfr — Scotch/Ampex #890/892
Item #17656 **\$8.95** ea.
2 for **\$16.00**

NICAD BATTERY PACKS (Rechargeable) "AA" Cells




12V @ 450ma
Contains 10 "AA" cells, connected in series. Recharge rate: 45 ma., 16–18 hrs. Case w/tab output connex.
Dim.: 2 1/8" x 2 1/8" x 2 1/8"
Mfr — GE #123233
Item #5443 **\$5.95** RFE

"Sub C" Cells

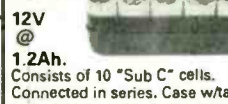

12V @ 1.2Ah.
Consists of 10 "Sub C" cells. Connected in series. Case w/tab output connex. Recharge rate: 100 ma. for 14–16 hrs.
Dim.: 4 1/2" x 1 3/4" x 1 7/8"
Mfr — GE or equiv.
Item #19677 **\$9.95** RFE

"C" Cells

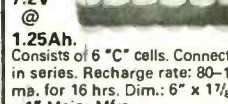

7.2V @ 1.25Ah.
Consists of 6 "C" cells. Connected in series. Recharge rate: 80–100 ma. for 16 hrs. Dim.: 6" x 1 7/8" x 1". Major Mfrs.
Item #19676 **\$9.95**

MECHANICAL KEYBOARDS...



48-KEY — Timex Z81/1000
Item #6712 New — **\$5.95**
75-KEY — Timex or Adam
For computer upgrade—
Item #7429 New — **\$5.95**
66-KEY — Commodore C-16
Item #9394 New — **\$5.95**

NEON TRANSFORMER (Hi-Voltage)



7300 VAC @ 5 Ma.
May be used for powering neon lights, replacing oil burner ignition transformer, building Jacob's ladder (spark gap). Hi-voltage output: 1/4 quick connect terminal & case ground input fully enclosed metal case. Wt. 12 lbs. Base mount case: 4 1/2"H x 5 1/2"W x 6 7/8".
Item #151 New — **\$14.95**

RADIO-ELECTRONICS

Active gives you more...

- SELECTION
- QUALITY
- SERVICE
- VALUE

1660 POINT QUALITY PROJECT BOARD

15⁵⁰



- * Ideal for full circuit designs
 - * 2 terminal strips with 1260 tie-points
 - * 4 distribution strips with 400 tie-points
 - * 3 binding posts for power connections
- ACT NO: 69311

QUALITY 2 TO 1 DB25 SERIAL SWITCH BOX

30⁴⁰



- * Permits low-cost sharing of peripherals
 - * Quality rotary switch construction
 - * Gold plated connector contacts
 - * No external power required
- ACT NO: 69393

QUALITY OSCILLOSCOPE PROBE KIT


34⁹⁹



- * Switchable X1 x10 attenuation ranges
 - * Input impedance (X1) 1Megohm (X10) 10Megohms
 - * Bandwidth (X1) 10MHz (X10) 100MHz
 - * Maximum input voltage 600V
 - * Compensation range 10-60pf
- ACT NO: 70138

QUALITY MINI BREAK-OUT BOX

42²⁰

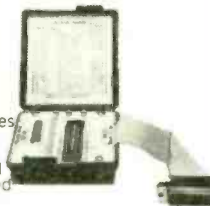

- * Allows complete testing of RS232 lines
 - * 24 DIP switches for reconfigurations
 - * 20 jumpers included
 - * 12 interface powered LED's for status monitoring
- ACT NO: 70196

QUALITY ANTI-STATIC FIELD SERVICE KIT

47⁵⁰



- * For in-the-field static protected conditions
 - * Tear-resistant, dissipative fabric
 - * Wrist strap and grounding cords included
 - * A must for all professional service personnel
- ACT NO: 69269

QUALITY EPROM ERASER


64⁰⁰



- * Erases up to 8 eproms in 15-20 minutes
 - * Two-part, high impact plastic case
 - * Recommended for hobbyist/student use
 - * Erases 24, 28 or 40 pin eproms
- ACT NO: 69492

QUALITY EFI SUPPRESSOR STRIP

105²⁵

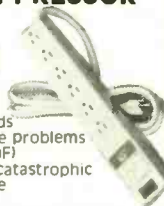

- * Handles up to 10 amp loads
 - * Under 1ns response to line problems
 - * Brownout protection (4.5uF)
 - * Protects against possible catastrophic failures due to line voltage problems/transients
 - * UL listed with circuit breaker/high impact plastic housing
- ACT NO: 69326

QUALITY, SUPER RUGGED TOOL CASE

120⁷⁰



- * Size 17 3/4 x 14 1/2 x 9"
 - * Numerous pockets for secure tool storage
 - * Quality high density polyethylene construction
 - * Anodized aluminum valence and draw bolt latches
- ACT NO: 86130
- Tools not included

Semiconductors and Integrated circuits... In stock for immediate delivery.

LINEAR			TRANSISTORS			SN74LS SERIES		
PART #	ACT #	PRICE	PART #	ACT #	PRICE	PART #	ACT #	PRICE
AM26LS31PC	54012	1.58	2N2222A	02185	3/1.58	SN74LS02N	05776	4/1.58
AM26LS32PC	54096	1.97	2N2946	02188	1.03	SN74LS04N	05780	4/1.58
TL062CP	54097	1.05	2N2904A	02190	3/1.36	SN74LS06N	05784	4/1.58
TL064CN	54041	1.81	2N2905A	02191	2/1.03	SN74LS08N	05786	4/1.58
TL071CP	54042	2/1.05	2N2907A	02193	3/1.58	SN74LS14N	05802	2/1.25
TL072CP	54043	2/1.05	2N3053	02194	2/2.08	SN74LS20N	05806	4/1.58
TL074CN	54044	1.47	2N3055	02196	1.58	SN74LS30N	05818	4/1.58
TL081CP	54142	2/1.05	2N3440	02198	2/2.19	SN74LS32N	05820	4/1.49
TL082CP	54046	2/1.36	2N3771	02193	2.36	SN74LS37N	05834	2/1.58
TL170CLP	54050	2/1.05	2N3772	02205	2.97	SN74LS73AN	05846	3/1.45
TL172CLP	54051	2/1.05	2N3773	02206	3.08	SN74LS74N	05846	3/1.25
TL173CLP	54427	1.14	2N3792	02214	2.36	SN74LS75AN	05850	3/1.25
MAX232CPE	54010	4.00	2N3819	02207	2/1.03	SN74LS76AN	05852	3/1.25
TL272CP	54437	1.05	2N3905	02211	5/1.03	SN74LS85N	05858	2/1.75
TL274CN	54103	1.36	2N3906	02212	5/1.03	SN74LS86N	05860	3/1.25
3001TC	06132	2/1.03	2N4401	02214	4/1.03	SN74LS90N	05864	3/2.08
311TC	06103	3/1.14	2N4820	02239	1.96	SN74LS93N	05866	3/1.58
318TC	06074	1.14	2N4823	02240	1.86	SN74LS123N	05888	2/1.58
319PC	06061	1.29	2N5064	02217	3/1.25	SN74LS125AN	05892	3/1.47
324PC	06025	3/1.36	2N5401	02224	5/1.25	SN74LS138N	05902	2/1.14
339PC	06042	3/1.25	BU406	26102	1.36	SN74LS139N	05904	2/1.14
347PC	06225	1.03	IRF530	26028	2.01	SN74LS148N	05906	1.64
349PC	06045	2/1.58	IRF533	26032	2.41	SN74LS153N	05909	2/1.14
353TC	06136	2/1.58	IRF520	26056	1.04	SN74LS157N	05913	3/1.64
358TC	06104	3/1.47	IRF520	26057	2.71	SN74LS161AN	05916	2/1.58
393TC	06105	3/1.36	IRF740	26058	3.75	SN74LS163AN	05918	2/1.58
TL494CN	54100	1.58	MJ302	26072	2.47	SN74LS164AN	05919	2/1.58
555TC	06106	3/1.03	MLE172	26083	1.03	SN74LS192N	05931	2/1.64
TL555CP	54404	3/1.54	26096	26096	1.14	SN74LS193N	05932	2/1.64
RLE555CP	54148	1.58	MPS102	44001	3/1.58	SN74LS221N	05936	2/2.08
558PC	06042	3/1.25	MPSA06	44003	4/1.05	SN74LS244N	05943	1.03
558PC	06225	1.36	MPSA06	44005	4/1.05	SN74LS245N	05945	1.03
567TC	06050	2/1.47	MPSA13	44070	3/1.05	SN74LS257AN	05952	2/1.14
733PC	06064	2/1.84	MPSA42	44013	3/1.05	SN74LS259N	05954	1.03
741HC	06122	2/1.54	MPSA43	44014	3/1.05	SN74LS273N	05956	1.03
741HT	06075	3/1.25	2N2222A	44077	3/1.05	SN74LS373N	05971	5/3.97
747PC	06049	2/1.14	TIP29C	29002	2/1.36	SN74LS374N	05970	1.03
TD41170N	54031	1.97	TIP30C	29004	2/1.36	SN74LS380N	05975	1.03
TD41170S	54040	1.25	TIP31C	29076	2/1.36	MORE IN STOCK-CALL		
MC1300A1P	54082	1.25	TIP30C	29077	2/1.75	SN7400 SERIES		
MC1350P	54019	1.06	TIP33C	29016	2.00	SN7400N	05500	3/1.14
MC1408B	54019	1.75	TIP41C	29019	1.36	SN7402N	05506	3/1.14
1458TC	06082	3/1.14	TIP42C	29080	1.36	SN7404N	05510	3/1.14
1488PC	06089	3/1.25	TIP50	29083	1.25	SN7406N	05516	2/1.03
1488PC	06087	3/1.25	TIP42	29039	2/1.47	SN7408N	05518	2/1.03
ULN2003AN	54401	2/1.97	TIP102	29001	2/1.47	SN7408N	05520	3/1.14
ULN2004AN	54402	2/1.97	TIP110	29040	2/2.54	SN7407N	05526	2/1.03
NR2206CP	54072	3.75	TIP112	29041	1.03	SN7416N	05528	2/1.03
2240PC	06061	1.36	TIP117	29043	1.65	SN7417N	05530	2/1.03
ULN2803A	54067	1.68	TIP120	29044	1.03	SN7430N	05546	2/1.03
ULN2804A	54068	1.47	TIP122	29081	1.72	SN7432N	05548	3/1.14
ULN2981A	54439	1.90	TIP125	29026	2/1.58	SN7438N	05550	2/1.03
MC3340P	54025	1.14	TIP127	29082	1.47	SN7442AN	05556	2/1.14
MC347ADP	54029	2.36	TIP147	29046	2.36	SN7445N	05562	1.03
MC3486P	54030	1.58	MORE IN STOCK-CALL			SN7447AN	05566	1.03
MC3487P	54031	1.58	TRIACS			SN7474N	05588	2/1.03
SGS524BJ	54426	2.58	TIC1060	29085	2/2.08	SN7475N	05592	2/1.03
3900PC	06210	2/1.36	TIC116M	29100	1.47	SN7476N	05594	3/1.47
4136PC	06215	2/1.36	TIC1260	29087	2.01	SN7490AN	05610	5/3.08
4151TC	06072	1.03	TIC260	29088	1.75	SN74121N	05640	2/1.03
4558TC	06220	3/1.25	TIC180	29090	2.08	SN74123N	05644	2/1.14
NE5532AP	54089	1.60	TIC280	29095	2.08	SN74150N	05670	1.64
NE5534AP	54034	1.58	MORE IN STOCK-CALL			MORE IN STOCK-CALL		


THE ACTIVE DIFFERENCE... QUALITY!

There are many mailorder companies to choose from — all trying to be competitive with their pricing... but pricing only tells a very small part of the story. All components and accessories sold by **ACTIVE** are of the highest industrial quality. No surplus... no seconds... no pulls. **ACTIVE** is a proud affiliate of **FUTURE Electronics** (the 8th largest electronic components distributor in North America). As such, **ACTIVE** has over one hundred million dollars of prime, first grade inventory. Our stores (20 now and more opening every month) have over **10,000 items in stock... FOR IMMEDIATE DELIVERY.** **FUTURE Electronics** is a franchised distributor for over 200 of the best known names in electronics. And since we have been supplying Industrial, Institutional, O.E.M.'s and service personnel for over 20 years, we know how to do it right.

Remember, all **ACTIVE** parts are first grade, industrial quality, are supplied to us solely by **FUTURE Electronics** and as such are totally suitable for use in any project or repair. And, you can count on that. **Judge us by the companies we keep...**

- | | | | | | | | |
|---------|--------|-------------|------------|---------|---------|---------|-------------|
| ALPHA | SAMS | CHEMTRONICS | H.H. SMITH | WELLER | STANCOR | BECKMAN | TAB |
| XCELITE | TPI | DAETRON | TSM | EDUKIT | VACO | UNGAR | SCORPIO |
| OK | WISHER | GC | | HITACHI | | MUELLER | AND MORE... |

Active

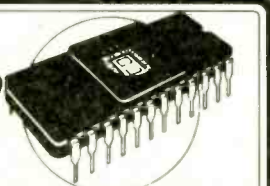

TOLL FREE ORDER NUMBER 1-800-ACTIVE 4

PARTIAL LISTING ONLY
ACTIVE HAS THOUSANDS OF DIFFERENT SEMI-CONDUCTORS AND INTEGRATED CIRCUITS AVAILABLE FOR OFF-THE-SHELF DELIVERY. IF THE TYPE YOU REQUIRE IS NOT LISTED, PLEASE CALL FOR PRICING.

ORDERING FROM ACTIVE IS EASY...

By Phone
 Our trained telephone order personnel are ready to take your order from 8:00AM to 6:00PM (Eastern). Orders are processed within 24 hours. Please have your credit card (Visa, Mastercard or American Express) handy when you call:
 1-800-ACTIVE 4 (In VT. CALL 1-800-ACTIVE 6)

By Mail
 Simply list the items you would like to order — total your order and add 4.00 (UPS Ground) or 7.00 (UPS Blue) shipping/handling (Massachusetts residents please add state sales tax) and send it, with a cashier's check or money order to cover the total amount to: **Active Mailorder Center, 133 Flanders Road, Westborough, Mass. 01581**

- | | | | |
|----------------------|-----------------|------------------|-----------------|
| In our Stores | Westborough, MA | Woburn, MA | Long Island, NY |
| | Mt. Laurel, NJ | Seattle, WA | Santa Clara, CA |
| | Chicago, IL | Los Angeles, CA | Detroit, MI |
| In Canada: | Quebec, QC | Montreal, QC (2) | Ottawa, ON |
| | Toronto, ON (3) | Winnipeg, MB | Calgary, AB |
| | Edmonton, AB | | Vancouver, BC |

Please call TOLL-FREE or use the Reader Service Card for a FREE copy of our NEW, 1989, 240 PAGE CATALOG

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

low available...Jameco's NEW 1989 Catalog

with 74 pages of Computer Peripherals, Components & More!


RS232 QUICK TESTER



The QTSS quickly determines the proper RS232 configuration required to interface two peripherals. Simply slide the switches and determine by the LEDs which configuration works best.

QTSS. \$49.95 \$29.95

JAMECO SOLDERLESS BREADBOARD SOCKETS

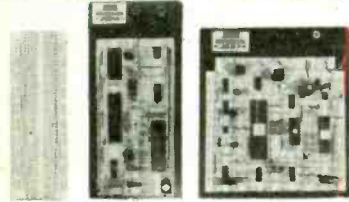

Part No.	Dim. L" x W"	Contact Points	Binding Posts	Price
JE23	6 1/2 x 3 1/4	200	0	\$ 2.95
JE21	3 1/4 x 2 1/2	400	0	\$ 4.95
JE22	6 1/2 x 1 3/4	630	0	\$ 5.95
JE23	6 1/2 x 2 1/2	830	0	\$ 7.95
JE24	6 1/2 x 3 1/2	1,360	2	\$14.95
JE25	6 1/2 x 4 1/4	1,660	3	\$22.95
JE26	6 1/2 x 5 1/4	2,390	4	\$27.95
JE27	7 1/4 x 7 3/4	3,220	4	\$37.95

COMPUTER PERIPHERALS

Jameco
IBM PC/XT/AT
Compatible
Motherboards



JE1001

• AMI BIOS ROMs Included

JE1001 4.77/8MHz (PC/XT). . . . \$ 89.95
JE1002 4.77/10MHz (PC/XT). . . \$109.95
JE3005 8/12MHz (AT). \$329.95

Jameco
Computer
Power



Protection JE1190
JE1190 Power Base. \$29.95
JE1191 6-Outlet Power Strip. . . \$11.95

Jameco IBM PC/XT/AT
Compatible Keyboards



JE1016 Pictured

JE1015 Standard AT layout (XT/AT) . . \$59.95
JE1016 Enhanced layout (XT/AT) . . \$69.95

DATA BOOKS

104100 NSC Linear Data Book-Vol I (88). . . \$14.95
104200 NSC Linear Data Book-Vol II (88). . . \$ 9.95
104300 NSC Linear Data Book-Vol III (88). . . \$ 9.95
210830 Intel Memory Handbook (88). . . \$17.95
230843 Intel Microsystem Hndbk. Set (88). . . \$24.95

U.S. Funds Only
Shipping: Add 5% plus \$1.50 Insurance
(May vary according to weight)

California Residents:
Add 6%, 6 1/2% or 7%
Sales Tax

© 1988 Jameco Electronics 12/88

IBM PC/XT 10MHz Turbo Compatible Kit With 640K RAM

4.77/10MHz Turbo Motherboard
(Zero-K RAM - Includes
AMI BIOS ROM) \$109.95
JE1014 Turbo Flip-Top Case. 69.95
JE1015 XT/AT Compatible Keyboard 59.95
JE1021 5.25" DSDD Disk
Drive (Beige Bezel). 89.95
JE1031 Mini 150W Power Supply. . . . 69.95
Multi I/O with Controller
and Graphics. 119.95
12" Monochrome
Amber Monitor. 99.95
4164-120 Parity RAM (2 chips). 5.90
41256-120 512K RAM (18 chips). . . 215.10
41464-12 128K RAM (4 chips). . . . 51.80

Regular List \$892.45

SAVE \$192.50!

JE3003 IBM Comp. PC/XT 10MHz Turbo Kit \$699.95

IBM COMPATIBLE DISPLAY MONITORS

12" Amber Monochrome -
TTL Input, High Resolution (PC/XT/AT)
AMBER. \$99.95

14" RGB Color - CGA Compatible
Amber/Green/Color Switchable, 640 x
200 Resolution (PC/XT/AT)

CTX2410. \$279.95 CTX2410

14" EGA Color - EGA/CGA Compat., 720 x 350 Max. Resolution (PC/XT/AT)
TM5154. \$399.95

14" EGA Monitor and EGA Card - EGA compatible. 720 x 350 Max.
Resolution - displays up to 16 colors (PC/XT/AT)

JE1059. \$519.95

14" Multiscan Color - VGA/PGC/EGA compatible, 800 x 600 Max. Reso-
lution (PC/XT/AT)

TM5155. \$549.95

IBM PC/XT/AT COMPATIBLE CARDS

Graphic
Display
Cards



JE1050

JE1050 Mono Graphics Card w/Printer Port (PC/XT/AT). . . . \$59.95

JE1052 Color Graphics Card w/Printer Port (PC/XT/AT). . . . \$49.95

JE1055 EGA Card with 256K Video RAM (PC/XT/AT). \$159.95

JE1071 Multi I/O with Drive Controller
and Mono Graphics (PC/XT). \$119.95

Multifunction, I/O and Expansion Cards

JE1060 I/O Card with Serial, Game, Parallel Printer
Port and Real Time Clock (PC/XT). \$59.95

JE1061 RS232 Serial Half Card (PC/XT/AT). \$29.95

JE1065 I/O Card with Serial, Game and
Parallel Printer Port (AT). \$59.95

JE1078 Expand to 384K (zero-K on-board) Multifunc. w/Serial,
Game, Parallel Printer Port & Real Time Clock (PC/XT) . . \$69.95

JE1081 2MB of expanded or extended memory
(zero-K on-board) (AT). \$119.95

JE1081 3MB of expanded or extended memory, parallel printer
port, serial port and game port
(zero-K on-board) (AT). \$169.95

JE1082 Floppy and Hard Disk Controller Cards

JE1040 360KB Floppy Disk Drive Controller Card (PC/XT). . . . \$29.95

JE1041 20/40MB Hard Disk Controller Card (PC/XT). \$79.95

JE1043 360K/720K/1.2MB/1.44MB Floppy Disk Cont. (PC/XT/AT) \$49.95

JE1045 360K/720K/1.2MB/1.44MB Floppy/Hard Disk
Controller Card (AT). \$149.95

COMPUTER PERIPHERALS

Zuckerboard 30Meg Hard Disk Drive
Board for Tandy 1000, 1000A,
1000SX, 1200, 3000 and 3000HL



• 30 Megabytes formatted capacity • Uses
only one slot • Pre-formatted with MS-DOS
T30MB 30MB Hard Disk \$599.95 \$399.95



Seagate 20,30
40 and 60MB
Half Height
Hard Disk
Drives
ST225K (Pictured)

ST225 20MB Drive only (PC/XT/AT). . . . \$224.95
ST225XT 20MB w/Controller (PC/XT/AT). . . \$269.95
ST225AT 20MB w/Controller (AT). \$339.95
ST238 30MB Drive only (PC/XT/AT). . . . \$249.95
ST238XT 30MB w/Controller (PC/XT/AT). . . \$299.95
ST238AT 30MB w/Controller (AT). \$389.95
ST251 40MB Drive only (PC/XT/AT). . . . \$429.95
ST251XT 40MB w/Cont. Card (PC/XT/AT). . . \$469.95
ST251AT 40MB w/Controller Card (AT). . . \$539.95
ST251-1 40MB Fast 28ms (Drive only). . . \$499.95
ST277 60MB Drive only (PC/XT/AT). . . . \$499.95
ST277XT 60MB w/Controller (PC/XT/AT). . . \$549.95
ST277AT 60MB w/Controller Card (AT). . . \$639.95

40MB Tape Back-Up for IBM PC/XT/AT
DJ10 40MB Tape Back-Up. \$349.95
TB40 40MB Tape Cartridge. \$24.95



Jameco 5.25" PC/XT
& AT Compatible
Disk Drives

JE1022 (Pictured)

JE1020 360K Black Bzt. (PC/XT/AT) . . . \$ 89.95
JE1021 360K Beige Bzt. (PC/XT/AT) . . . \$ 89.95
JE1022 1.2MB Beige Bzt. (PC/XT/AT) . . \$109.95

3.5" PC/XT/AT Compatible Disk Drives

3.5" 720KB (Bezels and Installation
Kit Included) (PC/XT/AT) \$129.95 \$109.95
3.5" 1.44MB (Bezels and Installation
Kit Included) (PC/XT/AT) \$149.95 \$129.95

Datatronic 2400/1200/300 Modems



NEW Pocket Version!

• Hayes command compat-
ible • Bell 103/212A com-
patible • Auto-dial/ auto-
answer • FCC approved
1-year warranty • Includes
MaxiMile Communication
Software (except 1200P)

1200P 1200/300 Baud Pocket Modem. . . . \$ 99.95
1200H 1200/300 Baud Internal Modem. . . \$ 69.95
2400S 2400/1200/300 Internal Modem. . . \$129.95
1200C 1200/300 Baud External Modem. . . \$ 99.95
2400E 2400/1200/300 External Modem. . . \$169.95

TEST EQUIPMENT



Metex M4650:

• Handheld, high accuracy
• 4 1/2 Digit LCD
• Manual ranging with Overload
Protection
• Audible continuity tester
• Tests: AC/DC Voltage,
Resistance, Continuity
Capacitance, Frequency
• One Year Warranty
• Size: 7 1/2 x 3 1/2 x 1 1/4"
M4650 \$99.95

Data Sheets - 50¢ each
Prices Subject to Change

Send \$2.00 Postage for a
FREE 1989 CATALOG

FAX Numbers: 415-592-2503
or 415-595-2664

Telex: 176043

\$20 Minimum Order

IBM is a registered trademark of International Business Machines



1355 Shoreway Road, Belmont, California 94002

24 HOUR ORDER HOTLINE (415) 592-8097 • The Following Phone Lines Are Available From 7AM-5PM P.S.T.:

• Customer Service (415) 592-8121 • Technical Assistance (415) 592-9990 • Credit Department (415) 592-9983 • All Other Inquiries (415) 592-7108

SEND FOR
FREE
1988 CATALOG...
56 PAGES

★ QUALITY PARTS ★ DISCOUNT PRICES ★ FAST SHIPPING
ALL ELECTRONICS CORP.

WE STOCK OVER
4,000 ITEMS...
CALL OR WRITE FOR OUR
FREE
CATALOG OF PARTS!



RESISTORS • CAPACITORS • DIODES • CABLES •
BRIDGE RECTIFIERS • CHOKE COILS • CRYSTALS •
CRIMP CONNECTORS • LAMPS • HEAT SINKS • MO-
TORS • SUB MINIATURE D CONNECTORS • TRANSIS-
TORS • I.C.'S • PROTO BOARDS • POTENTIOMETERS •
POWER SUPPLIES • JACKS • PLUGS • SWITCHES •
PERF BOARDS • FANS • FUSES • SHRINK TUBING • TIE
WRAPS • TOOLS • KEYPADS • VIDEO ACCESSORIES •
RELAYS • S.C.R.'S • TRANSFORMERS • TELEPHONE
ACCESSORIES • RIBBON CABLE • CIRCUIT
BREAKERS • VOLTAGE REGULATORS •
AND MANY OTHER ITEMS....

TRANSISTORS

CATA	TYPE	CASE	PRICE
PN2222	NPN	TO-92	5 for .75
2N2904	PNP	TO-92	3 for \$1.00
2N2906	PNP	TO-18	3 for \$1.00
PN2907	PNP	TO-92	5 for .75
2N3055	NPN	TO-3	\$1.00 each
PN3569	NPN	TO-92	5 for 50
2N3904	NPN	TO-92	5 for 75
2N3906	PNP	TO-92	5 for 75
2N4400	NPN	TO-92	5 for 75
2N4402	PNP	TO-92	5 for 75
2N5400	PNP	TO-92	4 for \$1.00
2N5880	PNP	TO-3	\$2.00 each
2N5882	NPN	TO-3	\$2.00 each
MJ2955	PNP	TO-3	1.50 each
MJE2955T	PNP	TO-220	75 each
MJE3055T	NPN	TO-220	75 each
TIP30	NPN	TO-220	75 each
TIP31	NPN	TO-220	75 each
TIP32	PNP	TO-220	75 each
TIP41	NPN	TO-220	75 each
TIP42	PNP	TO-220	75 each
TIP121	NPN	TO-220	75each
TIP126	PNP	TO-220	75each

**10 AMP
SOLID STATE
RELAYS**



ELECTROL# S2181
CONTROL:
Rated 5.5 to 10 Vdc
will operate on 3-32 Vdc
LOAD:
10 Amp @ 240 Vac
2 1/4" X 1 3/4" X 7/8"
CAT# SRRLY-10B
\$9.50 each
QUANTITY DISCOUNT!
10 for \$85.00
25 for \$175.00
50 for \$300.00
100 for \$500.00

SWITCHES

**MINIATURE TOGGLE
SWITCHES**
all rated 5 Amps

S.P.D.T.(on-on)
Solder lug terminals.
CAT# MTS-4
\$1.00 each
10 for \$9.00



S.P.D.T.(on-on)
Non threaded bushing.
P.C. mount.
CAT# MTS-40PC
75c each
10 for \$7.00



D.P.D.T.(on-on)
Solder lug terminals.
CAT# MTS-8
\$2.00 each
10 for \$19.00



**PIEZO WARNING
DEVICE**

Murata Erie #
PKB8-4A0
High pitched
audible alarm.
Operates on
3 - 20 Vdc @ 20 ma. 1" high
X 7/8" dia. P.C. board mount
CAT# PBZ-84 \$1.75 each



SOUND ACTIVATED BOARD

Designed to react to high pitched sounds. Each
board contains many useful parts
including a condenser mike.
Operates on 6 Vdc.
Instructions included.
CAT# SAB \$2.50 each



24 VOLT D.C. SOLENOID

Intermittent duty cycle. 240 ohm coil.
Mounting flange is 1 1/8" wide.
Solenoid body 1 1/2" X 1/2" X 1/2".
CAT# SOL-34 \$1.00 each • 10 for \$8.50
100 for \$75.00 Large Quantity Available



MINI PUSH BUTTON

S. P. S. T. momentary.
Push to make. 1/4"
threaded bushing.
Red button.
CAT# MPB-1
35c each • 10 for \$3.25



ITT PUSH BUTTON

ITT MDPL series. 3/4" X 1/2"
gray rectangular key cap.
S.P.S.T. N.O. Push to close.
RATED:
0.1amp
switching,
0.25 amp
carry current. P.C. mount
CAT# PB-8 65c each
10 for \$6.00 • 100 for \$50.00




XENON TUBE

1" long flashtube prepped
with 3 1/2" red and black
leads. Ideal for electronic
flash or strobe projects.
CAT# FLT-3 2 for \$1.00



NEW! STROBE KIT

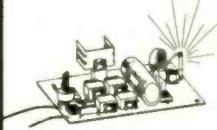Variable rate strobe kit, flash-
es between 60 to 120 times
per minute. Will operate on
either 6 or 12 Vdc depending
upon how you wire the circuit.
Comes complete with P.C.
board and instructions for
easy assembly.
CAT# STROBE-1 \$7.50 each



**SOUND & VIDEO
MODULATOR**

T# UM1381-1.
Designed for use
with T.I. comput-
ers. Can be used
with video cam-
eras, games, or
other audio/
video sources.
Built in A/B
switch enables
user to switch
from T.V. antenna without dis-
connection. Operates on chan-
nel 3 or 4. Requires 12 Vdc.
Hook up diagram included.
CAT# AVMOD \$5.00 each



**GRAB BAGS
\$1.00 EACH**

50 ASSORTED
DISC CAPS.
Cut leads. Many
common values,
some are 500 volts.
CAT# GRABDC
ASSORTED
1/4 WATT
RESISTORS
Approximately 200
pieces of assorted
values, some
cut leads.
CAT# GRES
ASSORTED
PARTS
Strips of 100 assorted
parts. Each strip
contains an assort-
ment of resistors,
capacitors,
diodes, coils,
etc. 100 pieces.
CAT# GRABTR
15 VALUES OF
ELECTROLYTICS
Assortment contains
15 values of 1 mfd and
up. Some cut leads.
CAT# GRABCP

**N-CHANNEL
MOSFET**

IRF-511
TO-220 case
CAT# IRF 511
\$1.00 each
10 for \$9.00
**LARGE QUANTITY
AVAILABLE...**



**HALL EFFECT
SWITCH**

MICROSWITCH #4BE3
Slanted keyboard
switch with hall
effect sensor.
Snaps into 5/8"
square chassis
hole. Hall effect
sensor slides easily from
switch and can be used in
other applications.
CAT# HESW 4 for \$1.00
10 for \$2.00
100 for \$15.00



**10 POSITION
MINI-ROTARY
SWITCH**

Grayhill#
56P36-01-1-10N-C
Miniature,
rotary switch.
Non-shorting.
1 deck, 10 positions.
.125" dia. shaft X
.375" long.
.377" behind the
panel depth.
P.C. pins.
CAT# MRS-10
\$2.50 each



**NICKEL-CAD
(RECHARGEABLE)
BATTERIES**

SPECIAL
AAA SIZE
Panasonic # P-18AAA
1.2 volt @ 180 mAh
CAT# NCB-AAAX
\$1.50 each
10 for \$13.50
100 for \$125.00
LARGE QUANTITIES



AA SIZE \$2.00 each
1.25 Volts 500 mAh
CAT# NCB-AA
AA SIZE \$2.20 each
WITH SOLDER TABS
CAT# NCB-SAA
C SIZE \$4.25 each
1.2 Volts 1200 mAh
CAT# NCB-C
D SIZE \$4.50 each
1.2 Volts 1200 mAh
CAT# NCB-D

**WALL
TRANSFORMERS**

ALL PLUG
DIRECTLY
INTO
120 VAC
OUTLET
6 Vdc @ 200 ma. \$2.25
CAT# DCTX-620
6 Vdc @ 750 ma. \$3.50
CAT# DCTX-675
9 Vdc @ 250 ma. \$2.50
CAT# DCTX-925
12 Vac @ 930 ma. \$3.50
CAT# ACTX-1293
18 Vac @ 1 Amp. \$3.50
CAT# ACTX-1885



**PROTO
BOARD**

Large enough to
design most
experimental circuits.
This proto board
measures
6 3/4" X 2 1/2".
Contains main board
and two power buss
strips.
CAT# PB-101
\$9.00 each



WIDE BAND AMPLIFIER

NEC#UPC1651G
1200 Mhz @ 3 db. Gain: 19db @ 1-500 hz 5 volt
operation. Small package 4mm dia. x 2.5 mm thick.
CAT# UPC-1651 2 for \$1.00
10 for \$4.50 100 for \$35.00



LIGHT EMITTING DIODES (L.E.D.)

STANDARD JUMBO LED
DIFFUSED
T 1-3/4 size
RED 10 for \$1.50
CAT# LED-1 100 for \$13.00
1000 for \$110.00
GREEN 10 for \$2.00
CAT# LED-2 100 for \$17.00
1000 for \$150.00
YELLOW 10 for \$2.00
CAT# LED-3 100 for \$17.00
1000 for \$150.00



FLASHING LED
with built in
flashing circuit.
operates on 5 volts...
RED \$1.00 each
CAT# LED-4 10 for \$9.50
GREEN \$1.00 each
CAT# LED-4G 10 for \$9.50



LED HOLDER
Two piece holder.
CAT# HLED
10 for 65c



**CLIPLITE LED
HOLDER**
Makes a L.E.D. look
like a fancy indicator.
Fits T 1-3/4 size LED.



BI-POLAR LED
Lights RED one
direction, GREEN the
other. Two leads.
CAT# LED-6 2 for \$1.70

CLEAR CAT# HLDCL-C
RED CAT# HLDCL-R
GREEN CAT# HLDCL-G
YELLOW CAT# HLDCL-Y

MAIL ORDERS TO:
ALL ELECTRONICS
P.O. BOX 567
VAN NUYS, CA 91408

TWX-5101010163
(ALL ELECTRONIC)

OUTSIDE THE U.S.A.
SEND \$1.50 POSTAGE
FOR A CATALOG!!

STORES:

LOS ANGELES
905 S. VERMONT AVE.
LOS ANGELES, CA 90008
(213)380-8000

VAN NUYS
8228 SEPULVEDA BLVD.
VAN NUYS, CA 91411
(818)997-1806

**TOLL FREE
800-826-5432**

INFO: (818)904-0524
FAX: (818)781-2653
MINIMUM ORDER \$10.00
QUANTITIES LIMITED
CALIF. ADD SALES TAX
USA: \$3.00 SHIPPING
FOREIGN ORDERS
INCLUDE SUFFICIENT
SHIPPING.
NO C.O.D.



AMAZING SCIENTIFIC & ELECTRONIC PRODUCTS

PLANS

Build Yourself — All Parts Available in Stock

LC7— BURNING CUTTING CO ₂ LASER	\$20.00
RUB4— PORTABLE LASER RAY PISTOL	\$20.00
TCCT— 3 SEPARATE TESLA COIL PLANS TO 1.5 MEV	\$25.00
IOG1— ION RAY GUN	\$10.00
GRA1— GRAVITY GENERATOR	\$10.00
EML1— ELECTRO MAGNET COIL GUN/LAUNCHER	\$8.00

KITS

With All Necessary Plans

MFT3K— FM VOICE TRANSMITTER 3 MI RANGE	\$49.50
VWPM7K— TELEPHONE TRANSMITTER 3 MI RANGE	\$39.50
BTC3K— 250,000 VOLT 10-14" SPARK TESLA COIL	\$249.50
LHC2K— SIMULATED MULTICOLOR LASER	\$44.50
BLS1K— 100,000 WATT BLASTER DEFENSE DEVICE	\$69.50
ITM1K— 100,000 VOLT 20" AFFECTIVE RANGE INTIMIDATOR	\$69.50
PSP4K— TIME VARIANT SHOCK WAVE PISTOL	\$59.50
STATK— ALL NEW SPACE AGE ACTIVE PLASMA SABER	\$24.50
MVPIK— SEE IN DARK KIT	\$199.50
PTG1K— SPECTACULAR PLASMA TORNAADO GENERATOR	\$149.50

ASSEMBLED

With All Necessary Instructions

BTC10— 50,000 VOLT-WORLD'S SMALLEST TESLA COIL	\$54.50
LGU40— 1MW HeNe VISIBLE RED LASER GUN	\$249.50
TAT30— AUTO TELEPHONE RECORDING DEVICE	\$24.50
GVPI0— SEE IN TOTAL DARKNESS IR VIEWER	\$349.50
LST10— SNOOPER PHONE INFINITY TRANSMITTER	\$169.50
IPG70— INVISIBLE PAIN FIELD GENERATOR MULTI MODE	\$74.50

• CATALOG CONTAINING DESCRIPTIONS OF ABOVE PLUS HUNDREDS MORE AVAILABLE FOR \$1.00 OR USE OUR PHONE FOR "ORDERS ONLY" 603-673-4730.

PLEASE INCLUDE \$3.00 PH ON ALL KITS AND PRODUCTS PLANS ARE POSTAGE PAID. SEND CHECK, MO, VISA, MC IN US FUNDS.

INFORMATION UNLIMITED
P.O. BOX 716 DEPT. RE, AMHERST, NH 03031

ADVERTISING INDEX

RADIO-ELECTRONICS does not assume any responsibility for errors that may appear in the index below.

Free Information Number	Page	Free Information Number	Page		
81, 192	A.I.S. Satellite	43	56	Parts Express	106
108	AMC Sales	28	68, 188	Philips ECG	56
—	AMCOM	104	250	Philips ECG	56
199	Ace Communications	96	101	Pomona Electronics	17
189	Active Electronics	116	78	Radio Shack	107
107	All Electronics	120	200	SCO Electronics	22
—	Amazing Concepts	102, 122	185, 186	Sencore	32, CV3
106	American Design Components	114	74	Solid State Sales	105
76	Associated Electronics/3M	22	—	Star Circuits	95
197	Atlantic Cable Distribution	92	83	Synergetics	34
184	Banner Technical Books	95	92	Tektronix	18
85	Blue Star Industries	43	123	Test Probes	18
109	C & S Sales	48	182	The Datak Corporation	92
196	CEI	102	195	United Electronic Supply	16
60	CIE	31, 37	181	WPT Publications	96
54	Chemtronics	95			
—	Command Productions	32			
176	Communications Specialists	96			
58	Cook's Institute	42			
190	Crystek	28			
194	DX Tele Labs	34			
—	Damark International	64			
43	Deco Industries	48			
82	Digi-Key	121			
—	Digital Research Computers	104			
—	Electronics Book Club	7			
121	Fluke Manufacturing	CV2			
—	Fordham Radio	CV4			
198	GEI	94			
—	Grantham College of Engineering	23			
183	HiTech Equipment	90			
86	Heathkit	3			
65	J & W	44			
59	JDR Instruments	5			
113, 177	JDR Microdevices	108, 109			
178, 179	JDR Microdevices	110, 111			
180	JDR Microdevices	112			
114	Jameco	118, 119			
104	Jan Crystals	28			
—	Joseph Electronics	27			
193	Kelvin	94			
—	Lindsay Publications	42			
87	MCM Electronics	113			
53	MD Electronics	122			
93	Mark V. Electronics	117			
—	McGraw Hill Cont. Education Series	41			
61	Microprocessors Untld.	90			
117	Mouser	22			
—	NRI	11			
191	Optoelectronics	15			
—	Pacific Cable	103			
187	PanaVise	60			

Gernsback Publications, Inc.
500-B Bi-County Blvd.
Farmingdale, NY 11735
(516) 293-3000
President: Larry Steckler
Vice President: Cathy Steckler

For Advertising ONLY
516-293-3000
Larry Steckler
publisher
Arlene Fishman
advertising director
Shelli Weinman
advertising associate
Lisa Strassman
credit manager
Christina Estrada
advertising assistant

SALES OFFICES

EAST/SOUTHEAST
Stanley Levitan
Eastern Sales Manager
Radio-Electronics
259-23 57th Avenue
Little Neck, NY 11362
718-428-6037, 516-293-3000

**MIDWEST/Texas/Arkansas/
Okl.**
Ralph Bergen
Midwest Sales Manager
Radio-Electronics
540 Frontage Road—Suite 339
Northfield, IL 60093
312-446-1444

**PACIFIC COAST/ Mountain
States**
Marvin Green
Pacific Sales Manager
Radio-Electronics
5430 Van Nuys Blvd. Suite 316
Van Nuys, CA 91401
1-818-986-2001

CABLE TV DESCRAMBLERS

JERROLD™ Tri-Bi Mode	\$105.00	10 Lot	\$85.00
JERROLD™ SB-3 OR 2	\$89.00		\$65.00
Hamlin MLD-1200	\$99.95		\$62.00
Oak N-12 W/V S	\$99.95		\$62.00
Oak M-35-B W/V S	\$99.00		\$78.00
OAK E-13	\$99.95		\$58.00
Zenith SSA VI	\$185.00		\$145.00
Eagle PD-3	\$120.00		\$85.00
Scientific Atlanta	\$129.95		\$105.00
S.A.-Combo's	CALL		\$Call
Tocom	\$350.00		\$295.00
Oak N-12 W/ Auto	\$140.00		\$105.00
Jerrold Starcom CSV	\$139.95		Call

M.D. ELECTRONICS
WILL MATCH ANY
ADVERTISED PRICE
IN THIS MAGAZINE

*NEW STARGATE 2000 CABLE CONVERTER



1-\$89.00 10-\$69.00 100-Call

Last channel recall-Favorite channel select-
75 channel-Channel scan-Manual fine tune-
One year warranty-surge protection-HRC & Stand-
ard switchable- and much more. **Call Today!**

INFORMATION(402)554-0417

Orders Call Toll Free
1-800-624-1150

M.D. ELECTRONICS
115 NEW YORK MALL
SUITE 133E
OMAHA, NE. 68114



CIRCLE 53 ON FREE INFORMATION CARD

With Just One Probe Hookup You Can Confidently Analyze Any Waveform To 100 MHz, 10 Times Faster, 10 Times More Accurately, Absolutely Error Free, Guaranteed Or Your Money Back ...



**With The SC61 Waveform Analyzer
\$3,295.00 PATENTED**

Promises of increased productivity from other oscilloscopes fade fast when compared to the speed and accuracy of the SC61. Eliminate the confusing menus, cursors and complexity of regular oscilloscopes at the push of a button. Here's what the SC61 does for you:

Analyze Waveforms Easily

- Accurate Waveform Display - 60 MHz Bandwidth (usable To 100 MHz) To Test The Latest Digital Circuits.
- Rock-Solid Sync - ECL Logic Circuits And Differential Amplifiers Give Fiddle Free Operation.
- Four Times The Measuring Range - Measure From 5 mV To 2000 Volts (3000 Volts Protection) For Expanded Signal Handling.

Autotracking™ Digital Readings Analyze The Whole Signal

- Autoranging DC Volts Through Single Probe, Even With AC Coupled.
 - Automatic Peak-To-Peak Volts - Even If Variable Control Is "Out Of Cal".
 - Automatic Frequency Measurements Without Sensitivity Adjustment Or Range Switching.
- CIRCLE 135 ON FREE INFORMATION CARD

Digital Delta Tests Analyze Any Part Of The Signal.

- Delta Peak-To-Peak Volts - Peak-To-Peak Volts Of Any Part Of The Signal.
- Delta Time For Any Time Reading - Including Delay Between Traces
- 1/Delta Time - Frequency Of Part Of The Signal - Finds Sources Of Interference Or Ringing.

Frequency Ratio Test - Tests Multiplier And Divider Circuits

Easy To Use - Human Engineered Controls And Virtually No Graticule Counting Or Calculations

The SC61 is designed to give you the measurements you need fast. We make one claim:

"Try the SC61 on your bench for 30 days. If it doesn't cut your present scope time in half, send it back for a complete refund, no questions asked."

Try the SC61 for 30 days, and discover true troubleshooting speed.

**Call 1-800-843-3338
In Canada Call 1-800-851-8866**

SENCORE

Fordham measures up

Quality • Price • Delivery

Mini-Meters with Maxi-Specs



SCOPE 3 1/2 Digit LCD Meter

- 0.5% Accuracy • DC Voltage • AC Voltage • DC Current • Resistance • Diode Test • Battery Life 300 Hrs. • Overload Protection: DC 500V, AC 350V, ohms 250V DC/AC.

Model DVM-630
Our Price **\$2995**

Zippered carrying case CC-30 \$4.50

NEW! SCOPE 3 1/2 Digit, LCD 8 Function with Transistor Tester

- 0.5% Accuracy • Audible continuity and diode test • 10 Amp measurement • Resistance • DC/AC Voltage.

Model DVM-632
Reg. \$60.00
Our Price **\$4495**

Zippered carrying case CC-30 \$4.50

SCOPE 3 1/2 Digit LCD with Autoranging

- 0.5% Accuracy • Auto/Manual range selection • DC Voltage • AC Voltage • AC Current • DC Current • Resistance.

Model DVM-631
Our Price **\$4995**

Deluxe carrying case CA-92 \$9.95

SCOPE Hand-Held Digital Multimeters

- Overload protection • Auto-decimal LCD readout • Polarity indication • 300 hr. 9V battery life • Low battery indicator.

- 8 Function, 37 ranges including Transistor and Capacitance measurements

Model DVM-636
Our Price **\$6750**



CA-92 Deluxe Padded Case for DVM meters \$9.95
TL-216 Transistor and Capacitance Test Leads \$9.90

- 11 Function, 38 ranges including Logic Level Detector, Audible and Visual Continuity, Capacitance and Conductance measurements

Model DVM-638
Our Price **\$8750**



NEW! SCOPE Frequency Counters

- 8-digit LED • Compact • lightweight • High performance • Automatic range and Hold function • High stability in reference oscillator.

Special

Model FC-7011
100 MHz Our Price **\$14995**

Model FC-7051
550 MHz Our Price **\$19995**



FORDHAM Frequency Counter

- 10 Hz - 150 MHz Range • 7-digit LED display • VHF/HF selection • Gate time 1 sec., 5 sec. • ±1 count accuracy.

Model FC-150
Our Price **\$13990**



NEW FORDHAM Function Generator

- 0.5 Hz - 500 KHz in 6 ranges • Sine, square & triangle wave forms • VCA and VCF inputs • Accuracy ±5% of full scale.

Model FG-202
Our Price **\$14990**



FORDHAM Signal Tracer/Injector

- Easy to operate • VU meter • Two LED mode indicators • 1 KHz test tone • 8 ohm speaker • Test leads.

Model SE-610
Our Price **\$11990**



FORDHAM LCR Bridge Meter

- Fully transistorized • 1 KHz signal generator • Measures resistance • Inductance • High mechanical and electrical stability • Battery operated.

Model LC-340
Our Price **\$14995**



SCOPE Digital Capacitance Meter

- Digital LCD display • LSI-circuit • High accuracy: 100 ppm 0.5% • Broad test range • Fast sampling time • Capacitor discharge protection • Compact, lightweight design • One-hand operation.

Model DCM-602
Our Price **\$5995**



Telephone Orders Now! EVERYDAY INCLUDING SATURDAY Mon. - Fri. 8 a.m. - 6:30 p.m. EST. Sat. & Sun. 9 a.m. - 3 p.m. EST

ASK FOR FREE CATALOG. Money orders, checks accepted. C.O.D.'s require 25% deposit



Fordham

260 Motor Parkway, Hauppauge, NY 11788

Toll Free **800-645-9518**

In NY State 800-832-1446

Service & Shipping Charge Schedule Continental U.S.A.

FOR ORDERS	ADD
\$25-50	\$4.50
\$51-100	\$5.50
\$101-200	\$7.00
\$201-300	\$8.00
\$301-400	\$9.00
\$401-500	\$10.00
\$501-750	\$12.50
\$751-1000	\$15.00
\$1,001-1,250	\$17.50
\$1,251-1,500	\$20.00
\$1,501-2000	\$25.00
\$2,001 and up	\$30.00