

DEVOTED ENTIRELY TO THE


25 CENTS

# RADIO SERVICEMAN

# RADIO

# MAINTENANCE

W. H. Melvin  
R.F.D. #7  
Hillsboro 3, Ohio

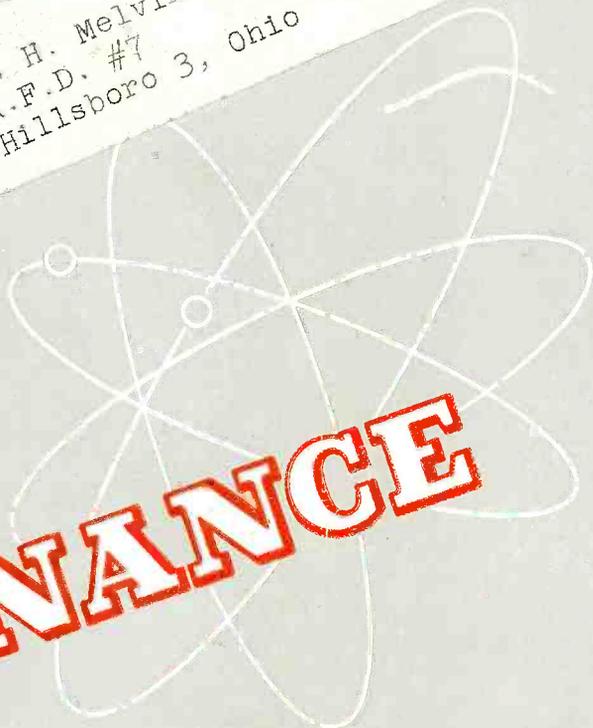

FEBRUARY 1947

SELENIUM RECTIFIERS




THE AUDIO OSCILLATOR

PART IV—THE OSCILLOGRAPH  
HOW TO USE IT

TELEVISION RECEIVERS—  
THE SOUND CHANNEL

A BOLAND AND BOYCE PUBLICATION

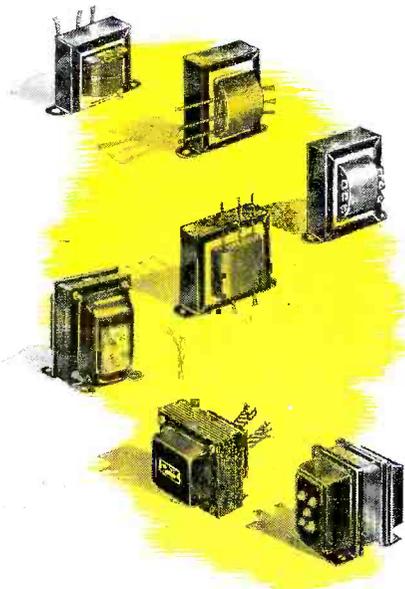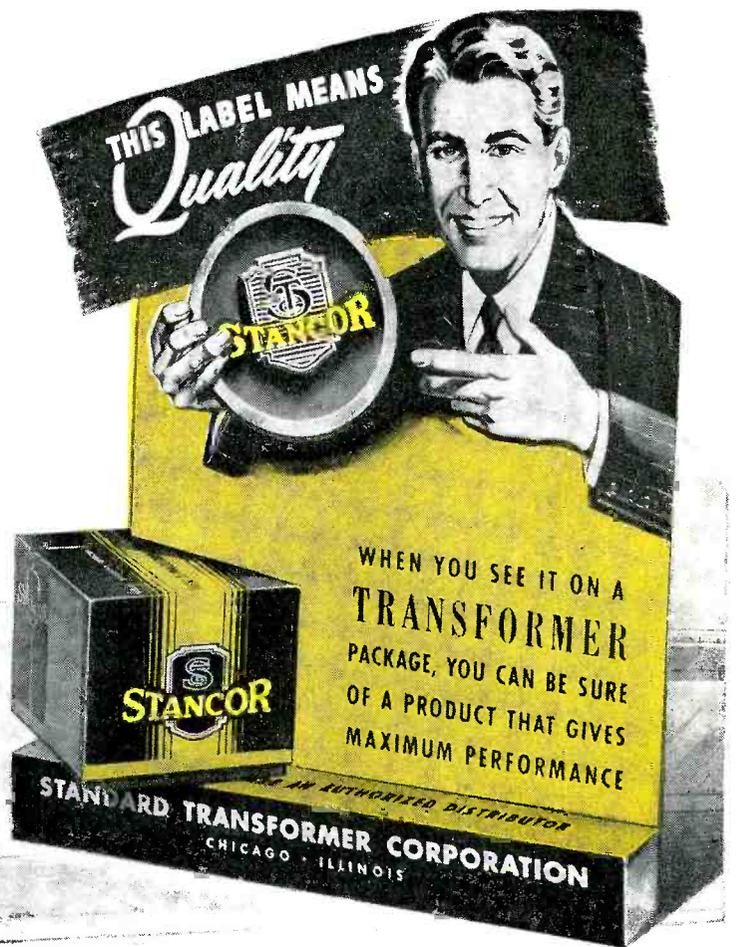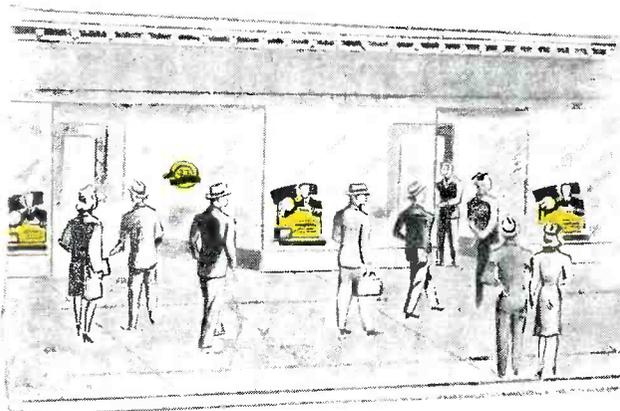where you see the  
name **STANCOR**  
you can count on  
**QUALITY**



STANCOR stands for the highest standard of transformer performance . . . Wherever you see the black-and-yellow STANCOR merchandise display, you know you can rely on the product and the distributor who stands behind it. Yes, STANCOR stands foremost with radio service men . . . for the most complete selection of Replacement and General Purpose Transformers . . . and for advanced designs and universal application . . . Now, STANCOR adds new streamlined plant facilities to serve you better and faster . . . to help you make your service business bigger and more profitable.

standardize on

**STANCOR**



**TRANSFORMERS**



STANDARD TRANSFORMER CORPORATION • CHICAGO, ILL.

# I WILL TRAIN YOU TO START A SPARE TIME OR FULL TIME RADIO SERVICE BUSINESS WITHOUT CAPITAL

**J. E. SMITH,  
PRESIDENT  
National Radio  
Institute**  
33rd Year of  
Training  
Men for  
success in  
Radio
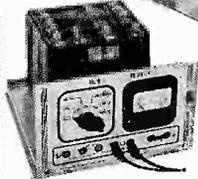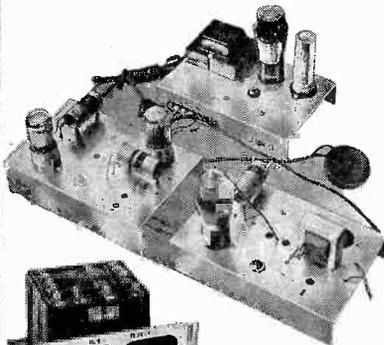
## You Build These and Many Other Radio Circuits with Big Kits of Parts I Supply


By the time you've conducted 60 sets of Experiments with Radio Parts I supply, made hundreds of measurements and adjustments, you'll have valuable PRACTICAL Radio experience for a good full or part-time Radio job!



You build MEASURING INSTRUMENT above early in Course, useful for Radio work to pick up EXTRA spare time money. It is a vacuum tube multimeter, measures A.C., D.C., R.F. volts, D.C. currents, resistance, receiver output.

Building the A. M. SIGNAL GENERATOR at right will give you valuable experience. Provides amplitude-modulated signals for test and experimental purposes.

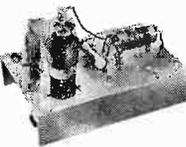You build the SUPERHETERODYNE CIRCUIT above containing a preselector oscillator-mixer-first detector, i.f. stage, diode-detector-a.v.c. stage and audio stage. It will bring in local and distant stations. Get the thrill of learning at home evenings in spare time while you put the set through fascinating tests!



APPROVED  
for training  
under  
G.I. BILL

The men at the right are just a few of many I have trained, at home in their spare time, to be Radio Technicians. They are now operating their own successful spare-time or full-time Radio businesses. Hundreds of other men I trained hold good jobs in practically every branch of Radio. Doesn't this PROVE my "50-50 method" of home training can give you BOTH a thorough knowledge of Radio principles and the PRACTICAL experience you need to help you make more money in the fast-growing Radio industry?

Let me send you facts about opportunities in the busy Radio field. See how knowing Radio can give you security, a prosperous future... lead to jobs coming in Television, Electronics. Send coupon NOW for FREE Sample Lesson and 64-page, illustrated book. Read how NRI trains you at home in spare time. Read how you practice building, testing, repairing Radios with BIG KITS of Radio parts I send you.

### Many Beginners Soon Make Extra Money in Spare Time While Learning

The day you enroll I start sending EXTRA MONEY JOB SHEETS. You LEARN Radio principles from my easy-to-understand, illustrated lessons—PRACTICE what you learn by building, testing and experimenting with parts I send—USE your knowledge to make EXTRA money fixing neighbors' Radios in spare time while still learning! From here it's a short step to your own full-time Radio Shop or a good Radio job!

### Future for Trained Men Is Bright in Radio, Television, Electronics

It's probably easier to get started in Radio now than ever before, because the Radio Repair Business is booming. Trained Radio Technicians also find profitable opportunities in Police, Aviation, Marine Radio, Broadcasting, Radio Manufacturing, Public Address work. Think of even greater opportunities as Television, FM, and many new, war-developed Electronic devices become available to the public! Soon, there will be more Radio equipment to install, operate, maintain and repair than ever before in all history! Get the facts on all these opportunities. Send for FREE books now!

### Find Out What NRI Can Do For You

Mail Coupon for Sample Lesson, "Getting Acquainted with Receiver Servicing," and my FREE 64-page book. It's packed with facts about Radio's opportunities for you. Read the details about my Course. Read letters from men I trained, telling what they are doing, earning. See how quickly, easily you can get started. No obligation! Just MAIL COUPON now in an envelope or paste it on a penny postal.


**J. E. SMITH, President, Dept. 7BY3,  
National Radio Institute  
Pioneer Home Study Radio School,  
Washington 9, D. C.**

### I Trained These Men
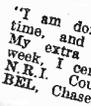
### SPARE TIME RADIO BUSINESS



"I have a spare time Radio and Electrical business of my own which has been very profitable, due to the efficient training I received from your Course. Last year I averaged over \$50 a month."  
—FRED H. GRIFFIE, Route 3, Newville, Pa.



"I am doing radio work in my spare time, and find it a profitable hobby. My extra earnings run about \$10 a week. I certainly am glad I took your N.R.I. Course." —FERDINAND ZIRBEL, Chaseley, North Dakota.



"About six months after I enrolled I started making extra money in radio. I am a farmer and just work on radio evenings and stormy days. That brought me a profit of \$600. In the last year."  
—BENNIE L. ARENDS, RFD 2, Alexander, Iowa.

### I Trained These Men

### FULL TIME RADIO BUSINESS



"Not long ago I was working 16 hours a day in a filling station at \$10 a week. Now I have my own radio business and average over \$60 a week. The N.R.I. course is fine."  
—ALBERT C. CHRISTENSEN, 116 - 10th Avenue, Sidney, Neb.



"Previous to enrolling for your radio hardware store, Now I operate my own repair shop, and often clear \$35 to \$45 a week."  
—FREDERICK BELL, 76 Golf Ave., St. Johns, Newfoundland.



"Am making over \$50 a week profit from my own shop. Have another N.R.I. N.R.I. men because they know radio."  
—NORMAN MILLER, Hebron, Neb.

## SAMPLE LESSON FREE

I will send you a FREE Lesson, "Getting Acquainted with Receiver Servicing," to show you how practical it is to train for Radio at home in spare time. It's a valuable lesson. Study it—keep it—use it—without obligation! Tells how Superheterodyne Circuits work, gives hints on Receiver Servicing, Locating Defects, Repair of Loudspeaker, I. F. Transformer, Gang Tuning, Condenser, etc. 31 illustrations.



**My Radio Course Includes  
TELEVISION • ELECTRONICS  
FREQUENCY MODULATION**

## GOOD FOR BOTH 64 PAGE BOOK SAMPLE LESSON FREE

**J. E. SMITH, President, Dept. 7BY3  
National Radio Institute, Washington 9, D. C.**


Without obligating me, mail your Sample Lesson and 64-page book, FREE. I am particularly interested in the branch of Radio checked below. (No salesman will call. Please write plainly.)

- |                                                                         |                                                              |
|-------------------------------------------------------------------------|--------------------------------------------------------------|
| <input type="checkbox"/> My own Radio Service Business                  | <input type="checkbox"/> Operating Broadcasting Station      |
| <input type="checkbox"/> Spare Time Radio Servicing                     | <input type="checkbox"/> Industrial Electronics              |
| <input type="checkbox"/> Service Technician for Radio Stores or Factory | <input type="checkbox"/> Public Address Systems              |
| <input type="checkbox"/> Aviation Radio                                 | <input type="checkbox"/> Ship, Harbor, Gov't. Military Radio |

(If you have not decided which branch you prefer—mail coupon for facts to help you decide.)

Name ..... Age.....  
Address .....  
City ..... Zone ..... State .....

**Approved for Training Under GI Bill**

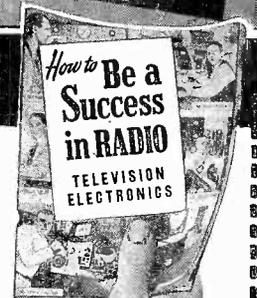

# WHAT SERVICEMAN COULDN'T MAKE MORE MONEY THIS WAY?

The business-like way to make money is to keep plugging ahead at your bench. If your stock is lean and you have to run to the distributor every time you need a volume control, you're frittering away your valuable "bench time" and income. Stock up too high on "special" volume controls and you may wind up behind an inventory 8-ball.

## HERE'S THE RIGHT ANSWER 9 OUT OF 10 TIMES

The sensible solution to your volume control replacements is the IRC *Century Line*. Over 90% (by actual analysis) of all jobs can be taken care of by these 112 types of volume controls. As a matter of fact, you don't even need the entire 112; a selection of only 70 Type D IRC Volume Controls and 11 Tap-In Shafts may handle most of your work. So see your IRC Distributor right away and save your bench time, patience, and money with IRC.

### THE IRC CENTURY LINE

The 112 Volume Controls and 5 Switches That Solve Over 90% of Your Replacement Problems . . . . .

- 70 Universal Type D Controls with 11 easily installed Tap-in Shafts
- 16 Popular Type Controls with Fixed Shafts
- 8 Clutch Type Controls with Fixed Shafts
- 7 Dual Controls with Fixed Shafts
- 9 Controls for Specific Service Used with Fixed Shafts
- 2 Special Controls for Power Requirements with Tap-in Shafts
- 5 Switches




Bring yourself up to date with the new No. 4 Edition of this amazingly popular and useful manual. Contains detailed replacement information on nearly all models up to 1946. Complete listing of 1941-42 models . . . the ones now coming in for repair. 156 pages. 25c at your IRC Distributor.


**INTERNATIONAL RESISTANCE COMPANY**  
401 N. BROAD STREET PHILADELPHIA 8, PA.

Wherever the Circuit says 

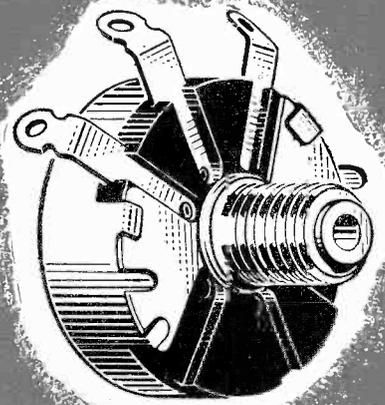In Canada: International Resistance Co., Ltd., Toronto, Licensee



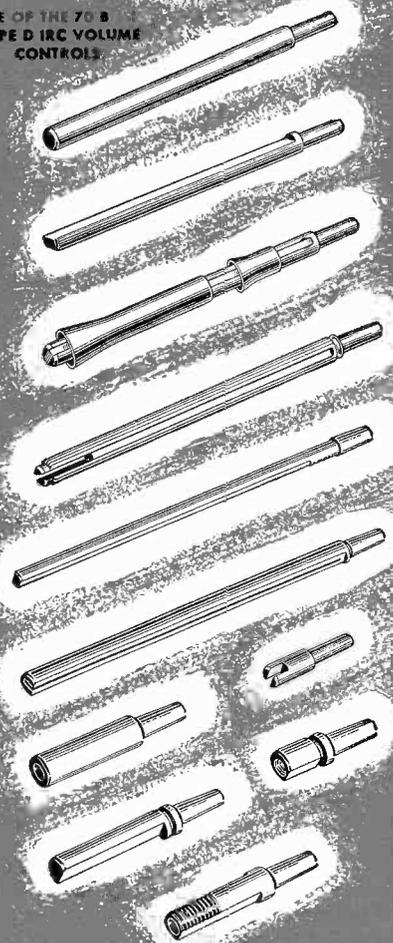ONE OF THE 70 D  
TYPE D IRC VOLUME  
CONTROLS




NOW THE CONVENIENCE OF 11 IRC TAP-IN SHAFTS  
—FOR ALMOST EVERY REPLACEMENT NEED.

# RADIO

# MAINTENANCE

INCLUDING  
ELECTRONIC  
MAINTENANCE

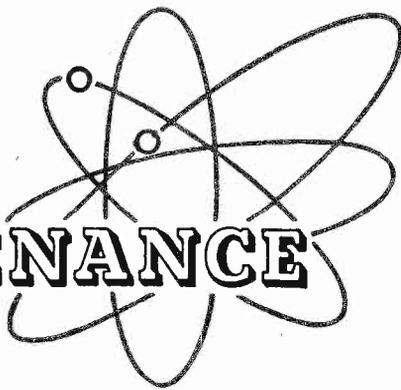

Volume 3

FEBRUARY 1947

Number 2

## Contents

<b>Selenium Rectifiers</b> .....	<b>Monroe M. Lange</b>	<b>6</b>
The theory and application of dry metal rectifiers		
<b>The Audio Oscillator</b> .....	<b>A. R. Knight</b>	<b>10</b>
Phase-shift and Wien Bridge oscillators		
<b>The Oscillograph—How to Use it, Part IV</b> . . .	<b>Karl R. Alberts</b>	<b>14</b>
Receiver Alignment		
<b>The Sound Channel—Television Receivers</b> . .	<b>Morton Scheraga</b>	<b>18</b>
The third section of the television receiver to be discussed		
<b>The Notebook</b> .....		<b>22</b>
Shop suggestions from readers		
<b>Industry Presents</b> .....		<b>24</b>
New products		
<b>Electronically Speaking</b> .....		<b>26</b>
News items		
<b>Over the Bench</b> .....	<b>John T. Frye</b>	<b>27</b>
What a serviceman thinks		
<b>The Patient</b> .....	<b>Don Blair</b>	<b>29</b>
You name it		

**WILLIAM F. BOYCE**  
Publisher

**JOSEPH J. ROCHE**  
Editor

**AL JOHNSTON**  
Jobber Sales

**LOUIS N. SMITH**  
Circulation Manager

**VICTOR M. TURNER**  
Art Director

**THOMAS A. BYRNES**  
Field Service Manager

Midwestern Advertising  
**STUART J. OSTEN**  
307 N. Michigan Ave.  
Chicago, Ill.  
Tel.: Dearborn 3507

**A. J. POLHEMUS**  
Assistant Editor

Eastern Advertising

**FRANK M. SCHMITT**  
460 Bloomfield Ave.  
Montclair, N. J.  
Tel.: Montclair 2-7101

**MORTON SCHERAGA**  
Contributing Editor

Copyright 1947, Boland & Boyce, Inc.

Radio Maintenance is published monthly by Boland & Boyce, Inc., at 34 No. Crystal St., East Stroudsburg, Pa., U.S.A.; Executive and Editorial Office, 460 Bloomfield Ave., Montclair, N. J. Subscription Rates: In U. S., Mexico, South and Central America, and U. S. possessions, \$2.50 for 1 year, \$4.00 for two years, single copies 25 cents; in Canada, \$3.00 for 1 year, \$5.00 for 2 years, single copies 30 cents; in British Empire, \$3.50 for 1 year, \$6.00 for 2 years, single copies 40 cents; all other foreign countries, \$4.00 for 1 year. Entered as Second Class matter Dec. 4, 1946, at Post Office, East Stroudsburg, Pa., under the Act of March 3, 1879.

Change of address: Four weeks' notice required for change of address. When ordering a change, please furnish an address stencil impression from a recent issue if you can. Address changes cannot be made without the old stencil as well as the new one.

*Just  
Out!*

**CONCORD**  
Bargain Catalog of  
**RADIO**  
Equipment  
FOR  
Immediate Shipment



## THOUSANDS OF ITEMS! OUTSTANDING VALUES!

Just off the press—48 exciting pages of radio parts, equipment, and supplies for dealers, servicemen, amateurs, maintenance, testing, building and experimenting—Thousands of items *NOW IN STOCK* and ready for *IMMEDIATE SHIPMENT!* Big feature sections of Radio Sets, Communications Receivers, Amplifiers, Replacement Parts, Ham Gear, Record Players and Portables, Record Changers and complete Sound Systems. Page after page of bargains in top-quality standard-make radio parts and electronic equipment.

### Mail Coupon NOW for FREE COPY

Mail coupon below *TODAY* for your *FREE COPY* of this latest Concord Buying Guide and Bargain Catalog of Radio needs you can order for *SAME DAY SHIPMENT* from complete stocks in Chicago and Atlanta.


# CONCORD

**RADIO CORPORATION**  
**LAFAYETTE RADIO CORPORATION**  
CHICAGO 7, ILL. ATLANTA 3, GA.  
901 W. Jackson Blvd. 265 Peachtree St.

**CONCORD RADIO CORP., Dept. RM27**  
901 W. Jackson Blvd., Chicago 7, Ill.

Yes, rush *FREE COPY* of the new Concord Bargain Catalog.

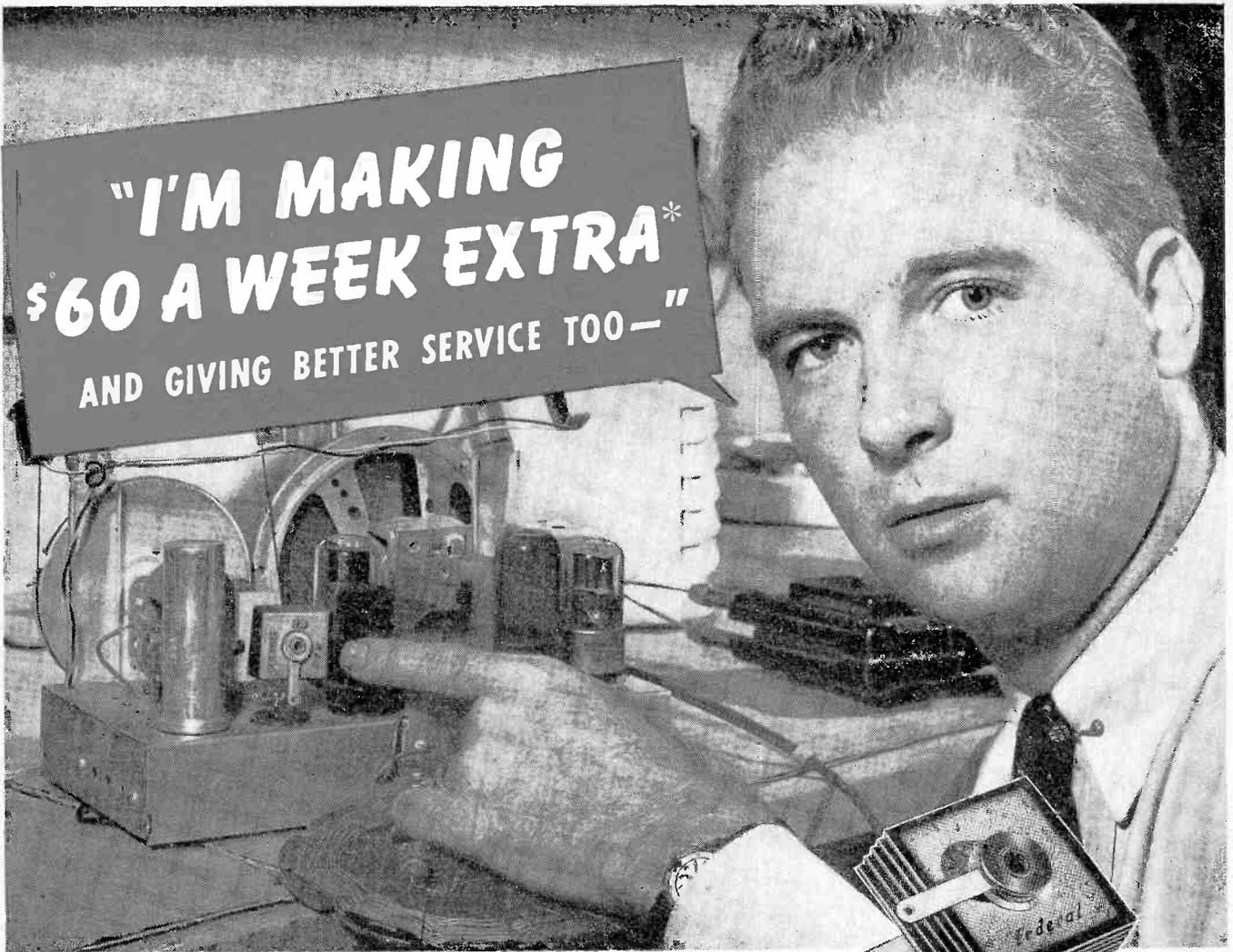Name.....  
Address.....  
City.....State.....



**by Installing Federal's Miniature Selenium Rectifier—in AC-DC home radio receivers to replace rectifier tubes**

HERE'S A REAL OPPORTUNITY for the progressive service man — a chance to make extra money and do a better job. For Federal's new, miniature Selenium Rectifier is more than just a substitute for a tube. It's the modern way to give old sets new performance — gives them instant starting without warmup, makes them run cooler, last longer—replaces 29 different rectifier tube types.

Only 1¼ x 1½ x 5⁄8 inches, it fits anywhere, with just a few simple soldered connections and minimum circuit changes. Once installed, it's in for the life of the set. It withstands overloads from defective electrolytic condensers, and is practically unbreakable.

This miniature Selenium Rectifier gives the same performance that has made Federal "Center-Contact" Selenium Rectifiers the standard of the industry.

**\*HERE'S HOW YOU CAN DO THE SAME**

By installing Federal's Miniature Rectifier in place of a tube, you earn from \$1 to \$2 extra per set serviced. Ten sets a day gives you \$60 a week (or more) added profit.

**Replaces these 29 different rectifier tubes:**

5T4	5Y3	6Y5	25Z6	50Y6
5U4	5Y4	6Z5	35W4	50Z7
5V4	5Z4	12Z5	35Z3	117Z3
5Z3	6X5	7Y4	35Z4	117Z6
5W4	0Z4	12Z3	35Z5	OY4
5X4	80	25Z5	35Z6	

**FREE** — New 8-page Booklet contains 20 circuit diagrams showing how Federal's Miniature Rectifier is being used in various types of electronic equipment. Write to Federal, Dept. R, today, asking for Bulletin F282. And see your nearest radio jobber for a trial order of Federal's Miniature Rectifiers, in 12-unit counter display, with free "How to Install" instruction book, window poster and mailing pieces.



*Federal Telephone and Radio Corporation*

In Canada:—Federal Electric Manufacturing Company, Ltd., Montreal.  
 Export Distributors:—International Standard Electric Corp. 67 Broad St., N.Y.C.



Newark 1,  
 New Jersey

# SPRAGUE TRADING POST

**FOR SALE**—10-watt phone/cw xmitter and superhet receiver, operates 6-12v D.C. complete, \$80. Also have handie talkies, \$5, BC342, S20R and Sky Buddy receivers, all new. Want Meissner signal shifter, W20EA, 712 Bergen Ave., Linden, N. J.

**FOR SALE**—QST's from 1942 to 1947 complete, or will trade all or part. What have you? Fred E. Vaughn, P.O. Box 546, Eugene, Oregon.

**WILL SWAP** German precision multi-tester, graph and instructions; electronic limit bridge for precision measurement with volt-ohm capacity meter with ear-phones. Want communications receiver or factory xmitter or? Borysewich W2GWQ, 1066 President St., Brooklyn 25, N. Y.

**WILL SWAP** Hallcrafters S-41W and Triplett 0-1 m.a. for SX-25 or S20R. Want 600-0-600 volt 200 m.a. 6v. and 5-3 volt transformer for 807. Howard E. Allen, 8 Green St., Brattleboro, Vermont.

**FOR SALE**—Phone/cw xmitter, 6V6, 6V6, 807, class B 6L6 modulator, 40, 20, 10 meter coils. Heavy duty components. Std. 19" panel has enclosed cabinet. \$60. Gordon Walter W3EYX, 1921 Kalamora Rd. N.W., Washington 9, D.C.

**WANTED** — Coto RTVL coil for 10 meters; also Johnson HI-Q variable inductor for 10 meters. Jack Abramowitz, 118 Clara St., Brooklyn 18, N. Y.

**FOR SALE**—Hallcrafters S-22R, new condition, also 8-tube amplifier, factory built. Robert Paxton, 10110 Hereford Place, Silver Spring, Md.

**FOR SALE**—51D8, 51T5 RCA, sealed cartons, at cost. Precision 510H portable tube tester, \$28. 100-watt Solar inverter DC-AC, \$15. Need 3" oscilloscope, cash or trade. Chester T. Martowicz, 116 E. 7 St., New York 3, N. Y.

**FOR SALE**—Supreme #85 tube checker, set of earphones and misc. coils, tubes, resistors and condensers. Write for list. Allen L. Admire, 1343 W. 255 St., Harbor City, Calif.

**WANTED**—McMurdo Silver Masterpiece V or VI. R. Klintworth, P.O. Box 3353, Daytona Beach, Florida.

**WILL TRADE** R.M.E. DB 20 for Meissner P.A. tuner or precision testing equipment. The Radio Laboratory, 912 W. 151st St., East Chicago, Ind.

**WANTED** — Dynamotors operating from 24v D.C. from sets converted to a-c operation. Want one from BC-375-E and one of 500v or less. Guy Black, 1414 E. 59th St., Chicago 37, Ill.

**WANTED** — Old issues of Radio Craft magazine. Cash or trade. What do you need? John Saul, 916 S. Mercer St., New Castle, Pa.

**WANTED** — Late model precision tube tester, v.t.v.m. and signal generator. Harcar Radio Service, R.D. #2, Birdsboro, Pa.

## SWAP - BUY - SELL

**WANTED** — Good spring-wound phono motor with 8" or smaller turntable. Have for sale a good 6v D-C to 110v A-C ATR inverter without vibrator, \$7.50. Donnie Brown, RD2, Jacksonville, Mo.

**WANTED**—Will pay cash for a 25- or 50-watt transmitter covering 10 meter phone. HT9 or HT6 preferred. W. W. Savelle, 108 So. Broadway St., Oklahoma City, Okla.

**FOR SALE**—28v transformer. Can operate surplus equipment. 115v, 200-watt primary, fully shielded, porcelain terminals, \$10 or will swap. J. E. Reidel, 1523-41 St., Brooklyn 18, N. Y.

**FOR SALE**—New Rider's 8 or 12, \$15. Solar Exameter, \$59. Tubes less 50%: 1G6; 1R5; 1S5; 1T4; 5Z3; 5U4; 5Y3; 5Y4; 6B4; 6C8, 6G6; 6H6; 6K7; 12A6; 12SA7; 12SG7; 12SK7; 12SR7; 27; 56. D. Angulo, 5229 Beaufort Ave., Baltimore, Md.

**SWAP**—Have 14-tube overhead recorder, RCP 802-803 tube and set tester, new 110 DC to 110 AC genemotor, UTC amplifier, etc. Want 14" or larger dynamics, Rider manuals, mutual conductance tube tester, etc. D. F. Knight, 1000 S. Glendale Ave., Glendale 5, Calif.

**WANTED**—Power transformer for Philco model 87 and power pack 9-P-6 for Majestic #90. Must be reasonable. M. L. Bridges, 2403 19th Ave., Columbus, Ga.

**NOT A SUBSTITUTE!**



### Replace Wet Electrolytics with SPRAGUE TYPE RW

When replacing wet electrolytic capacitors, use Sprague Type RW. They're not substitutes! They're dry electrolytics of very high voltage formation specifically designed for use as wet replacements or for other difficult applications. Due to their extremely low power factor, lower capacity values give you better filtering. For instance, Type RW-25 rated at 25 mfd. is at least the equivalent of a 40 mfd. wet electrolytic. They'll stand high peak surges. They'll handle a-c ripples—and they fit the standard mounting holes. Ask your jobber for Sprague Type RW.

Write for the complete Sprague Catalog listing Capacitors and \*Koolohm Resistors for every radio service, amateur and experimental need.

Address your ad to: Dept. RM-27

**SPRAGUE PRODUCTS COMPANY**

NORTH ADAMS, MASS.  
JOBBER DISTRIBUTING ORGANIZATION FOR PRODUCTS OF THE SPRAGUE-ELECTRIC CO.

**FOR SALE**—Triplett 1200-E volt-ohm-milliammeter in good working order, \$35. C. A. Kuhns, 3132 Broadway, San Diego 2, Calif.

**FOR SALE**—Stancor 10P transmitter complete with tubes, coil, crystal R9 1874 kc. DC. Milliamperes meter 0-100 movement. Will swap for good tube tester and cash. Franklin LaRue, RFD #3, Ogdensburg, N. Y.

**WANTED**—War surplus wide-band pass radar receiver or video amp. 3 or 4 mc. pass, such as in APS-4 radar. R. B. McGee, CPO Quarters, Ream Field, San Ysidro, Calif.

**WANTED**—U.S. Army handy-talkies SCR-536F. Prefer model F but others might do. Bob Derrick, 707 S. E. 6th Terrace, Gainesville, Fla.

**WANTED**—One 365 mmf. variable condenser; one 2A7 tube, new or used. Cash. Ralph Chrismon, Box 93, Elon College, N. C.

**WANTED**—Television receiver. Have Argus C3 camera and other photo equipment to swap. Jack's Radio Service, 296 Wainwright St., Newark 8, N. J.

**WANTED** — 15-25 watt phone xmitter using 6J5 osc., 6L6 mod., driving 807. Must be in working condition. Frank Crail, Cardwell, Mo.

**WILL TRADE** Hallcrafters S-20R (1938) Sky Champion for S-29. Sky Traveler plus cash difference either way. Give full details of your set and what you want. Wayne Shaw, Route #2, Pattonsburg, Mo.

**WANTED**—One 12B8 tube. F. P. Gifford, Box 246, Aurora, N. Y.

**FOR SALE**—CA10 signal tracer, almost new \$10; Triplett 1200A meter, new. \$15; Solar CB1-60 capacitor analyzer, new, \$15. John T. Hayes, 6000 Washington Ave., Merchantville, N. J.

**FOR SALE**—Supreme Audolyzer, practically new, \$75, or will swap for good moving picture camera. R.C.P. multi-tester R-55, \$23. perfect. Alfred Joltin, 285 Hawthorne St., Brooklyn, N. Y.

**WANTED**—Pair of 10-meter band spread coils for National ACGW3 receiver using type 58 and 27 tubes. Charles F. Stephens, 14 Union St., Randolph, Mass.

**WANTED**—Chassis and speaker for RCA model V-405 or Anniversary model. Either will do. Cash. G. W. Price, 1686 Langston Ave. SW., Atlanta, Georgia.

**FOR SALE** — 1-2 meter xmitter; 2-2 meter trans-receivers; 1-2 meter trans-receiver. Write for details. A. Freitag, 1437 Patapsco St., Baltimore 30, Md.

**WANTED**—Radio service parts, tubes and test equipment. Have Zeiss Ikonta 120, 3.5 lens to trade, also electric welder, complete, 80 amps. Joseph Cuzicka, 924-17 Ave. S.E., Cedar Rapids, Iowa.

**WANTED**—HQ 129X receiver complete No junk. Must be reasonable. Name lowest price. Geo. N. Harleben, 3009 Hurlbut Ave., Detroit 14, Mich.

## YOUR OWN AD RUN HERE FREE!



Sprague will gladly run your own Trading POST ad free of charge in the first available issue of one of the six radio magazines in which this feature appears. WRITE CAREFULLY or print. Hold it to 40 words or less and confine it to radio subjects. Sprague reserves the right to rewrite ads as

necessary, or to reject any that do not in our estimation fit in with the spirit of this service.

*Harry Nathan* Sales Manager

ASK FOR SPRAGUE CAPACITORS AND \*KOOLOHM RESISTORS By Name!

\* Trademark Reg. U. S. Pat. Off.

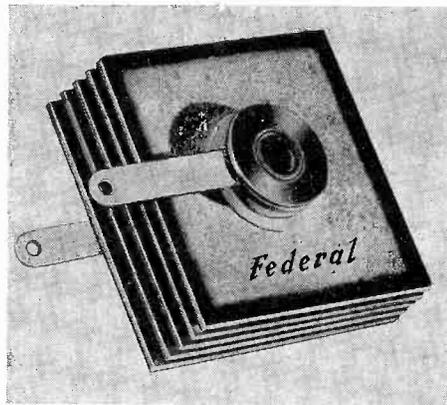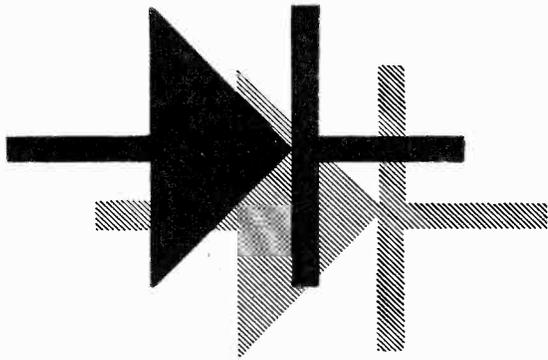

# SELENIUM RECTIFIERS

**The theory and application of the selenium and other dry metal rectifiers. Improvements recently made in these units are resulting in their widespread use.**

**by  
Monroe M. Lange**

**F**OR YEARS, science has known about the asymmetrical resistance properties of two dissimilar substances in close contact. However, it was not until quite recently that the modern home receiver benefited from this knowledge in the form of the selenium rectifier.

The roots of the dry metal rectifier are in the very familiar "cat's whisker" of the crystal set days. Even as far back as 1874, it was known that if a point contact were inserted into a crystal, current passed through the circuit more easily in one direction than in the other. This, of course, is the principle which later made possible the crystal detector.

The first solid rectifiers were of the detector type (low current requirements) and consisted of two separate pieces of unlike metals. Later, in the 1920's, the copper oxide rectifier, as such, was developed by L. O. Grondahl while studying the use of light sensitive cells as relays.

Various types of dry metal or junction rectifiers, as they are sometimes called, such as the copper oxide, magnesium-copper sulphide, and the selenium rectifier, have been utilized in electronics for some time, especially in Europe.

They have been applied to battery charging, DC control circuits (relays, magnets, solenoids), meter rectifiers, filament voltage rectifiers (to supply 6 or 12 volts at 7 amperes), to energize field coils of dynamic speakers, and even as mixer-detectors in low frequency superheterodynes. However, their use was limited by their high initial cost and large space and weight requirements when used for high voltages and currents. The Federal Telephone and Radio Corporation which originally introduced the selenium rectifier in this country in 1935 has overcome these disadvantages in their new miniature selenium rectifier shown in Fig. 1. To appreciate fully the qualities of the rectifier, and before considering its practical applications, it will be interesting as well as beneficial to examine the theoretical aspects of this type of rectifier.

## Application

Any device which conducts current much more easily in one direction than in the other may be used as a rectifier. In other words, if something has a very high resistance one way, and a correspondingly low resistance in the opposite direction, it may be used to change

AC to pulsating DC (see Fig. 2).

There are many such contrivances, all having a common characteristic of unidirectional conductivity. This, as we shall subsequently see, is only one of many factors to take into consideration when choosing a rectifier.

All dry metal rectifiers consist generally of a metal and crystalline metallic salt in close contact. The junction presents a low resistance from the metal to the compound, and a high resistance in the opposite direction. Fig. 3 shows a typical elementary unit of a copper oxide rectifier. The lead contact is the connection to the oxide. The selenium rectifier is formed by coating a metallic disc, such as iron, with a special alloy and selenium. Similar units may be connected in series or parallel so that a wide range of voltages and currents may be obtained. Previous to Federal's miniature rectifier, an increase in current and voltage requirements meant that the unit became prohibitively large. The new rectifiers vary from 1" diameter by 15/16" deep, for 75 ma, to 1 3/4" x 15/16" deep for a 200 ma unit. The disc or plate form aids in keeping the rectifier cool.

The selenium rectifier may be

compared to the ordinary diode with one side corresponding to the plate and the other to the cathode. Fig. 4A and 4B show the symbols of the diode and the dry metal rectifier respectively. It is interesting to note that, when the symbol for the latter was devised, current was thought to flow in the conventional manner from positive to negative. Although we now use the electron theory of direction of current flow, the symbol was never revised.

As previously mentioned, the rectifier must meet other demands beside furnishing the necessary voltage and current. Briefly, they are as follows:

1. Good regulation
2. Durability and ruggedness.
3. Low cost
4. Small size and weight
5. Low heating effects
6. Adaptability

While most of the above are self-evident, point number one perhaps needs further elucidation. A power supply rectifier, just as any other electrical unit, has a certain amount of internal resistance. When current is drawn through a rectifier, an IR drop occurs within it, resulting in a lower available voltage. Referring to Fig. 5, the lower the value of R int., the greater will be the

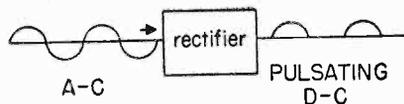


Fig. 2 The input and output voltage wave patterns of a half wave rectifier.

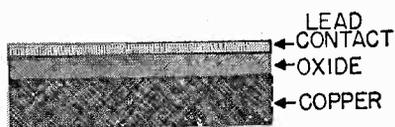


Fig. 3 Cross-sectional view of a simple copper oxide rectifier.

current drawn; and, consequently, the greater will be the internal voltage drop, resulting in a lower Et. By keeping R int. low, good regulation may be obtained. The percentage of regulation is the measure of the amount of voltage available under no load conditions, as compared to full load conditions

$$\left(\% \text{ of regulation} = \frac{E_{nl} - E_{fl}}{E_{fl}} \times 100\right).$$

The lower the percentage, the better the regulation.

Let us see how the selenium rectifier measures up to some of the above qualifications. An examination of the regulation curves shown in Fig. 6A and 6B indicates that the regulation is excellent, even with the voltage doubler circuit

which ordinarily has a poor regulation characteristic.

Since the filament of the rectifier is eliminated, there is little heating effect. This brings up another interesting point: In circuits where the rectifier furnished filament voltage for the rest of the tubes in the circuit, such as AC-DC battery portables, the equipment becomes instant starting as the rectifier filament warm-up time is not required. In applications such as intercommunication systems, this is a distinct advantage. The fact that little heat is generated also means longer life for all the components in the equipment.

One of the most common troubles with transformerless power supplies where there is no line volt-

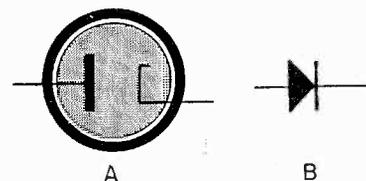


Fig. 4 A is the symbol for a vacuum tube diode, and B is the symbol for a dry metal rectifier.

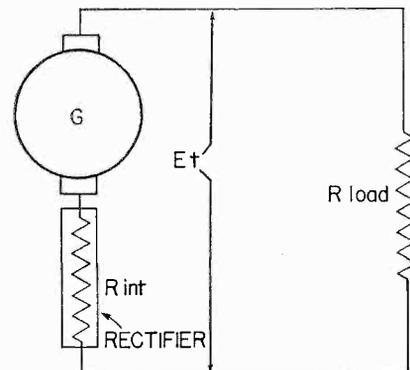


Fig. 5 Simplified diagram illustrating the effect of the rectifier internal resistance on the output voltage.

age dropping resistor for the filaments is the burning out or shorting of tubes and input filter condenser. These failures usually arise due to the high initial current surges while the filaments are still cold and their resistance low. The resistor used to replace the rectifier filament when a selenium rectifier is employed will limit this surge, thus minimizing these difficulties.

As for ruggedness and durability, there is no doubt that the selenium rectifier is tough. The manufacturer states that, based on

→ To Following Page

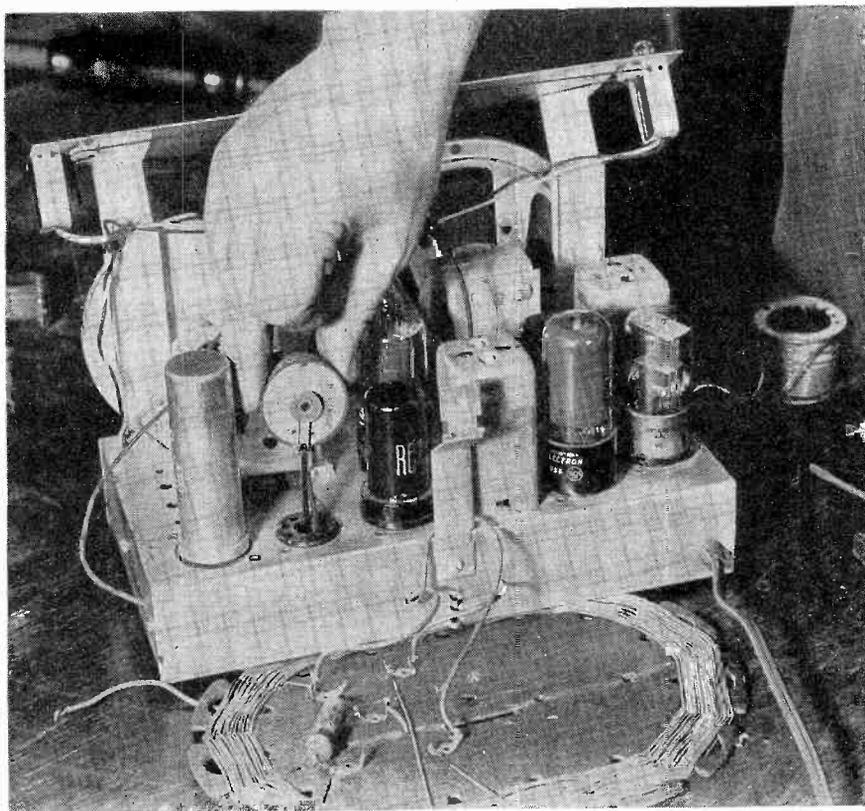


Fig. 1 A selenium rectifier being placed in mounting position above the rectifier socket of a small table model receiver.

# Selenium Rectifiers

→ From Preceding Page

their tests, the selenium rectifier has very long life. As the product is comparatively new, it is too early to make a statement from actual experience in the field. However, the outlook seems very promising.

The selenium rectifier may be

used in various types of power supplies. The most common, of course, is the conventional half wave AC-DC power supply shown in Fig. 9B. If higher voltages are desired, tripler and quadrupler circuits may be employed (Fig. 7A and 7B). Using the 200 ma rectifier and 40

ufd condensers, it is possible to obtain 325 volts at 200 ma with the tripler, and 425 volts at 200 ma with the quadrupler.

## Installation

The important question to the radio serviceman is naturally, "What special benefits can I derive from this new product?" These benefits should take the form of increased

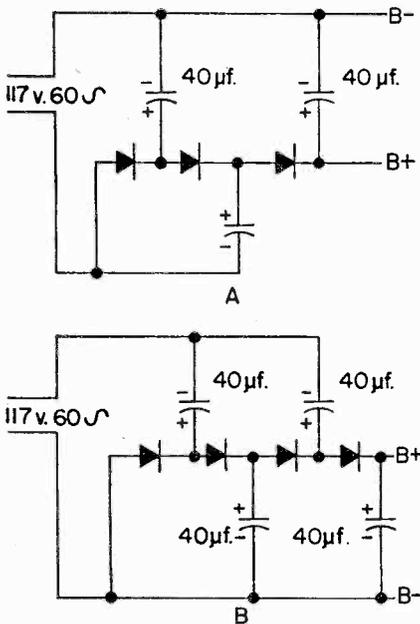


Fig. 7 A is a voltage tripler circuit using three 200 ma selenium rectifier units. B is a voltage quadrupler circuit using four 200 ma selenium rectifier units.

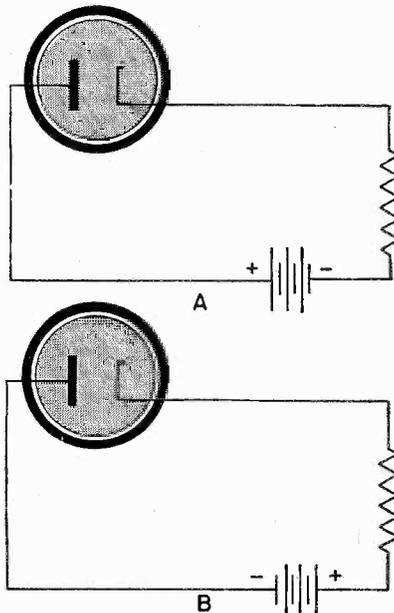


Fig. 8 In circuit A, current will flow through the diode. In circuit B, current will not flow through the diode. C is the effective circuit of an ohmmeter connected across a selenium rectifier. The meter reads 10,000 ohms. When the leads are reversed, as in D, the meter reads 100,000 ohms. The greatest current flow is, therefore, with the connections of C.


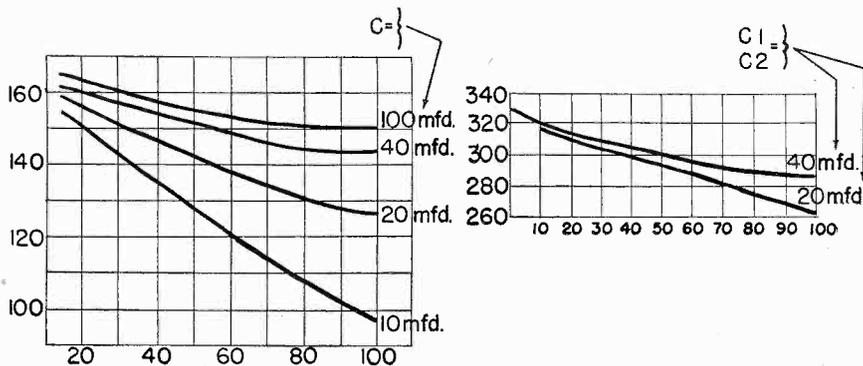


Fig. 6 A shows the voltage regulation curves of a half wave rectifier using a 100 ma miniature selenium unit. B shows the voltage regulation curves of a voltage doubler circuit using two 100 ma units.

profits, greater customer satisfaction, and the reputation of being "in the know" about all the latest developments. It is suggested that some time be spent explaining the advantages of the new rectifier, especially if the customer is new. The fact that the manufacturer guarantees it to last the life of the set should be pointed out.

Installation of the new component is a simple matter. Following are some hints and some typical installation procedures.

There are four Federal selenium rectifiers now available with maximum DC output currents of 75 ma, 100 ma, 150 ma, and 200 ma. By checking the circuit requirements and the tube to be replaced, the proper one is selected. Ordinarily, there is not enough room under the chassis to install it there without interfering with other parts. In case space is available, a cool spot should be chosen. The rectifier may

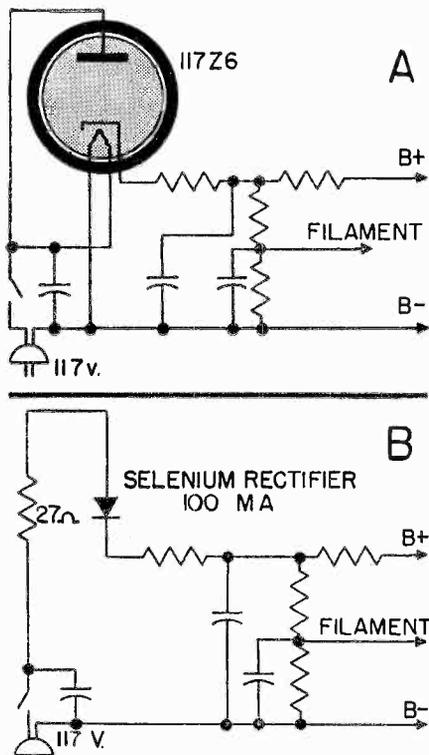

**Fig. 9** A is a typical power supply circuit using a 117Z6. B is the same power supply circuit after conversion to a selenium rectifier unit.


be mounted on the chassis by means of a screw inserted through the eyelet in the center of the unit. It has been found, however, that caution must be observed to prevent shorting the rectifier by applying too much pressure to the screw. An ohmmeter measurement taken between the two leads of the rectifier, after it has been mounted, will provide a check. The usual location for the new unit is over the rectifier tube socket.

While the manufacturer does indicate the polarity to be observed by a yellow and red dot on either end (corresponding to the plate and cathode respectively), it will be worthwhile, both from a theoretical and practical standpoint, for the serviceman to know how to determine the proper connections. A further analogy to the diode will make this obvious.

When the plate of a diode is made positive in respect to the cathode, the diode conducts. Hence, it may be said to have a low resistance (Fig. 8A). Conversely, when the plate is made negative with respect to the cathode, no current flows, in which case the diode represents a high resistance (Fig. 8B).

Keeping this thought in mind, let

→ To Page 28

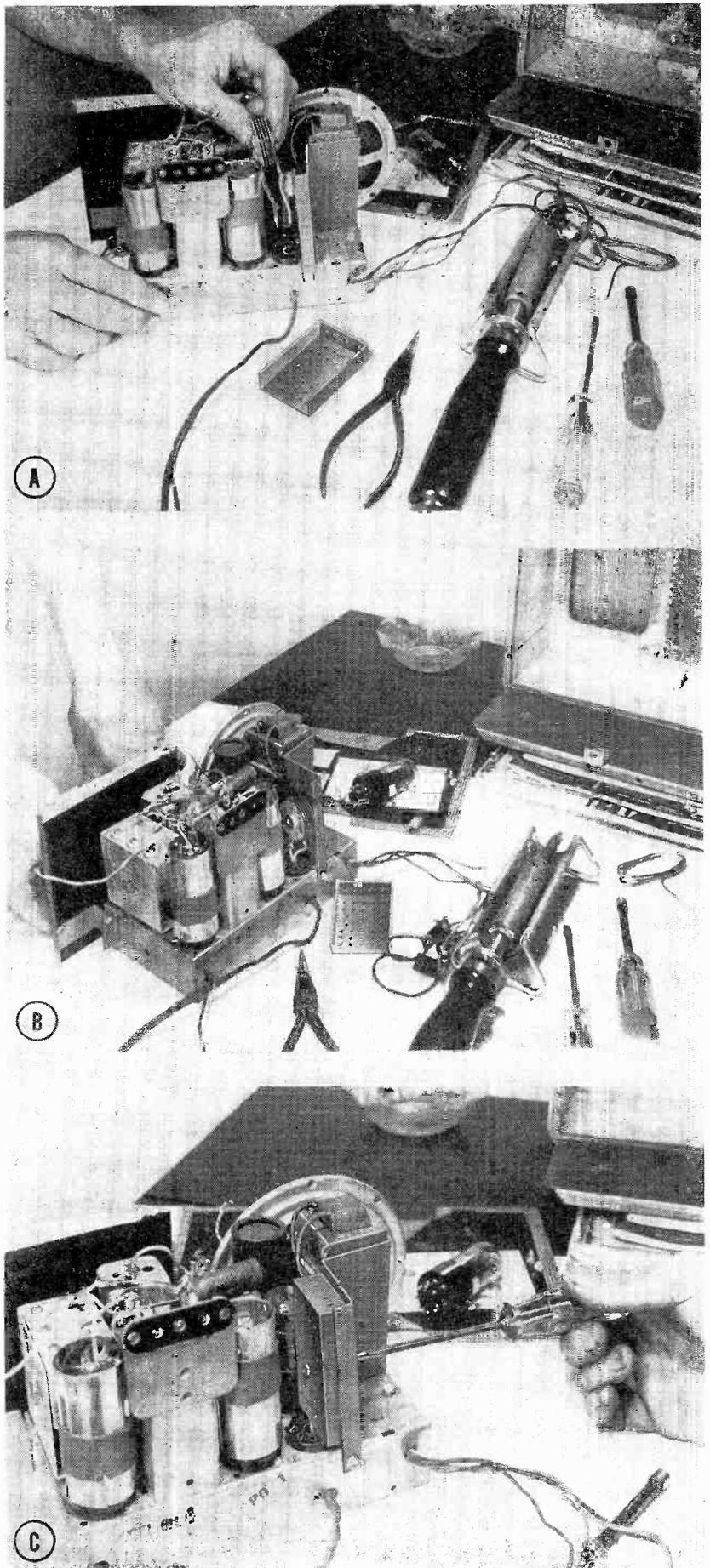

**Fig. 10** Steps followed in installing a selenium rectifier. The unit is mounted above the rectifier tube socket, and a shield is placed over it as illustrated.



# The Audio Oscillator

by A. R. Knight

**A good audio oscillator is a necessary instrument in the small shop. An understanding of the operation of this instrument is helpful in its choice and use.**

**T**HE AUDIO oscillator is an instrument whose function is the generation of sine-wave voltage signals in the audio-frequency range: About 20 cycles to 20,000 cycles. Its use to the radio serviceman is manifold:

1. Checking of response of public address systems;
2. Checking of audio stages in radio receivers;
3. Use as a modulating source for RF and IF signal tracing in a receiver;
4. Analyzing loud-speaker and transformer performance;
5. Measurement of frequency of an unknown signal, with the aid of the cathode-ray oscilloscope (See September issue, "Cathode-Ray Oscillograph . . . How It Works," section on Lissajous figures).

It is proposed in this article to discuss in some detail the theory of most types of audio oscillators. The Jackson Model 655 is illustrated above as a typical example of this type of instrument.

## General Theory of the Audio Oscillator

An audio oscillator is generally a resistance-capacitance (R-C) device with resistance tuning. Inductance-capacitance (L-C) oscillators are not employed because of the high values of components necessary at audio frequencies. For example, at 1000 cycles, a tank circuit of an L-C oscillator would have values of, say,

$$L = 250 \text{ mh, } C = .1 \text{ ufd}$$

(These values come about from the

$$\text{relationship } f = \frac{1}{2\pi\sqrt{LC}}.)$$

It is extremely difficult to arrange an inductance for continuous variation, and it is just as impractical to vary capacitance when it is of the order of .1 ufd.

Since it is just as simple to obtain a potentiometer of high value as of low value, resistance-capacitance oscillators with resistance as the variable element are usually the rule in

audio oscillators. No tank circuit of inductance and capacitance is used to control the frequency of oscillation.

There are two types of audio oscillators which are most widely known and used: The Phase-Shift Oscillator and the "Wien Bridge" Oscillator.

## The Phase-Shift Oscillator

This is the simpler of the two types and hence will be described first. It consists of one tube plus a resistance-capacitance network. To obtain oscillations with a single tube, it is necessary that positive feedback between the plate and grid be maintained; in other words, that a signal be fed back from the plate *in phase* with the signal on the grid. Now it is well known that an ordinary amplifier tube (for example, a triode) produces a voltage at the plate which is an amplified version of the grid signal voltage but 180° out of phase with it. This can be simply shown by Fig. 2. An amplified version of  $e_g$  (the grid signal voltage) appears on the plate

( $e_p$ ) but is  $180^\circ$  out of phase with  $e_g$ , from Fig. 2,

$$e_p = E_{(B_+)} - Ri$$

The plate current ( $i_p$ ) varies directly with the grid voltage ( $e_g$ ). As the grid voltage increases, the plate current increases; as the grid voltage decreases, the plate current decreases. Therefore, effectively, the plate voltage ( $e_p$ ) varies opposite to the grid voltage, or the plate voltage is  $180^\circ$  out of phase with the grid voltage.

In order for a single-tube amplifier to be used as an oscillator, the plate voltage must be so altered that it is in phase with the grid voltage; that is, the plate voltage must be shifted  $180^\circ$  in phase to bring it back into phase with the grid voltage. This is accomplished with three or more sections of resistance-capacitance phase-shifting networks. In Fig. 4 is shown a phase-shift oscillator with three of these networks. Consider first Section 1 alone as a series R-C circuit. If a sine-wave AC voltage  $e_p$  is applied across  $C_1$  and  $R_1$ , a current  $i_1$  will flow through  $C_1$  and  $R_1$ . This current will lead the applied voltage in phase because of the general property of a condenser which causes the current through it to lead the voltage in phase. This same current, flowing through  $R_1$ , will then create a voltage  $e_2$  which leads the applied voltage  $e_p$  in phase. Suppose  $C_1$  and  $R_1$  are adjusted so that this leading phase angle is  $60^\circ$ . If this voltage  $e_2$  is then applied to section 2, as shown in Fig. 4, a similar action will take place and a new voltage  $e_3$  which is  $120^\circ$  out of phase with  $e_p$  will result. By adding a third section, the voltage resulting ( $e_4$ ) will be  $180^\circ$  out of phase with the voltage at the input. We have thus produced a condition in which the grid voltage ( $e_g$ ) is made to lead the plate voltage ( $e_p$ ) by  $180^\circ$  in phase. This completely cancels the  $180^\circ$  by which the plate voltage lags the grid voltage by normal triode action explained above.

Of course, it might be argued, "Why not limit the number of R-C sections to two or even one?" The answer is that the maximum phase shift that can be obtained with an R-C circuit is  $90^\circ$ . This would mean a minimum of two sections. Since  $90^\circ$  is obtainable only when the resistance is made equal to zero, and since making the resistance zero would also make the voltage output from that section zero, more than two sections must be employed. A minimum of three must be used. If four sections were used, each could be adjusted to have a phase shift of  $45^\circ$ . It is not necessary for each section to have the same phase shift as the others. For example, in Fig. 4, sections 1 and 2 could be made

to have phase shifts of  $70^\circ$  each and section 3 a phase shift of  $40^\circ$ , making this last section the fine-tuning control element.

Oscillator action is as follows: Assume the tube initially to be at rest with only DC voltages on grid and plate. The tube is now in a condition of unstable equilibrium. If some slight electronic disturbance occurs (e.g., tube "noise," ripple in the B+ plate supply, etc.), it is amplified, shifted  $-180^\circ$  at the plate, passed through the R-C networks 1, 2, and 3, and returned to the grid to meet more of the original disturbance. The returned signal is then re-amplified

and the entire process repeated. This occurs again and again until no further amplification occurs because of saturation of plate current. The original signal can be considered to consist of a whole band of frequencies. However, only one frequency will be shifted exactly  $180^\circ$  by the three R-C networks and consequently only that frequency will be exactly in phase with the original signal on the grid.

All other frequencies, even those nearby, are rejected because they will be shifted by amounts other than  $180^\circ$  through the R-C networks and

→ To Following Page

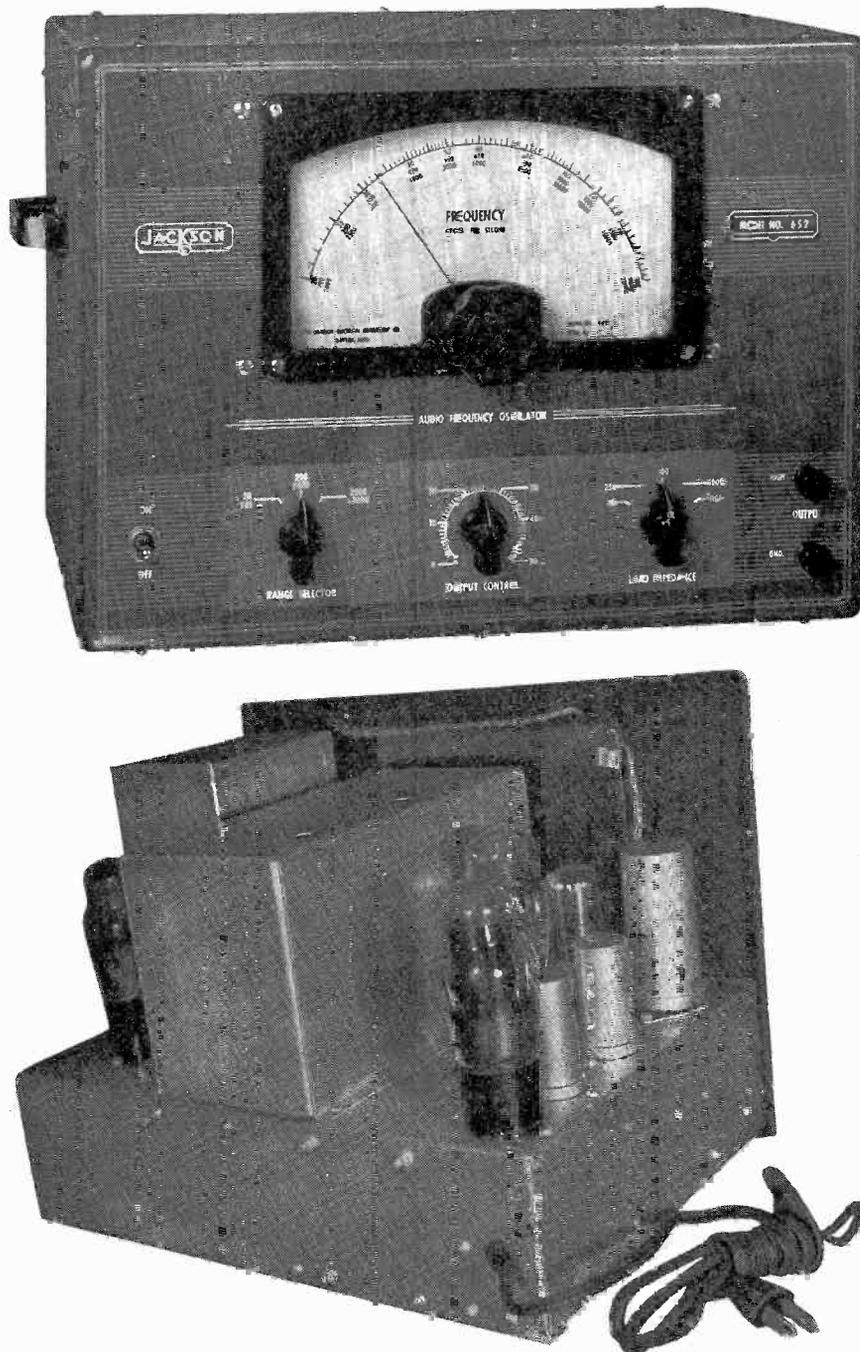


Fig. 1 The Jackson Audio Oscillator Model 652. This is an example of a well designed Wien bridge audio oscillator. Note the conveniently arranged controls and good internal construction.

# The Audio Oscillator

→ From Preceding Page

hence will arrive at the grid out of phase with the original grid signal by amounts depending on how far off-frequency they were. Each time these off-resonance frequencies are passed through the R-C networks, they are shifted farther and farther away from 180° and, consequently, in an exceedingly short time, they are completely rejected.

The output voltage from a phase-shift oscillator of this type is a nearly pure sine wave when the bias on the grid is adjusted to a correct value. The output frequency remains constant for given values for  $R_1$ ,  $C_1$ ,  $R_2$ ,  $C_2$ ,  $R_3$ , and  $C_3$ . To increase frequency, decrease any of the resistances or capacitances. To decrease frequency, increase any of the resistances or capacitances. Usually the capacitances are switched to obtain different frequency bands, and the resistances are potentiometers used as fine frequency controls.

## The Wien Bridge Oscillator

Essentially the same problem is solved by the Wien Bridge oscillator as by the phase-shift oscillator: That of producing, at a particular frequency, a 180° phase shift to cancel out the 180° phase shift produced by the amplifier tube. In this case, a second tube is used to produce an additional 180° phase shift which, added to the 180° produced in the first tube, equals 360° which, of course, is the same as 0°. The Wien Bridge is interposed in the feedback path between the second and first tubes. Its function is to cancel out all unwanted frequencies by shifting their phase further (either + or -) thus permitting only the oscillation frequency to go through without any further phase shift, and to attenuate unwanted frequencies so that their rejection is facilitated.

To examine the oscillator in greater detail, consider Fig. 5. Tubes  $V_1$  and  $V_2$  are both amplifiers, with  $V_2$  output fed back to  $V_1$  grid. Thus the two tubes, as shown above, are capable of acting as an oscillator without additional circuits. However, they would oscillate over a wide range of frequencies (the band-widths of the two amplifiers) and hence some additional apparatus is necessary to limit the oscillations to one frequency. This is the function of the Wien Bridge, shown enclosed in Fig. 5.

As in the case of the phase-shift oscillator, the signal voltages on the grid and plate of the tube  $V_1$  must

be made in phase with each other. This condition is satisfied by the two tubes for a wide range of frequencies; each tube shifts the signal 180°, resulting in a net zero shift. The Wien Bridge allows only one frequency out of this band to be effective because it provides (1) degeneration (negative feedback) and (2) phase shift for all extraneous frequencies. A part of the output of  $V_2$  is also fed back to the cathode of  $V_1$  through the voltage divider consisting of  $R_3$  and the lamp. This feedback voltage is *negative* feedback because its effect is to introduce a voltage 180° out of phase with that on the grid. (The cathode and grid of an amplifier tube are 180° out of phase with each other and a signal introduced into the cathode will be out of phase with a signal put on the grid.) All frequencies are given

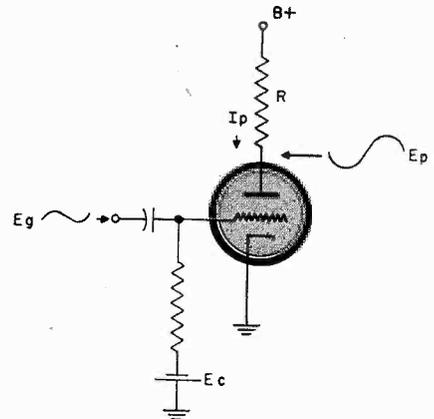


Fig. 2 The plate voltage variation is an amplified version of the signal fed to the grid.

the same amount of negative feedback by  $R_3$  and the lamp.

Function 1 of the Wien Bridge listed above provides that all fre-

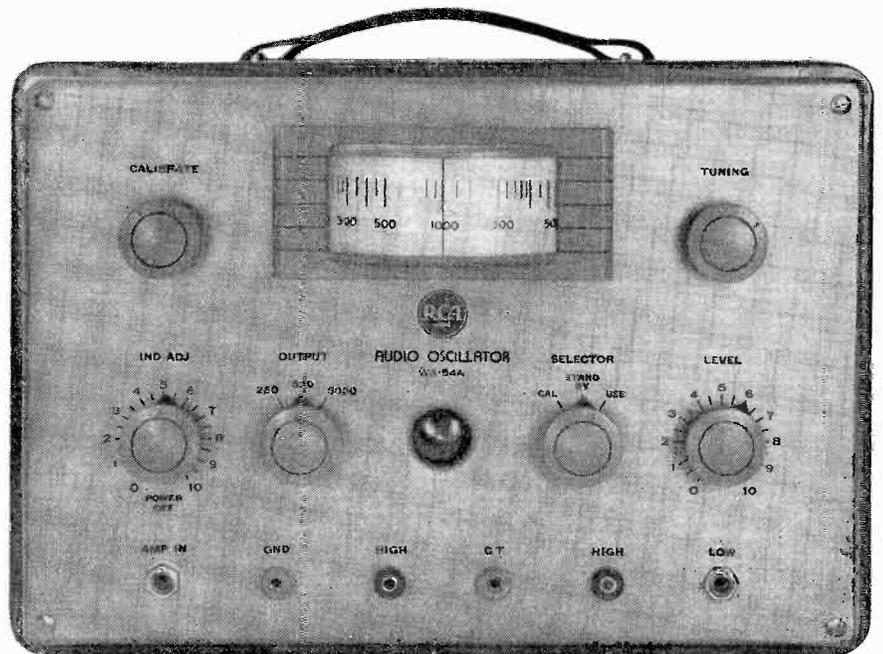
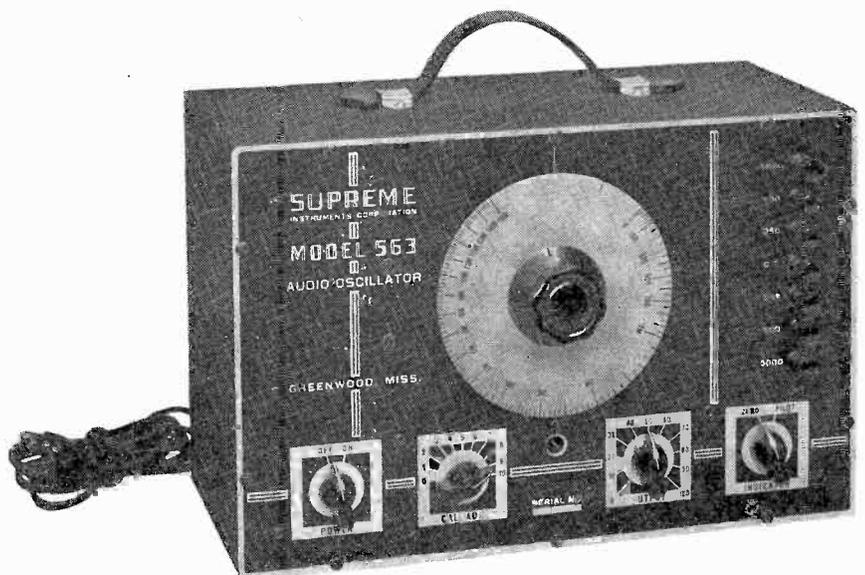


Fig. 3 Two examples of commercially constructed audio oscillators, the Supreme model 563 and the RCA model WA-54A

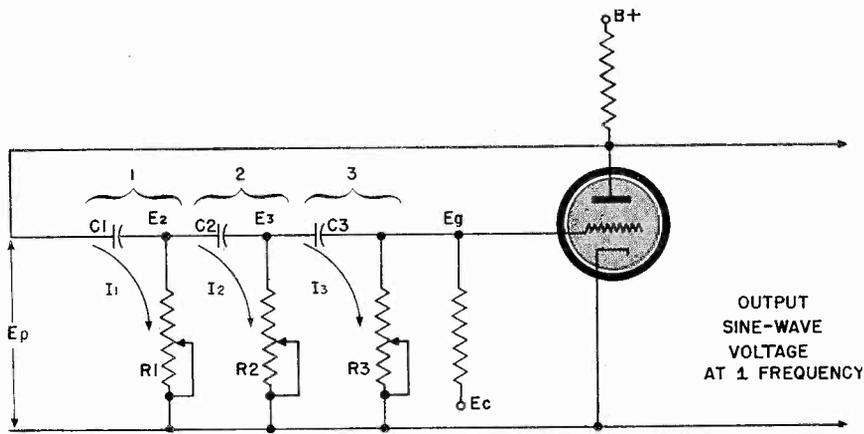


Fig. 4 A simplified schematic of the phase shifting network used in a phase-shift oscillator.

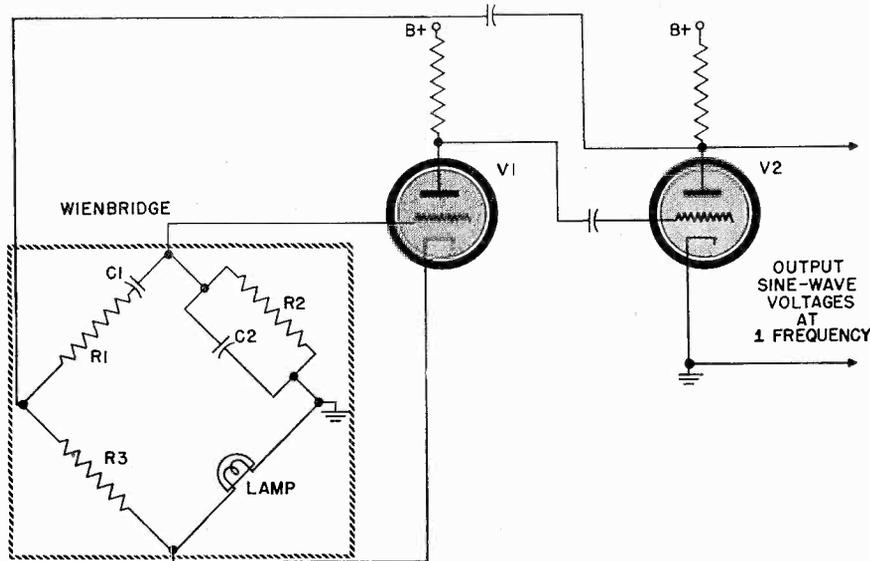


Fig. 5 A simplified schematic of a Wien bridge audio oscillator.

quencies other than those in the vicinity of the frequency of oscillation will be attenuated sufficiently so that the positive feedback from the plate of  $V_2$  to the grid of  $V_1$  is less than the negative feedback from the plate of  $V_2$  to the cathode of  $V_1$ . These frequencies will then not be amplified further in  $V_1$  and will thus be rejected. This attenuation of unwanted frequencies in the Wien Bridge comes about in the following manner: If the frequency is too low, the reactance (AC resistance) of  $C_1$  becomes so high that little of the  $V_2$  plate feedback voltage gets to the grid of  $V_1$ , and the grid voltage of  $V_1$  is brought close to zero. If the frequency is too high,  $C_1$  and  $C_2$  have negligible reactances and hence  $R_2$  is shunted by a low AC resistance, bringing the grid voltage of  $V_1$  close to zero.

At some frequency between these "too high" and "too low" frequencies, the voltage which gets to the grid of  $V_1$  is a maximum. Thus, frequencies other than those in a narrow band immediately around the center desired frequency are rejected. This action of the Wien Bridge is a broad one. Function 2 eliminates all the close frequencies and permits only the desired center frequency to pass.

Function 2, as noted above, is the characteristic of the Wien Bridge by which it acts as a phase-shifting device. From the theory of the Wien Bridge, it is proved that the voltage across the two branches  $R_3 + \text{lamp}$  is in phase with the voltage across  $R_2$  when  $R_1C_1 = R_2C_2$ . But the voltage across  $R_3 + \text{lamp}$  is the output voltage of  $V_2$ , and the voltage across  $R_2$  is the input voltage to the grid

→ To Page 37

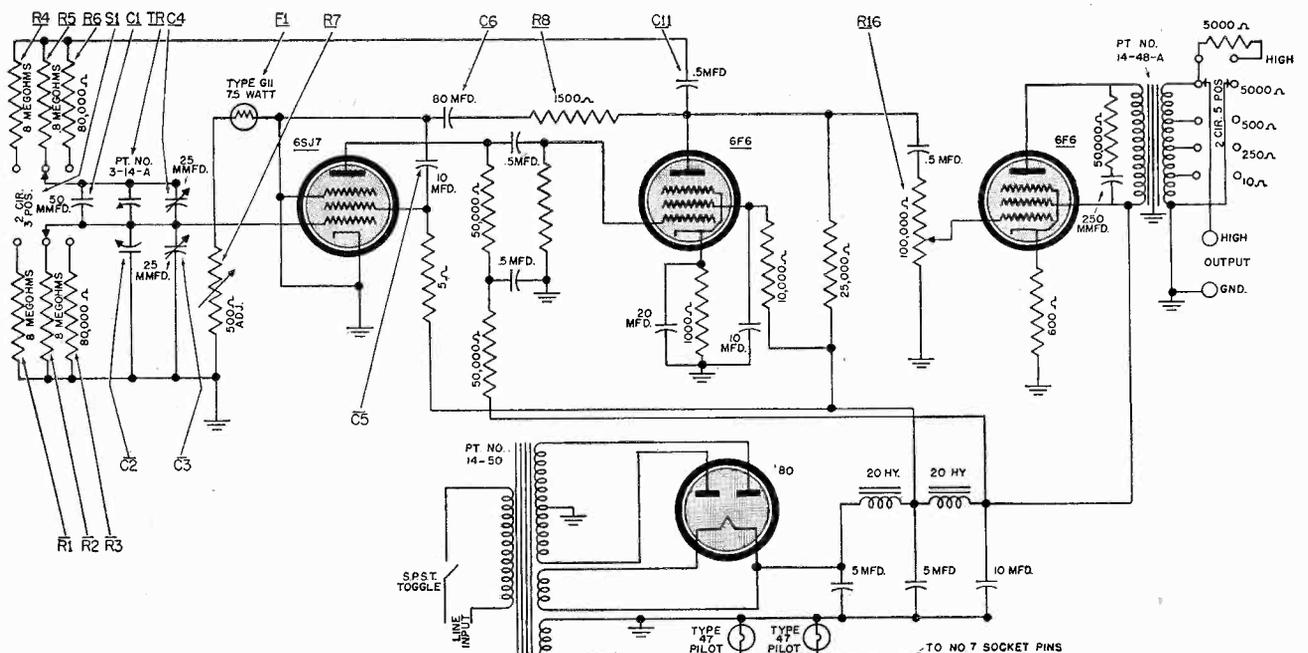


Fig. 6 A complete Wien bridge type audio oscillator.

This is the concluding article of a series on the use of the oscillograph. It covers the alignment of receivers, using the oscillograph and a frequency swept generator.

part IV

# the Oscillograph...how to use it.

by Karl R. Alberts

A BRIEF NOTE OF REVIEW may be profitable here before proceeding with this last article in the series of six on the cathode-ray oscilloscope. The last article dealt with means for detecting distortion in the IF and RF stages of a typical receiver. This distortion was of the form called *amplitude distortion* which comes about through overloading somewhere in the amplifier.

A second form of distortion is called *frequency distortion* which is in the term given to incorrect functioning of the amplifier when its band-pass characteristic is not what it should be when the amplifier is working normally. An intermediate-frequency amplifier has as its ideal characteristic a peaked curve which may be of the shape of any one of the curves of Fig. 1. For each one, the center (or "peak") frequency occurs at the nominal intermediate frequency of the amplifier. Deviations in the shape of this curve, or in the position of the peak along the frequency axis, represent frequency distortion in an IF amplifier.

There are three general types of coupling between stages of an IF amplifier: Single-tuned coil (coil between plate and succeeding grid circuits, tuned by trimmer condenser across coil, or slug through coil); single tuned transformer (secondary tuned); double-tuned transformer (primary and secondary tuned). Representative

curves for all three types are shown in Fig. 1.

## Alignment of the IF Amplifier

Alignment consists of adjusting the variable tuning and trimming condensers, or the metal slugs in coils using inductance tuning, until the proper band-pass frequency curve is obtained. When working on the IF stages, it is most convenient to have a continuous picture of the intermediate-frequency output (i. e., a curve of voltage output against frequency of signal input) while adjustments are being made. How can such a set-up be most expeditiously obtained so as to be most


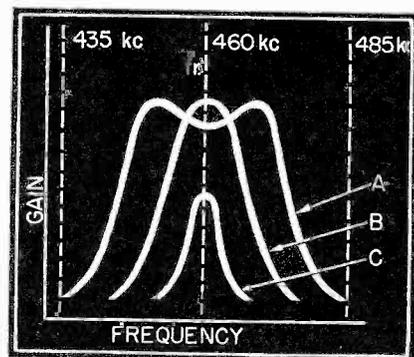


Fig. 1 Intermediate frequency curves with various degrees and types of transformer coupling. A is for double tuned transformer coupling when overcoupled. B is double tuned transformer coupling at critical coupling. Single tuned coil or single tuned transformer coupling gives a similar curve. C is the curve for double tuned transformer coupling when undercoupled.

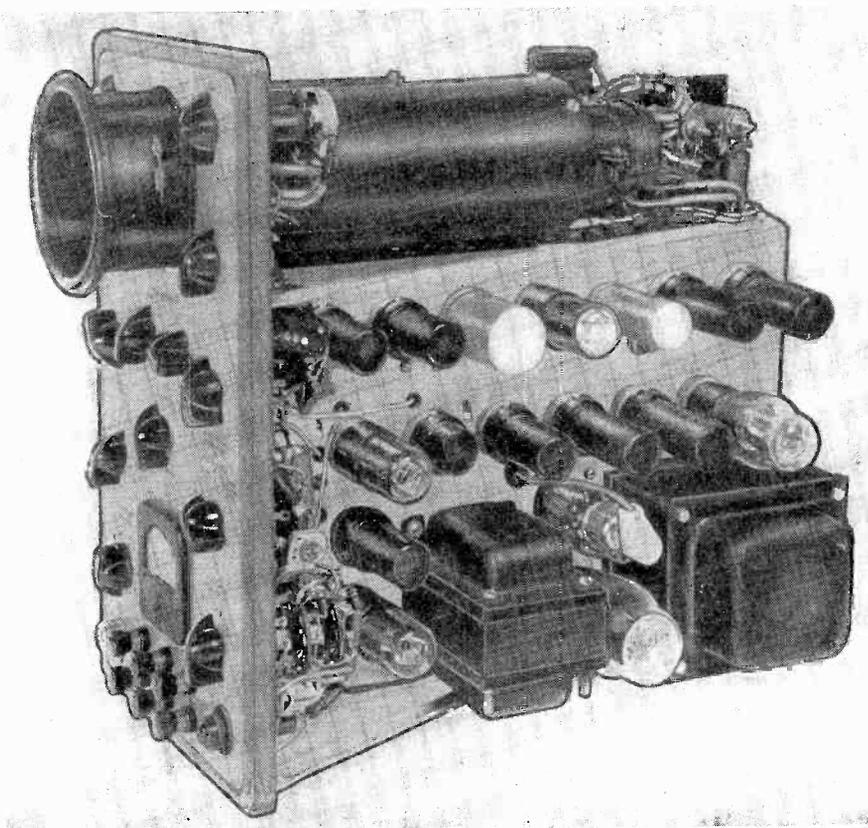

**The internal construction of the new oscilloscope shown in the lower right hand corner of the page. This 'scope is characterized by a wide frequency range and high gain.**

conveniently observable by the operator, and yet involve a minimum of complexity of apparatus so that the serviceman need not make an abnormally large fixed investment in equipment and saddle himself with burdensome circuits? The author has given the problem considerable thought before setting out to write this section, and has carefully reviewed all well known methods. The equipment and methods described below all require some special apparatus, but they more than repay the serviceman in convenience of testing and excellence of results obtainable. In other words, it is felt that the special apparatus specified, by the very fact that it will enable more sets to be checked competently and correctly in a given time, will be well worth the radio repairman's initial investment.

It is possible, of course, to check an IF amplifier by observing the amplitude of a straight vertical line on the oscilloscope as the input frequency to the amplifier is varied over the entire range. This was a practicable method for audio because in general an audio curve is a straight line over most of its range, and it is only necessary to

note where the curve slopes off to half-value on the low and high ends of the band. An IF band-pass curve, on the other hand, is a more complicated affair. To apply the foregoing method to the alignment of the IF would require hours of "diddling," consisting of alternate adjustments of the trimmers and running through the band-pass curve, the whole process repeated over and over until the desired curve appeared. With early broadcast receivers, it was possible to align by using the broadcast stations as signal sources, and the ear as an output indicator. This method is a poor one for several reasons:

(1) It is possible to tune the trimmers for maximum audio output and still have frequency distortion remaining somewhere in the receiver, distortion which would later be most evident when a high fidelity musical program was being broadcast;

(2) The audio modulation from a broadcast transmitter is not always absolutely constant over a long period of time;


(3) The response of the ear is not linear, i. e., a doubling in audio volume does not manifest itself as

a sound "twice" as loud in the ears; the minimum volume change which the ear can discern is about 20 per cent in voltage, which is a serious limitation on its use as an output indicator.

A far more practical and speedy method, whereby the results of tuning are instantly shown on the oscilloscope, is to be described here. Fig. 1 shows typical IF band-pass curves. The vertical parameter is voltage plotted against the horizontal frequency. If the IF output curve can be kept before the eye of the serviceman continuously as he tunes and adjusts, until the desired curve (like those of Fig. 1) is obtained, the whole process can take but a few minutes, and a greater degree of accuracy will have been achieved.

In order to maintain a picture of the band-pass of the amplifier constantly on the screen of the oscilloscope, some means of "sweeping" the input frequency to the amplifier must be obtained, and then the horizontal sweep voltage of the oscilloscope must be made coincident and synchronous with the sweep-frequency input to the amplifier under test. The curve traced on the oscilloscope screen will then be one of voltage plotted against frequency effectively. (Note that this interpretation of the oscilloscope screen pattern must be borne in mind clearly, for it represents a departure from our standard concept of

→ To Following Page

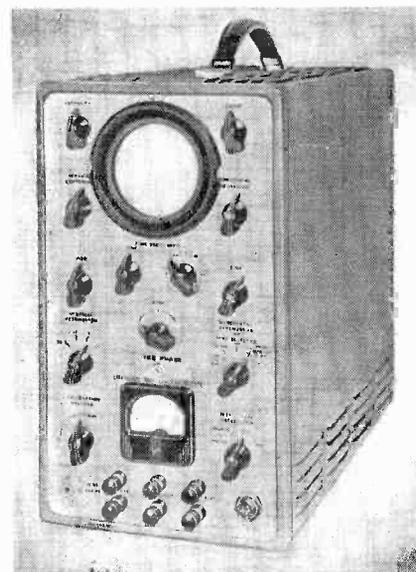

**The control panel of the new RCA general purpose oscilloscope Model WO-79A. This unit is unique in that it includes a built-in calibrated voltmeter.**

# The Oscillograph...how to use it

→ From Preceding Page

oscilloscope patterns: Voltage plotted against time.) The presentation on the screen thus is a complete trace of the IF band-pass characteristic.

## Sweep-Frequency-Modulated Signal Generator

In order to accomplish a sweep-frequency signal (i. e., a signal which varies in frequency at a linear rate with time, in exactly the same fashion as the horizontal sweep voltage in the cathode-ray oscilloscope circuits, as described in Part II of the series "The Oscillograph . . . How It Works"), a sweep-frequency - modulated signal generator is necessary. There are two general types available: The motor-driven rotating-condenser type, and the reactance-tube type.

### Motor-Driven Rotating-Condenser Generator

This type of variable sweep-frequency signal generator may be purchased as a complete unit containing oscillator, variable rotating condenser, and driving motor, or it can be made by modifying a standard signal generator by the addition of a motor and condenser. The motor is a small fractional horse-power AC synchronous or induction type. The electrical relationship between the rotating condenser and the tank circuit of the oscillator should be made such that a rotation of the condenser from maximum to minimum capacitance will vary the output frequency by an amount somewhat greater than the expected band-width of the amplifier. For example, a commercial superheterodyne type standard broadcast receiver having an intermediate frequency of 460 kilocycles will in general pass frequencies on the order of 10 kilocycles above and below this center frequency; then in order to gain a complete picture of the band-pass, the frequency modulation should cover the range from about 25 kc below to 25 kc above mean frequency. In a typical set-up, the variable rotating condenser can easily be made to produce frequency excursions of 25 kc, which means the output frequency from

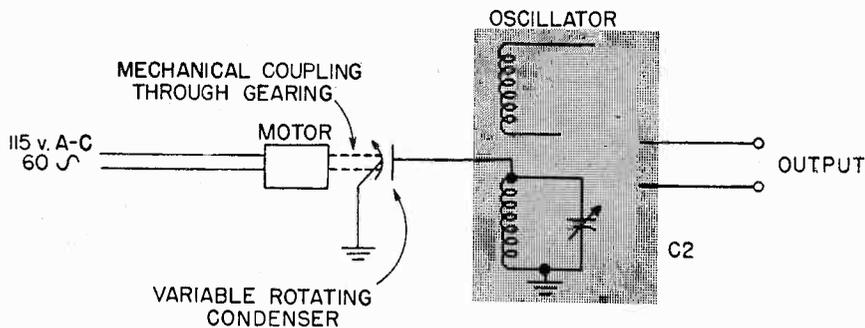


Fig. 2 A sweep frequency modulated signal generator using a motor-driven rotating condenser.

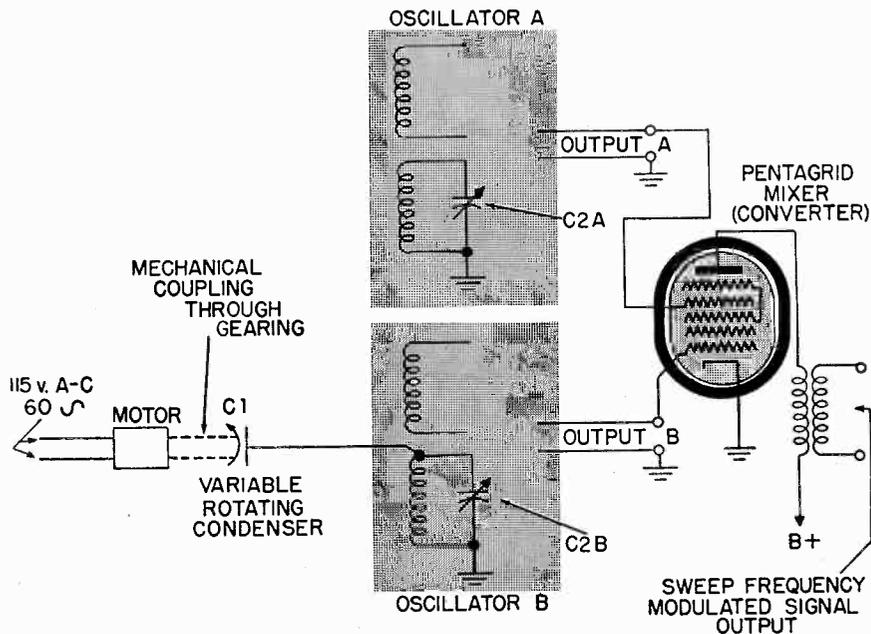


Fig. 3 Sweep frequency modulated signal generator using the double oscillator method. The sweep frequency remains constant for all center frequencies.

the signal generator will vary from 435 kc to 485 kc and back again, at a rate determined by the speed of the shaft on which the rotating condenser is connected.

With C1 of Fig. 2 connected to the oscillator tank circuit and its variable plates adjusted to approximately half capacitance (rotor and stator plates slightly less than half engaged), tune the oscillator (C2 is shown symbolically as the main tuning element of the tank circuit) to 460 kc. Then rotate the variable condenser C1 and determine whether or not the output frequency varies from approximately 435 kc to 485 kc and back to 435 kc for one complete revolution of C1. It is not necessary to have a frequency excursion of  $\pm 25$  kc but

the center frequency must be the desired mid-frequency of 460 kc. If the gearing between the motor and the rotating condenser is so arranged that C1 is driven at 60 cycles per second, or some multiple of 60 cycles, then the oscilloscope sweep circuit can be synchronized with line voltage. Otherwise, synchronize the oscilloscope internally.

(NOTE: Commercial sweep-frequency modulated signal generators have contacts arranged on the condenser shaft for synchronizing the oscilloscope externally.)

The type of frequency-modulated oscillator described above is characterized by variable band-width for different center frequencies because the same percentage frequency shift is always realized. Thus, if we ob-


tain, as above, a shift of 50 kc about a mid-frequency of 460 kc, the same *percentage* change would be experienced at any other mid-frequency setting of the oscillator. For example, unless the oscillator circuit were radically altered or the rotating condenser were changed, if a new mid-frequency of 1000 kc were desired, the frequency shift here would be 11 per cent

$$\left(\frac{50 \text{ kc}}{460 \text{ kc}} = 11\%\right)$$


of 1000 kc, or 110 kc, more than twice the shift at 460 kc.

**Constant band-width** at any output mean-frequency can be derived from a double-oscillator generator, as shown in Fig. 3. Here the outputs of two oscillators, one whose frequencies are varied by the rotating condenser, are mixed to produce a single difference frequency. It will be shown briefly how this double-oscillator circuit works. Oscillator A is the fixed frequency oscillator, and B is the oscillator whose frequency is varied by rotation of C1. For 460 kc, adjust A to some fixed frequency, say 500 kc. Then adjust B to a mean frequency of 960 kc. The output of the mixer tube will then be their difference, 460 kc, the desired center frequency.

If B is arranged so that complete rotation of C1 from maximum to minimum capacitance will produce a frequency range in B of from 935 to 985 kc, then the mixer output will be 435 to 485 kc. If now, for some particular new application, we desire a sweep-frequency output centered about 250 kc, then A should be adjusted to 710 kc and B maintained at a center frequency of 960 kc. Now, since B has not been changed, rotation of C1 will still produce an output from B which varies from 935 to 985 kc. The difference frequency at the lower limit will be  $935 - 710 = 225$  kc; at the upper limit,  $985 - 710 = 275$  kc. Thus, the output of the mixer tube will be a variable sweep-frequency whose limits are 225 and 275 kc, with a center frequency of 250 kc. The spread here is again  $\pm 25$  kc about the mean of 250 kc, exactly as it was for the first mean frequency of 460 kc. Thus this double-oscillator technique provides a band width which is the same no matter to what de-

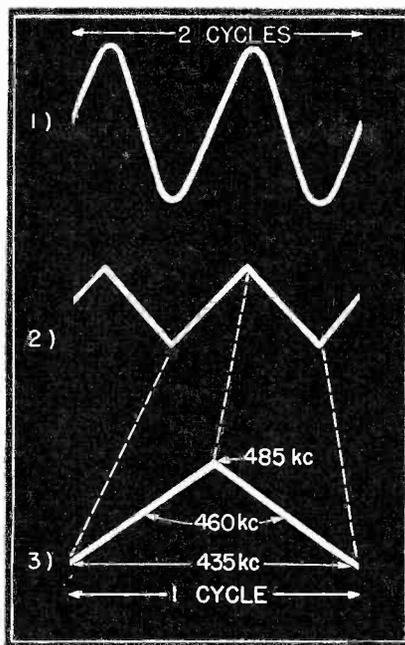

**Fig. 4** A pyramid saw-tooth wave. (1) is the 60-cycle line voltage wave from which it is developed.

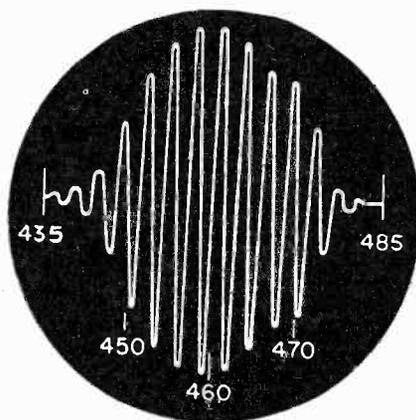

**Fig. 5** Wave form appearing across the secondary of an IF transformer when using a frequency swept signal. The actual wave as it appears on the 'scope will fill in.

sired value the center frequency is adjusted.

### Reactance-Tube Type

This is the more modern method of producing a sweep-frequency-modulated signal for IF alignment. The circuit comprises an oscillator whose tuned circuit is shunted by a *reactance tube*. The latter is a special circuit, consisting usually of a pentagrid-type tube plus associated components, so arranged that a change in bias level of the grid materially alters the transconductance of the tube and causes the impedance, "looking into" the plate-to-cathode terminals, to change, becoming effectively a greater or smaller inductance, or, by an al-

ternate arrangement, a greater or smaller inductance. This tube, then, connected across the tank or frequency-determining circuit of a standard oscillator, will cause the output frequency to change as its grid voltage is changed. If a linear sawtooth voltage wave is impressed on the grid of this reactance tube, the oscillator output frequency will vary approximately linearly with time. For convenience, the sawtooth voltage wave can be obtained from the 115-volt 60-cycle line voltage. See Fig. 4 which shows the development of the sawtooth waveform from the 60-cycle power voltage, and the output frequency of the oscillator under the influence of the reactance tube. The 60-cycle line voltage can then also be used to synchronize the oscilloscope sweep.

It is possible for the radio serviceman to construct a motor-variable condenser type of sweep-frequency-modulated signal generator; the reactance tube type, however, is too complex for further discussion here, and the serviceman is not encouraged to construct one of this type himself. All of the types described are available on the market.

### Connections for a Typical Set-up

In general, this method of alignment provides a visual curve showing the voltage output of the amplifier plotted against the frequency of the input signal, assuming the applied input signal remains constant in amplitude. So far, the requirements of the signal have been discussed with no mention made of the means of reading the amplifier's voltage output under the influence of this signal. If the oscillograph were connected across the secondary of the last IF transformer, the voltage of the signal could be observed on the cathode-ray tube. The signal at this point is an AC voltage, at the frequency of the IF amplifier. While this would serve, it has the characteristic of an AC signal — that is, it varies equally above and below zero; and furthermore, the pattern would give the appearance of a "filled-in" curve, as shown in Fig. 5.

For the alignment indication, a more suitable form is a single line indicating either the positive or the

→ To Page 34


# TELEVISION RECEIVERS

This article covers the third of the seven sections of the television receiver. The RF and Video sections have been covered previously.
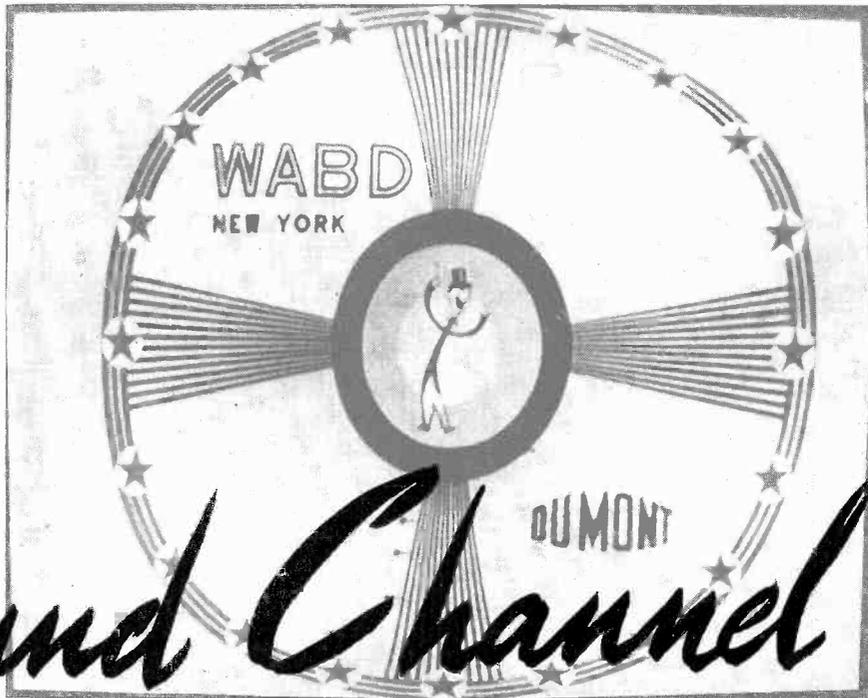
## The Sound Channel

by  
**Morton Scheraga**  
Allen B. DuMont Labs.

TELEVISION RECEIVERS marketed before the war had AM on both the sound and picture channels. As television technique progressed during the war years, the audio system was switched over to FM and will definitely continue in this manner in accordance with the new FCC standards announced in 1945. FM is not only superior to AM in reception, but it also lessens the possibility of interference from other nearby stations operating on the same frequency. There is also the consideration of transmission costs in favor of FM. Television stations have two separate transmit-



ters, one for video and another for audio. The lower audio power required to produce a given signal strength using FM makes this transmission system more desirable.

The two transmitters at the television station operate on separate carrier frequencies. The frequency

difference between the audio and video carriers is the same for all stations, namely, 4.5 mc. It is because of this fixed difference in carrier frequencies that correct tuning of a perfectly aligned television receiver is most easily accomplished by tuning for maximum sound.

Part I on the RF section told how the RF passband of 6 mc permits reception of the 4 mc video channel and its associated sound channel. The combined video and audio channels of a typical television station are shown in Fig. 1. Both signals are heterodyned by the local oscillator and appear at the output of the first detector at lower IF frequencies, 8.25 mc for the audio, and 12.75 mc for the video. It will be shown later how the 8.25

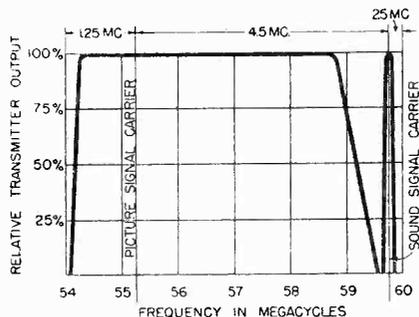


Fig. 1 The combined video and audio channels of a typical television station.


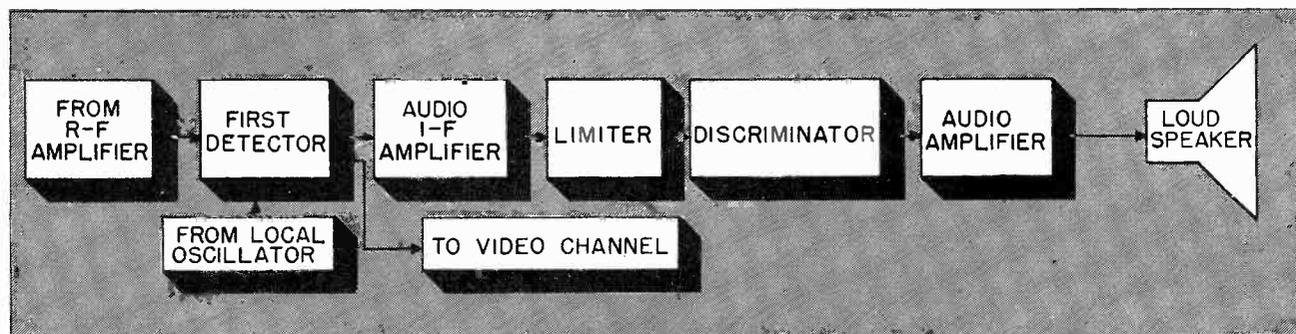


Fig. 2 A partial block diagram of a television receiver showing the audio and video channels. At the output of the first detector, the video and audio signals separate and feed into their respective intermediate frequency amplifiers.

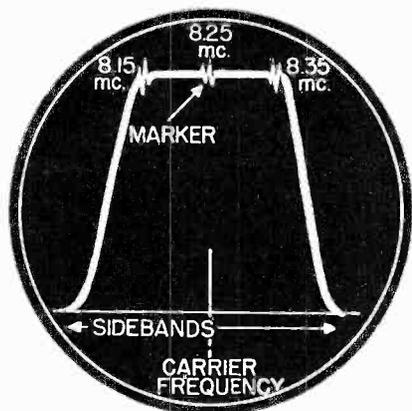

**Fig. 3** Typical response curve of a tuned IF amplifier as used in the audio system of a television receiver.

mc sound carrier is separated from the video information and directed through the remaining audio system.

Previous articles in this series have traced the signal path from the antenna through the RF section to the first detector. It was shown that at the first detector the video information was obtained and the audio rejected from the picture IF amplifiers by suitable filter traps. In this article, we again go back to the output of the first detector, but this time describe the manner in which the audio carrier is selected and amplified, while the video signal is rejected from the sound system. Fig. 2 is a block diagram of the sound channel of a television receiver which we shall treat in detail.

Referring to Fig. 2, we see that once the audio IF carrier has been separated from the video at the first detector, the succeeding stages are identical to a conventional FM receiver. The number of IF stages needed will depend upon the gain obtained in the RF section of the particular television receiver, while the use of more than one limiter will be governed usually by the quality of the receiver.

In the ordinary FM receiver, designed for use between 88 and 106 mc, each station is allowed side bands ranging up to 75 kc on either side of the carrier. For television audio, only 25 kc is used, the narrower band width simplifying somewhat the problem of receiving both the video and the audio carrier simultaneously. Despite the fact that the actual frequency deviation of the incoming audio signal amounts to only 50 kc (plus and

minus 25 kc about the carrier), the band-pass filters in the audio IF amplifiers are generally designed for a width of 200 kc. The extra band width is purposely provided to permit a small amount of frequency drifting in the high frequency mixer oscillator to occur without resultant detuning. A typical response curve for a tuned audio IF amplifier is shown in Fig. 3.

Any amplitude distortion introduced either in the IF amplifiers or by man-made or natural static is smoothed out by the action of the limiter. This operation of the limiter stage is shown in Fig. 4 with the limiter tube characteristic indicated for reference later.


The transforming of the frequency modulated signal into amplitude variations is performed by the discriminator which has a characteristic as shown in Fig. 5. At the

center frequency of 8.25 mc, the output voltage is zero and all frequencies below 8.25 mc result in positive output voltages, whereas all those above 8.25 mc give rise to negative output voltages. In this way, audio voltages varying in amplitudes that depend upon the frequency deviations are obtained.


The audio signal is then fed to a conventional audio amplifier and finally to the speaker.

The selection of the audio carrier and the rejection of video signals which would cause amplitude modulation of the signal is accomplished at the first detector by a parallel resonant circuit tuned to 8.25 mc. This circuit is shown in the schematic diagram of Fig. 6, and consists of L-1 and C-1 in parallel, shunted R-1. It will be recalled that the impedance of such a

→ To Following Page

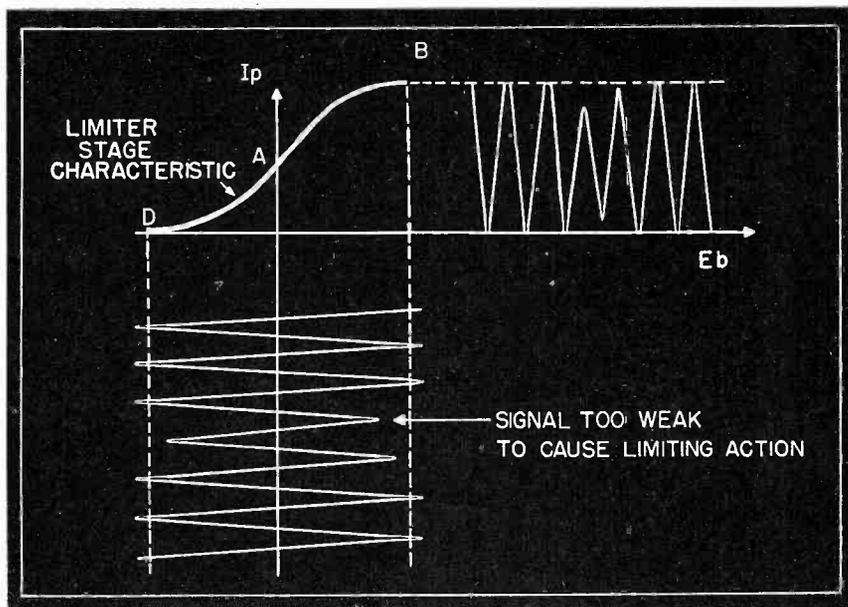

**Fig. 4** Limiter stage response curve showing the limiter action on the signal. When the signal is not strong enough to reach points B and D and saturate the limiter, no limiting action occurs.

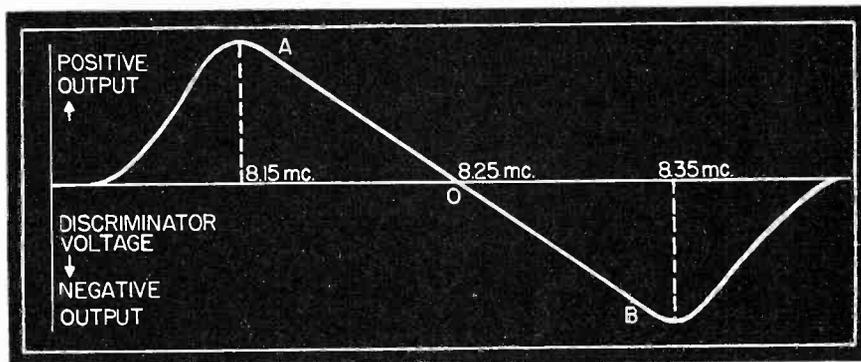

**Fig. 5** Characteristic response curve of a typical discriminator as used in a television receiver.

# The Sound Channel

→ From Preceding Page

parallel circuit is a maximum at the resonant frequency. Hence, at 8.25 mc, a strong IF signal voltage is developed across the tuned circuit. This voltage is coupled to the grid of the first sound IF amplifying tube. The circuit will not offer much impedance to the picture IF signal currents and therefore very little picture IF signal voltage will be applied to the first sound IF amplifier.

Usually two stages of IF amplification are required to bring the signal up to a level at which it can saturate the limiter so that it operates beyond point B on the curve in Fig. 4. From this point, the output of the limiter will remain constant. Should a signal be so weak that it causes the tube to operate within the region DAB, signal noise and distortion present will appear in the output and be passed on to the discriminator.

Greatest amplification is obtained from the limiter if grid-leak bias is used. See Fig. 7. The grid-leak resistor is also a convenient point to align the preceding IF amplifiers, for the voltage across this resistor will vary with the amplitude of the incoming signal. For the alignment of the audio IF stages, the vertical input terminals of the oscillograph are placed across the grid-leak resistor. The same sweep generator that was suggested for the alignment of the video IF stages may be used. It is fed into the IF amplifier across the control grid and ground. The curve that should be obtained is that shown in Fig. 3. To indicate the 8.25 mc on the pattern, place another oscillator in parallel with the sweep generator and set this unit to 8.25 mc. This will generate a marker point which appears as a slight pip on the curve. Now adjust the transformers of the audio IF stage until the response curve is flat to the 100 kc points above and below the 8.25 mc point. (These frequencies may be indicated by moving the frequency of the marker oscillator first to 8.15 mc and then to 8.35 mc. If there is a second IF stage, leave the oscillograph input across the grid-leak resistor, but move the sweep generator input to the next IF ampli-

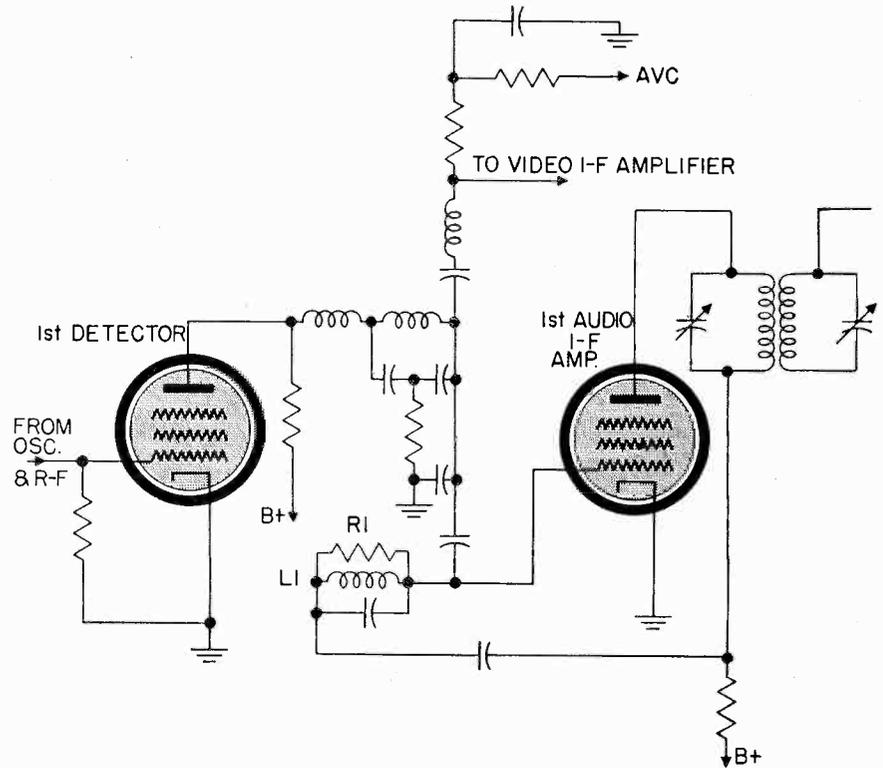


Fig. 6 Simplified diagram of first detector and first audio IF amplifier stages showing the parallel resonant circuit which is used to select the audio carrier and reject the video signal.

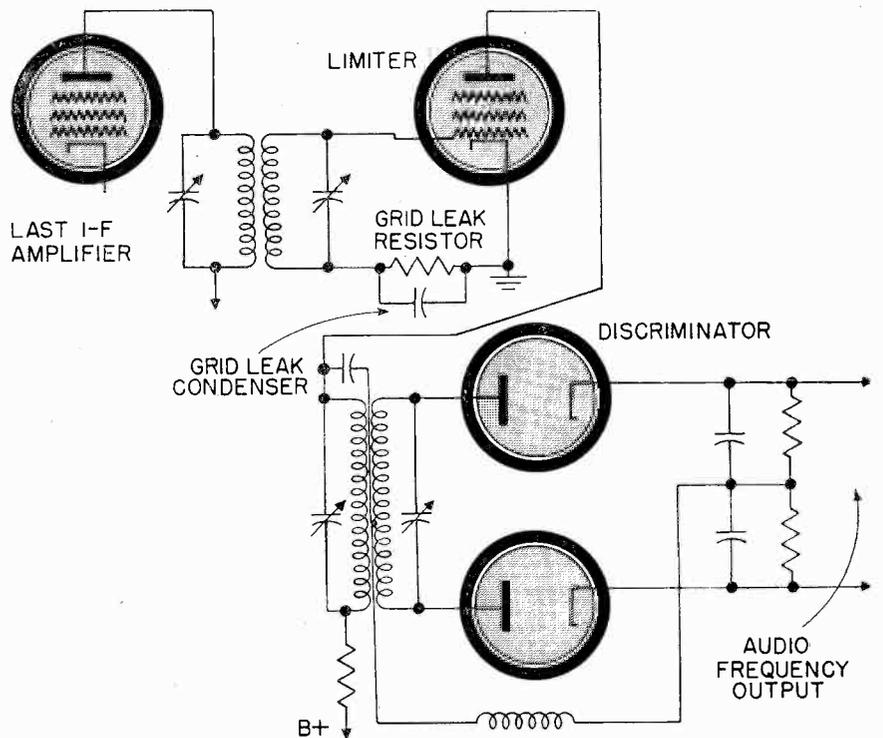


Fig. 7 Simplified diagram of the limiter and discriminator circuits. The limiter shown above uses grid leak bias.

# Don't Waste Time Figuring How to Take It Apart

## PHOTOFACT\* FOLDERS

give you complete  
disassembly  
instructions



Do you lose valuable time discovering how to take out chassis, speakers and record changers from some of the new combinations? Are you familiar in all cases with *the proper sequence of removal*? Whenever the procedure is complicated, PHOTOFACT FOLDERS give you complete disassembly instructions—enable you to do an efficient job without damaging panels, dials, grilles or any other parts of the set. Better still, you're sure of getting them back together again in the quickest possible time.

That's not all PHOTOFACT FOLDERS do. They make it easy to diagnose trouble, locate defective parts, decide on adequate replacements and *get them in a hurry*. They do this by means of exclusive numbered photographs, full-page easy-to-read schematics, complete parts listings, record changer anal-

yses and many other helps that assist you in making up to twice as many repairs a day.

PHOTOFACT FOLDERS are the result of actually examining and testing the instruments covered. They are based on *original research*—not on "canned" or copied information. They cover *all* the latest radios, phonographs, record changers, recorders, communications systems and power amplifiers. Sent to you in sets of 30 to 50 folders, they cost only \$1.50 a set. This includes membership in the Howard W. Sams Institute. Actually they cost you nothing for they pay for themselves over and over again in time saved.

Over 25,000 radio service engineers use and depend on them! Give servicing worries the go-by! Spend less time, do better work—and more of it—by seeing your distributor or by using the convenient coupon.

### PUBLICATION DATES

Set No. 13 . . . February 10

Set No. 14 . . . February 25

Cut this out and MAIL OR TAKE IT TO YOUR DISTRIBUTOR. If you do not know his name and address, send it directly to Howard W. Sams & Co., Inc., 2924 East Washington Street, Indianapolis 6, Indiana, and we will see that your nearest distributor gets it. In Canada, write to A. C. SIMMONDS & SONS, 301 King Street East, Toronto, Ontario. Canadian Price, \$1.75.

Send Set No. 14 (Feb. 25)

Send Set No. 13 (Feb. 10)

Send Set No. 12 (Jan. 25)

Send Set No. 11 (Jan. 10)

Send me Volume 1 (including Sets Nos. 1 to 10) with De Luxe Binder, \$18.39. Individual Sets Nos. 1 to 10, \$1.50 each.

Send me a De Luxe Binder (at \$3.39)

My (check) (money order) (cash) for ..... is enclosed. (If you send cash, be sure to use registered mail.)

PLEASE PRINT

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

Company Name \_\_\_\_\_

My Distributor's Name \_\_\_\_\_

City \_\_\_\_\_

\*Trade Mark Reg.

## HOWARD W. SAMS & CO., INC. RADIO PHOTOFACT SERVICE

In Canada—write to A. C. SIMMONDS & SONS, 301 King Street East, Toronto, Ontario

fier grid and repeat the procedure.

The discriminator is aligned by feeding the two oscillators (the sweep generator and the marker unit) into the grid of the first IF amplifier. The input to the oscillograph is connected across the output of the discriminator (the AF output terminals shown in Fig. 7). Another possible location would be at the grid of the first audio amplifier. The curve to be obtained when adjusting the discriminator tuned circuits is that of Fig. 5. The important thing to achieve in the alignment of the discriminator stage is the linearity of the portion of the curve between points A and B. If the discriminator input transformer has two adjustments, the primary winding adjustment will control the length of the linear portion of the curve. The secondary winding adjustment controls the position of the resonant frequency of the secondary, which should be midway between the two peaks.

The alignment of the audio amplifier is best done by a point-by-point check, feeding a sine wave from an audio oscillator and noting the output on an oscillograph. A complete description of this procedure is given in the December 1946 issue of *RADIO MAINTENANCE* in Part II of "The Oscillograph . . . How to Use It."

The understanding of the operation and alignment procedure of the sound channel makes the troubleshooting problem relatively simple. The usual faults fall into two basic categories in the audio system of a television receiver: (1) No sound at all, and (2) distortion of the sound.

Lack of sound is due to one of two types of general fault. The first is obvious and is due to an open lead or defective component in the audio channel. A stage-by-stage check should isolate such a fault quickly. The second cause for no sound reception lies outside of the audio channel in the RF section wherein the oscillator has drifted so far that the sound IF carrier and its associated side-bands fall outside the band pass characteristic of the amplifier system. This condition and methods for realignment were treated in detail in Part I. of this series on the RF section. It was shown that the easiest way to localize this type of fault to the


RF section is to tap the grid of the first audio IF amplifier. If the tapping sound comes through the speaker, the likelihood is that the audio channel is operating correctly but that the cause for no sound lies in the RF section.

Location of the causes for distortion is most quickly accomplished by an alignment check starting from the audio amplifier and working through the discriminator, limiter, and IF amplifiers, using the methods described above. This alignment procedure constitutes in reality the troubleshooting attack in the audio system. If in the course of aligning a particular stage it is impossible to obtain the required band-pass characteristic, then a check should be made of the tube, the operating voltages, and any suspected off-value components. Ref-


erence to the manufacturer's manual will help in this case, since the latter usually contains typical operating voltages and also the characteristic band-pass curves of each stage.

This discussion of the audio system in a television receiver and the two previous articles on the RF section and the video channel have covered the circuits which bring the signal from the antenna up to the picture tube in the case of the video and through the loud speaker in the audio system. There remains for discussion those circuits which operate the cathode-ray tube and control the motion of the electron beam so as to produce the composite picture on the face of the tube.

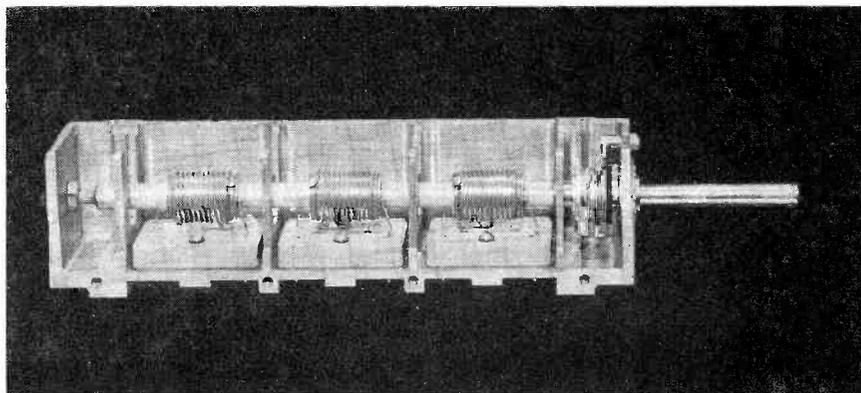In the next issue, we shall deal with one of these circuit units, the Vertical Sweep System. ✓ ✓ ✓



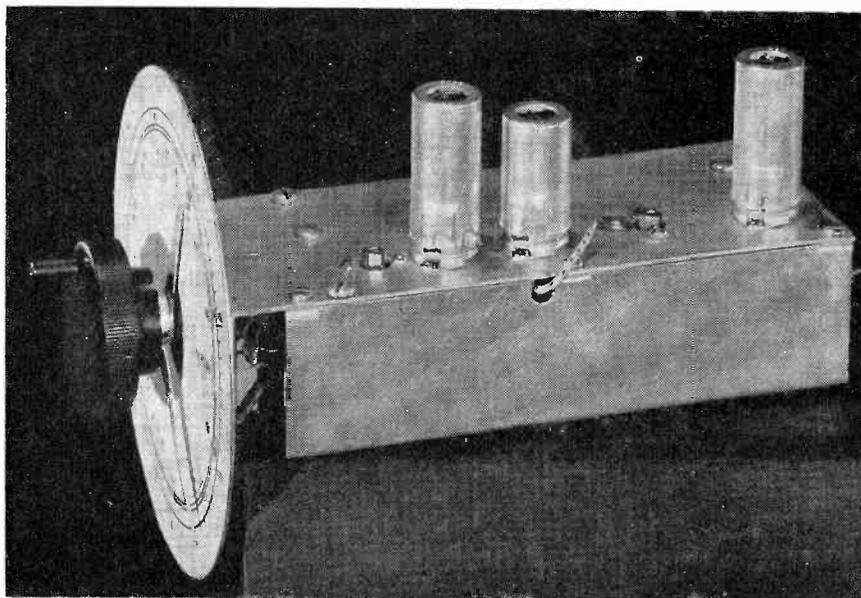**The Inductuner, a unit developed by Du Mont Labs. It provides an extremely wide tuning range from approximately 49 to 210 megacycles. Provision is made for RF stage, mixer stage and oscillator stage tuning.**




**The Inputuner, in which the Inductuner is used. The three shields cover the RF, mixer and oscillator tubes.**

# NEW

## Simpson Model 305RC Tube-Tester with

### "No Backlash" \* Roll Chart

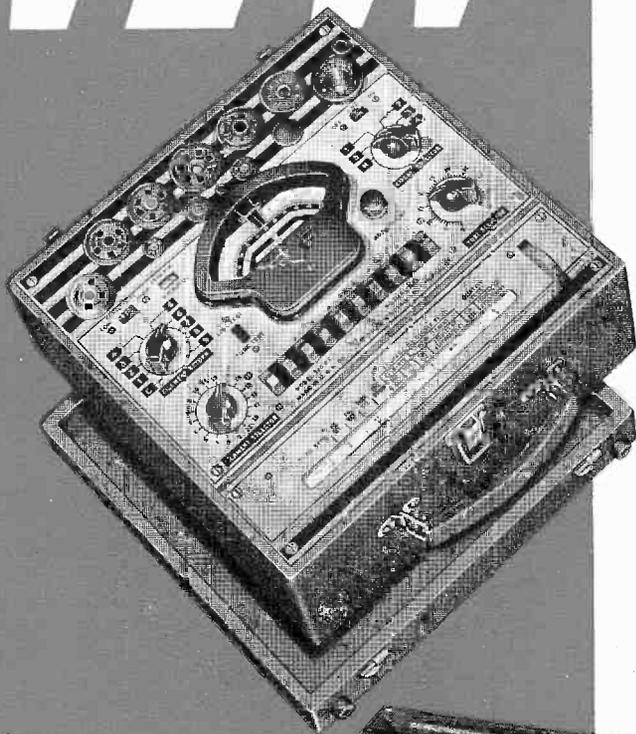

With the addition of the new Simpson "No Backlash"\* Roll Chart to the 1947 version of our Model 305, this famous instrument becomes beyond question the finest tube-tester on the market in its price range. Read the description of this new Roll Chart in the panel below.

Model 305RC provides for filament voltages from 5 volts to and including 120 volts. It tests loctal, single ended tubes, bantams, midgets, miniatures, ballast tubes, gaseous rectifiers, acorn tubes, Christmas tree bulbs, and all popular radio receiver tubes.

Like other Simpson tube-testers, the Model 305RC incorporates 3-way switching which makes it possible to test any tube regardless of its base connections or the internal connections of its elements. This method, the result of exhaustive research and expensive construction, protects the Model 305RC against obsolescence to a degree not enjoyed by competitive testers. No adapters or special sockets are required. In addition to having a complete set of sockets for every tube now on the market, this tester has a spare socket, to provide for future tube developments.

The Model 305RC has provision for testing pilot lamps of various voltages as well as Christmas tree bulbs. It tests gaseous rectifiers of the OZ4 type—also tests ballast tubes direct in socket for burnouts and opens. Has neon bulb of proper sensitivity for checking shorts. This tube-tester is fused, and has the latest improved circuit. It provides for line adjustment from 100 to 130 volts, with smooth vernier control.

Model 305RC is distinguished for its beautiful exterior. It has a two-tone metal panel in red and black on a satin-finished background. Sockets and controls are symmetrically arranged for quick operation. The large, modern, fan-shaped instrument has an exceptionally long scale. It has "good" and "bad" English markings, also a percentage scale for matching and comparing tubes. Cases, both portable† and counter style, are made of strongly built hardwood, durably and beautifully finished.

Size, 11"x11"x6". Wt. 10 lbs. Shipping wt., 15 lbs.  
Dealer's net price, portable or counter model.....\$59.50  
For 60 cycle 115 volt current only.

For 220 volt or 60 cycle, add..... 7.50  
Standard Model 305, with book-type speed chart 49.50

**Counter Model 305RC.** Same instrument as portable model, but set in fine walnut finished hardwood case, with tilted, easy-to-use panel.


†Finished hardwood cases are standard on portable models. When these are not available, the instrument is housed in attractive simulated-leather covered case.

**SIMPSON ELECTRIC COMPANY**  
5200-5218 W. Kinzie Street, Chicago 44, Illinois  
In Canada, Bach-Simpson, Ltd., London, Ont.

# \*6

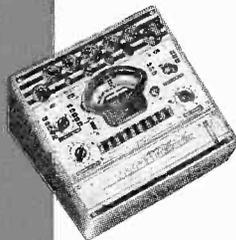
### Exclusive Features Make This the Finest Roll Chart Ever Designed for Tube-Testers

- "No Backlash" feature of this Roll Chart automatically takes up all slack in the paper chart and, by keeping it in constant tension, makes it impossible to turn the selector wheel without turning chart. Gives precision selection at all times. Also prevents chart from tearing or getting out of alignment.
- Gearing is such that only 6 turns of selector wheel will run the entire length of the 12½ ft. chart.
- Easy to read. The clear Lucite window is just wide enough to show 2 tube settings, or both settings on a multi-purpose tube.
- Entire unit removable by taking out four screws. Just lift from receptacle to make new entries or install new chart.
- Chart ingeniously fastened to rollers, affording easy replacement and constant alignment.
- Rigid, light-weight construction. Gear driving mechanism incorporates heavy-duty precision brass gears and parts.



# Simpson


INSTRUMENTS THAT STAY ACCURATE

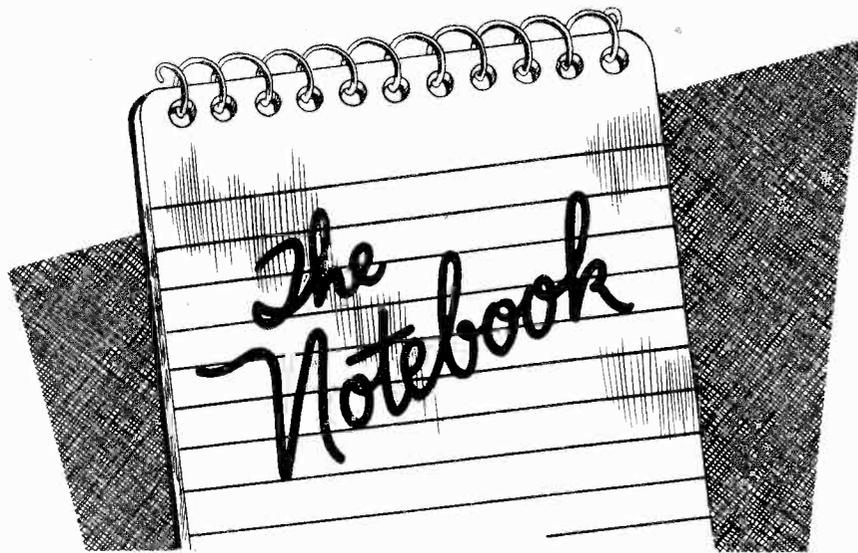

Each month the reader sending in the best suggestion receives a crisp ten dollar bill. For all others published, RADIO MAINTENANCE will pay five dollars. Let's hear from you.
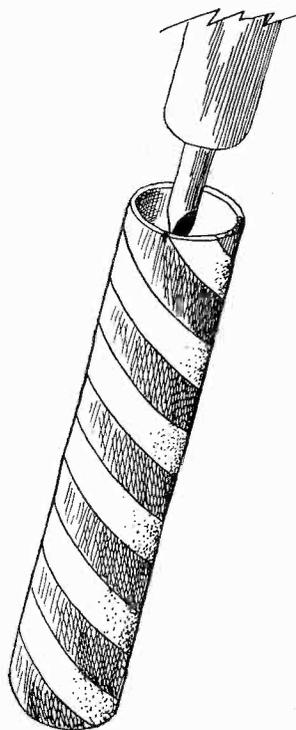
### Portable Soldering Iron Holder

A GOOD PORTABLE soldering iron holder can be made out of a piece of aluminum tubing about 10 inches long and 2 inches in di-




ameter. One end of the tubing is plugged with a piece of wood cut to fit. A piece of sheet iron or aluminum is tacked to the inside end of the plug to protect the wood from the hot iron. The tube is then

wrapped in two or three thicknesses of sheet asbestos and the whole thing covered with friction tape. Another piece of asbestos is placed inside on the plugged end. This holder answers the question of what to do with the hot iron when returning to the shop from an outside call.

Bob J. Oja  
Bob's Radio Electric Shop  
Laurium, Michigan
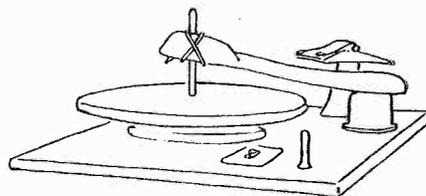
### Protecting Pickup Cartridges

When a unit containing an automatic record changer is being moved to or from the shop, the crystal cartridge and needle can be protected from breakage by tying the pickup arms to the center post as shown in the accompanying dia-




gram. The arm is placed near the top of the spindle and an elastic band is wound back and forth around them.

James E. Dalley  
3133 Jefferson Avenue  
Ogden, Utah
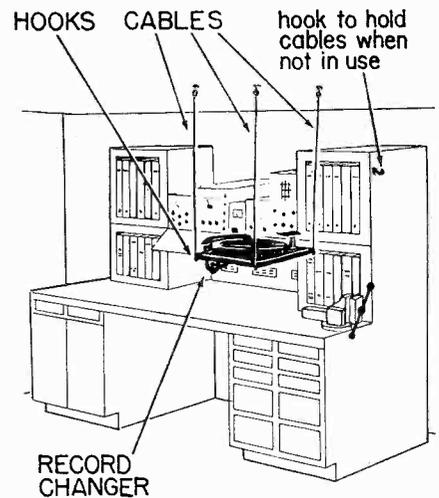
### Record Changer Rack

A good record changer rack for use while doing a repair job can be constructed with three sash cord chains. The three chains are fastened to the ceiling above the bench with screw eyes. Hooks are used



at the ends of the chains to hold the changer being worked on, as shown in the diagram. A hook or wire placed on the upper corner of the bench serves to keep the chains out of the way when they are not in use.

John Hoffman  
Supreme Radio Service  
St. Louis, Mo.

### Bridging Filter Condensers

When bridging filter condensers, it is difficult to listen to the output of the set for elimination of hum. A doctor's stethoscope greatly simplifies matters. The end of the stethoscope (incidentally, they sell for less than three dollars) is placed in front of the speaker. Thus it is possible for the serviceman to move his head around and locate the condenser to be bridged.


W. Stuedeman  
Radio Service Associates  
East Orange, N. J.

### Novel Bench

In small shops where it is often necessary to move a disassembled set from the test position, as when checking for an intermittent, or in large shops where a set is moved from one bench to another while being worked on, a bench con-

→ To Page 30


# THE INDUSTRY PRESENTS

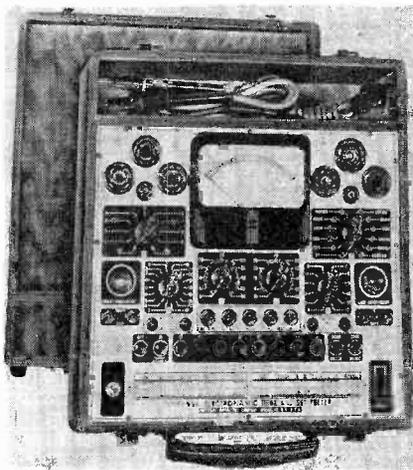
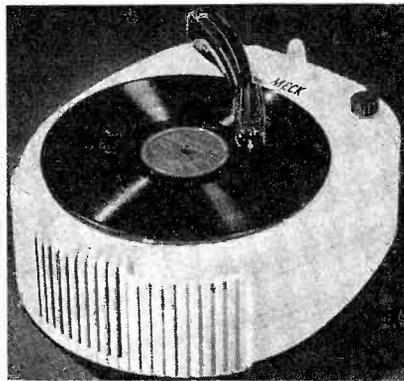
## NEW TESTER


Precision Apparatus Company of Elmhurst, N. Y., announces their 954-P Electronic Tube-Battery and Set Tester. This unit is a portable combination mutual conductance type vacuum tube tester, radio battery tester and 37-range supersensitive AC-DC multi-range set tester (ranges to 6000 volts AC and DC at 20,000 ohms-per-volt DC. It is useful for tube test, set measurement and other service problems in AM and FM. It has a wide-faced 4½ inch bakelite cased meter.

Outstanding feature is the Electronic circuit, which in one operation tests all radio receiving tube types for both mutual conductance and cathode structure. Tubes and batteries are tested under load conditions and are rated on a simple 3-colored "Replace-weak-good" scale, in addition to the calibrated reference scale. It features an automatic push-button system. All regular AC-DC analyzing connections are made through only two polarized pin-jacks. The 954-P provides wide range current scales from 60 microamperes to 12 amperes; resistance to 60 megohms and db ranges to 70 db.


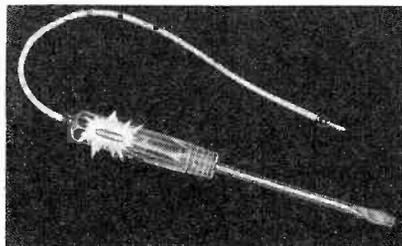
## TABLE RECORD PLAYER


The production of a new table-model record player, Model 3 A6-P8, by John Meck Industries, Inc., of Plymouth, Ind., is under way and distribution to dealers and jobbers is now in progress. This model, the Saratoga, is encased in a white plastic cabinet, approximately 11" wide, 4" high and 15" deep. It has an electronic amplifier, crystal pickup, a 4" electrodynamic speaker, and a heavy duty motor.


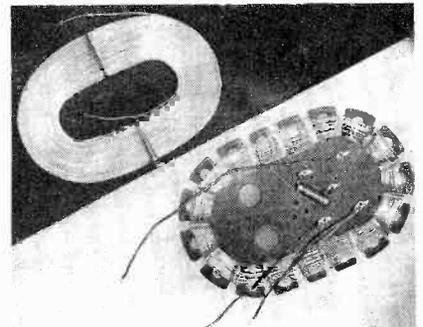
## ELECTRICAL SCREW DRIVER

A new combination circuit tester and electrical screw driver has been announced by the Ox-Wall Tool Co., of New York City. It is a safe electrician's screw driver with a

long-life transparent plastic handle, plus an all-purpose test lamp for fuses, outlets, cords, radios, etc., for 105-550 volts AC or DC. It operates on a principle that eliminates false indication. It is a neon test lamp that lights on any house voltage, won't burn out, won't light on capacity and leakage. The lead is detachable and leaves the tester free for use as a screw driver and for testing ignition circuits.



## LOOP ANTENNA WIRE

A small diameter, polyethylene insulated wire for home radio receiver loop antennas has been developed by Federal Telephone and Radio Corporation, Newark, N. J. K-1044 wire is constructed of bare soft copper #24 awg. This wire adds additional sensitivity and selectivity to the radio receiver. Electrical losses at radio frequencies are extremely low. The "Q" factor of an average size loop (6" x 9") reaches and often exceeds 200. Treatment of the wire with polyethylene makes it possible to design a coil without support. Polyethylene-insulated wire is highly resistant to water, acids, alkalis and oils, insuring efficient receiver operation under all atmospheric conditions.

**CAPACITORS  
and  
RESISTORS**

**JIFFY  
CHECKED**  
with the

**AEROVOX  
MODEL 76 BRIDGE**



● A twist of the knob . . . the positive wink of the indicator eye . . . a glance at the big, easy-to-read dial through the precision pointer . . . another glance at the multiplier switch—and you've got your capacitance or resistance reading. Power factor and leakage readings also available with equal simplicity. Checks for shorts and opens. It's all done in a jiffy—yet with real accuracy.

That's what you get in the Aerovox Model 76 Capacitance-Resistance Bridge just emerged from the Aerovox Engineering Laboratory in response to the demand for a simple, accurate, moderate-priced instrument for use in service shop, laboratory, or out in the field. You just can't afford to get along without it in this fast-moving postwar era!

• • • •

Ask your Aerovox distributor or write us for the "Jiffy Checking" descriptive bulletin. Have your distributor show you this instrument and try it for yourself. You'll want to take one with you!



**FOR RADIO-ELECTRONIC AND  
INDUSTRIAL APPLICATIONS**

**AEROVOX CORP., NEW BEDFORD, MASS., U.S.A.**  
Export: 13 E. 40th St., New York 16, N.Y. • Cable: 'ARLAB'  
In Canada: AEROVOX CANADA LTD., Hamilton, Ont.

# ELECTRONICALLY SPEAKING

organizations in their educational programs and is setting up a committee to obtain and distribute technical data and information.

**R**ADIO TUBE PRODUCTION is now 40 per cent above the 1941 monthly average, according to a year-end statement made by M. F. Balcom, Chairman of the RMA Radio Tube Committee and Treasurer of Sylvania Electric Products Inc. Though tube demands continue to be far above earlier estimates, the present rate should meet most requirements. As production is increasing, no serious tube shortage is anticipated by the end of the first quarter of 1947.

In spite of strikes, raw material and labor shortages during the first half of 1946, the salutary effect of OPA-authorized price increases, followed by the total decontrolling of all radio tubes and parts during the last quarter of the year, eased the situation. The release of military surplus standard type tubes also helped matters.

PENNSYLVANIA SERVICEMEN have taken a long stride forward in organization with the formation of the Federation of Radio Service Men's Associations of Pennsylvania. At present member organizations consist of the Philadelphia Radio Service Men's Association, The Luzerne County Radio Service Men's Association, The Radio Service Association of Pittsburgh, Associated Radio Service Men of Central Pennsylvania, and the Harrisburg Radio Service Men's Association.

Dave Krantz, President of the Philadelphia Association was elected Temporary Chairman of the Federation. Art Guild of the Central Pennsylvania Association is the Temporary Secretary. Dave Krantz states that the purpose of the Federation is to further the aims and purposes of the local organizations and their members. At present, the group is planning to assist member

THE FOURTH SESSION of the Du Mont Television Familiarization Course was held February 4-6 in New York City. Rigid screening examinations to prove themselves already familiar with television service were held for the servicemen applying for the course. This course deals specifically with Du Mont telesets and is for the purpose of insuring proper installation and maintenance.

AN UNUSUAL ADVERTISING CAMPAIGN has been started by John Meck Industries in the Saturday Evening Post. It consists of a series of half-column ads which suggest that radio owners should patronize their local radio repairmen in order to overcome the results of the wartime period when repair parts and service were difficult or impossible to obtain. There is no suggestion that new radios be purchased nor that the repairman chosen should have any connection with a Meck dealer.

"The radio repairman who somehow managed to survive the difficulties of the war years deserves all the help that can be given him by radio manufacturers," says John Meck. "He is an essential part of the radio business. Aside from that, he has a more thorough knowledge of radio from the consumer's viewpoint than anyone else."

THE FCC issued revised figures on receiver ownership in the United States late in '46. Standard or AM sets totalled 66 million; FM sets 500,000; television sets 7,000.

# OVER THE BENCH

by John T. Frye

**EDITOR'S NOTE:** "Over the Bench" will be a monthly feature from now on. Mr. Frye will present his ideas on a wide range of subjects. John T. Frye has been a serviceman since the late Twenties, and we feel that he is qualified to discuss these subjects. At present, he is hanging his sign in Logansport, Indiana. They will be his ideas and as he himself says, "They may not always agree with yours, nor may they always be right." If you have anything you would like to say about the subjects he discusses, write us. All letters will be thoughtfully read and anything we feel is of current interest to your fellow servicemen will be passed on in the pages of this publication.

Address all mail to Mr. John T. Frye, c/o Editor, RADIO MAINTENANCE, 460 Bloomfield Avenue, Montclair, N. J.

WHEN the editor of RADIO MAINTENANCE asked me about writing a column for this magazine, I accepted with unseemly haste. When such an opportunity to do what I had always wanted to do was in the offing, it was no time to be coy.

RADIO MAINTENANCE, you see, is the kind of magazine I have always wanted to see on the newsstand. I have long preached that it is high time radio servicing came into its own. It has been treated as a poor step-child far too long. The first step toward achieving such recognition is the acquiring of a "voice," that is to say, a magazine devoted to and interested in our problems—and in nothing else. Instead of having our interests pushed off into the back pages, we have in RADIO MAINTENANCE a whole magazine that is exclusively ours. Having a small part in the writing of such a publication is everything that I could ask for.

Let me make one thing clear at the outset: This column will wander over a wide range of topics in the following months, but it will always


be distinguished by two characteristics. First, it will always be written *for Servicemen*, for you solder-slingers yourselves. Sometimes the program may sound a little fuzzy, like a set with a leaky coupling condenser, but you had better listen anyway, for it is directed straight at you.

Secondly, it is written by a serviceman. These fingers on the keys right now have soldering-iron burns across the backs and little flecks of that stubborn speaker cement on the nails. Every day, just as you, I am sweating out intermittents, trying to get the oscillation out of four-tube midgets, tapping 75s and 6A7s on the gridcaps with a piece of fiber to see if they are the cause of those abrupt changes in volume. No longer than an hour ago, I patiently explained for the umpteenth time, "But, Madam, I know you had a new condenser put in last year, but this is a different one. You think that a radio has only one condenser, apparently; actually, it has around half a hundred."

I have to bite my tongue just as hard as you do when the customer says nonchalantly, "I am sure there's not much wrong with this set. It was playing all right when we shut it off last night, but it smoked when we turned it on this morning. Probably some little thing like a wire off, or something."

And just like you, I think about this radio servicing business while the soldering iron is heating, while I am waiting on an intermittent to cut out, etc. Out of this thinking have come several ideas that I should like to talk over with you, ideas that range all the way from the best thing to do with those jobs that "Jump away up in volume when we turn on a switch anywhere in the

**BUILT FOR SERVICE**

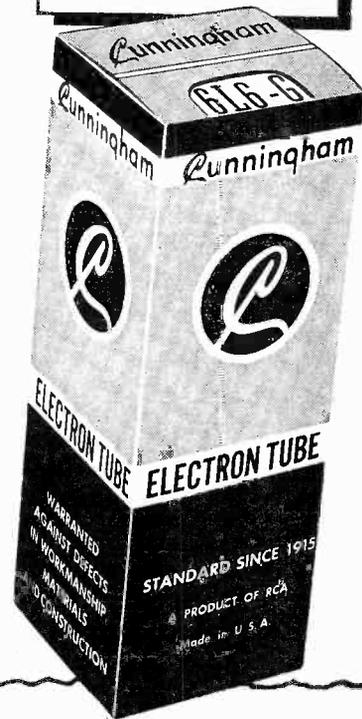

**Now—Quick-Reference  
Up-to-Date Tube Data**

Your Cunningham Distributor has waiting for you this new, up-to-the-minute booklet (1275-C) on Receiving Tubes for Television, FM and Standard Broadcasting. It includes in condensed, easy-to-use form the latest data on all new tubes, revised data on older types, and socket diagrams for the complete line. An added feature is the easy-reference system for immediately identifying miniature and metal types.



You'll find this handy reference guide the speediest answer to many of your technical tube problems... and you'll find Cunningham tubes the answer to improved customer relations. That's because Cunningham tubes are built for service.

For more service — TURN THE PAGE →

**Cunningham  
Electron Tubes**

A product of  
**RADIO CORPORATION OF AMERICA**  
Harrison, N. J.

→ To Page 33

# Selenium Rectifiers

→ From Page 9

us consider the construction of an ohmmeter. It may be represented in simplified form as a milliammeter in series with a resistor and a battery (Fig. 8C). Assume that the ohmmeter is placed across the selenium rectifier with the polarity of the meter as indicated in that diagram and that it reads 10,000 ohms. Reversing the meter leads, as in Fig. 8D, results in a reading of 100,000 ohms. In an ohmmeter, the current through the meter increases as the resistance being measured decreases. This indicates that the proper direction of current flow for the rectifier being checked is from B to A.

Comparing the selenium rectifier to a diode in which the current flows from the cathode to the plate, B is equivalent to the cathode and A is equivalent to the plate. Therefore, A should be connected to the AC line. The manufacturer's marking would show a yellow dot at A and a red dot at B. Following this simple test procedure will, in case of doubt, avoid erroneous connections and ruined rectifiers.

The first sample replacement procedure to be described is for a 117 volt rectifier tube. In this type of rectifier circuit (shown in Fig. 9A), the filament voltage for the other

tubes in the circuit and the B+ voltage are secured from a voltage divider, and are therefore proportional. The internal resistance of the rectifier is an important factor in maintaining the proper filament voltages. If this resistance should be decreased, both the B+ and filament voltages would necessarily increase. The latter, of course, is undesirable as it shortens the life of the filaments. Hence, when a 117 volt tube is being replaced by a selenium rectifier, the difference in the internal resistance of the two must be taken into consideration.

The following operational steps (Fig. 10 illustrates these steps) are recommended:

1. If the tube being replaced is still good, measure the original B+ and filament voltages.
2. Add properly color-coded extension leads (red for the positive side and yellow or black for the

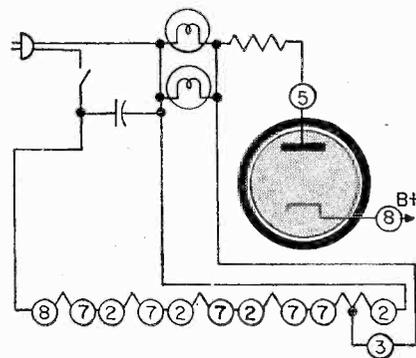


Fig. 11 A power supply circuit using a 35Z5 rectifier tube and two pilot lights.

negative). If the unit is to be self-supporting, number 12 or 14 bus wire may be used.

3. Solder the red lead to the cathode pin of the tube socket.

4. Solder the yellow lead to one end of a 27-ohm, 1-watt resistor.

5. Solder the other end of the resistor to the plate pin of the tube socket.

6. Check to see if the B+ and

→ To Page 32

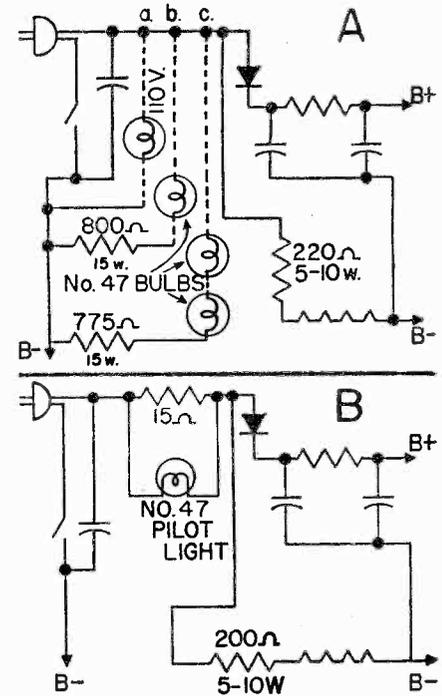


Fig. 12 Four ways in which the pilot light may be connected when converting a power supply using a 35Z5 rectifier to a selenium rectifier unit.


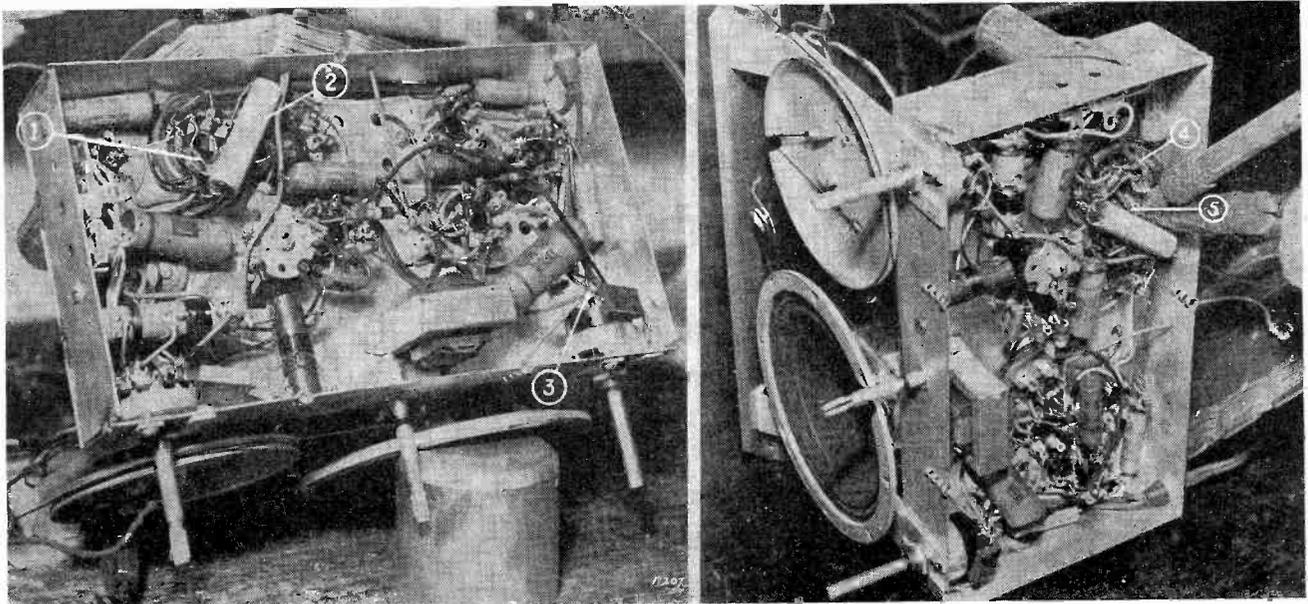


Fig. 13 Underside view of a chassis showing the connections used when installing a miniature selenium rectifier.

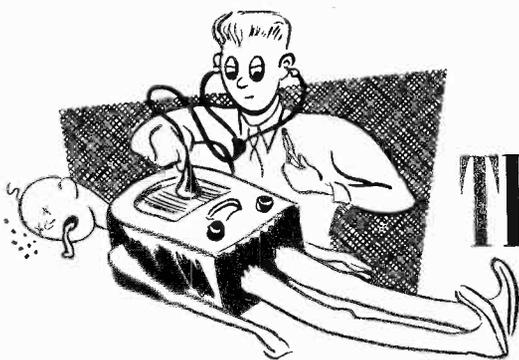

# THE PATIENT

Don Blair

**A**CCURATE TROUBLESHOOTING is the cornerstone upon which a successful repairing career is built. Neat soldered joints and the workmanlike replacement of defective parts are always the sign of a careful worker; but sharp diagnosis will forever remain the screen that separates the gold from the sand.

Thorough diagnosis defines not only the immediate source of trouble, but goes deep enough to ascertain the original cause, and thus points out a repair procedure to prevent the trouble from recurring.

Simply replacing a defective part without debating the cause of its failure is very often the reason for a call-back. And every repairman worthy of the name knows how embarrassing and unprofitable these can be. We should remember that even a simple job entails checking every possible question if the job is to be completely and honestly done. Fortunately, in the majority of routine repair jobs, the investigation of basic cause requires only a moment.

For every effect or failure then, there will be a cause; and our diagnosis will not be complete and dependable unless that cause is found, examined, and remedied.

The need for examining the basic cause for a tube or part failure is constant even in new equipment. Engineers and designers are human and fallible, just as we servicemen are fallible. But a point to remember is that it is never wise to condemn another man's work until we are thoroughly certain he was wrong. In the case of the designer, he is under pressure to keep costs down; and skirts the danger line between safety factor and parts failure many times oftener than his failures would imply.

Complete diagnosis requires more than the investigation of trouble

and its causes. It thrives on experience and accurate memory of similar cases, to wit:

Doc pulled his car up in front of the shop one evening just as I was dousing the lights after a long, hard day.

"Car radio on the bum," he said. "I've got some traveling to do tonight. Could you fix it now?"

"I'll try," I answered, wearily turning the bench lights on again.

Investigation showed mechanical hum, but no sound in the speaker.


"Sounds like a bad tube," I said, suspecting an OZ4. The set was mounted in such a way that it seemed easier to remove it from the car than to try to replace the tube in under the dash. When I opened the set on the bench, I found the RF-IF assembly but no audio or rectifier. Then I remembered that the power supply and audio section in that model was crowded into the innocent looking round speaker case. So I replaced the radio, removed the speaker housing and found the thing I had been looking for—a bad OZ4.

As I finished the job, Doc chided me, "Faulty diagnosis, but the patient survived."

Tired, I replied, "Yes, but you fellows have an easy job compared to ours. You work on the same two models all the time! Why, if you doctors find a patient with his stomach upside down, you make the front pages of all the newspapers in the country. And if that engineer had not put your radio's heart where its larynx ought to be, we'd have been out of here an hour ago." ✓ ✓ ✓

Coming:

Articles on  
**ANTENNAS**

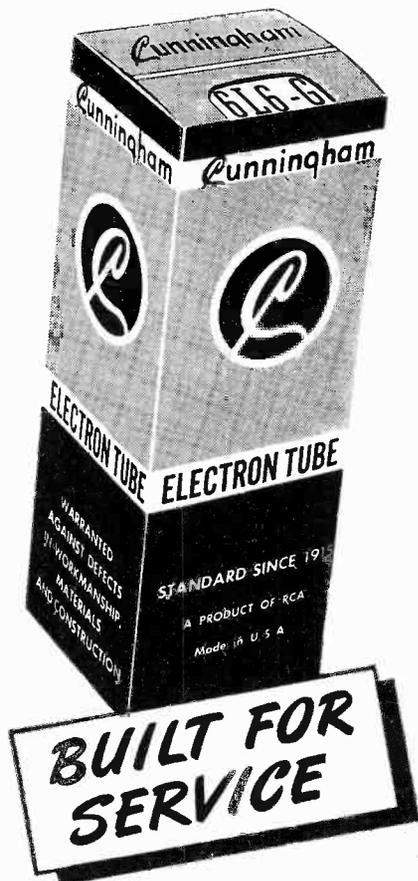

**New Double-Duty Tags  
Build Customer Confidence**

Job No.	Description			Price	Cost
Make	Model	Year	Make	Model	Year
Tube	Quantity	Price	Cost		
Component					
Repairman					
Other Parts					
Label					
Total					
Make	Model	Year	Make	Model	Year

This tag is perforated so that the bottom section, carrying your name, may be used as a claim check. When the job is completed, you can file away the top part as a permanent record of repairs and for maintaining your prospect list.

You'll find these inexpensive repair tags will sell your customers on your dependability... just as the dependability of Cunningham tubes contributes to your prestige.

Here's one of Cunningham's business aids for you—a double-duty repair tag that will keep you and your customers straight on charges and work done. The tag is perforated so that the bottom section, carrying your name, may be used as a claim check. When the job is completed, you can file away the top part as a permanent record of repairs and for maintaining your prospect list.

You'll find these inexpensive repair tags will sell your customers on your dependability... just as the dependability of Cunningham tubes contributes to your prestige.

For more sales—TURN THE PAGE →

**Cunningham**  
Electron Tubes

A product of  
**RADIO CORPORATION OF AMERICA**  
Harrison, N. J.

# NEW SOLDERING GUN

*Heats in 5 Seconds*



## SPECIAL SOLDERING GUN ADVANTAGES

TIP STAYS TINNED  
NO BURNING



SEE WHERE  
YOU SOLDER



SOLDER AROUND  
CORNERS



Service and maintenance men can save time by the fast heating of the Soldering Gun. By use of the new induction principle, 5 second soldering heat is supplied from a light weight built-in transformer.

The loop type tip gives you other advantages that are important in soldering. Good balance with weight close to your hand makes it easier to use. The narrow tip gets in between a lot of wiring with ease. Connections can be made without burning insulation. The tip can be formed readily to work in tight places.

See your radio parts distributor for a demonstration, or write direct for descriptive bulletin.

- ★ 100 Watts 115 Volts 60 Cycles
- ★ Intermittent Operation With Trigger Switch
- ★ Can't Overheat or Burn Out
- ★ Impact Resisting Case
- ★ Handle Stays Cool
- ★ Good Balance—Weight Close To Hand

812 PACKER ST.


**WELLER MFG. CO. Easton, Pa.**

Export Dept.—25 Warren Street, New York 7, N. Y.  
In Canada—Atlas Radio Corp., Ltd., 560 King Street N. W., Toronto, Ont.
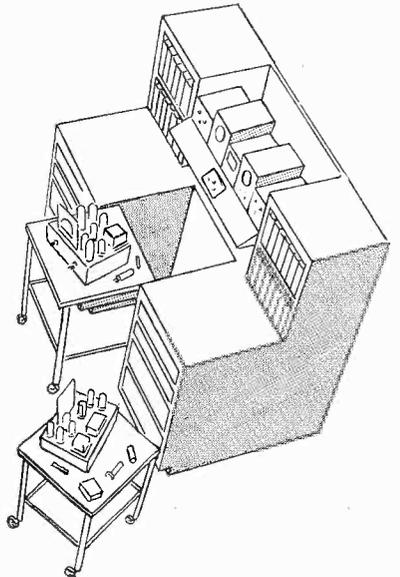
## The Notebook

→ From Page 24

structed as shown in the accompanying diagram is very useful. The center section of the bench is cut away and two or more small tables are built to fit into the space. The tables are mounted on casters



and can be moved in and out of the test position at will. In this way a disassembled set can be moved about the shop without difficulty.

Clay B. Seidel  
Neighborhood Radio Service  
Camden, N. J.

## Dial Belt Kits Ne-O-Lite Testers



### G-C SERVICEMEN'S DIAL BELT KITS



Fine woven replacements for all sets. Easy to install. Supplied in kits of various quantities with steel box. No. G-25—kit of 25 belts—

List **\$6.70**

### G-C RADIO SERVICE CEMENT

Best cement for speaker and radio work. Especially suitable for cementing replacement cones and repairing rattling and torn cones. Dependable, waterproof, fast-drying. No. 30-2—2 oz. bottle, brush attached

List ..... **50c**




Available at  
all leading  
distributors  
Write today  
for catalog

A complete alignment and neutralizing kit in steel box. Contains every tool necessary to service any set; 30 tools in steel box. List ..... **\$19.95**

## Cement Alignment Kits
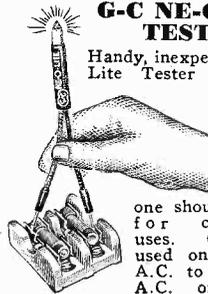
### G-C NE-O-LITE TESTER


Handy, inexpensive Ne-O-Lite Tester that every



one should have for countless uses. Can be used on 60 V. A.C. to 500 V. A.C. or D.C.

No. 5100—single tester on card. List ..... **50c**
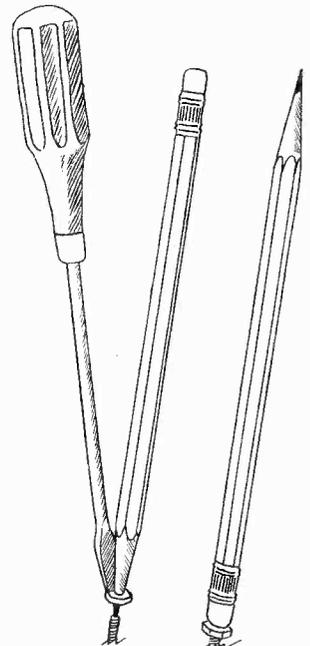
### G-C No. 5025 PROFESSIONAL ALIGNMENT KIT



### Starting Screws

It is sometimes very difficult to start a small nut on a screw in a close place. A lead pencil and small

→ To Opposite Page


RADIO DIVISION DEPT. E

**GENERAL CEMENT Mfg. Co., Rockford, Ill., U. S. A.**  
Manufacturers of over 3,000 products • Sales offices in principal cities

# OHMITE

## Little Devil

INSULATED  
COMPOSITION  
RESISTORS

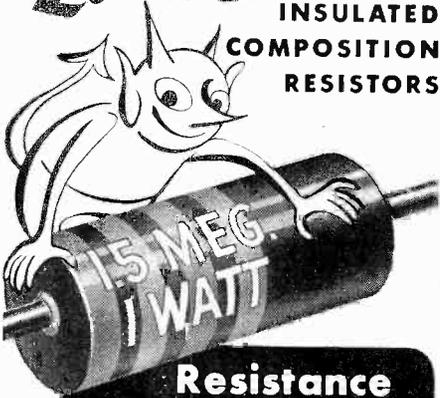


Resistance  
and Wattage  
marked on  
**EVERY UNIT**

Here is a new composition resistor—tiny but exceptionally rugged. Not only color coded, but individually marked for quick identification. *Little Devils* are sealed and insulated by molded plastic. They dissipate heat rapidly, have a low noise level and low voltage coefficient, are light, compact, and easy to install. Millions of these units have proved their value in critical war equipment. Available from stock in Standard RMA values from 10 ohms to 22 megohms. Tolerance + 10%.

Available only from Ohmite Distributors

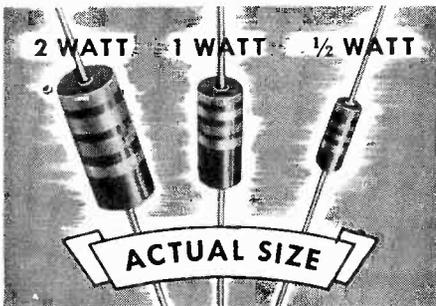**OHMITE MANUFACTURING CO.**  
4912 FLOURNOY ST.  
CHICAGO 44, ILL.



Send Now for  
Bulletin No. 127

Gives complete data and list of RMA values. Includes dimensional drawings and handy color codes.




*Be Right with...*

**OHMITE**  
RHEOSTATS  
RESISTORS • TAP SWITCHES

→ From Opposite Page

screwdriver used as shown in the diagram are of great assistance. The nut is placed on the sharpened end of the pencil and pushed lightly until it is held. The pencil point is placed on the end of the screw; and using the screwdriver, the nut is pushed off the pencil and held in place. The pencil is then reversed, and the eraser end is used to start the nut. (ED. NOTE: A pencil can also be used to advantage when starting a machine screw in a hard-to-get-at spot, as shown in the accompanying photograph.)

D. G. Ballard  
Belmont, N. C.

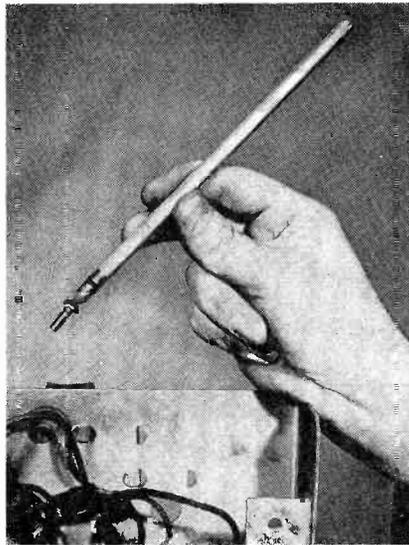


### IMPORTANT

**RADIO MAINTENANCE** is inaugurating a new department for the purpose of reporting on the activities of servicemen's organizations.

We feel that this column will be of vital interest to our readers. If you are a member of an organization, we would like to hear from you. We would also like to know the names and addresses of the officers of your group so that we may write them and tell them how your organization can obtain writeups in this new column.

Many other organizations have already expressed a desire to participate. So let's hear from you.

**BUILT FOR  
SERVICE**

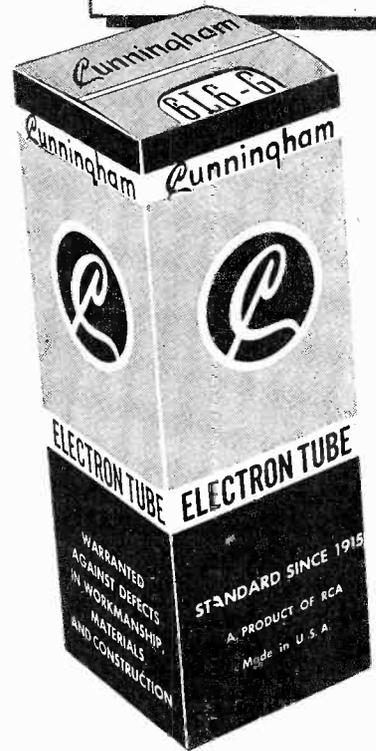

**Your Name Out Front  
on a Cunningham Sign**



Catch customers' eyes—and their business—with this new blue and orange outdoor sign that ties your name up with Cunningham tubes and their 30-year reputation. The 3½ x 15-inch hanging metal pendant will give your name the prominence it should have along the street.

Arrange with your Cunningham Distributor today to get one of these signs so that you can "hang out your shingle" and cash in on Cunningham tubes. That's an easy way to build customer confidence, because Cunningham tubes are *built for service*.

For expert guidance—TURN THE PAGE →

**Cunningham**  
Electron Tubes

A product of  
**RADIO CORPORATION OF AMERICA**  
Harrison, N. J.

# WARD

WORLD'S FINEST  
AND FASTEST SELLING

## Aerials

Here's Your Newest Profit Builder!  
A striking, three-dimensional display which catches the eye of every customer. It's completely assembled, ready to place on your counter and bring in easy, extra sales. You pay only for the four fast moving models mounted. The display itself is FREE!



**Model 61-7**  
**PROFIT BUILDER**  
LIST \$22.00

Each of these models is engineered and equipped to fit every car!

# WARD

## Aerials

Every Ward model has been tested and approved by car and radio set manufacturers—your proof of quality inside and out.

THE WARD PRODUCTS CORPORATION • 1523 E. 45th STREET, CLEVELAND 3, OHIO  
EXPORT DEPARTMENT: C. O. BRANDES, MGR., 4900 EUCLID AVENUE, CLEVELAND 3, OHIO  
IN CANADA: ATLAS RADIO CORP., 560 KING STREET, WEST, TORONTO, ONTARIO, CANADA

lem. In this case, not only is the 35Z5 filament in series with the others, but in addition, the dial light derives its potential from half the filament as shown in Fig. 11. Unlike the 117 volt tubes, the drop across the tube may be neglected.

The size of the resistor to use in place of the filament may be calculated in the same manner as a line cord resistor by means of Ohm's Law. The filament voltages of the remaining tubes are added, and the result subtracted from 120. This difference is the voltage to be dropped across the substitute resistor. As the filament current is known, the value of the resistor may be found by the formula  $R = \frac{E^2}{I_1}$

It is essential to use the proper wattage rating as well. A wattage of twice the calculated value ( $W = E \times I$ ) is recommended. For the 35Z5, a 220 ohm, 10 watt resistor will suffice.

The pilot lamp circuit presents various possibilities depending on the original circuit. Fig. 12A and 12B illustrate four alternatives, as follows:

- (A) A 110 volt bulb across the line.
- (B) A number 47 (brown bead, 6-8 volt, 150 mil.) pilot light in series with an 800-ohm, 15-watt resistor across the line.
- (C) Two number 47 pilot lights in series with a 775-ohm 15-watt resistor across the line.
- (D) A number 47 pilot light in parallel with a 15-22 ohm 1-watt resistor, depending on the amount of illumination desired.

The sample replacement procedure for a 35Z5 illustrates the use of a 110-volt bulb such as the 10-watt 10C7. The advantage of this is twofold; more light and the isolation of the pilot light from the rest of the circuit.

The first step is, as before, to solder properly color-coded extension leads on to the selenium rectifier. A jumper wire is then placed between pins 2 and 3 (1 on Fig. 13, photo) to short out the original pilot light circuit. Next a 220-ohm, 10-watt resistor is soldered between pins 3 and 7 (2 on Fig. 13).

The extension leads may then be brought down through the tube socket. One side of the 110 volt bulb and the yellow lead of the rec-

## Selenium Rectifiers

→ From Page 28

filament voltages are within at least 10 per cent of the required values. If not, the 27-ohm resistors must be changed to obtain the correct reading.

In order to save time when determining the correct value of resistance to be placed in series with the rectifier, two Fahnestock clips connected to two alligator clips and leads may be mounted on the work bench. The experimental value of resistance may be placed between the Fahnestocks and the alligator clips connected to the yellow lead of the selenium rectifier and the plate pin respectively. The voltage readings may then be taken; and when the proper value of resistance has been determined, it may be soldered permanently into the circuit. Incidentally, this same set-up may be used for general troubleshooting purposes.

The replacement of such tubes as the 35Z5 presents a different prob-

**Radiomen: WANT YOUR OWN BUSINESS?**

**FEDERATED GETS YOU STARTED**  
**for as little as \$195.00**

For Servicemen starting a radio repair business—Federated has a plan to smooth the way! Backed by our huge stocks of radio and electronic components, and our many years of experience in filling the needs of the radio serviceman, we can help YOU, because

**WE KNOW WHAT YOU NEED**

A special department in our organization, staffed with special personnel qualified by long actual experience in radio service work, will help you get started. Test equipment, tubes, replacement parts, tools, manuals, EVERYTHING you will need, to set you up in a profitable radio repair business, all included in our plan! For interesting details:

**WRITE DEPARTMENT 27-M**

**Federated Purchaser**  
INCORPORATED  
distributors of RADIO - ELECTRONIC and SOUND EQUIPMENT  
80 PARK PLACE, N. Y. 7  
Phone: WH 4-2080

# OUR NEW CATALOG IS READY

PLUGS

PILOT LIGHT SOCKETS

JACKS

BARRIER TERMINAL STRIPS

HARDWARE, ETC.

The Herman Smith Catalog is a volume that belongs in the "stock" of every dealer and serviceman. You'll find hundreds of items . . . many of the hard-to-find variety. All first quality . . . all fully guaranteed. Send for your FREE copy today.

**Herman H. Smith, Inc.**  
405 44th Street, Brooklyn 20, N. Y.

tifier are then soldered to pin 5 (4 on Fig. 13, photo). The red lead is then soldered to pin 8 (5 on Fig. 13) and the other side of the 110 volt bulb to B—. A handy place for this connection is the "dead" side of the "on-off" switch. Placing it on the other side of the switch would obviously cause the light to be on all the time. After completing the installation, the B+ voltage and the overall performance of the set should be checked. In situations where no series resistor is used with the rectifier, an optional refinement

is to insert a fuse where the resistor would be ordinarily be. Then if the input filter condenser should short, causing a shorted rectifier, the house fuse would not be blown.

Many other tubes may be replaced by the selenium rectifier. Unfortunately, it is impossible to cover all these installations. However, the ones described are typical. It is suggested that the serviceman keep a record of pertinent information when making a replacement so that it will be available for future reference. Having this information at hand will save valuable time. ✓ ✓ ✓

## Over the Bench

→ From Page 27

house" (No, I don't mean burning them in the furnace!) to whether radio servicing should be termed a profession or a trade.

Naturally, since I am their parent, I am proud of all of these ideas; but that does not signify that they are all good. That is where you come in. I want to hear from you. Let me know what you think of what I write. If you disagree, tell me where I make my mistake. If you think along the same lines, let me know what you have to add; pick up the idea where I leave off and take it from there. Anything that applies to radio servicing is of deep interest to me, and anything you have to say on that subject will be thoroughly studied.

To give you something to be thinking about, here are some of the ideas that I expect to take up in detail in future columns:

I believe that radio servicing has proved during the war that it is a remunerative business in itself, instead of the "rent payer" or "customer contactor" that many insisted on considering it prior to the time it was forced to carry the load during the years when there was nothing tangible to sell. If a garage can operate independent of an automobile sales room, so can a radio repair shop operate upon repair business alone—if it is properly handled.

I think that the radio serviceman is doing a job that calls for much more intelligence, training, and experience than many servicemen themselves realize. There are too many people who think of radio

→ To Page 40

## JOHN RIDER SAYS...


### The First Impression



"Have you ever visited the pretentious offices of a professional man—or, for that matter, any establishment which was clean, orderly, obviously well conducted and bespoke affluence—a business which catered to the higher income earners? There is hardly a human being who does not develop certain favorable mental reactions under such conditions.

"As the client or customer—you feel that you'll pay for what you're getting—maybe a bit more than you would have to pay elsewhere—but it's probably worth it. You're inclined to think: the individual *must* be good to afford such a layout! Even when you feel that you're paying more than you might elsewhere—you take pride in doing business with such a man or such a store . . . the air of the place—the courtesy tendered makes you sell yourself. It accomplishes effects never possible through advertising alone. That first impression is extremely important. *Are you cultivating such an approach in your shop?*"

*Built for Service*

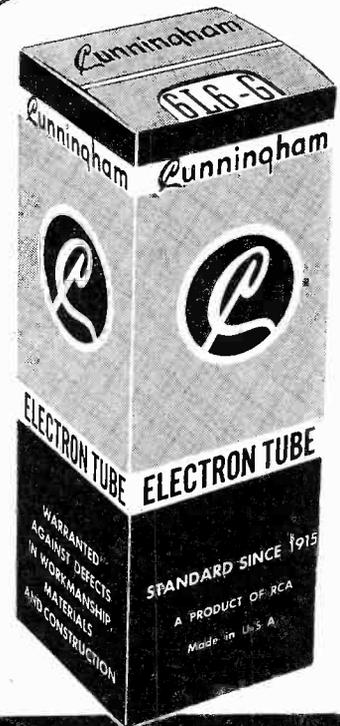

**Cunningham**  
Electron Tubes

A product of  
RADIO CORPORATION OF AMERICA  
Harrison, N. J.

# The Oscillograph...

## How to use it

→ From Page 17

negative envelope of the signal. This is available at a different part of the circuit. With a diode detector, for example, the envelope of the IF signal is available across the diode load resistor, and this same voltage envelope is also available across the volume control in conventional circuits, as shown in Fig. 6. Therefore, the high side of the oscilloscope vertical amplifier input may be connected at A and the low side to ground. In all cases, the low (or ground) side of the oscilloscope should be connected to the chassis ground of the receiver.

In receivers using infinite impedance detectors, the high side of the oscilloscope should be connected to the cathode of the detector, and the low side to ground. In the case of grid leak and biased detectors, the high side of the oscilloscope should be connected to the plate of the detector; the low side to ground. If the plate load for this type of detector is a choke coil, or if the detector is coupled to the first audio stage by means of a transformer, insert a 20,000 ohm resistor in series with the plate and short-circuit the choke or the primary of the transformer in order to eliminate the reactive component of the load. This arrangement is shown in Fig. 7.

Connect the sweep-frequency-modulated signal (from whichever type generator is being used) to the grid of the last IF stage through a .001 ufd condenser. Set the mean frequency to the intermediate frequency of the set (usually 460 kc, exact value obtainable from manufacturer's service notes). We will here consider 460 kc as the IF. With the oscilloscope connected as above, adjust the oscilloscope controls to obtain a pattern of suitable intensity, properly focused, with the sweep and synchronizing controls set to give one synchronized pattern for each complete frequency variation (e. g., 435 to 485 to 435 kc). With the signal generator on, turn off frequency modulation and turn horizontal gain of the oscilloscope to minimum. Adjust the IF

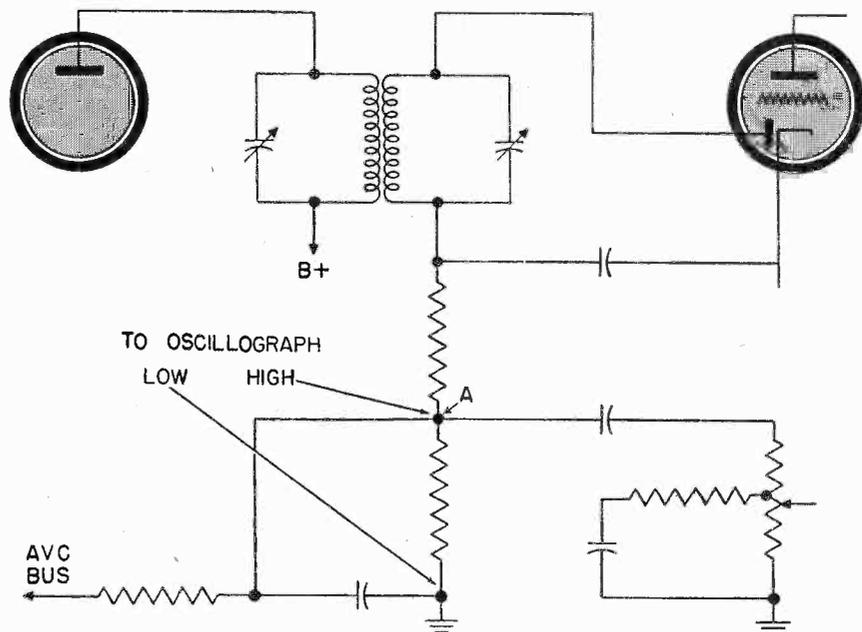


Fig. 6 Points at which the oscillograph leads are connected to a receiver using a diode second detector.

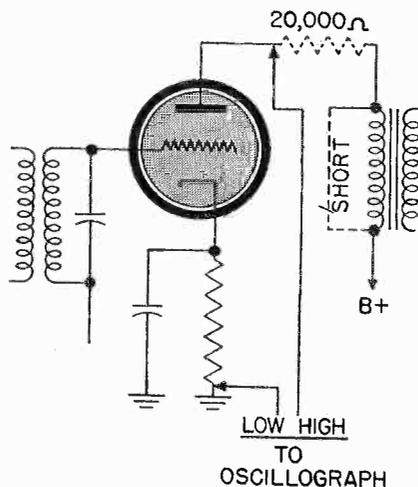


Fig. 7 Points used when connecting the oscillograph to a receiver using biased detector. A 20,000 ohm resistor is inserted in the plate circuit and the primary of the transformer is shorted out.

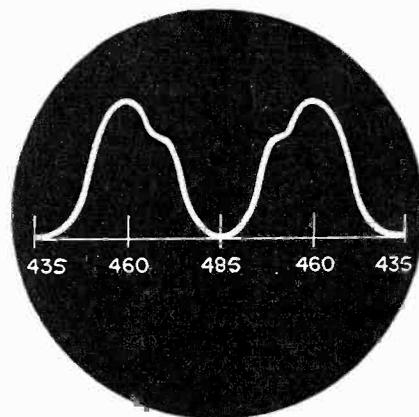


Fig. 8 The appearance of an improperly adjusted IF amplifier with the oscillograph synchronized at a rate of one sweep per rotation of the motor-driven condenser. If a reactance tube modulator is being used, the synchronization is at power line frequency.

trimmers to obtain a vertical line of maximum amplitude. Keep the signal generator output as low as possible to prevent AVC action from flattening the response. If necessary, turn up the vertical gain of the oscilloscope. Set the receiver tuning dial of the set to some point where no interfering signal is passed on to the IF amplifier, and short the antenna input terminals. Turn on the frequency modulation to the signal generator. The pattern on the screen should now be similar to Fig. 8. This is purely an example since the IF re-

sponse can be almost any curve at this point.

Fig. 8 shows a typically unbalanced response curve. It will be noted that the two curves are near mirror images of each other. In order to obtain a clearer idea of the distortion present, both curves can be superimposed on each other by doubling the oscilloscope's horizontal sweep rate. When properly synchronized, the oscilloscope will now show a double trace representing the two curves: 435 kc—485 kc and 485 kc—435 kc. The pattern should now resemble Fig. 9, or

rather the relationship between the two curve patterns observed should be the same as that shown in this example. Readjust the IF trimmers to make the two curves of maximum amplitude and as symmetrical as possible (i.e., overlap as closely as possible). When properly adjusted, the two curves appear as one line. Now, reduce the output of the signal generator and shift the input connection to the grid of the first detector or mixer tube. The pattern should change its appearance, becoming narrower and more peaked. Adjust the trimmers of the first IF transformer for maximum amplitude, retaining the symmetry of the two traces (readjust the other trimmers slightly, if necessary). If the IF amplifier has variable selectivity, make these adjustments at the sharp or maximum selectivity position; then check the curves at the broad or minimum

→ To Following Page

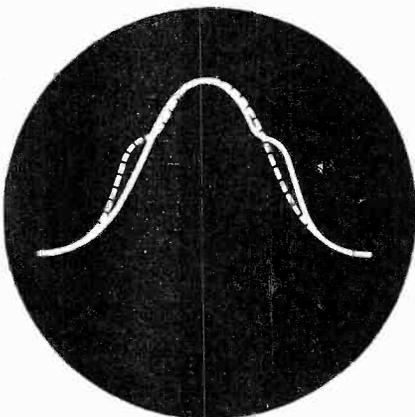


Fig. 9 The same intermediate frequency response as that shown in Fig. 8 with the oscillograph sweep synchronized at twice the former rate. The solid line indicates the response for the half cycle at increasing frequency, and the dotted line represents the response at the decreasing frequency half cycle.

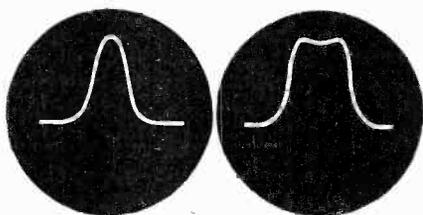


Fig. 10 The response traces for two different degrees of selectivity: On the left for sharp, and on the right for broad.



● In making phonograph repairs or replacements, it is always wise to duplicate parts originally engineered for and used by the manufacturer of such equipment. Substituting "strange" parts is gambling with results. This is particularly true of Phonograph Pickup Cartridges, the characteristics of which may be suitable to one instrument and unsatisfactory for another. To make these replacements in the many types of machines in use, The Astatic Corporation manufactures and ships thousands of

Crystal Cartridges in different but necessary types, each day. Keep Astatic Crystal Pickup Cartridges in your service kit and insure speedy, satisfactory replacements with full measure of operating efficiency.



Visit your Radio Parts Jobber or Write for New Catalog.

IN CANADA: CANADIAN ASTATIC LTD., TORONTO, ONTARIO  
Astatic Crystal Devices Manufactured under Brush Development Co. patents.

# The Oscillograph...

## How to use it

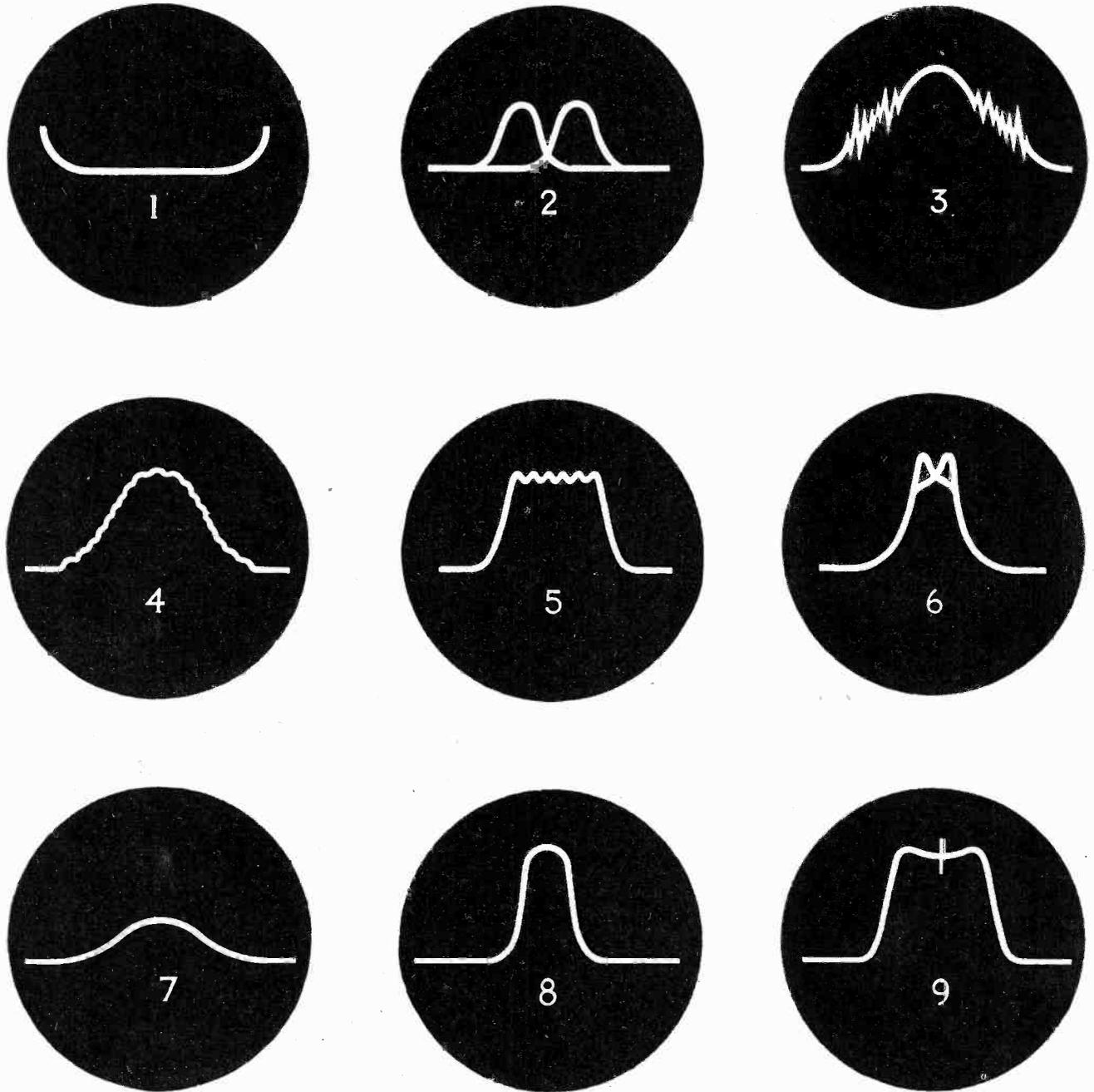


Fig. 11 Typical patterns observed on the oscillograph screen. (1) Signal approximately 20 kc off resonance of IF amplifier. (2) Signal approximately 5 kc off resonance. To correct (1) and (2), be certain signal generator frequency is right, then adjust trimmers to make curves coincide, as in (8). (3) shows presence of spurious signal from external source. (4) "singing" in IF amplifier. While (5) has good selectivity, as shown by steep sides of curve, ragged top indicates overload of oscillograph or IF amplifier. Reduce output of signal generator. (6) shows a symmetrical alignment. These two curves can be made to coincide by suitable adjustment of trimmers. (7) shows broad curve, such as is generally obtained from first step of the alignment, with only one tuned IF transformer. Increase the vertical gain of oscillograph to obtain higher curve, for greater ease in observing results of adjustments. (8) shows good curve for IF amplifier. Top of curve is fairly broad, and sides are steep. (9) shows double peak effect for higher fidelity. Curve is symmetrical, both peaks of equal amplitude, and equally spaced from frequency of resonance. Sides are fairly steep, a condition indicating good selectivity. Curve (9) characteristic of over-coupled double-tuned transformer-coupled amplifiers.

→ From Preceding Page

position. Fig. 10 shows the relative appearance of the traces for these two conditions.

Fig. 11 shows several different types of patterns that may be observed on the screen of the oscilloscope in the course of aligning an

IF amplifier. In all cases, the sweep range was  $\pm 25$  kc. Patterns 1 to 6 show incorrect conditions. Patterns 7 to 9 are satisfactory. ✓ ✓ ✓

**ALMO COVERS THE GLOBE**

**RIDER MANUALS NOW  
IN STOCK**

No. 10, 12, 14. \$15.00 ea.  
No. 15 \$17.50

**AUTO "A" ELIMINATORS**

14 amps. Will handle all size auto sets. . . . . Your cost \$32.50

**NEW JONES PORTABLE  
ELECTRIC DRILLS**

3/8" Size. . . . . Your cost \$21.50  
1/2" Size. . . . . Your cost \$24.50

**First Time Since 1941!  
WIRELESS**

**INTERCOMMUNICATING UNITS**  
No wires required. Just plug in.  
Sold in matched pairs \$42.00 pr.

**MEISSNER 6 TUBE 2 BAND  
SUPERHETS KIT**

550-1600 KC—6-18 MC. MODEL  
10-1199.

Kit includes all parts for construction, including detailed step by step instructions, with tubes and speaker. Your cost . . \$24.70

MAIL ORDERS FILLED PROMPTLY



509 ARCH ST., PHILA. 6, PA.  
LOmbard 3-0513

**Audio Oscillator**

→ From Page 13

of  $V_1$ . Therefore, for the plate of  $V_2$  to feed back a voltage with *no phase shift* to the grid of  $V_1$ ,  $R_1C_1$  must equal  $R_2C_2$ . Thus, for a given setting of  $R_1$ ,  $C_1$ ,  $R_2$ , and  $C_2$ , only one frequency will have zero phase shift through the Wien Bridge, and will hence be the only frequency to arrive at the grid of  $V_1$  exactly in phase with the original signal. This resonant frequency is


$$f = \frac{1}{2\pi \sqrt{R_1C_1R_2C_2}}$$

$$f = \frac{1}{2\pi R_1C_1} \quad (\text{since } R_1C_1 = R_2C_2)$$

The reason for the lamp in the cathode of  $V_1$  is this: If the amplitude of oscillation should increase, the plate current through the lamp will of course increase, making the filament of the lamp hotter and its resistance greater. This greater resistance increases the negative feedback voltage applied to the cathode of  $V_1$  directly from the plate of  $V_2$  (see Fig. 5). This lowers the gain of tube  $V_1$  and decreases the size of the oscillation to its normal condition. Similarly, should the oscillations fall off slight-

→ To Following Page

**SILVER "VOMAX"**

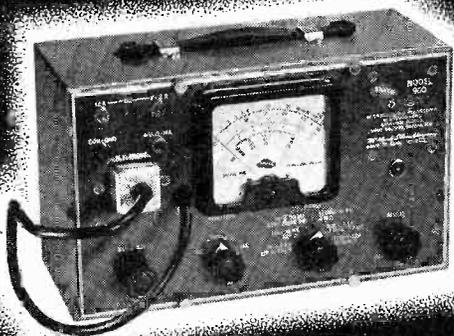

**IMITATION . . .  
SINCEREST OF  
FLATTERY**

The true worth of "VOMAX" is proven not alone by overwhelming preference by service technicians, by research laboratories. It gets operating through the copying of its new inventions by at least four manufacturers! No imitation provides the range, utility or universality exclusive to "VOMAX". Recognized by those "in the know", sales of "VOMAX" far exceed those of any would-be competitor. So, cast to you of the genuine, original "VOMAX" is from 10% to over 65% lower than its imitations. Only \$59.85 net.

So superior as to be imitated, "VOMAX" stands unequalled. It alone gives you the astronomically high meter input resistance so necessary to servicing AM, FM and TELE receivers — a feature not attained by imitations. Add a total of 51 voltage, current, resistance and db. ranges. That's why "VOMAX" is the overwhelming choice of experts — be it for use or copying. Can you afford less than the best — when the best costs you least?

**"SPARX"**

**"QUICKEST TROUBLE  
FINDER EVER"**

says J. P. FITZGERALD



... of his new "SPARX" visual-aural dynamic signal tracer, writing from Madison, Wis.: " . . . cannot afford to be without this valuable instrument one minute. It is the quickest trouble-finding apparatus I have ever used." To repair any radio you've first got to find the trouble. "SPARX" will locate r.f., i.f., a.f. trouble in 30 seconds per tube! Think what that means in profits to the thousands of your competitors already using "SPARX". It will boost your profits, too . . .

"SPARX" is the same great "buy" at only \$39.90 as "VOMAX", world's most popular, most copied, universal vacuum-tube voltmeter. Of matching size and style, thousands in use prove its vital worth to every service technician interested in guarding his profit. "SPARX" traces signals through a receiver from antenna to speaker, circuit by circuit, locating trouble points, both audibly and visually. Its speaker switches to panel jacks for shop test use — another SILVER plus-value.

Send Post Card for Catalog for new measuring equipment, communication receivers, transmitters, kits, parts. See them at your favorite Jobber.

OVER 36 YEARS OF RADIO ENGINEERING ACHIEVEMENT

*McMurdo Silver Co., Inc.*  
1249 MAIN ST., HARTFORD 3, CONNECTICUT

# every day is RADIO MAINTENANCE DAY in your shop!

*If you are not a subscriber:  
Each month Radio Maintenance  
features articles covering subjects  
vital to the radio serviceman.  
Every issue will be valuable to  
you so why not subscribe to  
and have the magazine brought  
to your door regularly?  
Fill out the coupon below  
and mail it with your  
remittance today.*

## Special Series on these:

- Your Test Equipment — How to get more out of your — Oscillograph — Sig. Generator — VTVM — etc.
- Your Trouble Shooting Procedures — Television AM — FM
- Your Public Address System — planning — installation — operation — maintenance
- Your Alignment Techniques — Television — AM — FM

## Departments on:

- Your Opinions
- Your Shop Layout
- Your Radio Service Bench
- Your Service Kit for outside jobs
- Your Business News
- Your Tools

**THE MAGAZINE**  
**WITH EVERYTHING YOU NEED**  
*under one cover .....*



### RADIO MAINTENANCE MAGAZINE

460 Bloomfield Avenue, Montclair, N. J.

Enclosed is my remittance. Please send me RADIO MAINTENANCE for:

2 years at 4.00

1 year at 2.50

Name .....

Address .....

City-State .....

\*Occupation .....

Title (Service Mgr., etc.) .....

Employed by .....

\*Business or professional classifications are required to complete our records. Each subscriber should write one of the following classifications in space indicated.

**INDEPENDENT SERVICEMAN—DEALER SERVICEMAN—SERVICE  
MANAGER—DEALER—DISTRIBUTOR**

State your classification if not listed.

→ From Preceding Page

ly, the plate current through the lamp will decrease, making the filament of the lamp cooler and its resistance consequently less. This lower resistance will decrease the amount of negative feedback applied to  $V_1$  cathode, increase the gain of the tube, and consequently restore the amplitude of oscillation to its correct higher value. The lamp thus serves as a stabilizing influence on the oscillator output. While the lamp is mentioned as in the negative feedback circuit, the same results can be obtained by placing it in the positive feedback half, with slight circuit modifications.

Beside this stability of output, the Wien Bridge type of audio oscillator is generally preferred to the phase-shift type of audio oscillator because it can more readily be made to cover a wide range of frequencies; and, once set to a given frequency, it is less likely to shift in frequency because of the two actions of the Wien Bridge: Attenuation and shifting of phase of unwanted or extraneous frequencies.

As an example of a complete Wien Bridge type of audio oscillator circuit refer to Fig. 6.


By comparing Fig. 6 with Fig. 5, it can be seen that  $R_4$ ,  $R_5$  and  $R_6$  of the complete oscillator correspond to  $R_1$  of the simplified Wien Bridge oscillator of Fig. 3;  $C_1$ ,  $C_4$ , and trimmer condenser correspond to  $C_1$ ;  $R_7$ ,  $R_8$ , and  $R_9$  correspond to  $R_2$ ;  $C_2$  and  $C_3$  correspond to  $C_2$ .  $R_5$  corresponds to  $R_3$ ;  $R_7$  and  $F_1$  correspond to the lamp branch of the Wien Bridge.  $C_6$  and  $C_{11}$  are merely coupling or blocking condensers and can be neglected in a critical study of the schematic diagram.  $C_5$  is a screen-to-cathode bypass condenser.

Two pentodes, a 6SJ7 and a 6F6, are used for  $V_1$  and  $V_2$ , the oscillator tubes. The output from the 6F6 is coupled through a gain control potentiometer (called *output control*) to the third tube, a 6F6, which further amplifies the oscillating wave. The output from this amplifier tube is connected across the primary of an output transformer with a multi-tapped secondary. Provisions are made, under control of a *load impedance* switch, to switch the output terminal to any one of four taps on the secondary or to the high side of a series resistor for high impedance output. The four secondary taps provide impedances of 10, 250, 500, and 5000 ohms. The proper output load tap should be used to match the impedance of the load circuit (input of the circuit to be connected to the oscillator) to the output of the audio oscillator, as closely as possible. The low side of all five

# U.S.R.S. MONTHLY SPECIAL
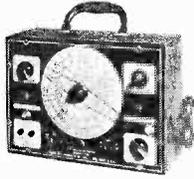
## RADIO CITY PRODUCTS SIGNAL GENERATOR

New post war model 705. Frequency range 95KC-100MC. Fundamentals in 5 continuous bands variable from 95KC-25MC. Modulated or unmodulated output 30% at 400 cycles. Individually shielded R.F. circuits, coil assembly and attenuator. Housed in durable metal cabinet.



46-110 Signal Generator—Net..... \$49.50

## PORTABLE TUBE AND SET TESTER

Model 802N incorporates all the newest circuits. Tests all receiving tubes, neon and pilot bulbs. Jeweled light on-off indicator. Housed in sturdy oak case. Comes complete with test prods and instructions.



46-101 Portable Tube and Set Tester—Net \$59.50

## R. C. P. COUNTER TUBE TESTER

MODEL 322. Tests all tubes, standard, miniature and sub-miniature. Tests leakage and shorts between elements. Line fuse protects against burn-outs.

46-100—Tube Tester—Net..... \$41.50

Write for Free Illustrated Flyer

# U.S.R.S.

## U. S. RADIO SUPPLY

5116 HARPER AVENUE  
CHICAGO 15, ILLINOIS  
DEPT. MA2

## CRITICAL RADIO TUBES

### MOST TYPES IN STOCK

50L6	\$.75	1N5	\$.90	25Z6	\$.68
35Z5	\$.58	1R5	1.10	117Z3	1.10
117L7	1.80	6K7	.68	12SA7	.90
12SG7	.75	32L7	1.33	12SK7	.75

BRAND NEW, IN SEALED CARTONS, 100% GUARANTEED REPAIRMEN and DEALERS: Write for complete list and discounts.

## RADIO EXPERTS

178 EAST 33rd STREET, Dept. M  
PATERSON 4, N. J.

JUST OUT

# VOLUME XV

ONE FEATURE ALONE  
WILL REPAY THE ENTIRE  
COST TO YOU...TIME, AND  
TIME, AND TIME AGAIN!

For years and years on end—for as long as 1946 receivers are in use—Volume XV will continue to pay you annual cash benefits by providing authorized time-saving servicing data complete and bound in a systematic form. The owners of Volume I, purchased 16 years ago, are still deriving benefits from it. A library of Rider Manuals is a lifetime, profit-paying investment.

Volume XV incorporates the latest Rider "first"—"clarified schematics," a plus service in which we have spent tens of thousands of dollars in order to save you hundreds upon hundreds of hours each year. Also, with each copy of Volume XV is the separate book "How It Works," a practical guide to the theories of operation of the new technical features of latest receivers.

Many post-war sets are equipped with record players and changers; these are covered in Volume XV. All the popular brands of "Ham" communication receivers are included. You are brought up to date on all Scott receivers.

Yes, on the 1984 pages of Volume XV, covering the sets of 121 American Manufacturers and the 150 pages of "How It Works" you will find the data and services that will make it pay its profitable way for years to come. Order from your jobber today.

### OTHER RIDER MANUALS

Volumes XIV to VII, each volume.....	\$15.00
Volume VI.....	11.00
Abridged Manuals I to V (1 vol.)....	17.50
Record Changers and Recorders.....	9.00

"clarified  
schematics"

"Clarified schematics" do a job which you have had to do on every multi-band receiver and combination set coming into your shop. They break down composite diagrams of hundreds of complicated multi-band receivers into individual schematics of each circuit as it exists with each turn of the wave band or equipment switch. With a "clarified-schematic" you save the time heretofore spent tracing out an original schematic to find which components are in operation under different positions of the wave band switch. Alone, this one feature will repay the entire purchase price of Volume XV year after year.



PRICE  
\$18.00

YEAR AFTER YEAR AFTER YEAR  
RIDER MANUALS  
Keep pouring profits for Servicemen

## JOHN F. RIDER PUBLISHER, INC.

404 FOURTH AVENUE, NEW YORK 16, N. Y.

Export Division: Rocke-International Corp., New York 16, N. Y. 13 E 40th Street, Cable ARLAB

outputs is a terminal connected to chassis ground. A fourth tube, type 80, is the rectifier for the B+ power supply.

Switch S1, range selector, selects combinations among R<sub>1</sub>, R<sub>2</sub>, R<sub>3</sub>, R<sub>4</sub>, R<sub>5</sub> and R<sub>6</sub> in the Wien Bridge circuit, to provide frequency ranges of 20 to 200 cycles, 200 to 2000 cycles, and 2000 to 20,000 cycles. C<sub>3</sub> and C<sub>4</sub> are ganged fine tuning condensers, each paralleled with trimmers. R<sub>16</sub>, output control, is a .1 megohm potentiometer.

### The Jackson Audio Oscillator

As an example of a well designed

Wien Bridge type audio oscillator recently to come out of the factories of a major electrical instrument company is the Model 655 Audio Oscillator manufactured by the Jackson Electrical Instrument Company of Dayton, Ohio.

In the Jackson audio oscillator, stabilization is accomplished in the positive feedback circuit. This instrument has a frequency range of 20-200,000 cycles with an accuracy of 3 per cent (or 1 cycle) at any frequency over the band. The scale is a large one—calibrated logarithmically. It is illuminated for the operator's convenience.

The range switch selects any of the four ranges: 20-200, 200-2,000, 2,000-20,000, 20,000-200,000 cycles. The load selector switch provides selection of the following loads: 10 ohms, 250 ohms, 500 ohms, 5000 ohms, resistive; approximately 1 watt power output is available throughout the audio range. The output waveform is guaranteed to have less than 5 per cent distortion at all frequencies. The frequency characteristic is as follows: Constant amplitude of oscillation within ± db over the range 30-50,000 cycles. The hum level is down more than 60 db from the maximum output voltage value.

**Sold Out**

**APRIL 1946**

PA SYSTEMS  
A MIDGET AUDIO FREQUENCY OSCILLATOR  
IF I WERE A SERVICEMAN  
AN EQUALIZED AMPLIFIER FOR MAGNETIC PICKUPS

**MAY 1946**

PA SYSTEMS  
TEST PANEL FOR THE MODERN BENCH  
RINGING THE BELL

**JUNE-JULY 1946**

FUNDAMENTALS OF TELEVISION  
VOLUME CONTROL TAPERS  
THE ELECTRONIC VOLT OHMMETER  
VECTOR ANALYSIS

**AUGUST 1946**

AVC CIRCUITS  
FM TROUBLESHOOTING  
TELEVISION RECEIVER FUNDAMENTALS  
RECORD CHANGERS

**SEPTEMBER 1946**

**Sold Out**

**OCTOBER 1946**

**Sold Out**

**NOVEMBER 1946**

PART II TEST & ALIGNING TELEVISION RECEIVERS  
DON'T FORGET THE DIAL LAMP  
THE OSCILLOGRAPH . . . HOW TO USE IT  
CRYSTAL PICK-UPS

**DECEMBER 1946**

TELEVISION RECEIVERS . . . THE RF SECTION  
TUNING INDICATORS  
PART II THE OSCILLOGRAPH . . . HOW TO USE IT  
REPLACING AUTO CABLES

**JANUARY 1947**

SERVICING BY EAR  
TELEVISION RECEIVERS . . . VIDEO CHANNEL  
PART III THE OSCILLOGRAPH . . . HOW TO USE IT  
MINIATURE TUBE CHART

**The Notebook**

→ From Page 33

servicing as "tinkering," when actually good radio servicing requires as much background study and training as many professions.

I think that there should be better mutual understanding of each other's problems on the part of radio servicemen and radio manufacturers. The former must realize that the manufacturer cannot build his set "bread-board" style so that it will be easy to service if he hopes to sell the housewife on buying it for her living room. On the other hand, the manufacturer must keep constantly in mind that the continuing satisfaction of the customer who bought his product is largely in the hands of the radio serviceman. If the serviceman cannot keep the set working through lack of service information or the inability to secure specialized parts, the dissatisfaction of the purchaser will be directed against the manufacturer. What is more, few people buy a new radio without consulting some authority, more often than not the serviceman, as to the comparative value of the various brands. There is a vast amount of potential goodwill, virtually untapped, awaiting the manufacturer who demonstrates his sympathetic interest in the serviceman's problems.

These are a few of the matters that I hope to develop at some length in the future. When I do, I want your comments; and it doesn't matter whether they are brickbats or bouquets. Both will be equally welcome! ✓✓✓

**Picture Credits**

*Radio Maintenance*, Feb. 1947

- P. 6 Fed. Tel. E. Radio Corp.
- P. 7 " " " " "
- P. 9 " " " " "
- P. 10 Jackson
- P. 12 Top: Supreme Instruments Corp.  
Bottom: RCA
- P. 15 RCA
- P. 18 Allen B. DuMont Labs.
- P. 21 " " " " "
- P. 28 Federal Tel. & Radio Corp.
- P. 31 H. Leeper



**OCTOBER 1945**

**Sold Out**

**JANUARY 1946**

THE PROBLEMS OF ORGANIZATION  
TELEVISION RECEIVER INSTALLATION  
RADIO MAINTENANCE IN AVIATION  
USING THE OSCILLOGRAPH FOR DISTORTION MEASUREMENTS

**FEBRUARY 1946**

**Sold Out**

**RADIO MAINTENANCE Magazine**  
460 Bloomfield Ave.  
Montclair, N. J.

Please send me the back numbers checked here. I am enclosing 25c for each copy.

- April 1946
- August 1946
- May 1946
- November 1946
- June-July 1946
- December 1946
- January 1946
- January 1947

Total Amount Enclosed \$ .....

NAME .....

ADDRESS .....

CITY ..... ZONE .....

STATE .....

ALL SET FOR

# Modern Servicing...



**DU MONT Type 274**  
**THE "MUST" INSTRUMENT**  
**designed for the go-getter**  
**serviceman**

At only \$99.50, here's your "Best Buy" today. Note its many fine features. With this popular instrument, you're ready to tackle the widest range of profitable service jobs today, and the still more profitable jobs coming up soon. A Type 274 Oscillograph pays for itself over and over again. Here's how:

### FEATURES AT A GLANCE . . .

- Big, detailed, easily-studied traces on the 5" Type 5B1 cathode-ray tube.
  - Frequency Range: Sine wave response (at full gain) uniform within  $\pm 20\%$  from 20 to 50,000 c.p.s., down less than 50% at 100,000 c.p.s.
  - Linear Time Base: Variable from 8 to 30,000 c.p.s. Synchronization from vertical amplifier or external signal.
  - Deflection Sensitivity: Amplifiers at full gain, 0.65 r.m.s. volt/in.; direct,  $\pm 18$  r.m.s. volts/in.
  - Power Supply: 115 volts, 50-60 cycles. Approx. 50 watts. Fuse protection: 1 amp.
- Weight: 35 lbs. Dimensions: 14" x 8 3/4" x 19 3/4".
- And handsome! Green wrinkle-finish steel cabinet. Plastic carrying handle. Modern design green front panel with white characters. Black knobs.

### TELEVISION RECEIVERS . . .



Forecasts indicate that within the next year thousands of television sets will be produced, bought, installed. Much of the servicing of the complex circuits is easily and quickly performed by the serviceman equipped with a Du Mont Type 274 Oscillograph.

### F-M RECEIVERS . . .

For faithful reproduction of tonal values, F-M receivers must be aligned right "on the button." For this critical job, too, Type 274 provides the best method of servicing.
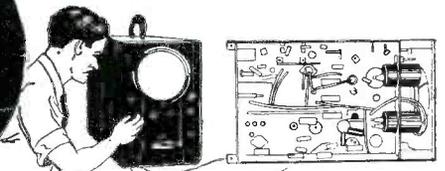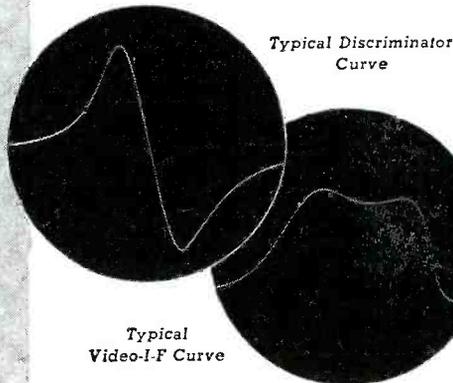
### A-M RECEIVERS . . .

The exceptional versatility of Type 274 can be put to good use with standard A-M receivers. For the accurate adjustment of radio and intermediate frequency circuits, as well as trouble-shooting audio-frequency amplifiers, this instrument is a time-saving tool.




ASK YOUR JOBBER TO SHOW YOU THE NEW DU MONT TYPE 274 OSCILLOGRAPH. OR WRITE US FOR LITERATURE.

© ALLEN B. DU MONT LABORATORIES, INC.

**DU MONT** Precision Electronics & Television

ALLEN B. DUMONT LABORATORIES, INC., PASSAIC, NEW JERSEY • CABLE ADDRESS: ALBEEDU, PASSAIC, N. J., U. S. A.

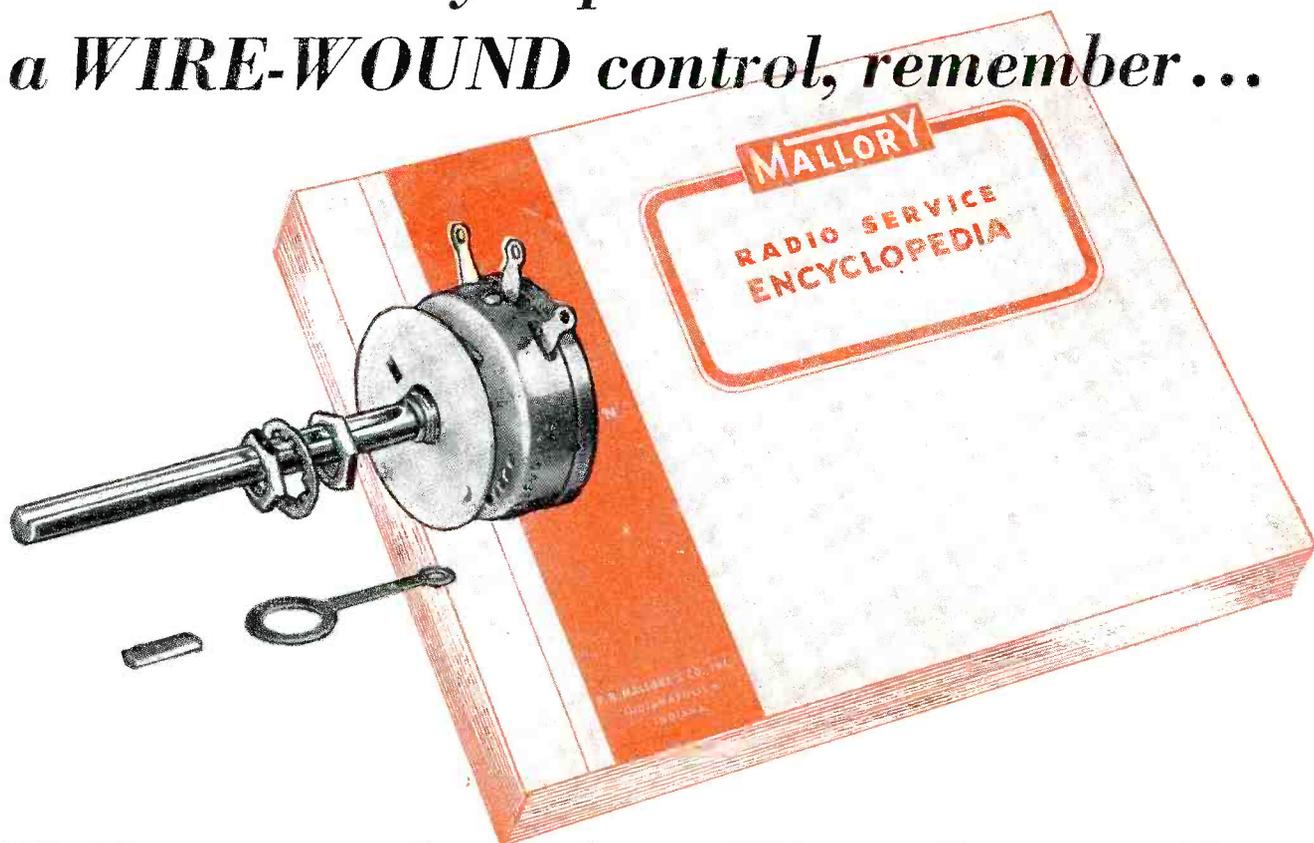*When the Encyclopedia recommends  
a WIRE-WOUND control, remember...*



## Mallory is the Line That Gives You **ALL** Needed Values

A PROPER servicing job on old type radios often calls for a tapered wire-wound control. The Mallory Radio Service Encyclopedia will tell you just what's needed. And you'll find what you need in the Mallory Catalog—and at your Mallory Distributor's.

Fact is, Mallory is the manufacturer who has always made a complete line of wire-wound controls. There are thirty-three types covering every resistance value and taper . . . many with the exclusive Mallory adjustable bias feature . . . all equipped with the universal channel shaft and insert that fits all types of knobs.

Make it a Mallory wire-wound control, and you can't go wrong.

*You Expect More—and Get More—from Mallory*

**Insist on MALLORY—the  
Complete Control Line**

*Mallory is the manufacturer  
that offers:*

- 33 Correctly Tapered Wire-Wound Controls
- 31 Values in Single Tapped Controls
- 10 Values in Double Tapped Controls
- 12 Clutch Type Controls
- 10 Universal Dual Controls
- 92 Popular Special Controls

**P. R. MALLORY & CO. Inc.**  
**MALLORY**

VIBRATORS . . . VIBRAPACKS\* . . . CAPACITORS . . . VOLUME  
CONTROLS . . . SWITCHES . . . RESISTORS . . . FILTERS  
. . . RECTIFIERS . . . POWER SUPPLIES.

\*Reg. U. S. Pat. Off.

**APPROVED PRECISION PRODUCTS**

P. R. MALLORY & CO., Inc., INDIANAPOLIS 6, INDIANA